

THE
AUSTRALASIAN

Registered at the G.P.O.
Sydney, for transmission
by post as a periodical.

VOL. 11 NO. 3

AUGUST 15, 1946

Radio World

1/-



**The latest Reinartz circuit
featuring Ferrõtuning.**



**A Stroboscope for checking
gramophone record speed.**



**Circuit of all-wave two-valve
set for battery operation.**



**Special sections devoted to
"Ham" notes and short-waves.**



LET US BE PRACTICAL


Fashions come and fashions go, even with dogs and radio circuits.

Fantasy and realism do not mix and there is no place for fantasy in quality Radio. Only the practical can stand up to the acid test of continued public acceptance.

The best in radio is still the tried and proven design built from tried and proven components.

Be practical and insist on "Crown" parts: B/C Coils, S/W Coils, I/F Transformers, Tuning Dials, Padders, Trimmers, etc.

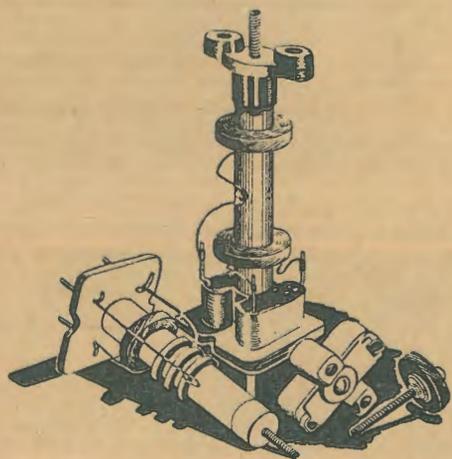"CROWN" parts are built to rigid standards and are precision tested before they leave the factory; that is your guarantee of quality.



Crown



RADIO PRODUCTS PTY. LTD.

51-53 MURRAY ST.

PYRMONT, SYDNEY. TELEPHONE: MW 2628

THE AUSTRALASIAN RADIO WORLD

Devoted entirely to Technical Radio

and incorporating
ALL-WAVE ALL-WORLD DX NEWS

★ EDITOR
★ PUBLISHER
★ PROPRIETOR—

A. G. HULL

336 Waverley Rd., East Malvern,
Vic.

★ SHORT-WAVE EDITOR—

L. J. KEAST

3 Fitzgerald Road, Ermington,
N.S.W.

★ HAM NOTES By—

D. B. KNOCK (VK2NO)

43 Yanko Av., Waverley, N.S.W.

★ ADVERTISING
REPRESENTATIVE FOR VIC.—

W. J. LEWIS

20 Queen St., Melbourne
Phone: MU 5154

★ ADVERTISING
REPRESENTATIVE FOR N.S.W.—
AMALGAMATED PUBLICATIONS
PTY. LTD.

83 Pitt St., Sydney

Phone: B 1077

★ SUBSCRIPTION RATES—

6 issues 5/3
12 issues 10/6
24 issues £1
Post free to any address in
the world.

Address for all correspondence:
AUSTRALASIAN RADIO WORLD
336 Waverley Rd.
East Malvern, SE5
Victoria

VOL. 11

AUGUST, 1946

No. 3

CONTENTS

CONSTRUCTIONAL—

A Handy Multi-Meter Kit	7
"All-Wave" Band Spread Two	13
The "Ferrotune" Reinartz	17
Sky-Cruiser Battery Four	21
The Fidelity Broadcast	25

TECHNICAL—

Outlook for "Ham" Market	5
Make Your Own "Stroboscope"	15
Getting Started at Set-Building	29
Ham Notes—Calling CQ	31

SHORTWAVE REVIEW—

Notes From My Diary	38
New Stations	39

THE SERVICE PAGES—

Answers	42
---------------	----

EDITORIAL

Further to last month's editorial, the progress of the radio trade is not very rapid in regard to peak production of new components. Apart from one or two real battlers, the rest seem to be happy enough to jog along with their old-style components, and with a comparatively limited production rate of even those.

There are so many obstacles to the production of new lines; so many hurdles to be overcome in order to obtain big quantities of raw materials and so little encouragement (from an income tax point of view) that it is not surprising that we find considerable difficulty in getting bright articles to fill our issues.

We had a big stunt lined up for this month's issue, but production difficulties held it up at the last minute. Fortunately, however, another interesting receiver turned up on time and so we are able to have a main feature article well up to standard. With regard to the support, too, we managed to find a way out of the difficulty which seems to have proved a lot better than we first expected. This takes the form of a trip into the past; a review of some of the articles which were published in Volume No. 1 in 1936 and 1937. These circuits were all popular in their time, proved themselves capable of giving splendid results and are just as useful today as when they were first published.

Since our circulation figures are four times greater today than they were when these circuits were published it is certain that they will be new to many of our present readers, and even to our long-time supporters they should not lack interest.

—YOUR EDITOR.

HOMECRAFTS PTY. LTD.

THE RADIO SPECIALISTS

A Division of Electronic Industries

Distribution in Five States



No Extra Charge for the Milk and Sugar

And there's no extra charge for THE EXTRA SERVICE which HOMECRAFTS extend to their clients.

ARE YOU ON OUR MAILING LIST?

if not send us your Name, Address and Service Licence No. Let HOMECRAFTS keep you up-to-date with the latest information on Stocks, Valve Releases—"B" Batteries, etc.

Write to our nearest Branch—If it's in Radio! Try HOMECRAFTS first.

Head Office: 290 LONSDALE STREET, MELBOURNE.

And at—
100 Clarence Street
Sydney

211 Swanston Street
Melbourne

307 Sturt Street
Ballarat

132 Moorabool Street
Geelong

Telegraphic Address: "Homecrafts," Each State.

26 Hunter Street
Newcastle

And at—
Toowoomba, Dalby &
Rockhampton, Qld.

140 Adelaide Street
Brisbane

Hobart, Launceston,
and Burnie, Tas.

OUTLOOK FOR THE "HAM" MARKET

Far from being treated as an afterthought in the field of radio manufacturing as in pre-war days, the Australian transmitting radio amateur is likely to merit much more consideration in the years to come. As the "Electronic War," recently concluded, progressed in technical intensity, the Ham came into his own. In every phase of warfare where communications were involved, hams were

By

DON B. KNOCK (VK2NO)

Experimental Radio Equipment
Dept., Philips Electrical Industries of
Australasia Pty. Ltd.

to be found. In the ranks of the service trained operators with no pre-war ham experience more than 80 per cent of them have since proved to be potential hams. In short, numbers of pre-war VK's is likely to be multiplied many times during the course of the next ten years. Very few Australian manufacturers really catered for transmitting amateur requirements prior to September, 1939 — and nobody could blame that apparent indifference. The demand wasn't large enough — yet I know of concerns, today very large industries, the foundations of which were definitely laid in the home constructor market between 1927 and 1939. There has always been a fair return for the manufacturer willing to supply popular lines for home constructors, but such a demand has only been created by the technical radio Press. Without publications such "Australasian Radio World," the maker of parts off all kinds would have been hard put to it to sell his goods. Intervention of the war undoubtedly saved a lot of people from trade doldrums by reason of war contracts at a time when anybody with a machine tool or two and a few feet of space could turn out items of value to the war effort. Now — that is all a thing

of the past, and one of the brightest stars on the radio trading horizon is undoubtedly Amateur Radio. I say this despite the era of "disposals" gear. The seller of partially complete ex-Service equipment and "bits and pieces" caters very nicely for the inveterate constructor Ham — which comprised nine-tenths of the pre-war breed. But a new generation of Hams is on the way — and the wise manufacturer will recognise that fact. Prior to the war Australian amateurs were often compelled to buy overseas components, for the simple reason that the products were not made locally. It wasn't so much a question of price — the Australian manufacturers just didn't make some items essential to the make-up of Ham stations. It was unwisely assumed that the Ham market wasn't worth consideration. Despite the fact that by the time duty had been taken into account, also exchange rate, there were many Australian Hams, and, for that matter, SWL's, who paid out lots of money for receivers of the type of the RME69, National HRO,

Hallicrafters and others. I knew one SWL who paid no less than A£250 for a much boosted overseas receiver of massive appearance, and incidentally, that receiver had plug-in coils — not band-switching! He could have done just as well from a technical constructional article in this and other magazines for less than £30, but he and others considered that they were getting good value for money by paying for a Name. Then, of course, there were the unregistered receivers of overseas origin that found their way about in one's and two's by diverse means. There was not a single Australian manufacturer producing a receiver designed expressly for Ham needs because there was not the proportionate demand.

Components were certainly fairly well represented — nevertheless — many of these gradually vanished as manufacturers concentrated more and more on the ready-made broadcast receiver-buying public. A vast increase in Australian amateur numbers is predicted for the following reasons:

(Continued on next page)



The station operated by Don B. Knock in 1926. This was A2NO, Cremorne, N.S.W. — a quarter KW affair with two T250's in parallel in a S. E. Hartley Rig. This picture of station and operator was taken at 3 a.m. during a "DX session" on "32 metres." Don says: "Those were the days — and nights — no phone — all CW and practically no inter-station QRM."

TECHNICAL BOOKS

1. Complete Radio Manual— "RADIO FOR THE MILLIONS"

Pop. Science Monthly Publ. Instructions for building 87 receivers, recorders, radio phonographs, etc.; from one tube to 8 tube sets; from vest pocket to floor models. Trouble-shooting, servicing, testing equipment. 100 wiring diagrams. 450 illustrations.



10/6
(post. 6d.)

2. "ELECTRICAL ESSENTIALS OF RADIO"

By M. Slurzberg and W. Osterheld. Basic principles of electricity explained according to electron value—drawings to illustrate. Communications, theory, circuits, magnetism, meters, inductance, capacitance, resonance. Appendices solve all problems without further reference.



28/-
(post. 9d.)

3. For Radio Engineers— "RADIO TECHNIQUE"

By A. G. Mills, A.M., Inst. B.E. The fundamental theory of electricity, transmission and reception, cathode-ray tubes, times bases and aerials, pulse generating and controlling circuits. Over 300 diagrams, 169 pages. Presented with a minimum of mathematics.



21/9
(post. 6d.)

4. HOW TO BUILD AND REPAIR RADIO RECEIVERS

"EVERYBODY'S RADIO MANUAL," a "Pop. Science Monthly" clear, non-technical instruction on building or repairing any kind of set. Hints, shortcuts, a wealth of diagrams that are easy to follow. 256 pages.



7/6
(post. 6d.)

5. Ninth Edition of F. J. Camm's "THE PRACTICAL WIRELESS ENCYCLOPEDIA"


An alphabetically compiled guide for the construction, operation, repair and principles of wireless receivers. Over 220,000 copies sold. Definitions, explanations, formulas, etc., rapidly consulted.



12/6
(post. 6d.)

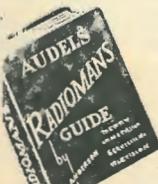6. 'AUDEL'S RADIOMAN'S GUIDE"

By F. P. Anderson. Here is a wealth of essential information simply presented and fully illustrated. Covers theory, construction, servicing, and includes television and electronics. 880 pages.



26/-
(post. 9d.)

HAM MARKET (Continued)

(1.) The majority of the newcomers are ex-servicemen who possessed no pre-war experience of the hobby, but because they were in close association with so many who *did* know the thrills of DX and everything that goes with private communication, are determined to get their "tickets" and break in to this fascinating field.

(2.) The increased popularity of radio in general by reason of press reports of war-bred achievements in the way of FM, television, and Radar.

(3.) The young generation — youngsters who can read for themselves in magazines such as this — and will undoubtedly "catch the bug." It can be taken for granted that the Australian, in common with British and American amateurs will run into a big family — with a healthy appetite for components and complete equipment. Components will be in big demand because the genus Ham is at heart an experimenter — even if only so in a modest way. But, in contrast to pre-war days, there will be a family of people who know more about actually operating equipment than constructing it personally. They will sail through operating examinations, and will acquire enough fundamental theory to take care of that side of it, and thus will obtain their license. With money put on one side for the purpose, these operator-hams will be in the market for ready-made gear such as receivers, transmitters, and test equipment for all purposes. The point to emphasise is that Amateur Radio in this country as in others, will definitely outgrow its former swaddling clothes — the demand will be there — and the wise manufacturer will not ignore the facts. But, he will be faced with a problem — that of producing an admittedly popular line of goods for a prolific, but low, or medium priced market, with materials supply as the aftermath of war a formidable obstacle. Despite such hurdles, they will be overcome, and amateur radio in the new Era will be amply supplied, to the mutual benefit of consumer and supplier.

ANGUS & ROBERTSON LTD.,
89 Castlereagh Street,
Sydney.

ORDER FORM

Please send me the books whose numbers I have encircled.

1 2 3 4 5 6

(A) For which I enclose payment. (B) Charge to my account.

NAME

ADDRESS

(Tech. R.W.1)

A HANDY MULTI - METER KIT

It may not be generally known that kits of parts with which to assemble a multi-meter can be readily obtained. The kit for building up the meter shown here was obtained recently from Vealls.

THIS versatile instrument has a wide range of application. It will measure voltage, current and resistance values accurately, and the design incorporates an efficient output meter. Following is a description of how the various sections are used. There are further and wider applications for this instrument which will manifest themselves as the operator becomes more familiar with the Multimeter.

Unless the operator understands the voltage and current readings of various circuits, it is advisable to always use the highest range available to obtain an approximate reading, and then choose a lower range which will be more suitable for an accurate reading. This will prevent damage to the meter from excessive overload.

D.C. VOLTAGES

Turn the central selector switch to the desired voltage range and make sure that the right-hand switch is turned to that position marked "D.C." The negative, or black, test lead is inserted in the negative jack on the instrument, and the red test lead inserted in the positive jack. The two test prods are then touched to the necessary parts of the apparatus under test, and the meter will read the difference in potential between the two points touched, which is actually the voltage. It is necessary to remember that voltage is the difference in potential between any two points.

If it is desired to measure the voltage on the elements of a valve, the metal chassis of a radio receiver or amplifier is usually regarded as forming the negative side of the circuit, and the elements concerned as forming the positive side of the circuit. For instance, if it is desired to measure the plate voltage of a valve, the appropriate range would

be selected, the test lead placed on the plate contact of the valve, and the negative test lead placed on the chassis. The meter would then read the valve's plate voltage. This method does not apply to the measurement of negative grid bias.

To measure the negative grid bias, the negative test prod is placed on the negative filament or cathode contact. The negative bias will then be indicated on the meter. This method will be inaccurate if a high value of resistance is included in the grid circuit, such as a resistance capacity coupled stage. In this case, the negative test prod should be placed on the end of the grid leak resistor, which does not connect to the grid.

When making voltage measurements, it is not necessary to remove or disconnect any wires.

A.C. VOLTAGES

To measure alternating voltage,

the only rearrangement of the controls on the instrument is to turn the right-hand switch to that position marked "A.C." The appropriate voltage range is then selected in the ordinary way on the range selector switch, and the test prods, when plugged into the instrument, can then be connected to the two points between which it is desired to measure the voltage difference. Since alternating voltage has no fixed negative or positive potential, the negative or positive test lead from the instrument can be placed on either of the two points which are under test. However, to form a safety habit, it is always wise to place the negative lead on the low potential side of the circuit or that side of the A.C. voltage which is connected to earth. If this is inconvenient, the operator need not worry any further.

When measuring alternating voltages on the 10 volt range, the lowest meter scale marked "10 V. A.C. only" should be used. When using the 50, 250 and 1,000 V. ranges, measurements should be made on the upper set of voltage graduations.

D.C. CURRENTS

In making current measurements, it is necessary to break the circuit and insert the test leads so that the meter is placed in series with the circuit. For instance, to measure the plate current of a tube, the wire on the plate contact would be removed and connected to the positive side of the meter. The negative meter lead would be connected to the plate contact and the selector switch would be turned to the desired range, and then the set switched on. The plate current of the valve would be registered on the meter. This procedure also applies to any other circuit in which it is desired to measure current in milliamperes. The circuit is simply

(Continued on next page)




The multi-meter which is assembled from the kit.

THE NAME
TO KNOW
IN RADIO!



Radiokes

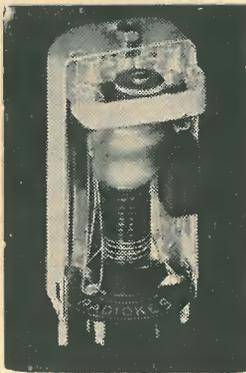RADIOKES D.W. UNITS. Highly selective with exceptional wide range. To match 'H' type gang condenser. Incorporates 4-in-1 padder. Solidly mounted with coils. Ask for type DWO-1



When buying radio parts and components, follow the lead of amateurs and experts alike — specify Radiokes — your guarantee of test-set performance, precision construction and technical excellence.

RADIOKES

PTY. LTD.

P.O. BOX 90

BROADWAY — SYDNEY

MULTI-METER KIT

(Continued)

broken and the meter inserted in the break to complete the circuit again.

Where the current value is unknown, it is always wise to commence on the highest range, and then turn the selector switch down to that range which gives the most convenient deflection of the needle on the meter.

It is essential when making D.C. current measurements, to make certain that the right-hand switch is turned to the position labelled "D.C." The instrument is only intended to measure alternating milliamps on the 1 m.a. range, in which case the upper voltage graduations are used. This range can be used in conjunction with a suitable current transformer for the measurement of higher values of alternating currents in excess of 1 m.a. without the use of a current transformer.

RESISTANCE

This instrument will measure values of resistance in four convenient ranges. 0-1,000 ohms, 0-10,000 ohms and 0-1 megohm.

To measure values of resistance below 1,000 ohms, the selector switch is turned to the position marked "R X 1." The test leads are inserted in the instrument, and then the test prods are touched together so that the meter needle will swing right over to the position marked "O" on the upper meter scale. If it does not exactly reach the "O" mark, the ohms compensator, at the left-hand side of the instrument, is turned until the needle indicates zero resistance. The meter is then ready for use.

To measure resistance, one side, or both, of the resistance or other part, should be disconnected from the rest of the circuit, and the test prods placed on its terminals. The value of resistance will be shown on the ohms range.

For values up to 10,000 ohms, the switch is turned to the position marked "R X 10," and the scale figures must be multiplied by 10 to give the correct resistance. For

example, if you are measuring a resistance of 4,000 ohms, and the switches are turned to the correct position, then the meter needle will indicate 400. Multiplying this by 10 gives 4,000, which is the correct reading, assuming that the resistor is in good order.

When measuring in the range of 10,000 ohms, it is necessary that the prods are touched together again and the needle adjusted for zero resistance by use of the ohms compensator.

For values up to 10,000 ohms, the range switch is turned to the position, marked "R X 100," and the procedure is carried out as explained previously. For measurements up to 1 megohm, turn switch to "R X 1,000," and proceed as before.

In measuring resistance, it is necessary that the right-hand switch be turned to the position marked "D.C." Always, before measuring resistance, make certain that the test prods are touched together and the ohms compensator adjusted, so that the meter reads zero before operation. The purpose of this ohms compensator is to compensate for any variation in battery voltage, which will enable you to obtain a maximum life from the built-in batteries.

CAUTION.—Before attempting to measure the resistance of any part of radio or electrical apparatus, be sure to switch off the power, or to disconnect one wire from each battery in the case of battery operated equipment.

OUTPUT METER

In addition to measuring ordinary A.C. voltages over a wide range, the Multimeter can also be used as an output meter. The right-hand knob on the instrument is turned to the position marked "OP," and the range selector is turned to an appropriate voltage range. The test leads are inserted in the instrument, and one lead is attached to the chassis, while the other lead is touched to the plate off the output or power valve in the receiver or amplifier under test.

Small push-on clips are provided with the instrument. These easily and conveniently fit on the test


leads, so that it will not be necessary for the operator to hold these on to the point under check in the chassis. They can be clipped on to any convenient wire or terminal, leaving the operator's hands free for alignment of the set.

If the range selector is turned to 10 volts when using this as an output meter, it will give a very sensitive reading. However, it will be found necessary for the volume control of the receiver to be kept low, so as not to damage the meter. This 10-volt range is recommended for aligning sets. If the output meter is required for a purpose other than alignment, the 50-volt or 250-volt will be found quite suitable.

Used in this manner, the instrument will facilitate the alignment of a receiver, especially when a modulated oscillator or signal generator is used as the source of signal.

BATTERY REPLACEMENT

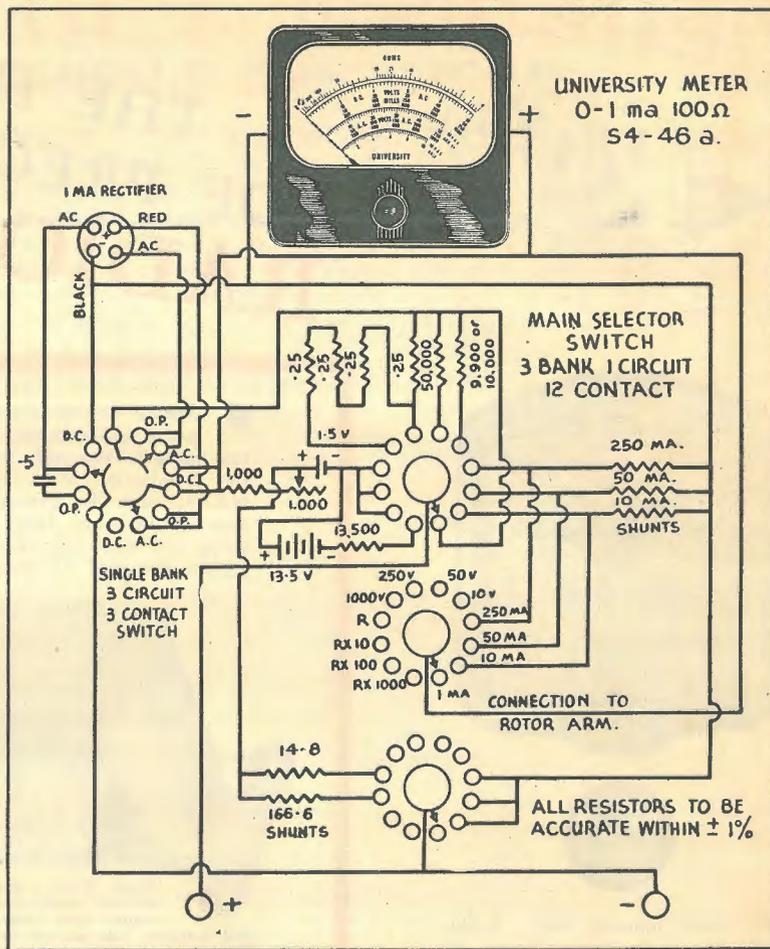The resistance measurement section of this instrument utilises a standard 1.5 volt 950 dry battery cell in conjunction with three type 703 dry batteries. These usually last up to nine months without replacement. It will be known when the battery is due for replacement



Circuit of the meter, showing the switching arrangements.

by the fact that the ohms compensator on the panel will not enable the pointer of the meter to be brought right to the zero mark.


To replace batteries, remove the four screws on the edge of the instrument, and the batteries will be seen in special clips inside the case. Unsolder the leads from each end of the 703 batteries and replace with new batteries in exactly the same position. Make sure that the lugs are soldered on to the new batteries in the same manner as they were to the old batteries. The type 950 battery is held in a clip at the side of the meter. To replace, first remove the four screws in the upper battery panel. Loosen the meter terminal nuts several turns, and clip in new battery in the same position as the original. Be sure to

tighten the meter nuts before replacing the upper battery panel.


GENERAL

The primary purpose of this instrument is to measure D.C. voltage, currents and resistances, as well as A.C. voltages and output voltages. The instrument is accurate, and is easily portable.


It will cover nearly all of the routine checking required in a radio receiver, and in general radio equipment. It must be remembered that voltage measurements in a receiver will not only indicate that there is voltage available, but if they are measured through any of the components in the receiver, they will indicate whether that component is open circuit or otherwise by the indication of voltage on the meter.

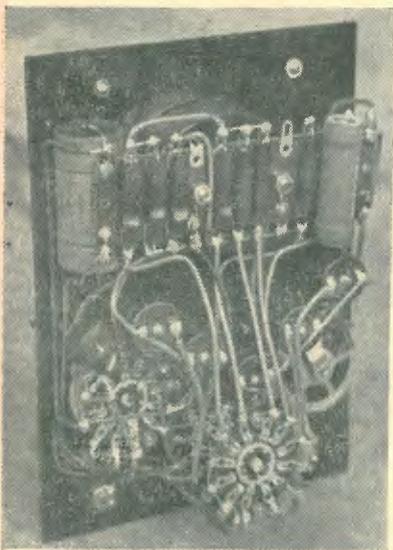

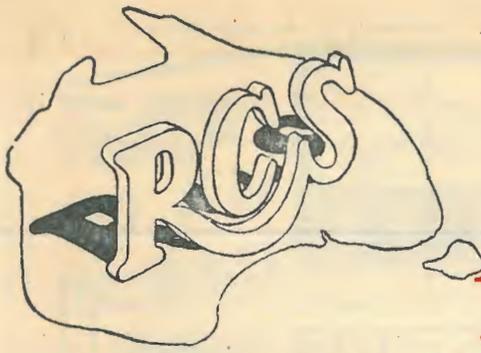Rear of the panel. The builder makes his own case of wood or metal to suit his requirements.



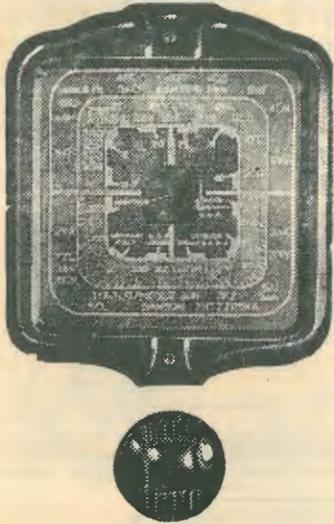THE HALLMARK OF PRECISION-BUILT RADIO PARTS!



The ever popular DA7 Radio Dial. Absent for many years, it is now back on your retailer's shelf. Ask for it — and other equally famous R.C.S. radio parts and components.

R.C.S. RESISTORS

R.C.S. Resistors wound with nichrome wire and are supplied complete with pigtails.
Ohms to 1500 Ohms
1" x 3/4" diam.
1500 Ohms to 10000 Ohms
2" x 3/4" diam.
C.T. Resistors
10 Ohms to 200 Ohms

R. C. S. RADIO PTY. LTD.

174 CANTERBURY ROAD
CANTERBURY

Recognised as the hall-mark of precision-built radio parts and components, R.C.S. has been the outstanding name in the radio industry for many years. And, with the installation of a modern new factory at Canterbury, N.S.W., plus the experience gained in wartime manufacture of intricate radio and electrical equipment, R.C.S. bring you new type coils and kit parts built to an even higher standard of accuracy and performance.



These R.C.S. quality components incorporate heavy copper wire wound on Trolitul bobbins. The use of Trolitul eliminates electrolysis, ensuring much longer effective life.


R. C. S. FILTER CHOKES Audio Transformer

TB4. A Class. Single
TB5 A Class. PP.
TB6 B Class. PP.
TC65. 50M/A 30. H.
TC60. 100M/A 30. H.
TA4 Audio Chokes
TC58 L.T. Vibrator Chokes
TC70 H.T. Vibrator Chokes.



R.C.S. I.F. Transformers are of registered design, are permeability tuned and feature the exclusive R.C.S. Trolitul base, with special condenser pockets. Coils are wound with 7/41 Litz wire.

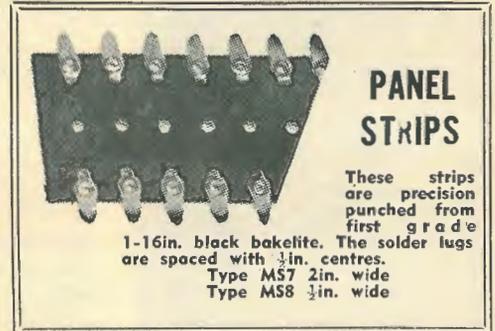IF 162 Permeability tuned. 460 K.C.
IF 163
IE 74 Permeability tuned 175 K.C.
IE 75



PANEL STRIPS

These strips are precision punched from first grade

1-16in. black bakelite. The solder lugs are spaced with 3in. centres.
Type MS7 2in. wide
Type MS8 3in. wide



R.C.S. Trimmers — Two-plate coil trimmers mounted on Trolitul base.
CG 15.

BEAM WITH A REPUTATION

SPLENDID EXAMPLE OF "HAM" ANTENNA

Consistent workers and observers of VK doings on the "Ten" metre band from the time the "all clear" was given early this year have noticed that one of the stations to which DX from places far and wide has a habit of responding is that of VK2AKR. The phone signal from this station, resulting from only a 45 watt rig, is probably the best known of all VK's on "Ten." Reason for the consistent performance is pictured here in the shape of the well-designed and engineered two-element rotary array; sufficient answer in every way to any arguments that multi-element arrays are essential if you want results. Owner-operator of VK2AKR is Jack Lindsay, and his location is to the West of Metropolitan Sydney, in the suburb of Lidcombe. Ex-Army hams may re-

means of the small centre stub in that description, but by means of telescopic tubing. Tenth wave spacing is used between radiator and director. Most important item is, naturally, the method of feed. From the centre of the radiator, a length of 70 co-axial line — 5 feet 5 inches, is followed by a quarter-wave Q bar section, thence into a 600 ohm line to the shack. So successful has this beam been on

"Ten" that with the opening of "Twenty," VK2AKR is now planning a similar structure above the present one, and at right angles, cut for the lower band. As he is also more than casually interested in "Six" for local QSO's, a ground-plane antenna will be added. The moral is one that we've always stressed: "A good antenna is more than half the battle."

—D.B.K.

CANADIAN FM

Canada's first broadcast FM transmitter started operating a few months ago from Mount Royal, Montreal. The transmitter, employing a frequency of 48.8 Mc/s with a power of 25W, uses the call VE9CM.

call it on the rail service to Liverpool, Ingleburn, etc. — but no such beam would then have been visible from the train windows. Since then, however, its presence has been enough to make a few G hams, RN visitors to VK, hop off the train and call to see what goes with the beam in the shack!

DESIGN DATA

Located at the top of a sturdy, well-braced tower, this rotatable array, controlled from the operating position, is in practice a simple arrangement fundamentally. Jack makes no claim for originality; and refers enquirers for practical details to the 1938 Edition of the old "Radio" Handbook, page 119. There is a difference, however, in that the director is not adjusted by



28 M/cs. Beam Array of VK2AKR, Lidcombe, N.S.W.

How much is a good Valve and Circuit Tester Worth?

The worth of a test instrument is dependent upon the work you get out of it. That is why University Instruments are bargains—on the job! The "University" Supertester is designed and built to speed up servicing, to last longer, and retain its original accuracy. Unless you use a Supertester you don't realise what an amazing instrument it is, how versatile, how efficient, how economic. This compact instrument combines all the functions of a multimeter, output meter, tube tester, paper and mica condenser tester, a really efficient electrolytic condenser impedance and leakage tester—a'1 in the one case. Write for illustrated folder of the complete "University" Range.

Price: AC/Vibr. model, plus 12½% Tax. **£28'10/-**

AC model only, plus 12½% Tax. **£27**



- ★ Tests ALL Radio Circuits
- ★ Tests ALL Valves
- ★ Tests Electrolytics for both IMPEDANCE and LEAKAGE.
- ★ Extended ranges for A.C. Volts, D.C. Volts, D.C. Milliamps and Ohms

RADIO EQUIPMENT PTY. LTD.

375 KENT STREET,
SYDNEY, N.S.W.

Telephones: M6391-2.

Telegrams: "Raquip,"
Sydney.



DISTRIBUTED BY


N.S.W.: All leading Distributors.
Queensland: Homecrafts; J. B. Chandler Pty. Ltd.; A. E. Harrold.
Victoria: Vealls Electrical & Radio Pty. Ltd.; Hartleys Ltd.;
Replacement Parts Pty. Ltd.; Victorian Agent, J. H. Magrath Pty. Ltd.

South Australia: Gerard & Goodman Ltd.; Radio Wholesalers Ltd.

Western Australia: Atkins (W.A.) Ltd..

Tasmania: W. & G. Genders Pty. Ltd.

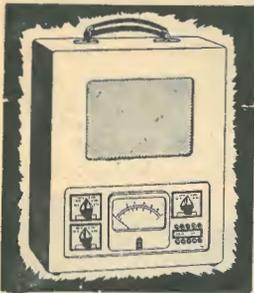New Zealand: Allum Electrical Company Ltd.



"University" Universal Speaker and Output Meters make set testing simple. No power connections required; just plug into any type speaker socket.



A new "University" five-band oscillation for the alignment of all types of radio receivers.

"ALL-WAVE BAND-SPREAD TWO"

A two-valve battery receiver using a 19 twin triode as combined detector and audio amplifier, resistance capacity coupled to a 1D4 output pentode. Has bandspread tuning, and covers both the shortwave and broadcast bands.

FOR set builders who want to get the utmost in enjoyment from their hobby at the lowest cost, the "All-Wave Band-spread Two" is an ideal little receiver. With a handful of parts, two valves, some batteries, and a pair of 'phones — representing a total outlay of a few pounds — a set can be put together that will bring in shortwave stations in all parts of the globe, and give speaker reception from broadcast stations besides.

Originally described in midget form in the May, 1936 "Radio World," the "All-Wave Two" has proved widely popular with readers, many of whom have built it and found that it can do all that is claimed for it.

THE CIRCUIT

Briefly, the "All-Wave Band-spread Two" uses a type 19 twin triode class "B" valve to perform two jobs. One triode section acts

as a leaky-grid detector, with reaction, and is resistance capacity coupled to the second section, acting as first audio amplifier. The latter is in turn resistance coupled to a 1D4 output pentode.

THE COILS

To tune continuously from about 17 to 90 metres and from 220 to 540 you will need five plug-in coils.

Number 24 enamelled wire is used for all short-wave secondaries, and 28 d.s.c. for all shortwave reaction windings, with 32 or 34 gauge enamelled wire for the broadcast coils.

Each shortwave reaction winding is put on below the secondary, with $\frac{1}{8}$ -in. between the two windings. The accompanying sketch shows the method of winding, and the pin connections, which are numbered correspondingly on the circuit and under-chassis diagrams.

The reaction windings for the broadcast coils are put on over, and

not below, the bottom end of the secondary in each case. The two windings should be separated by a layer of Empire cloth or oiled silk.



ABOUT THE CONSTRUCTION

The coil, valve, and battery sockets, four terminals, aerial series condenser, and on/off switch are mounted first. Remember that the "A", two "P" terminals, and aerial condenser must be insulated from the chassis.

Then place the front panel against the chassis, and mount the tuning, band-setting, and reaction condensers, and the rheostat. Before the tuning condenser is mounted, however, a lead should be soldered to the fixed plates terminal. This passes down through the chassis and is soldered to the corresponding terminal on the band-setting condenser. Also, if the set tends to be at all noisy when the dial is rotated, another lead should be soldered to the moving plates terminal and to the earth line underneath the chassis.

(Continued on next page)

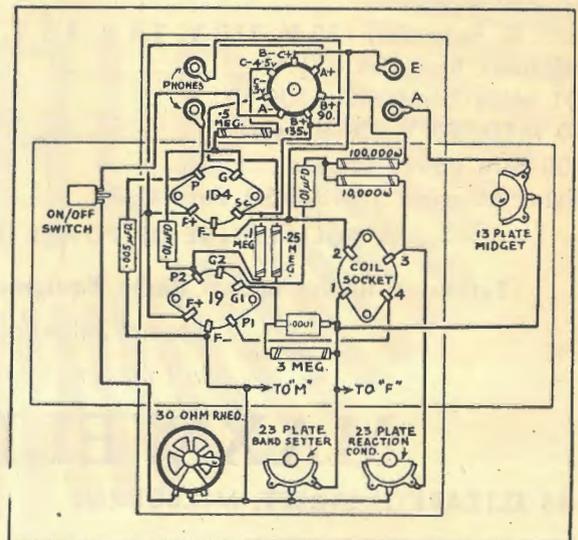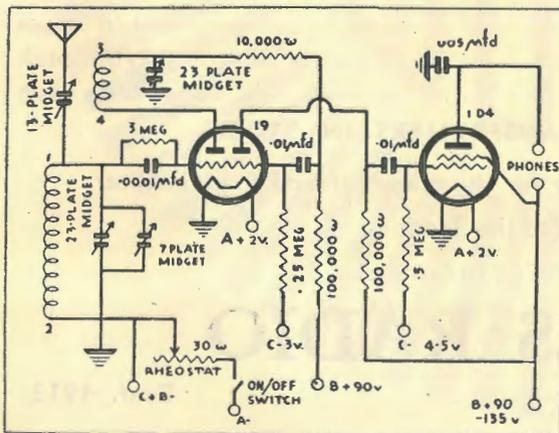Schematic circuit and wiring diagram for the "All Wave Band Spread Two" for battery operation.



ALL-WAVE 2

(Continued)

Either 18 or 20 gauge tinned copper wire, covered with spaggetti, can be used for wiring the set, or ordinary "push-back." Solder all joints, and test them by giving each a tug. The various fixed condensers and resistors are mounted directly by their pigtails.


The wiring will not be given word for word, as it is plainly shown in the diagrams. One detail that should be noticed is that all earth points are bonded together and taken to a 16 gauge tinned copper wire earth line, running direct to the earth terminal. This is to ensure that all earth connections will be of low resistance.

WIRING THE BATTERY PLUG

Next wire the battery cable to the 7-pin plug, and identify each pin, jotting down the colour of the lead running to it, and its designation.

SOME OPERATING HINTS

After everything has been given

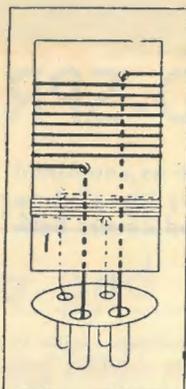

This sketch illustrates how the windings are put on the three plug-in coils that are needed to cover from 19 to 90 metres. Details of the number of turns for each coil are given elsewhere.

"BANDSPREAD TWO" COIL WINDING DETAILS

BAND	Grid	Reaction
17-30 metres	7	7
28-51 metres	15	10
48-90 metres	22	13
220-360 metres	136	32
360-540 metres	182	36

NOTE.—All reaction windings should be put on in the same direction as the grid windings, as shown in the coil sketch. Windings spaced $\frac{1}{8}$ -in.

a final check, plug in the valves, 80-metre coil, and the headphones, connect up the aerial and earth leads, and finally the battery plug. Switch on, and adjust the rheostat until two volts are applied to the filaments.

Next, set the aerial pre-set condenser about half-way out and slowly advance the reaction control. A hissing sound will be heard, followed by a soft "plop", indicating that the set is oscillating. The control should then be slackened off a trifle, and the tuning dial rotated to pick up stations.

The set should never be allowed to oscillate, because in this condition it will create interference with the reception of near-by listeners. Besides, it is never in its most sensitive condition when actually oscillating; for best results it should be just on the verge of oscillation.

For a small set like this, a good aerial and earth system is essential for best results.

MAXWELLS RADIO

48 ELIZABETH STREET, MELBOURNE

Cent. 4913

A FURTHER SERIES OF BARGAINS FROM MAXWELL'S RADIO

12 Volt Relays	8/11
H.D. B. Battreies, 180 V, 130 V, 7.5 V, 4.5 V, Tappings	10/- each
Minimax Batteries 62½ V	16/1
.01 Mica Condensers 600 V.	1/6 each
50 MFD. 40 V. Condensers	1/6 each
100 Mill Power Chokes	12/6 each
Nylox Sleeving 3 M.M. 50 Yard Coils	12/6 each

A FULL RANGE OF POWER TRANSFORMERS IN STOCK

Extensive Range of All Radio Equipment for the Amateur and Experimenter

Special Allowances to the Trade

Mail Orders Promptly Forwarded

MAXWELLS RADIO

48 ELIZABETH STREET, MELBOURNE

Cent. 4913

Make Your Own

"STROBOSCOPE"

A Stroboscope is a device for checking the correct speed of gramophone records. To make one you can cut out the diagram below and paste it on to a piece of cardboard or stiff paper, cutting a suitable

hole in the centre for the pin.

Placed on top of the revolving record and watched under the light from a lamp lighted by 50 cycle alternating current the lines will appear stationary only when the re-

cord is revolving at the correct speed of 78 r.p.m.

The speed should be checked when the pick-up is actually in working position on the record for the best results.




CONSTRUCT

THE NEW FERROTUNE REINARTZ
RECEIVER

Order your KFT2 Foundation Kit Now!

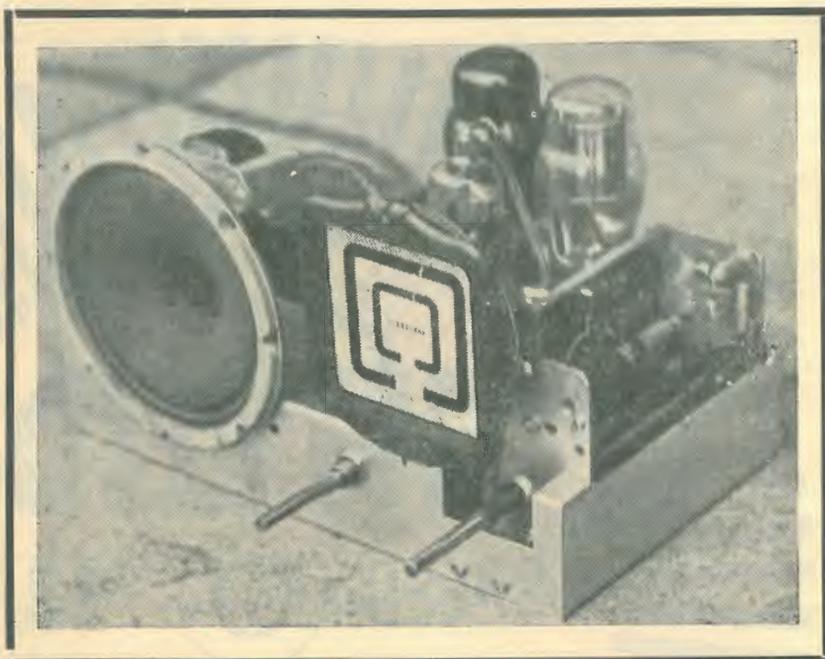Here's your chance to build the brand new KFT2 KINGSLEY FERROTUNE REINARTZ RECEIVER . . . the complete foundation-kit contains the new FERROTUNE unit. This, and the specially designed FERROTUNE-REINARTZ circuit assures the maximum gain and selectivity. The KFT2 foundation-kit is now coming off the production-line and will be available shortly.



Owing to the keen demand for all types of KINGSLEY FERROTUNE units and the limited production which is due to the shortage of essential materials, there may be some delay in delivery — but KINGSLEY'S on the job doing all it can to speed through your favourite radio supplies.

OBTAINABLE FROM AUTHORISED KINGSLEY DISTRIBUTORS



KINGSLEY RADIO

KINGSLEY RADIO PTY. LTD.

380 St. Kilda Road, Melbourne, Victoria . Phones: MX 1159, MX 3653

This Month's Feature :-

THE "FERROTUNE" REINARTZ


JOHN L. REINARTZ is a prominent radio "ham" and technician in America. I met him at Hartford when I was there in 1936. The name of Reinartz was applied to a receiver with regeneration in the early days of broadcasting, and somehow or other it seems to have stuck as a

By
A. G. HULL

general name for any set with a regenerative detector, and so I have no hesitation in again applying the title of Reinartz to this latest of baby receivers, a regenerative set featuring Ferrotuning.

Superhets may come and superhets may go, but these little Reinartz sort of sets always seem to find general favour with a certain class of set builder.

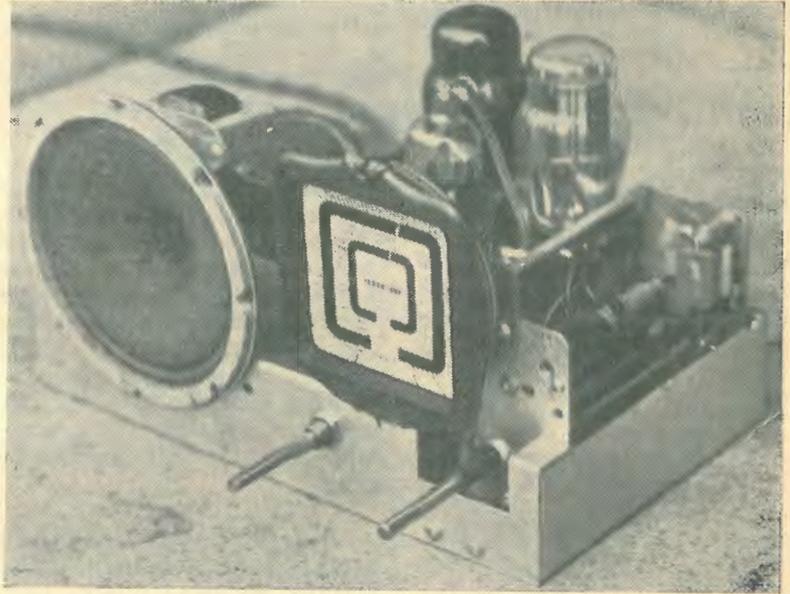They are exceptionally easy to build and as soon as they are built they can be expected to give immediate satisfaction without any



Front view of the chassis.

alignment worries or other messing about. Operation of the regeneration control calls for a certain amount of intelligence, but of all


the Reinartz circuits this latest one is the simplest in this regard, as the use of permeability tuning makes the regeneration control so constant that it works more like a volume control than a reaction control. In any normal locality where the signal strength of the various stations is anything like level it is possible to set the regeneration control and simply tune stations in one after the other almost like a superhet.

PERMEABILITY TUNING

Those of our readers who have studied recent issues will know all that there is to know about this latest innovation, but in case anyone hasn't grasped the idea we may as well run over some of the main points.

In order to tune in signals from a station on a given wave-length you need to have a circuit tuned to the frequency of that station. In order to have a tuning circuit you need inductance and capacity, and in order to be able to vary the resonant frequency you must vary

(Continued on next page)

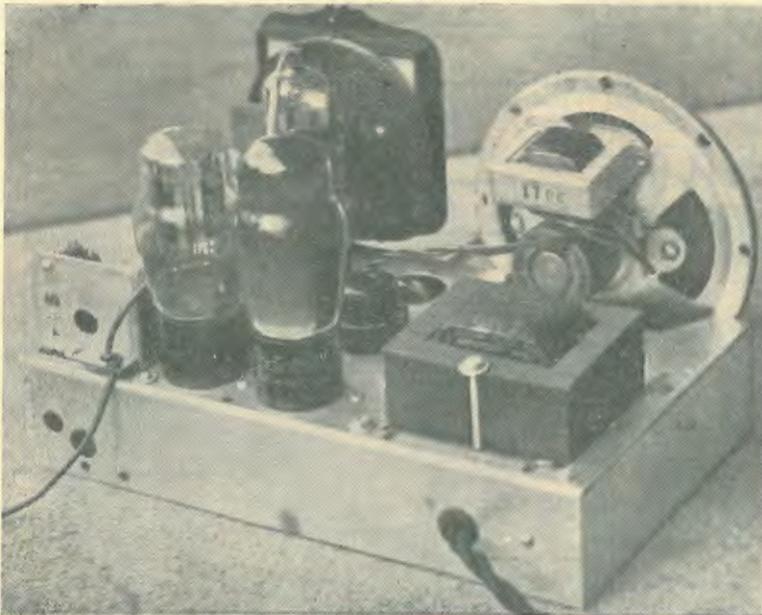


Rear view of the chassis.

dial calibrations, while the other is a series capacity in the aerial lead-in, thereby adjusting the aerial loading to compensate for different lengths of aerial which may be used with the set. To a certain extent it

The Kingsley "Ferrotune" kit for this receiver is known as type KFT2 and comprises the metal chassis, tuning unit complete with calibrated dial and also the r.f. choke.

The use of the complete foundation kit, as listed above, ensures that the lay-out will be correct, and is strongly recommended. The KFT2 foundation kit is in production, but as it is likely that orders will overwhelm the production rate there may be some delay with deliveries.

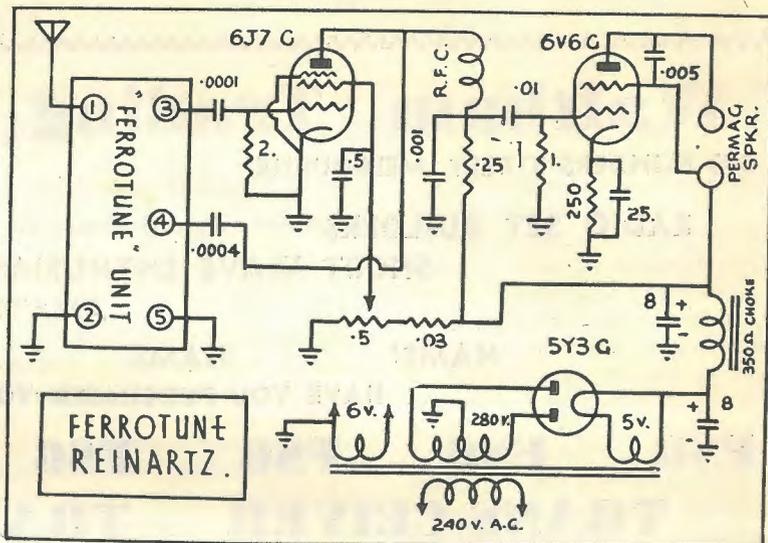gives a control over the effective selectivity and sensitivity of the set. It is extremely easy to adjust and can be set by ear to the position which appears to give the greatest gain at the same time as adequate selectivity for the particular location in which the set is being used.



The circuit diagram.


It will be found that as it is screwed in (clockwise) this trimmer control will give greater volume, other things being equal, but with less selectivity, so that the limit is reached when stations start to overlap. The setting may also have some effect on the reaction control. In certain difficult locations it may be found necessary to pay attention to the length of the aerial used, but in most cases the trimmer will provide sufficient control over the aerial loading.

To those who have never operated sets with regeneration it is necessary to point out that the set

gives its best performance at the setting of the reaction control just back a shade from where the set bursts into a squeal. Operated at this point a regenerative set has far greater gain and far sharper selectivity than without reaction. Advanced too far, the reaction control causes a squeal which not only makes reception impossible, but also re-radiates to cause interference with sets in the neighbourhood over a large radius, so the set must never be left in an oscillating condition.

WITH OTHER CIRCUITS

It should be clearly understood that the circuit we give is simply one suggestion. There are dozens of other circuit arrangements which could be used, such as the popular old "Direct Coupled Two" of 1931 vintage, or with a circuit using an audio transformer for coupling. The unit can also be used for one-valve headphone sets, or one-valve sets using a twin-triode like the 6SN7GT. In fact it can even be used for tuning a lowly crystal set. In this latter case the exceptional efficiency of the tuning unit can be expected to result in improved performance with a set of this type.

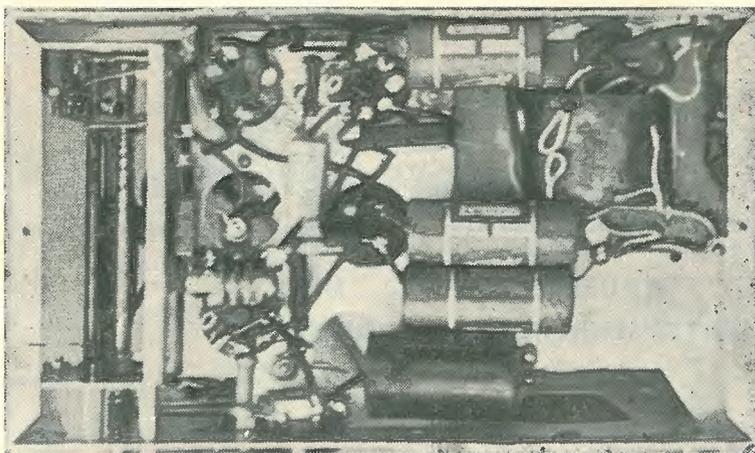

A photograph of the wiring.

Waltham Trading Company

393 FLINDERS STREET, MELBOURNE

'Phone: MU 4719

RADIO SET BUILDERS

SHORT WAVE ENTHUSIASTS

AMATEUR BROADCASTERS

HAMS!

HAMS!

HAMS!

HAVE YOU PURCHASED YOUR

FS6

FS6

FS6

FS6

FS6

FS6

TRANS-CEIVER

TRANS-CEIVER

Is your boy a radio ham? Radio is the coming profession. FATHERS, buy your lad his Christmas gift now. They will be sold long before Christmas. The most instructional and educational gift he could possibly receive. We are supplying the above, positively new and in Original Packing as supplied to the Forces by A.W.A.

£12/10/-

£12/10/-

£12/10/-

£12/10/-

COMPLETE WITH 8 VALVES, POWER PACK AND VIBRATOR

THEY ARE CHOCK FULL OF USEFUL RADIO PARTS. THE VALVES ARE BRAND NEW AS FOLLOWS:

2-1K7s, 2-1C7s, 1-1K5, 1-807 and 2-1L5s. These 8 valves IF sold separately would cost	£8	13	7
The Set is supplied with Palac 0-1 Thermo-Ampmeter priced at	4	4	0
The Power Pack is a separate unit and entirely self-contained, works off a 6-V battery and gives 290 Volts at 50 mil. or 175 Volts at 40 mil. The Pack would cost at least to build	15	0	0
The Vibrator is an A.W.A. gas-filled job, priced at	2	13	0
Army type Key, valued at	12	6	
The Trans-ceiver is built with the finest components and cost the Government over £100.				
Chock a-block full of condensers, valve sockets, carbon and wire wound resistors, tuning condensers, coils, dials, volume controls and I.F.'s, Morse Key, etc., etc.	25	0	0

TOTAL £56 3 1

REMEMBER!

REMEMBER!

REMEMBER!

The total value of these parts as listed in all retail shops is approximately £56/3/1 for the parts only. The completed Receiver cost the Government £100.

OUR PRICE COMPLETE FOR THE WHOLE LOT IS:

£12/10/-

£12/10/-

£12/10/-

£12/10/-

REMEMBER!

REMEMBER!

REMEMBER!

- | | |
|--|------------------------------------|
| The Price includes: (1) The Trans-ceiver | (4) The Power Pack |
| (2) The Valves. | (5) The A.W.A. Gas-Filled Vibrator |
| (3) The 0-1 Thermo Ampmeter | (6) Best Quality Morse Key |

The Receiver is an excellent short wave Receiver in itself and works from a 6-Volt Battery. It is ideal for country use. The transmitter uses 2 valves. 8 valves in all.

HURRY!

HURRY!

HURRY!

SPECIAL ATTENTION TO MAIL ORDERS

We have only a few left. Country Customers, note—The Power Pack can be used on any Set. It is self contained. It can be used on Amplifiers. Please add 10/- to cover cost of two wooden crates in which Receiver and Transmitter are packed. Please send money order or postal notes. We will carefully rail or ship anywhere in Australia.

DON'T FORGET! THERE ARE NOT MANY LEFT.

WALTHAM TRADING COMPANY

393 FLINDERS STREET, MELBOURNE

'Phone: MU 4719

RED




LINE

WIDE RANGE AUDIO EQUIPMENT

Low Level Output

Transformer Primary 20,000 ohms, Secondary 600 ohm Line + or - $\frac{1}{2}$ DB 25CPS to 12KC + 15DB.

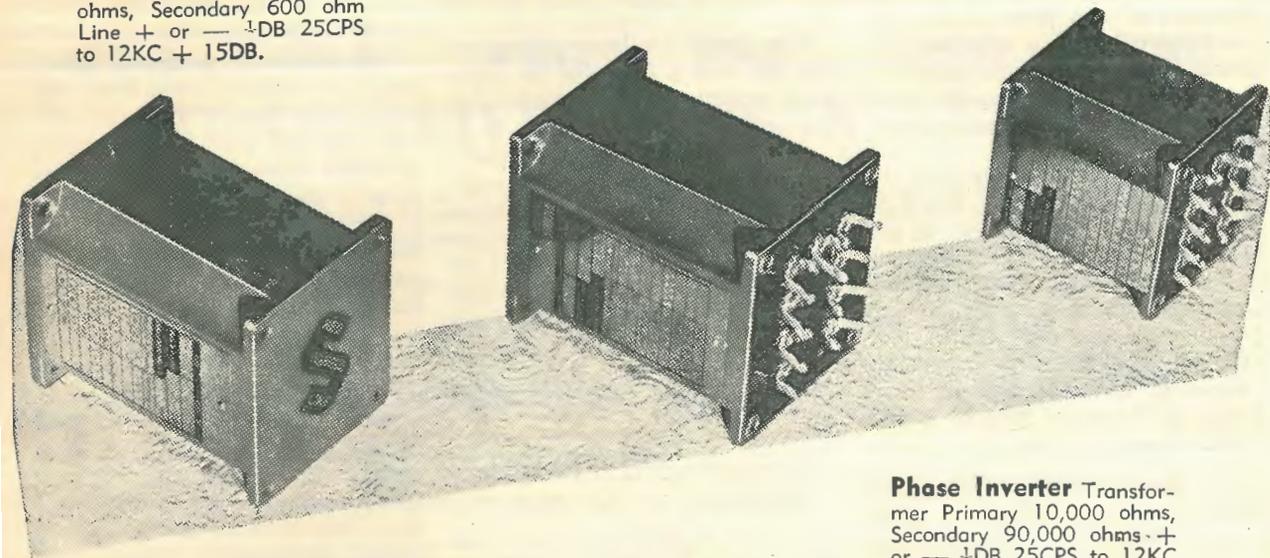Intervolve Driver Trans-
former Primary 20,000 ohms, Secondary 20,000 ohms Max. Unbalanced DC 6 MA + or - $\frac{1}{2}$ DB 25CPS to 10KC + 21DB.



Phase Inverter Transformer Primary 10,000 ohms, Secondary 90,000 ohms + or - $\frac{1}{2}$ DB 25CPS to 12KC + 10DB. Shunt Fed.



LOOK FOR THE RED LINE MONOGRAM

SWALES & SWANN

Technical Service, Wholesale
and Manufacturers:

**A. T. SWALES, Central 4773,
2 Coates Lane, Melbourne.**

Trade Sales:

**Allen SWANN,
MU 6895 (3 lines)
157 Elizabeth St., Melbourne.**



SKY-CRUISER (Continued)

frame, a direct connection is safest, particularly if coils with high-gain primaries are used.

COMPLETING THE WIRING

The filaments can now be wired up, and the remainder of the wiring put in systematically, starting from the "A" terminal and working through to the loud speaker socket. When wiring in the .1 mfd. by-pass condensers, connect them as closely as possible to the coil or valve socket lugs they are by-

the grid leak and condenser. A short lead with a grid clip on the end is soldered to the other.

A $\frac{1}{2}$ -watt leak and midget fixed condenser were used in the original set, but a 1-watt resistor and standard size condenser can be used equally well.

When the wiring is completed, it should be carefully checked over. Next, the battery cable leads can be soldered to the pins of the six-pin plug, and the speaker plug wired as well.

THE LINING UP PROCESS

The batteries can now be con-

nected, the valves and speaker plugged in, and the aerial and earth leads attached. Switch on, and with the volume control turned full on, slowly advance the reaction control until a hissing noise is heard, denoting that the set is on the verge of oscillation. Next, rotate the tuning control, and a station should soon be picked up.

To align the "Sky-Cruiser," set all three trimmers about half-way out, and tune in a station near the centre of the band — one that requires a fair amount of reaction

ENGLISH MINIATURE SUPERHET


A four-valve superhet in a moulded case $8\frac{3}{8}$ -in. x $3\frac{3}{8}$ -in. x $3\frac{3}{8}$ -in. has been designed by Vidor Ltd., Kent, and will be on the market shortly; the price will be in the region of £12. It operates from $1\frac{1}{2}$ -volt L.T. and layer-built 120-volt H.T. and grid-bias batteries. The case is provided with a leather carrying strap and the action of opening the lid switch on the set.

U.S. AMATEURS IN GERMANY

American amateurs in the Army of Occupation in Germany, like their British counterparts, are to be allowed to operate transmitters with 25 watts in the aerial. They will be allocated D4 calls and will be permitted to operate in the 21-21.5, 29-30 and 58.5-60 Mc/s bands.

passing. Also, in each case be sure to take the end marked "outside foil" to earth. The connections for the coils are supplied by the manufacturers.

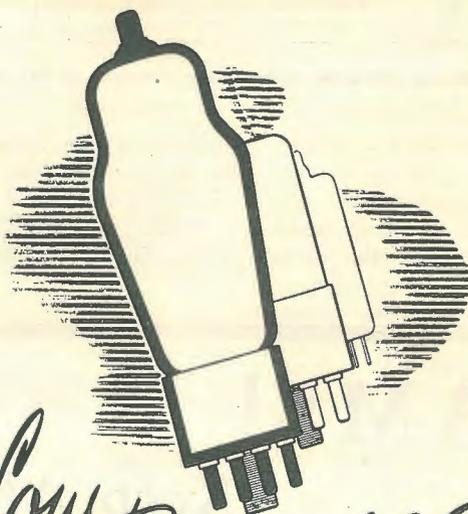A small strip of bakelite about 1 inch long, and with a solder lug mounted on one end, is bolted to the front of the condenser gang, as shown in the photographs. A lead from the fixed plates terminal from the top of the front section of the gang is run to the lug, to which is also connected one side of



Now Released!

Keep in touch with your Local Dealer for further releases of type ranges.



BRIMAR

VALVES

British Made

A PRODUCT OF

Standard Telephones and Cables Limited

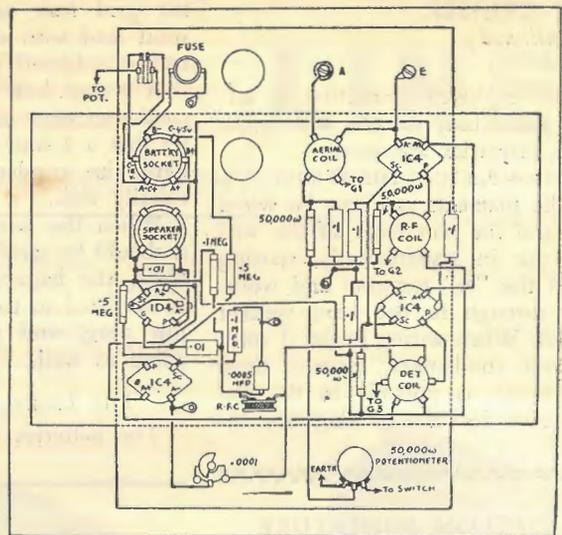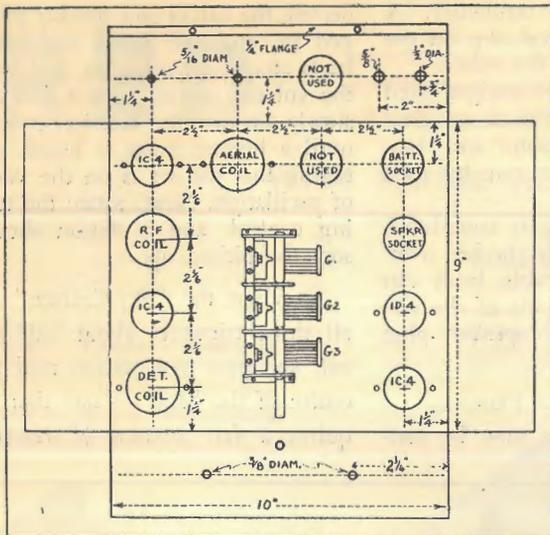

Base lay-out plan and picture diagram of the wiring for the "Sky-Cruiser" battery set.

SKY-CRUISER
(Continued)

to bring it up to quiet room strength. Now adjust the three

trimmers in turn, commencing with the detector, for loudest volume.

EXCELLENT DISTANCE RESULTS

Builders will find that, if a good aerial and earth system is used, the

"Sky-Cruiser" can bring in plenty of fine DX. With a good quality permanent magnet or magnetic type speaker, both tone and volume are also good.

HAMS!

Keep Abreast of the latest overseas developments.

Subscribe now to any of the following magazines.

Q.S.T.	20/-	WIRELESS WORLD	25/-
C.Q.	22/-	WIRELESS ENGINEER	42/-
RADIO	25/-	ELECTRONIC ENGINEERING	33/-
RADIO CRAFT	22/-	ELECTRONICS	56/-
RADIO NEWS	32/-	F. M. TELEVISION	32/-
SERVICE	24/-	COMMUNICATIONS	24/-

Orders are now being registered for the 1946 editions of A.R.R.L. and Radio Handbooks

SEND YOUR ORDER NOW TO—

TECHNICAL BOOK & MAGAZINE CO.

297-299 SWANSTON STREET, MELBOURNE

(Opposite Old Melbourne Hospital)

'Phone: Central 2041

Headquarters for Amateur Equipment

TYPE SI 4


Retail Price 5/-



TYPE SI 3
Retail Price 4/9



TYPE FT 4
Retail Price 6/9

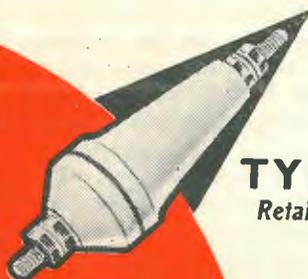

AEGIS CERAMICS

Vital little pieces of equipment which proved worth their weight in gold to the Services, these Aegis Ceramics are available right now to the Ham! The range is complete . . . and every one is typical Aegis quality . . .

TYPE SI 2
Retail Price 2/6



TYPE FT 2
Retail Price 4/7



TYPE SI 2A
Retail Price 2/9



TYPE FT 1
Retail Price 3/9



TYPE GT 2
Retail Price 8/3



TYPE BH 2
Retail Price 5/10




Attractive Discount to Licensed Amateurs

J. H. MAGRATH & CO.

DISTRIBUTORS OF AEGIS COMPONENTS

208 LT. LONSDALE ST., MELBOURNE

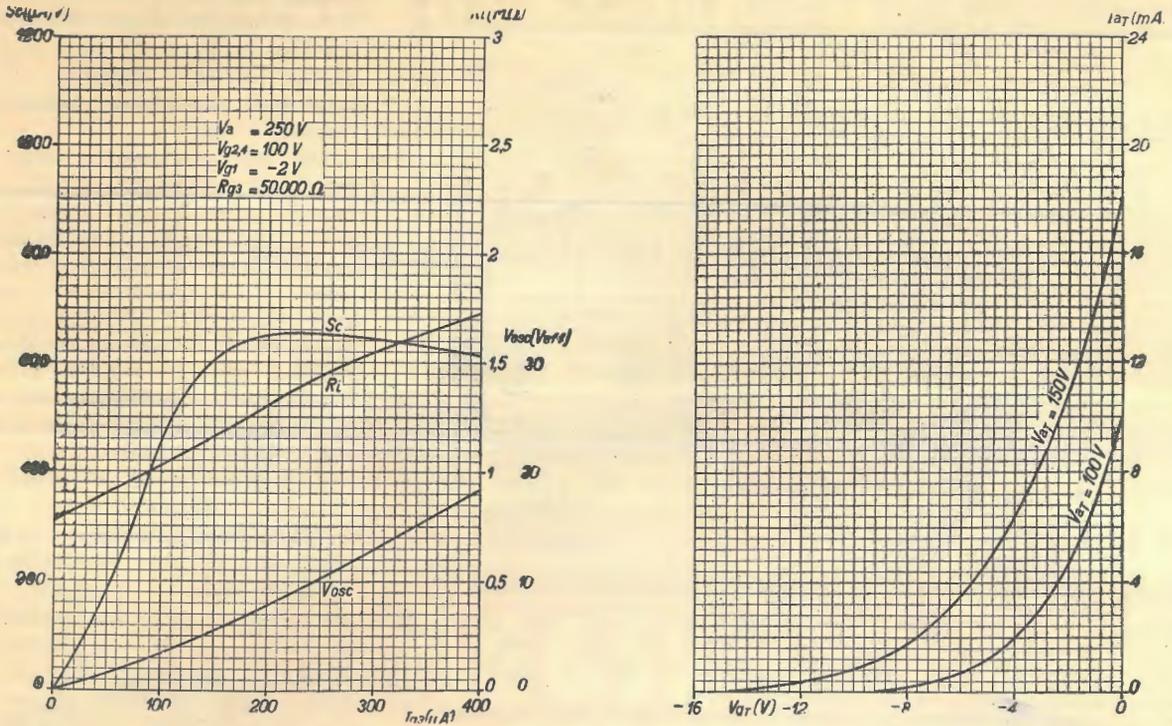The Graph is the Yardstick of Valve Performance



Philips Announce

RATINGS

Heater Volts	6.3
Heater Current	0.3 amps
Plate	250 volts
Plate Current	3.0mA
Neg. Grid Bias	-2 to -23 volts
Grids 2 plus 4 (screen)	100 volts
Screen Current	3.0mA
Conversion Con- ductance (micro-ohms)	-650
Plate Resistance	1.3 meg.
Osc. Anode	100 V — 3.3mA
Osc. Grid Current	0.2mA
Osc. Grid Resistor	50,000 ohms
Osc. Slope	2.8mA/V

ECH35 . . .

Triode-Hexode Frequency Changer

ECH35—a new mixer valve by Philips—has been designed to “measure up” to modern requirements in the following receivers:

- BROADCAST
- DUAL WAVE
- COMMUNICATIONS



★ These ECH35 graphs show: (left) conversion slope, internal resistance and oscillator voltage as functions of oscillator grid current; (right) plate current as a function of grid bias for triode section.

PHILIPS VALVES

FOR ELECTRONIC EQUIPMENT

PHILIPS ELECTRICAL INDUSTRIES OF AUST. PTY. LTD.
 SYDNEY — MELBOURNE — ADELAIDE — PERTH — BRISBANE

GETTING STARTED AT SET-BUILDING

ONLY those who have actually built a radio receiver, switched it on, and heard it work, can know the thrills that lie in the hobby of set-building. Even the cheapest and simplest of sets can give endless hours of enjoyment. For example, with a few simple tools to assist in mounting and wiring a handful of parts, anyone can in several hours put together a receiver that will bring in stations all over the world. This is not an exaggeration, for there are two such sets described in this issue.

Again, there is no end to the variety of receivers that can be built. Simple crystal and one-valve sets are best for a start, to gain experience, but even with these are dozens of different circuits to experiment with. After that, multi-wave receivers can be built, for short-wave, dual-wave and broadcast operation, of tuned radio frequency or superheterodyne types, and powered by batteries or from the electric mains.

The limit in radio experimenting and research work is never reached, even by the world's cleverest engineers. There is always "something new" in radio.

PITFALLS BEGINNERS CAN DODGE

There is no royal road to a theoretical knowledge of radio, but on the practical side there are many useful tips that can be passed on to help those breaking into the radio game to avoid the little pitfalls that crop up from time to time.

The commonest of these will be dealt with in this article, and a further instalment will be published next month.

CHOOSING AND USING RADIO TOOLS

There is almost no limit to the tools that CAN be bought, and which at some time or other will be found useful. At the same time, to build a kit-set only a pair of long-nosed pliers with wire-cutters,

a screwdriver, box spanner, and a soldering iron are required.

However, most, if not all, of the following tools will be found on the average set-builder's bench: Soldering iron, tin of flux and resin core (NOT acid core); solder; long and blunt-nosed pliers; side cutters; hand-drill (with an assortment of about half a dozen hardened steel bits, ranging in size from $\frac{1}{8}$ -in. to $\frac{1}{2}$ -in.); steel rule (graduated in inches and centimetres); reamer (to enlarge holes up to an inch in diameter); flat and three-cornered files; pocket knife (Boy Scout type); screwdrivers (large and small); hammer; and vice (small 4-in. size is suitable).

CHOOSING A SOLDERING-IRON

The first thing any set-builder must learn to do is to solder efficiently, because half the secret of success in set-construction lies in making good joints. A single dry joint can result in noisy reproduction, and can cut hundreds of miles off a receiver's range.

The type of iron used depends on whether mains power is available or not. If it is, then an electric iron is the only wise choice. Provided it is of good make, it will be trouble-free, clean, and will always maintain the same correct temperature.

Otherwise, an ordinary iron with

a medium-sized bit can be used, heated by gas or a small spirit lamp. A fire is not very satisfactory, but if one has to be used, then a simple way of keeping the iron clean is to slip it inside a five or six inch length of metal tubing before placing it in the fire.

GETTING THE CORRECT TEMPERATURE

The average electric iron is rated from 50 to 85 watts, which will produce the correct temperature at the end of the copper tip. A coarse file should never be used to clean or to remove pits from the tip, by the way, as this shortens it, which restricts the heat dissipation and makes the iron too hot. A good indication of an undesirably high temperature is obtained if a coat of black carbon forms on the tip every few minutes. If this happens, a new and longer tip is needed.

The best way to prevent the iron from becoming dirty and pitted is to wipe the tip occasionally with steel or asbestos wool, or a small wire brush. Also the iron should never be dipped into the flux tin.

With an iron that is heated by gas or a spirit lamp, a good indication of the correct temperature is obtained when a blue flame appears round the tip. If the flame turns yellow, the iron is overheated. If it is too cold, the solder will not flow freely, and a poor joint will result.

TINNING THE IRON

The preparation of an iron for soldering, or "tinning" the iron, as the process is called, is simple. After the tip has been cleaned and heated, a little flux should be rubbed over the faces. These should then be cleaned, leaving them glistening as if plated. The shine will soon disappear, however, and will be replaced by a dull silver coating. This is the normal appearance of the tip during use.

Any pits that form should be
(Continued on next page)

Six Simple Soldering DONT'S!

DON'T try to solder with a warm iron; it must be hot.

DON'T try to solder a joint that is not clean.

DON'T fail to tin the iron and the work.

DON'T fail to heat the spot with the iron before applying the solder.

DON'T melt the solder an inch or two above the work and expect it to drop into the joint and make a good job; it won't.

DON'T jar a joint until the solder has had time to cool.

STARTING

(Continued)

carefully taken out with a fine file or fine emery paper. The object is to have the tip faces flat, smooth, and tinned all over.

TOO MUCH FLUX MEANS TROUBLE

The two surfaces to be soldered should be spotlessly clean, and well tinned. If un-tinned copper wire is used for connections, each end to be soldered should be scraped until it is shiny. Then smear on a trace of flux with a wooden match-stick, hold the iron to it, and apply a touch of solder.

The tinned wire can then be overlapped on to the terminal or lead to which it is to be soldered, the iron applied to the joint and a little resin-cored solder run in. The joint is made when the solder flows freely and evenly over it, but when removing the iron be careful not to jar the new joint until the solder has hardened.

Resin-cored solder (NOT acid-

core) which is supplied in reels of various weights, is the handiest to use. If ordinary solder is preferred, a tin of flux is necessary as well. Under no circumstances should an acid flux be used, because of the danger of corrosion.

In radio wiring particularly, flux should always be used very sparingly, or a carbonised iron and dirty joints will be the result.

PREPARING A CHASSIS

Nowadays steel is nearly always used for commercial chassis, but constructors will find that aluminium is quite hard enough to work with makeshift tools.

At the same time, aluminium is so soft that it marks easily, and also, it tends to clog a drill. To avoid this, turpentine should be used as a lubricant, particularly when large holes are being cut. A wood bit is best for this job. The $1\frac{1}{8}$ -in. size is the most useful, being suitable for almost any coil or valve socket on the market.

To drill a hole with a bit of this kind, rest the chassis on a block of

wood so that the bit point can pierce into it. After a few turns of the brace handle, the hole will be grooved out, and at this stage a few drops of turpentine should be applied, otherwise the centre piece will be torn out rather than cut, and a poor job will be the result.

Any rectangular hole such as that needed for a power transformer should be marked out, and a few small holes drilled along the lines from the corners. A jig-saw or a hack-saw blade held with a cloth will finish the job.

After any cutting at all has been done, the edges of the hole should be cleaned up with a pocket-knife or a fairly coarse half-round file.

Smaller holes are required for other components, such as wet electrolytic filter condensers ($\frac{3}{8}$ -in. diam.) and large bushes ($\frac{1}{2}$ -in.). To make these, first drill a hole in the chassis to take the point of a plumber's reamer, which will then complete the job.

And Now . . .

POLYSTYRENE CEMENTS

WITH THE SAME UNQUALIFIED ELECTRICAL PROPERTIES OF
ETHOLEX POLYSTYRENE SHEETS AND RODS.

"STYLON" Liquid Polystyrene, for cementing Polystyrene units together.

"STYLON G.P." for joining Polystyrene to glass, plastics, ceramics, metal, rubber, etc. A general purpose insulating cement.

IN 3-OUNCE CONTAINERS, WITH INSTRUCTIONS FOR USE

3/- each (plus tax) Post free.

ETHOLEX PLASTICS

108 CHAPEL STREET, WINDSOR, MELBOURNE, AUSTRALIA

CALLING CQ!

By Don Knock, VK2NO

When the "balloon went up" recently on "Forty" and "Twenty," Sydney VK2's learned of the occurrence more or less by the "grapevine," plus the fact that the word speedily got around on "Ten." Efforts were made by local prime-movers to have the news broadcast through the National or other stations, but for some reason nobody rose to the occasion. Sydney's "Great Dailies" were conspicuous by their reticence to say anything about Ham radio; although, should war ever strike again, they and their satellites will be loud in their lauding of the key-punching amateur, and will no doubt wave flags as he marches off to the gunning show.

But they didn't say anything about the doling out of crumbs from the table of the frequency annexers. How different to Melbourne's newspapers, every one of which carried a story about the Australian radio amateur and his status quo! Particularly helpful was one lengthy inspiration which included this: "he is still by far the most illiberally treated of the amateurs of the world. He has only part of the operational facilities



Don Knock smiles as he looks over a butterfly h.f. tuner which he picked out of some salvage gear.

now available in Britain, America, South Africa, and New Zealand." Orchids for the gentlemen of the Press — Yarraside version! One paper carried a sub-heading reading: "Babel on 20-40 metres." How true *that is*, at least on "20."

* * *

If any Ham reader of these Notes can supply information regarding

the circuit details of an American receiver, a Wells-Gardner BC-348N, such information would be appreciated by old-timer Phil Levenspiel (VK2TX) of Wyong, N.S.W.

* * *

One can well imagine how an important subject for constant discussion among Ham POW's during their enforced stay as "Guests of the Enemy," would be one very prominent in their thoughts. Dick Rees, VK2APW, whom we referred to recently, sent up a sketch — the original drawing done by a G6 Ham who was a POW with Dick in Germany. Unfortunately it is not suitable for reproduction without redrawing and by so doing much of the original sentiment would be lost. It is a scheme, and

(Continued on next page)

INTERNATIONAL CONTEST BY W.I.A.

Federal Executive of W.I.A. is organising an International radio contest for transmitting and receiving amateurs in Australia some time during the current year. Many will remember the very popular 1934 Centenary Contest, upon which the proposed contest will be modelled.


A feature will be inclusion of VHF channels, and this should be a decided stimulus in the populating of

bands such as "Six" and "One and Three-quarters." It is anticipated that radio manufacturers will donate much valuable equipment for awarding as prizes. We shall have much more to say about this contest in the near future. Contest Manager is Bob Cunningham (VK-3ML) who can be reached at Box 2611, G.P.O., Melbourne.

a very workable one, for a combination Straight Crystal/Tritet/ECO functioning from a ganged switch. There is provision for indicator lights in the switching—says Dick, "Green for Safety . . . that's ECO; Red for 'watch your step' . . . that's Tritet; and White for 'plain crystal'." There is a lot to commend the idea, worked out in captivity, and "Anyway," says VK2APW, "it gave us a week's pleasure. If any readers are sufficiently interested, we will get the scheme drawn up as a circuit diagram and run it in some future issue.

* * *

A Danish Ham, a member of the "Short-wave Clan," writes to BSW-L998, Gordon J. S. Hepburn, 10 Mc'Gregor Street, Croydon, New South Wales, asking for the name and address of any Australian amateurs interested in corresponding with amateurs in Denmark. The idea is a good one as distinct from the usual quest for QSL cards, and pen friends in other countries can become material friends in times of travel. The OZ's are recovering from a bad time during the Nazi Occupation and overseas friends would do much to boost morale and life in general. Mr. Hepburne

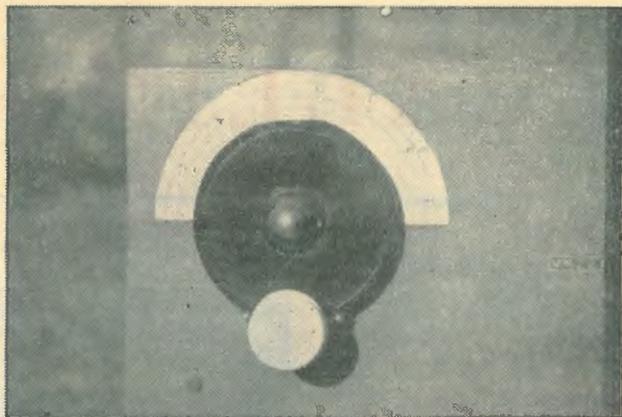

MODERNISING AN OLD 0-100 DEG. DIAL

Direct calibration is easily provided for by cementing a card scale with inked arcs in different colours to a rubber wheel-driven metal dial of the old "instrument" kind. A "Perspex" or celluloid indicator projects over the new scale and, if

this has small holes with an inked centre line, direct indicators can be made on the scale. The original 0-100 degree engraving on the edge of the dial is retained for quick reference.

will pass on the details to any interested reader — Ham or SWL.

ON THE DX BANDS

With the lid partially off on "Forty" and three parts so on "Twenty," the latter band in particular sounds like a bad case of

"the devil take the hindmost." No doubt things will even themselves up a bit later, but just now there is only one word for the din and that is "Chaos." As from the evening of June 30 last, the G's and others in the European scene made a start on the two bands (officially). The afternoon of July 1, from 3 to 6 p.m. E.A.T., was remarkable for the number of un-QRM'd Europeans on "20." In that time I noted Englishmen, French, Swiss, Dutch, Norwegians, and a station in Greenland, all merrily toting along on CW QSO's. At this time VK's hadn't received any word that the lid would be lifted, so it was a case of listening only at this end. The picture changed a few hours later when the Americans got the green light from their F.C.C. and then it was "ON" with a vengeance. Meanwhile, VK's got the OK — and thence onward the story becomes one of struggle through the terrific QRM, not so much from our own locals, but from the seething mass of W phones. There is nothing unreal about the picture — it was just what I expected.

Everyone to their own liking in

CHANNEL ECHOES

Consternation is rife among some Sydney VK2's as a result of official correspondence from the licensing authorities to individuals, stressing the need for the suppression of Harmonics. Idea prevalent with some of the recipients of the warnings is "What *does* it matter about harmonics hitting 56 M/cs. anyway?" Answer is, unfortunately, that it matters a great deal in these progressive times. The old amateur stamping ground of 56-60 M/cs. is likely to become a very important television or FM channel in the not-so-distant future, and the effect of powerful harmonics, etc., from DX hunters and "rag-chewers" is not difficult to visualise. There is nothing formidable about the cure — Handbooks deal amply with the

subject. A good scheme is the use of a Faraday shield between final "tank" and antenna coils, where direct inductive coupling is employed with a single-ended PA. Also, push-pulling the final link-coupling to the antenna circuit is a big help, especially where a direct earth connection is used. Therein can be inserted a tuned trap to absorb the unwanted harmonic and to take it to earth out of harm's way. In U.S.A. harmonic suppression is a "must" for B.C. stations, and has been so for a long time. We surmise that with crowded occupancy of "20" and the allocation of the old "Five" metre band for new Services, amateurs everywhere will need to clean house a little on the harmonic family.

amateur radio — but for me — I have a warmer spot in my heart than ever for the VHF's! Thank heaven we have "Six" and the next VHF band for a different, but equally satisfying phase of the game.

* * *

Readers shouldn't deduct from the foregoing remarks that I am "agin" the DX bands — far from it — in fact, I like 'em. So much so that I have already been and broken the ice on "Forty" and with soul-satisfying result. With only 50 Kc/s to play around in, the prospect is, of course, quite grim for the immediate future, unless those who hold the sword of Damocles relent and widen the band. But — having a crystal that puts me in the snippet of the band — also a handy little 6V6G crystal test oscillator in the shack — an idea was born and went into effect. A small power supply — a two turn link around the little "tank" to the antenna coupler on the wall — a key in the cathode circuit — and there we were! One brief CQ and back came ZL2AO with a 589 report, followed by similar ones from ZL1LZ and then VK4SN. Input

power? — all of 5 watts — and the antenna an end-fed W3EDP "hybrid." If that antenna is no great shakes on "Ten" it is a wow on "Forty!" You'll find it in the RSGB Handbook — sheer simplicity. Main thing is that this old band is as useful as ever for QRP CW rigs . . . at least until the QRM situation looms . . . as it surely will.

* * *

I had a rather unexpected experience on the evening of July 4, (maybe the "Independent" feeling accounted for it) and one which emphasises just how careful tuners up of ham gear should be to ensure operation in the correct band. Using my Philips R163 Communication receiver I had been listening on "80" to phone conversations between ZL's — and the receiver happened to be left switched on that range. Deciding to seek a key QSO on "40," I sent preliminary "T-E-S-T- de VK2NO" on 7175 Kc/s. and was considerably surprised to hear a strong phone on "80" calling VK2NO — a VK2 located about 200 miles from Sydney. Expecting that this was a re-

FINE RECEIVER

Best example we have seen in the receiver line is an effort by VK2AZ, who put together a compact high-gain super with 6AK5 R.F. ahead of 9001, 9002 mixer-oscillator combination. Nevertheless, we feel that our 955/955 Converter with EF50 at 21 mC/s into a Philips R163 receiver is an ideal arrangement. With **too much** R.F. pre-selection as may be produced by a 6AK5, car ignition and other noises are predominant. The Converter pulls in all the stations well, and much of the electrical QRM is avoided by the receiver.

Special "wonder R.F. pentodes" such as 6AK5's are applicable to full advantage at frequencies higher than 50 mC/s. They provide a fine answer to effective R.F. amplification at 166-170 mC/s. No, brother, I have NO 6AK5's and haven't been lucky enough to meet any other than in the pages of "QST."

markable overtone from "40," I hurriedly tuned the receiver to the band, but nary a sign could I find of the VK2 there. Thinking that there must be something queer about the whole thing, I called CQ on the key on 7175 Kc/s. and lo, and behold this VK2 phone again answered my on "80." With that, I answered the call, hooked up with the station and asked, "How come?" — inasmuch as, at the time of writing, (July 5), we haven't been given any OK on "80." I told this station that he was getting out fine on "80," but where was his sig. on "40"? Whereupon he thanked me for the tip, reckoned there must be something wrong, and decided to close down and look into things. There is a moral in this incident, my friends: Don't take things for granted — keep a "Spotter", a calibrated absorption meter in the shack — and make sure, if you are using a crystal at "80", that your final, or whatever stages follow the CO, is tuned to the correct band! Not everybody is "Frequency Conscious" regarding relation of L/C ratios in tank circuits, and the humble "Spotter" is then indispensable.

(Continued on next page)

SLAUGHTER OF VALUABLE GEAR

Our feelings about the wholesale destruction of valuable radio and electronic gear under the Lend-Lease ruling are those of any person with a liking for the ingenious products of clever brains and hands.

We cannot agree that such senseless action is imperative for the future welfare of this or any other country. Feelings of Service radio men at having to stand by and witness destruction of equipment are akin to a dream about QST's advertisement pages—an illustration that one possesses one of the superbly engineered receivers depicted therein—and then awakening to find that it was but a dream! Latest outburst comes from an ex-A.E.M.E. craftsman, who says: "I saw it happen many times on Bougainville during the last 16 months. When you have seen "Super Pros" and similar receivers, test equipment, cartons of valves, 1852's,

"Acorn" valves, miniature valves and heaps of other material burned before your eyes, whilst you are held off at revolver point, your scruples about honesty vanish quickly. Not only Americans and R.N.Z.A.F. are guilty, but our own forces as well. I saw one salvage depot burn Philips signal generators, super testers, multi-testers, etc., until I almost wept with rage."

So it goes—the post-war crazy world in which many an ex-Service radio man would at least appreciate the right to purchase a quantity, however limited, of such equipment. This picture applies not only to radio—but every imaginable kind of equipment. Arguments that destruction is necessary to guard future trade and employment may be sound, but we feel that it would have been better to store the stuff against a rainy day! Or maybe it will never rain again!!

HAM NOTES

(Continued)

Several English radio publications carry a par about a G8 Ham who in February last "made the first international amateur contact since 1939" by QSO'ing a Norwegian. That's rather a sweeping claim, and we assume that it is meant to apply to Britain only. VK's were working W's and others **officially** from the turn of the year.

* * *

Talking of ZL's on "80," a letter to a VK2 from a ZL3, just to hand, says that the Maorilanders now have the whole of the band-widths back, and that the ban on overseas working on "80" has been tossed overboard. That's not all, they are promised definitely in a matter of months that the new 21 to 21.5 M/cs. band will be available; also they now get 50-54 M/cs. plus all the VHF and SHF allocations that the Americans get. Comparison with VK conditions is, at the moment, extremely odious.

* * *

In a previous issue I said something about an American ad in an overseas Mag lauding the properties of a new war-developed adhesive for general purposes, and commented that a practical Ham could no doubt find a lot of uses for such a commodity. Almost immediately after having said that, a business colleague told me that just what I had been referring to is now available, in fact, is made in Australia. Acquiring a tin of this new "stickum," it was put to test, and I must say that I think the makers are almost modest in their claims. This adhesive is a real bonder. It literally bonds together practically anything. "Bakelite" type mouldings and suchlike are "pie" for it, and after applying a little of it to a roughened piece of bakelite, and putting that on the surface of matt finish aluminium, the impression is that the two have been welded together. At the present time the new adhesive is available only in limited supply, and so is supplied only to industrial concerns where

application is necessary for constructional purposes. The name of a great American industry is behind it, and I suppose the originators will commence to advertise their product at the appropriate time.

* * *

Talking of adhesives . . . the Ham is doing a lot with acrylic resins of the Perspex variety in these days, and I suppose more was done to popularise the use of these transparent plastics by the Digger, who fashioned all manner of trinkets from the cockpit covers of crashed planes, and sent them to his YL's back home. This material has lots of uses, and firstly, in Ham radio, the use is that of insulation. Be warned, however, that all that you can see through is not of the polystyrene family . . . some of the acrylics are composed of chemical constituents purely for light-pass-

ing qualities. Etholex-Polystyrene, for example, is a horse of a very different colour . . . tried and proved under rigid War specifications . . . this is insulating material par excellence. Much can be done with most of the transparent acrylics in the way of reforming by applying heat or by immersing in hot water. They soften quickly and refashion easily, setting hard again very speedily. Pieces can be cemented together, but here it becomes necessary to apply the correct cement, not any haphazard dope sold in tubes at the "5 and 10" store under weird sounding names . . . but cement produced especially for the job. In Sydney I located a supply of genuine Perspex cement which virtually welds the material. Pieces joined thus appear to be equally as strong as one solid portion.

—VK2NO.

WORKING ON 166 M/cs.

What is doing in other States and locations I know not, but in and around Sydney the VHF channel of 166 M/cs. is coming in for an increasing share of attention, with pleasing results, despite difficulties. On the evening of July 4, 1946, VK2LZ, at Wentworth Falls, 60 odd miles from Sydney, copied VK2NO at R7 on phone, and VK2WJ at R6 on MCW whilst using a small transceiver under quite adverse conditions. As VK's 2NO and 2WJ are on the coastline at Waverley and Maroubra, respectively, the reception comprises a bit of a record at the frequency of 166-170 M/cs. Two weeks previously VK2NP, of Gladesville, made a two-way QSO on this band with VK2KI operating mobile at Lawson, N.S.W. There is no doubt about it — ever since Eric Ferguson (VK2BP) and VK2NO started the ball rolling on "5 metres" in 1934, the Blue Mountains region has proved to be an Open Sesame for VHF's. We are finding snags about communication on 166 M/cs. in the form of complete local screening. Although the stations of VK2WJ and 2NO are only 4 miles airline apart, and both

stations can be heard at good strength 60 miles away up in the mountains the two stations have not yet succeeded in hearing each other. There are two rolling elevations in between, to say nothing of buildings. Trees are found to be prolific absorbers of radiated energy at this frequency range. The answer will no doubt lie in the use of high gain directive arrays to push the signals through and the immediate consolation is in the compact nature of such arrays. Stations using 166 M/cs. intermittently in and around Sydney are: VK's 2YE, 2KI, 2AFH, 2AGL, 2DP, 2NP, 2WJ, 2ABZ and 2NO. There will be others. Some of the stations quoted are using transceivers as yet, but at the writer's station separate receiver and transmitter are in use — also at VK2NP and 2WJ. Let me be emphatic to those intending communication of the band — standard valves and practice definitely will not do — anybody that tries to get away with the usual "5 metre gear" is in for a first-class headache. VHF receiving and transmitting valves are essential—valves of the acorn and "horned" types.

—D.B.K.

HAM LINGO IS SNAPPY

As a heritage from the days when the code was universally used by the amateur, today he has a language of his own that to the uninitiated sounds meaningless. The commonest abbreviations are quoted in the article below . . .

HAM lingo — the language of the radio amateur — is snappy, and highly descriptive. It is made up of idioms, abbreviations, technical terms and phonetic words. It's Greek to the public and a source of distress to the beginner. It is enough to set anyone on his ear!

Some of the idioms used by the ham have their roots in the field of commercial wire and radio telegraphy. The old-time Morse telegraphists originated the word "bug" as a happy and brief tag for the semi-automatic code keys used then, and now, for high speed transmission.

The early type of hand keys were made of brass, and the operators of such keys were dubbed "brass pounders." If an operator worked his key well, it was said of him that he had a "good fist," just as one might say that a singer had a good voice. Hand key operators were often subject to a temporary or permanent loss of muscle reaction which affected their sending, in which case they were said to have developed "glass arms." Double acting keys were known as "side swipers." These and other idioms originating with the old-timers have been kept alive by the ham.

Many of the abbreviations had their origin in the field of telegraphy. Such short-cuts as "abt" for about, "ck" for check, "fm" for from, "hr" for here, "sig" for signature, and "tks" or "tnx" for thanks, are good examples of a few of the many abbreviations the early amateur radio telegrapher appropriated for his own use. The substitution of the letter "x" for parts of a word, such as "tnx" for thanks, "dx" for distance, "px" for press, and "wx" for weather, had also

been taken up by the ham, and he has added a few others of his own, with the "x" tacked on to the front end of the word, such as "xtal" for A reversal in form is shown in the use of "rx" for receiver.


The ham also uses the International "Q" Code, together with a crystal, and "xmtr" for transmitter. few combinations of his own making. He employs such universal signs as "R," meaning okay; "K" meaning to go ahead; "SK" indicating the termination of a transmis-

sion; "73" meaning kind regards; and "88" meaning love and kisses.

AMATEUR ABBREVIATIONS

But ham lingo is far from being a borrowed language. When it comes to trick idioms and phonetic spelling, the ham has it all over the commercial crew.

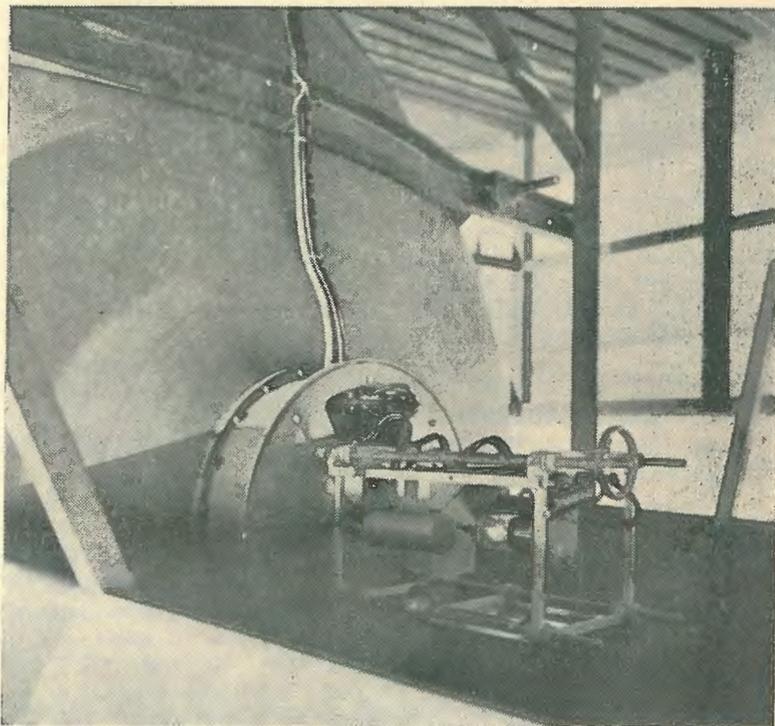It all started before vacuum tubes were in use, when powerful spark transmitters were called "rock-crushers," synchronous rotary spark gaps were called "sinks," and headphones were called "cans." The first continuous wave (c.w.) tube transmitters were cynically referred to as "peanut whistles" and their operators as ????. A particular



This might appear to be a modern example of application of a Magnetron oscillator and parabolic reflector for UHF's, but it isn't. This picture was taken at Lympne, (England) in 1936, and was the English end of a 60 centimetre telephone link with France. In Wellsian fashion it was truly a forerunner or "things to come."

HAM LINGO

(Continued)

type of transformer was called a "coffin," and an aerial became known as a "sky hook." When licenses came into being they were known as "tickets," and transmitting tubes were christened "bottles." The District Radio Inspector became the "R.I."

There were no radio-telephone stations in those days, and it was a task for one ham to carry on lengthy "rag-chew" with another ham by means of telegraphy unless he resorted to various forms of abbreviation. It thus developed that laughter was registered by simply transmitting the letters "HI," and the natural enthusiasm the ham had for the game was aired every few minutes by merely sending the letters "FB" — which, to you, is "fine business." Then, surprisingly enough, all hams, no matter their age, became old men, or simply "OM", over the air. Mother was referred to as "OW," which was alright since she couldn't decipher the code, and the girl friend became the "YL." If the ham married she immediately became an "XYL," which has never seemed quite complimentary, but the girls lap it up.

And then there was the phonetic spelling interspersed with abbreviations. Typical copy would read something like this: "SA OM IS TT UR YL I SAW U WID LAST NITE? SHE'S A SWL NO ES

NEW ZEALANDERS!

The quickest and simplest way
of subscribing to the
"AUSTRALASIAN RADIO WORLD"
is to get in touch with
H. BARNES & CO.
4 Boulcott Terrace
Wellington

SUBSCRIPTION: 10/6 Per Annum

They will arrange all the details
and give you prompt and cour-
teous attention.

DO IT NOW!

HW! HI!" Translated into English, this copy reads: "Say old man, is that your girl friend I saw you with last night? She's a swell number and how! (Laughter)."

The c.w. ham of today continues the use of the abbreviated form in his transmissions, but he is not, as a rule, apt to carry it to extremes. Aside from "es" for and "t" for that, "hr" for here, "hw" for how, and a few other straightforward short-cuts, he sticks fairly close to phonetic spelling. A few examples are: "fone" for phone, "gud" for good, "cum" for come, "sez" for says, "cud" for could, "ur" for your, and "sed" for said. Some words are given the phonetic spelling and additionally abbreviated, such as: "Sked" for schedule, "freak" for frequency, and "sine" for sign or signature.

NEW DEVELOPMENTS BROUGHT NEW TERMS

Improvements in vacuum tube transmitters brought a new group of words. High voltage, radio frequency currents were being used, and the word "hot," employed by electricians to denote a live wire circuit, came into use. Later on, high power radio-frequency current came to be known as "soup." This term is also used to denote background noise in reception, and if a signal is lost in interference, it is said that the signal is "down in the soup" or "in the mud."

When the ham commenced using radiophone equipment, such phonetic abbreviations as "mike" for microphone, and "fone" for radiophone, came into use. Some of the lingo of the c.w. ham was carried over, and it is far from uncommon today to hear a ham on fone use the abbreviation "HI" when he could just as easily laugh. It's just a case of habit. It's the same with "K" and "SK," most 'phone hams have resorted to such terms as "take it away," "toss is to you," "come in somebody," "over," or some such phrase when they are turning it back to the other fellow, but some of the fellows hang on to the "K" of their code days, and to "SK" when they are signing off.

The "Q" signals used by the ham are identical with those established by the International Radiotelegraph Convention. Each signal can be formed as a question or answer. "QRA"? for example, means: What is the name of your station? The answer would be: "QRA . . ." with name of the station. There are a large number of these "Q" signals, many of which are of no use to the ham. Those he does use are often given a slightly different or broader meaning so that they may better fit conditions.

For instance, the original meaning of QSO? is: "Can you communicate with direct (or through the medium of)?" But the ham also uses QSO to mean a two-way contact or conversation. In talking to another ham, he may pass the remark that he had a fine QSO with such-and-such a station, and in this sense the signal has practically the same meaning as the word "talk."

The following list of "Q" signals is not complete, but it contains the letter combinations most frequently used in amateur communications. The interpretations given are those adopted by the hams and are not necessarily identical with the originals. Each one can be used as a question or an answer.

QRA—What is your address?
QRG—What is my frequency?
QRK—Are my signals good?
QRM—Man-made interference.
QRN—Static interference.
QRP—Shall I decrease power?
QRT—Shall I stop sending?
QRX—Stand by.
QSA—What is my signal strength?
QSB—Do my signals fade?
QSL—Please acknowledge our QSO.
QSO—Two-way contact.
QSY—Shall I change my frequency?
QTR—What is your time?

Everyone should know that CQ is the general call for any station, and DX means long distance. The familiar ham call of CQ DX is an invitation from any distant station to reply.

INDEX TO VOLUME 10

At the request of several readers we have published this index to Volume 10. Back numbers are available at 1/- each post free by sending postal notes to Australasian Radio World, 336 Waverley Road, East Malvern.

THEORY AND FUNDAMENTALS

Short Course in Fundamentals, Part 5	June 1945
Short Course in Fundamentals, part 6	July 1945
Short Course in Fundamentals, Finale	Aug. 1945
Theory of Oscillation	July 1945
Power Supply Filters	July 1945
Making Paper Condensers	Aug. 1945
Decibel-Logarithmic Function	Aug. 1945
Proper Amplifier Design, Part 1	Aug. 1945
Part 2	Sept. 1945
Part 3	Oct. 1945
Vibratory Power Supplies	Oct. 1945
Hamond Electric Organ	Dec. 1945
Crystals Will Not Amplify	Apr. 1946
How Signals are Broadcast	Feb. 1946

CONSTRUCTIONAL ARTICLES

"Little Companion" 5-Valve D.W.	Nov. 1945
Home-Made Filter Chokes	Jan. 1946
"Metropolis Four" A.C. Broadcast	May 1946
Loud-Speaker Baffles	May 1946
Ferrotune Superhet	May 1946

RECEIVER CIRCUITS

Well-Tried Reflex	June 1945
Camera-Case Portable	Sept. 1945
Amplifying Crystal Circuit	Sept. 1945
Anti-Theorist	Feb. 1946
Long-Range Two-Valver (Battery)	Apr. 1946
My Own	Apr. 1946
A Decade of Battery Circuits	May 1946

AMPLIFIER CIRCUITS

Tone-Compensation Amplifier	July 1945
Answer to the Cathode Follower	Sept. 1945
New Cathode-Follower	Sept. 1945
Stereophonic Amplifier	Nov. 1945
Electronic Filter	Nov. 1945

TEST EQUIPMENT

Resistance-Capacity Meter	July 1945
Probe Adaptor for VTVM	Sept. 1945
Transitron Oscillator	Oct. 1945
Simple Service Oscillator	Jan. 1946
Signal Tracer in Miniature	Feb. 1946
Improved Modulated Oscillator	Apr. 1946
Simple Impedance Measurements	May 1946
Channel Analyser	May 1946

AMPLIFIER CONTEST

Vic. Amplifier Contest Preliminaries	Nov. 1945
Vic. Amplifier Championship Results	Dec. 1945
The Champion Amplifier Circuit	Jan. 1946

HINTS AND TIPS

Using a P.T. as an O.P.T.	June 1945
Eliminating Hum	Aug. 1945
Small Hints for Big Effects	Aug. 1945
Starting in the Radio Business	Sept. 1945
Standard Valves for 1945	Sept. 1945
Getting the Best from the Pick-up	Sept. 1945
Hints about Automatic Volume Control	Dec. 1945
Cathode Follower Tests	Jan. 1946
Duplex Speakers for Fidelity	Jan. 1946
Improving DX Performance	Feb. 1946
Using the 1852	Mar. 1946
Using Available Gangs	Mar. 1946

AMATEUR RADIO

Prolific Postwar Field	Oct. 1945
Ham Notes by Don Knock—Started in	Nov. 1945
Lamb Noise Suppressor	Dec. 1945
New Ham Technique	Feb. 1946
The VK2NO-V6	Mar. 1946
Efficient Aerials for VHF	April 1946
Polystyrene for Amateurs	April 1946
50-Watt Phone Transmitter	April 1946
What of the Future?	May 1946

RADIO LOCATION

War Winner	June 1945
Radar with the Navy	Oct. 1945
Principles of Radar	Jan. 1946
Growth of the Radar Chain	Feb. 1946
The Radar Proximity Fuse	Apr. 1946

GENERAL

Walkie-Talkies in Peace	June 1945
Adventures of Ship's Operator	June 1945
History of Microphones	June 1945
Radio in America	July, 1945
Radio for Model Planes	Aug. 1945
Trade with America	Aug. 1945
Future Application of Radio	Sept. 1945
Our Future Policy	Oct. 1945
Television on Rental Basis	Nov. 1945
Electro-Dynamics are Obsolete	Dec. 1945
Employment in Radio Trade	Dec. 1945
Trends in Set Design	Jan. 1946
Von Luckner was a Poor Spy	Feb. 1946
Wireless Set No. 10	Feb. 1946
New Permag. Speakers	Mar. 1946
Dismal Future for Trade	Apr. 1946
Personal—A. G. Hull	May 1946
About Disposals Bargains	May 1946
Sydney to Macassar	May 1946

Shortwave Review

CONDUCTED BY

L. J. KEAST

NOTES FROM DIARY—

VOICE OF DX IN AUSTRALIA

Ern. Suffolk, Publicity Officer of S.A. Australian DX Radio Club, writes: "The above Club has been able to inaugurate DX sessions from Radio Australia. Here is the set-up: Weekly sessions to the British Isles of 12 minutes duration commencing July 28 at 1.45 a.m. EST from VLA-3, 9.69 mc, 30.99 m. Weekly sessions to U.S.A. and Canada from VLC-9, 17.84 mc, 16.82 m, commencing July 28 at 11.10 a.m. EST. This session to commence with will be of 20 minute's duration, and later may be extended to 30 minutes. The sessions will be scripted as Voice of DX in Australia, and not as a local club affair. Therefore will be grateful to have any "dope" on DX, (or time of hearing) wave-lengths especially on new call signs skeds or change of skeds for any known stations."

Well, this looks like an excellent opportunity to publicise Australian DX and congratulations go to those enterprising South Australians who have engineered this scheme.

Mr. Suffolk's address is Lobethal, South Australia, and he will welcome any information or suggestions listeners care to send him.



SAYS WHO?

Bill Wright, of Plympton, South Australia, writes: "SEAC, Ceylon, advises that they are now on the air on 15.12 mc 19.84 m from 10.30 a.m.—9.45 p.m., and on 6.075 mc, 49.38 m from 10.30 p.m.—3 a.m. The transmitter in use is 100 k.w. output. On Friday, June 7, and Saturday, June 8, the 10.30 p.m.—3 a.m. transmission was radiated on 9.52 mc as a test. This frequency was used in lieu of the usual 6.075 mc. Address: "Recep-

tion Report," Radio SEAC, A.B.-PO., 9, Colombo, Ceylon.

"New Zealand's first Police transmitter, ZLPK, Wellington, is heard in the evenings on 1.680 mc."—Cushen.

"TBILISI or AZERBAIJAN on approximately 11.96 mc is heard at midnight in native tongue and music; signs at 1.03 a.m. Azerbaijan frequently mentioned."—Edel.

Dr. Gaden forwards me a letter he received from Armed Forces Radio Service, Los Angeles. It reads:

Dear Shortwave Listener:

This will acknowledge and thank you for your recent letter reporting shortwave reception from one or more of the Armed Forces Radio Service/OIC transmitters.

We sincerely regret that since Armed Forces Radio Service shortwave broadcasts are produced solely for the listening pleasure of members of the armed forces overseas, we are unable to (grant requests for schedules) (verify listener reports from private sources.

However, we are pleased to know that you find our programmes worthwhile, and appreciate your kind interest.

Cordially,

(Sgd.) JOHN V. ZUCKERMAN

1st Lt., Sig. Corps

Shortwave Section.

Phil Byard has had some splendid sheets made for keeping track of schedules, and he has sent me a lay-out of the Crosley stations. A colour code has been used so you can tell at a glance whether transmission is to Latin-America, North

Africa or Europe . . . A very nice job, Phil, let me know cost of sheets.

Rex Gillett in "Radio Call" reports hearing a Chinese station on 9.73 mc, 30.83 m, just after 11 p.m. which he thinks is no doubt KGOA. He says, "At the time mentioned a relay of XGOY's programme was being taken. Following the relay which consisted of a talk in English, the stations continued with their own programmes. XGOA is the call-sign for this frequency, the station has not been reported for some time." (XGOA used to be on 9.72 mc, 30.86 m, and then jumped to 9.728 mc, 30.83 m, but according to latest advice from Washington, U.S.A. they are back on 9.72 mc . . . Perhaps crystal trouble again? — L.J.K.)

Arthur Cushen has a verification from OAX6E, Arequipa, 6.333 mc, 47.39 m. They verified with two postcards; one a view of the city and the other a picture of the main studio during a concert. (That was pretty good to log this Peruvian, as "Radio Continental" only has a power of 300 watts.—L.J.K.)

Bill Wright says a new station broadcasting Indonesian-type programmes has been heard at 12.30 a.m. on 5.61 mc, 53.48 m. (I have not heard this one, but "Radio Republic Indonesia," Djokjakarta is listed on 5.66 mc.—L.J.K.)

Rex Gillett recently received a verification for his report on Radio Italiana, 31.15 m. The location of Radio Italiana is Busto Arsizio, in province of Lombardy. Other veries received are: ZOY, 41.13 m; TAQ, SBT, Durban 48.62 m; WNRA; WNRI; WNRX; COBL; PY-11; LRX; VE-9A1, 31.45 m; VL3AE on 3090 kc. (Victorian
(Continued overleaf)

NEW STATIONS

CBFZ, Montreal, 15.19 mc, 19.75 m: This was inadvertently missed from June issue. Phil Byard of Launceston wrote me on May 23: "Heard this Canadian, which I think is a new one with news at 10 p.m. and morning devotional service at 10.15. Very good signal."

I also heard from Bill Wright, of Plympton, South Australia. "First heard at 9 p.m. when a bright breakfast session was being presented. CBS news heard at 11 o'clock."

(This 7,500 watt station has been listed for some time, but I think the above reports are the first in this country.—L.J.K.)

Forestry Commission); and CBFX for temporary outlet of 31.21 m. The veri. stated this outlet is no longer used, being replaced by CBFZ, 15.19 mc, since April 28.

The "Malanda Tiger" has been prowling around again whilst the paint on the Model Aeroplanes dry, and elsewhere in this issue will be found some of his loggings. By the way, his model planes are splendid and my little grandson gets a great lot of fun out of his "Catalina." Hugh tells me he has bought a motorbike — just afraid that with the planes and now the temptation for a spin after he has tended his fine Jersey herd, DX-ing may take a miss-in-baulk.

"A new 100 kilowatt transmitter at Shepparton was recently testing on 6.10 mc, and radiated Radio Australia programmes during the test. Advice from the P.M.G., Melbourne, states that this transmitter will soon be put into service under the call sign VLB.—Wright."

Arthur Cushen is experiencing housing troubles like the Australian

RADIO BANDEONG, 4.80 mc, 62.50 m: Arthur Cushen reports this one. Is well received 10.30 p.m.—12.30 a.m. All Indonesian-Dutch. Uses chimes as identification.

RADIO SOFIA, Pavlovo, 7.67 mc, 39.11 m: This new frequency heard as well as on 9.35 mc. (Evidently this Bulgarian has settled down on 7.67 mc; they had been testing on 7.64 mc. I think Arthur means 9.325 mc for the other frequency. They were on 9.345 mc for a little while and also on 9.30 mc., but eventually went to 9.325 mc. —L.J.K.)

home builders, but at last writing expected to be in the Love Nest by end of June.

His verifications now total: Shortwave 565 and Broadcast 400 — well, there's no love's labour lost about that; it represents the result of burning midnight oil and setting the alarm on multitudinous occasions.

"Moscow is heard with news in Russian at dictation speed at 1 a.m. on 6.02, 12.25 and 12.06 mc."—Edel.

HELP WANTED

Dr. Gaden wants to know who is on about a dead 50 metres at night. Sounds like a Chinese station . . . very noisy spot . . . Nothing heard to give a clue.

UNIVERSALITE

The last batch of subscribers' names was sent early in May, and copies should be forthcoming any time now, although I have found mail from U.S.A. is very erratic and sometimes arrives 2½-3 months after date shown on envelope.

CE—, ? Santiago, 6.22 mc, 48.23 m: And still another from the newly-wed. Arthur says: "Heard at 2 p.m. with bagpipe notes similar to the identification signal of CE-1173, which, by the way, has not been used lately, so it looks like a change of frequency."

(CE-117, Santiago, whose slogan was "Radio Soc. Nacional de Minería," had a power of 5000 watts.—L.J.K.)

KZRH, Manilla, 9.64 mc, 31.12 m: This should not actually be in this category, although it will be new to some of those who have just taken up DX-ing. I am grateful to Leo Edel for bringing KZRM under my notice.

Announce: "Your station KZRH, The Voice of the Philippines." They are using the same frequency as pre-war. During the war the station was known as PIAM/N. Signal is best at 7 p.m., as later on it is badly interfered with by XGOY on same frequency. Reports are requested and should be sent to: Manila Broadcasting Co., Insular Life Building, Manilla. They could be relied upon before the war to verify correct reports with most attractive cards and often on Saturday nights would "call listeners."

NICO, Bikini, 9.14 mc, 32.82 m: Arthur Cushen reports hearing the station of the "Mt. McKinley," flagship of the Atomic expedition at 8 p.m. with a good signal.

NICO, Bikini, 5.625 mc, 53.33 m: Arthur Cushen also heard this other outlet of the "Mt. McKinley" on a Sunday at 6 p.m. with Church relay. Power is 300 watts.

NIGF, Bikini, 9.065 mc, 33.11 m: Mr. Cushen says this is the call of U.S.S. "Spindleye." Ask for reports to be sent to: NIGF, U.S.N.T. Spindleye, Navy 824

(Continued on page 41)

SHORT-WAVE STATIONS OF THE WORLD

Compiled by L. J. Keast - - August, 1946

All Times East Aust. Stand.

As the purpose of this list is more to provide, as far as possible, an accurate compilation of Shortwave Stations in frequency order and to enable the whole of the 20-25 metre band to be listed, schedules are not shown.

Call Sign	Mega-cycles	Metres	Location	Call Sign	Mega-cycles	Metres	Location
				CE1185	11.85	25.32	Santiago
					11.85	25.32	Rangoon
				JVU-2	11.845	25.33	Tokyo
					11.845	25.35	Paris
				VLC-7	11.84	25.35	Shepparton
				VLG-4	11.84	25.35	Melbourne
				OLR4A	11.84	25.35	Prague
				CXA-19	11.835	25.36	Montevideo
				CR7BF	11.835	25.36	L'enco Marques
				VUD-11	11.83	25.36	Delhi
				Radio Centre	11.83	25.36	Moscow
				VLW-3	11.83	25.36	Perth
				WCRC	11.83	25.36	New York
				WCRC	11.825	25.37	New York
				XEBR	11.822	25.38	Hermosillo
				GSN	11.82	25.38	London
				JVZ	11.815	25.39	Tokyo
				WGEA	11.81	25.40	Schenectady
				WLWL	11.81	25.40	Cincinnati
					11.805	25.41	Milan
				GWH	11.60	25.42	London
				JZJ	11.80	25.42	Tokyo
				VUD-3	11.79	25.45	Delhi
				KGEX	11.79	25.45	San Francisco
				KNBA	11.79	25.45	San Francisco
				WRUS	11.79	25.45	Boston
					11.78	25.47	Moscow
					11.78	25.47	Lahti
				HP5G	11.78	25.47	Panama
				OIX-3	11.78	25.47	Lahti
				Radio Saigon	11.78	25.47	Saigon
				KCBR	11.77	25.49	San Francisco
				KCBA	11.77	25.49	San Francisco
				VLA-4	11.77	25.49	Shepparton
				GVU	11.77	25.49	London
				SEAC	11.765	25.50	Colombo
					11.765	25.50	Algiers
				ZYB-8	11.765	25.50	Sao Paulo
					11.762	25.51	Berlin
				VLG-10	11.76	25.51	Melbourne
				VUD-7	11.76	25.51	Delhi
					11.75	25.53	Komsomolsk
				GSD	11.75	25.53	London
				CE1174	11.74	25.55	Santiago
				HVJ	11.74	25.55	Vatican City
				COCY	11.74	25.55	Havana
				CE1173	11.73	25.58	Santiago
				PCJ	11.73	25.58	Hilversum
				KGEX	11.73	25.58	San Francisco
					11.73	25.58	Paris
				WRUW	11.73	25.58	Boston
				WRUL	11.73	25.58	Boston
				KGEI	11.73	25.58	Sarn Francisco
				CHOL	11.72	25.59	Sackville
				PRL-8	11.72	25.59	Rio de Janeiro
				OTM-4	11.72	25.59	Leopoldville
				CKRX	11.72	25.59	Winnipeg
CE1227	12.275	24.45	Batavia				
KUSQ	12.27	24.45	Punta Arenas				
Radio Centre	12.265	24.47	Guam				
WXFG	12.26	24.47	Moscow				
TFJ	12.555	24.49	Adak				
	12.235	24.54	Reykjavik				
	12.23	24.58	Moscow				
	12.22	24.58	Changsha				
XLPA	12.21	24.59	Vienna				
Radio Wien	12.17	24.65	Moscow				
Radio Centre	12.165	24.67	Hanoi				
	12.126	24.74	Tananarive				
THA1	12.116	24.77	Algiers				
	12.115	24.77	Moscow				
ZNR	12.115	24.77	Aden				
H13X	12.11	24.77	Ciudad Trujillo				
GRF	12.095	24.80	London				
	12.08	24.80	Moscow				
PST	12.08	24.80	Rio de Janeiro				
	12.06	24.88	Moscow				
GRV	12.04	24.92	London				
CR-6R	12.024	24.95	Benguola				
CE1180	11.997	25.01	Santiago				
CSX	11.995	25.01	Lisbon				
Radio Brazza-ville	11.97	25.05	Brazzaville				
HEK-4	11.96	25.08	Bern				
GVY	11.955	25.09	London				
ZPA-5	11.95	25.09	Encarnacion				
GVX	11.93	25.15	London				
XGOY	11.918	25.17	Chungking				
	11.90	25.21	Saba				
	11.90	25.21	Phillipsburg				
	11.90	25.21	Moscow				
CE1190	11.90	25.21	Santiago				
OQ2AB	11.90	25.21	Elizabethville				
CKA10	11.90	25.21	Montevideo				
CKEX	11.90	25.21	Sackville				
JVU3	11.895	25.22	Tokyo				
WNBI	11.893	25.22	New York				
	11.89	25.23	Moscow				
	11.89	25.23	San Francisco				
KWIX	11.886	25.24	Paris				
VLH-4	11.88	25.25	Lyndhurst				
LRR	11.88	25.25	Rosario				
VLG-5	11.88	25.25	Melbourne				
	11.878	25.27	Moscow				
	11.87	25.27	Moscow				
VUD-9	11.87	25.27	Delhi				
WNBI	11.87	25.27	New York				
WOOW	11.87	25.27	New York				
VLC-3	11.87	25.27	Shepparton				
ZPA-3	11.865	25.28	Asuncion				
GSE	11.86	25.29	London				
	11.858	25.30	Singapore				



Sole Australian Concessionaires:

GEORGE BROWN & CO. PTY. LTD.
267 Clarence Street, Sydney

Victorian Distributors: J. H. MAGRATH PTY. LTD., 208 Little Lonsdale Street
Melbourne

The Ultimate factory has made the changeover from wartime production. Designs for the new models are now completed and production is about to commence.

These models should be available soon — they will be worth waiting for. Watch for further announcements.

SERVICE: Servicing of all kinds of radio sets, amplifiers and Rola speakers will continue to be available.

Call Sign	Mega-cycles	Metres	Location
HSP-5	11.715	25.60	U.S.S.R.
	11.71	25.60	Bangkok
	11.715	25.60	Dakar
VUD-3	11.71	25.62	Delhi
HEI-5	11.713	25.61	Bern
WLWS	11.71	25.62	Cincinnati
WLWK	11.71	25.62	Cincinnati
VLG-3	11.71	25.62	Melbourne
CBFY	11.705	25.63	Montreal
CKXA	11.705	25.63	Sackville
	11.705	25.63	Paris
SBP	11.705	25.63	Stockholm
JLG-3	11.705	25.63	Tokyo
GVW	11.70	25.64	London
XORA	11.69	25.65	Shanghai
	11.695	25.65	Singapore
HP5A	11.692	25.66	Panama
HVJ	11.688	25.68	Vatican City
GRG	11.68	25.68	London
	11.675	25.71	Moscow
XGTA	11.65	25.75	Shanghai
XTPA	11.65	25.75	Canton
Radio Centre			
	11.63	25.80	Moscow
	11.625	25.81	Berlin
	11.623	25.83	Havana
	11.535	26.00	Warsaw
	11.53	26.02	Douala
PZX-4	11.516	26.05	Paramaribo
	11.485	26.13	Tunis
	11.405	26.29	Dakar
HBO	11.402	26.31	Berne
PZR	11.332	26.47	Paramaribo
	11.315	26.51	Moscow
	11.26	26.64	Yaounde
KCBF	11.140	26.92	San Francisco
Emisora Nacional	11.09	27.05	Ponta Delgada
CSW-6	11.035	27.17	Lisbon
	11.00	27.27	Java
PDQ	10.99	27.32	Amsterdam
ZLT-4	10.98	27.32	Wellington
LSD-8	10.875	27.58	Buenos Aires
SDB-2	10.780	27.83	Stockholm
V07LO	10.73	27.96	Nairobi
ZIK-2	10.60	28.30	Belize
	10.54	28.45	Johannesburg
	10.445	28.72	Moscow
HED-4	10.405	28.83	Bern
HCHAC	10.312	29.09	Guayaquil
XRRA	10.25	29.25	Peiping
PSH	10.22	29.35	Rio de Janeiro
HH3W	10.135	29.62	Port-au-Prince
XBHX	10.12	29.63	Mexico
SUV	10.05	29.84	Cairo
WWV	10.00	30.00	Washington

WALKIE-TALKIE FOR FIRE BRIGADE

A peace-time use has recently been found for the portable or walkie-talkie radio transmitter-receivers recently used by the military authorities. During a big fire at West Ham, firemen carrying the walkie-talkie entered the burning warehouse and sent out orders to the pumps in the street, thus enabling hoses to be directed to the seat of the fire and otherwise assisting in overcoming the blaze quicker than under normal conditions. The fire commander afterwards announced the experiment to be a great success.

—Practical Wireless.

* * *

Do you recall how, in 1936, or thereabouts, the Jap commercial station JNB had a walloping harmonic at the L.F. end of "Ten"? That sig was often R9 for hours. Obviously, in the light of present day conditions engendered by 11 year sun-spot cycle considerations, there would have been easy QSO's with Ham stations in the island locations — if there had been any Hams up there in those times. I suppose one might say the same thing about the Moon — if Hams existed there, now that Radar echoes are being recorded!

NEW STATIONS

(Continued from page 39)

c/o Fleet Post Office, San Francisco.

NCLG, Bikini, 9.275 mc, 32.36 m: This is U.S.S. "Appalachian," which is also heard around 8 p.m. and reported by Arthur Cushman.

RADIO BADEN BADEN 6.33 mc, 47.39 m: This German station is reported by Arthur Cushman as coming in fairly well at 2.45 p.m. but mixed with COCW. Announcements are in German and French. Slogan is "Suedwestfunk."

(Baden Baden is listed in my latest advices from Washington as 6.315 mc, and COCW as 6.322 mc., so perhaps Arthur has made a typographical error. By the way, Baden Baden is listed as using 10,000 watts. — L.J.K.)

NCLG, Bikini, 10.64 mc, 28.19 m: Mr. Leo Edel reports hearing this station on the announced frequency of 10.64 mc, at 12.30 a.m. when Correspondents were talking about Atomic tests. Mr. Edel says they announced they were also on 11.24 mc.

RADIO AUSTRALIA

Overseas Shortwave Service of Department of Information

Several alterations took effect in July, so I have compiled a list of latest schedules.

7.15—9.00 am: VLA-6 Shepparton 15.2 mc, 19.74 m: Forces programme to Pacific, Japan and Asia.
 9.00—9.30 am: VLA-6 Shepparton 15.2 mc, 19.74 m: To Asia in Japanese.
 10.30—11.45 am: VLC-9 Shepparton 17.84 mc, 16.82m: To North America (East) and Canada.
 Noon—2.00 pm: VLG-6 Lyndhurst 15.23 mc, 19.69 m: Forces programme to Pacific, Japan and Asia.
 VLC-4 Shepparton 15.32 mc, 19.59 m:
 1.15—5.30 pm: VLA-6 Shepparton 15.2 mc, 19.74 m: Saturdays only.
 3.00—3.45 pm: VLG-4 Lyndhurst 11.84 mc, 25.35 m: To North America (West).
 VLC-4 Shepparton 15.32 mc, 19.59 m:
 4.00—4.45 pm: VLG-3 Lyndhurst 11.71 mc, 25.62 m: To Tahiti in French.
 VLC-4 Shepparton 15.32 mc, 19.59 m:
 5.00—6.15 pm: VLC-11 Shepparton 15.21 mc, 19.22 m: To British Isles. Except Sunday.
 5.00—6.15 pm: VLA-4 Shepparton 11.77mc, 25.49 m:
 5.30—6.10 pm: VLG-10 Lyndhurst 11.76 mc, 25.51 m: To Northern Asia in Japanese.
 6.15—6.53 pm: VLG-10 Lyndhurst 11.76 mc, 25.51 m: To New Caledonia in French.
 6.29—7.00 pm: VLG-6 Shepparton 9.615 mc, 31.2 m: Saturdays only. To Forces in Pacific, Japan and Asia.
 6.34—7.00 pm: VLC-6 Shepparton 9.615 mc, 31.2 m: Sundays.
 6.35—10.00 am: VLA-4 Shepparton 11.77 mc, 25.49 m: Forces programme to Pacific, Japan and Asia.
 6.58—8.00 pm: VLC-6 Shepparton 9.615 mc, 31.2 m: To Forces

in Pacific, Japan and Asia.
 VLG-5 Lyndhurst 11.88 mc, 25.25 m:
 8.00—10.00 pm: VLG-5 Lyndhurst 11.88 mc, 25.25 m: To Asia in Chinese, Japanese, English, Dutch and Malay.
 8.00—9.50 pm: VLC-6 Shepparton 9.615 mc, 31.2 m: To Asia, in Chinese, Japanese, English, Dutch and Malay.
 10.00—11.00 pm: VLG-5 Lyndhurst 11.88 mc, 25.25 m: To Asia and Forces.
 VLA-4 Shepparton 11.77 mc, 25.49 m:
 10.00—11.15 pm: VLC-5 Shepparton 9.54 mc, 31.45 m: To North America (East) and Canada.
 11.00—11.35 pm: VLG-5 Lyndhurst 11.88 mc, 25.25 m: To Indo-China in French.
 VLA-4 Shepparton 11.77 mc, 25.49 m:
 11.35—Midnight: VLG-5 Lyndhurst 11.88 mc, 25.25 m: To Siam in Siamese.
 VLA-4 Shepparton 11.77 mc, 25.49 m:
 VLC-6 Shepparton 9.615 mc, 31.2m:
 Midnight—12.29 am: VLA-4 Shepparton 11.77 mc, 25.49 m: To Pacific and India.
 Midnight—12.50 am: VLC-6 Shepparton 9.615 mc, 31.2 m:
 12.15—1.00 am: VLG Lyndhurst 9.58 mc, 31.32 m:
 1.00—2.00 am: VLA-3 Shepparton 9.69 mc, 30.99 m: To British Isles.
 1.00—1.45 am: VLC-6 Shepparton 9.615 mc, 31.2 m:
 1.00—1.45 am: VLG Lyndhurst 9.58 mc, 31.32 m:
 2.00—3.00 am: VLG Lyndhurst 9.58 mc, 31.32 m: To North America (West).
 VLC-6 Shepparton 9.615 mc, 31.2 m:
Lyndhurst Transmitter VLG (10 KW).
Shepparton Transmitter VLC (50 KW).
Shepparton Transmitter VLA (100 KW).

Speedy Query Service

(Conducted under the personal supervision of A. G. Hull)

R.D. (Parkes) enquires about a subscription to "Q.S.T."

A.—Yes, the technical magazine, "Q.S.T." is still in publication by the American Radio Relay League. Quickest way of arranging a subscription is to contact the Technical Book and Magazine Co. of 297 Swanston Street, Melbourne. You can send them £1 in Australian money and they will arrange to have "Q.S.T." posted regularly for 12 issues.

* * *

S.D. (Petersham) wants us to settle an argument.

A.—Whilst there is no actual reason why a high-fidelity modulator could not be used with a ham transmitter, it is generally considered a much better scheme to use one with greatly curtailed high and low note response. This allows a higher percentage of modulation on average speech without over-modulation on certain sounds, and also makes it much easier to avoid troubles with feedback, hum and so on. A comparatively narrow band of frequencies is all that is necessary to give comprehensible speech, and the ordinary voice does not use either extremely low or high notes.

HEADPHONES

Brand New! Just Released!

S.T.C. & STROMBERG CARLSON

Original cost, £2/10/- pr.

130 Ohms, 10/- pair

2,000 Ohms, 25/- pair

(Postage 1/6 pr. extra)

Can supply in quantity.

**DEITCH BROS.
210A GEORGE STREET
SYDNEY**

R.D. (Perth) is in trouble with a superhet using a 6K8 converter with ordinary oscillator coil kit designed for use with a 6J8.

A.—Normally the 6K8 will work well with ordinary commercial coils, but your only certain check is to whether the 6K8 is operating correctly or not is to measure the actual grid current. This can be done by fitting an 0 to 1 milliammeter in series at the cathode end of the 50,000 ohm oscillator grid leak. Unsolder it for this purpose. With the set operating and the meter in circuit the grid current should be between 100 and 200 microamps. The current will vary according to dial setting, but should not go outside these limits.

* * *

B.D. (Belmore) wants to know what resistance to use as shunt for an 0 to 1 milliammeter, which he is going to build up as a multi-meter.

A.—The shunt to use will depend entirely on the internal resistance of the meter itself, which can be found out by enquiry from the makers. The University meter S4-46A has its resistance marked at the bottom of the dial, and is 100 ohms.

To find the value of the shunt in ohms, divide the internal resistance of the meter by the full scale reading required, less 1. For example, for a full scale of 10 milliamps with a 100 ohm meter, you divide 100 by 10 less 1, which is 9, and gives you a required resistance of 11.111 ohms. For 50 milliamp scale the shunt will be 2.04 ohms and for 250 milliamps will be .4 of an ohm. If, however, the meter has an internal resistance of 50 ohms, the shunts will work out at 5.555 ohms for 10 ma., 1.02 ohms for 50 ma. and .2 of an ohm for 250 milliamps.

* * *


R. T. (Bendigo) asks about the next "ham" exam.

A.—Examinations for the amateur operator's certificate of proficiency are to be held on the second Tuesday in October.

NEW "VALVE" IS CRYSTAL

After a lapse of nearly twenty years the commonplace catswhisker crystal detector once again figures as an important item in an otherwise essentially modern radio receiver. As R.F. amplification is virtually unobtainable on the extremely short wavelength of 3 cm the successful operation of the equipment depends largely on the efficiency and reliability of these new crystal detectors.

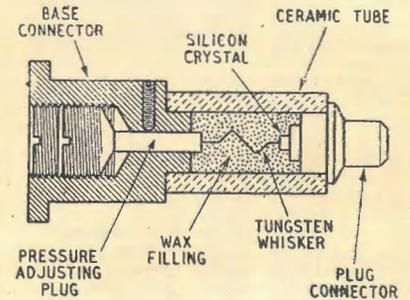Although generally known as a crystal valve, it is basically a silicon-tungsten detector, but externally bears no resemblance whatsoever to




its early prototypes. As the sectional drawing in Fig. 1 shows the crystal and tungsten catswhisker are contained in a small ceramic tube closed at each end by brass plugs and completely filled with wax. This form of construction results in a mechanically robust device in which the contact is quite undisturbed by normal shocks.

When used as a superheterodyne mixer careful control of the local oscillations is needed, and the best guide is a measurement of the rectified current passing through the crystal. This should be between 0.5 and 1 mA for average crystals.

Physically these crystal capsules are quite small, the overall size being just under 1-in. long and ¼-in. in diameter.

—Wireless World (Eng.)

IT'S HERE

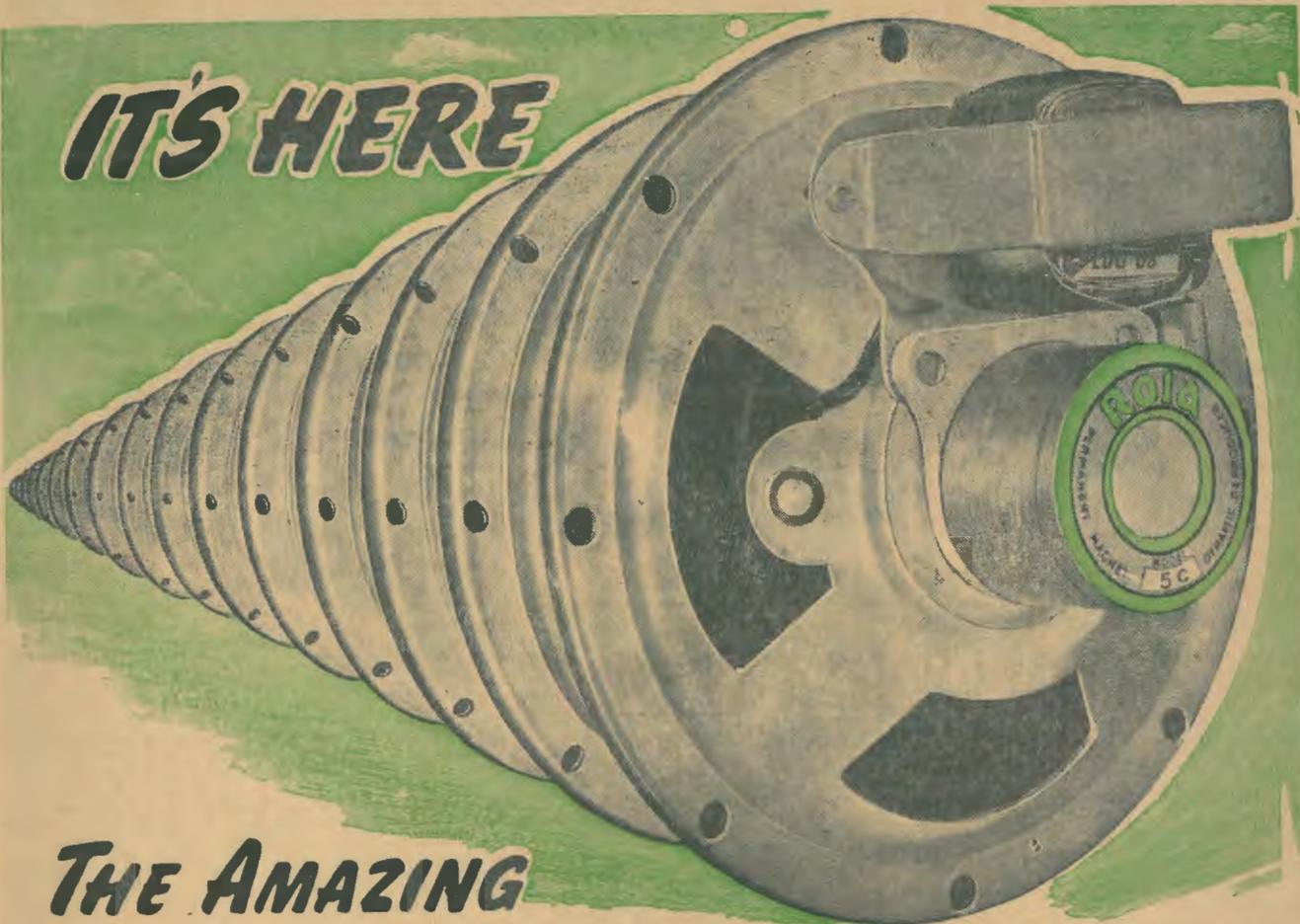

THE AMAZING

ROLA 5C SPEAKER with ANISOTROPIC ALNICO

Using Anisotropic Alnico to achieve the maximum efficiency to weight ratio, Rola 5C is the most modern of all five inch speakers. Ideally suited for use in a.c. and a.c. d.c. receivers, it also finds useful application in vibrator and battery operated receivers.

It occupies the barest minimum of space, weighs

only 12 ozs., and is thoroughly robust in construction and reliable in operation. Because of its eminent suitability in midget receivers, Rola 5C is unquestionably the most sought after speaker today. Retail price with K5 type transformer attached or detached26/6

(With small isocore transformer detached .. 29/-)

ROLA LOUD SPEAKERS with ANISOTROPIC ALNICO

AUSTRALIA WILL NEED THOUSANDS MORE COMPETENT RADIO SERVICEMEN!

With a prewar turnover of £8,000,000, the number of male personnel alone engaged in the Radio receiver field runs into thousands and the need for more grows each week.



Train quickly for a profitable career in RADIO ... or a prosperous business of your own!

One of the most attractive features of Radio in Australia is the scope offered to start your own business. With a total of 1,481,919 licensed radio receivers (remember civilian production ceased during the war), some idea can be gained of the pressing need for more and more trained servicemen. . . . Such servicemen make big money, too, in selling valves, components (of which over £1,000,000 annually were sold before the war) as well as associate electrical appliances.

We are entering now a Radio age, an Age which has a place for YOU. Radio, a young industry which has made remarkable progress in the past few years, will want trained men urgently to fill vital positions. If you want security, prosperity, and a recognised status in the community, start training NOW.

TRAIN AT HOME, OR AT OUR BENCHES

A.R.C. offers ambitious men a sound proven course in Radio Engineering. Sound because it is the result of many years' successful operation, proven because hundreds of ex-students owe their present success to the College. You can learn with equal facility at home

(by means of our correspondence course).

EARN GOOD MONEY WHILST LEARNING

You don't have to wait a year, or even six months, before you are ready to begin "cashing in." We will show you how to earn extra money almost from the word "go." Many students make £4, and up to £8, per week in their spare time whilst studying.

PREVIOUS KNOWLEDGE UNNECESSARY

You don't need a knowledge of Radio or Electricity—we'll give you all you need of both, in a simple, practical manner, that makes learning easy, presented too, in such a way that you remember what you're taught and how to put that knowledge to practical use.

COSTS LITTLE

Think of his—for a few pence per day—actually less than many fellows spend on tobacco—you can prepare yourself for a man-sized job in Radio NOW.

NOW IS THE TIME TO ACT!

Send in today for the free book, "Careers in Radio and Television." It's a book no man can afford to miss. It shows you the steps you can take to get into Radio immediately!

RADIO IS STILL A NEW INDUSTRY GROWING FAST!



£8,000,000 was estimated prewar sales of radio receivers and parts. The next few years should see these figures doubled.

Pre-war Radio Set output reached an estimated 280,000. All records are expected to be broken in near future.

Even a 25 per cent. increase in set sales will mean openings for perhaps 1,000 more Radio dealers—Over 130 Australian Radio Stations employ a vast number of skilled personnel—a team of specialists which would probably be tripled with the advent of F.M. transmission.

GET TRIS BIG FREE BOOK NOW!

AUSTRALIAN RADIO COLLEGE PTY. LTD.

Cnr. Broadway and City Roads, Sydney.

Phones: M 6391, M 6392



10/462

To Mr. L. B. GRAHAM, Principal,
Australian Radio College, Pty. Ltd.,
Broadway, Sydney. Phone M 6391-2.

Dear Sir—I am interested in Radio. Please send me, without obligation on my part, the free book, "Careers in Radio and Television."

NAME

ADDRESS

