

COMMUNICATIONS WITH INTERPLANETARY SPACECRAFT

electronics today

JULY 1978

INTERNATIONAL

\$1.25

BONUS
OP-AMPS
SUPPLEMENT
12 PAGES



ROBOTS TOYS FOR KIDS OR
TOOLS FOR SOCIETY

EPROM Programmer

Electronic Tacho

8080 Educational Interface

The competition don't like the sound of this at all.

For quite some time, other manufacturers have been trying to produce tape with the qualities of the Maxell UD-XL. At the same time, Maxell have been quietly perfecting an even better series.

The UD-XL I and UD-XL II tapes are designed to attain maximum performance at the ferric and chrome position on your tape deck. Whichever tape position you choose, Maxell can give you a better performance.

UD-XL I TAPE, FOR FERRIC (norm.) POSITION (120us)

UD-XL I offers an excellent sensitivity of 1 dB higher than even UD-XL. MOL performance is also 1 dB higher over the entire audio frequency spectrum. The result is a new standard in ferric tape, with wider dynamic range and less distortion than ever before.

How does the UD-XL I compare then, with ordinary low-noise tapes?

Sensitivity is higher by 2.5 dB, and MOL performance by as much as 6 dB.

Yet, for all this UD-XL I requires no special bias or equalization. Simply set your tape selector as you normally would at the ferric position – but there the comparison ends.

UD-XL II TAPE, FOR THE CHROME POSITION (70us)

UD-XL II tape is such a dramatic improvement on most other tape that can be used in this position, that comparison is really unfair.

For example, if you're familiar with conventional chromium-dioxide tape, you'll know of the associated problems of head wear, poor output uniformity and relatively high price – plus low maximum output level and rather high distortion.

UD-XL II tape offers you excellent MOL, sensitivity, and an output improvement of more than 2 dB over the entire frequency range.

Maxell's unique 'Epitaxial' process gives you absolute sensitivity and stability, and no drop-out problems. What's more, the shells are moulded in diamond cut dies, and made to tolerances 5 times greater than the Philips standard. And, like all Maxell tapes, UD-XL II has the unique 5-second cleaning leader.

In short, if you're recording in the chrome position, you can now achieve all the advantages – with none of the drawbacks.

A prospect we think you'll find very exciting – even if the competition don't.



maxell[®]
simply excellent

For details on all Maxell Recording Tape write to Maxell Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033

WT3/79

electronics today

INTERNATIONAL

Editorial: Les Bell

Publisher: Collyn Rivers



Cover: Are robots merely toys for kids, or are they really evolving into useful tools for society. Two major articles this month examine this question, while next month we ask: is it feasible to build your own robot? Photograph by John Knight.



A Modern Magazines Publication
* Recommended retail price only.

Registered for posting as a publication —
Category B

PROJECTS

318: Digital Car Tacho	50
<i>Uses PLL multiplier for quick response.</i>	
591: Up/Down Presettable Counter	56
<i>Just count the uses.</i>	
638: EPROM Programmer	85
<i>Low cost design is simple to build.</i>	
248: 12V to 22V Converter	94
<i>Lets you run gadgets from a 12V battery.</i>	
634: 8080 Educational Interface	105
<i>For interfacing and programming experiments.</i>	

FEATURES

Sound	13
<i>New tone arm, speakers.</i>	
Deep Space Tracking	26
<i>Communications with interplanetary craft.</i>	
Robots - The Facts	34
<i>How close are we to ultimate automation?</i>	
Robots - Brain Power	41
<i>How smart can a machine be?</i>	
Digital Electronics by Experiment	46
<i>Part five covers flip flops.</i>	
Special Offer: Tacho Kit	53
<i>All the parts for our tacho project, at a special price.</i>	
Special Supplement: Op-Amps	61
<i>28 useful circuits using op-amps.</i>	
Print Out	99
<i>News from the microworld.</i>	
Special Offer: Microwave Burglar Alarm	102
<i>Superb unit at special price.</i>	
Propagation - A Close Look	112
<i>How to make sense of those prediction charts.</i>	

NEWS & INFORMATION

News Digest	4	Amateur News	125
Sound Briefs	24	CB News	126
Mini Mart	117	Propagation Predictions	128
Printed Circuit Board		Ideas for Experimenters	131
Drawings	118	Index to Advertisers	138
SWL News	120	Reader Services	138

News Digest

Salt of the Earth?

XIT Rod Co. of Covina, California, has developed a grounding rod which grows electrolytic 'roots' to decrease the rod-to-earth resistance dramatically. The hollow tubular body condenses moisture from the air which trickles through a bed of coarse granulated metallic salt, dissolving a small quantity of it to form an electrolytic solution. This solution seeps through the bottom of the rod, thus growing 'roots' and dropping the earth resistance to a fraction of the value otherwise obtainable.

Ultrathin Radio

A new ultrathin AM/FM radio which incorporates a quartz clock and alarm will be on display at the National exhibit, Stand 57 in the Commemorative Pavilion, at the forthcoming Consumer Electronics Show to be held at the Sydney Showground, July 13-17.

Although this new unit, designated Model RF 016, is only 17.3 mm (less than $\frac{3}{4}$ "") thick and weighs a mere 180 g (6.4 ozs) with batteries, it contains a remarkable concentration of features.

These include a high-performance FM/AM radio receiver, an extremely accurate quartz clock with liquid crystal digital display, a light for night-time use, and a two-way alarm which either chirps or turns the radio on at a pre-selected time. This has been achieved by National's advanced technology in the miniaturisation of such components as speakers, capacitors and intermediate frequency transformers to achieve compactness and light weight without loss of performance or reliability.

Recommended Retail Price is \$125.00.



New Taxi System

The Minister for Transport, the Hon. Mr. Peter Cox, has commissioned a new taxi status, identification and alarm system for Taxis Combined Services Pty Ltd., in Sydney.

The Managing Director of Taxis Combined Services, Mr. R. L. Kermode, said more than 1200 taxis would be connected to the system. The fleet is one of the world's largest fleets of radio-controlled taxis.

The new Status and Identification System, designed by Philips-TMC Radio Division in Melbourne, is the first in its field in Australia and is capable of identifying up to 10,000 mobiles. Digital techniques combined with digital transmission are used to provide high speed data communication.

The system, in addition to speeding communication between the base and the taxi fleet, will provide facilities which should result in a reduction in the number of attacks on taxi drivers. A high standard of accuracy is achieved by using rapid data transmission methods, which ensure minimum possibility of human or transcription errors.

Mr. Kermode travelled extensively overseas in 1976 looking at transport systems and communications systems before deciding on the Australia-designed Philips equipment.

"The uniqueness of the system lies in the fact that it places control in the hands of the base operator," Mr. Kermode said. "Control is essential when dealing with the fleet of more than 1200 cabs which make up Taxis Combined Services and which operates on an 8 channel radio network in peak hours.

"When the base operator sends out a call, those drivers wishing to 'bid' for the job simply press a button on a small, dash-mounted console. The first driver to register his 'bid' on the operator's console gets the job. The base operator then informs the first driver that he has the job and gives him all the relevant information of address, person's name and any other details.

"Once the driver has the message he just presses a 'roger' button to let his base know he is on his way. If he did not understand some part of the information, he presses another button marked 'repeat' and the operator repeats all the information. On the other hand, if the driver wishes to speak to the operator, perhaps to tell him that the street number he was given does not exist, he presses another button marked 'query' and the base operator then allows him to use his normal microphone for a brief period.

"This system has real advantages. Instead of using valuable air-time to 'bid' verbally for a call, with possibly several drivers calling at the same time, and even causing a 'lock-out' situation, the driver is able to press a button that will send out a very short signal (milliseconds) but still register his 'bid'. This means that the radio channel is free to accept many more calls from many more taxis. The fast response time is invaluable during peak traffic conditions and its importance in emergency situations cannot be overstressed."

The system also has a built-in alarm system that could help to reduce the number of attacks on taxi drivers and lead to the capture and conviction of more attackers.

If a driver fears he may be attacked, he activates a hidden switch which automatically turns on the taxi transmitter and sends a special 'alarm' signal. This registers on the base operator's console.

At the base station, the operator knows immediately which driver is in trouble because his taxi number is flashed up on a separate display. The operator then presses a button which allows him to tell all other taxis on the frequency to keep off the air because of the emergency.

From this point, a series of events takes place that will help the operator to locate the driver and indicate the sort of trouble he is in. But, to spell out those events would only alert any would-be attacker and defeat the security aspects of the system.

What Philips will say, however, is that the system does work, it does have the support of the taxi industry, and with quick action by the base operator and police, more taxi driver attackers will be caught — and would-be attackers will be deterred.

Laser Scalpel

A new scalpel with a transparent blade, developed at the University of Washington, uses light from an argon laser to cauterise blood vessels. The light is 'piped' to the scalpel through a fibre optic guide and emerges from the cutting edge of the blade, which is made from quartz or sapphire. As the scalpel cuts, pressure from the blade forces the blood vessels closed, and the light cauterises them.

Several advantages are claimed over the conventional electro-surgical scalpel, which cauterises with an intense RF field, including less blood loss, less damage to adjacent tissue and the absence of a ground electrode, which can cause burns.

High Accuracy DMM

Dick Smith is now stocking the Seif Digital Multitester, "an instrument which offers an unusually high degree of accuracy considering it sells for only \$145", says Dick.

"We compared the Seif with five similar units selling for up to \$205, and none of them could match the 0.1% accuracy yet at the same time offer 100 μ V resolution, the number of ranges and the big (11 mm height) LED readouts. The closest any of them came to the Seif's DC accuracy figure was 0.25%."

Specifications of the Seif Digital Multitester are as follows:

DC Volt Ranges:	200mV, 2V, 20V, 200V and 1000V
AC Volt Ranges:	100mV, 2V, 20V, 200V and 700V
DC Current:	200 μ A, 2mA, 20mA, 200mA, 2A
AC Current:	200 μ A, 2mA, 20mA, 200mA, 2A
Resistance:	2K, 20K, 200K, 2M, 20M Ohms
Readouts:	11 mm high LED
DC Accuracy:	$\pm 0.1\% \pm 0.2\%$ RDG. ± 1 digit
Resolution:	100 μ V

Price: \$145.00 Catalogue No:

Q-1440. Available at all Dick Smith Electronics stores.


Reversing Buzzer

An instant audible warning device to tell pedestrians, especially children, of a vehicle reversing is being marketed by Swann Electronics.

A valuable safety aid for cars, trucks, vans and buses, the buzzer can be operated also from a switch mounted on the dashboard.

Obtainable from the Swann merchandiser at automotive accessory outlets, the warning buzzer costs \$6.21 plus tax.

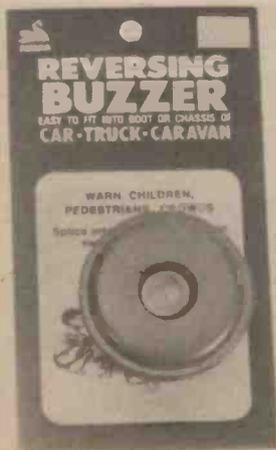Also available is a dashboard warning buzzer which can monitor oil pressure or water temperature, and a hazard warning light flasher.



Asynchronous Communications Element

A new Asynchronous Communications Element from National Semiconductor Corporation is claimed to incorporate many software-programmable and hardware control features that reduce system complexity and microprocessor overhead during serial data transfers. In addition to being a UART to perform serial-to-parallel and parallel-to-serial conversions, the INS8250 provides programmable baud-rate generation, programmable serial-message formatting, status reporting, and complete modem control.

The device contains a programmable baud-rate generator that accepts any clock input from dc to 3.1 megahertz, dividing it to select baud rates from 50 to 56,000. Divisors, loaded during initialization, are stored in two 8-bit latches using a 16-bit binary format. The device has double buffers on both the transmit and receive sections to compensate for any asynchronous anomalies.

The microprocessor specifies asynchronous data format through the INS8250 line-control register. Characters may have 5, 6, 7, or 8 bits; even, odd or no-parity bits and, either 1, 1½ or 2 stop bits. The unit deletes start/stop and parity bits from the serial data stream prior to converting to parallel for the system data bus. It also adds standard asynchronous communication bits to output serial data stream. Contents of the line control register can be retrieved for inspection, eliminating the need for separate storage in system memory.

Status registers inform the CPU of line and modem conditions at any time. Data ready, transmitter register conditions, as well as overrun, parity and framing error are signalled by the line status register. The modem status register indicates various clear, set, ready and other conventional data signals from the modem.

The INS8250 has on-chip interrupt capability that permits complete flexibility in interfacing to all popular microprocessors. To reduce software overhead during data character transfers, the device prioritizes interrupts from receiver line status, receive data ready, transmitter holding-register empty, and modem status.

In 100-unit quantities, the INS8250 is priced at \$8.10 each. Delivery is from stock.

16K from Rifa

Rifa recently announced details of the 16,384 bit MOS RAM manufactured by Fujitsu, one of the largest IC manufacturers in Japan. The Fujitsu MB 8116 is a full decoded, dynamic NMOs random access memory organized as 16,384 one-bit words. The design is optimized for high-speed, high performance applications such as mainframe memory, buffer memory, peripheral storage and environments where low power dissipation and compact layout is required.

Multiplexed row and column address inputs permit the MB8116 to be housed in a standard 16 pin DIP. Put-outs conform to the accepted industry standard.

Clock timing requirements are non-critical, and power supply tolerances are 10%. All inputs are TTL compatible; the output is three-state TTL.


For further information contact: Rifa Pty. Ltd., 202 Bell Street, Preston, Vic. or 23 Sloane Street, Marrickville, N.S.W.

New Heatsinks

A range of compact finger type and fan top heat sinks designed for use in computers, audio amplifiers, power supplies and calculators are available from Melbourne based company, Swann Electronics Pty. Ltd., of P.O. Box 350, Mt. Waverley, Vic. 3149.

fact: you can choose your microphone to enhance your individuality.

Shure makes microphones for every imaginable use. Like musical instruments, each different type of Shure microphone has a distinctive "sound," or physical characteristic that optimizes it for particular applications, voices, or effects. Take, for example, the Shure SM58 and SM59 microphones:

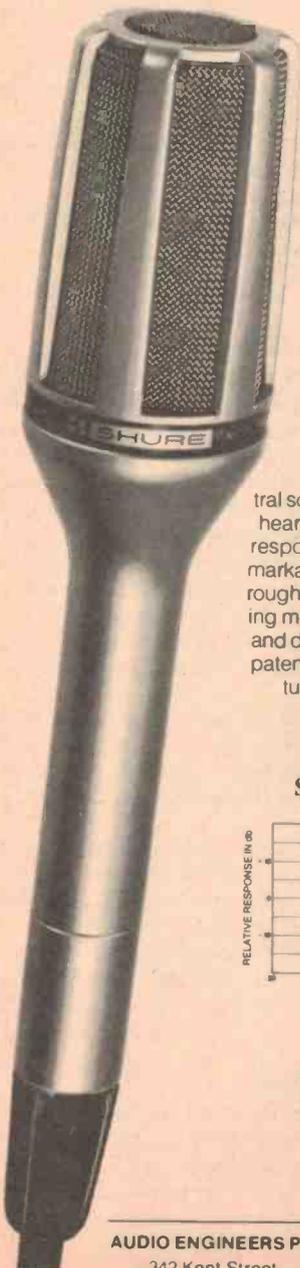


SM59

**Mellow, smooth,
silent...**

The SM59 is a relatively new, dynamic cardioid microphone. Yet it is already widely accepted as a standard for distinguished studio productions. In fact, you'll often see it on TV... especially on musical shows where perfection of sound quality is a major consideration. This revolutionary cardioid microphone has an exceptionally flat frequency response and neutral sound that reproduces exactly what it hears. It's designed to give good bass response when miking at a distance. Remarkably rugged — it's built to shrug off rough handling. And, it is superb in rejecting mechanical stand noise such as floor and desk vibrations because of a unique, patented built-in shock mount. It also features a special hum-bucking coil for superior noise reduction!

Some like it essentially flat...

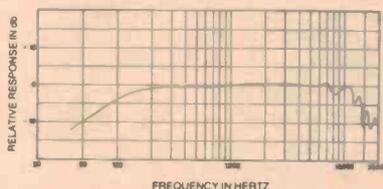


SM58

**Crisp, bright
"abuse proof"**

Probably the most widely used on-stage, hand-held cardioid dynamic microphone. The SM58 dynamic microphone is preferred for its punch in live vocal applications... especially where close-up miking is important. It is THE world-standard professional stage microphone with the distinctive Shure upper mid-range presence peak for an intelligible, lively sound. World-renowned for its ability to withstand the kind of abuse that would destroy many other microphones. Designed to minimize the boominess you'd expect from close miking. Rugged, efficient spherical windscreen eliminates pops. Lightweight (15 ounces!) hand-sized. The first choice among rock, pop, R & B, country, gospel, and jazz vocalists.

...some like a "presence" peak.

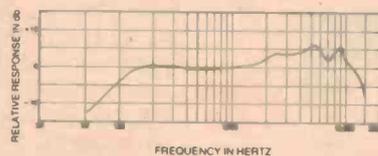

professional microphones...by



AE130/FP

AUDIO ENGINEERS P/L
342 Kent Street.
SYDNEY 2000 N S W


AUDIO ENGINEERS (Vic.)
2A Hill Street.
THORN BURY 3071 Vic

AUDIO ENGINEERS (Qld.)
51A Castlemaine Street.
MILTON 4064 Qld

ATHOL M. HILL P/L
33 Wittenoom Street.
EAST PERTH 6000 W.A.

HP Lab Supply

Intended for engineers who design and test breadboards and prototypes, a new low-cost, dual-output bench power supply from Hewlett-Packard offers two independently adjustable and isolated power sources in one compact unit. Both of the dc power sources are of the constant voltage/current limit type with each output voltage being adjustable continuously over a 0 to 25V range. The maximum current available per output is 0.2A and is limited automatically to prevent overloading.

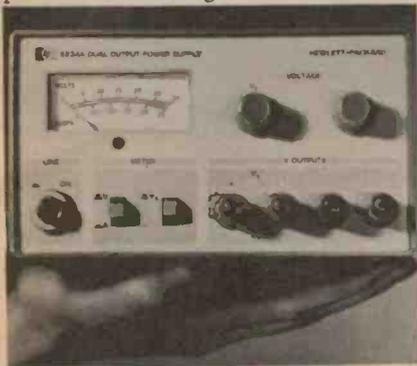


The HP 6234A offers considerable flexibility to the user with output voltages that can be arranged to provide identical or different voltages in any polarity combination with respect to 0 or other common positive or negative voltage points. The outputs can also be connected in series to provide up to 50V at 0.2A. Both sources are fully isolated to permit either of the output terminals to be grounded.

With dimensions of only 90 mm high, 155 mm wide and 190 mm deep (3 5/8" x 6 1/8" x 7 1/2"), the HP 6234A supply takes up a minimum amount of bench space. Its weight is 2.3 kg (5 lbs.). The unit can be powered from a 115V or an optional 230V, 47-63Hz ac input.

The Hewlett-Packard Model 6234A dual-output power supply is priced at \$185.00. Deliveries are eight weeks from date of order. For further information contact Hewlett-Packard Australia Pty Ltd, 31-41 Joseph St. Blackburn, Vic. 3130.

EMR-clean Room

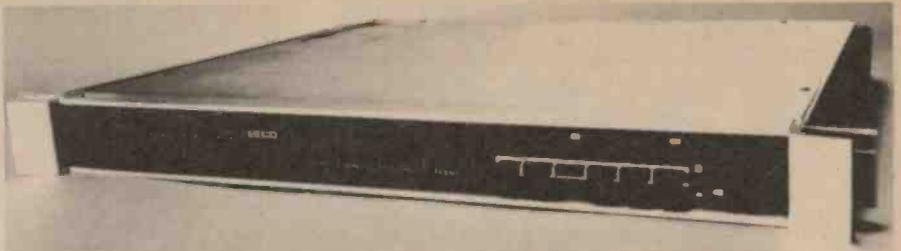A theory that electromagnetic radiation may in some way affect the health and recovery of patients is being tested at the General Hospital of Vienna, Austria, where Siemens have built 12 shielded rooms. The spectrum from 1 Hz to 10 GHz is blocked by steel walls and windows covered by honeycomb shields. Over 30 lines permit connection to instrumentation outside, allowing measurements down to 1 μ V.



Edit Code Generator

Ampex Australia Pty. Ltd. has announced the introduction of the EECO MTG 550 Series master time code generator which generates standard SMPTE/EBU Edit Code formats used for electronic indexing of video and audio tapes.

The generator incorporates the LSI time code generator chip which contains all the basic logic necessary for pre-setting the display time; inserting user bits, locking to video or other reference sources; external selection of 25 or 30 frames-per-second frame rates; and selection of drop or non-drop frame code.

Standard features of the MTG 550 include the ability to slave the generator to an external source of serial time code for add-on recording and the ability to derive proper reference sync from NTSC, PAL and SECAM video standards with an option to generate 24-frame code for the film industry. Encoding the auxiliary binary word from four different sources allows the user to insert 32 bits of information into the serial Edit Code output for additional scene identification.

Special status/alarm signals alert the user to loss of time code, loss of video/sync as a reference, loss of phase lock and of momentary power loss. Hexadecimal display is employed to allow selection of either Binary Word or Edit Code for display.

Further information is available from Ampex Australia Pty Ltd, 4 Carlotta Street, Artarmon, N.S.W. 2064, who are the distributors of EECO products in Australia.

Metal Glaze Resistors

Soanar Electronics Pty. Ltd. now include 1/4, 1/2 and 1 Watt Metal Glaze resistors in their comprehensive range of resistors and resistive components. Designated GLP and GL1, these thick Metal Glaze Resistors are Australian made and designed to provide the trade with economically priced 5% resistors of unusually small size.

The GLP resistor in particular, is dual rated for 1/4 or 1/2 Watt operation and exceeds the requirements of British Standards Specifications BSE 9111-N002 (Style FX) even at the 1/2 Watt (70°C ambient) rating. It measures a

mere 5.5 mm x 2 mm in size and occupies less board space than most 1/4 Watt carbon types.

GLP and GL1 Metal Glaze Resistors are available at Soanar Branches and Agents throughout Australia, and may be purchased as individual or bandoliered units. The resistance range covers 2.2 ohms to 1 Meg ohm.

Further information may be obtained from: Soanar Electronics Pty. Ltd., 30 Lexton Road, Box Hill, Vic. 3128.


New Design Duracells


The release in Australia of a completely new design of the well known Duracell long life alkaline dry battery has been announced by the manufacturers and distributors, Mallory Batteries (Australia) Pty. Ltd., of North Ryde, New South Wales.

Known as the 'FLAT-PAK', the alkaline battery is of the flat cartridge type and is presently available in several sizes and voltages, including the type 7K67, a 6-volt cartridge as used in Kodak instant picture cameras, and the type 5K65, a 9-volt being used in some models of calculators.

The new design of cartridge battery has been developed to assist designers of battery operated products to improve appearance and performance of their products, as well as simplify design and reduce assembly costs.

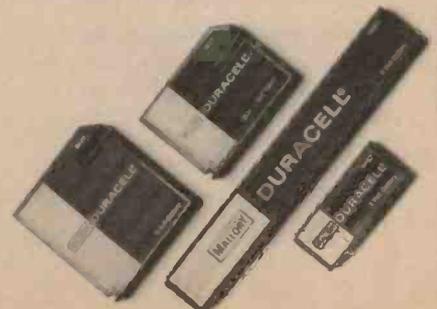The consumer also enjoys benefits with the use of the 'FLAT-PAK' because (a) the design makes it virtually impossible to insert a battery incorrectly, (b) the internal welding of intercell connections ensure positive contacts, and (c) the ultrasonically sealed plastic battery casing reduces risks of possible equipment damage from leakage or corrosion.



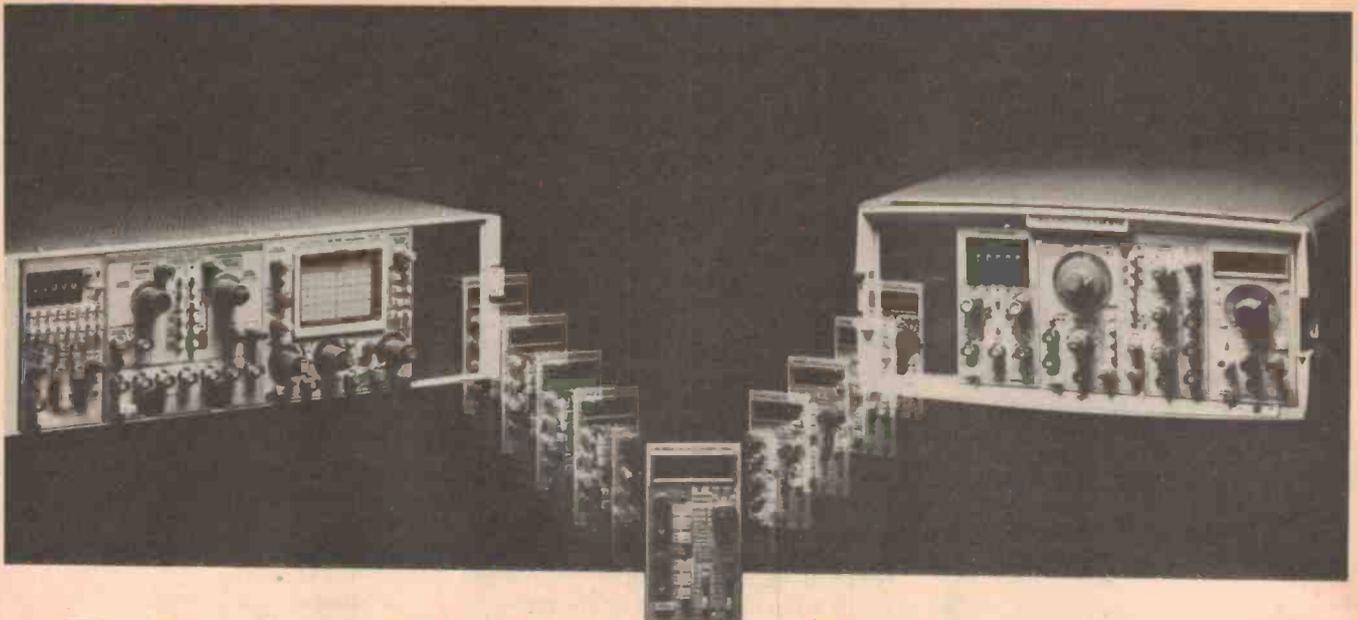

Stock Exchange.

If you want the highest return for your instrument dollar, take a look at the unmatched value of an electrically configurable TM500 test and measurement system from Tektronix.

Not only do you get Tektronix bluechip performance and reliability, but also the convenience and versatility of a plug-in instrumentation, at a very reasonable cost.

If your applications are diversified, TM500 gives you the power to configure literally thousands of plug-in combinations, all mechanically compatible in your choice of TM500 mainframes.

There are nearly 40 different plug-ins to choose from, in eight major categories:


DMMs	Oscilloscopes
Counters	Logic Analyzer
Generators	Word Recognizers
Amplifiers	Power Supplies

A single mainframe accommodates up to six plug-ins. Switching your system around from one application to another is just a matter of a simple stock exchange. Slip one plug-in out, slide another one in.

If your applications are growing, a TM500 system is a wise investment. You can update your system or add on new performance capabilities to your initial TM500 system without buying another mainframe. Since all plug-ins are powered through the mainframe, you won't be paying for an unnecessary power supply component with every new instrument you buy.

TM500 go-anywhere mainframes come in six different versions for benchtop, rackmount, rollcart or on-the-road engineering.

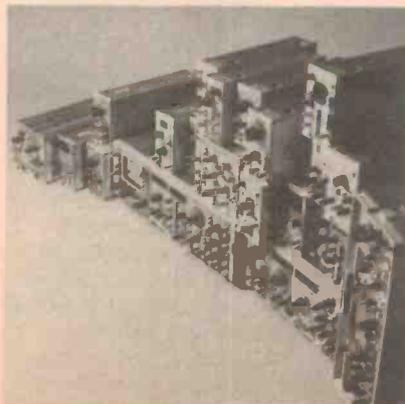Another long-term advantage is, as new standards are set in electronics, new instruments will be added to the TM500 family — like our 40 MHz function generator with log sweep, phase lock, AM and FM capabilities and a long list of added dividends.



Your investment is further protected by Tektronix Long-term Product Support Program and worldwide over-the-counter service.

So, if you're in the market for accurate, reliable instrumentation, take stock of what TM500 has to offer. In convenience, versatility and economical performance, TM500 pays big dividends.

TM 500 Designed for Configurability

Write for full technical details and prices to
Tektronix Australia Pty. Ltd.,
80 Waterloo Rd., North Ryde,
N.S.W. 2113
or phone Sydney 888 7066,
Melbourne 818 0594, Brisbane
31 2896, Adelaide 223 2811,
Perth 325 4198.

Tektronix®
COMMITTED TO EXCELLENCE

Power Engineering Scope

The BWD 880 Powerscope, produced by BWD Electronics Pty. Ltd., is claimed to be the first instrument of its kind dedicated to measurement of voltage, current, phase angles and time in the field of power engineering. World patent rights have been lodged for this innovative instrument, which should have an immediate appeal to power engineers needing a safe means of measuring high voltages and displaying them for visual evaluation.


Industries, utilities and educational establishments using thyristors, triacs, ignitrons, magnetic amplifiers, etc. to control 1, 2 or 3 phase power for motors, lights, heaters or welders can employ Powerscope for design, monitoring, field service and teaching.

Operator safety is provided by a fully insulated panel, controls and probes, fitted with shrouded high voltage connectors and closed conformity to IEC 348 safety requirements.

The high CMR of each amplifier enables signals down to 100mV p-p to be measured across components operating in 600V RMS 3 phase or 350V RMS single phase supplies.

Phase measurement is by a 1° wide intensified marker pulse with digital readout, selectable by an up/down counter from 0° to 359°. Zero reference is also selectable in 60° steps from 0° to 300°. Phase circuit operates automatically over the range 25Hz to 2KHz and may also be used to provide digital trigger delay in 1° steps for the time base.

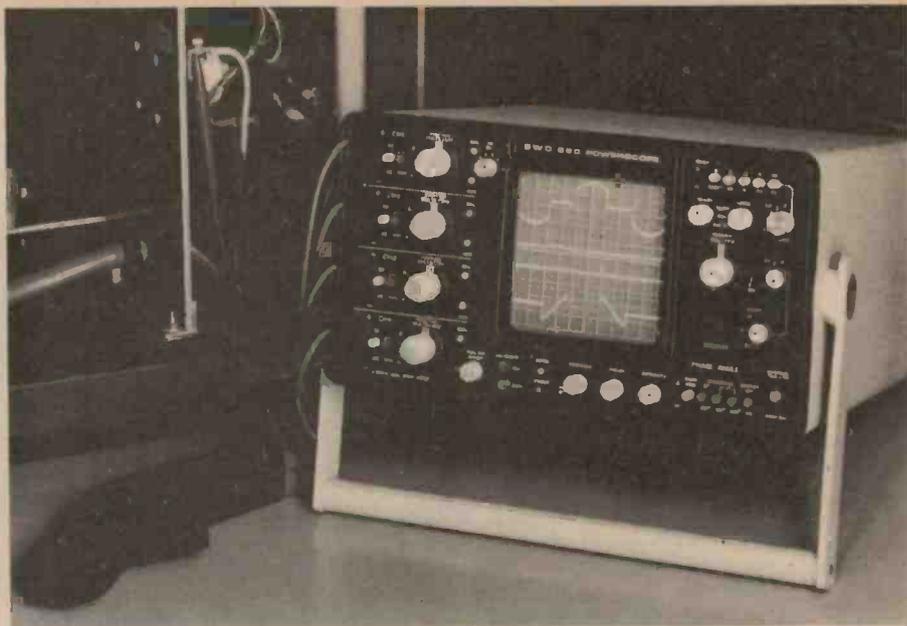Further details can be obtained from: BWD Electronics Pty. Ltd., Miles Street, Mulgrave, Victoria, 3170.



New DMM

Parameters has announced the new B & K-Precision Model 2810 which has a combination of features uncommon in a portable digital VOM. Basic DC accuracy is 0.5% with a 3½-digit display. Auto zeroing on all but the 10 ohm range minimizes set-up time, while the 100% overranging capability reduces the need for frequent range changes.

A highly valuable feature is the 10 ohm range. This range, with its .01 ohm resolution, is ideal for locating a shorted winding in a transformer, motor or coil. For high accuracy, a front panel 10 ohm ZERO control allows the user to zero-out the minute amount of test lead resistance.

The high/low power ohms switch is operated independently from the range switch allowing high/low selection on four ranges. The low power ohms position permits resistance measurements in solid-state circuitry without biasing semiconductor junctions.

Unlike many electronic voltmeters, the 2810 can also be used in RF energy fields. This includes use near business band, CB and amateur radio transmitters. When working with RF circuitry, the optional PR-21 probe is also helpful.

Like other B & K-Precision instruments the 2810 is well protected against overloads on all ranges. The ohms circuitry is protected against momentary overloads up to 1000 volts, DC or AC peak. Continuous ohms range protection is + 100 V and - 450 VDC or 300 VAC. Current ranges receive the double protection of diodes and a fuse.

For further information contact Bruce McCarthy, Parameters Pty. Ltd.,

68 Alexander Street, Crows Nest, NSW 2065.

ETI/Unitrex Contest

In the May issue, we posed a coin-tossing problem, and asked whether young Simon was wise to approve of a modified scheme with three coins. Needless to say, Simon ended up checking the contest entry envelopes one more time. You see, there are eight possible combinations in which the three coins could land, and four of them are winning combinations for Simon and four for me. So the situation was not better for Simon, it stayed the same, in fact, so he wasn't entirely wise. Garry Dunn, of Heathcote, NSW, was wise, and won the Unitrex calculator for his correct answer.

We've had a few easy contests recently, so here's a real toughie: Using the digit 4 four times in an arithmetic expression, with the standard mathematical operators +, -, x, /, and also parentheses, y^x and !, it is possible to make equations with several different values. For example $(4+4)/(4+4)=1$, $4/4+4/4=2$, $(4+4+4)/4=3$ and a more complex example would be $4^4-(4x4!)=160$.

Now you've got the idea, we'd like you to find equations for as many numbers as possible between 70 and 75 inclusive. If it's any consolation, we've only just started working these out ourselves, but have been assured that it can be done!

Seal an empty envelope, write your answer on the back of it and send it to: Unitrex Calculator Contest (July), ETI Magazine, 15 Boundary Street, Rushcutters Bay, NSW 2011. The closing date is Friday, 18 August.



A major independent research company proved that the ADC XLM MKII incurred no perceivable record wear over the life of your records!

Since then ADC's massive research programme has created a new state-of-the-art, top of the line model—the ZLM Aliptic—designed for ultimate stereo performance combined with the concept of zero record wear.

Greatly reduced tip mass

The ZLM has a tiny nude diamond with a .004" x .008" rectangular shank.

This achieves more lateral strength than the fashionable .006" square shank, plus a 10% reduction in mass.

The diamond is mounted on a new tapered stylus, which again reduces mass.


In fact, the ZLM has only half the tip mass of the famous ADC XLM MKII.

Less mass by patent

The patented ADC Induced Magnet system, where the magnet is suspended over the moving stylus arm instead of being attached to it, inherently means less mass for the record groove to move. This, coupled with major innovations in the pivot block stylus suspension (which have solved deficiencies in the old system), has resulted in greatly improved frequency response characteristics.

New low-wear ALIPTIC shape

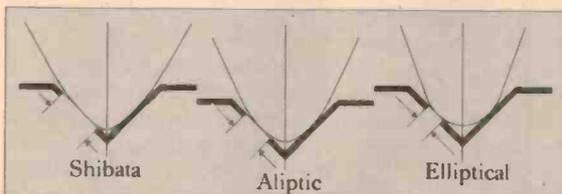The ZLM has a new tip shape that combines the advantages of the elliptical and Shibata shapes, while eliminating their disadvantages.



It is basically elliptical (.0003" x .0007"), but its bottom radius has been modified to extend the vertical bearing surface on the groove wall by 100%.

Large enough to greatly reduce record wear, while still small enough to prevent dirt particles being reproduced. This new shape is called ALIPTIC.™

The best polish available

We decided it was worth the extra cost to get the ultimate polish for the ZLM.

The method involves a cam action to shape and polish evenly while forming the elliptical surfaces simultaneously with the other radii. This Pathe-Marconi method is expensive, but the result makes another important contribution towards reducing record wear.

Spatial sound

You'll notice a distinct difference in sound quality. Words such as 'open,' 'spatial,' 'uncoloured' and 'true' spring to mind. Individual instruments are easily identified, and there's no hint of listening fatigue.

That's strictly for the competition with its peakier response.

The new ZLM Aliptic

The culmination of all ADC's research has resulted in the new ZLM Aliptic.

Its specifications below are some of the most impressive around, and with each cartridge you receive an individual, signed, frequency response testimonial.

Certain ZLMs fall within a range of $\pm 1/2$ dB 10Hz to 20kHz and ± 1 dB out to 26kHz.

These rare cartridges are called ZLM Select and are only available on special order.

The best cartridge we've ever made

The ZLM is without doubt the best cartridge we've ever made, but it's well worth taking a closer look at the new ADC XLM III which incorporates all of the reduced mass accomplishments of the ZLM, but with a tiny elliptical diamond. This also includes an individual specification.

Complementing the range, we have the new four-cartridge QLM Mk III series, incorporating our new design criteria and exciting innovations like the Diasa (diamond + sapphire) elliptical tip.

ZLM Aliptic specifications

Diamond tip	Nude Aliptic
Tracking force	1/4 to 1/2 gram
Frequency response	10Hz to 20kHz ± 1 dB 20kHz to 26kHz $\pm 1/2$ dB
Output	1.0mV per cm/sec
Output balance	1dB max. diff.
Channel separation	30dB at 1kHz/20dB at 10kHz
Inductance	580mH
Resistance	820 Ohms
Load resistance	47,000 Ohms
Load capacitance	275pF
Cartridge weight	5.75 grams
Accessories	Stylus brush, screwdriver, all mounting hardware and signed frequency response curve.

Please write for our illustrated brochure.



The new ZLM Aliptic™ cartridge.
The difference between
playing your records and
wearing your records.



Audio Dynamics Corporation,
A Division of BSR (A'asia) Pty. Ltd., Anne Street, St. Mary's, NSW 2760.

**See & hear
ADC Products at**

Sydney City and Metropolitan Area

Douglas Hi Fi
338 George St., SYDNEY 2000
Phone 233 3922

Russin Hi Fi
256 Liverpool Rd., ASHFIELD 2131
Phone 799 2421. John Russin.

Leisure Sound
871 Pacific Highway, CHATSWOOD 2067
Phone 411 4944 Alex Haindi
387 George St., SYDNEY 2000
Phone 291 364 Andres Goldfinch

Buyers World (NSW) Pty. Ltd.,
Shop 7, Lindfield Arcade,
Lindfield Ave., LINDFIELD 2070
Phone 467 2500. Rob Simpson.

Warringah Hi Fi,
Shop 5, Bungan St., MONA VALE 2103
Phone 997 5313. A. Preston.

Riverina Hi Fi
549 Pittwater Road,
BROOKVALE, 2100
Phone 938 2663. Nich Barovsky.

NSW Country

Springwood Hi Fi
170 Macquarie Rd., SPRINGWOOD 2777.
Phone (047) 513091. L. Johnston.

Wroth Hi Fi,
63 George St. (PO Box 452)
BATHURST 2795
Phone 31 6313. Michael Wroth.

Scotty Wallace Pty. Ltd.,
113 Rankin St., FORBES 2871.
Phone 522 300. Scott Wallace.

Hi Fi Gallery
(C/- P.O.), Tamworth Centrepoint,
374-388 Peel St., TAMWORTH 2340
Phone 66 2474. L. Taylor.

John Roworth Television Services,
11 White St., TAMWORTH 2340
Phone 66 4664. J. Roworth.

Taree Photographics
Graphic House, 105 Victoria St.,
(P.O. Box 295) TAREE 2430
Phone 52 1488. M. Small.

ACT Duratone Hi Fi Pty. Ltd.,
3A Botany St., PHILLIP 2606
Phone 82 1388. M/s Fay Cull.

VIC Douglas Hi Fi
202 Bourke St., MELBOURNE 3000
Phone 663 2211

QLD Brisbane Agencies Audio Centre,
72 Wickham St., FORTITUDE VALLEY 4006
Phone 268 3167. G. Eldund.

Ipswich Hi Fi Centre,
61 Limestone St., IPSWICH 4305
Phone 281 5485. Robert Smallwood.

Sight and Sound Investments,
Shop 8, Shaws Arcade,
TOWNSVILLE 4810
Phone 71 5618. Stephen Shaw.

SA Soundynamics Hi Fi Centre,
129 Payneham Rd., ST. PETERS 5069
Phone 42 1237. Peter Hazelwood.

Instrol,
54 Flinders St., ADELAIDE 5000
Phone 223 7622

WA Hub Record & Hi Fi Centre,
Gilmore Ave., CALISTA 6267
Phone 99 1256. R. Takes.

Albert's Hi Fi,
542 Albany Highway,
VICTORIA PARK 6100
Phone 62 1188

396 Murray St., PERTH 6000
Phone 322 4409

288 Hay St., East, PERTH 6000
Phone: 25 2699

Leslie Leonard Hi Fi
Shop UB City Arcade,
Upper Hay St., PERTH 6000
Phone 22 4304


TAS Quantam Sound Centre,
194 Liverpool St.,
(P.O. Box 1788) HOBART 7000.
Phone 34 3051. R. MacFie.

SERVICEMEN



Scratching your head
won't help
THIS WILL!

18 Years of service

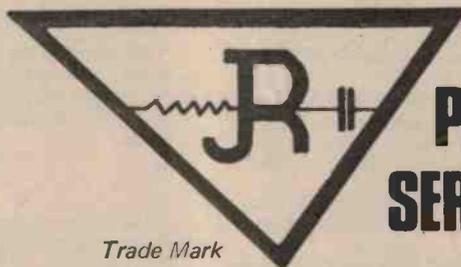

Trade Mark

PAL TELEVISION SERVICE HANDBOOK

Volumes 1, 2 & 3
1974 to 1978

Manuals on:

Colour and Monochrome. Also Cassettes and Transistor Radios.

Colour TV

Patchett's: Colour TV with Part Ref to PAL System.

Send for your brochure:—

J.R. PUBLICATIONS
P.O. Box 29
CHESTER HILL
2162

or call:

53 Stanley St.
Peakhurst
N.S.W. Aust.
Phone 53 6295

or:

VITAL BOOKS LTD.
P.O. Box 8601
Simon Street
AUCKLAND N.Z.

A SOUND SO PURE



GOLDRING G 900 SUPER E "Micro Mass" Moving Magnet Cartridge

The key to the outstanding performance of the G 900 SE lies in its extraordinary low stylus tip mass of only 0.32 mg — considerably less than most of its competitors. The following are comments quoted from various international reviews which, we believe, speak for themselves.

"The Goldring G 900 SE offers performance comparable to the best moving coils, and is superior to all moving magnets. Its mid range and high end are remarkably clear and low in distortion. Imaging and depth reproduction are also outstanding.

The Goldring is an outstanding value, offering performance comparable to the best cartridge systems costing 2 and 3 times as much.

("Sound Advice", the well respected American magazine for HI-FI enthusiasts)

"Its incredibly clear with a strong but fairly liquid treble quality. This helps to throw up much more detail; but strong treble signals that sound so bad, although reproduced with brutal honesty, sounded perfectly normal and acceptable

through sheer naturalness. The bass end was very firm, in good balance tonally and at times showed its true ability by turning out a real low that was frightening in realism.

Remembering that everybody has personal preferences in sound, I would class the G 900 SE as one of the very best cartridges available. Personally, I believe it is THE best cartridge that is widely available, especially considering the retail price."

(Phillip Mount in his column "Test Bench" published in "Gramophone" U.K.)

"Goldring have good reason to be proud of their achievements, for the G 900 SE displays characteristics that place it in the forefront of high-grade cartridges. It yields a firm, clear and fairly explicit sound with excellent stereo imagery. Its freedom from hard tonal quality or undue forwardness in the upper range offers an interesting contrast with some prestigious models."

(Clement Brown in the British publication "On Test")

High praise indeed! But check for yourself.

FOR SUPERIOR PERFORMANCE TRY THE G 900 SE. THE PURITY OF ITS SOUND WILL ASTOUND YOU. AND SO WILL ITS MODERATE PRICE.

In addition to the G 900 Super E our comprehensive range includes high quality magnetic cartridges to suit all types of turntables.

Sole Australian Distributors for GOLDRING PRODUCTS LTD., U.K.:

SOUNDRING DISTRIBUTORS

1/514 Miller St., Cammeray, 2062
P.O. Box 154, Cammeray, 2062.
Tel. (02) 92-1990

DEALER ENQUIRIES WELCOME

Agent in Victoria:
Jasper Coote Pty, Ltd.,
304 Coventry St, South Melbourne, 3205
Tel. (03) 699-4455

SOUND

Importers: Audio 2000,
Box 107, Brookvale 2100.

GFC Hadcock pickup arm

G.F.C. Hadcock is the manufacturer of an advanced unipivot pickup arm, the GH228 super. The arm, we understand, was originally designed with the Decca cartridges in mind, although this does not preclude its use with other cartridges, especially low-compliance moving coil models.

The Rev. George Hadcock has a fine background of audio experience including service with the BBC and his grasp of the problems of playing records is evident from the design of the 228 arm. It is a very rigid device, with a surprisingly secure unipivot based on an upward pointing shaft with a conical tip, and an inverted bearing cup fitted with a ball-race. Whilst this regime, also featured in the KMAL Mk. III mercury contact arm, is potentially less free of friction than the jewelled bearing system of the Formula 4 by JH, it is rather more rigid, minimising the tendency toward resonances in the pickup system. Complementing this, a substantial main tube, made from hard aluminium alloy, and a lightweight but very rigid metal headshell are employed.

The counterweight is fitted to a tube of similar diameter projecting from the rear of the bearing housing support hub. A decoupling bush is used to secure this tube, and the counterweight itself, which is mounted eccentrically, can be moved fore and aft using a set-screw. A further resilient bush is also used in the counterweight to provide a tight fit, so that it stays put when rotated to give correct lateral balance.

As with all unipivots, some form of pivot damping is needed to prevent wobbling when a record is being played. The usual viscous damping system is used, the bearing cup skirt extending into a reservoir filled with fluid about the bearing shaft. The damping rate can be adjusted by lowering the shaft so that the skirt can penetrate deeper into the fluid; in addition, the bearing cup can be lowered to prevent fouling of the main hub on the pedestal.

Routing of lead-out wiring is always a problem with unipivots. In the Hadcock, the four wires emerge from a small hole in the bottom of the main hub, and are looped round to disappear into a small hole in the pedestal. The loop is unshielded but could hardly give rise to hum and gives negligible resistance to arm movement in either plane.


The pedestal is a tight fit into a mounting base, which is itself threaded and fitted with an enormous brass securing nut, enabling the arm to be bolted very securely to the motor board.

Installation

Hadcock supplies an adaptor for use with turntables previously fitted with SME arms, and by good fortune we had at our disposal a Linn-Sondek board already drilled for an SME. Assuming the original SME cut-out to be correctly positioned, the arm is accurately lined up by use of this adaptor. Installation without the adaptor poses no problems, however, although a template would be useful. Nevertheless it is a simple job to make one up.

One of the most appealing features of the arm is its ability to be fully adjusted. The headshell, particularly, can be lined

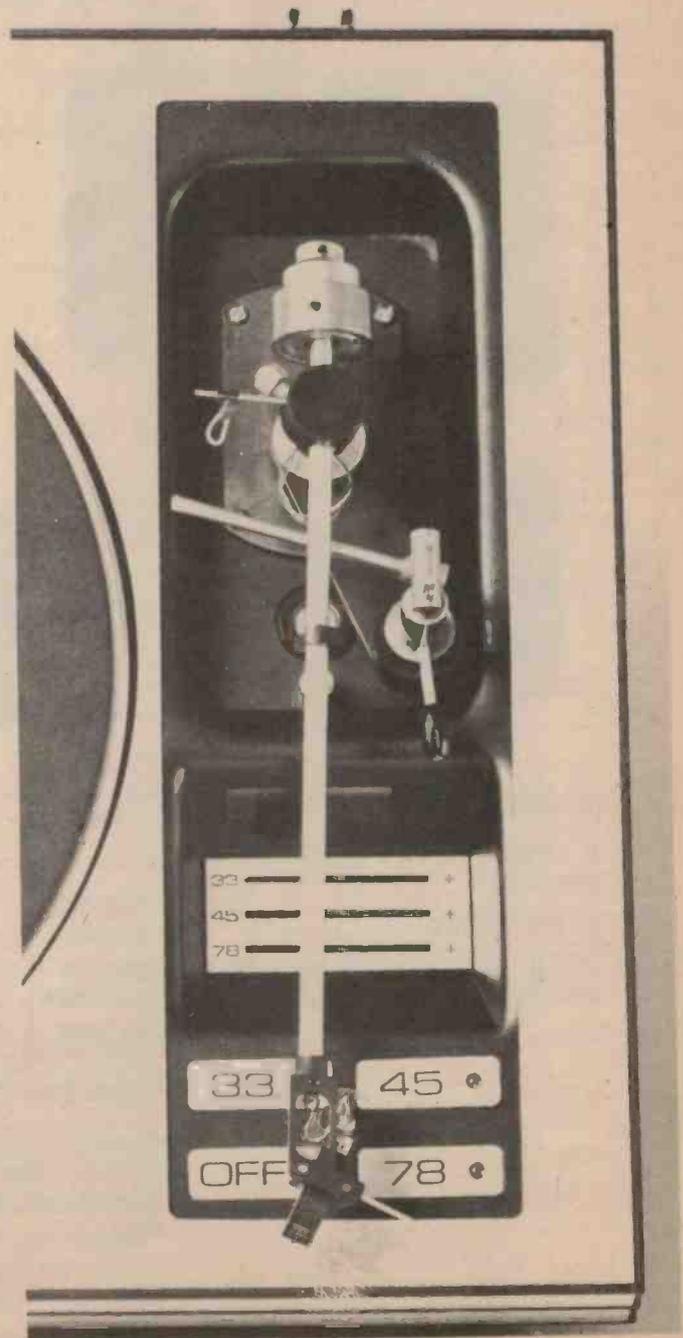up without difficulty using the top of the main hub as a sighting reference. Allen-key grubscrews are used throughout and can be tightened very easily to produce rigid metal/metal interfaces.



**PREMIER
RELEASE**



PLESSEY-FOSTER Speaker Kits



HX15-3W



HX12-3WA



HX12-3W



HX10-3W



HX8-2W

Harmonix Speaker Kits offer:

- A most extensive range of speakers
- At low prices
- Using superior Plessey-Foster components and design

Model	Speaker Size	Power	Frequency Range	Box Price	Component Price	Total
HX8-2W	28 litres	20 RMS	20Hz-75KHz	\$25	\$43	\$68
HX10-3W	33 litres	30 RMS	20Hz-20kHz	\$40	\$43	\$83
HX12-3W	53 litres	35 RMS	20Hz-22kHz	\$42	\$85	\$127
HX12-3WA	75 litres	70 RMS	20Hz-15kHz	\$50	\$87	\$137
HX15-3W	95 litres	70 RMS	18Hz-40kHz	\$65	\$98	\$163

Phone 519-5127 for a free brochure and your nearest dealer.

Currently available from:
Hi-Fi City, 269 Elizabeth St., Sydney.
Edge Electrix, Burwood. NSW.

Manufactured in Australia by
Harmonix Acoustix,
29 Vincent St., Marrickville. NSW. Phone 519-5127.

SOUND

Included with our sample was the Unilift Mk.III, fitted to a spacer strut which was secured to the pedestal during installation. The Unilift appears somewhat complex at first sight with its double shaft/link/lifter bar system. This gives a very flexible range of adjustment however, and there is also an adjustment for speed of descent. The operating lever swings laterally around the device rather than pivoting vertically as is more common. We found the Unilift was easier to use than most lifters because of this.

A generous quantity of damping fluid, rather less viscous than the sort supplied by SME, JH, Decca and KMAL, was supplied ready for use in a disposable hypodermic syringe, making the task of filling the fluid reservoir easy and accurate. The syringe also makes removal of excess fluid a simple operation (SME suggests you spoon their fluid out with a matchstick!).

A consequence of the particular design of the arm is that the entire carrying arm section can be lifted from the pivot, enabling cartridges to be mounted and changed without difficulty. Although no plug-in system is provided, and no cartridge position adjustment relative to the headshell is allowed for, spare headshells can be supplied and these are easily fitted. Fine adjustment can be carried out by moving the headshell along the arm tube.

The counterweight is made in two sections — the main weight with its captive set screw and an outer supplementary weight. Three of these outer weights are provided, each of different size allowing a very wide range of cartridge weights to be accommodated whilst maintaining the main arm/cartridge resonance at an optimum frequency.

We were very impressed at the ease of installation and setting up the arm, although the bias adjustment using a thread-and-weight system was fiddly and could be improved. The arm looked functional rather than beautiful although the precision of fit of each part was exemplary.

Performance

Tests using Decca 6E, Dynavector 20B and Supex 900 Super

cartridges revealed the arm was perfectly at home with lightweight and heavyweight low-compliance cartridges. The Decca tracked better in this arm than in any we've previously encountered, reducing the high frequency and stereo confusion observed in other situations. Bass sounded tighter and even more detailed than ever, and the definitive midrange performance for which this cartridge is renowned was further enhanced.

The Dynavector seemed less bass-shy and far smoother in the treble region than usual although we still feel the Dynavector arm (at a far greater cost) serves it best. Even so, the Hadcock gave an exemplary performance with the 20B and the combination can be recommended.

Likewise with the Supex, which is normally partnered with the Grace 707, suitably modified by decoupling and augmenting the mass of the counterweight. The high-frequency 'featheriness' of the Grace/Supex was not evident using the Hadcock, and while the sound was, perhaps, a trifle less 'spacious' it was also more detailed with improved dynamic contrasts.

This was also true of the other cartridges, which provided better transient performance than usual (although the Dynavector arm probably gives better transients than the Hadcock with the 20B).

Overall, we found the Decca/Hadcock combination by far the most dynamic, giving a very fine illusion of musical sound with superbly defined perspective and excellent side-to-side stability.

Conclusion

Like so many British products, the Hadcock arm looks rather untidy and its standard of finish simply doesn't compare with the best of Oriental products. The signal cable of our sample was poor and it was terminated in equally unimpressive RCA plugs. The cartridge connecting tags were too big and had to be replaced to fit the Supex. These criticisms aside, the arm was well engineered and certainly provided excellent conditions for the cartridges tested. A brief session with the Garrott P77 confirmed its suitability for medium/high compliance cartridges. At a price (complete with Unilift) of around \$165 rrp, the GH228 Super is highly recommended especially if you're a Decca freak.

Technics SB10000



MANUFACTURERS' and technicians' investigations into phase of crossovers and drive unit mounting as a dual entity were prompted by jet propulsion engineer Richard Heyser.

Heyser started the formulation of phase coherence in a 1967 J.A.E.S. paper, "Acoustical Measurements by Time

Delay Spectrometry." This was followed by "Loudspeaker Phase Characteristics and Time Delay Distortion: Part 1," of 1969.

It appears that similar investigations were underway in non-English speaking countries. In Japan, the Matsushita

THE LOUDSPEAKER THAT LOOKS AT MUSIC THE WAY YOU DO: JBL'S NEW L110.

You're at a concert. The sound surrounds you. There's a guitar. A piano. Some horns.

You hear all of it.

But more than that, you hear each part of it. Each sound. Every sound. All the sound.


Most loudspeakers can't do that. They only meet you half way. Only left and right, all or nothing. JBL's new L110 goes all the way. It looks at music the way you do.

Left. Right. Front. Back.

The L110 has almost perfect stereo imaging—a result of precise, uniform dispersion at every frequency.

Inside the L110, there's a brand new, super-sophisticated crossover network designed specifically to match the new components.

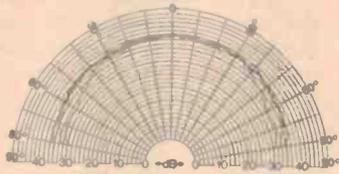There's a new 10" woofer which utilizes a massive 3" voice coil and 7½ lb. magnetic assembly—normally found in 12" woofers.



Frequency Dispersion of the L110

~~~~~ at 400Hz ~~~~~ at 2kHz ~~~~~ at 10kHz

JBL's new L110 loudspeaker is part of the same research and development breakthrough that created our no-tradeoff, top-of-the-line L212 system.

If this graph looks familiar, it should. The L212 produced an almost identical one.

The result is smooth, accurate bass, plus an amazing level of efficiency and power handling capability throughout the entire system. (One more nice: You get more headroom for your amplifier. Less clipping.)

Now look at the L110. The most acoustically transparent grille JBL has ever created is visually transparent, too. You can see right through to the satin black components inside.

If you'd like a lot more technical information on the L110, write us and we'll send you an engineering staff report. Nothing fancy. Except the specifications.

But you really should come listen to the L110. And ask for it by its first name: JBL. You'll be get-

ting the same craftsmanship, the same components, the same sound heard in the very top recording studios in the world.



Over four hundred of the leading recording studios in the world—from Los Angeles to London to Muscle Shoals to Munich to Tokyo to Tennessee—use our sound to make theirs. Shown here is Capitol Records in Hollywood, California.

Distributed by—  
HARMAN AUSTRALIA PTY. LTD., P.O. Box 6, BROOKVALE, N.S.W. 2100.

HA118/78

**JBL**  
GET IT ALL.





Electric Company's Technics division evolved a linear phase three-way speaker system that was first shown in 1975, the SB7000.

#### Demonstration

The Matsushita Hall of Science contains dozens of their patented components and, for the audio enthusiast, a most convincing display of loudspeaker phase is demonstrated. A two-way system, the SB 6000, is connected to an oscillator and dual beam oscilloscope. A microphone reads the speaker output which is compared to the original. The high range loudspeaker is motor driven on a sled . . . backwards and forwards . . . while a square wave signal is processed through the system. It is easier on the ears and eyes when the tweeter is correctly phased and both speakers unite in presenting a recognisable 1 kHz square wave.

With ideal driver matching and a phase coherent crossover network combined with ideal speaker driver placement all waveform components undergo an equal number of reflections and arrive at the same place, or plane, simultaneously.

The latest Technics linear phase speaker system is the giant SB 10000. This three-way system employs a 460 mm bass driver in a 226 litre vented cabinet; midrange and treble are horn loaded.

Each speaker system weighs in at 140 kg net. This is 22 stones in the old measure and about the weight of a junior sumo wrestler.

An important part of the linear phase requirement is wide range speaker units. The 15 Hz free air resonance of the bass driver naturally assists with low frequency response in such a large cabinet but the high range output seems to extend to around 1500 Hz although crossover frequency is 700 Hz.

The midrange horn has a reasonably flat response from about 450 Hz to nearly 8,500 Hz but is used from 700 Hz to 6,500 Hz.

A boron vacuum deposited high frequency diaphragm drives the treble horn through a range of about 1,500 Hz to 20,000 Hz with the lower frequency crossover point of 6,500 Hz.

No doubt the Technics crossover design follows earlier

driver tailoring such as a tweeter resonance cancellation circuit and rising impedance controls.

#### Performance

The power handling of the SB 10000 is claimed to be 200 watts continuous and 300 watts peak. The dynamic range using much lower powered amplification such as Radford 50 watt amplifiers was sufficient to elicit natural level fortes in a large living room.

These unique speakers were never strained in their presentation and appeared to never "squash" the dynamic range while reproducing such wide range discs as the Beethoven Appassionata direct cut piano recording or the Philips Rite of Spring with Colin Davis.

The output sound pressure level is quoted as 95 dB for one watt input measured at one metre.

The Technics speaker factory assembles and tests three of these speaker boxes every day. The factory studiously checks all speaker systems from the lowliest to this giant in an 'on-line' anechoic chamber with automated B & K oscillator and chart level recorder. The author has visited the room where these charts are preserved and obtained copies of charts for Technics systems he has heard in Australia.

The complete story of this company's loudspeaker system manufacture is most complex. This particular SB 10000 occupies some half dozen employees for a complete day; they work at nothing else. The internal bracing and framework is of knot-free dense pine about 75 mm by 100 mm while the cabinet itself is 44 mm thickness high density chipboard. The curved front and radiussed matching front verticals are made right alongside the complete assembly section. All sawdust is immediately extracted by suction piping.

This speaker system has a similar crossover design to previous Technics linear phase systems but also incorporates a set of external binding posts giving access to the individual drivers. These posts are situated within the cabinet top at the rear and underneath the removeable cover plate. Cabling ducts are adjacent to each separate input and against the built-in crossover, or normal, input.

These are very handy cable holes and make for a neat appearance. The cover has to be seen to be believed as tremendous attention to design has been lavished on an otherwise unseen item.

The terminal posts are sturdy two part metal items that allow light or heavy gauge wiring. Knotting the cables together and fixing to the binding posts ensures positive connection.

Impedance is quoted as six ohms with crossover frequencies of 700 Hz to 6,500 Hz. Separate tri-amplification crossover frequencies are suggested between 600 and 1,000 Hz for low to mid; and 4,000 Hz to 8,000 Hz for the mid to high frequencies, all at a minimum of 12 dB/octave with an 8Ω impedance for each driver.

#### Acid Test

The SB 10000's were tried in a known difficult position along a ten metre wall fitted with built-in shelves. They were spaced 2.75 metres between centres and some 4.2 metres was the average listening distance. The treble horn was centred 1150 mm above floor level and presented a good relationship between apparent height and recorded perspective on most modern orchestral recordings.


With the cabinets toed-in at about 30° this left about three metres of clear space before wall surfaces caused late reflection.

This position did not give any apparent degree of bass boost. This was later confirmed through tests with pink noise with the cabinets fractionally moved (they are very heavy).


# Wait till you hear what you have been missing



A

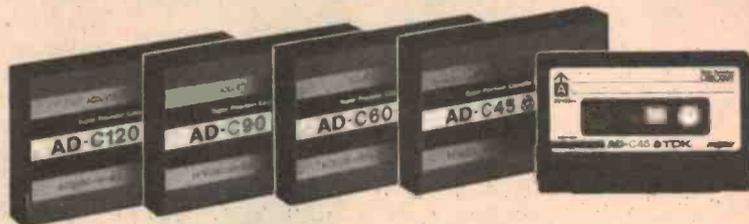


B

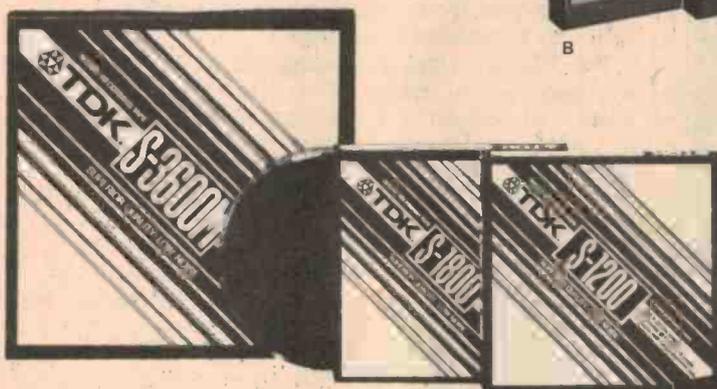

C



D

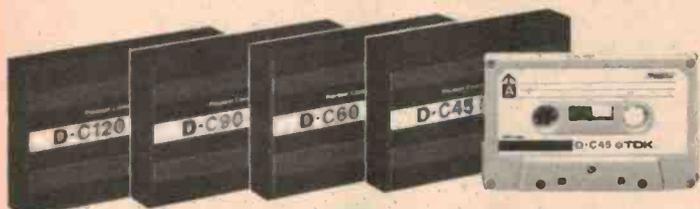

E



F



G

**A • SA Super Avilyn cassettes.** Exclusive technology AVILYN results in simultaneous suppression of high-end noise and delivery of a flat response curve with better highs. Equipped with auto-sensing openings which automatically switch bias and EQ settings. Highest signal-to-noise ratio, saturation and lowest distortion decrease the need for Dolby NR. Super Precision Cassette Mechanism engineered to tolerances in microns assures years of trouble-free operation.

**B • AD Acoustic Dynamic cassettes.** Higher maximum output and lower noise levels for dynamic range. Use on any cassette recorder without need for special bias/EQ settings. Cassette mechanism same premium quality as S.A.

**C • S Series Reel-to-reel.** High signal-to-noise ratio, broad dynamic range across the entire wide frequency response spectrum.

**D • D Dynamic cartridges.** Broad dynamic range for good "real-life" sound. High signal-to-noise ratio low harmonic distortion and noise levels assures bright, warm and mellow sound reproduction on all recorders with "Normal" bias settings.

**E • AD 8 Track cartridge.** Extended high-range performance. Excellent signal-to-noise ratio and broad dynamic range. Precision molded, jam-proof mechanism with mirror smooth coating prevents shedding and oxide rub-off, reduces headwear.

**F • EC Endless Loop cassettes.** Provides continuous-run repeat-message operation for sales displays, telephone answering, background music, point of purchase advertising. For use on most conventional cassette players and recorders.

**G • HC-1 Head cleaner.** Recommended for periodic use in all cassette recorders to clean and keep the recording head in good condition thus preventing serious loss of high frequency response and assure proper tape to head interface.

**H • LB Series Audua Reel-to-reel.** Back treatment is unique and assures a stable surface. Eliminates drop outs. Prevents uneven winding with friction-free running. Eliminates wow and flutter.



Music gets you up.  
**TDK**  
cassettes and tapes  
will take you higher.

**TDK**

For your nearest dealer, brochures and information contact  
CONVOY INTERNATIONAL PTY. LTD.  
4 Dowling Street, Woolloomooloo, N.S.W.  
2011. Tel (02) 358 2088


# NESSEL LOUDSPEAKERS

PROFESSIONAL SERIES



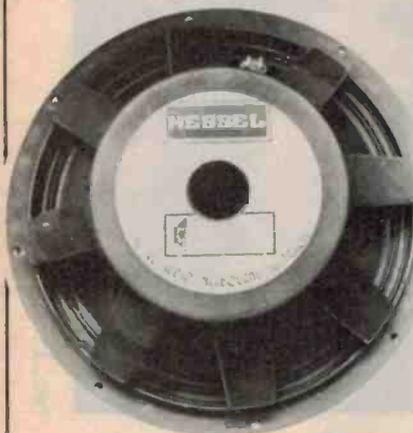**Rugged cast aluminium**

27½" W x 7" High x 19" deep.  
90° lip horn  
Throat adaptors for screw-on  
1 ¾" and 1" entry.  
500 c/s crossover



**Range of speakers**

### Model:

- SL1201: 12" 4" coil, 100W, Guitar Bass PA, 8 kg, 80 c/s.
- SL1502: 15" 4" coil, 150W, Guitar Bass PA, 9 kg, 55 c/s.
- SL1403: 15" 4" coil, 200W, Bass PA, 14 kg, 70 c/s.
- SL1803: 18" 4" coil, 200W, Bass, 14 kg, 50 c/s.

**TRADE ENQUIRIES WELCOME**

Available from



## NESSEL AUDIO

9 Nellbern Rd,  
Moorabbin East, Vic. 3189  
Ph (03) 95 9510

# NEW BOOKS

Just a few of the thousands in stock. Call in or write. Prices subject to fluctuation — correct at time of going to press. Mail orders by return. Please add 90c per parcel post (Vic) \$1.20 per parcel interstate.

|                                             |         |
|---------------------------------------------|---------|
| ARRL Radio Amateur's Handbook 1978 .....    | \$12.95 |
| Radio Amateur Callbook 1978 .....           |         |
| US Listings .....                           | \$19.50 |
| Foreign Listings .....                      | \$18.50 |
| Radio Communication Handbook, RSGB, 5th ed. |         |
| Vol 1 .....                                 | \$21.95 |
| Vol 2 .....                                 | \$18.90 |
| World Radio TV Handbook 1978 edition .....  | \$12.95 |

### NEW BOOKS ON CB

|                                                                                                                 |         |
|-----------------------------------------------------------------------------------------------------------------|---------|
| Best Book on CB — Includes all 40 channels and 1977 regulations, choosing equipment, installation and use ..... | \$6.25  |
| 99 Ways to Improve Your CB Radio — Buckwalter .....                                                             | \$5.60  |
| Pictorial Guide to CB Radio Install & Repair .....                                                              | \$8.50  |
| Practical CB Radio Servicing .....                                                                              | \$9.75  |
| The Truth About CB Antennas — Orr & Cowan .....                                                                 | \$8.50  |
| ARRL Radio Amateur's Handbook 1978 .....                                                                        | \$12.95 |
| World Radio TV Handbook 1978 Edition .....                                                                      | \$12.95 |

### RADIO & ELECTRONIC

|                                                                               |         |
|-------------------------------------------------------------------------------|---------|
| Advanced Applications for Pocket Calculators .....                            | \$8.50  |
| Amateur Radio Techniques — Hawker, RSGB .....                                 | \$8.20  |
| Amateur Radio Theory Course — Ameco .....                                     | \$7.80  |
| Antenna Handbook, ARRL .....                                                  | \$8.80  |
| Australian Radio Amateur Callbook 1977 .....                                  | \$2.85  |
| Active Filter Cookbook — Lancaster .....                                      | \$19.00 |
| Beam Antenna Handbook — Orr .....                                             | \$7.80  |
| Best of Creative Computing Vol 1 .....                                        | \$15.95 |
| Best of Creative Computing Vol 2 .....                                        | \$15.95 |
| Building Hi-Fi Speaker Systems .....                                          | \$3.95  |
| Building & Designing Transistor Radios — Warring .....                        | \$7.40  |
| Cubical Quad Antennas — Orr .....                                             | \$6.75  |
| CMOS Cookbook — Lancaster .....                                               | \$13.50 |
| Electronic Calculator User's Handbook — Babani .....                          | \$2.75  |
| Getting to Know Oscar — ARRL .....                                            | \$5.60  |
| High Fidelity Audio Amplifier Circuits — Texas Instruments .....              | \$3.30  |
| Ham & CB Antenna Dimension Charts — Noll .....                                | \$3.90  |
| Ham Radio Operating Guide, ARRL .....                                         | \$7.20  |
| How to Buy & Use Minicomputers & Microcomputers .....                         | \$13.50 |
| IC Op-Amp Cookbook — Jung .....                                               | \$17.80 |
| Installing TV & FM Antennas — Sands .....                                     | \$6.50  |
| International Transistor Selector — Towers .....                              | \$9.75  |
| International FET Selector — Towers .....                                     | \$10.75 |
| Introduction to Microcomputers, Vol 1 Basic Concepts — Adam Osborne .....     | \$12.55 |
| Introduction to Microcomputers, Vol 2 Some Real Products — Adam Osborne ..... | \$21.55 |
| Japanese Radio, Recorder Tape Player — Schematic Servicing Manual .....       | \$9.90  |
| Low & Medium Frequency Radio Scrap Book — Ham Radio Magazine .....            | \$9.85  |
| Magazines — Bytes, Interface Age, Kilobaud — each .....                       | \$4.00  |
| Magazine — Dr Dobbs: Personal Computing, Peoples Computers, each .....        | \$3.00  |
| Master Handbook of Digital Logic Applications — Hunter .....                  | \$10.95 |
| Master Handbook of 1001 Practical Electronic Circuits .....                   | \$13.95 |
| Master Tube Substitution Handbook .....                                       | \$6.95  |
| Microprocessor/Microprogramming Handbook — Brice Ward .....                   | \$9.75  |
| Phillips General Catalogue 77 .....                                           | \$4.00  |
| Programming Microprocessors, McMurrin .....                                   | \$9.75  |
| Radio Amateur's VHF Manual, ARRL .....                                        | \$8.00  |
| Radio Handbook, new 20th edition .....                                        | \$24.40 |
| Reference Data for Radio Engineers .....                                      | \$37.50 |
| RSGB Radio Data Reference Book .....                                          | \$9.35  |
| Servicing Electronic Organs — Tab .....                                       | \$13.95 |
| 73 Dipole & Long-Wire Antennas — Noll .....                                   | \$7.80  |
| 73 Vertical Beam & Triangle Antennas — Noll .....                             | \$7.50  |
| Test Equipment for the Radio Amateur, Gibson — and RSGB publication .....     | \$6.65  |
| Transistor Substitution Handbook, 15th ed. .....                              | \$5.65  |
| Understanding Amateur Radio, ARRL .....                                       | \$7.30  |
| VHF Handbook for Radio Amateurs .....                                         | \$8.50  |
| Introduction to Microcomputers, Vol 0 — The Beginners Book .....              | \$12.55 |
| VHF-UHF Manual, Evans & Jassop, RSGB, 3rd ed. ....                            | \$17.00 |

### TECHNICAL BOOK & MAGAZINE CO


299-199 Swanston Street, Melbourne 3000  
Ph: 663-3951

ACT-08



STUDIO A

Turn to page 20

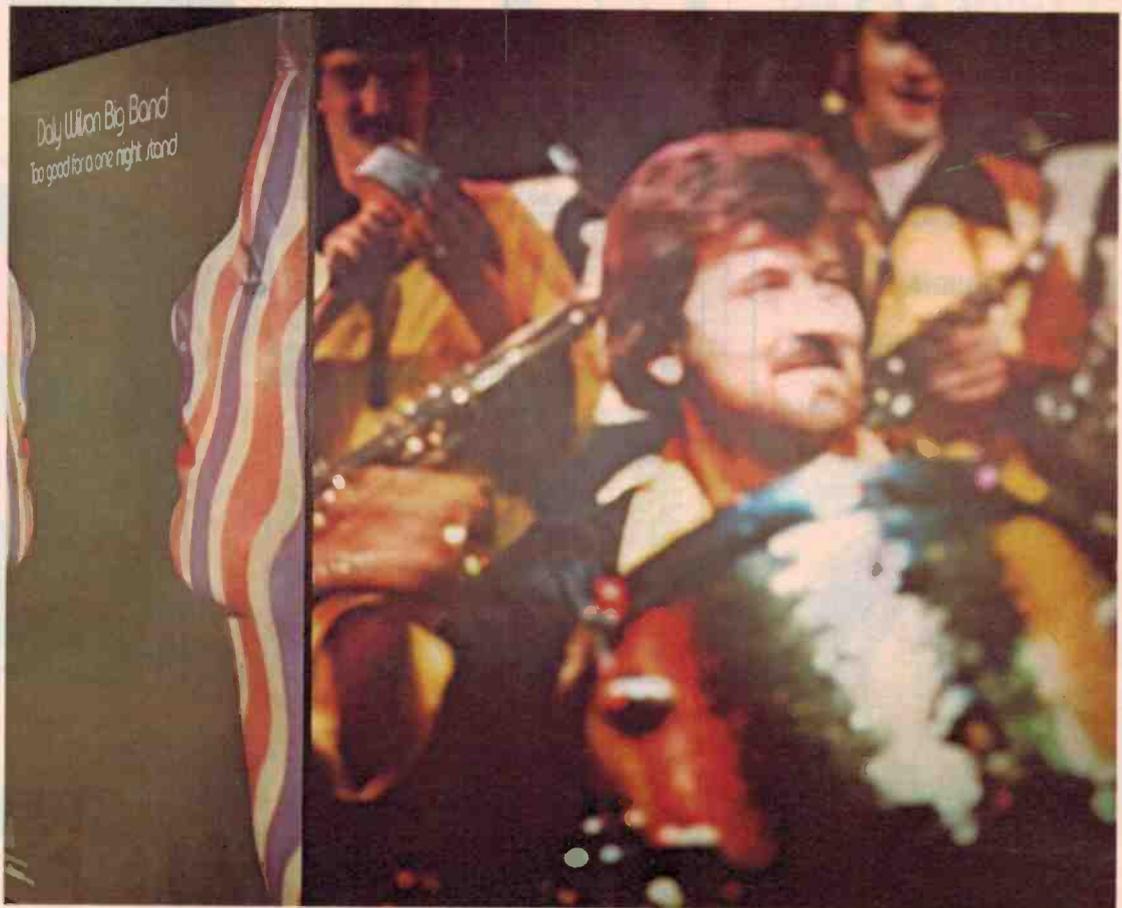

No. 1 in a collection

**Just for the record**

**The Daly Wilson Big Band  
tapes with  
Ampex**

The artistry . . . the atmosphere . . .  
the true and brilliant sounds of the  
musician . . . In professional recording  
studios throughout the world the  
tape used for the original "master"  
is Ampex. When you've made it with  
the professionals you'll accept  
nothing less.



Ampex Australia Pty Limited,  
4 Carlotta Street, Artarmon. Phone (02) 439 4077  
541 King Street, West Melbourne 3003 Phone (03) 329 0388





...and off the record

## Warren Daly and the band still tape with Ampex



The tape specified on experience by today's top recording engineers is equally at home with our uncompromising artists. And Ampex guarantee this impeccable performance—in studio quality cassettes and tapes from selected hi-fi stores, and retailers.

If it's worth taping it's worth Ampex.

**AMPEX** the professionals

## SOUND

The Durufle Requiem on CBS 235881 side two is a good test of low soft bass (quite apart from the beauty of the music). With the SB 10000 system at extremely low volume the bass speakers give a most thrilling account of held organ notes. Such ease of bass speech, apparently in good balance with higher output levels, indicates linear output with input. This is not often accomplished in a bass speaker.

This quality bass driver, a big cabinet and perhaps a knowledge of the pioneering work of Thiele and Small have produced a welcome change to well defined deep bass.

The midrange and high frequency horns have once or twice sounded 'horny'. The initial occasion was when demonstrating the speakers transient response with Maxwell Davies' "L'homme arme" on l'Oiseau-Lyre DSLO-2. Vanessa Redgrave actually used a megaphone in this section of the disc and for a few sides following this playing occasional horniness seemed to appear.

Midrange and high frequency controls are behind the front panel and were preferred slightly reduced from the marked 'normal' position.

Although furniture removalists delivered the units, they were easily slid on carpets to another much larger room where there was about three metres of clear space behind each cabinet. With a similar toe-in, half a metre to the side walls and a centres distance of 3.4 metres, the speakers were given a more realistic listening distance of 5.1 metres which is more in keeping with their size.

However, the three open archways against which the speakers were placed did not assist with forward projection. In fact, it was almost as if the units were deliberately

misplaced to cause complete acoustic imbalance.

This listening distance gave an almost straight ahead perspective which was not displeasing with loud piano solos but the source could have been higher on orchestral music. Personal preferences and live music experiences in the normal concert and opera halls are always at odds with manufacturers' presentations.

Again, the bass performance was unique for a commercial loudspeaker. The upper range became noticeably more coherent (perhaps due to the increased listening distance blending the bass-mid-treble driver spacing). Now, Indian drums, the tabla, originated in line with other instruments whereas, at a closer listening distance, they appeared to occasionally run from top to bottom of the speaker array.

Apart from the truly staggering size, appearance, weight, and, of course, the anticipated extreme five figure cost, the question of the value of linear phase applies.

Personal preferences of apparent source height could definitely favour available linear phase systems if the listening seats are not higher than about 400 mm and situated not more than about three metres from the speakers.

In any event, linear phase designed speaker systems offer the user a virtually tailored pair of sound sources. When correctly placed such 'matched' pairs offer the music lover equal amplitude outputs at all frequencies resulting in solid imaging.

Whether these particular Technics SB 10000 speakers will appear on the Australian market is now unknown. However, they will be on view at the 1978 Consumer Electronics Show. It is doubtful if they will be powered as their high efficiency could cause problems through inadvertant selection after less efficient speakers have been used.

# PLC 590—Pioneer

## Latest Pioneer Turntable

The new PLC-590 is Pioneer's first venture into an "armless" Quartz controlled, direct drive turntable which can meet the demands of the studio professional and advanced audiophile alike, and is the first Pioneer turntable which will accept most precision tone arms by means of a universal-type mounting panel to complete the custom-built component.

The PLC-590's drive system is based on a Hall element, high-torque brushless DC servo motor which reaches true speed within ½ rotation. To maintain rotational accuracy, a quartz crystal element is employed in the reference oscillator together with a PLL circuit.

## Pitch Indicator

When the Quartz Lock Control is switched off, one may adjust the speed by  $\pm 6\%$  and see a direct readout on the illuminated pitch indicator. The adjustment range represents approximately a half-tone interval, enough to "tune" your records with your piano or other musical instruments.

The PLC-590's controls also include a Quick Stop button, which when pushed reverses the polarity of the motor, applying torque in the opposite direction, and bringing the platter to a quick and sure stop. This same circuit comes into use when changing speeds, say from 45 RPM to 33 1/3 RPM, and provides a "quick down" effect not available on ordinary direct-drives.

Specifications on wow and flutter (no more than 0.25% WRMS) and signal-to-noise ratio (75dB) reach and exceed many professional requirements.

In comparison with other Pioneer units, the PLC-590 is rather conservative in appearance; the rrp of \$699.00 seems to be spent on the technology and not trimming.



# Ultimately It's Marantz. Go For It.



If you truly want the best reproduction of musical sound available anywhere — and are willing to spend a little more to get it — then go for it.  
Go for Marantz.

**marantz®**  
We sound better.

FOR BROCHURES WRITE: MARANTZ COMPANY\* P.O. BOX 604, BROOKVALE, N.S.W. 2100. TELEPHONE: 939 1900

Marantz have a superb range of High Fidelity products, including:  
Amplifiers, Receivers, Loudspeaker Systems, Cassette Decks and Turntables.

\*MARANTZ COMPANY IS A TRADING DIVISION OF SUPERSCOPE (AUSTRALASIA) PTY. LTD.

**Hi-Fi & Music** Most of our readers will know that our sister publication (previously) Hi-Fi Review recently changed its title to Hi-Fi & Music: its content being expanded to take in more music material.

The change has apparently been a great success. The July issue is extra-big as it contains the official Consumer Electronics Show catalogue. Also included are test reports on — Technics RS-1500US tape deck; Kenwood L-07C amps; B & W DM7 speakers; JVC's SM3 micro loudspeakers; Shure V15/IV cartridge. There's also a totally fascinating feature on record and tape production plus a special feature for opera lovers on the making of 'Norma'. The issue is on sale until the end of July. If you are in to hi-fi and/or music don't miss this special issue.

**Sansui — New Distributor** A new Melbourne-based company valled Vanfi has been formed to take over marketing and servicing of all Sansui products.

The company is headed by Clarrie Pearce — who has been associated with Sansui for over 12 years. He is backed up by Geoff Brown in Melbourne and Don Oates in Sydney.

There's a huge range of new Sansui products some of which will be seen at the Sydney CES this month.

**Chrome Dioxide Super** Many tape manufacturers claim that the compact cassette system first achieved hi-fi quality with the introduction of chrome dioxide.

Then followed cobalt-doped ferric-oxide cassette tapes with a good output in the lower frequency range but a lower output in the higher frequency range. Anti-chrome campaigns started claiming increased headwear with chromium dioxide compounds. These claims had to be withdrawn, as tests proved that headwear with chrome tapes was often less than experienced with ferric oxides.

Further proof of chrome's characteristics is the video technique, where chrome tapes are replacing cobalt-doped tapes because they no longer meet the high requirements of colour-recording today.

BASF have now introduced a "Chrome Dioxide Super" tape. With this tape the high level control in the area between 10,000 and 20,000 Hz is now up to 6 dB above the values of the "normal" chrome dioxide. Low level control is improved by approximately 2 dB and noise reduced by approximately 1.5 dB.

Manufacturers claim that the tapes surpass the dynamic of a studio tape with a speed of 38 cm/s in the low ranges.

**One-sixth Octave Analyser** White Instruments, manufacturers of audio filters, equalisers and real time analysers have announced a new range of active equalisers.

Features include one-sixth octave resolution from 40 Hz through 894 Hz and one-third octave resolution from 1000 Hz through 15 kHz. The adjustment range is +/- 10 dB using Mil-spec rotary controls. Optional plug-in low-level crossover networks facilitate either bi-amp or tri-amp outputs to the power amplifiers.

The company also offers one-sixth octave real time analysers to be used in conjunction with the new one-sixth octave equalisers.

For further information contact Harman Australia Pty Ltd, PO Box 6, Brookvale, NSW 2100. Tel: 939-2922.

**Record Playing Revolution** A totally new record playing system in which digitally recorded discs are played back via a diode laser is under development by Philips.

The technique is basically similar to that used in Philips' about-to-be-released video-disc system but modified specifically for audio.

The 'Compact Discs' resemble the earliest 78s in that only one side is encoded. Nevertheless the 114 mm discs carry one hour's stereo playing time. As a laser is used to pick the information off the disc there is no need for physical contact between disc and 'stylus' — this allows the disc to be coated with a protective film. The discs will therefore withstand very rough handling without sound degradation.

Philips' new system is scheduled to go on sale in the early 1980s — price is obviously not yet known but Philips hope it will be about the same as a top quality conventional turntable set-up.

**Marantz' New Turntable** A low profile direct-drive turntable has been released by Marantz. Designated 6350Q the unit has phase locked loop servo using a quartz crystal timing reference. Wow and flutter is specified as less than 0.025%.

**Hall-Effect Playback Head** Hitachi's new model D-7500 cassette tape deck uses a Hall effect semi-conductor element instead of the normal inductive pick-up playback head.

# ULTIMATE.

## Philips High Fidelity Laboratories.

In any range of equipment there is a leader. One which sets the standard by which the others are measured.

With Philips Hi-Fi Stereo, the Hi-Fi Laboratories range stands at the very top.

These state-of-the-art Hi-Fi components, which were developed in America, offer precision craftsmanship, technical perfection and outstanding performance.

### High-Fidelity Pre-Amplifier

The AH 572 High-Fidelity Stereo Pre-Amplifier is an ultra-low distortion (0.008%) two-channel unit featuring high-accuracy step detent controls,

illuminated function readouts and touch switches with LED indicators for smooth, silent, sophisticated programming. It also includes adjustable phono input levels and a tape selector that provides five separate tape modes.

### High-Fidelity Stereo AM/FM Tuner

The AH 673 High-Fidelity Stereo AM/FM Tuner incorporates touch switches with LED indicators and illuminated function readouts. Other features include ASNC (Automatic Stereo Noise Cancelling). Separate level controls for AM and FM. An FM interstation disturbance mute. And an exclusive AM centre-tuned meter for wide-band full fidelity AM reproduction.

### High-Fidelity Stereo Power Amplifier

The 210 watts RMS per channel high-performance AH 578 High-Fidelity Stereo Power Amplifier completes the Philips Hi-Fi Laboratories range. It comprises high-accuracy step detent controls, touch switches with LED indicators and illuminated power meters and protection indicators. Also incorporated in the AH 578 are a sub-sonic filter, thermal and overload protection, and provision for connecting two pairs of loudspeaker systems.




**Philips Hi-Fi  
Laboratories Range.**  
A step closer  
to sound perfection.

**PHILIPS**

We want you  
to have the best



# DEEP SPACE COMMUNICATIONS

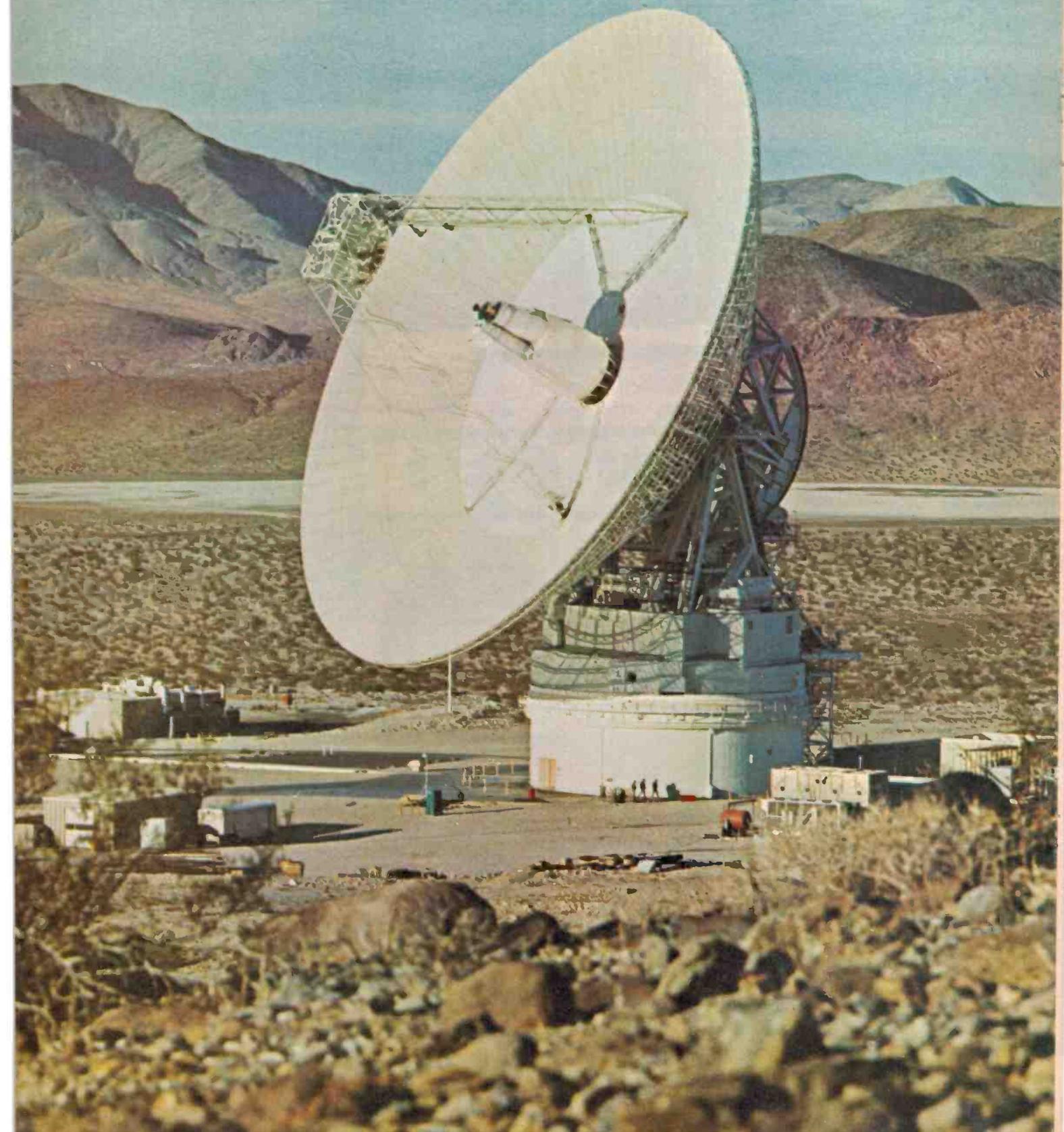

IT IS ONE of the triumphs of modern science that we can establish reliable communications with spacecraft at any point in the solar system provided they are not in the radio shadow of some large object as seen from the earth.

Deep space communications are required for three main purposes:

(i) To track spacecraft velocity and distance. This information is required to calculate trajectory and to compute velocity corrections so that the desired trajectory is obtained.

If a pulse is sent to the spacecraft and the on-board transponder immediately sends a pulse in response, the time delay before this pulse is received on earth is a measure of the distance of the craft. The Doppler frequency shift of this signal is a measure of its velocity to or away from the earth.

(ii) To transmit command or instruct signals to the spacecraft. Such a command signal may, for example, switch on a small jet so as to alter the velocity of the craft or it may cause a television camera to point in a certain direction and transmit a picture or it may switch on a piece of equipment. Many craft have a memory which will store command signals for use at a time when communications are not possible because the craft is behind a planet.

(iii) To send data and television pictures to the earth by telemetry.

During the past twenty years the USA has built up a world-wide network of Deep Space stations for interplanetary communication. This is in almost continuous use and is often receiving signals from quite a number of spacecraft simultaneously.

#### Brief History

The US Deep Space Communications Network is managed for NASA by the Jet Propulsion Laboratory of the California Institute of Technology (at Pasadena). Pioneering work on liquid and solid rocket propellants was carried out on the Pasadena site of the Guggenheim Aeronautical Laboratory as early as the mid-1930's. However, it was the Jet Propulsion Laboratory's work on tracking and data recovery systems for the US army's guided missiles during the early 1950's which resulted in the development of the present Deep Space Network.

The US space programme commenced on 31st January 1958 with the launching of satellite "Explorer 1". This 14 kg spacecraft continued transmitting from earth orbit until 23rd May 1958; it sent data to a three-station network established by the Jet Propulsion Laboratory

incidentally confirming the existence of the Van Allen radiation belts around the earth.

In September 1958, NASA was created by the US Congress for investigating problems for flight within and outside the earth's atmosphere 'for peaceful purposes to the benefit of mankind'. Two months later the control of the Laboratory was transferred from the US Army to the California Institute of Technology.

The Deep Space Network has provided tracking, command and data acquisition facilities for the Ranger, Surveyor and Lunar Orbiter projects for exploration of the moon, for the Mariner missions to Mars, Venus and Mercury and for the Viking missions for orbiting and landing on Mars. It also supported the Manned Space Flight Network and the Apollo lunar landing programme, apart from collecting data from Pioneers 10 and 11 and the Helios 1 and 2 craft which as the name implies were used to explore space close to the sun.

The Deep Space Network will be involved in even more work during the coming years. The current Pioneer mission to Venus involves receiving signals simultaneously from one large probe, three small probes, a 'bus' carrier vehicle and a Venus orbiting craft. The long duration Voyager 1 and 2 missions to the outer planets (Jupiter in 1979, Saturn in 1980/81 and possibly Uranus in January 1986 and Neptune in 1989) will be carried on simultaneously with work with the Viking craft on Mars and orbiting Mars. In addition, communications must be maintained with Pioneers 10 and 11 outside the orbit of Jupiter, support must be given to the West German space communications facilities working with the two Helios craft, and various other demands made by Deep Space Communications. A Jupiter Orbiter Probe is planned for launching by the Space Shuttle in January 1982 for arrival at Jupiter some two years and eight months later.

#### Seeking Life Out There

The Deep Space Network is used for many purposes besides deep space including pulsar and quasar studies. The aerials of this network are ideal for radar mapping the surfaces of the planets and the rings of Saturn. It is intended to use two of the aerials for Search for Extra-Terrestrial Intelligence (SETI) — starting about 1979 over a five year period and covering some 80% of the sky. A search will be made for evidence of radio signals from intelligent

extra-terrestrial life — advanced data processing being used to survey the sky over a million different frequency bands. A companion project to be undertaken by the Ames Research Centre will examine 500 selected stars to ascertain if any planets orbiting them are transmitting signals.


#### The DSN

The American Deep Space Network employs huge high-gain parabolic dish aerials and very low noise receivers at widely separated places at various longitudes around the globe; this ensures that a spacecraft travelling beyond earth orbit is never out of view of all of the Deep Space Network stations unless it is behind a large object as seen from the earth. Thus at least one of the stations can communicate with any craft at any time when it is not in radio shadow.

Deep space Network stations are located in groups at three places, Goldstone, California; at Madrid, Spain; and at Tidbinbilla, near Canberra, Australia. Each of these stations is equipped with a huge 64 m diameter dish aerial and two smaller 26 m aerials. Grouping the stations together saves money and avoids excessive duplication of equipment. All stations are linked by a special ground communications network which is part of the larger "NASCOM" network which provides communications between all of NASA's stations.

The ground communications facilities used by the Deep Space Network include INTELSAT communications satellite links and sub-oceanic cables as well as microwave links. Data received from spacecraft are transmitted over high speed data circuits. Wide bandwidth circuits may carry television pictures of planets and their moons from a Deep Space Network station to the Control Centre at a rate of up to one picture in 48 seconds. In addition, range and velocity information about the spacecraft are transmitted from the receiving station to the Control Centre for navigational purposes. Command signals are sent to the Deep Space Network stations for transmission to the craft. Before transmission they are loaded into a command processing computer which automatically checks them.

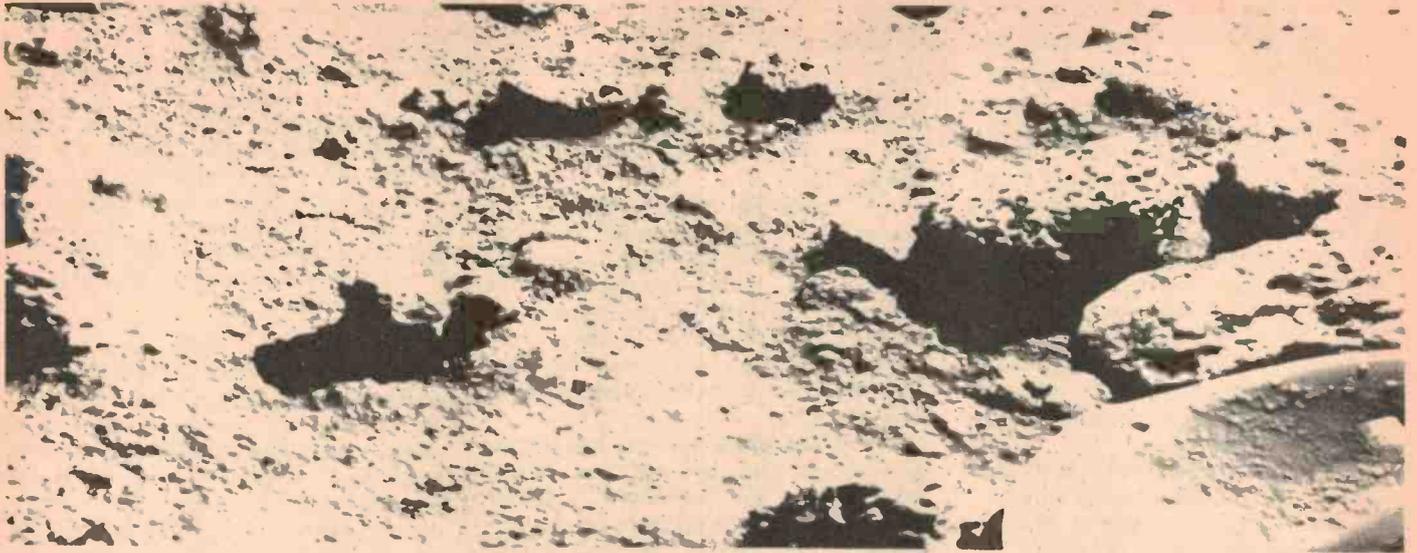The Deep Space Network is not used during the launching phase of a mission. Launches take place from Cape Canaveral, Florida and use the near-earth facilities of the US Air Force Eastern Test Range in the Atlantic together with the down-range elements of the NASA Spaceflight Tracking and Data Network



A view of the Martian surface.

(STDN) at Merritt Island, Florida. Communications ships and instrumented jet aircraft may also be employed during the launching stage. The STDN system is essentially concerned with manned space flights, earth satellites and lunar probes together with the launching phase of any spacecraft; it consists of 16 stations located throughout the world.

The Goddard Space Flight Centre located in Greenbelt, Maryland operates the STDN network and the NASCOM network which links all STDN and DSN stations with control centres. The NASCOM network permits the transmission and reception of written messages, facsimile, voice, telemetry and commands by high speed data lines.

The STDN system provides tracking and communications with the spacecraft during the launching phase, but about the time the launching vehicle is jettisoned and the spacecraft has been put onto its correct trajectory towards the desired planet, the Deep Space Network takes over all communications. It maintains a two-way radio link throughout the remainder of the deep space mission.

#### Frequencies

The standard frequency band used for deep space communications is 2.1 GHz for the up-link from earth to spacecraft and 2.3 GHz for the down-link from spacecraft to earth, these frequencies being in the 'S' band. However, some spacecraft are also equipped with 8.4 GHz (X band) transmitters. Mariner 10 carried a low power X band transmitter not modulated with telemetry, but used with the S band signal for a dual signal for a dual frequency radio experiment. Voyagers 1 and 2 will have both S and X band high power transmitters. The X band down link will be able to send at 115 000 bits/second from

Jupiter, but satisfactory reception at distances of  $6.88 \times 10^8$  km at the first encounter with this planet ( $9.27 \times 10^8$  km at the second encounter) may depend on weather conditions at the earth receiving station. Rain and other forms of precipitation can seriously degrade reception at X band frequencies, affecting the polarization of the signal, etc.

#### Power Levels

The 64 m antenna at Goldstone, California is equipped for radiating power levels up to 400 kW — the Spanish and Australian 64 m aeriels have 100 kW transmitters. Each of six 26 m stations is operated at 20 kW. Klystrons are used to generate the radio frequency power.

The Viking Mars craft use transmitters of about 30 W power output, the power being obtained from sunlight by the use of solar panels. The Viking craft which landed on the planet can transmit either directly to earth or to the orbiting craft which can relay the signal to earth.

The Venus Pioneer craft will use solar panels to provide over 200 W of power and will be equipped with a number of aeriels. The individual probes from the multi-probe craft will be powered by batteries for a short period after they have separated from the main craft and will transmit directly to earth at levels of 10 W to 40 W. However, the data rates will be relatively low owing to the simple aeriels used on these probes. Nevertheless, these data rates should be adequate, since no picture data links are needed.

The Voyager Jupiter craft have to be able to communicate with the earth from enormous distances. The intensity of sunlight is inadequate to provide enough power and therefore plutonium

—238 radioisotope thermoelectric generators will be employed. Each craft has three of these generators which are 584 mm in length and 398 mm in diameter and which weigh 12.1 kg. Each of these three generators provides 155 W initially, about 135 W after five years and about 125 W after 10 years, but only a fraction of this power is available for the transmitter.

The instruments on Voyager require some 99 W. Voyager will be equipped with a 3.7 m diameter dish aerial which will direct the beam towards the earth; this is the largest dish aerial yet built into a spacecraft.


At Jupiter it is expected that the Voyager craft will provide data rates of up to 115200 bits/second when used with a 64 m earth station and about 640 bits/second when used with a 26 m aerial. When the craft are in the vicinity of Saturn, the data rate will be limited to about 30000 bits/second when working with a 64 m aerial and 80 bits/second with a 26 m aerial.

The reason for this is that noise introduces errors. A lower rate enables a narrower bandwidth to be employed and this reduces noise. Errors of about one bit in thirty bits are tolerable for TV pictures, however, errors in command signal transmissions to a craft must be far smaller to avoid the craft being sent on an incorrect trajectory. Typically the error should be less than one bit in 100000 bits — command signal errors can be extremely expensive!

Data rates have greatly increased since Mariner 4 transmitted pictures from Mars at 8.3 bits/second — the increase is about 14000 over a period of ten years.

#### Sixty Four Metre Aeriels

The first of the huge Deep Space Network 64 m aeriels was constructed at

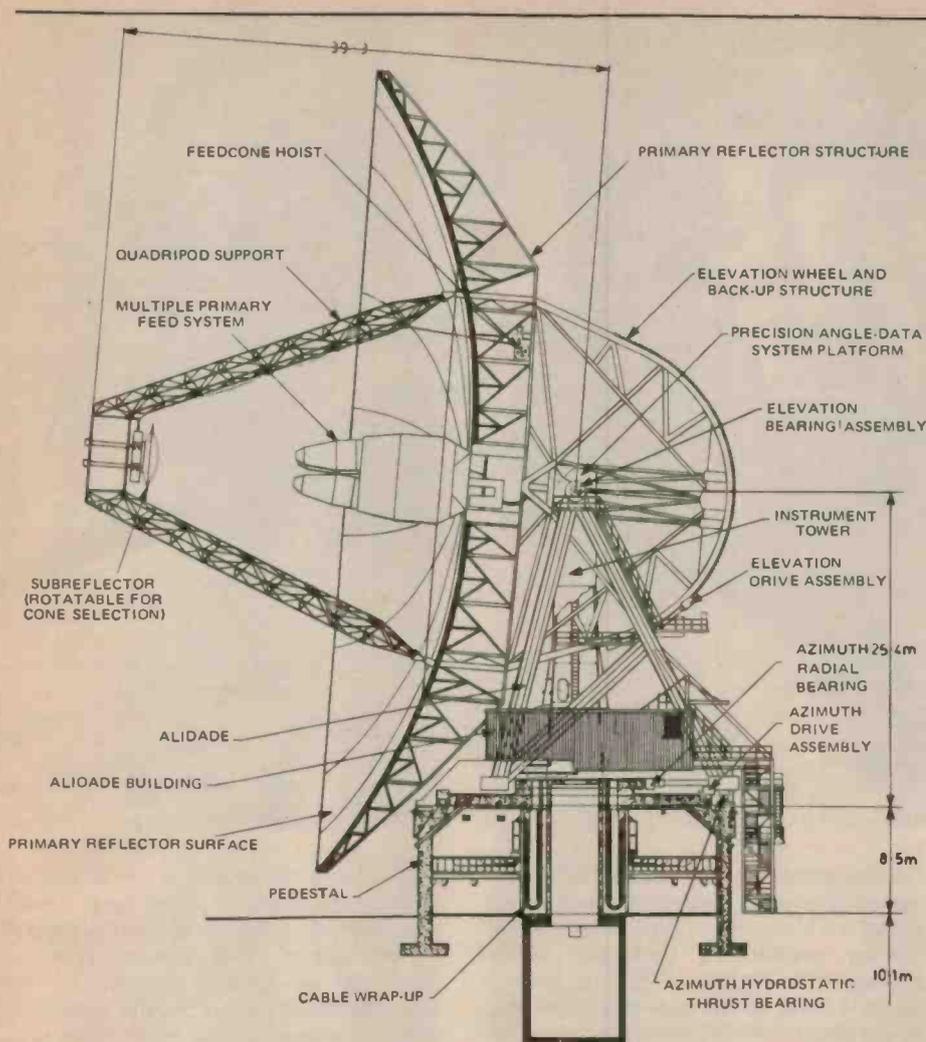

**Table 1: Antenna Dimensions**

|                                                                              |                     |
|------------------------------------------------------------------------------|---------------------|
| Diameter of reflector                                                        | 64 metres           |
| Total height (stowed)                                                        | 73.2 metres         |
| Diameter of sub-reflector                                                    | 6.4 metres          |
| Focal length                                                                 | 27,109 metres       |
| Focal length/diameter ratio                                                  | 0.4235              |
| Surface area                                                                 | 3,483 square metres |
| Depth of reflector                                                           | 9.4 metres          |
| Pedestal wall thickness                                                      | 1.07 metres         |
| Outside diameter of pedestal                                                 | 25.3 metres         |
| Overall height of instrument tower                                           | 42.4 metres         |
| Volume of concrete used in construction                                      | 1,912 cubic metres  |
| Antenna Component Weights:                                                   |                     |
| Overall                                                                      | 7,257,600 kg        |
| On elevation bearings                                                        | 1,147,600 kg        |
| On azimuth bearings (including bearings)                                     | 2,268,000 kg        |
| On soil                                                                      | 7,257,600 kg        |
| Total on azimuth bearings                                                    | 2,268,000 kg        |
| Total on elevation bearings                                                  | 1,134,000 kg        |
| Components:                                                                  |                     |
| Sub-reflector                                                                | 1,860 kg            |
| Feed cone and equipment                                                      | 29,500 kg           |
| Quadripod                                                                    | 17,700 kg           |
| Primary reflector surface                                                    | 26,300 kg           |
| Reflector assembly (including reflector, wheels and elevation counterweight) | 1,075,000 kg        |
| Alidade and buildings                                                        | 997,900 kg          |
| Azimuth bearings                                                             | 181,500 kg          |
| Pedestal and foundations                                                     | 4,536,000 kg        |
| Instrument tower (including wind shield)                                     |                     |
| Steel                                                                        | 43,500 kg           |
| Concrete                                                                     | 422,100 kg          |

Goldstone, California, part of the design being based on the Australian Radio Telescope aerial at Parkes, NSW; the Goldstone aerial became operational in 1967. Some six years later the Australian 64 m aerial at Tidbinbilla (named "Ballima", Aboriginal for "very far away") was brought into regular service, although it assisted with Apollo 17 tracking in 1972.

A 64 m antenna collects over six times the signal power compared with the earlier 26 m diameter aerials — since the area of a 64 m diameter aerial is so much greater. However, other improvements have been made which enable signals of ten times lower intensity to be received than the minimum required by a 26 m aerial.


The signal strength from a distant spacecraft is essentially inversely proportional to the square of the distance of the craft from the earth (inverse square law). If a spacecraft at a certain distance produces a signal which is just adequate to be satisfactorily received by a 26 m aerial, the same spacecraft will produce a satisfactory signal into a 64 m aerial when it is three times farther away. Alternatively a considerably greater data rate can be used with a 64 m aerial than with a 26 m aerial from the same craft at the same distance.

A 64 m diameter aerial is an enormous structure with an overall height of some 73.2 m when the aerial is in the horizontal position. The enormous dish must be contoured to an accuracy of  $\pm 1$  mm even at its edges so that the incoming signals of extremely low intensity are concentrated towards the focus of the huge paraboloidal aerial.

Table 1 shows the enormous weight and dimensions of the Tidbinbilla aerial, but the other two aerials of 64 m diameter in California and Spain are very similar. These enormous structures must be able to operate in winds of at least 80 km/hour and withstand gales of 190 km/hour when the dish is stowed horizontally.

The antenna must be able to point anywhere above the horizon. Motors with a total power of some 300 kW are used to achieve this. The antenna can be directed to any position in space above the horizon with an accuracy of a few thousandths of a degree, yet the huge structure can completely rotate and be moved from horizontal to vertical in about three minutes. The dish must move so that it continues to point at a spacecraft as it moves across our sky despite earth's rotation. Tracking the spacecraft is performed automatically by the station equipment.

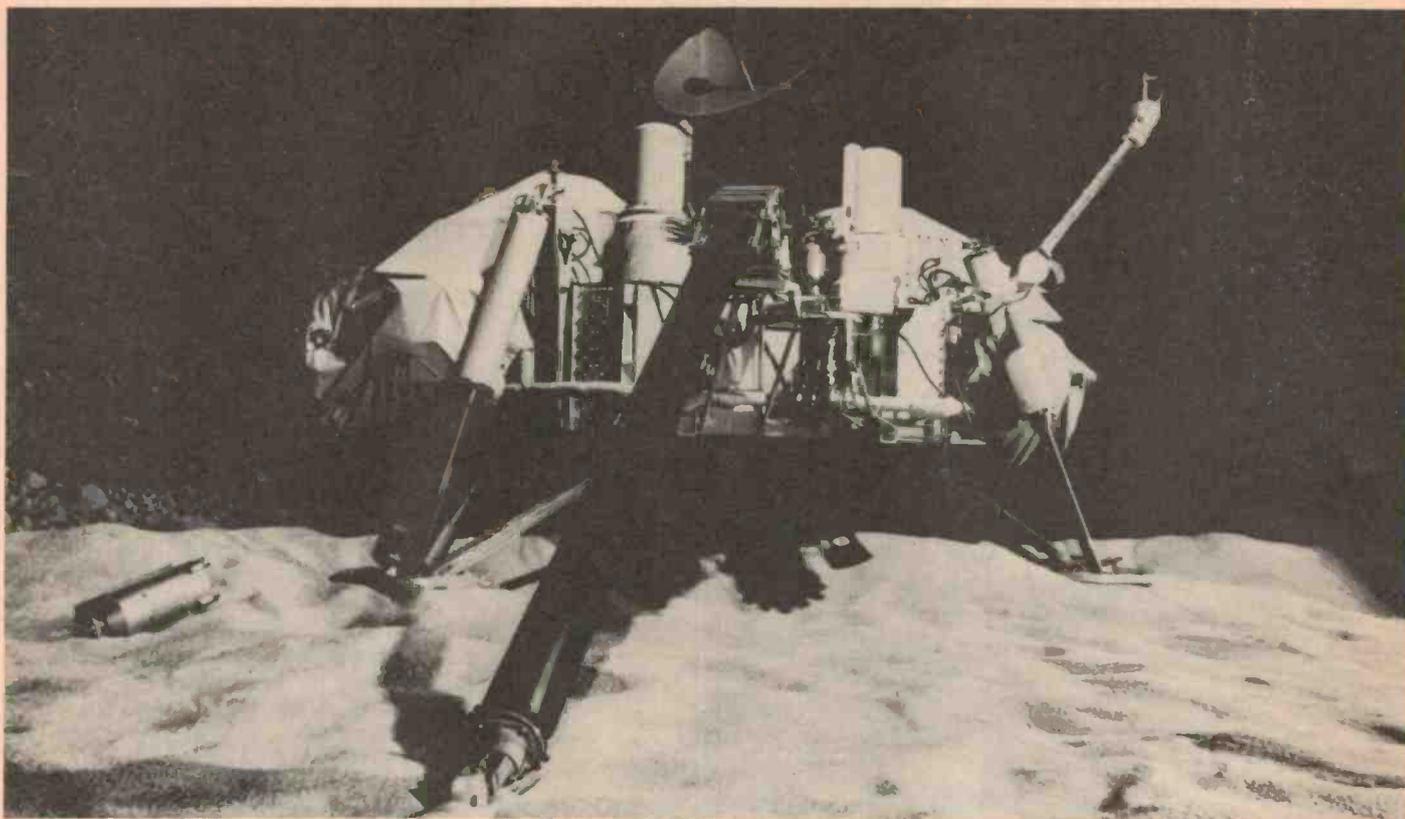Signals can be received as soon as the craft appears above the horizon, since



the aerial can be pointed in precisely the required direction beforehand. However, the establishment of two-way communication takes longer if the craft is at any distance; for example, a signal sent to a spacecraft in the vicinity of Jupiter will take about 45 minutes to arrive (depending on the position of Jupiter relative to the earth) — a further 45 minutes will elapse before any responding signal can be received back at the earth.

The 64 m Tidbinbilla aerial employs Cassegrainian feeds mounted in cones near the centre of the main dish. This type of Cassegrainian feed was first used in optical telescopes. A signal from a distant craft is reflected from the 3480 square metre surface of the main dish which focuses it onto a sub-reflector mounted on a quadripod structure above the main reflector. The sub-reflector can be positioned so that the signal is directed into the feed horn of any one of three cones.

A maser in the feed horn is used to amplify the signal by some 50 dB. The maser is cooled in liquid helium to a temperature of  $-269^{\circ}\text{C}$  — four degrees above absolute zero. This type of amplifier introduces less noise than any other type of amplifying device, but if it were not cooled, thermal motion of the molecules would add a considerable amount of noise to the signal.

The signal from the maser output is then fed to a receiver where it undergoes

further amplification before being converted to a lower frequency signal which is fed to a control station. The control station contains a computer which processes the signal so that it is in a suitable form for recording on tape and, in the case of the Spanish and Australian stations, for transmission by a satellite or sub-oceanic link to the Network Control Centre.

Control room computers at each station also process information and commands for transmission to the spacecraft and extract precise velocity and range information from the received signals for the navigation of the craft.

Apart from the 64 m or 26 m parabolic aerals, each station must have computers, special receivers, analogue and digital processing equipment, black and white and colour television screens, high speed printers able to read engineering data at 80000 characters per minute and communications equipment plus engineering laboratories, offices, canteens and dormitories which enable it to be self-sufficient. It must also have its own power plant to supply all of the station requirements — one cannot lose signal through power failure when one is performing such expensive experiments. Each station must also have an atomic time generator so precise that it is accurate to one second in 3000 years!

#### Future Improvements

In order to improve the facilities of the

Deep Space Network, it is hoped to increase the diameter of at least one of the 26 m diameter aerals to 34 metres by the end of 1978. The construction of a 100 m diameter antenna is also being considered, but as one moves to larger diameter aerals, engineering problems become more and more difficult and expensive relative to the increase in signal strength. The possibility of an orbital relay station in deep space is also being considered. The 64 m aerals give a gain of well over one million.

Time standard improvements could be achieved by replacing the rubidium vapour oscillators with hydrogen masers. Time standards are vital when one is calculating spacecraft trajectories. Very-long-baseline interferometry techniques are being considered for increasing the precision with which the location of each of the Deep Space Network stations is known.

#### Conclusions

The Deep Space Network is a vast engineering project which had to be provided to enable us to obtain information about conditions on other planets and in inter-planetary space. Although most of the work of planetary exploration has been carried out by Americans, Australia has provided a very substantial contribution to this work. There will be an increasing demand on the Network during coming years for higher data rates from more distant planets.

# WE'VE GOT THE ELECTRONIC COMPONENTS YOU REQUIRE NOW



## HEY HEY FEAST YOUR EYES ON ALL THESE KNOBS PLASTIC - BRONZE - ALUMINIUM



K2 Black with silver insert 40c



K2B Black with silver insert 40c



K16 Plain white 13mm long sleeve and clip 30c



K22 Small Aluminium, black centre 40c



K31 14mm high 26mm dia in diamond cut knurling 90c



K32 14mm high 26mm dia black indicator line up side 90c



K33 17mm high 23mm dia black indicator line on top 90c



K38A 12mm high 15mm dia Polished black with silver rim base 80c



K38B 12mm high 19mm dia slightly larger than K38A 80c



K38C 12mm high 22mm dia Larger version K38A 90c



K39 18mm high 15mm dia



K50/ 50A/ 50B  
K51/ 51A/ 51B  
20c each

Exclusive to Davred. All screw fixed to 1/8" diameter shafts and moulded from highly polished shatter resistant thermoplastic.

## BUY NOW BIG SAVINGS

### 10 WATT AMPLIFIER MODULE AND COMPONENTS

This is our kit 51 which includes a 10 watt Sanken Hybrid Amplifier S1-1010G and its ancillary components  
Normally \$11.95  
**LIMITED OFFER \$9.95**



### BREAK BREAK BREAK LOOK C B ACCESSORIES

P L 259 Aerial Plug

Normally \$1.29  
Now 99c

S O 239 Chassis socket

Normally \$1.30  
Now \$1.00

P C 258 Patch Cord/meter

Normally \$4.50  
Now \$3.25



### SEMICONDUCTOR SPECIALS

- BY 164 Bridge 40c
- A 40 D 20AMP Stud \$5.00
- A 40 M 20AMP Stud \$5.00
- JN 60 Diode 10c
- TIP 3055 74c
- TIP 2955 96c
- LM 555 Timer 60c
- LM 556 Timer Dual \$1.75
- LM 714 P O P 55c
- SN 76023N \$2.25
- SN 76001 \$1.15
- LM 301 85c
- BD 140 75c
- BD 139 75c


## RECHARGEABLE BATTERIES

**Noyer Rechargeable**  
Ideal for emergency lighting, alarms, etc.



NP8-6A NPK4.5  
**\$12.65 \$25.30**

| SPECIFICATIONS                                                                     | NP8-6A                                                                                   | NPK4.5-12                                                            |
|------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------|----------------------------------------------------------------------|
| 1. Nominal voltage                                                                 | 6 volts                                                                                  | 12 volts                                                             |
| 2. Nominal capacity 20 hr. rate                                                    | 8.6 A.H.                                                                                 | 4.5 A.H.                                                             |
| 3. Weight (approx.)                                                                | 3.96 pounds (1.8 kg)                                                                     | 2.2 kg                                                               |
| 4. Internal resistance of Charged battery                                          | 30 milliohms (approx.)                                                                   |                                                                      |
| 5. Maximum discharge current with standard terminals                               | 25 amperes                                                                               | 9 amperes                                                            |
| 6. Maximum short-duration discharge current                                        | 300 amperes                                                                              | 90 amperes                                                           |
| 7. Permissible temperatures<br>Charge<br>Discharge<br>Storage                      | 5°F - 113°F (-15°C - 45°C)<br>5°F - 122°F (-15°C - 50°C)<br>-40°F - 140°F (-40°C - 60°C) | Can be operated, charged, or stored in any position without leaking. |
| 8. Charge retention (shelf life) at 88°F (20°C)<br>1 month<br>3 months<br>6 months | 95%<br>90%<br>80%                                                                        |                                                                      |
| 9. Sealed construction                                                             | Can be operated, charged or stored in any position without leakage.                      |                                                                      |

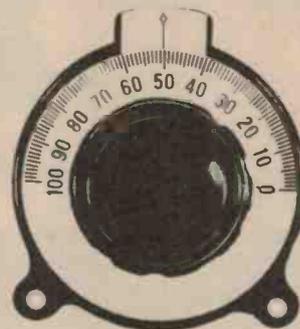

### Vernier Dial

T502 0-100 calibrated with 3.75:1 reduction. Ideal for fine adjustments on pots, tuner condensers, etc.

**Special Price \$4.50**

### LED NUMERICAL DISPLAY

- TIL 312 .3 red \$1.75
- SEL 521 .5 red \$2.75
- SEL 621 .5 green \$3.50
- Cathode Common



# DAVRED ELECTRONICS PTY. LTD.

104-106 King Street Newtown Sydney Australia P.O. Box 317 Newtown, N.S.W. 2042.

THE NEW BREED IN ELECTRONICS SERVICE

Telephone 516-3544

# INCREDIBLE!

DUE MID JULY. RING STORE FIRST!

## 12 VOLT QUARTZ CRYSTAL CLOCK/TIMER/STOPWATCH - WITH ALARM! (OR 24V WITH MODIFICATION TO SUIT TRUCKS, PLANES, ETC.)

LAST YEAR, WE SOLD A SIMILAR MODULE BUT WITHOUT ALARM AND SWITCHES FOR \$32.50!

### JUST LOOK AT THESE FEATURES:

- \* 12 volt operation with quartz crystal - incredible chronometer accuracy. Protected against accidental reverse polarity.
- \* Requires only 3.8mA with readout off - operate for a year off torch batteries. Uses only 79mA (approx) with readout on.
- \* Large fluorescent readout. Can easily be seen in daylight.
- \* No wiring required for standard operation - supplied complete. Just connect the leads to a 12 volt supply.
- \* Ideal for car, boat or aircraft operation.
- \* 12 hour operation - can be converted to 24 hour operation (requires one resistor).
- \* Audible alarm supplied - bells, lights, etc can be controlled by adding a relay.
- \* Seconds can be displayed by adding a simple switch (instructions supplied).
- \* Seconds count can be zeroed to allow for stop watch type operation. Ideal for boat races and auto rallies.
- \* Power failure indication - tells you if clock was turned off.
- \* Can be operated off AC power with a 12 volt adaptor.
- \* Accurate to one tenth of a second per day!

QUARTZ CRYSTAL FOR INCREDIBLE ACCURACY

ELECTRONIC ALARM UNIT

SWITCH ALLOWS SETTING OF TIME AND STOP WATCH

BAR INDICATOR SHOWS AM OR PM IN 12 HOUR MODE

CONNECTIONS FOR 12 VOLTS (+ & -) AND DISPLAY ON/OFF

LARGE-SCALE INTEGRATED CIRCUIT CONTAINS OVER 1000 TRANSISTORS

SWITCH ALLOWS ALARM FUNCTIONS

COMES WITH A SIMPLE, YET HIGHLY DETAILED 4 PAGE INSTRUCTION MANUAL SHOWING CIRCUITS FOR TIMERS, ALARMS, RELAY SWITCHING, STOP WATCHES, POWER SUPPLY INFORMATION, 24 HOUR AND SECONDS DISPLAY DETAILS, ETC.

**ONLY \$19.50**  
MODULE ONLY.  
Cat X-1045

## SPECIAL OFFER

The above clock module, complete with attractive case, front panel bezel and mounting bracket. Ideal for mounting on the dashboard of your car, truck, plane or boat. Ready to go - simply connect to power!

**\$24.50**

Cat X-1047



POST AND PACK ON EITHER ITEM \$2.00 EXTRA.

## DICK SMITH ELECTRONICS



SHOPS OPEN 9AM to 5.30PM  
(Saturday 9AM - 12 noon)  
BRISBANE 1/2 Hour earlier.

Many lines available from the Dick Smith Electronics Centres at

**GRACE BROS**

Broadway • Bondi Junction • Chatswood  
Liverpool • Miranda Fair • Mt Druitt •  
Parramatta • Roselands • Warringah Mall



**SYDNEY** 125 York Street, SYDNEY. Ph. 29 1126

147 Hume Hwy, CHULLORA. Ph. 642-8922

162 Pacific Hwy, GORE HILL. Ph. 439-5311

30 Grose Street, PARRAMATTA. Ph. 683 1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67 9834

656 Bridge Road, RICHMOND. Ph. 42-1614

166 Logan Road, BURANDA. Ph. 381-6233

**BRISBANE** 203 Wright Street, ADELAIDE. Ph. 212-1962

**ADELAIDE**

**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and pack extra.

Dealers across Australia.

# The world's best cartridge?



## Stanton 881-S

"Quite simply, it rendered the best tracking performance we have seen to date. Sound quality of the Stanton 881-S is neutral. It does not sound spectacular — one forgets about the cartridge when it is playing. When you come right down to the nitty-gritty, there can be no better comment than that."

"Electronics Australia", January, 1978.

"There is more detail at all frequencies, and stereo images have exceptional stability, even in complex, high level passages. There is also less tendency to become fatiguing, with an absence of the 'grittiness' that afflicts more modest cartridges to a greater or lesser extent".

"Hi-Fi Buyer's Guide", September, 1977.

"This is not a cartridge for the showman; it is a cartridge for the music lover, for the purist."

"Stereo Magazine", Winter 1978.

"This is one of the most neutral and uncoloured cartridges we have listened to. It sounds as flat as its frequency response curve implies and has an impressive freedom from audible tracking distortions of any kind. It provided a revelation when listening to some of our older, well-worn discs, providing a freshness in their sound that we had not suspected was there."

"Popular Electronics", December, 1977.

"In general, the sound of the Stanton 881-S is completely neutral. It injects no coloration, emphasis, or de-emphasis into any part of the frequency spectrum, and it has a notable freedom from audible tracking distortions of any kind. Since it is so easy to forget that there is a cartridge in the reproducing chain, this is the kind of cartridge we prefer to use when listening to records for musical enjoyment, rather than as a means to uncover flaws in cartridge performance."

"Stereo Review", November, 1977.

"Records heard via the Stanton sound bright, clear, and detailed with an especially smooth high end. Sharp, quick transients, such as those found on direct-cut discs from Telarc, Sheffield, and Umbrella are taken in stride and reproduced with a stunning sense of presence. The stereo image is vivid, plausible, and stable. In the short time that we have known the pickup it has become one of our favourites."

"High Fidelity", October, 1977.



STANTON

And remember, you can't get the best out of your Stanton Cartridge unless you use a genuine Stanton Stylus.

Sole Australian Distributors

**LEROYA INDUSTRIES PTY**

Head Office, W.A.: 156 Railway Pde., Leederville 6007. Phone 381 2930.

N.S.W. Office: 100 Walker St., North Sydney 2060. Phone 922 4037.

VICTORIA Office: 103 Pelham St., Carlton 3053. Phone 347 7620.

# Robots—the facts

Robots may take many forms. They are not necessarily Artoo-detoo like machines.

An automated washing machine for example can be seen as one form of simple robot as can the Strasborg clock made way back in 1354 — this contains a cock which moves, stretches and crows.

Here ETI's special correspondent Associate Professor Peter Sydenham, M.E., Ph.D., F.Inst.M.C., F.I.I.C.A., M.I.E.Aust presents the basic facts and analyses the many separate requirements common to robotics.

## TERMS

**Robot** — In Gothic it is akin to a word meaning "inheritance", in German to "work". An old Slavic word that is equivalent is "rabota" and in Czech and Polish "robota" means servitude or forced labour. Professor George's book (see list) says it is "a machine devised to function in place of a living agent".

**Robotics** — Gaining rapid acceptance, this term describes the discipline that designs and creates robot device structures and sub-assemblies. The following word is reserved for its system organisation.

**Cybernetics** — Study of multiple feedback loop, self-governing systems, usually of great complexity, as are found in living organisms and advanced man-made control systems.

**Automaton** — Any device that has apparently spontaneous action. (Plural is automata).

**Humanoid** — Robot form of man.

**Android** — Automaton of man-like form.

**Homunculus** — Inferior robot form of man.

**Prosthesis** — Man-made, human body replacement parts.


**Exoskeleton** — Robot frame that fits around human to give power to limbs.

**Golem** — Man-made creature not having man-like form.

**Manipulator** — Handling device.

**Telechiric** — Derived from Greek for "distant hand".

IN THE first half of the 17th century Descartes suggested that the physiological animal can be thought of as no more than a vastly complex machine. Intolerance of ideas, especially those that had religious implications, was extreme in those times and no doubt Descartes only spoke and wrote a little of his concept. Pascal, for example, was dangerously close to being the subject of a witch hunt after people saw his simple

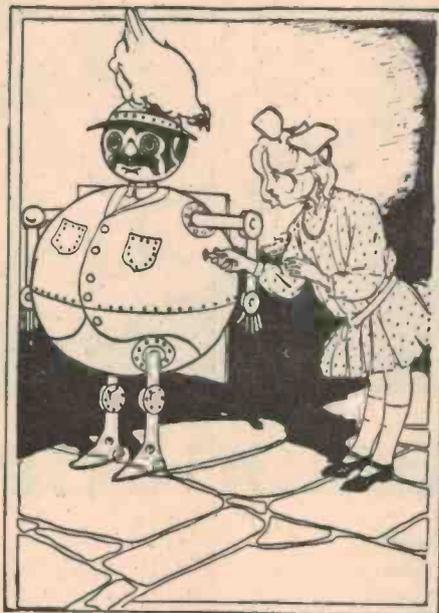

(to us!) add-and-subtract calculator — after all, it could do the tasks attributed then to a god.

The idea that animals are merely machines is known as the reductionist or mechanistic philosophy. As we cannot prove, by any means whatsoever, that there is more to man than man can ultimately devise, we cannot, at present, resolve this issue.

Nevertheless, there is much about animal systems that is reducible to plain engineering. It is these known facts that suggest that many jobs that were considered as man-suitable in the past could well be done by machines. The justification is, to use a well-known quotation, "to make human use of human beings". If an automaton can do the same tediously repetitive task that is done now by a bored and dehumanised human operator, then there is a case to make use of it. This is the story of man's industrialisation, especially since the 18th century.

The human animal is a fine example of a general-purpose, mobile, self-repairing, self-reproducing machine, one that can adapt to new tasks and new environments as need arises. It is not perfect for all jobs, but does provide a fine basis for modelling robots of work, even though the materials and strategies used are different in practice.

Animals can be thought of as hardware systems, consisting of several kinds of sub-systems put together to form the whole system. The complete system is capable of many modes of behaviour. A diagrammatic representation is given in Fig. 2. Let us look at the building blocks first.

**Structural framework** — This is the mechanical part holding everything together. Bones, skin, tissues can be equated to metal, wood or plastic frames. The framework is developed to satisfy, as a compromise, requirements of lightness, rigidity, appropriate articulation, protection for vital parts, and correct location of one part with respect to another. Note that robot machines do not use the same materials that are found in animal systems. To date it has been more profitable to use quite different substances because man knows too little about the production of regenerative, self-repairing materials used by nature.

**Actuators** — On to the frames are added converters that change the available energy form into mechanical work. On animals these are the muscles; on robots they are usually electric, hydraulic or pneumatic motors. Again, although muscle-like devices have been made, robot actuators use different principles of conversion and different energy sources from animals. Actuators cause limbs to move, hands to hold, and the whole to translate where needed.

**Sensors** — Automata that, for instance, play music, are pre-programmed. Regardless of external influences, once set going, they will attempt to keep playing despite changes to their en-

vironment. Robots can be much more sophisticated for they possess sensors, or receptors, that observe what is happening around and to the robot. Sensors provide signals that, after data processing, tell the actuators how and when to work in a way that modifies an otherwise hardwired kind of performance.

It seems that many animal senses work on the basis of having a multitude of on-off digital sensors built into each sensing device, the combined, parallel, signal output being a measure of sensor signal strength. Robot sensors rarely work this way for we are unable to handle as many parallel channels as nature. Robots usually incorporate

especially if one sticks to industrially marketed units in order to keep costs low.

**Data Processing Centre** — Signals from sensors are routed to data processing (DP) centres. The brain is the central unit of humans. Not all animals have only one brain. Some early prehistoric animals are believed to have had two brain centres. Signal pre-processing goes on in animals before a stimulus reaches the brain. This can also be the case in robots. Robots can have local brain-power plus a central unit.

We cannot make much of a comparison between DP of robots and animals, for we still have only a meagre idea of how the physiological brain

can make use of Nature's concepts but not her hardware methods.

**Energy Supply** — Animals derive energy from the conversion of foodstuffs into energy by chemical means in muscular tissue. Robots cannot do it this way, but make use of the sources known to man at this time. Electricity can be generated by converting fuel to electric current. In mobiles a usual source of energy is electricity from storage cells. Restricted mobility and fixed robots can obtain power by an umbilical supply cable. Hydraulic and pneumatic systems derive energy from their compressor unit — the lines act as energy transmission links to the converter unit.



Fig. 1. Projects of the Warwick University Robot Laboratory. Project on the left uses an inboard microprocessor. At the rear is a hand-like short arm manipulator. The tracked vehicle is originally

sold as the army bomb-disposal unit — it acts as a ready made vehicle to conduct research on. (Keystone Press Agency).

analogue output sensors — the so-called linear signal in integrated circuit jargon. To detect the seat of a fire, an automatic fire extinguisher will use a proportional signal infra-red detector homing the robot towards the position of maximum signal output. In some cases man-made robots do use digital output sensors but not so commonly as analogue ones. An example might be a digital shaft encoder sensor mounted to measure an arm's angular position.

We cannot measure every variable that arises in the material world. Even so, literally thousands upon thousands of sensors have been devised so the robot designer of modern times can go a long way with what exists already,

operates. Insight that we do have is enough to say that robot brains will be quite different in physical structure from animal brains. We tend to opt for non-redundant data processing methods using a limited number of binary locations. The brain appears to make use of massive redundancy and enormous bit storage capacity ( $10^{20}$  is an estimate).

**Communication Links** — Sensors feed signals to actuators via DP centres. The links we know and use in automatic machines are electric wires, optical fibres, air and oil tubes. Nature, however, uses the nerve links in which pulse signals are regenerated in mysterious ways by electrochemical methods. We

Robots that perform work will be somewhat inefficient for all energy systems will have losses. The human system consumes around 100 W at a rest condition (of which most is lost as heat) and can provide about three times this power as work for limited periods. This would, by implication, suggest that a robot doing the full tasks of a man needs a 400 W supply capability.

The man machine looks quite puny: 400 W is not exactly powerful. Robots are not so limited. For a start, a man begins to tire after a few hours at 200 W output — a machine equivalent can go on tirelessly. Robot manipulators can provide whatever power level is

desired. They are made to lift huge loads. An example is a framework that a man fits into, giving him arms that follow his own with greatly increased load capability.

**Motivational Mode** — There must be some inbuilt means to ensure that the robot constantly goes about the business for which it was created. This mode is temporarily given lower priority when circumstances dictate. As a simple example, a mobile designed to cut the grass of a lawn may need to divert its attention from grass cutting toward a battery recharge. After charge it must return to its duty.

**Survival Mode** — The programming basics must incorporate means to put the robot into behaviour modes that reduce and, hopefully, eliminate damage to the robot. The lawn cutter must

cause the robot to go and look for a task. In animals this is seen as inquisitiveness. Without it humans are referred to as lazy and unmotivated — as would appear a robot.

**Maintenance and Self-repair** — The good robot is one that does not deteriorate in performance. This is not a reality, however, for although wear rates of mechanical implements can be reduced by better design and more expenditure, it usually can only be done at greatly increased cost. It is to be expected that robots, at least for many years yet, will require greasing, bearing replacement and sliding surface repair.

The first thing the robot will need to do in this mode is diagnose its own troubles, deciding what repair action is to be taken. Then it must organise some way to replace parts. This mode is probably

(3) A robot must protect its own existence as long as such protection does not conflict with the First and Second Laws.

Asimov never intended the laws to be the one and only guide to robot designers — far from it, they were the result of science-fiction writing. They are not foolproof and do not extend to all situations, but do remind us of some basic ideals to consider in programming a robot's behaviour pattern.

### Programming the robot

A fully determined robot performance, that is, one that will obey instructions that are all preset before it begins to work, is little better than a special-purpose machine. It cannot do other than what is expected by its programmer. This basic level of performance is required

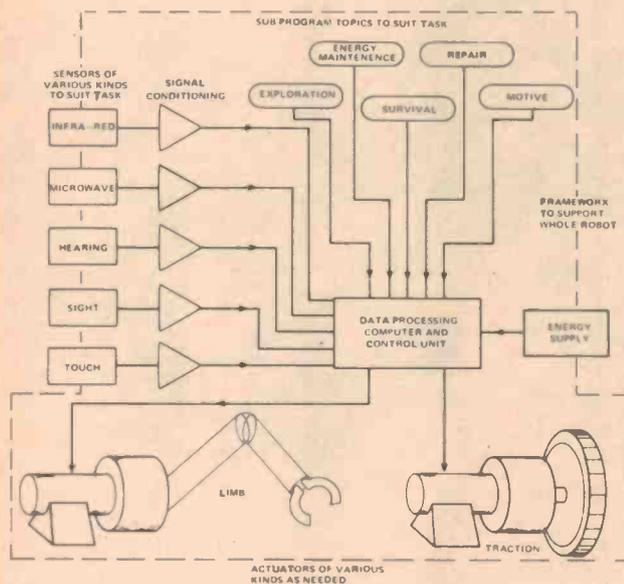


Fig. 2. Robot systems are made up from sensors, actuators and data processing systems operating together to satisfy a number of operational requirements.

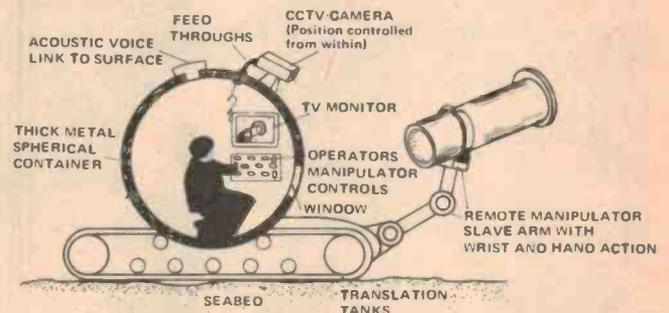


Fig. 3. Underwater a robot manipulator provides an operator with an effective ecoskin and increased ability to do work.

recognise that the concrete edging or stray stone must not be brought into contact with its blades. The survival mode must also extend to preventing the robot doing damage to its environment.

**Energy Maintenance Mode** — As well as the obvious need for the robot to ensure that it has power enough available for instantaneous load, it should also be able to prepare an energy budget of near future need. If it is a battery-fed mobile, it may find itself out of energy before it can return to the recharge point.

**Exploratory Mode** — Robots can have greater than one purpose. Such purposes may not exist all of the time and all in one place. When no purposeful sensor signals are received, actuators should be set by a sub-program to

more idealistic than real for most robots at present, but the software programmer and robot designer must, at least, give some consideration to this need.

### Robots and people

In 1942 Isaac Asimov put into words three laws of robotics that have become famous in this field. They refer to the relationship between robots and people that designers should bear in mind for obvious reasons. The laws are:

- (1) A robot may not injure a human being or, through inaction, allow a human being to come to harm.
- (2) A robot must obey the orders given it by human beings except where such orders would conflict with the First Law.

of many robots, but is not the complete capability. It might be preset by a punched-tape or magnetic tape in the same way as are many domestic knitting machines. Most manipulator robots get these instructions via an initial man-operated run using special controls that allow the operator to run the manipulator through the required manipulative routine. Once done it becomes a stored program routine.

Far better, if possible, is to servo the output required according to inputs of error. For example, to put a pin in a hole is better done by viewing the error between the pin and hole, reducing the error to zero, rather than pre-setting an arm to put a pin where the hole is expected to be.

The latter open-loop method assumes that all relative positions of limbs of the

robot are held within the final tolerances needed to put the pin into the hole — which are extremely tight limits in many cases. The former method makes use of feedback and it is a feature of servo systems that actuation components inside the loop can be reasonably inferior in quality. This is a most important system concept — think of the problem of finding a place on a map by dead reckoning from a set of distances and bearings, as opposed to improving one's situation as one goes by recognition of error still existing.

### Recent robots

Many authors on robotics include mention of a wide variety of inter-disciplinary automatic devices. This broadens the subject enormously and is a quite reasonable thing to do for robots can

by the 1950s. Studies of adaptive control, self-organising systems, AI and a new discipline called cybernetics were developing rapidly — research workers became very optimistic that machines would soon be able to design better machines. But they found over the successive years that it was not so easy!

Cybernetics was the term popularised by Norbert Wiener in 1947 for the discipline covering self-governing systems of all kind, seeing them basically as all the same thing, regardless of application. The term is derived from the Greek and means the art of steersmanship. It is of interest to include the fact that Ampere had previously used the term to describe the science of government.

Theory of automata became an established pursuit a little later. Pattern recognition was another related area

rated on seeing what could be learnt from biological systems — maybe this was not so fruitful considering that designers have to work with different materials than nature uses. Then came the mini computer, almost small enough to build into a reasonable size robot device. Costs at first were prohibitive. Computing power and speed were very limited for operating robots at the motional speeds and precisions needed. Today we now have the quite cheap micro-processor, where the larger part of its sale price is for market promotion, mechanical packaging and application notes.

### Before time

Advanced ideas usually meet opposition in a society. Bruno was burnt at the stake in the 1500s for suggesting astron-

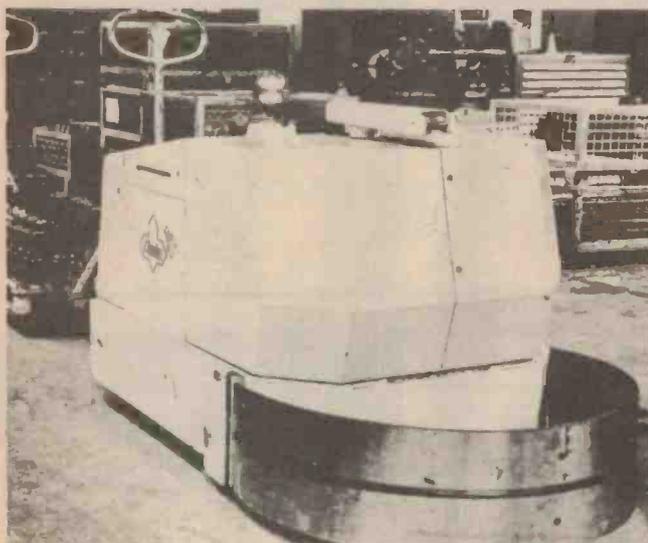


Fig. 4. The Ameise Teletrak driverless tractor train guides itself to follow a guide-wire set into the floor. One day it may be economic to provide the robot with navigational ability that compares with that of humans.

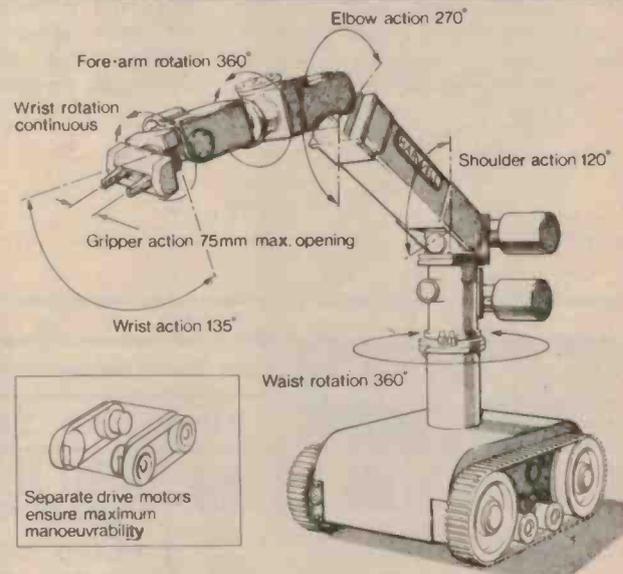


Fig. 5. ROMAN, a recent Harwell mobile, is made for use in hazardous industrial situations. It is electrically powered using cable control.

take any form. For reasons of space, we restrict ourselves here to mobiles and manipulators.

It is said that the term "robot" gained public acceptance as the result of a 1923 play by Karel Capek. It was at that time in history that ideas about automation began to flourish in earnest because of the favourable technological atmosphere. Electronic amplification was just available, mass production of consumer goods was established, sophisticated industrial control was emergent at a seat-of-the-pants level (theoretical considerations came later in the late 1940s).

Electrical computation began in the late 1930s, resulting in the first working vacuum tube system in the 1940s. Computer research no doubt stimulated interest in artificial intelligence (AI for short). Things were really happening

that became fashionable to work on. By the early 1970s the realisation that these ideas would not blossom so quickly, if ever, to give regenerative machines and robots replacing men in all their faculties, was accepted. Such goals are now seen to be much further away.

Today, the past efforts of many people have been tidied up, extended, ignored and much has been weeded out as irrelevant or false, leaving today's robot designers with a very useful and full theoretical and practical background to work from.

Mechanical design aspects of robots have advanced through work in prosthesis, in nuclear materials handling, in a relatively few academic engineering departments and within a small number of industrial groups.

Data processing for robotics concent-

omical theory was wrong. Pascal nearly went the same way for making his adding machine. Even Ohm had his simple law of the 1830s opposed by men of learning. The road car was held up in development for over 60 years by the need to walk in front of a vehicle with a red flag. Fear, preservation of the status quo, misplaced motives, politics and the natural and more healthy need for cautious acceptance usually emerge before a new concept finds acceptance.

So it has been with robots. Science fiction writers paint both gloomy and happy scenarios with robots. We tend to remember only the former. Robots are merely machines of greater capability and versatility than man has made to date. As with all of man's technology, he has to learn to use them appropriately. We should not fear the robot but

look deeply into its value to us.

Returning to earth from the levels of philosophy, it is quite certain that the robots we build over the next decade will not challenge our existence. We know too little at this time to build them with such powers. There are, however, numerous requirements where robot devices can replace men performing tasks too hazardous for men to do. Machines are the extension of man on earth and no force is likely to stop man's use of tools which has been part of his culture from the very beginning.

### University research

Robots of the future will make use of techniques discovered and developed in research groups working on artificial intelligence, robotics, computing science, electronics, plus many more areas.

The Science Research Council of Britain supports robot research. The main laboratory of the Robot group at Warwick University is shown in Fig. 1. In the same room is the computer ter-

minial to which the four projects shown are hooked-up to give them significant data processing ability. Around the walls are placed acoustic transducers used in positioning work.

A group at Edinburgh University works on putting artificial intelligence into robot devices. They have built a servo-controlled, computer-based, handling system.

A prime purpose of University research is to seek better ways to achieve goals. Theirs is not really a task of building devices that are totally engineered. For this reason one seldom sees a finished robot but more units in stages of change.

Never before has the field of robotics been so ready for development. Simple robots with quite sophisticated brainpower are in the price range of the non-professional. Amateurs can now enter the field knowing that the capability of their effort made now will be improved as efficient and powerful strategies are transferred to the general

public domain at low cost via mass-produced integrated circuitry and software packages. A good comparison is seen by remembering that visual display units that write words were wonders of the time ten years ago. Now the equipment is reasonably standardized, far more advanced and within the price range and building capabilities of many teenagers.

### Organisations

British Robot Association  
Secretary, Dr. M. Larcombe, Robot Laboratory, Department of Computer Science, University of Warwick, Coventry, U.K. (A professional body with leading manufacturing companies as members.)

Robot Institute of America  
20501 Ford Road, Dearborn, Michigan 48128, U.S.A. (This professional U.S. body has recently inaugurated a medal — the RIA Joseph G. Engleberger Award — for individual outstanding contributions to the science and practice of robotics.)



**EMONA**  
enterprises

Room 208/661 George Street, Sydney Phone: 212-4815

P.O. Box 188, COOGEE, NSW. 2034.

**FOR PROMPT MAIL  
ORDER SERVICE!**

## THE ULTRASLIM NS108

from National Semiconductor Ultraslim (7.5 mm thin) LCD Scientific Calculator!

### NS 108 FEATURES

Full 10-digit mantissa or 8-digit mantissa and 2-digit exponent plus sign. Display prompting alpha characters below the mantissa signal the calculator mode: "X10", "DEG", "RAD", or "GRAD"; "HYP" mode; "and" "out"; "P" or "2nd" indicates secondary function; Direct access accumulating memory: M, M-, MR, Memory store, Memory-Display exchange; Two levels of parenthesis; Trig and log functions, inverse trig and log, hyp functions; Algebraic logic; Statistical functions: three accessible, accumulating memories for summations; Sum X, X2, and n; Calculates mean and standard deviation, adding to and subtracting from the summations at will; Separate keys for permutations and combination calculations; Mode selection in degrees, radians, or grads; Rectangular/polar coordinates; Degrees, minutes, seconds; Square, square root and factorial X!; Reciprocals, powers, and roots; Integer/fraction isolation; Degree, radian, grad conversion. Complete with vinyl billfold style carrying case and 3 silver oxide batteries.



**\$47.00**

ALSO:  
NS201R, Scientific — \$26.85  
NS202R, Financier — \$29.84  
NS203R, Business — \$22.38

## NEW! TI-PROGRAMMER FROM TEXAS INSTRUMENTS HEXADECIMAL AND OCTAL CALCULATOR/CONVERTER FOR PROGRAMMERS.

**Number base conversions:** Enter a number base in 8, 10 or 16. Then with a touch of a key, that number is quickly and accurately converted to either of the other number bases.

**Number base calculations:** Quickly handles arithmetic computations in all 3 bases. Immediate answers to binary computer problems.

**Ideal for use with any size computer:** Gives you 8-digit capacity in all bases capability to handle even IBM 370 problems with ease.

**Versatile three key memory:** Lets you store, recall or sum to memory contents. Parentheses provide the capability to specify the order of operation execution in a problem — with up to 4 pending operations.

**TI Programmer can be a real time saver:** Does away with conversion tables and tedious longhand methods.



**ONLY \$53**

with vinyl carrying case, fast charge battery pack and AC adapter/charger.

## PROGRAMMABLE CALCULATORS:

TI-59 — \$262.00 | TI-57 \$74.00  
TI-58 — \$114.00 | TI-55 — \$56.00

PROFESSIONAL RANGE: SR-40 Scientific, \$32. T1-30SP Student Math Kid, \$20. MBA-Business, Financial & Programmability, \$76. T1-MM, Money Manager, \$21. T1-BA, Business Analyst, \$33. PC-100A, Thermal Printer, \$222.

BMC-LCD-BW Pocket Calculator, with clock & alarm — see May ETI, \$48. BMC-LCD-8M Billfold, \$23. BMC-1212PD 12 digit display and printer, \$125.

Also available: A full range of National Semiconductor, Fairchild & Unik Time watches, digital clocks & digital clock radios, micro cassette recorders, etc.

**NOTE:** To all calculator prices add 15 percent ST — if applicable. P&P — Int. \$3, NSW \$2 (up to \$50 value). Int. \$4, NSW \$3 (up to \$100 value). Goods valued over \$100 delivered by courier — freight paid by receiver.

**WRITE, PHONE or CALL IN!**

# hi-fi and music

JULY 1978 \$1.40\*

CE SHOW  
SPECIAL

Equipment - 5 Reviews

Portrait of a  
Recording Company

**ON SALE NOW**

• more  
music

\$1.40 at your newsagent

• more  
features

• more  
equipment  
reviews

The Making of Norma

# You'd be surprised where you're going to find us next

Silicon Valley — the retail division of Cema Electronics Pty. Ltd. recently released a Merchandising Stand so that dealers could participate in the fast growing business of electronic components, semi-conductors and do-it-yourself computer building.

These Merchandising Stands have been designed for location in electrical stores, radio and T.V. shops, specialist electronic stores, supermarkets, etc.,

Be a part of this rapidly expanding industry. Contact Silicon Valley and find out details on how you can make extra cash from the electronic components business.

Join our team of profit making stores.

#### SYDNEY:

Silicon Valley. Shop 4, P.O. Arcade, Joyce Street,  
Pendle Hill. Tel: (02) 636 6566  
Pre-pak Electronics. 718 Parramatta Road,  
Croydon. Tel: (02) 797 6144  
Martin De-Launay. Cnr. Druitt and Clarence Street,  
Sydney. Tel: (02) 29 5834  
In-Electronics. 86 Ramsey Street, Haberfield.  
Tel: (02) 799 3331  
Kit-Sets. 657 Pittwater Road, Dee Why.  
Tel: (02) 982 7500  
Silicon Valley. 23 Chandos Street, St. Leonards.  
Tel: (02) 439 2965.

#### WOLLONGONG:

Martin De-Launay. 270 Keira Street, Wollongong.  
Tel: (042) 28 6020

#### NEWCASTLE:

Martin De-Launay. Cnr. King and Darby Streets,  
Newcastle. Tel: (049) 2 4741

#### CANBERRA:

Daicom. 29 Colbee Court, Philip. Tel: (062) 82 3581

#### BRISBANE:

Kit Sets. 293 St. Pauls Terrace, Fortitude Valley.  
Tel: (07) 52 8391

#### MELBOURNE:

Rod Irving Electronics. 499 High Street, Northcote.  
Tel: (03) 489 8131  
Steward Electronics. 240b Huntingdon Road,  
Huntingdale. Tel: (03) 543 3910  
South West Electronics. 119 Hopkins Street,  
Footscray. Tel: (03) 689 3819  
Ellistronics. 298 Latrobe Street, Melbourne.  
Tel: (03) 602 3282  
Silicon Valley. 380 Bridge Road, Richmond.  
Tel: (03) 429 4780

#### ADELAIDE:

Silicon Valley. 170 Sturt Street, Adelaide.  
Tel: (08) 51 4080  
Ktronics. Peel Street, Adelaide. Tel: (08) 212 5505

#### PERTH:

Atkins Carlyle. 1-9 Milligan Street, Perth.  
Tel: (09) 321 0101

I require full details on: —  
The Silicon Valley Merchandising Stand   
Silicon Valley complete mail price list   
Silicon Valley mail information service

Name .....

Address .....

..... P/Code .....

Telephone No. ....

Post to Silicon Valley, P.O. Box 898, CROWS NEST, N.S.W. 2065

**silicon valley**

# Robots - brain power

Robots have logic systems that make them think they think! Dr. Michael Larcombe of Warwick University's Robot Laboratory explains.

ROBOTS do not have brains. 'Wet logic' technology - brains to you - is many orders more complex than the world's most complex machine (which is probably the International Telephone system, not any supercomputer). Robots are however extremely bright - for machines. They are much smarter than computers - which suffer from the so-called GIGO syndrome (Garbage In, Garbage Out). Unlike the dumb computer they answer back - ask a smart robot to walk through the wall and you will get the robot equivalent of a flea in the ear. Give them an unreasonable task and they will either (a) refuse to do it, (b) try to do it for a while and then

give up, (c) have a seizure (badly designed robots only - as we do not yet really know what makes a good design, this means most of them).

## Through a robot's eyes . . .

It is easy to be patronising while watching a robot at work - especially as their vision is either poor or non-existent. A few minutes attempting to perform the same task using the same robot body under remote control and using the robot's own sensors soon convinces the human that the robot itself is best qualified to control its body. Without direct visual feedback remote control becomes exceedingly difficult. When dealing with feedback from non-human sensors such as sonar or doppler radar it is virtually impos-

sible. In its own sensory environment the robot is a master of control. In our laboratory at Warwick where robots use sonar their behaviour in the dark is much superior to that of their designers.

No undisclosed miracle of technology lies hidden within the robot's carapace - no 'positronic brain' is required. Most of the more advanced robots contain - or are controlled by - computer, and frequently by multiple computers. With the advent of reasonably powerful micro-computers, with 16 bits or more to chew the computer power can now be contained within the robot body. The smaller 8-bit micro-processors tend to wheeze and groan under the processing load required for even a small robot. The really high IQ robots still tend to cling to the apron strings of a big computer but it is only a matter of five years or so before they can cut loose.

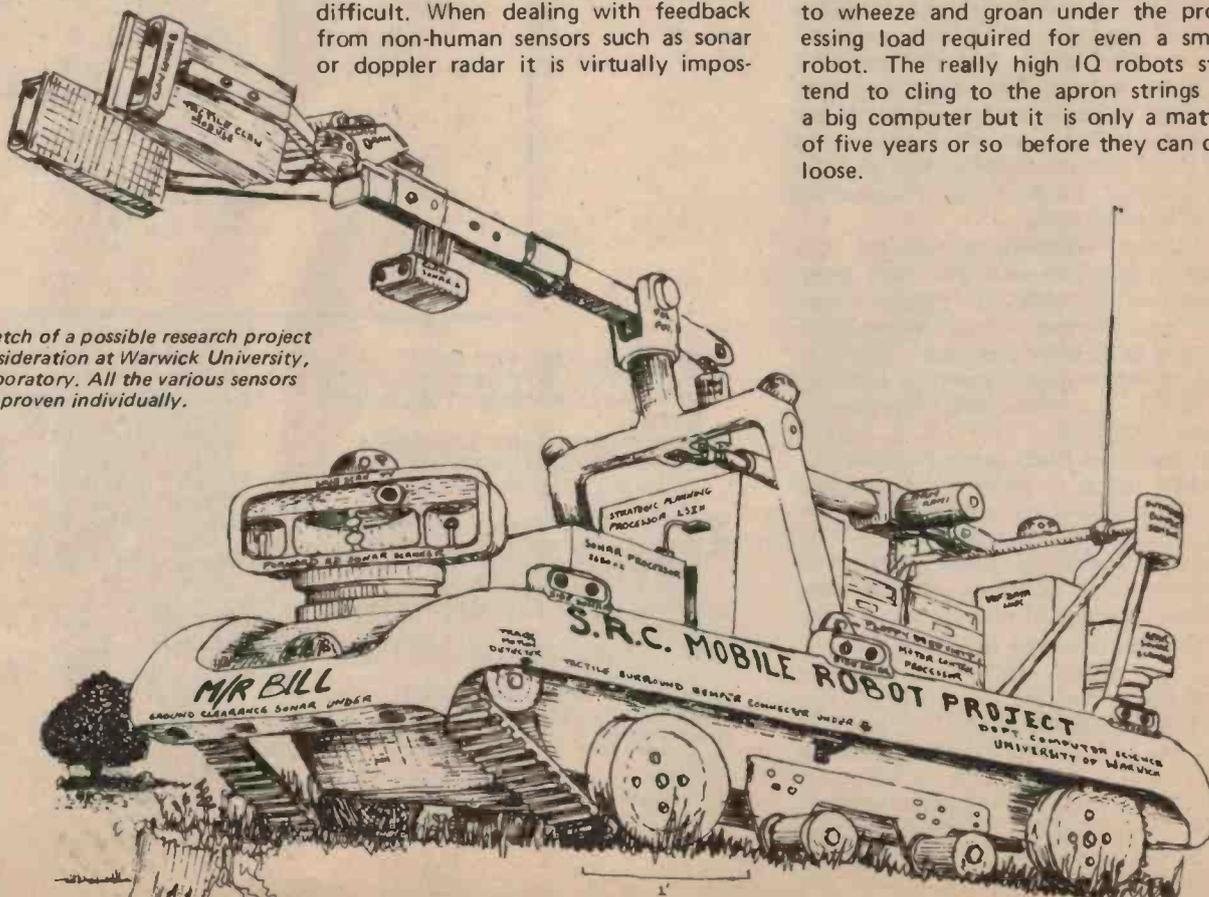


Fig. 1. Sketch of a possible research project under consideration at Warwick University, Robot Laboratory. All the various sensors have been proven individually.

In the first paragraph I was somewhat disparaging about computers. Yet computers control robots — how come the robot is smarter? Well the robot is a lot more than just computer — it has sensors and actuators and perhaps a boxful of specialist processing functions such as motor acceleration-deceleration control or positional servo systems. A small robot will have more input-output channels than many of the larger time-sharing computers. The robot's necessary data handling load may well exceed 10 megabits/second — much of this load is trivial — such as limit switch logic — and is easily handled by special logic. Nevertheless it must be handled. The road to automatic control is littered with sad and pathetic figures who thought all they had to do was connect the wires into a computer and it would do it all, 10 megabits/second requires a great deal of computer and a great deal of money!

### Flexibility

A robot program is unlike an ordinary computer program (such as a payroll program). A payroll program is a set of sequential steps moving data, making decisions and ultimately stopping. A robot program is attempting to weigh up a continuously changing 'situation' and assess what to do in that situation — much as an analogue computer is continuously monitoring both its inputs and its internal state. It is no good having a robot, which does not realise it is about to — or has — run into a 'wall' because the program has not got to the wall bumping bit yet. (I am supposed to be a bit absent-minded myself, but this is carrying 'thinking about something else' to extremes).

Further distinctions between the payroll programs and the robot programs may be made. The payroll computer does not require any knowledge of the nature of space and time — indeed it has no 'knowledge' of what it is doing. In fact it is a classic GIGO program — input 'BLOGGS, F PAY RATE — 97.5' and poor old Fred, gets a negative pay packet and is unlikely to be mollified by the apparent tax rebate and returned Medical Benefits contribution. The program does not know about the positive nature of pay — much less the negative attitude of Fred!


Central to many robot programs is a set of stored information which is generally called the world model. The complexity of this model is chosen to give the robot some knowledge of the real world without giving useless information. It is no use informing a robot that trees and grass are green if it uses infra-red vision — whereas the information that grass is on the ground and

trees stick out of it is useful.

The robot program need no longer take sensor or command data at face value. It compares incoming data with world model data for 'reasonableness'. If a wall appears to be moving (program checks sonar range to expected wall with world model distance between computed position and wall position and finds continuous variation) the program can quickly check with other fixtures to see whether it is sliding about itself or an unknown flat intruder is present or the wall is actually moving (the latter two cases may not be distinguishable). If an external command to move forward occurs the program can first check with the world model to ensure that no obstruction is to be expected and then check during the movement that an unexpected obst-

ruction does not exist.

The unexpected obstruction leads us into a really intriguing area of robot technology. Having found a palpably real 'thing' and perhaps having discovered a few useful facts about it (does it move by itself, is it round, how wide is it? can it be circumnavigated, does it emit ultrasound, does it emit light etc., etc.) these facts may then be entered into the world model by the robot itself. This may seem a small step, but for robot-kind it is a giant wheel-turn. The robot's behaviour is governed by comparing the incoming data with the stored world model data, but the robot itself is modifying this data — therefore the robot is modifying its future behaviour. This is at the very least a form of learning — that is to say, it is to some extent unpredictable.

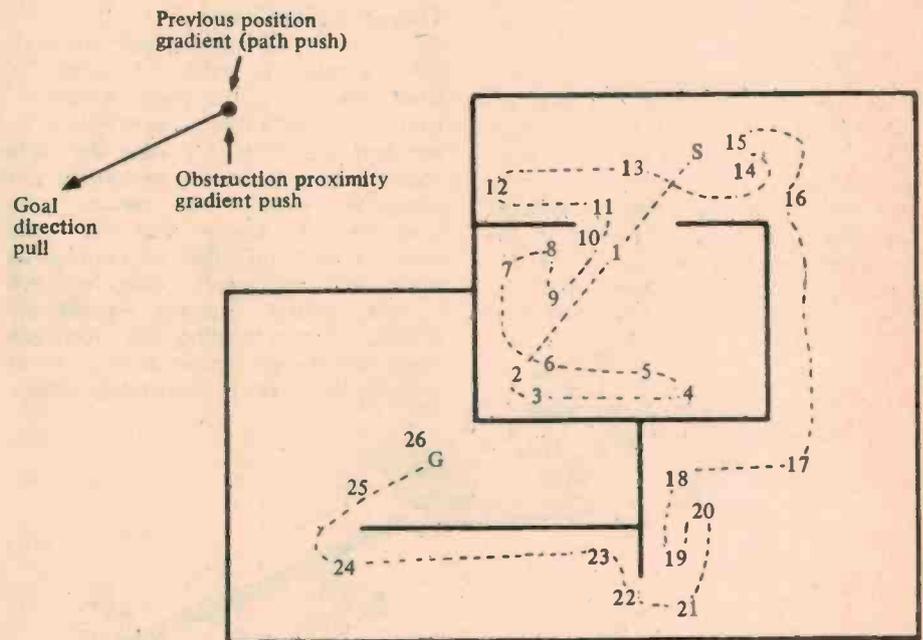

- 1 MAKES BEELINE FOR GOAL
- 2 WALL PROXIMITY DEFLECTS PATH
- 3 NEXT WALL PROXIMITY DEFLECTS PATH
- 4 PREVIOUS POSITION GRADIENT FALLS OFF AND OBSTRUCTION PROXIMITY & GOAL CAUSE TURNBACK
- 5 PATH AVOIDS PREVIOUS PATH
- 6 INERTIAL EFFECT OF PREVIOUS POSITION GRADIENT CARRIES IT ACROSS PREVIOUS PATH
- 7 CORNER CAUSES ROBOT TO TURN AGAIN
- 8 GOAL DIRECTION PULLING-PATH AT 7 PUSHING
- 9 TOO MUCH PREVIOUS PATH REPULSION ROBOT EXISTS
- 10 AVOIDING WALL AND PREVIOUS PATH
- 11 GOAL PULL TURNS ROBOT
- 12 CORNER CAUSES FOLDBACK
- 13 THE DOORWAY I 10 11 TOO FULL OF PREVIOUS POSITION

- REPULSION-INERTIA EFFECT CAUSES PATH CROSSING
- 14 15 16 DITHER CAUSED BY RAPID CHANGES IN RELATIVE IMPORTANCE OF GOAL PULL AND PATH OR OBSTRUCTION PUSH
- 17 CLEAR RUN DOWN WALL DIRECTED BY GOAL PULL AND OBSTRUCTION PUSH
- 18 19 20 FOLDBACK RESOLVED — PATH PUSH AND GOAL DIRECTION SORT IT OUT
- 21 22 DORWAY NEGOTIATED BY GOAL PULL AND OBSTRUCTION PUSH
- 22 DOORWAY NEGOTIATED BY GOAL PULL AND OBSTRUCTION PUSH
- 23 24 WALL FOLLOWING — INERTIAL EFFECT OF PATH PUSH OVER-COMES CHANGE IN GOAL DIRECTION
- 25 CLEAR HOME RUN
- 26 TWO JOULES OF DRAUGHT DC AND A PACKET OF CRISPS PLEASE!

## Free will

The robot is not deterministically programmed. There is an old saying about computers to the effect that the program is only as good as the programmer. In the case of robots this is no longer true in its original sense since two programmers are at work. In addition to the human programmer the totality of the robot's environment acts as a 'programmer'. Since the mechanics of the world are imprecise this second programmer never repeats its program exactly.

This indeterministic nature becomes clear when during a robot operation something surprising occurs and I am asked what is it doing. I usually have to say I do not know since the only way to find out for sure is to get the robot to explain in some way or to stop it


and inspect its memory. Either way can take some time. There is a well-known robot simulation program (illustrated) which deals with manipulations of stacks of geometric solids such as cubes upon cubes and pyramids on cubes (you cannot stack anything on a pyramid). This program has the advantage for the layman of communicating via a computer terminal in a reasonable facsimile of English. Having completed some long sequence of moves to stack a small blue cube on a big red cube (involving clearing everything on top of both cubes out of the way) the computer pauses and the programmer asks it: "Why did you move the green pyramid off the blue cube?: the computer answers "To reach the blue cube." The programmer probes further: "Why did you move the yellow cube off the

red cube?": The computer answers "So that the blue cube may be placed on the red cube." The programmer in great inquisitorial enthusiasm asks "Why did you place the blue cube on the red cube?": With the reserve only computers can muster, it replies "Because you told me to."

This 'back-tracking' is relatively easy in a simulation program and the computer used was very large. However, in a small mobile robot program space is at a premium and exotic 'chatty' communication impossible. The same space premium forbids the storage of all events — it is necessary to build in methods of selectively removing surplus data — a 'forgetory' if you like. This is akin to the short term memory system we appear to use: important stuff is kept and the junk is forgotten. This selective 'purging' may remove the data required for back-tracking and it may be impossible to determine why the robot behaved as it did in a particular situation. The robot may be given a bag of problem-solving tricks for using in conjunction with its memory, one of these may, for example allow it to solve the problems of getting about a maze-like environment as quickly as possible by 'mentally' finding the route before actually covering it (Fig. 2). There may be other specific stratagems for manipulation and so on. At the moment of writing however, the robot is not really capable of learning new tricks for itself. This may require an extension of the world model concept to cover more of the dynamic and sequential aspects of task learning.
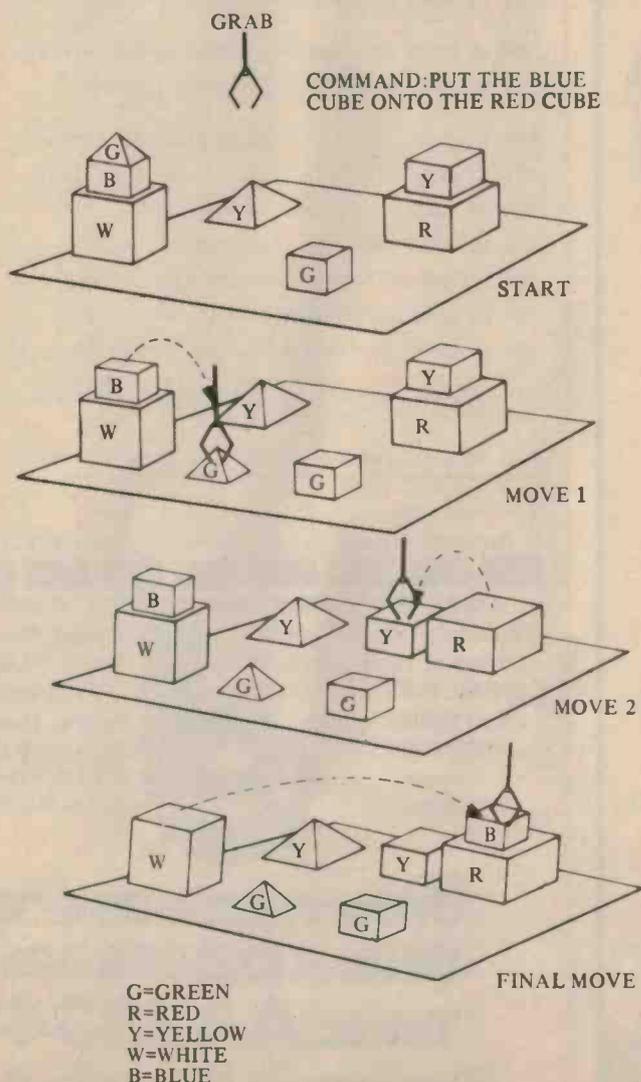
### Here, boy . . .

Robots are not yet capable of the full range of intelligence we expect even from an animal. They cannot learn new tricks, yet they can solve goal-seeking problems which would baffle a dog and can communicate in English with some degree of understanding. Clearly they do not fit into our usual categories for intelligence. The term 'machine intelligence' should be considered for the moment as standing apart from our normal spectrum of intelligence. When we know where to put it in that spectrum we will have learned much more about intelligence itself. Experiments with robots and in the field of artificial intelligence will help to elucidate this age-old puzzle of thinking. I suspect that just as in movement the robot is more likely to use wheels than legs it will use something dissimilar in structure to the brain for its 'thinking'. What is important is that as we understand the dynamic principles which govern both wheel and leg we also find the principles that govern both machine and biological intelligence.



# ARLEC

PROUDLY ANNOUNCE



## Not in age, for our origins go back further than that, but in Transformer Voltage Taps.

### Yes 21 Voltage Taps!

Just think of the advantages offered by a single transformer that provides a choice of 21 different output voltages including 3 centre tapped configurations.

FOR EXAMPLE: TRANSFORMER No. 2155A VOLTAGES AVAILABLE

1.0, 1.2, 2.0, 2.2, 2.4, 3.1, 3.2, 3.5, 4.1, 5.1, 5.5, 6.3, 7.5, 8.5, 8.7, 9.5, 12.6, 15.0 Volts  
2.0V CT, 12.6V CT, 15V CT

### But that's not all!

With 5 such transformers in our range there is a choice of output currents as well.

### And just in the way of a bonus!

We are able to offer these new transformers for a price considerably lower than comparable single tapped units while still maintaining the high standards of quality for which we are renowned.

### Like to know more?

Just ring your local Arlec branch.



What do we call them?

**ARLEC  
MULTI-TAP TRANSFORMERS**

*of course!*

**A+R ELECTRONICS PTY. LTD.**  
A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP

30 Lexton Road, Box Hill, Vic., 3128, Australia. Telex: 32286.

SALES OFFICES PHONES  
VICTORIA: 89 0661  
N.S.W.: 78 0281  
S. AUST.: 51 6981  
QUEENSLAND: 52 5421  
W. AUST.: 81 5500

# IF THERE'S A BETTER WAY TO BUY COMPONENTS, IT'S A WELL KEPT SECRET!

The following is just part of a Telex we received recently:

- QTY 50 STORE UNIT EACH ZENER DIODE BZX70 30 VOLT
- QTY 50 STORE UNIT EACH DIODE BZY96CV8
- QTY 20 STORE UNIT EACH IN5359B
- QTY 50 STORE UNIT RESISTOR 150 OHM TR8 2 %
- QTY 20 STORE UNIT EACH IC P/NO CA3018
- QTY 20 STORE UNIT EACH CANNON CONNECTOR 3 PIN MALE P/NO XLP-3-12
- QTY 10 STORE UNIT CAN INSTANT FREEZE COMPOUND
- QTY 24 STORE UNIT EACH CAPACITOR 2000MFD 100V
- QTY 100 STORE UNIT EACH CAPACITOR 3.3. MFD 50V TANTALUM
- QTY 50 STORE UNIT EACH CAPACITOR 18 MFD 50 V TANTALUM
- QTY 20 STORE UNIT EACH CAPACITOR 10MFD 50 V TANTALUM
- QTY 20 STORE UNIT EACH MINIBRIDGE PA40 RECTIFIER
- QTY 50 STORE UNIT EACH MINI PLUG 2.1 MM HOLE
- QTY 10 STORE UNIT EACH SILICON DIODE P/NO S5AN31
- QTY 10 STORE UNIT EACH SILICON DIODE P/NO S5AR31
- QTY 10 STORE UNIT EACH DIODE S12AR15
- QTY 10 STORE UNIT EACH DIODE S12AN15
- QTY 3 STORE UNIT EACH DIODE IRC P/NO 301U120A
- QTY 20 STORE UNIT EACH SCR GR 103 B
- QTY 20 STORE UNIT EACH METAL CAN IC P/NO F74108 7527
- QTY 10 STORE UNIT EACH 9 CONTACT OCTAL VALVE HOLDER CERAMIC SIMILAR TO PHILIPS 88-700-21

THIS TELEX IS FOR THE ATTENTION OF I.PURDIE

ELDI1ST AA23343

**CLIP THIS OUT YOU NEVER KNOW WHEN YOU'LL BE NEEDING US !!**

**CAPACITORS, SEMICONDUCTORS** — Fairchild, ITT, National (NS), NEC, Motorola, Philips, Plessey, RCA, Signetics, Texas. **RELAYS** — National (Japan), ITT. **CONNECTORS** — Acme/Kings, ITT/Cannon. **HEATSINKS** — Delco, Philips, Thermalloy. **RESISTORS** — Soanar, Beyschlag, Philips. **TRANSFORMERS** — Ferguson . . . **PLUS MORE**



**Orders: (02)636 6052**

**Office: (02)636 6222**

**Telex: AA23343**

**Electronic (Distributors)**

2-3 Post Office Arcade, Joyce Street, PENDLE HILL, NSW. 2145

ED3

# ICS now present another kind of E.L.O.



## Electronic Living Opportunities

The Electric Light Orchestra have a great sound. A sound which has won them numerous gold and platinum records, international acclaim and many thousands of dollars. But without the recording technicians – the electronics experts – ELO's talent would go unheard.

The booming pop music recording industry is just one example of how electronics is the very life source that powers virtually everything in our world today.

Qualifications in electronics are the passport to a whole world of fascinating jobs, opportunities and even life styles.

Now you can take advantage of the amazing "electronic living opportunities" available everywhere today by training with International Correspondence Schools.

Home-tutoring the ICS way allows you to work at your own pace and in your own time. So you can gain qualifications vital to a successful career in electronics without losing valuable income while studying.

Act now. The first step is simple. Fill out the coupon and post it today.

In return you will receive the ICS Electronics Career folder. This gives you all the details of the many courses available – Communications and Broadcasting, Industrial Electronics, Computer Servicing, Audio/Radio Servicing, all of which are endorsed by the Television and Electronics Technicians Institute of Australia.

It will also outline the advantages of in-home study with ICS, plus the many opportunities electronic qualifications will bring you.

Even if you aren't into music or ELO, don't let the "electronic living opportunities" an ICS course offers pass you by for another second. Clip and post this coupon immediately.

### International Correspondence Schools

400 Pacific Highway Crows Nest, NSW. 2065

18-20 Collins Street, Melbourne, VIC. 3000

125 Wakefield Street, Wellington, N.Z.

**Please send me, without cost or obligation, the ICS career guidance kit for the course marked below**

Electronics       TV Servicing

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

276740 \_\_\_\_\_

Age \_\_\_\_\_

Occupation \_\_\_\_\_

# ICS

**ICS courses are not recommended for School students.**

# Digital Electronics

## By Experiment pt5

Ian Sinclair has more to say on the subject of flip-flops. . .

WE HAVE SEEN earlier how the toggling action of a 7476 J-K flip-flop, which occurs when  $J=1$  and  $K=1$ , gives an output pulse train at half the frequency of the input clock pulses. We can use this output as the clock pulse for a second flip-flop, and we will make up a circuit to find the practical outcome of this.

### Frequency Divider

With power to the board switched off, set up the first flip-flop as before with  $J=1$ ,  $K=1$ . Connect a wire link from pin 15 (Q1) to pin 6 (CK 2), and attach a resistor and LED in the usual way to pin 11 (Q2) and a spare pad. This LED will indicate the state of the output of the second flip-flop whose J and K pins can be left floating.

With power applied, the output pulses from Q2 should now be at one quarter of the frequency of the oscillator so that this complete circuit is a divide-by-four, producing one complete pulse at the output for each group of four complete clock pulses into pin 1. This is shown in the clock pulse diagram of Fig. 1(b).

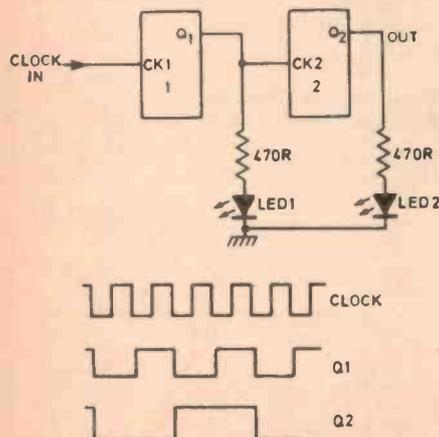


Fig. 1. Cascading 7476 flip-flops.  
(a) Circuit.  
(b) Pulse diagram.

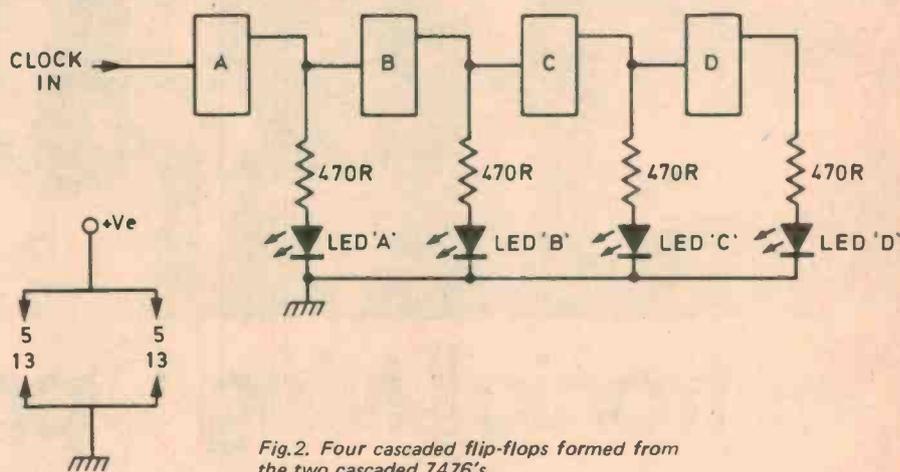


Fig. 2. Four cascaded flip-flops formed from the two cascaded 7476's.

With the supply disconnected again, connect up both halves of the second 7476 as shown in Fig. 2, so that we now have four toggling flip-flops in sequence. Connect a resistor and LED in the usual way onto the final Q output.

Can you predict what the count number of this circuit will be? (The count of a circuit is the number of complete pulses in to give one complete pulse out.) Using the slow clock pulse from the 7414 oscillator, count input pulses for one complete output pulse (0 to 1 to 0), and draw a clock pulse diagram.

### Asynchronous Counters

The type of circuit described above is a frequency divider, with each stage dividing the clock frequency by two. It can also be thought of as a scale-of-two counter, with a serial input and a parallel binary output.

Let us elaborate on this.

The pulses into the first clock input need not be at a steady rate, so long as each is separated from the next. This is a serial input — meaning one after the

other. The output of each flip-flop can be read, by means of an LED attached to each Q output, for example, and since all can be read together, this is a parallel set of outputs. Our counter, therefore, has serial input and parallel output.

More importantly, if we started putting the pulses into the input when the output of each flip-flop was zero (the counter cleared, or reset), we could tell how many pulses had appeared at the input if we stopped counting at some stage.

If we label our flip-flops A, B, C, and D (Fig. 2), with A the flip-flop at the input and D at the other end of the line, then we could also label B as 2, C as 4, and D as 8. We are able to do this because, starting at zero, QB will go to 1 after two input pulses (and back to zero on pulse number four), QC will go to 1 after four input pulses (and back to zero at eight), and QD will go to 1 after eight pulses, returning to zero at the sixteenth pulse. We would expect, for example, that after seven pulses, QD=0, QC=1, QB=1, and QA=1 because  $4+2+1=7$ .

This circuit is a binary asynchronous counter — binary because the counting is carried out in the scale of two instead of the more familiar ten, and asynchronous because the flip-flops are being clocked at different rates. The truth table of Fig. 3 shows the relation between the binary figures (the outputs from the Q terminals) and the number of pulses in (using decimal figures). Note that this arrangement counts to 15, and that all the flip-flops reset to zero on the sixteenth pulse.

| PULSES | QA | QB | QC | QD |
|--------|----|----|----|----|
| 0      | 0  | 0  | 0  | 0  |
| 1      | 1  | 0  | 0  | 0  |
| 2      | 0  | 1  | 0  | 0  |
| 3      | 1  | 1  | 0  | 0  |
| 4      | 0  | 0  | 1  | 0  |
| 5      | 1  | 0  | 1  | 0  |
| 6      | 0  | 1  | 1  | 0  |
| 7      | 1  | 1  | 1  | 0  |
| 8      | 0  | 0  | 0  | 1  |
| 9      | 1  | 0  | 0  | 1  |
| 10     | 0  | 1  | 0  | 1  |
| 11     | 1  | 1  | 0  | 1  |
| 12     | 0  | 0  | 1  | 1  |
| 13     | 1  | 0  | 1  | 1  |
| 14     | 0  | 1  | 1  | 1  |
| 15     | 1  | 1  | 1  | 1  |
| 16     | 0  | 0  | 0  | 0  |

Fig. 3. Truth table for four cascaded flip-flops.

#### Four-Stage Counter

Set up a four stage asynchronous counter on your board with a resistor and LED to indicate the state of each Q output. Label the LEDs to avoid confusion — QD furthest from the pulse input should be labelled 8, QC labelled 4, QB labelled 2, and QA labelled 1. Take the oscillator output through a gate which can be controlled by a switch, and connect the reset terminals (pins 3 and 8 of each 7476) to another switch so that all the outputs can be reset to zero by pressing the switch to connect the reset pins to the 0 V line.

Now apply power and check that the count sequence is as shown in the truth table of Fig. 3 when the gating switch is ON. Try switching the gate off and resetting.

Switch off the power and alter the connections between flip-flops A, B, C and D so that  $\bar{Q}A$  is connected to clock B,  $\bar{Q}B$  to clock C, and  $\bar{Q}C$  to clock D. Leave the LED indicators connected to the Q outputs as before (Fig. 4). Now switch on, and start the count. What is happening now?

Could you, (not necessarily using only the ICs on the board) design a counter using two 7476s which would count either up to 15 and reset, or down to zero (resetting) according to the position of a single switch, or the voltage on a gate? The number of gates needed makes this impossible on our board.

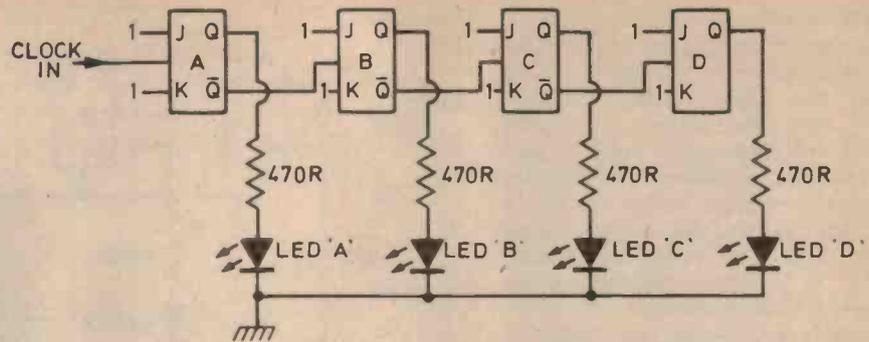


Fig. 4. Cascading from the  $\bar{Q}$  terminals — what does this counter do?

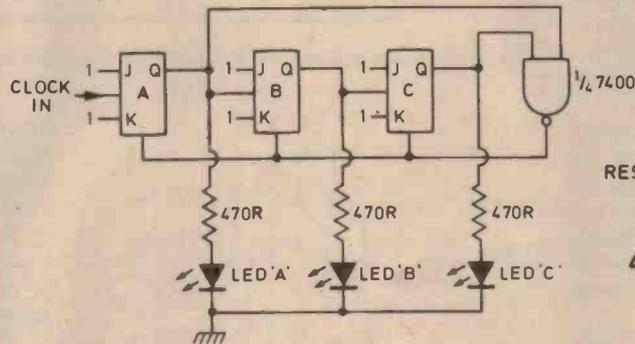


Fig. 5. A scale-of-five counter.

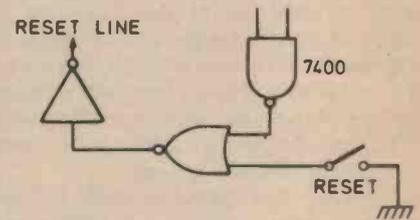


Fig. 6. Using a push-button reset with the circuit of Fig. 5. This could be accomplished in several other ways.

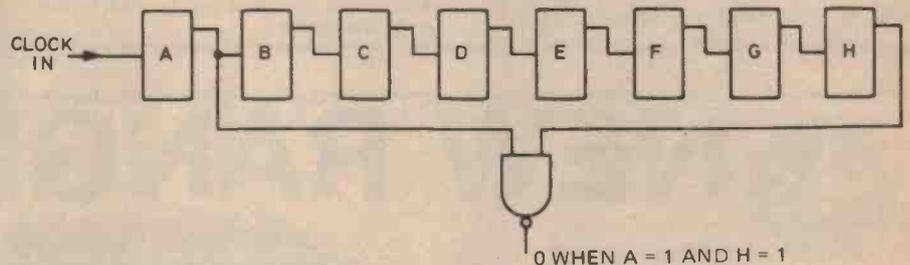


Fig. 7. A 'ripple counter'. This type of counter can suffer from 'race hazards'.

#### Interrupted Counts

We seldom want a counter which counts up to 15 and then resets to zero. We may want a decimal counter (0 to 9 and then reset to zero), or a counter which stops at some definite count, or which counts to some number, resets to zero and then stops. These operations can be achieved by using the Q outputs of the flip-flops together with gates.

Suppose, for example, that we want to count up to four, reset to zero at the fifth pulse, and then start again. What we need is some way of detecting the output at a count of five and using this to operate a reset. Detecting a count of five is easy enough since it is when QD=0, QC=1, QB=0, and QA=1. We can detect this by taking the Q outputs from C and A and connecting them to the inputs of a NAND gate, as shown in Fig. 5. When QC=1 and QA=1, the output of the NAND gate will be zero.

The simplest and most obvious way to use this is to connect the output of the NAND gate directly to the reset line of the flip-flops, replacing the reset switch we used previously.

Set up this circuit on your board. Use wire connections from QC and QA to the inputs of one of the 7400 NAND gates, and disconnect the switch from the reset line. Now switch on, with the slow oscillator input to the flip-flop first clock, and observe the count.

Can you now design a counter using four flip-flops which would reset at the tenth inward pulse? This will be a scale-of-ten (decimal) counter. Remember that ten in the binary scale is when QD=1, QC=0, QB=1, and QA=0. If, for any reason we want to use a separate switch-operated reset with this counter, we shall have to arrange an input through either an OR gate or a NOR gate as shown in Fig. 6.

## Ruined By Ripple

We can use this gating system to construct asynchronous counters which reset at the highest designed count number, but the system runs into problems with large count numbers and with high speed operation. For example, the first stage counter runs at the speed of the input pulses, and if these pulses are fast, then we may find "Race Hazards" — problems caused by the time delay in each flip-flop.

To take an example, we may be detecting the state 10000001. Now the 1 on the flip-flop H (Fig. 7), called "The Most Significant Figure", appeared just after the count had been 01111111, and if there is a time delay in the system flip-flop A may have gone to zero, to 1 and back to zero again before the clock pulse to flip-flop H has had time to work its way through all the stages in the counter. This time delay, caused by the need for a change to ripple through all the flip-flops, gives us the name "Ripple Counter", and can cause miscounting at high speeds.

Leaving this problem aside for the moment, our simple asynchronous counter has used the reset line for its reset action. For other types of count interruption we can make use of the J and K terminals of the J-K flip-flop, which is why they are provided. Con-

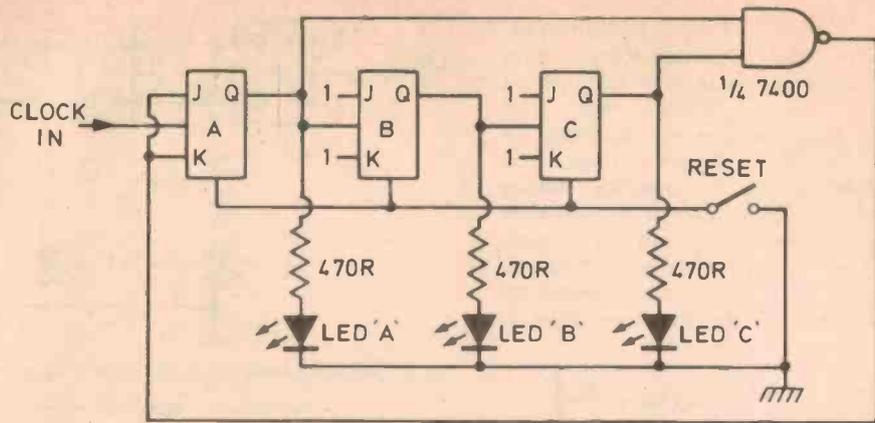


Fig. 8. What does this counter do? Build the circuit on your blob-board and draw up a truth table.

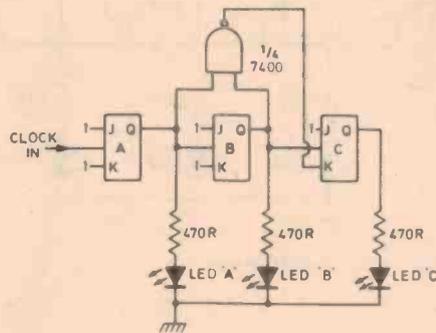


Fig. 9. What does this circuit do? Try to find out in theory, and then build up the circuit on the blob-board.

struct the circuit of Fig. 8 on your board. Can you predict what will happen? Try it out and draw up a count table.

Now try the circuit of Fig. 9. Can you predict what will happen when this is switched on? Try it and see if you were correct.

Could you now design and try a ripple counter which could start at any binary number selected by switches connected to the SET terminals of the flip-flops, then count down, stopping at zero, but leaving the reset terminals free to be used with a switch?



# NEW RANGE



**Model MS215 (available soon)**

**Price \$449\*** Dual trace-2ch.

**ALSO:**

**Model MS15**

**Price \$325\***

- 15mH bandwidth
- Ext & int trigger
- Time base-0.1 microsec to 0.5 sec/div-21 settings
- Batt or line operation
- Auto & lime sync modes
- Power consumption less than 15W
- Vert gain -0.01 to 50V/div -12 settings
- Weight 3lbs



**Model LM350 Model LM300**

**Price \$105\* Price \$95\***

- Measures DC volts, AC volts, ohms and current.
- Automatic polarity, decimal and overload indication.
- No zero adjustment and no full scale ohms adjust.
- Large LCD display for easy reading without interpolation.
- Size: 1.9" H x 2.7" W x 4" D.
- Parts and labour guaranteed for one year.



**Model RM351**  
**LED or LCD Display**  
**Full range available.**  
**from \$59\***

- MOS/LSI construction.
- Fits DIN or NEMA cutouts.
- Large 0.6" LED or 0.5" display
- No zero adjustment
- Programmable decimal
- Overload indication
- Automatic polarity
- Input voltage protection
- Low power requirement



**TRADE ENQUIRIES WELCOME**  
**NON-LINEAR SYSTEMS (AUST.) PTY. LTD.**

61 Lothian St. W. Melbourne Vic. 3015 Aust.

Ph. (03) 329-9951, (03) 329-9377

**DISTRIBUTED BY**

**PROTRONICS**  
174-180 Wright St,  
Adelaide.  
Ph. (08) 51-4713

**RADIO DESPATCH**  
869 George St,  
Sydney.  
Ph. (02) 211-0816

**RADIO PARTS**  
562 Spencer St,  
Melbourne.  
Ph. (03) 329-7888

\* Subject to sales tax.



TEAR THIS PAGE OUT NOW! PRICE LIST OVER 2,500 SEMIS

INTERFACE PRICE + Tax

Table listing interface components like HET20N, HET23N, HET24N, etc. with prices and tax.

CPI's 74LS00 TYPE PRICE + Tax

Table listing CPI's 74LS00 components like MCB800L, MCB800P, MCB800Q, etc. with prices and tax.

7400 TTL's TYPE PRICE + Tax

Table listing 7400 TTL components like 7400, 7401, 7402, 7403, etc. with prices and tax.

PHOTO OPTO DEVICES TYPE PRICE + Tax

Table listing photo opto devices like MTR148, MTR150, MTR152, etc. with prices and tax.

UJT SCR TRIACS TYPE PRICE + Tax

Table listing UJT, SCR, and TRIAC components like 2N2846, 2N2847, 2N2848, etc. with prices and tax.

4000 CMOS TYPE PRICE + Tax

Table listing 4000 CMOS components like MC14000, MC14001, MC14002, etc. with prices and tax.

FLAT CABLE TYPE PRICE + Tax

Table listing flat cable components like 14 Wire, 18 Wire, 20 Wire, etc. with prices and tax.

SHIFT REGISTER TYPE PRICE + Tax

Table listing shift register components like 5V1140A, 5V1140B, 5V1140C, etc. with prices and tax.

RAM's PROM's DYNAMIC RAM TYPE PRICE + Tax

Table listing RAM and PROM components like 16K72, 16K73, 16K74, etc. with prices and tax.

74C CMOS TYPE PRICE + Tax

Table listing 74C CMOS components like 74C00, 74C01, 74C02, etc. with prices and tax.

ZENERS TYPE PRICE + Tax

Table listing Zener diodes like 1Watt 3.3V, 1Watt 5.1V, etc. with prices and tax.

TRANSISTORS TYPE PRICE + Tax

Table listing various transistor components like 2N217, 2N218, 2N219, etc. with prices and tax.

IC SOCKETS TYPE PRICE + Tax

Table listing IC socket components like 8-Pin, 14-Pin, 16-Pin, etc. with prices and tax.

DIODES, RECT. TYPE PRICE + Tax

Table listing diode and rectifier components like 1N21B, 1N21C, 1N21D, etc. with prices and tax.

LINEAR TYPE PRICE + Tax

Table listing linear components like LM309, LM309A, LM309B, etc. with prices and tax.

MAD MAL'S PRE-PAK Electronics P/L P.O. Box 43, CROYDON, 2132 718 Parramatta Rd, CROYDON, NSW Ph: 797-6144 OPEN 7 DAYS POST FREE WHOLESALE PRICES All Prices PLUS SALES TAX or Company Order + Tax No Accepted. Credit: 30 DAYS

# DIGITAL CAR TACHO

---

Compact unit offers both 10 rev resolution and short response time.

---

WE HAD OFTEN considered the design of a digital tacho for automobile use, but had rejected several schemes as we were unable to get both good resolution and response time — the two seemed to provide a very good demonstration of Heisenberg's Uncertainty Principle.

Consequently, we were rather pleased when Mike Pratt of S M Electronics came to us with his phase-locked loop based design which got round the problem. Would we like to do it as a project, he asked? Obviously, we said yes, and here it is.

To make the project even more attractive, we arranged with Mike to do a special offer on a kit of parts — there's more information on the offer on page 53.

This tacho features a fast response time, coupled with 10 Hz resolution, through the use of a phase locked loop frequency multiplier. It can be set up, by means of a single link, to work on 4, 6 or 8 cylinder motors.

## Design Features

To measure the revolutions per minute of a motor is simply a matter of counting the number of ignition pulses over a given time. With a four cylinder, four stroke motor there is such a pulse twice per revolution. Therefore if we count these pulses for 30 seconds we will have revs/min with a one cycle resolution. Obviously this is much too long a sample period for practical use in a motor car and some compromise has to be made.



The usual solution is to use a 100 rev resolution and a sample time of 0.3 seconds (on 4 cylinders). We considered this inadequate which is why we have not published a design until now.

In this design an oscillator is used which is phase locked to the ignition pulses except at a higher frequency (x8 for 4 cylinder) allowing a short sample time (0.375 sec) with a 10 rev resolution. By using a different multiplication factor compensation for different numbers of cylinders can be made. Unfortunately with the multiplication factors used (x8, x6, x4) the sample time for 6 cylinders is not exactly the same as that used for 4 and 8 cylinder motors. Altering the ratios to x12, x8 and x6 would enable a 0.25 sample time to be used for all ranges, but this is not possible with the divider IC utilised in this design.

## Construction

Assemble the pc board with the aid of the overlay ensuring the components are orientated correctly. The tantalum capacitors normally have a + mark indicating the positive lead, or a dot on the side. When soldering the CMOS ICs (4, 6, 7) earth the tip of the soldering iron.

Note that there is one feedthrough or link between the two sides of the board near C10.

## Calibration

Initially place a link between the point 'C' and the terminal corresponding to the number of cylinders. Now with the power supply connected feed a 50 Hz signal of between 12 and 30V into the points input using the 0V as common. Now adjust RV1 until the display reads 1500RPM for 4 cylinders, 1000 for 6 or 750 for an eight cylinder car.

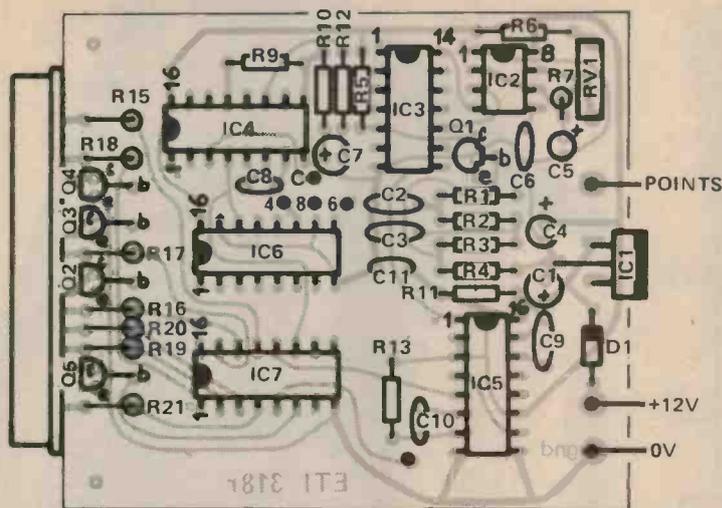


Fig. 1. The component overlay for the board. The board is double sided although only the lower surface is shown here. Note the link between the two surfaces of the board near C10.

### PARTS LIST - ETI 318

#### Resistors all 1/4 W, 5%

|        |          |
|--------|----------|
| R1,2   | 39k      |
| R3,4   | 22k      |
| R5     | 1k5      |
| R6     | 100k     |
| R7     | 100R     |
| R8     | not used |
| R9     | 10k      |
| R10    | 390k     |
| R11    | 10k      |
| R12    | 270k     |
| R13    | 10k      |
| R14    | not used |
| R15-21 | 27R      |

#### Potentiometer

|     |          |
|-----|----------|
| RV1 | 25k trim |
|-----|----------|

#### Capacitors

|      |                   |
|------|-------------------|
| C1   | 10μ 25V tantalum  |
| C2,3 | 56n polyester     |
| C4   | 10μ 25V tantalum  |
| C5   | 4μ 7 25V tantalum |
| C6   | 10n polyester     |
| C7   | 1μ 0 25V tantalum |
| C8   | 470p ceramic      |
| C9   | 56n polyester     |
| C10  | 10n polyester     |
| C11  | 10n ceramic       |

#### Semiconductors

|     |        |                 |
|-----|--------|-----------------|
| IC1 | 7805   | regulator       |
| IC2 | 555    | timer           |
| IC3 | 7413   | dual schmitt    |
| IC4 | 4046   | PLL             |
| IC5 | 74123  | dual mono       |
| IC6 | 4018   | divide by n     |
| IC7 | 74C925 | 4 digit counter |

Q1 . . . . . BC318

Q2-Q5 . . . BC338

D1 . . . . . 1N4004

Display . . . NSB5881

#### Miscellaneous

PC board ETI 318  
Case to suit

### SPECIFICATION - ETI 318

|                           |                                                                                           |
|---------------------------|-------------------------------------------------------------------------------------------|
| Range                     | 100 to 9990RPM                                                                            |
| Resolution                | 10RPM                                                                                     |
| Reading rate              |                                                                                           |
| 4 or 8 cylinders          | 2.66 per second                                                                           |
| 6 cylinders               | 3 per second                                                                              |
| Power supply              | 7 to 15V @ 400mA                                                                          |
| Suitable ignition systems | standard<br>CDI<br>transistor assisted<br>* it will not operate on<br>'pointless' systems |

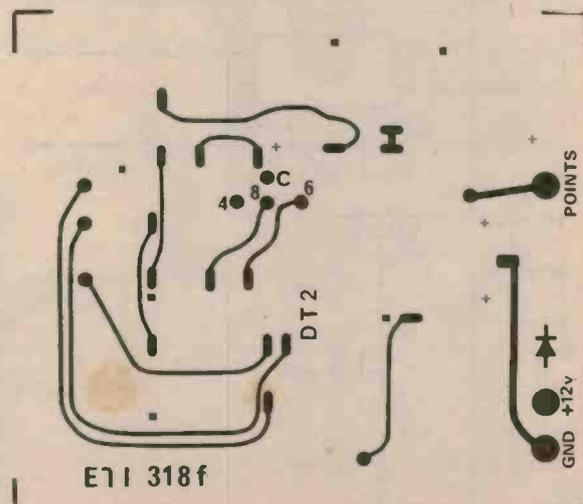
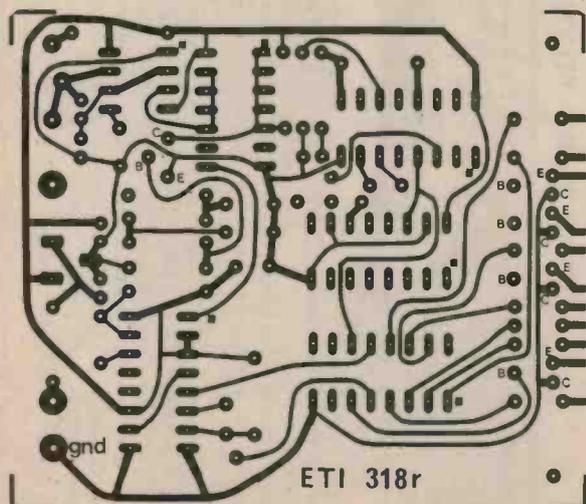


Fig. 2. The pc patterns shown full size. Unfortunately space did not allow us to reproduce these on the gloss paper and therefore they cannot be copied using our Scotchcal method.

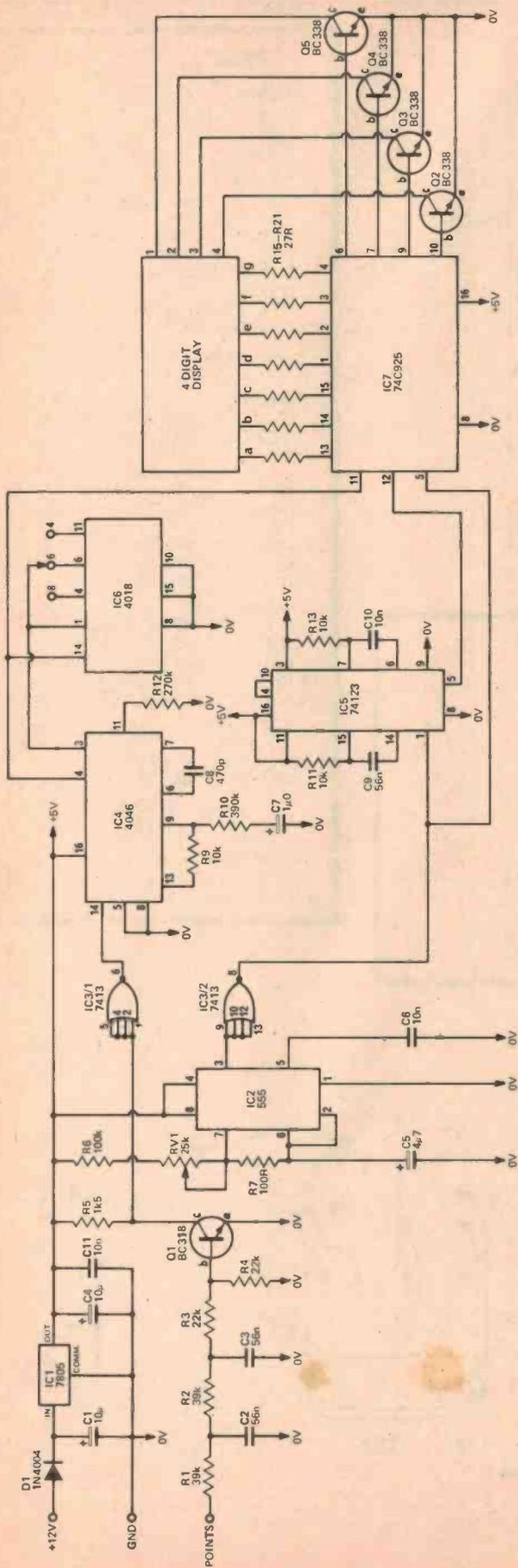


Fig. 3. The circuit diagram of the digital tachometer.

## HOW IT WORKS - ETI 318

The output from the points of the distributor is basically a 0 to 12V square wave with a 200 volt pulse on the rising edge. A filter network, R1-R4, C2, 3 is used to remove the high voltage pulse (and points bounce) and Q1 buffers it giving a +5 to 0V output on its collector. As the filter network removes the sharp edge of the input a schmitt trigger is needed on the output of Q1 to give fast edges. IC3/1 is used for this.


The output of IC3/1 is connected to the input of the phase-locked loop IC (4046). This IC has an internal voltage controlled oscillator and its output is divided by 4, 6 or 8 by IC6 and this lower frequency is fed back to the phase-locked loop IC. The IC then compares this frequency to that at its input and adjusts the internal oscillator until it is the same. The result is a frequency which is an exact multiple of the input.

The time base is generated by IC2 (555) which has a negative output pulse, about 300 µs wide every 375 ms (or 333

ms for 6 cylinders). This is inverted by IC3/2 and is used as the strobe pulse for the 4 digit counter IC7. This pulse also triggers the first of the monostables in IC5 which gives a 200 µs delay before triggering the second half of IC5; this gives a 40 µs pulse to reset IC7 back to zero.

IC7 is a 4 digit counter with a latch (store) and seven segment decoder driver. It needs four external transistors to drive the digits but the segment drivers are internal. As we need only a three digit counter, i.e. for a 10 Hz resolution, the right hand permanently zero the least significant digit is connected to the second right digit, etc., with the most significant digit connected to the right hand digit. Provided one does not exceed 9990 RPM this digit will remain on 0 as intended!

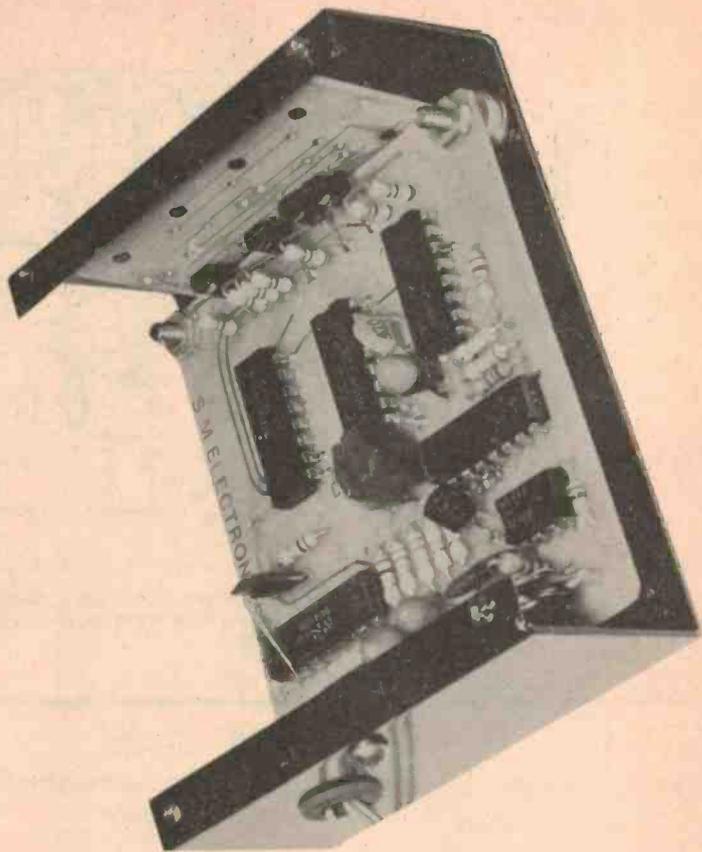The 555 timer, the TTL and the 74C925 needs a regulated +5V and IC1 provides this with D1 preventing damage due to reverse polarity inputs.



# ETI 318



# Tacho Kit \$29.95

# SPECIAL OFFER

WE HAVE arranged with Mike Pratt of S M Electronics for him to offer ETI readers a complete kit of parts for this project at the special price of \$29.95 plus \$2.00 for packing and certified postage.

The kit includes all components necessary to build the project, including a metal case which has a rectangular hole in the front for the LED display.

To order, complete the coupon below, and send it, with a cheque for the appropriate amount, to: Tacho Offer, Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW 2011. Cheques should be made payable to 'Tacho Offer'. Please allow 4-6 weeks for delivery.

Send to: Tacho Offer, Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW 2011.

Please forward . . . . . ETI 318 Tacho kits at \$29.95 each plus \$2.00 each certified postage and packing.

I enclose herewith cheque/postal order total . . . . .

Please make cheques, etc., payable to 'Tacho Offer'.

Name . . . . .

Address . . . . .

Postcode . . . . .

Offer closes 29 September, 1978 and is open to Australian residents only. Apologies to our overseas readers.

# Make pcb's, panels etc. at home!

YOU can make fully professional quality PCBs and front panels, etc at home — without special facilities or equipment. Let Dick Smith show you how easy it is — with a little help from

## Scotchcal<sup>®</sup> BRAND PHOTSENSITIVE PRODUCTS

Scotchcal from Dick Smith comes as either: Thin, adhesive-backed aluminium sheet, or Thin, orange-coloured plastic film.

These are both coated with a photo-sensitive emulsion which is exposed by ultra-violet light (the sun is ideal).

The aluminium sheet is usually used for front panels, name plates, etc, while the film is intended for transferring artwork into a form which enables exposure of panels, printed circuit boards, etc. Both products use the same developer, which is simply wiped on with a soft cloth or cotton wool.

### NOTE: NO DARKROOM REQUIRED!

#### PHOTO-ALUMINIUM FOR PANELS AND LABELS

Either red or black emulsion, grey (aluminium) background. Simply expose to ultra violet light through suitable transparency (or artwork on clear or translucent film) and develop. Image is negative of artwork (clear areas remain, black areas develop away). Supplied with a FREE sheet of polyester material on which you can draw your artwork. 250 x 305mm. RED emulsion, single sheet. Cat H-5692 ... \$6.00 BLACK emulsion, single sheet. Cat H-5694 ... \$6.00

#### EXPOSURE FILM — FOR PANELS OR PCB'S

Exposure and development identical to above process, but the base material is a clear polyester film. The image is orange, opaque to UV light. Ideal for exposing above or PCB resist. Also supplied with FREE artwork layout sheet, 250 x 305mm. Cat H-5690 ... single sheet ... \$3.90

#### SCOTCHCAL DEVELOPER

Suitable for either film or aluminium, enough for many sheets of material. Simply swab on with cloth or cotton ball. Cat H-5696 ... \$1.00

### MATERIAL FOR MAKING PRINTED CIRCUIT BOARDS

As well as our Scotchcal range, we also offer everything for the easy manufacture of PCB's. Blank board, etchant, photo-resist, developer, touch-up pens, etc. You can make PCB's at home up to commercial quality — in a fraction of the time they used to take.

#### PHOTO-RESIST (POSITIVE)

For photographically transferring the printed circuit board pattern on to the blank PCB. Positive acting, so it's ideal for prototypes from 1:1 tapes & pads, etc. Exposed by UV light. Enough resist for around 240 square inches of board. Cat H-5720 ... \$3.75

#### POSITIVE DEVELOPER

Develops above resist. Washes off the unwanted section. 80g pack makes up to solution — instructions enclosed. Cat H-5724 ... \$1.85

#### PHOTO-RESIST (NEGATIVE)

Similar to above resist, but is negative acting. Ideal for use with exposure film above to obtain patterns from magazines. Enough resistor for approx. 240 square inches. Cat H-5722 ... \$2.75

#### NEGATIVE DEVELOPER

Already made up in solution, enough to develop around 50g of negative photo resist. Cat H-5726 ... \$3.00

## WOT'S NEW?



\$3<sup>95</sup> X-1085  
**LITE-PROBE**

Light right where you want it! Fibre-optic torch allows you to get over, under, up into, anywhere you need light. Takes two standard penlight batteries (not supp.) and can also be used as normal torch if required. A great idea for experimenters, servicemen, etc. Small enough for the pocket (illustration approx 1/2 size).


#### PADDLE SWITCHES

Beautiful new switches will really make your project look pro! Piano-key-type paddle, DPDT 3A/240V switching. Through-hole (18mm) mounting from front. Black paddles available immediately, white (as shown) within 2 weeks. Classy!



\$2<sup>40</sup> S-1393

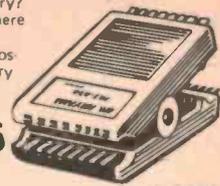Having trouble with IC circuitry? Test clip brings out pins to where you can easily attach probes, leads, etc. Spring loaded for positive contact, should be in every hobbyists tool box! 16 pins — use with all DIL ICs up to 16 pins.



IC TEST CLIP \$2<sup>95</sup> W-4600

\$1<sup>95</sup>



Z-4825


#### FREE POWER! SOLAR CELL

Straight from space research — these little solar cells are ideal for the experimenter. We've checked them up to 60mA in bright sunlight, with no-load voltage up to 0.55V. Series or parallel them for greater output. Fantastic value.

#### 4-WAY MAINS POWER BOX

Throw away dangerous double adaptors. Power box plugs into wall socket and gives you 4 switched sockets where you need them. Each double pole switched and safety shuttered, too. Everyone needs extra power at times. Here's the safety way to get it!

\$16<sup>50</sup> P-5610

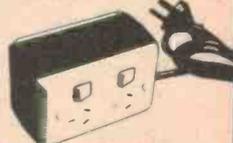

## WATCH THIS SPACE

### AND FIND OUT WHAT YOU MISSED!

Each month, our stores and mail order dept. feature an outstanding BELOW COST special. All you have to do is go into any of our stores or buy from mail orders to find out what it is.

### LAST MONTH:

A MULTI-TAP LOW VOLTAGE TRANSFORMER FOR ONLY \$3.25 — NORMALLY \$6.75

SAVING \$3<sup>50</sup>

### WHAT'S THIS MONTH'S SPECIAL? CALL IN AND FIND OUT YOURSELF!

Pre-cut high quality PC blanks with copper (1oz laminate) on one side. Available in fibreglass or bakelite.

| Size (mm)                 | Material   | Cat No. | Price  |
|---------------------------|------------|---------|--------|
| 150 x 75                  | Bakelite   | H-5500  | 85c    |
| 150 x 150                 | Bakelite   | H-5505  | \$1.20 |
| 300 x 300                 | Bakelite   | H-5510  | \$2.95 |
| 150 x 75                  | Fibreglass | H-5540  | \$1.00 |
| 150 x 150                 | Fibreglass | H-5545  | \$2.10 |
| 300 x 300                 | Fibreglass | H-5550  | \$5.20 |
| Double sided 1oz laminate |            |         |        |
| 228 x 150                 | Fibreglass | H-5560  | \$3.50 |

Blank 18 gauge aluminium sheet — ideal for making up heat sinks, small chasses, etc. Also use with rub-on lettering for your front panels, etc.

|             |            |        |
|-------------|------------|--------|
| 298 x 298mm | Cat H-2560 | \$2.00 |
| 149 x 149mm | Cat H-2558 | \$1.00 |

Ferric Chloride etchant for PCB's, etc. 4 oz jar to make up etching solution. Ferric Chloride Cat H-5652 \$1.90

Dalo touch-up pen, with unique ink that is also a resist to most common etchants. Ideal for repairing tracks in photo-resist (dust spots, etc) or for marking out simple PCB patterns. Valve-tip for fine ink control. Dalo 33 pen Cat T-5170 \$2.25

## POT-POURRI

EXPERIMENTERS: CLOCKS ROCKS. Incredible scoop purchase of 3.58MHz clock crystals — big quantity buy enables us to sell them at less than half normal price! Cat K-6031 ... Was \$6.50 ... \$3.00

AWA DIRECT DRIVE TURNTABLES — Only a few left!

See our advert on page 108 of June E.A. — this never-to-be-repeated offer is too good to miss out on. But you had better phone before coming in to the store — stocks may have already sold out! Don't dilly dally, pally. Cat A-3072 ... \$159.00

INSTANT MUSICIAN! You have to hear it — rhythm box gives a choice of 12, is ideal for bands, parties, etc. It is outstanding value at the price — compare others around. 240V. Cat. F-3114 ... \$115.00

CB ANTENNA ELIMINATOR won't give the game away — makes your car less of a target for the light-fingered lot. Uses your standard car radio antenna for the CB — and you can listen to both at once if you wish. Ideal for commercial travellers, etc, who aren't allowed to drill another hole in the car! Cat D-5516 ... \$24.50

## SAVE \$30<sup>00</sup>!!


Look what we found — hidden in a corner of the warehouse! Incredibly handy DC digital voltmeters — with the display in the probe, right where you want to see it! They sold like hot cakes at \$89.50 — we thought we'd sold out. Because they've been removed from our computer memory we can't afford to have them lying around. So we're prepared to knock off an incredible \$30.00 just to make sure they ARE sold out! But be quick — strictly limited stock. First in, first served!



\$59<sup>50</sup>

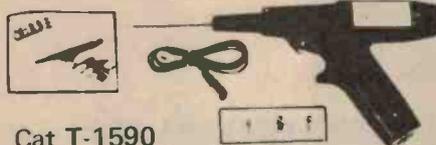
# SPECIAL OFFER!

Buy this Scope cordless iron for only \$45...



Cat T-1590

Yes! This Scope cordless iron was real value at \$45.00 — now you get the iron PLUS a matching charger for the same low price. That has to be the bargain of the year... Handy Scope iron goes with you on the job, no trailing wires or power problems to worry about. Easily available spare parts (uses Miniscope bit) and now the plug-pack charger to go with it. It's ideal for the serviceman, for the technician, for the hobbyist, for YOU. This offer is valid only for the month of July (or until stocks run out) and is not applicable in states where it contravenes consumer laws.

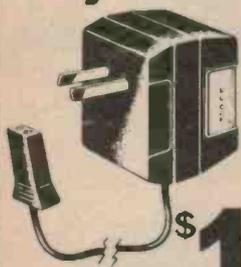

Cat T-1592

and we'll give you this \$12.25 charger FREE!

**\$12.25** JULY ONLY

## Gozinta

Wotsa Gozinta? Itsa thingamejig ya put thingsinta, of course!

Yes! The handiest carry box we've seen around. It's ideal for the handyman, the hobbyist, the service technician... even the wife for a sewing box, or for the fisherman, the mechanic... the list goes on and on. Neat, fold-away sections (2 trays and 15 compartments) Sturdy carry handle and lockable catch. 42 x 23 x 20cm. It's a little bottler!




Cat H-2600

BUY ONE FOR MUM, TOO...

**\$17.50**

## 2 tapes

**\$7.90**

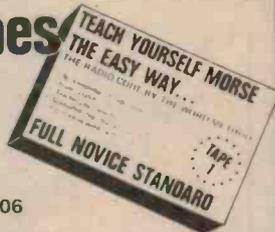

Cat D-7106

### WANT YOUR NOVICE LICENSE?

You know what the biggest hurdle is — the Morse Code. Dick's Morse tapes will help you get that coveted piece of paper. Starts off with the letters then forms them into words so you aren't learning the hard way. Ideal for the beginner or for exam practise. Two tapes — white is tape one and yellow tape two.

# PARTS FOR NEW KITS

### NEW FANTASTIC TV GAME (See July E.A.)

10 games — sound — on screen scoring... See our full page advert and the constructional article in this issue for full details of this exciting project. Complete kit, including instructions... Cat K-3472... \$49.50

SEPARATE PARTS:

|                                   |                  |         |
|-----------------------------------|------------------|---------|
| PC Board (only) .....             | Cat H-8344 ..... | \$3.95  |
| Fully built RF modulator .....    | Cat K-6040 ..... | \$3.00  |
| Fully built audio modulator ..... | Cat K-6042 ..... | \$4.50  |
| AY-3-8600 IC .....                | Cat Z-6852 ..... | \$15.00 |

### TRANSISTOR TESTER (See July E.A.)

See this issue for full details. Full kit with instructions: Cat K-3052... \$17.90

SEPARATE PARTS:

|                       |                  |        |
|-----------------------|------------------|--------|
| PC Board (only) ..... | Cat H-8350 ..... | \$1.95 |
| 1mA panel meter ..... | Cat Q-2010 ..... | \$7.90 |

### PHOTO TACHOMETER (See July E.A.)

Although we do not produce a full kit for this project, all parts are normal stock lines at our branches:

|                               |                  |        |
|-------------------------------|------------------|--------|
| PC Board (only) .....         | Cat H-8353 ..... | \$1.80 |
| FPT100 photo transistor ..... | Cat Z-1950 ..... | \$2.00 |

### SIMPLE CRYSTAL CHECKER (See July E.A.)

Not produced as a special kit — all parts are normal stock lines except the front panel.

### STUNT MOTORCYCLE GAME (See June E.T.I.)

A game of incredible skill and excitement yet it's so easy to build. Kit includes quartz crystal and pre-built, pre-aligned modulator — no tuning required. Full kit with instructions... Cat K-3474... \$29.50

SEPARATE PARTS:

|                                    |                  |         |
|------------------------------------|------------------|---------|
| PC Board (only) .....              | Cat H-8615 ..... | \$3.85  |
| Fully built RF modulator .....     | Cat K-6040 ..... | \$3.00  |
| AY-3-8760 IC .....                 | Cat Z-6854 ..... | \$19.50 |
| 3.58MHz atal (new low price) ..... | Cat K-6031 ..... | \$3.00  |

### AUDIO OSCILLATOR (See June E.A.)

Easy to build, very handy piece of test of test gear. Complete kit... Cat K-3469... \$25.00

|                       |                  |        |
|-----------------------|------------------|--------|
| PC Board (only) ..... | Cat H-8614 ..... | \$3.65 |
|-----------------------|------------------|--------|

### VK POWERMATE (See May E.A.)

Short form kit, includes all electronic components, but not metalwork, mains wiring or terminals. Short form kit: Cat K-3449... \$32.00

SEPARATE PARTS:

|                                     |                  |         |
|-------------------------------------|------------------|---------|
| PC Board (only) .....               | Cat H-8342 ..... | \$2.00  |
| Special electros (5600uF/40V) ..... | Cat R-4570 ..... | \$3.90  |
| Power transformer .....             | Cat M-2000 ..... | \$17.32 |

### R-C-L BRIDGE (See March E.A.)

Complete kit, supplied with printed, but un-punched front panel. Handy piece of test gear, real value price. Full kit with instructions: Cat K-3468... \$34.50

|                       |                  |        |
|-----------------------|------------------|--------|
| PC Board (only) ..... | Cat H-8339 ..... | \$2.50 |
|-----------------------|------------------|--------|

### ELECTRONIC MORSE CODE KEYS (See March E.A.)

Complete kit, supplied with paddle. Supplied in case with plain, un-drilled panels. Full kit with instructions Cat K-3470... \$37.50

SEPARATE PARTS:

|                                     |                  |         |
|-------------------------------------|------------------|---------|
| PC Board (only) .....               | Cat H-8340 ..... | \$3.75  |
| Paddle only .....                   | Cat D-7103 ..... | \$17.50 |
| 9 volt battery (special type) ..... | Cat S-3200 ..... | \$2.00  |

If your project is not listed, don't despair! Parts for most of the magazine articles are stocked at Dick Smith Electronics stores.

# WIN A TRIP FOR TWO TO TOKYO

Every purchaser of Yaesu equipment from Dick Smith or participating dealers receives an entry form in the fabulous 'Win a trip for two to Tokyo' contest, flying Qantas and staying in a luxury hotel. Full details wherever Yaesu/Dick Smith products are sold.

**FLYING QANTAS**  
AUSTRALIA'S AIRLINE TO THE WORLD.

REMEMBER — THE CONTEST CLOSES IN JULY — AND YOU NEED TO THINK ABOUT YOUR ENTRY. SO DON'T DELAY!



## CONTEST CLOSES 28TH JULY

# DICK SMITH ELECTRONICS

**SYDNEY** 125 York Street, SYDNEY. Ph. 29-1126  
147 Hume Hwy, CHULLORA. Ph. 642-8922  
162 Pacific Hwy, GORE HILL. Ph. 439-5311  
30 Grose Street, PARRAMATTA. Ph. 683-1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67-9834  
656 Bridge Road, RICHMOND. Ph. 42-1614  
**BRISBANE** 166 Logan Road, BURANDA. Ph. 391-6233  
**ADELAIDE** 203 Wright Street, ADELAIDE. Ph. 212-1962



welcome here

SHOPS OPEN 9AM to 5.30PM  
(Saturday 9AM - 12 noon)  
BRISBANE 1/2 Hour earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

**GRACE BROS**

Broadway - Bondi - Chiswick - Liverpool  
Miranda - Mt Druitt - Parramatta - Rensselaers  
and Warringah Mall



MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

### MAJOR DICK SMITH ELECTRONICS DEALERS:

Overland Communications 11/53 Wollongong St, Fyshwick ACT. Ph. 80-4307  
Trilogy Elect. Supplies 52 Princes Hwy, Wollongong NSW. Ph. 83-1219  
Sound Components 78 Brisbane St, Tantworth, NSW. Ph. 66-1363  
Hitel Hi Fi 145 Queen St, St Marys, NSW. Ph. 623-4442  
Don House Electronics 2 Merrivale St, Gordon NSW. Ph. 498-1398  
DGE Sales 44 Brown St, Newcastle NSW. Ph. 69-1222  
M&W Electronics 48 McNamara St, Orange NSW. Ph. 62-6491  
Double Diamond 18 Russel St, Goulburn NSW. Ph. 21-5440  
Greg McCartney 99 Fitzmaurice St, Wagga NSW. Ph. 21-3044  
Rivercom 9 Copeland St, Wagga NSW. Ph. 21-2125  
GCG Communications 385 Mulgrave Rd, Cairns QLD. Ph. 54-1035

The Elect. Hobby Centre  
Premier Sound  
Summer Electronics  
Aero Electronics  
Tasmanian Hi Fi  
Devon Electronics  
A E Cooling  
Hutchisson's Commun.  
Altronics  
BP Electronics

1168 Gold Coast Hwy, Palm Beach QLD. Ph. 34-1248  
239 Musgrave St, Rockhampton QLD. Ph. 27-4004  
97 Mitchell St, Bendigo, VIC. Ph. 43-1977  
123A Bathurst St, Hobart TAS. Ph. 34-8232  
87A Brisbane St, Launceston, TAS. Ph. 31-5815  
45 Ashburner St, Devonport TAS. Ph. 24-4216.  
Town Centre, Peoples St Bldg, Elizabeth SA. Ph. 255-9196  
5 Elizabeth St, Mt Gambier, SA. Ph. 25-6404  
105 Stirling St, Perth WA. Ph. 328-1599  
11 Duke St, Albany WA. Ph. 41-2681.

# UP/DOWN PRESETTABLE COUNTER

- \* 4 digit
- \* up/down counting
- \* drives LEDs directly
- \* latch
- \* presettable
- \* second register
- \* equal and zero outputs
- \* DC to 2MHz
- \* 5V operation

THE THREE DIGIT display (ETI 533) we previously published has proved to be one of our most popular projects. We have used it in a number of projects and we know of several commercial companies using it in their own equipment.

Many people have asked us for a 4 digit version and we have been looking round at ICs available. We have chosen this Intersil device because we believe it offers the best versatility at the moment. Apart from being a 4-digit counter-latch-decoder driver needing no external components except the displays, it also is an up-down counter and can be preset to any number. In addition, it has a separate register which also can be set to any number and comparators which give outputs when the counter is equal to the register and when it is zero - all in one IC!

## Construction

The unit is built on two small pc boards which are connected together with short links of tinned copper wire. Be careful to orientate the IC correctly as it is expensive!


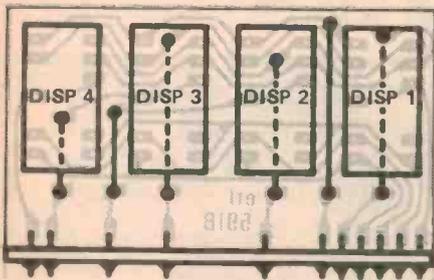



Fig. 1. The positioning of the displays and the links which must be installed before the displays.

Fig. 2. The component overlay for the main board. The common connection from each of the thumbwheel switches goes to the track next to the other connections.

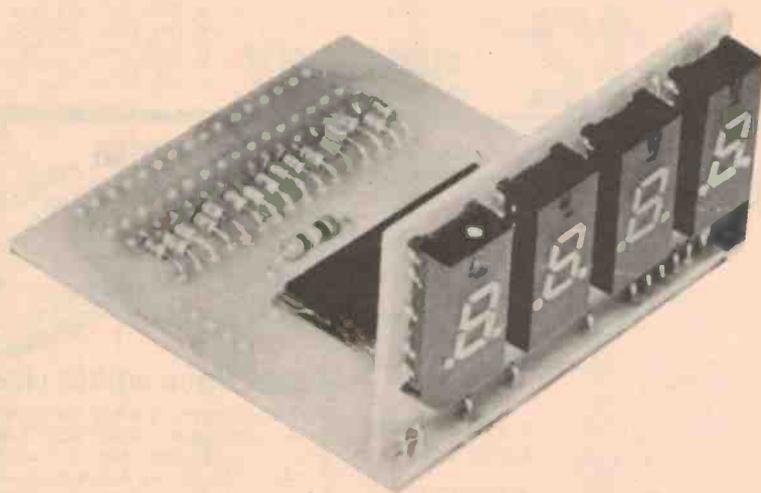

The preset system is designed to use a 4 digit BCD thumbwheel switch (closed = '1') but individual switches can be used if required. Input is in BCD, therefore the switches will have the weighted values 8, 4, 2 and 1. If the

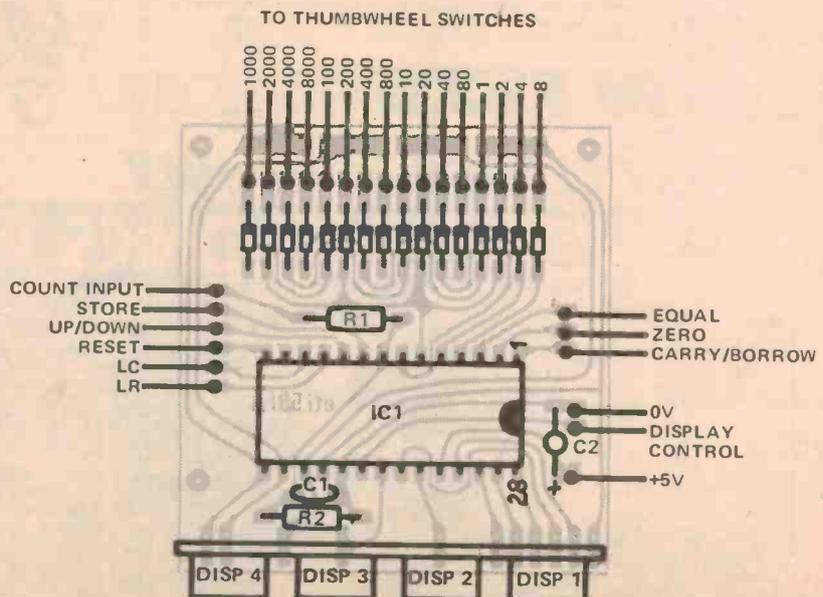preset is not needed then the diodes can be left out. If a preset is needed, but always to a fixed number, links can be inserted to replace the "on" switches and the other diodes left out.



## HOW TO USE IT - ETI 591

This section is normally How it Works but as it is only one IC there is not much to be said!

### Count Input - Pin 8

The counter is incremented or decremented on the leading edge of this input. A schmitt trigger is provided with a 500 mV hysteresis on a 2V trigger point. For high speed operation, or operation from a digital output, delete R2 and C1 and short out R1. Maximum frequency of operation is about 2 MHz.

### Up-Down - Pin 10

If this pin is left open or taken to +5V the counter will be incremented by the count input. If it is taken to 0V the counter will be decremented by the count input.

### Reset - Pin 14

If this pin is left open or taken to +5V the counter is free to be incremented or decremented. If it is taken to 0V the counters will be reset to zero and held there until reset is taken high again.

### Store - Pin 9

If this input is left open or taken to +5V the latches are "closed" and the information which was in the counters at the time the store input went high will be remembered, decoded and displayed. The counters can be reset, incremented or decremented without affecting the display.

If it is taken to 0V the counter contents will continuously be displayed for as long as this input is at 0V. Any change in the counter contents will be shown on the display.

### Load Counter - Pin 12

This is a 3 level input. If it is left open the counter works normally. If it is taken to +5V the counter is loaded with the BCD data which is set on the thumbwheel switches. If the latch is open, this number will also be displayed. If this input is taken to 0V the BCD I/O pins become high impedance. If a 3 level input is to be controlled by other logic outputs they must be tristate devices.

### Load Register - Pin 11

This is also a 3 level input. If it is left open the counter works normally. If it is taken to +5V the register is loaded with the BCD data. If taken to 0V the circuit goes to a low power state with the multiplexing oscillator stopped, the display off and the BCD I/O pins in a high impedance state. The operation of the counter is unaffected except that there is no display.

### Display Control - Pin 20

This is also a 3 level input. If it is left open, leading edge blanking occurs. If all digits are zero then all are blanked. If it is connected to +5V the display is completely blanked irrespective of the value. If taken to 0V all digits are ON irrespective of value.

## SPECIFICATION - ETI 591

|                   |            |
|-------------------|------------|
| Number of digits  | 4          |
| Readout           | LED        |
| Maximum frequency | 2MHz       |
| Input impedance   | 100k       |
| Output drive      | 1 TTL load |
| Supply voltage    | 4.5 - 5.5V |
| Supply current    |            |
| low power mode    | 500µA      |
| all eights        | 100mA      |

## PARTS LIST - ETI 591

### Resistors all 1/2W, 5%

R1 . . . . . 100k  
R2 . . . . . 1M

### Capacitors

C1 . . . . . 33n polyester  
C2 . . . . . 1µ0 35V tantalum

### Semiconductors

IC1 . . . . . ICM 7217A  
D1-D16 . . . 1N914  
DISPLAYS. DL704

### Miscellaneous

PC boards ETI 591A, ETI 591B

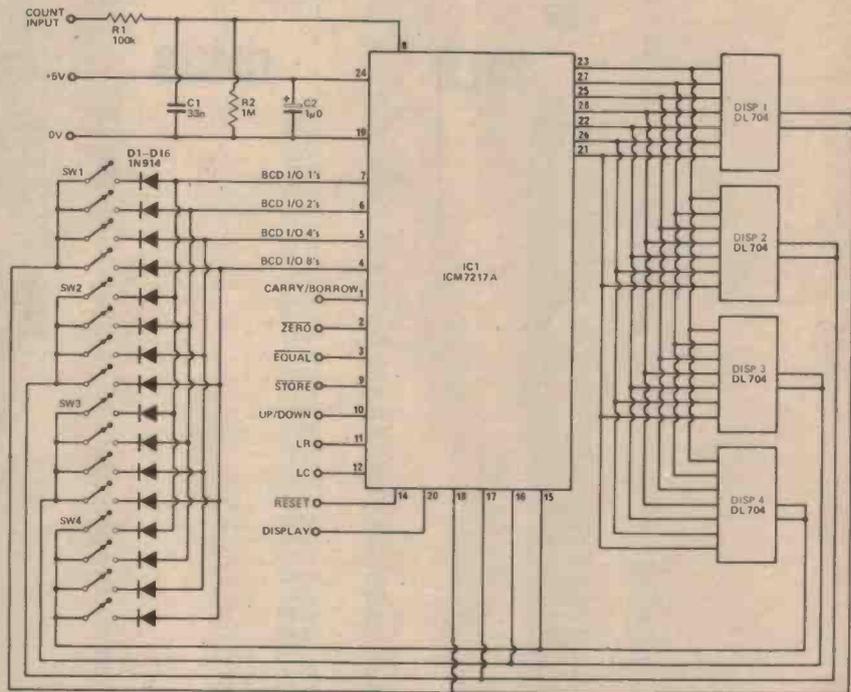


Fig. 3. The circuit diagram for the counter board.

### Scan - Pin 13

The internal multiplexing frequency is nominally 10 kHz giving a digit repetition rate of 2.5 kHz. With a 20 pF capacitor from this point to 0V the frequency drops to 5 kHz and with 90 pF it is about 1 kHz.

### BCD I/O - Pin 4-7

This is a multiplexed data port, normally an output which can drive 1 TTL load. It becomes an input when either LC or LR is at +5V. Pin 7 is the least significant bit.

### Digit Drives - Pins 15-18

These are used both to drive the LEDs and to provide data indicating which digit is being presented at the BCD I/O port. Pin 18 is the least significant digit.

### Zero - Pin 2

If the value of the counter is zero this output will be at 0V.

### Equal - Pin 3

If the value of the counter is equal to the value of the register this output will be at 0V.

### Carry/Borrow - Pin 1

When the counter goes from 9999 to 0000 or from 0000 to 9999 a 500 ns positive pulse occurs on this output. This is connected to the count input of a second unit when an eight digit display is needed.

# SUPER SPECIALS

BD 139 — 50c ea.      MJ2955 — 90c.  
 BD 140 — 50c ea.      2N3055 — 85c.  
 BC 547/8/9 — 15c ea.    T03 Mounting Kits — 5c ea.

## CANNON CONNECTORS

|             |        |
|-------------|--------|
| XLP-3-11    | \$2.30 |
| XLP-3-12c   | \$3.25 |
| XLP-3-31    | \$3.25 |
| XLP-3-32    | \$3.00 |
| XLR-LNE-11c | \$3.05 |
| XLR-LNE-32  | \$4.30 |

Weller cordless soldering iron kit, model WC100DKW — includes batteries, solder, 4 interchangeable tips, battery charger and instructions for only \$29.50.

## TTL

|       |      |       |      |
|-------|------|-------|------|
| 7400  | 28   | 74153 | 1.10 |
| 7401  | 28   | 74154 | 1.70 |
| 7402  | 28   | 74157 | 1.10 |
| 7403  | 28   | 74160 | 1.55 |
| 7404  | 37   | 74164 | 1.55 |
| 7405  | 37   | 74165 | 1.55 |
| 7406  | 50   | 74173 | 2.75 |
| 7407  | 50   | 74175 | 1.65 |
| 7408  | 34   | 74180 | 1.35 |
| 7409  | 34   | 74192 | 1.40 |
| 7410  | 30   | 74193 | 1.40 |
| 7411  | 37   | 74221 | 1.50 |
| 7413  | 54   | 74367 | 1.40 |
| 7414  | 1.03 |       |      |
| 7416  | 60   |       |      |
| 7417  | 60   |       |      |
| 7420  | 30   |       |      |
| 7422  | 30   |       |      |
| 7426  | 45   |       |      |
| 7427  | 45   |       |      |
| 7430  | 30   |       |      |
| 7432  | 43   |       |      |
| 7437  | 50   |       |      |
| 7438  | 50   |       |      |
| 7440  | 30   |       |      |
| 7441  | 1.50 |       |      |
| 7442  | 70   |       |      |
| 7447  | 1.25 |       |      |
| 7448  | 1.25 |       |      |
| 7450  | 35   |       |      |
| 7451  | 35   |       |      |
| 7453  | 35   |       |      |
| 7454  | 30   |       |      |
| 7460  | 35   |       |      |
| 7470  | 65   |       |      |
| 7472  | 45   |       |      |
| 7473  | 60   |       |      |
| 7474  | 65   |       |      |
| 7475  | 65   |       |      |
| 7476  | 45   |       |      |
| 7480  | 1.25 |       |      |
| 7483  | 1.25 |       |      |
| 7485  | 1.45 |       |      |
| 7486  | 65   |       |      |
| 7489  | 1.20 |       |      |
| 7490  | 75   |       |      |
| 7491  | 1.00 |       |      |
| 7492  | 75   |       |      |
| 7493  | 75   |       |      |
| 7494  | 1.10 |       |      |
| 7495  | .95  |       |      |
| 74100 | 2.45 |       |      |
| 74107 | .65  |       |      |
| 74121 | .60  |       |      |
| 74123 | 1.10 |       |      |
| 74132 | 1.25 |       |      |
| 74150 | 1.80 |       |      |
| 74151 | 1.10 |       |      |

## 74LS

|         |      |
|---------|------|
| 74LS00  | 30   |
| 74LS01  | 30   |
| 74LS02  | 30   |
| 74LS03  | 30   |
| 74LS04  | 35   |
| 74LS05  | 35   |
| 74LS08  | 30   |
| 74LS09  | 30   |
| 74LS10  | 30   |
| 74LS11  | 30   |
| 74LS12  | 30   |
| 74LS14  | 1.20 |
| 74LS20  | 30   |
| 74LS21  | 30   |
| 74LS27  | 30   |
| 74LS28  | 40   |
| 74LS30  | 30   |
| 74LS32  | 33   |
| 74LS37  | 45   |
| 74LS38  | 45   |
| 74LS40  | 30   |
| 74LS42  | 1.20 |
| 74LS73  | 1.20 |
| 74LS74  | 50   |
| 74LS75  | 70   |
| 74LS78  | 50   |
| 74LS85  | 1.50 |
| 74LS86  | 50   |
| 74LS90  | 1.20 |
| 74LS92  | 1.20 |
| 74LS93  | 1.20 |
| 74LS95  | 1.50 |
| 74LS109 | 50   |
| 74LS113 | 55   |
| 74LS114 | 55   |
| 74LS138 | 1.20 |
| 74LS151 | 1.20 |
| 74LS154 | 1.60 |
| 74LS157 | .90  |
| 74LS163 | 1.20 |
| 74LS164 | 1.30 |
| 74LS174 | 1.00 |
| 74LS175 | 1.00 |

## CMOS

|      |      |
|------|------|
| 4000 | 25   |
| 4001 | 25   |
| 4002 | 25   |
| 4006 | 1.40 |
| 4007 | 25   |
| 4008 | 1.25 |
| 4011 | 25   |
| 4012 | 25   |
| 4013 | 55   |
| 4014 | 1.35 |
| 4015 | 1.20 |
| 4016 | 50   |
| 4017 | 1.40 |
| 4018 | 1.40 |
| 4019 | .75  |
| 4020 | 1.60 |
| 4021 | 1.40 |
| 4022 | 1.60 |
| 4023 | 25   |
| 4024 | .90  |
| 4025 | .40  |
| 4027 | .80  |
| 4028 | 1.25 |
| 4029 | 1.90 |
| 4030 | .40  |
| 4040 | 1.30 |
| 4041 | 1.25 |
| 4042 | 1.25 |
| 4043 | 1.50 |
| 4044 | 1.50 |
| 4046 | 1.95 |
| 4049 | .60  |
| 4050 | .80  |
| 4051 | 1.20 |
| 4052 | 1.20 |
| 4053 | 1.20 |
| 4060 | 2.65 |
| 4066 | 1.00 |
| 4068 | .40  |
| 4069 | .35  |
| 4070 | .40  |
| 4071 | .40  |

|        |      |
|--------|------|
| 4072   | 40   |
| 4073   | 40   |
| 4074   | 40   |
| 4076   | 1.85 |
| 4077   | 40   |
| 4078   | 40   |
| 4081   | 40   |
| 4082   | 40   |
| 4510   | 1.50 |
| 4511   | 1.50 |
| 4518   | 1.50 |
| 4520   | 1.45 |
| 4528   | 1.20 |
| 4555   | 1.20 |
| 14553  | 7.50 |
| 14584  | 1.25 |
| 74C00  | 40   |
| 74C02  | 40   |
| 74C04  | 40   |
| 74C08  | 40   |
| 74C10  | 40   |
| 74C14  | 1.90 |
| 74C48  | 2.55 |
| 74C73  | 1.20 |
| 74C75  | 1.20 |
| 74C76  | 1.35 |
| 74C90  | 2.25 |
| 74C93  | 2.25 |
| 74C175 | 1.85 |
| 74C192 | 2.25 |
| 74C193 | 2.25 |

## LINEAR

|         |      |
|---------|------|
| 301     | 40   |
| 307     | .65  |
| 308     | 1.35 |
| 311     | .85  |
| 324     | 1.35 |
| 339     | .90  |
| 349     | 2.25 |
| 356     | 1.65 |
| 380     | 2.00 |
| 381     | 2.00 |
| 382     | 2.00 |
| 386     | 1.95 |
| 555     | .95  |
| 556     | .85  |
| 565     | 1.95 |
| 566     | 2.50 |
| 567     | 2.65 |
| 709     | .75  |
| 723(VR) | .55  |
| 741     | .35  |
| 747     | 1.25 |
| 3900    | .90  |
| 3909    | 1.25 |

## VOLTAGE REGS.

|       |      |
|-------|------|
| 309   | 2.25 |
| 317   | 3.50 |
| 323   | 8.25 |
| 325   | 2.60 |
| 723   | .55  |
| 7805  | 1.30 |
| 7806  | 1.30 |
| 7808  | 1.30 |
| 7812  | 1.30 |
| 7815  | 1.30 |
| 7818  | 1.30 |
| 7824  | 1.30 |
| 7905  | 2.25 |
| 7912  | 2.25 |
| 7915  | 2.25 |
| 78L05 | .50  |
| 78L12 | .50  |
| 78L15 | .50  |
| 79L05 | .85  |
| 79L12 | .85  |
| 79L15 | .85  |

## OPTO

|            |      |
|------------|------|
| FND507 C/A | 1.70 |
| FND 357C/C | 1.40 |
| FND 500C/C | 1.50 |
| Red LED    | .22  |
| Green LED  | .35  |
| Yellow LED | .35  |

## DIODES

|                |             |
|----------------|-------------|
| IN4148         | 6c — 5c/100 |
| IN4004         | .9c         |
| IN5625 5A 400V | 45c         |

## I.C. SOCKETS

|            |     |
|------------|-----|
| 8 PIN DIL  | .25 |
| 14 PIN DIL | .30 |
| 16 PIN DIL | .33 |


Also in stock Multimeters, relays, veroboard, solder, solderwick, soldering irons, transformers. All components brand new by top companies. Prices current till end of July.

# ROD IRVING ELECTRONICS

Shop 499, High Street, Northcote. Vic. 3070. Ph (03) 489-8131. Open Mon-Thurs 8 am — 5.30 pm, Fri 8 am — 7 pm. Sat 9 am — 1 pm. Mail Orders: PO Box 135, Northcote. Vic. 3070. Minimum 50c post and pack. Send SAE for free condensed catalogue.

# 16K RAM

Fully Assembled,  
Tested

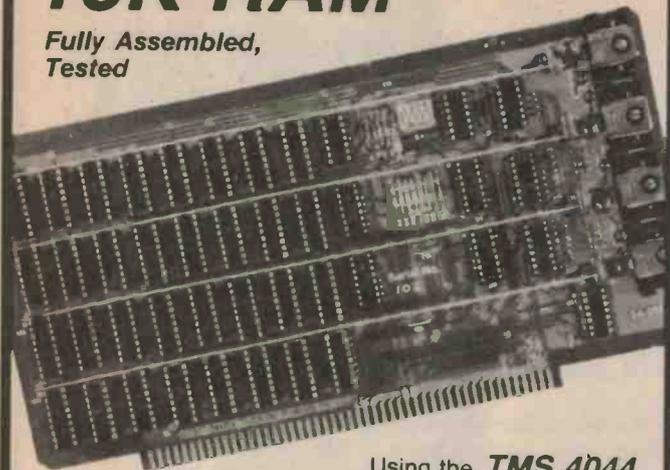

Using the **TMS 4044**

## FULLY S-100 BUS COMPATIBLE

250 nsec. chips-\$495

Z-80A 4 MHz fast — no wait states. If you have a slower CPU now, this board will loaf along — and it WON'T be obsolete when you upgrade!

450 nsec. chips-\$445

Fully static is best — Texas Instruments TMS 4044 chips — no clocks — no refresh — DMA compatible

Easy on your power supply — 8V at 1.7A nominal

Each 4k block addressable to any 4k slot, separately protected by DIP switches, and supplied through its own regulator. Jumpers to customize to any known S-100 system.

First quality factory parts — fully socketed and buffered — quality plated-through PCB with gold plated edge fingers, silk screened and masked both sides — busbars for lower noise

GUARANTEED FOR ONE FULL YEAR

COMING SOON — Professional quality S-100 power supply — uses constant voltage transformer and NASA grade capacitors for ultra-reliable performance.

Post, packing and insurance included in price — add 15 per cent sales tax. Dealer inquiries invited — generous discounts available.



# Centaur Industries

PO Box 37243,  
WINNELLIE, N.T. 5789.

# ... we've moved



## ELECTROCRRAFT PTY. LTD.

have moved to

68 WHITING STREET, ARTARMON. 2064.  
TELEPHONE 438-4308.

We have the largest range of  
antenna accessories in Sydney.  
(Check our prices)

### TRADE AND WHOLESALE SUPPLIED

#### CB EQUIPMENT — SPECIALS

**¼ WAVE SPIRAL TUNED BASE STATION AERIAL.** Omnidirectional (top view) radiation pattern with excellent ground wave and sky wave characteristics. Ideal for "point to point" and Skip communications. Sturdy plated base bracket, 4 telescopic radials and vertical radiator. Spiral tuning stub at base for quick and easy tuning. SWR of 1.1:1 possible. Aerial comes complete with SO 239 socket, U-bolt and saddle and detailed instruction sheet. \$29.00

**SWR & POWER METER.** Model ME-11X is SWR & Power Meter with Directional Coupler incorporated. For SWR measurement it uses the Directional Coupler, comparing the power supplied to and reflected from antenna, and this is indicated on the SWR meter. For power measurement, the power meter indicates the travelling wave power detected by Directional Coupler and its frequency range is determined by the figure of Variable Resistor which is for sensitivity adjustment. Specifications: maximum handling power 100W — SWR indication 1:1 to 3:1 — frequency range 3.5 to 150 MHz. \$16.20.

**BELLING & LEE HELICAL WHIP — Model CB 27/GM/T —** specially designed to provide maximum performance with reduced length. Helically wound on a resilient fibreglass core 76cm in length with complete base. 3.6 m of cable and connector. \$18.00 — below cost!

**BUILD YOUR OWN CB POWER SUPPLY** Ferguson transformers 240V to 18V, 60VA. 3.3A \$8.50. Metal boxes. L2000mm, W135mm, H 70 mm, Black vinyl covered. Holes drilled on chassis for transformers \$3.50.

Spirals ..... \$3.81  
Caravan Antennas from ..... \$13.70

#### FM ANTENNA'S

Channelmaster 7.el H. Gain ..... \$19.68  
Hills FM1 Local ..... \$9.35  
Hills 353 3.el Met. .... \$14.23  
Matchmaster FMG/2 Semi fringe ..... \$18.30  
Matchmaster FMG/6 Outer fringe ..... \$40.93


#### T.V. ANTENNA'S

Hills outer fringe CA.16 phase array ..... \$45.94  
Hills 215 (Australia's best selling high gain  
8.el antenna at a new low price) ..... \$25.20  
Hills EFC.3 (The best of the colour 75 ohm  
antennas very high gain, good anti-ghosting ..... \$65.00  
Channelmaster 3111A 300-75ohm. (Best metropolitan  
Anti ghosting antenna) ..... \$41.98  
Channelmaster 3110 300-75ohm local anti ghosting ..... \$27.96  
Belling Lee plugs ..... .80c  
Belling Lee Coaxial wall sockets ..... \$1.75  
R.F. Amplifiers. Mast-head & Distribution for FM & TV from  
16dB Ecraft ..... \$45.00  
25dB Ecraft ..... \$53.55  
Hills MH1 Masthead 300 ohms ..... \$61.00

Please enclose postage with all orders.

**WE ARE THE EXPERTS — 30 YEARS  
IN THE ANTENNA BUSINESS**

# Jaycar for Audio Kits and Components

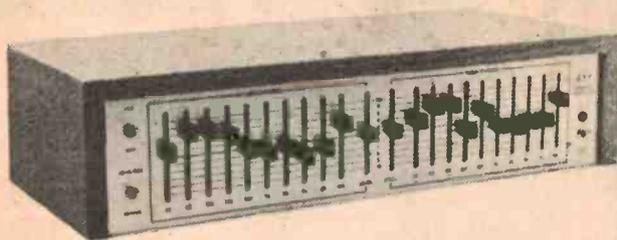


## 485 STEREO GRAPHIC EQUALISER

- This superb equaliser offers 10 octave-centred linear controls for each channel; level match control, in-out switch and tape monitor switch.
- The performance of this unit is equal to some of the best available.

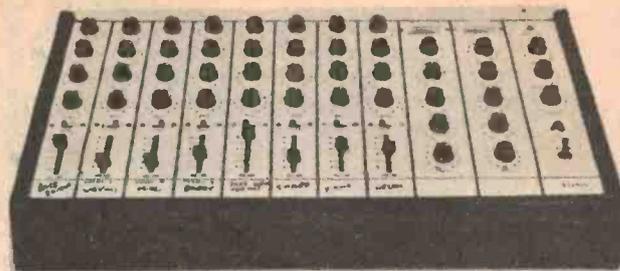**COMPLETE KIT \$105.00 PLUS \$2.50 Freight.**

*Send stamped addressed envelope for specification sheet or \$1.00 for complete construction manual.*



## 414 8-CHANNEL AUDIO MIXER

- 8 input channels each with linear fader, input attenuation switch, bass, treble, echo send and pan controls. High and low impedance PMG inputs.
- 2 output channels with 5 stage equalisation on each channel. VU meters, overload led, master pan, echo and volume controls.
- Black anodised front panel with yellow lettering. Vinyl covered cabinet.

**COMPLETE KIT \$254.00 plus \$5.00 Freight.**

**jaycar** PTY LTD

PO Box K39, Haymarket, NSW.  
2000. 405 Sussex St, Sydney.  
Tel. 211-5077.

— PTY LTD —  
**DEL SOUND** BRISBANE

1 Wickham Tce, (cnr. Wharf St.) 229-6155 (Park at rear)  
35 Logan Rd, Woolloongabba. 391-7048.

**IF WE CAN'T BEAT THE OPPOSITION PRICE,  
WE WILL TRY TO MATCH IT . . . IF WE DON'T STOCK IT,  
WE WILL TRY TO GET IT FOR YOU**

Guess who's now  
a Dick Smith dealer?

### ● SPECIALS IN ● TOP QUALITY COMPONENTS

|                                           |              |
|-------------------------------------------|--------------|
| Motorola 2N3055 . . . . .                 | 75c          |
| Motorola MJ2955 . . . . .                 | 90c          |
| Philips 555 8 P.I.C. . . . .              | 50c          |
| Philips 741 8 P.I.C. . . . .              | 45c          |
| Resistors 1/3 W . . . . .                 | 4c           |
| 10 Way Rainbow Cable. . . . .             | 65c metre    |
| 16 Way Rainbow Cable. . . . .             | \$1.00 metre |
| 6-Piece Jewelers Screwdriver Kit. . . . . | \$2.25       |


Sound Hire — DJ and party for all occasions.

*Old distributor for:*  
RCA Semiconductors and Swan Electronic Components.

**complete  
electronic  
supplies**

Wholesale, trade and mail orders welcome. Add 10%  
post and pack. Stocks and prices valid at 16.6.'78.

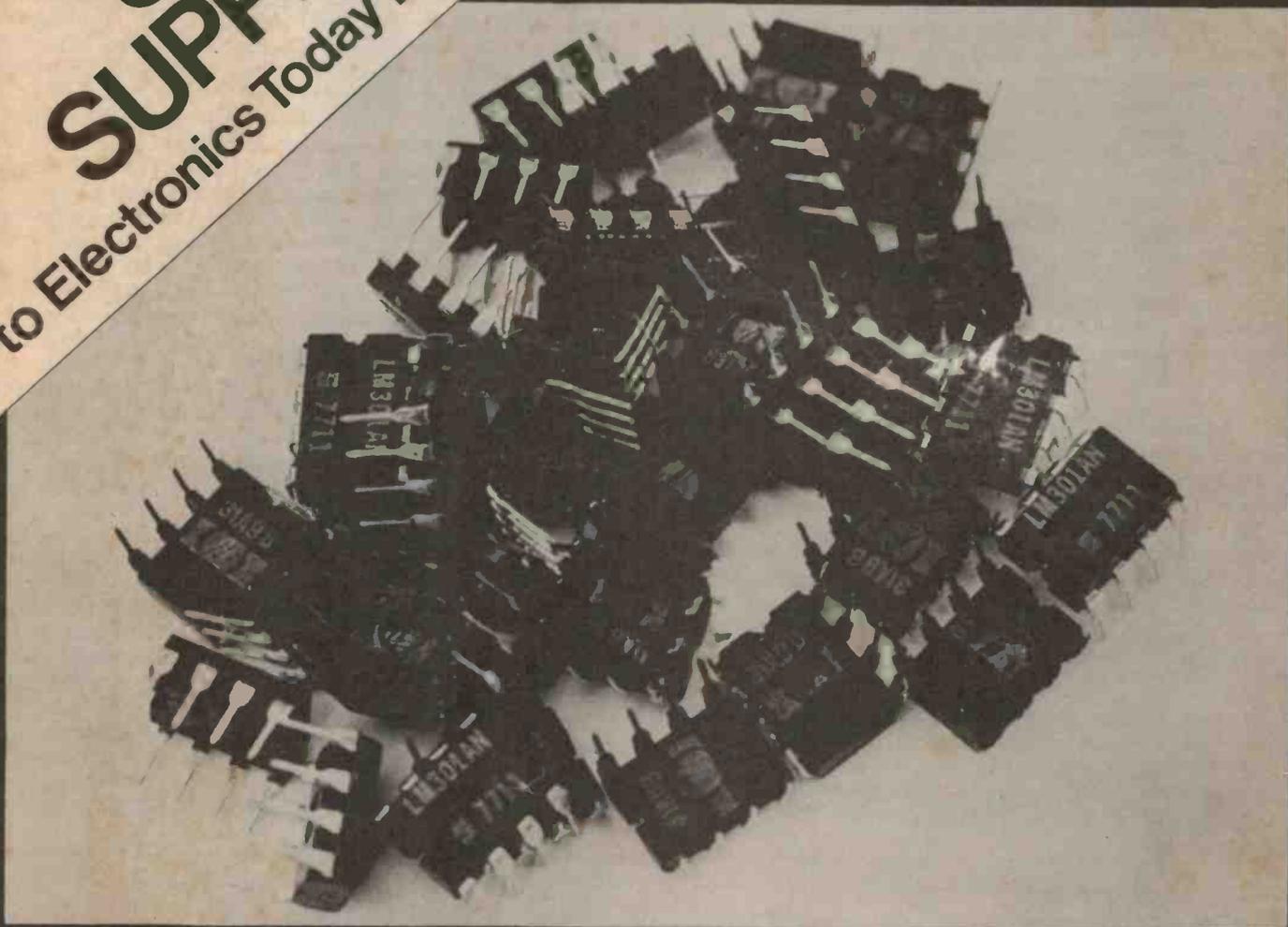**SPECIAL  
SUPPLEMENT**  
to Electronics Today International, July 1978



# **OPERATIONAL AMPLIFIERS**

## **28 USEFUL CIRCUITS**

# OP~AMPS

An operational amplifier is just a high gain amplifier — you stick a voltage in and a much larger one comes out. But you'd never know this from the data sheets. 'Overkill' confuses all but the most experienced. It really doesn't have to be so. Tim Orr explains...

OP-AMPS HAVE TWO inputs, inverting and non-inverting, denoted by - and + respectively. The op-amp amplifies the difference in the voltages applied to these two inputs, the output going positive if the + input is positive with respect to the - input, and vice versa. Without extra circuitry, though, an op-amp is virtually useless, for the gain is too high to be useable and distortion is excessive. Fortunately both parameters can be controlled by feedback.

An op-amp with negative feedback is shown in Fig. 1. Two resistors set the closed loop voltage gain, and as long as this is small compared to the open loop gain, it will be determined by the resistor ratio  $R_F/R_I$ . The open loop gain, the voltage gain when  $R_F$  is removed, is typically 1 000 000. This massive gain is clearly much too large to be used without feedback. Closed loop voltage gains of 100 are about as much as it is practical to use.

## Biased example

The arrangement in Fig. 1 is known as a 'virtual earth' amplifier. The non-inverting input is connected to earth, and the inverting input is maintained by the feedback applied via  $R_F$  at a voltage which is virtually earth potential.

The input impedance of the amplifier in Fig 1 is simply  $R_I$ . The output impedance is a little more complicated, approximately:—

$$\frac{\text{output impedance of the op amp} \times \text{closed loop gain}}{\text{open loop gain}}$$

Suppose we want an amplifier with a gain of 10, and an input impedance of 1M. This means that  $R_I$  is 1M. Therefore  $R_F$  must be 10 M (see Fig. 2). With a 1 V sinewave as the input signal we get a 10 V sinewave as the output. However, when the input signal is held at 0V, it is positive! This is an error


voltage, which may be undesirable. The cause of the problem is the 'INPUT BIAS CURRENT' of the op-amp. The input of many op-amps looks like the circuit shown in Fig. 3. If these transistors are to operate correctly they need a standing emitter current which implies that they need an input base current. It is this base current which is the op-amp's 'INPUT BIAS CURRENT'. For a 741 this current can be as large as  $0.5 \mu\text{A}$ . In the arrangement of Fig. 2 this current can only come through  $R_F$ , which means that the output voltage could be as large as  $0.5 \mu\text{A} \times 10 \text{ M}$ , which is +5 V! One way to remedy this error is to use the circuit shown in Fig. 4. A resistor has been inserted between the non-inverting input and ground. This resistor has the value of  $R_F$  in parallel with  $R_I$ . It allows both the inputs to sink slightly and thus maintain the voltage balance at the inputs. The output voltage is then nearly 0 V. However, the two input transistors may not be that well matched, so the bias currents into each input may be different. This is known as the 'INPUT OFFSET CURRENT' and its effect can be nulled by making the 910 k resistor in Fig. 4 a variable resistor. But even if the bias currents (for say a 741) were zero, then the output voltage would still not be 0 V.

## Get set, they're off

The output voltage could range between  $\pm 60 \text{ mV}$ . This is due to the 'INPUT OFFSET VOLTAGE' which for a 741 can be as much as  $\pm 6 \text{ mV}$ , which is then multiplied by the closed loop voltage gain of the stage (in this case 10 giving us  $\pm 60 \text{ mV}$ ). This can be compensated by using the circuit shown in Fig. 5. Terminals 1 and 5 on a 741 can be used to compensate for the input offset voltage. The input offset voltage is the  $V_{be}$  imbalance between the two input transistors.


Now that we know how to eliminate the spurious dc offsets, we can try designing some dynamic circuits and find out why they don't work as expected! For example, try
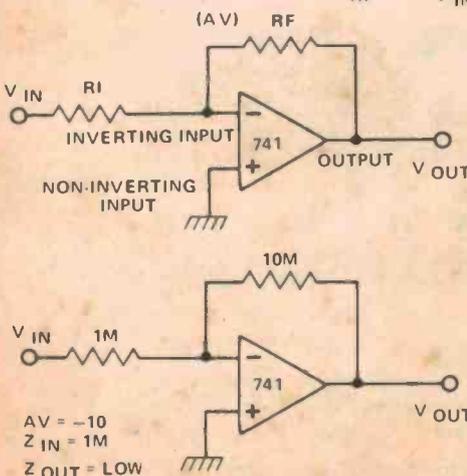
$$\text{CLOSED LOOP VOLTAGE GAIN} = -\frac{R_F}{R_I} = \frac{V_{OUT}}{V_{IN}}$$



Figs 1 and 2 show (upper) the basic inverting op-amp stage. Gain is given by the ratio of resistors  $R_F/R_I$ , input impedance is simply  $R_I$ , while the output impedance is more complicated (see text). Fig. 2 (lower) shows a stage with a gain of 10 and an input impedance of 1 M.

## NPN DIFFERENTIAL PAIR

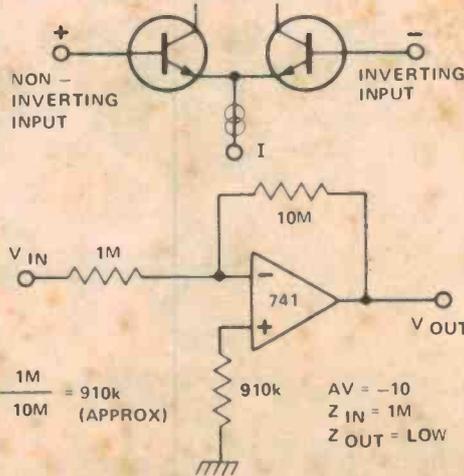

Figs 3 and 4 (left) show (upper) a typical op-amp input stage. This is a differential amplifier made up of a pair of NPN transistors driven by a constant current source. Fig. 4 (left) shows a 910 k resistor in series with the + input of the op-amp. This reduces the effects of the input offset current.

putting a 1 V sinewave at 200 kHz into the circuit shown in Fig. 5. What you would expect is a 10 V, 200 kHz sinewave at the output — but you don't get one. What appears is a rather bent 200 kHz triangle waveform. This is because the 'SLEW RATE' of the op-amp has been exceeded. The slew rate is the speed at which the output voltage can move, and for a 741 is typically 0.5 V/μs when it crosses zero, so the op-amp, faced with this demand, just gives up and slew limits, drawing out straight lines as it does so.

### Listen to the band (width)

Another limitation is 'BANDWIDTH'. A 741 has a GAIN BANDWIDTH product of approximately 1 MHz. This means that the product of the voltage gain times the operating frequency cannot exceed 1 MHz.

For example, if you want the amplifier to have a gain of 100, then the maximum frequency at which this gain can be obtained is 10 kHz. Figure 6 illustrates this phenomenon. Curve A is the open loop response, note that the voltage gain is 1 at 1 MHz, hence the gain bandwidth product of 1 MHz. The slope of the curve is -20 dB/decade, which is caused by a single 30 pf capacitor inside the IC. Now, if the resistor ratio is set to give a voltage gain of 100, then the op-amp gives a frequency response shown by curve C, which is flat up until 10 kHz. A gain off 10 rolls off at 100 kHz (D) and a gain of 1 000 rolls off at 1 kHz (B). Thus it is very easy to see just what the closed loop frequency response will be. However, don't forget the slew rate problem. You may be able to construct an amplifier with a voltage gain of 10, which works up to 100 kHz, but the output voltage will be limited to less than 3 Vpp! Another problem is distortion in the op-amp. Negative feedback is used to iron out any distortion generated by the op-amp, but negative feedback relies on there being some spare voltage gain available. For instance, say the op-amp generates 10% distortion and there is a surplus voltage gain of 1 000,

$$\text{i.e. } \left( \frac{\text{open loop gain}}{\text{closed loop gain}} \right),$$

then the distortion will be reduced to approximately,

$$\frac{\text{open loop distortion}}{\text{surplus voltage gain}} = \frac{10\%}{1\,000} = 0.01\%$$

So, negative feedback is used to eliminate distortion products. However, if there is no surplus voltage gain, as in the case of a 741 amplifier working at 10 kHz, with a closed loop gain of 100, the distortion will rise dramatically at this point.

### Current thinking

Most op-amps have a voltage output, although some have a

current output. If you short-circuit a voltage output then large currents could flow and thermal destruction might follow. To overcome this problem, most op-amps have a current limited output so that they can tolerate an indefinite short to ground. A 741 is limited to about 25 mA. Another current of note is the supply 'BIAS CURRENT'. This is the current consumed when the op-amp is not driving any load. For a 741 this current is typically 2 mA, which makes it unsuitable for some battery applications.

There are some op-amps which can be programmed by inserting a current into them so that their supply current can be controlled. This means that they consume only micropower when in their 'standby' mode, and can be quickly turned on to perform a particular task.

### Voltages differently

In the few examples shown so far, the op-amp has been used to amplify voltages which have been generated with respect to ground. However, sometimes, it is required to measure the difference between two voltages. In this case you would use a 'Differential' amplifier, Fig. 7. By using two matched pairs of resistors, the formula for the voltage gain is made very simple. It is thus possible to superimpose a 1 V sinewave on both the inputs, and yet have the output of the amplifier ignore this common mode signal and amplify only differential signals. The amount by which the common mode signal is rejected is called the CMRR (the Common Mode Rejection Ratio) and is typically 90 dB for a 741. Thus a common mode 1 V signal would be reduced to 33 μV.

Another rejection parameter to be noted is the supply voltage rejection ratio. For a 741 the typical rejection is 90 dB; that is, if the power supply changes by 1 V the change in the output voltage will be 33 μV.

When designing with op-amps it is very important to know what voltage range the inputs will work over, and the maximum voltage excursion you can expect at the output. For instance, the 741 can operate with its inputs a few volts from either power supply rail, and its inputs can withstand a differential voltage of 30 V (with a power supply of 36 V).

This is not true of all op-amps, some have a very limited differential input voltage range, for instance the CA3080 will zener when this voltage exceeds 5 V and the amplifier performance will then be drastically changed.

The output excursion of the op-amp is also important. The 741 can only typically swing within about 2 V of either supply rail, whereas the CMOS op-amp can swing to within 10mV of either rail so long as the load into which they are driving is a very high impedance.

Continued on page 80. . .

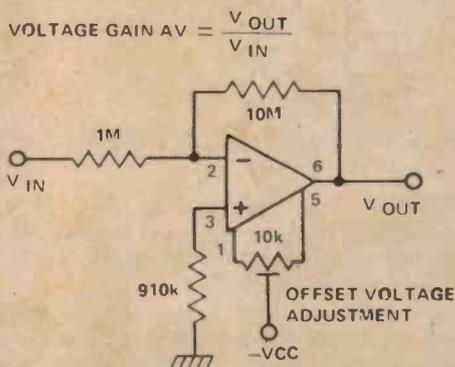


Fig. 5. A variable resistor connected between pins 1 and 5 of a 741 can be used to reduce the effects of the input offset voltage.

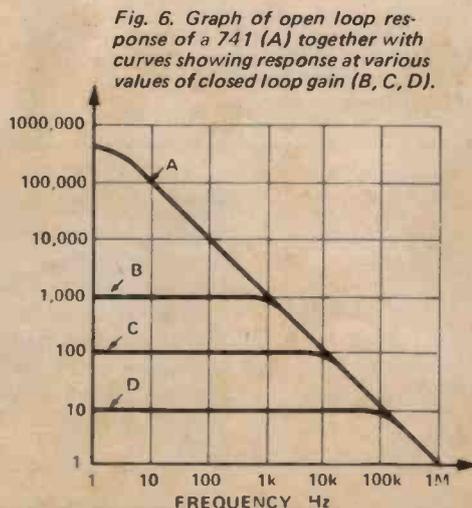


Fig. 6. Graph of open loop response of a 741 (A) together with curves showing response at various values of closed loop gain (B, C, D).

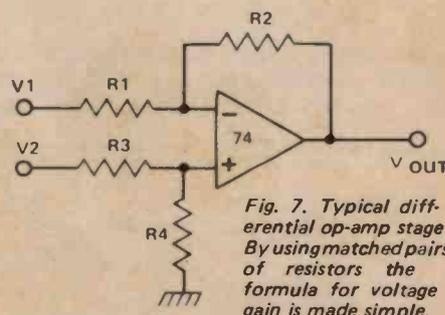


Fig. 7. Typical differential op-amp stage. By using matched pairs of resistors the formula for voltage gain is made simple.


$$V_{OUT} = \left[ \frac{R1 + R2}{R3 + R4} \right] \frac{R4}{R1} V2 - \frac{R2}{R1} V1$$

$$\text{BUT IF WE MAKE } R1 = R3 \\ \text{AND } R2 = R4$$

$$\text{THEN } V_{OUT} = \frac{R2}{R1} (V2 - V1)$$
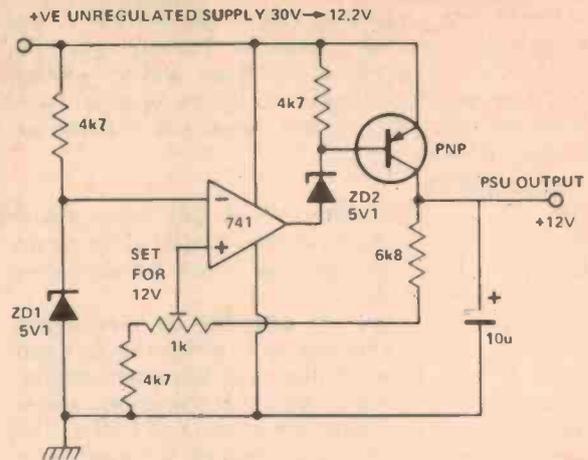
## 12 V REGULATED POWER SUPPLY

The large open loop voltage gain of an op-amp is very useful in providing a regulated low output impedance power supply. A 5V1 voltage reference is generated by a zener diode ZD1 (this voltage reference could be made more stable by running it at constant current). A PNP transistor is used as a series regulator. However, this transistor inverts the signal from the op-amp output, and so, in order to get negative feedback, the feedback is taken to the non-inverting input! The operations is as follows. The inverting input is held at 5V1. If the 'PSU OUTPUT' tries to fall, the voltage at the non-inverting input falls. Therefore the op-amp's output will also fall, thus turning on the PNP transistor which then pulls up the 'PSU OUTPUT'. Thus the output voltage is stabilised. Also, the output impedance is very low, due to this negative feedback. The output impedance at high frequencies (where the op-amp gain is low) is further reduced by the 10 μ capacitor. To squeeze the last drop of voltage out of the system, before a collapsing unregulated supply rail causes the regulated supply to drop out, a 5V1 zener diode (ZD2) has been included. This allows the op-amp output to work at about 7 volts below the unregulated supply rail. Thus, a regulated output is maintained until the PNP transistor saturates. This means that the unregulated rail can fall to within about 200 mV of the regulated rail!



## SIMPLE INTEGRATOR

An op-amp and a capacitor can be used to implement, to a high degree of accuracy, the mathematical process of integration. In this case, current is summed over a period of time and the resultant voltage generated is the integral of that current as a function of time. What this means that if a constant voltage is inputted to the circuit, a ramp with a constant slope is generated at the output. When the input is positive, the output of the op-amp ramps negative.

In doing so it pulls the inverting terminal negative so as to maintain a 'virtual earth' condition. In fact the input current ( $V_{in}/R1$ ) is being equalled by the current flowing through the capacitor, thus equilibrium is maintained. The equation governing the behaviour of a capacitor is  $C \times dV/dt = i$ , where  $dV/dt$  is the rate of change of voltage across the capacitor.


Therefore

$$\frac{dV}{dt} = \frac{i}{C}$$

Thus

$$\frac{dV}{dt} = \frac{V_{in}}{R1C}$$

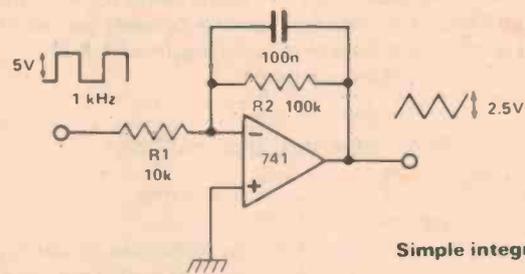So, when a square wave is applied to the circuit in Fig. 10, triangle waveforms are generated. R2 was added to provide DC stability. Its inclusion does slightly corrupt the



Simple integrator.

mathematical processes, but not enormously. A good point about this integrator design is that it has a very low output impedance. You can put a load on the output and the op-amp will still generate the same waveform — that's what is so nice about negative feedback.

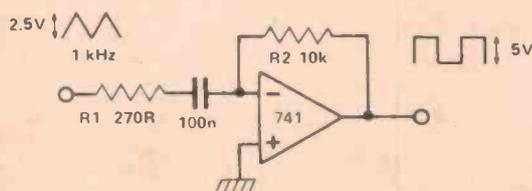


Fig. 11. Simple differentiator.


## SIMPLE DIFFERENTIATOR

Mathematically, differentiation is the reverse process to integration. Thus, in the differentiator circuit the C and the R are reversed with respect to the integrator circuit.


The input waveform is a triangle with a constant rise and fall slope. This constant slope, when presented to a capacitor will generate a constant current. When the slope direction reverses, then so will the current flow. This current when passed through a resistor (R1), will then generate a square wave.
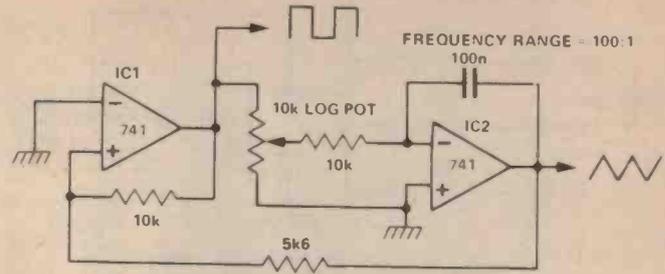
## TRIANGLE SQUARE OSCILLATOR

A Schmitt trigger and an integrator can be used to construct a very reliable oscillator which generates triangle and square waveforms. The operation of the circuit is very simple and always self starting. The Schmitt trigger is formed from IC1, the integrator from IC2. Suppose the output of the Schmitt is positive. This will cause the integrator to generate a negative going ramp. This ramp is then fed back to the input of the Schmitt. When the lower hysteresis level has been reached the output of the Schmitt snaps into its negative state, current is taken out of the integrator which then generates a positive going ramp. The integrator's output ramps up and down between the upper and lower hysteresis levels. The speed at which the integrator moves is determined by the magnitude of the voltage applied to it. In this circuit, the magnitude of the voltage and hence the oscillation frequency, are controlled by a potentiometer, giving a 100 to 1 control range. This




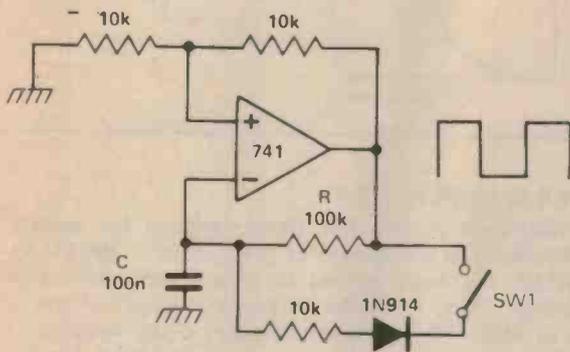circuit is the basis of most function generators. By bending the triangle it is possible to synthesise an approximation to a sinewave. With a bit more electronics it is also possible to make the oscillator voltage controlled.


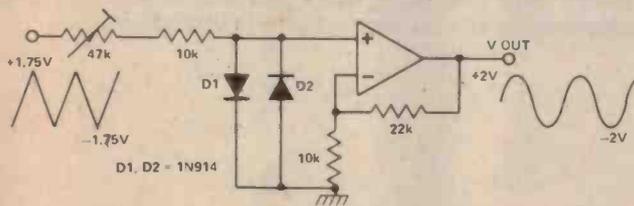
## SINGLE OP-AMP OSCILLATOR

This circuit has a Schmitt trigger and a 'sort of integrator' all built around one op-amp. The positive feedback is via the 10 k resistors. The 'integration', (the timing) is controlled by the RC network. The voltage at the inverting input follows that of the RC charging exponential, except that it is confined to be within the upper and lower hysteresis levels. Thus the hysteresis levels and the RC time constant determine the frequency of operation. It is possible to make the output square wave have a large mark to space ratio. By closing the switch SW1, the discharge time of the capacitor becomes eleven times faster than the rise time. Thus a square wave with an 11:1 mark space ratio is generated.




## SIMPLE TRIANGLE TO SINEWAVE CONVERTER


Here is a simple way of converting a triangle to a sinewave. The logarithmic characteristic of the diodes is used to approximate that of a sine curve. Distortion is 5% or so. However, the distortion may be tolerable if the sinewave is only used to generate audio tones.
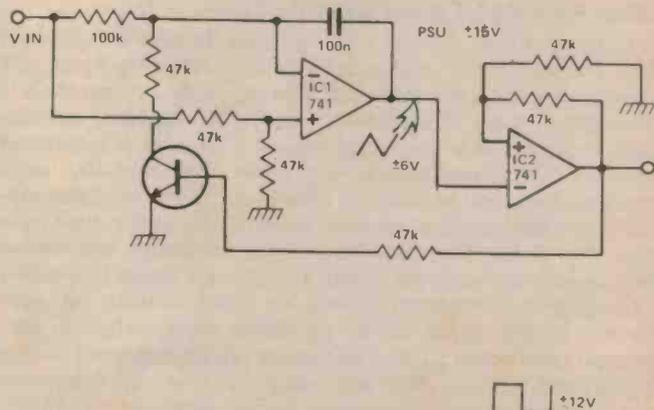
## LINEAR VOLTAGE CONTROLLED OSCILLATOR

This oscillator is very similar to the triangle square wave oscillator shown on this page, except that this one is voltage controlled. The integrator and Schmitt trigger action are the same as before, but the feedback has been altered. The input voltage  $V_{in}$  is applied differentially to the integrator via the resistor network. The larger the value of  $V_{in}$ , the faster the integrator ramps up and down. Thus the frequency of the operation is determined by an external positive control voltage. The frequency is linearly proportioned to this control voltage.

When the output of the Schmitt is low, Q1 is off and all the input voltage is applied to the inverting input. Half of the input voltage is always applied to the non-inverting input. Therefore the integrator's output ramps downward until the Schmitt flips into its positive state. Now, Q1 is switched on and the voltage at the inverting input is negative with respect to the non-inverting input. Hence the integrator now ramps upwards.




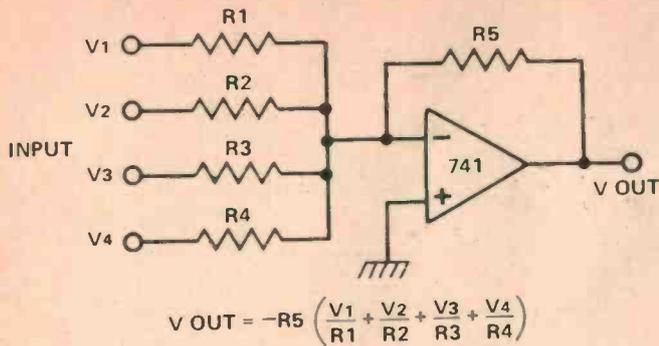


### BASIC SUMMING CIRCUIT (MIXER)

A virtual earth amplifier can be used to mix several signals together. The output voltage is a mixture of all the inputs. The amount of an input that appears at the output is inversely proportional to the input resistor. If the input voltages are fed into potentiometers before being fed to the mixer, then their individual levels can be manually adjusted. This is the basis of most audio mixers, although the cheaper units use op-amps. Most op-amp mixers will degrade the signal to noise ratio of the signals by more than a good discrete component amplifier.
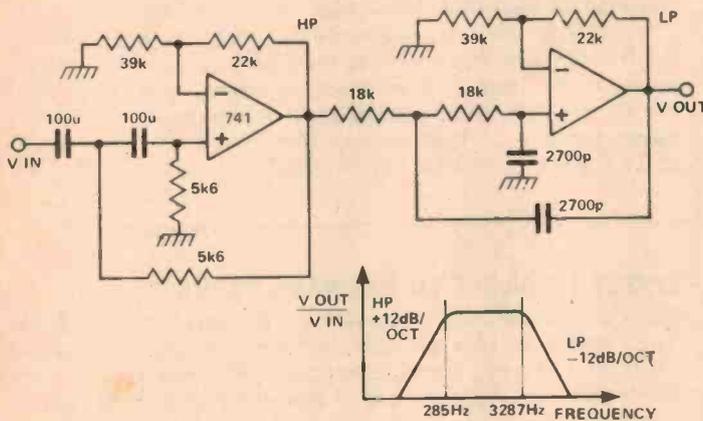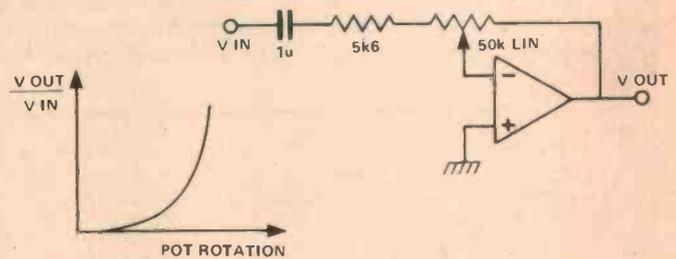
### TURNING A LINEAR POT INTO A LOG POT

By using the virtual earth characteristic of an op amp, a linear pot can be made to have the characteristics of a log pot. It seems to be fair to say that low cost linear pots are far more linear than log pots are logarithmic. Thus the linear pot can be turned into a better log pot than the actual log pot itself. By varying the resistor ratio 5k6 to 50 k, other laws can be produced, such as something in between log and linear or maybe a law that is even more extreme than log.




### SIMPLE SPEECH FILTER

The telephone system has been designed for speech communication. The bandwidth of the system is 300 Hz to 3400 Hz, which has been arrived at after many years of experimentation. Thus, it is true to say that much of the information in speech is contained between these frequency limits. The circuit shows a filter structure that will simulate the telephone bandwidth. It could have many uses, for instance as a 'speech filter' for noisy radio reception or land line communications, or as a voice detector for a light show.
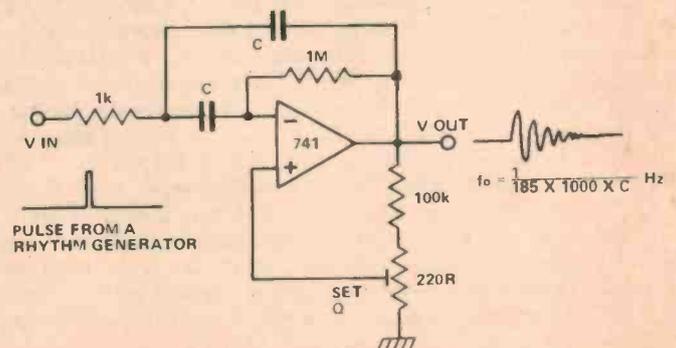
### SIMPLE MUSICAL CHIME GENERATOR

The circuit shown is that of a multiple feedback band-pass filter. The present is used to add some positive feedback and so further increase the Q factor. The principle of operation is as follows. A short click (pulse) is applied to the filter and this makes it ring with a frequency which is its natural resonance frequency. The oscillations die away exponentially with respect to time and in doing so closely resemble many naturally occurring percussive or plucked sounds. The higher the Q the longer the decay time constant. High frequency resonances resemble chimes, whereas lower frequencies would be like claves or bongos. By arranging several of these circuits, all with different tuning, to be driven by pulses from a rhythm generator an interesting pattern of sounds can be produced. There may be some stability problems when high Q or high frequency operation is involved. To achieve better performance, an op-amp with a greater bandwidth than the 741 should be used.

Alternatively, a different structure, such as a state variable filter could be used. Qs of up to 500 can be obtained with this latter circuit.




## MUSICAL ENVELOPE GENERATOR AND MODULATOR

A gate voltage is applied to initiate the proceedings. When the gate voltage is in the ON state, Q1 is turned on, and so the capacitor C is charged up via the attack pot in series with the 1 k resistor. By varying this pot, the attack time constant can be manipulated. A fast attack gives a percussive sound, a slow attack the effect of 'backward' sounds. When the gate voltage returns to its off state, Q2 is turned on and the capacitor is then discharged via the decay pot and the other 1 k resistor, to ground. Thus the decay time constant of the envelope is also variable.

This envelope is buffered by IC1, a high impedance voltage follower and applied to Q3 which is being used as a transistor chopper. A musical tone in the form of a squarewave is connected to the base of Q3. This turns the transistor on or off and thus the envelope is chopped up at regular intervals, the intervals being determined by the pitch of the squarewave.

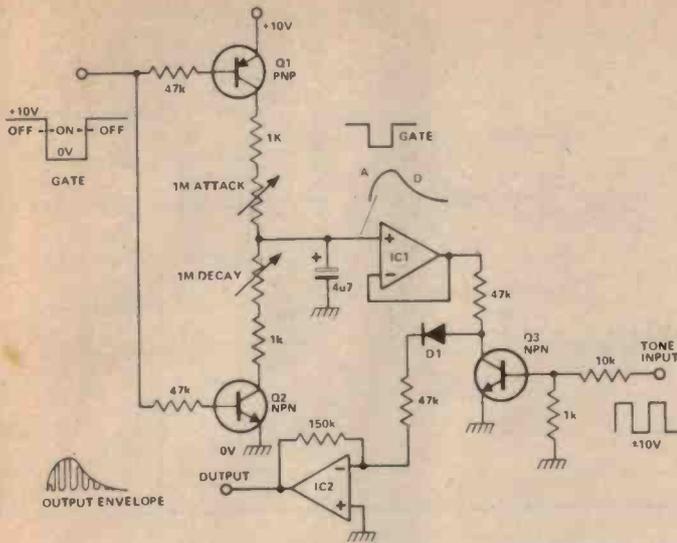The resultant waveform has the amplitude of the envelope and the harmonic structure of the squarewave. IC2 is used as a virtual earth amplifier to buffer the signal and D1 ensures that the envelope dies away at the end of a note.




## SIMPLE MUSICAL ENVELOPE GENERATOR


A simple generator can be constructed using the CA3080 (made by RCA). This circuit will also enable the use of an audio waveform the harmonic structure of which will not be significantly affected as it is modulated. The CA3080 is an op amp with a difference. It has a current output and an extra input into which a current,  $I_A$  is fed. The output is the product of the input voltage  $X I_A$ . Thus the  $I_A$  can be used to control the amplifier's gain.

The input voltage range for low distortion operation is very low, of the order of  $\pm 25$  mV.

The CA3080 is being used as a two-quadrant multiplier. A small voltage, ( $\pm 25$  mV), is applied to its non-inverting input. When the switch S1 is closed, the capacitor C is charged up and a current of about  $150 \mu A$  flows into the  $I_A$  input terminal. When S1 is opened, C discharges through the 150 k resistor into the  $I_A$  input. This current dies away exponentially. As the output is the product of the input voltage  $X I_A$ , then

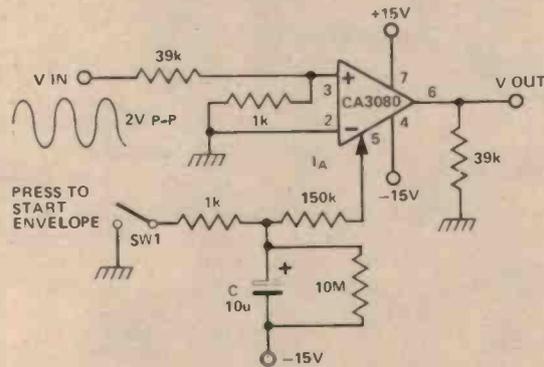

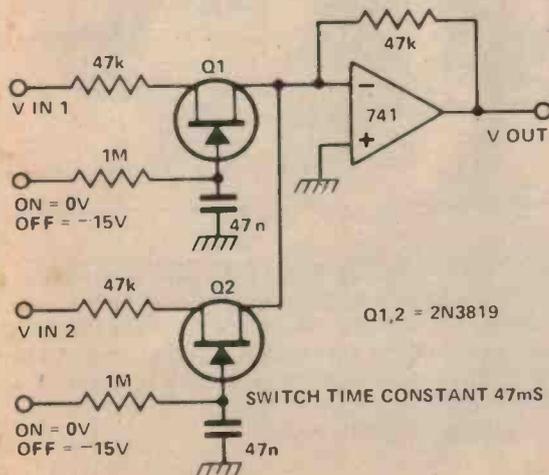an exponential envelope is generated. Breakthrough after the decay is very good, better than  $-80$  dB.




## SILENT AUDIO SWITCHING

Sometimes electronic switches for audio signals are required. FETs can be used to perform the switching, but they can cause distortion, the resultant output impedance is not very low and clicks generated by the switching signal can break through. The circuit shown virtually eliminates all of these problems. By using an op-amp a very low output impedance is obtained as well as the possibility of selecting or mixing one or more of many input channels. Because of the virtual earth mixing, the voltage across any FET that is switched on is very small. If the output voltage is 1V and the FETs ON resistance is 470R, then the voltage across the FET is about 10 mV. When large voltages are applied to a turned on FET, the distortion is large, but if the voltage is small, (10 mV say), the distortion could be less than 0.1%. Thus the virtual earth mixing enables low distortion operation. Lastly, to stop the generation of switching clicks, a time constant of 47 msec has been enforced at the gate of the FETs.
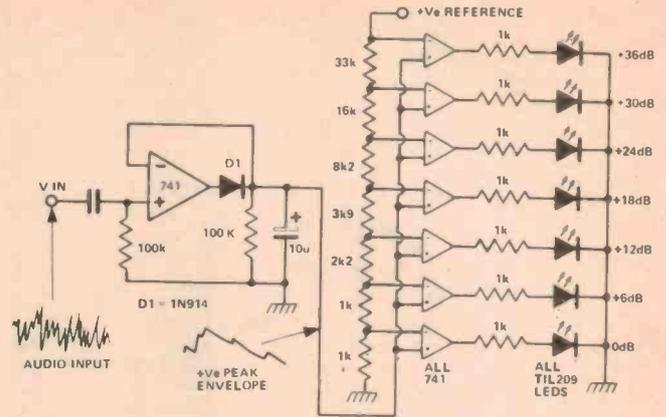
## LED BAR PPM DISPLAY FOR AUDIO


The peak voltage detector can be used to control an illuminated audio level monitor having the same characteristics as a PPM (Peak Programme Meter). A bar column of LEDs is arranged so that as the audio signal level increases, more LEDs in the column light up. The LEDs are arranged vertically in 6 dB steps. A fast response time and a one second decay time has been chosen so as to give an accurate response to transients and a low 'flicker' decay characteristic. The op-amps that drive the LEDs are used as comparators. On each of their inverting inputs they have a dc reference voltage, which increases in 6 dB steps up the chain. All of their non-inverting inputs are tied together and connected to the positive peak envelope of the audio signal. Thus as this envelope exceeds a particular voltage reference, that op-amp output goes high and the LED lights up. Also, all the LEDs below this are illuminated.


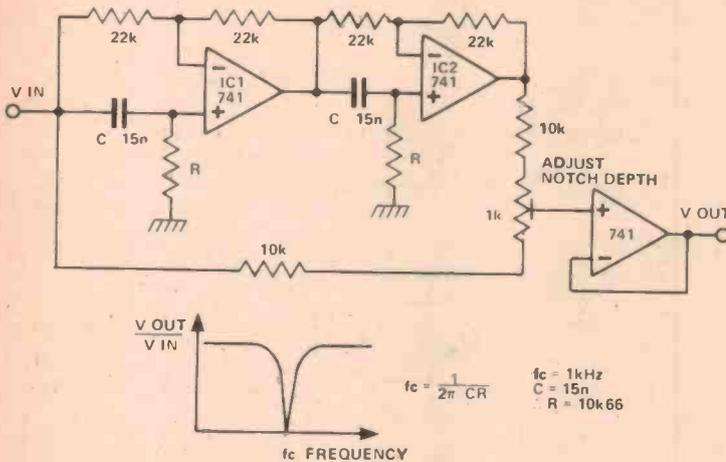
## ALL-PASS NOTCH FILTER



Sometimes when processing analogue signals a constant tone causes a nuisance and so an active filter is called upon to 'notch' it out. The filter can be tuned so that its notch is at exactly the same frequency as the unwanted signal so that it can be selectively attenuated. This method is sometimes used to remove mains hum. The circuit works as follows IC1 and 2 are a pair of all-pass filters. These filters have a flat frequency response, but their phase changes with frequency. Their overall maximum phase shift is  $360^\circ$ , a phase shift of  $180^\circ$  occurring at a frequency of  $1/2CR$  Hz. At this frequency the signals are inverted. Thus, by mixing the phase delayed signal with the original, cancellation can be produced which forms a notch in the frequency response. The preset is used to get the deepest notch available. The operating frequency can be changed by varying the two resistors R. For instance for 50 Hz operation, R should be:-

$$10.66k \times \frac{1000}{50} = 213.2k \quad \text{Nearest E12 fit is } 220k$$


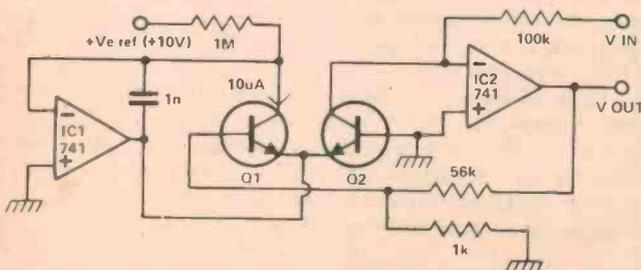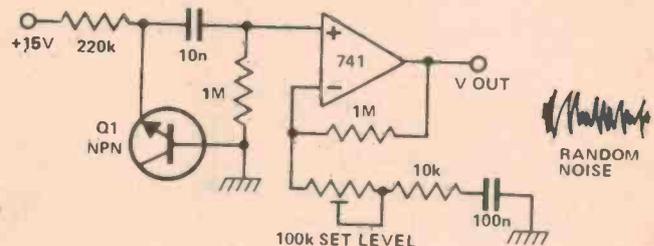
## NOISE GENERATOR

The zener breakdown of a transistor junction is used in many circuits as a noise generator. The breakdown mechanism is random and so generates a small noise voltage. Also this voltage has a high source impedance. By using the op-amp as a high input impedance, high ac gain amplifier, a low impedance, large signal noise source is obtained. The preset is used to set the noise level by varying the gain from 40 to 20 dB.




## LOGARITHMIC VOLTAGE TO VOLTAGE CONVERTER


The output voltage is logarithmically proportional to the input voltage. The difference between this circuit and the previous is that the exponentiator is in the feedback loop of the op-amp and hence the mathematical function has been inverted. The circuit is useful for performing true logarithmic compression or for converting linear inputs into dBs.
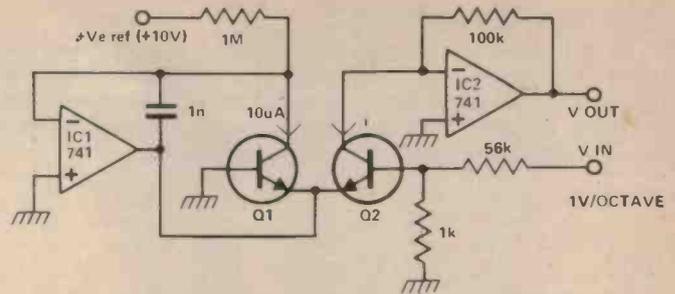
## EXPONENTIAL VOLTAGE TO CURRENT/VOLTAGE CONVERTER

The circuit shown converts a linear input voltage into an exponential current or voltage. This type of circuit is used in music synthesizers to change linear control voltages into musical intervals. That is, if the circuit were used to control an oscillator, input increments of 1 V would change the pitch by one octave. The exponential characteristics of a transistor are employed to generate the correct transfer function. Q1 and Q2 are matched pairs of transistors, preferably a transistor dual. IC1 maintains Q1 at a constant current. Thus, the op-amp serves only to bias the emitter of the second transistor Q2 into a suitable operating region. The purpose of Q1 is to generate this bias voltage. The base emitter junction of a transistor



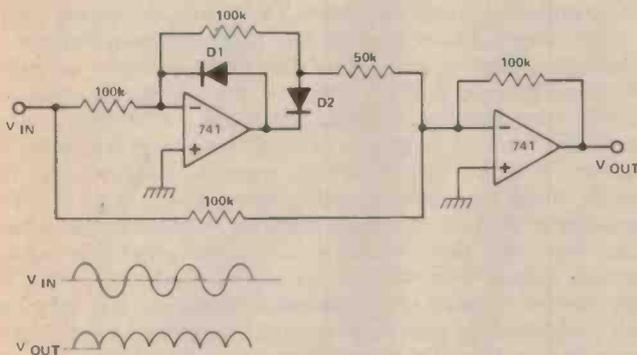has a high temperature coefficient ( $-1.9 \text{ mV}/^\circ\text{C}$ ) and so the reason for using a matched pair is to use the first transistor, Q1, to provide temperature compensation for the second.



## PRECISION HALF WAVE RECTIFIER

Rectifying small signals with any accuracy can be very difficult using diodes only due to their forward voltage drop of about 0.6 V. However, an op-amp can be used to reduce this voltage drop to virtually nothing. Consider the circuit shown. There is negative feedback so that 'virtual earth' circumstances exist. When  $V_{IN}$  is positive, D1 conducts to maintain the virtual earth, D2 is reverse biased and so the output is just a 100 k resistor connected to 0 V. When  $V_{IN}$  goes negative, the output rises positively, D2 is turned on and D1 turned off. As the virtual earth is being maintained, the output voltage is the exact inverse of the input voltage. This is true for all negative inputs. Therefore, the output is composed of positive going half sinewaves. Precision half wave rectification has occurred. In fact the diode error is very small, being equal to


$$\frac{600 \text{ mV}}{(\text{surplus voltage gain})}$$

Therefore as the input frequency increases, and the surplus voltage gain decreases, precision falls.

By adding together the original and the half wave rectified signals together in the right ratio, it is possible to fill in the half cycle gaps and thus to generate precise full wave rectification. The addition of one summing op-amp and three resistors is all that is needed as shown opposite.
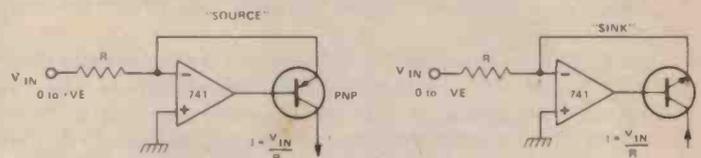
## VOLTAGE TO CURRENT CONVERTER

The virtual earth of an op-amp and the current source characteristic of a transistor can be combined to produce a precision linear voltage to current converter. Consider the 'SOURCE' circuit. A positive voltage is applied and the op-amp adjusts itself so that a 'virtual earth' condition is maintained. This means that a current  $i$  flows through the input resistor  $R$ , where  $i = V_{IN}/R$ . Now this current has to go somewhere, and so it flows through the PNP transistor and comes out of the collector and into its load. Thus, the input voltage generates a current which is linearly proportional to it. There are, however, three sources of error that will affect this linearity. First the input offset voltage of the op-amp may become significant at low levels of  $V_{IN}$ . Second, the input bias current may well rob a lot of the current when  $V_{IN}$  is low. Third, the base current of the transistor must be subtracted from the final output current. Note that the current gain of the transistor will change with collector current variations, and




so the base current loss is not a fixed percentage. However, a precise voltage to current converter can be made using an op-amp with a FET input so that the bias current is low. Also, an input balance can be used to zero out the input offset voltage, and if a FET is used to replace the bipolar transistor, then the base current problem can be removed.

The 'SINK' circuit merely swaps the transistor to an npn type. Note that the input voltage now must be negative.
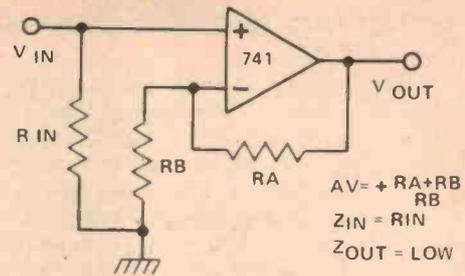
## NON-INVERTING AMPLIFIER:


An op-amp is used to provide voltage gain, but in this case the output is in phase with the input. The minimum voltage is unity and occurs when  $R_B$  is an open circuit. The op-amp has maximum bandwidth at unity gain, and any increase in the gain will cause a reciprocal decrease in bandwidth.



$$A_V = + \frac{R_A + R_B}{R_B}$$

$$Z_{IN} = R_{IN}$$

$$Z_{OUT} = \text{LOW}$$

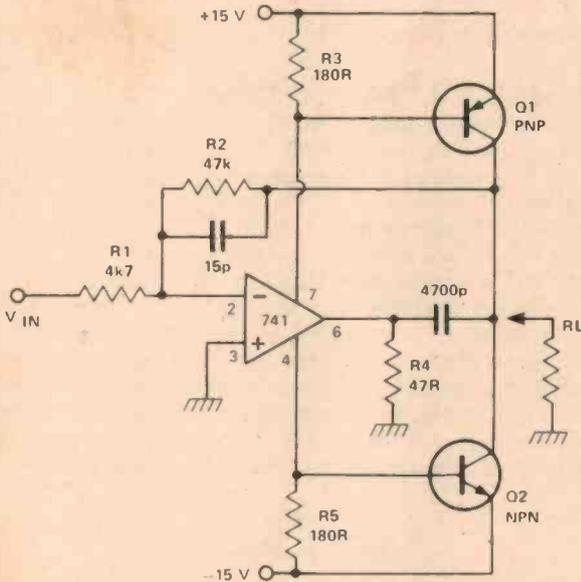

## HIGH SLEW RATE AMPLIFIER

The slow rate of the op-amp has been increased by increasing the overall current generating capability, by the addition of a pair of transistors. These transistors increase the output voltage range by allowing the voltage to swing to within 0V5 of either supply rails. The output of the op-amp hardly moves at all. Without an input signal, the output voltage is 0 V and the op-amp drains approximately 2 mA from the supply rails.

This current passes through the 180R resistors and sets up a voltage which is not quite sufficient to turn on either transistor. When a positive voltage is applied to the input, the op-amp tries to swing negative but it has a 47R ( $R_4$ ) resistor connected from its output to ground. Thus, as it tries to swing negative, it draws lots of current from the negative rail. This current flows through  $R_5$ , and in doing so turns on  $Q_2$ . This transistor then pulls  $R_2$  down and thus provides negative feedback. The same sequence of events occurs when the input is negative except that  $R_3$  and  $Q_1$  are then involved. Thus the high current capabilities of discrete transistors are combined with a high voltage gain of an op-amp to produce a moderately powerful amplifier. The voltage gain is set by  $R_2/R_1$ .

Transistors  $Q_1$  and  $Q_2$  introduce a phase shift, which may give rise to a high frequency instability and oscillation. This can be cured by some frequency compensation applied to the amplifier or by increasing the overall voltage gain.

## SCHMITT TRIGGER

When dc positive feedback is applied around an op-amp, its output will come to rest in one of two states, that is in its most positive or most negative position. This type of circuit is known as a Schmitt Trigger and it is said to exhibit the property of hysteresis.

Consider the circuit shown in Figure 15. Let us assume that  $R_B$  is 2 k and  $R_A$  is 1 k and the output voltage is +10 V. Therefore the voltage at the non-inverting terminal is 3V3. When the input voltage becomes more positive than 3V3, the output of the op-amp will start to swing negative and in doing so will increase the voltage difference between the inputs. This will in turn make the output swing even more negative. Thus the process becomes regenerative, the output finally 'snapping' into its negative state (-10 V say). The only thing that will now change the op-amp's output is if the inverting input goes more negative than the non-inverting input. When this occurs it will revert back to its original state. The two input voltages at which these transitions happen are known as the upper and lower hysteresis levels.

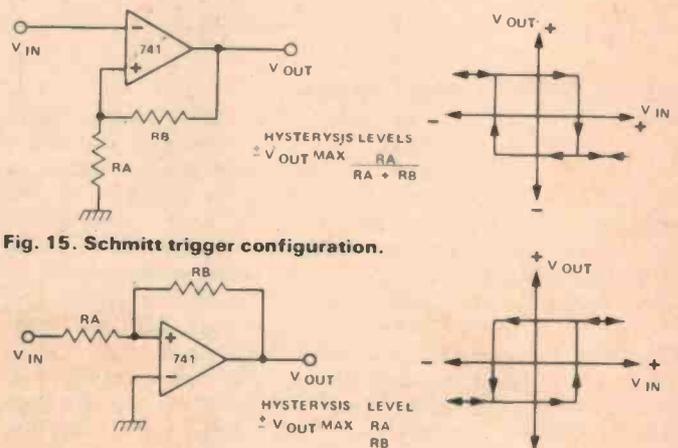


Fig. 15. Schmitt trigger configuration.


## HIGH PERFORMANCE SAMPLE AND HOLD

It is often necessary to have a circuit that will sample an analogue voltage and then remember it for a long time without any significant degradation of that voltage. This is known as a sample and hold circuit and one of its uses is to store the voltage from the keyboard connected to an electronic music synthesiser. The voltage is then used to control the pitch of a voltage controlled oscillator and so it is very important to have a high performance sample and hold. A drift of less than one semitone, (80 mV), in ten minutes is required. A sample and hold is simply an electronic switch, a storage capacitor and a high input impedance voltage follower. In the circuit shown, when switch SW1 is positive the FET is turned on, and has a resistance of about 400R. Thus the input voltage charges up the capacitor through the FET. When SW1 is negative, the FET is turned off, (pinched off), and can have a resistance of thousands of megohms. To get a long storage time the op-amp must have a very low input bias current. For the CA3140, this current is about 10 pico amps, i.e.,  $10^{-11}$  amps. Therefore the rate at which the capacitor will be discharged by this current can be worked out from the equation,  $C(dv/dt) = i$  where  $dv/dt$  is the rate of change of voltage on the capacitor.


Therefore:

$$\frac{dv}{dt} = \frac{i}{C} = \frac{10^{-11}}{0.47 \times 10^{-6}} = 22 \text{ uV/s}$$

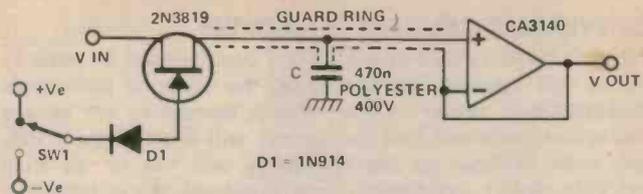This is a very low drift rate, much better than we need. However, the actual drift rate will probably be in excess of this, due to surface leakage on the printed circuit board, leakage through the FET, and internal leakage in the capacitor. It is advisable to use a high voltage, non-polarised capacitor in this



PRINTED CIRCUIT BOARD LAYOUT

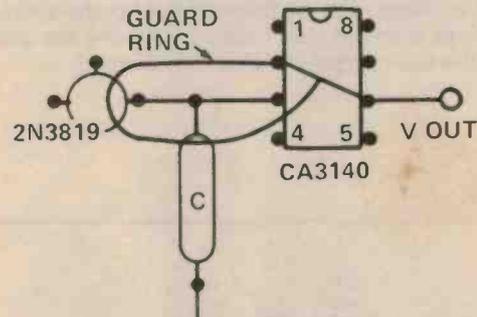


circuit to keep the leakage currents to a minimum. Also, to stop surface leakage a simple PCB trick can be used, that of making a guard ring around the sensitive components.

Normally any potential stored on the capacitor may leak to ground across the surface of the PCB, but if we make the surrounding surface a conducting track held at the same potential as that of the capacitor then the potential difference is virtually always zero, and hence the surface leakage is greatly reduced.
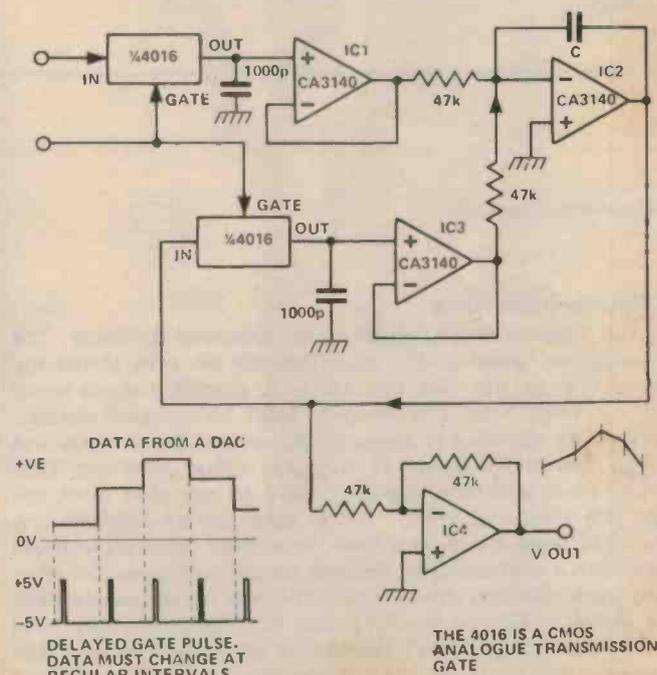
## CLEANING UP DIGITALLY GENERATED SIGNALS WITH TWO SAMPLE AND HOLDS AND AN INTEGRATOR

The output from a digital to analogue converter (dac) is composed of a series of steps which have been selected by a series of binary numbers. The output of the dac may represent the result of some computation done by a microprocessor or the contents of a digital memory. If the number of bits that control the dac is low (less than eight), then the output will look like a series of discrete steps, plus lots of digital 'glitches'. Therefore, if this signal is to be displayed on an oscilloscope, the overall picture quality will be very poor. One way to clean up would be to join up all the steps with straight lines and if done successfully a great improvement can be obtained. The only problem is that the distance between steps is continuously varying and so the slope of the straight lines will need to be variable as well. This process is known as linear point interpolation and can be achieved with two sample and holds and an integrator.



A delayed gate pulse is generated, so that once the dac's output has settled, the sample and hold switches momentarily open, sample the information and then close. The output of the first sample and hold (IC1) drives an integrator (IC2), the output of which drives the second sample and hold (IC3). The second unit provides negative feedback around the integrator, but it is delayed by one time interval. Thus a momentary positive going signal will pass through the first sample and hold and cause the integrator to ramp in a negative direction. When the next time interval arrives, the first sample and hold returns to 0V, and the second obtains a negative voltage. This then causes the integrator to ramp positively. The size of the



integrator's capacitor C should be chosen to suit the clock speed of the dac. An inverter, IC4 has been included to correct the inversion caused by the integrator.
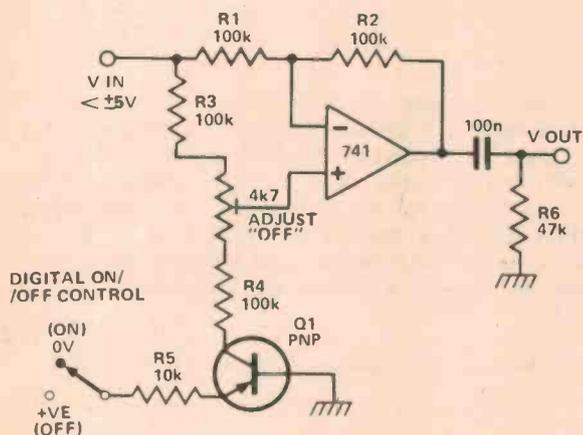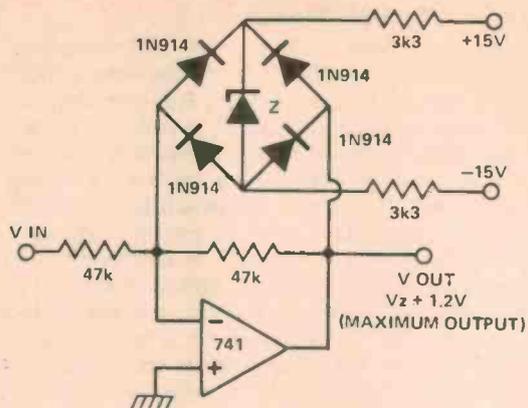
## FAST SYMMETRICAL ZENER CLAMPING

There are several problems with using zeners, back to back in series to get symmetrical clamping, the knee of the zener characteristics is rather sloppy, charge storage in the zeners causes speed problems and the zeners will have slightly different knee voltages so the symmetry will not be all that good. This circuit overcomes these problems. By putting the zener inside a diode bridge the same zener voltage is always experienced. The voltage errors due to the diodes are much smaller than those due to the zener. Also the charge storage of the bridge is much less. Lastly by biasing the zener on all the time, the knee appears to be much sharper.



## TRANSISTOR USED TO TURN AN OP AMP ON OR OFF

When transistor Q1 is switched off, the circuit behaves as a voltage follower. By applying a positive voltage to the emitter of Q1 via a 10 k resistor, the transistor is made to turn on and go into saturation. Thus the lower end of R4 is shorted to ground. The circuit has now changed into that of a differential amplifier (see fig. 7), but where the voltage difference is always 0 V. Now as long as the resistors in the two branches around the op amp are in the same ratio then there should be zero output. A 4k7 preset is used to null out any ratio errors so that the 'OFF' attenuation is more than 60 dB. The high common mode rejection ratio of a 741 enables this large attenuation to be obtained.


Continued from page 63.

## No Noise is Good Noise

The last op-amp characteristic to be discussed is 'Noise'. The noise figures given in the specifications are very confusing. This is due to the fact that noise is specified in so many different ways that it is often difficult to compare devices. One may be specified in terms of Equivalent Input Noise and another device in terms of  $nV/\sqrt{Hz}$  (nano volts per root Hertz)! As a generalisation it is true to say that most op-amps are relatively noisy. Some op-amps are labelled low noise, and these are quieter than the average op-amp but more noisy than a well designed discrete component amplifier. For audio work you can use ordinary op-amps for processing high level signals (100 mV to 3 V), but for amplifying low level signals (1 mV to 100 mV) you would be advised to use a low noise device. The larger the voltage gain you obtain from an op-amp stage, the worse will be the noise, therefore keep the closed loop gain to a bare minimum.

That is the end of the theory, now for some practical examples of op-amps in use.

For more great circuit ideas...

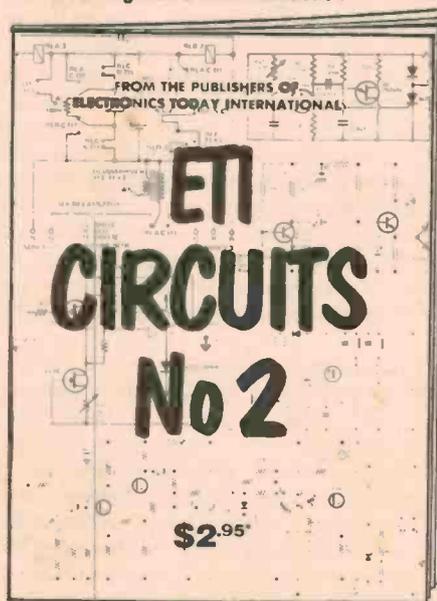

On sale now at all main newsagents \$2.95  
or direct from ETI at \$3.40 inc p & p.

The  
Motorola Family  
of  
Piezo Electric  
Tweeter Horns  
proudly presents



KSN 1001 A or 1005 A  
3.5" Super Horn.  
Response: 4K to 30K.  
Retail: \$16



KSN 1016 A  
2" x 5" wide dispersion horn.  
Response: 4K to 25K.  
Retail: \$20

## THE ARRIVAL OF A NEW MEMBER OF THE PIEZO FAMILY



## The KSN 1025 A

3" x 7" wide dispersion horn.  
Response: 2000 Hz to 22,000 Hz.  
Retail \$28

MOTOROLA PIEZO HORNS are being used by some of the worlds leading manufacturers of HI-FI speakers, disco equipment and musical instrument amplifications, due to their specific advantages over Dynamic counterparts.

For technical information send SAE to sole Australian importer:

### FREEDMAN ELECTRONICS Pty Ltd

89-91A Liverpool Road, Summer Hill. NSW. 2130.  
Tel. (02) 797-9941/797-0986.

Victorian Distributor:

### ZEPHYR PRODUCTS

70 Batesford Road, Chadstone. Victoria. 3148. Tel. 568-2922.

## SEMCON MICROCOMPUTERS PTY. LTD.

### ATTENTION OWNERS!


### MOTOROLA D2

If you want a functional,  
expandable system, you need:
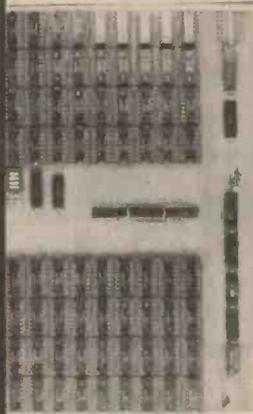
### 8K BYTE, STATIC MEMORY CARD

Australian Designed and Built

- Fast Access 350 ns Chips (2102LF)
  - Low Current - 1.3 Amps
  - Motorola Bus Compatible
  - Write Protect
  - Parity Generation/Checking available
  - Professional Finish
  - Plated through Holes
  - \$275 assembled board
  - \$219 in kit form
  - 298 Assembled with Parity
- \* \$110 for 8k kit without rams
- Built Boards Guaranteed 12 months



### CARD CAGE/BACKPLANE:

- Designed for Motorola Cards
- Anodised Aluminium chassis
- Sturdy Construction
- Tin Plated Backplane
- Accomodates 8 cards

**\$74.00**

### EDGE CONNECTORS —

43 x 2 x 0.156" \$8.50 each  
Eight for \$59.00


\$100 Connectors \$8.50



## NEW PRODUCT
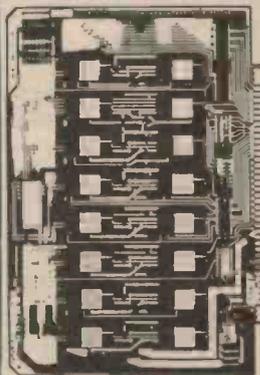
### 8K/16K EPROM— ROM MODULE

- Accepts up to 16 2708's.
- -5V generated on card.
- Motorola bus.
- Quality PCB.



\$135 ( this is a built  
board, however it does  
not include EPROM's

2708's 1-8 \$14-50  
9-16 \$13-50

### I.C. SOCKETS — LOW PROFILE

| SOLDER  |     | DIL — TIN |     | WIRE WRAP GOLD |      |
|---------|-----|-----------|-----|----------------|------|
| 8.....  | .25 | 22.....   | .35 | 24.....        | 1.40 |
| 14..... | .28 | 24.....   | .45 | 14.....        | .70  |
| 16..... | .28 | 28.....   | .50 | 16.....        | .70  |
| 18..... | .35 | 40.....   | .90 |                |      |

SHOWROOM: 1 Chilvers Road, Thornleigh, NSW 2120.  
MAIL ORDER: PO Box 61, Pennant Hills, NSW 2120.  
PHONE: 848-0800. Add 15 percent sales tax. P&P \$1.50.

**SOME OF AUSTRALIA'S LOWEST COMPONENT PRICES**

**POLYESTER FILM CAPS**

E12 10% 100V  
All values .001 to .01 — 7c ea.

|      |       |            |
|------|-------|------------|
| .01  | 7c.1  | 13c        |
| .012 | 8c.12 | 14c        |
| .015 | 8c.15 | 14c        |
| .018 | 8c.18 | 14c        |
| .022 | 8c.22 | 16c        |
| .027 | 8c.27 | 16c        |
| .033 | 8c.33 | 18c        |
| .039 | 9c.39 | 19c        |
| .047 | 9c.47 | 22c        |
| .056 | 9c    | All values |
| .068 | 10c   | in uF      |
| .082 | 10c   | in uF      |

10% off 100 same uF

NOTE: REGULAR PRICES NOT TEMPORARY SPECIALS — KEEP US IN MIND FOR THAT NEXT ORDER

**ELECTROCAPS (UPRIGHT) (per 100 prices in brackets)**

| Cap.              | 16V         | 25V                | 50V       |
|-------------------|-------------|--------------------|-----------|
| 0.47 uF thru to   | all         | all                | all       |
| 10 uF             | 5c(\$3 1/2) | 6c(\$3 3/4)        | 7c(\$4)   |
| 22 uF             | 6c(\$4)     | 7c(\$4)            | 8c(\$5)   |
| 33 uF             | 8c(\$4)     | 9c(\$5)            | 10c(\$6)  |
| 47 uF             | 9c(\$5)     | 10c(\$6)           | 11c(\$7)  |
| 100 uF            | 10c(\$6)    | 12c(\$7)           | 14c(\$11) |
| 220 uF            | 12c(\$8)    | 16c(\$10)          | 35c(\$17) |
| 470 uF            | 16c(\$12)   | 22c(\$16)          | 45c(\$30) |
| 1000 uF           | 22c(\$18)   | 30c(\$25)          | 75c(\$50) |
| 1000 uF/16V axial | —           | 20c ea. \$8 per 50 | —         |
| 2200 uF/50V axial | —           | 95c ea. \$8 per 10 | —         |

Full axial price list — SAE

LEDS: \$12 per 100, \$110 per 1000, or 17c each, 10 for \$1.50 clips 3c each all quantities. LEDS superb — 5mm red — well diffused. Wide viewing angle — sample 40c stamp.  
TO3 MOUNTING KITS: 10 for \$1 or \$4 box of 50. Generous kit includes mlca, screws, nuts, washers, tag, nylon brushes.

Potentiometers: 50c ea, rotary carbon (slng. gang) log or lin: 1K, 5K, 10K, 25K, 50K, 100K, 25K, 500K, 1M, 2M (metal shafts) Trlm Pots: 17c ea. — 10mm 1W horiz. or vert: 100 Ohm to 2M

ZENER DIODES: 15c each 400mW 5% E24 values 3V to 33V

2c RESISTORS — our 2 year old price still current. Opposition hoped we would go broke but our price remains at 2c ea. 1 Ohm to 10 M  $\frac{1}{4}$ W 5% E12 carb. film \$1.80 per 100 same value (or  $\frac{1}{4}$ W 3c, \$2.50 per 100 same value)

Keep electronics a hobby and not a luxury, compare our prices and buy from us. Same day turnaround service (unless swamped). All goods top quality and new. No minimum order. One P/P charge of 40c regardless of quantity. Advert current 3 months for late readers.

**DIGGERMAN ELECTRONICS**  
P.O. BOX 33, CORAMBA NSW. 2466.

| SCRs:             | TRIACS:                        | DIODES:                        |
|-------------------|--------------------------------|--------------------------------|
| 0.8A 30V C103Y —  | 35 2A 400V ESP240 —            | 65 1N4001 — 7c (1A 50V)        |
| 0.8A 200V C103B — | 60 6A 400V SC141D —            | \$1.30 1N4002 — 8c (1A 100V)   |
| 4A 30V C106Y1 —   | 40 10A 400V SC146D —           | \$1.50 1N4004 — 9c (1A 400V)   |
| 4A 400V C106D1 —  | 75 25A 400V SC260D —           | \$2.50 1N4007 — 12c (1A 1000V) |
| 8A 400V C122D —   | \$1.05 DIAC ST2 —              | 35 1N4148 — 6c \$4.50/100      |
| 8A 500V C122E —   | \$1.20 Chart to identify leads | —                              |
| 25A 400V C37D —   | \$2.50 Plus; trigger info.     | 15 \$38/1000                   |

**TRANSFORMERS**

| 12 or 24 Volt Range: Primaries 220-240 volts |       |          |                         |       | Miniature transformers with screens: Primaries 220-240 volts |           |         |                  |       |
|----------------------------------------------|-------|----------|-------------------------|-------|--------------------------------------------------------------|-----------|---------|------------------|-------|
| Ref.                                         | Amps  | Wt. Gms. | Secondary Windings      | \$    | Ref.                                                         | MA        | Wt. Gms | Volts            | \$    |
| 112                                          | 0.5   | 623      | 0-12-15-20-24-30        | 6.00  | 238                                                          | 200       | 85      | 3.03             | 3.50  |
| 79                                           | 1     | 737      | 0-12-15-20-24-30        | 7.50  | 212                                                          | 1A 1A     | 595     | 0.6 0.6          | 6.60  |
| 242                                          | 300MA | 150MA    | 198 0-12V at 150 MA x 2 | 3.50  | 13                                                           | 100       | 113     | 9.09             | 3.50  |
| 111                                          | 0.5   | 283      | 0-12V at 0.25A x 2      | 4.50  | 236                                                          | 330, 330  | 198     | 0.9, 0.9         | 3.50  |
| 213                                          | 1.0   | 425      | 0-12V at 0.5A x 2       | 5.00  | 207                                                          | 500, 500  | 566     | 0.8-9, 0.8-9     | 6.30  |
| 71                                           | 2     | 793      | 0-12V at 1A x 2         | 7.20  | 205                                                          | 500, 600  | 1077    | 0.15-20, 0.15-20 | 7.20  |
| 18                                           | 4     | 1020     | 0-12V at 2A x 2         | 9.00  | 214                                                          | 300, 300  | 623     | 0.20, 0.20       | 5.00  |
| 70                                           | 6     | 1538     | 0-12V at 3A x 2         | 11.40 | 221                                                          | 700 (DC)  | 737     | 20-12-0012-20    | 7.80  |
| 108                                          | 8     | 2268     | 0-12V at 4A x 2         | 15.00 | 206                                                          | 1A 1A     | 1304    | 0.15-27, 0.15-27 | 10.80 |
| 116                                          | 12    | 2722     | 0-12V at 6A x 2         | 16.80 | 203                                                          | 500, 500. | 822     | 0.15-27, 0.15-27 | 10.20 |
| 115                                          | 20    | 5300     | 0-12V at 10A x 2        | 24.90 | 204                                                          | 1A 1A     | 1417    | 0.15-27, 0.15-27 | 14.40 |

| 50 Volt Range: Primaries 220-240 volts |      |      |                    |       |
|----------------------------------------|------|------|--------------------|-------|
| Ref.                                   | Amps | Wt.  | Secondary Taps     | \$    |
| 50                                     | 0.5  | 737  | 0-19-25-33-40-50 V | 8.40  |
| 103                                    | 1    | 1304 | 0-19-25-33-40-50 V | 9.60  |
| 104                                    | 2    | 2495 | 0-19-25-33-40-50 V | 12.60 |
| 105                                    | 3    | 3176 | 0-19-25-33-40-50 V | 15.00 |
| 106                                    | 4    | 4100 | 0-19-25-33-40-50 V | 18.00 |
| 107                                    | 6    | 5444 | 0-19-25-33-40-50 V | 26.40 |

| 60 Volt Range: Primaries 220-240 volts |      |      |                    |       |
|----------------------------------------|------|------|--------------------|-------|
| Ref.                                   | Amps | Wt.  | Secondary Taps     | \$    |
| 124                                    | 0.5  | 737  | 0-24-30-40-48-60 V | 7.80  |
| 126                                    | 1    | 1361 | 0-24-30-40-48-60 V | 9.60  |
| 127                                    | 2    | 2495 | 0-24-30-40-48-60 V | 12.60 |
| 125                                    | 3    | 4083 | 0-24-30-40-48-60 V | 18.60 |
| 40                                     | 5    | 5670 | 0-24-30-40-48-60 V | 25.20 |

DOUGLAS TRANSFORMERS, DEPT. MO, BOX 23, COORANBONG, N.S.W. 2265.

**EXPAND YOUR M6800 D2 KIT**

- 16K MOTHER BOARD KIT.....\$49.20
- 4K RAM PLANE KIT (450 nS) ...\$75.25
- 4K ROM PLANE KIT.....\$34.90
- 2708's \$17.90 extra.
- 2708 EPROM PROGRAMMER. \$179.60
- Driver software (in 2708) \$24.00
- CDB-150 150 bytes/sec FAST AUDIO CASSETTE INTERFACE.....\$199.00 (includes software driver)
- BACKPLANE PCB (5 slots).....\$26.50 — EDGE CONNECTORS
- 5 for \$45.00 or \$9.48 each.
- BUFFER IC's (2x8T26, 3x8T97, 1x7430).....\$12.00

**Pennywise Peripherals**

**SPECIAL**

**8K RAM KIT**

(Mother Board & 2 RAM PLANES)

**\$189**

Offer open until 31/8/78.

All prices include tax

P&P \$2.00

19 Suemar St, Mulgrave, Vic.  
3170. Ph (03) 546-0308.

# Tandy Electronics No.1 Parts Place

## Buy Off the Shelf! Low Prices! Huge Selection!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to

pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. Always count on Tandy for the finest quality electronic parts.

### Linear ICs

By National Semiconductor and Motorola—first quality

| Type   | Cat.No.  | ONLY |
|--------|----------|------|
| 301CN  | 276-017  | 1.29 |
| 324N   | 276-1711 | 2.69 |
| 339N   | 276-1712 | 2.69 |
| 386CN  | 276-1731 | 1.99 |
| 555CN  | 276-1723 | 1.99 |
| 566CN  | 276-1728 | 3.29 |
| 566CN  | 276-1724 | 3.99 |
| 567CN  | 276-1721 | 3.99 |
| 723CN  | 276-1740 | 1.99 |
| 741CN  | 276-007  | 1.29 |
| 3300N  | 276-1713 | 1.99 |
| 3909N  | 276-1705 | 1.99 |
| 3911N  | 276-1706 | 3.99 |
| 4558CN | 276-038  | 1.69 |
| 75491  | 276-1701 | 1.49 |
| 75492  | 276-1702 | 1.49 |
| 7805   | 276-1770 | 2.19 |
| 7812   | 276-1771 | 2.19 |
| 7815   | 276-1772 | 2.19 |

### Computer Chips



#### Prime Devices

|                                    |       |
|------------------------------------|-------|
| 8080A Microprocessor, 8-bit, NMOS. |       |
| 276-2510.....                      | 24.95 |
| 2102 1K Static RAM, Under 450 ns.  |       |
| 276-2501.....                      | 6.95  |


### TTL and CMOS Logic ICs

Full-Spec Devices Direct from Motorola and National Semiconductor



| Type   | Cat. No. | ONLY |
|--------|----------|------|
| 7400   | 276-180  | .99  |
| 7402   | 276-1811 | .99  |
| 7404   | 276-1802 | 1.09 |
| 7406   | 276-1821 | 1.29 |
| 7410   | 276-1807 | .99  |
| 7413   | 276-1815 | 1.99 |
| 7420   | 276-1809 | .99  |
| 7427   | 276-1823 | 1.29 |
| 7432   | 276-1824 | 1.29 |
| 7441   | 276-1804 | 2.49 |
| 7447   | 276-1805 | 2.49 |
| 7448   | 276-1816 | .99  |
| 7451   | 276-1825 | 1.29 |
| 7473   | 276-1803 | 1.29 |
| 7474   | 276-1818 | 1.29 |
| 7475   | 276-1806 | 1.99 |
| 7476   | 276-1813 | 1.39 |
| 7485   | 276-1826 | 2.69 |
| 7486   | 276-1827 | 1.29 |
| 7490   | 276-1808 | 1.99 |
| 7492   | 276-1819 | 1.89 |
| 74123  | 276-1817 | 2.49 |
| 74145  | 276-1828 | 2.69 |
| 74150  | 276-1829 | 2.69 |
| 74154  | 276-1834 | 2.79 |
| 74192  | 276-1831 | 2.69 |
| 74193  | 276-1820 | 2.69 |
| 74194  | 276-1832 | 2.69 |
| 74196  | 276-1833 | 2.79 |
| 74C00  | 276-2301 | 1.09 |
| 74C02  | 276-2302 | 1.09 |
| 74C04  | 276-2303 | 1.09 |
| 74C08  | 276-2305 | 1.09 |
| 74C74  | 276-2310 | 1.99 |
| 74C76  | 276-2312 | 2.39 |
| 74C90  | 276-2315 | 3.99 |
| 74C192 | 276-2321 | 3.99 |
| 74C193 | 276-2322 | 3.99 |
| 4001   | 276-2401 | 1.09 |
| 4011   | 276-2411 | 1.09 |
| 4013   | 276-2413 | 1.99 |
| 4017   | 276-2417 | 3.69 |
| 4020   | 276-2420 | 3.69 |
| 4027   | 276-2427 | 1.99 |
| 4049   | 276-2449 | 1.59 |
| 4050   | 276-2450 | 1.59 |
| 4511   | 276-2447 | 3.99 |
| 4518   | 276-2490 | 3.69 |

### SEMICONDUCTOR REFERENCE HANDBOOK

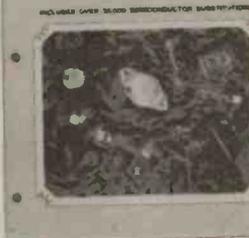

Sold Only at Tandy

**1.95**

### Semiconductor Reference Handbook


The most comprehensive "Substitution" manual we've ever offered. Includes full specs and applications of Radio Shack/Archer IC's, diodes, SCR's, bridges and transistors. A quick reference to transistor specs, and a cross-reference/substitution listing of over 36,000. Plus a glossary of words, symbols and abbreviations. 176 pages. 276-4001..... 1.95

### Wire Wrapping Accessories



IC Socket Wrapping Tool. Strips and wraps 30-gauge wire. 276-1570..... 7.95  
 14-Pin Wire Wrapping Sockets. 276-1993..... 1.99  
 16-Pin Wire Wrapping Sockets. 276-1994..... 2.19  
 DIP Header, 16 pins. 276-1980..... 1.89  
 15.24m Red 30-ga Kynar Wire. 276-501..... 2.99  
 15.24m White 30-ga Kynar Wire. 276-502..... 2.99  
 15.24m Blue 30-ga Kynar Wire. 276-503..... 2.99


### Trim Multi-Purpose Cabinets

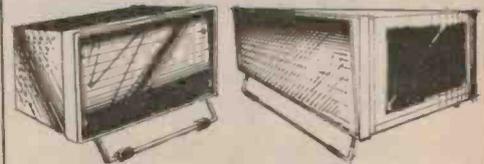

Compact. Makes even your small projects look professional. 14.9x22.86x12.38cm. 270-281..... 18.95  
 Low Profile. Slim design—only 14.9x28.8x8.89cm. 270-282..... 23.95

### LED Digital Displays

| Digits | Size | Drive | Ct. No.  | ONLY  |
|--------|------|-------|----------|-------|
| A. 1   | 0.6" | Anod. | 276-056  | 4.99  |
| A. 1   | 0.6" | Cath. | 276-066  | 4.99  |
| B. 1   | 0.3" | Anod. | 276-053  | 3.59  |
| B. 1   | 0.3" | Cath. | 276-062  | 3.59  |
| B. 1   | 0.3" | Anod. | 276-1210 | 12.95 |
| B. 1   | 0.3" | Cath. | 276-1211 | 12.95 |

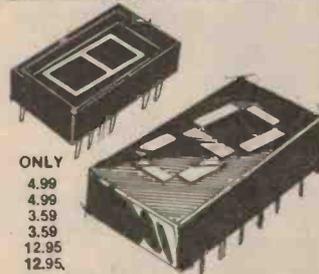


### IC Accessories



D. DIP Switch. For changing preset logic states. 275-1301..... 2.99  
 E. Right-Angle 16-Pin Socket. 276-1985..... 1.99

### MA1003 Automotive Clock Module

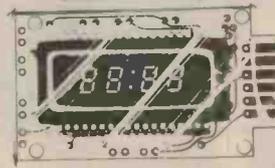

Just add switches and install! 12-hour readout, 0.3" digits, ± 0.5 sec/day accuracy. 12VDC. 27-1003..... 34.95

### Archer® Project-Boards—Predrilled PCB's



Time Base Generator. Built-in 10 MHz xtal or ext. input. Decade selector switch. TTL output. Requires 5VDC. 277-115 (PCB less parts)..... 7.99

#### Complete Package

Including all parts except hardware and case, sells for approximately \$46.95.

Shown Built with Recommended Parts and Cases

### Full-Wave Bridge Rectifiers



NEW


A. 1-Amp, 50 PIV. Mini DIP fits PCB or 8 and 14-pin sockets. 276-1161..... 1.19

### Mike Elements



Dynamic. Tiny yet delivers 80-10,000 Hz response. - 65dB. 200 ohms. 1.9x2.2cm. 270-093..... 1.99  
 Hi Crystal. 50-8000 Hz response. - 55 dB. 3.8x3.1cm. 270-095..... 1.69

### 2-Foot Mini Test Clips

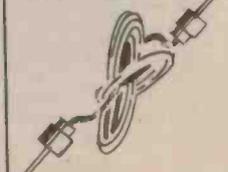


Red. 276-1158..... 1.99  
 Black. 276-1159..... 1.99

### Disc Capacitors

Up to 1000 WVDC

**2.99**

Pkg. of 100

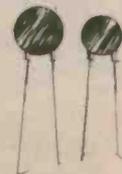

WHY WAIT FOR MAIL ORDER DELIVERY?  
 MOST TYPES IN STOCK NOW AT OUR STORE NEAR YOU!

**TANDY**  
 ELECTRONICS

OVER 8000 LOCATIONS IN NINE COUNTRIES

# Now. Two 3-way 40 watt speakers with nine tonal choices

## Save about \$50 per hour while you assemble them

Even if you didn't know them by number, you probably heard about the Philips AD12K12 MK11 Speaker Kits.

Because they are now a no.1 best-seller.

And here is the compact AD8K30, 8" 3-way compact system, with fine electronic and acoustic components (1" domed tweeters, 5" mid-range, super 8" bass drivers). Brilliant clean sound, with a frequency response closely following the ideal Bruel & Kjaer curve for hi-fi equipment measured in an actual listening room, using the "Third Octave Pink Noise Method".

Plus 9 combination tonal choices to adjust to the acoustics of your own listening-room.

You can assemble the AD8K30's in about two hours. You will get a professional result and save about \$100 per pair over a comparable system. Phone or send coupon now for full details of this and all our kits.

### PHILIPS ELECTRONIC COMPONENTS AND MATERIALS

Sydney 427 0888 • Melbourne 699 0300 • Brisbane 277 3332  
• Adelaide 45 0211 • Perth 65 4199



#### ELCOMA

Philips Electronic Components and Materials  
P.O. Box 50, Lane Cove, NSW 2066

Please send me full details and brochures on your loud speaker kits and a list of retailers who stock them.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

STATE \_\_\_\_\_ P/CODE \_\_\_\_\_

ETA



**Electronic  
Components  
and Materials**

# PHILIPS

# EPROM PROGRAMMER


This low-cost device will interface to just about any microcomputer, and requires only simple software to drive it. Based on a design by N.D. Hammond.

SO, YOU'RE BUILDING an ETI 640 VDU, you've written some I/O routines to drive it, and you're looking forward to the day when you'll be running BASIC and graphics and good stuff like that. Initially, at least, you'll have to use the keypad, or front panel, on your Morrow or D2 or whatever, to get the system started, and then load your VDU driver from cassette in order to use the VDU.

But wouldn't it be nice if the VDU driver was in there at power-up, so you didn't have to bootstrap the system into life? Well, the way to do this is to blow a PROM (Programmable Read Only Memory) with your routines and sit it in memory so that it is the first thing the processor looks at when it starts up. In fact, most hobbyists now use EPROMs (Eraseable PROMs) of the 2708 type, which are not now as expensive as they used to be, and have the advantage of allowing you to correct those inevitable bugs in your program, or reuse the EPROM for some completely different program.

That's all very well, I hear you say, but I don't have a way of programming 2708's. Plus, commercial EPROM programmers are too expensive for me to justify since I only program an EPROM a month. Thanks to reader N D Hammond of Torrens, ACT, (and of course ETI) your troubles are over. Here is an inexpensive, nay, cheap, 2708 programmer suitable for individuals or impecunious clubs.

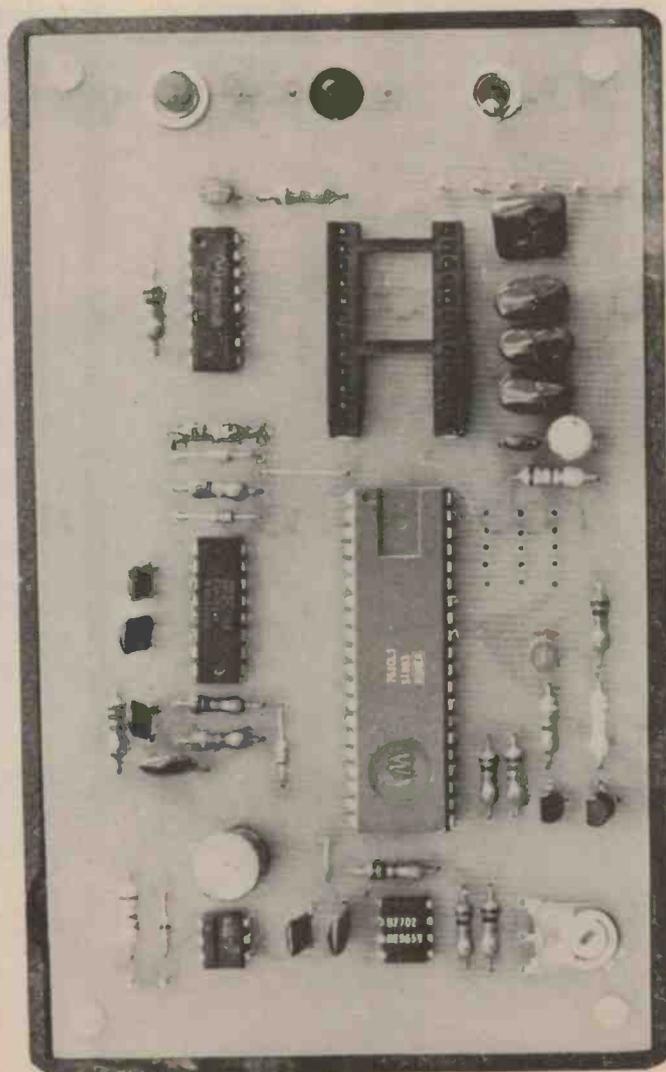The programmer is, in fact, slightly different from the original design submitted to us by Mr Hammond; we have replaced some TTL in his design with CMOS and added a data time-out synchronisation facility, on which more later.



# Project 638

## Design Features

The objectives of the original design were simplicity of construction and operation, and low cost. Another requirement which must be met is simplicity and versatility of interfacing — one of our bigger headaches is the fact that everyone's system seems to be different.

This project meets these objectives very well. The interface to the user's computer is *serial*, i.e. through a 20 mA current loop. Most computers, except for some evaluation kits, have a suitable serial I/O port, so this is a pretty well universal interface. As a bonus, the UART and a couple of one-shots provide all the necessary timing signals, so the component count is low and cost is low.

A useful by-product of our switch to a completely CMOS design was a spare gate, which we put to good use in providing a 'synchronisation' facility. The idea is that if a supply glitch or noise causes the UART to miss a byte of data, so that the 2708 addressing is out of step with the desired addressing, a ¼ second pause at the end of each cycle will reset the 4040 to zero. This means that only that cycle will be affected and subsequent cycles will be correct, increasing the programmer's tolerance to glitches.

There is one slight penalty that has to be paid — at 300 baud, it will take about 70 minutes to output all 1024 addresses 125 times. This is by no means


brilliantly fast compared to the theoretical minimum programming time of 104 seconds but it is a lot better than the several days that would be required by a commercial firm.

Mr Hammond originally supplied software for the 8080, but our tests of the circuit were done on a MEK6800D2, for which we have written a routine, reproduced here. Our routine incorporates a time delay of approximately ¼ second at the end of each run through the 2708 addresses, in order to take advantage of the time-out synchronisation feature. Mr Hammond's 8080 program does not include this facility, but it is easy to add a time delay loop which decrements (say) the BC pair using the DCX instruction. We hope to give this program next month (so much to do, so little time, sigh!), but Mr Hammond's routine should work with no modification.
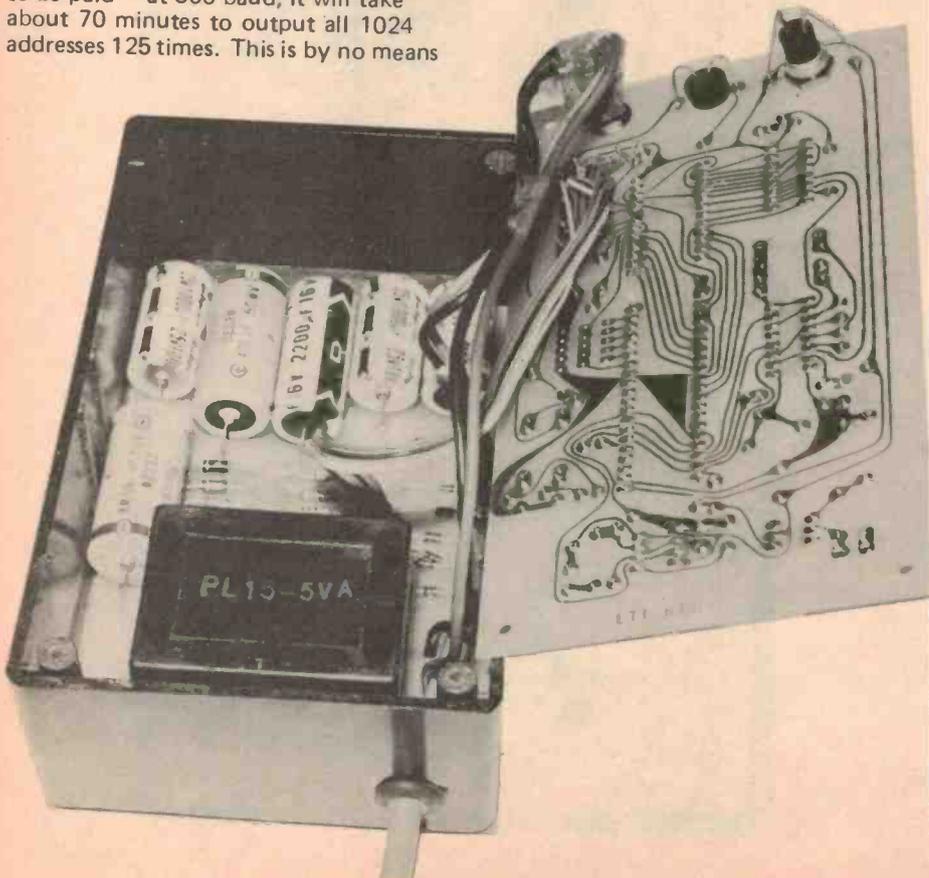
## Adjustment

Before adjusting the oscillator frequency first fit the links which set the start-stop bit arrangement of UART.

Now with power connected adjust RV1 until IC2 is operating at 4800 Hz.



## PARTS LIST — ETI 638 A

### Resistors all ½W 5%

|       |       |      |
|-------|-------|------|
| R1    | ..... | 180R |
| R2, 3 | ..... | 10k  |
| R4, 5 | ..... | 1k   |
| R6    | ..... | 10k  |
| R7    | ..... | 4M7  |
| R8    | ..... | 180k |
| R9    | ..... | 100k |
| R10   | ..... | 470R |
| R11   | ..... | 10k  |
| R12   | ..... | 1k   |
| R13   | ..... | 10k  |
| R14   | ..... | 33k  |
| R15   | ..... | 10k  |
| R16   | ..... | 47R  |
| R17   | ..... | 180R |

### Potentiometer

|     |       |          |
|-----|-------|----------|
| RV1 | ..... | 25k trim |
|-----|-------|----------|

### Capacitors

|         |       |                  |
|---------|-------|------------------|
| C1      | ..... | 8n2 polyester    |
| C2-C4   | ..... | 10n polyester    |
| C5      | ..... | 33n polyester    |
| C6, 7   | ..... | 10n polyester    |
| C8, 9   | ..... | 100n polyester   |
| C10     | ..... | 100µ 25V electro |
| C11, 12 | ..... | 100n polyester   |
| C13     | ..... | 10µ 35V electro  |

### Semiconductors

|     |       |                       |
|-----|-------|-----------------------|
| IC1 | ..... | 4N33 Opto coupler     |
| IC2 | ..... | 555 timer             |
| IC3 | ..... | MM5303 UART           |
| IC4 | ..... | 4049 Hex inverter     |
| IC5 | ..... | 4040 12 stage counter |

|    |       |        |
|----|-------|--------|
| Q1 | ..... | PN3638 |
|----|-------|--------|

|    |       |       |
|----|-------|-------|
| Q2 | ..... | BC548 |
|----|-------|-------|

|    |       |       |
|----|-------|-------|
| Q3 | ..... | BC558 |
|----|-------|-------|

|    |       |       |
|----|-------|-------|
| Q4 | ..... | BC548 |
|----|-------|-------|

|       |       |       |
|-------|-------|-------|
| D1-D4 | ..... | 1N914 |
|-------|-------|-------|

|      |       |  |
|------|-------|--|
| LED1 | ..... |  |
|------|-------|--|

### Miscellaneous

|                         |
|-------------------------|
| PC board ETI 638 A      |
| 24 pin IC socket        |
| Push button             |
| Plastic box 158x96x50mm |

## PARTS LIST — ETI 638 B

### Resistors all ½W 5%

|       |       |      |
|-------|-------|------|
| R1    | ..... | 1k   |
| R2, 3 | ..... | 120R |
| R4, 5 | ..... | 47R  |
| R6    | ..... | 470R |
| R7    | ..... | 100R |

### Capacitors

|       |       |                   |
|-------|-------|-------------------|
| C1    | ..... | 470µ 50V electro  |
| C2    | ..... | 2200µ 16V electro |
| C3-C5 | ..... | 1000µ 25V electro |
| C6    | ..... | 470µ 50V electro  |

### Diodes

|       |       |            |
|-------|-------|------------|
| D1-D6 | ..... | 1N4004     |
| ZD1   | ..... | 27V 1W     |
| ZD2   | ..... | 12V 400mW  |
| ZD3   | ..... | 12V 1W     |
| ZD4   | ..... | 5.1V 400mW |
| ZD5   | ..... | 5.1V 1W    |

### Miscellaneous

|                      |
|----------------------|
| PC board ETI 638 B   |
| Transformer PL15-5VA |
| Switch DPDT toggle   |
| 3 core flex & plug   |
| Cable clamp          |

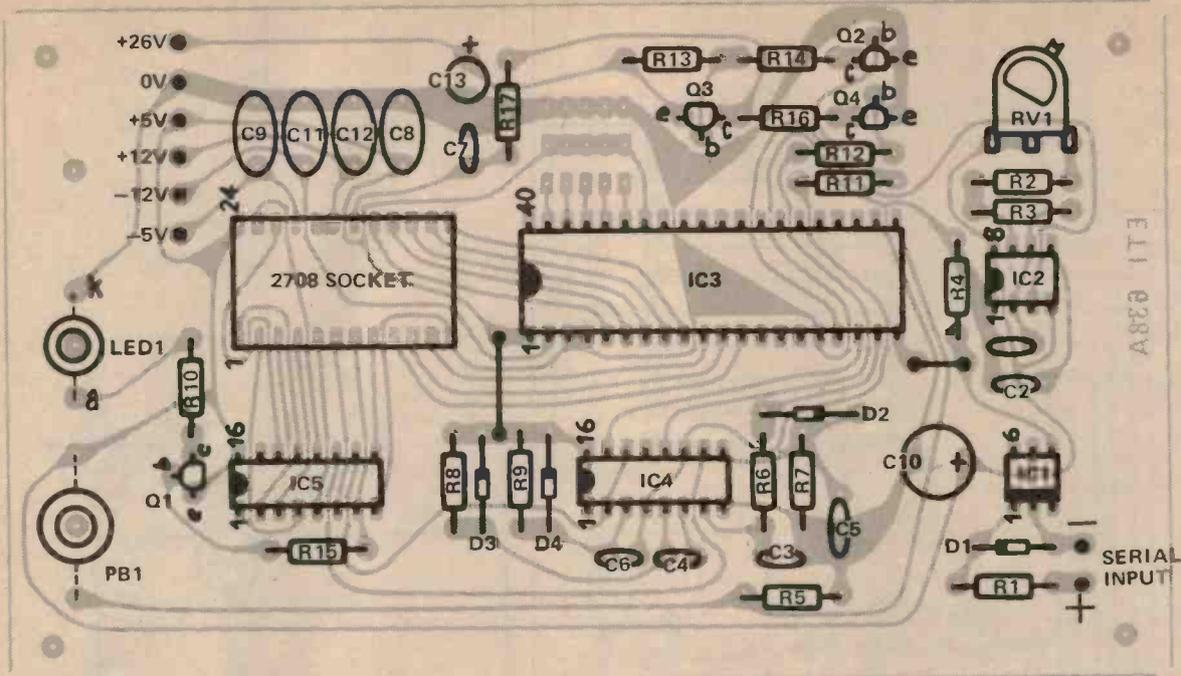


Fig. 1 The component overlay of the main board.

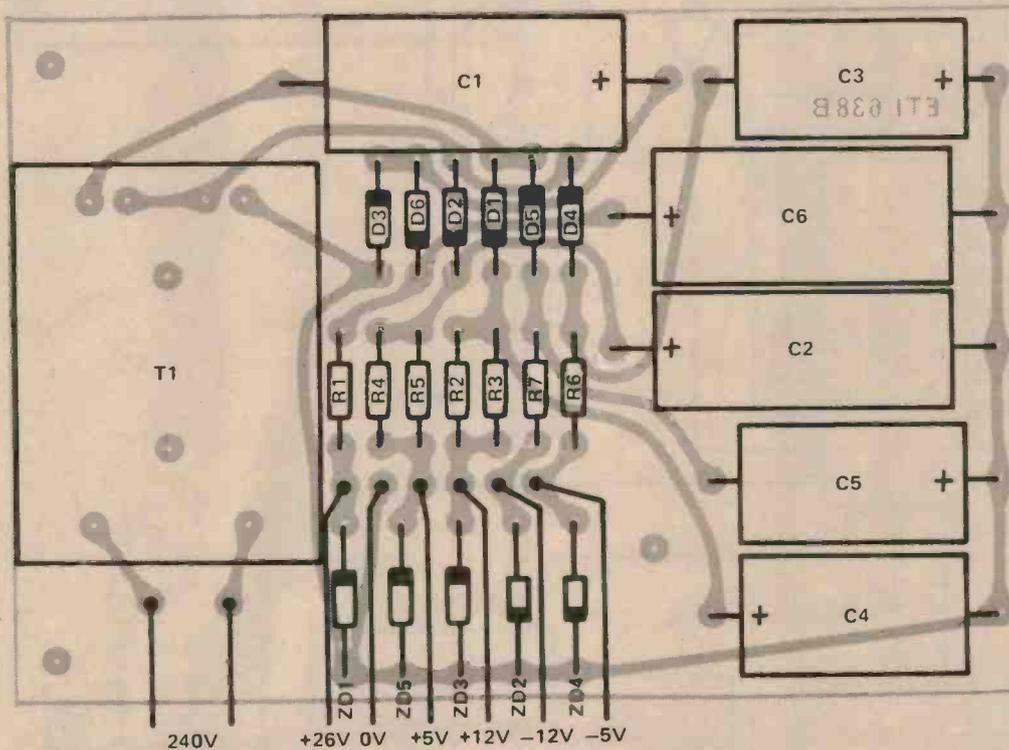


Fig. 2. The component overlay of the power supply.

### Construction

We built our prototype into a plastic box with the power supply on one board in the box itself while the logic board was used in place of the lid.

These boards should be assembled according to the overlays provided. Normal handling procedures should be

taken with the SMOC ICs and the UART. A good quality socket should be used for the EPROM as it will be used a lot. The pushbutton, LED and power switch are mounted on the logic board and connected from the rear.

With the power switch, due to the closeness of the capacitors on the lower board, the wires should be taken parallel

to the pc board and the rear of the switch epoxied over to give protection. The connection between the power supply and logic board can be done with a piece of ribbon cable as the connections follow the same sequence.

We used pc pins for the data input points but a socket could be used if desired.

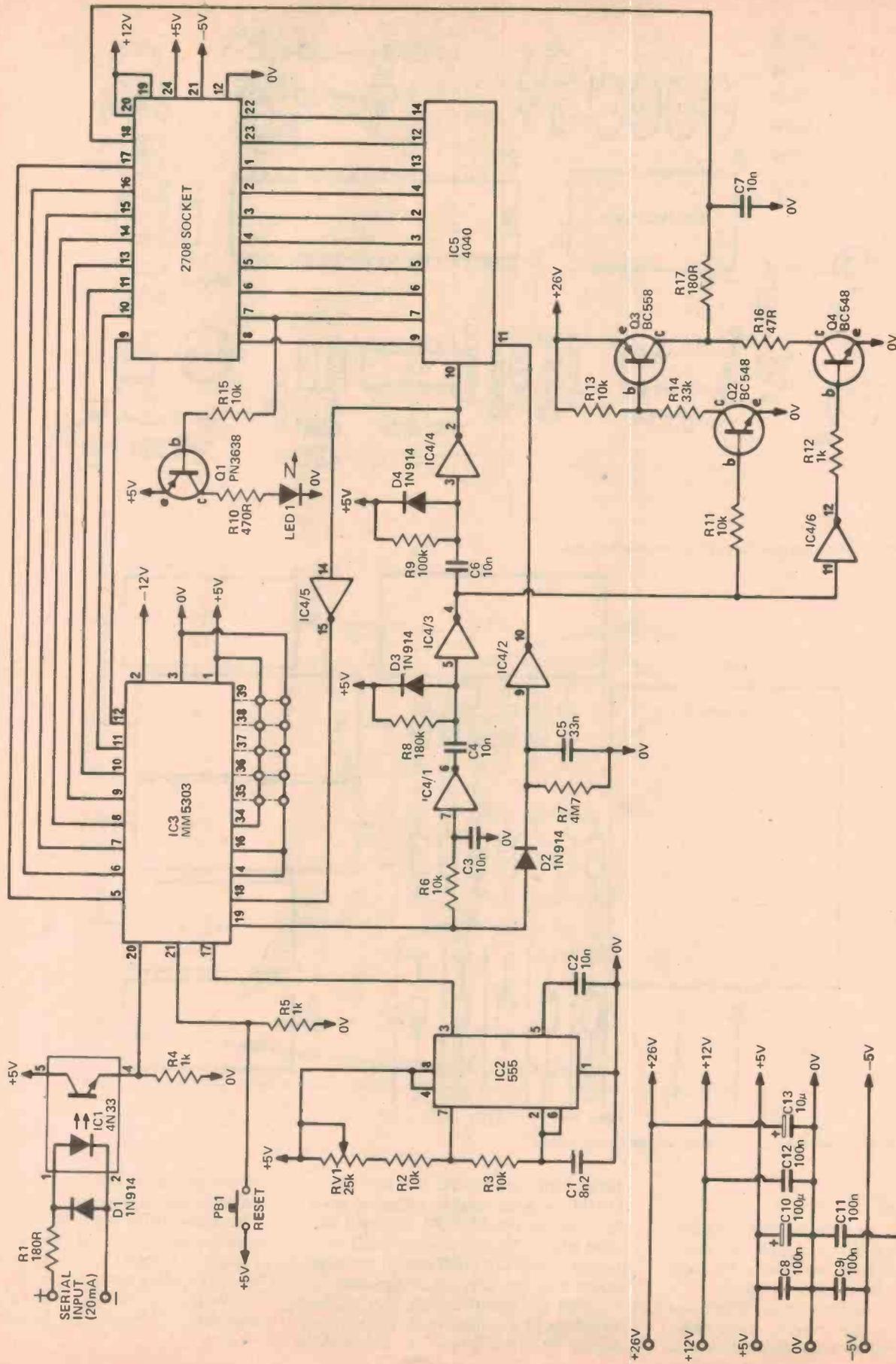


Fig. 3. The circuit diagram of the main circuit.

## HOW IT WORKS - ETI 638

used for this.

The address lines for the EPROM are supplied by IC5 which is a 12 bit binary counter (we use only the first 10 bits) and this is reset to zero when no data is being received. On pin 19 of the UART we have an output which goes high when the serial data has been received and after this has been delayed by about 100  $\mu$ s (R6/C3) the output of IC4/1 goes low. This triggers a 1 ms monostable (C4, R8, IC4/3) which drives the transistors Q2-Q4 to provide a 26V pulse to pin 18 of the 2708. At the end of this 1ms pulse a second mono is triggered (C6, R9, IC4/4), the UART is reset (pin 19 goes low again) and the address counter IC5 is incremented. The output (pin 19) of IC3 also charges C5 via D2 when it goes high. This causes the output of IC4/2 to go low allowing IC5 to be toggled (pin 11 of IC5 is the reset line). Provided the output of IC3 goes high regularly corresponding to data being received at 300 Baud C5 does not have time to discharge and the reset line remains low. If there is a pause at the end of a complete cycle the reset line will go high and will correct any error which may have been caused by a possible glitch.

The power indicator LED is driven by one of the outputs of IC5 and is turned on and off quickly indicating data is being received.

by byte at the port. As the programming pulse width is approximately 1ms, the whole 1024 bytes should be output at least 100 times. In practice, this should be increased by 25% or so to allow for the effects of component tolerances.

### Programmer Design

Use of the UART considerably simplifies the software requirements of the system which will drive the programmer, all that is necessary is a program which will output the required memory contents in order and repeat this for the required number of times.

A fully erased EPROM has every bit set to the "1" state. Programming sets selected bits to "0". To program a 2708 the selected address and corresponding data has to be applied to the EPROM and a 26V pulse applied to the program input pin. To make life more difficult each location has to be selected and programmed in sequence. Also a total time the program input has to be high for each location is 100 ms but the pulse used cannot be less than 100  $\mu$ s or longer than 1ms with about 1 ms recommended. This means that the IC has to be cycled through completely around 100 times for best results!

As we have a computer any way, (otherwise why the need for an EPROM!) we use it to provide the sequencing and timing needed.

The computer is programmed to copy data in its memory (1024 bytes) and sequentially transmit in serial form each byte 125 times. It also pauses for about 1/4 second each 1024 bytes.

The serial information is transferred from the 20 mA loop into a 0-5V signal by the opto coupler, IC1, whose output is fed into the input of the UART IC3. This IC then converts this information into parallel form on pins 5-12 which is presented to the EPROM on its data lines. This IC needs a clock input at 16 times the Baud rate (4800Hz for 300 Baud) and IC2 is

General Electric G15P8). The chip(s) should be placed about an inch or so from the tube and left for at least half an hour to ensure complete erasure.

To program the device, the pattern to be written should be available in RAM. The programmer is connected to the microprocessor's serial port which is configured for the appropriate signal format selected for the programmer (see table 3). The programmer is then reset to initialize the UART and ensure that the address counter starts at address zero. All that remains is for the microprocessor to output the contents of the selected RAM page,

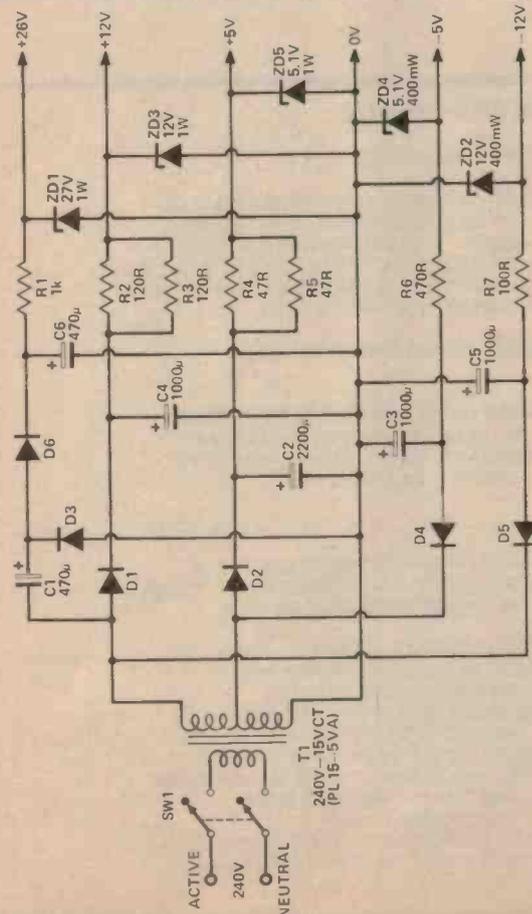


Fig. 4. The circuit diagram of the power supply.

### The 2708

At this point we digress to describe the 2708 and the steps involved in using and programming it.

The device is a static 8192 bit EPROM organised as 1024 x 8. It is packaged in a 24 pin DIP with a quartz window which allows the data stored in the memory to be erased by exposure to ultra-violet light.

Reading the device is quite straightforward. The appropriate address is applied at the ten address pins, the chip select pin is taken low and after the appropriate access time (120ns from CS or 450ns from address select) the data is available at the eight output pins.

Fortunately, and in contrast to its predecessors, the 2708 is also simple to program. The chip select pin is taken to the 'write enable' level of +12V and the applied address is cycled from 000H to 3FFH with the appropriate data applied at each address. After the data and

address lines have settled at each address, a 26V pulse of 0.1 ms to 1 ms duration is applied at the programming pin. The entire cycle of 1024 addresses is repeated until each address has received a minimum of 100 ms program pulse time.

Erasure is the simplest operation of all. The window is uncovered and the chip placed an inch or so away from an ultra violet tube. After half an hour or so, the memory is fully erased (to all '1's) and is ready for re-programming.

### Operation

A fully erased EPROM has every bit set to the '1' state. Programming sets selected bits to '0'. It follows that a 2708 can be reprogrammed without erasing if there are no cases where a bit must be changed from '0' to '1', otherwise the device must be erased by exposure to ultra violet light. Any 'germinal' UV tube is suitable for erasing (eg:

# Project 638

**TABLE 1. 6800 EPROM DRIVER FOR D2**

6800 EPROM PROGRAMMER DRIVER FOR D2

```

OUTCH      EQU    E37A
PAGESTART EQU    04
NEXTPAGE  EQU    08
ACIAS     EQU    8008
;INITIALISATION OF ACIA
0000 86 55          LDA A  # %0101001
0002 B7 80 08      STA A
;MAIN PROGRAM
0005 C6 7D          LDA B  125
0007 CE 00 00      NEWCYCLE: LDX PAGESTART
000A A6 00          NEXTBYTE: LDA A,  X
000C BD E3 7A      JSR  OUTCH
000F 08            INX
0010 8C 04 00      CPX  NEXTPAGE
0013 26 F5         BNE  NEXTBYTE
0015 36            PSH  A
0016 37            PSH  B
0017 86 FF         LDA  A  SFF
0019 C6 FF         LDA  B  SFF
001B 5A            LOOP: DEC  B
001C 26 FD         BNE  LOOP
001E 4A            DEC  A
001F 26 FA         BNE  LOOP
0021 33            PUL  B
0022 32            PUL  A
0023 5A            DEC  B
0024 26 E1        BNE  NEWCYCLE
0026 3F            SWI
    
```

For Test:  
000A 86 XX NEXTBYTE: LDA A XX  
outputs ASCII character XX  
\_or  
000A 4C NEXTBYTE: INC A  
000B 01 NOP  
outputs incrementing characters.

**TABLE 3 SIGNAL FORMAT OPTIONS**

| OPTION          | INPUT | UART PIN | LEVEL |
|-----------------|-------|----------|-------|
| No OF DATA BITS | 8     | NDB2     | 37 H  |
|                 |       | NDB1     | 38 H  |
| PARITY          | 7     | NDB2     | 37 H  |
|                 |       | NDB1     | 38 L  |
|                 | EVEN  | NPB      | 35 L  |
|                 |       | POE      | 39 H  |
|                 | ODD   | NPB      | 35 L  |
|                 |       | POE      | 39 L  |
| INHIBIT         | NPB   | 35 H     |       |
|                 | POE   | 39 X     |       |
| No OF STOP BITS | 1     | NSB      | 36 L  |
|                 |       | NSB      | 36 H  |

H=HIGH (+5V) L=LOW (0V) X=DON'T CARE

**TABLE 2 - INTERFACE PROGRAM FOR 8080/Z80**

```

;***** INTERFACE PROGRAM FOR 2708 EPROM PROGRAMMER *****
;
PAGESTART: EQU    04H          ; HIGH ORDER BYTE OF RAM ADDRESS
; TO BE LOADED IN EPROM ADDRESS
; ZERO - LOW ORDER BYTE IS ZERO
NEXTPAGE:  EQU    08H          ; HIGH ORDER BYTE OF PAGESTART + 1024
CTRL:      EQU    0           ; ADDRESS OF I/O STATUS & CONTROL PORT
DATA:      EQU    1           ; ADDRESS OF I/O DATA PORT
;
; INITIALIZATION - NOTE: SYSTEM DEPENDENT. THIS SEGMENT WRITTEN
; FOR AN INTEL 8251 SERIAL I/O PORT
;
0000: 3E 4E          MVI  A, 4EH          ; MODE INSTRUCTION. SELECT 1 STOP,
0002: D3 00          OUT  CTRL          ; 8 DATA AND NO PARITY FORMAT
0004: 3E 11          MVI  A, 11H         ; COMMAND INSTRUCTION. RESET 8251
0006: D3 00          OUT  CTRL          ; AND SET TX ENABLE
;
; MAIN PROGRAM
0008: 06 7D          MVI  B, 125         ; NO OF PROGRAMMER CYCLES TO B
000A: 26 04          NEWCYCLE: MVI  H, PAGESTART ; HIGH ORDER ADDRESS OF BYTE 1 TO H
000C: 2E 00          MVI  L, 0           ; LOW ORDER ADDRESS TO L
000E:                NEXTBYTE:
000E: DB 00          TESTPOINT: IN    CTRL          ; READ I/O PORT STATUS
0010: E6 01          ANI  01H           ; MASK ALL EXCEPT READY BIT
0012: CA 0E 00       JZ   TESTPORT      ; LOOP UNTIL READY BIT SET
0015: 7E            MOV  A, M           ; MOVE SELECTED BYTE TO ACC
0016: D3 01          OUT  DATA          ; AND SEND TO PROGRAMMER
0018: 23            INX  H             ; SELECT NEXT BYTE TO BE SENT
0019: 7C            MOV  A, H           ; TEST CONTENTS OF H TO SEE WHETHER
001A: FE 08          CPI  NEXTPAGE       ; LAST BYTE HAS BEEN SENT
001C: C2 0E 00       JNZ  NEXTBYTE      ; IF NOT, REPEAT LOOP
001F: 05            DCR  B             ; ELSE DECREMENT CYCLE COUNTER
0020: C2 0A 00       JNZ  NEWCYCLE      ; IF NOT FINISHED START NEW CYCLE
0023: 76            HLT                    ; ELSE HALT
    
```



## A WORLD OF ENERGY CONSERVATION

Think of how much energy is wasted in the production of millions of zinc or alkaline batteries. Once their energy supply has been used up, they are discarded.

The General Electric rechargeable battery system is the answer to power conservation. The G.E. battery is rechargeable and thus recyclable. Conservation of energy is the essence of this product. Don't throw away batteries. G.E.'s nickel cadmium rechargeable batteries can be recharged up to a thousand times. They last for years.

The features of the G.E. rechargeable battery are:-

- Constant voltage throughout the discharge period.

- Available in all standard sizes.
- Special heavy duty versions for industrial use.
- The heavy duty rechargeable batteries are designed to withstand high ambient temperatures and continuous discharge overload.

Be part of the energy conservation movement. Look into the General Electric Rechargeable Battery System.

For information on the G.E. nickel cadmium rechargeable battery system and list of stockists, fill in the coupon and return to Australian General Electric Battery Division, 86-90 Bay Street, Ultimo, N.S.W. 2007.

Name .....

Address .....

.....

Post Code .....

GENERAL  ELECTRIC



# FRG -7

## RECEIVER

for amateurs,  
novices  
and  
short-wave  
listeners



Latest model includes fine-tune adjustment

### MANUFACTURER'S TECHNICAL DATA

- Electronic band changing.
- 0.5-29.9 MHz continuous coverage.
- Uses Wadley loop (drift cancellation circuit) to derive synthesized heterodyne oscillator signal.
- LSB, USB, AM and CW.
- Frequency readout better than 10 KHz (readable to 5 KHz).
- Stability within 500 HZ during any 30-minute period after warm-up.
- Better than 0.7 V for 10 dB S N/SSB and CW. Better than 2 V for 10 dB S N/N AM.
- Selectivity 3 KHz at -6 dB, 7 KHz at -50 dB.
- Input Impedance high 0.5-1.6 MHZ. 50-75 ohm 1.6-29.9 MHZ.
- 234V AC 50-60 Hz or 12V DC (external or internal B dry cell).
- Size 340 mm x 153 mm x 285 mm.

### • Price \$348.00

- Prices include S/tax, freight extra. Prices and Specs subject to change.

Explore the wonderful world of short-wave listening.

Hear broadcast stations, amateurs, ships, aircraft and morse code from stations all over the globe.

Provides an introduction into many aspects of electronics and communications, CB's upgrade and widen your scope of operation. The FRG-7 will provide the means of listening to the amateur bands so that you can get the "feel" of amateur "ham" radio.

You can tune into the morse practice transmissions and broadcasts conducted by the Wireless Institute of Australia: the Radio Amateurs representative Society in Australia.

Write for a descriptive brochure and ask for information on study procedures etc. for the novice amateur licence.

Remember, BAIL has been the authorised agent for the YAESU MUSEN CO LTD since 1963. Our experience gathered over these years, and a lifelong participation in electronics, places us in a superior position to handle warranty, after sales service and advice on the wide range of Yaesu amateur radio equipment.

Avoid unauthorised handlers of equipment as it generally results in the supply of non-export 110V sets with 2-core AC power cables, instruction manuals printed in Japanese, lack of service etc. Consult us for advice on your requirements in the field of short-wave listening and amateur radio.

For further information call or write to the Amateur radio specialists.

Australian YAESU Agents since 1963.

**BAIL** 60 Shannon St., Box Hill North  
**ELECTRONIC SERVICES** Vic. 3129  
 Ph 89 2213

## EASTERN ELECTRONIC COMPONENTS

35 Mahoneys Road,  
Forest Hill. 3131.  
Telephone 878-7876.

### A NEW SUPPLIER OF ELECTRONIC COMPONENTS IN THE EASTERN SUBURBS

HERE ARE A FEW EXAMPLES OF OUR WIDE RANGE

#### LINEAR I.C.s

|        |      |        |      |
|--------|------|--------|------|
| LM 555 | 0-40 | LM 741 | 0-45 |
| LM 301 | 0-45 | LM 380 | 1-32 |
| LM3900 | 0-80 | 7805   | 1-20 |

#### TTL I.C.s

|      |      |      |      |
|------|------|------|------|
| 7401 | 0-31 | 7402 | 0-32 |
| 7408 | 0-32 | 7420 | 0-32 |
| 7492 | 0-81 | 7493 | 0-81 |

#### CMOS I.C.s

|      |      |      |      |
|------|------|------|------|
| 4000 | 0-32 | 4011 | 0-32 |
| 4024 | 0-70 | 4068 | 0-32 |

#### TRANSISTORS

|                 |      |
|-----------------|------|
| BC547, 548, 549 | 0-19 |
| BC107, 108, 109 | 0-30 |
| 2N 3638 SPECIAL | 0-10 |

|       |        |       |
|-------|--------|-------|
| 2708  | EPROM  | 20-00 |
| 2102  | RAM    | 1-75  |
| 2513  | ROM    | 19-80 |
| 93427 | PROM   | 3-00  |
| 3850  | F8 CPU | 14-95 |
| 3853  | F8 SMI | 12-95 |

#### THIS MONTH'S SPECIALS

|         |           |      |      |
|---------|-----------|------|------|
| 7400    | 0-16      | 4001 | 0-22 |
| FND 357 | 7-SEGMENT |      | 1-00 |
| BC208   | 0-10      | 7815 | 0-80 |

#### OTHER ITEMS INCLUDE

RESISTORS 1/4, 1/2, 1&5 Watt  
CAPACITORS disc, electro, tags and greencaps.

R.F. CHOKES 3.3μH - 800μH

SWITCHES and HARDWARE

MICROPROCESSORS including 6800, SC/MP, PACE, 2650, F8, 6100.

CHARTPACK PCB ARTWORK  
PRINTED CIRCUIT BOARDS for ETI and EA projects.

All of the above prices include sales tax.

Quantity discounts available  
Mail orders catered for. Pack and post 50 cents.

2702.12

\$ 1.00

each

**P&P FREE**

LOW POWER, 650 ns  
ACCESS TIME

BRAND NEW,  
FULLY GUARANTEED!

**MAILMAN**  
**ELECTRONICS**  
 P.O.Box 536 Lane Cove  
 PH: (02) 498-3405 A.H.

# RADIO PARTS

## VOLTAGE REGULATORS

|                                                                  |        |
|------------------------------------------------------------------|--------|
| LM300H TO5 Voltage Regulator                                     | \$3.60 |
| LM304H TO5 Negative Regulator                                    | 2.83   |
| LM305H TO5 Voltage Regulator                                     | 1.07   |
| LM309H TO5 5 Volt Regulator                                      | 2.61   |
| LM309K TO3 5 Volt Regulator                                      | 2.74   |
| LM317T TO220 3 Terminal Adjustable Regulator                     | 3.19   |
| LM317K TO3 3 Terminal Adjustable Regulator                       | 4.59   |
| LM320T TO220 Neg. 1 Amp Regulators, 5, 6, 8, 12, 15, 18, 24 volt | 2.74   |
| LM320K TO3 Neg. 1 Amp Regulators 5, 6, 8, 12, 15, 18, 24 volt    | 5.04   |
| LM323K TO3 Pos. 3 Amp — 5 Volt Regulator                         | 7.09   |
| LM340T TO220 Pos. 1 Amp Regulators 5, 6, 8, 12, 15, 18, 24 volt  | 1.59   |
| LM340K TO3 Pos. 1 Amp Regulators 5, 6, 8, 12, 15, 18, 24 volt    | 4.02   |
| LM723CH TO5 Voltage Regulator                                    | 1.20   |
| LM723CN 14 Pin Dtl Voltage Regulator                             | 0.71   |

Prices include sales tax.

## OPERATIONAL AMPLIFIERS/BUFFERS

|                                                           |        |
|-----------------------------------------------------------|--------|
| LM002CN 10 pin dfl Current Amp                            | 7.29   |
| LM0042CH TO5 low cost FET Op Amp                          | 5.69   |
| LM301H TO5 Op Amp                                         | 0.69   |
| LM301A 8 pin dfl Op Amp                                   | 0.41   |
| LM302H TO5 Voltage Follower                               | 3.83   |
| LM307H TO5 Op Amp                                         | 1.15   |
| LM307N 8 pin dfl Op Amp                                   | 0.66   |
| LM308N 8 pin dfl Op Amp                                   | 1.10   |
| LM318N 8 pin dfl Op Amp                                   | 3.17   |
| LM324N 14 pin dfl low power quad Op Amp                   | 1.10   |
| LM324N TO5 high voltage Op Amp                            | 8.13   |
| LM348N 14 pin dfl quad 741 Op Amp                         | 1.50   |
| LM349N 14 pin dfl wide-band decompensated quad 741 Op Amp | 2.30   |
| LM358N 8 pin dfl low power dual Op Amp                    | 0.97   |
| LM709CH TO5 operational amplifier                         | 1.10   |
| LM709CN 8 pin dfl Op Amp                                  | 0.82   |
| LM741CH TO5 operational amplifier                         | 0.61   |
| LM741CN 8 pin dfl Op Amp                                  | 0.41   |
| LM747CN 14 pin dfl dual Op Amp                            | 1.15   |
| LM1458N 14 pin dfl dual Op Amp                            | \$0.82 |
| LM3900N 14 pin dfl quad amp                               | 0.94   |
| LM4250H TO5 Programmable Op Amp                           | 2.32   |

Prices include sales tax.

## VOLTAGE COMPARATORS

|                                                                |      |
|----------------------------------------------------------------|------|
| LM311N 8 pin dfl voltage comparator                            | 0.89 |
| LM319N 14 pin dfl high speed dual comparator                   | 4.54 |
| LM339N 14 pin dfl low power low offset voltage quad comparator | 0.92 |
| LM360H TO5 high speed differential comparator                  | 5.23 |
| LM361H TO5 high speed differential comparator                  | 3.83 |
| LM393N 8 pin dfl low power low offset voltage dual comparator  | 1.25 |
| LM710H TO5 voltage comparator                                  | 0.94 |
| LM711H TO5 dual comparator                                     | 0.94 |

Prices include sales tax.

## AUDIO, RADIO AND TV CIRCUITS

|                                                         |        |
|---------------------------------------------------------|--------|
| LN370N 14 pin dfl AGC/Squelch amp                       | 5.48   |
| LM371H TO5 Integrated RF/IF amp                         | 4.02   |
| LM372H TO5 AM IF strip                                  | 4.78   |
| LM373H TO5 AM/FM/SSB IF AMP/detector                    | 6.18   |
| LM374H TO5 AM/FM/SSB IF video amp/detector              | 5.07   |
| LM375N 14 pin dfl oscillator and buffer with TTL output | 5.74   |
| LM377N 14 pin dfl dual 2 watt audio amp                 | 3.06   |
| LM378N 14 pin dfl dual 4 watt audio amp                 | 3.24   |
| LM379S 14 pin in line dual 6 watt audio amp             | 6.45   |
| LM380N 14 pin dfl audio power amp                       | 1.73   |
| LM381N 14 pin dfl dual preamp                           | \$2.87 |
| LM381AN 14 pin dfl low noise dual preamp                | 4.59   |
| LM382N 14 pin dfl low noise dual preamp                 | 2.23   |
| LM384N 14 pin dfl 5 watt audio power amp                | 2.55   |
| LM386N 8 pin dfl low voltage audio power amp            | 1.40   |
| LM387N 8 pin dfl dual preamp                            | 2.63   |
| LM388N 14 pin dfl 1.5 watt audio power amp              | 1.72   |
| LM1303N 14 pin dfl stereo preamp                        | 1.68   |
| LM1304N 14 pin dfl FM multiplex stereo demodulator      | 2.04   |
| LM1305N 14 pin dfl FM multiplex stereo demodulator      | 2.04   |
| LM3065N 14 pin dfl television sound system              | 1.61   |

Prices include sales tax.

ESTABLISHED SINCE 1942 . . . NOW CARRYING  
IN EXCESS OF 12,000 LINES

## DIGITAL IC'S

|                                                                                        |        |
|----------------------------------------------------------------------------------------|--------|
| SN7400N 14 pin dfl quad 2 — input nand gate                                            | \$0.28 |
| SN7401N 14 pin dfl quad 2 — input nand gate with open collector outputs                | 0.39   |
| SN7402N 14 pin dfl quad 2 — input nor gates                                            | 0.28   |
| SN7403N 14 pin dfl quad 2 — input nand gate with open collector outputs                | 0.40   |
| SN7404N 14 pin dfl hex inverter                                                        | 0.30   |
| SN7405N 14 pin dfl hex inverter with open collector outputs                            | 0.32   |
| SN7407N 14 pin dfl hex buffer with open collector high voltage outputs                 | 0.97   |
| SN7408N 14 pin dfl quad 2 — input and gate                                             | 0.39   |
| SN7410N 14 pin dfl triple 3 — input nand gate                                          | 0.32   |
| SN7411N 14 pin dfl triple 3 — input and gate                                           | 0.39   |
| SN7413N 14 pin dfl dual 4 — input nand schmitt trigger                                 | 0.51   |
| SN7414N 14 pin dfl hex schmitt trigger                                                 | 1.25   |
| SN7416N 14 pin dfl hex buffer with open collector high voltage outputs                 | 0.39   |
| SN7420N 14 pin dfl dual 4 — input nand gate                                            | 0.30   |
| SN7430N 14 pin dfl 8 — input nand gate                                                 | 0.32   |
| SN7432N 14 pin dfl quad 2 — input or gate                                              | 0.53   |
| SN7437N 14 pin dfl quad 2 — input nand buffers                                         | 1.32   |
| SN7441N 16 pin dfl BCD/decimal decoder/driver                                          | 2.42   |
| SN7442N 16 pin dfl BCD/decimal decoder                                                 | 1.84   |
| SN7446N 16 pin dfl BCD/7 — segment decoder/driver                                      | 0.97   |
| SN7447N 16 pin dfl BCD/7 — segment decoder/driver                                      | 1.90   |
| SN7472N 14 pin dfl and — gated J-K master-slave flip flop with pre-set and clear       | 0.90   |
| SN7473N 14 pin dfl dual J-K flip flop with clear                                       | 1.01   |
| SN7474N 14 pin dfl dual D positive — edge — triggered flip flop with pre-set and clear | 0.78   |
| SN7475N 16 pin dfl quad latch                                                          | 0.63   |
| SN7476N 16 pin dfl dual J-K flip flop with pre-set and clear                           | 0.51   |
| SN7489N 16 pin dfl 64-bit read/write                                                   | 6.53   |
| SN7490N 14 pin dfl decade, divide by 12, and binary counters                           | 1.04   |
| SN74107N 14 pin dfl dual J-K master-slave flip flop with clear                         | 0.48   |
| SN74154N 24 pin dfl 4-line to 16-line decoder/demultiplexer                            | 1.64   |
| SN74161N 16 pin dfl synchronous 4-bit counter                                          | 1.17   |
| SN74164N 14 pin dfl 8-bit serial in/parallel out shift register                        | 1.93   |

Prices include sales tax.

## ZENER DIODES 400 MW

All 20c each including sales tax

|            |           |
|------------|-----------|
| BZX79-C4V7 | BZX79-C10 |
| BZX79-C5V1 | BZX79-C11 |
| BZX79-C5V6 | BZX79-C12 |
| BZX79-C6V2 | BZX79-C15 |
| BZX79-C6V8 | BZX79-C16 |
| BZX79-C7V5 | BZX79-C18 |
| BZX79-C8V2 | BZX79-C24 |
| BZX79-C9V1 | BZX79-C27 |

## TRANSISTORS

|       |        |        |      |
|-------|--------|--------|------|
| AC128 | \$0.32 | BC559  | 0.20 |
| AC187 | 0.82   | BC637  | 0.20 |
| AC188 | 0.82   | BC640  | 0.20 |
| A0161 | 1.56   | BD135  | 0.71 |
| A0162 | 1.53   | BD137  | 0.65 |
| BC107 | 0.32   | BD139  | 0.77 |
| BC108 | 0.31   | BD140  | 0.79 |
| BC109 | 0.31   | BF115  | 0.71 |
| BC148 | 0.43   | BF167  | 0.91 |
| BC178 | 0.43   | BF173  | 0.97 |
| BC179 | 0.46   | BF179  | 0.97 |
| BC321 | 0.23   | BF180  | 0.97 |
| BC327 | 0.20   | BF200  | 0.87 |
| BC328 | 0.20   | BF335  | 1.02 |
| BC337 | 0.20   | BF337  | 1.02 |
| BC338 | 0.22   | BF338  | 1.05 |
| BC547 | 0.20   | BFY50  | 0.48 |
| BC548 | 0.20   | BU201  | 0.56 |
| BC549 | 0.20   | BU208  | 0.56 |
| BC557 | 0.24   | TIP31A | 0.82 |
| BC558 | 0.24   | TIP32A | 0.84 |

|         |        |                          |      |
|---------|--------|--------------------------|------|
| 2N1613  | 0.74   | 2N3568                   | 0.29 |
| 2N2102  | 0.82   | 2N3638                   | 0.24 |
| 2N2218  | 0.74   | 2N3638A                  | 0.29 |
| 2N2219  | 0.61   | 2N3643                   | 0.31 |
| 2N2222  | 0.48   | 2N3644                   | 0.24 |
| 2N2270  | 0.84   | 2N3645                   | 0.36 |
| 2N2369  | \$0.59 | 2N3819                   | 0.82 |
| 2N2904  | 0.66   | 2N3903                   | 0.36 |
| 2N2904A | 0.79   | 2N3906                   | 0.33 |
| 2N2905  | 0.69   | 2N4032                   | 1.12 |
| 2N2905A | 0.74   | 2N4033                   | 1.07 |
| 2N2906  | 0.54   | 2N4036                   | 1.07 |
| 2N2907  | 0.71   | 2N4037                   | 0.93 |
| 2N2907A | 0.84   | 2N4354                   | 0.46 |
| 2N3019  | 1.30   | 2N4355                   | 0.24 |
| 2N3053  | 0.66   | 2N4403                   | 0.43 |
| 2N3055  | 1.07   | 2N5459                   | 0.61 |
| 2N3565  | 0.28   | 2N6027                   | 0.88 |
| 2N3566  | 0.33   | Prices include sales tax |      |
| 2N3567  | 0.36   |                          |      |

## SILICON DIODES — 1 AMP

|        |            |      |
|--------|------------|------|
| IN4001 | — 50 PIV   | 0.13 |
| IN4003 | — 200 PIV  | 0.13 |
| IN4004 | — 400 PIV  | 0.14 |
| IN4005 | — 600 PIV  | 0.17 |
| IN4007 | — 1000 PIV | 0.23 |

Prices include sales tax.

## SINCLAIR PDM35

\$61.89 including sales tax  
Specifications:— Sensitivity: 3½ Digit LED Display (10 Meg Input DC); DC Voltage: 1MV to 1000V (Four Ranges); AC Voltage: 1V to 500V (40 Hz-5 kHz); DC Current: 1 MA to 200 MA (Six Ranges); Resistance: 1Ω to 20 MegΩ (Five Ranges); Dimensions: 153 x 76 x 39 mm; Power: 9 volt Battery (e.g. 216 Eveready).

## FLUKE 8020A

\$205.28 including sales tax  
Specifications:— Sensitivity: 3½ Digit Liquid Crystal Display (10 Meg all ranges); Dimensions: 180 x 86 x 45 mm; Power Requirement: 9 Volt Battery e.g. 216 Eveready (Further information available upon request).

## DOMINION PRO SERIES. HIGH QUALITY REGULATED POWER SUPPLIES

11 to 16 volts adjustable. Ideal where long continuous use and excellent regulation are required. All supplies are totally short-circuit proof.

NG3 3.5 amps — \$49.00 including tax. For CB, hobbyists, experimenters, school, etc. Input 240V AC, Output 11 to 16V DC, Regulation 0-3.5A 20mV. Ripple at 3.5 amps-4mV. Dimensions: 3¼" wide x 4½" deep x 6" high. Weight approx 5 lb.

NG7 6 amps — \$57.00 including tax. High power single side band CB radios, service bench repairs, 2-way radio base supplies. Input 240V AC, Output 11 to 16V DC, Regulation 0-6A 30 mV. Ripple at 6 amps-4mV. Dimensions: 5" wide x 5¾" deep x 6" high. Weight approx 8 lb.

NG12 12 amps — \$115.00 including tax. Heavy duty model. Ideal for operating high power linear amps, hybrid 2-way radios, etc. Input 240V AC, Output 11 to 16V DC, Regulation 0-12A 10mV. Ripple at 12 amps-1.5mV. Dimensions: 10" wide x 5¾" deep x 6" high. Weight approx 16 lb.

Manufactured by Radio Parts Group. Trade enquiries welcome.

## TMK VF4

\$21.27 including tax. Specifications:— Sensitivity: 2KΩ/Volt DC, 2KΩ/Volt AC; DC Voltage: 0.25V, 2.5V, 10V, 50V, 250V, 1000V; AC Voltage: 10V, 50V, 250V, 1000V; DC Current: 0-500 μA, 10MA, 250MA, 10A; Resistance: x1, x10, x100, x1K, 1.6, 6.0, 60.0, 600.0; Capacitance: 500 pF to 1 μF (in two Ranges); Decibels: —15 to plus 32dB (in four Ranges); Dimensions: 145 x 95 x 45 mm.

## TMK TP5SN

\$25.18 including tax. Specifications:— Sensitivity: 20KΩ/Volt DC, 8KΩ/Volt AC; DC Voltage: 0.5V, 5V, 50V, 250V, 500V, 1000V; AC Voltage: 10V, 50V, 250V, 500V, 1000V; DC Current: 0-50 μA, 5MA, 50MA, 500MA; Resistance: x1, x10, x100, x1K (60, 600, 6K, 60K Centre Scale); Capacitance: 50 pF to 0.1 μF (in two Ranges); Decibels: —20 to plus 36dB; Dimensions: 135 x 95 x 40 mm.

## TMK200

\$27.91 including tax. Specifications:— Sensitivity: 20KΩ/Volt DC, 10KΩ/Volt AC; DC Voltage: 0.6V, 6V, 30V, 120V, 600V, 1200V; AC Voltage: 6V, 30V, 120V, 600V, 1200V; DC Current: 0.06MA, 6MA, 60MA, 600MA; Resistance: 0-10KΩ, 100KΩ, 1MΩ, 10MΩ; Capacitance: .002 μF to 0.2 μF; Decibels: —20 to plus 63dB; Dimensions: 130 x 90 x 35 mm.

## TMK500

\$41.22 including tax. Specifications:— Sensitivity: 30KΩ/Volt DC, 13KΩ/Volt AC; DC Voltage: 0.25V, 1V, 2.5V, 10V, 25V, 100V, 250V, 1000V; AC Voltage: 2.5V, 10V, 25V, 100V, 250V, 500V, 1000V; DC Current: 0.05MA, 5MA 50MA 500MA, 12A; Short Test; Internal Buzzer; Decibels: —20 to plus 56dB; Dimensions: 160 x 85 x 70 mm.

## SWE-CHECK MODEL 300

Cathode ray tube tester and rejuvenator. Tests each gun separately indicating Shorts, Open Circuits, Emission and Cut-off characteristics. Also removes shorts and rejuvenates low emission tubes. Adaptors available to suit all colour tubes on the Australian market (see below). \$253.00 including sales tax.

## COLOUR PICTURE TUBE ADAPTORS

Part Nos. 107-116. To suit above Model 300. (Detailed listing of tube types for which each Adaptor is suitable is enclosed with every Adaptor). Now individually packaged in convenient and protective cylindrical containers. \$10.35 including sales tax.

## NEW "SOLDER-EATER" DESOLDERING BRAID (1.8m)

In cassette package. For standard PCB — Part No. 213. For miniature PCB — Part No. 214. \$1.60 each (exempt).

To: Radio Parts Group, 562 Spencer St., West Melbourne. (03) 329-7888.  
1103 Dandenong Rd., East Malvern. (03) 211-8122.

Please send me

I am enclosing cheque  money order

or please debit my Bankcard — Number

\$5 minimum order plus \$1 P&P. Orders in excess of \$25 freight free in Aust. Outside Aust. freight on. Write for our comprehensive Semi-Conductor price list.

Signature

Name

Address

P/Code

# SIMPLE 12V TO 22V CONVERTER

Simple voltage doubler powers op-amps and similar circuits from a 12V supply.

WHILE MOST AUTOMOTIVE equipment can be designed to operate on a single +12V supply it sometimes becomes necessary to develop a voltage above 12V, or a negative voltage. This project was initiated when one of our PC boards suppliers wanted to run one of the Philips TV type UHF pre-amplifiers as a booster for his UHF CB rig (receiver only). He needed 20–24V at 35mA. Then almost in the same week a reader came into the office wanting a circuit which will allow him to charge a 12 volt pack of Nicads at 150mA from the car battery.

While the obvious choice is an inverter the relative low power requirement weighed against the cost, complexity and noise generated by such a device made us look to an alternative design. With this unit we simply generate a square wave and then voltage double it to give 22V or, with a slight reconnection of the rectifier circuit, –10V. If both rectifiers are used both +22V and –10V (total 32V) is obtainable.

The circuit however is not limited to 12V and is useful over the 6–15V range. The output voltage is approximately twice the input less 2 volts.

## Construction

As this project is very simple any construction method may be used. However the PC board described makes the assembly very easy. The only point to watch is in the handling of the IC which is CMOS – avoid contact with the pins, and solder the power supply pins (7 & 14) first.



## SPECIFICATION – ETI 248

|                        |                      |
|------------------------|----------------------|
| Input voltage          | 6 – 15V              |
| Output voltage         | twice input, less 2V |
| Output impedance       | ≈ 15 ohms            |
| Maximum load           | 125 ohms             |
| Maximum output current |                      |
| 6V input               | 75mA                 |
| 8V input               | 105mA                |
| 10V input              | 130mA                |
| 12V input              | 165mA                |
| 14V input              | 190mA                |
| 15V input              | 210mA                |
| Idle current           |                      |
| @ 12V input            | 21mA                 |
| Efficiency             |                      |
| @ 165mA, 12V input     | 75%                  |

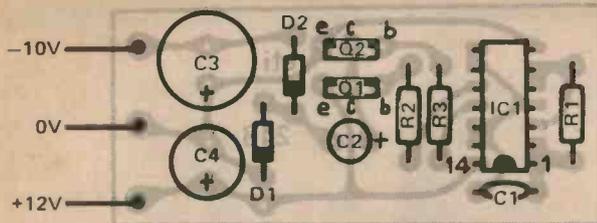


Fig. 1. The component overlay of the -10V version.

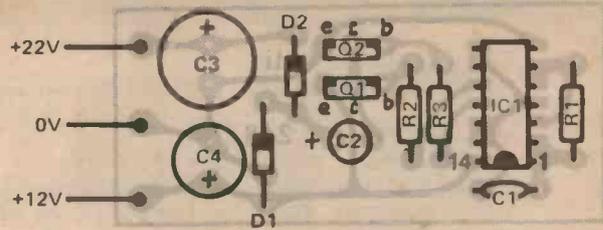


Fig. 2. The component overlay of the +22V version.

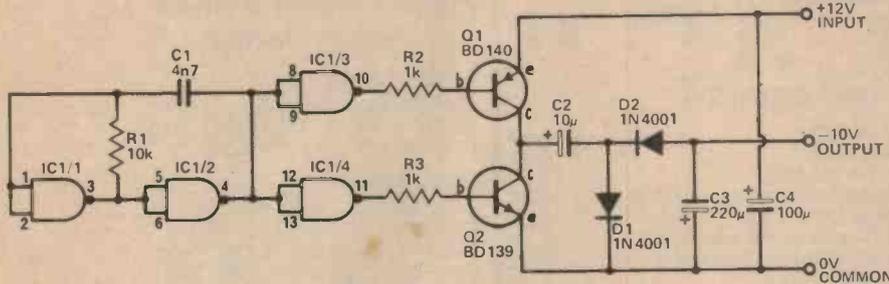


Fig. 3. The circuit diagram of the -10V version.

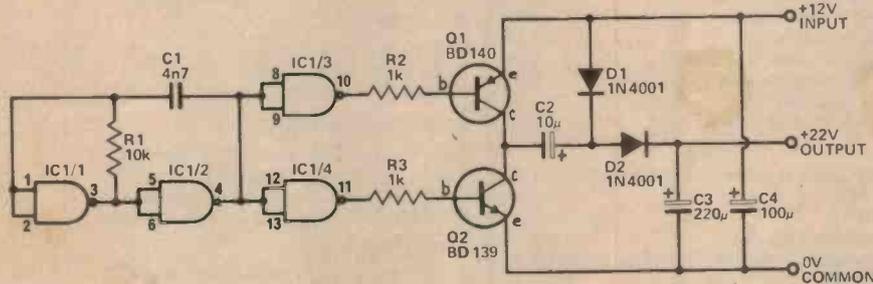


Fig. 4. The circuit diagram of the +22V version.

### PARTS LIST - ETI 248

Resistors all 1/2W 5%

R1 . . . . . 10k

R2, 3 . . . . . 1k

Capacitors

C1 . . . . . 4n7 polyester

C2 . . . . . 10μ 25V electro

C3 . . . . . 220μ 35V electro

C4 . . . . . 100μ 25V electro

Semiconductors

IC1 . . . . . 4001B or 4011B (CMOS)

Q1 . . . . . BD136 or BD140

Q2 . . . . . BD135 or BD139

D1, 2 . . . . . 1N4001

Miscellaneous

PC board ETI 248

### HOW IT WORKS - ETI 248

The first two parts of IC1 form a 10kHz square wave oscillator. The frequency is determined by the RC network R1 C1. Reducing either of these causes the frequency to increase and viceversa. The output of the oscillator is buffered by both IC1/3 and IC1/4. These drive Q1 and Q2 via R2 and R3 alternatively turning them on and off i.e. Q1 on Q2 off then Q1 off Q2 on etc. We have used two separate buffers as when the output of IC1/3 goes low, turning on Q1, it is not low enough to ensure Q2 would be turned off if it was driven by the same output.

Note that as the IC is connected as a quad inverter either a NOR (4001) or NAND (4011) can be used. It should however be the buffered (B series) type to ensure that the oscillator section will start.

The output at the collectors of Q1 and Q2 is a square wave between 12V and 0V. This is then voltage doubled by C2, 3 and D1, 2. Due to the natural losses involved in charging and discharging capacitors a maximum efficiency of 75% is obtained and increasing the power beyond the present ratings, while possible, is not practical. If a higher voltage is required voltage tripling or quadrupling is possible.

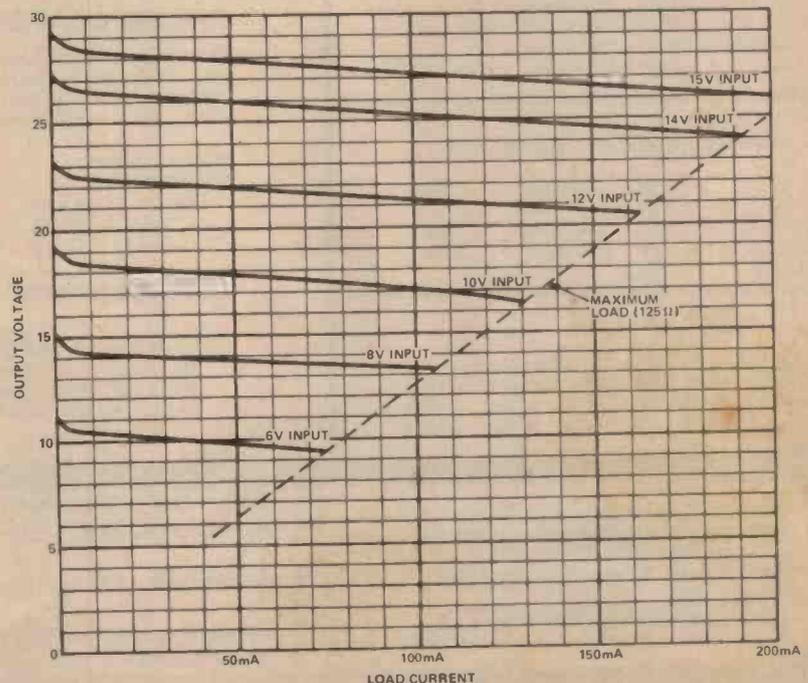


Fig. 5. Graph showing the relationship between the output voltage and load current for various input voltages.

# SPECIALS (Offer valid till August 15th 1978 or until stocks are depleted)

|               |                          |                       |               |
|---------------|--------------------------|-----------------------|---------------|
| 741 OP AMPS   | 5 for \$1.50             | 14 pin solder sockets | 10 for \$2.20 |
| 555 TIMERS    | 5 for \$1.50             | 16 pin solder sockets | 10 for \$2.60 |
| BC547/548/549 | TRANSISTORS 5 for \$0.75 | 6800 CPU (plastic)    | \$17.50 each  |
| BC557/558/559 | TRANSISTORS 5 for \$0.75 | 8080A CPU (plastic)   | \$14.50 each  |

## LOW POWER TTL

(new expanded range)

|         |      |         |      |
|---------|------|---------|------|
| 74LS00  | .32  | 74LS109 | .55  |
| 74LS01  | .32  | 74LS112 | .55  |
| 74LS02  | .32  | 74LS113 | .55  |
| 74LS03  | .32  | 74LS114 | .55  |
| 74LS04  | .35  | 74LS123 | 1.75 |
| 74LS05  | .35  | 74LS132 | 1.55 |
| 74LS08  | .35  | 74LS138 | 1.50 |
| 74LS09  | .35  | 74LS151 | 1.20 |
| 74LS10  | .35  | 74LS154 | 2.50 |
| 74LS11  | .35  | 74LS157 | .90  |
| 74LS12  | .35  | 74LS161 | 2.55 |
| 74LS13  | .85  | 74LS162 | 2.55 |
| 74LS14  | 1.55 | 74LS163 | 1.75 |
| 74LS15  | .40  | 74LS164 | 1.55 |
| 74LS20  | .35  | 74LS165 | 2.15 |
| 74LS21  | .35  | 74LS174 | 1.45 |
| 74LS27  | .35  | 74LS175 | 1.45 |
| 74LS28  | .42  | 74LS190 | 2.50 |
| 74LS30  | .35  | 74LS191 | 2.50 |
| 74LS32  | .35  | 74LS192 | 2.50 |
| 74LS37  | .46  | 74LS193 | 2.50 |
| 74LS38  | .46  | 74LS194 | 2.50 |
| 74LS40  | .35  | 74LS195 | 2.50 |
| 74LS42  | 1.25 | 74LS196 | 2.00 |
| 75LS51  | .40  | 74LS221 | 1.50 |
| 74LS73  | .65  | 74LS240 | 2.70 |
| 74LS74  | .65  | 74LS241 | 2.70 |
| 74LS76  | .60  | 74LS243 | 2.65 |
| 74LS78  | .55  | 74LS244 | 2.70 |
| 74LS85  | 1.50 | 74LS245 | 2.70 |
| 74LS86  | .55  | 74LS253 | 1.95 |
| 74LS90  | 1.20 | 74LS279 | 1.00 |
| 74LS92  | 1.20 | 74LS365 | 1.00 |
| 74LS93  | 1.20 | 74LS366 | 1.00 |
| 74LS95  | 1.60 | 74LS367 | 1.00 |
| 74LS107 | .60  | 74LS368 | 1.00 |

## MICROPROCESSORS

|       |         |          |       |
|-------|---------|----------|-------|
| 8080A | \$15.75 | SC/MP II | 16.75 |
| 6800  | 19.50   | Z80      | 35.00 |
| 2650  | 26.50   |          |       |

## SUPPORT DEVICES

|                                       |         |
|---------------------------------------|---------|
| 8212 8 bit I/O                        | \$ 4.95 |
| 8215 bus driver                       | 5.95    |
| 8224 clock generator                  | 8.50    |
| 8228 system controller/bus driver     | 10.95   |
| 8255 programmable peripheral I/O      | 16.50   |
| 3881 Z80 parallel I/O controller      | 15.50   |
| 3882 Z80 counter timer circuit        | 15.50   |
| 6810 128 byte RAM                     | 5.75    |
| 6820 PIA                              | 13.75   |
| 6850 ACIA                             | 13.75   |
| 6860 600 bps modem                    | 13.75   |
| 8T26 bus transceiver                  | 3.75    |
| 8T97/98 bus drivers                   | 1.95    |
| 8T31 bidirectional I/O port           | 5.75    |
| DM8131 6 bit address comparator       | 6.25    |
| DM8554 quad switch debouncer          | 2.25    |
| DM8553 8 bit addressable latch        | 4.25    |
| <b>ETC</b>                            |         |
| 2513 character generator (upper case) | 14.75   |
| 5303 UART                             | 5.75    |
| 1602 UART                             | 7.50    |
| 5740 keyboard encoder                 | 19.75   |
| 57109 number cruncher with data       | 19.75   |
| 2101 256 x 4 static RAM               | 3.75    |
| 2112 256 x 4 static RAM               | 3.75    |
| 2114 1K x 4 static RAM                | 14.25   |

## BISHOPS GRAPHICS HOBBY PACKS

### BLACK TAPES

CCT201 20 yd. rolls. Specify width; 0.031", 0.04", 0.05", 0.062", 0.08", 0.10", 0.125", 0.150", 0.20" **\$1.55**

### DONUT PADS

|        |                      |
|--------|----------------------|
| CCD216 | 88 pads 0.08" O.D.   |
| CCD101 | 88 pads 0.10" O.D.   |
| CCD102 | 125 pads 0.125" O.D. |
| CCD103 | 125 pads 0.150" O.D. |
| CCD138 | 125 pads 0.187" O.D. |
| CCD139 | 125 pads 0.200" O.D. |
| CCD141 | 125 pads 0.25" O.D.  |

### DUAL IN LINE

|         |                       |               |
|---------|-----------------------|---------------|
| CCD6014 | 16 only 14 pin        | <b>\$1.55</b> |
| CCD6004 | 16 only 16 pin        |               |
| CCD5020 | 2 strips 80 pads 0.1" |               |

### EDGE CONNECTORS

|        |                            |               |
|--------|----------------------------|---------------|
| CC6701 | 80 contacts 0.10" centres  | <b>\$1.55</b> |
| CC6705 | 80 contacts 0.125" centres |               |
| CC6794 | 80 contacts 0.15" centres  |               |
| CC6709 | 80 contacts 0.156" centres |               |

### ARTWORK FILM

(dropout blue 0.1" high stability grid)

|        |                  |               |
|--------|------------------|---------------|
| CC1489 | 8.5" x 11" sheet | .55           |
| CC1476 | 17" x 11" sheet  | <b>\$1.10</b> |

## MICROPROCESSOR CRYSTALS

|           |      |         |      |
|-----------|------|---------|------|
| 1 Mc/s    | 7.95 | 10 Mc/s | 7.95 |
| 2 Mc/s    | 7.95 | 12 Mc/s | 7.95 |
| 4 Mc/s    | 7.95 | 18 Mc/s | 7.95 |
| 4.43 Mc/s | 4.25 | 20 Mc/s | 7.95 |
| 5 Mc/s    | 7.95 |         |      |

## SOCKETS

|               |     |               |        |
|---------------|-----|---------------|--------|
| 8 pin solder  | .25 | 22 pin solder | .80    |
| 14 pin solder | .30 | 24 pin solder | .80    |
| 16 pin solder | .35 | 28 pin solder | .95    |
| 18 pin solder | .45 | 40 pin solder | \$1.00 |

## RISTON COATED PC LAMINATE

One of the most convenient systems for the production of one off or low quantity printed circuit boards. No messy difficult processing just expose, develop and etch. Full instructions supplied with each order.

### SINGLE SIDED FIBREGLASS

|           |        |
|-----------|--------|
| 5" x 6"   | \$2.25 |
| 6" x 10"  | \$4.50 |
| 11" x 12" | \$8.95 |

### DOUBLE SIDED FIBREGLASS

|  |         |
|--|---------|
|  | \$2.95  |
|  | \$5.75  |
|  | \$11.45 |

RISTON DEVELOPER 100 ml concentrate **\$1.20**

### SCOTCHCAL REVERSING FILM

|                               |        |         |
|-------------------------------|--------|---------|
| 10" x 12" sheet               | 8007   | \$3.20  |
| 10" x 12" sheets (pack of 10) |        | \$25.00 |
| 8500 developer                | 100 ml | .90     |



**APPLIED  
TECHNOLOGY  
PTY. LTD.**

POST & PACK COMPONENTS \$1.00


POSTAL ADDRESS: P.O. Box 355, Hornsby, 2077.

SHOWROOM 109-111 Hunter St., Hornsby 2077

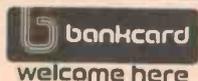
(9-5 Monday to Sat.)

PHONE 476 4758 - 476 3759

PRICES SUBJECT TO CHANGE AFTER AUG. 31st, 1978



# DG 640 SOFTWARE CONTROLLED VDU

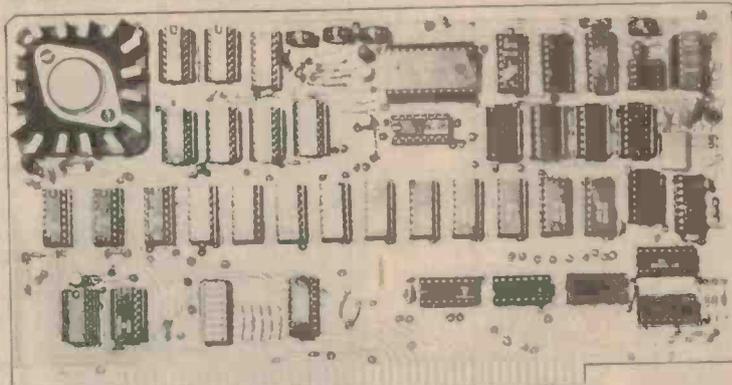

This superb design by David Griffiths and described in **ELECTRONICS TODAY** April, May, and June issues is possibly one of the most useful peripherals you can add to any microprocessor system.

Conforming to the hobby computer standard S100 bus, the DG640 is software controlled to produce

- 16 lines of 64 characters
- Upper and Lower case
- Black on white reversed characters
- Flashing characters
- Chunky graphics
- Direct RAM access

We are pleased to offer our **EXCLUSIVE DG640 OWNERS MANUAL** which expands the original ETI articles and covers such things as; step-by-step assembly, setting up and troubleshooting procedures typical waveforms, address decoding and software examples for use with 2650, 6800, 8080, Z80 microprocessors.

**ATTENTION 2650 USERS:** Ian Binnie has written a special operating system called "BINBUG" which is specifically designed to operate with the DG640 VDU and emulate "PIPBUG" thus ensuring that all software in the 2650 USERS GROUP is fully compatible and no I/O changes need be made. BINBUG is documented in the DG640 users manual and occupies 1K of RAM. Cassette tapes and a preprogrammed 2708 EPROM are available on request.

We are proud of the quality of the DG640 which uses a top grade plated through fibreglass PCB, reflow solder tinned and hard gold plated edge connectors. All components are prime quality and sockets are provided for all RAMS and the character ROM. The DG640 is not a beginners project but will suit even the most demanding microprocessor enthusiast. Each kit is backed by our famous technical support and warranty service (full details with each kit).

|                                        |                           |                                      |                             |
|----------------------------------------|---------------------------|--------------------------------------|-----------------------------|
| <b>DG 640 KIT COMPLETE WITH MANUAL</b> | <b>\$140 (tax paid)</b>   | <b>DG640 PCB with manual</b>         | <b>\$35 (tax paid)</b>      |
|                                        | <b>\$126 (tax exempt)</b> |                                      | <b>\$31.50 (tax exempt)</b> |
| <b>BINBUG CASSETTE FOR 2650</b>        | <b>\$5.00</b>             | <b>BINBUG IN PREPROGRAMMED EPROM</b> | <b>\$25.00</b>              |

## 2650 SYSTEMS

**EA2650 expandable to 4K** as described in E.A. May and using the latest 2114 4K RAMS an ideal beginners project. We supply all parts except case and transformer (suitable cases and transformers available separately).

**E.A. 2650 with all components and 1K RAM** ..... **\$89.50**

### KT9500 FULLY BUFFERED CPU

This popular kit enables you to expand your 2650 system to a fully buffered system with 2 8 bit bidirectional I/O ports, RS232 interface, TTY interface and on board clock.

..... **\$199.00**

## NEW E.A. VIDEO DISPLAY TERMINAL

Described in E.A. Feb/April 1978 this is an ideal serial terminal for microprocessor applications. It is not software controlled like the DG640 and is ideal for beginners who need only a serial interface to the computer.

- KIT 1: VDU LOGIC BOARD** complete with all components, plated through PCB, assembly and troubleshooting manual ..... **\$99.50**
- KIT 2: ENCODER/UART/78UT4** complete kit with all components and instructions but without transformers (see Kit 5 option) ..... **\$39.50**
- KIT 3: KEYBOARD KB04.** A top quality keyboard kit with our own PCB designed to simplify construction and interface directly with the 78UT4 ENCODER ..... **\$59.50**
- KIT 4: MODULATOR** connects video signal to TV Aerial inputs ..... **\$4.50**
- KIT 5: HEAVY DUTY TRANSFORMER** supplies 8V @ 10 Amps + and - 16V at 1 Amp (ideal for later expansion to S100) ..... **\$22.00**
- KIT 6: METALWORK.** For a really professional finish we now have available limited stocks of a timber sided, marviplate/aluminium extrusion keyboard enclosure. This enclosure has adequate room for all kits and is cut out to fit the keyboard. A microprocessor can also fit in the case resulting in a complete home computer ..... **\$49.50**



**POST & PACKAGING** . . . . . **\$2.00** all orders  
**CERTIFIED MAIL** . . . . . **0.50** extra  
**REGISTERED MAIL** . . . . . **2.00** extra

**POSTAL ADDRESS—P.O. Box 311, Hornsby 2077**  
**HEAD OFFICE/SHOWROOM—109/111 Hunter St.,**  
**Hornsby (9.00—5.00, MON. to SAT.)**

**PHONE: (02) 476 4758 General Enquiries — (02) 476 3759 (Technical Information)**  
**PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE**



# ETI PROJECTS

Reprints of many of our most popular projects are available in book form. Top Projects Vols 3 and 4 and our Test Gear book are available from most newsagents or directly from us. Our address is:— Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW. 2011. The Synthesizer book is available only from us and a limited number of specialist suppliers — it is not sold by newsagents.




**TOP PROJECTS VOL 3**  
Published in October 1976. Projects include FM Tuner, 25 Watt Amplifier, Active Crossover, Crossover Amplifier, Booster Amplifier, 50 Watt Power Module, 400 Speaker System, Audio Noise Generator, Dual Beam Adaptor, Tone Burst Generator, Digital Display, ETI Utiliboard, Linear IC Tester. \$2.50 plus 40 cents postage and packing.

**TOP PROJECTS VOL 4**  
Published in June 1977. Projects include Audio Expander/Compressor, 50-100 Watt Amp Modules, Stereo Amplifier, Dynamic Noise Filter, Audio Phaser, Audio Limiter, TV Game, Swimming Pool Alarm, Train Controller, Car 'Scope Testing, Temperature Alarm, Active Antenna, GSR Monitor. \$3.00 plus 40 cents post and packing.


AUDIO EXPANDER COMPRESSOR. 50-100 WATT AMPLIFIER MODULES. AUDIO LIMITER. SELECTA-GAME. AUDIO PHASER. ETI MINI...

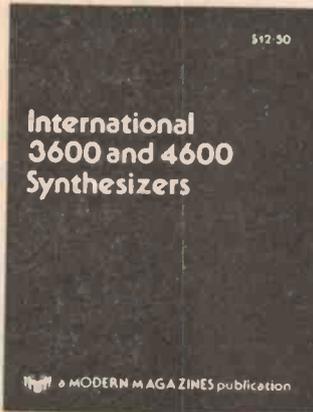**TOP PROJECTS VOL. 4** \$3.00  
...SWIMMING POOL ALARM. TRAIN CONTROLLER. ACTIVE ANTENNA. GSR MONITOR. DYNAMIC NOISE FILTER. SELECTA-GAME. 'SCOPE TEST YOUR CAR. TEMPERATURE METER. UNIVERSAL TIMER. KITS FOR ETI PROJECTS. 50-100 WATT AMPLIFIER MODULES. GENERAL PURPOSE POWER SUPPLY. AUDIO LIMITER. TEMPERATURE ALARM.



**INTERNATIONAL 3600 AND 4600 SYNTHESIZERS**  
A totally revised and updated reprint of ETI's phenomenally successful music synthesizer book. This book has been beautifully printed on heavy art paper and has a sturdy cover varnished for protection. Available only from ETI and some kit set suppliers \$12.50 including postage and packing.

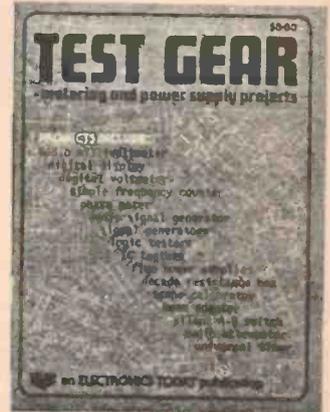**TEST GEAR**  
Published in June 1977. Thirty metering and power supply projects including Audio Level Meter, Impedance Meter, Audio Millivoltmeter, Simple Frequency Counter, Phase Meter, Temperature Meter, Audio Signal Generator, Tone Burst Generator, Cross Hatch/Dot Generator, RF Signal Generator, Logic Probe. \$3.00 plus 40 cents post and packing.



**TWO BYTES ARE BETTER THAN ONE**

## ESSENTIALS OF ANY GOOD MICROCOMPUTER

Before you spend good money on any computer, carefully check the features that it has. IMPACT presents the next instalment about what features to look for, and how the Technico T9916 measures up.

### 1ST REQUIREMENT: A FIRST-CLASS MICROCOMPUTER

The T9916 uses the world-renowned 16-bit TMS9900. (See ETI, March 1978, page 51.)

### 2ND REQUIREMENT: A HIGH-QUALITY CPU BOARD

The T9916 system has the Technico T-9900-SS board, which is a Single-board Stand-alone microcomputer in its own right, and can be expanded to operate as the CPU for a system of minicomputer size and power. (See ETI, April 1978, page 50, and May 1978, page 67) T-1.5K-SS version, \$440 unassembled, \$550 assembled; T-6K-SS version, \$660 and \$770.

### 3RD REQUIREMENT: PLENTY OF RAM MEMORY

This month we give you the good news about


#### THE T99MA MEMORY ADD-ON BOARDS

- Fully socketed 7" x 16" board, with 32K bytes capability.
- Uses Texas Instruments 4051 4K dynamic RAMs.
- Automatic hidden refresh, transparent to the CPU.
- Direct Memory Access (DMA) by CPU.
- Addressable at any 2K page boundary.
- CPU can directly access 64K bytes of memory, and up to 16 Megabytes with memory mapping (and even more, if needed).

Four configurations are offered, each of them available either unassembled (U) or assembled (A).

T99MA-8KB-U \$528    T99MA-16KB-U \$682    T99MA-24KB-U \$836    T99MA-32KB-U \$990  
T99MA-8KB-A \$638    T99MA-16KB-A \$792    T99MA-24KB-A \$946    T99MA-32KB-A \$1100 (plus Sales Tax, if applicable).

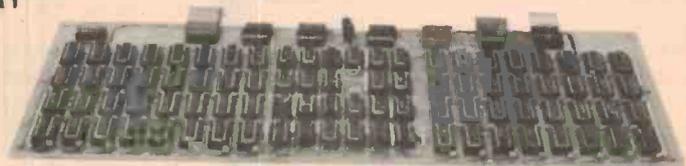The 8K, 16K and 24K boards can be further expanded at any time by plugging in 8K sets of chips, up to the board's full 32K capacity.



Is the T9916 the microcomputer for your home, personal and business needs?

I.M.P.A.C.T. LTD

P.O. Box 177, Petersham, NSW. 2049 (560-7603 AH)

Please send me more details about the T9916.

NAME .....


ADDRESS .....

STATE ..... POSTCODE .....

# PART 11

## ETI's COMPUTER SECTION

# NEWS

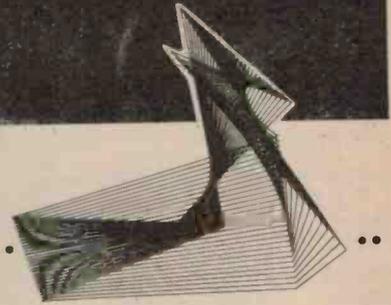

### New Pocket Terminal

The G. R. Electronics Pocket Terminal is a hand-held device capable of sending and receiving data in 8 bit serial ASCII code. It has a 40-key positive tactile response keyboard comprising two single function and 38 multi-function keys which give internal control of the unit and allow transmission of all 128 ASCII codes, with a maximum rate repeat facility.

The terminal has a simultaneous display capacity of eight characters in line on 16-segment 'starburst' LEDs which can generate all 64 ASCII upper case alphanumeric and symbols clearly and legibly.

An internal memory is provided, with capacity for the last 30 characters received. These may be assessed for display in blocks of eight adjacent characters.

Two versions of the Pocket Terminal

are available; interface for operation with 20mA current loop or at V24/RS232 levels. As standard the unit is fitted with an internal 'bleeper' which provides an audible response to reception of the 'BEL' code.

A removable panel on the rear of the unit gives access to a switch set allowing a number of operating options to be selected which include single or dual stop bits, parity and 300/110 Baud transmission rate.

The pocket terminal can be used for microprocessor programming, production data entry, warehousing, mobile data collection, training and education.

The unit operates off a single DC 5 volt supply drawing 450mA.

For further details contact: *The Dindima Group Pty. Ltd. P.O. Box 113, Balwyn, Vic. 3103.*

### COMPUTER CLUB DIRECTORY

**Sydney:** Microcomputer Enthusiasts Group, P.O. Box 3, St. Leonards, 2065. Meets at WIA Hall, 14 Atchison St., St. Leonards on the 1st and 3rd Mondays of the month.

**Melbourne:** Microcomputer Club of Melbourne, meets at the Model Railways Hall, opposite Glen Iris Railway Station on the third Saturday of the month at 2 p.m.

**Canberra:** MICSIG, P.O. Box 118, Mawson, ACT 2607 or contact Peter Harris on 72 2237, Meets at Building 9 of CCAE, 2nd Tuesday of month at 7.30 p.m.

**Newcastle:** contact Peter Moylan, Dept. of Electrical Engineering, University of Newcastle, NSW 2308. (049) 68-5256 (work), (049) 52-3267 (home).

**Brisbane:** contact Norman Wilson, VK4NP, P.O. Box 81, Albion, Queensland, 4010. Tel. 356 6176.

**New England:** New England Computer Club, c/- Union, University of New England, Armidale, NSW 2351. (New club; not restricted to students)

**Auckland:** Auckland Computer Club, P.O. Box 27206, Auckland, N.Z.

Computer clubs are an excellent way of meeting people with the same interests and discovering the kind of problems they've encountered in getting systems 'on the air'. In addition, some clubs run hardware and software courses, and may own some equipment for the use of members. Try one - you'll like it!

If your club is not listed here, please drop us a line, and we'll list you. The same applies if you are interested in starting a club in your area. Also, if established clubs know their programme of forthcoming events, we can publicise them.

**DIODES/ZENERS**

|         |       |              |     |
|---------|-------|--------------|-----|
| 1N914   | 100v  | 10mA         | .05 |
| 1N4005  | 600v  | 1A           | .08 |
| 1N4007  | 1000v | 1A           | .15 |
| 1N4148  | 75v   | 10mA         | .05 |
| 1N4733  | 5.1v  | 1 W Zener    | .25 |
| 1N753A  | 6.2v  | 500 mW Zener | .25 |
| 1N758A  | 10v   | "            | .25 |
| 1N759A  | 12v   | "            | .25 |
| 1N5243  | 13v   | "            | .25 |
| 1N5244B | 14v   | "            | .25 |
| 1N5245B | 15v   | "            | .25 |

**SOCKETS/BRIDGES**

|               |     |              |    |      |
|---------------|-----|--------------|----|------|
| 8-pin         | pcb | .20          | ww | .35  |
| 14-pin        | pcb | .20          | ww | .40  |
| 16-pin        | pcb | .20          | ww | .40  |
| 18-pin        | pcb | .25          | ww | .75  |
| 22-pin        | pcb | .35          | ww | .95  |
| 24-pin        | pcb | .35          | ww | .95  |
| 28-pin        | pcb | .45          | ww | 1.25 |
| 40-pin        | pcb | .50          | ww | 1.25 |
| Molex pins    | .01 | To-3 Sockets |    | .25  |
| 2 Amp Bridge  |     | 100-prv      |    | .95  |
| 25 Amp Bridge |     | 200-prv      |    | 1.95 |

**TRANSISTORS, LEDS, etc.**

|                               |                           |      |
|-------------------------------|---------------------------|------|
| 2N2222                        | NPN (2N2222 Plastic .10)  | .15  |
| 2N2907                        | PNP                       | .15  |
| 2N3906                        | PNP (Plastic - Unmarked)  | .10  |
| 2N3904                        | NPN (Plastic - Unmarked)  | .10  |
| 2N3054                        | NPN                       | .35  |
| 2N3055                        | NPN 15A 60v               | .50  |
| T1P125                        | PNP Darlington            | .35  |
| LED Green, Red, Clear, Yellow |                           | .15  |
| D.L.747                       | 7 seg 5/8" High com-anode | 1.95 |
| MAN72                         | 7 seg com-anode (Red)     | 1.25 |
| MAN3610                       | 7 seg com-anode (Orange)  | 1.25 |
| MAN82A                        | 7 seg com-anode (Yellow)  | 1.25 |
| MAN74A                        | 7 seg com-cathode (Red)   | 1.50 |
| FND359                        | 7 seg com-cathode (Red)   | 1.25 |

**C MOS**

|            |       |
|------------|-------|
| 4000       | .15   |
| 4001       | .15   |
| 4002       | .20   |
| 4004       | 3.95  |
| 4006       | .95   |
| 4007       | .20   |
| 4008       | .75   |
| 4009       | .35   |
| 4010       | .35   |
| 4011       | .20   |
| 4012       | .20   |
| 4013       | .40   |
| 4014       | .75   |
| 4015       | .75   |
| 4016       | .35   |
| 4017       | .75   |
| 4018       | .75   |
| 4019       | .35   |
| 4020       | .85   |
| 4021       | .75   |
| 4022       | .75   |
| 4023       | .20   |
| 4024       | .75   |
| 4025       | .20   |
| 4026       | 1.95  |
| 4027       | .35   |
| 4028       | .75   |
| 4030       | .35   |
| 4033       | 1.50  |
| 4034       | 2.45  |
| 4035       | .75   |
| 4040       | .75   |
| 4041       | .69   |
| 4042       | .65   |
| 4043       | .50   |
| 4044       | .65   |
| 4046       | 1.25  |
| 4049       | .45   |
| 4050       | .45   |
| 4066       | .55   |
| 4069/74C04 | .25   |
| 4071       | .25   |
| 4081       | .30   |
| 4082       | .30   |
| MC 14409   | 14.50 |
| MC 14419   | 4.85  |
| 4511       | .95   |
| 74C151     | 1.90  |

|      |      |
|------|------|
| 7400 | .10  |
| 7401 | .15  |
| 7402 | .15  |
| 7403 | .15  |
| 7404 | .10  |
| 7405 | .25  |
| 7406 | .25  |
| 7407 | .55  |
| 7408 | .15  |
| 7409 | .15  |
| 7410 | .15  |
| 7411 | .25  |
| 7412 | .25  |
| 7413 | .25  |
| 7414 | .75  |
| 7416 | .25  |
| 7417 | .40  |
| 7420 | .15  |
| 7426 | .25  |
| 7427 | .25  |
| 7430 | .15  |
| 7432 | .20  |
| 7437 | .20  |
| 7438 | .20  |
| 7440 | .20  |
| 7441 | 1.15 |
| 7442 | .45  |
| 7443 | .45  |
| 7444 | .45  |
| 7445 | .65  |
| 7446 | .70  |
| 7447 | .70  |
| 7448 | .50  |
| 7450 | .25  |
| 7451 | .25  |
| 7453 | .20  |
| 7454 | .25  |
| 7460 | .40  |
| 7470 | .45  |
| 7472 | .40  |

|       |      |
|-------|------|
| 7473  | .25  |
| 7474  | .30  |
| 7475  | .35  |
| 7476  | .40  |
| 7480  | .55  |
| 7481  | .75  |
| 7483  | .75  |
| 7485  | .55  |
| 7486  | .25  |
| 7489  | 1.05 |
| 7490  | .45  |
| 7491  | .70  |
| 7492  | .45  |
| 7493  | .35  |
| 7494  | .75  |
| 7495  | .60  |
| 7496  | .80  |
| 74100 | 1.15 |
| 74107 | .25  |
| 74121 | .35  |
| 74122 | .55  |
| 74123 | .35  |
| 74125 | .45  |
| 74126 | .35  |
| 74132 | .75  |
| 74141 | .90  |
| 74150 | .85  |
| 74151 | .65  |
| 74153 | .75  |
| 74154 | .95  |
| 74156 | .70  |
| 74157 | .65  |
| 74161 | .55  |
| 74163 | .85  |
| 74164 | .60  |
| 74165 | 1.10 |
| 74166 | 1.25 |
| 74175 | .80  |

**- T T L -**

|        |      |
|--------|------|
| 74176  | .85  |
| 74180  | .55  |
| 74181  | 2.25 |
| 74182  | .75  |
| 74190  | 1.25 |
| 74191  | .95  |
| 74192  | .75  |
| 74193  | .85  |
| 74194  | .95  |
| 74195  | .95  |
| 74196  | .95  |
| 74197  | .95  |
| 74198  | 1.45 |
| 74221  | 1.00 |
| 74367  | .75  |
| 75108A | .35  |
| 75491  | .50  |
| 75492  | .50  |
| 74H00  | .15  |
| 74H01  | .20  |
| 74H04  | .20  |
| 74H05  | .20  |
| 74H08  | .35  |
| 74H10  | .35  |
| 74H11  | .25  |
| 74H15  | .45  |
| 74H20  | .25  |
| 74H21  | .25  |
| 74H22  | .40  |
| 74H30  | .20  |
| 74H40  | .25  |
| 74H50  | .25  |
| 74H51  | .25  |
| 74H52  | .15  |
| 74H53J | .25  |
| 74H55  | .20  |

|        |      |
|--------|------|
| 74H72  | .35  |
| 74H101 | .75  |
| 74H103 | .55  |
| 74H106 | .95  |
| 74L00  | .25  |
| 74L02  | .20  |
| 74L03  | .25  |
| 74L04  | .30  |
| 74L10  | .20  |
| 74L20  | .35  |
| 74L30  | .45  |
| 74L47  | 1.95 |
| 74L51  | .45  |
| 74L55  | .65  |
| 74L72  | .45  |
| 74L73  | .40  |
| 74L74  | .45  |
| 74L75  | .55  |
| 74L93  | .55  |
| 74L123 | .85  |
| 74S00  | .35  |
| 74S02  | .35  |
| 74S03  | .25  |
| 74S04  | .25  |
| 74S05  | .35  |
| 74S08  | .35  |
| 74S10  | .35  |
| 74S11  | .35  |
| 74S20  | .25  |
| 74S40  | .20  |
| 74S50  | .20  |
| 74S51  | .25  |
| 74S64  | .15  |
| 74S74  | .35  |
| 74S112 | .60  |
| 74S114 | .65  |

|               |      |
|---------------|------|
| 74S133        | .40  |
| 74S140        | .55  |
| 74S151        | .30  |
| 74S153        | .35  |
| 74S157        | .75  |
| 74S158        | .30  |
| 74S194        | 1.05 |
| 74S257 (8123) | 1.05 |
| 74LS00        | .20  |
| 74LS01        | .20  |
| 74LS02        | .20  |
| 74LS04        | .20  |
| 74LS05        | .25  |
| 74LS08        | .25  |
| 74LS09        | .25  |
| 74LS10        | .25  |
| 74LS11        | .25  |
| 74LS20        | .20  |
| 74LS21        | .25  |
| 74LS22        | .25  |
| 74LS32        | .25  |
| 74LS37        | .25  |
| 74LS38        | .35  |
| 74LS40        | .30  |
| 74LS42        | .65  |
| 74LS51        | .35  |
| 74LS74        | .35  |
| 74LS86        | .35  |
| 74LS90        | .55  |
| 74LS93        | .55  |
| 74LS107       | .40  |
| 74LS123       | 1.00 |
| 74LS151       | .75  |
| 74LS153       | .75  |
| 74LS157       | .75  |
| 74LS164       | 1.00 |
| 74LS193       | .95  |
| 74LS367       | .75  |
| 74LS368       | .65  |

|                 |      |
|-----------------|------|
| MCT2            | .95  |
| 8038            | 3.95 |
| LM201           | .75  |
| LM301           | .45  |
| LM308 (Mini)    | .95  |
| LM309H          | .65  |
| LM309K (340K-5) | .85  |
| LM310           | .85  |
| LM311D (Mini)   | .75  |
| LM318 (Mini)    | 1.75 |
| LM320K5(7905)   | 1.65 |
| LM320K12        | 1.65 |

**LINEARS, REGULATORS, etc.**

|                   |      |
|-------------------|------|
| LM320T5           | 1.65 |
| LM320T12          | 1.65 |
| LM320T15          | 1.65 |
| LM324N            | 1.25 |
| LM339             | .75  |
| 7805 (340T5)      | .95  |
| LM340T12          | .95  |
| LM340T15          | .95  |
| LM340T18          | .95  |
| LM340T24          | .95  |
| LM340K12          | 1.25 |
| LM340K15          | 1.25 |
| LM340K18          | 1.25 |
| LM340K24          | 1.25 |
| 78L05             | .75  |
| 78L12             | .75  |
| 78L15             | .75  |
| 78M05             | .75  |
| LM373             | 2.95 |
| LM380 (8-14 PIN)  | .95  |
| LM709 (8, 14 PIN) | .25  |
| LM711             | .45  |

|              |      |
|--------------|------|
| LM723        | .40  |
| LM725N       | 2.50 |
| LM739        | 1.50 |
| LM741 (8-14) | .25  |
| LM747        | 1.10 |
| LM1307       | 1.25 |
| LM1458       | .65  |
| LM3900       | .50  |
| LM75451      | .65  |
| NE555        | .35  |
| NE556        | .85  |
| NE565        | .95  |
| NE566        | 1.25 |
| NE567        | .95  |

**9000 SERIES**

|      |     |       |      |
|------|-----|-------|------|
| 9301 | .85 | 95H03 | 1.10 |
| 9309 | .35 | 9601  | .20  |
| 9322 | .65 | 9602  | .45  |

**MICRO'S, RAMS, CPU'S, E-PROMS**

|          |      |         |       |
|----------|------|---------|-------|
| 74S188   | 3.00 | 8214    | 8.95  |
| 1702A    | 4.50 | 8224    | 3.25  |
| MM5314   | 3.00 | 8228    | 6.00  |
| MM5316   | 3.50 | 8251    | 8.50  |
| 2102-1   | 1.45 | 8255    | 10.50 |
| 2102L-1  | 1.75 | 8T13    | 1.50  |
| 2114     | 9.50 | 8T23    | 1.50  |
| TR1602B  | 3.95 | 8T24    | 2.00  |
| TMS 4044 | 9.95 | 8T97    | 1.00  |
|          |      | 2107B-4 | 4.95  |
| 8080     | 8.95 | 2708    | 9.50  |
| 8212     | 2.95 | Z80 PIO | 8.50  |

**INTEGRATED CIRCUITS UNLIMITED**

7889 Clairemont Mesa Blvd., San Diego, CA 92111 U.S.A.  
No Minimum

All prices in U.S. dollars. Please add postage to cover method of shipping. Orders over \$100 (U.S.) will be shipped air no charge. Payment should be submitted with order in U.S. dollars. All IC's Prime/Guaranteed. All orders shipped same day received.

**SPECIAL DISCOUNTS**

| Total Order    | Deduct |
|----------------|--------|
| \$35 - \$99    | 10%    |
| \$100 - \$300  | 15%    |
| \$301 - \$1000 | 20%    |

Phone (714) 278-4394

BarclayCard / Access / American Express / BankAmericard / Visa / MasterCharge

### Remote Controller

A new domestic remote controller from Mountain Hardware Inc. operates by sending 50 kHz control signals over the mains wiring. The Inrol system, which at present operates on 110 V only, has controllers for S100 or Apple II buses, while the power control modules, which plug into mains outlets, can each control two independent 500 W channels. The central controller can turn up to 64 units on or off, and can poll remote units asking for the status of each device.

### 4K CMOS RAM

A new 4K static CMOS RAM, developed by Hitachi, has a standard access time of 43 ns. The gate length on the chip has been shortened from 6 microns to 3 microns, thus halving the parasitic capacitance and doubling the speed.

### Albion Microcomputer Group

A very active group is running in Queensland, with monthly meetings on the second Friday of each month at Windsor State School, Harris Street, Windsor and an attendance of about 60 people at each meeting. The Group is now incorporated as an interest group under the IREE.

Apart from regular monthly meetings a series of ten week courses have been arranged with the Technical and Further Education Department. The second ten week course in the series is now under way; this is split into four groups, two of beginner's standard, one advanced standard and one on microcomputer programming. The courses are attended by just over 100 people.

Note that the phone number for the Group has changed to 356-6176 and the old number is disconnected.

### 9440 for S100

There's a rumour going round that Fairchild are developing a set of three cards for the S100 bus, which will carry a 9440 16-bit processor and 16 Kbytes of memory. As the 9440 (see last month's Printout) executes the instruction set of the Data General Nova minicomputer, this would make available a large amount of software for use in S100-based computers, particularly in business applications.

### Sydney Auction Night

Check right now in your social diary to see if you are free on the evening of Monday, 17 July. If you are, then a trip to the Microcomputer Enthusiasts' Group meeting at the WIA Hall, 14



The Sord M222 is a business model from the M200 series.

Atchison Street, St Leonards, would be well worth your while. Take some money with you, and if you've any spare microcomputer gear that you want to get rid of, take that along also, as the evening's programme is an Auction Night. There's always the chance of a great bargain!

### EPROM/ROM Compatibility

A new booklet from Intel Corp gives information on pin and signal compatibility of their EPROMs and mask-programmed ROMs. The booklet covers the 2758, 2716, and 2732 EPROMs, and the 2332 and 2364 mask-programmed ROMs; it also gives information on address decoding schemes.

Also new from Intel is the latest version of the 8085A, the 8085A-2, which Intel claim to be 'the highest performance 8-bit microcomputer available today'. This 5 MHz version of the 8085A features a 0.8  $\mu$ s instruction cycle yet maintains a memory access time of 350 ns - which is not unduly fast. Further information may be obtained from local Intel distributors, Warburton Franki or A J Ferguson.

### Sord Computers

Several interesting products in the Sord line of microcomputers are now available from Abacus EDP Services of 66-68 Albert Road, South Melbourne, Vic 3205. Sord Computer Systems, Inc. was founded in April 1970 by a group of ex-DEC engineers in Japan, and now boasts a broad line of microcomputers.

Top of that line is the Model 8050, a Z-80 based small business computer which can run RPG II and multi-user BASIC as well as FORTRAN-80. An


impressive range of peripherals is available, including a CRT unit, both hard and floppy disks, a range of printers, cassette and tape drives, card reader, paper tape punch and reader, intelligent keyboard and communications interface. The 8050 is modular in design, using mini-computer style mechanical construction, and utilising LSI for high reliability.

Perhaps of more interest to the hobbyist is the Sord M200 series of Z-80 based microcomputers. These are similar in construction to the Commodore PET, or a SOL with a built-in monitor, and utilise the S100 bus for expansion. Various different models are available, for business, lab or home use, including one with a built-in cash drawer. Both hardware and software are very advanced; for example, two 64 Kbyte memory areas are available, one for system software and the other for user code. Major software for the M200 series is a very advanced extended BASIC; FORTRAN IV will soon be released. As for the Model 8050, a wide range of hardware/peripheral options is available.

A lower-cost system, the M100, is specifically designed for home use. The Z-80 based M100 has 16 Kbytes of RAM as standard and runs an 8K BASIC. It provides a 64 x 24 display on a standard TV set, uses the S100 bus, and incorporates some interesting features such as an audio speaker, journal printer interface, and an 8-bit 2-channel A/D converter with joystick.

Abacus are also agents for Century Computers, and Soroc, whose IQ120 CRT terminal is extremely popular with computer hobbyists in the US. Further information on any of these products is available from Abacus EDP Services.

# Reader Offer — MIDEX SYSTEM 55

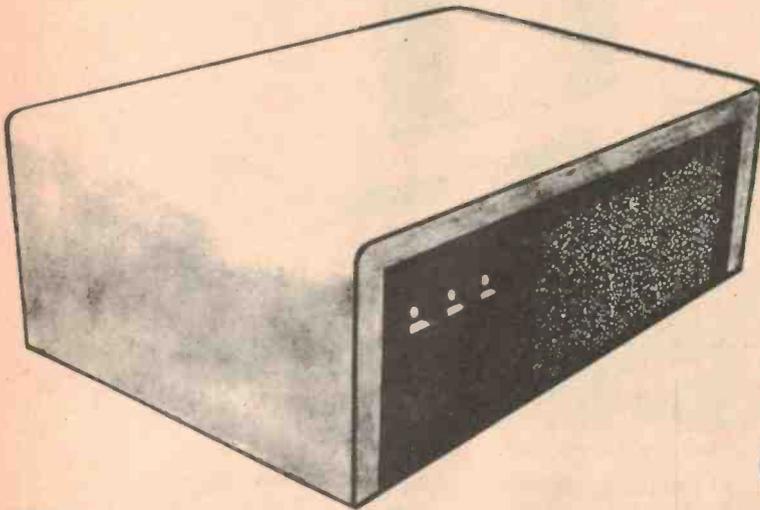

## SPECIFICATIONS:

**OPEN SPACE RANGE:** (main axis) 50 foot maximum  
**RANGE CONTROL:** Single turn potentiometer. Range adjustment from zero to full.  
**SENSITIVITY:** 1-2 steps within set range. Self-adjusting for constant (background) motion.  
**PROTECTION PATTERN:** Single lobe 50 foot maximum length, 20 foot maximum width.  
**EXIT TIMER:** 30 seconds  
**ENTRY TIMER:** 20 seconds  
**RECHARGEABLE STANDBY BATTERY:** 4 hours standby  
**POWER CONSUMPTION:** 8W maximum  
**ALARM CYCLE TIMER:** 1 minute  
**SIREN ALARM:** (Active during alarm cycle) 5W into 8 ohm speaker (or into any combination of speakers not resulting in less than 4 ohms)  
**AUXILIARY SENSOR INPUTS:** Normally closed contact  
**ELECTRONIC KEY SWITCH:** OFF (Test light active for walk test purposes). ON (timers activated. Until operational).

Until recent times intruder alarm systems were generally designed to sound an alarm if one or more external doors or windows were opened.

Such systems offer adequate protection for homes and offices with few external entry points but are less than adequate where there are large door or window areas. Installation can also be a major and costly business often involving hundreds of metres of easily damaged cable and a large number of switches and connections.

Because of this there is a growing trend toward self-contained systems which detect the movement of an intruder. The best of these use microwave energy: a Gunn diode projects a very high frequency (10.5 GHz) stable pear-drop shaped radiation pattern into the area to be protected.


Objects within the radiation area partially reflect the energy to the transceiver. If all objects within range are stationary the reflected waves will be at the original transmitted frequency. If they strike a moving object the movement will cause a (Doppler) frequency shift and the waves return at a slightly higher or lower frequency. The transmitted and received frequencies are compared and any difference is amplified and used to trip the alarm.

The radiation pattern is almost impossible for an intruder to detect and is not affected by air currents, noise, light, sound, temperature or humidity.

Maximum detection range is approximately 15 metres — controls are provided to reduce sensitivity if required.

The Midex unit contains a powerful amplifier siren circuit which should be used in conjunction with the blast horn type speaker specified.

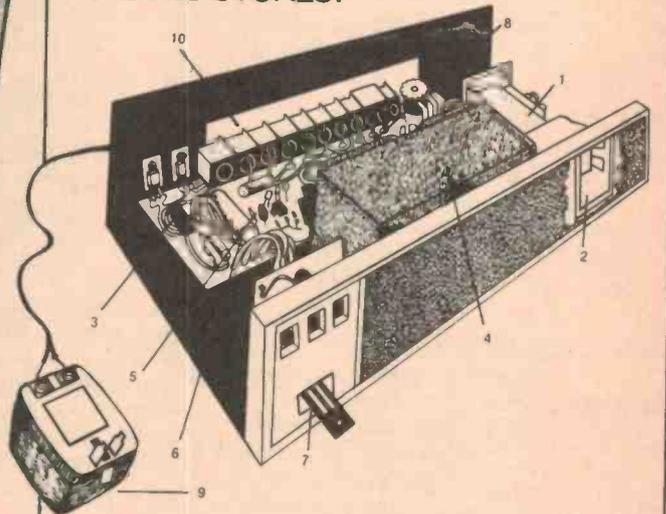FOR USE IN HOMES,  
MEDICAL/DENTAL OFFICES, SMALL  
RETAIL STORES.



1. Gunn diode transceiver
2. Antenna
3. Process electronics
4. Four-hour standby battery (rechargeable)
5. Timing circuits
6. Automatic reset
7. Coded electronic switching
8. Sweep siren and amplifier
9. Stepdown transformer adaptor (to Aust. pattern)
10. Inputs for additional external circuits.

The blast horn supplied (or equivalent) has such volume and penetration as to cause pain within 15 seconds of exposure. It is almost impossible for an intruder to stay within the area.

The Midex unit is 'armed' and 'disarmed' by a special coded electronic key. An inbuilt timing circuit allows 30 seconds to leave the building and 20 seconds to re-enter before the alarm is activated.

Also included as standard are connections for additional external closed loop circuitry (i.e. door and window sensors) and 'panic switches'.


The Caldor Corporation Pty Ltd has arranged to offer these units directly to our readers at \$299.95 (plus \$5 postage and handling). The recommended heavy duty blast horns are also offered at \$49.95 each (plus \$5.00 each post and packing). For total protection two such horns should be used. A lighter version is also available for \$29.95, (plus \$5.00 post and packing). This version is adequate for protecting small areas.

This magazine has inspected and tested the products offered and can thoroughly recommend them. They are properly engineered intruder alarms from one of the USA's leading and most respected manufacturers in this field (Midex Corp, Mountain View, Calif.).


**NOTE:** This offer is made by the Caldor Corporation, and this magazine is acting as a clearing office for orders only. Cheques should be made out to 'Midex Offer' and sent together with the order form to 'Midex Offer' Electronics Today International, 15 Boundary St, Rushcutters Bay, NSW 2011.

ETI will process orders and send them on to Caldor who will then send out the goods by certified mail. Please allow approximately four weeks for delivery.
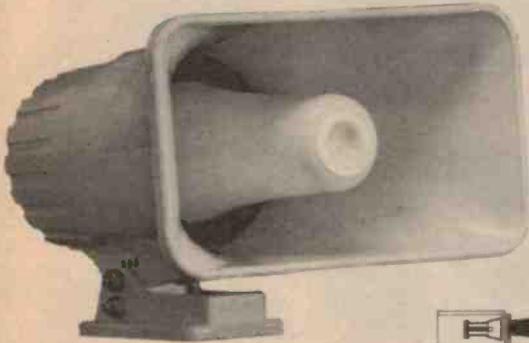
# PROFESSIONAL GRADE MICROWAVE LOCAL ALARM INTRUSION DETECTION SYSTEM



RADIATION  
PATTERN

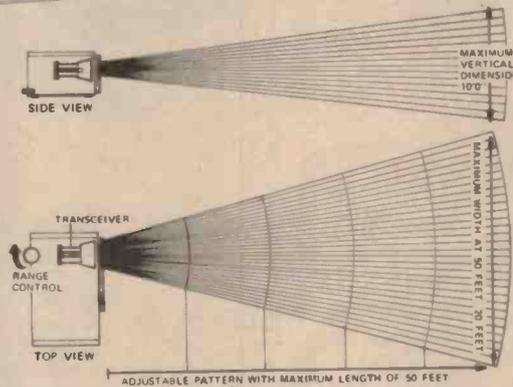

**FEATURES:**

- Microwave transceiver.
- Processing and signalling electronics.
- Precision die cast antenna.
- Four-hour rechargeable standby battery.
- Timing circuits permitting exit and entry.
- Automatic alarm reset.
- On-Off switching with coded electronic key.
- Fast sweep siren for connection to horn type 8 ohm speakers.
- Inputs for easy connection of external sensors such as door and window contacts, panic switches, smoke detectors.

EVERY MIDEX UNIT IS TESTED FOR 500 HOURS  
BEFORE SHIPPING FROM THE PARENT PLANT!

## MIDEX OFFER

Electronics Today International,  
15 Boundary St, Rushcutters Bay, NSW. 2011.

Please Supply:

Quantity

- Midex Control Unit at \$299.95 \$.....
- Large Blast Horn/s at \$49.95 each \$.....
- Small Blast Horn/s at \$29.95 each \$.....

Postage and packing \$5 per unit \$.....

Total \$.....

Name.....

Address.....

P/Code.....

Please make cheques/postal note payable to 'Midex Offer'.

Offer closes September 21st, 1978.

End noise  
and cross-talk  
with our  
exclusive  
Noiseguard™  
system

**Capacity:** 20 positions for edge connectors.  
**Edge Connectors:** S-100 type, 25" spacing.  
**Shielding:** Every signal fully shielded by both interconnected ground lines.  
**Termination:** Active termination of each line. Termination network includes LM201 op amp, 2N3904, 2N3906, TIP29 and TIP30 transistors, 2.4 volts, 180 ohms.

# The Wunder Buss™

A product of Morrow's  
Micro-Stuff for

## COMPUTER BITS

A DIVISION OF AUTOMATION  
STATHAM PTY. LTD.

47 Birch Street, BANKSTOWN  
N.S.W. 2200  
Phone (02) 709-4144  
Telex AA26770

NEW FROM JAPAN

**SORD**

# M100 PERSONAL COMPUTER



## SPECIFICATIONS:

### CPU

Using a Z-80 microcomputer chip.

### ROM

Up to 8K bytes capacity.

### RAM

16K bytes (M110) or 32K bytes (M120).

### KEYBOARD

Full ASCII keyboard and 20- BASIC command keys.

### CONTROLLERS

Audio cassette 2-channel. CRT monitor controller.

### INTERFACES

Modern Interface (RS232C) with edge connector. 8-bit digital input output. Journal printer interface. 8-bit 2-channel AD converter and joystick.

### SPEAKER

2 octave output speaker.

### S100

Bus signal edge connector.

### CLOCK

Provided.

### OPTIONAL UNITS

- Power Supply: Input 230 V 50 Hz, output 5 V, 4 A and 12 V, 0.5 A for M100 CPU.
- Colour graphic (256 x 192 dots) display controller.
- Black & white TV monitor (24 lines of 64 characters).
- SNO100 Bus extension cabinet.
- 8 outlet power control box.

## THE M200 SERIES FAMILY



• M220 Standard Model with optional dual mini-floppy disk drive.

• M230 Laboratory Model and printer.

• M252 Cash Register Model.

• M270 TSS Model, coupler and printer.

Z-80 on S-100: In the low price system range, SORD introduces a versatile computer... fully packed four key components and powerful software... Z-80 CPU on S-100 bus, CRT monitor display, mini floppy diskette and discharged-type printer... High speed extended BASIC for data processing. It's SORD SMALL BUSINESS COMPUTER M220.

## SPECIFICATIONS:

CPU: Using a Z-80 microcomputer chip.

ROM: Mask programmable variety.

RAM: 48K bytes capacity. Accessed by Z-80 through CRT display priority.

MINI FLOPPY DISKETTE: Compact in size, 5-inch diskette with 35-track, 71.5K bytes format capacity. Each track is of 8 sectors with 256 bytes, 125K bit per second and 300 RPM. Standard floppies available on Model M230.

KEYBOARD: Easy-to-operate, multi-purpose, intelligent-type 124-key system, 26 designated keys with four commands for frequently used characters in BASIC. Four mode and five shift keys. LEDs prevent operational errors. Normal-Reverse mode. Special keyboard arrangements available on request.

CRT DISPLAY: Built-in 12-inch flat face braun tube. 24 lines of 80 characters. 186 different alphanumeric and signals for a total of 1920 characters by means of dot matrix. Normal-Reverse mode. Graphics on a character-by-character base.

PRINTER: Built-in Discharged type. Max 2 lines of 40 characters per second. All 1920 characters in BASIC. I/O SERIAL PORT: 2 RS 232C serial ports for MODEM, Teletype, and a switch selectable additional audio cassette interface.

SOFTWARE: SORD Extended BASIC Plus. OPTIONAL UNITS: A to D, D to A converters, high speed line printer, D/D/O, IEEE 488 Interface Bus (HP-IB) MOD-EM. Typewriter keyboard on M222.

All models have powerful software available, SORD extended basic, and Fortran 1V, commercial accounting, word processing and property management systems.

Australian Distributors:

**ABACUS EDP SERVICES Pty. Ltd.**

66-68 Albert Road,  
Sth. Melbourne. Victoria. 3205.

Tel (03) 699-8555

and at

2 O'Connell Street,  
Sydney, NSW. 2000.

Tel (02) 232-8899.

To: ABACUS EDP SERVICES 66-68 Albert Rd, Sth. Melbourne. Vic. 3205.

We are interested in:

- A Dealership.
- Additional Information.
- Buying a SORD Series Computer.

Please contact:

M .....

.....

.....

..... P/Code .....

# 8080 Educational/Prototyping Interface

This paper by Dr Paul F Goldsbrough, of Canberra College of Advanced Education, describes an interface board for the 8080 which allows debugging of both software and hardware. It also allows educational experiments based on the 'Bugbooks'.

FOR THE ELECTRONIC ENGINEER, technician or OEM'er working in his small to medium scale electronics laboratory, the college or university professor wanting to effectively teach microcomputers, or for the hobbyist who would like a cheap flexible microcomputer system, the present microcomputer market presents some real problems. Two of the major problems for the user are which microprocessor (8080A, 6800, 2650, SC/MP etc.) to use?; and what type of development system or evaluation kit to commence with? A further problem relates to the required background knowledge. Since an understanding of assembly language programming and microcomputer interfacing is necessary to use microcomputers, the evaluation or development kit chosen should, ideally, be suitable for easily leading the user through these fundamentals before going on to more advanced experimental work. In other words, the user should be able to learn the fundamentals with his development system before going on to more advanced experiments and prototyping work.

The problem with the microcomputer market at the moment, however, is that there is really no product which is useful as *both* an educational microcomputer and also as a prototyping/development system. On the one hand, several teaching microcomputers of varying effectiveness and cost are available. These include the Intel Prompt 80 system, E & L Instruments' Mini Micro Designer (MMD-1) and Bug Books, and the ISIAS Company's "Computer in a Book". These educational systems are usually characterised by built-in educational interfaces in the form of key boards, LED displays, etc., which are so necessary for teaching microcomputer principles. Because of their

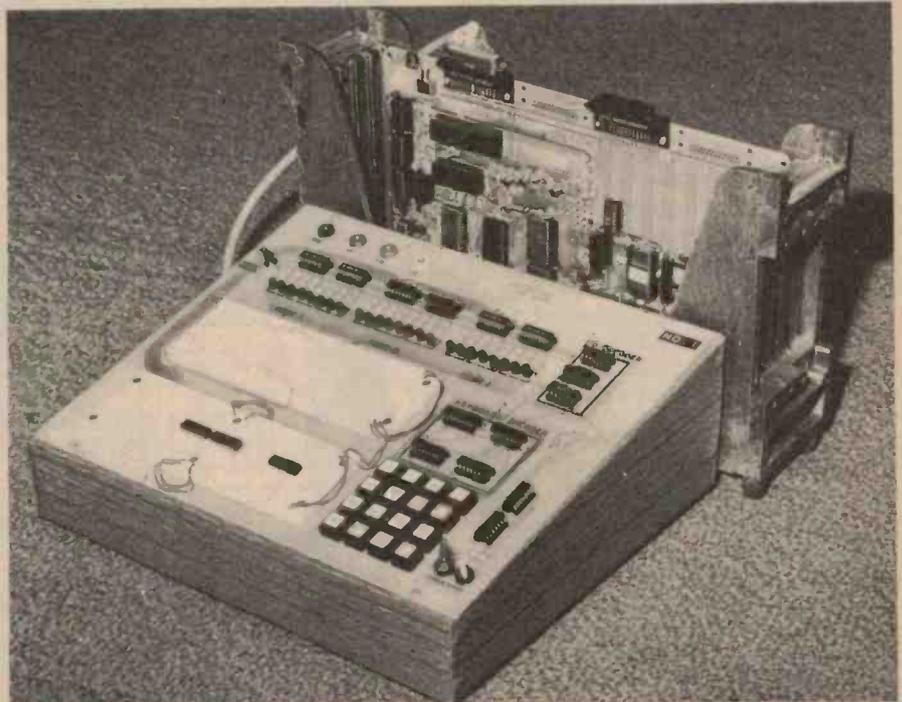


Fig.1. A prototype of the educational/prototyping microcomputer. The SKD-80 (at rear) is connected to the MMD-1 educational interface via the 43 pin P-1 edge connector and the 25 pin J-1 edge connector.

built-in educational interfaces. These systems are usually unsuitable both physically and functionally as software and hardware prototyping/development systems. On the other hand, systems which are designed specifically for prototyping/development work are available and some of these have been described in this magazine. These systems range in complexity and cost from small evaluation kits through to the large effective, but expensive, microcomputer development systems. These, in general, are unsatisfactory for direct use as educational microcomputers because they lack an educational interface and effective teaching literature.

The educational/prototyping microcomputer described in this article was designed by the author to provide an instrument which is useful as both an educational microcomputer, and as a prototyping/development system. The development work was carried out at the Virginia Polytechnic Institute and State University with Dr. Peter Rony, Mr. David Larsen, and Mr. John Titus, the authors of the popular Bug Book Series. The prototype system which was developed is shown in Figure 1. The educational interface used in this system is that of the Mini Micro Designer microcomputer for which two educational, self-teaching books<sup>(1)</sup> on digital electronics and

# Project 634

8080A programming and interfacing had already been written. This material has been tested with students and professional groups and found to be extremely effective for teaching microcomputer fundamentals. (4) Hence, because of this and the popularity of the Intel 8080A microprocessor in the U.S.A., the educational interface of the MMD-1 was retained and interfaced to the commercially available Intel SDK-80 prototyping microcomputer.

The system then can be used initially for educational and/or self teaching work. Assembly language programming is facilitated by key board data entry, which provides rapid data entry while still allowing the user to maintain close contact with the microcomputer. The SK-10 solderless bread-boarding socket which contains the data, address, control lines and 24 PPI lines, facilitates interfacing experiments which can be done in conjunction with Bug Books 5 and 6. In addition, hardware single step (single machine cycle) facilities, and a bus monitor are included in the educational interface as additional self-teaching aids. Keyboard data and command entry are controlled by a small monitor program known as KEX — the keyboard executive program.

For prototyping and advanced experimental work, the SDK-80 has facilities for teletype and VDU data entry, vectored interrupts, parallel data entry and I/O device configuration under program control via the 8255 programmable peripheral interface. During prototype system development, software and hardware system aids are necessary for program and system debugging. These aids can be 'added to' a stand alone prototype microcomputer system as is done for example, with the Intel In Circuit Emulator (ICE) and microcomputer development system. As a cheaper alternative, an effective software development aid, D-BUG, which was written by Dr. Chris Titus, of Tychon, Inc., Blacksburg, Virginia, has been incorporated in the system to be described, as an integral part of what is effectively the final stand alone microcomputer. In addition to the usual teletype monitor facilities for manual program entry, memory examination and program initiation, D-BUG has facilities for inputting and outputting programs to paper tape, thus avoiding the need for time consuming repetitive hand entry of programs; as well as a most effective break point and single-step feature for program debugging. The advantage of this 1K program is that when a break point is set and hit during program execution, the contents of

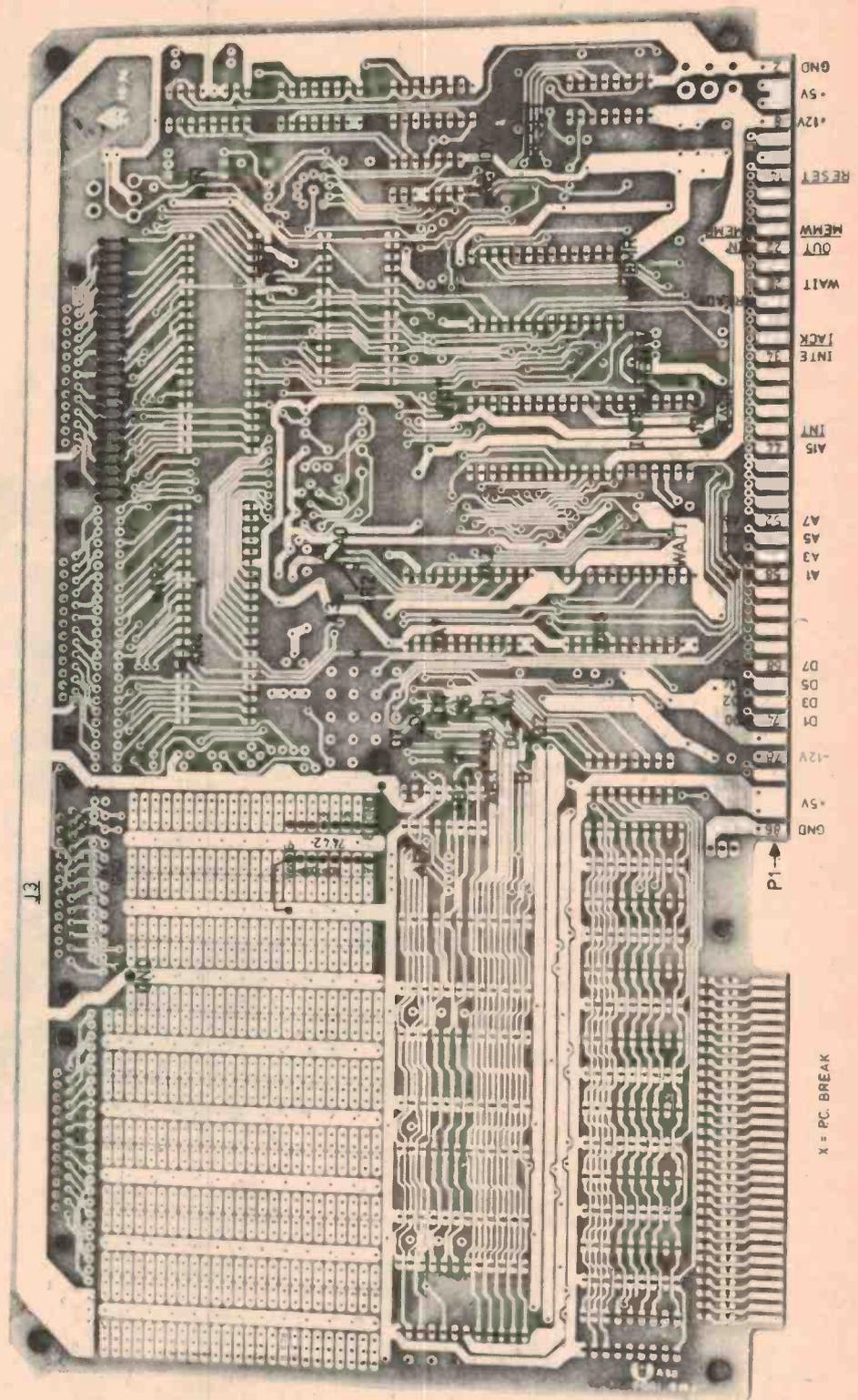


Fig.2. The rear of the SDK-80 PCB board showing the P-1 edge connector pin assignments. The positions from which the address, data and control signals are to be wired to P-1 are indicated with dots.

registers A, B, C, D, E, H, and L, the contents of the memory location addressed by register pair H, the stack pointer and the last two entries on the stack are automatically printed out, avoiding the need for manual exam-

ination. The program may then be single stepped (by pressing the S key) and at each step, all the above data is output, allowing full examination of program execution. Alternatively, another break point may be set and program execution

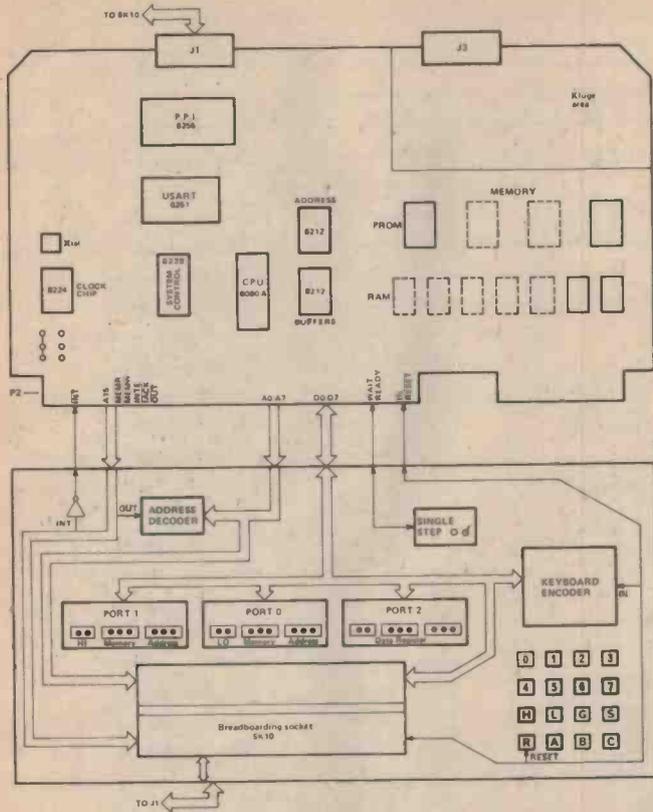


Fig.3. Block diagram of the Educational/Prototyping microcomputer showing the SDK-80 (top) and educational interface (bottom).

moderate cost (\$286 plus tax — the cheapest in the Intel range), and the simplicity and generality of its layout. The kit is supplied with a 1K EPROM or ROM for the system monitor, a spare 1K EPROM, 256 words of RAM, and a PPI and USART making it excellent value. Also supplied is a users guide (2), which provides clear directions for construction and check-out of the microcomputer. I estimate construction time at 4-5 hours. The jumper wiring of optional features is summarised in Table 2.

The SDK-80 board is physically compatible with the Intel MDS system and so has two base edge connectors P-1 and P-2. On other Intel systems, the address, data and control signals are brought down to the P-1 edge connector. However, this is not done on the SDK-80 although plated-through holes are provided at each edge connector pin to permit user wiring. Hence, once you have assembled the SDK-80 (and verified that it is operating using the supplied system monitor and a teletype if one is available), the next step is to bring the address lines (A0-A7, A15), data lines (D0-D7) and control signals (IN, OUT, MEMR, MEMW, INT, INTE,

continued. These features of DBUG are illustrated in Table 1.

Hardware debugging is aided by the hardware single step circuit, and the easy availability of the data, address, and control lines at the SK-10 socket for monitoring. Once the software and hardware for the stand alone application have been developed and tested, an identical system is constructed omitting the educational interface, KEX and DBUG. A PROM, which contains the program developed in RAM and which has been tested in the educational/prototyping microcomputer to run at the origin, is used to drive the new stand alone system. Program initiation is then by a system reset.

The system described here was used by the author in England during April, May, and June of 1977 for the development of a stand alone data logger for a natural gamma spectrometer. It was found to be most effective indeed for programs up to several hundred bytes. With memory expansion, a 6K resident editor-assembler can also be added to further speed the development cycle.

### The SDK-80 Prototyping Microcomputer

The SDK-80 was chosen as the prototyping microcomputer because of its

TABLE 1

TYCHON EDITOR-ASSEMBLER V-2

PAGE 01-001

/THIS PROGRAM IS USED TO ILLUSTRATE THE FEATURES  
/OF PROGRAM "DEUG"

```

*020 000
020 000 061    LXISP
020 001 000    000
020 002 024    024
020 003 001    LXIB
020 004 001    001
020 005 002    002
020 006 021    LXID
020 007 003    003
020 010 004    004
020 011 306    LOOP, ADI
020 012 004    004
020 013 003    INXB
020 014 303    JMP
020 015 011    LOOP
020 016 020    0

020 003 B
020 000 G
020 003
SZ I P 2 A B C D E H L M SP CS
01000110 000 002 001 000 000 000 000 303 024 000 377 377

S 020 006
01000110 000 002 001 004 003 000 000 303 024 000 377 377

S 020 011
00000010 004 002 001 004 003 000 000 303 024 000 377 377

S 020 013
00000010 004 002 002 004 003 000 000 303 024 000 377 377

020 011 B
C
020 011
00000010 010 002 002 004 003 000 000 303 024 000 377 377

```

Software diagnostic provided by DBUG for the above program.

# Project 634

(ACK, WAIT and READY) down to the P-1 edge connector. Figure 2 shows the SDK-80 PCB board layout, P-1 edge connector pin assignments and the positions on the board from which the address, data and control lines are wired down to P-1. To provide buffering and line drive for the address data and control lines, all lines are wired to the edge connector from the I/O side of the 8212's and the 8228 system controller.

## Educational Interface

The MMD-1 educational interface was modularised and wired to the SDK-80 via a 43 pin socket which matches the SDK-80 P-1 edge connector. Figure 3 is a functional block diagram of the assembled microcomputer showing the data, control and address lines paths. Figure 4 shows a circuit diagram of the educational interface. The construction of this circuit should not present any problems. The operation of the major part of the circuit was described in the May to July, 1976 issues of *Radio Electronics*. The main circuit features, however, can be summarised as follows:

- Data/command entry is via key switches and two 74148 priority encoders. The 74148's, together with 4 NAND gates and the EO output of the second 74148 are used to generate a 5 bit coded word which is buffered on to the data bus lines D0-D3 and D7 via an 8095 tri-state buffer.
- Debouncing of the KEY switches is done by software.
- Three 8 bit LED displays (O/P ports 0-2) are wired to the data bus using 7475 latches and LED's.
- Device select, latching pulses for O/P ports 0-2 are generated by uniquely decoding the device codes  $000_8$ ,  $001_8$  and  $002_8$  using a 74L42 and five inverters, and NOR'ing the resulting device select pulses with OUT.
- *Hardware single stepping* is achieved by raising the READY line of the 8224 clock chip on the SDK-80 using a 7474 flip flop which is then reset  $\approx 500$  ns later by the 8080 'WAIT' line going "low". The single step clocking pulse to the 7474 is optionally provided by either a debounced press button switch or an external single stepping clock.
- During normal operation of the MMD-1 educational interface, output port 1 is used to display the high memory address byte (A8-A15). Since this byte rarely if ever changes during teaching, port 1 has been used as a *bus monitor* by tying the enable inputs (pins 4 and 13) of the 7475's

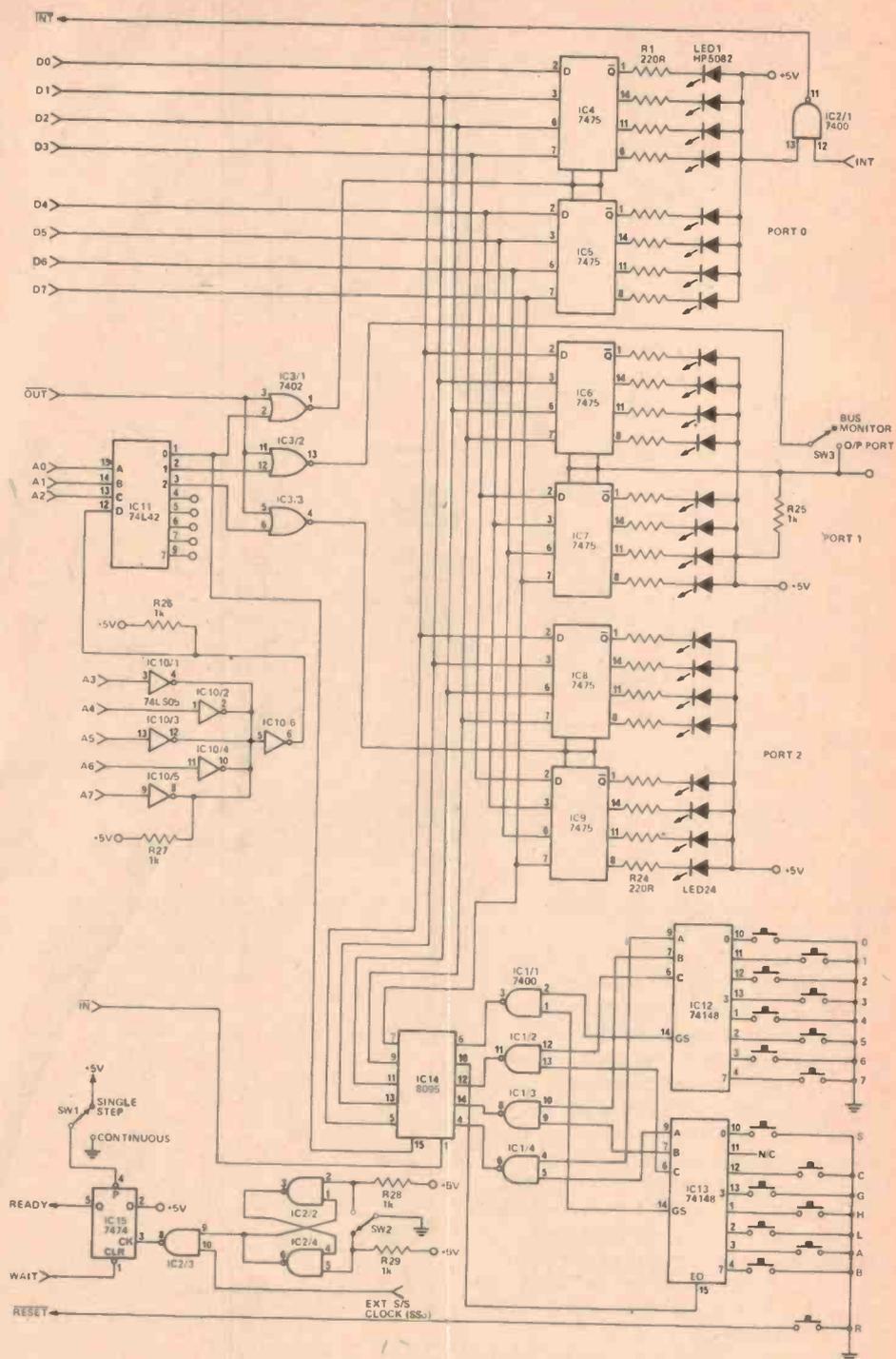


Fig.4. Educational interface circuit diagram.

to a logic one through a single-pole, single-throw switch. With the enable inputs at 'one' (switch closed), the outputs of the 7475's follow their inputs and the Port acts as a bus monitor. With the enable input lines 'low' (switch open), data is latched.

- An active low signal ( $\overline{\text{INT}}$ ) is required by the SDK-80 for interrupts. However, as the chapters on interrupts in Bugbook 6 uses an active high signal INT, an inverter has been used in the interface to invert INT for input to the SDK-80.

## Software Control and Device Code Considerations

Referring to Figure 5 which shows a memory map of the SDK-80, it can be seen that the first 4K words of memory are allocated in 1K blocks to ROM or EPROM. The fifth 1K block of memory is allocated to RAM in 4, 256 word segments. Since the kit supplied, resident, SDK-80 monitor required the top 30 words of RAM for stack and temporary storage, the 256 words of RAM supplied with the kit were located at address  $023_8 000_8$ .

The educational interface is controlled by a keyboard executive program, called KEX. This must reside in the first 256 words of ROM commencing at address  $000_8 000_8$  so that a reset key operation always transfers control of the microcomputer to KEX. Because of the SDK-80 ROM memory allocation arrangement, a 1K EPROM must be used to store the program.

A major feature of KEX operation is that it spends most of its time polling Port 0 (the keyboard) in search of user, key entered commands. Hence, it is important to ensure that the Port 0 device code ( $000_8$ ) and the other educational interface device codes ( $001_8$ ,  $002_8$ ) do not address any or all of the on-board SDK-80 I/O devices. Two important factors concerning SDK-80 electronics must be considered, viz.,

- non-unique, single bit or linear decoding is used to generate device enable pulses for the PPI's and USART and;
- the chip enables for the PPI and USART are *active low*.

Figure 6 shows the combined PPI and USART device code format. Because of the above factors, there is considerable SDK-80 device code redundancy. The educational interface device codes ( $000_8$  through  $002_8$ ) represent in fact, the worst case condition in which both PPI's and the USART are *simultaneously* enabled. Clearly, this situation would lead to excessive loading of all the I/O devices. However, the educational interface device codes must be retained as they are used throughout Bugbook 6. Hence, to ensure satisfactory computer operation, either the PPI and USART must be removed from the SDK-80 or their device codes must be changed and/or uniquely decoded. For initial system checkout described below, I suggest that you simply remove the USART and PPI. A permanent solution is presented later.

TABLE 2  
SDK-80 Jumper Wiring

| Function                                    | Action                                                                                  |
|---------------------------------------------|-----------------------------------------------------------------------------------------|
| To disable "HOLD"                           | J5-2 to J5-3                                                                            |
| To connect 8224 & 8080A "READY" lines       | J5-7 to J5-8                                                                            |
| To permanently "ENABLE" bus lines           | J5-4 to J5-5                                                                            |
| For 110 Baud                                | PADS 29 to 37, 4 to 5                                                                   |
| For Teletype "20 mA current loop" operation | PADS 1 to 2, 7 to 8, 10 to 11, 13 to 14, 15 to 16, 18 to 19, 21 to 22, 23 to 26, A to B |

Next month we shall conclude this project with full constructional details and application information. Owing to space limitations, we are unable to provide printed circuit board drawings for this project, but boards will be available from the usual suppliers (e.g. RCS Radio, Applied Technology, etc.). If you wish to make your own, positives or negatives (please state which) are available from Nebula Electronics, 15 Boundary Street, Rushcutters Bay, NSW 2011, for \$6 per set.

For similar reasons, it is impossible for us to include listings of the Keyboard Executive Program, KEX or tape dump program HTAPE in the magazine. However, photocopies of the listings with some documentation are available directly from ETI at a charge of \$2.50 to cover costs.

Concluded next month

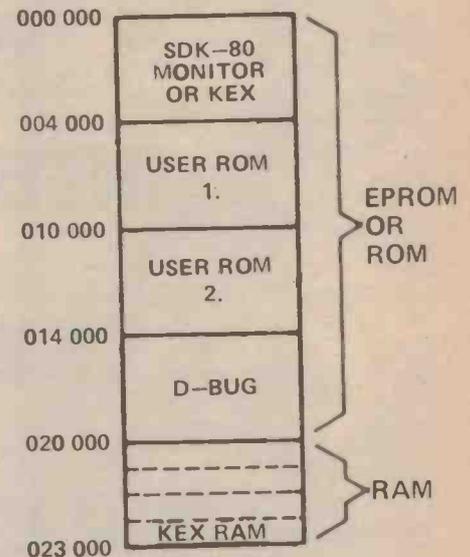


Fig. 5. SDK-80 memory map.

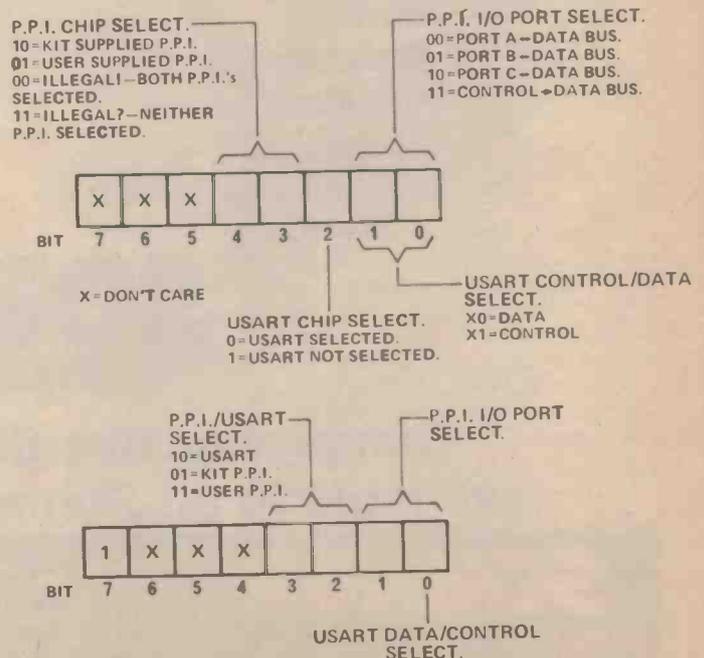


Fig. 6. SDK-80 combined PPI and USART device code format.

# FROM 1st JULY 1978 SOANAR

Appointed Distributor for  
Philips and Signetics

**INTEGRATED CIRCUITS  
AND  
SEMICONDUCTORS**



**PHILIPS**

Diodes  
Transistors  
Rectifiers  
Analog I.C.'s  
LOC MOS I.C.'s

**Signetics**

Analog I.C.'s  
Logic I.C.'s  
Memories  
Interface I.C.'s  
Microprocessors

**SOANAR**

Comprehensive Stocks will be readily  
available in all States throughout Australia.

**SOANAR SOANAR ELECTRONICS PTY. LTD.**

30 Lexton Road, Box Hill, Vic., 3128, Australia. Tel: 89 0661 Telex: 32286.

N.S.W.  
4 Close St.,  
Canterbury, 2193  
Tel.: 78 0281

S.A.  
286 Gilbert St.,  
Adelaide, 5000  
Tel.: 51 6981

W.A.  
17 Northwood St.,  
W. Leederville, 6007  
Tel.: 81 5500

QLD.  
71 Doggett St.,  
Fortitude Valley 4006  
Tel.: 52 5421

CONTINENTAL SPECIALTIES CORPORATION

# MAX-100

## 100 MHz 8-digit counter

- 20 Hz to 100 MHz (guaranteed)
- Accuracy:  $\pm 1$  count + Time base error.
- Input impedance: 1 M ohm shunted by 56 pF.
- 0.6" high LED display, lead-zero blanking.
- Battery operated with low battery indicator.
- Size: 4.5 x 14.2 x 19.7 cm.
- Weight: 680 gm with battery.



**EX-STOCK**  
\$180 + Sales Tax



**GENERAL ELECTRONIC SERVICES PTY. LTD.**  
99 Alexander Street, Crows Nest, NSW. 2065.  
Phone: 439-2488, 439-2399. Cables: SERVO SYDNEY.  
Telex: 25486 A/B SERVO.

Adelaide: 42-6651  
Canberra: 95-9138, 82-3581  
Brisbane: 277-4311  
Melbourne: 598-9207  
Newcastle: 69-1625  
Perth: 325-5722

## LOW COST EPROM PROGRAMMER — Model M103

**Kit \$99**  
**Assembled \$124**

**P&P Included**

A good investment for computer and microcomputer users.

Often-used subroutines, assemblers, diagnostics and control software can now be economically and reliably stored in EPROMs.

### Features:

- Programs and reads 8K, 16K and 32K EPROMs: 2708, 2704, 2758, 2716, 2732, TMS2716, TMS2516 and TMS2532.
- Conforms to EPROM manufacturer's programming specifications.
- Easy and non-critical interfacing to computer TTL-compatible, latch-type, programmable parallel I/O ports.
- Compatible with most microcomputer kits on the market.
- Programming is controlled by computer-based Control Program.
- A detailed flow diagram of the Control Program is provided which the user translates into his machine or assembler language.

- Control Program listing applicable to M6800-based systems is provided free with the M103 if requested.
- 4.5" x 6.5" PCB mates with 22 x 2, 0.156" edge connector.

**Also available:** mating edge connector — \$4, and Control Program EPROM pluggable into 6800D2 kit.

**MICROCONTROL**  
P.O. Box 361  
BROADWAY  
NSW. 2007.

# THE COMPLETE COMPUTER \$525.00

*that does more than teach*

This remarkable microcomputer is for anyone who wants to learn more about computers. The UC1800 is a complete training package — an assembled and tested CMOS computer, users manual and software. Everything you'll need to learn and apply, a small S-100 bus expandable computer.

**DATA AIDS** 100a West St Crows Nest, N.S.W. 2065. (02) 922-6833.



Please send descriptive brochure.

Name .....

Address .....

ET

# propagation a closer look

Roger Harrison concludes, in part III, his introductory essay on radio propagation and explores the inner meaning of those prediction curves.

LONG DISTANCE propagation on the HF bands is not all by means of multi-hop reflections between the ionosphere and the earth. Considerable distance can be covered, or paths not supposed to be 'open' can be worked — often well beyond the MUF — by means of a variety of "anomalous propagation" modes.

The ionosphere is not an homogeneous medium. The cream is not mixed in with the milk, so to speak. It is a curious mixture of 'thick' patches and 'thin' patches, bulges and tilts — all the time on the move under the influence of a variety of forces. Some of which have already been explained.

## "Chordal Hop" Propagation

The base of the ionosphere is not 'flat', nor parallel to the earth's surface in many places. This characteristic gives rise to 'tilts' in the base of the ionosphere which can be exploited to provide multiple reflections from the ionosphere *without intermediate ground reflections*.

This is now commonly referred to as "chordal hop" propagation. The concept is illustrated in Figure 12.

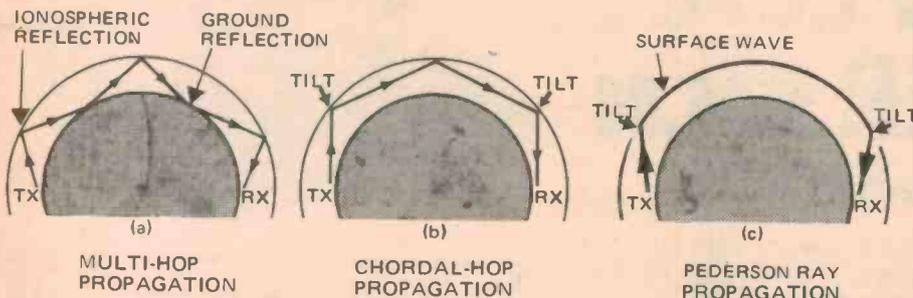


Fig. 12.

When tilts occur at suitable points along a path, particularly at the ionospheric reflection point nearest each terminal of a path (the 'control point'), then chordal hop propagation

often results. If a signal arrives at a tilt at a suitably low angle, then the ionosphere will support propagation well above the 'predicted' MUF and will also provide extremely strong signals on lower frequencies as the signal will spend less time travelling through the D-layer together with the decreased loss through successive ground reflections.

Chordal hop propagation has been exploited by amateurs working from Britain to Australia on several of the lower HF bands. Tilts occur in the base of the ionosphere at the 'sunset' zone and at regions either side of the geomagnetic equator. Using the tilt south of the geomagnetic equator in the Indian ocean area, and the sunset tilt over the Mediterranean, British and West Australian amateurs have been able to make contact on the 3.5 and 7 MHz bands at times when they would normally be 'closed'.

Low angle radiation from the antenna is necessary to exploit these modes but due to the ionosphere "focussing" the signal rays, and the low angle of incidence on the ionosphere, very little power is necessary to produce surprising signal strengths.

## "Pederson Rays"

Anomalies in the electron distribution well within the F-layer can entrap signals so that a sort of total internal reflection phenomena occurs.

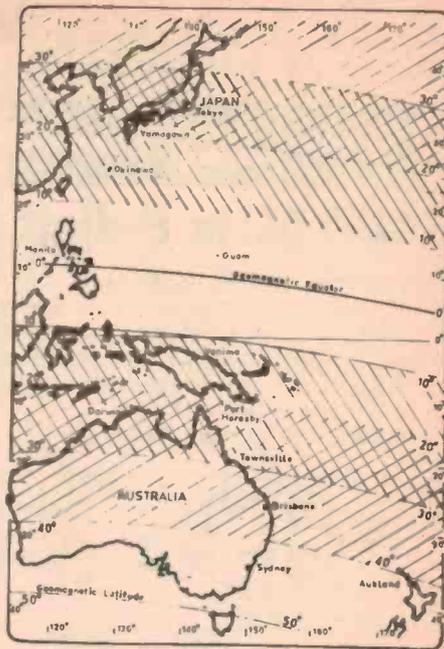


Fig. 14. Australasian sector of the world showing terminal zones for class I TEP (20° to 40° geomagnetic latitude) and class II TEP (10° to 30° geomagnetic latitude).

A signal trapped in such a manner can travel surprising distances, again without intermediate ground reflections, and re-emerge from the ionosphere via another anomaly or tilt.

Signals travelling through the ionosphere in this manner are referred to as Pederson Rays after the man who first described them. The phenomenon is illustrated in Figure 13.

A Pederson Ray generally travels through the ionosphere at considerable heights and experiences more "loss" than chordal hop signals. However, it is often experienced where high radiation angles occur from an antenna so that the signals enter the ionospheric anomalies at a favourable angle.

## Transequatorial Propagation

This mode of propagation was discovered by radio amateurs in 1947. Confirmed contacts on the 50 MHz band between amateurs in the USA and South America exploited certain characteristics of the equatorial ionosphere unknown at that time and which have taken some 30 years of research to explain — and it's not finished yet!

There are two types of TEP known as "afternoon-type", or class 1, and "evening-type" or class 2.

Afternoon-type TEP is a true chordal hop propagation mode and occurs generally between 1200 hours and 1900 hours local mean time. Stations situated in the zone between about 20° and 40° geomagnetic latitude are able to contact stations in a similar zone on the opposite side of the geomagnetic equator. Figure 14 shows the

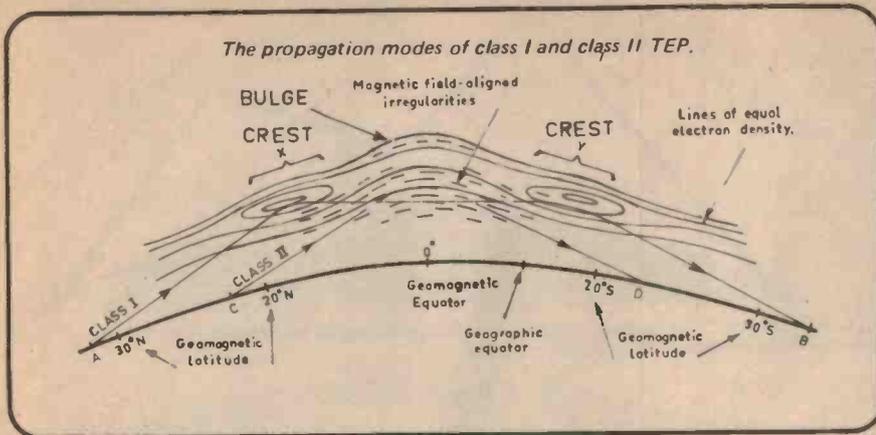


Fig. 15. The Propagation modes of class I and class II TEP.

Australasian sector of the world with the class 1 zones cross-hatched thus: // //.

Evening type TEP is generally experienced between 2000 hours and 2300 hours local mean time and stations located in the area between 10° and 30° geomagnetic latitude (cross-hatched // // in Fig. 14) can contact stations in the similar zone on the opposite side of the geomagnetic equator.

Transequatorial propagation is predominantly an equinoctial occurrence, peaking in the months March-April and September-October but it can occur over many more months around the equinoxes (21 March and 21 September), particularly during high sunspot activity.

The propagation modes for both classes of TEP are illustrated in Figure 15. The afternoon-type mode is generally called a "supermode". The signal is reflected from two dense 'bulges' in the ionosphere located either side of the geomagnetic equator. The density of these bulges, and the tilts associated with them, cause 'ray focussing' which gives rise to the surprising signal strengths observed on afternoon-type TEP signals. Fading on these signals is small; propagation distortion experienced on 'normal' ionospheric modes is absent giving rise to good quality signals as well.

Signals up to 65-70 MHz may be propagated by class 1 TEP, which represents a considerable extension of the conventional MUF for these paths. Occurrences will increase in coming years as the sunspot activity increases.

The best paths for class 1 TEP are those which cross the geomagnetic equator at angles close to 90°. Even so, paths which have considerable obliquity — such as USA to Australia — are occasionally bridged during good conditions.

Evening-type TEP is a "field-guided" mode. The equatorial bulges (X and Y in Fig. 15) that exist during the afternoon in the equatorial region of the

ionosphere break up after sunset and the ionosphere over the geomagnetic equator develops dense 'slabs' of ionisation which align themselves with the earth's magnetic field. If a signal is sent towards this area of the ionosphere so that it arrives more or less at a tangent to the magnetic field then it may become 'trapped' between the 'slabs' of dense ionisation and conducted across the equator by successive reflection from a series of these irregularities.

Again, signals will be quite strong on evening-type TEP but considerable 'flutter' fading is generally experienced — generally at a rate between 5 and 15 Hz.

Evening-type TEP will support signals of much higher frequencies than for afternoon type. Until recently, it was thought that the limit was in the vicinity of 100 MHz, but recent contacts between Australian and Japanese amateurs, as well as Puerto Rican and Argentinian amateurs, on the 144 MHz band clearly indicate that there is more to be learned about this mode of propagation.

Evening-type TEP is much more tolerant of path obliquity than afternoon-type. However, the paths are generally shorter.

The zones for each class of TEP shown in Fig. 14 are calculated from the geometry of the propagation mechanism and don't necessarily indicate the limits. Amateurs from Sydney right down to Hobart have worked into Japan on the six metre band on many occasions, via class 1 TEP.

Class 2 TEP rarely reaches as far south as Brisbane though. Extensions of the paths can occur if 'Sporadic E' propagation is available in suitable areas.

The propagation mechanism of evening-type TEP has only recently been explained. Research by scientists of the Australian Ionospheric Prediction Service has led to confirmation and explanation of class 2 TEP.

## Complex "Mixed" Modes

Many propagation paths can experience complex propagation modes involving both the F-layer and E-layer, particularly Sporadic-E. These modes are common on equatorial paths and can involve multiple reflections from the F and E layers both with and without intermediate ground reflection. These complex modes can give rise to extension of the MUF or disturb communications into particular areas.

Three types of complex modes are illustrated in figures 16, 17 and 18.

## Using the Prediction Charts

The ionospheric prediction charts published regularly in ETI show the frequency range which can be used over a particular path for a particular month (for the month ahead) and the variation over a 24 hour period.

The monthly predictions for each path show the maximum usable frequencies for less than 50% of the days of the month on the uppermost curve. This is the optimistic prediction. The curve below this indicates the predicted MUF for between 50% and 90% of the days of the month — a more reliable prediction. The absorption limiting frequency, the ALF, is indicated by the lower curve. Propagation over the path is not possible at times shown for the frequencies lower than the curve.

## Paths

The Australian Ionospheric Prediction Service provides ETI with computer printouts of monthly predictions for a total of 36 paths, but only the predictions for the common and/or most interesting paths will be reproduced each month. We have chosen the terminals of these paths so that the predictions will serve the widest range of reader's interest, both amateur and shortwave listener.

## Path Terminals

Four Australian terminals, serving the major population centres, have been chosen. These are as follows:

EAST COAST  
NORTH EAST  
SOUTH CENTRAL  
WEST COAST

These are more or less self-explanatory as regards the general area. The EAST COAST predictions serve the area from southern QLD to Tasmania. The NORTH EAST predictions serve northern QLD and to a large extent the Northern Territory.

The SOUTH CENTRAL predictions serve South Australia and the south area of the Northern Territory.

The WEST COAST terminal serves for Western Australia.

Continued from p. 113

As the paths are quite long, the only differences that will be noted by widely separated stations in the terminal service areas will be a slight time shift. From the published predictions it will also be noticed that several Australian terminal areas may be served by one path prediction. The similarity between predictions is so close that separate predictions are not warranted in these cases.

Consequently, although only 18 predictions may be published, as many as 28 paths may be covered by predictions.

There are nine overseas terminals chosen to provide predictions for major population centres or areas of particular interest. These are as follows:

- JAPANESE ARCHIPELAGO
- SOUTH PACIFIC
- NORTH AMERICA
- SOUTH AMERICA
- NORTH AFRICA
- SOUTH AFRICA
- CENTRAL USSR
- EUROPE-SHORT PATH
- EUROPE-LONG PATH

Predictions for the JAPANESE ARCHIPELAGO (labelled "JAPAN" on the graphs) will serve for Japan, Korea, south east Russia, Hong Kong etc, including the island chains near Japan. As this is a very good TEP circuit, watch for the predictions to exceed 40 MHz and signals up to 60 MHz or more may be experienced on Transequatorial Propagation.

The SOUTH PACIFIC predictions are centred on the Tuomoto Archipelago and serve the Gilbert and Ellice island group, Cook Islands etc.

The NORTH AMERICA predictions are centred on Colorado in the USA and should prove useful for USA, Mexico and Canada. The SOUTH AMERICA charts are centred on Bolivia and should

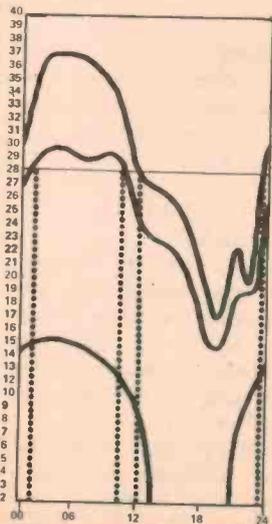


Fig. 19. Using the prediction graphs.

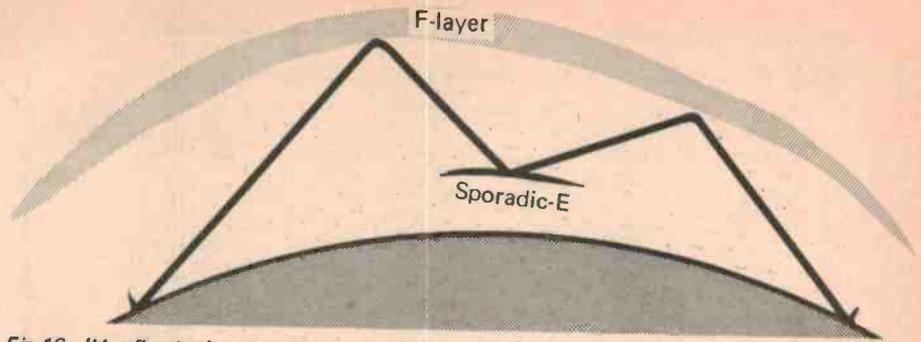


Fig. 16. 'M-reflection' - a complex propagation mode involving reflections from the F-layer and E-layer without intermediate ground reflection.

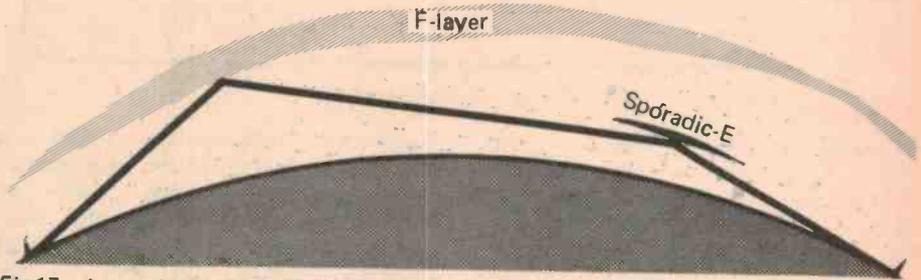


Fig. 17. A complex chordal hop mode involving reflections from the F-layer and E-layer without intermediate ground reflection.

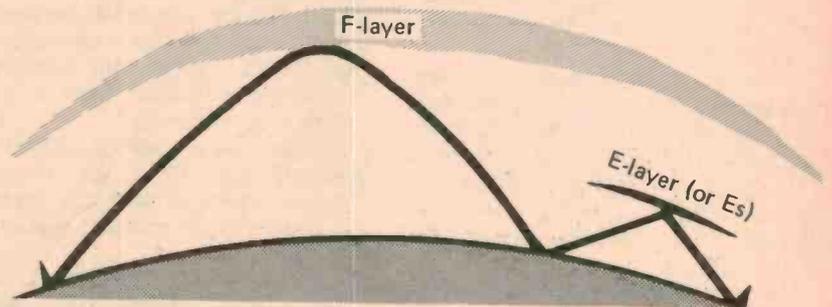


Fig. 18. A complex propagation mode involving one F-layer hop and one E-layer hop. Sometimes referred to as "N-reflection".

prove useful for most South American countries as well as Central America and the Bahamas.

The NORTH AFRICA chart is centred on Chad and should serve well for all of North Africa and the Mediterranean region. Predictions for SOUTH AFRICA are centred on Johannesburg and will serve south to central African countries.

The CENTRAL USSR prediction chart will serve the South Georgia, Novisibirsk to North India region.

Two prediction charts can be provided for EUROPE, "long path" and "short path". At present, the short path predictions are far and away the best, the long route suffering from severe absorption and is not 'open' at any times different to that for the short path.

If you are interested in a particular frequency band then the times it will be 'open' for propagation between the terminals given can be found from the graphs.

Project a line from the particular frequency band of interest across the

graph. Where this line crosses the MUF curve will indicate the times the path will be open for that frequency. Project lines down to the hours axis along the bottom of the prediction chart to read off the times.

The upper MUF curve will indicate that the path will be open for longer hours, but for fewer than half the days of the month. The lower MUF curve will show the band to be open on that path for fewer hours on most days of the month.

This is illustrated in figure 19 for the 28 MHz band. Note that 'Universal Time' (UT - better known as GMT) is used and you'll have to convert for your time zone. For the Australian East Coast, add 10 hours, for the Central Zone, add 9½ hours, for the West Coast add 8 hours.

Don't forget that in summer some states introduce daylight saving and an appropriate adjustment should be made.

Any enquiries about the predictions published in ETI should be directed to the magazine, not to the Ionospheric Prediction Service.

# Petanger Parametric Equaliser





The Petanger Dual 4 band Parametric is a state of the art stereo equalizer consisting of 4 independent filter sections in each channel. Each filter is capable of continuous adjustment of amplitude, frequency and bandwidth.

Petanger Audio Developments Dual 4 Band Parametric Equalizer gives you unprecedented accuracy in equalization — accuracy and simplicity — You can create just about any frequency response curve you can imagine. You no longer have to

compromise with tricky narrow band problems such as feedback, ring modes, pilot tones etc.

The large overlap margin even allows easy correction of broad and narrow band problems at the same time.

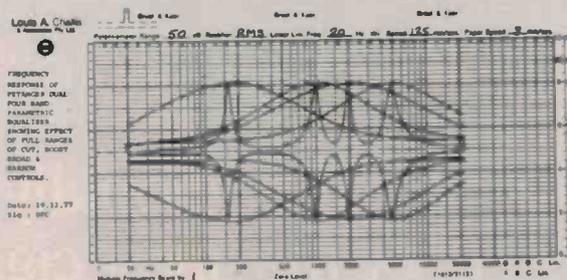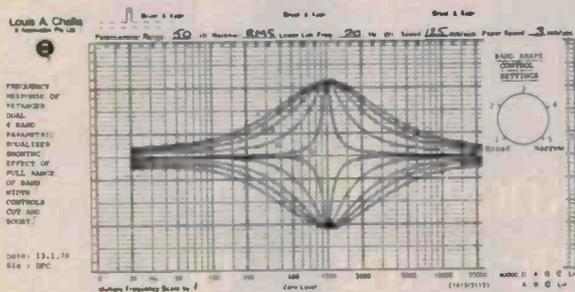Typical applications include: ● Feedback control ● Critical E.Q. requirements ● Room correction ● Microphone, instrument and vocal correction ● Noise and hum filter



Actual unretouched frequency sweeps

Distributed by:

# THE MUSIC DISTILLERY

PROFESSIONAL PRODUCTS GROUP  
503 Pittwater Rd, Brookvale, NSW. 2100.  
Tel: 938-4095/938.2372



INTERNATIONALLY acknowledged  
to be the finest cigarette in the world

**dunhill**

The most distinguished tobacco house in the world  
*London · Paris · New York*

# Mini-Mart

We'll print your 24 words (maximum) totally free of charge. Copy must be with us by the 7th of the month preceding the month of issue. Please, please write or preferably type your adverts clearly, using BLOCK LETTERS.

## CONDITIONS

Name and address plus phone number (if required) must be included within the 24 words allowed.

Reasonable abbreviations, such as 25 Wrms, count as one word. Private adverts only will be accepted. Please let us know if you find a commercial enterprise using this service.

Every effort will be made to publish all adverts received — however, no responsibility for so doing is accepted or implied.

Adverts must relate to electronics or audio — general adverts cannot be accepted.

PLEASE USE BLOCK LETTERS

|  |  |  |  |
|--|--|--|--|
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |
|  |  |  |  |

THE LADIES AMATEUR RADIO ASSOCIATION, LARA, HAS CHANGED ITS NAME TO THE AUSTRALIAN LADIES AMATEUR RADIO ASSOCIATION. ALARA, C/- 412 BRUNSWICK STREET, FITZROY, 3065.

SELL: COMPLETE 2650 SYSTEM INCLUDES 8K RAM EXPANDABLE TO 16K, CASSETTE INTERFACE WITH USERS GROUP DOCUMENTATION AND TAPES AND FULL ASCII KEYBOARD \$850. 4982707.

FOR SALE: STROBE \$15, INTERCOM \$8, ASSEMBLED PCB'S FOR ETI 4600 SYNTHESIZER — KEYBOARD CONTROL \$70, TRANSIENT 2 \$18, 2 X TRANSIENT 1 \$20. CARL VINE (02) 337 4681.

BRUEL & KJAER RLC DEVIATION BRIDGE \$90 10AMP REGULATED POWER SUPPLIES 2—50V \$70. ELECTRONIC MAINS STABILISERS 2—10kW. 25MHz LAB CRO & 2MHz CRO. 50kΩ DUAL SLIDERS \$20/100. (02) 604 5664.

CIRCUIT WANTED; 100 WATT OUTPUT STAGE (GUITAR) USING 6550'S OR SIMILAR; EG. 'WASP' OR 'BAEZ' AMPS. GARY KURZER 2/2 BELL STREET, WATSONS BAY. (02) 337 5348.

WANTED FUNDAMENTALS OF ELECTRONICS BY GROB AND KIVER WRITE P.O. BOX 279 KENMORE, 4069 QLD.

FOR SALE: ONE ASS & WORKING ETI-632 V.D.U. IN CABINET WITH SET OF 5 SPARE BOARDS. ALSO ONE SIGNETICS 2650 MINI COMPUTER INC MOTHERBOARD TESTED & WORKING BUT EXCLUDING XTAL RAM STICKS & P.S.U. BUT WITH ALL MANUALS ETC. ALL THE ABOVE FOR \$560.00 OR NEAREST OFFER 14 MOORE ST., WANGARATTA, VIC. 3677. OR PHONE (057) 21 2481.

SELL 200 E.A. MAGAZINES FROM 1944 TO 1976 G.C. WILL SEPARATE MUST SELL BEST OFFER. M.NEWMAM 34 TALBOT RD, MT. WAVERLEY, VIC. 3149 PHONE 2773125

SELL H.F. SPECTRUM ANALYSER S510 \$1100 ONO FT101 \$550 18 CH AIR HAWK BUET RIG \$150 18 CH LINER S878P \$175 P.O. BOX 22 HALLS GAP, VIC. 3381.

E.T.I. 1976—1977 COMPL. \$14 AMPL. 7W+7W NEAR NEW \$25 TURN TABLE BSR \$20 E.A. 1976—1977 PHONE 595572 (02).

WANTED URGENT CATHODE RAY SCOPE WILL PAY UP TO \$200 35 NESTOR AVE., BARDON, BRIS. 366863 P/S UP TO 10 MHz

COMPUTER PANELS OLD STYLE 2—2AU7 ASSORT. RESISTORS CAPICATORS ALL HIGH WATTAGE AND TOLERANCE GIVE AWAY PRICE 5c PER PANEL MIN. \$1 (02) 6428118 SYDNEY

SELL: 12 VOLT 5 AMP POWER SUPPLY. GOOD REGULATION, TESTED. IDEAL FOR C.BER or VK. \$40 PHONE (02) 5464716 AFTER 5PM. ST. GEORGE AREA.

WANTED CHEAP WORKING OSCILLOSCOPE SUITABLE AUDIO WORK. ALSO INTERESTED TO CONTACT MUSIC SYNTHESIZER ENTHUSIAST IN S.E. QLD. IAN CURRIE "MANDAZA", MARYVALE, QLD. 4370.

WANTED SIGNAL GENERATOR TF995 OR SIMILAR VK7JG PH (003) 443882 P.O. BOX 1311 LAUNCESTON.

SELL ETI632 C \$55 M.B. WITH P.S. \$25 SYNC \$15 B \$20 MEMORY 1K \$30 D.KING 47 WARDELL STREET ASHGROVE, BRIS. QLD. 4060. PHONE (07) 383878.

WANTED. T.T.I. OSCILLOSCOPE ASSEMBLY INSTRUCTIONS AND CIRCUIT. WILL COPY AND RETURN SAME. A. DAALMEISER, 11 DAHLIA STREET, GREYSTANES, SYDNEY 2145. 604-1072.

EDDYSTONE BOXES NO. 6908, TRADE \$6.00 EA, SELL \$3.00 EA. HITACHI 2SB468 TRANSISTORS 200V, 10W & 10A, TRADE \$6.40 EA, SELL \$3.00 EA. G. ABBENBROEK, 38 CLEMATIS AVENUE, FERNTREE GULLY. (03) 758 4650.

SELL: TRANSFORMER PR1240V SEC 650V/380V/2A \$25. ALSO TESTER NON-DESTRUCTIVE FOR CAPACITOR, METERED \$25. R. LAUBE, P.O. BOX 93, PYRMONT NSW 2009.

SELLING AMPLIFIER UHER CV140 33 WRMS/CHANNEL. SEPARATE INPUT VOLUME CONTROLS. FIRST TO HEAR WILL BUY \$215 9/3 FAIRLIGHT STREET, MANLY 9493275 AH.

COLOUR V.T.R. SHIBADEN SV700 WITH SERVICE MANUAL, AS MODIFIED BY EXENON IMPORTS UNUSED, \$600. VORTEX TAPE MECHANISM NEW \$20. R. STEWART 21 MALLA AVE., ROBINVALE, VIC. 3549.

HELP! NEED PHOTOCOPIES OF COMPLETE PRACTICAL ELECTRONICS RADIO CONTROL SYSTEM (9 CHANNEL) FROM ISSUES JUNE—AUGUST 1976 WRITE S. JAY 32 RAMSAY STREET, LAUNCESTON, TAS 7250.

WANTED CIRCUIT DIAGRAMS FOR EX-ARMY WC 62, A510, CPRC 26. LETTERS ONLY PLEASE TO J.A. FAULKNER, 56 COVENEY ST., BEXLEY NORTH, NSW. 2207. WILL PAY.

send your ad to —  
ETI MiniMart,  
Modern Magazines,  
15 Boundary Street,  
Rushcutters Bay,  
NSW 2011.






### Using ETI PCB Artwork

This method can be used to make negatives of ETI artwork from October 1977 on, provided the reverse of the page is printed in blue. The film used is Scotchcal 8007 which is UV sensitive and can be used under normal subdued light.

Cut a piece of film a little larger than the PC board and expose it to UV light through the magazine page. The non emulsion side should be in contact with the page. This surface can be detected by picking the film up by one corner - it will curl towards the non emulsion side. Exposures of about 20 minutes are normally necessary.

The film can now be developed by placing it emulsion side up on a table, pouring some Scotchcal 8500 developer on the surface and rubbing it with a clean tissue.

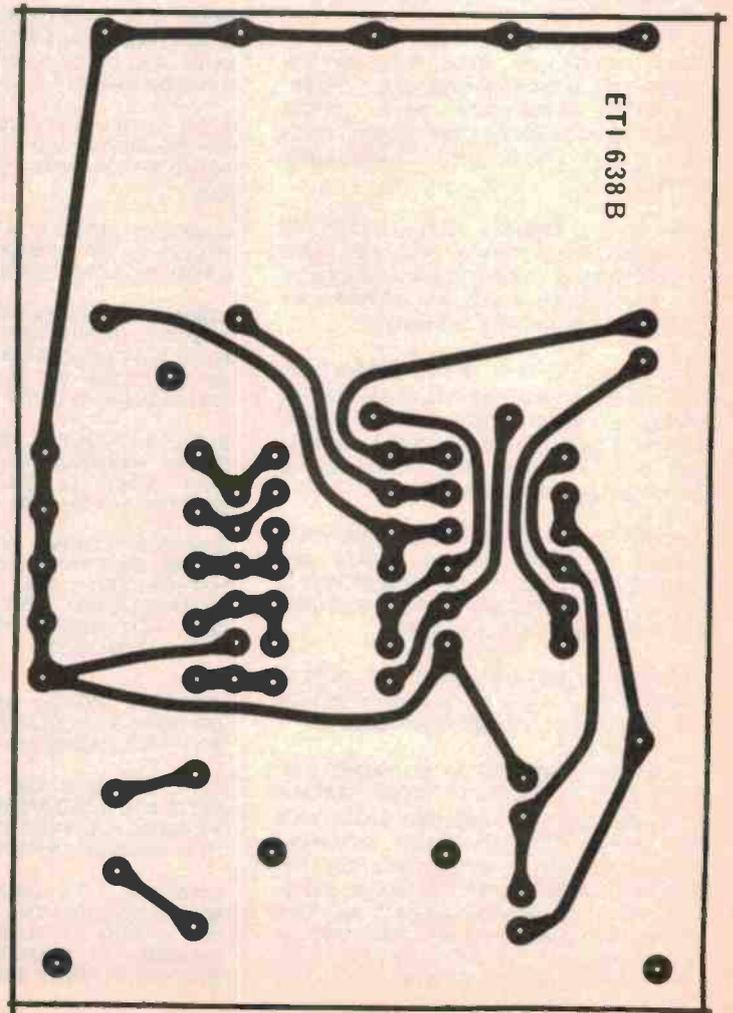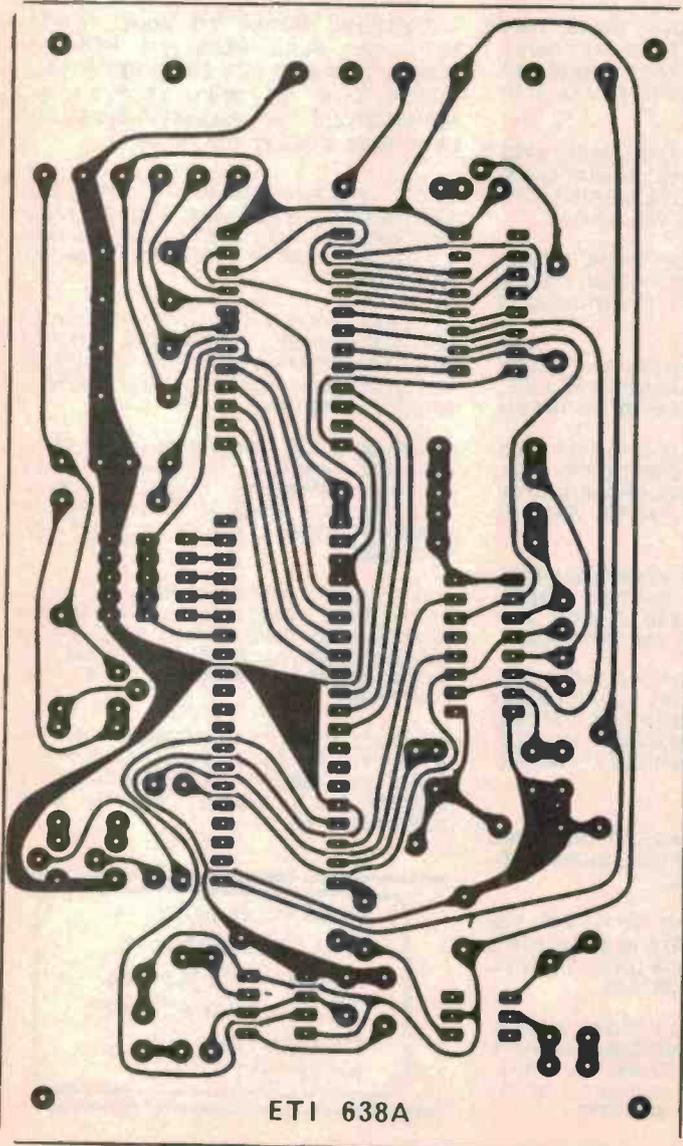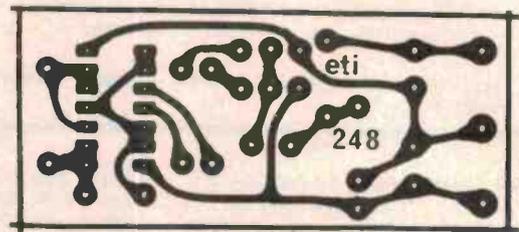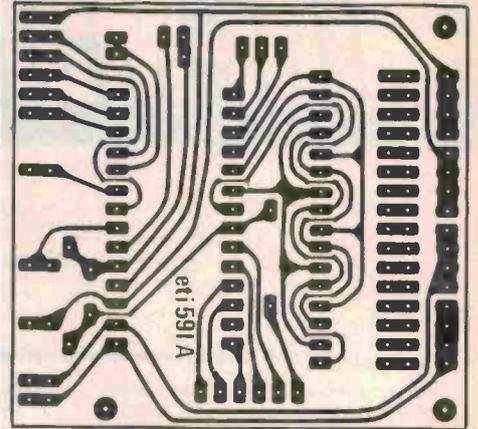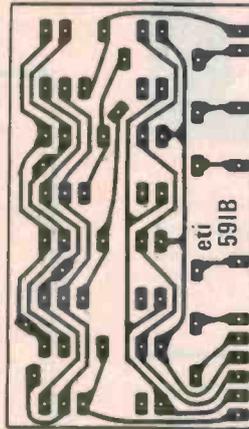Further information on Scotchcal and PCB manufacture can be found in the September and December 1977 issues of ETI. Please note also, that occasionally pressure on space may unfortunately prohibit the printing of blue type behind all PCB's, in which case the reader must resort to more conventional photographic techniques for PCB manufacture.



# A professional iron with adjustable temperature-wattage and tip size...

For the technician involved in high reliability soldering and desoldering who finds different jobs call for a different iron specification. With the scope TC60 240V 60W variable temperature iron.

- You specify exact temperature required without changing tip. Dial any intermediate temperature 200°-400°C and make adjustment while soldering. This will be controlled with unusual accuracy ± 2% of set temp. You no longer need to invest in a range of tips just to vary temperature.
- You specify exact tip profile required without affecting temperature. Screw on any one of 14 tip shape and weight combinations from 0.8 mm to 6.4 mm all iron plated for long life. No need to buy up to 3 irons to span this tip range.
- You specify that the desired wattage range lies between 10W-60W. Then let actual wattage required for the job be determined by the iron's simple mechanical sensing and control system. Consisting of expansion rod and micro switch in the handle.

- PROTECTION Component protection is aided by earthed tip and barrel. Critical components & operator can then be earthed to common point.
- COOLER FINGER GRIP Cooling fins keep your finger tips comfortable handle shape aids good balance and feel.
- TEMPERATURE KEY Is inserted into handle 40°C variation per quarter turn. Key is removable to discourage unwanted alteration to setting.
- NEON Indicates when power is being applied to element - monitors control system.
- 50V, 24V VERSIONS Are available with 50W elements.

**SOLDERING-DESOLDERING STATION**

ANTI SEIZE CONDUCTIVE PASTE      SAFETY STAND AND SPONGE

SOLDER REMOVER      I.C. DESOLDERER

**Long life tips for Scope TC60 iron.**

| DOUBLE FLAT |        |        |        |        |        | SINGLE FLAT |        |        |        |        |         |           |
|-------------|--------|--------|--------|--------|--------|-------------|--------|--------|--------|--------|---------|-----------|
|             |        |        |        |        |        |             |        |        |        |        |         |           |
| 0.8 mm      | 1.6 mm | 2.4 mm | 3.2 mm | 4.8 mm | 6.4 mm | 2.6 mm      | 1.6 mm | 2.4 mm | 3.2 mm | 4.8 mm | 6.44 mm | con-corde |

Iron plated screw-on pre tinned. \*This tip is fitted as standard.

## SCOPE TC60

The iron you completely adjust to your job.

**FOR YOUR NEAREST STOCKIST RING:**

MELBOURNE VIC.  
(03) 338 1566  
SYDNEY N.S.W.  
(02) 818 1166  
ADELAIDE S.A.  
(08) 212 3111

BRISBANE QLD.  
(07) 221 1933  
TOWNSVILLE QLD.  
(077) 71 3448  
ROCKHAMPTON QLD.  
(079) 27 3370

HOBART TAS.  
(002) 34 2811  
LAUNCESTON TAS.  
(003) 31 5545  
PERTH W.A.  
(09) 381 4155

AUCKLAND N.Z.  
54 6029  
WELLINGTON N.Z.  
85 9578

# SWL COMMUNICATIONS

Compiled by Peter Bunn,  
on behalf of the Australian Radio DX Club (ARDXC).

## WORLD ADMINISTRATIVE RADIO CONFERENCE 1979

In October 1979, in Geneva, the International Telecommunications Union (ITU) convenes the first World Administrative Radio Conference in 20 years.

WARC-79 is of vital importance for both international shortwave broadcasters and DXers as it is expected to determine the structure and the size of the shortwave broadcasting bands (i.e. that part of the frequency spectrum reserved for commercial shortwave broadcasting) for the remainder of this century.

Since the previous conference in 1959, there has been a tremendous increase in the number of broadcasting stations using shortwave, as well as an accelerating "power race" by major broadcasters who now use 250 kilowatt and even 500 kilowatt transmitters.

The consequent over-crowding of the frequency spectrum reserved for shortwave broadcasting has led some stations, such as Radio Sweden and the Swiss Broadcasting Corporation, to try experiments with single side band (SSB) transmissions. SSB transmissions narrow the bandwidth of the signal and make more effective use of transmitted power by eliminating the carrier which is present in normal AM signals. Such experiments have not been altogether successful, not least because many potential listeners use inexpensive receivers which lack the BFO (beat frequency oscillator) necessary to resolve SSB signals.

Another solution to overcrowding on the shortwave broadcast bands being adopted by an increasing number of broadcasters is the use of out-of-band frequencies, usually adjacent to the officially designated bands. The ITU regulations allow this, with the proviso that no interference is caused to the great variety of other facilities using the frequency spectrum. Frequencies immediately adjacent to most of the shortwave broadcast bands are generally reserved at present for international fixed services, mainly radio-telephone, radio-teletype and other such point-to-point services. With the growing use of satellites for these fixed services, these channels have been left vacant to a greater extent, thus providing frequencies for commercial shortwave broadcasting. This has led to a practical (though unofficial) expansion of many of the shortwave broadcast bands, and examples of this are just

below the 49 metre band (5950 - 5900 kHz), just above the 41 metre band (7300 - 7400 kHz), and above the 25 metre band from 11975 to 12100 kHz.

and examples of this are just below the 49 metre band (5950-5900 kHz), just above the 41 metre band (7300-7400 kHz), and above the 25 metre band from 11975 to 12100 kHz.

Two long term solutions to the problem of over-crowding of the shortwave broadcast bands certain to be considered are the expansion of the existing broadcasting bands, and secondly, the creation of new broadcasting bands.

Proposals for band changes were made at a meeting earlier this year of representatives of 14 international broadcasting organizations and a number of telecommunications authorities from western countries, including Australia. The major points of interest for DXers in the proposals of this meeting in Vienna are:

- Expansion of all present SW broadcasting bands (except the little-used 11 metre band) into adjacent channels eg: the lower limit of the 49 metre band would move down to 5740 kHz from the present 5950 kHz.
- Creation of a new band reserved for international broadcasting, from 13600 to 14000 kHz.
- Removal of amateur operators from the 41 metre band.
- Introduction of international SW broadcasting into the 60 metre band, which is currently reserved for local broadcasting in tropical regions.

The final proposal is certain to meet with strong opposition from Third

World countries at the World Administrative Radio Conference in October next year.

But whatever the outcome of WARC '79, it is certain DXers can look forward to a greater proportion of the frequency spectrum being reserved for shortwave broadcasting, and that means a reduction in both co-channel and adjacent channel interference in the broadcast bands during the 1980's.

## LITHUANIA

Radio Vilnius produces a daily service for North America in English, which is broadcast 2300-2330 GMT via transmitters throughout the USSR. The J-78 (May to September) schedule indicates the following outlets for this English service from Vilnius: 9600, 11780, 11790, 12060, 15180, 15405 and 11690 kHz. Bob Padula of Melbourne provides this schedule, and adds that the last mentioned outlet is not announced by the station, while 11870 kHz is announced on air but remains unheard. Readers are reminded that Radio Vilnius, in common with all international broadcasting stations, will introduce a new schedule from September 3 for transmission period S-78 which will remain in effect until November.

## ENGLISH FROM GHANA

The Ghana Broadcasting Corporation at Accra currently operates only one frequency for its Overseas Service, this being from a transmitter located at Tema, on 6130 kHz. English programming may be heard at 2000-2300 daily, though best reception is between 2245 and 2300 when English news may be heard, according to Peter Bunn in Melbourne.



GHANA BROADCASTING CORPORATION  
P.O. BOX 1633  
ACCRA, GHANA

Dear Sir/Madam,

Thank you for your reception report of our transmission(s)  
on 6130 kc/s heard at 2234  
2300 G.M.T. on July 16, 1976

We have pleasure in verifying your report which is much appreciated.



11 SEP 17 1976

For Director-General

# **KENWOOD** ...pacesetter in amateur radio



## THE ULTIMATE IN AMATEUR RADIO EQUIPMENT DESIGN

DISTRIBUTION SERVICE AND SPARES BY:  
 TRIO-KENWOOD (AUSTRALIA) PTY. LTD. 30 WHITING STREET, ARTARMON. (P.O. BOX 425 ARTARMON 2064) Ph: 439 4322  
AUTHORISED DISTRIBUTORS IN ALL AUSTRALIAN STATES.

# **DISTRIBUTORS**

**for the Electronic Industry**

## **ARE YOU AWARE??**

**THAT WE HAVE PROBABLY THE LARGEST RANGE IN AUSTRALIA OF TOP-BRAND, QUALITY PRODUCTS AT CURRENT MARKET PRICES WITH OFF-THE-SHELF AVAILABILITY.**

### **Semi-Conductors**

Delco  
E.D.I.  
General Electric  
Intermetall  
I.T.T.  
National Semiconductor  
N.E.C.  
Philips  
Sanyo  
Signetics  
Solitron  
Texas Instruments  
A.M.D.  
Intersil  
Monolithic Memories

### **Passive Components**

Bournes  
Elna  
Erie  
I.T.T. Capacitors  
I.T.T. Thermistors  
Philips (Elcoma)  
R.C.A.  
Soanar  
Sprague

### **Electro-Mechanical and Hardware**

Alco  
Cannon  
Delco Heatsinks  
I.T.T. Diecast Boxes  
I.T.T. Fans & Blowers  
Dica I.C. Accessories  
I.E.E.  
I.T.T. Relays  
Jean Renaud  
J.A.E.  
National Relays  
Pomona Accessories  
Rotron Fans  
Switchcraft Connectors  
Thermalloy Heatsinks  
T.I. I.C. Accessories  
Weller Soldering Erous  
G.E. Rechargeable Batteries

*Trade enquiries to:*

## ***Instant Component Service***

P.O. Box 2, Arncliffe. N.S.W. 2205. Ph (02) 597-1444  
Adelaide 267-2393. Melbourne 95-9566. Sydney 597-1444

# Instant Component Service

## DISTRIBUTORS:-

**NORTH.**  
**J. A. SEVERN**  
 P.O. Box 47  
 Epping 2121  
 869-1058

**EAST.**  
**RADIO DESPATCH  
 SERVICE.**

869 George Street,  
 Sydney, N.S.W. 2000  
 Phone: 211-0191

**NEWCASTLE.**  
**DIGITRONICS**  
 186 Parry Street,  
 Newcastle West, 2302  
 Phone: (049) 614991

**BRISBANE.**  
**NOW OPEN AT**  
 Cnr Montague Road &  
 Victoria Street,  
 West End. Qld. 4101.  
 Phone: 44-6667  
**RON BURR**

**CANBERRA**  
**ELECTRONIC**  
**COMPONENTS PTY. LTD.**

29 Woolongong St,  
 Fyshwick. ACT. 2609.  
 Phone 95-6811, 95-9138.  
 Telex 62468.

5/2 10/7


- MIRRORBALLS • BEACONS
- ROPELIGHTS • CHASERS
- STROBES • SOUND TO LIGHT
- STAGE DIMMERS • BUBBLE
- BLOWERS • ULTRA VIOLET



• LARGEST RANGE  
 OF 3" EFFECTS CASSETTES  
 AND 6" WHEELS.

Australia's most  
 helpful professional  
 supplier of effects  
 lighting equipment  
 and discotheque  
 consoles

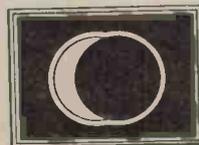**Solar, Tutor and  
 Aquarius effects  
 projectors and  
 accessories.**



**ECLIPSE LIGHTING  
 & ELECTRONICS**

100 Penhurst St.,  
 Willoughby, Phone 95-4212.

## FRONT PANEL DISPLAY




Designed for 8080 but will suit most systems. Input lines are 16 ADD Lines, 8 Data lines, 2 x 8 Bit prog, output port, status flags etc. All inputs buffered, flat cable interface. HEX DISPLAY with 1/2" high 7 seg. Led display for Address & Data bus. 4 Displays for address bus and 2 displays for data bus. 10" x 8" board size.  
**WITH HEX DISPLAY — KIT PRICE \$105.00.**

## NUMBER CRUNCHER

MM57109 Number Cruncher. Buffered I/O will suit 8080, 6800, SCAMP, etc. Will perform floating point and scientific calculations under software control. Full data and software support.

**KIT PRICE \$54.00  
 BUILT AND TESTED \$72.00**

## PAPER TAPE READER

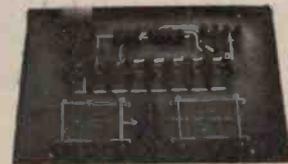

Manual operation, self-contained in case 160 x 110 x 50. Flat cable interface to I/O port. Handshake logic, Status LEDs, Data and software supplied. Simple to use on all systems 8080, 6800 etc.

**KIT PRICE \$78.00**

## BACKPLANE BOARDS



Quality fibreglass boards, 5 sockets per board with wide spacing, provision for linking boards together, even different types.  
 8" x 8" 6800 board with wide centres — \$26.50.  
 12" x 6" 8080 board with provision for both sockets — \$27.50.

## GOLD PLATED SOCKETS

To suit 8080 & 6800. 43 way double sided, \$9.50 or 5 for \$45.00.

## U.V. EPROM ERASER

Erase up to 4 eproms at once, such as 2708 etc in 15/30 mins. 240 V operation, small size 3" x 4" x 8" Assembled and tested only. \$47.50.

## SINGLE STEP CONTROL for 8080

Push button single step mode. Auto step low speed (Variable speed) mode, Interrupt facility. Run mode LED, will suit other systems, works off wait. & ready. lines. Panel mount. **KIT PRICE \$23.00.**

All Boards double sided with ground plane.

## ALL PARTS POST FREE

See advt Jan 78 EA for digital tach, stop watches, tran. ignition system, burglar alarm, etc.

*Built & Tested prices and Tax Free prices on application.*

## S.M. ELECTRONICS

10 Stafford Court, Doncaster East, 3109.  
 Box 19, Doncaster East, 3109. (03) 842-3950.



# A TV GAME KIT FOR THRILLS & SPILLS

# MOTOR STUNT CYCLE GAME

COMPLETE KIT  
**\$29<sup>50</sup>**  
 Cat. K-3474 ▲  
 P&P \$3.00



REQUIRES 6xAA batteries  
 Cat. S-3003 15c each.

What an incredible way to spend the cold winter nights! With this latest video game you can pit your skills against the latest in IC technology, in the form of motor cycle games. The games are complex enough to give many hours of pleasure and excitement but the construction is extremely simple, even for the raw beginner. There are two stages of skill (pro and amateur) and four games – Motorcross, Enduro, Drag and Stunt. Plug into your TV set and enjoy all of the thrills and spills of motor cycling from the comfort of your own armchair.

- \* Similar to the games costing over \$1,000 found in many hotels.
- \* See Electronics Today June 1978 issue for article.
- \* Computer IC contains 1000's of transistors and complex circuitry.
- \* Crystal controlled and exclusive pre-built modulator - absolutely no tuning required.
- \* Professional unit designed especially for the beginner.
- \* Fully pre-punched and pre-drilled front panel, for the professional look.
- \* Simply plug into your TV aerial socket.
- \* In-built speaker and on screen scoring.


## SPECIAL OFFERS- YOU CAN'T LOSE

**7 DAY INSPECTION OFFER.**  
 Buy the kit, take it home and have a good look at it. If you feel that it is beyond your capabilities then return it to us in its original packing and condition and we will refund your money.
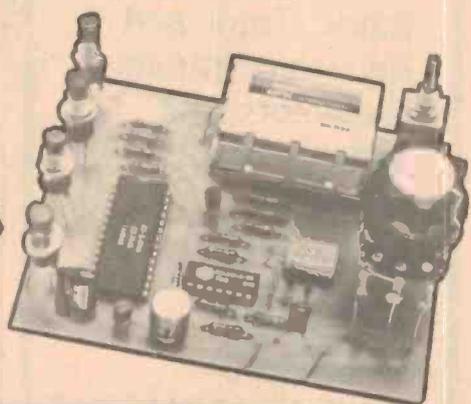
### 'SORRY DICK IT DOESN'T WORK' OFFER.

The Dick Smith kit is so complete and easy to build that even a complete novice will have no trouble building it with complete success. However even in the unlikely event that you can't get yours to work, don't worry! Every kit contains a "Sorry Dick it doesn't work" coupon. You send in your TV game, the coupon and for a service fee we'll fix it for you. The service fee covers everything except replacement of the IC, should this be necessary.

**THE HEART OF THE GAME.**  
*The printed circuit board showing how simple the construction is - with the kit you get full easy to follow instructions.*



**SPARE PARTS CORNER**

|                 |        |         |
|-----------------|--------|---------|
| PC Board (only) | H-8615 | \$3.85  |
| RF Modulator    | K-6040 | \$3.00  |
| AY-3-8760 IC    | Z-6854 | \$19.50 |
| 3.58MHz crystal | K-6031 | \$3.00  |

# DICK SMITH ELECTRONICS

**SYDNEY** 125 York Street, SYDNEY. Ph. 29-1126  
 147 Hume Hwy, CHULLORA. Ph. 642-8922  
 162 Pacific Hwy, GORE HILL. Ph. 439-5311  
 30 Grose Street, PARRAMATTA. Ph. 683-1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67-9834  
 656 Bridge Road, RICHMOND. Ph. 42-1614  
**BRISBANE** 166 Logan Road, BURANDA. Ph. 391-6233  
**ADELAIDE** 203 Wright Street, ADELAIDE. Ph. 212-1962

**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.



SHOPS OPEN 9AM to 5:30PM  
 (Saturday 9AM - 12 noon)  
 BRISBANE 1/2 Hour earlier.

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

**GRACE BROS**  
 Broadway • Bondi • Chatswood • Liverpool  
 Murrumbidgee • Mt Druitt • Parramatta • Roselands  
 and Warringah Mall



## LATIN AMERICAN ROUND-UP

Radio Luz y Vida at Loja, Ecuador, has been logged in Melbourne by Peter Bunn on the new outlet of 4850 kHz, having moved from 4830 kHz. Reception was fair with Spanish station identification at 1145. Sign-on time for Radio Luz y Vida is 1045 GMT.

Radio America at Lima, Peru, now appears to be running to a 24 hour schedule, with much US pop music. Reception in Melbourne is very good between 0600 and 0900 GMT on 6010 kHz.

Radio-television Dominicana at Santo Domingo in the Dominican Republic currently provides good reception in our evenings from 1000 GMT until past 1100 GMT. The station varies nightly in its operating frequency, as both 5970 kHz and the adjacent 5975 kHz have been noted on separate occasions.

## ECUADOR


The voice of the Andes, HCJB at Quito, has introduced a new frequency for daily broadcasts to Europe. In line with the current trend to higher frequencies due to greater sunspot

activity and the European winter, HCJB now uses 21490 kHz between 1500-2100 GMT. English program segments are aired at 1530-1800 and 1900-2030 GMT on this new outlet.
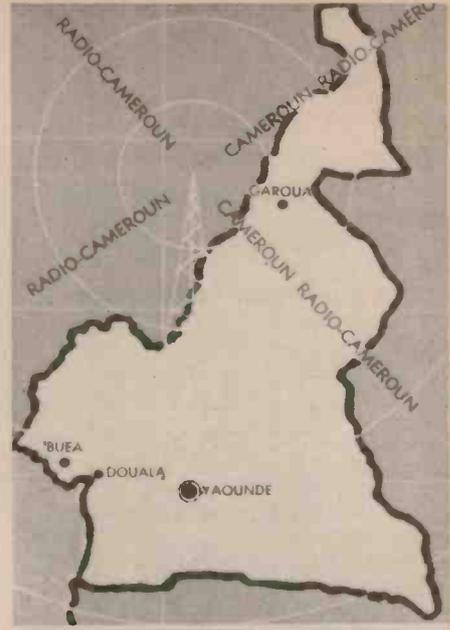
## AFRICAN SIGNALS

Our early mornings are the best time to tune to Africa. Two of the strongest signals are currently observed from Bangui in the Central African Empire on 5038 kHz until station close at 2300 GMT, and from Radio Garoua in Cameroon on 5010 kHz. Garoua closes transmission daily at 2200 GMT. Another station providing particularly good reception at the moment is Radio Ghana on 4915 kHz, which may be heard until sign-off at 2305 GMT. This is the Home Service program, and is separate from the Overseas service mentioned earlier. This outlet is easily found on the dial, as it is just below the strong signal put out by the ABC Brisbane regional service on 4920 kHz.

Meanwhile, Radio Nacional de Angola at Luanda may now be heard on the new outlet of 4790 kHz, replacing 4820 kHz. Bob Padula notes good signals between 2000 and 2300 GMT.



The Australian Radio DX Club is a non-profit body with headquarters in Melbourne. For further information on shortwave radio, and on the activities of the ARDXC, please write to the General Secretary, PO Box 67, Highett, Vic. 3190, enclosing a 30c. stamp for return postage.

# AMATEUR COMMUNICATIONS

## Trio-Kenwood Expansion

Trio-Kenwood (Australia) Pty Ltd was established in August 1977 and commenced operations in October 1977 to distribute the Hi-Fi products of its parent company, Trio-Kenwood Corporation of Japan.

More recently (and more importantly), Trio-Kenwood Communications Division was registered as a subsidiary of the Australian company with the dedicated objective of providing 'professional facilities to amateur radio operators'.

Administration and Accounts will be handled through the main Australian company (TKA) at 30 Whiting Street, Artarmon, NSW, but the communications company has its own premises, including warehouse, showroom, offices, service department and spare parts store, across the street at 31 Whiting Street, Artarmon. Any questions? Phone: 439-4322.

## Begonia Award

The Ballarat Amateur Radio Group, Victoria, has initiated the "Begonia Award" Certificate which is available to amateur operators or SWL's who can show confirmation of working or hearing Ballarat amateurs.

As from 1 January 1978, the requirements for issue of the certificate are:-

1. **DX stations or SWL's.**  
Work or hear 5 Ballarat amateur stations. Any band, any mode. Cost 8 IRC's.
2. **VK stations or SWL's.**  
Work or hear 10 Ballarat amateur stations. Any band, any mode. Cost \$2.00.

## LOGS:

Send a list of stations worked stating callsign, name, date, band, mode and time in Zulu. Do not send QSL cards.

## SEND LIST TO:

Award Manager, R E Barker, 22 Pauls Crescent, Wendouree, Victoria, Australia, 3355.

# CB COMMUNICATIONS

## Ah so - Asahi

The Asahi brand name has been closely associated with CB products since before... well, since before most current CBers remember.

Asahi antennas are well known by the 'old hands' of CB and a new Asahi

antenna release is obviously worth some scrutiny.

The 'Million CW7' is a top-loaded, cowl mount mobile antenna that is reputedly tops amongst European CBers.

It mounts in the ordinary car radio antenna hole on a vehicle cowl or fender and, for this reason, the CW7 includes an adjustable ball and locking screw.

This allows the antenna to be adjusted to a vertical position, regardless of the slope of the car body panel on which it is mounted.

Over-all length is 1.4 metres and the antenna is supplied with a coax cable including connectors on each end.

The Million CW7 is distributed through Imark Pty Ltd, 66 Banfield St, Ararat, Vic., 3377, (053) 52-2697.

## Tallest legal base antenna?

A new design threequarterwave base antenna has just been released on to the market by Dick Pullem's Electric Bug - Adelaide's "biggest little CB shop".

They claim their design has the highest performance as tested against other leading half and five-eighth wave base antennas.

We'd like to test one - especially since reading what all the theory books have to say about 3/4 - wave antennas!

The antenna is constructed using cadmium-plated steel for the base, stainless steel in the driven element support, PTFE insulator (polytetra-

# CB COMMUNICATIONS

luorethylene – to the chemists, and that's what you call a proper insulator) and all joints are bolted right through (no self-tappers!).

If you want to try one of these out you'll have to crack the piggy banks for all of \$69.86 and trundle down to Dick Pullem's Electric Bug at 264 Torrens Rd, Croydon, SA. 5008. Phone 46-3019.

## Dick in Grace Bros.

Dick Smith has taken over the electronic equipment concessions previously held by Audio Shack in Grace Bros' Sydney suburban stores.

The Dick Smith Electronics departments at Grace Bros stock most of the products sold in Dick's eight electronics enthusiasts' shops around Australia.

There is special emphasis on electronic products for the home handyman, car buff and hi-fi enthusiast.

Many of these products are imported directly by Dick Smith and are exclusive to his electronics departments at Grace Bros and his own retail outlets.

## New Mura SWR meter

The latest SWR meter from Mura, their CBT-35, is a deluxe unit featuring separate meters for simultaneous measurement of SWR and RF power.

It includes an antenna tuner for precise antenna-feedline system tuning.

Like its little brothers (or is that sisters?), the CBT-15 and CBT-25, the new model has backlit meter scales and includes an integral 610 mm coax lead and PL259 connector – no "jumpers" necessary.

The CBT-35 has two power ranges: 10 watts and 100 watts, and indicates percentage modulation as well.

Two special brackets are included for easy attachment of the instrument above or below your transceiver or whatever you want to mount it on.

The matcher is claimed to match impedance between 25 and 140 ohms down to the required 50 ohms.

The CBT-35 is a handy 160 mm by 54 mm by 70 mm, and makes good use of the two relatively large meter scales.

The Mura CBT-35 is distributed in Australia by President Electronics, 15 Boundary St, Rushcutters Bay 2011, (02) 33-3727 – with dealers all over.

In Melbourne, try Just CB of 546 Whitehorse Rd, Mitcham, Vic, 3132 (03) 873-2673.

## Sawtron UHF from Imark

Owen Smart of Imark, Victorian CB supplier from Ararat, returned from Japan recently with news that he will be releasing a range of UHF CB rigs under the Sawtron brand name between June and August this year.

There are to be three rigs in the range; an economy mobile, a deluxe mobile and a deluxe base station.

The two mobile rigs will have control consoles which can be separated from the transceiver portion of the rig. This allows the transceiver section to be mounted in any safe, convenient position away from the controls – and possible rig snatchers – in the vehicle boot, under a seat etc, in the same fashion as "hide away" HF rigs.

The deluxe mobile will feature a "selective calling" facility. This allows communications only between stations fitted with the appropriate electronic circuitry that adds a special 'tone-burst' signal to the transmission that opens the other station's mute.

The deluxe base station features a control panel that looks more like a desk-top calculator than a CB console. It has no conventional knobs. There is a keyboard entry for the selective calling feature (selecall) a built-in base-type microphone, push button channel change and slide controls for squelch, volume control etc.

There are two LED digital readouts, one for the channel number, the other for the selecall.

The big advantage with the base station is that the transceiver section can be situated up to 200 metres away from the control console. Thus, it can be located close to the antenna, mini-

missing the length of coax feedline necessary (saving money on expensive low-loss coax!) and reducing the amount of power and signal lost in the coax. This allows top performance to be obtained.

Naturally, everybody's asking about price. The economy mobile will retail for around \$300 to \$350. The deluxe mobile for about \$350 to \$400. The deluxe base station will sell for a very competitive \$450 – \$500.

Imark will also be making a range of antennas available for the UHF CB band for both mobile and base applications.

Want to know more about what CB radio is coming to? – contact Imark at 66 Banfield St, Ararat, Vic., 3377 (053) 52-2697.

## RB14 - ho, hum delayed again!

The revised RB14, which has been promised to us since ... um, ah, jeez, it's so long I've forgotten, has been delayed again.



More red tape it seems. Nobody can be satisfied with all the proposals in the draft - and the first thing we're likely to see will only be a draft anyway - so why can't it be released, warts and all, for everyone to comment and then thrash it out from there?

If you want to know what might be in the all-new singing-dancing, virginal white, lemon-fresh RB14 then get a copy of the June issue of CB Australia from your local newsagent.

Do we get to see it before Christmas? – said the Bishop to the actress!


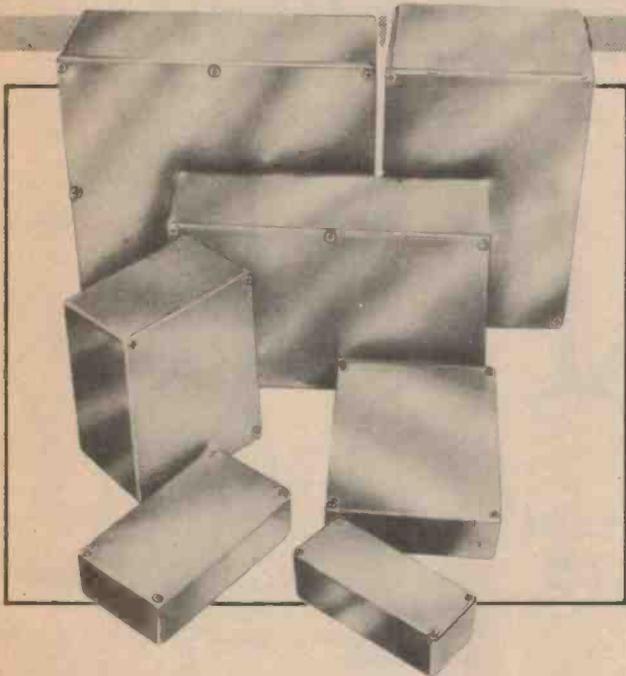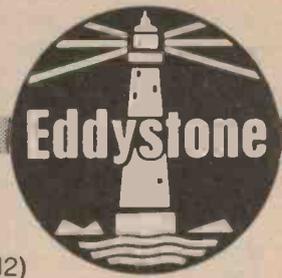
# BOX IT WITH EDDYSTONE DIECAST BOX FAMILY



The boxes are diecast aluminium alloy (B.S.1490 LM2) made to suit various applications such as: instrument and meter cases, filter network and cable distribution housings, switch containers, audio and radio frequency distribution and other screened requirements and external covers.

- Robust ● High screening properties
- Proportioned for maximum applications
- Sensible range of sizes ● Weatherproof ● Supplied unfinished and will accept any finish including cellulose.

Available from:


**R.H. Cunningham**  
Pty. Ltd.

and Electrical Wholesalers

Sydney 9092388 Perth 3283655  
Brisbane 525881 Melbourne 3299633

## UHF/CB Antennas Citizens Band radio

**CB410**  
High Performance mobile whip.  
Requires no tuning.  
Overall height 21"

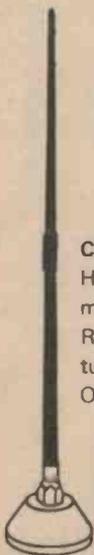

**CB470**  
6 dB gain co-linear base antenna.  
Enclosed in fibreglass radome.  
Length 8'.




**CB421**  
High Performance Dual Channel  
477 and 27 MHz mobile co-linear.  
Use with DX50 signal combiner  
overall height 42".



**DX50 Signal Combiner**  
For simultaneous reception  
and transmission on both  
27 MHz and 477 MHz.

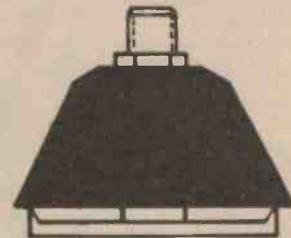Scalars UHF Mobile mount  
for correct termination of  
Co-Ax at UHF frequencies  
Pat. Pending No. 20506/76



Model OB

### SCALAR INDUSTRIES PTY LTD

TRADE  
ENQUIRIES  
WELCOME

VIC. 20 Shelley Avenue, Kilsyth, 3137. Tel: 725-9677. Cables: WELKIN. Telex: AA34341  
N.S.W. 20 The Strand, Penhurst, 2222. Telephone: 570-1392. Telex: AA27067  
QLD. Scalar (Qld.) P/L., 969 Ann St., Fortitude Valley, 4006. Tel: 52-2594. Telex: AA43007  
DESIGNED AND MANUFACTURED IN AUSTRALIA.




# predictions

## Ionospheric Predictions for the month of August


THESE PREDICTION GRAPHS have been prepared courtesy of the Ionospheric Prediction Service Division of the Department of Science. Any enquiries about these predictions should be directed to ETI, not to the Ionospheric Prediction Service.

The graphs indicate the maximum usable frequency (MUF) on HF circuits between various centres in Australia and selected points overseas.

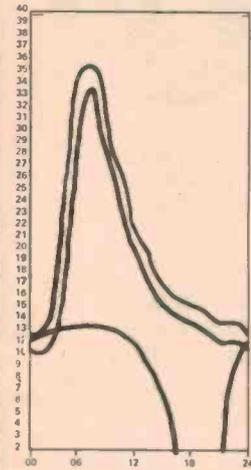
For less than 50% of the days of the month the highest frequencies propagated will be at least as high as the uppermost curve. Between 50% and 90% of the days of the month the MUF will be at least as high as the curve beneath the upper curve. The absorption limiting frequency (ALF), which affects the lowest frequencies that will be propagated, is indicated by the lower curves on the graphs.



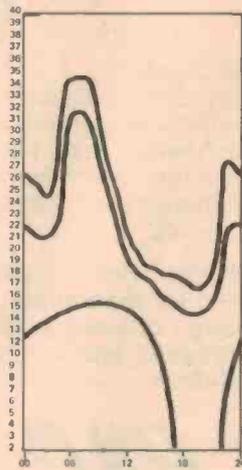
East Coast - South Africa (also serves South Central)



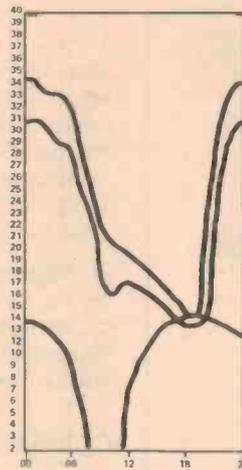
East Coast - North Africa (also serves South Central)



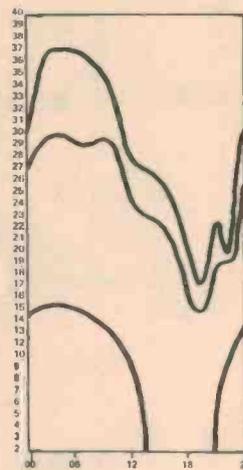
East Coast - South America (also serves South Central)



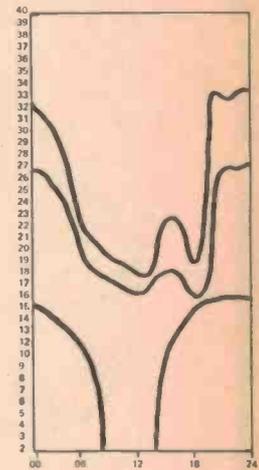East Coast - Central USSR (also serves South Central)




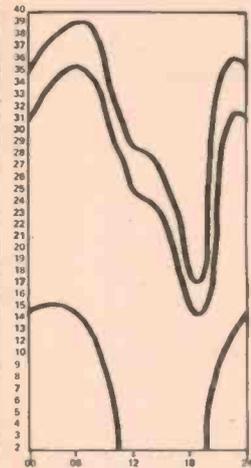East Coast - North America (also NE and South Central)




East Coast - Japan (also serves NE and South Central)


East Coast - South Pacific

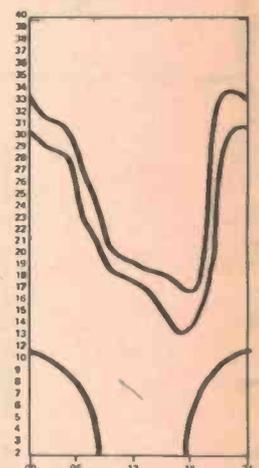


## SWL and AMATEUR COMMUNICATIONS

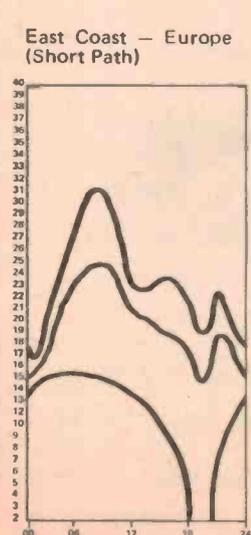


East Coast - Europe (Short Path)

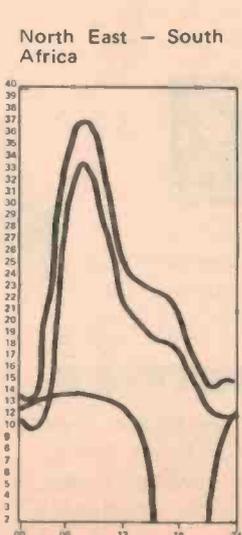


North East - South Africa

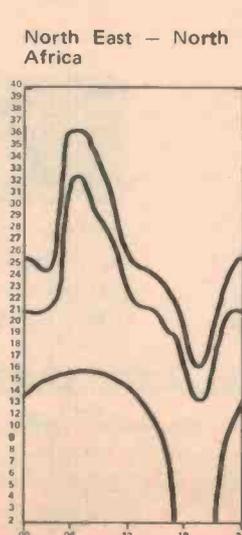

North East - North Africa

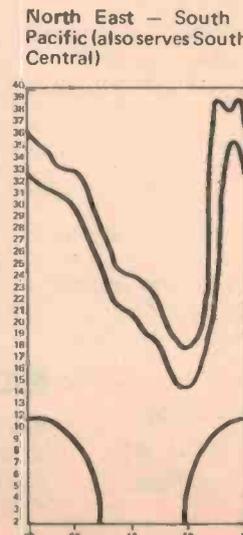

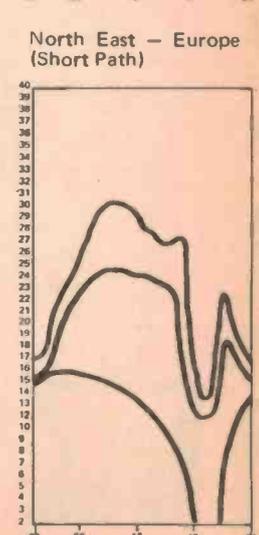North East - South Pacific (also serves South Central)




North East - Europe (Short Path)

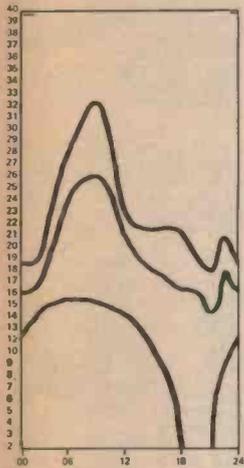
# WHERE IN MELBOURNE CAN YOU BUY




South Central — Europe  
(Short Path)(also West  
Coast)




West Coast — Japan

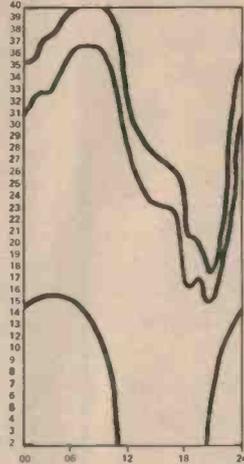


West Coast — North  
Africa

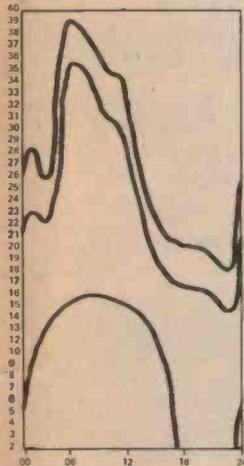


West Coast — North  
America

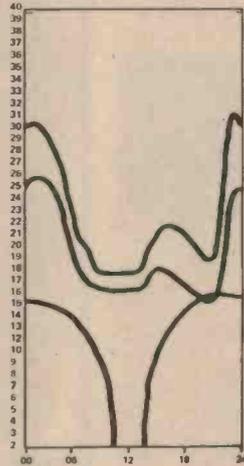

West Coast — Central  
USSR

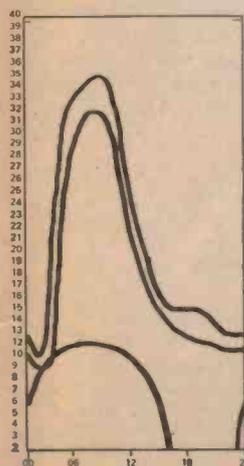

West Coast — South  
Africa

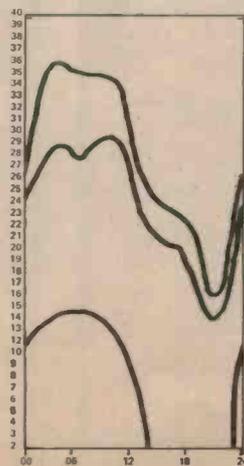

## SPECIAL OFFER

- Sinclair PDM35 Digital Multimeter .... \$62.50 ea. P&P \$2.50
- Arlec DMM10 Digital Multimeter ..... \$82.50 ea. P&P \$2.50
- Ferguson Husky 4 amp continuous battery charger..\$25.96 ea  
P&P \$5.
- Ferguson 13.8V 2A continuous CB power supply..\$30.00 ea  
P&P \$5.00
- Expo 3 way 8 ohm 25W speaker system..... \$80.00 pair.
- Expo 2 way 8 ohm 25W speaker system..... \$44.50 pair.
- Expo 2 way 8 ohm 10W speaker system..... \$30.00 pair.
- Expo 8 ohm stereo headphones..... \$6.75 pair.
- BSR auto turntables C/W base and cover ..... \$42.50 ea.
- 2 Station Intercom sets..... \$9.75 pair.
- 5 Bank Isostat switches C/W knobs ..... \$2.00 ea.
- 24V 5 digit electromechanical counters ..... \$2.00 ea.
- LM340 6v Voltage Regulators ..... \$1.00 ea.
- 400v 35 amp Bridge Rectifiers ..... \$3.50 ea
- Full Spec. 2N3055 ..... 90c ea.
- Full Spec. 2N3054 ..... 60c ea.
- Full Spec. PC208 (plastic 108)..... 15c ea.
- 4001 ..... 25c ea.
- P/B Micro Switches 250v 3 amp ..... 85c ea.
- Permeability Tuners, Broadcast ..... 75c ea.
- P.C.I. Project Boxes ..... \$4.15 ea.
- 240v Prim 115v sec. at 95vA ..... \$7.50 ea.
- 200v 1.2 amp Diodes ..... 10c ea.
- 50v 1 amp Diodes ..... 10c ea.
- 741 Op Amps ..... 40c ea.
- 555 Timers at 10 for ..... \$4.00 or 45c ea.
- 0A90 Diodes ..... 10c ea.
- BA217 — Similar IN914 Diodes..... 5c ea.
- Project Boxes from only ..... 60c ea.
- Resistors, 1/2 watt, all values ..... 3c ea.
- Disc Ceramic Capacitors, 1 pF to .2 uF  
..... 5c ea. (.47 uF 10c ea).
- 5 Watt Wirewound Resistors .47 ohm to 5.6 K ohm... 20 ea.
- BT100A 300v 4 amp S.C.R..... 60c ea.
- VU meters ..... \$2.50 ea.
- 12v AC 2 c/o 5 amp Contact Miniature Relays ..... \$1.50 ea.
- BC147, BC157, BF198, BF199, PN3694 ..... 10c ea.
- 500 mW Zener Diodes ..... 20c ea.

at 289 Latrobe St, Melbourne  
and at 297 Lt Lonsdale St, Melbourne, 3000.  
Phone 602-3282.

# ELLISTRONICS

WHERE JUST ABOUT EVERYTHING  
ELECTRONIC COSTS YOU LESS!



## ADVISORY SERVICE AND SPARE PARTS SUPPLIED TO TRADE

Full Service facilities for all communications equipment. CB radio, Stereo, and HiFi etc.



*Service facilities for  
trade and public*

# 419-3342

## ROAD RUNNER COMMUNICATIONS

39 Vere St, Collingwood 3066

# BRIGHT STAR CRYSTALS

ESTABLISHED FOR THE  
PAST 35 YEARS FOR  
★ ALL YOUR ★  
REQUIREMENTS

STILL ON TOP  
ELECTRONIC UNITS

● DECADE COUNTING UNITS TO 1 Hz ● WIDE BAND AMPLIFIER FOR your counter 1 MV sensitivity, band width 1-250 MHz.

DEVOTED EXCLUSIVELY TO  
THE MANUFACTURE OF  
PIEZO ELECTRIC  
CRYSTALS

Contractors to Federal & State  
Government Departments.



"All Types of Mountings"

### REPRESENTATIVES -

- |      |                                                                                             |
|------|---------------------------------------------------------------------------------------------|
| NSW  | Hose & Equipment Co.<br>Pty Ltd,<br>11 Salisbury St.,<br>Botany, 2019<br>Phone 666-8144     |
| S.A. | Rogers Electronics<br>P.O. Box 3,<br>Modbury North, S.A.<br>Phone: 42-6666                  |
| QLD  | Fred Hoe & Sons Pty Ltd,<br>246 Evans Road,<br>Salisbury North, Brisbane,<br>Phone: 47-4311 |
| W.A. | Communication Systems,<br>32 Rudlock Road,<br>Morley 6062<br>Phone 76-2566                  |
| TAS. | Dilmond Instruments,<br>P.O. Box 219,<br>Bellerive, Hobart, Tas.<br>Phone: 479-077.         |

*Send stamped addressed  
envelope for new catalogue or  
quote for your requirements.*

**BRIGHT STAR CRYSTALS P/L.**  
35 EILEEN ROAD, CLAYTON,  
VICTORIA, 546-5076

**UT UNIK TIME**  
presents:  
the world's thinnest  
DIGITAL TIMEPIECE



- Featuring:**
- 5 function, 4-digit quartz crystal accuracy Hour, minute, second, month, date
  - Super thin styling (6 mm) with 4 elegantly styled faces
  - Removeable battery hatch for easy customer battery replacement
  - Gold or silver toned case with lizard or mesh band options
  - High contrast, easy to read liquid crystal display with command backlight
  - Full year warranty with worldwide service

An ultra thin slice of time offering accuracy, comfort, elegant jewellery styling and long life. Supported by unexcelled quality and world-wide service. Ask your Unik Time representative about our full line of digital watches and clocks.

### CHRONOGRAPH Electronic LCD Digital Watch

6-digit 11 function chronograph  
Hour/Minute/Second/Month/Date/Day/  
Stop Watch (hour/minute/second/  
1/100 sec.)

OTHER MODELS OF  
UNIK TIME WATCHES  
AVAILABLE



## LED ELECTRONIC DIGITAL ALARM CLOCK

12 hour or 24 hour  
(Ideal for Hams) display.



**Features:** ● Stylish design ● Large bright LED display ● Colours: white, yellow, black, red. ● Tilted front panel, easy viewing ● Silent operation, all electronic ● Space age technology LSI circuitry ● Alarm ● 9 minute snooze time ● Seconds display ● Bright-dim control.

### Technical Data:

Power: AC Line source.  
Size: 105 mm wide x 115 mm deep x 55 mm high.  
Weight: 400 gm approx. (Net).


*Trade enquiries welcome*



Distributed by:  
**EMONA ENTERPRISES**  
CBC Bank Building, Room 208  
661 George Street, Sydney, 2000.  
Phone: Bus. 212-4815, AM 399-9061
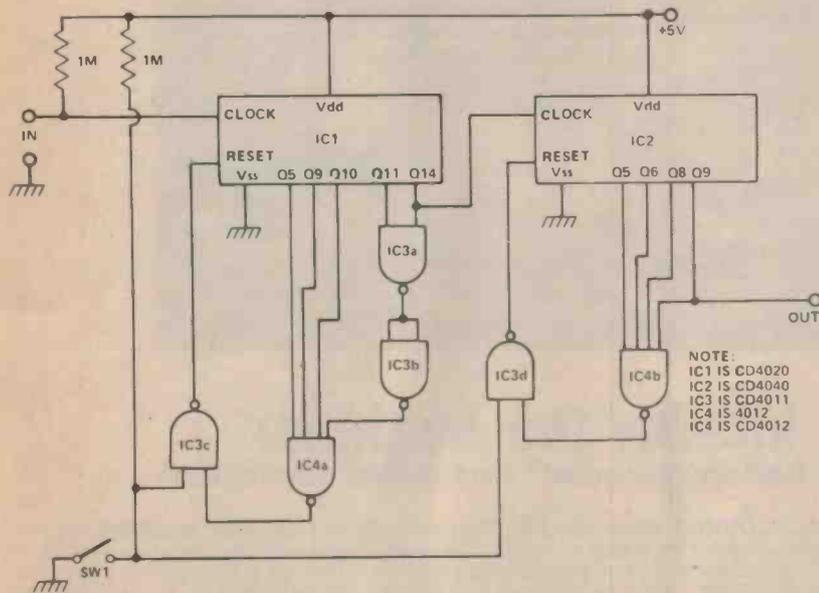
# Ideas for experimenters

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details. Electronics Today is always seeking material for these pages. All published material is paid for — generally at a rate of \$5 to \$7 per item.



## Divide by 4,320,000 Counter

So what is a 4320000 counter good for? Well,  $50 \times 60 \times 60 \times 24 = 4320000$  so that if you feed in 50 Hz at the input the counter will give 1 pulse per 24 hours, e.g. it can form the basis of an extremely accurate 24 hour alarm. Such an alarm never requires setting once the counter has been reset to zero at the required time of day and will thereafter give the alarm at exactly the same time every day. It can thus be used for instance to wake oneself up every morning without fail.

## Automatic Nicad Charger


The problem of ensuring that expensive Nicad cells are not damaged in the recharging process is twofold. First, as the cells have a low internal resistance, they are susceptible to damage by excessive charging currents. Second, damage will also occur if the charging process is carried out for too long a period.

The first problem may be overcome by charging at a constant current. The

second problem may be overcome by the use of an automatic sensing comparator circuit, which compares the voltage from the cells with a preset voltage, related to the fully charged value. In practical terms, the circuit appears as shown in Fig. 1. A red LED supplies the voltage drop to ensure that Q1 passes a constant current of about 25 mA to the cells under charge. This charging current may be adjusted, if

Such a circuit is very easily built using just 4 cheap CMOS chips, IC1, a 14 stage binary counter is set to divide by 10000 (binary 1001100010000) by resetting to 0 on the count of 10000. Similarly IC2, a 12 stage binary counter divides by 432 (binary 110110000). IC3 and IC4 provide the necessary decoding to reset the counters (which are reset by a logic '1' unlike TTL where a logic '0' is usually required). Additionally the gating allows the counter to be reset to 0 by SW1.

# BLOB BOARD

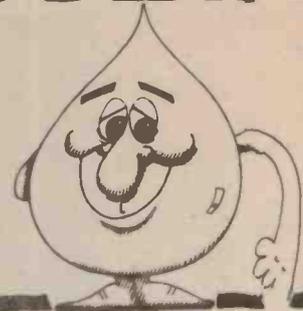

## for Digital Electronics by Experiment

Mr. Blob says: "The Technique of inserting components on one side of a board and soldering on the other is done for reasons which are now completely out of date; Namely this technique was established originally because heavy and bulky components were used. This no longer applies and has big disadvantages, the circuit is impossible to follow unless the board is continually turned over to inspect each side, its difficult to work on both sides of the board and soldering basically needs three hands. A common fault is to mount both leadout wires on the same track.

Blob — Boards give you the modern, low cost, easy to build circuits. Blob — Boards are roller tinned circuit boards on which each roller tinned copper track is identified by the letter and or number system. Simply tin the end of the component, butt the component lead against the roller tinned track, apply a blob of solder and the component is blobbed into place. All construction is from one side, component location could not be simpler, soldering is much easier, sub-circuits can be tested, then assembled together, the plain side of the Blob-Board is free and so the Blob-Board can be mounted flush on case walls. And they can be re-used. Simply apply a soldering iron to the Blob and remove the component."


**Now start Digital Electronics by Experiment.**

No need to lose your way round a circuit board that needs a layout drawing — Blob-Boards make construction easy. Blob-Boards have numbered tracks that make layout drawing out of date, the tinning ensures easy soldering, and the tracks don't strip off when you unsolder components. Blobbing components on to the tracks (no holes, no drilling) makes layout easy to follow. Use the 8-IC board for 'Digital Electronics by Experiment' in this Issue, but remember that we have "A Blob for every job".

Your nearest dealer?  
Write to:

**BLOB BOARD ASSOCIATES**  
P.O. Box 23, Surrey Hills,  
Vic. 3127 or ring (03) 89-1019.

# KITS for KIDS!

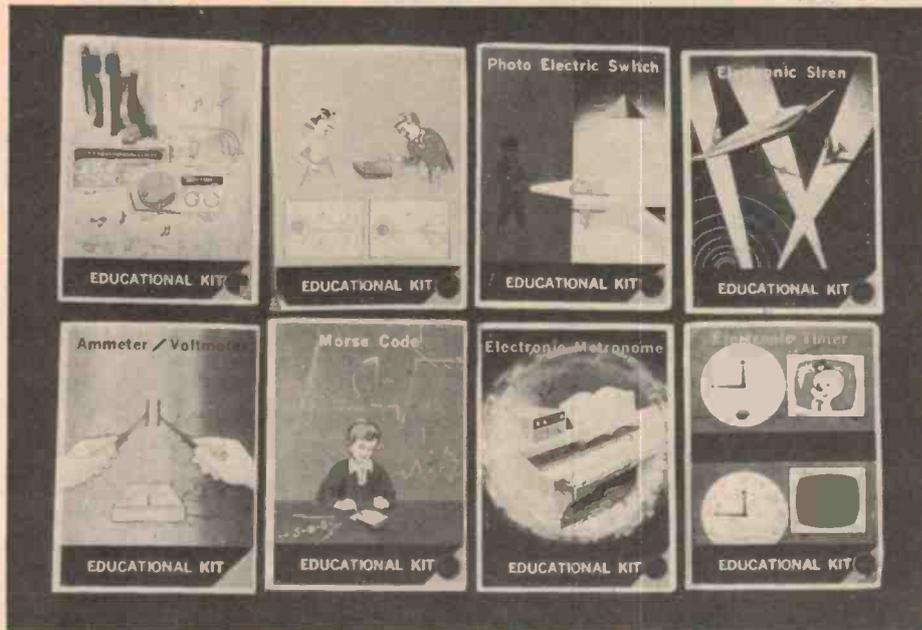

## Project kits for the beginner

Completely safe - battery operated\* - no mains connection

- A. ELECTRONIC ORGAN.** Unit has 11 note touch board complete with 2" speaker. Sounds good .....\$5.60
- B. ELECTRONIC FLASHER.** Complete with lamps, has many uses .....\$4.50
- C. ELECTRONIC SOUND SWITCH.** Uses small mic to pick up sounds, amplifies them and operates a lamp, many other uses .....\$4.50
- D. ELECTRONIC TOUCH SWITCH.** Has many uses. Use your finger to turn the circuit ON/OFF .....\$4.50
- E. ELECTRONIC DECISION MAKER.** A must for every home, used by Parliament and other official organisations ....\$4.50
- F. ELECTRONIC SLEEPING BELL.** Induces sleep by making soft sounds from a 2" speaker. The "sounds" represent rain .....\$4.50
- G. ELECTRONIC MAGIC TOUCH.** An ideal child's toy, develops concentration, good for parties etc. unit delivers tone if wand touches metal bridge - 2" speaker.....\$4.50
- H. ELECTRONIC RAIN ALARM.** This kit would better be called a "water" alarm. Unit has many uses in homes where the entry of water must be detected, use for bed wetting.....\$4.50
- I. PHOTO ELECTRIC SWITCH.** This project makes use of a CdS to automatically turn on a light when it is dark and turn it off when exposed to light-Similar to street lights.....\$4.50
- J. ELECTRONIC SINGING BIRD.** This kit produces the sounds of a nightingale. Easy to make, works well.....\$4.50
- K. MORSE CODE PRACTICE SET.** A must for all who want to obtain their Novice Amateur Licence. Kit gives clean crisp tone into 2" speaker.....\$4.90
- L. ELECTRONIC SIREN.** This kit simulates the actual sounds of an emergency vehicle. Push button controls output ..\$4.50
- M. ELECTRONIC WATER PURITY TESTER.** This kit allows the user to test the quality of water and compare it with salt water and other solutions. A must for students.....\$4.50
- N. TRANSISTOR RADIO.** Kit makes a simple one transistor radio with ferrite aerial, wire, earphone - Works well.....\$4.50
- O. ELECTRONIC METRONOME.** This kit is used by many music students to set a tempo to play against. Controlled tempo speed, very small, easy to hear - 2" speaker.....\$4.50
- P. AMMETER/VOLTMETER.** A very simple test set for measuring both voltages and current. Very good for testing these kits.....\$4.50
- Q. ELECTRONIC TIMER.** This simple device uses the principle of larger electronic timers to indicate that a given time has passed. Control allows for various times. Ideal for many home uses - Save on S.T.D. calls, boiling eggs etc.....\$4.50
- R. ELECTRONIC MOSQUITO REPELLER.** Unit emits a high frequency sound that drives mosquitos away. Ideal for campers and home - Simple to use...\$4.50
- S. ELECTRONIC POLICE CAR SIREN.** A real winner with all kids, small enough to use on bicycles, big 2" speaker for lots of "noise". A very popular kit .....\$4.90
- T. ELECTRIC FAN AND COLOUR WHEEL.** A fully controlled electric fan with speed adjustment. Kit contains small motor, fan blades, colour disc, and adjuster .....\$4.50

\*Batteries not included

## KIT BITS

110 Rosemead Road,  
HORNSBY, NSW. 2077.  
Phone (02) 476-3975.  
Trade enquiries welcome.

To: KIT BITS, 110 Rosemead Rd, Hornsby, NSW. 2077

Please send me Kit/s .....


I enclose Cheque/postal note for \$.....

NAME .....

ADDRESS .....

..... P/Code.....

# Ideas for experimenters

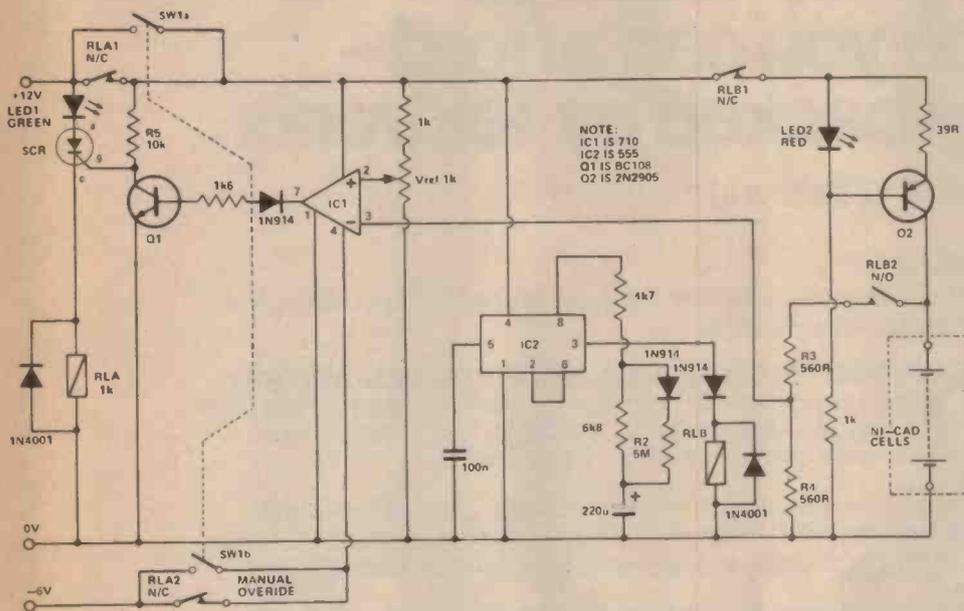

desired, by changing the value of R1. The 555 runs in the astable mode. However, the duty cycle is adjusted to be less than 50%, by incorporating a diode and resistor in parallel with R2. How this is accomplished may be easily understood if one remembers that charging of the capacitor takes place through these paralleled components, whereas, due to the blocking diode, discharging current only flows through R2. The 'off' time is around 15 mins. and the 'on' time less than 0.5s. The relay coil RLB, thus receives a positive pulse of short duration every 15 mins. Contact RLB1 opens, disconnecting the charging supply and contact RLB2 closes. A sample of the total voltage across R3 and R4 is applied to the

variable input of the 710 comparator. This input voltage is compared to the preset reference voltage and if found to be greater, the output will drop to -OV5 (from +3V2). The inverting action of Q2 causes the gate of the thyristor to undergo a positive transition, via R5. The gate causes the device to conduct, causing the contacts RLA 1 & 2 to open and disconnect the supply from the rest of the circuitry. The green LED is illuminated, indicating the termination of the charging period.


This circuit may be used to charge a total of six 1V5 cells. Of course  $V_{ref}$  may need adjustment so as to be commensurate with the voltage across R4. A manual override switch is also provided.

## Slide Switch

One of the disadvantages of slide pots is the unavailability of matching slide switches, as with rotary switches and pots, but slide pots can be given switching action by the use of this circuit.

Each analogue switch is only turned on when the comparators driving the respective EX-OR gate are in opposite states, i.e. when the voltage on the slider wiper is between the appropriate two preset voltages.

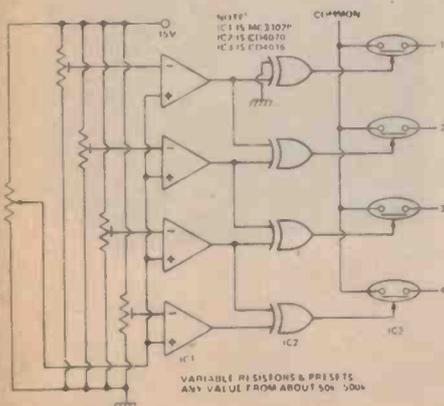The example is a 4-way, 1-pole switch with off but any-way, any-pole switches can be made, using 741s as comparators if economic. A little mechanical ingenuity can provide click stops, if required.



## Position Vacant PRODUCTION MANAGER

We are manufacturers of Australian-designed computers, and other electronic equipment for local and export market. We now need a person who will be responsible for production organisation, scheduling and quality control. Experience in all these areas is desirable.

As we are presently arranging to re-organise our production area in response to increased demand, it is desirable that the new Production Manager will be involved with these arrangements so that the best possible results may be obtained. Working conditions are comfortable and some flexibility is available regarding working hours. The ideal person will take considerable pride with the quality of goods leaving the factory and will be suitably remunerated through a generous bonus scheme.

Please phone Mr. Ryrrie,  
(02) 31-3606.

Fairlight Instruments  
Pty. Limited  
Rushcutters Bay, Sydney.

## BINDERS



Holds 12 copies of ETI

Protect and file back issues of ETI with these attractive binders.

Price \$4.50

(plus p&p 80c NSW, \$1.70 other states)

Subscription Dept, Electronics Today  
International, 3rd Floor, 15 Boundary  
Street, Rushcutters Bay, NSW. 2011.

# Performance features at a price you can afford— and fully backed by Tektronix

Only Telequipment offers you:

## TEKTRONIX GUARANTEE

The Telequipment family of oscilloscopes is fully guaranteed by Tektronix, the world's leading oscilloscope manufacturer.

## PERFORMANCE FEATURES YOU NEED AT A PRICE YOU CAN AFFORD

**Model D61a** Designed for portability and easy operation, the D61a is a dual trace 10 MHz scope. For easy, accurate viewing, the D61a features automatic triggering and bright stable waveforms on an 8 x 10 cm display.

**Model D83** A plug-in oscilloscope with a big display. The D83 sets high standards of performance, versatility and value. Plug-in options include 50 MHz dual trace at 5mV/div., single or delayed sweep and high gain differential.



**Model D32** When you demand an extremely portable scope, the D32 is ideal. Battery or ac line operated, this 10 MHz dual trace scope weighs only 10 lbs. An optional shoulder strap or attache carrying case can be used to take your scope into the field.

## IDEAL FOR MANY APPLICATIONS

If you're servicing pocket calculators, T.V., radio, microwave ovens, alarm systems or dozens of other consumer products, Telequipment scopes can do the job for you. Easy viewing and operating make Telequipment ideal for classroom use too.

**TELEEQUIPMENT...  
THE CHOICE FOR YOU**  
Performance features at a price you can afford, plus full backing by Tektronix make Telequipment a wise choice when you're looking for low-cost oscilloscopes.

**Tektronix**  
COMMITTED TO EXCELLENCE

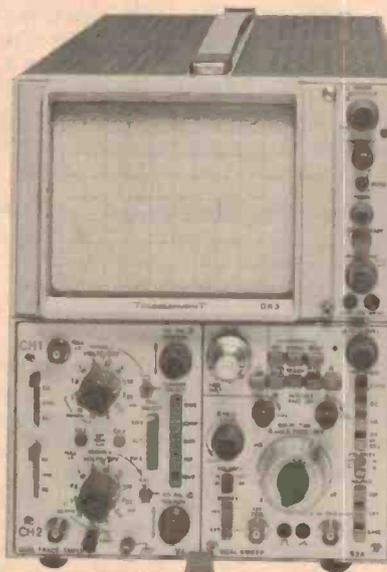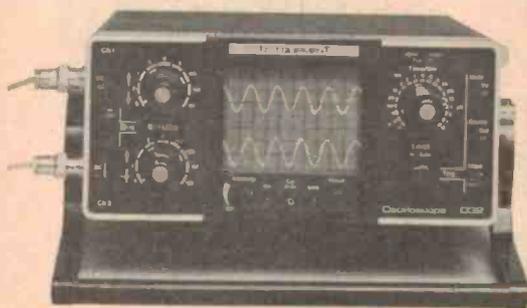


For more information about Telequipment oscilloscopes, contact  
**Tektronix Australia Pty. Ltd.**, 80 Waterloo Road, North Ryde 2113.  
Sydney 888 7066, Melbourne 818 0594, Brisbane 31 2896,  
Adelaide 223 2811 Perth 325 4198.

# Ideas for experimenters
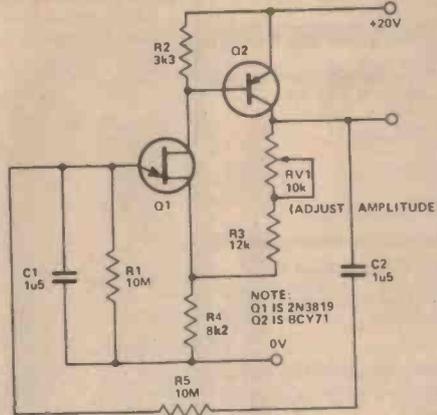
## VLF Sine Generator

Generating very low frequency sine waves (i.e. less than 0.1 Hz) presents several problems. Timing capacitors usually have to be large valve electrolytics, any amplifier used must be D.C. coupled, and the amplifier's input impedance must be very high. One standard method is to first generate low frequency square waves, and then to shape these into an approximation of a sine wave by the use of several non linear devices, such as diodes. The circuit shown in Fig. 1 is a relatively simple approach based on the familiar Wien bridge. An n-channel FET and a pnp transistor are arranged in a DC coupled circuit and the voltage gain is determined by the negative feedback R3 and R4. The gain need only be about three, thus if the bias required by the FET is 3V the output level will be approximately half the supply voltage.

Since R1 can be a high value resistor the value of the capacitor is only 1u5




for sine wave outputs of 0.01 Hz. This capacitor is available in polycarbonate. The amplitude of the output can be adjusted by RV1 to give low harmonic distortion and to be about 10V peak to peak. As expected, with this Wien bridge circuit, frequency stability is good with changes in both supply voltage and temperature.

## Voltage Stabiliser

Here is a voltage stabiliser with good performance and low component count which will operate well, even when  $V_{in} - V_{out}$  drops to 2 V. Only a few milliamps are dissipated through the zener, making it suitable for battery operated equipment.

Most circuits of this type (but with the FET replaced by a resistor) suffer from zener saturation when  $V_{in}$  is getting low, or in excessive zener current when  $V_{in}$  is high.

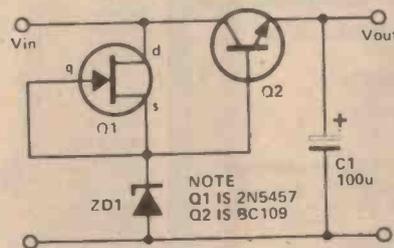Actual component values can be varied to suit individual applications.



## 3-way CMOS switch


When the input is switched positive the voltage across the zener is sufficient to bias the junction between R3 and the zener high, producing a high output at C.

With the input unconnected, the junction between R1 and R2 is high while the junction between the zener

and R3 is low. This will produce a high output at B.

Connectin the input to 0V causes output A to go high.

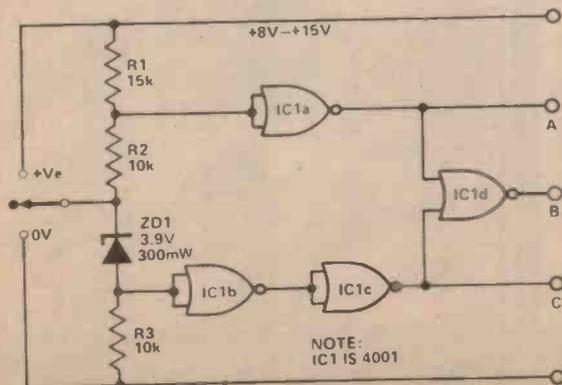The circuit was primarily designed to be used with quad CMOS switches (i.e. 4016, 4066) for audio switching but can be used for a variety of applications.




Available from leading Electronic Stores  
**PARAMETERS LTD**  
 Sydney: 439 3288 Melbourne: 90 7444  
 #PM86

### SG402 R.F. Signal Generator

- Covers frequencies from 100 kHz to 30 MHz in six ranges as a versatile wide band signal generator
- The output voltage 0.1V rms min., is continuously variable with an incremental attenuator switch and fine control
- Either internal or external modulation may be switch selected
- Compact, lightweight construction and unique control arrangement make the instrument easy to use
- All solid state circuitry assures stable operation
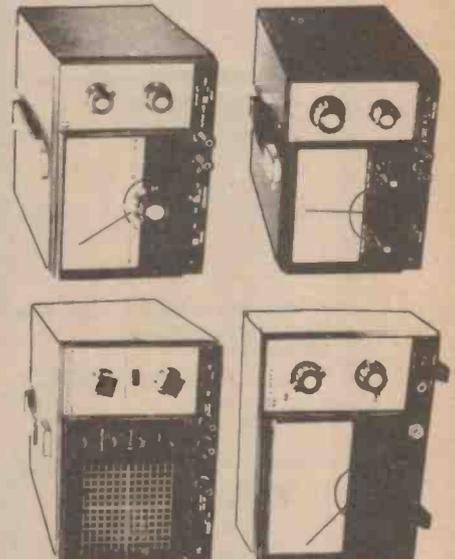
### AG202A CR Oscillator

- A single-scale dial directly reads oscillator frequency ranging from 20 Hz to 200 kHz on four bands
- Output voltage of 10V rms at maximum can be attenuated to -20 dB and -40 dB with a front panel attenuator. It also can be continuously varied with a smooth dial knob
- Compact and lightweight. The scale is easy to read with a smooth dial knob
- An external sync. input connector allows output frequency to synchronize with more accurate external signal
- A front panel switch selects either low distortion sine wave or sharp rising square



# TRIO TEST INSTRUMENTS

## CO1303D 5MHz Single Trace Oscilloscope

- A high vertical sensitivity of 10 mV/div and a wide bandwidth of DC to 5 MHz make the CO-1303D a versatile all-purpose instrument
- Its vertical and horizontal DC amplifiers permit observation in a variety of applications particularly at very low sweep rates below 1 Hz
- A direct-coupled vertical deflection allows observation of waveforms up to 450 MHz
- External synchronization assures you of a more stable waveform observation

## VT108 Volt-Ohm Meter

- Measures DC voltages 0 to 1500V, AC voltages 0.1 to 1500V r.m.s., and resistances 0.1Ω to 1000 MΩ
- All solid state circuitry including FETs, makes the instrument compact and lightweight. Handy enough to be brought to any location where electrical measurements are made. Unique appearance with controls arranged for maximum ease
- Only four "C" size batteries assure one month, or longer, service
- A measured value can be stored for a moment for later reading
- The bandwidth is as wide as 15 Hz to 5 MHz





Call your Air Force Careers Officer now. For a whole new lifestyle. Brisbane: 226 2626. Townsville: 71 3191. Sydney: 212 1011. Newcastle: 2 5476. Wollongong: 28 6492. Wagga: 21 1100. Canberra: 82 2333. Melbourne: 61 3731. Hobart: 34 7077. Adelaide: 223 2891. Perth: 325 6222 or write to the Air Force Careers Officer, G.P.O. Box XYZ in your nearest capital city.

Name .....

Address .....

Date of Birth .....

State .....

AFAC64.FP.38



Today's Air Force.

**Become an Air Force pilot, navigator, or air electronics officer and you've got one of the most satisfying jobs in the sky. And a flying start on any management career on earth.**

## READERS' LETTERS

No charge for replies but a foolscap-size stamped addressed envelope must be enclosed. Project queries can only be answered if related to item as published. We cannot assist if project is modified nor if components are otherwise than specified. We regret we cannot answer readers' enquiries by telephone.

## SUBSCRIPTIONS AND BACK ISSUES

ETI subscriptions cost \$17.00 per year (inc. postage) within Australia. Cost elsewhere is \$17.65 (inc. postage - surface mail). Airmail rates on application.

Back issues cost \$1.25 (Sept. onwards) each plus post and packing.

We can supply only the following issues.

1976: Nov., Dec.

1977: All issues except Jan, Feb, March.

Photostats are available of any article ever published in ETI. We charge a flat \$1.00 regardless of page quantity from any one issue of ETI. Thus if the article is in three issues the cost is \$3.00. Send orders to address below.

Binders \$4.50 plus 80c post NSW, \$1.70 other States.

## COPYRIGHT

The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

## LIABILITY

Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

## A MODERN MAGAZINES PUBLICATION

Managing Director: Arnold Quick  
Secretary: Charles O'Leary  
Publisher: Collyn Rivers

## PRODUCTION

Art Director: Jim Hattersley  
Assembly: Bill Crump  
Production Manager: Bob Izzard  
Subscriptions & Circulation: John Oxenford  
Project Design: Nebula Electronics  
Acoustical Consultants: Louis A Challis & Assoc.

## ADVERTISING

**Sydney:** Bob Taylor (Manager), Geoff Petschler (NSW Manager), 15 Boundary St., Rushcutters Bay 2011. Tel: 33-4282.  
**Melbourne:** Tom Bray (Manager), Poppe Davis, Suite 24, 553 St. Kilda Rd, Melbourne. Tel: 51-9836.  
**Brisbane:** Geoff Horne, 60 Montanus Drive, Bellbowrie, Qld. 4070. Tel: 202 6229.  
**Adelaide:** Tony James, 16 Montrose Ave, Netherby. 5062. Tel: 79 4740.

**Perth:** Aubrey Barker, 133 St. George's Terrace, Perth. 6000. Tel: 322 3184.  
**Hobart:** H.W. Lincone, 23 Lord St, Sandy Bay, Tasmania. 7005.  
**Tokyo:** Genzo Uchida, Bancho Media Service, 15 Sanyocho, Shintoku-Ku, Tokyo 160.  
**London:** Electronics Today International, 25-27 Oxford St, London, W1R 1RF. Tel: 01-434-1781/2.  
**U.S.A.:** Elmatex International, PO Box 34607, Los Angeles, CA. 90034. Tel: (213) 821 8581. Telex: 18 1059 (Elmatexint USA)

# Advertisers Index:

|                               |                |
|-------------------------------|----------------|
| Abacus EDP Services           | 104            |
| Advanced Computer Products    | 136            |
| Ampex                         | 19, 20-21      |
| Applied Technology            | 96-97          |
| A & R Sonar                   | 44, 110        |
| Audio Engineers               | 6              |
| Aust. General Electric        | 91             |
| Automation Statham            | 103            |
| Bail Electronics              | 92             |
| Blob Board                    | 131            |
| Bright Star Crystals          | 130            |
| BSR                           | 10, 11         |
| Cema                          | 40             |
| Centaur Industries            | 59             |
| Convoy                        | 18             |
| Data Aids                     | 111            |
| Daved                         | 31             |
| Defence Recruiting            | 137            |
| Delsound                      | 60             |
| Dick Smith                    | 32, 54-55, 124 |
| Diggerman                     | 82             |
| Douglas Transformers          | 82             |
| Eastern Electronic Comp       | 92             |
| Eclipse Lighting              | 123            |
| EEE                           | 44             |
| Electrocraft                  | 59             |
| Ellistronics                  | 129            |
| Emona                         | 38, 130        |
| Fairlight Instruments         | 133            |
| Friedman Electronics          | 81             |
| General Electronic Services   | 111            |
| Hagemeyer                     | 2, 139         |
| Harman Aust.                  | 16             |
| Harmonix Acoustix             | 14             |
| IC's Unlimited                | 100            |
| Impact                        | 98             |
| Instant Component Service     | 122, 123       |
| Inter. Correspondence Schools | 45             |
| Jaycar                        | 60             |
| JR Publications               | 11             |
| Kit Bits                      | 132            |
| Leroya                        | 33             |
| Mailman Electronics           | 92             |
| Microcontrol                  | 111            |
| Misc Distillery               | 115            |
| National Panasonic (Aust) P/L | 140            |
| Nessall Audio                 | 19             |
| Non Linear Systems            | 48             |
| Parameters                    | 135            |
| Pennywise Peripherals         | 82             |
| Philips                       | 25             |
| Philips Elcoma                | 84             |
| Pre Pak                       | 49             |
| Radio Parts                   | 93             |
| R.H. Cunningham               | 127            |
| Roadrunner                    | 130            |
| Rod Irving                    | 58             |
| Rothmans                      | 116            |
| Scalar Industries             | 127            |
| Scope Labs                    | 119            |
| Semcon                        | 81             |
| S.M. Electronics              | 123            |
| Sounding Distributors         | 12             |
| Superscope                    | 23             |
| Tandy                         | 83             |
| Tech. Book & Mag. Co.         | 19             |
| Tektronix                     | 8, 134         |
| Trio-Kenwood                  | 121            |

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St., Rushcutters Bay NSW 2011. It is printed (in 1978) by Wilke & Co., Browns Rd, Clayton, Victoria and distributed by Australian Consolidated Press.


# FILL OUT THIS COUPON AND WE'LL SEND YOU 30 NEW WAYS TO ENJOY HI-FI


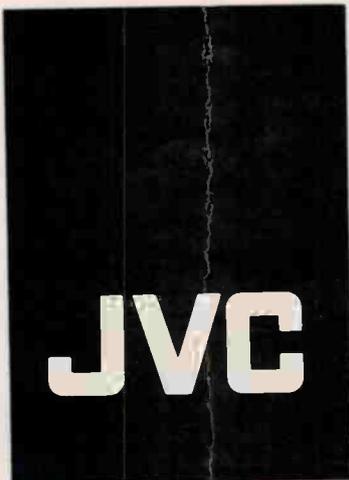
## FREE! COLOUR HI-FI CATALOGUE

JVC have just released 30 new Hi-Fi products.  
And how many companies in this magazine can make  
that statement?

It's worthy to note that these new JVC Hi-Fi Products are not just a design or cosmetic change, but are the culmination of years of research and development. Resulting in innovations and performance features such as:— Quartz locked turntables with uncanny accuracy; Receivers/Amplifiers, some with built in SEA Graphic Equaliser and DC, class A/B amplification. Cassette decks with the revolutionary Spectro Peak Indicators; Computer designed speaker systems; Separate but matching components designed to complement one another, perfectly. In fact, the finest JVC audio range ever produced.



Altogether you'll find out what's available and new in terms of JVC Hi-Fi enjoyment.

And all this know-how is yours... merely for the asking.

Just fill out this coupon and we'll fill you in...

Name .....

Address .....

..... Post Code .....

ET1

I am especially interested in...

- |                                           |                                     |
|-------------------------------------------|-------------------------------------|
| <input type="checkbox"/> Cassette Decks   | <input type="checkbox"/> Speakers   |
| <input type="checkbox"/> Amplifiers       | <input type="checkbox"/> Turntables |
| <input type="checkbox"/> Matching Systems | <input type="checkbox"/> Receivers  |

WT51/78

the right choice

ADDRESS YOUR ENVELOPE TO... JVC ADVISORY SERVICE, POST OFFICE BOX 49, KENSINGTON, N.S.W. 2033

Pro. Series



**RS-9900US.  
Two components  
for one reason:  
To outperform  
all other  
cassette decks.**

Audio enthusiasts the world over have come to expect exciting innovations from Technics. The RS-9900US is one of them. Unlike other cassette decks it is a 'cassette system'—the separation of the sensitive amplifier electronics from the mechanical tape transport to obtain optimum performance from each.

Features in the transport unit include a closed loop, double-capstan, 3-motor drive to provide smooth tape travel and closest tape-to-head contact; pitch control of  $\pm 5\%$  and full IC logic control of all transport functions to ensure tape safety when switching modes. The true 3-head system permits professional-type tape/source monitoring.

Outstanding among the amplifier unit's many features is the fixed plus variable calibration controls for equalisation lines, and Dolby\* record and playback levels. Complete with peak reading meters of studio standards, Dolby\* noise reduction circuitry and a built-in 400Hz/8kHz test oscillator for level calibration and head azimuth adjustments.

An evaluation of the Technics RS-9900US capabilities will provide the answer to any contradictions about cassette equipment performance.

\*Under licence from Dolby Laboratories Inc.

 **Technics**  
hi-fi