

JANUARY 1984 \$2.35\* NZ\$2.75



**ELECTRONIC  
TODAY  
INTERNATIONAL**

**SPECIAL OFFER!**  
**Hewlett Packard Logic Probes**  
B-ETI TERMINAL OFFER EXTENDED

# CIRCUIT SOURCE GUIDE

*16 page special supplement*

**FREE CALENDER  
CHECK INSIDE**

**MICROBEE  
PROGRAM  
POTPOURRI**


**TO BUILD:**

**Microprocessor  
bug debugger**

**For tennis fans  
electronic 'let' caller**

**Serial-parallel interface**

**HI-FI: \$399 B&W  
speakers reviewed**

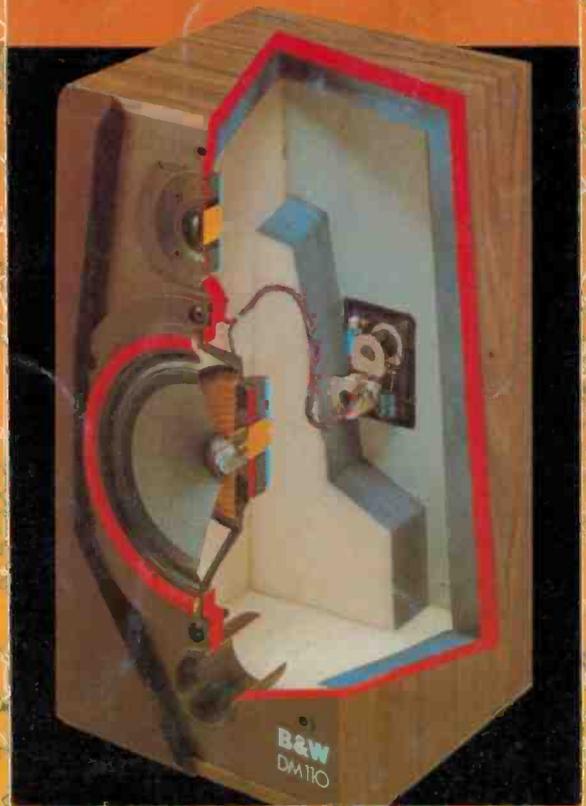


**JAPAN AUDIO & ELECTRONICS SHOWS REVIEWED**

# NOW! ALL-IN-ONE RECORD CLEANER
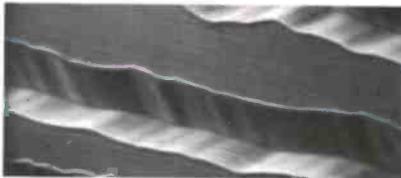
## RC5 PLUS™




Made in U.S.A. exclusively for  
Stanton Magnetics, Inc. Plainview,  
N. Y. 11803 by Record Care, Inc.



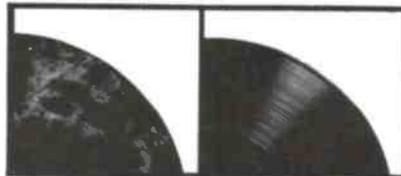
### Cleaner

RC5 Plus contains a specially formulated cleaning fluid which safely dissolves oily film, loosens microdust and other debris from the record groove and leaves no residue.


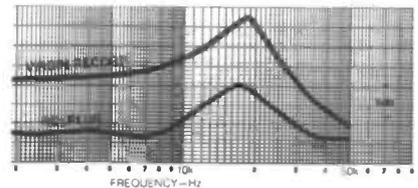
### Anti-Static Property

RC5 Plus liquid contains an antistatic ingredient that removes the static charges from a record. The result — clean records stay cleaner because dust is not attracted to the record surface.



### Noise Reduction

The result of the above two features allows for a quieter record as measured by the Real Time Analyzer. Even a virgin record fresh from the sleeve can be quieted by the application of RC5 Plus.

### "Polarized" Brush and Conductive Handle

The RC5 specially designed brush is directional for best dust debris removal. The conductive handle aids in drawing static charges away from the record. RC5 properly used cleans 150 records, both sides.

## SOUNDINDEX

Pty. Ltd. importers & wholesalers of audio equipment

**STANTON**  
THE CHOICE OF THE PROFESSIONALS

Head Office: 82 Colin Street, West Perth, Western Australia 6005. Telephone (09) 322 2854 Telex AA93241  
NSW Office: 7 Jordan Road, Wahroonga, NSW 2076. Telephone (02) 487 2543.

## EDITOR

Roger Harrison VK2ZTB

## ASSISTANT EDITOR

Jennifer Whyte B. App. Sc.

## EDITORIAL STAFF

Geoff Nicholls B.Sc./B.E.

Jane Hodson

## ASSOCIATES

David Tilbrook VK2YMI

Jonathan Scott

B.Sc./B.E. (Hons) VK2YBN

## DRAUGHTING

David Currie

## PRODUCTION

Steve Landon

Mark Davis

## ADVERTISING SALES

Bob Taylor (Group Manager)

John Whalen (National)

Steve Collett

## ART STAFF

Ali White B.A.

Bill Crump

Dean Shirley

## READER SERVICES

Carmel Gatt

## ACOUSTICAL CONSULTANTS

Louis Challis and Associates

## HEAD OFFICE

140 Joynton Avenue, (PO Box 227)

Waterloo, NSW 2017.

Phone: (02) 663-9999 Sydney.

Telex: 74488, FEDPUB.

## ADVERTISING OFFICES

### AND AGENTS:

Victoria and Tasmania: Virginia Salmon and Mel Godfrey, The Federal Publishing Company, 23rd Floor, 150 Lonsdale Street, Melbourne, Vic. 3000. Phone: (03) 662-1222 Melbourne. Telex: 34340, FEDPUB.

South Australia and Northern Territory: The Admedia Group, 24 Kensington Road, Rose Park, SA 5067. Phone: (08) 332-8144 Adelaide. Telex: 82182, ADMEDIA.


Queensland: Geoff Horne Agencies, 16 Bellbowrie Centre, Bellbowrie, Qld 4070. Phone: (07) 202-6813 Brisbane.

Western Australia: Cliff R. Thomas, Adrep Advertising Representative, 62 Wickham Street, East Perth, WA 6000. Phone: (09) 325-6395 Perth.

New Zealand: Chris Horsley, 4A Symonds Court, Symonds Street, Auckland. Telex: 260753, TEXTURE.

Britain: Peter Holloway, John Fairfax and Sons (Australia) Ltd, Associated Press House, 12 Norwich Street, London EC4A 1BH. Phone: (01) 353-9321 London. Telex: 262836, SMHLDN.

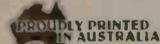Japan: Genzo Uchida, Bancho Media Services, 5th Floor, Dai-ichi Nisawa Building, 3-1 Kanda Tacho 2-chome, Chiyoda-ku, Tokyo 101. Phone: (03) 252-2721 Tokyo. Telex: 25472, BMSINC.



## ELECTRONICS TODAY INTERNATIONAL

is published monthly by the Electronics Division of the Federal Publishing Company Pty Limited, 140 Joynton Avenue, Waterloo, NSW 2017. Managing Editor: Bob Izzard. Typeset and printed by ESN-The Litho Centre, Sydney. Distributed by Gordon and Gotch Limited, Sydney. Cover price \$2.35 (maximum and recommended Australian retail price only; recommended New Zealand price, \$2.75). Registered by Australia Post, Publication No NBPO407. ISSN No 0013-5216.

COPYRIGHT © 1984, THE FEDERAL PUBLISHING COMPANY

## FEATURES

NEWS DIGEST .....	8
JAPAN ELECTRONICS SHOW .....	12
SPECIAL OFFER HEWLETT PACKARD LOGIC PROBES .....	16
SPECIAL OFFER THE 'BETI' TERMINAL .....	77
CIRCUIT SOURCE GUIDE .....	99

## SIGHT & SOUND

SIGHT & SOUND NEWS .....	18
ALL JAPAN AUDIO SHOW .....	20
B & W DM110 LOUDSPEAKERS REVIEWED .....	23

## COMPUTING TODAY

SOFTWARE NOT COPYRIGHT .....	31
COMPUTING TODAY NEWS .....	32
COMX 35 COMPUTER REVIEWED .....	45
PROJECT 675 MICROBEE SERIAL-PARALLEL INTERFACE .....	52
MICROBEE PROGRAM POTPOURRI .....	58
COMPUTER CLUB LIST .....	63
UPGRADING THE '668 EPROM PROGRAMMER .....	69
VIC-20 COLUMN .....	72
'660 COLUMN .....	74
ZX COLUMN .....	76
SPECIAL OFFER THE 'BETI' TERMINAL .....	77

## TECHNICAL

SPECIAL OFFER HEWLETT PACKARD LOGIC PROBES .....	16
EQUIPMENT NEWS .....	79
COMPONENT NEWS .....	85
PROJECT 656 PROGRAM BUG DEBUGGER .....	89
PROJECT 273 LET CALLER .....	95
CIRCUIT SOURCE GUIDE .....	99
SAW DEVICES, PART 2 .....	118
IDEAS FOR EXPERIMENTERS .....	125
IDEA OF THE MONTH .....	129
SHOPAROUND .....	135

## COMMUNICATIONS

COMMUNICATIONS NEWS .....	136
LOADED AND TRAP DIPOLES .....	139

## GENERAL

COMMENT .....	5
ADVERTISERS' INDEX .....	5
MAIL ORDER BOOKS .....	65
LETTERS .....	143
MINI-MART .....	145
DREGS .....	146

**COPYRIGHT:** The contents of *Electronics Today International* and associated publications is fully protected by the Commonwealth Copyright Act (1968). Copyright extends to all written material, photographs, drawings, circuit diagrams and printed-circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by bands (for example) constructing one or more items for use in connection with their performances. Commercial organisations should note that no project or part project described in *Electronics Today International* or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publisher, The Federal Publishing Company, or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

**WE are a No.1 Kit Supplier**

**Build One During Your Holidays**



# SERIES 5000

**PRICES SLASHED**

As designed by ETI

## PREAMPLIFIER

**PRICES SLASHED**  
this month only

Save \$10 as a Xmas bonus

~~\$269~~  
**\$259**

### SPECIFICATIONS

Frequency response: High-level input: 15Hz-130 kHz, +0, -1 dB Low-level input — conforms to RIAA equalisation, ±0.2 dB  
Distortion: 1kHz <0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation).  
S/N noise: High-level input, master full, with respect to 300 mV input signal at full output (1.2V): >92 dB flat > 100 dB A-weighted.  
MM input, master full, with respect to full output (1.2V) at 5 mV input, 50 ohm source resistance connected: >86 dB flat >92 dB A-weighted.  
MC input, master full, with respect to full output (1.2V) and 200 µV input signal: >71 dB flat >75 dB A-weighted.



## POWER AMPLIFIER

Over 500 sold

Please note that the "Superb Quality" Heatsink for the power amp was designed and developed by Rod Irving Electronics and is being supplied to other kit suppliers. This product cost \$1,200 to develop so that your amplifier kit would have a professional finish as well as sound. We also have a new range of rack mounting boxes which will be released soon.

### SPECIFICATIONS

Power output: 100W RMS into 8 ohms (±55 V supply).  
Frequency response: 8 Hz to 20 kHz, +0-0.4 dB 2.8-Hz to 65 kHz, +0-3 dB. NOTE: These figures are determined solely by passive filters.  
Input sensitivity: 1V RMS for 100W output.  
Hum: -100dB below full output (flat).  
Noise: -116 dB below full output (flat, 20 kHz bandwidth).  
2nd harmonic distortion: <0.001% at 1 kHz (0.0007% on prototypes) at 100 W output using a ±56 V supply rated at 4 A continuous. <0.003% at 10 kHz and 100 W.  
3rd harmonic distortion: <0.0003% for all frequencies less than 10 kHz and all powers below clipping.  
Total harmonic distortion: Determined by 2nd harmonic distortion (see above).  
Intermodulation distortion: <0.003% at 100 W. (50 Hz and 7 kHz mixed 4:1).  
Stability: Unconditional



**Price Slashed**  
~~\$309~~ **\$299**

## THIRD OCTAVE GRAPHIC EQUALIZER

Over 200 sold

**SPECIFICATIONS E.T.I. Dec. 1982**  
Bands: 28 Bands from 31.5 Hz to 16 kHz  
Noise: <0.008 mV, sliders at 0, gain at 0 (-102 dB),  
20 kHz bandwidth  
Distortion: 0.007% at 300 mV signal, sliders at 0, gain at 0;  
max. 0.01%, sliders at minimum.  
Frequency Response: 12 Hz-105 kHz, +0, -1 dB, all controls flat  
Boost & Cut: 14 dB



**1 unit \$195**  
**2 units \$379**  
**Assembled & Tested \$325**

## MX-1200 MICROPHONE/AUDIO MIXER

Over 100 sold



**MX 1200 \$659 this month only**

**XMAS SPECIAL \$659**

**RRP \$759**

This unit features: 12 microphone line inputs with pan, bass, treble, effect and fold back controls for each channel • LED peak indicators for each channel • 2 turntable inputs with cross-fade and individual output controls • master equaliser for bass, midrange and treble • variable headphone output etc. etc. • complete with carrying case.

**SPECIFICATIONS:**  
INPUTS  
Line 22 dB/15K ± 12  
Phono 32 dB/50K STEREO × 2 (2mV) at 1kHz  
Effect Return (Aux) 20 dB/50K × 1  
OUTPUTS  
Level/Impedance L & R 0 dB/2K  
Effect Send 0 dB/2K FR Out 0 dB/2K  
Headphone Stereo -10 dB/100 (100-1K)  
EQUALISATION  
Channel  
Bass ±15dB  
Treble ±15dB  
Master  
Bass ±12dB  
Treble ±10dB  
Middle ±12dB

**FADER & CONTROLLERS**  
12 channel fader: Slide 60mm LOG 25%  
2 Master fader: Slide 60mm LOG 15%  
12 FB Volume, 300 LIN  
1 FB Master level, 300 LIN  
12 Effect Send, 300 LIN  
1 Effect Return, 300 LOG 15%  
2 Phono, 300 LOG 15%  
1 Head Phone, 300 LOG 15%  
S/N, 58DB  
FREQUENCY RESPONSE: 20-20 KHZ  
TOTAL HARMONIC DISTORTION: Less than 0.1%  
METER 2 illuminated VU Meters 0db = 0.775V  
PEAK INDICATOR: 12 LED Peak Indicators  
VOLTAGE: 240 VAL 50Hz  
POWER CONSUMPTION: 7.2 watts  
DIMENSIONS: 520 (W) × 145 (D) × 108 (H) mm (supplied complete with carrying case)

### Hand Built Units

#### EXTRA FEATURES OF OUR KITS

- POWER AMPLIFIER**  
KIT PRICE \$299 P&P \$8.00
- 1% Metal Film Resistors are used where possible
  - Prewound Coils are supplied
  - Aluminum case as per the original article
  - All components are top quality
  - Over 200 Kits now sold
  - We have built this unit and so know what needs to go into every kit.
  - SUPER FINISH Front panel supplied with every kit at no extra cost to you
  - We are so confident of this kit that we can now offer it assembled and tested so that people who do not have the time can appreciate the sound that this amplifier puts out. This is done on a per order basis delivery approx. two weeks after placement only \$425
- \* All parts available separately for both kits*

#### PREAMPLIFIER

- KIT PRICE \$259 P&P \$8.00
- 1% Metal Film Resistors are supplied
  - 14 metres of Low Capacitance Shielded are supplied (a bit extra in case of mistakes)
  - English "Lorin" Switches are supplied no substitutes as others supply
  - We have built and tested this unit and so know what needs to go into every kit
  - Specially imported Black anodised aluminum knobs
  - Again as with the power amp we are offering this kit A & T at a price which we do not believe there is a commercial unit available that sounds as good. Same delivery as the PA only \$425

No. \_\_\_\_\_  
Expiry Date \_\_\_\_\_  
Name \_\_\_\_\_  
Signature \_\_\_\_\_

Bankcard mail orders welcome  
Please Debit my Bankcard

**ORDER FORM**



## ROD IRVING ELECTRONICS

425 High St., Northcote, Vic. 48-50 A'Beckett St., Melb., Vic.  
Phone (03) 489 8866, (03) 489 8131, Mail Order Hotline (03) 481 1436  
Mail orders to P.O. Box 235 Northcote 3070 Vic.  
Minimum P & P \$3.00. Errors & omissions excepted.

Please address tax exempt, school, wholesale, and dealer enquiries to:

### RITRONICS WHOLESALE

1st floor 425 High St. Northcote 3070 (03) 489 7099 (03) 481 1923 Telex AA 38897

Errors and omissions excepted.

## ADVERTISERS' INDEX

AED	50,51
Altronics	40,56,62 78,88,93,133,142
Adaptive Elect	30
Anderson Digital	50
Applied Technology	6,7
Aust. School of Electronics	14
Avtek Electronics	115
Centre Industries	81
COM X	11
Daneva	44
Data Parts	73
Dick Smith	28,29,48 49,116,117
Electromedical Eng.	98
Elmeasco	15
Emona	124
Emtronics	124
Esis Pty Ltd	41
Ferguson Trans.	37
Flex Electronics	37
Geoff Woods Elect	84
GFS Electronics	81
Hewlett Packard	16,17
ICS	120
Imark Pty Ltd	38
Jaycar	42,43,82,83,121 122,123,130,131,138
McGraths	126,127
K-Nar	73
Lamron Pty Ltd	86
Len Wallis Audio	27
Mini Tool	135
Pre-Pak Electronics	132
Radio Despatch	98
Rod Irving	4,34 87,94,134
Rose Music	OBC
Scientific Devices	80
Sheridan	39
SME Systems	36
Software Source	57,73
Sony (Aust)	IBC
Stanton Magnetics	IFC
SWTPC	33
Truscott Elect	120

## COMMENT



Roger Harrison

Editor

I RECENTLY ATTENDED a 'Communications Summit' in Canberra, organised by the Department of Communications. The theme of this conference was "Australia's Communications — where now?". From that, I expected an examination of our current 'position' with regard to communications in this country and some forecasts of what may lie ahead. I got something quite different.

The Minister for Communications, Mr Michael Duffy, opened the conference with a flurry of announcements with regard to Aussat and gave something of a 'serve' to the broadcasting industry with regard to sports programming. I rather thought we would be hearing discussing, the *form* and not the *content* of our communications industry and policies. But, hobby horses pop up in the most unexpected places, and generally leave unwelcome messages. Fortunately, Mr Duffy's comment was largely treated with ignore.

The eight papers presented over the two days covered the questions of community pressure on policy development, the issue of UHF TV channel spacing, the growth of technology, regulation, engineering and social pressure, and our role vis-a-vis developing countries. In the main, the papers were well researched and panel discussions lively and enlightening. However, I came to the view that they were all essentially standing in the 'here and now' and looking backwards. It reminded me of Spike Milligan's song *I'm Walking Backwards For Christmas*.

About the only speaker to seriously address the question in the conference's title was Barry Mansfield, Federal Secretary of the Australian Telecommunications Employees Association. He was the after-dinner speaker at the conference dinner, and could only address himself to some aspects of the broad question and urged support of the Government's commitment to a public monopoly telecommunications network.

I think the question needs further airing and I hope we can address it in issues to come.

I trust you have all survived the festive season and wish you all the best for a prosperous year ahead.

*One of the greatest pains to human nature is the pain of a new idea.*

— Walter Bagehot

## NEXT MONTH

### MICROBEE 'CHATTERBOX'

Can your Microbee say "Owen Hill has laryngitis"? We'll bet it can't even say "bother!". Here's another Tom Moffat ripperbewdysport project for the 'Bee bugs. Based on the SC-01 voice synthesiser, it runs from the parallel port, requires four ICs, two transistors, a loudspeaker and little else. Not expensive either.

### RELAYS

They're simple electromechanical devices, aren't they? No. Electromechanical, yes, simple? — no! If you thought you knew all there was to know about relays, this feature will

probably teach you as much again. Relay technology is like nostalgia — it ain't what it used to be. If you knew little or nothing about relays before — this will keep you right up to the moment. Don't miss it.

### DAMN FAST NiCAD CHARGER

If you really have to charge NiCads in a hurry — this project is for you. A radio-controlled model can go through dry batteries disappointingly fast and photo flashes always run out of flash at the most inopportune moment. This project will get them back 'on the air' in quick time.

### THREE MORE CD PLAYERS REVIEWED

Louis Challis continues reviewing examples of the rash of new CD players currently storming the market — from Philips, Technics and Marantz. There could be some interesting results here.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.

## SERVICES

**TECHNICAL INQUIRIES:** We can only answer readers' technical inquiries by telephone after 4.30pm Mondays to Thursdays. The technical inquiry number is (02) 662-4267. Technical inquiries by mail must be accompanied by a stamped, self-addressed envelope. There is no charge. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. We try to answer letters as soon as possible. Difficult questions may take some time to answer.

**GENERAL INQUIRIES:** For all inquiries about back issues, subscriptions (\$20.00 for 12 months/12 issues), photocopies of articles, artwork or submitting articles, call (02) 663-9999 or write to: ETI Reader Services, 140 Joynton Avenue (PO Box 227), Waterloo, NSW 2017.

**CONTRIBUTIONS:** Submissions must be accompanied by a stamped, self-addressed envelope. The publisher accepts no responsibility for unsolicited material.







microbee®

# DYNAMIC SOFTWARE

New for '84

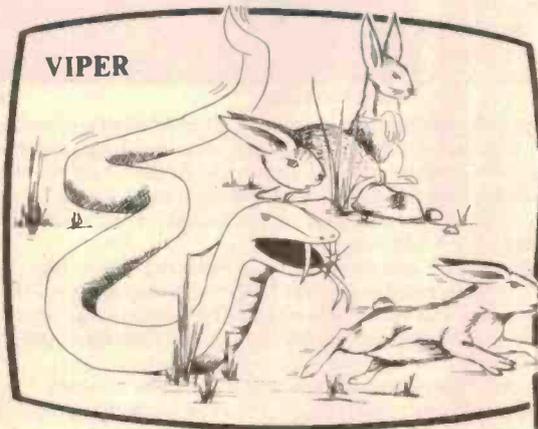


VIPER

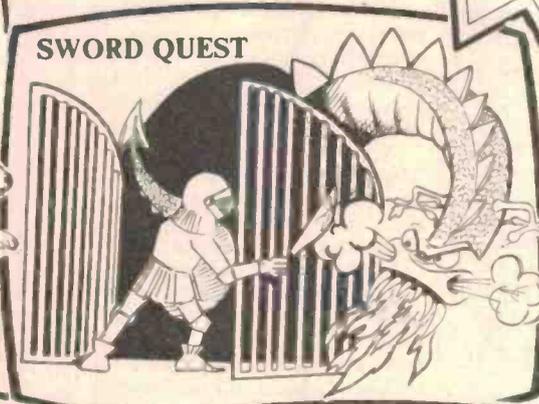

SWORD QUEST



BEE MONOPOLY

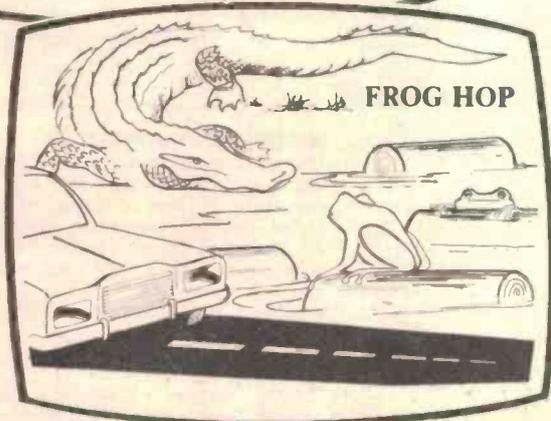

FROG HOP

EDUCATIONAL  
UTILITY  
GAMES

### VIPER

A highly addictive game. You must eradicate the rabbits before they reach plague proportions but each time you catch a rabbit your tail grows.

Cassette \$14.95 . . . . . Diskette \$19.95

### BEE MONOPOLY

Now a full graphic version of the old family game of the same name. The entire board, players, Community Chest and Chance cards are displayed as required in this fast moving game. Full details of land ownership and finances. Superb graphics and sound effects. (Requires 32K).

Cassette \$14.95 . . . . . Diskette \$19.95

### SWORD QUEST

Just like the 'Dungeons and Dragons' series. Select your characters level of armour, weapons, strength and skill. Explore in search of treasure and the Great Sword, and battle with the dungeon's creatures.

Cassette \$14.95 . . . . . Diskette \$19.95

### FROG HOP

A most graphic variation of the popular arcade game. You must hop across a busy street (watch out for the trucks . . .) and across a crocodile infested stream before your frogs are safely home. Guaranteed to appeal to all ages.

Cassette \$14.95 . . . . . Diskette \$19.95

**NOW AVAILABLE  
ON CASSETTE  
OR DISKETTE**

**MANY HAVE JOYSTICK  
CONTROL & COLOUR OPTIONS**

**ROBOT MAN '84**

Now one of the most popular games ever written for the microbee has been rewritten with new twists, a joystick and colour option.  
Cassette \$14.95 ..... Diskette \$19.95

**MICROSPACE INVADERS '84**

New update of one of the original microbee games. Now with full colour and joystick option. Sound and speed controls. Turn your microbee into a home arcade machine.  
Cassette \$14.95 ..... Diskette \$19.95

**SCRAMBLER**

A full colour version of the popular arcade game. You are the sole surviving defender of earth and you must destroy the aliens at all cost... very effective colour graphics (also suitable for non colour microbees).  
Cassette \$14.95 ..... Diskette \$19.95

**EYE OF MIN**

A graphic adventure game that will absorb you for hours. If you can solve this excellent mystery then you can proceed to the next saga 'Sabre of Sultan'. (Requires 32K).  
Cassette \$14.95 ..... Diskette \$19.95

**ELECTRONIC HOBBY MATE**

A real first. This clever program deals with resistors, capacitors, electronic terms and contains a wealth of 'live' information. A must for all experimenters. Your microbee will become a useful design aid.  
Cassette \$14.95 ..... Diskette \$19.95

**TUTORIAL: Touch Typing Tutor and Basic Tricks.** The microbee is an ideal educational computer recommended by educational authorities across Australia. This package enables you to learn to touch type using the Pitman touch typing method. For those who want to master Microworld Basic there is a series of hints and suggested subroutines arranged in a most effective menu driven style.  
Cassette \$14.95 ..... Diskette \$19.95

**RING OF DOOM**

Your quest is to search for the Dark Lord of Saurean's Ring of Power. This action adventure game will operate in a 16k microbee.  
Cassette \$14.95 ..... Diskette \$19.95

**SKETCH PAD**

Use the high resolution graphics in your microbee with this most effective drawing aid. Ideal as an introduction to Cad techniques and you can create complex shapes with a little practice. You can also 'trace' from images taped onto the screen to generate faithful reproductions. Have you ever wondered how programmers create the graphics for their software?  
Cassette \$14.95 ..... Diskette \$19.95

**CHOPPER PILOT**

Fly your helicopter through a small city and a series of mazes without crashing into the scenery. Has a training mode as well as the real thing for those who want to practice first. Now with joystick option.  
Cassette \$19.95 ..... Diskette \$19.95

**GENIUS AND INSANITY**

Yes, those insanity blocks are back! The game has several levels of difficulty but really serves as a vivid demonstration of the microbee colour graphic capability.  
Cassette \$14.95 ..... Diskette \$19.95

**CHESS/CHESS TUTOR**

For those who enjoy a serious graphics game it is hard to beat Chess. If your game needs improving try the tutorial first. You can select from 6 levels of play and these can be altered during the game. This program features very good graphics and, particularly at the higher play levels, becomes a most worthy opponent. (32k microbee recommended).  
Cassette \$14.95 ..... Diskette \$19.95

**TARGET/TREK**

These are two of the 'classics' of computer games and will still impress with the use of characters to emulate graphics (remember they only had teletypes on the 'old' days around 1976). The challenge of Trek will attract even the most ardent 'anti games freaks'.  
Cassette \$14.95 ..... Diskette \$19.95

**LEARNING CAN 'BEE' FUN**

Now the full series by John Grimley in one value package containing 6 cassette tapes (or 1 diskette). Utilizing well known games such as 'Donkey Kong', 'Frog Hop' and 'Rescue' you can enjoy the game and learn at the same time.  
Cassette Library Pack ..... \$49.95  
Diskette ..... \$39.95

**WORD ADVENTURE**

A powerful and gripping educational program. Follow the trails by solving problems involving homonyms, synonyms and antonyms. Various creatures will meet you along the trails and give you clues to the words you seek. If you make too many errors you will certainly have to face the spelling serpent who will test your fate. Once you master the first game you will learn a password which will enable you to load the next secret program. (Requires 32K).  
Cassette \$14.95 ..... Diskette \$19.95

**'BEE' CASINO**

Another value package with a collection of all the popular gambling/casino games written for the microbee. No need to take the wife to Las Vegas or Wrest Point! This makes ideal party material for after the kids go to bed.  
Cassette Library Pack ..... \$39.95  
Diskette ..... \$39.95

**BEE SCIENTIST: Physics and Chemistry Laboratory.**

A collection of practical experiments and courses on physics and chemistry. You can study chemical equations, valency, Keplers laws, Coulombs Laws and Milliken's experiment. A valuable teaching aid now used in schools.  
Cassette Library Pack ..... \$49.95  
Diskette ..... \$39.95


**FREE DELIVERY  
OF SOFTWARE  
for Direct Orders**

Ask your nearest microbee dealer for a catalogue of over 100 microbee programs now available on cassette, diskette and ROM covering applications in education, games and utility functions.

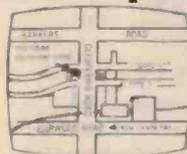
**microbee computer shops**



**1 Pattison Ave,  
Waitara 2077.  
Phone (02) 487 2711**



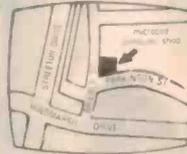
**729 Glenferrie Rd,  
Hawthorn 3122.  
Phone (03) 818 2244**



**Cooleman Court,  
Weston A.C.T. 2611.  
Phone (062) 88 6384**



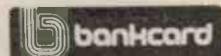**141 Stirling Highway,  
Nedlands, Perth.  
Phone (09) 386 8250**



welcome here

**DIRECT ORDERS  
PHONE (02) 487 2711**

**APPLIED  
TECHNOLOGY  
RETAIL  
PTY LTD**



**microbee**

**Authorised Dealers:**

**NSW:** Jaycar, (inc. Electronic Agencies)  
117 York Street, Sydney.  
115 Parramatta Road, Concord.  
121 Forest Road, Hurstville.  
Cnr Carlingford and Pennant Hills Road, Carlingford.  
Compu-K, 7 Casino Street, Lismore.  
Comput/Ed, 8 Park Arcade, Park Avenue, Coffs Harbour

**ACT:** Computech, Belconnen Churches Centre, Benjamin Way, Belconnen.  
**VIC:** Computerland South Melbourne, 37 Albert Road, Melbourne.  
**S.A.:** Key Computers, 1061 South Road, Edwardstown.  
77 Grenfell Street, Adelaide.  
**W.A.:** Altronics, 105 Stirling Street, Perth.

**QLD:** Software 80, 105 Milton Road, Milton.  
**Electrographic Office Systems,** 25 Grafton Street, Cairns.  
**Town and Country Computers,** CTL Centre, Anne Street, Aitkenvale, Townsville.  
**TAS:** Central Data, 14A Goodwin Street, Launceston.

# DOES THE FUTURE LIE WITH VLSI?

**A**ustralian engineers have the resources and skills to play a leading role in microelectronics systems engineering. At a time when talk of new high technology enterprises is very much in the air, it is now that innovative engineers can develop new products based on the new approach to silicon engineering, say Prof. Graham Rigby and Dr Kamran Eshraghian.

Prof. Rigby of the University of NSW, and Dr Kamran Eshraghian of the University of Adelaide, were speaking at a national series of seminars sponsored by The Institution of Engineers, entitled 'Silicon Systems Engineering'.

Very Large Scale Integration (VLSI) is a term used to describe a new technology capable of placing thousands, and possibly millions of devices on a single silicon chip.

The ability to create large systems on a single chip will have a significant impact on numerous disciplines such as engineering, science, medicine and medical care, communication and transportation.

The impact of this technology revolution can be likened to the one that the engine has had on society over the last one hundred years. If engines can be considered as an extension of human muscular power, then in a similar way, the VLSI technology can be viewed as the extension of human mental capabilities.

As the teaching and practice of VLSI spread in the United States and Europe, Australian research groups took up the ideas with

energy and enthusiasm. CSIRO launched its multi project chip (MPC) program in 1981 and several of Australia's leading Universities and Institutes of Technology launched courses and research programs in VLSI.

For example, research is currently being conducted at the University of Adelaide towards the development of 200 000 transistor silicon chip for signal processing.

In the seminar, Rigby explained that most of the high-performance modern technologies — both bipolar and MOS could be exploited for VLSI design. But two were of special significance: NMOS and CMOS. NMOS has become the mainstream technology for microprocessors and memories.

Advances in technology have reduced linewidths down nearly to the one micrometre level. The result is that gate delays of the order of one nanosecond are being achieved and this technology is competing with bipolars for high speed logic.

The silicon-gate process used for NMOS makes chip layout simple, compared with older technologies, and this has made

it the prime medium for VLSI design.

Both Eshraghian and Rigby believe, however, that complementary MOS (CMOS) will emerge as a more important technology for future VLSI systems. Its lower power and simplified electrical design rules make it particularly attractive.

In reviewing Australia's position in the silicon chip business, Rigby pointed out that there are two chip producers and numerous CAD research groups.

These, he believes, can provide the capability to put a new silicon design into production. This is vital if the new VLSI skills are to become a commercially significant force. But he warned that there is a difference

between a prototype chip and a product.

The production engineering costs involved in making this transition are a significant part of total project costs, but they can be minimised if designers make use of design modules which have been fully characterised and make thorough use of the simulation tools which are available in modern CAD systems.

For further information, contact Prof. Graham Rigby, Director, Joint Microelectronics Research Centre, University of NSW (02)663-0351 or Dr Kamran Eshraghian, Senior Lecturer, Department of Electrical and Electronic Engineering, University of Adelaide. (08)228-5333.

## RSTV PROPOSALS

**T**he Minister for Communications, Mr Michael Duffy, said he would be inviting proposals from both private enterprise and the ABC for the provision of radiated subscription television (RSTV) services in Australia.

Mr Duffy said it was important to note that the Government had yet to make decisions on whether RSTV was to be introduced.

RSTV is a service which typically provides programs such as

recently released feature films to home subscribers for a fee. Subscribers receive transmissions over the air through a special decoder attached to their television sets. Usually they pay a monthly fee for the service.

"We have confirmed our belief that cable television cannot be justified at this time. However, RSTV could be a different matter. It is less capital intensive than cable and is able to be transmitted using existing technology," the minister said.

## AUSTRALIAN TELECOMMUNICATIONS TECHNOLOGY FOR UK

**B**ritish Telecom have chosen to install Australian designed call forwarding equipment in telephone exchanges throughout Britain.

Austas Communications introduced their microprocessor controlled call forwarding equipment to British Telecom in 1980 and appointed Dynamic Logic of Bracknell, UK, as licensed manufacturers for the UK and Europe.

Following the evaluation of similar equipment from a number of manufacturers and field trials of several hundred Austas units, British Telecom have now placed an initial order with the UK licensee amounting to over A\$3 000 000.

Call forwarding is a system which enables incoming telephone calls to be automatically re-directed to an alternate number, without the caller being

aware that a re-direction is taking place.

The Austas desk-mounted Divert-A-Call unit is installed in over 5 000 locations throughout Australia, whilst the unit developed for British Telecom is exchange mounted, and the customer may remotely control its functions from any telephone.

Austas Communications is a national Australian owned company largely known for its tele-

phone answering and message processing services, but has in recent years also established an on-going department for the development of specialised telecommunications equipment.

For further information, contact Ken Webster, Austas Communications Pty Ltd, 1-15 Little Collins St, Melbourne Vic 3000. (03)63-9363.

## POLICE RADAR IS STILL FALLIBLE

In March 1981, ETI published an article which exposed the fallibility of police radar units, discussing three different possibilities of failure.

The Standards Association of Australia has now begun preparation for an Australian standard for radar speed detection equipment and a code of practice for its correct use.


The decision to proceed with the project was taken following discussions between the SAA and representatives of state police departments, road user groups, expert technical bodies and radar equipment manufacturers.

During the talks, the representative of the Australian Automobile Association, Mr Joe Kenny, expressed his organisation's concern that tests showed that some radar speed guns were capable of measuring the speed of any vehicle within an arc of up to 60° from the point at which they were aimed.

The ETI article pointed out two other possibilities for error, even though they are both very rare. Briefly, one type of failure may arise because the unit pays no heed to the constancy of the mark to space ratio of the pulses within an averaging period. A particular situation could occur which would lead to an erroneous measurement. However, the probability of such a sit-

uation remaining stable long enough to take a reading is extremely small.

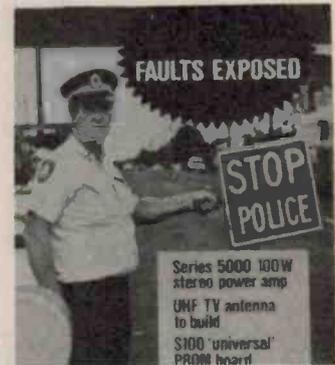The other possible error results from the mixing function used to derive the audio tone. The rare situation arising which would allow any failure here is virtually only possible in a certain type of unit.



Most importantly, the method of using the unit determines its reliability. At this stage different police forces use different methods of training.

Overall, the meeting expressed the view that an Australian standard for radar and a code of practice for the use of the equipment would remove those areas of uncertainty which had created doubts amongst the nation's motorists about the accuracy of readings taken by these devices.


## NATIONAL COMPUTER CENTRE FOR HOBART

The Deputy Director of Britain's National Computing Centre, Mr Eric Howe, is conducting a feasibility study into a proposal that Hobart should become the technological research and training centre for developing Australia's computer industry.

The study was announced by the Tasmanian Premier, Mr Robin Gray, after talks with the Department of Industrial Development and David Fairbairn, Director of the National Computing Centre, which has its headquarters in Manchester, England.

The UK National Computing Centre was established by the British government. It is now independent and has set standards and devised training schemes for Britain's computer industry. Some of these have been adopted worldwide.

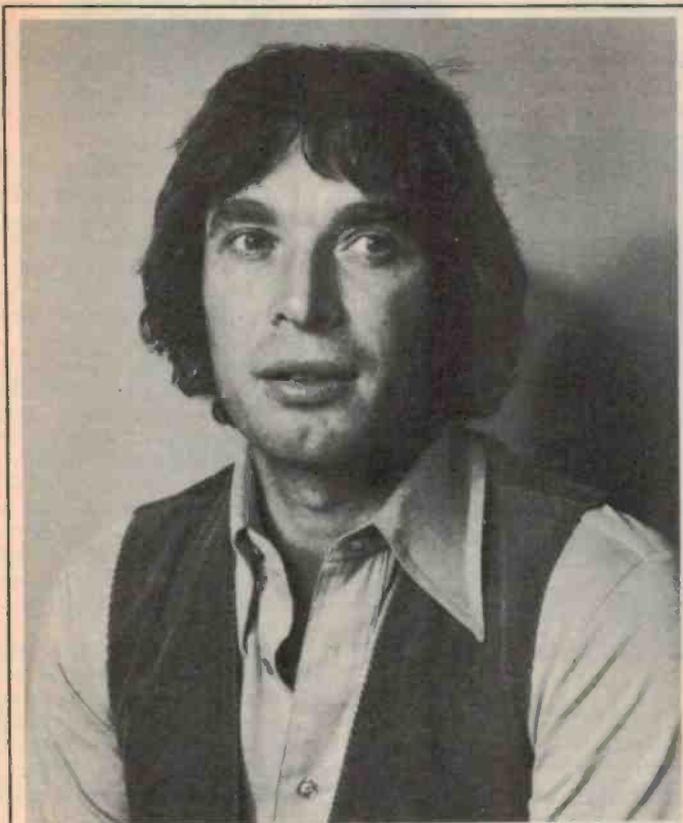Tasmania has succeeded in taking the proposal to the feasibility study stage because it persisted in its attempts to establish a high-technology base in the State and because a computer centre needed to maintain its independence of national government and the larger population centres.



### BOB TAYLOR

It is with great sadness and an infinite sense of loss that we report the untimely death of ETI's advertising sales manager, Bob Taylor.

Bob was just 40. The tragic car accident that took his life happened on Thursday 15th December — just a few days after his birthday.

He had lunched with my wife and me that day, enthusing, as always, about the myriad of activities that filled his life.

And there were many — for Bob did more things in a year than most do in their lifetimes.

He spoke of hang gliding, wind surfing, jet skiing, selling advertising, motor cycle racing, of his cherished companion Virginia, and of his friends.

Bob came to ETI early in 1976, having worked previously

for Thomson Publications. He became sales manager shortly after, and group sales manager a year or so later.

In those seven or so years Bob built up a rapport and mutual friendship with colleagues and clients alike which must be without parallel in our industry.

Bob was somehow so much larger than life that it's all but impossible to accept that he has gone.

As Saint-Exupery wrote, in *The Wisdom of the Sands*, "He who has gone, so we but cherish his memory, abides with us, more potent, nay, more present, than the living man."

Our sympathy goes out to Virginia, his parents, sisters, son Matthew, and his especial friends, including John, Mac, Roger, Sean, Jan, and Jenny. He was my friend too.

Collyn Rivers

### APOLOGY

Pro-Log (Australia) Pty Ltd apologises for an error in their advertisement in ETI, December 1983. It should have read "and purchase 250 of any of our boards and the manufacturing rights to that board are yours".

## SELF-INDEXING WIRE TERMINATOR HAND GUN

**M**olex has released a self-indexing, hand held wire terminator for the insertion of discrete wires into Molex insulation displacement connectors.

It features snap-on modular dies for termination of wires on 2.5 mm, 2.45 mm, 3.96 mm, 5.0 mm and 5.08 mm centreline Molex connectors. A module is available to terminate 1.27 mm ribbon cable to the MX 50 connector.

A pneumatic bench terminator with foot pedal and a filter for the air supply line is also available for all modular dies except the MX 50 insert.

For further information contact Utilux Pty Ltd, 14 Commercial Rd, Kingsgrove NSW (02)50-0155.



## AUTOMACH AUSTRALIA

**P**remier Minister Hawke has endorsed Automach Australia 84, Australia's first high-technology conference and exhibition to be held at the Royal Hall of Industries in Sydney, May 23-25 1984.

The purpose of the three-day event is to stimulate the use of integrated manufacturing systems by Australian industry, leading to improved productivity.

The high-tech event is sponsored by the Society of Manufacturing Engineers, its Australasian chapters and two constituent associations of SME, Robotics International and the Computer and Automated Systems Association.

In addition, Automach is supported by Australia's leading engineering and industrial associations and academia, SME said.

Mr Barry Jones, Minister for Science and Technology, will deliver the keynote address at Automach Australia on May 23.

Mr Neville Wran, Premier of New South Wales, will formally open the exhibition and participate in the opening press conference with SME officials.

More than half of the exhibit space at the Royal Hall of Industries already has been assigned, said Adolf Greco, chairman of

SME's Australasian chapter and chairman of Automach.

These exhibitors include Computervision, IBM, Prime Computer, Hewlett Packard, Perkin-Elmer, ESEA, Zenford-Ziegler, Ferrocast Williams, Management Information Services, Javelin Electronics, Sandvik, Ceanet and Jordan Computers.

To date, these exhibits represent the manufacturing equipment, systems and services of

more than 70 companies from over 10 countries, Greco said, adding that a wide range of numerically-controlled machinery, CAD/CAM, robotics, software, tooling and accessories, and computer-based equipment will be demonstrated.

For further information contact A. Greco & Associates, 3/D Tyrone, 80 Shirley Rd, Wollstonecraft NSW 2065. (02)439-4014.



## AID FOR THE AGED

**I**n 1979 in Victoria alone, 379 people over 55 years of age died as a direct result of accidental falls. In many cases the panic arising from the situation is likely to have been a major contributing factor.

Norman Wiggett has set up a company, HAETAS Australia Pty Ltd to manufacture and market his projects designed to help the aged and disabled. One of these, the Emergency Call Service and Library, operates a low cost, 24 hours a day, automatic telephone monitoring system — in the event of an emergency, help is just the press of a button away.

Users carry a compact, lightweight, unobtrusive transmitter which will activate the telephone to call the monitoring service, who will immediately summon help from nominated friends, neighbours, relations, or if necessary, the police.

Once initial funding is available, the Emergency Call Service and Library will be formally established as a non profit, community based organization in each state. Those who cannot pay for the service receive it free. The manufacturer, HAETAS, will continue to make and service the units, selling them exclusively to the Emergency Call Service and Library on a non profit basis. The current cost per unit is \$299.

HAETAS will also provide the 24 hour monitoring service under contract to the Emergency Call Service and Library. The monitoring cost is \$1.50 per unit per week. Mr Wiggett is looking for more ideas for aids to the aged and disabled, and is also looking for a source of good cheap components.

"Once we have supplied the Australian market with our service, we have nineteen other countries interested in this project and our export could be in the billions of dollars worth of electronic equipment that can be produced in Australia," he says.

For further information, contact HAETAS Australia Pty Ltd, P.O. Box 220, Bayswater Vic 3153. (03)725-7095.





# Reflecting obsessions — The Japan Electronics Show

## Computer report

Japan gears up to grab a share of the home computer market with Microsoft compatibility, while computerised television and mini robots become even more sophisticated.

Dennis Lingane

THE JAPANESE may have finally come up with a way to break into the booming home computer market. At the Japan Electronics show in Osaka last month, twenty of the leading manufacturers announced they had designed their computers to run Microsoft programs under the logo MSX.

### MSX standardization

Microsoft is one of the leading independent software companies in the USA and the decision by multi-national companies such as Sony, Toshiba, Hitachi, National Panasonic, and others, means Microsoft may become the official Japanese software system.

However the three leading computer companies NEC, Sharp and Fujitsu have not agreed to go along with the scheme yet. Their reluctance to join the rest is obvious. They are the three companies that have so far managed to gain overseas acceptance, as well as dominating the Japanese market.

To go along with MSX standardisation would effectively be opening the doors to

both Japanese and overseas markets for their competitors.

There is more than enough competition in the market place at the moment.

The MSX-compatible home computers are being launched in the market in time to try and grab a share of the one million home computers expected to be sold in the pre-Christmas period in Japan. All companies with MSX were making a lot of noise about it at the Osaka show which was visited by over 300 000 people.

### IBM protects copyright

While MSX may become the standard for Japanese home computers, the policy in the personal computer area (over \$1000) is to make the machines IBM compatible. This was done following a recommendation from Japan's MITI (Ministry for International Trade and Industry). But that may now be running into problems following the agreement by Hitachi to let IBM police everything it makes in the next five years to

ensure it doesn't breach IBM copyright and patents.

This five year policing of Hitachi products by IBM was part of the out-of-court settlement following the court case in which Hitachi and several of its employees pleaded guilty to stealing and trying to export IBM's trade secrets. Hitachi and Mitsubishi were caught red handed over 12 months ago by the FBI in an undercover 'Sting' operation.

In the settlement, Hitachi agreed to pay all IBM's legal expenses (described by IBM as substantial), to return all IBM secret documents, and to let IBM examine all Hitachi products for five years to make sure they did not contravene IBM patents and copyright.

This has sent the rest of the Japanese manufacturers into panic. They had hoped that Hitachi would fight the case and set a precedent. However, Hitachi was under a court injunction not to sell computers until after the case was settled. It had already

dragged on for over a year and the company was losing out in the market place.

### Compatibility causes concern

They settled, and in doing so left the question of IBM compatibility open, with the threat of a test case still an issue to worry about; It also gave IBM the opportunity to keep a close eye on what was possible and not possible. In other words, if Hitachi is not able to come up with an IBM compatible machine without contravening IBM patents and copyright, then every IBM compatible machine made must come under suspicion.

If the Japanese do build their personal computer industry on the back of IBM, only to lose a test case in a few years, they could find themselves having to pay huge licence fees and royalties to IBM for the right to be IBM compatible. It's a situation that they had hoped would be resolved by Hitachi. Now it's still an open issue hanging over them as they crank up their production lines to get some of the computer action.

A few days after the settlement, the other manufacturers came back with a counter attack accusing Hitachi of endangering Japanese technology.

They argued that, by agreeing to a five-year policing of Hitachi computers, IBM would be in a position to learn about and copy Japanese computer developments and breakthroughs. Hitachi has denied that Japanese technology would be at risk, and both IBM and Hitachi have agreed to refer disputes to a panel made up of a member of Hitachi, a member of IBM and an independent authority, to make a ruling.

There is no doubt that IBM has pulled off a master stroke. When I visited IBM in New York last year, they told me then that they regard Japanese competition very seriously. It is obvious now just how serious.

Interestingly, Canon announced on the eve of the show they have signed an agree-




The Sharp PC-5000 portable computer.

It has a fold down liquid crystal display, built-in printer, removable bubble memory packs and optional modem.

ment with Apple to sell Apple computers in Japan, which takes them out of the market battle.

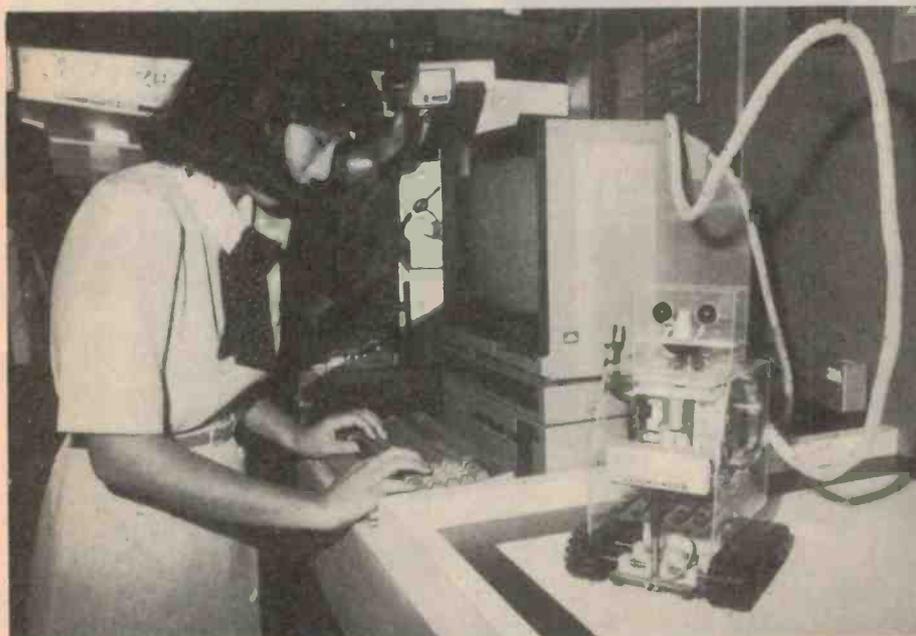But getting back to the electronics show.



Mini robots. They were definitely the order of the day at the show as a way of displaying the versatility of the computers.

### Computerised TV's

As far as computers are concerned, the Japanese are still selling hype rather than machines. Like electronics magicians, they promote the futuristic aspect of home computers with home monitoring systems and sensor touch TV data selection.

National Panasonic showed a TV set with in-built computer that was menu driven, but instead of a keyboard, you simply touched the TV screen with your finger. The part of the menu you wanted was searched out and displayed. To continue, or abort, you simply touched the words on the screen instead of hitting a key on a typewriter keyboard. It's a good idea but will lead to very grubby TV screens.

I don't know how my son, who tends to lie back on a couch or on his bed with a keyboard on his lap with a three metre cord connecting him to his TV, would react if he had to keep walking to his TV set to search through a menu.

The program they ran was a home control system. So, if you wanted to close the windows, or curtains or turn out the light then you just called up the room, and touched the things you wanted activated. Mind you, by the time you turned on the TV set, loaded the program, found the section, and then touched the section you wanted to activate, it would probably be quicker to walk to the room — unless you live in a mansion.

Talking intelligent TV sets. Sharp says that a TV set without a computer won't be a TV set in coming years. They launched a TV computer system last year that was an instant hit. The TV was designed to display ▶

your computer program over the TV picture. This meant that you could watch a TV program and compute at the same time. It was an instant success with the kids.

Now they have produced a budget version of this computerised TV that is a lot cheaper called the C1, but it has limited applications. Instead of an alpha-numeric keyboard you get a hand controller with a joystick and three buttons. The alphabet is displayed at the bottom on the screen, and you move a cursor to the letters you want and press a button.

A bit more laborious than an alpha-numeric keyboard, but this system does sell for only \$100 more than an equivalent TV set. There are ports for a cassette and cartridge. So you can play games, run educational programs for children, or leave messages for other members of the family. The messages are locked into a memory so when the TV set is turned on the message is automatically displayed. There is also an indication light to let you know there is a message in memory anyway.

### 80 column portable computer

The other magic product Sharp showed at this show was a portable computer with bubble memories, and a fold down liquid crystal screen that will display up to 80 columns wide and eight lines down.

It is a travelling person's dream. The on-board memory is 128K and it has a printer built in. (See illustration). The screen folds down over the keyboard and the whole sys-

tem is no larger than an average portable typewriter. The printer is dot matrix with thermal as well as ribbon printing. The bubble memory packs are removable and can be used for data storage — each has 128K of memory — the equal of the on-board memory.

It is due for release in Australia in a few months. There is a modem port, as well as disk drive (RS232), but there isn't an outlet for a TV monitor. But with 80 columns and eight lines, Sharp probably figures there isn't a need for a TV monitor. It will be released in Australia in a few months but will be a lot more expensive than the Tandy and NEC machines, which are all we have seen so far as portables with liquid crystal screens. They have 40 column screens however.

### Language computer

The other eye catching product at the electronics show was a language computer from Mitsubishi.

This was a sort of sophisticated version of Texas Instruments Speak and Spell. But this not only says the words in very good clear English voice as distinct from the TI Yankee drawl, but showed on a liquid crystal display both the English and Japanese words.

The unit holds up to 750 words and it sells for around \$100. Several junior schools have placed orders. One good feature is that you can get the word repeated slowly to enable students to pick up the enunciation.

An add-on module is available that expands the unit to 1500 words and 1000 sentences.

While everyone was trying to prove that the idiot box would be running our lives, Toshiba championed the telephone as the way to remote control the home. Pick up the phone, either from outside or inside the house, tell the computer what you want done and it does it. Much quicker, but not as impressive when you have guests you want to show off to.

### Robots

The other obsession at this electronics show was robots. Not large industrial ones, but mini ones no bigger than the Action man dolls. These were being run to prove how versatile the computers are. But if these manufacturers really thought about it, they could probably do a lot better making mini robots to run off Apple, Commodore and Atari computers.

One last word on TV screens. NEC is pioneering a new TV tube that will enable you to have a receiver monitor that will handle an 80 column computer.

Currently the holes on TV masks (pixels to computer buffs) are around six microns. This limits the display to around 40 columns because you can't get the resolution. But NEC is now making TV sets in Japan with four micron holes and this enables you to run 80 column computers. Unfortunately it means the TV picture quality drops dramatically. You lose brilliance and contrast. But then you can't have your cake and eat it. ●

# Master the Microprocessor

Learn how Microprocessors really work ... the practical way.

## The Purpose of this Course

There is a considerable, expanding and world-wide demand for people with a real knowledge of microprocessors and general computer technology. Such people are needed to design and evaluate systems and to assess and develop the enormous range of possible applications, both present and future, of microprocessors and to understand the installation and servicing of the main types of equipment of which they may form the most vital component.

(A microcomputer has already been produced to replace the mechanical programmer on a domestic washing machine, for example.)

This Course provides the necessary basic information to enable a student to really understand the functioning of microprocessors and their supporting circuitry.

usually referred to as the "hardware". This is backed up by showing how to program a microcomputer (or produce its "software") in the most fundamental form of computer language called "machine code". No previous knowledge of computers is necessary, though a little basic knowledge of electronics plus digital and logic circuits will be found helpful.

A special introductory short course is available to provide this background information, if required by an individual student on the course without extra fee.

## Student—Tutor Contact

A qualified Tutor is available to every Student throughout this Course in order to deal with any queries which may arise and to assess certain questionnaires which are issued in Students throughout the period of training.

## Certificate

Issued to all Students completing the Course successfully. Course covers main requirements of the City and Guilds Certificates in Computers.

# Practical Self Study Course

## FREE COLOUR BROCHURE

Post coupon now The Australian School of Electronics Pty Ltd, P.O. Box 108, Glen Iris, Victoria, 3146. Offices at 219 Balaclava Rd., Caulfield North

Please send your brochure without any obligation to:

Name .....

Address .....

Postcode .....



## How the Course is organised

The basis for the practical work in the Course is the Microcomputer.

This is supplied completely assembled and ready to use.

The Course text is carefully arranged in sequence so that each new section follows logically from previous work. Hardware description and programming technique progress together, so that the Student is discouraged from treating them as distinctly separate subjects.

Following each section of descriptive text, detailed instructions are given in order to use the Microcomputer to provide a practical demonstration of each new function or technique. This provides a very powerful way of learning precisely how the system operates, and enables any possible ambiguities in the Student's mind to be quickly resolved.

# The Digital vs. Analog battle is over.

From **\$110** buys you the new champion. **The new Fluke 70 Series.**

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

So call or write for more information.

#### Fluke 73

**\$110\***

Analog/digital display  
Volts, ohms, 10A diode test  
Audible continuity  
Autorange  
0.1% basic dc accuracy  
2000+ hour battery life  
3-year warranty

#### Fluke 75

**\$129\***

Analog/digital display  
Volts, ohms, 10A mA diode test  
Audible continuity  
Autorange/range hold  
0.5% basic dc accuracy  
2000+ hour battery life  
3-year warranty

#### Fluke 77

**\$165\***

Analog/digital display  
Volts, ohms, 10A mA diode test  
Audible continuity  
Touch hold function  
Autorange/range hold  
0.3% basic dc accuracy  
2000+ hour battery life  
3-year warranty  
Multipurpose holster



**FLUKE**

SOLD & SERVICED IN AUSTRALIA BY

**ELMEASCO**

**Instruments Pty. Ltd.**

P.O. Box 30, Concord,  
N.S.W. 2137  
13-15 McDonald Street,  
Mortlake, N.S.W.  
Telephone (02) 736 2888  
Telex 25887

P.O. Box 107, Mt. Waverley,  
Victoria 3149  
21 23 Anthony Drive,  
Mt. Waverley, Victoria.  
Telephone (03) 233 4044  
Telex 36206


G.P.O. Box 2360, Brisbane,  
Queensland 4001.  
243 Milton Road,  
Milton, Queensland.  
Telephone (07) 369 8688.  
Telex 44062.

Adelaide. (08) 271 1839  
Perth: (09) 398 3362

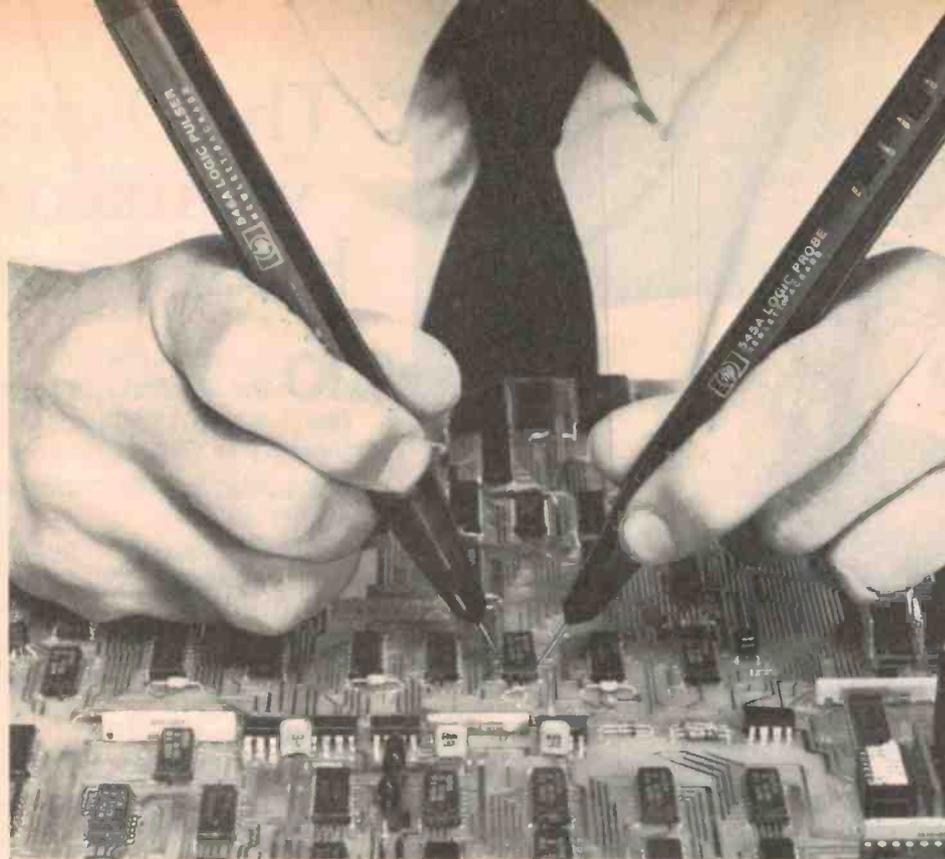
**bankcard**

N.S.W. Ames Agency 699 4524 • George Brown 519 5855, (049) 69 6399 • Bryan Call 522 4923 • DGE Systems (049) 69 1625 • Davred 267 1385 • Macelec (042) 29 1455 • Radio Despatch 211 0191 • Sheridan Electronics 699 6912 • Standard Components 896 1755 N.T. Thew & McCann (089) 84 4999 A.C.T. George Brown (062) 80 4355 VIC. Radio Parts 329 7888 • Browntronics 419 3986 • G.B. Telespares 328 4301 • Elanco 428 4345 • Ellistronics 561 5844 • Stewart Electronic Comps 543 3733 • SIRS Sales (052) 78 1251 QLD. L.E. Boughen 36 1277 • Colourview Wholesale 275 3188 • ECO Electronics 376 5677 • Electronic Shop (075) 32 3632 • W.G. Watson (079) 27 1099 • GEC Electrical Wholesale (079) 51 3155 • Nortek (077) 79 8600 • Solex (077) 72 2015 • Fred Hoe & Sons (07) 277 4311 S.A. Trilo Electrix 51 6718 • Protronics 212 3111 • Lab Service 278 7488 W.A. Atkins Carlyle 321 0101 • Protronics 362 1044 • Brookeades 276 8888 • Cairns Instrument Services 325 3144 T.A.S. GHE Electronics (002) 34 2233 & (003) 31 6533

\* All prices are plus Sales Tax if applicable and subject to change without notice.


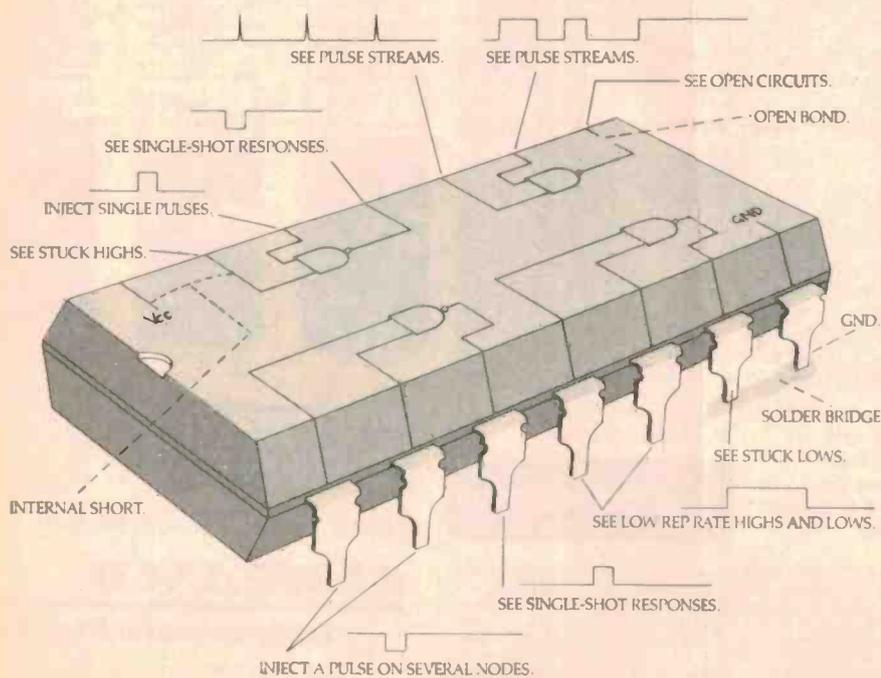
# Hewlett-Packard IC Troubleshooters to show it like it is:



1


**The Model 545A Multi-Family Probe.** See logic highs, lows, bad levels and open circuits with logic probes. Capture one-shot pulses. See pulse streams.

2

**The Model 546A Pulsar.** Inject a pulse or pulses into a circuit without trace cutting or unsoldering. Automatically drives low nodes high or high nodes low. The Model 546A Logic Pulsar creates your programmed number of logic pulses and has multi-family capability.



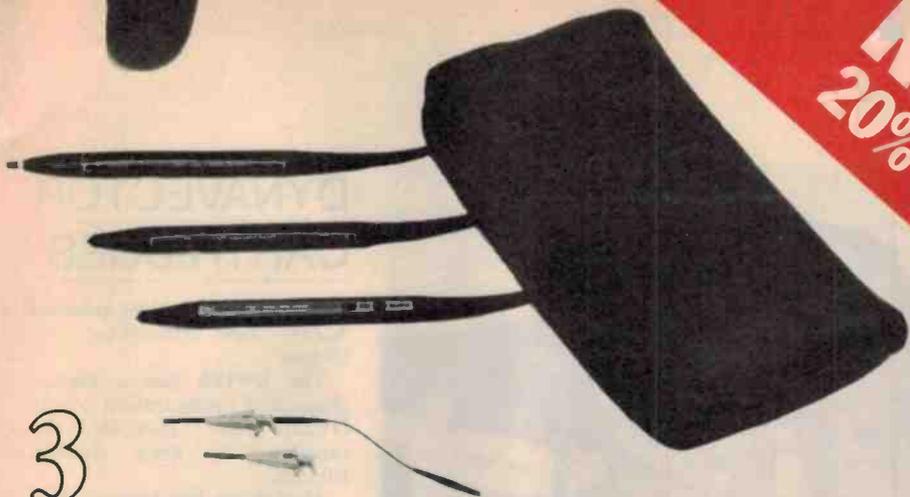**ETI**  
**READER OFFER**  
**20% OFF! SAVE UP TO \$197**



3

**The kit puts it all together.** The HP5024A Kit puts the logic tool kit all together in a convenient carrying case. In addition to the Multi-Family Probe and Pulser, the kit contains the model 547A Current Tracer. The 547A will trace current when you reach

a node where the logic probes cannot work because the node is stuck low and you don't know which bus component of many is faulty. No pc board trace cutting or good component removal is necessary.

**INSPECTION.**  
 You are welcome to inspect the Logic Troubleshooters during office hours at the following locations:

**SYDNEY**  
 ETI Offices,  
 Federal Publishing Company,  
 140 Joynton Avenue, Waterloo.  
 OR  
 Hewlett-Packard Australia Limited,  
 17-23 Talevera Rd., North Ryde.

**MELBOURNE**  
 Federal Publishing Company,  
 150 Lonsdale St., Melbourne.

**BRISBANE**  
 Hewlett-Packard Australia Limited,  
 10-14 Payne Rd., The Gap.

**ADELAIDE**  
 Hewlett-Packard Australia Limited,  
 153 Greenhill Rd., Parkside.

**PERTH**  
 Hewlett-Packard Australia Limited,  
 261 Stirling H'way, Claremont.

**HOW TO ORDER YOUR TROUBLESHOOTER.**  
 Fill out the coupon here and enclose a cheque, bank cheque or money order for the amount required made out to HEWLETT-PACKARD AUSTRALIA LIMITED. If you are not paying sales tax, please quote your sales tax number on the coupon or use an official order. Schools, colleges, etc. should enclose a tax declaration on official letterhead. The completed coupon, together with your payment should be sent to:  
 Hewlett-Packard Troubleshooters Offer  
 C/- ETI,  
 140 Joynton Avenue, Waterloo, N.S.W. 2017

**Delivery.** Hewlett-Packard will endeavour to deliver your Troubleshooters in less than four (4) weeks from receipt of payment.

**Nothing else quite measures up.**



**ORDER NOW! OFFER CLOSING JANUARY 31, 1984**

Please supply, on the terms outlined in this offer and the Terms and Conditions of Sale of Hewlett-Packard Australia Limited.

Qty. \_\_\_\_\_ HP545A Logic Probe @\$139 (normally \$176) each.  
 Qty. \_\_\_\_\_ HP546A Logic Pulser @\$215 (normally \$275) each.  
 Qty. \_\_\_\_\_ HP5024A Logic Kit @\$790 (normally \$987) each.

Sales Tax No. \_\_\_\_\_  
 (if applicable)  
 All prices excluding tax. Add 16% if applicable

Name \_\_\_\_\_ Position \_\_\_\_\_ I enclose \$ \_\_\_\_\_ total  
 Address \_\_\_\_\_  
 \_\_\_\_\_ Postcode \_\_\_\_\_

Cheque or Money Order No. \_\_\_\_\_ Signature \_\_\_\_\_

Send completed coupon with payment to: Hewlett-Packard Troubleshooters Offer.  
 C/- ETI,  
 140 Joynton Avenue, Waterloo, N.S.W. 2017



## CHEAP POCKET TV

**A** rival to the pocket transistor radio has been launched — a cheap pocket TV set. Costing less than A\$136 in Britain and under US\$100 in the US, the new Sinclair flat-screen pocket TV is being geared for millions of sales worldwide. Sir Clive Sinclair, founder and chairman of UK Sinclair Research Company, said he had plans for a large flat-screen colour TV and a pocket set that will combine TV and radio.

Although Sir Clive claims he produced the first flat-screen TV tube he was narrowly beaten to the market-place with it by a Japanese rival. However, when he unveiled the pocket set in London he announced a price tag of A\$135.91 including tax and said it would be sold in the USA for well under US\$100. This is said to be less than a third of the price of its rival set.

Sir Clive maintains his 50.8 mm screen set represents a whole series of firsts in technical advances. It is smaller than an average paperback book at 140 x 90 x 30 mm, weighs 280 gm and has only two controls; an on-off/volume switch and a tuner. Its special flat battery provides 15 hours of viewing, up to six times longer than that of its competitors, it is claimed.

Experts have tried for years to reduce the bulky depth of the

conventional cathode ray tube. Many have said that once this problem has been solved the family TV pictures will be on something like a picture hanging on the wall. Sir Clive's solution was to send the cathode rays from the side, bending them round to fall on a screen and form a picture.

The tiny Sinclair screen is up to three times as bright as normal and uses between one quarter and one tenth the power of a conventional tube. The screen is recessed to increase brightness and contrast.

Apart from the tube innovations, the new set uses a single integrated circuit which was designed by Sinclair Research in collaboration with the Ferranti electronics company. The set is the first TV set to use just one chip for its circuitry. Sir Clive says the chip, which is subject to

a 'flood' of patents, is unique. "Nobody else has anything like it," he added.

The complex chip ensures that most of the set's functions are automatic. The set is designed to handle all 625 and 525 line systems and most UHF transmissions around the world except France. A combined UHF/VHF set will follow later and replace the present UHF set. The chip analyses the incoming signal, automatically decides which line system is being received, and adjusts itself accordingly.

The new TV, which is about to enter full production in Britain, will be available at first by mail order only. The aim is to build up production to a rate of 10 000 a month by the end of this year. After initial sales in the UK, the set will be launched in the US next year and progressively throughout the world; including Japan.

More information about this tiny TV, which has been used successfully in cars and trains, can be obtained from Sinclair Research Ltd, 25 Willis Road, Cambridge CB1 2AQ England.

## DYNAVECTOR CARTRIDGES

**C**oncept Audio has released two new Dynavector cartridges.

The DV19A has a similar shape and configuration to the DV23R ruby. However, the cantilever is even shorter, 1.9 mm.

Aluminium has been used in the construction of the cantilever, lowering cost and also making the cartridge more resistant to customer abuse. The unit is priced at \$248.

The second new cartridge, the DV17DS, features a tapered diamond cantilever, enabling a reduction in the equivalent moving mass of 21% over the current 17D model. This increases tracking ability at ultra-high frequencies of more than 20 KHz.

A Micro Reach stylus has also been introduced. Its unique shape enables a very wide frequency range, excellent dynamics and low distortion. This unit is priced at \$698.

For further details, contact Concept Audio, 17/98 Old Pittwater Road, Brookvale NSW 2100. (02)938-3700.

## INFRARED TV

**S**ennheiser's latest infrared television transmitter, the SI406-SY, is designed for television sets which do not have a headphone socket as standard equipment.

The transmitter comes with an angled electret microphone for mounting on the side of the television set, with the microphone itself positioned directly in front of the loudspeaker aperture. This enables it to pick up the full acoustic quality of the sound, says Sennheiser.

The transmitter, which can be mounted without interfering with the interior of the television set, is identical to the long-established SI406-S transmitter. It is ideal for hard-of-hearing applications.

For more details, contact R. H. Cunningham, 146 Roden Street, West Melbourne Vic. 3003. (03)329-9633.

## GOOD HEAD FROM AKAI

A more portable entertainment centre is the AKAI Bandearo — a new micro-mini 2 band AM/FM stereo headphone receiver.

Engineered with AKAI's "You Can't Miss" concept, the Bandearo uses the latest monolithic chip design to maintain sound reproduction which is usually attributed to full size hi fi systems.

A highly sensitive radio tuner, a whip antenna, a stereo amplifier and a long life power pack integrate perfectly in the slim-line head-phones.

The auxilliary jack and the patch cord provided hook up to stereo equipment and the Bandearo can be connected to another set of headphones.

The unit retails for \$69. Contact AKAI, Unit 11, Eden Park, Waterloo Rd, North Ryde NSW 2113. (02)887-2311.



## EXTRA HIGH GRADE VHS VIDEO CASSETTES

TDK (AUSTRALIA) Pty Ltd has released its new range of extra high grade VHS video cassettes.

The cassettes feature packaging consisting of a plastic view-case outer sleeve which protects the cassette much greater than normal cardboard sleeves do.

Since the advent of Super Avilyn material in 1978, this magnetic medium has been the standard to which most of the audio and video industry has related.

The Extra High Grade range of TDK VHS video cassettes employs Super Avilyn magnetic



## THE MOBILE COMPACT DISC

Following the highly successful market introduction of the Compact Disc digital audio system during 1983, Philips has displayed a prototype car Compact Disc player at this year's Berlin Funkausstellung audio/video exhibition, held from September 2-11.

It will be particularly welcomed in view of the current demand for in-car sound quality of the same level that is expected in the home.

Other important advantages of the compact disc are significant for in-car use. Its ease of handling and operation will contribute to safety, while the durability and resistance to wear of the 120 mm compact discs make this new medium well suited for mobile use, Philips claims.

The widespread appeal of the

compact disc medium may be expected to increase still further as new applications for the system are developed — for example, the areas of high-quality portable and personal audio products.

The prototype in-car compact disc player shown at Berlin is expected to undergo a number of changes before a final production version is reached. Size of the player will be reduced further, to allow it to be positioned as conveniently as possible inside the car.

Special attention will also be given to the disc loading system and disc storage in the car to optimise ease of use, and hence driving safety.

Philips expects that production of a car compact disc player could start within a time span of some two to three years, by

which time the Compact Disc system is expected to have reached a high degree of market penetration.

Looking further ahead, the compact disc system should be well suited to some exciting future in-car applications, thanks to its extremely large information-storage capability.

These could include the presentation of route or tourist information, for example, with a single compact disc replacing a number of conventional maps and guide books.


Developments like these will ensure that the system remains at the forefront of attention during the coming years.

For further information contact Peter Brownlee, Philips Industries Holdings Ltd, North Sydney NSW. (02)925-3333.

Extra High Grade VHS video tape is shown by the following technical specifications: Signal-to-noise ratio is up 3 dB in video, +5 dB in colour, compared to TDK's reference standard; Coercivity stands at 680 Oe, meaning precise response and input/output linearity; Audio frequency response is flatter across the range and offers better fidelity than normal video cassettes.

The recommended retail price of TDK's Extra High Grade VHS video cassettes are: E60 — \$16.99, E120 — \$19.99, E180 — \$23.99.

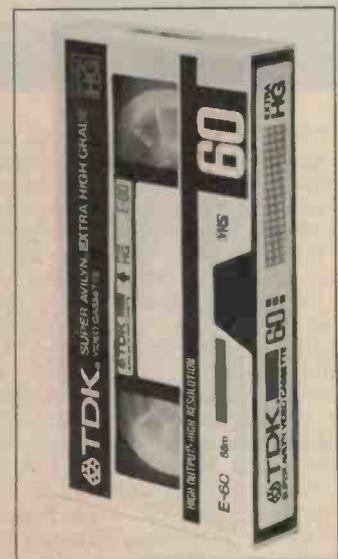Detailed specifications are available from TDK (Australia) Pty Ltd, P.O. Box 100, Pyrmont NSW 2009.



# The All Japan Audio Show Reviewed

In its 32nd year the show reflects the shift towards the merging of sound and video.



NOW in its 32nd year, the All Japan Audio Show is billed as the largest audio show in the world. With 80 companies exhibiting some 6000 products and an attendance of 300 000 people, the claim is beyond dispute. With video hi-fi, video disc, and gadgets for creating visual interpretations of sound on TV sets called audio video synthesisers, the show was more a visual experience this year than an audio one. One can be left in no doubt after seeing this show, that sound without picture will soon belong in the past.

During the previous two weeks touring around Japan visiting various companies, all they had been able to talk about was compact disc, and I walked through the turnstiles into the huge hangar — like buildings at Harumai expecting to be buried in CD technology.

## Dennis Lingane

Indeed there were some 40 new CD models compared to only 10 last year. But they were almost lost in the glare of TV sets and video graphics. Every manufacturer had banks of TV sets, and on them was everything from Flashdance, opera and concerts to images from VU meters and real time graphic analysers. However, most of the new products were really only revamped old products with a new facia or a different colour. The Japanese are mad on colour these days, and we are already seeing the trend in Australia, in the portable market where fashion colours are all the rage.

## Nakamichi reverse

In the pure hi-fi arena Nakamichi and other traditionalists had some new audio products to show. Nakamichi unveiled a budget version of its TX 1000 computer controlled turntable, the Dragon CT, and a reverse play cassette deck called RX202.

The reverse play raised a few eyebrows, because it is generally accepted that you can't get the same sound quality from a reverse play cassette deck as you can from a conventional one-way system.

But Nakamichi has overcome that problem by building a revolving platform on the front of the cassette deck. The cassette deck has conventional mechanics, and the cassette is physically turned around. Effectively the RX202 does mechanically what we do manually.

The budget version of its now famous TX 1000 computer controller analogue record is far from budget, since it's priced in the multi-thousand dollar range. The main purpose of both turntables is to compensate for poor record production. Nakamichi says that very few records are cast with the hole dead in the centre, and this creates wow when the record is played.

Both these turntables measure how far off axis the record spins, and then adjust the platter to achieve a perfect rotational axis. The more expensive TX 1000 does this electronically using a computer. In the Dragon CT the measurements are done by the microcomputer but the adjustment is done mechanically. It's still an impressive looking turntable.

Nakamichi fans will be relieved to know that he is now working on a CD player.



### Budget CD

Currently, (except for Sony) the whole thrust of the Japanese CD production is to the budget market. The name of the game is to get production up and prices down. Technics and Yamaha are leading in this campaign with price points of around \$500 in Japan.

But while they pursue this course, they are losing the support of the audio 'maniac' as audiophiles are called in Japan. The elitists are giving CD a big miss.

Sony is the only company that is looking after the needs of the audio maniac with the CDP 701 player which has separate digital to analogue converters for each channel. This machine costs almost \$2000 here in Australia and does have a demonstrably



Banks of TV sets. Video hi-fi video disc and video synthesizers were very prominent at the show, indicating the trend towards a complete merger of audio and video.

◀ The 'budget' computer turntable. The Dragon CT does away with wow with computer measurement and mechanical adjustment.

better mid range than the popular CDP 101.

Getting back to the Japan Audio Show — virtually all these second generation players are now drawer-loading systems like the Sony/Philips/Marantz. Philips says that the Japanese have found that this is the best way to have a disc spinning because the centre of gravity is working with the disc to create stability. Something Sony and Philips knew from the start.

But all Japanese companies I spoke to denied this was the reason they had shifted to drawer-loading.

They said they adopted the front-loading drawer system because it was slimmer and fitted in better with current hi-fi systems.

Whatever the reason, nearly every new model demonstrated at the show had front


drawer loading, thus probably setting the industry standard.

### Cars and the CD


There were one or two car digital disc players demonstrated but according to all information sources this is unlikely to become a reality for years.

The vibrations in a car are a major problem. But even if they bend all their expertise to beat the vibrations, the discs present another problem that looks unbeatable.

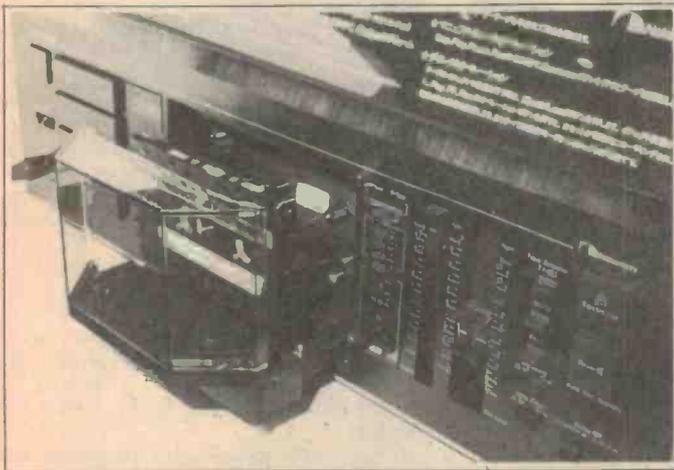The discs warp at around 60°C and the heat in cars in Australia often gets up around 105°C. So the practicality of putting a player in a car is questionable. We are likely to see it incorporated in portables before we see it in a car, says Sony. ▶



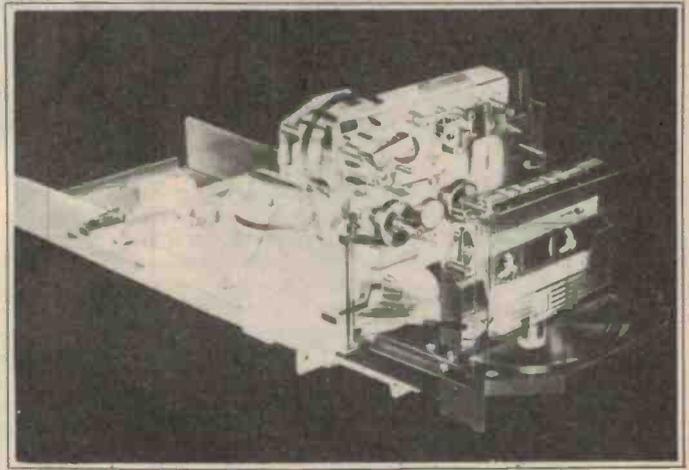The revolving platform. The Nakamichi reverse play physically spins the cassette around and replaces it in the machine.



The mechanics. A view showing internal detail.

# The All Japan Audio Show




Peak/VU level



Sound image



Musical scaling

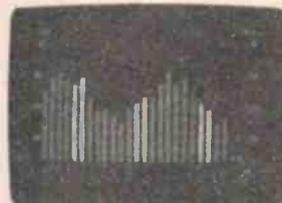

Spectrum analyser



Sound space

## The CD juke box

Denon showed a professional CD juke box that holds around 100 discs and will sell for about the price of one of the more expensive traditional juke boxes.

Technics was rumored to unveil a home juke box at the show that would hold about 10 discs and could be programmed to play any tracks off any discs. But it didn't appear and a spokesman for Technics says that it wasn't ready for the show and is still under development.

Technics is one of the companies to watch over the next year or so in the CD race. A late starter, they are pouring on the pressure to catch up with the leaders Sony, Marantz and Philips. Technics has a brand new five story building in Osaka dedicated to CD development and technology. On the top floor an army of scientists (around 150 would you believe) work with computers designing chips and components for the CD era.

On the next floor they have production lines for the laser diodes, and also a plant capable of producing 200 000 compact discs a month.

Technics produces all the Telarc and A & M discs, and are looking for contracts from many of the leading record companies. They are producing around 100 000 a month currently, and plan to crank the system up to full capacity in the next six months.

The main production lines occupy two other floors. Plastic powder is delivered to the front door and emerges at the back door as a CD player, boxed up ready for shipping.

So expect to see a very aggressive approach to marketing CD players from Technics over the next couple of years. There is a good reason for their interest in CD. They currently have around 30% of the world turntable market and if CD is going to take over from traditional turntables they will want to be in the box seat to make sure they don't lose the business.

## Video hi-fi

But while CD is important at the audio show, the biggest area of interest was video hi-fi. These new video machines give audiophiles and videophiles super high quality audio.

Sound with pictures. JVC's audio video graphic synthesiser has an impressive variety of ways to represent sound graphically, as the illustrations above show.



The dynamic range is claimed to be around 90 dB, and frequency response 20-20 000 Hz. These machines have already taken 20% of video turnover in Japan and look long term as if they will replace all current video recorders in the \$800 and over price bracket.

But while the main purpose of video hi-fi is to be a video recorder, over 40% of these machines bought are not connected to a TV set. They are bought by audiophiles who use them simply as an audio recorder because they are the only analogue system capable of recording CD.

These allow the mix of multi video and audio systems and incorporate sound enhancers as well as video intensifiers.

The video sound processors basically have a noise reducer at 14 kHz, a five-band graphic equaliser, two-band expander, stereo processor for mono recorders, mike mixing, and audio mixing.

## Sound and picture

My favorite gadget of the whole lot was JVC's video graphic analyser. This black box will sell for around \$399 in Japan when released this month. It monitors the audio signal from your hi-fi set and turns it into graphic pictures on your TV set. There are five modes in this JVC unit. The first is a real time spectrum analyser so you can sit back and watch your music translated into a graphic. Or by a flick of a switch it can be turned into colourful VU meters.

These functions, JVC argues, have practical applications for audio enthusiasts who can use them for monitoring performance in recording and replay. But the rest are pure entertainment. One of the modes creates a space trip to music. Even the meteors rocketing past your space ship do so in time to the music.

There are weird shapes that expand sideways in time to the music, or you can have the music translated into a musical

score with the notes dancing onto the screen as the music plays. Very educational, argues JVC. I thought it was great fun and fills the missing link in the audio video marriage.

Eventually, compact discs will have some sort of illustrations incorporated on the discs. There is enough room for half a page of text every second on the discs. That could be used for librettos, or words of a song for a singalong, or even the story of a symphony.

The compact disc will also be able to reproduce still photographs such as the portrait of the pop star, or a graphic to illustrate the song, such as a cannon in the 1812 overture, or even the title of the musical piece.

Whatever form, ultimately CD will have graphics, and Technics is one company pushing Philips to agree to standards as soon as possible. In fact, if you look at the rear of a Technics CD player you'll notice a DIN socket. That is there ready for the day graphics are available with CD. Technics will simply sell an add-on black box. One or two other companies are providing a similar socket.

So with audio linked to pictures what will happen with our old records and cassette tapes? This gadget from JVC fills the gap nicely. When your music doesn't offer a picture from your CD, laser video disc, or video hi-fi, JVC's graphic gadget will do the job instead.

## Sound on chest

Finally as another talking point, mention must go to Pioneer's motorcycle jacket called a Sound Vest. A waterproof tape player fits in one pocket, a booster in another and there is a pair of speakers in the shoulders.

It gives the motorcyclist music on the move without needing to wear headphones. Much safer, if not as peaceful for people around.

# B & W DM 110 loudspeakers

The DM110s are something of an enigma. The performance at the bottom end of the audible spectrum could be improved but generally they perform well. Obviously one of the best speaker buys around.



BOWERS & WILKINS in the United Kingdom have created an enviable reputation over the last decade with their loudspeakers. Their innovative technical approach to research and production is the envy of many of their competitors, but even B & W have to acknowledge that some of their competitors' ideas are worthy of consideration.

New concepts in products we have recently seen from Scandinavia and other European manufacturers have resulted in significant cost savings which have made B & W reassess some of their tried and proven production methods.

An exciting development in production is the use of plastic mouldings for construction of both drivers and cabinets. This makes it easier to mass produce speakers at a cost which decreases at almost the same rate as the quality of the finished speakers improves.

B & W's DM110 loudspeakers are probably one of the best examples of this production philosophy that we have seen since we reviewed the Jamo CBR 1703 loudspeakers (ETI July 1983).

The appearance of this bookshelf speaker

## Louis Challis

system is particularly neat; the designers have incorporated most (but not all) of the features that the user would be seeking at a reasonable price. This has been achieved by using well designed front and rear panels fully moulded from plastic, with dampening and bracing accommodated within the design.

The mounting screw holes, speaker mounting holes, venting ports, panel retention clips for front covers and even the recessed terminal blocks are all accommodated neatly, effectively and most economi-

cally in the design. The two sides, top and bottom are constructed from high density particleboard and covered by simulated American Walnut plastic veneers.

The speakers also make extensive use of plastic mouldings which minimises their cost without significantly prejudicing any of their electro-acoustical performance.

The DM110 uses two drivers in a vertical arrangement with a 26 mm tweeter near the top of the cabinet. The dome and coil

construction of the tweeter is based on a new construction approach; polyamide materials achieve lower distortion and a higher quality than was previously thought possible.

The bass/midrange speaker is a 200 mm driver with a high temperature voice coil supplemented by an impregnated, composite short fibre cone which is mounted near the bottom of the cabinet. This driver has a soft-roll surround which facilitates reasonably large cone excursions. The face of this driver incorporates a coloured retention ring; in the examples we received this was red but the manufacturer's data sheet states that it may also be blue. ▶

Immediately below the bass mid-range driver unit is a 50 mm diameter venting port with a 80 mm port length. The front panel cover is fabricated from particleboard with neatly contoured edges, plastic retention clips and an attractive, open-weave, brown, artificial fibre whose flow resistance is extremely low. The inside of the cabinet uses reticulated plastic acoustical foam for sound absorption.

The back panel incorporates two coloured universal terminals in the moulded well assembly, behind which is attached the crossover network. This particular crossover network is a first order difference filter which is not simple; the designers have managed to incorporate a 'fourth order Butterworth squared' filter that has relatively smooth crossover characteristics which do not appear to detract from the performance of the individual drivers.

### Objective testing

The manufacturer's literature makes many claims for these speakers. Three specifications which immediately caught my eye are: the frequency response is  $\pm 3$  dB from 70 Hz to 20 kHz; the free field cut-off frequency is 60 Hz; the second harmonic distortion at 90 Hz for 96 dB sound pressure level at one metre is less than 3%.

These claims are very enticing, especially for a pair of speakers selling at \$399. The back page of the manufacturer's brochure,

it should be noted, shows a picture of a CD disc and the equally enticing words 'Digital Monitors'.

We measured the acoustical performance of one pair of DM110s and then measured a second pair of these speakers.

In the anechoic room our first hopes were dashed when the frequency response proved to have a  $-3$  dB response of only 90 Hz at one metre on the axis. However, the frequency response at higher frequencies is remarkably flat all the way up to and beyond 20 kHz. In fact, the frequency response is so flat that it makes many much more expensive speakers pale by comparison.

Obviously, with the speakers mounted on a stand (which does not come with the speakers) at the right height above the floor, this low end frequency response would be readily improved.

The manufacturer has made a brash statement that the claimed free field cut-off frequency is 60 Hz; we could not achieve this, no matter how hard we tried.

The claimed distortion characteristics for these speakers were our next problem. We tested four speakers but their performance did not come anywhere near the performance claimed in the brochure.

At frequencies above the knee of the cut-off frequency i.e. 115 Hz or above, the distortions most certainly fall within the range claimed by the manufacturer. However, at

frequencies below this the selective cut-off characteristics of the speaker response results in a significant boost in the distortion products. It was physically impossible (at least in the units that we tested) to achieve the manufacturer's claimed performance.





By this time we were a little bit disturbed that we had really come upon a 'lemon' and proceeded with the testing with even more trepidation than that which prevailed when we started our testing.

However, from that point on the test results assumed a completely different character. The tone burst testing revealed characteristics which were extremely good and which exemplified a speaker system with excellent transient characteristics.

The phase response proved to be remarkably flat and was a credit to the speaker designers. The decay response spectra also turned out to be remarkably good and was extremely clean right across the important high frequency region.

An examination of the impedance curve revealed what we believe is the basic problem with the DM110s; the designers have tried to achieve far too much performance with a cabinet that has a volume which is just too small.

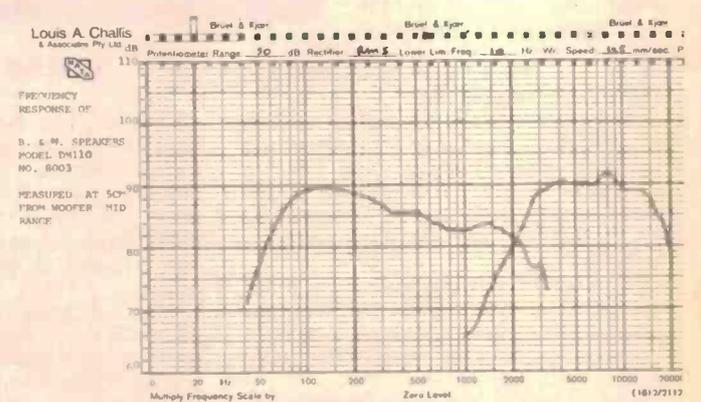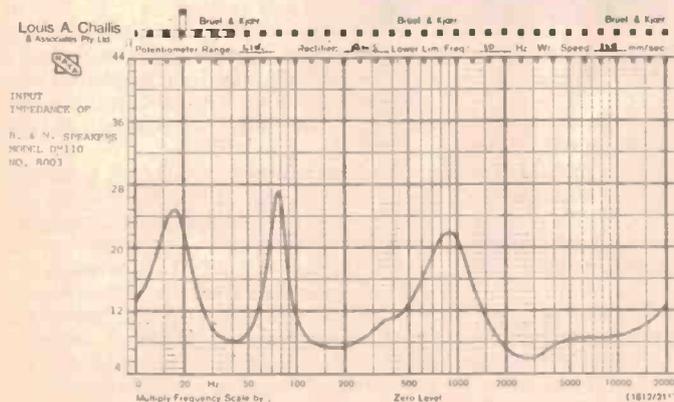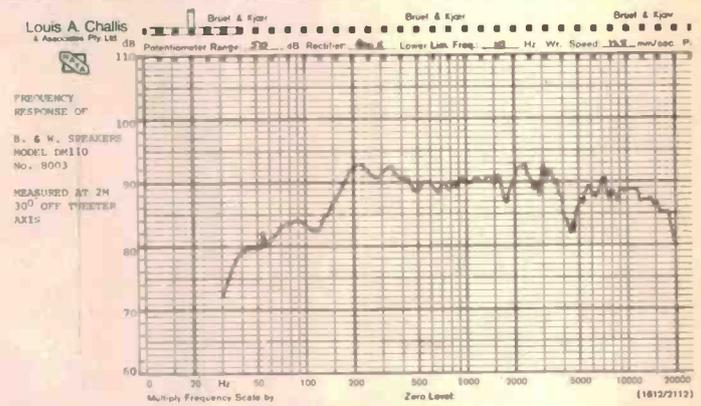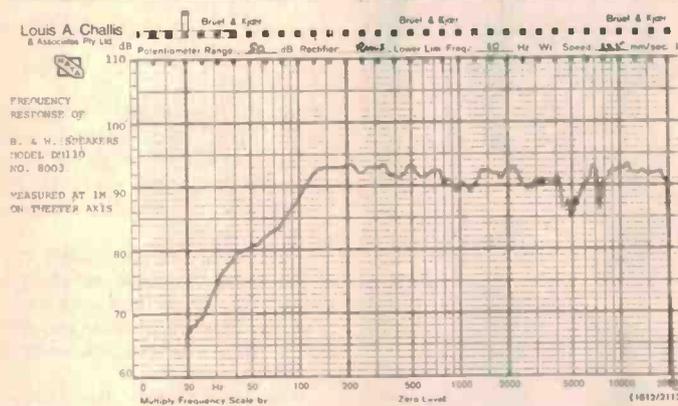A close look at the impedance curve revealed that the fundamental cabinet resonance occurs at 15 Hz, which is far too low; the second order resonance occurs at 80 Hz, which is not a particularly



## MEASURED PERFORMANCE OF B & W MODEL DM110

SERIAL NO. 08003



**FREQUENCY RESPONSE:** 90 Hz - 20kHz  $\pm$  3 dB  
**CROSSOVER FREQUENCY:** 2.5kHz  
**SENSITIVITY:** 6.7 VRMS = 5.6 Watts (nominal into 8 ohms)  
 (for 90dB average at 2m)

### TOTAL HARMONIC DISTORTION:

Total harmonic distortion at specified sound pressure levels (at 1m)

	80Hz	100Hz	115Hz	125Hz	150Hz	1kHz	6.3kHz	%
90dB	4.2	2.0	1.1	0.9	0.8	0.8	0.8	%
93dB	6.0	4.2	1.3	0.9	0.9	0.7	0.7	%
96dB	36.0	24.0	2.1	1.1	0.9	0.6	0.7	%

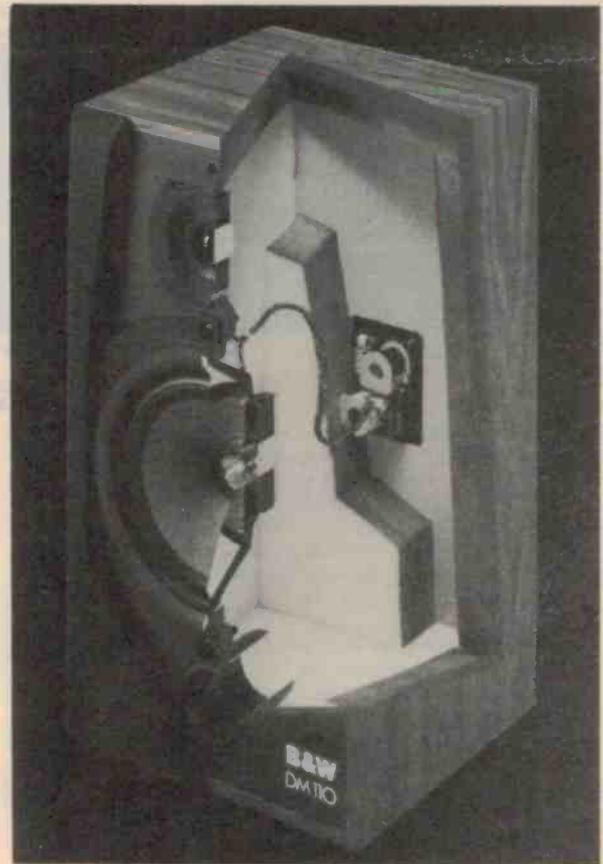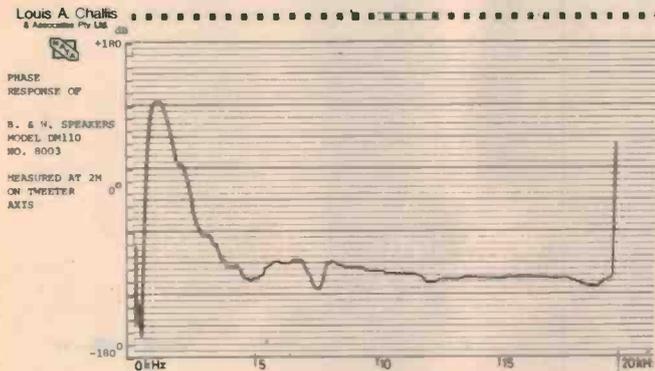**INPUT IMPEDANCE:** 100Hz 11.2 ohms  
 1kHz 21.2 ohms  
 6.3kHz 8.5 ohms  
 Minimum at 2.4 kHz 6.0 ohms



inappropriate frequency and the speaker crossover takes place at approximately 2.5 kHz.

The minimum impedance is eight ohms, except in the region of the crossover frequency, where it drops down to 6.5 ohms. This means that this speaker system can be easily paralleled with a second eight ohm speaker system, without embarrassing most amplifiers.

Taken overall, and with the price of the speakers clearly in mind, the performance that the designers have achieved is still very good.

### Subjective testing

The subjective evaluation of the speakers took considerably longer than it would normally have done as one of my children latched onto the DM110s whenever I wasn't listening to them. They fitted on his bookshelf as if they had been designed for that role. This, of course, is what B & W intended; they realised that most users want a set of speakers with just those dimensions and costing no more than \$399.

The first thing I noticed was that provided you don't play very loud rock-n-roll, or extended passages containing drum or organ music, or treat the speakers as having the potential to replace a set of studio monitors, then the results are exhilarating and on occasions almost astounding.

The subjective assessment of the speakers proved to be a far less difficult task than I had imagined. I started the subjective assessment by comparing their performance against a set of B & W 801s, a pair of Quad electrostatics (Vintage 1970) and three other speaker systems which are renowned for their performance, albeit at three to five times the price.

### B & W DM110 LOUDSPEAKERS

<i>Dimensions:</i>	490 mm x 260 mm x 250 mm.
<i>Weight:</i>	8.7 kg
<i>Price:</i>	Rrp \$399 per pair
<i>Manufacturer:</i>	B & W Loudspeakers, Meadow Rd., Worthing UK.
<i>Distributor:</i>	Convoy International, 400 Botany Rd, Alexandria NSW 2015. (02)698-7300.

As I was in the middle of evaluating a series of new CD players I thought it appropriate to use them to evaluate the DM110s, particularly as the manufacturer claims that these speakers were designed primarily to be used with CD players.

The two discs that I chose are representative of the best of the new digitally recorded discs. The Phillip's disc, Mozart Piano Con-


certo in B Flat with the Academy of St. Martin-in-the-Fields (No. 400 018-2), revealed a magnificent stereo imaging capability and a quality of sound which was positively exhilarating. This was achieved at sound levels up to, but not exceeding, 100 dB. At higher levels the distortion tended to be unacceptable.

The Vertigo disc with Communique by Dire Straits (No. 800 052-2) was a sample disc provided by Phonogram Ltd. It contains some excellent passages of soft rock which the DM110s coped with quite happily at modest levels (less than 90 dB at one metre). However, they complained audibly at higher levels in the presence of low frequency content.

The results of this testing revealed that the DM110s can hold their own against almost any speaker system where the important or dominant frequency content is above 110 Hz, or the sound levels at two metres are kept below 85 dB (unweighted). The transient performance of these speakers is quite exceptional and on all of the test materials to which I listened I was impressed by their fidelity and clarity.


Their ability to handle speech is particularly good and as speech monitors they are really excellent. The transient performance is exemplified by the decay response spectra which is the best performance we have seen in any speaker system selling under \$600. ▶

# SOUND REVIEW

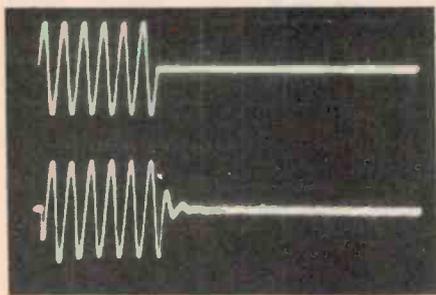


Output at 100 Hz (20 ms/div).

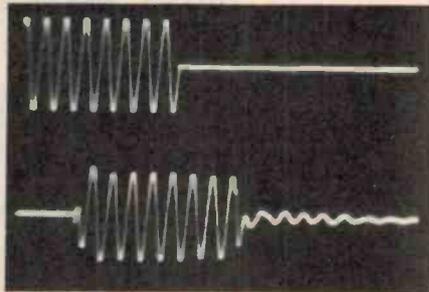Tone burst response of the B & W DM110 loudspeakers. For 90 dB steady state sound pressure level at two metres on axis.



Output at 1 kHz (2 ms/div).

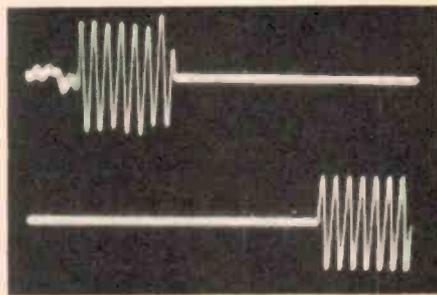Upper trace is electrical input. Lower trace is the loudspeaker output.




Output at 6.3 kHz (0.5 ms/div).

## Conclusion

Yet for all this, the performance at the bottom end of the spectrum is in no way comparable with the performance at the top end. At frequencies below 110 Hz you tend to get what you pay for and in the case of the DM110s you are not paying for studio monitors or for a pair of large vented enclosures.


The basic problem with the DM110s is the conflict of purpose in the design which attempts to use a vented enclosure where a sealed enclosure might well just have the edge. Be that as it may, it is obvious that B & W could achieve a dramatic breakthrough by incorporating the same design philosophy in a larger member of the family. This would remove the obvious limitations and achieve the attributes which we are all seeking.

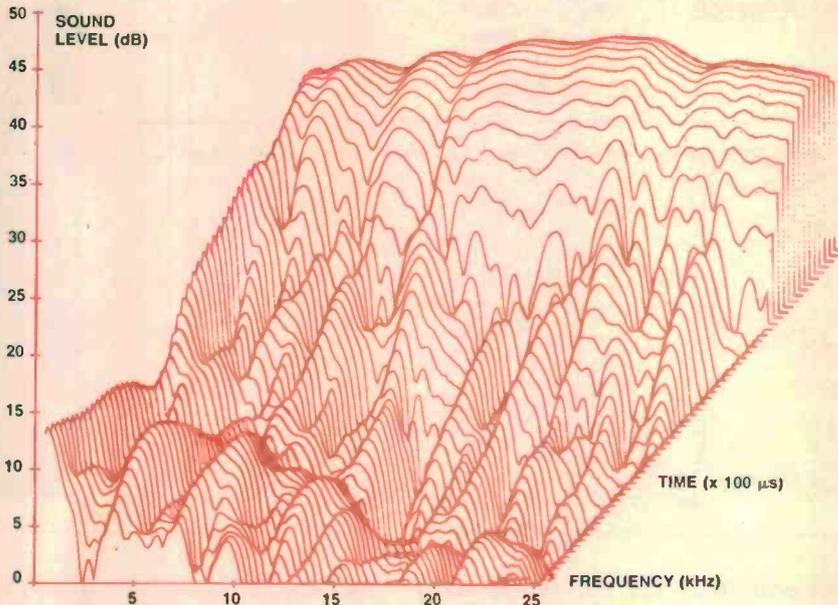The DM110s are currently something of an enigma; they provide a general performance which is excellent but with obvious limitations which really only affect the performance at the bottom end of the audible spectrum. Even with these limitations clearly in perspective, the DM110s are still obviously one of the best speaker buys around at the moment.




Decay response spectra. Extremely good above 5 kHz; below 5 kHz the picture tells a different story.

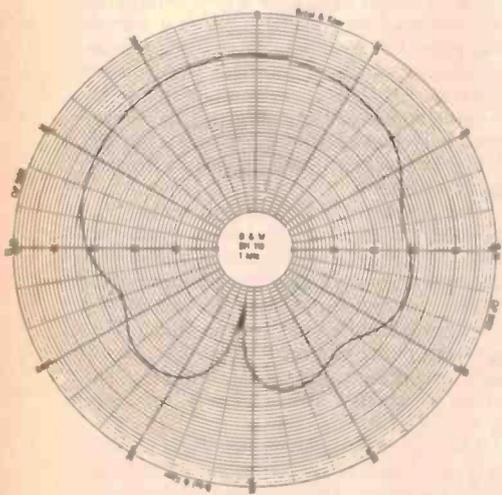
Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



1 kHz

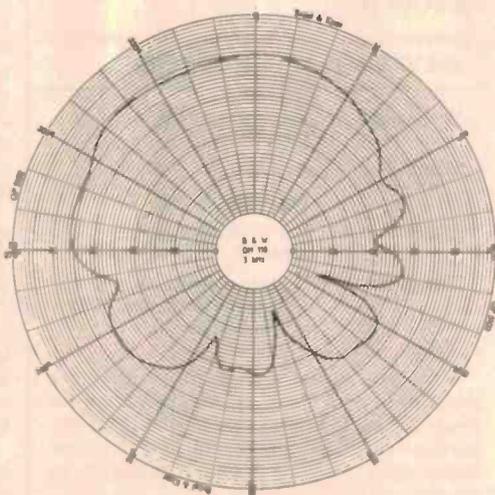

3 kHz

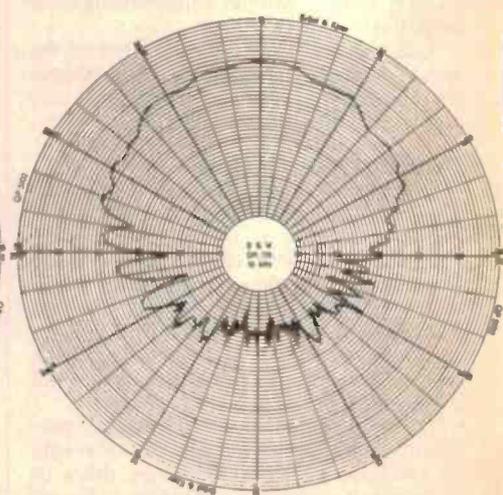

10 kHz

B & W DM110 polar response curves.

*“I want the best  
I can buy for  
my dollar.”*

We at Len Wallis Audio hear that statement nearly every day.

And, with great satisfactions, we know how to give you value for money.

Figures prove it.

In a Sydney-wide survey, over 98% of Len Wallis Customers stated that the knowledge and experience of the sales staff helped decide their purchases above and beyond their satisfaction.

And they in turn recommended their friends to purchase hi-fi equipment from Len Wallis Audio. That amounted to almost 35% of sales by referral.

The Len Wallis Sound Studio and staff show you exactly what your dollar can buy.

We know the ins, outs and capabilities for the equipment listed below.

Please don't come and see us . . . come and *hear* us. We know what we're talking about, and you'll *understand* what we're talking about.

We're all after the same thing . . . satisfaction of a good sale.

*Len  
Wallis  
Audio*

**When you're serious about hi-fi.**

9 'The Village' 43 Burnsbay Road,  
Lane Cove, NSW 2066  
Ph. 427-1204, 427-1205

Open Thursday nights and all day Saturday.

Pernaux, Accuphase, Akai, Yamaha, Acoustic Research, Aiwa, N.A.D., Dual, System-Dek, Spondor, Rogers, Denon, Audio Technica, Meridian, Rega Pllamar, Sota, Nakamichi, B & W, Pro-Ac.

# 1984\* SAVINGS START HERE!

## DICK SMITH HANDBOOKS

Data for the professional and weekend professional!

### Australian Semiconductor Handbook

This great book contains data, suggested circuits & new information on an enormous variety of commonly-used devices. Cat B-4200

### Australian Radio Frequency Handbook

This superb publication from Dick Smith Electronics gives the how, when, where, why, which and whee of this exciting hobby. Cat B-9600

### Marine Radio Handbook

The Australian Marine Radio Handbook... all the facts and figures for fitting and using a marine radio. Cat B-9604

### DON'T THROW 'EM BIND 'EM!

Magazines are too expensive to throw out. Keep them for later reference with our deluxe binders. Fits EA, ETI, AR, ARA, Your Computer. Cat B-4045

### INTO COMPUTERS? GET INTO THESE!



ALL AT DICK SMITH  
LOW LOW PRICES!

Z-80 CPU	Z-9100	\$8.95
Z-80 PIO	Z-9101	\$8.50
5303 UART	Z-9204	\$6.95
2513 Character Generator	Z-9206	\$22.50
2516 2K EPROM	Z-9207	\$6.95
2532 4K EPROM	Z-9208	\$14.75
2732A EPROM	Z-9209	\$17.50
2102 2K Static RAM	Z-9302	\$2.50
2114 4K Dynamic RAM	Z-9306	\$3.50
4116 16K Dynamic RAM	Z-9310	\$3.95
4164 64K Dynamic RAM	Z-9312	\$10.95

### SEMI SAVERS!

AY-3-8112 Tuner/Clock IC	Z-6832	\$8.75
uA709 Op Amp	Z-6352	60¢
SC-01 Synthesiser	Z-6818	\$5.95
95H90 Counter/prescaler	Z-5360	\$9.95
MM5369 50Hz divider	Z-5782	\$2.75
EYRN		

Stock up now  
while these  
bargains last!

FANTASTIC  
SAVING!

### OUR MATRIX PRINTER

Wow! A \$100 saving on our most popular printer - the famous Seikosha GP-100 Dot Matrix Printer. The ideal low-cost printer for all computers - and now it's even lower cost! Suits standard 240mm wide fan-form paper.

Was amazing value at \$395.00  
Now Fantasma Dicksagorical value at only...

**\$295**

Cat X-3250



**\$100  
OFF**

ALL NEW  
ALL MODE  
ALL POWERFUL...

### FT757GX

NOT \$1399!  
NOT EVEN \$1199!

OUR PRICE ONLY **\$999**

Cat D-2940



### NEW EVEREADY BLACK PREMIUM BATTERIES

Yes! A heavy duty battery at a light duty price... and because we have such an incredible battery turnover, you KNOW they're fresh!



S-3270 BLACK	4xAA	\$2.35
S-3272 BLACK	2xC	\$1.60
S-3274 BLACK	2xD	\$1.95
S-3276 BLACK	9V	\$1.80

JUST RIGHT FOR ALL  
THOSE BATTERY  
OPERATED THINGS YOU  
GOT FOR CHRISTMAS!

### Avoid this with the Dick Smith Back-up Sensor

Blind spots in your rear vision? Reverse park by the touch method? Easy to fit and lets you forget about ding! \$59.00  
Cat A-8520

SCOOP  
PURCHASE

### QUALITY PHILIPS

#### Car Speakers

Twin cone for really thrilling sound! 4 ohms impedance and 20 W rating. \$40? No! \$30? No! Our crazy price is just...

**\$9.95**

Cat A-6988

AMAZING!

### LEDS

PREMIUM  
QUALITY

At last! LED's matched for brightness & colour characteristics for when appearance is important. Sure they cost a little more... but top quality is worth the extra!

		Price 10
Z-4077	3mm RED	30 25
Z-4079	3mm GREEN	35 30
Z-4081	3mm YELLOW	50 45
Z-4083	3mm ORANGE	50 45
Z-4085	5mm RED	30 25
Z-4087	5mm GREEN	35 30
Z-4089	5mm YELLOW	40 35
Z-4091	5mm ORANGE	40 35
Z-4093	5mm RED	35 30
Z-4095	5mm GREEN	35 30

### HIGH QUALITY DRILL SET AT A LOW PRICE!

At last! A high quality drill set for all uses. Famous Frost brand (13 pieces) in handy plastic pack Cat T-4801

VALUE \$15.50  
AT

See page 117 for  
full address details.

# DICK SMITH

**THAT'S THE WAY TO START THE NEW YEAR!**

**LOWEST PRICE IN AUSTRALIA!**

FOR QUALITY TOP NAME! **\$12<sup>50</sup>**

**POLAROID VIDEO CASSETTES**

WARNING! You may see unknown brands at a lower price. they can cause \$\$\$ damage to your recorder heads as they are abrasive. Stick to the top name brands.

VHS 3hr Cat C-3410  
BETA 3hr Cat C-3415

Now you can record **VIDEO TO VIDEO**

Having trouble with video leads? No more! This incredible video lead pack will match ANY video to ANY video with its unique system!



was \$18.95

**\$14<sup>95</sup>**



WANT TO PUT TOGETHER A LOW COST PUBLIC ADDRESS SYSTEM?

**NEW DICK SMITH PA AMP**


Fantastic value for youth groups, fetes, churches, etc - quality PA Amp has microphone & line inputs, operates from 12V DC or 240V AC (so it will go anywhere). Huge 20W output./ Cat F-2035

**\$110<sup>00</sup>**



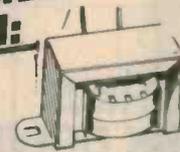**HOBBYIST TRANSFORMER BARGAIN:**

12V and 4 amps output - think of the huge range of uses! Battery chargers, power supplies, paper weights . . . and look at the ridiculous price!



NORMALLY \$15.00 or more

**\$7<sup>50</sup>**

**WHILE STOCKS LAST**

Cat M-3700

**ARLEC SUPERTOOL**

It polishes! It cuts! It grinds! It engraves! It sands! It mills! It drills! It's what every hobbyist has always wanted!

Now from Arlec, The Fantastic supertool makes a super hobbyist! Cat T-4754



**\$39<sup>95</sup>**

WHY PAY MORE

**WHY PAY MORE! COMPUTER CONNECTORS**

**S-100 BUS EDGE CONNECTOR**

Standard 100 pin socket for S-100. High contact life for maximum efficiency. Cat P-2670

**\$40<sup>95</sup>**

**'D' TYPE PLUG**

25 pin plug for RS-232C port and Sorcerer parallel port. Cat P-2690

**\$3<sup>95</sup>**

**'D' TYPE SOCKET**

25 pin socket for RS-232C port and Sorcerer parallel port. Cat P-2691

**\$4<sup>75</sup>**

**PRINTER PLUG**

57N-36 type, suits most printers. With cover. Cat P-2680

**\$19<sup>95</sup>**

**3V, 6V, 9V DC (200mA)**

The three most used voltages for battery powered equipment - simply plug in & save battery dollars! Cat M-9525



**\$10<sup>95</sup>**

**Ni Cad BATTERIES**

NiCads work out much cheaper in the long run because they can be recharged up to 200 times. Rated at a massive 500mA/h, this battery is suitable for almost all devices using standard batteries.



AA size Cat S-3300

**\$2.75**

C size Cat S-3302

**\$12.40**

D size Cat S-3304

**\$13.20**

9V Cat S-3307

**\$16.95**

**DICK'S BULK BARGAIN BUYS!!!**

**TOP VALUE CERAMIC CAP. PACK**  
\$7 VALUE

**TOP VALUE METAL FILM RESISTOR PACK**  
WORTH \$18

**TOP VALUE ELECTROLYTIC CAP/PACK**  
WORTH \$13 AROUND

**TOP VALUE RESISTOR PACK**  
\$12 VALUE

**TOP VALUE POLYESTER CAP. PACK**  
WORTH \$13

**GET AN ANSWERING MACHINE FOR XMAS?**

Avoid hang-ups! Use the amazing Ape Tapes. Your callers will be enjoying the voices so much, they won't hang-up - and they will leave their message! Tape contains 12 different voices.



Cat Y-2172

**\$8<sup>95</sup>** each

**STUDIO QUALITY ELECTRET MICROPHONE**

When you want really top quality, this is it. As used by bands, etc. Low impedance, complete with cable. A bewdy!



Cat C-1055

**QUALITY MIC LEAD**

Huge 20m length of quality mic-cable fitted with Cannon-type plugs & sockets. Cat W-1100

**\$29<sup>95</sup>**

**CERAMIC CAP. PACK**

Over 60 top quality ceramics, none less than 50VW, some as high as 630VW. Includes selection from complete range 10pF to 0.1uF. Cat R-7050

**\$4<sup>75</sup>**

**METAL FILM PACK**

Our new 1% metal film types in a computer selected pack. Now there's no excuse not to use 1% resistors in all your projects: especially at this price! Cat R-7015

**\$21<sup>00</sup> ONLY \$9<sup>95</sup>**

**ELECTROLYTIC CAP/PACK**

55 top quality single ended electrolytics. Save around \$5.00! 2.2-470uF. Voltages from 10 to 25. Cat R-7030

**\$6<sup>75</sup>**

**RESISTOR PACK**

300 1/4 watt types worth \$12.00! 60 values, quality 5% types. Cat R-7010

**\$12<sup>00</sup> ONLY \$5<sup>90</sup>**

**POLYESTER CAP. PACK**

Top quality greencaps. 100V ratings. Selected values from .001 to 0.22uF. 60 in all. Cat R-7040

**\$8<sup>95</sup>**

**Electronics**

**PRICES LIKE YOU HAVE A 'BIG BROTHER' IN THE BUSINESS!**

# TANDON DISK DRIVES



## TANDON NEW EIGHT-INCH THINLINE DISK DRIVES


- Direct drive.
- Proprietary, high-resolution, read-write heads patented by Tandon.
- D.C. only operation—no A.C. required.
- Industry standard interface.
- Three millisecond track-to-track access time.

## TANDON MODEL TM500 SERIES WINCHESTER DISK DRIVES

Tandon's low cost 5¼" rigid disk drive features an on-board microprocessor which calculates the optimum positioning algorithm, yielding an Average Access Time of 110 milliseconds. This product family includes 1, 2, and 3 platter models with unformatted capacities of 6.4, 12.8, and 19.1 megabytes, respectively.

Up to four Tandon TM500's can be daisy-chained on a single bus, which provides a capability of up to 76 megabytes of on-line storage (unformatted) in a single system.

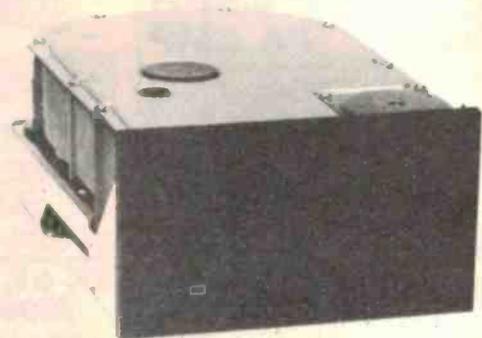These drives are compatible with controllers that use an industry standard interface (ST 506).



## Tandon Model TM-100 Mini-Floppy Disk Drives


Tandon's TM-100 family of mini-floppies offer the absolute highest storage capabilities of any 5¼" high-speed, random access disk drive available in two single head and two double head models, all double density.

**Unsurpassed Storage Capacity**—Up to an incredible 1000K bytes information on 160 tracks. Recording density is 5877 BPI.

**Advanced Dual-Head Design**—Tandon Magnetics has for years been the leading designer and supplier of read/write heads to most major disk drive manufacturers.

**Increased Throughput**—Tandon's TM-100 have a track-to-track access time of only 5 milliseconds (an incredible 3 milliseconds double track density).

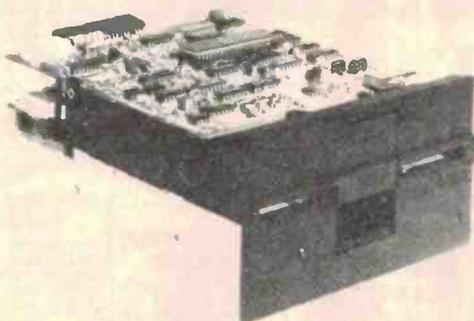**Proven Reliability**—Designed for total reliability, as demonstrated by more than 50,000 production models in operation.



**AE ADAPTIVE  
ELECTRONICS P/L**

418 St. Kilda Rd. Melbourne, 3004. Phone (03) 267 6800  
Sydney: Phone (02) 419 5579. Newcastle: Phone (049) 23 343

# JUDGE RULES SOFTWARE NOT COPYRIGHT

Justice Beaumont of the Federal Court, in an action brought by Apple Computer Australia against Computer Edge Pty Ltd over the distribution of 'fake' Apples, ruled that none of the computer programs Apple claimed to hold copyright over was a literary work within the meaning of the Copyright Act.

"In my view, a literary work for this purpose is something which was intended to afford either information or instruction or pleasure in the form of literary enjoyment.

"The function of a computer program is to control the sequence of operations carried out by a computer", the Judge said.

David Roman, Apple Computer Australia's marketing manager was reported to be 'disappointed' at the result. Apple are likely to appeal.

The ruling, handed down in December last year, ended a seven-month court battle between Apple and Computer Edge who were selling the 'Wombat', a Taiwanese-made personal

computer with many features similar to the Apple and incorporating operating system software alleged to be copies of the Apple OS.

Apple has a worldwide policy of taking action against manufacturers and distributors of look-alike computers, all of which have been successful to date in other countries, notably the US (against Franklin), South Africa and Taiwan.

This decision marks the first time Apple has lost such a case anywhere in the world.

Mike Suss, Director of Computer Edge, was 'ecstatic' over the result. He plans to start manufacturing Wombat computers locally this year.

The tape transport is available in vertical, horizontal or desktop mounting. Data recording is nine-track, and all drive support up to 26 cm reels.

IDT has also added a new 13 mm magnetic tape subsystem for the IBM/PC and XT users.


The TD-1012/PC-STR is a complete 13 mm subsystem using the TD-1012 transport in both the start/stop (12.5 ips) and streaming mode (100 ips) and includes basic application software.

For further details, contact Mostyn Enterprises, 35 Alexander Street, Dundas NSW 2117. (02)871-6297.
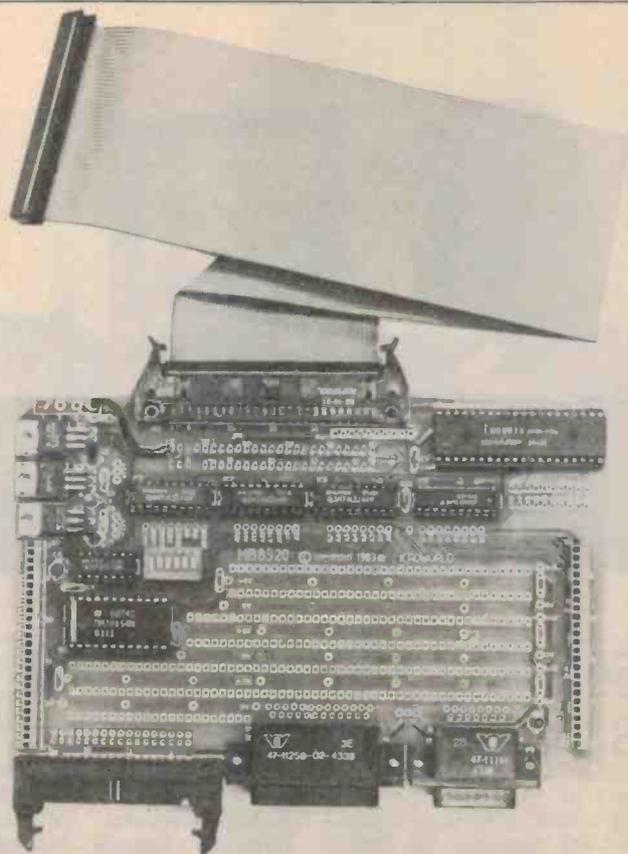
## IDT TAPE SUBSYSTEMS

Innovated Data Technology (IDT), developer and manufacturer of tape transports and intelligent peripheral systems, has introduced two new 13 mm nine-track 1600 cpi, IBM, ANSI, ECMA and ISO-compatible magnetic-tape systems for DEC Unibus and Q-bus computer systems.

The tape subsystems utilise the IDT Series 1012 Virgo, which operates at 100 ips 'streaming' and 12.5 ips 'start/stop'.



## MICROBEE EXPANSION EXPERIMENTER BOARD

Applied Technology has come up with an expansion board to suit all you 'Bee owners who aren't afraid to wield a soldering iron and wish to experiment with all sorts of circuits and add-ons.

The board incorporates the following facilities: buffers for the address lines, bidirectional data buss buffer, buffers on outgoing control lines, decoding for 16 ports, two parallel ports using the spare ports decoded on the Microbee and on-board voltage regulators to give +5 V, +12 V and -12 V.

Other features include: input/output sockets, a generous prototyping area and two edge connectors to add an extra board for further experiments.

Applied Technology kindly gave us production board No. 1 for a quick look just as we went to press. It's a well-manufactured board, has a dry film solder mask and topside silk-screened overlay so you 'know where you are' on the board.

To make full use of it requires

making a small mod. to your 'Bee to use the spare internal ports. It's simple; cut two tracks and add two links — voila! Plug in the expansion board and you have two extra parallel I/O ports to use.

Ports available on the expansion board are nos 4, 5, 6 and 7 linked together, and port 0A, plus 16 ports located at any 10 hex boundary between 20 and 70 hex. That's a total of 21 ports. If this isn't enough, you can add another decoder to get a further eight or 16 ports.

Applications — are up to you. Ours came with documentation outlining a door bell and burglar alarm system. We think this board has lots of possibilities. Sorry, no firm price yet, but it shouldn't strain the cash resources of most keen computerists.

Further details from Microbee dealers or direct from Applied Technology, 1 Pattison Ave, Waitara 2077 NSW. (02)487-2711.



## SANYO'S ANSWER TO IBM

Sanyo Data Systems will launch its answer to IBM's personal computer this month, the MBC 555.

The MBC 555 is seen as a true personal computer, as distinct from Sanyo's range of business computers.

The new computer features an 8088 16-bit processor and 128K memory, expandable up to 256K. The computer's 32K video RAM means the MBC 555 can also provide high resolution graphics (640 x 200 dots) when using the optional high resolution monitor. Dual disk drives give disk storage of 320K, and an additional 320K

option will be available early in 1984.

"We see the MBC 555 as a real alternative to IBM's personal computer," said Mark Johnston, Sanyo's Managing Director. "It is compatible with the IBM, yet offers the additional incentive of being half the cost of the IBM.

Mr Johnston said the MBC 555 is the first of three new computers to be launched by the company towards the end of the year.

For further information, contact Sanyo Data Systems, 127 Walker St, North Sydney NSW 2060. (02)929-4644.

## T/MAKER COMBINES WORDS AND FIGURES

Alfatron has started to distribute the T/Maker software package in Australia. It is available for both CP/M 80 and CP/M 86 plus several other operating systems.

T/Maker is used for word processing, as a spreadsheet calculator, bar charting, file management, list sorting and tallying. It allows the user to manipulate words, numbers and lists singly or all at once.

The word processing is done with a screen editor which allows configuration to use cursor control keys and/or specific function keys.

Alfatron has also been granted

the distribution rights to the popular card cage and board from Electronic Solutions in the United States. These products include multibus card cages from 3 to 72 slots capacity in both horizontal and vertical mounting types.

Industrial and heavy-duty cages are also available for standard racking systems. Cages are available with two different spacings between cards to suit wire wrap cards.

For further details, contact Alfatron, 1761 Ferntree Gully Road, Ferntree Gully Vic. 3156. (03)758-9000.

## NEW ATARI MODULES

Futuretronics, the Australian distributor for Atari, has announced the release of three new expansion modules for the Atari.

'Paint' is a program that allows the user to create computer graphics without having to program anything. 'Paint' turns the computer screen into a canvas and the joystick into a paint brush. Available on diskette, the program allows the user to mix colours, make patterned paint, draw perfect lines, circles and rectangles and even zoom in to do close work and zoom out again to see the results.

Atari Logo is now available in a 16K cartridge that can be used on an Atari home computer with as little as 16K RAM memory.

This is the only full-featured version of Logo that can be used with so little memory.

The third new expansion module is an external microprocessor upgrade that allows high-powered CP/M software to be used with all models of Atari home computers as it is fully compatible with either the Atari 810 or Atari 1050 disk drives. The CP/M add-on offers 40 or 80-column video display output on a switchable basis.

Also planned for release is the Atari Expansion Box and the 64K Memory Module. For further information, contact Futuretronics Australia Pty Ltd, 1076 Centre Road, Oakleigh Vic. 3166. (03)579-2011.

## CICADA MODEM-PHONE

Centre Industries is following up the successful Cicada 300 baud data modem with a 'new, improved' version featuring an integrated telephone.

The new Cicada 300T can be simply installed by the purchaser, without any need for a Telecom technician.

According to Centre Industries sales manager, Mr George Weisske, pricing on the new 300-baud modem with telephone will be within about \$40 of the current \$229 recommended retail price of the Cicada 300 model, which has now been on the Australian market for about nine months.

The Cicada 300 has developed a strong share of the modem


market, with substantial government interest in addition to hobbyists and business users.

The new Cicada 300T is a compact, answer-and-originate unit designed to plug directly into a standard telephone wall socket for computer interface, using either an RS232C or a V24/V28 system.

The modem is aimed at home and small business users of local, STD and ISD facilities for inter-computer communication. The unit measures 203 x 152 x 63.5 mm and holds Telecom approval number C83/37/1011.

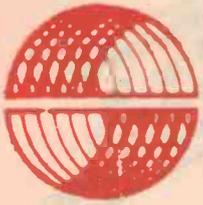For further information, contact Centre Industries, P.O. Box 184, Brookvale NSW 2100. ▶





**SPHERE**  
COMPUTERS

PRESENTS  
AN INTELLIGENT  
TERMINAL

**FANTASTIC VALUE**



**Keyboard**

- Detachable, capacitive, typewriter-style keyboard
- N-key rollover with auto repeat capability
- 4 LED indicators for caps lock, on line, block mode and keyboard lock/protect
- Audible keyclick enable/disable
- Auto repeat enable/disable
- Keyboard lock enable/disable
- Repeat rate 20 characters per second
- 5 cursor control keys, 10 editing function keys with 14-key numeric key-pad

**Communication**

- Code: 128 ASCII characters
- Baud rate: 75, 110, 150, 300, 600, 1200, 1800, 2400, 4800, 9600, 19,200
- Parity: Odd, even, mark, space
- Operating Mode: Full duplex, half duplex or block mode
- Interface: EIA RS-232C or 20-mA Current Loop

**OEM  
DEALERS WELCOME  
SPECIFICATIONS**

**Emulation**

- LEAR SIEGLER ADM-3A, HAZELTINE 1500, ADDS VIEWPOINT

**Screen Presentation**

- Display format: 24 lines x 80 characters
- Display unit: 12-inch, non-glare Green CRT
- Character type: 7 x 9 dot matrix

- Refresh rate: 50/60Hz

- Character set: 96 ASCII characters, 15 graphic symbols, 32 control character symbols

- 5 screen attributes: Blink, underline, blank, reverse, dual intensity

- Cursor type: Selectable slow, fast blinking or steady cursor, block, underline or invisible cursor

**Editing Function**

- Cursor: up, down, left, right, home
- Insert character, delete character, insert line, delete line, erase to end of line, page and field, field tab, field back tab, column tab, column back tab, block mode on/off, protect mode on/off, graphic mode on/off, clear unprotected.

**External Control**

- Power on/off
- Contrast adjustment
- Baud rate
- Parity and data format
- End of message
- Emulation mode
- Refresh rate
- Half duplex or full duplex
- Auto line feed
- Auto new line
- EIA or 20-mA Current Loop
- Reverse video or standard video

ENQUIRIES FROM: AVAILABLE FROM OFFICES AND SHOWROOM **PARIS RADIO ELECTRONICS**, SHOP 1, 165 BUNNERONG ROAD, KINGSFORD, NSW 2032. TEL. (02) 344 9111. TELEX AA22579.


**MAGRATHS ELECTRONICS** 55 A'BECKETT ST, MELBOURNE, 3000 VICTORIA. TEL. (03) 347 1122.

# RITRONICS WHOLESALE

425 HIGH STREET NORTHCOTE 3070 MELBOURNE (03) 489-8131  
48-50 A'BECKETT STREET MELBOURNE (03) 347-9251

This Month Only  
\$695 inc. tax  
Buy one to build  
during your Xmas holidays

## "BIG BOARD II"

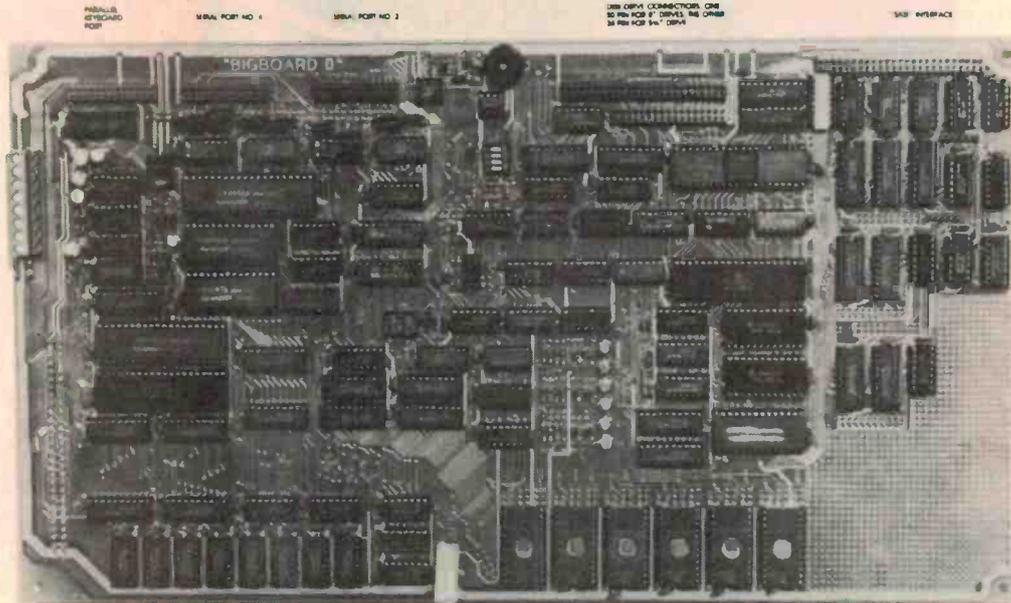

EPROMs  
shown only  
for clarity.

STD  
Bus  
Connector

Prototyping  
Area

Jim Ferguson, the designer of the "Big Board" distributed by Digital Research: Computers, has produced a stunning new computer called "Big Board II", it has the following features:

### 4 MHz Z80 — CPU AND PERIPHERAL CHIPS

The Ferguson computer runs at 4 MHz. Its monitor code is lean, uses Mode 2 interrupts, and makes good use of the Z80-A DMA chip.

### 64K DYNAMIC RAM + 4K STATIC CRT RAM + 24K E(E)PROM OR STATIC RAM

"Big Board II" has the three memory banks. The first memory bank has eight 4164 RAMs that provide 60K of user space and 4K of monitor space. The second memory bank has two 2Kx8 SRAMs for the memory-mapped CRT display and space for six 2732 As, 2Kx8 static RAMs, or pin-compatible E(E)PROMs. The third memory bank is for RAM or ROM added to the board via the STD bus. Whether bought as a bare board, a full kit, or assembled and tested, it comes with a 450ns2732 EPROM containing the monitor.

### MULTIPLE-DENSITY CONTROLLER FOR SS/D5 FLOPPY DISKS

The new Ferguson single-board computer has a multiple-density disk controller. It can use 1793, 1797, or 8877 controller chips since it generated the signal with TTL parts. The board has two connectors for disk signal with 34 pins for 5.25" drives, the other with 50 pins 8" drives.

### VASTLY IMPROVED CRT DISPLAY

The new Ferguson SBC uses a 6845 CRT controller and 8002 Video Attributed controller to produce a display that will rival the display of quality terminals. Characters are formed by a 5x7 dot matrix on 15.75 KHz monitors and 7x9 dot matrix on 18.60 KHz monitors. The display is user programmable with the default display 24 lines of 80 characters. 8002a chip supplied for 18 to 60 KHz monitors.

### STD BUS CONNECTOR

The Ferguson computer brings its bus signals to a convenient place on the PC board where users can solder an DSTD, bus cards can be plugged directly into it, and it can as well be connected by bus cable to industry-standard card cages.

### DMA

The new Ferguson computer has a Z80-A DMA chip that will allow byte-wise data transfers at 500K bytes per second and bit serial transfers via the Z80-A S10 at 880K bytes per second with serial processor overhead, though the monitor for the new computer uses the DMA chip mainly for transferring data to and from disk, the chip can readily be used for other things since its "wait/ready" pin can be connected under software control to some half a dozen signal lines. When a hard-disk subsystem is connected to the "Big Board II" via its "SASI" interface, the DMA chip makes breathtaking disk performance possible.

### "SASI" INTERFACE FOR WINCHESTER DISKS

The "Big Board II" implements the Host portion of the "Shugart Associates Systems Interface". Adding a Winchester disk drive is no harder than attaching a floppy-disk drive. A user simply 1: Runs a 50-conductor ribbon cable from a header on the board to any of several inexpensive controller cards for Winchester drives that implement the controller portion of the SASI interface. 2: Cables the controller to an appropriate drive, and 3: Provides power for the controller-card and drive. Since our CBIOS contains code for communication with hard-disk, that's all a user has to do to add a Winchester to a system!

### A Z80-A S10/0 = TWO ASYNCHRONOUS/SYNCHRONOUS SERIAL PORTS

### A PARALLEL KEYBOARD PORT = FOUR OTHER PARALLEL PORTS USER I/O

The new Ferguson single-board computer has one parallel port for an ASCII keyboard and four others for user-defined I/O. When the computer is powered-up or reset, the monitor looks for a carriage-return at the keyboard and serial ports. If the first carriage-return gets comes from the parallel keyboard, the monitor uses the board's video display circuitry to communicate with the user via a CRT. If the first carriage-return is typed at an ASCII terminal attached to a serial port, the monitor autabauds and makes the terminal the system console.

### TWO Z80-A CTCs = EIGHT PROGRAMMABLE COUNTERS/TIMERS

The new Ferguson computer has two Z80-A CTCs. One is used to clock data into and out of the Z80-A S10/0, while the other is for systems and application use.

### PROM PROGRAMMING CIRCUITRY AND SOFTWARE

The new Ferguson SBC has circuitry and drivers for programming 2716s, 2732(A)s, or pin-compatible (E)EPROMs. Software \$25 extra.

### CP/M

CP/M with Russell Smith's CBIOS for the new Ferguson computer is available for \$220. The CBIOS is available separately for \$65.

Actual board size: 39.6cm x 22.2cm. 5 inch BIOS being developed. Approx price \$95.

### Pricing and Availability:

Available ex-stock

In single quantities, full kits cost \$695 inc. tax, and A&T'd computers cost \$895. There are attractive discounts that range to 35% for OEM's and dealers. For details about them please call Rod Irving on (03) 489 7099. ie: 3 Ferguson II "Big Board" are less 20% off the one-off price, hard disks disk controllers, boxes and power supply to suit both 8" & 5 1/4" systems will be available.

Bare board with main chips now available (includes PCB, Manual, PALS, Monitor ROM, SMC chips). You have to add rest of components at \$395 + tax

## VIC EDUCATION FROM COMPUTER CLASSICS

Despite the popular notion that children hate the discipline involved in the learning process, education experts have found that children want and love to learn — provided they are not exposed to stress, boredom and frustration.

Computers can teach basic skills in such subjects as maths and language — and make the learning fun at the pace necessary for each child.

Incorporating fun in the learning experience is the essence of VIC education, a new concept in skills-teaching by Computer Classics.

The VIC education series is designed for use on the VIC-20 home computer and the 1530 Commodore Datasette. The programs comprise a maths series and a language series, each teaching basic skills at progressive levels, plus a challenging 'game' called Supermind which sharpens observation and memory skills.

VIC Education was developed by a team of computer educationists in Australia, and is geared toward Australian schoolchildren, an advantage over most education programs from overseas.



Every program has been tested by children of all ages and abilities, and their experience helped develop final programs.

For further information contact Computer Classics, 11-15 Falcon St, Crows Nest NSW 2065. (02)438-4866.

## BOOST FOR DIGITAL ELECTRONICS

Digital Electronics has announced the stepping up of plans for its own 68000 processor and major commitments to the Unix operations system, following a large investment by Business Loans and Equity Capital (BLEC).

The investment, totalling almost \$500,000, was said by BLEC general manager Harold Tilley to be his firm's largest to date.

BLEC, a subsidiary of the Westpac Banking Corporation, backs small and medium Australian businesses with loans while taking shares in the companies it finances.

As a result of the investment, Sydney-based Digital Electronics, which has grown in 14 years' operation to a \$6.5 million turnover, will implement marketing and technical plans, such as the 68000 processor and Unix.

## MICROTRIX MOVE

The Melbourne-based firm of S100 board specialists, Microtrix, has moved from its former address at Montmorency to new premises at Eltham.

Well-known for its comprehensive range of locally made and imported S100 products, Microtrix has recently introduced a new SBC from Octagon which sports both an 8-bit and a 16-bit CPU, two serial ports, a floppy disk controller with DMA and an interrupt controller, among other features.

Also recently released is its new 64K CMOS static RAM board for the S100 buss (to IEEE-696), featuring extended addressing, bank select, battery backup, 6 MHz operation with a Z80B or 8-10 MHz operation with 16-bit processors.

For details on these and more S100 goodies, contact Microtrix, now at 24 Bridge St, Eltham Vic. 3095. (03)439-5155.

## CONTROL DATA SUPPORTS VIDEOTEX

Control Data Australia has announced its support of The Minister for Communication's announcement that Telecom was to provide a national public videotex service.

Since February 1982, Control Data has operated a national public access videotex service targeted at the business community. This service, 'Cybertel', is based on the 'Prestel' protocol using the IVS software supplied by Aregon International of the UK.

Customers of Control Data's videotex service include General Motors-Holden, Jetset Tours, Northern Territory Development Corporation, Syme Media, Creative Communications, Australian International Finance Corporation (AIFC) and Bass Communications.

Mr Bob Easson, Control

Data's business development manager, who has planned and managed Cybertel since its inception, said, "Control Data has always publicly supported the role of Telecom providing a national videotex service; as long as Telecom also provides interactive 'gateways' at low cost to private or other semi-public videotex hosts such as Cybertel.

"Telecom is in the enviable position of being the monopoly carrier which, at the lowest cost, can maximise community access and offer remote users cost-effective access to the same information available to users in metropolitan areas. Current and future customers of Control Data will benefit from the availability of this wider access provided by Telecom, above and beyond Control Data's national communications network. Pro-

vided Telecom adopts a fair and realistic pricing policy for the proposed videotex services, Control Data believes it will compete favourably with Telecom's information offerings."

Mr Easson said it was Control Data's intention to 'gateway' Cybertel to Telecom's service immediately it was available. "Now potential information providers have the opportunity of 'getting started' without risk using Cybertel videotex today. The compatibility of Cybertel and Telecom videotex databases (Prestel format) underwrites the investment in creating the information provider's initial database, or conducting a 'trial' using Cybertel."

For further information contact Control Data Australia, 493 St Kilda Road, Melbourne Vic. 3004. (03)268-9500.

## PUT IT IN YOUR MIT!

Interact Technology, a new market development company specialising in Australian electronic and computer products, has announced a new low-cost computer access device known as the 'MIT' (Miniature Inquiry Terminal).

The MIT is a portable unit that is placed over the mouth-piece of a telephone. By pressing the numeric buttons on the MIT the user can communicate directly with a computer.

Any computer can be equipped with a voice modem to answer the user with pre-recorded voice responses. The computer can therefore provide information requested, or ask the caller to enter data on the MIT. The MIT will sell for approximately \$50.

Applications include; credit card verification where a vendor can obtain immediate authorisation advice; telephone purchasing where customers or sales people can obtain availability or pricing information



and place orders, and data collection of any simple data needs to be acquired rapidly, such as financial data or opinion surveys.

The device operates by emitting an audible tone that is unique for each of the twelve

keys provided. These tones are the same as those used for touch-tone dialling.

At the computer end, a voice modem is necessary to decode to tones received from the MIT, and also to cause the pre-recorded voice responses to be sent.

The computer must have a program that interprets the information received from the MIT, and can select the appropriate voice responses from its memory.

Interact Technology, the company behind the MIT, aims to fill a growing need in the expanding high technology industries. That need is the ability to take an innovative product from the design stage through to manufacturing and successful marketing.

Interact examines product opportunities and those that meet its selection criteria are evaluated as possible product joint ventures. For further information contact Interact Technology, 518 Camberwell Road, Camberwell Vic. 3124. (03)299-2099.

## ANDERSON JACOBSEN AGENT

Mostyn Enterprises has been appointed the Australian distributor for Anderson Jacobsen modems and acoustic couplers.

Anderson Jacobsen, of San Jose, California, is one of the world's leading suppliers of modems and acoustic data couplers. The firm currently boasts the only commercially available 4800 bps full-duplex two-wire modem, the AJ4048. This modem is currently used overseas as a dial-up modem for connection to the public switched network and it can also be used on two-wire leased lines.

For further information, contact Mostyn Enterprises, 35 Alexander Street, Dundas NSW 2117. (02)871-6297.

# MICROPRISM

## Superb Color Graphics for S-100 Bus Systems


Now color graphics can be installed in any S-100 Bus system with the new MicroPrism cards from SME systems.

Starting with high-resolution monochrome graphics for under \$500, your system can be expanded to allow the display of up to 256 colors from a palette of 16 million.

Ideal for CAD/CAM applications with 512x490 resolution, MicroPrism carries its command structure in on-board ROM — freeing up the host computer.

Made and fully supported in Australia, MicroPrism offers unbeatable graphics at an unbeatable price.

Call us today for details.

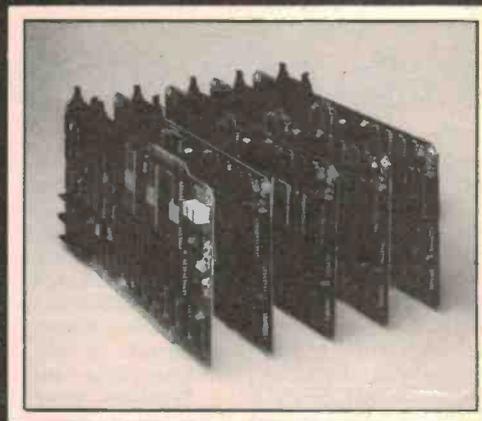

# SME SYSTEMS

SME SYSTEMS PTY. LTD.  
Incorporated in Victoria  
22 QUEEN STREET  
MITCHAM, VICTORIA  
AUSTRALIA, 3132  
PHONE: (03) 874 3666  
TELEX: AA 37213

## COLOUR VDT MAKES IT A WYSE TRILOGY

The Wyse WY-300 colour video display terminal was released at the 10th Australian Computer Conference.

Assembled in Australia by MicroProcessor Applications, the WY-300 completes a trilogy from Wyse, following the WY-100 and the WY-200.

The WY-300 offers the features of the WY-100, plus full colour. It is designed to operate in WY-100 mode and WY-300 mode.

The WY-300 is a smart editing character oriented video display which displays data in eight colours on the CRT screen. It also contains a soft character generator into which up to 256 custom symbols may be loaded from the host computer.

Features of the WY-300 include: clear, 80 column high resolution, eight colour display; hidden colour attributes; extensive alpha-numeric and line drawing symbols; soft downloadable character generator; compact ergonomic design with



swivel and tilt CRT and detached keyboard; text editing and forms data entry functions; 105-key keyboard; two independent RS232 ports to 19.2 Kbps; soft keycodes.

The WY-300 also has a Wyse (single page) compatible mode in which the monochromatic attributes of dim, reverse, etc, are translated to colours. This means that users can take

advantage of colour without having to reprogram the host computer.


The WY-300 includes a 12 inch (30.48 cm) diagonal CRT which can display red, green, blue, yellow, cyan, magenta, white and black. The display provides a screen format of 870 columns by 26 rows with each character position consisting of a 10 x 11 cell matrix.

A pre-defined set of symbols is permanently stored in ROM. These are automatically loaded into the soft character generator upon power-up. This symbol set includes the full 96 ASCII display symbols, the 32 ANSI control code symbols and an extensive drawing line set.

The soft character generator provides the capability to display many symbols for line drawings, bar charts and histograms. Speeds, bits per character, stop bits and parity are switch selectable by DIP switches on the keyboard.

For further information contact MicroProcessor Applications, 48 Rutland Road, Box Hill Vic. 3128. (03)890-0277.

## PUT POWER ON BOARD

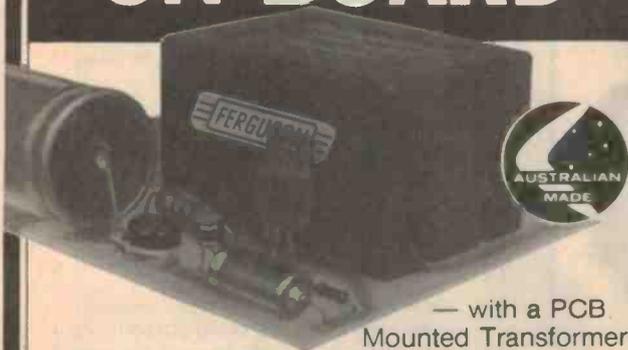

— with a PCB Mounted Transformer

- 3 ranges - 2.5/3VA : 5/7VA : 12/15VA
- Manufactured to AS3126
- Telecom approved
- Standard PCB grid


TALK TO FERGUSON - THE AUSTRALIAN COMPANY WITH NEARLY 50 YEARS EXPERIENCE OF MANUFACTURING IN AUSTRALIA FOR AUSTRALIAN CONDITIONS

Ferguson Transformers Pty. Ltd.

331 High Street, CHATSWOOD 2067 Tel: (02) 407 0261  
Telex: AA25728. Melbourne (03) 328 2843

**FERGUSON**

## FLEX 9 Single Board Computer

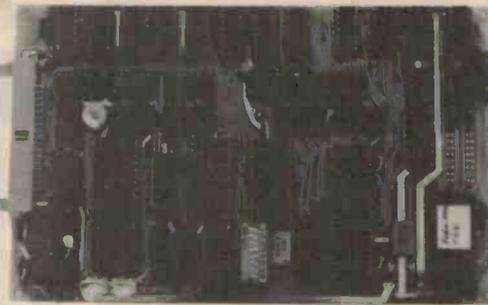

"LITTLE FLEX BOARD"

- ★ 6809 Microprocessor
  - ★ 2 serial ports
  - ★ EPROM with monitor & boot
  - ★ WD2797 disk controller
  - ★ 64K DRAM
  - ★ Runs 'off the shelf' FLEX9
- ★★ Australian made ★★

The FMD-09 "Little Flex Board" is manufactured in Australia by Flex Electronics. The board is a single board computer measuring 185mm x 118mm, capable of running a standard version of FLEX9. The board contains two RS-232 ports, normally dedicated to VDU and Printer. A Western Digital floppy disk controller WD2797 is used to control 5" disk drives, single or double density. 64K of dynamic RAM is supplied. The ROM socket contains a 2732 with resident monitor and FLEX9 bootstrap routine.

Bare board only  
FMD-09-B  
**\$93**

Complete kit  
FMD-09-K  
**\$396**

Complete board A&T  
FMD-09-A  
**\$598**

Add 20% where sales tax applicable.  
Delivery \$6.50 overnight courier.  
FLEX9 is Trade Mark of TSC.

Bankcard Welcome

**FLEX** TECHNICAL SERVICES

P.O. Box 75 Camberwell 3124  
132 Burwood Hwy Burwood Vic.  
(03) 288-4411.


N.S.W. — Microbits (02) 89 3145



If you shop anywhere else - you're paying TOO MUCH!!



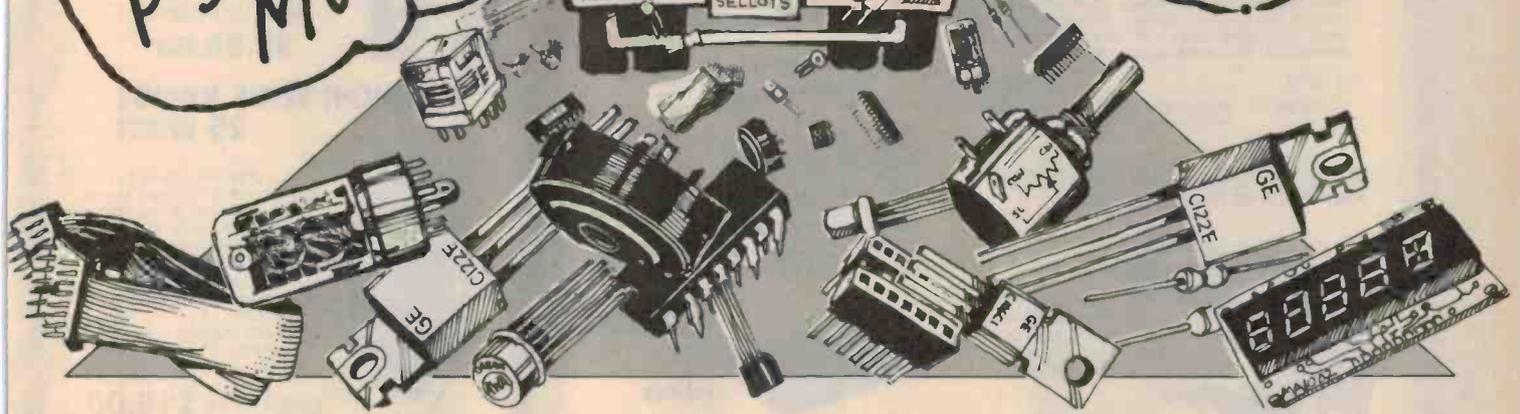Best prices in Australia by the truckload!



# AUSTRALIA'S BIGGEST AND BEST RANGE OF ELECTRONIC COMPONENTS AT UNBEATABLE PRICES



Ozzie Pommy and proud of it!!



Phone on the Hotline for instant service:

**699 6912**  
**699 5922**

## SHERIDAN ELECTRONICS

164-166 Redfern Street, Redfern NSW 2016. Phone (02) 699 5922, (02) 699 6912

# ALTRONICS SUPER SALE

Dear Customer, These bargain prices for quality Altronics products are available until close of business 31st January. As we expect many products to sell out quickly we urge you to order right now! Don't forget our Toll Free Order line — bankcard holders can simply phone 008 999 007 (from anywhere in Australia for the cost of a local call) and your order is on its way.

PRICES VALID UNTIL 31st/1/84

Regards,

*Jack O'Donnell*



## "MICROBEE KEYBOARD"




Full 60 Key Qwerty Computer Keyboard exactly the same type as has been used up to now with the famous Microbee Computer. SPST keys. Complete with mounting plate, all key caps etc. Fully assembled. Incredible value — Be Quick!

D1510 ..... **\$29.95**

Microbee is registered trademark of Applied Technology Pty. Ltd.

## KEY OPERATED SWITCH

HALF PRICE! BE QUICK, 500 ONLY.

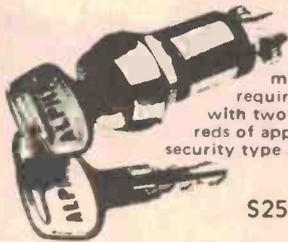

19.5mm mounting hole required. Supplied with two keys. Hundreds of applications for security type applications.

\$2500 **\$3.50**




## VINYL BINDER

Holds 12 magazines, each on a spring out wire rod. Just the shot for each year's set of Electronics Australia, ETI or any of your favourite magazine.

Suits all A4 size publications (275 x 210). Very smart Royal Blue colour with beautiful gold embossing.

B 9999 ..... **\$5.50**  
**THIS MONTH**

\$5.00 each  
4 or more \$4.50 each

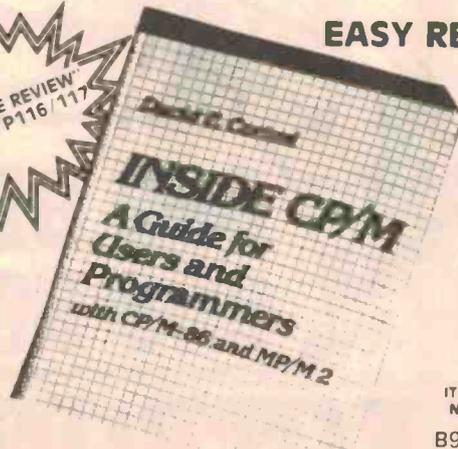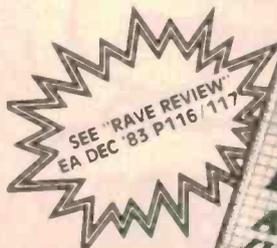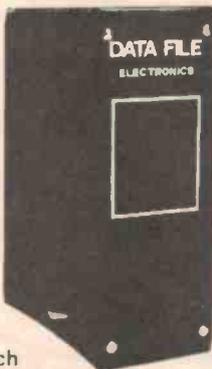


## HUGE IMPORT PURCHASE SCOOP


### D RANGE COMPUTER CONNECTORS

### QUALITY GOLD PLATED PINS

MASSIVE SAVINGS

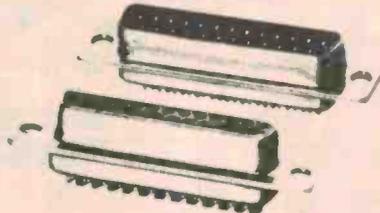

	ea.	10 +	25 +
P0880 DB9 Male 9 Pin	2.20	1.95	1.80
P0881 DB9 Female 9 Pin	2.70	2.50	2.00
P0885 DB9 Backshell	2.50	2.30	2.00
P0890 DB15 Male 15 Pin	2.50	2.29	2.00
P0891 DB15 Female 15 Pin	3.00	2.80	2.30
P0895 DB15 Backshell	2.50	2.30	2.00
P0900 DB25 Male 25 Pin	3.95	3.60	3.00
P0901 DB25 Female 25 Pin	4.50	3.98	3.50
P0905 DB25 Backshell	2.50	2.30	2.00

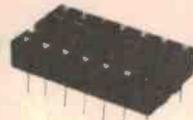

## IC SOCKETS

### DIL

### LOW PROFILE

	ea.	10 +	25 +
P0550 8 Pin	.18	.15	.10
P0560 14 Pin	.20	.18	.15
P0565 16 Pin	.20	.18	.15
P0567 18 Pin	.30	.25	.20
P0570 24 Pin	.45	.40	.35
P0575 40 Pin	.65	.55	.45



## WEATHERPROOF SIREN HORN

12V DC operated — Deafening Siren Wall. Super handy for audio signalling, security systems etc. Current drain 500MA approx. Completely weatherproof. Attractive off-white PVC finish.



S 5058 ..... **\$19.50** NOW **\$15.00 ea.**  
**STRENGTH!**

## EASY READING GUIDE TO CP/M 2.2

FOR THE NOVICE AND EXPERIENCED PROGRAMMER ALIKE

Devoted primarily to CP/M 2.2 this manual is equally applicable to most other CP/M systems. Cortesi divides the book in two sections: an absorbing, explanatory, tutorial covering setup and operating procedures and a comprehensive reference section.

As a learning tool — IT'S INVALUABLE  
As a Reference —

IT WILL TAKE PRIDE OF PLACE NEXT TO ANY CP/M SYSTEM

B9080. ONLY **\$41.95**

## CEILING SPEAKER GRILL



Suits 200 mm (8 In.) speaker. Ideal for PA/Background music systems, c. Lension speakers etc. Colour White.

C 0800..... **\$2.75**

Now incredible

**\$1.50 ea**

## DAINICHI WIDE RANGE

### 25 Watt



200 mm (8 In.). This superbly smooth high power speaker comes from Dainichi, one of Japan's finest speaker manufacturers (they produce OEM Speakers for Pioneer). Max. input power 25W 8 OHM Z. Resonant to 60 HZ. Huge 10 OZ Magnet frequency response 40 HZ-18 KHZ.

WAS \$22.50

C2001 NOW **\$15.00**  
**\$13.50 10 UP**

## DUAL CONE WIDE RANGE



200 mm (8 In.). 10 Watts Max. power input. Public Address, Background Music. Ideal HI FI extension speaker. Includes transformer holes at 51 mm.

Over 50,000 sold in Australia!  
Mounting holes 140 x 140 mm

C2000 NOW **\$6.50**  
WAS \$9.50... **\$6.00 10 UP**

## Powerful 6000 RPM Mini Drill for PC Work



Tons of Torque. Just the shot for PCB work. 12V DC operated from external Power Pack 1.2mm chuck capacity. Supplied c/w 1mm drill bit.

T2302  
Incredible value now only..... **\$10.00**

Drill Bits:  
T2320 (0.8mm) ..... **\$1.25**  
T2325 (1.0mm) ..... **\$1.25**

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

## MICROSOFT COMES ASHORE

The Microsoft Corporation (USA) has announced the purchase of the Sydney-based Wiser Laboratory's Wiser-Microsoft division.

Wiser-Microsoft was appointed Microsoft's exclusive distributor for Australia and New Zealand 18 months ago. Since then, Wiser has grown to become the second largest Microsoft distributor in the world.

Scott Oki, Vice-President of Microsoft International, says, "Microsoft Corporation's commitment to the Australian marketplace is expanding and both Wiser and ourselves feel

that it is desirable to change this form of Wiser-Microsoft in order to better realise this larger commitment. This is why we've made the distributorship our wholly owned subsidiary."

Microsoft will be introducing a comprehensive range of personal business software tools during the coming year. Wiser Laboratory's General Manager, Linda Graham, will now be General Manager of the new Company.

For further information contact Wiser-Microsoft, 21 Tepko Road, Terry Hills NSW 2084. (02)450-2522.

## GORTEK MAKES CHILD'S PLAY OF PROGRAMMING

Commodore Computer has given birth to Gortek, a robot-like character designed to help children learn computer programming, in a series of books and cassette tapes.

The first series, entitled *Gortek and the Microchips*, is aimed at children up to 14 years and consists of two cassette tapes containing 12 educational programs. It also includes an instruction book with colour illustrations, large easy-to-read

type and a language-level aimed at older children. It can also be used by younger children, with parental guidance.

Gortek, which is designed for use on the Commodore 64 microcomputer, was developed by three British school teachers who wanted to make programming fun to learn.

For further information, contact Commodore Computer, 5 Orion Street, Lane Cove NSW 2066.



## MOBILE THERMAL PRINTER

Datel has added a mobile 20-column thermal printer to its printer product line. Called the Model APP-M20D, it is smaller than a CB radio and weighs only 1.2 kg complete. The unit is available in either parallel or serial RS232-C versions.

Applications include ambulances, delivery vehicles, communications vehicles, police, fire brigade and military vehicles, as well as meteorological and oceanographic vessels.

A mounting bracket with slides is shipped with each printer for easy installation and removal. A spring-loaded single-plunger locking mechanism is also provided to prevent theft when left unattended.

The APP-M20D has micro-

processor-controlled interface, compact size and quiet, rapid printing.

Both versions of the APP-M20D print the full ASCII character set in 20 columns across 59 mm wide thermal paper. A dot-line thick film, thermal printhead forms 5 x 7 dot-matrix characters which are 3 mm high. The print rate is 63 lines per minute. A standard 45-metre roll of paper, prints almost 9,000 lines at two lines per centimetre spacing.

The printer outline dimensions are 113 x 69 x 222 mm.

For more information, contact Elmeasco Instruments, 15 McDonald Street, Mortlake NSW 2137 (02)736-2888.

## STD BUS

MULTIBUS™ INTEL CORP.  
VME/EUROCARD

Many cards, cardframes, power supplies, etc.

Cases for systems.

PULSAR LLB complete CP/M computer on an STD Bus card. Kits \$425; Board & EPROM \$132.

VDUs PRINTERS  
SOFTWARE 8" DRIVES

## PROM PROGRAMMERS & PROGRAMMING SERVICE



Range of single and gang programming units for EPROMs, Bipolars, Pals.


PROMSET  
PROGRAMMING  
EPROM ERASERS
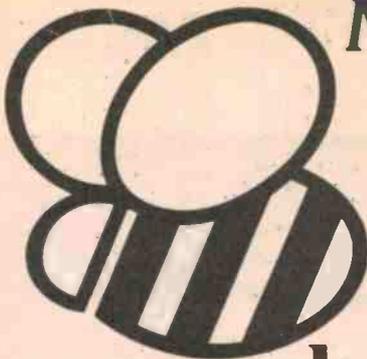
## IN-CIRCUIT EMULATOR for Stand Alone Debugging



For Z80, 8085, 8086 192K RAM, 8" Fl. drive, CRT, 2K x 32 bit trace memory, Prom Programmer, to 27128. Many useful features.

ALFATRON PTY. LTD. 1761 FERNTREE FULLY RD., FERNTREE GULLY, VIC. (03) 758-9000.  
ESIS PTY. LTD. P.O. BOX 281, ROSEVILLE 2069. (02) 467-2032.




**microbee**

# Microbee-No.1 for computers Jaycar -No.1 for Microbee

Jaycar Electronic Agencies is proud to announce the 1984 range of microbee computers - at new low prices!! The microbee Series 2 machines are ALL supplied with built-in communications capability, dual font 80 character by

24 line & 65 character by 16 line displays. Remember, your microbee is obsolete-proof with g'reed upward expandability.

**NEW  
LOWER  
PRICES**

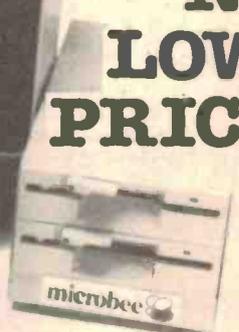

**CALL IN  
TO OUR STORES  
FOR A FREE  
COLOUR MICROBEE  
CATALOGUE**

## microbee Series 2 EXPERIMENTER

By popular request, the low cost microbee Series 2 Experimenter has been designed for those who are starting out in the fascinating world of computers or those who want to share the fascination of exploring the exciting developments in the fast moving MICRO WORLD.

Demand for projects using the microbee is so great that 'Electronics Today' are now planning to run a microbee project every month during 1984. So far ETI has described the light pen, EPROM programmer, a radio TTY printer, the world's first home facsimile receiver and ROM expander board for the microbee. Virtually every local computer magazine has run reviews and/or columns devoted entirely to the microbee. If you want to be part of the MICROCOMPUTER GENERATION in 1984 then microbee Series 2 Experimenter is the ideal starting point. Of course you can expand your microbee Series 2 Experimenter as your need grows.

## microbee Series 2 EDUCATOR

The microbee Series 2 was specifically designed to serve the needs of the EDUCATION MARKET. Let's face it, the primary non-business use for most personal microcomputers is to increase our learning capabilities either about computers (computer awareness) or about life itself. microbee Series 2 has now been officially approved by Education Departments in NSW, WA and Queensland and is being carefully considered in virtually all other states and by the National Schools Commission at the time this ad was going to press.

The microbee Educator uses BATTERY BACKED NON-VOLATILE CMOS RAM so your programs are saved in the microbee Series 2 after the power is switched off. Students can bring the microbee Series 2 Educator home from school to complete assignments ready for class the next day. With the optional BEEMODEM you can use your microbee Series 2 Educator to talk to other computers or information networks.

## microbee Series 2 PERSONAL COMMUNICATOR

With the BUILT-IN WORDBEE in ROM as well as MICROWORLD BASIC and NETWORKING, the Personal Communicator is a powerful home computer ideal for virtually any home use from wordprocessing, spreadsheet analysis, education and even experimentation with the computer concepts as they evolve during the year. With the optional BEEMODEM you can send WORDBEE files across any telephone line to another computer. Be the first on your block to have home telex!

## microbee Series 2 ADVANCED PERSONAL COMPUTER

Now for the first time in Australia: the microbee Series 2 Advanced Personal Computer with 400K disk drive. Then add bounded world class software such as CP/M, MICROSOFT BASIC, MULTIPLAN, WORDSTAR and a powerful library of support programs and you will have some idea as to why the microbee Series 2 Advanced Personal Computer is the most powerful and best price/performance computer in its class. What's more any existing microbee owner can convert his microbee to the Series 2 APC at any time.

The microbee Series 2 APC uses the popular Z80 microprocessor and runs standard CP/M so that users have access to the vast library of CP/M software available world wide. MICROSOFT BASIC is now supplied on disk. WORDSTAR, according to independent surveys now accounts for 50% of ALL word processing software now in use so the designers of the Series 2 APC decided to purchase the OEM rights for your benefit. MULTIPLAN is considered by many to be one of the most powerful spreadsheets yet produced for the microcomputer.

**\$399**



Cat. XE-4000

*Note: the software that is supplied with each machine - at no extra charge!!*

**\$449**



Cat. XE-4050

**\$499**



Cat. XE-4100

**\$1495**

**\$1795**

DUAL 400K DISK DRIVE

Cat. XE-4200

SINGLE 400K DISK DRIVE

Cat. XE-4300

# MICROBEE

## KITS-KITS-KITS-KITS-KITS-KITS-KITS

ETI 733 RTTY Converter. Ref: ETI April 1983. This simple project allows you to hook up your MicroBee to a HF receiver and print radio teletype messages on a monitor screen. Listen to world news for FREE!!  
Cat. KE-4654

ONLY \$17.95

ETI 649 MicroBee Light Pen. Ref: ETI August 1983. This simple, low cost device plugs into the Bee's 8 bit port. The "pen" gives you an entry into the world of light pens and interactive software.  
Cat. KE-4656

SHORTFORM \$19.50

SPECIAL PROBE CASE TO SUIT (as specified in ETI article) Cat. HB 6400 \$19.95  
ETI 668 MicroBee EPROM Programmer. Ref: ETI February 1983. This simple, low cost EPROM programmer just plugs into the Bee's I/O port and enables you to save programs in any of the 5 different common EPROMs available (2716, 2532, 2732, 2732A, 2764). Kit comes complete with 'Personality' plug and all IC sockets.  
Cat. KE-4650

\$39.95


Parallel Interface Kit for the MicroBee. Includes 15 pin 'O' plug - add \$15.00 if Centronics plug required.  
Cat. KE-7017

\$15.00

# BRILLIANT!
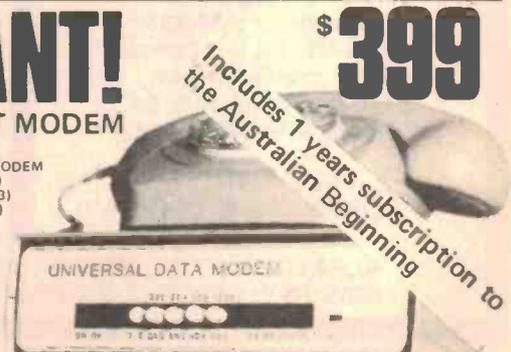
## DIRECT CONNECT MODEM

- KEY FEATURES
- \* DIRECT ATTACH AUTO ANSWER MODEM
  - \* 300 BPS FULL DUPLEX (CCITT V21)
  - \* 1200 BPS HALF DUPLEX (CCITT V23)
  - \* 75 BPS BACK CHANNEL (FULL V23)
  - \* AUTO DIAL
  - \* BELL FREQUENCIES INCLUDED
  - \* TELECOM APPROVED
  - \* 1 YEAR WARRANTY
  - \* NO ADJUSTABLE CIRCUITRY
  - \* DESIGNED IN AUSTRALIA
  - \* MADE IN AUSTRALIA
  - THIS IS NOT A "TOY"



**\$399**

Includes 1 years subscription to the Australian Beginning

Jaycar has made a bulk purchase to bring them to you at the incredibly low price of \$399. Amazing value for a FULL DUPLEX unit. Cat. YC.1350

# UNBEATABLE VALUE

## microbee SOFTWARE



**DISASSEMBLER** By Dreamcards  
Some may say "Not another Disassembler". But this one has a difference. It allows you to set out where the data fields are so the computer is saving time, not trying to disassemble data. A program you shouldn't be without.  
Cat. XE-6915 \$15.00

**CHEAPIE** By Dreamcards  
Two top quality programs for the price of one. The best Hangman we've seen yet on side A and a superb version of Battleship on side B. Both have excellent graphics.  
Cat. XE-6920 \$15.00

**CANNIBALS AND MISSIONARIES**  
The old logic problem game of transferring 3 Cannibals and 3 Missionaries from one side of a river to the other in a boat that holds two. If there are more Cannibals than Missionaries on either side at any time the Cannibals revert to their favourite form of feeding.  
Cat. XE-6925 \$14.95

**COMPOSER BEE**  
This is a very well written program for music. This program allows you to compose, play, edit, transpose as well as being able to load and save your music. A program that has been a long time in the writing and well worth buying.  
Cat. XE-6930 \$22.50

**WORD ADVENTURE**  
A program with very good graphics using little characters to entice the user to think what word is either a synonym, antonym or homonym of the word they are showing. Everytime you get it wrong you are given more clues. After the clues run out you must face the Dragon when you must spell the word he is holding correctly before you.  
Cat. XE-6935 \$14.95

**PONTOON**  
A quality fast moving card game where up to 6 players can play against the computer who is banker.  
Cat. XE-6940 \$14.95

**MUSIC - B - MYTEK**  
MusicB is a music Composer/Editor that lets you create and save music and sound effects with a flexibility that makes choosticks of the Basic PLAY command. MusicB is a great way to learn and play music! Comprehensive instructions are included.  
Cat. XE-7010 \$20.00

**TRSBEE - MYTEK**  
TRSBEE is a package of three programs that loads TRS-80 Model 1 and 3 program tapes into the MicroBee without any additional hardware. Although some program editing will still be required prior to their running, the majority of program typing time is saved by TRSBEE. The first program loads TRS-80 BASIC programs into MicroWorld BASIC. Most programs may then be edited and run. The second program in the package loads any TRS-80 machine code file into MicroBee memory. The third program loads TRS-80 assembler files into the MicroBee EDITOR/ASSEMBLER. Any TRS-80 Model 1 or 3 tape may be loaded. TRSBEE opens up a whole new world of possible software on your MicroBee!  
Cat. XE-7005 \$30.00

**HOUSEHOLD REGISTER**  
This program will simplify the task of determining the value of your home's contents for insurance purposes, as well as providing descriptions of all listed items in the event of their loss or destruction. Effects are catalogued by name, description and value. Nine separate rooms are provided, and up to 28 items may be listed in each.  
Cat. XE-7000 \$15.95

**STAT PACK - STATISTICS**  
This program is a general purpose graph plotting, linear regression, line of best fit and correlation program. It features a t-test of significance for the correlation coefficient and, if no evidence of correlation is found, a determination of minimum sample size is performed.  
Cat. XE-8999 \$14.95

**BASIC TUTORIAL**  
Is a super teaching aid for any classroom. Basic Tutorial is a set of 9 interactive exercises designed for teaching Basic to the computer novice. No previous knowledge is assumed. Basic Tutorial uses a unique double screen technique to display both the normal computer output and the tutorial exercises at the one time. This allows the student to use the MicroBee in the normal way, while the tutorial instructions appear in the lower half of the screen.  
Cat. XE-6860 \$20.00

**MACHINE CODE TUTORIAL - MYTEK**  
Consists of 8 interactive exercises designed for teaching machine code programming and related topics as they apply to the MicroBee computer. Only a general knowledge of the BASIC language is assumed. Machine Code Tutorial is designed to bridge the gap between BASIC programming and being able to understand and use typical Z80 manuals.  
Cat. XE-6855 \$25.00

**BUDGET - SPREADSHEET**  
This program is designed to speed up and simplify the task of framing a usable financial budget. Applications range from personal or household to small business finances. A quality program.  
Cat. XE-6850 \$15.95

**DECODE**  
Basic decoder and listing formatter  
This programme will be an invaluable aid to anyone taking first steps in understanding machine code or wants to expand their library of proven machine code routines. Decode will (a) print imbedded machine code routines fully and accurately (b) print all unprintable characters (c) provide a clearer, easier to read listing and send all output to a printer if so required. ED ASM is not required.  
Cat. XE-6765 \$15.95

**DATABEE**  
This program is a well written data base management system that utilised the MicroBee to its fullest to provide a Data Management System similar to those found on larger and more expensive systems. This comes complete with large bound manual.  
Cat. XE-6945 \$19.95

**ASTEROIDS PLUS - MYTEK**  
Asteroids Plus is one of the finest high resolution graphic arcade games available for the MicroBee computer. It features 3-D point by point resolution graphics, shields, sound effects, intelligent objects, guided missiles, black holes and a score board. If you enjoy playing computer games, you will be captivated by Asteroids Plus.  
Cat. XE-6297 \$22.50

**BEEZ 80 - MYTEK**  
This secret code disassembler will disassemble any code sequence. Nothing is illegal. It will allow you to program with codes that no other disassembler can decipher!  
Cat. XE-6298 \$20.00

**SPACE INVADERS**  
One of the most popular programmes ever released. This version was written especially for the MicroBee.  
Cat. XE-6030 \$14.95

**FDRTH**  
A new language for the MicroBee. Comes complete with interpreter on one side of the tape and supporting programs on the other side. As well as this it includes a very well written, bound manual.  
Cat. XE-6965 \$45.00

**PSYCHOTEC** By Dreamcards  
Psychotec provides a striking example of artificial intelligence, allowing a dialogue in English between computer and operator, the computer playing the role of psychiatrist and the operator being a "patient" on the couch. Leaves other "similar" types for dead.  
Cat. XE-6875 \$15.95

**MERLIN** By Dreamcards  
Merlin is a 32K adventure set in England during the dark ages. Your task is to search through the dark forest inhabited by robbers, outlaws and creatures with awesome magic powers to find a legendary sword. An excellent adventure.  
Cat. XE-6870 \$25.00

**PROGRAMMING HINTS**  
Consists of a collection of modules which you may use to improve your own BASIC programs. They are all linked together under a menu driven display which allows you to RUN or LIST each module to see how they work.  
Cat. XE-6895 \$14.95

**LOG - GENERAL PURPOSE INDEX**  
This program is designed to suit a wide range of records where indexing (and later searching) can be on one or two words, or on a string of up to 15 characters. Each record consists of its index heading, plus up to 12 lines of text. Each line can contain up to 41 characters.  
Cat. XE-6890 \$15.95

**MINE DROP**  
You are a tank running around a maze gathering all the supplies you can. It sounds easy, but you have a guided missile hot on your trail. Your only defence is a remote controlled mine which you drop and explode at will. A very fast joystick or key controlled game.  
Cat. XE-6960 \$14.95

**PENETRATOR**  
A low resolution graphic version of the popular game "Scrambler". You must defeat the rockets and bomb the radars in an effort to get to the next stage which is even harder. This game can be either controlled by a Joystick or by keys. Being in Lores graphics it is a very fast game. If you are bored with the same land pattern you can devise your own.  
Cat. XE-6955 \$19.95

**SPACE PATROL**  
A lot like Penetrator but in high resolution graphics. You must battle your way through the various stages where at the last stage you have four chances of blowing up a neutron bomb shelter. If you are successful, the next round is a lot harder.  
Cat. XE-6950 \$16.95

**METEOR RESCUE - MYTEK**  
Your mission is to rescue stranded astronauts. You are the commander of the Landing Module docked in space with the mother ship. It is your responsibility to guide the landing module through a meteor field, down to the surface of the planet, to land safely on a landing pad. An astronaut will then run to your landing module and you will blast off. You must use your lasers if necessary and dock with the mother ship again. A total of six astronauts must be shuffled to the mother ship.  
Cat. XE-7020 \$17.50

**CORVILLE CASTLE**  
Corville Castle is an adventure which will take you to a far away place of mystic castles, fierce monsters and evil warlocks. You must enter the warlocks castle and find some dark secret which will help you to destroy the warlock. But remember, you only have until dusk.  
Cat. XE-6285 \$16.95

## NEW SOFTWARE FOR JANUARY

**KING KONG - from MYTEK**  
Just like the arcade game of a similar name. The game consists of several frames which you must complete to rescue your sweetheart from Kong. Excellent graphics and sound. Joystick compatible.  
Cat. XE-7054 \$20.00

**CHOPPER - from MYTEK**  
A fast action packed game which must rate as one of Mytek's best. You have full control of a helicopter and you must fly over enemy lines to rescue your allies. Fast realistic graphics and excellent sound.  
Cat. XE-7055 \$20.00

**SKETCH PAD**  
A program to help you design your own P.C.G. characters. Simple commands allow easy drawing of circles, polygons and boxes etc. These then can be dumped to tape to be used in a future program. Comes complete with manual.  
Cat. XE-7056 \$19.95

**PRINTERS MATE**  
This program is two screen dump programs to suit CP80, MX80, DT80, 80DP and FAX80 printers. One program is a screen dump utility while the other prints out memory contents in both hexadecimal and ASCII characters. A must for use with printers.  
Cat. XE-7051 \$17.50

**DUO - ONE**  
Another two programs for the price of one from Dreamcards. One side has poker, and the other is Casino which is a three reel poker machine. Both use hires graphics. Excellent value.  
Cat. XE-7052 \$15.95

**EXTENDED TURTLE**  
A "Turtle" program which has been written by a teacher and has been several months in the writing. This is one of the best Turtle programs written and comes complete with a 40 page clearly written manual with many helpful drawings.  
Cat. XE-7053 \$29.50

**DEFENDER - FROM MYTEK**  
This long awaited program is finally available. Defender needs no introduction. The Defender arcade game is one of the most popular ever produced and the Mytek version is brilliant, a rival for Asteroids Plus.  
Cat. XE-7036 \$22.50

**DESTROYER**  
You are the UFO and you must destroy the enemy city buildings before you can land. You have no control over the UFO except for the three bombs on every pass you make over the city. But beware the UFO gets lower with every pass. Good graphics and sound.  
Cat. XE-7048 \$14.95

**COULOMBS LAW**  
This program is another in the series of Physics simulations. The first part is a tutorial and the second is a simulation of the experiment.  
Cat. XE-7049 \$14.95

**BACKGAMMON - FROM MYTEK**  
This game conforms exactly to that set down in the official rules of the International Backgammon Association, including the rules of doubling and scoring.  
Cat. XE-7050 \$17.50

**POOLS AND LOTTO**  
Two programs to help make life easier for the Pools and Lotto enthusiasts. The first program chooses your numbers for the week and the second program allows you to input your numbers into a program and when Lotto night arrives you can input the winning numbers and the computer will check your Lotto for you.  
Cat. XE-7045 \$14.95

**WONDER WORDS**  
This program allows you to input 20 words and the computer will create a Wonder Word puzzle. This can be either sent to a printer or solved on the screen or let the computer solve it. Just the program for Wonder Word enthusiasts.  
Cat. XE-7046 \$14.95

**GEO-TECH DRAWING**  
This is the first tape in a series to assist students in grasping the fundamentals of geometric and technical drawing. It uses good graphics with excellent explanations.  
Cat. XE-7047 \$14.95

## Jaycar Incorporating ELECTRONIC AGENCIES

SYDNEY SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
TELEX: 72293  
CARLINGFORD  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444  
CONCORD  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077  
HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

## NUMBER 1 FOR KITS

PDST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)  
"Free INSURANCE for Road & Registered Post over \$200"  
All heavy or bulky items (over 20kg) sent Comet Road Freight \$12.00 anywhere in Australia.  
SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE  
Mon - Fri 9am - 5.30pm; Sat - 9am - 12pm; Thurs night 8.30pm  
SHOP HOURS SYDNEY  
Mon - Fri 8.30am - 5.30pm; Sat - 8.30am - 12pm; Thurs night 8.30pm  
MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137.



Mail Order By



BANKCARD Via Your Phone

# at the leading edge

## **SHARP ADDS 24 OPTO INTERRUPTERS AND 8 NEW PHOTOCOUPPLERS TO RANGE**

Already a leading light in opto devices, Sharp of Japan has launched a vigorous design effort to second source nearly all U.S. and European devices.

Recent releases include the OPIC range in which the receiving element incorporates its own voltage regulator, amplifier and Schmitt trigger. OPIC is available in Telecom approved optocouplers as well as transmissive and reflective photointerrupters.

## **WESTERN DIGITAL SLASHES WINCHESTER CONTROL COSTS**

A revamp of the WD1000-05 dropped its 100 piece price to under \$250 plus tax. Looking very much like the WD179X floppy interface, the WD1000-05 will make engineers feel very much at home with an old friend. The 5¼" drive form factor and its drive signals are based on the Seagate ST506, ST412 and other compatible drives.

## **BELL 103 FSK MODEM CHIP — FIRST IN G.I. FAMILY**

Designated AY-7-1203 General Instrument's CMOS. 300 baud full-duplex modem abounds with features such as digital filtering, power down mode, single 5V Rail, self test and echo suppress or inhibit tone facility. Later devices in the family will include CCITT V.21, CCITT V.23 (Modes 1 and 2) and Bell 202.

The AY-7-1203 will be in volume production early in 1984 and predictions are that the product will be very cost effective.

## **10 MBYTE "SKINNY WINNIE" CHALLENGES 5 MBYTE PRICING**

Volume production and high yields have given Miniscribe Series III half height drives a considerable cost benefit edge over their rivals.


Miniscribe's Model 3012 not only saves space and money but power requirements are also reduced to around 17 Watts which is well under the industry average. This solves two problems — Start-up surge and ongoing thermal regulation.

Seek times are kept to a respectable 155m/Sec and a microprocessor controller internal self diagnostic routine provides fast performance verification. Interface? ST412 Floppy look-alike!
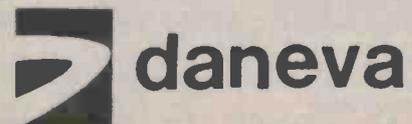
### **daneva australia Pty Ltd**

66 Bay Rd., Sandringham, Vic. 3191  
P.O. Box 114, Sandringham, Vic. 3191  
Telephone: 598-5622. Telex: AA344939

Sydney: (02) E&M Electronics 51-5880  
Adelaide: (08) DC Electronics 223-6946  
Perth: (09) Micro Controls 445-2544  
Brisbane: (07) Ballec 369-5900



# The Comx 35 — some promise there



Many designers play it safe when they set out to develop a product by sticking to the conventional lines. But Comx have taken some chances with a different BASIC and an 1802 microprocessor in their home computer.

The 1802 would be virtually unknown but for its use in two eight-chip computers, the RCA VIP and the ETI-660.

Nonetheless, they could have a winner, particularly amongst hobbyists.

## Frank Rees

LAUNCHING a budget-priced home computer into today's extremely competitive market is a risky venture. Comx has apparently been clever enough to come up with what appears to be a well-designed little computer offering 32K RAM, colour graphics, sound, a 55-key keyboard, an inbuilt joystick and a unique dialect of BASIC which works well.

Ten programs are supplied with the computer, five of these are games and five are 'serious'.

The Comx plugs into an ordinary cassette player, with cables supplied. A disk drive and a printer are going to appear on the

market shortly, according to the company.

The keyboard is calculator style, 'soft' keys, with what is basically a QWERTY layout of 55 keys. A robust joystick is built-in but all it does is generate key presses (136-139 for up, right, down and left) so that you can read it with the KEY function in BASIC.

### The screen

The use of a UHF modulator and the inbuilt sound of the Comx 35 makes it compatible with both of the two major PAL television systems currently in use throughout the world. Australia, like New Zealand, West

Germany and some others, use the system employing a VHF tuner and a 5.5 MHz sound IF, while the UK uses a UHF tuner and a 6.5 MHz sound IF.

If you are contemplating the addition of a video outlet for a black and white monitor, then the Comx's inbuilt sound is very handy. However, at present, it means that you not only have to have a colour TV with a UHF tuner, but also need some modifications to your set if you don't have channel 5A on your VHF tuner.

When UHF tuners were first fitted to colour TVs, the VHF tuners often did not have the extra position 'U' for the UHF ▶

# Comx 35

front end which converted the UHF signal to a VHF signal to be received by the VHF tuner. Many sets had the channel 5A position marked 'U' but the UHF front end was actually packed in a plastic bag at the back of the set. It is fortunate that I am a TV technician because mine was one of these and I had to make the necessary modifications to the set.

Once the Comx is plugged into the TV, it produces a stable 40 x 24 line eight-colour display with 128 different characters available. Lower case isn't standard, but if you wanted it, the SHAPE command can easily redefine the whole set. This is about it as far as graphics are concerned — there are no pixel or bit-mapped high resolution graphics.

The colour partially compensates for this. Comx BASIC will put your typing up in one colour and the response up in another, which is quite helpful. Eight background colours and 12 character colours are available to make fast multi-coloured displays.

The sound is very simple, consisting of a single note channel opened at any of eight octaves with MUSIC or TONE and white noise controlled by NOISE. Fortunately VOLUME control is available as the sound can be very loud.

## The 1802 processor, etc.

The 1802 is a CMOS eight-bit chip equipped with a well-ordered instruction set and plenty of 16-bit registers. It is backed up by a set of three RCA support chips — the 1869, 1870 and 1871, for screen, input/output, sound and other functions. The rest of the computer is a bank of 32K RAM and another block of 3K RAM which gives you 35K and hence the Comx 35 it's name.

There must have been good reasons for the manufacturers to select the 1802 micro-processor for the Comx 35. Although it is easy to raise objections about available machine code routines and programs, and the shortage of programmers experienced in 1802, so far the software made available by Comx looks good, and an independent supplier is already advertising programs for it.

The 1802's structure lends itself to use by the hobbyist with only a simple monitor program, instead of an assembler with all the trappings. However, with a 35K memory and the 1802's tidy structure, I'm sure a basic assembler will become available soon. The clean, tidy logic of 1802 will appeal to many as an introduction to machine language, as well as to those who want to learn it as a way of extracting maximum performance from their computers.

Machine language is supported by a full array of BASIC instructions and has the ability to handle hex numbers without messy conversions. This is really important in a 35K computer, as the use of decimal numbers over 32767 (7FFF hex) would require additional conversion to two's complement expressed as a negative number (yuk).


As a user of machine language, I found the Comx system really geared towards making machine language an easy-to-use, integral part of BASIC.

## Comx BASIC

The BASIC is fairly impressive, especially considering that 1802 BASICs are rare and Comx had to write their own. I think they've been very successful. Some of the common BASIC commands have been changed for a variety of reasons. 'INKEY\$' has been changed to 'KEY' because it is the numerical code input of the key pressed, rather than the character itself. D for DATA and P for PROGRAM prefixes 'SAVE and LOAD' memory to, or from, cassette instructions. Besides MUSIC, TONE and VOLUME, the sound instructions include NOISE which forms an important part of realistic sound effects.

On the inside. There's not much to it these days! RAM located at lower left, keyboard interface at lower right. The expansion interface connector can be

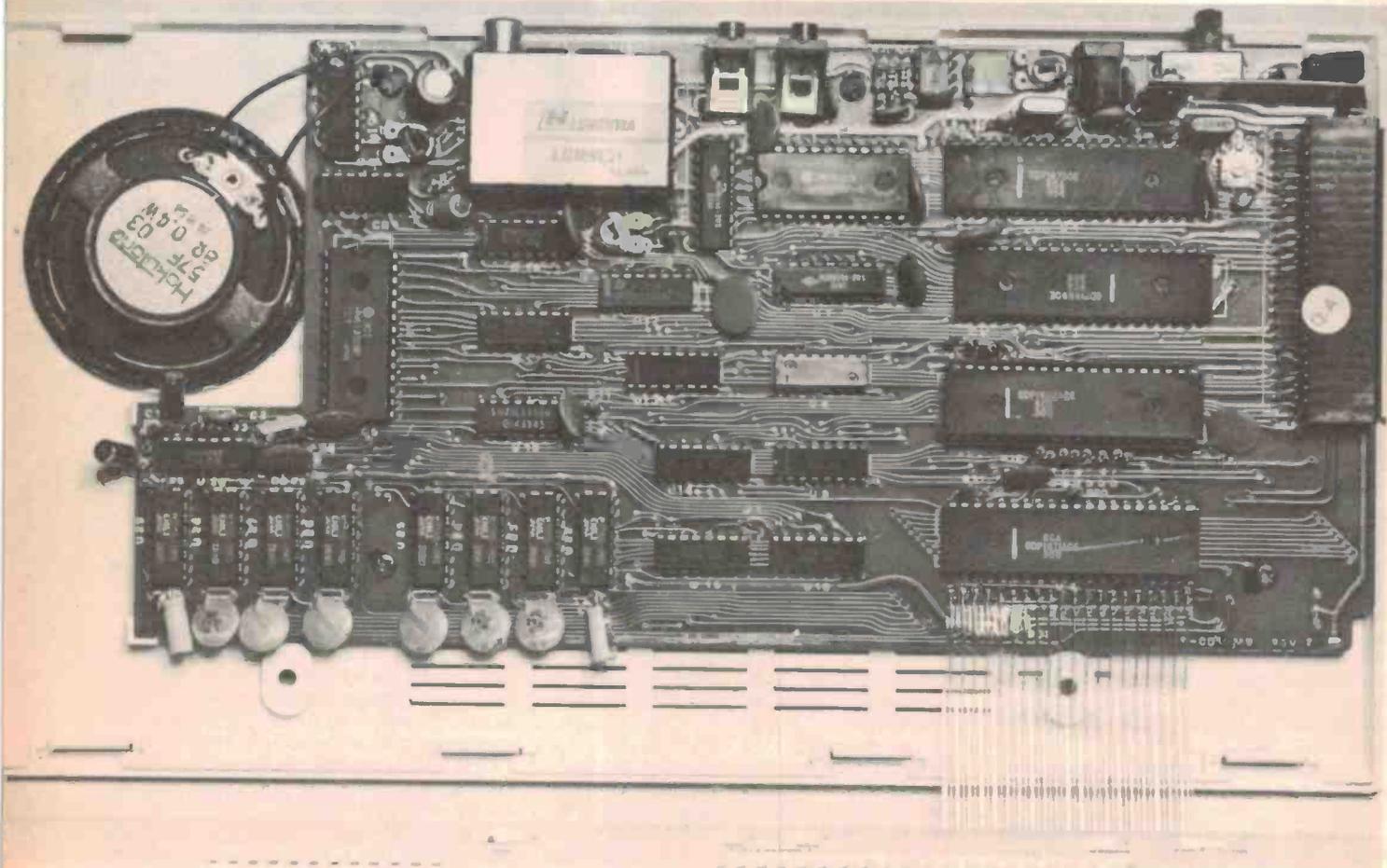seen at far right, RF modulator at middle upper part of the pc board. The tape input/output sockets are to the right of the modulator.





**Keyboard closeup.** The keyboard is more or less the standard QWERTY layout. 'Rubber' keys are used but they're firmer than the usual ones seen on most

other machines about, and the keys are concave sculpted, which is definite help. It's a wise idea to hit the space bar in the middle for reliable operation.

A **RUN+** statement converts literal GOTO destinations into absolute addresses i.e: it does time consuming branch calculations first. This speeds up the already fast BASIC. **TIME** starts an internal interrupt timer. When it reaches zero, the BASIC GOSUBs to the routine specified by **TIMOUT**. Timed interrupts allow you to play a tune under program control with a game under way at the same time.

Other new or changed BASIC commands are:

- SCREEN** sets background to one of eight colours.
- COLOUR** sets characters to one of twelve colours.
- CPOS** sets cursor to position X,Y.
- CTONE** sets the character to the same colour as the background but brighter than it.
- EOD** gives hex address to end of data.
- EOP** gives hex address to end of program.
- EXIT** to exit a for/next loop.
- EXP** exponent e.
- FIXED** fixes number of decimal places.
- FNUM** rounds numerical expression and converts to floating point.
- FORMAT** specifies field width of numbers.
- DEFUS** defines USR program start location.
- FVAL** evaluates numbers in string and is unique to the Comx.
- INUM** force function to integer mode.
- KEY** 'no wait' key input numerical (ASCII) code value.
- MOD** function module.
- MUSIC** a music note set for frequency and amplitude.
- VOLUME** programs the sound level.
- WAIT** simpler than a FOR/TO for delay.
- RENUMBER** tidles up line numbers of a patched program.
- RUN+** speeds up program running by doing time consuming branch calculations first.
- SHAPE** generates your own character or graphic shapes.

- TRACE** used to debug by showing line number on screen as executed.
- MIDS** serves as LEFT\$ and RIGHT\$
- JOYSTICK** the four-position switch types are read like keys.
- TIME** sets timer
- TIMOUT** command performed when timer zeros

Editing is an old-fashioned serial line editor invoked by **EDIT**. The cursor is positioned underneath the point you want to change and by typing I, D or C, it will be either inserted, deleted or changed by control S.


The owners manual is better than most, and I suspect that if I used it enough, I would find it a reference that I'd want to keep. However, I'm sure beginners would

need more than the manual before they could use the Comx.

PAL and NTSC graphics can be different, so if you write programs to submit to the 'Comx International Users Club', leave out line 9 of the graphic **SHAPE** command because this can only be reproduced on the PAL system.
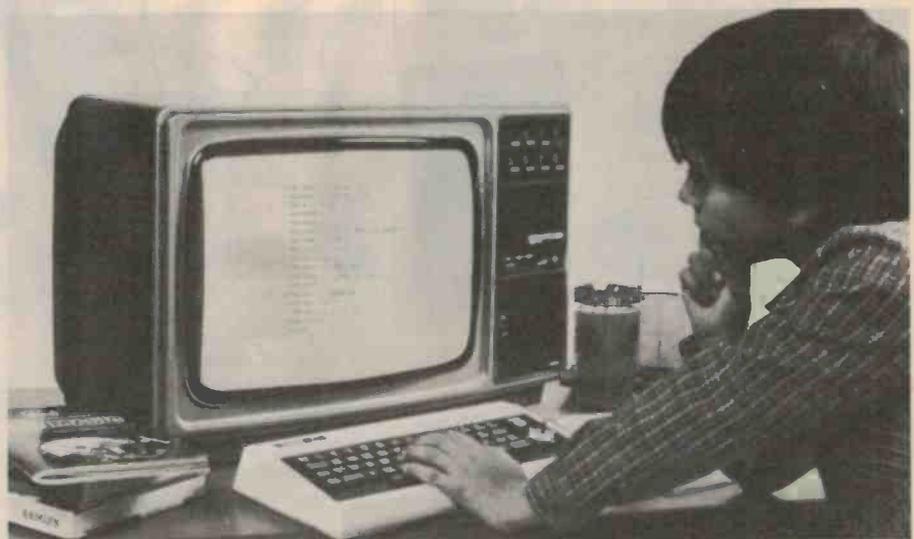
### Summary

The Comx 35 has something different to offer, is low-priced and works according to expectations. It has some promise if you want to get into machine code and the 1802 microprocessor is good for learners in that respect. The BASIC in the Comx 35, while different, is at least 'friendly'. ●




# "Now for Fun Way 3 projects using



"Here it is - the one everyone's been asking us for! A completely new volume of Fun Way into Electronics, leading on from the incredibly successful Volumes 1 & 2.

This one has 10 exciting new projects, all based on integrated circuits - making it an ideal choice for anyone who's worked their way through the introductory books and kits.

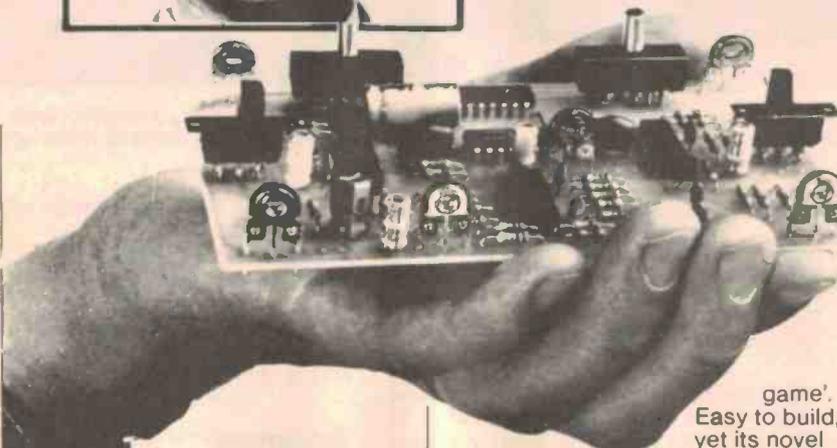Join the many thousands of hobbyists, school students and club members who have learned Electronics the Fun Way. It could lead to an exciting new career!"



## 1 LIGHT AND SOUND

Not just one project, but many! You can use it to produce all sorts of sound effects, to flash lights, as a strobe, as a continuity tester, even a Morse Code practice set. Simple and easy to build, too. Cat K-2665

**\$8<sup>95</sup>**



## 2 TWO UP

Put yourself in the winner's circle with this space-age electronic version of Australia's 'national

design gives realistic 'flick of the wrist' operation. Cat K-2661

game'. Easy to build, yet its novel

**\$9<sup>95</sup>**



## 3 CRICKET

Put this project in a quiet, dark place, and it starts chirping; turn on the light or make a noise, and it stops! Infuriating



- just like a real Nocturnalis Stridulus Gryllidae (Cricket to you). Cat K-2663

**\$9<sup>95</sup>**

## 4 MINI STEREO AMPLIFIER

Just the shot for turning your headphones-type 'Walkie' stereo or FM radio into a full speaker system for your bedroom! Or you can use it as an amplifier for a loudhailer or mini PA system. Cat K-2667



**\$14<sup>95</sup>**

## 5 MINDER

Another one that's really many projects in one - this time for the car or boat. A 'lights on' or 'door not shut' warning, or a burglar deterrent flasher. It's almost as good as a real alarm! Cat K-2660

**\$7<sup>95</sup>**



\* Note the boxes shown are not supplied in the basic kits. The front panels are in the Fun Way 3 book.

# -ten exciting new Integrated Circuits!"

## 6 MINI COLOUR ORGAN



Just like the light show at the local disco. Connects to your radio or cassette recorder, adds an extra dimension to your musical entertainment. Easy to build and can be battery operated, so it's safe.

Cat K-2664  
**\$12<sup>95</sup>**

## 7 COMBINATION TIME LOCK SWITCH

Use it as a combination lock for a burglar alarm, or as a challenging 'brain teaser' party game. Just try cracking the combination without setting off the alarm! It's really good.

Cat K-2666  
**\$12<sup>95</sup>**



## 8 LI'L POKEY

Just like the one-arm bandits at the club! A barrel of fun to play, but you won't risk losing your shirt or your pocket money. A satisfying project - your friends will be most impressed!

Cat K-2662  
**\$19<sup>95</sup>**



## 9 BINARY BINGO



A lot harder to play than it looks - just try it and see! Tests your reaction time, also helps you learn binary numbers. Four levels of skill. Easy to build, battery operated for safety.

Cat K-2668  
**\$19<sup>95</sup>**

## 10 MINI SYNTH

Incredible - a real music synthesiser, with decay, frequency doubling and halving, tremolo. Its really unique feature is that YOU become the note generator! Whistle, hum or sing and see what interesting effects you produce!



Cat K-2669  
**\$19<sup>95</sup>**

\* Please note: all projects shown with optional cases. The labels shown are all printed in the Fun Way 3 book.

And the book... Dick Smith's Fun Way Into Electronics, Volume 3: over 100 pages with easy-to-follow instructions for all these projects, plus handy information every hobbyist needs.

**ONLY \$6<sup>95</sup>**

Cat B-2610

# DICK SMITH Electronics

See page 117 for full address details.



**EXCLUSIVE TO DICK SMITH**  
HURRY... FIRST PRINTING  
ALMOST SOLD OUT!

# ONE COMPUTER BOTH 8

## AUSTRALIAN COMPANY HAS MORE TO OFFER THAN INTERNATIONALS

THERE are a number of flaws in assuming that large international companies can provide a better product. In particular some Australian companies are able to provide support not matched by the "big guns" such as IBM, Apple, and Digital Corp. When phoning an IBM service centre can you speak directly with the people that designed the machine? Acoustic Electronic Developments, known nowadays as AED COMPUTERS have displayed an uncanny ability to provide superior product technology as well as service unsurpassed in the industry.

### **JUMP FROM PROGRAM TO PROGRAM — First for Australia**

Previously CP/M-based microcomputers were only able to run one program after the other, resulting in their inability to reach full potential in minute-to-minute business activities.

Analysing small businesses it becomes apparent that businessmen are required to swap randomly from function to function. One moment they are production controllers, the next sales persons, next the accountant, etc. By the very nature of office life they seldom finish one task before being interrupted by one more urgent.

The microcomputers inability to rapidly swap from function to function has been overcome by a revolutionary new operating system concept (MPS Multiple Program Selection) developed by AED. At a touch of the keyboard the current task is saved in suspended animation. The user then selects one of nine other tasks, which complete with its screen image, is loaded into the computer and released. The swap takes only six seconds (about 20 times faster than conventional systems). When done with the new task the operator returns instantly to the original.

Swapping programs on conventional microcomputers is slow, requires many keystrokes, and normally there is no menu prompting. MPS, however, is extremely fast, requires only three keystrokes, and is completely menu assisted. Other attempts have been made to solve this problem by creating a fully integrated suite of programs. This approach yields an improvement though still suffers slow swap time and only specially written programs are available for the system. MPS resides in the operating system, therefore offers extreme speed and is compatible with any standard CP/M program.

### **SUPERAED — The CP/M your having when your not just having CP/M**

In the first two years of manufacturing microcomputer systems AED became aware of many features that were not provided by the popular CP/M operating system. This shortcoming was holding back microcomputers from reaching their full potential in business, office automation and engineering applications.

Analysing alternative operating systems revealed that some had advantages in some areas but still lacked the end-user oriented features that were of primary concern. It appears that computer system programmers give total priority to hardware, disk file structures, programmers facilities, and the command power to impress engineers and technicians. This explains why these operating systems, while more powerful, still lack the basic facilities that would make the computer infinitely more useful to the businessman, engineer, doctor, etc., that use it from day to day.

Solving this problem by designing a new op-system was due to the incredible software base available for CP/M. Other company's CP/M look-alikes all have compatibility problems and AED didn't want to join the list. The alternative of developing an extension package to CP/M was adopted with some startling results, all achieved without corrupting one byte of CP/M or it's CCP.

After 12 months in development AED released SUPERAED which was an immediate success leading to increased sales of the "AED SUPERCOMPUTER I" and drew considerable interest overseas. After a further 18 months development a new version with a unique multiple program selection capability (MPS) was released, along with a new computer "AED UNIVERSE Supercomputer II" which combined 8 & 16-bit operation in one machine.

### **Superaed provides many features unique to a CP/M-based system including:**

**Intelligent Terminal Driver.** A special driver for the extremely fast AED JN-SERIAL terminal, providing display speed control and intelligent software control over cursor and all screen characteristics.

**Keyboard Substitution.** Allowing application software to talk to the computer

as though it were the operator. At last one program can use another to participate in the job at hand.

**Automatic background memory testing.** SUPERAED continuously scans the computers memory, warning the operator of any faults before they cause subtle data errors to creep into your files.

**Selection of multiple printers.** CP/M provides for only one printer. "SUPERAED" provides for 8 printers which may be selected directly from the keyboard or under software control. Orders can be automatically directed to a printer loaded with order forms, invoices to a printer with invoice forms, etc.

**A powerful diagnostic monitor.** This is one of the most startling features of "SUPERAED". Unlike other systems the monitor can be entered even when a CP/M program is in use. After using the monitor for diagnostics, experimental, or debugging purposes, you can return right back to the CP/M application. At last you can look deep into the software and hardware system of your computer while the sample is still under the microscope.

### **OPERATING SYSTEMS — TO GO**

The majority of microcomputer systems have either 8-bit 8080, 8085, or Z80 CPUs or 16-bit 8086 or 8088 CPUs. The CP/M operating system has been adopted internationally as the standard for 8-bit machines. CP/M-86 and MS-DOS operating systems share the market for 16-bit machines. Owners of 8-bit machines are limited to 8-bit CP/M software of which there is an abundant variety. Owners of the technically superior 16-bit machines have access to a respectable, yet somewhat more limited variety of software. Choosing which machine to buy can become a nightmare when weighting-off performance, software availability, and the future. The AED UNIVERSE computer simplifies this choice offering the best of both worlds. By employing a software selectable dual 8 & 16-bit CPU the UNIVERSE can run all of the most popular operating systems: CP/M, MP/M, I/OS, Multi/OS, CP/M-86, MS-DOS and more to follow. This approach opens the door to a wide application software range than almost any other computer system. AED are planning to release

# & 16-BIT

additional bus master CPUs such as 68000, 16032, and 80286, extending even further the range of operating systems available.

## **HARDWARE — Built for speed and expandability**

The AED UNIVERSE electronics is based on a 20 slot IEEE 696 S100 bus structure. This is the only bus endorsed by an international standards organisation. There are many systems that claim compatibility with this standard but beware as compatibility with and compliance to IEEE 696 mean two different things. An S100 system has many advantages over integrated proprietary systems as it offers greater expandability as products are available from a broad range of vendors. S100 tends to be the first to introduce new technology in a practical form and offers the greatest performance cost ratio.

The universe uses a dual 8 & 16-bit CPU which boasts the highest clock speeds available, that is 6MHz on the 8-bit and 8MHz on the 16-bit. The systems memory cards work in both the 8-bit and 16-bit modes making extension of the system to future 16-bit and 32-bit processors viable. The UNIVERSE employs intelligent Direct Memory Access (DMA) temporary bus master floppy and hard disk controllers employing their own processors to remove burden from the system CPU. This technique yields speed far exceeding systems from the large corporations.

Printer and communications input and output are handled by what must be the most powerful I/O system ever offered on a microcomputer system. This card has its own on board Z80 CPU combined with 256K-bytes of memory to dynamically buffer all input and output from the two centronics and two programmable serial ports. The card also boasts a clock/calendar, programmable interrupt system, programmable counter/timers, and a unique power supply monitoring system.

The UNIVERSE terminal is part of the computers main memory system making it several times faster than conventional serial terminals. In fact, the UN-SERIAL terminal is so fast that under WORDSTAR word processing software the UNIVERSE performs more like a sophisticated dedicated word-processor than a normal computer.

# UNIVERSE

## SUPERCOMPUTER



**SLOW:** Non standard 5 1/4" discs  
**SLOWER:** 16 bit only CPU  
**LIMITED EXPANDABILITY:** Cards from only a small number of manufacturers  
**FEWER APPLICATION PROGRAMS:** Due to its 16 bit only CPU

**FASTER:** 8 & 16 MHz 8 & 16 bit dual CPU  
**MORE APPLICATIONS:** on CP/M, CP/M 86, MS-DOS, MULTIOS & MP/M 86  
**HIGHER SPEED:** 8 & 16 MFC, DMA, Floppy & DMA 16 MEG hard disc, fixed & removable  
**MORE EXPANDABLE:** Due to S100 IEEE-696 compatible from hundreds of manufacturers  
**THE ONLY SYSTEM** with the magnificent "MPS" INSTANT TASK SWAPPING CAPABILITY.

**DEALER FRANCHISE ENQUIRIES**  
 for  
**BRISBANE, ADELAIDE & PERTH**  
 WELCOME!

We can help you with  
 • CONSULTANCY • SERVICE CONTRACTS • CUSTOM SOFTWARE • STANDARD SOFTWARE

## The choice is yours.



Contact AED for your local dealer or information kit.



For details or an information kit contact:

**Sydney:** AED COMPUTERS, 24 Darcy St, Parramatta, NSW 2150.

Phone (02) 689 1744, (02) 681 4966. Telex AA70664 GIRFRI.

**Melbourne:** AED COMPUTERS (Melbourne): ELSTON COMPUTERS PTY LTD,

53 Waverley Road, East Malvern, Vic. 3145.

Phone (03) 211 5542. Telex AA30624 ME447.

**Canberra:** AED COMPUTERS (Canberra), 217 Northbourne Ave, Canberra, ACT 2601.

Phone (062) 47 5348. Telex AA62898 HARSUR.

## **SUPPORT more the merrier**

Engineering and service support for AED systems is second to none in the industry. Phoning an AED sales and service centre puts you in contact with engineers rather than salesmen. Usually the engineer was involved in one or more aspects of the machines electronic or operating system design. Few if any multi-nationals can offer this ready access to engineering support. AED has chosen as agents, engineering companies involved in sales instead of sales companies involved in engineering and provide complete engineering service and sales support

in Sydney, Melbourne, and Canberra, and intend to soon include Brisbane, Adelaide, and Perth.

AED can provide complete System analysis and consultancy. SOFTAED a Sydney-based division of AED produces custom written applications where off-the-shelf software is not suitable. AED installs the systems and provides any necessary training.

Service contracts are available covering most of NSW and Victoria. AED were one, if not the first computer company in Australia to provide a one-year warranty, a true reflection of the reliability of the machines and the companies belief in them.

# RS232-to-Centronics interface

Geoff Nicholls

Most microcomputers worth owning have an 'RS232' connector, or port, through which serial communications (input/output) is conducted. It is a convention that, for listing on a printer, the BASIC LLIST or LPRINT command assumes a printer is connected to the RS232 port. Problem is, serial interface printers are more expensive than parallel 'Centronics' interface printers. Save some money, build this interface.

WHILE I designed and constructed this project to drive an Admate or TI 850 80-column dot-matrix printer from the lab. Microbee, it is 'universal' enough to suit any application requiring an interface between an RS232C port and a Centronics interface.

Printers with a parallel, or 'Centronics', interface are around \$80 to \$150 cheaper than with a serial, or RS232C, interface. However, the 'default' printer output on most microcomputers is via the serial interface and a serial interface printer is assumed when LLISTing or LPRINTing from BASIC. This project can be constructed for considerably less than the difference between the cost of a printer with a serial or a parallel interface.

## Features

The project simply plugs directly between the computer's RS232C socket and the printer's Centronics connector. It is powered from the +12 V line on the RS232C interface. It is preset to operate at a speed of

1200 baud, but provision has been made for selectable baud rates of 300, 600, 2400 and 4800 (depending on choice of one IC), in addition to that. The data format is also preset, to eight data bits one stop bit/even parity, but other formats can be selected.

Tracks etched on the pc board preset the speed and data format, but provision has been made to use either links or DIL switches.

The interface is built around a single supply rail UART ('universal asynchronous, receiver-transmitter) from General Instruments, the AY-3-1015D. This chip pretty well does the whole job, even supplying the acknowledge signal (handshake) for the RS232C port. A 4.9152 MHz crystal is divided down to provide baud rate clock outputs. Either of two IC types can be used here — a 4020B or a 4040B. The 4040B provides only the lower three baud rates (300, 600 & 1200) while the 4020B provides the full complement. However, whichever type is used, it must be capable of running at

5 MHz on a 5 V supply. The minimum speed spec. for Philips and Fairchild devices equals this, but it is lower for National Semiconductor devices — though some chips may run at this speed.


## Construction

Assembling the project is quite straightforward. However, there are a few points to watch. Firstly, whether you're using a ready-made pc board or have etched your own, check that all the tracks are intact and that there are no bridges, particularly where tracks run between IC pins. Also see that all the holes are drilled correctly.
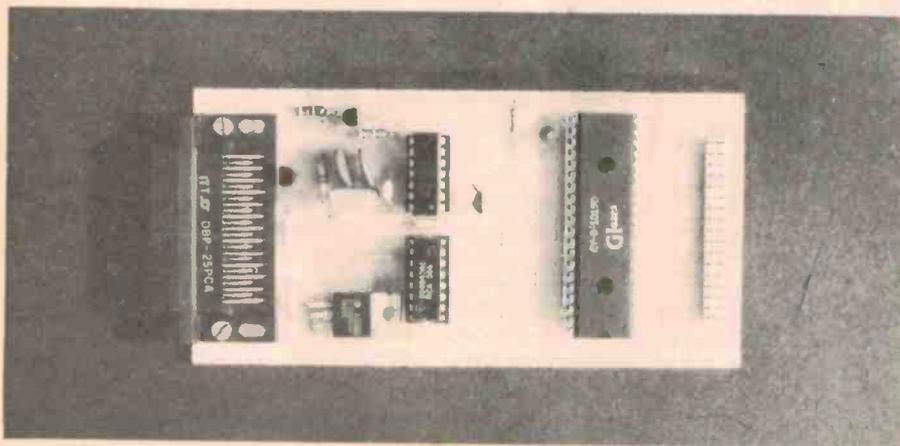
## HOW IT WORKS ETI-675


Most of the circuitry in the interface is inside IC1, a universal asynchronous receiver/transmitter, or UART. I have only utilised the receiver section, hence the large number of unused pins. Serial data enters the UART on pin 20 after being inverted and level shifted by Q1 to convert from RS232 voltages to TTL levels. When a complete word has been received the Data Available line (DAV) goes high, indicating that the word is ready to be read out. The DAV low-to-high transition triggers the monostable made from IC3 a, b, c. This generates the Data Strobe signal for the Centronics cable. The DAV signal also drives the Clear To Send (CTS) line on the RS232C side via inverting buffer Q2. This inhibits any further characters from the sending device (i.e. Microbee) until the printer has read the last one sent. When the printer is ready for another character it momentarily lowers the ACKnowledge line on the Centronics cable, which resets the DAV line via the UART input RDAV. This returns CTS to the high voltage and we are back where we started, ready to receive a new character.

The baud rate clock comprises IC3d, a standard crystal oscillator using a high speed CMOS gate, and IC2, a multistage divider. The divided outputs are brought to a



Plug in and go. There's not much to this project. The prototype here is configured to plug straight into a Microbee, but the project's suitable for any micro with an RS232C port.

# rs232-centronics interface

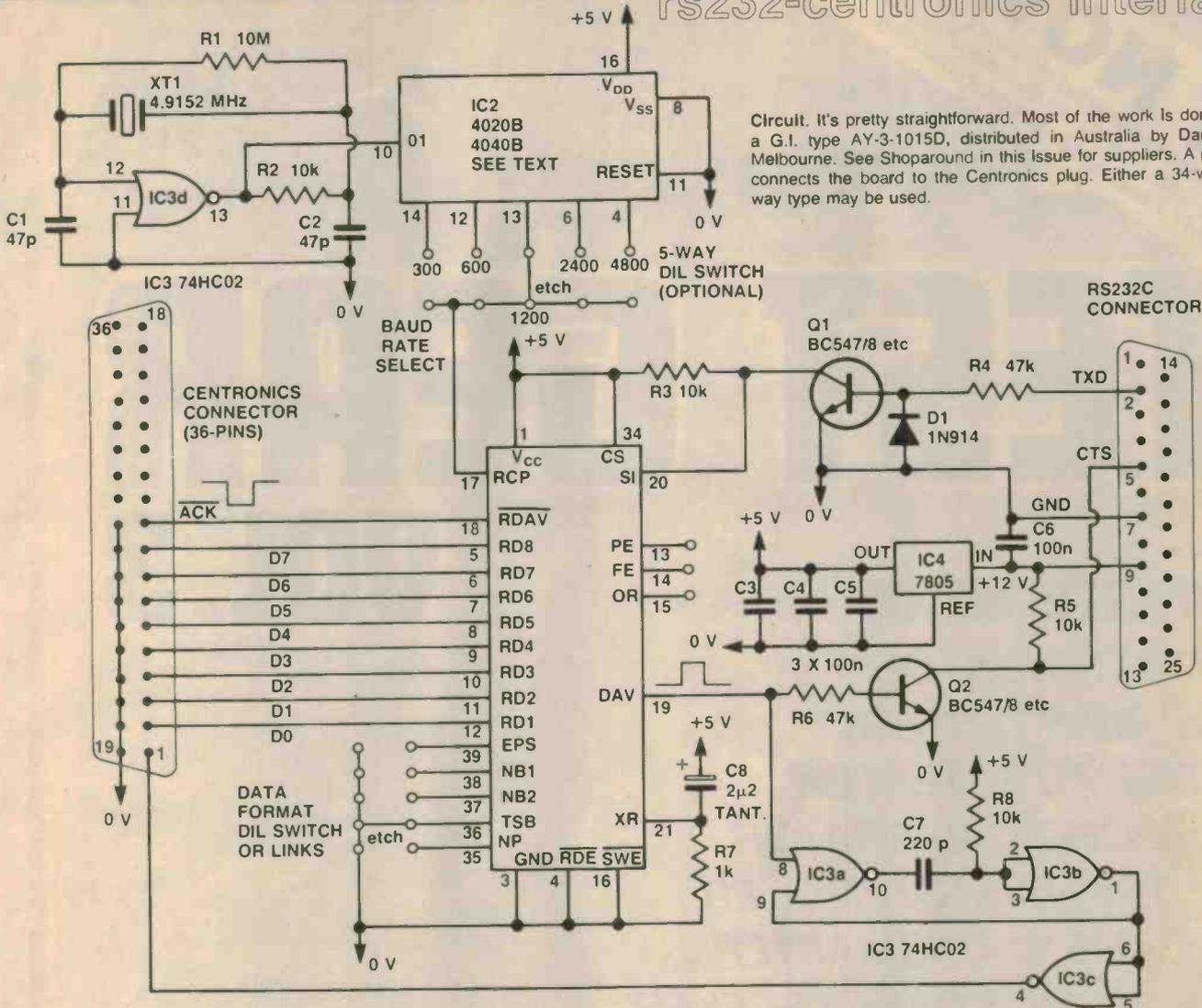

Circuit. It's pretty straightforward. Most of the work is done by IC1, a G.I. type AY-3-1015D, distributed in Australia by Daneva from Melbourne. See Shoparound in this Issue for suppliers. A pin header connects the board to the Centronics plug. Either a 34-way or 36-way type may be used.

pad array, which can be used with a 5-position DIL switch to change rates if you wish. The PC board is etched to only use 1200 baud, so that Microbee users need not change anything. Either a 4020B or 4040B can be used for IC2, but the highest two baud rates will be different (1200 baud is unaffected). The overlay shows the rates for a 4020B i.e: 300, 600, 1200, 2400 and 4800 baud. If a 4040 is used then the lowest three rates will be the same but extra links will have to run to get 2400 and 4800 baud, owing to the different pinouts. IC2 must be able to run with a 4.9 MHz clock at 5 V, which is slightly faster than the typical spec. for National devices, but is the

minimum spec. for Fairchild or Philips (HEF4020B, HEF4040B). The symptom of a slow device is that the first stage divides by three instead of two, so look at pin 9 with a counter to make sure all is well. The CR network of C8 and R7 reset the UART on power-up while IC4 and associated components develop the +5 V rail from the RS232C's positive supply. The pads near pins 35-39 of the UART set up the parity and bit length of the serial conversion, they are preset by board tracks to suit the Microbee.



between the UART and ICs 2 and 3. This allows the selection of different baud rates, parity and stop bits. The PC board comes with tracks etched to set eight data bits, one stop bit, no parity bit and 1200 baud. These suit most uses, but if you want to run some other combination then you will have to cut the two tracks and install wire links or DIL switches. The signal definitions are as per the diagram here and Table 1.

### OPTIONAL DIP SWITCHES

The PC board has been laid out to allow the option of fitting two 5-way DIL switch banks,

TABLE 1

SIGNAL	FUNCTION
EPS	ON — ODD PARITY      OFF — EVEN PARITY
NB1, NB2	NUMBER OF BITS PER CHARACTER
	NB2
	ON                      ON                      5
	ON                      OFF                    6
	OFF                    ON                    7
	OFF                    OFF                   8
TSB	ON — 1 STOP BIT      OFF — 2 STOP BITS
NP	ON — NO PARITY      OFF — PARITY EXPECTED

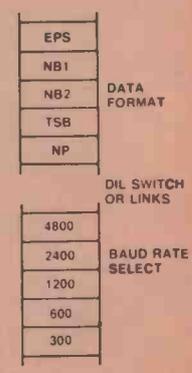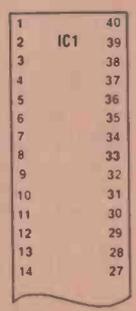

NOTE THAT YOU CAN ONLY GET 2400 AND 4800 BAUD WHEN USING THE 4020B FOR IC2

Only one switch in the baud rate bank may be on at one time, otherwise improper operation will occur.

**OUT NOW!**  
available at newsagents and selected electronics stores, or you  
can get it by mail order from ETI Book Sales, P.O. Box 227,  
Waterloo NSW 2017. Please add \$1 for post and handling.

**ELECTRONICS  
TODAY  
INTERNATIONAL**


**\$4.95\***  
**NZ \$5.95**

# TEST GEAR VOL.3



## PROJECTS INCLUDE:

- RF ATTENUATOR
- OP-AMP TESTER
- THE 'AUTO TESTER'
- TACHO CALIBRATOR
- TRANSISTOR TESTER
- THE 'MAINSMASTER'
- MAINS CABLE SEEKER
- ELECTRIC FENCE TESTER
- ELECTRONIC DUMMY LOAD
- 'PROTOTYPER' BREADBOARD
- FIVE-MODE LOGIC PULSER PROBE
- 13.8 V REGULATED HIGH CURRENT SUPPLY
- SIMPLE AND ACCURATE DIGITAL pH METER
- A PORTABLE CORE-BALANCE RELAY
- SIMPLE ANALOGUE FREQUENCY METER
- 30 V/1A PROTECTED POWER SUPPLY
- 'AUTO-PROBE' FOR TESTING VEHICLES
- LINEAR SCALE CAPACITANCE METER


## PIN HEADER (OPTIONAL)

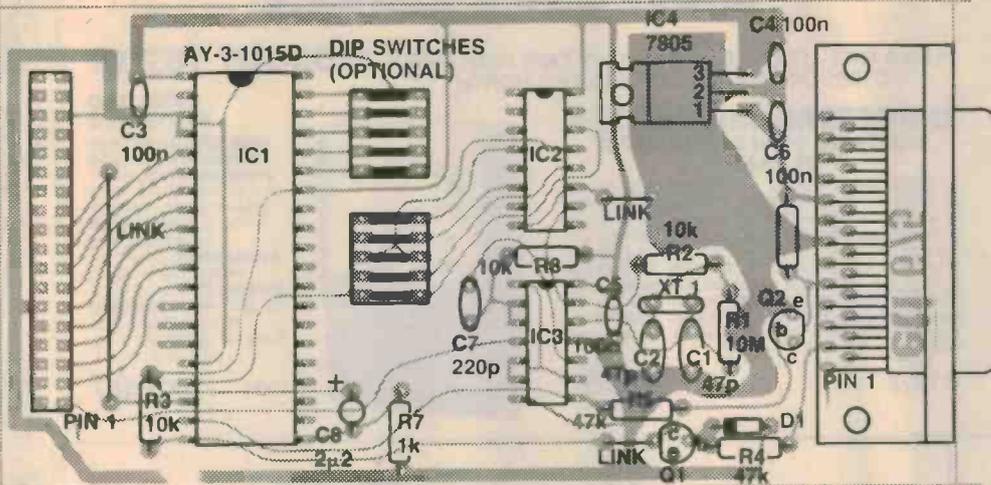


### VOLTAGE REGULATOR

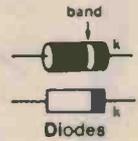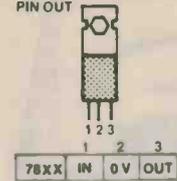

### Capacitors

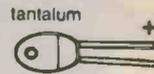

### RIGHT ANGLE PC MOUNT DB25P

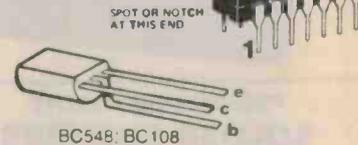


## PARTS LIST — ETI-675

- Resistors** ..... all 1/4W, 5%
  - R1 ..... 10M (10% OK)
  - R2, 3, 5, 8 ..... 10k
  - R4, R6 ..... 47k
  - R7 ..... 1k
- Capacitors**
  - C1, C2 ..... 47p NPO ceramic
  - C3, 4, 5, 6 ..... 100n 'bluechip' ceramic
  - C7 ..... 220p ceramic
  - C8 ..... 2µ2/6 V tantalum
- Semiconductors**
  - IC1 ..... AY-3-1015D (G.I.) or exact equiv.
  - IC2 ..... 4020B or 4040B (must run at 4.9 MHz on 5 V supply)\*
  - IC3 ..... 74HC02
  - Q1, Q2 ..... BC547, BC548 etc.
  - D1 ..... 1N914
- Miscellaneous**
  - XT1 ..... 4.9152 MHz crystal, HC18/U

ETI-674 pc board; right angle pc mount DB25 plug; 34-way pin header (0.1 x 0.1") — optional; 34-way female IDC plug (optional); IDC Centronics plug (if required); 34-way ribbon cable; two 5-way DIL switches (optional); etc.

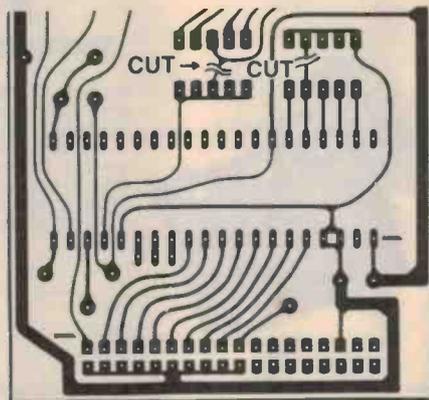**Price estimate: \$28-\$58**

\*Philips HEF4020B/HEF4040B and Fairchild 4020B/4040B known to work.



A cut above. To obtain other baud rates and data formats, the two tracks marked above must be cut. Links or DIL switches can be used to select the required configuration.

the other two are CMOS. Take the usual precautions against static damage.

Make up interconnecting cables to suit your individual requirements (see next section). If you're using a Centronics plug, I strongly recommend you use an insulation displacement type as the solder pin type is much harder to assemble, with a chance of errors and poor connections.

## Mounting

Actual mounting details are left up to you, as requirements will vary widely. The board can be mounted inside your printer, in which case the DP25P plug and 34-pin header may be dispensed with and the board wired-in directly. Alternatively, the board may be mounted inside a zippy box, or other suitable case, and cables wired to it with suitable connectors on the end. Or, if you have a Microbee, you can do as I did and plug it straight in to the DB25 socket on the rear of the cabinet and let it hang out the back. A couple of 'feet' might be useful, though. These could consist of two standoff pillars with rubber grommets attached, bolted to the end of the board either side of the 34-pin header. The overall price of the project depends on the connectors and case used — or not used.

## Using it


With a Microbee, just plug it in and go! With other micros, setting the baud rate and data format is simply a matter of cutting the two tracks (as indicated in the diagram here) and either installing links or DIP switches and linking the appropriate outputs across as per Table 1.

Happy LLISTing!

Solder all the resistors and capacitors in place first. Make sure you get the tantalum capacitor (C8) the right way round. Next solder D1 in place, making sure you get it the right way round, too. Follow with the two transistors, Q1 and Q2.

Solder the three links in place next, followed by the three IC sockets and the crystal. The three-terminal regulator (IC4) can be soldered in now. Note that a heatsink is not required for it. If you are using DIL switches for baud rate and data selection, these should be soldered in place next.

Last of all, solder the 34-pin header strip and DB25P right angle connector in place. The latter should be bolted to the board firmly before soldering so that no stress is placed on the solder joints. Insert the ICs now. The UART is an NMOS device, while

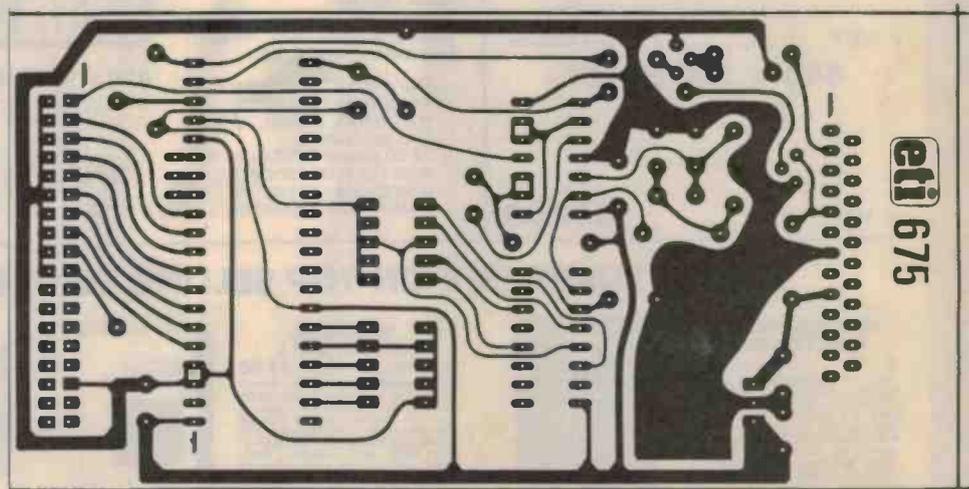

**eti 675**

Board artwork. Full-size reproduction of the pc board. ▶

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY



## SUPER PRICE SAVINGS

PLUS A FREE "LEATHER LOOK" CARRY CASE WITH EVERY ECONOMY TESTER Q1001 OR Q1002 PURCHASED THIS MONTH

### UNIVERSAL MULTIMETER PORTABLE WITH BENCH STAND ★ 23 RANGES ★

- 20,000 OHMS/Volt DC • 10,000 OHMS/Volt AC
- Mirror backed scale • Overload protected
- Unique carry handle doubles as a bench stand
- High-impact resistant case • Uses 1 AA Penlight battery (incl.) • Comes complete with battery, test leads and instructions.

**RANGES: DC Voltage** 0-25, 1, 2.5, 10, 25, 100, 250, 1000. **AC Voltage** 0-10, 25, 100, 250, 1000. **Decibels** 20 to + 22 db. **DC Current** 0-50, 500 UA, 0-5, 50, 500MA. **OHM Meter** 0-6 megohms in 4 ranges, 30 ohms centre scale. **Sizes** 135 x 91 x 39.

Q1002 ..... **\$19.50**



**OVERLOAD PROTECTED**  
High 2000 OHMS/Volt sensitivity overload protected. Dimensions 90 x 60 x 30. Mirror back scale prevents Parallax error. **Complete with test leads and instructions.** Uses 1 AA Penlight batt. (incl.) **Ranges:** DC and AC 0-10, 50, 250, 1000V. **Decibels:** 10 to + 22 db. DCA 0-100MA. OHMS 0-1 meg. OHM in 2 ranges.

Q1001... **\$11.00**

### PROFESSIONAL QUALITY SOLDER SUCKERS

Not to be compared with inferior "Hobby types". Saves countless hours in fault finding and repair of complex PCB's. **SINGLE HANDED OPERATION** SELF CLEANING PLUNGER **LONG LIFE TEFLON TIP** **DOUBLE DIAPHRAGM, DUAL O-RING SEAL** 225mm x 20mm(d) 50mm STROKE **POWERFUL SUCTION**



T1240... only **\$11.95**

T1241. Replac tip. **\$1.95**

### MINI STRIP 100 HOLES


P 1000..... **\$1.95**

### 640 HOLES



P 1005..... **\$8.50**

### 640 + 100 HOLES

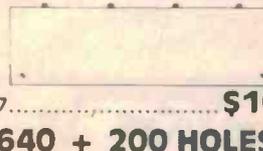

P 1007..... **\$10.00**

### 640 + 200 HOLES



P 1009..... **\$12.00**

### PROTOTYPE SOLDERLESS BREAD BOARDS


**NON-CORROSIVE NICKEL ALLOY CONTACTS** **RELIABLE FOR 50,000 INSERTIONS**

There's a limit to just how many times you can resolder components while prototyping before you either destroy the component or lift a track from the vero.

These solderless breadboards enable circuits to be literally thrown together in an instant, yet all components remain reusable.

A necessity in all research laboratories to save on expensive development costs.

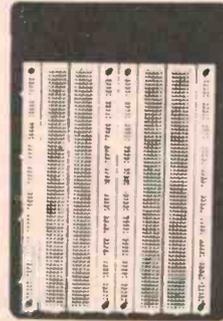- ☆ Standard 0.1 inch spacings.
- ☆ Accepts all LSI'S, semis, transistors, diodes, leds and passives.
- ☆ 22-30 gauge solid hook up wire for interconnections.
- ☆ Boards are "keyed" to enable easy expansion.




### 400 + 1280 HOLES

ACCEPTS UP TO 16 x 16 pin D.I.L. IC'S

SCREW TERMINALS FOR PS CONNECTIONS

P 1012..... **\$26**

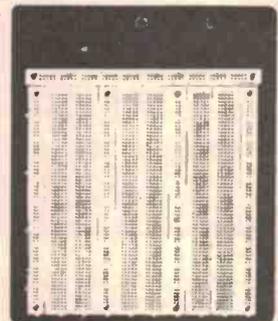

### 500 + 1920 HOLES

ACCEPTS UP TO 24 x 16 pin D.I.L. IC'S

METAL BACKING PLATE FOR SHIELDING OF SENSITIVE CIRCUITRY

P 1015..... **\$38**

### SUPER BUY ON TOP SELLING DATA BOOKS

#### MOTOROLA MASTER SELECTION GUIDE

B 1104..... **\$5.00**  
The most useful book ever printed. Covers MOS IC'S listed by function. LINEAR IC'S listed by function. INTERFACE IC'S listed by function. LSI memory, TTL ECL power products, SCR'S, diodes, transistors listed by application and ratings. RF, small signal and audio devices listed by application and ratings. Essential data given for all devices. **TERRIFIC VALUE**




#### MOTOROLA MEMORY DATA

B 1105..... **\$7.50**  
An absolute must for the micro-processor buff. This is the latest reprint of Motorola's famous Memory Data Manual and includes all the latest specifications and design application data on TTL RAM, TTL PROM, MECL MEMORY, MECL RAM, MECL PROM, MOS dynamic RAM, MOS static RAM, MOS EPROM, MOS EE PROM and MOS ROM. **Worth many dollars more!**


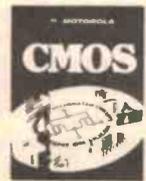
#### MOTOROLA CMOS DATA

B 1113..... **\$6.50**  
A comprehensive reference covering 800K, 450K CMOS family along with speciality devices such as LCD drivers, telephone and general communication functions and industrial control. **862 pages essential in all spheres of electronics.**



...a wide  
...ons in-  
...allows  
...students  
...are in  
...Hospital  
... (State)  
...contact Mr  
...Radiographer,  
...M. E. NORLE,  
...Address Officer,  
...HOSPITAL  
...TOR.  
...mitted from  
...a vacancy  
...Centre,  
...school of  
...and a diplo-  
...or equiv-  
...vacant will be  
...ical and class  
...formation con-  
...nce, Head of  
...to: Miss  
...of Nursing,  
...pital, P.O.  
...AE  
...est.  
...for:  
...i wages  
...Please  
...3 2222  
...60 bed  
...area  
...vine full

# POSITIONS VACANT

**OFFICE MANAGER  
FILING CLERK  
TYPIST  
BOOK KEEPER  
ACCOUNTS TYPIST  
DESPATCH CLERK**

St. Vincent's  
hospital  
medical  
located  
area and  
owned by  
Australia  
Ipswich  
approx  
only 40  
viced re  
Both th  
shire an  
expansi  
fation an  
offered.  
Respon  
total man  
ing Depar  
nursing sta  
dern Oper  
Director of  
integral man  
management  
The hos  
volved in  
programme  
While  
Administ  
emphasis  
experien  
ministrati  
mitment  
velopment  
Salary is  
Applicat  
confidentia  
The Execu  
839, Ipsw  
ST. VINCE  
DA  
CATER  
The st  
St

# MAYBE YOU JUST NEED A COMPUTER AND OUR SPELLBINDER WP SYSTEM.

Spellbinder is a full feature word processing system that helps you in the day to day running of your office.

Standard prompts and messages are built in to help you over the initial stages of use. Mailmerging and sorting extras on other systems are standard on Spellbinder. And even special features such as these are easy to use.

Also, Spellbinder has a flexible print format. It can drive inexpensive dot matrix printers, letter quality precision printers and typographic quality ones to full capacity.

And our powerful macro capability allows you to add features that help with any unique requirements you might have. So if you're looking for help in the office perhaps you should stop writing out classified advertisements and start filling in the coupon.

See Software Source for Basic/z, C-86, Directory Sort, Modem 86, Punctuation & Style, SuperCalc, WordPlus, VSpool & VEdit.

**Software Source Pty Ltd.**

P.O. Box 364 Edgecliff, N.S.W. 2027.  
Please send me full details of your Spellbinder system.

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_

## ONE ARM BANDIT

R.T. Webb, Canterbury NZ

This program is of a one-arm slot machine using PCG graphics.

When I was writing this program I found that there was a problem between the plot commands and the poked PCG characters. To overcome this interaction I first plotted the machine and calculated the PCG used which was 102. I then poked my characters in at 63488 + 103 \* 16. This solved the problem.



## NO NAME GAME

Llew Ashdown Camira Qld

I came up with this short routine while attempting to write a graphics orientated game for the kids. It's guaranteed not to crash and even a four years old child can play it happily.

The controls are: 'P' up; 'L' west; '.' east; '.' down; (space bar) halt.

### NO NAME GAME

```
00100 CLS
00110 LORES
00120 A=INT(RND*120)+1
00130 B=INT(RND*45)+1
00140 INVERT A,B
00150 A1$=KEY$:IF A1$="" THEN 150
00160 IF A1$="." THEN 220
00170 IF A1$="P" THEN 290
00180 IF A1$="L" THEN 430
00190 IF A1$="." THEN 360
00200 IF A1$="N" THEN 100:REM NEW GAME
00210 GOTO 150
00220 IF A>126 THEN 150
00230 A=A+1
00240 A2$=KEY$:IF A2$="" THEN 150
00250 INVERT A,B
00260 FOR S=1 TO 50 :NEXT S
00270 IF A>125 THEN 150
00280 GOTO 230
00290 IF B>46 THEN 150
00300 B=B+1
00310 A3$=KEY$:IF A3$="" THEN 150
00320 INVERT A,B
00330 FOR F=1 TO 100 :NEXT F
00340 IF B>45 THEN 150
00350 GOTO 300
00360 IF A<1 THEN 150
00370 A=(A-1)
00380 INVERT A,B
00390 A4$=KEY$:IF A4$="" THEN 150
00400 FOR C=1 TO 50 :NEXT C
00410 IF A<2 THEN 150
00420 GOTO 370
00430 IF B<1 THEN 150
00440 B=(B-1)
00450 INVERT A,B
00460 A5$=KEY$:IF A5$="" THEN 150
00470 FOR D=1 TO 100 :NEXT D
00480 IF B<2 THEN 150
00490 GOTO 440
```


```
00100 HIRES:SPEED 0:POKE 220,60:DIM Q1(4)
00110 CURS 205:PRINT "***** ONE ARM BANDIT *****"
00120 CURS 282:PRINT "R.T.WEBB."
00130 CURS 344:PRINT "KAIAPOI. N.Z."
00140 CURS 523:PRINT "YOU HAVE $50 AT THE START OF THE GAME":CURS 663:PRINT "$1
for each try"
00150 CURS 906:PRINT "IF YOU WISH TO ABORT PROGRAM PRESS KEY S"
00160 PLAY 24;16;24;16;24;16;12;4;12;4;12;4;12;4
00170 S=0:P=63488+103*16
00180 FOR A=P TO P+16*24-1
00190 READ B:POKE A,B
00200 NEXT A
00210 IF S=1 THEN GOTO 470
00220 CLS:L=1
00230 FOR Y=1070 TO 1100 STEP 10
00240 X=2:GOSUB (Y):PLAY 24:X=X+6:GOSUB (Y):PLAY 24:X=X+6:GOSUB (Y):PLAY 24:X=X+
6:GOSUB (Y):PLAY 24:X=X+2:PRINT " PAYS $10"
00250 L=L+2
00260 X=2:GOSUB (Y):PLAY 10:X=X+6:GOSUB (Y):PLAY 10:X=X+16:PRINT TAB(X) "PAYS $2
"
00270 L=L+2
00280 NEXT Y
00290 CURS 104:PRINT " $1 A TRY"
00300 CURS 744:PRINT "ALL OTHER "
00310 CURS 808:PRINT "COMBINATIONS"
00320 CURS 872:PRINT "LOSE"
00330 FOR I=1 TO 2000:NEXT I
00340 HIRES:PLOT 125,185 TO 283,185 TO 283,150 TO 125,150 TO 125,185
00350 PLOT 123,187 TO 285,187 TO 285,148 TO 123,148 TO 123,187
00360 PLOT 123,187 TO 103,207 TO 265,207 TO 285,187
00370 PLOT 103,207 TO 133,217 TO 345,217 TO 265,207
00380 PLOT 123,158 TO 123,118 TO 285,118 TO 285,187
00390 PLOT 123,118 TO 96,58 TO 258,58 TO 285,118
00400 PLOT 265,58 TO 345,98 TO 345,217
00410 X=103:FOR I=1 TO 17:X=X+9:PLOT X,207 TO X+18,187:NEXT I
00420 X=126:FOR I=1 TO 51:X=X+3:PLOT X,145 TO X,122:NEXT I
00430 PLOT 139,179 TO 269,179 TO 269,156 TO 139,156 TO 139,179:PLOT 171,176 TO 1
71,159 :PLOT 203,176 TO 203,159:PLOT 236,176 TO 236,159
00440 PLOT 139,179 TO 123,187:PLOT 269,179 TO 285,187:PLOT 269,156 TO 285,148:PL
OT 139,156 TO 123,148
00450 CURS 16,11:PRINT [A18 47]:CURS 17,10:PRINT [A18 47]:CURS 15,12:PRINT [A18
47]
00460 CURS 465:PRINT " * B A N D I T * "
00470 PCG:CURS 338 :PRINT"ghi":CURS 342:PRINT "jkl":CURS 346:PRINT"mno":CURS 350
:PRINT"pqr":CURS 359:PRINT "vw":CURS 423:PRINT "xy":CURS 487:PRINT "z(":CURS 551
:PRINT "):":NORMAL
00480 CURS 10:PRINT "Press any Key to pull the handle"
00490 W1=50
00500 REM
00510 CURS 940:PRINT "YOU HAVE $";W1;" "
00520 A1$=KEY$:IF A1$="" THEN GOTO 520
00530 IF A1$="S"OR A1$="s" THEN GOTO 1150
00540 W1=W1-1
00550 CURS 896:PRINT "
00560 CURS 940:PRINT "YOU HAVE $";W1;" "
00570 FOR V=1 TO 20
00580 PCG:CURS 338:PRINT"stu":CURS 342:PRINT "ust":CURS 346:PRINT"tus":CURS 350:
PRINT"stu"
00590 CURS 338:PRINT "tus":CURS 342:PRINT "stu":CURS 346:PRINT "ust":CURS 350:PR
INT "tus":NORMAL
00600 REM PLAY 1
00610 NEXT V
00620 REM
00630 B=338:FOR V=1 TO 4:Q1(V)=0:NEXT V
00640 FOR V=1 TO 4
00650 C=INT(RND*4)+1
00660 PCG
00670 IF C=1 THEN CURS (B):PRINT "ghi":Q1(V)=1
00680 IF C=2 THEN CURS (B):PRINT "jkl":Q1(V)=7
00690 IF C=3 THEN CURS (B):PRINT "mno":Q1(V)=15
00700 IF C=4 THEN CURS (B):PRINT "pqr":Q1(V)=21
00710 IF V=1 THEN CURS 342:PRINT "stu":CURS 346:PRINT "ust":CURS 350:PRINT "tus"
00720 IF V=2 THEN CURS 346:PRINT "stu":CURS 350:PRINT "stu"
00730 IF V=3 THEN CURS 350:PRINT "ust"
00740 NORMAL:LET B=B+4
00750 NEXT V
00760 REM
00770 T1=Q1(1)+Q1(2)+Q1(3)+Q1(4):S1=Q1(1)+Q1(2)
00780 REM
00790 IF T1=4 OR T1=28 OR T1=60 OR T1=84 THEN GOTO 1110
00800 IF S1=2 OR S1=14 OR S1=30 OR S1=42 THEN GOTO 1120
00810 IF W1<1 THEN GOTO 1130
00820 GOTO 510
00830 DATA 0,127,112,104,103,102,102,127,127,102,102,103,104,112,127,0
00840 DATA 0,255,0,0,255,129,66,60,60,66,129,255,0,0,255,0
00850 DATA 0,254,14,22,230,102,102,254,254,102,102,230,22,14,254,0
00860 DATA 0,124,6,3,65,32,16,127,127,16,32,65,3,6,124,0
00870 DATA 0,24,24,24,165,231,60,255,255,60,231,165,24,24,24,0
00880 DATA 0,62,96,192,130,4,8,254,254,8,4,130,192,96,62,0
00890 DATA 0,126,102,102,102,102,102,102,102,102,102,102,102,102,102,126,0
00900 DATA 0,66,126,24,24,255,255,0,0,255,255,24,24,126,66,0
```

# MICROBEE PROGRAM POTPOURRI

```

00910 DATA 0,126,102,102,102,102,102,102,102,102,102,102,102,126,0
00920 DATA 0,120,72,120,7,7,7,0,0,7,7,7,120,72,120,0
00930 DATA 0,60,60,60,129,129,255,102,102,255,129,129,60,60,60,0
00940 DATA 0,30,18,30,224,224,224,0,0,224,224,224,30,18,30,0
00950 DATA 0,72,0,73,73,0,36,0,73,0,0,34,0,0,65,0
00960 DATA 0,65,0,8,33,0,0,37,37,37,0,0,68,0,17,0
00970 DATA 0,36,0,65,0,0,34,0,73,0,64,0,146,146,146,0
00980 DATA 63,63,41,41,63,9,9,9,63,41,41,63,9,9,9,127
00990 DATA 255,255,37,37,255,36,36,36,255,37,37,255,36,36,255
01000 DATA 127,3,3,3,3,3,3,3,3,3,3,3,3,3,3,3
01010 DATA 255,240,240,240,240,240,240,240,240,240,240,240,240,240,240
01020 DATA 3,3,3,3,3,3,3,3,3,3,3,3,3,3,3,3
01030 DATA 240,240,240,240,240,240,240,240,240,240,240,240,240,240,240
01040 DATA 3,3,3,3,3,3,3,3,31,48,96,192,192,96,48,31
01050 DATA 240,240,240,240,240,240,240,240,255,48,96,192,128,192,96,255
01060 DATA 0,0,0,0,0,0,0,0,128,64,32,16,16,32,64,128
01070 CURS X,L:PCG:PRINT"gh1";:NORMAL:RETURN
01080 CURS X,L:PCG:PRINT"jk1";:NORMAL:RETURN
01090 CURS X,L:PCG:PRINT"mno";:NORMAL:RETURN
01100 CURS X,L:PCG:PRINT"pqr";:NORMAL:RETURN
01110 CURS 896:PRINT " YOU HAVE WON $10 " :PLAY 19,8;10;24,10:W1=W1+10:GOTO
510
01120 CURS 896:PRINT " YOU HAVE WON $2 " :PLAY 24;20;24;20:W1=W1+2:GOTO 51
0
01130 CLS:CURS 524:PRINT"YOU HAVE LOST ALL OF YOUR MONEY !!!":PRMT (?):PLAY 24;
23;22;21;20;19;18;17;16;15;14;13;12;11;10;9;8;7:CURS 651:INPUT"DO YOU WISH TO PL
AY AGAIN (yes/no)";K1$
01140 IF K1$="YES" OR K1$="yes" THEN GOTO 340
01150 IF W1<50 THEN CLS:CURS 530:PRINT "YOU HAVE LOST $";50-W1:CURS 590:PRINT "G
AMBLING IS NOT YOUR SCENE":POKE 220,111:END
01160 IF W1>50 THEN CLS:CURS 470:PRINT "YOU HAVE WON $";W1-50:CURS 527:PRINT "WE
LL DONE ! YOU KNOW WHEN TO STOP.":POKE 220,111:END
01170 IF W1=50 THEN CLS:CURS 530:PRINT "YOU ARE ALL EVEN.":CURS 582:PRINT "COME
ON WHERE'S THAT GAMBLING SPIRIT,PLAY AGAIN.":POKE 220,111:END

```

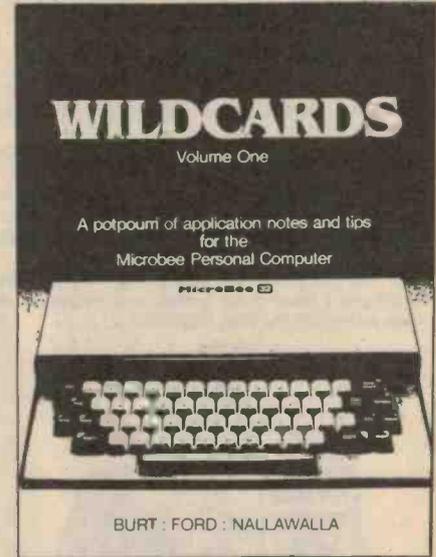

## BOOK REVIEW

**Wildcards** by Peter Ford, Ash Nallawalla and Bob Burt; published by BF & N Publishing, Williamstown Vic. 3016.

**Tom Moffat**  
39 Pillinger Drive, Fern Tree Tas. 7107

Have you noticed how the practice of computerism seems to be splitting into two groups, which we'll call Group A and Group B.

Group A people have probably spent around \$3000 on their systems. They surround themselves with spinning disk drives and high-res monitors, and they understand things like Augmented Transition Networks and the meaning of Ada.

Their computers are highly developed, operating to a tightly structured set of rules. Any attempt to bend the rules usually results in an angry beep and an error message, and that's that.

Nevertheless, many Group As consider themselves to be the real programmers, and the rest of us are, well, the Group Bs.

Group Bs use the cheapie computers, the VIC 20s, the ZX-81s, the VZ200s, the Commodores and the Microbees.

The Group B's computer may even be home made. Group B may own a printer that doesn't work, but at least it was cheap. Group B may put rude comments in REM statements just for the shock effect on others who read his software.

Group B doesn't object to using GOTOs even though they're not in fashion at the moment, and they may even understand what a Z80 uses its IORQ line for.

Group B will try anything once, and their computers may be just tolerant enough to let them get away with it. Wildcards is aimed fair and square at Group B.

Although Wildcards was written specifically for the Microbee, users of other small computers will find it a good read. It's not a book of programs, although there are several complete programs in it. It's more a book of ideas, hints, data, and some jolly good experiments.

The very first bit of advice in Wildcards is to backup your programs onto cassette, and the authors even provide appropriate cassette labels with an

invitation to photocopy them as required.

Because of the experimental nature of some of the programs some crashes are likely, and back-ups will save a lot of typing. It's a bit scary to spend an hour typing in a program, run it once, then delete most of it to find it still runs normally.

Wildcards then moves off to 'Tips and Techniques' — merging programs, mixing machine code and BASIC, and the book's first mention of embedding machine code in REM statements.

Next come some "Did you know that's" . . . like, did you know that (PRINT "TEST": PRINT: PRINT: PRINT: PRINT "TEST1": PRINT: PRINT) can also be written as (PRINT "TEST"////"TEST1"//)? That's only one of many sneaky tricks in Wildcards.

A major section of the book is devoted to the use of the Microbee's sound capabilities. There's a diagram of a piano keyboard and some standard musical notation, showing how the notes relate to the Microbee's PLAY command. Did you know that PLAY 0 can be used to generate a silent time delay up to 32 seconds long? Now why didn't I think of that?

There are several sound demo programs in the section, including another machine-code-into-REM job that lets you experiment with sounds other than PLAY . . . burbles and whistles and gliding tones.

The next few pages then take this sound program apart, modify it, explain it, and show you how to use its tricks in your own programs.

A section called 'Utilities' has such goodies as a program for investigating the contents of cassette headers, including those of non-Microbee origin. There's a program for printing your own 'fancy' cassette labels, and an interesting routine for making the Microbee think a BASIC program is a Wordbee file.

There's a whole section devoted to the efficient use of printers, but it's a pity there's no info on how to get a Microbee and a parallel printer to peacefully co-exist, especially outside of BASIC. The authors state they all use serial printers so they probably haven't met up with the MicroBee's stubborn parallel routines.

'Graphics', gets into the Microbee's programmable character generator in a big way, with some good advice and good examples. One program mixes BASIC with REM-embedded machine code and REM-embedded data, finishing off with a block move of the

whole screen to an area just above BASIC, where the whole works can be saved to tape.

The program takes one page and then an explanation of how it works, complete with disassemblies of the machine code routines, takes the next five. Good stuff.

But, I must now reveal, this program MLPAT1 contains a ripper of a bug. If you leave out spaces and some REMs, it will bomb out because it's too short!

It took a bit of work to figure out how this comes about, and I'm not going to reveal it here. It would be like giving away the plot of the book, and as I see it, that's what Wildcards is all about; figuring things out.

There are a couple of games presented, and at first sight you'll say "oh, no, not again!". They're Nim and Tic-Tac-Toe. But the authors have included them to show how all the good graphics stuff can be combined into a package. Once again, lots of notes on their workings.

We're not quite finished yet, there's still the appendix with graphics characters, hex/decimal/binary conversions, PCG address calculations, and an extensive memory map. There's even a library of DATA statements which make up graphics pictures.

Most of them seem to be for games programming . . . battleships, aircraft, bombs and sea monsters. I wrote a little program to try some of them.

One called 'ship with billowed sail' is particularly nice, and there's even a 'palm island' to run the ship into. The last picture is an outline of Australia, and speaking of islands, I'm happy to report that the authors did not leave Tasmania off, as was done at the Commonwealth Games and various other places.

All in all, I could only find one real complaint about Wildcards, in a section on setting audio levels into a cassette recorder's mic input. The authors show a voltage divider circuit of two to one. I've found something on the order of 50 to 1 is more appropriate. Many cassette reliability problems stem from recording at an extremely high level, resulting in distortion and bad data.

Is Wildcards good value? The asking price may at first seem a little steep at \$15, but look at it this way; you wouldn't blink at spending that much on a program tape, and chances are you'll get more adventures out of Wildcards.



# MICROBEE PROGRAM POTPOURRI

## MACHINE CODE MONITOR

Tony Clay, Lagon Qld

This program allows you to enter in a machine language program and save and use it under BASIC control.

The program should be entered in hex which is then converted to decimal which can then be POKEd into memory.

To convert from hexadecimal to decimal the ASCII code is used of the depressed key; this gives 48-57 (0-9) or 65-70 (A-F), and then either 48 or 55 is subtracted to give a value of 0-16. The first hex character is multiplied by 16 and the second one added to give a value of between 0 and 255 (one hex byte).

The second half of this program allows the machine language program to be saved and used again. It creates DATA statements which can be merged with another program and executed with READ and POKE statements.

If you make a mistake while entering, finish the byte and then hit back-space and try again.



```

00100 DIM Z(5) :I=0 :CLS
00110 PRINT " PRESS [BACK SPACE] TO EDIT , [ESC] TO FINISH"
00115 REM CONVERT HEX ADDRESS TO DECIMAL
00120 PRINT"\\"STARTING ADDRESS (IN HEX)"
00130 K=ASC(KEY): IF (K<48 OR K>57) AND (K<65 OR K>70)THEN 130
00140 PRINT CHR(K); :IF K<58 THEN LET K=K-48 ELSE LET K=K-55
00150 Z(I)=K: I=I+1 :IF I<4 THEN 130
00160 S = Z(0)*4096+Z(1)*256+Z(2)*16+Z(3): T=S :CLS
00170 UNDERLINE :PRINT"00 01 02 03 04 05 06 07";
00180 PRINT" 08 09 0A 0B 0C 0D 0E 0F" : NORMAL
00190 A=ASC(KEY)
00195 REM CHECK FOR ESCAPE OR BACKSPACE
00200 IF A=27 THEN 310
00210 IF A=8 THEN PRINT [A4 8]; :S=S-1 :GOTO 190
00215 REM ONLY LET 48-57 OR 65-70 ASCII CODES THROUGH
00220 IF (A<48 OR A>57) AND (A<65 OR A>70) THEN 190
00230 PRINT CHR(A);
00240 B=ASC(KEY)
00250 IF(B<48 OR B>57) AND (B<65 OR B>70) THEN 240
00260 PRINT CHR(B);" ";
00265 REM CONVERT ASCII CODE TO DECIMAL NUMBER (0 TO 16)
00270 IF A<58 THEN LET A=A-48 ELSE LET A=A-55
00280 IF B<58 THEN LET B=B-48 ELSE LET B=B-55
00285 REM CREATE EQUIVALENT OF 1 BYTE hex (0 TO 255) AND POKE
00290 N= A*16+B: POKE S,N: S=S+1
00300 GOTO 190
00305 REM CREATE DATA STATEMENTS ON TAPE
00310 PRINT " Set up tape recorder , Press a key when ready"
00320 K0%=KEY : IF K0%="" THEN 320
00330 C=0: L=10000: OUT#2 ON: PRINT L;" DATA";
00340 FOR J=T TO S-1
00350 PRINT PEEK(J);",": :C=C+1
00360 IF C<16 OR J=S-1 THEN 380
00370 L=L+10: PRINT CHR(13); CHR(10); L;" DATA"; :C=0
00380 NEXT J
00390 PRINT CHR(26) :OUT #2 OFF
00400 END
    
```

## DATA 70 CHARACTER SET

D. J. Whyatt, Sth Plympton, SA

To give your programs an authentic computer look, why not use Data 70 typeface?

The necessary data is given for 10 numerals and 26 upper case alphabetic characters. The UNDERLINE statement is used to set up the rest of the PCG RAM without the underscore to allow

punctuation marks and spaces to be used.

This program can be merged on to an existing program with a GOSUB 1000 early in the host program to set up the PCG RAM, and set up PCG mode.

Data like this is a real pain to type in, but once done it can be recorded and used wherever you like. An example of the type is shown to encourage you to wade through it.

### DATA 70 CHARACTER SET

```

01000 REM ***** DATA 70 TYPEFACE CHARACTER SET *****
01010 UNDERLINE:S=63488+ASC(" ")#16
01020 FOR L=S+15 TO S+94#16+15 STEP 16:POKE L,0:NEXT L
01030 RESTORE 1090:S=63488+ASC("0")#16
01040 FOR L=S TO S+10#16-1:READ D:POKE L,D:NEXT L
01050 RESTORE 1200:S=63488+ASC("A")#16
01060 FOR L=S TO S+26#16-1:READ D:POKE L,D:NEXT L
01070 RETURN
01080 REM ***** DATA FOR NUMERAL SET *****
01090 DATA 0,0,0,127,65,65,65,65,65,65,65,127,0,0,0
01100 DATA 0,0,0,12,4,4,4,4,31,31,31,0,0,0
01110 DATA 0,0,0,31,1,1,1,31,16,16,16,31,0,0,0
01120 DATA 0,0,0,62,2,2,2,62,3,3,3,63,0,0,0
01130 DATA 0,0,0,96,96,96,96,96,99,127,3,3,0,0,0
01140 DATA 0,0,0,127,64,64,64,127,1,1,1,127,0,0,0
01150 DATA 0,0,0,120,72,64,64,64,127,65,65,127,0,0,0
01160 DATA 0,0,0,127,65,1,1,15,8,8,8,0,0,0
01170 DATA 0,0,0,62,34,34,34,127,99,99,99,127,0,0,0
01180 DATA 0,0,0,127,65,65,65,127,3,3,3,0,0,0
01190 REM ***** DATA FOR ALPHABET SET *****
01200 DATA 0,0,0,62,34,34,34,127,97,97,97,97,0,0,0
01210 DATA 0,0,0,126,66,66,66,127,97,97,97,97,127,0,0,0
01220 DATA 0,0,0,127,65,64,64,96,96,96,96,97,127,0,0,0
01230 DATA 0,0,0,127,65,65,65,97,97,97,97,127,0,0,0
01240 DATA 0,0,0,126,64,64,64,126,96,96,96,96,126,0,0,0
01250 DATA 0,0,0,126,64,64,64,126,96,96,96,96,96,0,0,0
01260 DATA 0,0,0,127,65,64,64,99,97,97,97,97,127,0,0,0
01270 DATA 0,0,0,65,65,65,65,127,97,97,97,97,0,0,0
01280 DATA 0,0,0,8,8,8,8,12,12,12,12,12,0,0,0
01290 DATA 0,0,0,2,2,2,2,3,3,3,3,67,127,0,0,0
01300 DATA 0,0,0,66,66,66,66,127,97,97,97,97,97,0,0,0
01310 DATA 0,0,0,64,64,64,64,96,96,96,96,126,0,0,0
01320 DATA 0,0,0,127,73,73,73,105,105,105,105,105,0,0,0
01330 DATA 0,0,0,127,65,65,65,97,97,97,97,97,97,0,0,0
01340 DATA 0,0,0,127,67,65,65,65,65,65,65,127,0,0,0
01350 DATA 0,0,0,126,66,66,66,126,96,96,96,96,0,0,0
01360 DATA 0,0,0,127,65,65,65,65,65,65,65,79,127,0,0,0
01370 DATA 0,0,0,126,66,66,66,127,97,97,97,97,97,0,0,0
01380 DATA 0,0,0,127,65,64,64,127,3,3,3,67,127,0,0,0
01390 DATA 0,0,0,127,8,8,8,12,12,12,12,12,0,0,0
01400 DATA 0,0,0,65,65,65,65,97,97,97,97,97,127,0,0,0
01410 DATA 0,0,0,97,97,97,97,97,97,97,97,97,0,0,0
01420 DATA 0,0,0,73,73,73,73,105,105,105,105,105,127,0,0,0
01430 DATA 0,0,0,33,33,33,33,127,97,97,97,97,97,0,0,0
01440 DATA 0,0,0,66,66,66,126,24,24,24,24,24,0,0,0
01450 DATA 0,0,0,127,65,1,1,127,96,96,96,97,127,0,0,0
    
```


THIS IS DATA 70. IT CAN ADD A TOUCH OF CLASS TO OTHERWISE DULL PROGRAMS.  
THE NUMERALS LOOK LIKE : 1 2 3 4 5 6 7 8 9 0

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

# MICRON SUPER 80

80 CPS : 80 COLS  
BIT IMAGE GRAPHICS  
FRICTION FEED AND  
ADJUSTABLE SPROCKET FEED

MADE IN JAPAN  
QUALITY

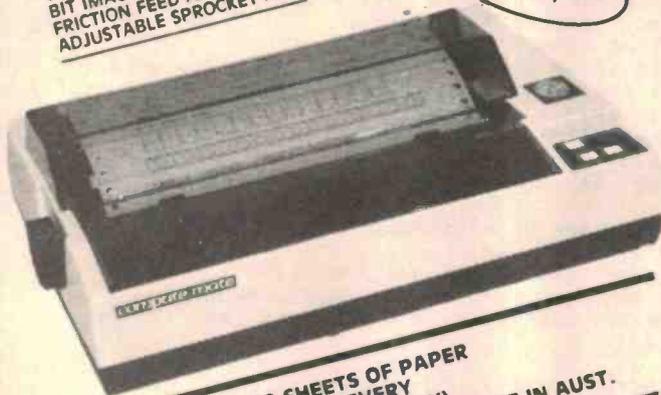

**BONUS OFFER**


1000 SHEETS OF PAPER  
FREE WITH EVERY  
PRINTER (JAN. ONLY)  
• \$10 DELIVERY ANYWHERE IN AUST.

**A FEATURE  
PACKED DOT MATRIX  
PRINTER FOR UNDER \$500**

Your "Super 80" printer will enable you to print letters, reports, graphics generated pictures, etc and importantly for the programmer, Hard Copy of program listings. Operating under software control from any general purpose micro-computer the Super 80 features 13 different print types including emphasized (LETTER QUALITY). Bidirectional print action ensures smooth, quiet operation.

**228 ASCII Characters, Handles 4" to 10" Paper  
STANDARD CENTRONICS INTERFACE**

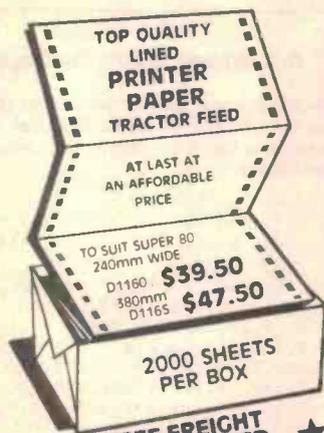- VALUE PACKED AT D1174..... **\$499.50**
- INTERFACE CABLE TO SUIT MICROBEE D1190..... **\$45.00**
- SPARE RIBBON D1175..... **\$12.50**



## CENTRONICS PLUG

36 WAY  
D1192  
**\$14.95**



When you buy one of our printers you'll need a centronics plug. If you are MICROBEE USER, have a look at our INTERFACE KITS on the opposing page.

## DIRECT IMPORT PRICE ON QUALITY JOYSTICKS




SELF CENTERING TYPE \* HEAVY DUTY SUCTION CUPS — STAYS IN PLACE \* SILVER PLATED SWITCH CONTACTS \* PISTOL GRIP \* VERY RESPONSIVE.

- TO SUIT COMMODORE VIC-20, ATARI, etc. D1410 ..... **\$19.50**
- TO SUIT MICROBEE D1420 ..... **\$29.50**
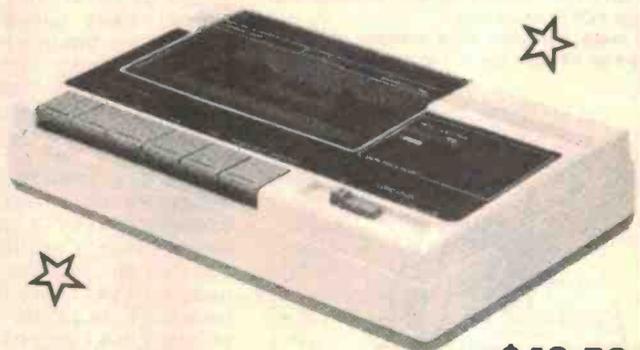
## NEW MODEL DATA CASSETTE

UNCONDITIONALLY GUARANTEED TO SAVE/LOAD THE RAWEST OF DATA EVERYTIME!



D1122..... **\$49.50**

A recorder designed solely for the purposes of data storage now at an unbelievable price

- \* SLIDE VOLUME CONTROL a **must** for quick checking of levels.
- \* TAPE COUNTER a **must** for easy location of programmes.
- \* INBUILT PEIZORANSUDUCER enables you to listen audibly to tape level
- \* 6V DC operation - USE WITH M9000 PLUG PACK ensures low hum levels.
- \* ROBUST CONSTRUCTION OF BOTH INTERNAL MECHANISMS AND EXTERNAL CASE.
- \* LONG LIFE ALKALINE BATTERY SUPPLIED (4 x AA CELLS)

## C20 DATA CASSETTES

Quality MICRON brand.

- D1141 ..... **\$1.50** (10 UP) ..... **\$1.25**

Unit shown has extra key

## MULTI-TURN TRIMMERS INDUSTRY PREFERRED TYPE

ALL ONE PRICE  
**\$1.95**  
10 up ..... \$1.80



Resist-ance	Cat	Resist-ance	Cat	Resist-ance	Cat
100 R	R 2410	5K	R 2423	200 K	R 2433
200 R	R 2415	10 K	R 2425	500 K	R 2435
500 R	R 2417	20 K	R 2427	1 M	R 2437
1 K	R 2419	50 K	R 2429	2 M	R 2439
2 K	R 2421	100 K	R 2431		

Great for powering small Micro's, TV Games, Slot Car Sets, etc.

Eliminate the need for batteries, when testing or operating new projects.

Both Plug packs come with instructions and a 4 way multiplug 1.6m lead.

**M9000**  
240v AC — 3, 4.5, 6, 7.5, 9,  
12v DC @ 300mA  
ONLY ..... **\$12.50**  
4 OR MORE ..... **\$11.00**

**M9005**  
240v AC — 6, 9, 12v DC  
@ 500mA  
ONLY ..... **\$14.95**  
4 OR MORE ..... **\$13.50**



## DC PLUG PACKS

AT LAST . . . DIRECT IMPORT PRICES  
ON FULLY APPROVED PLUG PACKS

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

# Computer club list

This list was compiled courtesy of Your Computer magazine Data Base.

## A.C.T.

**ACT Micro 80 Users Group**, Bill Cushing, 10 Urambi Village, Kambah, 2902, 062 313630.

**ACT Vic 20 Users Association**, Chris Groenhout, 25 Kerferd St, Watson, 2602, 062 41 2316, Meetings 1st Monday each month at Boy's Grammar Scout Hall, Red Hill, 7.30 onwards.

**ACTARI**, Chris McEwan, Co-Ordinator, ACTARI, P.O. Box E112, Canberra, 2600, 062 88 7861.

**Apple User Group (ACT)**, Jeff Brock, 1 Buckley Circuit, KAMBAH, 2902, 062 313630.

**Australian ZX80 Users Group (AZUG)**, David Brudenall, 19 Godfrey Street, Campbell, 2601, for ZX80/Microace owners.

**Canberra ACT Sirius User Group**, Jim Bland, 062 81 2824, 062 81 2832.

**Canberra Compucolor Club (CCC)**, Meets 7.30 on first Sunday of every month at the offices of Digital Equipment, 28 Lonsdale Street, Braddon ACT.

**Canberra Microbee Users Group**, Hugh Gibson, Microbee Store, Level 1, Cooleman Court, Weston, 2611, 062 88 6384.

**Canberra Microbee Users Group**, Adrian Van Wierst, 9 McGowan Street, Dickson, 062 49 7030.

**Micsig**, Registrar, P.O. Box 446, Canberra, 2601.

**Omega**, Geoff Cohen, 72 Spoforth Street, Holt, 2651.

**Sorcerer Users of Australia**, Mr G.T.Dick, 31 Cresswell st, Campbell, 2601.

## N.S.W.

**Albury-Wodonga Dist Mbee U.G.**, Eric Eulenstein, 202 Kooba St, Albury, 2640, 060 25 1601.

**Apple Users Group**, Colin Rutherford, P.O. Box 505, Bankstown, 2200, 02 520 0926.

**Atari Computer Enthusiasts**, Gary Francis, 78 Ayres Road, St. Ives, 2075, 2 0933 ext 354, or 789 1379.

**Ausbug**, Stephen Ford, P.O. Box 62, Londonderry, 2753.

**Australasia ZX80 Users Group**, Tony Mowbray, 87 Murphys Ave, Kieraville, 2500, 042 28 5296, for ZX80/81 Microace owners.

**Australasian ZX80 Users Newsletter**, 87 Murphys Ave, Kieraville, 2500.

**Blue Mountains Microbee Computer Club**, Roger Cooper, 047 58 7238.

**Blue Mountains Computer Club**, Eric Linsay or T. Macindoe, C/- P.O. Faulconbridge, 2776.

**Central Coast Computer Club**, Ron Thornton, P.O. Box 36, Ettalong Beach, 2257, 043 28 2862, 1st and 3rd Tuesday every month at Applied Technology, West Gosford, for all computers.

**Commodore Users Group**, John Guldice, G.P.O. Box 4721, Sydney, 2001.

**Compucolor Users Group**, David Brown, 91 Regent Street, Chippendale, 2008.

**Cumberland Computer User Group**, S. O'Neil, 02 682 3851. 80-AT, The Australian 8080-Z80 Users, P.O.Box 165, Lakemba, 2195.

**A.P.F. Users Group**, Norm McMahon, 288 Kissing Point Road, TURRAMURRA, 2074, 02 44 2645.

**Hawkesbury MicroBee Computer Club**, Bruce Rennie, 045 67 7329.

**Hunter U. G.- All Microcomputers**, Secretary, P.O. Box 39, BROADMEADOW MNSW, 2298, Meets on the second Wednesday of each month in Room 308, building W, University of Newcastle at 7.45pm. Membership is primarily Apple II orientated, but anyone with interest in micros welcome.

**Illawarra Microbee Computer Club**, Ronald Read, 49 Beatus Street, Unanderra, 2526.

**Illawarra Super 80 Users Group**, Jim O'Grady, Chairman, P.O. Box 1775, Wollongong, 2500. **MEGS (Microcomputer Enthus. Group)**, John Whitlock, P.O. Box 3, St Leonards, 2065.

**Macarthur Computer Association**, R.G. Freind, 109 Campbellfield Ave., Cambelltown, 2560, 046 25 2752.

**Mi Computer Club**, Norma Jackson, P.O. Box 21, Waterloo, 2017, 02 662 8888.

**Newcastle Microcomputer Club**, Mr. Gordon Johnson, Electron Microscope unit, University of Newcastle, 049 685045.

**N.S.W. 6800 Users Group**, 27 Georgina Ave., Keiraville, 2500.

**Northern Beaches Vic User Group**, E. Tuxford, 161 Barrenjoey Rd., Newport, 2106, Ph 997 2467, Community Centre.

**Northern N.S.W. MICC Chapter**, Alen Hartley, Dundurrabin via Dorrigo, 2433, 066 57 8160.

**Northside Microbee Computer Club**, Tony Williams, 6 Tunks Street, WAVERTON, 2060, 267 7747 bh, Meets on third Saturday of each month from 1-5pm at McMahons Point Community Centre. This is at the junction of Lavender St and Blues Point Rd, just short walk from Nth Sydney station.

**N.S.W. Peach User Club**, Daniel Soussi, 02 698 8286, weekly meetings on Saturday from 2pm at 'Cybernetics Research' 120-122 Lawson St Redfern.

**Pocket Computer Users Club**, George Antonijevic, 02 683 4296, for those interested in pocket computers, whatever the brand. Meetings held on the first Wednesday of each month at 7.30pm at the 'Woodstock' Community Centre, Church St. Burwood.

**Sorcerer Users Group**, Mr. Ian King, P.O. Box 62, St James, 2001.

**Sutherland Super 80 Group**, Jim Traeger, 02 525 2018, Super 80.

**Sydney Forth Group**, Peter Tregagle, 10 Binda Road, Yowle Bay, 2228, 02 524 7490, Forth Computer Language.

**Sydney MicroBee Users Club**, Tony Wilson, 02 909 3957.

**Sydney Peach User Group**, Ben Sharif, 261 Northumberland Street, Liverpool, 2170, 02 601 8493.

**T.I. Sydney Home Computer U.G.**, P.O. Box 149, Pennant Hills, 2120.

## Victoria

**Apple Users Society of Melbourne**, G. Halprin, 03 859 5835.

**AT Microcomputer Club**, Grant Forest, 03 8792257ah, 03 699 2888 bh. This club has been formed for people interested in the Applied Technology DGOS Z80.

**Atari User Groups Melbourne**, Kelvin Eldridge, P.O. Box 173, 3073.

**Australian Forth Interest Group**, Tony Latermore, P.O. Box 704, SALE, 3850, 051 44 2011.

**Australian North Star Users Assoc.**, P.O. Box 194, WANGARATTA, 3677.

**Ballarat Computer Users Group**, Publicity Officer: John Preston, 053 31 4363.

**BUG 80 (Burwood Users Group)**, P.O. Box 46, BLACKBURN SOUTH, 3130.

**Chip 8, 6800, 1802 User Group**, Frank Rees, 27 King Street, BOORT, 3537.

**Compucolor Users Group**, L Ferguson, 12 Morphett Avenue, ASCOT, 3342.

**Forth Interest Group**, Lance Collins, P.O. Box 103, CAMBERWELL, 3124, 03 29 2600, Meets on the first Friday of the month.

**Geelong Computer Club**, Peter McKeon, P.O. Box 93, GEELONG, 3220.

**IBM & Columbia Computer Users Club**, Giles Bray, 22/11 Auburn Grove, Hawthorn East, 3123, 82 7632, 2nd Tuesday each month, 7.30 at the Victorian College of Pharmacy.

**KAOS (Ohio Scientific)**, David Anear, 49 Millewa Crescent, DALLAS, 3047.

**Kaypro Users Group**, Stephen Foley, 03 857 7236.

**Latrobe Valley Colour Computer U.G.**, George Francis, 31 Donald Street, Morwell, 3840, 22 1389, for TRS-80 & MC10 users.

**Melbourne Atari Computer Enthusiast**, Group is an Atari 400/800 personal computer user group for Australians and New Zealanders. Meetings held on first Sunday of each month at 12pm at 3M Australia Cnr. Blackburn & Ferntree Gully Rd., Melbourne.

**Melbourne MicroBee Users Group**, 03 741 5534.

**Melbourne Super 80 Users Group**, Hon. Sec. Victor Shuttleworth, 03 723 2713.

**MICOM**, Microcomputer Club of Melb., P.O. Box 60, CANTERBURY, 3126.

**National Sinclair User Group**, P.O. Box 148, GLEN WAVERLEY, 3150.

**National ZX80 Users Club**, 24 Peel Street, COLLINGWOOD, 3066.

**North/Westn Sub. Comp. Users Group**, John King (Secretary), 284 Union Road, MOONEE PONDS, 3039, 03 338 9304, Contact CP/M Data Systems.

**Ohio Superboard Club**, 27 McGown Road, MT ELIZA, 3930.

**Peninsula Computer Club**, George Thompson, 3 Patterson Street, Bonbeach, 3196, 772 2674, 2nd Tuesday each month at Chisholm College, Frankston, many types of computers are catered for. ▶

# Computer club list

**SMUG, SCORD M100 Users**, Robin Miller, 60 Winnmalee Drive, GLEN WAVERLEY, 3150.

**Sorcerer Computer Users (Australia)**, Secretary, P.O. Box 144, DONCASTER, 3108.

**The Motorola User Group Soc. (MUGS)**, Clive Allan, 11 Haros Avenue, NUNAWADING, 3131, 03 878 1298, Group is interested in 6800/02/09 based computers, particularly if running Flex although this is not a prerequisite to join.

**Vic. Assoc. of Computer Educators**, Arthur Totrall, P.O. Box 69, WHITTLESEA, 3757.

**Victorian VZ200 User Group**, Luigi Chiodo, 24 Don St., Reservoir, 3073, 03 460 3770.

**ZX81 Software Exchange, C/Chips Taens**, 5 Muir Street, MT. WAVERLEY, 3149.

## QLD

**Apple-Q the Brisbane User Group**, The Secretary, P.O. Box 721, SOUTH BRISBANE, 4101, Has User Group days every third Sunday of month at Hooper Education Centre, Kuran St. Wavell Heights. Centre is open from 8.30am till 4.30pm, members encouraged to bring Apple along.

**Australian Sirius Users Group**, P.O. Box 204, CHERMSIDE, 4032, 07 350 2611, Looks after the needs of Sirius One and Victor 9000 computer users. For membership form write to above address.

**Brisbane Super 80 Users Group**, Gary Gatfield, 08 355 3173. CBM/VIC Users Group of N.T., Ian Diss, 089 27 9208.

**Brisbane Youth Computer Group**, A. Harrison, P.O. Box 396, Sunnybank, 4109.

**Commodore Computer Users Group QLD**, Mrs D D Dillan, P.O. Box 127, STONES CORNER, 4120.

**Commodore Users Group**, John Egan, P.O. Box 274, SPRINGWOOD, 4127, 07 287 2705, Is for owners of Pet/CBM and Vic-20 machines. Meetings held on the first Tuesday of the month at 130 Petrie Terrace, Brisbane.

**Computer Owner's Group**, Betty Adcock, 42 Lucan Ave, Aspley, 4034, 263 4268, 2nd Wednesday each month, 7.45 pm, all kinds of computer are catered for.

**Gold Coast Microbee User Group**, Col McLaren, 1-100 Imperial Parade, Labrador, 4215, 075 314610, meetings first Sunday each month, 3.00 at the Southport High School.

**IREE Microcomputer Interest Group**, N Wilson, P.O. Box 811, ALBION, 4010.

**Mackay Microbee User Group**, Geoff Gehring, Box 230, Mackay, 4740, 079 42 3214.

**Superboard Users Group**, Ed Richardson, 146 York Street, NUNDAH, 4012.

**The Microcomputer Society**, The Secretary, P.O. Box 580, FORTITUDE VALLEY, 4006, Meetings are held on the second Friday of each month in the Old Town Hall, corner Vulture and Graham Streets, Sth Brisbane. Meetings start at 7.30pm if main gate is closed use the back stairway.

**Townsville MicroBee User Group TMUG**, Chris Hayes, 077 796065ah, Meets at 7pm on the second Monday of the month. Another 'user' meeting is held later in the month. Meetings are held at Town and Country Computers, CTL Centre, Anne St. Aitkenvale QLD.

**TRS80/System 80 Interest Group QLD**, 396 2998, Meets on the first Sunday of each month at 21 Rodney St, Lindum, at 2 pm.

**ZX 81 Club**, P. Carswell, 22 Braud Street, BUNDABERG, 4670.

## S.A.

**Adelaide Atari Computer Club**, Shirley Cornish, 11 Sweetwater Street, Secombe Gardens, 5047, 08 296 6553, 1st Monday each Month at 6 Mosely Street, Glenelg.

**Adelaide Micro User Group**, R. G. Stevenson, 36 Sturt Street, Adelaide, 5000, for TRS-80 and System 80 Users.

**Beebnet**, P.O. Box 262, KINGSWOOD, 5062, The group intends to produce a newsletter on a monthly basis. It is interested in any software producers or distributors who would be interested in serving the groups market requirements.

**Commodore/Vic Computer Users Assoc.**, Mr Eddie Hann, 13 Miranda Road, PARALOWIE, 5108, The SA branch meets monthly.

**Compucolor-Intecolor User of S.A.**, P.O. Box 86, Torrensville, 5031, 08 352 3296.

**Darwin Microbee Users Group DBUG**, Felino Molina, P.O. Box 3111, DARWIN, 5794, 089 82 5613bh, 089 88 1455ah.

**Kaypro User Group**, Myles Wakeham, 100 Pirie Street, Adelaide, 5000, 08 223 6333, meetings 1st Tuesday each month.

**Microbee Users Club of S.A. MUCSA**, Ross Savas, 26 Denman Terrace, Lower Mitchum, 08 277 7697.

**N.T. 80 Computer User Group**, R T O'Brien, 433 McMillans Road, Jingili, Darwin, 5792.

**S.A. Commodore Computers U.G.**, Eddle Hann, The Secretary, P.O. Box 427, North Adelaide, 5006, 258 6367, meetings second Tuesday each month, 7.30 at Royal Caledonian Hall, 379 King William St, Adelaide.

**S.A. Hitachi User Group**, Cliff Hignett, 45a Ormond Ave, Daw Park, 5041, 08 274 9341.

**S.A. Microprocessor Group Inc SAMG**, The Secretary, P.O. Box 113, Plymton, 5038, 08 278 7288.

**Sorcerer Users Group of S.A.**, Jeremy Webber, 22 Delange Avenue, BANKSIA PARK, 5019.

**South Australian Apple Users Club**, The Secretary, SAAUC, C/- The Bookshelf, 169 Pirie Street, Adelaide, 5000.

**The Microcomputer Assoc. of the N.T.**, Andy Smith, Darwin Community College, CASUARINA, 5792.

## W.A.

**CU WEST WA Compucolor/Intecolor U.G.**, John Newman, 8 Hillcrest Drive, Darlington, 6070.

**OSWEST-Osborne Users Group of W.A.**, 09 330 3439.

**Perth 80 Users Group**, C Powell, 09 457 6849, for System 80 and TRS 80 Users.

**Perth Hitachi Peach Club**, The Secretary, 1 Chaff Court, Riverton, 6155, 09 367 5880, for Hitachi Peach & 6809s.

**Sorcerer Computer Users of Aust.**, The Secretary, 90 King George Street, PERTH SOUTH, 6151, 09 367 6351.

**Super 80 Users Group Perth**, Garry Black, 19 Bendigo Way, CITY BEACH, 6015, 09 385 8813.

**The W. A. Atari Computer Club**, Mr Alf Gaebler (Secretary), P.O. Box 7169, Cloisters Square, PERTH, 6000.

**W.A. Microbee Club**, Mike Oborn, 09 447 5366.

**Vic-Ups**, G. Padfield, 09 451 4629.

**W.A. ZX Users Group**, Phil Taylor, 09 328 4111, (bh).

**WA University Computer Club**, 2nd Floor, University of WA, Guild Building, 09 386 1455.

## Tasmania

**Devonport Computer Interest Group**, John Steveson, R.S.D 422, SHEFFIELD TASMANIA, 7306, 004 92 3237.

**Spectravideo Computer Users Group**, Mr W. P. Deckert, 48 Heather Street, LAUNCESTON, 7250, 44 4836, Membership to the club costs \$15 which entitles members to a newsletter and to discounts in computer equipment. Monthly meetings of the club are held.

**TAS-Micro**, Peter Deckert, Unit 1/456 West Tamar Road, RIVERSIDE, LAUNCESTON, 7250.

**Tasmanian Commodore Users Assoc.**, Vincent T. Staggard, The Secretary, G.P.O. Box 391D, Hobart, 7000, 002 72 0295, Commodore and others

**Tasmanian OSI User Group**, David Tasker, 111 Bass Highway, Westbury, 7303.

## N.Z.

**1802 Users Group**, P.O. Box 6210, AUCKLAND, NEW ZEALAND, For those who own an ETI-660 or a COSMAC VIP, you can contact the 1802 Users Group. Be kind and send them a return addressed envelope and some International Reply Coupon.

**Nelson Vic Users Group**, Peter Archer, Nelson VIC Users Group, C/o P.O. Box 860, Nelson N.Z., for Vic and Commodore.

**Wellington Microcomputer Soc. Inc**, Lindsay Williams, 2 Pope Street, PIMMERTON, NEW ZEALAND.

**ZX81 Club**, R Skelton, C/- Harbourside Orchard, WAIUKU NEW ZEALAND. ●

# ETI Book Sales

## electronics textbooks

### ELEMENTS OF ELECTRONICS — BOOK 2

**A0004B** \$9.95  
Alternating current theory.

This series is an introduction to modern electronics. All the maths is taught as the reader progresses. The course concentrates on the understanding of concepts central to electronics, rather than digressing over the whole field. The author anticipates where difficulties lie and guides the reader. Book 1 covers all fundamental theory necessary to full understanding of simple electronic circuits and components.

### ELEMENTS OF ELECTRONICS — BOOK 3

**A0005B** \$9.95  
Semiconductors technology leading to transistors and ICs.

### ELEMENTS OF ELECTRONICS — BOOK 4

**A0006B** \$9.95  
Microprocessing systems.

### ELEMENTS OF ELECTRONICS — BOOK 5

**A0007B** \$9.95  
Communications.

### BASIC ELECTRICITY/ELECTRONICS — VOL 1

**A0008P** \$15.95  
Thorough theoretical and practical background to the overall subject of electricity and electronics.

### BASIC ELECTRICITY/ELECTRONICS — VOL 2

**A0009P** \$15.95  
Builds on the basic information in Volume 1 by giving detailed information on AC and DC circuits — covering series and parallel circuits, electro-magnetism, resistance, capacitors and inductance plus associated calculations.

### BASIC ELECTRICITY/ELECTRONICS — VOL 3

**A0010P** \$15.95  
Valves and transistors, from an introduction to vacuum tube — through multi-element tubes, semiconductor devices, power supplies, amplifiers, oscillators, pulse circuits — to special semiconductor devices.

### BASIC ELECTRICITY/ELECTRONICS — VOL 4

**A0011P** \$15.95  
Construction, operation and usage of electronic test instruments. Included are analogue and digital multimeters, vacuum-tube voltmeters, oscilloscopes, tube testers, bridge instruments and signal generators.

### BASIC ELECTRICITY/ELECTRONICS — VOL 5

**A0012P** \$15.95  
The principles of motors and generators, three-phase systems and power converters. The final chapter covers servo control systems.

### ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

**A0013B** \$5.95  
Supplies the electronics hobbyist with the background knowledge which will exactly suit his specific requirements. Minimum maths.

### ELECTRONICS: IT'S EASY — VOL 1

**A0016E** \$12.95  
Meters, resistance, capacitance and inductance, emitter followers, op-amps, power supplies and electronic filters. Hardcover.

### ELECTRONICS: IT'S EASY — VOL 2

**A0017E** \$12.95  
Digital sub-systems, counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes. Hardcover.

## reference and data handbooks

### WALL CHART — HOW TO IDENTIFY UNMARKED ICs

**B0019B** \$2.95  
This chart shows the reader how, with just a test-meter, to go about recording the particular 'signature' of an unmarked IC which should enable the IC to be identified with reference to manufacturers or other data.

### WALL CHART — RADIO, ELECTRONICS, SEMI-CONDUCTORS AND LOGIC SYMBOLS

**B0020B** \$2.95  
Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks!

### WALL CHART — RADIO AND ELECTRONIC COLOUR CODES AND DATA

**B0021B** \$2.95  
This chart covers all colour codes in use throughout the world. For all radio and electronic components made in Britain, United States, Europe and Japan.



### FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

Normally \$4.95; this month only,

**\$3.70**

Full constructional data, circuits, components lists for many practical projects including audio distortion meter, guitar amp, metronome, etc. To order, quote book number CX035B.  
Limited supplies

### FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

**B0025B** \$5.95  
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Britain, Japan, United States, Europe and Hong Kong, and includes types produced by more than 120 different manufacturers.

### SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

**B0026B** \$6.25  
Interchangeability data covers semiconductors manufactured all over the world. Immediate equivalents are shown and possible substitutes are included.

### PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE

**B0027B** \$9.95  
For the practical person's workbench. Bridges the gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. High maths avoided where possible.

### HANDBOOK OF ICs EQUIVALENTS AND SUBSTITUTES

**B0281B** \$6.95  
Contains full interchangeability data on more than 9500 ICs with possible alternatives and equivalents shown. Covers many types of digital and linear ICs. Recently reprinted.

### INSTRUMENTATION: TRANSDUCERS, EXPERIMENTATION AND APPLICATIONS

**B0310P** \$19.95  
Presents a basic approach to instrumentation designed to show how measurement systems operate. Includes basic measurement and meter design, potentiometric, capacitive, inductive and resistive transducers.

### HANDBOOK OF ELECTRONIC TABLES AND FORMULAS

**B0320P** \$19.95  
Covers formulas and laws, constants and standards, symbols and codes, service and installation data, design data and mathematics. Fifth edition.

### WIND/SOLAR ENERGY

**B0324P** \$19.95  
Covers solar energy and photovoltaic converters, wind energy, batteries and inverters. Also includes practical solar power supplies with applications for radio communications and low-power electrical systems.

## electronics for beginners

### HI-FI LOUDSPEAKER ENCLOSURES

**C0028B** \$4.95  
Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

### HOW TO BUILD GOLD AND TREASURE DETECTORS

**C0033E** \$3.95  
Tells you how metal detectors work and how to construct the different types of detectors: discriminating, BFO, induction balance and a professional deep-seeking unit.

### RADIO CONTROL FOR BEGINNERS

**C0034B** \$5.95  
How complete systems work with constructional details of solid-state transmitters and receivers. Also included — antennas, field strength meter, crystal controlled superhet, electro-mechanical controls. Section dealing with licensing, etc, is not applicable to Australia.

### FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

**C0035B** \$4.95  
Full constructional data, circuits, components lists for many practical projects including audio distortion meter, guitar amp, metronome, etc. ▶

Save time and trouble with mail order — simply fill out the reply-paid coupon!

140 Joynton Avenue, Waterloo, NSW 2017, Australia. Phone (02) 663-9999 Sydney. Telex 74488.

Postal Address: ETI Book Sales, PO Box 227, Waterloo, NSW 2017.

### HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS

**C0036B** \$6.95  
Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

### BEGINNER'S HANDBOOK OF IC PROJECTS

**C0037P** \$19.25  
The novice is guided in mastering the fundamentals of building, troubleshooting and testing electronic projects. In addition to many elementary projects, more advanced ones are included concerning bipolar integrated circuits and medium and large-scale integrated circuits.

### ELECTRONIC GAMES

**C0040B** \$5.95  
How to build many interesting electronic games using modern ICs. Covers both simple and complex circuits for beginner and advanced builder alike.

### SOLID-STATE SHORTWAVE RECEIVERS FOR BEGINNERS

**C0044B** \$5.95  
Design and construction of several solid-state shortwave receivers giving high level of performance yet utilizing few components.

### SIMPLE PROJECTS — VOL 2

**C0256E** \$2.95  
Contains easy projects plus chapters on construction techniques and useful information on components.

### 15 SATURDAY ARVO PROJECTS

**C0268E** \$1.50  
Projects include transistor-assisted ignition, sound bender, radio microphone, simple sound effects, Alien Invaders, etc. etc.

### ETI PROJECT ELECTRONICS

**C0269E** \$4.95  
Twenty-six projects for beginners, including battery saver, electronic siren, Morse practice set, FM antenna, etc. etc. Fifth edition.

### BASIC ELECTRICITY AND AN INTRODUCTION TO ELECTRONICS

**C0311P** \$16.95  
Simply worded explanations of electrical symbols, basic electrical laws, direct current, cells and batteries, magnetism, alternating current, distribution, radiation, etc. with many diagrams and illustrations.

### HOW TO READ SCHEMATIC DIAGRAMS

**C0367P** \$10.95  
Covers the various types of electronic diagrams and explains resistors, capacitors, coils, transformers, electron tubes, semi-conductors, switches and relays. An invaluable aid for reading and interpreting the schematic.

## constructional projects

### ELECTRONIC PROJECTS FOR YOUNG SCIENTISTS

**D0045E** \$3.95  
PH meter, gelger counter, helium-neon laser, sound-level meter, solar cells, negative ion generator and more.

### REMOTE-CONTROL PROJECTS

**D0046B** \$6.95  
Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial use.

### ELECTRONIC HOUSEHOLD PROJECTS

**D0048B** \$5.95  
Most useful and popular projects for use around the home. Includes two-tone buzzer, intercom, smoke and gas detectors, baby alarm, freezer alarm, etc. etc.

### ELECTRONIC PROJECTS USING SOLAR CELLS

**D0049B** \$6.75  
Includes a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

### BUILD YOUR OWN HI-FI AND AUDIO ACCESSORIES

**D0052B** \$4.95  
Essential for keen hi-fi and audio enthusiasts. Projects include stereo decoder, three-channel mixer, FET preamp for ceramic pick-ups, mic preamp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, etc.

### 28 TESTED TRANSISTOR PROJECTS

**D0053B** \$4.50  
Some circuits are new, others are familiar designs. Projects can be split and/or combined.

THIS MONTH'S SPECIAL

### LEARNING TO WORK WITH INTEGRATED CIRCUITS

Normally \$2.35; this month only, \$1.75

Discover the basics of integrated circuits while building a simple and useful electronics project. A complete collection of the popular American OST series. To order, quote book number EX318R. Limited supplies.

### MODEL RAILWAY PROJECTS

**D0054B** \$6.75  
Projects include such things as controllers, signals and sound-effects units. Construction stripboard layouts provided for projects.

### CB PROJECTS

**D0055B** \$6.75  
A number of useful designs include a speech processor, interference filters and a simple CB radio receiver. Stripboard layouts, wiring diagrams and notes on construction are provided.

### HOW TO MAKE WALKIE-TALKIES

**D0056B** \$6.95  
This treatise on low-power transmitter-receivers (walkie-talkies) covers many aspects, from licensing requirements and bands, through practical circuitry and construction to the types of aerials that may be used.

### PROJECTS IN OPTO-ELECTRONICS

**D0057B** \$6.75  
Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and detectors, modulated light transmission and also photographic projects, etc.

### SINGLE IC PROJECTS

**D0058B** \$5.50  
Simple to build projects based on a single IC. A few projects use one or two transistors as well. A stripboard layout is given for each project plus special constructional and setting up info. Contents include low-level audio circuits, audio power amps, timers, op-amps and miscellaneous circuits.

### SECURITY SYSTEMS

**D0294P** \$14.95  
Step-by-step instructions show you how to carry out a security survey of your home and then plan, install and maintain an alarm system.

### EXPERIMENTER'S GUIDE TO SOLID-STATE ELECTRONICS PROJECTS

**D0323P** \$9.75  
A large collection of easy-to-follow electronics projects and tests, including experiments with solid-state devices such as solar cells, fibre optics, LEDs and linear and digital ICs. Projects include a transistor checker, a series regulated power supply and a solar cell battery for a portable radio.

### THE COMPLETE GUIDE TO SECURITY

**D0343P** \$19.95  
This comprehensive non-technical guide covers locks and alarm systems, security for the home, office, car and travel. Includes practical hints on telephone security, closed-circuit television, ultrasonic and photoelectric burglar alarms and rf bug detectors.

### BUILD YOUR OWN ELECTRONIC EXPERIMENTER'S LABORATORY USING ICs

**D0324P** \$2.75  
Projects include a simple audio frequency oscillator, a TTL pulse detector, a simple square wave generator and a high impedance voltmeter. Limited supplies.

### 52 PROJECTS USING IC741

**D0386B** \$3.95  
Projects include remote thermometer, servodriver, rev counter for petrol and diesel engines, voltage amplifier and a record amplifier with bass boost.

### 99 PRACTICAL ELECTRONIC PROJECTS

**D0392P** \$9.95  
Includes audio, automotive, musical instrumentation, photography, remote control and power supply projects.

### ELECTRONIC SCIENCE PROJECTS

**D0413B** \$5.95  
Twelve electronic projects with a scientific flavour — each project includes details on how it works, construction and use. Includes a simple infra-red laser, a low-cost solid-state oscilloscope, a pH meter, and electronic stethoscope and an electronic seismograph.

## circuit techniques and design

### DESIGN OF TRANSISTOR CIRCUITS, WITH EXPERIMENTS

**E0051P** \$22.75  
A self-teaching course in transistor circuits — seven chapters explore the fundamentals of active semi-conductors and their operating principles and procedures. Experiments in design and semiconductor testing provide hands-on experience.

### PRACTICAL TRANSFORMER DESIGN HANDBOOK

**E0075P** \$38.95  
An easy to understand, illustration-filled guide to designing and constructing transformers. Reviews the fundamentals of electricity, magnetism and algebra needed to understand transformer theory, and covers general design considerations, transformer types, power losses and transformer use in converters and inverters.

### ETI CIRCUIT TECHNIQUES — VOL 1

**E0076E** \$4.95  
The how, what, which, where, why and how much anthology of components, circuits and techniques. Second printing.

### ETI CIRCUIT TECHNIQUES — VOL 2

**E0077E** \$4.75  
See Volume 1.

### ETI CIRCUIT TECHNIQUES — VOL 3

**E0078E** \$4.95  
See Volume 1.

### TTL COOKBOOK

**E0083P** \$18.50  
A complete look at TTL logic circuits — what TTL is, how it works, and how to use it. Many kinds of practical TTL are included, such as digital counters, electronic stopwatches, digital voltmeters, etc.

### ACTIVE-FILTER COOKBOOK

**E0084P** \$24.25  
Learn to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

### UNDERSTANDING IC OPERATIONAL AMPLIFIERS

**E0085P** \$12.25  
Latest edition of this book covers theoretical and practical aspects of operational amplifiers and associated circuits. Includes material on BiFET and BiMOS and CMOS op-amps.

### IC TIMER COOKBOOK

**E0087P** \$26.95  
Gives you a look at the hundreds of ways IC timers are used in electronic instrumentation.

## CMOS COOKBOOK

**E0086P** \$21.00  
This book explains CMOS technology and its application to 'real world' circuitry. A mini-catalogue is included, which lists more than 100 devices, giving pinouts and application notes.

## IC OP-AMP COOKBOOK

**E0088P** \$25.75  
Basic op-amp theory in detail, with 200 practical, illustrated circuit applications: JFET and MOSFET units are featured, plus manufacturers' data sheets and company addresses.

## DESIGN OF OP-AMP CIRCUITS, WITH EXPERIMENTS

**E0089P** \$17.50  
The design of the fundamental circuits that are the basic building blocks of more sophisticated systems. A series of 35 experiments illustrates the design and operation of linear amps, differentiators and integrators, voltage and current converters, active filters, and lots more.

## 555 TIMER APPLICATIONS SOURCE BOOK, WITH EXPERIMENTS

**E0090P** \$11.25  
The construction of the 555 timer and numerous practical examples of its applications in all areas of electrical and computer engineering, including 17 simple experiments.

## PRACTICAL SOLID-STATE CIRCUIT DESIGN

**E0094P** \$14.95  
An introductory course in practical solid-state circuit design for the experimenter, designer or technician who is interested in constructing tailor-made circuits.

## SCRs AND RELATED THYRISTOR DEVICES

**E0095P** \$21.25  
Written for experimenters, technicians and engineers, this book is a practical and comprehensive guide to the theory, operation, specifications and applications of silicon-controlled rectifiers (SCRs) and related thyristor devices.

## REGULATED POWER SUPPLIES

**E0096P** \$29.75  
Comprehensive discussion of the internal architecture and operation of the latest solid-state regulators. Explains when regulated supplies are needed and how to incorporate them in your projects, and discusses modern circuitry including linear and switching circuits and late ICs.

## ANALOG INSTRUMENTATION FUNDAMENTALS

**E0097P** \$29.75  
Numerous practical, hands-on lab experiments and solved problems are included, plus discussions of movements, dc ammeters, voltmeters, ohmmeters, bridges, filters and attenuators. No calculus is required.

## SOLAR CELLS

**E0098P** \$37.95  
In-depth description of the basic operating principles and design of solar cells. It also covers the techniques used to produce solar cells and reviews applications.

## ELECTRONIC DESIGN WITH OFF-THE-SHELF ICs

**E0099P** \$14.70  
It contains virtually all the information you need to design and build electronic circuits, systems and subsystems with readily available ICs. Shows how to interface them into highly complex systems.

## MODERN FILTER DESIGN

**E0100P** \$49.95  
This book details the advances in active RC filters, both from a practical standpoint and from a state-of-the-art point of view. Gives detailed analysis and design procedures for switched capacitor filters.

## ELECTRONIC CIRCUITS

**E0288P** \$15.95  
Includes fundamentals of transistor theory, bias circuits, equivalent circuits, transistor data sheets, gain considerations in amplifiers, frequency characteristics of amplifiers, multistage and feedback amplifiers and FETs, with many examples and illustrations.

## MODERN CONTROL THEORY

**E0289P** \$15.95  
Includes fundamentals of matrix algebra, vectors and linear vector spaces, transformations, eigenvalues and eigenvectors, nonlinear equations and perturbation theory, with many examples and solved problems.

## DIGITAL ELECTRONICS

**E0292P** \$15.95  
Includes device theory, basic passive logic and basic active logic, advanced active logic gates, flip-flops and monostables and astables with many examples and illustrations.

## ED NOLL'S SOLID-STATE CIRCUIT FILES (TWO VOLUMES)

**E0315P** \$23.95  
Volume 1 of this two-volume set covers bipolar transistor, FET and linear IC circuits. Volume 2 covers TTL and CMOS circuits. Together, they provide a ready-made set of experiments for circuit study (\$23.95 for both volumes).

## LEARNING TO WORK WITH INTEGRATED CIRCUITS

**E0318R** \$2.35  
Discover the basics of Integrated circuits while building a simple and useful electronics project. A complete collection of the popular American QST series.

## UNDERSTANDING DIGITAL LOGIC CIRCUITS

**E0321P** \$28.35  
Written for the working technician, with many illustrations, this book explains logic principles, digital ICs, adders, counters, encoders, interfacing, TTL and CMOS devices, and much more.

## DIGITAL LOGIC CIRCUITS — TESTS AND ANALYSIS

**E0374P** \$25.95  
This working handbook covers the theory of digital logic circuits, starting with simple gates, illustrations of IC pinouts and an introduction to truth tables. Includes tests and analysis.

## test equipment and fault-finding

### USE OF THE OSCILLOSCOPE

**F0117P** \$27.95  
Programmed instruction course for use in a basic electrical engineering laboratory course. Author assumes basic knowledge of DC and AC circuits but none of oscilloscopes. This is an essentially practical course — thoroughly recommended.

### TEST GEAR — METERING AND POWER-SUPPLY PROJECTS

**F0118E** \$3.00  
Includes many types of meters, audio noise and signal generators, CMOS tester, oscilloscope calibrator, etc.

THIS MONTH'S SPECIAL

### THE 6809 COMPANION

Normally \$6.95; this month only,

**\$5.15**

A discussion of the features of the 6809 and a reference guide. Don't be deceived — it's more than just a beginner's guide to microprocessors. To order, quote book number JX154B.  
Limited supplies

### TEST GEAR — VOL 2

**F0119E** \$3.95  
Projects include audio oscillator, transistor tester, true RMS voltmeter, RF signal generator, versatile logic test probe, microwave oven leak detector, etc.

## AUTOMOTIVE TUNE-UP AND EMISSION-CONTROL SERVICE

**F0120P** \$22.75  
Car owners who wish to save money and maintain their cars at peak performance will learn how to adjust, repair and maintain the systems that ensure best operation.

## EFFECTIVELY USING THE OSCILLOSCOPE

**F0258P** \$16.95  
Describes the potential uses of the scope, ranging from audio and television tests and measurements to performance tests.

## electronic music and audio/video

### CHEAP VIDEO COOKBOOK

**G0123P** \$11.75  
Complete discussion of a new, low-cost way to get words, pictures and opcode out of your computer and onto any ordinary television screen, using a seven-IC easy-to-build circuit which you can build for \$20.

### AN INTRODUCTION TO VIDEO

**G0124B** \$6.95  
This book is written in layman's language and is for anyone who is thinking about buying or renting or who has just bought or rented a video recorder and wants to get the best out of the machine.

### ELECTRONIC SYNTHESIZER PROJECTS

**G0133B** \$5.95  
For the electronic music enthusiast, an invaluable reference. This book is full of circuits and information on how to build analogue delay lines, sequencers, VCOs, envelope shapers, etc. The author takes a clear and logical approach to the subject that should enable the average enthusiast to understand and build up what appears to be a quite complex instrument.

### AUDIO PROJECTS

**G0134B** \$6.95  
Covers a wide range of audio projects, including preamplifiers and mixers, power amplifiers, tone controls and matching, etc. Board layouts and wiring diagrams included.

### ELECTRONIC MUSIC PROJECTS

**G0135B** \$5.95  
Provides constructors with practical circuits for the less complex music equipment including fuzz box, waa-waa pedal, sustain unit, reverb and phaser, tremolo generator, etc. Text covers guitar effects, general effects, sound generators, accessories.

### ELECTRONIC MUSIC AND CREATIVE TAPE-RECORDING

**G0136B** \$6.95  
Shows how electronic music can be made at home with the simplest and most inexpensive of equipment. Describes how the sounds are generated and how these may be recorded to build up the final composition.

### PRACTICAL CONSTRUCTION OF PREAMPS, TONE CONTROLS, FILTERS, ATTENUATORS

**G0137B** \$5.25  
This book shows the enthusiast how to construct a variety of magnetic tape recording, microphone and disc preamplifiers, and also a number of tone control circuits, rumble and scratch filters, attenuators and pads.

### AUDIO IC OP-AMP APPLICATIONS

**G0138P** \$15.25  
This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

### AUDIO PROJECTS FROM ETI

**G0260E** \$5.00  
Projects include Series 4000 moving-coil cartridge preamplifier, general-purpose 150 W MOSFET power amp module, versatile public-address amplifier, etc. etc. ▶

### 30 AUDIO PROJECTS

**G0274E** \$3.95  
Projects include 25 W amp, general-purpose preamp, bucket brigade delay line, active crossover, tape noise limiter, etc., etc.

### THE COMPLETE GUIDE TO HIGH FIDELITY

**G0305P** \$23.75  
Includes explanations of digital recording, amplifiers, tuners, drive motors, preamplifiers, proximity effect and impedance matching. Thirty basic systems, for limited to unlimited budgets, are also discussed.

### SON OF CHEAP VIDEO

**G0345P** \$15.95  
Don Lancaster's sequel to *The Cheap Video Cookbook* (ETI Book Sales No. G0123P) Includes new and improved circuits to get alphanumeric and graphics video out of a microcomputer and on to an ordinary television.

### PRACTICAL TRANSISTORISED NOVELTIES FOR HI-FI ENTHUSIASTS

**G0382B** \$2.95  
Includes quadrophony, stereo headphone adaptor, phasing stereo loudspeaker systems, high impedance four-channel mixer and speaker gain control. Limited supplies.

### AUDIO ENTHUSIAST'S HANDBOOK

**G0383B** \$2.75  
Includes the record/playback curve, stylus compliance, acoustic feedback, stereo tape track standards, compensating sideways drag and amplifier power ratings.

### CHOOSING AND USING YOUR HI-FI

**G0385B** \$4.95  
Provides basic information on the technical specifications of hi-fi equipment. Offers advice on what to look for in equipment in order to obtain real high-fidelity sound and reproduction.

## computers for beginners

### PEANUT BUTTER AND JELLY GUIDE TO COMPUTERS

**H0150A** \$16.75  
A simple, easy-to-digest source of information on personal computing for the potential buyer who is less than an expert in the field.

### INTRODUCTION TO WORD-PROCESSING

**H0151A** \$17.95  
Written for the non-technical reader, this book tells about the concepts common to all word-processing systems, then analyses all features.

### FROM CHIPS TO SYSTEMS: AN INTRODUCTION TO MICROPROCESSORS

**H0152A** \$29.75  
Explains exactly what a microcomputer system is and how it works. Introduces fundamental concepts and covers all aspects of microprocessors and related components: internal operation, memories, interfacing and system development, etc.

### DON'T (OR, HOW TO CARE FOR YOUR COMPUTER)

**H0153A** \$19.95  
A guide to computer and peripheral preservation. Specific advice for the computer, floppy disks, hard disks, the CRT terminal, the printer, tape units, the computer room, software and documentation.

### KIDS AND THE APPLE

**H0300P** \$25.75  
How to write programs for the Apple computer, including action games, board games and word games.

### FOUNDATIONS OF COMPUTER TECHNOLOGY

**H0312P** \$29.95  
A thorough introduction to computer technology for business people, engineers, professionals, students and hobbyists. Assumes no prior knowledge of computers, electronics or mathematics.

## computer hardware and techniques

### COMPUTERS AND COMPUTING YEARBOOK '83

**J0014E** \$4.95  
Includes ZX81, Epson MX80 printer, System 80 joystick project, 660 software, ZX80 programs, etc., etc.

### Z80 MICROCOMPUTER DESIGN PROJECTS

**J0156P** \$20.75  
A complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

### DON LANCASTER'S MICRO COOKBOOK

**J0159P** \$20.75  
This 'cookbook' starts with the very fundamentals of microprocessors and microcomputers and takes you through number systems, codes, etc., till you can work intelligently with micros.

### THE S100 AND OTHER MICRO BUSES

**J0160P** \$13.25  
The key to successful computer expansion is a complete understanding of the bus system, through which the computer communicates with peripherals. This book will give you that understanding.

### USING THE 6800 MICROPROCESSOR

**J0163P** \$13.25  
Guides the reader through the conception, configuration, writing and running of a variety of programs that demonstrate practical use of a 6800 system.

### STD BUS INTERFACING

**J0164P** \$21.75  
Explains what the STD bus is, in easy-to-understand language.

THIS MONTH'S SPECIAL

### FIFTY BASIC EXERCISES

Normally \$17.95; this month only,

**\$13.25**

Designed to teach BASIC through actual practice, this book contains graduated exercises in maths, business, operations research, games and statistics. The programs were designed to run directly on a TRS-80 but will run on any system with MicroSoft BASIC. To order, quote book number KX188A.  
Limited supplies

### Z80 MICROCOMPUTER HANDBOOK

**J0171P** \$17.50  
This handbook covers hardware, software and microcomputers built around the Z80.

### PRACTICAL COMPUTER EXPERIMENTS

**J0172B** \$5.95  
How to build typical computer circuits using discrete logic. Useful intro to devices such as adders and storers as well as a general source book of logic circuits.

### PC DOS: USING THE IBM-PC OPERATING SYSTEM

**J0278J** \$22.95  
This self-paced guide teaches you how to become an accomplished user of all the major disk-operating system functions and utilities, no matter how much or how little computer experience you have.

### A Z80 WORKSHOP MANUAL

**J0283B** \$8.95  
Intended for those who want to progress beyond BASIC programming to topics such as machine-code and assembly language programming or who need hardware details of the Z80-based computer.

### EASY ADD-ON PROJECTS FOR SPECTRUM, ZX81 AND ACE

**J0285B** \$7.75  
The projects include a pulse detector, picture digitiser, five-key pad, model controller, bleeper, lamp flasher, light pen, etc., etc.

### MICROSOFT FORTRAN

**J0291A** \$24.95  
Various techniques involved in MicroSoft programming are explained, including structural programming and top down programming. Compiler, editor and linker are discussed, along with the various uses of the printer, disk and video terminal.

### TV TYPEWRITER COOKBOOK

**J0297P** \$14.50  
A complete guide to low-cost television display of alphanumeric and graphics data for microprocessor systems, computer hobbyists, television titling, word-processing and video games.

### THE ART OF PROGRAMMING THE ZX SPECTRUM

**J0395B** \$7.95  
For beginners and seasoned programmers. Covers low- and high-resolution graphics, sound, moving graphics, PEEK and POKE and advanced graphics.

## computing software

### INTRODUCTION TO THE UCSD P-SYSTEM

**K0106A** \$22.45  
Explains the UCSD Pascal operating system, or "p-system". You will learn how to enter a Pascal program in the computer, edit it, store it on a file and then manipulate files.

### INTRODUCTION TO PASCAL, INCLUDING UCSD PASCAL

**K0113A** \$26.95  
For both beginners and experienced programmers, this book covers all aspects of Pascal, from the basic concepts of program development. Extensive appendices. Second edition.

### AUSTRALIAN MICROCOMPUTER HANDBOOK

**K0175E** \$8.95  
A detailed buyer's guide to microcomputer systems and application packages in commercial, industrial, scientific, educational and home/hobby areas.

### PROGRAMMING IN BASIC FOR PERSONAL COMPUTERS

**K0186P** \$18.95  
Simple instructions show how to give BASIC commands and statements a wide range of applications, from programming video games to developing business or scientific programs.

### BASIC FOR EVERYONE

**K0187P** \$19.75  
Some 350 pages of BASIC information for all purposes.

### FIFTY BASIC EXERCISES

**K0188A** \$17.95  
Designed to teach BASIC through actual practice, this book contains graduated exercises in math, business, operations research, games and statistics. The programs were designed to run directly on a TRS-80 but will run on any system with MicroSoft BASIC.

### INSIDE BASIC GAMES

**K0189A** \$19.95  
The medium of games teaches readers how to design error-free, interactive BASIC programs. Rules, algorithms and coding differences for the PET, Apple II and TRS-80 are also included.

### THE PASCAL HANDBOOK

**K0200A** \$23.50  
Summarises the entire Pascal vocabulary, including the variations introduced by different commercial versions of Pascal. All in dictionary format.

All prices of publications in this catalogue listing are subject to change without notice.

# Upgrading the ETI-668 Microbee EPROM programmer

Soup up that EPROM programmer. Speed up those verifies and option-up the software. Here's all the good oil from the collected wisdom of a number of project builders/modifiers.

Geoff Nicholls & readers

THE ETI-668 HAS BEEN one of the most popular Microbee projects and has stimulated a number of readers to offer suggestions to improve its performance. Most of the submissions received deal with speeding up the *Read*, *Verify* and *Test* routines so that they no longer take the same time as the *Program* routine. This modification requires making minor hardware and software changes.

Firstly though, a number of readers have told me that the software as published in February '83 does not assemble from the source code. I must confess that this is my fault, not Tom Moffat's.

At the time the project was prepared, we at ETI had a 64K Microbee without the Editor-Assembler. When Tom sent up the listing nobody at ETI knew anything about the assembler and it was left to yours truly to get the program going. When I came across the message routines in the source code they had been written as ASCII string definitions and only the first byte of each line had been assembled and listed, so I coded the rest by hand and we inserted the machine code in the listing.

(Later I discovered that the assembler had been set up to avoid wasting paper by printing the assembled code for such strings unless a special switch is used.)

The long and the short of all this is that the lines between 2060 and 2130 of the listing in Feb. '83 should be changed to the following if you are assembling from source code;

```
2070 MSG  DEFM 'ETI 668/ MICROBEE'
2080      DEFM 'EPROM PROGRAMMERS'
2090      DEFM 'START ADDRESS?'
2100      DEFM 'FINISH ADDRESS?'
2110      DEFM 'COMMAND?'
2120 ERRM DEFM '*%/&@ ERROR!'
```

NOTE: Thanks to Ross Carter VK2SS for taking the trouble to write pointing this out.

## Microbee clock speeds

One point to note about software timing routines (as used for the 55 millisecond delay around line no. 1330) is that they are obviously dependent upon the clock speed of the processor executing them. Most of the early Microbees ran at 2 MHz and the published software was for this speed. The Plus series also run at 2 MHz, but the colour/IC series run at 3.375 MHz. Applied Technology state that all systems from June 1983 have the 3.375 MHz clock. (The ETI



Lab. Microbee seems to be something of a bastard since it runs at 3.000 MHz!)

If you use software timed to wait 55 ms on a 2 MHz machine, but your machine runs at 3.375 MHz, then the actual delay will only be about 33 ms, and incorrect operation will result. The solution is to increase the value loaded into the BC registers at line 1330 from 1000 to 2000. This is more than is strictly necessary so there is room to optimise the delay time.

## Programming problems

A few readers have found that in attempting to program EPROMs, the  $V_{pp}$  voltage folds back to a few volts due to the 30 mA current limiting.

Daniel Ford wrote suggesting that the problem arises from the instruction sequence on page 49 of the original article, specifically the way the power was switched on before the EPROM was inserted. ▶



```

01040 VRFY1 IN A,(0) ;get byte from eprom
01050 LD C,(HL) ;get byte from memory
01060 CP C ;are they the same?
01070 JR NZ,ERROR
01080 CALL SHODL
01090 JR VRFY1
01100
01110 ;Show an ERROR message.
01120
01130 ERROR LD HL,ERRM
01140 LD BC,0F299
01150 CALL MESS
01160 LD B,7
01170 CALL 800CH ;BEEP!
01171 CALL 8006H ;Get key.
01172 CP 1BH ;ESC key?
01173 JR Z,EXIT ;yes,return to EDASM
01174 CP 03 ;BREAK key?
01175 JR NZ,ERROR ;no,loop back.
01176 LD BC,400H
01177 POP HL ;clear RET off stack
01178 JP START ;restart
01179
01180 ;Exit from program to EDASM.
01181
01182 EXIT JP 0C000
01190
01200 ;Show HL and do time delay.
01210
01220 SHODL LD BC,0F224;screen location
01230 LD A,0A0H
01240 LD (BC),A ;show a white space
01250 INC BC
01260 INC HL ;to match eprom counter
01270 LD A,H
01280 CALL SHOW ;show H register
01290 LD A,L
01300 CALL SHOW ;show L register
01310 LD A,0A0H
01320 LD (BC),A ;show a white space
01380 PUSH HL
01385 SCF ;reset carry flag by setting it
01386 CCF ;then complementing it
01390 SBC HL,DE
01400 POP HL
01410 RET C ;finished?
01420 LD BC,21FH ;for partial screen clear
01430 POP HL ;get RET off stack
01440 JP START ;finished
01450
01460 ;Show "A" register as a hex value.
01470
01480 SHOW PUSH AF
01490 RRCA
01500 RRCA
01510 RRCA
01520 RRCA
01530 CALL $+4
01540 POP AF
01550 AND 00FH
01560 ADD A,0B0H
01570 CP 0BAH
01580 JR C,$+4
01590 ADD A,007H
01600 LD (BC),A
01610 INC BC
01620 RET
01630
01640 ;Enter an address,show it and put it in DE.
01650
01660 ADDR CALL $+4
01670 LD D,E
01680 CALL KEY
01690 RLCA
01700 RLCA
01710 RLCA
01720 RLCA
01730 LD E,A
01740 CALL KEY
01750 OR E
01760 LD E,A
01770 RET
01780
01781 ;Clear RET's off stack, restart program.
01782
01783 RST POP HL
01784 POP HL
01785 LD BC,400H
01786 JP START
01787 ;
01790 ;Get a key,convert to hex and show it.
01800
01810 KEY INC BC
01820 KEY1 CALL 8006 ;key input into A
01825 CP 1BH
01826 JR Z,EXIT
01827 CP 03
01828 JR Z,RST
01830 LD (BC),A
01840 SUB 30 ;convert ASCII to hex
01850 JR C,KEY1 ;if less than zero

```

```

01860 CP 00AH
01870 RET M ;if between 00-99
01880 SUB 007H
01890 CP 00AH
01900 JR C,KEY1 ;if less than 0AH
01910 CP 010H
01920 JR NC,KEY1 ;if more than 0FH
01930 RET
01940
01941 ;Delay 55mS subroutine
01942
01943 DELAY LD BC,02000H ;adjust BC to optimise
01944 DEC BC ;pulse length(see text)
01945 LD A,B
01946 OR C
01947 JR NZ,$-3
01948 RET
01949
01950 ;Initialize PIO and/or show a message.
01960
01970 INIT LD A,4FH ;set PIO for input
01980 OUT (001H),A
01985 DI ;disable interrupts
01990 MESS LD A,(HL)
02000 INC HL
02010 CP '$' ;"$"=MSG terminator
02020 RET Z
02030 LD (BC),A
02040 INC BC
02050 JR MESS
02060
02070 MSG DEFW 'ETI 668/MicroBee
02080 DEFW 'Eprom Programmer
02090 DEFW 'START ADDRESS?%'
02100 DEFW 'FINISH ADDRESS?%'
02110 DEFW 'COMMAND? $'
02120 ERRM DEFW '$%$% ERROR!%'
02130
02140 ;Command labels, reverse video.
02150
02160 PROGM DEFW 0D0A0 ;PROG%
02170 DEFW 0CFD2
02180 DEFW 24C7
02190 READM DEFW 0D2A0 ;READ%
02200 DEFW 0C1C5
02210 DEFW 24C4
02220 STEPM DEFW 0D3A0 ;STEP%
02230 DEFW 0C5D4
02240 DEFW 24D0
02250 TESTM DEFW 0D4A0 ;TEST%
02260 DEFW 0D3C5
02270 DEFW 24D4
02280 VRFYM DEFW 0D6A0 ;VRFY%
02290 DEFW 0C6D2
02300 DEFW 24D9
02310
02320 END

```

#### HEX DUMP

Addr	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0E00:	01	00	04	21	00	F0	36	20	23	0B	78	B1	20	F8	21	53
0E10:	0F	01	8D	F0	CD	4A	0F	01	15	F1	CD	4A	0F	CD	03	0F
0E20:	D5	01	95	F1	CD	4A	0F	CD	03	0F	01	15	F2	CD	4A	0F
0E30:	CD	06	80	FE	10	28	1D	FE	12	28	2D	FE	13	28	38	FE
0E40:	18	28	42	FE	16	28	50	FE	03	20	E5	FE	18	28	7A	01
0E50:	1F	02	18	AF	21	AC	0F	3E	0F	CD	47	0F	E1	7E	D3	00
0E60:	CD	3C	0F	CD	CC	0E	18	F5	21	B2	0F	CD	45	0F	E1	DB
0E70:	00	77	CD	CC	0E	18	F8	21	B8	0F	CD	45	0F	E1	DB	00
0E80:	CD	CC	0E	18	F9	21	BE	0F	CD	45	0F	E1	DB	00	FE	FF
0E90:	20	17	CD	CC	0E	18	F5	21	C4	0F	CD	45	0F	E1	DB	00
0EA0:	4E	B9	20	05	CD	CC	0E	18	F5	21	9F	0F	01	99	F2	CD
0EB0:	4A	0F	06	07	CD	0C	80	CD	06	80	FE	1B	28	0B	FE	03
0EC0:	20	E7	01	00	04	E1	C3	03	0E	C3	00	C0	01	24	F2	3E
0ED0:	A0	02	03	23	7C	CD	ED	0E	7D	CD	ED	0E	3E	A0	02	E5
0EE0:	37	3F	ED	52	E1	D8	01	1F	02	E1	C3	03	0E	F5	0F	0F
0EF0:	0F	0F	CD	F6	0E	F1	E6	0F	C6	B0	FE	BA	38	02	C6	07

Addr	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0F00:	02	03	C9	CD	07	0F	53	CD	1D	0F	07	07	07	07	5F	CD
0F10:	1D	0F	B3	5F	C9	E1	E1	01	00	04	C3	03	0E	03	CD	06
0F20:	80	FE	1B	28	A4	FE	03	28	EC	02	D6	30	38	F0	FE	0A
0F30:	F8	D6	07	FE	0A	38	E7	FE	10	30	E3	C9	01	00	20	0B
0F40:	78	B1	20	FB	C9	3E	4F	D3	01	F3	7E	23	FE	24	C8	02
0F50:	03	18	F7	45	54	49	20	36	36	38	2F	4D	69	63	72	6F
0F60:	42	65	65	20	45	70	72	6F	6D	20	50	72	6F	67	72	61
0F70:	6D	6D	65	72	24	53	54	41	52	54	20	41	44	44	52	43
0F80:	53	53	3F	24	46	49	4E	49	53	48	20	41	44	44	52	45
0F90:	53	53	3F	24	43	4F	4D	4D	41	4E	44	3F	20	20	24	23
0FA0:	25	5C	26	40	20	45	52	52	4F	52	21	24	A0	D0	D2	CF
0FB0:	C7	24	A0	D2	C5	C1	C4	24	A0	D3	D4	C5	D0	24	A0	D4
0FC0:	C5	D3	D4	24	A0	D6	D2	C6	D9	24						

# THE VIC-20 COLUMN

## ★ ENCOURAGEMENT ★

Ozi-Soft, in conjunction with Computer Technics, is offering to donate a VIC-20 expansion board for the best software item submitted to this column every month.


The board is Australian-designed and manufactured and simply plugs into the VIC-20's expansion slot. It features three sockets that can be independently switch-selected, plus an on-board reset switch. With it you can plug in up to three separate expansion units to your VIC-20 and avoid the hass-

le of plugging things in and out and turning the computer on and off each time.

It is distributed by Computer Technics, 123 Clarence Street, Sydney (G.P.O. Box 4936) NSW 2000. (02)29-7244. The board costs \$59.95.

All submissions must be accompanied by a signed letter from you stating that it's your original work. The winning submission will be judged by the Editor and no correspondence will be entered into. All published submissions will be paid for.

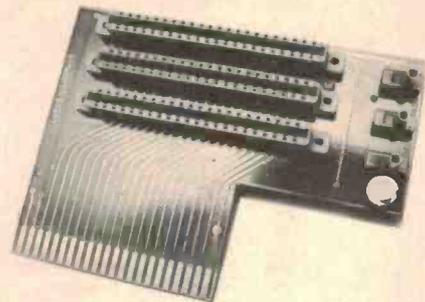Send entries to: The Editor, VIC-20 Column, ETI Magazine, P.O. Box 227, Waterloo NSW 2017.



Peter Terren of Yokine WA is the January winner of the VIC-20 expansion board. The program he wrote to control radio-controlled model servos is multi-functional. It could also be used to control robot arms, mechanical latches/locks, plotting devices etc. As you can see, the results are good and the number of applications are limited only by your imagination.

## CONTROL MODEL SERVOS

Peter Terren, Yokine WA

This program allows the VIC to easily control radio-controlled model servos; these are readily available matchbox-sized devices with a mechanical output shaft rotating through approximately 180° in response to a positive electrical pulse of 1-2 ms duration, with pulse lengths proportional to the angle of rotation.

These servos run off four NiCads of typically 5 V, with a current drain of 20-50 mA with no load and up to 150 mA to 1 A stall current. For many simple applications this is quite within the capacity of the VIC's power supply and does not seem to cause interference to either the power supply or the servos.

These servos are available for \$30 upwards new but many radio-control modellers with model cars, planes, boats etc, will have a few lying around.

Applications could include anything requiring electrical to mechanical conversion in a controllable fashion e.g: robot arms, 'turtles', running radio-controlled models directly via computer, mechanical latches/locks or plotting devices.

I have used three servos to control a simple plotter with a resolution of 170 x 170 using the servos to control the X co-ordinate, Y co-ordinate and pen lift. See the accompanying results.

The program allows independent control of six servos, however, I suggest that you run no more than three servos off the VIC; any more would require an external power supply.

Output to the servos is directly via the user port, pins PB0-PB5. The program sets up a machine code routine to output pulses on the user port. Each pulse width is determined by the contents of locations 7664-7669 respectively for servos 1-6.

To operate the program one pokes values between 1-170 into each location required and executes the machine code routine SYS7408. This SYS may need to be repeated up to 200 times maximum (approx. one second) for mechanical equilibrium e.g: to get servo one to midposition and servo two to full clockwise (0°).



```
100 POKE 7664, 85: POKE 7665, 1
101 FOR T= 1 TO 100: SYS7408: NEXT
```

Using the simple example shown in the listing one can input any value and see the result. Note:

1. This program runs on the unexpanded VIC only.
2. When connecting the servos, there are three wires; +5 V, pulse, 0 V. The polarity of the wires can be determined from the manual, measured in use with a radio-controlled setup or tested for continuity of +5 V, 0 V with battery leads. Or the same colour code as the battery leads can be used.
3. There is approximately 1.5K of program space left for BASIC to develop this program in an application.
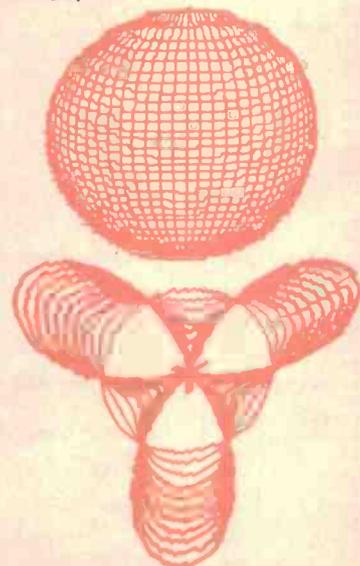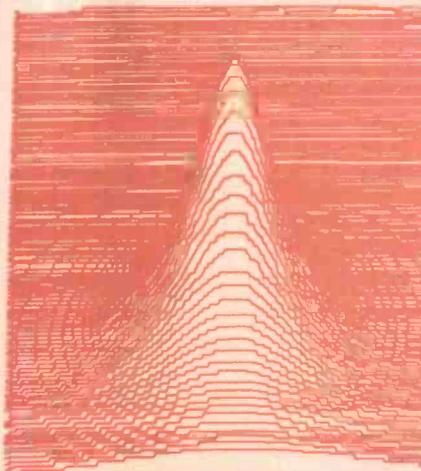
## CONTROL MODEL SERVOS

```
1 PRINT "SERVO CONTROLLER [C] P TERREN 1983 FOR UNEXP. VIC"
2 PRINT "SERVO 1 IS CONNECTED TO PB0 AND IS RUN BY "
3 PRINT "POKING MEM LOCATION 7665 WITH A NUMBER BETWEEN 1 - 170"
4 PRINT "THEN: SYS7408. THIS MAY NEED TO BE REPEATED UP TO 200 TIMES IN A"
5 PRINT "LOOP BEFORE MECHANICALEQUILIBRIUM OCCURS"
6 PRINT "PRINT SIMILARLY FOR SERVOS 2 TO 6 WITH PB1 TO 5"
8 PRINT "AND LOCATIONS 7666 TO 7670"
12 REM PROTECT MEMORY
13 POKE 51, 239: POKE 52, 28: POKE 55, 239: POKE 56, 28
17 S1=7665: S2=7666: S3=7667: S4=7668: S5=7669: S6=7670: POKE 7671, 80
18 REM MACHINE CODE *
19 FOR X=0 TO 240: READ A: POKE 7408+X, A: NEXT
20 DATA 169, 63, 141, 18, 145, 169, 0, 120, 168, 169, 63, 45, 16, 145, 141, 248
22 DATA 29, 169, 1, 13, 248, 29, 141, 16, 145, 162, 0, 232, 236, 247, 29, 208, 250, 200
24 DATA 204, 241, 29, 208, 250, 169, 0, 13, 248, 29, 141, 16, 145, 169, 0, 168, 76
26 DATA 39, 29, 234, 234, 169, 2, 13, 248, 29, 141, 16, 145, 162, 0, 232, 236, 247, 29
28 DATA 203, 250, 200, 204, 242, 29, 208, 250, 169, 0, 13, 248, 29, 141, 16, 145, 169
30 DATA 0, 168, 76, 77, 29, 234, 234, 169, 4, 13, 248, 29, 141, 16, 145, 162, 0
32 DATA 232, 236, 247, 29, 208, 250, 200, 204, 243, 29, 208, 250, 169, 0, 13, 248, 29
34 DATA 141, 16, 145, 169
36 DATA 0, 168, 76, 115, 29, 234, 234, 169, 8, 13, 248, 29, 141, 16, 145, 162, 0
38 DATA 232, 236, 247, 29, 208, 250, 200, 204, 244, 29, 208, 250, 169, 0, 13, 248, 29
40 DATA 141, 16, 145, 169
42 DATA 0, 168, 76, 153, 29, 234, 234, 169, 16, 13, 248, 29, 141, 16, 145, 162, 0
44 DATA 232, 236, 247, 29, 208, 250, 200, 204, 245, 29, 208, 250, 169, 0, 13, 248, 29
46 DATA 141, 16, 145, 169, 0, 168, 76, 191, 29, 234
48 DATA 234, 169, 32, 13, 248, 29, 141, 16, 145, 162, 0
49 DATA 232, 236, 247, 29, 208, 250, 200, 204, 246, 29, 208, 250, 169, 0, 13, 248, 29
50 DATA 141, 16, 145, 88, 96, 0, 255, 255
100 REM *****
101 REM EXAMPLE *****
105 PRINT "PRINT ENTER SERVO POSITION (1 TO 170) (ALL SERVOS)"
107 INPUT: IF B<1 OR B>170 THEN 107
108 REM REPEAT SYS UNTIL KEY PRESSED **
120 POKE S1, B: POKE S2, B: POKE S3, B: POKE S4, B: POKE S5, B: POKE S6, B
125 SYS 7408: GET A$: IF A$="" THEN 125
130 GOTO 107
READY.
```



# K-NAR JANUARY SPECIALS

Start your own system with an SD Systems MPB-100, Z-80 CPU card (4MHz, 2K Eprom, front panel i/face).  
**\$125**  
Unbelievable value.

2708/16K Eprom cards-switch selectable for 8K, full address decodable.  
**\$40**  
Unbeatable value.

Turn your Olympia ES-100 typewriter into WP printer and full duplex terminal.  
**\$180**  
Never before value

Steal of the year! 5 1/4" disk drives. Secondhand, in full working order.  
**\$220**  
(5 only). Full cost

**OTHER S-100 CARDS AVAILABLE AT OUR NORMAL KEEN DISCOUNTS ...**

GDC-512 High-RES Graphics Card. Unbeatable value and features  
**\$450**

CMC-10 Color Graphics Palette Card  
**\$450**

SBC-800 Single Board Computer  
**\$415**

FDC-II Enhanced Floppy Disk Controller  
**\$389**

CRC-64 64K CMOS RAM card  
**\$593**

DRC-II 64K Dynamic Ram card  
**\$593**

MPU-100 10-slot bench-mount card cage  
**\$450**

(with boards)  
**\$3600**

DDU-8 Twin 8" drive unit (2MB)  
**\$1660**

MPC-6 Multi-channel I/O card  
**\$450**

ADC-32 32 channel A/D card  
**\$337**

All boards assembled and tested and backed with 90-day guarantee.

All unbeatable value from

# K-NAR COMPUTER CARDS

PO Box 412, Dandenong 3175. Phone (03) 795 5858.  
Authorised distributor of SME Systems products.

\*Limited time offer only.  
For retail prices add 20% tax.

# IMPORT BARGAINS

2114 RAM (ANY QTY.)	\$1.29
4116 RAM (ANY QTY.)	\$1.29
6166 RAM (ANY QTY.)	\$4.88
4864 RAM (ANY QTY.)	\$5.88
2716 RAM (ANY QTY.)	\$3.65
2732/2532 EPROM	\$3.99
2764/2564 EPROM	\$8.99

### IC SOCKETS

8 PIN QUALITY TEXAS	0.09
14 PIN INSTRUMENTS BRAND	0.12
16 PIN INSTRUMENTS BRAND	0.15
18/20/22 PIN INSTRUMENTS BRAND	0.18
24/28 PIN INSTRUMENTS BRAND	0.20
40 PIN INSTRUMENTS BRAND	0.33

### CONNECTORS

DB 255	\$2.40
DB 25P	\$2.20
CENTRONIC'S 36W MALE	\$9.99
CENTRONIC'S 36W FEMALE	\$9.99

CHECK OUR PRICE ON OTHER CONNECTORS, CABLES & TOOLS.  
WELLER SOLDERING STATIONS

\$66.50

### DISKETTES

Verbatim 5 1/4 D/D	\$27.90 (10)
Verbatim 8" D/D	\$37.80 (10)

### DISK DRIVES

MPI B51	\$199.00
MPI B502	\$289.00
MITSUBISHI 4853	\$359.00
MITSUBISHI 4854	\$369.50

NB: ALL PRICES ABOVE EXCL. TAX.  
ALL GOODS FREIGHT FREE IN AUSTRALIA.

### COMPUTER BARGAINS

#### COMMODORE VIC-20

DATASET & FREE GAMES

WITH JOYSTICK

\$318.00 (incl.)

COMMODORE '64, Dataset

Joystick and free games

\$468.00 (incl.)

ATARI 400 Package deal

\$298.00 (incl.)

### MONITORS

Hi-RES GREEN \$199.00

Hi-RES COLOUR (RGB) \$489.00

### PRINTERS

EPSON RX80 \$539.00 (incl.)

FAX (A MUST) 80 \$429.00 (incl.)

TEC 40 CPS DAISEY \$1695.00 (incl.)

PHONE FOR GREAT PRICE ON OTHERS.

### APPLE COMPATIBLE

SLIMLINE DISK DRIVES \$359.00 (incl.)

CARDS — MOST UNDER \$100.00

PHONE FOR YOUR DEAL.

OSBORNE 100 COL. D/DENSITY COMPLETE

NEW BOXES incl. ALL S/WARE \$1795.00

(incl.)

NO FREIGHT CHARGES

# DATA PARTS

SHEPARTON, 11 EDWARD STREET,

PH: (058) 21-7155

(MAIL ORDER CENTRE)

Also at

BENDIGO (054) 43-4866

27 BATH LANE.

ALBURY (060) 21-8080

458 DEAN STREET.

Straight from the

# Source

No. 1 in a series

With Software Source's programme "Punctuation and Style" there's only a slim chance you'll be transformed overnight into the new Charles Dickens or, God help you, the new Harold Robbins. However the programme will - in seconds - make your letters, documents and even your novels clearer and more concise. A second programme called "The WordPlus" will actually scan your texts and pick up any spelling mistakes. Available from most computer software outlets, the Software Source programmes are on floppy discs and need to be linked to a word processor.

As the title indicates, "Punctuation and Style" can be used to find punctuation errors in your copy. Of course, the programme won't actually modify your text. "Punctuation and Style" picks up errors and makes suggestions about how they could be corrected.

If, for instance, you typed: "The contract what which I wrote ...", the programme would swiftly and politely say that you'd just indulged in some sloppy English grammar. It would then suggest an alternative. The key to "Punctuation and Style" is its inbuilt phrase dictionary which contains about 500 most commonly misused phrases.

The phrase dictionary can also be modified by its user - eg, lawyers can make up a specific legal dictionary which can be programmed to find messy phrases.

"The WordPlus" programme has a 45,000 word dictionary.


It not only signals when it sights spelling mistakes, it can also count the number of words in a text. Other "pluses" involve a readout of the frequency of word usage... perhaps you're littering your copy with too many "buts" or "howevers". You can even use the programme (psst! don't breathe a word of this) to cheat at crossword puzzles. "Punctuation and Style" sells for \$239 retail, including tax. "The WordPlus" sells for \$249 retail, including tax.

**Software Source Pty Ltd.**  
PO. Box 364, Edgecliff, NSW 2027. Phone (02) 389 6388.  
Please send me full details of your WordPlus and Punctuation and Style systems.

Name \_\_\_\_\_ Company \_\_\_\_\_ Address \_\_\_\_\_ ETI

AHEARN SS5

ETI January 1984 — 73

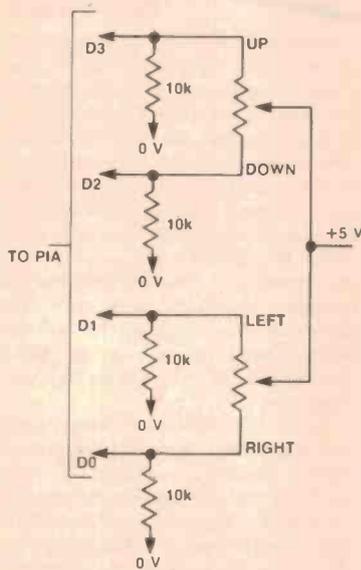

## JOYSTICK MODIFICATION

Tony Southern, Titahi Bay NZ

If you find multi-fingered games difficult to play, you can modify the '660 so that you can use a joystick to get the feel of a real arcade game.

If you connect the user PIA to the unused socket adjacent to the 6821, you can connect the joystick to the '660 via a ribbon cable and plug. All eight data lines, CB1, CB2, the stable input Z, the outputs 1, 7 and 4 and both rails can terminate neatly on the socket.

The routine to initialise the PIA is machine code at 0F00 and the Chip 8 routine and machine code to read it is at 0F18. To modify most Chip 8 programs to use the joystick try the following suggestions. Note that register 0 is modified by these routines.

1. Place a 1F20 instruction at address 0600 and replace the original instruction at address 0F22.

2. Locate the key pressed routine in the program you wish to modify and at the first location place a 1F26 instruction. Make the remaining instructions test register 0 for 01 — left, 02 — right, 04 — down and 08 — up. Fill any spaces with 00FFs.

3. At address 0F34 put the value of the I pointer before the key test routine (the PIA routine changes it) and at 0F36 put the address of the first direction test instruction you inserted into the program.

You will have just created two patches to initialise and then to read the PIA.

0F00 93BF F883 AFEF F800 5F62 2F2F 5F62 F820  
0F10 5F62 D400 0000 0000 93BF F886 AFEF 6AD4  
0F20 0F00 ZZZZ 1602 0F18 AF86 F065 8006 8006  
0F30 8006 8006 AYYY 1XXX

Note that 0F80-0F87 are used as access addresses by this routine.

**SPACE INVADERS MKIV.** These are the required changes to the Space Invaders MKIII program which was published in ETI, November 1982.

0600 1F20  
0624 1F26 4001 74FF 4002 7401 4004  
0630 6600 00FF 00FF  
0F22 A68C  
0F34 A688 1626

Move the joystick down to fire the missile.

## BLOCK EXTERMINATION

W. F. Kreykes, St Albans Vic.

To gain the highest score you must exterminate all blocks before the fuel is depleted. You can only fire at the blocks when the colour of your ship is the same as the colour of the block above or below.

The score starts at 50 000 and is added to when the blocks explode. When a block is hit which is not the same colour as the ship, the score is deducted according to the scale: black 0; red 100; blue 200; violet 300; green 400; yellow 500; light blue 600; white 700.

For a bonus you get up to six boxes in the top clone worth ten times their current value. But a pitfall is that you can lose up to six boxes in the bottom clone with ten times their current value deducted from your score.

If you fire and fail to exterminate a box, fuel is wasted and the box changes colour to red or black. The more a ship is moved the more fuel is used; when a block is exterminated some fuel is saved.

A new game starts if all the blocks are exterminated before the fuel is depleted. Another set of blocks will appear, your score is doubled, the background colour changes to red and the blocks are worth double what they were in the first round. However, you will have less time than in the first round.

Game A (black background) ends when the fuel is depleted. Press any key to restart. When game B (red background) ends you will hear a continuous sound; press RESET "8" to start game A again.

The controls are: 1 fire up; 9 fire down; B move left; D move right.

The following variables are used:

V0-V5 Various, add and deduct, score display.  
V6 Fuel line, amount presently left.  
V7 Timing of fuel consumed.  
V8 Various, value of box to add to score.  
V9 Number of boxes exterminated.  
VA Memory advance box dealing with,  
VB Explosion display co-ordinate.  
VC-VD Ship display co-ordinate.  
VE Detects up/down, top/bottom.  
VF Detection, timing, sound effects.

0600-069A sets up the start of the game to play game 'A'. Note that the section from 0604 to 062A physically changes instructions that are underlined in the program.

069C-06AA develops and saves bonus and dud boxes, then saves them in a stack starting at 0C88; V0-V2 = bonus, V3-V5 = duds. No provision has been made to prevent the same number being developed more than once, thus you may not always have six boxes of each.

06BC-06FE runs the main program; this calls subroutines as required. The 4300 @ 06CC detects move left or right, this stops the ship flashing in a stationary position.

When a fire button is pressed VE = 1 for up and 9 for down; this is used by other segments of the program to detect up/down top/bottom clone. The 8875 @ 06F6 checks to see if V7 is over 80/A0 and if so VF will be equal to 0 and thus the 27D6 will reduce the fuel line and change the colour of the ship.

070C-072A prints the scores. The 4420 @ 0720 makes the 1000s space in the score. This is included so that the same routine can be used to print the bonus and dud amount but not the space as V4 will only be equal to 20 when printing the score (when V4 starts @ 14).

073A-0780 adds and deducts the score stored in decimal @ OCD8 which is set to 0500 at the start of each game. The last two zeros are placed there at the start of the game and do not change. This gives the effect of x 100. This special routine had to be made because Chip-8 cannot add over 255 and will now show a true negative score. The routine has been designed to have an upper limit of 9999 but can add over this limit.

0782-0796 notice how it is possible to add a variable to itself, i.e. 8884!

07D6-0870E this routine performs three functions; it reduces the fuel line, then changes the ship's colour, then checks to see if all the fuel is depleted. As at this stage V0 is not in use, the AD20 F165 takes the present ship's colour out of memory and it is V1. This saves memory as the alternative would be AD21 F065 8100. V0 is then developed and compared with V1; if they are the same V0 is re-developed by the 9010.

By the way, check out this routine when V6 is equal to 40. This is the restart, but what I mean is the fact that in this case the subroutine originally called at 06FA returns to itself, thus cancelling out the requirement of ending in 00EE!

0810-0850 is the heart of the program and is several subroutines in one (if you follow through the program). When called @ 06FC develops VA to a random value between 0 and 67 @ 0818. It then checks with the video refresh memory to see if this box is still alive and if so develops a new colour with V0, converts VA to V1 and V2 and then changes the box to the new colour. The A488 3E01 A540 is required as VA memory advance cannot hold a value over FF.

0852-0876 fires the shells and detects a hit or a miss. The value of VE determines whether to fire up or down.

0878-08D8 is several subroutines in one. Its job is to convert after a hit VC & VD to VB & VA and compare the colour of the box with the ship. If they are not the same colour it deducts the points from the score, changes the colour of the box to red or black, adds to the fuel loss (7708), then replaces the shells and returns to the main program. The 9800 @ 08BA detects a match.

08DA-093E does all the fancy work when you've got a match. The explosion is displayed in seven segments; in between these it produces the sound effects, changes the box colour, checks for bonus or dud, adds the value of V8 to the score and changes the box colour to yellow in the end to give a moving effect.

Note that the 8884 @ 0924 is set to 00FF for game 'A' at 060C. It also checks the number of boxes struck.

0940-0978 changes the instructions to work game 'B', doubles the score, changes the background colour to red then restarts the game. The value of V0 @ 095C sets the amount of fuel for each colour change; this value can be altered.

09CC-09FA is a machine code subroutine that colours a block as shown in the April 1982 issue. I have changed the address at 09CD and 09D0 to 0AA8; this is where V0, V1 and V2 are stored for colouring a block.

It must be understood that for this program to check and compare colours the stack address @ 09E5 (0C) & 09EA (80) making 0C80 must not be altered. The position of each colour block on the screen is directly related to a location in this stack.

## BLOCK EXTERMINATION

600	09B9	680	3C40	700	6001	780	00EE	800	3640	880	7CFE	900	91A0	980	7700
	09BC	BLK.	167C	BOT. CLONE	A82B	8080	8080	00EE	00EE	6A00	6A00	17AA	17AA	CHECK IF BONUS BLOCK	7777
	6000	COL INT.	7D17		F055	6100	6100	60FF	60FF	83B0	83B0	92A0	92A0	IF 3RD.	7700
	2702	SKP	3D2F		A7ED	6200	6200	F600	F600	4304	4304	17AA	17AA		7777
	61FF	BLK	167A		F055	6300	6300	F018	F018	1894	1894	A99B	A99B		7700
	A924	8884 OFF	6E00		00EE	2712	2712	F00A	F00A	4300	4300	DBD5	DBD5		2050
	F155	00FF	6400		ACD8	8884	8884	00EE	00EE	1894	1894	600A	600A	GREEN	2020
	A6F5		2818		F365	8480	8480	1604	1604	7A01	7A01	282E	282E	4th.	0000
	60A0	TIMING	7401		6414	8884	8884	CE01	CE01	73F8	73F8	A9A0	A9A0		2020
	F055	80/AO	3400		652A	8884	8884	4E00	4E00	1886	1886	DBD5	DBD5		F800
	A6FD	50% CHANGE	168E		F029	8844	8844	00EE	00EE	83D0	83D0	3E09	3E09		00F8
	6010	BOX COL.	7E01		2726	6100	6100	CE01	CE01	3E01	3E01	1924	1924		2070
	F055	WRONG HIT RED.	3E02		F129	2846	2846	CA67	CA67	73EC	73EC	93A0	93A0		D870
	A8C5		168E		2726	7201	7201	A488	A488	4307	4307	17B8	17B8		20A8
	6001		AC88		F229	284A	284A	3E01	3E01	7A20	7A20	94A0	94A0		70D8
	F055		CO67		2726	284A	284A	A540	A540	430B	430B	17B8	17B8		70A8
620	A80D	6A0	C167	720	4420	7A0	7101	820	FA1E	8A0	7A40	920	95A0	9A0	8850
	60E0	RESTART	C267		7401	7A0	72FE	FA06	F065	430F	430F	17B8	17B8	CHECK IF 4TH EXPLOSION	D850
	F055	HIT 128 BLOCKS TO GAME	C367		F329	3108	3108	4000	4000	7A60	7A60	8884	8884	DOUBLE 8" ADD.	8800
	A943	STARTING BALANCE \$0.000	C467		D455	179A	179A	00EE	00EE	4E01	4E01	2752	2752	5th.	5000
	6044		C567		7404	00EE	00EE	C007	C007	7DFD	7DFD	AC80	AC80	6th.	7070
	F055		F555		00EE	6401	6401	4000	4000	AC80	AC80	3E01	3E01	7th.	7000
	6000		6C1E		A9AE	2782	2782	6007	6007	AD50	AD50	AD50	AD50	8th.	FFFF
	6105		6900		6C01	F800	F800	610F	610F	PA1E	PA1E	PA1E	PA1E	9th.	FOFO
	6200		6601		DCD2	6401	6401	81A2	81A2	F065	F065	7901	7901	10th.	FOFO
	6300		FC00		7C08	2712	2712	82A2	82A2	8800	8800	6005	6005	11th.	FOFO
	277C		FC18		3C41	1908	1908	4220	4220	AD20	AD20	282E	282E	12th.	FOE9
	6215		6700		1730	6431	6431	6202	6202	F065	F065	A989	A989	13th.	61E9
	6004		A991		00EE	2782	2782	4240	4240	9800	9800	DBD4	DBD4	14th.	61D4
	2798		18D4		ACD8	6F60	6F60	6204	6204	18DA	18DA	3980	3980	15th.	F839
	6102		A991		F365	FF00	FF00	4260	4260	270C	270C	18D2	18D2	16th.	AF96
	6005		6300		4000									17th.	
640	279A	6C0	680B	740	1748	7C0	27CA	840	6206	8C0	2762	940	F918	9C0	BFEF
	6002	BLUE DUD	E8A1		710A	6431	6431	3E01	3E01	270C	270C	1944	1944	18th.	F82C
	6106		63FE		70FF	2712	2712	720C	720C	6001	6001	2700	2700	19th.	5F62
	279A		680D		173E	2762	2762	284A	284A	282E	282E	ABC5	ABC5	20th.	2FF8
	6005		E8A1		4200	1928	1928	7201	7201	7708	7708	6000	6000	21th.	205F
	6212		6302		00EE	F518	F518	AAA8	AAA8	6F10	6F10	F055	F055	22th.	62D4
	2798		4300		730A	F515	F515	F255	F255	6050	6050	6088	6088	23th.	F80A
	6208		16E6		72FF	F507	F507	09CC	09CC	P000	P000	6184	6184	24th.	EEF8
	2798		7701		1748	3500	3500	00EE	00EE	PF18	PF18	A924	A924	25th.	AAAE
	6209		6002		273A	17CE	17CE	A98C	A98C	A98C	A98C	F155	F155	26th.	EE72
	2798		F000		8410	00EE	00EE	DCD6	DCD6	6D11	6D11	A6FD	A6FD	27th.	FA07
	6D13		F018		8384	60B0	60B0	6805	6805	16P2	16P2	F055	F055	28th.	5E1E
	272C		DCD6		ACCD	F000	F000	F800	F800	16P2	16P2	F055	F055	29th.	FOFA
	A9AD		8C34		F333	6328	6328	F818	F818	A989	A989	A6F5	A6F5	30th.	1FFE
	6D27		4CFE		F065	FD18	FD18	3E01	3E01	DBD4	DBD4	6080	6080	31th.	
	272E		7C02		8404	A9EA	A9EA	6D15	6D15	6003	6003	F055	F055	32th.	
660	6C12	6E0	4C3E	760	1774	7E0	D631	860	A990	8E0	F000	960	A943	9E0	FEFE
	6D29		7CFE		273A	7601	7601	7DFP	7DFP	F018	F018	6040	6040	33th.	FE5E
	A9B0		DCD6		8410	6700	6700	3E01	3E01	7001	7001	F055	F055	34th.	F80C
	DCD7		6E01		8385	AD20	AD20	7D02	7D02	3015	3015	A80D	A80D	35th.	7C00
	7C04		EEA1		3F00	F165	F165	DCD2	DCD2	18E0	18E0	6000	6000	36th.	BDF8
	3C2E		1852		1770	C007	C007	4F01	4F01	77FF	77FF	F055	F055	37th.	80F4
	1666		6E09		74FF	4000	4000	1878	1878	F018	F018	00E0	00E0	38th.	AF9D
	270C		EEA1		7364	6007	6007	7801	7801	A996	A996	273A	273A	39th.	7C00
	6200		1852		ACCD	9010	9010	DCD2	DCD2	DBD5	DBD5	8114	8114	40th.	BD8F
	6300		7701		F333	17EA	17EA	4815	4815	270C	270C	8830	8830	41th.	2EF4
	271C		6880		ACCB	6100	6100	18C8	18C8	AC88	AC88	2754	2754	42th.	ADED
	A97A		8875		F433	6209	6209	1862	1862	F565	F565	09B7	09B7	43th.	9F5D
	6D01		3F01		ACCC	2846	2846	DCD2	DCD2	3E01	3E01	1656	1656	44th.	63E2
	6C00		27D6		F365	7101	7101	7C02	7C02	1908	1908	7777	7777	45th.	D4.
	DCDF		2810		ACD8	3108	3108	6BFC	6BFC	90A0	90A0	7700	7700	46th.	
	7C08		16BC		F355	17F6	17F6	8BC2	8BC2	17AA	17AA	7777	7777	47th.	

W.F.K. 8212

# ZX COLUMN

## STOCK MARKET

**Bénjamin Smith, Mount Nelson Tas.**

Stock Market is an investment simulation game. You are asked to enter the names of four companies in which you may wish to hold shares. A 'status-report' then appears giving your capital (initially \$10 000) and the current net value of your shares in each of the four companies (this begins at \$0).

A prompt is displayed at the bottom of the screen asking you to specify whether you wish to buy or sell shares in any of the companies. You should type 'B' to buy or 'S' to sell.

Entering 'E' (for Exit) ends the game, the display giving the total value (including capital) of your assets; the higher this sum is, the better, and if it is greater than \$10 000 (the starting capital) you may consider yourself to have won.

If you choose to buy stock, you are required to enter the name of the company and the amount (in dollars) that you wish to invest. The computer will continue to prompt until you specify a valid company name and a sum of money not exceeding your capital.

Selling stock is achieved in much the same way, but the amount you enter is added back on to your capital, not subtracted from it.

Fairly frequently you will receive a 10% return on your investment in a particular company; the value is displayed on the screen and credited to your capital.

In addition, share values may rise or fall (sometimes dramatically) and it is often advisable to sell stock back when it is particularly valuable. A new status report appears after each transaction.

Finally, Stock Market will run on both a ZX81 and a ZX80 with the drop-in ROM modification. 16K of user memory is required.

### STOCK MARKET

```

10 REM *** STOCK MARKET ***
20 DIM C$(4,10)
30 DIM T$(10)
40 DIM C(4)
50 LET C=10000
60 PRINT "ENTER 4 COMPANY NAME
S
70 PRINT
80 FOR I=1 TO 4
90 INPUT C$(I)
100 PRINT C$(I)
110 NEXT I
120 CLS
130 PRINT "      --- STATUS REPO
RT ---
140 PRINT "
-----
150 PRINT "
160 PRINT "      CAPITAL $ ",C
-----
170 PRINT "
-----
180 PRINT "
190 PRINT "COMPANY", "INVESTMENT
-----
200 PRINT "      " "
-----
210 PRINT
220 FOR I=1 TO 4
230 PRINT C$(I), " $ ",C(I)
240 PRINT
250 NEXT I
260 PRINT

```

```

270 PRINT "
-----
280 PRINT "BUY/SELL? "
290 INPUT U$
300 IF U$="E" THEN GOTO 630
310 IF U$(">"S" AND U$("<"B" THEN
GOTO 290
320 PRINT U$," COMPANY "
330 FOR I=1 TO 4
350 IF T=C$(I) THEN GOTO 330
360 NEXT I
370 GOTO 330
380 PRINT T$
390 PRINT
400 PRINT "AMOUNT $ "
410 INPUT A$
420 IF A(">"A) OR A(">"C(I) AND U$="S"
OR A(">"C AND U$="B" THEN GOTO 410
430 PRINT INT A
440 CLS
450 IF U$="S" THEN LET A=-A
460 LET C=C-INT A
470 LET C(I)=C(I)+INT A
480 PRINT AT 5,3
490 FOR I=1 TO 4
500 LET A=INT (AND+10-19)
510 IF A=0 THEN GOTO 500
520 LET C(I)=INT (C(I)/C(I)/A)
530 IF C(I) AND .3 OR C(I)(<10 THEN G
OTO 570
540 LET A=INT (C(I)/10)
550 LET C=C+A
560 PRINT C$(I), "RETURN $ ",A
570 NEXT I
580 IF C=0 THEN GOTO 630
590 PRINT
600 PRINT " < HIT ANY KEY TO C
ONTINUE )"
610 PAUSE 110
620 GOTO 120
630 CLS
640 FOR I=1 TO 4
650 LET C=C+C(I)
660 NEXT I
670 PRINT AT 5,0,"*** YOU FINIS
H WITH $ ",C," ***"

```

## TEXT INVERTER

**Colin Burchall, Ashwood Vic.**

The following program was written for my ZX80 when I decided that REMark statements were not easily findable in a program. It simply converts the text to its inverse.

The program loads in the first character of the program and if it's a REM, then it proceeds to invert the next characters by adding 128 to their code, until it reaches the NL code, 118. It then loads in the next character until it finds another REM etc.

The program ceases execution when it gets to VARS which is the end of the program and the begin-

ning of variables.

After the program is typed in, RUNNING it will cause it to invert its own REMark statements. If the program is run again it will not convert already inverted characters back to normal.

### TEXT INVERTER

```

9980 REM THIS PROGRAM SHOULD BE
9981 REM LOADED IN BEFORE TYPING
9982 REM IN YOUR PROGRAM.
9983 REM WHEN YOU HAVE FINISHED
9984 REM TYPING IN YOUR PROGRAM
9985 REM TYPE "GO TO 9989" AND
9986 REM IT WILL CONVERT ALL THE

```

```

9987 REM "REM" STATEMENTS TO
9988 REM THEIR INVERSE VIDEO.
9989 LET A = 16424
9990 IF PEEK (A) = 254 THEN GO TO 9994
9991 LET A = A + 1
9992 IF A = PEEK (16392) + 256 * PEEK (16393)
THEN STOP
9993 GO TO 9990
9994 LET A = A + 1
9995 LET B = PEEK (A)
9996 IF B = 118 THEN GO TO 9991
9997 IF B < 64 THEN LET B = B + 128
9998 POKE A, B
9999 GO TO 9994

```

## SPACE VOYAGE

**Stephen Meddings, Shepparton, Vic.**

In this game you are flying through a swarm of Tie fighters. The way to score is to fire at them using key 'O'. You score five points for the outside and ten for the centre.

If you are hit or the time runs out you change and must not hit anything except the inverse '=' which are escape pods from an exploded space craft. If you do hit anything or your time runs out again your score and hi-score are shown.

The game is saved by GOTO 500 and it will then auto-run displaying hi-score and who it is held by.

### SPACE VOYAGE

```

5 LET HS=0
10 LET A=0
15 LET B=15
20 LET S1=0
30 LET S2=0
40 LET G=0
50 CLS
60 PRINT AT A,B;
LET P=PEEK (PEEK 16398+256*
PEEK 16399)
70 PRINT "V"
80 IF P=18 THEN GOTO 165
90 IF P=19 THEN GOTO 165
100 IF P=21 THEN GOTO 165
110 LET U=INT (AND+30)
120 PRINT AT 20,U;"(+)"
130 LET B=B+(INKEY$="8")-(INKEY
$="=")
140 IF B<=0 THEN LET B=0
150 IF B>=31 THEN LET B=31

```

```

95 IF INKEY$="0" THEN GOSUB 12
100 SCROLL
105 IF G=300 THEN GOTO 165
110 LET G=G+1
115 GOTO 40
120 FOR F=1 TO 12
125 PRINT AT F,B;
PEEK 16399)
135 PRINT "....." AT F,B;" "
140 IF O=18 THEN LET S1=S1+5
145 IF O=19 THEN LET S1=S1+5
150 IF O=21 THEN LET S1=S1+10
155 NEXT F
160 RETURN
165 LET G=0
170 PRINT AT A,B;
PEEK 16399)
180 PRINT "S"

```

## PIRATE

**Frank Papadopoulos, Dulwich Hill, NSW**

In this game a treasure is hidden in a 40 by 40 grid. The player is required to find the treasure in nine or less attempts.

The ZX81 picks a point in this grid between (0,0) and (39,39). However, it will not tell you where it is. It does give you a hint. After each guess it will tell you how far away you are.

As each number uses five bytes some numbers have been substituted by other methods. For example, NOT PI is equal to 0 and PI/PI = 1.

```

10 PRINT "YOUR FIRST COURSE IN
PIRACY IS TO FIND A TREASURE."
12 PAUSE VAL "200"
15 CLS
20 LET X=INT (AND+40)
30 LET Y=INT (AND+40+2)
40 LET N=NOT PI
50 PRINT "GIVE YOUR X AND THEN
Y (BOTH 0 TO 39)"
60 INPUT X1
70 INPUT Y1
75 CLS
80 LET Z=39
90 CLS
95 IF X1>Z OR Y1>Z THEN PRINT
"RE-ENTER"
98 IF X1>Z OR Y1>Z THEN GOTO 5
0
80 LET N=N+PI/PI
90 PLOT X1,Y1+2

```

```

100 LET D=((X1-X)*(X1-X)+(Y1+2-
Y)*(Y1+2-Y))*.5
110 IF D=NOT PI THEN GOTO UAL "
150"
120 PRINT (INT (D+10))/10;" PAC
ES AWAY, NEU X,Y?"
130 IF N<=9 THEN GOTO UAL "60"
140 CLS
150 IF N=1 THEN PRINT "WHAT A F
LUKE..."
160 IF N<=5 THEN PRINT "HOW DID
YOU DO IT?"
170 IF N<=9 THEN PRINT "YOU GOT
IT IN ",N," GOES."
180 IF N>9 THEN PRINT "YOU'LL N
EED EXTRA PIRATE TUITION"
190 PRINT "IT WAS AT ",X," ",Y-
2
200 STOP

```

# EXCLUSIVE ETI READER OFFER

## THE "B-ETI" LOW-COST SERIAL TERMINAL

By special arrangement between ETI magazine and Applied Technology, makers of the famous Microbee personal computer, we introduce the B-ETI serial terminal.

Essentially, the B-ETI makes a low-cost "glass teletype". It consists of a 'stripped-down' Microbee and supports the following data formats, all software selectable from the keyboard: 7 or 8 bit ASCII with odd, even or no parity, or Baudot (5-bit) code. Selectable data speeds of 45/50/75/110/300/200/1200 baud, no handshaking, or 2400/4800 with handshaking (pin 20 on DB25), all full or half duplex. It can also drive a parallel printer. The B-ETI emulates the popular ADM-3A and most of the 'Televideo 912' formats, making it simple to install in CP/M systems.

The B-ETI has dozens of applications with computer, and computer-related, project and equipment. It is ideal as a low-cost terminal for the ETI-690 Little Big Board computer published in the October '83 issue of ETI for example, or as part of a radioteletype system in an amateur radio station.

The screen format is 80 characters wide by 24 lines. Upper and lower case characters are available and each character key auto-repeats if held down longer than one second.

The video output can be plugged directly into one of the low-cost monitors currently available. Many of these have a 12 Vdc output socket which can power the B-ETI directly. Alternatively, it can be powered

from any suitable 12 V dc source capable of supplying 700 mA. A power pack is not included. As the low-cost monitors available are generally priced at around \$200 or less, you can have a complete serial terminal for less than \$500!

This is an introductory offer. The B-ETI serial terminal has not yet been offered for sale through retail stores. When it is, it is expected to sell in the \$330-\$340 range so you save around 20-25% by taking advantage of this offer.

This offer is made by Applied Technology Pty Ltd (Incorporated in NSW) in cooperation with ETI magazine and ETI is acting as a clearing house for orders. All orders will be despatched by road freight for \$10, insurance included, anywhere in Australia. While deliveries will be generally ex-stock, please allow up to four weeks for delivery to cover order processing and any delays that may occur.

### HOW TO ORDER YOUR B-ETI SERIAL TERMINAL

Fill out the coupon here, or a photostat of it, and enclose a cheque, bank cheque or money order for the amount required, made out to **APPLIED TECHNOLOGY PTY LTD.**

Cut out the coupon and send it to: **B-ETI TERMINAL OFFER**  
c/o ETI Magazine, P.O. Box 21, Waterloo, NSW, 2017.

Please rush me ..... B-ETI Serial Terminal(s)  
@ \$275 each plus \$10 freight.

I enclose \$..... total.

Cheque or Money Order No.....

Signature .....

Name .....

Address .....

Postcode .....

Offer extended to Jan. 31, 1984



### INTRODUCTORY PRICE

#### 90 DAY WARRANTY

The B-ETI is manufactured especially for ETI readers by Applied Technology and a full 90-day warranty is available as well as normal backup service.

#### APPLICATIONS

- low-cost computer terminal. Use with ETI-690 Little Big Board.
- use with modem as remote computer terminal.
- use with radioteletype (RTTY) converter/modulator in amateur radio station.

#### FEATURES

- 300/1200 baud operation, software selectable.
- powered from 12Vdc supply.
- low cost — only \$275.
- 80 characters x 24 lines screen format.
- auto-repeat on all character keys and space bar.


BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

### BNC & PL 259 CONNECTORS



P 0514 Plug ea. 10 +  
P 0515 Socket 1.95 1.80  
1.95 1.80

### UHF CONNECTORS

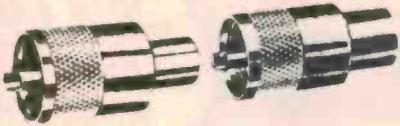

REDUCER FOR P 0503  
P 0502 (PL259 for RG58 Coax) 1.40 1.25  
P 0503 (PL259 for RG8 Coax) 1.40 1.25  
P 0504 Reducer .25 .20

### UHF SOCKETS



P 0509 Soc. SQ MNT ea. 10 +  
P 0510 Soc. RND MNT 1.20 1.00  
P 0508 F/F Coupler 1.40 1.25  
1.95 1.65

### MICRON 30 WATT

This brilliant little 30 watt iron is just the "bee's knees" for the electronics hobbyist, electrician or home handyman. We searched the world for a low cost yet quality iron which met the criteria of \* light-weight \* screw in interchangeable tips \* efficient thermal transfer from element to tip \* tip temperature maintains within the limits suitable for electronic work and also small household jobs \* and of course, fully S.E.C. tested and approved.



Comes fitted with T 2435 Tip

WAS \$12.95

### REPLACEMENT TIPS

T 2430 \$9.50  
T 2434 Flat Tip .95  
T 2435 Conical Tip .95  
T 2436 Instrument Tip .95

### SOLDER

200 gram reel. 1mm universal gauge. Suitable for all types of electronic soldering. Resin cored and includes bit saving additive.

T 1200 \$4.95  
5 up \$4.50 ea.



ETI CIRCUITS NO. 1, 2 and 3.  
~~\$2.50 ea.~~ \$2.00 PROJECT ELECTRONICS  
~~\$4.50 ea.~~ \$3.00



Contains hundreds of circuit and application notes.



### VELOSTAT

Non-static sheeting for storing CMOS IC's, LSI's etc. 1000 times better than aluminium foil. Will store up to 150 IC's on one 225 x 150mm sheet.

H 0600..... \$2.50 per sheet




### MINI SPEAKER 57mm

Large Ferrite Magnet. Ideal replacement speaker. Great for hobby projects.

C 0610... ~~\$1.95~~  
Now \$1.25 ea.

### SOLDERING IRON STAND UNIVERSAL TYPE

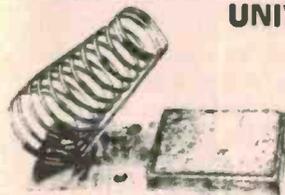

T 1302 NOW ~~\$8.50~~  
\$5.00

### MINI BUZZER 5-15V DC



Handy little solid-state audio "Buzzer" or signalling device. Just the shot for communicator panels, or for timer alarms or in the car. Polarity conscious.  
S.5062 . . . \$1.00

### OOPS WE MADE A BOO BOO!

Right now we have around 1/2 million Premium Quality Genuine Phillips IN914/IN4148 Signal Diodes — Out they go at never to be repeated prices.

20101.....  
1's 100's 1000's  
4c 3c 2c

SAVE ON BULK QUANTITIES

### HALF PRICE Z80 A


FULL SPEC FAMOUS S.G.S. BRAND



Z9001 CPU WAS \$8.95 NOW \$4.50  
Z9005 PIO WAS \$8.95 NOW \$4.50

### NEW PRODUCT

#### 10 SEG. RED BAR GRAPH MODULE

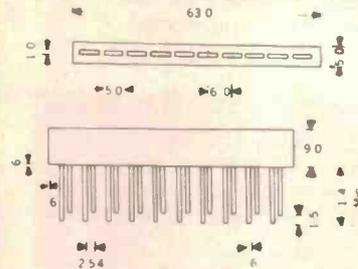

Z 0180 \$2.50 10 up \$2.20 ea.  
100 UP \$1.80

### MINI TOGGLE SWITCHES

OEM QUALITY 250V 2 AMP RATED  
6mm mounting hole  
12mm x 12.7mm x 20mm (D)



	ea.	10 +	25 +
S1010 SPDT	\$1.25	\$1.10	.95
S1025 SPDT C/OFF	\$1.50	\$1.25	\$1.10
S1020 DPDT	\$1.50	\$1.25	\$1.10
S1030 DPDT C/OFF	\$1.95	\$1.75	\$1.50

### MU 45 PANEL METERS QUALITY CLASS 2.5

Overall dimensions 58W x 52H. Bolt Mounting Centres 38 x 38. Hole required 44mm. Nuts & Washers provided.



### SAVE ON BULK QUANTITIES

	FSD	Resistance	Price	10 Up
Q 0500	1MA	200	8.25	7.25
Q 0505	50UA	3500	8.25	7.25
Q 0510	5A	.02	8.25	7.25
Q 0520	20V	2000	8.25	7.25
Q 0525	30V	3000	8.25	7.25
Q 0535	VU		8.50	7.50

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY



## DIAGNOSTIC DC/AC CURRENT METER

**T**he H.E.M.E. 1000 is a revolutionary new instrument and a powerful new diagnostic tool for use by engineers and designers involved in setting up ac and dc motors, variable speed drives, motor vehicles, battery powered equipment, welding equipment, electroplating apparatus or equipment where surge current values are of paramount importance.

The new device registers on a digital display the maximum surge value and there is a hold facility to assist both surge and normal current values to read efficiently.

An analogue output socket permits RMS current to be displayed or monitored on a chart recorder or instantaneous examination by cathode ray oscilloscope, enabling complex current waveforms to be displayed.

The device is a clip-on, hand held, battery powered meter and as such there is no need to power down apparatus to insert ammeters. The new device from H.E.M.E. therefore makes diagnostic current measurement quicker, easier and safer than voltage measurement.

The instrument is autoranging from 0-1000 A and will operate from dc to 1 kHz, indicating polarity. Accuracy, which is  $\pm 1\%$  of range, is only minimally

affected by the position of the conductor relative to the jaws, the proximity of the return current and by stray magnetic fields from adjacent components.

Resolution is 100 mA from 1 A to 199.9 A and 1 A from 200 A to 1000 A. Display includes low battery warning, dc polarity and ac indications.

The device uses the long known Hall Effect which describes the production of a voltage when an electrical current is applied to a thin semi-conductor placed transversely to a magnetic field.

For further information contact Warsash Pty Ltd, P.O. Box 217, Double Bay NSW 2028. (02)30-6815.

## NEW DMM

**A** new digital multimeter on the market is the Keithly Instruments model 175.

This  $4\frac{1}{2}$  digit, autoranging DMM features digital calibration and a battery option, making it fully portable.

The 175's 100-point data logger monitors drifts, determines rates of change, and collects response curve data without a printer or output cables.

The data logger has six different store rates ranging from one reading every 400 ms, to one



reading every hour. Data recall is 'push-button' easy.

For further information con-

tact Scientific Devices Australia Pty Ltd, 2 Jacks Rd, South Oakleigh Vic. 3167. (03)579-3622.

## HAND HELD SPECTRUM ANALYSER

**V**ipac claims that its newly released spectrum analyser, the LD800 offers the widest display range of any other available sound level meter or acoustic analyser.

Features include 60 dB span linear LED display and 10-150 dB measuring range with in-built  $\frac{1}{3}$  octave band analysis. An extensive array of peripherals consisting of calculators, software, printers, plotters and data storage devices are available from Vipac.

Accessories include the model 801 signal processor with four computer-selected microphone inputs, internal white or pink noise generators, programmable signal output levels and peripheral equipment switch channels for rotatable booms or floor tappers.



The Model 802 accelerometer preamplifier enables inputs from two tri-axial accelerometers (six channels total). It has programmable input sensitivities and provision for high and low impedance accelerometers with electronic integration for the measurement of displacement, velocity and acceleration.

For further details contact Vipac Instruments Pty Ltd, 30-32 Claremont St, South Yarra Vic 3141. (03)240-841. ▶

## AWA's 50 MHz OSCILLOSCOPE

The LBO-525L Dual Trace Oscilloscope from AWA features a 150 mm rectangular CRT with high brightness assured by the 12 kV accelerating potential.

This Leader oscilloscope has a dc bandwidth to 50 MHz at 5 mV/div sensitivity which can

be increased to 500  $\mu$ V/div with a bandwidth of 5 MHz.

The signal delay line enables observation of the leading edge of fast rise time pulses and display modes include Ch.1, Ch.2, Chop, Alt, Add and Ch. 2 Invert.



Dual time bases provide a

wide range of sweep facilities including continuous delayed sweep, trigger delayed sweep and alternate triggering for synchronizing two different waveforms. Sweep times are 'A' 0.2  $\mu$ S/div to 0.2 S/div and 'B' 0.2  $\mu$ S to 0.5 mS/div. The 10X magnifier gives a maximum sweep of 20 nS/div.

The sensitivity is 0.5 div/0.2 V p-p for both Normal and Auto up to 10 MHz and 1.5 div/0.6 V p-p up to 50 MHz. In X-Y mode the dc bandwidth is to 1 MHz, with less than 3° phase difference at 100 kHz.

The LBO-525L is supplied with two probes and available options include accessory pouch, front panel cover, hood and rack mounting kit.

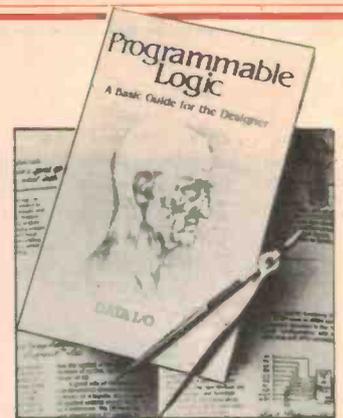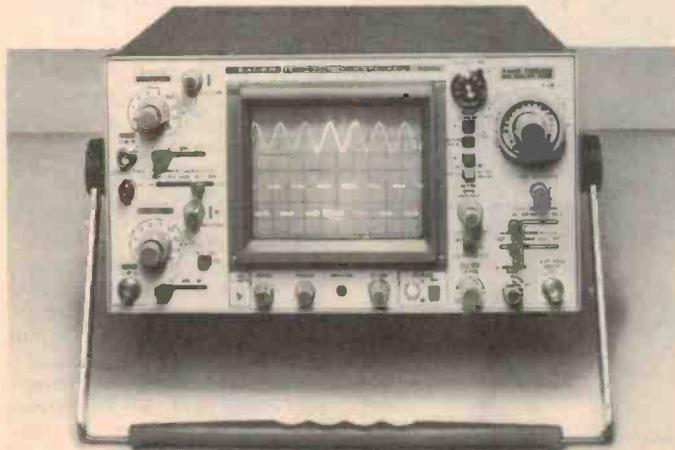Further information available from Amalgamated Wireless (Australasia) Ltd, North Ryde Division, Cnr Talavera & Lane Cove Roads Macquarie Park, North Ryde NSW 2113. (02)887-7111.



## FREE GUIDE

Available from Warburton Franki is a 32 page guide book published by Data, which explains programmable logic and its advantages over fixed-function LSI/MSI logic and custom logic.

The book details an actual design problem, showing how design equations are generated and translated into fuse tables and how a PAL or AFL device is programmed and functionally tested.

For a free copy contact Warburton Franki, 199 Parramatta Rd, Auburn NSW 2144. ●

## MODEL 175 AUTORANGING BENCH/PORTABLE DMM

### KEITHLEY INSTRUMENTS



The new Model 175 Autoranging Bench Digital Multimeter, from Keithley Instruments, Inc., combines the measurement capabilities of much higher-priced system DMMs with several new features to extend its utility, yet retain simplicity of use. Ideal for use as a bench meter in production or lab work, this 4-1/2 digit autoranging DMM also has a field-installable battery option, making it fully portable. Fast autoranging (up to 200ms per range change on DCV) enables the user to concentrate on getting the reading without worrying about choosing the appropriate range.

The Model 175 features digital calibration for reduced cost of ownership, as many users can now calibrate the meter in-house. With the Model 1753 IEEE-488 (GPIB) option, the 175 is the lowest-priced IEEE-interfaceable DMM available. Model 175's 100-point data logger monitors drifts, determines rates of change, and collects response curve data without a printer, output cables, or complicated hook-ups. The data logger has six different store rates from one reading/400ms to one reading/hour, and data recall is "push-button" easy.

Other features of the Model 175 include:

- 4-1/2 digit LCD display with annunciators for function, range, and feature indication
- 10 $\mu$ V/10m $\Omega$ /10nA sensitivity
- 0.03% basic DCV accuracy
- True RMS AC
- 10A capability
- 100kHz bandwidth in AC
- dBm/relative function
- Relative reference
- Max/Min reading hold
- Safety input jacks
- Front panel accessible amps fuse

For more information on the Model 175 Autoranging DMM, or on a variety of other industrial electronic testing and measurement equipment, contact:



SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.

VIC. 2 JACKS RD., SOUTH OAKLEIGH, 3167  
PHONE (03) 579 3622 TELEX AA 32742  
N.S.W. OFFICE 2, 35-37 HUME ST., CROWS NEST, 2065  
PHONE (02) 43 5015 TELEX AA 22978  
S.A. 31 HALSEY RD., ELIZABETH EAST, 5112  
PHONE (08) 255 6575 TELEX AA 88125

# NEW MODEL!



**THE PRICE/PERFORMANCE  
WINNER**



CIC300T01

**CICADA  
300T**

**DATA MODEM  
WITH INTEGRATED TELEPHONE**

For user installation to a standard phone socket without Telecom assistance, the new Cicada 300T 300-Baud data modem features fully integrated phone for maximum convenience. With all the legendary performance and reliability of the standard Cicada 300:

Or, buy the continuously improved standard Cicada 300 for use with your own telephone. Now operated by hundreds of government, business and private users, the Cicada series modems carry a full, meaningful warranty.

**Specifications** (Both modems): Compact answer-and-originate units for direct connection to phone lines and for computer interface utilising either RS232C or V24/28 systems. Unit measures 203mm x 152mm x 63.5mm. Telecom approval number C83/37/1011.

Available now from Centre Industries or leading retailers.



187 Allambie Road, Allambie Heights, NSW 2100  
Telephone (02) 451 5555 After Hours (02) 451 6244  
Telex AA 22671

## JIL SX-200 COVERS 26-88 MHz & 108-180 MHz & 380-514 MHz



### A BETTER SCANNING MONITOR RECEIVER.

Monitors over 33,000 frequencies from 26 to 88 MHz, 108 to 180 MHz and 380 to 514 MHz. Bands included within this range are HF and UHF CB, 27 and 155 MHz MARINE, Australian LOW BAND, AIRCRAFT band, VHF SATELLITE band, 10 Mx, 6 Mx, 2 Mx and 70CMx AMATEUR BANDS, VHF High BAND as well as UHF two-way band.

Mechanically rugged the SX-200 uses high quality double-side Epoxy-Glass printed circuit boards throughout. Some of its other outstanding features include 3 MODE SQUELCH circuitry which allows the lockout of spurious and carrier only signals, extremely low spurious count, AM and FM detection on all bands, FINE TUNING control for off channel stations, 240 VAC or 12 Volt DC operation, Accurate QUARTZ CLOCK, Squelch operated OUTPUT for switching a tape recorder etc, 16 Memory channels, MEMORY BACKUP, which lasts up to two years, high SENSITIVITY and SIGNAL-TO-NOISE ratio on all bands, CRYSTAL FILTER for excellent SELECTION and easy serviceability due to component layout as well as a 90 day warranty.

Its high quality and performance is testified by the fact that it is in use by a large number of State government and Federal bodies including most state and federal police departments.

**Contact GFS, the Australian Distributors, or our Interstate outlets for full technical specifications.**

We also market a range of pocket scanning receivers and transceivers. Contact us for full details.

**PRICE \$599 INC. S.T. + \$12 P & P; SERVICE MANUAL \$12 + \$1.50 P & P; SCAN-X BASE ANTENNA \$62 + \$10 P & P; EXP-32-32 CHANNEL MEMORY EXPANDER KIT \$53 + \$5 P & P; A4-AM AUTO AM KIT FOR AIRBAND \$32 + \$5 P & P; CVR-1B CONVERTER 225-380 MHz \$199 + \$5 P & P; CVR-2 CONVERTER .5-26 MHz \$189 + \$5 P & P; LOG S DIRECTIONAL ANTENNA 100-520 MHz 9el \$89 + \$10 P & P; LOG-SP DIRECTIONAL ANTENNA 65-520 MHz 13el \$125 + \$10 P & P; INTERSTATE DEALERS: NSW: (02) 211 0531; QLD: (07) 397 0808; SA: (08) 269 4744; WA: (09) 328 4160; VIC: (03) 329 7888.**

**GFS Electronic Imports  
17 McKeon Road, Mitcham, 3132, Vic.  
Telex 38053 GFS. Phone (03) 873-3777**

# 10-50% OFF SALE!!

STOCK! WE'RE CHOKING IN IT. WE HAVE SO MUCH STOCK AT JAYCAR/ELECTRONIC AGENCIES WE HAVE NO WHERE TO SIT! WE HAVE TO SACRIFICE MANY LINES AT COST OR EVEN BELOW TO MAKE WAY FOR NEW 1984 PRODUCTS. SO IF YOU HAVE GOT ANY MONEY LEFT AFTER CHRISTMAS, GET ON DOWN TO JAYCAR - No.1 FOR SPECIALS! MOST OF THE ITEMS SHOWN ARE 10 - 50% OFF OUR NORMAL LOW PRICES!!



## FANTASTIC Multimeter

- FUSE/DIODE PROTECTED!
- 4mm BANANA SOCKET PROBES!
- BIFURCATED SELECTOR SWITCH CONTACTS!
- ABS IMPACT-RESISTANT CASE!
- LARGE MEASURES 90(w) x 135(h) x 45(d)mm

**SPECIFICATIONS:**  
 DC 0 - 0.25 AC 0 - 10  
 0 - 10 0 - 50  
 0 - 50 0 - 250  
 0 - 250 0 - 1000  
 0 - 1000 AT 9,000 ohms/volt  
 AT 20,000 ohms/volt

**RESISTANCE DC CURRENT**  
 0 - 5K 0 - 0.05  
 0 - 50K 0 - 25  
 0 - 500K 0 - 250mA

dB: 20 to +22dB  
 BATTERY CHECK FACILITY: AA, C & D CELLS  
 ACCURACY: DC +/-3% F.S. AC +/-4% F.S.

OHMS +/-3%  
 BANANA PLUG PROBES AND BATTERY INCLUDED  
 This is an unbelievable meter bargain. Normally this unit would sell for around \$25. Japanese made quality.  
 Cat. QM-1005

NORMALLY (a low price anyway) ~~\$17.95~~

THIS MONTH

**\$15.95**

SAVE WELL OVER 10%

## BT151-650R

This is the 650 volt version (for extra safety) of the C122E SCR which we use in the popular 'Fluorescent Lamp Starter' Kit as described in October 1982 EA. Normally \$1.50 each. This month only \$0.95 each! (Minimum 5 pieces). Makes the Fluoro starter kit very cheap! (PCB's for the kit) Cat. HPB747

ONLY \$1.95



Cat. ZX7022  
 (8 amp 650V SCR)

## Quartz Crystal Clock movement

Cat. XC600Q




- Very compact and reliable
- Self-starting one second stepping motor has strong torque
- Powered by 1.5V AA battery that lasts for a year
- Supplied with two sets of hands, one short and one long
- +/- 15 second/month accuracy
- 56mm square, 15mm deep

~~\$14.95~~

SAVE \$2  
 JANUARY ONLY  
**\$12.95**
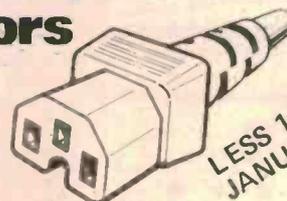
## IEC Cable Connectors

Most imported equipment these days now uses IEC-320 style AC power inlet connectors. Indeed, the electronics mags will soon be specifying these connectors on many of their mains-powered projects to simplify (and therefore make safer) mains wiring. Jaycar now stocks a range of ELECTRICITY AUTHORITY APPROVED mains line cords. We have them in straight entry, left and right entry with and without standard 240V mains moulded plug. Each cord is a generous 2 metres long and is rated at 7.5 amp continuous.



LESS 10% FOR JANUARY ONLY

Cat. No	Description	Price
PS4302	LINE CORD STRAIGHT ENTRY 2M	\$3.95
PS4304	LINE CORD R/HAND ENTRY .2M	\$3.95
PS4305	LINE CORD L/HAND .2M	\$3.95
PS4306	LINE CORD STRAIGHT ENTRY WITH 240V PLUG .2M	\$4.95
PP2302	IEC 320 CHASSIS PLUG	\$2.95
WM4530	2 PIN 240V PLUG MOULDED TO 2M FIG. B	\$2.95
	7.5 AMP CORD - BLACK IN COLOUR	\$2.95

(Note: the first 5 items are grey in colour)

## low cost IC inserters AND EXTRACTORS

Up until now these have cost a fortune!!

Features:

- CMOS SAFE conductive plastic
- Exclusive bent pin alignment guides in handle . 8 to 40 pins.
- Ground strap can be connected.
- One hand operation.

INSERTERS

Cat. No	Model	Description	Normally	NOW
TH1810	CIT820	8 - 20 pin	\$5.95	\$4.16
TH1812	CIT22	22 pin	\$6.50	\$4.55
TH1814	CIT2428	24 - 28 pin	\$6.95	\$4.86
TH1816	CIT3640	36 - 40 pin	\$8.95	\$6.26

EXTRACTOR

Deceptively simple looking device. One piece metal construction. 8-40 pins

TH1818 ET480

\$2.95  
 NOW \$2.06



30% OFF JANUARY

## MOTOROLA CMOS DATA



Normally \$14.50


NOW ONLY \$9.95

862 pages crammed with up-to-the minute information on 4000, 4400, 4500 devices. A complete product index is included along with comprehensive data on every device (almost 200 described). As the part numbering system is standard, you can use this reference for other manufacturers products with the same generic numbers. This book normally sells for \$14.50.

Cat. BM-4210

## RIBBON tweeter

SAVE \$16.95

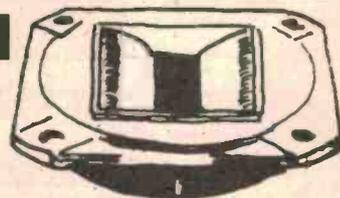

Unique regular phase design drives the entire diaphragm, uniformly and completely in phase over the full frequency range. The performance of an electrostatic speaker with the ruggedness and ease of use of a dynamic.  
 Cat. CE-2042

NORMALLY \$36.50 ea

ONLY \$19.95

- 91dB sensitivity
- 50W system power
- 5,000-40,000Hz
- No voice coil

# 10-50% OFF SALE!!

## SAVE A FORTUNE!

### LOW COST DIGITAL MULTIMETER KIT

Ref: EA March 1983 (This month)  
Almost everyday we are asked for a multimeter kit. Up until now we thought that it was just not worth it considering the fine low cost built up units available. The DP2010 changed all that.

This kit, fully imported from the UK uses the famous OPA929 custom LCD/Volmeter to achieve phenomenal accuracy at very modest cost!

All parts are included to complete the meter including an attractive and colourful front panel, a 9V battery (is required)

Set of test probes to suit \$2.95

Probe to suit Cat. WTS312

ONLY \$2.50

Eveready 216 (red)

9V Battery Cat. SB2370

ONLY \$1.40



ONLY \$45

SAVE OVER 15%

DP2010 kit Cat. KJ7010  
ONLY \$45  
SPECIFICATIONS

Function	f.s.d.	Resolution	Accuracy	Protection
Volts (d.c.)	2V	1mV	1%±1 digit	500V for one minute
	20V	10mV	1%±1 digit	one minute
	200V	100mV	1%±1 digit	one minute
	500V	1V	1%±1 digit	one minute
	2mA	1µA	1%±1 digit	1A/250V
Current (d.c.)	20mA	10µA	1%±1 digit	
	200mA	100µA	3%±1 digit	
	2000mA	1mA	5%±1 digit	
Volts (a.c.)	2V	1mV	2%±5 digit	500V for one minute
	20V	10mV	2%±5 digit	one minute

AC VOLTAGE AND CURRENT RANGES  
When 53a selects a.c. functions the output from either the voltage attenuator or current shunt is fed through C1 to remove any d.c. component.

200V	100mV	2%±5 digit
500V	1V	2%±5 digit
2mA	1µA	2%±5 digit
20mA	10µA	2%±5 digit
200mA	100µA	4%±5 digit
2000mA	1mA	7%±5 digit
2K	1	1%±1 digit
20K	10	1%±1 digit
200K	100	1%±1 digit
2000K	1K	1%±1 digit
2V	1mV	1%±1 digit

### AMAZING VALUE

WAS \$45  
THIS MONTH SAVE... **\$37<sup>95</sup>**



### 8 CHANNEL MIXER KIT

SAVE JANUARY ONLY

Ref: EA March/April 1983  
This great 8 channel 'live' mixer is perfect for bands, churches, theatre groups, home recording, disco etc.

Each input channel accepts either microphone (balanced) or line (1V) levels. Powerful equalisation foldback effects facilities are provided. The left and right master channels can drive balanced or unbalanced lines with 5 band "graphic" equalisation. Separate foldback and "effects" are provided.

The unit can be rack mounted or housed in a console chassis (which accommodates the power supply). Attractive wooden end-pieces finish the console to form a professional looking unit.

**\$495** AMAZING VALUE

FREE!!  
Console mount chassis and power supply INCLUDED FOR \$495!  
NORMALLY \$98 EXTRA

### TWIN SCREENED AUDIO CABLE

Twin screened round audio cable. (Two screened conductors NOT fig '8')

This cable normally sells for \$0.48/metre or \$42.00/roll

Cat. WB-1504

\$20.00/roll



**\$20<sup>00</sup>**  
PER ROLL  
SAVE OVER 50%.

### SPRAY ON CONDUCTIVE PLASTIC...

**\$6<sup>95</sup>**

This handy 200 gram spray enables you to do all manner of things. You can spray sheets of Styrene foam and make them suitable for storing your MOS IC's. Far cheaper than other methods! You can make conducting screens inside plastic boxes to shield RF. You can re-coat the back of CRT's. You can make conductive parts of equipment cabinets to reduce static. The paint dries to a hard varnish like film. Non-Inflammable and Non toxic. Grab a can now. You never know when you will need it!



### 115 VOLT COMPUTER FANS

**\$12<sup>95</sup>** THIS MONTH

NORMALLY \$14.95

We have made a scoop purchase of computer grade Box Fans. They measure a standard 80 x 80 x 40mm. But there's a catch! They are only available in 115V! Great if you are making equipment for export to the USA - or use 2 in series! No problem!

ONLY \$14.95



SAVE \$2.00 OR OVER 10%

### Lyrebird Piano Kit REF: EA 11/81-1/82

GREAT NEW FEATURES!  
- FREE! A stand (like the one illustrated but not exactly the same). Worth around \$50 but yours at no extra charge with each 73 or 88 note kit.  
- FREE! A soldering iron (worth around \$19). Yours to keep to give years of faithful service after you have completed your Lyrebird. (88 note only)  
- FREE! A 200g roll of solder. You will need some to build the Lyrebird but there will be plenty left over for other projects. (73 & 88 note versions).  
- FREE! Quality IC sockets provided in both kits.

HUNDREDS SOLD!!!

REMEMBER!! THE LYREBIRD OUTPERFORMS READY BUILT PIANOS COSTING UP TO THOUSANDS OF DOLLARS MORE. WHY PAY MORE WHEN YOUR CONSTRUCTION KNOWLEDGE CAN SAVE YOU A FORTUNE?



The stand that we provide for the piano kit is not the same as the one shown in the illustration.

88 NOTE VERSION  
NORMALLY \$589  
THIS MONTH \$489  
SAVE \$100!!

73 NOTE VERSION - NORMALLY \$475  
THIS MONTH \$425 - SAVE \$50!!


### 10" ELECTRIC GUITAR SPEAKER

Quality Pioneer brand check the specs! Check the price!!

Impedance	8 ohm
Voice Coil Dia.	1 1/2 (inch)
Power Rating	60 WATT (RMS)
Resonant Frequency	80Hz
Sensitivity	98 (dB/W)
Response	80Hz - 7,000Hz
Total Flux	61,100 Maxwell
Flux Density	8,300 Gauss
Net Weight	1,540 gm



**\$29<sup>95</sup>**

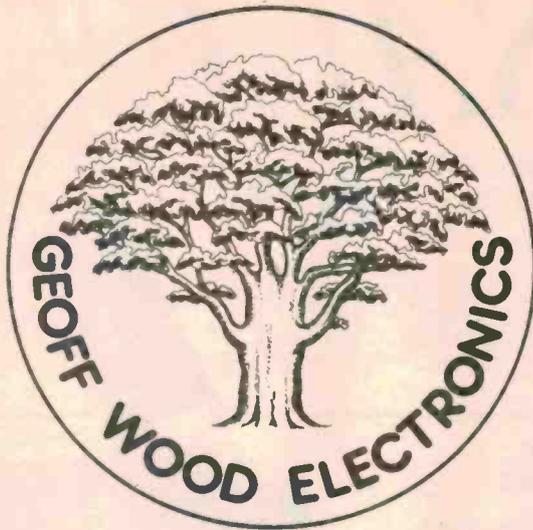

Geoff Wood is well known on the retail electronics scene in Sydney. Now he's opened his own store in a brand new location and he's stocking the broadest range of prime quality National Semiconductor product ever stocked at a retail level in Sydney.

The specials listed will be available only while stocks last - so get your orders in early. Many other specials for personal shoppers only.

### GEOFF WOOD ELECTRONICS PTY LTD

Incorporated in N.S.W.  
656A Darling St, Rozelle 2039  
(One door from National Street)  
Tel: **810 6845**

8.30 to 5 Monday to Friday, 8.30 to 12 Sat.  
Mail Orders add \$3.00 to cover postal charges.  
Next day delivery in Sydney add \$5.00.  
All prices INCLUDE sales tax.  
Tax exemption certificates accepted if line value exceeds \$10.00.



#### LINEAR DEVICES

LM349N	0.95
WIDE BAND UNCOMP QUAD 741 OP AMP	
LM309K	1.80
5V TO-3 REGULATOR	
LM338K	8.80
5A ADJUSTABLE REGULATOR TO-3	
LM381N	1.45
LOW NOISE DUAL PREAMPLIFIER	
LM386N-1	0.55
LOW VOLTAGE AUDIO AMPLIFIER	
LM565CN	0.95
EVER POPULAR PHASE LOCK LOOP	
LM723CN	0.45
14 PIN DIL ADJUST VOLTAGE REGULATOR	
UA741HC	0.95
METAL CAN VERSION	
UA741PC	0.35
MOST POPULAR OP AMP EVER MADE	
LM7805CT	0.75
TO-220 5 VOLT POSITIVE REGULATOR	
LM7812CT	0.75
TO-220 12 VOLT POSITIVE REGULATOR	
LM7815CT	0.75
TO-220 15 VOLT POSITIVE REGULATOR	
LM7905CT	0.85
TO-220 5 VOLT NEGATIVE REGULATOR	
LM7912CT	0.85
TO-220 12 VOLT NEGATIVE REGULATOR	
LM7915CT	0.85
TO-220 15 VOLT NEGATIVE REGULATOR	
LM78L05ACZ	0.35
TO-92 5 VOLT NEGATIVE REGULATOR	
LM78L12ACZ	0.35
TO-92 12 VOLT POSITIVE REGULATOR	
LM78L15ACZ	0.35
TO-92 15 VOLT POSITIVE REGULATOR	
LM79L05ACZ	0.70
TO-92 5 VOLT NEGATIVE REGULATOR	
LM79L12ACZ	0.70
TO-92 12 VOLT NEGATIVE REGULATOR	
LM79L15ACZ	0.70
TO-92 15 VOLT NEGATIVE REGULATOR	
RC4195	0.50
PLUS/MINUS 15V AT 100mA, TO66 PKG	

<b>CAPACITOR SCOOP</b>	
SIEMANS	10.00/C
.047 250 VOLT	

**74LS HARD TO GET?**  
NOT AT GEOFF WOOD ELECTRONICS AT  
PRESENT. GET YOURS TODAY.

#### CMOS

CD4007C	0.40
DUAL COMPLEMENTARY PAIR PLUS INV.	
CD4008C	0.85
4 BIT FULL ADDER	
CD4015C	0.75
DUAL 4 BIT STATIC REGISTER	
CD4028B	0.85
BCD-DECIMAL DECODER	
CD4050B	0.45
HEX NON INVERTING BUFFER	
CD4069	0.35
HEX INVERTER	
CD4070	0.35
QUAD 2 INPUT EXCLUSIVE OR	
CD4160B	0.95
DECADE COUNTER, ASYNCHRONOUS CLEAR	
CD4175B	0.95
QUAD D FLIP FLOP	
CD4584B	0.85
HEX SCHMITT TRIGGER	
CD4724B	0.85
8 BIT ADDRESSABLE LATCH	
HM74C04	0.35
HEX INVERTER	
HM74C86	0.35
QUAD 2 INPUT EXCLUSIVE OR	
HM74C150	3.80
16 TO 1 MULTIPLEXER	
HM74C160	0.95
DECADE COUNTER, ASYNCHRONOUS CLEAR	
HM74C162	0.95
DECADE COUNTER, SYNCHRONOUS CLEAR	
HM74C175	0.95
QUAD D FLIP FLOP	
HM80C97	0.70
THREE STATE HEX BUFFER	

#### INTERFACE PARTS

DS1488	0.92
MOST COMMON RS232 LINE DRIVER.	
DS1489	0.92
QUITE USEFUL WITH DS1488	

#### SUPER REG

LM396K	20.99
10 AMP ADJUSTABLE REGULATOR WE NOW HAVE LIMITED QUANTITIES IN STOCK.	
PM001	32.50
9V 10AMP TRANSFORMER TO SUIT 396 IDEAL FOR 5V SUPPLY.	

#### MICROPROCESSORS

8085A	12.68
THEY TELL US SOME COMPUTER MOB HAVE BOUGHT UP WORLD PRODUCTION FOR THE NEXT FEW MONTHS. THEY AINT GOT OURS.	

#### SOCKETS

100-S	3.95
TRUE 9100 BUS EDGE CONNECTOR FITS MOTHER BOARD WITHOUT MODIFICATION.	
AXR-3-11	3.95
FEMALE	
AXR-3-12	2.05
MALE	
AXR-3-31	4.40
FEMALE	
AXR-3-32	2.40
MALE	
AXR-LNE-11	6.25
FEMALE	
AXR-LNE-12	6.10
MALE	
AXR-LNE-31	6.25
FEMALE	
AXR-LNE-32	3.45
MALE	
DB25P	2.35
D TYPE PLUS SOLDER	
DB25S	3.45
D TYPE SOCKET SOLDER	

#### MEMORY

MM2114N	1.95
1024 X 4 RAM	
MM2114N-055	0.95
1024 X 4 RAM 0-55 DEG C	
MM2716Q-1	10.49
POPULAR 350ns UV PROM	

#### LOGIC WINNERS

DM7406N	1.20
30V INVERTER ALMOST IMPOSSIBLE TO GET.	
DM7407N	1.20
LIMITED QUANTITIES ONLY BE QUICK	
DM7438N	1.20
QUAD BUFFER-A BEAUTY	

#### LITTLE TRIMMERS

3326H-1	0.30
BOURNE SINGLE TURN 5K TRIMMER LIMITED QUANTITIES ONLY	

#### NATIONAL SEMICONDUCTOR DATA BOOKS

AUDIO/RADIO	9.25
CONTAINS HEALTH OF INFORMATION ON PREAMPS, AM/FM/STEREO, POWER AMPS AND FLOOR/DUST.	
ADV. LOGIC	9.25
COVERS ADVANCED LOGIC FAMILIES (74ALS AND 74AS).	
CHOS	10.95
CONTAINS DETAILS ON 74C AND CD4000 SERIES. INCLUDES SPECIAL FUNCTION LOGIC, MEMORY AND APPLICATION NOTES.	
INTERFACE 83	17.00
NEW NEW NEW NEW NEW NEW NEW NEW CONTAINS LINE DRIVERS/RECEIVERS-PALB DISPLAY DRIVERS-BIT SLICE-BIPOLAR MEMORY AND MUCH MORE.	
LIN APPLIC	17.00
SORRY SOLD OUT	
LINEAR DATA 2 VOLS	
PER PAIR	20.00
THE FINEST COLLECTION OF DATA AND TYPICAL APPLICATIONS ON OP AMPS, REGG COMPARATORS, REFERENCES, INSTRUMENT AMPS, ANALOG SWITCHES, SAMPLE & HOLD, BUFFERS, SPECIAL FUNCTION, AUDIO AND SPEECH DEVICES EVER PUBLISHED.	
LOGIC	9.95
COVERS 7400, 74L, 74H, 74LS, 74S PLUS A WIDE RANGE OF PROPRIETARY PARTS.	
TRANSISTOR	7.00
WHO NEEDS TRANSISTORS? APPARENTLY EVERYONE. THIS BOOK INCLUDES 2N, PN, NJ, TIP, FETS ALL IN ONE HANDY VOLUME.	
VOLT REGUL.	9.25
NOT REALLY A DATA BOOK, MORE A DESIGN TEXT ON POWER SUPPLY CONSIDERATIONS, HEAT SINKING AND POWER DISSIPATION.	

#### AD/DA

ADD3501	12.00
3 3/4 DIGIT DVM LED OUTPUT	
DAC0808	2.25
8 BIT D TO A	

#### HIGH POWER SPECIALS

NEC701	POA
800 VOLT, 500 AMP DIODE	
BTY99-600R	50.00
600 VOLT, 100 AMP SCR	

#### OPTO

MA1026ALR	27.00
TIME/TEMPERATURE MODULE	
DL1416	36.00
4 DIGIT ALPHA NUMERIC DISPLAY MODULE WITH INBUILT DECODER/DRIVER.	
NSM39152	9.95
10 SEGMENT BARGRAPH MODULE ALL GREEN WITH INBUILT LOGARITHMIC DRIVER.	
NSL4855	0.15
RED 5 MM	
NSL4955	0.20
GREEN 5 MM	
NSL5086	0.15
RED 3 MM	
TIL313	1.50
4.3" COMMON ANODE WITH RIGHT HAND DECIMAL POINT.	
RED BEZEL	1.95
4 DIGIT 0.9" BEZEL WITH INTEGRAL BLACK SURROUND.	
OTHER BEZELS ALSO AVAILABLE PLEASE ASK.	
<b>DISCRETE</b>	
PK40F	2.50
400V 12AMP BRIDGE	
1N914	0.05
OLD OLD FAVOURITE SIGNAL DIODE	
2N2222A	0.48
NPN GENERAL PURPOSE TO-18	
2N2904	0.40
PNP GENERAL PURPOSE TO-18	
2N3019	0.69
NPN MEDIUM POWER TO-5	
2N3053	0.64
NPN MEDIUM POWER TO-5	
2N4032	0.64
NPN MEDIUM POWER TO-5	
2N4360	0.60
VERY POPULAR FET	
2N5485	0.70
MFT/FM TO-92	
2N5656	0.92
NPN POWER TO-18A	
2N6707	0.49
NPN MEDIUM POWER TO-92 PLUS	
PN3563	0.18
NPN LMF TO-92	
PN3643	0.18
NPN MEDIUM POWER TO-92	
TIP3055	1.20
NPN POWER TO-220	

specialising in electronic components for the professional and hobbyist.

# VARISTORS PROTECT LOW VOLTAGE CIRCUITS

**F**abricated from zinc oxide, GE-MOV II varistors can protect sensitive, low voltage devices like microprocessors, from transient voltages that can cause malfunctions and failures.

By increasing the size of the material's grains, General Electric was able to obtain a low voltage rating without making the metal-oxide wafer too thin and thus too fragile to make. Each grain represents a potential of between two and three volts.

The devices are suitable for use in data-communications systems, business machines, elec-

tronic games, personal computers and also instrumentation systems.

The company claims that these zinc-oxide varistors perform better than silicon devices in overstress situations, continuing to deliver a degree of functional transient protection even when pushed beyond normal limits.


The low-voltage device, the

V8ZA1, is rated for protection against 0.4 J, 100 A transients. At a 1 mA test current for an 8 to 20 second duration, the voltage suppressor has a 22 V maximum clamping voltage.

Also available is a high-energy GE-MOV II varistor, rated to 70 000 A and 1000 J. This device is available in 13 voltage ratings from 420 to 2800 V and 560 to 3500 V dc.

For further information contact General Electric, P.O. Box 174, Willoughby NSW 2068. (02)888-8111.

## PHILIPS MATCHES INTEL'S 8051

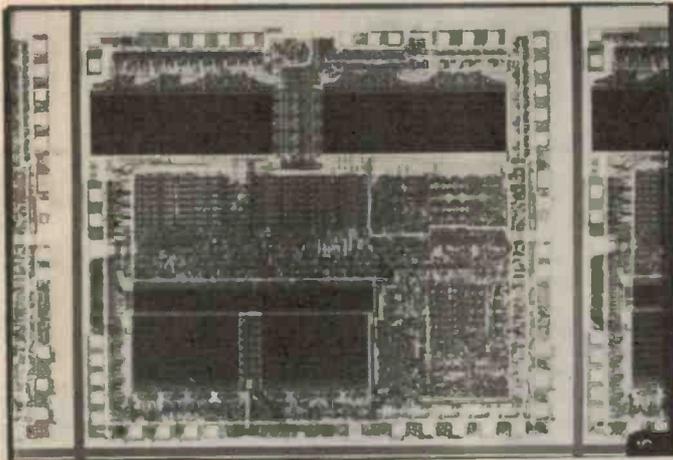

An alternate source for Intel's 8051 is offered by Philips complementing its present family of MAB8048H 8-bit microcontrollers.

This latest addition to the range, the MAB8051, offers extended on-chip memory capacity, enhanced architecture and a larger instruction set.

Fabricated in HMOS, it is

now available in a single, 40-pin plastic DIL package (SOT-129) from Philips' Hamburg factory.

The MAB8051 8-bit microcontroller is a single chip device designed for stand-alone use in real-time applications such as instrumentation, industrial control and intelligent computer peripherals.

Hardware features of the

MAB8051 include 4K of programmable, non-volatile ROM (extendable to 64K); 128 bytes of volatile RAM for data storage (extendable to 64K); four 8-bit ports and 32 I/O lines; two 16-bit timer/event counters; a five-source, two-priority level, nested interrupt structure; a full duplex serial port and on-chip oscillator and timing circuits.

Extra capability, in the form of standard TTL compatible memories and logic can be added.

Architectural enhancements allow the device to function as an arithmetic processor, with facilities for both binary and BCD arithmetic plus bit-handling capabilities.

To further enhance the series, both a CMOS version and a CPU only version (needing external ROM) are expected early in 1984.

For further information contact Philips Electronic Components & Materials, 67 Mars Road, Lane Cove NSW 2066. (02)427-0888.

## CMOS 14 DIGIT LCD DISPLAY DRIVER

**S**harp's new programmable SCMOS LCD driver interfaces serially with your CPU to directly control and drive liquid crystal displays in static or dynamic mode.

The LH5008 may be operated in 1/2, 1/3 or 1/4 duty cycles to yield up to 14 digits of a 7-segment display or eight digits of a 14-


segment display.

Features include a blinking mode and an 8-bit serial character input.

The 7-segment drive mode outputs numerics 0-9 and six symbols, whereas in the 14-segment driver mode, 36 alphanumeric and 13 symbols may be addressed.

Packed in a compact 60 pin flat pack, the LH5008 is compatible with the UPD 7225.

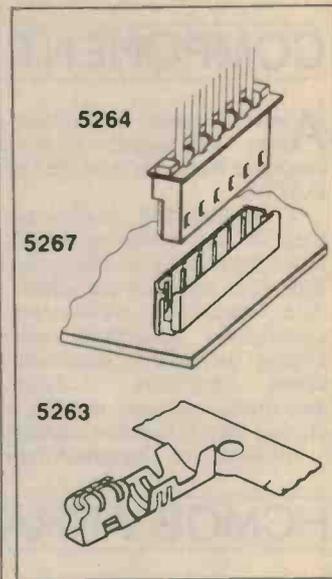For further details contact Philip Jackson or Joanne Oxley, Daneva Australia Pty Ltd, P.O. Box 114, Sandringham Vic 3191. (03)598-5622.



## LOW PROFILE PC BOARD CONNECTOR

**L**atest in the Molex range, distributed in Australia by Utilux, is a very low profile 2.5 mm centreline Mini-Spox connector housing of special interest for manufacturers and assemblers of radios, stereos and video cassette recorders.

Only 8 mm high and 3.9 mm wide, the 94V-0 nylon connector housing has moulded-in pull tabs, polarisation, frictionlock, and provides for 2-15 circuits in line. Catalogue number is 5264.

Also released for use with the 5264, is the 5263 spring-box type crimp terminal. Of pre-tinned phosphor bronze, the pin contact area is inside the box, which prevents contamination from handling during the assembly process. Available in continuous strip or loose form, it accommodates AWG 22-28, with an insulation diameter of 1.9 mm maximum.

An assembled connector made up of the 5264 housing and the 5263 terminal, mates with the Molex 5267 straight or the Molex 5268 right-angle, fully-shrouded Mini-Spox headers.

Both hand and semi-automatic crimp tooling are available from Utilux.

For further information contact Utilux Pty Ltd, 14 Commercial Road, Kingsgrove NSW. (02)50-0155. ▶

## COMPONENT CATALOGUE


A new, 376 page data conversion component product catalogue has been produced by DATEL.

It contains full engineering data on the following monolithic, hybrid and modular products: A/D and D/A converters, data acquisition subsystems, sample-and-hold amplifiers, operational amplifiers, instrumentation amplifiers, isolation amplifiers, analogue multiplexers and special function circuits.

Products are organised into

quick selection tables that are arranged by function and performance to ease product selection for any given application. Complete data sheets are included for key products along with tutorial information and an ordering guide.

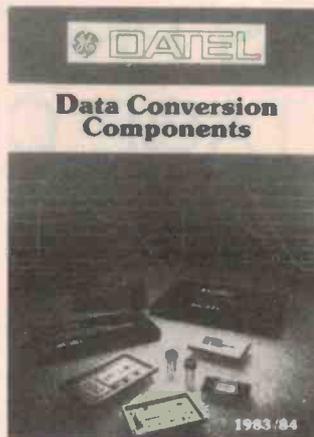A copy may be obtained by request on an official organisation letterhead to: Elmeasco Instruments Pty Ltd, P.O. Box 30, Concord NSW 2137. (02)736-2888.



## OP AMP

Teledyne claims that its new chopper stabilised op amp, the TSC 7650 practically removes offset voltage error terms from system error calculations.

The 5  $\mu$ V maximum Vos specification represents a 15 times improvement over the industry standard OPO7E and the 50 nV/ $^{\circ}$ C offset drift is over 35 times lower than the OPO7E, they say.

The TSC 7650 uses an elegant feedback technique whereby an auxiliary on-chip amplifier continually senses input versus output errors on the main amplifier and supplies a correction signal.

The IC features input offset voltage typical of 0.7  $\mu$ V, input bias of max 10 pA, an open loop gain of 120 dB min, a 20 mW power drain, a 2.5 V/ $\mu$ s slew rate and is accommodated in eight pin or 14 pin DIL packs.

For further information contact Promark Electronics, 6 Clarke St, Crows Nest NSW. (02)439-6571.

## HCMOS ARRAYS

Motorola has introduced a family of four HCMOS Macrocell Arrays; the HCA6348 with 4860 equivalent gates, the HCA6324 with 2295 equivalent gates, the HCA6312 with 1200 equivalent gates and the HCA6306 with 648 equivalent gates.


The arrays are processed in three micron silicon gate CMOS two layer metal technology, which yields typical loaded on-chip gate delays of 2 ns. Input buffers operate at either TTL or CMOS voltage levels and output buffers are capable of driving ten LSTTL loads.

National Semiconductor is Motorola's fully compatible alternate source for HCMOS, ALS and ECL Macrocells Arrays.

A variety of standard packaging is available ranging from 28 pin DIL packages to 124 terminal leadless chip carriers, pin grid arrays and chip carriers.

For more information contact Motorola Semiconductor Products, 250 Pacific Hwy, Crows Nest NSW 2065. (02)438-1955.
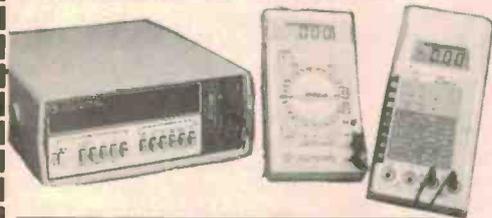
### DIGITAL MULTIMETERS THAT MEASURE CAPACITORS




MODEL	7601	7605	7901	7905
Test/measure	Transistor		Capacitors	
DC Volt	100 $\mu$ V-1000V		100 $\mu$ V-1000V	
Basic Accuracy	.1%	.5%	.1%	.5%
AC Volt	100 $\mu$ V-750V		100 $\mu$ V-750V	
Basic Accuracy	.5%	1%	.5%	1%
DC Current	1 $\mu$ A-10A		1 $\mu$ A-10A	
Basic Accuracy	.5%	.5%	.5%	.5%
AC Current	1 $\mu$ A-10A		1 $\mu$ A-10A	
Basic Accuracy	.5%	.5%	.5%	.5%
Resistance	.1-20Meg		.1-20Meg	
Basic Accuracy	.2%	.5%	.2%	.5%
Hfe @ 10 $\mu$ A	0-1000		##	##
Capacitance	##	##	1pF-20 $\mu$ F	
Basic Accuracy	##	##	.5%-1.5%	
Diode test	1mA	1mA	1mA	1mA

PRICE 112.50 89.50 125.50 101.90

6 month warranty. Test leads, carry case and instruction manual supplied.

P/P NSW \$3.60 VIC \$4.50 All others \$5.50


### SWITCH MODE POWER SUPPLIES

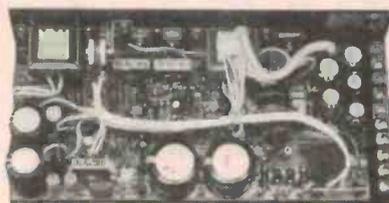

- Single & Multiple outputs to 650 watts
- Open and enclosed styles
- Models to suit Apple and other computers.
- Wide range to select from.

PRICE FROM \$85.00

### S100 SYSTEM PRODUCTS

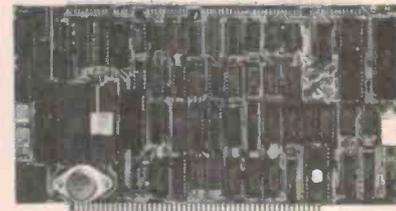

- 8/16 Bit dual processor uses NSC-800/8088 runs all 16 bit software without forsaking your 8 bit software.
- 256K Static RAM 8/16 bit requests each 64K block can be one of 256 addresses up to 16Mb.
- 4 Mb single board disc emulator complete with print spooler.
- 64K Static RAM boards.
- 6Mhz single board computer with 128K bank select memory and disc controller. Run CP/M 3.0 (plus).
- Many other S100 products available.

## LAMRON PTY. LTD.

P.O. Box 438,  
Ryde, N.S.W. 2112  
85-2599, 85-6228

20 Stamford Ave.,  
Ermington, 2115  
Tlx. AA71551 Lamron.

My cheque/order form for ..... is enclosed.

Please send me product data sheets. (I enclose 4 stamps).

Please include me on your new product mailing list. I am mainly interested in systems for:  
 Hobby,  Industrial use,  Education,  Process control,  Business  Other.

I wish to order .....

Please debit my Bankcard No. ....

Name ..... Expiry Date .....

Address .....

Signature .....



# C. Itoh PRINTERS

FROM ROD IRVING ELECTRONICS



### Pro/Writer Printer 8510

**Print Features:** Number of columns—136 col. max. Print Speed—120 CPS. Print Direction—Single-directional and Bidirectional, Switch Selectable. Throughput Speed—From 44 to 152 lpm. Character spacing (max. number of columns per line)—Pica 10 CPI (80), Double Width 8 CPI (60), Compressed Font 17 CPI (136), Double Width 8 CPI (68), Elite 12 CPI (96), Double Width 6 CPI (48), Proportional Double Width Proportional Line Spacing—Variable to 1/16". Print Width—203 mm (8") max.  
**Forms Type:** Fan Fold Roll or Cut Sheet. Width—113 mm to 254 mm (4.5" to 10.0"). Total Thickness—0.05 to 0.28 mm (0.002" to 0.011"). Number of Copies—Original + 3 copies normal.  
**Form Feed:** Method—Tractor or Friction. Form Loading—Either rear or top.  
**Interface—Serial:** Method—EIA RS232-C and 20mA (40 & 60mA switchable option). Current Loop Serial Interface. Baud Rate (BPS)—110, 300, 600, 1200, 2400, 4800, 9600.  
**Transmitting Method—**Half Duplex. Synchronous—Asynchronous.  
**Interface—Parallel:** Method—TTL compatible. 7-bit, parallel interface. Control Signals—ACK, BUSY, SELECT, DATA STB, INPUT PRIME FAULT, INPUT BUSY, BAPER EMPTY.  
**Instruction Codes—**(ASCII): CR, LF, VT, FF, CAN, SO, SI, DEL, DC1, DC2, DC3, DCA, GS, BS, US, FS, EM; GRAPHIC SYMBOLS; BIT GRAPHICS.  
**Error Detection:** (1) Parity (VRC)—Odd, Even, No-parity, Switch selectable. (2) Framing Error—Stop bit check. (3) Overrun Error—Error is detected when data are received before the previous data have been processed.  
**Physical dimensions:** 395 mm W x 130 mm H x 285 mm D (15.7" W x 4.7" H x 11.2" D).  
**Weight:** 8.5 kg (18 lbs. 12 oz.)

tax exempt

P\* \$795 (\$695)  
S\*\* \$1095 (\$945)

### Model 1550

The Model 1550 is a compact desk-top dot matrix serial impact printer used for data communication terminals, hard copy of CRT displays, peripheral terminals for minicomputers and microcomputers, and small-sized business systems.  
**The character format is a dot matrix of 7(8) x 9(8) or 8(8) x 9(8).**  
**Print speed is 120 characters/second. Up to 136 characters can be printed per line at 10 CPI.**  
**Its main features are:** • Compact desk-top dot matrix printer • 136-column print • Lightweight • Low power-consumption • High-quality print • Bit image graphics • Graphic Symbols • Prints in six different languages • High reliability • Low cost.

P\* \$1095 (\$995)  
S\*\* \$1395 (\$1295)

### F-10 Printmaster Daisy Wheel Printer

**Print Speed:** 40 CPS. **Print Method:** Static Print Impact. **Number of Printable Columns:** 136. **Variable Character Spacing:** 1/120 inch (minimum). **Line Spacing:** 1/68.  
**Return Time:** 300 msec. **Line Feed Time:** 40 msec. **Paper Width:** 406 mm (maximum).  
**Print Characters:** 96. **Printwheel:** Industry Standard 96 Character Wheel. **Interface:** Industry Standard 8-bit Parallel. RS232-C Compatible, X-ON, X-OFF, 12-bit Ounce and Diablo Compatible. **Dimensions:** 574 mm W x 405 mm D x 153.5 mm H (22.5" W x 15.9" D x 6" H). **Weight:** 14 kg (30.8 lbs.) with cover and power supply. **Noise:** Less than 65 Db (1M from Plateau, A Scale).

P\* \$1950 (\$1675)  
S\*\* \$2100 (\$1775)


### NEW VIDEO MONITORS

Get a clear honest image!

Computer data and graphic displays never looked better, brighter, sharper
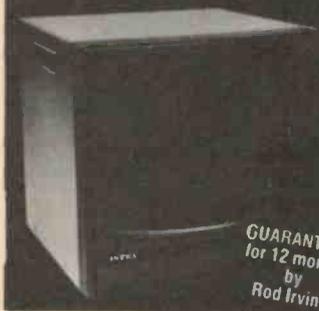
### High Resolution

- Recommended Display Characters: 1920 (80x24).



GUARANTEED for 12 months by Rod Irving

SCHOOL AND CLUB BULK BUYS  
Please ring for pricing

- High quality, non-glare CRT
- Compact and Lightweight with all Controls inside Front Panel.
- All units 100% Factory Burned in.
- 900 lines centre resolution
- Suitable for Apple II and other computers. (Apple is a registered trademark of Apple Computer Computer, Inc.)
- Green or Orange Phosphor available.
- 18 MHz
- First Shipment arriving middle of June, 1983.
- Direct Import Price for June

Green Phosphor \$199 (\$179 Exempt)  
Orange Phosphor \$229 (\$189 Exempt)


GREAT VALUE Ex Stock

## 'THE PRINTER PEOPLE' SPECIALS

Just Arrived

A NEW PRINTER NOW!

## CP-80/1, 80-COLUMN IMPACT PRINTER

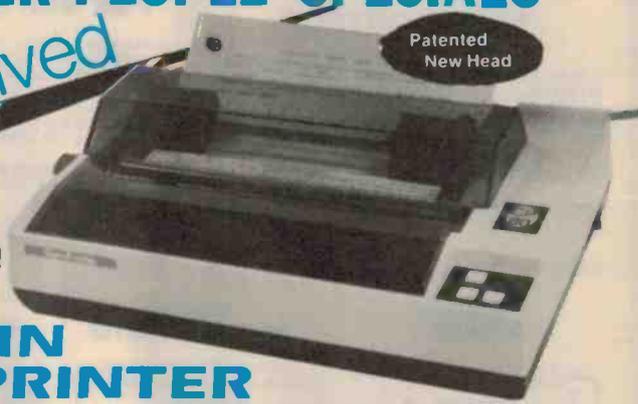

### SPECIFICATIONS

#### Functional Specifications

**Printing method —** Serial impact dot matrix  
**Printing format —** Alpha-numeric — 7 x 8 in 8 x 9 dot matrix field. Semi-graphic (character graphic) — 7 x 8 dot matrix. Bit image graphic — Vertical 8 dots parallel horizontal: 640 dots serial/line  
**Character size —** 2.1 mm (0.083")-W x 2.4 mm (0.09")-H/7 x 8 dot matrix  
**Character set —** 228 ASCII characters. Normal and italic alpha-numeric fonts, symbols and semi-graphics  
**Printing speed —** 80 CPS. 640 dots/line per second  
**Line feed time —** Approximately 200 msec at 4.23mm (1/6") line feed.  
**Printing direction —** Normal — Bidirectional logic seeking. Superscript and bit image graphics — Unidirectional, left to right  
**Dot graphics intensity —** Normal — 640 dots/190.5mm (7.5") line horizontal. Compressed characters — 1280 dots/190mm (7.5") line horizontal  
**Line spacing —** Normal — 4.23mm (1/6") and Programmable in increments of 0.35mm (1/72") and 0.18mm (1/216")  
**Columns/line —** Normal size — 80 columns. Double width — 40 columns. Compressed print — 142 columns

Compressed/double width — 71 columns.

The above can be mixed in a line  
**Paper feed —** Adjustable sprocket feed and friction feed  
**Paper type —** Fanfold. Single sheet. Thickness — 0.05mm (0.002") to 0.25mm (0.01"). Paper width — 101.6mm (4") to 254mm (10")  
**Number of copies —** Original plus 3 copies by normal thickness paper

#### Mechanical Specifications

**Ribbon —** Cartridge ribbon (exclusive use), black  
**MTBF —** 5 million lines (excluding print head life)  
**Print head life —** Approximately 30 million characters (replaceable).  
**Dimensions —** 377mm (14.8")-W x 295mm (11.6")-D x 125mm (4.9")-H incl. sprocket cover.

Parallel CP80 \$449  
Serial CP80 \$599

\* Parallel Interface \*\* Serial Interface

ERRORS AND OMISSIONS EXCEPTED

425 High St., Northcote, Vic. 48-50 A'Beckett St., Melb., Vic.  
 Phone (03) 489 8866, (03) 489 8131, Mail Order Hotline (03) 481 1436  
 Mail orders to P.O. Box 235 Northcote 3070 Vic.  
 Minimum P & P \$3.00.

Please address tax exempt, school, wholesale, and dealer enquiries to:

**RITRONICS WHOLESALE**

1st floor 425 High St. Northcote 3070 (03) 489 7099 (03) 481 1923 Telex AA 38897



Bankcard mail orders  
**ORDER FORM**  
 Please Debit my Bankcard

No. ....  
 Expiry Date .....  
 Name .....  
 Signature .....

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

## QUALITY VIDEO KITS

Video has been booming for quite a while, finally a range of video accessories in kit form.

Two video amplifiers for both VCR and Computer use, a brand new Video Enhancer and our popular VCR Stereo Synthesizer. All four represent outstanding value for money and all are assembled with Altronic's Extra Care.

### VIDEO AMPLIFIERS



**DISTRIBUTION TYPE**  
Simple, low-cost project will allow you to drive five video monitors from one source, such as a video cassette recorder or a computer. Great for piping video around the house, or for clubs meetings when screening lectures etc. or for computer demonstrations.

★ THE ALTRONICS KIT includes all components as specified by ETI plus all power supply components.

K5830..... Only..... **\$45.00**



### SINGLE OUTPUT

#### INVERSE AND NORMAL OUTPUT

Brilliant new kit from EA, Super cheap and Super Effective. Whilst our K5830 is suitable primarily for VCR use this video amplifier is best suited to use with computers. The EA documentation supplied is extremely well written and provides details for installation into television sets.

NO MORE SMEARY COLOURS, SIGNAL BEATS OR RF INTERFERENCE

NOTE ★ NOT SUITABLE FOR USE WITH LIVE CHASSIS TV SETS.

K5850..... **\$14.95**

### FUNCTION GENERATOR



The most essential piece of test gear second only to a good multimeter on any hobbyist's bench is some kind of audio signal generator. This design utilizes the latest circuit techniques to produce stable, low distortion waveforms.

A 8 digit frequency readout (eliminates time-consuming calibration) — typical accuracy ± 2% — 3 overlapping ranges 10, 100, 1000 Hz nominal Output — continuously variable 10V — 2.5V p-p Distortion — sine wave — less than 0.7% at 1kHz Linearity — triangle wave — better than 1% at 1kHz Squarewave rise time — 5V/μs maximum output — Amplitude stability — better than 0.1db on all ranges.

With the exception of the display all components mount on a single PCB making this kit suitable for all constructors.

K2505..... **\$85.00**

### DIGITAL CAPACITANCE METER



with Deluxe Instrument Case

NEW DELUXE FINISH  
We are pleased to announce the release of the Digital Capacitance kit housed in our Deluxe 40480 ABS Instrument Case. This superb Test Instrument kit now compliments our top selling Digital Frequency Counter and Function Generator Project kit. Electronics Australia Project. Measures capacitance of both polarized and non-polarized capacitors from 1 picofarad to 99.99 microfarads in 3 ranges. Check values of unmarked capacitors, especially those little trimmers that are never coded. Select precise values for filters and timing networks within ease.

EXCLUSIVE TO ALTRONICS

Each kit includes precision measured capacitors for accurate calibration of each range.

K2521..... **\$55.00**



### VIDEO ENHANCER

Here's a simple but effective Video Enhancer that is super easy to build at a fraction of the cost of commercial models. Unit sharpens picture detail, and can actually improve the quality of a copy by amplifying the top end of the video signal.

#### AT LAST A VIDEO ENHANCER KIT

K5825..... **\$35.00**

### ENJOY THE PLEASURES OF STEREO SOUND

(See EA Sept. 1982)



### STEREO SYNTHESIZER FOR VCR'S AND TUNERS

Synthesize realistic stereo from virtually any monophonic source by simply connecting this unit between the source and your stereo amplifier.

- Quality Phillips MN3001 (not second source dropout).
- Provision for 2 different signal sources.
- Selection of either source via front panel switch.
- Normal or stereo sound selection.
- Complete kit includes all hardware, cables etc., even solar.

Important ★ beware of Kitset suppliers who sell this kit for less ★ you get less!

K5810..... **\$55.00**

### 7 DIGIT FREQUENCY COUNTER



#### UNBELIEVABLE 0.005% ACCURACY

Frequency and Period measurement to 500 MHz (with optional prescaler) High input sensitivity. Professional unit at a fraction of the cost of built up units. IC sockets provided throughout. Low age rate 10 000 MHz XTAL. Quality ABS plastic case with deluxe front panel. Specified I.S.

K2500..... **\$119.50**

PRESCALER

K2501..... **\$26.00**

DECIMAL POINT

K2502..... **\$7.50**

## THE EVER POPULAR MUSICOLOUR IV EA PROJECT



K5800..... **\$89.50**

Combination Colour Organ and Light Chaser. Four channel colour organ, internal microphone or connect to speakers for colour organ operation. (The lights connected to each channel pulse in beat to the music proportional to portion of frequency spectrum concerned.) Four chaser modes forward and reverse. Output lamp load capacity a massive 2400 watts — that's 100 party globes. Full instructions and every last nut and bolt included. Great for parties, shop signs, display windows etc.

## POWER SUPPLIES

If you're thinking of buying a power supply then buy from us, we are the experts on power supply kits and carry a supply to suit most enthusiast and professional requirements. READ ON.



### BENCH STANDARD

- 3-30V Output @ 1 Amp.
- Fully Regulated. Fully Protected from Thermal Overload and Short Circuits.
- Based on EA Design.

K3200..... **\$42.50**

- All the features of above PLUS Current Limit.
- ETI Design.

K3205..... (PICTURED)..... **\$49.50**

### DUAL TRACKING

- ± 1.3 to ± 22v Output @ 2 Amps. + 5v @ 0.9 Amps.
- Fully protected.
- 10 turn pot enables Voltage adj. to within 10mv.
- EA Design (March '82).

K3220..... **\$89.50**

### HIGH CURRENT

#### MICROCOMPUTER PS

- + 5 Volts @ 3 Amps. + + 12 Volts @ 2 Amps.
- - 12 Volts @ 200 milliamps.


This universal design has enough grunt to power most disk drives.

K3350..... **\$59.50**

13.8 VOLTS @ 10 AMPS HAM'S & CBER'S  
Save the expense of a Mains Powered Rig.

K3250..... **\$89.50**

### HIGH CURRENT — DUAL METERING

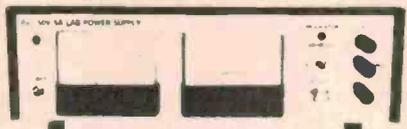

#### EA SWITCH MODE DESIGN

- 2-50 Volts at massive 175 Watts.
- CLEVER DESIGN — a fully mains isolated supply with a "Switchmode" low voltage circuit.
- Easy to build.

K3300... (EA MAY, JUNE '83)... **\$139.00**

K3301... (10 TURN VOLTAGE CONTROL OPTION) ... **\$10.00**


K3302... (± 12V OPTION) ... (EA JULY '83)... **\$12.50**

#### ETI SERIES REGULATOR DESIGN

- 0-40 Volts @ 5 Amps — that's 200 Watts.
- Current limiting 0-5 Amps variable.
- Specifications Second to None.
- Free from the hum and noise sometimes associated with other techniques.

#### A PROFESSIONAL SUPPLY

K3325..... (PICTURED)..... **\$175.00**

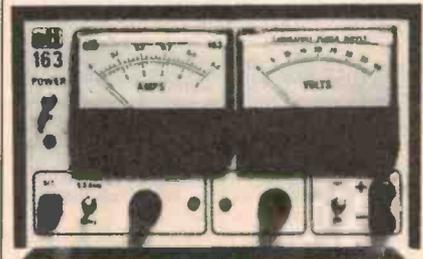

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

# The program bug debugger

Ever burnt a program into an EPROM and found it wouldn't run? Without a logic analyser it's nigh on impossible to debug. This project costs far less than a logic analyser and gets you out of the jam. The Bug Debugger provides 'mirror image' RAM (battery-backed if you like), permits the addition of program breakpoints and interception of R/W control. Lots of other uses, besides.

Graeme Teesdale

MANY MICROCOMPUTER programmers would have, at some time or another, experienced the situation where, having written a program in CP/M or assembler, burnt an EPROM from the hex listing, placed it in the board and executed a test run — to find nothing has happened!

Shriek, expletive deleted, tearing of hair, pounding of bench, attacking of keyboard, recitation of magic incantations, utterances such as "bother!" and like manifestations of frustration rend the air on such occasions.

Without a logic analyser, it is difficult to debug the unit. However, if you could load the contents of the EPROM into a mirror image RAM where breakpoints can be inserted and R/W control removed, debugging is possible.

This project is designed to produce the hardware for the system which will plug into a standard 2716/2516 EPROM socket. Depending on the microprocessor used, you may need to write a short memory-block move routine. Many micros have such a command in their primitive VDU monitor software.


The project hardware can be used in three ways:

- (1) As a temporary extension socket for existing EPROM.
- (2) For additional RAM, using the extra *chip select*: In this mode the existing EPROM is placed into the debugger board so that the flying lead CS2 can be inserted into the original socket.
- (3) As a mirror RAM debugger. In this mode the chip select switch is set to RAM position and the R/W switch off. The result is a volatile ROM (non-volatile if battery-backup is used).

With battery backup, the program can be stored in the RAM for many months as the current drain is very, very low (less than  $5 \mu\text{A}$ ; the prototype was measured at  $3.2 \mu\text{A}$ ).
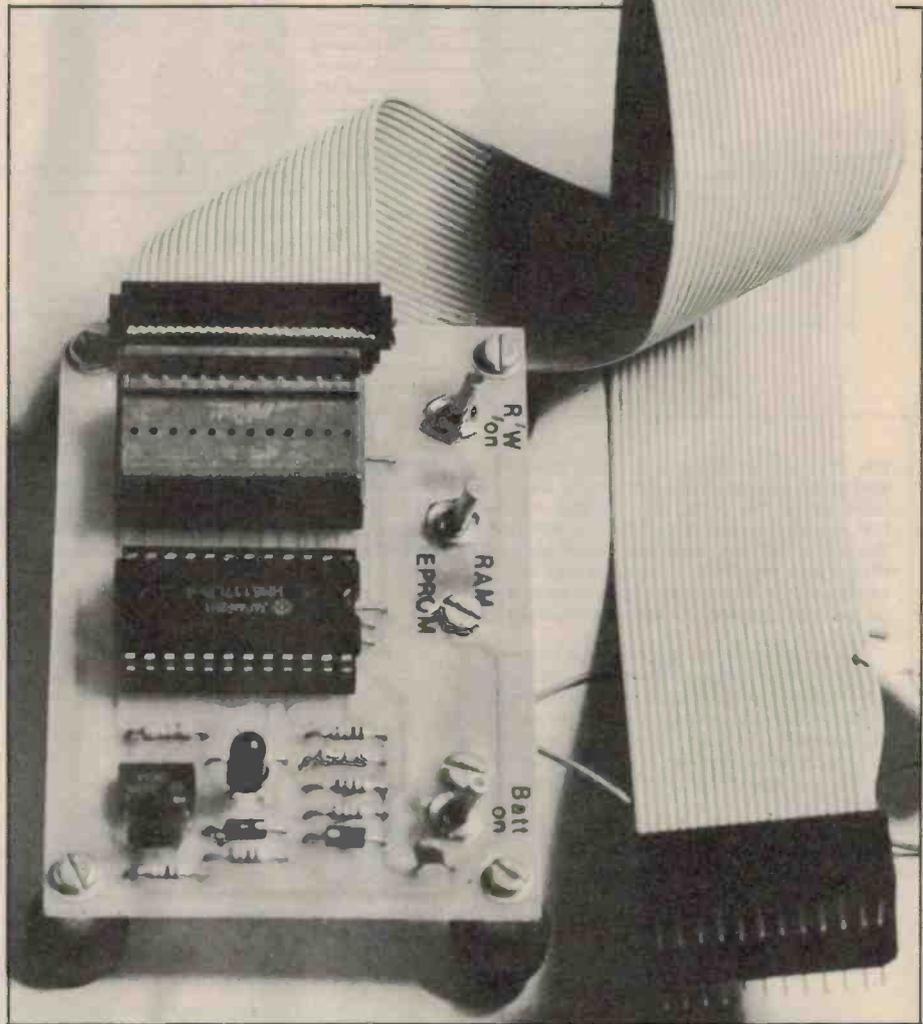
## Design details

The circuit makes use of a Hitachi CMOS 2K x 8-bit RAM chip, type HM6117LP, and an Intersil micropower under/over-voltage detector, type ICL7665. The HM6117LP is a version of the HM6116LP, the previously used *output enable* line (OE), pin 20 is a second *chip select*, CS2, in the 6117, and acts as a *de-select* pin on power-down.




With the 6116, on power-down it is necessary to have pullup resistors on the address and data lines, determining input status, to obtain minimum standby current. Also, additional gating of WE and CE1 is required. The very low price differential between the 6117 and the 6116 made the former the obvious choice for this project.

The ICL7665 contains two individually programmable voltage detectors on a single chip, referenced to an internal 1.3 V source. The outputs from the two voltage comparators drive four open-drain FETs.

Out 1 (pin 1) and Out 2 (pin 7) are N-channel. Hyst 1 (pin 2) and Hyst 2 (pin 5) are P-channel.

Each section is independent of the other but both use the same 1.3 V reference. The input impedances of the two inputs, Set 1 and Set 2, are each extremely high, with typically 10 femptoamps (0.01 nanoamps!) leakage current. Total current drawn by the 7665 is very low, typically  $2.5 \mu\text{A}$ . The output MOS transistors are capable of sinking and sourcing LED currents, a fact I made use of here to indicate battery voltage. ▶

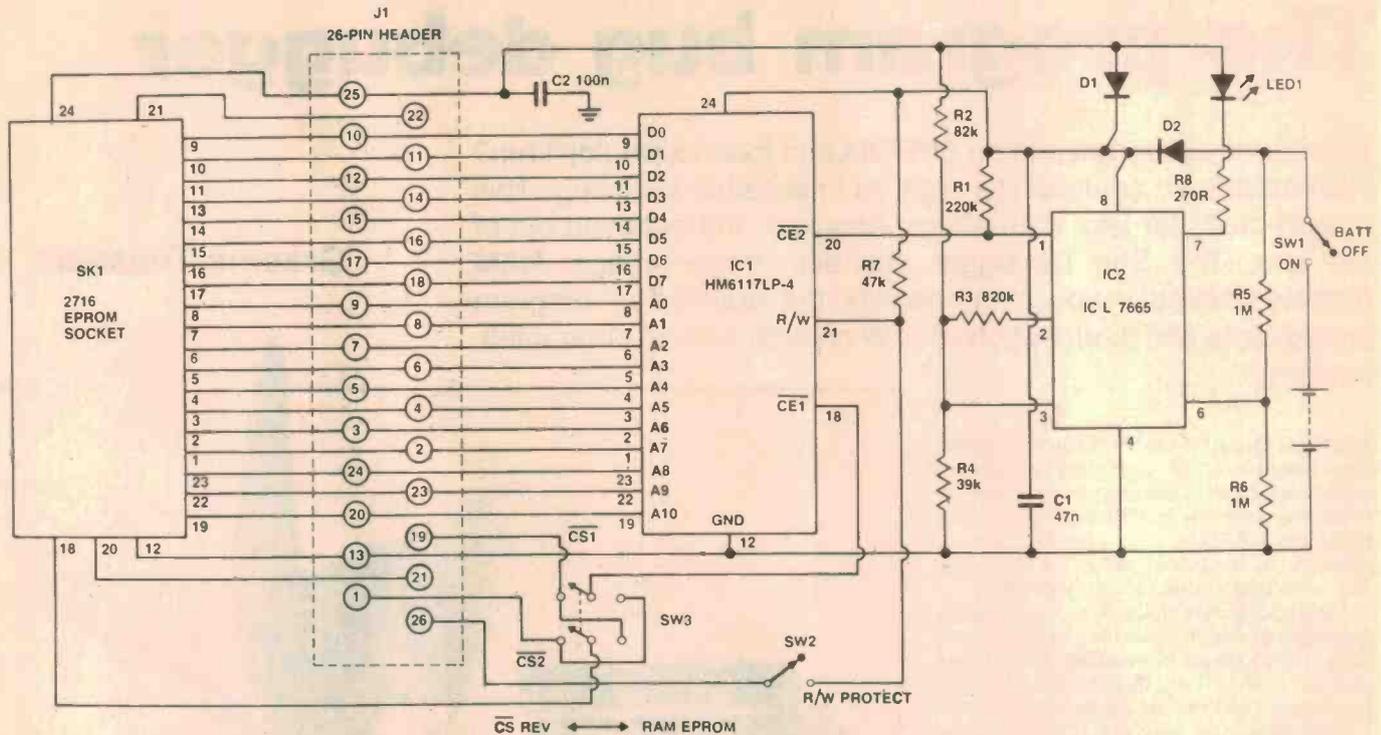

## HOW IT WORKS — ETI-656

The 2716 socket SK(1) is a direct copy of the socket the project plugs into on the microcomputer board. The RAM, J(1), requires additional R/W and chip select lines from the main board. The rest of the data and address lines are bussed across from the EPROM socket except for pin 20 and pin 18. Pin 20 is controlled from an output on the over-voltage detector and is normally at logic '0'.

The set input on the over-voltage comparator is taken to the centre of the voltage divider (R2-R4) between the +5 V rail and 0 V. Hysteresis is added to the over-voltage comparator to reduce the possibility of false switching or oscillations as a result of fluctuations in the supply rail down to the top switching point. The upper switch voltage is:

$$V_H = \frac{R4 + R2}{R4} \times 1.3$$

$$= \frac{82k + 39k}{39k} \times 1.3$$

$$= 4.03 \text{ V}$$

The lower switching point is below the voltage where the Out 1 MOS transistor is off. Resistor R1, in this case, is used as a pullup resistor, pulling pin 20 of IC1 up to the supply rail. For data retention, pin 20 must be within 0.2 V of the voltage on the supply rail — pin 24 of IC1. The lower switching point is:

$$V_L = \frac{R4 + R2 + R3}{R4} \times 1.3$$

$$= \frac{39k + 82k + 820k}{39k} \times 1.3$$

$$= 3.78 \text{ V}$$

The undervoltage comparator is used to monitor the battery voltage. When it's below the setpoint, the Out 2 MOS transistor is on, switching the LED on. The LED only indicates battery condition when the project is plugged into the EPROM socket on a micro board and is deriving supply from there.

The under-voltage trip voltage is given by:

$$V_U = \frac{R6 + R5}{R6} \times 1.3$$

$$= \frac{10^6 + 10^6}{10^6} \times 1.3$$

$$= 2.6 \text{ V}$$

Diodes D1 and D2 are used as blocking diodes, isolating the +5 V and battery supplies from one another. The only precaution recommended by the manufacturers of the ICL7665 (Intersil) is decoupling very close to the supply pins.

Under certain circumstances, like very rapidly increasing power supply input, the four-layer PNP type structure of the chip can latch-up, drawing excessive supply current. The problem is more likely to happen when the Debugger's battery is switched on before the Debugger is plugged into the microcomputer's power supply. Generally, growth and decay of the micro's +5 V supply would have a much longer time constant, presenting no problem.

## Construction

Before commencing assembly, check the printed circuit board for shorts between tracks — particularly the data and address lines, no matter whether you've purchased a ready-made board or etched your own. A visual check alone may not show hairline shorts, so use an ohmmeter or continuity checker. Also check that all the holes have been drilled to the correct diameter.

I used a Scotchcal label to indicate the switch functions on the board. If you're making your own, do it now. Attach the label to the appropriate position on the

board, which can be seen from the accompanying photograph.

The first thing to do is solder the four links in place. Use 22g tinned copper wire.


Start component assembly by mounting J1, the 26-pin header plug strip, followed by the IC socket and the EPROM socket (SK1). I used a low insertion pressure socket here to avoid problems with pins that might get bent under when inserting an EPROM. After soldering these three components in place it is important to recheck for shorts between data and address lines as board tracks run between pins. If, or when, all is well, proceed by inserting and solder-

ing resistors R1 to R8 in place, followed by capacitors C1 and C2, switches SW1, SW2 and SW3. The switches are wired up with short lengths of tinned copper wire, direct to the pads on the board as shown in the underside wiring diagram.


Next, insert the diodes, D1-D3, ensuring you get them all the right way round. Last of all, insert and solder IC2 in place, making sure that it, too, is correctly orientated.

If you're using battery backup, it is best to check the action of IC2 before proceeding to assemble it.

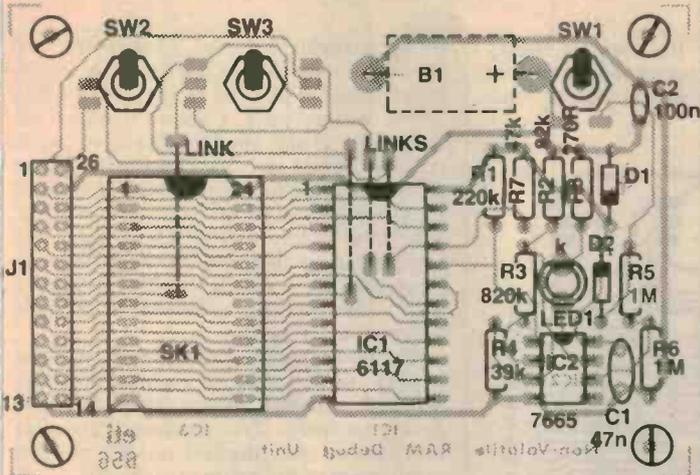
Connect a 5 V source between pins 24 and 12 of SK1 (EPROM socket). IC1 is not



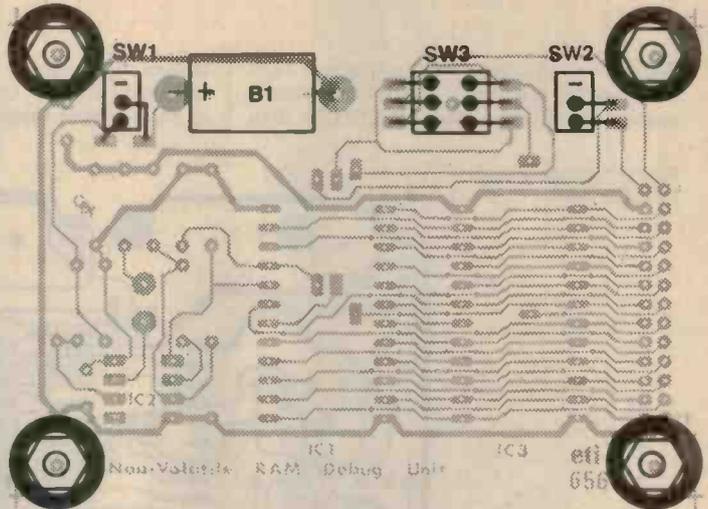
Topside overlay. Showing component placement. Put the links in first of all.



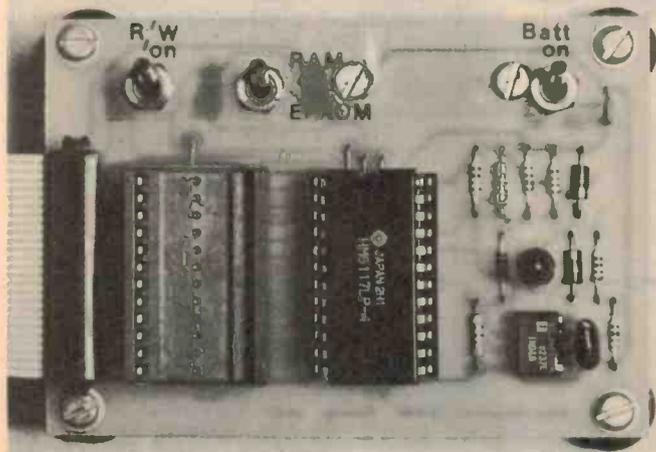Bottomside overlay. Showing switch wiring and battery placement.



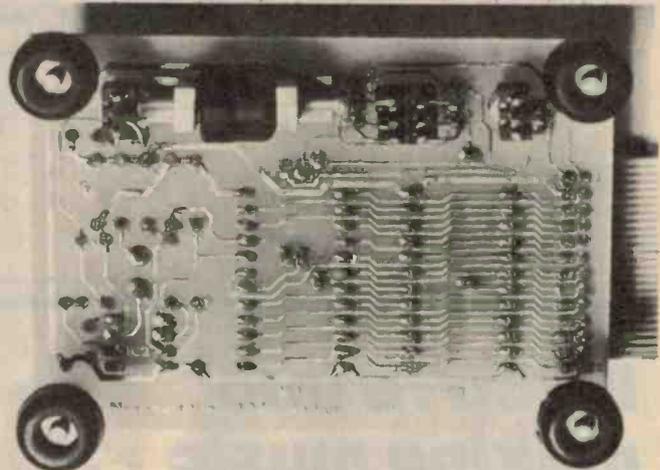
Topside view. Compare with the overlay above.



Bottom side view. Compare with the overlay above.
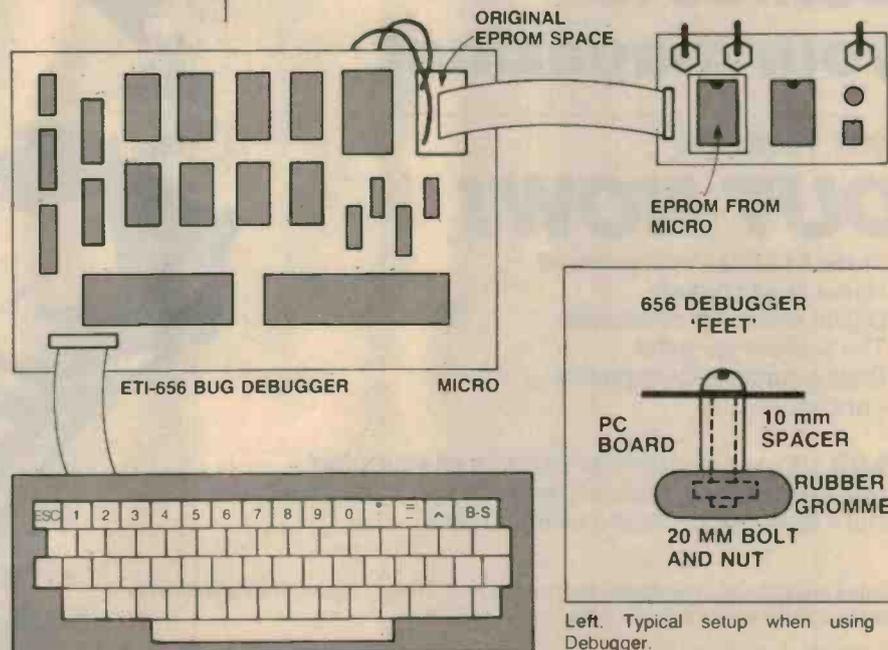
## ETI-656 PARTS LIST

- Resistors**.....all 1/4W, 5%
- R1.....220k
  - R2.....82k
  - R3.....820k
  - R4.....39k
  - R5,R6.....1M
  - R7.....47k
  - R8.....270R
- Capacitors**
- C1.....47n greencap
  - C2.....100n bluechlip ceramic
- Semiconductors**
- IC1.....HM6117LP-4
  - IC2.....ICL7665
  - D1,D2.....1N4001
  - D3.....TIL220R or similar
- Miscellaneous**
- ETI-656 pc board; Scotchcal label; 1 x 24-pin low insert pressure socket (SK1) — Robinson-Nugent type TSN246; 1 x 24-pin IC skt; 26-pin header; 24-pin DIP adaptor plug & cover (R-N type MPB-246, MPC-246-1); 2 x SPST min. toggle switches; 1 x DPDT min. toggle switch; min. 3 V NiCad; 26-way ribbon cable; nuts, bolts, standoffs, grommets.



Left. Typical setup when using the Debugger.

# Project 656

inserted for this test. Now, connect a variable supply, set to 5 V, across the battery pads on the board. Switch SW1 to ON, then


reduce the output of the variable supply until the LED just comes on. Measurement of the variable supply should yield a value

of approximately 2.6 V. Change the two supplies around so that the fixed 5 V supply is connected in place of the variable supply, at the battery pads. Connect a meter between pin 20 and pin 12 (0 V) of IC1. The reading should be very close to  $5 - 0.7 = 4.3$  V. Increase the variable supply from its previously set value of 2.6 V, towards 5 V. When the supply reaches about 4.0 V the meter reading should drop to nearly 0 V. Decrease the variable supply, output to 3.78 V. Pin 20 of IC1 should have changed to about 4.3 V again.


The power supplies can be removed, the battery switch set to OFF and the battery assembly attached to the board, *Observe battery polarity*. The particular assembly arrangements will depend on the physical arrangement of the battery you will be using, so exact construction details are not provided. IC1 can be inserted once the battery is in place. Now make up the cable assembly. A length of 26-way ribbon cable has a 26-pin IDC socket attached at one end. This plugs into J1 on the board. The other end goes to a solder DIP adaptor plug, as can be seen in the accompanying photograph. Flying leads for the CS2 and R/W lines are attached to pins 1 and 26, with small identifying labels stuck to them.

Go debug those bothersome bugs! ●

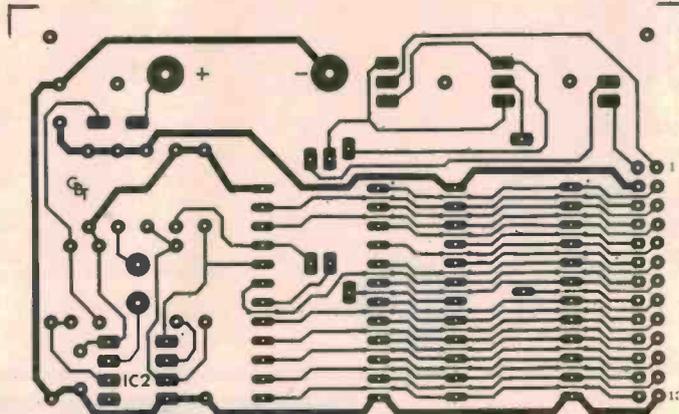Right. Full-size artwork for the pc board.



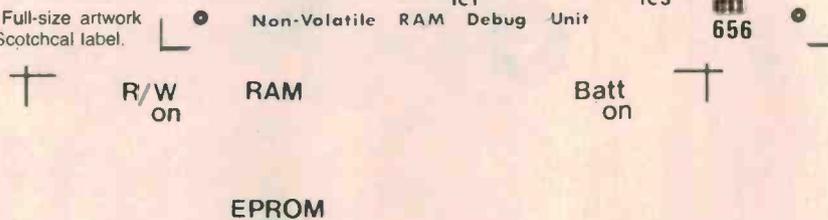Below. Full-size artwork for the Scotchcal label.



## If you're into making music . . . Sonics is your magazine!


1984 Yearbook

### OUT NOW!

- \* Three \$1500 synths reviewed
- \* Home studio basics
- \* Digital recording introduced
- \* The well set-up guitar
- \* Build-yourself effects pedals
- and more . . .

**PLUS** 100 pages of directories listing all equipment involved in making, recording and reinforcing music — what it is, what it costs and where to get it.

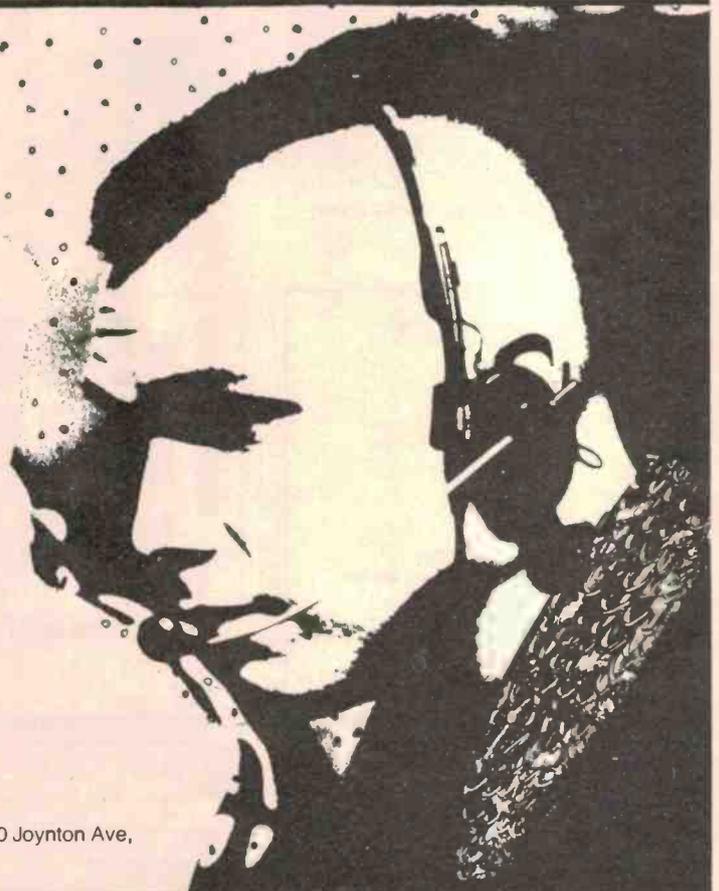Sonics is published quarterly by the Federal Publishing Company, 140 Joynton Ave, Waterloo NSW 2017. (02) 663-9999.




BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

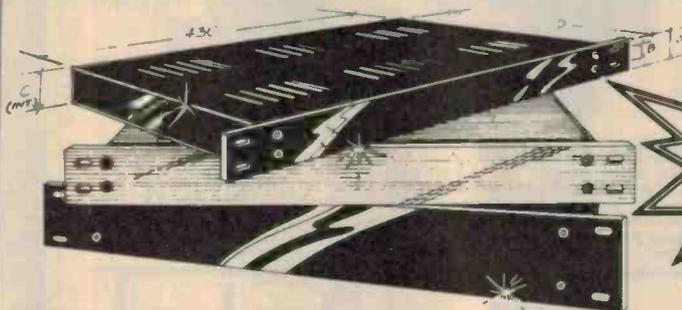**WILL YOUR BUDGET PROBABLY WON'T STRETCH TO AFFORD OUR PROFESSIONAL SERIES ALL ALUMINIUM RACK CABINETS**

NOW YOUR PREAMPS, AMPS, CONTROL MODULES MONITOR PANELS ETC. CAN LOOK EVERY BIT AS GOOD AS TECHNICS, NAKAMICHI AND OTHER TOP MANUFACTURERS




**INTERNATIONAL STD SIZING BLANK RACK PANELS**

(Elongated mounting holes provided only)

	Height	Finish	ea.	10+
H0421	44mm	Nat. Anod.	6.50	5.90
H0422	88mm	Nat. Anod.	11.50	10.50
H0423	132mm	Nat. Anod.	14.95	13.95
H0426	44mm	Blk. Anod.	7.50	6.90
H0427	88mm	Blk. Anod.	12.95	12.15
H0428	132mm	Blk. Anod.	16.95	15.95

**LUGS**

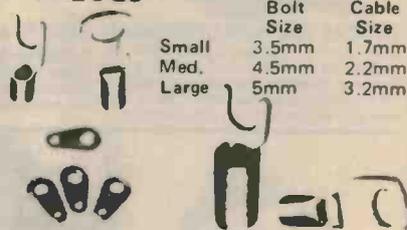

\* These beautifully crafted rack cabinet boxes will give your equipment a real 1st class appearance. \* All aluminium construction. \* REMOVABLE TOP AND BOTTOM PANELS. \* All dimensioning conforms to the International Standard. \* Natural or Black finish. \* Ventilated lid. \* Deluxe

brushed finish anodised front panel. \* Individually cartoned. \* Supplied in Flat Pack Form — Easily assembled in minutes.

Side Elevation:  
D = 254mm C (Internal Chassis Height)  
B (Mounting Bolt Centres)

Cat. No.	Finish	A	B	C	Was	NOW
H 0401	Natural	44	34	38	\$45.00	\$39.00
H 0402	Natural	88	57	82	55.00	49.00
H 0403	Natural	132	89	126	59.95	54.00
H 0411	Black	44	34	38	45.00	39.00
H 0412	Black	88	57	82	55.00	49.00
H 0413	Black	132	89	126	59.95	54.00

H 1500	Solderlugs Pack 50	1.00
H 1501	Solderlugs Pack 1000	9.50
H 1510	Crimplug Small Pack 25	1.60
H 1511	Crimplug Small Pack 500	19.50
H 1512	Spadelug Small Pack 25	1.60
H 1513	Spadelug Small Pack 500	19.50
H 1520	Crimplug Med. Pack 20	1.60
H 1521	Crimplug Med. Pack 500	22.50
H 1522	Spadelug Med. Pack 20	1.60
H 1523	Spadelug Med. Pack 500	22.50
H 1528	Crimplug Large Pack 20	2.40
H 1529	Crimplug Large Pack 500	32.50

Beware of other rack boxes that do not conform to International Rack Sizing.

**SAVE A FORTUNE ON ALTRONICS DIRECT IMPORT HARDWARE — JUST CHECK OUR BULK PACK PRICES — THEY ARE A FRACTION ON WHAT YOU'RE PAYING NOW!**



**1/8th inch WHITWORTH**

STEEL NUTS AND BOLTS ROUND HEAD ZINC PLATED

	Length	Pack Qty.	Price
H 1000	9mm	25	\$ .85
H 1002	9mm	500	4.50
H 1005	12mm	25	.85
H 1007	12mm	500	4.95
H 1009	25mm	25	.95
H 1011	25mm	500	6.95
H 1020	Hex Nut	30	.75
H 1022	Hex Nut	500	5.95
H 1030	S/Proof Washer	50	.95
H 1032	S/Proof Washer	500	6.95
H 1040	Flat Washer	50	.95
H 1042	Flat Washer	500	6.95

Huge Savings with Trade Packs (Contents: 500)

**BA NUTS AND BOLTS**

Bolts Cheesehead Steel, Nuts Brass

		Pack	Price
H 1045	4BA x 6mm	25	\$ .95
H 1047	4BA x 6mm	500	5.95
H 1050	4BA x 12mm	25	.95
H 1052	4BA x 12mm	500	6.95
H 1060	6BA x 12mm	25	.95
H 1062	6BA x 12mm	500	7.50
H 1070	Nut Hex 4BA	25	1.00
H 1072	Nut Hex 4BA	500	12.50
H 1080	Nut Hex 6BA	25	1.00
H 1082	Nut Hex 6BA	500	12.50
H 1090	4BA S/Proof Washer	50	.95
H 1092	4BA S/Proof Washer	500	5.95
H 1095	4BA Flat Washer	50	.95
H 1097	4BA Flat Washer	500	6.95

**SELF TAPPING SCREWS**

Nickel Plated Steel From less than 1c each

		Pack	Price
H 1100	No. 4 x 6mm	25	\$ .75
H 1102	No. 4 x 6mm	500	4.50
H 1110	No. 4 x 12mm	25	.95
H 1112	No. 4 x 12mm	500	5.50
H 1120	No. 8 x 12mm	25	.95
H 1122	No. 8 x 12mm	500	6.95

From less than 1c each.

**NYLON NUTS & BOLTS**

Super Handy for Mounting Semis, PCB's or anywhere an Insulated mounting is required

		Pack	Price
4BA	Cheesehead		
H 1200	4BA x 12mm Bolt	10	.85
H 1202	4BA x 25mm Bolt	10	.95
H 1210	4BA Nuts	10	1.65
H 1215	4BA Washer	10	.65
6BA	Cheesehead		
H 1220	6BA x 12mm Bolt	10	.75
H 1222	6BA x 25mm Bolt	10	.90
H 1225	6BA Nuts	10	1.45
H 1228	6BA Washer	10	.65

**RUBBER FEET**

With 3mm Mounting Hole

Standard



Stickon Type



	Size (diam.)	Pack Qty.	Price
H 0914	13mm	8	\$ .85
H 0913	13mm	100	7.50
H 0917	16mm	8	.95
H 0916	16mm	100	8.00
H 0940	12mm Stickon	4	.80
H 0942	12mm Stickon	100	9.60
H 0950	20mm Stickon	4	.95
H 0952	20mm Stickon	100	11.50

**SPACERS (STANDOFFS) SUPERB NICKEL PLATED BRASS**

UNTAPPED 4 BA or 1/8" CLEARANCE

TAPPED 4 BA

Cat.	Length	Pack Qty.	Price	Cat.	Length	Pack Qty.	Price
H 1305	6mm	8	\$ .95	H 1379	9mm	8	\$1.00
H 1359	6mm	100	8.50	H 1380	9mm	100	9.50
H 1362	9mm	8	.95	H 1383	12mm	8	1.20
H 1365	9mm	100	9.50	H 1384	12mm	100	12.50
H 1372	12mm	6	.95	H 1387	25mm	4	1.00
H 1373	12mm	100	11.00	H 1388	25mm	100	17.50
H 1375	25mm	4	.95				
H 1376	25mm	100	15.00				

# ROD IRVING ELECTRONICS

425 HILTON STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA. Ph (03) 489 8131. Telex No. 38897

## This Month's Kits



**ETI-656 THE BUG DEBUGGER**  
Ever burnt a program into EPROM and then found it wouldn't run? Without a logic analyser, it's difficult to debug the system. This project costs far less than a logic analyser and will get you out of that jam.



**ETI-675 Microbee parallel-to-serial interface**  
When you're on a good thing... Here's another Microbee project, but this one can be readily adapted to other machines, too.



**ETI-273 LET CALLER**  
Play tennis anyone? This unit provides you with clear indication when a ball 'tips' the net in flight—requiring a LET call. Much more reliable than umpires and ball boys. Avoid disputes and tantrums (sorry Mac...). Cheap and simple to build.



**ETI Dec '83**  
**ETI 674 MICROBEE PROPORTIONAL JOYSTICK CONTROLLER**  
On the joy of a 'proper' joystick! Most computer joysticks are of the switch type. But, when you want to get into some 'real' joystick action, nothing beats a proportional joystick with potentiometers. This straightforward project for the Microbee, in our continuing popular series, simply plugs into the Bee's parallel port.

**\$37.50**



**ETI-268 NICAD FLOAT CHARGER**  
**\$9.00** ETI MARCH '83

Keep your NiCad batteries in tip-top condition with this cheap, simple charger.




**ETI Oct 83**  
**ETI-412 PEAK PROGRAMME METER**  
This project uses a 10-LED bargraph display module to show audio level from -23 dB to +6 dB. It's simple to build and set up.



**ETI Oct 83** **\$16.50**  
**ETI-672 MICROBEE TELETYPE INTERFACE**  
The "Claytons" of printers is the old surplus teletype—such as the Model 15 etc. For around a tenth the price of a dot-matrix printer, you can have hard copy from your microbee using this simple interface.



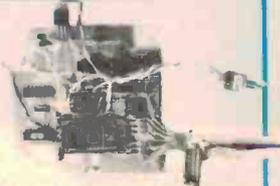**ETI MAY '83**  
**ETI-163 LAB SUPPLY** **\$159**  
Fully variable 0-40 V current limited 0-5 A supply with both voltage and current metering (two ranges: 0-0.5 A/0-5 A). This employs a conventional series-pass regulator, not a switchmode type with its attendant problems, but dissipation is reduced by a unique relay switching system switching between taps on the transformer secondary.



**ETI-668 MICROBEE EPROM PROGRAMMER** **\$47.50**  
ETI FEB '83  
Simple, low cost programmer for the MicroBee can program 2716s, 2732s and 2764s.


**ETI-153 TEMP. PROBE**

**\$19.95**  
ETI JUNE '83

Can measure temperature from -50°C to +150°C. It simply plugs into your multimeter—great for digital multimeters. Accuracy of 0.1°C, resolution of 0.1°C.



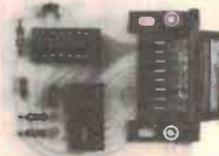**ETI MAY '83**  
**ETI-323 HEADLIGHT DELAY UNIT** **\$17.50**  
Park your car and turn off the lights. Can't see where you're going? Press the button and the headlights come on to light your way, switching off automatically after 50 seconds. This is a simple, easy to build, low cost project.



**ETI Oct 83** **\$12.50**  
**ETI-671 MICROBEE PRINTER INTERFACE**  
A simple interface unit for parallel printers.



**ETI-162 30 V/1 A FULLY PROTECTED POWER SUPPLY** **\$47.50**  
ETI DEC '83  
The last power supply we did was the phenomenally popular ETI-131. This low cost supply features full protection, output variation from 0 V to 30 V and selectable current limit. Both voltage and current metering is provided.



**ETI-654 APPLE II ANALOGUE/DIGITAL INTERFACE** **\$159.00** ETI MARCH '83  
This project will give your Apple a set of 8-bit digital inputs and outputs plus one analogue input and one analogue output. Applications include: driving a robot, recording science experiment results, etc. (digital only shown).



**ETI-688 BIPOLAR PROM PROGRAMMER** **\$47.50** ETI JUNE '83  
Every digital workshop should have one! Can be used to program the popular fusible-link PROMs like the 74S188/288, 82S23 and 82S123 etc.



**ETI Oct '82** **\$20.00**  
**ETI-461 GENERAL PURPOSE BALANCED INPUT PREAMP**  
This project can be used as a balanced mic amp, with low impedance input, a low or high impedance input differential amplifier or a balanced input instrumentation amplifier.



**ETI Oct 83** **\$475 inc. tax**  
**ETI-690 LITTLE BIG BOARD**  
Just what you've always wanted in a computer—a 'big' computer on a little board! This design runs a Z80A at 4 MHz, comes with 64K RAM, two RS232 ports and a floppy disk controller. It will run CP/M 2.2 and the board fits the soon-to-be popular STD buss.



**\$29.50**  
**ETI Dec '83**  
**ETI-1518 VIDEO ENHANCER**  
This simple to build project features three controls for curing video 'image ills'—floor, ceiling and enhancement. It's designed to be installed either 'stand alone' or in with the ETI-1517 Video Distribution Amplifier.



**ETI-335 PUSHBUTTON PROGRAMMABLE WIPER CONTROLLER** **\$28.50** ETI MARCH '83  
No more fiddling with knobs and not getting the delay between wipes that you want—this windscreen wiper controller is simply 'programmed' with two pushbuttons to provide the wiping delay you need.



**ETI-733 RADIOTELETYPE CONVERTER FOR THE MICROBEE** **\$20.00**  
ETI APRIL '83  
Have your computer print the latest news from the international shortwave news service. Just hook up this project between your shortwave receiver's audio output and the MicroBee's parallel port. A simple bit of software does the decoding. Can be hooked up to other computers too.

# For tennis players — an electronic 'let' caller

This low cost, simple to build project detects when a ball 'tips' the net cord as it passes over — no more disputes about whether it did or it didn't! No false alarms either.

Geoff Nicholls

TENNIS IS a popular outdoor sport, particularly in summer. But a 'friendly' game can be spoilt by bad feelings arising from a dispute — particularly where a 'let' call is involved, where the ball is seen to 'tip' the net cord wire as it passes from one side of the court to the other. This little project will solve such disputes and is safe from 'human fallibility', provided it is correctly set up — a simple procedure.

When I first thought of this project, I realised some sort of sensor and detection system that was free from false alarms would be necessary. This ruled out using a microphone attached to the net cord. As net cords are (usually) steel, I hit upon the idea of using some sort of magnetic sensor. It was obvious that trying to slip a coil over the net cord was out of the question, so some other scheme had to be devised. Then again, winding coils is tedious, so a ready-wound coil of some description was necessary. Casting around for something suitable we discovered reed relay coils were cheap and readily available, so I did some experiments to see if one could be pressed into service. It worked!

Thus, the sensor consists of, simply, a reed relay coil, a few brackets and a small bar magnet. This assembly is attached to the steel net cord, as shown in the accompanying diagram. When the ball strikes the net cord, a travelling wave moves out from the point struck by the ball, toward the net cord supports. The movement of the steel net cord in the magnetic field in the vicinity of the sensor coil causes a small variation in the magnetic field, inducing a voltage across the ends of the coil. This voltage pulse is detected and an alarm is sounded.

## Construction


Everything except the sensor mounts in a small plastic box, the printed circuit board slots in to the grooves on the walls of the box with the 9 V battery on one side and space for the switch and sensor socket on the other side. The front panel is dressed up with a Scotchcal label.

The only unusual part of the project is the sensor, so I'll start with it. The heart of it is a reed relay coil, with a  $\frac{1}{8}$ " (3 mm) steel screw down the middle clamping a small right angle steel bracket to each end. (See the accompanying photo). To create a good magnetic circuit I screwed two nuts up to



Neat and simple. All the bits for the Let Caller. There's not much to it, but it's certainly effective. The sensor coil is shown in the foreground. It mounts on the net cord (see diagram next page).

# Project 273

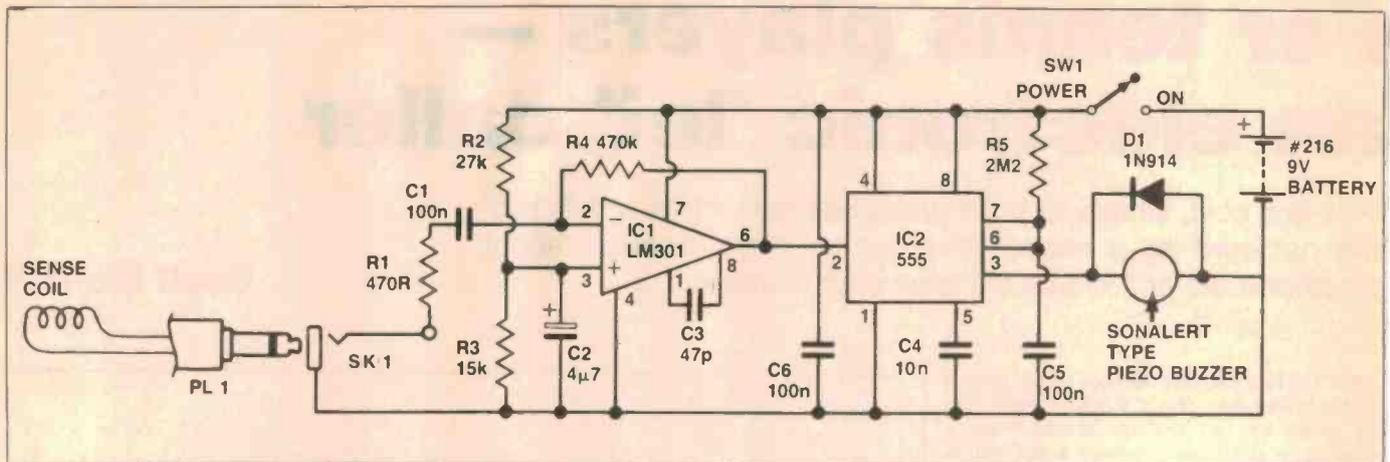

the head end and put three nuts on the other end.

The sensor connects to the main unit via a 500 mm length of shielded cable, with a 70 mm length of 4 mm dia. heat-shrink tubing over the join. Secure the cable to the coil body with tape to relieve stress on the wires. Complete the sensor by soldering a 3.5 mm plug to the other end of the cable.

The Scotchcal label can be attached to the box lid now, the corner markers should be a few mm outside the lid area, so that they won't show when the label is trimmed. To get a good finish with a white background label I usually spray the lid with flat white paint and let it dry before sticking the label down. Once the label touches the lid it sticks fast, so it is important to carefully align it beforehand. Rub any trapped air pockets toward the edges and drill the holes for the switch and socket, then trim the four corner holes and lid edges with a sharp knife.

The piezo buzzer mounts on the plastic bottom of the box; the one I used required two holes in the box to pass the wires to its connecting pins. The buzzer easily attaches with double-sided adhesive tape.

Check that the pc board slots onto the box, trim by filing if necessary.

The pc board can be assembled now. The only point to watch is the orientation of the two ICs and the tantalum capacitor.

Solder a twisted pair of hookup wire between the pc board and the 3.5 mm socket, with 0 V going to the shield side. Complete the wiring to the battery and switch, then check that everything goes together. If the lid won't fit it is probably due to wires passing over the pc board. There are two solutions to this; either solder the offending wires to the copper side of the pc board or file an angle at the corner of the board for the wires to fit in.


The last thing to consider is how to attach the box and sensor to the tennis net. I used a plastic clip for the box called a Kurly-Lok On Base. Richco part no. KLB-750A. It is 40 mm high, has an adhesive base about 12 x 25 mm and is made by Richco, distributed

here by Mayer Krieg & Co. You may be able to find another method of mounting but I bet it won't be as good as this curly clip which fits perfectly over the threaded rod used to tension the net.

The sensor and magnet work best when clamped onto the bare steel net wire about 150 mm from the post, with the wire bet-

ween the two. I used wire ties as supplied with loaves of bread, although a clothes peg may be adapted to make it easier to attach.

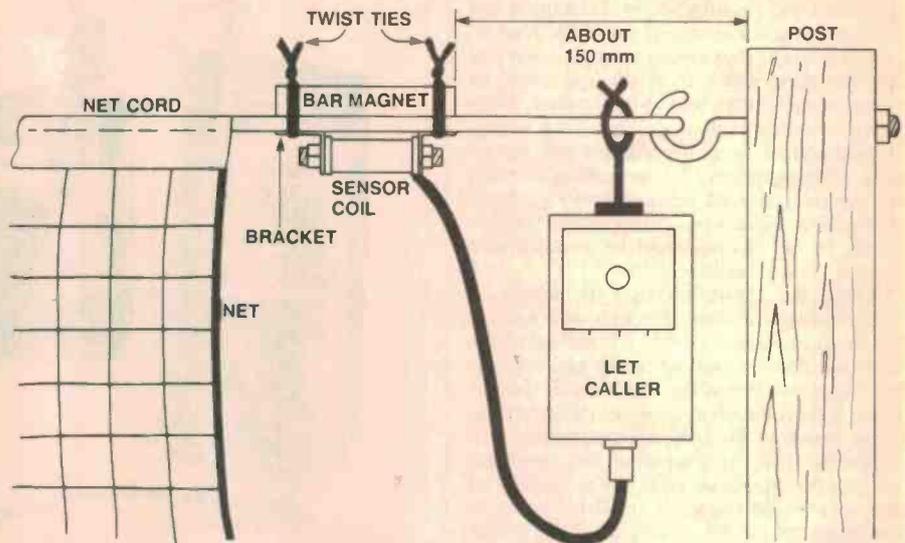The sensitivity is directly related to the strength of the magnetic field at the sensor coil. A small bar magnet is adequate, an old speaker magnet is superlative! (but probably 'overkill').



**Installation.** It's simple. Tie the sensor coil and magnet on the net cord about 150 mm from the post and hang the box near the post.

## HOW IT WORKS — ETI-273

The sense coil is magnetically coupled to the net cord steel wire so that any change in the flux through the coil causes an induced voltage to appear across the coil.



If the net wire is struck by the tennis ball the vibrations set up modulate the flux through the coil, thus producing an alternating voltage. This is amplified by IC1, an ac inverting amplifier designed with a gain of about 500 at 1 kHz, and a roll off of -20 dB per decade each side of that frequency.

Resistors R2 and R3 bias the amplifier's

output to just over one-third of the supply voltage, C3 filters that bias voltage. IC2 is a 555 timer configured as a monostable multivibrator or one-shot with an interval of a quarter of a second.

When the voltage at the trigger input (pin 2) is less than one-third of the supply voltage, a timing interval is initiated, which sounds the piezoelectric buzzer. So any slight disturbance in the flux in the sense coil will cause the voltage at pin 2 of IC2 to drop below one third of the supply and activate the buzzer.

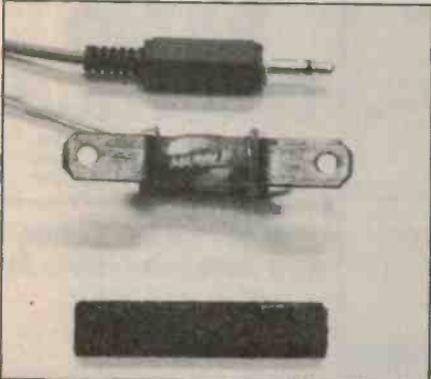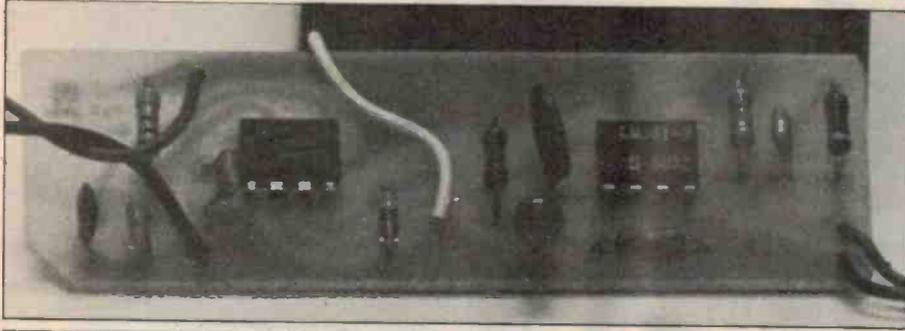Diode D1 clamps any reverse voltage spikes from the buzzer, preventing false triggering.




### Using it

The Let Caller will beep once on power up, and may beep continuously if the sensor is not plugged in.


Since it responds to high frequency vibrations, a very slow serve may not 'twang' the net cord enough to trigger the unit, although I have used it for several hours and it never missed one. The wind doesn't seem to affect it either, and balls hit into the bottom of the net won't always trigger it. This confirms the validity of the sensor design and its superiority to a microphone-based system.

Having dispensed with the umpire, have a happy tennis game!

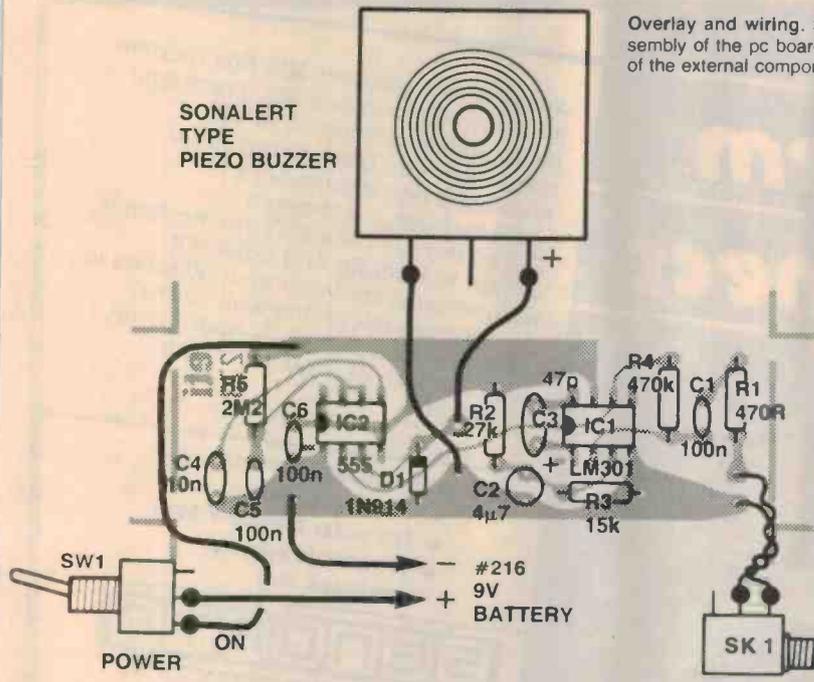The bits. Above is a view of the completed pc board, below is a view of the completed sensor coil assembly.



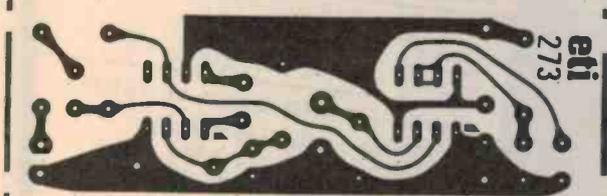Overlay and wiring. Showing assembly of the pc board and wiring of the external components.



Board and panel. The pc board artwork is at left, panel artwork on the right. Both are shown full-size.

### OTHER USES

The pc board could be used for a number of other purposes besides a Let Caller. For instance, the sense coil may be replaced by most transducers, as long as R4 was adjusted to suit the particular unit. The pulse length from IC2 can be increased by replacing C5 with a higher value tantalum capacitor. You could experiment and come up with a motor-bike alarm etc. The 555 IC can easily drive relays, so a high power load could be switched. The power supply can be anything up to 15 Vdc, so experimenters, go to it!


### PARTS LIST — ETI-273

- Resistors**.....all 1/4W, 5%
- R1.....470R
  - R2.....27k
  - R3.....15k
  - R4.....470k
  - R5.....2M2
- Capacitors**
- C1, C5, C6.....100n ceramic
  - C2.....4μ7/35 V tant.
  - C3.....47p disc ceramic
  - C4.....10n ceramic or greencap
- Semiconductors**
- IC1.....μA301, LM301, μA308, LM308
  - IC2.....555 timer

### Miscellaneous

ETI-273 pc board; Scotchcal front panel label; plastic 'zippy' box 80 x 50 x 30 mm; piezoelectric buzzer — Sonalert, Murata or similar; reedy relay coil — D.S.E. cat. no. S-1948 or similar; 3.5 mm plug and socket (optional); 500 mm shielded cable; type 216 9 V battery and snap connector; single-pole single-throw (SPST) miniature toggle switch; m two right angle steel brackets 12 x 12 mm; 1/8" x 2" Whitworth (3 mm x 50 mm) steel bolt and five nuts; curly-clip — Richco KLB750A or similar; 50 mm long bar magnet; double-sided stick tape; hookup wire etc.

Price estimate: \$20-\$24

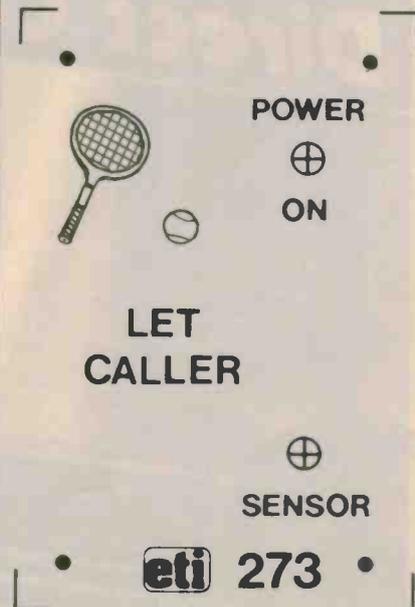

# TO THE ELECTRONICALLY MINDED.

(Professionals, Hobbyists, Students & Enthusiasts.)



**Texas Instruments**  
**TI-99/4 Home Computer**

For over 40 years Radio Despatch Service has been serving the electronics industry. Our team of sales personnel can assist you with your requirements. We carry an extensive range of components, switches, batteries, connectors ... and the popular Texas Instruments Home Computer & Software.



### MULTI-METERS

- UNIVERSITY
- FLUKE



### CALCULATORS

- CASIO
- HEWLETT PACKARD
- TEXAS INST.

## RADIO DESPATCH SERVICE

869 George St., Sydney  
NSW 2000 (Near Harris St.)

Tel. 211 0816  
211 0191

Open: Mon-Fri 8.15am to 5.30pm  
Thursday night late shopping  
till .30pm Sat 8am to 11.45am



"QUALITY COMES FIRST" has been our trading principle for over 40 years. This enables us to give you the best in service and the best in products ... ensuring durability in what you buy and guaranteed satisfaction.

**MAIL ORDERS TO RADIO DESPATCH SERVICE**  
869 George St., Sydney 2000 Tel. (02) 211 0191 • 211 0816

# Sendata 300 Modem Direct Connect

A new direct connect 300 bps modem that is no taller than a 50c piece and fits snugly under the base of a telephone, has been released by Australian communications manufacturer, Electromed. Called the Sendata 300 the modem is simple to operate and does not require operator training. It attaches to the existing telephone wall socket plug and becomes fully operational with the flick of a switch by the operator.

- No installation costs.
- Simple operation.
- Fits under telephone base.
- Attaches to existing telephone plug

## SENDATA

OEM AND DEALER ENQUIRIES WELCOME

**ELECTRO-MED**  
ELECTRO-MEDICAL ENGINEERING P/L

69 SUTHERLAND ROAD, ARMADALE,  
VICTORIA 3143, AUSTRALIA  
TELEPHONE: (03) 509 5844.  
TELEX: AA34008




# Circuit source guide '84

Here is a collection of circuits selected from the voluminous files of your Editor, Roger Harrison and some other sources. From this anthology you should be able to derive other circuits or assemble a system from a variety of 'blocks' to suit a particular application or solve a circuit problem. Applications covered range from audio to RF, timing to dc control, measurement to musical, etc. You may have seen some of these ideas before, but there are bound to be plenty you haven't.

This feature is intended for the experienced experimenter, and construction details are not given. While the circuits have been checked for accuracy and feasibility, they have not necessarily been built and tested. We are unable to answer queries on individual modifications or construction techniques.

## OPTO

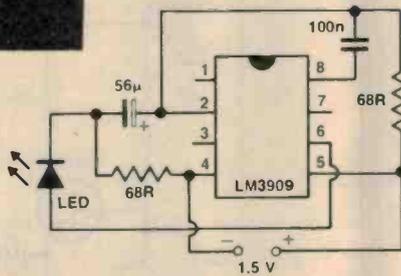


### LED Light Booster

The LM3909 LED flasher IC is well known. It can be used to boost the brightness of ordinary LEDs by providing them with high current pulses at around 20 kHz — too fast for the eye to see flashing — giving an impression of increased brightness.

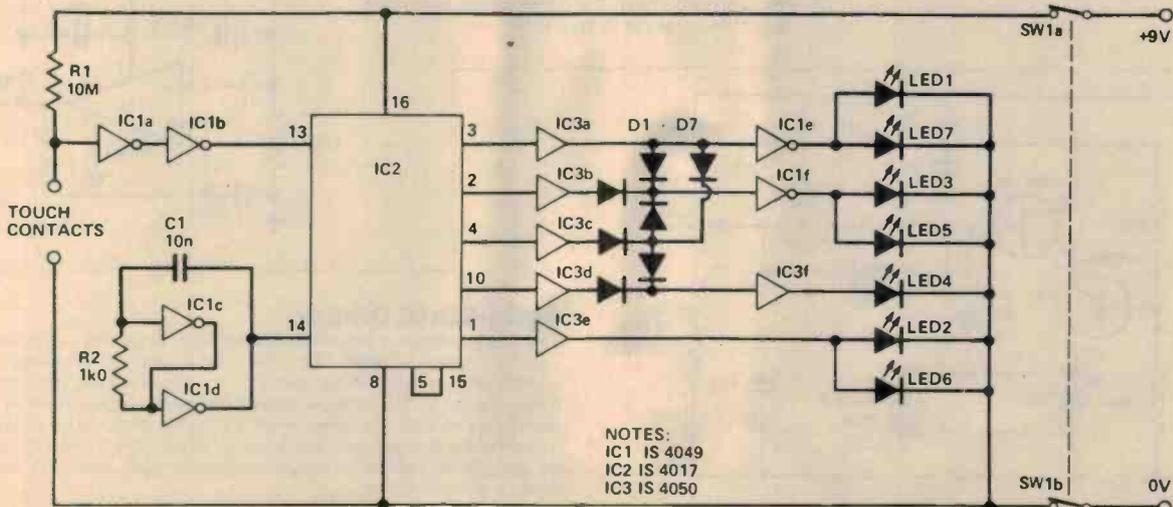
## Die/dice Roller

A dice is more than one die — a six-sided solid with faces numbered 1 to 6 (i.e.: a cube with numbered faces — you've all seen at least one). This is the electronic version. It comprises an oscillator and a counter with a 1 to 6 display output to LEDs. The LEDs can be arranged in the traditional die face, as shown.




NOTES:  
IC1 IS 4049  
IC2 IS 4017  
IC3 IS 4050

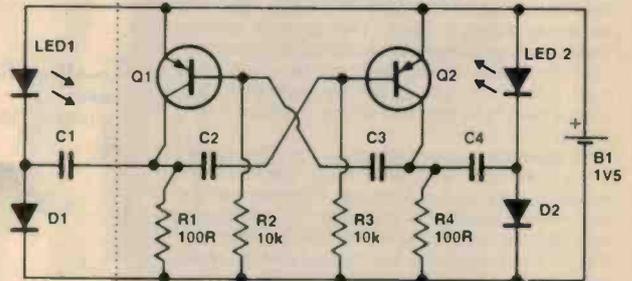NOTE:  
Q1,2 ARE AC126  
D1,2 ARE 0A47  
LED1,2 ARE TIL209 OR SIMILAR


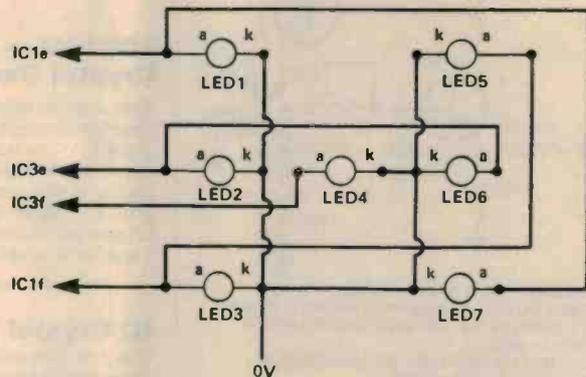
### LEDs on 1.5 V Battery


As most LEDs require a forward voltage between 1.6 and 2.3 volts, it's difficult to power them from a 1.5 V battery. This circuit is an astable multivibrator and voltage doubler that boosts the voltage across the LEDs. To make the LEDs appear to be on continuously, C1 and C2 should be 47n, C3-C4 10µ. To make the LEDs flash alternately, C1-C2 should be about 100µ, C3-C4 should be about 10 times that. To operate a single LED, omit LED1, D1 and C1.


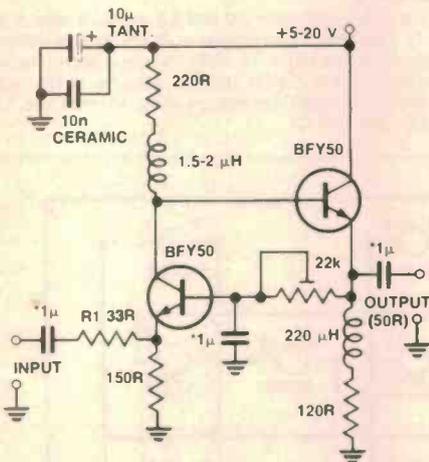
### Wideband Power Amplifier

Well, not all that much power — in the milliwatt range, really. This uses the same configuration as the common-base/common-collector amp opposite, but power gain is provided and the circuit will deliver between about 10 and 180 mW output, depending on power supply voltage. The common collector stage provides current gain, transferring power to the load. This stage has to operate at a fairly high quiescent current. In fact, to get the bandwidth, both stages have to be operated at high quiescent current levels.


Common base stage compensates for the input capacitance of the common collector stage. The RFC in the emitter of the output device gives 'lift' at high frequencies, helping broaden the bandwidth. R1 can be used to match the input to the source driving impedance. Two of these amplifiers can be cascaded to deliver around half a watt output with little decrease in overall bandwidth. Increase the 1µ capacitors to decrease lower cutoff.



MIDBAND POWER GAIN 13-15 dB.  
POWER OUTPUT (5 V SUPPLY) APPROX. 10 mW  
(20 V SUPPLY) 180 mW; BANDWIDTH APPROX.  
50 kHz-15 MHz.  
\* 50 V METALLISED POLY OR MONOBLOCK  
(LOW INDUCTANCE) TYPES.
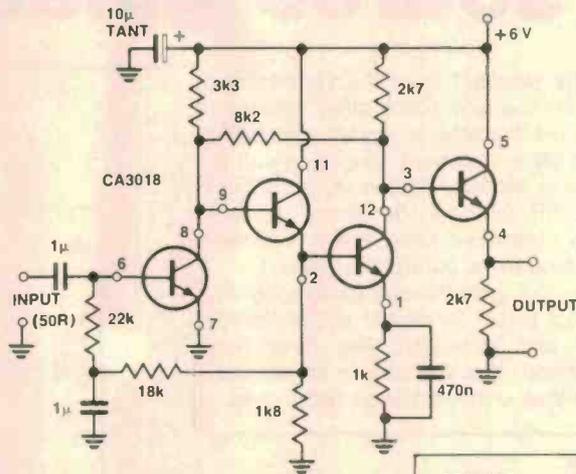
### Wideband Amp with dc Feedback


For high, stable gain, a wideband amp requires several stages with multiple dc feedback paths. The two left hand and two right hand transistors here form common emitter/common collector pairs, the common collector devices providing a high impedance load for the previous transistor and a low source impedance for the following stage. This reduces internal capacitive feedback. A CA3018 transistor array IC is used. The lower cutoff is determined by the capacitor values. Use low self-inductance metallised poly low voltage types.



MIDBAND GAIN APPROX 50 dB  
BANDWIDTH (-3 dB) 1 kHz-30 MHz.  
MAX INPUT APPROX. 4 mV RMS

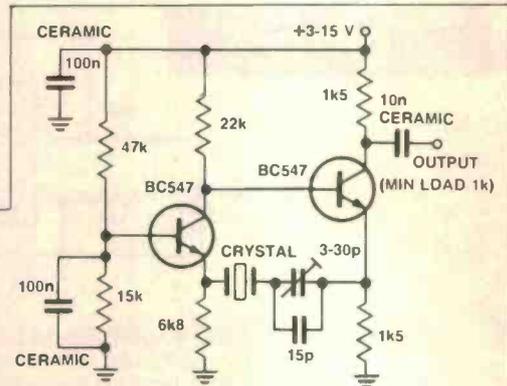
### 100 kHz — 10 MHz Crystal Oscillator

This untuned crystal oscillator will operate reliably over the range from 100 kHz to 10 MHz. Output level depends on supply rail, generally around one-third (peak-to-peak). Output is basically sinewave, but you can 'square up' the output by decreasing the value of the emitter resistor of the output transistor. Dropping it to, say, 220 Ohms gives good harmonics beyond 30 MHz from a 100 kHz crystal. While BC547 transistors are recommended, many types can be used, providing their gain-bandwidth product is 250 MHz or above. e.g. 2N5777, 2N3563 4, 2N3642, 2N2222, BF115, BFY90 etc. For crystals below 100 kHz, transistors with good LF gain are recommended — such as the 2N3565. Supply voltage can range from 3 V to 15 V. The trimmer capacitor is to set the crystal on frequency if necessary. If not, use a 100p ceramic.



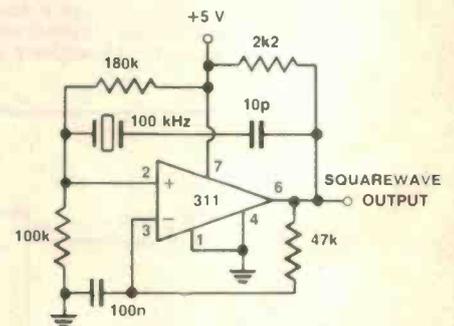
### IC Crystal Oscillator

This low frequency crystal oscillator provides an essentially squarewave output. Upper frequency limit is below 10 MHz. The output voltage swings virtually from rail to rail (5 Vp-p here).



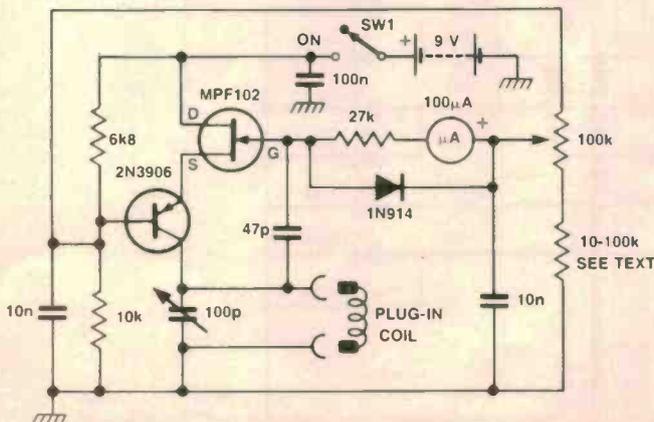
### Solid-State Dipper

This circuit employs a grounded-base oscillator to provide tuning via a single-gang variable capacitor where the rotor plates can be grounded. Simple two-terminal plug-in coils can be used too. The circuit will oscillate over quite a wide frequency range. The 100k pot adjusts the oscillation amplitude to suit the meter and battery voltage. The series resistor to common should be adjusted to cut-and-try so that the pot operates over its range. At upper VHF, the 47pF capacitor should be reduced. All capacitors should be ceramic types and short leads are recommended in construction.


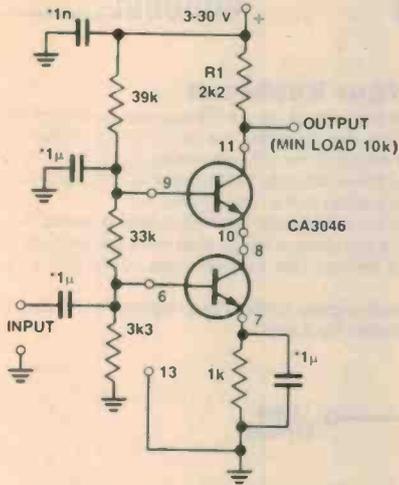
## Wideband Cascade Amplifier


The major feature of the cascade amplifier configuration is the isolation between input and output. This makes for very good stability regardless of the load reactance. The 'lower' transistor is connected as a common emitter amplifier, the 'upper' one operating in grounded base. This circuit employs two transistors as a common substrate from a transistor array IC (CA3046), each having  $h_{FE}$  of 110 and  $f_T$  of 450 MHz. Upper cutoff determined is by R1. Increase all capacitor values to reduce lower cutoffs. A CA3018 may be used or discrete transistors such as 2N706, 2N2369, 2N3607, MPS3646 or 2N5769.



MIDBAND GAIN (LOADED) APPROX. 32 dB.  
BANDWIDTH (-3 dB) APPROX. 5 kHz-4 MHz.  
ALWAYS GROUND PIN 13 OF CA3046  
\* 50 V METALLISED POLY TYPES  
OR TAG TANTALUMS (WATCH POLARITY)
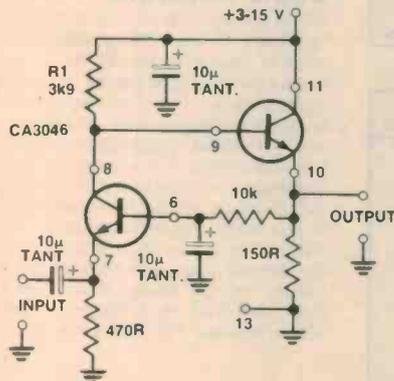
## Common Base/Common Collector Wideband Amp

This amplifier configuration has the advantage of low input and low output impedances — around 100 Ohms here. Two devices from a transistor array IC are used. Use dipped tantalum capacitors and keep leads short for best results. You can match the input impedance to the impedance of the source by varying R1, which varies the emitter current of the common base stage and hence the input impedance. Linearity of this configuration is very good, but gain is not high.



MIDBAND GAIN APPROX. 17 dB.  
BANDWIDTH (-3 dB) APPROX. 150 Hz - 3.5 MHz.  
MAX. INPUT AT 5 V SUPPLY APPROX. 40 mV RMS  
ALWAYS GROUND PIN 13 OF CA3046

## TYPICAL PERFORMANCE CURVES (MHW710-2)

FIGURE 1 — INPUT POWER, EFFICIENCY AND VSWR versus FREQUENCY

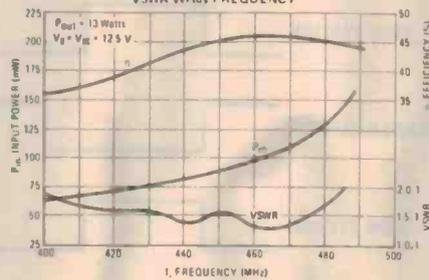


FIGURE 2 — OUTPUT POWER versus INPUT POWER

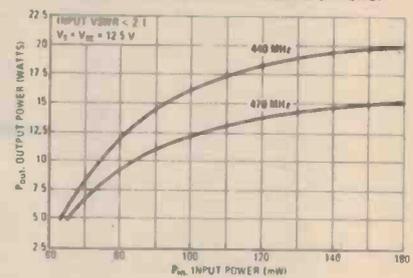


FIGURE 3 — OUTPUT POWER versus VOLTAGE


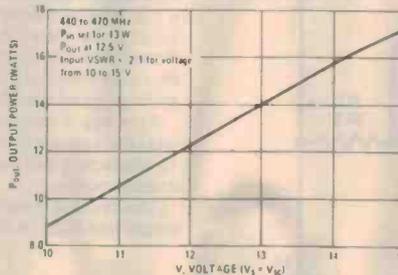



FIGURE 4 — OUTPUT POWER versus GAIN CONTROL VOLTAGE

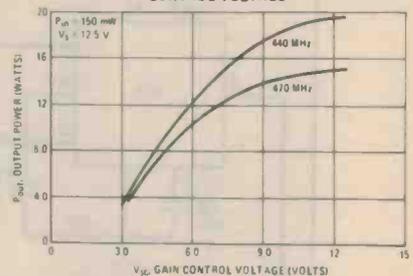

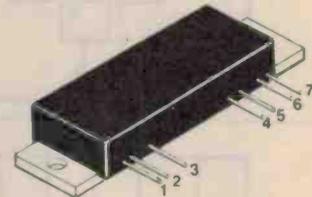
## Amateur TV Modulator/Output Stage


According to Les Jenkins VK3ZBJ, high level modulation for amateur TV applications has distinct advantages over low level modulation followed by a string of linear amplifiers. The main problem with the latter approach is getting the linearity, particularly with solidstate stages. This circuit (from Les) does the job, only requiring about 100 mW of RF drive at 426.25 MHz and standard level composite video input from the camera. Peak RF output is 10 watts which will put quite a respectable signal on the air.

The Motorola MHW710 UHF 'gain block' is readily available and comparatively cheap. Good UHF construction practices should be used. The MHW710 is made for stripline termination to the pins. It should be bolted directly to a heatsink with double-sided pc board (glass fibre or teflon-glass) butted beneath the pins with appropriate tracks to provide termination. C1 and R1 should have virtually no leads. The output filter need not be anything fancy, a stripline or coaxial bandpass type should do the job. Remember, you're dealing with video bandwidths, keep it broad.



MHW710 PINOUT

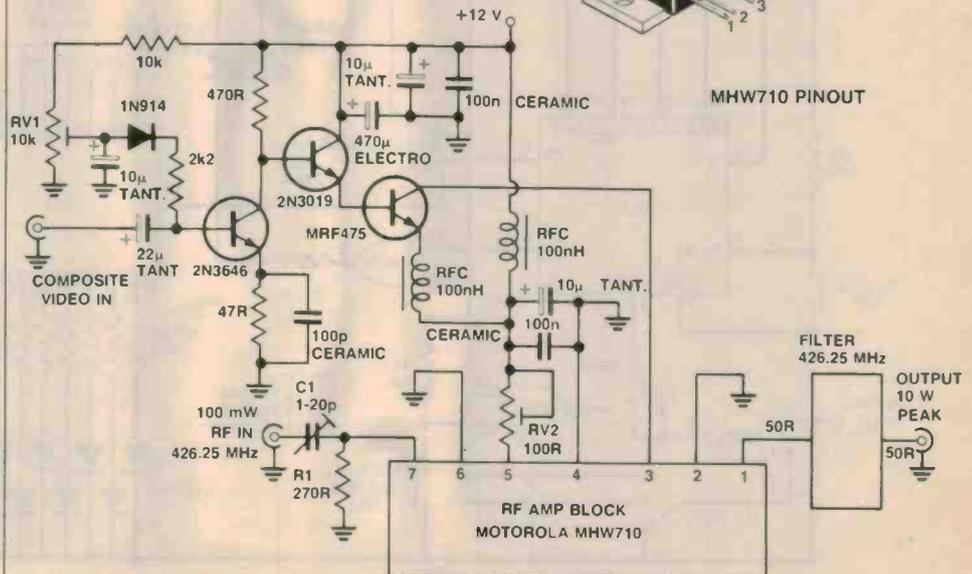

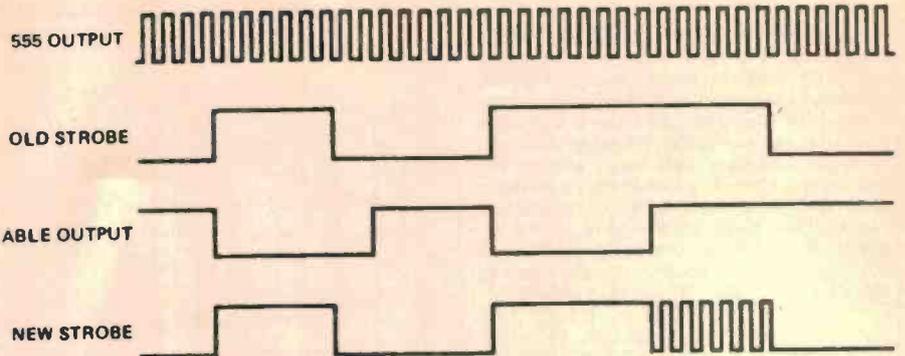


## Auto-repeat For Your Keyboard


If your keyboard does not have auto-repeat, here's the solution. Just insert this circuit in the old keyboard strobe line. Basically, the strobe line activates the monostable IC2, disabling the output of the 555, preventing its pulses reading the new strobe line. After about three seconds, the output of IC2 changes state and the signal from the 555 is passed to the 'new strobe' line.

If the key is released before the monostable finished its timing period, only one character will be sent. For a key press of longer than three seconds, about 10 characters per second will be sent (the frequency set by the 555 in its astable mode).

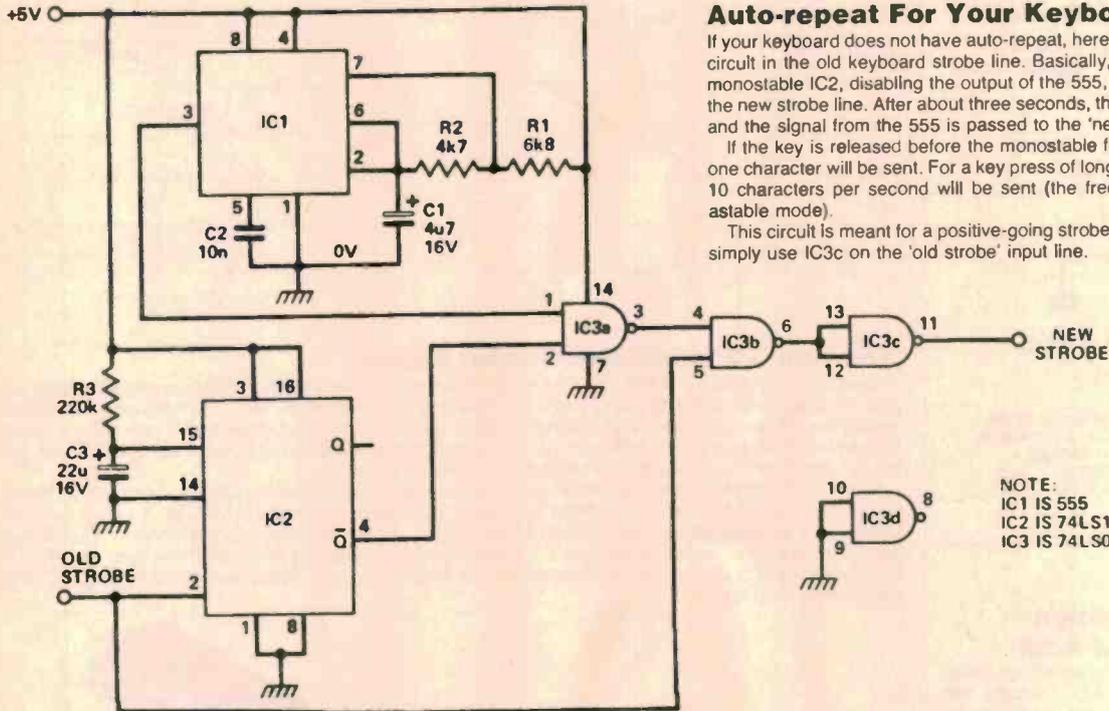This circuit is meant for a positive-going strobe. For a negative-going strobe, simply use IC3c on the 'old strobe' input line.



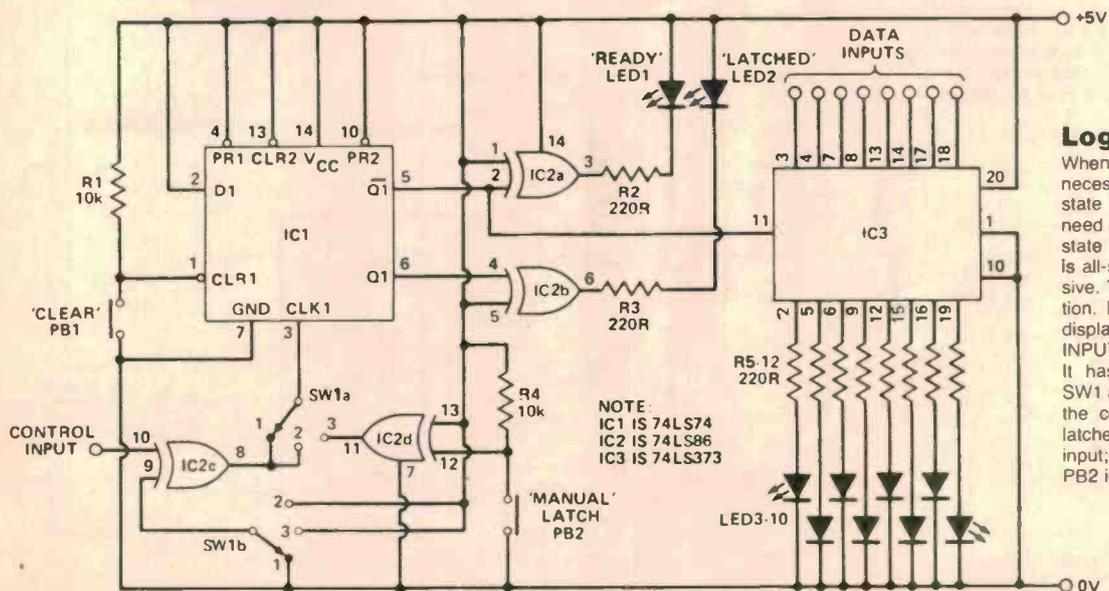
NOTE:  
IC1 IS 555  
IC2 IS 74LS123  
IC3 IS 74LS00



NOTE:  
IC1 IS 74LS74  
IC2 IS 74LS86  
IC3 IS 74LS373
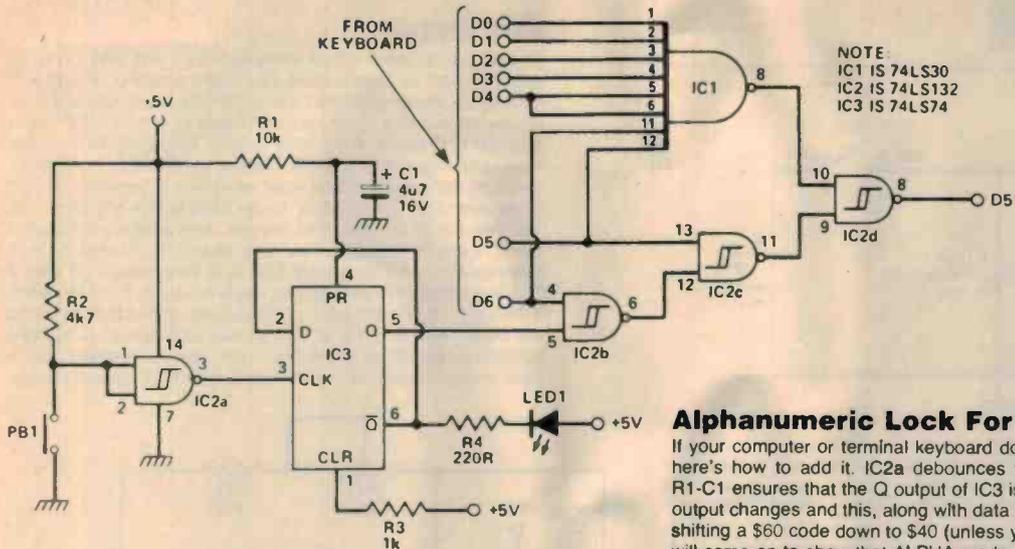
## Logic Analyser

When testing logic circuits it is often necessary to know the simultaneous state of several nodes. To do it, you need a bunch of logic probes or a logic state analyser. The 'professional' tool is all-singing-and-dancing, and expensive. This circuit is a simpler implementation. Eight input bits are latched and displayed, controlled by the CONTROL INPUT from the circuit being analysed. It has three triggering modes: with SW1 at 1, it latches on a rising edge on the control input; with SW1 on 2, it latches on the falling edge control input; with SW1 on 3 it latches when PB2 is pressed. PB1 clears the latch.



NOTE:  
IC1 IS 74LS30  
IC2 IS 74LS132  
IC3 IS 74LS74



### Alphanumeric Lock For a Keyboard

If your computer or terminal keyboard does not have an alphanumeric lock key, here's how to add it. IC2a debounces the alpha-lock key PB1. On power-up, R1-C1 ensures that the Q output of IC3 is high. Each time PB1 is pressed, the Q output changes and this, along with data bit 6 being high, will make D5 a low thus shifting a \$60 code down to \$40 (unless you pressed the DELETE key). The LED will come on to show that ALPHA mode is selected when PB1 is pressed.

To insert this into your keyboard it is only necessary for the original D5 line to pass through this circuit (D5 to D5') and add a keyswitch for PB1.
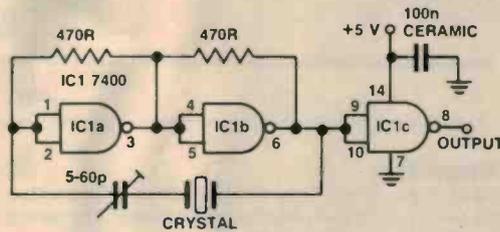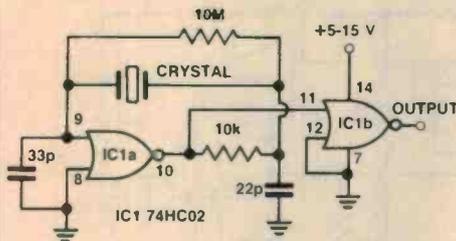
### HCMOS Crystal Oscillator

This circuit works well with crystals in the MHz region, up to 15 MHz, perhaps more. It starts reliably and can be operated on any supply rail between 5 V and 15 V. The 22p and 33p capacitor values may need to be increased for lower frequency crystals — but maintain the ratio.



### Reliable TTL Crystal Oscillator

Many TTL crystal oscillators have been published over the years, and many exhibit unreliable oscillation — particularly on startup. This one has none of

those problems. This will work with crystals in the 1 MHz to 20 MHz range as well as with 'Ceralock' ceramic resonators. The trimmer is to set the crystal to frequency, if necessary. If not, substitute a 100pF ceramic capacitor.


## GENERATORS

### Quadrature Sinusoid Oscillator

This oscillator provides two sinusoid outputs precisely 90° apart. All capacitors should be 1% types. R1C1 = R2C2. The oscillation frequency is given by:


$$f = \frac{1}{2\pi\sqrt{C2R2C3R3}}$$

(R1C1 = R2C2)

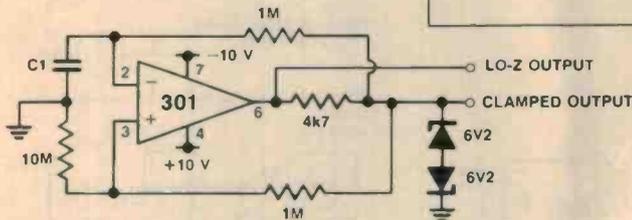

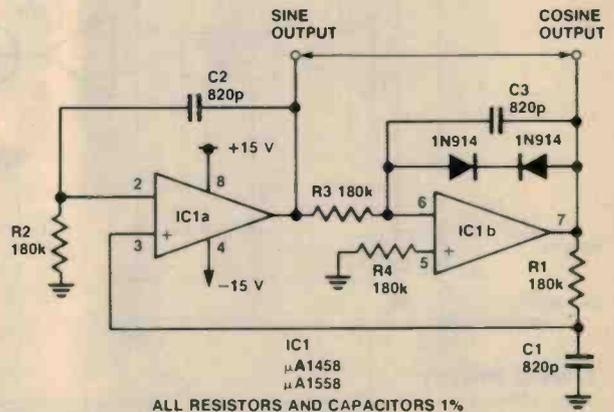
### Low Frequency Squarewave Generator

The output frequency of this generator is determined by C1 and the 10M resistor. A low impedance output, that swings almost from rail to rail, can be taken from pin 6 of the 301, or a clamped output — limited by two 6.2 V zeners — gives a 6.8 V peak-to-peak output. Maximum supply voltage is ±18 V.



ALL RESISTORS AND CAPACITORS 1%



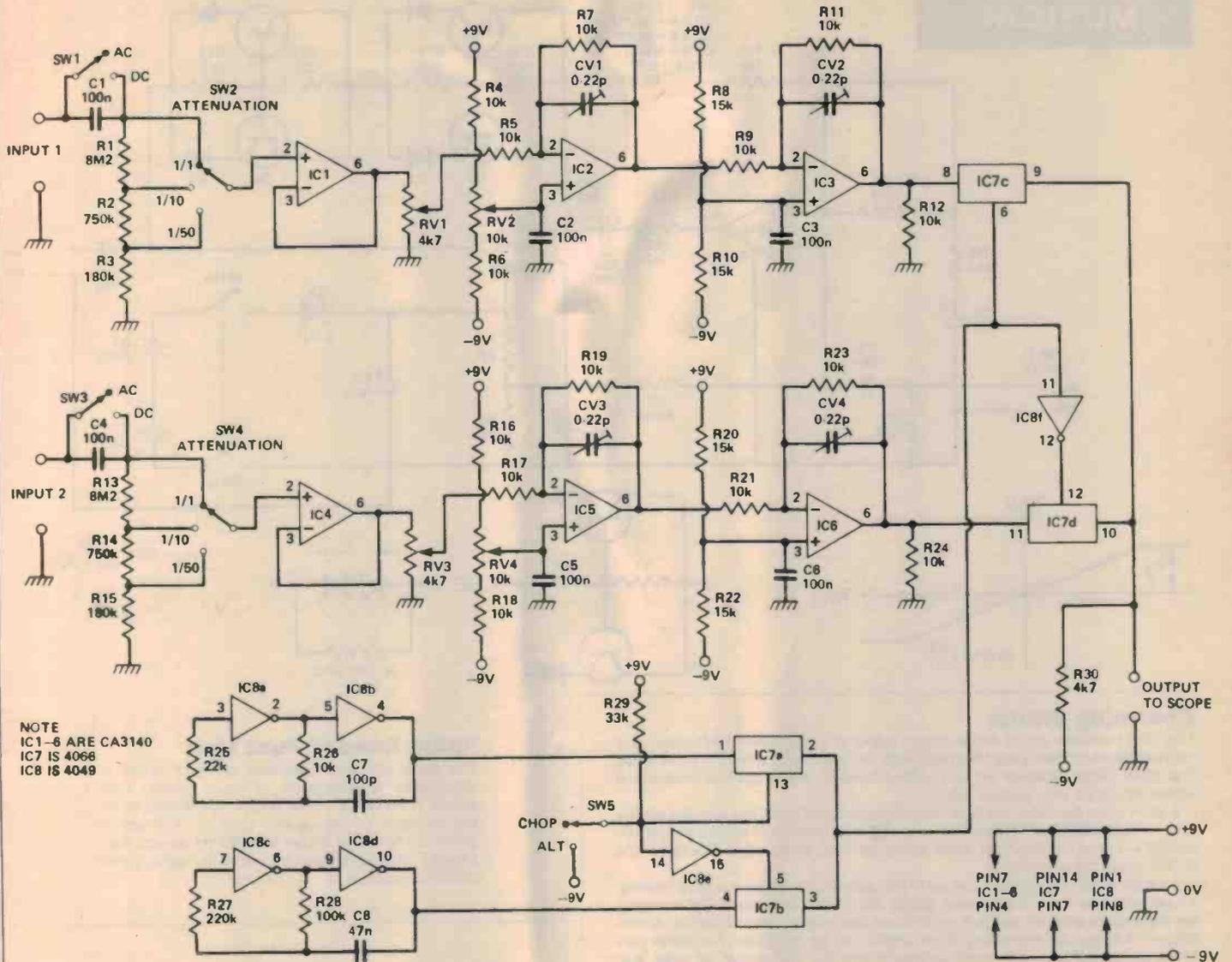


### CRO Dual-Trace Switch

This permits a single-channel CRO to be turned into a dual-trace unit. Two modes of display are provided: 'chop' and 'alternate'. When examining frequencies between dc and about 15 kHz 'chop' mode is used as trace speed across the screen

(timebase speed) is relatively slow. About 15 kHz, 'alternate' mode is used when the timebase makes separate sweeps of the screen for each trace.

Two preamps are used, each having a bandwidth extending from dc to about 2000 kHz. The outputs of the channels are switched to the CRO input by an electronic changeover switch comprised of IC7c-d and IC8f, driven by an oscillator. Two oscillators are used, one for the chop mode, one for the alternate mode, as different switch speeds are necessary.

Setting CV1-CV4 is critical. Procedure is identical for both channels. Inject a 1 Vp-p 100 kHz squarewave into Input 1 and set SW2 to the 1/1 position. Setting of SW1 is unimportant. Set RV1 to maximum and RV2 to mid-position. Connect a CRO to the output of IC2 and adjust for the best squarewave response. (No overshoot and least rounding). Then move to IC3's output and adjust CV2 for best response. Repeat the procedure for the other channel.



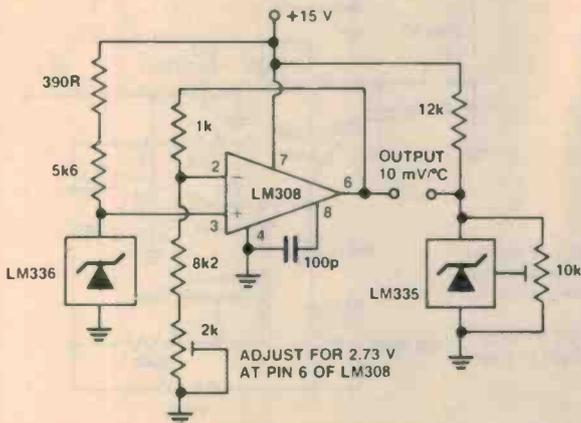


### Centigrade Thermometer

This simple circuit can be used to measure temperature in Centigrade degrees and will read out directly on a standard digital multimeter. The LM336 is a precision 2.5 V voltage regulator, the LM335 a precision temperature sensor. The LM308 output provides a 'stiff' reference scaled up from absolute zero. The 2k trimpot is set to provide 2.73 V between pin 6 of the 308 and common. The 10k trimpot is set so that you get 2.982 V across the LM335 at 25°C. The LM335 can be used for contact temperature measurement.
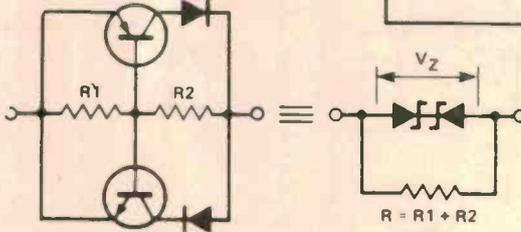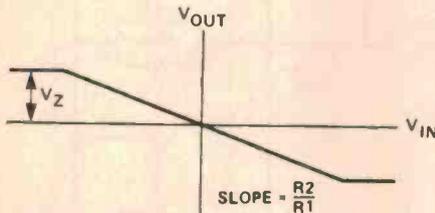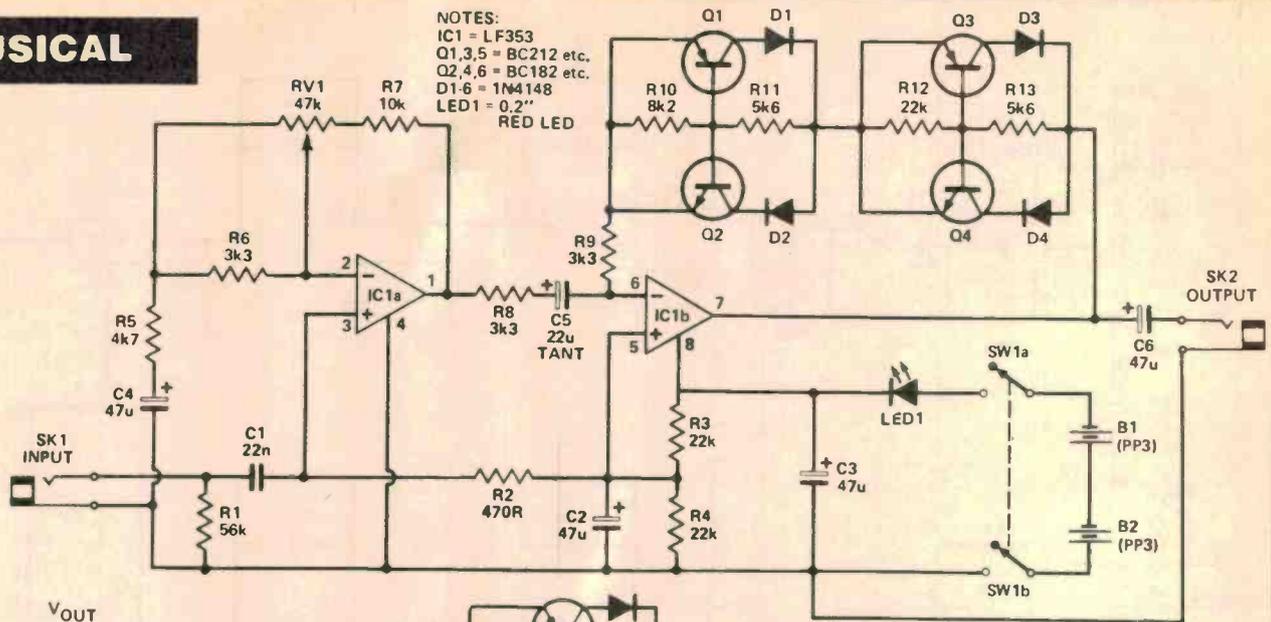
# MUSICAL

NOTES:  
 IC1 = LF353  
 Q1,3,5 = BC212 etc.  
 Q2,4,6 = BC182 etc.  
 D1-6 = 1N4148  
 LED1 = 0.2" RED LED




$$V_Z = 0.6 \times \frac{R2}{(R1 + R2)}$$

## Charming Chime

This circuit enables you to add a 'chime' output to a percussion synthesiser. It is multiple feedback bandpass filter that 'rings' in response to a narrow pulse input. The 220R preset labelled 'set Q' provides variation of the positive feedback. It should be set for best 'ringing' results.

A short pulse applied to the input causes the circuit to break into damped oscillation — the amplitude of the oscillation peaking rapidly and then dying away exponentially — hence the ringing or chime sound, as if you struck a bell. The higher the Q, the longer the decay time.

If the oscillation frequency,  $f_0$ , is set in the upper audio range, you get a 'tinkling' sound, whereas lower frequencies sound like claves or bongos. By arranging several circuits with their inputs in parallel and their outputs mixed together, all with different tunings, an interesting chime chord can be produced. For better performance, an op-amp with wider bandwidth than the 741 should be used. e.g. TL071, 5534 etc.

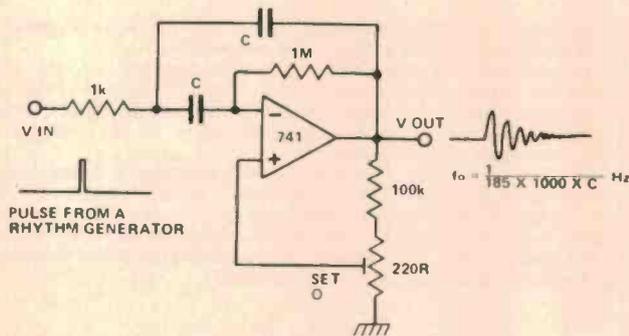


## Chopper Echo Effects Unit


Music signals which have a sharp attack/slow delay envelope, such as guitar etc, can be 'chopped' to give an effect not unlike an echo. Here, IC1 is just a unity gain non-inverting amplifier. The VN67AF FET is turned on and off to short the signal or pass the signal, respectively. If this is done at a slow rate to a slowly decaying note, an 'echo' effect is obtained.

IC2 and associated components form a low frequency pulse generator in which the 'on' and 'off' times can be independently set by RV1 (on time) and RV2 (off time). The 100k preset determines the amount of attenuation afforded by the VN67AF (effect 'depth').
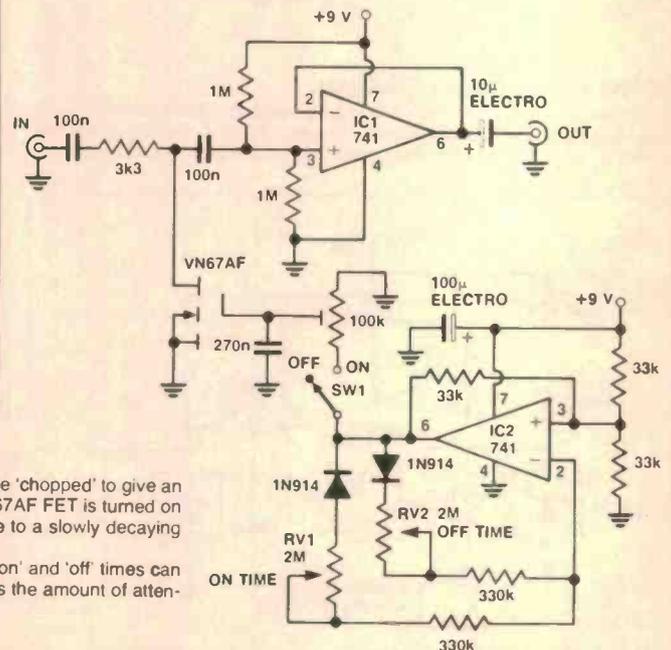
## "Blue Suede" Fuzz Unit

This guitar effects unit provides 'soft fuzz', giving a reasonable approximation to valve guitar amp sound. A series of 'active zeners' are employed in the feedback of the op-amp IC1b. A third active zener can be added to give an extra breakpoint. The existing breakpoints can be varied by varying the values of resistors 10, 11, 12 and 13.




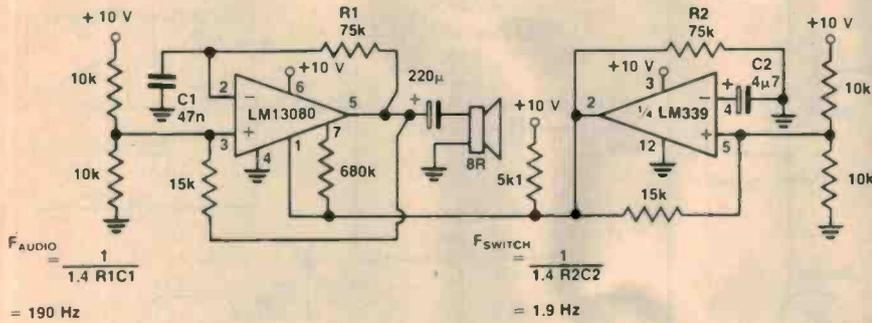


## Two-state Siren

Here is a siren that keys a burst of 190 Hz tone on and off twice per second. The LM13080 power op-amp is arranged as an oscillator, keyed on and off by the LM339 arranged as a low frequency multivibrator. Note that a 12 V supply can be used.
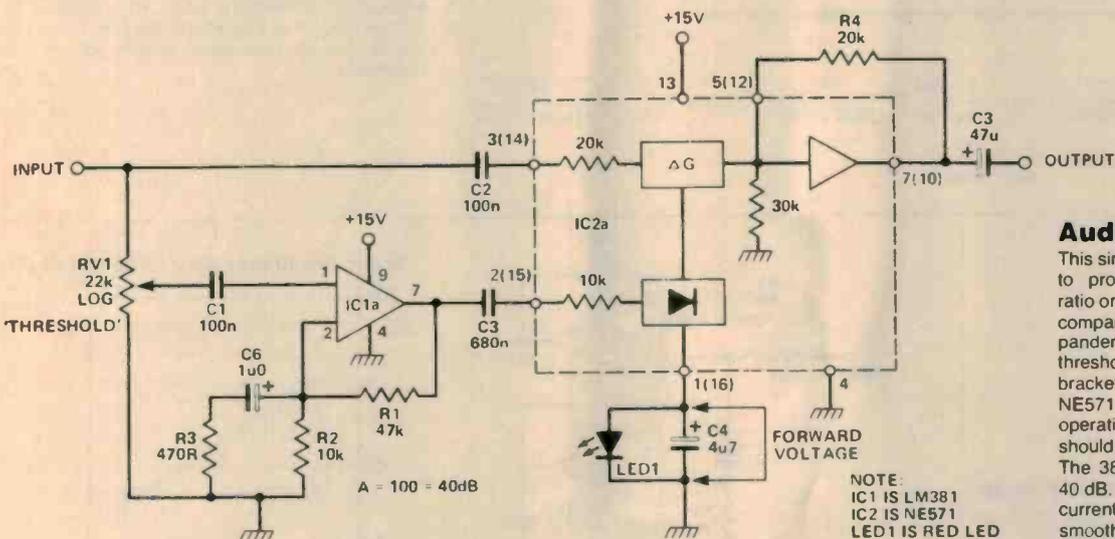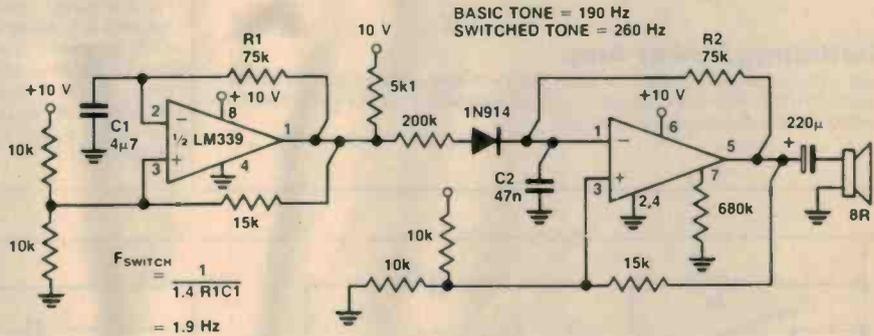
## Two-tone Siren

In this siren circuit, the LM13080 power op-amp is arranged as an oscillator that is switched between two frequencies (190 Hz and 260 Hz). The LM339 is a low frequency multivibrator operating at around 2 Hz.




FOR STEREO USE, THE FORWARD VOLTAGE OF THE RED LED<sub>s</sub> SHOULD BE MATCHED (ABOUT 1V5) (INJECT SIGNAL TO L+R UNTIL BOTH LED<sub>s</sub> ARE LIT)

## Audio Expander

This simple expander gate can be used to provide improved signal-to-noise ratio on records and tapes. The NE571 compander chip is used here as an expander with a red LED used to set the threshold at pin 1. Pin numbers in brackets are for the other 'half' — the NE571 is a dual compander. For stereo operation, the two threshold LEDs should be matched for forward voltage. The 381 amplifies the input signal by 40 dB. This is rectified by the internal current mirror of the NE571 and smoothed by C4. When the voltage reaches the forward voltage of the LED, it draws current and limits the current to the gain cell. This then provides linear operation above the threshold.


## AUDIO

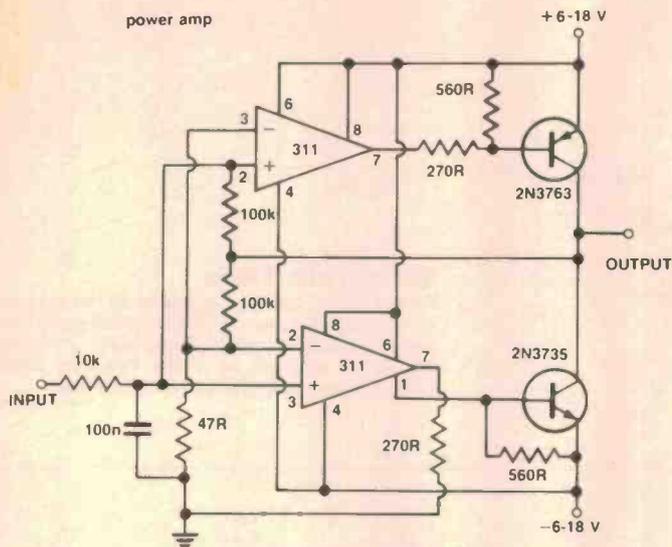

### Switching Power Amp


Two 311 comparators used in a class B power amp. The output devices only switch on when alternate input cycles exceed a small voltage threshold. Feedback largely reduces the crossover distortion.

## FILTERS

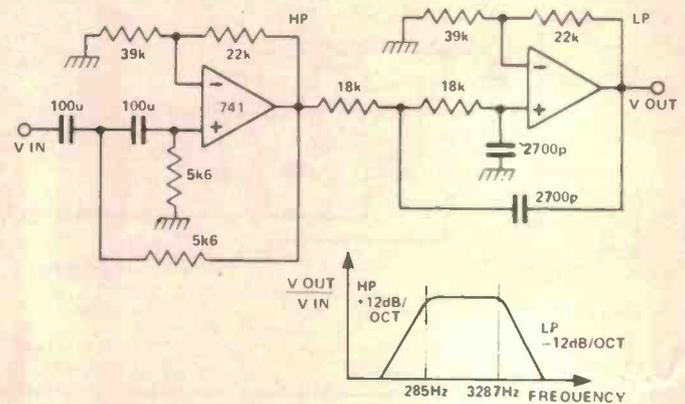
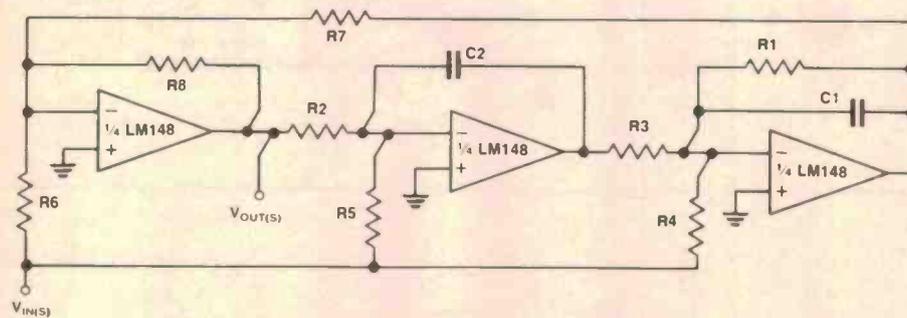
### Speech Filter

For any purely speech audio system application — communications receivers, transceivers, dictaphones etc. — it is desirable, for best intelligibility, to limit the audio bandwidth to provide relatively steep rolloff below about 300 Hz and above about 3 kHz or so. Most speech information is contained between these limits. This circuit shows a simple bandpass filter system with 12 dB/octave rolloff below 285 Hz and above 3287 Hz. One unusual application of such a filter would be in a 'light show' system so that the display varies with voice variations of an announcer or performer.



### Bi-quad Audio Notch Filter


This notch filter provides good predictability and better noise performance than the state-space approach. Three op-amps from a quad package are employed. For a notch of 3 kHz, R1 is 270k, R2-R3-R5 are 20k, R4 is 27k, R6-R8 are 10k, R7 is 100k, C1-C2 are 1n (use good quality poly or mica capacitors).

$$Q = \sqrt{\frac{R8}{R7}} \times \frac{R1C1}{\sqrt{R3C2R2C1}} \quad f_0 = \frac{1}{2\pi} \sqrt{\frac{R8}{R7}} \times \frac{1}{\sqrt{R2R3C1C2}} \quad f_{\text{NOTCH}} = \frac{1}{2\pi} \sqrt{\frac{R6}{R3R5R7C1C2}}$$


$$\text{Necessary condition for notch: } \frac{1}{R6} = \frac{R1}{R4R7}$$
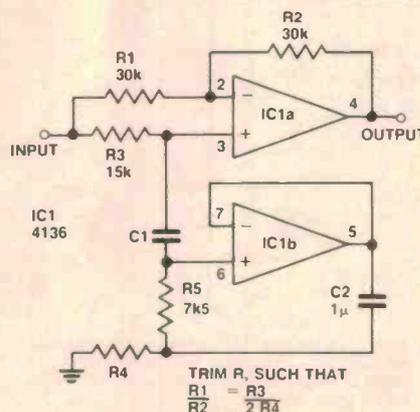
### Gyrator Audio Notch Filter

Using two op-amps from a 4136 quad package, you can implement a very effective notch filter with common component values, the notch frequency ranging from 20 Hz to 2 kHz. Capacitors should be good quality, low voltage metallised poly types.





### Notch Frequency as a Function of C1

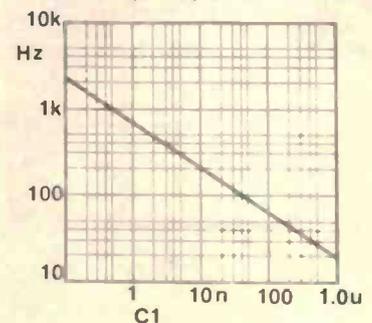
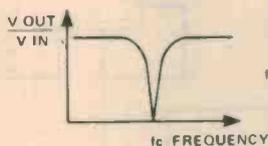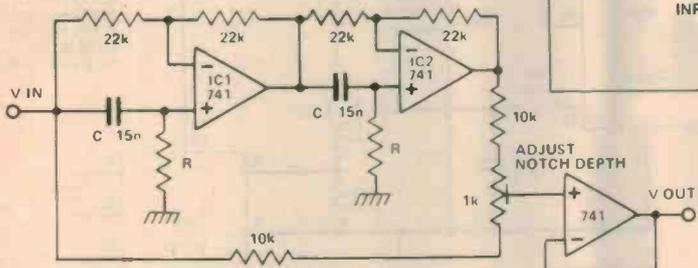
### All-pass Notch Filter

This circuit provides adjustable notch attenuation ('depth'). IC1 and IC2 are arranged as 'all pass' filters. They have a flat frequency response but the phase changes with frequency. Overall maximum phase shift is 360°, a phase shift of 180° (reversal) occurring at a frequency of  $1/2CR$  Hz. By mixing the phase-shifted signal with the original, cancellation will form a narrow 'notch' in the frequency response.

The 1k preset varies the amount of phase-shifted signal mixed with the original so the notch attenuation can be varied. The notch frequency,  $f_c$ , can be varied by varying the two resistor marked R. e.g. for a notch at 50 Hz, R should be 220k.



$$f_c = \frac{1}{2\pi CR}$$


$$f_c = 1\text{kHz}$$

$$C = 15\text{n}$$

$$R = 10\text{k}66$$

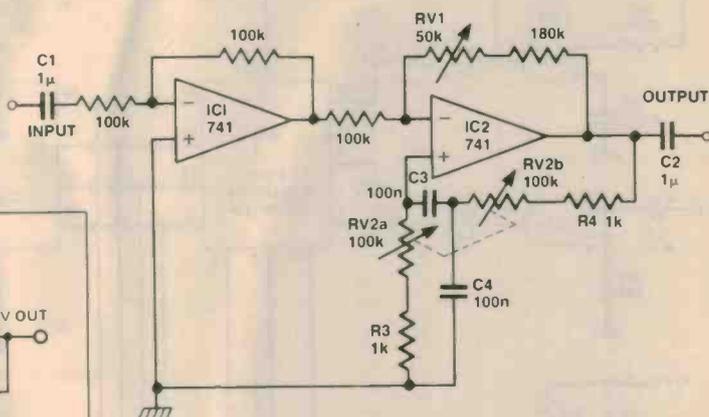
### Tunable Audio Filter with Adjustable Selectivity

This filter can be tuned from 20 Hz to 1 kHz and features adjustable bandwidth. RV2 sets the frequency, RV1 sets the selectivity. This is a positive feedback control. Advancing it beyond a certain point causes oscillation. Set it just below the point of oscillation for minimum selectivity. The capacitors should be low voltage metallised poly types, 5% or better.



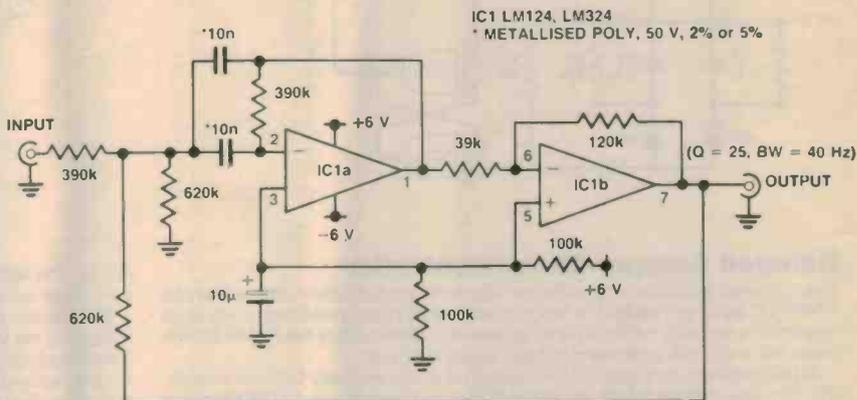
### Active 1 kHz Bandpass Filter

This circuit provides a 40 Hz-wide 'window' at 1 kHz. Two op-amps from a quad op-amp IC are used. For best results, the two 10n capacitors should be metallised poly, low voltage types, with a 2% or 5% tolerance — matched values if possible.



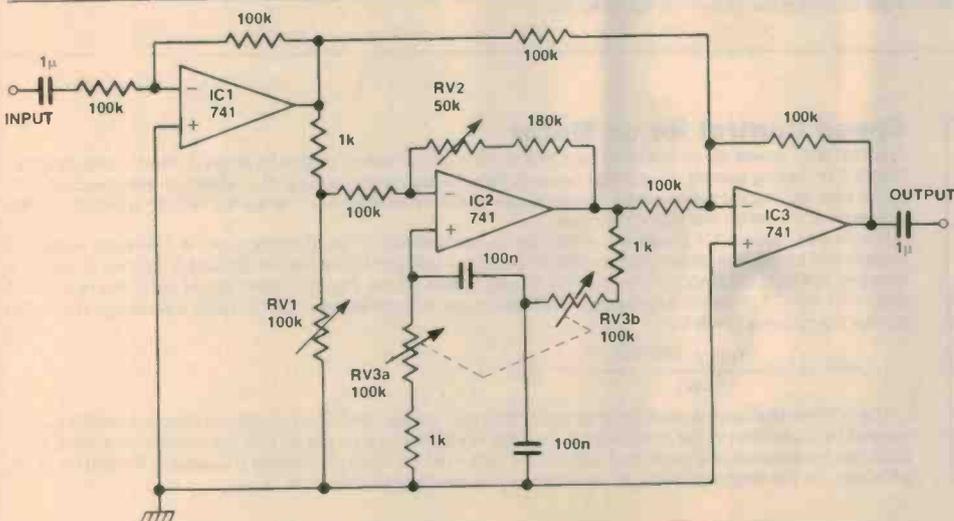
IC1 LM124, LM324  
\* METALLISED POLY, 50 V, 2% or 5%



### Tunable Audio Notch Filter with Variable Selectivity, Attenuation

This is a modification of the previous circuit to provide a notch, rather than a peak. The original input and the filtered signal are summed in anti-phase at the input of IC3. Hence, the filter circuit provides attenuation at the filter frequency. RV1 sets notch depth, RV2 sets notch width, RV3 sets notch frequency.

# POWER SUPPLIES/DC CONTROL

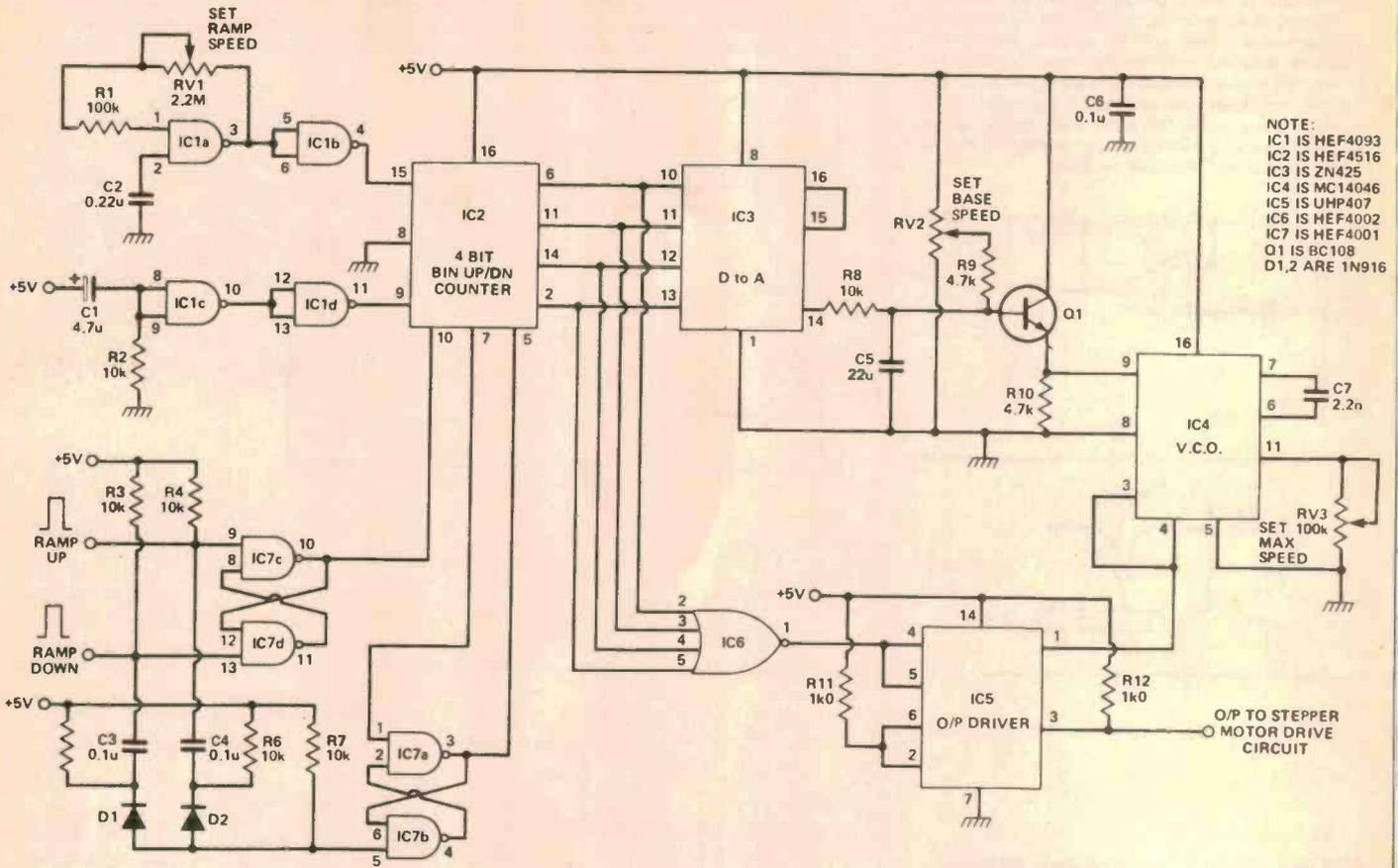


## Ramped Stepper-Motor Controller

This has great applications for robotics. When the motor is at rest, the receipt of a RAMP UP pulse will cause the motor to start at its base speed then ramp up to maximum speed and run for as long as required. On receipt of the RAMP DOWN pulse, the motor will slow down to base speed then stop.

IC1a/b provides clock pulses (ramp speed) to a four-bit binary up/down counter, IC2. On receipt of the RAMP UP pulse IC7c/d sets count up and IC7a/b enables the counter. Unless a RAMP DOWN pulse is received the counter will reach its maximum count (max. speed) and hold at this until the RAMP DOWN pulse is re-

ceived. The latter will set count down and enable the counter which then counts to zero (base speed) and hold again until the next RAMP UP pulse.

The counter output drives the D-to-A converter IC3, the ramping output of this controlling the VCO, IC4. The lower frequency of the VCO (base speed) is set by the bias adjustment of Q1. Upper frequency (max. speed) is set by the 100k pot, RV3. IC5 provides open-collector drive for the output pulse train and also the on/off gate, controlled by IC6, when the counter is set to zero. IC1c/d provides a set zero pulse to IC2 to ensure that the output, at pin 3 of IC5, is off each time the generator is switched on.

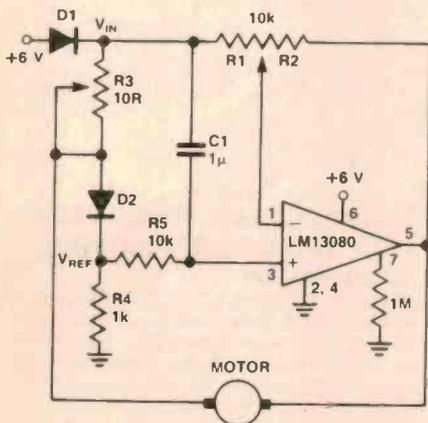


## Speed Control for dc Motor

The LM13080 power op-amp is used here to provide a simple speed control for small dc motors requiring less than 0.5 A starting current. This circuit operates by impressing the multiple of a reference voltage across the motor then varying the reference by means of quasi-positive feedback to change the voltage across the motor whenever the load on the motor changes.

It works as follows: D1 brings  $V_{IN}$  within the common-mode range of the op-amp. A reference voltage is established by the combined voltage drop through the 10R pot R3 and diode D2 and is applied to the non-inverting input of the LM13080. Resistor R4 is used to bias D2 on. The 10k speed adjust pot is two resistors in one — R1/R2. R1 is the input resistance, R2 is the negative feedback resistance. Thus, the voltage impressed across the motor is given by:


$$V_{MOTOR} = \frac{(V_{BE2} + I_3 R_3) R_2}{R_1} + V_{BE}$$

The positive feedback is developed as a change in the voltage across R3 due to the change in motor current caused by a variation in the motor's load. Resistor R3 is shown as a pot so that the amount of positive feedback can be adjusted to smooth operation of the motor (no 'hunting' or 'cogging'). Capacitor C1 and R5 serve as a filter for the reference voltage. Use a polyester low voltage capacitor.

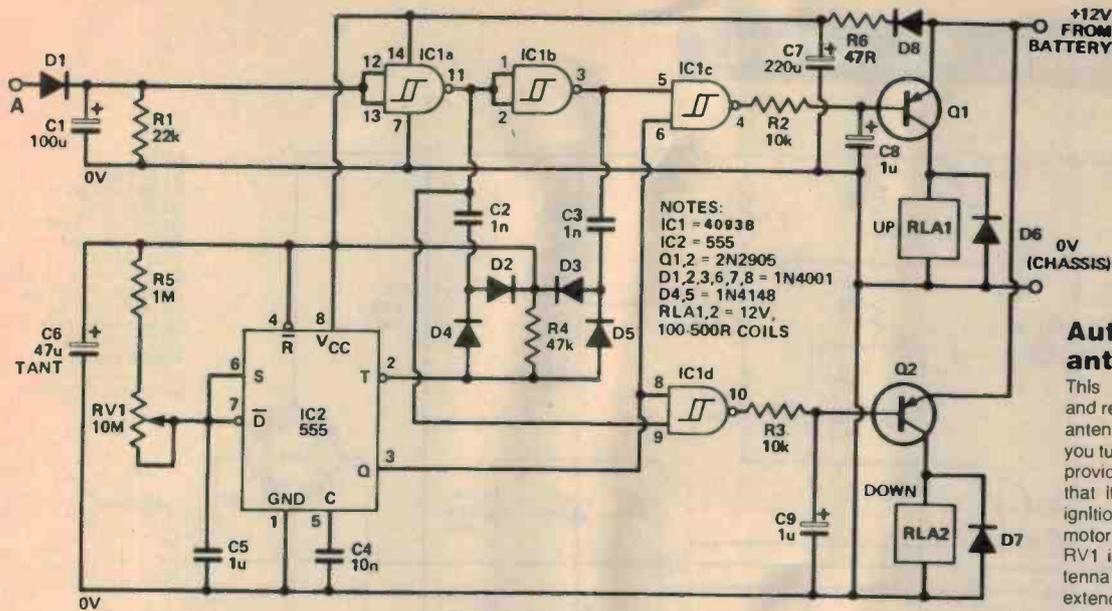

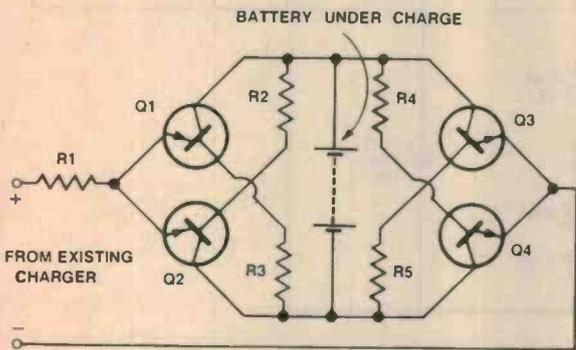
### Automatic car antenna

This unit provides automatic extend and retract for an electrically driven car antenna. The input at A senses when you turn the ignition on and the up relay provides drive for the antenna motor so that it extends. When you turn your ignition off, the down relay reverses the motor drive, retracting the antenna. RV1 is set to provide drive to the antenna motor for sufficient period to just extend or retract the antenna to the full extent. It can be permanently connected as current consumption is under 10 mA. Use tantalums or low-leakage electrolytics for the polarised capacitors.


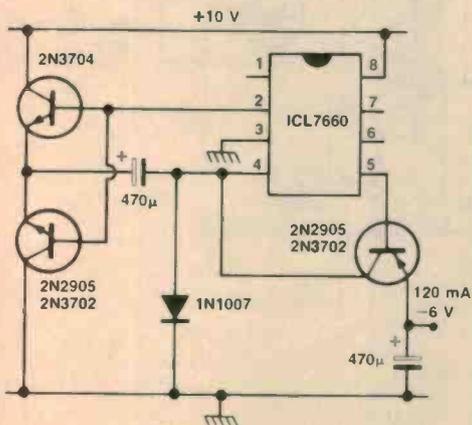
### Nicad Polarity Saver

Avoid charging your Nicad batteries back-to-front — which will certainly destroy them. Residual battery potential determines the charging polarity by switching on either the pnp or npn transistors. Thus, this will not work with completely discharged Nicads. Resistor R1 is simply there for charging current limiting. If your charger has current limiting, omit R1. For a 3 V charger, R2-R5 can be around 1k8-2k2. Suitably-rated silicon transistors can be used (i.e. TP31B). Use germanium types for single cells (1.2 V).




### High Current Voltage Rail Inverter


The ICL7660 (TSC7660) is a positive-to-negative power supply rail inverter. It will only supply low current output though. This circuit boosts the output so that some 120 mA can be drawn from the negative rail provided by the 7660.
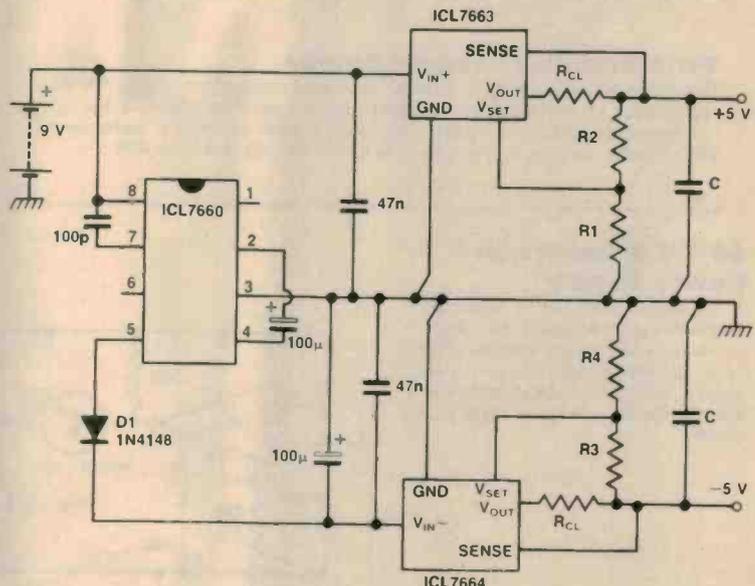
### Dual 5 V Rails from a 9 V Battery

A 7660 positive-to-negative rail inverter is used here in conjunction with a pair of CMOS IC regulators, a 7663 for the positive rail and a 7664 for the negative rail (all ICs from Intersil, second-sourced by Teledyne). These regulators draw only 3.5  $\mu$ A quiescent current but will regulate up to 40 mA output current. Output voltages are determined by the ratios of R2:R1 and R3:R4. The 47n capacitors on the regulator inputs should be ceramic types and are there to prevent instability. Circuit continues to function at battery voltages down to 6 V.



# POWER SUPPLIES/DC CONTROL

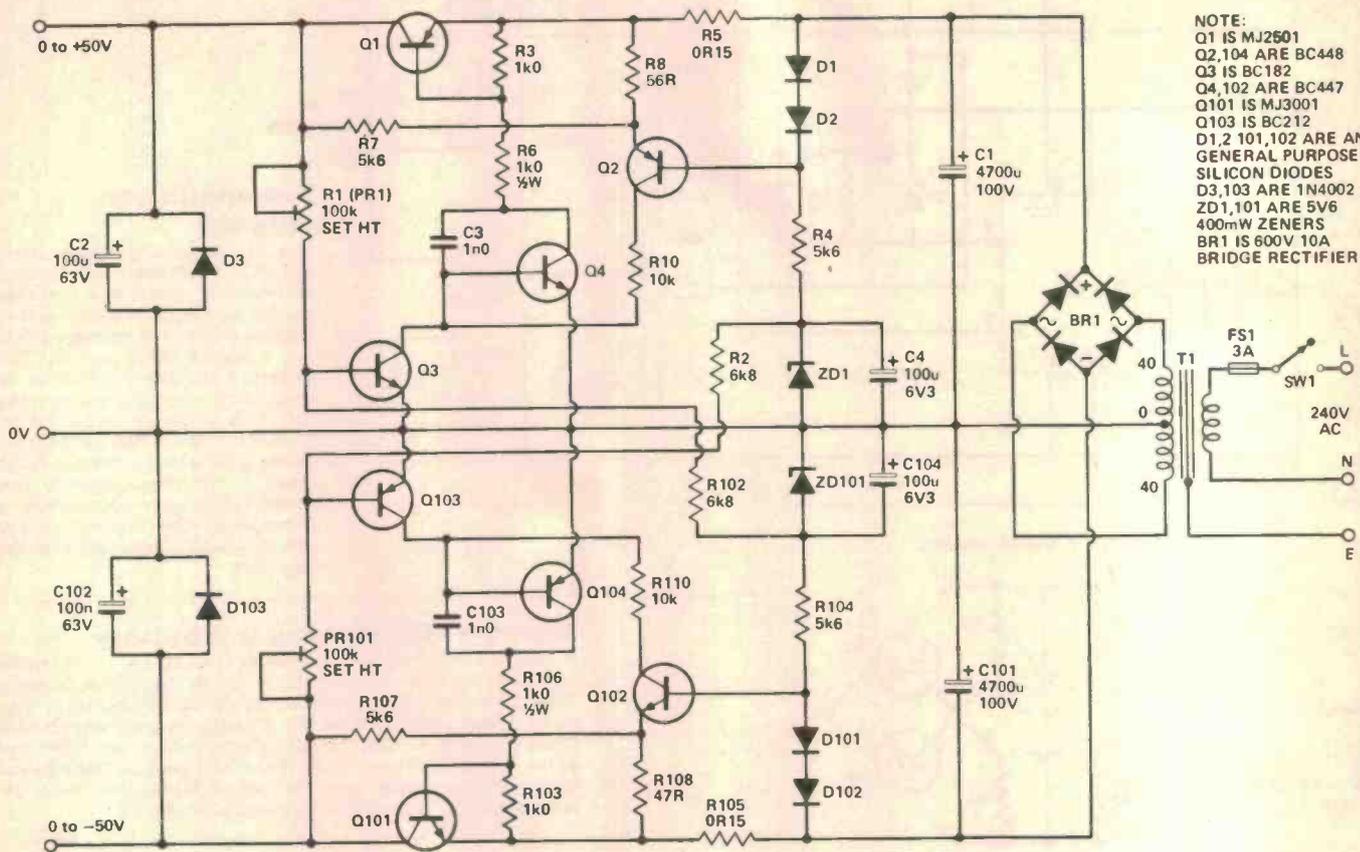



## Twin Stabilised Power Supply

This circuit will deliver up to 50 V on the two output rails at current up to 3 A. The secondary of T1 must be rated at 4.5-5 A to deliver these output currents. Full current limiting protection is provided. This circuit is ideal for use with audio power amp modules requiring supply rails up to 50 V. Note: R8 should be 47R.
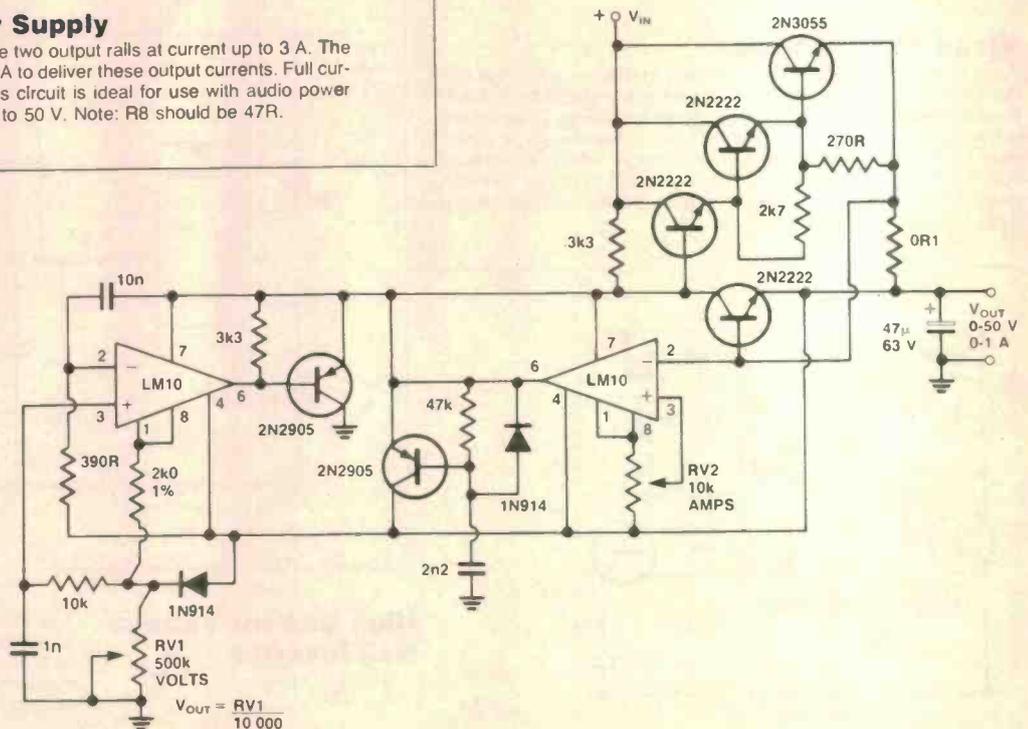
## 50 V/1 A Laboratory Power Supply


A series-pass regulator is employed here with separate circuits for voltage reference and current limiting. The input voltage should be at least 55-60 V, well filtered. The LM10 has an internal reference, which is made use of here.



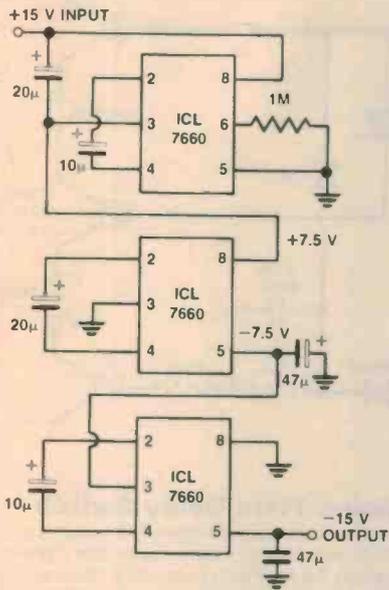


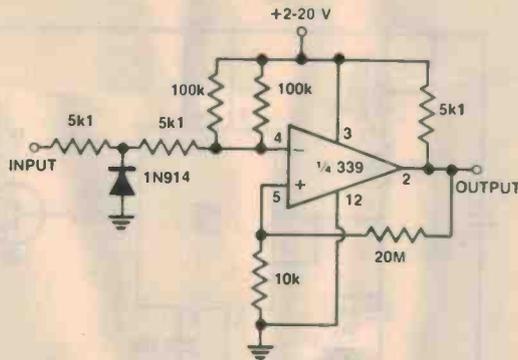
## +15 V to -15 V Supply Rail Inverter

Cascading three 7660 positive-to-negative rail inverters to obtain -15 V from a +15 V supply. Output impedance is about 250 Ohms, so it won't supply much current.



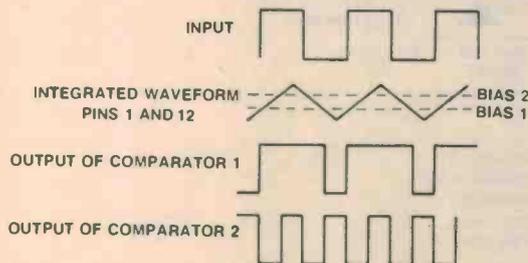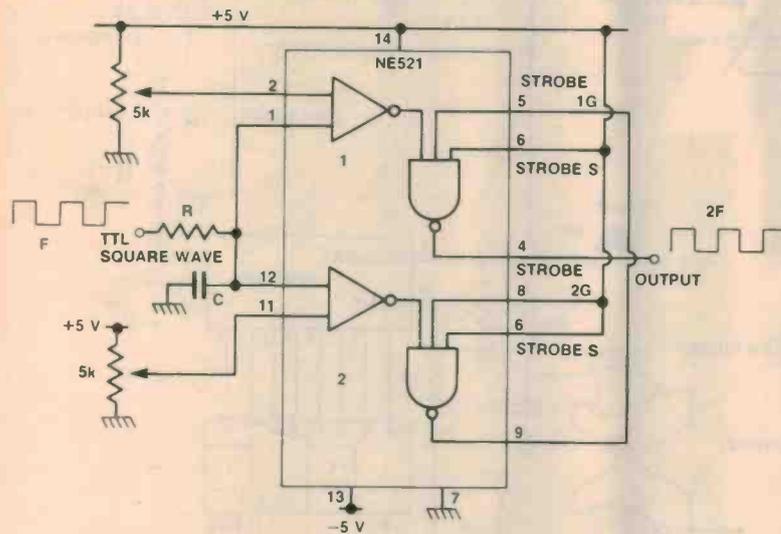
## Zero-Crossing Detector

The output of this circuit goes high at a negative-going zero-crossing, low at a positive-going zero-crossing. The input can be a sine, square or complex wave.


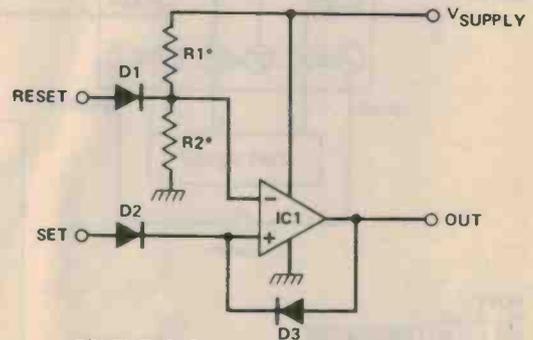
## Digital Frequency Doubler

Digital frequency dividers are commonplace, but digital multipliers are not. This circuit employs the NE521 dual differential comparator. The input is integrated, the triangular resultant being applied to the two comparator non-inverting inputs. Setting the two 5k bias pots appropriately will provide a doubled output. This will work right up to 50 MHz with the NE521.



TRUTH TABLE

SET	RESET	OUT
0	0	NC
0	1	0
1	0	1
1	1	1

NC = NO CHANGE

\*SEE TEXT


NOTE:  
IC1 IS ANY OP-AMP  
D1-3 ARE 1N4148

## Op-amp RS Flip-Flop


While CMOS or TTL gates are commonly used to make an RS flip-flop, op-amps can serve the same function and are often overlooked, particularly in analogue circuits where the simple RS digital function is required and using digital gates would be 'overkill'. With this circuit, you can exploit a spare op-amp from a dual or quad package. Any op-amp may be used. The high and low voltages at the output are only a function of the op-amp's internal output drive configuration.

Resistors R1 and R2 should be chosen so that  $R2 = 2.4R1$  and R2 is less than  $V_{supply}$  divided by 0.05. All changes of state occur on the input low-to-high transition.

# TIMING

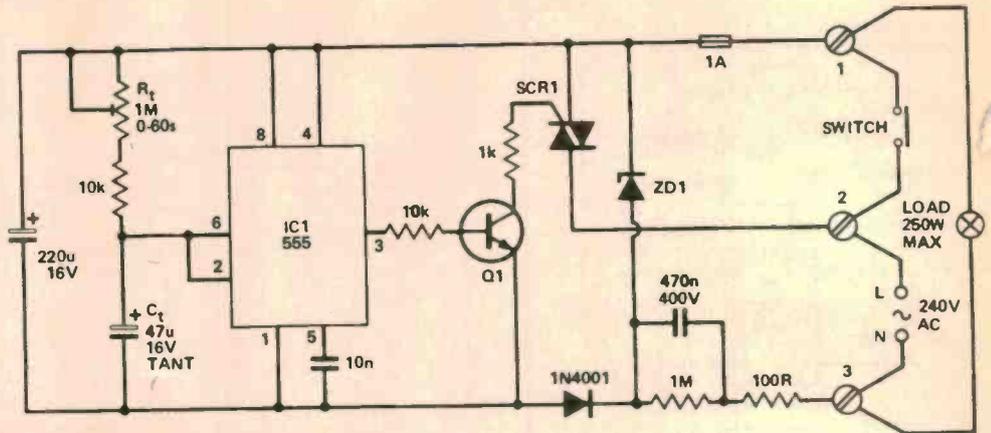


TYPICAL CONNECTION SCHEME

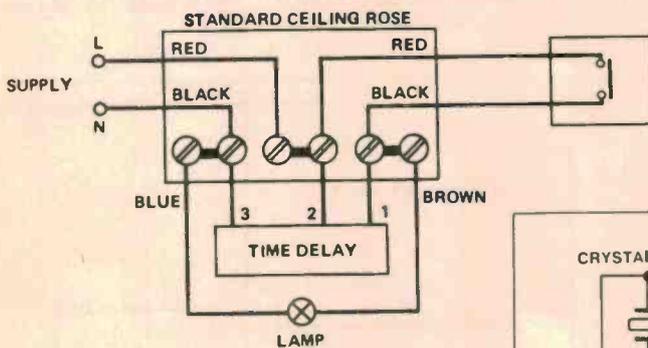
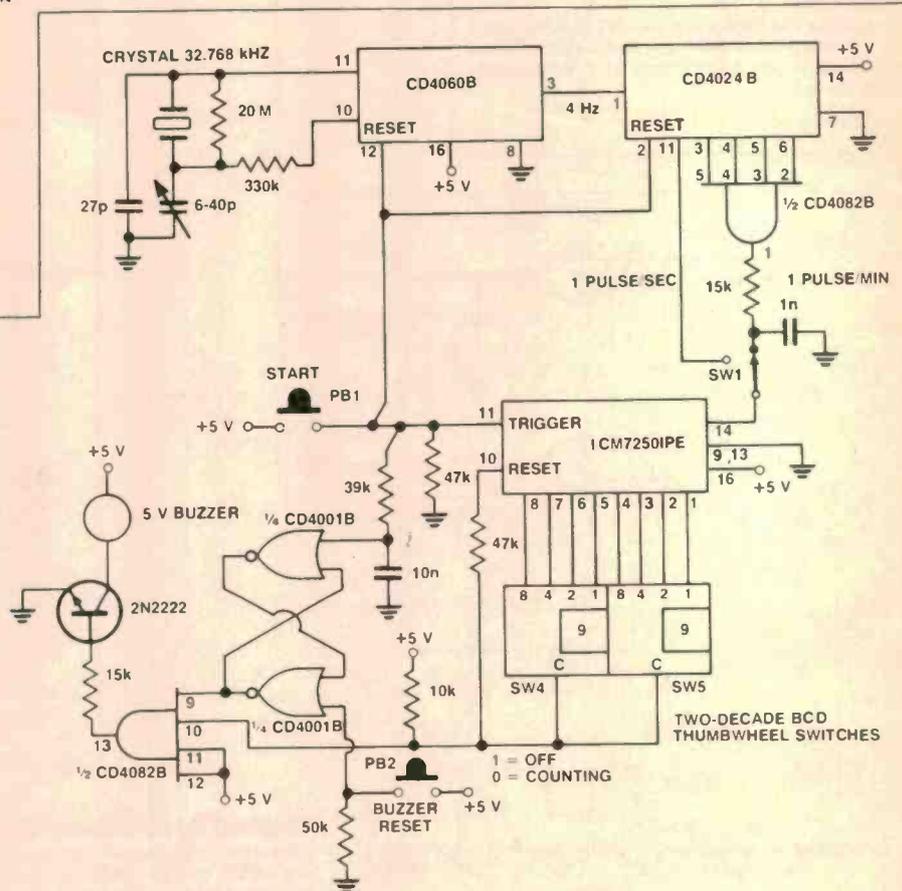
## Mains Time Delay Switch

Ideal for a corridor light timer. The switch is a main-rated momentary action pushbutton. When it's pressed, the timer will operate for a time equal to  $1.1 R_t C_t$ . At the end of this period, both the load and the circuit are disconnected.

NOTE:  
IC1 IS 555  
PIN 7 IS NOT CONNECTED  
Q1 IS BC337, ZTX300 ETC.  
SCR1 IS TIC 206  
ZD1 IS 12V ZENER



## Programmable 0-99 Seconds/Minutes Timer

This precision programmable timer can be set to time elapsed intervals up to 99 seconds in one second increments or 99 minutes in one minute increments, using two BCD thumbwheel switches. The timebase is selected with SW1 (seconds or minutes). The period is selected with the thumbwheel switches. This sets the 7250 programmable counter. The start pushbutton, PB1, resets the oscillator and counters and counting begins. The 7250 counts until the pre-programmed value is reached, at which time it resets, pin 10 of the 4082 is enabled and the buzzer sounds. Pressing PB2 turns it off.

# No 2 - WE TRY HARDER...

## MULTIPROM INTERFACE KIT

**\$99**  
MICROBEE 



SEE ETI NOVEMBER 1983

XM-1 - This is a totally new product developed EXCLUSIVELY for AVTEK - It takes two sets of EPROMs (e.g. WORDBEE and EDASM) and allows you to choose between them by simple KEYBOARD COMMANDS. It will take a short time to assemble and is simply installed inside the MICROBEE with one DIP plug (supplied) and two solder connections.

XM-1 - suits early model MICROBEE plus models using 2532 type EPROMs. These have serial numbers starting with 8 - ONLY \$19.95


XM-2 - same as XM-1 but suits the 'MICROBEE IC' and is even simpler to fit. Also responds to PAK1 and PAK2 commands. These have serial number starting with 9 - ONLY \$16.95

**MULTI ROM  
BOARDS SPECIAL**  
\$15 each JAN ONLY

See ETI Oct 1983

PCB - Manual and ROM \$149.00  
FULL KIT \$450 Jan Only Save \$25  
CP/M in 8" or 5 1/4" 1200 or 9600 Baud  
(please specify) ONLY \$150

## LITTLE BIG BOARD

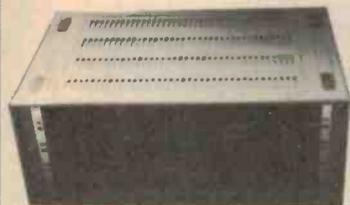

## EURO CASE SCOOP PURCHASE

4 UNIT HIGH IEC STANDARD RACK ENCLOSURE  
VENTED - NOTE THIS RACK SUITS THE APPLIED  
TECHNOLOGY RACK S-100 CARDFRAME  
HAS BEEN SOLD FOR \$189 - NOW ONLY \$99.00

AVTEK in  
the heart of  
"SILICON ALLEY"

## NEW STORE

## SPECIALS

20% SAVING

XLR CONNECTORS (CANNON TYPE)


3 PIN		5 PIN	
LINE MALE	\$2.80	LINE MALE	\$5.20
LINE FEMALE	\$2.80	LINE FEMALE	\$6.00
CHASSIS MALE	\$2.56	CHASSIS MALE	\$4.40
CHASSIS FEMALE	\$2.80	CHASSIS FEMALE	\$5.20



ONLY \$1.99

IEC MAINS LEADS - NO MAINS PLUG - OVER 1  
METRE - DON'T PAY \$3.95 - ONLY \$1.99  
LIMITED STOCK.

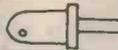5mm GREEN LED's - 10 FOR \$1.00 - THAT'S ONLY  
10 CENTS EACH!!




LOGIC PROBE AND UNIVERSAL PROBE BOTH  
REDUCED FROM \$9.50 TO \$5.95 EACH!

SAVE  
\$3.55

60 - 160pF TUNING CAPACITORS AS USED IN  
TRANSISTOR RADIOS AND LOTS OF OTHER  
PROJECTS - ALSO HAS SECOND GANG FOR FM  
2 FOR \$1.00

2 for \$1.00

2716 EPROMS ONLY \$3.50 EACH

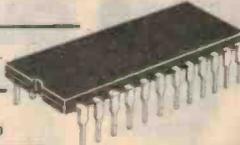

KEYBOARD SWITCH BUTTONS  
WITH BLANK TOPS ONLY \$1.00

SPECIALS FOR JAN ONLY  
OR WHILE STOCKS LAST

172 LIVERPOOL ROAD, ENFIELD  
Phone: (02) 745 2122

## AVTEK MULTI MODEM

See EA Jan 1984

EXCLUSIVE - ONLY \$229  
COMPLETE KIT



## NEW PRODUCT

RIGHT ANGLE MOUNTING LED - HIGH QUALITY  
HEWLETT PACKARD - AS USED IN AVTEK MULTI  
MODEM - COLOURS: RED, GREEN, YELLOW  
DON'T PAY \$1.40 ONLY 99 CENTS EACH



DON'T FORGET WE ARE PROBABLY  
THE LARGEST SELLER OF IC'S,  
COMPONENTS, IDC CONNECTORS,  
ALTRONICS KITS ETC. IN SYDNEY

**AVTEK**  
(ELECTRONICS) Pty. Ltd.



TWO GREAT LOCATIONS  
119 YORK STREET, SYDNEY 2000  
PHONE: (02) 267 8777  
(Above Charlie Browns Place)  
172 LIVERPOOL ROAD (HUME HIGHWAY), ENFIELD  
PHONE: (02) 745 2122  
All Correspondence to:  
P.O. BOX Q302, QUEEN VICTORIA BUILDING,  
SYDNEY 2000



POST AND PACKING  
Divide the value of your order by 20 (5%) to get post and  
packing value and then add \$2.00 - it's that simple!  
All Bankcard orders can only be sent to a normal address  
(NOT a P.O. Box). All Bankcard orders will be sent by  
registered mail (add \$3 to P&P charges).  
ENFIELD OPEN ON SUNDAY



**Critics rave about Dick's low prices!**

**BEST BARGAIN BASEMENT BOOK BUYS**

The story of Dick Smith's incredible Helicopter flight.

**The Earth Beneath Me**

The book everyone's been waiting for. Over 250 magnificent pages tracing Dick's epic solo flight across the world. Every step of the way is carefully detailed with superb full colour photographs. You'll be amazed at the quality.

● Maps of the journey.  
● The planning and co-ordination.  
● The equipment.  
● Even how to fly the helicopter.

**ONLY \$19.95**

SEEN ON JOHN LAWS' WORLD

**Radio & Television**

**Dick Smith's Australian Radio Frequency Handbook**

Get into the fastest growing hobby in Australia - scanning! This superb publication from Dick Smith Electronics gives you the how, why, where and when of this exciting hobby. Find out what's what and who's where! A must for scanner enthusiasts!

**2nd EDITION \$12.95**

Want Marine Radio facts?  
**Dick's Book Tells It All!**

The Australian Marine Radio Handbook - all the facts and figures for fitting and using a marine radio. Ideal if you've just bought a marine radio or considering purchasing one! Cat B-9604 **\$12.95**

**ARRL RADIO AMATEURS H'BOOK**

This amazing book just seems to get better each year! This volume contains new projects for 160m, VHF, power supplies and lots, lots more! **SAVE \$2 \$17.95**

Cat B-2218 WAS \$19.95

**WORLD RADIO/TV HANDBOOK**

Keep up to date! This authoritative directory of international radio and TV contains all the information you may want to know, including addresses, frequencies, call-signs, transmission times and more! Cat B-2083 WAS \$22.50 **SAVE \$4 \$18.50**

**COMPUTER BOOKS**

**BASIC Computer Games**

Learn how to write your first BASIC program in just one hour! This excellent book will teach you the basics of BASIC, the most popular computer programming language in the world!

Cat B-2368  
by Dr. Zaks  
**ONLY \$14.95**

**More BASIC Computer Games**

Evade man eating rabbits, play a war game with convoy, try & knock down a missile from the sky only on co-ordinates etc, etc! 84 fascinating and exciting games for solo and group play. Fascinating games in standard Microsoft BASIC from the world of Creative Computing mag.

Cat B-2354  
**ONLY \$11.50**

101 detailed games in Microsoft BASIC. Ideal programs for your System 80, TRS 80, Apple etc. Every game is complete with the actual program run, a sample of the game and an explanation by the author of the game.

Cat B-2351  
by D.H. Ahl  
**ONLY \$11.50**

**REFERENCE**

**AUSTRALIAN SEMICONDUCTOR HANDBOOK**

Murphy's law says you can never find the information you need. Murphy was wrong! This great book contains data, suggested circuits and an enormous variety of commonly-used devices. Written just for Australia! Cat B-4200

**ALL THE DATA YOU'RE LIKELY TO NEED! ONLY \$7.95**

**IC TIMER COOKBOOK**

Walter Jung 287 pages

Cook your own unique circuits with the dozens of recipes given in this book 50 applications of the timer IC's in individual circuits and larger systems are shown. Also explains the theory of operation of timer circuits. Cat B-1244

**ONLY \$13.50**

**CMOS COOKBOOK**

Don Lancaster - 416 pages

Superb publication crammed full with explanations, practical applications, and a mini catalogue of over 100 devices including pinouts and usage descriptions. Learn all about CMOS with this book. Cat B-1248

**ONLY \$19.95**

**VZ-200 OWNERS!!**

**Getting Started**

Impress your friends, instruct your kids & create your own utility and games programs in a matter of hours! Step-by-step instructions show you how simple it is to operate your new computer. Cat B-7206

**\$9.95**

**VZ-200 Introduction to Computing**

Are you lost when it comes to computing? Try this - written just for you in a language you can understand. It'll have you conversant with Dick's VZ-200 computer in just a few days! Cat B-7200

**\$9.95**

**First Book of Programs**

Tried, trusted and true programs for your VZ-200. There's something for everyone and remember, they're all written in BASIC so you can save these on cassette - you only have to key them in once! Cat B-7202

**\$6.95**

**Further Programming**

After mastering BASIC, what comes next? It's all in this book - moving graphics, using MODE(1), music and PEEK & POKE. As well as lessons, there are also 15 or so games which you're sure to enjoy. Cat B-7208

**\$9.95**

**VZ-200 Technical Manual**

Want to get the most from your VZ-200? This technical manual explains all the ins and outs, ups and downs. For the real computer enthusiast or the beginner who wants to know more! Cat B-7204

**\$9.50**

**The Giant Book of Games**

An exciting collection of some favourite computer games guaranteed to provide you with hours of fun. There's even a section devoted entirely to games ideas which you can convert into computer games. Cat B-7210

**\$9.95**

# NEW STORE: SOUTHPORT QLD.

## STORE LOCATIONS

<b>NSW</b>	Cnr. Swift & Young Sts. Parramatta Rd & Melton St T55 Terrace Level 613 Princes Hwy Oxford & Adelaide Sts 531 Pittwater Rd 147 Hume Hwy 162 Pacific Hwy 315 Mann St 4 Florence St Elizabeth Dr & Bathurst St 173 Maitland Rd, Tighes Hill Lane Cove & Waterloo Rds George & Smith Sts The Gateway, High & Henry Sts 818 George St 6 Bridge St 125 York St Tamworth Acde & Kable Ave 263 Keira St	<b>ALBURY</b> 21 8399 <b>AUBURN</b> 648 0558 <b>BANKSTOWN SQ</b> 707 4888 <b>BLAKEHURST</b> 546 7744 <b>BONDI JCT</b> 387 1444 <b>BROOKVALE</b> 93 0441 <b>CHULLORA</b> 642 8922 <b>GORE HILL</b> 439 5311 <b>GOSFORD</b> 25 0235 <b>HORNSBY</b> 477 6633 <b>LIVERPOOL</b> 600 9888 <b>NEWCASTLE</b> 61 1896 <b>NORTH RYDE</b> 88 3855 <b>PARRAMATTA</b> 689 2188 <b>PENRITH</b> 32 3400 <b>RAILWAY SQ</b> 211 3777 <b>SYDNEY</b> 27 5051 <b>SYDNEY</b> 267 9111 <b>TAMWORTH</b> 66 1961 <b>WOLLONGONG</b> 28 3800 <b>FYSHWICK</b> 80 4944 <b>COBURG</b> 383 4455 <b>FRANKSTON</b> 783 9144 <b>GEELONG</b> 78 6766 <b>MELBOURNE</b> 67 9834 <b>RICHMOND</b> 428 1614 <b>SPRINGVALE</b> 547 0522 <b>BRISBANE</b> 229 9377 <b>BURANDA</b> 391 6233 <b>CHERMSIDE</b> 359 6255 <b>SOUTHPORT</b> 32 9211 <b>TOOWOOMBA</b> 38 4300 <b>TOWNSVILLE</b> 72 5722	<b>ACT</b> <b>VIC</b> <b>QLD</b> <b>SA</b> <b>WA</b> <b>TAS</b>	<b>ADELAIDE</b> 212 1962 <b>DARLINGTON</b> 298 8977 <b>ENFIELD</b> 260 6088 <b>CANNINGTON</b> 451 8666 <b>PERTH</b> 328 6944 <b>PERTH</b> 321 4357 <b>HOBART</b> 31 0800
------------	---	--	--	--



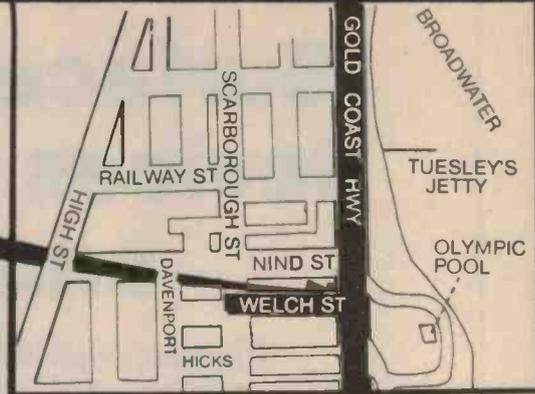
## STORE HOURS

All Dick Smith stores are open for trading during the normal trading hours for their particular area (either 9 - 5.30 or 8.30 - 5). Many stores are also open for late night trading. Please ring the store concerned for their particular hours.



Terms available to approved applicants through...



## MAJOR RESELLERS

● **Atherton Qld:** Maarten's Music Centre 55 Main St 91 1208 ● **Ballina NSW:** A. Cummings & Co 91-93 River St 86 2285 ● **Broken Hill NSW:** Hobbies & Electronics 37 Daise St 89 4098 ● **Calross Qld:** Electronic World Shop 27 K-Mark Westcourt Plaza, Mulgrave Rd 51 8555 ● **Caimeo Qld:** Thompson Instrument Services 79-81 McLeod St 51 2404 ● **Campbelltown NSW:** Fishers' Chip Shop, Shop 3, 274-276 Queen St 27 1475 ● **Coffs Harbour NSW:** Coffs Harbour Electronics, 3 Coffs Plaza, Park Ave 52 5984 ● **Darwin NT:** Vertronics, 24-25 Cavanagh St 81 3491 ● **Dawidville NSW:** Dan Electronics, 220 Drossy St 81 3672 ● **East Maitland NSW:** East Maitland Electronics 99 High St 33 7327 ● **Echuca Vic:** Webster Electronics 220 Pakenham St ● **Geraldton WA:** KB Electronics & Marine, 361 Main Terrace 21 2178 ● **Gladstone Qld:** Purely Electronics Shop 2 Cnr Herbert & Auckland Sts 72 4321 ● **Gosford NSW:** Tomorrow's Electronics & HiFi 68 William St 24 7245 ● **Inverell NSW:** Lyn Willing TV 22A Evans St 22 1821 ● **Katharine NT:** Cascade Electronics Shop 7 Commonwealth Bank Acde 72 2564 ● **Kingston Tas:** Kingston Electronics Channel Court 29 5082 ● **Launceston Tas:** Advanced Electronics 5A The Quadrant 31 7075 ● **Lisamosn NSW:** Decro Electronics 3A, 8-18 Carrington St 21 4137 ● **Mackay Qld:** Stevens Electronics 42 Victoria St 51 1723 ● **Merrybourn Qld:** Keller Electronics 219 Adelaide St 21 4559 ● **Mt Gambier SA:** Hutchesson's Comm 5 Elizabeth St 25 6404 ● **Mildura Vic:** McWilliams Electronics 173 Summer St 62 6491 ● **Port Macquarie NSW:** Half of Electronics 73 Norton St 83 7440 ● **Rockhampton Qld:** Purely Electronics 15 East St 21 058 ● **Shoeperton Vic:** G. V. Electronics Centre 1898 Coro St 21 8966 ● **Southport Qld:** Amateurs Paradise 121 Neering St 32 2644 ● **Toowoomba Qld:** Mum's Electronics 18 Nairn St 32 9677 ● **Townsville Qld:** Tropical TV 49 Fulham Rd, Vincent Village 79 1421 ● **Wagga NSW:** Wagga Wholesale Electronics 89 Forsyth St ● **Whyalla SA:** Mellor Enterprises Shop 2 Forsythe St 45 4764

## SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone your order and Bankcard details - it's so simple!

(02) 888 2105  
ORDER ONLY ON THIS NUMBER  
ENQUIRIES: (02) 888 3200

HEAD OFFICE AND MAIL ORDER CENTER:  
P.O. Box 321, NORTH RYDE, NSW 2113.  
TEL. (02) 888 3200

POST & PACKING CHARGES		CHARGE	
ORDER VALUE	CHARGE	ORDER VALUE	CHARGE
\$5.00 - \$9.99	\$2.00	\$50.00 - \$99.99	\$5.00
\$10.00 - \$24.99	\$3.00	\$100.00 or more	\$6.50
\$25.00 - \$49.99	\$4.00		


Charges are for goods sent by post in Australia only - not airmail, overseas or air freight.

### Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days. Or unforeseen circumstances might hold up shipments so that advertised lines are not in the stores by the time the advert appears. And very occasionally, an error might slip through our checks and appear in the advert (after all, we're human too!). Please don't blame the store manager or staff - they cannot solve a dock strike on the other side of the world, nor fix an error that's appeared in print. If you're about to drive across town to pick up an advertised line, why not play it safe and give them a call first... Just in case!

Thanks

Dick Smith & Staff

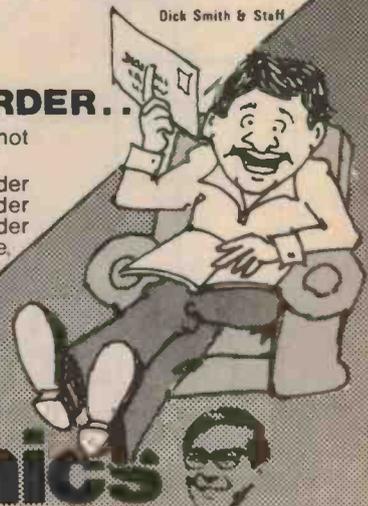

## CONSIDER THE ADVANTAGES OF SHOPPING BY MAIL ORDER...

\* Lightning Fast Service - our fully computerised mail order centre will have your goods speeding back to you within 24 hours of receipt - maximum! (Normally, they're even quicker!)

\* Special 14 day Satisfaction Guarantee - our normal 7 day Satisfaction Guarantee is extended to 14 days for mail order customers: If you're not absolutely delighted, return your purchase within 14 days (in original condition) for a full refund. What can you lose?

\* New products, mail-order-only specials, etc: as a mail order customer, you'll receive up to 6 bargain packed mailers per year AND, from time to time,

special offers for mail order customers only (not even available from our stores!)

\* Above all, our 15 years of reliable mail order experience. You know when you send us an order we'll be around to serve you: some mail order companies have given the industry a bad name, but Dick Smith Electronics sets the high standards others try to match. You can trust Dick Smith Electronics.

# DICK SMITH Electronics

DSE/A681/PA1

# Surface acoustic wave devices — fundamentals and applications

The basic physics of SAW devices was examined in part 1. In this article a major application of time coded SAW filters, spectrum analysis, is explained.

P. J. Hall

Physics Department, University of Tasmania

## Part 2

THE THIRD MAJOR use of time-coded SAW filters is in spectrum analysis and, as in chirp radars, the basic component is the dispersive delay line (Figure 10).

Before examining SAW spectrum analysis methods, it is useful to consider alternative techniques and their limitations. This section is mainly concerned with analysis systems designed for on-line signal processing applications. In such applications, spectrum analysis is used to obtain information about signals on a real-time 'as the action happens' basis, perhaps in order to control some other process e.g. the electrical steering of an antenna array to minimise interference to a radio link.

The most obvious way of analysing a given bandwidth is to assemble a bank of

frequency contiguous filters covering the analysis bandwidth and to relate the output of each filter to the spectral energy falling within the passband of that filter. Filterbanks are commonly used in audio, radio astronomy and some military applications with refinements dependent upon the specific use.

Unfortunately, when a large bandwidth is to be analysed with good frequency resolution, the number of filters becomes prohibitively great and the analyser becomes large, expensive, difficult to align, and difficult to keep in alignment. Filterbanks consisting of SAW bandpass filters are now available and offer an excellent alternative to LC filters in some RF applications, although in most situations the more elegant SAW techniques to be described would normally be used.

## Spectrum analysis

Conventional scanning spectrum analysers are acceptable for laboratory use but are too slow and too wasteful of signal energy to be used in most signal processing roles. A signal shorter than the time the analyser takes to scan the analysis bandwidth can come and go without ever registering on the instrument.

In military jargon, the analyser has a very low probability of intercept (POI). If the scan rate is increased to raise the POI, the available frequency resolution is decreased. The scanning analyser wastes energy because if 'N' frequency resolution cells are resolved across the analysis bandwidth, the time spent actually looking at each cell is only 1/Nth of the total observing time.

Digital spectrum analysers based on the Fast Fourier transform (FFT) algorithm are

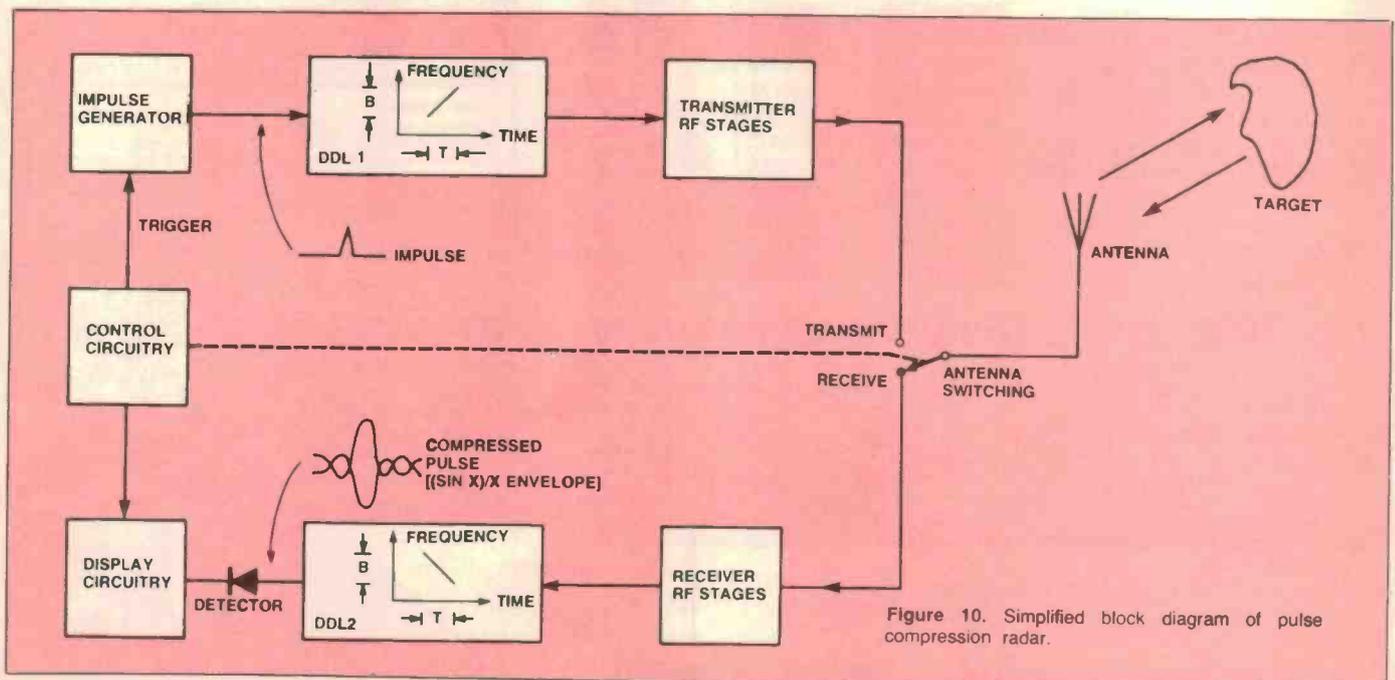


Figure 10. Simplified block diagram of pulse compression radar.

now familiar in audio test and development laboratories as well as in some signal processing applications. FFT methods produce accurate spectra and are capable of conveniently providing a true Fourier transform i.e. phase as well as amplitude, or power of spectral components. Unfortunately, the analysis bandwidth for real-time FFT processors is currently rather limited with most commercial units being essentially audio analysers.

A second digital method of power spectrum analysis, the auto-correlation technique, can be extended to wide bandwidths but is not suitable as a general approach, particularly in applications where high time resolution i.e. large number of spectra per second is needed.

Another instrument sometimes used for spectrum analysis in radio astronomy and military applications is known as the acousto-optical spectrum analyser. This device relies on the interaction of laser light with RF sound waves in a translucent piezoelectric crystal. Wide bandwidths can be analysed with good frequency and time resolution but current designs are plagued with a number of practical problems, the most serious being mechanical and thermal instability and limited dynamic range.

Coherent (phase sensitive) acousto-optical processors have been described but with existing technology, practical problems in such systems are acute. Integrated acousto-optical processors which utilise the interaction of light from a solid state laser with surface acoustic waves may substantially avoid the problems of existing optical analysers.

SAW dispersive delay line spectrum analysers overcome many of the disadvantages of the other types of instruments and offer a state-of-the-art solution to the problem of real-time, wideband Fourier analysis.

### Compressive receiver

A block diagram of a SAW 'compressive receiver' spectrum analyser is shown in Figure 11. This configuration, which is only one of several possible arrangements, uses two SAW dispersive delay lines (DDLs) similar to the type used in the chirp radar system described earlier.

One DDL is used to expand an impulse into a chirp, and this chirp is then mixed with signals in the band to be analysed. Consider CW input signals for simplicity. Each signal produces a chirp from the mixer which is time co-incident with, but offset in frequency from the other chirps. This is illustrated in the frequency-time diagram for the process (Figure 12).

Signals spaced in frequency at the input produce chirps which enter the passband of the second DDL, the convolver, at different times. The chirp slope of the convolver is the exact inverse of the expander DDL chirp slope so chirps entering the convolver emerge as compressed pulses, just as in the pulse compression radar. In this case however, chirps due to different input frequencies enter the convolver at different times, so the compressed output pulses are separated in time.

Hence, separation in frequency at the compressive receiver input produces separation in time at the output, so the instru-

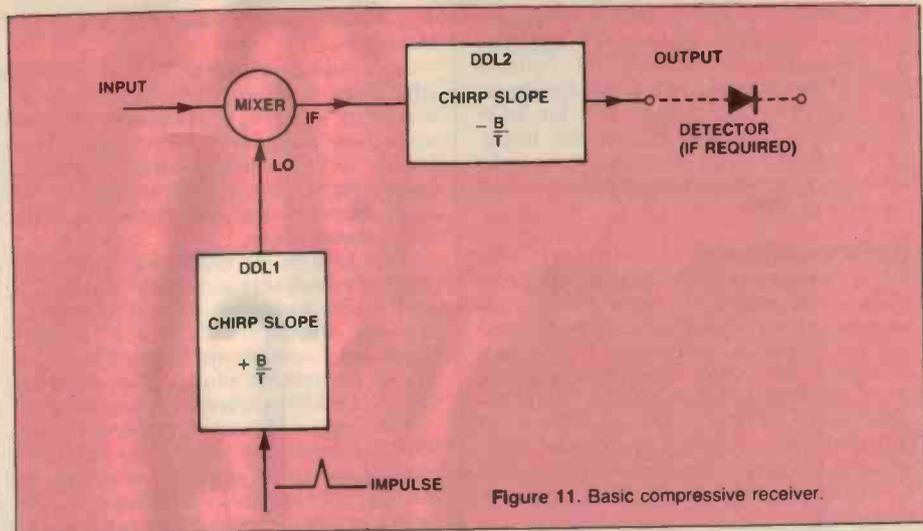


Figure 11. Basic compressive receiver.

ment functions as a spectrum analyser. The time axis on a display device e.g. an oscilloscope can be read as frequency by using the convolver chirp slope as a scaling factor, i.e.  $f = (B/T)t$ . This process is an example of the 'chirp transform' and, as mentioned earlier, other practical implementations are possible.

Several key characteristics of the compressive receiver are related to the time-bandwidth product,  $N = BT$ , of the convolver. As expected, the width in time of the compressed pulses is of the order of the reciprocal bandwidth,  $1/B$ . The receiver takes  $T$  seconds to analyse the total bandwidth,  $B$ . The number of identifiable frequency resolution cells is therefore about  $T/(1/B)$  or  $N$ , so the time-bandwidth product is analogous to the number of channels in a filterbank or the number of points in a

digital FFT analyser. The equivalent width in frequency is simply  $B/N$  or  $1/T$ .

It can be shown that if a compressive receiver is designed to give a frequency resolution equivalent to a scanning spectrum analyser, the compressive receiver can analyse the input bandwidth a factor of  $N$  faster than the scanning analyser. Since  $N$  can be up to 20 000 with currently available SAW devices, the advantage can be very large. As shown in Figure 12, it is usual to use an expander chirp with twice the bandwidth and duration of the convolver impulse response.

This ensures that chirps due to signals at either edge of the analysis bandwidth emerge from the convolver fully compressed, but it also means that chirps due to some very short duration input signals can fall outside the convolver bandwidth for part of the active cycle of the receiver. ▶

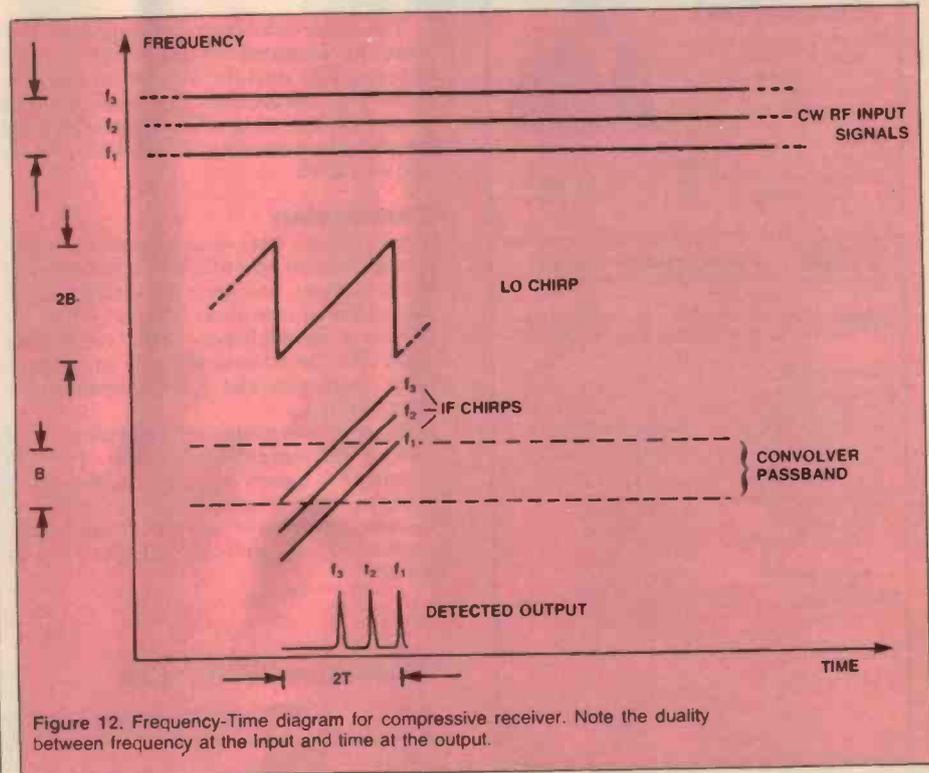


Figure 12. Frequency-Time diagram for compressive receiver. Note the duality between frequency at the input and time at the output.

The effect is to lower the POI to 50% for signals of duration less than T (typically microseconds). Nevertheless, this figure is much higher than the POI factor for almost all other analysers. A high POI for SAW compressive receivers makes the instruments popular with military users, who often use more advanced techniques to raise the POI to 100%.

### SAW analysers

When compared with digital spectrum analysis techniques, the most obvious advantages of SAW analysers are high speed and wide analysis bandwidth. It has been estimated that SAW analysers exhibit a speed advantage of from 100 to 10 000 depending on the DDLs used and the type of digital instrument used as the basis for comparison. In certain applications the overall benefit of adopting SAW technology can be very great.

For example, the authors of a U.S. paper describing a sophisticated SAW signal processing module claim an advantage factor for SAW technology over digital methods of 12 000. This figure is based on a system figure of merit defined as 'the equivalent number of complex multiples per second per dollar of development cost'.

SAW processors are similar to digital instruments in that both are capable of providing amplitude and phase spectra and, as such, are useful in roles requiring coherent signal processing. Part of the recent work in radio astronomy at the University of Tasmania has been to demonstrate that coherent SAW spectrum analysers are

viable now, using existing technology and techniques.

In contrast, coherent optical methods (the main rival to SAW technology for wideband, real-time applications) are some way from being fully developed. As a bonus, SAW technology offers a dramatic improvement over optical methods in the areas of mechanical and thermal stability, and dynamic range.

The limitations associated with SAW spectrum analysers are fairly minor. The analog transformation process exhibits an accuracy equivalent to a 6 or 7 bit digital transform. For many applications this is sufficient, particularly when the speed advantage of a SAW instrument is considered.

The second practical problem is that SAW analysers are simply too fast to be directly useful in applications where the instruments need to be interfaced to computers or other digital post-transformation devices. For example, two University of Tasmania spectrum analysers output data at a rate of around 40 ns per frequency resolution cell, and this is the rate at which a digital processor needs to sample the detected output.

We have solved the problem by producing 'digital video integrators', or DVIs, to act as an interface between the SAW analysers and slower logic. A DVI samples the analyser output at high speed and adds together many spectra before the integrated spectrum is output to a computer or other device. The DVI runs continuously so there is no loss of new data while the integrated spectrum is output.

This process degrades the time resolution slightly but, even so, the integrated spectrum time resolution can approach 100  $\mu$ s with existing data acquisition computers. Of course, the wide-band, coherent processing capability of SAW spectrum analysers is retained.

The DVI techniques developed in Tasmania have created interest overseas, and it is hoped that with the local VLSI program underway, further work can be undertaken on the design of an Australian produced parallel processor ship for use in the back-end of a DVI.

### Conclusion

These articles have summarised some important current uses of SAW technology but the treatment has been necessarily brief. Discussion of important devices such as reflective array compressor (RAC) dispersive delay lines, non-linear acoustic convolvers, SAW oscillators and SAW memories has been omitted.

Interested readers are referred to the general references listed below. For the benefit of designers considering using SAW devices I have provided a list of suppliers known to me. Most companies can supply customised as well as standard stock devices.

### GENERAL REFERENCES

1. Butler, M.B.N., 'Surface acoustic wave devices', *Electronic Engineering*, June 1980, July 1980, February 1981.

- Dieulesaint, E. and Royer, D., 'Elastic waves in solids', Wiley, 1980.
- Hartmann, C.I.S. et al., 'SAW devices for military, communications, radar and EW systems', *Microwave Journal*, July 1982.
- Oliner, A.A. (Ed.), 'Acoustic surface waves', Springer-Verlag, 1978.
- Penimuri, D. and Havens, D.P., 'Surface acoustic wave filters prove versatile in VHF applications', *Electronics*, July 5, 1979.

### SAW DEVICE SUPPLIERS

- Andersen Laboratories Inc., 1280 Blue Hills Avenue, CT 06002, USA. TWX 710-425-2390.
- Crystal Technology Inc., 1035M E. Meadow Cir., Palo Alto, CA 94303, USA.
- GEC—Marconi Research Centre, Great Baddow, Essex, CM2 8HN, U.D. Telex 99201.
- Hughes Aircraft Company, Gound Systems Group, P.O. Box 3310, Fullerton, CA 92634, USA.
- Racal-MESL Ltd., Lochend Industrial Estate, Newbridge, Midlothian, EH28 8LP, U.K. Telex 72384.
- RF Monolithics Inc., 4441 Sigma Road, Dallas, Texas 75234, USA.
- Siemens Ltd., Australian Office, 544 Church Street, Richmond, Victoria, 3121. Telex AA30425.
- Signal Technology Ltd., Cheney Manor, Swindon, Wiltshire, SN2 2PJ, U.K. Telex 444410.
- Thomson-CSF, Chemin des Travails, B.P. 53, 06802 Cagnes-Sur-Mer, France. Telex 204.780F.

## Train at home for a better career

Choose from 32 opportunities!

Now without attending school or university, without any previous experience, you can train at home in your spare time for a money making career... even obtain a Career Diploma. Send for free facts about the exciting programme that interests you most. Mail coupon today and you will receive complete information that shows you how easy it is to qualify for a great new career or advancement in your present job.



**ICCS** — SEND FOR FREE FACTS!

International Correspondence Schools  
400 Pacific Highway, Crows Nest  
NSW 2065

**YES!** Please send me without cost or obligation free facts on how I can study at home for the career I have chosen.

#### TICK ONE BOX ONLY!

- |   |   |
|---|---|
| <input type="checkbox"/> Computer Programming           | <input type="checkbox"/> TV Technician          |
| <input type="checkbox"/> Business Management (IBA)      | <input type="checkbox"/> Sales/Marketing (AMI)  |
| <input type="checkbox"/> Executive Management           | <input type="checkbox"/> Civil Engineering      |
| <input type="checkbox"/> Small Business Owner           | <input type="checkbox"/> Electrical Engineering |
| <input type="checkbox"/> Refrigeration/Air Conditioning | <input type="checkbox"/> Mechanical Engineering |
| <input type="checkbox"/> Hotel/Motel Management         | <input type="checkbox"/> Pharmacy Assistant     |
| <input type="checkbox"/> Practical Accounting           | <input type="checkbox"/> Secretarial            |
| <input type="checkbox"/> Management Accounting          | <input type="checkbox"/> English Language       |
| <input type="checkbox"/> A.C.I.S. Coaching              | <input type="checkbox"/> Recreational Art       |
| <input type="checkbox"/> Auto Mechanic                  | <input type="checkbox"/> Commercial Art         |
| <input type="checkbox"/> Motorcycle Maintenance         | <input type="checkbox"/> Photography            |
| <input type="checkbox"/> Building                       | <input type="checkbox"/> Interior Design        |
| <input type="checkbox"/> Builder's Draftsman            | <input type="checkbox"/> Guitar                 |
| <input type="checkbox"/> Drafting                       | <input type="checkbox"/> Commercial Writing     |
| <input type="checkbox"/> Architecture                   | <input type="checkbox"/> Short Story Writing    |
| <input type="checkbox"/> Electronics                    | <input type="checkbox"/> Dressmaking            |

Mr/Mrs/Miss

Address

P/code

Phone

(Home)

Tick Here If Full Time Student

0682

Ian J. Truscotts

## ELECTRONICS WORLD

For all your Electronic needs

- KITS
- COMPONENTS
- TOOLS ETC.

Resellers of Dick Smith Alltronics

Call in and browse around

Cnr. Bayswater & Eastfield  
South Croydon

Phone  
723 3860

# JAYCAR QUALITY MEANS PERFORMANCE RESULTS

## FM Transmitter Module

We have been working on this one for years!! Basically we wanted something akin to the \$6.50 kit "wireless microphone" transmitter but with greater signal strength and far, far greater frequency stability. WE NOW HAVE IT!! Basically the (potted) unit measures a small 90 x 22 x 15mm and has connections for power, antenna and input. An AC signal between 20 and 15kHz will modulate the transmitter. The signal can be coded single or multiple frequency tone bursts etc.

### FEATURES

- Ultra low noise output (-60dB or better attainable with a suitable tuner)
- Excellent frequency stability
- Not a kit - ready for immediate use
- Connections required
  - (a) Power supply or battery
  - (b) Antenna
  - (c) Audio input
- Full instructions supplied
- Suits any application where a stable low noise FM link is required

### SPECIFICATIONS

- Frequency - 88 - 108MHz adjustable
- Useable range - 50 metres
- Supply - 6 to 9V at 20mA
- Input sensitivity - adjustable - maximum 30mV
- Pre-emphasis - 50µ/second standard
- Dimensions - 90 x 22 x 15mm (approx)

Cat. DT5450 **\$49<sup>95</sup>**



## SOLDERING IRON TEMP. TESTER

### EASY TO USE!!

Apply solder to the tip of soldering iron and then press the temperature sensor as shown.



READS TEMP IN DEGREES CENTIGRADE!

**NEW**

**\$29<sup>95</sup>**

Cat. QT-2100


**IDEAL FOR ALL TEMP. CONTROLLED IRONS**

Temperature is the most important factor for soldering! Prevent precision parts from burning intermittent connection.

When you solder electronic parts to the printed circuit board, you should know the proper temperature. Improper temperature can cause damage to parts or cold soldering.

## UNIDIRECTIONAL ELECTRET MICROPHONE INSERT

**NEW**

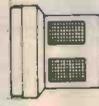

only **\$3<sup>95</sup>**



Just out in time for the new EA Parabolic Microphone project! (Ref: EA Nov. '83). This brand-new direct import unit has an average sensitivity around 7dB BETTER than the common low cost Electret insert.

The unit (Cat. AM-4012) has a front-to-back ratio of 1.5:1. The power requirements are the same as for the low cost mic. insert.

Each insert is supplied with a comprehensive data sheet which includes connection details, specs, and frequency response graph.

Be early as they may be in short supply around Xmas.

Cat. AM-4012

ONLY \$3.95


## Z-80 MICROCOMPUTER DESIGN PROJECTS

### Z-80 MICROCOMPUTER DESIGN PROJECTS

Gives you a solid, in-depth look at the highly popular Z-80 microprocessor, the heart of many contemporary microcomputers. Provides a complete look at the internal architecture of the Z-80, and even shows how to build a microcomputer, the EZ-80, using this powerful chip. The book may be used by the experienced electronics enthusiast as a training course and is also highly valuable to the computer hobbyist. By William Barden, Jr. 208 pages, 8½x11" soft.

Cat. BS-0596

\$23.95

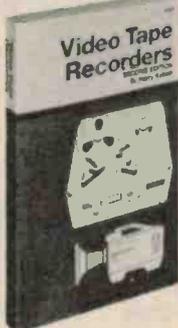

### TELEPHONE PUSH BUTTON PAD

High quality heavily gold plated (over \$0.90 worth of gold in each unit) contacts! (Each contact is a type of double-wipe changeover) Very high quality, as removed from imported telecommunications equipment. Virtually brand new. Each of the 12 keys is separately addressable. The possibilities are endless!!!

GRAB A FEW, THEY WON'T LAST!! ONLY \$3.95 each!!

Cat. SP-0750



### QUALITY!! "USELESS" COIL VOLTAGE ANRITSU Quality

Japanese Relay  
- As used in Telecom equipment  
- 6 Changeover contacts!!  
- 48 Volt Coil?  
48V Coil!!!!

How useless you say?  
Well, if you can find a use you won't pay much!  
ONLY 50 cents each - Cat. SY-4015

**ONLY 50c each or 10 for \$3!!**


## VIDEO TAPE RECORDERS (2nd Edition)

VIDEO TAPE RECORDERS (2nd Edition)  
In this completely revised 2nd edition of Video Tape Recorders, the author tells in simple language how helical vtr's work and how to operate or service them. Includes numerous examples of electronic circuits and mechanical systems. By Harry Kybett. 400 pages, 5½x8½" soft.

Cat. BS-0610

\$15.95

**ONLY \$15.95**

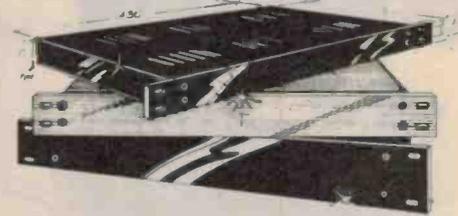

Beautifully crafted all aluminium rack cabinets with top and bottom removable panels. Plain or black finish. Ventilated lid. Deluxe brushed anodised front panel. Supplied in flat pack but take only minutes to put together. Dimensions conform to International Standard.

Cat. No.	FINISH	PRICE 14	PRICE 5 or MORE	Front panel	
				height	width
HB-5411	Natural	\$42.50	\$39.95	44	132
HB-5413	Natural	\$49.95	\$47.50	44	132
HB-5415	Natural	\$55.00	\$49.95	88	132
HB-5410	Black	\$42.50	\$39.95	88	132
HB-5412	Black	\$49.95	\$47.50	132	132
HB-5414	Black	\$55.00	\$49.95	132	132

### QUALITY "AIRPAX" DC CIRCUIT BREAKER

Unbelievable Bargain. Quality Airpax US MADE unit features large on/off rocker switch and snap-in panel mount capability.

#### Specs:

- Trip current 10 amps
- Full load 8 amps @ 50V DC
- Delay 59ms
- Measures: 35(d)x40(h)x18(w)mm body only

**10+ \$1.95 ea**

Cat. SY-4080



## Jaycar Incorporating ELECTRONIC AGENCIES

SYDNEY

SHOWROOMS

117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614

TELEX: 72293

CARLINGFORD

Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

CONCORD

115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

### NUMBER 1 FOR KITS

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)

\*Free INSURANCE for Road & Registered Post over \$200\*

All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE

Mon - Fri 9am - 5.30pm Sat - 9am - 12pm Thurs night 8.30pm

SHOP HOURS SYDNEY

Mon - Fri 8.30am - 5.30pm Sat - 8.30am - 12pm Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order By



**BANKCARD Via Your Phone**

# 10-50% OFF SALE!!

## low cost hi fi

That's right a 3-WAY HI FI speaker kit from only \$19.98!!  
 Each kit contains a massive 10" (250mm) woofer, cone midrange and DOME tweeter!! You also get, at no extra charge, the special cross-over capacitors!  
 The system is rated at approximately 20 watts RMS so it is ideal as an economical but reasonably powerful main Hi Fi unit or as a second system for another room or outdoors.  
 Each 3-way kit comes with a recommended enclosure design which you can build yourself easily!  
 You would normally pay well over \$60 for the equivalent from major kit speaker suppliers so this is an outstanding bargain. Sensitivity of system 93dB/1m/1 watt. Cat. AK3700  
**HURRY LIMITED STOCKS and they are made in JAPAN!!**



SAVE \$5

Amazing Value

Woofer not to same scale as other components

3-WAY SYSTEM  
\$24.95 a set

NOW \$19.95

2 SETS FOR STEREO (6 spkrs)  
ONLY \$39.95

NOW \$34.95

SAVE A FURTHER **20%**

## UHF AMPLIFIER SENSATION

MASSIVE SCOOP PURCHASE! MANUFACTURERS DISTRESS STOCK!  
 Jaycar has purchased a quantity of genuine Brand New MOTOROLA Brand MHW-710-1 UHF Power Amplifier modules. These units are designed for Industrial and commercial FM transmitters!  
 The unit (pictured) is a rugged, tuned train of RF Power Amplifier transistors featuring thin-film gold metallization, laser trimmed Nichrome resistors and MOS capacitors. The MHW-710-1 bolts to any flat metal surface to assist heat dissipation.


**SPECIFICATIONS:**  
 - RF POWER OUT @ 12.5V 13 WATTS - RF POWER OUT @ 15V 17 WATTS!!  
 (BOTH OF THE ABOVE RATINGS ARE LIKELY TO BE EXCEEDED AS MOTOROLA'S POWER RATING CLAIMS ARE CONSERVATIVE)  
 - 19.4 dB (Min) POWER GAIN. TYPICAL DRIVE LEVEL TO FULL POWER 90 - 150mW  
 - FREQUENCY BAND 400 - 440MHz. Will work to 450MHz and therefore covers the AUSTRALIAN UHF AMATEUR BAND!!  
 CIRCUIT DIAGRAM INCLUDED

Each MHW-710-1 comes individually packed with full manufacturers data. A manufacturers recommended circuit is included (only a few external components required), as well as a PCB pattern for the circuit. This component makes an ideal base for a "Home Brew" UHF Linear Amplifier! GREAT for UHF Mobile! SERVICEMEN

The MHW-710-1 has been used extensively in Australian Manufactured UHF Mobile 2-way radios. If you own or service a UHF radio that uses this part, now is your chance to grab a spare at an unrepeatable price! The MHW-710-1 sells for A\$68 plus tax in the USA.

QUANTITIES STRICTLY LIMITED  
 To be fair to all, we have limited this offer to 2 per person. Jaycar's Scoop offers are so successful that usually hundreds miss out. Even at 2 per customer we will probably run out quickly. Be early to avoid disappointment!!

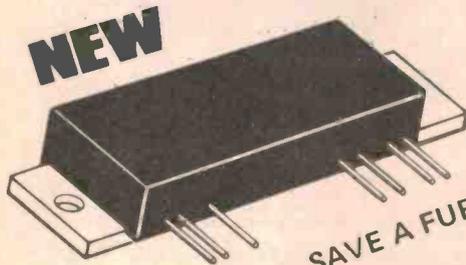STAGGERING VALUE! ONLY \$39.95!! - Cat. ZK 8882



NEW

AMATEURS PLEASE NOTE  
UP TO 25% OFF!!

SAVE A FURTHER \$10  
**BIG SAVINGS**

NORMALLY \$39.95 THIS MONTH \$34.95

10 UP PRICE FOR CLUBS - \$29.95 EACH

### 12" WOOFER



THIS PRICE CAN NEVER BE REPEATED  
 80 WATT HANDLING - ABOUT 40W R.M.S.  
 EUROPEAN QUALITY - MADE IN DENMARK  
 FREQ. RESPONSE 35 - 4000Hz  
 RESONANCE FREQUENCY 35Hz  
 Cat. CE-2130

SOLD WELL FOR  
 \$29.75  
 IN NOVEMBER  
 JANUARY ONLY  
 \$19.95 SAVE 33%

## codemaster

ONLY \$4<sup>98</sup>

This is a very popular game that is well known under another name! The Codemaster measures 140(l) x 85(w) x 25(d)mm, looks similar to a pocket calculator and runs off a 9V cell. The idea of the game is to come up with the hidden code in the minimum of moves.  
 Cat. XM-7015

SAVE **50%** 10 UP  
 \$4.50 ea

ONCE SOLD FOR \$24.50!



TOP QUALITY LINED  
 PRINTER PAPER  
 TRACTOR FEED

At last at an affordable price

TO SUIT SUPER 80 240mm WIDE  
 XE-1260 \$39.50  
 380mm XE-1262 \$47.50

2000 SHEETS PER BOX

CENTRONICS PLUG  
 36 WAY  
 Cat. PP-2420  
**\$14.95**



"MAGNAVOX" QUALITY  
 8" WOOFER

POPULAR MODEL 8J  
 8 ohm 8" widerange  
 - Power handling 12W RMS  
 - Freq. Resp. 55 - 7000Hz  
 Cat. CE-2333

\$7.50 each

Quality Speakers \$7.50 at low price



# 10-50% OFF SALE!!

## Sparkrite

The Brandleaders in Auto Electronics

THE BRAND LEADER

Each kit is complete down to the last nut & bolt. All fittings included! SX-2000, UK's largest selling electronic ignition! "Reactive Discharge" system - NOT CDI - with great reliability. Cat. KJ-6650

### Sparkrite SX2000

- A Reactive Discharge System combines all features of the SX500 plus.
- Reactive Discharge electronics combining all the advantages of both Inductive and Capacitive Discharge for maximum spark performance.
- Gives the most thorough combustion of air/fuel ratios especially current lean mixture emission controlled engines.
- Voted "Accessory of the Year" and the best as tested by Popular Motoring Magazine.
- Patented clip-to-coil fitting.
- Systems Function Light as well as Static Timing Light.
- The ultimate brand leading contact-breaker triggered system.



outstanding

\$ 59 \*

TX-2002. Breakerless Ignition! Full fitting kit to convert 90% of all cars! All contactless hardware supplied. No drilling or tapping. You can easily convert - and even use your points to work the TX-2002! Cat. KJ-6652

### Sparkrite TX2002

- A Reactive Discharge System - with unique auxiliary circuit. Combines all features of the TX1002 plus:
- Reactive Discharge electronics combining all the advantages of Inductive and Capacitive Discharge for maximum spark performance.
- Gives the most thorough combustion of air/fuel ratios especially current lean mixture emission controlled engines.
- Unique 3-way change-over switch incorporating an auxiliary back up circuit. "ELECTRONIC/OFF/AUXILIARY"
- Robust die-cast case. Fully resistant to moisture and heat.
- The ultimate system - REACTIVE DISCHARGE - CONTACTLESS OR CONTACT TRIGGERED - AUXILIARY BACK UP CIRCUIT - CLIP-TO-COIL FITTING - FOUR CONNECTIONS ONLY - ALL PARTS IN ONE BOX TO FIT OVER 500 APPLICATIONS.




\$ 99 \$115

TX APPLICATIONS  
No separate fixing kit required. All parts in one box, to fit more than 500 vehicles.
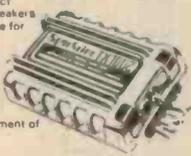
### Sparkrite TX1002

- An Inductive Discharge System
- Can be operated utilising "Hall Effect" triggerhead, or existing contact-breakers
- Extended dwell Inductive Discharge for maximum spark efficiency.
- Three position switch.
- Static Timing Light.
- Systems Function Light.
- Patented clip-to-coil fitting.
- Robust die-cast case.
- Fully waterproof.
- Protected from the hostile environment of the engine compartment.



\$79

amazing value only \$ 69 \*

### Sparkrite AT-80

\$99 Value \$ 89

Brilliant Computer Programmable Car Security System! This kit, the famous British Sparkrite AT-80 is absolutely unique. It uses a self-adhesive sensor pad that attaches to the inside of your gear mechanism. You have a special key fob (2 are supplied) and you program YOUR SPECIAL CODE in from the OUTSIDE OF THE CAR to get back in. The windscreen pad is a REAL deterrent device! Cat. KJ-6650



BEWARE! CHECK TO SEE IF "APPARENTLY" CHEAPER UNITS OFFER THE SAME FEATURES AS THE VOYAGER. @ p. FUEL CONSUMPTION IN LIT/100KM AND MPG!



### CAR COMPUTER

BELOW \$200

Value

\$199

THIS MONTH

\$179

SAVE \$20!!



COMPLETELY BUILT AND TESTED - NOT A KIT!!

#### FEATURES


- INSTANT FUEL CONSUMPTION IN LITRES/100KM AND MPG!! (MOST OTHERS HAVE ONLY ONE OF THE ABOVE) JUST SWITCH FROM ONE TO THE OTHER AS YOU DRIVE ALONG.
- INSTANT SPEED, TIME AND OTHER FUEL DATA.
- VISUAL AND AUDIBLE EXCESS SPEED ALARM.

SEND SAE FOR MORE DATA

Cat. XC2010

HURRY LIMITED STOCKS!!! \*
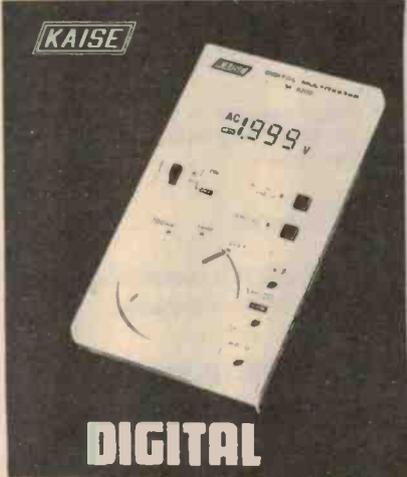
### THE ALL SINGING ALL DANCING MULTIMETER



- Scoop purchase of quality "KAIZE" Japanese 3 1/2 digit LCD digital multimeter.
- Manual range override (Normally auto-ranging)
  - A must. Zero adjust button. Calibrates meter if you change test probes
  - Virtually "open circuit" input impedance
  - Magnificent clear LCD readout
  - Most significant digit flashes if out of range
  - Tone beeper for status identification
  - 4-1000V DC, 600V AC
  - Resistance & Current ranges (AC & DC)
  - Lo ohms range for checking semis
  - 4mm banana plug leads on industry standard 19mm centres
  - High current shunt available
  - Fuse protected. Spare fuse provided
  - Inside case.
- Cat. OM-1525

### DIGITAL MULTITESTER

\$59.95

#### SPECIAL NOTE...

Jaycar will not be knowingly undersold FOR GOODS OF THE SAME QUALITY. If you find that a competitor is cheaper, get all the facts and tell us! If you are right we will match OR LOWER his price! Please understand that we cannot match the price of goods that are NOT the same quality as ours.

## Jaycar

Incorporating ELECTRONIC AGENCIES

SYDNEY SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
TELEX: 72293  
CARLINGFORD  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444  
CONCORD  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077  
HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

### NUMBER 1 FOR KITS

PDST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)

"Free INSURANCE for Road & Registered Post over \$200"  
All heavy or bulky items (over 20kg) sent Comet Road Freight \$12.00 anywhere in Australia.  
SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE  
Mon - Fri 9am - 5.30pm; Sat - 9am - 12pm; Thurs night 8.30pm  
SHOP HOURS SYDNEY  
Mon - Fri 8.30am - 5.30pm, Sat - 8.30am - 12pm; Thurs night 8.30pm  
MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order By



BANKCARD Via Your Phone

## THE MICROPROFESSOR SERIES



### MPF-1 PLUS

COMPLETE Z-80 BASED MICROCOMPUTER SYSTEMS FOR HARDWARE/SOFTWARE TEACHING & DEVELOPMENT

The Micro-professor 1 gives you all you need to join the growing world of microcomputing. It's a fully developed, tested and proven system that gives you step by step, start-to-finish hands on instruction.

#### The Original MPF-1B

- Interactive 2K Monitor Enter program in RAM & execute useful debugging functions. Other support functions
- 2K RAM, 4K ROM (expandable to 4K RAM or 8K ROM)
- 6 digit 7 segment display
- 36 keys: 16 Hex, 19 Function & 1 user defined
- Tiny 2K Basic interpreter
- Provision for on-board Z80 PIO & Z80 CTC
- Bread-board/wire wrap area

#### The New MPF-1 PLUS

- Interactive 8K Monitor • Two Pass Assembler & Text • Editor • Line Assembler • Disassembler • Direct Data Entry (Hex)
- 4K RAM, 8K ROM (Expandable to 16K)
- 20 digit, 14 segment display
- 49 key 'QWERTY' type keyboard
- Optional Languages — BASIC & FORTH
- RAM backup battery
- Both models include: Z80 CPU • Z80 Bus socket for external Interfacing • Cassette I/O • Speaker • 3 User's Manuals & Optional Student Work Book.

MPF-1 PLUS \$207.00 MPF-1B \$138.00

#### MPF-1 OPTIONS:

IOM-MPF-IP, Input Output and Memory Board (MPF-IP only)	\$132.00
PRT-MPF-I, Printer Board	\$105.00
EPB-MPF-I, Eprom Programming Board (Incl. AC/DC adapt.)	\$159.00
SSB MPF-1 Speech Synthesizer Board	\$159.00
SGB-MPF-I, Sound Generation Board	\$105.00
AC/DC-Mains Adaptor (for IOM, PRT, SSB & SGB)	\$ 11.50

\* Micro-Professor is a trade mark of Multitech Industrial Corporation.

\* Z80 is a trade mark of Zilog Inc.

\* ALL PRICES — PLUS 20% SALES TAX, IF APPLICABLE.



Available from:  
**EMONA ENTERPRISES PTY LTD.**  
 CBC Bank Bldg,  
 661 George St, Sydney NSW, 2000.  
 Tel (02) 212-4815. Tlx AA74500  
 (Dist. in all States)

## AUSTRALIA'S TOP SCANNER WORLD'S FIRST 3 IN 1

- 3 Mode SCANNER
- 3 Mode COMMUNICATION RECEIVER
- 3 Mode VHF-UHF Monitor



**AR-2001 ONLY \$699**

INCL. TAX

#### FEATURES:

- 25-550 MHz continuous
- AM — for Air band monitoring
- NBFM — for communication
- 20 CH memory
- WBFM — for BC & TV monitoring
- Priority Channel
- Clock

#### SPECIFICATIONS:

Frequency Range:	25MHz - 550MHz Continuous	
Search Frequency Increments:	5KHz, 12.5KHz, 25KHz	
Mode:	Narrow band FM	AM
	Wide band FM	
Number of Memory Channels:	20 including Mode informations	
Sensitivity:	Narrow FM 0.3uV	12DB SINAD
	Wide FM 1.0uV	12DB SINAD
	AM 0.5uV	10DB S/N
Threshold Squelch:	NFM 0.2uV	
	WFM 2.5uV	
	AM 0.2uV	
Selectivity:	NFM ±7.5KHz @6DB, ±20KHz @70DB	
	WFM ±50.0KHz @6DB, ±250KHz @60DB	
	AM ±5.0KHz @6DB, ±10KHz @70DB	
Spurious and Image Rejection:	-50DB	
Modulation Acceptance:	NFM ±7.5KHz	
	WFM ±50KHz	AM 100%
IF Frequencies:	1st IF 750MHz	SAW Filter
	2nd IF 45.0275MHz	Crystal Filter
	3rd IF 455KHz (WFM) 5.5 MHz	Ceramic Filter
Reference Oscillator:	(Synthesiser) Crystal Controlled	
Scanning Rate:	Approx. 5 Channels per Second	
Search Scanning Rate:	Approx. 6 Seconds per mega-Hertz	
Scan Delay:	Normal	Approx. 1 second
	With Delay Option	Approx. 2.5 seconds
Search Delay:	Approx. 2.5 seconds	
Priority Sampling Rate:	Approx. 2 seconds	
Audio Output:	1W @10% or less Distortion	
Speaker (Internal):	8 Ohms	
Power Requirements:	12V - 14V DC	
Frequency and Message Readout:	LCD Type	
FCC Certified:	Part 15 Subpart C	
Size:	138mm Wide x 80mm High x 200mm Deep	
Weight:	1.1 kgs	

DEALER ENQUIRIES WELCOME

# EMONA electronics

All Mail to: P.O. Box K21, Haymarket,  
 N.S.W. 2000. Ph: (02) 211-0531  
 649 George St., SYDNEY

## Economy analogue frequency meter

H. Nacinovich of Gulgong NSW says that this circuit is simple, easy to build and get going, and uses very little standby power.

There is no reason why it could not run off a 9 V radio battery but some form of power supply voltage regulation is recommended.

The circuit might be built into a suitable case, complete with a meter, or it could be used as an outboard adaptor (i.e. minus meter movement) which can be plugged into an ordinary multimeter.

Alternatively, although I have not tried this, it could be built into an existing multimeter case. For example, if a spare multimeter is on hand one might be willing to sacrifice, say, the 'Ohms' ranges and convert the associated switch positions to 'Frequency' ranges. The modification should not be beyond the ingenuity of most hobbyists.

Another possibility is to incorporate it into an audio signal generator.

I must confess that the circuit does not involve any new ideas. However, I have not seen any analogue frequency meter projects published recently. So, I thought that this project might be appreciated, if not by the advanced enthusiast, then at least by the newcomer or one with limited cash and limited spare time.

There have been plenty of digital frequency meter circuits published recently. Bearing in mind the performance capability of such circuits and the relatively low cost of digital ICs these days, the popularity of DMFs is not surprising. Even so, I would not consider a DFM either a simple or a cheap project to build.

Despite all the obvious advantages of a DFM there are many situations in which one might get by quite happily with an analogue meter which covers the audio to sub-radio spectrum and has about the same order of

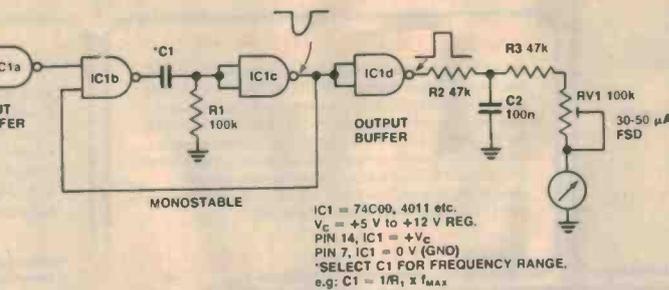


Figure 1. Simple monostable configuration.

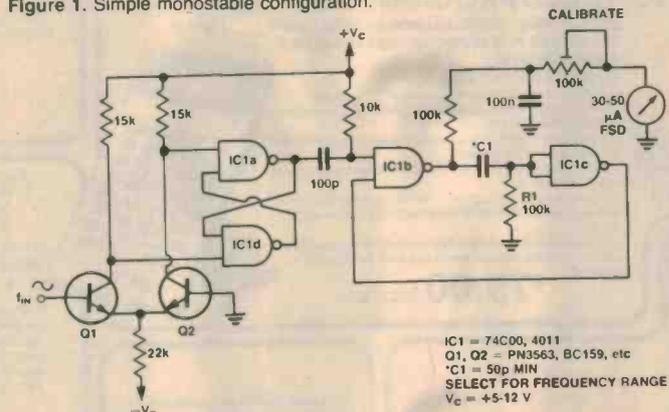


Figure 2. Modified frequency meter.

R1	C1	Theoretical max. frequency of measurement	Recomm. calibration FSD
100k	100n	143 Hz	100 Hz
100k	10n	1.43 kHz	1 kHz
100k	1n	14.3 kHz	10 kHz
100k	100p	143 kHz	100 kHz

accuracy as, say, an ordinary multimeter. Now, if such a device could be built using a single, low cost IC, a few passive components, a simple power supply and, possibly, a meter which is already on the workbench or lying idle in a cupboard somewhere, well...

The circuit described has the best balance of the desired features. I incorporated it into a Wien bridge-type audio oscillator which I had previously built and used the meter to monitor the output frequency.

The obvious advantage of this arrangement is that I need not rely on the dial calibration which is subject to too many sources of error. From tests I have made to date, the linearity and stability which can be obtained with the circuit are surprisingly good over the entire range of my oscillator, 20 Hz to 200 kHz.

The circuit shown in Figure 1 is based on the use of CMOS NAND gates in a simple monostable configuration. It

produces an output current signal which is linearly proportional to the input frequency.

Two gates, IC1b and IC1c of a quad package form the heart of the monostable. IC1a and IC1d are employed as input and output buffers respectively. Their purpose is mainly to square up any rounded corners on the input and output signals.

The output from IC1d is in the form of a series of positive rectangular pulses of constant width (determined by the time constant  $R1C1$ ) and a frequency equal to the input frequency. These pulses are integrated and the resultant signal is applied to a meter movement of suitable sensitivity.

I used an ordinary multimeter movement with 30  $\mu$ A FSD sensitivity but there seems to be no reason why a less sensitive movement (e.g. 1 mA FSD) could not be used provided that the values of R2, R3 and RV1 are adjusted accordingly.

Calibration will depend on the choice of component values, the meter sensitivity and on variations between ICs from different manufacturers. Thus some experimentation with component values may be necessary and the values shown are therefore meant as a guide only.

With any combination of R1 and C1, the upper limit of frequency which can be measured will depend on the product  $R1C1$ . As a rough rule of thumb choose R1 C1 to be equal to  $1/f_{max}$ , where  $f_{max}$  corresponds to the chosen input frequency for full scale deflection.

Then, with an input signal of known frequency adjust VR1 for a suitable meter deflection. It is possible to cover different frequency ranges simply by switching in different values for C1, leaving all other component values as they are. For example, to increase the range by 10, reduce the value of C1 by 10, and vice versa. Some trimming of component values may be necessary.

Calibration will also depend on the supply voltage which should be regulated. I have used a 12 V mains powered regulated supply, but if a 9 V battery is used I would recommend the use of a series regulator with low standby current, such as the  $\mu$ A105.

Figure 2 is a modified version of Figure 1 and it gives a very good performance. It is useful when the input signal needs to be conditioned, such as low level sine waves, to produce a square wave input to the monostable portion of the circuit.

Basically, IC1a and IC1d are wired as a flip-flop which changes its output state with a snap action when the inputs to these gates alternately go low. There are a number of different ways of driving such a flip-flop, but in this case I chose to use a pair of transistors connected as a differential amplifier.

This has the advantage that it can be dc coupled to low frequency, ground referenced signals and it also gives a modest amount of signal amplification. However, this arrangement does need a dual power supply. The input sensitivity is better than 200 mV p-p, depending on the gain of the transistors and the supply voltage. ▶

## STEREO SYNTHESIZER FOR VCR'S AND TUNERS

Synthesize realistic stereo from virtually any monophonic source by simply connecting this unit between the source and your stereo amplifier.

- Quality Phillips MN3001 (not second source dropout).
- Selection of either source via front panel switch.
- Normal or stereo sound selection.
- Provision for 2 different signal sources.
- Complete kit includes all hardware, cables etc., even solder.

K5810 **\$55.00**

## KIT SUPPORT FOR THE MICROBEE

### EPROM PROGRAMMER

Versatile, low cost and easy to build. Plugs straight into the microbee 1/0 port. Suitable for 2716, 2732, 2532, 2732A and 2764 Eproms. Burn your games programmes and eliminate cassette loading time. **KIT FEATURES** Sockets for all other IC's 1 x 2716 supplied - get started straight away. Front Panel and Mains SEC approved transformer 28 pin and 16 pin wire wrap sockets to flush mount personality plugs (2 included) and ZIF socket (included) DB 15 Plug Complete to last nut and bolt.

K9668 **\$55.00**

### RADIOTELETYPE DECODER

Display RTTY encoded messages on your video Monitor. Receive up to date weather information, International News before the Papers, all sorts of coded military info. Simple circuit uses PLL techniques Single PCB Construction. Kit includes DB15 Plug and backshell for connection to microbee. Shielded pretinned PCB.

K9733 **\$19.50**

### TI. SLIM LINE TI. 30-11. TI. LCD PROGRAMMER.

#### ECONOMICAL LCD SLIDE-RULE CALCULATOR FOR STUDENTS.

- Easy to read Liquid Crystal Display (LCD).
- AOS™ Algebraic Operating System allows you to enter mathematical sequences in the same order that they are algebraically stated.
- Constant Memory™ feature holds numbers in a user memory even while the calculator is turned off.


**\$23.00**



#### HEXADECIMAL, OCTAL, DECIMAL, CALCULATOR/ CONVERTER. FOR COMPUTER PROFESSIONALS AND HOBBYISTS.

- FEATURES & FUNCTIONS:**
- Performs arithmetic in any one of the three number bases.
  - Integer, two's complement arithmetic (using the [-] / [key] in OCT (base 8) and HEX (base 16).
  - Signed floating point arithmetic in DEC (base 10) for the key use in day to day decimal computations.
  - Number conversions - converts integer numbers between base 8, base 10 and base 16.
  - Parentheses - 15 sets available at each of 4 processing levels to allow you to dictate the order of interpretation of a mathematical sequence.
  - Constant Memory - Independent memory with summation to memory capability. Retains memory even when the calculator is turned off.

**\$79.00 inc. tax.**

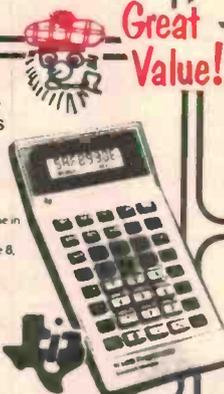

### MICROBEE LIGHT PEN

AT LAST - a light pen for the Bee. This pen works in the low-resolution graphics mode and connects directly to the 1/0 port. Complete kit including DB 15 2m CORD. Fully documented with software example.

PROVIDES DIRECT PERSONAL CONTACT WITH YOUR BEE!

K9649 **\$19.95**

### MULTIPROM INTERFACE FOR THE MICROBEE

- 44K OF PROGRAM STORAGE \* FULLY SOFTWARE SELECTABLE \* SUITS BOTH IC AND PLUS MACHINES
- 8 OUTPUTS FOR CONTROL APPLICATIONS\*

A sensational new kit for the MICROBEE, requires no modification to the computer except for the fitting of a 50 pin expansion socket. This project is easy to build and will allow you to store and software select up to 44K of eprom storage - acts like a mini disk drive system with the speed of RAM. Extra units may be added to further increase storage.

- Full set of IC sockets
- Double sided, plated through board
- Assembled connection lead to Microbee
- Fully documented
- Cassette monitor included (plus sourcefile).

K9673

**\$99.50**

THE MICROBEE KIT OF 1983

### COMPUMUSE

YOUR GAMES WILL NEVER BE THE SAME

A computer music synthesizer that is easy to build and easy to use, connects to any computer with a Centronics-style parallel port and provides music over a five octave range and a wide variety of sound effects.

EXPERIMENTAL KIT-PCB, COMPONENTS & SOFTWARE

K9834

**\$26.50**



### BX 80 DOT MATRIX PRINTER

- Printing method: Serial impact dot matrix.  
 Printing format: Alpha-numeric - 7 x 8 in 8 x 9 dot matrix field. Semi-graphic (character graphic) 7 x 8 dot matrix. Bit image graphic - Vertical 8 dots parallel horizontal 640 dots serial/line.
- Character set: 228 ASCII characters. Normal and italic alpha-numeric fonts, symbols and semi graphics.
- Printing Speed: 80CPS. 640 dots/line per second.  
 Printing direction: Normal - Bidirectional logic seeking.

- Dot graphics density: Superscript and bit image graphics - Unidirectional, left to right. Dot graphics density up to 1280 dots per line.
- Columns/line: Ribbon, cartridge type. Normal size - 80 columns. Double width - 40 columns. Compressed print - 142 columns. Compressed double width - 71 columns.
- Paper feed: The above can be mated in a line. Adjustable sprocket feed and friction feed.
- Paper type: Fanfold Single sheet. Thickness - 0.09mm (0.002") to 0.25mm (0.01"). Paper width - 101.6mm (4") to 254mm (10").

**\$460.00**

This project allow you to decode the signals of shortwave stations, transmitting radio facsimile weather maps, satellite pictures etc and then reproduce them on your dot-matrix printer.

K9733

### KITS

SOUNDBENDER	\$26.39
RADIO MICROPHONE	\$6.20
ELECTRONIC IGNITION	\$31.88
MICROBEE EPROM PROGRAMMER	\$52.96
MUSICOLOUR IV	\$91.39
NEGATIVE ION GENERATOR	\$39.28

### MAGRATHS

THE ONLY CITY SOURCE  
 Now you can make professional quality PC artwork and boards



**E-Z CIRCUIT™**  
 BY BISHOP GRAPHICS INC  
**PRESSURE SENSITIVE DRAFTING AIDS**

Ideal for small volume OEM users, Consultants, Breadboarders, Experimenters, Designers, Hobbyists Bishop quality in small, economical packages.

### SCOPE COMMODORE MODEL PH20 370°C

Now a Production Quality 20W Iron that air cools your fingers. . . \* 240VAC

Designed for continuous production line use

- for students
- serious hobbyists.

A professional quality non-temperature-controlled soldering tool. Earthed tip and barrel for component safety.

\*Iridium temperature subject to variations in line voltage and ambient conditions.



**\$17.19**

**SUPER BARGAINS AT MAGRATHS**

ALL PRICES INCLUDE SALES TAX



SEAL OF SATISFACTION  
**MAGRATHS**  
 WORLD OF ELECTRONICS

### TEXTTOOL ZERO INSERTION FORCE SOCKETS

16 PIN	\$10.83
24 PIN	\$10.06
28 PIN	\$14.49
40 PIN	\$17.83



### TC48/ TC64-IC TEST CLIPS

14 PIN	\$7.00	22 PIN	\$19.65
16 PIN	\$7.34	24 PIN	\$20.33
16 PIN LFI	\$13.80	28 PIN	\$22.44
18 PIN	\$15.43	40 PIN	\$29.85
20 PIN	\$17.68	64 PIN	\$43.52

**MAGRATHS ELECTRONICS** Phone or Mail.  
 55 A'BECKETT STREET, MELBOURNE, 3000  
 Tele (03) 347 1122, Telex AA31001

Prices subject to change without notice.

bankcard  
 welcome here

ALL ITEMS EX-STOCK AT THE TIME OF ADVERTISING

**DISC DRIVES**  
M4853



**MITSUBISHI**

- SLIM-LINE 5.25"
- DOUBLE SIDED
- DOUBLE DENSITY
- 80 TRACKS PER SIDE
- 1.0M BYTES UNFORMATTED

**\$378.55**

**LITHIUM MEMORY SUPPORT BATTERIES**

MEMOGUARD LM & LF Series. Horizontal or Vertical mounting. The ideal power source for memory back up!

LITHIUM MEMORY SUPPORT BATTERIES SERIES LH & LF

**\$5.34 EA.**



**PRINTING PAPER**  
**WORD PROCESSING PAPER**

242mm x 279mm  
250 SHEETS \$7.04  
500 SHEETS \$13.72

**BLUE LINED FAN FOLD**

381mm x 279mm  
250 SHEETS \$8.33  
1000 SHEETS \$30.11

**MAGRATHS PRODUCT OF THE MONTH!**  
**DIGITAL MULTIMETER**



0.1% and 0.25% Basic DCV Accuracy  
Overload Protected on All Ranges  
2,000 and 200 Hour Battery Life  
Current Ranges to 10 Amps  
Hi-Lo Volt Resistance Tests  
Rugged construction  
26 Ranges  
3 1/2 Digits  
Low Cost

**ONLY \$100.91**

**SPEAK & SPELL**  
as featured in **E.T.**



**E.T. PACK INCLUDES**

- One Speak & Spell learning aid
- The new E.T. Fantasy Module
- New photo-filled activity book
- Colorful movie poster
- T-shirt decal with E.T. and Elliot

**HI-FI/ACCESSORIES**

GN33 GOOSENECK 33cm LONG	\$5.52
MH3 MICROPHONE HOLDER	\$2.76
MH2 MICROPHONE HOLDER	\$2.76
PL1 240V 2PIN CORD	\$2.55
THD1/A HEAD DEMAGNETIZER	\$7.08
THD4 ELEC. HEAD DEMAGNETIZER	\$25.42
DM17 MICROPHONE	\$3.73
JS20 HEADSHELLS	\$4.98
RCB-2 CARBON-FIBRE RECORD	\$5.60
BULK TAPE ERASER	\$37.51

**NEC 1 uF 50V**

**SUPER CAP**  
THE NEW RELIABLE POWER SOURCE TO MAINTAIN VOLATILE MEMORY BANKS DURING AC POWER FAILURES

The high capacitance of one farad and low leakage current of this supercapacitor makes it an efficient, reliable and cost-effective storage device with the following advantages:

- It never needs replacing or maintenance.
- Unlike nicads it does not exhibit discharge memory.
- Lack of polarity enables it to be wired either way.
- It can be soldered onto P.C.B.s with other components.
- It can be charged at high and low current rates, i.e. microamps to amps.
- Completely safe. It will not explode under extremes of temperature, nor will it leak.

**\$14.95**

**GOING AWAY FOR HOLIDAYS?**  
THE BOSCH DIGITIMER WILL SWITCH ANY OF YOUR LIGHTS, T.V., RADIO, STEREO ETC ON AND OFF AT PRESET INTERVALS TO DISCOURAGE POTENTIAL BURGLARS.

**Bosch digitimer**  
a fully programmable Digital Computer Clock with 4 independently switched power outlets

- Time.
- Day of week.
- Calculator-type key entry for programme setting.
- 4 independently switched power outlets.

Equipped with a programmable computer which can switch four power outlets independently to control most appliances up to 10 amps. The computer is programmed via a calculator type key entry facility to perform up to 20 daily or weekly switching functions.

**Ideal for both home and industry, the Bosch Digitimer DT201 can be used for:**

- Security Lighting.
- Shop Window Lighting.
- Radio/Hi-Fi.
- Electric Blankets.
- Air Conditioners and Heaters.
- Most Kitchen Appliances.

**\$86.25**

**TI-99/4A COMPUTER**

PERIPHERALS	WAS	NOW
EXPANSION BOX RS-232 CARD	\$299.00	\$200.00
DISC CONTROLLER CARD	\$199.00	\$175.00
EXPANSION DISC DRIVE	\$256.00	\$100.00
32K MEMORY CARD	\$452.00	\$399.00
SPEECH SYNTHESIZER HAND CONTROLLERS	\$299.00	\$199.00
	\$39.00	\$29.95
SOFTWARE		
TIWRITER	\$149.00	\$49.50
MICROSOFT MULTIPLAN	\$199.00	\$108.00
MAILING LIST	\$69.00	\$34.95
EXTENDED BASIC	\$109.00	\$59.95
VIDEO CHESS	\$69.00	\$34.95
LOGO	\$139.00	\$59.95
SPEECH EDITOR	\$44.95	\$29.95
ALPINER	\$49.95	\$29.95
MUNCHMAN	\$39.95	\$34.95
CAR WARS	\$39.95	\$29.95
TI INVADERS	\$39.95	\$29.95
TOMBSTONE CITY	\$39.95	\$29.95
CHISHOLM TRAIL	\$44.95	\$29.95
PARSEC	\$46.95	\$34.95
TI TREK	\$29.95	\$24.95
ADVENTURE (DISC)	\$59.95	\$24.95
MINI-MEMORY	\$109.95	\$49.50

**BMC - BM12A**  
**GREEN SCREEN MONITOR**

- NON GLARE SCREEN
- 15 MHZ BANDWIDTH
- 90 DAY WARRANTY

**HURRY! STOCKS ARE LIMITED!**



**WHILE STOCKS LAST -**  
**\$149.50**  
INCLUDING TAX AND DELIVERY

SEND CHEQUE OR MONEY ORDER DIRECT TO MAGRATHS.



**PLEASE SEND MY BM12A MONITOR IMMEDIATELY.**

MY CHEQUE IS ENCLOSED.

OR CHARGE MY BANKCARD No. .... Signed .....

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Mail or phone orders add \$2.00 up to £14.00 pack post. Special rates for heavy items on request.

# IDEAS FOR EXPERIMENTERS

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.


## Car alarm modification

Anthony Park of Middle Cove has come up with a modification to the car alarm project, ETI-084. It provides an entry delay system, removing the need for an external switch and making the alarm easier to install, more convenient to operate and more difficult for thieves to disarm.

As the original alarm design allows for unlimited exit time, the modification required is simple yet more sophisticated than the usual entry/exit delay systems. And best of all, the extra parts should only cost about \$1.

When the alarm is triggered pin 3 of IC1 goes low (about 0.6 V). This action initiates the entry delay provided by IC4, C8 and R13. C8, normally charged at 12 V, begins to discharge through R13 and after ten seconds or so the voltage at pins 2 and 6 of IC4 reaches 4 V.

This action sets pin 3 high,

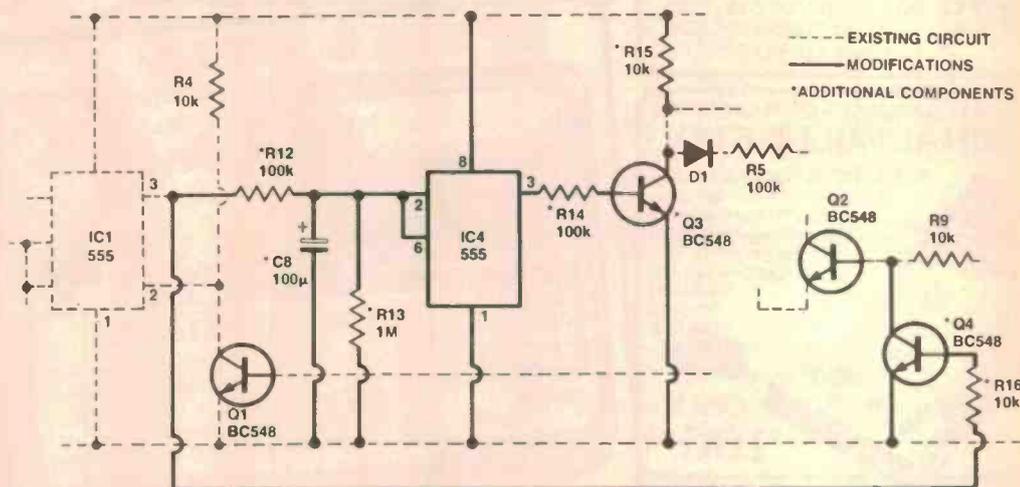

thus turning on Q3 and allowing the relay to pulse via Q2 and also trigger off the 45 second reset delay as previously designed. After this delay time, pin 3 of IC2 goes high, switching on Q1 which resets IC1, followed by IC4 and IC2, completing the sequence.

The only change to circuit performance is that there is a delay time before the circuit is fully

reset due to the time required to charge C8. This should not pose any problems except when the alarm is initially turned on, taking about 17 seconds to charge C8 fully.

The purpose of Q4 is to disable Q2 so that the relay is not pulsed while C8 is charging, otherwise the horn would be beeping for 17 seconds when the alarm is first turned on.


This modification is very simple to install as only one track, from pin 3 of IC1, on the pc board has to be cut. All the other connections can be made directly by soldering wires on to the existing pc board. Veroboard can be used to house the extra components.

The alarm should have a ten second delay before the horn or siren begins to sound.
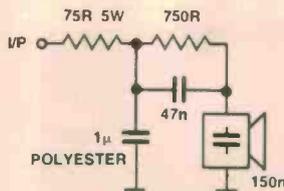
## Motorola speaker filter

Phillip Dennis of Chippendale NSW has designed a circuit to smooth the lower cut-off point of Motorola Piezo Ceramic speakers, in particular, the 3 1/2" Super Horn (models KSN 1001A, 1005A, 1032A and 1003A).

Although they are rugged, very efficient and reasonably cheap, they suffer from a fairly high, lower cut-off point at about 4 kHz with a very savage cut-off slope of approximately 20 dB/octave. The proposed circuit smooths out the fast cut-off at the expense of sensitivity. However, the loss of sensitivity is not really a problem since the drivers are very efficient.



The circuit is a two stage filter made from resistors and capacitors only. No inductors are used which makes the circuit attractive, and the input impedance is still quite high, preserving the 'no load' effect of the driver.

The idea was to reduce the cut-off slope to about 6 dB/octave for as long as possible without undue loss of sensit-

ivity. Therefore the 3 dB of the filter was chosen at about 2 kHz. This determines where the roll-off resumes its rapid plunge. The second half of the filter has a step response, where roll-off starts at about 1 kHz and levels out again around 4.5 kHz.

The capacitive load presented by the tweeter (150n) is quite handy, and I use it as part of the filter. It also allows the use of filter sections that are basically non interactive, which simplifies design and implementation.

The circuit was originally used with Magnavox 8-30 bass drivers as a stop gap measure.


The filter significantly cuts

back the harshness of the tweeter since it broadens the response, although I did find it necessary to use a little treble boost to add some brilliance. I had hoped that the staggered roll-off points would smooth the response without too much attenuation, since the signal to the tweeter is basically reduced by the same factor as the roll-off point.

By including a resistor of 20-30 ohms in series with the 1µ capacitor, the first section of the filter can be altered to give a step response similar to the second section.

Well it's worth trying and the only really expensive part is the tweeter.

# IDEA OF THE MONTH

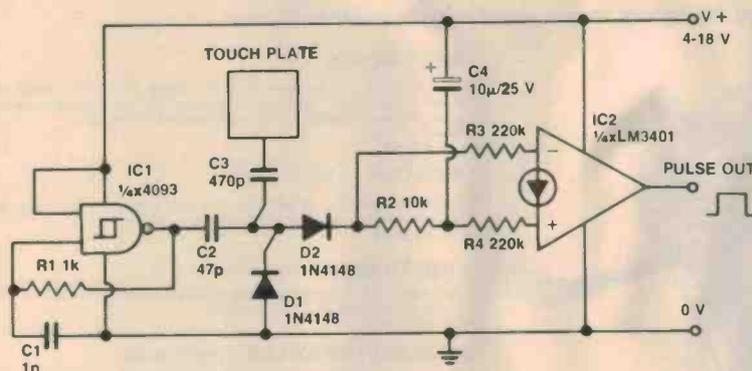

## Wide range touch switch ☆☆☆

Steven Sims, St Peters NSW.

Most capacitive touch switch circuits use a comparator, where the reference input must be trimmed, and retrimmed if the supply voltage is changed.

I wanted to avoid this as I wished to use the switches in a logic designer, with the supply variable over the CMOS range.

The resulting circuit needs no adjustment and operates happily over the range 4-18 V (the lower limit of the op amp to the upper limit of the Schmitt trigger).

The output of the Schmitt trigger astable IC1, R1 and C1, is fed to the capacitive divider C2 C3, rectified and then sent to

both inputs of the Norton op amp comparator. The capacitive divider principle is well known and previously published. However, the way it is employed in this circuit is my own idea.

R2 biases the non-inverting input just below the inverting input, thus the output is normally low. When the plate is touched, the resulting drop in voltage is sent to both inputs, but in the case of the non-inverting input it is delayed by R2 C4. Thus the inverting input momentarily goes below the non-inverting input, turning the op amp on for that time and

producing a short positive pulse at the output.

The op amp swings over virtually the entire supply range, resulting in a reasonably clean pulse with no switch bounce. This pulse may be used as a trigger for a monostable; or sent to a Schmitt trigger for squaring up; or sent to an op amp or JK flip-flop toggling circuit; or any other controlling function.

A LM3900 can be used instead of the LM3401. As both the op amp and the Schmitt trigger come in quad packages, the circuit is ideal for banks of four switches.

## Dewatering fluid test device

This test setup was constructed by L. W. Brown of Burwood Victoria to compare assorted cans of electrical (dewatering) spray.

The device is a 25 mm square of single-sided epoxy, glass fibre, copper laminate with a single, deep knife scratch across the middle.

A multimeter capable of measuring above one megohm was used to detect the presence of moisture.

A can of instant freeze (canned cold) is sprayed across the scratch to clean the board and then condense moisture from the atmosphere. Once the ice on the board has melted it will provide a leakage path of around one megohm.

Finally the de-watering fluid under test is used to remove this moisture; the results are alarming!

## 'IDEA OF THE MONTH' CONTEST


### COUPON

Cut and send to: Scope/ETI 'Idea of the Month' Contest, ETI Magazine, P.O. Box 227, Waterloo NSW 2017.

"I agree to the above terms and grant *Electronics Today International* all rights to publish my idea in ETI Magazine or other publications produced by it. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright."

\* Breach of copyright is now a criminal offence.

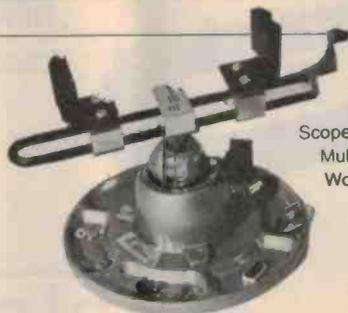Title of Idea .....  
 Signature .....  
 Name .....  
 Date .....  
 Address .....  
 Postcode .....



Scope Panavise Multi-Purpose Work Centre.

Scope Laboratories, which manufactures and distributes soldering irons and accessory tools, is sponsoring this contest with a prize given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column — one of the most consistently popular features in ETI Magazine. Each month, we will be giving away a Scope Panavise Multi-Purpose Work Centre, Model 376/300/312, comprising a self-centering head (376), standard base (300) and tray base mount (312), all worth about \$90! Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, each winner will be paid \$10 for the item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

### RULES

This contest is open to all persons normally resident in Australia, with the exception of members of the staff of Scope Laboratories, The Federal Publishing Company Pty Limited, ESN, The Litho Centre and/or associated companies.

Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked prior to and including the date of the last day of the month.

The winning entry will be judged by the Editor of ETI Magazine, whose decision will be final. No correspondence can be entered into regarding the decision.

The winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning idea, will be published in the next possible issue of ETI Magazine.

Contestants must enter their names and addresses where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words, you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in states where local laws prohibit entries. Entrants must sign the declaration on the coupon that they have read the above rules and agree to abide by their conditions.


PRIZE WORTH \$90!

# NO 1 FOR KITS

JAYCAR/  
ELECTRONIC  
AGENCIES

FROM \$39.95

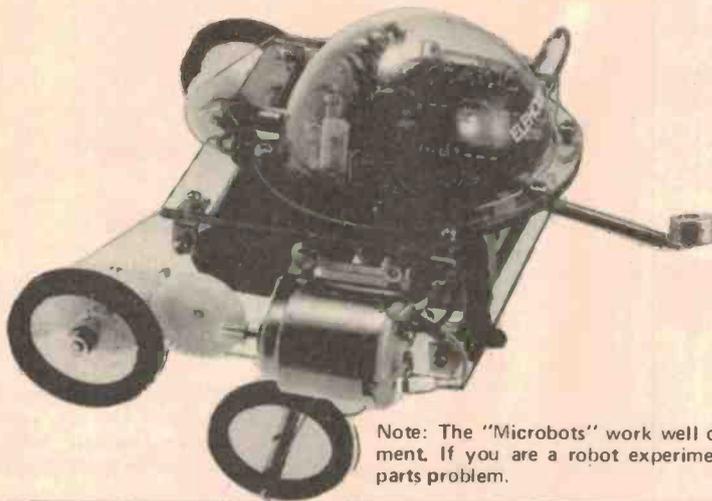Jaycar Electronics is proud to announce a range of very low cost "Turtle" like robot kits. Don't let the low prices fool you — they are not toys. The units feature solderless connections with explicit illustrations to ease assembly. Only simple tools (i.e. screwdriver, pliers etc.) are needed to assemble.



## PIPER MOUSE

This "microbot" is powered by 2 DC motors that drive wheels. When a special ultrasonic whistle is blown, the unit goes left, right, straight ahead according to your command. Complete, including perspex dome cover!  
Be a Pled Piper!  
Cat. KJ-6680

ONLY \$39.95

## AVOIDER (not illustrated)

Similar to the Piper Mouse, but this unit travels on its own. It avoids objects because it has an infra-red beam system. Very clever!  
Cat. KJ-6682

\$44.95

## LINE TRACER (not illustrated)

This robot will automatically follow a black line drawn onto a sheet of paper. It uses an infra-red feed back system.  
Cat. KJ-6684

\$39.95

## MEMOCON CRAWLER (not illustrated)

This robot is controlled by a keyboard which is supplied. The operation of the unit is programmed by the keyboard and stored in RAM. All movements can be controlled as well by lights (beams) and sound (buzzer). A very sophisticated unit.  
Cat. KJ-6686

\$79.95

Note: The "Microbots" work well on their own but can also be used as a platform for robotic development. If you are a robot experimenter you will find them useful as they help resolve the mechanical parts problem.


## 30W + 30W

### STEREO PREAMPLIFIER STEREO AMPLIFIER

- Fully built and tested
  - Separate bass, treble, balance and volume controls
  - Less than 0.1% distortion
  - Mic, phono and aux. inputs (line)
  - Power supply components on board
- Back at last! No hassle amplifiers. Just connect a transformer, speakers a signal and you're away!

STAGGERING VALUE

only \$34.95

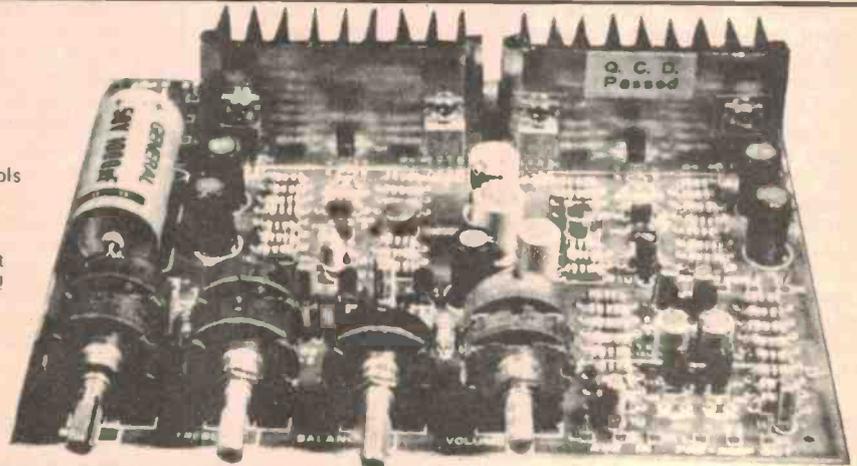

## minitune

Ref:  
EA  
June  
1983

Following the spectacular success of the DP2010 Digital Multimeter kit, we now have an ENGINE ANALYSER KIT! But the spectacular thing is the price! It is ACTUALLY CHEAPER than the DPM-05 Display and Case! The Minitune will measure voltage, resistance (down to a very low range), RPM and Dwell Angle.  
Cat. KJ-7012

TEST LEADS TO SUIT ONLY \$2.95

\$42.95

Specification			
Function	F.S.D.	Resolution	Accuracy
Voltage (d.c.)	20V	10mV	0.5% - 1 digit
Resistance	2000	100Ω	0.5% - 1 digit
	20kΩ	100	0.5% - 1 digit
R.P.M.	20,000	100 μm	1% - 3 digits
Dwell	90	0.1	2% - 3 digits

\$42.95



## NEW ETI JOYSTICK CONTROLLER

Ref: ETI Dec '83  
True proportional control with this kit. Includes recommended joystick unit.

ONLY \$24.95



## BBD EFFECTS BOX

Fantastic low cost instrument using the versatile MN3001 Bucket-Brigade Delay Line to achieve brilliant sonic effects. Now you can emulate the commercial rock groups with Phasing, Flanging, Reverb and Echo. The Jaycar kit includes all components INCLUDING IC sockets and the TU-04 box. (Not cut down but this is easily done). Jaycar has a specially built cabinet for this kit with all holes pre-punched etc., at only \$10 extra but only if you buy the original kit from us. Available as a separate item for \$29.50. WHEN THE KIT IS PURCHASED WITH THE DE-LUXE CASE THE TU-04 CASE WILL NOT BE SUPPLIED.

Special cabinet to suit Cat. HB-6445 \$10  
Complete Kit Cat. KE-1522 ONLY \$79



## 3 1/2 DIGITAL PANEL METER




(not illustrated)

Low cost unit. Completely self-contained. No longer an expensive proposition! This easy-to-build kit (takes about 1 hour) is self-contained, compact and even comes with a front panel filter/bezel. It can be battery 6V or DC powered.

- 200mV. Full scale (+/- 199.9mV)
- Input impedance 10 to the twelfth ohms
- Required DC 5-6V @ 150mA
- Guaranteed to reset to zero at zero input voltage
- Automatic reverse polarity indication
- Assembly instructions include notes on using your DPM for: Amp-meter, AC-Voltmeter, Ammeter, Thermometer, Frequency Counter, Capacitance Meter (circuits supplied)

STAGGERING VALUE  
Cat. KJ-6670

\$29.95

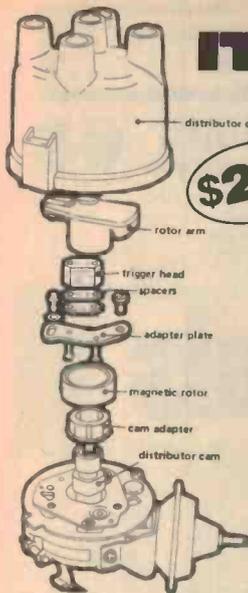

# IT HAD TO HAPPEN

**\$29<sup>95</sup>**

New PCB for TAI Kit includes Hall Effect interface. Cat. HP-8786 ONLY \$3.95

A professionally-engineered electronic ("breakerless") contact breaker system. Yes, only Jaycar has a complete Hall-effect triggerhead assembly designed to adapt to an extensive number of cars. Each kit contains the following:

- HALL EFFECT TRIGGER HEAD
- MAGNETIC ROTORS FOR BOTH 4 & 6 CYLINDER CARS
- OVER 6 CAM LOBE ADAPTORS
- OVER A DOZEN DIFFERENT ADAPTOR PLATES FOR YOUR PARTICULAR DISTRIBUTOR
- OTHER HARDWARE (i.e. SCREWS etc.)
- YOU CAN REMOVE THIS SYSTEM AND RE-EQUIP YOUR CAR WITH THE ORIGINAL BREAKER POINTS WHEN YOU SELL THE CAR!
- AS EASY TO INSTALL AS A SET OF POINTS!
- INSTRUCTIONS (SIMPLE-TO-FOLLOW) INCLUDED!

This set is designed to fit most European and Japanese cars. In fact it will also fit many Australian cars fitted with Lucas, Bosch, Motorcraft, AC Delco or Autolite electrics. If you wish to check first, please send SAE for car/distributor list.

Because we have no way of knowing, you get the fitting set for ALL of the distributors available. Basically you end up with a jar full of parts that you don't need to use! (Perhaps for your next car?)

Quite frankly, we are amazed that we can supply such a comprehensive kit for this price. To produce a kit that will adapt to the dozens of different distributors around is amazing!

Remember, once you have installed a breakerless system it will never wear out and that part of your system will remain in tune FOR EVER.

We expect this kit to sell well. To ensure that you receive one, check with us early!  
Cat. KJ6655

With this kit and the interface electronics you can forget about contact breaker point problems!  
Cat. KJ-6655 \$29.95

**PLEASE NOTE**  
This system must be used in conjunction with an electronic ignition. The Hall Effect device will not switch enough current to replace the contact breaker points on their own!

Jaycar will not be knowingly undersold FOR GOODS OF THE SAME QUALITY. If you find that a competitor is cheaper, get all the facts and tell us! If you are right we will match OR LOWER his price! Please understand that we cannot match the price of goods that are NOT the same quality as ours.

## 500MHz DFM

Ref: EA Dec '81 - Feb '82  
Jaycar has by far the best kit version of this project in Australia. We now supply 2 x GOLD plated BNC input connectors at no extra cost!  
KA-1390 (500MHz) \$129  
KA-1392 (500MHz option) \$20



## VIDEO ENHANCER

Ref: EA Oct 1983  
Get improved performance from your VCR.  
Cat. KE-7016




## Breath Tester

In all states and territories in Australia it is an offence to drive a vehicle with an alcohol/blood concentration above a certain limit. In most states it's 0.05 others 0.08. Either way it's only a relatively small number of alcoholic drinks. Because it's only a small number of drinks, many people (quite wrongly) believe that they remain below the statutory limit.

The KA1522 Breath Tester can help here. A unit with the same circuit diagram was featured in May "Electronics Australia". It CANNOT give you an actual blood/alcohol content reading, however it can go close. And it can give you a relative reading between inebriated friends!!! Great at parties!!! Grab the whole kit now for only \$29.95. You never know, it may save your licence or your life!

ONLY **\$29<sup>95</sup>**

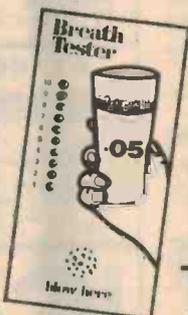

**\$35**

## Video Amplifier/Buffer

Ref: EA Aug 1983

The answer to a maiden prayer!  
This device can be made to fit inside a TV set or in a separate box (if necessary). It basically enables you to connect straight into the video drive of your TV, turning it into a colour monitor. This means that the video signal from your computer, VCR, TV game etc. does not need to be converted to RF and go through the TV IF stage. You will be amazed by the clearer, sharper signal that has less interference! Notes on how to fit to various TV sets are included.  
Cat. KA 1527 \$14.95



Jiffy Box to suit  
HB-6003 \$2.20

## INFRA RED DIMMER KIT

**\$25<sup>95</sup>**

Ref: EA January 1984  
Now you can dim or turn off the lights from the comfort of your armchair!  
Short form kit contains all parts for I.R. kit. Note this must be used with a Jaycar KA-1509 Touch Sensitive Dimmer (\$19.95)  
Cat. KA-1530 \$25.95




## VK POWERMATE - NEW MODEL

Ref: EA Dec '82  
Get up to 13.8V @ 10 amps to run those mobile rigs at home!  
The Jaycar kit is complete.

**\$89.95 comp**

**\$89<sup>95</sup>**

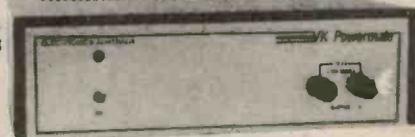

## 50V/5A laboratory power supply

Ref: EA May/June 1983  
Cat. KE 1520

**\$149.00**

## VIDEO SENSATION AT LAST A Video Enhancer/ Distribution Amplifier designed EXCLUSIVELY for AUSTRALIA



NOT A KIT  
BUILT, TESTED  
AND GUARANTEED

**\$59<sup>95</sup>**

Jaycar has had designed a high quality, high performance Video Enhancer which is specifically for the Australian 625 line 50 frame PAL-D system.  
As far as we know it is the ONLY Australian designed, Australian built unit available!!  
But, guess what? The Jaycar AV6501 Enhancer is CHEAPER than its inferior imported Asian counterparts!!  
This unit is professionally designed and University tested! It works and it works well.


## ETI 644

### DIRECT CONNECT MODEM

Ref: ETI  
October 1982

SHORTFORM KIT Cat. KE-4600 ONLY \$169  
COMPLETE KIT Cat. KE-4601 ONLY \$199  
LESS SPECIAL DISCOUNT  
JANUARY ONLY 10%

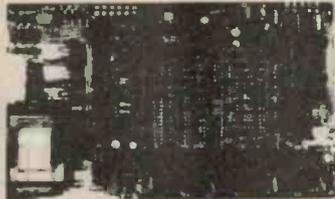"NEW UPGRADED MODEL FEATURING THE LATEST IMPROVEMENTS AND MODIFICATIONS"



## Jaycar Incorporating ELECTRONIC AGENCIES

SYDNEY SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
CARLINGFORD  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444  
CONCORD  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077  
HURSTVILLE 121 FOREST ROAD PHONE: (02) 570 7000

### NUMBER 1 FOR KITS

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)

\*Free INSURANCE for Road & Registered Post over \$200\*  
All heavy or bulky items (over 20kg.) sent Comart Road Freight \$12.00 anywhere in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE  
Mon - Fri 9am - 5.30pm; Sat - 9am - 12pm; Thurs night 8.30pm

SHOP HOURS SYDNEY  
Mon - Fri 8.30am - 5.30pm; Sat - 8.30am - 12pm; Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order By

BANKCARD  
Via Your Phone

**BRAND NEW PLESSEY ETC.**

**DB25 FEMALE SOCKETS**

**EACH \$2**

**HURRY! HURRY!**

**THIS MONTH ONLY! STOCKS ARE LIMITED.**

**CENTRONICS \$5 PRINTER PLUGS**

Extremely small, ribbon-contact connectors suit computers and std. CENTRONICS printer input. Comprises 36 pin plug with gold-plated contacts and metal cover, polarised.

**BRAND NEW! THIS MONTH ONLY. LIMITED QTY!**

**NEW PLESSEY EDGE CONNECTOR**

WITH 80xGOLD-PLATED CONTACTS AT 0.156" PITCH, YOU CAN FULFILL ALL YOUR EDGE CONNECTOR NEEDS - YOU CUT THEM TO LENGTH!

**BRAND NEW! THIS MONTH ONLY! 50c EACH**

**\* PACK/POST \$2 PLUS 5% OF ORDER VALUE.**

**FLUORO BALLASTS**

NEW, 20 WATT OR 6/8 WATT STANDARD FLUORO LIGHTING BALLASTS EX MANUFACTURER. (Normally \$4.90) SORRY, NO MAIL ORDERS ACCEPTABLE!

# Checkout our Specials

WE WANT TO BUY USED COMPUTERS AND PERIPHERALS IN GOOD WORKING ORDER ALSO ELECTRONIC TEST EQUIPMENT, CRO's, AND CB OR HAM RADIO TRANSCEIVERS, ETC.

## WANTED

WE WANT TO BUY EXCESS STOCKS AND DISCONTINUED INVENTORIES OF ALL TYPES OF NEW, MODERN ELECTRONIC PARTS. FOR QUICK CASH SETTLEMENT! NO QUANTITY TOO LARGE OR SMALL - ALL OFFERS CONSIDERED! RING NOW.

**FACTORY REJECT SPEAKER BOXES**

8" 2&3 Way WITH SPEAKERS

**PRICE CUT!**

DO-IT-YOURSELF AND SAVE.

**\$39**

WERE \$69

PERSONAL SHOPPERS ONLY

## Power Transformers 1/2 PRICE

**240V Inputs**

AUST. MADE, AT HALF NORMAL PRICE

TYPE	INPUT	OUTPUT/S
A	0-120, 0-120	0-24V, 4A
		0-10V, 1A
		0-20V, 1A
B	0-120, 0-110-130	0-25V, 5A
		0-20V, 1A
		0-110V, 200mA
C	0-110, 0-110-130	0-24V, 1A
		0-24-28-30V 1Amp
D	0-110, 0-110-130	0-22-24V 2A
		0-27V, 1A
		0-12V, 1A
E	0-240	0-18V, 400mA
	17.5	0-17.5-60-180-300V, 100mA
F	0-240	0-18V, 2A
		0-8.5V, 3A
G	0-110-240	0-33V, 1.25A
H	0-240	0-12.6V, 1A
I	0-240	0-12.6V, 500mA
J	0-240	20-0-20V 2 Amps
K	0-240	0-24V 1.25 Amps
L	0-240	0-24V 4.2 Amps

**EX-COMPUTER TESTED FANS**

**25% DISCOUNT**

110V 220V

5" NOW ONLY \$6 OR \$7.50

**EX-COMPUTER capacitors.**

1,000's of mids TESTED and G'TEED

**IC's 'SWEEPINGS OFF THE FACTORY FLOOR'**

Approx 100 FOR \$10.00 \$90

## LARGEST RANGE AVAILABLE

30,000uf	5v...\$ 3.00	84,000uf	30v...\$11.00
100,000uf	5v...\$ 5.00	60,000uf	30v...\$12.00
150,000uf	5v...\$ 6.00	100,000uf	30v...\$14.00
12,000uf	10v...\$ 2.00	15,000uf	35v...\$ 6.00
25,000uf	10v...\$ 3.00	25,000uf	35v...\$ 8.00
29,000uf	10v...\$ 3.50	30,000uf	35v...\$ 9.00
42,000uf	10v...\$ 4.00	7,200uf	40v...\$ 4.00
62,000uf	10v...\$ 4.75	9,400uf	40v...\$ 4.50
76,000uf	10v...\$ 5.50	10,000uf	40v...\$ 5.00
90,000uf	10v...\$ 6.00	12,000uf	40v...\$ 6.00
100,000uf	10v...\$ 6.50	12,900uf	40v...\$ 6.50
150,000uf	10v...\$ 7.75	20,000uf	40v...\$ 7.50
160,000uf	10v...\$ 7.00	21,000uf	40v...\$ 8.00
184,000uf	10v...\$ 7.50	21,500uf	40v...\$ 8.00
200,000uf	10v...\$ 8.00	31,000uf	40v...\$ 9.00
17,000uf	15v...\$ 3.50	32,000uf	40v...\$ 9.50
21,000uf	15v...\$ 3.75	33,000uf	40v...\$10.00
30,000uf	15v...\$ 4.00	48,000uf	40v...\$12.00
31,000uf	15v...\$ 4.25	20,000uf	45v...\$ 9.00
34,000uf	15v...\$ 4.50	3,500uf	50v...\$ 3.00
47,000uf	15v...\$ 4.75	5,000uf	50v...\$ 3.50
50,000uf	15v...\$ 5.00	5,000uf	50v...\$ 4.00
51,000uf	15v...\$ 5.00	6,000uf	50v...\$ 4.50
60,000uf	15v...\$ 5.50	7,000uf	50v...\$ 5.00
63,000uf	15v...\$ 5.50	8,000uf	50v...\$ 5.50
73,000uf	15v...\$ 6.00	12,000uf	50v...\$ 6.00
80,000uf	15v...\$ 6.50	12,000uf	50v...\$ 8.00
83,000uf	15v...\$ 7.00	15,000uf	50v...\$ 9.00
140,000uf	15v...\$ 8.00	22,000uf	50v...\$10.00
16,000uf	16v...\$ 4.00	23,000uf	50v...\$11.00
68,000uf	16v...\$ 8.00	34,800uf	50v...\$14.00
10,000uf	20v...\$ 3.50	20,000uf	55v...\$10.00
25,000uf	20v...\$ 6.00	7,800uf	60v...\$ 6.00
39,000uf	20v...\$ 7.50	20,000uf	60v...\$11.00
90,000uf	20v...\$10.00	30,000uf	60v...\$12.00
7,700uf	25v...\$ 3.50	25,000uf	62v...\$12.00
10,000uf	25v...\$ 4.00	4,500uf	64v...\$ 5.00
11,000uf	25v...\$ 4.50	9,000uf	75v...\$ 8.00
12,000uf	25v...\$ 4.50	10,000uf	75v...\$ 9.00
13,000uf	25v...\$ 5.00	12,800uf	75v...\$10.00
14,000uf	25v...\$ 5.50	16,800uf	75v...\$12.00
15,000uf	25v...\$ 6.00	20,000uf	75v...\$14.00
19,000uf	25v...\$ 6.50	24,000uf	75v...\$15.00
25,000uf	25v...\$ 7.00	2,800uf	100v...\$ 3.50
32,000uf	25v...\$ 7.50	8,500uf	100v...\$ 9.00
44,000uf	25v...\$ 8.00	14,500uf	100v...\$13.00
47,000uf	25v...\$ 8.50	20,000uf	100v...\$15.00
50,000uf	25v...\$ 9.00	3,000uf	150v...\$ 4.00
55,000uf	25v...\$10.00	3,000uf	200v...\$ 6.00
12,500uf	30v...\$ 5.00	3,300uf	200v...\$ 6.50
24,000uf	30v...\$ 7.00	4,800uf	200v...\$10.00
30,000uf	30v...\$ 8.00	5,400uf	200v...\$11.00
37,000uf	30v...\$ 9.00	5,500uf	200v...\$11.50
40,000uf	30v...\$10.50	2,900uf	250v...\$ 8.50

## GREAT VALUE-FOR-MONEY

## START YOUR SAVINGS BONANZA NOW!!!

**NEW**

20MHz Response.

FREIGHT \$12

## ORANGE SCREEN COMPUTER MONITORS

ORANGE SCREENS GIVE A CLEAR, HONEST IMAGE! Computer data and graphic displays never looked better, brighter, sharper.

ORANGE SCREENS AREN'T A SIGHT FOR SORE EYE'S! Positive research indicates that orange causes least eye fatigue.

**High Resolution \$199**

1000 lines at centre resolution.

Display characters: 1920 (80x24) Incl S/Tax

**MONEY-BACK OFFER IF NOT FULLY SATISFIED**

LIMITED STOCK AT THESE PRICES

BRING YOUR OWN COMPUTER FOR A FREE DEMONSTRATION. BANKCARD ORDERS OK.

## APPLE® 100% COMPATIBLE PRODUCTS



**SPEECH SYNTHESIZER BOARD**...UNLIMITED VOCABULARY COMPLETE WITH SPEAKER AND DISK...\$75

**PRINTER BOARD**...FOR PARALLEL PRINTERS...\$95

**WILD COPY CARD**...ULTIMATE DISK BACK-UP...\$99

**PROTOTYPING BOARD**...DESIGNERS HELP...\$25

**JOYSTICKS**...SELF-CENTERING, ADJUSTABLE...\$40

New 80 Column card, Z80 CPU card, 16K RAM card, PAL Colour card, etc now available.

## \$365 SLIM-LINE DISK DRIVE



WITH READ/WRITE DISK PROTECT SW! Price does not include disk drive card.

**DISK DRIVE CONTROLLER CARD** plugs into an expansion slot and will run up to 2 disk drives.

Limited quantity avail at \$79

Bring your APPLE for a free in-store demonstration. Bankcard OK.

## NEW Products

**1 UNIVERSAL FLOPPY DISK CONTROLLER**

Suits Super 80, System 80, TRS-80, Microbee or any Z80 based computer. (board fitted with std S100 connector)

- Can operate up to 4 x 8" or 5 1/4" drives.
- Includes DMA.
- CP/M routines for most popular Z80 systems.
- Uses M02793 Controller



**2 S100 VIDEO BOARD**

- 80 x 25 screen format
- Graphics resolution: 225 x 560 dot addressable
- Graphics software available

Please send SAE for further information on any products.

FROM QT COMPUTER SYSTEMS S100 Specialists!

**3 FDC-1 SINGLE BOARD COMPUTER**

- Z80A 4MHz or
- Z80B 8MHz option
- 2 Serial ports avail.
- 2 Parallel ports avail.
- NEC765 Floppy Disk controller
- Up to 8K RAM or ROM

Just add memory and you have a complete system - easy upgrade to multi user operation.

## SPECIAL OFFER! 256K DYNAMIC RAM WAS \$995 NOW \$695

**NOW SAVE A MASSIVE \$300**

- 16K to 256K bytes; uses 4116 or 4516 or 4164 memory devices.
- Guaranteed to operate at 4MHz with no wait states (6MHz: 1 wait).
- Adjustable timing allows operation with Z80, 8080, 8085 micros.
- Can be divided into max. 16 banks, each variable in 4K add-ons.
- Each 4K segment can be individually enabled or disabled easily.
- Each bank can be located on any 4K boundary.

NEW, LOWER PRICE INCLUDES M-DRIVE OR CACHE Q SOFTWARE SUPPLIED FOR SYSTEM IMPROVEMENT



PRE-PAK electronics p/l

1a WEST ST, LEWISHAM, NSW

569-9797 24 HR PHONE ORDER SERVICE

Phone or mail order BANKCARD accepted

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

## GO ANYWHERE 12-240V POWER

**MASSIVE  
300 WATTS**



These great inverter kits enable you to power 240V appliances from a 12V DC power source. Tremendous for camping, fishing etc. Install into your Car, Boat or Caravan.

A fully regulated and overload protected design, featuring XTAL locked frequency. Use to power hi-fi, TV sets, even electric drills for short time periods.  
**MANY OF THESE KITS ARE NOW IN USE FOR EMERGENCY LIGHTING PURPOSES.**  
ALTRONICS' KIT features → Gold plated edge connector and PCB huss → Low age rate XTAL → Sockets for all IC's → High Efficiency Transformer.

K6750..... (EA JUNE '82) ... **\$199.50**

(\$10 DELIVERY AUSTRALIA WIDE)

### 40 WATT MODELS


Suits small appliances, i.e. Turntables, Tape Decks, Shavers etc. Variable frequency adjustment enables speed control of turntables. Works as a trickle charger when mains power is available.

EASY CONSTRUCTION → VALUE PLUS

K6700..... **\$55.00**


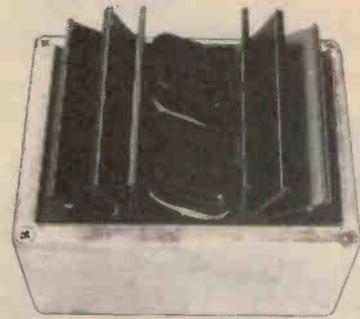
### TRANSISTOR ASSISTED IGNITION WITH DWELL EXTENSION



The Altronics Kit includes all components for the modifications, detailed by Electronics Australia Feb. 1983.

Yes, it's bad enough paying \$2.00 a gallon for petrol without wasting a fortune on an out of tune engine. Fit this transistor assisted ignition kit in minutes and start saving money from the very next petrol stop. Easy to build!

K4010..... **\$35.00**

## ★ KIT SUPPORT FOR THE MICROBEE ★

### MULTIPROM INTERFACE

44K OF PROGRAM STORAGE



A sensational new kit for the MICROBEE, requires no modification to the computer except for the fitting of a 50 pin expansion socket. This project is easy to build and will allow you to store and software select up to 44k of eeprom storage — acts like a mini disk drive system with the speed of RAM. Extra units may be added to further increase storage.

The Altronics Kit comes complete in every way

- Full set of IC sockets.
- Double sided, plated through board.
- Assembled connection lead to Microbee.
- Fully documented.
- Cassette monitor included (plus sourcefile).

THE MICROBEE KIT OF 1983


K9673..... **\$99.50**

### PARALLEL INTERFACE

BUILD YOUR OWN INTERFACE AND SAVE \$\$\$

A simple kit to build — takes about 20 minutes, save on the cost of a built interface and save the cost of a serial printer.

K9671..... **\$29.95**

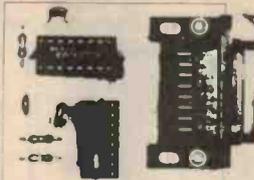

INCLUDES CENTRONICS PLUG AND CABLE

PRICE BREAK THROUGH



### 50 PIN EXPANSION SOCKETS

Right angle type to suit Microbee, floppy disk controllers etc.  
Mounts on PCB and mates with IDC sockets.

D1196... **\$8.50** EA... 10 + ... **\$7.50**

### PROPORTIONAL JOYSTICK



K9674

**\$32.50**

(ETI DEC '83)

### AT LAST AN ANALOGUE JOYSTICK

Plot X-Y co-ordinates on the screen, sign your name. A great graphics aid. Complete kit including case, software example.

### EPROM PROGRAMMER

(ETI JAN '83)



K9668

**\$55.00**


Versatile, low cost and easy to build. Plugs straight into the microbee I/O port. Suitable for 2716, 2732, 2532, 2732A and 2764 Eproms. Burn your games programmes and eliminate cassette loading time.

**KIT FEATURES** → Sockets for all other IC's → 1 → 2716 supplied → get started straight away → Front Panel and Mains SEC approved transformer → 28 pin and 16 pin wire wrap sockets to flush mount personality plugs (2 included) and ZIP socket included → DB15 Plug → Complete to last nut and bolt

(See Review ETI AUGUST 1983)

### RADIOTELETYPE DECODER

(ETI APRIL '83)

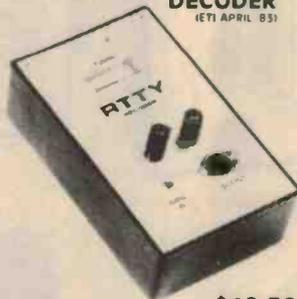

K9733

**\$19.50**

Display RTTY encoded messages on your video Monitor. Receive up to date weather information International News before the papers. All sorts of coded military info. Simple circuit uses PLL techniques. Single PCB Construction. Kit includes DB15 Plug and backshell for connection to microbee. Shielded pretinned PCB.

### MICROBEE LIGHT PEN

(ETI AUGUST '83)



PROVIDES DIRECT PERSONAL CONTACT WITH YOUR BEE!


K9649

**\$19.95**

AT LAST! A light pen for the Bee. This pen works in the low resolution graphics mode and connects directly to the I/O port. → Complete kit including DB15 2m Cable → Fully documented with software example.

### FAX-DECODER

(ETI SEPT '83)

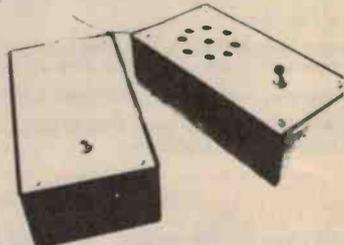

K9733

**\$24.50**

This project allows you to decode the signals of shortwave stations transmitting radio facsimile weather maps, satellite pictures etc. and then reproduce them on your dot matrix printer. → Complete kit of parts includes DB15 Ribbon Cable. → SOFTWARE LISTING.

### BOGGLE GOGGLES

**\$9.60**



Short form

### PH METER

**\$139**



with probes

OVER 200 NOW SOLD

### EA INVERTER INCLUDING TRANSFORMER 300 WATTS

**\$195**



JUNE EA 1982

P & P \$10.00  
Anywhere in Australia

#### SPECIFICATIONS FOR 300W INVERTER

Nominal Supply Voltage	12V DC
Output voltage	see table
Frequency	50Hz ± 0.05%
Regulation	see table
Maximum Load	300VA
Current Limiting	30A (primary)
Efficiency	see table

Resistive load W	Output voltage (RMS)	Input current (A)	Efficiency (%)	Battery life 40Ah/20h rate (minutes)
no load	210	1.2	0	—
40	235	4.5	60	240
100	240	11.3	62	80
140	240	15.0	69	60
200	240	20.1	78	50
240	240	24.0	79	32
300	235	29.6	82	28

### Tacho/dwell meter with digital display



MAY EA 1982

**\$79**

### 12/240 volt Inverter 40 WATTS



MAY EA 1982

**\$49.50**



### Engine Analyser Kit

**\$48.50**



JANUARY EA 1982 INCLUDES TEXTOL SOCKET

**\$55.00**

### Eprom Programmer

### REMOTE INFRARED TV SOUND CONTROL



E.A. JANUARY '83

**\$40**



Designed to relieve the long-suffering TV viewer from painful, brain-killing advertisements, our TV Sound Control provides remote control of volume. It gives eight steps of control, including full off, when total silence is called for. Give yourself a break and relieve advertising tedium today.



**\$55.00**
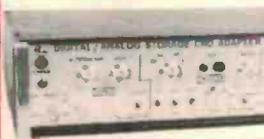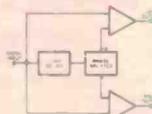
### STEREO SYNTHESISER FOR TUNERS AND VCRs

Enjoy the benefits of stereo sound from your video cassette recorder, TV or AM tuner with this Stereo Synthesiser. The circuit uses just four ICs and is easy to build.



**\$189.00**

### Analogue and Digital Storage CRO Kit

### EA DIGITAL READOUT FOR SW RECIEVERS

**\$72.00 COMPLETE**


OCTOBER EA 1982



### EA EASY-TO-BUILD FREEZER ALARM

**\$21**

OCTOBER EA 1982

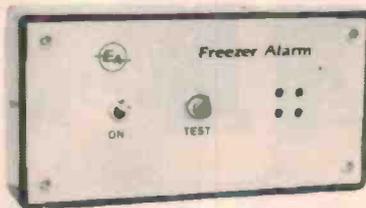

### Dual Tracking Power Supply



**\$87.50**

### 100w Sub-Woofer Amplifier

**\$85.00**



JULY EA 1982

Want to add digital frequency readout to an AM radio or shortwave communications receiver that uses an old-fashioned analog dial? This unit features a bright four-digit LED display, 1kHz resolution, and a 0.2s update time that's fast enough to follow the tuning knob.

#### SPECIFICATIONS

Ranges (full scale): 0-10MHz and 10-30MHz (optional).


Display: Four digit

Resolution: 1kHz with division switch set to divide by one; 10kHz with division switch set to divide by 10.

Sensitivity: Less than 100mV from 500kHz to 30MHz.

Offset frequency: Prototype set to 455kHz, but any offset frequency can be programmed.

### EA THEREMIN \$34.50

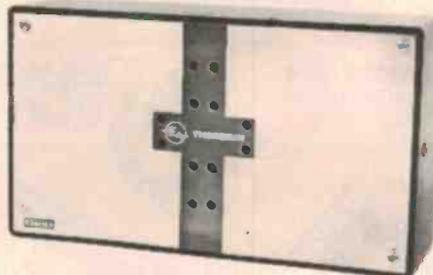

JUNE EA 1982

### PLUG PACK REGULATOR



**\$14**

Plugpack Extra

### EA ELECTRONIC STARTER FOR FLUORESCENT LAMPS



**\$5**

OCTOBER EA 1982

## ROD IRVING ELECTRONICS

425 High St., Northcote, Vic. 48-50 A'Beckett St., Melb., Vic.  
Phone (03) 489 8866, (03) 489 8131, Mail Order Hotline (03) 481 1436  
Mail orders to P.O. Box 235 Northcote 3070 Vic.

Minimum P & P \$3.00. Errors & omissions excepted.

Please address tax exempt, school, wholesale, and dealer enquiries to:

**RITRONICS WHOLESALE**

1st floor 425 High St. Northcote 3070 (03) 489 7099 (03) 481 1923 Telex AA 38897

# SHOP AROUND

This page is to assist readers in the continual search for components, kits, printed circuit boards and other parts for ETI projects and circuits. If you are looking for a particular item or project and it is not mentioned here, check with our advertisers.

## ETI-675 serial-parallel interface

It's a fact of life that computer peripherals, like printers, are available cheapest with a parallel interface but computers themselves generally have their output handling routines configured for serial operation. Inevitably, you want a printer, but balk at paying the extra \$100+ for the serial interface version. Well, now you can buy a printer at the best price (parallel interface) and still enjoy the convenience of your computer's serial output handling routines. Build this project!

The project is based on a UART made by General Instruments, the AY-3-1015D, distributed in Australia by Daneva of Melbourne. This chip has a number of features Geoff Nicholls took advantage of. It is fully double buffered, supports full duplex operation and can handle multiple baud rates, has tri-state outputs and only requires a single 5 V supply rail. Baud rate is externally selectable. It's got a lot going for it. The AY-3-1015D is the only 'special' component in the whole project, but stocks should be readily obtainable. We purchased one for the prototype from Avtek in Sydney.

This project will doubtless get wide support from kit suppliers, so you should have little difficulty. Initially, try Altronics in Perth, Avtek in Sydney and Rod Irving Electronics in Melbourne.

Components for the project should be readily available. If you want ready-made pc boards, then try Jaetronics in Melbourne, Jemal in Perth, Better PC Boards in Sydney or Mini Tech in New Zealand.

If you want to make your own pc board, then film positive or negative can be obtained from 'ETI-675 Artwork', ETI Magazine, P.O. Box 227, Waterloo NSW 2017, for the princely sum of just \$4.00, post paid.

## ETI-656 bug debugger

If you're right into micros and micro systems, devising your own software and generating your own 'firmware' in EPROMs, then this project will get you out of difficulties when

your new firmware stubbornly refuses to behave!

You should not have too much difficulty obtaining the components, but you may need to shop around a little to find the 6117 RAM chip.

Low insertion pressure sockets are much cheaper than zero insertion force (ZIF) sockets, but you might like the luxury of the latter for SK1 — the PROM socket on-board. Either type should not be difficult to source.

If you're using battery backup, the 3 V NiCad might take a little searching out. One place to try is Powersonic, 100-102 Buckingham St, Surry Hills 2010 NSW; (02)699-2722.

If you're making your own pc board and Scotchcal label, film positive or negative artwork can be obtained for just \$2.60, post paid, from 'ETI-656 Artwork', ETI Magazine, P.O. Box 227, Waterloo 2017 NSW.

## ETI-273 let caller

Give the umpire a serve! Build our let caller. Constructors should have little difficulty sourcing components for this one. The sensor coil is actually a reed relay coil and most electronics suppliers stock this item. As a point of reference, the one used in the prototype came from Dick Smith Electronics and is known as cat. no. S-1948. It costs just \$1. The box is a standard small (UB5) 'zippy' box. The piezoelectric buzzer used on the prototype was made by Murata and is distributed here by IRH in Sydney. Many types of piezo buzzer can be used — just make sure you get one that's loud enough for you. Tandy stores stock a whole range. Try their "super-loud" piezo buzzer, cat. no. 270-060, for example. The Richco KLB-350A curly-clip is distributed by Mayer Krieg (Sydney and Adelaide). Rod Irving Electronics will be stocking kits, and you might also try All Electronic Components — both in Melbourne.

If you want to make your own pc board and Scotchcal front panel, combined artwork can be obtained for just \$2.40, post paid, from 'ETI-273 Artwork', ETI Magazine, P.O. Box 227, Waterloo NSW 2017.

## ETI-166 function-pulse generator

We've had numerous 'phone calls from readers enquiring as to where a kit for this popular project could be obtained. Well, we're happy to report Altronics will be supplying them from next month. You can order by 'phone for the cost of a local call as they have an INWATTS line. The number is 008-999-007. The kit will include everything, including the things we didn't think of, according to Kevin Thompson, Altronics' Kit Manager. That should save you the hassle of running around trying to buy all the bits yourself.

## Printed circuit boards

Almost every pc board (and most front panels) ever published by ETI may be obtained from:

All Electronic Components  
118 Lonsdale St  
Melbourne Vic 3000

For pc boards produced in recent years, the following suppliers either keep stocks on hand or can supply to order:

Jemal Products  
P.O. Box 168  
Victoria Park WA 6100

Jaetronics  
58 Appian Drive  
St Albans Vic 3021

Better PC Boards  
112 Robertson Rd  
Bass Hill NSW 2197

Mini Tech  
P.O. Box 9194  
Auckland N.Z.

the following retailers generally keep stocks on-hand of pc boards from recent years' ETIs:

Rod Irving Electronics  
425 High St  
Northcote Vic 3070

Billco Electronics  
Shop 2, 31 Pultney St  
Dandenong Vic 2175

Jaycar  
117 York St  
Sydney NSW 2000

## IS FINISH A PROBLEM?

Trim and Rework whilst Assembling?  
Special shapes? Prototype construction?  
Product need that little touch?

**WE HAVE THE ANSWERS**

	Jigsaw 12V DC	000-62-108 JIGSAW—\$39.22 inc. S/Tax. Cuts anywhere—1mm radius corners. Wood, plastic, fibreglass, aluminium, PCB's—to 1/4" thick. A MUST! 000-62-117 Coarse, 000-62-144 Fine Blades—\$2.49 Set of 10.
	Angle Grinder 12V DC	000-63-605—ANGLE GRINDER \$47.70 inc. S/Tax. REAL BITE—Dresses boards and parts easily and quickly. Essential for production line—speeds up assembly operations.
	Gravilo 12V DC	Engrave Names and Numbers—Fine finishing 18000 RPM. 12V power supply. 000-62-608 \$17.40 inc. S/Tax.
	Wood 000-63-669 \$4.16	
	Metal 000-63-678 \$8.16	
Fit these blades to your Angle Grinder—Use it in the Drill Stand—dock those connectors, strips, sockets, etc.		

Send Self Addressed Envelope for full price and accessory list. Accessories include points, cutters, blades, files, brushes, stones, etc.

NAME .....  
ADDRESS .....  
BANKCARD NO. OR CHEQUE .....  
EXPIRY DATE ..... VALUE ..... SIGNED .....

**minitool**  
AUSTRALIA PTY. LTD.  
134A AYR STREET,  
DONCASTER VIC. 3108  
Tel. 850 9887



Post & Pack  
To \$25+\$3.50  
To \$100+\$5.00  
To \$150+\$7.00  
To \$400+\$10.00  
Over \$400+\$14.00

# STC CHAIRMAN WINS WORLD COMMUNICATIONS YEAR AWARD

**M**r Allen Deegan, Chairman and Managing Director of Standard Telephones & Cables Pty. Limited, has won the prestige World Communications Year Award.

The award, sponsored by the Federal Department of Communications and the Overseas Telecommunications Commission (OTC), is for the Australian who has furthered the influence of communications on Australian life.

Mr Deegan, 59, of Sydney, is also President of the Australian Electronics Industry Association, which represents 40 of the nation's leading companies in the telecommunications and electronics field. He is a Vice-president of the NSW Branch of the Metal Trades Industry Association and a member of the Electronics Advisory Council.

He is also Chairman of STC-Cannon Components, Austral Standard Cables and Bly's Industries, and a Director of

Standard Telephones & Cables (New Zealand), International Telephone and Telegraph Corporation (ITT) New Zealand and the Australia-New Zealand Businessmen's Council.

Nominees for the award, to mark World Communications Year, were received from both the technical side of the industry and from those who have shown leadership in putting communications into use.

Mr Deegan joined STC at the age of 15. He served with the RAAF during the War in the electronics branch and returned to STC in 1945, rising through the ranks to become Managing Director in 1970 and Chairman of the Board seven years later.

His visionary attitude in initiating and guiding many dev-

elopments involving communications, has made STC a leader in high technology. These developments include the establishment of a new \$10 million factory at Liverpool for the manufacture of undersea electronics repeaters for the Sydney to Vancouver ANZCAN communication cable and sophisticated harness cable

equipment for Aussat and other satellites for export overseas.


The judging panel for the award was the OTC General Manager, W. T. Schmidt; secretary of the Department of Communications, R. B. Lansdown and former ABC chairman, Dame Leonie Kramer.

## ENCODER/DECODER SUITS 'MANDATORY QUIET BASE'

**S**ignalling Technology has released two new Australian-made continuous-tone coded squelch (CTCSS) modules, as sub-audio control signalling elements in VHF/UHF portable and mobile radio equipment.

Under the Federal Department of Communications' new policy, it is mandatory for all new systems to have a quiet base-station facility.

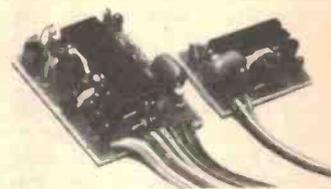The CTCSS modules enable quiet base/quiet mobile operation, eliminating annoying chatter and interference by other channel uses. Key features are their small size and ease of



installation, making them suitable for virtually all types of radio communications equipment.

For further information, contact Signalling Technology, 2 Apsley Place, Seaford Vic. 3198. (03)786-0077.

## MARINE RADIO HANDBOOK

**T**he boating industry is booming, despite the harsh economic climate. Unfortunately, more people are getting into trouble on the water, something authorities believe could be avoided in many cases if communications on the water were improved.

However, there is still considerable confusion surrounding the essentials of marine radio. Dick Smith's new book, 'Australian Marine Radio Handbook' is designed to help answer many questions about marine radio. Questions covered include; what is marine radio? Which one is right for me? What about licences, antennas, installation, correct procedures and frequencies?

The book is edited by Tony Clegg, an authority on Australian marine radio who states, "If just one life is saved, the book will have achieved its purpose."



The 'Australian Marine Radio Handbook' is listed in Dick Smith's catalogue as No. B-9604 and retails for \$12.95. In addition to Dick Smith stores, the book is also available from newsagents.

## INTERFERENCE FROM CORDLESS TELEPHONES

**U**napproved cordless telephones being sold to residents and businesses were causing serious interference to telecommunications in the Gold Coast area, said a spokesman for the Department of Communications.

The spokesman said that many of the users might not be aware that they were operating illegal equipment because in many cases false approval stickers had been attached.

Apparently this warning had become necessary following the receipt of numerous complaints

recently of serious interference to television reception and to other radiocommunications services, caused by the use of unapproved equipment of this type.

People requiring further information should ring Mr Boyd Rayment, Department of Communications, (07)52-8822, or write to the State Manager, Radio Frequency Management Division, Department of Communications, Aviation House, Cnr Wickham and Ballow Streets, Fortitude Valley Qld 4006.

## MOTOROLA'S 'EXPO' HANDHELD REDUCES SIZE AND WEIGHT

Motorola Australia Pty. Limited announced its new "Expo" series portable radio claiming it provides a "dramatic breakthrough" in size and weight.

Two-way portable radios are indispensable to many segments of business, industry, public utilities, police and firefighters plus many other people who are frequently on foot... on-the-go and need to communicate.

In addition to the demand for dependable two-way portable radio performance by these users, there has always been a need for a radio that is not only compact in size, but light weight as well, providing ultimate carrying convenience.

Motorola has turned these requirements into reality... thanks to years of experience, combined with advanced technology and a new generation of microelectronics, they say.

Only 224.53 cm<sup>3</sup> in volume and 358 g in weight, Expo is the smallest and lightest handie-

talkie Motorola has ever built!

The Expo series portable radio meets a variety of severe environmental tests established by US Military Standard 810C, plus Motorola's own unique stringent Accelerated Life Test.

For optimum protection if you work in or near a wet environment, certain Expo models have been designed, tested, and built to withstand complete submersion in up to three feet of fresh water for two hours.

A long list of options and unique accessories are available with the Expo series radio such as... private-line and digital private line coded squelch protection to reduce co-channel message reception and Quick-call II for the benefits of portable and paging communications in one small package.

The remote radio adaptor allows it to operate as a remote speaker microphone with antenna for both improved audio reception and RF radiation.



Additional information about Motorola's Expo series FM portable radio is available from Motorola Australia Pty. Limited, 666 Wellington Rd, Mulgrave Vic. 3170. (03)561-3555.

## BROADBAND HF ANTENNA

Antenna Engineering Australia's new broadband HF antenna, the Model 4104B, needs only a 15-metre pole, mast, tree or building for support.

It also does not require any adjustment, or special antenna tuning unit, as it is broadband over its full operating range of 2 MHz to 14 MHz.

Suited to the low-power (400 W PEP) SSB HF transceivers, the Model 4104B needs only 20 metres between the main support and the low stub mast. The antenna comes complete with a halyard and pulley for attachment to a support structure.

The radiation pattern of the antenna is basically omnidirectional, and it is suitable for communications over distances up to 1000 kilometres.

For further details, contact Antenna Engineering Australia, P.O. Box 191, Croydon Vic. 3136. (03)728-1777.

## 27 MHz CB BASE ANTENNAS

Imark has released three new base antennas for use by 27 MHz CB radio operators.


The Hoxin GP-27 is a 5/8-wave antenna, 6.48 metres high and has a gain of 4.2 dB. Three radials are included, and no VSWR adjustment is necessary.

The Hoxin GPA-27 is a half-wave antenna, 5.4 metres high with 3.4 dB of gain. No radials are used and no VSWR adjustment is necessary. It is described as a simple, efficient antenna with the least wind-load area.

The Hoxin GPV-2 is another half-wave antenna, 5.4 metres high and with a gain of 3.4 dB. It has three short radials and features a pi-VSWR matching system.

The Hoxin antennas, which are made in Japan, feature aluminium construction. All tubes are 'deburred' to prevent seizing during assembly.

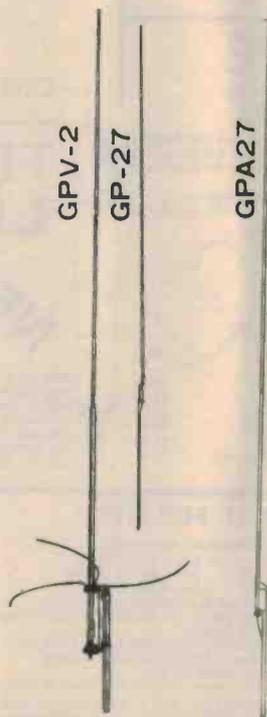Further details can be obtained from Imark, 167 Roden Street, West Melbourne Vic 3003. (03)329-5433.



## COMPUTERISED RADIO DESPATCH SYSTEM

Omnitronics has announced the release of the DL800 computerized vehicle despatch system.

Developed in conjunction with the West Australian Police Department, the transmission medium is the existing VHF (or UHF) radio network, the equipment type being irrelevant.

Previous attempts in this area have been hindered by the lack of a visual display unit suitable for the confines of a vehicle. The DL800 uses the latest in LCD technology to present 160 characters of alphanumeric information. A further 640 characters can be stored for later viewing.

Keyboards can be supplied to order — the standard is a 15-function status keypad plus full alphanumeric keyboard. The printer used by the WA police

has 40 columns and uses plain paper. This allows clear type at the lowest possible cost.

Omnitronics can provide interfacing to mainframe or minicomputers to allow complete system installation by one company. Although a mainframe or minicomputer allows the DL800 to operate to full advantage, connection to personal computers such as the Tandy Model 3, Apple etc, is quite feasible.

Other features of the DL800 include single, group and all call addressing modes, data encryption, remote equipment disabling should vehicle be stolen and high speed transmission of 1200 baud, PSK.

For further information, contact Omnitronics, Unit 3, 42 Osborne Place, Stirling WA 6021. (09)445-2633.

# GREAT NEW PRODUCTS

# FOR '84

## NEW uniden® WORLD BAND RADIO MODEL CR-2021



- SPECIFICATIONS:**
- AM/SSB/CW/FM
  - 150KHz - 29.999MHz (AM/SSB/CW)
  - FM - 108MHz
  - TRIPLE SUPERHET (AM/SSB/CW)
  - 3-WAY POWER AC/BATTS/DC (CAR)
  - BACKUP BATTERIES FOR MEMORY
  - WILL MEMORISE UP TO 6 PRESET FREQUENCIES
  - IT'S ALSO A SCANNER! WILL SCAN THE HF BAND BETWEEN PRE-SET LIMITS. FM SCAN AS WELL!
  - NARROW BAND FILTER
  - FACILITY FOR EXT. ANT. AND EARTH
  - SIZE: 320 x 155 x 65mm WEIGHT 2.1kg
- Quite frankly we are astounded at the quality of this unit. It is one of the smartest looking modern radios around!
- Each unit comes with an extensive manual which includes detailed info on Short Wave Listening as well as a comprehensive list of major Short Wave stations, their frequencies and their correspondence address.

**SPECIAL INTRODUCTORY PRICE**

HURRY STOCKS ARE STRICTLY LIMITED - SO ACT NOW!

# \$299 SAVE!

## 'TRADE' PACKS OF SCREWS & NUTS etc. NEW

By popular demand, Now you can get commonly used hardware in bulk and save a fortune!!

Cat. No.	DESCRIPTION	Price
HE-0736	Rubber feet stick-on 12mm Pkt.100	\$9.60
HE-0738	Rubber feet stick-on 20mm Pkt.100	\$11.50
HE-0913	TO-3 Mica insulator kit Pkt. 100	\$12.50
HE-0922	TO-220 Mica insulator kit Pkt.100	\$9.80
HP-2742	6BA Flat washer Pkt. 500	\$6.95
HP-2752	4BA Flat washer Pkt. 500	\$6.95
HS-1521	8BAx1/2" Cheesehead screw Pkt.500	\$7.50
HS-1522	4BAx1/2" Cheesehead screw Pkt.500	\$5.95
HS-1527	4BAx1/2" Cheesehead screw Pkt.500	\$5.95
HP-2712	6BA Hex nut brass Pkt.500	\$12.50
HP-2722	4BA Hex nut brass Pkt.500	\$12.50
HS-1607	No.4x1/2" Self tapper Pkt.500	\$4.50
HS-1609	No.4x1/2" Self tapper Pkt.500	\$5.50

## NEW SEALED PCB MOUNT ROTARY SWITCHES



We have decided to discontinue our range of open "skeleton" wafer switches for these. The new switches have contacts enclosed in a fully moulded plastic housing - reminiscent of European design rotaries. The silver-plated contacts are terminated with PCB pins instead of the usual eyelet. You can solder to the pin, of course, but the pin also inserts straight into a PCB. Another feature of the switch is its programmability. A removable ring with tab can be inserted into the switch several ways to your particular requirements. For example, if you purchase a 1 x pole 12 way (max) switch you could convert it to, say, 1 pole 7 way between stops. Versatile! Naturally the switches feature 3/8 x 32 TPI bush mount and a 1/4" shaft with standard flat. The shaft is hard nylon - moulded to help reduce signal capacitance problems.

They are almost the same price as the inferior wafer units.


Cat. No.	Description	Price
SR-1210	1 Pole x 12 way	1-9 ONLY \$1.95 ea
SR-1212	2 Pole x 6 way	
SR-1214	3 Pole x 4 way	
SR-1216	4 Pole x 3 way	10+ ONLY \$1.75 ea
SR-1218	6 Pole x 2 way	

## NEW MINI BREADBOARD

Just the right size for many small projects. This board has the same features as our larger breadboards but measures a compact 80mm x 60mm. It has 420 holes.

Perfect for the occasional project

Cat. PB-8808 \$6.95

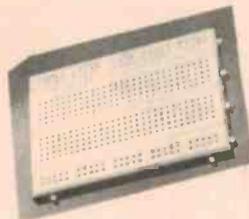

# SAVE \$6.95

## WHAT ARE STICKIES?

As you can see, "stickies" are stick-on templates. Attach the template to a panel (note the crosshairs for accurate alignment) and proceed to cut out a perfect hole! The plastic film also protects the panel from scratches while you are working on it.

Stickies are available for the common irregular hole cutouts i.e. Cannon DB 25, XL series chassis plug and socket and IEC-320 chassis (mains) plug.



Cat. No.	DESCRIPTION	Price
NL-4010	25 way 'D' template Pack of 6 templates	\$1.95
NL-4014	XLR-31 Series template Pack of 6 templates	\$1.95
NL-4018	XLR-32 Series template Pack of 6 templates	\$1.95
NL-4020	IEC 320 Chassis plug Pack of 6 templates	\$1.95
NL-4024	DIN Chassis socket template Pack of 6 templates	\$1.95

## NEW GAMES JOYSTICK

New low price! This unit, which is similar to our competitors units offers a huge saving. Why? Direct Import! The unit is not fitted with a connector either because a specific connector limits its use to specific computers. Fit the connector yourself and save a fortune!

Cat. XE-7032 \$19.95

## NEW 60-KEY COMPUTER KEYBOARD

- AS USED IN THE FAMOUS MICROBEE!
- SPST CONTACTS
- FRAME MOUNTED
- QUALITY UNIT

Cat. XE-3522



ONLY \$29.95

## TECHNICIANS LIGHT PROBE

# NEW \$12.95



This NZ made unit enables you to place a spot of bright light in the most awkward places. Ideal for servicemen or kit assemblers. A flash-light or lamp always seems to cast a shadow where you need to see! The exclusive design allows you to "poke light" around corners!! The unit is solidly made (Aluminium) and takes 2 penlight cells. A two function switch (lock-on and press-on) is also a feature.

Cat. TH-1838 \$12.95

## Jaycar Incorporating ELECTRONIC AGENCIES

**SYDNEY SHOWROOMS**  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
TELEX: 72293

**CARLINGFORD**  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

**CONCORD**  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

**HURSTVILLE** 121 FOREST ROAD - PHONE: (02) 570 7000

## NUMBER 1 FOR KITS

POST AND PACKING CHARGES	
\$5 - \$9.99 (\$1.50)	\$10 - \$24.99 (\$3.20)
\$25 - \$49.99 (\$4.50)	\$50 - \$99.99 (\$6.50)
\$100 - \$198 (\$8.00)	Over \$199 (\$10)

\*Free INSURANCE for Road & Registered Post over \$200\*

All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

**SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE**  
Mon - Fri 9am - 5.30pm; Sat - 9am - 12pm; Thurs night 8.30pm

**SHOP HOURS SYDNEY**  
Mon - Fri 8.30am - 5.30pm. Sat - 8.30am - 12pm; Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order

By



BANKCARD

Via Your Phone

# Design of loaded and trap dipoles — using a computer program

This article describes a method of designing simple HF antennas which are self-resonant on one or more frequencies. It includes a computer program (in BASIC) to simplify the calculations involved.

A. P. Boon VK7AW

A **SUITABLE ANTENNA** is a very necessary companion for any radio transmitter. There are many different types to choose from — multiband, broadband, monoband — to name but a few. An antenna can be self-resonant on the operating frequency or can be teamed with an antenna tuning unit which transforms the antenna impedance to the impedance required by the transmitter (usually 50 ohms resistive). This article describes a method of designing antennae which are self-resonant on one or more frequencies, and includes a computer program to simplify the calculations involved.

## The loaded dipole

A dipole antenna which is shorter than a half wavelength can be resonated at a given frequency by adding lumped inductance as shown in Figure 1. Provided that the value of L is chosen correctly, this antenna will behave like a physical halfwave dipole, at the resonant frequency. The direction of maximum radiation is at right angles to the dipole, and the impedance is resistive and about 70 ohms (depending on the height above ground), although the bandwidth for a given VSWR is less than for a full length dipole. Such a configuration often has advantages, especially in restricted-space applications.

For the person who wishes to build such a dipole with a minimum of fuss, it is useful to be able to calculate the values of L, the loading inductance, before constructing the prototype. In an article in *QST*, September 1974, Jerry Hall (K1PLP) published an empirical formula giving the value of L, shown in the panel here.

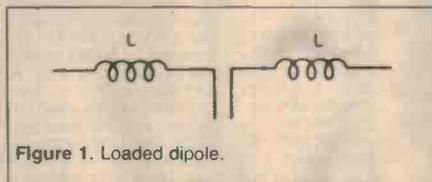


Figure 1. Loaded dipole.

This is a bit of a mouthful, even if you have a scientific programmable calculator! Subsequently, an article by Dick Sander (K5QY) appeared in *CQ*, December 1981, with a computer program for calculating the value of L for a simple loaded dipole. The program applied the formula directly, substituting wire gauge for diameter.

The main routine of the program described here uses the formula of K1PLP, rearranged for metric dimensions. Additional routines are included to ensure that most of the facilities required for the design of loaded, trapped and loaded-trap dipoles are available in the one program.

## Program description

The program is written in BASIC and provides eight options which appear in a menu (lines 200-285). After an option is selected and executed, the user is given the choice of performing further calculations (line 340), returning to the menu if so desired. Some checking of the range of input data is included, but gross errors (e.g. trying to input alphabetical characters in response to a request for a numerical value) will cause the program to halt abruptly.

The first option available calculates the loading inductance required for a dipole

which is shorter than a half wavelength at its operating frequency. The input data are *frequency* (MHz), *overall length* (metres), the *distance of the loading coil* from the centre of the dipole (metres) and the *dipole wire or tube diameter* (mm).

Intermediate expressions S1 to S5 are used to make the final expression for L (represented by S6 in line 1280) less complex than the original formula.

The second option on the menu calculates the physical length necessary to make a dipole resonant on a given frequency, with loading coils of value L micro-henries at a distance of B metres from the centre. This, in a sense, is the inverse of the first option, and uses an interactive technique to find the resonant length. The assumption is made that the resonant length lies outside the loading coils, but inside a half wavelength.

The initial guess is the average of these two values, and part of option 1 is called as a subroutine to calculate the value of loading required if the antenna were that length. The calculated value of loading is compared with the actual value, and the decision is made as to whether the resonant length is longer or shorter than the initial guess. This process is then repeated, with the interval of uncertainty being halved at every iteration.

The process halts when the calculated inductance for an estimate is within 10 mH of the actual value. Such a scheme may not be an optimum strategy for this particular calculation. However, it is only carried out once, and therefore the processing time is not significant.

Option 3 is a straightforward conversion of inductance into inductive reactance, at a given frequency. The inclusion of this function makes life a little easier in the design of trap dipoles, as will be seen later.

Option 4 calculates the values of inductance and capacitance required for a parallel LC trap, given the resonant frequency and the inductive reactance at a lower frequency. This function is essential for the design of trap dipoles.

Option 5 also calculates values for an LC trap. Given any two of the resonant frequency, the inductance and the capacitance, it will calculate the third value. ▶

$$L = \frac{10^6}{68\pi^2 f^2} \left\{ \frac{\left[ \ln \left( \frac{24 \left( \frac{234}{f} - B \right)}{D} \right) - 1 \right] \left[ \left( 1 - \frac{fB}{234} \right)^2 - 1 \right]}{\frac{234}{f} - B} - \frac{\left[ \ln \left( \frac{24 \left( \frac{A}{2} - B \right)}{D} \right) - 1 \right] \left[ \left( \frac{fA}{2} - fB \right)^2 - 1 \right]}{\frac{A}{2} - B} \right\} \mu\text{H}$$

where A is the overall length of the dipole in feet, B is the distance from the centre of the dipole to the loading coil. D is the diameter of the radiator (wire or tube) in inches, and f is the frequency in MHz.

Option 6 calculates the inductive reactance of an LC trap at a frequency below the resonant frequency. The inductive reactance is then converted into an equivalent inductance at the lower frequency; this calculation is also required in the design of trap dipoles.

Option 7 applies the well known formula (found in any ARRL *Radio Amateurs Handbook*) to find the number of turns required on a former to provide a specified inductance value. Option 8 is the way out.

## APPLICATIONS

### Simple loaded dipole

Determining the loading inductance required to resonate a dipole with an overall length less than a physical half wavelength is a straightforward application of menu option 1. For example, if you have space for a dipole 20 metres long, and you wish to load it for operation on 3.6 MHz, then select option 1 from the menu, enter 3.6 for the frequency, 20 metres for the overall length, your choice of the distance of the loading coil from the centre of the dipole, and the diameter of the wire being used.

The distance of the coil from the centre is not predetermined — you must specify it. The further from the centre is the coil, the higher the value of L, and thus the higher the resistance of the coil, for a given wire diameter. On the other hand, the closer the coil is to the centre, the higher will be the current flowing in it, and thus the higher the power dissipated in the (lower) resistance of the coil.

There will be an optimum position for maximum efficiency for a given set of physical parameters (dipole length, wire size, etc.), but this position is not determined by the program. Thus, there remains some scope for experimentation!

To get back to the example, if you select a position 5 metres from the centre and use wire 1.6 mm in diameter, the program will respond with "Loading Coil is 41.6 microhenry", and give you the option of doing further calculations. You can then select menu item 7 to calculate the number of turns required with a given former and wire size, to produce the required inductance.

### Two-frequency trap dipole

Let us suppose you have space for a dipole 30 metres long, and you wish to use it as 3.6 and 7.05 MHz. Since 30 metres is longer than a half wavelength at 7.05 MHz you can put traps, resonant at 7.05 MHz, a quarter wavelength from the centre, thus achieving a half-wave dipole at 7.05 MHz; the trap is inductive at 3.6 MHz, and will act as a loading coil at 3.6 MHz. The requirement is to select the inductance (and thence the capacitance) of the trap correctly. Proceed as follows:

- (i) Select menu option 1.
- (ii) The operating frequency is 3.6 MHz.
- (iii) The overall length of the dipole is 30 metres.
- (iv) Calculate a quarter wavelength at

7.05 MHz, less 5% to be 10.11 metres (not in the program — use your calculator!). This is the distance of the loading coil (i.e. the trap) from the centre of the dipole.

(v) Input the wire diameter, say 2 mm.

(vi) The program gives the required loading, 28.0 microhenry.

(vii) Use menu option 3 to convert the loading inductance (28.0  $\mu$ H) into inductive reactance at 3.6 MHz. The program returns a value of 633.35 ohms.

(viii) Use menu option 4 to calculate the trap values required. The resonant fre-

quency is 7.05 MHz, the trap has an inductive reactance of 633.35 ohms at 3.6 MHz. The program returns values of 20.7 microhenry and 24.6 picofarad.

By using parallel resonant traps of 20.7  $\mu$ H and 24.6 pF, the dipole will be resonant on both 3.6 and 7.05 MHz.

Of course, the value of 24.6 pF is not a preferred value. To use the nearest standard value (27 pF), calculate the inductance necessary to resonate with 27 pF at 7.05 MHz, using menu option 5. Enter "?" for the value of inductance, and the program will calculate the required value, in

```

100 REM * LOADED DIPOLE DESIGN PROGRAM.
120 REM * WITH ADDITIONAL ROUTINES NECESSARY FOR TRAP AND
130 REM * LOADED-TRAP DIPOLE DESIGN.
140 REM *
160 REM * PREPARED BY ANDREW BOON, VK7AW, 12th OCTOBER 83.
170 REM *
180 REM * Menu of available functions.
200 PRINT: PRINT "The Following Functions Are Available:": PRINT
230 PRINT "1. Calculate Inductance of Loading Coil for Loaded Dipole."
235 PRINT "2. Calculate Length of Dipole with Given Loading Inductances."
240 PRINT "3. Convert Inductance into Inductive Reactance."
250 PRINT "4. Calculate L,C for a Trap Filter, Given f0, fL & XL."
260 PRINT "5. Calculate f0, L, or C for a Trap (one unknown)."
270 PRINT "6. Calculate Equivalent Inductance of a Trap at Lower Freq."
280 PRINT "7. Calculate Number of Turns For a Given Inductance."
285 PRINT "8. Exit From This Program.": PRINT
300 INPUT "Your Selection (1 to 8, Return) ":S
310 IF (S<>INT(S)) OR (S<1) OR (S>8) THEN 300
315 IF S=8 THEN END
320 ON S GOSUB 1000,2000,3000,4000,5000,6000,7000
340 PRINT: INPUT "Any More Calculations (Y/N, Return) ":A$
350 IF (A$<>"Y") AND (A$<>"N") THEN 340
360 IF A$="Y" THEN 200 ELSE END
1000 REM * Dipole Loading Coil Calculation.
1010 REM * Based on formula of Jerry Hall (K1PLP) in "QST", Sept. 1974.
1020 REM *****
1040 PRINT: PRINT "Dipole Loading Coil Calculation.": PRINT
1060 INPUT "Operating Frequency in MHz ":f
1065 IF f>0 THEN 1070: GOSUB 10000: GOTO 1060
1070 INPUT "Total Length of Dipole in Metres ":A
1075 IF A>0 THEN 1080: GOSUB 10000: GOTO 1070
1080 INPUT "Distance from Centre of Dipole to Loading Coil, metres ":B
1085 IF B>0 AND B<A/2 THEN 1090: GOSUB 10000: GOTO 1080
1090 INPUT "Diameter of Wire used in the Dipole (mm) ":D
1095 IF D>0 THEN 1098: GOSUB 10000: GOTO 1090
1098 GOSUB 1200
1100 PRINT: PRINT USING "Loading Coil is ###.#",S6:
1105 PRINT " microhenries.": PRINT
1110 RETURN
1200 REM Calculate loading coil inductance.
1210 REM For formula see "QST", Sept. 1974, p.28.
1230 S1=1E6/(223.1*(PI*f)^2): S2=71.32/f-B
1250 S3=1-f*B/71.32: S4=A/2-B: S5=2000/D
1280 S6=S1*(LOG(S5*S2)-1)*(S3^2-1)/S2 - (LOG(S5*S4)-1)*(S4+f/71.32)^2-1/S4)
1290 RETURN
2000 REM * Determine Physical Length of a Resonant Dipole with Loading Coils
2020 REM * of Inductance L microhenry, B metres from Centre of Dipole.
2040 REM *****
2050 INPUT "Value of Loading Coils, uH ":L
2055 IF L>0 THEN 2060: GOSUB 10000: GOTO 2050
2060 INPUT "Frequency of Operation (MHz) ":f
2065 IF f>0 THEN 2070: GOSUB 10000: GOTO 2060
2070 INPUT "Diameter of Dipole Wire (mm) ":D
2075 IF D>0 THEN 2080: GOSUB 10000: GOTO 2070
2080 INPUT "Distance of Loading Coil from centre (m) ":B
2082 REM Check that Coils are not too far out.
2090 W=0.5*300/f+0.95: REM 95% of a half-wavelength.
2100 IF (2*B<W) THEN 2120
2110 PRINT "Loading Coils Beyond Quarter-Wavelength.":RETURN
2120 MI=2*B: MA=W: REM Minimum and Maximum possibilities.
2125 A=0.5*(MA+MI): REM Next Guess for A is midway between Min and Max.
2130 GOSUB 1200: REM Calculate Loading Coil for this Position.
2140 IF ABS(L-S6)<0.01 THEN GOTO 2170
2150 IF S6<L THEN MA=A ELSE MI=A
2160 GOTO 2125
2170 PRINT USING "Resonant Length with Loading Coil is ####.##",A:
2175 PRINT " metres.": PRINT
2190 RETURN
3000 REM * Convert Inductance to Inductive Reactance, at a given Frequency.
3020 REM *****
3030 INPUT "Inductance, microhenry ":L
3035 IF L>0 THEN 3040: GOSUB 10000: GOTO 3030
3040 INPUT "Frequency, MHz ":f
3045 IF f>0 THEN 3050: GOSUB 10000: GOTO 3040
3050 PRINT USING "Inductive Reactance is ####.##",2*PI*f*L:
3060 PRINT " Ohms.": PRINT

```

# Design of loaded and trap dipoles

this case 18.9 microhenry. Then, using menu option 6, the equivalent inductance of the trap at 3.6 MHz is calculated i.e.: 25.6  $\mu$ H. Use menu option 2 to calculate the exact length of a loaded dipole operating at 3.6 MHz with a 25.6  $\mu$ H loading coil at a distance of 10.11 metres from the centre. The value obtained is 30.48 metres. By cutting the dipole to 30.48 metres overall length (including the physical length of the loading coil formers), you have a dipole which is resonant on both 3.6 and 7.05 MHz, and a trap which uses standard values of capacitance, i.e: 27 pF.

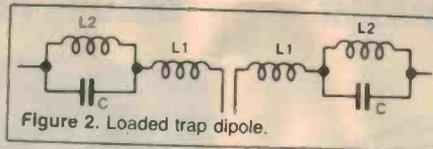


Figure 2. Loaded trap dipole.

## Loaded trap dipole

For applications in more restricted space than Example 2, the dipole could be loaded for operation on the higher frequency. For example, if only 20 metres was available for the dipole and operation on 3.6 and 7.05 MHz was required, one possibility

would be to place a loading coil three metres from the centre, and a 7.05 MHz trap six metres from the centre. We thus form a loaded dipole on both frequencies, with two pairs of loading coils for the lower frequency, as in Figure 2. Proceed as follows:

(i) Select option 1 to calculate the value of the inner loading coils, L1. Use 7.05 MHz, 12 metres as the overall length, three metres from the centre to the loading coil and, say, 2 mm wire. The program calculates 14.4  $\mu$ H as the loading coil value.

(ii) Use option 2 to calculate the physical length of a dipole resonant at 3.6 MHz, when loading coils of 14.4  $\mu$ H are placed three metres from the centre. The value calculated is 27.21 metres. The full span of a half wave dipole at 3.6 MHz is 95% of the actual value, i.e: 39.58 metres. Thus the loading coil has the effect of shortening the half wave dipole by 39.58 - 27.21 = 12.37 metres.

(iii) Use option 1 to calculate the inductance required of the traps to resonate a dipole of length 20 + 12.37 = 32.37 metres, at 3.6 MHz, when the trap (loading coil) is placed 6 + 12.37/2 = 12.19 metres from the centre. This gives a value of 30.3  $\mu$ H.

(iv) Use option 3 to convert 30.3  $\mu$ H to inductive reactance at 3.6 MHz. The value returned is 685.37 ohms.

(v) The trap must resonate at 7.05 MHz and have an inductive reactance of 685.37 Ohms at 3.6 MHz. Use option 4 to calculate the values of L2 and C for the trap. The program returns values of 22.4  $\mu$ H and 22.8 pF.

Once again, a similar procedure can be followed as for Example 2, to calculate the value of L2 and the length of the outer section of the dipole, if a standard value of capacitance (e.g: 22 pF) is used.

No more examples will be presented here, but the procedures detailed above can be extended, for example, to tri-band trap dipoles. Simply work outwards from the centre, considering the highest frequency first; the trap for the highest frequency becomes a loading inductance for the lower frequencies. The middle frequency uses a loaded trap dipole (as for Example 3), and the lowest frequency has two loading inductances.

As regards the accuracy of the calculations, K1PLP made the comment (in the QST article) that "the final inductance values found by cut-and-try pruning for lowest SWR at the desired frequency have been so close to the value from calculations that a laboratory bridge was necessary to measure the difference." This was referring to simple loaded dipoles.

A loaded trap dipole was recently designed using the procedure of Example 3; the traps and loading coils were made up to the calculated values, and when the antenna was erected, no pruning was required. The SWR minima occurred within 3 kHz of the design values.

```

3070 RETURN
4000 REM * Calculate Values of L,C for a Trap Filter, given the Resonant
4010 REM * Frequency and the Inductive Reactance at a Lower Frequency.
4020 REM *****
4030 INPUT "Resonant Frequency of Trap, MHz "f0
4040 IF f0>0 THEN 4050: GOSUB 10000: GOTO 4030
4050 INPUT "Inductive Reactance at Lower Frequency, Ohms "XL
4060 IF XL>0 THEN 4070: GOSUB 10000: GOTO 4050
4070 INPUT "Lower Frequency, MHz "fL
4080 IF fL>0 AND fL<f0 THEN 4090: GOSUB 10000: GOTO 4070
4090 WO=2*PI*f0: WL=2*PI*fL
4100 C=WL/(XL*(WO*WO-WL*WL))*1E6
4110 L=1/(WO*WO*C)*1E6
4120 PRINT USING "Values for Trap are: L=####.#,L1: PRINT " uH"
4130 PRINT USING " C=####.#,C1: PRINT " pF"
4140 RETURN
5000 REM * Find Resonant Frequency, Inductance or Capacitance of a Parallel
5010 REM * Tuned Circuit, given 2 out of 3 of the values.
5020 REM *****
5030 INPUT "Resonant Frequency, MHz (or '?' if unknown) ",f0$
5040 IF f0$='?' OR VAL(f0$)>0 THEN 5050: GOSUB 10000: GOTO 5030
5050 INPUT "Inductance, microhenry (or '?' if unknown) ",L$
5060 IF L$='?' OR VAL(L$)>0 THEN 5070: GOSUB 10000: GOTO 5050
5070 INPUT "Capacitance, picofarad (or '?' if unknown) ",C$
5080 IF C$='?' OR VAL(C$)>0 THEN 5090: GOSUB 10000: GOTO 5070
5090 IF f0$='?' AND VAL(L$)>0 AND VAL(C$)>0 THEN 5200
5100 IF L$='?' AND VAL(f0$)>0 AND VAL(C$)>0 THEN 5300
5110 IF C$='?' AND VAL(f0$)>0 AND VAL(L$)>0 THEN 5400
5120 PRINT "Must have 2 values given and 1 unknown.": GOTO 5030
5200 REM Calculate Resonant Frequency.
5210 L=VAL(L$): C=VAL(C$): f0=1E3/(2*PI*SQR(L*C))
5220 PRINT USING "Resonant Frequency is ###.##,f0: PRINT " MHz,"
5230 RETURN
5300 REM Calculate Inductance.
5310 f0=VAL(f0$): C=VAL(C$): L=1E6/(4*PI*PI*f0*f0*C)
5320 PRINT USING "Inductance Required is ###.#,L:PRINT " microhenry,"
5330 RETURN
5400 REM Calculate Capacitance.
5410 f0=VAL(f0$): L=VAL(L$): C=1E6/(4*PI*PI*f0*f0*L)
5420 PRINT USING "Capacitance Required is ###.#,C: PRINT " pF,"
5430 RETURN
6000 REM * Calculate the Equivalent Inductance of a Parallel Resonant
6010 REM * Trap, at a Frequency below the Resonant Frequency.
6030 REM *****
6100 INPUT "Resonant frequency of Trap, MHz "f0
6110 IF f0>0 THEN 6120: GOSUB 10000: GOTO 6100
6120 INPUT "Inductance of Trap, microhenry "L
6130 IF L>0 THEN 6140: GOSUB 10000: GOTO 6120
6140 WO=2*PI*f0: C=1E6/(WO*WO*L)
6150 PRINT USING "(Capacitance should be ###.#,C: PRINT " pF,)"
6160 INPUT "Lower Frequency, MHz "fL
6170 IF fL>0 AND fL<f0 THEN 6180: GOSUB 10000: GOTO 6160
6180 WL=2*PI*fL: LE=L/(1-(WL*WL)/(WO*WO))
6190 PRINT USING "Equivalent Inductance at Lower Frequency is ###.#,LE:
6200 PRINT " microhenry,"
6210 RETURN
7000 REM * Calculate Number of Turns For a Given Inductance Value.
7020 REM * Coil Former Diameter, Pitch and Wire Diameter.
7030 REM *****
7040 INPUT "Diameter of Coil Former (mm) "A
7050 IF A>0 THEN 7060: GOSUB 10000: GOTO 7040
7060 INPUT "Diameter of Wire (mm) "D
7070 IF D>0 AND D<A/2 THEN 7080: GOSUB 10000: GOTO 7060
7080 INPUT "Coil Pitch (mm per turn) "P
7090 IF P>D THEN 7100: GOSUB 10000: GOTO 7080
7100 INPUT "Inductance Required (uH) "L
7110 IF L>0 THEN 7120: GOSUB 10000: GOTO 7100
7120 A=A*D: REM Calculate average diameter of coil.
7125 B=1016*P*L/(A*A)
7130 N=(B + SQR(B*B + 1828*L/A))/2
7140 REM Formula from ARRL Handbook, re-arranged and metricated.
7150 PRINT USING "Number of Turns Required is ####.#,N: PRINT
7170 RETURN
10000 REM * Subroutine executed when out-of-range data is detected.
10020 REM *****
10030 PRINT "Check the Value of Your Data Input.": PRINT
10050 RETURN
    
```

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS — PHONE ALTRONICS TOLL FREE 008-999-007 FOR NEXT DAY JETSERVICE DELIVERY

### KAISE DIGITAL MULTIMETER SK 6100



WAS \$89.95

Now \$59.95 Cat 01100

Check the specifications/features of this superb Digital Multimeter. **Autorange** with manual override **Auto Polarity** displays — sign when probes reversed **overrange indication** "Blink" and Buzzer warning **Low Battery Warning BATT** Sign shows. **Sampling Rate** 2 times SEC **Power Supply** 2 x A penlight batteries (300 hour continuous operation). **Fuse Protected**, spare fuse provided. **Zero Adjustment**, zero adjust button — a must if you change test probes. **LCD Display**, magnificent clear readout. **Inbuilt Buzzer**, available for continuity test, overload warning and switch warning. **Ranges** +/- 1000 V DC/600 V AC, AC and DC current, resistance 200 (Resolution .1 OHM) to 2000K OHM (resolution 1K OHM) in 5 ranges autorange **ACCURACY** .5% DC, .8% AC.

### DELUXE ABS INSTRUMENT CASE



Case color light grey front-rear panels black.

Our superb new instrument case will give your projects the professional appearance they deserve.

- \* Internal mounting posts enable a wide combination of PCB's, Transformers, etc. to be accommodated (screws supplied).
- \* PCB guide rails provided internally allow vertical PCB positioning to several locations.
- \* Removable front and rear panels. Attractive textured finish one side and plain the reverse side. (Enables direct engraving, silk screen printing etc. to plain side.)
- \* Great for test instruments and other high grade projects.

Overall Size: 200W x 160D x 70mmH

WAS NOW 10 + 50 +  
H0480 .. \$13.50 .. \$10.00 .... \$9.00 .... \$8.50

### MOLEX PIN SOCKETS

For use with single pins up to .5mm diam.  
Make your own sockets for IC's displays, LSI's etc.



P0700 Pack of 100. \$ 1.00  
P0701 Pack of 1000. \$12.50

Supplied on "Break off" header pre-spaced .1 Inch.

GET A TRADE PACK FOR YOUR WORKSHOP NOW.

# ALTRONICS

105 STIRLING ST. PERTH — FOR INSTANT SERVICE

008 999 007 TOLL FREE

(09) 328 1599 PERTH METRO AREA & AFTER HOURS RECORDED SERVICE

All Mail Orders: Box 8280, Stirling St, Perth WA 6000.

### ALTRONICS RESELLERS

Please note that resellers may not have all the items advertised in stock, and as resellers have to bear the cost of freight, prices may be slightly higher than advertised. ALTRONICS reseller prices should however represent a considerable saving over our competitors' prices.

VICTORIA	QUEENSLAND	WESTERN AUSTRALIA	SOUTH AUSTRALIA	NEW SOUTH WALES
<b>CITY</b> All Electronic Components ..... 662 3506 Electronics ..... 602 3499 MaGraths Electronics ..... 347 1122	<b>CITY</b> Deisound PL ..... 229 6155 <b>SUBURBAN</b> <b>BIRKDALE</b> Wholesale Sound Accessories ..... 207 2502 <b>FORTITUDE VALLEY</b> St. Lucia Electronics ..... 52 3547 <b>PADDINGTON</b> ECO Technics ..... 369 1474 <b>SALISBURY</b> Colourview Wholesale ..... 275 3188 <b>SLACKS CREEK</b> David Hall Electronics ..... 208 8808	<b>COUNTRY</b> <b>ALBANY</b> BP Electronics ..... 41 2681 <b>ESPERANCE</b> Esperance Communications ..... 71 3344 <b>GERALDTON</b> Geraldton TV and Radio ..... 21 2777 <b>KALGOORLIE</b> Todays Electronics ..... 21 5212 <b>MANDURAH</b> Kentrionics ..... 35 3227 <b>WYALKATCHEM</b> D & J Pease ..... 81 1132	<b>CITY</b> ADN Electronics ..... 212 5505 Protronics ..... 212 3111 <b>SUBURBAN</b> <b>BRIGHTON</b> Brighton Electronics ..... 296 3531 <b>CHRISTIES BEACH</b> Force Electronics ..... 382 3366 <b>ELIZABETH GROVE</b> A.E. Cooling ..... 255 2249 <b>KESWICK</b> Freeway Electric Wholesalers ..... 297 2033 <b>PROSPECT</b> Jensen Electronics ..... 269 4744	<b>CITY</b> Avtek Electronics ..... 267 8777 David Reid Electronics 267 1385 Jaycar ..... 264 6688 Radio Despatch ..... 211 0191 <b>SUBURBAN</b> <b>BIRKENHEAD</b> Birkenhead Electronics 81 4077 <b>CARLINGFORD</b> Jaycar ..... 872 4444 <b>CONCORD</b> Jaycar ..... 745 3077 <b>DEE WHY</b> David Ryall Electronics ..... 982 7500 <b>ENFIELD</b> Avtek ..... 745 2122 <b>HURSTVILLE</b> Jaycar ..... 570 7000 <b>LEWISHAM</b> PrePak Electronics ..... 569 9770 <b>MATTRAVILLE</b> Creative Electronics ..... 666 4000
<b>COUNTRY</b> <b>BENDIGO</b> Lindrea & Johnson ..... 41 1411 <b>MILDURA</b> Electronic and Digital Services ..... 23 3380 <b>SHEPPARTON</b> GV Electronics ..... 21 8866 <b>WODUNGA</b> A & M Electronics ..... 24 4588	<b>COUNTRY</b> <b>CAIRNS</b> Thompson Instrument Services ..... 51 2404 <b>GLADSTONE</b> Purley Electronics ..... 72 4321 <b>IPSWICH</b> P & P Electronics ..... 281 8001 <b>NAMBOUR</b> Namboour Electronics ..... 41 1604 <b>PALM BEACH</b> The Electronics Centre ..... 34 1248 <b>ROCKHAMPTON</b> Purley Electronics ..... 2 1058 <b>TOOWOOMBA</b> Hunts Electronics ..... 32 9677 <b>TOWNSVILLE</b> Solex ..... 72 2015	<b>NT</b> <b>DARWIN</b> Radio Parts Darwin ..... 81 8508 Ventronics ..... 81 3491 <b>ALICE SPRINGS</b> Ascorm Electronics ..... 52 1713 Farmer Electronics ..... 52 2967	<b>PORT PIRIE</b> G.F. & J.A. Pointon ..... 32 5141	<b>BROKEN HILL</b> Crystal TV ..... 4803 <b>COFFS HARBOUR</b> Coffs Harbour Electronics ..... 52 5684 <b>GOSFORD</b> Tomorrows Electronics ..... 24 7246 <b>KURRI KURRI</b> Kurr Electronics ..... 37 2141 <b>NEWCASTLE</b> D.G.E. Systems ..... 69 1625 George Brown & Co. .... 69 6399 <b>NOWRA</b> Vincom Electronics ..... 21 4011 <b>PENRITH</b> Acorn Electronics ..... 21 2409 <b>PORT MACQUARIE</b> Hall of Electronics ..... 83 7440 <b>RICHMOND</b> Vector Electronics ..... 78 4277 <b>TOUKLEY</b> TES Electronics ..... 96 4144 <b>WINDANG</b> Madjenk Electronics ..... 96 5066 <b>WINDSOR</b> M & E Electronic Communications ..... 77 5935
		<b>ACT</b> <b>CITY</b> Electronic Components ..... 80 4854 Scientronics ..... 54 8334	<b>TASMANIA</b> <b>CITY</b> D & I Agencies ..... 23 2842 <b>GEORGE HARVEY</b> Hobart ..... 34 2233 Launceston ..... 31 6533	<b>BATHURST</b> Sound of Music ..... 31 4421

RESELLERS WANTED IN ALL AREAS (Including WA).

Phone: STEVE WROBLEWSKI (09) 381 7233 for details.

# LETTERS



Sir,


Tom Moffat's article on a fax decoder (ETI, Sept. '83) was good to see but unfortunately there are a few errors which could lead to an incorrect understanding by some readers.

Firstly, amateur fax reception was very popular in the UK about 1959-61. Even in Australia I saw computer board amateur fax systems in 1970.

Secondly, the actual frequencies used, and the method of modulation seem to be misunderstood. In almost every case I have come across in the world, the high tone is exactly 2400 Hz. The reason for this will become clear later. An 800 Hz shift down to 1500 Hz is also common.

The modulation method is not just SSB as indicated. In normal amateur SSB systems the carrier may be suppressed by up to 40-60 dB and is really termed *single sideband-suppressed carrier*. However, in most fax work, although only one set of sidebands is transmitted, the carrier is only reduced by about 10 dB, giving rise to the term *single sideband — vestigial carrier*. (See Figure 1.) This vestige of carrier is used in the receiver to phase-lock a carrier insertion oscillator, thus ensuring freedom from drift. (See Figure 2).


Figure 1.

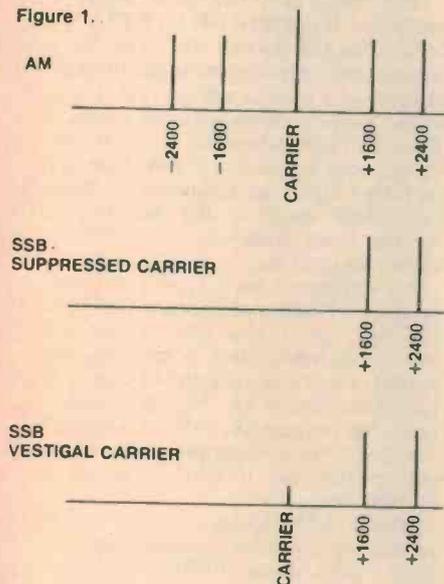

This can be quickly demonstrated on station AXM in just a few minutes. With my FRG7 receiver on 5100 kHz it was actually possible to recover some signal, even in the AM mode. Sure, the level was reduced because of the reduced carrier and only one sideband, but it was still receivable. Going to SSB resulted in a higher output level but introduced unacceptable drift in the 2400 Hz signal.


The requirement for an exact 2400 Hz is a fourth method of synchronisation which was not mentioned. In this method, a

Figure 2.

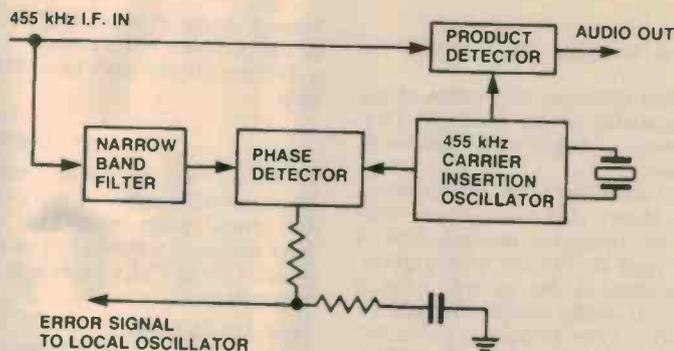

2400 Hz oscillator is phase-locked to the incoming 2400 Hz. The output from the oscillator is then put through a divider chain which produces a 50 Hz or 60 Hz signal which, when amplified, is used to drive the synchronisation motors. This ensures perfect synchronisation because the motors at the transmitting end are similarly driven from the divided output of a 2400 Hz oscillator there which is used to modulate the transmitter. This removes any reliance on common power grids or drift-free oscillators. (See Figure 3).


Figure 3.

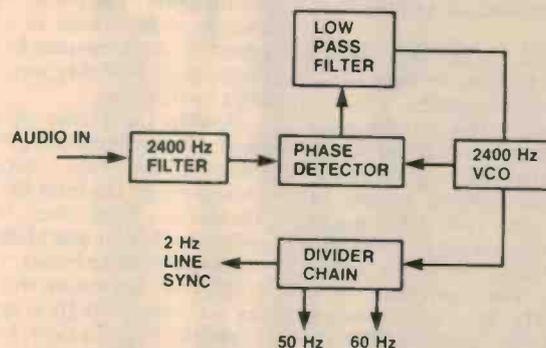

The simple phase detector/voltage comparator circuit shown in the article is very prone to noise because it really doesn't use the two frequencies which are transmitted, but will activate on the presence or absence of one of the frequencies alone. Modifying the LM311 comparator circuit to provide hysteresis should greatly improve performance.

An even better performance for binary type pictures is achieved by having separate narrowband filters for each frequency. The outputs are then detected and used as the inputs to an edge-triggered flip-flop. In this

Figure 4.

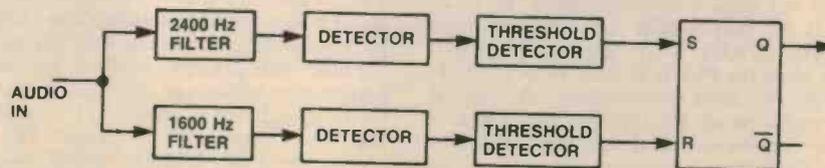

case, the absence of the last frequency will not cause a change of state, only the presence of the other frequency will cause it. This type of circuit is very immune to noise. (See Figure 4).


In systems which amplitude modulate the 2400 kHz, the level of the 2400 Hz signal is always kept more than 10% of the maximum level, this residual 10% being enough to lock on to.

Doug Rickard  
Leichhardt, NSW

Thanks for your letter and comments on the ETI-736 fax decoder. Detailed information on the system, modulation and demodulation methods was in short supply, so Tom 'went' with what he could get. The project was kept simple, yet effective and it does work quite well. The PLL detector does not work on the basis of the presence or absence of one of the two tones, it requires both tones, (one of which is always present). Adding some hysteresis to the LM311 may improve things.

Roger Harrison  
Editor, ETI.

# LETTERS

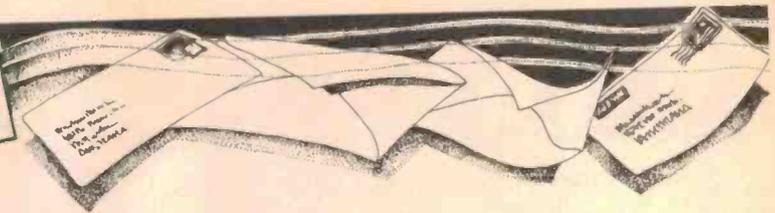

Dear Roger,

Thank you for your letter re the fax decoder.

A very good technical description of fax systems is available in the *Radio & Television Engineers Reference Handbook*, edited by Say.

Your other comment re the phase-locked loop (PLL) shows that you as well misunderstand the operation of phase-locked loops when used in this sort of operation. You are not alone in this, as even a lot of commercially available equipment makes a similar mistake. You can quickly prove this by setting up one of those IC types of PLL and then injecting signal which is different to the rest frequency of the PLL but within capture band. Without any input the output will be the quiescent error voltage. As soon as the input signal is turned on, a different error voltage will be generated as the PLL comes into lock. Remove the input signal and the error voltage will return to the quiescent state. Two frequencies are *NOT* required, just one frequency different from the PLL quiescent frequency. All that using two frequencies gives is an increase in the amplitude of the output signal if the two frequencies are at opposite sides of the PLL quiescent frequency.

A similar problem occurs with many modem circuits and particularly with some of the Kansas City tape decoders.

Another place where this is seen is in frequency discriminators which use cycle counting or timing techniques e.g: Electronics Australia's digital cassette system of about two years ago. To differentiate between the two frequencies of 2400 and 1200 Hz it used a timing technique where the timing interval was equivalent to a frequency of 1800 Hz. If a zero crossing occurred within the timing period a 2400 Hz signal was assumed, and if no zero crossing occurred within the timing period, then a 1200 Hz signal was assumed. However, it is patently obvious that the actual absence of any signal at all would similarly be detected as 1200 Hz i.e: the 1200 Hz signal was totally redundant and unnecessary.

As an example of a *good* design, see the article from *73 magazine* of September, 1982. Although originally designed as an RTTY decoder, it would make an excellent fax decoder. It uses a progressively soft limiter, important in relationship to *signal supervision factor* in PLLs. It also uses separate NE567 PLLs for each of the two frequencies. A very important point about the 567 tone decoder is that the output signal is *not* the error voltage from the PLL, but is the output of a coherent amplitude detector (CAD), so an output is generated only when the PLL is actually in lock. (N.B: Watch the loop bandwidths). A 7400 is employed as an RS flip flop to provide a 'slicer' action so that the actual presence of the alternative frequency is required to

cause a change of state, *not* just the absence or the presence of frequency.

Hoping all this may have been of some help.

Doug Rickard  
Leichhardt, NSW

(P.S. Yes — I have had a bit to do with phase-locked loops — I worked for NASA for several years using PLL systems and have designed a number of satellite ground stations using PLLs as well as many other applications.)

Dear Mr Rickard,

I have received via ETI two letters from you expressing dissatisfaction with my article on facsimile in that magazine. I will now answer some of the points you have made, after which I will consider the matter closed.

First, the matter of previous enthusiast activity in this field. Fair enough, anyone can go out and buy a fax machine, and receive weather pictures at home. Quite a few people are known to do this in America, paying well over a thousand dollars for a fax machine. Perhaps as you say, fax was popular in the UK around 1959-1960. That's not the point. The point of the article was to encourage the owner of a small computer system to use a resource he already has for a purpose he probably never thought of, at little further cost.

Now to the matter of fax transmission itself. The information given in the article came from some textbooks devoted exclusively to fax from the State Library of Tasmania, from the Weather Bureau offices in Hobart and Melbourne, and from my own reference books. I didn't just make it up. Your suggestion that the high tone of fax is exactly 2400 Hz is probably correct in a landline-based system, but the article concerned radio-facsimile, which is normally transmitted as pure FSK (frequency-shift keying).

The article instructed the user to switch his receiver to the SSB mode, the reason being to re-insert the carrier and allow demodulation to audio tones. In this case, the tones can be anything at all, depending on receiver tuning, and I chose 2300 Hz as the high one to ensure it could pass easily through a cheap receiver without a filter.

If you can hear a carrier, other than the two tones, from AXM you've got better ears than I have. The information booklet from AXM, dated 1 March 1983, specifies their class of emission as "F4". The book *Reference Data for Radio Engineers* (of which I am one) defines F4 as "facsimile by direct frequency modulation of the carrier". In other words, frequency-shift keying.

Phase-locked loops — there are always people who either say they don't work, or try to complicate a simple and elegant circuit into a mathematical jungle. The fact remains that the ETI-736 circuit, as pub-

lished, works extremely well. And it works by locking on to the frequency being received and following it, generating an error voltage which in fact becomes the recovered signal.

I didn't just make this up... the same information is available in data sheets on the 4046 PLL published by National Semiconductor, Phillips and Signetics, all of which I consulted before writing one word about the use of the chip. These include interesting discussions of how the PLL follows step changes in frequency, as found in RTTY and binary fax. If you still feel the PLL works in some different way, I suggest you build up the 736 circuit and investigate its operation with an oscilloscope. A picture is worth a thousand words.

Now we're up to your second letter, having brought into doubt the competence of Roger Harrison and experienced equipment manufacturers around the world. The experiment you describe, turning the signal to a PLL on and off, simply shows that it locks up with the signal there and loses lock when the signal disappears. I'd hate to rely on a PLL doing this in step with a signal containing modulation components up to 600 Hz or so.

This brings us to the 'good' design in *73 magazine*. It might be OK for RTTY but it's useless for fax. Here's why: The 567 tone decoder can only respond to the presence or absence of a tone at a finite rate. It's given in the *National Semiconductor Linear Data Book* as Fo/20 where Fo is the frequency the decoder is tuned to detect. Taking your preferred high tone frequency of 2400 Hz, the "fastest on/off cycling rate" is 120 Hz. At the black frequency of 1600 Hz, the cycle rate is 80 Hz.

My "inferior" fax system is required to produce a horizontal resolution of 590 dots per line, so if you take a line full of white/black/white/black transitions, over a period of half a second, the frequency to be recovered would be 590 Hz, nearly five times the frequency a 567 could reproduce. The 567 system might produce a recognizable picture but it would certainly be a blurred one.

The ETI-736 decoder is quite capable of recovering a picture element only one dot wide, even from 10 000 miles (16 000 km...Ed.) away. You can see individual dots in the picture on page 92 of the article, making up the latitude and longitude lines.

I do hope this letter has properly answered most of the points you made. It's interesting that other correspondence on this project has all been quite complimentary. By the way, I worked for NASA as well... Nevada Test Site 1964, Bermuda 1964, Hawaii 1965, and then back to Nevada again. Did we cross paths somewhere?

Regards  
Tom Moffat

# MINI-MART

Where readers can advertise —  
For Sale/Wanted/Swap/Join

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — please — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received; however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

• Conditions: Name and address plus phone number (if required) must be included with the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted.

Send your advert to:

ETI Mini-Mart,  
140 Joynton Ave, Waterloo NSW 2017.

## AUDIO

FOR SALE: SME model 3009 series II Improved arm, mint condition \$52. JH Formula 4 pickup arm, \$65, Microselk I tone arm, \$85 (02)46-5451.

FOR SALE: QUAD II valve amp, \$110; model 22 quad pre-amp, \$90. Complete circuit and spare set of KT66s. (02)46-5451.

FOR SALE: VALVE amplifier, Sansul AY-70, 20/20 W RMS, mint conditions, complete with circuit and spare valves. \$130 ono. (02)46-5451.

## COMMUNICATIONS

FOR SALE: TRIO transceiver TS510 complete with mic and instruction book. 10-80 metres, Suit novice. \$150. K. Peters (02)98-7151 VK2ATP.

WANTED: INFORMATION on construction of MW DX radio or VHF TV DX antenna. All replies answered. Write only please. B. Taylor, 38 Cecil St, Australind WA 6232.

FOR SALE: JIL SX-200 SCANNER receiver. Frequency range 26 MHz to 514 MHz. FM/AM operation. Only six months old. Bargain at \$499 (02)98-9447.

FOR SALE: TRANSCEIVER Yaesu FT-one all band SSB. Full technical handbook. Near new condition. \$1650 ono. Ken Munyard (07)351-4433.

## MISCELLANEOUS

WANTED: 'PRACTICAL Electronics', March 1983 or a photocopy of part two of 'Into the real world'. B. Le Marshall, 6 Exchange St, Ballarat Vic 3350. (053)32-2793.

WANTED: TDK magnetic, gold-plated ladies necklace. L. Hollow, 844 Burke Rd, Canterbury Vic. 3126. (03)82-6758.

FOR SALE: OSCILLOSCOPE, National portable VP-5650A with dual trace dc 50 MHz delayed sweep. As new with all probes, manual etc. \$1000 Peter (099)36-6035.

FOR SALE: ETI YEAR books, 1-4, 1971-1975 in mint condition. J. Cloosterman, PO Box 232, Hindmarsh SA 5007. (08)333-0529.

FOR SALE: BWD 820, 25 MHz dual trace oscilloscope, near new, \$800 ono. Maurice Hamilton, PO Box 106, Indooroopilly Qld. 4068. (07)370-7529.

FOR SALE: LARGE assortment of components ideal for enthusiasts workshop. Resistors, caps, various semiconductor boards etc. Cheap. Mal, 21 Alstrope Ave, Modbury SA (08)264-8207.

FOR SALE: OSCILLOSCOPE 60 MHz, Tektronix 2213, \$1450. Digital multimeter, Beckman 3010 \$150 Panbrake metal bender \$40. All in mint condition. Ron Coleman (062)88-5369.

FOR SALE: VIDEO cartridges, Sanyo VT20C, new \$8 each. Also top brand video tapes in 1" and 1/2" sizes at bargain prices. G. Terel, 8 Wurth P1, Chiffley ACT 2606. (062)81-5091.

WANTED: AWA Voltomyst VTVM. Bruce Rush-ton, 5 Nandi St, Coonabarabran NSW 2357. (068)42-1894 after 7 pm.

## COMPUTERS

FOR SALE: 8" Shugart floppy disk drives (two) in chassis with power supply and fan. Single sided. \$800. Adrian (092)349-3684.

FOR SALE: ATARI 400 16K computer, all manuals, tape recorder, BASIC cartridge, 30 games. Complete systems as new. \$575 ono. Robert Lang (02)499-2355 ah.

FOR SALE: ITOH 8300P printer, tractor feed, Centronics interface, 125 cps, as new with user and maintenance manuals, spare ribbons. \$280 ono. Steve (03)818-7898 ah.

FOR SALE: DEFENDER, very fast machine code game for Dream 6800, 1K version \$2, 2K version \$4. K. Bennett, 6 Barilla Court, Burwood East Vic. 3151.

FOR SALE: TEAC 5 1/4" slim line Apple compatible drive minus controller but lead to fit card. Excellent condition, hardly used, \$250 ono. Ralph Teichel (03)898-6798.

FOR SALE: INTEL multibus SBC type 86/05 (8086 processor). Still in original packing with manual. \$1100 ono. Also 8087 maths co-processor \$400, GPIB interface \$400. D. Phillips (085)27-2190 bh or (085)22-3132 ah.

FOR SALE: TRS-80 32K extended colour basic computer, two disk drives, joysticks. Purchased July 1983. \$1700 ono. Michael (03)606-8362 bh or (03)842-2004 ah.

FOR SALE: SUPER 80 disassembler, \$9. Sprocket fanfold paper 243 mm x 280 mm, \$19 a box. Siemens M100 Teleprinter \$60. R. Vowels, 93 Park Drive, Parkville Vic 3052.

FOR SALE: 16K ZX81 SOFTWARE: ZX monopoly \$12, shape table plotter \$9, tape copier \$9, the lot \$25. N. Kefford, 120 Church St, Yass NSW 2582. (062)26-2631.

FOR SALE: FLOPPY disk drive 1 Meg Shugart SA 850/851 DSDD STD Shugart SA 800 I/O compatible IBM 3270 format or hard sector compatible, new in box. \$390. Ralph (047)59-1721.

FOR SALE: S100 BOARDS. MW 6545 VDU and 4 MHz DGZ80 to match. Also included set of PROMS to go with CCS 2422 controller to make a complete 8 or 5 inch disk system. Software included. \$370 ono. East Ryde. (02)888-7624.

FOR SALE: DGZ80 S100 CPU, DG640 VDU, DGOS SD Expando RAM with 32K, motherboard, power supply, keyboard, monitor, basic plus S/W. Best offer. Gordon (02)587-3449.

FOR SALE: MICROBEE 16K plus, with heaps of software. \$350. David (02)871-7090 ah.

WANTED: MICROBEE user in Kingaroy would like to contact others in the area. C. Cuvel, 21 Patrick St, Kingaroy. (071)62-3219.

FOR SALE: NEW computer Hitachi MB 6890, 48K, RS232, Centronics and lightpen port, RGB-colour o/p, 2 x 320K DS/DD drive, green monitor, \$2200 ono. Robert (02)662-4150 ah.

WANTED: MICROSOFT Fortran diskette and documentation to suit System 80 or TRS Model 1. Paul Spresser, 2nd Field Supply, Bn Lavarack Bks, Townsville Qld 4813. (077)71-7760.

FOR SALE: MICROBEE complete system including 32K Bee, serial printer, computer monitor, data recorder, all applied tech software and more, blank cassettes, manuals, \$1299 ono. Andrew Petty (02)48-3807.

FOR SALE: DISK drive, controller, DOS manual and printer serial interface for Apple II \$390. Tested but unused (bought Microbee instead). Alex (03)341-5424.


FOR SALE: DICK Smith VZ-200 colour computer with \$30 worth of software and literature. Cost around \$230, sell for \$195. Peter (03)584-6731.

FOR SALE: LATEST Rev. 7 Apple II Europlus 64K with lower case chip, 16K RAM card, B & W monitor, colour card with RF modulator, disk drive with controller card, Z80 softcard, 80-column card, GP-80M Seikosha dot matrix printer, box of fan-fold printer paper, spare printer ribbon, TKC hand paddles, TG Products joystick, includes all manuals plus extra programming books, over 1500 of original software plus a stack of public domain software, computer fan, box of 10 diskettes, serial printer interface card, plastic protective keyboard cover. \$4000 ono. Brian Knott (089)62-3073.

FOR SALE: VIC-20 computer games and utilities. \$2 per program, cheaper for bulk. Send SAE for a complete list. Chris Groenhout, 25 Kerferd St, Watson ACT 2602.

FOR SALE: ACT VIC-20 bi-monthly magazine. Many interesting articles and programs. December issue \$1.50. Bi-monthly \$8 per year. Chris Groenhout, 25 Kerferd St, Watson ACT 2602.

# DREGS

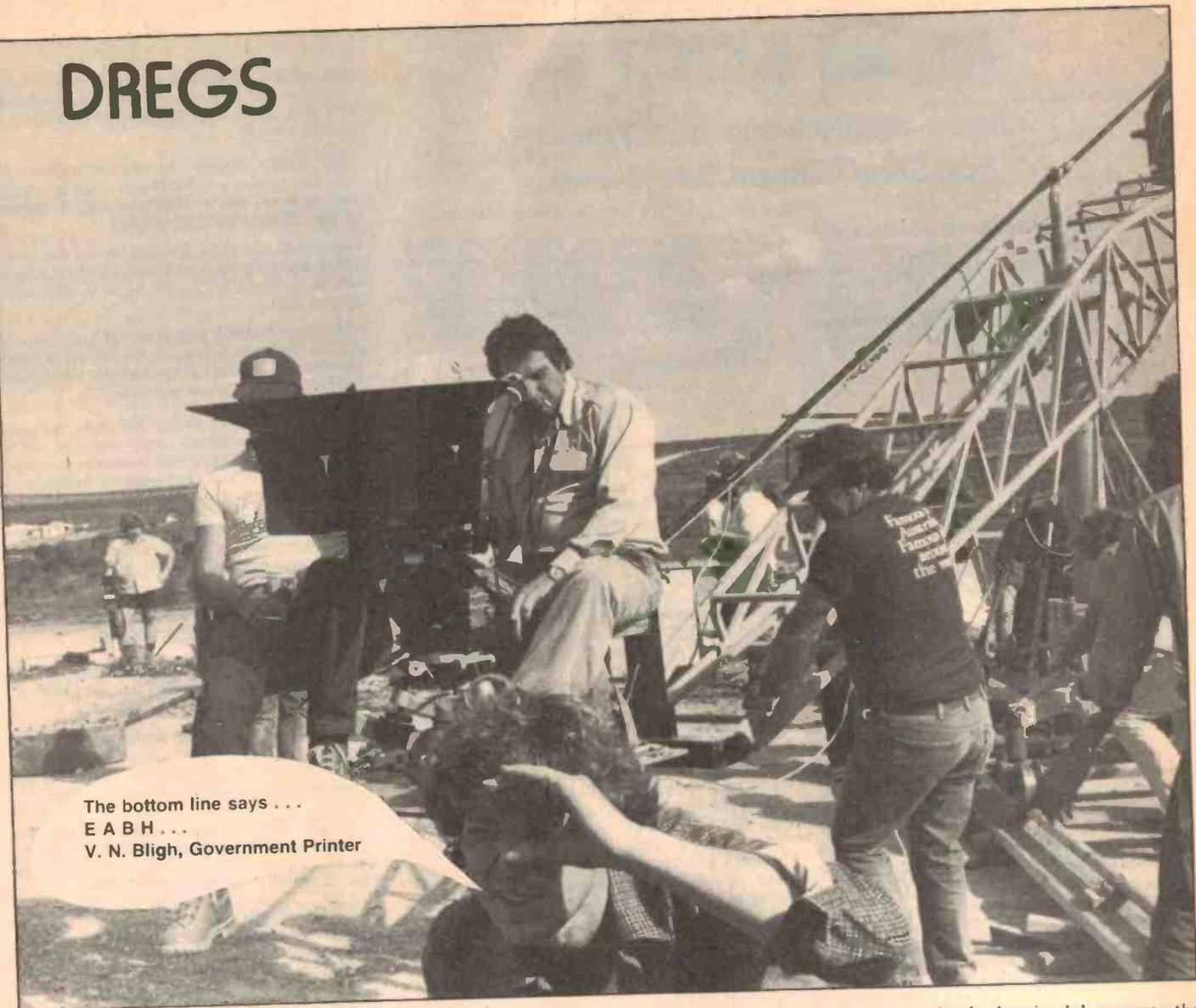

The bottom line says . . .  
E A B H . . .  
V. N. Bligh, Government Printer

I ALWAYS KNEW physics and chemistry couldn't be mixed. Now I'm sure of it. I had to give chemistry away as a high school student after what is best described as 'an unfortunate incident'.

Early on in my high school career I fell in with a bunch of inveterate experimenters. They'd experiment with literally anything they could get their hands on. Lucky I was smaller than my peers, otherwise . . . This, you understand was before we discovered (quick glance over shoulder, say it soto voce) . . . the opposite sex. Those sort of experiments came later.

Anyhow, this bunch, including myself, having satisfied the urge to explore the physics of flattening dry cells (D cells take 7 minutes, 47 seconds, on average) turned to more spectacular, if disruptive, pursuits. Making 'touch powder'. Arranged on the stairs of the school science block before morning assembly was dismissed, it proved a smugly satisfying experience to hear the strains of 'Colonel Bogey' punctuated by assorted loud noises and shrieks of surprise from the first group marched to the classrooms.

That experiment over, we went on to

greater heights; missile propulsion. We knew all about the physics of paper aeroplanes and spit balls. As missiles went, they had their limitations, i.e. they're only effective at close quarters, have very limited range and can almost invariably be traced to the person who launches them.

Rocketry represented the ultimate. So we combined a little chemistry (made solid fuel) and physics (ignited the fuel by an electric spark). Some (clandestine) early experiments met with success, so we made 'the big one'. It was a thing of beauty. The body was hand polished, the nose cone turned and buffed in the machine shop lathe. The ignition system was a masterpiece of electrical engineering (for the technology of the time, you understand).

What with so much preparation, a great many people had come to hear of this 'best thing since Von Braun's V2'. The maiden flight was to be staged from the (then new) football field one afternoon, witnessed by (at a distance) almost the entire school (or so it seemed). Came the countdown, the switch was thrown . . . we had ignition — a loud bang, a blinding flash, a billowing cloud of richly coloured smoke — and small

pieces of rocket body rained down upon the assembled throng who had the temerity to guffaw loudly and make rude, but salient, remarks. Grass still refuses to grow right there, over 20 years later.

We learned our lesson. Chemistry and physics should not be mixed.

It seems others in this world have not learned the same lesson. A respected British medical journal reported recently that the current practice of using nitroglycerine for treating heart conditions should be accompanied by some cautionary practices. Apparently, a 'patch' is attached to the chest and the drug seeps through the skin to effect its work on the heart. However, it was reported that some poor chap who was receiving this treatment, was rushed to hospital suffering from a heart attack. An electric defibrillator was applied — with obvious result and much to the surprise of those administering the treatment. As very little nitroglycerine is used, it's claimed there's little risk and it was reported that not much damage was done, though the patient did not survive his heart attack.

I remain firmly convinced that you can't mix physics and chemistry. ●



CDP-101

COMPACT  
disc  
DIGITAL AUDIO

# Hear digital perfection.

## Introducing the Sony Compact Disc Player.

When we used our long experience in digital technology to create the CDP-101 Compact Disc Player, we wanted to give you something more than the world's clearest sound.

**WIRELESS REMOTE CONTROL** Full-function remote control.

**3-WAY MUSIC SEARCH**  Instant direct access to any selection with the 10-key pad on remote control unit.  AMS (Automatic Music Sensor) allows access to the beginning of next or previous selection.  2-speed bi-directional search to find any desired music passage.

**REPEAT FUNCTION** Program to repeat the entire disc, one selection, or a specific portion of music.

**3-FUNCTION DIGITAL READOUT DISPLAY**  Selection number.  Time lapse of selection being displayed.  Remaining time on the disc.

**LINEAR SKATE DISC LOADING** Just press the button, platter control and cueing are automatic.

Get even more perfect sound with the Sony Digital Audio Component System, "Precise Series".



**SONY**

AUD 0391

# Ladies and gentlemen, be seated. (While you tune your receiver)

The best place to tune your receiver is where you listen to it, sitting down.

And with the new Yamaha R100 you can do exactly that.

Its unique remote control gives you push button command over the R100's Computer Controlled Sound System which allows you to select from five different preset frequency response curves.

And that's in addition to all input functions like phono, video auxiliary, tuner and both tape monitors as well as remote selection of any one of ten preset AM and FM stations.

The tuner itself has Computer Servo Lock Tuning to automatically select the optimum signal, a Dynamic Noise Canceller for exceptionally quiet, noise free reproduction from tape, disc or tuner and a Stereo Spatial Expander to broaden the total stereo sound field.

The new Yamaha R100 is literally the 'state of the art' in stereo receivers, a phrase often used by others but a level of perfection only Yamaha builds to.

And as with all Yamaha audio equipment, the R100 is covered by Yamaha's unique 5 year full parts and labour warranty.

For a free brochure on the remarkable Yamaha R100, see your Yamaha dealer or clip the coupon below.

Post to: Yamaha R100 Receiver Brochure,  
Rose Music Pty. Ltd. 17-33 Market Street,  
South Melbourne, Vic 3205.

Name .....

Address .....

Postcode .....

# YAMAHA

MCR/RM 5155

