



# electronics today

AUGUST 1981 VOL 10 NO 8 INTERNATIONAL

## FEATURES

- |                     |    |                                 |
|---------------------|----|---------------------------------|
| DIGEST              | 11 | News from the electronics world |
| AUDIOPHILE          | 25 | Monogramania                    |
| ASTROLOGUE          | 36 | Inside UOSAT                    |
| THE RECORDING CHAIN | 47 | From vocals to vinyl            |
| SPOT DESIGNS        | 55 | Circuit ideas                   |
| DESIGNER'S NOTEBOOK | 63 | Bootstraps and bistables        |
| TECH TIPS           | 81 | Readers write for us            |

## PROJECTS

- |                      |    |                            |
|----------------------|----|----------------------------|
| HOME SECURITY SYSTEM | 18 | Watch out... with Watchdog |
| HEARTBEAT MONITOR    | 31 | Check you're not dead      |
| SYSTEM A POWER AMP   | 40 | Heavy hi-fi                |
| FLASH SEQUENCER      | 57 | Repeat series              |
| HANDCLAP SYNTHESISER | 68 | Applausible idea           |
| DISCO MIXER          | 76 | Input information          |
| FOIL PATTERNS        | 90 | The collected works of ETI |

## INFORMATION

- |                  |    |                        |
|------------------|----|------------------------|
| CB EXHIBITION    | 12 | Autumn eyeball         |
| NEXT MONTH'S ETI | 15 | We have the technology |
| COME AND JOIN US | 22 | Project yourself       |
| BOOKS            | 60 | Improve your mind      |
| SUBSCRIPTIONS    | 75 | Reserve your ETIs      |
| BINDERS          | 75 | For safe storage       |
| ETI PRINTS       | 84 | The ultimate transfer  |


Disc discussion p.47



Burglars beware p.18



Class A quality p.40

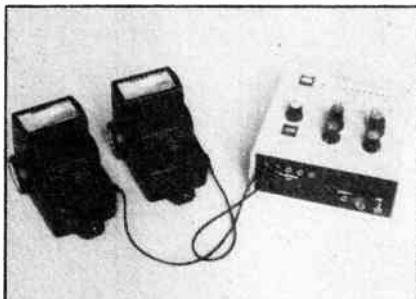

Flashgun fun p.57

ETI AUGUST 1981

### EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.  
Telex 8811896.

Ron Harris B.Sc. Editor  
Paul Wilson-Patterson Group Art Editor  
T.J. Connell Managing Director

Peter Green Assistant Editor  
Tina Boylan Editorial Assistants  
Judith Jacobs

Alison Lilly Assistant Art Editor  
Paul Edwards Drawing Office Manager  
Ray Marston Project Editor  
Steven Rowe Advertisement Manager

OVERSEAS EDITIONS and their EDITORS  
AUSTRALIA — Roger Harrison  
CANADA — Halvor Moorshead  
GERMANY — Udo Wittig  
HOLLAND — Anton Kriegsman



Member of the Audit Bureau of Circulation



PUBLISHED BY Modmags Ltd., 145 Charing Cross Road, London WC2H 0EE  
DISTRIBUTED BY Argus Press Sales & Distribution Ltd. 12-18 Paul Street, London EC2A 4JS (British Isles)  
PRINTED BY QB Limited, Colchester  
COVERS PRINTED BY Alabaster Passmore

Electronics Today is normally published on the first Friday in the month preceding cover date. © MODMAGS LTD 1981: All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. Subscription Rates: UK £11.25 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR46AR.

# MAPLIN make it easy



in  
**SOUTHEND**  
284 London Road  
Westcliff-on-Sea  
Essex  
Tel: (0702) 554000  
(Closed Mondays)



in  
**HAMMERSMITH**  
159-161 King Street  
Hammersmith  
London W6  
Tel: 01-748 0926  
(Closed Mondays)

For personal service visit one of our stores.  
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our  
**CATALOGUE**

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!  
Don't miss out on your copy.

On sale now in all branches  
WH Smith  price £1.

In case of difficulty check the coupon below.

by  
**MAIL ORDER**  
A fast service  
You can rely on

- \* Same day service on in-stock lines
- \* Very large percentage of our stock lines in stock
- \* All prices include VAT
- \* Large range of all the most useful components
- \* First class reply paid envelope with every order
- \* Quality components—no rejects—no re-marks
- \* Competitive prices
- \* Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

## make it easy... with MAPLIN

The  
**Maplin Matinée**  
Amazing value for  
only £299.95 plus £99.50  
for cabinet if required

Easy to build,  
superb specification.  
Comparable with organs selling for  
up to £1,000. For full construction details  
refer to Electronics & Music Maker.



**MAPLIN** ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911

### Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

ET1881



**H**ave you heard about CB? Citizens' Band radio is to be legalised this Autumn; yes, that's right, our very own personal two-way radio system that can be used in the car, the home — anywhere. As you can imagine, CB will be a real boon to the motorist, the housebound, those who go for outdoor activities — and don't forget that CB can save lives!

With all this in mind **Citizens' Band** magazine, the country's leading CB publication, will be holding a **major** CB exhibition in September, timed as closely as possible to coincide with legalisation. If you want to know more about CB, or you are a CBer, come along to the Royal Horticultural Hall on 11th, 12th, 13th September and see Britain's biggest ever CB show.

There will be stands and exhibits from many of the country's leading CB accessory dealers plus, for the first time ever, working examples of the new legal rigs that will be on sale this Autumn. That's right, a number of manufacturers and importers will be on hand to show the new CB equipment that almost anyone can buy and use.

There's something for everyone, CBers old and new. The latest accessories and antennas, gadgets — in fact everything connected with CB including the new equipment.

Come along in September and see what CB can do for you. Even if you've never heard of CB, you soon will, so don't miss out — whether you're a motorist or a small businessman with an eye to the future, CB is for you! CB is the future of two-way communications. . . .



**BRITAIN'S FIRST NATIONAL CB SHOW!** **ROYAL HORTICULTURAL SOCIETY HALL, VINCENT SQUARE, LONDON SW1 (SEPTEMBER 11th-13th INCLUSIVE)**

WHY QUEUE? ORDER YOUR TICKETS NOW FROM:-

Advance Tickets CB81  
Modmags Ltd, 145 Charing Cross Road,  
London WC2H 0EE.

Please send . . . . . tickets @ £2.00  
. . . . . tickets @ £1.00 (OAP or child under 10 yrs)

To .....

.....

.....

I enclose PO/cheque for £ .....

This is the **BIG ONE** for breakers. Whether you're a confirmed fanatic or an interested beginner, this is the place to be in September!

**OPENING TIMES**

Friday 11th Sept 10am-7pm  
Saturday 12th Sept 10am-6pm  
Sunday 13th Sept 10am-4pm

# 20 POWER AMPS


# 19 FUNCTIONAL MODULES

# DAWN

**POWER UP TO 480 WATTS RMS SINGLE CHANNEL**
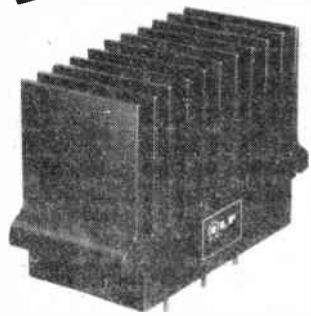
### Which amplifier?

I.L.P. Amplifiers now come in three basic types, each of which is available with or without heatsink. Having decided the system you want – home hi-fi (models HY30, 60 or 120 for example), super quality hi-fi with extra versatility (MOS120, MOS200) or Disco/PA/Guitar (HD120, HD200 or HD400) you will then decide whether amplifiers housed within their own heatsinks or plate amplifiers for bolting to a metal chassis will suit. With choice such as this and a brilliant new range of I.L.P. functional modules to choose from you now have the chance to build the finest audio system ever offered to the constructor.




**AMPLIFIER WITH HEAT SINK**

BIPOLAR Standard, with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts rms	DISTORTION		SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
		T.H.D. Typ at 1kHz	I.M.D. 60Hz/7kHz 4:1											
HY30	15w/4-8Ω	0.015%	<0.006%	±18±20	76x68x40	240	£7.29	£1.09						
HY60	30w/4-8Ω	0.015%	<0.006%	±25±30	76x68x40	240	£8.33	£1.25						
HY120	60w/4-8Ω	0.01%	<0.006%	±35±40	120x78x40	410	£17.48	£2.62	HY120P	120x26x40	215	£15.50	£2.33	
HY200	120w/4-8Ω	0.01%	<0.006%	±45±50	120x78x50	515	£21.21	£3.18	HY200P	120x26x40	215	£18.46	£2.77	
HY400	240w/4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£31.83	£4.77	HY400P	120x26x70	375	£28.33	£4.25	

Protection: Load line, momentary short circuit (typically 10 sec) Slew rate: 15V/μs Rise time: 5μs  
 S/N ratio: 100db Frequency response (-3dB): 15Hz - 50kHz  
 Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400

HEAVY DUTY with heatsinks										Without heatsinks				
HD120	60w/4-8Ω	0.01%	<0.006%	±35±40	120x78x50	515	£22.48	£3.37	HD120P	120x26x50	265	£19.84	£2.98	
HD200	120w/4-8Ω	0.01%	<0.006%	±45±50	120x78x60	620	£27.38	£4.11	HD200P	120x26x50	265	£23.63	£3.54	
HD400	240w/4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£38.63	£5.79	HD400P	120x26x70	375	£34.28	£5.14	

Protection: load line, PERMANENT SHORT CIRCUIT (ideal for disco/group use should evidence of short circuit not be immediately apparent).  
 The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs. as for standard types.

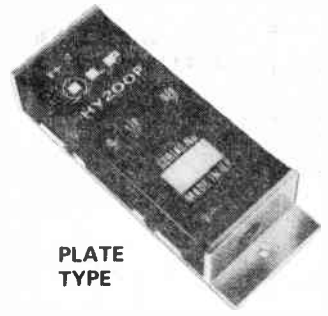

**PLATE TYPE**

MOSFET Ultra-Fi, with heatsinks										Without heatsinks				
MOS120	60w/4-8Ω	<0.005%	<0.006%	±45±50	120x78x40	420	£25.88	£3.88	MOS120P	120x26x40	215	£23.32	£3.50	
MOS200	120w/4-8Ω	<0.005%	<0.006%	±55±60	120x78x80	850	£33.46	£5.02	MOS200P	120x26x80	420	£28.53	£4.28	
MOS400	240w/4Ω	<0.005%	<0.006%	±55±60	120x78x100	1025	£45.39	£6.81	MOS400P	120x26x100	525	£38.91	£5.84	

Protection: Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).  
 Ultra-fi specifications:  
 Slew rate: 20V/μs Rise time: 3μs S/N ratio: 100db Frequency response (-3dB): 15Hz - 100kHz  
 Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400




**PSU**

POWER SUPPLY UNITS			
MODEL NO.	FOR USE WITH	PRICE	VAT
PSU30	± 15V combinations of HY6/66 series to a maximum of 100mA or one HY67 The following will also drive the HY6/66 series except HY67 which requires the PSU30.	£4.50	£0.68
PSU36	1 or 2 HY30	£8.10	£1.22
PSU50	1 or 2 HY60	£10.94	£1.64
PSU60	1 x HY120/HY120P/HD120/HD120P	£13.04	£1.96
PSU65	1 x MOS120/1 x MOS120P	£13.32	£2.00
PSU70	1 or 2 HY120/HY120P/HD120/HD120P	£15.92	£2.39
PSU75	1 or 2 MOS120/MOS120P	£16.20	£2.43
PSU90	1 x HY200/HY200P/HD200/HD200P	£16.20	£2.43
PSU95	1 x MOS200/MOS200P	£16.32	£2.45
PSU180	2 x HY200/HY200P/HD200/HD200P or 1 x HY400/1 x HY400P/HD400/HD400P	£21.34	£3.20
PSU185	1 or 2 MOS200/MOS200P/1 x MOS400/1 x MOS400P	£21.46	£3.22

All models except PSU30 and PSU36 incorporate our own toroidal transformers.

**FP480 BRIDGING UNIT FOR DOUBLING POWER**  
 Designed specially by I.L.P. for use with any two power amplifiers of the same type to double the power output obtained and will function with any I.L.P. power supply. In totally sealed case, size 45 x 50 x 20mm, with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%.  
 Price: £4.79 + 72p. V.A.T.

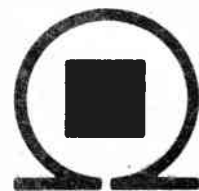

**I.L.P. ELECTRONICS LTD.**

FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.  
 Telephone (0277)54778 (Technical (0227) 64723) Telex 965780

Available also from MARSHALLS, TECHNOMATIC, WATFORD ELECTRONICS and certain other selected retailers.

**GOODS BY MAIL ORDER DESPATCHED WITHIN 7 DAYS**

# OF A NEW ERA



## Which modules?

In launching eighteen different units all within amazingly compact cases to help make complete audio systems using I.L.P. power amplifiers, we bring the most exciting, the most versatile modular assembly scheme ever for constructors of all ages and experience. Study the list – see how these modules will combine to almost any audio project you fancy – and remember *all I.L.P. modules are compatible with each other*, they connect easily. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm. They are so reliable that all I.L.P. modules carry a 5 year no quibble guarantee.



MODEL NO.	MODULE	DESCRIPTION/FACILITIES	CURRENT REQUIRED	PRICE	VAT
HY6	MONO PRE AMP	Mic/Mag. Cartridge/Tuner/Tape/Aux + Volume/Bass/Treble	10mA	£6.44	£0.97
HY7	MONO MIXER	To mix eight signals into one	10mA	£5.15	£0.77
HY8	STEREO MIXER	Two channels, each mixing five signals into one	10mA	£6.25	£0.94
HY9	STEREO PRE AMP	Two channels mag. Cartridge/Mic + Volume	10mA	£6.70	£1.01
HY11	MONO MIXER	To mix five signals into one + Bass/Treble controls	10mA	£7.05	£1.06
*HY12	MONO PRE AMP	To mix two signals into one + Bass/Mid-range/Treble	10mA	£6.70	£1.01
*HY13	MONO VU METER	Programmable gain/LED overload driver	10mA	£5.95	£0.89
HY66	STEREO PRE AMP	Mic/Mag. Cartridge/Tape/Tuner/Aux + Volume/Bass/Treble/Balance	20mA	£12.19	£1.83
HY67	STEREO HEADPHONE	Will drive headphones in the range of 4Ω – 2KΩ	80mA	£12.35	£1.85
HY68	STEREO MIXER	Two channels, each mixing ten signals into one	20mA	£7.95	£1.19
HY69	MONO PRE AMP	Two input channels of mag. Cartridge/Mic + Mixing/Volume/Treble/Bass	20mA	£10.45	£1.57
HY71	DUAL STEREO PRE AMP	Four channels of mag. Cartridge/Mic + Volume	20mA	£10.75	£1.61
*HY72	VOICE OPERATED STEREO FADER	Depth/Delay	20mA	To be announced	
*HY73	GUITAR PRE AMP	Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix	20mA	£12.25	£1.84
†HY74	STEREO MIXER	Two channels, each mixing five signals into one + Treble/Bass	20mA	£11.45	£1.72
†HY75	STEREO PRE AMP	Two channels, each mixing two signals into one + Bass/Mid-range/Treble	20mA	£10.75	£1.61
†HY76	STEREO SWITCH MATRIX	Two channels, each switching one of four signals into one	20mA	To be announced	
†HY77	STEREO VU METER DRIVER	Programmable gain/LED overload driver	20mA	£9.25	£1.39

The modules are encapsulated and include latest design high quality clip-on edge connectors.

For easy mounting we recommend B6 Mounting board for modules HY6 – HY13 78p + 12p. V.A.T.

B66 Mounting board for HY66 – HY77 99p + 13p. V.A.T.

All I.L.P. modules include full connection data.

**I.L.P. Products are of British Design and Manufacture.**

\* Ready August – may be ordered now  
† Ready September – may be ordered now

All the above modules operate from ±15V minimum to ±30V maximum – higher voltages being accommodated by use of dropper resistors. HY67 can only be used with the PSU 30 power supply unit.

See our advertisement on page 87

## TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. If sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order. When ordering, U.K. customers must include the appropriate V.A.T. as shown.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED.

## ALL WITH I.L.P.'S 5 YEAR NO QUIBBLE GUARANTEE

To: I.L.P. ELECTRONICS LTD. ROPER CLOSE CANTERBURY CT2 7EP

Please supply .....

..... Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No .....

NAME .....

ADDRESS .....

Signature .....

4/8

ALL U.K. ORDERS DESPATCHED POST FREE

# OF RECEIVING YOUR ORDER

## HOW IT WORKS

The circuitry of the main unit can be broken down into two distinct sections, with the basic alarm circuitry plus alarm recorder to the right of key switch SW1a, and the burglary-detection circuitry to the left. The circuitry to the right of SW1a is permanently enabled and can be activated at any time by the panic and fire inputs: the burglary-detection circuitry is active only when the system is turned fully on by SW1.

The operation of the basic alarm circuitry and the alarm recorder is fairly simple. IC2a-IC2b is a long-period monostable (several minutes) and can be triggered by applying a high (logic 1) signal to R13 via the D2-D3 OR gate; the mono can thus be triggered by closing any of the fire-detecting thermostats or the panic buttons, or by a high output from IC1d. When the mono is triggered, the output of IC2b goes high for the duration of the monostable period and thus drives RLA (and the external alarm) on via Q1 for a preset period. Simultaneously, the output of IC2a goes low and causes special-purpose bistable IC2c-IC2d to self-latch into a state in which the output of IC2d goes low, driving LED6 (the visual alarm recorder) on and activating the IC3-IC4 audible alarm recorder circuitry. When the monostable turns off at the end of its timed period the external alarm also turns off, but the audio-visual alarm recorder remains active, giving a permanent indication that an alarm action has occurred. The monostable and the recorder can both be reset by briefly moving SW1 to the reset position.

The audible alarm recorder circuitry is quite simple. IC3a-IC3b form a low-frequency astable, which is gated on by a low input signal. IC3c-IC3d form a high-frequency astable (a couple of kilohertz) which is gated by the output of IC3b. The output of the high-frequency astable is fed to acoustic transducer TX1 via bridge-configured driver IC4. Thus, when the circuitry is activated by a low input signal, an audible pulsed-tone signal is generated by TX1.

The burglary-detection circuitry is designed around IC1 and is active only when SW1 is switched to the on position. Here, the N.O. and N.C. burglar-detecting security switches are wired in such a way that a high voltage is normally applied to R3, but this voltage goes low if any of the N.C. switches are opened or the N.O.

switches are closed. The R3 voltage is inverted by both IC1a and IC1b, so that LED2 turns on and a high voltage is fed to one input of IC1c if an intrusion occurs; C1 and R5-C2 filter the signals from R3, to eliminate the effects of lightning-induced signals and transients. The other input of IC1c is controlled by the C3-R7 time-controlled network, which causes IC1c to be effectively disabled for a minute or so after SW1 is first moved to the on position or after the optional re-entry switch is momentarily closed. The output of IC1c is inverted by IC1d and fed to the D2 input of the D2-D3 OR gate, where it can control the action of the main alarm circuitry.

Thus, when the burglar alarm circuit is first switched on by SW1 the IC1a-IC1b section is fully enabled, so that LED2 will turn on if any of the security switches are incorrectly set, but IC1c-IC1d are disabled by the C3-R7 network, so that the main alarm will not activate under this condition. After a minute or so, however, the IC1c-IC1d section becomes fully enabled, so the main alarm will sound instantly if any subsequent intrusion is detected.

Note that the main Watchdog unit is powered by a single PP9-style Ni-Cd battery, which is intended to be permanently trickle-charged by an external mains-powered charger circuit. Also note that the circuit is provided with a total of seven LEDs, which give visual indications of the existing operating mode, the presence of sensor faults/actions, the presence of the charger current, and the record of an alarm action.

The charger circuit is very simple and is intended to apply a permanent trickle-charge current of roughly 70 mA to the Ni-Cd battery of the main Watchdog unit. Here, the mains voltage is stepped down, full wave rectified and smoothed by T1-D9-D10-C8, to provide roughly 13 V DC across C8. This voltage is used to power the constant-current generator that is designed around ZD1-R26-Q2-R27. ZD1 sets a standing voltage across emitter resistor R27, which thus determines the emitter current of Q2: since the emitter and collector currents of an active transistor are virtually identical, the collector of Q2 effectively acts as a constant-current source and is used to feed a trickle-charge current to the Watchdog Ni-Cd via D8. LED7 (in the main unit) illuminates when the charger is active.

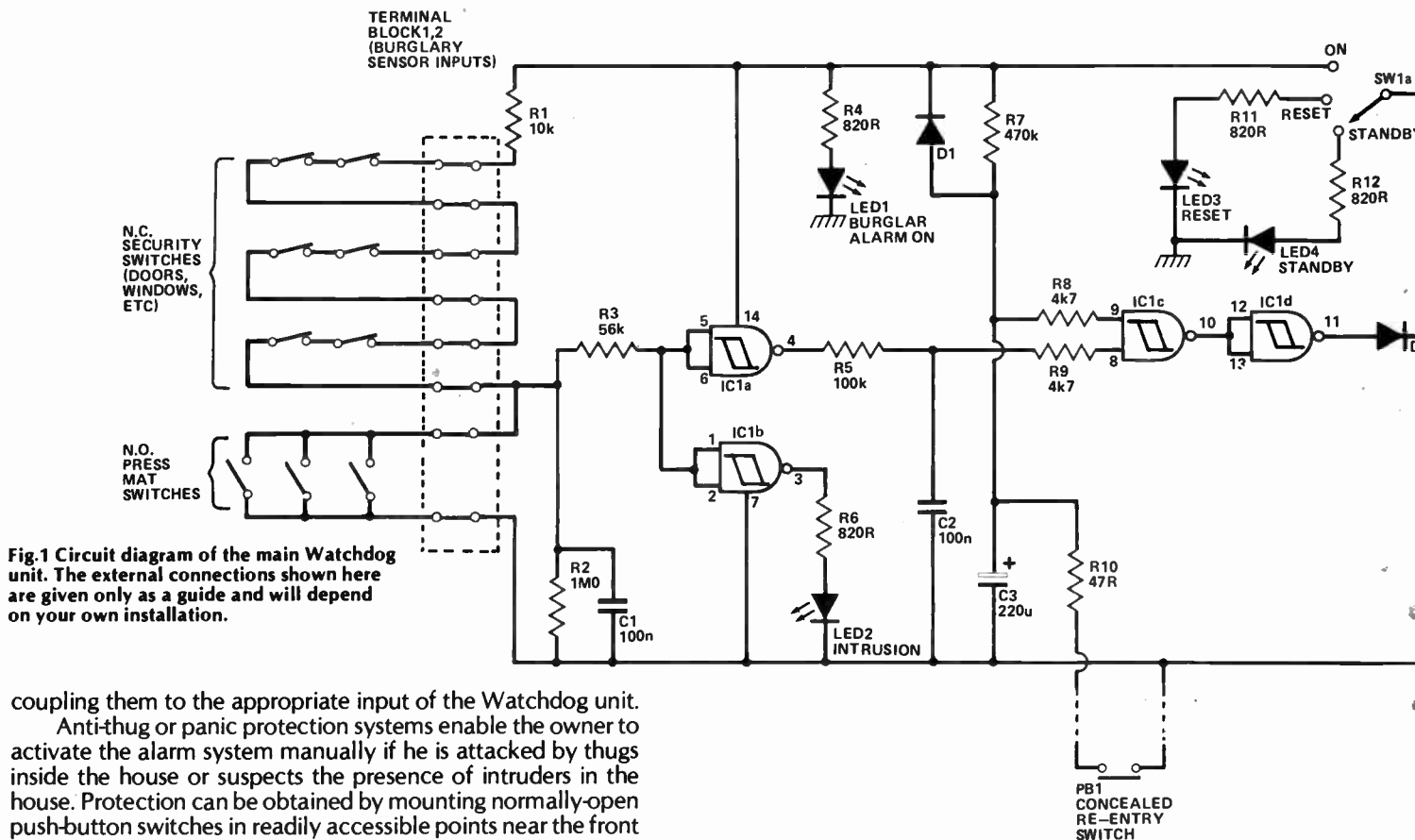


Fig.1 Circuit diagram of the main Watchdog unit. The external connections shown here are given only as a guide and will depend on your own installation.

coupling them to the appropriate input of the Watchdog unit.

Anti-thug or panic protection systems enable the owner to activate the alarm system manually if he is attacked by thugs inside the house or suspects the presence of intruders in the house. Protection can be obtained by mounting normally-open push-button switches in readily accessible points near the front and rear doors and in the lounge and bedrooms and then wiring all of the switches in parallel and coupling them to the Watchdog unit.



complete with its own power supply arrangement, can then be coupled to the output of the unit so that it activates when relay RLA closes.

If you decide to mount a re-entry switch on the front door of the house (so that you can enter the building without activating the alarm), take care to conceal its wiring. If required, a number of re-entry switches can be wired in parallel so that, for example, the system can be temporarily disabled from either the front door or the main bedroom.

The alarm system is very simple to use. The panic and fire alarm side of the circuit is permanently enabled and can be operated at any time. The anti-burglar section is enabled only when the main key switch is set to the on position. If LED2 lights at the moment of turn-on it means that part of the burglary sensor system is either open or closed when it should not be, possibly due to an open door or a chair resting on a pressure mat, for example. The fault must be rectified before the system is put to full use.

If you leave the house or pass through a protected area after turning the system on, remember to use the re-entry facility before returning to the unit, or you'll sound the alarm and annoy the neighbours.



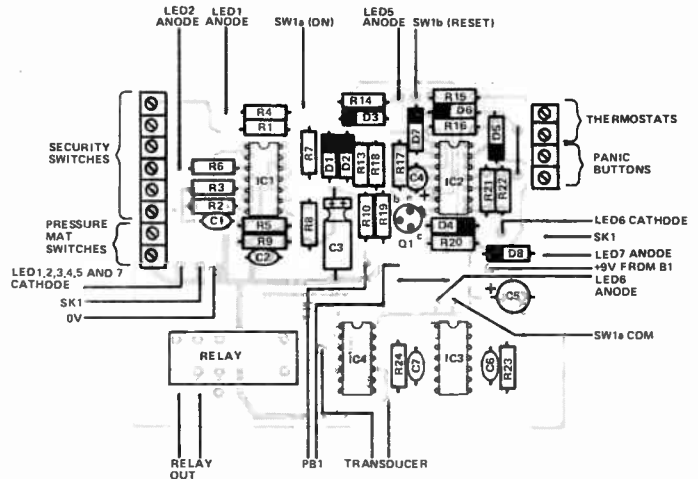


Fig.3 Overlay for the main board. Note that R11,12 and 25 are mounted off-board.

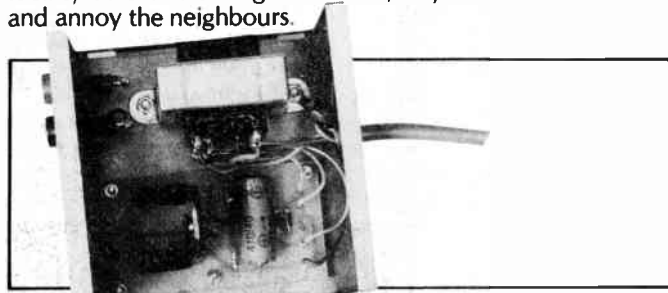

## PARTS LIST

<b>Resistors (all 1/4 W, 5%)</b>	
R1,13,18,19	10k
R2,23	1M0
R3	56k
R4,6,11,12,14	820R
R5	100k
R7	470k
R8,9	4k7
R10	47R
R15	4M7
R16,24	22k
R17,22,25	1k0
R20	18R
R21	12k
R26	2k2
R27	22R
<b>Capacitors</b>	
C1,2	100n ceramic
C3	220u 16 V axial electrolytic
C4	100u 10 V tantalum
C5	100u 16 V electrolytic (PCB type)
C6	220n polycarbonate
C7	10n polycarbonate
C8	470 40 V axial electrolytic
<b>Semiconductors</b>	
IC1	4093B
IC2,3	4001B
IC4	4011B
Q1	BC109
Q2	TIP32A
D1,4,8,9,10	1N4001
D2,3,5,6,7	1N4148
ZD1	BZY88 2V7
LED1,4,7	0.125" green LED
LED2,3,5,6	0.125" red LED
<b>Miscellaneous</b>	
T1	9-0-9 @ 75 mA
SW1	two-pole six-way wafer key switch
SK1	DC socket and plug
SK2,3	4 mm sockets (and plugs)
TX1	piezo-electric transducer
RLA	6 V DPCO, PCB-mounting
PCB-mounting terminal blocks; Verocase (order code 202-21031G); case for charger unit (order code Samos 002).	

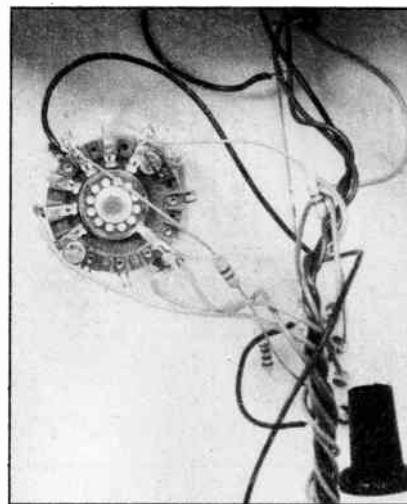

Details of the keyswitch wiring. The off-board resistors can also be seen.

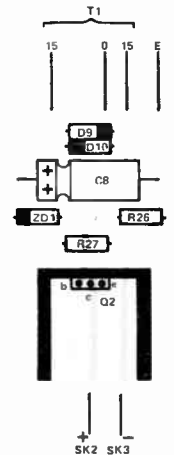


Fig.4 The charger overlay.

ETI

## electronics today

ELECTRONICS TODAY INTERNATIONAL, Britain's leading electronics monthly, is seeking to expand its workshop facility and a vacancy now exists for a

### PROJECT EDITOR

The successful applicant will be expected to be able to design and build a variety of electronic projects for the home constructor. In addition he will write up the design as an article for the magazine (this is the easiest part of the job and training will be provided if necessary!).

A thorough knowledge of circuit design is considered essential, as is the ability to maintain the magazine's high standards of constructional quality.

We are flexible as to age and experience, but would imagine that the most likely candidate will be in his twenties or thirties and already employed as an engineer/technician within the electronics industry.

Salary is fully negotiable and is dependent upon background. Write, in the first instance, enclosing C.V. to:

Ron Harris, Managing Editor  
Modmags Ltd  
145 Charing Cross Road  
London WC2H 0EE



Publishers of: Electronics Today International, Hobby Electronics  
Computing Today, Video Today  
145 Charing Cross Road, London WC2H 0EE. Tel. 01-437 1002

ETI AUGUST 1981



# MICROCOMPUTER COMPONENTS

LOWEST PRICES

FASTEST DELIVERY

DEVICE	PRICE	DEVICE	PRICE	DEVICE	PRICE
<b>CPU's</b>		74LS15	0.15	74LS377	0.97
6502	5.50	74LS20	0.13	74LS378	0.73
6800	3.82	74LS21	0.15	74LS379	0.56
6802	5.74	74LS22	0.15	74LS386	0.29
6803	14.53	74LS26	0.19	74LS390	0.68
6809	12.00	74LS27	0.15	74LS393	0.61
8085A	8.02	74LS28	0.17	<b>CMOS</b>	
Z80 CPU	4.00	74LS30	0.14	4000	0.12
Z80A	5.92	74LS32	0.14	4001	0.12
<b>SUPPORT CHIPS</b>		74LS33	0.17	4002	0.12
6520	3.15	74LS37	0.17	4006	0.69
6522	5.60	74LS38	0.17	4007	0.14
6532	7.75	74LS40	0.14	4008	0.61
6821	1.93	74LS42	0.40	4009	0.31
6840	5.87	74LS47	0.42	4010	0.37
68488P	9.38	74LS48	0.70	4011	0.13
6850	1.95	74LS49	0.62	4012	0.19
6862	7.09	74LS51	0.14	4013	0.34
6871A1T	20.90	74LS54	0.15	4014	0.62
6875P	4.16	74LS55	0.15	4015	0.64
6880	1.07	74LS73	0.22	4016	0.28
6887	0.80	74LS74	0.18	4017	0.54
8212	1.95	74LS75	0.30	4018	0.59
8216	1.95	74LS76	0.22	4019	0.36
8224	2.50	74LS78	0.25	4020	0.66
8228	4.20	74LS83	0.54	4021	0.70
8251	4.75	74LS85	0.77	4022	0.68
8253	9.90	74LS86	0.18	4023	0.19
8255	4.20	74LS90	0.36	4024	0.39
Z80 CTC	4.00	74LS91	0.81	4025	0.15
Z80A CTC	4.90	74LS92	0.40	4026	1.12
Z80 DMA	14.97	74LS93	0.39	4027	0.36
Z80A DMA	11.52	74LS95	0.48	4028	0.64
Z80 DART	7.20	74LS109	0.26	4031	1.55
Z80A DART	7.67	74LS112	0.26	4033	1.30
Z80 PIO	4.00	74LS113	0.26	4034	1.60
Z80A PIO	4.40	74LS114	0.26	4035	0.85
Z80 SIO-0	17.90	74LS122	0.45	4036	2.25
Z80 SIO-1	17.90	74LS123	0.57	4039	2.45
Z80 SIO-2	17.90	74LS124	1.07	4040	0.67
Z80A SIO-0	22.90	74LS125	0.29	4041	0.70
Z80A SIO-1	22.90	74LS126	0.29	4042	0.56
Z80A SIO-2	22.90	74LS132	0.51	4043	0.62
<b>MEMORIES</b>		74LS136	0.29	4044	0.62
2101	3.68	74LS138	0.40	4045	1.30
2114 200ns	2.54	74LS139	0.40	4046	0.75
Low power	1.35	74LS145	0.78	4047	0.78
2708	1.73	74LS148	1.13	4048	0.44
2716 (5v)	2.67	74LS151	0.35	4049	0.28
2732 or 2532	7.59	74LS153	0.35	4050	0.27
4116 150ns	1.25	74LS155	0.50	4051	0.62
4116 200ns	1.20	74LS156	0.50	4052	0.62
6810P	1.43	74LS157	0.36	4053	0.62
<b>REGULATORS</b>		74LS158	0.40	4054	1.02
7805	0.55	74LS160	0.43	4055	1.00
7812	0.55	74LS161	0.43	4060	0.88
7905	0.65	74LS162	0.43	4063	0.94
7912	0.65	74LS163	0.43	4066	0.38
<b>CRT CONTROLLERS</b>		74LS164	0.51	4067	0.22
9364AP	8.64	74LS166	0.37	4068	0.21
6845	11.72	74LS173	0.77	4069	0.15
<b>BUFFERS</b>		74LS174	0.78	4070	0.23
81LS95	1.20	74LS175	0.60	4071	0.20
81LS96	1.25	74LS181	1.50	4072	0.20
81LS97	1.20	74LS190	0.61	4073	0.20
81LS98	1.25	74LS191	0.61	4075	0.20
8T26A	1.50	74LS192	0.69	4076	0.67
8T28A	1.50	74LS193	0.69	4077	0.23
8T95N	1.50	74LS194	0.42	4078	0.20
8T97N	1.50	74LS195	0.42	4081	0.20
8T98	1.50	74LS196	0.68	4082	0.20
<b>MISC. SUPPORT CHIPS</b>		74LS197	0.68	4085	0.45
AY-3-1015 or	3.49	74LS221	0.64	4086	0.56
AY-5-1013 equiva-	3.19	74LS240	1.01	4093	0.43
AY-5-2376 lent	7.00	74LS241	1.15	4502	0.80
MC1488	0.75	74LS242	0.85	4507	0.37
MC1489	0.75	74LS243	0.85	4508	2.25
MC14411	6.99	74LS244	0.84	4510	0.67
MC14412	7.99	74LS245	1.21	4511	0.51
<b>DATA CONVERTERS</b>		74LS247	0.41	4512	0.63
ZN425E	3.50	74LS248	0.74	4514	1.53
ZN426E	3.00	74LS249	0.74	4515	2.38
ZN427E	6.28	74LS251	0.46	4516	0.72
ZN428E	4.78	74LS253	0.46	4518	0.72
ZN429E	2.10	74LS257	0.57	4519	0.56
ZN432	28.09	74LS258	0.40	4520	0.71
ZN433	22.59	74LS259	1.15	4521	1.65
Data Converter		74LS261	3.12	4522	1.15
Handbook	1.00	74LS266	0.25	4526	0.75
<b>74LS SERIES</b>		74LS273	0.97	4527	1.00
74LS00	0.11	74LS279	0.37	4528	0.79
74LS01	0.15	74LS283	0.45	4532	0.90
74LS02	0.14	74LS290	0.60	4541	1.15
74LS03	0.14	74LS293	0.53	4543	1.15
74LS04	0.13	74LS365	0.39	4553	2.50
74LS05	0.15	74LS366	0.38	4555	0.40
74LS08	0.14	74LS367	0.38	4556	0.47
74LS09	0.15	74LS368	0.38	4585	1.05
74LS10	0.13	74LS373	0.79	<b>CRYSTALS</b>	
74LS11	0.15	74LS374	0.79	4 MHz	1.80
74LS12	0.15	74LS375	0.50	<b>E.&amp;O.E.</b>	
74LS13	0.29				
74LS14	0.51				

DIL SOCKETS  
Pins  
Price

8 14 16 18 20 22 24 28 40  
7 8 9 14 16 18 20 24 32

OFFICIAL ORDERS WELCOME  
MIDWICH COMPUTER CO. LTD.  
(Dept. ETI)  
Hewitt House, Northgate Street  
Bury St. Edmunds, Suffolk IP33 1HQ  
Telephone: (0284) 701321

QUANTITY DISCOUNTS AVAILABLE  
All prices exclude post and packing on  
order under £10 (50p) and VAT (15%).  
ALL ORDERS DESPATCHED ON DAY  
OF RECEIPT WITH FULL REFUND FOR  
OUT OF STOCK ITEMS  
24-hour Telephone Credit Card Orders  
Telephone: (0284) 701321

CREDIT CARD ORDERS WELCOME

TTL	LS TTL	CMOS-B	MEMORIES	TRANSISTORS					
7400	11p	LS00	13p	4001	14p	2102	95p	AC127	25p
7402	11p	LS01	13p	4002	15p	2112	250p	AC128	25p
7403	14p	LS02	15p	4006	80p	2114-3	195p	BC107	10p
7404	14p	LS03	15p	4011	17p	2114L-3	195p	BC109	10p
7407	30p	LS04	15p	4012	18p	4116-3	210p	BC147	9p
7410	14p	LS05	22p	4013	40p	2708	350p	BC148	9p
7413	30p	LS10	18p	4016	32p	2716SVI	450p	BC157	9p
7414	35p	LS12	20p	4017	66p			BC158	9p
7416	25p	LS13	38p	4019	41p	<b>REGULATORS</b>		BC184	9p
7420	15p	LS14	48p	4021	88p	<b>TO-220</b>		BC214	9p
7426	35p	LS20	18p	4022	84p	7805	55p	BD131	40p
7430	16p	LS26	26p	4023	20p	7812	60p	BD132	40p
7441	64p	LS30	20p	4024	48p	7815	60p	BF194	10p
7442A	64p	LS42	64p	4025	20p	7905	60p	BF195	10p
7445	95p	LS47	72p	4027	90p	7912	60p	BF197	10p
7446	90p	LS51	22p	4029	40p	7915	65p	BF259	32p
7447A	48p	LS54	22p	4040	84p			BF337	30p
7451	16p	LS73	44p	4046	96p	<b>LINEAR</b>		BU205	120p
7454	16p	LS74	27p	4049	32p	CA3130	90p	BU208	150p
7473	26p	LS75	44p	4050	32p	LM301A	27p	TIP31A	40p
7474	27p	LS85	75p	4051	69p	LM311	70p	TIP32A	40p
7475	38p	LS86	36p	4052	68p	LM380	80p	TIP42A	52p
7485	100p	LS90	38p	4053	68p	LM381A	160p	2N3055	44p
7486	30p	LS92	64p	4054	130p	741C-8	18p		
7490A	30p	LS93	57p	4055	110p	NE555	22p		
7492A	40p	LS95	110p	4060	110p	NE556	60p		
7493A	30p	LS96	110p	4069	20p	TBA800	90p		
7495	65p	LS107	44p	4070	22p	TBA810S	95p		
7496	64p	LS109	64p	4071	22p	TBA820S	85p		
74107	32p	LS122	70p	4072	22p			<b>DIODES &amp; BRIDGES</b>	
74109	44p	LS123	60p	4075	25p			1N514	4p
74121	44p	LS125	44p	4076	84p	<b>LEDS</b>		1N4001	6p
74122	45p	LS126	44p	4081	25p	Green, Red		1N4002	6p
74123	48p	LS132	60p	4082	25p	SMALL	12p	1N4004	6p
74125	50p	LS151	55p	4089	150p	LARGE	15p	1N4006	7p
74126	50p	LS153	55p	4093	54p			1N5401	14p
74132	50p	LS156	80p	4502	99p			1N5404	18p
74141	48p	LS157	55p	4503	64p	<b>OIL SOCKETS</b>		1N5407	24p
74142	200p	LS160	85p	4511	90p	8 pin	8p	W05	26p
74143	250p	LS161	85p	4517	450p	14 pin	9p	W01	30p
74151A	55p	LS162	90p	4518	88p	16 pin	10p	W04	36p
74152	65p	LS163	90p	4520	88p	18 pin	16p		
74157	65p	LS164	90p	4543	140p	20 pin	18p	<b>OPTO</b>	
74160	75p	LS168	90p	4555	70p	22 pin	22p	DL704	95p
74161	75p	LS169	200p	4556	70p	24 pin	20p	DL747	150p
74162	90p	LS174	99p			28 pin			

# Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD.  
KINGSGATE HOUSE  
KINGSGATE PLACE  
LONDON NW8 4TA.  
MAIL ORDER 01 424 8582 24HR SERVICE  
INDUSTRIAL SALES 01-328 1009

ALSO RETAIL SHOPS AT  
325 EDGWARE ROAD, LONDON NW2 0JZ 4242  
40 CRICKLEWOOD BDY., LONDON NW2 0JZ 4242  
108A STOKES CROFT, BRISTOL, 0272 428801  
86 WEST REGENT STREET, GLASGOW, 041-332 4133

WE TAKE ACCESS - AMERICAN EXPRESS - BARCLAYCARD CARD - DINERS

PLEASE ADD POSTAGE/PACKING 60p UNLESS STATED  
ALSO 15% VAT ON TOTAL - ALL ITEMS ON THIS  
ADVERTISEMENT SPECIALLY SELECTED FOR EX-STOCK  
DELIVERY. WATCH FOR SPECIAL REDUCTIONS ON  
STARRED ITEMS

## RECHARGEABLE NICKEL CADMIUM BATTERIES & CHARGERS

TYPE	VOLTS	AV. CAP.	PRICE
S101 (HP7)	1.25	0.5AH	£0.98
Sub C (HP11)	1.25	1.2AH	£1.75
Sub D (HP2)	1.25	1.2AH	£1.95
S104 (HP11)	1.25	1.8AH	£2.00
S103 (HP2)	1.25	4.0AH	£3.75
Penlight 4 Charger for 1-4 HP7			£5.25
Combibox FW611 Charger for HP7, HP11, HP2			£13.25
Combibox FW610 Charger for HP7, HP11, HP2			£19.95

## CAPACITORS

SIEMENS LAYER B32560 7mm				SIEMENS LAYER B32561 10mm				SIEMENS ELECTROLYTIC AXIAL			
001 to 015400v	0.08	01 - 022/400v	0.08	47 100	13	22/40	16	47 100	13	22/40	16
002 to 027/250v	0.08	033 400v	0.09	10/53	16	22/53	18	10/100	18	22/100	20
003 to 1/250v	0.10	022/250v	0.08	10/100	18	22/100	20	47/25	26	47/40	19
015/250	0.12	068/250v	0.10	47 50	20	47/100	24	100/25	20	100/40	19
022/250	0.14	22/250v	0.16	100/25	20	100/40	19	220/16	19	220/25	22
01/100	0.12	22/100v	0.18	220/40	24	220/63	27	100/63	21	100/100	44
022/100	0.45	68/100v	0.30	220/100	51	470/15	23	1000/40	75	1000/25	60
047/100	0.26	0.68/100	0.34	470/40	47	470/63	72	2200/18	50	2200/25	95
				2200/40	123	4700/15	23	4700/25	150	4700/16	120

MANY OTHER RANGES CAPACITORS INCLUDE MULLARD C280  
MULLARD/SIEMENS CERAMIC, SIEMENS 841070 RADIAL.  
HIGH VOLTAGE DISC CERAMIC, ETC.

## LINEAR INTEGRATED CIRCUITS

LF 1331N	2.70	SAA 5000	3.04
LF 13741H	2.70	SAA 5010	7.11
LM 301-8	0.26	SAA 5012	7.11
LM 308N	0.48	SAA 5020	5.33
LM 348	0.90	SAA 5030	8.26
LM 380 N14	0.50	SAA 5040	15.14
LM 383	1.56	SAA 5050	8.51
LM 386N	0.75	SAS 560	1.60
LM 389N	0.92	SAS 570	1.60
LM 340T5	0.50	SAS 580	1.80
LM 710-14	0.42	SAS 590	1.80
LM 723 CH	0.60	SFF 96800A	6.25
LM 723 C14	0.40	SFF 96810A	4.28
LM 741 C14	0.58	SFF 96821A	5.19
LM 923	0.44	SN 76115	0.70
LM 1303	1.00	SN 76228	1.00
LM 1458	0.40	SN 76116	1.25
LM 1801	2.04	SN 76666	0.70
LM 1871	1.95	TAA 263	1.00
LM 1872	1.95	TAA 521	0.75
LM 3900	0.50	TAA 621	2.49
LM 3909	0.67	TAA 700	1.50
LM 3914	2.20	TAD 100	1.55
LM 3915	2.20	T8A 120	0.75
LM 4250	1.42	T8A 500	0.45
NE 531	0.95	T8A 550	3.50
NE 543K	1.55	T8A 570Q	2.20
NE 544	1.60	T8A 810S	1.00
NE 555	0.21	T8A 920	2.75
NE 556	0.73	T8A 990Q	2.65
NE 558	3.12	TCA 270S	3.15
NE 562	3.12	TDA 2540	3.85
NE 565	1.05	TDA 2611	1.58
NE 566	1.53	TLO 81CP	0.32
NE 567	1.10	TLO 82CP	0.56
NE 570	3.50	TLO 84CN	1.00

## SINCLAIR INSTRUMENTS

Digital Multimeter		p/p	
" " PDM35	£34.50	£0.60	
" " DM235	£52.50	£1.30	
" " DM350	£72.50	£1.30	
" " DM450	£119.00	£1.30	
Digital Frequency Meter			
PFM200	£49.80	£0.60	
Low Power Oscilloscope			
SC110	£139.00	£1.30	
TF200 Frequency Meter	£145.00	£1.30	
TGF 105 Pulse Generator	£85.00	£1.30	
NEW			
LCD Multimeter TM353	£84.00	£1.30	
LCD Multimeter TM351	£99.00	£2.50	
LCD Multimeter TM352	£49.95	£1.30	
Prescaler TP600	£37.50	£0.60	

## LEADER INSTRUMENTS

Just a selection			
Singletrace Oscilloscope 510A 5"	£127.00	£3.00	
Doubletrace Oscilloscope 308S 3"	£419.00	£2.50	
Coubletrace Oscilloscope 508A 5"	£299.00	£3.00	
LSG 16 Sig. Gen. TV/Radio	£55.00	£2.00	
LDM 815 Dip Meter	£45.00	£1.00	

## CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09	
CE 1004	Power Amp	£23.43	
CE 1003	Power Amp	£26.30	
CE 1704	Power Amp	£33.48	
CE 1708	Power Amp	£33.48	
CPS 1	Power Unit	£19.52	
CPS 3	Power Unit	£23.52	
CPS 6	Power Unit	£30.00	
CPR 1	Pre Amp	£32.17	
CPR 1S	Pre Amp	£42.52	

U.K. Postage and Packing + 10%

## TRANSISTORS/DIODES STOCK CLEARANCE

2N 697	.10	AD 161	.25	8C 184L	.05	8F 195	.10
2N 914	.10	AF 106	.10	8C 212A	.05	8F 196	.10
2N 929	.05	AF 109	.10	8C 2138	.05	8F 199	.05
2N 3133	.10	AF 126	.10	8C 213L	.05	8S Y 28	.10
2N 3566	.50	8C 115	.05	8C 214	.05	MJE 371	.30
2N 3638	.05	8C 118	.05	8C 2148	.05	MPSA 05	.05
2N 3642	.10	8C 154	.10	8C 214L	.05	2TX 500	.05
2N 3708	.05	8C 157A	.05	8C 2388	.05	AA 119	.05
2N 3711	.05	8C 157B	.05	8C 239C	.05	8A 102	.05
2N 3794	.05	8C 158	.05	8C 2518	.05	8A 142	.05
2N 3771	.75	8C 159	.05	8C 253	.08	8A 144	.05
2N 3905	.08	8C 1678	.05	8C 3088	.08	8A 154	.05
2N 3962	.10	8C 1688	.05	8C 350	.05	8A 316	.05
2N 4286	.05	8C 1698	.05	8C 347	.05	8A 317	.05
2N 4400	.05	8C 1708	.05	8C 414	.05	8A 318	.05
2N 5220	.05	8C 1718	.05	8C 415A	.05	8AW 49	.05
2N 5222	.10	8C 172	.06	8C 416A	.05	8AX 13	.05
AC 126	.15	8C 172C	.06	8C 517	.12	8AY 93	.02
AC 127	.15	8C 173	.05	8CY 71	.05	8B 1058	.10
AC 132	.05	8C 1748	.05	8CY 72	.09	8Y 126	.14
AC 152	.15	8C 1788	.14	8D 138	.10	CV 7641	.05
AC 188	.15	8C 182A	.05	8F 161	.08	GEX 23A	.03
AC 188K	.15	8C 183	.05	8F 177	.05	ITT 44	.05
AC 187K	.15	8C 1838	.06	8F 180	.08	ITT 921	.05
ACY 22	.05	8C 183L	.05	8F 181	.05	OA 47	.10
ACY 30	.05	8C 183 LA	.05	8F 194	.05	OA 90	.05

## ILP HI FI MODULES

Power Amplifiers		Pre Amplifiers	
HY30	£7.29	HY6	£6.44
HY60	£8.33	HY66	£12.19
HY120	£17.48	Power Supplies	
HY200	£21.21	PSU30	£4.50
HY400	£31.83	PSU36	£8.10
MOS120	£25.88	PSU60	£13.04
MOS200	£33.46	PSU70	£15.92
		PSU180	£21.34

Postage & Packing to U.K. included.

CD4000	£0.17	CD40138	£0.44	CD40248	£0.60	CD4049	£0.33	CD4069	£0.14	CD4095	£1.00
CD40018	£0.20	CD4014	£0.72	CD40288	£0.60	CD40508	£0.33	CD40718	£0.16	CD4096	£1.00
CD4002	£0.20	CD4015	£0.72	CD40298	£1.05	CD40518	£0.70	CD4072	£0.20	CD40998	£1.40
CD4007	£0.20	CD4016	£0.36	CD40348	£2.20	CD40528	£0.70	CD40738	£0.16	CD4507	£0.44
CD40088	£0.74	CD40178	£0.70	CD40358	£1.05	CD40608	£1.10	CD40758	£0.16	CD45108	£0.90
CD4009	£0.40	CD40188	£0.75	CD4040	£0.90	CD4063	£1.10	CD40818	£0.16	CD4511	£1.02
CD4010	£0.40	CD40198	£0.44	CD40418	£0.80	CD40668	£0.45	CD4082	£0.20	CD4514	£2.20
CD40118	£0.20	CD40208	£0.90	CD40428	£0.64	CD4067	£4.20	CD4085	£0.90	CD45208	£0.90
CD4012	£0.20	CD40228	£0.78	CD40478	£1.02	CD4068	£0.30	CD4086	£0.90	CD4522	£1.10

## SIEMENS LEDS

5.8mm Red Yellow Green	£0.14	T1L 209	£0.18
3.2mm Red	£0.12	T1L 228	£0.35
3.2mm Green/Yellow	£0.14	T1L 78	£0.54
Flashing Diodes (3Hz)	£0.90	8PW 34	£1.18
Rect Leds 2.5 x 5.0mm Red	£0.12	SFH 205	£0.80
Rect Leds 2.5 x 5.0mm Green/Yellow	£0.18	ORP 12	£1.20
		4N25	£0.90

MA 1032 Digital LCD Clock Module £11.50  
.5" 12 or 24hr mode, 24 alarm with on/off control, sleep timer, snore timer etc. 1.5v batt. low consumption

MA 1026 Alarm/Thermometer Module £11.50

MA 1003 12v Car Clock Module, Special Price £12.50 whilst stocks last

NSN3914, 3915, 3916 End Stackable Led Bar

Graphs Arrays with Driver All @ £4.95 each.

## PRESENSITISED POSITIVE FOTO RESIST PC BOARDS 1.6mm THICK

SIZE	SINGLE SIDE	DOUBLE SIDE
100 x 160mm	£1.40	£1.65
100 x 220mm	£1.95	£2.60
203 x 114mm	£1.70	£2.10
233.4 x 220mm	£3.75	£4.50


KIT FOR UV EXPOSURE UNIT FOR DEVELOPING FOTO BOARDS  
COMPLETE WITH BOX & GLASS SCREEN 228 x 152mm £34.50  
OR WITHOUT BOX £19.50

SN7400	£0.19	SN7420	£0.15	SN7445	£0.91	SN7460	£0.15	SN7496	£0.20	SN74164	£0.91
SN7401	£0.19	SN7423	£0.19	SN7446	£0.24	SN7472	£0.20	SN74107	£0.20	SN74165	£0.91
SN7403	£0.19	SN7426	£0.21	SN7447	£0.24	SN7484	£0.51	SN74121	£0.20	SN74174	£0.60
SN7404	£0.15	SN7432	£0.21	SN7448	£0.30	SN7490	£0.25	SN74141	£0.24	SN74182	£0.60
SN7410	£0.19	SN7440	£0.15	SN7450	£0.19	SN7491	£0.35	SN74145	£0.77	SN74190	£0.60
SN7412	£0.15	SN7441	£0.30	SN7453	£0.15	SN7492	£0.20	SN74155	£0.50	SN74192	£0.91
SN7414	£0.55	SN7442	£0.20	SN7454	£0.15	SN7493	£0.20	SN74157	£0.70	SN74197	£0.60

DIGITAL FUEL STRETCHER SYSTEM GIVES ACTUAL Mpg. OR L/100Km  
EASILY FITTED - SUITABLE FOR MOST CARS. £58.50 p/p £1.30  
FLOW SENSOR S8011 £14.75  
SPEED SENSOR S8010 £11.95

SEND LARGE SAE FOR DETAILS OF SENSORS & PARTS TO BUILD OWN FUEL STRETCHER SYSTEM.  
MINI METAL DETECTOR FOR LOCATING PIPES/CABLES UNDER PLASTIC - A MUST FOR EVERY HANDYMAN £9.95

ALL PRICES EXCLUSIVE OF VAT

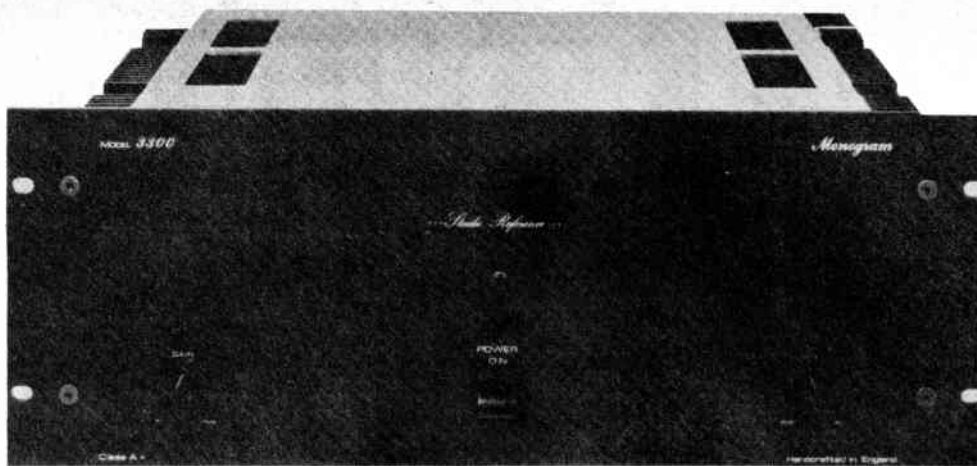

Although not strictly part of the review intended, I could not resist the prospect of a chance at the 3300 power amp. Rated at slightly less than twice the power of the 109, it promised to be an interesting beast under test.

As you can see from the test results it did not disappoint. The PSU contained herein is rated in excess of 1 kW in order that constraints upon this part of the design never become a stricture on the amplifier as a whole.

The sound quality produced by the 3300 is little different to that of the 109, as might be expected. If anything I'd give the 109 the slight edge under dynamic conditions, using a domestic system. Maybe the separate supplies, although individually lower rated impart to it a better coherence under hard drive. Otherwise all comments made herein on the 109 apply equally to the 3300.

The unit was primarily designed for studio usage, of course and so would be much more rugged — witness the massive metal work, ¼" jack connectors (or Cannons), fan mounting holes etc. etc.

The normal recommended retail of the beast is around £650, but interested parties should contact Monogram for the present price which is more £200 less than this, since the model is being phased out to allow the company to concentrate on the 106/109 range. At under £400 the 3300 is excellent value indeed for those needing a lot of power into any loading conceivable.

TABLE 2

Table 2. Test results: Monogram 109 and 3300 power amplifiers

	109	3300
<b>Power output:</b> 120 W (8R) (both driven 274 W (4R) per channel) 430 W (2R)*		215 W (8R) 347 W (4R)*
<b>Transient delivery:</b>	> 300 W (4R)*	> 400 W (4R)*
<b>Half-power bandwidth:</b>	10 Hz-70 kHz	10 Hz-50 kHz
<b>THD:</b>	<0.05% (20 Hz-20 kHz at 120 W)	<0.05% (20 Hz-20 kHz at 200 W)
<b>Damping factor:</b>	> 150 (20 Hz-20 kHz) > 400 (<1 kHz)	> 100 (20 Hz-20 kHz) > 400 (<1 kHz)
<b>Hum and noise:</b>	-100 dB (ref 100 W) — 120 dB (ref 200 W)	
<b>Input impedance:</b>	10k	15k-22k (gain setting)
<b>Input sensitivity:</b>	0 dB (775 mV)	0 dB (775 mV)
<b>Price:</b>	£340 (including PSU) £POA (see above).	

\*Burst power and sustained power into 2R is given in this form because both these amps exceeded my test rig capabilities. From current measurements it would appear that the 109 delivers in excess of 450 W into 2R and the 3300 around 560 W. Both figures are the highest I have measured from a domestic amplifier and illustrate an unrivalled ability to provide undistorted and unclipped power into any load.

As the output impedance is less than 600R, long leads to power-amps are no problem, as the load will not affect frequency response.

Overall the standard of construction is very high indeed and a clever PCB layout minimises both interwiring and noise/hum paths within the box. A toroidal transformer is fitted, to aid the hum figures still further.

As you can see from the spec the standard is a high one — and the 106 exceeded that spec on every parameter I measured. In some cases it bettered the limits of my test gear, thus leaving me simply to agree that the figures are 'reasonable'!

## Powerful Amps

The 109 power amps are separately cased, with the PSUs also residing in their own matching case. The two amp cases share a common front panel and are linked together by the casing system. Sensible power connectors are employed, and good large screw terminals are provided for speaker connections. Little points maybe, but correct connectors indicate that thought has been expended on all aspects of the design.

Input is via phono plugs — and all preamp outputs will be of this variety also. Being a confirmed hater of all things DIN, I find this most encouraging!

The PSU for each channel — they are separate — is rated at more than that required for 100 W output (we will return to this later). Toroidal transformers are again present and the constructional standard is impeccable. It is nice to be able to praise a British company for finish and construction for a change — too often is this the sole preserve of Oriental offerings.

Circuitry is of a mode entitled 'enriched bias' which means that for 90% of the available output, the amplifier runs in pure class A and will only switch to AB at powers in excess of that 90%. In this way class A sound can be obtained without the otherwise necessary hardware.

It is worth noting that Monogram marketed a design using this configuration many years before the Japanese production

ETI AUGUST 1981

Multiple triggering is rare, even at high noise levels, due to a hysteresis level detector (4093) and the use of CMOS circuitry throughout means low current consumption (less than 50 mA, inclusive of the light source current) and therefore portability. A stabilised voltage supply (78L05) for certain parts of the circuitry ensures a stable operation of the preamp and reliable frequency reading for a battery voltage as low as 7 V.

## Construction

The construction of this project should present no problems if the overlay and photographs are followed — the only precautions are to avoid touching the IC pins in case of damage by static, and to keep the PCB clean in order to minimise leakages around IC2. The sensor assembly is fairly easy to make, using a small piece of scrap aluminium and a Velcro band. The leads to the sensor should be shielded — see

the photographs.

To calibrate the unit a reference frequency has to be fed to the input — the simplest method is to place an LED in front of the phototransistor. The reference frequency required is quite low and can be obtained either from a low frequency generator or by dividing down from a higher frequency (or the 50 Hz mains). With the reference at 0.66 Hz, adjust PR2 to give a zero reading on the scale — this corresponds to the minimum reading of 40 beats per minute. Now alter the reference to a suitable upper limit (eg 2 Hz gives an FSD of 120 beats per minute), and adjust PR1 to give FSD on the meter.

Many interesting experiments can be set up with this piece of equipment, although it must be pointed out that non-approved instruments cannot be used for medical purposes. Female readers wishing to participate in experiments on the heartbeat rate of staff members should apply to the editorial department at the usual address.

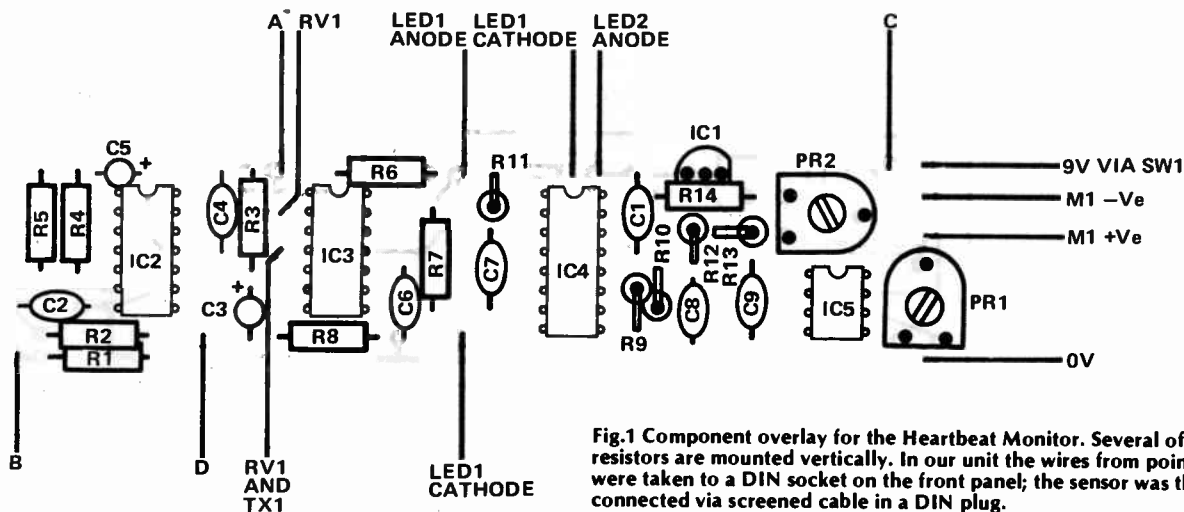


Fig.1 Component overlay for the Heartbeat Monitor. Several of the resistors are mounted vertically. In our unit the wires from points A-D were taken to a DIN socket on the front panel; the sensor was then connected via screened cable in a DIN plug.

## HOW IT WORKS

The circuit consists of a signal extractor and conditioner, followed by a very low frequency meter.

Infra-red light is emitted from the LED in OCS1 and a small fraction is reflected back to the phototransistor from the bloodstream. The photocurrent from the sensor is sunk by IC2a, an enhancement mode MOS transistor which acts as an adjustable current source with a gate voltage of about 3 V. The R2/C2 network fixes the rate at which current sinking can alter: any variations with a higher frequency are passed on to the next stage via C3.

Transistors IC2b,c form an inverting pair polarised to half supply voltage by R3 — the gain of this stage is fixed by the ratio of C3 to C4. C5 transmits the signal to the next stage formed by inverting pair IC2d,e, polarised by R4 and offset by R5 so as to switch over only on the positive peaks of the signal. This is a high gain stage as the signal is fed directly to the inverter input.

All the previous stages are working at very high impedances as the photocurrent is of the order of nanoamperes. All the MOS transistors are working linearly in this circuit.

Any noise in the signal is removed by IC3a, a Schmitt NAND gate, which provides a clean digital impulse for the frequency meter. The output of IC3a also drives LED1, giving a visual indication of the beat rate, and gates on audio oscillator IC3b. Gates IC3c,d effectively double the driving voltage to the audio transducer.

The frequency measurement is made by locking IC4, a 4046B phase-locked-loop, onto the heartbeat frequency and displaying the control voltage of the PLL VCO on an analogue meter. This is just about possible if C7 is a good quality capacitor and with high resistances at R9 and R10. The linearity is very good, and the design of the low-pass network means that the instantaneous frequency of each beat can be displayed. A smoothed voltage from C9 is buffered by IC5 in a voltage follower configuration and both the maximum and minimum frequencies can be calibrated using PR1 and PR2 respectively.

## BUYLINES

The only unusual component used in this project is OCS1, a TIL139 optically-coupled switch used as the sensor. This device is available from Marshall's and Watford Electronics. The PB-2720 is available from Ambit International.

You should be able to get Velcro from the haberdashery department of any large department store.


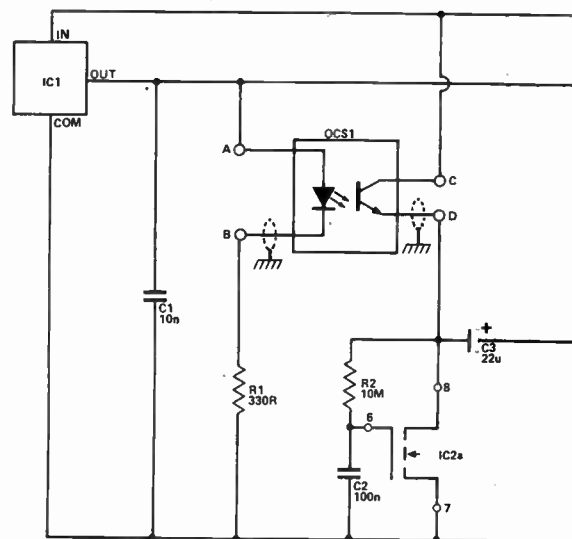


Fig.2 Circuit diagram of the complete unit.  
ETI AUGUST 1981

# PROJECT : Heartbeat Monitor

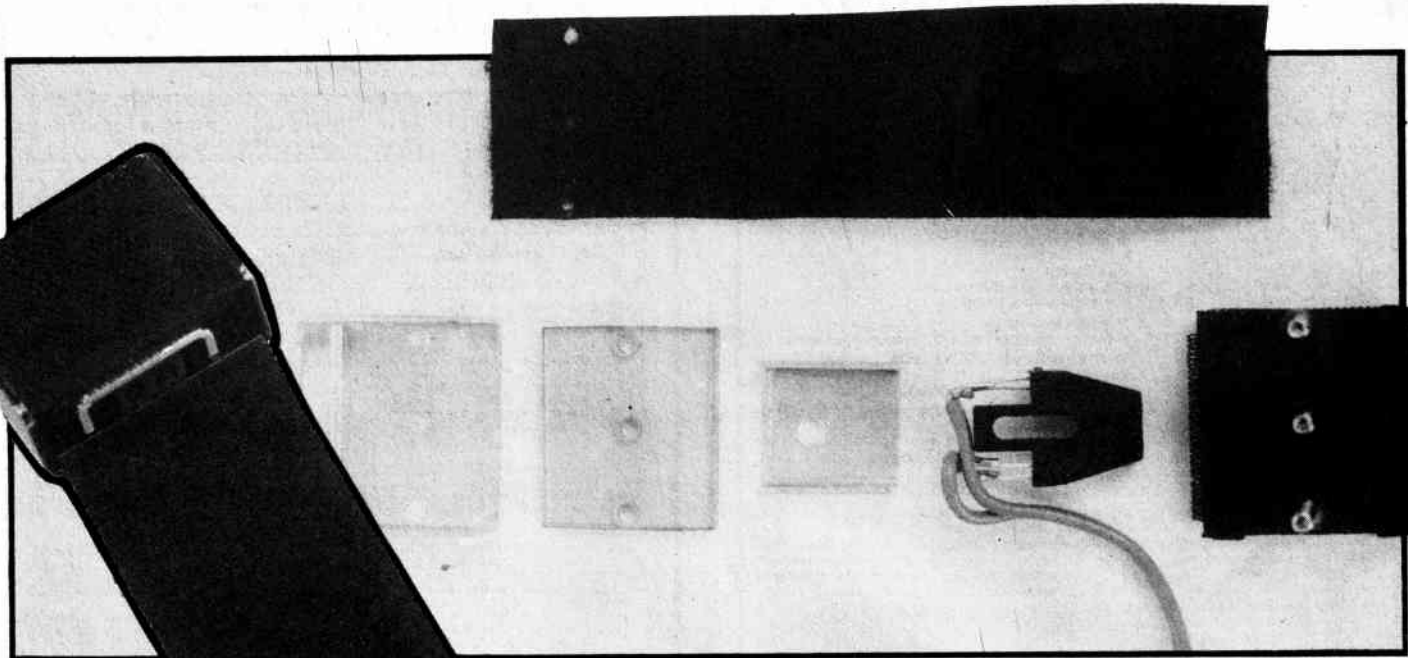

The parts that make up our sensor, and (inset) the completed assembly. The optoswitch is sandwiched between sheet aluminium and the Velcro strips are clamped by the Perspex squares. The finished sensor is fastened to the thumb by the Velcro strap with OCS1 in contact with the skin.

## PARTS LIST

### Resistors (all 1/4 W, 5%)

R1	330R
R2, 5	10M
R3	3M3
R4	1M2
R6,7,11	1k0
R8	15k
R9,12	1M0
R10	6M8
R13	1M8
R14	10k

### Potentiometers

RV1	100k linear with integral switch
PR1,2	4k7 miniature horizontal preset

### Capacitors

C1,6	10n polyester
C2	100n polyester


C3	22u 16 V tantalum
C4	47n polyester
C5	2u2 35 V tantalum
C7,9	1u0 polycarbonate
C8	220n polycarbonate

### Semiconductors

IC1	78L05
IC2	4007UB
IC3	4093B
IC4	4046B
IC5	CA3140
OCS1	TIL139

### Miscellaneous

TX1	PB2720
M1	1 mA FSD moving coil meter
Battery holder	(six HP7)

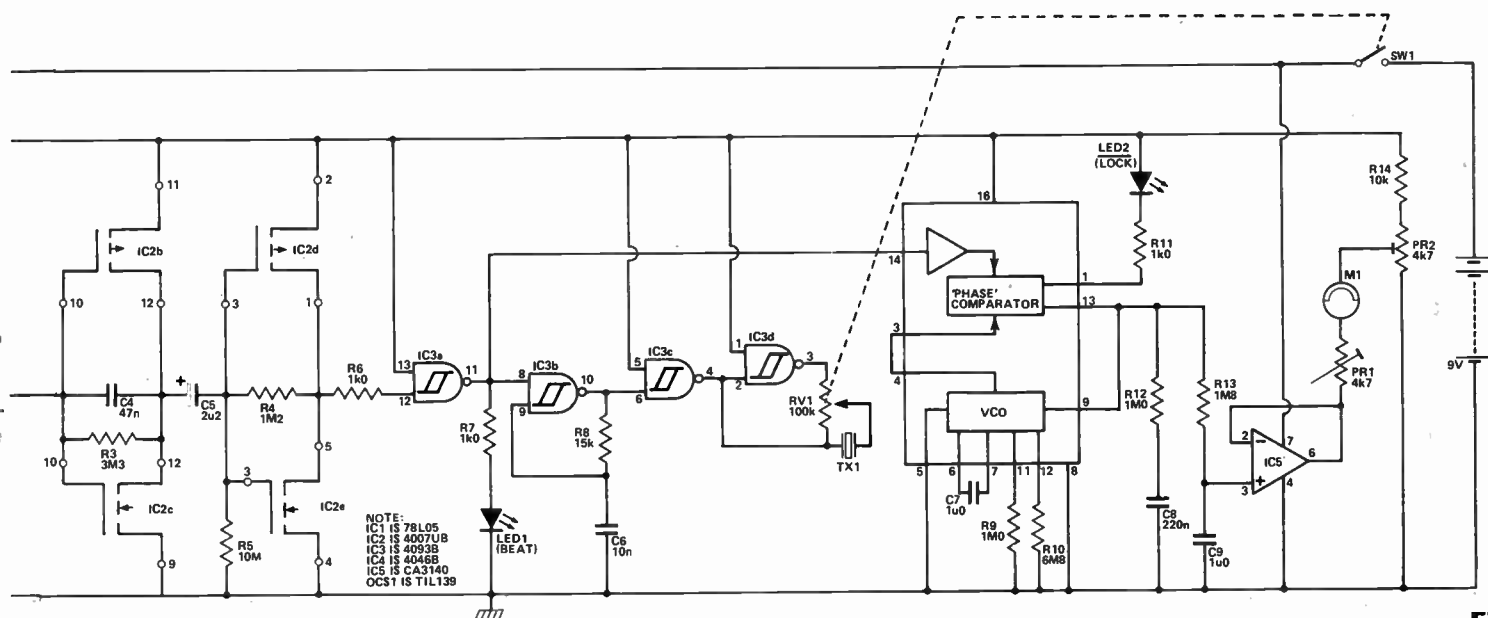

# CLEF ELECTRONIC MUSIC

## MASTER RHYTHM

As published in Practical Electronics



KIT - £79. BUILT - £114

FULLY PROGRAMMABLE  
TWENTY-FOUR PATTERNS

EIGHT PARALLEL TRACKS

TWELVE INSTRUMENTS

SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

### PIANOS

SPECIALISTS SINCE 1972  
"TAME & DOMESTIC TYPES"



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufacture.



SIX OCTAVES £207  
7½ OCTAVES £232

### STRINGS £174

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

### ROTOR-CHORUS

£89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

### KEYBOARDS

Square Front with two hole actuator—easily cut.


49 NOTE £25; 73 NOTE—£41  
88 NOTE £49.50

#### OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

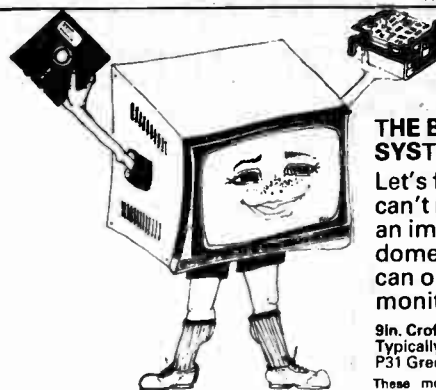**CLEF PRODUCTS (ELECTRONICS) LIMITED** (Dept. E.T.I.)  
44A BRAMHALL LANE SOUTH, BRAMHALL,  
STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297



### THE BODY OF ANY SYSTEM

Let's face it — you can't produce as crisp an image on a domestic TV as you can on a Crofton monitor.

9in. Crofton Monitors  
Typically P4 White..... £84.97  
P31 Green..... £79.32

These monitor prices are dependent upon sterling/dollar conversion rates. Phone us for up-to-date prices.

### SHUGART FLOPPY DISK DRIVES

No case. No power supply.

SA 400 5¼in. S.S.S.D. .... £149.05  
SA 450 5¼in. D.S.S.D. .... £283.31  
SA 800 8in. S.S.S.D. .... £340.52

### FLOPPY DISKS — BOXES OF TEN

Single-sided 35/40 Track ..... £26.45  
Double-sided 35/40 Track 5¼in. .... £37.95  
Single-sided 77 Track ..... £41.40  
Double-sided 77 Track 5¼in. .... £47.15  
Single-sided 8in. .... £40.25

### IKEGAMI 12in. MONITORS

P4 White..... £171.50  
P31 Green..... £184.97

2/3in. FULLY INTERLACED C.C.T.V. CAMERAS..... £149.00

ALL THE ABOVE PRICES INCLUDE V.A.T. AND CARRIAGE



ALL MAJOR CREDIT CARDS  
ACCEPTED: Small surcharge




**CROFTON ELECTRONICS LTD.**

35 Grosvenor Road, Twickenham, Middx, TW1 4AD  
01-891 1923/1513


Chokes, block filters, ceramic filters, resonators, IFTs, oscillator coils, audio filter blocks etc.
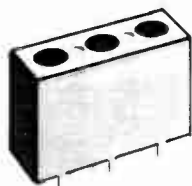
### LOW PASS FILTERS

Now from 10kHz to 20MHz  
TOKO's recently expanded LPF series covers from the audio spectrum through to 20MHz in a series of LPFs for mpX, video, radio etc.




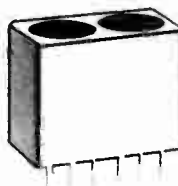The LPFs are based on 7&10mm formats with up to 4 LC tuned elements per block. Many stock types available.



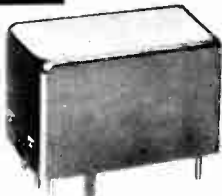
### HELICAL FILTERS 2 & 3 elements available for VHF and UHF:

Featuring low insertion losses, -80dB at the +/- 21.4MHz points. Ask for details.



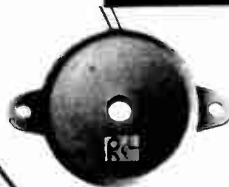
### CERAMIC RESONATORS & PIEZO SOUNDERS

Audio buzzers now down to 1kHz - low cost 400-600kHz crystal replacements for MPUs, RCs etc. Low cost - wide range.


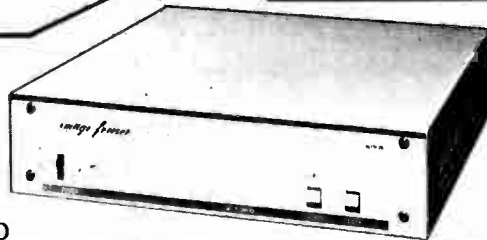
### VIDEO FRAME STORES

- \* 525/625 operation
- \* 512 pixell/line
- \* Local or remote control
- \* Top/bottom & L/R reverse
- \* Models available with digitized I/O



Video frame stores are a new addition to TOKO's memory product range. They permit easy analysis of low dose X-Ray pictures, digital processing of picture information (including the VFM10D with 8" disk drive) with much better resolution than available from VTR

**AMBIT international** TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG  
200 North Service Road, Brentwood, Essex

term current delivery and, equally important, current-sinking capability far in excess of any known Class AB power amplifier of similar rated output power.


## Amp Of Substance

The output stage is quite substantial, using a total of six 250 W power transistors. Fairly 'old-fashioned' power transistors have been used (the MJ4502/802 family) in preference to some of the higher performance devices now available. They have been chosen because the die used to mount the semiconductor junction is of a large area; the device is quite rugged and can handle high currents. The short-term current capability of the output stage is, in fact, of the order of 90 A, somewhat in excess of the current capability of the wiring!

The power supply is equally substantial, using a 500 VA toroidal mains transformer and two massive computer grade reservoir capacitors. These components are expensive but essential. The rest of the construction is equally massive with a steel chassis supporting six very large heatsinks. However, construction is straightforward provided that the builder has strong arm muscles, and circuit alignment simple — there are but two adjustments — quiescent current and DC offset voltage nulling.
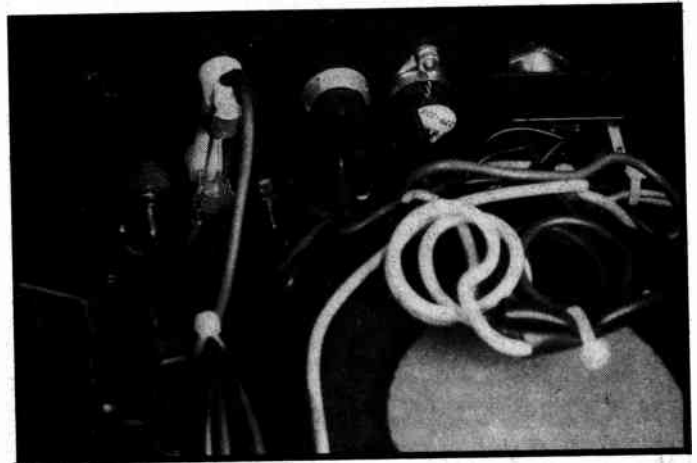
## Construction

The constructional layout shown in the drawings and photographs should be followed as closely as possible. (With such high currents flowing down the cable forms, problems can easily occur if too many changes are made.) The heatsinks and the power supply components are assembled onto the baseplate and wired up in accordance with the wiring diagram. The recommended wire types and gauges should be adhered to.



Close-up of fuse wiring on back panel.

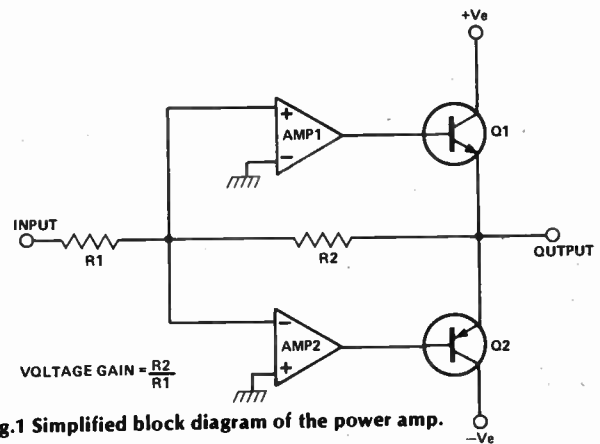


Fig.1 Simplified block diagram of the power amp.

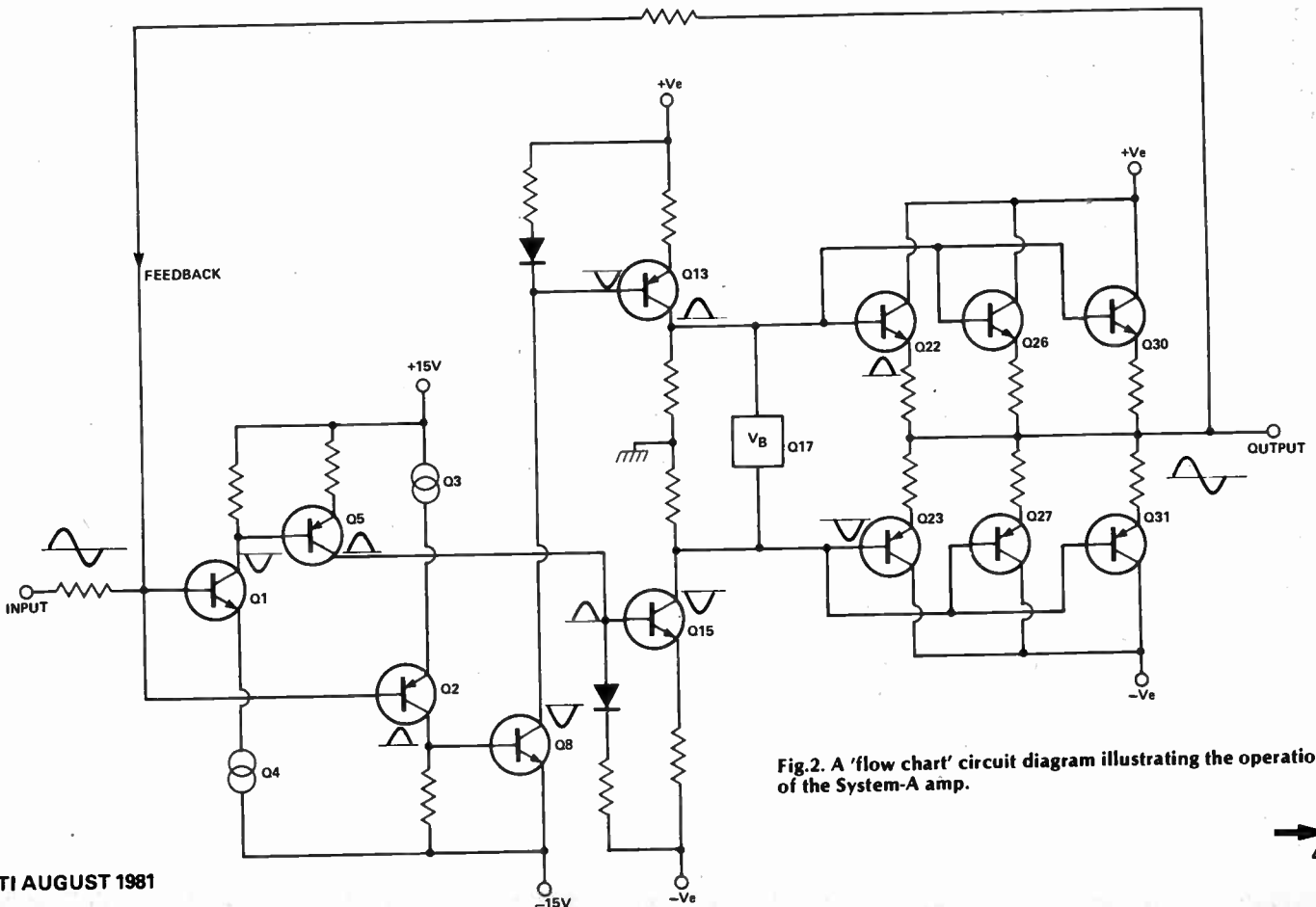


Fig.2. A 'flow chart' circuit diagram illustrating the operation of the System-A amp.

# PROJECT : System A Power Amp

Left: a detail shot showing how the PCB is wired into the case.

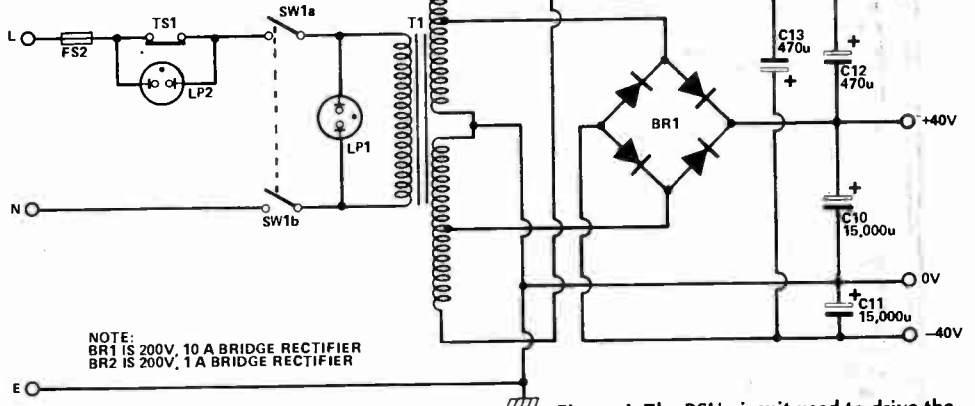
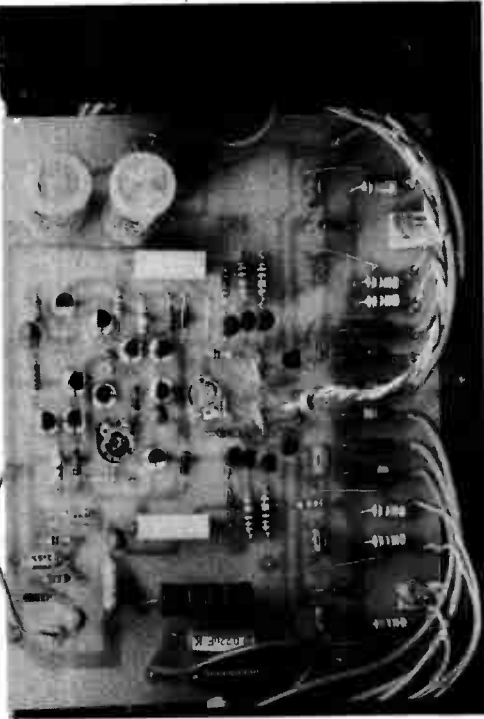



Figure 4. The PSU circuit used to drive the power amps.

## BUYLINES

Most of the components specified are readily available from the usual suppliers except for the connectors and the low noise transistors. The board-to-board gold-plated connectors (horizontal, 45°) are type 434-172, and the vertical input-to-board connectors are type 434-188. These are available from RS Components Ltd, and can be ordered via a local stockist.

Kits of parts for the System A amplifier are available from Jelgate Ltd, 215 High Street, Offord Cluny, Cambs. Prices are as follows:  
 Preamp Kit 1 containing two chassis (preamp and PSU), toroidal transformer, and all the chassis-mounting components; £28.  
 Preamp Kit 2 containing the A-PR and A-PSU PCBs and all components; £26.

Preamp Kit 3 containing A-MM/A-MC PCB and components; £12 for either version.  
 Set of four input transistors, selected for low noise; £2.  
 Power Amp Kit 1 containing all the metalwork, heatsinks and chassis-mounting components; £105.  
 Power Amp Kit 2 containing transformer, capacitors, power supply components and power transistors; £65.  
 Power Amp Kit 3 containing A-PA PCB and components; £23.  
 All these prices are exclusive of VAT and carriage. The cases are all ready-painted and screen-printed. Items can be bought separately; a comprehensive price list can be obtained from Jelgate.

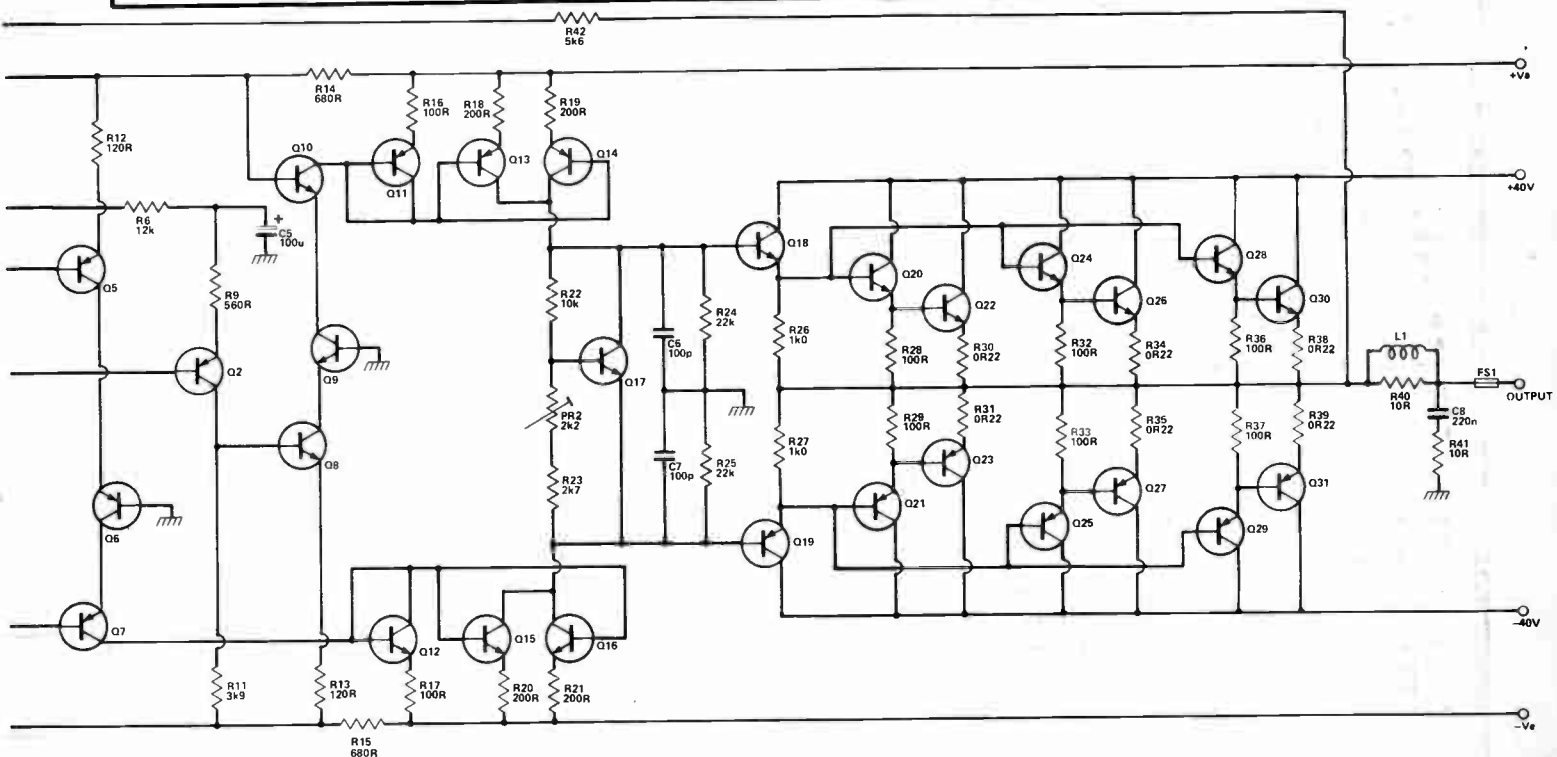



# PROJECT : System A Power Amp

## PARTS LIST

Resistors (all 1/4 W, 5% except where stated)

R1	47k
R2,10,26,27	1k0
R3,22	10k
R4,9	560R
R5,11	3k9
R6	12k
R7,8,23	2k7
R12,13	120R
R14,15	680R 4 W
R16,17,28,29,32,33,36,37	100R
R18,19,20,21	200R
R24,25	22k
R30,31,34,35,38,39	0R22 2W5
R40	10R 1 W
R41	10R 2 W (not wirewound)
R42	5k6
R43	18k
R44	300R

Potentiometers

PR1	20k miniature horizontal preset
PR2	2k2 miniature horizontal preset

Capacitors

C1	10u 35 V tantalum
C2	1n0 polystyrene
C3	100p polystyrene

C4,5,9

C6,7

C8

C10,11

C12,13

Semiconductors

Q1,4,8,9,10,17,18

Q2,3,5,6,7,19

Q11,13,14

Q12,15,16

Q20,24,28

Q21,25,29

Q22,26,30

Q23,27,31

ZD1,2

100u 6V3 tantalum

100p miniature ceramic

220n polycarbonate

15,000u 50 V electrolytic (Sprague type

36D)

470u 63 V electrolytic (PCB type)

MPSA06

MPSA56

MPSA93

2N6515

BD379

BD380

MJ802

MJ4502

15 V, 1W3

Miscellaneous

SW1

TS1

LP1

LP2

FS1

FS2

DPST mains switch

Thermal cut-out switch

Red neon

Orange neon

1 1/4" 5 A—10 A (to suit loudspeaker)

20 mm 3.15 A

Toroidal transformer, 1 1/4" chassis-mounting holder, 20 mm panel-mounting holder, phono input socket, loudspeaker screw-terminals, chassis and heatsinks, mounting hardware.


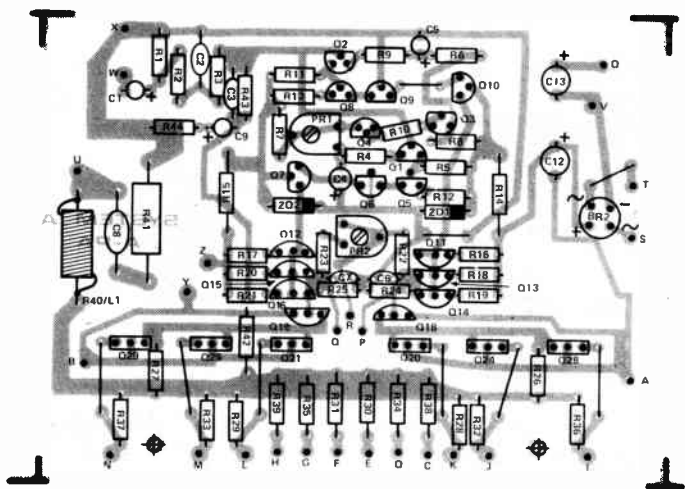


Figure 5. Component overlay for the power-amp PCB.

Next month: we conclude the amplifier project with the PSU and interwiring details.

### PIN CONNECTIONS


A	+ 40 V	N	Q31 base
B	- 40 V	O	Wire link to pin Y (underside of PCB)
C	Q30 emitter	P	Q17 collector
D	Q26 emitter	Q	Q17 emitter
E	Q22 emitter	R	Q17 base
F	Q23 emitter	S	Transformer
G	Q27 emitter	T	Transformer
H	Q31 emitter	U	Output
I	Q30 base	V	Wire link to pin Z (underside of PCB)
J	Q26 base	W	Input
K	Q22 base	X	Ground
L	Q23 base		
M	Q27 base		

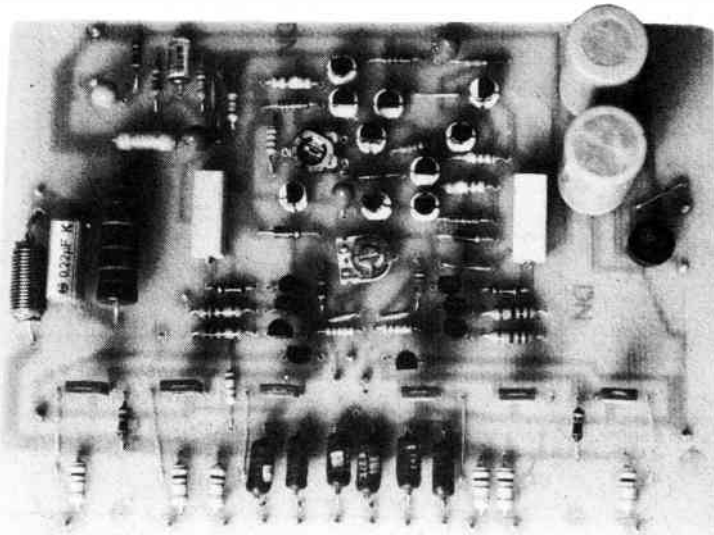

# QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

## BECKER Hi-Fi Speakers

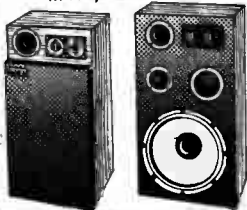

### All models multi-speaker systems

With controls, attractive woodgrain finish. RMS ratings for 8 ohm.

12.60 12" 4 speaker system 60 watts 28 1/2" x 14 1/2" x 11" ..... £115.95 pair

15.90 15" 5 speaker system 90 watts 28" x 17 1/2" x 11 1/2" ..... £135.95 pair

ON DEMONSTRATION TO CALLERS

Collection only

## COLES CIRRUS BOOKSHELF SPEAKERS

Teak or walnut finish. Size just 6 1/4" x 11 1/4" x 6 1/4". Response 95Hz-25KHz.



Small high quality hi-fi bookshelf speaker system with the latest Coles Advanced Technology providing amazing response for such small speakers, particularly at the LF end. Ready to use. Per pair. (UK c/p £5)

£96

LARGE RANGE OF CHASSIS SPEAKERS ALWAYS IN STOCK



## JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO TECHNICA AT100 STEREO CARTRIDGE.

★ S shaped tone arm  
★ Belt drive  
★ 12" Platter ★ Calibrated counter-balance weight

★ Anti-static device

Size 12 3/4" x 15 1/2" (C/P £1.55)

£29.95


## TV SOUND FROM YOUR HI-FI

High quality TV sound converter plugs into serial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at... but just listen!

★ Fitted slow-motion drive (Mk III)

(UK Post etc. 65p)

On Demonstration for callers. £11.50

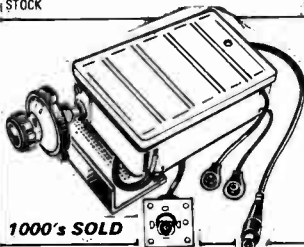

1000's SOLD

## SEAS SPEAKER KITS

8 ohm



Professional sound hi-fi speaker kits with high sensitivity (89-92dB). Extended frequency response [223-50-20kHz, 253-35-25kHz]. Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans, tweeters/crossovers/leads etc. ★ On Demonstration to callers.

- ★ Hi-Fi 223. 30/45 watt 3 speaker 8" system £43.50 pair
- ★ Hi-Fi 253. 60/100 watt 3 speaker 8" system £34.50 each
- ★ Hi-Fi 403. 60/100 watt 3 speaker 10" system £44.50 each
- ★ Hi-Fi 003. 80/150 watt 3 speaker 12" system £84.50 each.

(UK C/P £7.50)

COMPLETE RANGE OF SEAS CHASSIS SPEAKERS ETC ALWAYS IN STOCK ALSO STOCKISTS FOR AUDAX, GOODMANS, KEF, PEERLESS ETC.

## PIEZO TWEETERS



Clear sound, very low distortion tweeters. No crossover required. Suitable up to 100 watts - more in series.

- 1 Mid-range horn for disco/pa/groups ..... £8.95
- 2 Tweeter horn for hi-fi/disco/pa ..... £5.50
- 3 Popular hi-fi and disco ..... £4.40
- 4 Flat type hi-fi ..... £3.50

On Demonstration to callers. C/P 50p (up to 4 items)

## STEREO ACCESSORIES

- ★ GE1305 Hi-Fi Frequency Equaliser ..... £59.95
- ★ APW 200 Peak programme meter (twin scale) £39.95
- ★ MS3219 Twin Scale audio output meter £12.95
- ★ MC350 Tape echo chamber ..... £84.95

## FREE CATALOGUE

Large range of speakers/stereophones/microphones/mixers/PA equipment etc - and much more! Plus huge range of test equipment. ALL PRICES INCLUDE VAT SEND LARGE 20p SAE

PRICES CORRECT 1-6-81.

# ELECTRO SUPPLIES

## LINEAR ICs

CA3012	45p	SAJ110A	150p	TDA1170	175p
CA3080	50p	SAS580	100p	TDA1190	200p
LM324	60p	SAS590	100p	TDA2524	150p
LM741	15p	TAA320	40p	TDA2541	150p
LM1458	40p	TBA120S	60p	TDA2560	150p
LM3900	60p	TBA651	100p	TDA2581	175p
MC1307	75p	TBA661B	125p		
MC1310	100p	TBA800	70p		
MC1349	90p	TBA810S	80p		
MC1350	90p	TBA920	150p		
MC1558	100p	TCA270S	150p		
NE535T	50p	TDA0470	150p		
NE555	22p	TDA1010	150p		

**SPECIAL OFFER**  
AY-5-3507 DVM CHIP (with data) £2.00 (limited quantity).  
150p

LOW PROFILE IC SOCKETS	
14 pin - 12	100 (150 £10)
16 pin - 10	100 (130 £10)
22 pin - 7	100 (100 £10)
24 pin - 6	100 (70 £10)
40 pin - 3	100 (40 £10)

35-amp 50-volt Stud Diodes, c/w mounting kit 4 £1

Semi-conductor Packs. Diodes/Transistors/SCRs/ICs. over 100 items (no rejects)

£1.50 each, two for £2

For larger quantities please phone for prices

## SPECIAL OFFERS

LM1011N (DOLBY B I/C) c/w data	£2.50
TDA2020 (20 watt amp)	£2.50
MM57105 (PAL colour TV game I/C)	£2.00
MM53100N (TV clock timer)	£2.00
AY-5-1013 (UART) c/w data	£2.00
Z80A c/w data	£5.00
4116-4 c/w data	£1.75
Red LEDs .2"	12 for £1.00

## MISCELLANEOUS

80-way DS .1" pitch edge connectors	£3.00
16-pin DIL 4 p/co switch	£1.00

## CMOS

4001B - 6	£1.00
4011B - 7	£1.00
4013B - 4	£1.00

Prices include VAT, please add 50p P&P

S.A.E. for Lists

MAIL ORDER DEPT.  
(Callers please phone first)  
BOWNESS MILL  
SHAWCLOUGH RD  
WATERFOOT  
ROSSENDALE, LANCS  
TEL: ROSSENDALE 215556

RETAIL SHOP  
(Open 6 days)  
6A TODD ST  
MANCHESTER  
(next to Victoria Stn.)  
TEL: 061-834 1185

## AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND.  
TELEPHONE 01-724 3564 OPEN 9-6 Mon-Sat  
ALSO AT HENRY'S RADIO,  
404/406 EDGWARE ROAD, LONDON W2 1ED

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS OR CALL IN AND SEE FOR YOURSELF



amplify the pipe tones, but violins and brass also need 'space' to develop proper tonality, and even amplified guitar will sound thicker and richer in an acoustically 'live' environment.

Second, a musician needs to hear both his own instrument and those of the others in the group; this is not always easy in studios where the total sound pressure level attenuation over 10 feet can be as much as 56 dB! For the recording engineer, however, this very heavy damping is necessary — some would say essential — if he is to make clean recordings. Too much acoustic reverberation produces a muddy, bass-heavy sound from individual instruments and will cause 'spill' (acoustic crosstalk between a sound source and adjacent microphones), reducing the separation between tracks of the recording and probably resulting in a blurred stereo perspective and/or further loss of clarity.

Critically damped acoustics allow the engineer maximum creative freedom and control. Reverberation and tonality can be easily adjusted using the sophisticated electronics of the mixing console and 'outboard' signal processors, whereas he has very limited influence over the acoustic characteristics of the studio itself. In fact there is nothing 'magic' about acoustically 'dead' rooms; many producers and musicians will avoid them at any cost. The ultimate criteria is 'the sound', so that one studio will develop a reputation as a good rock'n'roll studio while another will be popular for disco or advertising jingles.

In recent years, the design and construction of recording studios has itself become an industry, geared to producing the 'perfect' recording environment. Inevitably this involves a compromise between the conflicting requirements of engineers and musicians. A practical solution is to provide more easily


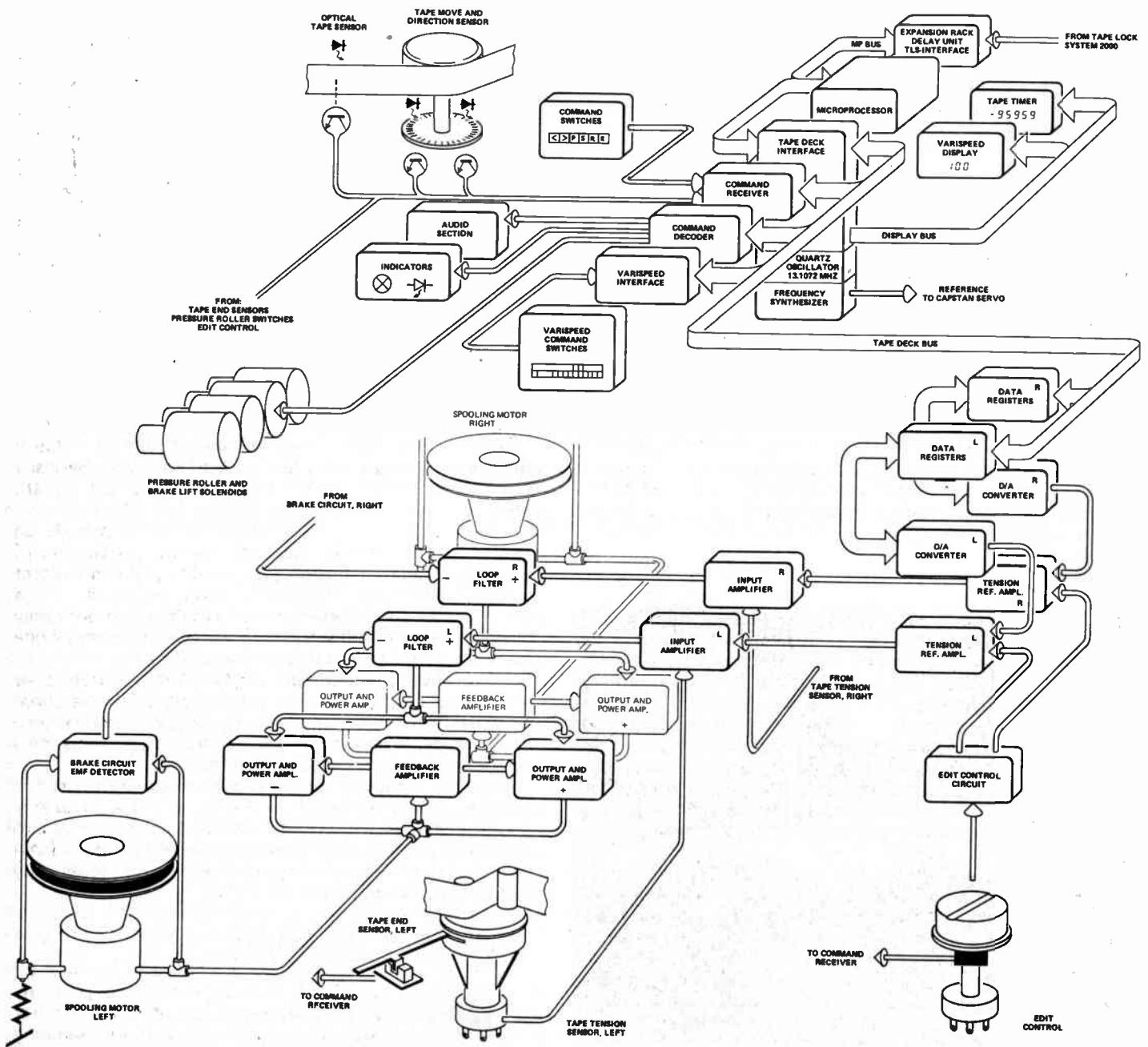


Fig.1 Block diagram showing the spooling motor controls and sensors of a multitrack recorder/reporter (Studer A800).

**£395**  
incl.VAT& P&P

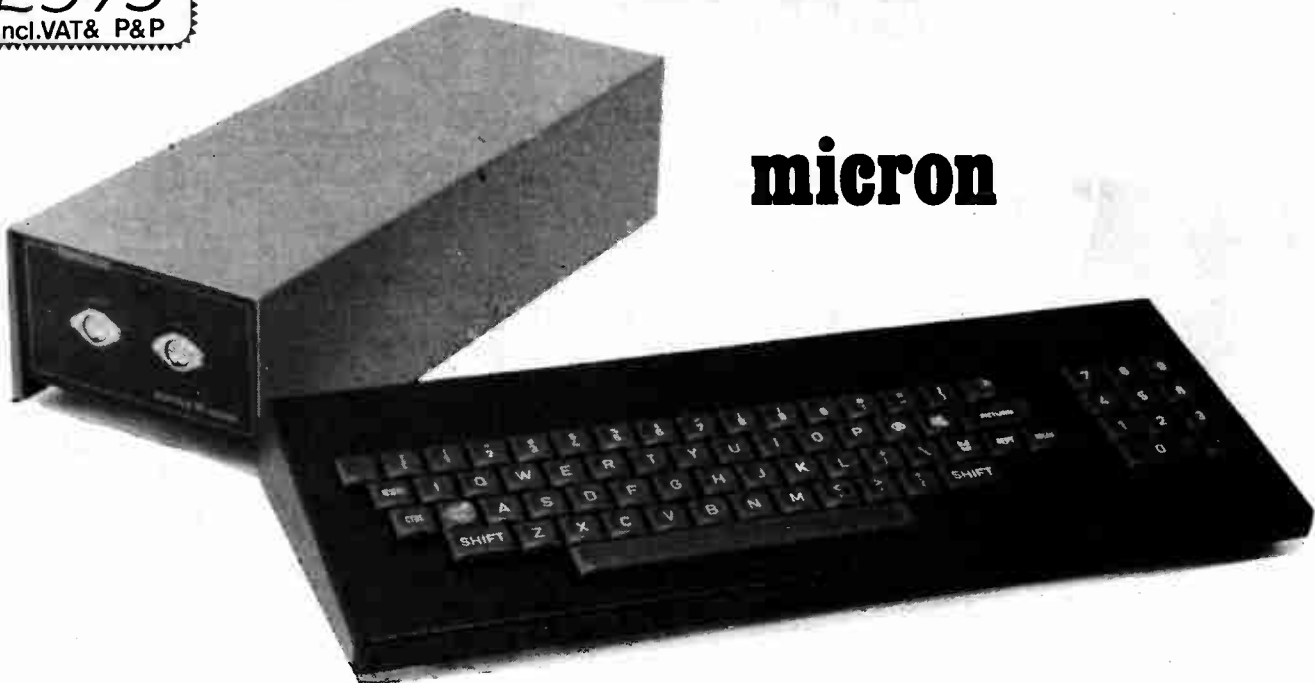

**micron**

'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you Micron, a ready built and tested computer of outstanding value. Fully supported by comprehensive documentation, Micron represents an ideal starting point in personal computing. We've taken a full O.E.M. licence for Microsoft Basic, which means that you'll have the support of the most popular Basic available, (as used on PET, APPLE, TANDY etc.). If you want to expand Micron there's no problem, just move into the system rack and choose from the range of Microtan modules. Read the information, study what the magazines have to say about us and compare what we have to offer with other systems, then we feel sure that you'll be convinced that we've produced an excellent product.


- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- 1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.

- SOFTWARE
- 10K EXTENDED MICROSOFT BASIC.
  - ALL THE USUAL BASIC COMMANDS.
  - INTEGER AND REAL NUMBERS.
  - INTEGER AND REAL ARRAYS.
  - INTRINSIC FUNCTIONS: ABS, INT, RND, SGN, SIN, SQR, TAB, USR, ATN, COS, EXP, LOG, TAN.
  - USER DEFINED FUNCTIONS.
  - READ AND DATA STATEMENTS.
  - DUMP AND LOAD PROGRAMS.
  - PROGRAM EDITING COMMAND.
  - STRING FUNCTION FOR TEXT I/O.
  - BASIC CAN CALL MACHINE CODE SUB-ROUTINE.
  - USER MACHINE CODE INTERRUPT HANDLER INTERFACES WITH BASIC.
  - XBUG.
  - DATA CASSETTE FILE HANDLING IN BASIC

**TANGERINE**  
COMPUTER SYSTEMS LIMITED

Forehill Works  
Forehill Ely Cambs England Tel: (0353)3633

# microtan 65

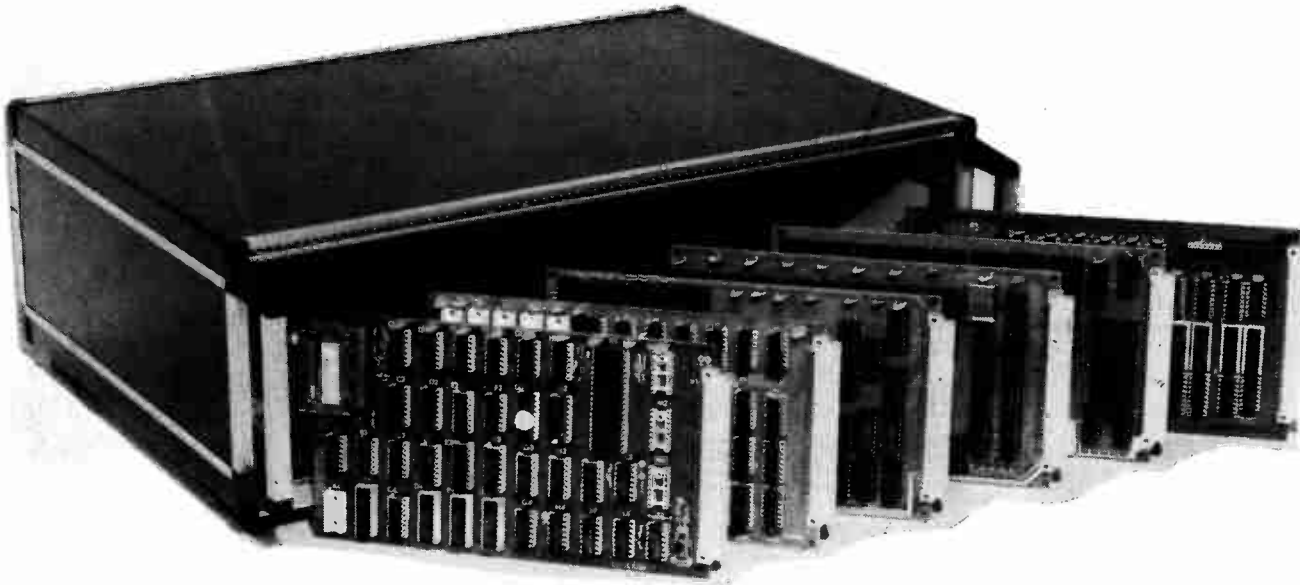

The Microtan system is rapidly becoming accepted as the ultimate approach to personal computing. Start with Microtan 65, a 6502 based single board computer, and expand to a powerful system in simple and in-expensive stages. The Microtan system is a concept and not an afterthought, this means expansion is easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow Microtan, and you won't be wasting your money on a product that will only last you a few months! When you are ready to expand, Tanex is waiting. The features offered by Tanex are tremendous, and you can start into them for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in extra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers a serial I/O line with RS232/20mA loop and full modem control, XBUG - a firmware package containing cassette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, **PLUS 10K EXTENDED MICROSOFT BASIC**, a suped-up version of the Basic as used by major manufacturers such as Apple, Tandy and Nascom, **NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE.** O.K. so you want more memory, try Tanram for size! Upto 40K bytes on one board starting for as little as £50.60. RAM freaks will be pleased to hear that our system mother board offers page memory logic which will support 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack (as used on Micron), which accepts Microtan and Tanex, or our system rack pictured above. The system rack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O modules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O ports respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D and D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and TANDOS - a 6502 CPM system. So there's plenty to keep you busy. Send for more details, and find out how you can get started for just £79.35! **ALL PRICES QUOTED INCLUDE V.A.T.**

## AIM 65, KIM 1, SIM 1 USERS- READ ON!

We have produced a T.V. interface module which simply connects to the expansion socket of your computer and produces a display of 16 rows by 40 characters! Of even more interest will be our Buffer module, which allows you to expand into our system rack, giving you access to the full range of Microtan modules.

Please underline the information required.

AIM T.V. INTERFACE.      MICROTAN SYSTEM.

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

PLEASE ENCLOSE 12p STAMP. THANK YOU. \_\_\_\_\_

# SPOT DESIGNS

## Points Controller


The electric points used in model railways are operated by a simple mechanism which utilises two solenoids, providing movement in opposite directions. Thus, briefly connecting power to one solenoid changes the state of the point and a short burst of power to the other solenoid changes it back to its original state. It is essential that the power is only applied in short bursts, since the current consumption of each solenoid is typically in the region of 1-2 A, and continuous power would almost certainly cause the solenoid to burn out.

It is possible to eliminate any chance of accidentally destroying a solenoid by using a capacitor discharge controller such as this simple design. This takes its power from an auxiliary AC output of a train controller. It will also work from a DC output of a controller if necessary. D1-4 form a bridge rectifier, which full wave rectifies the input. The resultant pulsing DC signal is used to charge C2 via R1. The purpose of R1 is merely to limit the current that can flow continuously through

the points solenoids to a safe level (about 100 mA or so).

The high current required to activate the point is available from C2, but this can only provide short bursts of current as it quickly discharges through the low impedance provided by the solenoids. The value of C2 is chosen to give pulses of power that are sufficiently long to give reliable operation of the point, but offer no possibility of burning out the solenoids. SW1 or SW2 is closed to select the appropriate point and then either SW3 or SW4 is operated to switch the point over.

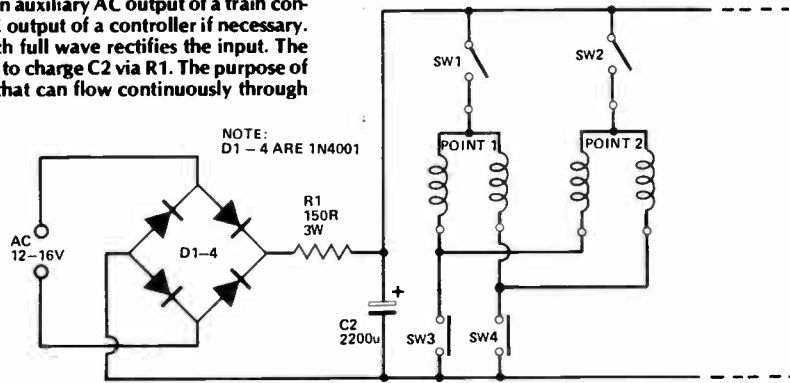Although only two points are shown in the circuit diagram, obviously any number of points can be connected to the unit, an additional switch being required for each one. SW3 and SW4 must be heavy duty types having a current rating of at least 2 A.



©COPYRIGHT MODMAGS Ltd

## Seatbelt Reminder


This simple seatbelt reminder circuit connects to the battery via the ignition switch, and sounds an audible reminder signal when the ignition switch is turned on. The audio signal is cancelled by operating a push button switch.

The audio signal is generated by IC2 which is an ICM7555 (the CMOS version of the standard 555) used in the astable mode. The CMOS version is preferable in this application since it has a higher maximum supply voltage rating and is less likely to be damaged by an excessive supply voltage. C3 couples the output of IC1 to a high impedance loudspeaker which should not have an impedance of less than 50R.

The oscillator is controlled by the voltage fed to pin 4 of IC2; with a voltage of less than about 0V5 the oscillator is disabled. IC1 is a

CMOS quad two-input NOR gate, but only two of the gates are used, and these have their inputs wired in parallel so that they operate as simple inverters. They are connected in series and have DC positive feedback via R2 so that a simple latch circuit is produced. C1 provides a positive input pulse to the latch so that initially the input (and therefore the output as well) assumes the high state. Thus the oscillator operates when power is first applied to the circuit, and the reminder signal is produced. Briefly operating PB1 takes the input (and output) to the low state, so that the unit functions properly when the ignition switch is operated again.

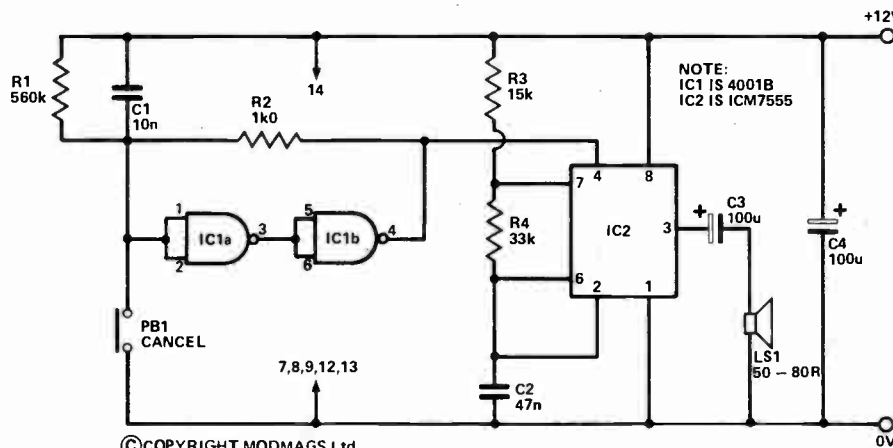As the quiescent current consumption of the unit is less than 1 mA the unit does not have a detrimental effect on the car battery (which has a very high capacity), especially as the unit is only connected to the battery when the ignition switch is turned on.



©COPYRIGHT MODMAGS Ltd



# PROJECT : Flash Sequencer



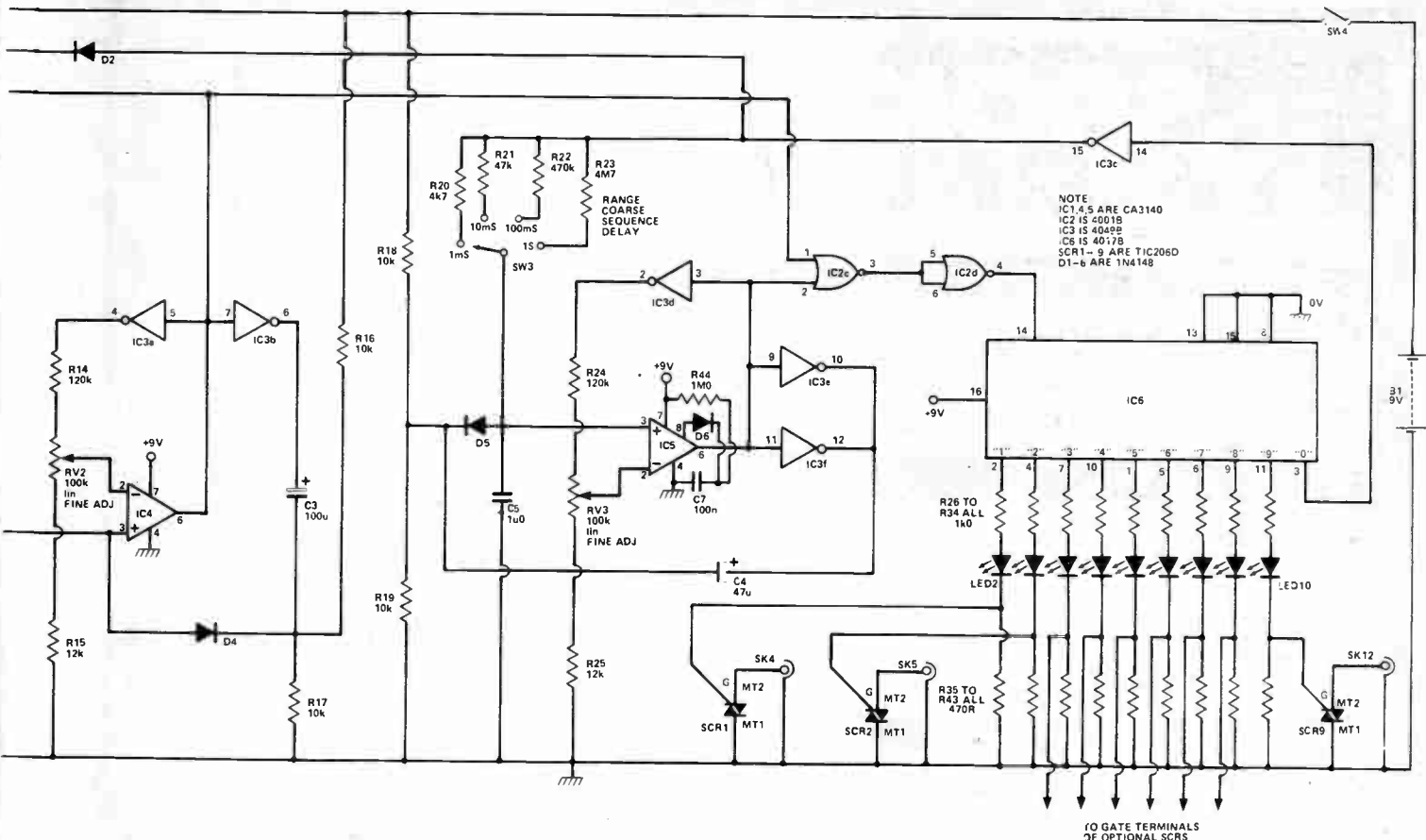


Fig.2 (left) Overlay for the sequencer. Some of the tags of SW2 and SW3 are cut off before mounting — the dots indicate which tags remain.

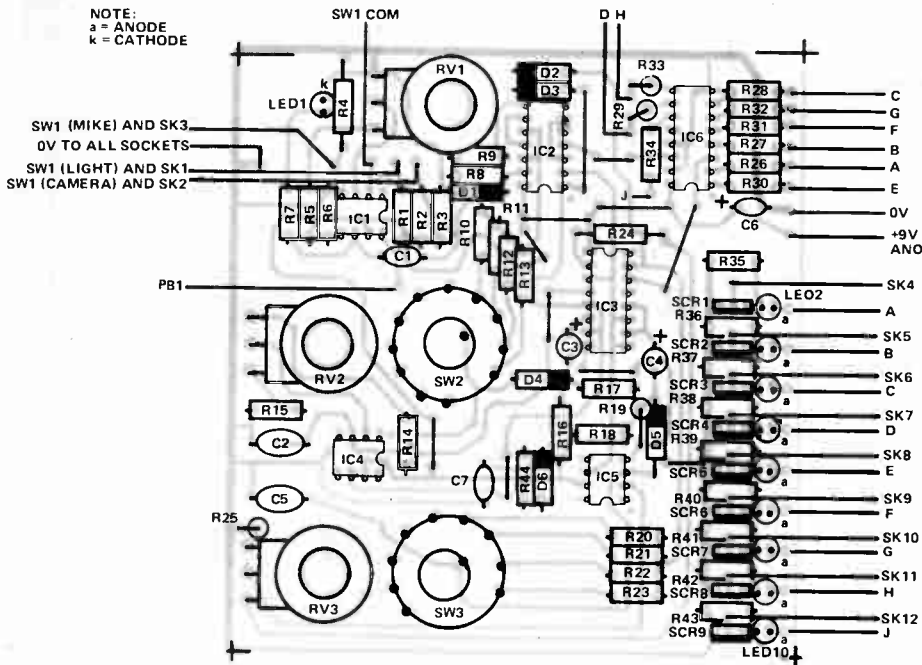

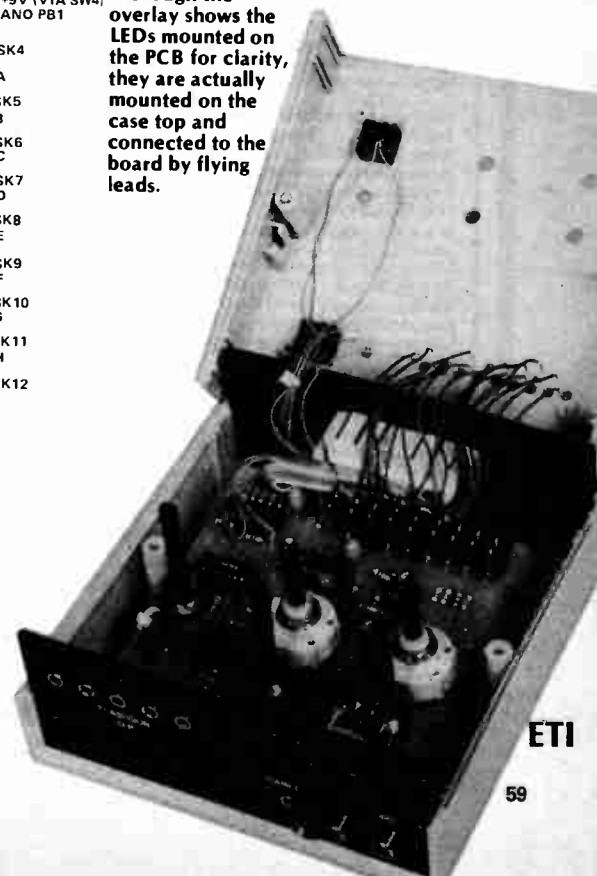Below: inside the sequencer. Although the overlay shows the LEDs mounted on the PCB for clarity, they are actually mounted on the case top and connected to the board by flying leads.



## BUYLINES

The 3 mm coaxial sockets (and a camera extension lead, if required), can be obtained from Vanguard Instruments, 233 High Street, Brentford, Middlesex. Telephone: 01-560 7667.

The case was chosen from the CM range offered by OK Machine and Tool Ltd, Dutton Lane, Eastleigh, SO5 4AA, telephone 0703 610944/5. The case order code is CM6-225.

PB1 and PB2 are available from Watford Electronics, and all the other components are common types and should cause no problems.



# electronics today international **BOOK SERVICE**

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

## BEGINNERS

Beginners Guide to Electronics Squires **£4.25**  
Beginners Guide to Transistors Reddihough **£4.25**  
Beginners Guide to Integrated Circuits Sinclair **£4.25**  
Understanding Electronic Circuits Sinclair **£5.10**  
Understanding Electronic Components Sinclair **£5.10**  
Beginners Guide to Radio King **£4.25**  
Beginners Guide to Audio Sinclair **£4.25**

## COOKBOOKS

TV Typewriters Cookbook **£7.75**  
CMOS Cookbook **£8.20**  
Active Filters **£11.30**  
IC Timer Cookbook **£7.65**  
IC Op-AMP Cookbook **£10.70**  
Video Cookbook **£5.50**  
ITL Cookbook **£7.55**  
The Basic Cook **£4.10**  
IC Converter Cookbook **£9.50**  
Master IC Cookbook Hallmark **£7.45**

## APPLICATIONS

How To Build Electronic Kits Chapel **£3.25**  
110 Electronic Alarm Projects R.M. Marston **£4.95**  
110 Semiconductor Projects for the Home Constructor R. M. Marston **£4.95**  
110 Integrated Circuit Projects for the Home Constructor R. M. Marston **£4.95**  
110 Thyristor Projects Using SCRs R. M. Marston **£4.95**  
110 Wave Form Generator Projects R. M. Marston **£4.95**

## COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book **£10.00**  
Beginners Guide to Computers and Microprocessors with Projects C. Adams **£6.05**  
BASIC Computer Games Ahl **£6.05**  
BASIC for Home Computers A self-teaching guide B. Albrecht **£6.60**  
Illustrating BASIC D. Alcock **£4.25**  
Troubleshooting to Microprocessors and Digital Logic Goodman **£5.90**  
Z-80 Microcomputer Handbook W. Barden **£7.75**  
How to Program Microcomputers W. Barden **£7.25**  
Introduction to Microcomputers and Microprocessors A. Barna **£9.50**  
Microprocessors in Instruments and Control R. J. Bibbero **£13.10**  
Basic BASIC J. S. Coan **£7.25**  
Advanced BASIC J. S. Coan **£6.40**  
Getting Acquainted with Microprocessors L. Frenzel **£7.25**  
Beginners Guide to Microprocessors C. M. Gilmore **£4.90**  
1001 Things to do with Your Personal Computer Sawusch **£6.00**  
Microprocessor Programming for Computer Hobbyists N. Graham **£7.15**  
Miniprocessors from Calculators to Computers Heiserman **£5.35**  
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn **£17.40**  
Microprocessor Systems Design E. Kingman **£18.80**  
Intro to Microprocessors Leventhal **£11.25**  
Microprocessor — Technology, Architecture & Applications D. R. McGlynn **£11.30**  
BASIC with Style P. Nagin **£4.50**  
Software Design for Microcomputers Ogdin **£9.25**  
Microcomputer Design Ogdin **£7.45**  
Microcomputer Base Design Peatman **£6.10**  
Hands on BASIC with a PET Peckham **£11.95**  
Complete Microcomputer Systems Handbook **£9.75**  
6800 Software Gourmet Guide and Cookbook Scelbi **£9.20**  
8080 Software Gourmet Guide and Cookbook **£9.20**  
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony **£8.35**  
8060/8085 Software Design Titus **£7.60**  
How to Design, Build and Program Your own Working Computer System **£7.10**  
Your Own Computer Waite **£2.25**  
Microprocessor/Microprogramming Handbook Ward **£6.20**

## LOGIC

Designing With TTL Integrated Circuits Texas Instruments **£10.95**  
How To Use IC Circuit Logic Elements J. Streater **£4.85**  
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston **£4.95**  
Understanding CMOS Integrated Circuits R. Meien **£4.60**  
MOS Digital ICs G. Flynn **£5.25**

## TEST INSTRUMENTS

The Oscilloscope In Use Sinclair **£4.00**  
Working with the Oscilloscope A. Saunders **£4.60**  
Servicing with the Oscilloscope A. King **£7.50**  
Radio Television and Audio Test Instruments King **£8.30**

## OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) **£9.20**  
110 Operational Amplifier Projects for the Home Constructor R. M. Marston **£4.95**  
Designing With Operational Amplifiers Burr Brown **£26.50**  
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) **£8.95**

## COMMUNICATIONS

Digital Signal Processing Theory & Applications L. R. Rabiner **£24.40**  
Electronic Communication Systems G. Kennedy **£8.95**  
Principles of Communication Systems H. Taub **£8.40**

## THEORY

Introduction to Digital Filtering Bogner **£12.25**  
Transistor Circuit Design Texas Instruments **£10.95**  
Foundations of Wireless Electronics M. G. Scroggie **£6.10**  
Electronic Circuit Design Handbook 4th Edition **£16.75**  
Master Guide to Electronic Circuits Adams **£9.25**

## REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner **£38.00**  
Electronic Components M. A. Colwell **£3.40**  
Electronic Diagrams M. A. Colwell **£3.40**  
International Transistor Selector T. D. Towers New update **£10.70**  
International FET Selector T. D. Towers New update **£4.60**  
International Op-Amp Linear IC Selector Towers **£8.00**  
International Microprocessor Selector (NEW) Towers **£16.00**

## MISCELLANEOUS

Electronic Fault Diagnosis Sinclair **£4.00**  
Printed Circuit Assembly Hughes & Colwell **£3.40**

Fallen behind recent advances?  
Just starting out?  
Need a decent reference book?  
**ETI Book Service** provides an easy way of getting your hands on the right title.

## DIGITAL THERMOMETER

This is one of our range of PROJECT KITS. The kit includes all the parts required to complete the project, including the case and battery. Calibration is simple and an accuracy of up to 1% can be obtained.

The instrument covers the range  $-50^{\circ}\text{C}$ . to  $+150^{\circ}\text{C}$ . Readout is on an LCD display. Powered by a 9V battery it is an ideal instrument for home or laboratory. Full building instructions included.

PROJECT KIT 800104 £26.50

**£3 off**

**SPECIAL SUMMER OFFER!!!**  
THIS KIT IS NOW ONLY £23.50 if ordered before September 30, 1981.

## PROJECT PACKS

These PROJECT PACKS include PCB, Components and data.

### AERIAL AMPLIFIER

Up to 20DB of gain on your TV or FM radio signal. Order TV or FM (VHF) version (80022) ..... £5.45

### DISCO LIGHT DISPLAY

Three lamps controlled by an audio filter/triac circuit. Ideal for Discos and Parties..... £5.80

### DRILL SPEED CONTROLLER

Controls the revs on your mains electric drill..... £4.80

### LOGIC ANALYSER

The first Analyser for the home constructor. Useful to track down problems in your digital systems. Send for full specification (81094)..... £87.25

### HIGH COM NOISE REDUCTION SYSTEM

Performs better than other tape noise reduction systems. Developed by Telefunken. Pack contains pre-built and tested modules (81117)..... £49.55

### IONISER

Generates negative ions for a real healthy atmosphere. Easy to build (9823)..... £10.50

### SOUND EFFECTS GENERATOR

An experimental circuit that produces train, motorbike, and space noises. Lots of fun (81112)..... £8.30

### PROGRAMMABLE SLIDE FADER

Uses computer techniques for you to program, on tape, a slide show for two projectors. Fades and changes are reproduced automatically (81002)..... £46.50

### TALK FUNNY

Simple Ring Modulator circuit that distorts your voice, or musical instrument (80052)..... £10.00

### MINIMIXER

Mixer on a single PCB for two microphones, tape and two turntables. Ideal for Discos, etc. (81068)..... £37.50

## NEW SUMMER 1981 CATALOGUE - NOW AVAILABLE

Send a 14p stamp for your copy. Over 70 projects for you to build. Our comprehensive ranges of high-quality components, integrated circuits and hardware are listed. Lots of ideas for your hobby in 44 pages of information. SEND FOR YOUR COPY NOW.

### HOW TO ORDER

Send a cheque or postal order to DORAM ELECTRONICS LTD. or write or phone your ACCESS account number. Please add 40p for postage and packing in the UK. All our prices include V.A.T. A telephone answering service is available outside our office hours.

**DORAM ELECTRONICS LTD.**  
FITZROY HOUSE, MARKET PLACE, SWAFFHAM, PE37 7QH



(0760) 21627



# Doram

ELECTRONICS LTD

ETI AUGUST 1981

# Has seven years of success gone to our heads?



**NEW IMPROVED**

## MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

### POPULAR HI-FI

"Switching to the Minimax's" from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." Comparative test **OCTOBER 1975**.

### HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" **JANUARY 1975**.

**PRACTICAL HI-FI & Audio**  
"The depth, clarity and openness of sound produced is quite astonishing". **JUNE '75**

### WHAT HI-FI

"... the ability of the Mini

max to take a lot of power and still sound good could be decisive" - Comparative test, **APRIL 1977**.

### PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". **JANUARY 1981**.

### Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.  
Frequency Response: 80Hz - 20KHz  $\pm 5\text{dB}$ .  
Finish: natural teak, veneer with black frets.  
Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.  
Weight: 4.1 Kgs (9 lbs) each.

**ONLY £69 95 A PAIR**

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

**VIDEOTONE**

98 CROFTON PARK ROAD  
LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4.

ET2

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

# DESIGNER'S NOTEBOOK

In this month's edition of Notebook, Ray Marston first looks at high impedance 'bootstrapping' techniques, and concludes by showing some unusual 4001B/4011B CMOS monostable and bistable circuits.

**B**ootstrapping is an in-phase (positive) feedback technique that can be used to greatly increase the apparent (AC) value of a resistor or reduce the apparent value of a capacitor. The technique is of particular value in the design of ultra-high input impedance AC amplifiers. We'll take a brief look at some practical examples of the technique in the first part of this edition of Notebook.

The easiest way to understand why the bootstrapping technique is needed is to look at the simple AC emitter follower circuit of Fig. 1. A major attraction of the emitter follower circuit is that it is capable of presenting a high input impedance to external signals, the actual impedance (looking into the base of the transistor) being equal to the product of the transistor  $h_{fe}$  (current gain) and the emitter load impedance ( $R_e$ ): thus, the base impedance of the Fig. 1 circuit is equal to 220k. In practice, however, the emitter follower circuit cannot work unless it is DC-biased in some way, and in Fig. 1 potential divider R1-R2 is used as the biasing network. Unfortunately, this network is effectively in parallel with the input (base) of Q1 and thus reduces the true input impedance of the circuit to a mere 10k or so. Not very good.

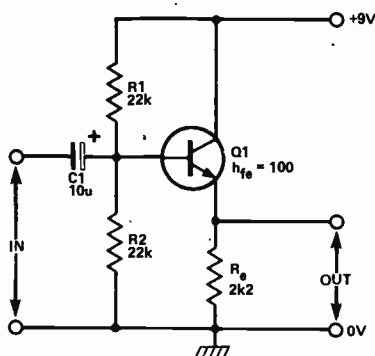


Fig.1 This simple AC emitter follower circuit has a true input impedance of only 10k or so.

Now look at Fig. 2, which shows how the so-called 'bootstrapping' technique can be used to raise the true AC input impedance of the circuit to nearly its theoretically-attainable maximum. Here, 22k resistor R3 is wired between the R1-R2 junction and the base of Q1, so the transistor is still correctly biased, and the AC input signal is fed directly to the base of Q1. The important point to note, however, is that the output of the emitter follower is AC-coupled back to the R1-R2 side of R3, so that in-phase AC signals appear on both sides of R3. What's the effect of this action?

ETI AUGUST 1981

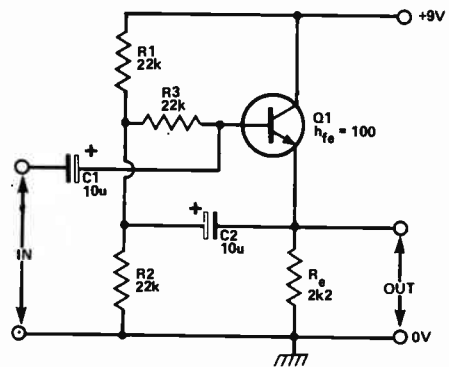


Fig.2 This 'bootstrapped' version of the AC emitter follower has a true input impedance of about 180k.

Suppose that our Fig. 2 emitter follower has an AC voltage gain of 0.98 (a reasonable figure). In this case, when an input signal is applied, all (100%) of the input signal appears on the 'base' side of R3, and an isolated but in-phase copy of this signal, with 98% magnitude, appears on the R1-R2 side. Consequently, the signal current flowing in R3 equals only 2% of that which would be expected from the original input signal alone. In other words, the AC input signal sees R3 as having a value of  $100/2 \times 22k$ , or 1M1: this impedance is in parallel with the base impedance of Q1, so the final input impedance of this bootstrapped emitter follower circuit works out at about 180k. Pretty good.

You can see, then, that the bootstrapping principle is very simple. By feeding an input signal to one side of passive component and a less-than-unity in-phase copy of the signal to the other side, the apparent impedance of the component can be increased. If 50% feedback is used, the impedance is doubled ( $100/50$ ), if 90% feedback is used, the impedance increases by a decade ( $100/10$ ). 99% feedback raises the impedance by a factor of one hundred ( $100/1$ ), 100% feedback raises the impedance to infinity. If bootstrapping is applied to a resistor, the apparent resistance is increased: if the technique is applied to a capacitor, the apparent capacitance value is reduced. Clever stuff.

## Bootstrapped Op-Amps

The basic bootstrapping technique can easily be applied to op-amp circuits, to produce non-inverting AC amplifiers with ultra-high input impedances, as shown by the examples of Figs. 3 to 7. In our first example (Fig. 3), the op-amp is biased by R1-R2 so that it can operate from a single-ended supply, and the input

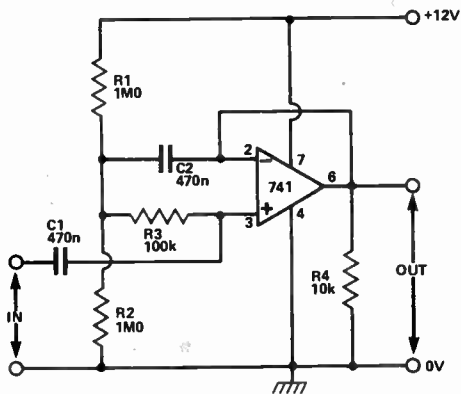


Fig.3 This single-supply version of the unity-gain non-inverting AC amplifier has an input impedance greater than 100M.

signal is AC-coupled to the op-amp side of R3 while the other side of this resistor is bootstrapped (via C2) from the output of the op-amp. The gain of the op-amp is so close to unity that the apparent (AC) impedance of R3 is increased to near-infinity, giving the circuit a true AC input impedance in excess of 100M. Without bootstrapping, the input impedance would be a mere 600k.

Note at this point that the attainable input impedance of the bootstrapped op-amp circuit is so high that in practice the true impedance is actually determined by the surface leakage impedance of the PCB and IC socket, etc. An easy way around this problem is to provide the area of the PCB surrounding the op-amp input pin with a 'guard ring', as shown in Fig. 4. This guard ring effectively bootstraps the leakage impedances of the PCB and raises them to near-infinite levels.

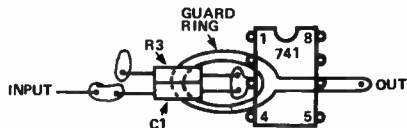


Fig.4 Method of providing a guard ring on the PCB, around the op-amp input terminal of the Fig.3 circuit, so that the PCB leakage impedances are effectively bootstrapped.

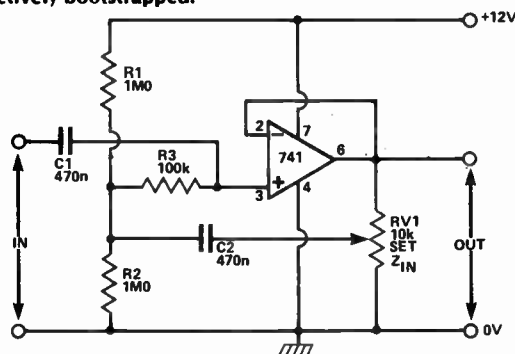


Fig.5 A variable input impedance unity-gain non-inverting AC amplifier. The impedance can be varied from 100k to 100M using RV1.

Figure 5 shows how the Fig. 3 circuit can be modified so that it acts as a variable-input-impedance circuit in which the impedance can be varied from roughly 100k to 100M using RV1. With RV1 slider set to the top of the pot, 100% bootstrapping is applied and the input impedance is 100M. With RV1 slider set to the bottom of the pot, zero bootstrapping is applied and R2 is bypassed to ground via C2, so the input impedance is about 100k.

Figure 6 shows how to bootstrap the unity-gain non-inverting op-amp circuit when operating it from split supplies. R1-R2 are the DC bias resistors, with R1 bootstrapped from the op-amp output via C2. The circuit has an input impedance capability of about 500M.

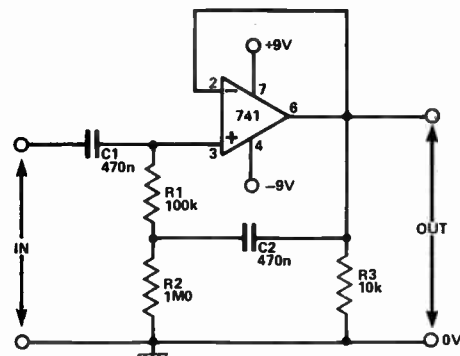


Fig.6 This bootstrapped split-supply unity-gain amplifier has an input impedance of about 500M.

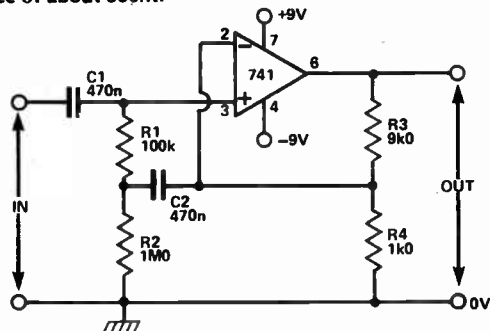


Fig.7 A high input impedance, x10 non-inverting AC amplifier. Note that the guard ring of this circuit (if used) should be taken from across R4 (not from the op-amp output).

Finally, Fig. 7 shows how to apply the bootstrapping technique to a non-inverting amplifier with a gain greater than unity. Here, the gain is determined by the R3-R4 values and equals 10 with the values shown. Note that the bootstrapping signal is taken from the output of R4, rather than directly from the op-amp output. Also note that if a guard ring is used on the PCB, it must be bootstrapped from the same source.

## Modified Monos

Now for a complete change of topic. If you've ever used the 4001B or 4011B CMOS ICs in the standard monostable configuration you'll know just how useful these circuits are in non-precision applications. They are easy to trigger, give clean outputs, and can cover a very wide timing range. The only trouble is, they're non-resettable; once they've been triggered they simply latch on until their timing periods end naturally. Figures 8 and 9 show a couple of easy ways of modifying these circuits to give easy reset operation.

Figure 8a shows the circuit of the conventional 4001B version of the standard monostable: with the R2 value shown, the circuit gives a timing period of about 0.5 s per microfarad of C1 value. The circuit is triggered by a positive-going input signal and generates a positive output waveform which is direct-coupled back to one input of IC1a to effectively maintain a 'trigger' input once the true trigger signal is removed.

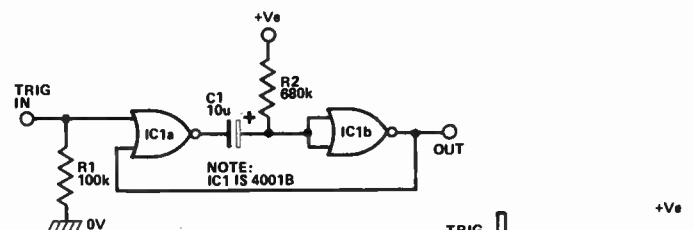
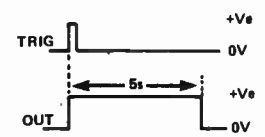
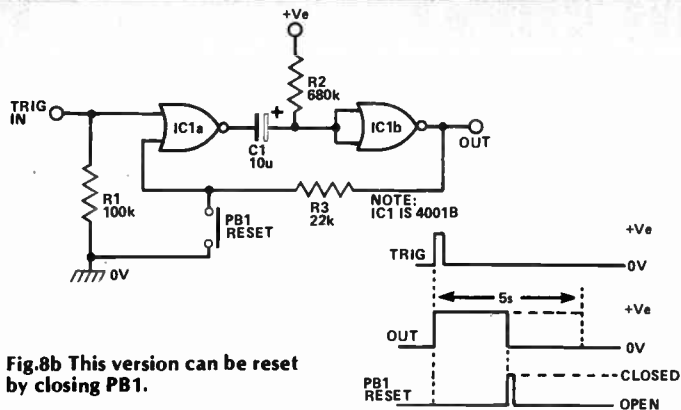
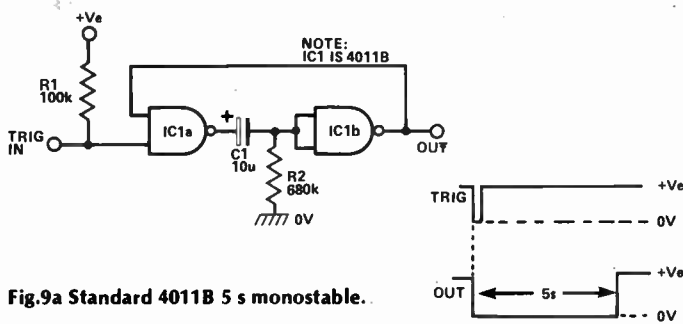


Fig.8a Standard 4001B monostable with a 5 s timing period.

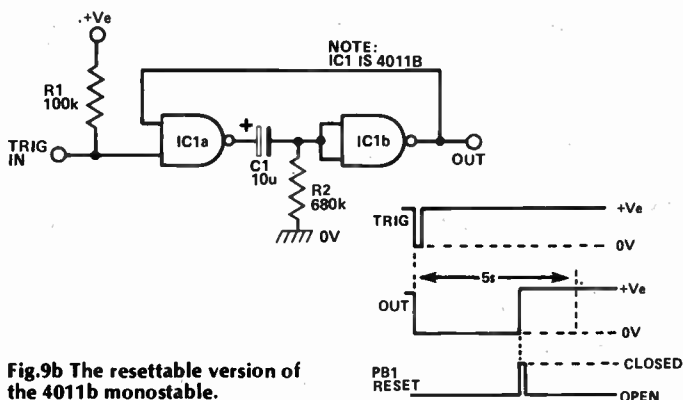





**Fig. 8b** This version can be reset by closing PB1.




**Fig. 9a** Standard 4011B 5 s monostable.



**Fig. 9b** The resettable version of the 4011b monostable.

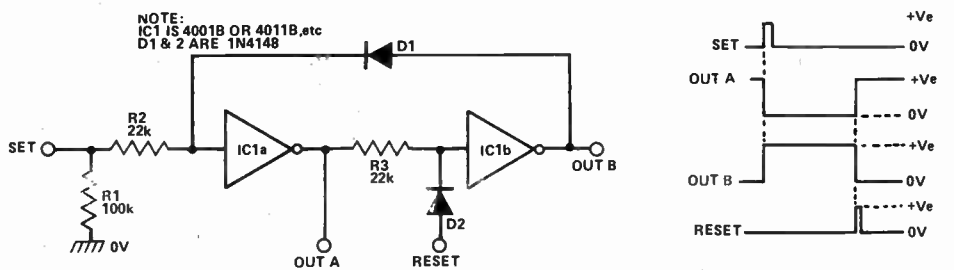

**Fig. 10** Positively-triggered bistable circuit.

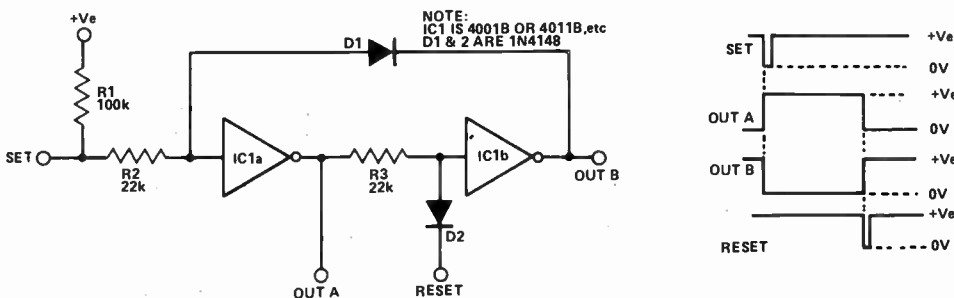

**Fig. 11** Negatively-triggered bistable circuit.

Figure 8b shows how the above circuit can be modified to give resettable operation. Here, the feedback connection from the IC1b output to the IC1a input is made via R3. Consequently, once the circuit has been triggered and the original trigger signal has been removed, the circuit can be reset at any time by simply pulling the feedback input of IC1a to ground. In the diagram we've shown this reset function accomplished using a simple push-button switch, but in practice it can be done using a gated transistor or CMOS switch, for example.

Figure 9 shows the 4011B version of the monostable unit, with the standard design in (a) and the resettable version in (b). Note here that the circuit is triggered by a negative-going input pulse and generates a negative or low output waveform.

## New-fangled Flip-flops

Finally, to complete this edition of Notebook, Figs. 10 and 11 show a couple of unusual CMOS bistable circuits, each capable of being built using simple CMOS inverters or inverter-connected 4001B or 4011B gates. You'll sometimes find in project design that at some stage you'll have a couple of 'spare' 4001B or 4011B gates in a circuit, and at the same time need to use a simple bistable in the design, only to find that the spare gates are not compatible with the kind of bistable operation that is needed. The conventional 4001B bistable, for example, needs positive set and reset pulses, while the 4011B bistable needs negative set and reset pulses. The Fig. 10 or 11 circuits may solve your problems in such cases.

The operation of Fig. 10 circuit is pretty simple. Normally, the input of IC1a is held low by R1, the output of IC1a and the input of IC1b are high, the output of IC1b is low, and the circuit is in a stable state. If a positive 'set' pulse is momentarily applied across R1, the output of IC1b flips high and D1 then pulls the direct input of IC1a high and latches the circuit into this state, irrespective of subsequent actions of the set signal. The circuit can be reset by momentarily applying a positive pulse to the input of D2, thereby driving the output of IC1b low and latching the circuit back into its original state. Note that this circuit is triggered (set and reset) by positive-going input signals.


Figure 11 shows an alternative version of the bistable circuit, which in this case is triggered by negative-going inputs. The circuit is similar to that of Fig. 10, except that the polarities of the two diodes are reversed and the input of IC1a is normally biased high by R1. Note that both of these circuits have two outputs, thus providing either type of output polarity.

# CHROMASONIC electronics

48 JUNCTION ROAD, ARCHWAY LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes  
 TELEPHONE: 01-263 9493/01-263 9495

## YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPUTERS

### PET



**4008 8K RAM**  
**4016 16K RAM**  
**4032 32K RAM**  
**4040 Dual Drive Disk**

The new PET printer.  
**A** 4022 80 column tracks feed.  
**B** 3023 80 column friction feed.  
**C** C2N Cassette Unit.  
 For the business man we stock the 8000 range inc 8032 and 8050 with daisy wheel printers coming soon.

PHONE FOR MOST COMPETITIVE PRICES WORD PROCESSING AND 32K SYSTEMS PHONE FOR DETAILS

### UK101

**DOWN IN PRICE**

UK101 Kit £149  
 Ready Built £199  
 Complete in case £225  
 4K Expansion 8x2114 £14  
 Memory Expansion Kit 8K £79.95  
 16K £106.95  
 Printer Interface £29.95  
 Sound generator plus PIO kit £29.95  
 Cases £24.50

**NEW**  
 Chromasonics Sound Kit £24.95  
 Colour Kit £84.95

Inc Demo Tape & Full Documentation Send for details



### VIDEO GENIE



**£279 EG3003**

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features. Simply plugs into monitor or UHF TV. With V.U. Meter.

PARALLEL PRINTER INTERFACE INC CABLE £33.00  
 CHROMASONICS PROGRAMMABLE SOUND KIT £24.95  
 SOUND KIT (FITTING EXTRA) £7.00  
 LOWER CASE KIT (FITTING EXTRA) £27.50  
 COLOUR KIT £34.95  
 EXPANSION BOX WITH/WITHOUT RS232 £215/£185  
 16K/52K RAM CASE £94/£129

### APPLE

**APPLE II PLUS**  
 Complete Systems

16K Machines £549.00  
 32K Machines £579.00  
 48K Machines £595.00

Disk Drive with Controller £349.00  
 Disk Drive without Controller £299.00

Accessory cards, Software all available — Phone for Details



### PRINTERS



Interfaces and Cables for APPLE II, PET, TRS80, RS232, UK101, Sharp Superboard All Available.

**EPSON MX80 £359**  
 Dot-matrix printer with Pet graphics interface. Centronics parallel and serial. Pet and Apple compatible. True bidirectional, 80 cps.

**EPSON MX80 FT/1 £399**  
 Dual single sheet friction and tractor feed, 9 wire head, true descenders.

**EPSON-MX FT/2 £449**  
 An FT/1 with high resolution graphics.


**EPSON MX70 £259**  
 Tractor feed, 7 wire head, high resolution graphics.

**SEIKOSHA GP80A £199**  
 Dot matrix 5x7, 80 columns, 30 cps graphics, double width characters.

JUST PHONE FOR FURTHER DETAILS
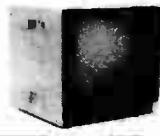
### MONITORS

EG100 12" Black & White £65.00  
 MONI9" (illust) B&W £82.00  
 Hitachi professional monitors  
 9" Black & White £99.95  
 12" Black & White £149.00



### VIC 20

**Colours**  
 24 total. 8 for characters, 8 for border, 16 for screen mixed as you wish. Basic colours on program keys are black, white, red, blue, light blue, green, yellow and purple.


**Sound**  
 3 Tone Generator for music, "White Noise" Generator for language and sound effects. Each Generator gives 3 octaves. Reproduction is through TV speaker.

**Character/Line Display**  
 22 Characters by 23 lines, 64 ASCII characters, pet-type graphic character set.

**Keyboard**  
 DIN typewriter keyboard with 8 programmable function possibilities via 4 special function keys. Colours are directly addressable from the keyboard.

**Peripherals/Accessories**  
 VIC Datas cassette with special interface to guarantee high reliability read/write quality (PET/IBM compatible).  
 VIC 1515 — Low cost VIC DOT Matrix printer.  
 VIC 1540 — Single disk unit with 170K Byte capacity.

Price only £165.00. Cassette with 6 free programmes only £34.75.



### TANTEL

**PRESTEL BY TANTEL**  
**COMMUNICATIONS AT YOUR FINGERTIPS FOR BUSINESS & HOME. UP TO DATE INFO**

180,000 pages of information on Travel, News, Investment, Holidays, Hotels Etc., Etc.

**£170**  
 TANTEL IS POST OFFICE APPROVED. SEND FOR DETAILS.  
 DEMONSTRATION AVAILABLE AT OUR SHOWROOM.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost. All other items P&P 30p. Place your order using your Access or Barclaycard (Min. tel. order £5). Trade and export enquiries welcome. Official orders welcome.



# HAND CLAP SYNTHESIZER



Does your snare drum suffer from nervous skin tension, lack of timbre? Then revive it with the ETI Hand-clap Synthesiser. Designed to simulate the staccato effect of multiple hand-claps, the unit can be triggered by a microphone or footswitch. Design by Roger Shore. Development by Steve Ramsahadeo.

It would seem that no disco record is complete without the familiar hand-claps that faithfully accent the snare drum's down beat. One can imagine a group of people centred around a studio microphone, palms reddening, acting like human metronomes. We are happy to report that such a form of torture is now unnecessary in this electronic age!

It's generally accepted that the advent of the synthesiser in the late 60s was the commercial starting point of electronic music, not so much in the way of percussive synthesis but with such effects as tremolo, fuzz, flanging, reverberation and phasing, all of which are added to give expression to a piece of music.

## Synthetic Control

The reproduction of synthetic voices, be it in digital or analogue form, requires precise control of all levels contributing to the original make-up of the sound. Musicians, producers and arrangers are continually striving for new creative sounds, and the pressure eventually falls on the engineer who is called upon to wave his magic wand and come up with the latest synthetic sound which will send the fans wild.

As in any new venture, whatever approach is used will be an expensive one. At present there are some systems commercially available. The Fairlight CMI (Computer Musical Instrument) is one, retailing at around £15,000 with its sophisticated electronics and hardware. It can create any musical sound you care to name. With such technology available creativity is limited only by the operator. However, if you prefer a dedicated instrument the LM1 Drum Computer can offer some interesting prospects. The unit is programmable, capable of accepting 100 drumbeats in real time, and there are real drum sounds — digital recordings stored in computer memory. Twelve percussive voices are provided (all tunable in pitch), there are facilities for versatile editing, a 'human' rhythm feel is made possible by special timing circuitry, and so the list goes on.

It is therefore not surprising that when designing the ETI Hand-clap Synthesiser some ground work was required.

## No Applause Please

Multiple or 'ensemble' hand-clapping may be analysed subjectively in two distinct sections:

1. A general 'crash' — which may be simulated with a short burst of tuned noise.
2. Individual claps — this can be simulated by generating pulses which cause a multiple feedback band-pass filter to ring. Several different combinations of individual claps were

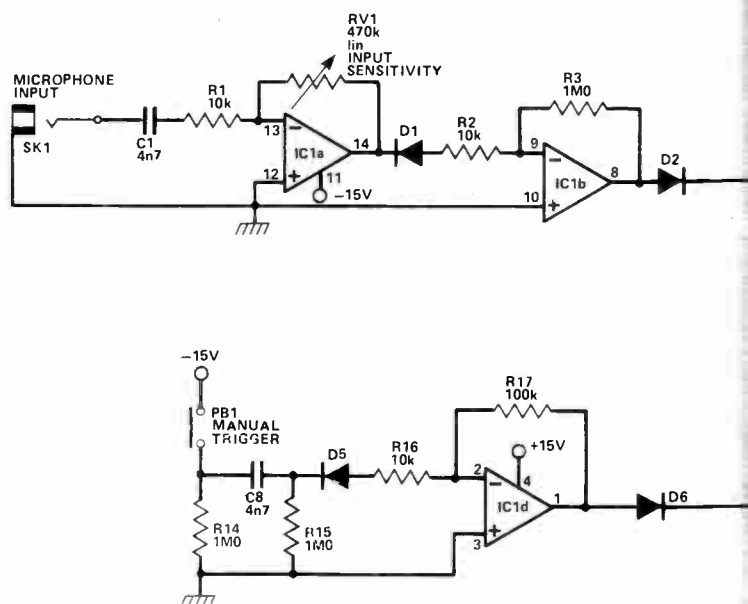


Fig.1 Circuit diagram of the Hand-clap Synthesiser.

## HOW IT WORKS

tried from one to seven, at both regular and irregular intervals, but two provided the best subjective results.

Setting up a unit such as this will depend on personal preferences and also on the type of amplifying system used. It is preferable to use a unit with reverberation where possible as this will greatly enhance the effect.

The problem of which variables should be external and which should remain preset is also one of personal taste. As circumstances dictate different settings we decide to make all seven controls external.

## Construction

No problems should be encountered in constructing the Hand-clap Synthesiser. The power supply section should be built first; care should be taken to sleeve the mains terminals on the PCB and the on/off switch.

When this is completed, connect a voltmeter across the output pins of the supply. A reading of +15 V and -15 V should be available at the output. If all is well the rest of the control circuit can be constructed observing the usual CMOS handling procedure and the orientation of polarised components.

The unit can be triggered from either a momentary push-button (PB1) or from a suitable transducer, eg a microphone placed near a snare drum.

In the first case, pressing PB1 causes a negative-going pulse to be developed across C8. This is steered via D5 to the inverting input of IC1d, causing a positive pulse to appear at the cathode of D6.

Alternatively, an input signal from a microphone is differentiated by C1 and R1. This prevents false triggering from other nearby sources. The signal is amplified and inverted by IC1a with RV1 acting as a sensitivity control. Further inversion by IC2b is required to provide a positive pulse at the cathode of D2. These trigger pulses appearing at the cathodes of D2 or D6 are fed to both the anode of D3 and pin 1 of IC2a.

When D3 is forward biased by the trigger pulse it allows C3 to charge positively. The rate of discharge is determined by R5 and the setting of RV2; this ramp is buffered by IC1c, the output of which is connected to D4 and C4 via R8.

The base-emitter junction of Q1 is reversed biased to produce the required noise. A low noise transistor is chosen to give a cleaner noise source. This noise is amplified by IC3a and fed to the cathode of D4. When a trigger pulse causes a positive ramp to appear at the output of IC1c, D4 conducts allowing noise to pass via D4 and C4 to the band-pass filter formed by IC3b and associated components. The length of this noise pulse is determined by the setting of RV2, the ramp discharge time.


R9 normally holds the anode of D4 at approximately -1V5 to prevent noise peaks from turning D4 on intermittently.

The band-pass filter is tuned over the 'useful' part of the noise spectrum for this application. Although the Q of the filter network will vary (because RV4 is not 'ganged' with R10), this does not pose any problem in this non-critical situation.

At the same time as the noise pulse is generated, the trigger pulse is applied to pin 1 of IC2a, turning on the monostable formed by IC2a and IC2b and allowing pin 10 to assume a high state. This positive voltage is developed across C10, causing the band-pass filter formed around IC3c to ring at a frequency determined by the position of RV5. (The two band-pass filters are of identical design.) At a time determined by RV3 and C9 the monostable will reset and the negative-going edge at pin 10 of IC2b allows a second ringing pulse to be generated by the band-pass filter. These two ringing pulses are the individual claps and are mixed with the noise pulse via the balance control RV6 and through R23, R24 to the output amplifier IC3d.



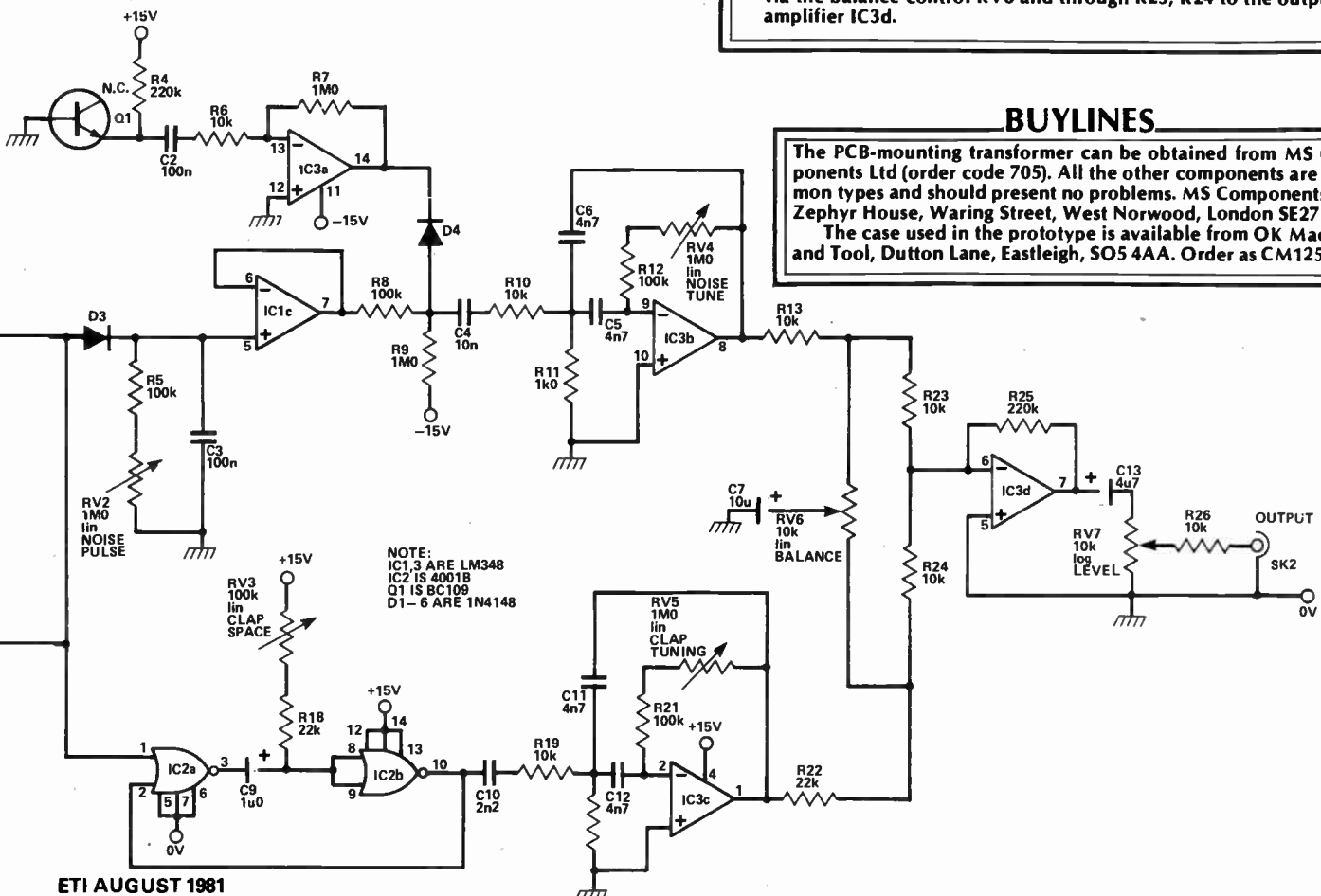Back panel of the synthesiser. Sockets are provided for the manual trigger (an external footswitch) or a microphone, triggered by the snare drum for example.




## BUYLINES

The PCB-mounting transformer can be obtained from MS Components Ltd (order code 705). All the other components are common types and should present no problems. MS Components Ltd, Zephyr House, Waring Street, West Norwood, London SE27 9LH. The case used in the prototype is available from OK Machine and Tool, Dutton Lane, Eastleigh, SO5 4AA. Order as CM125-225.






# PROJECT : Clap Synth

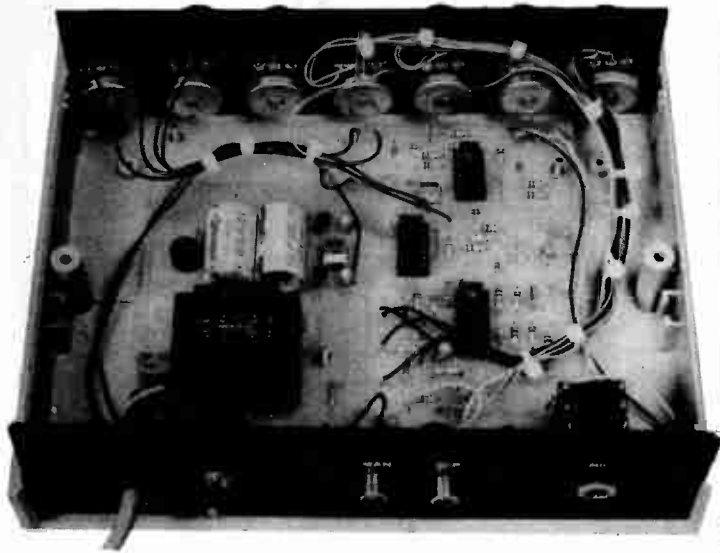

The Hand-clap Synthesiser with the lid removed. The sockets and switch mount on the rear panel, and the potentiometers and LED on the front; all the other components, including the mains transformer, fit onto the single PCB, making construction extremely easy. Follow the overlay and this photograph when interwiring and position the wiring looms exactly as shown, in order to minimize hum and noise. Plastic cable ties will keep everything neat and tidy.

ETI
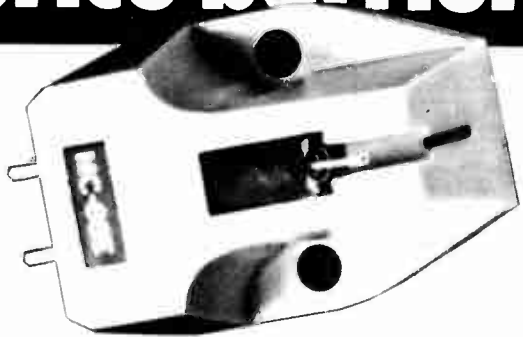
# A moving coil cartridge that breaks the price barrier!



## the new MC88E from CORAL

The new MC88E represents a breakthrough in high output moving coil cartridges. No step-up device or amp is required and it is available at a sensational price of only £39.95.

The high output voltage of 2.5mV does away with the need for a head amplifier or step-up transformer, which add to the expense of using most previous moving coil cartridges.

We can't emphasise enough, just how advanced the technology that has produced this breakthrough is – a miniaturised and specially shaped armature; unique coil winding technique; a magnet that is so compact,

yet generating high magnetic flux density; compliance of 17 cu's. The result is a cartridge with flat frequency response over the super wide range of 20Hz - 40KHz, removing the distortion caused by certain frequencies, which can be found in many conventional cartridges. Coral's considerable experience in moving coil cartridges has enabled them to offer the ultimate in quality and performance at this incredibly low price.

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

**VIDEOTONE** 98 CROFTON PARK ROAD LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. ET2

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

BELLS & HOUSINGS-CAR ALARM-CARAVAN ALARM-CONTACTS

CONTROL PANELS-PRESSURE MATS-SIRENS-WINDOW FOIL-ETC

## BURGLAR ALARM EQUIPMENT FOR THE D.I.Y. MAN

**LINTON**  
ELECTRONICS

4 HELSTON CLOSE, LINTON,  
BURTON ON TRENT, STAFFS. DE12 6PN  
PHONE: BURTON (0283) 761877  
24 Hour Phone Answering Service

ETI AUGUST 1981

## VLF/TR DISCRIMINATOR AT NEW LOW PRICE

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



**Shadow VLF/TR.** Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target: now you can reject nails bottle caps even aluminium foil and ring pull tins! Full ground effect exclusion over normal or high permeability soils. The head is thermally and capacitively shielded. 4 modes: despeaking VLF plus 3 TR discriminating ranges. Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI. Complete kit now only **£75.00** inc. VAT & post!! (Was 287.67).

**Shadow TR/VCO**

Individual parts: Search head £27.33 PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10. LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

**Shadow TR/VCO.** An advanced version of the TR/18. Use as a sensitive 18 machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. SORRY — SOLD OUT.

Matching stereo headphones for all Shadow models £7.50 inc. VAT and Post.

**Shell Kit.** Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £14.48 inc. VAT and Post.

# ALTEK

(ETI), 1 Green Lane  
Watton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please.  
Phone (0443 22) 44110 anytime.

## S & M (ANGLIA) LTD.

**SPECIAL THIS MONTH** due to bulk purchase direct from country of origin:

- ★ Digital Multimeters from £20.
- ★ Digital Car Tune-Up Kits.
- ★ Electronic Speed Alert.
- ★ CB Accessories.

Trade enquiries welcome. Special terms for new businesses. Monthly delivery free. No extra charge.

Please rush me a FREE catalogue and further details.

Name.....

Address.....

ETI 8-81

## S & M (ANGLIA) LTD.

QUEEN SQUARE, HAVERHILL, SUFFOLK  
Tel. 0440 61419. Telex 995801 GLO TLS8

## NEW DISTRIBUTORS WANTED

For your FREE Catalogue  
Send 30p to cover P&P

### WK-7 INSERTION EXTRACTION KIT



**EX2**

CMOS SAFE DIP I.C. EXTRACTOR TOOL

### MOS 2428

MOS-2428 24-28 PIN, MOS, CMOS SAFE INSERTER



**MOS 40**

MOS-3640 36-40 PIN CMOS SAFE INSERTER

For highly sensitive MOS & CMOS I.C.'s. Ground strap may be easily attached. Durable chrome plated ABS construction features precision parts for long life and easy one-hand operation.

### MOS 1416

MOS-1416 14-16 PIN, MOS, CMOS SAFE INSERTER



**EX1**

EXTRACTOR TOOL

# ELECTROWARE\*

DUTTON LANE EASTLEIGH SO5 4AA TEL(0703)610944/5

AVAILABLE FROM ALL LEADING ELECTRONIC DISTRIBUTORS

Cobbles Ltd., London. 01-699-2282  
Microdigital Ltd., Liverpool. 051-227-2535  
Electronica CG Ltd., Manchester. 061-788-0656  
Spectron Electronics (Manchester) Ltd., Salford. 061-834-4583

Jee Distribution Ltd., Middlesex. 01-897-3429

Watford Electronics Ltd., Watford. 0923-37774

Technomatic Ltd., London. 01-452-1500

Transam, London. 01-402-8137  
A. Marshall (London) Ltd., London. 01-624-0805  
Interface Components Ltd., Amersham. 02403-22307  
New Bear Computing Store Ltd., Newbury. 0635-30505

\* A DIVISION OF OK MACHINE & TOOL UK LIMITED

# Self Instruction Courses from Cambridge Learning


They're faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction — you know that you are learning and without mindless drudgery. With a good self-instruction course you become the world's best teacher.

## MICROCOMPUTERS ARE COMING— RIDE THE WAVE! LEARN TO PROGRAM!

MILLIONS OF JOBS ARE THREATENED, BUT MILLIONS MORE WILL BE CREATED
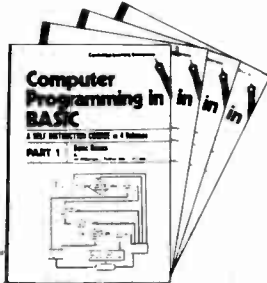
### LEARN BASIC

The language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flow-charting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest, and computer games.



### COMPUTER PROGRAMMING IN BASIC (CPB) 4 Vols. £10.50

**Book 1** Computers and what they do well: READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.  
**Book 2** High- and low-level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.  
**Book 3** Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.  
**Book 4** Advanced BASIC: subroutines; string variables; files; complex programming; examples; glossary.

### THE BASIC HANDBOOK (BHB) £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

### A.N.S. COBOL (ANS) £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

### Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here, as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


### THE ALGORITHM WRITER'S GUIDE (AWG) £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

## JOIN THE DIGITAL REVOLUTION!
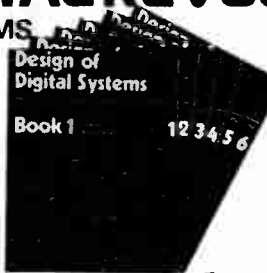
### DESIGN OF DIGITAL SYSTEMS (DDS) 6 Vols. £14.00

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers



**BOOK 1** Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems. **BOOK 2** OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic. **BOOK 3** Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division. **BOOK 4** Flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMS and RAMS. **BOOK 5** Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding. **BOOK 6** CPU; memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems.

Digital calculators and watches came in during the 1970's. Soon you will see digital cash cards, telephones, car instruments, and TV messages from your friends.

### DIGITAL COMPUTER LOGIC AND ELECTRONICS (DCL) 4 Vols. £8.50

A course covering the material in *italics* on the left, but at a slower pace. (4 vols)



**GUARANTEE** — No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition within 28 days. Our free booklist is sent with each order.

## CAMBRIDGE LEARNING LTD. (Registered in England No. 1328762)

Unit 15, Rivermill Site, FREEPOST, St. Ives, HUNTINGDON, Cambs PE17 4BR. Phone 0480 67446

## Order Form

To: Cambridge Learning Ltd., Unit 15, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

PLEASE SEND: Quantity

CPB (£10.50)   
BHB (£11.50)   
ANS (£5.90)   
AWG (£4.00)   
DDS (£14.00)   
DCL (£8.50)

THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL: Europe, North Africa, Middle East, add 1/2 to price of books. Japan, Australia, New Zealand, Pacific Islands add 3/4. Elsewhere add 1/2.

U.K. Delivery: up to 28 days (or send 60p per item for 1st class post)

Name .....

Address .....

Phone No. ....

### FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Credit our Giro Account No. 278 9159
- 4) Please charge my Access/American Express/Barclaycard/Diners/Visa/Mastercard/Trustcard

Card No. ....

Expiry Date .....

Signed .....

Or phone us with these credit card details on 0480 67446 (24 hour ansafone service)

# SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1981 . . . . . available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.25 we'll send you twelve issues of ETI.

To claim your years' supply of ETI, send your PO or cheque direct to :

ETI Subscriptions Department,  
513 London Road,  
Thornton Heath,  
Surrey CR4 6AR.  
Tel: 01-684 3157.



## IT'S A DOGS LIFE!

Mighty mongrel strikes again!



Stop your powerful pooch carving up your carefully collected ETIs with his canine choppers and live in hardback harmony with a profusion of precious project books by armour-plating your archives.

Invest in an ETI binder. You know it makes sense. You can have any colour you like as long as it's black.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

EASIBIND LTD., 4 UXBRIDGE STREET,  
LONDON W8 7SZ. Tel: 01-727 0686

Please allow 3/4 weeks for fulfillment of order.

**it's easy with EASIBIND**

Easibind Ltd., 4 Uxbridge St., London, W8 7SZ.

Nat. Giro No. 5157552.

### Order Form

ELECTRONICS TODAY INTERNATIONAL

I enclose p.o./cheque value .....

for ..... binders

Years required .....

BLOCK LETTERS PLEASE

Name .....

Address .....

.....

.....

Date .....

Registration No. 307469



The input board. The input and output sockets are all PCB-mounting and connections to the panel board are made via multiway cable and a Molex connector.

## BUYLINES

A complete set of parts for this project, including fully finished metalwork, nuts, bolts etc, will be available from Powertran Electronics for £97.50 plus VAT for the mixer and £9.90 plus VAT for the power supply, post free. For delivery by Securicor add £2.50 (VAT inclusive). Powertran also supply the separate parts for the mixer, eg metalwork set, PCB, semiconductors etc. Telephone Andover 64455 or write to Powertran Electronics, Portway Industrial Estate, Andover, Hants SP10 3NM.

## PARTS LIST

## Resistors (all 1/4 W, 5%)

R1,12,32,34,52,53,99,117,142,	47k
160,162,164,170,172,176	
R2,13,33,35,69	1k0
R3,5,14,16,29,30,36,38,87,152	1M0
R4,15,31,37,51,54,89,97,143,	100k
179,180,182,188,189,191,199,	
206	
R6,17,28,39,50,55,144	5k6
R7,8,18,19,26,27,40,41,48,	390R
49,56,57,145,147	
R9,11,20,22,23,25,42,44,45,47,	10k
58,60,61,62,67,98,101,106,107,	
108,109,110,111,112,113,114,	
115,119,124,125,126,127,128,	
129,130,131,132,134,146,148,	
158,165,166,171,202,203	
R10,21,24,43,46,59	6k8
R63,71,81	1k3
R64,65,72,73,79,80	1k8
R66,70,82,95	68k
R68	2k0
R74,83	8k2
R75	130k
R76	39k
R77	36k
R78	1k2
R84,175	2M2
R85,86	10M
R88,92,93,94,100,102,105,116,	150k
118,120,123,135,163	
R90	820R
R91,181,183,190,192	200k
R96	560k
R103,104,121,122,154,156,	18k
169,174	
R136,139,149,177	22k
R137,138,140	27k
R141,173	1k5
R150,184,193	2k2
R151,153	330k
R155,197,204	220k
R157	180R
R159,178,185,194	4k7
R161	470k
R167	12k
R168	33k
R186,195,198,205	3k3
R187,196	47R
R200,207	2R7
R201,208	15R

Note that R133 is not used

## Potentiometers

RV1	100k dual antilogarithmic rotary
RV2	10k logarithmic rotary
RV3	10k linear rotary
RV4	10k dual linear rotary
RV5	10k logarithmic slider
RV6,7,8,9,10	100k dual linear slider
RV11	47k dual logarithmic slider
RV12,13	47k logarithmic slider
PR1,3,5,7	1k0 miniature horizontal preset
PR2,4,6,8,10,11,12	220R miniature horizontal preset
PR9	470k miniature horizontal preset
PR13	4k7 miniature horizontal preset
PR14,15	22k miniature horizontal preset

## Capacitors

C1,8,21,22	47p ceramic
C2,9,20,23,29,30,40,111,112	10u 16 V tantalum
C3,10,19,24	3n3 polycarbonate
C4,11,18,25	680p ceramic
C5,12,17,26,31,34,37,38,39,41,	100n polycarbonate
55,80,82,92,95,100,103,105	
C6,13,16,27,32,35,75,76,78,81,	1u0 35 V tantalum
89,90	
C7,14,15,28,33,36,50,51,64,65	1n0 polycarbonate
C42,56,87,88	15n polycarbonate
C43,45,57,59	680n polycarbonate
C44,47,58,61,84,85,86	150n polycarbonate
C46,60	33n polycarbonate
C48,52,62,66	8n2 polycarbonate
C49,63	39n polycarbonate
C53,67	470p ceramic
C54,68	2n2 polycarbonate
C69	2u2 16 V tantalum
C70,91,93,96	470n 35 V tantalum
C71,73	220n polycarbonate
C72,74	100p ceramic
C77,99,106	4u7 16 V tantalum
C79,83	4n7 polycarbonate
C94,97,101,102,104,107	220u 16 V electrolytic, PCB type
C98,108	22n polycarbonate
C109,110	2200u 25 V axial electrolytic
C113,114	47n 50 V disc ceramic

## Semiconductors

IC1,3,4,6,7,11,12,13,18,19,20,	RC4558
21,22,23,24,25,26	
IC2,5,8,10	LM13600
IC9,15,27	741
IC14,16,17,28,31,33	1458
IC29	TL081 or equivalent
IC30	LM1877N-9
IC32,34	LM3915
IC35	7812
IC36	7912
Q1-7	BC212L
Q8	BC182L
D1-24	1N4148
D25-28	1N4002
ZD1	6V2 400 mW
LED1-3,5-13,15-23	0.2" red LEDs
LED4,14	0.2" green LEDs

## Miscellaneous

SW1,2,5,6	DPDT slide switch
SW3	four-pole three-way rotary switch
SW4	SPDT toggle switch
SW7	three-pole four-way rotary switch
SW8	push-to-make non-locking switch
SK1,2,5	five-pin DIN sockets (PCB type)
SK3,4	1/4" mono jack socket (PCB type)
SK6	1/4" stereo jack socket (PCB type)
SK7	1/4" stereo jack socket

Transformer (15-0-15 @ 300 mA), fuse (500 mA), fuseholder, mains lead, cabinet, knobs to suit, eight-pin DIL sockets (27 off), 16-pin DIL sockets, (four off), 14-pin DIL socket (one off), 18-pin DIL sockets (two off), flexible multiway cable and Molex PCB plugs, mounting hardware to suit.


is controlled by a five section graphic equaliser with two octave spacing as well as a special beat lift device. A voice-over unit (ducking) has been included as well as an override function for interrupt announcements. The microphone input can also be modulated, at a variable rate, to produce growl effects. A monitor section with a stereo headphone output allows the operator to listen (pre-fade listen) to any of the music inputs. The level of the selected signal path is displayed on an LED PPM.

Voltage controlled amplifiers have been used to control the signal levels in all seven audio paths. They have the ability to produce automatic cross-fades and ducking, as well as reducing crosstalk. The signal is not transmitted anywhere until the control voltage is correct. Therefore it will not crosstalk until it has been faded up, and then it doesn't matter.


TABLE 1.

Noise chart for converting dBm into voltage.

0 dBm	775 mV <sub>RMS</sub>
-10 dBm	245 mV <sub>RMS</sub>
-20 dBm	77.5 mV <sub>RMS</sub>
-30 dBm	24.5 mV <sub>RMS</sub>
-40 dBm	7.75 mV <sub>RMS</sub>
-50 dBm	2.45 mV <sub>RMS</sub>
-60 dBm	77.5 uV <sub>RMS</sub>
-70 dBm	24.5 uV <sub>RMS</sub>
-80 dBm	7.75 uV <sub>RMS</sub>
-90 dBm	2.45 uV <sub>RMS</sub>
-100 dBm	7.75 uV <sub>RMS</sub>
-110 dBm	2.45 uV <sub>RMS</sub>

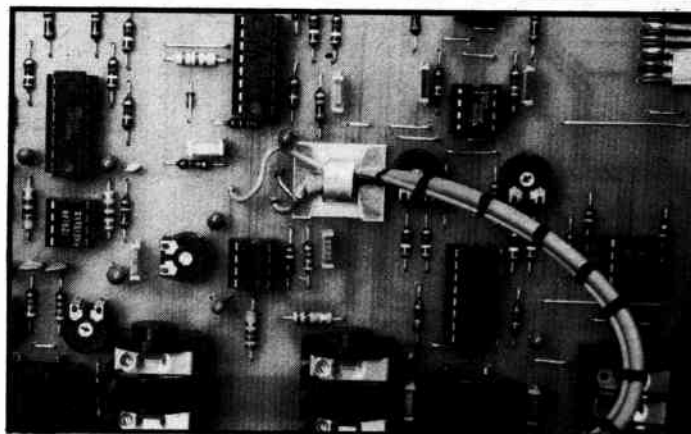

Close-up showing the wiring to Molex connector 'A' (on the input board).

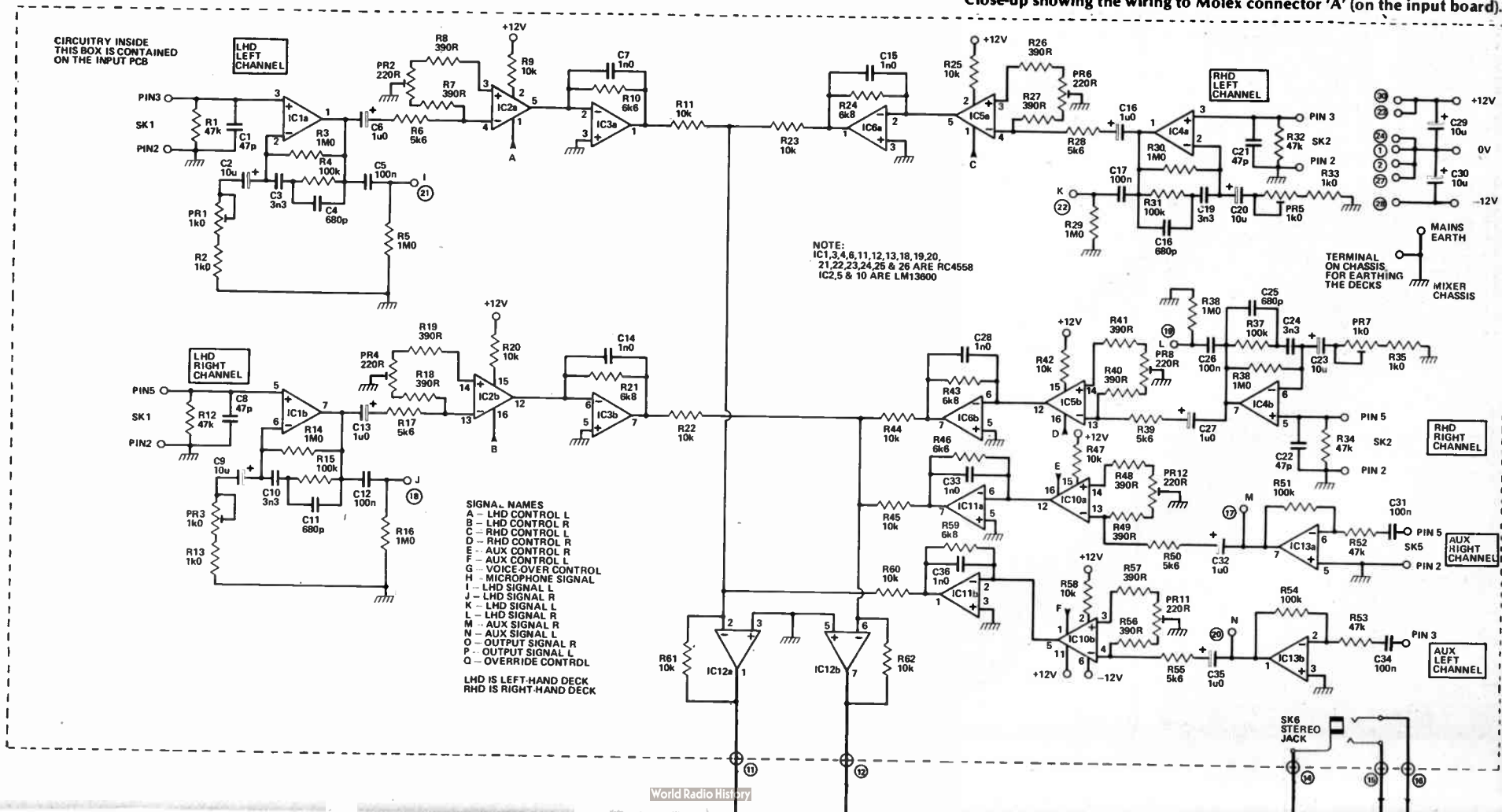

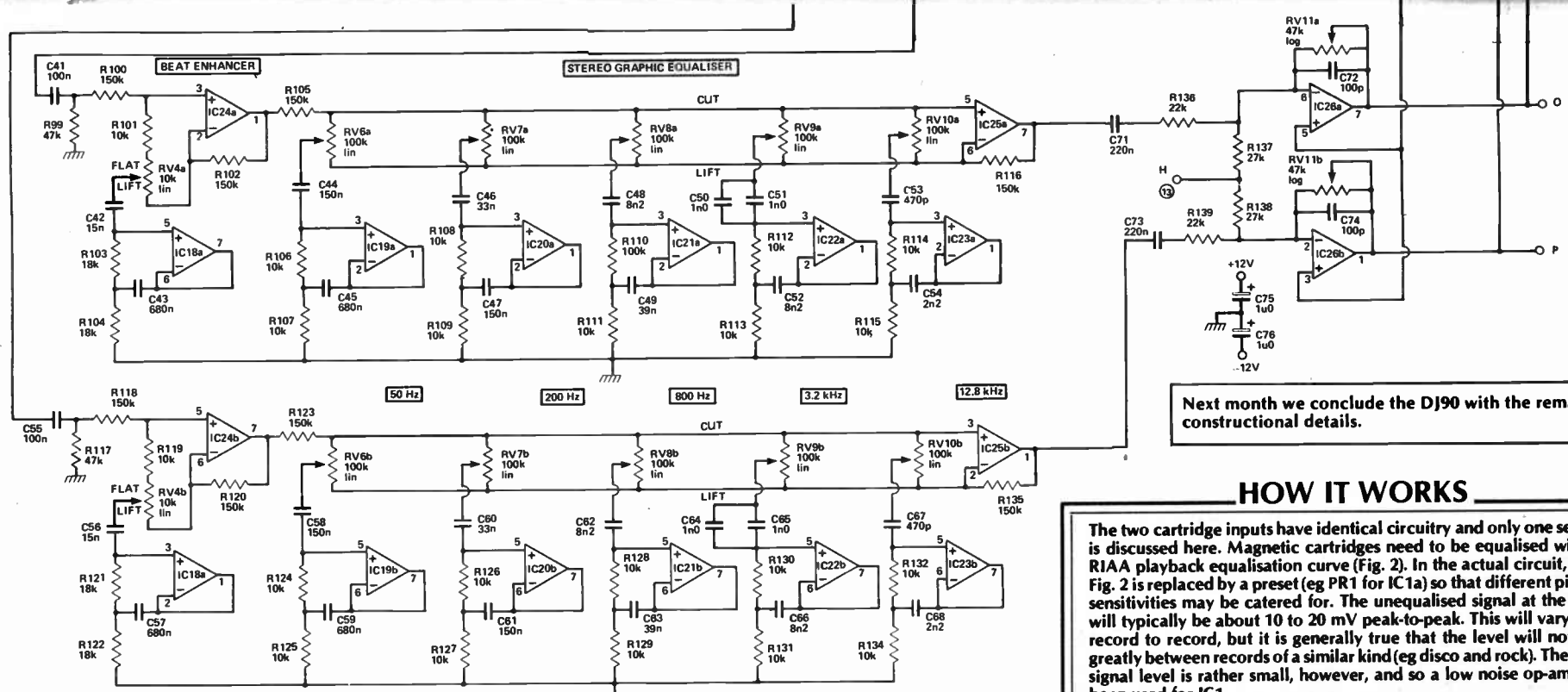


Fig.1 Circuit diagram for the music input and graphic equaliser sections.

Next month we conclude the DJ90 with the remaining constructional details.

### HOW IT WORKS

The two cartridge inputs have identical circuitry and only one section is discussed here. Magnetic cartridges need to be equalised with an RIAA playback equalisation curve (Fig. 2). In the actual circuit,  $R_B$  of Fig. 2 is replaced by a preset (eg PR1 for IC1a) so that different pick-up sensitivities may be catered for. The unequalised signal at the input will typically be about 10 to 20 mV peak-to-peak. This will vary from record to record, but it is generally true that the level will not vary greatly between records of a similar kind (eg disco and rock). The input signal level is rather small, however, and so a low noise op-amp has been used for IC1.

The VCA unit uses the LM13600 Operational Transconductance Amplifier; in the actual circuit this section comprises IC2 and IC3. The gain of the unit depends on the control current  $I_{ABC}$ , so the unit should actually be called a current controlled amplifier (ICA); however, we shall stick to the misnomer of VCA. The LM13600 has a diode predistortion network included in the IC which actually reduces the THD of the unit by as much as 10 dB. It was decided to operate the VCA at a  $V_{IN}$  level of 0 dBm (2V2 peak-to-peak). This gives a THD of 0.055% (typical best) and a signal-to-noise ratio of 80.5 dB. It also gives an overhead of about 18 dB. The output noise at 0 dBm is well below that of the RIAA stage and so it can be ignored.

The AUX input uses the same VCA (IC10, 11), but it does not have an RIAA circuit. Instead it has a +6 dB gain, flat frequency response preamplifier, built around IC13.

All three music inputs are mixed together by IC12 and fed into the beat lift and graphic equaliser section. The beat lift circuit is a peaky 90 Hz resonator, designed around IC18 and IC24, that can provide a variable lift. This tends to emphasise the beat in the music. The graphic equaliser (ICs 19 to 23 and IC25) uses the same circuit as the beat lift except that it can provide both lift and cut.

The circuit operates as follows. Each section (IC19a, C44, R106, R107, C45, for example) is a fixed frequency resonator. At resonance the resonator looks like a short to the ground. By connecting this resonator to the wiper of a pot which is connected across the input and the feedback of an amplifier, the amplifier can be made to provide cut and lift respectively at the resonant frequency. The resonator selectively shorts out the input signal or the feedback signal. The output of the equaliser is fed into a variable gain mixer, IC26, together with the output from the microphone section. Throughout the system, the operating signal level is 0 dBm, although gain can be provided in the equaliser. The output is also capable of generating 6 dB of gain.

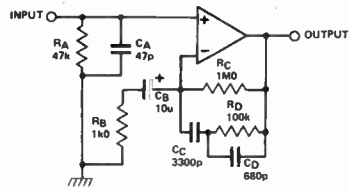


Fig.2 The RIAA equalisation block and the associated equations. The graph shows the frequency response.

$$F_1 = \frac{1}{2\pi R_C C_C} = 50\text{Hz}$$

$$F_2 = \frac{1}{2\pi R_D C_D} = 500\text{Hz}$$

$$F_3 = \frac{1}{2\pi R_D C_D} = 2120\text{Hz}$$

$$A_v \text{ AT } F_1 = \frac{R_C}{R_B} = +40\text{dB}$$

$$A_v \text{ AT } F_{2,3} = \frac{R_D}{R_B} = -40\text{dB}$$


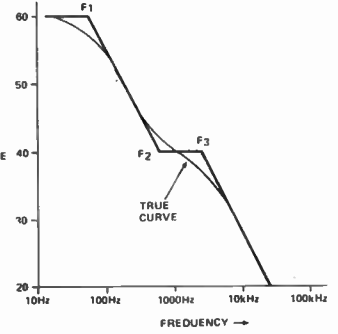



Fig.3 The basic VCA unit and a table showing the performance figures (see text).

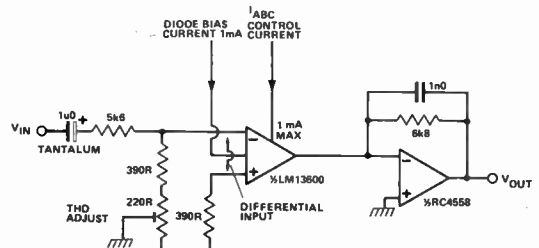

MEASUREMENTS TAKEN OVER A 20 kHz BANDWIDTH AT 100 Hz, 1 kHz AND 10 kHz. I<sub>ABC</sub> SET AT 1 mA. THE PRESET IS SET TO THE BEST THD POSITION.

TYPICAL MEASUREMENTS			
V <sub>IN</sub> dBm	V <sub>IN</sub> V <sub>pp</sub>	DIFFERENTIAL INPUT mV <sub>pp</sub>	OUTPUT THD% / OUTPUT S/N RATIO
+12dBm	0.8V	80mV	0.8% / 92.5dB
+6dBm	0.4V	40mV	0.2% / 98.5dB
0dBm	0.2V	20mV	0.055% / 80.5dB
-6dBm	0.1V	10mV	0.04% / 74.5dB
-12dBm	0.05V	5mV	0.02% / 68.5dB



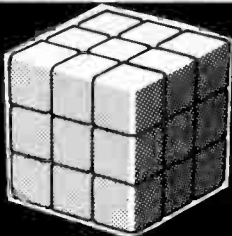


## CUBE MANIA — FREE OF CHARGE!

With purchases totalling over £17.50. Only on request at time of ordering. Offer closes 31/8/81. Subject to availability.
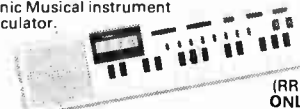
### BECOME AN INSTANT MUSICIAN NO EXPERIENCE NECESSARY

The success story of 1981. Hundreds sold already! As featured on "Tomorrow's World" Create your own music with a VL-TONE. You combine the sound, rhythm and tempo and the VL-1 plays it back... beautifully!  
**CASIO VL-TONE (VL-1)**  
Electronic Musical instrument and calculator.



(RRP £39.95)  
ONLY £35.95

VL-1 records and plays back up to 100 notes as a melody. **One Key Play** or **Auto Play** of Piano, Violin, Flute, Guitar and Fantasy, or create your own unique sounds with **A.D.S.R.** 10 built-in **Auto Rhythms** and **Tempo** control. LCD digital readout of notes and tempo. Also a calculator. Battery powered with memory and program retention. Integral amplifier/speaker. Output jack. With Song Book. Dims.: 1 1/8 x 1 1/4 x 3 in.

### CASIOTONE POLYPHONIC KEYBOARDS

With built-in amplifier and loudspeaker.

MT-30



(RRP £115)  
ONLY £95

22 instruments over 3 octaves. 4-position sound memory. Battery or mains. O/P jack. Dims.: 2 1/8 x 22 3/4 x 6 1/2 in. 6lb.

### ★★ NEW ★★ CASIOTONE CT-202

"Son of success... The two harpsichords demonstrate the Casiotone's talent for sparkling, crystal clear tones... Even more impressive is the clav... (Melody Maker).



49 instruments over 4 octaves. 4 voice memory function with push-button selection. 3 vibrato settings and sustain. Pitch control. O/P jacks. AC only. 3 3/8 x 34 1/8 x 11 3/16 in. 15.8lbs.

CT-301



(RRP £285)  
ONLY £245

14 instruments over 4 octaves. 8 x 2 rhythm accompaniments. Vibrato and delayed vibrato. Start/stop, synchro start, tempo control, tempo indicator, and rhythm volume. Pitch control. AC only. O/p jacks. 4 3/8 x 31 3/8 x 12 1/8 in. 27lbs.

CT-401



(RRP £345)  
ONLY £295

As 301 plus following: 16 rhythm accompaniments, with fill-in. Casio Auto Chord for one finger or auto accompaniment. Plays major, minor and 7th chords with bass. Balance control, C.A.C. lever, chord lever, memory lever and octave switch. Dims. as 301. Weight 28.2lbs.

### CASIO SCIENTIFIC CALCULATORS WITH LIQUID CRYSTAL DISPLAY

for long, long battery life.


FX81 FX100 (FX550)



**FX81.** 8 digits. 30 scientific functions. 4,000 hours battery life. Auto Power Off. 3/4 x 3 x 5 7/8 in. £12.95.  
**FX100.** 10d, 44f, 7,500 hrs. A.P.O. 3/4 x 3 x 5 7/8 in. £16.95.  
**FX550.** Replaces FX510 shown above, 1 lithium battery lasts 13,000 hrs. A.P.O. 10d, 50f. 3/8 x 2 7/8 x 5 1/4 in. £19.95.  
**SUPER SCIENTIFICS** with time dimension.  
**FX8100.** 46f. Clock, calendar, alarm, hourly chimes, countdown alarm, stopwatch. 1/4 x 2 3/4 x 5 1/8 in. £24.95.  
**FX7100.** Card version, without calendar. £24.95.  
**FX6100.** Hand held version of FX7100. £17.95.
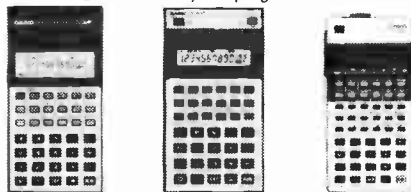
### CASIO PROGRAMMABLES

with A.P.O. and memory and programme retention.



FX180P FX3500P (FX602P)

**FX180P.** 10d, 55f, 2 programmes, 38 functional steps. Integrals and Regression analysis. 3/4 x 3 x 5 7/8 in. £19.95.  
**FX3500P.** As FX180P but 61f, g/32 x 2 7/8 x 5 1/4 in. £22.95.  
**FX602P.** As FX501P shown above but with alpha-numeric display. 10+2d, 51f, 256 steps, 22 memories, 10 unconditional jumps, 9 subroutines (9 levels) 18 parentheses (6 levels) £74.95.

### CASIO MELODY ALARM CLOCK CALCULATORS



MQ1200

**MQ1200** 12 melodies, 2 alarms, hourly chimes, date memories, anniversary memories, calendar. 1 1/16 x 6 x 2 9/16 in. £19.95.  
**ML-90.** Wallet version of above, with stopwatch. £14.95.  
**ML-75.** Card version of ML-90. 3/16 x 3 3/8 x 2 3/16 in. £15.95.  
**ML2000** Office version of MQ-1200. 1 3/4 x 4 x 6 1/4 in. £22.95.



UC365

UC3000

**UC365.** 3 melodies, universal calendar, date memories, two date alarms, daily alarm, hourly chimes, countdown alarm/stopwatch, time memory. 1/4 x 4 1/2 x 2 1/2 in. £19.95.  
**UC360.** Card version of above. 7/32 x 3 3/8 x 2 3/16 in. £19.95.  
**UC3000.** Office version. 1 3/4 x 4 x 6 1/4 in. £27.95.  
Send 20p for our illustrated catalogue.

### THESE SPACE INVADERS WILL ALARM YOU — THE PRICE WON'T

Casio's most amazing watches ever!

CA-90 (left)  
£24.95



CA-901 (right)  
£29.95

Time and auto calendar, calculator, alarm, hourly chimes, stopwatch, dual-time. **DIGITAL SPACE INVADER GAME.**

### 100 METRE WATER RESISTANT WATCHES

with alarm and stopwatch



W-150 (left)  
£32.50

W-150C (right)  
£25.95

Time and auto calendar, alarm, hourly chimes, countdown alarm timer with repeat memory function. Time is always on display, regardless of mode. S/S.

W100 (left)  
£19.95



UC50W (right)  
50m W/R  
£19.95

W100

UC50W

W100 is the resin case/strap version of W150 UC50W. 50 metre water resistant with universal full month calendar display with forward and backward stepping.

### LCD ANALOGUE/DIGITAL



AA81 (left)  
Chrome  
£29.95

AA82 (right)  
Stainless Steel  
£39.95

Dual time, analogue and digital. Alarm, hourly chimes, countdown alarm timer, stopwatch, auto calendar.

### 12 MELODY ALARM AND STOPWATCH

M12 Resin £17.95. M1200 S/S £29.95.

### SYMPHONIC ALARM CLOCK

MA-1  
£9.95

Mozart No. 40 or Buzzer. Hourly chimes. Snooze facility 1 3/4 x 4 1/2 x 3 in.



MA-1

PRICE includes VAT and P&P. Send cheques, P.O. or phone your ACCESS or BARCLAYCARD number to:

# TEMPUS


Dept. ETI, FREEPOST,  
164-167 East Road, Cambridge CB1 1DB  
Tel. 0223 312866

# TECH TIPS
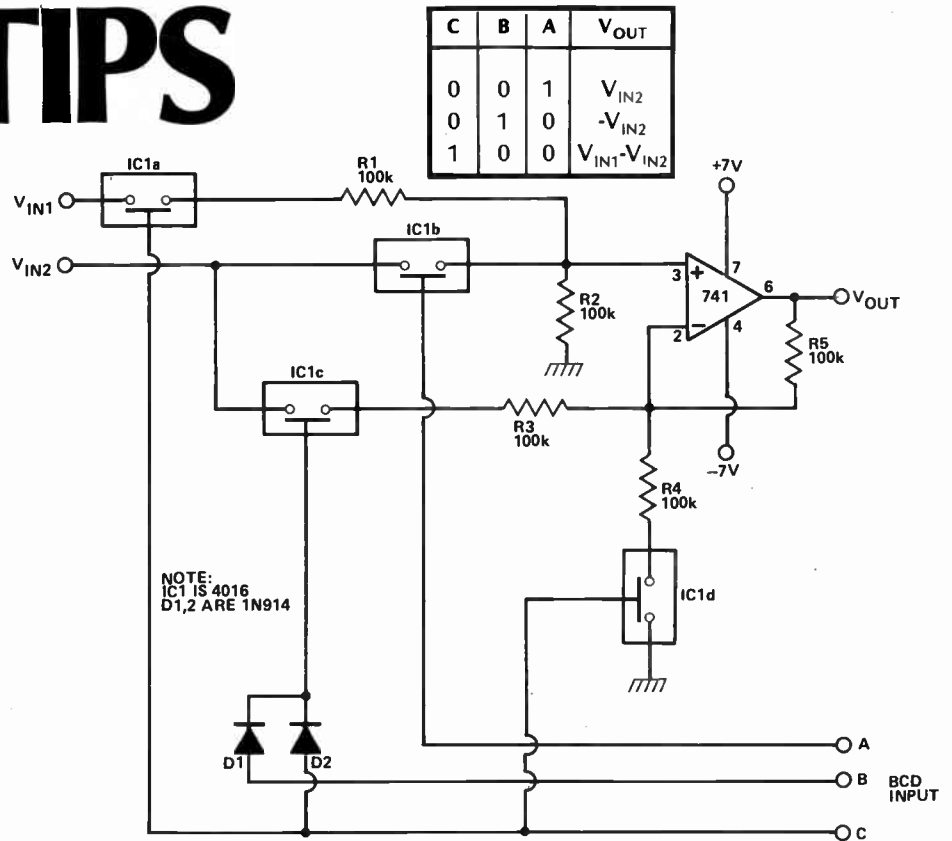
## Programmable Op-amp

J. P. Macauley, Crawley

This circuit was developed for experimental purposes and enables an op-amp to be operated in either the inverting, non-inverting or differential mode. This is accomplished by switching inputs into the circuit by means of IC1, a quad bilateral CMOS transmission gate. A diode matrix connects the control voltage for the gates together so that the operating mode can be controlled by a simple BCD-encoded word. As presented here the gain of the op-amp is unity, although this can be altered by the simple expedient of altering the respective resistor values. Note, however, that the output may distort if resistor values of less than 10k are used. This is due to the transmission gates, which like to 'see' at least this resistance as a load.




## Computer-controlled Synthesiser Keyboard

K. Wood, Ipswich

Referring to P. McChesney's idea published in Tech Tips, May '81 issue, it is possible to obtain an output voltage of an accuracy similar to that of the 12 bit code given without resorting to a second digital-to-analogue converter.

The logarithmic property of music allows this to be done. For each octave higher a note is, its frequency (and hence the control voltage of a linear oscillator), must double. Thus it is possible to generate voltages for the top octave of a keyboard, and obtain control voltages for lower octaves by dividing it by two, four, eight and so on, according to the number of octaves required.

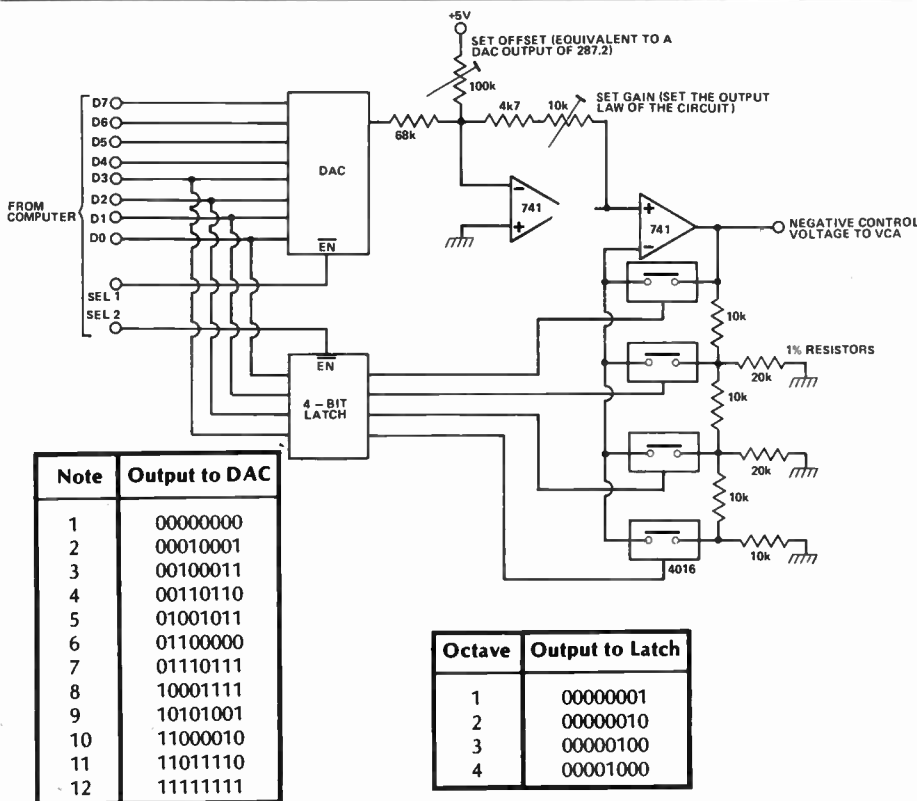An alternative arrangement is outlined to cope with these ideas. The note is output to the DAC, and its octave number is sent separately to the divider network by the computer system. A bias is added to the voltage to eliminate another bit from the 12 bit code, reducing it to the eight bit capability of the DAC.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

# LED Peak Meter

G. Durant, Selby

This circuit gives a bar display when connected to an audio source, such as the speaker outputs of an amplifier. Each channel is fed to one of the drivers IC1a, IC1b, which are op-amps wired as peak voltage detectors; they also rectify the signal and give the output voltage the characteristic PPM fast attack and slow (1 s) decay times.


The display section is multiplexed for low cost. A row of comparators (IC1c-IC2d) have their inverting terminals held at a particular voltage by a resistor chain and a reference voltage derived from a zener diode. The audio signal is fed to the non-inverting terminals of the comparators and as it reaches the reference level on each inverting input, the corresponding output goes high.

The output of each comparator is taken to two LEDs via a current-limiting resistor. Two independent displays are formed by taking the cathodes of each pair of LEDs to one of two common lines; each line can be connected to ground by one of the switches IC7c, IC7d. The two remaining switches in IC7 select which channel is to be sampled by the comparator section.

A clock formed by IC3a,b,c and running at about 100 Hz feeds a retriggerable flip-flop built around IC4. The two outputs control the IC7 switches so that each channel is measured and displayed on the appropriate LEDs in alternation.


A brief peak which reaches the top two LEDs on each channel may be too short to notice. When the top two comparators are triggered, they activate the peak hold circuitry built around IC5 and IC6. These are 555 timers wired in the astable mode and prolong the time for which the LEDs are illuminated to about 600 ms and 1.2 s respectively. This gives the same impression as a commercial peak hold meter.

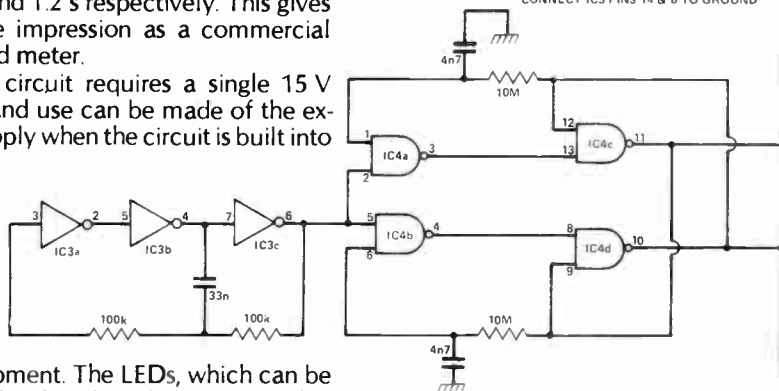The circuit requires a single 15 V supply, and use can be made of the existing supply when the circuit is built into



the equipment. The LEDs, which can be rectangular if preferred, are mounted in two rows of six and labelled with the level in dB (which is only approximate). The number of display LEDs can be extended by adding more resistors and comparators to the existing chain.

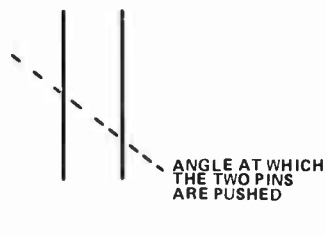Below and right: Constructing a cheap tilt switch.




## Cheap Tilt Switch

M. J. Woodbridge, St. Albans


The ETI Musical Box needs a mercury tilt switch, but there are cheaper ways of providing one. One way is to use a plastic biro refill end about 1.5-2 cm long. Thick pins are pushed into the soft plastic tube at one end as shown, at 180° to one another. The pins are then bent down at right angles to the tube and soldered to a

Below: 'Magnetic' tilt switch.

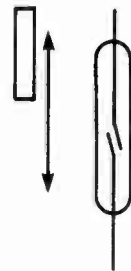

small piece of Veroboard. The end of the tube nearest the pins is blocked up using glue, or by melting the plastic with a hot object. A small ball bearing is inserted, which will short the pins when it touches them. Blocking up the other end of the tube leaves you with a passable tilt switch.

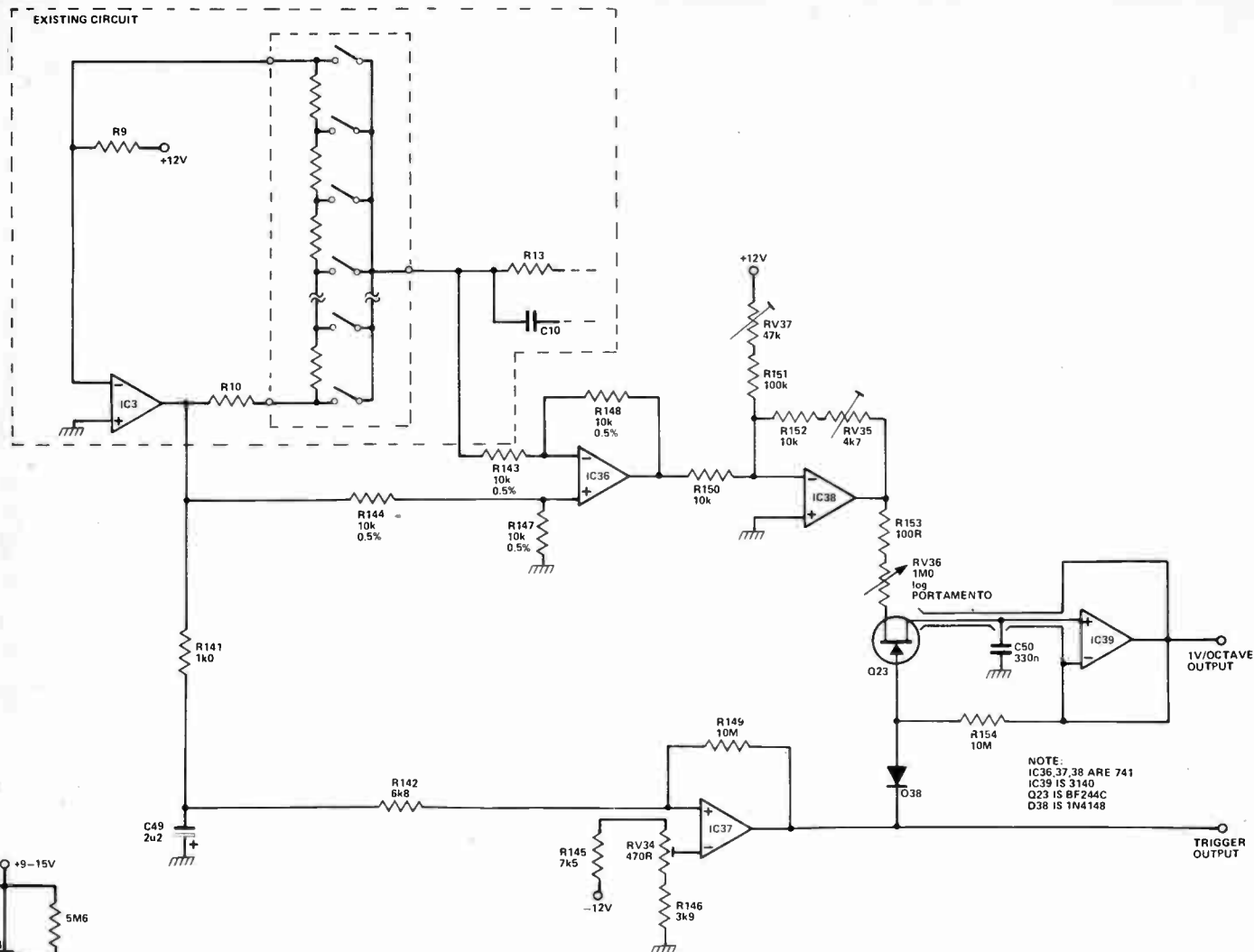A second way of making a tilt switch is to have a magnet moving up and down in a plastic channel near a reed switch.



## Duophonic Synthesiser Keyboard

P.R. Williams, Stevenage

Most synthesisers, including the otherwise excellent ETI Transcendent 2000, are strictly monophonic; only one note can be keyed at a time. True polyphonic synthesisers are, however, complex and expensive. The circuit described here is a very simple modification which can be made to the Transcendent 2000 to make it a duophonic instrument; that is, any two keys can be pressed simultaneously to produce two notes.

The circuit relies on the fact that the keyboard resistor chain is fed by a constant current source, IC3. When more than one key is pressed, one or more resistors in the chain are short-circuited, resulting in the output of IC3 becoming more positive to keep the current constant. The output voltage of the normal keyboard circuit is then equal to that corresponding to the highest note pressed. The change in voltage at IC3's output is thus proportional to the number of keys between the highest and lowest pressed.


Thus, to obtain the voltage cor-

responding to the lowest key pressed, the change in voltage at IC3's output must be subtracted from the normal keyboard voltage. This is done at IC36. IC38 provides a scaling factor to achieve the common 1 V/octave output, which is adjustable by RV35. An offset is also introduced at this point to put the voltage in a useful range. RV37 controls this.

A trigger signal derived from the change in IC3's output is produced by the level detector, IC37. R141 and C49 de-bounce the contacts, while R142 and R149 provide some hysteresis for additional triggering reliability. RV34 is set so that IC37 will reliably detect when two or more keys are simultaneously pressed. Q23 and IC39 form a sample and hold circuit, which has been duplicated from the Transcendent 2000 design. RV36 could be ganged with the existing portamento control.

The output can then be used to control either an external VCO or another synthesiser.

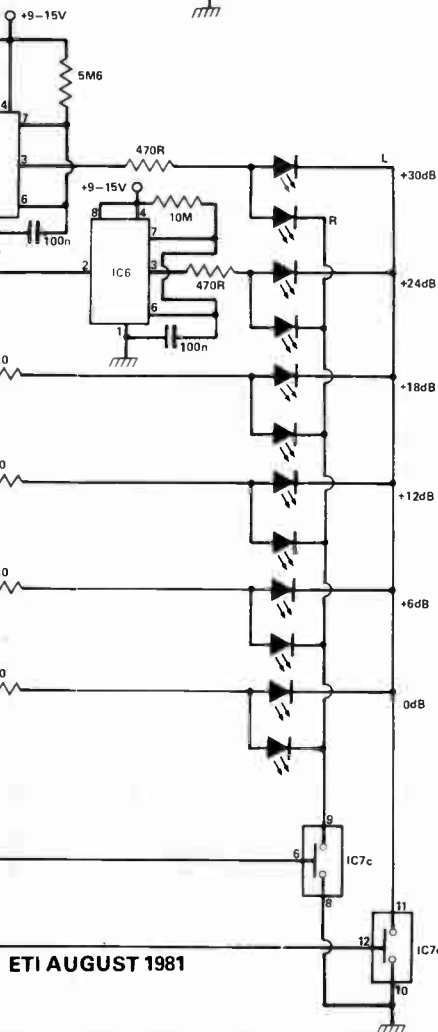Although this circuit was primarily designed as a modification to the Transcendent 2000, it could be easily adapted for use with any synthesiser that uses a constant current keyboard resistor chain.



# ETIPRINTS

ETIPRINTS offer you the easy way to produce high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

## PARTS LIST

040A	ETI 80 VCO/VCLFO	Feb 80	Speed Control	
			DTM Switching Board	
			RIAA Preamp	
040B	ETI 80 PSU	Feb 80		
	Tuning Fork			
	Hi-Lo Filter			
	Coin Toss			
041A	Audiophile Driver Amp	Mar 80		
	VCA			
	Signal Tracer			
	Heater Controller Main Board			
	Electromyogram			
041B	ETI 80 VCM	Mar 80		
	Heater Controller Sensor			
046A	ETI 80 Dual VCA	Aug 80		
	100 W Power Amplifier			
046B	Capacitance Meter	Aug 80		
	US Alarm			
	BGM 100 W Amplifier			
	Logic Tester			
	100 W Power Amp			
047A	Digital Test Meter	Sep 80		
047B	Vocoder Internal Excitation	Sep 80		
047C	ETI 80 Envelope Shaper	Sep 80		
	TV Sound			
	Survival			
048A	Sustain/Fuzz Box	Oct 80		
	Flash Trigger			
	FM Radio Control Receiver:			
	(Top side)			
	(Bottom side)			
	FM Radio Control			
	Transmitter			
048B	Vocoder Slew Rate Control	Oct 80		
	Vocoder Output Amp			
	Vocoder Input Amp			
	Vocoder PSU			
	Vocoder LED PPM Display			
048C	Cassette Interface	Oct 80		
	ETI 80 Monitor Amp			
049	AF Generator	Nov 80		
	Multi-Option Board			
	Space Invasion PSU			

## BUYLINES

Sheets for Sep 79, Dec 79, Jan 80 and April - July 80 are temporarily out of stock.

Earlier ETIPRINT sheets are available.

Send a cheque for PO (payable to ETI) for £1.20 per sheet with details of the project for which you require an ETIPRINT and the month and year of publication to:

ETIPRINTS,  
ETI,  
145 Charing Cross Road,  
London WC2H 0EE.

## HOW IT WORKS

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

# ETIPRINTS

**PARNDON ELECTRONICS LTD.**

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded in colour coded.  
 £1.00 per hundred mixed. (Min 10 per value)  
 £8.50 per thousand mixed. (Min 50 per value)  
 Special stock pack. 60 values. 10 off each £5.50

**DIODES:** IN4148 3p each Min order quantity - 15 items.  
 £1.60 per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed base - solve those programming problems  
 4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each

**DIL SOCKETS:** High quality, low profile sockets.  
 8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.  
 22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
 MIN. ORDER - U.K. £1.00. OVERSEAS £5 CASH WITH ORDER PLEASE

**RADIATION DETECTORS**

**BE PREPARED**

VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ON TO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture

Tested and fully guaranteed. Ex-stock delivery.

**HENRY'S**

01-723 1008/9

404 EDGWARE ROAD, LONDON W2 1ED

FREE RECHARGE SERVICE AFTER PURCHASE

**£6.95**

inc. VAT Post & Pack 60p

COMPLETE WITH DATA



**I.L.P. TRANSFORMERS**  
 INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

**NOW 95 TOROIDALS FROM 30<sup>VA</sup> TO 625<sup>VA</sup>**

TYPE	SERIES NO.	SECONDARY R.M.S.		PRICE
		Volts	Current	
<b>30va</b> 70 x 30mm 0.45 Kg regulation 18%	1X010	6 + 6	2.50	<b>£4.48</b> + 0.87p P&P + 0.80p V.A.T.
	1X011	9 + 9	1.66	
	1X012	12 + 12	1.25	
	1X013	15 + 15	1.00	
	1X014	18 + 18	0.83	
	1X015	22 + 22	0.68	
	1X016	25 + 25	0.60	
	1X017	30 + 30	0.50	
<b>50va</b> 80 x 35mm 0.9 Kg regulation 13%	2X010	6 + 6	4.16	<b>£4.93</b> + £1.10 P&P + 0.90 V.A.T.
	2X011	9 + 9	2.77	
	2X012	12 + 12	2.08	
	2X013	15 + 15	1.66	
	2X014	18 + 18	1.38	
	2X015	22 + 22	1.13	
	2X016	25 + 25	1.00	
	2X017	30 + 30	0.83	
<b>80va</b> 90 x 30mm 1 Kg regulation 12%	3X010	6 + 6	6.64	<b>£5.47</b> + £1.43 P&P + 1.04 V.A.T.
	3X011	9 + 9	4.44	
	3X012	12 + 12	3.33	
	3X013	15 + 15	2.66	
	3X014	18 + 18	2.22	
	3X015	22 + 22	1.81	
	3X016	25 + 25	1.60	
	3X017	30 + 30	1.33	
<b>120va</b> 90 x 40mm 1.2 Kg regulation 11%	4X010	6 + 6	10.00	<b>£6.38</b> + £1.43 P&P + £1.17 V.A.T.
	4X011	9 + 9	6.66	
	4X012	12 + 12	5.00	
	4X013	15 + 15	4.00	
	4X014	18 + 18	3.33	
	4X015	22 + 22	2.72	
	4X016	25 + 25	2.40	
	4X017	30 + 30	2.00	

TYPE	SERIES NO.	SECONDARY R.M.S.		PRICE
		Volts	Current	
<b>160va</b> 110 x 40mm 1.8 Kg regulation 8%	5X011	9 + 9	8.89	<b>£8.44</b> + £1.43 P&P + £1.48 V.A.T.
	5X012	12 + 12	6.66	
	5X013	15 + 15	5.33	
	5X014	18 + 18	4.44	
	5X015	22 + 22	3.63	
	5X016	25 + 25	3.20	
	5X017	30 + 30	2.66	
	5X018	35 + 35	2.28	
	5X026	40 + 40	2.00	
	5X028	110	1.45	
5X029	220	0.72		
5X030	240	0.66		
<b>225va</b> 110 x 45mm 2.2 Kg regulation 7%	6X012	12 + 12	9.38	<b>£10.06</b> + £1.73 + £1.77
	6X013	15 + 15	7.50	
	6X014	18 + 18	6.25	
	6X015	22 + 22	5.11	
	6X016	25 + 25	4.50	
	6X017	30 + 30	3.75	
	6X018	35 + 35	3.21	
	6X026	40 + 40	2.81	
	6X025	45 + 45	2.50	
	6X028	110	2.04	
6X029	220	1.02		
6X030	240	0.93		
<b>300va</b> 110 x 50mm 2.6 Kg regulation 6%	7X014	18 + 18	8.38	<b>£11.66</b> + £1.73 + £2.01
	7X015	22 + 22	6.82	
	7X016	25 + 25	6.00	
	7X017	30 + 30	5.00	
	7X018	35 + 35	4.28	
	7X026	40 + 40	3.75	
	7X025	45 + 45	3.33	
	7X033	50 + 50	3.00	
<b>500va</b> 140 x 60mm 4 Kg regulation 4%	8X017	30 + 30	8.33	<b>£15.53</b> + £2.05 + £2.64
	8X018	35 + 35	7.14	
	8X026	40 + 40	6.25	
	8X025	45 + 45	5.55	
	8X033	50 + 50	5.00	
	8X042	55 + 55	4.54	
	8X028	110	4.54	
	8X029	220	2.27	
8X030	240	2.08		

TYPE	SERIES NO.	SECONDARY R.M.S.		PRICE
		Volts	Current	
<b>625va</b> 140 x 75mm 5.0 Kg regulation 4%	9X017	30 + 30	10.41	<b>£21.54</b> + £2.20 + £3.56
	9X018	35 + 35	8.92	
	9X026	40 + 40	7.81	
	9X025	45 + 45	6.94	
	9X033	50 + 50	6.25	
	9X042	55 + 55	5.68	
	9X028	110	5.68	
	9X029	220	2.84	
	9X030	240	2.60	

**IMPORTANT**

All voltages quoted are for **FULL LOAD**. Please add regulation figure to secondary voltage to obtain **OFF LOAD** voltage.

**CHOICE OF 3 PRIMARY INPUTS**

(L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows (Secondaries can be connected in series or parallel):

For 110V Primary insert 0 in place of "X" in type number.

For 220V Primary (Europe) insert 1 in place of "X" in type number.

For 240V Primary (U.K.) insert 2 in place of "X" in type number.

EXAMPLE: 50va 240v. 6 + 6v 4.16a = 2 2 0i0.

**5-YEAR GUARANTEE**

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. All I.L.P. Toroidal Transformers carry our full 5-year guarantee.

FOR SINGLE AND SMALL QUANTITY ORDERS

GOODS DESPATCHED WITHIN 7

DAYS OF RECEIPT OF ORDER

See also our ad. on pages 16 and 17 of this issue

- ★ CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.
- ★ FREEPOST FACILITY (U.K. only). Simply send your order in envelope to FREEPOST to address below. NO STAMP REQUIRED.
- ★ TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd. or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. U.K. customers must include V.A.T. with payment.
- ★ Also available from ELECTROVALUE, MAPLIN, MARSHALLS, TECHNOMATIC and WATFORD.



FREEPOST T4, GRAHAM BELL HOUSE, ROPER CLOSE  
 CANTERBURY CT2 7EP. Phone (0227) 54778. Technical (0227) 64723. Telex 965 780

To: I.L.P. ELECTRONICS LTD., CANTERBURY CT2 7EP

Please supply Transformer(s) ..... No.(s) .....  
 ..... Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order   
 Debit my Access/Barclaycard Account No. ....

NAME .....

ADDRESS .....

Signature ..... 4T/6

# MICRO TIMES

19 Mill Street, Bideford, North Devon EX39 2JR  
Telephone Bideford (023 72) 79798  
(Dept. ETI 8)

★★★★ THIS MONTH'S SUPER SAVERS ★★★★★

MEMORIES	1+	25+		
2114 450ns	£1.35	£1.30		
2114 300ns	£1.45	£1.40		
FROM TOSHIBA TC 5514P				
4K (1k x 4) 450ns	£3.65	£3.45		
CMOS RAM 5101	£3.45	£3.40		

**6809 Single Board Computer ★Kit★**  
IEEE S-100 Standard  
Complete kit £160 plus 15% VAT £1 P.&P.  
Uses Motorola's Powerful MC6809 CPU  
4K/8K/16K ROM, 2K RAM, ACIA, PIA, 8080  
simulated I/O, RS-232 Handshake, 8 Sel. Baud  
Rates. Manual includes: 11 x 17in. Schematic  
Parts list. User Notes. Software listings and  
more!  
Bare Board **£48★**  
Uses 6809, 6850, 6821 - buy set for **£18.50**  
ADMONS (2716) **£24.00**  
Data available. S.a.e. please.

Low Profile D Face Wipe DIL Sockets	THYRISTORS C106D	28p
40 pin 39p	TILs	
28 pin 29p	TIL32 45	
24 pin 25p	TIL209 red 10p	
22 pin 24p	TIL232 green 18p	
18 pin 20p	TIL212 yellow 16p	
16 pin 18p	TIL216 red 18p	
14 pin 16p	TIL228 red 20p	
8 pin 12p	TIL220 red 12p	
Quantities 100+	TIL224 18p	
Discount 5%	TIL31 £5.50	
	TIL312/3 £1.00	
	TIL321/A £1.15	
	TIL330/A £1.15	

LINEAR ICs	18p
NE555	NE556
RC4136	LM301AN
LM311P	LM318
LM324N	LM339N
LM348N	LM358P
LM380	LM3900N
LM3914	LM3915
LM3915	LM13600
SN76477N	UA709
UA709	LM741
UA733	UA747
UA747	UA748
UA748	TLO74CN
TLO74CN	TLO81CP
TLO82CP	TLO84CN
LM3302	TL490
TL490	1488
1488	1489
8T25	8T28
8T28	8T95
8T95	

ENCODER/ TRANSMITTER	LM1871	£1.90
RECEIVER/ DECODER	LM1872	£1.90
VOLTAGE REGULATORS	1A	
7805	5V 55p	
7812	12V 55p	
7805	5V 60p	
7812	12V 60p	
78L05	5V 29p	
78L12	12V 29p	
79M12	12V 64p	
79M05	5V 64p	
723	32p	

CPUs	£5.45
6502	£5.45
6504	£7.25
6802	£5.70
6809	£15.00
8080A	£4.15
8085A	£6.45
Z80	£5.80
Z80A	£5.80

SUPPORT DEVICES	£3.15
6520	£5.00
6522	£7.80
6532	£2.50
6810	£1.90
6821	£15.00
6845	£1.95
6850	£3.30
6852	£1.75
8212	£3.95
8216	£4.00
8228	£4.25
8255	£4.25
Z80CTC	£4.25
Z80PIO	£5.40
Z80ACTC	£5.40
Z80ADMA	£16.00
Z80ADMA	£18.00
Z80S10/0	£18.00
Z80AS10/0	£24.00
Z80S10/1	£18.00
Z80AS10/1	£24.00
Z80S10/2	£18.00
Z80AS10/2	£24.00

SN76477N SOUND CHIP	£1.70
A single chip versat-	
ile SOUND	
EFFECTS GENERA-	
TOR SN76477N is	
ideally suited for ap-	
plications such as	
arcade or home	
video games,	
alarms, sound	
effects boxes and	
toys.	
Kit - parts + instructions for	
easy assembly	
DATA: £1.25,	
50p Large S.A.E.	

## KITS FOR BEGINNERS

AROUSE THE MICRO CHIP INTEREST IN THE YOUNGSTERS  
STARTER KITS

<b>ULTRONIC FLY REPELLER</b> A must for campers. Features: -LED indication. -Pocket size case. -Low power consumption. Kit + all parts - case + in- structions for easy assembly. Battery not included. <b>£4.50</b>	<b>LIGHT ACTIVATED SWITCH</b> Used for automatic lighting control, elec. appliance control electronic gun, burglar alarm and auto-open door system. Switch on/off 200W elec. appli- cances. Kit - parts + instructions for easy assembly <b>£3.50</b>	<b>ELECTRONIC WHEEL OF FORTUNE</b> Fun kit. Easy to assemble. Case included. Wonderful game <b>£5.00</b>
---	--	---

**ORDERING INFORMATION**  
Please add 50p P&P plus 15% V.A.T. to all  
orders. EXPORT ORDERS ACCEPTED.  
Add 15% P&P on total order. V.A.T. not appli-  
cable.  
ACCESS/BARCLAYCARD WELCOME  
Schools, colleges, universities official  
orders welcome.

It is our policy to offer you brand new, full  
spec. devices. Prices subject to change with-  
out notice.



**OHIO SCIENTIFIC COMPUTERS**  
Our prices are so low we dare not print them!  
Special offer: Superboard 3 + free Cegmon mo-  
nitor ppa. Super board 3 + free power supply,  
modulator and guard band kits ppa. Series 2  
Challenger ppa. Power supply kit £11.95. Mo-  
dulator £3.50. Guard band kit £10. 4K extra ram  
£12. Case £27. Cegmon £29.50. Wernon £19.95.  
Assembler/Editor tape £25. Word processor  
program £10. Display expansion kit for  
Superboard 2 £14. Centronics interface kit £10.  
610 expansion board £159. Cased minifloppy  
disc drive with DOS and psu £275. Cassette re-  
corder £18. Colour adaptor board £65.

## VIDEO GENIE £289



## PRINTERS



Buy any of those below and get a free interface  
kit and word processor program for UK101 or  
Superboard: Epson MX70 £259. Epson MX80T  
£359. Epson MX80F/T1 £399. Epson MX80F/T2  
£449. Epson MX100 £575. OKI Microline 80 £299.  
OKI Microline 82 £399. OKI Microline 83 £699.  
Centronics 737 £395. Seikoshpa G80A £199.

**SINCLAIR PRODUCTS\***  
Sinclair Products only are all Post free. SC110  
Oscilloscope £139, adaptor £4, rechargeable bat-  
teries £7.95, x1 Probe £8.95, x10 Probe £8.95,  
carry case £8.80, PFM200 £52.40, adaptor £4,  
case £1.73, connector kit £11.27, PDM35 £32.95,  
adaptor £4, case £1.73. DM235 £56.50, DM350  
£78, DM450 £107, adaptor £4, case £8.80, re-  
chargeable batts. £7.95. Microvision TV £69,  
adaptor £8.95.

**BATTERY ELIMINATORS\***  
3-way type 6/7.5/8v 300ma £3.50. 100ma radio  
types with press studs 9v £4.95. 9+9v £6.25. Car  
converter 12v input, output 3/4.5/6/7.5/9v £3.04.

**BATTERY ELIMINATOR KITS\***  
100 ma radio types with press-studs 9v £1.79,  
9+9v £2.50. Stabilised 8-way types  
3/4.5/6/7.5/9/12/15/18v 100ma £3.12, 1amp  
£8.50. Stabilised power kits 2-18v 100ma £3.12,  
1-30v 1A £8.50, 1-30v 2A £15.30. TTL and compu-  
ter supplies 5V stabilised 1.5A £9, 3A £14, 6A  
£22, 12v car converters 6/7.5/9v 1A £1.62.

**TV GAMES\***  
AY-3-8500 + kit £12.98. RY-3-8550 + kit £9.26.

**PRINTED CIRCUIT MATERIALS\***  
PC etching kit: economy £3.42, standard £5.76.  
40 sq. ins. pcb 50p. 1 lb FeCl £2.20. Etch resist  
pens.: economy 50p, data 90p. Drill bits 1/32" or  
1mm 35p. Etching dish 92p. Laminate cutter  
£1.30.

**BI-PAK AUDIO MODULES\***  
AL30A £4.35, PRA12 £9.31, PS12 £1.75, T538  
£2.90, S450 £27.90, AL60 £5.62, PA100 £19.94,  
SPM80 £5.26, BMT80 £6.36. Stereo 30 £24.14,  
AL80 £8.56.

**COMPONENTS\***  
1N4148 1.5p. 1N4002 3.7p. NE555 8 diil 2p. 741 8  
diil 20p.  
bc182, bc184, bc212, bc214, bc547, bc549 6.1p.  
Resistors 5% 1/4W £12 10R to 10M 1.5p. 0.8p for  
50+ of one value. Polyester capacitors 160v .015,  
.08mf 2.9p, .047, .1mf 4.4p, .01mf 3.3p, .022,  
.033mf 3.7p, .15, .22, .33mf 5.4p, .47mf 6.6p.  
Polystyrene capacitors £12 63v 10 to 10000p 4p,  
1n2 to 10n 5p. Ceramic capacitors 50v £6 22p to  
47n 2.5p, electrolytic capacitors 50v 5, 1, 2mf 6p,  
25v 5, 10mf 6p, 15v 22, 33mf 6p, 47mf 5p, 100mf  
7p, 330, 470mf 9p, 10000mf 15p, zeners 400mW  
£24 2V7 to 33V 7p. Preset pots subminiature  
0.1W horiz or vert 100 to 2M2 8p. ic sockets 8 diil  
8/7p, 14 diil 10.1p, 16 diil 12p.

**SWANLEY ELECTRONICS**  
Dept. ETI, 32 Goldsel Road, Swanley, Kent, BR8 8EZ  
Postage £3.50 on superboard. £4.50 on printers and 45p on other orders. Lists 27p post free.  
Please add V.A.T. to all prices except those sections marked with a \* which already include it at  
the old 15% rate. Overseas and credit orders welcome.

# Happy Memories

4116 200ns	£1.50	2114 200ns	£2.95
2114 450ns	£1.95	2716 5 volt	£3.70
2708 450ns	£3.35	2732 450ns	£9.95

**SOFT-SECTORED MINI-DISCS** for PET, TRS-80,  
etc. Supplied in Free Library case **£21.95 per 10**

**Low Profile I.C. Sockets by Texas**  
Pins ..... 8 14 16 18 20 22 24 28 40  
Pence ..... 10 11 12 16 17 20 21 28 37

**Memory Upgrade Kits** for Apple, 2020, TRS-80,  
etc. .... from **£12.00** please phone

Quantity prices available on request. Govern-  
ment and Educational Orders welcome. Trade  
accounts opened.

**ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON  
ORDERS OVER £15, OTHERWISE ADD 30p**

Access and Barclaycard Welcome

**HAPPY MEMORIES**  
Dept. ETI  
Gladestry, Kington  
Herefordshire HR5 3NY  
Telephone (054422) 618

## Quality support for; ATOM

### ZX80 ACTION !

2 games per cassette - for only £4!!

Flicker-free action games for your ZX80.  
Only 1K RAM needed, and the original (4K) ROM.

Cassette C80A: **BRKOUT** ----- **ACK-ACK** £4-  
Cassette C80B: **SHELL GAME** ---- **INVADERS** £4-

## ZX80 ZX81

### The ZX80 Magic Book

\*NOW WITH 8K ROM / ZX81 SUPPLEMENT\*. Games programs, computer music, converting programs written in other BASICs, RAM and I/O circuits, and much more. £4.75  
Supplement also available separately for 50p.

### Getting Acquainted with your ZX81

A Tim Hartnell masterpiece. £4.95  
23+23 WAY ZX80/81 EDGE CONNECTOR SOCKET £3.50

### ATOM CASSETTES; £5 each

CAAA: **BREAKOUT+CUPBALL+3D MAZE+SIMON 2**

CAAB: **PINBALL+LETTERS+SPACEWAR+DRIVE**

CAAC: **HAMMURABI+OTHELLO+SCRAMBLE+HEXPAWN**

### The ATOM Magic Book

\*RECOMMENDED BY ACORN\*

A wealth of games and other programs; storing speech in your ATOM, converting programs written in other BASICs, tape recording hints, plus many other useful hardware and software tips. £5.50

### 32K Byte ATOM RAM Board £125.00

Single Eurocard; fits inside ATOM's case. Built and tested. Complete with connectors and buffer IC's.  
Also suitable for other 1MHz 6502 / 6800 computers.

ALL PRICES INCLUDE U.K. P&P + VAT WHERE APPLICABLE

**TIMEDATA Ltd. 57 Swallowdale, Basildon, Essex**

## DISCO LIGHTING KITS!!!

First class constructional projects. c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

**LK1**  
£9.90

3 channel sound-to-light.  
300 w/channel 1v - 100w input

**LK3**  
£8.90

2kW slider dimmer  
suitable for clubs/pubs.  
A professional unit c/w  
**FACE PLATE**

**LK2**  
£17.90

3 channel 3kW  
zero voltage firing  
200mV - 100 watts input.

**LK4**  
£16.50

4 channel 4kW  
audio - forward/reverse  
auto - two speed ranges.



circuit, comprehensive  
instructions & full  
parts guarantee

Suitable case for  
LK 1/2/4 £3.50  
100w spots ES or BC  
£1.50.  
Coloured pigmy lamps  
65p.  
8m rope lights  
£39.50

Carriage on above 70p



## UNREPEATABLE HI-FI BARGAIN

### 3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- \* 6 1/2" linen surround bass unit
  - \* 5" mid range unit
  - \* 3" tweeter
  - \* 3 way crossover, fixing screws & baffle
  - \* 20 watts handling capability.
- Full instructions provided  
Must be heard to be believed!!!

£10.50 or 2 kits for £20 Carr. £1 per kit

## SAXON ENTERTAINMENTS (ETI)

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.

(01) 684 8007

Order by phone - Access Barclaycard/C.O.D.  
Open Mon. - Sat. 9am - 5pm.

## ETI PROJECT KITS FROM MAGENTA ELECTRONICS LTD

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.T.I. Projects. We supply carefully selected sets of parts to enable you to construct E.T.I. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.T.I. which includes the project - you will need to order the instruction reprint as an extra 45p each.

Reprints available separately 45p each + p&p 40p

SMART BATTERY CHARGER, July 81	£29.14
SUPER DICE, July 81	£37.96
WAA PHASE, June 81, less pedal	£12.22
LED JEWELLERY, June 81, Cross	£2.25
Spiral	£6.55
Star	£8.56
ALIEN ATTACK, Jan 81	£17.97
ANTENNA EXTENDER, June 81	£19.71
MINI DRILL SPEED CONTROLLER, June 81	£22.85
DIGITAL CLOCK, May 81 (round leds)	£39.98
CARAVAN LIGHTS CHECKER, April 81, less glue	£9.24
SOUND ANALYSER, April 81 less case	£68.95
GUITAR NOTE EXPANDER - ETI, April 81	£14.98
DRUM MACHINE, April 81	£59.95
MUSICAL BOX, April 81	£11.40
ENGINEERS STETHOSCOPE, Mar 81	£17.45
SOUND PRESSURE LEVEL METER, Feb. 81	£45.75
PULSE GENERATOR, Feb 81 less case	£32.12
Case extra	£24.98
INFRA RED ALARM, Feb 81	£49.99
UNIVERSAL TIMER, Jan 81	£28.89
MULTI-OPTION SIREN, Jan 81	£24.47
LED TACHO, Jan 81 less case	£31.61
4 INPUT MIXER, Dec 80	£17.98
BENCH AMPLIFIER, Dec 80	£21.85
MUSICAL DOORBELL, Dec 80	£10.56
AUDIO TEST OSCILLATOR, Nov 80	£16.64
RIAA PRE-AMP (stereo), Nov 80	£6.21
2W POWER AMP, Nov 80	£5.54
METRONOME, Nov 80	£5.44
LIGHT SWITCH, Nov 80	£7.77

### 1981 ELECTRONICS CATALOGUE

KITS  
ICs  
TRANSISTORS  
CAPACITORS

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery.  
Send 70p in stamps or add 70p to your order.

TOOLS  
RESISTORS  
HARDWARE  
CASES

TOUCH BUZZER, Nov 80	£5.56
SUSTAIN/FUZZ BOX, Oct 80	£22.72
CASSETTE INTERFACE, Oct 80 less case	£10.52
ULTRASONIC BURGLAR ALARM, Aug 80	£24.39
CAPACITANCE METER, Aug 80	£18.42
CMOS LOGIC TESTER, Aug 80	£9.98
SIGNAL TRACER, Mar 80	£10.98
TUNING FORK, Feb 80	£13.48
ACCENTUATED BEAT METRONOME	£16.28
CLICK ELIMINATOR, April 79 less case	£34.25
Case extra	£14.98
GUITAR EFFECTS UNIT, April 79	£13.44
DIGITAL MODULE, Jan 79 less switch and case	£23.83
COMPLEX SOUND GENERATOR, Oct 78 less case	£19.98
TELEPHONE BELL EXTENDER, Oct 78, less speaker	£14.98
Horn speaker extra	£6.83

I.C.s		LM348N	£1.73	SN76477	£2.80
555	32p	LM380N	99p	TDA1022	£6.98
741	28p	LM384N	£2.50	4013B	55p
CA3140E	57p	LM386N	£1.04	4024B	76p
LF353	96p	LM387N	£1.39	4030B	69p
LF356	99p	LM3914N	£2.98	4046B	£1.39
ICM7555	£1.19	NE570N	£6.30	4093B	89p
LM317K	£3.56	NE571N	£5.71		

Printed Circuit Boards - E.T.I.  
Fully etched, drilled and ready to use, pcbs for E.T.I. projects listed.  
Send s.a.e. for pcb price list.

### The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

The Instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the Instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk. 2. Circuits are built on a plug in Eurobreadboard. Kit is available with or without the breadboard. INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85; or less Eurobreadboard £21.65.  
INSTRUCTOR COURSE NOTES AND OPERATING INSTRUCTIONS -

## MAGENTA ELECTRONICS LTD.

ET3, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS., DE14 2ST  
0283-65435. 9-5 MON.-FRI. MAIL ORDER ONLY

ALL PRICES INCLUDE VAT  
ADD 40p P&P TO ALL ORDERS


Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling.




Access and Barclaycard (Visa) orders accepted by phone or post.




# PCB FOIL PATTERNS

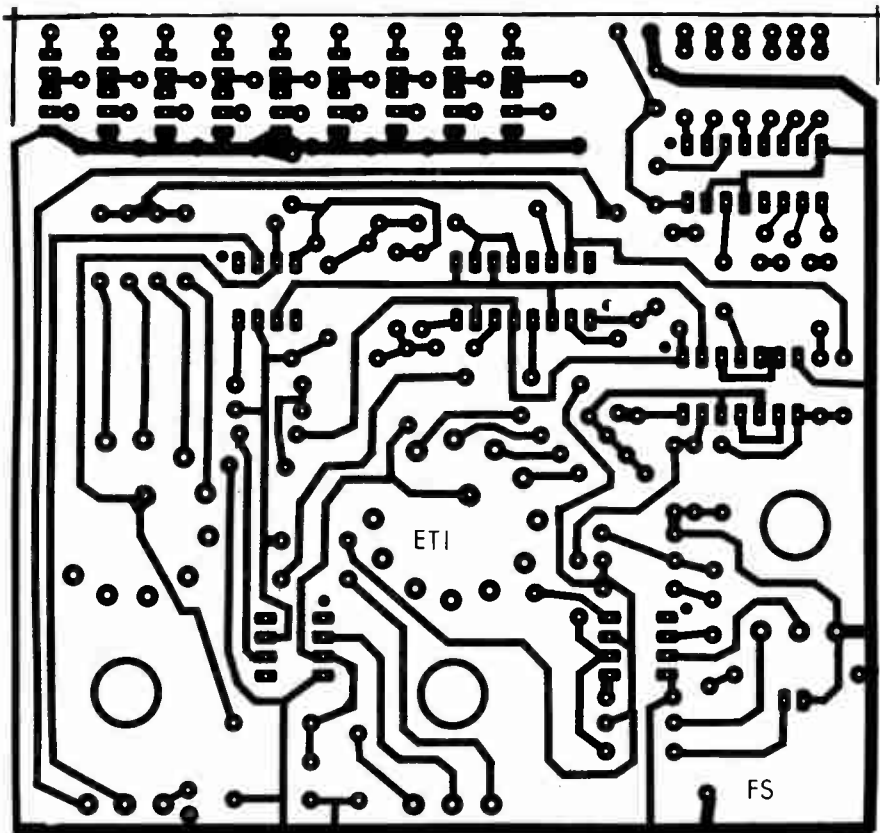

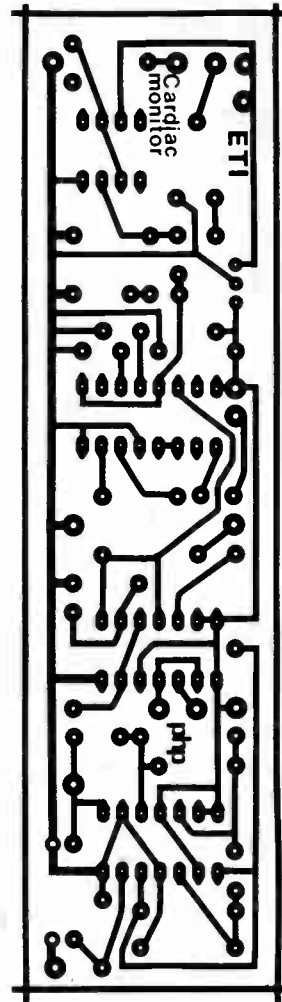
Above: the foil pattern for the Flash Sequencer.




Above: the Heartbeat Monitor board.

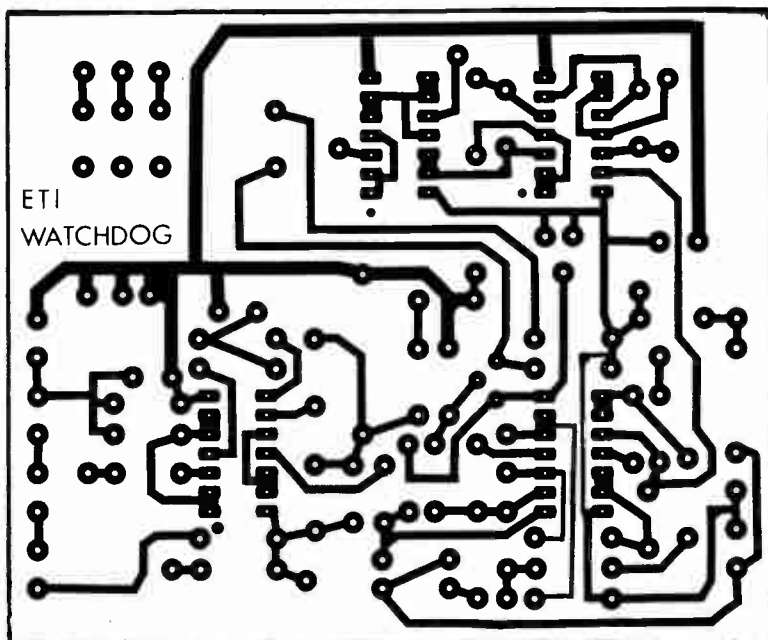

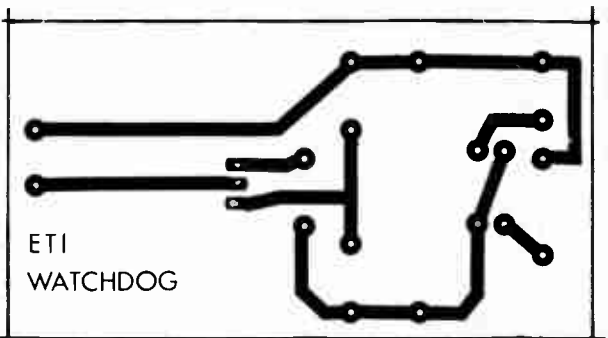
Left and below: the PCBs for the Watchdog main unit and the Ni-Cd charger.



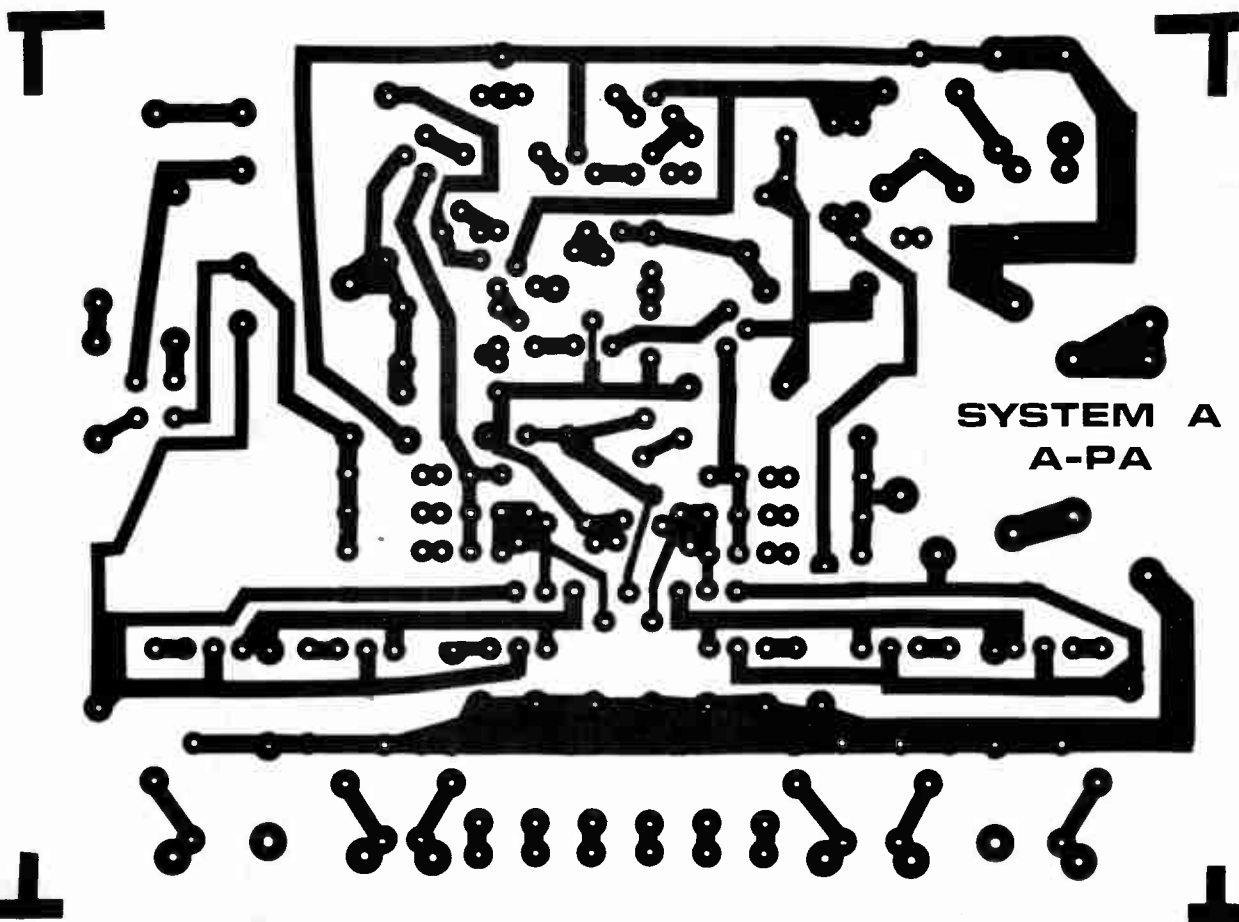

SYSTEM A  
A-PA

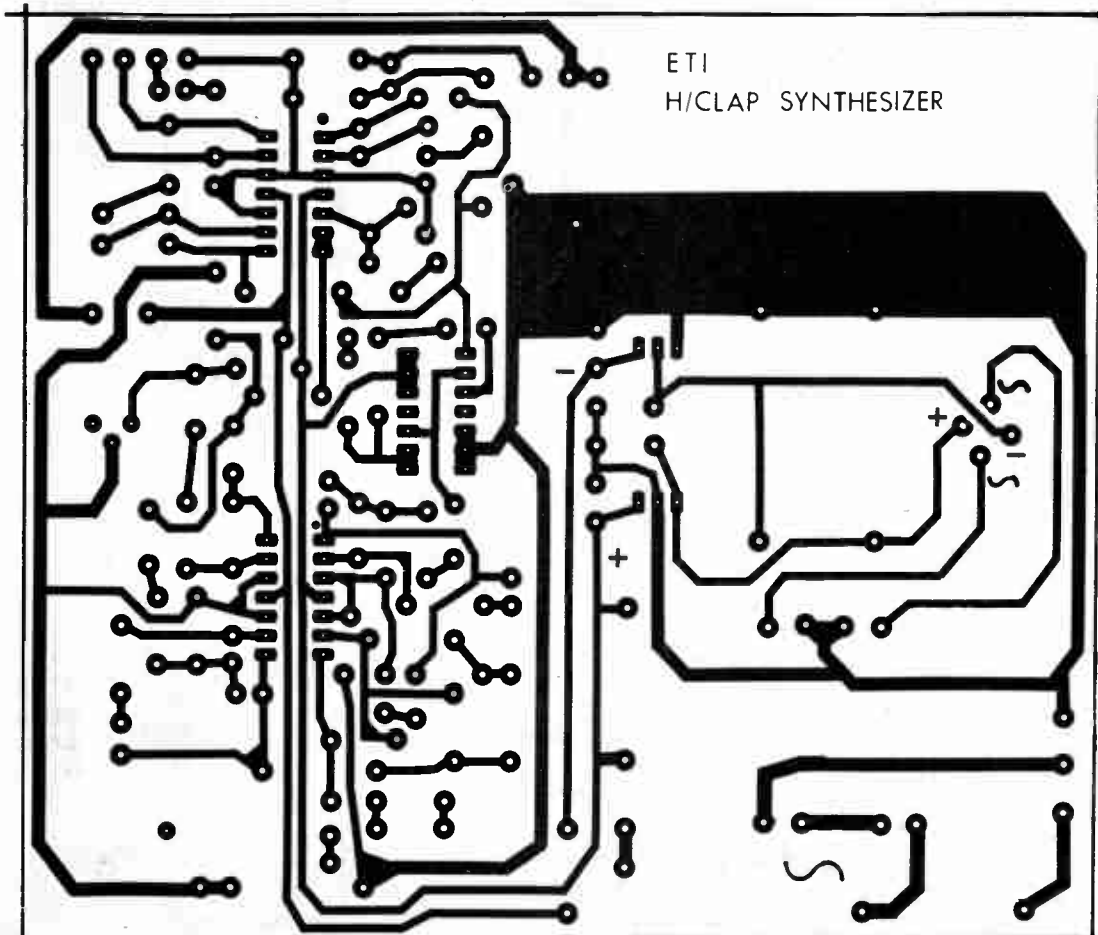Above: the System A power amplifier foil pattern.



ETI  
H/CLAP SYNTHESIZER

Left: the Hand-clap Synthesiser PCB.

The DJ90 PCBs are too large to fit in the magazine; an SAE to us will secure a photocopy. Commercial companies should note that these, and the System A boards, are copyright and may not be reproduced without permission.

# CLASSIFIEDS

**ETI RATES**  
 1-4 Insertions £9.00 per scc  
 5-11 Insertions £8.00 per scc  
 12+ Insertions £7.00 per scc  
 30p per word (min 12 words)  
 Box No. £2.00  
 Closing date 1st Friday in month preceding publication.

**HE RATES**  
 1-3 Insertions £5.00 per scc  
 4-11 Insertions £4.50 per scc  
 12+ Insertions £4.00 per scc  
 18p per word (min 15 words)  
 Box No. £1.50  
 Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepaid.  
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

## BARGAIN OFFER

Massive clearout of electronic components. Ideal for home constructors, experimenters and beginners

2lb Box ..... £2.00 plus £1.50 P&P  
 10lb Box ..... £10.00 plus £2.50 P&P  
 Prices include VAT. Money back if not satisfied on goods returned within 14 days.

Send your order to:  
**HARRISON BROS**  
 PO Box 55  
 Westcliff-on-Sea  
 Essex S50 7LQ

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**ZX80 & ZX81.** Join ZX guaranteed. All games/programs guaranteed to work. £5 year. Frustrated National ZX80 club people are welcome. - Bobker, 29 Chaderton Drive, Unsworth, Bury, Lancs.

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components  
 Full range of HE printed circuit boards normally ex-stock. same day despatch at competitive prices  
 P.C. Boards to individual designs.  
 Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Allfac range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
 MASONS ROAD  
 STRATFORD-ON-AVON  
 WARWICKS. Tel. 4879

## LARGE QUANTITY OF 4K x 1 DYNAMIC RAMS (4027s)

Used and untested  
 £15 for 20, £50 for 100 inc. VAT & PP  
**P. KINGSLEY-WILLIAMS**  
 40 Churchyard Close  
 Chester, Cheshire

**T. & J. ELECTRONICS COMPONENTS** - Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

**ELECTRONIC KIT BUILDERS.** You supply the kit - we build it for 60% of kit price. For quotation telephone 0604 56248 or 0908 564542.

## WANTED

Test equipment, valves, tubes and scrap electronics.

Reasonable prices paid. Distance no object (UK mainland only).

**FRG General Supplies**  
 Unit 3, Longhill Industrial Estate  
 March, Cambridgeshire  
 PT15 8NQ

Tel: March (03542) 56614  
 or 01-404 5011  
 Telex: 24224 Quote Ref. 3165

## ADAM HALL

Cabinet & Flightcase Fittings, fretcloths, coverings handles, castors etc. Jacks & sockets. Cannons. Bulbuns, reverb trays. Emular compression drivers. AKG mics. Celestion speakers. ASS glassfibre horns

Send 30p postal order for illustrated catalogues to  
**ADAM HALL (E T SUPPLIES)**  
 Unit B, Cherriton Court  
 Grainger Road, Southend-on-Sea  
 Essex SS2 5BZ

**CENTURION BURGLAR ALARM EQUIPMENT.** Send s.a.e. for free list or a cheque/p.o. for £5.95 for our special offer of a full-sized decoy bell cover. To: Centurion, Dept. ETI, 265 Wakefield Road, Huddersfield, West Yorkshire. Access and Barclaycard. Telephone orders 0484 35527.

**BUILD A 12 into 2 mixer for £100.** Details £3.50. P.O. to Mr J. A. Lovatt, Flat 5, 36 William Ave., Margate, Kent.

**TRANSCENDENT DPX,** recently professionally built, great sound, £300 inc. V.A.T. Ring Weybridge (0932) 54778 (day) or 43436 (evenings).

**WANTED.** Electronic components and test equipment. Good prices given. Q Services, 29 Lawford Crescent, Yatley (0252) 871048, Camberley, Surrey.

## BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

1. With alarm repeat. S.R.S.P. of £17.00 Offered at £3.95, inc. VAT, or 3 for £9.95, inc. VAT
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00 Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT

These will be sold as received from our customers with the existing fault(s) and without guarantee. U.K. only

Discounts available on large bulk purchase

**PRESCOTT CLOCK & WATCH CO. LTD.**

PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER



**CCTV CAMERA**

£126.50 + P&P £3.45 (inc. VAT) Total £129.95

**BEST OFFER EVER Camera Kit, Lens, Vidicon & Modulator**

**CROFTON**

35 GROSVENOR ROAD  
 TWICKENHAM, MIDDX.

**COPPER CLAD BOARD DOUBLE-SIDED FIBRE-GLASS:** - 1,000 sq. inches of assorted sizes £6,800 sq. inches of assorted sizes £5,600 sq. inches of assorted sizes £4 and 400 sq inches of assorted sizes £3. Postage free. Also complete P.C.B. services. H.C.R. (Chelmsford), 1 Bankside, off New Street, Chelmsford.

**ZX81 1K SPACE INVADERS** - Written in machine code - FAST moving graphics (the 'SLOW' mode is too slow for this game). On screen scoring - protective shields - laser control and missile firing through the keyboard. £4.00 for listing. MACRONICS, 26 Spiers Close, Knowle, Solihull B93 9ES.

**VHF/FM TRANSMITTER KIT.** New silicon chip design means low price (beats any one else) and better performance. Very small - ideal bug, etc. . . . Fully tuneable 88-108MHz. Instructions, etc. all included. **INTRODUCTORY OFFER £2.50 inc. P&P** (unlicensable). M. Henry, Dept. ET1, 30 Westholme Gardens, Ruislip.

**1920's ONWARD valves, wireless.** Lists 25p. S.A.E. Sole Electronics, ET1, 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

**MICROTYPE STAK-PAK**  
CASSETTE STORAGE SYSTEM FOR EASY PROGRAM FILING.



- \* Each drawer section takes 2 cassettes
- \* Drawers lock together vertically
- \* Each twin pack comes with 2 C10 digital cassettes
- \* Each 'pak' is complete with index cards, cassette and drawer labels.

FIVE TWIN PAKS (10 CASSETTES) FOR £6.80 INC. VAT & P&P

Send cheques or Postal Orders to:  
**MICROTYPE, PO Box 104  
HEMEL HEMPSTEAD  
HERTS. HP2 7QZ**

**ET1 PCBs**

Drilled 1.5mm Glass Fibre. Fry's Roller Tinned

April '81 DPI (drum kit) .....	£2.36
May '81 Set of IR control .....	£4.62
June '81 Antenna extender .....	£2.33
Waa Phase .....	£1.15
July '81 Superdice 'a' .....	£3.72
Superdice 'b' .....	£2.24
Battery Charger .....	£1.24
Aug. '81 Cardiac Monitor .....	£1.37
Flash Sequencer .....	£2.63
Clap Synthesizer .....	£2.96

For full list and current PCBs send S.A.E. PCBs also produced to customers own masters. Trade enquiries welcomed. Write for quote. C.W.O. please. Add 35p P&P to complete order. Europe 70p.

**PROTO DESIGN**  
14 Downham Road, Ramsden Heath  
Billericay, Essex, CM11 1PU  
Tel: 0268 710722

**PARAPHYSICS JOURNAL** (Russian translations); Psychotronic Generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9". Paralab, Downtown, Wilts.

**CLOSE ENCOUNTERS GROUP.** Personal introductions/dances, parties, talks, social events. Meet interesting attractive people. All areas. Tel. 01-278 0203/051-931 2844.

**ZX81 GAMES.** Six super games on cassette, £3 (plus additional free game and other info.) or SAE list/details. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

**RADIATION DETECTORS**

**BE PREPARED**

**VIEW THRU LENS**

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture. Tested & fully guaranteed. Ex-stock delivery.

**£6.95** inc. VAT Post & Pack 60p

Ideal for the experimenter  
**COMPLETE WITH DATA**

**HENRY'S**  
404 EDGWARE ROAD, LONDON W2 1ED



**PROGRAPH BOARD** for UK101/SUPERBOARD, gives 128 User defined characters. Kit £39.50, built and tested £47. **SOFTWARE CASSETTES-UK101, C1E, ZX81 £2.** Components-Resistors 75p, 2114 £1.60, etc. S.a.e. for details - Haven Hardware, 4 Asby Road, Asby, Workington, Cumbria.

**MK14 KITS.** We have 50 items for Mk14 computers. Send s.a.e. for price list. 20-page catalogue 90p plus 25p post. - Redditch Electronics, 21 Ferney Hill Avenue, Redditch, Worcestershire B97 4RU. Tel. 0527 61240, evenings.

**TELEPHONE ANSWERING MACHINES,** Super Phones, Radio Phones, etc. Ring G.W.A.S. 0274 682674.

**WE BUY** surplus electronic components, PCB's, etc., for cash. Tel: (0703) 785862.

**FREE FREE FREE**  
parking for 4,000 cars at the  
**SUSSEX MOBILE RALLY**

Brighton Raceground

**JULY 19, 1981**  
10.30 to 6 p.m.

All the usual traders exhibiting. Many attractions for all the family.

**ADD ZILOG** power to your Elektor Microcomputer System. A Z80 card complete with 1200 Baud 1/0 is now available. Can be used with existing monitors. £60. Also available 16 extra op-codes for the SC/MP £3.50. S.a.e. for details - B. Jones, 13 Albert Street, Cheltenham.

**EPROM PROGRAMMING** £2.50/K (your chip) + 50p p. & p. and ins. or 2708 at £7.50, 2716 + 5 at £10.50, 2532 at £22.50, all inclusive. Reduced rates for repeat orders, modifications, etc. C.W.O. S.A.E. enquiries. - Seamist S.S.D., 45 Oak Street, Fakenham, Norfolk.

**BATTERY ELIMINATORS,** 8V/500mA, £12; 5V/3A £33; 5V/1A £19. Carriage £2/unit. - Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

**HAVE YOU SEEN THE GREEN CAT?**  
1000s of components (C.B., Radio & Electronic). Aerials, Plugs, SWR Meters & Accessories, Audio, Hi-Fi, Experimental devices. In fact anything electronic at unbelievably low prices. Something for everyone. Send 25p stamps, cheque, P.O., and RECEIVE FREE GIFT.  
MYERS (Dept. ET1), 14/16 Clifton Grove, Harehills, Leeds 9. Mail Order Only

**BUILDING AUDIO EQUIPMENT?**

You need the ATEK catalogue. Lists 100s of components/accessories. 100w modules; £9.95, 120w Mos-Fet modules; £14.95. Also POWERTEK speakers, 60w from £10.95, heatsinks, connectors, knobs, switches, wire, hardware, cabinet materials, etc. **PLUS LOTS MORE.** Catalogue 70p post free, includes discount offers. Mail order only. **ATEK (ET1) 1, 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL. Tel: 02514 22303.**

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 30, London E.4.

**ENAMELLED COPPER WIRE**

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

**SILVER PLATED COPPER WIRE**  
14 to 30 6.50 3.75 2.20 1.40

**TINNED COPPER WIRE,**  
14 to 30 3.85 2.36 1.34 0.90

Prices include P&P and V.A.I.  
Orders under £2 please add 20p.  
SAE for List of Copper and Resistance Wires. Dealer enquiries welcome

**MK. 14.** Simple V.D.U. interface, circuit description plus software, £5; 40-key, low profile, matrix keyboards, £10. PC1211 programs: Maze; Calendar; 350 variables; Alien Attack. Listings £1 each. - D. Harris, 41 Norris Rise, Hoddesdon, Herts.

**HALF PRICE** components, switches, coils, etc. S.a.e. for lists - Gaze Electronics Ltd., 132 Gladstone Street, Darlington, Co. Durham.

**'A'-LEVEL** Electronic Systems. Details of two-year F.T. course plus full range of A-levels at South East London School. - Telephone 692 1803.

**SHARP POCKET COMPUTERS**

CE122 Printer/Cassette interface .....	£63.25
PC1211 Pocket Computer .....	£91.95
CE121 Cassette interface .....	£13.80

Free Papermate Pen with all orders. All prices include 15% V.A.T. and U.K. delivery.

**ELKAN ELECTRONICS, 28 Bury New Road  
Prestwich, Manchester, M25 8LD**

**KEYBOARD FOR ZX81.** Build-up our full-size keyboard for your ZX80 or ZX81. Kit £19.95 + p.&p. In/out port to control up to 24 lines £14.95. Edge connector £3.95. P.&P. 95p. S.a.e. for price list and details. — Redditch Electronics, 21 Ferney Hill Avenue, Redditch, Worcestershire B97 4RU. Tel. 0527 61240, evenings.

**AMAZING ELECTRONICS PLANS.** Lasers; Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 75p. — From Placentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

**DIGITAL WATCH BATTERY REPLACEMENT KIT**



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.



**BOLSTER INSTRUMENT CO. (ET27)**  
11 Percy Avenue, Ashford, Middx. TW15 2PB

**UNIQUE OPPORTUNITY** to acquire an established work-from-home organ service in the S.E. Turnover £15,000 p.a. rising. Full instruction given. Details: Box No. ET1201, 145 Charing Cross Road, London WC2H 0EE.

**EX-COMPUTER PARTS,** mains, relays, 30p; switches 15p. P&P 20p. Lots more silly prices. SAE for lists. SK Electronics, 36 Manchester Road, Mossley, A-U-L, Lancs.

**MAIL ORDER PROTECTION SCHEME**

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser so affected and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures has not been complied with, at the discretion of this publication *Electronics Today International*, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc. received as a result of answering such advertisements). Classified advertisements are excluded.

**SITUATIONS VACANT**

**ELECTRONIC TEST TECHNICIANS**

(up to £6,000 p.a.)

**ELECTRONIC INSPECTORS**

(up to £100 p.w.)

Exciting opportunities exist to help test and inspect our Simfire range of laser-based microprocessor controlled simulators which are used in the training of tank crews and other military personnel. The need for high reliability in the product's varied operating environment demands skilled and experienced staff.

In our Test area, you will be expected to test and diagnose faults from P.C.B. level through to system integration using a wide variety of both commercial and special purpose test equipment. You should have at least two years' similar experience and have a relevant City and Guilds examination (or equivalent).

For our Quality Control area, you should have at least three years' experience as an electronics inspector preferably holding an MoD or similar stamp. You should be familiar with the use of standard test meters and be able to work with the minimum of supervision carrying out

detailed inspection on any of our products or systems.

Although based mostly within the factory, you will as part of a closely knit team, in both areas, become regularly involved in final testing of the equipment at our nearby outdoor testing range. For this a clean driving licence is essential.

For further details and an application form please contact:— Carol Allibone on 01-366 1100,

ext. 50 or write to her at:— Weston Controls, Great Cambridge Road, Enfield, Middx. EN1 3RX.



**WESTON  
Schlumberger**

**GIUITAR/PA.** 100-watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50; 60 watt £44; 200 watt £68; 100 watt twin-channel sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four-channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £34; 200 watt £60; 250 watt £70; 500 watt £140. Fuzz Boxes, great sound, £12; bass Fuzz £12.90; overdriver Fuzz with treble and bass boosters, £22; 100 watt Combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £98; twin-channel £115; Bass Combo £118; speakers 15in., 100w., £36; 12in. 100 watt £24; 60 watt £16; microphone, Shure Unidyn B, £25; 3-channel sound/light, £26. Send cheque/P.O. to: Williamson Amplification, 62 Thorncliffe Avenue, Dukinfield, Cheshire. Telephone: 061-308 2064.

**AMP-SPECIAL!** ● Klifco return AN-AD No. 4 ● Simply return + £3 (inc.) for any 1 amplifier module + data! ● 3-watt + pre-amp 9v ● 5-watt + preamp 18v ● 10w-preamp 25v ● 20w less preamp 25v ● PSU 240v £4 (inc.) - From Klifco The Electronic People.

**NCR 399 COMPUTER**, working order, maintained by NCR during only five years' use. Useful for parts which include standard cassette head, electric motors, golf-ball printer, many ICs, diodes, LEDs, resistors, transistors, etc. Offers to RAY on ERITH 49018.

**CIRCUIT DESIGN**, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. - Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

● **KLIFCO RETURN AN-AD: No. 3** ● Return this ad. + £19.95 (inc.) for A SUPERB VALUE STEREO POWER AMPLIFIER. Stabilised PSU; 2N 3055 output; stereo 60 watt R.M.S.; IC Preamp. Case includes controls, volume, selector, etc., din output/inputs for magnetic pick-up/microphone (3.mv) + Tuner + Tape/Aux. 26 transistors - 2 IC Screened Douglas Transformer, 240 V AC mains lead. NEW - TESTED - DATA. KLIFCO ELECTRONICS, 1 REGENT ROAD, ILKLEY, W. YORKSHIRE, LS29 9EA.

**BURGLAR ALARM** Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

**BUY BULK - SAVE MONEY!!!**

All goods new full spec. devices sent by return. Post £1 any qty. No V.A.T. S.A.E. list.

1N4148	£10/1000	555	£13/100
1N4003	£20/1000	4001B	£10/100
BC1831L	£25/1000	4011B	£10/100
2N3055	£30/100	4049A	£19/100
74L74	£14/100	4060B	£38/100
4016A	£16/100	4511B	£60/100

PC ELECTRONICS, 1 Thornhill, Romsey Road, Whiteparish, Salisbury, Wilts. Mail only.

**COMPUTER SALE:** 2118 Dynamic RAM's (16K) Single +5V. supply; (150ns). Superb devices - 22:50 for 8. 4116 Dynamic RAM's (200ns), 16 for £15.00. 64K memory boards 15 x 25 cms (200ns), £55, complete with circuit diagrams. Lambda Power Supplies +5V & 25A - £45. Carriage rates: Chips 40p, boards £1, power supplies £7. Cash with order to: J. Wright, 27 Broomhill Drive, Glasgow G11 7AB. SAE for details.

**FORMANT SYNTH**, card frame system, sample and hold, less one v.c.o. All working. £250. - Tel: 061-865 3533.

**35 LEDS (RED) £5**

AEG 5mm matched, full spec. Inc. P&P, VAT and Clip  
Mail order only  
**COVE COMPONENTS**  
58 Southwood Road  
Cove, Farnborough  
Hampshire GU14 0JJ

**BREAKER, BREAK**

Build your own C.B. rig. Circuit diagrams, parts lists, etc. All components readily available in U.K. (27 MHZ, A.M. TRANSCEIVER). Send a large SAE and £3.95 to P. Sherwood, 8S, Aylesstone Walk, Manchester, M10 9NU. I'm down and on the side.

**WRONG TIME?**

**MSF CLOCK** is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto. G.M.T./B.S.T. and Leap Year, can expand to Years, Months and Milliseconds, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE ACCURACY, £62.80.  
**60KHZ RUGBY RECEIVER**, as in MSF Clock, serial data and audio outputs, £17.90.  
Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage, etc.; money-back assurance; so GET yours NOW!  
CAMBRIDGE KITS  
45(TV), Old School Lane, Milton, Cambridge

**DIGITAL WATCH REPAIRS**

Digital watches and clocks, cassette recorders, radios, calculators, etc. Send item and S.A.E. for quote. Repairs guaranteed, reasonable prices. New watches - low prices. Digatron Electronics (ETI), 2 Christchurch Drive, Daventry, Northants, NN11 4RD. Tel: (032-72) 3693.

**BRAND NEW, NOT SURPLUS BARGAIN PACKS**

10 7400 £1, 10 BC183L £1, 10BC213L £1, 2 7805 £1. Prices include V.A.T. Postage 25p. C.W.O. to: Micro Musical Ltd., The Old Vicarage, 37 Wood Lane, Shilton, Coventry, CV7 9LA.

**ADVERTISEMENT INDEX**

Aitek Instruments	72	Marshalls	24
Ambit International	34 & 35	Mawson Associates	92
Audio Electronics	45 & 94	Micro Times	88
Audio Video Services	23	Midwich Computer Co	23
Bi-Pak Semiconductors	54	Mitrad	9
BK Electronics	34 & 46	NIC Models	29
B.N.R.S.	93	OK Machine & Tool	72
Calculator Sales & Service	34	Parndon Electronics	87
Cambridge Learning	73	T. Powell	29
Chiltmead	74	Powertran	2, 6 & 7
Chromasonics	66	Rapid Electronics	92
Clef Products	35	J. W. Rimmer	86
Crimson Elektrik	28	R.T.V.C.	99
Crofton Electronics	35	Saxon Entertainments	89
Delta Tech & Co	85	Science of Cambridge	38 & 39
Display Electronics	30	Silica Shop	8
Doram Electronics	61	S&M (Anglia) Ltd	72
Electronize Design	92	Strathand Ltd	85
Electro Supplies	45	Swanley Electronics	88
Electrovalve	93	Tangerine Computers	52 & 53
Greenbank	56	Technomatic	10
Greenweld	29	Tempus	80
Happy Memories	88	Timedata Ltd	89
Henry's Radio	87 & 93	TK Electronics	67
ILP Electronics	16, 17 & 87	Transam Components	62
LB Electronics	86	Videotone Ltd	61 & 71
Linton Electronics	71	Watford Electronics	4 & 5
Magenta Electronics	89	WETAB, Wallden Trading AB	23
Manor Supplies	92	Wilmslow Audio	85
Maplin	100		

**ELECTRIFY YOUR SALES! • CLASSIFIED ADVERTISEMENT**

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15

Advertise nationally in Electronics Today International/Hobby Electronics. Simply print your advertisement in the coupon here (left), indicating which magazine you require. Or telephone for more information.

Name .....

Address .....

.....

Tel. No. (Day) .....

Send, together with your cheque to:  
Jenny Naraine, ETI/HE,  
145 Charing Cross Rd., London WC2H 0EE.  
Tel: 01-437 1002 Ext. 50.

Please place my advert in: Electronics Today International  
(Delete as applicable) Hobby Electronics

**NEW**

# PRACTICAL ELECTRONICS

## STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System

### Features

VHF - M.W. - L.W. Bands. Interstation muting and A.F.C. on VHF Tuning Meter. Two back printed P.C.B.'s Ready made chassis and scale Aerial. AM - Ferrite Rod, FM - 75 or 300 ohms. Stabilized power supply with "C" core mains transformer All components supplied are to P.E. strict specification Front scale size 10 1/2" x 2 1/2" approx.

Complete with circuit diagrams and instructions.



INTRODUCTORY PRICE-ONLY

**£17.95**

plus £2.50 p&p

## PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



### 2 WAVE BAND MW LW

\* Easy to build \* 5 push button tuning

\* Modern styling design \* All new unused components

\* 6 watt output \* Ready etched & punched P.C.B.

\* Incorporates suppression circuits \* Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia

The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird Pre-aligned push button tuning unit. The radio fits easily in or under dashboards

Complete with instructions.


**£10.50**

plus £2.00 p&p

### CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete

**£1.95** per pack, plus £1.15 p&p

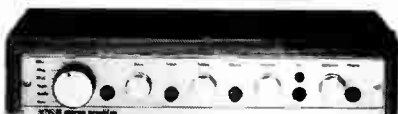

## 30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED


Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx.

READY TO PLAY **£32.90** plus £3.80 p&p
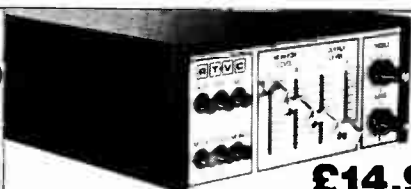
## HI FI STEREO AMPLIFIER MODULES



- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. **£1.95** plus 70p p&p.
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. **£4.95** plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. **£3.95** plus £1.15 p&p
- Matching power supply kit with transformer. **£3.00** plus **£1.96** p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. **£1.70** plus 80p p&p
- Complete with application notes



**£14.95**

plus £2.90 p&p

## 10+10 WATT STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection
- Mullard Stereo Preamplifier module
- Attractive black vinyl finish cabinet Size 9" x 8 1/4" x 3 1/4" approx
- Converts to a 20 watt Disco amplifier

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit

### SPECIFICATIONS

Suitable for 4 to 8 ohms speakers  
Frequency response 40Hz — 20KHz  
Input Sensitivity P.U. 150mV Aux 200mV Mic 1.5mV  
Tone controls Bass ± 12db @ 60Hz  
Treble ± 12db @ 10KHz  
Distortion -1% typically @ 4 watts  
Mains supply 220-250 volts 50Hz

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus **£3.15** p&p when purchased with amplifier Available separately **£10.50** plus **£3.16** p&p



**8" SPEAKER KIT** 2 8" approx. twin cone domestic use speakers. **£4.75** per stereo pair plus **£1.70** p&p when purchased with amplifier. Available separately **£6.75** plus **£1.70** p&p.


### STEREO MAGNETIC PRE-AMP CONVERSION KIT

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p



323 EDGWARE ROAD, LONDON W2  
21 E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
**ALL PRICES INCLUDE VAT AT 15%**  
All items subject to availability. Price correct at 1.6.71 and subject to change without notice.  
For further information send for instructions 20p plus stamped addressed envelope.  
NOTE: Goods despatched to mainland and N. Ireland only.  
Persons under 16 years not served without parent's authorisation.  
RTVC LTD. reserve the right to alter, update or improve their products without notice.

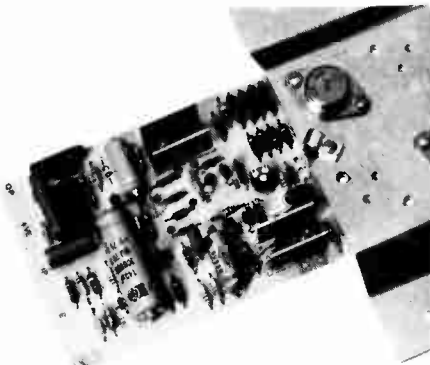

## HIGH POWER MODULE KITS

125 WATT MODEL **£10.50**

plus £1.15 p&p (illus)

200 WATT MODEL **£14.95**

plus £1.15 p&p

### SPECIFICATIONS

Max. Output power 125 watt RMS  
Operating voltage (DC) 50-80 Max.  
Loads 4-16 ohms  
Frequency response measured at 100 watts 25Hz-20KHz  
Sensitivity for 100 watts 400mV @ 47K  
Typical T.H.D. @ 50 watts 4 ohms load 0.1%  
Dimensions 205 x 90 and 190 x 36 mm

The power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

### ACCESSORIES

Suitable LS coupling electrolytic for 125W model

**£1.00**

plus 25p p&p

Suitable LS coupling electrolytic for 200W model

**£1.25**

plus 25p p&p

Suitable Mains Power Supply Unit for 125W model

**£7.50**

plus £3.15 p&p

Suitable Twin Transformer Power Supply for 200W model

**£13.95**

plus £4.00 p&p

## MULLARD LP1183 STEREO PREAMP

Original listed price over £5.00 Suitable for ceramic and auxiliary inputs when you purchase 2 power module kits.

**FREE!**

## 50 WATT MONO MIXER AMPLIFIER

Six individually mixed inputs for two pick ups (Cer or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux inputs  
Power output 50 watt R.M.S. (continuous) for use with 4 to 8 ohms speakers. Finish: Attractively styled black vinyl case, with matching fascia and knobs. Complete and ready for use.

**£39.95**

plus £3.70 p&p



## 100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls  
Size approx 14" x 4" x 10 1/4". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading in. VU meter monitors output level  
Output 100 watts RMS 200 watts peak

**£76.00**

plus £4.60 p&p

Personal Shoppers EGGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N IRELAND ONLY