

# ELECTRONICS

**Australia**

**HIFI  
NEWS**

OCTOBER, 1976  
AUST \$1.00\* NZ \$1.20

STC'S PORTABLE  
MICROWAVE LINK  
FOR COLOUR TV  
BROADCASTERS



BAUDOT-ASCII PROM

**RHYTHM UNIT FOR ORGANS**  
**CAR REVERSING ALARM**  
**PRINTING VIDEOTAPES**  
**CAPACITANCE METER**

Register as a periodical - Category B

**TANDY ELECTRONICS**  
**116-PAGE FREE**  
**CATALOG**



# 3 moves into **Cassette Hi Fi** from \$270

Move in with the Sony Cassette Recorder TC135SD for \$270. For greater sophistication choose the TC136SD or the TC138SD. Both under \$500.

They all exceed Sony's own tough criteria for true Hi-Fi.

Check the specifications. There's one that meets your needs, suits your budget.

Whichever your choice you have the quiet satisfaction of knowing that it's backed by Sony craftsmanship, Sony care, Sony warranty.

Nobody else can say the same.



## TC135SD \$270\*

Frequency response: 30Hz-15kHz  
with Sony Fe-Cr, Cr02. Signal to  
noise: 59dB at 1kHz with Dolby on.  
Wow & flutter: 0.1%

Line/microphone selector

Auto shut-off.

Ferrite & Ferrite head.

Tape selector for all tapes.

Dolby noise reduction system.



## TC136SD \$320\*

Frequency response: 30Hz-16kHz  
with Sony Fe-Cr, Cr02. Signal to  
noise: 59dB at 1kHz with Dolby on.  
Wow & flutter: less than 0.1%

Line/microphone mixing

Mechanical auto-stop

FM pilot signal filter

Ferrite & Ferrite head

Tape selector for all tapes

Dolby noise reduction system



## TC138SD \$420\*

Frequency response: 20Hz-17kHz  
with Sony Fe-Cr, Cr02. Signal to  
noise: 64dB at 1kHz with Dolby on.  
Wow & flutter: 0.07%

Line out level control

FM pilot signal filter

Memory counter

Direct coupling system

Line/microphone mixing

Peak level indicator

Ferrite & Ferrite head

Dolby noise reduction system

\* recommended retail

# SONY®

Hear the difference research makes

For your nearest stockist call SONY Sydney 20 221, Canberra 95 2100, Melbourne 874 8222, Brisbane 44 7504,  
Adelaide 268 3444, Perth 81 3422, Newcastle 61 4991, Wollongong 84 8022, Launceston 2 5322, Townsville 71 4105.

GAC.S.7650






# ELECTRONICS Australia

Australia's largest-selling electronics & hi-fi magazine


VOLUME 38 No 7

## CONTENTS—OCTOBER, 1976

### world of electronics and hi-fi

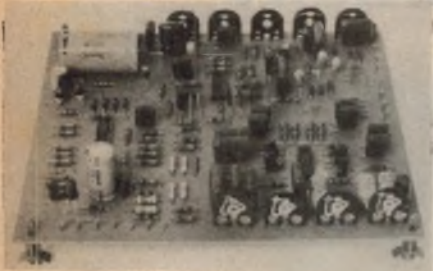

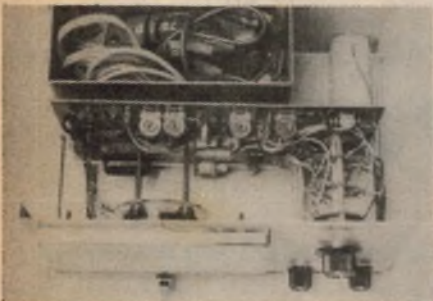Developed in our laboratory, this auto rhythm unit should find particular appeal with those readers who have been building up the Playmaster 760 organ. This month we give details of the sound circuitry which is capable of simulating eight percussion instruments. See page 38.



There must be many Saturday-afternoon mechanics who wish that they had access to an engine analyser to do their own auto tune-up work. One unit worth consideration is the Heathkit Model CM-1050 Engine Analyser, which comes as a build-it-yourself kit. Our article on page 52 has all the details.

### On the cover

The introduction of colour TV into Australia in 1975 provided the impetus to locally produce a new range of outside broadcast (OB) links. From STC Pty Ltd comes the OB7 Portable Microwave Link, a rugged, high-performance unit operating in the 7GHz band. The unit shown on the cover is currently in use with ATN-7 in Sydney. Inset depicts the evolution of our ASCII-Baudot translator program featured in this issue on page 84. The program commences as characters printed on a page, passes through the punched paper tape stage, and is finally stored in a PROM.

- 3 Editorial: Are our brand names worth saving?
- 9 Hi-Fi News:
  - Quadraphonic: dead or alive — From Audio Telex Communications Pty Ltd — Shure M24H for CD-4 quadraphonic — Digital delay system — Compatible records*
- 14 Special quality pre-recorded cassettes
- 15 How to clean cassette heads
- 19 Review: Realistic STA-90 stereo receiver
- 22 Microphones: Basics of sound and hearing
- 25 Review: B&W DM5 loudspeaker
- 30 High speed video tape printer
- 35 Hewlett-Packard Model 9825A desktop calculator
- 36 New laser may solve bio-chemical mysteries
- 60 Forum: A further look at "Instant Democracy"

### projects and technical

- 38 Auto rhythm unit for electronic organs
- 46 A direct reading capacitance meter
- 50 Audible reversing alarm for your car
- 52 Heathkit Model CM-1050 engine analyser
- 56 Build your own AC-DC multimeter
- 64 Using the CA3130 operational amplifier
- 68 Further thoughts on amateur microwaves Pt 2
- 70 The serviceman: Modern TV sets—more and more complex
- 75 Circuit and design ideas:
  - Hee-haw siren for toys — An audio-powered noise clipper — Modification to digital frequency counter — Magic-eye wide range GDO — Simple sine-wave oscillator*
- 78 Getting into microprocessors: The National SC/MP
- 84 Our first microprocessor project: ASCII-Baudot translator
- 90 Introduction to digital electronics — 9: Flipflops in registers
- 106 New products:
  - Yaesu Musen FRG-7 communications receiver — Digital clock kit from Tandy — Dynatel 500 telephone cable locator — Weston 551M marine radio telephone — Switch support bracket — Compact, low-cost digital multimeters — Changes at Optro*

### regular features

- 26 News highlights
- 97 Record reviews — classical
- 101 Record reviews — devotional, popular, jazz
- 113 Letters to the Editor
- 114 Book reviews
- 117 The amateur bands
- 120 Shortwave scene
- 123 Information centre
- 126 Marketplace — classified
- 128 Index to advertisers
- 124 Notes and errata



# Once again Europe sets the standard for speakers

## -and you install them yourself!



Sooner or later in the search for that perfect sound you come up against an inescapable fact. You have to turn to Europe.

Today's range of Philips High Fidelity Loudspeakers represents the finest that Europe has offer. We can supply full instructions for you to install them yourself.

The Philips range comprises tweeters, squawkers and woofers which you can combine into systems to satisfy the hardest-to-please sound fanatic. Some of the systems are available in kit form complete with woodwork and full assembly instructions.

To assist you in your selection we supply full performance data and details on mounting and enclosure for each speaker.

If you would like to know more about these superb imported European units, then send in this coupon:—

#### Philips Electronic Components and Materials

Sydney.....	42 1261
Melbourne.....	699 0300
Brisbane.....	277 4822
Adelaide.....	223 4022
Perth.....	65 4199

Philips Electronic Components and Materials,  
P.O. Box 50, Lane Cove N.S.W. 2066

Please send me details and enclosure  
information on your  
High Fidelity Loudspeakers.

Name .....

Address .....

..... Postcode.....



**Electronic  
Components  
and Materials**

# PHILIPS





# Editorial Viewpoint

## Are our brand names worth saving?

Involved, as we are, in the modular hifi field, we have tended to become progressively less sensitive to the inclinations and reactions of those people who still tend to think in terms of stereograms and traditional Australian brand names.

According to an executive of one of Sydney's leading retailers, people like that still exist in large numbers, and they still come into stores looking for the modern counterpart of what they've been accustomed to buying. Instead, they are faced with an array of hifi units, which have to be accommodated on table tops or shelves and interconnected with a festoon of cables and power leads. Out front there's an array of knobs far in excess of anything they have ever encountered before.

Most dyed-in-the-wool hifi fans tend simply to applaud this situation: "it's about time the mob was educated into our world, and our way of thinking"! Perhaps so, but there's one aspect of this education that I don't like.

My informant insists that there is a ready market for equipment that could be produced in Australia without too much effort, but that local companies are opting out because their managements are adopting the "easy-way-out" approach: "Let's buy something overseas and stick our name on it!"

While it may provide a short cut to a few bucks, it also forces yet more dollars out of Australian factories and into the pockets of overseas manufacturers, some large and well established, others obscure and transitory. And when later, if not sooner, the purchaser discovers that he has bought an overseas product, the credibility of the local brand name will have been thoroughly undermined, along with anything up to fifty years of institutional advertising.

I am not for one moment seeking to denigrate imported components, which nowadays dominate the local hifi scene. Nor am I deploring a natural trend from "lowfi" and "midfi" to hifi. It's just that I'm concerned about the apparent surrender of initiative—to the extent that a store executive says "we have to talk them out of a local product they want, into an imported product we can supply!"

While people have been variously happy, or unhappy, with the way colour television has blossomed in Australia, it has at least emphasised that planning, initiative and economic factors can combine to produce a logical sharing of the market between the local and imported product. And even if many smaller imported receivers carry local brands, the implications are less serious when it is common knowledge that the manufacturers concerned do have local factories, employing local people and local expertise, to produce other models in the range.

It is commonly tipped that colour TV sales will taper back from here on and the question arises as to what is going to happen to any surplus capacity. Are we going tamely to shut factories down or to seek second order activities—like family stereograms—to help sustain an indigenous electronics industry?

*Neville Williams*

### EDITOR-IN-CHIEF

Neville Williams  
M.I.R.E.E. (Aust.) (VK2XV)

### EDITOR

Jamieson Rowe  
B.A. (Sydney), B.Sc. (Technology, NSW)  
M.I.R.E.E. (Aust.) (VK2ZLO/T)

### ASSISTANT EDITOR

Philip Watson  
M.I.R.E.E. (Aust.) (VK2ZPW)

### SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

### PRODUCT REVIEWS

Leo Simpson

### TECHNICAL PROJECTS

David Edwards, B.E. (Hons, Tasmania)  
Ian Pogson (VK2AZN/T)

### GRAPHICS

Robert Flynn

### PRODUCTION

Daniel Hooper

### ADVERTISING MANAGER

Selwyn Sayers

### CIRCULATION MANAGER

Alan Parker

ON SALE THE FIRST MONDAY OF EACH MONTH

Printed by Dalley-Middleton-Moore Pty Ltd, of Wattle St, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

\*Recommended and maximum price only

### Editorial Office

57-59 Regent St, Sydney 2008  
Phone 699 3622.

Postal Address: PO Box 163, Beaconsfield 2014.

### Advertising Offices

Sydney—57-59 Regent St, Sydney 2008  
Phone: 699 3622.

Representative: Narcisco Pimentel.

Melbourne—392 Little Collins St, Melbourne  
3000. Phone: 67 8131.

Representative: Keith Watts

Adelaide—Charles F. Brown & Associates Ltd  
168 Melbourne St, North Adelaide 5006

Representative: Tom Duffy 267 4377.

Perth—454 Murray Street, Perth 6000.

Representative: Jack Hansen 21 8217.

### Subscriptions

Subscription Dept, John Fairfax & Sons Ltd,  
GPO Box 506, Sydney 2001.

### Circulation Office

21 Morley Ave, Rosebery, Sydney 2018  
Phone 663 3911.

### Distribution

Distributed in NSW by Sungravure Pty Ltd  
57-59 Regent St, Sydney, in Victoria by Sun-  
gravure Pty Ltd, 392 Little Collins Street, Mel-  
bourne; in South Australia by Sungravure Pty  
Ltd, 101-105 Weymouth St, Adelaide; in

Western Australia by Sungravure Pty Ltd, 454  
Murray Street, Perth; in Queensland by Gordon  
and Gotch (A Asia) Ltd; in Tasmania by Ingle  
Distributors, 93 Macquarie St, Hobart; in New  
Zealand by Gordon and Gotch (NZ) Ltd, Adel-  
aide Rd, Wellington.

### Copyright. All rights reserved

Devices or arrangements shown or described  
herein may embody patents. Information is  
furnished without responsibility for its use and  
without prejudice to patent rights.

All manuscripts, photographs and other  
material submitted to Electronics Australia for  
publication must be accompanied by a stamped,  
addressed envelope. Contributions are submit-  
ted at the sender's risk, and responsibility for  
loss cannot be accepted by Electronics Aust-  
ralia.





## If he were around today we know he would use it.

Throughout his career as a composer and performer, there is no doubt that Franz Liszt went first class all the way. So it's logical to suppose, if he was around today, he would choose a chromium dioxide tape for recording and playback.

It is equally logical to suppose he would choose Agfa Stereo Chrom. If you want to go first class too, choose Agfa Stereo Chrom and get unsurpassed recording characteristics, high frequency replay response, outstanding H.F. output and dynamic range, clearer tone with enhanced presence. Even the cassette features a special mechanism for better tape transport.

Agfa Stereo Chrom C60 and C90 cassettes are available at hi-fi specialists, music stores and photo dealers.

\*Registered  
trademark of  
AGFA-GEVAERT  
Antwerp/  
Leverkusen.







Lencoclean L as shown optional extra

**Presented  
with pride...**

# Lenco.

**Swiss engineered for near perfect sound reproduction.**

Photimport presents with pride, the Lenco range of precision-engineered Hi-Fi turntables. Australian test results have shown that wow and flutter are almost impossible to measure in Lenco

equipment! So, people who are looking for near-perfection in sound reproduction . . . listen to Lenco. Combine this superb reproduction with Lenco's very reasonable price and you have a very sound bargain!

**Three superb Lenco turntables.**

## Model L90

The L90 Lenco Electronic Hi-Fi. A superb, top-ranking belt-driven transcription turntable. 16-pole synchronous motor, illuminated strobe, dampened spring suspension and anti-skating device. As precise as a Swiss watch.

## Model L65

The L65 Lenco Automatic belt-driven Hi-Fi turntable. Light aluminium tone arm. After selection of record diameter, tone arm lowers itself onto the record. After playing, it returns itself to tone arm rest. Viscously dampened suspension. A high quality instrument for excellent reproduction.

## Model L60

The L60 turntable, precision engineered for great sound reproduction! Manual operation, but with all other advanced features of the L65. The L60 . . . the way to get renowned sound reproduction at a moderate price.

# PHOTIMPORT

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY


For descriptive literature and specifications, send a 30 cent stamp to  
Qualitron Industries Division of Photimport (Australia) Pty. Ltd.

Head Office: 69 Nicholson Street, East Brunswick, Vic. 3057 Australia. Telephone: 380 6922

PA10L


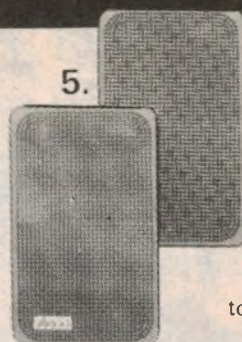
# 5 exciting new models from Nakamichi Research Inc.



1. **NAKAMICHI 610.** This highly sophisticated and versatile Control Pre-Amplifier can enable you to obtain even better results from your existing Hi-Fi equipment. The 610 can truly become the heart of any sound system due to its many and varied inputs and its superb electronic specifications — An absolute must for the true Hi-Fi enthusiast.

2. **NAKAMICHI 620 POWER AMPLIFIER** together with the 610 control pre-amplifier are both units with extraordinary performance specifications. The most striking aspect of the Nakamichi 620 power amplifier is the fact that its barely measurable total harmonic and intermodulation distortion figures are an entire order of magnitude lower than those of most high quality pre-amplifiers at all power levels right up to and beyond its conservatively rated maximum output of 100 watts continuous sine wave per channel.

3. **NAKAMICHI 250 CASSETTE PLAYER.** An entirely new compact playback only deck featuring mechanical and electrical excellence that separates it from all other cassette players of a similar size.

4. **NAKAMICHI 350 unit** has the same physical dimensions as the model 250 but with full record/playback facilities. Features include 3 low noise/low impedance microphone inputs, 8 ohm stereo headphone output, Dolby noise reduction, tape selection and a single 35dB range peak reading level meter that indicates the higher of the two channels at any given instant.

5. **ADS 2001/2002 MINIATURE HI-FI speakers** when used with either the Nakamichi 250 or 350, these speakers provide a top quality hi-fi system for use in cars, boats, bachelor flats etc., or anywhere where space is limited.

and of course the already familiar Nakamichi TT1000, 700, 600 and 550.

TT1000



**VICTORIA:** Allans Music (Aust) Ltd. (03) 63 0451 • Encl Electronics Pty. Ltd. (03) 42 3761 • Instrol Hi-Fi (Vic) Pty. Ltd. (03) 67 5831 • Southern Sound (03) 67 7869 • Southern Sound (03) 97 7245 • Tivoli Hi-Fi (03) 80 4956 • E & B Wholesale (052) 9 6616 • The Sound Craftsman (03) 509 2444 • N.S.W. Convoy Sound 357 2444 & 29 1364 • Instrol Hi-Fi Pty. Ltd. 29 4258 & 290 1399 • Milverson Pty. Ltd. 938 2205, 412 2122 & 635 3588 • Riverina Hi-Fi 938 2663/4 • United Radio Distributors Pty. Ltd. 232 3718 • Wests (Burwood) Pty. Ltd. 747 4444 • Pitman's Radio & TV (069) 25 2155 • **QUEENSLAND:** John Gipps Sound (07) 36 0080 • Premier Sound (079) 28 2701 • **TASMANIA:** Bel Canto (002) 34 2008 • **WESTERN AUSTRALIA:** Audio Distributors (092) 31 5455 • Alberts Hi-Fi • Lesley Leonards • A.C.T. Pacific Stereo (062) 95 0695 • **SOUTH AUSTRALIA:** Blackwood Sound Centre (08) 278 1281 • Ern Smith Hi-Fi (08) 51 6351 • Allans Music (Aust) Pty. Ltd. (08) 223 5533.



# WHERE THERE'S A NEED THERE'S A STANTON



Stanton have always satisfied the needs of those whose job it is to play records — of any sort. Here are some of the specific record playing tasks Stanton have been called on to cope with:—

- Lacquer masters • Metal Mothers • Quality Control • Equipment Calibration
- Transcribing of historic 78's with non standard grooves • Transcribing of cylinders • Back cueing in Radio stations and Discotheques.

Stanton developed specific cartridges and styli to satisfy these needs.

Another need arose.

Hi Fi enthusiasts and music lovers wanted performance as close as possible to the unequalled 681EEE but at a substantially lower price.

Accepting the challenge, Stanton produced the 680EE. It has many of the universally acclaimed qualities of the 681EEE. It tracks at the same pressure as the 681EEE (0.75—1.5 gms) it has the same unsurpassed channel separation of 35dB (at 1KHZ) and its frequency response is almost as wide.

**At \$51 (R.R.P.) it's almost too good to be true.**

**Audition one today and judge for yourself.**

Sole Australian Distributors:



Available at quality-conscious  
Hi-Fi dealers  
throughout Australia.

**LEROYA INDUSTRIES PTY LTD**

<b>Head Office, W.A.:</b> 156 Railway Parade, Leederville, Western Australia, 6007. Phone 81 2930.	<b>N.S.W. Office:</b> 100 Walker Street, North Sydney, N.S.W. 2060. Phone 922 4037.	<b>Victoria Office:</b> 103 Pelham Street, Carlton, 3053. Phone 347 7620.
---	---	---

LER 149





AU-11000

## The True Hi-Fi AU-11000 integrated amplifier. Involve yourself.

As the top of our line of new amplifiers, the AU-11000 really knows how to open up.

Here are some of the facts:

There is high power output to ensure the famed Sansui tonal quality. 110 watts, min. RMS, per channel, both channels driven into 8 ohms over the 20 to 20,000Hz bandwidth, with no more than 0.08% total harmonic distortion.

What this means is that you have an extra power margin that doesn't waste a fraction of the wide dynamic range and musical clarity that you'll certainly seek in an amplifier this advanced.

The AU-11000 also gives you a new toroidal power transformer and two oversized capacitors in the power supply. This assures stable power output and dynamic musical reproduction.

Finally, we've added unlimited versatility with source control convenience. A tuner switch. A tape play switch. A tape copy switch. A mode switch. Balance control. Muting switch. Level set switch. And so on. Not to mention Sansui's exclusive Triple Tone Control, which gives you an extra control for midrange sounds, in addition to bass and treble.

There are now eight new Sansui integrated amplifiers in the AU series, each with a different power rating and price tag.

If you're seeking to *involve* yourself in hi-fi, come hear us.

Sansui true hi-fi involves you at the highest levels, and lets you hear the music the way it was recorded.

It's the only product we make. It *better* be good.

### Sansui True Hi-Fi

EASTERN AUSTRALIA: RANK INDUSTRIES AUSTRALIA PTY. LTD. SYDNEY: 12 Barcoo Street, East Roseville, N.S.W. 2069  
Phone: 406 5666 MELBOURNE: 68 Queensbridge Street, South Melbourne, Vic. 3205 Phone: 62 0031 ADELAIDE: 234  
Currie Street, Adelaide, S.A. 5000 Phone: 212 2555 BRISBANE: 14 Proe Street, Fortitude Valley, Brisbane, Qld. 4006  
Phone: 52 7333 CANBERRA: 25 Molonglo Mall, Fyshwick, Canberra, A.C.T. Phone: 95 2144 / WESTERN AUSTRALIA:  
ATKINS CARLYLE LTD. 44 Belmont Avenue, Belmont, Western Australia 6104 Phone: 65 0511 / SANSUI ELECTRIC CO.,  
LTD. 14-1, 2-chome, Izumi, Suginami-ku, Tokyo 168, Japan





## Quadraphonic: Dead or alive?

Enthusiasts and the trade generally can be excused for feeling exasperated about quadraphonic sound. It's easy to write it off as dead, but then one has to explain some rather persistent signs of life. Looking at the corpse, some commentators are tipping that it's likely to be revitalised—this time without the conflict that laid it low the first time around!

by NEVILLE WILLIAMS

The quadraphonic story has been told too many times to need lengthy repetition at this point.

Sufficient to say that, a few years back, the hifi industry saw it as a technological revolution that could displace conventional stereo and create a bonanza for manufacturers of hifi hardware and software alike. So, around the world, they worked behind closed doors, played the patents game, refused to communicate and cooperate—and came up with two highly divergent methods, each with its own set of variants.

The hifi public, which was supposed to be intrigued and entranced by this new technological wonder—four signals in the one record groove—were harangued and confused by claims and counter-claims, with different interests upholding their own method and putting down all the others. As an industry exercise, it could not have been more effectively mis-handled.

The hifi public was interested, to be sure, but the uncertainty created by the argument provided them with a ready-made excuse for not facing up to the practical challenge of quadraphonic sound: where to put the four loudspeakers in the average listening room.

As for the dealers, rather than see customers perched on the horns of a dilemma, it became a lot easier to point up the uncertainties of quadraphonic and to sell them back on to high quality stereo. And that's about where we stand now; you can buy quadraphonic hardware if you want it, and you may enjoy the resulting sound no end, but you'll do it despite—not because of—the average hifi salesman!

So runs "quadraphonic is dead" story and it would seem to have been reinforced for those who had occasion, re-

cently, to look at the new range of JVC equipment at the local hifi shows.

JVC—the Victor Company of Japan—was one of the heavyweights in the quadraphonic battle. In collaboration with RCA of America, it developed and pushed the CD-4 system which made it possible to record and recover four distinct signals from the groove of a basically compatible long playing disc record. They faced and solved a lot of technological problems but, because their system makes the greatest demands in terms of hardware and software alike, it has been in the least favourable position to overcome inertia and resistance.

So while JVC have built and sold a lot

of CD-4 equipment, they can no longer afford to have their hifi fortunes tied to it. They are spreading the message that, whatever your reactions to 4-channel, JVC is still 'The Right Choice' for hifi gear of any description.

In line with this, JVC's high fidelity catalog, handed out at the Consumer Electronics Show claims credit for the CD-4 quadraphonic system and other important technological developments but goes on to feature only 2-channel stereo components suited to the market as it now stands: high performance stereo receivers with power outputs ranging up to 180 watts per channel, attractively designed integrated amplifiers, AM/FM stereo tuners, record playing systems, a whole range of cassettes decks and record players, loudspeaker systems, graphic equalisers, headphones and microphones.

It's a pretty impressive array, much of it new.

It comes through strongly that JVC's considerable resources have been re-directed into the 2-channel field until such times that the quadraphonic situation has re-developed. (For information on the latest JVC products: Hagemeyer (Australasia) B.V., 59 Anzac Parade, Kensington, NSW 2033.)

By sheer coincidence, about the time JVC distributors in Australia were emphasising 2-channel stereo, the agents for Shure passed over to us one of the last things we were expecting to see from them—a compatible stereo/quadraphonic cartridge designed for the CD-4 system.

Compatible cartridges are not new, of course, and quite a few of them have been released by other manufacturers. However, jealous of their reputation, climaxed in the V-15 Mark III stereo cartridge, Shure have for a long time shied

## FROM AUDIO TELEX COMMUNICATIONS PTY LTD



Rod Craig



Mr. Rod Craig (left) General Manager of Audio Telex Communications Pty Ltd says that his company can now offer a range of compact cassettes designed specifically for high speed duplication. Available in C30, C45, C60 and C90, the cassettes feature anti-jamming mechanics and screwed boxes; they are available boxed or unboxed, with or without labels. Audio Telex have also been appointed as Australian distributors for Bogen sound products, well known in the field of public address, intercom and background music in the USA and Canada. Audio Telex is at 54 Alfred St, Milsons Point 2061, or at 828 Glenferrie Rd, Hawthorne 3122.



# According to TRUTONE RECORDS..“The Stanton calibrated 681 series is our total point of reference in our Disc Mastering Operation”



“Carl Rowatti, Chief Engineer, adjusting the Program limiters prior to cutting a master lacquer”.

Trutone can be described as a family enterprise... but what a family! Father Lou Rowatti is the President; Son Carl is Vice President and Chief Engineer; and daughter-in-law Adrienne handles the business end of the operation. They have great pride in their family, in their family's enterprise and in their products. That's why they insist on using the best — always.

Trutone Records in Northvale, New Jersey always uses the Calibrated Stanton Triple-E for A-B comparisons between tape and disc. They also use the Triple-E to check the frequency response of the cutter head (they'll record a 1,000 Hz tone and a 10 kHz tone twice a day to check the condition of the cutting stylus and the high end frequency response of the cutter head).

They make test cuts and play them back, using the Triple-E for reference, as high as 15 kHz all the way down to 30 Hz. Carl Rowatti says “We use the Stanton Calibrated 681 series as our total point of reference in our disc master-

ing operation. Everything in the studio is judged — and we think perfectly judged for quality—with this great cartridge”. Professionals can't afford to take chances with quality. That's why they depend on Stanton in their operations.

Each Stanton 681 Triple-E is guaranteed to meet its specifications within exacting limits, and each one boasts the most meaningful warranty possible. An individually calibrated test result is packed with each unit.

Whether your usage involves recording, broadcasting, disco or home entertainment your choice should be the choice of the professionals... the Stanton 681 TRIPLE-E.

Write today for further information to:  
**LEROYA INDUSTRIES PTY. LTD.**  
 156 Railway Pde. Leederville,  
 Western Australia 6007 Tel. 81-2930  
**FOUNTAIN MARKETING LIMITED**  
 P.O. Box 5029 - Auckland, New Zealand  
 Phone 763-064



Lou Rowatti inspects a master lacquer, Adrienne checks the lathe



Carl Rowatti adjusts the pitch computer on the mastering lathe.



Carl installs the Stanton Calibrated 681 Triple-E on the playback table



Lou Rowatti (The Prez) adjusting the high frequency limiter in his cutting room.



away from the compromises which they feared they might have to accept in a compatible design.

At a seminar in Sydney a couple of years back, Ken Reichel, Shure's Chief Sales Engineer, claimed that the V-15 Mark III was very close to the design optimum for a practical stereo pickup, with low stylus mass, high compliance, very good tracking capability, the right kind of frequency response over the audible range—all this combined with a low tracking weight.

He claimed that the performance of a cartridge in the audio band (eg, up to 16kHz) would most likely be compromised by any attempt to stretch its passband to 50kHz. Almost certainly it would need to operate at a higher tracking weight and Shure was not prepared to sponsor a product that would involve trading off basic audio band characteristics for a CD-4 facility. At some time in the future they might come up with an appropriate design but until then...

Apparently that elusive day in the future has now arrived with Shure's announcement of the M24H compatible stereo/"quadriphonic" cartridge (their spelling). They claim that the M24H ranks with the finest stereo-only cartridge on the market, being "second only to Shure's V-15 Mark III... in stereo performance". The tracking weight penalty is very small: "an additional 1/4 gram of tracking force".

In its further role playing CD-4 pressings, the M24H is credited with the lowest effective stylus mass yet for a quadraphonic cartridge (0.39mg), resulting in the highest trackability (25cm/sec at 30kHz) and the lowest discrete carrier distortion at a tracking force or 1 to 1 1/2 grams.

A new hyperbolic stylus is used and a re-designed electro-mechanical structure that minimises high frequency loss and ensures a strong carrier output.


Rated audio band signal output is 3mV per channel at 1000Hz (5cm/sec), inter-channel balance within 2dB, separation 22dB at 1000Hz and load for discrete 4-channel applications: 100k in parallel with a capacitance of 100pF per channel, total. Performance curves for the cartridge are as shown herewith.

(Further details of the Shure M24H cartridge can be obtained from Audio Engineers Pty Ltd, 342 Kent St, Sydney, 2000.)

As distinct from the CD-4 "discrete" approach, the alternative matrix quadraphonic system seeks to minimise technological problems by matrixing (or encoding) the four input signals directly at audio frequencies in such a way that (hopefully) they can be unscrambled (or decoded) when the recording is played back.

While the matrix method makes very little extra demand on disc and cartridge manufacturers, it does suffer from cross-talk in that each channel ends up with a high or significant proportion of the signals that are supposed to belong to other

## SHURE M24H FOR CD-4 QUADRAPHONIC

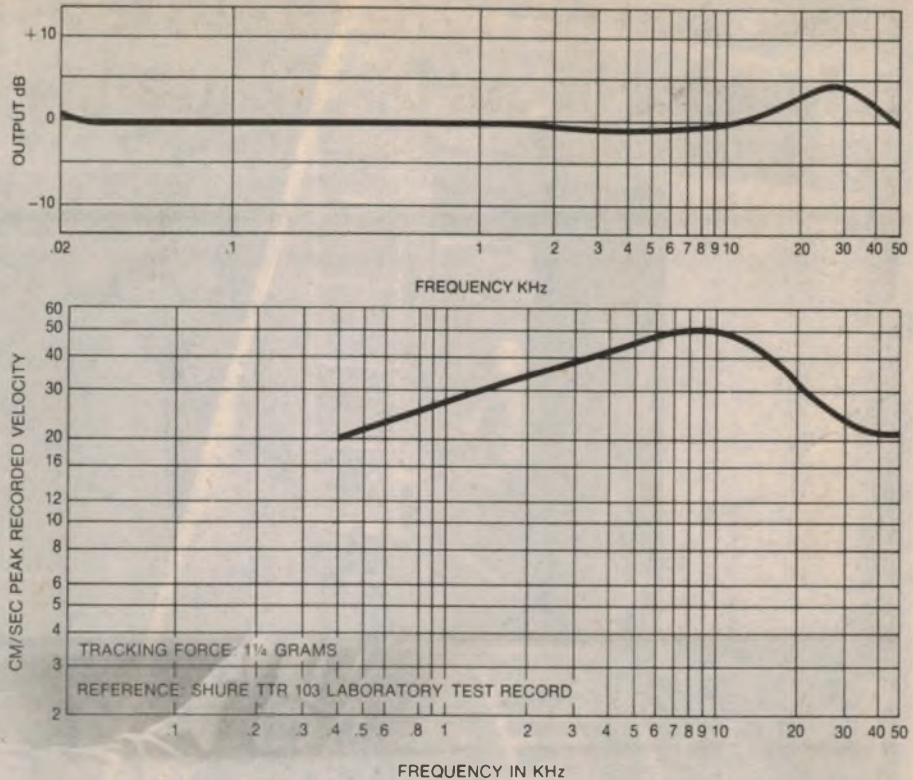

Shown at the top is the maker's published curve for the M24H which was substantially verified by our own tests. Tracking, as indicated by the second curve, was also verified, being somewhat below the top-of-the-line Shure V-15 Mark III but comparable with other premium grade cartridges. The M24H cartridge itself is pictured on the left.

channels. Separation could be up to 20dB or as low as 3dB, depending on the circuitry and channels involved.

Since those early days, Motorola, CBS, Sansui and others have come up with a variety of "logic" and "wave matching" circuitry to improve the subjective directional effect. By continually sensing the dominant signal and boosting it relative to others, the 3dB minimum figure can be pushed up to around 15 or 20dB.

This sort of signal processing can lead to much more convincing demonstrations on selected material, but it does not dispense with the basic arguments. Critics insist that, while the techniques make it possible to separate out a dominant signal or signal group, they can do nothing to improve the real separation between, say, four dominant signals occurring simultaneously, one in each channel.

While this is probably true, public acceptance of such a system depends less on laboratory tests than on the subjective appeal of typical recorded program material to typical listeners. If the appeal is high and the technology is straightforward, the ingredients for success are there, at least in the opinion of those who have a stake in the matrix system in one form or another.

So, despite the temporary lull, industry

leaders see a resurgence of quadraphonic sound reproduction within the next few years, possibly to a dominant position. Interests like Sony/CBS and Sansui have little doubt that it will centre on the matrix system because of its (externally) simpler technology and because of the fact that matrix encoded recordings can be (and are being) broadcast by FM/stereo stations without breaching the technical parameters of their licence.

Both have even more sophisticated decoding and matrix systems in their labs but both are reportedly watching closely work being done by Tate Ltd, a British audio company, and the National Semiconductor Corporation.

Just what is behind the Tate/NS endeavour is not clear at this point in time. Tate say that they have developed their approach mainly from the SQ matrix but, rather than try to patch the limitations with bigger and better logic circuitry, they've "gone back and fixed the maths"—whatever that means.

Joseph Dash, director of new product marketing for CBS is quoted as saying: "From what we've seen and heard so far, the Tate system is far ahead of anything in the marketplace or in development. If it can be successfully produced in integrated circuit form, it will bring





# Stones' Rolling Studio.




A complete recording studio in a van? For Mick Jagger, it's almost a necessity. Mick and the Stones can be inspired to produce their next hit anytime; but when they're on tour or vacationing, the best recording studios aren't always around the corner. For these moments of midnight inspiration, the Stones rely on their Shure-equipped mobile studio for the unmatched recording perfection they insist upon. Whether in a recording session or on stage, the Stones' Shure SM53, SM58, SM5C, SM33, and SM54 microphones are their assurance of consistent quality and natural sound.

Three more new Microphones from the Shure range.



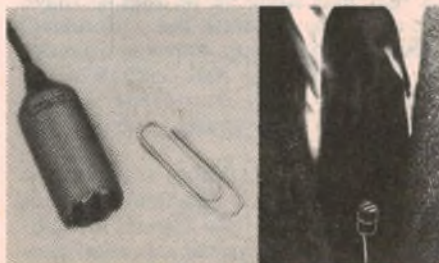
**Model PE52 Vagabond Close-Talking Microphone**



**Shure SM11 Dynamic Element Lavalier Microphone**



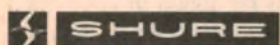**PE5EQ. The first Equalizer Microphone.**



**AUDIO ENGINEERS P/L**  
342 Kent Street,  
SYDNEY 2000 N.S.W.

**AUDIO ENGINEERS (Vic.)**  
2A Hill Street,  
THORNBURY 3071 Vic.

**AUDIO ENGINEERS (Qld.)**  
57 Castlemaine Street,  
MILTON 4064 Qld.

**ATHOL M. HILL P/L**  
1000 Hay Street,  
PERTH 6000 W. A.



## HIFI NEWS—continued

quadraphonic sound back to life".

Functionally, three chips would be required to process the normal output from the basic SQ decoder and, at last report, NS had the new chips to the stage where prototypes should be available about now. If everything works out as Tate and NS hope, it will return tens of millions of dollars over the next four or five years.

That's not a bad expectation from something that's dead!

Design target figures by the way are: 30dB separation in all directions; 0.05% total harmonic distortion; 70dB signal/noise ratio; DC controls for volume, balance and dimension; low external component count; full 4-channel hifi performance from 20Hz to 30kHz.

### DIGITAL DELAY SYSTEM

Just in case there should be any shortage of 4-channel program material (there won't be) an American company Audio/Pulse have developed a stereo digital delay system priced at well under \$1000 US intended specifically for the hifi market. It accepts the original stereo signals and produces random delay "echoes" to simulate those from an auditorium. By feeding these to a separate amplifier and to rear loudspeakers, in the manner of a quadraphonic system, a synthetic ambience can be obtained.

The Audio/Pulse unit presumably operates on the same principles as the "bucket brigade" device featured in our December 1975 issue. The incoming signals are translated into digital form and fed into a shift register which shuffles them along at a supersonic "clock rate", delaying them in the process. By sampling the signals at various points along the register, turning them back into analog form and recombining them, the end result is a synthetic multiple echo signal, rather like that obtained from earlier and less practical electro-acoustic or electro-mechanical devices.


Audio/Pulse claim that their new unit has a bandwidth of 8kHz and is free of the overtones and colourations of many such units as, for example, spring reverb units. As such, it should appeal to hifi enthusiasts who want to enhance their mono and stereo recordings without having to accept the (allegedly) overdone effects in typical quadraphonic pressings.

### COMPATIBLE RECORDS

So much for the hardware, which is where quadraphonic started a few years back, leaving software—the records—to catch up. If quadraphonic gets a new push, it may well be from the other direction, with software nurturing a consumer demand for new equipment.

When quadraphonic first made its

*Auriema (A'Asia) Pty Ltd have recently introduced five new high definition loudspeaker systems featuring increased sensitivity and crossover controls allowing them to be set flat or to suit individual listening rooms. Pictured at right is the HD 88 floor standing model with a power rating of 200W program and priced at \$550 each. Four "bookshelf" models HD 77, HD 66, HD 55, and HD 44, the last named rated at 60W program and selling for \$258 per pair. (Details from Auriema (A'Asia) Pty Ltd, PO Box 604, Brookvale, NSW 2100.)*

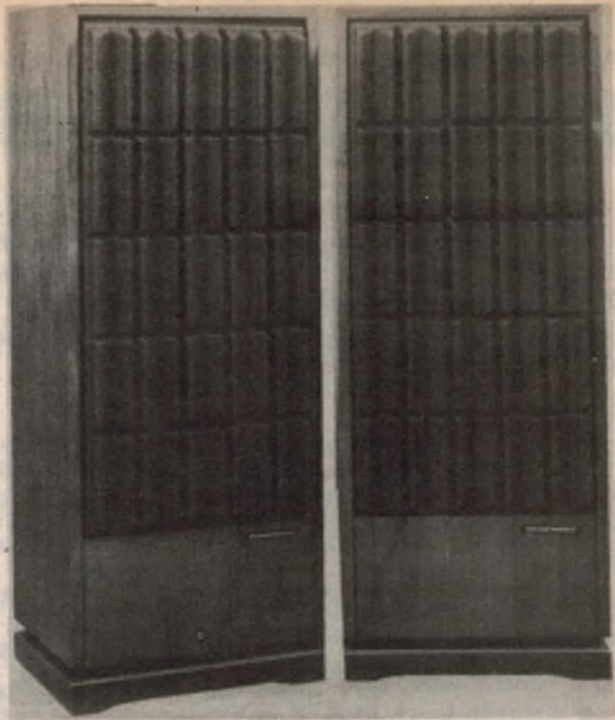

appearance, record companies made quite a fuss about their 4-channel releases. The jackets were prominently branded and, as often as not, they were grouped in a special display in retail shops. They attracted attention, to be sure, but they also underscored any failure by the retailer to stock the stereo equivalent of a quadraphonic release, and vice versa. Talk about the records being compatible didn't help much either; if a customer wanted a particular pressing, he wanted that pressing, and that was all there was to it.

It was a replay of an earlier era when shops found themselves with a dual inventory of mono and stereo pressings.

A few months back, Britain's record giant EMI decided they'd had enough of the double inventory business. As an SQ licensee, they were not willing to drop quadraphonic so they opted for the other course: whenever an SQ pressing was available, it would become the standard one for release. If the marketing situation seemed to justify it, the record would be released as compatible stereo/quadraphonic, with the jacket suitably endorsed.

Alternatively, the same pressing might simply be marketed as stereo.

While the policy is relatively new in the formal sense, it would appear that matrixed pressings have been crossing the channel into Europe for some time under "Stereo" labels and, even in Australia, the occasional "Stereo" pressing has decoded so well as to suggest that it was no technical accident. Now of course, officially designated stereo/quad compatible discs are stocked and sold here as a matter of course.

In America, things have moved more slowly but, in the latest edition of "Audio", E. T. Canby reports that

Capitol/Angel, the American arm of EMI, has also gone over to single inventory compatible. From now on, buyers of American Columbia pressings will find themselves with an SQ encoded disc in a great many cases.

Canby tips that the move by Capitol/Angel will, at the one time, confirm and establish the trend: Once again, the disc record will have re-shaped its destiny on the basis of compatibility, but now as mono-stereo-quad: one disc which can be played in three modes.

In the course of time, record collectors are going to find themselves with an increasing number of quadraphonic discs and perhaps with an inclination, next time around, to up-date to 4-channel equipment. The urge will be reinforced, for many, by the knowledge that an increasing number of FM broadcasts are also quad encoded. There may be some hang-up about SQ, QS, RM, &c, but, in the listening room, it all manages to emerge, at least, as "surround" sound.

Overall, the position looks promising for the matrix system in one form or various forms, simply because a progressive move to matrix is relatively painless at the software level. The future for CD-4 is another matter.

It could be rejected in the marketplace as "too hard", leaving JVC and RCA to lament.

Alternatively, a future 4-channel revolution could proceed beyond matrix to the disc system that offers intrinsic separation between channels.

The same could apply to 4-channel cassettes or their newer jumbo counterparts: they may be too specialised in the marketplace, or they may be taken up as the obvious way of getting full channel separation without the sum-and-difference convolutions of CD-4. ☺



# SPECIAL QUALITY PRE-RECORDED CASSETTES

by W. N. WILLIAMS

Parker Recordings, in association with M7 Records Pty Ltd, have planned a pilot marketing exercise to assess the potential demand for high quality pre-recorded cassettes. Under the name "Spectra-Frequency" the initial release involves three local popular organ recordings and two popular instrumental double albums.

The new recordings are being made at normal traverse speed on high grade tape and, while costing more, should provide a standard of reproduction well ahead of what is normally available on pre-recorded cassettes.

Behind the Parker/M7 venture lies the whole question of the quality of present-day cassette recordings. Are they good, bad or indifferent? How do they compare with the quality of disc pressings?

At the outset, it is essential to make one very clear distinction—that between a premium quality recording that an enthusiast may produce in his own home, and what he might buy over the counter in pre-recorded form.

As we have said on other occasions, the quality which is obtainable in the home with a good cassette and a good deck is such that a carefully made tape is virtually indistinguishable from the source recording, in A-B listening tests.

The burning question surrounds pre-recorded cassettes, which many enthusiasts must face up to as an alternative to discs. What is their role and how do they compare, on the whole, in terms of quality?

Certain things are obvious, of course. Cassettes are more versatile in that they can be played in the home, in the family car or in a battery powered portable. They don't need to be stored and handled as carefully as discs and it is even possible to erase them and record a new program on the same tape.

Against this, they have their own mechanical problems, they carry a minimum of jacket information and they offer a more restricted catalog choice. They cost more than discs and, overall, would appear to be not as good in terms of playback quality.

In fact, there is a close relationship between cost and quality. With discs, once the presses have been set up, the unit cost is quite modest, allowing LP albums to be offered on occasions for under \$2.00. Cassettes, however, have to be recorded, assembled and checked individually, using components that are more costly in total than a vinyl biscuit. The constant battle, therefore, is to get the price down to a figure that does not look too daunting alongside that of the equivalent disc.

In order to speed up the transfer from master tape to cassette tape, it is usual

to run both at several times their normal traverse speed, transferring all four tracks in a single pass. This makes heavy demands on the mechanics, the heads and the electronics and, in particular, increases the audio frequencies by the same ratio. Assuming that the transfer takes place at from 8 to 16 times normal speed, the higher audio frequencies are stepped up to somewhere between 100kHz and 240kHz.

While such frequencies are not exceptional in terms of video technology, the price level at which the end product has to be sold is—and this includes the tape, which has to receive an RF signal, deliver an AF signal and cost not a cent more than it strictly has to. The manufacturers' first objective must be to satisfy the mass market; whether they can also meet the demands of hifi enthusiasts is another matter.

Such a statement may be highly controversial but it has a practical basis.

Disc production is a highly developed technology which is intrinsically capable of yielding wide frequency response, low

distortion and a very low noise level. Whether a manufacturer achieves these results is not a matter of basic technology but of fairly routine quality control.

With cassette duplication, on the other hand, there is a sharp conflict, at present, between performance and price. A high quality cassette, recorded at normal speed on good equipment, can hold its own with any record. But, as the process is speeded up and cheaper tape is substituted to reduce price, quality falls along with it.


There are exceptions, of course: better than average cassettes and poorer than average discs. What is more, playback equipment and the enthusiast's own ears can influence opinion.

Typically, a prominence in the cartridge or speaker system around 6-8kHz can greatly exaggerate surface noise from a disc, and this is behind a great many of the comments one hears that "discs are noisy".

Tape doesn't suffer this problem but it can suffer from hiss and a loss of top audio response.

Thus a middle-aged listener may genuinely conclude that cassettes are quieter than discs and just as good in terms of response; just as genuinely, a younger listener may reject cassettes as "hissy" and lacking in sparkle.

My own reactions along these lines

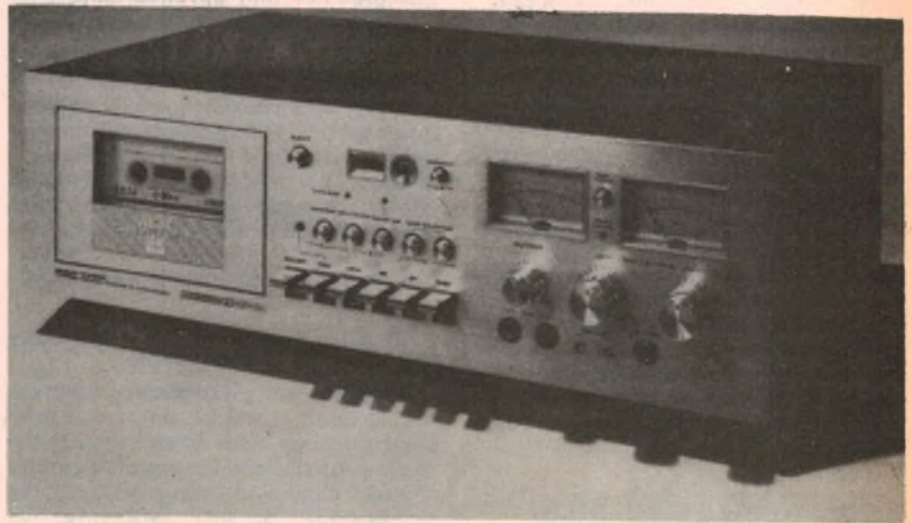

With a modern cassette deck, a hifi enthusiast can make recordings virtually indistinguishable from the source, as judged by ear. The problem is to obtain pre-recorded cassettes of equal quality. The deck pictured is Akai's new front loading model GXC-740D. Three heads make possible true off-tape monitoring, while a closed loop, double capstan drive system minimises wow and flutter. Separate Dolby circuits are provided for recording and playback and there is internal provision for accurate setting up. The meters can operate either as VU meters or for peak indication, while peak warning lights flash at the 7VU level.



have been sharpened recently by a series of listening tests involving direct A-B comparisons between commercial discs, commercial pre-recorded cassettes with and without Dolby processing, and high quality cassette dubbings made directly from sub-master open reel tapes. The inescapable conclusion was that, while high-speed pre-recorded cassettes may sound okay in isolation, and meet the needs of the bulk market, they fall consistently short of the equivalent disc played with a high quality cartridge.

From the viewpoint of the quality enthusiast, a problem therefore remains to be solved.

Curiously, the poorest cassette in the whole batch was one which had been Dolbyised, apparently with dire results to the top end. It reminded us of remarks we had seen in overseas journals indicating that Dolby-boosted highs can easily be attenuated again, "crushed" by a tape that lacks "headroom". When the recording is played back Dolby fashion, what is left of the highs tends to be attenuated further, leading to very dull sound indeed.

The lesson is simple enough: If Dolby is to be used and specified, it has to be used properly!

About 12 months ago, Convoy, in association with Goldring released their Contata series of special quality cassettes, employing Dolby-B but also recorded on TDK tape. Broadly, the Contata cassettes have received good reviews, but in isolation, and without the opportunity for comparison with their disc counterparts. When making the cassettes available to us for review, Malcolm Goldfinch, Managing Director of Convoy, indicated strongly that their release represented a conscious effort to offer customers an above average product from the viewpoint of playback quality, directed initially to the popular and drive-time market.

The new "Spectro-Frequency" cassettes are something else again, largely reflecting the personal interest of Parker Oakes of Parker Recordings and Ron Hurst of M7 Records. They go the whole way, in terms of quality, by being recorded directly on top quality cassettes at normal playing speed. Since they are copied from a high quality 15ips sub-master, they should readily stand comparison to a top quality disc pressing of the same material.

When the project was first envisaged, Parker Oakes spent many hours personally evaluating blank cassettes and, while there were many candidates and many excellent cassettes available, his choice finally fell on TDK Super Avilyn—the most expensive of the group in terms of his own buying price.

Since he would be working from masters which had been mixed and monitored for the needs of recording, and since "headroom" would not be likely to be a problem, it was further decided that all Spectro-Frequency cassettes would

## HOW TO CLEAN CASSETTE HEADS

Just as the stylus of a disc record player has to be kept free of lint or other build-up, so it is necessary to keep clean the heads of tape recorder/players. It is particularly important with compact cassette equipment because of the very narrow tracks and the fact that the heads are tucked away out of sight—and out of mind!

While manufacturers seek to ensure a good bond between the coating and tape base, some rub-off of coating and lubricant does inevitably occur—a minimal amount in the case of the best tapes, considerably more with tapes of more dubious origin. Where a build-up does occur, evident as a brownish coating on the exposed surface of the head, it tends to lift the magnetised coating away from the magnetic gap, reducing output and high frequency response during playback and impairing recording as well.

The amount of build-up tends to vary with the particular deck and the type of tape commonly used with it, but the fact remains that all tape deck owners should be alert to the possibility of head fouling and must expect to encounter it from time to time.

The question which follows, of course, is how to keep the heads clean and this leads naturally to the observation as to how NOT to do it. Heads must NEVER be scraped with a tool nor rubbed with emery cloth or any other workshop or household abrasive. Such treatment may roughen the residue without totally removing it, or it may score the head, or it may cause microscopic chipping. A further danger is that any force applied to the head may upset its quite critical alignment.

Much the preferred method is to dissolve and remove the coating with the aid of a "cotton bud" or equivalent (a small ball of cotton wool on a match-stick) moistened with methylated spirit. If you want to be ultra-fussy, use the pure form obtainable from a chemist. A couple of rubs every now and again will keep the head surfaces completely clean.

Use only methylated spirit or a cleaning expressly provided with a deck for head cleaning. Deck manufacturers are nervous about using other general purpose "electrical" fluids on tape heads, because of the possibility of some of the

be recorded Dolby-B. For optimum results therefore, the playback deck should be set for "Dolby On" and "Cr0-2"—the latter being explained by the fact that TDK-SA is normally recorded with the same settings as for chromium dioxide tape.

Where the deck does not have either or both of these provisions, the "Cr0" requirement can be ignored and the "Dolby" characteristic approximated by a small amount of treble cut in the



reacting on materials involved in the head construction.

If the heads are inaccessible, or you are nervous about fiddling with them anyway, a simple alternative is to purchase and use a head cleaning cassette such as the one pictured, put out by TDK. It contains a short length of a specially fabricated tape, carrying just enough cleaning formulation to remove the coating from heads, without damaging them. In fact, the literature claims that periodic use of the Head Cleaner cassette type HC-1 will control build-up on other components such as guides, capstans and rollers.

The head cleaner is loaded with the specified side up and operated in exactly the same way as an ordinary cassette. TDK suggest that it be placed in position and the deck switched into play mode. When the tape stops, rewind and repeat the procedure.

As a guide, they suggest that it be used after about 10 playings of ordinary cassettes, limiting use of the cleaner to about 24 occasions. On this basis, one TDK head cleaner would typically cope with about 200 hours of deck use.

But, even if you decide to rely in some degree on the cotton bud and metho treatment, a head cleaner cassette would obviously be a handy gadget to have around as a quick and easy method of making sure.

Distributors for TDK in Australia are Convoy International Pty Ltd, 4 Dowling St, Woolloomooloo, NSW 2011.

amplifier setting.

The Spectro-Frequency cassettes are individually copied at normal speed on Nakamichi decks, fed with signal from a Revox A77 playing the working master at its correct speed of 15ips.

Four albums were selected for the initial Spectro-Frequency release—two double albums from the M7 label and two "Parker" single albums.

The double albums are "Apollo 100" and "Rogers, Hammerstein & Hart", the



# C.E.C. has a turntable to turn YOU on...



BD1000

**the ideal system starter  
BD1000 complete with  
EMPIRE 2000 E cartridge**

- Wow and flutter less than 0.12%.
- Rumble better than 40DB.
- Complete in fully imported base and cover.


Frequency response 10HZ to 30KHZ tracking 1 to 3GM.



BD7000

## for the audiophile BD 7000

- DC Hall motor—Servo controlled.
- Built-in strobe light.
- Fine speed adjustment.
- Auto or manual operation.
- Wow and flutter less than .04% (WRMS).
- Signal to noise ratio 65DB (DINB).
- Tracking weight 0.25 to 3GM.
- J-shaped tone arm with hydraulic cueing.
- Magnificent, fully imported base and cover.  
The BD7000 is supplied without cartridge.

The  turntable range includes the semi-automatic BA300 and fully automatic BA600. One of the four models is right for you. All have the famous C.E.C. 5-YEAR WARRANTY.



 **harman australia pty ltd**  
271 Harbord Road, Brookvale, Tel 939 29 22  
PO Box 6, Brookvale NSW 2100



latter recorded in the Sydney Opera House with Tommy Tycho and his Good Music Orchestra. Double albums like these lend themselves to the Spectro-Frequency concept because they will fit on to the one C90 blank cassette, thereby simplifying production and minimising cost. It is anticipated that each double album cassette will retail for about \$11.98.

The two "single album" cassettes are both of music from the Parker label: "Beyond The Blue Horizon" with Reubert Hayes playing the Conn Theatre organ, and "Ray Thornleigh Entertains, Vol 1", another organ record but this time a Lowrey. These tapes will be priced at \$7.98 each, as compared with \$5.98 for the ordinary high speed cassette and \$4.98 for the disc.

Because of their specialised nature and limited release, the Spectro-Frequency cassettes may not be available ex-stock from all suppliers but they can be ordered by record dealers and departments from M7 Records Pty Ltd, at 28 Cross St, Brookvale, NSW.

Another M7 release, Reubert Hayes' very successful "Favourites of the Forces Sing-Song", recorded in the first instance by Parker, is also being made available in the new format cassette. However, it will be available only by mail order direct from Parker Recordings at P.O. Box 134, Toongabbie, NSW 2146. The price is \$7.98 plus 50c pack and post (for each cassette) within Australia.

At the time of writing, we have had the opportunity of comparing four of the five special cassettes with their disc counterparts. Each pair was played back on high (but typical) quality disc and tape decks, started simultaneously, fed into the one amplifier and directly compared by switching from one to the other.

With "Rogers, Hammerstein and Hart", there was virtually nothing to choose between cassette and disc.

With "Favourites of the Forces Sing-Song", and "Ray Thornleigh Entertains", opinion marginally favoured the cassette.

With "Beyond The Blue Horizon", the cassette was well ahead of the original disc PRS-008. However, the disc has more recently been recut by Ross Sheard of Sheard & Co Pty Ltd, and simultaneously re-balanced using UREI third-octave graphic equalisers; it now carries the number PKS-008. We marginally preferred this new disc to the cassette because, while the latter was slightly brighter at the top end, the disc had better weight and "roundness" in the middles.

However, in passing such opinions, we are splitting straws. The interesting point is that M7 and Parker have decided to test the market with pre-recorded cassettes that lose nothing by comparison with good discs played on good, flat pickups.


Whether quality enthusiasts will respond is something that the respective backers will have to discover the hard way!

## STYLI, CARTRIDGE REPAIRS

A new venture by Messrs Bay Road Electronics, of Cheltenham, Victoria, spells good news for users of magnetic pickup cartridges. The company has set up facilities for the repair and adjustment of cartridges and, as well, specialises in fitting new parabolic diamond styli.

Fortunately, cartridge service and the replacement of worn styli is not a universal problem. In many cases, back-up service is available from the distributors but, there are brands and models where adequate service facilities do not exist or where they are uncertain or expensive.

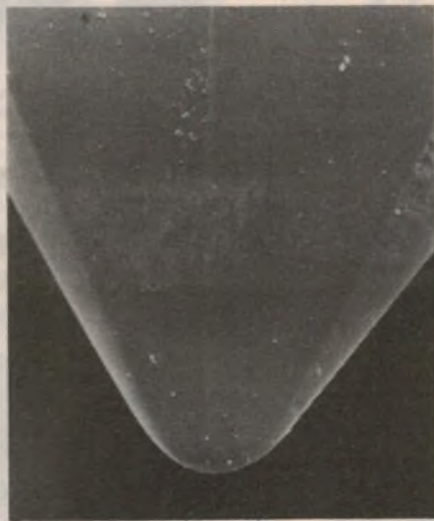While it might be too much to hope that a repair facility could cope with any model of cartridge, we gathered from Mr Peter Wright that Bay Road Electronics



A microphotograph of an elliptical stylus, magnified 1850 times, and taken by the Electron Microscope Unit of the Royal Melbourne Institute of Technology.

are building up stocks of spare parts and, in special cases, they can fabricate such items as stylus cantilevers, etc. Their expertise also extends to moving coil cartridges.

This is only half the story, however. As a vital part of their involvement in cartridge servicing, Bay Road Electronics are specialising in fitting new parabolic diamond styli in the place of original, worn styli or more conventional shape. They claim that they are "grain orientated" and polished to a precision well beyond that of normal production styli. As a result, record wear is minimised, as well as stylus wear.

If a cartridge is in good condition otherwise, with only the original stylus worn, the policy of the company is to remove the original diamond and replace it with a new parabolic type, leaving the cantilever and suspension otherwise untouched.

As for the parabolic shape, it has been brought into prominence by concentrated work on the CD-4 quadraphonic system which makes it desirable to dis-



A microphotograph of a parabolic stylus also magnified 1850 times. Note the two shoulders, forming an angle of 90 degrees, which sit snugly against the walls of the groove,

tribute the playing weight vertically up the groove sides, while retaining the ability to track frequencies to well over 40kHz. As a result of this work, it has become possible to produce specially shaped styli to within very close tolerances and at a price which has allowed Bay Electronics to extend the practice into standard non-CD4 stereo cartridges.

As an indication of their service, Bay Road Electronics submitted to us several examples of well known cartridges fitted with the normal manufacturer's styli and their own special parabolic styli. We were invited to make comparisons between them.

Here we were at a disadvantage. While it sounds easy to say: let's check a few cartridges for waveform and trackability at a variety of typical playing weights, the job of actually fitting up each cartridge and performing the tests can become quite time consuming—too much so, in fact, to make possible a statistically adequate sample. We remained in some doubt therefore, as to what extent we were looking at cartridge differences rather than styli differences.

The one thing we can say with certainty, however, is that the refitted cartridges behaved as we would have expected them to do and this would be the vital consideration for any hifi enthusiast faced with a traumatic stylus problem.

(For further information: Bay Road Electronics, 36 Luxmoore St, Cheltenham, Vic 3192. Tel. Melb. 93-1201).





## Does your system hunger for one?

Hi fi systems also need the right kind of nourishment. One of the most effective ways of providing it is featured above: the AKAI AA-1020 AM/FM Tuner Amplifier.

It puts out 20 effortless watts RMS per channel (both channels driven, from 20 to 20,000 hz, no more than 0.4% THD into 8 ohms load). It comes with the kind of facilities that produce the best kind of sound. And at \$340†, the price isn't likely to turn you off.

But maybe your system hungers for a lot more power, in which case

you should see our more powerful models.

Of course, like all AKAI hi fi equipment distributed by AKAI Australia, it comes with our Complete Protection Plan\*. Which simply means 12 months full parts and labour warranty on all Tape Equipment, 2 years full parts and labour warranty on all Amplifiers, Turntables and Speakers and a lifetime warranty on all GX Tape Heads.

So, if your amplifier isn't all it should be, see your AKAI dealer. He'll put your mind at ease.

The AKAI Hi-Fi Professionals are: **NEW SOUTH WALES — SYDNEY CITY AND METROPOLITAN** Sydney: Douglas Hi-Fi, 338 George Street; Duty Free Travellers Supplies, 400 Kent Street; European Electronics, 187 Clarence Street; Instrol Hi-Fi, Cnr Pitt & King Streets; Magnetic Sound Industries, 32 York Street; Jack Stein Audio, 275 Clarence Street. **Bankstown:** Selsound Hi-Fi, Cnr North Terrace & Apian Way. **Burwood:** Electronic Enterprises, 11 Burwood Road; Edge Electric, 31 Burwood Road. **Concord:** Sonarta Music Services, 24 Cabarita Road. **Cremorne:** Photo Art & Sound, 287 Military Road. **Crows Nest:** Allied Hi-Fi, 330 Pacific Highway. **Hurstville:** Hi-Fi House, 127 Forest Road. **Liverpool:** Miranda Stereo & Hi-Fi Centre, 166 Macquarie Street. **Miranda Fair:** Miranda Hi-Fi & Stereo Centre, Shop 67, Top Level. **Mona Vale:** Warringah Hi-Fi, Shop 5, Mona Vale Court. **Parramatta:** Gramophone Shop, Shop 151, Westfield Shoppingtown; Selsound Hi-Fi, 27 Darcey Street. **Roselands:** Roselands Hi-Fi, Gallery Level. **South Hurstville:** Selsound Hi-Fi, 803 King George's Road. **Summer Hill:** Fidela Sound Centre, 93B Liverpool Street. **Sutherland:** Sutherland Hi-Fi, 5 Boyle Street. **Waitara:** Hornsby Hi-Fi, 71 Pacific Highway. **Westleigh:** Sound Incorporated, 16 Westleigh Shopping Centre. **NEW SOUTH WALES COUNTRY** **Albury:** Haberech's Radio & TV, 610 Dean Street. **Bega:** East Downs, 187-191 Carp Street. **Bowral:** Fred Hayes, 293 Bong Bong Street. **Broken Hill:** Pee Jay Sound Centre, 364 Argent Street. **Gosford:** Gosford Hi-Fi, 163 Mann Street; Miranda Stereo & Hi-Fi Centre, Cnr. **Dunnison & Baker Streets**. **Moss Vale:** Bourne's Merchandising, 1 White Street. **Newcastle:** Ron Chapman Hi-Fi, 880 Hunter Street; Eastern Hi-Fi, 519 Hunter Street. **Nowra:** Nowra Hi-Fi, Shalhaven Arcade. **Taree:** Taree Photography, Graphic House, 105 Victoria Street. **Wagga Wagga:** Haberech's Radio & TV, 128 Bavis Street. **Wollongong:** Hi-Fi House, 268 Keira Street; Selsound Hi-Fi, 2-6 Crown Lane. **A.C.T. CIVIC:** Allied Hi-Fi, 122 Bunda Street. **Fyshwick:** Allied Hi-Fi, 3 Paragon Mall; Gladstone Street. **QUEENSLAND** **Brisbane:** Chandler's, 120 Edward Street; Chandler's, 399 Montague Road. **West End:** Stereo Supplies, 95 Turbot Street; Tel Air Electronics, 187 George Street. **Nambour:** Custom Sound, Currie Street. **Mt Isa:** The Sound Centre, West Street. **Rockhampton:** Chandler's, 144 Alma Street. **Southport:** Stokes Electronics, Scarborough Street. **SOUTH AUSTRALIA:** **Adelaide:** Ernsmiths, 48-50 King William Street; Flinders Trading Co., 55 Flinders Street; J.B. Electronics, 115 Gouger Street. **Blackwood:** Blackwood Sound Centre, 4 Coromandel Parade. **Glenide:** Steiner Electronics, Conygham Street. **Moana:** Bob Carmen, 185 Commercial Road. **VICTORIA** **Melbourne:** Douglas Hi-Fi, 191 Bourke Street. **Warrnambool:** A.G. Smith, 159 Liebig Street. **WESTERN AUSTRALIA:** **Perth:** The Audio Centre, 883 Wellington Street. **Calista:** Hub Hi-Fi, Kwinana Hub; Gilmore Avenue. **East Victoria Park:** Japan Hi-Fi, 889 Albany Highway. **Nedlands:** Audio Distributors, Broadway Shopping Centre, Broadway. **Midland:** Midland Audio, 16B Great Northern Highway. **Mosman Park:** Audio Distributors, 14 Glyde Street. **W.A. COUNTRY** **Bunbury:** Aabel Music, 130 Victoria Street. **Kalgoorlie:** Hambley's Hi-Fi, Shop 13, Central Arcade. **Hannan Street.** **TASMANIA** **Burnie:** James Laughran & Sons, 29-31 Wilmut Street. **Hobart:** Quantum Electronics, 181 Collins Street. **Launceston:** Wills & Co., 7 Quadrant. **NORTHERN TERRITORY:** **Darwin:** Pfitzner's Music House, Smith Street.

\*The Complete Protection Plan does not cover equipment purchased outside Australia. †Recommended retail price only.

70813R

**AKAI**  
The name you don't have to  
justify to your friends.



# Realistic STA-90 stereo receiver

The "Realistic" brand is available only from Tandy stores. Here we review the Realistic ST-90 AM / FM stereo receiver, which has a conservative power rating of 44 watts RMS per channel. It has comprehensive control facilities and conforms to Australian electrical safety standards.

Some high fidelity enthusiasts may have the impression, mistaken though it is, that "Realistic" is an economy line with all the compromises in quality which often seem to accompany an economy price. This review will clearly demonstrate that the Realistic STA-90 is a high performer which more than favourably compares with its many Japanese competitors.

In fact the Realistic STA-90 is manufactured in Japan to the American design, using the same high quality components as used in most well-known Japanese receivers.

Styling of the STA-90 follows conventional lines with an extruded aluminium control panel with "scratch-grain" finish, matching knobs and "blackout" dial. Overall dimensions are 485 x 147 x 360 (W x H x D) including knobs, rubber feet and rear terminals. The swing-down AM rod antenna requires an extra 50mm of clearance at the rear. Mass is approximately 12kg.

Control facilities on the front panel are again fairly conventional, with the exception of some minor features which set the receiver apart from its competitors. Two sets of loudspeakers can be controlled by the Loudspeaker selector which provides functions: Off, A, B, A + B and Q VOX. The last setting is an abbreviation for Quatravox which is Realistic's term for the "synthetic quad" mode obtained

by connecting the rear loudspeakers in series across the stereo output sockets.

When either the AM or FM tuner is in use the dial lights up together with the tuning meters. An unusual stereo beacon is employed. Instead of having a stereo beacon light on the dial, the dial pointer changes colour from white to red when a stereo FM station is being received.

Two meters are provided to facilitate tuning. They have no calibrations but they still perform useful signal indication.

Two jack sockets are provided for a pair of stereo headphones and "Dub Out". The latter refers to a signal output for convenient connection to a tape recorder. This would normally be connected to the "Line Input" sockets of a tape recorder in the same way as would the two pairs of "Tape Rec" outputs on the rear of the receiver.

Five positions are provided on the Input Selector: Auxiliary, Phono, AM, FM and FM Mute. The last-named gives muting of interstation noise when tuning. An interesting feature of the Selector is that its rotary knob controls a large multi-contact slide switch.

An interesting feature of the rear panel is the clamp for the mains cord which provides capacitive coupling into one of the 300 ohm FM antenna terminals. This rudimentary antenna can be satisfactory

in strong signal areas, but those not so well served will have to make their own folded dipole with 300 ohm ribbon or resort to a more elaborate roof-mounting antenna.


Two 2-pin AC outlets are provided on the rear panel and Tandy have taped them over with warning labels noting that they are 240VAC not 120VAC.

Removing the timber wrap-over cover of the STA-90 reveals the large chassis. The PC board at the rear accommodates the AM and FM tuners while the much larger PC board at the front accommodates the preamplifiers and power amplifiers. A large black-anodised aluminium extrusion provides generous heatsinking for the four power transistors.

Circuitry of the STA-90 is fairly conventional, with discrete transistors used throughout the preamplifiers and power amplifiers while a mixture of integrated circuits and transistors is used in the tuners.

The power amplifiers have balanced positive and negative supply rails and direct coupling to the output by dint of the differential input stages. The output stages operate in quasi-complementary mode. Two small-signal transistors monitor the current in the output stages and remove the input signal from the driver stages if the output is short-circuited or otherwise overloaded.

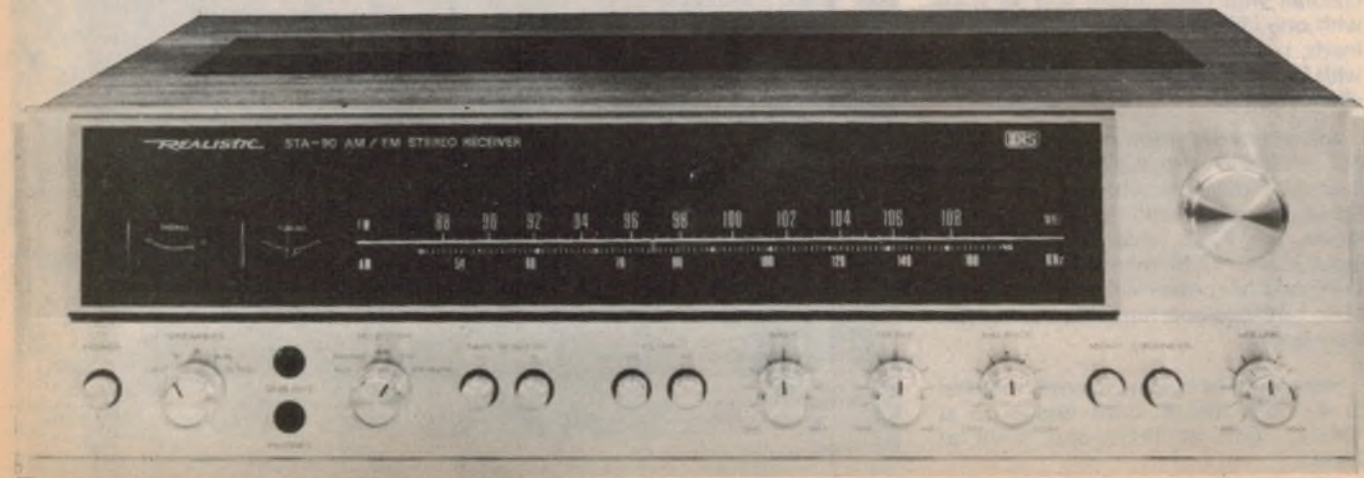Complementing this short-term overload protection system is a thermal cutout which interrupts the AC mains if the main heatsink temperature becomes excessive. As well, there is a fuse in the primary circuit of the power transformer.





## REALISTIC STA-90 RECEIVER

We would also like to see fuses installed in the positive and negative supply lines to the power amplifiers. These would blow in the case of internal damage to the amplifier, and thus help prevent possible damage to the loudspeakers. Alternatively or in addition, a separate loudspeaker protection circuit could be installed. This general comment applies to any receiver or amplifier with direct-coupled outputs. Replacement loudspeakers can be very expensive!

Performance specifications of the STA-50 as shown in the owner's manual is brief and apparently conservative. Power output is quoted at 44 watts RMS per channel into 8 ohm loads over the range 20Hz to 20kHz, and at less than 0.5% harmonic distortion. This spec was

Phono sensitivity is 3mV for 40 watts while overload capability at 1kHz is more than adequate at 150mV. RIAA equalisation is within 1dB over the range 100Hz to 15kHz with a slight boost at 50Hz and rolloff below 30Hz. Frequency response of the preamplifiers and power amplifier is 1dB down at 20Hz and 20kHz. Square wave response was good, and stability with capacitances shunting the load was satisfactory. There was a slight anomaly in the response when the load was shunted with a 2uF capacitor. This produced a boost of 7dB at 30kHz.



We can sum up the FM tuner performance as excellent and likely to be bettered by few receivers, regardless of price. This applies particularly to the Quieting curves. Total harmonic distortion for mono reception was 0.2% at

100Hz, 0.1% at 1kHz and 0.5% at 6kHz. In stereo, THD results were 0.4% at 100Hz and 1kHz and 1.2% at 6kHz. 19kHz residual was 47db with respect to 100% modulation.

AM tuner performance is typically poor, as we have come to expect from most stereo receivers. Never mind . . .

We found the STA-90 easy to use with its uncomplicated control layout. All controls operate smoothly and progressively, and the unit is quiet when no signals are present. Nor is electrical interference a problem.

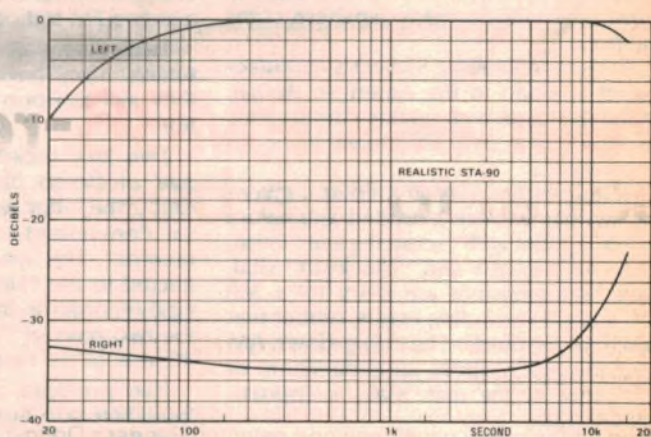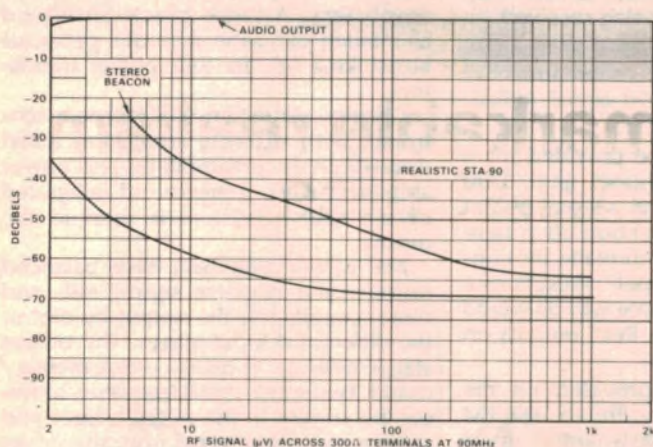In short, high marks can be awarded for the performance of the STA-90 by Realistic. It is a well made product with the advantage of a large distributor network and extensive servicing facilities. Recommended retail price of the STA-90 is \$399.95. Discounts are available if purchased in a package deal. Realistic audio products are available from Tandy stores throughout Australia. (L.D.S.)




Above are the excellent Quieting characteristics plus the frequency response and separation between channels of the STA-90 FM tuner circuitry.

confirmed with plenty to spare.


We measured maximum power output at 53 watts per channel into 8 ohm loads with both channels driven. With one channel, the result was 62 watts. With 4 ohm loads, the result was 30 watts per channel with both driven and 36 watts with one channel driven. With 16 ohms loads, power was 36 watts per channel with both driven and 39 watts with one channel driven.

Maximum distortion reading was 0.2% but readings were typically much less than 0.1% over the whole audio range. Signal to noise ratio for the auxiliary inputs was 75dB while for the phono input it was 72dB referred to 10mV at 1kHz and full power with a typical magnetic cartridge and turntable connected. Very good!

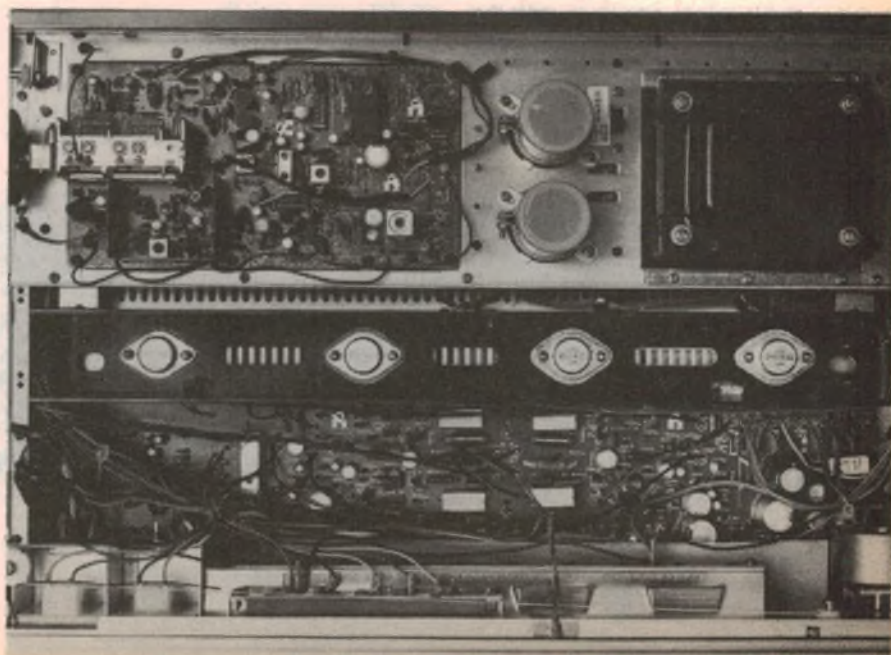Separation between channels referred to 40 watts into 8 ohms was 37dB at 100Hz, 50dB at 1kHz and 37dB at 10kHz.





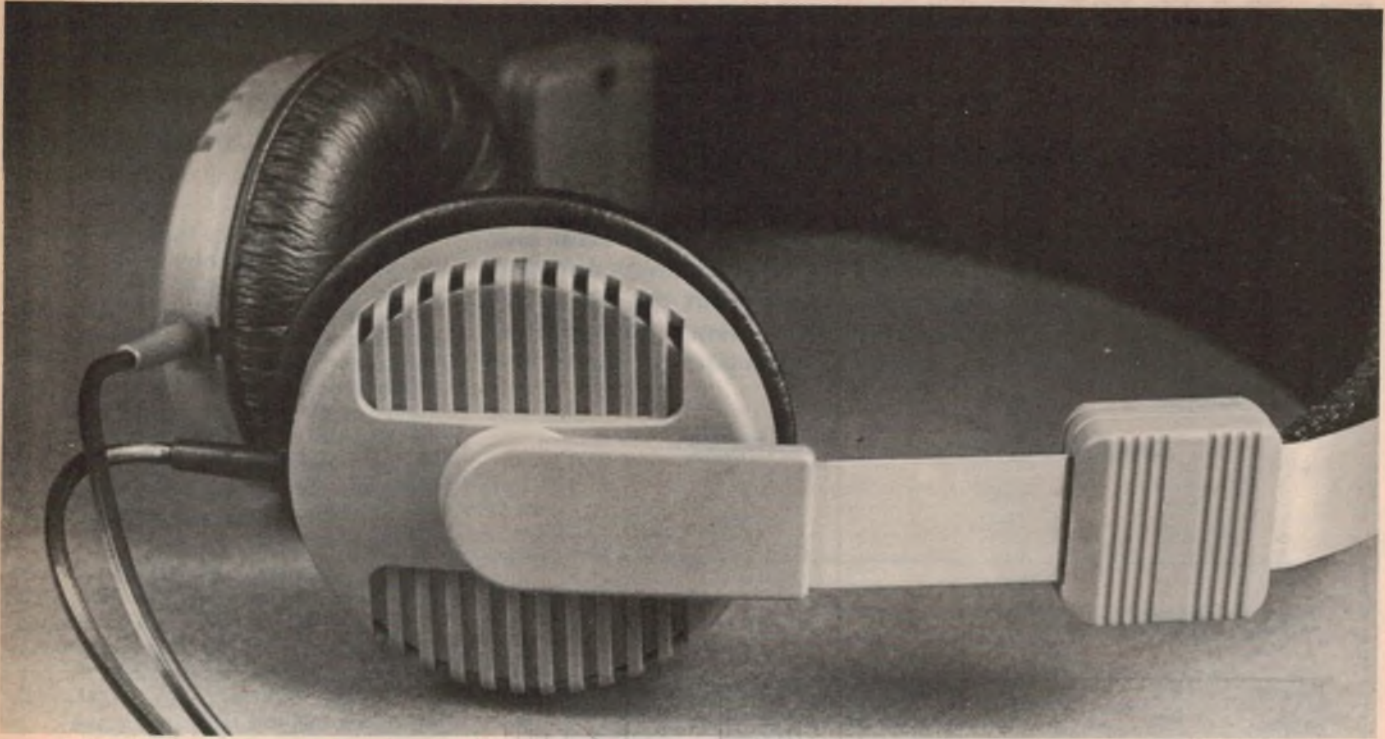

# Peerless PMB6 - remarkable realism equal to the best electrostatics

## New Peerless Orthodynamic principle - this is really living

With Peerless PMB6 headphones everything you hear is true. Based on the newly developed and patented Peerless Orthodynamic principle, PMB6 headphones deliver reproduced sounds equal in quality to the most sophisticated electrostatics. Peerless bring it back alive - sounds so real, you feel you're actually there.


## In one ear and in the other - in total comfort

There's nothing more annoying than headphones that clamp you in a head-lock. With Peerless featherweight construction, fine fit and pillow-soft ear pads, absolute comfort is certain over long time listening.
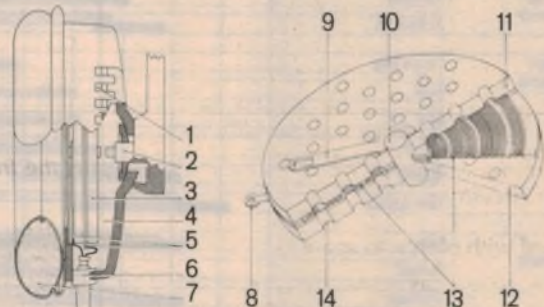
## Until you've heard it through Peerless - you just haven't heard it!

Between two perforated ferrite magnet discs lies an ultra thin diaphragm/voice coil. This light and very elastic diaphragm, whose total surface is put into motion, makes crystal clear high frequency reproduction possible. Its construction also ensures uniform phase characteristics and low distortion. The diagram below details this novel new design.

In your favourite piece of recorded music, you'll hear notes and nuances you'd never have believed existed.




1. Air holes. 2. Ball joint suspension. 3. Drive unit. 4. Damping material. 5. Terminals. 6. Cable grip. 7. Ear pads. 8. Terminal. 9. Terminal. 10. Centre axle. 11. Magnet. 12. Magnet. 13. Diaphragm/voice coil. 14. Hole in magnet.

## Peerless PMB6 Technical Data

Frequency:	Range 16-20,000 Hz
Impedance:	140 Ohms
Max. Constant Load:	40 dB
Operating Power:	2.5 mW
Distortion:	1%
Rated Input:	2W (DIN)
Weight:	210 g
Colours:	Black, Red and Olive Green

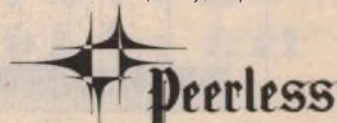**Peerless PMB6 \$49**

Electrostatic quality, superb comfort and a realistic price



Danish Hi Fi Shop 9, Southern Cross Hotel, Melbourne. Telephone 63 8930. Danish Hi Fi 698 Burke Road, Camberwell, Victoria. Telephone 82 4839. Convoy Sound 1 Maclean Street, Woolloomooloo, N.S.W. Telephone 357 2444. Convoy Sound 387 George Street, Sydney. Telephone 29 4466. Brisbane Agencies 72 Wickham Street, Fortitude Valley, Queensland. Telephone 221 9944. Danish Hi Fi 308 Walcott Street, Mt. Lawley, Western Australia. Telephone 71 0100.



# MICROPHONES

## Part 1: Basics of sound and hearing

This series of articles, reproduced by courtesy of Sennheiser Electronic, is especially intended to assist sub-professionals and amateurs who need to use microphones, but without the advantage of formal acoustic training. This first part is concerned primarily with the nature of sound itself, and is directed particularly to amateur recordists.

by G. PRAETZEL and E. F. WARNKE\*

**NATURE OF SOUND:** "Sound is a wave movement which takes place in acoustic media". For our purposes we can convert this definition into "Sound is a wave movement of the air, audible to the human ear". By restricting it to the "wave movement of the air" we disregard mechanical vibration, i.e., the sound propagation in solid bodies; by restricting it to "audible to the human ear", we disregard the "infrasound" below and the "ultrasound" above the threshold of human hearing.

**PITCH, OCTAVE, FREQUENCY:** The human ear, as a sensing organ has some rather special properties. For instance, musical tones whose fundamental frequencies are in the ratio of 2:1 are perceived as being closely related. Musicians call this ratio an "octave".


Musical instruments, between them, cover a range of about 10 octaves, from the subcontra octave (16.4Hz) to the six-line octave (16000Hz). The letters Hz are short for "Hertz" which is the modern abbreviation for vibrations per second or, more familiarly, cycles per second. All these terms relate to what we call "frequency".

The vibrating parts of musical instruments—strings, bars of wood or metal, stretched diaphragms, or air columns—generate overtones or harmonics in addition to their fundamental tone. These higher frequency "overtones", or "harmonics", or "partials", impart an extra brilliance, or edginess, or "colour" to the sound, which gives it a particular quality or "timbre". It is important, therefore, that they be not lost during recording or reproduction, or changed significantly in strength.

A still further point, well illustrated by a piano, is that the sound composition of a note can change between the moment it is struck and when it dies away to inaudibility. This "transient" quality is also vital in discerning and preserving the nature of an instrumental sound.

Frequencies corresponding to very low tones (in the subcontra octave, i.e., below about 32Hz) are rarely called for by composers or played by musicians, nor can they be readily reproduced by loudspeakers in living rooms.

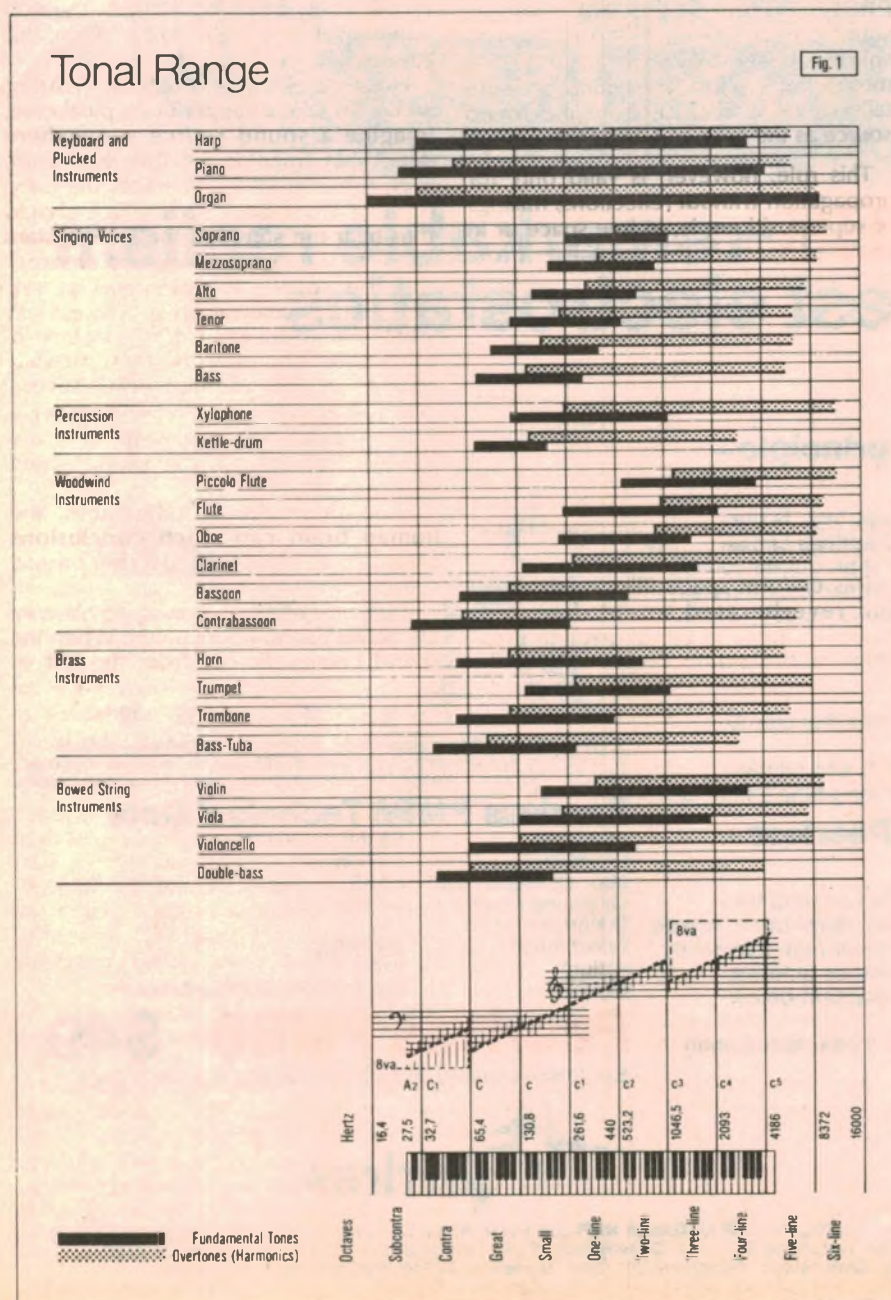The spectrum, i.e., the range between the lowest and the highest tone to be heard, stored, transmitted or reproduced is commonly called the "bandwidth" and is also specified in Hz.



\*Reproduced by arrangement with Sennheiser Electronic. Translated by T. M. Jaskolski and adapted for magazine publication by W. N. Williams.



**AUDIBLE FREQUENCIES:** According to experts in the subject, the human ear starts to age from babyhood, a 3-month old child being able to perceive frequencies between 20 and 20,000Hz. However, the upper limit of hearing falls by about 2000Hz for each decade of life. A 10-year-old hears up to about 18,000Hz, a 20-year-old to about 16,000Hz, a thirty-year-old to about 14,000Hz, a 40-year-old to 12,000 Hz, a 50-year-old to 10,000, and a 60-year-old to about 8,000Hz.

Fig. 1 shows how important the range of the human ear is for full perception of sound, by illustrating important musical instruments and human voices, with their respective fundamental tones and overtone ranges. While the fundamental tones determine the perceived tone pitch, the overtones and "formants" determine the typical sound colour (timbre) of a particular instrument or an individual human voice. Formants arise from resonance formation in sound sources and are marked by frequency ranges of increased intensity.

The falling perception of higher tones with growing age leads to the fact that older people do not discriminate overtones, characterizing individual instruments, with such clearness as do younger people.

**DYNAMIC RANGE:** Considered musically, "dynamic range" refers to the different loudness levels in a musical interpretation, e.g., the span of volume between fortissimo and pianissimo. When recording a live sound performance with microphones, every effort must be made to transfer the true dynamic range. Technical risk includes increased distortion during transmission of very high levels, while very low levels may disappear in hum and noise. For this reason the dynamic range for a recording—especially in classical works—must be reduced somewhat in almost all cases.

Any such reduction of the original dynamics in the transmission or recording of a musical composition requires considerable empathy, on the part of the recording engineer, with the score of the composition concerned.

Well before an approaching pianissimo, which might otherwise be lost in the noise of the system, the gain of the microphone channel(s) will be slowly and carefully increased, then lowered back to normal for what follows.

By contrast, anticipating an approaching fortissimo, which may overload the system and produce distortion, the microphone gain may be slowly eased back to keep the peak level within manageable limits.

Needless to say, musical compositions with a lower dynamic range present much less of a problem. Mainly, one has only to ensure that the loudest passage, while approaching the limits of the system, does not cause actual overload. This can usually be established during setting-up and rehearsal.

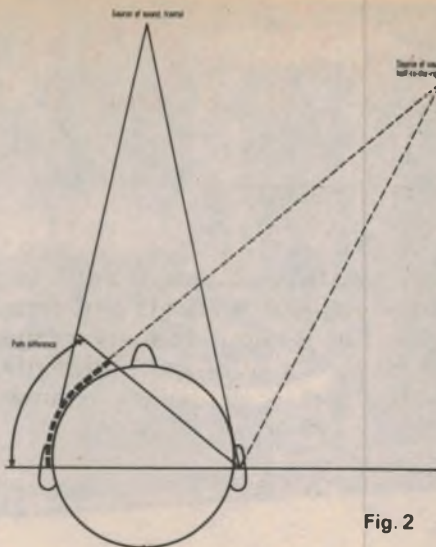


Fig. 2

**PROPAGATION OF SOUND:** Airborne sound propagates from the sound source spherically with a velocity of approx. 330 metres per second. The sound pressure falls with the distance from the sound source as the ratio of 1/distance.

This rule, however, is valid only for propagation without reflections, mixings or superpositions, ie, in free space or in enclosed space in the immediate proximity of the source of sound.

**REVERBERATION:** When a sound source is placed thus in an enclosed space, the sound waves are repeatedly reflected to and fro by the boundary planes. After a short time, a complete intermixing takes place of sound waves which penetrate each other mutually in all directions. Thus, at greater distance from the sound source, the space is uniformly filled with sound.

This uniform space filling with direct and reverberated sound does not, however, apply to the immediate proximity of the sound source. Here, the direct sound from the source prevails over those sound waves which are reflected by the walls. A microphone placed in proximity of the source thus reacts more to the direct sound and less to the room reverberation; to change the ratio between direct sound and reverberation, the source-to-microphone distance has to be varied.

The distance where the direct sound and the reverberation are in balance is called in German "Hallradius". Within this radius the direct sound prevails while, beyond this radius, the reverberation is stronger than the direct sound.

How large this "radius" is depends to a great extent upon the reflecting properties of the walls, the ceiling and the floor, as well as the furnishing and the size of room concerned. It is obvious that strongly reflecting walls, ceilings and floors and hard furniture, as well as a small room dictate a short radius. However, for reasons which will be explained

in a later article, we cannot place our microphone (or microphones) very near to a large sound source; therefore a larger and more attenuated room is preferable for microphone recordings than a small and undamped room.

In short, reverberation time is a property of the recording room, and it determines critically, the quality of a sound recording. It is defined as the time which elapses until a sound event dies away to the millionth part of its energy, or to -60dB relative to its maximum sound pressure.

The optimum reverberation time varies for particular types of music. In general, it can be said that reverberation times not exceeding 1.5 seconds are optimum for recordings of classical and modern music. Rooms for pop—or jazz music—should have a reverberation time below 0.8 second.

**STEREOPHONIC HEARING:** Pairs of human sensing organs provide spatial information.

How does human spatial hearing work? To take a simple but typical case, imagine a sound source somewhere directly in front of the listener's head. Such a source will be at exactly the same distance from both ears, which should thus hear the sound at the same instant and with the same volume and timbre.

If the source is envisaged at the right/front position as in Fig. 2, sound will reach the right ear slightly before it reaches the left. It will also be somewhat weaker in the left ear, after having travelled around the head and, as well, differences in the behaviour of some overtones may slightly change the timbre of the sound.

From these minute differences, the human brain can reach conclusions about the direction of the sound source.

It is somewhat fascinating to observe the actual quantities involved: When the sound comes directly from the left or directly from the right, it has to cover an extra path of 13 to 16 centimetres to reach the other ear around the head. Sound travels 330 metres in one second. Thus less than one thousandth of a second is required by the sound to reach the other ear and this is the longest time delay. In cases of a sound coming only slightly from the right or left the time difference shrinks down to less than a ten thousandth of a second. Yet our hearing centre is still able to evaluate time delay differences of such a low order.

What is more, the facility cannot be switched off. We hear everything spatially, street traffic noises as well, as a symphony orchestra. To be reminded of the differences, select a good stereo record, then switch it to mono!

Having done so, you will perhaps decide to make your own recordings exclusively in stereo. It is better, often easier, although the cost in terms of microphones and tape recorder is higher. (To be continued)





*The superb Luxor 'Music Centre' with record player, cassette deck, AM/FM radio.*

# Introducing the Luxor 'Swedish Sound'

Sweden's largest-selling range of high quality stereo systems is here to spread its superb sound around Australia

In 1923 at Motala in Sweden, Luxor first began mass production of radio sets. Today, Luxor are Sweden's largest selling, high quality stereo systems.

**Record players of precision and reliability.** Luxor features include a magnetic dynamic cartridge with adjustable stylus pressure. And a 16-pole synchronous motor and belt-drive for low wow and flutter.



*The popular Luxor Record Player*

**Amplifiers with the quality of 'Ambiophonic sound'.** Luxor have developed a 4-channel stereo system, called 'Ambiophonic sound', as a feature of the larger amplifiers. Other features include easily-operated slide controls, and switches for automatic frequency control, AM/FM radio, tape recorder, record player, headphones and loudness compensation.

**Cassette decks for fast, smooth operation.** With a Dynamic Noise Limiter or Dolby noise suppression.

Automatic switching for chrome dioxide tapes. And, 90 second fast-forward and rewind on C-60 tapes.



*The Luxor Cassette with Dolby noise suppression.*

### Speakers to suit all systems.

From the Omni-directional Luxor loudspeaker with a 20 cm bass unit and four 5 cm treble units. To the 15 W speaker with a 13 cm drive unit and 6.5 cm treble unit.

*The Omni-directional loudspeaker for floor standing adjacent to wall.*



**They look as good as they sound.** Luxor stereo systems combine a careful attention to detail with an unmistakable touch of design flair. Elegant and sleek. In superb cabinets of walnut, teak and rosewood. And black or white lacquer.

**The superb Swedish sound.** As Sweden has developed in the world of music, so Luxor has developed in reproducing that sound.

The more you know about Luxor stereo systems, the more impressive they become.

**The need for distributors and stockists to spread the sound.** Distributors are required in Queensland, South and Western Australia and Tasmania. And stockists are required in all States. See the coupon below.

**LUXOR**  
of Sweden

To: Luxor, P.O. Box 307,  
Collingwood, Victoria, 3066  
I am interested in becoming a Luxor  
stockist and would like to know  
about the Luxor range of products.

Name

Company

Address

State  Postcode   
(Luxor, c/- 77 Wellington Street,  
Collingwood, 3066)

LUX 148



# B&W DM5 Loudspeaker

The B&W DM5 is a compact two-way loudspeaker system employing the same tweeter as the highly rated DM6 system. Frequency response is within 5dB over the range from 80Hz to 20kHz. They are sold in matched pairs and each system is supplied with an individual frequency response curve.

In contrast with the larger B&W DM2 and DM6 loudspeakers, the DM5 is quite conventional in appearance. It has a well finished cabinet in veneered particle board and has a black acoustic-foam front which can be peeled off for a look at the loudspeakers. Dimensions are 226 x 455 x 257mm (W x H x D) including the foam front.

While the black foam front certainly appears to be acoustically transparent and non-resonant, we gained the impression that it was too easy to remove. It could be a particular temptation for young children with curious fingers.

In fact, we sometimes wonder why grille assemblies are being made so easily removable. It may serve to display a set of impressive-looking drivers but that is no indication that the system will produce a high quality sound.

Be that as it may the tweeter in the DM5 is recognisably the same as that used in the DM6 reviewed in these pages in August 1976. It has woven polyester dome approximately 20mm in diameter. The woofer appears to be similar if not identical with the midrange unit of the DM6. It has a woven synthetic fibre cone with a roll surround.

Also occupying the front panel is a heavy gauge metal plate which is screen printed with a typical frequency response plot of the DM5. This is actually the mounting panel for the crossover network PC board. The board is quite thick at about 2.5mm and accommodates

two inductors and four metallised polyester capacitors.

Protection against overdrive or possible catastrophic amplifier faults is provided by a 2 amp fuse. This is a worthwhile feature for any good loudspeaker system. It will result in a small degradation in system damping factor and perhaps also a small increase in distortion due to the non-linear resistance of fuse wire, but the nett effect would probably be insignificant.


The impedance curve shows a well damped woofer resonance at 70Hz and another peak at 2.5kHz presumably indicates the crossover frequency. Minimum impedance occurs at about 180Hz and 18kHz. At these points the impedance dips to 5 ohms which may be a little low for some amplifiers.

Listening tests confirm the supplied frequency response curves. It is very smooth and well maintained up to the limit of audibility. Bass is not emphasised but is still quite strong to below 50Hz. Modest bass boost can be applied without doubling occurring. Overall system balance is very good.


Superb results can be obtained on almost all types of music, although pipe organ enthusiasts will doubtless find the system wanting in the lowest octave. Overall, the DM5 can be rated as a compact system of very high quality. Over most of the audio range it gives results comparable with many systems of much higher price.

Further information and demonstrations can be obtained from high fidelity retailers or from the Australian distributors for B&W, Convoy International Pty Ltd, 4 Dowling Street Woolloomooloo, NSW 2011. (L.D.S.)

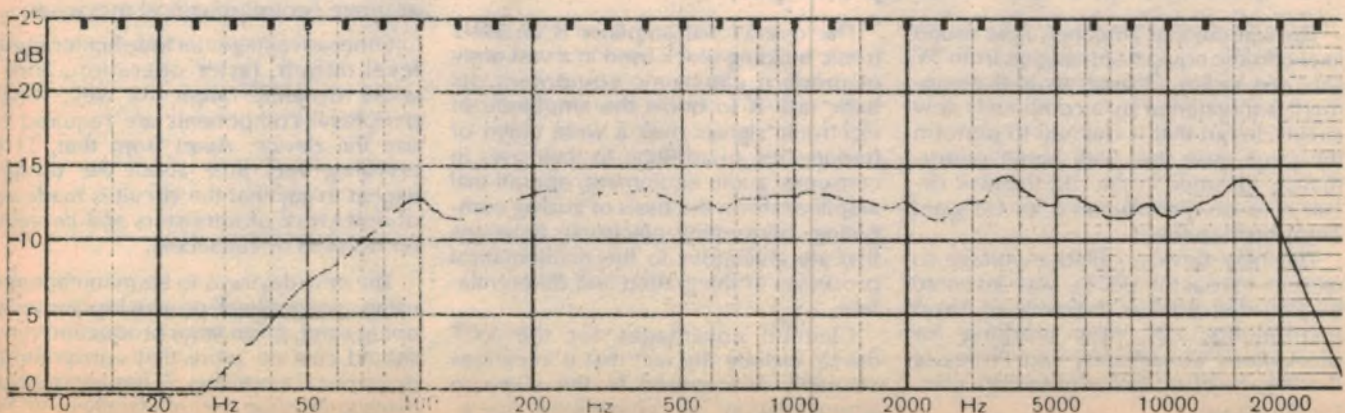*The black foam front of the DM5 peels off to reveal the two loudspeakers on the baffle. Below is one of the individual frequency response plots supplied with our sample pair of DM5's.*





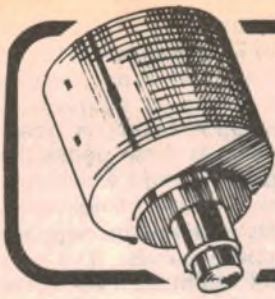

# News Highlights




## University research team makes practical transistor

Although the theoretical aspects of semiconductor operation have been well known for years, design and fabrication techniques of practical devices are not so well known. Device fabrication has been confined almost exclusively to large electronics companies which, not surprisingly, are unwilling to divulge detailed information of manufacturing techniques.

Anyone starting out from scratch therefore has to learn the hard way, and a research team at the University of NSW has done just that. Working in the University's Department of Solid-State Electronics, the team recently succeeded in designing and manufacturing a practical, working transistor.

The transistor, a MOSFET device, was designed by Dr Peter Ladbroke and PhD student Star Huang following 6 years of effort by the team as a whole to establish a laboratory for semiconductor device research and manufacture. The laboratory and much of its equipment was designed and constructed by Dr Richard Vaughan, Professional Officer Dr Peter Kosel, Research Student Michael Strudwick, and Technical Officer Brian Varley.

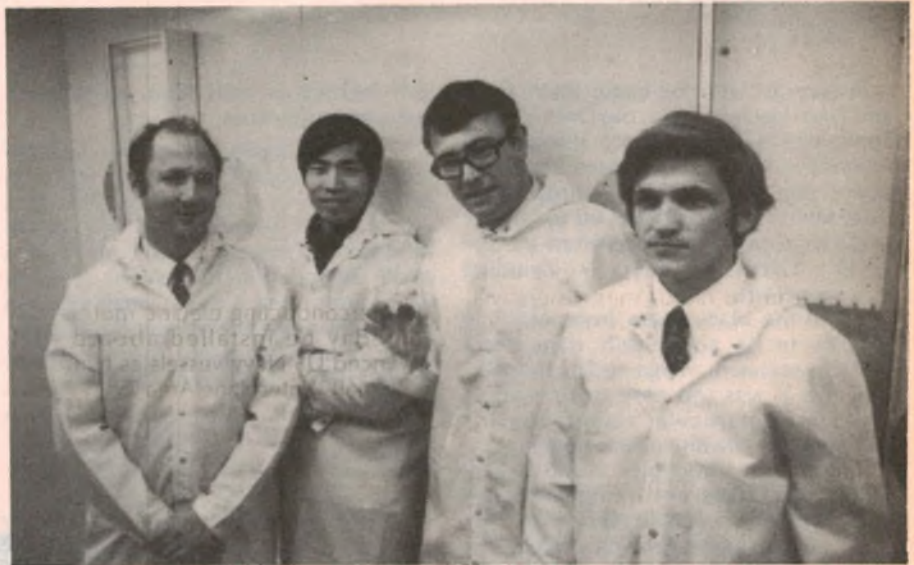One of the main problems facing the research team was the development of clean room facilities. There are, according to Dr Vaughan, approximately 10 million particles of dust per cubic foot in ordinary air. The clean room facilities reduce this figure to 1 or 2 per cubic foot.



Pictured in the "clean room" where the transistor was made are (left to right) Dr Richard Vaughan, Mr Star Huang, Dr Peter Ladbroke and Dr Peter Kosel.

Very precise furnace temperatures are also required during the manufacturing process. The furnace at the University of NSW is capable of regulating the temperature to within  $\frac{1}{4}^{\circ}\text{C}$  at  $1000^{\circ}\text{C}$ .

MOSFETs are regarded as the most difficult transistors to make, and the type developed at the university takes some 72 man-hours to process. According to Dr Ladbroke, "it is comparable with commercial devices currently available from semiconductor device manufactur-

ers and uses the same technology as the MOS integrated circuits found in everything from pocket calculators to spacecraft."

Now that the technology hurdle has been overcome, the aim is to produce a range of original transistor and integrated circuit designs. In particular, the team hopes to concentrate on very high frequency FETs and integrated circuits for medical equipment, as well as developing specialised ICs in support of university research projects.

## A replacement for the op amp?

The operational amplifier, now found in electronic equipment ranging from TV sets and radios through to hi-fi equipment is threatened by a completely new circuit design that is claimed to perform the same tasks, but with better performance. Invented in the UK, the new circuit is to be manufactured by US giant Texas Instruments.

The new device, called a voltage to current transactor (VCT), was invented by Carl den Brinker (formerly of Texas Instruments, UK, now working for Mackintosh Consultants) and Professor Gosling, head of Bath University's electronics group.

The operational amplifier is an electronic building block used in a vast array of modern electronic equipment. Its basic task is to boost the amplitude of electronic signals over a wide range of frequencies. In addition to their uses in consumer audio equipment, operational amplifiers form the basis of analog computing, performing electronic functions that are analogous to the mathematical processes of integration and differentiation.

Claimed advantages for the VCT device include the fact that it integrates smoothly as opposed to the stepwise approximations of conventional opera-

tional amplifiers. This will make for more accurate control of critical processes.

Other advantages include higher signal level output, faster operation, and a wider dynamic range. As well, fewer peripheral components are required to use the device. Apart from that, TI is revealing very little about the design, except to say that the circuit is made up of a network of transistors and contains no resistors or capacitors.

The new device is to be manufactured using conventional, proven bipolar technology and, given large production runs, should cost no more than conventional operational amplifiers. TI has announced plans to develop a whole family of VCTs.



## The push is on for CB radio

A non-clandestine organisation calling itself the National Citizens' Radio Association (NCRA) was recently formed in Sydney with the aim of lobbying the Government to legalise CB radio. The organisation, formed by Sydney advertising executive Mr Bill Payne, has already had significant talks with government representatives and an inquiry is now under way.

The NCRA emphasises that it is not a "pirate" organisation. It sees itself primarily as a pressure group in the campaign for legalised 27MHz CB radio, and is asking for volunteers to help in the campaign.

Volunteers are also required to man the NCRA's Citizens' Radio Emergency Service Team (CREST) which will involve monitoring Channel 9 (27.065MHz) of the 27MHz band. This channel has been set aside by the CREST as an emergency channel and is the same as the one used on American CB radio. Shift rosters will be involved, and the ultimate aim is to provide a 24 hour monitoring service.

Members of CREST will relay emergency calls on their own transceivers, usually from cars. Typical emergency situations would include road accidents and bushfires, and members will be on the alert for these, particularly in remote locations. Technically, though, these people will be breaking the law since their CB equipment is not licensed.

The purpose of the monitoring service is two-fold: (1) to render assistance to any emergency calls by advising the appropriate authorities; and (2) to demonstrate the usefulness of CB radio to the authorities. Those readers interested in helping the CREST should write, nominating the hours they can monitor, to The National Director, National Citizens' Radio Association, Box M101, Sydney Mail Exchange, NSW 2012.

## Low-cost microfilmer



The Kodak Oracle Microfilmer is one of four products in a new family designed for rapid filming of documents. Up to eight 11 x 14in documents per minute can be filmed and encoded.

## Supercold motors will power US Navy

Supercold electric motors, chilled 450°F below zero, may power high-speed US Navy ships on antisubmarine, oceanic-research, and cargo-carrying missions of the 1980s.

Two 3,000-horsepower superconducting electric motors—the forerunners of the 20,000-to-40,000-horsepower supercold units of the future—are being designed at the General Electric Research and Development Center and constructed by the company's Large Motor and Generator Department, both in Schenectady, NY, under a \$US4.57 million contract with the US Naval Sea Systems Command. The first motor is scheduled for sea trials beginning in late 1977.

At the heart of each motor is a 350-pound magnetic coil shown here emerging from a liquid helium dewar following tests at Intermagnetics General Corporation's plant in nearby Guilderland, NY.

Superconducting electric motors may someday be installed aboard such advanced US Navy vessels as hydrofoils and Small Waterplane Area Twin-Hulled (SWATH) craft. Both vessels ride high out of the water—a hydrofoil on underwater steel "wings", and a SWATH craft on submerged tubular hulls. The SWATH design provides a relatively smooth ride even in heavy seas, while the hydrofoil is capable of high-speed maneuvering.

In early designs of these super-fast



ships, power from a deck-level turbine was transmitted to the propeller by means of a right-angle drive shaft. In a superconducting system, the turbine would drive a super-cooled generator, which would provide the electricity to power GE's motors.

This means that the mechanical transmission would be replaced by alignment-free electric cable running from the generator to the motor, which would power the propellers. Since the propellers would spin independently of the turbine, the latter always could be operated at optimum speeds for minimum fuel consumption.

## Data terminal responds to voice commands

Widespread use of spoken words as a means of communication with computers has been forecast by the EMI group following the introduction by its subsidiary, EMI Threshold Limited, of a low-cost data terminal which is operated solely by the human voice.

Designated the Threshold 500, this advanced simple-to-operate data entry station is designed to replace or complement conventional intelligent video display units or keyboard terminals, both in minicomputer applications and large multi-terminal data processing installations. A range of standard output interfaces makes the equipment plug-compatible with virtually every data processing system.

The Threshold 500 terminal is ideal for increasing job efficiency in situations where manually-operated data entry techniques cannot be applied because an operator's hands and, perhaps, eyes are already fully occupied. It overcomes the limitations of conventional computer communication methods especially in eliminating the intermediate paperwork associated with data preparation.

Basically, the unit comprises a speech processor unit, an alpha-numeric display, and a microphone headset. It is able to

recognise words spoken in any language—from Japanese to Punjabi—irrespective of vocabulary, accent, dialect or speech impediment, and even against the background sounds of an operational environment. The standard 500 machine has a minimum vocabulary of 32 words or short phrases, which can be expanded as required.

Users of the Threshold 500 terminal 'train' the equipment to understand their individual pronunciation of the vocabulary by repeating each word either 5 or 10 times into a noise-cancelling microphone. The repetition of each word enables the 500 terminal to obtain an average voice pattern from the slight variations which occur each time the speaker pronounces a word.

In use, each operator calls up his own voice pattern, identified by a reference number set on a control unit. As each word is spoken, it appears on a visual display unit allowing the user to verify, at a glance, that the terminal has correctly understood the communication. An instruction or control word such as 'go' or 'action' from the operator causes the system to despatch the inserted data to the computer installation.



# THE INCOMPARABLE SONY 'V-FETS'



## Sony's TA Series – A new breed of amplifiers so advanced they lift world standards in fidelity.

SONY research takes the art of solid-state amplification a giant leap forward. Now amplifiers offer all the true warmth and brilliance of the classic vacuum tube without any of its drawbacks. In fact, Sony's V-FETs are the biggest thing in stereo hi-fi since the vacuum tube.

Tubes are inefficient, they deteriorate and wear out. They also require an output transformer to drive speakers. And there's no way they can be set up in true complementary circuits with true wave form symmetry.

Sony's V-FET amplifiers overcome all that with high current utilization ratio and uniform thermal flow for exceptionally stable operation under greatly varying conditions.

### "Watts per dollar" is no longer the test

Amplification goes into a new era, a "V-FET Era" with Sony's new TA series. Both the TA4650 and TA5650 give great power and superb natural fidelity, with literally dozens of applications and facility features, typical of Sony design ingenuity.

To list a few:

Complete FET protection circuits which prevent circuitry or speaker damage, professional controls designed for utmost accuracy and precision, including

instant 20db muting volume control and level control memory. Tape monitor and dubbing facilities are thoroughly professional and very comprehensive as are the rear panel connection facilities.

The TA5650 boasts a powerful 50W RMS per channel power output, frequency response 10 Hz – 100KHz and a harmonic distortion figure of 0.05% (at rated output). Truly a magnificent performer. From only \$500\*

The TA4650 delivers a linear smooth 30W RMS per channel, frequency response 10Hz – 100KHz, harmonic distortion an amazing low 0.05%. From only \$400\*

Whatever your demands, the new SONY V-FET Amplifiers deliver a superb performance with looks to match. Naturally they're perfectly compatible with SONY's new range of space-age Hi-Fi equipment.

If you're into sound, you must be into SONY.

\*Recommended retail price.

## "IT'S A SONY"

Hear the difference research makes

For your nearest stockist call SONY Sydney 2 0221, Canberra 95 2100, Melbourne 874 8222, Brisbane 44 7504, Adelaide 268 3444, Perth 81 3422, Newcastle 61 4991, Wollongong 71 5777, Launceston 2 5322, Townsville 71 4105.

GAC.S.7823



# NEWS HIGHLIGHTS

## Electronics industry vital for defence

Continuity of production and research is essential if a viable Australian defence electronics industry is to be maintained and its skilled labour force kept intact, Mr J. A. L. Hooke, the Chairman of Amalgamated Wireless (Australasia) Limited, said in a recent press statement.

"Stop-start activities are simply not economic and have no place in the future", he said.

Mr Hooke said the Government had shown itself aware of the problems and recently made most welcome initiatives in the field of defence industrial planning.

"The electronics industry today has undergone major changes which greatly increase the difficulty of maintaining a

viable defence industry that can be called upon in the event of national emergency", Mr Hooke said. "Recent past policies have greatly reduced the components industry and in-depth manufacturing in Australia, and clearly new policies are required."

Mr Hooke said that virile industries that could swing rapidly from a peace to a war footing must rank with the armed services as being essential to our ability to defend ourselves.

In another recent press statement, the Chairman of the Australian Telecommunications Development Association (ATDA), Mr T. E. Hodgkinson, made a similar plea for the future of Australia's electronics defence industry. According

to Mr Hodgkinson, "the telecommunications industry sector employs by far the greatest proportion of electronic engineers and... is readily adaptable to the design and manufacture of service equipment."

Mr Hodgkinson said that in the case of a war starting the defence forces will need the active support of back-up industries with the technological expertise to keep the defence system operative. Because of the importance of electronics (in defence equipment) we must have a strong electronics industry... if our long term defence aims are to be achieved."

"What will be the use of having adequate armaments if these are to become inoperative in the event of Australia being cut off from the source of supply of essential spares and technical expertise?", Mr Hodgkinson asked. He went on to state that we must stop looking at short term economic advantages and develop our key industries by laying down firm policies.

## Low-cost autopilot for small boats

A new automatic pilot capable of steering most pleasure craft and small commercial vessels is now available in Australia through the Marine Division of Amalgamated Wireless (Australasia) Ltd.

The compact, all solid-state autopilot, designated Course Setter 21, is produced by the Benmar Division of Cetec Corporation, USA. It is priced at just \$625.

Features of the design include an automatic variable rudder rate design which provides instantaneous correction for course errors as small 0.1°. An automatic rudder trim continually removes trim errors, even on hydraulically steered boats without the need for rudder feedback devices. Side loads, such as trailing nets or single engine operation on dual engine boats are automatically neutralised.



*The Course Setter 21 autopilot combines operational simplicity with low cost.*

Operation is simple—the helmsman need only select the desired heading and engage the pilot. A remote control handset and a limit switch kit are available as accessories.

## American solar energy expert visits Australia

American solar energy expert, Dr Joseph Lindmayer, recently visited Australia to give evidence before a Senate committee on the future possibilities of solar energy. Dr Lindmayer is President of Solarex Corporation, Rockville, Maryland, and at Solarex developed an inexpensive photovoltaic technology that has reduced the market price of photovoltaic systems by a factor of thirty in the past two years.

During a talk given to industry representatives in Sydney last August, Dr Lindmayer outlined the research that was going on, and discussed the potential uses of solar energy. The talk revealed no surprising new facts, revealing instead a steady research program at improving solar cell efficiency and lowering production costs. According to Dr Lindmayer, a great deal of research effort is concentrated on ways of automating production, and producing large area cells.

Dr Lindmayer said that the roof area of the average dwelling was more than sufficient to meet domestic electricity needs, assuming cells of 10% efficiency. His company currently makes silicon solar cells of the order of 15% efficiency. Although these cost somewhere in the \$30/watt region, the long term goal is, according to Dr Lindmayer, to reduce the cost to around the 50c/watt mark.

In short term, however, Dr Lindmayer sees a range of consumer applications for solar cells—in torches, transistor radios, wrist watches, pocket calculators, beacons, boats, and street lights, to name just a few. Solarex Corporation is represented in Australia by Transmission Products Pty Ltd, 33 Bellona Ave, Regents Park, NSW 2143.

## Dick Smith secures new supply sources

Gary Johnston, Manager of Dick Smith Electronics Pty Ltd, recently returned from an extensive visit to several Asian countries. Dick Smith and Gary Johnston have both been extremely concerned about the "lamentable" deliveries of electronic components and equipment out of the Asian area recently.

"The CB boom in the United States has tied up production capacity completely in hundreds of factories", Mr Johnston said. "Unfortunately, this increase in demand from the US coincided with a tremendous increase in usage of parts by us.

"Because of the tremendous success of our 1976/77 catalog, issued in this magazine last April, we have been hard

pressed to keep supplies up to our mail order customers. This terrible situation should be rectified shortly, however, as we have negotiated with new sources of supply as a result of the trip".

Mr Johnston visited Hong Kong, Taiwan, South Korea and Japan while he was away.



*Gary Johnston*



# High Speed Video Tape Printer

Magnetic recording, while highly regarded for its quality and flexibility, has always suffered the disadvantage that there has been no simple way to make duplicates from the original recording. Recently, however, the National company of Japan has introduced a high speed video tape copying system which overcomes this problem.

by PHILIP WATSON

Even in the audio field, the problem of making duplicates in quantity, at a reasonable price, held back the distribution pre-recorded tapes for a long while, in spite of their potential high quality.

Discs can be duplicated in almost any quantity by pressing. The process is cheap and, with modern techniques, virtually loss-free. More important, the time needed to make a duplicate bears little relationship to the playing time of the disc.

The situation is similar for film. Granted, it is a little more complex and losses can be higher if precautions are not taken but, again, the duplicating time is not necessarily tied to the playing time.

But tape? Well, that's always been the hard one. Initially—and until recently—the only way to duplicate any kind of tape has been to re-record it, i.e., decode the information with a replay head, pass it through a suitable amplifier, then feed it to a recording head on the new tape. This is commonly called head-to-head duplicating, or "dubbing".

There are several disadvantages to this system; some obvious, some not so obvious. One of the obvious ones is that, in its simplest form, it takes as long to make the duplicate as it takes to play the master. Where mass duplication is the object this is an intolerable limitation. Another obvious objection is that some loss of quality is inevitable.

This includes both electrical and mechanical losses; transport irregularities in both replay and record mechanisms, signal losses in the amplifying network, plus the natural noise level of the master tape superimposed on the noise of the slave tape.

A less obvious, but equally important, disadvantage is the wear and tear on the master tape, coupled with the wear on the various heads. Both effects add to the cost structure of the exercise.

In the audio field most of these problems, if not actually overcome, have been reduced in magnitude to an accept-

able level. The time factor has been reduced by increasing the speed of both tapes by up to 10 times, although this introduces problems of its own. Increasing tape speed by 10 times jacks the signal frequencies up by this amount, so that the amplifying system upper frequency limit has to be similarly upgraded.

To take care of the wear and tear of the master tape this so-called "master" is in reality a duplicate itself, the true master being used only to make second generation masters which are expendable. (Even the true master is only a master in that it represents the final mix-down from the original multitrack recording. Technically, it is also a duplicate.) The final copy will therefore be almost certainly a fourth generation duplicate—at least—with an appropriate accumulation of losses and noise.

Nevertheless, such copies can still achieve a very high standard, partly because the original recordings are that much better than the commercial standard required and partly because

progressive improvements in technology have minimised the transfer losses. The technique is in fact the basis of the pre-recorded audio tape industry today.


But what of video tape? This is very much a different story. With video signals in the 4.5MHz region any attempt to speed up the re-recording process would call for extremely complex wide-band amplifiers, a difficult requirement to satisfy.

Just as difficult—or perhaps more so—would be the speeding up of the mechanical parts of the system, some of which already operate at quite high speeds.

So, until now, video tape duplication has invariably been on a "real time, head-to-head" basis, with all the disadvantages already discussed, plus some peculiar to the video scene.

One of these involves the different video systems employed by various countries; SECAM, NTSC, or PAL. To duplicate a tape made to any one of these the duplicating equipment must be designed for that system.

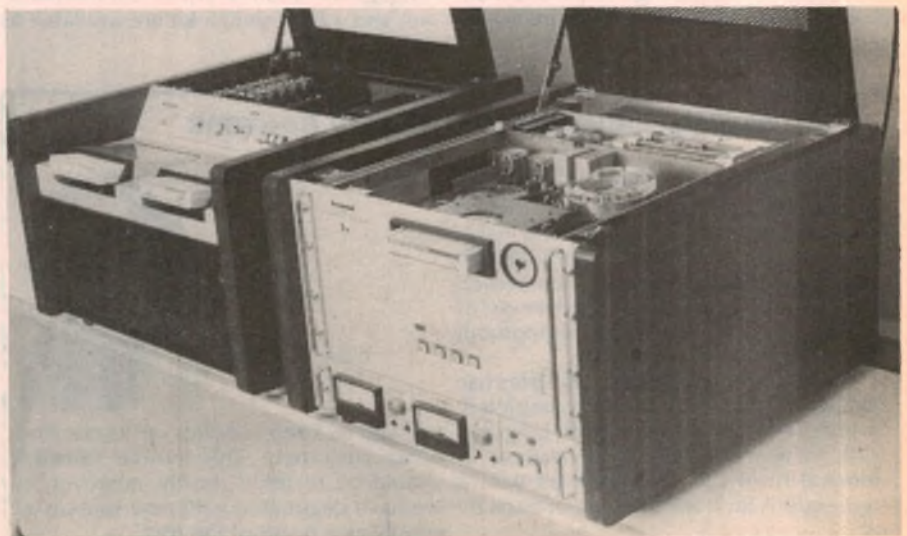
Another, more serious, disadvantage can add to the time needed to make a duplicate. It is possible for various malfunctions to occur during a head-to-head transfer—typically a dirty head—whereby part of the transfer will be degraded or lost. The only way to be completely sure that this has not happened is to replay the entire tape.



The complete setup for duplicating video tapes. On the right is the special recorder which produces a mirror image master tape from any signal source, including an existing tape. On the left is the high speed duplicator.



## Thermal Transfer System

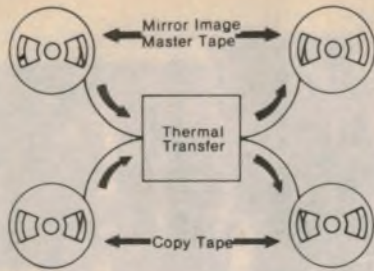

On this basis, to duplicate, and check, a half hour recording takes at least an hour of one person's time, plus setting up time. Since this may often be prohibitively expensive, checking may be confined to spot checks with a significant risk of faulty tapes being overlooked.

There have been several attempts in the past to duplicate tapes by another process. Most audio enthusiasts will be aware of—or have actually experienced—the phenomenon called “print through”. This is the transfer of information on one part of a tape to an adjacent layer, when conditions are favourable. In practice, it is usually encountered when the signals have been recorded at a higher than recommended level for the particular tape.

This normally unwanted characteristic can be turned to good use. If two tapes are brought into intimate contact, with the oxide faces touching, there will be a more effective “print” from one to the other, though still too low to be of much practical value.

A much more effective transfer can be achieved by two methods. One involves


*Three typical tape duplication systems. The running contact systems call for precise transport mechanisms which do not permit relative movement between the two tapes.*

passing the mated tapes through an AC field, the other passing them through a heat cycle which raises the copy tape to its Curie temperature.


A problem with the AC field system is that the field tends to erase both tapes as well as aid the transfer. This is overcome by making the master on a high coercivity tape, while the slave is a relatively standard tape of moderate coercivity. This permits a field strength which gives an effective transfer without significantly erasing the master tape. The broad name for this method is the anhyseretic system.

A similar problem exists with the heat
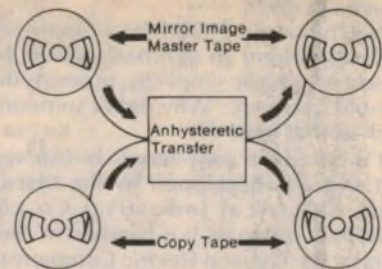
## Anhyseretic Transfer—Running Contact System




## Anhyseretic Transfer—Bi-filar System

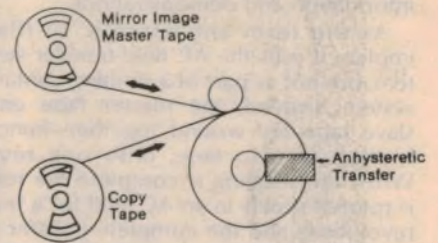

transfer—or thermal—process, and it is necessary to use a slave tape with a Curie temperature lower than that of the master tape.

Both systems have been used to date, with some success, all based on the idea of holding the two tapes in contact over a short distance while both are wound at high speed past the transfer device. This is called the “running contact” system.

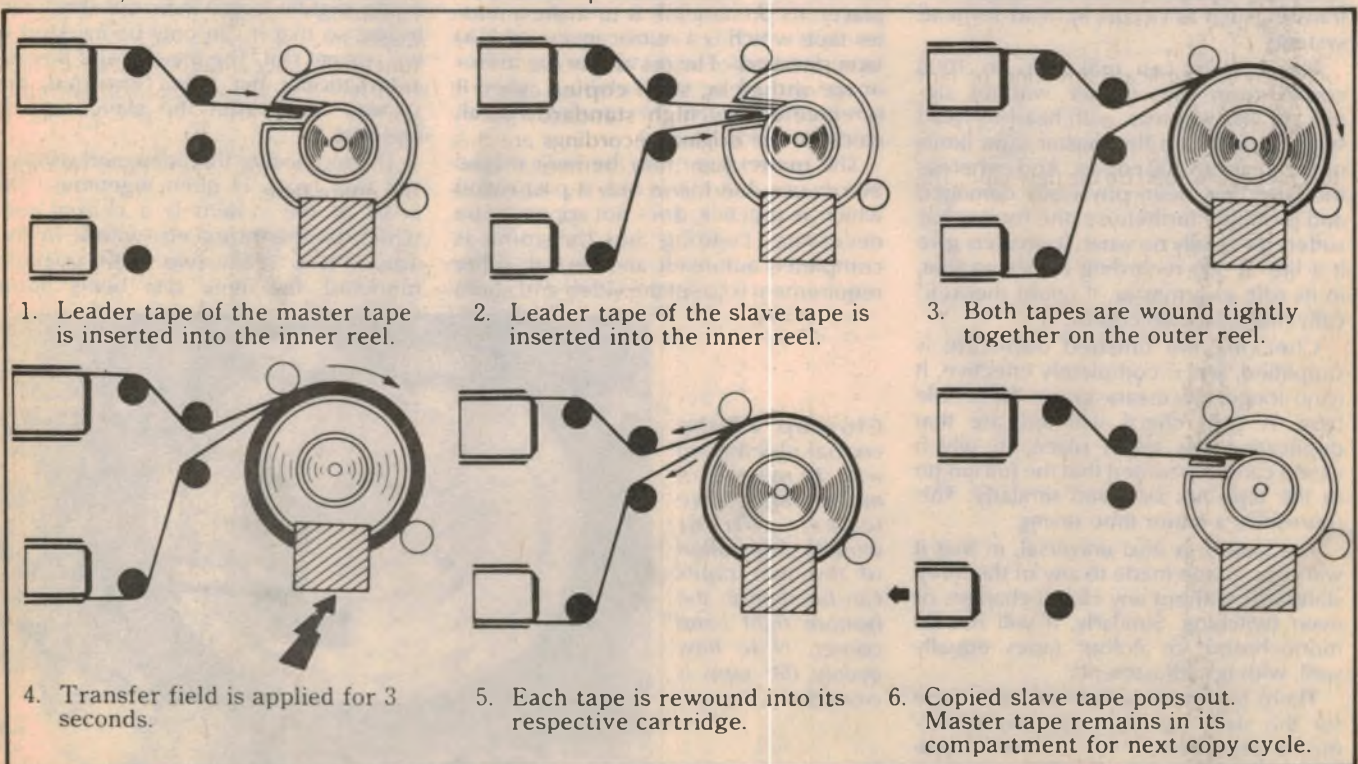A major problem with any such system is that of ensuring that all parts of the tapes are held in absolute contact during the transfer, and also that they do not move relative to one another. Either con-



Six main steps in making a bifilar anhyseretic duplicate. All steps, including tape threading and capture by the inner reel are completely automatic. Total copying time for a 30 minute

tape is about three minutes, most of which is winding and rewinding time, the actual copying taking only a few seconds. One master can make 1000 copies.



dition will result in loss or degradation of signal transfer.

Which brings us to the latest approach to this problem; an approach which, by reason of its basic simplicity, prompts the age-old question, "Why didn't someone think of that before?"

It is called the anhysteretic bi-filar system and was developed by the Matsushita Electrical Industrial Co Ltd (National) of Japan. It is handled in Australia by the General Electric Company of Australia Ltd (Electronics Division) to whom we are indebted for technical information and demonstrations.

As the term anhysteretic bi-filar implies, it uses the AC field transfer system, but not as part of a running contact system. Instead, the master tape and slave tape are wound together—hence bi-filar—face to face, onto one reel. When the winding is complete the reel is rotated slowly in an AC field for a few revolutions and the complete transfer is made in about three seconds. The tapes are then rewound onto their respective reels and the slave tape is ready for immediate replay.

The sound track is transferred on a head-to-head basis, using the high speed techniques already discussed. This takes place during the rewind function.

The total time needed to duplicate a 30 minute tape is only three minutes, all but about three seconds of which is winding and rewinding time.

The makers claim a number of advantages for this system. The obvious one is the saving in time but, equally important, there is virtually no loss of quality in the transfer, such as occurs in head-to-head systems.

The system can make up to 1000 copies from one master without significant loss whereas, with head-to-head systems, wear on the master tape limits its life to about 200 copies. And, whereas the latter has been physically damaged and is of little further use, the former has suffered virtually no wear. Its makers give it a life of 500 recording cycles so that, in its role as a master, it could theoretically make 500,000 copies!

Checking the finished duplicate is simplified, and is completely effective. It is no longer necessary to run the whole tape. A spot check will indicate that duplication has taken place, in which case it can be assumed that the full length of the tape has behaved similarly. This represents a major time saving.

The system is also universal, in that it will copy a tape made to any of the three standards without any circuit changes or even switching. Similarly, it will handle monochrome or colour tapes equally well, with no adjustments.

There is a much wider choice of tape for the slave function, and no adjustments are needed for different type tapes. With head-to-head recording, changes to bias level, etc, may be necessary for optimum performance.

The equipment is also much more



The open reel version copier with cover removed. The coaxial reel is clearly visible on the left with the AC field magnets directly above it. The master tape (cartridge) and the slave tape (reel) are on the right.

compact and can be used by an unskilled operator following simple instructions.

The equipment demonstrated to us by The General Electric Company (GEC) consisted of two units; a master tape recorder and controller and the tape printer proper, both designed for the 0.5in wide tape, both for the EIAJ (Electronic Industrial Association of Japan) standards.

The master recorder will accept signals from virtually any video source; camera, TV receiver, film scanner or video tape player. Its primary job is to make a master tape which is a mirror image of EIAJ tape standards. The reason for the mirror image should be fairly obvious when it is remembered that the copying is on an oxide-to-oxide basis.

The master tape may be bulk erased before use, but this is only a precaution which, in practice, does not appear to be necessary. Loading and threading is completely automatic and the only other requirement is to set the video and audio


levels on the appropriate meters on the front panel of the controller.

Both master and slave tapes are in "cartridge" form, although this term is open to debate. More accurately, they are simply the same reels as used in earlier reel-to-reel machines, housed in a box. In fact, they can be removed from the box if it is desired to use them on a reel-to-reel machine.

The finished master is transferred to the copier and inserted in the appropriate slot. This cartridge is deliberately made slightly larger than the slave cartridge, so that it can only be inserted in the correct slot. The master tape threads automatically but, once threaded, the system waits until the slave tape is inserted.

The method of threading and winding the two tapes is quite ingenious. The heart of the system is a coaxial reel, which is illustrated elsewhere in this article. It is really two reels coaxially mounted, the inner one being about

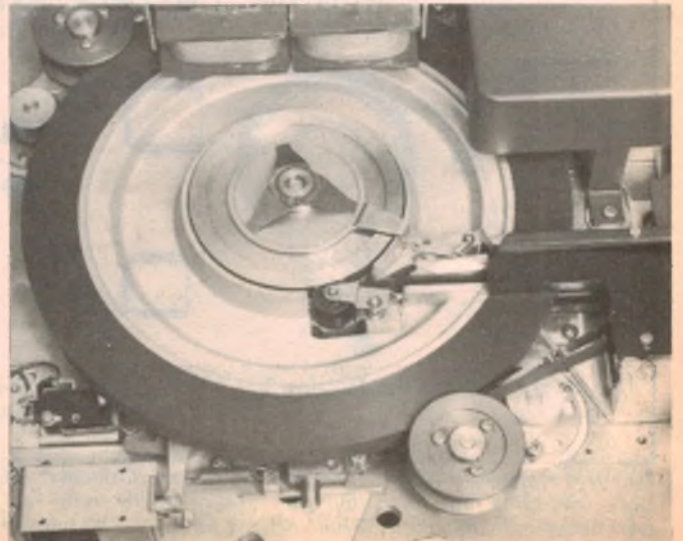Closeup of the coaxial reel loaded with 30 minutes of master and slave tapes, bifilar wound. Separation of the two tapes can be seen in the bottom right hand corner. Note how evenly the tape is wound.





88mm diameter and the other about 180mm.

The inner one rotates during the loading sequence and captures, in turn, the master tape leader and the slave tape leader, these being fed to it through a slot in the outer reel. When both leaders are captured the two reels lock together, rotate as one, and wind the two tapes on the 1/2in wide edge of the outer reel. Two guide pulleys ensure even winding. The reels remain locked until the end of the rewind sequence.


When the outer reel is fully loaded winding ceases automatically, the AC transfer field switches on, and the reel rotates slowly for about three seconds in this field. Both tapes then rewind automatically, the slave tape is ejected, while the master tape leader remains captured, ready to accept another slave.

Two copiers were demonstrated by GEC. One accepts cartridges for both master tape and slave tape. In this unit the slave tape threads automatically. The other unit is almost identical but is designed to accept slave tapes on open reels, as used on some older recorders. The master tape is still a cartridge type and threads automatically, but the slave tape must be threaded manually, though this is quite simple.

Results from both machines are identical and the author can vouch that the slave tape is indistinguishable from the master.

The equipment is beautifully con-

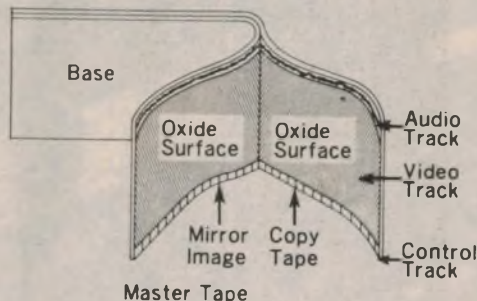structed and has obviously been designed to withstand the heavy handling which equipment of this kind has to withstand in the field. It is both robust in the purely mechanical sense, and skilfully designed with the ham handed operator in mind. Carefully thought out interlocks make it virtually impossible for incorrect operation of the controls to cause



*The master and slave tapes are wound oxide to oxide. This is the reason the master tape must be a mirror image.*

damage to either the machine or the tape.

The copier is aimed mainly at educational authorities and similar organisations which have a need to generate and distribute large numbers of tape copies of educational and similar subject matter. At the time of writing the equipment has been demonstrated to educational authorities at all levels, in Queensland,

NSW, Victoria, South Australia, and the ACT.

Other possible users would be industrial and sales organisations. At the industrial level, with the increasing complexity of modern technology, it is becoming more and more important that technical staff be regularly instructed or re-trained as new equipment and new processes are introduced.

Audio visual presentation has long been recognised as the most effective means of instruction, and often far safer and less costly than initial instruction on the equipment itself. And tape has the versatility and quality which makes it ideal in many such applications, provided duplicates for distribution to all branches and sections of a company can be made relatively cheaply.

Again, tape is often an ideal medium for sales promotion—provided duplicates can be readily created to cover, say, a nation wide advertising campaign.

On a longer term basis this system, or something like it, may help to establish the video tape player in the home. At the present time the two barriers to the general use of tape players is their relatively high cost and the limited amount of program material available to buy or rent. Even assuming the hardware cost can be reduced, some means of producing adequate quantities of pre-recorded tapes, at a reasonable cost, must still be found.

## FOR UNDER \$500 IT MUST BE ONE OF THE BEST SYSTEMS AVAILABLE



**KENWOOD KS-3000**

- FM / AM Stereo Receiver 50 watts per channel (8Ω Music Power)
- MIC Mixing to add your own voice
- The Powerful Kenwood Speaker System
- The Precision Kenwood Turntable and its Automatic Functions

# APOLLO HI-FI CENTRE

283 Victoria Road, Marrickville. Telephone: 560 9019





SC-2002

## The True Hi-Fi Front-Loading Cassette Deck. It makes sense.

A well-made cassette tape deck these days gives open reel a good run for the money.

If you're involved with music at the true hi-fi level, here's a reliable one from Sansui. Note:

Front-loading convenience means positioning your tapes right-side up and keeping them vertical and fully visible at all times. Important? You'll discover front-loading saves a lot of tape trouble.

The electronic DC servomotor gives constant speed regulation regardless of voltage changes or tape loads. Independent capstan drive contributes to very low wow/flutter (0.1%). Fully automatic stop and shut-off is even more operating convenience.

The SC-2002 makes sense in other ways, too. Dolby noise reduction ensures recordings made from any source will playback with a drastically reduced tape hiss and noise content.

And such features as output level control, left/right independent recording level controls and wide dynamic range mic circuits contribute to fine sound performance.

The SC-2002 is one of four fine Sansui front-loading decks now available in different styles and price ranges.

When you come right down to it, our true hi-fi components sound so good because hi-fi is the only thing we make.

Maybe this is why we always make sense to people who love music.

**Sansui True Hi-Fi** *Sansui*

EASTERN AUSTRALIA: RANK INDUSTRIES AUSTRALIA PTY. LTD. SYDNEY: 12 Barcoo Street, East Roseville, N.S.W. 2069  
Phone: 406 5666 MELBOURNE: 68 Queensbridge Street, South Melbourne, Vic. 3205 Phone: 62 0031 ADELAIDE: 234  
Currie Street, Adelaide, S.A. 5000 Phone: 212 2555 BRISBANE: 14 Proe Street, Fortitude Valley, Brisbane, Qld. 4006  
Phone: 52 7333 CANBERRA: 25 Molonglo Mall, Fyshwick, Canberra, A.C.T. Phone: 95 2144 / WESTERN AUSTRALIA:  
ATKINS CARLYLE LTD, 44 Belmont Avenue, Belmont, Western Australia 6104 Phone: 65 0511 / SANSUI ELECTRIC CO.,  
LTD. 14-1, 2-chome, Izumi, Suginami-ku, Tokyo 168, Japan



# Powerful desktop calculator from Hewlett-Packard

*... programmable unit features live keyboard*

The trend towards powerful desktop calculators is dramatically illustrated by Hewlett-Packard's recently announced model 9825A. This is a programmable calculator with many features previously found only on minicomputers, and is suitable for both process control and stand-alone applications.

The new HP 9825A desktop calculator is designed primarily for use in the fields of engineering, research and statistics. The 9825's speed, interfacing abilities and computer-like features make it particularly well suited for use as the controller of an instrument system, for pilot process control applications, remote data collection and production control.

As supplied in basic form, the 9825 comes with an 8k byte memory. The operating system is hard wired, and is separate from the main 8k byte memory. Optional plug-in ROMs are available to extend the language capabilities of the calculator. For example, a matrix ROM adds standard matrix operators such as inversion and multiplication, plus a large number of multi-dimensional array operators.

Significant features embodied in the 9825 that provide major user benefits include: two-level priority interrupt; live

keyboard; direct memory access with input speeds up to 400,000 16-bit words per second; high performance, bidirectional tape drive; multi-dimensional arrays; and automatic memory record and load.

The built-in maths functions provide the standard exponential and trig functions, plus some unexpected additional functions. A random number generator and two kinds of rounding functions provide additional convenience. Accuracy to 12 digits with a dynamic range of  $10^{-99}$  to  $10^{+99}$  and an internal calculation range of  $10^{-511}$  to  $10^{+511}$  are all part of the 9825's capabilities.

The 9825 uses a high level programming language called HPL. This formula-oriented language is easy to learn and ideally suited for controller applications as well as for data processing. HPL handles subroutine nesting and flags, and allows 26 simple variables and 26 multi-

dimensional array variables, limited only by the size of the calculator memory.

Edition of lines and characters is simple, and error locations are identified by a flashing cursor in the display. Fixed and floating point formats can be set by the user from the typewriter-like keyboard.

The 9825's keyboard has 12 special function keys that, with a shift function, can handle 24 different operations. The keys help in program writing and in peripheral and instrument control. They can serve as immediate-execute keys, call keys for sub-routines, and as typing aids.

A special feature of the 9825 is the live keyboard, a feature previously not found on a desktop calculator. With the keyboard, the user can examine and change program variables, perform complex calculations, call subroutines, and record and list programs while the calculator is performing other functions.


The ability to accommodate a number of tasks simultaneously is another important feature of the 9825. This is known as interrupt ability, and is available in the Extended I/O ROM. The calculator can thus act as a controller for several instruments or peripherals which require attention at unpredictable rates or times.

Data readout from the 9825 is via a new 32-character LED display and a built-in 16-character thermal printer, which provide upper and lower case alphanumeric read-out. The display and printer provide the full ASCII character set. Some European and Greek characters are also available in an optional ROM.

The tape cartridge has two tracks and can hold up to 250k bytes of data. Data transfer rate is 2.75k bytes per second, and automatic verification ensures that important information has been successfully stored on tape.

Using the cartridge, the operator can perform rapid memory load and record operations. In the event of a power failure, this feature, coupled with the "autostart" feature, can reload the calculator's memory and continue whatever program had been running.

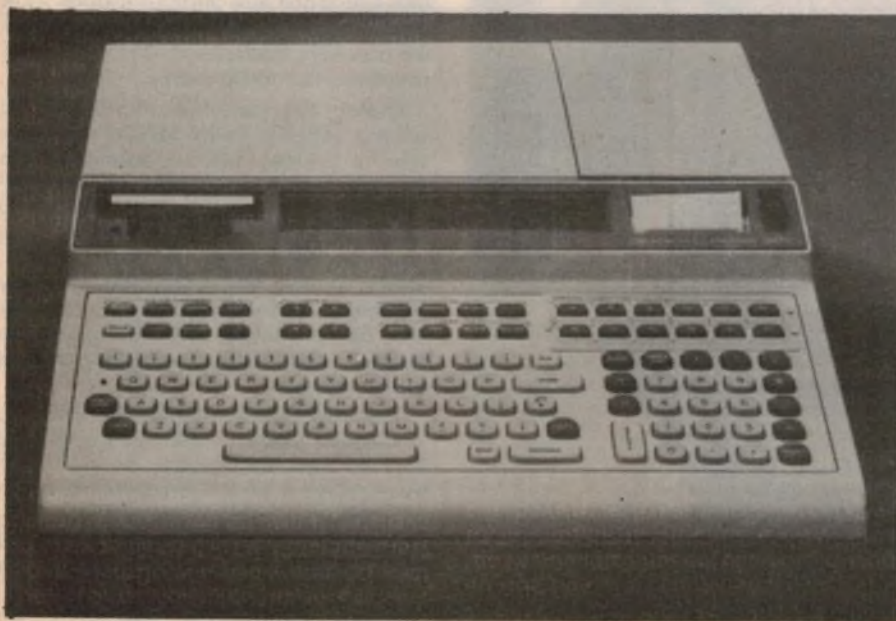The HP 9825A desktop calculator is priced around the \$5720 mark (plus sales tax). For further information, contact Hewlett-Packard Australia Pty Ltd. ☉



The HP 9825A programmable desktop calculator can interface with or control a variety of instruments, including printers, paper tape readers and chart plotters.



*In the world of the picosecond . . .*

# New laser may solve bio-chemical mysteries

At London University's Imperial College a research team has developed a laser capable of producing pulses as short as one third of a picosecond. Coupled with the parallel development of X-ray operating frequencies, the new laser promises to open the way to scientific investigation of events that occur at molecular speed, and to provide more detailed molecular structural analysis.

The "big" sciences, which need large and costly machines such as accelerators or radiotelescopes, tend to dominate the research expenditure of most countries. But it is cheering, if paradoxical, that many of the most important advances in understanding and technology depend on the insight of individuals working quietly and relatively inexpensively in small laboratories.

Firmly entrenched in this "small" science tradition is a small group of scientists in the optics section of the physics department at Imperial College, London University.

Working under Professor D.J. Bradley, and in conjunction with a small laser-

optics group at Queen's University, Belfast, Northern Ireland, they have taken Britain into the lead in the very competitive and rather esoteric world of ultra-short pulses of laser light.

In recent years, lasers have found an enormous number of applications, for example in range finding, metal cutting and even surgery (the welding of detached retinas). Right now, there is increasing research pressure in three directions: scientists trying to produce lasers of ever greater power; to produce lasers working at ever higher frequencies—thus producing light beams in the ultraviolet and soft X-ray regions beyond the visible spectrum; and to produce

by **ANTHONY TUCKER**

Science correspondent, "The Guardian", London.

pulses of laser light of incredibly short duration.

These very short times have names of their own, some of which are familiar. A millisecond is a thousandth of a second, a microsecond one millionth, and a nanosecond a thousandth part of a millionth of a second.

A picosecond—and believe it or not this is not the smallest current unit—is a mere millionth of a millionth of a second.

Although the importance of these extremely short times will begin to emerge more clearly as time goes on, the basic reason for their importance in research is that they typify the kind of timescale on which molecular events take place. When, in its miraculous and still mysterious way, a catalyst transforms one substance into another it does so at picosecond speed. It is still mysterious for precisely that reason—for it happens much too fast to be seen.

During the past few months, using what is called a mode locked dye laser whose pulses are measured by a specially modified streak camera, the Imperial College group has consistently produced pulses of light that are only one third of a picosecond in duration. This is at least ten times, and probably 50 times, shorter than any other laboratory has produced. Even the ability to measure such extremely short pulses is itself a triumph.

The importance of such short pulses, in the first place, is that they open the way to new techniques of scientific investigation which promise to open windows on events happening at molecular speed—rather as ultra-high speed photography can "stop" a bullet in flight.

Further, coupled with ability to control the frequency and energy intensity of the beam and using the property of fre-



*Professor D. J. Bradley (left) and a member of his research team demonstrate the new laser. Pulses as short as one third of a picosecond can be produced.*



quency resonance at molecular level, they open the way to new and potentially very specific and very efficient chemical transformations and separations. One of these might be the fusing of hydrogen isotopes to produce helium and large amounts of energy—the controlled nuclear fusion reactor.

However, while it is true that the drive for ultra-short pulse and high energy laser research has stemmed from fusion research, the greatest benefits might accrue from quite different fields. The key timescale of molecular functions (as distinct from structures) is around or less than a picosecond. This is the time it takes for electrons to trigger a process, or for molecules to transform in chemical and photo-biological processes.

One of the most important unsolved scientific mysteries is what happens during those first few fragments of a microsecond of natural absorption of light energy in the photosynthetic process. So far, interpretations have been indirect and incomplete. Unlocking the secrets of that process alone could provide man with new and powerful routes towards solving both his food and energy shortage problems.

The range of possibilities is large and, with the obtainable wavelengths of laser light shortening all the time (the Imperial College group is already producing laser beams in the hard ultraviolet and expects to produce its first soft X-ray beam within a year or so), the detail that might be observed by ultra-short pulse investigation might be much greater than by other techniques.

Because the amount of information that can be revealed by light as an investigatory tool depends on its wavelength, and the shorter the wavelength the greater the detail that can be revealed, the development of soft X-ray lasers — even without the parallel ultra-short pulse technology — might greatly simplify the task of molecular structure investigation.

At present, and in spite of the aid of automatic systems and computer analysis, the determination of structure rests on extremely difficult and complex interpretation of X-ray diffraction patterns. All present X-ray sources are incoherent — that is, they consist of radiations in a range of wavelengths.

X-rays are necessary because their wavelengths relate to molecular atomic distances and can therefore record the positions of individual atoms, but the range of wavelengths in the beams currently used for necessary structural analysis produce patterns of immense complexity.

The use of coherent X-ray beams, even if these were at first of fairly long wavelength (soft X-rays), would greatly simplify the determination of basic three dimensional molecular structure, providing a tool of greater directness and power than anything so far possessed by crystallographers.

**DSS**

**DIRECT SUPPLY SWITCHES**

**PROFESSIONAL QUALITY SWITCHES FOR  
THE HOBBYIST AT REALISTIC PRICES  
WITH MAIL ORDER CONVENIENCE  
HONEYWELL MICRO SWITCH**



**SERIES 8 PUSHBUTTONS**

**ALTERNATE ACTION  
(PUSH ON PUSH OFF)**

**8N1011 1 POLE C/O \$1-52**

**MOMENTARY ACTION**

**8N1021 1 POLE C/O \$1-52**

**8N2021 2 POLE C/O \$2-67**

**INCLUDES PLASTIC PUSHBUTTON IN  
RED WHITE OR BLACK, STATE CHOICE**




**SERIES 8 TOGGLES**

**8A1011 1 POLE C/O \$1-05**

**8A2011 2 POLE C/O \$1-31**

**8A3011 3 POLE C/O \$2-10**

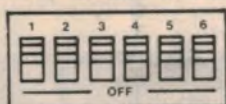


**DUAL IN LINE DIP SWITCHES**

**DSS106 6 POLE \$2-79**

**DSS107 7 POLE \$3-26**

**DSS108 8 POLE \$3-75**

**DSS110 10 POLE \$4-67**

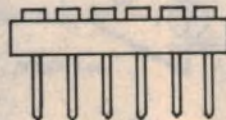

**MANY OTHER TYPES AVAILABLE  
SEND \$1 FOR CATALOG  
MAIL YOUR ORDER WITH CHEQUE  
OR MONEY ORDER TO**

**P.O. BOX 100 SCORESBY 3179**

**INCLUDE \$1 FOR POSTAGE & PACKING  
VICTORIA ONLY OR \$1-50 INTERSTATE**



# Auto Rhythm Unit For Electronic Organs

Here is the first of a two part article giving constructional details of a rhythm unit for use with electronic organs, or as a self-contained rhythm unit. In this first part the author gives details of a unit capable of simulating eight percussion instruments.

by DAVID EDWARDS

A rhythm section, as used in an electronic organ or similar instrument, consists of three main parts. An oscillator, adjustable in frequency over a suitable range, is used to set the basic tempo of the rhythm, and drives the next section, called the rhythm generator. This consists of a large read-only memory or ROM containing the selected rhythm patterns, and the associated drive circuitry. The remaining part is the instrument simulators themselves, which are triggered by the outputs from the rhythm generator.

The number of bits of ROM memory storage required is determined by the length of the rhythms, the number of rhythms, and the number of instruments required to be driven. With a typical system having eight instruments and twelve rhythms with each rhythm repeating after 32 steps or elementary times, a memory capacity of  $8 \times 12 \times 32 = 3072$  bits is required.

While memories of this size can be fabricated from diode arrays, the number of diodes required is prohibitive, and there are also problems concerning physical assembly and reliability. For this reason semiconductor manufacturers have developed rhythm generators using integrated circuit technology, which are a much more practical proposition.

These are now available in single order quantities, and form the basis of the present article. Using these chips, all that is required is a suitable oscillator, power supply and instrument generator. In this article we present a design for eight percussion instrument simulators, and in a future article will give details of the various rhythm generator chips which are available, and how to use them.

The eight instruments which we have simulated are as follows: bass drum, tom tom, low bongos, high bongos, snare drum, short cymbals, long cymbals and maracas. These can all be triggered directly with simple switches, so that it

is possible to use them alone, for special effects, as well as in a manual percussions or rhythm section.

The switches used can be simple momentary contact types, arranged in a bank of eight, and operated by hand as a test signal generator. It would also be possible to build the simulator into a console, with a suitable arrangement of switches so that it could be played in a similar manner to a conventional percussion grouping.

Such a console would probably have some foot operated switches, as well as various types of hand operated ones. A

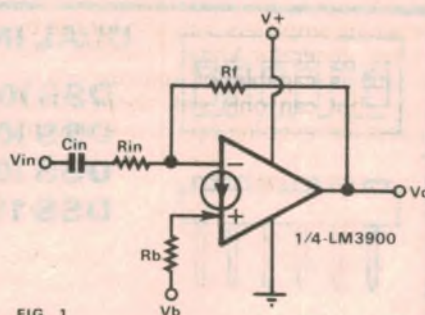


FIG 1  
This diagram shows the basic circuit of the LM3900, as used in the instrument simulator.

complete copy of a percussion grouping could be made, so that the same types of hand and foot movement would be required to "play" it, or a more convenient constructional arrangement could be used, with simple hand or finger operated switches.

Another idea would be to use touch operated switches, such as those featured in the March 1976 CDI section, to replace the mechanical switches. This approach may prove to be cheaper, as costly switches will be eliminated.

Organ enthusiasts may also care

to experiment with schemes which trigger the sounds when various pedal or manual keys are operated.

We envisage that if a spare keying line was available, say from the bass pedal section, then this could be used to trip the bass drum simulator, which would then operate when any of these pedals were operated. If such facilities were not available, it may be necessary to provide circuitry which could extract suitable trigger pulses from the relevant audio signals.


Other possibilities include providing an auxiliary manual or pedal board, to operate particular sections of the simulator, or even utilising little used keys or pedals for this purpose. The circuitry necessary for these provisions will of course depend on the particular organ, and its internal circuitry.

We have implemented our design using a quad op-amp IC. We used the National Semiconductor LM3900 device, which contains four current differencing amplifiers. These do not require a split supply rail for their operation. Before discussing the circuit in detail, we will first consider the operation of the basic amplifier, as a good understanding of this will be required to follow the operation of the complete circuit.

Fig. 1 shows a basic AC coupled amplifier. Note the different symbol for the amplifier. This is recommended to avoid confusion with standard op-amps, as basic circuit operation is different. The current source symbol between the inputs implies the current mode of operation, and also signifies that current is removed from the negative input. The current arrow on the positive input indicates that this functions as a current input.

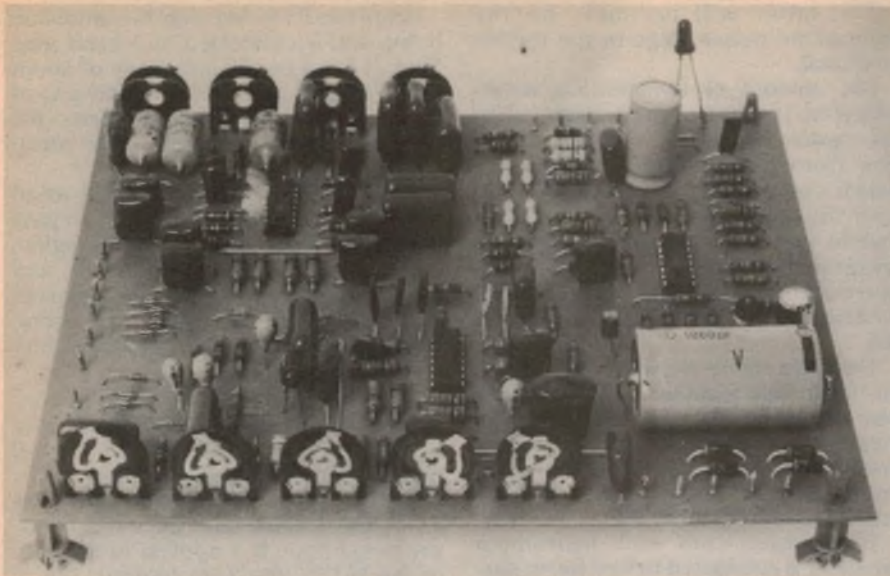Consider first the DC biasing circuit, formed by  $V_b$ ,  $R_b$  and  $R_f$ . Neglecting the input bias current, and remembering that both input are clamped one  $V_{be}$  above





ground, we can determine the currents flowing into the inputs. (The inputs are forced to this voltage by the operation of the internal circuit of the amplifier.)

The current flowing into the negative input is given by  $V_o/R_f$ , and the positive input current is given by  $V_b/R_b$ . The applied negative feedback forces these currents to be the same, so that  $V_o/R_f = V_b/R_b$ . Thus  $V_o = V_b R_f/R_b$ , and if  $V_b = V+ / 2$ , and  $R_f = R_b$ , then  $V_o = V+ / 2$ .

In other words, if the two resistors are equal, and if the bias supply voltage is half the supply voltage, then the output is biased at half supply voltage too. Of course, the bias voltages source can be used to bias more than one amplifier, as it is required to supply only the combined bias currents.

In similar fashion, the AC gain can be determined, and as might be expected, is given by  $-R_f/R_{in}$ . The input impedance is determined solely by  $R_{in}$ , and is limited only by the input biasing current required by the negative input and by the magnitude of the noise voltage produced by  $R_{in}$ . A non-inverting amplifier can be achieved simply by connecting  $R_{in}$  to the positive input, rather than the negative input.

Before continuing, we should emphasise that the circuits about to be described are basically experimental in nature, in that they can be modified to suit particular needs and tastes. The sound effects are all capable of being "tailored", for example. However, we have designed a printed circuit board for use with the circuit configuration described, which should form a good base from which to commence.

A small power supply has been incorporated on the board, and made available for external use. Our prototype was able to supply in excess of 50mA at +30VDC, and was able to source or sink in excess of 5mA at +15VDC, in addition

to the currents taken by the circuitry on the board itself. A transformer with a 24V secondary is required. Higher rated (voltage) transformers can be used, provided due notice is taken of the increased dissipation in the regulator.

Turning now to the main circuit diagram, Fig. 2, we can examine the various sections. The power supply is formed by a simple zener regulated unit. The zener controls a BC547 general purpose NPN transistor, which is capable of supplying currents of up to 100mA. A 33uF electrolytic capacitor ensures adequate ripple rejection.

Amplifier A2 is used to split the supply rail, to supply the bias voltage for the remaining amplifiers, and also for use by rhythm generator chips. Normally, the LM3900 is capable of sourcing about 18mA, but can only sink about 1.2mA (unless the inverting input is overdriven). So to ensure symmetrical source/sink characteristics, a 1.8k resistor to ground has been provided. This means that we can sink or source about 9mA.

Amplifiers C1, C2, C3 and C4 are all connected with twin-T networks in the feedback paths, and are used to simulate drum type instruments. They are identical except for the frequency determining capacitors. Output biasing is determined by the 100k, 82k and two 10k resistors, so that the output voltage is approximately +14V.

The bias supply voltage is decoupled by a 1k/470uF resistor/capacitor combination. This prevents interference from other sections of the circuit triggering the drum simulators. This decoupled supply also used to feed other sections of the circuit.

Each drum-effect circuit is adjusted to be just below the point of oscillation by the 4.7k trimpots, so that when excited, a damped, decaying sinusoidal waveform results. The length of the resulting waveform is dependent on the set-

## PARTS LIST

### SEMICONDUCTORS

- 3 LM3900 quad op-amps
- 1 BC547 NPN silicon transistor, or equivalent
- 2 2N4360 P channel FETs, or equivalent
- 1 8.2V 400mW Zener diode
- 1 30V 400mW Zener diode
- 4 EM401 silicon diodes
- 17 1N4148 silicon diodes (see text)
- 1 red LED

### CAPACITORS

- 1 1000uF 63V pigtail electrolytic
- 1 470uF 25V PCB electrolytic
- 1 33uF 35V PCB electrolytic
- 2 10uF 35V tantalum
- 4 2.2uF 35V tantalum
- 6 0.47uF plastic
- 1 0.22uF plastic
- 3 0.15uF plastic
- 3 0.12uF plastic
- 14 0.1uF plastic
- 1 0.047uF plastic
- 4 0.01uF plastic
- 4 0.0022uF plastic
- 2 330pF plastic
- 1 10pF ceramic or polyester

### RESISTORS (all 1/2W rating)

- 1 10M, 17 1M, 5 470k, 1 330k, 1 180k,
- 3 120k, 19 100k, 4 82k,
- 2 26 10k, 4 6.8k, 1 3.3k, 2 1.8k, 2 1k,
- 1 270 ohm
- 3 2.2M trimpots
- 1 1M trimpot
- 1 10k trimpot
- 4 4.7k trimpots

### MISCELLANEOUS

- 1 printed circuit board, 180 x 152mm, coded 76pi9
- 1 transformer, 240V to 24V, 150mA or larger
- printed circuit board pins, insulated
- PCB standoffs, solder, hook-up wire, tinned copper wire

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with high ratings may generally be used provided they are physically compatible.

ting of the trimpot, and the frequency on the capacitors used. The 0.01uF capacitor in parallel with the 82k resistor serves to roll off the frequency response above 150Hz. (All four networks operate at lower frequencies than this.)

Excitation pulses are supplied by momentarily upsetting the bias conditions. This gives a predictable amount of excitation, without altering the damping or frequency of the wavetrain. Each input is via an RC combination, and the inputs are intended to be connected to the +30V rail by a mechanical switch or transistor.





**the speaker  
engineers**



**speaker  
systems**



**speaker  
units**



**speaker  
kits**

Distributed by Audioson International Pty. Ltd.

Sydney 938 1186    Melbourne 329 6066    Adelaide 337 7000    Perth 25 9993

The latter will normally be the appropriate output stage of the rhythm generator.

The amount of excitation is determined by the size of the resistor, while the capacitor prevents a further excitation from being supplied when the switch opens again. The diode in series with the input is necessary only for rhythm generators which do not have uncommitted outputs. With uncommitted outputs, and also if mechanical switches are used, the diode can be deleted.

The extra diode shown connected to the high bongo input serves to trigger this unit also when the snare drum input is triggered, to give the full effect of a snare drum. The diode prevents the snare drum from operating when the high bongos are operated, however.

The output from each instrument simulator is attenuated before being passed to the mixer stages. This is necessary to prevent overloading of the mixer.

We have used fixed resistors for the attenuators, although these could be made variable if desired. This may be advantageous if the unit is used as the basis of a percussion group, in which case they could be varied by the player during operation.

The remaining instruments, the low cymbals, high cymbals, maracas and snare drum, all utilise a white noise source, and gain their characteristics from suitable filters, in conjunction with envelope shaping.

Amplifier B4 is used as a non-inverting AC amplifier to boost the intrinsic output of the zener diode noise source. The gain is adjusted by varying the 10k trimpot, to give maximum undistorted noise. Note that it may be necessary to adjust the 180k resistor used to set the current level through the zener, to obtain a good undistorted noise signal.

A 10pF capacitor is used to restrict the bandwidth of the noise signal to about 15kHz. This is required to prevent slew rate limiting in the following stages.

Amplifier B1 is fed with the amplified noise, and is connected as a band pass filter. It has a centre frequency of about 2kHz, a band pass gain of 1, and a Q of about 1. The filtered noise forms the basis of the snare section of the snare drum.

Amplifier B3 is also connected as an active filter, but this time as a high pass filter. It has a gain of 1 in the pass region, a corner frequency of about 2kHz, and a Q of about 1. Its output signal serves as the basis of the three remaining instruments, the short cymbals, long cymbals and maracas.

Two P-channel FETs are used to control the amplitudes of the filtered noise signals. For the snare drum, a control pulse is generated when the input is connected to the +30V rail. This pulse has a very short attack time, but a much longer decay time. It is applied to the gate of the FET by the 2.2M trimpot. This is adjusted so that at maximum pulse amplitude, pinch-off is only just achieved.

Thus the noise signal at the source of the FET rises rapidly to a peak, and then decays slowly. As with the drum instruments, the input diode is not necessary for open drain type switches.

The long and short cymbal control signals are generated in a similar manner, and applied to the gate of the second FET by diodes. These diodes prevent interaction between the instruments. The maracas signal differs in that it has a much longer rise time, so that the resulting noise signal rises and falls in intensity at a much lower rate.

The controlled noise signals are then summed in amplifier B2, before being attenuated and passed to the mixer. This is composed of amplifiers A3 and A4, and has three outputs, Right, Left and Mono. The mono signal is 20dB lower in intensity than the other two signals.

Ten resistors are provided, enabling the five inputs to be spaced across the stereo image. The values we have chosen can be varied if required. The mono sig-



*LEFT: Use this photograph of the completed board assembly as an aid to construction. Note the use of circuit board pins for all external connections.*

*RIGHT: This circuit diagram shows all the components which are mounted on the printed circuit board. The twelve op-amps are contained in only three packages.*







# A New Range of Mixing Units with More Facilities Per Dollar



Allen & Heath, the British made range of mixing units renowned for their versatility, are now available in Australia through Optro Pty. Ltd. One of these units will meet your stage or studio needs — and at a sensible price.

#### THE MINIMIX

A miniature six channel stereo mixer with giant capabilities. Even though its size, ruggedness and battery provision make it extremely portable it is capable of the highest quality results suitable for broadcasting or mastering. The minimix can also be extended as your needs grow.

#### THE MONMIX

A five channel line stereo mixer.

#### THE AUXBOX

Designed for studio conditions when several auxiliary facilities become necessary.

#### THE POP-MIXER

A 18 channel (max.) stereo output, modular, portable sound reinforcement mixer with a host of special features. It's ideal for use by pop groups because it is lightweight, small, rugged, compatible, positive in operation, reliable and professionally presented.

#### MODULAR CONSOLE

This unit features all the sophisticated functions that the recording engineer needs for up to sixteen track recording and mixdown. These facilities are coupled with modular construction for easy expansion.

For full technical information on any unit contact the sole Australian agent —

**OPTRO PTY. LTD.**  
17 Arrawatta Street, Carnegie, Victoria  
Phone 569 0978, 569 0979

**OPTRO**  
PTY LTD



## Rhythm Unit

nal is produced by summing the left and right signals across a 1k resistor.

The remaining amplifier, number A1, is used to drive a LED, as a downbeat indicator. It can be triggered from either a positive or negative going input pulse, and turns on the LED for about 350ms. The printed circuit board overlay shows


the connections required for negative edge triggering. To obtain positive edge triggering, simply change the 10k resistor connected to ground for a diode, and place the input diode in the alternative position.

Assembly of the components on to the PCB should not be difficult. The PCB is coded 76pi9, and it measures 180 x 152mm. As you can see in the photograph, all the trimpots are mounted on the edges of the board. Input and output points are also at the edges of the board.

We recommend the PCB stakes be used for all connections to the board. This will prevent the fine tracks from lifting due to mechanical strain. Commence construction by fitting them, and then fit the five links, which need not be insulated.

Next fit all the resistors to the board. These are all ½ watt types, and should be mounted close to the board. It will

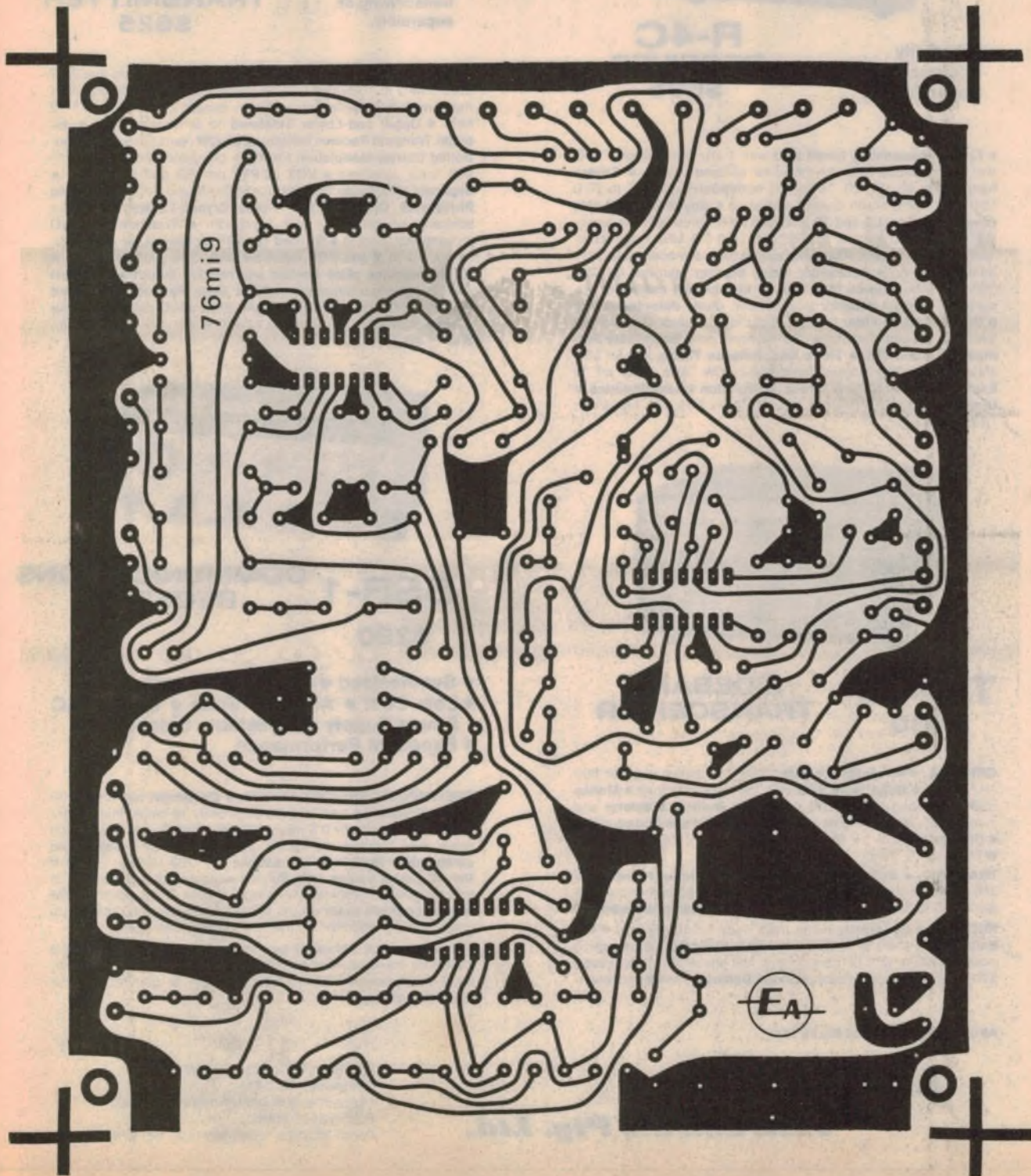*This is a full sized reproduction of the PCB pattern, shown from the copper side, and can be traced if desired.*







# DRAKE

## AMATEUR C LINE

### Superior performance—versatility!



Versatility . . .  
Accuracy . . .  
Dependability . . .

### R-4C RECEIVER \$695

• **Linear permeability tuned VFO** with 1 kHz dial divisions. VFO and crystal frequencies pre-mixed for all-band stability • **Covers ham bands** 80, 40, 20, 15 meters completely and 28.5 to 29.0 MHz of 10 meters with crystals furnished • **Any fifteen 500 kHz ranges between 1.5 and 30 MHz** can be covered with accessory crystals for 160 meters, MARS, etc. (5.0-6.0 MHz not recommended) • **Electronic Passband tuning** gives sideband selection, without retuning • **Accessory Noise blanker** operates on CW, SSB, and AM • **Notch filter and 25 kHz crystal calibrator** are built-in • **Product detector** for SSB/CW • **diode detector** for AM • **Crystal Lattice Filter** gives superior shape factor and ultimate selectivity for better adjacent channel rejection • **Solid State Permeability Tune VFO** • **Three AGC Release Times**, two for SSB and AM plus fast release for break-in CW. Also AGC off • **Excellent Overload and Cross Modulation characteristics** • **Dimensions:** 5½"H, 10¾"W, 12¼"D (14.0 x 27.3 x 31.1 cm), **wt.:** 16 lbs. (7.3 kg)



### TR-4C \$630 SIDE BAND TRANSCIEVER

**GENERAL:** • **All amateur bands** 10 thru 80 meters in seven 600 kHz ranges • **Solid State VFO** with 1 kHz dial divisions • **Modes** SSB Upper and Lower, CW and AM • **Built-in Sidetone** and automatic T/R switching on CW • **30 tubes and semi-conductors** • **Dimensions:** 5½"H, 10¾"W, 14¾"D (14.0 x 27.3 x 36.5 cm), **WT.:** 16 lbs. (7.3 kg)

**TRANSMIT:** • **VOX or PTT** on SSB or AM • **Input Power:** SSB 300 watts PEP; AM 260 watts PEP, controlled carrier compatible with SSB linears; CW 260 watts • **Adjustable pi-network.**

**RECEIVE:** • **Sensitivity** better than ½µV for 10 dB S/N • **I.F. Selectivity** 2.1 kHz @ 6 dB, 3.6 kHz @ 6 dB • **AGC** full on receive modes, variable with RF gain control, fast attack and slow release with noise pulse suppression • **Diode Detector** for AM reception.

ABOVE PRICES INCLUDE SALES TAX

## ELMEASCO

### Instruments Pty. Ltd.



Use VFO of either  
R-4C or T-4XC for  
transceiving or  
separately.

### T-4XC TRANSMITTER \$625

• **Covers ham bands** 80, 40, 20, 15 meters completely and 28.5 to 29.0 MHz of 10 meters with crystals furnished; MARS and other frequencies with accessory crystals, except 2.3-3, 5-6, 10.5-12 MHz • **Upper and Lower Sideband** on all frequencies • **Automatic Transmit Receive Switching on CW** (semi break-in) • **Controlled Carrier Modulation for AM** is completely compatible with SSB linear amplifiers • **VOX or PTT** on SSB and AM built-in • **Separate VOX Delay Controls** for SSB/AM and CW • **Adjustable Pi-Network Output** • **Two 8-pole Crystal-Lattice Filters** for sideband selection, 2.4 kHz bandwidth • **Transmitting AGC** prevents flat topping • **Shaped Grid Block Keying** with side tone output • **200 Watts PEP Input on SSB**—200 watts input CW • **Meter indicates plate current and relative output** • **Compact size; rugged construction** • **Solid State Permeability Tuned VFO** with 1 kHz dial divisions • **Solid State HF Crystal Oscillator** • **Dimensions:** 5½"H, 10¾"W, 12¼"D (14.0 x 27.3 x 31.1 cm), **Wt.:** 14 lbs. (6.4 kg)



### SSR-1 \$290 COMMUNICATIONS RECEIVER

• **Synthesized** • **General Coverage**  
• **Low Cost** • **All Solid State** • **Built-in AC Power Supply** • **Selectable Sidebands**  
• **Excellent Performance**

**PRELIMINARY SPECIFICATIONS:** • **Coverage:** 500 kHz to 30 MHz • **Frequency** can be read accurately to better than 5 kHz • **Sensitivity** typically 0.5 microvolts for 10 dB S + N/N SSB and better than 2 microvolts for 10 dB S + N/N AM • **Selectable sidebands** • **Built-in power supply:** 117/234 VAC ± 20% • **If the AC power source fails** the unit switches automatically to an internal battery pack which uses eight D-cells (not supplied) • **For reduced current drain** on DC operation the dials do not light up unless a red pushbutton on the front panel is depressed.

The performance, versatility, size and low cost of the SSR-1 make it ideal for use as a stand-by amateur or novice-amateur receiver, short wave receiver, CB monitor receiver, or general purpose laboratory receiver.

P.O. Box 30, Concord, N.S.W. 2137.  
Telephone: 736 2888  
Melbourne: 233 4044; Adelaide: 42 6666;  
Brisbane: 36 5061  
Perth: 25 3144; Wellington N.Z.: 69 7566.



# Rhythm Unit

help later troubleshooting if they are all aligned with the colour bands oriented similarly, so that the values can later be read off easily.

Now fit all the smaller capacitors, as well as the diodes and transistors. Pay particular attention to the orientation of the tantalum and electrolytic capacitors, as well as the orientation of the diodes. The larger capacitors should be fitted last, so that they do not interfere with the mounting of the smaller components.

The remaining passive components can now be fitted, and the board then checked thoroughly for mistakes. Once you are sure that all is OK, the three integrated circuits can be fitted. These do not require sockets, and can be soldered directly to the board, using a minimum of heat and solder.

The board is now ready for testing. You will require a 24V AC supply, a stereo amplifier and speakers, nine momentary contact switches, four 10k resistors, four 1k resistors, and some shielded cable. If an AC supply is not available, a 35V DC supply will suffice.

First, set all trimpots in the extreme anti-clockwise position, when viewed from the edges of the board. Connect up the supply, and monitor the voltage on the emitter of the regular transistor. This should be about 30V. Then check the voltage at the +15V output terminal, and the voltage on the filtered +14V rail. This is available at the link above IC "C".


Now remove the supply. Connect the four 10k resistors to the drum inputs, and the four 1k resistors to the noise inputs. Then, using shielded cable, connect the free end of each resistor to the +30v rail (available between the two sets of inputs) via the switches.

The shields are used as the connector to the +30V rail. The remaining switch is connected between the +30V rail and the downbeat input. Mount the LED on the output terminals, with due regard to polarity.

You may require isolating capacitors for the inputs to the amplifier. If in doubt, fit 0.1uF plastic types in series with the active leads. The common lead connects near the right input.


Now apply power again, and check the operation of the downbeat LED. If you have fitted negative edge triggering, the LED should emit when the switch is released, and should last for about 350ms. Conversely, if you have fitted positive edge triggering, it should emit when the switch is closed. No clicks should be heard in the speakers when the downbeat is operated.

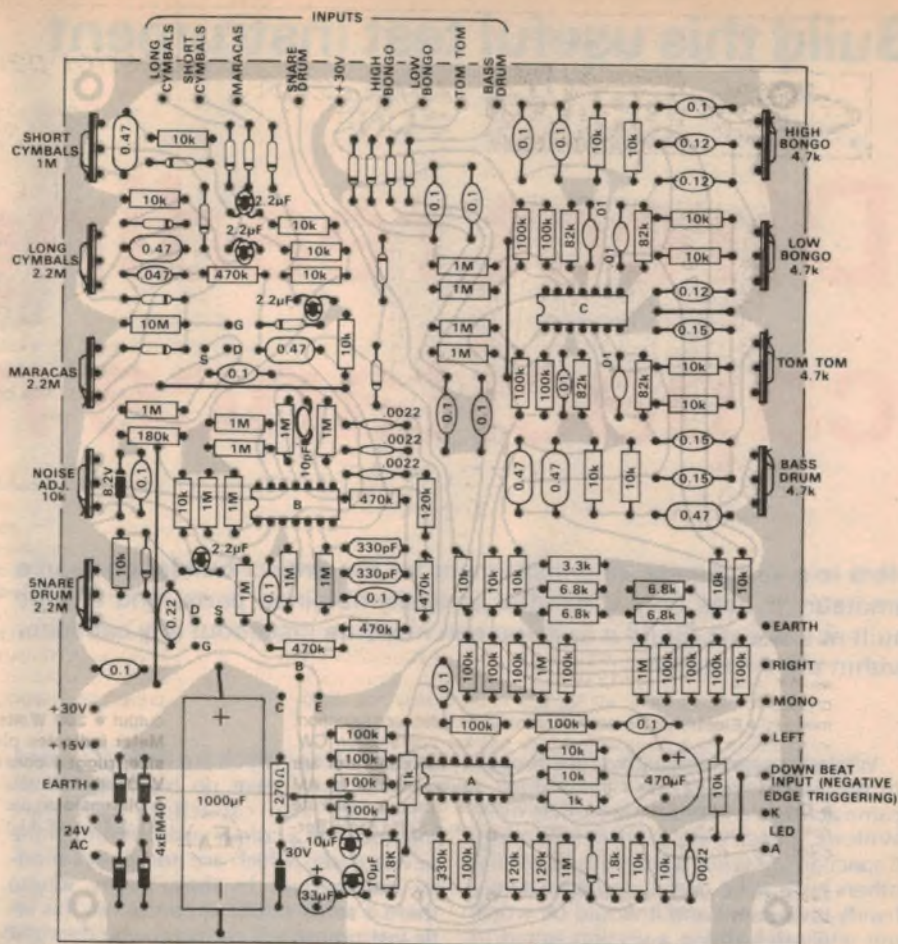The drum synthesisers are next on the checklist. Sounds should be produced when all four drum switches are operated. The length of each sound can be adjusted with the appropriate trimpot.



ABOVE: Use this overlay diagram as an aid to the placement of components. It is for the negative going downbeat input.

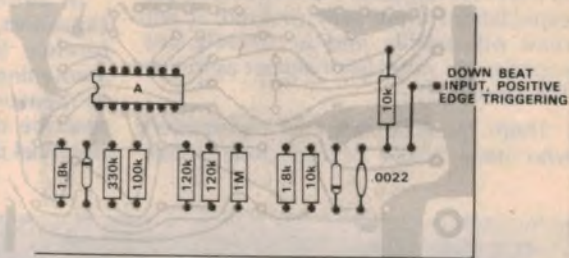RIGHT: This section of the overlay shows the components which need to be changed for the positive going downbeat input. Other components remain the same.



Care is required while making these adjustments, however, as if the twin-T circuits oscillate, very loud continuous sounds will be produced.

The actual length required is a matter of judgement. It helps if you are musical, or have a good memory for sounds. We found that the best effects were obtained if the lower frequency drums were adjusted for "thumps" rather than "rings".

You should now be ready to adjust the remaining circuits. Leave the noise adjusting trimpot in the maximum anti-clockwise position, and while triggering each input in turn, adjust the appropriate trimpot. The long cymbals, short cymbals and snares should be set so that there is no period of constant intensity sound before the decay starts. Do not trigger the inputs too rapidly, as otherwise the correct sound will not be obtained.

When the snares are adjusted, readjust the high bongo trimpot so that the drum

sound lasts as long as the snares. You should, at this stage, have discovered that when the snares are triggered, the high bongos also sound.

The maracas are adjusted in a similar manner to the cymbals, so that they rise to a peak fairly slowly, and then commence to decay again immediately. Once all instruments are working correctly, adjust the noise trimpot so that a suitably balanced sound is obtained.

Do not set this level too high, as otherwise slew rate limiting may occur in amplifier B4. This will cause a sudden increase in distortion, and is best avoided.

Your instrument simulator is now operational, and can be connected up as you desire. Details will be published in next month's issue of the various rhythm generator chips available, and how to use them with the percussion unit. Alternatively, you may care to experiment with some of the possibilities mentioned earlier in the article.



## Build this useful test instrument

# Direct reading capacitance meter

Here is a very handy little instrument for the project builder and radio amateur. It uses only a handful of easily-obtained parts, and can be built at low cost. Build it and you can measure just about any capacitor within a few seconds.

by IAN POGSON

While browsing through a recent copy of the English magazine "Television", I came across a constructional article by A. Willcox, describing a Direct Reading Capacitance Meter. It was agreed among others here at EA that it would be a very handy instrument and it would be worth our while describing a version suited to our Australian conditions and availability of parts. Having built the instrument, our expectations were fully realised; it will read off readily and accurately any capacitance value from almost as low as 1pF up to 5uF.

There must be many of our readers who have boxes of capacitors which

have markings which are difficult to read, or even now have no markings at all. There are also capacitors which are marked with a colour code, or one of the newer codes which are not always readily understood. In these cases where there is some doubt or confusion, this little instrument will come up with the right answer in a few seconds.

In addition to measuring ordinary capacitors, as there is a potential difference between the two terminals amounting to a volt or two, it is possible to measure electrolytics. The polarity must be observed of course. Also, this potential difference makes it possible to


measure the reverse biased capacitance of diodes, at the voltage appearing across the terminals. This is not all. Such other capacitance measurements as the junctions of transistors, coaxial cable, etc may also be made.

The device is quite simple, as may be seen from the circuit and the pictures. Following on from this, the cost is quite modest on current standards. The operation of the circuit is centred on the ever popular 555 timer IC. I will give a very brief description of the operation, but for readers who would like to go into this at a greater depth, I suggest that you refer to the original article by Mr Willcox, in the May, 1976 issue of "Television".

The two resistors selected by the range switch, together with the .01uF capacitors and part of the 555 timer, form an oscillator. After undergoing switching in other parts of the 555 timer the output emerges at pin 3 in the form of pulses. One part of the pulse is discharged through capacitor Cx, via the diode to the supply rail. The other part of the pulse discharges through the other diode and the meter. These pulses are integrated by the meter and give a reading in accordance with the capacitance Cx.

Calibration is achieved by adjusting the 47k trimpot, on any one of the ranges. This means that all other ranges will be correct, provided that all resistors of other ranges are close tolerance types. In point of fact, the four top resistors are important in this regard and 2% or better are advised. However, the 8.2M value is not readily available in such a close tolerance and 5% is normally used under these circumstances. Needless to say, we would not calibrate the device on this range.

The bottom row of switched resistors

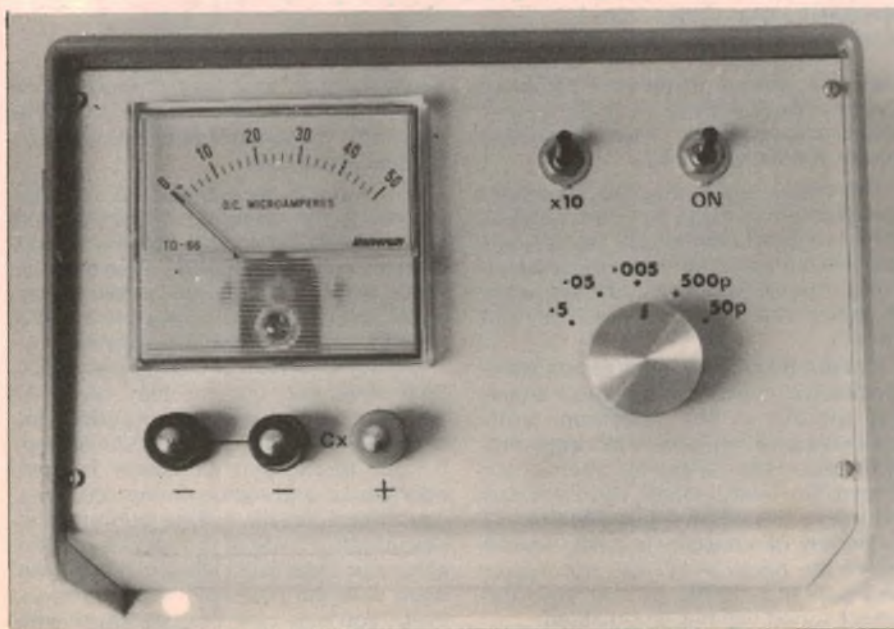

Above is a photograph of the completed capacitance meter. A standard plastic case with an aluminium front panel was used to house the prototype.









# DICK SMITH AND CHANNEL MASTER

## a must for good reception!

Installing your own TV or FM antenna is much simpler than you think! Why waste good money when you can do it yourself for a fraction of the price. All you need is a little commonsense, and my guide: 'How to install your own TV or FM antenna' Just 25c a copy or free when you order one of my Channel Master TV antennas.

Look what I received with MY Channel Master!



### Colorays!


**3110 COLORAY**  
Don't let this apparently simple antenna fool you! A revolutionary design, the 3110 combines moderate gain with amazingly high directivity and high front-to-back ratio which doesn't just kill ghosts in primary reception areas, it buries 'em, too! It has a built-in matching transformer which permits the use of either 300 ohm twinlead or 75 ohm coax without the need for a balun. It has insulation-piercing washers so there's no need to strip back the insulation on twinlead. How simple can you get?

CAT L-4024 ..... \$32.00

### SUPER COLORAY 3111

If the 3110 kills and buries ghosts, this one sets about exorcising the set, too! For particularly stubborn ghosts in the metropolitan area. The 3111 has 5dB more gain than the 3110, AND 3.5dB more ghost-killing power, too. It has all the features of the 3110, such as flat gain across the channel for peak color reception; such as rugged aluminium construction, etc, etc. This is the antenna to use if you don't like watching two (or ten!) pictures at once on the same set.

CAT L-4028 ..... \$48.00

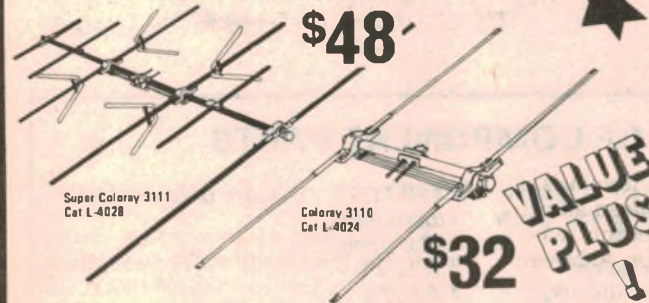

\$48

VALUE PLUS \$32

Super Coloray 3111  
Cat L-4028

Coloray 3110  
Cat L-4024

### SPIRAL INDOOR ANTENNA

If you're lucky enough to live in a strong signal area, you'll probably just get by with one of these spiral antennas - even with a colour set. But don't expect miracles if you are out of sight of the towers or over a few miles away. You then need an outside antenna.  
Cat L-4010 ..... \$5.20


### Indoor spirals



\$520
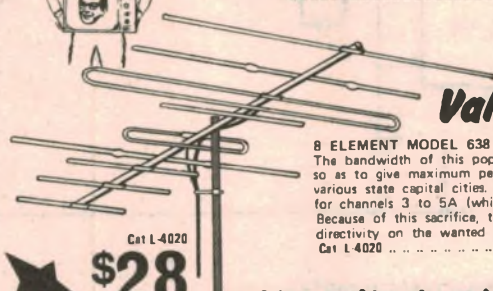
### Valiant 638

**8 ELEMENT MODEL 638 FOR CHANNELS 2 & 6-11**  
The bandwidth of this popular antenna is deliberately restricted so as to give maximum performance on the channels of the various state capital cities. This antenna would not be suitable for channels 3 to 5A (which also includes the FM radio band) Because of this sacrifice, the antenna features excellent gain and directivity on the wanted channels.  
Cat L-4020 ..... \$28.00




Cat L-4020

\$28

### FM radio is alive (and well)
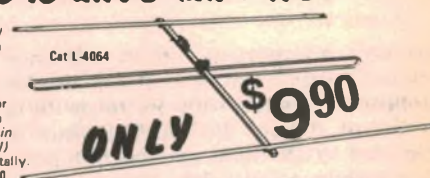
#### 3 ELEMENT FM ANTENNA

You can run your FM tuner from the TV antenna or a simple dipole hoisted up the wall, but you won't get optimum results. For just a few dollars, you can erect an antenna specifically designed for the FM bands (and your tuner will reward you for it!) This 3 element antenna is designed to cover the full 88-108MHz FM band (just in case we ever happen to get more stations!) and can be mounted vertically or horizontally.  
Cat L-4064 ..... \$9.90



Cat L-4064

ONLY \$9.90

## ACCESSORIES & BITS

Dick has a large range of accessories & bits-n-pieces to make your installation look really professional. For example: You could leave the lead-in draped across the wall, or you could do it properly:

### You may need something to get the signal down to the set...

**300 OHM RIBBON (TWINLEAD)** Does not unduly attenuate signal, but must be carefully routed to avoid metal, etc, which affects impedance.  
Cat W-2070 ..... 15c/metre. Bulk price 100m or more 8c/m.

**75 OHM COAX CABLE** Slightly higher attenuation, but not as prone to ghosting or impedance change. Ideal for color installations and 'trouble' areas.  
Cat W-2080 ..... 30c/metre. Bulk price 100m or more 20c/m.

And if you want to run more than one TV...

**4 SET TV/FM COUPLER** If you want to run TV sets or tuners from the same aerial, use one minimum loss and interaction. 300 ohms impedance.  
Cat L-4220 ..... \$3.50

**2 SET TV/FM COUPLER** As above but for 2 sets. Cat L-4218 ..... \$2.50

**4 SET TV/FM COUPLER** As above but 75 ohms impedance. Cat L-4474 ..... \$4.00

**2 SET TV/FM COUPLER** As above but for 2 sets. 75 ohms imp. Cat L-4472 ..... \$3.00

**FM/TV SPLITTER** This useful accessory splits the incoming 300 ohm twinlead into 3 different signal leads: VHF TV; UHF TV & FM Radio.  
Cat L-4210 ..... \$3.50

**3 WAY ANTENNA SWITCH** Attaches to the back of the TV set and allows up to 3 different antennas to be used for troublesome areas or long distance reception.  
Cat L-4232 ..... \$3.50

**BALUN - 75 TO 300 OHM** Allows you to use coax (for less ghosting) with sets of 300 ohms input impedance. Can also be used as an antenna balun (300 - 75 ohm) if waterproofed.  
Cat L-4464 ..... \$2.00

Cat W-2070

Cat W-2080

Cat L-4210

Cat L-4464

Cat L-4472

Cat L-4510

Cat L-4514

Cat L-4512

Cat P-2080

Cat P-2020

Cat L-4504

Cat L-4236

**WOODSCREW STANDOFF** Holds ribbon or coax flat, but out from walls and gutters, etc. Stops it flapping around in the breeze.  
Cat L-4510 ..... 25c each, 10 or more 20c each

**NAIL-IN STAND OFF** For ribbon only, lets you run it neatly along skirting boards, etc. Gives a neat, professional job.  
Cat L-4514 ..... 25c each, 10 or more 20c each

**STANDOFF ASSEMBLY** Use for standing off masts, etc. Complete with strap assembly (holds ribbon or coax).  
Cat L-4512 ..... 70c each, 10 or more 60c each

**RIBBON WALL PLUG & SOCKET** Designed to mount on wall or skirting board, gives professional looking connection.  
Cat P-2080 ..... 80c


**75 OHM WALL SOCKET** Mounts on wall or skirting board. Saves tripping over trailing leads when the set is not in use.  
Cat L-4504 ..... \$1.75

**FLUSH MTG 75 OHM WALL SOCKET** The deluxe job. Clean, flush fitting - designed for wall or skirting board mounting.  
Cat L-4053 ..... \$3.25

**75 OHM COAX CABLE PLUG** Terminates coaxial cable neatly and properly. Suits the 75 ohm wall socket.  
Cat P-2020 ..... 60c

**TV ANTENNA CLIP** Quick way to connect lead-in to set. Ideal when using portable sets. Strong plated springs with screw terminals & plastic handles.  
Cat L-4236 ..... 40c

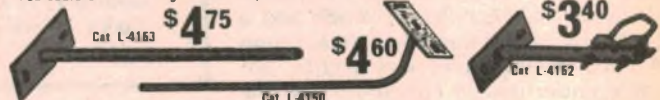Then, of course, the antenna cannot stay in mid-air by itself. You could use something to hold it up?



\$4.75

\$4.60

\$3.40

Cat L-4163

Cat L-4150

Cat L-4162

**BARGE BOARD MOUNT:** This is designed to mount practically any TV antenna from a vertical surface (such as a wall, barge board, chimney, etc) It is 55 inches (1.4m) long.  
Cat L-4160 ..... \$4.60

**CHIMNEY MOUNT:** Use the brick chimney to gain extra height and stability. This is a double arm, single strap, easy to mount unit. Complete with mast mount assembly.  
Cat L-4154 ..... \$6.80

**WALL MOUNT:** This can be used for wall or barge board mounting of a vertical mast up to 2 inches (50mm) in dia. Complete with 'u' bolt and nest assembly. 11 inches (28cm) long.  
Cat L-4162 ..... \$3.40

**WALL MOUNT:** Similar to previous unit, but 27 inches (68cm) long, to help clear wide eaves, etc. Also complete with 'u' bolt and nest mounting assembly.  
Cat L-4163 ..... \$4.75

Cat L-4154

\$6.80

Cat L-4163

**FREE\***  
WITH ANY ANTENNA PURCHASE

HOW OFTEN DO YOU SEE SOMETHING FREE THESE DAYS?

### This handy do-it-yourself guide to correct TV & FM antenna installation.

#### PLANNING TO PUT UP AN ANTENNA?

As Dick says, it is simple to do but there are a few pitfalls - traps for young players, if you like. Don't fall into them - let this do-it-yourself guide from Dick help you out. It's free when you buy an antenna from Dick. If you've got an antenna, and you've got problems, this guide can also help you out. Purchased separately, it's 25 cents. That's 25c which could save you a lot of time and effort, not to mention eye strain on a crook picture!

Cat B-4500 ..... 25c\*  
\* or free with any antenna purchase. Please request.



### DICK SMITH DEALERS :-

**HOBART - Aero Electronics - 34 8232**

123 A BATHURST STREET, HOBART, TASMANIA, 7000.

**DARWIN - Veneman & Wyatt Electronics - 81 3491**

24 STUART HIGHWAY, STUART PARK, N.T., 5794

Dick Smith Dealers carry many of our products - Prices may be slightly higher to cover freight costs.

## DICK SMITH ELECTRONICS GROUP

Head Office: Phone 439 5311. Telex AA20036. Cable Diksmi't Sydney.

Mail Orders: P.O. Box 747, Crows Nest, N.S.W., 2065.

N.S.W. Branches: GORE HILL - 162 Pacific Highway. 439 5311.

SYDNEY - 125 York St., 29 1126. BANKSTOWN - 361 Hume Hwy., 709 6600.

QLD. - 166 Logan Rd., Buranda, 391 6233.

Interstate Branches: VIC. - 656 Bridge Rd., Richmond, 42 1614.





## Capacitance Meter

and the insulated terminal. This terminal is the common Jabel brand and is mounted through a  $\frac{1}{4}$ in diameter hole. The resulting error in our case is about 0.5pF.

It may be possible to improve this zero error somewhat by punching out a hole in the metal panel about  $\frac{3}{8}$ in (16mm) in diameter and screwing a piece of insulating material over the hole. The terminal will then be mounted on the piece of insulation. We did not go to this trouble as we considered that the advantage gained was not really worth the extra effort.


As I said earlier, construction is not critical and it is left fairly open as to the way each individual tackles it. We used a piece of our general-purpose DIP PCB to mount the majority of components. All components, except the power supply, switches, meter and terminals, are mounted on the PCB. This may be seen in some detail in the photograph.

The 555 IC is mounted more or less centrally, with five of the oscillator resistors (including link) grouped on either side of the IC. The rest of the components are located around the IC. Interconnecting makes use of copper on the PCB where possible. Otherwise, links of some sort are used. In a number of cases, I drilled a hole through the board and the appropriate copper pad and then pushed a piece of 20B&S TC wire through the hole and made a link between points on the clear side of the board. This makes for a neat assembly.

To complete this assembly, I drilled two large holes so that the board could



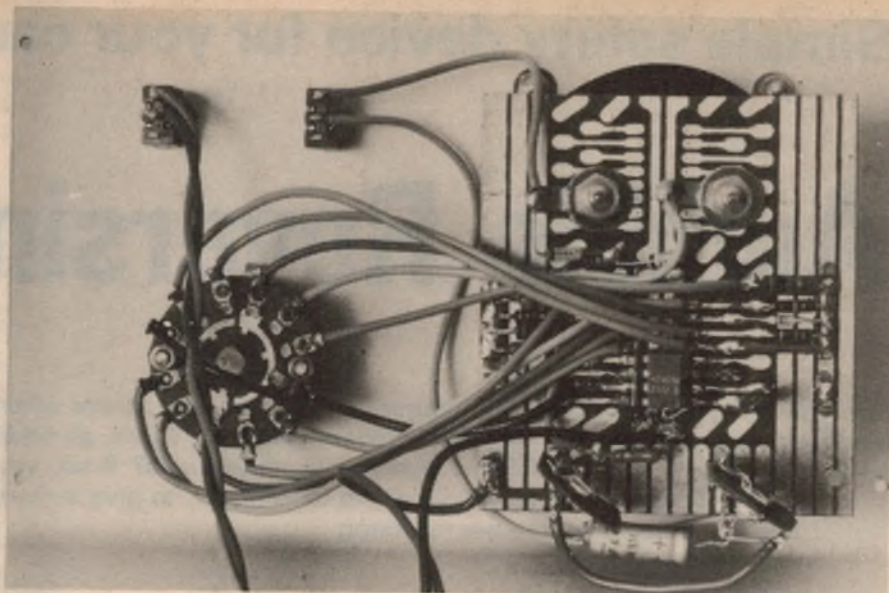*This view shows the simple power supply regulator mounted next to the battery. The necessary components are mounted on a piece of 5-tag strip.*



*Interior view of the prototype. Most of the components were mounted on a piece of general-purpose DIP PCB which, in turn, is bolted to the meter terminals.*

be mounted on the meter terminals. By the way, you may have noticed an extra resistor on the PCB assembly which could not be accounted for. Although I did not mention it earlier, I could not get a 1k trimpot in a hurry and so I settled for one of 470 ohms. The extra resistor is 330 ohms connected in series with the 470 ohm trimpot.

Components for the power supply regulator, consisting of the transistor, zener diode, resistor and capacitor, were mounted on a 5-tag strip, with one mounting tag. This was located at the bottom of the case and adjacent to the battery.

The terminals, switches and meter may now be fixed to the panel and the PCB assembly may also be screwed to the meter. It now only remains to do the interconnecting wiring between the PCB, power supply, switches and terminals to complete the unit. You may have noticed that I have included two negative terminals. These are paralleled and they have been included so that capacitors with short leads may be accommodated readily, just as larger capacitors may be connected across the two outer terminals more conveniently.

If you should elect to operate the instrument from the mains, then it is quite an easy matter to dispense with the battery and substitute the transformer and electrolytic capacitor in its place. There is sufficient room for these components in the case which we used.

Having completed the wiring, it is always a good idea to make a thorough check to make sure that there are no errors or omissions. Satisfied that all is well, you are ready to switch on and calibrate the instrument.

To do the calibration, you need at least one capacitor of known value and close tolerance. Preferably, you should have

five capacitors, such that when paralleled across the Cx terminals, you can check each of the five cardinal points on the meter. The lowest and the highest ranges could best be avoided for calibration, but any of the remaining three could be used.

I calibrated our unit on the middle range with five close tolerance .001uF polystyrene capacitors. These were added across the Cx terminals progressively and each of the relevant points checked and noted for any signs of non-linearity. The 47k trimpot is adjusted to give the most accurate readings across the meter scale.

If you only have one capacitor for calibration purposes, it should preferably be one which gives close to a full scale reading on the meter.

In addition to the basic calibration, we still have to calibrate the x10 multiplier. To do this, the range switch is set to the 0 to 0.5uF range. You will also need a capacitor of known value close to the maximum scale reading of 5uF. The 1k trimpot is set so that the reading on the meter scale corresponds with the value of the calibrating capacitor. The capacitance meter is now ready for use.

In using the capacitance meter, one precaution must always be taken. Before adding a capacitor to the Cx terminals, the range switch should be rotated to the extreme left or 0 to 0.5uF position. If this is not done and a large capacitor is connected to the terminals, the meter will be "slammed", which is a practice which should be avoided as much as possible.

A few minutes with the capacitance meter, with a handful of assorted capacitors, some electrolytics under 5uF, some diodes of various types, transistors, coaxial cable, etc., and you will soon appreciate how useful and versatile this little instrument can be.



## Simple safety device for your car:

# Audible Reversing Alarm

Are you worried about possible dangers to children and others when reversing your car? Do you feel that ordinary reversing lights, as fitted to most cars, are not a sufficient warning to pedestrians? If so, you may consider fitting an extra audible alarm to your car, to give a more noticeable indication that you are reversing.

by DAVID EDWARDS

First and foremost, readers and motorists should realise that when reversing their car, the onus is on them to avoid all collisions and dangerous situations. In particular, when crossing the footpath, pedestrians have right of way. This applies whether the car is reversing or moving forward normally.

As part of the design rules for Australian cars, all new cars must be fitted with visual reversing indicators. These can be either separate white lights, or the amber indicator lights. In either case, they must come on when reverse gear is selected, and the ignition is on.

This requirement has been in force for some time, so that the majority of cars now on the road are fitted with one or other of these warning systems. In general these systems are adequate, and do not require supplementing.

However, situations do exist when some form of additional indication is warranted. Perhaps the most obvious example is that of a car reversing from a garage across the footpath and onto the

street. The possibility exists, especially in daylight, that pedestrians may not see the reversing lights, or hear the car itself.

In these situations, the car driver may not be able to see the pedestrians either, and so there is a chance that the pedestrian may be knocked down and injured. The fact that the driver was not able to see the pedestrian does not absolve him from blame; the law requires that he exercise the necessary care required to prevent such accidents.


One possible solution to this problem is simply to reverse into the garage, rather than out of it. This means that when leaving the garage the driver will have much better vision, and that he has a clear, unobstructed view when reversing into the garage.

In some cases, however, this course of action is not practicable, and the car must be reversed from the garage. In these situations, a majority of pedestrians who realise that the car is about to reverse will yield right of way, even though they are not required to by law. The car driver must still be vigilant, however, as not all pedestrians may see and act upon the normal reversing light indications.

It is in these situations that it can be worthwhile to have an additional indication that the car is reversing. One quick and simple way of doing this is to operate the car horn briefly. This is a universal sound that is usually acted upon promptly by pedestrians.

Blowing the horn does require conscious action from the driver, which may not always be carried out. In addition, car horns tend to produce extremely loud sounds, which may not be appreciated by those in the vicinity. What is really required is a softer sound which will operate automatically.

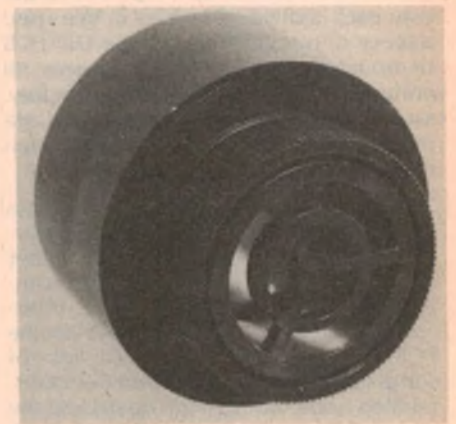This can be done quite simply by wiring a suitable sound source in parallel with the reversing lights. Such a sound source should be cheap, robust and easy to fit. Completely solid state piezoelectric transducers fit this bill completely.




Shown above is the solid state piezoelectric transducer, which forms the basis of the alarm. It can be connected for either pulsed or continuous operation.

A new device of this type has recently come on the market. Distributed in Australia by C & K Electronics (Aust). Pty Ltd, the AudioLarm VL150RM continuous tone/deep unit operates from voltages between 5 and 16VDC. With a supply voltage of 12V, the output sound level averages 92dB. Operating frequency is a nominal 2900Hz.

The unit is sealed into a plastic case, with two tin plated screw type terminals. A third control lead simply emerges from the potting compound at the rear. If this lead is connected to the negative terminal, the unit operates continuously. But if it is connected to the positive terminal, the unit beeps with a duty cycle of about 70%. Current consumption is less than 100mA in both modes.

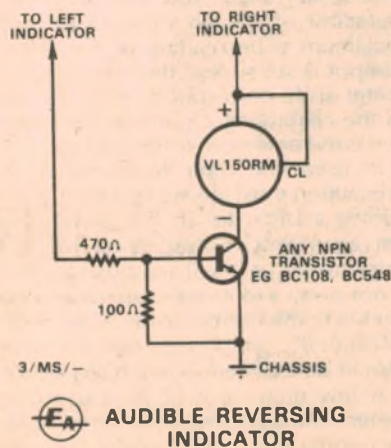The AudioLarm has diode protection against reverse polarity. It will operate over a temperature range of  $-20$  to  $+65$  degrees C. It will continue to operate even when submerged in water (we tried it!), and it cannot be damaged by sharp objects entering the grill. The unit is



Note that this circuit is suitable only for negative earth cars which use the indicator lights as reversing lights. See text for details on other types of cars.



mounted onto a panel from the rear, using a 28mm dia. hole and the supplied retaining rim.

The remaining problem then is simply how to connect the unit into the wiring system of your car. If your car is fitted with separate reversing lights, then all you have to do is find the appropriate wire, and connect the AudioLarm between it and the car chassis, with appropriate polarity. If your car has a negative earth system, connect the negative lead from the unit to the chassis, and the positive and control leads to the wire.

For positive earth cars, simply reverse the leads from the AudioLarm. We should mention that the unit will only operate satisfactorily on 12V cars. With 6V systems, the sound produced is too low in intensity to be of use.

Cars which use the rear indicator lights for the reversing lights pose a slightly harder problem as far as interconnection is concerned. The AudioLarm could be connected across the reversing switch, but this would involve running additional wiring from the front of the car to the rear, where the unit is best mounted. If you feel capable of finding the switch, and sorting out which leads are the correct ones, as well as running the extra wires, go ahead by all means.

However by simply adding a single transistor it is still possible to keep all wiring in the boot area of the car. The circuit, which is shown in the diagram, functions as a simple AND gate. Any small general purpose NPN transistor can be used.

In order for the AudioLarm to be energised, both left and right indicators must be on. If either one is on alone, such as when the direction indicating system is in operation, the unit will not sound. If a disabling switch is required, it should be connected in parallel with the 100 ohm resistor. This will keep the switch contacts wetted, and ensure reliable operation.

If the car is fitted with a hazard warning system, the alarm will operate when this system is used. It will be pulsed on and off in sympathy with the hazard lights. If your car has a positive earth electrical system, use a PNP transistor, and reverse the connections to the alarm unit.

The transistor and associated components can be mounted on a small piece of tagstrip, and placed in any convenient position inside the boot. The alarm unit itself should be mounted in the vicinity of the rear bumper bar, facing downwards so as to minimise the chance of dirt or other foreign materials clogging the grill. Ideally it should be mounted so that it will not be struck by stones flung up by the road wheels, and so that it cannot be easily seen.

So there you are: a simple and easily installed audio alarm system, to supplement the normal reversing light indicators. Using a minimum of parts, it should be very reliable in operation. ☺

## COMPUTER COMPONENTS

<b>MAGNETIC TAPE DRIVES</b> c/w Reed Switch Alpha-Numeric Keyboards—Suitable Microprocessors or Audio Modification—9 Track, 800 bits/inch. \$160.00	<b>POWER SUPPLIES</b> Regulated Input 240V AC Output + 6V (Adj) 50A +12V (Adj) 10A -18V (Adj) 50A. \$250.00
<b>DISC DRIVE UNITS</b> c/w Power Supply—2 Megabit Capacity. \$450.00	<b>DRUM BLOWERS</b> 115V 7.0 A 1550 RPM 1/5HP 10" dia x 4" Drum. Reconditioned—in Housing with Filter. \$45.00
<b>CARD KEY PUNCH &amp; PRINTER</b> —80 Col. Card—New \$400.00	<b>DRUM BLOWERS</b> Rotron 115V 2.A 3100RPM 6" Dia. x 3" Drum. \$20.00
<b>ALPHA-NUMERIC KEYBOARDS</b> —Mechanical. \$10.00	<b>MUFFIN TYPE FANS</b> Large 115/220V 6" Dia. x 3". \$20.00
<b>MOTORS</b> 115/230V 50Hz Reversible 920RPM 1/10 HP approx. \$15.00	<b>FANS</b> —Rotron 8" Dia. Blade 115 1.1A c/w Guard and Cowl. \$10.00
<b>DRUM PRINTER</b> 115V—Single Column. \$25.00	<b>PAPER TAPE READER</b> —Head Assembly. \$45.00
<b>POWER SUPPLIES</b> Input 95-240V AC Output 48V 2A, 10V 1A—c/w Constant Voltage Transformer; 13,000 uF 73VCap. 4 Pole Single Pole, 3 Pole c/o Relay 48VDC 2 Pole Contactor 48V DC. 6 Fuse Holders. \$30.00	<b>PAPER TAPE PUNCH</b> —Head Assembly. \$45.00
	<b>RELAYS</b> —Mercury Wetted High Speed—Octal Base. \$3.50
Smaller items shipped collect by rail to nearest station (please advise) Large items shipped road. freight to be prepaid.	

**FRASER PRODUCTS, 425E PENNANT HILLS RD,  
PENNANT HILLS. PHONE BUS. 02-848 9133.  
AH. 02-639 0432.**

## For fine detail work — a hands free magnifier



The **Magna-Sighter** is a precision 3-D binocular magnifier that leaves your hands completely free for work. It has hundreds of applications, and is invaluable for scientists, technicians, craftsmen, toolmakers, hobbyists, etc. Slips easily over the head—over glasses, too. Proved and used by many U.S. universities, space research bureaux, government departments and major industrial organisations. Available in 3 different magnifications. Price \$21.00

STC 846

## MAGNA-SIGHTER

For further information send this coupon today:

**STOTT TECHNICAL SERVICES** MEA 10.76  
(Division of Stott's  
Technical Correspondence College Pty Ltd.)  
159 Flinders Lane, Melbourne, Vic., 3000

Please send me full information on the 3-D Magna-Sighter. I understand that no Sales Representative will call.

Name.....  
Address.....  
Postcode.....



Save on car service costs with the

# Heathkit CM-1050 engine analyser

One of the most useful instruments that one can have for auto tune-up work is an engine analyser to enable correct adjustment of the carburettor and ignition system, and to check on battery, voltage regulator and alternator condition. This build-it-yourself engine analyser from Heathkit should meet the needs of both garages and Saturday-afternoon mechanics alike.

by GREG SWAIN

With the cost of petrol edging closer to the inevitable \$1 per gallon mark, there is now more incentive than ever to keep the family car in a good state of engine tune. A well tuned engine will not only give better performance, but will also give reduced fuel consumption and save a few of those hard-earned dollars. And if you do your own tune-up work you can save on service costs as well.

There are many Saturday-afternoon mechanics who could take advantage of these potential savings—if only they had the right equipment. If you are one of these people, then this project from the Heath Company should really hit the

spot. It is the Model CM-1050 Engine Analyser which, for an initial outlay of around the \$118 mark, will enable you to maintain your car in a good state of tune, and save on service and fuel costs. It could well pay for itself in a very short time.

A glance at the specifications panel will give some indication of the capabilities of this versatile test instrument. Basically, the instrument is supplied as a kit of parts, complete to the last nut and bolt, and intended for assembly in the home using a minimum of tools. The aim is that the purchaser derive a deal of satisfaction from building up the kit, and on com-

pletion be rewarded with a useful piece of test gear.

Facilities offered on the Model CM-1050 Engine Analyser include provision for measuring voltage, current, resistance, engine speed (rpm), dwell and spark (voltage comparison between plugs). The unit is supplied complete with test cables which are clipped to various points in the wiring, but most frequently to the distributor terminals.

There is provision also to measure the voltage across the closed stationary points. This voltage is interpreted as points resistance, and read off the meter scale as "good" or "bad". In addition, the unit may be used to substitute a capacitor (condenser in automotive terms) in place of the existing capacitor in the distributor to check on its condition, and to check alternator condition.

Voltage measurements are performed on one of three ranges calibrated 0-3.2V, 0-16V, and 0-32V. A special "battery adapter" consisting of a large 0.25 ohm 50W resistor and a shorting strap, enables charging voltage to be measured. The 0.25 ohm resistor is placed in series with the battery to isolate the battery from the regulator.

Current measurements call for the use of a special current shunt which, when connected in series with any circuit, allows current measurements as high as 90 amps to be made. Charging current may be measured by using the shunt in conjunction with the battery adapter.

All measurements are read off a large, easy-to-read 11cm x 15cm meter movement.

Perhaps the most useful measuring facilities on the Model CM-1050 engine analyser are the tachometer and dwell ranges, at least as far as everyday tune-up work is concerned. A tachometer of known accuracy is essential for adjusting the idling speed. This is particularly the case for cars with automatic transmission.

For example, the idling speed of a typical 6-cylinder car with automatic transmission is generally somewhere in the vicinity of 600 rpm with the transmission in drive. If the idling speed is too



A comprehensive range of measuring facilities makes the CM-1050 Engine Analyser an invaluable service tool for engine tune-ups and fault finding.



high, the car will tend to creep more than normal, and if it is too low the engine will run roughly, have a tendency to stall, and have higher than usual bearing wear.

Note that modern cars tend to have higher engine idling speeds than earlier models, this because engine idle mixture is leaned off (and the adjustment sealed) to meet anti-pollution requirements. Whatever model car you own, it is important that all engine adjustments and settings be made according to the manufacturers' specifications. Invest in a workshop manual if you don't have one.

Ignition timing adjustments also require the use of a tachometer. For example, the initial ignition timing advance on 1971-1973 Holden HQ 6-cylinder models is 5 degrees BTDC (before top dead centre) at 480 to 520 rpm. This engine speed is obtained with the vacuum line to the distributor diaphragm disconnected and plugged.

So a tachometer is a very useful aid to the home mechanic. The instrument described here actually has two tach ranges, one calibrated 0-1200 rpm and the other 0-6000 rpm. The lower range is used for idling speed adjustment, while the higher range may be used if you have occasion to test the engine speed under road conditions or calibrate a permanently installed tachometer.

Although the high range is marked 0-6000 rpm, this should not be taken as a licence to run any engine up to 6000 rpm while in neutral. In fact this is quite likely to put a piston through the head, and that is a very expensive repair job indeed.

It is also necessary to adjust the dwell before making ignition timing adjustments. Dwell is the number of degrees the distributor cam rotates while the ignition points are closed. This measurement, also called "cam angle", affects timing. (Note, however, that timing does not affect the dwell.)

Before carrying out timing adjustments, therefore, the dwell angle should be set to the manufacturer's specified figure. For Holden 6-cylinder engines, this is given as 30-35 degrees. If the measured dwell is less than the specified figure, the point gap is too wide and must be decreased. On the other hand, if the measured dwell is too high, the gap is too narrow and must be increased.

There is another reason why proper dwell adjustment is important.

In the ignition system, the spark for ignition is generated when the distributor points, which are in the coil primary circuit, are opened and the magnetic field in the coil collapses. This collapse is very rapid and causes a high induced voltage in the secondary of the coil, firing the plug.

To prepare for the next spark, the distributor points must close and let the magnetic field build up again in the coil. This build-up of the magnetic field is not

instantaneous, and if the distributor points do not remain closed for long enough it will not have time to build up to its maximum level. The result will be a low secondary voltage and a weak spark.

This phenomenon is particularly noticeable at high speed, and can cause misfiring. It can also make the engine harder to start, particularly in cold weather. For these reasons, it is necessary to allow the points to remain closed for as long as possible, and the manufacturer's recommendations should be followed when making adjustments.

A change in dwell angle reading or a wavering of the meter pointer can mean one or a combination of several faults. A fluttering pointer at high engine speeds

Fig. 1 shows a simplified schematic of the dwell circuit. When SW1 is in the dwell position, transistor Q1 acts as a switch to supply operating voltage to transistors Q2 and Q3. Transistor Q1, in turn, is controlled by diode D1.

When a voltage greater than 4.5V is present at the positive input, or the positive input is disconnected, diode D1 is reversed biased and no current can flow through resistors R18 and R19. This means that transistor Q1 is turned off, and no voltage is applied to Q2 and Q3.

However, if the inputs are shorted together, as when the ignition points close, current flows through R19, D1 and R18. This turns Q1 on and the internal battery voltage is applied to Q2 and Q3.

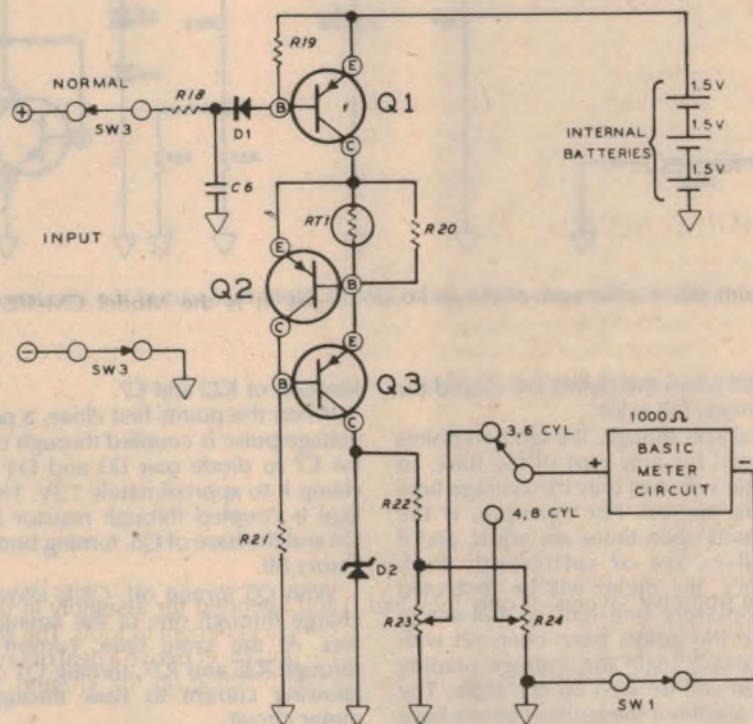


Fig. 1: simplified schematic of the dwell measuring circuit.

can indicate points bounce. Increased tension on the moveable-point spring can correct this fault. If the meter pointer wavers, the distributor cam shaft could be wobbling due to worn bearings, or the cam could be worn.

The circuit details of the tacho and dwell ranges are described in some detail below. Other ranges, including voltage, current and resistance measurements, function in a manner similar to a conventional multimeter and are not detailed.

The main exception here is the capacitor test facility. As indicated previously, for this test the engine analyser simply switches a substitute capacitor in place of the existing capacitor in the distributor. Circuit details are given in the construction manual. The other exception is the spark test circuit, which is also detailed in the manual.

Capacitor C6 and resistor R18 remove large voltage spikes that occur when the ignition points open.

Resistors R20 and R21 provide bias voltage for Q2 and Q3. Q3 is a constant current source with voltage reference provided by the combined base-emitter drops of Q2 and Q3. The current from Q3 flows through zener diode D2, causing the zener reference voltage to be applied to the resistor network made up of R22, R23, and R24. Thermistor RT1 is used to compensate the circuit for temperature variations.

Voltage is applied through either R23 or R24 by SW2 to the basic meter circuit. With the inputs shorted together, R23 is adjusted for a full-scale meter reading of 60. R24 is adjusted for a "full-scale" meter reading of 45. Thus, when the ignition points are open, the meter reads







## Engine Analyser

the do-it-yourself enthusiast, that is as a kit of parts.

To summarise, the kit is presented with typical Heathkit thoroughness, carefully packaged, and accompanied by the customary detailed assembly manual. As with the exhaust analyser described last month it went together with few problems, worked right from switch-on, and was rugged and attractive in finished form.

From a physical standpoint, the unit is constructed in a simple U-shaped chassis with a blue marvplate cover. Most of the electronics is contained on a single PCB which is mounted vertically inside the chassis and held in place by the switches and the meter terminals.

The most involved part of the job has to do with the switch wiring. However, this is carefully detailed in the assembly manual, and is greatly simplified by the use of a factory-prepared wiring loom.

The one hassle encountered concerned the tachometer calibration procedure. This procedure calls for a 50/60Hz input from the mains, and a calibration cable with a two-pin plug is supplied for this purpose. A 10k 1W resistor in series with one of the leads completes the cable.


The problem is that the procedure assumes a mains voltage of 120VAC, and no provision is made for other voltages. There is a simple solution to the problem though—just solder a second 10k 1W resistor in series with the first and plug into the 240VAC 50Hz mains. The RPM CAL control is then adjusted so that the meter reads 1000 rpm.

Although an American style two-pin mains plug is supplied as part of the calibration cable, it isn't really necessary that you replace it with an Australian-approved 3-pin type. It takes only a few seconds work to carry out the calibration procedure, after which the calibration cable is no longer used (except perhaps for occasional checks on tach accuracy).

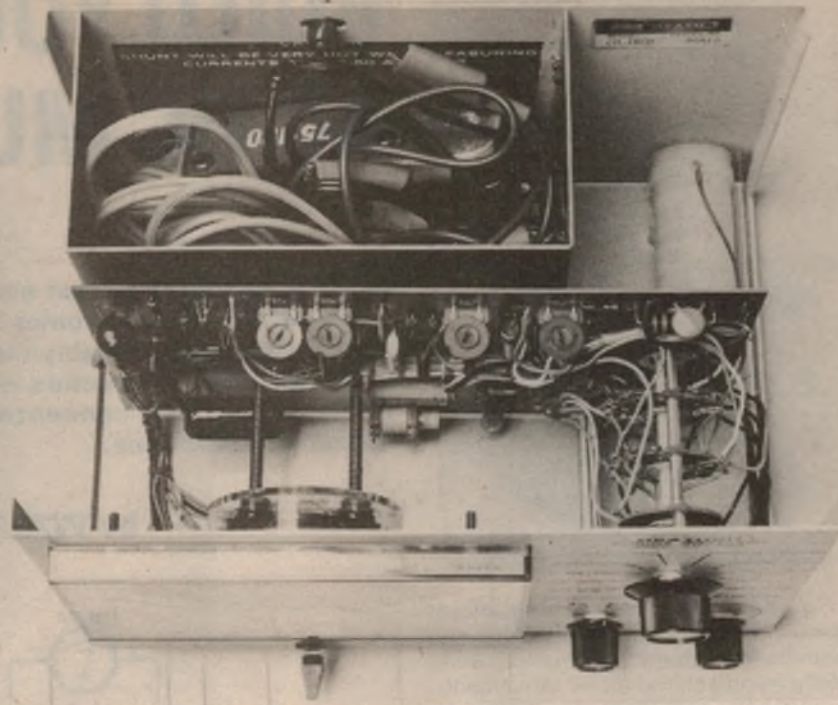Exercise extreme caution when carrying out the calibration procedure to ensure personal safety. If you feel at all unsure of yourself, wind some insulation tape around the connections between the test leads and the calibration cable.

Operation of the completed instrument is described in a comprehensive handbook accompanying the kit. The procedure for obtaining each of the various measurements of which the instrument is capable is described in some detail, and the various electrical connections shown in pictorial form.

For those unlucky enough not to get the instrument going first try, the assembly manual contains a detailed section on troubleshooting procedures. In the event of further difficulties, advantage may be



## SPECIFICATIONS

### ELECTRICAL

Voltmeter .....	Three ranges: 0-3.2 volts DC, $\pm 3\%$ of full scale. 0-16 volts DC, $\pm 3\%$ of full scale. 0-32 volts DC, $\pm 3\%$ of full scale.
Ohmmeter .....	Two ranges: R x 1 (100 ohm centre scale) $\pm 3^\circ$ arc. R x 100 (10k ohm centre scale), $\pm 3^\circ$ arc.
Tachometer .....	Two ranges: 0-1200 rpm, $\pm 3\%$ of full scale. 0-6000 rpm, $\pm 3\%$ of full scale.
Dwell Meter* .....	Two ranges: 0-45° (on 0-60° scale), $\pm 3\%$ of full scale. 0-60, $\pm 3\%$ of full scale.
Amperes .....	-5 to +90 amperes DC, $\pm 3\%$ of full scale.
Spark Output .....	0-50
Point Resistance .....	Good/Bad.
Alternator .....	Good/Bad.
Condenser .....	0.22 $\mu$ F, 10%.

### GENERAL

Cables Supplied .....	Two 2.4m two-conductor test cables. One 60 cm alligator lead. One 60 cm alligator to push-on connector.
Accessories Supplied .....	90-ampere shunt. 0.25 ohm resistor assembly.
Batteries Required .....	Three 1.5V C-cells.
Battery Life .....	100 hours average.
Dimensions (overall approx.)	27 cm wide x 19 cm high x 22 cm deep.

taken of the full technical back-up and factory repair service offered by the company.

The Heath Company is represented in Australia by Warburton Franki Pty Ltd, who have branch offices in all state capitals and in Wellington NZ. Readers

should either write to The Heath Centre, 220 Park St, South Melbourne, Vic 3205, or ring one of the following numbers: Sydney 648 1711, Melbourne 699 4999, Brisbane 52 7255, Adelaide 356 7333, Perth 65 7000, Hobart 23 1841, Wellington (NZ) 69 8272.



# BUILD YOUR OWN AC-DC MULTIMETER



While a vast array of test equipment is currently being sold—and used—within the electronics industry, the ordinary multimeter still holds its place as probably the most useful single item. This article discusses the construction of a typical bench multimeter from a do-it-yourself kit, concentrating particularly on how such an instrument functions.

by WALTER NEVILLE

Up till a few years ago, a significant proportion of the multimeters in use in Australia were home constructed, using locally manufactured meter movements, components and hardware. More recently, however, there has been an influx of multimeters, mainly from Asian countries, of such a quality and at such a price level that locally assembled instruments have not been able to compete.

That position still holds and is not likely to change in the foreseeable future, so that anyone who aspires to build up their own multimeter may as well forget the idea or else settle for a wholly imported kit, which can be expected to be price competitive.

But why build your own multimeter when a complete, commercial instrument can be bought for a comparable figure? The answer simply is that plenty of enthusiasts like to build things, partly for the satisfaction of doing so, and partly because the practical experience reinforces their appreciation of how the various gadgets actually work.

The multimeter pictured in this article was put together by the writer from an imported multitester kit branded as "Archerkit" No 28-4013 and sold by Tandy Electronics stores throughout Australia. The advertised price is \$19.95 and compares with a figure of \$24.95 for the same instrument fully built-up. Since the kit contains a detailed how-to-build-it brochure, the emphasis of our remarks here will be on how a multimeter works.

A "multimeter" or "multitester" normally contains a single moving coil or "D'Arsonval" meter movement with associated circuitry and calibration which allows it to read voltage, current and resistance appropriate to the needs of anyone involved in electronics—from engineer to enthusiast. This being the case, such instruments are sometimes referred to as "volt-ohm-milliammeters", or "VOMs".

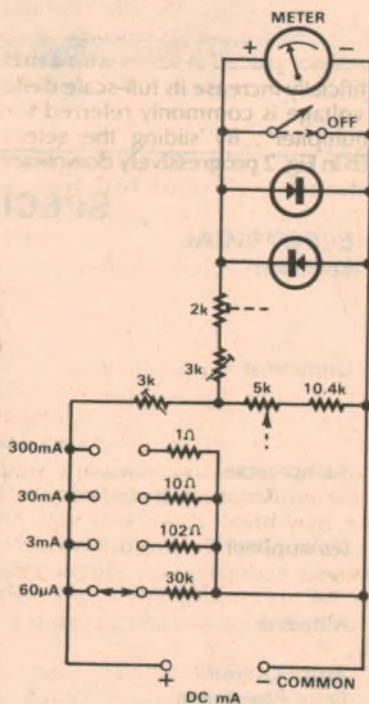


Fig. 1: Illustrating the circuitry in use when the instrument is set to measure direct current in milliamps.

The Archerkit 28-4013 is fairly typical in that it measures volts up to 1200DC and 1200AC, current up to 300 milliamperes and resistance up to about 2 megohms. It has an "off" switch position to minimise the effects of vibration while the meter is being carried and electrical protection to reduce the hazards of accidental overload.

To illustrate what is involved in this particular (and fairly typical) multitester, we have separated out the various functions, beginning with Fig. 1, which shows that part of the circuitry which is involved in the measurement of current. Some of the components shown have more to do

with the other functions but, inasmuch as they are in circuit at all times, they have been shown with their values as marked in the manufacturer's main circuit diagram.

The basic meter movement is marked 2k 0-37, which can be taken to mean that it has an internal coil resistance of 2000 ohms and a sensitivity such that the pointer would traverse the full scale with a current through the meter of 37 microamps DC.

When the main selector switch on the front of the multitester is in the "off" position, it places a short-circuit directly across the meter, as indicated in Fig. 1. Thus shorted, the meter is electrically damped and there is much less tendency for the pointer to sway to and fro as the meter is carried about. As a precaution, users should develop the habit of switching the meter to "off" when not in use.

It will also be noted that the meter is shunted by a pair of silicon diodes connected in opposite polarity. In normal circumstances, these do not conduct, since the voltage across the meter, even at full scale, is not more than 74µV (ie, 37µA through 2000 ohms)—this being well below the turn-on voltage of the diodes. However, if the current through the meter should accidentally be increased, the voltage across it will increase and, at a certain point, one or other of the diodes will turn on, thereby absorbing some of the excess current. This diode protection scheme will not stop a meter pointer from being slammed over hard by accidental overload, but it can often prevent irreversible damage to the mechanism or an actual burn-out of the very fine wire comprising the moving coil.

If the external "+" and "-" tip jacks and leads were run directly and only to the meter movement, it would be possible to have the meter measure currents up to a full-scale figure of 37 microamps.



In fact, the network of resistors in parallel and series with the meter movement reduces its sensitivity so that, with the side switch in the bottom position as drawn, the effective sensitivity is 60 microamps full scale—with 37uA flowing through the meter and 23uA through the resistive network.

There are at least two reasons for arranging things this way. One is convenience, in that part of the resistive network can be made adjustable (in this case the upper 3k resistor) so that the sensitivity can be adjusted precisely to 60uA, taking account of slight differences in the meter movement. This is one of the preset adjustments in the particular kit.

The second reason is that, by choosing a figure like 60, the meter scale can be divided up logically into segments of conveniently related whole numbers: 3, 6, 12, 15, etc, thus simplifying the job of laying out and interpreting the scales on the meter face.

When the slider is moved up one position, from "60uA" to "3mA", most of the current flows directly between the external "+" and "-" connections through the 102 ohms resistor. But why an odd value like 102 ohms? The answer simply is that,

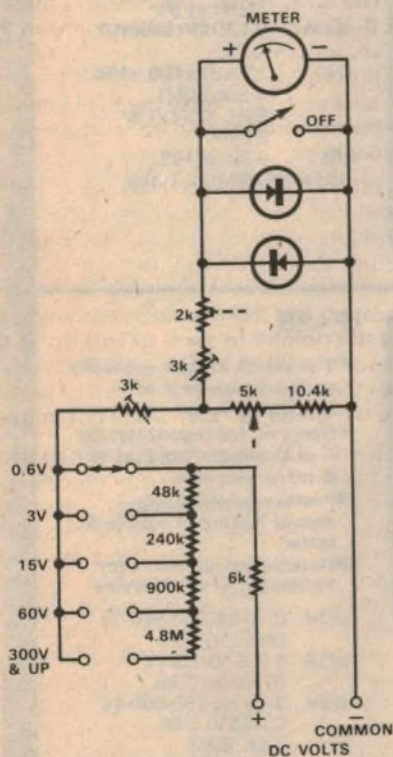


Fig. 2: To measure volts, "multiplier" resistors are introduced in series with the meter.

with this particular value shunted across the meter circuit, the current divides proportionately with, say, 37uA flowing through the meter and 2.963mA through the 102 ohm "shunt" resistor. Since this relationship is fixed while ever the instrument is set to this position, the meter face can be marked and read just as if the movement was, in fact, reacting

to current from 0 to 3 milliamps full scale.

By using lower value shunts (10 ohms and 1 ohm) a greater proportion of the current to be measured passes through these shunts allowing the meter to be calibrated and read as if it were indicating 0 to 30mA full scale, and 0 to 300mA full scale. Other multimeters may use different ranges or more ranges but the principle remains the same.

Fig. 2 shows the configuration of the circuit when the multimeter is switched to measure DC volts. With the slider in the topmost position, as drawn, a 6k fixed resistor and a 3k adjustable is introduced between the external "+" terminal and the rest of the metering circuit. Why these values? Because, with 0.6V applied between the external "+" and "-" test connections, the current through the meter can be adjusted so that it will read exactly full scale. In other words, a meter which as we saw would deflect fully with about 74uV across its terminals is made to behave as though it needed 0.6V for full deflection.

A resistor placed in series with a meter to artificially increase its full-scale deflection voltage is commonly referred to as a "multiplier". By sliding the selector switch in Fig. 2 progressively downwards, additional multiplier resistors are brought into circuit (48k, 240k &c) allowing the meter to function as a voltmeter reading 0-3V, 0-15V, 0-60V, &c.

Note that the final position shows "300V & Up". On the actual multimeter, it is possible to measure 600V and 1200V—but not by further rotating the switch. Instead, the switch is left at the "300V & Up" position and the external lead plugged into other appropriately marked tip jacks. The reason is simply that the insulation of an ordinary rotary switch may break down with very high voltages applied. To avoid this risk, the additional multipliers are simply strung from the extra test points to the switch so that it is never stressed by more than 300V.

As a point of interest, if one looks at the 300V range, the amount of multiplier resistance in circuit is approaching 6,000,000 ohms. If one divides this figure by 300 the result is 20,000. From this comes the maker's specification of the instrument as 20,000 ohms/volt DC indicating the amount of loading which the meter imposes, as a voltmeter, upon the circuit under test. The above figure and the further specification of 10,000 ohms/volt AC are average and typical, these days, although some multimeters have an even higher specification. Old fashioned multimeters, with an internal resistance of 1000 ohms/volt or lower are no longer favoured because they load circuits under test unnecessarily.

To measure AC volts, special provision has to be made, because an ordinary moving coil meter movement will respond only to DC through the coil. The standard approach is to pass the alterna-

ting current entering the metering circuit through a rectifier system, which changes it into DC, to operate the meter. By careful choice of circuitry and components, the pointer deflection caused by the resultant DC can be read off in terms of the AC voltage applied to the external test points.

Thus, an AC voltage applied to the external terminals of Fig. 3 will cause a

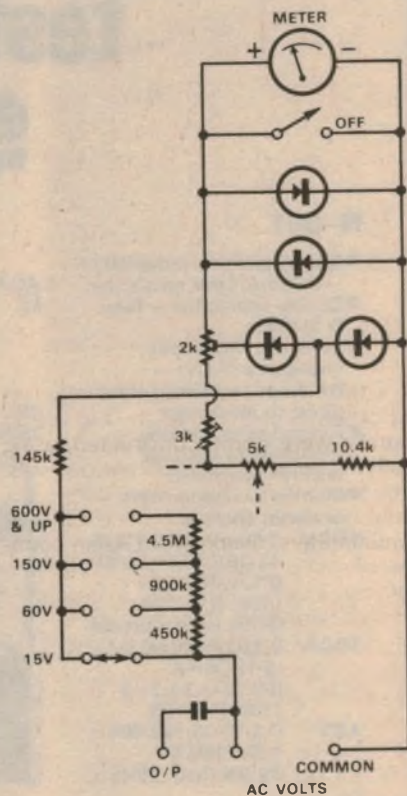


Fig. 3: To measure AC volts, rectifiers are necessary in addition to multipliers.

current to flow through one or more multiplier resistors to the junction point of two diodes. Here the current is rectified and fed as DC to the meter terminals via a 2k adjustable potentiometer. With the values and switch setting shown in Fig. 2, 15V AC rms applied to the external terminals can cause the meter to deflect to full scale. In short, it can be calibrated and read as a 0-15V AC voltmeter.

By introducing additional resistors (450k, 900k, 4.5M) the meter can be made to read 0-60V AC, 0-150V AC, 0-600V AC, and 0-1200V AC using an additional tip jack.

As a normal extension of the AC voltage function, most multimeters include an extra tip jack connection marked "Output" or "O/P". This is tied to the active AC terminal by a series capacitor, which will have the capability of blocking any DC voltage, while passing AC voltage to the metering circuit. The test leads may thus be connected to the plate of an output valve, or the collector or emitter of a transistor stage and will respond only to the amplitude of any AC signal present, ignoring the DC supply voltage.

One other special point is worthy of



# Your next electronic circuit tester should be a Sanwa

## N-501

- 2 $\mu$ A suspension movement – 0.05mA/1mV resolution
  - Double protection – fuse & Si diode
  - Constant 1M $\Omega$  input impedance (ACV) – RF-diode rectified current direct to movement
  - Revised scale marking – intermediate readings readily determined
  - Multifarious application – as circuit analyser
- $\pm$ DCV 0-60mV 0-0.3-1.2-3-12-30V (500k $\Omega$ /V)  
 0-120-300-1.2k (50k $\Omega$ /V)  $\pm$ 2%  
 0-30k (w/HV probe)  
 $\pm$ DCA 0-2 $\mu$ S 0-0.03-0.3-1.2-3-12-30mA  
 0-0.12-0.3-1.2-12 (300mV)  $\pm$ 2%  
 ACV 0-3-12-30-120-300-1.2k (1M $\Omega$ )  
 $\pm$ 2.5% Freq. 20Hz

to 50kHz ( $\pm$ 1dB)  
 0-1.2-12A  
 x1 x10 x100 x1k  
 x10k x100k (max. 200M)  
 Batt. 1.5Vx1 & 9Vx1  
 -20 to +63  
 252x191x107mm 1.95kg



## 460-ED

- 10 $\mu$ A movement – 100k $\Omega$ /V, varistor protected
- Polarity reversal switch – negative measurements
- Equalizing transformer – common shunts & jacks for 1.2A & 12A DC/AC
- Detachable indicator block – easy maintenance

- Accurate DC reading – no HF current interference
- $\pm$ DCV 0-0.3-3-12-30-120-300 (100k $\Omega$ )  
 1.2k (16.6k $\Omega$ /V)  $\pm$ 2% 30k (w/HV probe)  
 $\pm$ DCA 0-12 $\mu$ A 0-0.3-3-30-300mA 0-1.2-12A (300mV)  $\pm$ 2%  
 ACV 0-3-12-30-120-300-1.2k (5k $\Omega$ /V)  $\pm$ 3% Freq. 20Hz to 1MHz at 3V  
 ACA 0-1.2-12 (300mV)  $\pm$ 3%  
 $\Omega$  x1 x10 x100 x10k (max. 50M) Batt. 1.5Vx1 & 9Vx1  
 dB -20 to +63  
 184x134x88mm 1.3kg



## U-60D


- Measurement ranges available.
- DCV 0.1 0.5 2.5 10 50 250 1000 (20k $\Omega$ /V) (25kV w/HV probe extra)  
 ACV 2.5 10 50 250 1000 (8k $\Omega$ /V)  
 DCmA 0.05 2.5 50 500 (500mV drop; 100mV for 0.05mA)  
 $\Omega$  Range – X1 X10 X100 X1k  
 Midscale –50 $\Omega$  500 $\Omega$  5k $\Omega$  50k $\Omega$   
 Maximum – 5k $\Omega$  50k $\Omega$  500k $\Omega$  5M $\Omega$   
 Batteries 1.5V dry cell (UM-3 or equivalent) X2  
 LI 0.06mA 0.6mA  
 LV 3V 3V




LI 6mA 60mA  
 LV 3V 3V  
 ● Allowance.  
 Within  $\pm$ 3% f.s.d. for DCV & DCmA  
 Within  $\pm$ 4% f.s.d. ( $\pm$ 6% for 2.5V) for ACV  
 Within  $\pm$ 3% of scale length for  $\Omega$   
 ● Size & weight.  
 133X92X42 mm & 300 gr
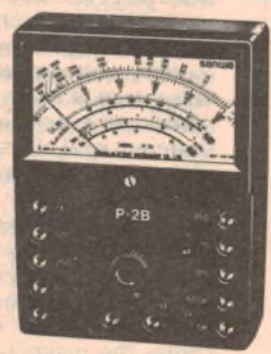
## P-2B

- The sturdy midget – quality quality instrument of functional design
  - Designed for rugged service – phenol-resin front panel & metal rear case
  - Positive range setting – special feature of a pinjack tester
  - Reserve instrument – for household or field service
- DCV 0-10-50-250-500-1k (2k $\Omega$ /V)  $\pm$ 3%  
 DCA 0-0.5-10-250m (670mV)  $\pm$ 3%  
 ACV 0-10-50-250-500-1k (2k $\Omega$ /V)  $\pm$ 4%  
 $\Omega$  0-5k 500k Batt. 1.5Vx1  
 dB -20 to +36  
 M $\Omega$  0.1–50 ) using  
 $\mu$ F 0.0002–0.6 ) external power  
 120x88x40mm 325gr



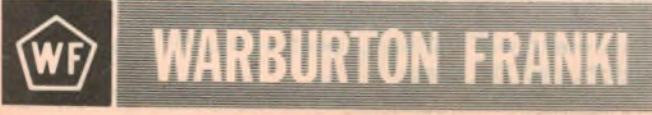**W.F.**  
 75 years of service  
 to Australian industry.



- ADELAIDE 356-7333 ● BRISBANE 52-7255 ● HOBART 23-1841
- MELBOURNE 699-4999 ● PERTH 65-7000 ● SYDNEY 648-1711
- WELLINGTON N.Z. 698-272



## MULTIMETER-continued

mention in regard to the AC voltage scales. Typical rectifiers are not precisely linear, in that the DC out is not exactly proportional to the AC in. It is therefore not unusual to find a scale for the AC voltage ranges separate from that for the DC ranges. Sometimes a special scale is provided only for one or two of the lower voltage AC ranges, common practice being to use red printing to distinguish them. The important point is to be aware of the possibility and to make sure to read the scale intended by the manufacturer.

Fig. 4 shows the configuration of the metering circuit when switched to measure the resistance in ohms of any circuit or component introduced between the test points. In this case, a single 1.5V cell is introduced between the active external connection and the rest of the metering circuitry.

As the circuit stands, with no electrical connection between the two external

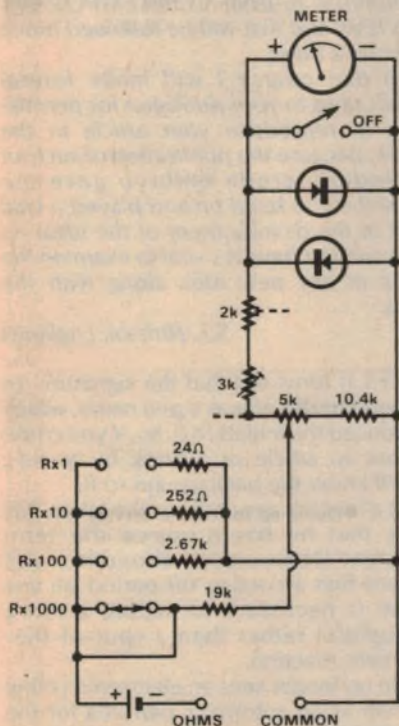


Fig. 4: For resistance measurement, the circuit is different again, involving a battery.

test points, no current flows through the meter and the pointer remains in its at rest position. In terms of the ohms scale, it can be said to be indicating "open circuit".

Conversely, if a direct short is placed between the two external test points "common" and "ohms", current will flow through the 19k resistor into the network associated with the meter, thence through the meter itself, causing the pointer to deflect. The purpose of choosing the values shown is to make it possible, by adjusting the 5k potentiometer,

to make the pointer read exactly full scale. Thus, full scale deflection signifies a short circuit between the test points. If different values of resistance are now introduced between the test points—i.e., something between open-circuit and short-circuit—the pointer will take up some intermediate position. By suitable calibration, the resistance can be read straight off the ohms scale.

Because the voltage delivered by a typical cell is likely to vary somewhat during its useful life, it is normal to make the "Ohms Adjust" potentiometer accessible on the panel of multimeter. Each time the ohms scale is used, the test prods should be touched together and the potentiometer reset, if necessary, to bring the short-circuit condition to exact full scale.

A problem of virtually all multimeter ohms ranges is that the highest and the lowest values are rather difficult to read accurately to any one scale. It is common practice, therefore, to introduce additional resistors, as shown in Fig. 4, which serve to increase the current through—and the voltage drop across—lower values of resistor under test. By carefully choosing the values involved it is possible to modify the resistance calibration by factors of 10 so that a greater range of values can be read within the more meaningful centre portion of the resistance calibration.

While the use of shunts can extend the usefulness of the ohms ranges downwards into lower values—important with transistor circuitry—values under test above about 0.5 megohm cause only a very tiny deflection on even the most sensitive scale and therefore cannot be read at all accurately.

Some multimeters gain a small advantage by using a somewhat higher internal supply voltage to start with but the advantage is quite limited. For accurate measurement of high resistance values a different kind of instrument is desirable.

So, there you have it—the workings of a traditional (yet up-to-date) multimeter. If it merely clarifies the type of instrument for you for the first time, the article will have served a purpose. If it motivates you to study, to understand and to build one for yourself, so much the better.

# OPTRO

## OPTRO PTY. LTD.

17 Arawatta Street,  
Carnegie, Melbourne.  
Victoria, 3163, Australia  
Tel. 569 0978, 569 0979

ADELAIDE:

35 Halifax Street, Adelaide  
Tel. 08 212 2217

Agents For

### AMPEX TAPES

Professional quality  
Audio cassette  
Reel to reel  
Full range

### JBL SPEAKERS

Superb quality  
Range for professional  
and domestic use

**COME IN AND HEAR  
THE WHOLE RANGE  
FOR YOURSELF**

Phone or Mail  
Orders Welcome


## AEGIS PTY. LTD.

347 Darebin Rd, Thornbury.  
Vic. 3071. Phone 49-1017

Manufacturers of Wound Components for Electronic Applications

- ★ Miniature Aerial, RF, Oscillator Coils and IF Transformers for Transistor Receivers
- ★ Replacement Coils and IF Transformers for Valve Receivers
- ★ Radio Frequency Chokes and Video Peaking Chokes
- ★ Ceramic Insulators
- ★ Coil Formers, Bobbins, Cans, Cores, etc.
- ★ Interference Suppression Units:
  - Aerial Filters
  - Mains Filters
- ★ Crossover Network Inductances
- ★ Wide Range of Instrument Knobs

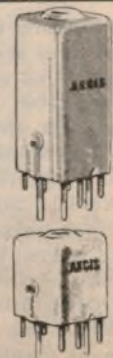Stocked by all leading electronics suppliers







# Forum

Conducted by Neville Williams

## A further look at "Instant Democracy".

Those who have been regular readers of these columns may recall discussion, in February 1975, under the heading "Out with the ballot boxes. In with what?". After some debate in subsequent issues, the subject dropped out of sight — until just recently, when we had a letter of acknowledgement and thanks from the original correspondent.

What started it all was a letter from a reader M.F., then resident at Glenroy, Victoria, who lamented that conventional procedures for conducting elections, referenda and opinion polls were hopelessly inefficient and protracted when viewed against what would now be possible using modern technology. He felt that they could be up-dated to advantage, but nobody seemed interested in publishing his ideas.

Briefly, he proposed setting up booths throughout the nation in which members of the public could register votes or opinions by electronic means. The resulting data would be validated, classified and summed in centralised computer installations. People eligible to vote would use an individual voting card with a magnetically recorded number but the centralised equipment, while reacting to both identification and vote, would not correlate the two, so that secrecy could be preserved.

Because it would be possible to obtain a very short-term public reaction to questions of major importance, a union ballot on an impending strike, shareholders' opinion on company policy, etc., the system might conceivably be called "E.I.D.", short for Electronic Instant Democracy. Rather more conservatively, it might be dubbed "E.V.C." for Electronic Vote Collecting.

Commenting on this proposal, which was put to us at considerable length, we suggested that one reason why he had not been able to secure coverage in newspapers and magazines was his excessive enthusiasm for the proposition and his virtual dismissal of obvious and very practical problems: keeping cards, rather than rolls up to date; the liability of cards to loss, falsification and duplication; the possibility of "rigging" a computer program; the chance of the computer being made to print out the identity of people voting in a particular


way; the strong chance that many groups would not accept individual secret voting.

But, in addition, we suggested that snap polls would not necessarily be in the public interest because what M.F. fondly referred to as "Instant Democracy" might be described more appropriately as "spur-of-the-moment democracy". There could well be merit in the existing voting system which, by its very nature, gives people time to think, and to consider long-term as well as short-term effects.

Events in Australia since that was written have emphasised just how vulnerable all Governments are in mid term when they are involved in an unpopular strategy intended (allegedly, anyway) to produce a result which will be seen, in longer term, to produce a commendable end result.

In short, a voting or opinion system which is too easily invoked could militate against long term planning.

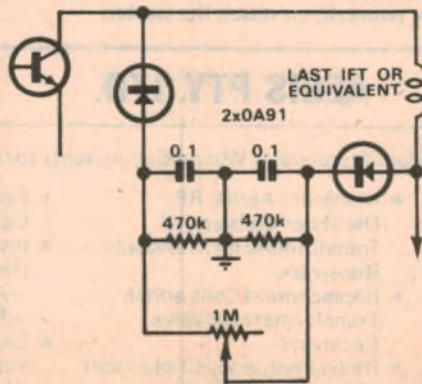The discussion prompted a good deal of personal comment and one letter, which we published in the June issue,



Suggested by Ian Pogson in the March 1976 issue, this simple noise limiting circuit may be of some assistance in remote areas.

sought to "take us apart" for being negative and critical — despite the fact that we were the one magazine which had published M.F.'s proposals. And also despite the fact that we commended the correspondent for his statement of a problem, and his desire to be constructive, ending with the suggestion "back to the drawing board".

As it transpired, M.F., who is now resident in England, followed our advice, as the following excerpt will show:

Dear Mr Williams:

Thank you very much for giving so much space to my idea in EA 2/75: Since then I've been following the reaction with much interest and your readers may be interested in the latest developments.

I have indeed gone "back to the drawing board" and have come up with an updated system that takes account of your criticisms and is much more practical. Indeed, the privately-circulated updated version has aroused enough interest in certain quarters in Britain to secure its publication later this year in the influential journal CONTEMPORARY REVIEW, and that will be followed much later by a book.

In due course I will make formal application to your publisher for permission to reproduce your article in the book, because the publication of such an incredibly crude embryo gave me something to build on and played a vital part in the development of the idea. As you said last June, it's vital to examine the cons of any new idea along with the pros.

S.F. (Bristol, England)

S.F.? It turns out that the signature on the original letter was a pen name, which produced the initials M.F. So, if you come across an article or a book by an S.F., you'll know the background to it.

In a lengthy appendix to the letter, S.F. says that he has dropped the term "Instant Democracy" altogether and agrees that a cooling off period on any issue is necessary to secure a more thoughtful rather than a spur-of-the-moment reaction.

He no longer sees an electronic voting system as an automatic panacea for the community's ills, but he says that living in Britain has convinced him more than ever that the community needs a more effective voice in all levels of Government. With one Parliament for 55 million people, "the legislative process has the reactions of a dinosaur when it needs the reactions of a shrew".

Having looked at the matters of accuracy, "rigging" and security, S.F. is convinced that they would not present a problem provided scrutineers were chosen for their understanding of the technology, rather than for their present ability to count pieces of paper. A record of votes cast could be kept by equipping each booth with a paper tape and punching mechanism.



Technology shock . . . the problem of people faced for the first time with buttons instead of voting slips? People are becoming daily more accustomed to electronic presentations, as witness the current developments in Britain where all kinds of print-out information may soon appear on individual television screens by pushing a button on the "Viewdata" attachment.

And cost? Would it be any more than 100 miles or more of new expressway?

S.F. has a lot more to say, complete with quotes, all aimed at establishing the idea that his idea is not merely for a more efficient method of: "electronic vote collecting". It's for a system which will give the "silent majority" a new initiative in influencing the governmental "dinosaur".

In fact, S.F. seems quite sold on this word "initiative" and I tip that it will figure large in his future writings.

To change the subject completely, I would like to refer to a letter from a reader who must surely qualify as an inhabitant of that area described by such Australianisms as "back o' beyond" or "out past the black stump". While this may not be strictly true of Cobar in regard to everyday comforts, it would certainly seem to apply as far as radio reception is concerned.

Dear Sir,

The area in which I live is serviced by a sole ABC relay station located some 70 miles away (2BY, Byrock). While one learns to live with "Blue Hills", etc, one often yearns to hear sounds from the "big smoke".

Alas, even at night when reception is possible, the fading and inter-station interference makes the position rather dismal.

I was wondering if you could come up with a project for a "we of the never never" type of receiver, or, alternatively, a few hints and ideas on how to improve reception by such means as:

- (a) active aerials;
- (b) filters to remove such noise as from reticulation transformers, the neighbour's welder and other electrical devices;
- (c) a clipping device to reduce the effects of lightning peaks;
- (d) reducing the bandwidth to reduce interference from stations on closely allocated frequencies.

Before closing, may I compliment you on the excellent magazine you produce, and which I have enjoyed reading for some years now. Indeed, your magazine must be good, to judge by the number of people who beg, borrow or flog it off my desk every month!

C.K. (Cobar, NSW)

We certainly appreciate the "bouquet" but the last sentence does tend to make us weep silently in the corner. Surveys have shown that our regular

readership is well over 200,000. If only they would all buy their own copy!

But, getting down to the substance of C.K.'s letter, it is indeed sobering to realise that, in this day and age, the options of some listeners are so limited. What with national, commercial, ethnic, FM and other nearby stations, listeners in Sydney can take their pick of about 14 "local" radio programs and at least 4 television programs. How we'd react if this were suddenly cut down to one vulnerable signal from a national regional 70 miles away!

Curiously, C.K. doesn't mention short-wave reception, to which I personally have turned on occasions, when marooned in a radio desert.

As for his request for assistance, I doubt that there is much chance of us attempting the design and description of a specialised build-it-yourself receiver, at least in the immediate future. These days, the construction of receivers in Australia, and the provision of components for same is just about at a standstill.

As for modifying an existing receiver, we hesitate to encourage readers to dive into commercial equipment, with iron a'smoking, in case they get into troubles outside the manufacturer's willingness to rectify.

It may be possible, for example, to sharpen up the selectivity by doctoring the IF channel wiring to nudge it closer to the point of oscillation, but it's a pretty dicey nudge. Say no more!

On the subject of noise limiters, a simple circuit that could perhaps be tried in many existing receivers was shown on page 89 of our March 1976 issue and a copy of the circuit is reproduced herewith. It may help with those isolated static crashes, although probably not with recurrent buzzing type electrical interference.

On this point, I am not very optimistic about beating electrical interference at the receiver, by the use of a mains filter, as suggested. My experience suggests that the only effective place for a mains filter is at the noise source, to prevent the hash getting into the mains. Once it does so, it tends to be radiated and to become just another radio signal, to be picked up along with the wanted station. The problem is that in a population centre well away from radio stations, the total noise ambient is produced by any number of fluorescent lights, switches and appliances, TV receivers, leaky line insulators, etc — and it just isn't possible to track them all down and treat them individually.

A clue as to the possible effectiveness of a local line filter can be obtained by listening at the site with a battery operated receiver connected to the proposed aerial and earth. If it suffers less from electrical hash than one powered from the mains, a local line filter may just help.

The only other thing I can suggest is that C.K. experiment with the old idea of

R.H. Cunningham  
Pty. Ltd.

## THEY'RE EVERY MICROPHONE YOU EVER WANTED.



# SENNHEISER

We've taken the latest advances in electret technology one step further. By combining them with advanced acoustic technology to make professional condenser microphones more portable.

One common powering module (K2U) serves three different compact heads: omnidirectional (ME20), cardioid (ME40) and mini-shotgun (ME80). Thus, for most studio and location situations, it's no longer necessary to carry three different microphones. Each head contains its own microphone capsule and "front-end" electronics, all exactly matched to its own precisely-controlled acoustical environment.

The Powering Module runs on a single 5.6V battery, or phantom-powered directly from your recorder, preamp or other auxiliary equipment. Best of all, of course, is the great versatility. In a matter of seconds, you screw on whichever head you need and go!

Powering module and heads are available separately.

Australian Agent

R.H. Cunningham  
Pty. Ltd.

VIC.: 493-499 Victoria St. West  
Melbourne, 3003 Ph: 329 9633  
N.S.W.: 4-8 Waters Rd. Neutral  
Bay, 2089 Ph: 909 2388  
W.A.: 256 Stirling St. Perth,  
6000 Ph: 28 3655  
QLD.: L. E. BOUGHEN & CO.,  
Cnr. Milton & Baroona Rds.,  
Milton 4064 Ph: 36 1277  
S.A.: Werner Electronic  
Industries Pty. Ltd. Unit 25,  
28 Gray St., Kilkenny, 5009  
Ph: 268 2801

Telex: Melbourne 31447  
Sydney 21707 Brisbane,  
41500 Perth 93244

RHC 6566





# THE TERRIFIC TRIO: DICK SMITH & **TRIO** & LOW, LOW PRICES!

## Professional TRIO Test Gear at DICK'S Special Low Prices.

Trio 'E' Series instruments are outstanding value. Take your pick of R.F. and audio signal generators, scope and FET Volt-ohm-meter. These instruments are popular with advanced hobbyists, education establishments and many professional laboratories. Check the specs below and you'll see what we mean.

I've reduced my already low prices on famous TRIO test equipment. Now everyone can afford to have a really well equipped workshop at a fraction of the price you would pay anywhere else. Come in and have a look at the TRIO range at any of my five stores in Sydney, Melbourne and Brisbane.

**NEW MODEL D SCOPE:  
WITH EXTENDED  
BANDWIDTH TO 5MHz.  
CHECK FULL SPEC. BELOW.**

**PRICES SHOWN AT  
RIGHT INCLUDE  
SALES TAX. SEE  
BELOW FOR TAX-  
FREE PRICES.**



CO1303D 5MHz Scope	SG402 R.F. Generator	VT108FET Volt-Ohm-Meter	AG202A Audio Generator
<b>CRT:</b> Vert. sensitivity: 20mV/cm Attenuator: 1/1, 1/10, 1/100 plus fine control Bandwidth: DC to 5MHz (13dB) AC: 3Hz to 5MHz (13dB) <b>Input R&amp;C:</b> 1 Mohm, 30pF <b> horiz. sensitivity:</b> 300V (DC+AC peak) or 500V P-P 500mV/cm <b>Attenuator:</b> QC to 230kHz <b>Input R&amp;C:</b> 1 Mohm, 40pF <b>SwEEP free:</b> 10Hz to 100kHz in 4 ranges <b>Synchronisation:</b> Internal (-) <b>Power requirements:</b> 100/117/230V AC 50/60Hz	<b>Freq. range:</b> 100kHz to 30 MHz in 6 ranges <b>Freq. accuracy:</b> ±1% <b>Output voltage:</b> 0.1V <b>Attenuator:</b> HIGH/LOW (10:1) and variable control <b>Modulation:</b> Internal: 400Hz, 40% mod. degree Requires 1.5V RMS for 40% mod. deg. External: 100/117/230V AC 50/60Hz 6W <b>Power requirements:</b> 189W x 131H x 220D 1190W x 154W x 245D (max dim.) <b>Dimensions: (mm)</b> <b>Weight:</b> 2.5kg	<b>DC Voltmeter:</b> 0.5 to 1500V in 6 ranges 11 Mohms on each range ±3% at full scale <b>AC Voltmeter:</b> 1.5 to 1500V RMS full scale ±3% at full scale <b>Ohm meter:</b> 0.1 ohm to 1000Mohm in 7 ranges <b>Accuracy:</b> ±5% at full scale 15Hz to 5MHz ±10% 30Hz to 2MHz ±3% <b>Frag. response:</b> 2% of setting range at scale 0.3-3 10% of setting range at scale 0.3-10 <b>Memory 1% scale variation:</b> Approx 30 seconds <b>Input impedance:</b> 1 Mohm <b>(Any other voltage):</b> 4.2 to 4200V P-P <b>Input impedance:</b> 80kΩ at 300-3500V range	<b>Frequency range:</b> 20Hz to 200kHz in 4 ranges ±(3% + 2Hz) <b>Frequency Accuracy:</b> ±(3% + 2Hz) <b>Sine wave characteristics:</b> Output voltage: 10V RMS ±10% Distortion: 0.5% at 60Hz; 100kHz <b>Square wave characteristics:</b> Output voltage: 10V P-P Overheat: 3% Base: 10% at 20kHz 800 ohms <b>Output attenuation:</b> 10V P-P Level ±0.5dB <b>External synchronization:</b> 10V approx 3V RMS 10kHz <b>Max input voltage:</b> 3V RMS <b>Input impedance:</b> 10kΩ
CAT Q-1230 ..... \$190.00 tax inc. \$167.00 tax free	CAT Q-1250 ..... \$85.10 tax inc. \$74.00 tax free	CAT Q-1210 ..... \$86.60 tax inc. \$54.00 tax free	CAT Q-1220 ..... \$85.10 tax inc. \$85.00 tax free



# TRIO CS1562 NEW Dual Trace, Triggered Sweep

Dick's special price:  
**\$435.80**  
(Tax Free Price \$379.00)

- \*DC to 10MHz BANDWIDTH
- \*10mV/div SENSITIVITY
- \*1uS to 0.5S/div SWEEP

Ideal for TV, Education, Research, etc., etc. . .

- TV-V and TV-H sync + 5x magnified sweep
- X-Y operation plus Z mode
- CHOP/ALT automatically selected
- Dual FET vertical amp
- Stabilised EHT DC-DC converter
- Die-cast front panel

\* With FREE X10 probes worth \$70! \*

**DICK SMITH ELECTRONICS GROUP**  
Head Office: Phone 439 5311. Telex AA20036. Cable 'Diksmi' Sydney.  
Mail Orders: P.O. Box 747, Crows Nest, N. S. W., 2065.  
N.S.W. Branches: GORE HILL - 162 Pacific Highway, 439 5311.  
SYDNEY - 125 York St., 29 1126. BANKSTOWN - 361 Hume Hwy., 709 6600.  
QLD. - 166 Logan Rd., Buranda, 391 6233.  
Interstate Branches: VIC. - 656 Bridge Rd., Richmond, 42 1614.


Cat Q-1242..... \$435.80; (\$379 tax free)

**SHOP HOURS**  
MON - FRI : 9 to 6.30  
SAT : 9 to 12

**POSTAL CHARGES**


ORDER VALUE	CHARGE	BY COMET FREIGHT THE MINIMUM PACKING AND HANDLING CHARGE
\$5 to \$9.99	\$1.00	IS \$1.00 WE DESPATCH "FREIGHT"
\$10 to \$24.99	\$1.50	ON AND YOU PAY WHEN YOU RECEIVE THE GOODS.
\$25 to \$49.99	\$2.50	
\$50 to \$99.99	\$3.50	
\$100 or more	\$5.00	

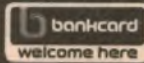FOR C.O.D. SEND \$2.40 EXTRA PLUS \$3.00 DEPOSIT  
MINIMUM MAIL ORDER AMOUNT IS \$5.





## LOOP AERIAL REDUCES INTERFERENCE

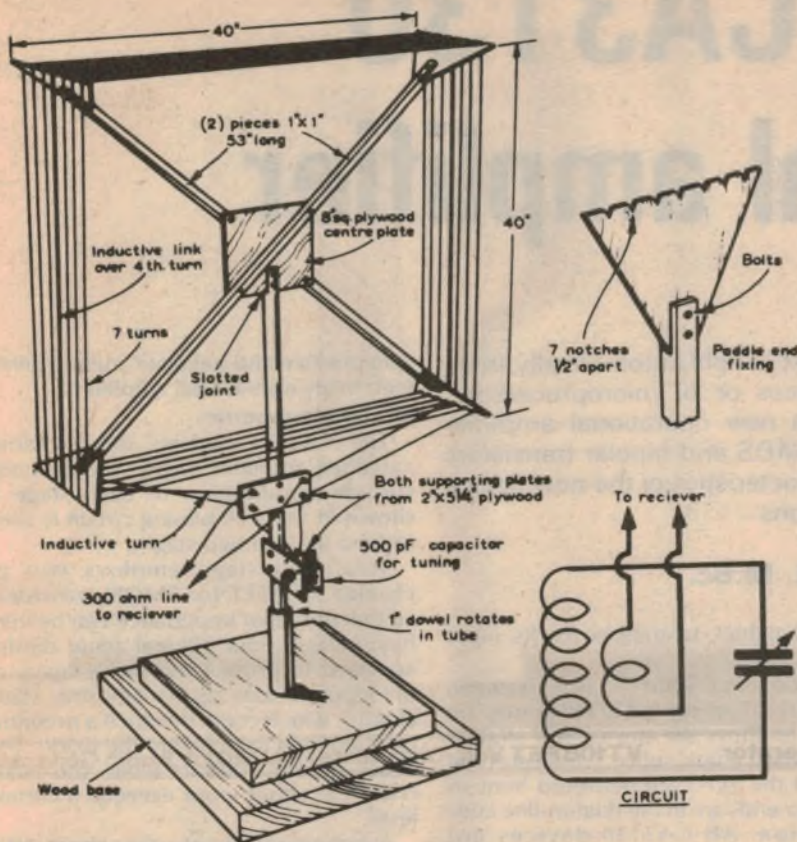

Listeners wishing to receive broadcast band signals (52kHz to 1600kHz) in remote or difficult locations might well consider the loop aerial illustrated.

This type of antenna is directional; maximum pick-up is along the plane of the windings, minimum pick-up along a line at right angles to the windings. The depth of the null (degree of signal suppression) depends on the electrical balance of the windings so it is important that they should be symmetrical.

The loop is very simple to use. Tune in a station on the receiver, peak it with the loop tuning control and rotate the loop to optimum reception. Frequently it is possible to null-out different stations on the same frequency, where these are located roughly at right angles to each other from the point of reception.

Similarly, static from summer thunderstorms may often be minimised when listening to stations at right angles to the direction of the storm.

The 40in loop is a compromise between pick-up and convenience. A larger loop will have greater pick-up. Alternative sizes can be constructed, using approx 100ft of plastic covered wire of about 22SWG for the main winding which should be wound to a whole number of turns. If the loop will not tune to the HF end of the band there are too many turns. If it will not tune to the LF end then add turns or increase the value of the tuning capacitor. The pick-up loop consists of a single turn wound alongside the fourth turn of the main winding, as shown in the illustration.

a rotatable loop aerial along the lines of the one in the panel, reproduced from our Projects and Circuits book. A loop aerial can discriminate to a degree against local electrostatic noise impulses, while it can also null out signal sources (noise or unwanted stations) which are exactly broadside to it.

If the receiver has a normal aerial coil, connect the pickup loop to the aerial and earth terminals. Where the receiver is a portable, with its own internal ferrite rod, it is essential to make sure that the natural pickup of the rod does not compete with that of the loop. If the receiver has external aerial and earth terminals, try rotating the receiver to see which way reinforces the pickup of the large loop. Either that,

or stand the receiver on end, to minimise direct pickup by its ferrite rod.

Where the receiver is small enough, don't worry about connecting the loop to it at all. Mount the receive inside the large loop, so that it rotates with the loop, with the ferrite rod running through the loop like an axle. The large loop will couple magnetically into the rod. Too much trouble? I guess it depends on how desperate one is to hear something other than "Blue Hills".

One final point: it may be that other readers are in a position to help C.K. with practical experience in similar situations. Or may be there's a receiver or two on the market which is particularly suited to "back o' beyond" situations.

It's over to you.

116 pages  
crammed with  
bargains

OVERLEAF:

## TANDY ELECTRONICS 1977 CATALOG

KEEP THE  
CATALOG BY YOU  
FOR FUTURE  
REFERENCE

Open the catalog out flat  
and identify the two staples  
which secure it into the  
magazine. Open the  
staples, pull out the catalog  
and reclose staples.

Advertised goods are avail-  
able from over 100 Tandy  
Electronics stores throughout  
Australia, or by mail order.



# Using the CA3130 operational amplifier

When the word 'CMOS' is mentioned, most people automatically think of the well known series of digital devices or of microprocessors. However, RCA has recently introduced a new operational amplifier which combines the advantages of both CMOS and bipolar transistors on a single chip. Here we examine the characteristics of the new device and describe some typical circuit applications.

by J. BRIAN DANCE, M.Sc.

Designated the CA3130, RCA's new operational amplifier offers several attractive performance features. It has an input impedance of typically  $1.5 \times 10^{11}$  ohms, while input current is typically 5pA and input offset current is about 0.5pA at 25°C. The gain-bandwidth product is around 15MHz, and the slew rate is about 10V/us.

Typical applications include use in a wide variety of circuits, such as high input impedance comparators, long duration timers and monostables, high input impedance wideband amplifiers, voltage regulators, and photodiode amplifiers, etc. Several circuits are described later in the article.

## Types

The CA3130 is available only in an 8 lead TO-5 type circular metal can. The CA3130A is selected for lower input voltage and input offset current than the more economical CA3130. The CA3130B

has still tighter tolerances for its input specifications.

An additional suffix 'T' (for example, the CA3130T or the CA3130BT) may be added to show the device has straight leads, whilst a final suffix 'S' indicates the leads of the TO-5 are delivered bent so that their ends are in the dual-in-line configuration. All CA3130 devices are specified over the full 'military' temperature range of -55°C to +125°C.

## Power supply

The CA3130 can operate from any supply voltage in the range 5V to 16V, or with balanced power supplies in the range  $\pm 2.5V$  to  $\pm 8V$ . The device can be operated with the input voltage 0.5V below the potential of the negative supply rail, whilst the output voltage can swing almost to the potential of either supply rail. These features render the device very suitable for use with a single positive power supply line instead of the

split positive and negative lines required with many operational amplifiers.


## Electrical properties

The CA3130 contains three internal cascaded amplifier stages. The gain and current consumption of each stage is shown in Fig. 1. A biasing circuit is used to feed the first two stages.

The input stage employs two p-channel MOSFET (or PMOS) transistors so that the input impedance can be very high indeed. Four internal zener diodes are used to protect the oxide layers of the input devices against any stray static charges which could produce a potential large enough to puncture the oxide. The zener diodes conduct when the static charge at either input exceeds a certain level.

A potentiometer of value about 100k may be connected between pins 1 and 5, with the wiper arm connected to the negative supply line (pin 4), so that the offset can be 'nulled'. A fine offset-null adjustment can usually be effected with the slider arm near to the mid-point of its range.

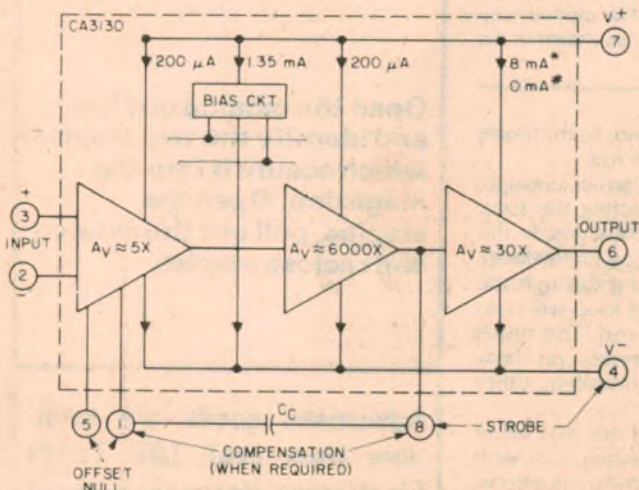The CA3130 input current is typically 5pA at 25°C, this being mainly leakage current passing through the gate protecting diodes. The value of this current is roughly doubled for each 10°C rise in temperature, as with any reverse biased semiconductor junction. The variation of



TOTAL SUPPLY VOLTAGE (FOR INDICATED VOLTAGE GAINS) = 15 V  
 \* WITH INPUT TERMINALS BIASED SO THAT TERM 6 POTENTIAL IS +7.5 V ABOVE TERM 4  
 \* WITH OUTPUT TERMINAL DRIVEN TO EITHER SUPPLY RAIL

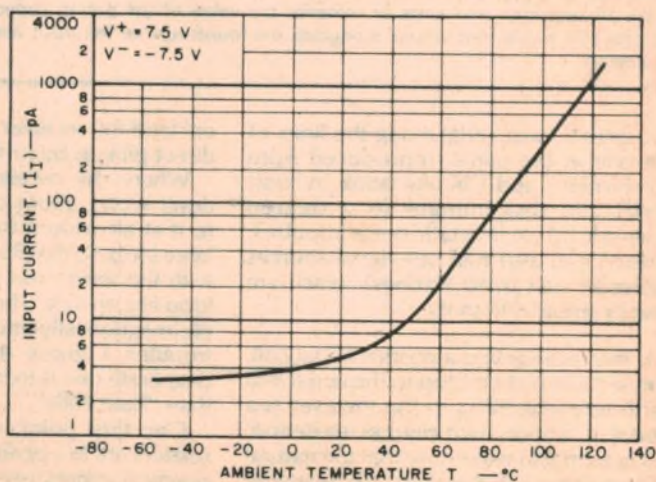


Fig.1 (left): the three internal amplifiers of the CA3130 in block form. A biasing circuit is used to feed the first two stages. Fig. 2 (above) is a plot of the variation in input current with temperature for the CA3130.



the input current with temperature is shown in Fig. 2.

The second amplifier of the CA3130 provides most of the overall gain. It contains a single NPN bipolar transistor which drives a cascade connected load. Frequency compensation is effected by connecting a small capacitor of value about 47pF between terminals 1 and 8.

The output stage consists of a drain-loaded inverting amplifier using CMOS transistors operating in class A. When this stage feeds a high impedance load, the output voltage can swing to within a few mV of the potential of either supply line. The gain of the output stage is dependent upon the load impedance.

#### Handling

The gate electrodes of the MOSFET input transistors of the CA3130 are protected against high potentials which can arise as a result of static charges forming at the input. Nevertheless, it is wise to exercise reasonable care in handling the CA3130 to reduce the possibility of damage.

The following precautions are recommended:

- (1) Soldering iron tips, tools and any metal handling facilities should be grounded.
- (2) CMOS devices should not be inserted into or be removed from circuits whilst the power is applied, since transient voltages can cause damage.
- (3) Signals should not be applied to the input when the power supply is off.
- (4) Input terminal currents should not exceed 1mA.

#### Typical applications

**Voltage follower:** In a voltage follower circuit, the output voltage 'follows' the input voltage very closely. The source of the input voltage may have a very high impedance so that it is not suitable for supplying current directly to a load, but this input can feed a CA3130 voltage follower which in turn feeds current to the load. The high input impedance of the CA3130 makes it especially suitable for this application.

A CA3130 voltage follower operating from dual power supply lines is shown in Fig. 3, whilst Fig. 4 shows a similar circuit operating from a single power supply line.

Circuits such as these may be employed in the input stages of digital voltmeters, etc.

(2) **Astable circuit:** A simple astable circuit which generates square waves is shown in Fig. 5. Resistors R1 and R2 bias the non-inverting input of the CA3130 to a point mid-way between the two supply line voltages. The timing capacitor is selected by S1. If the voltage across this timing capacitor is initially low (ie, a low voltage at the inverting input), a high output voltage at pin 6 will be produced.

The timing capacitor charges through VR1 and D1 until the inverting input potential exceeds that of the non-inverting input and the circuit switches.



## -that's where the money is!

Stott's course is totally comprehensive — and includes both sophisticated electronic equipment and project materials you need to gain a thorough understanding of servicing techniques.

Divided into three self-contained sections, the course covers:

Part 1 — Introduction to Electronics (theory and practice)

Part 2 — Monochrome Television Receivers

Part 3 — Colour Television, including processing circuitry, service techniques, fault tracing and trouble shooting techniques.

Like all Stott's courses, you work with your own instructor who is an expert in this exciting and rewarding field, at your own pace, in your own home.


If you are a beginner, Stott's will teach you everything you need to know concerning television principles and receiver circuitry.

If you are already working in the field, or have completed some studies in electronics, you may be eligible to enter the course at an advanced stage. Whether your aim is to enter the TV service industry or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course which will help you make it!

Other electronics courses offered by Stott's include:

Radio for Amateurs — Amateur Operator's Certificate

For full information mail this coupon today:

<b>Stotts</b> 	
TECHNICAL CORRESPONDENCE COLLEGE The name to trust in correspondence education Please send me, without obligation, full details of the following courses.	
Stott's undertake that no sales counsellor will call	
Mr., Mrs., Miss	Age
Address	
Postcode	
159 Flinders Lane, Melbourne. 383 George Street, Sydney. 290 Adelaide Street, Brisbane.	66 King William St. Kent Town, S.A. 89 St. George's Terrace, Perth P.O. Box 3396, Singapore 1.
STC815	EA 10, 76



# E.D.&E. (SALES) PTY. LTD.

## EDUC-8 COMPUTER—COMPLETE KIT

(OCT-NOV-DEC 1974)

**\$402.40 (Plus Tax)**

OR INDIVIDUAL COMPONENTS  
AS REQUIRED

K  
I  
T  
S

K  
I  
T  
S

**MAJOR STOCKISTS OF ALL GENERAL RADIO & ELECTRONIC COMPONENT PARTS — YOU NAME IT — WE WILL QUOTE**

Valves — Transistors — Zener & Power Diodes — Semi-Conductors — Diacs — Triacs — S.C.R.'s — I/C's. Speakers — Microphones — Coils — IFT's. Transformers — Inst Cases — Metalwork Players & Changers — Meters — Relays — Condensers — Resistors — Bezels — Styli — Cartridges — Recording Tape — Probes — Instruments — Potentiometers — Crystals — Ferrite Beads — Cores — Baluns — Terminals — Co-Axial Plugs & Sockets — Multi Connectors — Printed Circuit Boards — Copper Winding — Wire — Etc. — Etc.

## POPULAR KITS — TOP QUALITY — LOWEST PRICES

### AUDIO

- 1 Direct Reading A.F. Gen.
- 2 SQ Wave Gen-10Hz-1MHz.
- 3 Solid State A.F. Gen.
- 4 Additive Freq. Meter
- 5 A.F. Tone Burst Gen.
- 6 Laboratory Solid State A.F. Gen.
- 7 Scaler/Divider Unit
- 8 Crystal Freq. Calibrator
- 9 Direct Reading A.F. Meter (0-200KHz — 10MV.2V)
- 10 High Performance A.F. Gen.
- 11 White Noise Gen.
- 12 —
- 13 —
- 14 —

### AUTOMOTIVE UNITS

- 15 Tacho & Dwell Angle for Service Stations
- 16 Dwell Extender Unit
- 17 Solid State — CDI
- 18 All Electronic Ignition System
- 19 Windscreen Vari-Wiper
- 20 Tacho & Dwell Unit
- 21 Brake Light Warning
- 22 Emergency Flasher
- 23 High Efficiency Flasher
- 24 Solid State Volt Reg.
- 25 Car Theft Alarm System
- 26 Ignition Analyser & Tachometer Unit
- 27 Strobe Adaptor for Ignition Analyser
- 28 Car Burglar Alarm
- 29 1975 C.D.I. Unit

### BATTERY CHARGERS

- 30 6 Volt — 1 Amp
- 31 12 Volt — 1 Amp
- 32 Automatic H/Duty
- 33 1.14 Volt — 4 Amp
- 34 1973 Automatic Unit
- 35 Constant Current Unit
- 36 —
- 37 —

### CONVERTERS — INVERTERS

- 38 12 VDC 300/600V 100W
- 39 12 VDC 240 VAC 20W
- 40 12 VDC 240 VAC 50W
- 41 24 VDC 300 VDC 140W
- 42 24 VDC 800 VDC 160W
- 43 —
- 44 —

### C.R.O. UNITS

- 45 1963 3" Calibrated
- 46 1968 3" C.R.O.
- 47 1968 3" Audio C.R.O.
- 48 C.R.O. Electronic Switch
- 49 C.R.O. Wideband P/Amp
- 50 C.R.O. Calibrator
- 51 —
- 52 —

### INTRUDER WARNING SYSTEM

- 53 Electronic Thief Trap
- 54 Infrared Alarm System
- 55 Simple Burglar Alarm
- 56 Light Beam Relay
- 57 Car Burglar Alarm

### MULTIMETERS & V.O.M.

- 58 Protected D.C. Multimeter
- 59 Meterless Voltmeter
- 60 Wide Range Voltmeter
- 61 F.E.T. D.C.
- 62 1966 V.T.V.M.
- 63 1968 Solid State V.O.M.
- 64 1973 Digital V.O.M. (1)
- 65 1973 Digital V.O.M. (2)
- 66 High Linearity A.C. Millivoltmeter
- 67 —
- 68 —

### PHOTOGRAPHIC UNITS

- 69 50 Day Delay Timer
- 70 Regulated Enlarger Line
- 71 Slave Flash Unit
- 72 Sound Triggered Flash
- 73 Solid State Timer
- 74 Auto Trigger For Time Lapse Movies
- 75 —
- 76 —

### REGULATED POWER SUPPLIES

- 77 Laboratory Type 30/1 Unit
- 78 Laboratory Type Dual Power Supply
- 79 Serviceman's Power Supply
- 80 Solid State H.V. Unit
- 81 IC Variable Supply Unit
- 82 1972IC Unit (E/T)
- 83 Simple 5V 1A Unit
- 84 Simple 3-6V 3.5A Unit
- 85 S/C Proof 0.30 VDC at 1A
- 86 Reg. 0.30VDC at 3A O/L Protected
- 87 Variable Reg. 12V-0.5A
- 88 Reg O/Load & S/C Protection 60 VDC at 2A (1973) — EA
- 89 —
- 90 —

### R.F. INSTRUMENTS

- 91 Solid State Test Osc.
- 92 Signal Injector & R/C Bridge
- 93 Solid State Dip Osc.
- 94 'Q' Meter
- 95 Laser Unit
- 96 Digital Freq. Meter 200KHz
- 97 Digital Freq. Meter 70MHz
- 98 IF Alignment Osc.
- 99 27MHz Field Strength Meter
- 100 100KHz Crystal Cal.
- 101 1MHz Crystal Cal.
- 102 Solid State Dip Osc.
- 103 V.H.F. Dip Osc.
- 104 V.H.F. Powermatch

- 105 V.H.F. F/S Detector
- 106 S.W.R. Reflectometer
- 107 R.F. Impedance Bridge
- 108 Signal Injector
- 109 1972 FET Dipper
- 110 Digital Freq. Meter
- 111 Simple Logic Probe
- 112 Frequency Counter & DVM Adaptor
- 113 Improved Logic Probe
- 114 Digital Logic Trainer
- 115 Digital Scaler/Preamp
- 116 Digital Pulser Probe
- 117 Antenna Noise Bridge
- 118 Solid State Signal Tracer
- 119 1973 Signal Injector
- 120 Silicon Diode Sweep Gen.

### TRAIN CONTROL UNITS

- 124 Model Control 1967
- 125 Model Control with Simulated Inertia
- 126 Hi-Power unit 1968
- 127 Power Supply Unit
- 128 SCR-PUT Unit 1971
- 129 SCR-PUT Unit with Simulated Inertia 1971
- 130 Electronic Steam Whistle
- 131 Electronic Chuffer

### TV INSTRUMENTS

- 134 Silicon Diode Sweep Gen.
- 135 Silicon Diode Noise Gen.
- 136 Transistor Pattern Gen.
- 137 TV Synch & Pattern Gen.
- 138 Cross Hatch & Bar-Gen

### VOLTAGE CURRENT CONTROL UNITS

- 142 Auto Light Control
- 143 Bright/Dim Unit 1971
- 144 S.C.R. Speed Controller
- 145 Fluorescent Light Dimmer
- 146 Autodim-Triac 6 Amp
- 147 Vari-Light 1973
- 148 Stege etc. Autodimmer 2KW
- 149 Auto Dimmer 4 & 6KW

### RECEIVERS — TRANSMITTERS — CONVERTERS

- 153 3 Band 2 Valve
- 154 3 Band 3 Valve
- 155 1967 All Wave 2
- 156 1967 All Wave 3
- 157 1967 All Wave 4
- 158 1967 All Wave 5
- 159 1967 All Wave 6
- 160 1967 All Wave 7
- 161 Solid State FET 3 B/C
- 162 Solid State FET 3 S/W
- 163 240 Communications RX
- 164 27 MHz Radio Control RX
- 165 All Wave IC2
- 166 Fremodyne 4-1970
- 167 Fremodyne 4-1970 R.F. Section Only
- 168 110 Communications RX
- 169 160 Communications RX

- 170 3 Band Preselector
- 171 Radio Control Line RX
- 172 Deltahet MK2 Solid State Communications RX
- 173 Interstate 1 Transistor Receiver
- 174 Crystal Locked H.F. RX
- 175 E/A 130 Receiver
- 176 E.A. 130 Tuner/Receiver
- 177 Ferranti IC Receiver
- 178 Ferranti IC Rec/Amp
- 179 7 Transistor Rec.
- 180 —
- 181 —

### TRANSMITTERS

- 182 52MHz AM
- 183 52MHz Handset
- 184 144MHz Handset

### CONVERTERS

- 187 MOSFET 52MHz
- 188 2.6MHz
- 189 6-19 MHz
- 190 V.H.F.
- 191 Crystal Locked HF & VHF

### AMPLIFIERS PREAMPS & CONTROL UNITS MONAURAL

- 194 Mullard 3-3
- 195 Modular 5-10 & 25 Watt

### STEREO

- 196 1972 PM 129 3 Watt
- 197 Philips Twin 10-10W
- 198 PM 10 + 10W
- 199 PM 128-1970
- 200 PM 132-1971
- 201 ETI-425 Amp & Preamp
- 202 ETI-425 Complete System
- 203 ETI-416 Amp
- 204 PM 136 Amp 1972
- 205 PM 137 Amp 1973
- 205A PM 143

### GUITAR UNITS

- 209 P/M 125 50W
- 210 E/T 100 100W
- 211 P/M 134 21W
- 212 P/M 138 20W
- 213 Modular 200W
- 214 Reverb Unit
- 215 Was-Was Unit
- 216 Fuzz Box
- 217 Sustain Unit

### PUBLIC ADDRESS UNITS

- 219 Loud Hailer Unit
- 220 P.A. Amp & Mixer
- 221 P/M 135 12W
- 222 Modular 25W
- 223 Modular 50W

### CONTROL UNITS

- 225 P/M 112
- 226 P/M 120
- 227 P/M 127

### MIXER UNITS

- 229 FET 4 Channel
- 230 ETI Master Mixer
- 231 Simple 3 Channel

### TUNER UNITS

- 232 P/M 122
- 233 P/M 123
- 234 P/M 128
- 235 Simple B/C
- 236 PM 146 AM-FM

### PREAMPLIFIERS

- 237 Silicon Mono
- 238 Silicon Stereo
- 239 FET Mono
- 240 Dynamic Mic Mono
- 241 Dynamic Mic Stereo
- 242 P/M 115 Stereo
- 243 —

### MISCELLANEOUS KITS

- 244 Geiger Counter
- 245 Direct Reading Impedance Meter
- 246 —
- 247 Electronic Anemometer
- 248 Simple Proximity Alarm
- 249 Pipe & Wiring Locator
- 250 Resonance Meter
- 251 Electric Fence
- 252 Metronome Ace Beat
- 253 Transistor Test Set
- 254 Electronic Thermometer
- 255 Flasher Unit
- 256 Lie Detector
- 257 Metal Locator
- 258 Stroboscope Unit
- 259 Electronic Canary
- 260 240V Lamp Flasher
- 261 Electronic Siren
- 262 Probe Capacitance Meter
- 263 Moisture Alarm
- 264 AC Line Filter
- 265 Proximity Switch
- 266 Silicon Probe Electronic Thermometer
- 267 Transistor/FET Tester
- 268 Touch Alarm
- 269 Intercom Unit
- 270 Light Operated Switch
- 271 Audio/Visual Metronome
- 272 Capacitance Leakage
- 273 Audio Continuity Checker
- 274 Bongo Drums
- 275 Simple Metal Locator
- 276 Keyless Organ
- 277 Musicolor
- 278 Stereo H/Phone Adaptor
- 279 Attack Decay Unit
- 280 Tape Recorder Vox Relay
- 281 Tape Slide Synchroniser
- 282 Tape Actuated Relay
- 283 Auto Drums
- 284 IC Vol Compressor
- 285 Audio Attenuator
- 286 Thermocouple Meter
- 287 Door Monitor
- 288 Earth 'R' Meter
- 289 Shorted Turns Tester
- 290 Zener Diode Tester
- 291 Morse Code Osc.
- 292 Simple Electronic Organ
- 293 Pollution & Gas Analyser
- 294 Universal H/Phone Adaptor
- 295 Super Stereo ETI-410
- 296 'Q' Multiplier
- 297 Optamin

PHONE  
662-3506

**E. D. & E. (SALES) PTY. LTD.**  
118 LONSDALE STREET, MELBOURNE — 3000 — VIC.

PHONE  
662-3506



## CA3130 op amp

The output voltage falls to a low value and the timing capacitor now discharges through D2 and VR2. When the potential at the inverting input falls below that at the non-inverting input, the output will switch back to its former high voltage state.

The use of the high input impedance CA3130 device in this type of circuit has the advantage that one can use high value resistors in series with the two diodes and therefore the frequency can be very low, even with fairly small values of timing capacitor. The ON (output voltage high) and OFF (output voltage low) times are independently adjustable using VR1 and VR2 in the circuit shown.

If one wishes to alter the ON time whilst simultaneously changing the OFF time in the opposite sense, VR1 and VR2 should be replaced by a single potentiometer which has its slider connected to the positive line and its track ends to R4 and R5 respectively.

The circuit shown in Fig. 5 enables the pulse periods to be adjusted over the very wide range of 250:1 with each of the capacitors shown. The timing capacitors used in the S1 circuit must not be electrolytics, since the latter type of capacitor passes a relatively high leakage current which could not flow through VR1 and VR2 when these components are set near to their maximum value.

### Waveform generator

A circuit which generates triangular and square waves is shown in Fig. 6. Perhaps its most remarkable feature is that the frequency of oscillation can be adjusted over a range of 1,000,000:1 (0.1Hz to 100kHz) by the use of a single variable resistor without any range changing. A voltage-control input is also available for remote sweep control.

The CA3080 is an operational transconductance amplifier used here as a voltage controlled current source. The output

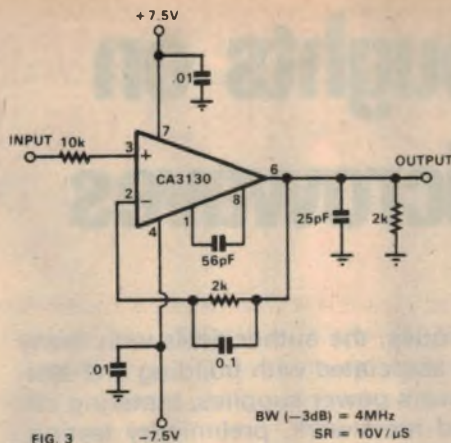


FIG. 3 BW (-3dB) = 4MHz SR = 10V/μs

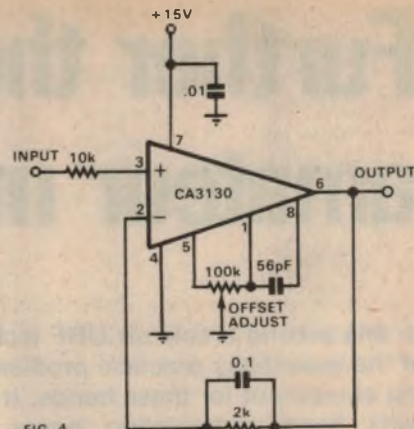


FIG. 4

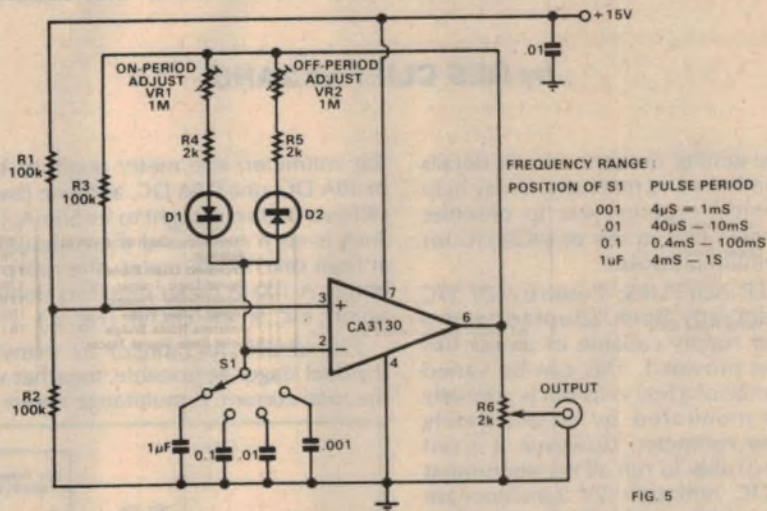


FIG. 5

from this stage is a current which is applied directly to the integrating capacitor C1 in the feedback loop of the CA3130 which provides the triangular wave output.

The final CA3130 stage is a switch which sets the limits of the triangular wave output and provides a square wave output. This square wave signal is also fed back via R4 to switch the current source to generate the required positive or negative current. The variable

capacitor C2 can be used to adjust the corners of the square wave output for optimum shape.

### Other applications

Various other applications of the CA3130 are given in the data sheet (RCA File number 817), including its use as an error signal amplifier in regulated power supplies, its use in peak signal detectors, in ideal full wave rectifiers, and in 9-bit digital to analog conversion.

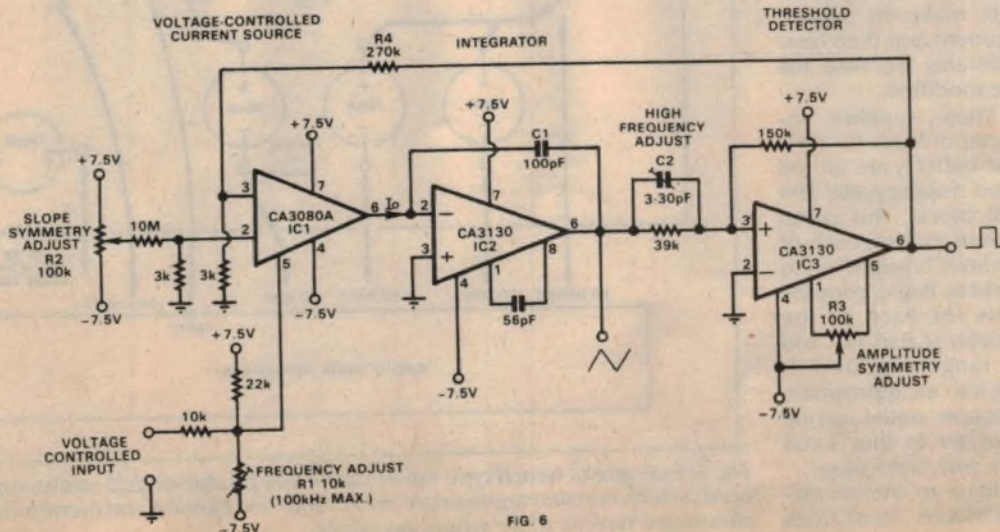


FIG. 6



# Further thoughts on amateur microwaves

## Part 2

In this second article on UHF techniques, the author deals with many of the essentially practical problems associated with building and testing equipment for these bands. It covers power supplies, metering circuits, board construction, boxes and metalwork, preliminary testing, etc., as well as some of the unexpected problems which can occur.

### by DES CLIFT VK2AHC

Before getting down to circuit details for transmitters and receivers, it may help the potential experimenter to describe the arrangements in use at VK2AHC for development purposes.

**POWER SUPPLIES:** Positive 12V DC has reluctantly been adopted, and a stabilised supply capable of about 10A has been provided. This can be varied over a range of a few volts but is normally set and monitored by an accurately calibrated voltmeter. However, it is not always possible to run all the equipment off 12V DC. Although 12V transistors are available which would do the job, they are usually expensive and not available as surplus. On the other hand 18V, 24V and 28V types can be obtained much cheaper and in some cases, surplus. So an 18V and 24V 2A dual stabilised supply has been provided for these. These supplies need not be elaborate.

Two or three 6V lantern batteries are also most useful, last for years, and are a good back up to the above. For anything requiring more than the basic 12V, the writer prefers to complete the design work using bench supplies. Only then provide the supply, rather than speculate on the requirements, make the supply, use it in the development and then have to modify it considerably because the basic plan had to be modified.

**METER PANEL.** These supplies, together with a hefty pair of leads for connection to a 12V car battery, are all fed into a bench mounted sloping panel unit via a large terminal block. This panel contains several current meters, each of which has its connections brought out to front panel 5mm sockets. It also contains 5mm socket outlets for each of the supplies and a voltmeter scaled 12V and 30V. The voltage range required is selected by plugging into an appropriate socket. Thus, each supply outlet can be fed via a selected meter to the circuit under test using links with 5mm plugs.

Obviously, the choice of meters depends on what is available. Apart from

the voltmeter, one meter ought to be 5 or 10A DC, one 0.5A DC, and one (better still two or three) ought to be 50mA. One 5mA is very useful and there should be at least one 100µA meter—the more the better. A 100µA meter monitors detector points, etc., in the circuit. (Fig. 5.)

The idea is to monitor as many individual stages as possible, together with the total current. A multirange meter can

then be used to full advantage, not being permanently connected to the circuit. The arrangement may seem expensive on meters but these are available in surplus equipment.

Dozens of meters from units which were "unsaleable" for less than the price of the meters themselves, have been salvaged and put to good use. There are also quite inexpensive meters around these days—indication rather than accuracy is often the real requirement; 10% to 15% is quite OK.

**PROTOTYPE BOARDS.** For circuits using transistors and I/Cs, and operating up to 460MHz, the method described in Electronics Australia October '73, is still preferred at VK2AHC. This uses Zephyr pins mounted in holes milled out of both sides of double sided board.

The RF components are strung from feed through or stand off by-pass capaci-

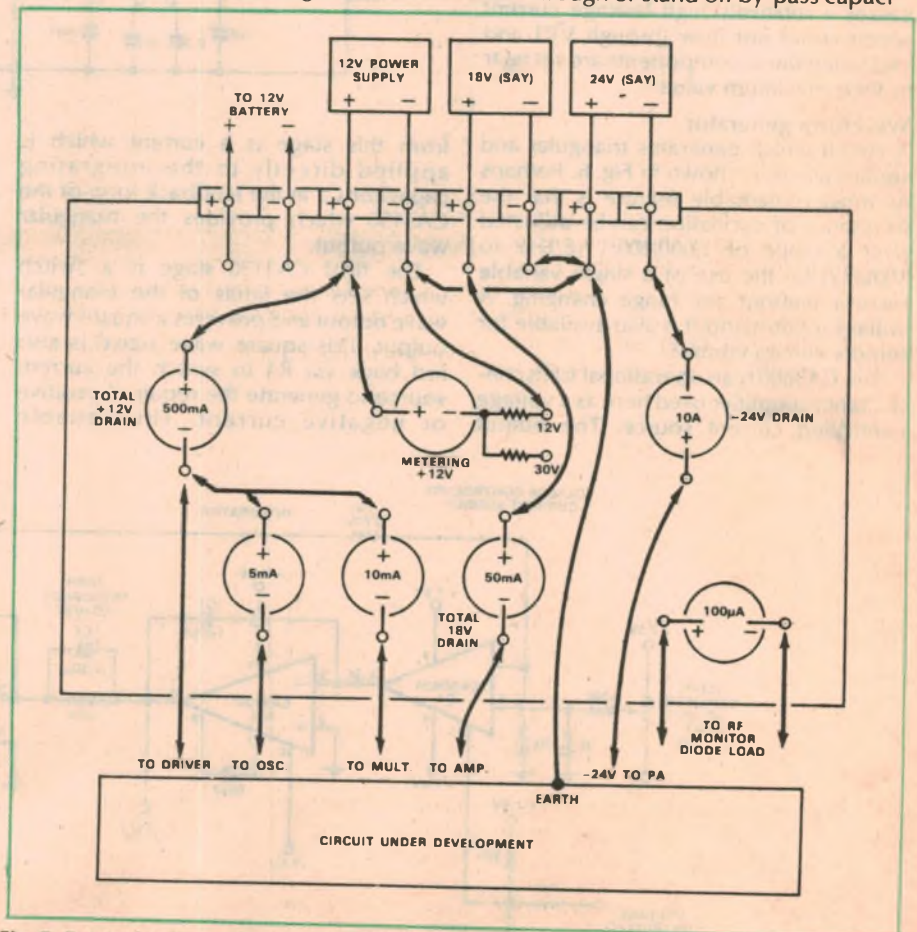


Fig. 5. Example of bench type meter panel. The double ended arrows represent patch cords which connect appropriate meters into any circuit to be monitored. The meters shown are typical; more would be better.



tors. It is usually necessary to make a real prototype of the initial stages such as the crystal oscillator, modulator and first two buffer or multiplier stages. When the placement of the parts has been made and its output measured, the final model is made on a piece board cut to the size required by the box or chassis used.

The later multiplier stages, which are usually much simpler in design and layout, are then added stage by stage to the driven unit. It is very advantageous to do a mock up layout of the final stages, starting from the output and working back. The layout should closely follow the circuit diagram.

It is important to link together both sides of double sided board, at frequent intervals. Drill suitable size holes at about 3in intervals around the outer edge, and at each side of the transistors, pass a piece of tinned copper-wire through each hole and solder it to the copper on both sides.

Try not to use all the space and leave enough to add a low level stage should the desired output not be achieved. This is facilitated by making the output of the driver unit 50 or 75 ohms and the input of the final stages the same, both linked by a short length of coaxial cable.

Use of the widely available (but not cheap) cast boxes is highly recommended for complete separation and modular construction. About their only disadvantage is that they usually require a piece of circuit board as a sub-chassis. Think twice about using the lid as a chassis—it is often more effective and convenient to use the circuit board sub-chassis mounted on stand off pillars.

This necessitates having all the tunable controls on one side. An example of this form of construction is shown in Fig. 6. It is helpful to use both sides of the board as an aid to stability and space saving. During construction, use four decent size stand-off pillars on both sides of the board to prevent damage to the components.

**GENERAL COMMENTS:** Transistor circuits cannot usually be dipped in situ like valve circuits. However, as the higher frequency collectors and outputs are normally tapped well down the coil, the tuned circuit can be dipped before assembly and an allowance made for the loading. Very early in the chain one usually reaches the top of the dip oscillator range and has to rely on experience to get the circuits to resonate. It is surprising how easy it is to get a stage off its desired frequency so that it amplifies the fourth harmonic rather than the third and so on.

It is not unusual for the crystal oscillator frequency to appear in quite large proportions at the output, which may be 8 or 9 times the crystal oscillator frequency. It may be filtered off at the low level 8 or 9 times stage by a separate interstage trough line bandpass filter, which also helps to clean up other spurious. Try to avoid exclusive use of capacitor

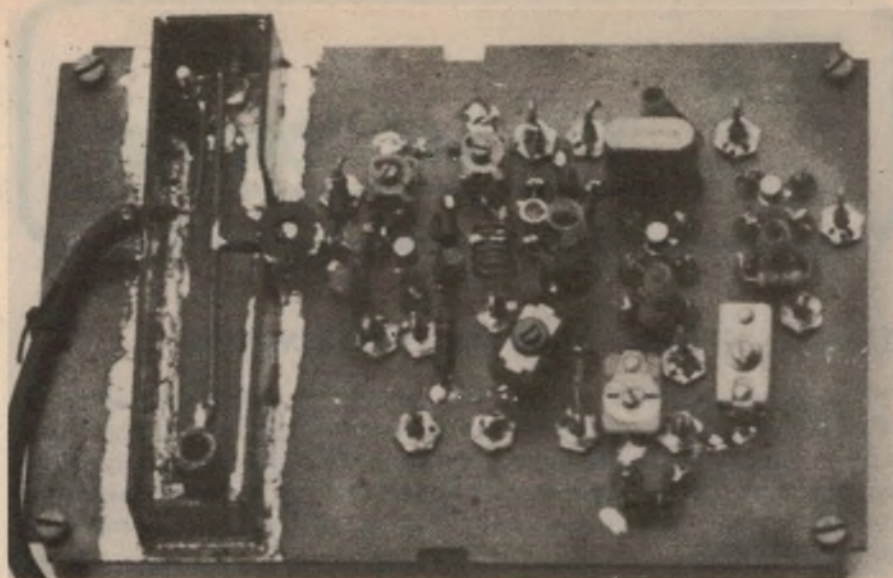


Fig. 6. Example of a circuit board used as a sub-chassis. It is fitted with stand off pillars to facilitate mounting in a die cast box.

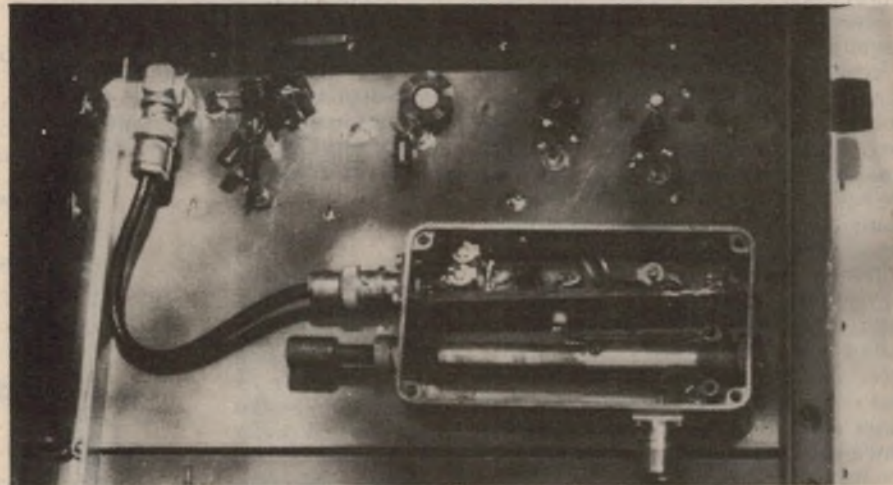


Fig. 7. Tuned lines are best adjusted by starting at one quarter wavelength and pruning to save space. Shown is part of a tripler from 193.6MHz to 581MHz.

couplers throughout the whole chain by using at least one LC bandpass coupler.

Air capacitors should be used wherever possible. Polar 0-10pF obtained new or surplus are very useful but have to be handled with great care as they very easily short. The renowned Philips concentric air trimmers are very useful but can present problems, due to their size, at 300MHz and up. E.F. Johnson type "T", "U" and "V" in various values (imported by General Electric Services) are available through the usual sales outlets and seem superior in that they come in a wider range, are small and seem less prone to short.

Only high quality dielectric type concentric trimmers should be used. Home made concentric air trimmers are best for tuning trough line circuits above 500MHz.

As an aid to getting the circuits for these frequencies correct, use a line as long as possible to start with (nearly one quarter wavelength) and then, only if necessary to save space, gradually prune this and progressively add capacitance to

make it resonate. An example is a tripler from 193.6MHz to 581MHz; part of a 3400MHz crystal controlled set. (Fig. 7.)

A word of warning. Check the effectiveness of bypass capacitors as each stage is made up. Make sure that adding a .01uF or 0.1uF across the selected bypass makes no difference to the drive to the next stage.

Also, when measuring current in a HT line for tuning make sure that returning a bypass lead to its proper position in the HT feedline, rather than through long temporary leads, makes no difference to the next stage drive.

A recent experience of instability in a three stage amplifier tuned to 104MHz showed the tuned circuit to be actually resonant at nearly 150MHz when bypassed with a particular type of stand-off 1000pF bypass capacitor used without a parallel capacitor. Two other types of 1000pF bypass capacitors gave the correct resonant frequency of 104MHz and the instability disappeared. ☉

(To be continued)





# The Serviceman

## Modern TV sets—more and more complex

The modern colour TV set is a far cry from the black and white set of yesteryear, which was more like a crystal set by comparison. Apart from the fundamental differences between black and white and colour, we now have touch tuning and remote tuning systems; extremely complex circuits in their own right. For the serviceman they represent quite a challenge.

This story is about a Toshiba colour TV set with a most unusual fault. It is a story worth remembering because, without a certain amount of luck I might still be trying to track it down.

While Toshiba sets are available in Australia, being handled by EMI, this particular model is not. Apparently it had been bought in Japan while the owner was on an overseas trip. Also, it appeared to have been made for the German market in the first instance, judging by the German words on the chassis.

The part for concern was the tuner. It was a touch control type capable of selecting eight channels. Each circuit had a trim pot which, in association with a three position switch, was used to set that circuit to any VHF channel or a UHF tuner with which the set was also fitted. Once adjusted, a finger on the touch button was all that was needed to select that channel.

The owner—or somebody—had set up the first four touch buttons to select the four Sydney channels; 2, 7, 9, and 10. Then, apparently on an impulse, they had set up the remaining four buttons in a repeat configuration. And the complaint? Channel 7, if selected by the upper button, would not produce colour, but would if selected by the lower button.

Perhaps it is a comment on our times, and the blase attitude which comes with familiarity, that the customer found this situation mildly annoying. A few years ago most of us would have been prepared to travel quite long distances, and press any number of buttons, just to see colour TV!

Nevertheless, the complaint was genuine enough in the technical sense. It should have been possible to receive any selected channel by means of that circuit, and in colour. And, in any situation where all eight channels needed to be used, failure on one could be a real problem.

Initially, I imagined that the problem would amount to no more than an off-frequency setting of the pot, which could

be restored with a minor adjustment. Sure enough, a quick twiddle was all that was needed to restore the colour.

Fortunately, I put the set to one side and let it run for a while, just in case. And just as well, because the next time I looked at it the colour had vanished. Another tweak of the pot shaft brought it back but I quickly realised that it was a heat sensitive fault.

*Simplified circuit of portion of the touch selection system. When any one transistor is switched on by the touch button circuit it connects the channel selecting pot to the 40V rail. The diodes in the moving arms isolate the pots from each other. It was one of these diodes which developed the temperature sensitive fault.*

The question was, which component had become heat sensitive? My first reaction was to blame the oscillator circuit varicap, but a few moments' thought ruled that idea out. The varicap is common to the oscillator circuit, so that any fault would show up on all channels.


That seemed to leave only the trim pots as being peculiar to each channel and I found it hard to accept that one of these had become heat sensitive.

Fortunately, the owner had had the foresight to obtain a service manual with the set (none was available in Australia) and I pulled this out and took a closer look at the tuner and associated circuitry.

The first thing that struck me was the complexity of the touch button mechanism and the fact that it was still being made with discrete components. With three transistors for each channel it used no less than 24 active components, plus several times this in passive devices—nearly as many as used by some complete TV sets in years gone by! Such a configuration would be a logical candidate for an IC and I was surprised to find it in this form.

But all that is by the way; it was the actual channel selecting mechanism that interested me. At a quick glance, it seemed to follow the broad general principles of most that I have seen so far. The tuned circuits—oscillator, RF stage etc—were tuned by varicaps which, in turn, were controlled by two voltages via a suitable mixing circuit. One voltage was from a pot connected to a regulated supply rail, the pot being the control used to select the channel. The second voltage was from the sound discriminator, via an amplifier, and provided the AFC function in what is now a fairly standard arrangement.

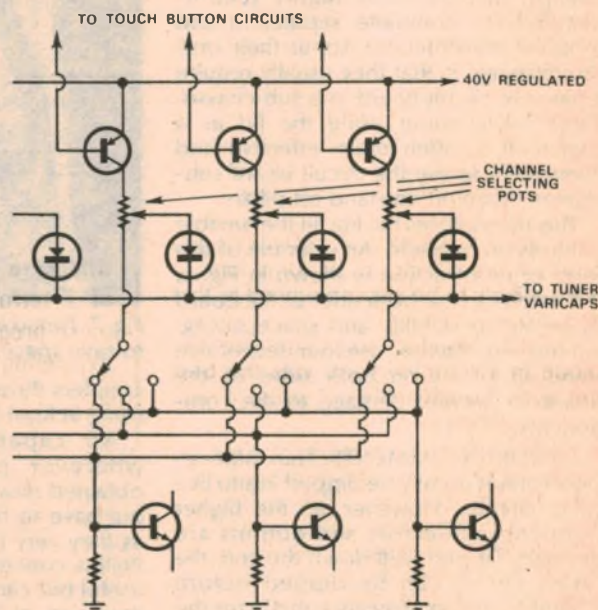The "top" of each of the eight pots was fed from a regulated voltage via the touch tuning circuit; selecting a channel applied voltage to that pot. The moving arm of the pot was then adjusted to sup-



ply the correct voltage to the varicap to select the required channel.

This meant that, in effect, each moving arm was connected to a common rail; the rail that applied the appropriate voltage to the varicaps. To effectively isolate each pot, each moving arm was connected to the varicap rail via a diode.

The "bottom" of each pot was eventually returned to chassis via one of three rails, the particular one being selected by the setting-up technician according to whether the channel required was a low band or high band one, or whether the UHF tuner was required. In the process of returning to chassis it activates one of three "band switching" transistors.



Having sorted all that out, I asked myself what would be most likely to cause a temperature drift in one particular channel. Well, it had to be something which was peculiar to that channel, and it had to be something which was likely to develop a temperature sensitive fault.

Assuming that we ruled out resistors for the moment (they were all metal-oxide types) it seemed to me that the two most likely culprits were either the switching transistor connecting voltage to the pot, or the diode in series with the pot moving arm. I did consider the transistor connected to the bottom of the pot, but ruled it out on the grounds that it was common to several channels.

From a purely practical point of view, I was anxious to make the best assessment possible. None of the components in this part of the set were particularly accessible and I had no wish to indulge in a series of awkward replacements on a "suck-it-and-see" basis.

At this point I rang a colleague who, as well as being well versed in the basic principles of voltage controlled tuners, was rather better informed than I on the behaviour of diodes—including varicaps—and transistors under varying temperature conditions.

Having outlined the circuit I put my suspicions to him. In general, he agreed with me, but went on to explain that the temperature behaviour of a bottomed transistor was not necessarily the same as that of a diode junction. Most of the voltage developed between emitter and collector was due more to a resistive like mechanism than to a junction effect. And, while it would undoubtedly have a temperature coefficient of some kind, it was unlikely to be as pronounced as that of a diode junction.

On that basis we concluded that the diode in the moving arm was the best bet, even though neither of us could suggest the nature of the fault.

Back at the bench I tackled the task of removing the diode. It was an awkward job, to say the least, calling for fine tweezers, my smallest iron, and a set of double jointed fingers! When it was finally out my main thought was that our joint reasoning had better be right.

Without too much optimism I put the diode across the ohmmeter, hoping I might get some indication of a fault. But it wasn't going to be as easy as that; the diode read normal in both directions. Even so, having taken it out it was no harder to replace it with a new one, which I did.

Then I switched on, selected channel 7, and tuned it up for a good picture. After that there was nothing I could do but wait. Happily, after several hours of running, the picture was still in full colour and I considered the point proved. After some more tests the following day I returned it to the customer, then rang my friend to tell him the good news and

thank him for his help.

And what was wrong with the diode? That remains a mystery. Apart from the obvious fact that it seemed to be excessively temperature sensitive, neither my colleague or I can suggest why this should have been so.

Still, I found it, and that is the main thing.

Finally, a brief comment by another serviceman (C. A. of Rutherford N.S.W.) about my story in the July issue concerning the faulty focus pot in a Pye receiver. He writes, "It was with some surprise that I read your article in the July magazine. The fault you describe is so common as to be monotonous, so much so that Pye have now introduced a modified version of the focus assembly."

Then he goes on to mention several other sets which suffer from a similar problem. These include HMV, Healing, Philips and Siemens. Some, in fact, use the identical component.

Thank you, C. A., and I'm sure our readers will be grateful for your help. As for being surprised that I should describe this fault—well, what is so strange about that. It was the first time I, or several colleagues, had encountered the fault and I was intrigued by it, just as I imagine you were, the first time you struck it.

(Editorial note: There is another aspect which the correspondent could not appreciate. For a variety of reasons, stories must often be held over for several issues. This was one such; it would have been more topical when it was written.)

## KNOW

### Where you are going?

Choose a career in the field of Electronics — the Nation's most progressive and fastest expanding industry

BROADCASTING  
COMMUNICATIONS — marine  
APPLIED SERVICING



Classes are conducted at  
67 Lords Road,  
Leichhardt

Day 9.00 a.m. to 4.00 p.m.  
Evenings 6.00 p.m. to 8.30 p.m.  
or by Home Study Courses  
(except practical instruction on equipment)

### SEND FOR PROSPECTUS

There is no obligation.

NAME.....

ADDRESS.....

MARCONI SCHOOL OF WIRELESS  
Box 218, P.O. Leichhardt 2040.  
A service of  
Amalgamated Wireless (Australasia) Ltd.

# LAFAYETTE

27 MHz TRANSCEIVERS  
FOR THE NOVICE AMATEUR

## Telsat SSB-75 SSB/AM 23 CHANNELS



\$259.50 (All Crystals Included)

- Selectable Upper Sideband, Lower Sideband, and AM.
  - Crystal Lattice Filter.
  - Fine Tune Clarifier.
  - Signal Strength/Power Meter.
  - Size—2-3/4 H x 7-15/16 W x 9-5/8" D.
- LAFAYETTE'S newest—a superb SSB and AM rig, beautifully constructed with all the features which have made Lafayette famous. Sensitivity is better than 1uV on AM, 0.25uV on SSB. RF power input 5 watts AM, 15 watts P.E.P. SSB; Output 4 watts AM, 12 watts P.E.P. SSB at 13.8 V DC. Supplied complete with Microphone, Mounting Bracket, DC Power Cable and Operating Manual.

## Micro 723 AM 23 CHANNELS



\$159.50 (All Crystals Included)

- Dual Conversion Receiver.
- 5-Watt "Range-Boost" Transmitter.
- Signal Strength/Power Meter.
- Size—1-15/16 H x 6-1/8 W x 7-1/16" D.

Another transceiver in the popular LAFAYETTE Micro series, the Micro 723 offers excellent multi-channel performance. Features include a 455 KHz mechanical filter and "Range-Boost" modulation circuitry. Sensitivity is better than 1uV. RF Power Output 4 watts at 13.8 V DC. Supplied complete with Microphone, Mounting Bracket, DC Power Cable and Operating Manual.

NOTE: Operators of the above equipment should hold a Novice or General Class Amateur Licence.

# LAFAYETTE

ELECTRONICS

div. of Electron Tube Distributors P/L  
94 ST. KILDA RD., ST. KILDA,  
VIC. 3182. Phone 94-6036.





# THE AUSTRALIAN COMPANY

## MUSICOLOUR Mk3 KIT

ADD AN EXCITING NEW VISUAL DIMENSION TO YOUR FAVOURITE MUSIC!  
Features new circuit with special compressor stage to make the unit less dependent on amplifier volume setting. \* 3 separate channels.  
\* Fully isolated audio input for safety

- \* Strong steel chassis.
- \* Will drive normal 240 volt coloured globes.
- \* Simply driven by your stereo amplifier.
- \* Simply connects to speaker terminals.
- \* Kit comes with all parts and instructions

**FULL KIT**  
**\$49.50**  
SEE E.A. SEPT. 76.

## MUSICOLOUR Mk3 PCB + CONTROLS ONLY

YOU GET ONLY WHAT YOU WANT - THE PRINTED CIRCUIT BOARD, ALL COMPONENTS INCLUDING TRANSFORMERS & CONTROL POTENTIOMETERS.

**SAVE \$20.00**

ON THE COMPLETE KIT  
Ideal for all those who wish to mount this new unit into existing equipment - or were discouraged by the high cost of the full kit. Add your own hardware, wire etc.  
Cat. K-3141... \$29.50

**GENERAL PURPOSE STOP PRESS PREAMP**

SEE E.T.I. 445 JULY 1976

**ONLY \$7.50**

Single PCB - Only ONE IC. Supplied with PCB pins. Runs on 10V to 40V DC. Complete with all parts for -  
1 - Magnetic Preamp (RIAA)  
2 - Tape Preamp (NAB)  
3 - Microphone 40-55 or 80dB gain.  
Cat. K-3427... \$7.50

## SPECIAL KIT PARTS

RE-4 Reverb Spring	Used in Reverberation Kit	Cat. X-1035	\$9.75
UB-5 Zippy Box	Used in TV Game Kit	Cat. H-2755	\$1.10
76/VG5 Printed Circuit Board	Used in TV Game Kit	Cat. H-8308	\$5.50
76/M5 Printed Circuit Board	Used in TV Game Kit	Cat. H-8310	\$1.50
74C00 CMOS Integrated Circuit	Used in TV Game Kit	Cat. Z-5410	\$0.50
74C02 CMOS Integrated Circuit	Used in TV Game Kit	Cat. Z-5412	\$0.50
76/R4 Printed Circuit Board	Used in Reverberation Unit	Cat. H-8314	\$2.00
76/SA4 Printed Circuit Board	Used in Twin 25 Amplifier Kit	Cat. H-8302	\$3.95
75/L11 Printed Circuit Board	Used in Twin 25 Amplifier Kit	Cat. H-8275	\$1.75
Special LED Displays. 10 Green, 1 Yellow, 1 Red	Used in LED VU Meter	Cat. SEM5	\$3.60
76/LM5 Printed Circuit Board	Used in LED VU Meter	Cat. H-8315	\$2.00
76/S7 Printed Circuit Board	Used in 650 MHz Prescaler	Cat. H-8316	\$2.50
76/E04 Printed Circuit Board	Used in 760 Organ Keyer Module	Cat. H-8305	\$3.20
4016 CMOS Integrated Circuit	Used in 760 Organ Keyer Module	Cat. Z-5616	\$1.05
11C90 Integrated Circuit	Used in 650 MHz Prescaler	Cat. Z-5364	\$19.75
MTI Box	Used in 650 MHz Prescaler	Cat. H-2495	\$4.25
ETI 602 Silver Plated F/Glass Board	Used in Mini Organ Kit	Cat. H-8603	\$4.90
MusicoLOUR III Printed Circuit Board	Used in MusicoLOUR III	Cat. H-8318	\$3.95
MusicoLOUR III Metalwork	Used in MusicoLOUR III	Cat. H-3160	\$10.90
MusicoLOUR III Front Panel	Used in MusicoLOUR III	Cat. H-3162	\$3.50
76EX 10 Printed Circuit Board (F/glass)	Used in Novice Transmitter	Cat. H-8894	\$6.00
ETI 602 P.C.B. (Fibreglass + Overlay)	Used in Mini Organ Kit	Cat. H-8604	\$4.90
ETI 445 G.P. Stereo Preamp	Used in General Purpose Preamp Kit	Cat. H-8603	\$1.60

## INSTANT REPAIRS

**\$3.90**  
12 Volt Soldering Iron Model FS30, 15 watts

This fantastic little iron operates from any 12 volt AC or DC source (car or boat battery or 12 volt Transformer). Complete with plated tip & 14ft lead  
Cat. T1910... \$3.90  
Cigarette lighter plug to suit 50c  
Spare tip to suit only 50c

**\$24.75**

**JUST RELEASED** SEE E.T.I. AUG. 76.  
**ETI 602 MINI ORGAN KIT**  
COMPLETE WITH TREMOLO SILVER PLATED FIBREGLASS KEYBOARD - TWO VOICES.  
Cat. K-3430 (Case NOT included) ONLY \$24.75

## BASF TAPE SPECIALS!

Two excellent 7" reel tapes with that extra special sound quality!  
BASF 7" 1800 ft. Low Noise Super  
Cat. C-3412 ..... \$11.50  
BASF 7" 2400 ft. Low Noise Super  
Cat. C-3414 ..... \$13.50

Dick is proud to offer this professional tape at a RIDICULOUS PRICE. So all you Revex, Ferrograph etc owners get your orders in for this extra special deal. Fantastic quality!  
BASF LPR35H 10.5" 3600ft. NAB Centre  
Cat. C-3420 A RIDICULOUS PRICE \$29.95

For all you 8 Track recorder owners Dick is offering the superb 45 minute and 90 minute closed loop 8 track blanks from BASF. Dick's prices are STUPIDLY LOW to buy new.  
Cat. C-3422 - 45 minute cartridge \$3.25  
Cat. C-3424 - 90 minute cartridge \$4.25

## MAGAZINE BINDER

Keep your Electronic Magazines in good shape. Binder holds 12 issues.  
Cat. B-4045 ..... \$4.50

**ONLY \$4.50**

## SIGNAL INJECTOR \$4.75

This Signal Injector (TE-101) uses a circuit designed to make blocking modulation for high frequency at low frequency of 1 KHz. Transistorised. Complete with battery.  
Cat. Q-1270 ..... \$4.75

## VIDEOLYMPIC TV GAME HUNDREDS SIMILAR

**\$49.50** **UNITS SOLD at \$99.50**

PLAY YOUR OWN TV GAMES TONIGHT AT LESS THAN HALF THE COST AS PREVIOUSLY OFFERED. NOW ONLY \$49.50. Just plug into the aerial terminal of your TV set. Play such games as Tennis - Catch Ball - Traps Shooting - Solo  
Cat. X-1125..... \$49.50

SIMILAR UNITS WERE \$99.50

**LISTEN IN!**

Listen to the bands most radios miss. Police, fire, ambulance, taxis etc., as well as normal AM, FM and TV sound. Runs on internal batteries or 240 volt mains power.

AM: 535 - 1605 kHz  
FM: 88 - 108 MHz  
TV1: 56 - 108 MHz (ch. 1-5)  
TV2: 174 - 217 MHz (ch. 6-10)  
Cat. D-2840..... \$24.95

was \$29.90  
NOW \$24.95

**NOVUS B-38 EXECUTIVE CALCULATOR**

WAS \$34.95  
**\$24.50** INCL. TAX

A wallet-size computer that won't flatten your wallet! Big bright, 8 digit LED display. Data storage memory. Full floating decimal system. Percent key. Battery-saver disp. Handsome wallet - Ballpoint pen - Note pad - Pockets etc.  
Cat. Q-3280... Tax free \$21.49 inc. tax \$24.50

## ELECTRONIC ALARM CLOCK RADIO

- \* POWERFUL AM/FM RADIO \* SNOOZE ALARM
  - \* SECONDS DISPLAY FACILITY
  - \* ATTRACTIVE LOW PROFILE MODERN CABINET
  - \* EASY TO OPERATE PUSH BUTTON CONTROLS
  - \* POWER INTERRUPTION INDICATOR
  - \* EASY-TO-SET ALARM RADIO
  - \* MANUAL OR AUTO OPERATION
  - \* SOFT GREEN ELECTRONIC DISPLAY - BRIGHT/DIM SWITCH
- CAT. A-4442 ..... \$39.90

**\$39.90**

WAKE UP TO MUSIC!

## ALARM MODULE \$47.90

The Nidac Alarm Module SPR-3 is a high quality reliable unit. One power switch controls entire operation, including all tests. Solid state Light Emitting Diodes for showing operating condition. Instant seal confirmation. Fixed exit time of 2 minutes. Variable entry time up to 45 seconds. Variable siren timer from 1 to 20 minutes. Full control over exit - entry delay and alarm condition. Heavy duty relay contacts. Flexible mounting considerations.  
Cat. L-5055 ..... \$47.90

**NO MORE FUSES TO REPLACE!**  
**\$7.95** EACH

**CIRCUIT BREAKERS**

Wilco Circuit Breakers completely replace the old-fashioned wired fuses. Just plug them into existing Fuse Holders. If power is overloaded the circuit breaker automatically turns off power... just press green button to re-set. Fits most household boards.  
Cat. S-5508 8amp Cat. S-5515 15amp. \$7.95

**LOOK! FANTASTIC 3AMP DIODE OFFER**

**FULLY BRANDED STC MADE**  
DS-5402 200VOLT MIN. AT 3AMPS  
GIVES 6AMPS IN A BRIDGE  
**IDEAL FOR ALL GENERAL PURPOSE, POWER SUPPLIES ETC.**

Cat. Z-3222 1-9 **30c** 10 UP **25c**

**UNIVERSAL "RUBBER DUCK" CB ANTENNA**

DON'T RUN THE RISK OF DAMAGING THE AERIAL ON YOUR HAND - HELD TRANSCIVER!

Cat. D-4629... \$8.75  
ONLY 12" HIGH

**\$8.75**

## DICK SMITH ELECTRONICS GROUP

Head Office: Phone 439 5311. Telex AA20036. Cable 'Diksmi't Sydney.  
Mail Orders: P.O. Box 747, Crows Nest, N.S.W., 2065.  
N.S.W. Branches: GORE HILL - 162 Pacific Highway, 439 5311.  
SYDNEY - 125 York St., 29 1126. BANKSTOWN - 361 Hume Hwy., 709 6600.  
Interstate Branches: QLD - 166 Logan Rd., Buranda, 391 6233.  
VIC. - 656 Bridge Rd., Richmond, 42 1614.  
(PARK IN THE BOULEVARD)

## SCOOP D.S.E. DRILL SPEED CONTROL

SEE E.A. JULY 76.  
**\$9.75** This kit includes all the parts of the basic speed controller PLUS a small box with pre-punched Marvi-plate front panel and complete instructions. Easy to build, build! Makes your drill turn slow enough to be used as a screwdriver. E.A. Design.  
Cat. K-3080..... \$9.75


## SHOP HOURS

MON - FRI: 9 to 5.30  
SAT: 9 to 12

## POSTAL CHARGES

ORDER VALUE	CHARGE
\$5 to \$9.99	\$1.00
\$10 to \$24.99	\$1.50
\$25 to \$49.99	\$2.50
\$50 to \$99.99	\$3.50
\$100 or more	\$5.00

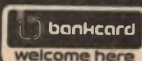RECEIVE THE GOODS.  
FOR C.O.D. SEND \$2.40 EXTRA PLUS \$3.00 DEPOSIT.  
MINIMUM MAIL ORDER AMOUNT IS \$5.






# WITH CHEAPER PRICES!



## PLAYMASTER TWIN 25

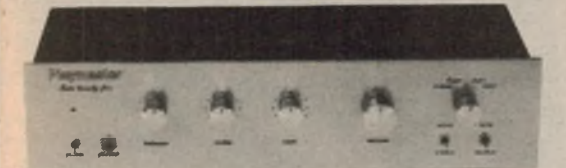

**DICK'S PRICE: \$89.50**  
**Why pay the extra \$4.50?**

Dick may be a nut, but he's no mug! He fully realises you can buy the fabulous Playmaster Twin 25 kit cheaper elsewhere - so why does his cost more?  
**Simple: Dick's kit is a better kit!**  
 Look at the features: You'll agree that Dick's kit is worth a little bit more. (In fact, it's worth a lot more, but Dick's not greedy.)  
 Dick does NOT recommend upgrading the Twin 25 by adding a higher voltage transformer. Many components will be operating outside their ratings.  
**Dick's Playmaster Twin 25: The kit to beat all kits.**  
 Cat K 3410 ..... \$89.50

- \* Dick's 16 page assembly manual. He went to a lot of trouble (and it cost him over \$2000) so you shouldn't have any trouble. It gives you hints and information on the article missed out on.
- \* And if you do have trouble, Dick has a full service back-up for a nominal charge. You MUST get this amplifier working, and working properly.
- \* Dick's imported champagne front panel with control graduations, and matching imported knobs. Gives a truly professional finish!
- \* Power transistor sockets at no extra charge.
- \* And Dick's trouble-free kits.

## 27MHz MARINE RADIO

You can be on the air for under \$40 with a simple, yet efficient 1W hand held (walkie talkie) transceiver which will give a range of 10 miles or so on land (depending on terrain) and more on water.  
 Cat D-1100 ..... \$39.75  
 Or for just a little more, you can have the increased power and range of this value-packed 3 watt, 3 channel hand-held.  
 Cat D-1252 ..... \$59.50

Here come the mobiles: We have this 5 watt, 3 channel transceiver which operates from the car or boat battery.  
 Cat D-1400 ..... \$89.50  
 This Midland set has 6 channel capacity for increased versatility; otherwise it is similar to above set.  
 Cat D-1406 ..... \$109.50



CB Radio - 2-way communication in the 27MHz (11m) band - is becoming very, very popular (even though, at the moment, it is still illegal for anyone except licensed amateur & novice operators). More and more people are finding out about this world-wide hobby; and most are turning to Dick Smith Electronics for world-famous MIDLAND CB Radio equipment.

Then there's the daddy of them all: A 23 channel SSB/AM transceiver most CB operators would give their eye teeth for. The ssb gives extra 'punch' to get through where am sbs are still battling in the mud. All the features you'd expect from one of the top rigs in the world.  
 Cat D-1700 ..... \$239.50

## CQ CB... CQ CB..

Perhaps the most attractive feature of CB radio is that it is not an expensive hobby:

If you want the full 23 channels, we have the budget-priced 13.830 Automatic noise limiter, variable squelch, etc. A very economic way to get the 23 channels.  
 Cat D-1430 ..... \$109.50  
 The Deluxe version of the 830 is the 887B. It also has noise blanking, delta tone (helps resolve off channel calls) and an antenna warning light to protect the transmitter. Fast becoming the most popular set in Australia.  
 Cat D-1436 ..... \$149.50

Fifty (yes, 50) 1 amp 50 volt diodes. Brand new STC EM4005, but unmarked. Ideal for all power supplies etc.  
 Cat Z-9009 ..... \$1.00  
 Hey! that's only 2 cents each!!!!!!



## AM & VHF: SAVE \$5

Here's value! The VHF communicator radio - covers AM broadcast band, and 56 to 217MHz VHF bands: that's the FM band, most TV stations, taxis, police, aircraft, amateurs, etc, etc. AND here's the good news: They've come down in price. Again. Dick has hundreds of these in stock and he needs the space to you benefit! They were \$59; he dropped them to \$49.90, and now, for a short time only, he's clearing them out at \$44.90 - that's a further 10% off! They can't last at this price, so get yours now.  
 Cat D-2833 ..... \$44.90

## FANTASTIC SPECIAL!

### LOOK MICROPROCESSOR USERS

Standard teletype keyboards with gold plated contact switches. All switches are independent and allow you to connect into any form of output. Fully ASCII; neat professional finish.  
  
 Limited quantity in stock - hurry; get yours today. A must for all microprocessor units.  
 Cat X-1180 ..... \$49.50

## VALVES (ALSO KNOWN AS FETS WITH PILOT LIGHTS)

These popular amateur transmitting valves are now lower in price. They can't last so get in for your spares now!  
 6K06 Cat D-7200 ..... \$8.50  
 6S46 Cat D-7201 ..... \$8.25  
 6145A Cat D-7202 ..... \$9.00

The serviceman's 'Bible' Written by an Aussie, the best book on Aust. & NZ PAL television Covers colour TV theory & practice in a not-too-technical way. PAL Colour TV for Serviceman.  
 Cat B-3610 ..... \$12.50  
 (That's nearly 20% off our list!)

## ROCKS 'N' STICKS

FANTASTIC CRYSTAL SPECIAL Speaking of rocks, Dick must have them in his head. He's selling these two most popular channels (9 & 11) crystals for \$1.00 off!  
 Cat D-6006 (27.065MHz) ..... \$6.50  
 Cat D-6008 (27.085MHz) ..... \$6.50  
 Add that extra channel to your transceiver - while they're cheap!  
 62" (sorry, approx. 1.5748M) HELICAL ANTENNA for 27MHz This 27MHz mobile antenna is a quarter wave helical, made by Mobile One. Get your signal out nine sumpin'-else! (Without base)  
 Cat D-4144 ..... \$3.00  
 Scalar base to suit.  
 Cat D-4055 ..... \$4.75

## TRIO CROS

High bandwidth + high sensitivity The TRIO CS-1562 dual trace CRO has bandwidth to 10MHz. Specs are too long to list so ask for the TRIO leaflet at any Dick Smith Store.  
 Cat O-1242 ..... \$435.80  
 (Sales tax free price) ..... \$379.00  
 Don't need all that bandwidth? Then why pay for it? The CA1300A is a budget-priced 75mm CRO with 1.5MHz bandwidth. Ideal for the experimenter and workshop.  
 Cat O-1229 ..... \$149 (Tax-free price \$135.83)

FANTASTIC \$149  
  
 Cat L-4452 ..... \$2.50

## INCREDIBLE BARGAIN!

BRAND NEW DL704 common cathode large 0.3" LED readouts - ideal for all projects, clocks etc.  
 WERE \$2.50 each. NOW ONLY \$1.20 each OR 6 for \$6.60  
 From all Dick Smith stores and dealers  
 Cat Z-4110 ..... \$1.20

## KILL SPOOKY

HIGH QUALITY WEATHERPROOF BALUN  
  
 300.75 ohm balun will mount atop the mast or next to the TV. It's completely sealed against moisture. Convert your 300 ohm twinlead to non-ghosting 75 ohm coax now!  
 Cat L-4452 ..... \$2.50

## 2 GREAT LITTLE SWITCHES

MINI TOGGLE DPDT 3 position, spring return to centre from one position. Can be used as a momentary contact. What a versatile little switch!  
 Cat S-1287 ..... \$1.70 or 10 up \$1.50  
**\$1.70**

## MINI ROTARY 2 POLE 4 POS

Here's another little beauty! A miniature rotary complete with knob. Contacts rated 240V 1A.  
 Cat S-2380 ..... \$3.90

## NOVICES: NEW KIT - SEE EA SEPT, P50.

A NEW ADDITION TO OUR RANGE: A 3.5MHz xtal controlled exciter module for novice transmitter. Fibreglass PCB and all components, but no case, meter or hardware.  
 We already have the 80 metre linear amp available in kit form (KIT K-3133) so simply add this new exciter module K-3135 and you have got a simple, cheap crystal controlled transmitter. It's a great way to start!  
 Cat K-3133 (linear amp) ..... \$34.50  
 Cat K-3135 (exciter) ..... \$29.50

## ICOM VHF

Here are some transceivers for the Z-calls (and others!) who chase the elusive butterfly (also known as VHF DX).  
 These ICOM transceivers are ideal for portable tropospheric DX operation, SSB or CW. The IC502 is a 6 metre rig, covering 52.53 MHz. A vernier driven calibrated dial makes life easy, as does the Lamb type noise blanker and an S meter with RF output level. Comes complete with whip antenna and batteries.  
 ICOM 502 (6m) Cat D-3044 ..... \$180  
**ONLY \$180**  
 ICOM 202 (2m) Cat D-3040 ..... \$184  
 The IC202 is very similar to the IC502, but covers the 2 metre band between 144 & 145MHz.  
**NEW MODEL**

## RIGHT ON BEAM

Want to make your own beam? Or repair one? These'll make you happy. They're aerial elements. Brackets, in two styles. Passivated steel (takes 1/2" to 5/8" rod) and an insulated polystyrene type (takes 3/8" rod).  
  
 Cat D-4650 (poly) ..... 45c  
 Cat D-4652 (steel) ..... 65c

## MATCH THIS:

Is half your power being lost because of poor antenna matching? You can match into a piece of wet string with this deluxe HC-500 antenna coupler. It will tune any aerial for a 1:1 SWR from 3.5 to 300MHz. 52 ohms input; output 10 to 600 ohms bal or unbalanced.  
 Save \$10 on our catalog price!  
 Cat D-5500 ..... \$139  
**SAVE \$2.50**  
 Even if you DON'T want to match into a piece of wet string, you should still go for the lowest SWR you can - and that's where an SWR bridge earns its keep. It also has a field strength meter built in. Up to 150MHz, 52 or 75 ohms impedance.  
 Cat D-1350 ..... \$12.50  
 Has Dick gone mad? That's near 20% off!!!!

## GET ORGAN-ISED

Build your own organ and save!!! Technology has now advanced to the stage where it is economic to build your own organ - just a dream until recently. EA's Playmaster Organ is ideal for home construction; you can make it as simple or as pretentious as you like. And Dick Smith has the kits for the Playmaster Organ. He has the keyboards, he has the key contacts. He has the inbuilt mini amplifier. He has the reverberation module. In fact, he's got the lot! You can buy as much as you want, or all the kits. You can buy it in dribs and drabs, or you can buy it in one swoop. How's that for service? Here are Dick's kits:  
 \* Kimber-Allen keyboards, 49 note, with set of key contacts. Ideal for Playmaster Organ.  
 \* Set of 50 spare key contacts, SPDT, gold plated. For the Kimber Allen keyboard (1 spare).  
 \* Mini amplifier, around 2 watts into 8 ohms. Used in organ, but suitable for many other projects, too.  
 \* Reverberation: makes the organ "come alive" and sound much like a big pipe organ.  
 Organ keyboard (inc contacts), Cat K-6018 ..... \$87.50  
 Set of 50 spare key contacts, Cat K-6019 ..... \$24.50  
 Organ kit (less keyboard), Cat K-3421 ..... \$91.50  
 Organ mini amp, Cat K-3422 ..... \$4.75  
 Reverb kit, Cat K-3424 ..... \$14.75

## DICK SMITH ELECTRONICS GROUP

Head Office: Phone 439 5311. Telex AA20036. Cable 'Diksmi' Sydney.  
 Mail Orders: P.O. Box 747, Crows Nest, N.S.W., 2065.  
 N.S.W. Branches: GORE HILL - 162 Pacific Highway, 439 5311.  
 SYDNEY - 125 York St., 29 1126. BANKSTOWN - 361 Hume Hwy., 709 6600.  
 QLD. - 166 Logan Rd., Buranda, 391 6233.  
 Interstate Branches: VIC. - 656 Bridge Rd., Richmond, 42 1614.  
 PARK IN THE BOULEVARD

**DICK SMITH DEALERS :-**  
**HOBART - Aero Electronics - 34 8232**  
 123 A BATHURST STREET, HOBART, TASMANIA, 7000.  
**DARWIN - Venemon & Wyatt Electronics - 81 3491**  
 24 STUART HIGHWAY, STUART PARK, N.T., 5794.  
 Dick Smith Dealers carry many of our products - Prices may be slightly higher to cover freight costs.





## With these two there is scarcely a radio service job you couldn't handle

The Philips PM 6456 FM stereo signal generator and PM 5324 RF generator are fully compatible instruments for use in workshop or on call. They offer precision and versatility at a remarkably competitive price. With them you are equipped to diagnose practically every problem ever likely to be encountered in AM, FM and stereo servicing. Check these features for yourself:-

### Philips PM 6456 FM stereo generator

- complete stereo signal
- separate L and R signals
- internal LF modulation: 1 and 5 kHz
- external modulation facility
- X-tal controlled pilot
- adjustable amplitude of multiplex signal
- tunable 100 MHz RF signal

### Philips PM 5324 RF signal generator

- frequency range 100 kHz-110 MHz
- X-tal calibration
- special band spread ranges
- high frequency stability
- electronically stabilised output
- calibrated output attenuator
- facilities for internal and external AM and FM
- wobulating with sweep width control
- simultaneous AM and FM
- big easy to read illuminated dial with LEDs to read range

### And servicing TV too... ...with the PM 5334 sweep generator



This highly versatile TV sweep generator allows quick and easy alignment of colour or monochrome receivers in the workshop or on call. Its excellent

specification makes it ideal for service and small production departments, as well as development and educational establishments.

**Features include:** ● radio and TV service equipment 8 frequency ranges, 3 MHz-860 MHz ● sweep frequency adjustable, 8-50 Hz ● one variable and three fixed markers ● signal frequency is highly accurate and thermally stable ● stabilised output into 75Ω load ● built-in floating bias source  
If you would like further information send in this coupon:

Philips Scientific and Industrial Equipment—  
Test & Measuring Instruments:  
P.O. Box 119, North Ryde, 2113.

Please send me further information on:

- PM 6456 FM stereo generator
- PM 5324 RF signal generator
- PM 5334 TV sweep generator

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

TEL. \_\_\_\_\_



**Test and  
Measuring  
Instruments**

# PHILIPS

38.2639



# Circuit & Design Ideas

Conducted by Ian Pogson


Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

## Hee-haw siren for toys

This hee-haw siren was installed in a toy fire engine in order to provide a more interesting realistic toy. Although many siren circuits have been described, this one has the advantage that a wide variety of transistors may be used, and it also provides one or two flashing beacons.

Transistors TR1 and TR2 form a multivibrator with a period of about 0.6 second, flashing the LED beacons and "frequency modulating" the multivibrator formed by TR3 and TR4. TR5 amplifies the output and drives the speaker.

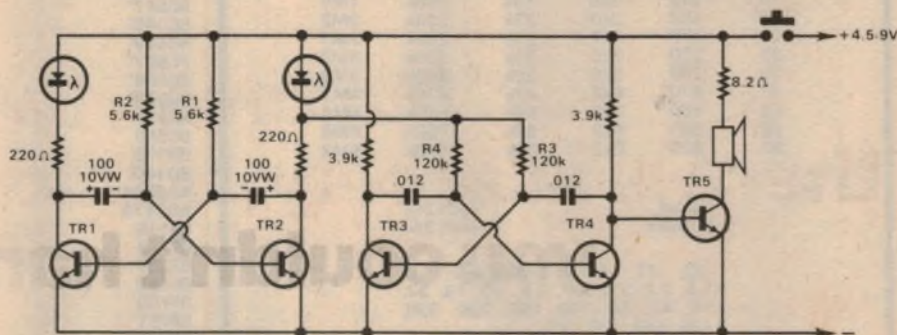In the unit constructed, the output transducer was a telephone receiver insert, which has the advantage of being rugged and waterproof. A small speaker from a scrapped transistor radio could also be used. If a speaker with an impedance greater than 22 ohms is used, the series resistor may be omitted. If only



one beacon is required the LED in the collector circuit of TR1 may be omitted and 220 ohm resistor increased to 560 ohms. A normally open push-button is used as an on/off switch, as this cannot be left on unintentionally by a child.

An intriguing toy may be made by replacing R1/R2 and R3/R4 with 10k and


220k ganged potentiometers respectively and mounting the circuit in a small plastic case. The resultant wide variety of pulsed tones and variable frequency flashing lights can keep children occupied for long periods.

(By Mr A. Ohsberg, PO Box 178, Nedlands, WA 6009.)

## An audio-powered noise clipper

Unlike many noise suppression or clipper circuits which involve complex modifications to the average receiver, this audio powered noise clipper can be quickly inserted in the speaker circuitry. The transistorised audio powered noise clipper, shown in the diagram, is designed to operate in 4 to 8 ohm receiver speaker output circuits. The original circuit was designed to operate in 600 ohm radio telephony circuits. The author added 600-to-8 ohm line transformers for impedance matching and substituted other transistors for the JAN (militarised) transistors.

The use of the 600-to-8 ohm impedance matching transformers provides for two requirements. In order to use this noise clipper in 4 to 8 ohm speaker circuits, an 8-to-600 ohm transformer must be used on the input side and a 600-to-8 ohm transformer must be on the output side. The second need for this change in impedance is that the voltage levels in the 8 ohm circuit may not be high enough to allow the noise clipper to operate effectively. Tests made by the author showed that the voltage clipping level has a minimum level of approxima-

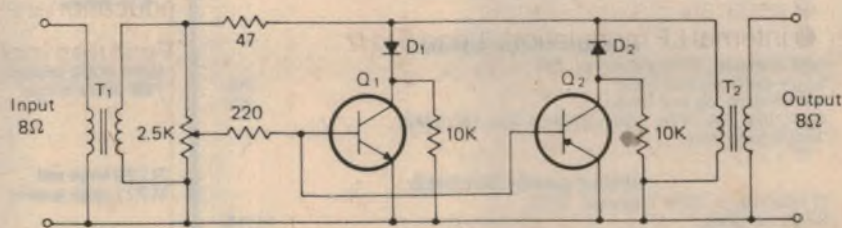

tely 1.5V peak-to-peak.

The circuit is quite straightforward. Two transistors, powered by the audio power contained within the signal, will short out signal peaks which exceed the threshold established by the 2.5k potentiometer. The diodes are used to isolate the positive and negative clipping circuits represented by the NPN and PNP transistors, respectively. The adjustment of the 2.5k potentiometer is left to the discretion of the user. Normally, a desired audio operating level can be established and the potentiometer needs little or no further adjustment. However, it is to be noted that adjusting the potentiometer to a no clipping level effectively removes both transistors from the circuit and the

noise clipper presents very little insertion loss in the speaker audio circuit.

(By Clayton Laster, W5ZPV, in "CQ".)

Editorial note: In the parts list, the author specifies Archer type 273-1379 transformers, or any transistor radio output transformer with 500-to-4 ohms impedance. If neither alternative is available, it is possible that small power transformers, such as Ferguson type PL24/5VA could be used instead. Also type 1N270 diodes are specified. If these are unavailable, then any general purpose germanium diode, such as the 0A91 should be satisfactory. Q1 is a 2N2222 and Q2 is a 2N2907. These should be available but if not, suitable substitutes should be easy to get.



## SPECIAL OFFER

All those returning this square with 90c will receive our new 16 page catalogue plus an 8 pin DIP741 integrated circuit.

# BHN

BOX 787, POTTS POINT 2011

# Electronics Supply Service

### CARBON FILM

½ Watt 3c : \$2.00 per hundred.  
1 Watt 6c : \$5.00 per hundred.

Available in the following values:

10	100	1k0	10k	100k	1M0
12	120	1k2	12k	120k	1M2
15	150	1k5	15k	150k	1M5
18	180	1k8	18k	180k	1M8
22	220	2k2	22k	220k	2M2
27	270	2k7	27k	270k	2M7
33	330	3k3	33k	330k	3M3
39	390	3k9	39k	390k	3M9
47	470	4k7	47k	470k	4M7
56	560	5k6	56k	560k	5M6
68	680	6k8	68k	680k	6M8
82	820	8k2	82k	820k	8M2

5 Watt. each 20c  
10 Watt. each 35c

.33, .47, .68, in 5 Watt only. 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1k0, 1k5, 2k2, 3k3, 4k7, in 5 Watt only

### MINIATURE REPLACEMENT POTS

VC1	5k log with switch, 16mm Dia.	30c
VC2	5k log, switch, National type	45c
VC3	5k log, switch, subminiature	45c
VC4	5k log split knurled shaft	65c

### PRESET POTENTIOMETERS

Screwdriver and hand adjustable, .2 inch pin spacing, .15 Watt. 18c  
100, 220, 470, 1k0, 2k2, 4k7, 10k, 22k, 47k, 100k, 220k, 470k, 1M0, 2M2, 4M7.

### WIRE-WOUND POTENTIOMETERS

Three watt wire-wound potentiometers \$1.95  
10, 22, 47, 100, 220, 470, 1k0, 2k2, 4k7, 10k.

### CARBON TRACK ROTARY

½ hole mount, 20% tolerance, 2W. 40c  
Single gang log and linear  
Double gang log and linear 90c  
4k7\*, 10k, 22k, 47k, 100k, 220k, 470k, 1M, 2M2  
\*Single gang only

### SINGLE GANG SWITCHED

½ hole mount, 20% tolerance DPST. \$1.15  
Single gang log  
4k7, 10k, 22k, 47k, 100k, 220k, 470k, 1M, 2M2.

### CARBON TRACK SLIDER

45mm travel, 20% tolerance, 2W. 75c  
Single gang log and linear  
Double gang log and linear \$1.10  
4k7\*, 10k\*, 22k, 47k, 100k, 220k, 470k, 1M, 2M2  
\*Single gang only

### SLIDER TYPES

30mm travel, 20% tolerance, 2W. 70c  
1k0, 10k, 22k, linear, single.  
1M0, log, single. 70c

### TRANSISTOR LISTING

AC127	65c	TIP32A	80c
AC128	65c	TIP31C	\$1.25
AC187	70c	TIP32C	\$1.25
AC188	75c	TIP33A	\$1.40
AD161	\$1.50	TIP34A	\$1.60
AD162	\$1.50	TIP2955	\$1.00
ASZ15 (OC28)	\$3.40	TIP3055	\$1.00
ASZ18 (OC36)	\$3.40	TT800	95c
BC547*	14c	TT801	95c
BC548*	14c	2N301	\$2.60
BC549*	14c	2N2955	\$2.50
BC557*	14c	2N2102	95c
BC558*	14c	2N2646 (MU10)	80c
BC559*	14c	2N2904	85c
BC639	60c	2N2904A	99c
BC640	60c	2N2905	85c
BD139	75c	2N2905A	99c
BD140	75c	2N3055	\$1.20
BD266A	\$2.50	2N3563	65c
BD267A	\$2.50	2N3564	50c
BF115	75c	2N3566	60c
BF173	90c	2N3568	70c
BF337	\$1.40	2N3569	60c
BF180	\$1.10	2N3638	40c
BFY50	70c	2N3638A	50c
BFY51	70c	2N3642	42c
BFY52	70c	2N3643	50c
MPF102	50c	2N3644	40c
MPF103 (5457)	50c	2N3645	50c
MPF104 (5458)	95c	2N4250	70c
MPF105 (5459)	50c	2N4355	67c
MPF106 (5485)	50c	2N6027 (D13T1)	95c
TIP31A	80c	40411	\$2.50

\*Equivalents may be supplied.

### DIODES

BZX70C8V2 to C75*	70c	A14N 2.5A, 800V	36c
EM404	10c	A15A 5.0A, 100V	30c
EM410	17c	A15 5.0, 600V	69c
OA91	22c	AA119	20c
OA200	25c	BA219	22c
ST2	90c	BYX21L/200	\$2.00
ST4	90c	BYX21L/200R	\$2.00
1N914	7c	BZX79CV7 to C75V*	22c

\*E24 Valves

### BRIDGE RECTIFIER

WO4 400V bridge	\$1.55	PA40	\$5.00
PB8 800V bridge	\$1.85	PB40	\$5.50

### LIGHT EMITTING DIODES

TL220 large red	32c	TL209 small red	22c
TL221 large green	50c	TL211 small green	60c

### SILICON CONTROLLED RECTIFIERS

C106Y1	\$1.00	C230D	\$2.45
C106D1	\$1.20	SC141D	\$1.70
C122D	\$1.95	SC146D	\$1.90

### TRIACS

## NEW RETAIL SHOP . . . NOW OPEN

179 VICTORIA STREET, KINGS CROSS

(JUST DOWN FROM CREST HOTEL)

## ARE YOU DISSATISFIED WITH YOUR PRESENT MAIL ORDER SERVICE—WHY NOT TRY US?

Prompt supply of goods or your money back! Our prices already include pack and post charges, no further charges for delivery within Australia. All items are of top quality and do not include rejects or disposals. Payment may be made by money order, postal note, or crossed cheque, and payment must be sent with order. We are unable to supply COD or accept telephone orders. The minimum mail order value is \$5.00. Many kits and items are available, please enclose stamped addressed envelope for enquiries.







# The National SC/MP

We continue our survey of microprocessors this month with a more detailed look at National Semiconductor's 8-bit SC/MP chip. We also take a look at the low-cost SC/MP evaluation kit, which has already aroused a lot of interest, and its more powerful "big brother" the SC/MP development system.

by JAMIESON ROWE

In addition to the 16-bit PACE microprocessor which was examined in our August issue, National Semiconductor also currently produces an 8-bit chip. This is called SC/MP, which is short for "Simple Cost-effective Micro-Processor" (and pronounced "scamp"). As the name suggests, SC/MP was designed primarily for lower level applications

than PACE; applications where cost effectiveness is a major consideration.

Like the PACE chip, SC/MP is an MOS/LSI device using silicon gate, P-channel technology—although it uses depletion mode devices instead of the enhancement mode devices used in PACE. A faster N-channel version of SC/MP is currently in development, and

is mooted for early in the new year.

The basic architecture of SC/MP may be seen from the diagram on this page. There are a total of 10 internal registers, five of which are 8 bits in length while the other five are 16 bits long. Data input and output takes place via an 8-bit parallel bidirectional bus, while there is a separate dedicated 12-bit address bus.

There is only one nominal 8-bit accumulator register, but this is effectively supplemented for logical and arithmetic functions by the 8-bit extension register. The other 8-bit registers are the status register, the data I/O register, and the instruction register.


Of the five 16-bit registers, one is an output address register which is transparent to the user. The remaining four are pointer registers, one of which is dedicated as the program counter. The other three are available to the programmer as addressing pointers.

As the program counter and pointer registers are 16 bits long, this means that SC/MP has the ability to directly address 65,536 bytes of memory, or "65K". However the chip's address bus handles only the 12 least significant bits, the remaining four bits being multiplexed out of the chip on four of the data bus lines. In addition there is no carry-over to the four most significant bits when the program counter (PC) is incremented, so that memory space is effectively divided into sixteen pages of 4096 bytes each.



Of the 8 bits in the status register, three are used for user flag signals which are made available at device pins. Another two bits are sense bits, again brought out to device pins. One of the sense inputs also serves as an interrupt input if another of the status register bits is set to a 1. The remaining two bits are an overflow bit and a carry/link bit, used for arithmetic and shift-rotate functions.

The SC/MP chip provides five control signals to facilitate data input-output and bus accessing. These are address strobe (NADS), read strobe (NRDS), write strobe (NWDS), bus request (BREQ) and enable outputs (ENOUT). There are also five control inputs, namely reset or initialise (NRST), continue (CONT), bus enable (ENIN), bus busy (BREQ) and extend I/O cycle (NHOLD). Note that the BREQ pin is used for both input and output of control signals.

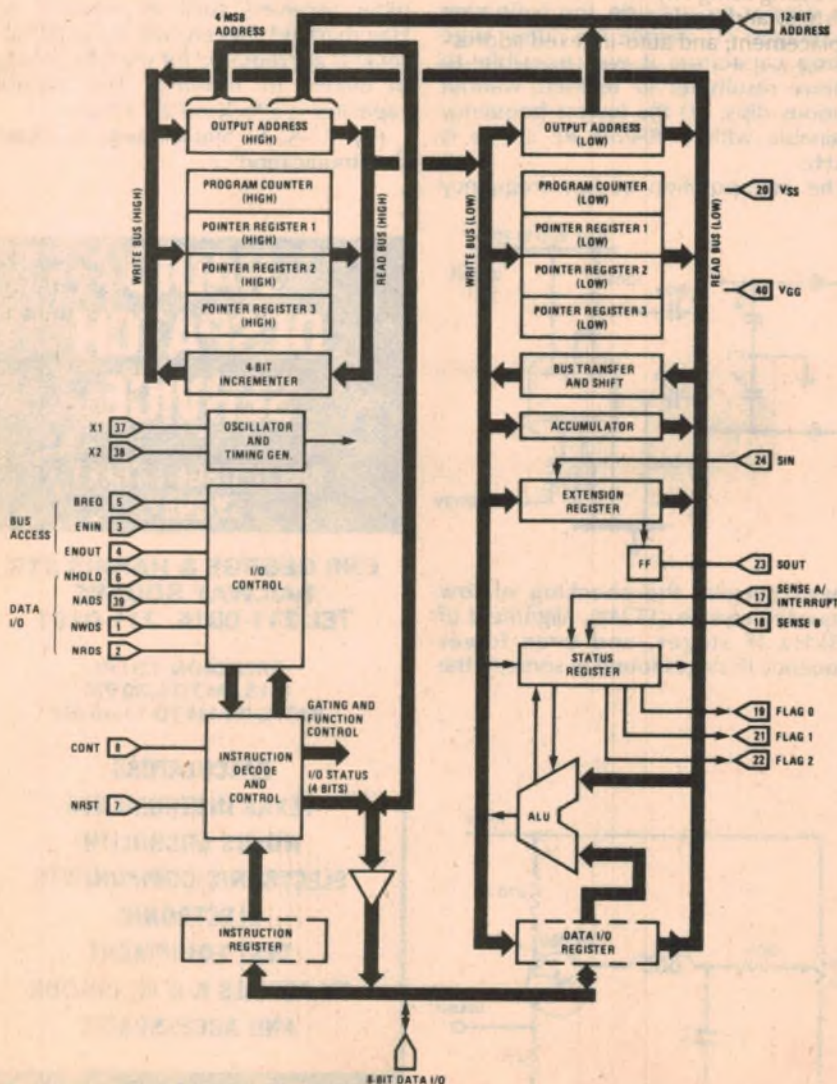At left is the basic architecture of the SC/MP chip, taken from the maker's data.





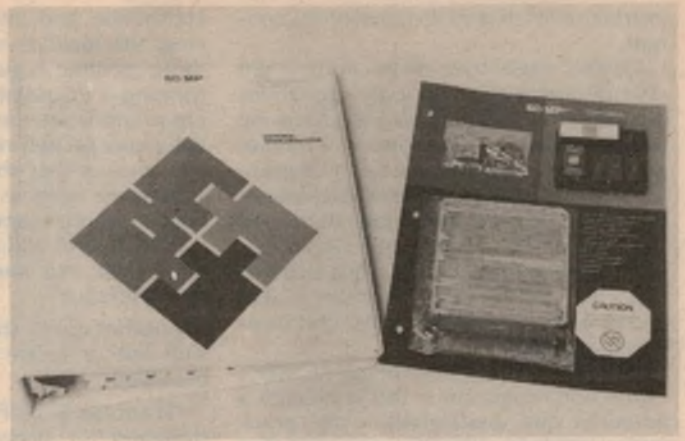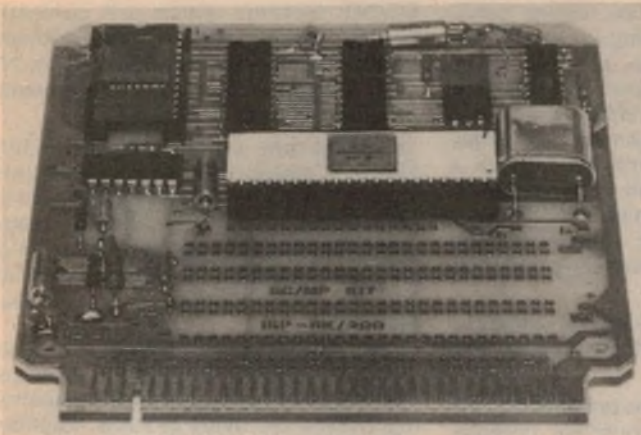


Many of the control signals provided by the SC/MP chip are not required for simple systems, but are used in more elaborate systems for such purposes as direct memory access (DMA) and similar operations.

SC/MP has its own internal clock oscillator, which can use either a capacitor or a quartz crystal for timing as required. Alternatively the oscillator can be disabled and the chip fed from an external clock source, via the two timing terminals.

In short, then, the SC/MP chip is quite a flexible 8-bit microprocessor. While designed primarily to make it capable of forming the heart of low cost minimal-device controllers and dedicated systems, it is also provided with many of the facilities required for more elaborate systems.

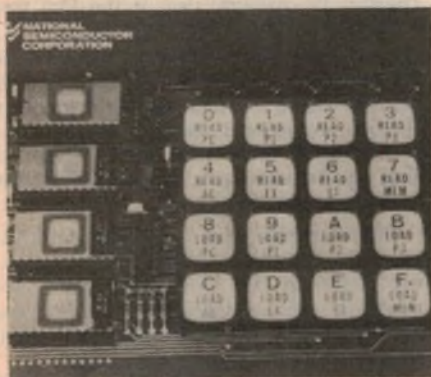On the software side, SC/MP has a repertoire of 46 basic instructions of which 22 are 2 bytes in length, and the rest are a single byte. Fourteen of the 2-byte group are memory reference instructions, and comprise load, store, AND, OR, exclusive-OR, decimal add, add, complement and add, increment and load, decrement and load, jump, jump if positive, jump if zero, and jump if not zero.



At right is a view of the larger SC/MP development system, with a close-up of its keyboard and EPROMs shown above.

Above is the low-cost SC/MP evaluation kit as it comes, while at left is a view of the assembled PC board. An edge connector is supplied.


Each of these fourteen instructions may use one of three addressing modes. These are PC-relative addressing with a signed 8-bit displacement (giving a range of from -128 to +127, decimal); indexed addressing using any of the three pointer registers, and again with a signed 8-bit displacement; and auto-indexed addressing where the pointer register is either post-incremented or pre-decremented depending upon the sign of the 8-bit displacement.

In addition to these normal memory reference instructions there are no less than seven immediate-addressing instructions, wherein the data or mask operand is contained in the second byte of the instruction itself. The seven instructions are load immediate, AND

immediate, OR immediate, exclusive-OR immediate, decimal add immediate, add immediate, and complement and add immediate.

Note that both the normal complement-and-add instruction and the complement-and-add immediate instruction may be used for 2's complement subtraction, by setting the carry/link bit beforehand.

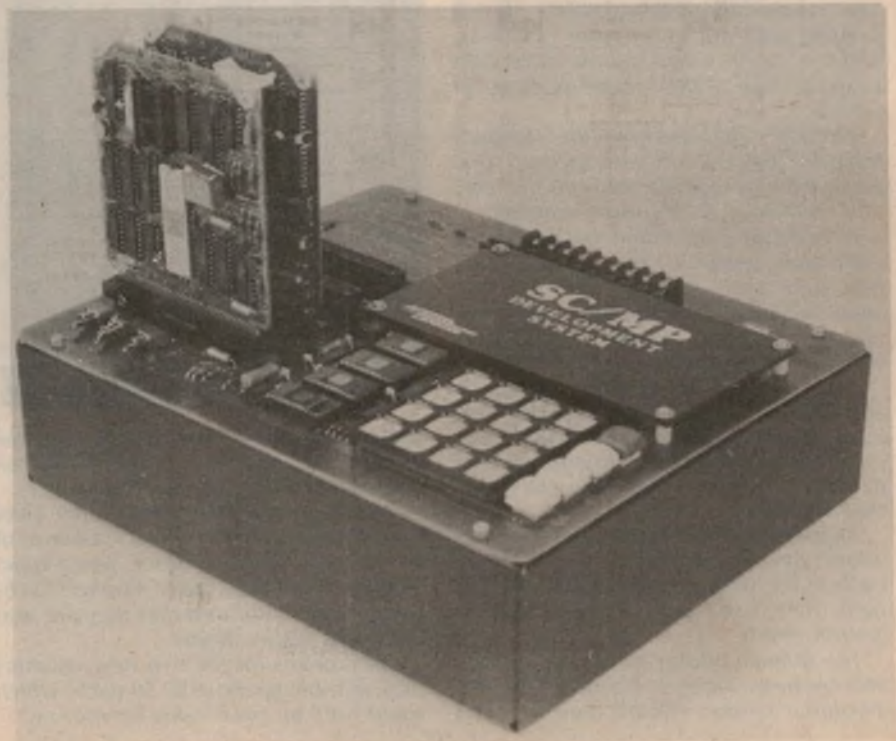The remaining double-byte instruction is a delay instruction. This may be used to provide programmable delays of from 13 to 131,593 machine microcycles, or from 26 microseconds to 263.186 milliseconds with a 1MHz clock. The delay is a function of both the displacement in the second byte of the





instruction itself, and the current AC content.

Of the single-byte instructions, eight provide arithmetic and logic operations involving the accumulator and extension registers. Three more provide pointer register move operations, to cover pointer loading and PC-pointer exchanges. Five more provide shift, rotate and serial I/O operations, while the remaining eight provide miscellaneous instructions: halt, clear and set carry, interrupt enable and disable, copy status to AC and vice-versa, and NOP.

Overall, our impression of SC/MP's instruction repertoire is that it is quite a powerful one, particularly in the arithmetic and logic function area and that involving immediate instructions. These plus its "special features" such as the delay instruction and the inbuilt serial I/O would make it very well suited to dedicated computer and controller applications.

It would be less suitable for general-purpose computer applications, due to a number of limitations. One is the lack of true absolute addressing. Another is the relatively clumsy way it handles

subroutine and interrupt routine servicing; this involves setting up one of the three pointer registers, and then performing a PC-pointer exchange to both enter and leave the routine. Apart from tying up a pointer register each time, this also means that the machine leaves a subroutine with its exit address in the pointer, so that subroutines which are to be called over and over must effectively have their exit immediately preceding their entrance!

Another minor shortcoming is that no shift left or rotate left instructions are provided.

Of course SC/MP was presumably not designed for general-purpose computing, so these criticisms must be judged accordingly. It is also true that given almost any instruction set one can write almost any program, once one gets fully familiar with its strengths and weaknesses. With most of us the main limitation on our programming is likely to be our own skill, whatever the chip we elect to use!

Having looked at the SC/MP chip itself, let us now look at the two small

SC/MP systems which are currently available from National Semiconductor. In Australia these are available from NS Electronics Pty Ltd, or in one-off quantities through their distributors.

The system which is more widely known at present is the low-cost "SC/MP Kit", which is a minimal-system do-it-yourself evaluation kit. It comes as a large ring binder containing a complete set of parts in a blister pack, together with full assembly and programming information.

The assembled kit forms a very basic system, but one which is quite sufficient to allow development of small programs. It provides 256 bytes of RAM, together with 512 bytes of ROM containing "Kitbug"—a very basic monitor-debug program. The kit provides a 1MHz crystal for the SC/MP clock, together with the interfacing circuitry required to communicate with an ASCII teleprinter or similar 110-baud asynchronous serial terminal using a 20mA current loop.

The kit requires an external power supply providing +5V at approximately 350mA, and -12V at 200mA.

There are only three commands recognised by Kitbug: Type (T), Modify (M) and Go (G). The T command causes printout of successive memory locations and their contents, in hexadecimal, until a keyboard input is detected. The M command is similar, except that it types out a single location and provides for modification of the contents followed by either a return to Kitbug, or progression to the next location. This is the command used to load programs into the kit, and also the means for setting up the starting address and initialising the SC/MP registers prior to running. Finally the G command transfers control to the user's program, to run it.

A fourth command can be simulated, namely a user's program halt which transfers control back to Kitbug. This may be done only where the user's program does not disturb the contents of pointer register P3, making use of the fact that Kitbug stores its own return address in that register when it transfers control to the user's program. Hence by inserting an "exchange PC with P3" instruction in the user's program, control may be transferred back to Kitbug when required. This can be used as a simple breakpoint system when debugging.

Price of the low-cost evaluation kit is currently quoted as \$79.95 plus tax, making it the lowest cost microprocessor evaluation kit available and the cheapest possible way of acquiring practical experience with microprocessors.

The more elaborate of the two SC/MP systems currently available in Australia is the Low Cost Development System or "LCDS", which as the name suggests is

## EXCELLENT TEXT ON MICROPROCESSORS

**AN INTRODUCTION TO MICRO-COMPUTERS**, by Adam Osborne. Published by Adam Osborne and Associates, Inc, 2950 Seventh St, Berkeley, California. Soft covers, 133 x 206mm, about 380pp. Price in US \$7.50.

*In the last year, this book has apparently broken just about all previous US sales records for technical books. Its first printing sold out in a matter of weeks, and we had to wait a couple of months to get a copy of the second printing for review.*


*Already it has become the standard introductory text on microprocessors, and is used by many factory-run seminars and courses as an accompanying text.*

*Actually we understand that due to the enormous response, the original book has just been expanded into two separate volumes. By the time this review appears, the two volume version may well be the only one available.*

*The original book is divided into two sections: an introductory section which leads the reader through all the basic concepts of microprocessors in general, and then a survey of specific chips and their features.*

*Apparently the new 2-volume version adopts the same approach, but by giving each of the two sections a volume of its own, they have both been treated in greater depth.*

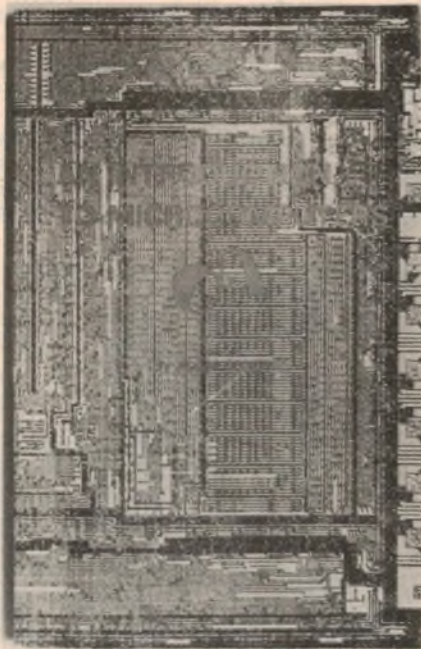*The original book is very well written, and has been widely acclaimed. The new 2-volume version should thus be even*



*better, and an excellent book for anyone looking for a good up-to-date text on microprocessors and microcomputers.*

*We understand that Dick Smith Electronics have supplies of both volumes of the new version on order, and expect supplies by mid-October. Applied Technology have indicated that they are also obtaining stocks shortly.*

*Local prices for the two new volumes look like being about \$7.50 each, which should still be good value for money.*



intended not so much as an evaluation kit, but as a small system for the development of programs and application systems.

The basic LCDS consists of a base supporting a large PC mother board, on which are mounted four 72-way edge connectors together with a small keyboard array, a display panel with six 7-segment LED readouts, and various other ICs including four 512-byte PROMs with a resident monitor-debug program. With the assembly comes a plug-in PC card which provides the SC/MP CPU, its clock, a 256-byte RAM and a full complement of buffers for all data, address and control lines.

Hooked up to a +5V/-12V power supply, the basic LCDS forms a limited but self-contained system using the on-board keyboard and LED display for communication. However the resident monitor-debug firmware also has provision for asynchronous serial interfacing, so that it is only necessary to connect up a teleprinter or similar terminal in order to begin more serious development work.

In teleprinter mode, the LCDS resident debug program has a powerful set of functions: It can type out the contents of all SC/MP registers, alter any of these contents at will, type out memory locations singly and modify these at will, type out sections of memory, set or remove a breakpoint, punch a selected range of memory into paper tape, load a program into memory (either the original locations, or into another area as required), and initiate execution.

The basic LCDS thus forms a more powerful "big brother" to the small evaluation kit, and as such is much more suitable for serious development of SC/MP programs.

Of course the 256-byte RAM provided on the basic CPU card is a limitation when it comes to developing larger programs. Accordingly National make available two further types of plug-in card, which may be purchased separately and plugged in as required to expand the system. One card provides an additional 2k bytes of RAM, while the other provides sockets for up to 4k of ROMs or PROMs. Both cards may be programmed using wire links to respond to a specific range of addresses in the total SC/MP memory space, so that a number of cards may be used to expand the system as far as required.

Price of the basic LCDS system complete with the CPU card is currently quoted at \$405 plus tax. The optional 2k byte RAM cards are quoted at \$130 each plus tax, while the 4k ROM/PROM card (less ROMs or PROMs) is \$100 plus tax.

NS Electronics kindly made available to us one of the SC/MP kits for evaluation, and the author was able to put it

```

200 C4 01 LDI 01 /SET UP P3 FOR CALLING GECO
202 37 XPAH P3
203 C4 65 LDI 65
205 33 XPAL P3
206 3F XPPC P3 /GO LOOK FOR INPUT CHAR, ECHO
207 E4 0D XRI 0D /CR? (AC WILL HAVE ZERO IF YES)
209 9C FB JNZ (PC)-5 /NO; KEEP GOING
208 C4 C4 LDI C4 /YES; SET UP P3 FOR CALLING PUTC
20D 33 XPAL P3
20E C4 0A LDI 0A /GO PRINT LF
210 3F XPPC P3
211 C4 02 LDI 02 /SET UP P1 AS ANSWER POINTER
213 35 XPAH P1
214 C4 25 LDI 25
216 31 XPAL P1
217 C1 00 LD (P1)+0 /FETCH ANSWER CHAR
219 3F XPPC P3 /PRINT
21A C5 01 LD # (P1)+1 /FETCH CHAR AGAIN, INCREMENT PTR
21C E4 0D XRI 0D /CR?
21E 9C F7 JNZ (PC)-9 /NO; KEEP GOING
220 C4 0A LDI 0A /YES; PRINT LF
222 3F XPPC P3
223 9D DB JMP (PC)-37 /RETURN TO LOOK FOR NEW INPUT

225 47 4F 20 /START OF ANSWER BUFFER
228 41 57 41
22B 59 2C 20
22E 49 27 4D
231 20 42 55
234 53 59 21
237 0D /ANSWER MUST END WITH A CR

```

TO RUN IN SC/MP KIT, PUT SA OF 200 IN PC STORAGE LOCATIONS 2F7 AND 2F8, THEN GIVE "G" COMMAND TO KITBUG

Written for the low-cost SC/MP evaluation kit, this simple answer-back program utilises the TTY servicing routines in the Kitbug ROM.

together and gain "hands-on" experience with a minimum SC/MP system.

The assembly instructions which come with the kit are quite explicit, and I found no difficulty putting it together. Just to be safe I observed the usual precautions when soldering in MOS devices, but even this is really only necessary with the RAM devices because both the SC/MP chip itself and the ROM are provided with sockets.

In operation the Kitbug program provides pretty basic debug facilities, but once you get used to it you can develop small programs fairly easily. Out of interest I developed a novelty "answer-back" program, to duplicate the one I did for the 2650 system described last month. Again this was interesting, as the program makes use of the teleprinter servicing routines in Kitbug.

The program went together fairly easily, once I got used to the slightly tricky aspects of SC/MP subroutine servicing. It is reproduced here in the article so that readers can try it out if they feel so inclined.

NS Electronics also very kindly loaned us one of the LCDS development systems, partly to allow us to compare it with the smaller system, and partly to assist in our development of a project we have been putting together based on a SC/MP kit.

The LCDS system was complete with

one of the 2k-byte RAM cards, and when I "fired it up" the increased flexibility compared with the small kit quickly became apparent. Not surprisingly, it is much easier to develop programs when you can dump and load them conveniently using paper tape, and when you can quickly insert and remove breakpoints in the program to check out sequences and isolate bugs.

In fact I found the LCDS a very convenient development system, and one which makes development of SC/MP programs a very efficient and smooth business. At the price asked, it should be a very attractive investment for anyone intending to do serious development of SC/MP programs and systems.

Both the SC/MP evaluation kit and the LCDS system components should be available in all states via NS Electronics distributors. If you require further information, this should be available from NS Electronics at either Cnr. Stud Road and Mountain Highway, Bayswater, Victoria 3153, or 2-4 William Street, Brookvale, NSW 2100.

**PACER PRICE:** NS Electronics has advised that the prices quoted for the PACER system, and given in our August article, were in error. The actual price for the unassembled unit is \$728 plus tax, while the assembled unit is \$833 plus tax.





# SC/MP Low Cost Development System

The SC/MP Low Cost Development System (LCDS) is a simple controller configured to provide maximum flexibility at affordable cost. It provides all the features necessary for development and testing of SC/MP hardware and software designs for a user's applications.

The minimum SC/MP Development System is configured with a SC/MP

CPU Card plugged into one of four sockets in a Card Bus on a 10" x 12" motherboard. Also on the motherboard are a 16 key, dual-function, hexadecimal keyboard; four function keys; 3 control switches and a 6 digit hexadecimal display.

Control logic, scratchpad memory, and ROM based firmware on the motherboard allow the user to

examine and alter the SC/MP registers, examine and alter memory locations, run SC/MP programs in continuous or single instruction mode or operate with an optional Teletype® using SC/MP DEBUG.

## FEATURES

Salient operating characteristics of the major items comprising the LCDS are as follows.

### SC/MP CPU Card

The basic block diagram of the SC/MP CPU card (ISP-8C/100) is shown in Fig. 2. It provides the CPU interface for execution of user-generated application programs and development system resident firmware.

### Pre-wired Application System Interface

Four prewired 72-pin edge connector sockets provide a plug-in interface for SC/MP family cards and permit interconnection of additional SC/MP applications hardware via user fabricated cabling. A fifth 72-pin edge connector can be added by the user. In addition, a flat cable connector can be added for coupling to an external card cage.

### Interface Logic

Provides control and monitor functions that permit transfer of control between development system resident firmware and user-generated application programs.

### Development System Resident Firmware Program

This firmware contains subroutines that permit entry of software debug commands via the programmer's control and display panel, or an optional Teletype.

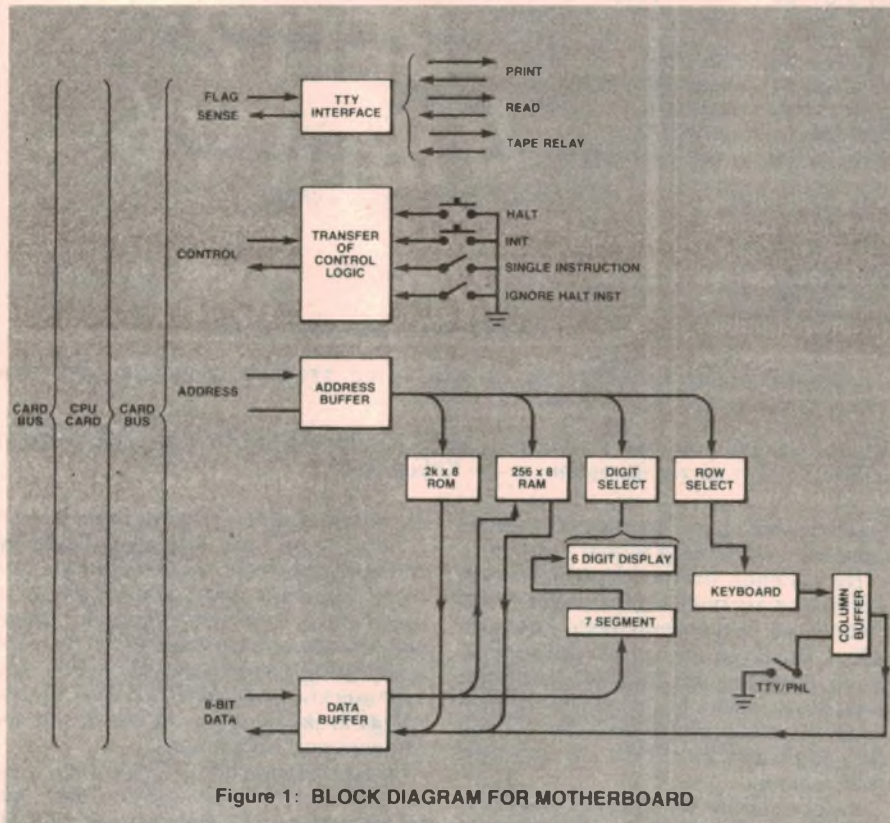


Figure 1: BLOCK DIAGRAM FOR MOTHERBOARD

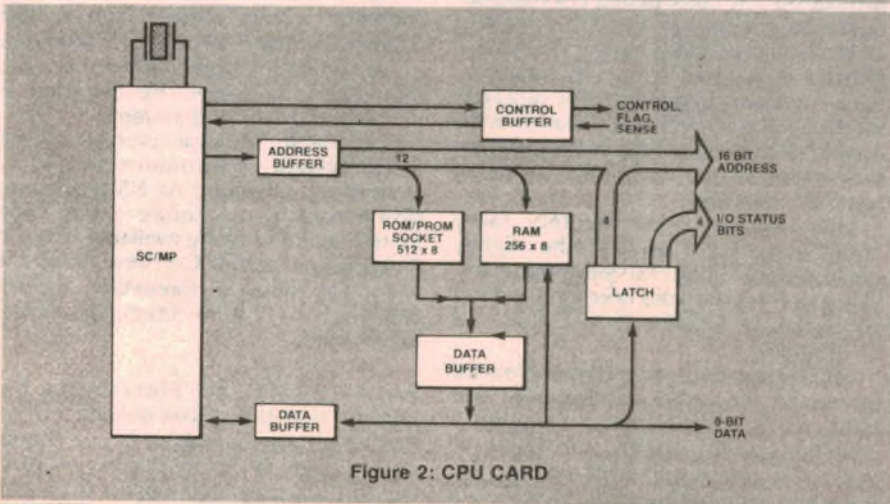


Figure 2: CPU CARD



For further information contact NS Electronics Pty. Ltd. Melb (03) 729 6333, Syd



## Programmer's Control and Display Panel

Provides the following software debug capabilities:

- Display contents of SC/MP program counter, registers, and accumulator in hexadecimal format.
- Alter contents of SC/MP program counter, registers and accumulator.
- Display contents of any memory location in hexadecimal format.
- Alter contents of any memory location.
- Initiate execution of user-generated application program at any memory address.
- Select single instruction or normal execution of user generated application program.
- Interrupt execution of user-generated application program at any point.

## Expanding the SC/MP Low Cost Development System

National Semiconductor offers various cards which may be used in conjunction with the SC/MP LCDS System. The 2K x 8 Read/Write Memory Card (ISP-8C/002) and the 4K x 8 ROM/PROM Card (ISP-8C/004) can be used to provide additional memory for user application or system development.

The standard Cards can be plugged into any of the connectors on the Card Bus. The bus is easily expanded by use of flat-cable to external user supplied modules.

Typical use of the system provides capability to debug user systems with program in RAM, using features of DEBUG such as single instruction or

breakpoints. Changes to the program can be made directly from the keyboard or teletype. When the program is running correctly, it can be dumped to paper tape for programming ROM or PROM.

## Ordering Information



The SC/MP LCDS and supporting cards may be ordered directly from National Semiconductor or National's franchised distributor near you.

<b>SC/MP Development System (includes one CPU Card)</b>	<b>ISP-8P/301</b>
<b>SC/MP RAM Card (2K x 8)</b>	<b>ISP-8C/002</b>
<b>SC/MP ROM/PROM Card (4K x 8) (includes eight 5204 PROMs)</b>	<b>ISP-8C/004P</b>
<b>SC/MP ROM/PROM Card (4K x 8) (without PROM Memory)</b>	<b>ISP-8C/004B</b>
<b>SC/MP CPU Card</b>	<b>ISP-8C/100</b>
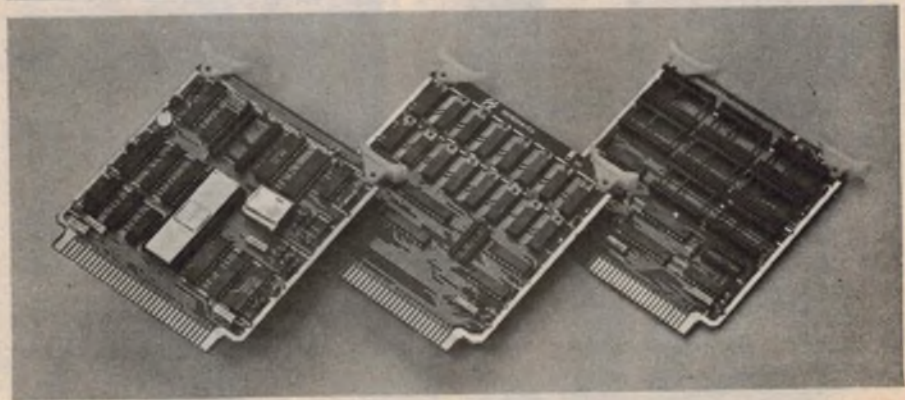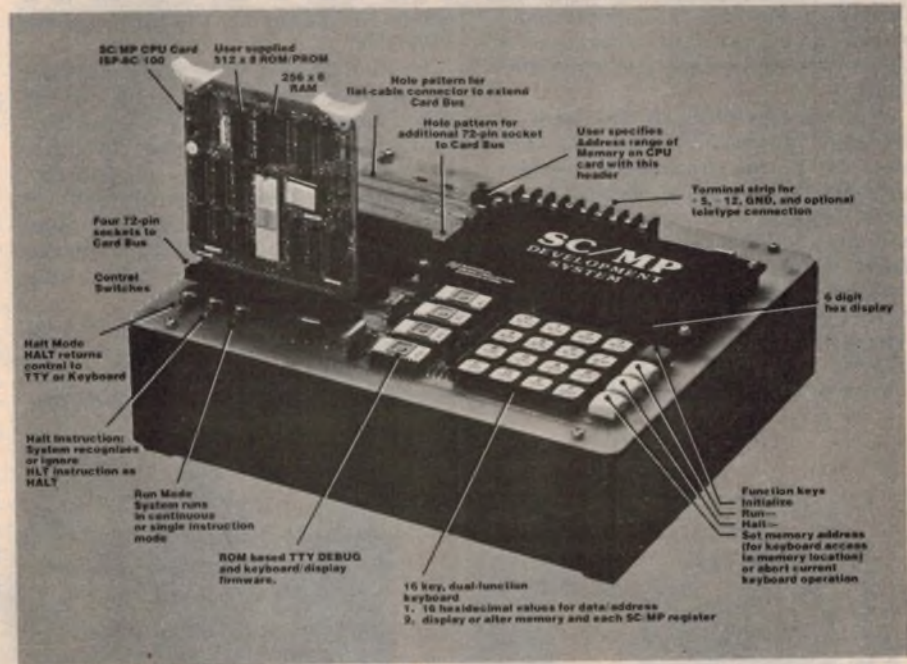
## Teletype Interface

Provides standard 20-milliampere interface for interconnection of optional Teletype. Expanded software debug capabilities associated with teletype option include:

- Print contents of SC/MP program counter, registers, and accumulator
- Alter contents of SC/MP program counter, registers, and accumulator
- Print contents of any single memory location or selected range of memory locations
- Alter contents of any memory location or selected range of memory locations
- Set a breakpoint halt in RAM for user-generated application program
- Initiate execution of user-generated application program at any memory address
- Save application program by punching selected memory range to paper tape
- Load development system generated paper tape into memory
- Load IMP-16 or FORTRAN Cross Assembler generated paper tape into memory.



(02) 93 0481; Q1d (07) 36 6604; WA (092) 25 5722; SA (08) 46 3929; Tas (002) 44 1337; NZ 491 282



*First project using a dedicated microprocessor:*

# ASCII-Baudot translator

As far as we know this project is a world first—the first electronics construction project based on a dedicated microcomputer. Built around a SC/MP evaluation kit, it forms a "black box" which can interface a low-cost surplus Baudot teleprinter to any computer or microcomputer system requiring a 110-baud ASCII teleprinter. It should interest anyone looking for a way of "talking to" one of the new low-cost microcomputer systems at low cost.

by JAMIESON ROWE

Like most small mini-computers, most of the microcomputer evaluation kits and development systems currently becoming available have been designed to converse with the user via a computer-type teleprinter such as the well-known Teletype model ASR-33. Communication is via 20mA current loops, at a rate of 110 bauds (bits per second), and in the ASCII code.

While teleprinters of this type are available fairly readily in the USA, where most of the microprocessor systems originate, they are not at all easy to come by in Australia. New, they are likely to cost you something like \$1500 plus tax—hardly within the grasp of the average small user or would-be computer hobbyist, and rather out of proportion to the current cost of a typical microprocessor system.

Very few machines have appeared

from time to time on the second-hand market, but even these have been relatively expensive. You could expect to pay anything from \$400 up, depending upon condition. This is still rather a lot to pay if one wants to use it to talk to a microcomputer kit costing around \$100-200!

In contrast with these computer-type teleprinters, quite good supplies of the older Baudot-type teleprinters are currently available at much lower cost, from firms dealing in surplus equipment. Machines of British, German and US manufacture are available, most of them having been sold as obsolete plant by the Army, Telecom and other public utilities.

For example you can currently pick up a Teletype model 15 page teleprinter for around \$100, or a model 14 typing reperforator for about half that price. Similarly,

Creed model 7A page teleprinters are available at about \$120.

These machines are obviously quite attractive in terms of price, compared with the computer-type machines. However, they are not directly compatible with the majority of computer systems, for a number of reasons. The most obvious of these is that they use the 5-level Baudot code, instead of the 7-level ASCII code.


In itself, this is not an insurmountable problem. Code translation can be performed using suitable ROMs, although even this is not as simple as one might expect. This is because Baudot code is really a 6-bit code in which the normally missing 6th bit is effectively sent only when it changes value. It is sent in encoded form as special "letters" and "figures" characters, so that any code conversion system must be capable of performing the appropriate storage and "housekeeping" functions.

Quite apart from the problems associated with code translation as such, there is also another problem: speed. Computer-type machines mostly run at 110 bauds, and with a total of 11 bits per character, this gives a maximum character rate of 10 per second. In contrast, Baudot machines typically run at 50 bauds, and with a total of 7.5 bits per character, this gives a maximum character rate of around 6.5 per second.

In fact, because of the need to send the special "LTRS" and "FIGS" characters interspersed with the actual characters, the maximum character rate of 50-baud Baudot machines in practice is nearer 5 per second—less than half that of a 110-baud computer teleprinter.


The difference in speed doesn't pose a problem for "inward" data flow, from the teleprinter keyboard to the computer system, because here the speed differential assists rather than opposes. However, the problem comes with "outward" data flow, from the computer system to the teleprinter print mechanism. The system is geared to output characters at a rate of 10 per second, while the Baudot printer can only "digest" them at a rate of about 5 per second.

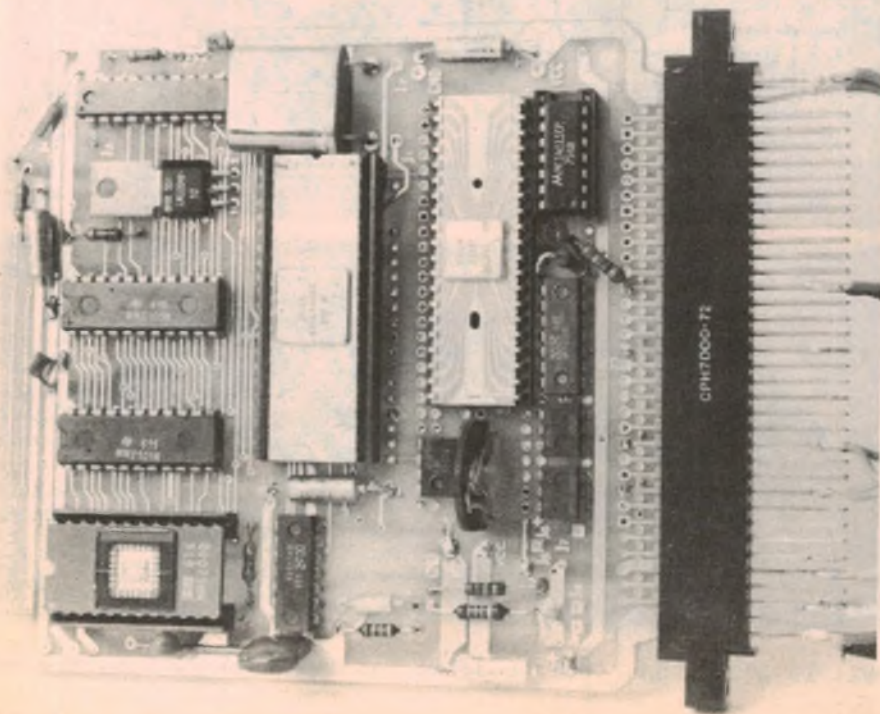As a result, it becomes necessary to provide temporary storage or "buffering", between the system output and the printer. The buffer must be of the "first-in-first-out" (FIFO) type, capable of accepting characters at the high rate,



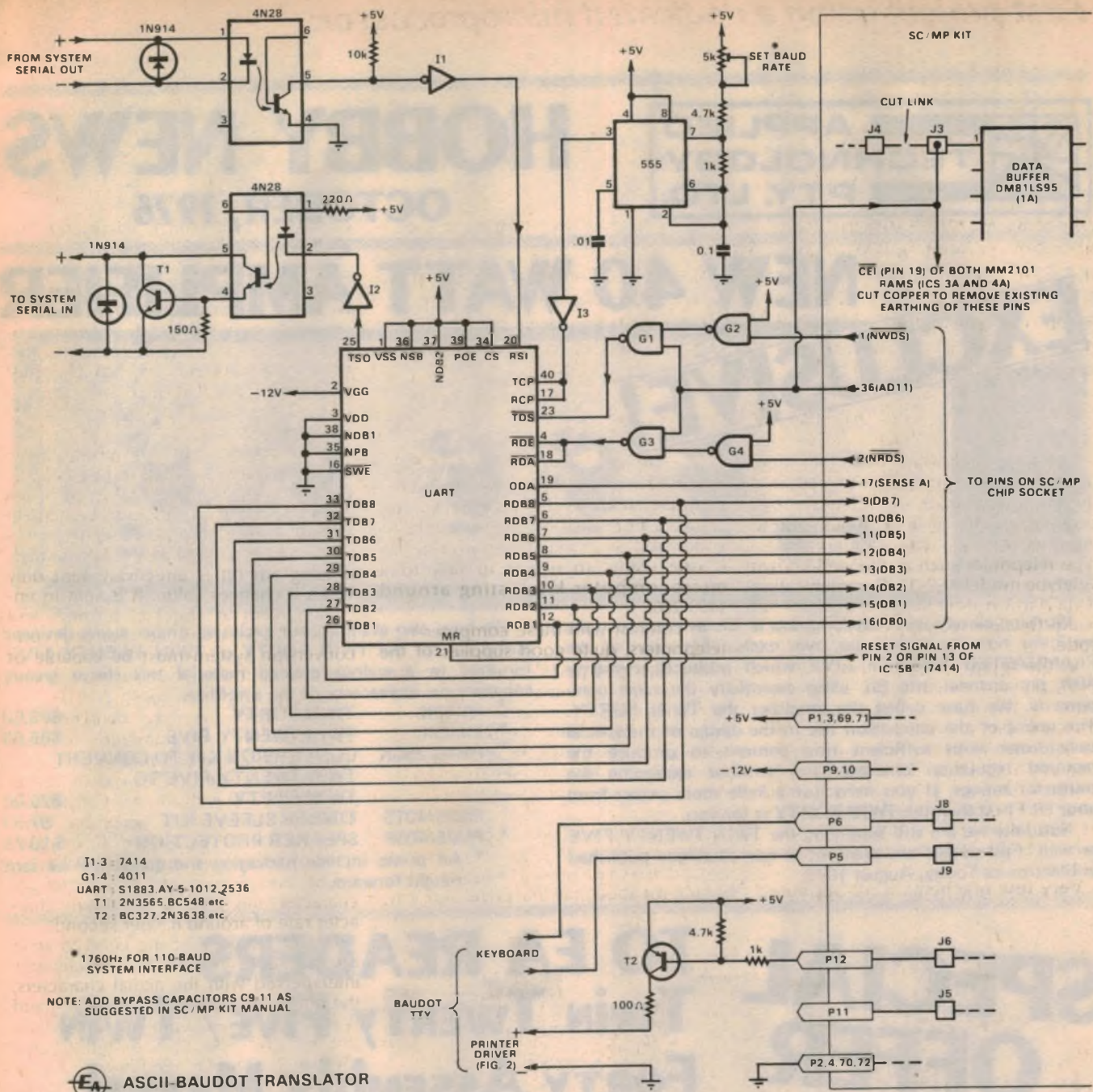*A view of the ASCII-Baudot translator, built up on the SC/MP kit PC board.*





supplying them at the slow rate, and accumulating the difference as required.

Hopefully you can see from all this that interfacing a surplus Baudot teleprinter to a microcomputer system isn't exactly the proverbial "piece of cake". There are quite a few functions to be performed, and to do the job with a conventional wired logic circuit would involve quite a lot of ICs and a complex PC board.

Happily, thanks to modern IC technology there is now an easier and more elegant way of doing the job. This is to use one of the low-cost microprocessor evaluation kits currently available, and turn it into a dedicated "black box".

This is the approach I have taken, and the ASCII-Baudot translator which will now be described is based on the SC/MP

evaluation kit currently selling for around \$80 plus tax.

On the hardware side, most of the functions of the translator are performed by the basic SC/MP kit circuitry. However, six additional ICs are required, along with two transistors and a hand-full of minor components. Most of these fit on the spare space provided on the SC/MP kit PC board.

The main supplementary IC required is a UART (universal asynchronous receiver-transmitter), which performs the 110-baud ASCII interfacing to the main computer system. The UART may be an S1883 (American Micro-systems Inc), an AY-5-1012 (General Instruments), a 2536 (Signetics), or any other exactly equivalent device. Note that not all UARTs cur-

rently available are exactly equivalent to these, however.

A 555 timer IC is used to generate the 1760-Hz clock signals required by the UART. Two 4N28 or similar low-cost opto-couplers are used to perform the actual interfacing to the main computer, to ensure that the translator is fully compatible with all systems designed for 20mA current loop signals. Transistor T1 is used to boost the current switching ability of the outgoing opto-coupler.

Schmitt trigger elements I1, I2 and I3 are used for inversion and signal squaring, while gates G1-4 are used to perform address decoding for the UART so that it effectively occupies location FFF in the SC/MP memory space. Transistor T2 is used to perform interfacing between the





# HOBBY NEWS

OCTOBER, 1976

## NEW 40 WATT AMPLIFIER

**EXCLUSIVE!**



Working closely with Leo Simpson at Electronics Australia we have now developed our own exclusive version of the PLAYMASTER TWENTY FIVE which produces a mighty 40W per channel into  $8\Omega$  using essentially the same components. We have called the amplifier the TWIN FORTY. The secret of the conversion lies in the design of the special transformer with sufficient iron content to produce the required regulation characteristics without exceeding the transistor ratings. If you need just a little more power from your HI FI rig then the TWIN FORTY is for you.

Naturally we are still supplying the TWIN TWENTY FIVE as well. Full details are available in our catalogue published in Electronics Today, August 1976.

We have also available our exclusive timber sleeve designed especially for the TWIN FORTY or TWIN TWENTY FIVE. Finished in a walnut grained material this sleeve greatly enhances the appearance of the amplifier.

- \* PM40K TWIN FORTY \$99.50
- \* PM25K TWIN TWENTY FIVE \$85.00
- \* PM40/25CK CONVERSION KIT TO CONVERT TWIN TWENTY FIVE TO TWIN FORTY \$25.00
- \* PM25/40TS TIMBER SLEEVE KIT \$7.50
- \* PM25/40SP SPEAKER PROTECTION \$10.75

\* All prices include packaging and goods will be sent freight forward.

## SPECIAL OFFER

## TO EA READERS TWIN TWENTY FIVE / TWIN FORTY ASSEMBLY MANUAL

### ANNOUNCEMENT - SATURN 5 TV GAME

The demand for Saturn 5 TV Games kit has been so great that the current backlog of orders has resulted in a delay of 6 weeks in supply. We regret that we can accept no new orders postmarked after September 30, 1976 as it is becoming increasingly difficult to purchase the CMOS devices required. We trust you will understand . . . .

We have now redesigned and reprinted our STEP-BY-STEP assembly manual which describes the construction of these exciting amplifiers. This manual includes a unique colour coded assembly drawings and a detailed troubleshooting guide written by our own engineers. If you are even contemplating building one of these exciting amplifiers the manual is a must.

As a customer service we are prepared to supply these manuals FREE TO ALL readers (limit one per reader) please enclose 50c to cover postage. The offer expires November 30, 1976.



POSTAL ADDRESS: THE ELECTRONIC MAILBOX, P.O. BOX 355, HORNSBY 2077.  
WAREHOUSE & SHOWROOM: 109-111 HUNTER STREET, HORNSBY, N.S.W. 2077.  
Telephone: 476 3759 476 4758

TRADING HOURS: 9-5 WEEKDAYS, 9-12.30 SATURDAY



existing serial output of the SC/MP kit and the driver in the Baudot teleprinter.

Most of the signals required for the additional circuitry are taken from various pins on the SC/MP chip socket, on the kit PC board. However, there are also three small modifications which must be made to the basic kit board. All three are to ensure that the RAMs and ROM are disabled whenever SC/MP addresses the UART.

One of the three modifications is quite straightforward. It involves cutting the link provided in the PCB pattern between pads J3 and J4, adjacent to pin 1 of the DM81LS95 data buffer IC. A wire is then added to the board so that it connects pin 1 of the IC to pin 36 of the SC/MP socket. This causes the data buffer to be disabled whenever address bit AD11 is high, corresponding to the UART being addressed.

The other two modifications are similar, but a little more tricky in the mechanical sense. The PCB copper pattern on the kit normally earths pin 19 of both MM2101 RAMs, but the translator uses these pins to prevent the RAMs from writing when the UART transmitter is addressed. Accordingly the copper laminate should be removed from around the pin 19 hole for both ICs (preferably before the ICs are mounted on the PCB). This allows the pins to be wired as before to pin 36 of the SC/MP socket, so that both RAMs are disabled when the UART is addressed.

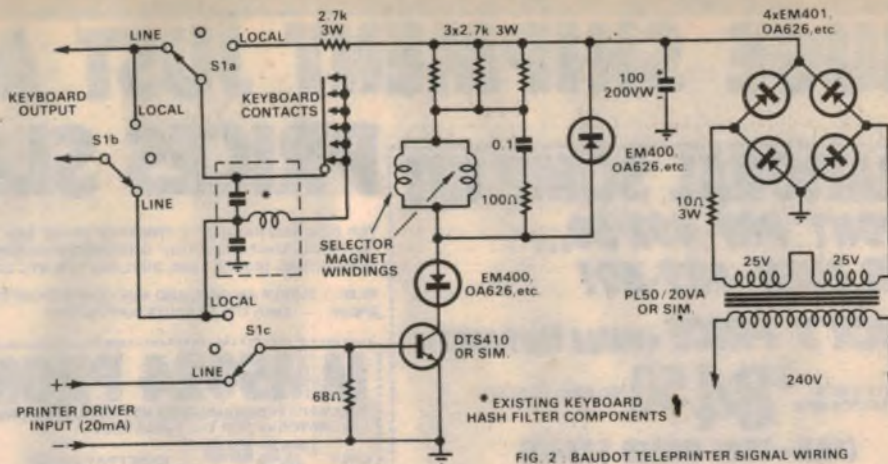


FIG. 2 BAUDOT TELETYPE SIGNAL WIRING

The only other change required to the basic SC/MP kit to convert it into the translator is replacement of the original 512-byte ROM containing "Kitbug", with a pin-compatible EPROM containing the ASCII-Baudot translator program I have written. The EPROM required is the National Semiconductor MM5204, and it may be ordered from the various NS distributors with the translator program resident.

The program is actually "Mark 7", or the seventh version—it took a while to come up with a program which did all the right things at the right times, and would interface to all systems!

Actually I obtained good results with "Mark 4", but it used the reverse interfac-

ing scheme to that shown here—the UART was used for interfacing on the Baudot side, with the SC/MP program performing the ASCII side interfacing. The only problem with this arrangement was that it wasn't capable of receiving an ASCII character while it was sending one; this caused problems when it was connected to computer systems which "echo" keyboard input on a bit-by-bit basis rather than on the more usual whole-character basis. So I finally elected to reverse the system of interfacing, and rewrite the whole program, in order that the translator would be fully compatible with all systems.

The complete final program fits into 512 bytes, including its lookup table of ASCII-Baudot code equivalents. It uses the first six addresses in the SC/MP kit RAMs as a "stack", for storage of counters and pointers, leaving the remaining 250 locations in the RAMs as the character buffer. Since the buffer only accumulates characters according to the difference between the ASCII input and Baudot output rates—i.e., at about 5 characters per second, this gives the translator the capacity to cope with quite respectable character strings.

A complete listing of the program in symbolic form would be far too long to permit publication here. However, I am publishing a full hexadecimal listing, for the benefit of those who may wish to program their own PROMs.

The program itself starts at location 001, which is where SC/MP normally fetches its first instruction upon being powered up. Hence the translator needs no deliberate initialisation by the user—all one does is turn on the power, and away it goes.

Most of the Baudot teleprinters available on the surplus market have printer selector magnets with dual windings, which were intended for either series operation in nominal 20mA loops, or parallel operation in nominal 60mA loops.

The windings have quite high inductance, however, and are not suitable for

Here is complete hex listing of the translator program, resident in an EPROM.

```

0000 08 04 C4 02 35 C4 00 31 C4 00 37 C4 45 33 C4 06
0010 C9 04 C4 07 C9 05 C4 07 C9 06 06 D4 FE 07 C4 40
0020 C9 02 90 24 06 D4 10 98 18 C4 02 36 C1 05 32 C0
0030 CF D4 7F CE 01 A9 05 9C 04 C4 06 C9 05 C4 36 90
0040 02 C4 78 8F 09 3F 90 DC 06 D4 10 98 1A C4 02 36
0050 C1 05 32 C0 AB D4 7F CE 01 A9 05 9C 0A C4 06 C9
0060 05 90 04 C8 9B 90 6C 06 D4 20 9C 67 C4 10 C9 00
0070 C4 00 01 3F 06 D4 20 9C 5A 3F 3F 06 D4 20 98 02
0080 C1 00 01 58 01 C1 00 1C C9 00 9C ED 3F 40 E4 02
0090 9C 04 C4 0D 90 CD 40 E4 08 9C 04 C4 0A 90 C4 40
00A0 E4 04 9C 04 C4 20 90 BB 40 98 B8 E4 1F 9C 04 C9
00B0 01 90 20 40 E4 1B 9C 06 C4 20 C9 01 90 15 C4 01
00C0 36 C4 6E 32 C1 01 58 01 C6 02 98 97 60 9C F9 C2
00D0 FF 90 90 C1 05 03 F9 04 98 7A C4 02 36 C1 04 32
00E0 C2 00 01 40 E4 0D 9C 04 C4 02 90 42 40 E4 0A 9C
00F0 04 C4 08 90 39 40 E4 20 9C 04 C4 04 90 30 40 E4
0100 40 9C 04 C4 2B 90 27 40 98 24 D4 40 E1 02 98 0F
0110 40 D4 40 C9 02 98 04 C4 1F 90 1E C4 1B 90 1A C4
0120 01 36 C4 6F 32 C6 02 98 05 60 9C F9 C2 FD 01 A9
0130 04 9C 07 C4 06 C9 04 90 01 01 06 DC 01 07 C4 10
0140 C9 00 3F 3F 40 D1 00 98 05 06 D4 FE 90 03 06 DC
0150 01 07 90 02 90 10 C1 00 1C C9 00 9C E5 3F 3F 06
0160 D4 FE 07 3F 3F 3F C4 00 36 C4 47 32 3E 08 2D 30
0170 3D 31 39 32 30 33 2A 34 21 35 35 36 3C 37 2C 38
0180 23 39 18 41 13 42 0E 43 12 44 10 45 16 46 0B 47
0190 05 48 0C 49 1A 4A 1E 4B 09 4C 07 4D 06 4E 03 4F
01A0 0D 50 1D 51 0A 52 14 53 01 54 1C 55 0F 56 19 57
01B0 17 58 15 59 11 5A 33 3F 32 24 3E 28 29 29 3A 07
01C0 37 2F 38 2D 2E 3A 2F 3D 31 2B 34 27 27 2E 26 2C
01D0 2B 40 36 25 25 26 32 2A 37 3B 18 61 13 62 0E 63
01E0 12 64 10 65 16 66 0B 67 05 68 0C 69 1A 6A 1E 6B
01F0 09 6C 07 6D 06 6E 03 6F 0D 70 1D 71 0A 72 00 00

```



# HUGE SHIPMENT JUST ARRIVED —

## NATIONAL SC/MP KIT

**DONT PAY \$92.50...  
OR EVEN \$89.50!**

**DICK'S PRICE (WHILE THEY LAST)**

COMPLETE WITH INSTRUCTION BOOK **\$84.50** INCLUDING SALES TAX.

**(TAX-FREE PRICE \$75.51)**

PLENTY OF STOCK AT TIME OF GOING TO PRESS.

## PRICES SLASHED!

YES! DICK NOW HAS H-U-G-E STOCKS OF BRAND NEW, FAMOUS "NATIONAL SEMICONDUCTOR" INTEGRATED CIRCUITS, TRANSISTORS, DIODES, LEDS, DISPLAYS, ETC., ETC., ETC.

HE WILL SUPPLY ANYONE, AND ANY QUANTITY AT THE PRICES SHOWN — EVEN OTHER PARTS SUPPLIERS!!!!

## MM5024 PROM

FULLY PRE-PROGRAMMED BY NATIONAL SEMICONDUCTOR LABORATORIES FOR THE E-A ARTICLE

ONLY **\$35.00** (DON'T PAY \$40.00!)

TAX-FREE PRICE **\$30.95**



**INCREDIBLY CHEAP** SEMICONDUCTORS FROM OUR **HIGHLY EFFICIENT** RETAIL OUTLETS & MAIL ORDER!

## INCREDIBLE BARGAINS ON C-MOS & TTL IC'S AND OTHER SEMICONDUCTORS

### C-MOS — SLASHED!

4000	Dual 3 input NOR with inverter	.30
4001	Quad 2 input NOR	.30
4002	Dual 4 input NOR	.30
4006	18 stage static shift register	1.90
4007	Dual complementary pair plus inverter	.30
4009	Hex buffer (inverter)	.90
4011	Quad 2 input NAND	.30
4012	Dual 4 input NAND	.30
4013	Dual D flip flop with reset	.70
4014	8 stage shift register	2.00
4016	Quad bilateral switch	.70
4017	Decade counter/divider	1.80
4018	Presetable divide by N counter	2.00
4021	8 stage static shift register	2.20
4022	Divide by 8 with 8 decimal outputs	1.60
4023	Triple input NAND	.30
4024	7 stage ripple carry binary counter	1.40
4025	Triple 3 input NAND	.30
4027	Dual J-K flip flop	.90
4028	BCD/decimal decoder	1.60
4029	Presetable up/down 4 stage counter	1.80
4030	Quad exclusive OR	.80
4049	Hex buffer/TTL driver inverter	.80
4050	Hex buffer/TTL driver non inverter	.80
4071	Quad 2 input OR	.30
4081	Quad 2 input AND	.30
4416	DPDT switch	.90
4426	Decade counter/7 segment dec/driver	3.20
4449	Economy hex inverter	.30
4511	BCD/7 segment decoder/latch	2.30
4518	Dual BCD up counter	2.00
4520	Dual 4 stage binary up counter	2.00
4528	Dual retriggerable monostable multiv.	1.50
4553	3 Digit BCD counter	7.00
5411	Osc. 18 stage divider with buffer	3.50
74C00	Quad 2 input NAND	.31
74C02	Quad 2 input NOR	.31

### SPECIAL PURPOSE IC'S — SPECIAL PRICES

723	GP Regulator (2 - 37V)	.80
301	Op amp	.55
308	Op amp	1.60
380	Audio power amp	1.50
381	Low noise dual preamp	1.90
382	Low noise dual preamp (equalised)	1.90
555	Timer	.55
556	Dual timer	1.50
709	Op amp	.50
741	Op amp	.35
3900	Quad op amp	1.00
3909	LED flasher	1.10
ZN414	TRF radio chip	3.50
CA3130	FET op amp	1.50
SAK140	Tachometer	1.50
UAA170	Spot-o-light analog to LED display	2.25
UAA180	Bar-o-light analog to LED display	2.40

### T-T-L — L-O-W

7400	Quad 2 input positive NAND	.31
7401	Quad 2 input positive NAND with o/c outputs	.31
7402	Quad 2 input positive NOR	.31
7403	Quad 2 input positive NOR with o/c outputs	.31
7404	Hex inverter	.31
7405	Hex inverter with o/c outputs	.31
7408	Quad 2 input positive AND	.31
7409	Quad 2 input positive AND with o/c outputs	.31
7410	Triple 3 input positive NAND	.31
7413	Dual NAND Schmitt trigger	.75
7420	Dual 4 input positive NAND	.31
7430	8 input positive NAND	.31
7437	Quad 2 input positive NAND buffer	.65
7440	Dual 4 input positive NAND buffer	.31
7441	BCD to decimal decoder/driver	1.10
7442	BCD to decimal decoder	.90
7447	BCD to 7 segment dec/driver with 15V outputs	1.25
7450	Expander dual 2 wide 2 input AND OR INV	.31
7451	Dual 2 wide 2 input AND OR INV	.31
7453	Exp. 4 wide 2 input AND OR INV	.31
7454	4 wide 2 input AND OR INV	.31
7460	Dual 4 input expander	.31
7470	Gated J-K flip flop	.55
7472	J-K master slave flip flop	.55
7473	Dual J-K master slave flip flop	.80
7474	Dual D type edge trig flip flop	.80
7475	Quaduple bistable latch	.90
7476	Dual J-K m/s flip flop w/ pres & clear	.80
7480	Gated full adder	1.50
7482	2 bit binary adder	1.80
7483	4-bit binary full adder (lock ahead carry)	1.25
7486	Quad 2 inp excl. OR gate	.55
7490	Decade counter	.70
7491	8 bit shift register	1.10
7492	Div by 12 counter	.70
7493	4 bit binary counter	.70
7495	4 bit right/left shift register	2.00
7496	5 bit shift register	1.80
74107	Dual J-K master slave flip flop	.90
74121	Monostable multivibrator	.55
74141	BCD to decimal dec/ driver	2.90
74192	Preset. sync. decade up/down count.	1.80
74193	Preset. sync. 4-bit binary u/d count.	1.80

### DIODES — FROM 6 CENTS!

OA91	GP germanium diode	.12
1N914	GP silicon diode	.06
1N4004	400V 1A power diode	.08
1N4007	1000V 1A power diode	.15

### 'GARDEN VARIETY' TRANSISTORS — ALMOST GIVEN AWAY!

BC107/547	NPN audio	.12
BC108/548	NPN audio	.12
BC109/549	NPN low noise	.12
BC177/557	PNP audio	.12
BC178/558	PNP low voltage	.12
BC179/559	PNP low noise	.12

### DRIVER & POWER TRANSISTORS — DOWN TOO!

BC839	NPN 80V 1W driver	.55
BC640	PNP 80V 1W driver	.55
BD139	NPN 80V 8W driver	.75
BD140	PNP 80V 8W driver	.75
MJ2955	PNP 115W power	1.50
2N3055	NPN 115W power	.80
2N3638	PNP 500mA switch	.35

These special prices are only available from Dick Smith stores in Sydney, Melbourne and Brisbane; and from our mail order department in Sydney.

However, Dick Smith Dealers will also have special semiconductor prices this month, (though not necessarily on the same lines or at the same prices).

NOTE: We can only hold these low, low prices until 1st December, 1976. (So buy all you need now, commercial quantities included)

IF, before 1st December, you see a lower price advertised by an Australian company tell us about it — and we will adjust our price even lower if we can!

### ZENERS — JUST 25 CENTS!

BZX79 XXXX	400mW Zener diode	
	all voltages from 3.3 - 20	.25

### SCR'S — WAY DOWN

C122D	400V 8A SCR	1.50
-------	-------------	------

### LEDS & DISPLAYS — DISCOUNTED!

TIL220	Red LED	.22
RL209	Red LED	.20
DL704	0.3" comm. cath display	1.20
LL707	0.3" comm. anode display	2.00
DL747	0.63" comm. anode display	3.00

### EXPRESS SEMICONDUCTOR MAIL ORDER

If you order semiconductors from us by mail order, your order will be despatched within 4 hours of receipt. (It's easy to fill such a simple order!)

However: if you order other products from our full range, it will take just a little longer... the difference between an express and an all stations (?)

# DICK SMITH ELECTRONICS GROUP



Mail Orders: P.O. Box 747, Crows Nest, N.S.W., 2065.

N.S.W. Branches: GORE HILL - 162 Pacific Highway, 439 5311.

SYDNEY - 125 York St., 29 1126. BANKSTOWN - 361 Hume Hwy., 709 6600.

QLD. - 166 Logan Rd., Buranda, 391 6233.

VIC. - 656 Bridge Rd., Richmond, 42 1614.



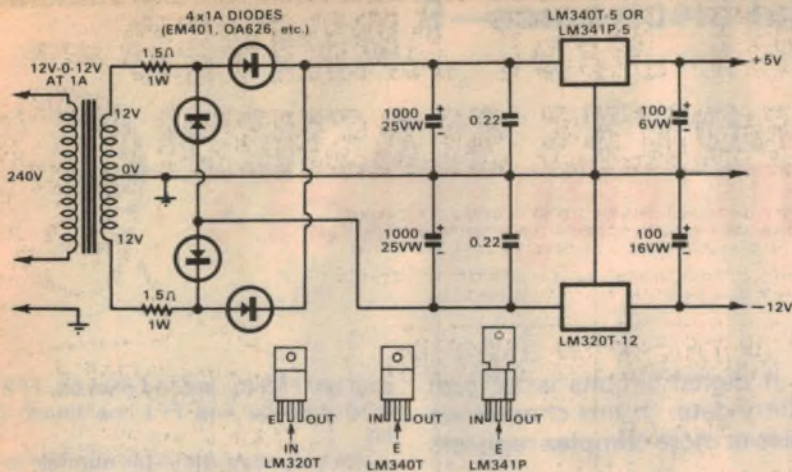


FIG. 3. POWER SUPPLY FOR TRANSLATOR

direct connection into low-voltage circuitry. They should be operated from a substantially constant-current source in order to obtain reliable character decoding. This generally means operating with the windings in parallel, and from a current source employing at least 50 volts. Accordingly a driver transistor must be used, to allow the low-voltage circuitry in the translator to control the magnet current.

Fig. 2 shows the power supply and driver circuit I have built into my machine, a Teletype model 15. It works very well, yet uses only a few easily obtained parts. The driver transistor is a Delco DTS410, but any similar high-voltage medium-power NPN transistor would be suitable. It is operated in switching mode, and does not dissipate significant power.

The circuit of Fig. 2 shows switching which allows the keyboard and printer driver to be connected together for "local" operation, if desired. This is not essential, but I have found it convenient.

Note that the input drive current required by the driver stage is a nominal 20mA, so that it would also be quite suitable for use with solid-state radio-teletype demodulators.

Fig. 3 shows the circuit of a small power supply suitable for the translator itself. It is quite straightforward, and uses two low-power 3-terminal regulator devices to provide the +5V and -12V supplies required. It would of course be possible to power the translator from the power supply used for the main computer system, if it has the capacity to supply around 400mA at +5V and 250mA at -12V additional to its existing loading.

If your Baudot teleprinter is one of the Teletype machines, you will need a step-down transformer to run its 115V motor from the 240V mains. The motor draws about 1.2 amps, calling for a transformer with a rating around 140VA. A double-wound type is recommended because the insulation of the motor may not be capable of withstanding 240V. I have used a Ferguson Transformer type

TS115/125, which although nominally rated at 125VA, runs quite cool even after many hours of continuous operation.

An important point to note if you are using the translator with Teletype machines is that the printing mechanism of these machines is fitted with an optional "down-shift on space" facility. This MUST be disabled for use with the translator, or the translator and printer will get out of step in terms of letters-figures shifting.

On the page teleprinters, models 15 and 19, the facility is controlled by a small horizontal lever at the very bottom of the printer mechanism, right at the front and centrally placed beneath the horizontal selector vanes which convey the character code to the moving type carriage.

To disable the automatic downshift, the keyboard should be removed by undoing the two knurled thumbscrews on each side, and then sliding it out the front. Then using a short screwdriver, loosen the locking screw on the down-

shift lever and move its rearward end towards the left until it hits the stop. Finally, tighten the lock screw again, and replace the keyboard.

On the model 14 typing reperforator the automatic downshift facility is controlled by the position of the vertical selector bar at the extreme left-hand end of the fixed type basket, looking from the front. To disable the downshift, the bar must be moved from the deeper of the two available slots, on the right, to the shallow slot on the left. This prevents it moving when a "space" character is decoded. The bar can be moved by hand; no tools are necessary.

Before closing, there are a few comments which should be made.

If you get the translator going and it seems to make consistent printing errors

LOWER CASE (LTR): ABCDEFGHIJKLMNOPQRSTUVWXYZ  
UPPER CASE (FIGS): -7:537REF ( ), 5014 57\*2/6+

Fig. 4: Both cases of the Baudot character set assumed by the translator program.

with some of the figures-case characters, this will almost certainly be due to your Baudot teleprinter having coding which differs from that assumed by the translator.

This possibility exists because Baudot machines are not all consistent in terms of upper-case characters and coding. Most of the machines available in Australia use the so-called "International Telegraph Code No. 2", and this is the code I have assumed in designing the translator. However you may be unlucky enough to get a machine with different coding, in which case you will get printing errors. They will be consistent, however, so that once you get used to them they should be only a minor irritation.

You can check the coding of your  
(continued on page 124)

## MICROCOMPUTERS

ASSEMBLED OR KIT FORM

**AIS HAS IMSAI NOW!**

AND MORE ON THE WAY

**PROFESSIONAL AND DEVELOPMENT  
SYSTEMS WITH ENHANCEMENTS  
FOR SPECIAL APPLICATIONS**

For illustrated catalogue just send a note detailing your application with \$1 and large S.A.E. to: A.I.S.

Phone 709 4144

47 Birch Street  
BANKSTOWN.  
N.S.W. 2200.







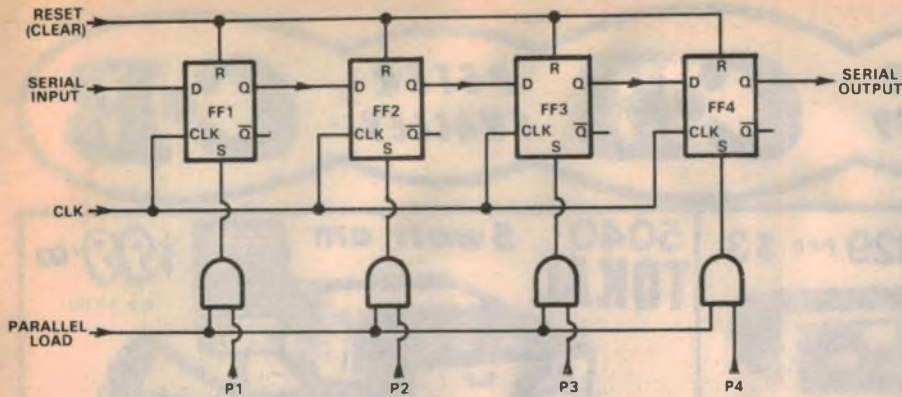


FIG. 3: 4-BIT SHIFT REGISTER WITH CLEAR AND PARALLEL LOADING

of each FF in the register to be connected either to the Q output of its neighbour to the left, as before (via the AND gates marked "A"), or to the Q output of its neighbour to the right (via the AND gates marked "B"). The two AND gates associated with each input connect to it via an OR gate, as shown.

The control inputs of all the "A" AND gates are connected together, as shown, as are the control inputs of the "B" AND gates. Thus by applying a logical 1 to the control line for the "A" gates, the register can be set up for shifting data to the right. Alternatively a logical 1 can be applied to the control line for the "B" gates, and this will set up the register for left shifting.

It would be usual to label the "A" gate control line as a "shift right enable" line, signifying that its function is to enable the shift right capability of the register. Similarly the "B" gate control line would be labelled "shift left enable".

In the shift registers of Figs. 1 and 2, the only way of getting data into the register is serially—i.e., one bit at a time. This can be too slow in many applications, and accordingly many registers are provided with a facility to load data in parallel fashion (all bits simultaneously). One way of doing this is shown in Fig. 3.

Each flipflop of the register is provided with direct set or S inputs, as you can see, and each S input is fed by an AND gate. One of the two inputs of each AND gate is connected to a common control line, while the remaining inputs are kept separate and become the parallel inputs of the register—P1, P2, P3 and P4.

To load the data present at the parallel inputs into the register, a short enabling pulse is applied to the gate control line (in other words, the line is taken briefly to the logic 1 level). Those gates whose data inputs are at logic 1 level will therefore be enabled, and their outputs will accordingly go to logic 1 level also. This will cause their associated FFs to be forced into the set state, if they were not previously in that state. If they were already in the set state, they will remain there. Either way, the logic 1's present at the data inputs effectively will have been loaded into the FFs.

Note, however, that when the gate control line is pulsed, only those gates whose

data inputs are at logic 1 level will be enabled. The other gates will not be enabled, because their data inputs will be at logic 0. As a result the flipflops associated with these gates will not be affected—even if they happen to be set to a 1, which is the exact opposite of the data bit we are trying to load in.

Because of this problem, the flipflops of Fig. 3 are provided with direct reset or "clear" inputs as well, and these are connected together to form a common reset or clear line. This is used to reset all of the FFs together, before the actual parallel loading is performed.

This means that just before the input gate control line is pulsed, all of the flipflops in the register are forced into the reset state, wherein they contain 0's. Hence when the gate control line is pulsed and the gates whose data inputs are at logical 1 level force their associated FFs into the set state, the remaining FFs will all remain in the reset state—effectively storing the 0's present at the data inputs of their gates, even though these gates actually remain inactive.

So that with a register provided with the simple type of parallel data loading scheme shown in Fig. 3, parallel loading actually becomes a two-step process. First the reset or clear line is pulsed, to clear the register, and then the parallel load enable line is pulsed to allow the input gates to enter the "1" data bits as appropriate.

While this form of parallel data loading is adequate for many purposes, there are situations where the required two-step process can be inconvenient. There are

also other situations where it is required to perform parallel loading of data synchronously—i.e., in step with the system clock pulses.

To cope with such situations, another type of parallel data input loading can be used. This is known as "jam transfer", and as the name suggests it allows parallel data to be jammed into the register flipflops regardless of the data bit values or the previous states of the flipflops. And the transfer takes place in response to a normal clock pulse, so that it meets the synchronism requirement.

One way of achieving jam transfer parallel loading is shown in Fig. 4. As you can see the D input of each FF is provided with a gating system rather like that of Fig. 2, with two AND gates feeding each input via an OR gate. And as before, the "A" gates are used to connect the D inputs to the Q-output of the preceding FF (or the serial input, in the case of FF1), for right shifting.

Here the other set of AND gates (labelled "B") are used not to set up the data paths for left shifting, but to enter the parallel data. The data input of each gate becomes the parallel input for its associated flipflop. So that when a clock pulse is applied to the register clock line, data bits from the parallel inputs P1, P2, P3 . . . will be forced into the flipflops if the "B" gates have been enabled by a logic 1 level applied to their control inputs.

Note that this will be a true jam transfer, because when a D-type FF is clocked, it is forced to adopt the state corresponding to the logic level present at its D input. In other words, we have a jam transfer here because a flipflop D input is active at both logic levels, whereas the S inputs used in Fig. 3 are active only when taken to the true logic level.

Quite incidentally, Fig. 4 shows the control lines for the two sets of gates interconnected via an inverter. This is a technique often used, with the idea of reducing the number of separate control signals required to control register operation. With the scheme shown, a logic 1 level applied to the "Mode" input causes the "A" gates to be enabled, so that the register performs the shift right operation. However if the logic level at the Mode input is changed to an 0, this not only dis-

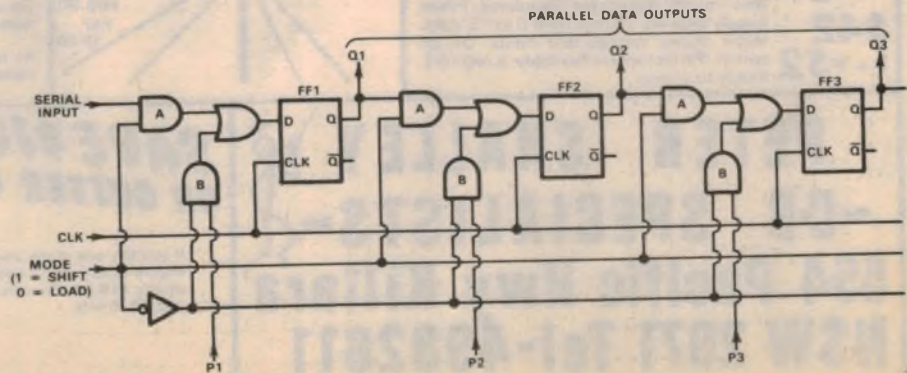


FIG. 4 SECTION OF A SHIFT REGISTER WITH JAM-TRANSFER PARALLEL LOADING



# C·B

## PETER SHALLEY

# C·B

## PETER SHALLEY

# C·B

### NEW! KRACO 5 watt am

**SPECIAL BUY  
LIMITED QUANTITY**


This exciting American style CB Transceiver is loaded with features. Apart from its smart black all metal cabinet it has a functional and attractive chrome control panel surround. Heavy duty control knobs with finger grips. Positive push button controls for automatic noise limiter. Public address. A most useful map lite is also incorporated. Illuminated channel indicator, variable squelch etc. 29 semiconductors plus I.C. dual conversion. Introductory offer only if you buy before Dec. 30th. Free Aerial valued at \$19.50 with each purchase of Kraco



\$129 P+P \$3

### 5040 5 watt am TOKAI

~~\$99.00~~  
pp \$3.00

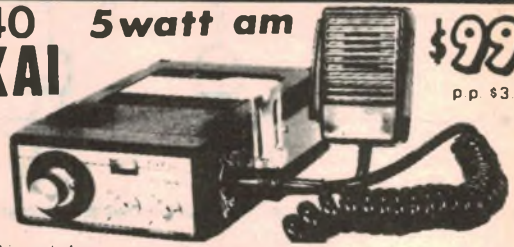

NOVICES this one's for you. Fully synthesised to give 23 American CB channels at the flick of a switch. Squelch & meter, press to talk mike complete with mounting cradle which can also be used as a desk stand. Very compact and highly efficient. Also available as a straight transceiver TC5041 approved for boating. \$119 (with 2 sets x'tals)

- 32 SEMICONDUCTORS
- 12 VOLT DC · MINI SIZE
- FULL WARRANTY · PUSH
- TO TALK MIKE
- POST & PACK \$2.00



### UTAC 5 watt am

Made by TOKAI branded UTAC

This is a handsome chunky 5 watt made for the American CB market with the full compliment of 23 American channels. You couldn't buy the bits for this sort of money. So get one while stocks last.

- 31 Semiconductors
- All metal case
- Fully synthesised
- P/T/T mike
- Cradle mounting
- 12 Volt DC
- PUB ADD FAC.
- P & P \$3.00

\$99 P+P \$3

### SSB-AM 15 WATT P.E.P. TOKAI

\$229 P+P \$3



This is the pride of our range of TOKAI Transceivers. Everyone wants to own this, but it's not cheap. How can it be with 81 semiconductors including F.E.T.'s. A magnificent sturdy metal case and all the goodies in the way of controls and facilities.

• 5 Watt AM—15W SSB · AM USB LSB & PUB. ADD  
• Triple AM & Dual SSB Conversion · P & P \$3.00



### MOBILE SSB AM

Mobile Transceiver for 12 to 16 Volts D.C. Fully synthesized on all 23 U.S. C.B. Channels

Output: A.M. 4 Watts  
S.S.B. 12 Watts (not input to final)

Dual Conversion: P.E.P. Receiver: Power and S Meter.

Sensitivity: less than .5 uv for 10db. Transistors: 36  
Thermistor 41 for use with Novice License.

\$199 P+P \$3



### REGULATED POWER SUPPLIES

0-15 VOLT

\$42  
P+P \$2

New model Adjustable Regulated Power Supply Delivers 3 Amps from 0 to 15 Volts. Meter shows Voltage and Amps On/off switch. Perfect where flexibility is required. Ready to wire in.

### Ground Plane Antennae

**27MC 36**  
High Efficiency Ground Plane Antenna for CB base station. All aluminium construction. Accepts PL 259 connector. Solid aluminium 108 inch heat treated radials and radiator. Elements supplied in two 54 inch lengths joined by threaded coupling nuts. Radial droop for 50 ohm match. Accepts 114 inch tubing and PL 259 connector. Frequency Range 27 MHz Impadance 50 ohms VSWR Less than 1.51 Weight 45lbs Wave 14.

\$49.95  
P&P \$5.00



### 27MC GPV BASE LOADED

A ruggedly constructed low cost high performance vertically polarized omni directional base station antenna. It develops transmitting gain of 38dB through pattern compression and a lowered angle of radiation along with improved signal to noise ratio. The matching stub places it at DC ground potential which substantially lowers the residual noise level and results in gains as high as 19dB in signal to noise ratio. Gain 38dB VSWR (At resonance) 1.25 1 Coaxial Feedline 52 ohms

Omni Directional Pattern.

Overall Height 212 inch  
Diameter of Radiator 112 inch to 1/16 inch  
Mast Bracket Accepts Up to 1.58 inch Weight 55lbs Full 12 Wave.

\$65.00  
P&P \$5.00

### BASE AM



Base Station dual Voltage 240V. AC or 12V. DC. Fully equipped with 23 American C.B. Channels.  
Input to final: A.M. 8 Watts min. S.S.B. 25 Watts P.E.P.  
Dual conversion: 7 I.F. Ts and 6 I.F. stages  
Noise Blanker: Delta tune (Clarifier) + - 300 Hz.  
Meter for: Signal in, R.F. out, S.W.R.  
Sensitivity: .5 uv @ 6db Noise: 33 x 13.5 x 24.5 cm.  
Wt. 7 1/4 kg For use with Novice License.

\$249 P+P \$5

THE TRANSCEIVERS ADVERTISED HERE ARE BUILT TO AMERICAN F.C.C. SPECIFICATIONS. A NOVICE OR HAM LICENCE IS REQUIRED TO OPERATE SUCH EQUIPMENT IN THIS COUNTRY.


See our comprehensive range of CB test equipment & aeriels, SWR meters from \$17. Power meters etc.

All mail enquiries must be accompanied by a self addressed, stamped envelope.

# PETER SHALLEY

## «C·B SPECIALISTS»
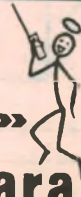
### 554 Pacific Hwy Killara NSW 2071 Tel-4982611



### SAVE \$10! ON GUTTER GRIP AERIAL

If you buy any of the above Transceivers you will be eligible to buy one Guttergrip or Roof Mount Aerial—usually \$19.50—For only \$9.50. Offer lasts till 30th Dec. 1976 only



\$19.50 P+P \$2



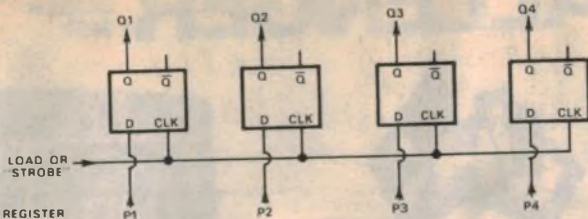


FIG. 5 4-BIT LATCH REGISTER

ables the "A" gates but also enables the "B" gates via the inverter—so that the register performs the parallel loading operation. A single control signal is thus able to determine the register's mode of operation.

The flipflops in Fig.4 are also shown with their Q outputs brought out, with labels Q1, Q2, Q3, etc. This is done with some shift registers, as it allows a further degree of flexibility: data bits can be taken from the register in parallel, as well as being loaded in parallel.

One important use for registers fitted with parallel data inputs or outputs is serial-parallel and parallel-serial conversion. For example, a binary number available only in parallel form may be converted into serial form by loading it into a register via the parallel inputs, and then shifting it out bit by bit.

Conversely a binary number available only in serial form may be converted into parallel form by shifting it into a register via the serial input, and then sensing the bits simultaneously at the parallel outputs.

Some pre-packaged flipflop registers are provided with parallel inputs and a serial output, expressly for parallel-to-serial conversion. Others are provided with parallel outputs and a serial input, expressly for serial-to-parallel conversion.

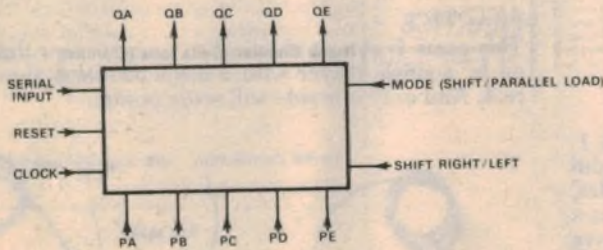


FIG. 7 MULTI-PURPOSE 5-BIT REGISTER

Still others are provided with all of these, and are therefore capable of performing both types of conversion quite apart from pure shifting and data storage.

Not all flipflop registers are shift registers, though. In fact one simple type of register quite often encountered is the latch register, which is used purely for parallel data storage. As you can see from Fig.5, it consists essentially of nothing more than a row of D-type flipflops with their clock inputs connected together. A clock pulse applied to the common clock line effectively causes each FF to load in the data bit present at its D input, so that the D inputs become the parallel data inputs of the register and the clock line

becomes a "load", "store" or "strobe" control line.

While Fig.5 shows a latch register for only four bits, pre-packaged latch register ICs are available which provide for up to eight or ten bits. And of course longer latch registers may be assembled if required, using multiple devices. This also applies to registers of the type shown in Figs. 3 and 4.

The registers we have looked at so far in this chapter have been only capable of shifting data right or left, parallel loading, or clearing. While these are the operations most commonly performed by registers, other operations are at times required,

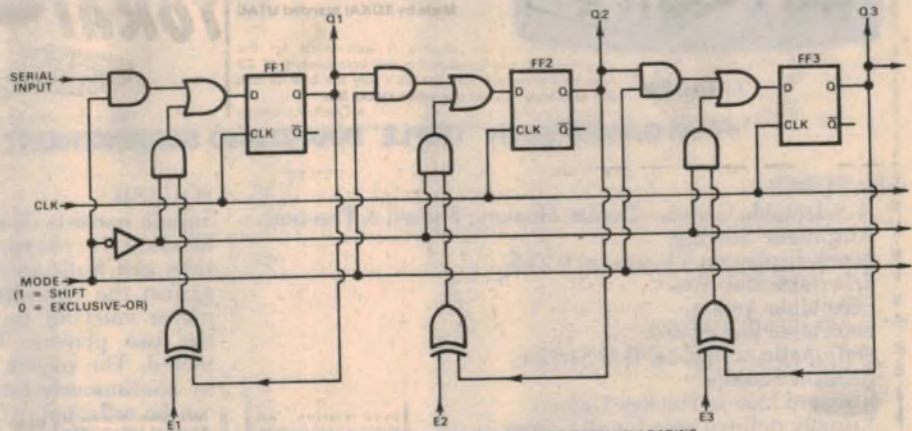


FIG. 6 SECTION OF A SHIFT REGISTER WITH EXCLUSIVE-OR PARALLEL LOADING

is the ability to "rotate" the bits of the stored data, either to the right or the left. This is similar to shifting, except that a data path is opened between the FFs at the two ends of the register so that none of the bits are "lost".

To rotate data to the right, for example, the Q output of the FF at the right-hand end of the register is connected via gating to the D input of the FF at the left-hand end, while all of the other D inputs are connected as in Fig.1 for right shifting. A clock pulse then causes all of the data bits to be shifted to the right, except for the rightmost bit which is rotated back into the leftmost FF.

Similarly, by using gating to connect the D input of the rightmost FF of a register to Q output of the leftmost FF, in addition to connecting all the other data paths for left shifting, it becomes possible to perform a "rotate left" function.

Other facilities which may be provided on registers include parallel logic functions such as AND, OR, and exclusive-OR. These are found somewhat less frequently, but have important uses in data

processing. Broadly speaking they are provided rather like jam-transfer parallel loading, except that additional gating is used to provide the required logic.

This is illustrated in Fig.6, which shows a basic shift-right register provided with an alternative exclusive-OR facility. As you can see, it is broadly similar to Fig.4. The difference is that instead of being directly applied to the D inputs of the FFs when the Mode line is taken to logic 0, the parallel data inputs are fed via exclusive-OR gates where they are compared with the existing data bits in the FFs. This is done by connecting one input of the ex-OR gates to the FF Q outputs.

When registers are implemented using single ICs, it is not usual to show all of the internal FFs and gating on a logic diagram. Thus a single-IC register of 5-bit capacity may be shown by a symbol like that in Fig.7, with a simple rectangle representing the register as a whole. All that is shown are the various control signal inputs, together with the data inputs and outputs. This is generally quite adequate for design purposes, providing the functions of the various inputs and outputs are clearly defined.

and accordingly some registers are provided with the appropriate facilities.

One such facility is the ability to complement the stored data bits—in other words, each FF of the register may be toggled to its opposite state. This can be of value where a register is used for binary arithmetic, as we will see later on.

To provide such a bit complementing facility, gating is provided so that application of a suitable control signal causes a data path to be opened up between the D input of each FF and its own Q-bar output. A clock pulser then causes each FF to adopt the state formerly present at its Q-bar output—ie., it toggles.

Another facility which may be provided



# TV CHALLENGER<sup>®</sup> SERIES 3000

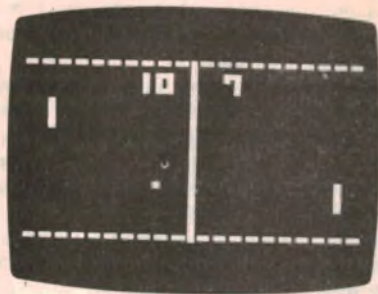


FIGURE 1

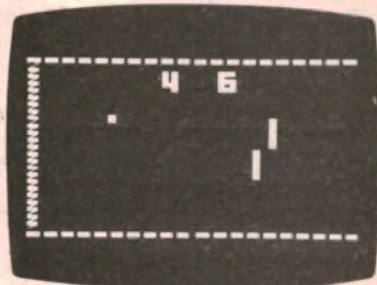


FIGURE 3

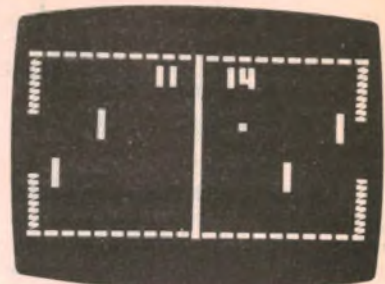
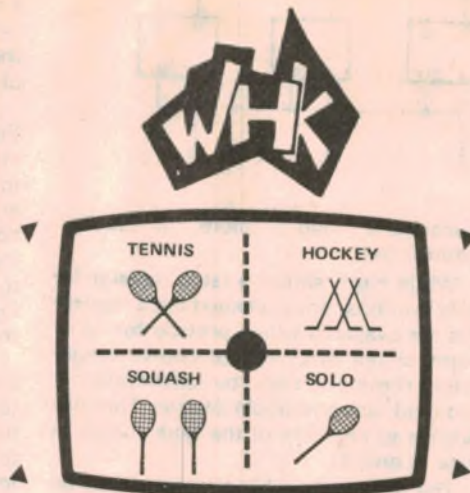


FIGURE 2

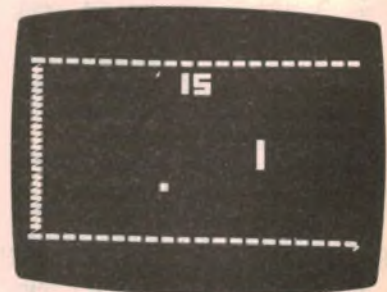


FIGURE 4

FOUR GAMES WITH "TRIPLE" SOUND AND SCORING RIGHT ON YOUR TV SCREEN.

## FEATURES

- \* 4 Selectable Games - Tennis, Hockey, Squash & Practice.
- \* Automatic Scoring.
- \* Score display on TV screen, 0 - 15.
- \* Selectable Bat Size.
- \* Selectable Angles.
- \* Selectable Ball Speed.
- \* Automatic or Manual Ball Service.
- \* Realism Sounds.
- \* Forward Man in Hockey Game.
- \* Visually defined area for all Games.

## GAME DESCRIPTION

### TENNIS

The game will appear on your screen as shown on figure 1. It is played by the players who use the left and right paddle controllers to vertically raise or lower their paddles. Play starts upon depressing the reset switch which causes the score to reset to 0 - 0 and when the manual serve switch is in the automatic position will serve the ball from either the left or the right court. The player who is served must hit the ball back to his opponent, who must then return it. When either player misses his shot, a point is scored for his opponent and the next ball is served to him from the opponents court. Scoring is automatically displayed. The game ends with the first player to reach 15 points.

### HOCKEY


This game will appear on your screen as shown on figure 2. Hockey, while similar to tennis, is a much faster and more exciting game. Each player controls his GOALIE who moves in a vertical motion, and one forward MAN who also moves vertically. These MEN move up and down as a group. As in tennis, the opening serve comes cross-court to either player on a random basis. Further serves are to player who has just lost a point. Since each player has two MEN who can return the puck, the play is very fast. Scoring is the same as in tennis - first player to reach 15 points is the winner.

### SQUASH

Squash consists of a court as depicted in figure 3. It plays identical to tennis except only one player operates at a time and both are on the same side of the court, playing against the opposite wall. After the ball is served the left player must hit the ball first and then alternates between the two players. This action continues until a point is scored. The object of the game is to keep the ball in play by continuously hitting it to the back court wall. The ball can be reflected off 3 sides - the top, bottom, and left wall. Again the first player to score 15 points is the winner.
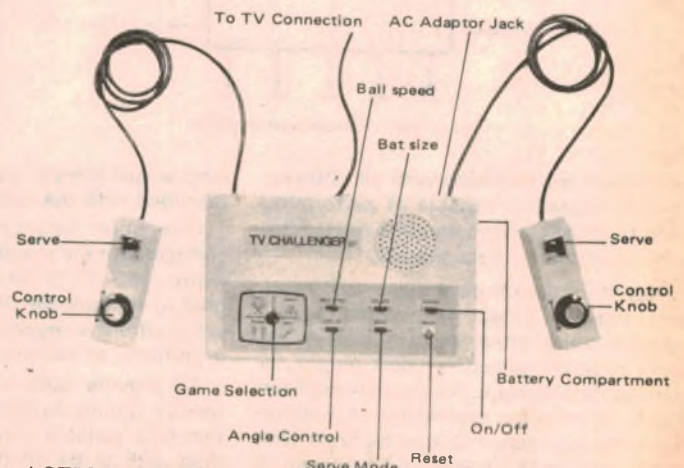
### PRACTICE

This game is almost identical to squash except that it is played by a single player with a single paddle as shown on figure 4. And only one side will score points.



### ACTION SOUNDS

- In all games three types of sound are heard
- a) Sound when the ball reflects of boundaries.
  - b) When the ball hits a paddle.
  - c) When a score is made.









# 2+4!!

## UNCOMPROMISED STEREO & QUAD

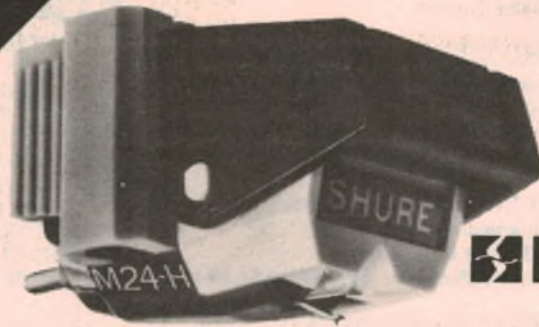

... UNDENIABLY

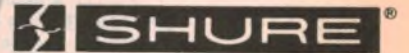

We call it "2+4": a *totally different concept in a phono cartridge* that combines Shure's traditional pre-eminence in *stereo* and state-of-the-art *quad* technology. It's the first such cartridge that doesn't sacrifice stereo for quad capability!

For quad enthusiasts, both matrix and discrete, this M24H Cartridge represents the distillation of the most advanced quadriphonic technology — PLUS new Shure advancements, such as the lowest effective stylus mass (0.39 mg.) available in quadriphony, and a new hyperbolic stylus tip for improved groove contact.

Each of these dimensions in hi-fi performance would be a best seller in its own right, but with "2+4" synergism, the M24H will be the blockbuster the hi-fi enthusiast has been waiting for.


The M24H does not compete with the V-15 Type III or M95 Cartridge. The M24H is for those who want excellent stereo and quad without having to change cartridges every time they change records.

FEW CARTRIDGES AVAILABLE TODAY CAN OFFER THIS COMBINATION OF STEREO SUPERIORITY AND QUAD CAPABILITY.

### WIDE-RANGE DYNETIC® PHONOGRAPH CARTRIDGE

#### BRIEF SPECIFICATIONS

**Frequency Response** 20 to 50,000 Hz.

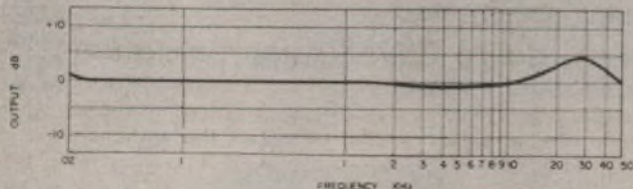

**Output Voltage** 3.0 mV per channel (at 1,000 Hz, 5 cm/sec peak recorded velocity).

**Channel Balance** Within 2 dB.

**Channel Separation** (minimum) 22 dB at 1 kHz.

**Optimum Load** Stereo and Four Channel Matrix: 20,000 to 100,000 ohms resistance in parallel with 100 to 250 picofarads total capacitance\* per channel.

Discrete Four-Channel: 100,000 ohms resistance in parallel with 100 picofarads total capacitance\* per channel.

\* Total capacitance includes the capacitances of the tone arm wiring, phono cables, and the amplifier input circuit.

**Tracking Force** Optimum: 1 1/4 grams.

#### STEREO OR FOUR-CHANNEL MATRIX

This Wide-Range Dynetic® cartridge is compatible with all conventional stereo or four-channel matrix systems. Set function switch on amplifier as required.


#### Trackability

400 Hz	20 cm/sec*
1,000 Hz	28 cm/sec*
5,000 Hz	47 cm/sec*
10,000 Hz	50 cm/sec*

\* Peak recorded velocity.

(Measurements made using a Shure/SME Tone Arm.)

#### TRACKABILITY CURVE

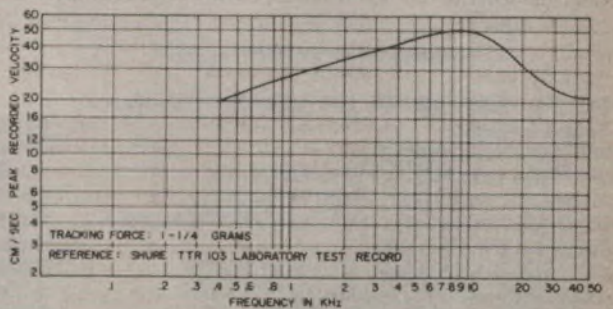


**Stylus Model N24H:** 8 x 18 microns (.0003 x .0007 in.) hyperbolic diamond tip.

**Weight Net** ..... 5.8 grams (0.2 oz)
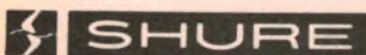
#### DISCRETE QUADRIPHONIC OPERATION

For optimum discrete quadriphonic performance, be sure to use low-capacitance cables (less than 100 pF). Adjust decoder or receiver separation, level and other controls as required.



**AUDIO ENGINEERS P/L**  
342 Kent Street  
SYDNEY 2000, N.S.W.

**AUDIO ENGINEERS (Vic.)**  
2A Hill Street  
THORNBURY 3071, Vic.

**RON JONES PTY. LTD**  
57 Castlemaine Street  
MILTON 4064, Qld.

**ATHOL M. HILL P/L**  
1000 Hay Street  
PERTH 6000, W.A.



# Classical Recordings

Reviewed by Julian Russell



## Strauss—An Alpine Symphony

**STRAUSS — An Alpine Symphony. The Los Angeles Philharmonic Orchestra conducted by Zubin Mehta. Decca Stereo SXLA 6752.**

Geoffrey Crankshaw, who wrote the sleeve notes for this work, displays unusual enthusiasm for what is generally regarded as second-rate Strauss. He writes that Strauss uses "an unusual range of instruments to depict a wide range of natural phenomena, yet is also profoundly human, setting personal endeavours in a universal environment."

There can be no disagreement with the first part of this statement. The Alpine Symphony is scored for no fewer than 20 horns, quadruple woodwind, six trumpets, six trombones, a great variety of percussion of different materials and, of course, enough strings to balance this formidable ensemble. Some of the brass play off-stage but, in the hall, Strauss adds a wind machine, a thunder sheet and various other paramusical devices.

Admittedly Strauss could make an orchestra produce sounds that describe with uncanny realism objects not usually associated with music. Indeed he himself claimed to be able to describe a glass of beer in musical terms. Even in pre-inflation days the cost of assembling such a congregation put a performance of The Alpine Symphony beyond the ordinary resources of concert managements, so that a live performance has always been a rare occasion.

But I think the second part of Crankshaw's statement must be accepted with more reserve. Strauss personally was not a sensitive man though, surprisingly, he had a great gift for musical characterisation, not only in his vast output of operas but also in orchestral works. But not even his greatest admirers — and I include myself in this category — could call him noble. He was often boorish and his ideals of personal endeavour were never quite as lofty as Crankshaw claims, but were very much more bourgeois.

At his greatest he was an unquestionable genius, although not in this work which describes almost step by step the ascent and descent of a mountain with many of its attendant hazards. True he achieves the purely descriptive elements with unmatched realism. But nobility of human endeavour were not in his otherwise wide range of expression.

Also Sprach Zarathustra can in no way, except perhaps its now hackneyed mighty first theme, be compared to his brilliant Till Eulenspiegel, the latter an inspired portrait of a mischievous imp who would be the last to claim nobility of character. In An Alpine Symphony, when Strauss seeks to express nobility, he becomes more than usually rhetorical.

But despite all the objections I have set down — and some might well call them prejudices — this disc is still very worth while owning. It has beautiful moments and some exciting ones, too, and Mehta misses no opportunity of communicating them in a recording of great tonal splendour, faultlessly engineered. Despite the often extreme complexity of the score there is no crowding of the numerous strands.

In the same way as few can remain unmoved by the majesty of the Alps, the symphony has a similar appeal in parts.

Although Strauss was fully mature when he composed it there are constant reminiscences of Wagner's and Strauss' own earlier works. For instance the Rosenkavalier is never completely forgotten. But it's all echt-Strauss with its wide ranging melodies modulating characteristically from key to remote key. And there are passages as exquisitely delicate as any he ever wrote.

The music is very much of the "program" variety and if you follow Crankshaw's notes on this aspect the various activities are very easy to follow. Strauss describes them with undeniable ingenuity. You can actually "hear" the party losing its way. But all this is, to me, marred by a bagful of tricks that he had used often before, and there is something faded about many of his romantic melodies. Some even sound a little second hand.

I don't know if Mehta used all the instruments and other devices that the score demands but he gives a grand reading, spacious on most occasions, and sensitively understanding on others. Strauss is quoted as saying that it was his finest work. Yet when the Americans occupied Bavaria towards the end of the last war an American scouting squadron looking for barracks spotted a grand villa, on a hill overlooking Garmisch-Partenkirchen, in which Strauss lived. This, they thought, is it. But when they arrived there they were greeted at the door by an old gentleman who said simply, to the captain in charge: "I am the composer of Rosenkavalier". He was left undisturbed. The composer of An Alpine Symphony would have meant nothing to soldiers.

## Jean Martinon conducts Ravel—recommended

**RAVEL — Bolero; Scheherazade Overture; Rapsodie Espagnole; and La Valse. Played by the Orchestre de Paris conducted by Jean Martinon. HMV Stereo/Quadraphonic OASD 3215.**

I saw a lot of Jean Martinon, who died last March, when he came out here for an Australian tour some years ago. During my many conversations with him he usually finished up by introducing the subject of rhythm in orchestral playing, insisting that it was one of its most important features. He communicated this opinion to many of the orchestras he conducted here, with highly satisfactory results.

In this splendid disc you will hear the effects of this — one could even call it an obsession — on the Orchestre de Paris which, after a rather shaky start a few years ago, has now developed into a very good combination indeed, especially in the playing of French music.

Martinon starts his concert on this fine new issue with Ravel's Bolero, a work which of course, relies almost entirely on rhythmic treatment to be heard at its

most effective. Bolero is a subtle attack on the nerves of the audience with its seemingly endless repetition of the same tune and tempo, differently scored each time it is heard and gradually increasing in volume towards its final exciting climax. It is interesting to compare it to modern pop music that often essays the same thing but which usually achieves nothing but mindless repetitious banality.

The string tone is not as voluptuous as that of some other first class orchestras but I am not sure that this is very important in a piece like Bolero. The rest of the orchestra plays superbly without ever missing a breath, so to speak. You have probably heard Bolero countless times, as I have, but this should not spoil your enjoyment of this magnificent achievement.

The second item is what Ravel described as a Fairy Overture to his unfinished opera Scheherazade. It is a student work and like so many other student adventures is powerfully influenced by the music of previous composers. Yet it already shows traces of the



# SPECIAL PURCHASE—NEW GARRARD RECORD CHANGERS AT A FRACTION OF LIST PRICE

## Garrard M82 Transcription Record Changer

**\$57.00**

Recommended retail price **\$120.00**



### SPECIFICATIONS

Type: fully automatic transcription turntable • Motor: four-pole synchronous • Mains switch: double-pole switch with suppressor • Drive: intermediate wheel • Record

play: plays up to six records automatically and single records automatically or manually as required • Turntable: 10½in diameter cast aluminium • Pickup arm: aluminium section, resiliently mounted adjustable counterbalance weight, slide-in C3A cartridge carrier, precision-loaded ball-bearing pivots • Stylus force: adjustable up to 4gm by sliding weight, minimum recommended ¼gm • Bias compensation: lever and weight calibrated for conical and elliptical styli • Cue and pause: damped action Record speeds: 33½, 45 and 78 rev/min • Tab controls: auto/stop/start, man off/on, cue/play/lift. Supplied with Pickering Magnetic Cartridge with Diamond stylus. Post & Packing: (Reg. post) N.S.W. \$3.60, Vic. S.A., Qld. \$4.74, Tas. \$5.50, W.A. & N.T. \$6.75.

## GARRARD ZERO 100 TRANSCRIPTION CHANGER.



**\$80.00!**

(Normal recommended retail price **\$198.00.**)

### AUTOMATIC OR MANUAL OPERATION

Variable speed control with illuminated stroboscope. Supplied with Pickering AM2 magnetic cartridge & diamond stylus. Post & packing (reg. post) N.S.W. \$4.50, Vic. S.A. & Qld. \$5.75, Tas. \$6.50, W.A. & N.T. \$8.75.

The heavy 11½'' diecast dynamically balanced two speed (33½ & 45 RPM) turntable is driven by the famous Garrard Synchro-Lab synchronous 4 pole motor. Incorporates the Garrard parallel tracking pick-up arm which is internationally recognised for its negligible tracking error. This arm has an integral magnetic bias compensator and will accept cartridges requiring a stylus force as low as 0.75gm. Stylus force setting is simple & accurate.

A viscose fluid damping queuing system is used with convenient finger tip tab controls.

## New C800 STEREO AMPLIFIER

**\$149**

(freight extra)



### By classic


- Elegant and functional design
- Push-button controls
- Microphone input with separate control
- Provision for simulated 4-channel stereo
- Cabinet in teak or walnut oiled finish with matching metal trim.

### SPECIFICATIONS

- Power output: 25 watts per channel R.M.S. Total output 50 watts R.M.S. 8 ohms.
- Frequency response: 20 cycles to 30,000 ± 1dB.
- Hum and noise: Aux. 70 dB. Mag 60 dB.
- Input sensitivity: Mag. 2mv. Aux. 250mv.
- Equalised: Mag. RIAA.
- Tone controls: Bass 50cs ± 13dB Treble 10Kcs 15dB.
- Harmonic distortion: Less than 0.1 percent.

- Loudness control: 50cs 10dB.
- Scratch filter: (high filter) at 10kcs 5 dB.
- Rumble filter: (low filter) at 50cs 5 dB.
- Provision for tape recorder: Record or playback with din plug connector.
- Speaker switching: two sets of speakers can be connected and selected by switch on front panel.
- Headphones: headphone jack is situated on front panel.
- Dimensions: 16½in x 11in. deep x 5in high.
- Weight 16 lbs.
- Power supply: Regulated power supply with switching protection for output transistors.
- Semiconductors: 33 Silicon transistors plus 7 diodes.

## Garrard 6-400 Record Changer

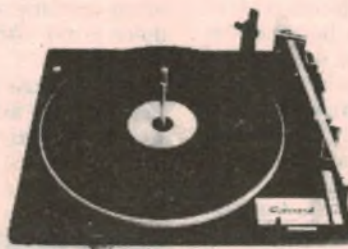

**\$28.50**

Recommended retail price \$48.00 (POST & PACKING SAME AS M82)

### SPECIFICATIONS

Fully automatic turntable plays up to six records automatically and single records automatically or manually as required. 10'' turntable. Bias compensation. Cue & pause control with damped action. Record speeds 33½, 45 and 78 rev/min. Finished in black with silver trim. Player and changer spindles supplied. Supplied with high quality Garrard/Sonotone Ceramic Cartridge with Diamond stylus. Bases in walnut or teak with perspex covers available.

## New MAGNAVOX—MV50— 50 WATT SPEAKER SYSTEMS

As featured in Feb. 1976 issue of Electronics Today

Complete kit of parts (less cabinet) comprising Magnavox 10-40 10'' bass unit. 625 mid range 6'' two XJ3 dome tweeters, crossover network, innabond, speaker silk & plans of cabinet.

**\$72.00**

Per Kit freight extra per rail or air freight. Cabinet available

## MAGNAVOX 8—30 SPEAKER SYSTEM (4 Way)

DRIVE UNITS: Magnavox 8-30 high performance 8'' bass unit. Magnavox 6J 6'' mid range speaker. Magnavox new high fidelity dome tweeters (two supplied). SPEAKER KIT: (less cabinet) comprises above speaker, 1mh inductance, 1 8mfd

and 1 4mfd. polyester capacitor, 1-3'' and 1-6'' tube, innabond, speaker silk and plans of cabinet.

**\$49.00**

Post & pack (reg. post) \$6.50 W.A. \$10.50 per kit. Cabinets available

# CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045  
PHONES 798 7145, 798 6507



composer's own inimitable style and is well worth its inclusion despite its lack of formal security. Its main interest is to be found in its prophecy of Ravel's superb gift for orchestration. By the way, in this piece the strings play with a much more voluptuous tone than in Bolero.

Next comes Ravel's first really mature big orchestral work, Rapsodie Espagnole, a piece exquisite in conception, and on this disc in execution too. I will stake my reputation on the statement that under Martinon it is easily the finest recording of the work I have ever heard, and I cannot count the number of times I have heard it played by different orchestras and conductors over many years.

You will hear quite wonderful rhythmic treatment in the Malaguena and just as fine, though different, Havanera. And again, the same pulse quickening handling of the final Feria.

The concert ends with La Valse, starting in mysterious darkness and finishing in near blinding incandescence. If you love the best of French music as much as I do please don't miss this disc. By the way I listened to this compatible stereo/quadrasonic disc on stereo equipment with the happiest of results. I am happy to be able to say that this extravagant pocket raider has proved a disaster to its manufacturers and the four-channel repertoire is as scanty as a bikini.

★ ★ ★

**RACHMANINOV** – Rhapsody on a Theme by Paganini for Piano and Orchestra.

**DOHNANYI** – Variations on a Nursery Song for Piano and Orchestra. Cristina Ortiz (piano) and the New Philharmonic Orchestra conducted by Kazuhiro Koizumi. EMI Stereo/Quadrasonic OASD 3197.

Here is a thoroughly workmanlike performance by soloist and orchestra of the Paganini, a piece chosen so often by hopeful competitors in piano competitions. Wherever possible the tempos are brisk though there is a tendency to slow down the contrasting sequences a little too much. The engineering is spacious with a wide but not overpowering dynamic range.

Unfortunately there is no information about the conductor who I take to be Japanese, and a highly competent director. The same applies to the brilliant soloist except for a coloured photograph on the face of the sleeve of a very personable young woman.

The Dohnanyi Variations have long been a favourite of mine though I haven't heard them for many years. It is a consistently witty work using many of the variations as parodies of various musical forms. It begins with an immensely pompous introduction which strains to lay a pigeon-sized egg – the theme which corresponds closely to our well-known nursery rhyme, Baa, Baa Blacksheep.

The eleven variations and fugal Finale are full of surprises, all with easily recognisable relationship to the original theme. As in the Rachmaninov noted above the slower portions of the score seem to me just a little too retarded, but otherwise the performance by both soloist and orchestra is admirable. There is, however, a particular obtrusive and nasty toned piccolo solo in the item preceding the music box variation.

Here are two works for piano and orchestra set down by composers who knew how to write a virtuoso part for the solo instrument without adding unnecessary showy padding. Enthusiastically recommended. I played this, too, on stereo equipment with excellent results.

★ ★ ★

**DVORAK** – Piano Concerto in G Minor. Justus Frantz (piano) with the New York Philharmonic Orchestra conducted by Leonard Bernstein. CBS Stereo SBR235779.

As the sleeve notes state you will hear in this early effort by a great composer much varied and attractive material though not always treated with the formal resources of his later works. Bernstein, as might have been expected, starts off with a nervously tense introduction before the piano enters. Dvorak himself was not much of a pianist though he performed better on the violin, and the piano writing here is nowhere nearly up to the standard of treatment of the cello part in his great concerto for that instrument.



Conductor Leonard Bernstein.

Throughout the Piano Concerto some of the themes are just plain banal as is their working out which is only too easily predictable, but here and there you come across a real Dvorjakian melody that quickly jolts the listener's interest back. The piano tone is often a little shallow though the soloist's technique is satisfactorily fluent.

I can't imagine the concerto ever becoming popular, even with a visual accompaniment of Bernstein's balletic improvisations on the rostrum. Philip Ramey, who wrote the accompanying sleeve notes, seems to have included as many pejorative – but amusing – criticisms of the music as he could. I'm afraid I cannot welcome this new issue with any great enthusiasm.

# TELEX®

## PUSH BUTTON – INSTANT CASSETTE COPIERS

Desk top units to suit every need



### ECONOMY COPIER

- High speed, copies a C60 in 2 minutes
- Two button operation, automatic rewind.



### COPIER I

- High speed, copies a C60 in 2 minutes
- Two button operation
- Track selectable erase, automatic rewind.



### STEREO COPIER IV

- High speed, copies a C60 in less than 3 minutes.
- High fidelity stereo copies. Track selectable recording and erase for four channel operation.
- Two button operation – automatic rewind.

### SLAVE COPIER

- When plugged into the Copier I or Copier IV, provides an additional two copies simultaneously.
- Two slave copiers can be connected.

FOR FURTHER INFORMATION:

AUDIO TELEX COMMUNICATIONS PTY. LTD.

**SYDNEY**  
54-56 Alfred Street,  
Milsons Point 2061  
Telephone: 929-9848

**ADELAIDE**  
Werner Industries,  
28 Gray Street,  
Kilkenny 5009  
Telephone: 268-2801

**BRISBANE**  
Bruce Window Elect.  
10 Buchanan Street,  
West End 4101  
Telephone: 44-6844

**MELBOURNE**  
828 Glenferrie Road,  
Hawthorne 3122  
Telephone: 819-2363

**PERTH**  
Audio Equipment Ltd.  
36 Gairloch Street,  
Applecross 6153  
Telephone: 64-4736

**HOBART**  
Video & Sound Services,  
141 Murray Street,  
Hobart 7000  
Telephone: 34-1180



# Dokorder.

## A superb range that has sound quality taped.

Increasingly advanced recording techniques mean that near perfect sound is available to the music lover. To fully appreciate this sound, you need equally sophisticated reproduction equipment. And that's what Dokorder is all about!

A range of highly sophisticated tape recorders and decks . . . seven models to select from. One for every need and budget. For instance, the new 1140 . . . Dokorder's finest professional tape deck. Studio quality and a host of features. And the 8140 4-channel

tape deck with multi-sync, for fun, flexibility and fine sound. Then, there's the new MK550 stereo cassette deck featuring servo controlled drive system, built-in Dolby, Cue and Review system, Peak Level Indicators, Normal/Chrome equalization and a switched FM multiplex filter—features you should insist on in any first-class deck. With Dokorder, there certainly is a unit to suit every need! And every Dokorder gives you superb sound quality.

### Dokorder.

## PHOTIMPORT

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY

For descriptive literature and specifications, send a 30 cent stamp to **Qualitron Industries Division** of Photimport (Australia) Pty. Ltd.

Head Office: 69 Nicholson Street, East Brunswick, Vic. 3057  
Australia, Telephone: 380 6922



PA11D





## Lighter Side

Reviews of other recordings

### Devotional and organ

**THE ARCHERS. Things We Deeply Feel. Stereo, Light, LS-5679-LP. (From Sacred Productions Australia, 181 Clarence St, Sydney and other capitals).**

The jacket notes introduce the Archers as a group of seven young people, presumably with the backing here of a dozen extra musicians playing keyboards, Moog, guitar, steel guitar, drums, percussion, electric fiddle, and so on. With their own special arrangements, and with the support of Ralph Carmichael, it's all very professional, as further evidenced by the fact that the group have toured the USA, Canada, and Europe and are under professional management sited on Sunset Boulevard. And that's the talent they bring to bear on eleven modern rock style Gospel songs:

Music — Giver Of Life — Sit Yourself Down — Lord, You've Been Good To Me — It Wouldn't Be Enough — I'm With Jesus — Brand New Day — You Are My Inspiration — If You Can't Believe In Love — It's Love To Me — Praise Him.

Recorded in Hollywood, I doubt that there's a note out of place in the whole performance, which plays for about 37 minutes. It's a performance by youth for youth, and for others who like soft rock and mod. style Gospel vocals. In short, another one for after-church youth groups—and groupers. (W.N.W.)

★ ★ ★

**MY SAVIOUR FIRST OF ALL. Rudy Attwood. Stereo, Word WST-8603-LP. (From Sacred Productions Aust, 181 Clarence St, Sydney and other capitals).**

Rudy Attwood, well known some years ago as the pianist for "The Old Fashioned Revival Hour" is just as likely to refer to himself, these days, as "the last of the squares". And certainly, the man who was once regarded as an exponent of tasteful Gospel music ornamentation, sounds more than usually restrained on this album.

But, if you like the old hymn tunes for their own sake you might easily find his unhurried playing very restful: When

Morning Gilds The Skies — O Jesus I Have Promised — He Lifted Me — What A Friend We Have In Jesus — Only Jesus — The Glory Of His Presence — My Saviour First Of All — Ivory Palaces — Why Should He Love Me So — Sitting At The Feet Of Jesus — Does Jesus Care?

Rudy Attwood may indeed be rated as a "square" but his phrasing is impeccable and those who have enjoyed "The Old Fashioned Gospel Hour" through the years could find his latest album enjoyable and restful. (W.N.W.)

★ ★ ★

**DIE NEUE ARCO ORGEL IM MOZARTEUM ZU SALZBURG. Various organists. Stereo/mono compatible, Pelca PSR-40 539. (From Crest Record Co, 122 Chapel St, St Kilda, Vic 3182).**

If I could read the jacket notes for this imported German recording, I would run less risk of saying the wrong thing. However, I gather that it is one of the Pelca label's "Organ Profile" series and is devoted to the new organ in the Great Hall of Mozarteum in Salzburg. Constructed by Professor Wolfgang von Karajan and by Prof. Oscar Peter in its latter stages, the organ is a magnificent

4-manual instrument which, while satisfying traditional requirements, has nevertheless been designed to offer the greatest possible versatility—as required by the academic staff and by advanced students of the Mozarteum.

In keeping with the "organ profile" theme, the jacket notes deal mainly with the instrument, ending with its specifications—and what a range they reveal, from multiple 32ft stops on the pedals, to 1ft on the positive manual, plus a variety of mixtures and fractionals, seven coupling modes, tremulants on every manual, and whatever else there might be which I failed to work out from the notes!

And the obvious purpose of this album is to reveal the versatility of the organ, its sharpness when required, its attack and clarity and its massive power—all well captured by the recording.

But, let me sound a warning: if you're expecting traditional organ recital music, you're doomed to disappointment.

Item 1, "Transition" (George Pirckmayer) played by Herbert Tachezi, has a modern, almost atonal quality.

Item 2, "Ornamente, Partita fur Orgel" played by Ernst Leitner is somewhat more conventional and displays the organ to advantage, but . . .

Item 3 "Signum fur Orgel" (Gerhard Wimberger) played by Stefan Klinda, is really "way out" and could be transported bodily to the sound track of a science fiction horror film.

Item 4 "Hosanna Filio David" (Cesar Bresgen), also played by Klinda confirms the more traditional scope established by Item 2.

It's an album that should intrigue the classical organ buff but it's scarcely one that will endear him/her to other members of the household—or neighbours if played at the volume level it invites! (W.N.W.)

### Instrumental, Vocal and Humour

**CARISSIMA. Barenboim conducts Elgar with the English Chamber Orchestra. CBS stereo SBR 235774.**

Elgar's music is difficult for many people to appreciate. Its often delicate introspection is often ruined by conductors so that it becomes morbid. Daniel Barenboim succeeds better than most in preserving the true character of the music but still needs to be listened to carefully to be fully appreciated. This record contains both popular and less well-known Elgar compositions and is a good acquisition for those requiring an introduction to this composer. Recording quality is good.

Compositions featured on this disc are: Salut D'Amour — Romance For Bassoon And Orchestra — Rosemary — Carissima — Sospiri, Op 70 — Chanson

De Matin, Op 15 No 1 — Chanson De Nuit, Op 15 No 2 — Elegy for Strings, Op 58 — Serenade In E Minor For Strings, Op 20. (L.D.S.)

★ ★ ★

**ROBERT STOLZ CONDUCTS JOHANN STRAUSS. Wiener Symphoniker. Somerset (Astor) stereo MWC 1007.**

At its worst, the music of Johann Strauss can be awfully hackneyed. At its best, it can be charming. This collection falls into the latter category, fortunately. Little more need be said about apart from the comment that the recording quality is good.

Tracks featured are: Die Fledermaus Overture — Annen Polka — 1001 Nights Intermezzo — Radetzky March — Kaiser Waltz — Unter Donner Und Blitz — Gypsy Baron Overture — Tritsch Tratsch Polka. (L.D.S.)

Reviews in this section are by Neville Williams (W.N.W.), J. Rowe (J.R.), Leo Simpson (L.D.S.), Norman Marks (N.J.M.) and David Edwards (D.W.E.).



## LIGHTER SIDE: Popular cassettes



The QUAD Electrostatic was the first full range electrostatic loudspeaker produced commercially and is still the standard by which all others are judged. Using closely coupled moving elements some two hundred times lighter than the diaphragms of moving coil loudspeakers and being entirely free of cabinet resonances and colouration, this loudspeaker overcomes the usual major problems of loudspeaker design and provides remarkably natural reproduction of sound. This explains why the QUAD electrostatic loudspeaker is used by broadcasting and recording organisations all over the world, in applications where quality is of prime importance, and as a standard of reference by the majority of loudspeaker manufacturers.

QUAD for the closest approach to the original sound.

# QUAD

For details of your nearest dealer write to British Merchandising Pty Ltd, 49-51 York St, Sydney 2000. Or telephone 29-1571.

BM3

**VIENNA, CITY OF MY DREAMS.** Richard Tucker, the Columbia Symphony Orchestra conducted by Franz Allers. Stereo cassette, Harmony (CBS) HMC-545.

Pictured in formal attire, complete with top hat, and backed here by the Columbia Symphony Orchestra, Richard Tucker is very much the traditional dramatic tenor. But don't let that put you off, if it's likely to: his program is eminently listenable and a welcome change for ears that may have had more than a fair dose of TV style vocalists:

Vienna, My City Of Dreams – I Have Been In Love Before – Medley from "Boccaccio" – Roses From Tyrol – Lovesong Of May – Frasquita's Serenade – Yours Is My Heart Alone – Medley For "The Count Of Luxembourg" – In Our Secluded Rendez Vous – Love You Invaded My Senses – Wonderful World – Darling, Trust In Me – I Long For Vienna.

The more I listened to Richard Tucker, the more I felt that he would be a change also from the usual fare one tends to envisage for the car stereo player! Quality is generally good and this is one I must recommend. (W.N.W.)

★ ★ ★

**THE GLITTERING LIBERACE.** Harmony stereo cassette (CBS) HC-1135.

The Liberace who smiles back at you from this particular cassette pack looks to be a much younger man than the one I watched on television recently! I fancy that the program is also "vintage" Liberace, typical highly ornamented piano plus orchestra, done without audience, and punctuated by a couple of

**SPRINGTIME IN MOSCOW.** The Violins of the Bolshoi Theatre conducted by Yule Reyentovitch. HMV Melodiya Concert Classics, stereo SOXLP-30188.

This album of "favourite music" was recorded in the USSR at various times between 1963 and 1968. The choice of familiar, tuneful snippets, the preponderance of strings and the completely unhurried playing would suggest that there is an audience in the USSR also which likes to be soothed during the late evening:

Moto Perpetuo, Op 11 (Paganini) – Humoresque Op 101 No 7 (Dvorak) – Largo (Handel) – Melodie from "Orpheus and Eurydix" (Gluck) – Poem Op 41 No 14 (Fibich) – Variations On A Theme Of Corelli (Kriesler) – Meditation From "Thais" (Massenet) – Melody In F (Rubenstein) – Vocalise Op 34 No 14 (Rachmaninov) – Valse Triste From "Kuolema" (Sibelius) – Romance From "The Gadfly" (Shostakovitch) – Perpetuum Mobile (Novacek).

Because of their age and lack of

vocals in his better-than-average bathroom baritone:

Cornish Rhapsody – Traumerei – Lieberstraum – Gershwin Medley – Sonata No 9 – Concerto In B-Flat Minor – Rhapsody In Blue – Sincerely Yours – El Cumbanchero – Minuet In G – Tea For Two – Polonaise In A-Flat – Beer Barrel Polka.

In terms of quality, I was conscious of vague wow effects here and there but, overall, the sound is adequate for casual, or background listening, or for use in the family car. (W.N.W.)

★ ★ ★

**HOLIDAY WITH JAMES,** the Sid Sidney Orchestra. Contata cassette, Dolby stereo A-113. (From Goldring Sales & Service in all capitals.)

Make of it what you like – James Last or James "Harry" – but what you actually get is a string of medleys played by the Sid Sidney Orchestra, plus chorus, plus an audience that claps and talks and carries on in a "we're really enjoying it" manner. I doubt that many people would consciously select this one to play in the home but it would probably come off much better in the family car on holiday!

There are far too many titles to permit them being listed here but a few that catch the eye include: Delilah – What Now My Love – Puppet On The String – Strangers In The Night – Love Is Blue – What A Wonderful World – Cielita Lindo – La Cucaracha.

Quality is average but adequate for a tape which mainly seeks to put you alongside a big band and an audience having fun. (W.N.W.)

ambience, in some cases, the recordings are not noteworthy for their quality but, heard as a gentle background, the sound is adequate and many could find it thoroughly relaxing and enjoyable. Generous background notes are provided by W. A. Chislett. (W.N.W.)

★ ★ ★

**LOS REALES DEL PARAGUAY.** The South American Way. Astor stereo GGS 1486.

Combine a Paraguayan harp, two guitars plus assorted percussion and Hammond organ plus the zesty voices of the "Kings of Paraguay" and you have the ingredients for some of the brightest Latin-American music ever produced. Recording quality is very good.

There are twelve tracks in all: Llevame Contigo (Take Me With You) – Numa 1 – Y Viva Espana – Yo Vendo Onos Ojos Negros – Centavos Y Pesetas – Vaya Con Dios – Aquellos Ojos Verdes (Green Eyes) – Alla En El Rancho Grande La Bamba – Na Juana – La Paloma – Que Sera – Hasta La Vista. (L.D.S.)



**THE AMAZING BAVARIAN STOMPERS. Stereo, Astor Golden Hour GH 597.**

If your musical fancy runs to oompah-pah German bands this hour long record of medley style tracks of mainly non Bavarian music may be worth an audition. The sound quality is reasonable, considering the amount of dynamic compression that must take place to cram 30 minutes on each side, there being over 40 titles under 16 headings.

Some of these are: Happy Wanderer - Wooden Heart - Der Treue Husar - Daisy Bell - My Bonny Lies Over The Ocean - Liechtensteiner Polka - Tavern In The Town - Little Brown Jug - Colonel Bogey - So Leben Wir - In Munchen Steht Ein Hofbrauhaus - Liberty Bell - Nach Tausen - Life On The Ocean Wave - Rule Britannia. A party sing-along starter would be a good description. (N.J.M.)

**QUADRAPHONIC ALBUMS**

**TUBULAR BELLS. Mike Oldfield. QS matrix quadraphonic, Virgin (Festival) L-35127.**

Entering the rock music scene at the age of 14, Mike Oldfield first played in a family group, then formed "Barefeet" which lasted a mere two years, and landed him back into routine session work. At 17 he began to develop the idea of his first major composition—"Tubular Bells"—a full orchestral work which he was to do virtually alone, by means of overdubbing. His first effort, made with a 4-track recorder, aroused interest, but that was all. So he did it all again with better equipment and, just when it seemed like bombing out, "Tubular Bells" suddenly took off and raced to the top of the charts with sales of around five million.

Described somewhere as "symphonic rock", the mood of the first side is relatively subdued—a reflection, presumably, of Oldfield's natural reserve at the time, and his tendency to escape into a tranquil world with the very guitar that at other times would belt out solid rock.

But the tranquility gives place to abrupt changes of mood and theme. It's a characteristic that becomes more plainly evident on side 2, which ultimately explodes into a maelstrom of rock sound, switches back to organ, then to a frantic jig and, just when it would seem to be all over, into a weird background sound. I guess it's this smorgasbord of mood and theme that has captivated listeners around the world, added to the thought that it's largely the concept and creation of one man, with just a little help beyond the 17-odd instruments he plays himself, plus the odd vocal sound effect.

The quality is okay and, if you have a 4-channel outfit, you may as well get this quadraphonic version, the more effectively to get yourself submerged in the Oldfield sound. (W.N.W.)

**I ONLY HAVE EYES FOR YOU. Tony Mottola, guitar. Matrix quadraphonic, Project 3 (Festival) LQ-35839.**


While Roy Atkinson of Festival had most to say about their quadraphonic version of "Tubular Bells", it was this one by Tony Mottola that caught my admittedly square ears, perhaps by way of relaxation!

Produced by Enoch Light and with backing by such well known associate instrumentalists as Dick Hyman, Vinnie Bell, Phil Kraus, Jule Ruggiero and Ronnie Traxler, it is very musical, undemanding and very easy on the ear. The track titles include: I Only Have Eyes For You - One - Send In The Clowns - Don't Stand A Ghost Of A Chance With You - What Did I Do For Love - Jelly Belly - Our Day Will Come - Time In A Bottle - The Most Beautiful Girl - Solace - A Stranger In The Town - Love Won't Let Me Wait.


While the sound is pleasant, what will really catch the ear of any hifi fan is the complete freedom from stress or distortion and the way it all emerges out of absolute silence. The even dynamics would have helped but Enoch Light has a name for this kind of quality. And the quadraphonics? What if it does exaggerate the dimensions of the guitar here and there, it keeps Tony Mottola out front while the other musicians sit around the room doing their gentle thing. Recommended. (W.N.W.)

Mike Oldfield's  
masterpiece  
**TUBULAR  
BELLS**

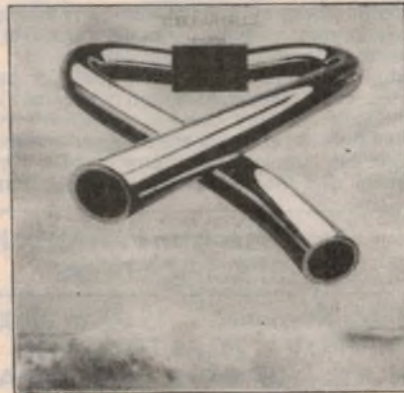now available on  
**4 CHANNEL STEREO**  
QS MATRIX SYSTEM



Virgin Q 35127

 

**Selected Titles From Festival's Quadraphonic Catalogue**

Project 3 Quadraphonic Test Record as Reviewed by Electronics Australia Q 35182

4 Channel Demonstration Album		The Brass Menagerie	
Enoch Light Orch.	Q 34459	Enoch Light	Q 34493
4 Channel Musical Sampler - V.A.	Q 34460	Breakthrough	
Disco Disque - Enoch Light Orch.	Q 35663	Louis Benson Orch.	Q 33113
Warm Wild And Wonderful		Carole King - Music	Q 34435
Tony Mottola	Q 33045	Swing And Sway - Sammy Kaye	Q 34744
Superstar Guitar - Tony Mottola	Q 34494	4 Channel Goes Poo	
Big Band Hits Of The 20s		Greenwich Strings	Q 34849
Enoch Light Orch.	Q 34467	Hawaiian Gold	
Big Band Hits Of The 30s		Tennessee Guitars	Q 35009
Enoch Light	Q 34297	Future Sound Shock	
Big Hits Of The 70s - Enoch Light		Enoch Light Orch.	Q 34944
2 Record Set	Q 45665/6	Beagle Classics	
Movie Hits - Enoch Light Orch.	Q 34611	Enoch Light Orch.	Q 35251

Superlative Sounds of the 70's





NEW RELEASE !!!



# G.H.E. PRECISION parabolic Cartridge

- PRECISION POLISHED NATURAL DIAMOND STYLUS ENGINEERED IN WEST GERMANY
- GREATER CLARITY AND DEFINITION
- REDUCED SURFACE NOISE
- INCREASED STYLUS AND RECORD LIFE

After hundreds of hours of laboratory testing, G.H.E. in conjunction with the parabolic specialists, have selected this cartridge as that which most compliments the features of the precision parabolic stylus. In A/B testing with high quality cartridges costing over the one hundred dollar mark we believe that it parallels and exceeds their performance in subjective listening tests. Come in and compare for yourself with the G.H.E. multi-cartridge comparator.

## G.H.E. Precision PARABOLIC SPECIFICATIONS

- Freq. Response — 15 HZ to 25,000KHZ
- OUTPUT — 7Mv ● TRACKING ANGLE — 15° ● CHANNEL BALANCE — within 1.5dB ● Tracking Force — 1 to 2 grams.

**Price \$53**

### SPECIAL RELEASE OFFER!!!!!!

Free post and packing Australia wide—

ENCLOSED IS CHEQUE FOR \$.....

NAME.....

ADDRESS.....

# G.H.E.

966-968 HIGH ST, ARMADALE,  
MELBOURNE, VIC, 3143.  
TEL 509 0374, 509 9725



## LIGHTER SIDE—continued

**THE WORLD OF CHILDREN'S CLASSICS.** Various artists, conductors, orchestras. Stereo, Decca SPA-366.

The titles and the little blond miss on the cover seek to classify the album but I really wonder how many such kiddies in the home environment would choose to listen to it, despite the "animal" titles; in school, maybe, but seldom at home. Even "Peter and the Wolf" is presented minus the narration. The full track list:

Carnival Of The Animals (Saint-Saens) — The Little White Donkey (Ibert) — Puss-In-Boots And The Little White Cat (Tchaikovsky) — Flight Of The Bumble Bee (Rimsky-Korsakov) — Sheep May Safely Graze (Bach) — Trout Quintet Theme & Variations (Schubert) — Peter And The Wolf (Prokofiev).

They're all very well known, of course, and all very well played, but I would suspect that they'd be enjoyed more by the adult kids in the home than the real ones! Compiled from Decca's extensive classical repertoire, the recordings date from as far back as 1958, but don't let that deter you. The quality, even now, is a reminder of just how far ahead Decca was in those days. And George Malcom's version of Bumble Bee on harpsichord (1962) is a "bottler".

Call it what you like, it's a typical, easy listening collection of evergreen classical snippets. (W.N.W.)

★ ★ ★  
**HIGHLIGHTS FROM THE MERRY WIDOW BALLET.** Franz Lehar. The Adelaide Symphony Orchestra and Adelaide Singers conducted by John Lanchbery. HMV stereo SAN 7588.

This record is destined to become a collector's item. The world premiere of this balletic version of The Merry Widow was given by the Australian Ballet in Melbourne on the 13th November, 1975. This recording was produced in conjunction with the ABC in the ABC studios, Adelaide.

And while I cannot comment on the standard of the ballet in this Australian production I can state that the musical arrangements are very bright and fresh. In fact, I liked this version more than the original operetta. Recording quality is superb and a credit to the ABC and EMI. (L.D.S.)

★ ★ ★  
**THE VERY BEST OF BRASS.** Studio 2 Stereo TWOX 1048. EMI Release.

I don't recommend this record if you have a headache or are feeling a bit fragile after the night before, as the band comes on strong on every track, with sixteen brass standards like: The Stars And Stripes Forever — The Dam Busters — Grand March From 'Aida' — Radetzky March — The Liberty Bell — Blaze Away — Men of Harlech. The tracks are taken from masters ranging from 1963 to 1975 and the band or bands remain anon.

The stereo image is quite noticeable on some tracks and overall quality is quite good, making it an excellent record to give to that brass band enthusiast you know. Or else buy it to get your own back on the neighbours! (N.J.M.)

★ ★ ★  
**RICOCHET.** Tangerine Dream. Virgin Records L 35736. Festival release.

This is another offering from Tangerine Dream, the German electronic music specialists. This one was recorded live in England and France late in 1975. As is usual with their records, there are no definite tracks, the whole album is intended as a continuous piece of music, which flows smoothly from one segment to the next.

As one would expect, a large number of synthesisers of various sorts have been used to produce the usual synthesiser type sounds. But don't get me wrong, this record is not just a collection of sounds, it is a blended whole, and should be listened to as such.

This style of music obviously appeals to a limited audience. I have not as yet decided whether or not I belong in this class, so I have not been able to come to a definite conclusion about this record. Technically, however, the production is excellent, with good tonal balance, and little background noise. (D.W.E.)



**NO EARTHLY CONNECTION.** Rick Wakeman and the English Rock Ensemble. A & M Records L 35885. Festival Release.

This is another concept album from Rick Wakeman, following on from his earlier efforts, "Journey To The Centre Of The Earth" and "The Myths And Legends Of King Arthur And The Knights Of The Round Table". Musically, this piece seems to differ only slightly from his earlier works, and it gives the overall impression of staleness.

"I've always believed that if you

provide something for the eyes as well as the ears, there's more chance of getting people to pay attention to the music", Rick is quoted as saying. To me, however, it seems that this album is rather like the sound-track of a B-grade movie, purposeless if you haven't seen the movie.

In the case of this album, the accompanying lyrics and pictures do help to fill in a few of the gaps, but do not seem to give the music the lift it requires. Summing up, this album will undoubtedly appeal to devoted fans, but will be

unlikely to win any new ones. As usual with Festival releases, record quality is excellent. (D.W.E.)

★ ★ ★

**NAT KING COLE.** The King Cole Trio. Trip TLP-5811. Distributed by Astor Records.

Before Nat King Cole became really popular in the fifties as a singer he saw some hard times. He played piano and did the occasional vocal in the King Cole Trio which was formed in 1939. Do not expect high quality sound from this album as it is remastered from 78's made back in the 40's. It makes pleasant listening if you make allowance for the quality and provides an interesting insight into Nat King Cole. Buyers will also appreciate the well written album notes.

Track titles are as follows: Slow Foot Joe - 1-2-3-4 - Crazy 'bout Rhythm - Off The Beam - King Cole Blues - Jiving With The Notes - Early Morning Blues - Bed Time - Honey Hush - French Toast - Vine Street Jump - B Flat Blues - You Send Me - Love Is My Alibi - Pogo Stick Bounce. (L.D.S.)

## Reader's Digest: Popular organ

**21 POPULAR ORGAN FAVOURITES.**

Various organists and instruments. Stereo, Reader's Digest, record RD4-130. Also on cassette RDCP4-131. Price in both cases \$2.99 post-free from Reader's Digest, Box 65, GPO, Sydney 2001.

While this collection will most obviously appeal to enthusiasts of the popular organ, it could also find a place as a typical organ disc in the average collection. Old-timer Reginald Dixon opens in fine style with his famous Black-pool Ballroom pipe Wurlitzer, and provides four other tracks as well. The remaining tracks use electronics: Richard Wayne and Ken Griffen play Hammonds, Richard Wayne (again) and Harry Stoneham play Lowreys, while Bob Benson features on a Baldwin.

Track titles include Happy Days & Sally - Summer Samba - Don't Get Around Much Anymore - Take The "A" Train - Hawaiian War Chant - If You Knew Susie - You Can't Be True, Dear - Tennessee Waltz - Patricia - Tip Toe Through The Tulips - Love Letters In The Sand - Tico, Tico - Cruising Down The River - In The Good Old Summer Time - Bali Ha'i - In A Little Spanish Town - Anniversary Song - Four Leaf Clover & Bye Bye Blackbird.

As you can see, you get quite a lengthy program, for your money, of good average popular organ music, and the opportunity to compare styles and instruments - with the odds favouring

Reginald Dixon and his big traditional Wurlitzer.

Having both disc and cassette available, I was able to play them simultaneously and make instant A-B comparison. They're both okay but, if you have a good magnetic cartridge, take the disc, which also provides jacket notes. (W.N.W.)

### YOU ARE ABOUT TO REPLACE YOUR STYLUS SO STOP AND READ THIS

Our product is the famous Parabolic stylus and is so tiny that you can hardly see it!

—Yet its performance is **BIG . . . . . VERY BIG.**

Here's what they're saying about it . . . . .

"Heard detailed sound such as never before"—*Melbourne Audio News*  
"Vastly superior performance . . . significant and sometimes dramatic improvements in fidelity"—*Electronics Today International*

"The most detailed treble I have yet to hear from records"—*Hi-Fi Review*

To obtain such performance for yourself post your stylus assembly or cartridge at once with a cheque for \$40.75 to Bay Road Electronics, 36 Luxmoore Street, Southland Centre, VICTORIA 3192. (03) 93 1201.

We will post back your unit promptly with a Parabolic stylus fitted.

Melbourne clients ring 93 1201 for nearest agent.

Join our many hundreds of delighted clients!

# DECCA

## Record Cleaner WORKS AS YOU PLAY...

This new DECCA Record Cleaner removes dust and grit as your record spins on the turntable. It consists of an arm carrying a brush made from a newly-developed man-made fibre. Its "bristles" are incredibly fine, incredibly soft yet strong, and are also electrically conductive to remove static as well as dust. The result - improved sound quality, reduced record wear.

\*\$13.95 at hi-fi stores and record bars.

Australian agent: British Merchandising Pty. Ltd.,  
49-51 York Street, Sydney. Telephone 29 1571.

\*Recommended retail price.





# New Products

## Yaesu Musen Communications receiver

For those on the lookout for a modern, general purpose communications receiver, the Yaesu Musen FRG-7 is well worth closer investigation. It is compact, self-contained and employs the now well known Wadley Loop principle to provide stable and predictable coverage of the frequency range from 0.5MHz to virtually 30MHz.

The Wadley Loop principle was described in detail some years ago by Ian Pogson, as a preamble to his description of the Electronics Australia "Deltahet" receiver. (Ref. Electronics Australia, June 1963, January 1971.) The principle is also explained in the instruction book which accompanies the receiver, the most obvious differences being in the choice of intermediate frequencies.

Conforming to the Wadley Loop configuration, the FRG-7 is essentially a triple-change superhet. Incoming signals between 0.5 and 30 MHz pass through an RF amplifier stage and then are fed to an up-converter which shifts them into the first IF channel having a pass-band 1MHz wide centred on 55MHz.

These signals are heterodyned, in turn, by a frequency of 52.5MHz approx., synthesised from a mix of the first variable tuned oscillator (serving the up-converter) and the harmonics of a 1MHz crystal locked oscillator. This time, the signals are down-converted into a second IF channel, again 1MHz wide but centred on 2.5 MHz.

By making both conversions dependant on the one tuneable oscillator, it is possible to arrange matters so that any drift in the front-end circuitry tends to cancel, ensuring that the second IF resultant will be rock steady.

A tuneable oscillator in the range 2455 to 3455kHz, which can be expected to be intrinsically stable, is used to down-convert to 455kHz and to a conventional circuit configuration thereafter.

In terms of the panel controls, the most obvious result of this unusual circuit configuration is that the tuning dial for the second variable oscillator 2455 to 3455 can become the main "bandspread" dial always covering exactly 1MHz and with an appropriate 1MHz bandspread scale calibrated to every 10kHz. In effect, this dial serves to display any 1MHz segment of the total frequency range (0.5 to 30MHz) as selected by the front end.

As might be expected, a different



The Yaesu Musen FRG-7 is compact and self-contained. The preselect dial (top left) is used in conjunction with the bandswitch below it. Alongside it is the MHz selector which is used in conjunction with the "lock" indicator light. In the centre is the main bandspread dial with the S-meter just above it. The remaining switches and knobs are as mentioned in the text.

tuning procedure is used: To select a certain frequency—say 14.12 MHz—the band switch is set to position D covering 11-29.9MHz.

The Megahertz knob is rotated next to bring the 14MHz figure under the hairline in the MHz window. When it is properly set, an adjacent red "Lock" indicator light goes out.

The Preselect knob is now adjusted to bring up the desired frequency indication in its window, after which the main tuning dial can be set to 120kHz to produce the final figure of 14.120MHz.

It sounds complicated but it only takes a few minutes to become accustomed to the procedure, after which a frequency can be dialled or read-off without hesitation, and in the knowledge that it will be substantially accurate and will stay put!

Other controls include a volume control and a mode switch, the latter providing for upper sideband and CW reception, lower sideband, ordinary AM,

and AM with automatic noise limiter in circuit.

Four panel switches provide optional attenuation for very strong signals, three settings for audio bandwidth, an on-off switch for the panel lighting and a general on-off switch which is effective for both external power and for internal batteries where these are being used as an alternative supply.

A phone jack is provided for private listening and insertion of the phones cuts out the loudspeaker automatically. The "Record" jack above it provides about 50mV of signal for an external tape recorder irrespective of the setting of the volume control.

Internally, the circuitry involves 2 integrated circuits, 9 FETs, 13 transistors, 14 diodes and 2 zener diodes. Normal operation is from the AC power mains, but alternatives include an external negative earth 12V supply or 8 internally fitted UM1 type dry cells. Voltage regulation is effective in all modes. Overall size is

340mm (W), 153mm (H) and 285mm (D), and weight without batteries is 7kg.

For broadcast band listening (0.5 to 1.6 MHz) an ordinary high impedance (long wire) aerial is assumed. For frequencies above 1.6 MHz, the makers have provided for an input of 50 ohms unbalanced, on the assumption that, for some applications at least, a resonant dipole will be used. Provision is also made for an earth connection and for muting when the receiver is paired with a transmitter.

Manufacturer's specifications put the sensitivity as better than 0.7 $\mu$ V for SSB/CW for a S/N of 10dB; better than 2 $\mu$ V at S/N 10dB for AM. Selectivity is given as  $\pm$  3kHz at -6dB and  $\pm$  7kHz at -50dB. Stability: Less than  $\pm$  500Hz at any 30 minutes after warm-up. Audio output: 2 watts into 4 ohms.

As supplied, the FRG-7 comes complete with a 16-page instruction manual and a large fold-out circuit diagram. The manual contains a general description,



specifications, user instructions, a description of the circuit principles, alignment and maintenance details, voltage chart and parts list. An additional loose sheet indicated means of setting the dial calibration to any available standard frequency signal.

As distinct from bench measurements, which we were prepared to take for granted, in this case, two members of our staff adopted the user approach and simply took the receiver home to see how it performed under typical conditions.

While we had the advantage of being familiar already with the Wadley Loop system, our impression is that it would take very little time for even the uninitiated to become thoroughly at home with the tuning procedure. In fact, provided the user can think in terms of frequency—and what amateur and DX listener can't—the system is likely to be less confusing than the more usual bandset/bandspread/calibrate system where all the calibrations are interdependent.

As it was, we found that the receiver could be set to any frequency using 10kHz calibration marks, or interpolating for intermediate figures. Calibrations generally were within the tolerance one normally puts down to parallax and there was certainly no urge to attempt to adjust them more precisely.

All controls worked smoothly, with tuning on SSB signals needing care but

not posing any problem for the initiated operator.

The selectivity was somewhat down on that of our own "Deltahet" design and it was therefore not able to separate out congested signals quite as well. With only one ceramic filter at 455kHz, the designers have apparently settled for a passband which will give reasonable selectivity in a communications role, without being too sharp on normal double sideband AM.

On the other hand, they have exercised a lot of care with that bugbear of multi-change superhets—spurious responses. While we did not search the whole spectrum diligently for them, they were certainly not evident in ordinary usage.

That phrase "the whole spectrum" is itself significant. The FRG-7 does give complete, fully calibrated, bandspread coverage of the whole spectrum. The purchaser does not face an agonising choice as to what parts of the spectrum he really wants to cover, or over what parts the bandspread is to be most effective. The FRG-7 would therefore seem to be an excellent choice for the listener who wants to listen to almost anything going, anywhere in the HF spectrum.

Further details of the Yaesu Museu FRG-7 can be obtained from Bail Electronic Services, 60 Shannon St, Box Hill Nth, 3129 Vic. (WNW & ILP)

## DIGITAL CLOCK KIT FROM TANDY

Currently available from Tandy Electronics is a complete kit for an electronic digital clock, priced at \$19.95. An attractive project, it can be assembled by a home handyman, who does not need to have any special electronic skills to complete the job.



Branded "ArcherKit", an associate company of Tandy and Radio Shack in America, the project comes as a boxed set complete with general construction hints and a fully illustrated step-by-step construction guide. Typically, construction would involve about three evenings' work, although it could be completed in shorter time if one really tried.

The clock takes its timing pulses from the mains. Links on the board accommodate to either 50Hz or 60Hz, the former being appropriate for Australia. The constructor also has the option of 12-hour or 24-hour display, time being shown in hours, minutes and seconds.

The kit contains two printed circuit boards, the larger one carrying the 24-pin LSI clock chip (MM5314) already mounted. All other components are "discrete": 9 diodes, 20 transistors, 37 resistors and 4 capacitors, plus sundry hardware. Mounting all these takes time and patience, but it is also a practical lesson in assembly for those who are keen

to gain experience along these lines.

Needless to say, the instruction book should be carefully studied before construction begins.

The actual time is displayed on six 7-segment fluorescent readout tubes, as distinct from LEDs. They provide a blue-green display which can be seen clearly, even in a brightly lit room. A switch at the rear allows the display to be dimmed or switched off, which is just as well, because it is bright enough to double as a night light in a darkened room!

Other controls on the back of the clock offer two speeds of fast forward cycling for rough time setting, and a hold switch allowing the clock to be restarted in synchronism with a time signal.

The ArcherKit electronic digital clock kit (Cat. no. 28-4040) is currently available from Tandy stores throughout Australia. In the event of difficulty, Tandy can provide a back-up service, while spare parts should be available for at least 5 years. (W.N.)



TRIMMER POTENTIOMETERS

SERIE PT

PT 10



PT 10 h (2'5)



PT 10 v

PT 15



PT 15 h (2'5)



PT 15 v (12,5)

Piher Trimpots are available  
Interstate from:—

VICTORIA

Zephyr Products Pty. Ltd.  
PH. 568 2922.

SOUTH AUSTRALIA

Graphic Electronic Industries  
Pty. Ltd. PH. 42 6655

QUEENSLAND

Fred Hoe & Sons Pty. Ltd.  
PH. 277 4311.

NEWCASTLE

Digitronics, PH. 69 2040.



ELECTRONIC  
DEVELOPMENT  
SALES PTY. LTD.  
27 BUCKLEY ST.,  
MARRICKVILLE.  
N.S.W. 2204

EDS 517007



# FERGUSON

Manufacturers of:  
Electrical / electronic  
equipment, wound  
components and  
lighting control  
equipment.

**BRANCHES  
IN  
ALL STATES**

**Ferguson Transformers  
Pty Ltd.**

Head Office  
331 High Street, Chatswood  
NSW 2067

PO Box 301 Chatswood,  
NSW, Australia 2067

Phone: 02-407-0261

## NEW PRODUCTS

### Dynatel 500 telephone cable locator

The Dynatel 500 is a new concept in telephone cable location and identification. When combined with Dynatel's 710A Portable Cable Resistance Fault Finder, fault location time is greatly reduced, even in congested joint service areas.

The Dynatel 500 features a silent test tone transmitter which avoids interference to adjacent working lines and minimises the "pulling effect" of adjacent pipes and cables. The same concept makes the 500 immune to power line interference, prevents audible noise on the line under test, and permits tests even while the line is in use.

The transmitter output can be coupled to the line under test by means of a unique "Dynacoupler". This device makes it extremely simple to place tracing tone on any cable without removing the shield bonding or ground.

The Dynatel 500 is designed to make operation and hookup simple, safe procedures. The lightweight receiver unit is made for one-handed operation and features fingertip adjustment controls plus an easy to read meter. There are no clumsy wands, cords or ground rods. An integral monitor speaker with volume control and earphone jack is provided.



Both null and peak readings can be made at the flick of a switch, depending on the nature of the locating job. In addition, the 500 offers a highly accurate vertical depth measurement technique that is superior to the 45° triangulation method.

For further information contact Aegis Pty Ltd, PO Box 49, Thornbury, Vic 3071. Telephone 49 1017.

## TTL FROM TECHNIPARTS

### TTL DIGITAL

Type	Description	Price Ea.	Type	Description	Price Ea.	Type	Description	Price Ea.
7400N	Quad 2-Input NAND Gates	.45	7451N	Dual 2-wide 2-Input AND-OR INVERT Gates	60	74164N	8 bit Serial In/Parallel Out Shift Register	3.10
7401N	Quad 2-Input NAND Gates open collector	.45	7453N	Expandable 4-wide AND-OR INVERT Gates	.60	74165N	8 bit Serial In/Parallel Out Shift Register	3.10
7402N	Quad 2-Input NOR Gates	.45	7454N	4-wide AND-OR-INVERT Gates	.60	74166N	8 Bit Parallel In/Serial Out Shift Register	3.97
7403N	Quad 2-Input NOR Gates open collector	.45	7460N	Dual 4-Input Expander	.60	74174N	Hex/Quad D FF with clear	3.10
7404N	Hex Inverter	.45	7470N	AND JK Pos Edge Trigger FF Present and clear	1.00	74175N	Hex/Quad D FF with clear	4.55
7405N	Hex Inverter open collector	.45	7472N	AND JK Master Slave FF Present and clear	.76	74176N	Presetable decade and binary counter	3.16
7406N	Hex Inverter open collector High Voltage	1.15	7473N	Dual JK FF with clear	.76	74177N	Presetable decade and binary counter	3.16
7407N	Hex Inverter open collector High Voltage	1.15	7474N	Dual D Pos Edge Trigger FF Present and clear	.76	74180N	9 Bit Parity generators/checkers	4.30
7408N	Quad 2-Input AND Gates	.45	7475N	Quad Latch	1.20	74181N	Arithmetic Logic Unit/Function Generator	12.00
7409N	Quad 2-Input AND Gates open collector	.45	7476N	Dual JK FF Present and clear	.95	74184N	BCD to Binary and Binary to BCD Convertors	4.36
7410N	Triple 3-Input NAND Gates	.45	7483N	4 Bit Binary Adders with fast carry	1.80	74185AN	BCD to Binary and Binary to BCD Convertors	4.36
7411N	Triple 3-Input AND Gates	.55	7485N	4 Bit Magnitude Comparators	4.74	74190N	Synchronous Up/Down Counters with Mode Control	3.85
7413N	Dual 4-Input NAND Schmitt Triggers	.78	7486N	Quad Exclusive-OR Gates	.95	74191N	Synchronous Up/Down Counter with Mode Control	3.85
7414N	Hex Schmitt Triggers	4.30	7490N	Decade and binary Counter	.90	74191N	Synchronous Up/Down Counter with Dual Clock	3.00
7416N	Hex Buffer Open collector High Voltage	1.30	7491AN	8 Bit Serial Shift Register	1.40	74193N	Synchronous Up/Down Counter with Dual Clock	3.00
7417N	Hex Buffer Open collector High Voltage	.80	7492N	Decade and Binary Counter	1.00	74194N	4 Bit Bidirectional Universal Shift Register	3.80
7420N	Dual 4-Input NAND Gates	.45	7493N	Decade and Binary Counter	1.00	74195N	4 bit parallel Access Shift Register	1.75
7425N	Dual 4-Input NOR Gates	1.00	7495N	4 Bit Parallel Access Shift Register	1.80	74196N	Presetable Decade and binary counter	2.40
7426N	Quad 2-Input High Voltage NAND Gates	1.05	7496N	5 Bit Shift Register	2.00	74197N	Presetable Decade and binary counter	3.16
7427N	Triple 3-Input NOR Gates	1.00	74107N	Dual JK Master Slave FF with clear	1.10	9001	JK Master Slave FF	1.50
7430N	8-Input NAND Gates	.45	74121N	One Shot Multivibrator	.80	9368	5 bit latch BCD to 7 Segment decoders	3.20
7432N	Quad 2-Input OR Gates	1.00	74123N	Dual Retriggerable one shot multivibrator with clear	1.80			
7437N	Quad 2-Input NAND Buffers	1.00	74141N	Use 7441N				
7438N	Quad 2-Input NAND Buffers open collector	1.15	74145N	Use 7445N				
7440N	Dual 4-Input NAND Buffers	.45	74147N	Use 7447N				
7441N	BCD to Nixie Driver/Decoder	1.80	74148N	Use 7448N				
7442N	BCD to Decimal Decoder	1.20	74150N	Data Selectors-Multiplexer 1 of 16	3.29			
7445N	BCD to Decimal Decoder/Driver 80MA Sink	4.24	74151N	Data Selectors-Multiplexer 1 of 8	1.70			
7446N	BCD to Decimal Decoder/Driver Comm Anode 40MA Sink 30V	3.04	74153N	Dual 4 to 1 line Data Selector-multiplexer	1.60			
7447N	BCD to Decimal Decoder/Driver Comm Anode 40MA Sink 15V	1.50	74154N	4 to 10 line Decoder multiplexer	2.90			
7448N	BCD to Decimal Decoder/Driver Comm Cathode 6MA Sink 5V	2.00	74155N	Dual 2 to 4 line Decoder Multiplexer	2.60			
7450N	Dual 2-wide 2-Input AND-OR INVERT Gates	.60	74157N	Quad 2 to 1 line Data Selector multiplexer	1.70			
			74160N	Synchronous 4 bit counter	2.78			
			74192N	Synchronous 4 bit counter	2.78			
			74162N	Synchronous 4 bit counter	2.78			
			74163N	Synchronous 4 bit counter	2.78			

**TECHNI  
PARTS**

Woolworths Arcade,  
95 Latrobe Terrace,  
PADDINGTON. 4064  
P.O. Box 118,  
PADDINGTON. 4064  
Ph: Brisbane (07) 36 1474  
Trading Hours (8.30am - 5.00pm  
Mon. - Fri., 8.00am - 11.15am Sat.)



## Weston 551M marine radio telephone


The recent introduction of a VHF marine radio service (see EA, September 1976) has created a demand for commercial equipment to suit this service. Recently submitted to us for review was the Weston model 551M marine radio telephone.



The model 551M is an all-Australian product designed to meet the exacting specifications laid down by the authorities for mobile radio telephones in general, and those for the marine service in particular. In fact, the 551M is a modification of the well established and proven model 551 land mobile unit. This unit earned the coveted Good Design label of the Industrial Design Council of Australia.

The 551M is an all solid state unit with an impressive list of specifications. It is designed for use in the 156 to 174MHz band and can be fitted with up to 10 channels, within a bandwidth of 500kHz. It operates from a conventional 12V electrical system as normally available in most vessels, being actually designed around a voltage of 13.8,  $\pm 10\%$ . On standby, with no signal, the receiver draws 0.1A.

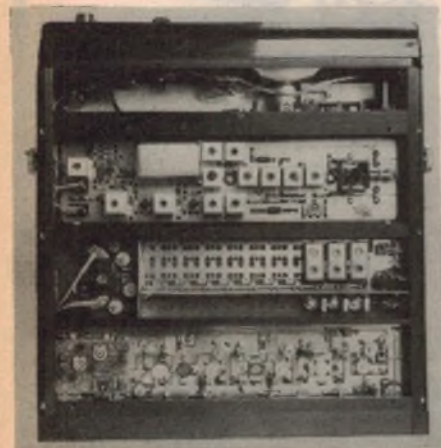Other receiver specifications are: Usable sensitivity, better than 0.4 $\mu$ V for 12dB SINAD. Quieting sensitivity, better than 0.5 $\mu$ V for 20dB. Squelch sensitivity, better than 0.35 $\mu$ V. Adjacent channel selectivity,  $-85$ dB.



The Model 551M is all solid state and features rugged, modular construction.

The audio power output is 3W with a distortion of less than 5%. The frequency response follows a 6dB per octave deemphasis characteristic (+1,  $-3$ dB), which is complementary to the transmitter characteristic, within the range 300 to 3000Hz.

The transmitter has two power output levels: 25W and 1W. Current drain on transmit is 4A for the 25W position and 1.5A on the 1W position. Deviation is  $\pm 5$ kHz (max.) and spurious emission is less than 2.5 $\mu$ W.

The complete unit measures 76mm (H)  $\times$  268mm (W)  $\times$  297mm (D) and weighs 4.1kg. It may be mounted in any position and comes complete with substantial mounting cradle and brackets, microphone, whip antenna with coax cable and connector, and battery cable with connector.

The unit is very solidly made and employs a modular form of construction, which simplifies modifications to suit individual customers' requirements and also simplifies service.

Optional extras include a remote handset, or a remote control unit, for use where it is desired to mount the main unit in an out-of-the-way location. Selective calling can also be fitted, eliminating the nuisance of irrelevant traffic on shared frequencies.

A sample unit was set up in our own laboratory and, even when connected to an aerial inside the building, on a shelf immediately above it, provided clear signals from both land based and mobile marine transmitters.

Overall, our impression is one of a well designed, ruggedly constructed unit which should stand up to years of hard work in a marine environment.

Price, including two mandatory channels, and sales tax, is approximately \$680.00. Additional channels cost \$35.00 each.

Further details from Weston Electronics Company, 215 North Rocks Rd, North Rocks, NSW, 2151. (P.G.W.)

**BUILD THIS  
RECHARGEABLE  
CALCULATOR  
for just \$18.95\***

**including separate,  
tailored desk set**



### FUN TO BUILD & SUPERB QUALITY

Build this Heathkit battery-operated portable calculator. Comes with separate battery charger plus tailored executive desk set with built-in charger, note pad and Schaeffer pen. Complete assembly instructions included.

Check the functions. Nickel-cadmium batteries give five to eight hours' use between charges. Unit can be left connected to desk set charge for indefinite operation. 8 digit capacity. 4 arithmetic functions. Full floating decimal. Constant key. Negative answer indicator. Battery saver circuitry. Low battery indicator. And best of all — the calculator you build yourself is the calculator you service yourself!

**\*ORDER BY COUPON OR COME  
TO OUR SHOWROOM NOW!**

220 Park St., South Melb. Phone 699 4999

400 other kits: Call & collect your free 96 page catalogue.

PLEASE SEND ME:

Heathkit electronic calculator kit IC-2009.

Cheque/money order for \$ \_\_\_\_\_ enclosed.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

P/CODE \_\_\_\_\_



**HEATHKIT** KIT CENTRE

P.O. BOX 35, South Melbourne, Vic. 3205

EA 76



# printed circuits

- Accurately machine printed / etched
- Phenolic & fibreglass-gold / tin plated
- Special manufacturers packs of 10
- EA R & H. ET, Philips, Mullard available
- Specials to your drawing
- POSTAGE: small 60c large \$1 00

78PC9	4.40	78EX10	2.80	ET602	6.50
ET448	2.50	ET533A/C	3.50	ET533A/C	3.50
ET448	2.50	ET553C	2.00	ET533A	2.60
ET711	7.60	ET543B	2.50	ET543A	2.50
ET445	2.60	ET241	2.80	ET780B	2.50
ET780A	3.00	ET541	2.50	ET444	2.50
78SA7	2.50	78M17	2.50	78LM5	2.60
78SS8	3.00	78SW4	2.00	78R4	2.50
78M5	2.50	78VG5	5.00	78E04	3.00
78VG5	5.00	78M5	2.50	78R4	2.50
ET708	2.50	ET740A	4.50	ET740B	3.50
ET514	2.60	ET707A	2.50	ET707B	2.50
ET708	2.50	ET130	2.50	78RT3	3.00
78T2	2.50	78A03	2.50	78G3	2.50
78E02	5.50	75SWILA/Bpr4	4.00	DRS-AC1	4.00
75PC12	2.50	EA78F1	2.80	ET534	2.50
ET514	2.50	ET129	2.50	ET28	2.50
ET439	3.00	ET420Q	2.50	ET123B	2.50
ET123A	2.50	ET119	2.80	75F2	2.50
75L11	2.50	ET438	2.50	75V12	2.60
75F12	2.80	ET1124	2.50	ET1122	3.00
75CL9	2.50	75PC12	2.50	ET121	2.50
ET120	2.50	FT118	2.50	ET117A-B	2.80
ET704	2.60	ET500	2.50	75T19	2.50
75R7	3.00	75CD7	2.50	75FM5	2.50
75TU10	3.50	75FE5	2.50	75TU8	5.00
75TU9	3.50	ET533A-B	2.50	ET440	4.50
ET400	2.50	75W3	2.50	ET532	2.50
ET529B	3.30	ET529A	4.50	ET702	2.50
ET601R	2.80	ET601P	2.50	E85RT	3.00
75EM6	2.50	75SD4	2.50	75A01	2.50
ET414E	2.50	ET414D2	3.20	ET430	2.50
ET314	2.50	ET118	2.50	E85	3.00
E8K1	3.00	ET528	2.50	ET312	3.00
7501	2.50	74MX120	3.50	74MX12C	2.60
74MX12B	3.20	74MX12A	2.80	ET701	2.50
ET527	2.50	ET428	2.80	ET313	2.50
ET530	2.50	ET427	2.50	ET426	2.50
74MX8	2.60	74EM9	2.50	74TU8	2.50
ET429	2.60	E8X	5.00	E810T	5.00
E8P	5.00	E8M	5.00	E8D	5.00
E8A	5.00	E8T	5.00	E8F	8.00
E8C	8.00	74C9	4.20	7408	4.00
ET424	2.50	ET311	2.50	ET526	2.50
ET114	2.50	74SA5	4.00	ET801M	2.50
ET801L	2.50	ET422	3.30	74S3	2.50
ET801J	3.00	ET423	2.50	ET420E	3.30
ET521B	2.50	ET801M	2.50	ET801G	2.80
74A1	2.50	74HPL	2.50	7312T	2.80
ET801D	2.50	ET801C	2.80	ET420C	2.50
ET420D	2.50	ET420B	2.80	ET420A	2.50
ET524	2.80	ET801R	3.30	ET801N	3.30
ET801F	2.80	ET801E	3.90	ET801A	3.30
73TU11	2.80	73P11	2.80	EY520A-B	4.40
73C12	4.90	73BA9	2.80	ET113	3.10
ET419	2.50	ET218	3.50	ET417	2.50
ET309	2.80	ET414D	2.50	73TU7	2.80
73S8	2.50	ET521	3.90	ET213	2.50
ET418	3.30	7301	2.50	ET518	2.50
733C	2.80	73T1	2.80	ET414C	2.80
ET414B	2.80	ET414A	2.80	72M12	2.80
72SA9M	2.80	ET413	2.80	ET034A	3.10
72S11	2.80	72G7	2.80	72110	2.50
7211T	3.30	ET037-40	8.00	72SA10	3.10
72C8	2.80	ET029	2.50	72S10	2.80
72R9	2.80	72SA9	2.80	ET033	3.30
72MX8	3.10	72T3	3.30	ET028	2.80
721F8	2.50	71A8	2.50	72P3	2.80
72R2	2.80	72T20	2.50	ET023	2.80
ET021	2.80	72T2A-B-C	4.40	73V18	3.30
73V1A	8.80	72SA1	3.30	71C12	4.40
ET019	2.80	ET018	2.80	ET017	2.80

## ALL SILICON 30/60w PA PORTABLE AMPLIFIER



6 1/2" W x 3 1/4" H x 8 1/2" D  
 12-16V two inputs, 5 &  
 100mV, 15 ohm output No.  
 763D. Also 125, 250, 500 ohm  
 output No. 763A. All \$70 each  
 For 240V operation \$33 extra  
 Freight collect

COILS and IF's 3/4" x 3/4" x 2 1/4" All \$2.50 ea plus post 60c.

RF CHOKES Plus post 80c.  
 381 AIR 2.5mh 50ma—Pye 70c.  
 381 IRON 10uh to 1,000uh 25ma 70c.

FILTERS 27' Line filter 2 amp \$14.  
 29' Line filter 10/20 amp \$37.50.  
 30' Pulse filter 2 amp \$12.

MAIL cheque or money order  
 (add postage) direct to —

# RCS radio pty ltd

651 FOREST RD BEXLEY  
 NSW 2207 587 3491

# BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD CLAYTON, VICTORIA 546 5076

## ATTENTION!!


All constructors of the July-August project on the low frequency receiver entitled "Derived Frequency Reference from North-West Cape".

*Crystals Are Available Ex-Stock*

With more than 36 years experience BRIGHT STAR can supply your Crystal needs.
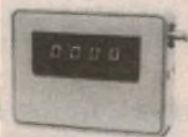
## NOW AVAILABLE

★ Precision Regulated Power Supplies 1 and 5 AMP



★ 4 to 8 Digit Event Counter



★ Crystal Oscillator Modules up to 140 MHz.



## Send SAE For Catalogue

COMMUNICATION SYSTEMS  
 PERTH. PHONE 76-2566

ROGERS ELECTRONICS  
 ADELAIDE. PHONE 42-6666

FRED HOE & SONS PTY. LTD.  
 BRISBANE. PHONE 47-4311

DILMOND INSTRUMENTS  
 HOBART. PHONE 47-9077

## TECHNICIANS! Special Prices on Test Equipment



**YF-20K**  
**High-Sensitivity**  
**Multitester**

20,000 Ohms Per Volt DC,  
 10,000 Ohms Per Volt AC  
 V.DC: 0—5—25—125—500 &  
 2.5k Volts.  
 V.AC: 0—10—50—250—1000  
 Volts.  
 DC Current: 0-50uA—250mA  
 Resistance: 0—R x 10—R x 1K  
 Ohms.



**YF-330**  
**High-Sensitivity**  
**Multitester**

V.DC: 0.3V 3V 12V 30V 120V  
 300V 60V 1.2kV 6kV (20kV).  
 V.AC: 6V 30V 120V 300V  
 1.2kV (8k /V)  
 DC Current: 0.6mA 3mA 30mA  
 300mA 12A (300mV) Ohms:  
 Range — x 1 x 100 x 1k x 10k  
 Midscale—25 2.5k 25k 250k  
 Maximum — 5k 500k 5M 50M

FOR INFORMATION AND PRICES TELEPHONE


## AUSTRALIAN TIME EQUIPMENT PTY LTD

192 Princes Highway, Arncliffe, N.S.W. 2205  
 Phone: 59 0291



## NEW PRODUCTS

### Switch support bracket

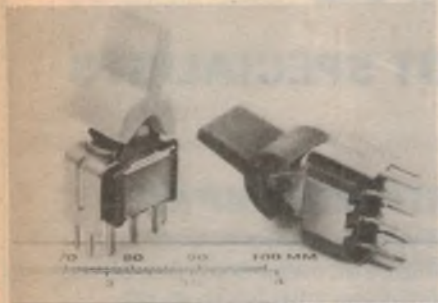

The C & K range of subminiature switches are now available with vertical support brackets for PC mounting applications. The brackets are designed to absorb actuation stress, thereby reducing stress at the switch terminals, and can be supplied to user specifications as required.

Further information from C & K Electronics, Office 2, 6 McFarlane St, Merrylands, NSW 2160. Telephone 682 3144.

### Compact, low-cost digital multimeters

Two compact, low cost digital multimeters have recently been released by the John Fluke Manufacturing Company, Seattle, USA, and are available in Australia from Elmeasco Instruments Pty Ltd. They are the 3½-digit 8030A and the 4½-digit 8040A.

Both instruments feature excellent overload protection and measure DC voltages, AC voltage (true RMS), DC current, AC current (true RMS) and resistance. The 8030A also features a diode test facility, while the 8040A provides for both auto and manual ranging.

Power supply requirements may be met either by disposable alkaline batteries, rechargeable NiCd batteries, or from a mains supply. A full range of accessories is available, including carrying case, high voltage probe, 2 RF probes, and a 600A current probe.

Elmeasco Instruments also wish to advise that they have been appointed Australian sales representatives for the range of function generators manufactured by Exact Electronics, Oregon, USA. A catalogue is available.

Also available from Elmeasco is a 17-page brochure put out by Teledyne Philbrick entitled "How to Choose an Operational Amplifier". The brochure discusses monolithic, hybrid and discrete module construction and offers practical advice on the selection of op-amps.

Further information from Elmeasco Pty Ltd, PO Box 30, Concord, NSW 2137.

### Changes at Optro

During the past few months, Optro Pty Ltd has undergone a restructuring process with the aim to provide more efficient customer service. Although, production will now be somewhat limited, the company intends to continue with its standard local products on a sub-contract basis. These include equalisers, limiters, logo generators, and audio processors.

Optro has also secured many excellent agencies in the audio and video fields, including Advent large screen television, Allen and Heath consoles, Cadac professional consoles, Ampex audio tape, JPL speaker systems, IGM Automation, Taber audio equipment, and STL test tapes.

Further information from Optro Pty Ltd, 17 Arawata St, Carnegie, Vic 3163.

**R.H. Cunningham**  
Pty. Ltd.

### Why improvise? There is a Bulgin battery holder for all regular size batteries . . .



**List Nos.: B.3, B.2, B.1.**  
Three, Two and One 1035 Cell respectively.



**List No. B.11**  
Range of three models accepting one, two or three 1015 size cells. Panel mounting with rear support bracket.



**List No. B.1**  
Further three panel mounting models accepting one, two or three 1050 size cells.

#### BULGIN Products include:

- Fuse Holders
- Switches — Toggle, Micro, Key operated & Semi-Rotary
- Bezel Lampholders
- Plugs and Sockets

Available from Wholesalers or the Australian Agents

**R.H. Cunningham**  
Pty. Ltd.

VIC.: 493-499 Victoria St. West Melbourne. 3003 Ph.: 329 9633  
N.S.W.: 4-8 Waters Rd., Neutral Bay. 2089 Ph.: 909 2388  
W.A.: 256 Stirling St., Perth. 6000 Ph.: 28 3655  
QLD.: L. E. BOUGHEN & CO., Cnr. Milton & Baroona Rds. Milton 4064 Ph.: 36 1277  
S.A.: Werner Electronic Industries Pty. Ltd., Unit 25, 28 Gray St., Kilkenny. 5009 Ph.: 268 2801

Telex Melbourne. 31447  
Sydney. 21707 Brisbane. 41500 Perth. 93244

## ELECTROLUBE REGD. FREEZER SPRAY

For isolating faults in transistors, diodes and other semi conductors, finding dry joints and bad contacts. Protecting heat sensitive components whilst soldering, checking thermostats and thermal cut-outs.

Electrolube is non-toxic and will not affect any paints, plastics, or rubbers.

Available from leading electrical wholesalers.



Information on FREEZER SPRAY and other ELECTROLUBE products is available from Australian agents:

**RICHARD FOOT (AUSTRALIA) PTY. LTD.**

63 HUME STREET, CROWS NEST, N.S.W. 2065. Telephone: 43-0326.



R.F. 2266C



# EDUCAL

## KIT SPECIALISTS



### AM-FM STEREO TUNER KIT **\$89**

#### FEATURES

- PRE-ALIGNED FM MODULES (3)
- MONO / STEREO
- LOCALLY PRODUCED—NOT IMPORTED
- 4 PRE-SET STATIONS ON FM
- FULL RANGE MANUAL TUNING AM-FM
- 75 or 300Ω INPUT
- A.F.C.
- STEREO BEACON
- PROFESSIONAL FINISH

#### SPECIFICATIONS

TUNING 88-108MHz  
BANDWIDTH 300 KHz  
I.F. 10.7 MHz  
I.F. REJECTION 65dB  
IMAGE SUPPRESSION 40dB  
A.M. REJECTION 40dB  
CHANNEL SEPARATION 38dB (min.)  
DIMENSIONS 13.75" x 10.5" x 4.25"

#### STEREO-AMP KIT

30 WATTS / CHANNEL RMS  
FREQUENCY RESPONSE 8Hz-30 kHz  
(3dB down) 20Hz-20kHz (FLAT)  
DISTORTION 0.1% INTO 8Ω  
FULL BASS & TREBLE CONTROLS  
LOUDNESS CONTROL  
DIN SOCKET PHONES SOCKET  
TEAK VENEER CASE  
MAG. CARTRIDGE INPUT  
AUX. INPUT TAPE INPUT

ALLOW  
P & P + INS.  
\$2.50

### **\$79**

**EDUCAL, 21 WELLS AVENUE, BORONIA, VIC. 3155**

### *and now... quality in australia*


We are very proud to present a wide range of extremely high quality microphone stands which are manufactured in Australia and are retailing at very competitive prices.

Our range of microphone stands has been carefully designed and field tested and reflects the continual benefit we gain from the practical comment of field operators, engineers and experienced users.

The stands incorporate a number of functional features which make them extremely smooth, silent and sleek ... a well balanced combination that makes them more than comparable to anything available from overseas.


A complete range of spare parts and accessories is always readily available.

Contact us for brochure and price list.

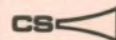

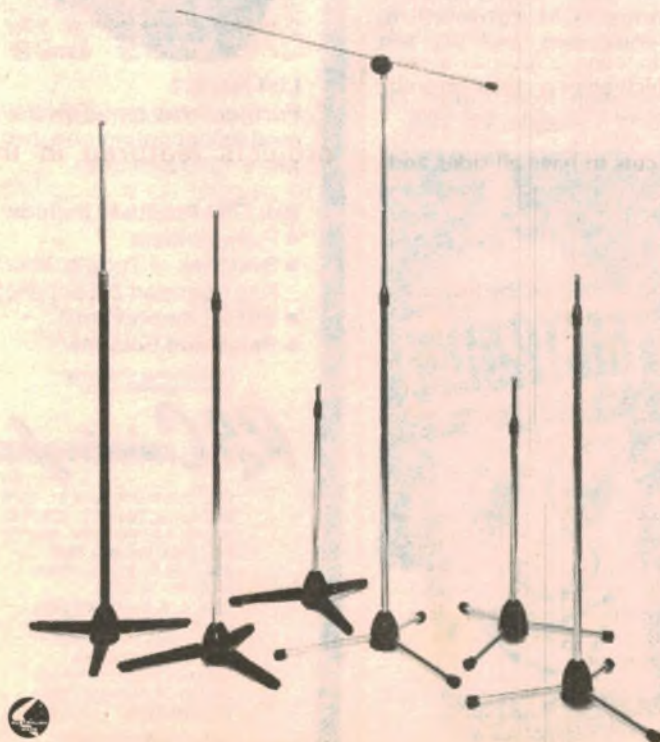**C. S. SERVICES PTY. LTD.**  
135 WENTWORTH RD., ENFIELD  
N.S.W. 2136. PHONE: (02) 747 6363

CONSTANTLY STRIVING TO MEET  
THE DEMAND FOR QUALITY SOUND  
REINFORCEMENT EQUIPMENT







# Letters to the editor

## Logic expressions

With reference to your Logic Design articles in the May and June editions, may I point out some rather significant errors before the would-be logic-designers amongst your readers commit suicide. I must apologise to these readers for not commenting last month, but assumed that you would be inundated with letters on the subject.

In the May issue, Page 94:

$$Z = \dots + \overline{A.B.C.D.} + \overline{A.B.C.D.}$$

should read

$$Z = \dots + \overline{A.B.C.D.} + \overline{A.B.C.D.}$$

and in the June issue, Page 89, Fig. 5 (b):

$$\overline{A.B.C.} \text{ should read } \overline{A.B.C.}$$

$$\overline{A.B.C.} \text{ should read } \overline{A.B.C.}$$

$$\overline{A.B.C.} \text{ should read } \overline{A.B.C.}$$

and Page 91:

$$Z = \overline{A.B.C.} + \overline{A.B.C.} + \overline{A.B.C.}$$

should read

$$Z = \overline{A.B.C.} + \overline{A.B.C.} + \overline{A.B.C.}$$

E. F. Atkins  
Carine, WA

**COMMENT:** These are not strictly errors if one adopts the convention that all conjunctive terms must be enclosed within brackets. The continuation of the negation bar where two or more adjacent terms are both negated tends to have advantages for typesetting, and this is why we used it in the cases you cite. However, we agree that it can cause confusion, and thank you for drawing the attention of readers to this.

## TV interference

Upon reading your article in June EA regarding RFI, I thought some of your readers may be interested in a couple of solutions I have found for TVI in particular.

Several of my neighbours complained to me of interference resulting from operation of my amateur station on 7 and 14MHz.

The fault appeared to be severe cross modulation of the composite video signal, resulting in tearing of the picture and interruption of the sound.

After many hours of work, I found that the simplest cure for common mode conducted TVI is the insertion of a longitudinal choke in the coax to the receiver, installed close to the input socket. A

longitudinal choke consists of several turns of the coax feedline threaded through a large toroidal ferrite core (the sort used for audio crossover coils).

In another case, where the viewer was using an antenna with 300 ohm feedline, I simply made up a balun to convert it to 75 ohm and installed a longitudinal choke between the balun and 75 ohm input connector of the receiver. For particularly stubborn cases, it may be necessary to use a coax fed antenna, high pass filter and longitudinal choke.

If TV set manufacturers installed these components as a matter of course, everyone would be happier.

D. Diamond, VK3XU  
Ashwood, Vic.

## Speaker boxes

As one in the process of construction the 3-45L Speaker System, I was interested in the 3-41L design in the June 1976 issue. I would point out however to anyone else manufacturing their own speaker boxes that the 45 litre box is the simplest to construct.

Readily available from most timber distributors is the 300 x 18mm particle board in 4 metre lengths. The board is designed for shelves and has an added advantage in that one edge has a soft wood insert which gives a clean smooth front to the speaker boxes. One length of this cost me approx \$7.00 and I only had to make 8 cuts to have all sides and tops for the boxes with only about six inches of waste.

R. G. Watts  
Wallsend, N.S.W.

**COMMENT:** Thank you for the information. Constructors working with this material may as well take advantage of the extra internal volume. No other changes will be necessary. Our observations were made after talking with manufacturers who normally work from metric size sheets.

The views expressed by correspondents are their own and are not necessarily endorsed by the editorial staff of "Electronics Australia". The Editor reserves the right to select letters on the basis of their potential interest to readers and to abbreviate their contents where this appears to be appropriate.

## FUNDAMENTALS OF SOLID STATE

\$3.00 plus 60c p & p

Electronics Australia

Box 163, Beaconsfield, NSW 2014

# STAR DELTA

## CO. PTY. LIMITED

INCORPORATING

P. A. HENDERSON & CO.

TRANSFORMER

MANUFACTURERS

- SINGLE & 3 PHASE TRANSFORMERS TO 20 KVA.
- MOTOR STARTING AUTOTRANSFORMERS TO 600 HP.
- NEUTRAL REACTORS

8 East St.,

Granville, N.S.W. 2142.

P.O. Box 31, Phone

637-7870.

# "COWPER"


Cabinets and chassis for all projects featured in this magazine are available from
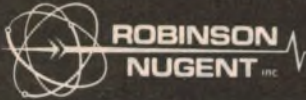
## COWPER SHEETMETAL & ENGINEERING

- CASES
- CHASSIS
- GENERAL SHEET METAL WORK FOR THE ELECTRONICS INDUSTRY
- PANELS
- BOXES
- WELDING
- PRESS CAPACITY TO 75 TONS

11 Cowper Street,  
Granville, N.S.W. 2142  
Phone 637-8736





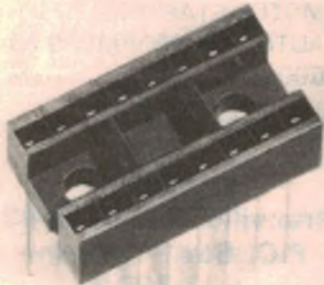
## IC Sockets

FOR ALL APPLICATIONS:

- Gold or tin plated
- Solder or wire-wrap
- Mil-spec or commercial
- D.I.L. or to-type
- E-Z entry or standard



### ICN-163-WB3

16 pin, commercial wire-wrap,  
gold plated standard entry

# EX-STOCK

Available from:

SYDNEY: Dick Smith, Radio Despatch, Pre-Pak  
ADELAIDE: Graphic Electronic Industries Pty Ltd  
PERTH: W. J. Moncrieff Pty Ltd  
BRISBANE: Fred Hoe & Sons Pty Ltd  
CANBERRA: The Electronic Shop  
NEWCASTLE: Digitronics Pty Ltd

or direct from:



99 ALEXANDER STREET  
CROWS NEST  
NEW SOUTH WALES

Telephone: 439 2488



# Books & Literature

## For radio amateurs

**VHF-UHF MANUAL.** By D.S. Evans G3RPE and G.R. Jessop G6JP. Third edition, published by the Radio Society of Great Britain. Hard covers, 416pp 245 x 190mm, fully illustrated with photographs and circuits.

RSGB publications have a reputation for being informative and well produced, and this latest edition of their VHF-UHF Handbook is certainly no exception. Looking through it, one could easily get the impression that, if its not in the handbook, you don't need to know it anyway!

Devoted to that part of the spectrum above 30MHz, the text is a mix of basic theory, essential reference data and practical "how-to-build it" information.

Chapter headings are: Introduction — Propagation — Tuned Circuits — Receivers — Transmitters — Filters — Aerials — Microwaves — Space Communication — Test Equipment and Accessories — Data.

According to the publisher's notes, the book has been revised and up-dated throughout but not to the point where they have expunged valve circuits, where there is a point in retaining them. What is completely new is a chapter on microwave techniques for bands up to a24GHz, and another on space communication techniques, mainly to do with the OSCAR satellites.

All told, it appeals as a book which would be invaluable to any amateur or aspiring amateur interested in frequencies above 30MHz.

Review copies were received both from the UK publisher and from Dick

Smith Electronics, of P.O. Box 747, Crows Nest NSW 2065, who advised that their catalog number is B2054, and that the book is priced at \$12.50 (W.N.W.)

## Radio & hi-fi

**TUNERS AND AMPLIFIERS** by John Earl. Published 1970 by Fountain Press, London. Hard covers, 187 pages 220 x 145mm, illustrated by photographs and circuits. Price in Australia \$7.50.

I reviewed this then-new book by John Earl in January 1971, making the remark that its value would be somewhat down-graded for Australian readers because of our lack, then, of a stereo/FM service. The initiation of such a service is possibly one of the reasons why the distributors are once again drawing attention to the book, indicating that it is available from stock.

Chapter headings are: Modern Equipment — State Of The Art — Choice Of Equipment — Use Of The Amplifier — Use Of The Tuner — The Tuner-Amplifier — Systems and Compacts — Specifications.

Written in 1970, the text reflects the technology of the time, based on solid state, but with integrated circuits and related techniques still largely in the labs. Furthermore, the equipment discussed is predominantly of British manufacture, with little hint of the huge array of Japanese designs long familiar on the Australian market.

If you want a direct guide to the choice of currently available hifi gear, this book therefore won't help you much. On the other hand, if you want to reinforce your understanding of basics, you will find the



THE AUDIO/VISUAL SPECIALISTS

## THE VIDEO HI-FI CENTRE

Full range video equipment—colour and black and white • Colour TV and Hi-Fi equipment • Continuous demonstrations • Special Prices • Blank Video Tapes of Formats • Video Repairs and Modifications.

2nd Floor, Telford Trust Building,  
79-85 Oxford St, Bondi Junction. Ph. 387 2555





text well written and highly readable. Our copy came from Thomas C. Lothian Pty Ltd, 4-12 Tattersall's Lane, Melbourne, 3000. (W.N.W.)

## Design charts

**ELECTRONIC DESIGN CHARTS**, by Norman H. Crowhurst. Tab Books, Pennsylvania. Soft covers, spiral binding, 220 x 285mm, 128pp. Price \$9.75, plus postage where applicable.

This is the fourth printing of well-known US writer Norman Crowhurst's collection of electronic design charts, tables and graphs. Dick Smith Electronics tell me they have been specially importing it, because of the demand from customers. I can well understand this, because the book certainly provides a wealth of useful reference information—and for a quite modest cost by modern book standards.

There are simple charts, like that to convert from frequency to wavelength, right through to a set of multi-step design charts for iron-core inductors. Each one is accompanied by text which explains exactly what the chart is capable of telling you, and how to drive it.

In short, the book gives every evidence of the care and thoroughness we have usually come to associate with the name of Norman Crowhurst. This together with the value of the data itself should ensure it a place on the reference shelf of almost all serious electronics designers, whether professional or amateur.

The review copy came from Dick Smith Electronics Pty Ltd, of 162 Pacific Highway, Gore Hill, NSW 2065, from whom it is available both directly and via mail order. (J.R.)

## Higher maths

**CONVOLUTION AND FOURIER TRANSFORMS FOR COMMUNICATIONS ENGINEERS** by R. D. A. Maurice, first edition, published 1976 by Pentech Press, London. Hard covers, 198 pages, 51 illustrations, size 220 x 144 mm. Price in London: £7.50.

Intended for broadcasting and telecommunications engineers and technician engineers, as well as for students pursuing undergraduate or postgraduate courses in communications engineering, this book explains the process of convolution from basic concepts. Many examples, chosen from real life situations, are used to compare the convolution process with the more widely known Fourier or Laplace transform processes.

There is a certain amount of bias in the examples given towards the broadcasting and television sides of communications engineering, but this does not detract in any way from the main subject matter.

The review copy was obtained direct from the publishers, and no details were supplied as to Australian price or availability. (D.W.E.)

# NEW BOOKS

JUST A FEW OF THE THOUSANDS ALWAYS IN STOCK. CALL IN OR WRITE GIVING YOUR REQUIREMENTS. All books reviewed in "Electronics" can be ordered from us.

## 1976 ANNUALS

**WORLD RADIO & TV HANDBOOK INCLUDING HOW TO LISTEN TO THE WORLD**—Combined 1978 Ed. \$10.80  
**A R R L RADIO AMATEURS' HANDBOOK 1978**—American Radio Relay League \$9.95

## TV & TV SERVICING

**BASIC TELEVISION PRINCIPLES & SERVICING**—B Grob New 1975 edition just received \$14.45  
**BASIC TELEVISION**, Schure, 6 volumes combined in one. Simplified text with hundreds of easy to understand illustrations. The ideal basic training course. \$28.95  
**COLOUR TV PICTURE FAULTS**—Bohman. Quick location and repair by means of picture fault examples in colour. \$9.30  
**COLOUR TV THEORY**—Hutson \$12.00  
**MONOCHROME JAPANESE TV SERVICE MANUAL**, TAB \$5.95  
**PAL COLOUR TELEVISION FOR SERVICEMEN**—W. C. Cook. A new book by an Australian \$16.00  
**PIN POINT TV TROUBLES IN 10 MINUTES** \$7.70  
**SLOW SCAN TELEVISION HANDBOOK**—D. Miller, 73 Magazine \$7.10  
**SMALL-SCREEN TV SERVICING MANUAL** with circuits including Japanese & U.S. brands. TAB \$8.50  
**TELEVISION BROADCASTING**—Tape and Disk Recording Systems—Harold E. Ennes \$20.35  
**TRANSISTOR TV SERVICING MADE EASY**—Darr \$6.35  
**TV SERVICING GUIDE** arranged by Trouble Symptoms—Deane & Young (Our best seller) \$4.75

## SPECIAL OFFER!

~~\$18.40~~ \$12.00

**PAL RECEIVER SERVICING** by Seal

Scoop purchase of this outstanding Colour T.V. Service book enables us to make this offer

While Stocks Last!!!

Add Post & Pack  
 Vic \$1.00  
 Interstate  
 \$1.80



## RADIO

**ANTENNA HANDBOOK**—A R R L \$5.10  
**AMATEUR RADIO TECHNIQUES**—Hawker, RSGB \$7.40  
**AMATEUR RADIO THEORY COURSE**—Ameco \$7.00  
**BEAM ANTENNA HANDBOOK**—Orr \$7.00  
**CUBICAL QUAD ANTENNAS**—Orr \$5.70  
**HAM NOTEBOOK—Volume 1** \$4.20  
**HAM HANDBOOK—Volume 2** \$5.30  
**JAPANESE RADIO RECORDER TAPE PLAYER SCHEMATIC SERVICING MANUAL** \$7.25  
 From Ham Radio Magazine  
**PIN-POINT TRANSISTOR TROUBLES IN 12 MINUTES** \$9.65  
**RADIO & ELECTRONIC LABORATORY HANDBOOK**—Scroggie. New 8th edition \$15.70  
**RADIO HANDBOOK**, New 20th edition \$23.45  
**RADIO VALVE AND SEMICONDUCTOR DATA**—A. M. Ball 10 Ed. \$6.10  
**RADIO AMATEURS VHF MANUAL**—A R R L \$5.10  
**SIMPLE LOW COST WIRE ANTENNAS FOR RADIO AMATEURS**—Orr \$6.40  
**TEST EQUIPMENT FOR THE RADIO AMATEUR**—Gibson—An RSGB publication \$6.65  
**73 VERTICAL BEAM & TRIANGLE ANTENNAS**—Noll \$6.35  
**VERTICAL ANTENNA HANDBOOK**—Paul Lee, CO Series \$7.10

## HI FI & SOUND

**ELECTRIC GUITAR AMPLIFIER HANDBOOK** \$8.90  
**FROM TIN FOIL TO STEREO**—Evolution of the Phonograph. This classic at last reprinted. A must for all collectors of early reproducing machines. \$11.95  
**HI FI DESIGNS (WIRELESS WORLD)**—tape, disc, radio, amplifiers, speakers, headphones \$3.00  
**HI FI LOUSPEAKERS AND ENCLOSURES**—Revised 2nd Edition—Cohan \$6.10  
**HOW TO BUILD SPEAKER ENCLOSURES**—Badmaieff & Davis \$5.70

## ELECTRONIC

**DIGITAL IC EQUIVALENTS WITH PIN CONFIGURATIONS** De Muiderkring \$11.95  
**DIODES EQUIVALENTS**—De Muiderkring. European, American, Japanese types. A companion to Transistor Equivalents \$5.95  
**DIRECT TRANSISTOR SUBSTITUTION HANDBOOK**. Direct graded substitutes for nearly 12,000 transistors \$4.95  
**IC OP-AMP COOKBOOK**, Jung. \$15.55  
**INTERNATIONAL TRANSISTOR SELECTOR**, Towers. Over 10,000 U.S., Japanese, British & European Transistors with substitutes. TAB \$5.95  
**IT'S EASY TO USE ELECTRONIC TEST EQUIPMENT**, Klein & Gilmore \$6.75  
**PRACTICAL OSCILLOSCOPE HANDBOOK**, Vols 1 & 2 R. P. Turner \$10.95  
**PRACTICAL PA GUIDE BOOK**, Crowhurst. How to Install, Operate & Service PA systems \$6.75  
**SECURITY ELECTRONICS**—Cunningham \$5.75  
**SEMICONDUCTOR HANDBOOK**—De Muiderkring. Characteristics, Specifications, etc.  
 Part 1—Transistors \$8.95  
 Part 2—Diodes & Thyristors \$7.95  
**SOLID-STATE IGNITION SYSTEMS**—R. F. Graf & G. J. Whalen \$5.75  
**THE SEMICON INTERNATIONAL TRANSISTOR INDEX**, 6th edition, 1975-76 \$25.85  
**THE WORLD TRANSISTOR CROSS-REFERENCE GUIDE** \$10.85  
**TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR**, 3rd edition, Douglas \$15.00  
**TRANSISTOR EQUIVALENTS**—European, American and Japanese, 9000 types and 5800 substitutes, 8th edition \$5.95  
**TTL DIGITAL INTEGRATED CIRCUITS**—with equivalents. De Muiderkring  
 Part 1—Series 7400-74132 \$8.95  
 Part 2—Series 74141-74298 \$10.95  
**UNDERSTANDING AND USING THE OSCILLOSCOPE** C. Hallmark \$6.40  
**WORKING WITH THE OSCILLOSCOPE**, Saunders \$5.95

## MANUFACTURERS' MANUALS

**FAIRCHILD SEMICONDUCTOR**—Full Line Condensed Catalog \$5.00  
**FAIRCHILD SEMICONDUCTOR CMOS DATA BOOK** \$5.00  
**GENERAL ELECTRIC SCR MANUAL INCLUDING TRIACS & OTHER THYRISTORS** \$5.40  
**GENERAL ELECTRIC SEMICONDUCTOR DATA handbook**—1482 pages \$8.00  
**GENERAL ELECTRIC TRANSISTOR MANUAL** \$4.00  
**MOTOROLA SEMICONDUCTOR PRODUCTS LIBRARY**—3 VOLUMES & MASTER INDEX—DISCRETE PRODUCTS, Series A \$20.00  
 Further volumes sold separately—  
**VOLUME 4—MECL INTEGRATED CIRCUITS**, Series A \$8.70  
**VOLUME 5—CMOS INTEGRATED CIRCUITS**, Series A \$5.85  
**VOLUME 6—LINEAR INTEGRATED CIRCUITS**, Series A \$6.70  
**National Data Books And Catalogues**  
**CMOS INTEGRATED CIRCUITS** \$5.70  
**DIGITAL INTEGRATED CIRCUITS** \$4.35  
**INTERFACE INTEGRATED CIRCUITS** \$7.60  
**LINEAR APPLICATIONS, Vol 1** \$7.60  
**LINEAR INTEGRATED CIRCUITS** \$7.60  
**MOS INTEGRATED CIRCUITS** \$5.70  
**TRANSISTORS SMALL SIGNAL FIELD EFFECT POWER** \$3.25  
**TTL DATA BOOK** \$7.60  
**RCA SOLID-STATE DEVICES MANUAL (Replaces Transistor Manual)** \$7.95  
**RCA SOLID-STATE SERVICING** \$5.75  
**RCA LINEAR INTEGRATED CIRCUITS** \$3.75

**Texas Instruments**  
**THE LINEAR & INTERFACE CIRCUITS DATA BOOK** \$6.80  
**PIN CONFIGURATION GUIDE**—File Box with Index cards \$5.60  
**THE POWER DATA BOOK** \$6.90  
**THE TRANSISTOR & DIODE DATA BOOK—Vol. 1** \$6.90  
**THE TRANSISTOR & DIODE DATA BOOK—Vol. 2** \$6.90  
**THE TTL DATA BOOK** \$6.90  
**SUPPLEMENT TO THE TTL DATA BOOK** \$6.90

MAIL ORDERS BY RETURN  
 per parcel interstate

PLEASE ADD 90c per parcel postage (Vic) \$1.70

**TECHNICAL BOOK & MAGAZINE CO.**  
 295-299 Swanston St., MELBOURNE 3000 Ph. 663 3951



**NEW... WITH FM!**



Yes, the famous Barlow Wadley General Coverage Receiver with crystal controlled reception of am/1sb/usb/cw now includes the Australian FM band!

**BARLOW WADLEY STANDARD \$269 + P&P**

**WITH FM \$298 + P&P**

The new Yaesu FRG-7 General Coverage Receiver features ac/dc operation and the famous Wadley Loop principle with spin tuning and phase-locked synthesiser providing complete coverage from 500 KHz and 30 MHz to an accuracy better than 5 KHz. Please write for further technical details (enclosing SAE).

**OUR PRICE \*\$255 plus P&P**

**RECEIVE ANTENNAS**

Listener 1 "V" type Antenna. Covers 3-30 MHz with special trap. Ideal for DX reception. **\$21 + P&P.**

Listener 3 Long range wire dipole antenna 3-30 MHz complete with Balun, feed wax, VHF plugs, insulators. Ideal for the serious SWL. **\*\$42.00 plus P&P.**

**SPECIAL**  
\* \$255

**HAM RADIO**

- ANTENNA COUPLERS**
- C1-666, 2.5kW, 30-10m, heavy duty, superb construction ..... \$235
  - C1-66, 500W 30-11m, built-in 4 position coax switch ..... \$ 98
  - C1-99 200 watts for 2m band ..... \$ 47
- TEST GEAR**
- YC-100 monitor/scope ..... \$218
  - YC-355D frequency counter ..... \$290
- 2 METRE ANTENNAS**
- AKN2 Ringo vertical ..... \$ 40
  - DINGO X2 identical to above but locally manufactured ..... \$ 35
  - LA210W twin boom 11el stacked beam ..... \$125
  - AS210AN twin boom 11el gain ..... \$ 99
  - AS210AN single boom 14.5dB gain ..... \$ 38
  - V7 crossed v-eg. 7el with 7dB gain ..... \$ 65
- HUSTLER WHIPS**
- RM-80 (80 metres) ..... \$ 26
  - RM-40 (40 metres) ..... \$ 25
  - RM-20 (20 metres) ..... \$ 20
  - MO-2 mast ..... \$ 26
  - RM-2 bumper mount ..... \$ 15
- HF TRAP DIPOLES**
- Midy HIN trap dipole 40-10m ..... \$ 38
  - Midy VN trap dipole 80-10m ..... \$ 44
  - AI-40DXN trap dipole 40-80m ..... \$ 38
  - AI-240DXN trap dipole 20-40m ..... \$ 28
- ANTENNA ACCESSORIES**
- Ham II Heavy Duty Rotator ..... \$175
  - E-1844 medium Duty rotator ..... \$140
  - E-200 light Duty rotator ..... \$ 62
  - Rak dipole balun ..... \$ 22

**ICOM**

**.. where quality counts!**

The New IC215 3w 2 metre handy portable transceiver complete with 3 channels.

**FM \$164**


The popular IC502 3w 6 metre handy portable, vfo controlled 52-53 MHz. SSB and CW modes

**SSB \$175**

The IC202 3w ssb/cw 2 metre handy portable, VXO control, noise blanker.


**SSB \$185**

All portables have provision for external 13.8 Vdc and antenna. Set includes dry cells, mic, carry-strap, plugs. All sets given pre-sales checkout and as VICOM are the Distributors for Australia, a comprehensive range of spare parts are available.



**ATLAS 210X/215X**  
Solid-state **\$625.**  
HF TRANSCEIVER

**KENWOOD TS-700A**



**\$575**

The promise of 2 meter operation. The Kenwood way. The TS-700A operates all modes SSB (upper & lower) /FM/AM/CW and provides the dependability of solid state circuitry. Has tunable VFO and 4 MHz band coverage (144 to 148 MHz). Automatically switches transmit frequency 600 KHz for repeater operation. AC and DC capability through its built-in power supply. Outstanding frequency stability. Complete with microphone and built-in speaker.

**uniden** "the best value."



The fabulous Uniden 2020 phase-locked-loop transceiver offers separate usb/lsw 8-pole crystal filters as standard and 81dB's in the final with screen voltage stabilisation for minimum distortion products. Features plug-in pcb's and even the front panel can be swung out for easy servicing. A full spares catalogue is available together with change-over pcb's. Compare the Uniden 2020 with other HF transceivers and you'll be quickly convinced that it offers the best value! The price \$570 includes mic, cables, plugs, English manual and ATCOM 90day warranty! But don't get caught - \$570 is the only factory authorised dealer for Australia.

**the COMMUNICATIONS EXPERTS!**

Increase average "talk power" by connection to the transmitter microphone circuit - Model MC33A ac/dc includes 2 tone generator and built-in compression level meter **\$62 + P&P.**

Model MC22 as above less meter **\$49 + P&P.**



**DUMMY LOAD**  
5 watt lighted dummy lead fitted into UHF (PL259) plug. Glows when transmitter is on making this handy accessory ideal for tuning and testing. **\$2.50**

**GET THOSE EXTRA "S" POINTS!**

Quality 2 position coax switch, low loss (0.2 dB) will handle up to 2.5 kW pep to 500 MHz. Suberb construction **\$18 + P&P.**

Suberb quality low pass filter (32 MHz cut-off) will handle up to 1 kW pep. 50 ohms impedance with insertion loss better than 0.3 dB. Copper construction with SO239 sockets. **\$28 + P&P**

Popular VC 2 SWR/Pwr METER operates 3-150 MHz with power measurement 12/120 watts. Will handle up to 100 watts. 50 ohm impedance, twin meters. A bargain! **\$29.80**

**NOVICE OR MARINE**  
A great rig. Includes auto noise limiter, squelch, AGC, 5w dc input, 12 vdc operation, sensitivity 0.5 uV 10 dB s/n. Includes 2 marine crystals in 27 MHz band. **\$235 plus \$5 P&P.**

**\*\*\* 27MHZ**

**COMPARE OUR PRICES!**

**TVI ?**  
THEN TRY THIS !! **SAVE**

**NEW ! INNO-HIT**



**CR-1000**

**\$245**

**27MHz SSB SYNTHESISED**

This superb new rig is the ultimate in quality and sophistication! The rig is synthesised and requires no crystals - accuracy is within 0.001%! There are 69 available modes, 23 AM, 23 LSB, 23 USB at 5 watts AM and 15 watts pep. Runs from 13.8 vdc either positive or negative earth. Controls include squelch, rf gain, clarifier, noise blanker (RF type) and transceiver PA system switch. Front panel meter indicates "s" points or RF output. The rig comes complete with mic, mobile mounting brackets, dc cable and VICOM 90 day warranty.

**IDEAL FOR THE NOVICE**

- PLUGS AND SOCKETS**
- minimum mail order \$5
  - PL259 plugs with reducer **\$1.20**
  - SO239 chassis socket **\$1.20**
  - SO239/PL259 rt angle connector **\$1.95**
  - SO239 3 female "T" adapter **\$2.00**
  - "T" connector **\$2.20**
  - Solderless in-line RG58 splice **.90**
  - 18" coax jumper lead with PL259's **\$2.00**
  - 3' coax jumper lead with PL259's **\$2.20**
  - 3 pin mic plugs & sockets **\$1.50**
  - 4 pin mic plugs & sockets **\$1.20**
  - RG58A/U 52 ohm coax - 45c per metre
  - RG18 low loss coax - 45c per foot

**27MHZ WHIPS**

Base loaded stainless-steel whip, 40.5 inches, 50 ohm impedance, vswr less than 1.5. Includes roof-top mount, optional boot lid mount, spring and coax with PL259 plug. Tensile strength 260,000 lbs/one sq inch!

**\$22**



- DISTRIBUTORS:**
- Adelaide: Graham Stallard, 27 White Ave, Lockleys. Phone 43 7981
  - Brisbane: Elite Electronics, 69 Wardell St, Dorrington. Phone 38 4480
  - Canberra: Daicom, 32 Kalgoorlie Crs, Fisher. Phone 88 4899
  - Perth: Netronics, 388 Huntriss Ave, Woodlands. Phone 46 3232

**VICOM INTERNATIONAL** Telegrams "IZYCOM" Melbourne, Australia  
PTY. LIMITED

Head Office & mail orders . . .  
**139 Auburn Rd, Auburn, Vic. 3123 Ph: (03) 82-5398**  
Sydney Branch . . .  
**23 Whiting St, Artarmon, NSW 2064 Ph: (02) 439-1271**

Prices and specifications subject to change without notice. Prices include Sales Tax but exclude freight and Insurance. Allow 50c per \$100, minimum \$1



# The Amateur Bands

by Pierce Healy, VK2APQ



## 19th Jamboree-on-the-Air

For the past eighteen years this unique event has, through the collaboration of amateur radio and world scouting organisations, enabled Boy Scouts and Girl Guides to exchange greetings and personal expressions of good fellowship.

The 19th Jamboree-on-the-Air to be held over the weekend 16th and 17th October, 1976 will again provide that opportunity for young people to participate in this worldwide event.

In addition, the annual J-O-T-A can demonstrate to communities large and small, irrespective of nationally, size, or wealth that amateur radio can stimulate a sincere and friendly link between nations, on a scale that cannot be surpassed by any of the usual communication channels.

His Excellency the Governor-General and Chief Scout of Australia, Sir John Kerr, will perform the official opening ceremony for Australian participation in the 19th J-O-T-A.

The ceremony will take place from the official Headquarters station, VK1BP. The broadcast will be made as near as possible to the following frequencies, 7070kHz and 14170kHz at 10.00am on Saturday 16th October, 1976. It is hoped that propagation conditions will permit all branches in Australia to hear this important ceremony. It is planned to monitor both frequencies to allow reports to be passed to the headquarters station VK1BP.

The World Scout Bureau, Geneva, has suggested that the starting time be 0001 hours local time Saturday 16th October and terminate 48 hours later, ie, 2359 hours local time Sunday, 17th October, 1976.

The event is not a contest. Each station is free to select its own times and periods of operation.

All local regulations relating to the amateur service must be adhered to. Listen before you call "CQ Jamboree", to ensure that the frequency is not in use.

The 25th World Scout conference designated 1976 as "Scout Communications Year" and the symbol designated by the conference has been incorporated in the 1976 J-O-T-A emblem.

The official world Scout station, HB9S (Geneva), will operate around the following frequencies:

Band	Phone	CW
80 Metre		3595kHz
40 Metre	7090kHz	7030kHz
20 Metre	14290kHz	14070kHz
15 Metre	21360kHz	21140kHz
10 Metre	28990kHz	28190kHz

It has been suggested by the World Scout Bureau that stations make breaks during long contacts to check if any DX station wants to contact them. During the 1975 J-O-T-A 16 Queensland Rover Scouts visited HB9S but could not break in on Australian stations they could hear, because of lack of listening breaks by Australian and other stations.

VHF operation should not be overlooked. In the past many troops have had interesting contacts with nearby troops. With the expanding repeater usage contacts over a much further range can be made. Amateur satellites will also add additional interest.

The background of J-O-T-A is interesting. The most recent highlight was the award of the Scout Association's highest award—"The Silver Wolf"—to the founder, Les Mitchell, G3BHK, who in 1948, conceived the idea. It was not until 1958 that his efforts saw the inauguration of the first J-O-T-A. Since then the event has grown until it is now a world wide amateur radio and scouting event.

Noel Lynch, VK4ZNI, Australian National J-O-T-A organiser, extended congratulations to Les on behalf of Australian scouts and amateurs. Here is an extract from Les's reply.

"You may be interested to learn that the actual presentation took place on St. George's Day, 23rd April, 1976 at Baden Powell House, London, and was made by our chief scout, Sir William Gladstone.

"On the following Sunday I was privileged to attend the annual parade of Queen's Scouts at Windsor Castle which was reviewed by HRH the Duke of Kent. This was followed by a service in the 500 year old St. George's Chapel where award holders were allowed to sit in pews normally reserved for Knights of the Realm. This was a very imposing service during which the entire congregation re-affirmed their scout law and promise."

Referring to the commencement of J-O-T-A in 1958 Les's comments were:

"This arose from the wonderful assistance received from scouts, radio amateurs and headquarters staff around the world. As Australia has always been a leading country where J-O-T-A is concerned I would like you all to feel that part of this particular 'Silver Wolf' really belongs to you as, without your help, this award would not have been made."

Incidentally, Les Mitchell spent some time in Sydney, Australia around 1945. During that period he was Sea Scoutmaster for a year with the 1st Leichhardt Sea Scouts and spent many weekends camping down the south coast at Austinmer and Thirroul. Les operates G3RSS during his lunch hour and would welcome calls from any Australian stations that may hear him.

The spirit of fellowship and the value of amateur radio as a means of international communication was expressed by delegates of 86 countries at the 25th Scout Conference. Meeting in Copenhagen the conference noted that J-O-T-A annually involves some 6000 amateur stations in 70 countries with participation by more than 100,000 members of the scout and guide movements.

A resolution titled "Cooperation with Amateur Radio Services" was carried and the 25th World Scout Conference requested all member organisations to—

1. Urge their governments to resist any attempt to reduce the number and size of frequencies presently

allotted to the amateur radio service and

2. Cooperate with their national amateur radio organisations in actions designed to this end.

Surely this is the type of outlook towards amateur radio that should be fostered, particularly in view of the pressures most likely to be met, in relation to amateur frequency allocations, at the World Administrative Radio Conference in 1979.

On this aspect alone, apart from the personal pleasure to be gained from participating in J-O-T-A, amateurs are urged to contact local scout or guide groups and offer their services, even for a short period, during J-O-T-A weekend.

## RADIO CLUB DIRECTORY

Do not let your radio club miss this opportunity to publicise its location, meeting place etc. See August issue of these notes for format details.

This is the final reminder for 1976.

Do not delay—write now. Amateur radio needs to be publicised throughout the community.

## REMEMBRANCE DAY CONTEST

The annual Remembrance Day Contest, organised by the WIA, was held on the 14th and 15th August, 1976. A large amount of activity was heard on the bands and several high contact numbers were among those heard being exchanged.

The opening address, recorded by the Prime Minister of Australia, the Hon. Malcolm Fraser, broadcast over all official stations, was introduced by Ted Pearce, VK1AOP, president of the Australian Capitol Division, WIA.

The following is a transcript of Mr Fraser's address:—

"I am very pleased to be given the opportunity to open the Remembrance Day contest for 1976, and in a small way assist in your tribute to the amateur radio operators who laid down their lives for Australia.

"Since the Remembrance Day Contest is a friendly contest, those who take part will be carrying on the tradition of amateur radio itself.

"Making friends over the air and helping to develop international understanding through this remarkable leisure activity, is a most fitting way to perpetuate the memory of those whose names are inscribed on the honour roll.

"I am a little disappointed that amateur radio is not allowed in some countries. But, I understand that most of you listening will be in regular contact over the air with amateurs in most countries of the world; your contacts providing valuable addition to goodwill and international understanding, so badly needed in today's world.

"Your administrators and amateur radio should continue to be on the alert to meet new challenges. The achievements of amateur radio operators are considerable. They include technical advances, constructional assistance to aspiring amateurs and those starting their careers in electronics, demonstrations of using and commanding amateur satellites are just a few.

"Communications originated by amateurs during the Guatemala earthquake and other disasters bear witness to their intrinsic value.

"Here at home the value of amateur communications during cyclone Tracey, the Brisbane floods, bushfires and other emergencies are duly recognised by emergency organisations and official bodies.

"I commend this kind of community effort to all amateurs and hope every advantage will be taken of practice exercises, training sessions and other ways to maintain a high standard.

"With these few thoughts I am delighted to declare open the 1976 Remembrance Day Contest."

## AMATEURS ASSIST IN AN EMERGENCY

Amateur radio and the Newcastle channel 6 repeater, VK2RAN, were the means of rapidly obtaining assistance for the victims of a serious road accident on Sunday 1st August, 1976.

About 6.00pm EST, a two car accident occurred on the Pacific Highway about 50 metres south of the Fraser Park turnoff between Doyalson and Swansea. Jim Cleary, VK2ZMC operating mobile while returning to Newcastle from Gosford, had just made con-

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent direct to Pierce Healy at 69 Taylor Street, Bankstown 2200.





## When his mini-computer, one day, refused to compute, Alvin was in strife... THEN he remembered!

Alvin's one of those self-styled electronic wizards, totally dedicated to his hobby—his array of expensive equipment assembled over the years is proof positive. He knows that electronic equipment requires dust and moisture-free atmospheric conditions for maximum efficiency, and so, when, one day, his pride-and-joy mini-computer refused to compute, he knew what to do... damp contacts, dusty computer heads, contaminated points... spray with CRC CO Contact Cleaner—lifts, dissolves, evaporates completely,



effectively, immediately, all residual contaminants and moisture. No disassembly of complicated units, no expensive parts to replace... just a simple application of an incredible product like CRC CO Contact Cleaner to "dissolve" the problem. If you're a dedicated "Alvin" too, you'll want to try CRC CO Contact Cleaner yourself. Ask for it at your nearest electrical/electronics retailer, or for more info about it write to: CRC Chemicals Australia Pty Ltd, Centre Court, Paul Street, North Ryde, NSW, 2113

THE SOLUTION SOLUTION

**CRC CHEMICALS AUSTRALIA PTY. LTD.**  
Centrecourt, 25-27 Paul St., Nth. Ryde 2113. Phone: 888-3444

## AMATEUR BANDS

tact through the repeater VK2RAN with Keith Howard, VK2AKX, when he arrived at the scene of the accident which had only just happened.

Enquiries quickly indicated that an ambulance was needed as well as police to direct and control traffic. The request was passed to VK2AKX who made the necessary telephone calls. An ambulance arrived at the scene about twenty minutes after the call. Two police cars and a second ambulance arrived a little later. Five persons were injured in the accident, two being stretcher cases.

Because of the comparative isolation of this part of the highway, there may have been considerable delay in obtaining assistance without the aid of amateur radio.

Expressions of thanks have been passed to Jim, VK2ZMC, Keith, VK2AKX and his second operator Paul for handling the emergency traffic willingly and capably. Also to other amateurs who monitored the repeater frequencies and kept the channel clear while it was needed for emergency traffic.

This is an example of the service amateur radio can willingly give to the community.

## RADIO CLUB NEWS

**WAGGA DISTRICT RADIO CLUB:** With good average attendances at the regular monthly meetings and new members joining, the WDRC is making good progress. Currently courses for the novice and LAOCP amateur licence are being conducted.

The Wagga repeater, VK2RAG (channel 3) is providing very good coverage over most of the Riverina—MIA and Murray areas. The rate of usage has increased and mobileers travelling via the Hume, Olympic or Newell Highways can rely on many contacts through VK2RAG.

Most towns within 200km and mobiles around 80km in most directions can now easily gain access to the system. Many other areas gain access under favourable propagation conditions.



*Doug Menneke, VK2ZMP, checking out the Wagga repeater at Mt. Flakeney during installation in June 1976.*

The installation, shown in the photograph, is located at Mt. Flakeney. It is basically a Phillips—TCA 1677 base station modified for repeater use. Twin aerials are used. One 'ARRL type' cavity filter is used in the transmitter coaxial feeder and two in the receiver coaxial feeder.

In a note, Sid Ward, VK2SW, publicity officer WDRC, said, "With the RD contest now behind us, the next major on air activity will be the Jamboree-on-the-Air. Various social activities are planned for the remainder of the year. These include hidden transmitter hunts, visits to places of technical interest,



films and a dinner-dance evening to involve the ladies."

For further details about WDRC, write to PO Box 71 Koorringal, Wagga 2650, or drop into a monthly meeting on the last Friday of each month in the Wagga Rescue Clubrooms. Visitors and new members welcome.

**ILLAWARRA AMATEUR RADIO SOCIETY:** The Illawarra WICEN group held a very successful exercise on Sunday 25th July, 1976. Held in conjunction with the Illawarra Vintage Car Club the exercise took the form of convoy escort communications. Nine mobile units took part and activities were coordinated by Jim Potts, VK2BBG acting as WICEN control. Communication was on two metre FM channel 40 and IARS mobiles were required to report position and progress of the IVCC vehicles.

Moonbounce report; A scheduled EME test was made on the 3rd July, 1976. Those present were Lyle Patison, VK2ALU, Charlie Proctor, VK2ZEN, Ken Grimm and Eric Jamieson, VK5LP.

The first test was with SMSLE who gave VK2AMW an "M" (most letters copied) report. Due to auto ignition interference was only a "T" (odd letters copied) report could be given to SMSLE.

The next test was with PA0SSB when "M" reports were exchanged. The final test was with LX1DB but signals were not heard, except VK2AMW's echoes which were peaking at 7dB above the noise.

On the 30th July, 1976 contact was made with SMSLE when signals were "M" copy both ways.

On the 1st August, 1976 a special test was carried out with HK1TL operating portable in Columbia, South America. However, no signals were heard. All the moonbounce equipment, antenna and personnel for the test from HK1TL came from W3CCS, the Mt. Airy VHF Radio Club, Philadelphia, USA.

A QSL card confirming the first EME contact with VK2AMW has been received from W1JAA. The point-to-point distance is 16270km. WK2AMW operates on 43MHz band from Dapto, NSW.

### AMATEUR IN AIR RACE

Dick Smith, of Dick Smith Electronics, will be flying his Piper Twin engined Commanche aircraft—reg VH-DIC—in the Australian air race from Perth to Adelaide, Melbourne and Sydney from October 20th to the 24th.

He will be operating continuously on all two metre amateur channels using an FDK Multi 7 feeding a quarter wave whip (call sign VK2ZIP).

Dick will be on the lookout for contacts and will QSL with an attractive 'air race' QSL card. He will make an award for the contact with the longest communication distance (we hear one amateur is setting up on Ayers Rock!).

Co-Pilot for the race will be famous Australian aviatrix, Nancy Bird-Walton. If you are planning to travel to a remote mountain top write to Dick first and he will listen for you.

Route segments are as follows:

October 20th — start Perth — Norseman-Forest.  
October 21st — Forest — Cedwa — Port Augusta — Adelaide.  
October 22nd — Adelaide — Camerai — Warrnambool — Melbourne.  
October 24th — Melbourne — Narrandera — Parkes — Bathurst — Sydney.

**GEELONG AMATEUR RADIO-TV CLUB:** In a report published in the August, 1976 issue of the GARC newsletter, the club president Haydn Chittock, VK3BFL stated—"It has been the concern of the club for some time that, although the population of Geelong has expanded in recent years, the amateur population has remained dormant. This situation should not be tolerated by Geelong amateurs; we must have the numbers if we are to survive and enjoy our hobby. To do this we, as amateurs, must support schools, clubs and organisations who support amateur radio.

"This year the club is to take a step in promoting amateur radio by conducting classes for the novice level amateur licence. These classes will be open to the public and will be conducted by qualified teachers."

Membership of the club is not a pre-requisite for enrolment in the classes.

Contact GARC Public Relations Officer, Alan Bradley, VK3LW, PO Box 520, Geelong 3220, or

## IONOSPHERIC PREDICTIONS FOR OCTOBER

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.

10 76

7MHz EAST	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								
14MHz GMT	15	16	17	18	19	20	21	22	23	24	01	02	03	04	05	06	07	08	09	10	11	12	13	
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								
21MHz EAST	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	
EAST AUST TO BARBADOS (SR)																								
JOHANNESBURG																								
McMURDO SOUND																								
NEW DELHI																								
NEW YORK																								
RIO DE JANEIRO																								
TOKYO																								
VANCOUVER																								
WELLINGTON																								
WEST AFRICA																								
WEST EUROPE (SR)																								
WEST EUROPE (LR)																								
ADELAIDE TO SYDNEY																								
BRISBANE TO MELBOURNE																								
PERTH																								
SYDNEY																								
DARWIN TO SYDNEY																								
MELBOURNE TO PERTH																								
SYDNEY																								

telephone 437 550; for more details.

Meetings are held each Friday night in the clubrooms, Storer Street, East Geelong.

**AUSTRALIAN CAPITAL TERRITORY DIVISION WIA:** A new look for their monthly newsletter. The July 1976 issue is a 14 page, 24cm by 16cm photo-offset printed. The contents include a resume of coming activities, thought provoking guest editorial, WICEN notes, technical details of the Canberra repeater Mk II duplexer, and advertisements from radio trade houses.

Amateurs residing in the VK1 call area who have not already become a member of the ACT division are invited to join and add their support to promotion of amateur radio status in the ACT. Those interested in becoming amateurs are also catered for.

Write to WIA, ACT Division, PO Box 1173, Canberra City, ACT 2601 for details.

**CENTRAL COAST AMATEUR RADIO CLUB:** Plans are already in hand for their field day to be held on 20th February, 1976. This event draws the largest attendance of amateurs, families, and friends in Australia. Make plans to attend.

Here are some details of the CCARC repeater VK2RAG operating on channel 3. The transmitter and receiver are valve type and, in order to cut down the power bill, the repeater control system closes down the transmitter if not used for eight minutes.

The repeater turn on procedure is:

1. Transmit a burst of carrier with your call sign,
2. If the repeater does not come on immediately wait for four seconds.
3. The repeater will come on automatically and transmit its call sign, channel number, and time (EST), in Morse code using a 960Hz tone at 15wpm. It is then available for use by adequately modulated transmissions.

A frequency checking circuit allows users to set their transmitting frequency in the centre of the repeater receiver bandpass. To use this facility it is necessary to provide a strong signal to the input of the repeater for about five seconds including iden-

tification. If the signal to the repeater is plus or minus 1.5kHz a tone burst will be heard. If the frequency was low a 630Hz burst is transmitted or if a high 1400Hz tone transmitted. No tone indicates that your transmitted frequency is within the bandpass.

Operators should note that an adequate level of speech modulation is necessary to ensure proper operation of the system. Persistent button pushing will cause the repeater to automatically switch off until sufficient amplitude and duration of speech resets it. Time out is 4 minutes.

**WAIT AMATEUR RADIO CLUB:** Members of the West Australian Institute of Technology Radio Club are looking for contacts on 14.170MHz on Wednesday afternoons at 2.00pm; 3.00pm and 4.00pm West Australia standard time (0600GMT; 0700GMT; 0800GMT). Also on Wednesday evenings on 14.170MHz and 3685kHz at 8.00pm and 9.00pm (1000GMT and 1100GMT).

CQ calls will be made for five minutes at the above times from the club station VK6PD.

### SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to

**THE COURSE SUPERVISOR,  
W.I.A.  
14 ATCHISON STREET,  
CROWS NEST, N.S.W. 2065**



# Shortwave Scene

by Arthur Cushen, MBE



Radio New Zealand resumed short-wave transmissions on June 5 following a wave of protest letters to the New Zealand Government after its closure on May 1st. Since that time, further action has been taken to bring back some of the station's more popular programs, including Arthur Cushen's DX World.

The short-wave transmissions are now a relay of the Radio New Zealand National program heard over the medium-wave network. The shortwave service, as such, had no special inserted programs. To overcome this Radio New Zealand has reintroduced onto the national program two popular sessions heard formerly on shortwave only.

Arthur Cushen's DX World is now heard on the first Sunday of each month at 1015GMT on the YA Network of Radio New Zealand, and on 6105kHz. This DX World program is unique. It has been broadcast for the past 16 years, and is the only DX Session written and broadcast by the listener himself from his own observations. Furthermore it is unusual in the broadcasting field, as it is read from a Braille script.

The Mailbox session, in which letters received by Radio New Zealand from listeners throughout the world were answered, has also been reintroduced. This is now heard on the third Sunday of each month, also at 1015GMT.

Comperes of the session in the past year have been Bryan Clark and Tony King, two well known Wellington listeners whose knowledge has added a touch of expertise in answering the questions posed by overseas listeners. The return of these two programs will be welcomed by short-wave listeners throughout the Pacific and Australia. The present schedule is as follows: to the Pacific 1800-2000GMT 9770, 11780kHz; 2000-0050GMT 11960kHz; 2000-0450GMT 15130kHz, 0100-0450GMT 11705kHz; 0500-0700GMT 9540kHz, 0500-1030GMT 11780 or 6105kHz and to Australia 0700-1030GMT 6105kHz.

## RECENT VERIFICATIONS

**GRENADA:** Radio Grenada has confirmed our reception on 15105kHz with a card. The present schedule is 3300kHz 2205-0230GMT, 9550kHz 1545-1800GMT, and 15105kHz 1945-2200GMT. The power on all frequencies is 5kW and the address is Radio Grenada, Broadcasting House, St George's, Grenada, West Indies.

**SRI LANKA:** The Sri Lanka Broadcasting Corporation confirmed reception with a coloured card showing a native girl. Our reception was for reports on 3385 and 11800kHz. The verification was signed by J. N. Heath, Superintendent Engineer, Sri Lanka Broadcasting Corporation, Colombo 7, Sri Lanka. The frequency of 11800kHz is used 0300-0830 and 1330-1730GMT, while 3395kHz replaces 3385kHz 0015-1730GMT.

## SPAIN CONTINUES TESTING

Madrid has been heard on three frequencies on a test basis with its new transmission to Europe in English 2030-2130GMT and with the same program repeated at 2130GMT. The transmissions were first noted on 5955kHz, then on 6075kHz. The most recent frequency used is 6100kHz. The station is announcing that at 2030GMT they are using 9505kHz

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are in GMT. Add 8 hours for WEST, 10 hours for EAST, and 12 hours for NZT.

and at 2130GMT 6075kHz and 9505kHz. The frequency of 9505kHz is blocked by Radio France, while 6100kHz has interference from Moscow and Cologne after 2130GMT.

A DX Session in English has been noted on Sundays at 0145GMT on 11880kHz, and it is also announced as being carried on 6065kHz. Madrid is anxious for reception reports on the test transmission which should be sent to The English Transmission to Europe, Radio Television Espanola, Madrid 24, Spain.

## BANGLADESH EXPANDS SERVICE

Radio Bangladesh, Dacca, has announced a major expansion of its radio services on both medium and short-wave. According to the BBC, a new 12-storey building will house 25 studios and all the offices of Radio Bangladesh at present located in the Dacca area. The most modern and sophisticated equipment will be installed, including computerized operational facilities for the national and external services.

Some idea of the extent of new transmitting services, either now in operation or planned for the next few years, can be gauged from the following summary. Two 250kW shortwave and three 100kW medium-wave transmitters are to be installed within the next two years. These, together with the recently inaugurated 1,000kW medium-wave transmitter in Dacca, will cover the entire country with national and regional programs. They will also make it possible for several external service programs to be broadcast simultaneously to "friendly nations to the east and west".

The regional stations of Radio Bangladesh at Chittagong, Khulna and Rajshahi, which at present have 10kW medium-wave transmitters, will each have a 100kW transmitter installed, enabling them to reach shipping in the Bay of Bengal when storm warnings are broadcast. In addition the Chittagong station will broadcast programs for the tribal people residing in the Chittagong Hill Tract Region.

Under its development plan, Radio Bangladesh will set up independent broadcasting organizations in Khulna, Rangpur and Sylhet and in this connection the transmitter power of the Sylhet station is to be increased from 2kW to 20kW. Work is progressing on six FM transmitters to improve reception of the VHF service.

## SWISS UPGRADES SERVICE

The Swiss Broadcasting Corporation at Berne has come a long way since 1938, when Swiss Broadcasting Corporation's first regular short-wave broadcast was sent out over a 25kW transmitter at Schwarzenburg, just a few miles from the studios in Berne.

Today, the Swiss Post, Telephone and Telegraph Administration (PTT) operates five different short-wave broadcast stations, the newest being at Lenk and Samen. These new SBC voices are each 250kW and completely automated—two of the most modern short-wave facilities in Europe. Along with the older installation at Beromunster, these stations operate omni-directionally in the 75, 49 and 31 metre bands.

Bridging the longer, overseas gap between studio and listener are the directional installations at Schwarzenburg and Sottens. The Sottens station near

Lausanne, consist of a 500kW transmitter and a huge, rotatable curtain antenna—one of the few types in the world.

In its continuing program of modernization, the Swiss PTT is currently starting out on an ambitious plan to replace three, old 100kW transmitters at Schwarzenburg with the same number of 250kW transmitters. These will supplement two other 250kW transmitters, which have been in service for several years. In addition, a new multi-band, multi-directional antenna will be built, giving the Schwarzenburg signals the boost they need to better serve their listeners in the remotest corners of the globe.

Berne has two English transmissions to Australia and New Zealand and these are broadcast 0700-0730 and 0900-0930GMT. This service is broadcast on 9590, 11775, 15305 and 17840kHz. A later transmission 1315-1345GMT is beamed to Western Australia and carried on 11775, 15430, 17830 and 21520kHz. Swiss Merry-Go-Round is broadcast on the second and fourth Saturdays, and contains technical information for the short-wave listener.

## VILA USES 4975kHz

Radio Vila in the New Hebrides has been noted using 4975kHz at 0120GMT by Dene Lynneberg of Wellington. It is presumed that this frequency replaces 7260kHz for the transmission 0030-0200GMT.

Radio Tanafo has made a frequency change to 3990kHz and has now been heard with English announcements at 0800GMT. The station broadcasts from Santo and uses the power of 60 watts. It operates from 1930-2030 and 0730-0830GMT, although at times the latter has been extended to 0900GMT.

## LISTENING BRIEFS

**MONACO:** Trans World Radio at Monte Carlo has been heard on the new frequency of 5945kHz with a program in German at 0440GMT. This frequency and program appears to be new. The transmission lasts 30 minutes and leaves the air at 0510GMT.

**PORTUGAL:** Libon has introduced a further transmission in English, heard from 0500 to 0530GMT on 6025kHz. The signal is fair, but there is severe interference from Radio Kuwait also on 6025kHz.

**EAST GERMANY:** Radio Berlin International has been noted on 15125kHz from 1200 to 1245GMT. This English transmission is reported by Frank Proepster, Hove, SA. According to the announcement transmissions to East Asia include 0645-0730GMT 15240 and 17800kHz; and 1200-1245GMT 11965, 15125, 21540kHz.

**NORWAY:** The latest transmission schedule of Radio Norway, Oslo, gives details on the use of the new 250kW transmitter: 0100-0230 and 0300-0430GMT on 6180kHz, 0500-0630GMT on 11870, 0700-0830GMT on 15135, 1100-1230GMT on 6015, 1300-1430GMT on 15345, 1500-1630GMT on 15175, 1700-1830GMT on 11860, 1900-2030GMT on 15175, 2100-2230GMT on 15345, and 2300-0300GMT on 9645kHz.

**SWEDEN:** Radio Sweden continues to relay the home program for reception in Australia and New Zealand 0630-0800GMT. A frequency change has been made and 9605kHz replaces 11705kHz. At the same time the transmission is beamed to Europe on 6065kHz and to Africa on 15390kHz. Other changes in the English schedule include 1830-1900GMT on 11790kHz replacing 15240kHz; 1600-1630GMT on 9665kHz replacing 9650kHz and 11740kHz replacing 15240kHz.

**NORTH KOREA:** Radio Pyongyang has been heard on two new frequencies with the English Service at 1000GMT. The frequencies are 7203 and 9768kHz, and both give good reception. The old channel of 9420kHz has been replaced by 9768kHz, but at 2000GMT, when a further broadcast in English is received, 9420kHz carries the programme.

**IRAN:** Radio Tehran has been noted in English at 2030GMT on the new frequency of 11770kHz. John Mainland of Wellington NZ reports reception at 1930GMT in French and at 2000GMT in English.

**TAIWAN:** The Voice of Free China, Taipei, is using only one frequency to Australia reports Bill Vogel of Adelaide in DX Post. They are using 11825kHz 0200-0300GMT and 0300-0400GMT in the English broadcast.



# A.C.E. RADIO

## SOUNDDESIGN AM-FM STEREO RECEIVER



Features • Slide controls for Volume, Balance, Treble and Bass Loudness control—Hi and Lo Filters • Push-button function switches • Blackout or Lighted Slide Rule Dial • Front and Rear Speaker Outlets (8 ohms) for quad effect • Brushed Aluminium front panel • Attractive cabinet.

Stereo Headphone Input, AFC Control • Specs. • 5 Watt RMS per ch. • Aux 400 MV Tape Out 100 MV • Ceramic Cart. 300 MV • Mag. 5MV • Provision for 300/75 OHM Aerial

**SPECIAL \$96.00 p.p. \$3.75 W.A. \$5.75**

## PLAYMASTER 25 + 25 STEREO AMPLIFIER



Complete kit of top quality parts  
\$89.00. Fully constructed \$118.00  
P.P. N.S.W. \$3.50 interstate  
\$4.50

Chassis and cover only \$16.95 p.p. \$3.50  
Brushed aluminium front label \$7.30 p.p. \$1.20  
Printed circuit board \$4.95 P & P \$1.00

## MUSICOLOUR II



Magical Colour Organ operates in conjunction with your home stereo or PA system—simple to connect and operate. 3 channels. 1500 watt max load per channel.  
Complete kit of parts \$59.50  
Constructed ready to operate \$69.50  
P.P. \$3.50 W.A. \$4.50

## MUSICOLOUR MK 3

Complete Kit of Parts \$69.50  
p.p. \$3.50 W.A. \$4.50

## PLAYMASTER 3-45L LOUDSPEAKER SYSTEM



Features the mighty 8-30 woofer, 6J midrange and the incomparable Philips AD016 TB tweeter. This top quality low cost 3 way hi-fi system is available from stock in either walnut or teak veneer and complies with the specs as per April '75.

\$84.00 ea.

## 1" THICK INNERBOND

2.50 SQ. YD. P.P. \$1.00

## C-B 27MHZ COMMUNICATION EQUIPMENT

GEAR TO SUIT BUSHWALKER, FISHERMAN, CAR, TRUCK, BOAT OWNER

Model NC-310. Features 3 channels. Battery checker, squelch control, tone call switch, external aerial, speaker and power jacks, battery charger jack, spec. 13 transistors, RF input power, 1 watt, TX freq. Tol.  $\pm 0.005\%$ . Tone call freq. 2000 HZ, RX. Sen. 0.7UV at 10dB SN, sel. 45dB at  $\pm 10$ KHZ. If freq. 455 KWZ  
\$49.95 complete with book and circuit, p.p. \$1.60 interstate \$2.95

Model 2 Mobile 6 channel 5 watts 14 transistors, 8 diodes, squelch control, sig. strength/RF meter, microphone, book and circuit, 12 volt operation. Size 4 3/4" WX 1 1/2" HX 6 3/4" d.  
\$99.00 p.p. \$2.50 interstate \$3.50

Aerials base station ringo \$54.00 p.p. \$3.50

Mobile model 27R—stainless steel whip with centre loaded coil. No holes required

Has strong magnet base, tested to 200 MPH wind, install and dismantle in seconds. Length 27" with 11" 52 ohm cable, freq. 26.5/27.5 MHz

VSWR, less than 2. \$29.95 p.p. \$2.50



## SOUND SYSTEMS—SLEEK AND SLENDER FOR COMMERCIAL OR HOME HI FI

Black Vinex Covered Cabinets Rugged and Attractive Inner-board Lined for Richer Sound. Excellent Frequency Response 8 or 16 ohms. Floor or Wall Mounting. 3 Models.

15WRMS	25W RMS	40W RMS
2 SPEAKERS	4 x 6" SPEAKERS	4 x 8 HEAVY DUTY SPEAKERS
Size 19 1/2" H 11" W	33" x 10" x 8"	37" x 12" x 8"
7" D	\$49.00	\$65.00
\$35.00		

## E-TONE 60 WATTS RMS LOUDSPEAKER

30cm (12") 8 and 15 ohms VC dia. 5.1cm  
Big 3KG magnet. Freq. 40-7000 Hz for bass guitar. Organ. Guitar weight 4.5 Kg.  
\$45.00 p.p. \$3.50  
Send S.A.E. for price & data of other models incl. 38 CM 100W


WE REGRET THAT PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

## TV-FM BOOSTER

The Power Booster is designed to operate either one, two or three sets off one aerial for improved reception

SPECS gain one set.  
10db 54.88mhz 6.5db 174-216mhz  
Two sets 5db. 54-88mhz 2db 174-216  
Three sets. No signal loss 54-216mhz  
Input/output 300 1hms. \$23.95  
Power 240v 50hz Pack and Post \$1.50

## GARRARD MODEL 82

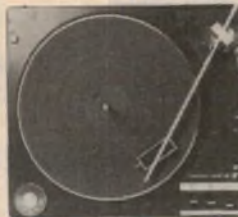

A superb 3 speed transcription changer / player Auto/manual operation 4 pole magnetically shielded syn motor Resiliently mounted Counterbalanced Elegant tone arm with slide-in cartridge carrier calibrated Antiskate. 265mm (10 1/2") Aluminium platter Cue and pause control Cartridge tilting lever. Magnetic cartridge diamond stylus. Size 375 x 335 x 170mm (14 1/4" x 13 1/4" x 6 3/4") 4.5kg (10 lbs) P & P \$2.50 Interstate \$3.50

## GARRARD CHANGER / PLAYER

MODEL—6400 3 speed auto manual changer—player 2 spindles Motor 2 pole 240V 50Hz 10 1/2" turntable cue and pause, tubular section pick up arm, Sonatone cartridge. Great value \$28.50

Mounting base and perspex dust cover for either model \$28.50 Send S.A.E. for more details

\$57.00.

## NEW MODEL MAGNAVOX SPEAKERS

10-40 10" base 15 and 8 ohms \$20.95 625 6" mid range 8 ohms \$14.95. XJ3 dome tweeter \$7.80 Famous 8-30 8 ohms \$14.95 Magnavox 3 way cross-over for 10-40, 625 and 2 XJ3 \$19.50. P & P N.S.W. \$1.40 Interstate \$2.20

## HI FI CABINET KITS

Do it yourself—big savings. Our kits are extra easy to finish. Top, bottom, each side and back are factory assembled, baffle is pre-cut Veneered pyneboard. Teak or walnut. Complete with innerboard and speaker grille cloth. 8-30 3-45L 3-41L systems \$48.00 pair  
MV-50 system \$65.00 pair

## MAGNAVOX WIDE RANGE TWIN-CONE SPEAKERS

8-16 OHMS	30-16,000HZ
6WR MK5 12W RMS	\$9.90
8WR MK5 16W RMS	\$10.75
10WR MK5 16W RMS	\$12.65
12WR MK5 16W RMS	\$14.95

p.p. NSW 95c. Interstate \$1.50

## SANYO CALCULATOR RECORDER OFFICE MACHINE



N.B. Both the calculator and recorder can be operated at the same time

\$78.00

p.p. \$2.50 WA \$4.50.

## SPEAKER SALE

BRAND NEW STOCK TO CLEAR

Rola C4D 4" x 3.5 ohm	\$1.40
Rola 4D 4" x 3.5 ohm	\$1.30
Jap 4" x 15 ohm	\$1.20
Rola 5" x 4" x 15 ohm	\$1.95
Magnavox 5" x 3" x 33 ohm	\$1.40
Magnavox 6" x 4" x 33 ohm	\$2.25
Magnavox 6" x 4" x 15 ohm	\$1.50
MSP 6" x 4" x 3 ohm	\$1.90
Magnavox 7" x 5" x 27 ohm	\$2.25
Magnavox 6" x 2.7 ohm	\$2.40
Magnavox 6AX Twin 8 ohm	\$4.50
Rola 6H 6" x 15 ohm	\$3.40
Rola 6" x Twin 15 ohm	\$4.00
Rola 8H00 8" x 15 ohm	\$4.50
Rola 9" x 6" x Twin 8 ohm	\$5.50
Magnavox 8JX Twin 27 ohm	\$4.50
Magnavox 8ER Twin 27 ohm	4.50
Tesla 10" x 6" x 8 ohm	\$4.50

## SANYO NI-CAD

Rechargeable Batteries  
Type A Nightlight \$1.85 ea. 4 for \$6.90  
Type C \$3.20 ea. 4 for \$11.50  
Type D \$3.65 ea. 2 for \$6.80.  
P.P. N.S.W. \$1.00 other states \$1.75

## EASY TO READ PANEL METERS

Clear Plastic Front. 120 x 110 M.M. Barrel  
Dia. 8.5MM.  
Stock Clearance Prices.  
30 AMP DC, 10A DC 1A DC, 500 VDC,  
500 VAC, 300 VAC, 15 VDC, 10MA, 1 MA  
NO SCALE

\$6.50 each P.P. 90c  
v.u. 500UA, 100UA \$8.50

## POWER TRANSISTORS

2N441, 2N442 3 FOR \$2.00

## EX SURPLUS RADIO GEAR TO CLEAR

BC 221 frequency meter. 1 25-20MHZ  
Complete with calibration book and crystal  
\$35.00  
240VAC power supply to suit BC221  
\$15.00.  
Mullard CTA20 valve tester (no cards)  
operates off 240VAC  
Included is 3" Mullard. display CRO tube  
\$25.00.  
APN-1 RA IO altimeter, with wobulator as  
used for sweep generator \$10.00.  
Test set for APN-1, model TS-161-APN  
\$47.50  
Plessey C42 transceiver 36-60MHZ  
\$40.00.  
BC-929 radar indicator unit with 3BPI CRO  
tube, shield and socket \$17.50 bendix. Left/  
right indicator IN41 \$3.75

No. 19 250 watt RF amplifier 12VDC  
\$17.50. AWA RF signal generator type  
17R 7490 140-300 MHZ 240VAC  
powered \$69.00  
Plessey wireless set 847, 39-56 MHZ.  
Complete with 240VAC supply and speaker  
\$57.50  
120VAC, 60HZ, 1PH. 2500W. lighting  
plant coupled to 4 CYL 6.5HP coupled to  
4 CYL 6.5HP petrol engine. 1 1/2 gal per hr.  
\$350.00

Stop fading, use an ex-RAAF dual diversity  
adaptor 2 x 3A, crystal controlled local  
oscillator. 240VAC, 1.5/32MHZ. DC-11  
455 HC crystal \$27.50

## NEW BLOCK CAPACITORS

25MFD 440 VAC 3 1/2" x 3 x 5H	\$3.50
50MFD 125V DC 3 1/2 x 3 x 4 1/4	\$2.00
25MFD 200VDC 2 x 2 1/2 x 4 1/4	\$2.00
15MFD 1000VDC 3 1/2 x 3 1/4 x 4 1/2	\$3.00
16MFD 400 VDC 4 1/2 x 2 1/2 x 4 1/2	\$2.50

P.P. NSW \$1.00 Interstate \$1.75



**BC221  
FREQUENCY METERS**

Brand new in original packing cases—unopened complete with 240 volt power supply Charts etc \$90 each—cartage to rail \$1. Freight payable at nearest attended railway station.

**P.M.G. TYPE TELEPHONES**

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

**\$35.00**  
(2 TELEPHONE SETS)

\$1 cartage to rail. Freight payable at nearest attended railway station.

**TEN CHANNELS  
VHF TRANSCEIVER**

TR1956 125-150 MHz. 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator.

**\$33.00**

**TUNING UNITS**

T U Series. Contains variable condenser suitable for aerial tuning, vernier 5" Ceramic Coil Former, etc. 19" rack mounting, only \$9.50 ea. Post A \$2.30. B \$3.75. C \$4.80. D \$6.55.

**FREQUENCY METERS**

AN URM 37 A 120 KHz to 1000 MHz, with 240V power supply. \$125 \$1.00 cartage to rail. freight payable at nearest attended railway station

**ILFORD 17.5 mm  
SPROCKETED  
MAGNETIC TAPE**

1000 ft reels brand new original packing available \$4.00 ea. quantity

Post A \$1.30 B \$2.00  
C \$2.30. D \$2.80

**No. 62 TRANSCEIVER**

With headphones, accessories etc **\$60**

**TELEPHONE WIRE**

1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$35 per drum \$1 cartage to rail freight payable at destination

**PRISMATIC COMPASSES**

Genuine ex-army Mk 3. liquid damped, as new \$45.00 P & P A \$1.70. B \$2.25. C \$2.40. D \$2.65

**MORSE KEY** \$1.40 Post 40c  
**MORSE KEY BUZZERS** \$4.25 Post 60c

**DYNAMIC  
TRANSISTOR CHECKER**

Provides a visual indication of signal output Tests: electrode open circuits, short circuits current gain. \$14.95 ea  
P & P A \$1.70. B \$2.25. C \$2.40. D \$2.65

**MULTIMETER**

A compact and handy tester for workshop or lab where quick circuit checks are required  
DC Voltage 5-2.5K (20,000 OHMS per volt) AC Voltage 10-1000V (10,000OHMS per volt) DC Current 0.50 UA. 0-2.5 MA. 0-250 MA. Resistance 0-4 Megohms Decibels — 20 to plus 22 DB Complete with instructions.

Only \$17.25 ea. Post \$1.05  
30 000 ohm per volt. \$23.75 P & P \$1.05

**BENDIX PIONEER**

Drift Sight  
Type B3  
\$250.00

**4 DIGIT RELAY COUNTERS**

50 volt DC. suit slot car Lap counters, etc  
\$1.25 each P & P 60c

**NIBBLING TOOL**

Cuts sheet metal like a punch and die, trims, notches and cuts to any size or shape over 7/16inch.

**ONLY \$9.95**  
Post \$1.10

**NIFE CELLS**

1.2 Volt, fully charged, 4in x 3in x 1in 4 AH  
\$1.50 each P & P 60c

**MUIRHEAD**

Decade oscillator. Type DG 38A  
\$100.00

**HANDY SIGNAL INJECTOR**

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On/Off Switch and indicator lamp. Size 1 1/2" Diam. 5" Long Only  
\$6.50. Post \$1.10

**TELESCOPES**

25 x 30 \$6.50  
P & P A. \$1.70. B. \$2.25.  
C. \$2.40 D. \$2.65

**SMALL CLIP-ON  
POCKET TELESCOPE**

15X \$3.95 Post 60c

**ZOOM  
TELESCOPES**

60 magnification with a 60mm coated objective lens with tripod.

**\$75.00**  
as illustrated

P & P A \$1.90. B \$2.75.  
C \$3.20. D \$3.95

**WALKIE TALKIES  
2-WAY RADIO,  
PMG APPROVED**

1 watt, 11 transistor \$130.00 set of 2

P & P A \$1.80. B \$2.50. C \$2.80.  
D \$3.20

**SMALL COMPUTER  
PANELS**

3in x 2in containing 2 valves, qty of resistors, etc.  
ONLY 75c P & P 60c

**ELECTRONIC FREQUENCY  
COUNTER**

Austronic type DFC 4 240V 50 cycle 0-100KHz  
**\$150**

**IMPELLER PUMPS**

New gunmetal body, Stainless Steel Shaft Neoprene Impeller. Up to 15ft Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sillage drains, etc. Approx size 8" x 5"

3/8" \$23.30

1/2" \$31.95

P & P A. \$1.90. B. \$2.75. C. \$3.20. D. \$3.95

**RECEIVER No. 210**

2-16 M/cs \$65.  
Transmitter No. 11 suits 210 \$36.  
24 volt Power supply to suit above \$15.  
Or complete station with Headphones, Mic, Morse Key. Antenna \$110

**LAVOIE FREQUENCY METER**

Fr-6U  
100 to 500 M/HZ  
240 Volt operated  
PERFECT CONDITION  
\$375.00

522 Transceivers 100 150M CS

**\$35.00**

**5" CRO TUBE 5 BPI \$6.50 each**

Post A. \$1.40. B. \$2.25. C. \$2.70. D. \$3.45

**POSTAGE KEY:**

A: NSW  
B: Vic, Qld  
C: SA, NT, Tas, New Guinea,  
D: WA.

**VALVES**

**BRAND NEW IN CARTONS**

65N7GT	95c	CV850	\$1.50
5U4G	95c	1H6G	75c
EF50	75c	832	\$5.00
5Y3	\$2.25	6X4	\$2.25
2 x 2	75c	VR64	75c

P & P 40c

**AIRCRAFT CLOCKS**

Genuine eight day jewelled movement sweep second hand. Dash mounting.  
\$29.50 EA. P & P. \$1.10

**CONDENSER LENS**

1 1/2" Diam 4 1/2" F.L. 75c 2 1/2" Diam 2" F.L. \$1.50 each. Or \$2.50 per pair. P & P 40c

**TELESCOPES  
ZOOM FOCUSING**

30 x 30 \$23.95 — 45 x 40 \$36.50

P & P A \$1.70 B \$2.25  
C \$2.40 D \$2.65

**SPY TELESCOPES**

8 x 17 mag size of a rifle cartridge extends to 8" Only \$4.75 each. post 60c.

**BINOCULARS**

**PRISMATIC Coated Lenses - Brand new Complete with case**

7 x 35 Wide Angle	\$35.50
8 x 40 Wide Angle	\$39.50
7 x 50	\$31.50
10 x 50	\$32.50
12 x 50	\$33.45
20 x 50	\$37.95

P & P A \$1.80. B. \$2.50. C. \$2.20.  
D \$3.20

**SOLENOIDS**

Plunger Type 12V 300MA. Suit electric camera control, miniature trains, radio, etc.  
\$2.50 P & P 20c  
200 MA 24 volt, 1/2in push movement.  
\$2.50 P & P 20c.

**SELSYN MOTORS  
MAGSLIP**

MK 11 \$5.25 ea

**3000 TYPE RELAYS**

P.M.G. 200Ohms — 1'500Ohm  
Coils \$2.50 each P & P 60c

**P.M.G. TYPE KEY SWITCHES**  
45c P & P 20c

Cintel Oscillator and Electronic Counter, type 388  
**\$250**

**SPECIAL lucky dip valve offer. 15 new valves in cartons for only \$2.95. We haven't got time to sort them, so you reap the benefit.**  
P & P A \$1.80. B \$2.50 C \$2.80 D

**RADAR TRANSCEIVER**  
X BAND WITH KLYSTRON  
ETC. **\$45.00**

**PANORAMIC ADAPTOR**

E.M.I. type PRA-1 455 variable Kc  
Course 440-520 Kc  
Centre Freq 520-440 Kc  
Fine Centre Freq 20-0-20  
Filter band with 50, 100, 200 L.F.  
200 H.F. Sweep band width 0-200.

**\$75.00.**

**TRANSCEIVERS  
Ex Army**

No C42 set. 36 to 60 MHz complete with 24V power supply, headphone, mic, leads etc \$65.00.

No C45 set. 23 to 38 MHz complete with mast, headphones, mic. 24V power supply etc \$95.00.

\$1.00 cartage to rail, freight payable at nearest railway station

Hartley double beam oscilloscope. Type 13A with probes.  
Working \$150.00

77D x RCA STUDIO RIBBON MICROPHONES Variable pattern & response music or speech \$80.00 ea. Post A \$3.30 B \$4.00 C \$4.30 D \$4.80

**EX-ARMY TWO-WAY  
FM RADIOS**



1.2 WATTS OUTPUT  
SUPERHET

PRC9 AND 9A 27 to 39 M/HZ  
PRC10 AND 10A 38 to 55 M/HZ  
COMPLETE WITH HANDSET  
ANTENNA AND BATTERY  
ONLY \$25 EA

P & P A \$2. B \$4.50. C \$4.50. D \$6.35

**16MM SOUND PROJECTORS  
IN GOOD WORKING ORDER**

240 volts operated. Complete with Speaker and Amplifier

NEVOX \$150.00  
BELL & HOWELL \$250.00  
SIEMENS \$375.00

\$1 Cartage to Rail. Freight payable at nearest attended Railway Station.



**MICROPHONES  
OMNI DIRECTIONAL  
50K OHMS**

FREQ RESPONSE 100-10,000Hz  
Sensitivity 56dB complete with 5ft cable. Microphone Holder and Stand Base only \$7.95 ea  
P & P A \$1.70. B \$2.25. C \$2.40. D \$2.65.

**REPERFORATOR**

Genuine Siemens Type 33c \$65.00

**Deitch Bros.**

**70 OXFORD STREET, SYDNEY 2010**

SORRY NO C O D



# INFORMATION CENTRE

**PLAYMASTER TWIN 25:** I have just read your interesting articles on the 25 watt per channel amplifier and was particularly interested in the preamplifier using a 741 IC plus two extra transistors, to combat the noise level of the 741. I am enclosing a cutting from the English magazine "Popular Electronics" which describes a new Ferranti IC, ZN424, which may be of interest to you.

Also the loudspeaker protection circuit using a relay is interesting, but I am wondering if you have ever thought of using SCR crow-bar protection. According to overseas writers this is ever so much quicker in action than fuses and relays.

Finally, how about extending the tone controls to include a midrange control with a choice of roll-off for the bass and treble, as in the Sansui and other amplifiers. I do not remember any local circuits ever going beyond the usual bass and treble.

I have been an interested reader of "Electronics Australia" for about 26 years and always enjoy the hifi articles. (G.S., Preston, Vic.)

• Thank you for your favourable remarks. At this stage we have not seen the specifications for the new Ferranti device so we cannot comment further.

While it is true that SCR "crow-bar" circuits can act very fast, especially when protecting power supplies, the normally used Triac "crow-bar" circuit to protect loudspeakers against faults in DC coupled amplifiers is, in practice, not appreciably faster than the relay circuit we have used. This is because the main

factor which determines the circuit operating speed is the low pass filter which is necessary to distinguish between large AC output signals and DC fault conditions.

Moreover, there is a serious drawback involved with loudspeaker protection circuits of the crow-bar type: Suppose for example, a fault occurs in the amplifier which causes the output of the amplifier to present a large DC voltage to the loudspeaker. This may or may not be due to a blown output transistor. The fault condition normally means that one of the output transistors is fully conducting (while the other is either damaged or turned off). The Triac crow-bar circuit merely puts a short-circuit across the loudspeaker line to remove the DC voltage condition—and in doing so, burns out the fully conducting output transistor.

Thus the repair bill is bigger than it would have been if a relay protection circuit was used. To our knowledge, crow-bar circuits are not used any more. The relay circuit is more satisfactory (it does not blow components unnecessarily) and it can incorporate switch-on and switch-off muting.

As far as midrange tone controls are concerned, we are dubious as to whether they are worth the extra complexity. Variable turnover points for the bass and treble controls are easily provided, merely by switching the relevant capacitors. To lower the bass turnover frequency, the .047uF capacitor across the bass control potentiometer should be increased; similarly, to raise the treble turnover frequency, reduce the .0068uF capacitors in series with the treble potentiometer.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

**PHOTOSTAT COPIES:** \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

**METALWORK DYELINES:** Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

**PRINTED BOARD PATTERNS:** Dye-line transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

**REPLIES BY POST:** Limited to advice concerning projects published within the past 2 years. Charge \$2. We cannot provide lengthy answers, undertake special

research or discuss design changes.

**BACK NUMBERS:** Only as available. Within last 6 months, face value. 7-12 months, add 5c surcharge; 13 months or older, add 10c surcharge. Post and packing for 60c per issue extra.

**OTHER QUERIES:** Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

**COMMERCIAL SURPLUS EQUIPMENT:** No information can be supplied.

**COMPONENTS:** We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

**REMITTANCES:** Must be negotiable in Australia and made payable to "Electronics Australia".

**ADDRESS:** All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

TV tuners  
valve type

\$10.

Pack & Post \$1.00



SUPER SPECIAL B.S.R.  
RECORD CHANGER



12 inch turntable balanced arm  
cueing device etc. \$35, pack and  
post \$1.50. Interstate \$2.50.



SPEAKER  
SPECIAL

\$5

6 1/2 inch Dual Cone  
4 ohm



VU  
METER

\$3.00 pair

LEVEL AND BALANCE  
METERS 1200 Ohm  
100 microamps

\$2



GARRARD  
MINI-CHANGER  
Stereo \$19.00

Pack and post \$1.00  
Interstate \$2.50

BSR 4 SPEED 240V GRAM



Motor and Pickup \$7.95

POST \$1 INTERSTATE \$1.50

SPEAKER SYSTEM

8/ohm 10 watts, includes  
2/6 inch dual speakers,  
size 16 x 10 1/4 x 8.

\$16 each.

P&P NSW \$3. WA \$6.

Other States \$5.



L. E. CHAPMAN  
(ESTABLISHED 1940)  
103 ENMORE ROAD  
ENMORE 2042.  
PH. 51 1011



**HAM****RADIO ELECTRONICS  
BARGAIN CENTRE****390 Bridge Road, Richmond, Vic.  
42-5174**Please allow for postage & packing  
when ordering by mailPlenty of **BARGAINS** for the  
Radio Amateur or the Hobbyist.**NEW 4 TRACK STEREO CARTRIDGE  
PLAYERS.** 5 watts output 12V D.C.  
operation. In sealed carton. \$15.  
P&P \$2.50.**"CAPITOL" 8 TRACK RECORDING  
CARTRIDGES** \$2 each or 3 for  
\$5.25.**"B.A.S.F." C90 CR02 CHROM-  
DIOXIDE CASSETTES** \$3 each P&P  
30c.**6ft 240V AC POWER CORDS** with  
moulded 3 pin plug 75c each or 10  
for \$6.50.**STEREO TONE ARMS** complete with  
ceramic cartridge \$5.90 each P&P  
30c.**EDGEWISE 0-1 mA METERS** 2½" x ½"  
face 3" deep calibrated 0-5 \$3 P&P  
75c.**PANEL METERS** 5¼" x 4¼" face with  
0-1 mA movement. Various scales on  
meters (gas analyser, etc) \$5 P&P  
75c.**NEW QQEO 6/40 CERAMIC VALVE  
SOCKETS** \$2 P&P 40c.**MORSE CODE PRACTICE KEYS** \$1.50  
P&P 30c.**BATTERY ELIMINATORS** to suit trans-  
istor radios and cassette recorders  
AC-DC 6 volt 300 mA. PS6300  
\$7.50 P&P 75c.**SPEAKER CABLE,** colour codes twin  
flex 20c yd.**CAR RADIO ANTENNA,** 5 section lock  
down \$2.50 each P&P 75c.**CAR EXTENSION SPEAKER CON-  
TROLS.** Use both speakers together  
or separately. \$1.50 P&P 30c.**JACKSON SLOW MOTION DRIVES** 6:1  
ratio \$2.30 P&P 30c.**THIS MONTH'S SPECIAL**Brand new 2 track reel to reel tape  
decks. 3 speed (7¼-3¾-1 7/8) will  
accept 7" reels, fitted with counter  
and pause control 240V A.C. opera-  
tion. \$19.50 P&P \$3.**15 kHz CRYSTAL FILTERS** 10.7 MHz  
M.E.W. \$5 each P & P 75c.**2N3055 TRANSISTORS** \$1 each.**58 ohm COAX CABLE** 100 yd Rolls, ¼"  
diam. \$12 roll P&P \$1.75.**52 ohm COAX CABLE** ¼" diam. 45c yd.  
50c metre.**DOW KEY COAXIAL RELAYS** 48 volt  
D.C. operation \$15 P&P 75c.**3 "N" TYPE CONNECTORS** to suit  
above \$5.**SPLIT STATOR CAPACITORS** with  
screwdriver slot drive, 9 pF, 17 pF or  
25 pF. Brand new Eddystone type \$3  
each P&P 75c.**3ft TWIN CABLE AUDIO LEADS** with  
3.5 mm plug fitted 10 for \$2 P&P  
30c.**2" SQUARE FACE 0-1 mA METERS**  
calibrated 0-60 \$3 P&P 75c.

Prices correct at time of going to press.

**MAIL ORDERS WELCOMED.**Please allow pack and post items  
listed on this page, if further infor-  
mation required send a stamped  
S.A.E. for immediate reply from  
the above address.**INFORMATION CENTRE****DYNAMIC RANGE ENHANCER:** Con-  
gratulations on a very fine magazine. As  
a student on a limited income and a bud-  
ding hifi enthusiast I appreciate your  
excellent articles dealing with the con-  
struction of good quality hifi compo-  
nents.I have built the Playmaster 144 cassette  
deck, Twin 25W stereo amplifier and the  
excellent 3-41L speaker system and I am  
very impressed with their performance.  
However, may I make a suggestion as to  
what might be a very popular project  
amongst record users?How about an article describing the  
construction of a dynamic range enhancer?  
I have seen and heard commercial  
units and been very impressed with their  
operation. (J.P., Alderley, Qld.)● A number of integrated circuits for use  
in dynamic range enhancers have re-  
cently become available, and we hope to  
produce a suitable circuit using these in  
the near future.**NOTES & ERRATA****TRANSISTOR ASSISTED IGNITION SYS-  
TEM** (August 1975, File No 3/TI/13): The  
BDY98 is now obsolete. Suitable substi-  
tutes are the higher rated BDY97 or  
BDY96. We also suggest that a 220 ohm  
½ watt resistor be connected across the  
three-diode string to ensure that T1 and  
T2 are positively turned off.**SYNC-A-SLIDE** (June 1976, File No.  
2/MS/40). The FET (TR7) is incorrectlydesignated as 2N3640. This should be  
2N4360.**AMENDED 50 Hz CRYSTAL DRIVE** (July  
1976, File No 7/CL/23): The zener diode  
in the mains-powered version is shown  
reverse-connected.**ASCII-Baudot . . . from p. 89**machine by either looking at the type-bar  
heads, or running it in local and typing  
out each of the keys in alphabetic order,  
in both lower case (LTRS) and upper case  
(FIGS.) Either way, you can compare the  
results with the coding type-out shown  
in Fig. 4, which is that assumed by the  
translator.The translator itself does make one  
minor decoding error, which proved diffi-  
cult to obviate. It affects only the "at"  
or "per" sign (@), occurs only during  
ASCII-to-Baudot translation (i.e., during  
printing), and even then not every time.You will find that whenever the  
character occurs immediately following  
figures or other upper-case Baudot  
characters, it will be translated and  
printed correctly. However, when it  
occurs immediately following letters, you  
will find that it will be mis-translated and  
printed as a G—its lower-case Baudot  
equivalent.The reason for this error is that in ASCII  
code, the "at" sign is effectively an  
alphabetic character—it has the same  
coding for the three most significant bits  
as do the first 15 letters. However, in  
Baudot code, where the character is  
present, it is regarded as an upper-case  
character or "figure".Full processing of the character by the  
translator program would involve not  
only recognising and translating its code,  
but also performing the Baudot case  
checking and modification procedure  
which the program does with all other  
printing characters. This would involve  
sending the appropriate "FIGS"  
character ahead of the character itself, if  
the printer happened to be in letters  
mode.This proved to be rather difficult, so I  
ended up compromising. The "at" sign  
is correctly translated into the  
appropriate 5-bit Baudot code, but is  
otherwise treated like one of the non-  
printing characters like space, carriage  
return or line feed. This means that the  
program does not perform the usual case  
checking or modification, because in  
Baudot code the non-printing characters  
are "caseless"—they are the same in both  
cases, and hence do not affect printer  
case mode.When you're using the translator and  
a Baudot machine with a system, remem-  
ber that the translator buffer can only  
cope with an accumulation of 240  
characters. So if you want the system to  
print out a long hex listing or some text,  
do it in modest slabs.If you forget and try printing out a large  
character string, you'll find that the  
translator will "lose" 240-character  
chunks of the string, due to the buffer


**FRG-7**  
**SYNTHESIZED  
RECEIVER**

for  
Amateurs,  
Novices,  
and  
Short-Wave  
Listeners.

**TECHNICAL DATA**

- Electronic Band Changing.
- 0.5 — 29.9 MHz. Continuous Coverage.
- Uses Wadley Loop (drift cancellation circuit) to derive synthesized heterodyne oscillator signal.
- LSB, USB, AM and CW.
- Frequency Readout better than 10 KHz (readable to 5 KHz).
- Stability within 500 Hz during any 30 minute period after warmup.
- Better than 0.7 μV for 10 dB S + N/NSSB and CW.
- Better than 2 μV for 10 dB S + N/N AM.
- Selectivity ± 3 KHz at -6 dB, ± 7 KHz at -50 dB.
- Input Impedance, high 0.5 — 1.6 MHz. 50-75 Ohm 1.6 — 29.9 MHz.
- 234V AC 50-60Hz or 12V DC (external or internal 8 dry cell).
- Size 340 mm x 153 mm x 285 mm.

**FRG-7** \$259

Above prices include S.T. Prices and specifications subject to change.

60 Shannon St., Box Hill North  
**Electronic Services** Vic., 3129  
Ph 89 2213



input pointer having overtaken the output pointer. This causes no problem to the translator, but it does foul up your print-out! So if you find that chunks of a printout are missing, simply try again with the system delivering the characters in smaller strings.

By the way, the use of a code translator inevitably involves a time delay in either direction—mainly because characters must be fully strobed in before they can be translated and then sent out again. This means that when characters are keyed in from the teleprinter keyboard there is a noticeable delay before they are echoed by the printer. The delay is particularly noticeable when the computer system itself echoes on a complete-character basis, giving a total "round trip" delay time of around 450 milliseconds.

This takes a little getting used to, but it is one of the prices one pays for using a teleprinter which "speaks a different language".

Finally, a word on using Baudot teleprinters with computers. Baudot machines were developed around 1906, long before electronic digital computers were a reality. Presumably their designers didn't anticipate that anyone would ever want to use them to send lots of mixed letters and numerals, so they adopted the system of using "letters" and "figures" modes, with the two special case-change keys used to change back and forth between modes as required.

It won't take you long to realise that this makes the machines quite clumsy when it comes to keying in programs in hexadecimal code. You'll have to develop the habit of always sending "LTRS" before you want to key in letters, and always sending "FIGS" before keying in figures.

The technique takes a while to get used to, and even then it is mildly irritating—especially if you are used to working with the more elegant ASCII machines. Still, Baudot machines have one big advantage—they're available, and they're cheap!

## STOP PRESS: SC/MP GETS "TINY BASIC"

Just as this issue was going to press we received some happy news from NS Electronics regarding the SC/MP low cost development system described in our story on pages 78-81. By the time you read this, NS distributors should be able to supply a PROM card for the LCDS with a version of "Tiny BASIC".

No price information was available at the time of writing, but we understand that the program fits in 6 512-byte PROMs—i.e., 3k.

This news should be of particular interest to those seeking a way of getting into higher level programming at moderate cost.

We hope to give more details in a later issue.

**DYNAMIC ELECTRONIC INDUSTRIES**  
P.O. BOX, 162, SEAFORD, VICTORIA 3198 (PH. 786 6045)

# THIS MONTH'S SPECIAL!

## CAR RADIOS

Cat. No.

DAM — A.M. Manual \$25. 8 Transistors, 2 Diodes

DAP/D — A.M. Push Button \$42. DELUXE Model: 7 Transistors, 2 Diodes

DAP — A.M. Push Button \$38. Standard: 7 Transistors, 2 Diodes

DAPF — A.M./F.M. Push Button, 10 Transistors, 2 F.E.T.S., 2 I.C.'S

11 Diodes ONLY \$55.00

DAPFX — A.F./F.M. Push Button, 19 Transistors, 2 F.E.T.S., 4 I.C.'S, 11 Diodes, ONLY \$85.00

ALL PRICES INCLUDE Speakers and Aerial

\*Option Fibreglass Antenna only \$3 extra.

P/P \$3 extra

## ALSO AVAILABLE

### T.T.L. DIGITAL

I.C. No.	Description (All Dual in-line packs)	
7400	Quad 2 input nand gate	45c
7401	Quad 2 input nand gate open/collector	45c
7402	Quad 2 input nor gate	45c
7403	Quad 2 input nand gate/collector	45c
7404	Hex inverter	45c
7405	Hex inverter open/collector	45c
7408	Quad 2 input and gate	45c
7409	Quad 2 input and gate open/collector	45c
7410	Triple 4 input nand schmitt trigger	45c
7413	Dual 4 input nand schmitt trigger	45c
7420	Dual 4 input nand gate	45c
7430	Single 8 input nand gate	45c
7437	Quad 2 input nand gate/buffer	70c
7440	Dual 4 input buffer	45c
7441	1 of 10 decoder/driver	\$1.30
7442	B.C.D. to Decomal decoder/driver	\$1.10
7447	B.C.D. to 7 segment decoder/driver	\$1.70
7450	Dual and/or gate inverter/expander	45c
7451	Dual 2 input and/or invert gate	45c
7453	Expandable 4 wide 2 input and/or invert gate	45c
7454	4 wide 2 input and/or invert gate	45c
7460	Dual 4 input expander	45c
7470	J.K. edge triggered flip flop	60c
7472	J.K. M/S flip flop	70c
7473	Dual J.K. M/S flip flop	95c
7474	Dual D flip flop	95c
7475	4 Bit Latch	\$1.10
7476	Dual J.K. M/S flip flop	90c
7480	Full Adder	\$1.75
7482	2 Bit full adder	\$1.85
7483	4 Bit full adder	\$1.50
7486	Quad exclusive or gate	70c
7490	Decade counter	90c
7491	8 Bit shift register	\$1.30
7492	Divide by 12 counter	90c
7493	Binary counter	90c
7495	4 Bit right/left shift register	\$2.10
7496	5 Bit shift register	\$1.90
74107	Dual J.K. M/S flip flop	95c
74121	One-shot Multivibrator	70c
74141	B.C.D. to decimal decoder/driver	\$3.10
74192	Up/down decade counter	\$2.45
74193	Up/down binary counter	\$3.80
9001	J.K. M/S flip flop (74105)	\$1.30
9368	5 Bit latch BCD to 7 seg. decoder	\$3.10

### SCR's

C103B	200V	800mA	\$1.65
C106YI	30V	4A	95c
C106DI	400V	4A	\$1.40
C122D	400V	8A	\$2.00
C122E	500V	8A	\$2.50

### DIACS

ST2	\$1.20
ST4	90c

### TRIACS

SC141D	400V	6A	\$1.90
		10A	
SC146D	400V	(Use SC151D)	\$2.00
SC151D	400V	15A	\$2.20
SC250D	400V	15A	\$8.00

### LINEAR I.C.'s

LM301	8DIL	General Purpose Op. Amp.	90c.
LM308	14DIL	Super Beta Op. Amp.	\$2.30
LM339	14DIL	Quad Comparator	\$3.20
LM380	14DIL	5W. Power Audio Amplifier	\$1.70
LM381	14SDIL	Dual Low Noise Pre-amplifier	\$3.30
LM709	14DIL	High Performance Op. Amp.	\$1.00
LM741	8DIL	Frequency Compensated Op. Amp.	\$1.00
LM1808	14DIL	Sound IF	\$4.65
LM3900	8DIL	Quad Op. Amp.	\$1.60

### SILICONE BRIDGE RECTIFIERS

PD10	100	1.8A	\$1.30
PD40	400	1.8A	\$1.70
PD100	1KV	1.8A	\$4.10
PA40	400	8A	\$5.80
PA60	600	8A	\$6.60
PA100	1KV	8A	\$8.50
PB40	400	25A	\$7.00
PB100	1KV	25A	\$9.00*

### SILICONE RECTIFIER DIODES

A14A	100V	1A	20c
IN4002	200V	1A	20c
IN4004	400V	1A	20c
IN4007	1KV	1A	30c
IN5624	200V	5A	\$1.50
IN5625	400V	5A	\$1.70

All chips are supplied by National Semiconductors and Motorola

POST AND PACKAGING 50c

Prices correct at time of going to press

5% discount on orders over \$15.00.  
5% discount on quantities of 100 and over  
Please send me the following items and/or your free catalogue

Enclosed is a cheque for .....

Name .....

Address .....

E A 10.76





# WORLD imports

## HIGH-FIDELITY SPEAKERS

Fully imported  
PHILIPS SPEAKERS

AD0140/T8 new Tw. \$10 ea.  
AD0160/T8 Tw. \$11 ea.  
AD5060/SQ8 M/R \$13 ea.  
AD0210/SQ8 M/R \$32 ea.  
AD8066/W8 Bass. \$17 ea.  
AD10100/W8 Bass \$40 ea.  
AD1265/W8 Bass 28 ea.  
AD12100/W8 Bass \$45 ea.  
ADF500/4500/8 C/O

\$13.50 ea.

ADF12K12 atten. \$4 ea.  
ADF600/4000/8 C/O \$27 ea.  
System 7A pair \$165  
System 14 pair \$220  
Timber kits 82L pair \$40  
AD8K40 kit \$125  
AD12k12 kit \$220  
KEF Concerto SK3 \$275  
Baffle board kit \$320  
Cadenza board kit \$220

TANNOY HPD 315 12" \$360  
TANNOY HPD 385 15" \$470

Goodmans component speakers and kits for Hi-fi P.A. & Musical.

HOKUTONE 12" 3-way kits including HT37 Horn Tw. and C/overs \$120 pr.

CORAL, ETONE, CLARION, FANE, PIONEER, PLESSEY. All these and many more.

*And the biggest discounts on topname hi-fi equipment*

### WORLD IMPORTS

232 RUNDLE ST, ADELAIDE  
SOUTH AUSTRALIA

# Marketplace

**TRANSFORMER BARGAINS.** All 240V pri. 12VCT. 1A or 25VCT. 4A \$4.50; 25VCT. 1.2A or 40VCT. 7A \$7; 12VCT. 4.5A or 18V. 3A or 40VCT. 1.4A or 70VCT. .8A \$10; 18V. 4A or 25VCT. 2.5A or 40VCT. 1.7A or 70VCT. 1A \$10.50; 18V. 6.5A or 25VCT. 5A or 40VCT 3A or 70VCT. 1.7A \$15.50 Special offer 10V. 35A & 38VCT. 35A \$3.50; 30V. 3A & 9VCT. 1A \$9.70. Project & audio transformers, crossover, R.F. & project coils also. Send S.A.E. for catalog. **METAL BOXES,** galv steel & cover. 26ggs. 6 x 11 x 10 (cms) \$2.30; 22ggs. 10 x 20 x 13 \$3.50. 8 x 15 x 12 \$3.20. 10 x 23 x 17 \$4. All prices include postage, 10% discount above \$20. R.K.O. Electronics, P.O. Box 150, Springvale, Vic. 3171. Phone 96 2061.

**URGENT STOCKTAKING SALE . . . DISCOUNT FOR BULK SALE** MOST OF THE FOLLOWING LINES HAVE BEEN REDUCED EVEN MORE TO BE SOLD OUT. WE'LL SAY NO MORE. LOOK AT THESE GIVEAWAY PRICES!!! **SEMICONDUCTORS AT CRAZY PRICES!!!** 40250 (2N3054)—10 for \$11. 2N6107—10 for \$8. 2SA 353 (AF126)—10 for \$5. BC157—10 for \$3. 8F198—10 for \$4.50. AS320—200 for \$20. AS148—200 for \$20. AS149—200 for \$20. XA101 (OC45)—100 for \$10. **INTEGRATED CIRCUITS**—HA1322 Audio Power I.C. Incl. Cct diagram 5.5 Watts Peak—4 for \$7 or 20 for \$28. CA3012 (Can)—5 for \$5. CA3013 (Can)—5 for \$5. CA3018 (Can)—5 for \$5. **ELECTROLYTICS** (Pigtails): 1000uf/25v—25 for \$9. 2uf/300v—100 for \$11. Buf/300v—25 for \$6. 40uf/200v—10 for \$6. **STYROSEAL CAPS**—Top Quality At Ridiculous Prices. These won't last long 100pf/125v—200 for \$5. 680pf/125v—100 for \$2.75. 680pf/630v—100 for \$3. 680pf/1000v—200 for \$10. **TANTALUMS**—(Miniature) 7uf/3v—100 for \$3. **POWER RESISTORS**—Top Quality. 5.6k, 5%, 7w—100 for \$15. 5.6k, 5%, 6w—100 for \$14. 4.7k, 5%, 7w—100 for \$16. **COPPER CLAD BOARD**—Top Quality. IDEAL FOR GROUP BUYERS OR QUANTITY BUYERS. 6 1/2" x 5"—10 for \$4.50 or 50 for \$20. 9" x 12"—10 for \$15. (Please don't forget to add extra postage for these quantities) **HIGH VOLTAGE CERAMIC DISC CAPACITORS**—4700pf/500v—100 for \$3. 100pf/3kv—10 for \$1.75. 330pf/2.5kv—10 for \$1.40. 180pf/4kv—10 for \$1.50. **TUNING CONDENSORS**—(2-gang)—5 for \$10. **FEED THROUGH CERAMICS**—(1000pf/350v)—20 for \$1.80. ON TOP OF THESE SUPER VALUES THERE IS A FURTHER DISCOUNT OF—10% For Orders Over \$100, 12% For Orders Over \$200, 13% For Orders Over \$300. **STOCK UP NOW OR YOU'LL BE SORRY!!! POST YOUR ORDER TODAY THE BARGAINS YOU WANT MAY BE GONE TOMORROW!!!** Post and Pack Basic 60c or extra for heavy parcels. **MICRONICS,** P.O. Box 175, Randwick, N.S.W. 2031

**AERIALS, TELEVISION AND F.M.** For the best selection of aerials in Melbourne Adrian Michell's TELEVISION REPLACEMENTS Rear 139 Union Rd. Surrey Hills, Vic. 3127. Phone 89 1019. Where the T.V. technicians meet.

## TIME CLOCKS



<b>SANGAMO</b> \$16.00 DAY OMIT DEVICE	<b>VENNER</b> \$16.00 now with spring reserve	<b>SANGAMO</b> \$13.50 LESS DAY OMIT DEVICE
---	--	---

240V 50 cs      15A Contacts

Used tested and guaranteed  
PACK & POST N.S.W. \$2.00  
Vic. & Qld. \$2.50 W.A. \$3.00

**CLOCK DISPOSAL CO.**  
P.O. Box 147  
LINDFIELD, N.S.W. 2070

**RESISTORS AND CAPACITORS.** Resistors all E12 values. 1/2 watt carbon film. 10 ohm to 1 meg 2 cents each I.R.H. GL 1/2 or GLP. 1/2 watt Metal glaze 10 ohm — 470k 3 cents each or 2.5 cents over 250. 1 watt 1 ohm to 1k 6 cents each or 5 cents over 100 PACKS STANDARD PACK contains 5 each of E12 values in ranges shown. **COMPUTER PACK** contains quantities based on general usage 1/2 watt 285 resistors \$7.00 1/2 watt 305 resistors \$5.90. **CAPACITORS** ELECTROLYTICS single ended uprights Mfd 35 v.w. 1, 2, 2, 3, 3, 4, 7, 10, 22, 10 cents each. 33 47, 15 cents. 25 v.w. 100 16 cents each. 220 25 cents each. 470 35 cents. Polyester Greencaps 100 v.w. 001, 0022, 0033, 0047, 0056, 0068, 7 cents each. 01, 022, 033, 047, 056, 068, 082, 10 cents each. 1, 22, 13 cents each. Poly Pack 5 cents of these values \$6.00. 75 capacitors Other components see E.A. June, 1976. All components brand new from manufacturers or agents. Each value of component individually packed. Post and packing included in all orders over \$6.50. For orders less than \$6.50 add 40 cents for post and packing. 5% discount on orders over \$35.00. 10% discount on orders over \$75.00. Send orders to RAM ELECTRONICS, 575 Sydney Road, Seaforth, N.S.W. 2092. Please send cheque or money order.

**AUSTRALIAN RADIO DX CLUB** — Covering overseas and long distance radio reception, including short-wave and medium-wave. Monthly bulletin for all members. For full details, write enclosing 40c to ARDXC, 3 Kadana St, Oak Park, Victoria 3046.

**LCD DIGITAL CLOCK**—\$40 others. Digital Clock from \$15. Write Hong Kong Electronic Bargain Centre, PO Box K2618, Hong Kong, for free catalogue.

**P.C. BOARDS** are available for P.E. JOANNA Touch Sensitive Electronic PIANO, PUBLISHED July, 75 in Practical Electronics. A complete set of 14 P.C. boards \$30.99, P & P \$1.20.

Hear the sound and various voicing effects of P.E. JOANNA Electronic Piano. Cassette Tape Recording (Approx. 20 min.) \$4.50, P & P \$0.60.

P.C. Boards for RHYTHM GENERATOR, Practical Wireless, June, 76 a set of 3 \$11.50, P & P \$0.60.

NOVELTY MART, P.O. BOX 390  
MASCOT, N.S.W. 2020

**SHORTWAVE LISTENERS & DXERS:** The "Southern Cross DX Club" is for you! Members in all states. Details for 18 cents stamp to — GPO Box 336, Adelaide, South Australia 5001.

**PC LAMINATES TO CLEAR**—3 1/2" x 24" x 1/16", single-sided phenolic. 1 oz copper. \$2.50 for a pack of 5. Please add postage. Weight 700gm. **Hobby Hire,** 16 Coveney St, Bexley, 2207. Tel 50 4361

**BOOMERANG TAPE RECORDING CLUB** — Full details 9" x 4" S.A.E. P.O. Box 118, Wallington, N.S.W. 2820.

**STEREO SANYO DCX 2000K AM FM HI FI Amp** 20w per Ch \$179. **BELT DRIVE T.** Table superb arm mag cart. in box with hinged lid \$89. **SPEAKERS** 8" wf 2" tw in walnut boxes \$89 pr. also **WHARFDALES** 12" wf 3" tw in walnut boxes \$149 pr. All brand new in cartons fully guaranteed. **STAFFORD TV,** 3897122, 245 Bronte Rd, Waverley, NSW 2024.

## INSTRUMENT HIRE

All types of test and measuring instruments. Phone or write for

**FREE CATALOGUE**

Address: **HOBBY HIRE**  
**16 COVENEY ST**  
**BEXLEY 2207**  
**P.O. BOX 177**  
**BEXLEY 2207**

Phone: **(02) 50 4361**

*We Deliver*

*Anywhere in Australia*  
**BANKCARD WELCOMED**



**DISCOVER the exciting world of EXPLORATION!**



**VISIT OUR MODERN SHOWROOMS—SEE OUR FASCINATING DISPLAY**

Telescopes for every purpose, build-it-yourself kits binoculars from pocket size to giant 15 x 80 models, microscopes and weather equipment for the student and hobbyist, astronomy books, charts and atlases.

Send 45c to Dept. 'A', P.O. Box 568, Crows Nest, 2065 for informative catalogue.

**Astro-Optical Supplies Pty. Ltd.**

11 CLARKE STREET CROWS NEST, SYDNEY N.S.W. 2065 PH: 43 4360  
200 BOURKE STREET MID CITY ARCADE MELBOURNE VIC. PH: 663 2761

**WILLIS TRADING CO. PTY. LTD.**

PERTH G.P.O. Box No. X2217 W.A. 6001 429 MURRAY ST. PERTH W.A. 21 7609 21 7600

**MULTIMETER KIT**


Build your own meter—complete with PC board and full instructions. 16 ranges. \$16.95 ea.



**Drake General Coverage Receiver**  
.5mHz to 30mHz Battery & Mains  
\$299.00 Plus P & P.

All prices plus P & P

**TRANSISTOR RADIO CHASSIS**

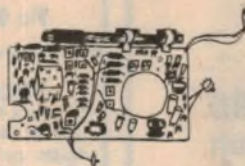

As in most small radios. Some AM-FM types. Complete with all components, except speakers. Most in working order. Priced at only 75c ea.

**Electronic Tool Kit \$19.75**



Tweezers  
File  
Soldering Iron  
Solder  
Philips S/Driver  
2 Screw Drivers  
Long Nose Pliers  
Flat Nose Pliers  
End Cutters  
Vinyl Zip Case



**VHF CONVERTER TUNER**  
110-136 MHz couples to broadcast receiver. \$7.95 ea.

**1 Watt 3 channel C.B. transceiver**  
• With call system  
• External aerial

Provision for external speaker, aerial and power supply \$50.00 Post \$1 extra.

And other types available.

**NC310 1 WATT TRANSCEIVER**



FM Monitor Receiver 12 Channel available for either Low or High Band \$110.00 plus Crystals.

**ELECTROCRAFT PTY. LTD.**

106A Hampden Rd. Artarmon, 2064 Phone 411-2989

Distributors of Belling Lee, Channel Master, Ecraft, Hills, Hi.Q, Lab Gear, Kingray, Matchmaster. Largest Television range of aerial equipment in Sydney.

**TELEVISION AERIALS, DISTRIBUTION AMPLIFIERS, EQUIPMENT AND ACCESSORIES WHOLESALE, TRADE AND RETAIL SUPPLIED.**

**ECRAFT**

	Price
Neosid Balun 75/300 uncased	\$0.65
O S A B Outside aerial balun (water proof)	3.81
6 SB 6ft Balun Fly Lead	3.65
P.S.B. Plug and Terminal Balun	2.53
2 75 T/S 2-way 75 ohm Transformer Splitter box	6.74
3 75 T/S 3-way 75 ohm Transformer Splitter box	8.41
4 75 T/S 4-way 75 ohm Transformer Splitter box	8.94
5 75 T/S 5-way 75ohm Transformer Splitter box	12.66
2 3T 2-way 300 ohm Splitter box	4.48
3 3T 2-way 300 ohm Splitter box	5.86
4 3T 2-way 300 ohm Splitter box	7.12
Adjustable Low Band Attenuator	6.31
10" diameter degaussing coil	24.00

**TELEVISION AERIALS FOR COLOUR**

	Price
<b>CHANNELMASTER</b>	
9el Colour Crossfire 3615A	\$38.34
13el Colour Crossfire 3614A	43.91
17el Colour Crossfire 3613A	57.45
21el Colour Crossfire 3612A	66.64
24el Colour Crossfire 3617A	70.87
28el Super Crossfire 3617A	106.79
Super Colouray the 3111 Ghost Killing Aerial	36.50
2el Small Colouray 3110	22.75

**HILLS E.F.C. RANGE 75 ohm**

E.F.C. 1	\$24.17
E.F.C. 2	32.06
E.F.C. 3/24	46.65
E.F.C. 4/24	58.69



**HILLS THE NEW TELRAY RANGE—**  
All Australia V.H.F. Channels & F.M.

6el	TL1	\$19.52
8el	TL2	26.84
9el	TL3	32.70
11el	TL4	39.70

**HILLS AERIALS**

2010 Airways	\$42.50
CA16 Phased Array	33.16
Extra Gain Lift els for CA16	3.33
8el 215	19.26

**AUSTENNA STARFIRE RANGE**

7EL	CC7FA	\$26.39
9EL	CC9FA	31.18
13EL	CC14FA	57.00
18EL	CC19FA	62.17

**FM AERIALS**

Hills	2EL FM1	\$8.17
HILLS	3EL 353	11.16
Hills	3EL FM3	17.54
HI-Q	4EL	17.05
HI-Q	Gutter clip	11.55
Matchmaster	G2FM	17.54
Austenna	FM3F	19.96

**COAXIAL CABLES**

	Attenuation per 100ft at 200MHz	Reel Size	Price
Beiden 9242 Double screened with	4.0 dB	500 ft	\$42.28
Beiden 9248 Duofoil and Braid Aluminium	3.1 dB	500 ft	58.61
TVM1A Concordia Copper Screened	4.4 dB	100 metre	30.15
Hartland WH89 Copper Braid	3.3 dB	100 metre	36.92
Hartland WH87 Copper Braid	6.0 dB	100 metre	26.65
Hartland WH86 Copper Braid	6.5 dB	100 metre	19.25
300 ohm Feeder Cable	1.8 dB	100 metre	8.80
Open wire line 300 ohm	1.5 dB	100 ft	9.90
Open wire line 300 ohm	1.5 dB	300 ft	29.80

**LAB GEAR AMPLIFIERS**

	Price
<b>VHF</b>	
Mast head 22 dB 75 ohm	\$72.43
CM 6014/DA 20 dB	60.25
CM 6034/DA 4 outlets 8 dB each	54.90
CM 6036/DA VHF 30dB UHF 28dB	84.63
Talaverta (VHF to UHF frequency converter)	67.48

**KINGRAY AMPLIFIERS**

	Price
D15/500 m/V	\$48.80
D30/500 m/V	57.95
D40/600 m/V	79.30
D12/1500 m/V	67.10
MH 20 mast Head 300-75 ohm	64.63

**TELESCOPIC MASTS**

20ft	1.8g steel in 10ft sections must be guyed.	\$19.30
30ft		\$30.81
40ft		42.00
50ft		54.42

**Stolle Aerial Rotator with Thrust Bearing for heavier rigs \$101.43**

**ALL TYPES OF HARDWARE IN STOCK**

Wall Brackets, Chimney Mounts, J Brackets, Guy Rings & Guy Wire Masts from 8ft to 50ft.



# SCOOP BUY FROM SHEEN!

NEW MODEL 909



**\$12.95 each**

- FEATURES:** 8 Digit Display • Exchange Key (M + M-MRMS) • 4 Key Memory • Square Root • Percentage • Sign Change



**ALSO AT THE NEW LOW PRICE \$19.95 EACH**

**Adaptor Available For Each Model**

**\$7.50 EXTRA P. & P. \$2.00**

Only a limited number of the famous "Sheen" model "1000" scientific calculator available at this price, so be early.

**Features**

- 8 Digit display
- $\sqrt{x}$   $\pi$   $1/x$
- Cos, Sin, Tan
- M + M - MS
- $\cos^{-1}$ ,  $\sin^{-1}$ ,  $\tan^{-1}$
- Guaranteed
- Log  $Y^X E^x$

Send cheque or money order to:  
**SHEEN ELECTRONICS AUST  
5 FREIGHT ROAD  
TULLAMARINE, VIC. 3043**

# LANTHUR ELECTRONICS

69 Buchanan Avenue, North Balwyn,  
Vic. 3104 P.O Box 162. Ph. 85 4061

## ELECTRIC MOTOR SPEED CONTROLLER KITS.

Especially for hand tools, drills etc. or other brush type ac/dc motors. Consists of triac, resistor diodes, pot., knob, 3 pin base & plug and circuit. 10 amp. (2400 watt) rating \$9.75  
Price includes postage.

## LAMP DIMMER KITS

Will control incandescent lamps down to out. Contains triac, diac, caps, resistors, pot. knob, ferrite rod, enamel wire & circuit. 10 amp. (2400 watt) rating. \$7.95  
Price includes postage.

## PLASTIC CABINETS

Suitable for above speed controller and lamp dimmer. \$1.55  
Post free if supplied with dimmer or controller. Otherwise post 0.40.

## BATTERY CHARGER KITS

For charging wet batteries. 12 volt at 2 amp. Consists of transformer, bridge rectifier, ballast resistor and circuit. \$9.50  
Plus postage-Vic. \$1.00, WA \$2.50, Other \$2.

## POWER SUPPLY KITS

Replace batteries in radios, tape recorders, instruments etc.

Will supply dc. voltages from 6 to 15. Consists of tapped transformer, bridge rectifier, filter cap. & circuit.

One amp rating \$8.50  
Plus postage Vic \$1.00, WA \$2.00, Other \$1.80.

Two amp. rating \$17.50  
Plus postage Vic \$1.00, WA \$2.50, Other \$2.

## METERS

Ten amp. ac/dc moving iron type. Approx. size 55 x 55mm \$4.95

## BRIDGE RECTIFIERS

Miniature silicon type. 400 piv at 1.5 amp. \$1.20 each. Five for \$5.00

## SILICON DIODES

Automotive stud mount type. Rating 200 piv at 25 amp. Fwd. or rev. avail \$1.95

## BATTERY CHARGER RECTIFIERS

Selenium plate bridge rated at 25 volt 6 amp. \$6.95

Above 4 items are post free.

# Advertising Index

ACE Radio	121
Aegis Pty Ltd	59
Agfa Gevaert Ltd.	4
Akai Electric Co	18
Apollo Hi-Fi Centre	33
Applied Technology Pty. Ltd.	86
Astro Optical Supplies Pty. Ltd.	127
Audio Engineers Pty. Ltd.	12,96
Audio Telex Communications Pty. Ltd.	99
Australian Time Equipment Pty. Ltd.	110
Automation Instruments Pty. Ltd.	89
BKX Electronic Supply Service	76
Bail Electronic Service	124
Bay Rd. Electronics	105
Bright Star Crystals Pty. Ltd.	110
British Merchandising Pty. Ltd.	102, 105
CRC Chemicals Australia Pty. Ltd.	118
CS Services	112
Chapman L. E.	123
Classic Radio	98
Clock Disposal Co.	126
Convoy International Pty. Ltd.	6
Cunningham R.H. Pty. Ltd.	61, 111
Danish Hi-Fi	21
Deitch Bros	122
Dick Smith Electronics Pty. Ltd.	48, 62, 72, 73, 88
Dynamic Electronics Industries	125
E. D. & E. (Sales) Pty. Ltd.	66
Educational Kits	112
Electrocraft Pty. Ltd.	127
Electronic Development & Sales Pty. Ltd.	107
Elmeasco Instruments Pty. Ltd.	44
Ferguson Transformers Pty. Ltd.	108
Festival Records	103
Fraser Products	51
George Hawthorn Electronics	104
General Electronic Services Pty. Ltd.	114
Haco Distributing Agencies Pty. Ltd.	OBC
Hagemeyer Australia	IBC
Ham Radio Electronics	124
Harman Australia Pty. Ltd.	16
Heath Kit Australia	109
Hobby Hire	126
Interson Pty. Ltd.	40
Lafayette Electronics	71
Lanthur Electronics	128
Marconi School of Wireless	71
NS Electronics	82, 83
OBC Imports	24
Optro Pty. Ltd.	42, 59
Peter Shalley	92
Philips Elcoma	2
Philips Test & Measuring Instruments	74
Photimport	5, 100
Radio Despatch Service	77
RCS Radio Pty. Ltd.	110
Richard Foote (Australia) Pty. Ltd.	111
Sansui Electric Co.	8, 34
Sheen Electronics Austr.	128
Sony Kemtron	IFC, 28
Star Delta Co. Pty. Ltd.	113
Stanton Magnetics	10
Stott's Magna Sighter	51
Stott's Technical College	65
Tandy International Electronics Pty. Ltd.	centre catalog
Technical Book & Magazine Co. Pty. Ltd.	115
Techniparts	108
Vicom International	116
Video Hi-Fi Centre	114
WHK Electronics	94, 95
Warburton Franki Pty. Ltd.	58
Webster Electronics	37
Willis Trading Co.	127
Wireless Institute of Australia	119
World Imports	126

# SUBSCRIPTION SERVICE



## Subscription Rates

**\$A14.00 per year within Australia.**  
**\$A17.00 per year elsewhere.**

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney, 2001. Subscription will start with first available issue.

Name . . . . .  
Address . . . . .  
Postcode . . . . . Enclosed is . . . . . for . . . . . years



# For what you are about to receive.



You're going to be very thankful. Because our new line-up of stereo receivers are in the best traditions of our expertise in the sound field. Apart from the many technical innovations inside, all models reflect the best in modern design combined with control layouts to give you an ease of operation you've never experienced before. Best of all, each lives up to our firm policy of Original Sound Realism.

Features JVC-JR-S600 FM/AM TUNER (illustrated) With 5-way SEA: tape dubbing: hi and low filters: THD 0.1%: FM noise reduction circuit: 110 watts minimum per channel RMS: FM sensitivity, 1.7uV: signal to noise ratio, 65dB (Stereo): AM suppression, 55dB: stereo separation, 1KHz-50dB: alternate channel selectivity, 80dB.

Others in the JR-S range: JR-S400 — 70 watts per channel RMS minimum. JR-S300 — 50 watts per channel RMS minimum. JR-S200 — 35 watts per channel RMS minimum. JR-S100 — 20 watts per channel RMS minimum.

## JVC

the right choice

For details on JVC Hi Fi Equipment, write to: JVC Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.





ST7200

SU7200

# Matching Pair Performance and Appearance

What comes out of a tuner and amplifier is only as good as what goes into them.

And we've put a lot into both.


Both specially matched for the finest and most authentic music reproduction.

First the ST7200 Tuner allows you to enjoy FM/AM Radio that is second to none. Pin point accuracy is assured by the full sized dial and signal/Tuner meter.

As for our SU7200 amplifier, we list a full 22 watts RMS per channel, 41 click stop volume control, low distortion circuit, loudness switch, tape monitor switch, and a power bandwidth of 5-100 KHz.

Impressive features?

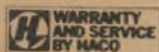Any way you want to look at it, you'll agree this matched pair from Technics would be hard to beat.



For a National Technics Catalogue please write to:  
National Technics Advisory Service, P.O. Box 49, Kensington, NSW 2033  
(Specifications subject to change without notice.)



**Technics**  
hi-fi

WT.GD122T