

ELECTRONICS

Australia

HiFi, Radio & Computers

JUNE 1979

AUST. \$1.40* NZ \$1.40



TYPEWRITER, CONTROL
CENTRE FOR THE DISABLED

NEW CHESS COMPUTER
SPEAKS!



HOW THEY TRIED TO KEEP THE
"SKYLAB" SATELLITE IN ORBIT

- LOW COST STEREO AMPLIFIER
- NEW ELECTRONIC LOCK HAS
10 MILLION COMBINATIONS!

The High Speed DC integrated amplifier has arrived!

(It's fast. It's accurate. It's three-dimensional)

Think of the most mind-bending music you know. Or an orchestra playing a full crescendo. The Kenwood High Speed DC integrated amplifier lets you hear every note. Clearly.

It will also let you hear the subtle sound of fingers stroking guitar strings. Or the sounds made by the lips of your favourite singer articulating each word, just in front of the mike.

In other words, we're talking about *quality* in reproduced sound. And authenticity.

We could tell you about the astonishing transient

response of the Kenwood amplifiers. And about their wonderfully clean low end response, free of phase distortion. About their remarkable clarity throughout the audible range.

Or we could describe the state-of-the-art circuitry that produces all this.

But you must hear for yourself just how much musical space and depth these amplifiers can offer. Fresh from your own speakers.

It's a whole new world of realism in music.

"You can see full range of Kenwood new High-Speed Amplifier at '79 Australian CES"

THE AUDIBLE DIFFERENCE

HI-SPEED



KA-907

KA-701



KA-801



 **KENWOOD**

For information, please write to: HM-SECTION,
TRIO-KENWOOD CORPORATION 6-17, 3-chome, Aobadai, Meguro-ku, Tokyo, Japan.
TRIO-KENWOOD (AUSTRALIA) PTY. LTD. 30 Whiting St., Artarmon, N.S.W. 2064, Australia Tel: 439-4322


ELECTRONICS

Australia


VOL. 41 No. 3

JUNE, 1979

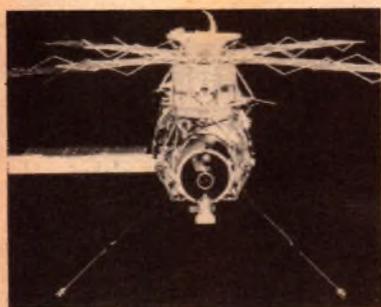Australia's largest selling electronics & hi-fi magazine



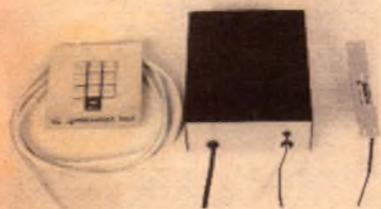America's Skylab will re-enter the Earth's atmosphere and crash sometime towards the end of this month; but only after an incredible battle by NASA to save the ailing space station. The story of this battle begins on page 10.



Give your home increased security with this space-age electronic combination lock. Full construction details are on page 44.

On the cover

Called "Popstar", this typewriter has been specially designed for the disabled and can be operated using pressure pads, a joystick, or a suck/blow unit. For more information on Popstar, refer to page 4 of the February issue. Inset shows the new Voice Chess Challenger, the computer that plays chess and talks (see p5). Main picture courtesy British Information Service; inset courtesy Futuretronics Pty Ltd.

FEATURES

- SKYLAB: A RESCUE EFFORT THAT FAILED** *The story of a doomed space station* 10
CHARLES DAVID TANDY *From a paper boy to a billion dollars* 17
INTERFERENCE-FREE DATA TRANSMISSION *Linking data to optical fibres* 18

HIFI TOPICS AND REVIEWS

- SEEING IS BELIEVING — ESPECIALLY WITH STYLI** *Improving the hifi stylus* 29
AUDIO TALK: RUMBLE — A PROBLEM OF MEASUREMENT *Check your hifi* 36
HIFI REVIEW *Teac A-300 3-head stereo cassette deck* 39
HIFI REVIEW *Sennheiser HD420 & HD430 dynamic headphones* 42

PROJECTS AND CIRCUITS

- AN ELECTRONIC COMBINATION LOCK** *Increased security for your home* 44
DESIGNING VOLTAGE REFERENCE CIRCUITS *Using low-cost parts* 54
A PLAYMASTER AMPLIFIER FOR FLATS & HOMES UNITS PT. 2
The construction details 56
PRACTICAL ELECTRONICS: SOLDER, FLUXES & IRONS *How to use them* 66
INDUCTANCE RANGES FOR THE DIRECT-C METER *Measure from 0.1 uH to 3H* 75

MICROCOMPUTERS

- SOUTHWEST'S CT-82 "SUPER INTELLIGENT" TERMINAL** 81
DREAM 6800 COMPUTER PT. 2 *Easy to build, fun to drive* 82
A POWER SUPPLY FOR THE DREAM 6800 *Three rails: $\pm 5V$ & $+12V$* 90
A LED DISPLAY FOR THE 2650 MINI COMPUTER *The most complex clock in town!* 94
MICROCOMPUTER NEWS & PRODUCTS 96

AMATEUR RADIO, CB SCENE, DX

- AMATEUR RADIO** *Sydney hosts WARC 79 preparatory seminar* 106
SHORTWAVE SCENE *Sunspots force the use of higher frequencies* 112
CB SCENE *CB: more than its share of awkward questions* 115

COLUMNS


- FORUM** *They're working on 3D films and TV — but don't hold your breath* 24
THE SERVICEMAN *The same symptoms, but quite different faults* 78
RECORD REVIEWS *Classical, popular, devotional, jazz* 99

DEPARTMENTS

- EDITORIAL 3 — NEWS HIGHLIGHTS 4 — CIRCUIT & DESIGN IDEAS 71 — NEW PRODUCTS 118 — BOOKS & LITERATURE 123 — INFORMATION CENTRE 124 — MARKETPLACE 126 — INDEX TO ADVERTISERS 128 — NOTES & ERRATA 125**

ONLY \$9-40

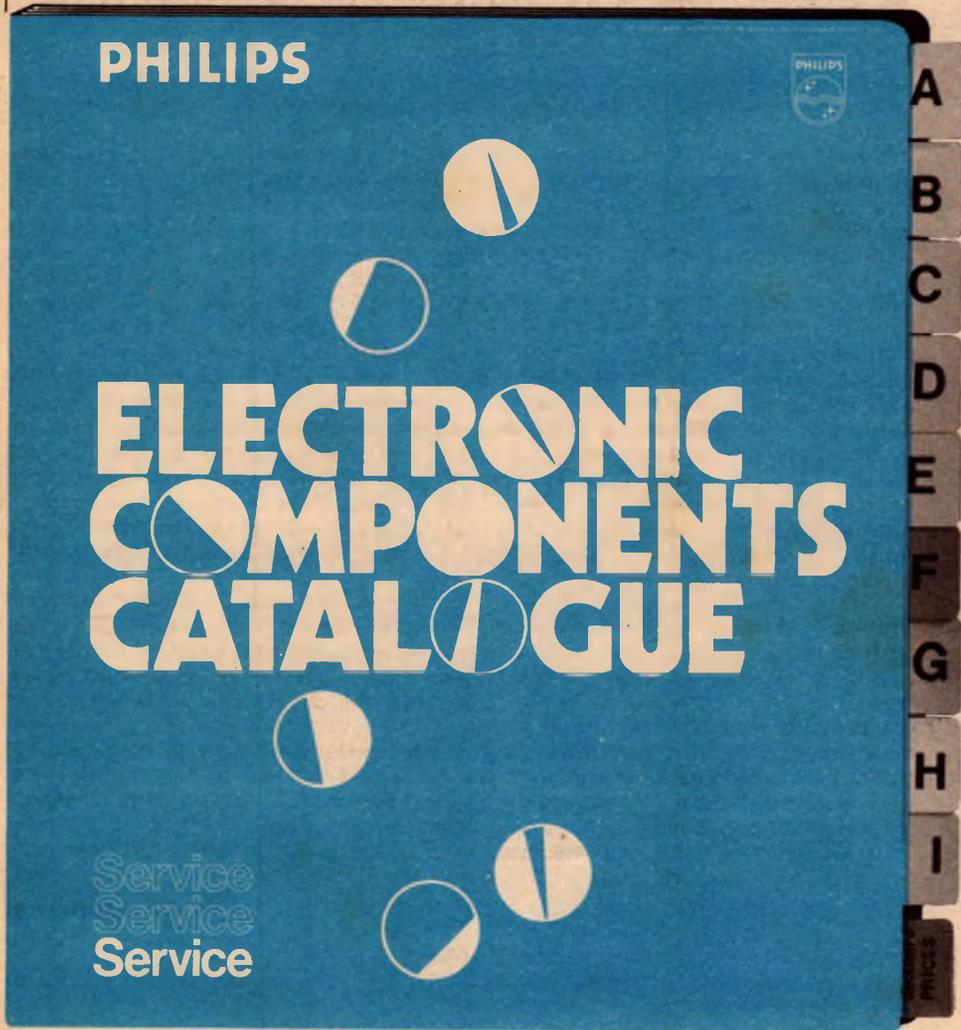FOR THIS COMPREHENSIVE ELECTRONIC COMPONENTS AND ACCESSORIES LOOSE-LEAF CATALOGUE.



- PAGES UPDATED WITH NEW PRODUCTS
- PRICES UPDATED
- REPLACEMENT PAGES AVAILABLE

The new Electronic Components Catalogue from Philips Service is a comprehensive guide to Electronic components and accessories available in Australia.

It is compiled of 350 regularly updated pages complete with an easy-to-follow, alphabetical index system.

The price also includes the updating and page replacement services to keep you informed of current prices and new products.

SEND IN FOR YOUR COPY TODAY.
Or for further enquiries, please telephone:

Sydney 736 1233, Newcastle 61 1631,
Canberra 95 0321, Melbourne 699 2731,
Hobart 28 0121, Brisbane 221 5422,
Townsville 79 7422, Adelaide 223 4735,
Perth 322 4653.

PHILIPS

To: Philips Central Service Division,
443 Concord Road,
RHODES NSW 2138

Please send me catalogues @ \$9.40 each
Cheque/postal order for \$ _____ is enclosed.

Name: _____

Position: _____

Company: _____

Address: _____

Telephone: _____

McCann 184.0009



Editorial Viewpoint

A consumer's right: the circuit diagram

EDITOR-IN-CHIEF

Neville Williams
M.I.R.E.E. (Aust.) (VK2XV)

EDITOR

Jamieson Rowe
B.A. (Sydney), B.Sc (Technology, NSW)
M.I.R.E.E. (Aust.) (VK2ZLO/T)

ASSISTANT EDITOR

Philip Watson
A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

PRODUCT REVIEWS

Leo Simpson

TECHNICAL PROJECTS

Ron deJong, B.E. (Hons, NSW), B.Sc.
Ian Pogson (VK2AZN/T)

GRAPHICS

Robert Flynn

PRODUCTION

Danny Hooper

ADVERTISING MANAGER

Selwyn Sayers

CIRCULATION MANAGER

Alan Parker

I noted with interest this month that the Television and Electronic Services Association, representing many electronic service technicians and firms, has recommended to the Minister for Business and Consumer Affairs that it be made mandatory for a circuit diagram to be provided with all electronic equipment sold. The Association made the point that this would not only facilitate servicing of equipment currently very difficult to have repaired, but would also be likely to reduce servicing costs as a whole by reducing servicing time.

This seems to me such a sensible and worthwhile suggestion that it deserves the full support of everyone — not just those in the servicing industry, but all of us with electronic appliances and equipment.

It has long seemed to me incredible that all sorts of electronic equipment could be sold without even the most basic and essential servicing information: the circuit diagram. Having been involved in part-time servicing myself in the past, I know just how difficult it is to service equipment without this vital information.

Not that a circuit diagram provides all of the information needed for efficient servicing, by any means. But it is a tremendous improvement over having nothing, which is often the situation at present. This is particularly so when it comes to esoteric brands of imported domestic appliances, many specialised items of industrial and medical equipment, some amateur radio and CB gear, and quite a few personal microcomputers.

Of course, some suppliers will argue that servicing manuals are often available for much of this equipment, at least in theory. But most service people will tell you that even they find these manuals at times almost impossible to obtain. If they find it difficult, you can imagine how hard it would be for the average consumer. In any case, service manuals are generally regarded as an "optional extra", and can cost quite a few dollars.

It seems to me that consumers have a right to expect that any piece of equipment they buy comes complete with the basic information necessary to service it, as a matter of course. For electronic and electrical equipment this should mean a "captive" circuit diagram, at the very least.

In short, I think the TESA recommendation deserves the widest possible support. If you agree, why not write to the Minister yourself?

— Jamieson Rowe

Registered for posting as a publication — Category B.

Printed by Magazine Printers Pty Ltd. of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd of Regent St. Sydney

Editorial Office

57 Regent St. Sydney 2008.
Phone (02) 699 3622
Postal Address: PO Box 163, Beaconsfield 2014

Advertising Offices

Sydney — 57 Regent St. Sydney 2008
Phone (02) 699 3622
Representative: Narciso Pimentel.

Melbourne — 392 Little Collins St. Melbourne
3000 Phone (03) 602 3033
Representative: Keith Watts

Adelaide — Charles F. Brown & Associates Ltd.
254 Melbourne St. North Adelaide 5006

Representative: Tom Duffy, (08) 267 4433.

Perth — 454 Murray Street, Perth 6000

Representative: Ashley Croft, (09) 21 8217

Subscriptions

Subscription Dept. John Fairfax & Sons Ltd. GPO
Box 506, Sydney 2001

Enquiries: Phone (02) 20944, ext 2589

Circulation Office

21 Morley Ave. Rosebery, Sydney 2018

Phone (02) 663 3911

Distribution


Distributed in NSW by Sungravure Pty Ltd, 57 Regent St. Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St. Adelaide; in Western Australia by

Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A Asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.

*Recommended and maximum price only.

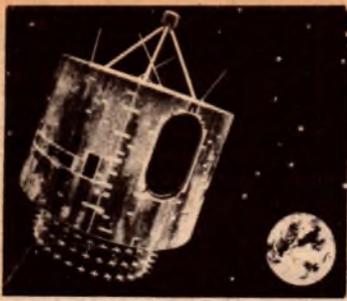

News Highlights

Squabble over satellite space

A conference which concluded in Sydney last April has laid ground rules for serious international politicking in September over a natural resource 36,000 kilometres in space.

by Ian Reinecke,
Australian Financial Review

The resource concerned is the geostationary satellite orbit, a fairly loosely defined strip of nothingness which encircles the earth above the equator.

It has assumed a significance greater than any other piece of space because it is along this tramline in the sky that "fixed" communications satellites

travel. They remain in a position constant with the earth's surface as it revolves with the result that the ground stations to which they transmit need not have complex and expensive "tracking" facilities.

Like most other natural resources, the geostationary orbit is finite but is "worn out" only by the way it is used. Inefficient, unco-ordinated use of the orbit wears it out quicker than if it is managed by international agreement to minimise interference between satellites operating within it.

Mr E. Craig, assistant director, advanced techniques, for Telecom Australia, delivered a keynote address on management of the resource at the conference, jointly sponsored by the

Australian Government. It is the final conference in a series of three regional meetings as a lead up to the International Telecommunications Union's World Administrative Radio Conference in Geneva in September.

Here, competing nations will seek to maintain access to the geostationary orbit, particularly the Third World countries. Their concern is the possibility of being blocked out of the resource by the satellites of the developed countries, which will multiply quickly as launch costs decline.

There is room within the orbit for a huge number of satellites but it becomes crowded when signals from different satellites interfere sufficiently with each other to cause problems.

Lexicon translator now in Aust!

Readers may recall that in the March issue we ran a news item on the Lexicon LK-3000 — a pocket-sized computer which can be used to translate languages. The device is now being imported into Australia by Hanimex Pty Ltd, and should be available in major department stores by the time this item appears.

At last reports, the LK-3000 was rapidly earning a fortune for its inventor Anastatos Kyriakides, a young Greek migrant in the United States. The device, which looks like a pocket calculator, works by entering a message into the unit via the keyboard and pressing a button. Almost instantly, a translation of the sentence in a designated language appears across a red LED display.

The LK-3000 is programmed by plug-in modules that simply slot into the back of the keyboard and display assembly. Each module houses an 8-bit microcomputer and a 64k ROM which



stores some 1500 words or phrases in both English and the language it is to translate.

Currently available modules are capable of translating English into Spanish, French, German, Italian, Polish, Portuguese and phoenitic Greek. Soon to come are Swedish and phonetic Russian and Japanese transla-

tion modules.

But the LK-3000 is more than just a language translator — it's a miniature computer terminal as well. The device will be used as the official hand-held translator for the 1980 Olympic Games in Moscow, and Lexicon will offer modules containing records and statistics of previous Olympic events.

Computer plays chess — and talks!

American manufacturer Fidelity Electronics Ltd has added a voice to its now famous Chess Challenger, a microprocessor based chess game. The new game is called "Voice Chess Challenger", and takes its place alongside the earlier Chess Challenger 7 and Chess Challenger 10 games.

Voice Chess Challenger is based on the Zilog Z80A CPU and is said to include the most powerful chess program ever placed in a microprocessor. Backing up the CPU are 8k bytes of ROM to store the game program and rules, another 4k bytes of ROM to store the voice program, and 1k bytes of RAM to store the positions of the chess pieces.

The voice program allows the latest in the Chess Challenger line to be used by the blind. Each move and capture is audibly read out, and the



board positions can be audibly listed on demand. At the conclusion of the game, the computer displays the number of moves played.

The Voice Chess Challenger will

be released in Australia on July 18 next, and will be available from Futuretronics Australia Pty Ltd, 79-81 Levenswell Road, Moorabbin 3189. Retail price will be \$495.00.

NS announces record profit

National Semiconductor Corporation has announced a record third quarter for the 12 weeks of fiscal 1979, ended March 4th, 1979. Third quarter revenues totalled \$165.3 million, up 49% over the same quarter of the prior year. Net earnings of \$7.8 million or 59 cents per share were 50% ahead of the third quarter of Fiscal 1978.

For the 40-week fiscal year to date, revenues were \$518.3 million and earnings were \$24.6 million or \$1.86 per share. For the same period of last year, revenues were \$360.8 million and earnings totalled \$16.2 million or \$1.24 per share.

Switching transistors near 1000V barrier

Multiepitaxial Mesa technology, developed by SGS-Ates (Italy), has given rise to a new family of high voltage, high power NPN transistors. These are: BUW 34, 35 & 36 and BUW 44, 45 & 46 with VCBO (min) in the range of 500 to 900V and switching times of 0.2 μ s typical. Other characteristics include VCEO(min) = 400-450V and a saturation voltage of 1.5V.

The new transistors should find ready application in switched mode power supplies.

New aid for the disabled

This prototype glove could overcome the almost insurmountable difficulties the inexperienced have in communicating with the deaf and mute.

Simple enough for a child to use, it comprises a left hand glove with the 26 letters of the Roman alphabet, numerals 0-9 and symbols such as question marks and pound signs printed on fingers, thumb and palm. The person would simply spell out words on the gloved hand.

The glove is the brainchild of Edinburgh architect Stuart Matthew, who has worked for many years with the disabled. He believes that it is the



answer to the limitations that sign language and the standard deaf and dumb alphabet imposes on them.

NASA fuel research contract to UK

A British research team at Sheffield University has won a \$136,000 grant from the US National Aeronautics and Space Administration (NASA) to study fuel combustion in high-altitude supersonic aircraft.

The 14-man team, headed by Dr Norman Chigier, will form part of a NASA research program into the effect supersonic planes have on the environment. Although the US has no civil supersonic aircraft, it does operate many military jets capable of flying at up to three

times the speed of sound.

Dr Chigier's team has developed a technique which allows the size and velocity of individual droplets in liquid spray flames to be measured. This will enable the scientists to study the vaporisation of fuel droplets in the pre-mixing chambers of gas engine combustors.

The team has also developed special computer facilities to process the information, and work is now under way on a new high-temperature wind tunnel.

A professional iron with adjustable temperature – wattage and tip size...

Automatic Wattage Selection

Let the actual wattage required for the job be decided by the iron's simple mechanical sensing and control system.

Automatic Temperature Control


Dial any intermediate temperature 200–400°C without changing the tip; holds $\pm 2\%$ of any selected temperature.

You Decide Tip Size

Without the need to buy up to three irons to cover tip sizes normally used, you can screw on any tip shape and weight combination from 0.8mm to 6.4mm.

Cooler Finger Grip

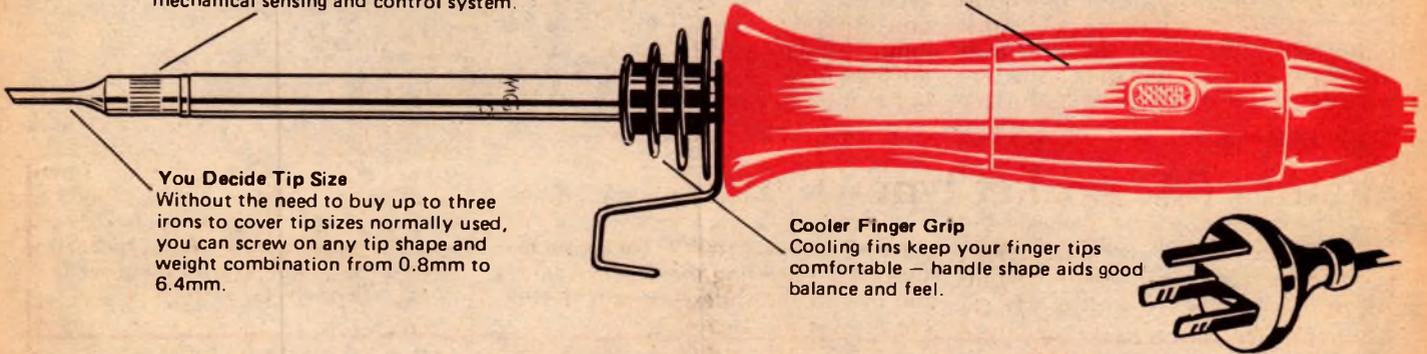Cooling fins keep your finger tips comfortable – handle shape aids good balance and feel.



● 240V Mains Operated

Have you experienced the frustration of starting to use your 15 watt iron only to realize the tip is going cold before the solder flows – alternatives?

(a) Wait 5–10 minutes to heat up your 30 watt (even though the tip on it is really too big). (b) Be a supreme optimist and hope your 15 watt will eventually heat up the joint before you cook the component and lift the track. (c) Switch on your SCOPE TC60 and while waiting the 45 seconds to heat – screw on the tip size you really want.

The SCOPE TC60 will decide the wattage required for each joint.

SOLDERING—DESOLDERING STATION



SOLDER REMOVER



ANTI SIEVE CONDUCTIVE PASTE



SAFETY STAND AND SPONGE



I.C. DESOLDERER

Long life tips for Scope TC60 iron.

DOUBLE FLAT						SINGLE FLAT					
											
0.8	1.6	2.4	3.2	4.8	6.4	2.6	1.6	2.4	3.2	4.8	6.44
mm	mm	mm	mm	mm	mm	mm	mm	mm	mm	mm	mm

Iron plated screw-on pre tinned. *This tip is fitted as standard.

SCOPE TC60

The iron you completely adjust to your job.

Some other SCOPE TC60 features –

- **Component Protection** is aided by earthed tip and barrel. Critical components and operator can then be earthed to common point.
- **Simplicity** of temperature control system suggests less maintenance. An expanding metal probe detects temperature variations inside each tip and operates a mini micro switch in the handle.
- **Temperature Key** is inserted into handle. 40°C variations per quarter turn. Key is removable to discourage unwanted alteration to temperature setting.
- **Neon** indicates when power is being applied to elements – monitors control system.

50V, 24V Versions are available with 50W element.

FOR YOUR NEAREST STOCKIST RING:

MELBOURNE VIC.
(03) 338 1566
SYDNEY N.S.W.
(02) 818 1166
ADELAIDE S.A.
(08) 212 3111

BRISBANE QLD.
(07) 221 1933
TOWNSVILLE QLD.
(077) 71 3448
ROCKHAMPTON QLD.
(079) 27 3370

HOBART TAS.
(002) 34 2811
LAUNCESTON TAS.
(003) 31 5545
PERTH W.A.
(09) 381 4155

AUCKLAND N.Z.
54 6029
WELLINGTON N.Z.
85 9578

NEWS HIGHLIGHTS

No danger from video terminals says Aust. Radiation Laboratory

Recently, there has been some conjecture over the possible emission of harmful radiation from Video Display Units (VDU) which are coming into wide use in Australian commerce and industry.

In Australia, the National Health and Medical Research Council and the Standards Association of Australia recommend that exposure rates to ionising radiation produced by equipment shall not exceed 0.5mR (millirotegen) per hour averaged over an area of 10cm² at a distance of 5cm from any point on the external surface

under all conditions.

Recently, the Australian Radiation Laboratory, together with some State Departments of Health, surveyed over 50 different types of VDU on the Australian market and evaluated them against the above requirement.

No single case has yet been encountered of a VDU which produced detectable amounts of X radiation, even though the lower limit of detection was as low as 0.01 to 0.05mR per hour. The laboratory concluded that, in the light of these results, the VDU does not constitute a public health risk.



Checkbook calculator

Available from National Semiconductor, the Datachecker checkbook calculator features three "permanent" memories, a calculator, and an 8-digit liquid crystal display. It allows users to maintain and update a checkbook balance, for example, and balances for any two selected charge accounts.

The calculator functions independently of the memory system. Two silver oxide batteries power the unit, and maintain the data in the memories even when the calculator is switched off.

World's first pocket typewriter

The world's first pocket typewriter has been invented by an American living in London. Mr Cy Endfield, who directed the 1964 film "Zulu", has been working on the machine for five years. He calls it the Microwriter.

Regarded as a potential replacement for the typewriter, the Microwriter has just 7 keys — 5 basic keys for the 5 fingers of the right hand, one key of control functions, and a capital shift key. Yet the machine can produce the Roman alphabet, as well as number and punctuation marks, and has full correction and editing capabilities.

The text is keyed in by pressing combinations of one or more buttons at a time, according to a code which has to be learnt. This code is said to be easy to learn, as Endfield has deliberately chosen combinations that are easy to

remember. The letter "I" for example is formed by pressing the buttons under the thumb and index finger to resemble the vertical stroke.

Indeed, the inventor claims that, after three days training, the Microwriter is as fast as a normal typewriter!

As the text is keyed in, it is displayed — 12 characters at a time — on a 16-segment LED display. The text is stored in an 8K CMOS RAM (around 8 pages of typescript) and is controlled by an RCA Cosmac microprocessor. This information can be transferred to a regular audio cassette tape for additional storage while the writer continues his manuscript.

The machine itself does not produce words on paper. Instead, the unit is plugged into a high-speed printer which, on command from the Microwriter's keyboard, types the text at over 500 words per minute.

Vicom backs WIA for WARC '79



Vicom International Pty Ltd has donated \$1000 to the WIA as a contribution to maintaining a WIA presence at the coming World Administrative Radio Conference. Photograph at left shows Russell Kelly VK3NT (Vicom Commercial Director) signing a cheque for presentation to Dr David Wardlaw, the WIA Federal President. Peter Williams VK3IZ (Vicom Technical Director) looks on.

Britain plans oil-from-coal plants

Britain is planning to build pilot plants to demonstrate two new processes for extracting petrol and chemical feedstocks from coal.

Under an agreement signed in London, the UK Government will contribute £800,000 (\$1,448,000) and the National Coal Board £400,000 (\$724,000) towards the cost of carrying out engineering design and feasibility studies. These will lead to a decision in 15 months' time on whether to go ahead with building the two demonstration plants.

The two oil-from-coal plants have been proposed by the National Coal Board and would each handle 25 tonnes a day. One plant would produce road transport and aviation fuels such as petrol, diesel fuel and kerosene by dissolving coal in a liquid solvent. The solution would then be processed through a hydrocracker in a similar way to natural crude oil.

In the second plant, it is proposed to use a high-pressure hot gas to produce a solution which is turned into such products as benzene and chemical feedstocks used in manufacturing plastics, rubber, artificial fibres and paint.

Chrysler success in economy run

Many readers will remember that in the March 1979 issue we ran a story on Chrysler's "Electronic Lean Burn" (ELB) system. ELB is a form of electronic ignition that uses a computer to fire the spark in the combustion chamber at precisely the right moment.

The success of the system was recently demonstrated when a 4-litre Valiant equipped with ELB won the Award of Merit for achieving 30.23mpg in the Total Oil Economy Run. Second placing went to the V8 Holden Commodore with 23mpg, and third to the ELB Chrysler Regal Automatic with 25.34mpg.

The awards are based on an efficiency formula which takes account of weight, engine size, tyres, gear ratios and other factors.

The Valiant with the new fuel-saving ELB system achieved about 7mpg better than a non-ELB Valiant run in last year's event, an improvement of 30 per cent.

Consumer electronics show diversifies

Organisers of the Consumer Electronics Show have announced details of a substantially diversified show in 1979. The show will be staged at the Sydney Showgrounds from Wednesday, July 18 to Sunday, July 22.

Although previous shows have drawn wide support from the hi-fi industry, organisers this year are looking to a greater range of products to fully justify the "consumer electronics" title.

Amongst the projected list of displays are: digital watches and clocks, computer games, personal computing

equipment, dictating machines, lighting equipment, records, amusement machines, antennas, PA systems, security systems, electronic calculators, microwave ovens, batteries, photo systems, professional sound recording equipment and radios.

For further information contact Riddell Exhibition Promotions Pty Ltd, 166 Albert Rd, South Melbourne 3205.

NBS signs accord with Soviet Academy

The US Department of Commerce's National Bureau of Standards (NBS) has signed a memorandum of cooperation with the Soviet Academy of Sciences.

The accord falls within the framework of the US-USSR Agreement on Cooperation in the Fields of Science and Technology, established in 1972. This marks the first time, however, that NBS has had its own cooperative arrangement with Soviet scientists.

The agreement provides for cooperation in the fields of thermal physics, thermodynamics, materials science, spectroscopy, chemistry, chemical kinetics, and cryogenic science. It also provides that "other fields may be additionally included by mutual agreement."

Computer-aided design at Hendon

A new computer-aided design (CAD) system has been installed in the Integrated Circuit Facility at Philips Hendon Works in South Australia. The system, which is directly compatible with systems at Philips centres in Europe and elsewhere, give Australia immediate access to overseas microelectronics technology.

Viewdata goes public

The world's first public viewdata service is now in operation following the launch last March of the British Post Office's Prestel service. The service is initially only open to residents in London, but will later be extended to Birmingham, Manchester and Edinburgh, with full coverage of the entire country to follow.

Invented by the British Post Office, Prestel uses a combination of telephone and television to give viewers access to a central computer information bank. The range of information available is considerable. Immediately available at the touch of a button are: news, sports fixtures and results, share prices, weather reports, traffic information, house prices, restaurants, a car buyers' guide, entertainment guides, holiday information and train, shipping and airline timetables.

For relaxation, Prestel offers a variety of games and puzzles.

The introduction of Prestel established for Britain a substantial lead in the mass marketing of electronic information. The British Post Office has already sold the technology to the United States, West Germany, the Netherlands and Hong Kong, and is now engaged in sales discussions with a number of other countries.

Philips says that the Hendon CAD installation will be used for the custom design of ICs and for circuit analysis. In addition, computation and analysis of test results from diffusion and production runs will be handled, and problem areas in hybrid design catered for.

The equipment installed by Philips includes a Systems Engineering Laboratories 32/55, a Tektronics 4014 graphics display unit, and a Calcomp 1039 plotter.



control, flap control, air speed indicator, altimeter, vertical speed indicator, artificial horizon and glide slope indicator.

Low-cost flight simulator for clubs

This low-cost prototype aircraft landing simulator has been developed by the National Physical Laboratory in Britain. It could bring a realistic simulator for training student pilots in the critical landing phase of a flight well within the reach of small flying clubs.

Called MALTA (microprocessor aircraft landing training aid) it is based on a microprocessor and comprises a graphic terminal and a control console. The display shows the parallelogram shape of an aircraft landing area as seen during the approach and shows how it alters as an imaginary craft descends. Both angle

of descent and the size of the runway can be varied. For those who find the approach a bit too easy, cloud cover and strong wind speeds can be randomly generated.

The graphics terminal also indicates the horizon and has a readout showing the air speed, the vertical rate of climb, and descent and altitude. This expensive terminal will be replaced by a TV monitor in the commercial version of MALTA, to reduce its cost.


The control console is fitted as for a standard light aircraft, with instruments that include a stick or yoke control column, throttle con-

The Complete Colour Package in Swiss made miniature LED indicator lamps

*Yes! Red, Yellow and Green
and in 2 body styles*

From SLOAN AG, Switzerland, these quality packed lamps are the ultimate in miniature perfection... nickel plated brass body, mirror finish reflectors and incorporating high surge voltage resistant Gallium Phosphide LEDs, all combined with C&K product compatibility. Yes, these long life, competitively priced indicators are designed to blend with C&K panel dress nuts providing complete instrument

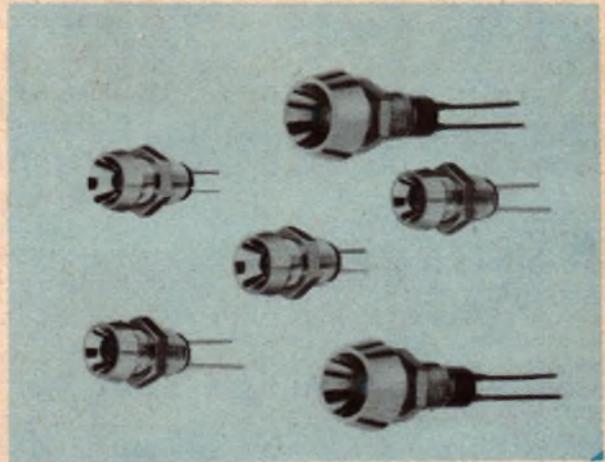panel uniformity and state-of-the-art design elegance. Employing the same size mounting holes as C&K subminiature toggle switches for both sizes, labour and tooling costs are minimised when coupled with C&K switches. The result... superb panel presentation from Swiss craftsmanship and C&K reputation... consider the advantages.



C&K Electronics (Aust.) Pty Limited


Office 2/6 McFarlane Street Merrylands NSW 2160
PO Box 101 Merrylands 2160 Telephone 682 3144 Telex AA23404
Agents Melb. 598 2333/Adel. 269 2544/Bris. 36 1277/Perth 458 7111

Obligation-free and comprehensive data is yours for the asking.

Obligation free and comprehensive data is yours for the asking

MAIL ORDERING FROM US MAKES CENTS FOR YOU! PRICE INCLUDING SALES TAX SHOWN IN BRACKETS

SCHOOL AND COLLEGE SPECIALS

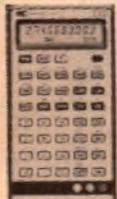

NATIONAL SEMI-CONDUCTOR NS108 LCD, 50 functions, 850 hours battery. In Billfold style wallet, ideal keyboard layout.
\$36 (\$41)

CANON F41 \$16.90 (\$18.99)
CASIO FX-120 44 functions \$32 (\$36)

TEXAS Ti25 LCD 1000 hours battery life \$27 (\$30)
TEXAS Ti55 \$52 (\$58)
60 functions, 10 memories, Programmable, 32 steps

HEWLETT PACKARD

HP's ONLY — POST FREE!
(New low prices) an extra measure of quality



HP31-E \$60 (\$67)
All basic funcs incl P-R, metric conversions, 4 data registers
HP32-E \$80 (\$89)
Advanced scientific/stats, linear regression, conversions, 15 data registers
HP33-E \$100 (\$112)
Advanced scientific/stats, programmable 49 lines, 8 data registers
HP 29C \$162 (\$181)
Similar 33-E, continuous storage of 98 lines of program and 16 of 32 data registers
HP 19C \$210 (\$234)
Same as 19C plus built-in thermal printer
HP38-E \$120 (\$134)
Advanced financial, programmable 8 to 99 lines, 7 to 20 data registers, built-in calendar
HP 87 \$450 (\$501)
Top model programmable 224 lines, 26 data registers, magnetic cards
HP 97 \$760 (\$835)
Portable desk model of 87 with built-in printer, vast selection of programs available

We can equip your business for dollars less.

Desk Calculators
Mini Computers
Answering and Dictating Machines,
Cash Registers

TEXAS PROGRAMMABLE SYSTEMS

PC100 Alpha-Numeric Printer \$278 \$210 (\$234)


For Ti59 and 58 — Lists, Traces, Prints Words (64 characters), Plots Graphs, etc

MODULES \$95 \$32 ea. plug into Ti59 or 58. Pre-programmed with approx 5000 steps.

- Leisure Time
- Marine Navigation (\$28 ea.)
- Aviation
- Real Estate and Investment
- Statistics
- Surveying and new!
- Business Decisions
- Securities Analysis

NEW MODULES

- Maths/Utility
- Electrical Engineering

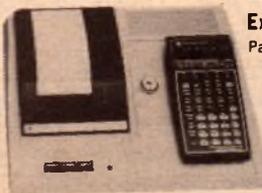

Ti59 + PC 100E

Ti59 \$328 (\$245 (\$274))

Programmable to 960 steps or 100 memories, also master module with 5000 steps, magnetic cards, 3 manuals, program pad, charger carrying cases, etc

Extra Magnetic Cards

Pack of 40 and case \$15

Specialty Pakettes \$10 ea

- Programs for mag. cards —
- Electronic Eng
 - Civil Engineering
 - Statistics
 - Programming Aids (Decoders and disassemblers)
 - Securities
 - Oil/gas energy
 - Black body
 - Printer utility

ALSO

- Ti58 \$141 \$108 (\$120) Programmable to 480 steps or 60 memories, otherwise same as Ti59 except for magnetic cards
- MBA \$82 \$75 (\$83)

Send SAE for our free complete price list

any of these models are advertised in this magazine at a lower price, tell us and we will supply them at a better price.

Pack and Post — All LCD models \$1.50 anywhere in Australia. Otherwise \$2.00 for NSW, elsewhere \$3.00 per order (Extra \$1.50 for registered) Sales Tax Forms must be duly signed and stamped (Forms available).

WE WILL NEGOTIATE PRICE ON QUANTITY ORDERS


Copy and complete Please debit my Bankcard

No Expiry Date

Signature

ELECTRONIC CALCULATOR DISCOUNTS

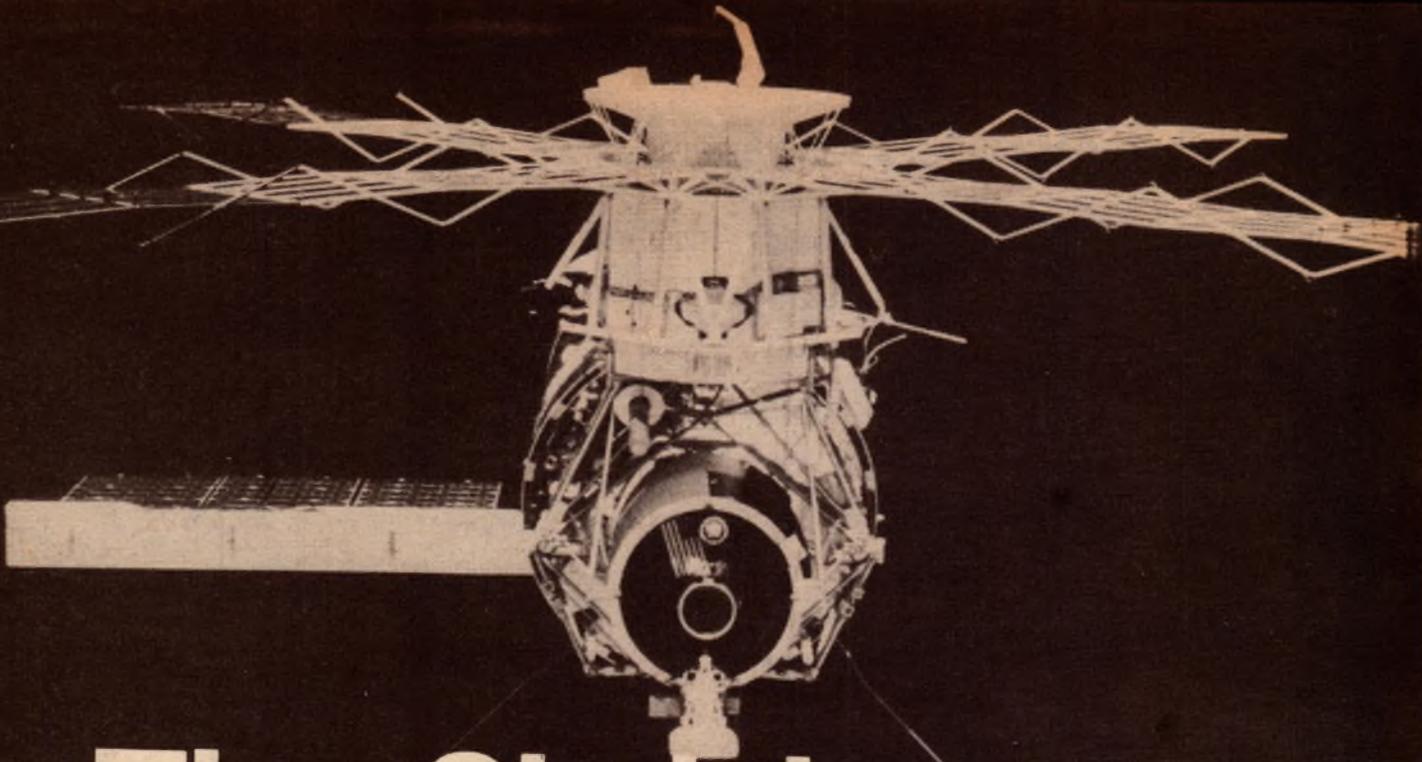Phone (02) 624 8849 (8am till 3pm) P.O. Box 106, Baulkham Hills, N.S.W. 2153



The Skylab story: a rescue effort that failed

Glinting in the sunlight, Skylab looms lopsided against the blackness of space. The solar wing at left lost its twin during launch. This head-on shot of the space station was taken in 1974 by the last

Skylab crew before they returned to Earth. Four years later, Skylab's remaining solar arrays were still able to generate the power needed to stop its fatal fall.

by **EDWARD EDELSON**

When I interviewed NASA's Bill Peters at the Johnson Space Center on July 5 last year, we both thought that the long fight to save Skylab had been won.

We sat in a small office in Houston, just off the empty, echoing room that had housed Mission Control for the Apollo Moon flights. Step by step, Peters led me through the complex story of how he and a few other NASA specialists had awakened a spacecraft that had been sleeping for four years in the hostile emptiness of outer space.

They had scrounged equipment, made up rules to cover situations not found in any book, used a few scattered clues to diagnose what was happening more than 320km above the Earth, and invented techniques to handle unique

problems. And they apparently had slowed Skylab's spiraling descent to Earth, putting the 85-tonne craft in an attitude that would reduce atmospheric drag and keep it aloft until the Space Shuttle arrives next year.

You couldn't exactly say they had accomplished the impossible. But you could say that they had done what no one had ever even tried to do before, and had done a few things that everyone said couldn't be done.

So while Peters wasn't relishing another one of the 18-hour work days that had become routine during the Skylab rescue effort, he had good reason to feel satisfied. On that steamy Houston morning, it seemed that only a few finishing touches remained before the effort could be marked down as a success.

Neither of us could know that the Skylab story was only just beginning. Before that week was over, almost all the gains that had been made so

painstakingly since the rescue effort started in March 1978 were to vanish. Soon Skylab would go completely out of control again. Only some endless days of disciplined work would bring it back into line. Even as I write this, the ultimate end of the Skylab story is in doubt.

But if the July rescue project had failed, the end would have been certain: a fiery death as Skylab plunges back to Earth some time in 1979, scattering metal over an area up to 4,800km long and 160km wide. A few of those chunks could weigh more than two tonnes. If they should hit a city — which NASA says is extremely improbable — they could do serious damage.

It was the prospect of such a death for Skylab that sent Bill Peters and a few other NASA experts to Bermuda last March. Why Bermuda? If you understand that, you can better appreciate some of the factors that have made the Skylab story so peculiar.

NASA's Skylab space station is about to plunge back to Earth, scattering chunks of metal weighing up to two tonnes over a wide area. This is the story of how a handful of NASA men mounted an incredible battle to save the doomed space station, a battle that will shortly end in failure.

Improvised spacelab

To start with, Skylab was essentially a salvage operation — an attempt to keep the space program going in the face of funding cutbacks. The spacecraft is really an upper stage of a Saturn 5 rocket, one of the launch vehicles that was left over when NASA scrubbed some planned Moon missions because Congress slashed the budget. To make that upper stage into a living space that could support three-member crews in space for months on end NASA engineers used whatever equipment happened to be on hand. For example, a lot of Skylab's hardware — including its radio equipment — was built for use in the early '60s Gemini missions.

That was why Bill Peters and crew went to Bermuda. When Gemini was designed, NASA was using ultra-high-frequency equipment for space communications. Later, the agency switched to microwave frequencies. Of NASA's 12 tracking stations only Bermuda and Madrid still had UHF capabilities. (Later, compatible equipment was installed at the Goldstone, Calif., station.)

That Skylab needed saving was in itself peculiar. Though the craft was plagued with troubles immediately after its launch it had successfully housed three crews. When the last astronauts left the orbiting lab in February 1974, it was left in an orbit designed to keep it safely aloft until at least the early 1980s.

Enter, of all things, sunspots. Skylab — and every other spacecraft in Earth orbit — will come down sooner or later because of drag caused by the few wisps of atmosphere in what we usually think of as outer space. Sunspot activity has a direct effect on the thickness of the atmosphere out there. More sunspots mean that the Sun is spewing forth more of the matter and energy called the solar wind. That energy heats the atmosphere. As it is heated, it expands, and more gas molecules and ions from lower altitudes drift up. Density increases, and so does drag.

NASA's belief that Skylab was in a safe orbit was based on a relatively low estimate of solar activity in the 11-year sunspot cycle that began in 1976. Other experts predicted a higher level of sunspot activity and a shorter life for Skylab.



By late 1977, the North American Defense Command's (NORAD) satellite tracking system was telling NASA that Skylab probably would come down to Earth by the middle of 1979. It was bad news at a bad time because the space agency was starting to think of lots of things that Skylab could do when the Space Shuttle starts operating. The Shuttle, a reusable launch vehicle will be able to put boxcar-size payloads into orbit. Unfortunately, development of the Shuttle costs a lot of money, and Congress is still in a penny-pinching mood about space. So Skylab, a fully equipped house already in orbit, began to look more attractive to NASA.

Plans developed quickly. NORAD had determined that Skylab was coming down faster than scheduled because it was in a highdrag attitude in orbit (see diagram). So a group of NASA experts would re-establish contact with the spacecraft, start its dormant control systems working again, and put it in the ideal minimum-drag attitude that would keep it up for a year or so until the Shuttle was ready. Meanwhile NASA contractors would build a \$30-million gadget called the Tele-operator Retrieval System, a strap-on rocket system that the Shuttle would carry up to boost Skylab into a safe orbit.

For the rescue mission, NASA began assembling some of the old Skylab gang. Early in March, eight men — four from the Johnson Space Center, four from the Marshall Space Center — arrived at Cooper's Island, a NASA facility in Bermuda.

"The first thing we did was to establish that we could even communicate with Skylab," said Bill Peters, the head of the team. "There were all kinds of theories as to what would happen to a spacecraft that had been in space for over four years. We had to prove that we could talk to it and it could talk to us."

Communicating with Skylab wasn't something that could be done at leisure. For 13 hours a day, the spacecraft's orbit kept it completely out of range of the Bermuda station. For the other 11 hours, the station could contact Skylab once every 90-minute pass, when the spacecraft flew into the zone of coverage of the Bermuda antennas. On a good pass, when Skylab flew right through the middle of the zone, the station could keep contact for 11 minutes at most. On orbits when Skylab sideswiped the zone, the NASA

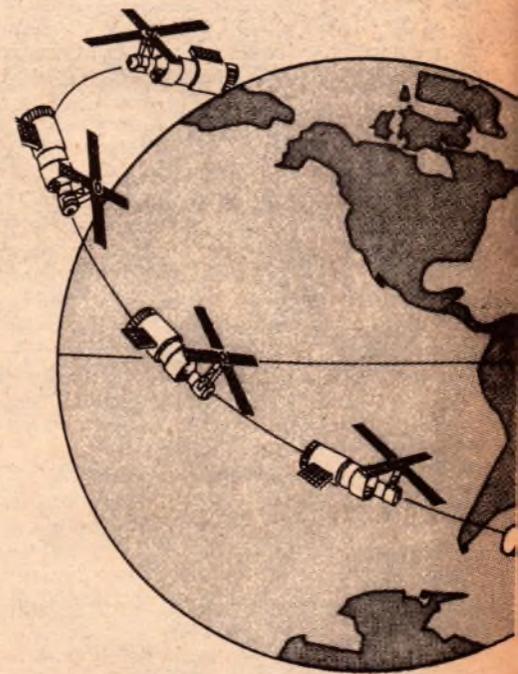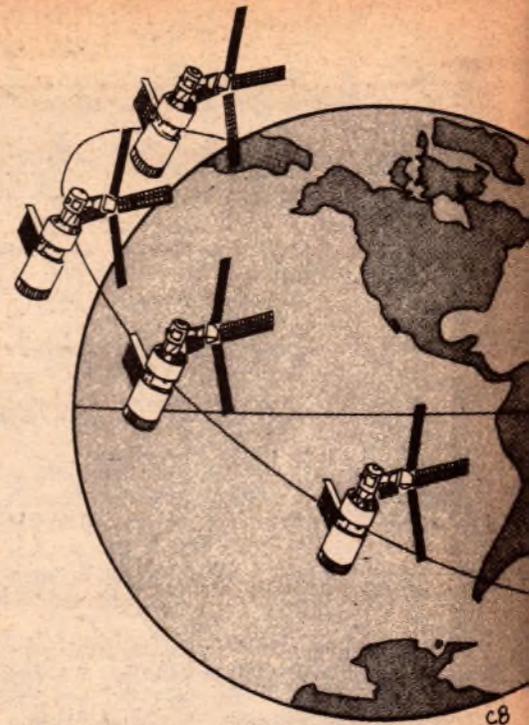

With its nose pointing 90 degrees away from its direction of flight (top), Skylab was flying perpendicular to its orbital plane — presenting its full length broadside to the thin atmosphere dragging it down. To compound the problem, the craft was performing a complex dance in space — both rolling rapidly on its axis and wobbling around in a wide, cone-shaped path. In its current end-on velocity-vector orbit (bottom), Skylab flies with minimum drag, its nose always headed in the direction of flight, and its solar panels always facing the Sun. To maintain this attitude, the craft must slowly rotate on its pitch axis once every orbital pass.

"The basic cause of the trouble: Skylab required constant

team would have to settle for as little as three minutes of communication.

Wake-up call to space

First contact came on the evening of March 6, 1978. It proved to be a microcosm of the Skylab rescue effort: unexpected success followed by a puzzling, mind-stretching problem.

Contact was made through the only two pieces of equipment the astronauts had left operational. They'd turned off everything in the Apollo Telescope Module (ATM), the tower perched atop Skylab's Docking Module or nose. Left on were two digital command systems in the Airlock Module (AM) — the section between the cylindrical craft's nose and the Orbital Workshop where the astronauts stayed. The AM contains the electrical control and distribution gear for the entire spacecraft.

The digital command systems receive messages and put them in proper form to run other instruments in Skylab. These two working instruments were hooked directly to the paddle-like solar array on one side of the spacecraft. That meant they could operate only when the solar cells were pointed at the Sun. (The AM's batteries were completely discharged.) "We had a 50-50 chance of the solar array being in the sunlight," said Peters. "We just happened to be in the right attitude."

A signal was sent to turn on the telemetry in the AM so that the NASA team could get information about the status of the various systems on board Skylab. When the first signal was sent, the telemetry went on and Skylab began transmitting data after four years of silence. The pens on the five strip-chart machines at the Bermuda station began recording the jagged lines that represented pressures and temperatures on Skylab.

Then trouble: The Skylab signal began to fluctuate. After two minutes, it stopped. When it came back on a few minutes later, the spacecraft's transmitter sent only the carrier frequency, not the modulation that carried information.

It took a while to figure that out. Finally, the NASA team arrived at an explanation. The transmission had stopped because the spacecraft was rolling much faster than they had thought. The solar cells had rolled out of sunlight, cutting off the electricity. (Later analysis showed that the rate of roll was more than one degree a second.) When the transmission returned, the signal was flawed because one of the spacecraft's three DC-to-DC converters, which provided the level voltage needed by the instruments, had failed.

The failure apparently was caused by the low, irregular voltage that the converter got as the solar cells rolled into

and out of sunlight. To prevent another converter burnout, the team decided to charge four of the eight batteries in the AM. They instructed the spacecraft to use the power generated by the solar cells to charge the batteries — first a trickle charge to condition the nickel-cadmium batteries' electrolytes, then a full charge to bring the batteries up to their 33-amp-hour capacity. The men on the ground waited nearly three days while the batteries were charged, and the outcome was by no means a sure thing.

"There were theories that the solar panels could be severely degraded by having spent that long in space," Bill Peters said. There were also concerns about the condition of the batteries. As it turned out, there was very little degradation on the panels — so little that it could hardly be measured. And the batteries were almost as good as brand new. Explained Peters, "If you take a nickel-cadmium battery and discharge it completely for a long period of time, you apparently build up its capacity to store energy."

With the batteries fully charged, the AM's telemetry again turned on. This time nothing went wrong. With the AM transmitter sending good data on each pass, the NASA team started to bring the ATM, the other section of Skylab, back to life. This module is powered separately by its own X-shape array of solar cells.

The first step was simple: Close a relay between the AM and the ATM. This activated its receiver-decoder — equipment similar to the digital command system in the AM. On command, this equipment turned on the ATM's transmitter, which immediately began sending telemetry down to Bermuda.

There was a tougher challenge: recharging the ATM's 18 batteries. If you went by the book, it was impossible. The ATM's batteries were designed with a special circuit that would take each battery off line as soon as the voltage dropped below 27 volts. So if a small charge began trickling into the battery, the circuit would take it off line almost instantly. Given that circuit, it seemed that the batteries just couldn't be recharged.

The only glimmer of hope came from a malfunction: One of the ATM's batteries was working, even though it wasn't supposed to. Every time the solar cells rolled into sunlight, the battery put out power. So the NASA team began figuring out how they could do on purpose what one battery had done by accident.

Tricky trouble-shooting

They came up with an ingenious method based on the difference between "instantly" and "almost instantly." It seemed that the circuit took

10 milliseconds to shut down a battery. Someone figured out that by giving the battery many thousands of 10-millisecond pulses, they could build the voltage up to the magic 27-volt level.

It was a tedious task, but by this time the eight NASA men on Bermuda knew that it had to be done. When they had gone down there, they had thought that Skylab could be saved if they simply started it tumbling. The spacecraft was flying more or less broadside (see diagram), so that its drag was at a maximum. Tumbling the spacecraft should reduce the drag by half. But it turned out that a 50 percent reduction wasn't good enough. Skylab was coming down faster than had been thought. It would have to put into a minimum-drag orientation and held there, and that couldn't be done unless the ATM batteries were recharged.

To do this, the NASA team had to return to home base. Before leaving Bermuda, they verified that the Skylab computer was operating. Then, for a month and more, the team hammered out and tested the procedures they would use to bring the spacecraft under complete control.


Herman Thomason, leader of the Marshall Space Center contingent did innumerable dry runs on simulation equipment there. In Houston, Bill Peters and his crew began building the control center that would carry out the actual procedures.

They used the bare room that had once housed the equipment that received data from instruments on the Moon. The room was available because money for monitoring the instruments had run out. The crew's equipment — a computer and some terminals, and a few cathode-ray tubes for displaying data — came out of storage or was switched from other assignments.

The technique used to give Skylab orders was equally improvised. The command sequence was anything but automated. By telephone, someone at Houston would order an operator at one of the three UHF tracking sites to load a three-digit command number in a Spacecraft Command Encoder. The operator would acknowledge the order over the telephone, then send the command to the digital command systems, which would in turn send it to the appropriate system on the spacecraft.

The Houston command center began operations on April 23, 1978. For more than a month, it did nothing but charge Skylab's batteries. It was a tedious operation. Every time Skylab came into radio range of one of the tracking stations, instructions would be sent at the maximum possible rate — two a second — to the two ATM receiver-decoders. Each instruction would put a

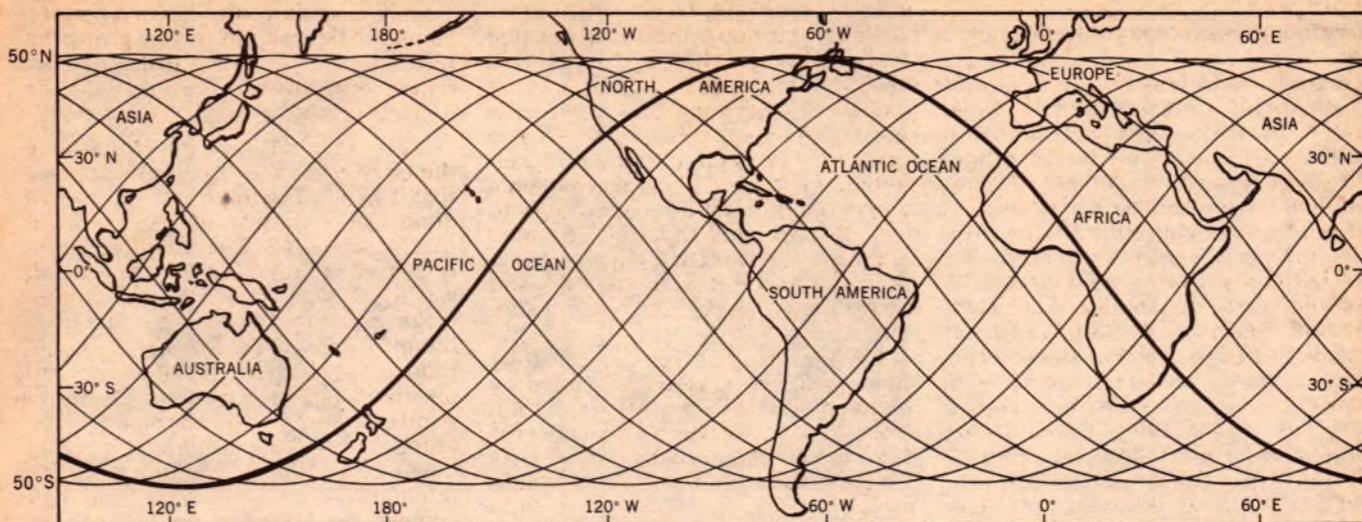attention. But, at times, it was out of contact for 20 hours”



Skylab's angled flight path ranges 50 degrees above and below the equator. If the Earth didn't spin, Skylab would trace out the same path on every pass. Instead, the craft traces out a series of different

passes, each orbit taking 90 minutes. A few possible paths are shown. It is almost impossible to predict where Skylab would crash if it should fall.

10-millisecond trickle of electricity from the solar panels into one battery. Over many days and with many thousands of instructions, battery voltage would slowly build toward the 27-volt level. When it reached that point, it would shoot up suddenly to full charge.

Four of the ATM battery systems were defective. By the end of May, the other 14 were fully charged, as were the eight AM batteries. That was just a prelude for the trickiest and riskiest part of the entire mission — the effort to put Skylab into a stable, low-drag attitude.

Complex command sequence

In theory it was simple. Skylab was flying belly forward, rolling once every five minutes and 40 seconds. The basic job was to move the spacecraft so that its Sun sensor, located in the middle of the X-shape solar-panel array, would lock onto the sun. To do that, Houston had to turn on three systems.

First, Houston had to start the two 400kg control moment gyros rotating. These regulate the craft's pitch, yaw, and roll. A third huge gyro had gone out of control during the manned mission, making the task of adjusting the spacecraft's attitude considerably more complicated.

Next, the team had to start the small rate gyros that sense the spacecraft's position. And finally, they had to turn on the computer that commands the attitude-control system of small, nitrogen-gas rocket thrusters.

But there were complications. While they were recharging the batteries, the NASA team found that Skylab was moving in an odd way. Not only was it rolling, but it also had a complicated wobble. Its wide end was moving in a bigger cone than the narrow end. This

erratic wiggle would make locking on the Sun sensor even more difficult. In addition, all the equipment couldn't be turned on at once. Since the solar panels were rolling in and out of sunlight, full operation for more than a day would run down the batteries completely. The NASA team had to work with three constraints: the eight-hour period every day when Skylab was out of reach of any station; limited periods during the other 16 hours when the spacecraft could be contacted from the ground; and the even more limited time during those passes when the solar cells were in sunlight.

They worked out a sequence. Just before an eight-hour gap, the control gyros would be started. These take 12 hours to spin up to speed. When they were ready, the rate gyros and the computer would be turned on, at a time when the solar sensor was pointing toward the Sun. The sensor would be locked onto the Sun by computer instructions to the thrusters.

On June 8 the control gyros were turned on. On June 9 the rate gyros and the computer were turned on. Within a minute the sensor picked up the Sun and locked onto it. Some corrections were still necessary, because it developed that Skylab was tilted about 10 degrees from the Sun but those were accomplished over the next few hours.

A phantom command

Then came the first sign of real trouble. Before they closed out the day, the Houston team decided to send instructions that would let the backup computer take over in case of emergency. It was strictly routine, except for a Skylab switch selector that had developed a baffling habit of now and then sending two commands after receiving one order. In this case, the switch selector

sent a signal that removed control of one of the gyros. The other gyro continued controlling, and its torque began twisting the spacecraft out of correct attitude. The computer sensed the error and used the nitrogen thrusters to bring Skylab back into line. It was a full orbit before the NASA controllers in Houston were able to correct the problem. By then the spacecraft had used up a lot of precious nitrogen — precious because it's needed to hold Skylab steady for docking with the Teleoperator Retrieval System.

Once that problem was corrected, the next task was to refine Skylab's orbit. Skylab was now in what Bill Peters calls a "solar-inertial attitude," meaning that its solar panels were always pointed at the Sun. In solar inertial, Skylab was still flying broadside about half the time. On June 11 a series of commands was sent that used the control gyros to put Skylab in an "end-on velocity vector," the minimum-drag orbit (see diagram).

It seemed that the mission was almost accomplished. One small chore remained. The Sun's apparent position relative to Skylab's orbit changes gradually through the year, moving first up to a maximum of about 72 degrees above the plane of the orbit and then back down to 72 degrees below the plane. Skylab had to be instructed to roll slowly so that its solar panels would keep facing the Sun. In every orbit, the computer and gyro instructions would have to be updated to correct for the change of about three degrees a day in the Sun's position.

Early in July, the Sun reached its maximum angle — and Skylab could not remain in end-on velocity vector. It was put back into solar-inertial attitude. When I interviewed Bill Peters, he was beginning what he hoped would be the

Saving Skylab . . .

last 18-hour workday of the mission, a day during which Skylab would be put back into end-on velocity vector. It seemed rather minor, the final finishing touch to a gruelling but successful operation that had rewritten the book on space missions. Apparently, Skylab's life had been extended for as long as a year, long enough for the Shuttle to get there. I packed up my notebook and headed back to write the story.

Then, early on Sunday, July 9, the phone woke Marshall's Herman Thomason from a sound sleep. "They told me they had lost contact with the vehicle," he said. "We came in and tried to regain attitude, but it had drifted so far out that we couldn't."

The basic cause of the trouble: Skylab required constant attention. First the NASA team had hoped that one set of instructions would keep Skylab in the proper attitude. Then they hoped that corrections every day or so would be enough. As it turned out, the position-sensing rate gyros do not function properly, so almost constant corrections for drift were needed. That means continual monitoring from the ground.


But the patchy ground coverage then available would not permit constant monitoring. At times, Skylab was out of contact for 20 hours — long enough for the errors to multiply fatally. The worst thing that can happen to Skylab is for its solar panels to drift away from the Sun, so that the spacecraft loses power. That was what happened. The ATM batteries began tripping off line, the computer's power source was cut off, and the spacecraft was once again out of control.

Back to square one

Again began the painstaking, tedious work of bringing the ATM batteries back on line by giving them thousands of 10-millisecond pulses. Again the tricky sequence of bringing the control gyros, the rate gyros, and the computer back on line so that Skylab could be put back into solar-inertial attitude. Again the effort of getting the Sun sensor to lock on the Sun. And all of this was done by exhausted men whose normal office day was 18 hours, with everything else in life — eating, sleeping, or whatever activity — crammed into the other six.

And to made life more interesting, one of the biggest X-ray solar flares ever observed erupted on July 11. The flare did not stop the Skylab rescue effort, but it was another ominous sign of high solar activity and a denser upper atmosphere.

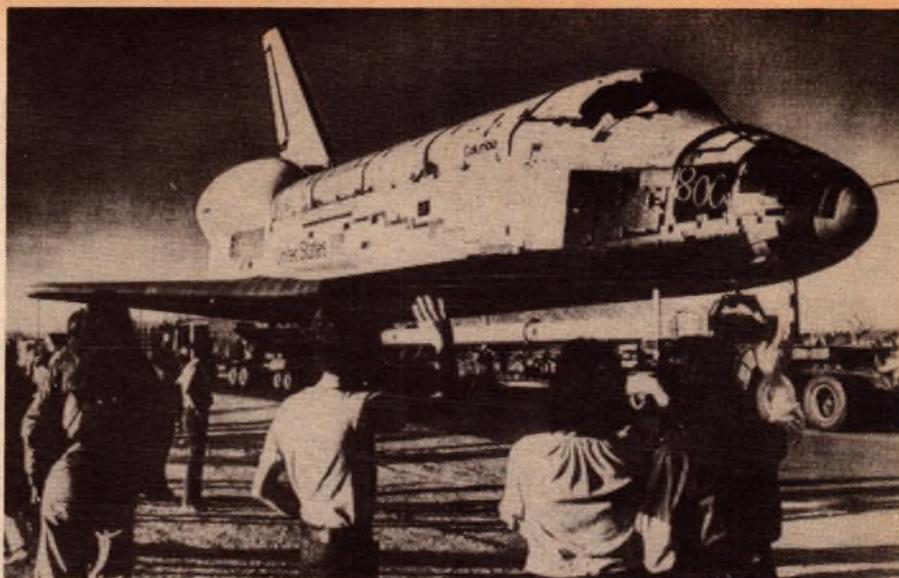On July 19 Skylab was put back into solar-inertial attitude. On July 25 the spacecraft was put back into end-on velocity vector, the minimum-drag attitude. "Right now it looks very good,"



The Space Shuttle will not arrive on time to save Skylab. Here spectators wave to the Shuttle Orbiter "Columbia" as it moves through the streets of Lancaster, California, en route to Edwards Air Force Base, and thence to Cape Kennedy.

"Several future factors will decide Skylab's fate. One is the level of sunspot activity. Another is the Space Shuttle schedule. A third is the ability of Skylab's systems to keep on working properly. None of the three looks particularly good".

Thomason said a week later.

But by this time Christopher Kraft, the head of the Johnson Space Center, had just about written Skylab off. "People are used to NASA accomplishing miracles, but maybe this is one miracle we can't pull off," Kraft said. "I don't think the odds are very good."

Several future factors will decide Skylab's fate. One is the level of sunspot activity. Another is the Space Shuttle schedule. A third is the ability of Skylab's systems to keep on working properly. None of the three looks particularly good.

Sunspot activity continues to be heavy. The Space Shuttle is having trouble with its engines, putting its timetable in doubt. Even if the Shuttle sticks to the timetable, the Skylab rescue mission must occur during the Shuttle's second test flight which is cutting things very fine. And then there is the antique hardware on Skylab to consider.

"If we can just keep our systems working . . ." Thomason said. "Some of that hardware was built for the Gemini program back in 1963, 1964. Those old systems were never designed for this. They've been very cooperative with us so far, but . . ."

Thomason and Peters and the other NASA controllers are still working to save Skylab. Some time last October, a tracking station in Santiago, Chile, joined the Skylab monitoring network, so that the network is now able to keep contact with the spacecraft for 24 hours a day. The NASA team has gone on a round-the-clock schedule from here to the end.

The end could come with the death of Skylab. Or it could come when the Shuttle arrives in time. At this stage of the game, all you can say is that the rescue team has given it one hell of an effort.

Epilogue

As this issue of "Electronics Australia" went to press, things looked bad for Skylab. Since the preceding story was written, Skylab's orbit has deteriorated to the point where NASA now says that the 87-tonne space giant should plunge back to Earth — in pieces — sometime between June 15 and July 2.

The most likely date, according to a recent NASA statement, is June 21.

Most of the space station will burn up from friction as it plunges through the atmosphere. But NASA estimates that 400 to 500 pieces will survive, scattering over a path 6,440km long and 160km wide.

Most pieces will be small, but there are two large chunks, each weighing about two tonnes, that are likely to make it to Earth intact. Experts believe that the chance of anyone being hit is less than the chance of being hit by a meteorite, because 75 percent of Skylab's orbit is over water and most of the rest is over open land.

Reprinted from Popular Science with permission; copyright 1979 Times Mirror Magazines, Inc.



TWO HEADS ARE BETTER THAN ONE

There are good reasons why these two superb Philips models make such a fine contribution to the unique characteristics of headphone listening. Each, in its own way, offers ultimate performance and remarkable value in the realm of Hi-Fi stereo equipment.

That is why two heads are better than one. It gives your customers the choice of two exceptional systems in design technology.



Philips N6325 Electret Headphone (Above)

The electret principle embodies all the advantages of electrostatic sound reproduction, yet manages this without cumbersome weight or expensive power supplies. There is no reduction in performance, but there is a significant fall in cost.

Philips N6330 Electrodynamic Headphone (Below)

Although N6330 (Philips' range leader) is a conventional electrodynamic headphone, there is nothing conventional about the revolutionary design concepts that ranks these phones with any competitor in the world today. And **not** as expensive as you would expect.



Service
Service
Service

For further information
send coupon to:
Philips Central Service Division,
443 Concord Road,
Rhodes, N.S.W. 2138.

PHILIPS

Please send me further information on:

N6325 N6330

Name: _____


Position: _____

Company: _____

Address: _____

Telephone: _____

EA6

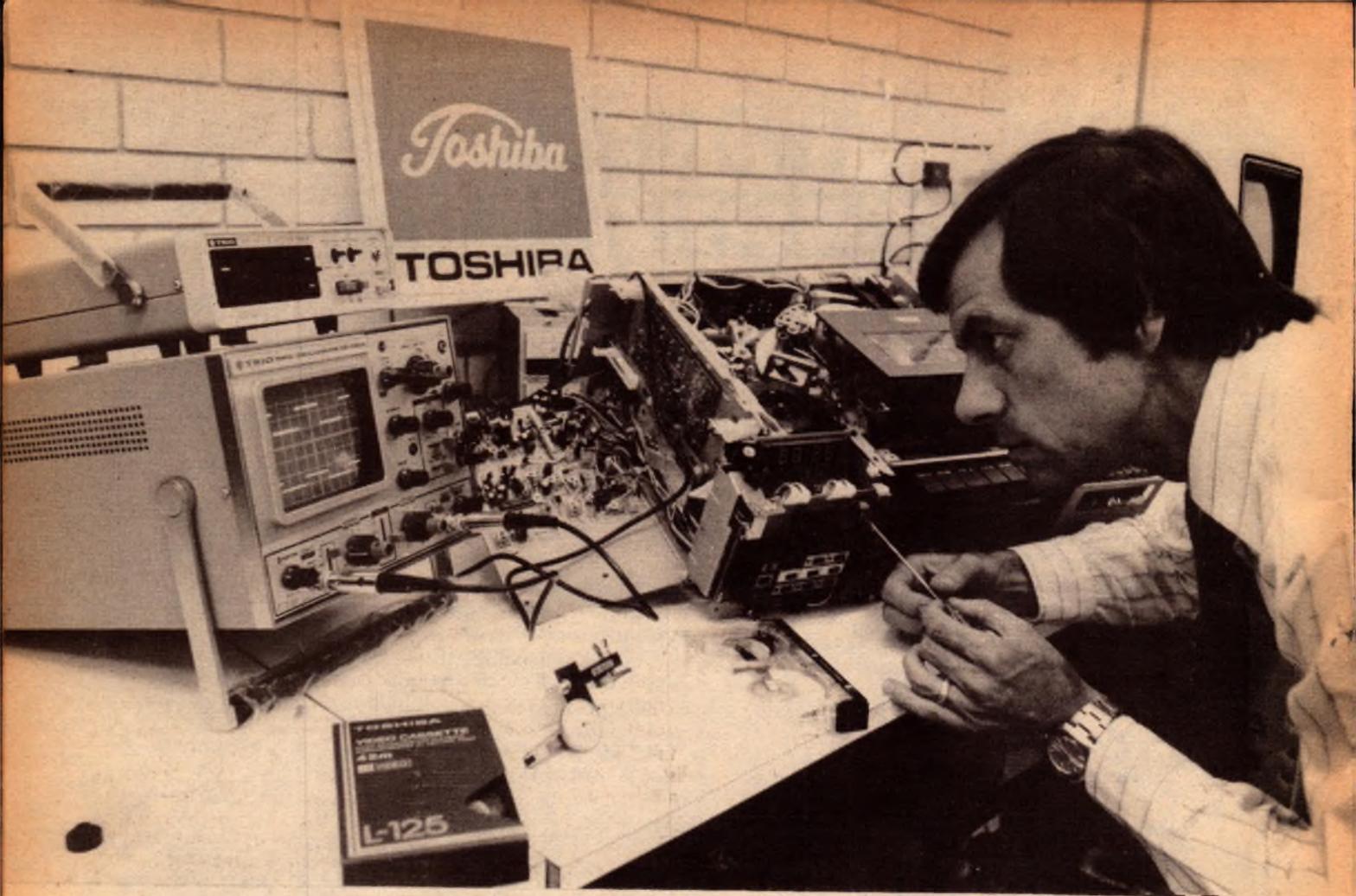

“Resolution of the 4.43MHz sub-carrier was better on the TRIO CS1560A scope...” says Ian West, National Service Manager, Toshiba Australia.

Ian West is responsible for all Toshiba service within Australia. This includes three service divisions and liaison with over 500 service agents. We asked him why he chose the Trio CS1560 scope for service use.

“We found that for TV., audio and VCR servicing, the Trio has a brighter display on H.F. signals. The Resolution of the 4.43 MHz subcarrier is better due to the scopes’ 15MHz bandwidth.

“Also my job involves training other technicians, so we were looking for a scope that’s easy to drive. The 1560 has proved ideal for setting up VCRs. Using its chop facility we can easily compare counted down signals with the original.

“We are using quite a few Trio instruments. They offer excellent value with just the right extra features that we need.”

Check the full Trio range from . . .

PARAMETERS^{PTY} LTD Sydney 439 3288
Melbourne 90 7444

NSW SYDNEY	George Brown & Co	519 5855
	Martin de Launay	29 5834
	Radio Despatch	211 0191
	Dick Smith Stores	439 5311
	Standard Comps	660 6066
	Brian Bambach	24 7246
	D.G.E. Systems	69 1222
GOSFORD	Electronic Comps	95 6811
N'CASTLE	Audiotronics	44 7566
A.C.T. CANBERRA		
QLD. BRISBANE		

CS 1560 15MHz, 10mV, Dual Trace.



- 130mm CRT
- DC 15MHz/10mV
- Automatic sweep (AUTO FREE RUN)
- Display modes (CH1 CH2 DUAL ADD SUB)
- Full sensitivity X-Y operation
- SPECIFICATIONS
- Bandwidth DC to 15MHz (-3dB)
- Deflection 10mV div to 20V div
- Factor
- Input R.C. 1M Ω 22pF
- Risetime 23nsec
- Overshoot Better than 3%
- Sweep time 0.5 μ s/div to 0.5s/div
- Magnifier $\times 5$
- Linearity Better than 3%
- Calibrator 1Vpp 1kHz square wave
- Intensity More than 20Vpp
- modulation
- Phosphor P31
- Power AC 100/120/220/240V, 50/60Hz, 23W
- Dimensions W260 x H190 x D385 (mm)
- Weight 8.4kg



VIC. MELBOURNE	Browntronics	419 3986
	Douglas Radio	211 1698
	J.H. Magrath	663 3731
	Radio Parts	329 7888
	G.B. Telespares	328 4301
	Teleparts	21 7288
S.A. GEELONG	K.D. Fisher & Co.	269 2544
ADELAIDE	Gerard & Goodman	223 2222
	Trio Electrix	51 6718
	Henderson Inst.	381 4477
W.A. PERTH	W.J. Moncreiff	325 5722
	Willis Trading Co	321 7609
TAS. HOBART	Imbros Scientific	28 5997

Charles David Tandy

FROM A PAPER BOY TO A BILLION DOLLARS

1918-1978

Charles David Tandy, founder of the huge Radio Shack and Tandy chain of electronic stores, died recently at the age of 60. Just before his death, he had seen his Company's annual turnover nudge the billion dollar mark — no mean accomplishment for someone who, as a child, had experienced the rigours of the great depression.

by **NEVILLE WILLIAMS**

Charles Tandy's father, David L. Tandy, owned a small leatherwork store in Fort Worth, Texas and reject off-cuts helped supplement his schoolboy son's income from selling papers on the streets. Young Charles would teach his mates how to make leather belts and other knick-knacks — thereby "creating a demand" — and then supply them with the raw material they needed!

Some time later he got a real job — in the basement of a department store selling ladies shoes. In later life he would characteristically remark: "If you could sell ladies shoes, you could sell anything!"

He was sent to college on borrowed money and promptly rewarded his father by failing the course. But the experience taught Charles Tandy that, to succeed, he would have to work. And work he did, for the rest of his life!

In 1940 he graduated from the Texas Christian University, entered the Harvard Business School and, a year later, joined the U.S. Navy, serving as an officer for the remainder of World War II.

While in the Navy, he set a record for selling war bonds and it proved to be an indicator of what was to come: It sharpened his business sense and gave him a feel for large sums of money even if, at the time, it belonged to other people!

After the war, Charles Tandy returned to the family business in Fort Worth and set about to expand and diversify its activities. In the process, in 1963, he made a vital decision: to purchase "Radio Shack", a chain of nine retail stores in the Boston area, with a marker value of about \$2,500,000.

Facing the new challenge, Tandy plotted a unique and deliberate course. Recognised giants of the American radio scene, like RCA and G.E. were

turning away from retailing to concentrate on large scale manufacturing and distribution. Surely that would open the way for a specialist retail chain that could become known nationwide. The larger the chain, the greater would be its buying power and the keener its pricing.

The chain would bulk-buy, import, arrange manufacture, provide service and do whatever else was necessary but the emphasis would remain firmly on retail stores and the customer.

Since then, the 9 original stores have multiplied and spread across America and overseas. At the last count, there was something like 4200 company owned stores handling Tandy brand products, plus nearly 3000 associated retail outlets. Corporation turnover has grown apace, to hit the billion dollar mark in the year ended June '78. For Charles Tandy, it was an ambition that was fulfilled right on target, at age 60.

But while the Tandy empire expanded worldwide, Charles Tandy's personal loyalties remained centred in the Fort Worth area and especially around his old university. It was no accident that the twin towers of the multi-million dollar Tandy Centre, commenced in 1975, served to revitalise the downtown area of Fort Worth, very close to where his father established the original leathework business. When the project is complete, it will have grown into a whole new business centre involving eight city blocks.

In retrospect, there is no doubt that the Tandy dream changed the face of radio marketing in America.

An editorial in the February issue of "CQ" magazine recalls the pre-1960 era, when amateurs were able to browse through any number of small, independent radio shops. The fashion, in those days was to build your own

gear, and the multitude of shops made it easy.

But, in the late 1950's there was a downturn in this activity, with amateurs preferring commercial equipment and the number of parts suppliers diminishing rapidly. It is difficult to separate cause and effect, says "CQ" but the downward spiral was all too obvious.

CQ continues: "Mr Tandy, through Radio Shack, reversed that trend. Mr Tandy got us back to building again. With over 6000 radio stores available to the amateur, it is not surprising to find numerous articles in the amateur journals keying their parts lists to Radio Shack catalog numbers.

"... Mr Tandy was not an amateur. He never worked DX... never climbed a tower nor strung a dipole. But he did bring the smell of solder back to the ham shack."

In Australia, the 180-odd Tandy stores and dealerships are not so directly involved with radio amateurs. They are much more concerned with hifi enthusiasts and the electronic hobbyist. It would certainly be true to say that the attraction and accessibility of Tandy stores has provided the initiative for many hesitant handymen in Australia to have a go, and do it themselves!

One of Charles Tandy's major decisions, prior to his death, was to commit the Corporation to the development and promotion of a microcomputer intended expressly for small businesses and individual enthusiasts. Out of that came the TRS-80, which has already made its mark around the world in this new and burgeoning field.

In fact, it may well prove to be a whole new reach for the Tandy Empire. The TRS-80 is being supplemented by a whole range of peripherals and the Company is well advanced in its program to open no less than 50 specialised Radio Shack computer centres during the current year. Unfortunately, Charles Tandy did not live to see the result of what, at the time, must have been a quite far-sighted vision. ☺



Interference-free data transmission

Optical fibres are rapidly coming into service in telecommunications systems and to distribute television programs. A new development is a system using optical fibres for interference-free telemetry, in which data inputs can be clipped onto the fibre without breaking into it, almost as simply as pegs are put onto a clothes-line.

by **PROFESSOR D.E. DAVIES & DR B. CULSHAW**

Optical fibres are thin strands of glass or silica (quartz) which can guide light over long distances. No thicker than a human hair, they can carry information if the light travelling along them is suitably coded, for instance, by on-off modulation of the light source. The attenuation of an optical fibre has fallen dramatically over the past five years from over 40dB/km (decibels per kilometre) to figures now typically in the region of 1dB/km.

People are mainly interested in optical fibres for public telephone networks. One of these tiny strands can carry thousands of telephone conversations while taking up only a very small

space, so that theoretically the telephone administrations can considerably expand their facilities without having to lay new ducting under the streets. Because of this, optical-fibre technology is now one of the fastest growing fields in electronics.

Optical fibres have several interesting properties when compared with conventional copper cables for transmitting information. A fibre does not radiate the signal it carries, nor is it affected by any local electromagnetic interference. So fibres may be freely used in areas of strong electromagnetic fields that might otherwise interfere.


This makes them useful for aircraft and satellites, too, where a great deal of copper cabling has hitherto been used to shield unwanted signals rather than

to transmit information; here the fibres' light weight is another advantage. Because the fibre is an electrical insulator, it does away with expensive voltage and current transformers normally needed when coupling electrical measuring instruments to high-voltage power lines. Interference problems often caused by current flowing in 'earth loops', that is, closed circuits formed by a series of earthed conductors, are also avoided when fibres are used.

Hazards

An optical signal travelling along a fibre, though electromagnetic, does not cause a spark when exposed to the atmosphere through a chance break in the cable. This means that optical fibres can be used in hazardous areas, for instance, in chemical and petroleum plant, without risk of fire. Such fibres are a cheap means of communicating through areas where so-called 'intrinsically safe' equipment is normally called for, without degrading performance.

The information is usually passed along the fibre by modulating a light source; that is, by impressing intelligence on it. This is done by switching the source on and off in a binary code. The source itself may be a light-emitting diode (LED) or a laser. With the former, the light may be modulated only by changing its intensity. In the latter, we can still change the intensity but, because a laser is an optical equivalent of an ordinary radio transmitter (which means it is a 'coherent' or pure source), we can also put information on to an optical 'carrier' wave by varying its phase. The phase is the position of the wave in relation to its starting point. If we move all the peaks and zeros backwards or forwards along the direction in which the wave is travelling, usually by less than one wavelength, we have shifted the phase of the wave in sympathy with the information. This form of modula-

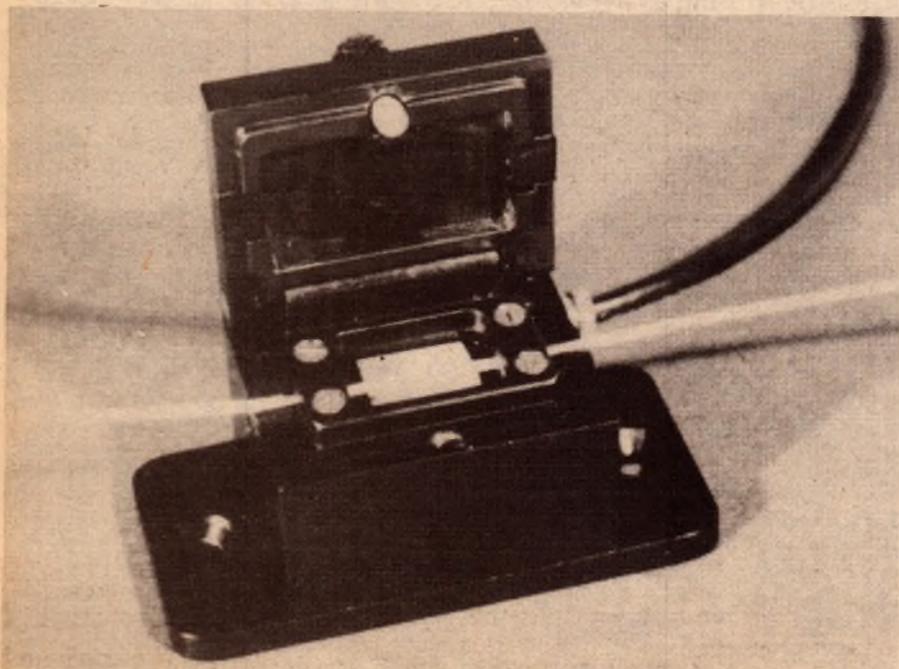

A typical transducer attached to an optical fibre. The ultrasonic pressure wave launched into the fibre imposes a linearly related phase change on the light wave passing along it.

tion can be decoded by a phase detector.

Being able to modulate the light by varying its phase has a number of interesting consequences which we will deal with in more detail later. But it is useful to point out at this stage that the phase of an optical signal passing along a fibre may be changed by altering the length of the fibre or the temperature, or by applying mechanical pressure to the fibre. So, if the fibre carries coherent light from a laser, it is important that the modulation and detection technique for the wanted information is insensitive to such physical or environmental changes. Conversely, we may measure the changes if the detection technique is made sensitive to the phase changes the cause.

Data Highways

These properties of optical fibres have led to a range of applications well beyond the original idea of using them for telephone work. Interest in optical-fibre information distribution systems is growing, and there is a plan for an optical-fibre communications network throughout a new city in Japan.


Communication and telemetry in many industrial and military applications involve the use of one-way or two-way 'data highways', which allow information to be fed in and/or received at a number of points simultaneously. A number of data highway systems now incorporate optical-fibres, but the components used in optical junctions cause considerable loss of signal strength; a loss in the region of 3dB (half the power) or more is typical. Even plugs and sockets can lose up to about 1dB. Moreover, because it is essential to break the optical path when introducing a new data signal, it is often necessary to regenerate a new data signal from the old one at each feed-in point.

The data is usually sent around the highway in the form of a synchronized binary signal, divided into time slots corresponding to the various data sources. The information is coded by the simple on/off technique, so the sources of light may be lasers or LEDs.

Phase Modulation

One exception to this general scheme of things is a unique form of data highway now being developed here. It offers simple, one-way telemetry from many sources to one destination, using a laser and exploiting phase modulation introduced in the fibre path by a pressure change on the fibre.

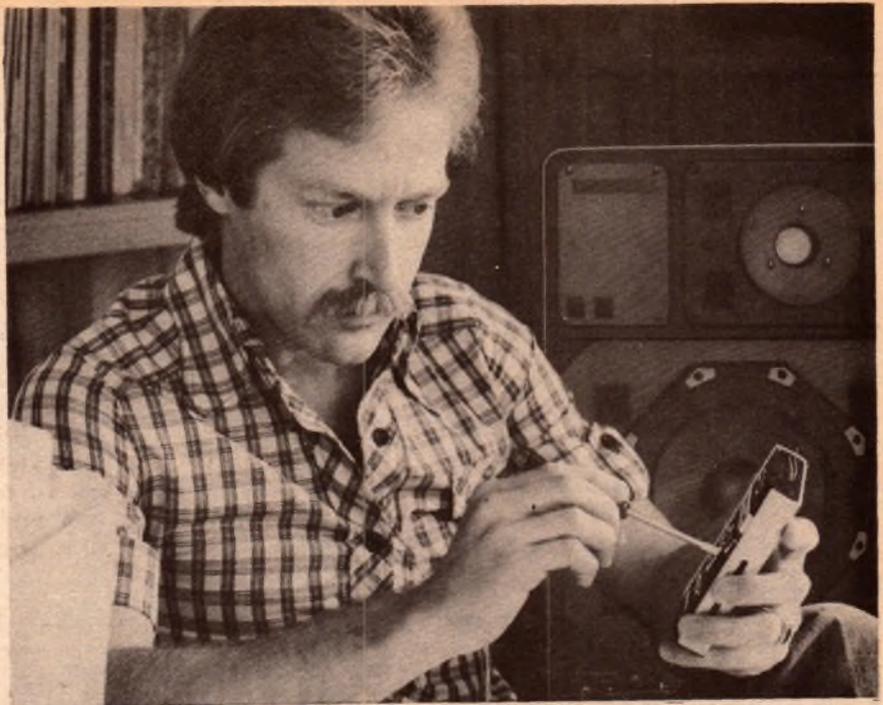The laser used is highly coherent, with low noise. This means that the wave it produces is stable and very pure. At present we are using a gas laser, but developments in solid-state laser technology and improvements in the system will soon enable us to use a solid-state source. The output from the laser is fed into a length of multimode optical fibre, so-called because it has



“HOW TO TURN ELECTRONIC THEORY INTO PRACTICE AND MAKE IT PAY...”

“If you understand and enjoy radio and electronics and want to extend your knowledge and experience, then we at Stott's can help you.

Stott's have home-study courses for complete beginners in Radio theory and basic Electronics through to the standards needed to maintain and service Colour Television.

Anyone who has these skills at their fingertips can make it pay by turning a fascinating hobby into a lucrative part or full time profession.”

A H Kelly

Athol H. Kelly B. Com. (Hons.) A.A.S.A. F.C.I.S.
Principal, Stott's Technical Correspondence College



Stotts



The name to trust in
correspondence education.

TECHNICAL CORRESPONDENCE COLLEGE

Melbourne, 159 Flinders Lane, 3000. Tel: 63 6212
Sydney, 383 George Street, 2000. Tel: 29 2445
Brisbane, 290 Adelaide Street, 4000. Tel: 31 1627
Kent Town, 66 King William Street, S.A. 5067. Tel: 42 5798
Perth, 89 St. Georges Terrace, 6000. Tel: 322 5481
Hobart, 1st Fl. 29 Argyle Street, 7000. Tel: 34 2399
Singapore, P.O. Box 3396, Singapore 1

Please send me free, and without obligation, full details of the following courses:

(PLEASE PRINT)

MR MRS MISS _____ AGE _____

ADDRESS _____

POSTCODE _____

Stott's undertake that no sales counsellor will visit you.


The Stott's range of courses in
Electronics are:

Radio for Amateurs
Introduction to Electronics
Digital Electronics
AM Radio Receivers
Radio/TV Servicing
Colour Television
Amateur Radio Operators'
Certificate

A full range of Hobby and
Business courses also
available.

ALA/ST547/EA/679

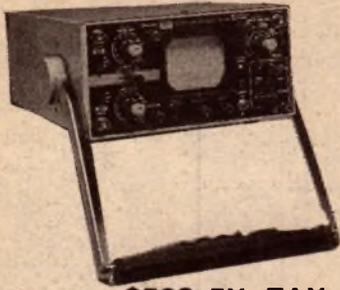Quality Test Instruments at Affordable Prices



**\$598 EX. TAX
\$687.70 INC. TAX
FROM STOCK**

TTM303 15MHz Mains/Battery operated oscilloscope

BRIEF SPECIFICATIONS:

The TTM Dual Trace Portable Scope Mode 303 offers a high sensitivity of 5mV/DIV with DC to 15MHz bandwidth. The 3-inch CRT with 1.5kV regulated accelerating voltage gives a clear bright display.

This Portable Scope operates from standard line voltage (240V) or from the internal rechargeable Ni-Cad battery, that provides 2 hrs operation before recharging is required. It also operates from any external DC voltages of 11 to 30V, eg car batteries, standard "C" size cells, etc.

SENSITIVITY:— 5mV to 10V/DIV 1-2-5 step with fine control BANDWIDTH:— DC to 15MHz (-3dB) RISE TIME:— 24ns. OPERATING MODES:— CH-A, CH-B and Dual Trace TIME BASE — 1 usec to 500 mS/DIV with fine control EXPANSION:— x 5 at all ranges X-Y OPERATION:— X-Y mode is selected by SWEEP TIME/DIV switch CH-A: Y axis CH-B: X axis. POWER REQUIREMENTS:— AC: 115/240V DC: 11-30V, 7.2VA. Battery: Ni-Cad Battery (up to 2 hour operation) SIZE: 113 (H) x 223 (W) x 298 (D) mm approx WEIGHT:— 4.5kg



**\$625 EX. TAX
\$718.75 INC. TAX
STOCKS DUE IN JUNE**

Application BS610 15MHz No Parallax display oscilloscope

BRIEF SPECIFICATIONS:

The BS-610 employs a high brightness 140mm Rectangular CRT with internal graticule assuring easy and accurate observation of waveforms without any parallax.

External DC-Powered operation expands the versatility of this oscilloscope to FLOATING Measurements as well as field operation.

Other features including TV SYNC and HF REJ, make this scope ideal for research and development, production lines or in-the-field service applications from computers to electrical appliances.

SENSITIVITY:— 5mV to 10V/DIV on 11 ranges in 1-2-5 step with fine control. BANDWIDTH — DC to 15MHz (-3dB) RISE TIME — 24ns. OPERATING MODES: CH-A, CH-B, DUAL, ADD and CHOP TIME BASE:— 0.5usec to 0.5sec/DIV in 19 ranges and X-Y in 1-2-5 step with fine control MAGNIFIER:— x5 at all ranges X-Y OPERATION — X-Y mode is selected by SWEEP TIME/DIV switch CH-A: Y axis CH-B: X axis. POWER REQUIREMENTS:— AC: 115/240V DC: 11 — 30V, 7.2VA SIZE:— 145 (H) x 280 (W) x 369 (D) mm. WEIGHT:— 6.7kg

**SP100 probes 100MHz, 10:1, 1:1, off posn.
To suit TTM303 and BS610**

**\$30 EX. TAX FROM
\$34.50 INC. TAX STOCK**



8020A 7 Function, 29 Range Hand Held DMM. Has unequalled capabilities



**\$177 EX. TAX
\$203.55 INC. TAX**

Designed for the widest possible range of applications, the 8020A offers every one of the important functions and features in demand today by DMM users, and more. Measurement performance is fully specified and clearly stated for every parameter, and conservative Fluke design means you get instrument specifications you can depend on. Low cost of ownership, worldwide Fluke service and a complete range of measurement accessories make the 8020A ideal for use by anyone engaged in trouble-shooting or servicing electrical and electronic equipment

FROM STOCK

BRIEF SPECIFICATIONS:

10 VOLTAGE RANGES: 100uV to 1000 Vdc, 750 Vac

Basic DCV Accuracy: +0.1% Basic ACV Accuracy: +0.75%

6 RESISTANCE RANGES: 100m to 20M Basic Accuracy: +0.1%

3 DIODE TEST RANGES: 2k to 200k 20M

2 CONDUCTANCE RANGES: Measure leakage from 500 to 10,000M Measure beta

8 CURRENT RANGES: 1uA to 200mA Basic DC Current Accuracy: +0.75% Basic AC Current Accuracy: +1.5%

STOP PRESS!

Arriving soon. The Fluke 8022A DMM. Similar to the 8020A but slightly less accurate and without the conductance ranges. \$144 Ex Tax. \$165.60 Inc. Tax.

AVAILABLE FROM SELECTED ELECTRONICS STORES OR:

ELMEASCO


SYDNEY
PO Box 30, Concord, NSW 2137
13-15 McDonald St,
Mortlake, NSW, Ph (02) 736 2888.
Telex 25887

Instruments Pty. Ltd.

MELBOURNE
PO Box 107,
Mt Waverley, Vic 3149.
21-23 Anthony Drive, Mt Waverley, Vic
Ph (03) 233 4044. Telex 36206



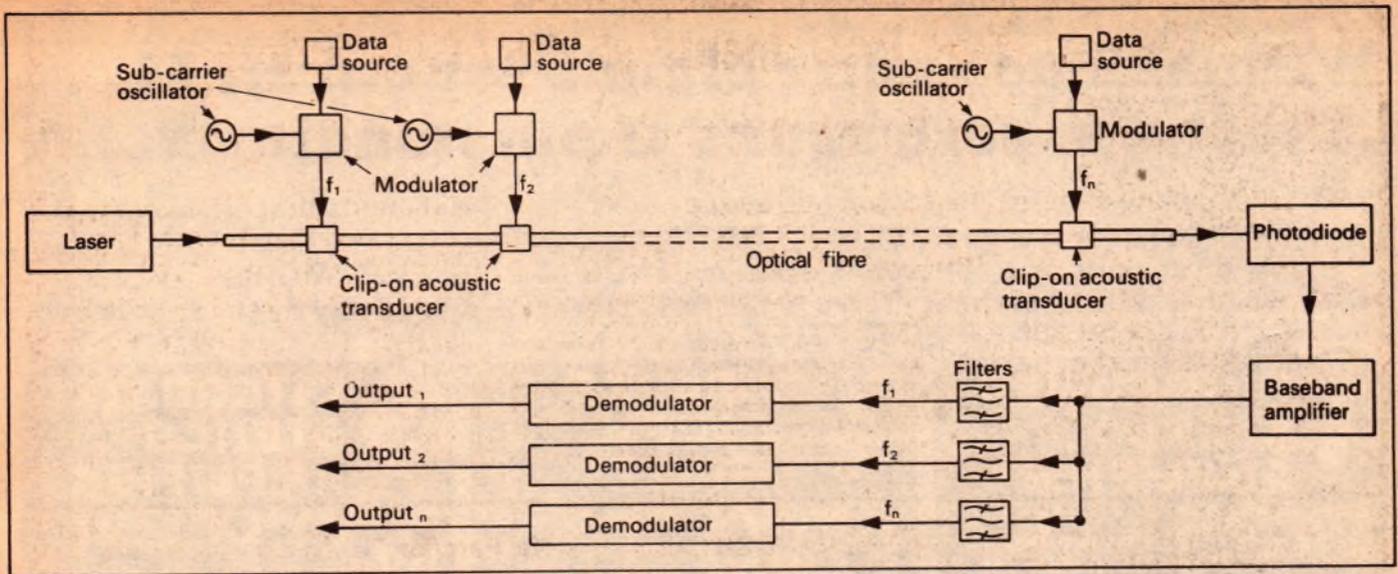ADELAIDE
Phone (08) 51 3521
PERTH
Phone (09) 325 3144
BRISBANE
Phone (07) 229 3161



Simple one-way telemetry system from several sources to a single destination. Each modulator operates at a distinct frequency, the sum effect being a complex phase modulation of the laser-produced wave in the fibre. The receiving system uses filters to analyse the signal into individual components corresponding to the various data inputs.

tion of the laser-produced wave in the fibre. The receiving system uses filters to analyse the signal into individual components corresponding to the various data inputs.

numerous possible paths for the rays to travel from input to output, involving slightly different overall path lengths. Phase modulators are attached to the fibre at various input points.

Each modulator operates at a distinct frequency, known as the sub-carrier or centre frequency, and is keyed on and off in pulses representing the binary code of the data. Its output modulates the wave travelling in the fibre, by shifting its phase to and fro at a rate corresponding to the sub-carrier frequency. At any instant, the phase shifts introduced by all the modulators add together, thereby producing a complex overall phase modulation that can be analysed by receivers, at the data collection point, back into the components generated by the individual modulators. In this way data from individual modulators is identified and separated out.

Fading

In multimode fibres, the multipath propagation of the light causes interference between the rays arriving at a phase-sensitive detector, somewhat akin to the fading met with in short-wave radio communication, so we have to provide means of detecting the rays from the different paths separately and combining the outputs to give an acceptable level. Our team is now investigating a number of simpler, alternative systems for overcoming this problem.

Probably the most important advantage of the phase-modulated data highway is the fact that we can feed data into it wherever we like, without breaking into the optical path with a coupler. All we have to do is clip on the transducer, rather like putting a peg on a clothes line. That, and the low power needed, is what makes it so attractive for telemetry.

The phase modulation technique is particularly simple. An ultrasonic, piezoelectric transducer is attached to the fibre and energized at its resonant frequency with the required data signal. An ultrasonic pressure wave is thereby launched into the fibre and a phase change linearly related to the pressure changes is imposed on the light passing along the fibre. This means that we modulate the light in the fibre without breaking the optical path. So a single laser source and a single fibre with no direct connectors can provide access to a very large number of data sources and carry the data to a common reception point. The associated electronics system is simple, too, for there is no need to regenerate the entire data stream. The system is, of course, restricted to feeding only one receiving terminal.

Sensitive

Optical fibres are extremely sensitive to these changes of pressure. To find out how sensitive a fibre is, we can induce a phase change of the sort that might be expected from a change in the fibre temperature, or from a change in the strain or in the ambient pressure, by changing the physical length of the fibre, its refractive index or its diameter.

We may change one or more of these at a time, and if we measure the changes we can calculate the overall fibre sensitivity. Such calculations, supported by experiment, show that optical fibre is so sensitive that pressure variations a lot smaller than those caused by sound waves at the threshold of hearing are strong enough to give a detectable change in the optical output signal. This means that the fibres are highly microphonic; that is they are sensitive enough to pick up ambient

noise, so the sub-carrier frequencies of the modulators must be well above the upper limit of the noise spectrum, which may be as high as 50kHz.

This extreme sensitivity gives the phase-modulated data highway an important advantage. It means that the ultrasonic power needed to modulate the light in the fibre is roughly proportional to the square of the bandwidth, or range of frequencies contained in the modulation. For many data signals, for example those from temperature flow rate sensors, the bandwidth is less than 1kHz. This means that the power needed for modulation is about 100uW (microwatts) and the power consumed by the electronic circuits to handle this is only in the milliwatt region.

So it is realistic to think of a data input station run by a battery that would have years of life. For equipment to sense data in hazardous areas, where the hardware has to be sealed in a box, without power leads, this is important. It is also an attractive feature where data has to be collected from a large number of sensors in, say, a pipeline system, where it is better not to have to distribute electrical power to the data input points. Moreover, because the optical fibres do not attenuate the signal heavily, a link could be several miles long.

We have already referred to the use of multimode fibres, in which the light follows numerous ray paths. The technique may also be used with single-mode fibre, where there is only one ray path, but such fibre is very small and the mechanical tolerances at the modulator and receiver are less than 1um (micrometre). Because of these tight tolerances, such a system is difficult to align optically, though it has the advantage of being electronically simple.

We make no exotic claims for our Hi Fi just a superb sound & outstanding value


YES, you reap the benefit! Dick Smith introduces this range of Hi Fi units that offers our usual remarkable value for money BUT THATS NOT ALL

. . . . Buy these units as a complete system AND YOU'LL SAVE EVEN MORE!!

Dick Smith Hi Fi will become a force in the Hi Fi market — don't delay be the first to own quality Hi Fi at a DIRECT IMPORT PRICE!!

1 HIGH POWER STEREO AMPLIFIER

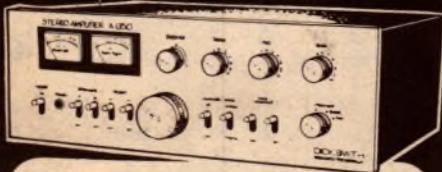\$299 OR \$30 dep. and less than \$15 per month over 24 months.




The super power amplifier from Dick Smith. A tremendous 55 watts RMS per channel into 8 ohms plus a truly superb array of controls. An outstanding feature of this amplifier is the midrange control a part of the audio spectrum ignored on most other amplifiers. The circuitry is direct coupled OCL and there are 37 transistors and 30 diodes PLUS a separate power supply for each channel for increased stability. Dimensions 420(w)x150(h)x352(d)mm. Net weight 10.5kg

A-1350

2 DELUXE AM/FM TUNER

\$239 OR \$24 dep. and less than \$12 per month over 24 months.


Top of the range AM/FM Stereo Tuner from Dick Smith. This unit has a superb performance coupled with complete user control. Muting of noise between FM stations, hi-blend of high frequency for a more mellow sound plus a control for setting output level. Excellent performance is maintained through the use of 1 FET, 1 stage RF amplifier, 3 gang variable capacitor, 5 stage limiter, PLL MPX, 9 transistors and 7 diodes. Dimensions 420(w)x150(h)x352(d)mm.

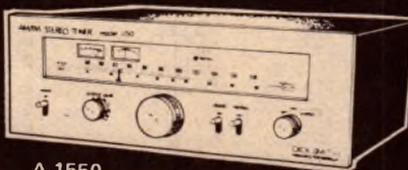

A-1550

3 INTEGRATED STEREO AMPLIFIER

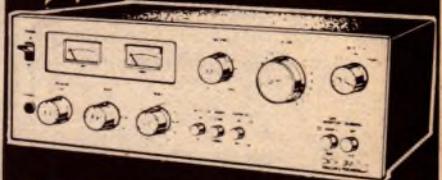\$249 OR \$25 dep. and less than \$13 per month over 24 months.



A fabulous 30 watts RMS per channel from this very modern looking Dick Smith Integrated Stereo Amplifier. Visual power meters lets you know what power is being applied to your Playmaster speakers. Use more than one pair of speakers, have tape dubbing, low filter and many more controls for you to contour your sound. Frequency response 30Hz to 20kHz. Semiconductors: 35 transistors and 12 diodes. Dimensions 400(w)x135(h)x290(d)mm. Net weight 4.6kg.

A-1300

SAVE \$124

The basic system comprises the superb Dick Smith 55 watts RMS per channel amplifier (A-1350) PLUS the Garrard 125SB turntable (A-3070) PLUS the Playmaster 3/75LC speaker system (A-2364) — Reference 1, 6 and 7.

Normal separates price

~~\$823~~

SAVE \$175

Move up the scale and add the Dick Smith deluxe AM/FM stereo tuner (A-1550) to the basic system above. Reference 1, 2, 6 and 7.

~~\$1062~~

SAVE \$211

Top of the line system incorporates all of the above components PLUS the Dick Smith Dolby™ stereo cassette deck (A-3500) Reference 1, 2, 5, 6 and 7.

~~\$1261~~

SAVE \$104

The second basic system incorporates the Dick Smith 30 watts RMS per channel stereo amplifier (A-1300) PLUS the Garrard 125SB turntable (A-3070) PLUS the Playmaster 3/53LC speaker system (A-2362) Reference 3, 6 and 8.

~~\$703~~

SAVE \$143

Take the basic system and add the matching Dick Smith AM/FM stereo tuner (A-1500) for increased performance. Reference 3, 4, 6 and 8.

~~\$892~~

SAVE \$183

Add the Dick Smith Dolby™ stereo cassette deck for a complete package. Reference 3, 4, 5, 6 and 8.

~~\$1091~~

\$699

OR \$70 dep. and less than \$22 per month over 48 months.

\$887

OR \$89 dep. and less than \$28 per month over 48 months.

\$1050

OR \$105 dep. and less than \$33 per month over 48 months.

\$599

OR \$60 dep. and less than \$19 per month over 48 months.

\$749

OR \$75 dep. and less than \$23 per month over 48 months.

\$908

OR \$91 dep. and less than \$28 per month over 48 months.

For more information on specifications of the equipment shown on these two pages, please check out the **Dick Smith 1979 Jumbo Catalogue** available from all Dick Smith stores at 75¢ each or send in your remittance to our Mail Order Centre (address below) and we will post you a copy.

Take advantage of our **BELOW COST FREIGHT** to anywhere in Australia — the charge of **\$6.00** covers individual items or if you purchase a complete system we will charge you only **\$6.00** for freight on the complete system.

TERMS shown are approximate due to varying stamp duty in different states. Terms are only applicable to approved applicants and apply to personal shoppers only.


4 STEREO TUNER

\$189

OR \$19 dep. and less than \$12 per month over 18 months.

Switch on your Dick Smith AM/FM stereo tuner and enjoy the delightful world of quality FM stereo broadcasts plus the normal range of local AM stations. Built-in signal and tuning meters enables you to put the correct amount of signal into your amplifier and for it to be precisely in tune. Smooth flywheel type tuning control takes all of the effort out of finding stations.

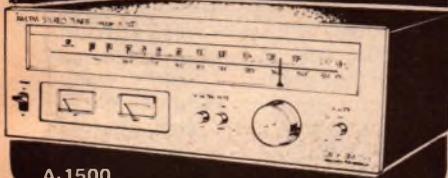Semiconductors: 1 FET, 3 IC's, 5 transistors, 3 diodes and 1 LED. Dimensions: 400(w)x135(h)x290(d)mm. Net weight 4.6kg.




A-1500

5 DOLBY CASSETTE DECK

\$199

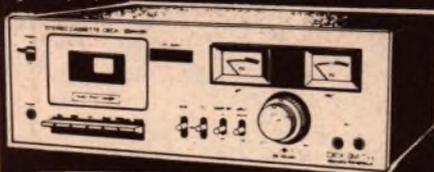OR \$20 dep. and less than \$13 per month over 18 months.



This excellent Dick Smith Dolby Stereo Cassette Deck complements all of the Dick Smith audio units and the front loading design enables stacking of units to be easily accomplished.

The frequency response of 40Hz to 12.5kHz and wow and flutter figure of 0.12% WRMS means superlative performance from your tapes. Bias and equalisation are adjustable for Chrome, Ferrichrome and normal tapes. Complete fingertip control gives total satisfaction.

Semiconductors: 13 transistors, 2 diodes, 1 Zener diode, 1 bridge rectifier, 2 Dolby IC. Dimensions: 400(w)x135(h)x290(d)mm. Net weight 5kg. Power supply 240V AC.


A-3500

6 GARRARD TURNTABLE

\$129

OR \$13 dep. and less than \$9 per month over 18 months.

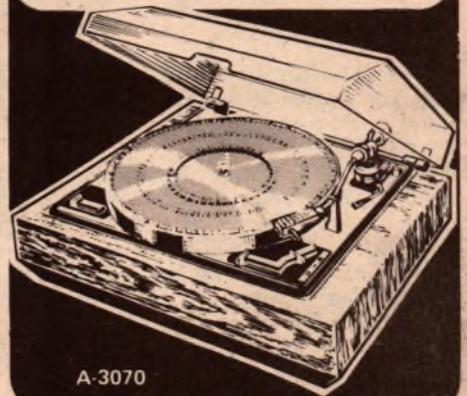The craftsmanship of a British product — belt drive stability — superb magnetic cartridge with diamond styli — deluxe modular base and cover with fitted audio leads — The Complete Turntable System. Dimensions: 163(h)x364(w)x325(d)mm.



A-3070

Playmaster

The Sound Of Excellence

Dick Smith offers you the **QUALITY** of PLAYMASTER in ready made form **PLUS** a five year warranty on the driver units and crossovers.

Two systems are available: the 30cm three way system, model 3/75LC, with built in fader controls for the midrange and tweeter levels and a power handling capability of 80 watts peak into 8 ohms. Size: 71(h)x47.5(w)x29.3(d)cm.

The second system, model 3/53LC, is also a three way system utilizing a 24cm woofer with a power rating of 60 watts peak into 8 ohms. Size: 62(h)x39.3(w)x29.3(d)cm.

Both systems have a superior simulated walnut vinyl veneer finish, including the front baffle board, and a removable deluxe foam grille.

Complement the Dick Smith audio units with the Playmaster excellence.

7 Playmaster 30cm System

Cat. A-2364

RRP \$411 (incl. GST) plus \$20 per month over 18 months.


\$395 per pair

8 Playmaster 24cm System

Cat. A-2362

RRP \$331 (incl. GST) plus \$17 per month over 18 months.

\$325 per pair

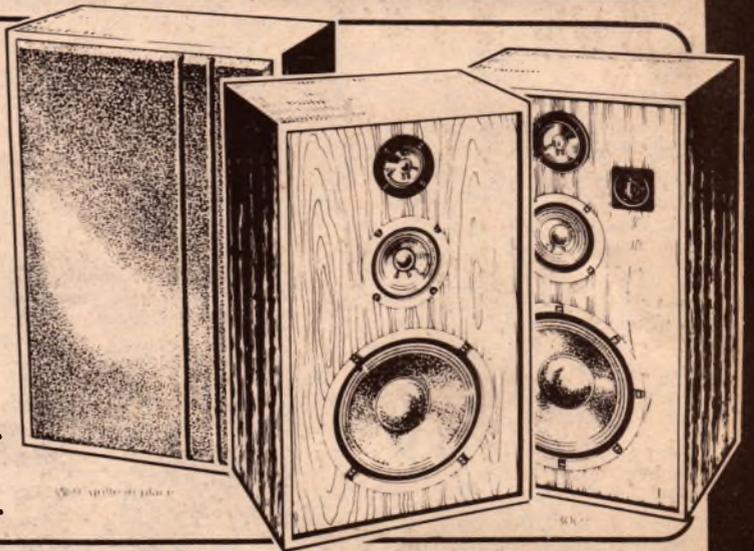

DICK SMITH ELECTRONICS

NSW 125 York Street,
147 Hume Highway,
162 Pacific Highway,
30 Grossa Street.

SYDNEY Phone 290 3377
CHULLORA Phone 642 8922
GORE HILL Phone 439 5311
PARRAMATTA Phone 683 1133

ACT 96-98 Gladstone Street,
VIC 399 Lonsdale Street,
656 Bridge Road,
QLD 166 Logan Road,
SA 203 Wright Street,
WA 414 William Street

FYSHWICK Phone 80 4944
MELBOURNE Phone 67 9834
RICHMOND Phone 428 1614
BURANDA Phone 391 6233
ADELAIDE Phone 212 1962
PERTH Phone 328 6944

Opening soon in WOLLONGONG. Watch for store address!

EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

MAIL ORDER CENTRE: PO Box 747, CROWS NEST NSW 2065. Ph 439 5311. PACK & POST EXTRA.

bankcard
welcome here

SHOPS OPEN 9AM to 5.30PM
(Saturday: 9am till 12 noon)
BRISBANE: Half hour earlier.
ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH PRODUCTS IN MOST AREAS OF AUSTRALIA.





They're working on 3D films and TV — but don't hold your breath!

If you want to start an argument around the EA office, all you need do is to claim to have achieved 3D (3-dimension) viewing without the use of differential images for presentation to the respective eyes. Add a few more unlikely claims for good measure and you can expect a real babble of protesting voices!

The explanation for the above heading and introduction in a news item which was published a few weeks ago in the Sydney "Sun-Herald".

It stated that a commercial had been running on Australian television for some time which, unknown to the sponsor and to the viewing audience, had been shot in such a way that it had the potential to be viewed in 3D. The system was credited to Melbourne cameramen Vok Mol and Mike Browning, and was being promoted on a world-wide basis by the well known columnist, humourist and film maker Phillip Adams.

There was a hint of wider applications and reference to special substitute taking lenses, which could be fitted to any camera, movie or still. Mention was also made of special viewing glasses, but no hint of any means by which the system could record or present complementary left/right stereo images — the very core of any genuine 3D system.

In fact, it is difficult to envisage any commercially practical method whereby compatible, full colour, complementary stereo images can be presented on a normal television screen yet, by inference, this seemed to be the substance of the published claim.

There was more to follow: the report went on the state that the system could convert any existing colour film to 3D and any existing black and white film to colour and 3D as well. It could eliminate scratches, and such anomalies as a distant aeroplane which might appear in the sky when a period film was being shot.

The last couple of points raised no special queries because they could come within the ambit of modern

video processing techniques. But 3D pictures without differential images and colour prints without colour information could scarcely escape the expected guffaws of ridicule from our technically orientated staff members.

Nor were we alone in this reaction. Various well informed people had also read the item and mentally rejected it along with other past claims by would-be inventors of no-hassle 3D. Their description of the news item tended to draw heavily on bovine imagery!

Behind such a reaction is a question of fundamentals, rather than mere technical bias or rigidity. Human stereoscopic vision relies on the fact that our eyes are separated by 7 or 8cm, so that each receives a slightly different version of the object or scene being viewed. The difference between the two images, along with various other clues, is processed by the brain to produce a subjective impression or



"I'll start enjoying Chaplin when they re-do him in 3D, wide screen colour and quadraphonic sound!"

judgment of distance.

Because of this, all genuine 3D systems of visual reproduction must start with appropriate complementary images, normally recorded from positions 7 or 8cm apart. Subsequently, these are presented separately to the appropriate eyes, using such devices as the old-fashioned stereoscope, selective red and green filters, polarized light filters, lenticular screens, prismatic overlays on postcards, etc. The methods have varied widely but they have all sought to satisfy the basic requirement of binocular presentation.

If by choice or necessity a scene or an object is photographed from one point only, there is no way in which the sole resulting image can be processed to produce a genuine differential counterpart as necessary for true 3D presentation. In short, there is no way in which photographic, or video, or computer technology can generate details that were never recorded in the first place.

Let me illustrate:

On the desk in front of me, at the moment, is a plastic tape dispenser. It is exactly in line with my left eye and, viewed along that axis, I can see only the front surface and, above it the top edge of the tape and the top inside-back surface. From that view, or a single photograph along that axis, there would be no way of man or machine telling whether the sides were gloss or matte, completely plain or embellished with a maker's brand or motif.

But, when I open my right eye, I can see along one side: it is plain, slightly convex, with no hint of a manufacturer's brand. But it is also glossy and carries a strong, distorted reflection of the page of type on which it is resting.

In short, my right eye is registering information that is just not available to the left eye.

If it is impossible to capture a true stereo image along a single axis, it is also impossible to recover one from an existing non-stereo single-axis print, be it in colour or black and white. The differential information is just not there. As in the case of my tape dispenser, it was obscured from the taking lens!

But having said all that, the news release in the Sun-Herald still had me intrigued. What had inspired it? Surely the people behind it were not totally ignorant of the foregoing and well known basics. So I began to back-track.

Although the unofficial test run of a "3D" commercial had been on Australian TV some of the information at least had reached the Sun-Herald newspaper via the New York Times — a curious and roundabout route.

But there was more to it than that. Another U.S. publication ("Television Digest", Jan 22, 1979) had carried a reference to the Australian involvement but credited the system primarily to Digital Optical Technology Systems (DOTS) of Amsterdam Netherlands. It

was being further developed in America, they said, by the Ancom Company, drawing on the expertise of quite a string of technical people having previous association with companies like CBS and Fairchild.

From "Television Digest" as above, and other scattered clues, it would appear that the consortiums real objective is to increase the eye appeal of all forms of visual media. The possible application to movies and television made good headlines for the "Sun-Herald" but there is at least as much interest, if not more, in the area of home photography and printed matter. This last would add reason for the local involvement of Consolidated Press Holdings.

In trying to compose a technical whole from what rapidly became a jigsaw of bits and pieces, we were able to establish, with a fair degree of certainty, that the system did not use complementary images and was therefore not a true 3D system — despite the headlines. That requirement remains as difficult to meet, commercially, as it ever was.

The new effort is directed, rather, towards achieving what might better be described as "depth enhancement", by maximising what we referred to earlier as "other clues". At best, it is ersatz-3D.

It also became apparent that they consortium is not relying on a single key process, but a whole array of concepts and measures which combine towards the desired end result. Photographic techniques, optics, video technology, computer processing and human intervention are all involved at one stage or another.

From this point, we began to look at the options which might conceivably be open to anyone striving towards an impression of enhanced depth. How many of the available options we nominate and how many bullseyes we score remains to be seen! All we have to go on are technological and commercial "leaks".

As a starting point, reports on the DOTS system refer to the development of taking lenses which simply replace those fitted to a normal still, or movie or TV camera. The resulting image must undoubtedly be modified in some way, but it remains a single, full colour image, which may be printed, projected, and transmitted in the usual fashion without the viewer being necessarily aware that it has some special quality.

There is also talk of discrimination between in-focus and out-of-focus areas, and this suggests the first option: a sense of depth can be imparted to some pictures at least, by ensuring that the object of interest in the foreground is in sharp focus, with objects in the background in progressively "softer" focus.

The trick has been used by painters for centuries and by photographers for a shorter period. In the latter case, they take advantage of the limited depth of

field exhibited by longer focal length lenses at full aperture. However, this can present practical difficulties and, if the photographer is forced by circumstances to settle for a shorter focal length and to stop down, he is faced with a much greater depth of field whether he wants it or not!

On this basis there may be times when a photographer — or a TV cameraman — might welcome some additional technological aid.

In fact, it is possible to conceive a

"I'm sorry dear and I don't want to argue but, even if it was good, I wouldn't admit to liking it!" ("TV Times")



range of special lenses in which the action of stopping-down would progressively block the centre of the elements, restricting light transmission to the perimeter. I gather from those who know about these things, that stopping down in this fashion would not add to the depth of field.

Option number one!

Another hint from the DOTS report suggested that the system involves some slight colour fringing. Technologists normally bend over backwards to avoid this but I gather that deliberate fringing is part of the DOTS technique: not enough to spoil the picture viewed normally, but sufficient to give a desired effect when using their "3D" glasses.

More about those in a moment.

If fringing is a requirement this, too, could be brought about in the lens by ensuring that its transmission properties varied slightly for light of different wave lengths. Whether or not this is inter-related with possible depth of field characteristics I wouldn't know, but it emerges as option number two!

One other option suggested by our Editor, Jim Rowe, is manipulation of the colour saturation in the defocused background scene — something that may or may not be feasible, depending on circumstances.

Summing up all this, what emerges is a basic image — on paper, or on a TV or projection screen — which looks ordinary enough at first glance. But closer inspection may reveal emphasis on the in-focus and out-of-focus differential, slight but deliberate colour

fringing, and possible reduction in the background colour saturation.

This under normal direct viewing.

Now where do the viewing glasses fit in?

While following all this through, our Assitant Editor, Philip Watson, drew my attention to an article "The Amateur Scientist" by Jearl Walker in "Scientific American" (Dec. 1978, p. 182). The article is mainly a discussion of the old-fashioned stereoscope, but the author makes a number of interesting points:

While the pictures used are normally a genuine stereo pair, they are presented to the eyes in such a way that the eyes look straight ahead and at much the same focus as they would if looking at the original scene. These two factors strongly reinforce the stereo illusion, by assuring the brain that the scene is not printed on a card a few inches away but is much larger and much farther away: involving infinity focus and minimal declension of the eyes.

Walker declares that, for many people, the stereoscope still gives a credible illusion of depth with pictures other

Now available

top quality rebuilt colour picture tubes

B & W also supplied

Prompt service

Very competitive prices

Write or phone:

COLOR TUBES INTERNATIONAL


1 CARTER ROAD, BROOKVALE, NSW 2100

(Office and Factory)

(02) 938 4063

VICOM

International
Pty. Limited

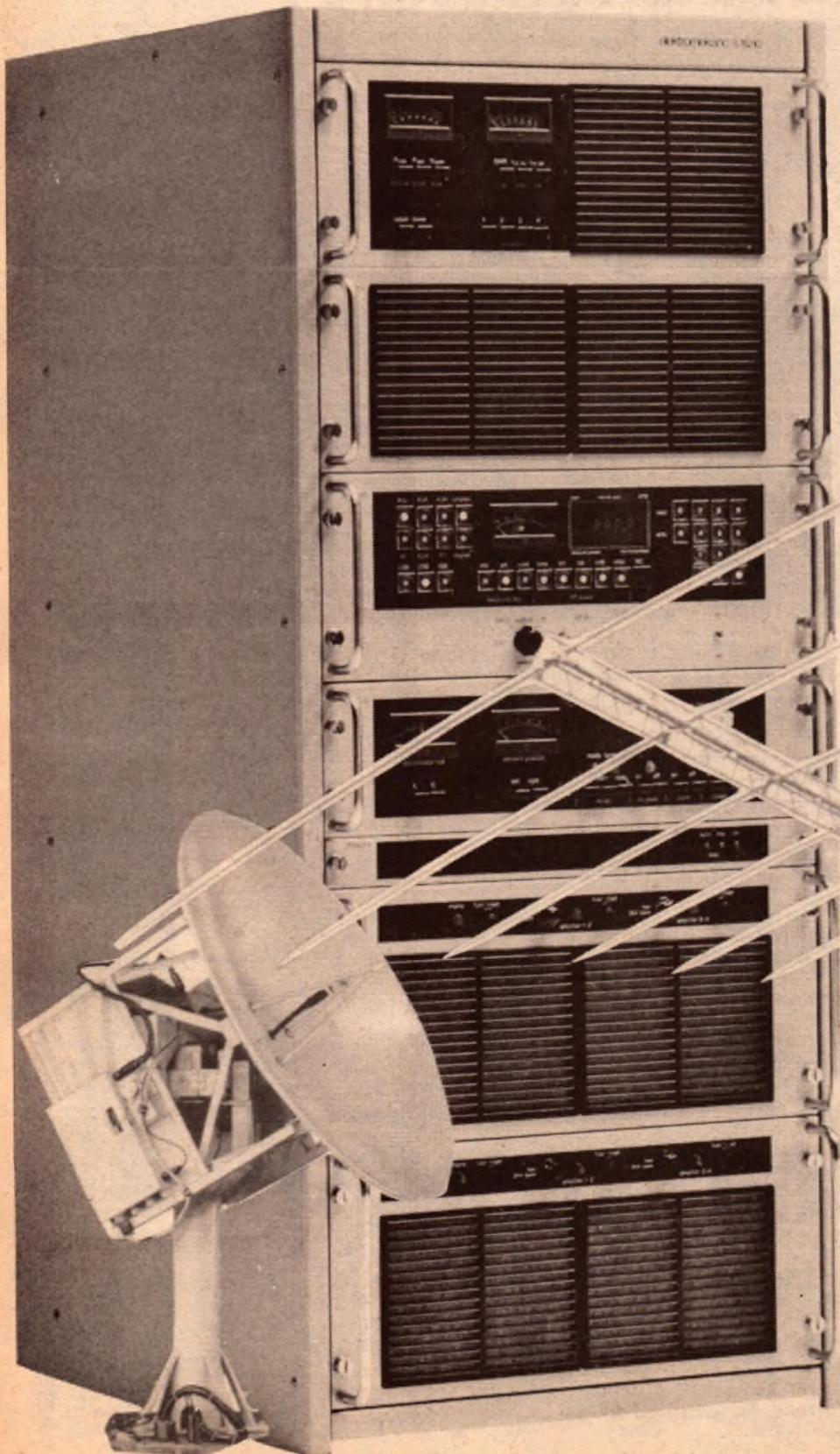

PROFESSIONAL PRODUCTS DIVISION

Supplying Australia
and the Pacific:

- Electronic Surveillance
- Low Light Video Surveillance
- Omega Receivers
- Rhombic & LPA Antennas
- Speech Security Systems
- Frequency Standards
- RF Signal Sources
- ISB HF Transceivers
- Marine Radar
- Counters 40GHz
- Digital & Analogue Test Equipment
- Spectrum Analysers
- Underwater Communications
- Tracking Oscilloscopes


**LET US QUOTE FOR YOUR
SYSTEM**

VICOM PROFESSIONAL PRODUCTS DIVISION,

68 EASTERN ROAD,
SOUTH MELBOURNE, VIC. 3205.
PH. (03) 699-6700
TELEX. AA30566

PROFESSIONAL

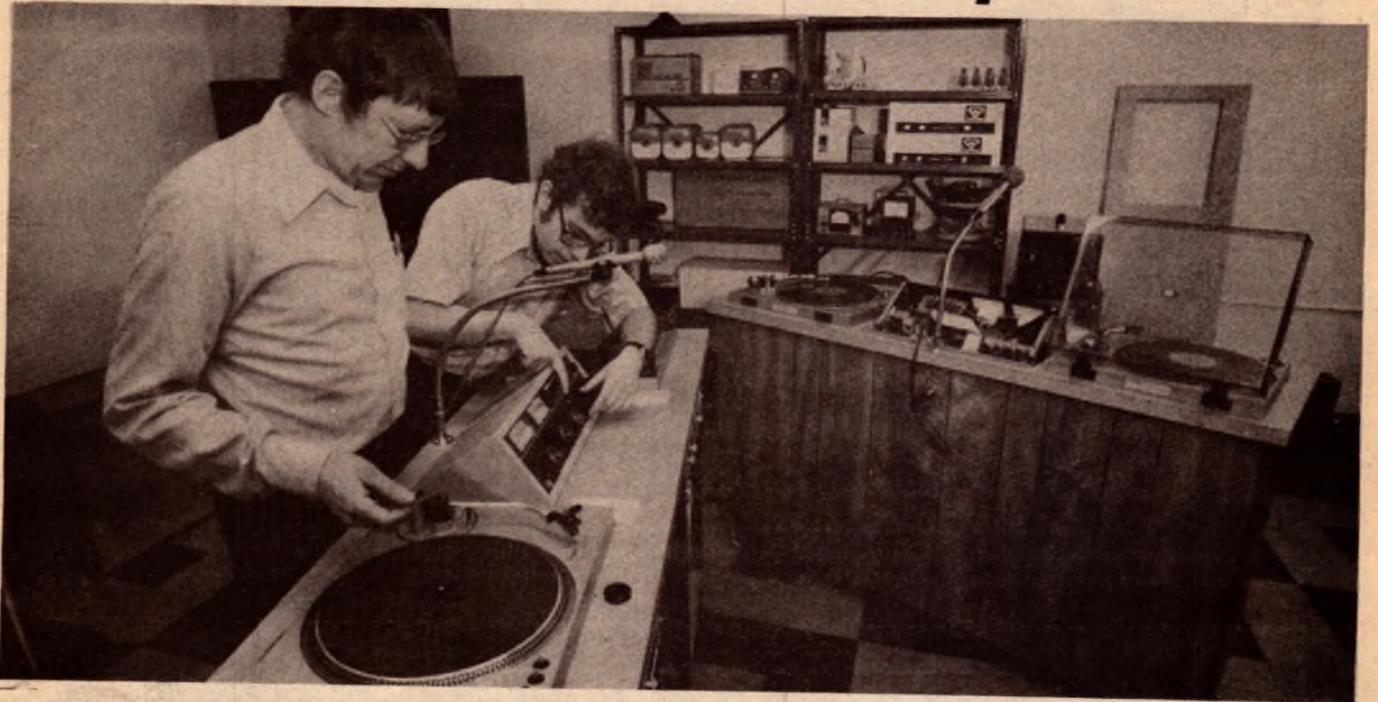**Ohio Disco Packager, SWB Electronics,
uses Stanton Exclusively.**



Larry L. Decker, Designer/Owner, examines finished control table for Disco use.

The trend to Portable Disco continues strong. An ambitious Company in Canton, Ohio, SWB, is achieving excellent success with their units (their goal is a national franchising operation). James C. Fravel, General Manager/Promotions, writes to Stanton, "We use Stanton cartridges in each and every unit we sell. Two of our units have been running for about a year and a half without failure. We are proud of the track record of our units and the Stanton cartridges."

They use the 500AL because it's a durable cartridge and "gives SWB a 4 dB base boost that we like to have with the music we play. It has been, by far, the best cartridge we have used (and we have tried many)".

So, Stanton, world famous for its top-of-the-line calibrated cartridges, the 881S and the 681 series, also serves the professionals in the Disco Industry.

Whether *your* usage involves recording, broadcasting, archives, disco or home entertainment, your choice should be the overwhelming choice of the professionals in every field . . . Stanton Cartridges.



STANTON!

The choice of the professionals™

Sole Australian Distributors

LEROYA INDUSTRIES PTY

Head Office: 156 Railway Pde. Leederville, Western Australia, 6007. Phone 81 2930
NSW Office: 100 Walker St. North Sydney 2060. Phone 922 4037



Hi Fi Topics

SEEING IS BELIEVING — ESPECIALLY WITH STYLI!

The use of a scanning electron microscope has enabled engineers of Stanton Magnetics Inc to verify or revise ideas about phono cartridge styli which had previously been based on supposition. They have also been able to make interesting observations on the effect of various groove cleaning methods.

by **W. N. WILLIAMS**

Stanton invested in their scanning electron microscope about four years ago, with the thought that it might assist towards a better understanding of styli shapes and behaviour. It certainly did that and led, amongst other things, to the development of a curious saddle-shaped styli which was capable of playing record stampers. Being the counterpart of a disc, the styli had to ride on a ridge rather than in a groove!

An article on the saddle styli was published in our August issue, last year, extracted from paper presented to the Audio Engineering Society (USA) by Stanton engineer George Alexandrovich. In a companion paper, the same Author summarised some of the other work then in train, using the SEM (a common contraction of scanning electron microscope).

More recently, an advertisement on page 26 of our March 1979 issue featured a microphotograph of a Stanton "Stereohedron" styli tracking a record groove. While the printed illustration suffered by comparison with the original photograph, the excellent fit of styli to groove was clearly evident.

In explaining the operation of Stanton's SEM, Alexandrovich says that it consists essentially of a viewing chamber, which is capable of being sealed and evacuated during use. On top of the chamber is a tube, in which an electron beam

can be generated, focussed and deviated, more or less in the same way as the beam in a cathode-ray tube.

In use, a styli or other object to be viewed is placed on a platform in the chamber, which is then evacuated. Five control knobs on the front of the instrument permit movement of the platform, during operation, to optimise viewing conditions.

When the finely focussed electron beam strikes the surface of the object, electrons are scattered but some are reflected towards a "scintillator". Here the incident electrons produce photons, which are detected by a photomultiplier, to provide an electrical signal.

In use, the electron beam is deflected so as to scan the surface of the object, in much the same manner as in a TV camera. The signal from the photomultiplier, varying according to the surface detail of the object, modulates the intensity of a second, synchronised beam, scanning a picture tube screen. The resulting image can be viewed or photographed as desired.

The effective magnification of the system depends on the ratio of the viewing screen size to the area of the object being scanned by the original beam. ((The ultimate resolution is largely dependant on how finely the object scanning beam can be focussed.)

According to Alexandrovich, one of the early and im-

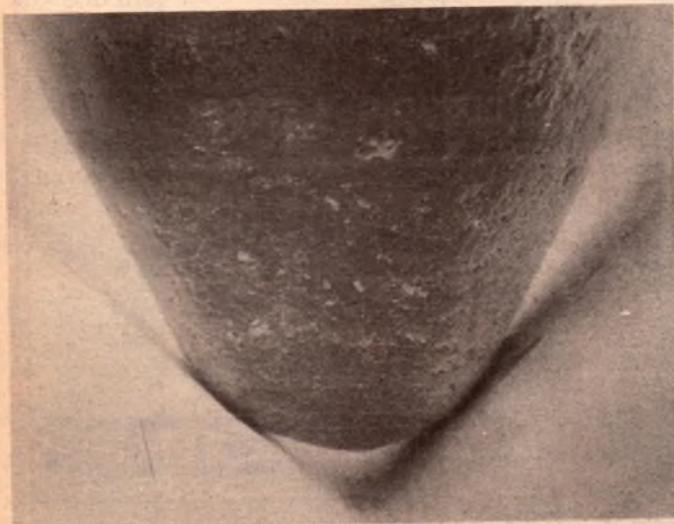


Fig. 1: A conventional spherical styli having a tip radius of 0.7 mil resting in a groove. Note the limited contact area, which has to support the total playing weight.


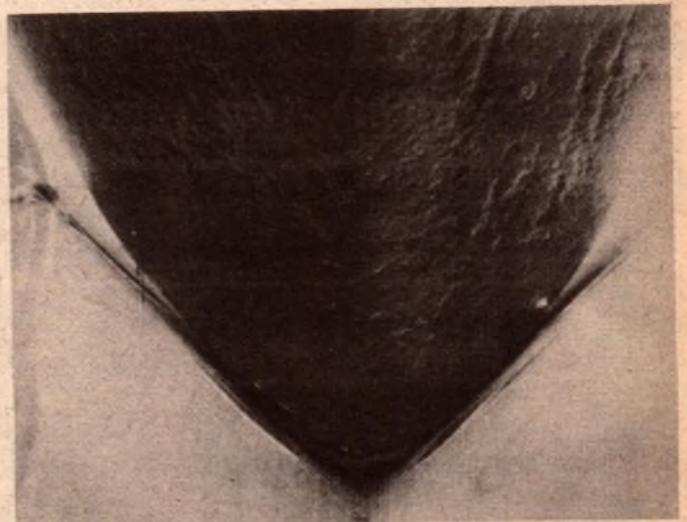



Fig. 2: A Stanton "quadrahedron" styli resting in a similar groove. The weight is distributed along a vertical segment of each wall, causing less pressure per unit area.

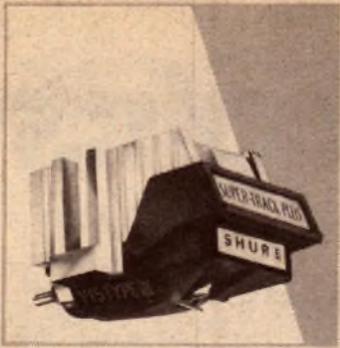

V-15 Type III ... critics called the Type III the finest cartridge ever when it was introduced. The ultimate test, however, has been time. The V-15's engineering innovations, the uniform quality, and superb performance remain unsurpassed by any other cartridge on the market today. 3/4 to 1-1/4 gram tracking force.



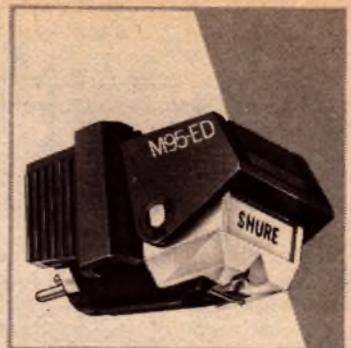M24H ... the cartridge that does not compromise stereo reproduction to add four-channel capability. Superb stereo trackability and quadriphonic carrier signal retrieval. New hyperbolic stylus tip, high energy magnet, and low-loss laminated electromagnetic structure. 1 to 1-1/2 gram tracking force.



M95ED ... second only to the V-15 Type III in stereo reproduction. A thinner, uninterrupted pole piece minimizes magnetic losses. Its 20 to 20,000 Hz response remains essentially flat across the entire frequency range for excellent sound quality. 3/4 to 1-1/2 gram tracking force.



M91ED ... excellent trackability at a lesser price. Shure Hi-Track has a smooth 20-20,000 Hz frequency response, 3/4 to 1 1/2 grams tracking force and an output voltage of 5.0mv per channel. Nude mounted diamond stylus tip.



M70EJ ... the easiest way to upgrade your hi-fi stereo system without straining your budget. Basically flat response is comparable to other brand cartridges costing twice as much. 1-1/2 to 3 gram tracking force.




SC35C ... Shure professional studio phono cartridge actually improves on-the-air playback quality of all recorded material. Curaway stylus grip design and 'band alignment point'. Frequency response 20 to 20,000 Hz.

The People's Choice-World-wide.

From Singapore to London to New York, Shure hi-fi pickup cartridges outsell every other brand — according to independent surveys. And for good reason: Shure cartridges, no matter where they're purchased, are guaranteed to meet the exacting published specifications that have made them the Critics' Choice in every price category.

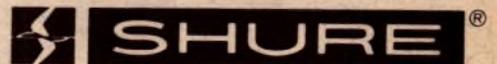Distributed in Australia by
Audio Engineers Pty Ltd, 342 Kent St., Sydney. Write for catalogue.



AUDIO ENGINEERS PTY LTD
 342 Kent Street
 SYDNEY 2000 NSW

AUDIO ENGINEERS (VIC)
 2A Hill Street
 THORNBURY 3071 VIC

AUDIO ENGINEERS (QLD) PTY LTD
 51A Castlemaine Street
 MILTON 4064 QLD

ATHOL M. HILL PTY LTD
 33-35 Wittenoom Street
 EAST PERTH 6000 WA

portant discoveries made with the SEM was a method of observing and measuring the area of contact between a stylus and a groove. In fact, the technique emerged by accident.

In order to view electrically non-conductive materials like diamond, it is necessary to gold sputter the sample. The thin layer of gold on the surface serves a dual purpose: (1) it makes the sample conductive so that electrons from the constant bombardment do not build-up an electrostatic charge, thereby distorting or repelling the incident beam; (2) over and above this, gold reflects the electrons very efficiently, generating a strong image as a result.

However, the gold coating turned out to have another quite different use. In the very act of aligning a treated stylus in a groove segment for observation, Stanton engineers noted that the gold surface was scuffed off. It became immediately obvious that a gold coating could serve as a precise indicator of those areas which came into contact with the groove wall under various conditions. The position and the size of the scuffed area on the stylus could be assessed with a high degree of precision.

In pursuing this, the engineers discovered that, while some exotic shapes of styli gave commendable results when new, their contact areas changed drastically with progressive wear. In some cases the deterioration was such that they were producing greater groove wear and higher distortion than would be expected from a conventional spherical or elliptical stylus after the same number of playings.

Lengthy observations like this, combined with other listening and performance tests, led ultimately to the production of Stanton's own "Stereohedron" tip, as fitted to their top-ranking 881S cartridge. They claim that, not only does it exhibit the desired tracking capability, but it also retains the shape of its contact area for a longer period, thereby ensuring lower distortion, long-term, and lower record wear.

Another effect which was strikingly identified was that of skating force. When a record is being played by any conventional, pivoted pickup, the drag of the record on the stylus applies an oblique force which tends to pull the stylus inwards and against the inner wall of the groove. This accelerates wear of that particular wall and that particular side of the stylus. In addition, the imbalance of forces on the tip tends to increase the risk of mis-tracking, with increased distortion.

Alexandrovich says that they didn't have to look far to identify old discs which were worn asymmetrically by having been played without skating force correction on the pickup arm. Nor was there any doubt that stylus life was shortened under these conditions. The lesson is therefore clear; make



Fig. 3: Loss of gold plating from the shoulders of a modern stylus indicates the area of groove contact. The tip has almost — but not quite — touched the bottom of the groove.

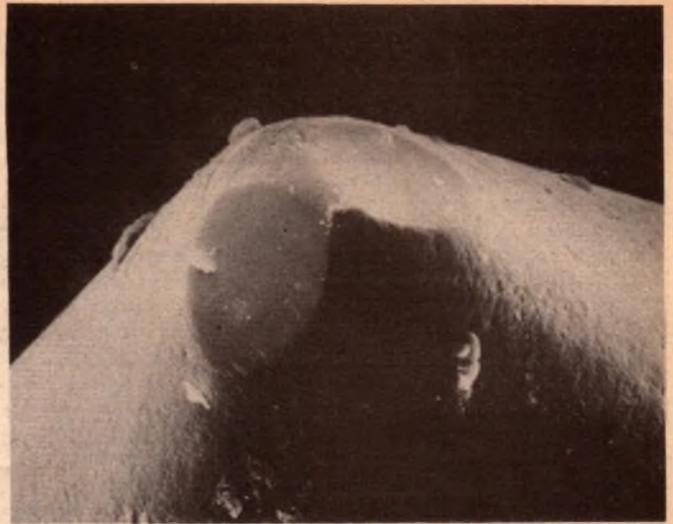


Fig. 4: With properly adjusted anti-skating, wear on the stylus is symmetrical, ensuring maximum playing life. Note that, despite the wear, the tip is still clear of the groove bottom.

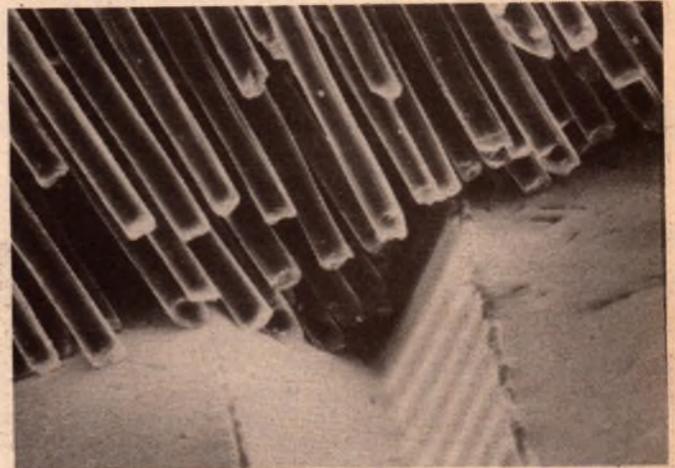


Fig. 5: Carbon fibres from a cleaning brush resting against the surface of a disc. Tests showed that they can dispel electrostatic charges but they are generally too soft to cope with anything but minimal lint and particle deposits. Fewer and thicker bristles under greater unit pressure are necessary to dislodge and pick up troublesome foreign matter.

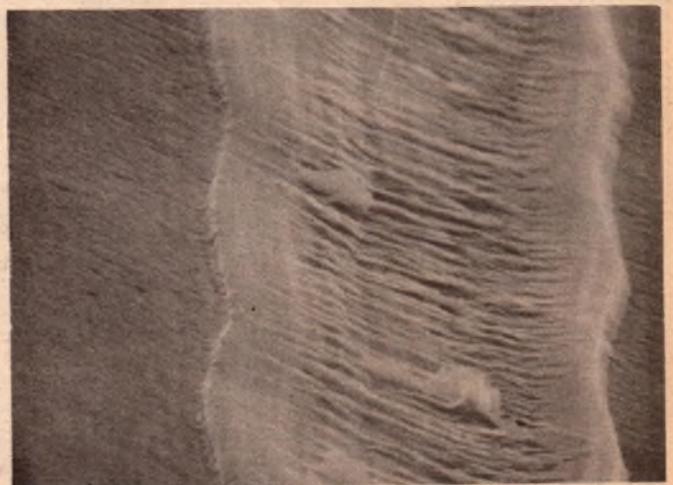


Fig. 6: A surprising observation was the effect of playing a disc when moistened with water. Far from lubricating the surface, it actually produces a tearing effect as shown.

sure that any record-player you buy has provision for skating force correction and use it as the manufacturer suggests. It isn't just a sales gimmick!

A side issue of anti-skating tests concerns those broadcasters and other professionals who "back-cue" — the practice of placing the stylus in a groove and spinning the record backwards to pick up the start of a musical item. The skating force is then outward and adds to anti-skating correction to place a heavy load on the outer groove wall and the outer shoulder of the stylus. If the practice must be followed, there is good reason to reduce or even eliminate the anti-skating provision.

Another area for investigation concerned various measures that are adopted against clicks and plops produced by foreign particles in the grooves. They looked at nylon brushes, velvet cleaners, brushes using carbon fibres, roller type dust collectors and so on. Concerning these, Alexandrovich says:

"To clean dirty records, one has to exert a certain amount of force to remove dirt particles clinging to the surface of the vinyl. From all record cleaning devices, those with thicker shorter bristles did a much better job of removing debris collected even at the bottom of the groove. Because there are fewer bristles, pressure per bristle is even greater in this type of a cleaning brush and the job is done better. Combination of two types of bristles thick and thin, was advantageous for record cleaning before playing. Once the record has been cleaned and placed on the turntable, constant cleaning of the record with the brush attached to the cartridge or attached to the separate tone arm keeps the grooves clean.

"Devices using carbon fibers are too soft and if you divide the total force applied to the brush by the number of fibres, each fiber will exert pressure of less than 0.1 mg against the record surface. Needless to note, these devices are very good to remove any electrostatic charge when they are grounded but they do not remove nor attract dust like other ungrounded devices with heavier bristles.

"It is interesting to note that the brushes with thicker nylon fibers attract and collect dust as effectively as the thin fiber brushes. The action of such brushes is analogous to the moving magnet picking up iron filings and dragging a trail of them behind. Dust picked up electrostatically by the brush



Otari MTR-90 24-track

Of considerable potential interest to professional recordists is this new Otari 24-track unit, "designed for the 1980's" but currently available in Australia. Using standard 2-inch tape, it can operate at either 15 or 30ips, and with spools up to 14in diameter. The main capstan operates without a pinch roller from a direct-drive motor, servo controlled, to provide stepless speed variation within plus and minus 20%. The percentage figure is indicated on a digital display. Three other motors are included, two for spooling and one to operate the head shield. The heads themselves are mounted on plug-in blocks with easy access for azimuth adjustment. The MTR-90 has a range of operating facilities and performance specifications appropriate to the professional market. It is also available in a straight 16-track version, or in a hybrid version fitted for immediate 16-track use but pre-wired for easy conversion to 24-track. For further information, contact Klarion Enterprises Pty Ltd, 63 Kingsway, South Melbourne 3205.

is dragged behind in a similar manner."

Last but not least, Alexandrovich uncovered some fascinating evidence to do with the playing of discs when the surface had been deliberately wetted. An instinctive reaction would be to expect a reduction in groove wear because of lubrication of the surfaces.

In fact, the opposite appeared to be the case, with a thin film of water producing a quite unexpected deterioration of the vinyl in of the area of stylus contact.

The explanation appears to be that, under the pressure of a fast-moving stylus, the vinyl actually liquefies momentarily at the point of contact. The stylus therefore floats on this liquid film, which, of course, solidifies immediately afterwards.

The Author likens this to ice skating, where the metal blade does not really skate on ice at all, but on a very thin film of water, due to momentary melting of the ice. He points out that, if the temperature is too low for this to happen, one simply cannot skate!


Tests at Stanton Magnetics Inc. have shown a definite connection between ambient temperature and the tendency of the vinyl surface to tear under pressure at the point of stylus contact. It seems likely that the cooling effect of water on the groove surface prevents the vinyl from behaving in a liquid/elastic fashion, thus increasing rather than decreasing surface abrasion.



A new wow and flutter meter announced by Philips makes it possible for service technicians to check the performance of both video and audio cassette recorders, as well as phono turntables. Identified as type PM 6307, it can display drift and flutter on a pair of analog meters, each in 3 ranges and calibrated to 3%. Measurements can be made to DIN standard 45507 and a DIN socket on the front makes for easy connection to many of the units likely to be tested. It is possible to differentiate between mechanical and electrical faults. For further information: B. W. Druery, 15 Blue St, North Sydney, Tel: (02) 922 01081 Ext 246.

The most valuable link in your Hi-Fi chain.

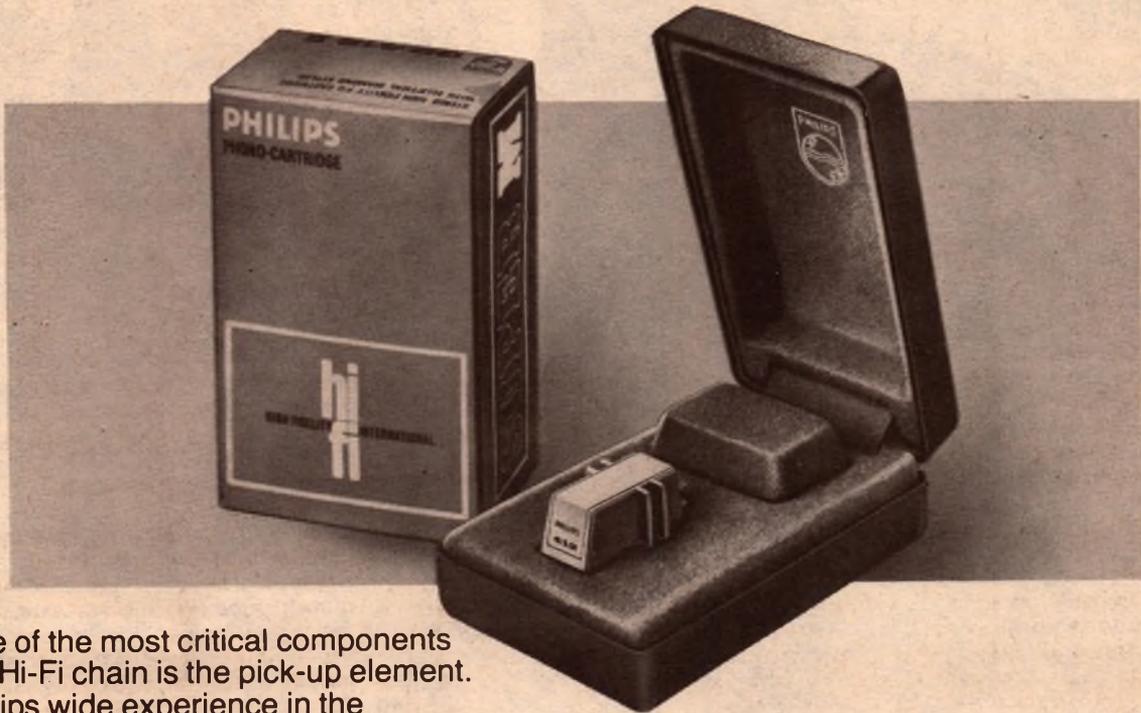Introducing the Philips Mark II range of Hi-Fi
magneto-dynamic pick-up cartridges.



One of the most critical components
in the Hi-Fi chain is the pick-up element.

Philips wide experience in the
manufacture of audio equipment plus
constant research in the fields of electro
mechanical construction and materials,
have made it possible to produce this
superb range of cartridges.

To whet your appetite, look at the
following specifications for the GP412II:

Frequency Response (Hz)	20-25,000
	±2dB
Output asymmetry at 1 kHz	< 1dB
Channel separations at 1 kHz	> 30dB
Frequency intermodulation distortion (at recommended stylus force)	< 0.7%

For further information, post the coupon
below to

Philips Central Service Division,
443 Concord Road,
RHODES NSW 2138

Or contact your local Philips Service Branch on:

Sydney 736 1233, Newcastle 61 1631,
Canberra 95 0321, Melbourne 699 2731,
Hobart 28 0121, Brisbane 221 5422,
Townsville 79 7422, Adelaide 223 4735,
Perth 322 4653.

Service
Service
Service

PHILIPS

Please send me further information on the
Philips Mark II range of Hi-Fi magneto-
dynamic pick-up cartridges:

Name

Position:

Company:

Address:

Telephone:

EA JUNE

McCANN 184.0012

AUDIO CONNECTORS


FERRIS: 45+45 FM AND TAPE STEREO FOR CARS



Called the MOFI — presumably a contraction of Motor-Fi — a new Ferris release comprises an FM/stereo tuner and an auto-eject cassette deck, plus a 45W per channel amplifier. Features include FM muting, S-meter, loudness control, bass and treble controls, and automatic play on the cassette deck. In this class of equipment, the MOFI is competitively priced at \$469. A range of loudspeaker systems to suit the MOFI are available from Ferris as additional items. For information: Mr J. J. Manneken, Ferris Audio Products, 42 Grantham St, West Brunswick, Vic 3055.

AMPEX Vice President G. J. Ziadeh, also general manager of the company's tape division, visited the Sydney plant recently. He revealed that the Ampex Corporation had developed their own version of the new metal particle tape which offered a saturation capability 10dB higher than normal gamma-ferric tapes at the top end, and 5dB better than the high-bias formulations. It will be offered first in audio cassettes but may not be freely available on the Australian market for another 12 to 18 months.

ALTAIR POWER ATTENUATOR. Incredible as it may seem, electronic musicians say that they prefer the sound of an overloaded output stage to the "fuzzbox" overload involving an input stage. The problem is that, even for them, the noise level from a powerful system at overload level is often too great. So Altair in America have produced their PW-5 "Power Attenuator". It connects between the amplifier and loudspeaker system and can be set to produce attenuation levels in 4dB steps from 4dB to 44dB. This lets the musicians enjoy the overload sound they prefer, without exceeding the desired (or legal) sound pressure levels.

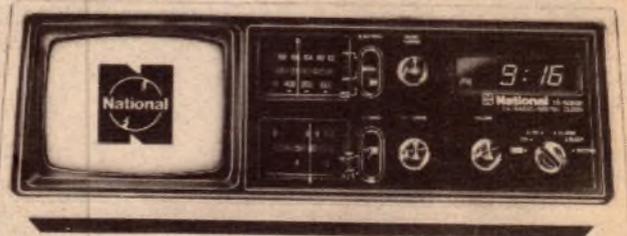

A most attractive item for bedside use is this new National Panasonic TR-5020A which combines a 13cm monochrome TV receiver with an AM/FM radio and digital clock. It has provision for a 60-minute automatic switch-off for the TV receiver — a "doze" switch — and an "alarm" function which can turn on the TV or radio at any preset time. The cabinet has a woodgrain finish. The TR502A should be available through a wide range of retail outlets at an RRP of \$245.00.

Neutrik has precision-engineered the world's most advanced XLR-Type Audio Connectors. These electro-mechanical components are Swiss-crafted to meet the demanding requirements of professional, industrial and commercial application. (Available in nickel finish with silver-plated pins or black finish with gold plated pins.)

NEUTRIK

"THE SWISS CONNECTION" from:

R.H. Cunningham
Pty. Ltd.

VIC. 493-499 Victoria St., West Melbourne.
Ph. 329 9633. N.S.W. 4-8 Waters Rd.,
Neutral Bay. Ph. 909 2388.

ZEPHYR PRODUCTS of 70 Batesford Rd, Chadstone 3148 advise that their well established 100EXR and 200EXR amplifiers have been replaced with new models designated as 2100 and 2200. Included now are protective relay circuits and LED displays which indicate watts output in terms of either 4 or 8-ohm loads. In addition, they have a new line of New Zealand made Perreaux equipment including a no-frills preamplifier model SP-50 and an 80W per channel integrated amplifier model SA80B. They draw on the same basic circuitry as the EXR series but with fewer facilities and at reduced cost.

METAL PARTICLE TAPE standards have reached the tentative agreement stage, following a conference of the Electronics Industry Association of Japan (EIAJ). By common consent, member companies have agreed not to talk about the technical details but final agreement is expected at the next meeting, followed by publication of the standards shortly afterwards. That could be anytime from now on.

3M AUSTRALIA PTY LTD are making available to technicians a "Wollensak" brand cassette recorder alignment kit, similar to those used in their American factory. The kit includes cassettes for: 1kHz reference level; 8kHz azimuth; 10kHz azimuth; 3kHz flutter (all these

are full track); head alignment gauge; Wollensak/3M torque cassette. The boxed kit costs \$150 and is indented from America as required. Inquiries: Mincom Division, 3M Australia Pty Ltd, 950 Pacific Highway, Pymble NSW 2073. Telephone (02) 498 0033.


PIONEER ELECTRONICS AUST PTY LTD are offering a new tone arm, the PA-5000, which should interest those who are fitting up a playing deck with separate motor and arm. The arm has all the characteristics expected of a top quality unit but also features a dynamic brake which is intended to flatten the "Q" of any resonance formed between arm and cartridge in the subsonic region. As a further step, it uses a magnesium alloy headshell, which combines very light weight with a carefully designed content of rigidity and internal loss. Tracking force can be adjusted in units of 50mg, height is adjustable, as also is the anti-skating force, which involves a modified method of application. While the new arm can be considered with any motor and deck, Pioneer say that it mates logically with their PLC-590 "armless" turntable and their PC-600 moving magnet stereo cartridge. Price of the arm alone is quoted as \$239. (Pioneer Electronics Australia Pty Ltd, 178-184 Boundary Rd, Braeside, Vic 3195. Tel. (03) 90 9011).

HIFI SHOWS IN FOUR CAPITALS

As indicated in our last issue, this month will see the first of four major hifi shows, each running from 12.00 noon to 10.00pm on Friday, 10.00am to 10.00pm on Saturday and 10.00am to 6.00pm on Sunday. Commencing dates

listed at \$3040.00. From there, systems and components range all the way down to the "under \$100" group, with Akai offering their HC 550 cleaning kit for tape heads and rollers for a modest \$5.95!

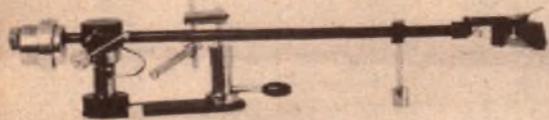Hundreds of hifi systems and components will be on show, including less widely advertised brands. At left: the Hadcock GH228 Super Arm. Below: The STD 305D turntable.



are: June 22 at the Sydney Chevron; July 27 at the Brisbane Park Royal Motor Inn; September 7 at the Melbourne Southern Cross Hotel; September 14 at the Adelaide Town House. (See advertisement elsewhere in this issue.)


Admission in all cases is free. As an additional attraction, those attending the shows will have the opportunity to win a complete Yamaha stereo system comprising a YP-D8 turntable, NS-69011 loudspeakers, CA-810 amplifier, TC-720 cassette deck, CT-810 tuner and YH-1000 headphones.

A very wide range of hifi products will be on show at all venues. Among the high budget items listed for likely showing is the Naim NAP250/NAC pre/power amplifiers, rated to deliver 70W RMS per channel from 20Hz to 20kHz with a THD of .001%. The price is



Rapar


PUBLIC ADDRESS AMPLIFIERS YOU CAN DEPEND ON

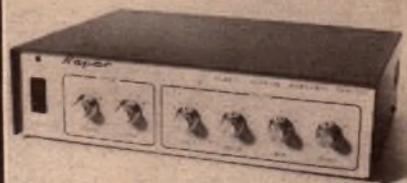

TPA 50

Specs.
RMS power, 25 watts. Frequency response: 50Hz to 15kHz (+3dB at 8 ohms). Multiple outputs: 4, 8 and 16 ohms. 70 and 100 volt lines. Inputs: Mic. 1, 47k ohms, Mic. 2, 600 ohms. Aux. 300mV, Phono 2.5mV.
Size: 310mm (width), 230mm (depth), 80mm (height). Weight 3.8 kilos. Finish: Durable two-tone baked enamel.

***\$146.97**

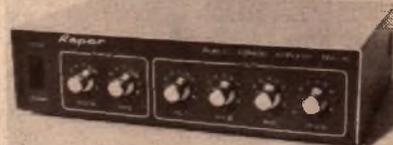

MODEL TPA 70

Specs.
RMS power, 50 watts. Frequency response: 50Hz to 15kHz (+3dB at 8 ohms). Multiple outputs: 4, 8, 16 ohms, 70 and 100 volt lines. Inputs: Mic. 1, 47k ohms, Mic. 2, 600 ohms, Aux. 300mV, Phono 2.5mV.
Size: 310mm (width), 230mm (depth), 80mm (height). Weight: 4.3 kilos. Finish: Durable two-tone baked enamel.

***\$182.50**

TRADE AND DISTRIBUTOR ENQUIRIES WELCOME

MANUFACTURED BY:

RADIO PARTS GROUP



562 SPENCER STREET,
WEST MELBOURNE, VIC. 3003.
TEL. (03) 329-7888.

1103 DANDENONG ROAD,
EAST MALVERN, VIC. 3145.
TEL. (03) 211-8122.

D.I. SERIES

P.A. AMPLIFIERS

NOW FIRST CHOICE FOR SYSTEM
INSTALLERS THROUGHOUT
AUSTRALIA



Compare these technical features:—

- XLR microphone sockets.
- Balanced low impedance microphone inputs.
- Separate bass and treble controls.
- Constant voltage and multi-tap low impedance outputs.
- Master gain control.
- Self contained or rack mounting

LOW COST

35 watt	\$177.00
60 watt	\$220.00
100 watt	\$266.00

from the BOGEN people

AUDIO TELEX COMMUNICATIONS PTY. LTD.

SYDNEY

54 Alfred St.,
Milsons Pt, 2061
Tel: 929 9848

MELBOURNE

7 Essex Rd.
Mt Waverley 3149
Tel 277 5311

BRISBANE

394 Montague Rd.
West End, 4101
Tel: 44 6328

ADELAIDE

Werner Industries,
Unit 5, 28 Gray St.,
Kilkenny, 5009
Tel: 268 2801

PERTH

Electro Acoustic Co. Video & Sound
55 Frobisher St., Services
Osborne Park, 6017 11-13 Andrew St.,
Tel: 444 8688 North Hobart, 7000
Tel: 34 1180

NEW ZEALAND

Direct Imports.
PO Box 72 Hastings.
Tel 8 9184

TRADE ENQUIRIES INVITED



AUDIO TALK

by LEO SIMPSON

Rumble — a problem of measurement

Ever wonder why we do not quote specific figures for rumble when we do turntable reviews? The reason is that the rumble of modern belt-drive and direct-drive turntables is so low that it is difficult, if not impossible, to measure.

Typical records bought over the counter may have considerable more rumble content than the turntable you use to play them, although only the dedicated hifi enthusiast may notice it. This rumble on records takes several forms. The first and perhaps most easily identifiable, is recorded rumble, ie, rumble appearing on the original master tapes.

Recorded rumble such as this may be due to a number of sources at the site of recording. It may be due to seismic disturbance such as traffic noise and underground railways. Closer to hand, it may be due to noise from elevators or other heavy machinery vibration in the same building as the studio. Most (but not all) studios would be reasonably well isolated from these sources of low frequency vibration, but they can still show up on recordings.

Further down the recording chain, the rumble may be induced into the record at the master cutting stage. Inevitably, quality standards vary from company to company, so that some recording lathes will have more bearing rumble than others.

More rumble is introduced at the pressing stage. Called "pressing rumble" (what else?) this is inherent in the way the vinyl flows into the tightly constricted space between the two steam/heated platens. The way the plastic flows and subsequently cools inevitably places a more or less random rumble "imprint" on each disc pressing.

Before readers become concerned at the degrading effects of all this rumble, let me state that none of these effects is audible during normal listening. Where it might become audible is during critical listening with loudspeakers or headphones having an extended bass response and with volume levels high. Even then the rumble is only likely to

be noticeable during quiet passages.

Now that you have all resolved to listen out for this defect, I will tell you how to distinguish some of the rumble. Recorded rumble present on master tapes will not be present during the lead-in and lead-out grooves, or between tracks. The same can be said of tape hiss. Any other rumble present in the system is due to the recording lathe used to make the master, pressing rumble or (horror of horrors) your own treasured turntable.

How do you tell if the rumble is predominantly due to the turntable? Well have a critical listen to a variety of records, preferably using good quality headphones. This enables you to block out extraneous ambient noise, assuming the headphones have good acoustic isolation. Secondly, headphones avoid confusing the issue with low frequency acoustic feedback.

Having listened critically to a number of records you should find that the rumble content varies from record to record and even from track to track. But if the rumble appears to be constant in tenor then perhaps it is predominantly due to your turntable.

Before concluding the worst about your turntable, it is wise to look further. Have a listen to the system with the stylus on the record but the platter stationary. In all likelihood, this may indicate that the supposed rumble is coming from the amplifier on the same shelf or in the same cabinet (transformer vibration). Or perhaps it is due to the air pump for your fish-tank, the fan for the oil heater or your next-door neighbour's air-conditioner.

What a can of worms we have opened here! At least, if you do find that "rumble" in your system is originating from other sources, you can try improving the acoustic isolation of your turntable. Some turntables have much better acoustic isolation than others. But if you think the problems of totally eliminating rumble in domestic situation are difficult, consider the problems of making accurate measurements in the laboratory

situation.

Even when I have made allowances for all these external sources of rumble and have achieved a system measurement signal-to-noise ratio of around 70 to 80dB with respect to a 10 millivolt signal, there is still a problem. Where do you get a source of quiet, unmodulated grooves? Test records are immediately suspect — they are just as prone to rumble as ordinary records, although they are probably subject to better quality control.

So most test record pressings can be regarded with a jaundiced eye, as far as rumble testing is concerned — although possibly some discs are quite good in this respect. We use an acetate disc which has been selected for a high degree of flatness and cut on a very well maintained recording lathe. Is it completely free of rumble? To that I must answer, "I dunno".

There is no reason to believe that even the best recording lathes have appreciably less rumble than the best turntables. So there is "even less" reason to believe that the rumble on our acetate disc is at least 10dB less than the rumble on one of today's excellent turntables. This condition has to be met before we can quote a rumble measurement which means anything.

Some readers may ask, "Well, why not test the turntable using a recording blank, with no grooves in it, at all?". Alas, that does not work either because the stylus typically generates a lot more noise of its own when playing a blank disc than it does when playing unmodulated grooves. We're not too sure why this happens, but it does.

So where does that leave us as far as quantitative rumble tests are concerned? Right up the proverbial creek without a paddle (or variations on that theme).

All that we can do is to check turntable for rumble and see that it gives a result which is objectively and subjectively low. Then we can state, fairly, that rumble is (qualitatively) low. And make no mistake, rumble on most belt-drive and direct drive turntables is very low. But with the current state of test equipment available we do not feel confident in quoting a quantitative result.

Some, if not most, manufacturers quote very low figures for their turntable rumble (mostly a DIN standard measurement). How do they measure it? That is an interesting question . . .

THE "ELECTRONICS AUSTRALIA"

LOG BOOK

FOR: RADIO AMATEURS
DX LISTENERS
CB OPERATORS

\$2.95

From "Electronics Australia", 57-59 Regent St. Sydney OR by mail order from PO Box 163, Beaconsfield 2014. Price includes postage.

Soldering printed circuits?


The Duotemp soldering tool will idle all day on half-wave AC without overheating.



A touch of the button converts it to full wave, instantly doubling the thermal capacity

- Correct temperature for printed circuits.
- Fast heat-up and heat recovery.
- Power boost for long sequences or heavy joints.

MODEL D30	3mm tip
MODEL D50	5mm tip
MODEL D65	6.5mm tip

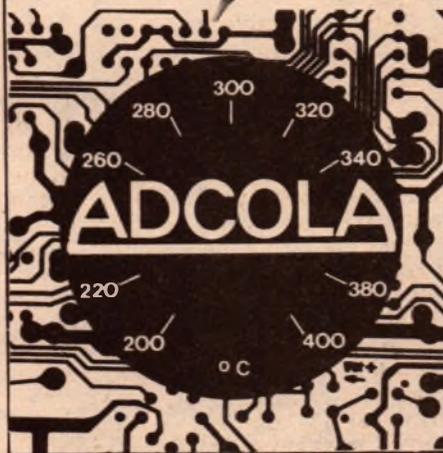

DUOTEMP

A new standard in soldering tools — by Adcola.

The Duotemp protects circuits and components at a cost far lower than soldering tools with automatic temperature control.

For electronic feedback temperature control please call for brochure for 'THERMATIC' line voltage, or 'ECT' super sensitive and powerful low voltage soldering systems.

FROM YOUR
ELECTRONIC PARTS SUPPLIER
or enquire from

ADCOLA PRODUCTS

Melbourne 848 3777 Sydney 709 5293
Brisbane 44 0131 Adelaide 42 6655
Hobart 34 2233 Launceston 31 2511
A781 Perth 381 5500

TASMAN ELECTRONICS

12 Victoria Street, Coburg 3058. Phone (03) 354 5062

FOR TOP QUALITY COMPONENTS
AT ROCK BOTTOM PRICES

Transistors & ICs, resistors, capacitors, transformers, switches, wire and cable, diodes, bridges, SCRs, triacs, audio and TV leads, plugs and sockets, power supplies & adaptors, stylii, DMMs, calculators, instrument cases and boxes, knobs, heat sinks, fuses, cassettes, batteries, TV antennas, musical instruments and accessories, etc, etc.

We are also dealers for "AIWA" quality hi-fi products.



A splendid performance....

deserves a splendid performer

Priced at around \$350.



The TEAC A-300 is a surprisingly affordable 3-head cassette deck that really gets down to business when it comes to reproduction performance. The reason is an exceptionally stable transport system.

With three heads, the requirements for tape-to-head contact, flutter and tape speed stability are critical.

An inferior transport can actually result in reduced recording and playback quality—even though the unit may boast independent erase, record and playback heads.

That's why we put so much effort into making sure that the A-300 transport complements the three-head system perfectly.

We even went so far as to add a mechanical tension servo in the tape path between the supply reel and heads to assure optimum tape-to-head contact from the beginning to end of every reel.

Technically, the result is improved recording efficiency and extended frequency response with playback level fluctuation and dropouts virtually eliminated.

To you, it simply means stunning sound quality plus the convenience of real-time monitoring.

You can even monitor your tapes Dolby-decoded as you record,

since the A-300 has a double Dolby NR system—four processors instead of the usual two.

And there's a whole list of other features that make recording more convenient and enjoyable.

Try a TEAC A-300, and find out what 3-head reproduction is really all about.

TEAC AUSTRALIA PTY. LTD., 165 Gladstone Street, South Melbourne, Vic. 3205. Telephone: 699 6000.
INTERSTATE AGENTS: BTS Sales, 66 Dickson Ave., Artarmon, NSW. 2064. Phone 439 6262. BTS Sales, 51 Norma Rd., Myaree, WA. 6154. Phone: 330 1255. BTS Sales, 91 Robertson Rd., Fortitude Valley, QLD. 4006. Phone: 52 8900. P.G.A. Associates Pty. Ltd., 62 Hindmarsh Sq. Adelaide, SA. 5000. Phone: 223 3024.
RETAILERS: VIC. Brash's, Douglas Hi-Fi, QLD. Stereo Supplies, NSW. Douglas Hi-Fi, Miranda Hi-Fi, Autel Sales, Hamilton Hi-Fi Centre, Newcastle, SA. Truscott Electronics, WA. Albert's Hi-Fi, Audio Centre, A.D. Urquhart, TAS. Quantum Electronics, Hobart, United Electronics, Launceston, Audio Services, Burnie, ACT. Kent Hi-Fi, NORFOLK ISLAND Miltons Department Stores.

(LEA)3051

TEAC
Where Art and Technology Meet

"Dolby" is a trademark of Dolby Laboratories.

Teac A-300 3-head stereo cassette deck

Following the introduction of the highly successful A-107 cassette deck which we reviewed in August 1978. Teac have now introduced a 3-head version at what must be regarded as a very attractive price. As well as having all the features of the A-107, the new A-300 also has mic/line mixing.

At first sight, the new Teac A-300 looks a "dead ringer" for the 2-head A-107 machine referred to above. The A-300 has exactly the same control layout, the same number of knobs and switches and the same overall dimensions. Only a closer look reveals that the type number, A-300, and the control labelling is different.

In fact, apart from the fact that the cassette compartment lid is labelled "Three Head System", there is absolutely nothing to indicate that the machine actually has three heads. Even a glance inside the cassette compartment only reveals two heads, leading to the exclamation "Hey, where is the third head?"

With the cassette compartment lid removed for closer examination, no third head is suddenly revealed to verify the third head claim; the machine appears to have a normal record-play head just like any other conventional stereo cassette deck. Hmm ...

What Teac have actually managed to do is to build two separate stereo tape heads within the one case, so that the

result looks just like a normal two-head set-up. This avoids having to poke a third head into a part of the cassette which was never intended for that purpose, and means that the same transport can be used as on the other conventional decks in the range. Clever, cunning Teac!

Teac have yet to tell the story of how they managed to fit two heads into the one case, and perhaps they will not do so. But it would be interesting to know whether there was any compromise to know whether there was any compromise in performance involved with the necessarily different head structure. Perhaps we will have to draw our own conclusions from the results of our performance tests.

As far as the transport is concerned, it provides the same functions as in the A-107 and related A-100 series models. Seven piano levers control the mechanism. They work well and only require moderate pressure.

The A-300 may be set up initially for recording by first depressing the Pause button and then pressing the Record and Playback levers. There is a trick to


this, as we found with the A-107: the Record lever must first be fully depressed and then held down while the Playback lever is pressed down. This locks the transport into the recording mode.

Apart from this wrinkle, the transport works very well and is particularly quiet at all times. Like most other decks it has automatic stop at the end of tape travel in all modes, and also features "memory" rewind whereby the tape can be rewound to a preset "000" on the tape counter and then stop. Rewind time for a C-60 cassette was about 76 seconds.


Recording facilities on the A-300 are improved compared to those on the A-107. Whereas the A-107 gave a choice between recording from microphones or line inputs, the A-300 enables mixing from both these sources for much more flexible recording. The microphone and line input controls use two concentric knobs with both halves (of each pair) clutched together for normal operation.

The two level meters have easily readable calibrations and characteristics which appear to be similar to those of VU meters. Unfortunately, the accuracy of the calibrations is none too precise, particularly at the low end of the scale.

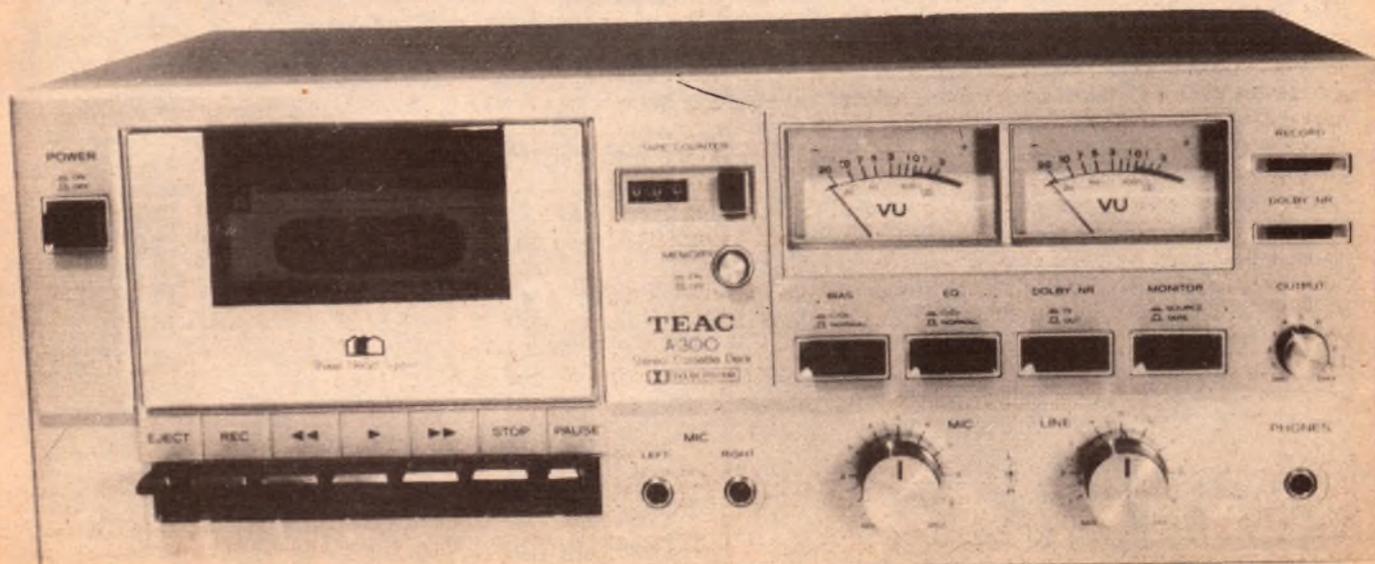We would have preferred to see some sort of overload indicators in ad-



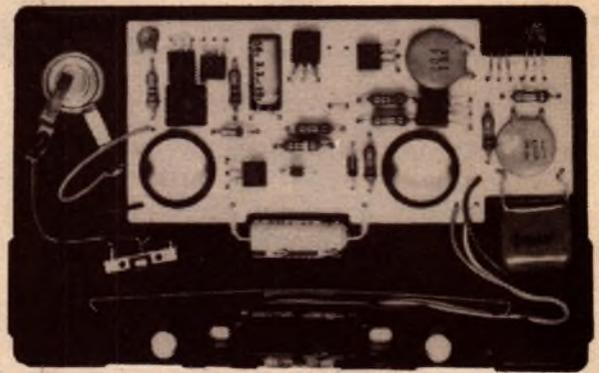TDK's Revolutionary New Product — The HD-01 Head Demagnetizer Built into a Cassette Shell.




Simply load the HD-01 into any cassette recorder as you would a standard audio cassette and depress the 'play' button.

The HD-01 Head Demagnetizer was designed by TDK for easy, convenient head demagnetization of any cassette deck, insuring crystal-clear, perfect recordings every time.

The TDK HD-01 Head Demagnetizer features:

- A unique cassette format, designed to insure complete compatibility with any cassette deck.
- Powerful de-gaussing circuit instantly demagnetizes recorder heads the moment the play button is depressed. The above diagram depicts the oscillating waveform applied to the recorder heads, removing every trace of residual magnetism in only one second!
- A red LED (Light Emitting Diode) built into the HD-01 cassette shell will light up the moment your recorder heads have been completely demagnetized.

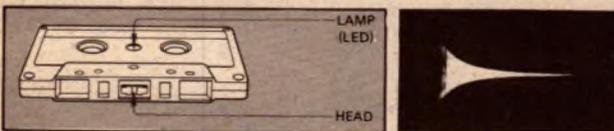

The TDK HD-01 Head Demagnetizer ends forever the fuss and mystique surrounding the demagnetization process and is much easier to use than conventional wand-type tools. Anyone can use the HD-01 and get perfect results every time.

The TDK HD-01 Head Demagnetizer is completely self-contained, battery operated and portable. It can be taken anywhere and stored with your present audio cassettes. The TDK HD-01 is ideal for all types of cassette decks especially those with heads located in hard to get at places such as:

- recorders with heads positioned in the front of the unit but which point to the rear.
- those with 'pop up' loading mechanisms which can not be detached, thus making the heads almost inaccessible.
- cassette decks with heads positioned laterally with respect to cassette loading (car decks are good example of this type).
- automatic loading machines.


WHY IS DEMAGNETIZING SO IMPORTANT?

TDK, in conjunction with many cassette deck manufacturers, recommend that cassette decks be maintained on a regular basis. Cleaning the heads, capstan and pinch rollers is one important aspect of that maintenance program. — Periodic demagnetizing, about every thirty hours of use, is the other. Failure to do so will cause a build-up residual magnetism on the heads, which can seriously affect tape and machine performance in the following critical areas:

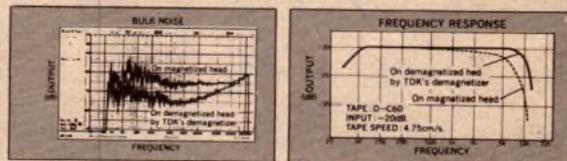1. The noise level in the low and midrange frequencies is increased by 5 to 7dB, thereby reducing the overall signal-to-noise ratio.
2. Pre-recorded tapes can also be affected with midrange and high frequency distortion, as well as attenuation by as much as 2 to 6 dB, virtually eliminating any hopes for clear sound reproduction.

The interaction of these factors will not only prevent both the tape deck and tape from displaying their true performance capabilities, but will severely limit the Dynamic Range properties of both, rendering pure sound reproduction an impossibility.

The following comparison data clearly demonstrates the effect of residual magnetism on recorder heads in the areas of both Noise Level and Frequency Response.



TECHNICAL DATA


Major Components:

- Transistors (8)
- Diodes (2)
- LED (Light Emitting Diode)

Power Supply — Control Section — Oscillation Section — Head Section

Specifications:

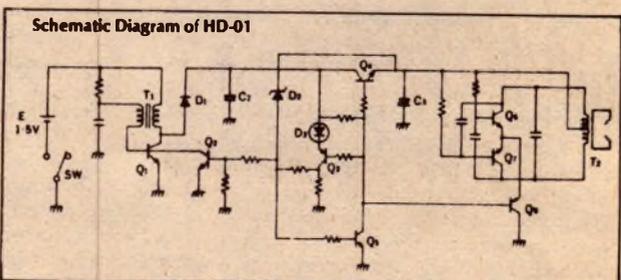- Maximum Magnetic Flux Density 200 Gauss
- Oscillation Frequency 630 Hz
- Shape (External Dimensions) Conform to IEC Standards
- Battery for Power Supply G-13 1.5 volt, Silver Oxide Battery (option)



For additional information, direct all inquiries to:

TDK AUSTRALIA PTY LTD
4 Dowling Street, Woolloomooloo, N.S.W. 2011
Telephone: (02) 358-2088. Telex: AA23111



TEAC A-300

dition to the meters, which are relatively slow in their response. There are two lamp indicators, one for the recording function and the other to show that Dolby is in use.

The four bar-shaped pushbuttons on the front panel provide the following functions: Bias, Equalisation, Dolby Noise-reduction and Monitor. The last named function allows monitoring of the Source being recorded or the signal off the tape, via the third (playback) head. The output level to the line sockets is controlled by a small knob at the right hand side of the panel. This does not affect the drive level to the headphone socket.

Sockets of 6.5mm are provided for stereo headphones and two low impedance microphones (600 ohms or more). The rear panel is bare except for the four RCA sockets and accompanying DIN socket.

Removing the cover of the A-300 reveals many similarities to, but quite a few differences from the A-107 model. The compact transport mechanism is virtually identical except for extra sets of contacts for the Pause function. The transport employs a single DC motor with tachometric feedback. It drives the capstan via a flat belt.

One of the interesting features of the A-300 transport is the eject mechanism. This controls the speed of opening of the cassette compartment lid via a gear driven flywheel system. This works quietly and well.

While most readers would regard the interior of the sample A-300 we reviewed as being relatively uncluttered and tidy, the model which will actually be on sale to the Australian public is even tidier. The model we reviewed is the Teac "general export" model which has a crude and rather dangerous PCB and slide system for selection of mains voltage. The Australian model does not have a multi-tap primary winding on the transformer, and thus no voltage selector.

One point which did cause some concern was a couple of loose screws in a bracket which retains the meters. We did not notice this fault until after the photographs were taken. We hope that this does not indicate a lack of vigilance in Teac quality control. Admittedly our review sample was probably a demonstration model which has been rattled around much of Australia.

One major difference is to be expected between the A-300 under review and the A-107 and that concerns the main PCB. While the main PCB on the A-300 is only slightly larger (wider) than the PCB in the A-107 and accommodates roughly twice as much circuitry, the switching is considerably less complicated.

This is because the A-300 uses com-

pletely separate circuitry for the recording and replay functions, while most conventional two-head machines use the same circuitry for both functions. This latter approach involves virtually turning the record-play amplifier inside-out by using a large multi-contact switch to switch bias, equalisation, inputs and outputs. The A-300 does away with all of that so that its recording switch is very small and mainly controls the bias and erase oscillator. So even though the A-300 has considerably more circuitry, the absence of complicated switching must be an aid to reliability. Anyway, its certainly more appealing from an engineering point of view.

One feature which we would have liked to see in this three-head machine is the facility for optimising bias to suit

within ± 2.5 dB from 30Hz to 15kHz, but nowhere near as flat when Dolby was switched in. With TDK SA tape the frequency response was within ± 3 dB from 30Hz to 15kHz and although the response with Dolby changed, it remained within the same limits.

Frequency response above 15kHz is heavily attenuated by the inbuilt 19kHz filter.

Harmonic distortion was reasonably low, the figures at OVU being 1.1% at 100Hz, 1.5% at 1kHz and 1.5% at 10kHz.

Unweighted signal-to-noise ratio without Dolby applied was 48dB. With Dolby applied, this figure improved to 50dB, which does not reflect the increased improvement at the high frequency end. In fact, most of the noise from the A-300 is of a low frequency nature which means that subjectively, the unit is very quiet.

Wow and flutter checked out at around 0.15% according to the DIN 45507 measurement.

Overall sound quality on playback is



particular tapes. This is relatively easy to provide on this sort of deck. Still, we have to acknowledge that the machine is very competitively priced.

The instruction manual is written in no less than five languages and since these are all laid out across each two-page spread, it is a little confusing to read. But we do approve of the fact that the circuit diagram is included in the manual.

Bias and equalisation settings for a total of 18 different tape types are given in a handy chart form at the front of the manual. This is another good feature of the manual.

Our tests of the A-300 indicate that while it is well-designed and has a high degree of running refinement, its electrical performance is not quite up to the mark of the A-107. Frequency response with BASF Cr02 tape was

good without Dolby, although some tape hiss is noticeable. With Dolby applied, the hiss largely disappears although the high frequency response suffers to a small degree.

In spite of our conclusion that the electrical performance of the Teac A-300 is not quite up to the mark set by the A-107 model we reviewed in August 1978, our overall reaction to the A-300 is enthusiastic. It is a three-head machine offering just about all the facilities which most people are likely to want, at a very keen price. Recommended retail price is \$314, including sales tax.

Further information on the Teac A-300 can be obtained from high fidelity retailers or from the Australian distributors, Teac Australia Pty Ltd, 165 Gladstone Street, South Melbourne, Victoria. (L.D.S.)

Sennheiser HD420 & HD430 dynamic Headphones

The well known range of Sennheiser headphones has recently been augmented by the addition of two new models designated as HD420 and HD430. Both use the so-called "Open-Aire" approach and both are dynamics of 600 ohms nominal impedance, suitable for a wide range of applications.

At the lower end of the existing Sennheiser range of dynamic headphones is the AD400, styled like a stethoscope and retailing for \$38. At the top end is the HD224X, using fully enclosed drive units and selling for \$122.50. The new HD420 is listed at \$75.50, while the HD430 is listed at \$110. At that figure, it becomes the most expensive of the open-back types.

Taking first the HD420s, the immediate impression is one of excellent design and workmanship, resulting in phones which look substantial without being cumbersome.

The drive units are mounted inside a spoked framework moulded from matte black plastic. They are faced with a cushion of gold, velvet-like material, while a further open weave layer occupies the space between the spokes at the rear.

Because of this "Open-Aire" construction, listening may be less "private" that might otherwise be the case. However, Sennheiser claim that it provides a more natural listening environment, with the sound source being less obviously clamped to the head.

The connecting cables look conventional but actually attach to the phones by means of small but stout polarised plugs. The phones are normally supplied with 3m cables having a 6.3mm stereo jack-plug termination, but they are also available with unterminated cord or with DIN multiplug connector. The literature mentions a variety of other accessories, such as a 3 or 6-channel junction box, chain connectors for 10 or 30 pairs of phones and cables with inbuilt volume/balance controls.

Manufacturer's data quotes the weight of the phones without cables as 129g, the frequency response as 18-20,000Hz (no dB reference), distortion as less than 1.0% (DIN 45500) and sound pressure level at 94dB (1mW input at 1kHz).


The headband has an outer arc of spring steel which presses the phones

inwards against the ears and, being hinged, they automatically assume the correct angle. Inside the spring steel arc is a soft strap which can be slid up or down as necessary to support the phones at the appropriate level. Once adjusted, the phones sit firmly but comfortably in place.

Observed on a range of program material, the sound is clean and well

The more expensive model, HD430, is of generally similar construction but with the obvious difference that the phones carry pads which surround the ears, rather than cushions which rest directly on them. Sennheiser stress, however, that the phones still qualify as "Open-Aire" types, because the back is open and accessible to normal room ambience.

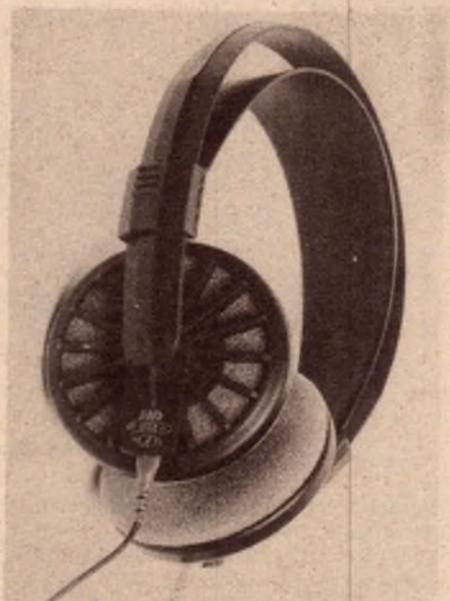Specifications of the HD430 are marginally higher than those of the HD420 but we doubt that too many would notice any significant difference in the subjective sound quality. The bass was judged to have a slightly more "shut in" sound and the upper middles to be slightly more restrained. But, again, these are niggling observations



On the left, the HD420 and, on the right, the HD430 phones.

balanced. While the drivers are not sealed against the head, the bass is nevertheless firm and subjectively equivalent to what one would expect to hear from the same material quality loudspeakers.

There is a slight tendency to emphasise speech sibilants in the range around 4kHz, but it is much less apparent than with many other phones. To many listeners, the effect will merely tend to increase the "presence" of both speech and music; overall, they should be very easy-to-live-with phones.

about a product that would be very easy to live with.



At 190g, the HD430 phones are heavier and the pads make them look larger. But we know from experience that some prefer phones to be built this way, finding pressure on the skull less objectionable than on the pinna. It's very much a subjective reaction, which we leave with the individual.

For further details: R. H. Cunningham Pty Ltd, PO Box 453 Melbourne 3001. Or PO Box 214, Neutral Bay Junction, NSW 2089. (W.N.W.)

Hi-Fi storage when and where you want it, in real Pine...


Unit (below) consists of:
2 x 78cm sideframes,
4 x 46cm Shelves,
and a cross brace.
Complete at only

\$58

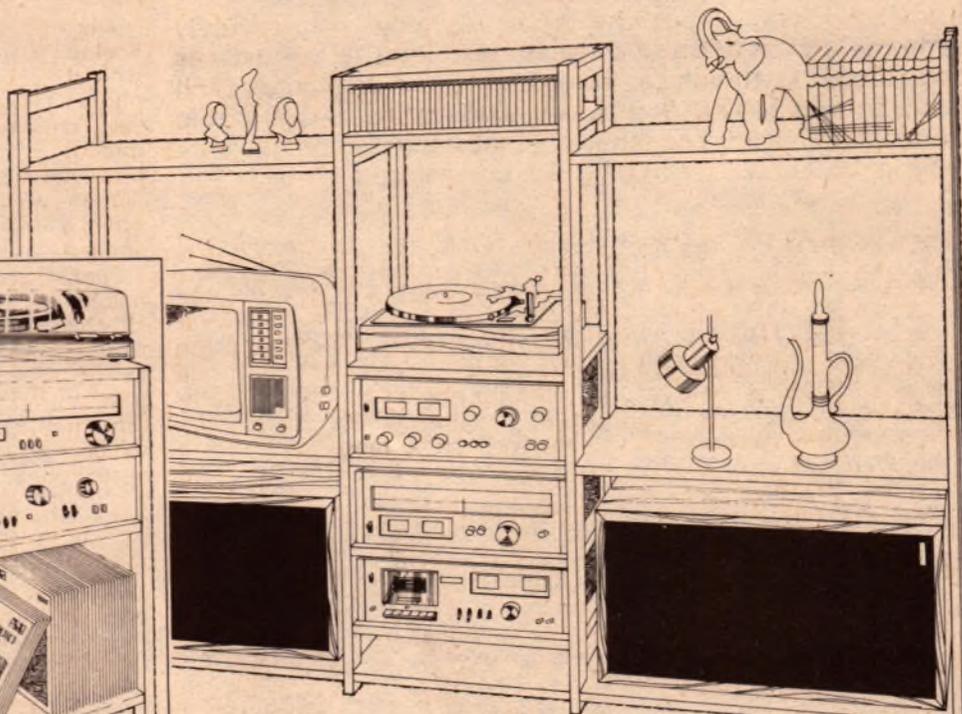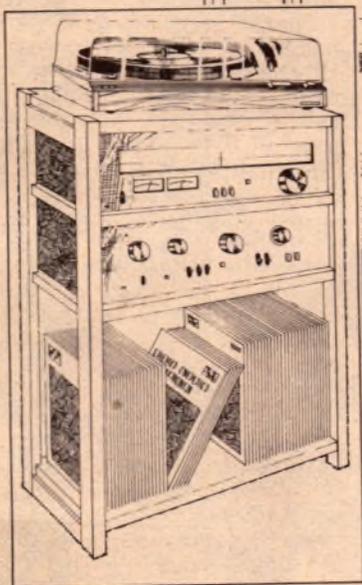

Unit (above) consists of: 4 x 128cm sideframes,
6 x 80cm shelves, 7 x 46cm shelves, and a cross
brace. Complete at only

\$194

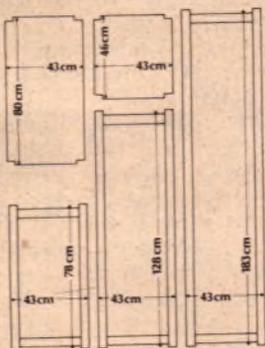

Create your own individual storage system. Pine Plus is freestanding and comes in two depths, three heights, four lengths. The 3/4" thick real timber shelves are adjustable every two inches. Start with a basic unit then . . . as your needs grow, add corner shelves, tidy boxes, drawers and cupboards. Think of the possibilities . . . under windows — around beds, difficult corners or fireplaces.

See how economical the PINE PLUS solid timber system is at these stockists. Some open weekends, phone first.

- | | |
|-------------------|---|
| NSW: ST. LEONARDS | Freeform Furniture, 174 Pacific Hwy., Ph: 43 1958 |
| ALEXANDRIA | Freeform Warehouse, 26 Mitchell Rd., Ph: 699 4897 |
| BONDI JUNCTION | Mark Eaton's, 89 Oxford St., Ph: 389 6738 |
| ACT BELCONNEN | Whitewood Warehouse, Cohen St., Ph: 51 4474 |
| VIC HAMPTON | Precedence, 421 Hampton St., Ph: 598 7643 |
| QLD HERMIT PARK | Easibild, 120B Charles Towers Rd., Ph: 71 3876 |
| SA Nth ADELAIDE | Concept, 24 O'Connell St., Ph: 267 4808 |

PINE PLUS

We specialise in direct and economical delivery anywhere in Australia. So if you are not within reach of a stockist, contact us for brochures, price list and direct delivery.

INVICTUS TRADING CO. P/L.
BOX 521 P.O. LANE COVE 2066. PHONE 428 4173

An electronic combination lock

Give your home, flat or office increased security with this space-age electronic combination lock. Low in price and easy to build, it can be programmed to respond to any desired seven-digit code. This means that an intruder or other unauthorised person has only one chance in 10,000,000 of finding the correct code!

by RON DE JONG

Here is a new electronic combination lock design which we think should become very popular. It offers the security of more complex designs with the simplicity and low cost of simpler and less secure circuits. You can fit it fairly easily to almost any home, flat or office front door, and it can even be fitted with multiple input keyboards if you wish.

The actual code combination to which the lock responds is set by seven wire programming links inside the lock case — which is separate from the entry keyboard, for both convenience and security. While not normally accessible,

the same time leaving no indication of what the code may be. The lock circuit is arranged so that the only way to release the door latch is to enter the correct code digits in the correct order, and with no false digits between them. Any false digits will immediately cause the circuit to reset, even if some correct digits were keyed in.

Like most electronic combination locks, the unit is designed to activate an electric latch release mechanism of the type commonly used in flats and home units. This type of latch release can be used in conjunction with an ordinary key-activated door latch, in place of the

can use the latter arrangement by itself, so that the combination lock provides the sole means of gaining entry from the outside. The only problem with both of these arrangements is that in the event of a power failure, it can be very difficult to gain entry!

Assuming mains failure is not regarded as a problem, you could also use this combination lock with two keyboards — one on the inside and one on the outside of the door. This will give a "deadlock" effect, so that even if illegal entry is made via a window or other means, stolen items cannot be moved out by opening the door from the inside.


The electronic part of the lock uses only seven inexpensive CMOS integrated circuits and a transistor, all powered from a simple 12V supply. But the simplicity of the circuit belies its performance.

The easiest way of following circuit operation is to divide it into two distinct functional parts: the keyboard scanner and the code verification circuits.

At the centre of the keyboard scanner section is IC6, a 4017 decade counter with internally decoded outputs. This is driven by a clock oscillator formed by gates IC4b, IC4c and IC4a, and the oscillator is normally free-running at about 1kHz.

Each of the ten output lines of the counter is connected via the keyboard switches to the input of gate IC5b. This in turn is used to control the clock oscillator. As a result if any of the keys is pressed, the clock oscillator is disabled by IC5b as soon as the corresponding output of the counter goes high — which will happen within ten milliseconds. The counter will thus stop with the output line which corresponds to the pressed key held in the high state.

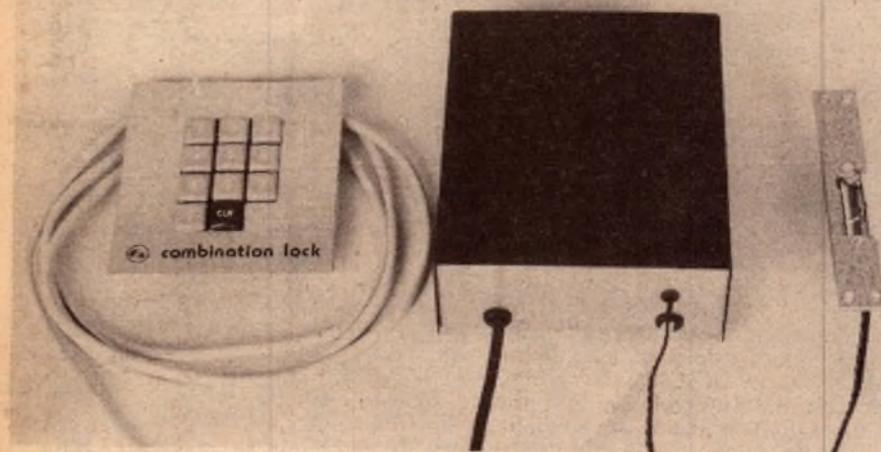As well as being used to stop the keyboard scanning clock, the output from IC5b is also processed by IC5d and




The completed unit together with the keypad and the door latch mechanism.

the links can be changed at any time if desired, if you suspect that the code has become known to any unauthorised person. The code may be set to any desired combination of seven decimal digits — giving a total of 10,000,000 possibilities to choose from!

In use, the lock is triggered by entering in the code digits via a small keyboard whose keys are labelled 0-9. This provides elegant and fast entry, at

usual fixed striker plate. If this is done, you can gain entry by using either the combination lock or the normal key.

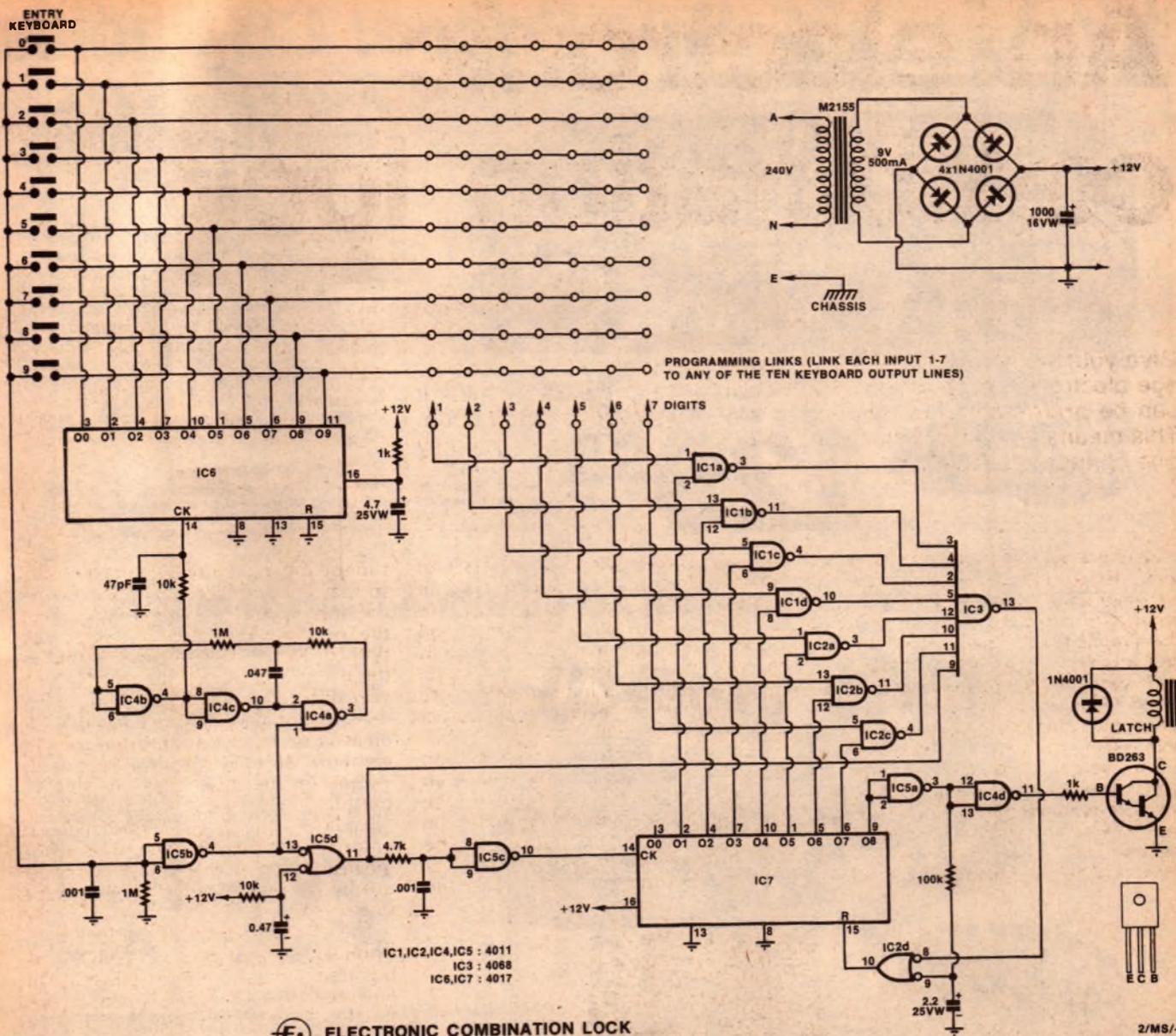You can of course use the combination lock and release mechanism quite separately from the normal key-operated latch, to provide additional security. In this case it would probably be used with an "exit latch" door bolt, which can otherwise only be opened from the inside by a turn unit. Or you



E-A ELECTRONIC COMBINATION LOCK

2/MS/-

Seven low-cost ICs make up the circuit; programming links are added to make up the desired 7-digit code.

IC5c to produce two "key pressed" strobe signals for the code verification circuitry. The 4.7k/.001uF combination between IC5d and IC5c ensures that the signal from IC5c is slightly delayed with respect to that from IC5d, as this is required by the verification circuit.

The main reason for using this keyboard scanning circuit is to ensure that only one output line goes high, no matter how many keys may be pressed simultaneously. This is because the 4017 can only have one of its outputs high at any particular time. As a result, it becomes impossible to "fool" the code verification circuit by pressing all keys down at once.

A further advantage of the scanning approach is that the .001uF capacitor and 1M resistor at the input of IC5b effectively debounce all of the keyswitches at once.

finally released, IC6 does not immediately revert to scanning the keyboard again: there is a short delay. Partly this delay is due to the .001uF/1M combination at the input of IC5b, which produces a delay of around 1ms before the input of IC5b falls to logic low, its output rises to logic high and the clock oscillator is allowed to restart.

The remainder of the delay is produced because the input of IC6 is driven from the output of IC4b in the clock oscillator, rather than from the more usual point at the output of IC4a. As a result when the clock oscillator restarts there is a half-cycle delay before the input of IC6 receives its first positive-going clock transition. Since IC6 is triggered only by positive-going clock edges, this ensures that the output of IC6 remains "frozen" for approximately 1.5ms after the release of the keyswitch.

the "key pressed" strobe signals, IC5d and IC5c are also used to generate a similar pair of pulses when power is first applied to the lock circuit. These pulses are generated by the 10k/4.7uF combination connected to the second input of IC5d, and are used to initialise the code verification circuitry.

The code verification section of the circuit takes the consecutive outputs from the keyboard scanning section, as a series of keys are pressed, and checks if the correct keys have been pressed in the programmed sequence. Only if the sequence is correct in all respects does it finally activate the latch release mechanism.

This section of the circuit is again based on a 4017 decoded decade counter device, IC7. In broad terms the circuit works by starting with the counter in the zero state, and incrementing it by one count for every correct digit entered in its correct position in the

When the key which was pressed is

Note that in addition to producing

Sale Ends 30th June, 1979

REALISTIC®

Quality Base Station on a Budget



Regular Retail
Price 149.95

129⁹⁵

Realistic Navaho® TRC-441. Loaded with features at minimum price! Dual ceramic IF filters give you superior selectivity and adjacent channel rejection. Hysteresis-type adjustable squelch compensates for fading to reduce signal "chopping." LED modulation indicator and digital channel readout. S/R/F meter. Up-front speaker, jacks for external speaker and headphone. With plug-in mike, AC power cord. 21-9441

Specifications

Sensitivity for 10 dB S + N/N: 0.5 microvolt. Adjacent Channel Rejection: 80 dB. Audio Output: 5 watts max. RF Output: 4 watts max. Spurious Radiation: Better than -65 dB. Frequency Tolerance: Better than 0.002%. Modulation Capability: 90 to 100%. Power Requirement: 240VAC. Size: 12.0x30.0x24.7cm.

REALISTIC Low-Cost AM CB with Advanced Features



Realistic TRC-420. Compact, yet loaded with features for "big radio" performance. Auto-modulation to maximise your talk-power. Two ceramic filters for superior selectivity and freedom from adjacent channel interference. Features lighted S/R/F meter, full-time ANL, external speaker jack. With mobile mounting bracket, dynamic mike with locking plug. DC power cables. 21-9420


79⁹⁵

Regular Retail
Price 89.95

Specifications

Sensitivity for 10 dB S + N/N: 0.5 microvolts. Adjacent Channel Rejection: 60 dB at 10 kHz. Audio Power Output: 5 watts maximum. RF Power Output: 4 watts maximum. Power Requirement: 12VDC positive or negative ground. Size: 4.1x13.3x19.6cm.

AM/SSB Base — Goes Mobile Too!

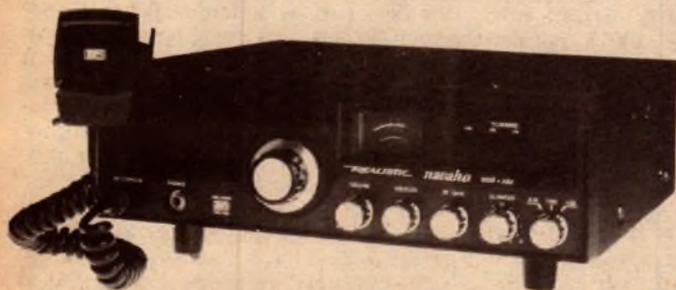

- Auto-Modulation control
- LED Channel readout
- ANL

449⁹⁵

Realistic TRC-458. Put your signal across with far more power than the best AM radios. PLL circuitry for rock-stable performance on all 18 AM and 36 upper/lower side-band channels. Includes jacks for mobile PA and remote CB speakers, front panel ¼" headphone jack, RF gain control and S/R/F meter. Adjustable mounting bracket, AC and DC power cords. 21-9458

AM/SSB CB Transceiver Budget Priced! Noise Blanker and RF Gain Control




- 12-watt P.E.P. SSB output
- 18 AM Channels, 36 SSB Channels

229⁹⁵

TRC-448. Includes many fine features like PLL circuitry, clarifier for fine tuning SSB reception, dual IF's and a crystal/ceramic filter for superb selectivity. Noise blanker cuts impulse interference and an automatic modulation gain circuit provides 100% "talk power" without a power mike! Mobile bracket. Push-to-talk mike, DC power cord with inline fuse. 21-9448

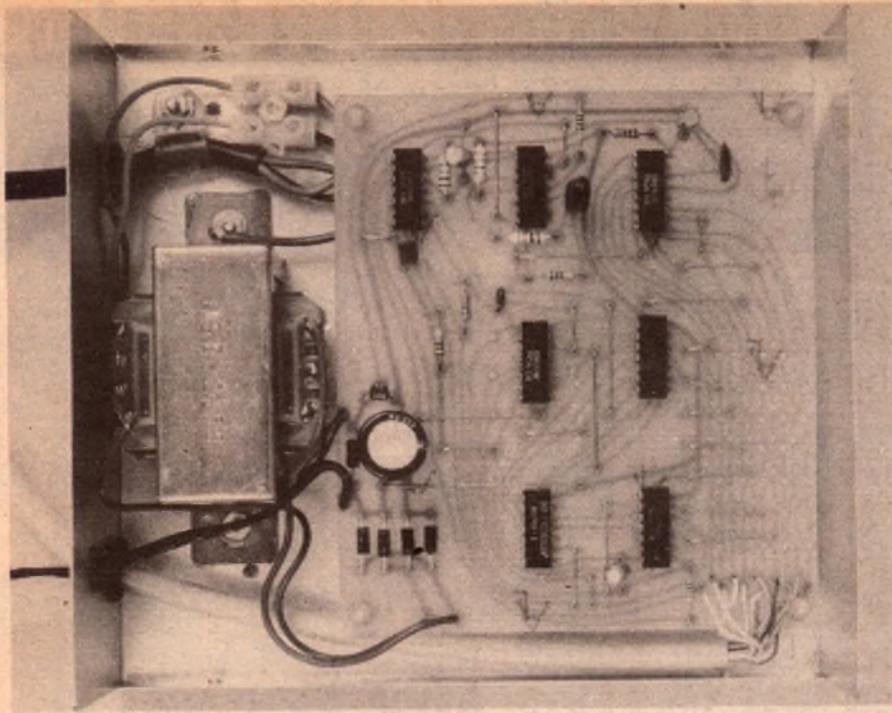Available at all Tandy Stores and participating Authorised Sales Centres



Inside the completed electronic combination lock. Programming links have been added here to give a 0123456 demonstration code.

sequence. Any incorrect digit or correct digit in the wrong position immediately causes the counter to be reset to zero again. Only if all seven digits have been keyed in correctly does the counter reach the count of 7, and cause the latch release to be activated.

In greater detail, note that each of the outputs 01-07 of the counter is taken to one input of a series of 2-input NAND gates, IC1a — IC2c. The other input of each gate is connected to one of the seven programming links, and thence to one of the 10 output lines from the keyboard scanning section. The outputs of the 2-input gates are taken in turn to seven of the inputs of IC3, an 8-input NAND gate. The output of IC3 is taken via IC2d, connected as a negative-input OR gate, to the reset input of the counter.

The second input of IC2d is connected to the output of IC5a via a 100k/2.2uF delay circuit, which performs two functions. One function is to hold the second input of IC2d low when power is first applied to the circuit, forcing the output of IC2d high and ensuring that IC7 powers up in the reset-to-zero state. The second function will be made evident shortly.

Of the two "key pressed" strobe signals generated by the keyboard scanning circuit, the undelayed signal from IC5d is taken to the eighth input of IC3. The delayed signal from IC5c is taken to the clock input of IC7, the verification counter.

Although IC7 is reset to zero when power is first applied to the circuit, this is not the verification circuit's normal

We estimate that the current cost of parts for this project is approximately

\$35.00

This includes sales tax, but does not include the cost of the electric latch release mechanism required.

"quiescent" condition — which is with IC7 set to the count of 1. It moves into this state as soon as any key is pressed (it doesn't matter which key).

This happens in the following manner. With IC7 reset to zero, none of the gates IC1a — IC2c are enabled because outputs 01-08 of the counter are all at logic low. Regardless of the key pressed, then, all of the outputs of these gates will remain at logic high. As a result the undelayed "key pressed" pulse from IC5d will be able to progress through IC3 and then IC2d, and force IC7 back to the reset-to-zero state (in case it was not already in that state). However shortly afterward the delayed pulse from IC5c will be fed to the clock input of IC7, incrementing it to the count-of-1 state.

It is in the latter state that IC7 becomes capable of responding to the correct sequence of input digits as programmed by the wire links.

PARTS LIST

- 1 Instrument case, 184 x 70 x 160mm
- 1 Power transformer, 9V at 1A; A&R type 2155, PF2155, M-2155 or similar.
- 1 PC board, 114 x 130mm, coded 79CL7
- 1 Pack of 11 keyswitches (see text)
- 1 PC board, 89 x 91mm, coded 79KB7
- 1 Mains cord and plug
- 1 Length of 6-pair telephone cable
- 1 Length of 2-wire cable, light figure-8 type
- Grommets, cable clamps, termination block, etc.

SEMICONDUCTORS

- 4 4011 CMOS integrated circuits
- 2 4017 CMOS integrated circuits
- 1 4068 CMOS integrated circuit
- 1 BD263 Darlington transistor
- 5 1N4001 power diodes or similar

CAPACITORS

- 1 47pF ceramic or polystyrene
- 2 .001uF polyester
- 1 .047uF polyester
- 1 0.47uF 25VW tantalum
- 1 2.2uF 25VW electrolytic PC-type
- 1 4.7uF 25VW electrolytic PC-type
- 1 1000uF 16VW PC-type electrolytic

RESISTORS

- All half-watt 5%: 2 x 1k, 1 x 4.7k, 3 x 10k, 1 x 100k, 2 x 1M

Note: Resistor wattage ratings and capacitor voltage ratings are those used in the prototype. Components with higher ratings may generally be used, providing they are physically compatible. Components with lower ratings may also be used in some cases, provided that the ratings are not exceeded.

When the circuit is awaiting the first digit in the sequence, IC7 has a high logic level at output 01 (pin 2). This enables gate IC1a. If the correct key is then pressed, corresponding to the keyboard line connected to IC1a's input via link 1, this gate will therefore produce a logic low at its output.

As a result of this, gate IC3 will be disabled and the "keypressed" signal from IC5d will not be able to pass through to reset IC7. When the delayed signal from IC5d arrives at the clock input of IC7 it will therefore be able to increment the counter to its next count, with output 02 high ready for the next digit.

The thing to note is that the undelayed "key pressed" pulse from IC5d is only prevented from resetting IC7 if the correct digit key has been pressed, to enable the currently active two-input gate and disable IC3. Pressing any other key will not cause IC3 to be disabled, and the counter will be reset to zero and then incremented back to 1 again.

Centronics. Simply better.

You won't find a better family of printers for the price.

It's that simple.


Now, the features that make our model 700 the best, lowest-priced serial printer are available in a family of eleven models: uncomplicated modular construction; the reliability of fewer moving parts; high parts commonality; and low price. All of which means a lower cost of ownership.

The new 700 family covers a full range of serial printer requirements: 80- and 132-column format; 60 to 180 cps speed range; bi-directional and logic-seeking operations; and 110-1200 baud KSR and RO teleprinters.

Like all Centronics printers, the 700 family is better because we back them with a wide choice of customizing options and accessories.

Centronics financial stability and dependability is proven with over 95,000 world wide installations and is backed with support, sales and service in New Zealand and Australia-wide. Simplicity of design, full range capabilities, and better back-up make our 700 series printers simply better.

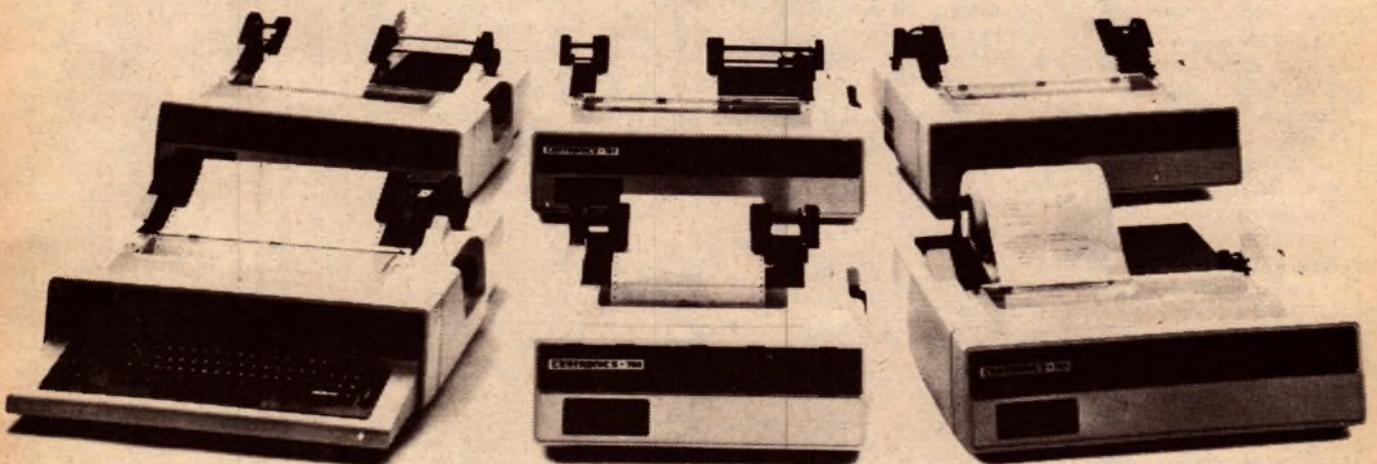Melbourne: 03-267 4388 Sydney: 02-922 3100 Brisbane:
07-364799 Adelaide: 08-272 3588 Canberra: 062-80 6573 Perth:
09-3215855 Auckland NZ: 09-778543 Wellington NZ: 09-850221.




SIGMA DATA
GENERAL PRODUCTS DIVISION

Combination lock

Exactly the same thing happens for each of the succeeding digits. Once the counter has reached the count of 2, for example, the only key that can make it progress to the count of 3 is the key which causes gate IC1b to produce a low output and disable IC3. Any other key allows IC7 to pass the reset pulse, so that IC7 is forced back to the count of 1 again. And so on.

So that only the correct sequence of digits keyed in without a false digit between them will cause IC7 to count up to the count of 8. Any false digit anywhere in the sequence will force IC7 right back to "first base".

Note that in the foregoing explanation, we have talked about the "key pressed" pulses from IC5d and IC5c as if they were narrow pulses. In fact they are quite long, lasting as long as a key is held depressed. However the essential thing is that the clock signal from IC5c triggers IC7 on its positive-going transitions, which occur about 5 microseconds after the reset signal from IC5d falls to the inactive level — just after the key is released.


What this means is that when a key is pressed, IC7 will either be immediately reset to zero if the wrong key is pressed, or will remain at its current count if the correct key is pressed. Then when the key is released, the counter will increment — to either the count of 1 or the next appropriate count, as the case may be.

Assuming the correct sequence of digits has been keyed in, counter IC7 finally reaches the count of 8 and its output 08 goes high. As gate IC5a is connected to this output as an inverter, its output accordingly goes low. This does two things, the first of which is to activate the latch release mechanism via gate IC4d (also wired as an inverter) and the BD263 Darlington transistor.


The second thing that happens is that the low at the output of IC5a is fed to the second input of IC2d, via the 100k/2.2uF delay circuit. As a result the second input of IC2d goes low after approximately 150 milliseconds, resetting IC7 to its zero state once again and deactivating the latch release mechanism.

Note that since IC7 is again reset to the zero state, it must be forced into its count-of-one state before it can accept the correct code sequence again. As when power is first applied, then, you have to key in a "dummy" digit before you key in the correct code. This is really no trouble, and if anything will make it harder for an intruder to find the correct combination.

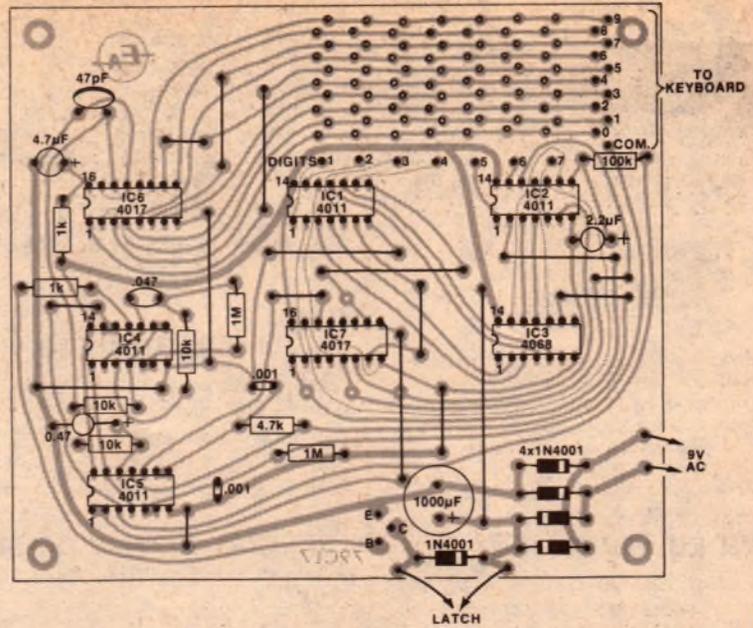The latch release or "electric strike" mechanism we have used with the lock is designed for pulsed operation, and thus operated quite happily from the



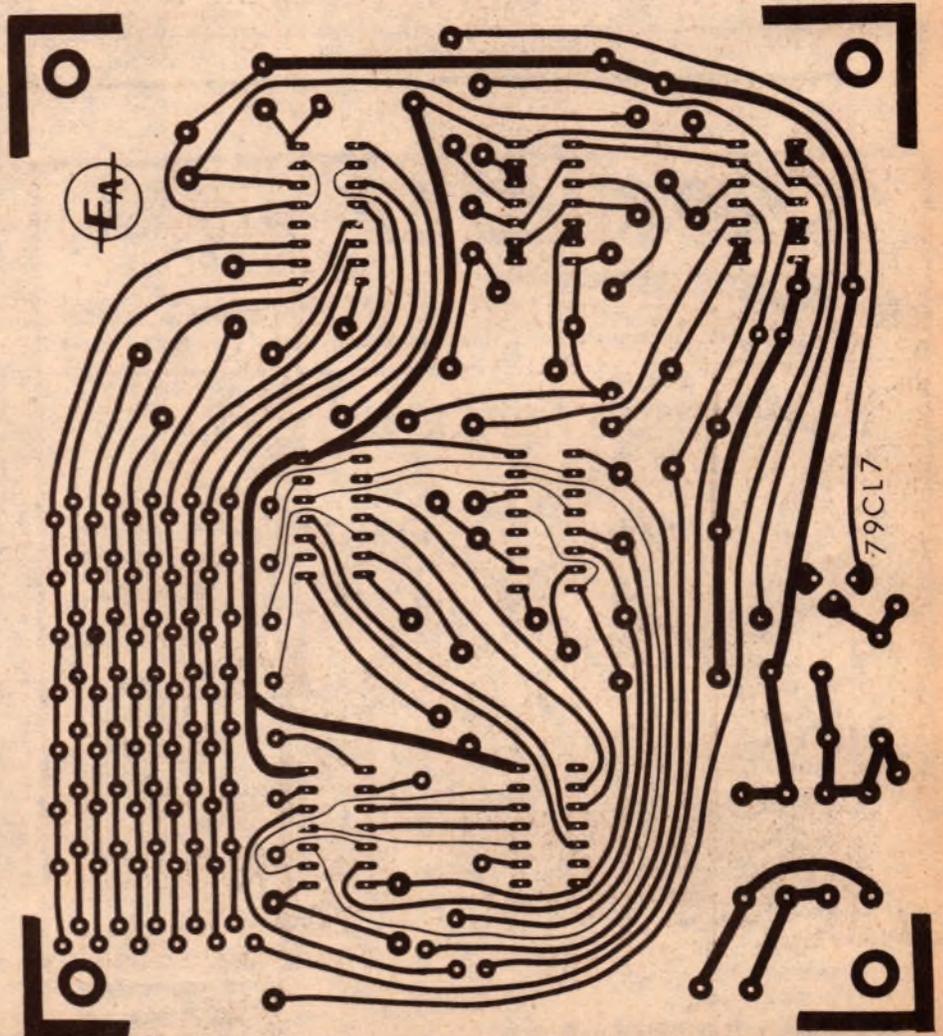Use this overlay diagram in conjunction with the circuit to assemble your unit. Don't forget to add programming links to make up the 7-digit code you require.




Here is an actual size reproduction of the main PCB pattern.



VIDEO TECHNICS

THE CAROUSEL CENTER SHOP 17 & 18, 530 OXFORD ST., BONDI JUNCTION
P.O. BOX 50, BONDI ROAD, BONDI 2026, NSW 2022 TEL. 387 2555
3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE,
BRISBANE 4064 PH. 36 1257

3 HOURS VCR VIEWING

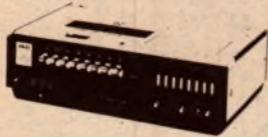

3 hours continuous recording/playback 1-2-3 operation simplicity Video head and azimuth recording system: key to perfect picture reproduction The ingenious yet simple "M" loading system, low 35 watts power consumption
Units available — Sony, Philips, National, etc.

VIDEO MOVIES FULL LENGTH FEATURES — MANY TITLES AVAILABLE AUSTRALIA WIDE

BW 12' RECEIVER/MONITOR

Ideal for computer VDU.
Can be switched over as
TV receiver, can also be used
on CCTV — \$159.00
Will accept composite video signal

VIDEO EQUIPMENT —

Sony, Akai and JVC Colour and BW Portopacks. We have several BW Portopacks traded on colour sets. Also agents for JVC, National, Sony and Nec Umatic equipment. All formats and brands colour and BW recorders, editors, generators and blank video tapes available. New and used equipment. Trade and terms.
Specials. Also transfers from Super 8 film to video tape.

SPECIAL CLOCK TIMERS

Can be set to switch equipment up to 4 days ahead.



Starting time accurate to a second

\$195 + P.P.



FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA

VESCO

ELECTRONIC SUPPLIES

318 Huntingdale Road, Huntingdale, Vic 3186 Telephone: 543 4826
Cnr. Hume Street

1ST BIRTHDAY SALE

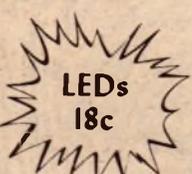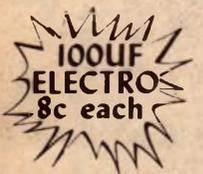

We have in stock semi-conductors at low prices.
Speaker cable — 1/2 price \$8.00 per 100 metres.
Multimeters, Capacitors, Resistors, Transformers, Audio Accessories, Valves, Instrument Cases.

PLUS MANY MORE
Send 45c for price list

MAIL ORDER ENQUIRIES WELCOME



Combination lock

150ms pulse delivered by the circuit. The pulse of current triggers an internal release mechanism, which allows the door to be opened at any time afterwards — there's no need to hurry. The release resets as soon as it springs back into place when the door is opened.

Made in Spain by Golmar S.A., the mechanism is designated type CV-24 and is rated to draw about 1A from a nominal 12V DC supply. It is imported by Habitech Pty Ltd, of 14 Northcote Street, St. Leonards, NSW 2065, who sell directly to the public, but you can also buy it from their interstate distributors or from specialist locksmiths. The recommended retail price is \$37.00.


In Sydney you can buy them from North Shore Locksmiths of 75 Willoughby Road, Crows Nest 2065, or from Independent Locksmiths of 92 George Street, Parramatta 2150. In Melbourne they are available from Style Finnish (Security) Pty Ltd, Factory 5, 42 New Street, Ringwood 3134 (PO Box 80), and in Perth from Style Finnish (WA) Pty Ltd, 398 Rokeby Road, Subiaco 6008. In Brisbane the distributors are Vacuumatic Distributors Pty Ltd, 36 Gladys Street, Stones Corner 4120.

As normally supplied the CV-24 mechanism is intended to replace a mortise-type strike plate, mating with a mortise-type spring return latch. A surface-mounting adapter plate is available if required, for an additional \$3.00. Habitech also have available a version of the CV-24 which will operate with combination bevel-bolt latches and double-throw deadlocks, such as the Cisa type 52111 unit which they are also able to supply.

One thing you should bear in mind is that latch release mechanisms like the CV-24 will not work with some types of deadlock and deadlatch and may need modification to work properly with other types. We suggest that you seek advice from the suppliers listed or from your local locksmith, before committing yourself.

A somewhat more rugged, heavy-duty electric strike mechanism is also made locally by DK Security. Known as the DKS unit, it is available from North Shore locksmiths in Sydney. However this unit is designed for "continuous" rather than pulsed operation — that is, it will only release the latch while power is applied. It is also rather more expensive than the price of the Golmar unit.

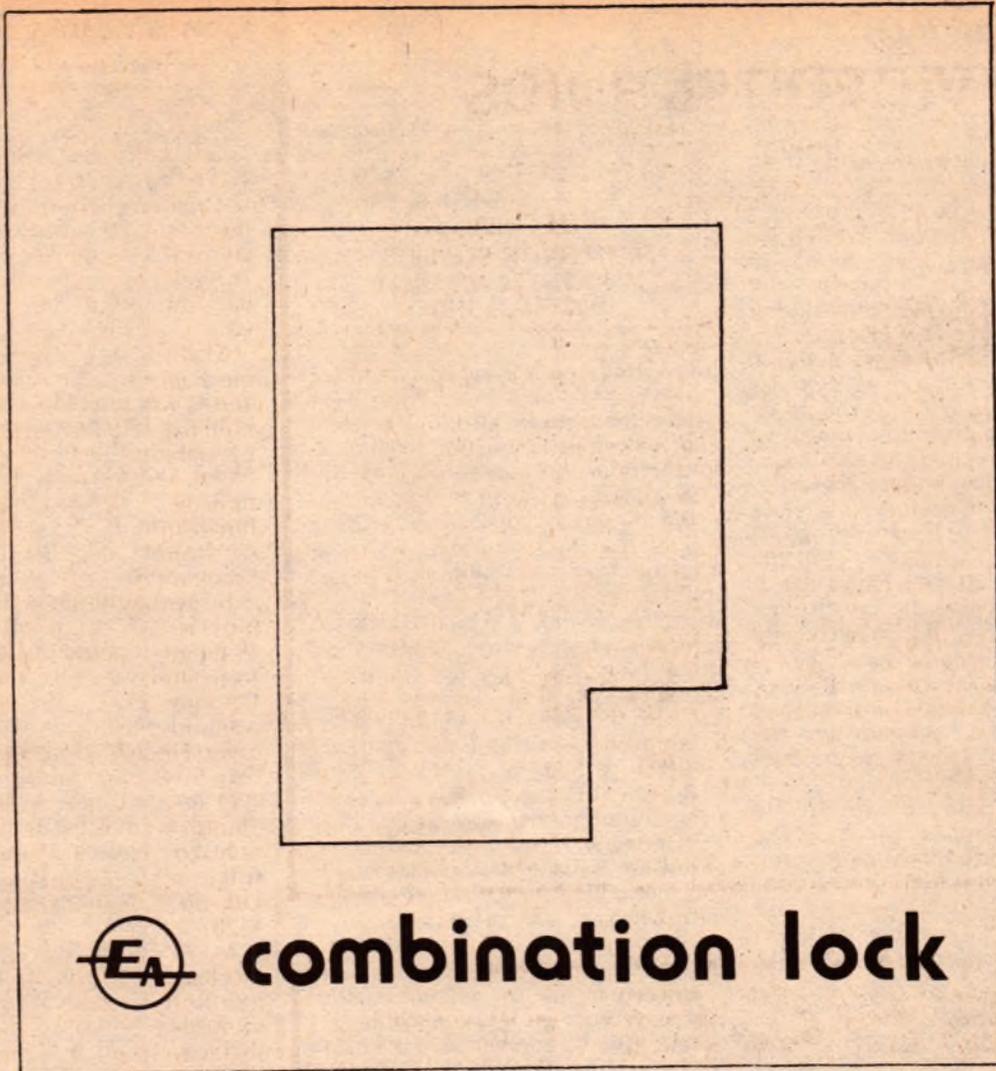To use the DKS unit with our lock design, you will need to modify the circuit so that it energises the release for considerably longer than the 150ms provided for a pulsed release. You can do this by increasing the values of the



combination lock

Actual size reproduction of the keyboard artwork.

RC delay components between IC5a and IC2d. If you increase the resistor from 100k to 1M and replace the capacitor with a 22uF/25VW solid tantalum, the release will be energised for about 12 seconds — which should be adequate.

This modification should also allow the lock circuit to be used with other "continuous" type release mechanisms. For example there is a Golmar release of this type, the CV-14, which is otherwise similar to the CV-24 unit. You could use the CV-14 unit with our lock, if you wish, by making the same modification.

As mentioned before, the code combination to which the lock responds can be programmed as you wish, to any combination of seven digits. Each digit is set simply by connecting the appropriate 2-input gate to the corresponding output line from the keyboard scanning circuit.

Don't make the code too simple — like 1234567 — or it is likely to be guessed too easily. Similarly it might not be a good idea to make it too complex, or it might be too hard to remember! A familiar telephone number might be

worth using, although it might not be wise to use your own — a burglar might well have the foresight to look up your name and number! Another idea might be to use your birthdate, or some other significant figure.

If you don't really want the full protection of a seven-digit code, you can shorten the required code sequence simply by connecting the input of IC5a to one of the earlier outputs of IC7, rather than to 08. Hence by connecting it to 06 you will need only a 5-digit code, and so on.

We have designed a PC board to accommodate virtually all of the combination lock circuitry, and make construction easy. The only components which don't fit on the PCB are the power transformer, which is too bulky, and the keyboard and latch release mechanism which are in any case best separated from the main unit.

The PCB measures 114 x 130mm, and is coded 79CL7. The pattern is reproduced actual size in this article, for those who may wish to trace it or copy it photographically. Alternatively, transparencies will be available from the Information Service, and you



combination lock

A close-up view of the keyboard. The "CLR" key is a dummy.

should also be able to buy finished boards shortly from the usual suppliers.

Wiring up the unit should be fairly straightforward using the PCB overlay diagram and the photographs as a guide. We suggest that you leave the ICs until last when wiring up the unit, however, as they are CMOS devices

Combination lock

and can be damaged by excess static charge.

As you can see the PCB provides a matrix of holes near one corner for convenient setting of the combination code. The seven gate inputs for the verification circuit are along the side of the matrix, and all you have to do is fit a wire link from each one to any of the 10 digit lines available in a staggered row along from it. The entry keyboard or keyboards also connect to a row of holes at the end of the matrix area.

We suggest you connect the entry keyboard to the main lock unit via a length of 12-conductor ("6-pair") telephone cable, which is available from many parts stockists. This cable is round, and can be easily run through holes in walls, skirting boards and architraves. An alternative would be flat "rainbow" cable. The circuit will work reliably with up to about 5 metres of cable between the keyboard and the main lock unit, which should be adequate for most applications.

The entry keyboard should be mounted conveniently adjacent to the outside of the door to which the release mechanism is fitted. If the door is on an external entrance, the keyboard should be suitably protected from the weather as most switches are not fully waterproof.


For the keyboard itself we used a set of keyswitches which were kindly supplied by Pre-Pak Electronics, of 718 Parramatta Road, Croydon, NSW. There are eleven switches in the set, and they come with integral numbered keytops. The eleventh key is labelled "CLR". The set is available from Pre-Pak for \$5.50, plus postage if applicable.

We have designed a small PCB to mount these switches. It measures 89 x 91mm, and is coded 79KB7. As you can see from the photographs it provides for the CLR switch as well as the ten numbered switches, even though the CLR switch is not connected into circuit. The idea behind this is that the CLR key becomes a dummy, to provide further potential confusion to an unauthorised person trying to gain entry.

As an alternative to the keyswitches we have used, you could use ten standard miniature pushbuttons and perhaps mount them in a small diecast metal box. The choice of keyboard and how you mount it near the door is up to you.

Don't forget that as well as the cable between the lock unit and the keyboard you also need to run a 2-wire cable to the latch release mechanism. However this can be light-duty figure-8 cable of the type used for hifi speaker connections, so it should pose few problems.

The lock circuit PCB and power

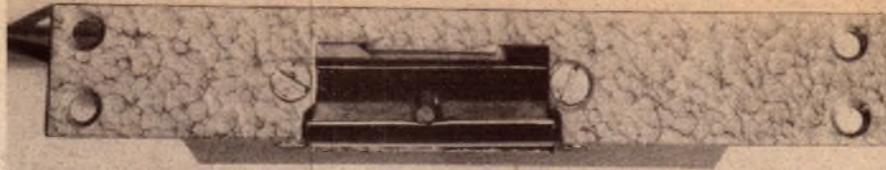

Close-up view of the Golmar CV-24 door-latch mechanism.

transformer are housed in a small inexpensive instrument case. The case we used came from Dick Smith Electronics, and measures 184 x 70 x 160mm. It is listed under the number H-2744 in the DSE catalog.

We mounted the PCB on "Richco" moulded nylon supports, which are available from most parts stockists. The transformer was at the rear of the PCB, with the power, keyboard and latch release cables entering via grommeted holes. Needless to say the mains cable should be properly clamped after entry, with the active and neutral taken to a connector strip and the earth lead soldered to a lug bolted to the case.

When the keyboard cable and programming links are wired to the PCB along with the power supply parts and other passive components, the ICs can be added to complete the job. Remember to take the usual precautions when dealing with CMOS devices: use a small soldering iron, preferably of the low voltage separate-element type, and use a cliplead to connect the tip and barrel of the iron to the "earthy" copper track on the PCB.


When soldering in each IC it is a good idea to solder the two supply pins

first, so that the internal protection diodes can function as soon as possible. With the 16-pin devices these are pins 8 and 16; for the 14-pin devices they are pins 7 and 14.

When you have finished wiring up the electronic lock we suggest that you check over all PCB connections, etc before turning on the power for the first time. Similarly it is a good idea to make sure all of the polarity or orientation-conscious components are mounted the correct way around on the PCB.

If all is well, it should be possible to turn on, key in a dummy digit and then the code combination you have programmed into the links, and hear the release mechanism operate.

A final point. Although we have described the electronic combination lock with a simple mains-type power supply, it would obviously be possible to power it from a 12V battery supply if required. This means that you could use it for a car, boat or other application away from the mains. It also means that you could use a battery back-up system, to allow the lock to operate in case of power failure. We leave these optional elaborations up to you.

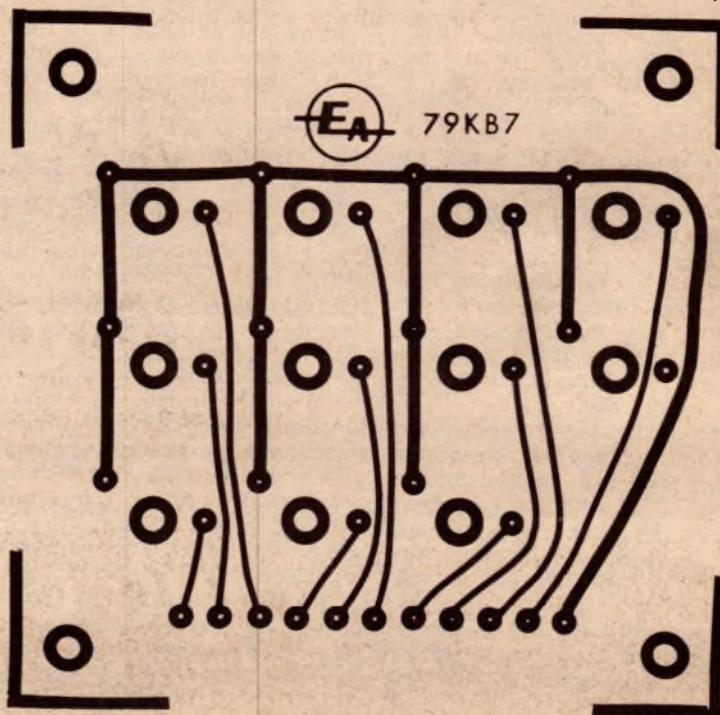

Actual size reproduction of the keyboard PC pattern.

FOR THE PAST 20 YEARS WE HAVE CATERED
FOR TOMORROW'S ELECTRONICS ENGINEERS.

ALL ELECTRONIC COMPONENTS

formerly

E.D. & E. (SALES) PTY LTD

K
I
T
S


K
I
T
S

COME TO THE PEOPLE WHO SPECIALISE IN KIT SETS

NOW at last we have received stocks of Negative Photo Resist "coated copper" on fibreglass board.

No pre or post baking required. Just place negative in contact, add UV light, develop and etch a beautiful PCB. All your own work. All chemicals available.

How it works:

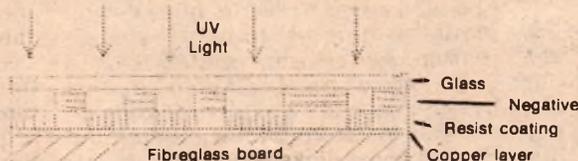

UV light passes through the clear areas of the negative and sensitises the Resist. Black areas on the negative prevent the UV light from reaching the Resist. During development the unsensitised areas of Resist are removed, leaving the acid resistant sensitised image.

1mm thick positive working black aluminum material also available.

Ideal for front panels, excution plates, etc. Achieve a truly professional finish.

**WE ARE THE SOLE VICTORIAN AGENTS FOR THIS FABULOUS PRODUCT
WHOLESALE AND TRADE ENQUIRIES WELCOME**

You asked for it — here it is!

Fantastic new inverter from E.A.

Ideally suited for remote locations, outback areas, boats, yachts, vehicles, etc, where regular AC power supply is unavailable or unreliable.

EA 12-230V inverter kitset (See EA Feb '79)

Input 12V DC, Output 230V at 50Hz 300VA — \$195.50 inc. tax.

YOU NAME IT — WE'VE PROBABLY GOT IT!

WE HAVE ... one of the biggest ranges of kits, parts & P.C.B.'s in Australia.

WE HAVE ... over 300 different types of I.C.'s.

WE HAVE ... over 250 different types of transistors.

ONLY "RECOGNISED BRANDS" STOCKED

TOP QUALITY & LOW PRICES

SPECIAL SERVICE FOR SCHOOLS — EVERYTHING THE YOUNG ELECTRONIC STUDENT WOULD NEED

INQUIRE ABOUT OUR MAIL ORDER SERVICE

WE STOCK A COMPREHENSIVE RANGE OF TOP QUALITY P.C.B.'s FOR E.A. & E.T.I. PROJECTS (For full list refer to E.A. November 1978)

FOR FULL LIST OF KIT SETS REFER TO E.A. JANUARY 1979

ALL ELECTRONIC COMPONENTS

THE FAMILY BUSINESS

TELEPHONE
662-3506

118 LONSDALE STREET, MELBOURNE 3000

TELEPHONE
662-3506

Designing voltage reference circuits

It is often necessary in electronic circuit design to provide a stable voltage source for reference purposes. In this short article the author describes low cost ways of providing such a voltage reference.

by **STEPHEN DOLDING**

26 Rickard St, Merrylands NSW 2160

The need frequently arises in electronic circuits for the provision of a stable voltage source for reference by comparators, level detectors, current and voltage regulators and so on. In many cases the prime requirement in the case of the reference voltage is not so much its absolute precision, but rather its stability with respect to supply voltage and ambient temperature variations. It is normal practice to connect only a small and fixed load to such a reference supply, so that unlike voltage regulator circuits load regulation is not a problem.

The simplest approach to providing such a reference is to use a zener diode. This is connected in shunt mode, in virtually the same manner as used for a

simple regulator (Fig. 1). The zener is operated in its "reverse breakdown" mode, where its terminal voltage remains substantially constant over a wide range of current. This is illustrated by the graph in Fig. 2, where you can see that in the breakdown region the diode's voltage drop remains substantially constant at V_z for a significant range in current I_z .

The equation used to calculate the circuit values for Fig. 1 is:

$$R = (V_s - V_z) / (I_z + I_L)$$

As an example let us say V_s is 12V and the zener voltage is to be 6.2V, with a load current I_L of 0.8mA. Most low power zener diodes have their nominal terminal voltage specified at a current of

the breakdown region (see Fig. 2).

Obviously the steeper the slope of the characteristic, or the lower its "slope resistance", the more stable will be the zener voltage with variations in unregulated supply voltage.

Low power zener diodes are readily available in a range of voltages in preferred value steps from 2.7 volts to 75 volts or more, usually with tolerances of $\pm 5\%$. However, on closer observation it is seen from data on these devices that the zener diode with the lowest slope resistance in any particular production series occurs at about 6.2 volts. Hence for best results a 6.2 volt zener should be used where possible. If a lower reference voltage is required a potential divider may be used,

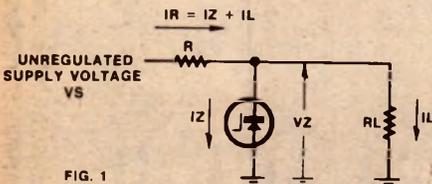


FIG. 1

Simple zener diode voltage reference.

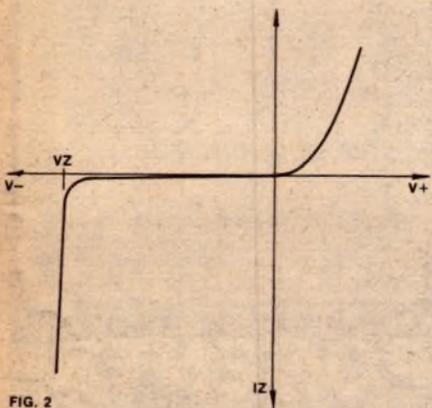


FIG. 2

Graph showing how zener diode voltage drop remains substantially constant at V_z for a large range in current I_z .

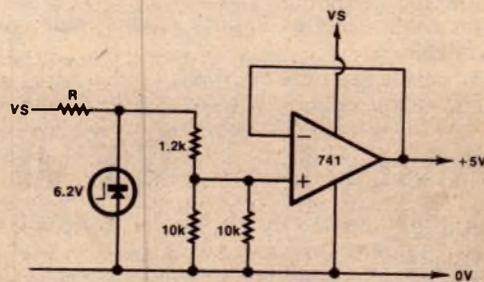


FIG. 3

A 6.3V zener, a voltage divider, and a 741 op amp make up this +5V reference.

5mA, so we can set I_z at this value. Hence

$$R = (12 - 6.2) / 5.8 \times 10^{-3} = 1k$$

If the zener diode current is reduced much below 5mA, the diode voltage will drop as the device operating point approaches the "knee" of its characteristic. On the other hand if the zener current is increased the diode voltage increases (as does its power dissipation). The voltage increase is due to the finite slope of its characteristic in

ed, preferably using metal film or metal glaze resistors for stability. Such a circuit is shown in Fig. 3. As you can see an op-amp is used as a buffer, to prevent load current from disturbing the divider ratio.

If a reference voltage higher than 6.2V is required, the circuit shown in Fig. 4 may be used. The DC gain of the amplifier is set by the ratio of two resistors:

$$\text{Gain} = (1 + R_1/R_2)$$

Because the most readily available zener diodes have a tolerance around

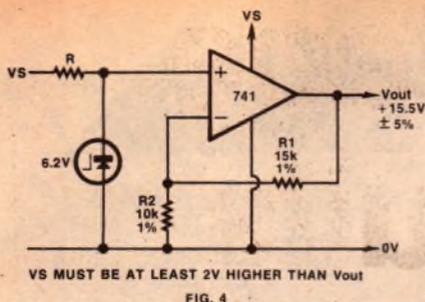


FIG. 4

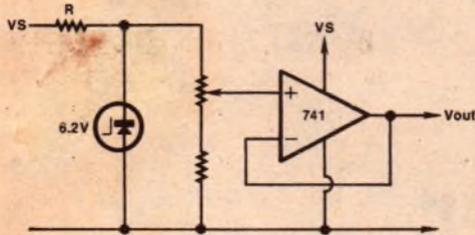


FIG. 5

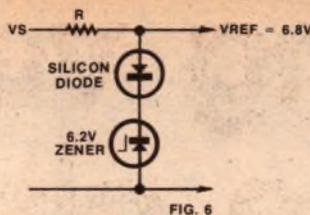


FIG. 6

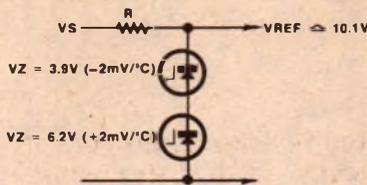


FIG. 7

Fig. 4: obtaining a reference voltage higher than the zener voltage. Fig. 5: using a preset pot to trim output voltage. Figs. 6 & 7: temperature compensated zener reference circuits.

±5% it is a good idea to include a preset potentiometer to trim the output voltage to the required level. If the wiper of the potentiometer is connected to an operational amplifier, as shown in Fig. 5, then any variations in load resistance will have no effect on the reference voltage (within the output capability of the op-amp).

On further investigation of the data sheets for zener diodes, it is also found that the ambient temperature has a marked effect on the zener voltage of any particular diode. The figure quoted is usually the temperature coefficient in mV/°C temperature change.

The lowest temperature coefficients are for zener diodes in the range 5.1 to 5.6 volts, the typical figures being -1mV/°C for 5.1V, +0.5 mV/°C for 5.6V and + 2 mV/°C for 6.2V.

If the unregulated supply voltage variations and load variations are not severe then a single 5.1V or 5.6V zener may be used, giving a reference voltage only changing by 1% for a temperature change of 50°C. Generally this is adequate for most purposes.

If better temperature stability is required a good trick is to use an ordinary forward-biased silicon diode in series with a 6.2V zener diode (Fig. 6). This makes use of the fact that the forward voltage temperature coefficient of a silicon diode is approximately -2mV/°C. The temperature coefficient of the silicon diode and the zener diode cancel out or compensate each other, giving a reference voltage with a

temperature coefficient very close to zero. Alternatively two zeners may be used in series, with equal and opposite temperature coefficients as in Fig. 7.

This gives a much better performance than a standard 10V zener, which has a temperature coefficient of about + 7 mV/°C. In both Fig. 6 and Fig. 7 the two diodes should be mounted close together so that they are at substantially the same temperature.

Several monolithic precision voltage reference ICs are available with typical output voltage temperature coefficients of less than 0.01% /°C change.

These references also usually have a very high degree of precision of the output voltage; however, they usually cost several dollars each. If precision is the main criterion, and if the load is constant, then another approach is to use one of the wide range of readily available 3 terminal monolithic voltage regulators, e.g. 7805, 7812, 7815, LM 340, LM 320 etc.

If these regulators are used with a constant and low load of about 10-20mA, then they will also have a temperature coefficient of about 0.01% /°C, while the output voltage variation is about 0.25% of any variation of the unstabilised input voltage. This represents a very cost effective alternative. No heat sinks are needed in this mode of operation, and a wide range of voltages from 5V to 24V is obtainable.

printed circuits

- Accurately machine printed etched
- Phenolic & fibreglass-gold tin plated
- EA R & H ET Philips Mullard available
- Specials to your drawing
- POSTAGE small 80c large \$1.10.

	\$	\$	\$
ET320	2.20	ET249	2.80
ET595	2.80	ET253	4.20
491	4.50	7905	3.00
79PS3	2.60	559	3.00
79P1B	2.80	78SE3	4.00
79C1A	3.00	79P1A	2.80
142B	4.00	558	2.50
79S1	4.50	142A	8.00
791T2	5.00	78W3	2.60
78S12A	5.50	78SB12	3.00
78N10	2.60	781M12	3.00
78DT10C	2.50	78C11	3.10
ET813	3.50	78DT10B	2.80
ET812	2.80	ET143	2.80
ET556	6.00	ET593	3.20
78B8d9	3.50	78DB11	2.80
650B	2.60	555	4.00
718	2.60	650A	4.00
590B	8.00	553	3.00
78E09	2.50	590A	8.00
ET391A	2.50	ET605	7.00
ET591C	2.20	ET551	3.00
78U79	16.00	ET550	2.80
78UM8	2.60	78MX9	3.30
ET638A	4.00	78CL8	3.00
ET591	4.00	ET248	2.30
78TSC7	2.50	ET810	2.80
ET137B	2.80	78PT7	2.50
78F6B	3.50	ET137A	3.50
246	4.00	ET587	7.00
78CD4	2.60	78N	2.80
78UP5	5.00	489B	2.50
ET1140P	5.50	78PS5	2.50
ET487A	7.50	ET140D	4.00
78U74	4.00	ET136	2.50
78B2	3.00	ET588 20	10.00
ET450A	2.80	78EK3	3.30
ET486	3.20	781A2	2.60
78AF2	3.00	ET716	4.00
78CB12	2.60	ET245	2.50
ET135	3.00	78S3	2.60
775C11	3.80	77PH12	2.60
77MX11	2.50	ET586	2.80
ET604	2.50	77PS11	2.50
ET713	3.00	77PS11	2.50
77T59	3.00	ET585T/R	3.00
ET134	2.60	ASC11	2.80
77DM9	2.80	ET603	3.00
ET067	2.20	77AL8	2.50
ET072	2.50	ET065	2.20
ET485	2.80	ET063	2.50
ET481M	2.50	ET085	2.20
ET547	2.50	ET085	2.20
77D7	2.50	ET084	2.50
77UP6	3.50	ET484	3.00
ET631/2	4.50	ET582B	2.60
ET444S	3.00	ET317	2.50
ET548	3.20	77TY6	2.50
77PY7	2.80	77PY6	2.50
77E05	3.50	77PRE5	2.50
ET081	2.20	ET062	2.50
ET632U	4.00	ET632	7.00
77C04	3.00	77UP2	3.00
ET632C	8.00	ET632B	6.50
77UT2	3.00	77F1B	2.50
ET633FR	6.00	77U72	3.00
ET632P	2.50	ET632M	7.50
ET482A	6.50	76CL12	2.50
76B4	2.60	ET480PS	2.50
ET631	7.00	ET630	2.20
ET064	2.00	ET449	2.20
ET448A	2.20	ET448	2.80
ET711B	2.20	ET068	2.00
ET044	2.00	ET043	2.00
ET711R	2.50	ET7110	6.00
ET544	2.50	76PC9	4.40
ET602	6.50	ET446	2.50
ET594	2.50	ET594	2.50
ET470	3.20	ET470	3.20
79A3	3.00	79A3	3.00
721	3.00	721	3.00
79PB2	3.20	79PB2	3.20
78C1B	2.80	78C1B	2.80
557	3.00	557	3.00
79UP1	5.00	79UP1	5.00
79C11	2.60	79C11	2.60
78S12B	2.20	78S12B	2.20
78UP10	7.00	78UP10	7.00
78DT10D	2.00	78DT10D	2.00
78DT10A	6.50	78DT10A	6.50
ET141	4.20	ET141	4.20
ET480	2.80	ET480	2.80
78UP9	6.00	78UP9	6.00
650C	2.60	650C	2.60
138	3.80	138	3.80
811	3.00	811	3.00
78MC10	4.00	78MC10	4.00
ET391B	2.50	ET391B	2.50
ET641	3.00	ET641	3.00
ET582	4.50	ET582	4.50
78T9	2.30	78T9	2.30
ET638B	2.60	ET638B	2.60
ET318	7.00	ET318	7.00
78TM8	2.80	78TM8	2.80
78VBG7	3.50	78VBG7	3.50
ET139	2.50	ET139	2.50
ET640	16.50	ET640	16.50
78A06	2.80	78A06	2.80
489A	2.80	489A	2.80
78C5	3.20	78C5	3.20
ET140A	14.00	ET140A	14.00
78MG4	7.50	78MG4	7.50
78T3	3.60	78T3	3.60
ET450B	2.60	ET450B	2.60
ET715	3.00	ET715	3.00
78C2	3.00	78C2	3.00
78CF1	2.80	78CF1	2.80
77PM12	3.50	77PM12	3.50
77MX11	2.50	77MX11	2.50
77UP6A	3.00	77UP6A	3.00
77PS11	2.50	77PS11	2.50
ET635	2.80	ET635	2.80
77UP11	6.50	77UP11	6.50
ET583	2.50	ET583	2.50
77T10	2.50	77T10	2.50
ET083	3.20	ET083	3.20
ET084	2.50	ET084	2.50
ET581	2.50	ET581	2.50
ET582A	3.00	ET582A	3.00
ET317	2.50	ET317	2.50
77DL7	6.00	77DL7	6.00
77QB7	3.20	77QB7	3.20
ET444M	2.50	ET444M	2.50
ET549A	2.50	ET549A	2.50
HMS3276	6.00	HMS3276	6.00
ET133	2.60	ET133	2.60
77UP5	8.50	77UP5	8.50
ET546	2.50	ET546	2.50
77TTY4	2.50	77TTY4	2.50
ET132	2.50	ET132	2.50
ET632A	6.50	ET632A	6.50
77F1A	3.20	77F1A	3.20
ET633	6.00	ET633	6.00
ET482B	2.80	ET482B	2.80
ET630	2.20	ET630	2.20
ET480	2.80	ET480	2.80
ET066	2.20	ET066	2.20
ET894	2.80	ET894	2.80
ET711C	2.00	ET711C	2.00
ET061	2.00	ET061	2.00
76M19	3.50	76M19	3.50
ET447	2.80	ET447	2.80
76EX10	2.80	76EX10	2.80
ET533A C	3.50	ET533A C	3.50

ALL SILICON 30/60w PA PORTAMP
 6 1/2"W x 8 1/2"D x 3 1/4"H 12 — 16V, two inputs 5 & 100mV 125 250, 500 ohm output only. No. 763A
 \$70 ea. 240V operation \$33 extra. Freight collect.
 COILS and IF's All \$2.50 ea plus post 60c
 3/4"W x 3/4"D x 2"H

MAIL cheque or money order
 (add postage) direct to —


RCS radio pty ltd
 651 FOREST RD BEXLEY
 NSW 2207 587 3491

NOW AVAILABLE

ELECTRONICS AUSTRALIA BINDERS

These attractive binders finished in brown plastic with gold lettering will keep your back issues of Electronics Australia neat and tidy.

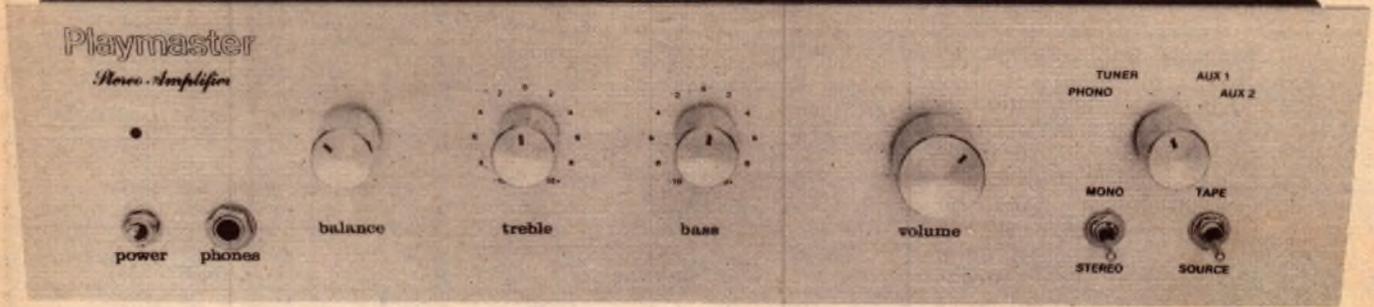Available from: Electronics Australia, 57 Regent St. Sydney. PRICE: \$4.50 or by mail order from Electronics Australia, P.O. Box 163, Beaconsfield 2014. PRICE \$5.50 NSW; \$6.50 other states.



A Playmaster Amplifier for flats and home units

Second article gives the construction details

Last month we introduced our new Playmaster Twin Ten stereo amplifier, explaining the basic design concept and discussing the circuit details of the input and control stages. In this issue, we cover the power stages and present the remainder of the constructional information.

by **RON De JONG**

The configuration of the output stage is well established for amplifiers of modest power and uses no more components than is necessary for good design.

The output transistors TIP31 and TIP32 are arranged in complementary symmetry. They are driven by a class-A stage composed primarily of a BD140 transistor and four 180-ohm resistors in series-parallel as its collector load circuit.

The particular transistors in each channel — driver and output pair — are of flat plastic pack construction, intended for direct attachment to a heat sink. We mounted them underneath the PC board in such a way that they could be bolted directly to the chassis base. Accordingly, the transistor leads are bent upwards and soldered to the track side of the board.

The arrangement is simple and economical and has the advantage that the PC board can be removed from the

chassis without having to unsolder the power transistors — an important consideration should access for servicing be required.

Comparison with the output stage of the Twin 40 shows that, whereas a constant current load was used for the driver in the Twin 40, a bootstrapped arrangement is employed here. Besides using one less transistor, in line with the basic philosophy of this amplifier, the available supply voltage is utilised to better advantage.

The role of the 220 μ F bootstrapping capacitor deserves special mention.

Under quiescent conditions, the minus side of the capacitor is at chassis potential, while the plus side is at about +10V DC. The value of the capacitor is such that it tends to maintain this charge, even under full signal conditions.

During one half of the output cycle, the output stage emitters will fall from an approximate 20V (quiescent)

towards 0V, thereby cycling the voltage at the loudspeaker output terminal from 0V towards -20V. At the same time, the bootstrapping capacitor will cycle the junction of the 180-ohm resistors from +10V towards -10V, thereby extending the effective supply to the driver and augmenting the available voltage drive to the TIP32.

If the output transistors were to operate from a true zero ambient current condition, "switching" or "crossover" distortion would assume major proportions. In practice, it is normal to arrange the bias so that both output transistors draw a small amount of current under no-signal conditions. With drive, and on the respective half-cycles, one transistor is driven towards saturation, while the other passes into full cut-off.

To be pedantic, one should really describe the condition as "class AB".

Estimated cost

We estimate that the current cost of parts for this project is approximately

\$85

This includes sales tax.

Not surprisingly, crossover distortion tends to fall as the quiescent current is increased — but at a price: higher average dissipation in both the output transistors and the power supply. The designer must therefore aim for a value of quiescent current which represents an acceptable trade-off between distortion and power dissipation.

In a complementary configuration, as here, the two output transistors take their signal drive from a common source but, to meet the foregoing bias requirement, each base must be referenced to a DC potential slightly positive or negative with respect to the common emitter potential. This means that they must be separated by a resistor or network such that each can assume its own required bias.

A purely resistive network is seldom favoured because the critical bias voltage may vary with supply. Again, it offers no easy way of countering possible "runaway" if high ambient temperature causes the output transistors to draw more current than they should.

It is for this reason that such bias networks often include one or more diodes between the two bases: Not only do diodes afford a measure of regulation but, in reacting to high ambient temperature, they can reduce bias and counter possible output stage runaway.

In the Twin Ten, we have taken the further step of bridging the bases of the output pair with a transistor (Q10), exactly as in the two earlier amplifiers. In this configuration the biasing transistor is often referred to as an "amplified diode" but we prefer the term "Vbe multiplier" as being rather more descriptive of its role.

The transistor configuration has the merits of the diodes mentioned earlier but, in addition, the collector/emitter voltage drop can be varied by means of the 100-ohm pot in the base circuit. This, of course, represents the voltage between the bases of the output pair, so that the 100-ohm preset pot provides a ready means of setting the quiescent current.

Ahead of the class-A driver is a BC549 voltage amplifier (Q6), with the input signal fed to its base and feedback to its emitter.

Because the stages are DC coupled with overall DC feedback, the bias applied to the base of the BC549 determines the mean potential at which its own emitter will stabilise, along with that of the bias network and the emitters of the output stage. In fact, the input bias network (100k, 100k and 220k) was selected with the aid of a CRO for symmetrical clipping and maximum power output. You can verify the choice if you want to but, in practice, and with the use of 5% resistors, voltages should work out closely enough, without further ado.

Incidentally, the 47 μ F capacitor

Performance of prototype

POWER OUTPUT

	One channel	Both channels
4 ohms	8W	7W
8 ohms	12W	10W
16 ohms	8W	7W

FREQUENCY RESPONSE

Phono inputs	RIAA equalisation within 1dB from 30Hz to 20kHz
High level inputs	30Hz to 30kHz \pm 1dB

CHANNEL SEPARATION

(with respect to 8W into 8 ohms)
1kHz -51dB; 10kHz -43dB

INPUT SENSITIVITY

Photo (1kHz)	2.8mV
Overload at 1kHz (.4% distortion)	150mV
High levels inputs	115mV

HUM & NOISE

(with respect to 10mV)

Phono	68dB unweighted
High level inputs	68dB unweighted with 4.7k input load

TOTAL HARMONIC DISTORTION

(Both channels driven into 8 ohms)
1kHz: 0.14% at 1W; 0.3% at 4W; 1.5% at 10W.

TONE CONTROLS

Bass	\pm 12, -13dB at 50Hz
Treble	\pm 13dB at 10kHz

DAMPING FACTOR

at 1kHz	24
at 50Hz	8

STABILITY

Unconditional

between the two 100k bias resistors provides essential decoupling to minimise hum injection into the base of the Q6. The capacitor must be rated to operate at more than 30V and must not be old or leaky, otherwise it will upset the bias levels.

Overall gain of the power amplifier is set by the ratio of the two emitter resistors connected to Q6. For the values specified, 1.5k and 150 ohms, the gain is about 11.

To ensure stability of the amplifier at supersonic frequencies, a 180pF capacitor was added between the emitters of Q6 and Q7. In addition, there is a "Zobel" R/C network across the output and an L/R combination to help cope with the highly reactive

nature of typical loudspeaker loads.

Headphone sockets have also been provided as in the Twin 25 and Twin 40 but the resistors in series with the headphones have been decreased from 330 ohms to 220 ohms to provide a higher proportion of the available power. The sound level with headphones, in fact, subjectively approaches the author's threshold of pain and should satisfy even the most masochistic pop music enthusiast!

As stated earlier, the power output into loudspeakers is about 10W per channel continuous, or 12W on intermittent music peaks. This can sound very loud indeed if fed into loudspeakers of medium (or better) efficiency. Low efficiency loudspeakers



RADIO PARTS GROUP

COMPREHENSIVE CATALOGUE

A FULLY ILLUSTRATED REFERENCE BOOK
WITH MORE THAN 12,000 LINES DESCRIBED IN DETAIL



THE CATALOGUE PRICE MAILING SERVICE

Over many years we have developed an effective computerised price service and catalogue which has become the reference book for the electronics trade. Order your copy now and increase your product knowledge and efficiency.

For your annual subscription of \$20 you will receive:

- 4 illustrated catalogue sections (as they become available).
- a new heavy duty, long lasting silver polypropylene cover fitted with a magazine holder with 6 metal rods for easy insertion of each section and price list.
- Up-dated computerised price services.
- Monthly specials lists, manufacturers surplus stock offers and the latest information on new products.
- Current valve and semi-conductor availability lists.

TRANSISTORS — DIODES — OPTOELECTRONICS — TRIACS

FREE

SEMI CONDUCTOR
SHORT FORM CATALOGUE
TO ALL OUR SUBSCRIBERS
OF OUR COMPREHENSIVE CATALOGUE

Details of the widest range of semiconductor devices available
anywhere in Australia.

ZENNERS — SCR's — TRIACS — REGULATORS — INTERFACE

DIGITAL — LINEAR

CMOS — MOS

TO RADIO PARTS GROUP, PO BOX 124, NORTH MELBOURNE 3051.

PLEASE SEND ME YOUR COMPREHENSIVE CATALOGUE & PRICE LISTS FOR A PERIOD OF 12 MONTHS

Enclosed is my Cheque/Money Order/Order No. (if Account Customer)


or please debit my Bankcard No. Signature: for copies at \$20.00 each.

NAME

COMPANY NAME

ADDRESS

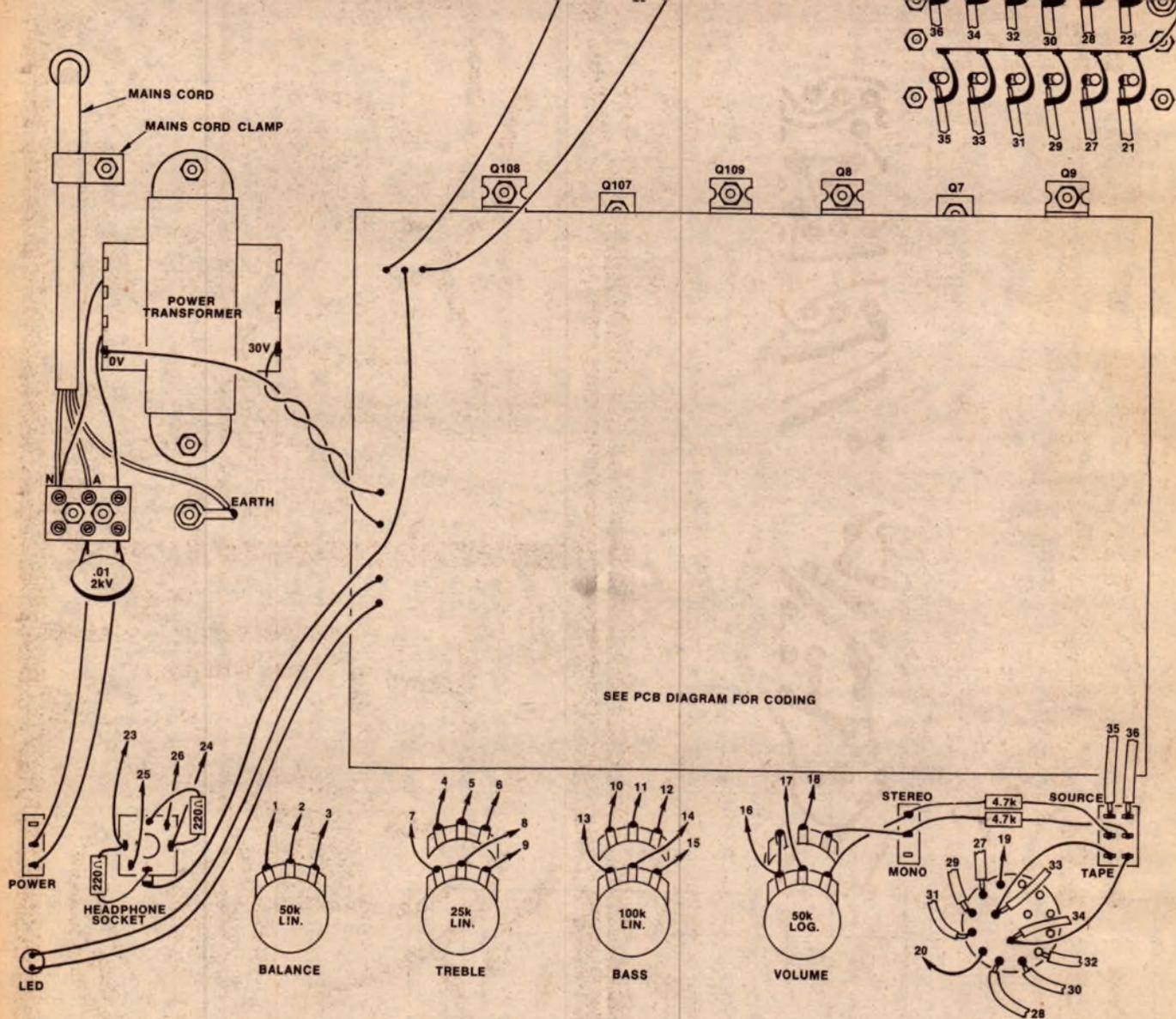PLEASE PRINT CLEARLY TO ENSURE CORRECT MAILING



Use this diagram in conjunction with the PCB layout to complete the amplifier wiring.

with appropriate plastic washers. If these cannot be obtained, cut a suitable thickness of plastic sheet to shape and wrap the bush of the headphone socket with insulating tape.

Although two 1 ohm 1W resistors have been specified for the emitter resistors of the power transistors, holes are provided on the PC board for single .47ohm higher wattage resistors if these are more convenient.

The choke referred to as RFC1 in the circuit diagram is constructed by winding one and a half turns of insulated wire on a 13mm balun core. Use normal hookup wire for the choke and bring the leads out on either side, as in the photograph.

Construction should begin by moun-

ting all components on the PC board. Particular attention should be paid to connecting the tantalum and electrolytic capacitors with the correct polarity (refer to the component overlay or the circuit diagram).

Mounting the transistors should present no special problem, unless you get involved with equivalent types. In this case, double-check the connections before wiring them into circuit.


The power diodes must also be oriented, so check these carefully. If you are still unsure "fire up" the power supply with the fuse and electrolytic removed to check the polarity of the DC output.

Next solder the power and driver transistors to the PC board. These

should be oriented so their metal faces come into contact with the chassis when the board is mounted. Bend the leads up about 2mm from the body and insert them through their respective holes in the PC board so that the leads just emerge from the top of the board; solder only one of each of the transistor leads.

Insert the board supports in the holes provided on the PC board, then manipulate the transistors so that their metal faces are all at the same level as the base of the plastic supports and the mounting holes of the transistors are aligned with those on the chassis. Mount the board temporarily on the chassis to check that the transistors are properly positioned and, if all is well,

79sa5

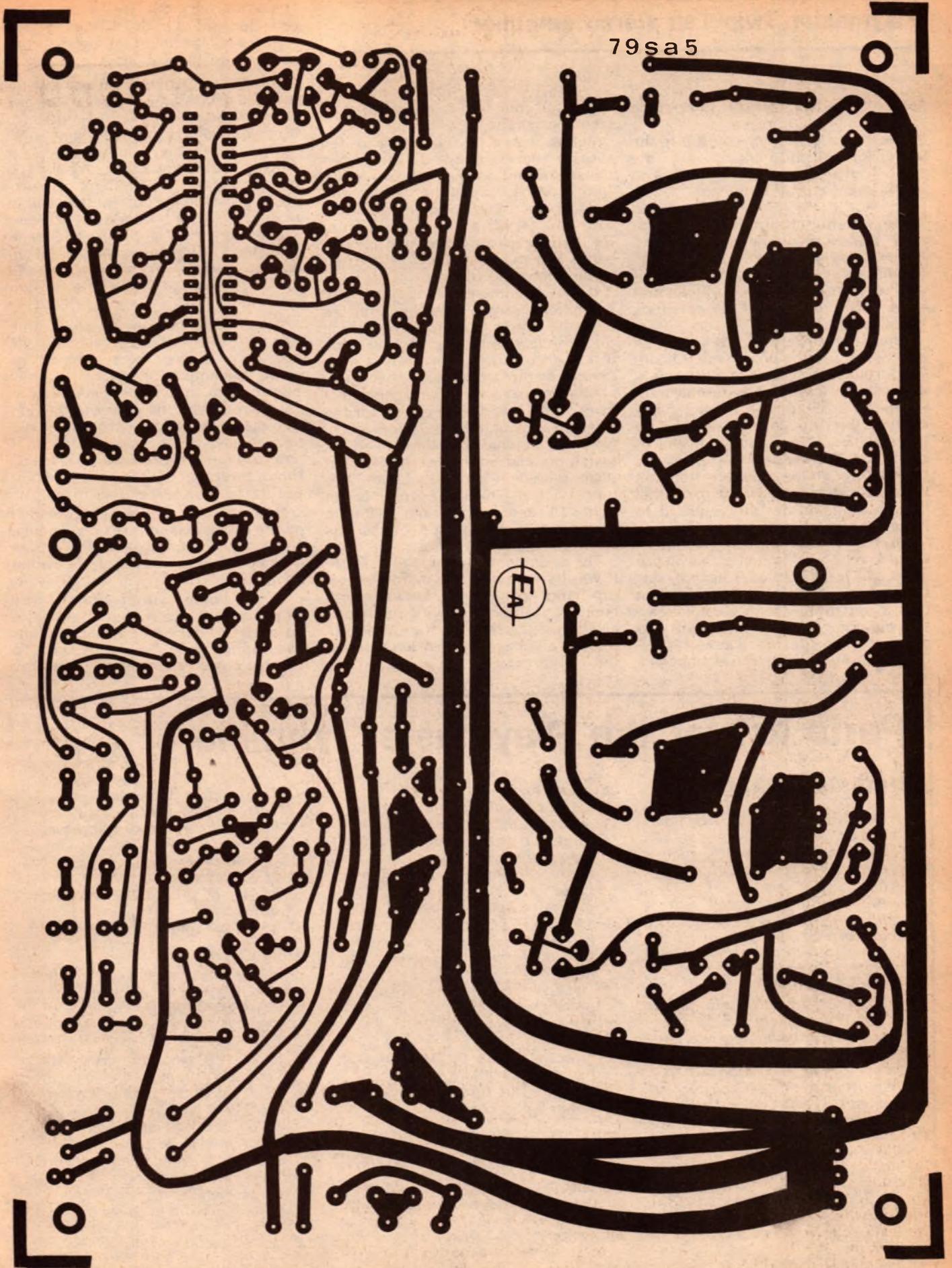

Here is an actual size reproduction of the PC board pattern.

Playmaster Twin Ten stereo amplifier

solder the remaining leads to hold the transistors firmly in place.

The next step is to attach leads to the board for ultimate connection to the tone controls, transformer and loudspeaker output terminals.

The lead to the tone controls should be kept as short as possible and "rain-bow" cable is recommended both for a neater appearance and to aid lead identification. The use of PC stakes is also recommended, since this permits wires to be reconnected without lifting the whole board.

After all the external leads have been attached, insert the board and its board supports into the chassis and prepare to anchor the driver and output transistors. This should be done by first sticking the TO-220 mica washers in place with silicone grease if this is available. Then push the insulating bushes through the mounting holes on the chassis and the transistor. (Note that no insulating bushes are required to mount the BD140 transistors).

Hopefully the power transistors should be isolated from the chassis, but don't take it for granted. Check by disconnecting the phono inputs from the chassis and testing with a multimeter for continuity between the chassis and any part of the circuitry. If a short is discovered, unbolt the transistors one at a

time until the short is removed; then take appropriate action.

Before wiring up the spring loaded speaker sockets, swap two of the terminals around so that the two active (red) terminals are in the middle. This reduces the risk of accidental shorts to earth and facilitates the connection of the .047uF capacitors between speaker earths and chassis via the lugs attached to the mounting screws.

It was mentioned earlier that the headphone socket must be insulated from the chassis so, before connecting the earth lead to the socket, check that it is in fact insulated by using a multimeter or other continuity checker.

Add the mains wiring and check that every thing is complete except for the shielded cabling to the selector switch. Now the amplifier can be readied for switch-on and setting of the output stage quiescent current. Centre the tone controls, turn the volume pot right off and adjust both 100-ohm preset pots so that the BC547 collectors are shorted directly to base.

The optimum current is about 30mA. If you have an accurate millivoltmeter on hand, connect it between the emitters of the respective output pairs and adjust the relevant trim pots until there is a voltage drop of 30mV across the 1 ohm circuit.

Alternatively, cut the link in the collector lead of each TIP31 and bridge it with a milliammeter. Adjust the trim-pot for a reading of 30mA.

Yet again, a 100 ohm resistor can be inserted temporarily in place of the link and the current adjusted to produce a drop of 3 volts across 100 ohms.

There is a tendency for the quiescent current to drift after being set but this is quite normal and is nothing to worry about provided the current stays within reasonable limits. Check the current again after the amplifier has been operated for 10 minutes with the lid on. If the current is now above 50 milliamps, reduce it back to 30 and leave it.

If your amplifier doesn't work, note that there are two links provided on the board which allow the supply voltage to the pre-amp, tone controls and the power stage to be independently disconnected. With the power to the output stage removed, the board need not be mounted to the chassis, so the pre-amp and tone controls can be checked through without the danger of the output transistors overheating.

Note also that the voltages provided on the circuit diagram are only nominal and that the actual voltages measured in your amplifier need only be within about 10%.

When correct operation of the amplifier has been verified, the shielded cables to the tuner auxiliary inputs and tape should be connected. To achieve a neater appearance bind the

Parts list for the Playmaster amplifier

CHASSIS & HARDWARE

- 1 transformer A&R 6672, Dick Smith M-6672
- 1 plated steel chassis 370 x 80 x 245mm (W x H x D) with cover
- 1 front panel
- 5 knobs to suit front panel
- 2 miniature SPST toggle switches
- 1 miniature DPDT toggle switch
- 1 6.5mm stereo jack socket with switch contacts
- 1 LED for pilot light
- 2 6-way RCA socket panels, Ralmar M421 or equivalent
- 1 4-way spring loaded terminal panel, Ralmar ST3 or equivalent
- 1 rotary 2-pole, 4 position switch
- 1 100k (lin) dual ganged potentiometer
- 1 50k (log) dual ganged potentiometer
- 1 50k (lin) potentiometer
- 1 25k (lin) dual ganged potentiometer
- 2 100 ohm large vertical trim pots
- 6 Richo CBS-6N PC board supports
- 4 rubber feet

8 solder lugs

- 1 mains cord clamp and grommet
- 1 3 way insulated terminal block
- 1 three pin mains plug and three core mains cable
- 1 metre of 10 conductor rainbow cable
- 2 metres of figure-8 shielded cable
- 6 sets of TO-220 mounting hardware, ie, mica washers, insulating bushes, plus screws and nuts
- 2 .047uF/100VW ceramic or polyester capacitors
- 1 .01uF 1kV ceramic
- 1 PC board, 79sa5
- 2 fuseclips, Swan (McMurdo) FC1 Part No. 1397-01-18
- 1 1.5 amp 3AG fuses
- 2 13mm balun cores

PRINTED CIRCUIT BOARD

SEMICONDUCTORS

- 4 1N5408 or 100PIV 2 amp silicon diodes
- 1 BZX79/C22 zener diode

- 2 TIP31 silicon power transistors
- 2 TIP32 silicon power transistors
- 2 BD140 silicon power transistors
- 12 BC549, BC184 NPN low noise transistors
- 1 BC337 NPN transistor
- 2 BC547, BC107, BC182 NPN transistors
- 2 uA741 op amp ICs

CAPACITORS

- 1 2500uF/50VW pigtail electrolytic
- 3 1000uF/25VW PC electrolytic
- 2 100uF 25VW PC electrolytic
- 4 220uF 25VW PC electrolytic
- 2 47uF/35VW PC electrolytic
- 2 10uF/25VW tantalum electrolytic
- 2 6.8uF/25VW tantalum electrolytic
- 6 4.7uF/25VW tantalum electrolytic
- 2 1uF/25VW tantalum electrolytic
- 4 0.47uF/25VW tantalum electrolytic
- 2 0.22uF metallised polyester
- 7 0.1uF/60VW metallised polyester (greencap) or ceramic
- 4 .047uF metallised polyester
- 4 .0068uF metallised polyester
- 2 .0056uF metallised polyester
- 2 .0033uF metallised polyester

Special points to watch

- ☆ transistor lead configuration
- ☆ insulation of the output transistors from chassis
- ☆ single point earthing at the point specified
- ☆ insulation of the headphone socket
- ☆ setting up procedure

cables together with cable ties, or if this is unavailable lace the cables together with ordinary hookup wire.

In use, and operating with no signal or at very low volume, the amplifier base will become merely warm to the touch. If it becomes hot under these conditions, there would be clearly something amiss, with the chance that the quiescent current has been inadvertently set too high. With protracted high level operation, the chassis will become noticeably warmer but certainly not such as to be described as "hot".

But there it is: having listened at some length to the prototype, both in the laboratory and in the home, one can only say that its performance completely belies its modest power rating.

- 2 .0012uF metallised polyester or polystyrene
- 4 .001uF metallised polyester or polystyrene
- 2 180pF ceramic or polystyrene
- 2 150pF ceramic or polystyrene
- 2 47pF ceramic or polystyrene
- 2 33pF ceramic or polystyrene

RESISTORS

(5% tolerance 1/4W, unless otherwise noted) 6x 1M, 2 x 560k, 2 x 270k, 6 x 220k, 2 x 150k, 4 x 100k 4 x 82k, 6 x 56k, 8 x 10k, 4 x 4.7k, 1 x 3.3k, 4 x 2.7k, 5 x 2.2k, 2 x 1.8k, 2 x 1.5k, 2 x 1.2k, 8 x 1k, 2 x 330 ohms, 4 x 220 ohms, 2 x 180 ohms, 2 x 150 ohms, 2 x 100 ohms, 2 x 22 ohms 1W, 8 x 180 ohms 1W, 2 x 10 ohms 1 1/4, 8 x 1 ohm 1W, or 4 x 0.47 ohm 5W.

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Where voltage ratings are not quoted, they should be 50V or more. Components with higher ratings may also be used provided they are physically compatible.

SPECIAL PURCHASE OF SPEAKERS & SPEAKER KITS

NEW AWA HI-FI SPEAKER KITS 8" 2 WAY 3 SPEAKER SYSTEMS

AT LESS THAN 1/2 LIST PRICE

POWER RATING 20 WATTS R.M.S. IMPEDANCE 8 OHMS
FREQUENCY RANGE 45 TO 18000 CYCLES

Supplied in kit form (less cabinet) each kit comprises: One AWA 8WAC 8in. bass unit, two AWA 4MBC 4in tweeters with ceramic magnets & curve-linear cones, crossover components, grille cloth, innabond lining and cabinet plans.

\$18.50 PER KIT

CABINETS AVAILABLE
Post & packing extra, NSW
\$2.50, Interstate \$3.50.

RANGE OF MAGNAVOX SPEAKERS STOCKED

SPEAKER GRILLE FABRIC AT 1/2 PRICE

AVAILABLE IN BLACK, BLACK
WITH GOLD FLECK, LIGHT &
MID BROWNS. WIDTH 60in.

\$6.00 Per YARD. post & pack. \$1.00
Send two 20c stamps for samples.

NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS


As featured in Feb. 1976 issue
of *Electronics Today*

Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters. crossover network, innabond, speaker silk and plans of cabinet.

\$87.00 Freight extra
per rail or air freight.
Cabinet available.
Per Kit

RANK- ARENA 2 WAY SPEAKER

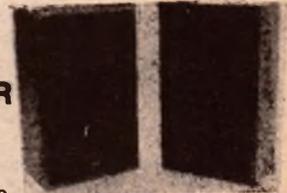- 10 Watts RMS
- 8 ohm impedance
- 8" woofer with tweeter
- Supplied with lead and plug



\$42.00

PER
PAIR

Dimensions
18"H, 11"W, 9 1/2"D
Freight extra
per rail, air or
road transport

GENESONICS 10 SOLID STATE PORTABLE



This sensitive & selective pocket radio using 6 transistors & 4 diodes is suitable for most local & country areas. Fitted with a 2 1/4" speaker and supplied in attractive & durable plastic cabinet. Earphone supplied. Operates on 2 1.5V pen cells.

\$3.95

Post & Packing 90c

GARRARD CC10A RECORD CHANGER \$15.75

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template & instructions. Post & Packing: N.S.W. \$2.50. Inter. \$3.50.

NEW IMPORTED HOKUTONE 12" HI-FI SPEAKERS

These 12" speakers have a frequency range power to 5000 cycles with a resonant frequency of 30 cycles. Max. power 30 watts. Post & packing NSW \$2.50 Interstate \$3.50.

\$17.50

NEW GOODMAN-FOSTER 3-WAY 4 SPEAKER HI-FI SYSTEM


\$39.00 PER KIT

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. RMS Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodman 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components. Condensers and inductance innabond, speaker fabric and plans of cabinet. Cabinet dimensions 23" x 13" x 10". CABINETS AVAILABLE.
Post & packing extra: NSW \$2.70. VIC. SA. QLD \$4.70. WA \$5.70. (REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available.

CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.

A

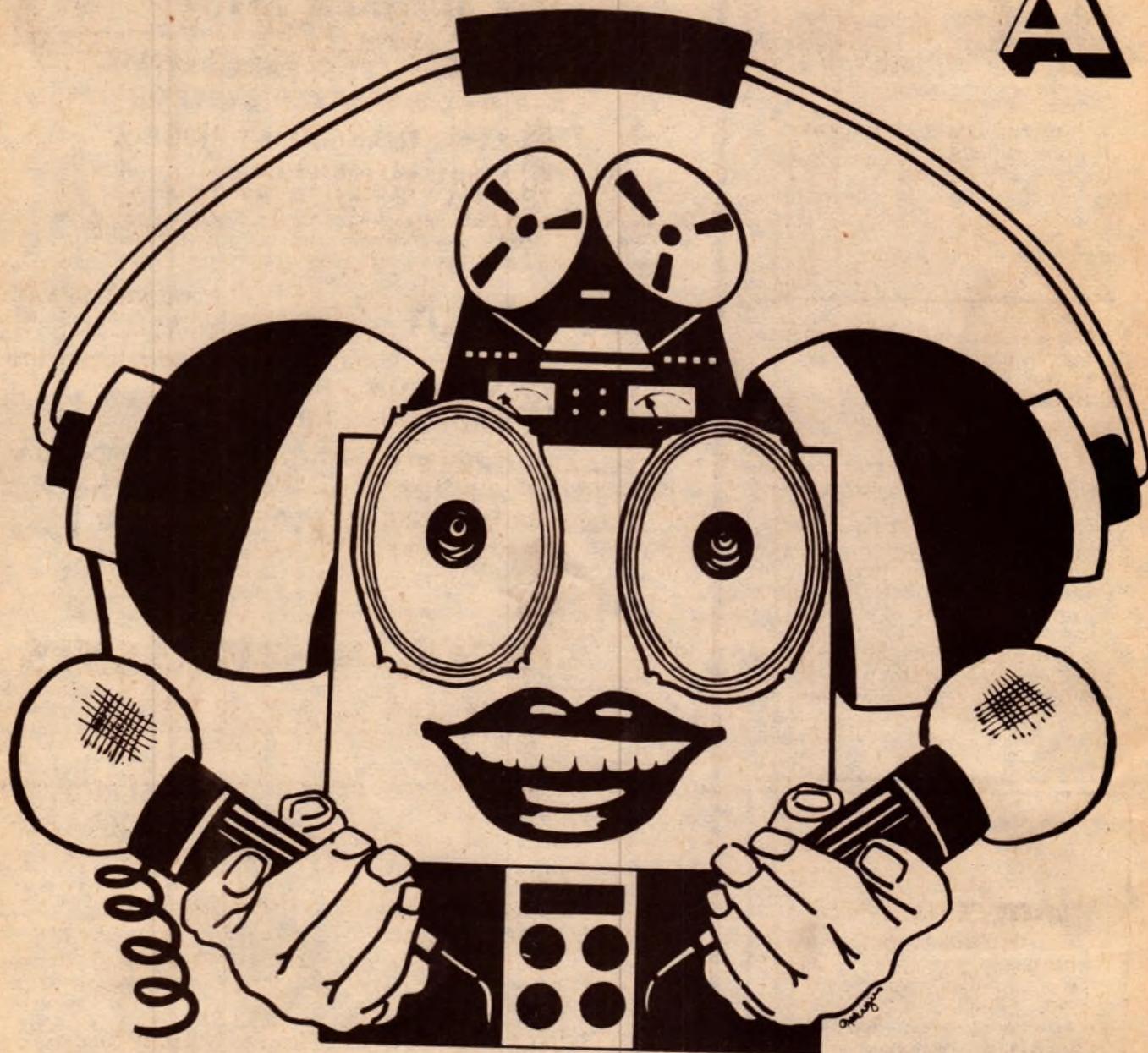

**Audio
Shows**

79

NEW WORLD OF SOUND

The 1979 series of *Australian HI-FI Audio Shows* will be bigger and better than ever. Designed to let you and your family hear and experience the joy of good music. Many of the most famous specialist manufacturers will be represented and demonstrating the widest-ever range of exhibits — record players, amplifiers, cassette and tape recorders, speakers, accessories, in fact everything related to hi-fi.

Special emphasis will be made on *FM stereo radio equipment to allow more people to receive transmissions from the 20 new FM radio stations recently announced.*

If you like music in your home be sure to visit the Audio Show nearest to you — and remember, bring all the family, admission is FREE!

LOOK OUT FOR THE SPECIAL SHOW ISSUES OF 'AUSTRALIAN HI-FI' MAGAZINE

Make a note of the dates and venues:

SYDNEY, Chevron Hotel, Kings Cross:

Friday, 22nd June, 1979 (12 noon to 10 pm)
Saturday, 23rd June, 1979 (10 am to 10 pm)
Sunday, 24th June, 1979 (10 am to 6 pm)

MELBOURNE, Southern Cross Hotel:

Friday, 7th September, 1979 (12 noon to 10 pm)
Saturday, 8th September, 1979 (10 am to 10 pm)
Sunday, 9th September, 1979 (10 am to 6 pm)

BRISBANE, Parkroyal Motor Inn:

Friday, 27th July, 1979 (12 noon to 10 pm)
Saturday, 28th July, 1979 (10 am to 10 pm)
Sunday, 29th July, 1979 (10 am to 6 pm)

ADELAIDE, The Town House, Hindley St.

Friday, 14th September, 1979 (12 noon to 10 pm)
Saturday, 15th September, 1979 (10 am to 10 pm)
Sunday, 16th September, 1979 (10 am to 6 pm)

● **ADMISSION IS FREE!**

● **SEE AND HEAR NEW MODELS**

● **BRANDS FROM AROUND THE WORLD**

● **EASY-TO-ENTER CONTESTS WITH SUPER PRIZES!**

Solder, fluxes, irons — and how to use them

The art of soldering has been part of what we now call electronics since the early days and looks like being around for a long time yet. It presents a minor hurdle for the beginner, but one which must be tackled. This article points out the major pitfalls and discusses the practical requirements for good soldered joints.

by PHILIP WATSON

Nobody gets very far in practical electronics before encountering the need to make soldered joints. While it is possible to get by with screw terminals, clips, twisted wires, etc for elementary — or temporary — projects, anything which is intended to be at all permanent really calls for soldered joints.

The reason is not difficult to understand. A properly made soldered joint comes about as close to a perfect electrical connection as we can get. It provides a low resistance connection between the two conductors, and one which should not deteriorate due to oxidation, as can happen with mechanical joints.

Soldering also offers good mechanical strength, often comparable with that of the conductors themselves, and at least adequate for most ordinary situations.

But note that we referred to a "properly made" soldered joint. Good joints don't just happen; they call for a certain amount of skill. Not a lot, and nothing to get hung up about, but it does involve some effort on the part of the student, and guidance from someone with more experience.

Which leads us to another important point: even though it may appear, superficially, to be normal, a poorly executed solder joint can cause a lot of trouble in service. (Ask anyone who has ever had to track down a "dry" joint in a piece of electronic equipment!)

While we would be the first to admit that the practical skill required cannot be learnt from a book, we can at least put the beginner on the right track.

After that he — or you — will have to learn by doing.

A formal definition of soldering might read thus: "The use of a low temperature molten alloy, flowing over the surfaces to be joined, and adhering to them, a flux being used to assist the adhesion." That is accurate enough as far as it goes.

It is not our intention to delve deeply into the "chemistry" of soldering. This has been done in many other articles, including those in this magazine in November 1962 and January 1963. Our aim here is put the reader on the right track regarding essentially practical requirements.

In a properly made soldered joint the solder will adhere to the metal with ex-

ceptional tenacity. It cannot be prised loose, nor can it be drained off by heating. The structure of the bond is quite complex but it is important to know what constitutes a good joint.

There are two basic requirements:


(1) The metal surfaces must be clean and free from oxides.

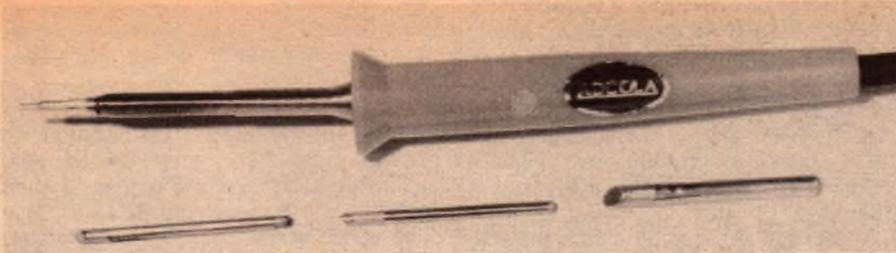(2) The temperature of the metal surfaces must be raised to that of the molten solder.

When these requirements are satisfied the molten solder will "wet" the metal surfaces and flow freely over them. The ability to recognise the "wetting" action is part of the skill to be learned. Also, from the "wetting" concept comes an opposite term: a "dry" joint. It implies that the solder has failed



Solder comes in many forms and grades but, for electronics work, the wire form, with multiple flux cores, is virtually standard. At left is a fine gauge, 0.71mm, and at right the more common 1.6mm gauge. Both are 250g reels.



Typical of modern soldering irons suitable for the beginner is this "Adcola" 240V, 12W unit. As well as the fine tip shown fitted to the iron there are three more tips displayed, intended for heavier jobs.

to wet the metal and therefore has not adhered to it.

Consider first the cleaning: in heavier applications, such as plumbing, it is customary to use files, wire brushes, glass paper, emery paper etc. In electronics, we can usually regard the surfaces as being basically clean as we receive them, since most terminals and wires are tin plated. However, bare copper wire may need to be scraped with a sharp edge or rubbed with glass paper to remove surface oxide.

Unfortunately, no matter how clean the surfaces are initially, they will not stay that way for very long when we start soldering. The act of raising their temperature to that of molten solder tends immediately to create an oxide coating, thus inhibiting the solder bond.

This brings us to the subject of fluxes. What might be termed the primary function of a flux is to provide a protective coating over the surfaces while they are being heated, to exclude the air and prevent the formation of oxides.

Petroleum oils, jellies, or waxes will perform this function and can serve as fluxes in ideal circumstances; they are seldom used in practice, however. The truth is that most surfaces, no matter how bright they might appear, are oxidised to some extent, so that practical fluxes need to provide a secondary function, that of dissolving residual oxides.

Acids as fluxes


Many acids will perform this function very well at, or below, typical soldering temperatures and so we find that most fluxes consist of or contain acid to a greater or lesser extent. These may range all the way from hydrochloric acid (spirits of salts) used by plumbers on galvanised iron to pure rosin for electronic work.

The problem with acid fluxes is that most acids are corrosive and any flux residue left after soldering can continue to attack the surrounding metal, particularly under conditions of high temperature and high humidity. This is not much of a problem for the plumber, who can slosh a bucket of water over the job and wash away the residue, but it can be a serious problem in electronics.

Corrosion in electronic equipment simply cannot be tolerated, particularly where fine wires are concerned, as in coils. It can eat away such wires, rendering the equipment useless.

It is for this reason that a lot of care has gone into the development of "non-corrosive" fluxes for the electronics industry, and also why the range of suitable fluxes is rather restricted.

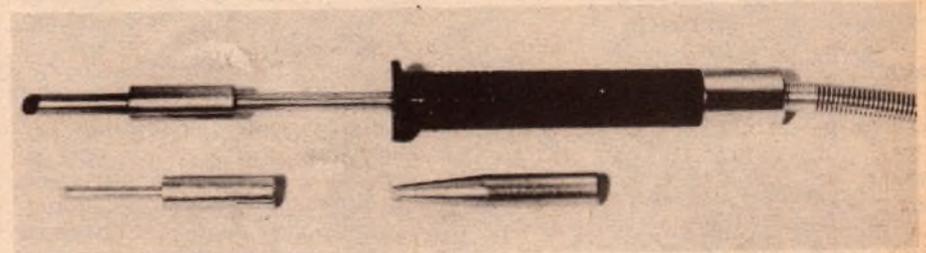For many years rosin was the standard and almost exclusive flux used in electronic equipment, usually in the form of a core in thin wire solder. Rosin releases an acid (abietic acid) at typical



Typical of low voltage irons is this "Mico" 12V, 10W unit, together with three of the most commonly used tips. Although requiring a transformer, many people prefer the smaller, lighter irons available in the lower voltage types.

soldering temperatures, but becomes inert again when it cools.

But pure rosin is still not the ideal flux. Where individual components have more than a certain amount of oxide coating and/or are contaminated with other foreign matter, rosin is not equal to the task. The result is a dry joint and, in mass production, it is inevitable that a percentage of these will not be recognised by the operators, or during subsequent inspection, and will go into the field. Sometime later they appear as intermittent faults.

This led to the development of activated fluxes; rosin fluxes to which are added small quantities of chemicals which release an acid vapour when heated and which makes for a much more effective flux. They are still regarded as "non-corrosive" because most of the chemical acid is vapourised and any that remains is rendered inert by the solidified rosin. This forms a hard glossy surface over the metal and protects it from any atmospheric moisture which might activate residual chemicals. In practice, they work extremely well.

This brings us to basic requirement

(2) which we listed earlier: that the temperature of the metal surfaces must be raised to that of the molten solder.

We normally melt the solder onto a joint by means of a hot copper bit, "tinned" with a coating of solder, and which is the business end of a complete implement commonly called a soldering iron.

The need to raise the temperature of the metal surfaces to that of molten solder should be obvious. The solder cannot remain molten while it is in contact with a metal surface at a lower temperature. Even if the main body of solder remains molten because it is in contact with the bit, there will be a thin layer against the cooler metal which will become solid.

"some authorities advocate . . ."

So important is this requirement, that some authorities advocate that the solder should never be applied to the bit, the bit being used only to heat the metal to the point where it (the metal) will melt the solder when it is applied. In this way the operator can be sure that

the metal is hot enough, since it will not melt the solder otherwise.

The theory behind this is sound enough, and it is often applied in practice, particularly in heavier duty applications, such as plumbing. "Yorkshire" fittings are a typical example, where a flame is used to heat the metal pieces until they melt the built-in solder ring, which then flows and completes the joint.

Conflicting requirements

Unfortunately, it is not quite that simple in the electronics field. A conflicting requirement here is to protect adjacent components and materials from excessive heat, while still ensuring that adequate heat is applied to the actual joint. To apply the aforementioned technique is to risk taking so long to complete the job that other components may be damaged.

One reason is the difficulty of making good thermal contact between the bit and the work, particularly as the latter may be irregular in shape. By flowing a little solder between the bit and the work, we use the solder to conduct the

Solder, fluxes, etc.

heat to a much larger area than can be reached by the surface of the bit alone.

This heats the metal quickly and, when it is hot enough, the solder will wet it and flow freely over the surface. Recognising this condition is part of the skill of soldering. A classic mistake is to observe that the solder flows freely over, say, a solder lug, but to neglect to check that it also flows correctly over the wire passing through the lug. The result is a wire passing through a hole in the solder, but completely "dry".

A bad habit, when using cored solder, is to carry molten solder to the job on the tip of the bit. This is a carry-over from situations where the flux is applied separately, before the solder. When using cored solder most, or all, of the flux can be vaporised in the time needed to convey the solder to the job. This applies particularly to the more volatile chemicals used in activated fluxes.

The practical approach

As a result of all the factors we have discussed, most workers follow a fairly standard procedure when making a joint. When using new components, already tinned, it is reasonable to assume a basic cleanliness; at least to the point where the flux will take care of slight contamination or oxides.

Normally, the bit and the solder is applied to the job at the same time and a little solder melted onto the tip of the bit to aid thermal conductivity between the bit and the job. When the solder flows, more can be applied if the size of the job demands it, preferably to the job rather than the bit.

Although the solder is designed to set quickly, it is important that no movement of the parts should occur during the setting period. If it does, it can produce a faulty joint, similar to a dry joint, at least as far as the end result is concerned.

Where one or more of the parts to be joined are other than bright and shiny, extra care is necessary. The usual procedure is to treat such components separately, before attempting to make a joint. Excessive dirt or oxide is best removed by scraping with either the blade of a knife or fine glass paper, until bright metal is revealed. The surface is then "tinned" with a coating of solder, particular attention being given to the manner in which the solder flows. If any doubt exists the process should be repeated.

The need to make joints quickly is most evident when working on printed boards. Prolonged heating can destroy the bond between the copper and the

base material, allowing the copper to lift. On the other hand, the copper pattern normally accepts solder very readily, the boards being sprayed with a protective coating, which is also a flux, while the copper is still bright. As a result, the solder should flow over the copper almost immediately it is applied.

Another factor which helps is that the mass of copper involved in any part of a printed board is very small, therefore reaching the required temperature very quickly. Be aware, however, that this may not apply to the wire being soldered to the pattern; it may form part of a substantial component and so take somewhat longer to heat.

In the event that a printed board joint does not "take" immediately, do not continue to apply heat and try to force the situation. The result will almost certainly be a damaged board. Back off and determine what has gone wrong. If it is a dirty pigtail, for example, clean it and tin it away from the board, before trying again.

So far we have made only passing mention of solder, flux, and the soldering iron, without delving too deeply into the practical form in which these are found. For the beginner, some elaboration is justified.

Electronics grade solder is normally supplied in wire form, with a core, or cores, of activated rosin flux. It is normally a 60/40 tin/lead alloy, the proportion being chosen deliberately because it combines a low melting point with rapid setting.

"Wire" solder is available in a variety of wire gauges, the most popular in the past being 16SWG or 1.6mm, and 18SWG or 1.25mm. More recently, thinner gauges, such as 22SWG or 0.71mm, have become popular for use with miniature components and, particularly, complex printed board patterns. Such boards often have terminating pads very close together and it is all too easy to apply excessive solder and thus bridge adjacent points. Thinner solder makes the amount applied easier to control.

The 250g reel is a popular size and, although it may look expensive, one reel will last the average hobbyist a long time.

Multiple flux cores

The use of more than one core of flux — five is a popular number — is intended to reduce the risk of no flux being available at a particular point, due to minor breaks in the flux continuity. The reasoning is that it is unlikely that several cores will all suffer a break at the same point.

There is a large variety of soldering irons available; so large that it is beyond the scope of this article to deal

with them all in detail. We may do that in a separate article. However, we will give a brief summary of the more usual types.

All are heated electrically and include 240V types for direct connection to the mains, and low voltage types operated from a transformer. Typical power ratings are from 10W to 25W. There are quick-heat types, which are turned on only when a joint is to be made, variable wattage types with manual adjustment, and automatic constant temperature types.

The more elaborate types may be hard to justify at hobby level, and a simple type, of about 15W rating, either 240V or 12V will suit most beginners. The quick heat type is handy in situations where there may be long breaks between joints, as when developing a circuit, but they are rather more expensive, and call for some additional skill in their use.

Care of the bit.

All irons are fitted with a removeable bit, since this will need to be replaced eventually. This also allows a variety of bit shapes and sizes to be used, according to the job requirements. In any case, the bit should be removed at regular intervals and both it and the barrel cleaned of scale. Failure to do so can result in the two becoming "frozen" together, with the chance of the iron being damaged in trying to free them.

The first thing to be done with a new bit is to tin it, by giving it a coat of solder over the working faces. Shape the bit, if necessary, with a file, then allow it to reach working temperature. This will normally cause the formerly bright copper surface to darken with the formation of oxides and may prevent the solder from wetting it, flux notwithstanding. A good idea is to give each face a quick rub with the file, while hot, then apply solder immediately.

In use it is desirable to clean these tinned surfaces if they become oxidised, usually by rubbing with a scrap of cloth. When the tinning shows signs of pitting or breaking up, the faces should be filed down to copper and retinned.

And that about sums up the soldering scene as it applies to the electronics hobbyist. Having digested all that we have said, it remains to put it into practice. Try making up some simple dummy circuits, but preferably using previously unsoldered pigtails, terminal lugs, etc. A little practice should enable the reader to appreciate the various points we have made throughout this article, and set him on the road to becoming a skilled worker.

But never take this skill for granted. Even the most experienced worker can make a dry joint if he becomes careless — every joint needs to be made with care.

ONCE ONLY!
SCOOP PURCHASE
 OF ENTIRE STOCK FROM MANUFACTURER!
FAMOUS SHARP 64 STEP
PROGRAMMABLE PROFESSIONAL
DESK CALCULATOR

500 ONLY
 SIZE 140(w) x 80(h) x 227(d)mm

240V AC OPERATION
 YOU'LL NEVER NEED
 TO BUY A BATTERY!



- † 240V AC OPERATION — NO BATTERIES REQUIRED
- † 15 DIFFERENT SCIENTIFIC FUNCTIONS 10 BUILT-IN PROGRAMMES
- SUPER INTELLIGENT
- † 10 DIGIT MANTISSA 2 DIGIT EXPONENT 6 WORKING REGISTERS 8 MEMORY REGISTERS
- † FULL 48 PAGE INSTRUCTION MANUAL
- † TRIG INVERSE TRIG HYPERBOLA EXPONENTIAL LOG FACTORIAL AZIMUTH POWER AREA TO NAME JUST A FEW FUNCTIONS
- † USE AS A 4 FUNCTION DESK CALCULATOR AND IMPRESS YOUR FRIENDS WITH THE EXTRA BUTTONS! (DICK DOES)

Cat. Q-3016

CALCULATOR PRICES ARE RISING — THIS COULD BE YOUR LAST CHANCE so ORDER NOW!

7 DAY, NO OBLIGATION TRIAL — SIMPLY RETURN IN ORIGINAL CONDITION FOR ANY REASON AND WE'LL REFUND YOUR MONEY

WAS \$184.00
NOW AN INCREDIBLE \$49.50
YES!
YOU REAP THE BENEFIT

ADD \$3.00 FOR POST AND PACKING ANYWHERE IN AUSTRALIA

DICK SMITH ELECTRONICS

NSW 125 York Street, 147 Hume Highway, 162 Pacific Highway, 30 Gross Street	SYDNEY Phone 290 3377 CHULLORA Phone 642 8522 GORE HILL Phone 439 5311 PARRAMATTA Phone 683 1133	ACT 96-98 Gladstone Street, VIC 399 Lansdale Street 656 Bridge Road QLD 186 Logan Road SA 203 Wright Street WA 414 William Street	FYSHWICK Phone 80 4544 MELBOURNE Phone 67 9834 RICHMOND Phone 428 1614 BURANDA Phone 391 6233 ADELAIDE Phone 212 1962 PERTH Phone 328 6944
---	---	---	---

Opening soon in WOLLONGONG. Watch for store address!
 EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.
MAIL ORDER CENTRE: PO Box 747, CROWS NEST NSW 2085 Ph 439 5311. PACK & POST EXTRA

bankcard
 welcome here





SHOPS OPEN 9AM to 5.30PM
 (Saturday: 9am till 12 noon)
 BRISBANE: Half hour earlier.
 ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY
 RE-SELLERS OF DICK SMITH PRODUCTS IN MOST AREAS OF AUSTRALIA

sanwa

... the long term reliable multimeter.

N501 Multimeter The executive choice!

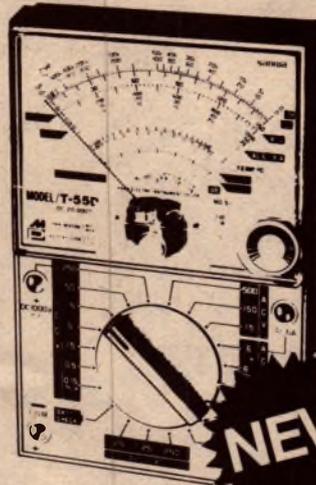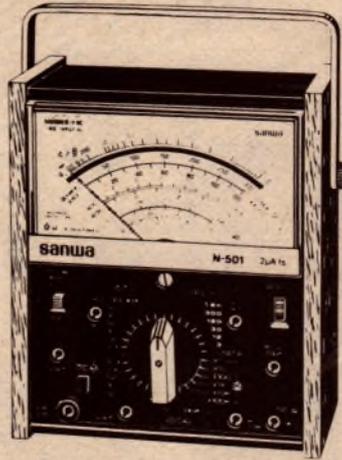- Measurements similar to a VTVM can be taken as the N501 has a constant $1M\Omega$ input impedance on the ACV ranges.
- Widespread coverage of the principal measurements is available as the N501 has AC + DC Volts to 1.2kV, AC and DC Amps to 12 Amps and 6 resistance ranges to 200 $M\Omega$ s.
- Attractive, 9mm thick walnut sideboards help protect the multimeter from accidental damage.



T-55 THD Multimeter (T-55D c/w optional temperature probe)

The latest lightweight
with heavyweight
features!

- Adds a temperature capability ($-50^{\circ}C$ to $200^{\circ}C$) to the newest thin-dimension multimeter. Lets you measure the temperature of industrial and commercial appliances or individual component heat.
- Offers a multi-role multimeter to cover normal requirements plus AC Amps, battery test, LED test and temperature selections.

NEW



U-60D UNIVERSAL MULTITESTER

- $44\mu A$ movement—quality performance, diode protected
- Stable ACV measurement—solid-state rectifier & enlarged frequency coverage.
- Linear scale characteristic—common scale reading for DCV and ACV
- Semiconductor test—simultaneous reading of load current & voltage with Ω
- Temperature measurement of $-30^{\circ}C$ to $+150^{\circ}C$ with extra probe



PDM500C INSULATION TESTER

- Easy push button operation.
- Large easily read scale.
- No wearing parts (transistorized for long trouble-free life).
- One-man operation—no handle to crank.

Specifications
Rated Voltage 500V.
Resistance 100 Megohm.
Effective scale reading:
0.1—100—200 Megohm.
Continuity Scale: 0—100 ohms.
Including vinyl-leather case with lead pouch, shoulder strap and insulated test leads.



460-ED MULTITESTER THE BEST BUY IN MULTIMETERS

100,000 ohms per volt
with $\pm 2\%$ accuracy for DC
ranges with only 10
microamperes loss at full
scale. H.F. current blocking
when making DC
measurements.

- $10\mu A$ movement— $100k\Omega/V$, varistor protected
- Polarity reversal switch—negative measurements
- Equalising transformer—common shunts & jacks for 1.2A & 12A DC/AC



BX-50S MULTITESTER

- Fast-response, $24\mu A$ movement—fuse & diode protected with high resolution factor ($0.4\mu A$ /scale division)
 - Revised scale marking—intermediate readings readily determined
 - Polarity reversal switching—negative measurements
 - Series capacitor terminal (OUTPUT+)—AF output level check
- RANGES: AC & DCV to 1.2kV (30kVDC with optional probe). AC & DCA to 12 amps



WARBURTON FRANKI

- ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841
- MELBOURNE 699-4999 • PERTH 277-7000 • SYDNEY 648-1711
- AUCKLAND N.Z. 77-0924 • WELLINGTON N.Z. 698-272

Circuit & Design Ideas

Conducted by Ian Pogson


Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

A comprehensive cable tester

Many of the faults in an audio system are caused by cables. Have you ever tried to find which cable is broken among the many connections in a stage audio system, especially with anxious people looking over your shoulder? One answer is to check each cable before the performance, a rather tedious business.

This cable tester checks not only for continuity and shorts to earth, but also shows up shorts between conductors and transpositions. This last point can be important as some DIN-to-DIN cords have deliberate transpositions. Also, since most cables will have different connectors at each end, with all sorts of custom wiring arrangements, we need to see at a glance which pin is connected to which.

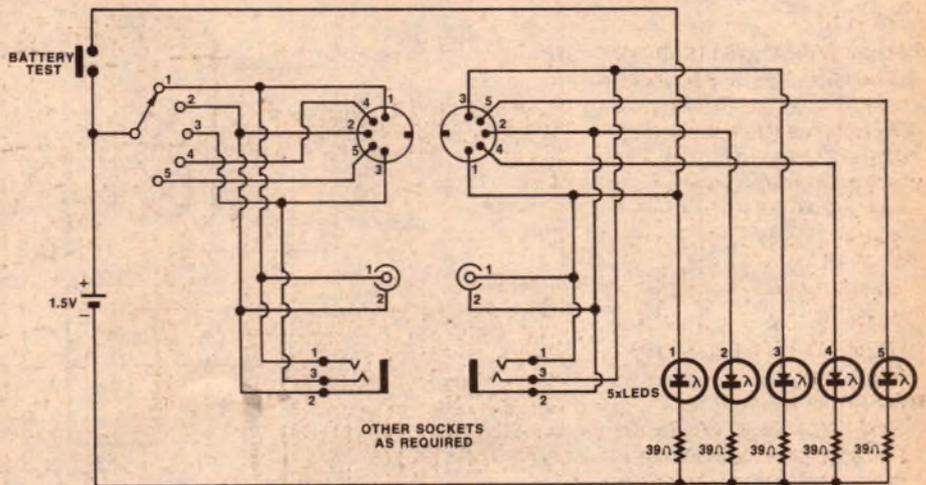The author has seen a design for a cable tester which does not show up transpositions, only tests for shorts to earth, can only cope with one inter-connection scheme between different connectors, uses a mains supply, two transistors, one FET and a TTL IC. It was probably published as a joke. One would hope so anyway.



The design presented here is powered by a single dry cell and needs no power switch since the act of plugging in a cable completes the circuit. The battery test button is operated momentarily before using the device. LED No 1 should light, indicating that the battery is OK.

In operation, the rotary switch is used

to select each conductor in turn and the appropriate LED should light. If more than one LED lights, you have a short. If they light in the wrong order, you have a transposition. If none lights, you have an open circuit.


(By Mr G. Leadbeater, 16 Ellison Street, Ringwood, Victoria 3134.)

General-purpose fault-finding probe

This probe may be used as a convenient substitute for the normal multimeter when fault tracing, since it eliminates the need to keep stopping to switch meter ranges etc. It provides an indication of the presence of either AC or DC potentials (indicating which) between 1.5V and about 500V, whether there is continuity between two points and some indication of the resistance between the two points. Of course it does not measure potentials and only gives a rough indication of ohms — but when carrying out quick checks on a piece of equipment this is not necessary, at least during preliminary checks.

The whole unit can be built into a small insulated case, for example the housing of a penlight flashlight, and operated from a miniature mercury battery. For other forms of construction a conventional battery could be used.

When the test leads are placed across

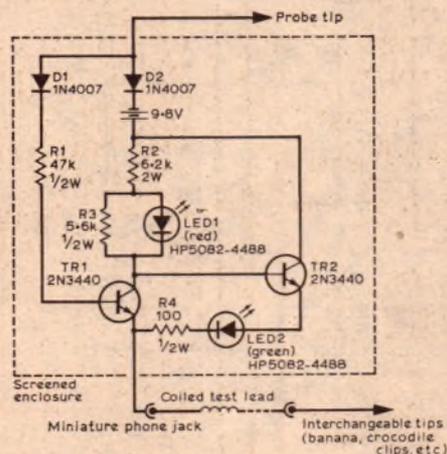

two points between which there is continuity but no potential difference, current from the internal battery forward biases TR2 and turns it on. The green LED then lights, but the small base current is not sufficient to cause

the red LED to light. The lower the resistance between the two points, the brighter the green LED. If the resistance is more than about 5k neither LED lights. One can use this facility not only to test component and wiring continuity, but also the operation of wipers on potentiometers etc. If the external circuit includes a semiconductor, the green LED lights only when the probe tip is connected to the N-type material, and this provides a further useful test.

Should the probe tip be connected to a point more than about +1.5V with respect to the test lead, the emitter-base junction of TR2 is turned on and the red LED lights, with the green LED staying dark. If neither LED lights, even when the test lead and test probe are interchanged, the two points are either open circuit or have more than 5k resistance between them. If the red LED lights no matter which way round the test lead and test probe are connected, then the potential difference between

the two points must be AC.

A few minutes' practical use with the fault finder is likely to underline its usefulness rather more than this description. The feature that seems really attractive is that the various checks can be carried out quickly, without having

to keep fiddling with the range switch of a multimeter.

The test leads should be kept from touching when not in use to prevent drain on the battery. For this reason, the test lead should be made

removable although a possible alternative, eliminating the need for the miniature jack and socket, would be to have an insulated cap fitting over the probe tip when not in use.


(From "Radio Communication".)

Opto-coupled magnet driver for teleprinters


This circuit will drive 30mA through the selector coils of a tele-printer and connects to the 20mA output of a microprocessor board, at the same time avoiding ground loops. Diodes D5 and D6 ensure that Q1 and Q2 can be completely turned off. Resistor R5 sets the current through the printer magnet coil. The value of $V_b + (R_4 / (R_5 \times V_b))$ governs the peak voltage appearing at T2 collector, with a 1:1 ratio then the peak will be 140V. The parallel resistance of R4 and R5 governs the collector current passed by T2.

A BF336 transistor was used for Q2 because it was readily available, but any NPN transistor with adequate V_{cbo} and I_c max could be substituted.

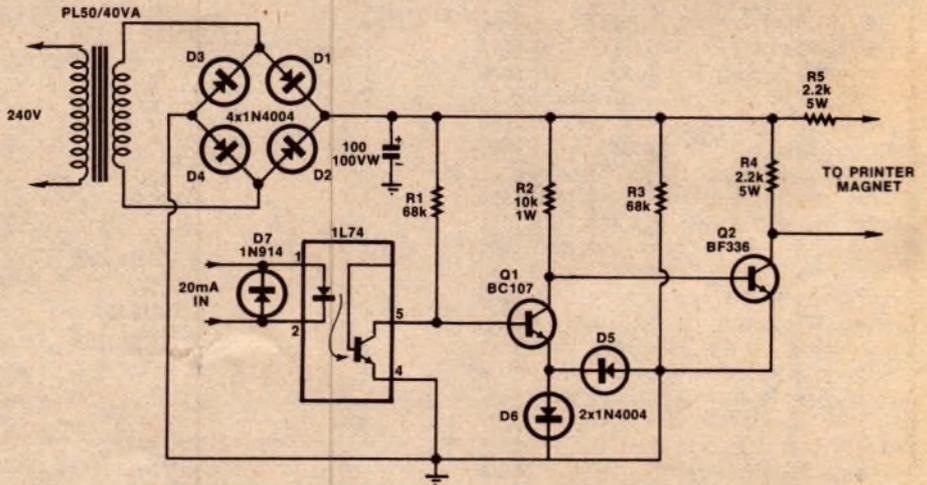(By Mr W. Gummerson, 13 Hindmarsh Road, Liverpool, NSW 2170.)




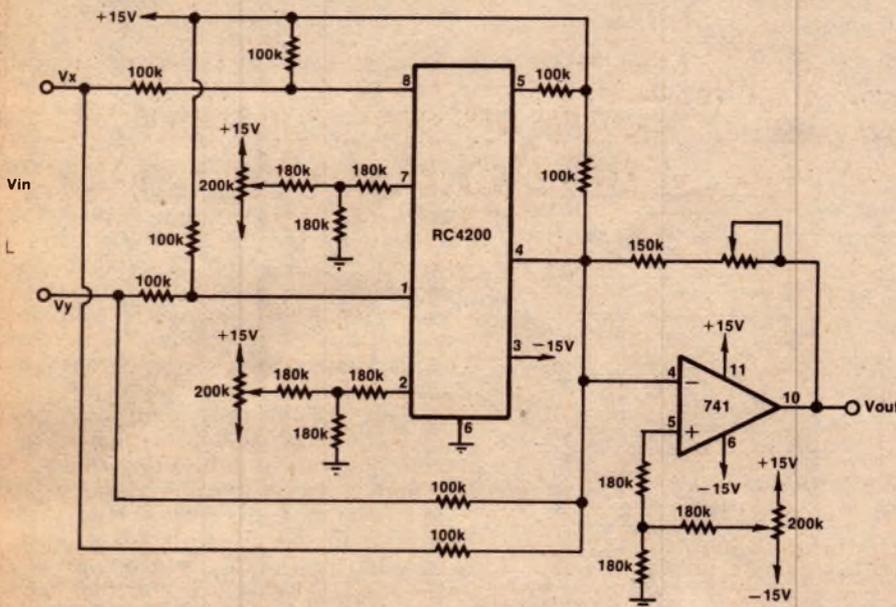Recording DC power using a chart recorder.



If you wish to keep a continuous record of DC power levels using a chart recorder, it is best to plot voltage squared, as power is then given by the area under the graph. In an experiment at Hartley College of Advanced Educa-

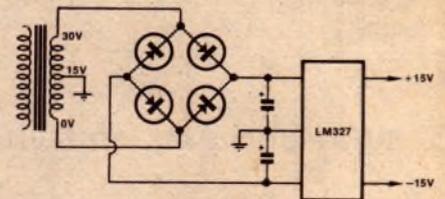tion, we wanted to record the daily power output of a silicon solar cell. We found that the circuit shown, based on the Raytheon RC4200 multiplying amplifier, was well suited to our requirements.




The following points may be of interest to readers wishing to construct the circuit: the RC4200 chip is very sensitive to voltage drift in the power supply. Our original power supply, using zener diodes, was not stable enough. The 4200 chip is linear only if the offsets on pins 2 and 7 are correctly adjusted. The offsets are easier to set if a 10k potentiometer is connected in series with each 200k potentiometer for fine adjustments. The drift in the circuit is less than 4mV.

(By Messrs R. D. Goodwin and P. Spooner, Hartley College of Advanced Education, 15 Lorne Avenue, Magill, SA 5072.)

Order your copy now of the
"ELECTRONICS AUSTRALIA"
PROJECTS & CIRCUITS NO. 2
 \$3.00 plus 60c p & p
 Electronics Australia,
 Box 163, Beaconsfield, NSW 2014

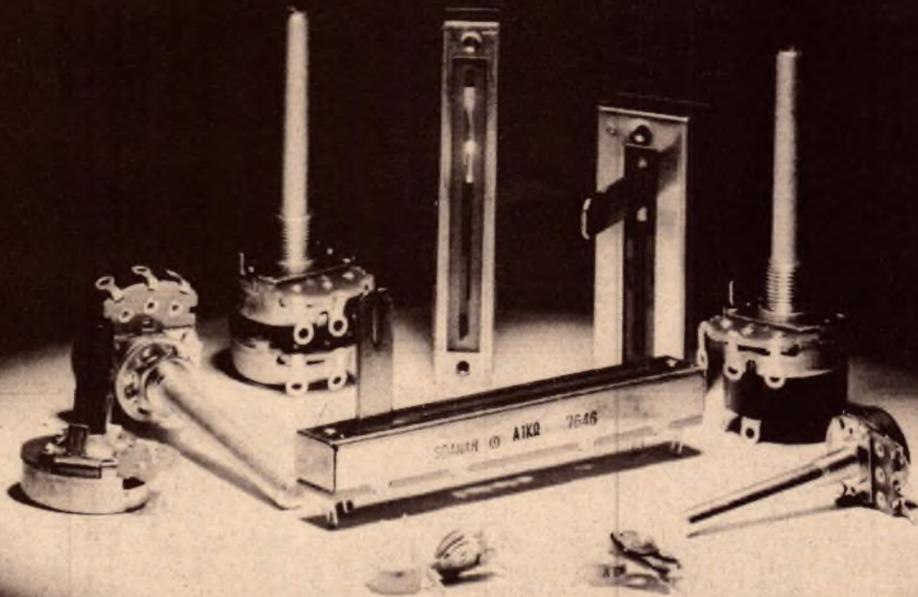Potentiometers for industrial and consumer electronics.



**CARBON · CERMET · TRIMMERS · PRESETS · ROTARY
SLIDE · STANDARD · MINIATURE AND WIREWOUND**
AVAILABLE EX STOCK IN ALL STATES

SOANAR

SOANAR Electronics Pty Ltd

A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP

30-32 Lexton Road, Box Hill, Vic., 3128, Australia. Telex: 32286.



SALES OFFICES PHONES
VICTORIA: 89 0661
N.S.W.: 789 6733
S. AUST.: 51 6981
QUEENSLAND: 52 5421
W. AUST.: 381 5500

Add inductance ranges to the direct-C meter

With a small amount of additional circuitry, the direct reading capacitance meter described in January can be arranged to measure inductance as well. This brief note gives the details.

The January 1979 issue of Electronics Australia featured an inexpensive, direct reading capacitance meter operation on the principle of charge storage to determine capacitance. With the addition of a few components plus some component value changes, the same basic meter can be used in a dual role for rapid measurement of inductance as well as capacitance.


The range of inductance measurement is from 3 microhenries to 3 Henries full scale, with a lower measurement limit in the order of 0.1 μ H set by stray inductance of the test leads. Measurement is possible even in the presence of moderate shunt capacitance or resistance.

Absolute accuracy of the meter cannot be compared with a precision RF bridge, but speed and convenience make it useful for construction, measurement or comparison of RF chokes, peaking inductors, loudspeaker crossovers, TV coils, IF transformers, audio filters, CRT scanning coils etc. Simplicity, component

availability and ease of calibration make the meter suitable for home construction. A variety of meter movements and calibration scales, such as 0-50 μ A or 0-100 μ A, can be accommodated by appropriate component variations.

In operation, the 555 timer switches the 2N3643 transistor rapidly between the on (saturated) and off states. During the on state, current through the test inductor builds up to a steady-state value determined by the effective series resistance in the collector circuit of the 2N3643. When the 2N3643 is switched rapidly off, decay of the inductor current generates back EMF to force an alternative current path through the 1N914 diode and meter circuit. It can be readily demonstrated that the time-averaged value of this current is directly proportional to the test inductance value.

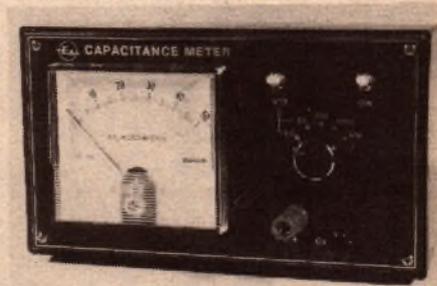For normal use, the L x 100 range is employed to minimise errors caused by inductor series (winding) resistance. The L x 1 range is used for very small inductances, or to reduce errors caused




The original capacitance meter, described in the January 1979 issue. Low in cost, it reads from a few pF to 5 μ F.

by unavoidable shunt capacitance and resistance.

A few brief experiments with a 1mH choke, or a short circuited 2 metre length of TV ribbon, plus a handful of resistors and capacitors to act as parasitic impedances, will soon establish a working familiarity with the meter. With appropriate techniques even magnetising and leakage inductances of gapless ferrite or iron cored transformers can be measured.

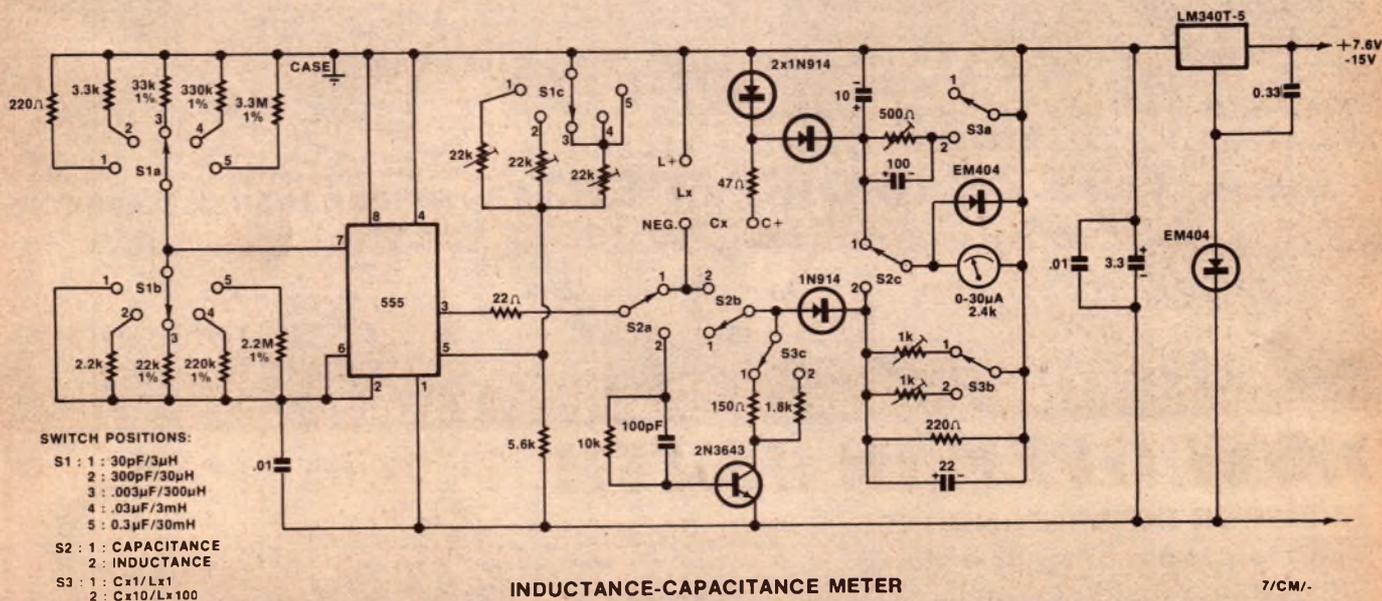You might be able to squeeze the meter into the original case, but it would probably be better to use the next size up.



Here is the complete circuit of the expanded meter. Only a handful of additional parts are required.

COMPARE OUR PRICES FOR VALUE-PLUS TOOLS . . .

ALL THE POPULAR SIZES — AT BUDGET PRICES!

MINI

30mm
Flat Cat T-4010
Philips Cat T-4020

30c ea
40c ea

STUBBY

45mm
Flat Cat T-4060
Philips Cat T-4065

95c

BABY

FLAT BLADED, 3 LENGTHS
50mm Cat T-4070
100mm Cat T-4075
200mm Cat T-4080

35c
40c
50c

POPULAR

FLAT BLADE, 2 SIZES
75mm Cat T-4085
150mm Cat T-4090

50c
80c

HEAVY

FLAT BLADED, 2 SIZES
75mm Cat T-4095
125mm Cat T-4100

80c
\$1.25

PHILIPS

3 POPULAR SIZES
75mm Cat T-4030
100mm Cat T-4040
125mm Cat T-4050

40c
85c
75c

JEWELLER'S SET

Chrome plated precision screwdriver set, complete in plastic storage case. 2 Philips, 4 flat blade

\$3.95

TV ALIGNER KIT

Versatile set of 4 alignment tools for general service work. Cover all shapes of cores, tough plastic const

\$2.50

GENERAL PURPOSE TOOL BOX



427 x 230 x 200mm. This handy polypropylene box is ideal for tools, fishing goods, artists, hobbies, etc. Foldaway compartments, locking provision

Cat H-2800
\$17.50

ADJ. HOLE CUTTER

\$6.90



Will cut holes from 23mm to 100mm in aluminium, plastic, wood, copper & steel. High quality USA made, locks positively into electric drill for easy cutting. Comes with instructions & turning speeds. Cat T-4870

NIBBLING TOOL

'Nibbles' any shape hole in sheet steel up to 0.6mm thick, light alloy to 1.5mm. A highly useful tool to add to your tool kit.

\$12.50



Cat T-4940

40 PIECE SOCKET SET

Top value 40 pieces both metric & SAE ideal for the hobbyist and home mechanic. Complete with ratchet drive. Ideal gift! Cat T-4870

\$16.50



MINI DRILL PC DRILL

Handheld drill ideal for PCB's, model making, jewellery, craft work, etc. Powered by two 'C' batteries. Fits drills 0.8 - 1.2mm. Batteries extra.

\$15.00



Stand to suit also avail. Cat T-4752: \$15.00

WATCH THIS SPACE AND FIND OUT WHAT YOU MISSED

Each month all of our stores feature an outstanding special which is actually BELOW COST! N.B. Specials are strictly while store stocks last. Don't miss out!

LAST MONTH: A 3 PIN MAINS PLUG:

Was 55c — now 30c
SAVING
near 50%!

DICK'S BULK BUYING BONANZA BARGAINS.

Reap the benefit of Dick's incredible bulk purchasing power. Here are just a couple of extraordinary bargains for hobbyists
2200uF/50V power supply electros
How much would you expect to pay? \$2.00, even more? You can buy these highly useful electrolytic capacitors from Dick from only 80c each. Famous 'Rubicon brand', ideal for power supplies, etc.
Cat R-4575 \$1.00 ea
(10 up 80c each)

SPST MICROSWITCHES:
Normally \$2.00 or more each — now from only 50c each. They're ideal for use in burglar alarms as limit switches, etc. etc. 240 volt rating. Buy now and save with this massive scoop purchase.
Cat S-1918 60c ea. (10 up 50c)

SUPER SPECIAL: 2114 Memory IC's at almost half price. 4k static RAM's, ideal for the experimenter, were \$14.50 NOW \$7.90. Be quick for this bargain!
Cat Z-9306

BOOKS
Dick has an incredible range of books for all interests. Call in to any of our stores for a browse. You're welcomed!

BOOK OF THE MONTH:
THE BASIC HANDBOOK, by Dr David Lien. 360 pages. This book is an ideal reference for anyone using BASIC lang: in detail the favourite microcomputers, as used on micros. of BASIC as used on micros. minis and main frames.
Cat B-2335 \$15.95

SUPERSOLDERER!

How's this for value? Incredible bargain 15 watt 12 volt soldering iron — was \$5.50, now only \$3.95. It comes complete with a car cigarette lighter plug and is ideal for all those jobs around the car, caravan, etc.
Cat T-1910

\$5.50 \$3.95

WELLER CORDLESS

Quality iron has re-chargeable cells, comes complete with charger. In-built light to help solder in dark places and is an ideal iron for use just anywhere. Easy to hold, too.
Cat T-1050

\$26.00

HI FI BUYERS . . .

Have you seen the superb new range of Dick Smith Hi Fi? Amplifiers, Tuners, a Dolby Deck, brand new and backed by the resources of the Dick Smith Electronics organisation.
See our other double page advert in this magazine describing the new range. Then go and see it in the Hi Fi Centre at your nearest Dick Smith Electronics store

SPARE TIPS ALWAYS IN STOCK FOR EITHER IRON.

BATTERY ELIMINATORS

CALCULATOR POWER SUPPLY
3V DC
150mA \$9.75
Save money when using your calculator at your desk. Ideal for all models which use 2 'AA' batteries (up to 150mA). 3.5mm plug fitted.
Cat M-9512

9V ELIMINATOR
9V
200mA \$5.95
Use this one anywhere a 9V battery would have been used. Up to 200mA output, suitable for radios, models, etc.
Cat M-9514

12V DC
450mA \$16.50
Cat M-9515
Yes, a whopping 450mA from a plug-pack. It's ideal for hand held CB radios, burglar alarms, etc. etc. — anywhere a nominal 12 volt, medium current supply is required.

IT GLOWS IN THE DARK

HOW HANDY! A switch rated at a massive 16 amps (12V) which has an in-built lamp to glow in the dark. Ideal for use in cases, promotes safer driving. Soft red glow won't dazzle you.
Cat S-1214 \$1.75

INSTRUMENTS FROM DICK:

SIGNAL INJECTOR

Here's one of the handiest little pieces of test gear you'll ever own — whether you're a beginner or an old hand, a signal tracer helps you solve many electronic problems. Find a serviceman who hasn't got one! This unit has a useful output from audio right through to HF, and includes a battery in the low, low price. Outstanding!

AC BRIDGE

Yes! You can accurately measure inductance, capacitance, resistance, transformer turns ratio, component comparisons, etc. etc. with this versatile instrument. It's battery operated (supplied), and includes a spot oscillator for a variety of different frequency checks. Size 215 x 135 x 70mm.

'DIPPER'

We don't have to tell amateur operators how handy a dipper is! But all electronics hobbyists should know the incredible usefulness of these instruments. Use them:
● As a signal generator ● To check circuit Q & resonance ● As an absorption wavemeter ● To check for harmonics ● To check AM modulation, etc. etc. How have you lived without one until now?

PRO-QUALITY MULTIMETER

This incredible multimeter would be a bargain if it was just a multimeter. 100kV, up to 10A AC & DC, etc. etc. etc. But it is more than a multimeter! It also measures transistors and capacitors! Yes, all this built into one of the handiest pieces of test gear going. The Dick Smith Multimeter/Transistor checker/Capacitor meter. A bargain!

\$69.50
Cat Q-1140
BUY DIRECT FROM THE IMPORTER & SAVE!

THIS CB IS DIFFERENT:

It is guaranteed for a whole TWO YEARS by Dick Smith. That's right, two year guarantee — with the backing of the Dick Smith organisation. You can't go wrong with a Dick Smith CB.

The WASP: Dick's deluxe AM transceiver with LED readout, up to the minute styling and RF gain control. Outstanding value for the CBR, also ideal for the amateur to convert to 10 metre operation.

FULLY APPROVED POWER SUPPLY
13.8 volts at a massive 4A peak — ideal for SSB as well as AM sets. Also great for a bench supply for any nominal 12V equipment.
Cat M-9545 \$39.50

Cat D-1820 \$89.50

Southern Star
12V DC POWER SUPPLY

1/2 PRICE TRANSISTOR PACK!

We still have a few experimenter's transistor packs left (you may remember them from February Electronics Australia). These transistors are ideal for the hobbyist, and at the price we are offering them for other exceptional value for money.
There are twenty transistors in all, equivalent to BC108's, BC107's, BC157's and BC158's.
PACK OF TWENTY TRANSISTORS: \$2.50 (plus 50c P&P)
(normal price for twenty transistors of this type approx. \$5.80!)
These transistors are guaranteed brand new, and are all within manufacturer's specifications. They are NOT seconds or surplus rejects.
Available through all Dick Smith stores, many Dick Smith re-sellers and the Dick Smith Mail Order Centre.


NOW OPEN IN PERTH

AND SOON IN WOLLONGONG!
Don't forget our other new stores:

CANBERRA: 96-98 Gladstone St Fyshwick, Ph 80-4944
HONG KONG: 39 Ashley Rd, Kowloon, Ph 3 689 352

PERTH: 414 WILLIAM STREET. PH. 328 6944

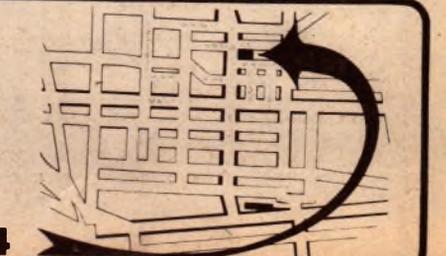Dick is now the best in the West! Yes, the new Dick Smith Electronics Centre is now open right in the heart of Perth. Our West Australian friends can now join the thousands of happy East Australian customers who enjoy dealing with the Electronic Dick.




SIMILARLY OPTIONED COMPUTERS SELL FOR THESE FIGURES:*

SORCERER:	\$1,434.50
TANDY TRS-80:	\$1,828.00
APPLE II:	\$2,887.00

SO WHY NOT SAVE UP TO 50%?

The Sorcerer computer is far and away the best value for money. But don't take our word for it. All you need do is compare any similar computer at present on the market, and list all of its features vs the Exidy Sorcerer. Sounds like too much work? The write for a copy of our new 4 page brochure. We've done it all for you. A straight, point-by-point comparison. No punches pulled. The brochure is free for the asking at any Dick Smith Store (or write to us c/- our Mail Order Centre and we'll send you a copy)

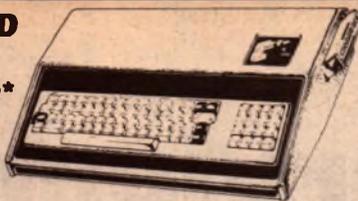

SEE DETAILS OF OUR NEW LINE PRINTER ON P89.

LOW COST MONITOR
Suits Exidy Sorcerer, Tandy, Apple, etc. Don't pay over \$200 for a monitor
Brand new & guaranteed - 12V DC/240V AC operation!
Cat X-1198 **\$149.50**

Basic 8k Sorcerer	Cat X-1190	\$1095.00
16k Sorcerer	Cat X-1192	\$1250.00
Cassette Recorder	Cat A-4092	\$35.00

* Price comparison based on currently advertised prices and information. All prices include sales tax; for full breakdown and analysis see the brochures mentioned above.



PARTS FOR NEW KITS

PLAYMASTER STEREO EQUALIZER (See EA May)
Complete kit including instructions Cat K-3500 \$99.50
UA41 36 Quad Op Amp Cat H-3184 \$3.60
PC Boards (set of 3 high quality boards) Cat H-8360 \$12.95

INTERSL LCD EVALUATION KIT (See Feb EA)
As used in the EA digital voltmeter Cat K-3450 \$39.50
6 DIGIT CLOCK (See Feb EA)

Complete kit, including instructions Cat K-3495 \$19.75
Case with mounting bracket and bezel Cat H-8357 \$9.75
AC Mains adaptor Cat H-9514 \$5.95

PLAYMASTER AM/FM TUNER (See Nov/Dec EA)
Complete kit, including instructions Cat K-3494 \$129.50

SEPARATE PARTS
Pre-wired and aligned tuner module Cat F-4610 \$59.00
Set of 4 PC boards Cat H-8357 \$9.75
Signal strength meter Cat Q-2100 \$4.95
Tuning meter - centre zero Cat Q-2095 \$4.95

Most other electronic parts for this project in stock

MODEL TRAIN CONTROLLER (See Oct EA)
Not produced as a kit - all parts available from stock

PCB only Cat H-8355 \$3.75
Zippy box Cat H-2752 \$3.00
2N3055 transistor Cat Z-2145 \$0.95
2N3053 transistor Cat Z-2130 \$0.80

FET INPUT AC-DC VOLTMETER (See Sept EA)
Not produced as a kit - all parts available from stock

PC board only Cat H-8353 \$2.75
1mA MRA-65B panel meter Cat Q-2060 \$12.50
Fabricate your own meter scale using Scotchcal 8005 black Scotchcal photo-sensitive aluminium Cat H-5694 \$6.00
CA-3140 FET op-amp Cat Z-5417 \$2.50

VARI WIPER Mk2 (See Sept EA)
Not produced as a kit - most parts available from stock

Relay Cat S-7125 \$4.80
C1010V1 SCR Cat Z-4315 \$1.00
2N2646 (DS2646) unijunction Cat Z-1786 \$1.20

UPGRADED 40/200MHz FREQUENCY COUNTER (See Aug EA)
Same as previous kit, but new circuitry means it's easier to build, set up and is more sensitive. Basic counter is 40MHz - by adding a single 95H90 IC the range is extended to 200MHz.

Complete kit for 40MHz, including instructions Cat K-3437 \$99.50
96H90 IC to extend range to 200MHz Cat Z-5360 \$12.50

SEPARATE PARTS
PC boards (set of two high quality boards) Cat H-8346 \$8.50
MC 10118 IC (triple differential amplifier) Cat Z-5415 \$1.95
MM-5363M IC (oscillator - divider) Cat Z-5781 \$2.50
74C92B IC (4 digit counter) Cat Z-5414 \$6.50
3 579545MHz crystal Cat K-6031 \$3.00
LT-303 7 segment display Cat Z-4103 \$1.50

All other components are normal stock lines at all of our stores.

WHAT'S NEW VIDEO BRAIN KEYBOARD

INCREDIBLE SCOOP PURCHASE!


Full function computer-style keyboard
● 37 Keys
● Silver Plated Double Sided PCB
● Double Sided Edge Connector (0.1")
Contains: All alphabet letters, 0-9 numerals, shift, %, X, +, - keys as well as !, " @ C / () \$ p : ; ' ? etc

High quality computer-grade push buttons with interchangeable tops!

Yes, it is true! The manufacturer of this quality keyboard has gone broke so you reap the benefit! This keyboard must have cost twice as much to manufacture as the price we are asking for it! All keys can be individually accessed by cutting PCB tracks.

DOUBLE SIDED EDGE CONNECTOR (0.1 SPACING)

37 KEYS!

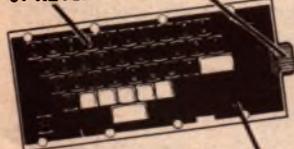

SILVER PLATED DOUBLE SIDED PCB

UNBELIEVABLE

\$17.50

Cat. X-1182

STOCK DUE IN MID JUNE. PLEASE RING & CHECK!

HEAT EXCHANGE ENGINE

IT REALLY WORKS!

Yes, this is an actual scale model of a 'Stirling Cycle' engine which you can use to power models, or demonstrate the principles of external combustion. Comes with a beautifully presented book describing Stirling Cycle theory & operation.

A great talking point at trendy parties, too!

\$39.95 VALUE!

X-1500

See a shrink!

Our popular heatshrink pack is back in stock! Popular sizes, ideal for the hobbyist!

200 pack

W-4060

16k UPGRADE KIT - SUITS TANDY, APPLE, SORCERER

Why pay up to \$430 and more when you can do it yourself in minutes. And save a fortune!

NEW!

\$149.50

(Cat X-1185)

★ Upgrade Tandy, Apple & Sorcerer to 16k, and/or Apple or Sorcerer 16k to 32k. Complete with easy instructions which YOU can follow

You can save \$280 by installing the expansion kit yourself!

And all our IC's are guaranteed brand new, prime spec devices. Don't be conned into paying \$400 or more. Do it yourself and save!

(Extra switches required for Tandy/Apple conversion - 2 for Tandy, 3 for Apple. Cat S-1808 DIP switch \$2.75 ea.)

WHAT'S NEW PUSH BUTTON TELEPHONE DIALER WITH MEMORY

• Ideal hobby use
• For private & experimenter's phone systems
• Dial quicker - remembers last number dialled (Simply push 1 button for auto re-dial up to 16 digits!)



ATTENTION: Although these diallers fit perfectly into standard Australian telephones (no soldering required) present regulations do not allow you to use them for this purpose.

X-1175 \$49.95

WHAT'S NEW DOOR ALARM/CHIME UNIT

Use it to scare away intruders - or welcome visitors. Unique door guard senses door opening, and depending on setting, chimes or sirens. 3-way on/button combination 'lock' allows legitimate entry.

\$29.50 L-6100
EASY DO-IT-YOURSELF INSTALLATION

MAIL ORDER SPECIAL

Incredible value! Quality EM C-30 cassettes at a fraction of the price you'd expect. Ideal for letters, lectures, computer use, music, etc etc etc. And look at the price again!



75¢

(SORRY - This special is for mail order customers only. Personal shoppers: watch your store for in-store bargains.)
10 or more 60¢ each! Cat C-3030

AMATEURS

THE YAESU PRICE WAR IS STILL ON !!!
Reap the benefits NOW - see our advert in the amateur radio magazines for full details

SHEER LUXURY!

Imagine! That first cold seat of a winter's morning could be the most delightfully warm seat you'll have all day. The Dick Smith warmed toilet seat. Perfectly safe, perfect luxury!



\$32.50

A COLD SEAT CAN RUIN YOUR WHOLE DAY!

CALLING BIG CONSTRUCTORS

The answer to space problems: This huge rack mounting case. Quality construction, measures a huge 425x250x140mm. Comes as shown with handles & pre-punched ventilation holes. Professional quality.



\$49.50
ROOM FOR EVERYTHING INCLUDING THE KITCHEN SINK!

SEND FOR OUR FREE COLOUR KIT CATALOGUE

MAJOR DICK SMITH RESELLERS

Listed below are the names and addresses of resellers who stock a large range of our products, however we cannot guarantee that they will have all items in stock and at the prices advertised.

- AAM Electronics**
78 High Street, Wodonga, Vic Ph 244 588
- Aero Electronics**
123A Bathurst Street, Hobart Tas Ph 348 232
- Brian Bambach Electronics**
88 William Street, Gosford, NSW Ph 247 246
- Coastal Electronics**
Unit 11 Commercial Centre, Ford St Moruya NSW Ph 742546
- Crystal TV Rentals Pty Ltd.**
86 Crispin Street, Broken Hill NSW Ph 6897
- Elektron 2000**
44 Brown Road, Broadmeadow, Newcastle NSW Ph 691 222
- Hutchesson's Communications**
5 Elizabeth St, Mt Gambier, SA Ph 258 404
- Keller Electronics**
218 Adelaide Street, Maryborough, Qld Ph 214 559
- Liamora Ktronics**
Cnr Magellan St & Brunner Hwy, Liamora NSW Ph 214 137
- M&W Electronics**
48 McNamara St, Orange NSW Ph 628 491
- Q.M. Electronics**
99 Fitzmaurice St, Wagga NSW Ph 213 044
- Summer Electronics**
95 Mitchell St, Bendigo Vic Ph 431 977
- Sound Components**
78 Brisbane St, Tamworth NSW Ph 661 363
- Advanced Electronics**
5a The Quadrant, Launceston Tas Ph 317 076
- Trilogy Electronic Supplies**
40 Princes Hwy, Fairy Meadow, Wollongong NSW Ph 831 219
- Tropical TV Services**
249 Fulham Rd, Vincent, Townsville Qld Ph 791 421
- Variety Discounts**
113 Horton St, Port Macquarie, NSW Ph 835 488

bankcard welcome here




SHOPS OPEN 9AM to 5.30PM (Saturday: 9am till 12 noon)
BRISBANE: Half hour earlier.
ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY
RE-SELLERS OF DICK SMITH PRODUCTS IN MOST AREAS OF AUSTRALIA.

DICK SMITH ELECTRONICS

NSW 125 York Street, 147 Hume Highway, 182 Pacific Highway, 30 Gross Street,	SYDNEY Phone 290 3377 CHULLORA Phone 842 8922 GORE HILL Phone 439 5311 PARRAMATTA Phone 883 1133	ACT 98-98 Gladstone Street, VIC 399 Lansdale Street, 858 Bridge Road, QLD 186 Logan Road, SA 203 Wright Street, WA 414 William Street,	FYSHWICK Phone 80 4944 MELBOURNE Phone 67 9834 RICHMOND Phone 428 1814 BURANDA Phone 381 8233 ADELAIDE Phone 212 1962 PERTH Phone 328 6944
--	---	--	---

Opening soon in WOLLONGONG. Watch for store address!
EXCEPT WHERE NOTED, ALL ITEMS SHOWN IN STOCK AT PRICES GIVEN AT TIME OF GOING TO PRESS.

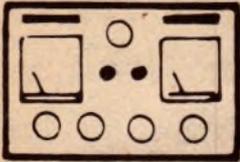MAIL ORDER CENTRE: PO Box 747, CROWS NEST NSW 2065. Ph 439 5311. PACK & POST EXTRA.



The Serviceman

The same symptoms, but quite different faults

The fact that identical symptoms do not mean identical faults may cause the layman to believe that he has either been "ripped off" — if the "same" job for someone else was cheaper — or that he is up for an expensive repair; again on the basis of someone else's experience.

This point was brought home rather forcibly by a couple of jobs I handled recently; the symptoms were virtually identical, but the nature of the faults — and the costs to the customers — were about as different as one could imagine.

The first job involved a National 26in set and, according to the owner, the screen was flooded with bright blue light to the point where, according to him, he could see nothing else on the screen. He added that the set seemed to behave normally when first switched on until about a minute after the picture appeared. As it turned out, this was an interesting observation.

There is not much point in trying to chase faults like this in the customer's home, so I brought the set back to the shop. And, while I hoped it wasn't the tube, this is one of the easiest things to check before delving into the works, so I did this first.

According to the tester all three guns showed normal emission, and there were no indications of any internal shorts. Feeling somewhat relieved on the customer's behalf, I was about to disconnect the tester when one of the short indicator lamps suddenly lit up. It was for the blue gun, and indicated a heater to cathode short. Small wonder that the blue gun ran amok, with all the bias removed.

Well that was straightforward enough, but I realised that I had nearly been caught. I hadn't taken sufficient notice of the customer's comment regarding the delay after switching on, before the fault appeared. Had I switched the tester off a few seconds earlier I would have imagined the tube was OK and wasted a lot of time checking the rest of the set.

Unfortunately, faults of this kind mean a new tube, and this is never the happiest news to pass on to a customer. In this case I was even less happy, since I knew that the customer wasn't particularly well off.

For a while I pondered on the possibility of using an isolating transformer to allow the heaters to float at the cathode potential. Such an idea is not new and it would certainly solve the problem as far as the DC potentials were involved. Unfortunately, it isn't quite as simple as that. The heater in the faulty gun is now at video potential, along with the cathode, and no matter how it is fed there is bound to be a substantial capacitance between it and chassis; the last thing that can be tolerated in a video circuit.

So, rather reluctantly, I scrubbed the idea. The next best approach was to fit a rebuilt tube rather than a brand new one, and I suggested this to the customer. This put him in something of a quandary; while he was worried about the cost, he didn't altogether trust the rebuilt tube idea — a not uncommon reaction. To help him decide I pointed out that these tubes are completely re-gunned and that the only active part of the tube which remains is the screen; something which experience has shown has a very long life, typically 10 years for average usage.

I went on to say that my own experience with these tubes had been a completely happy one. Quite a number of customers have used them on my recommendation, and I have had no cause to regret it.

I don't know whether that convinced him or not, but the price difference certainly did. A rebuilt tube is only about half the cost of a new one in most cases, and it also carries a new tube guarantee. That clinched it and he gave me the OK to go ahead.

Hardly was that job back in the customer's lounge room before another customer walked into the shop and calmly announced that he had a TV set in which the screen was flooded with green light. Had it been April Fool's day, I would have suspected someone was pulling my leg. But it wasn't, and they weren't, so I did

my best to keep a straight face.

At the same time, it would have been understandable had I suggested that he had a faulty tube. I didn't, in spite of the temptation, simply because I don't believe in making snap diagnoses based on guesswork. I have known some who did this, and it can sound very impressive at the time, but it can also rebound in a most embarrassing manner when the guess turns out to be wrong.

On top of that, the picture tube is about the worst thing one can guess at. It is probably the most effective way of convincing the customer that you are setting him up for a rip-off. He is just as likely to decide to "think about it", and that will be last you will see of him.

So, having resisted the temptation for all these good reasons, it rather set me back when I realised that some Job's comforter had already been at work on the customer and virtually convinced him that he would need a new tube. And, with stories of hundreds of dollars for a new tube, he wasn't very happy, particularly as the tube was only just out of warranty.

He wanted to know straight out if it could be the tube. And, of course, I had to answer truthfully that, yes, it could be the tube. But I hastened to add that it could be something else instead; like a faulty colour amplifier transistor.

Then he wanted to know how much it would cost. (I hadn't even seen the set at this stage, or even been told what make it was.) I explained, as briefly as possible, that it was not normally possible to quote for radio or TV repairs. The cost of the repair cannot normally be assessed until the fault is found, by which time a significant proportion of the work will already have been done. Whether I convinced him or not I don't know.

On the other hand there was no point in being deliberately unhelpful. Having determined the make and size of the set — it was a 26in Blaupunkt — I told him that, if he needed a new tube it would cost around \$200, plus fitting at the normal hourly rate. If he cared to settle for a rebuilt tube it would cost him a little over \$100, plus fitting as before. It is wise to allow a couple of

hours for fitting, even though it can usually be done in less.

As with my previous client, he wasn't too keen about the rebuilt tube idea, at least initially. After I had spelled it out in detail, and he'd thought about the price difference, he seemed more reconciled to the idea.

If it wasn't the tube, then the situation was less clear. I could only quote him the hourly rate I would charge, to which would have to be added the cost of components. Finally, I offered to test the tube for him, at no charge, if he was able to bring the set to the shop. If it turned out not to be the tube he could please himself whether I should proceed.

Rather surprisingly, he jumped at that. Not many people are keen to manhandle a 26in set into a vehicle and out again, but he seemed to think that he could organise it, and that it would be worth it. So we left it at that.

Sorry about that!

In my April notes I referred to an article on high voltage power line interference which appeared in the IREE "Proceedings".

Unfortunately I quoted two issues; November and December 1978. This has caused some problems for the IREE, particularly as the reference created considerable interest.

To set the record straight, the correct issue was DECEMBER, 1978.

Sure enough, a couple of days later his car pulled up outside and he and a friend manhandled the set into the shop. He wasn't able to wait while I tested the tube, but gave me a phone number to call when I had checked it. However, I did establish the vital piece of information that the fault did not normally show up until the set had been running for about 10 minutes. Remembering the previous job, I was glad I asked.

So I connected the tube to the tester and checked each gun for shorts and emission. Initially, at least, I could find nothing wrong, so I left the tester connected and the tube heaters running for the next 15 minutes or so. When nothing showed up in that time I re-connected the tube to the set and switched on.

As I expected, the picture came up normally and ran that way for the next 10 minutes or so then, just as the customer had said, there was a green background and faint retrace lines. There was still a picture from the two remaining guns, but with distorted colour values.

At this point I considered that the green colour amplifier was the most likely culprit and, in the ordinary way, would have made some voltage measurements at emitter, base, and collector. But not so with the Blaupunkt. The colour board carrying

these amplifiers is mounted hard against another board in such a way that it is impossible to get at these points. (It might be a nice set, but I wish the design engineers would think of the serviceman sometimes.)

The next best thing was to pull the board out and see if I could find anything with the ohmmeter. In particular, I measured between base and emitter and base and collector of the green amplifier, hoping to find either a short circuit or open circuit. In fact, there was no sign of either and, as far as this simple test was concerned the transistor was OK. Nor could I find any other faulty components in the green section.

So I replaced the board, switched on, and waited for the green to show up again. It did so after about five minutes and I deliberately let it run for the next couple of hours. During this time the green became progressively stronger, until it eventually wiped out the image from the remaining guns. As a check I disconnected the green lead from the tube, whereupon the red and blue images reappeared.

But that was by the way. What I really wanted was to get my meter prods on the board while it was good and hot. So, with everything at the ready, I whipped the board out and jabbed the prods between base and emitter of the green amplifier. It read open circuit. I moved one prod over to the collector and found that the base to collector was also open circuit.

"Gotcha, you beauty!"

From then on it was plain sailing. A new transistor was fitted and the set left running for the rest of the day, and for a couple more hours the next morning. With no sign of trouble I rang the owner and told him he could collect it any time he liked.

Naturally he was very happy, and even happier when I answered his tentative query about the cost. Since he had handled the transport of the set I had charged for one hour's labour, plus a dollar and something for the transistor — a tiny fraction of what he had feared when he suspected the picture tube.

I have an idea he will come back to me if he has any more troubles.

Looking back on the technicalities of the fault there is one point that puzzles me; while it is easy enough to visualise the transistor failing when it became hot, I cannot quite explain why it remained open circuit when it obviously could not have been passing any current.

I can only assume that there was sufficient heat from the red and blue transistors — the green one is in the middle in this set — to maintain this condition once it occurred. They are certainly close together and are fitted with small heat sinks, so this is quite possible.

But I still wish that board was accessible while in the set.

Lafayette))

VHF/UHF Scanning Type
Radio Broadcast Receiver

Bearcat[®] 210



The BEARCAT 210 is an advanced scanning receiver with digital frequency readout and push-button programming — no crystals required.

- 10 Channels within range 146-174 MHz, 416-512 MHz.
- Decimal frequency display.
- Push-Button Keyboard for easy frequency selection.
- Automatic track-tuning for optimum performance on all channels.
- Channel Lock-Out and Delay facilities.
- Automatic Search facility. Will electronically tune between selected frequencies, lock-on and display frequency of received signals.

An advanced technology receiver providing manual or scanning type operation on up to 10 channels without the need for extra crystals. Ideal for professional, commercial or amateur use, or for Government agencies.

Easy to use. Select the 10 frequencies you wish to scan and punch them in on the keyboard. The decimal display shows each frequency selected. To change frequencies, just enter the new ones.

Automatic search lets you scan any given range of frequencies within a band. When the receiver locks-on to an active channel the decimal display shows the frequency. Automatic track-tuning ensures circuits are always peaked for any broadcast.

SPECIFICATIONS

Frequency coverage: VHF — 146-174 MHz. UHF — 416-512 MHz. Sensitivity: VHF — 0.6µV for 12 db SINAD. UHF — slightly less. Selectivity: Better than -60 db @ + or — 25 KHz. Scan Rate: 20 channels per second. Antenna: Telescopic (Supplied). Provision for external antenna. Audio Output: 2 Watts.

Lafayette))

the Communicators


LAFAYETTE ELECTRONICS

Div. of E.T.D. Electronics Pty Ltd

94 ST KILDA RD, ST KILDA

Victoria 3182. Tel: 534 6036

ASPetite ^{UGH}

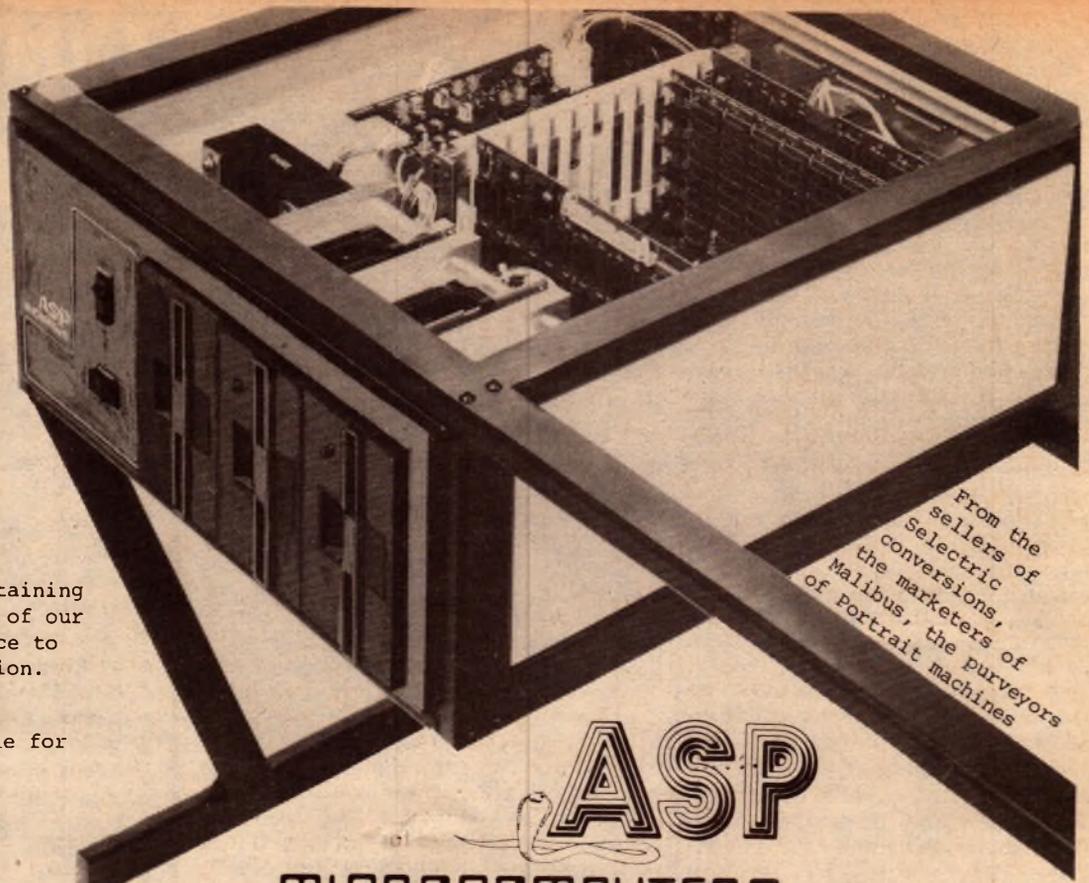A new 5 1/4" double density disk based computer system retaining the superb quality of our 8" system at a price to upset the competition.

Shown mounted in a desk, also available for desk top.

799 DANDENONG ROAD,
 EAST MALVERN 3145.
 VICTORIA AUSTRALIA.


Telephone - 2118855 2118344

From the
 sellers of
 Selectric
 conversions,
 the marketers of
 Malibus, the purveyors
 of Portrait machines

ASP
 MICROCOMPUTERS

"THE S100 BUS STOP" TM

S100 16K STATIC RAM KIT

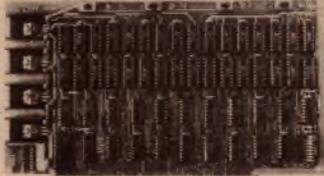

ETI 642

16K 2114. Low Power 1.2 Amps Typ. for 16K 300 or 450nS. 4K addressing. 4K write protect switches. Cromemco bank select wait states. plated thru holes. solder mask. See FEB ETI project for details. Assembled and tested \$366.00. \$5.00 P&P. Reg. mail. Kit Price \$299.00

UV EPROM ERASERS



New product range. LEE/T 15W tube — 20 min timer — up to 40 eproms — will erase in 10/15 min. Model MEE/T — 8W tube — 20 min. timer up to 10 eproms — will erase in 20/30 min. Model MEE is the same as MEE/T but with no timer. All erasers have safety cut out switch.
 PRICE. LEE/T \$105.00. MEE/T \$93.47. MEE \$73.90
 P&P \$3.00

S100/6800 CHASSIS




11 Slot back plane. 10 amp. power supply. fan. key switch. bench mount. rack mount. fully card guided. anodised alum

Basic Bench Mount Kit	\$189.00
Power Supply S100 Kit 8V. +16V. —16V	\$ 79.00
Accessory Kit	\$ 46.00
Basic Rack Mount Kit	\$166.00
Reg. Power Supply 6800 Kit	
5v. +12V. —12V	\$104.00
Sent F.O.B. Overnite Transport	

S100 16K Eprom Board Kit	\$90.00	P&P \$3.00
S100 Z80 4 MHz CPU Board Kit	\$149.00	P&P \$3.00
S100 Floppy Disc Controller Kit	\$168.00	P&P \$3.00
S100 11 Slot Back Plane	\$36.00	
S100 Active Termination Board	\$28.50	
S100 Sockets	\$8.00	
S100 Wire Wrap Board	\$28.50	
S100 Extender Board Kit	\$28.50	
Number Cruncher Kit (MM57109)	\$49.50	
Paper Tape Reader Kit	\$69.50	
Front Panel Display Kit	\$87.50	
8080 Single Step Control Kit	\$21.65	

S100 I/O PORT BOARD

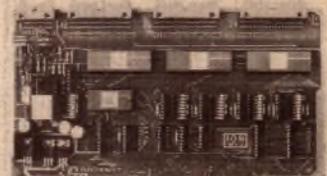

9 Parallel Ports (programmable). 1 Serial Port-TTY. RS232 or TTL. Baud rate generator 9600 to 75 fully address decoded. low power buffers. plated thru holes. solder mask

KIT PRICE \$164.00 P&P \$3.00
 ASS. PRICE \$189.00

DISC DRIVES

Shugart SA400 Mini	\$355.00	P&P \$5.00
Shugart SA800	\$580.00	P&P \$5.00

6800 PRODUCTS

6800 11 Slot Back Plane	\$36.00
6800 11 Slot Chassis (Basic)	\$166.00
6800 Active Termination Board	\$33.50
6800 Extender Board Kit	\$28.50
2708 EPROMS (ceramic)	
450nS. guaranteed quality	\$12.00
2716 Eproms (single supply)	\$47.50
2114 RAMS Low Power Hitachi. Super Rams	
450nS with 300nS available	\$8.50

Send 60c in stamps for computer printout catalogue for full production information and price list
 All products Aust. made and ex-stock (almost).
 Dealer enquiries welcome.

S.M. ELECTRONICS
 MELBOURNE



Give name, number, expiry date and signature. For mail order sales.

BUILT AND TESTED P.O.A.
 ALL PRICES ADD 15% S.T. IF APPLICABLE

S.M. ELECTRONICS

10 STAFFORD CRT. DONCASTER EAST, VICTORIA, 3109
 BOX 19 DONCASTER EAST, 3109.
 PHONE (03) 842 3950.

Southwest's CT-82

"super intelligent" terminal

The new CT-82 intelligent video terminal from Southwest Technical Products provides a bright and crisp 12MHz CRT display, together with an almost bewildering array of software-implemented control functions. Yet it provides these features at a cost lower than many "dumb" terminals.

by **JAMIESON ROWE**

When you first sit down in front of SWTP's new CT82 terminal, it doesn't seem much different from other terminals. You do notice a few special control keys like "Insert", "Delete" and "Transmit", but apart from that things look fairly familiar.

It's when you open up the CT-82's User Guide Manual that the differences soon start to become apparent. Then it hits you: with the CT-82 you can change virtually all of the operational functions and control parameters involved in such a terminal, and you can change them under software control by merely feeding in a few control characters.

This means that the terminal can be configured any way you wish, either from the keyboard of the terminal itself or from the computer to which it is connected. And it can be reconfigured at any time — on a dynamic basis if required!

What the SWTP people seem to have done is decide that if they were going to produce an "intelligent" microcomputer-based terminal, they would use the microcomputer to provide as much operational and functional flexibility as possible. So as well as provide the ability to edit a slab of text and then send it off as a nicely-prepared block, the CT-82's internal 6802 microcomputer also provides the ability to change all sorts of aspects of the terminal itself.

There are no less than 128 different control function codes recognised by the CT-82. Some of these correspond to standard ASCII control codes, while the majority are made up from two-character combinations.

Here are some examples of the terminal configuration flexibility provided. Six control codes are used to configure the CT-82's screen cursor: you can have a block cursor or an underline, blinking or non-blinking, or no visible cursor at all. Eighteen further codes provide for cursor movement control: bump up, down, left or right, move a specified number of positions in the same four directions, home to

any of the four display corners, or set either horizontal or vertical position or both.

Six codes are used to configure the CT-82's carriage return/line feed behaviour: you can set it for automatic line feed with carriage return, or not; automatic carriage return/line feed at the end of a line, or not; and automatic scrolling on line feed, or not. A further nine codes are used for configuring interface modes: upper case only, upper

or right of cursor, and insert character left or right or cursor.

As if functions like these weren't enough, the CT-82 also provides some powerful graphics display features. Some 11 codes are used for these, including the code to select graphics mode. With a display format of 22 lines of 92 six-pixel characters (66x184), the CT-82 lets you clear, set or invert any specified graphics pixel; clear, set or invert a straight line joining any two specified pixel addresses; or move the entire graphics display up, down, to left or to right. Some pretty impressive graphics functions, in other words!

There are a variety of other miscellaneous control codes. The CT-82 can automatically display a binary byte as two hexadecimal digits, if required, or display a two-byte number in left-



and lower, conversational mode or page edit mode, full or half duplex, set baud rate (31 speeds available from 50 to 38,400 baud), and shift mode normal or inverted. Another 22 codes control the CT-82's responses to control characters, and their display or non-display.

For text editing there are eleven different erase functions. Apart from a destructive backspace and line cancel you can erase the whole field, any of the four display quadrants separately, from the cursor to either the end or the start of the field, or from the cursor to the end or the start of the current line. Similarly there are 12 roll and slide functions: apart from scroll up or down, you can roll any of the four quadrants up or down independently, or the whole field to left or right. Eight further codes control insertion and deletion: delete line up or down, insert line up or down, delete character left

normalised decimal notation with leading zeroes suppressed. It can also read the current cursor position and feed this back to the computer, or do the same for an optional light pen attachment.

Add all this functional flexibility to a bright, crisp 12MHz CRT display and the reliability provided by state-of-the-art LSI technology, and the CT-82 emerges as a most impressive terminal. Particularly so when you consider that the cost for the basic version is only \$950 plus tax — less than the cost of many "dumb" terminals. Even with all options the cost of the CT-82 only rises to around \$1250 plus tax, making it outstanding value for money.

Further information on the CT-82 intelligent terminal is available from Southwest Technical Products (Australasia) at 7A Burton Street, Darlinghurst NSW, or PO Box 380, Darlinghurst 2010.

You could build this computer in just a few nights!

DREAM 6800

Second article on this innovative design

This month, author Michael Bauer gives the construction, testing and trouble-shooting procedures for the DREAM 6800. If you get started on yours now, you could have it ready to run the programs we will be featuring next month. Included in this article is the full hex listing of the DREAM's high-level interpreter/monitor program, CHIPOS.

Before soldering, inspect the PCB for flaws. Make sure the PCB is clean. If it is not tin-plated, scrub the copper pattern of the PCB thoroughly with soapy water and steel wool. Solder does not take very well to tarnished or lacquered copper.

You will need a low wattage (20 to 40W) or temperature controlled soldering iron with a fine tip. Some tracks on


the PCB come very close together, which means great care is needed to avoid solder bridging. Use 22 gauge, 60/40 resin-cored solder. Do not attempt the job with an old carbon-element iron like a "Mini-Scope" or "Birko". It's about time you bought a precision soldering instrument, anyway.

(Editor's note: The author's

recommendation against carbon-element irons refers to the possibility of damage from these irons to some ICs particularly CMOS types. This is because the heavy current flowing in the soldering iron tip prevents it from being effectively earthed. This allows the possibility of damaging voltages being applied to an IC while it is being soldered.)

Bend the leads of components (and links) with pliers before insertion into the board to avoid stressing the casings. Splay the leads outward on the solder side of the board to hold the part in place during soldering. IC's can be held with masking tape, or a finger if you've got three hands. Note that all resistors (except one) have standard half-inch lead spacing. Use the minimum amount of solder practicable for each joint; don't make blobs!

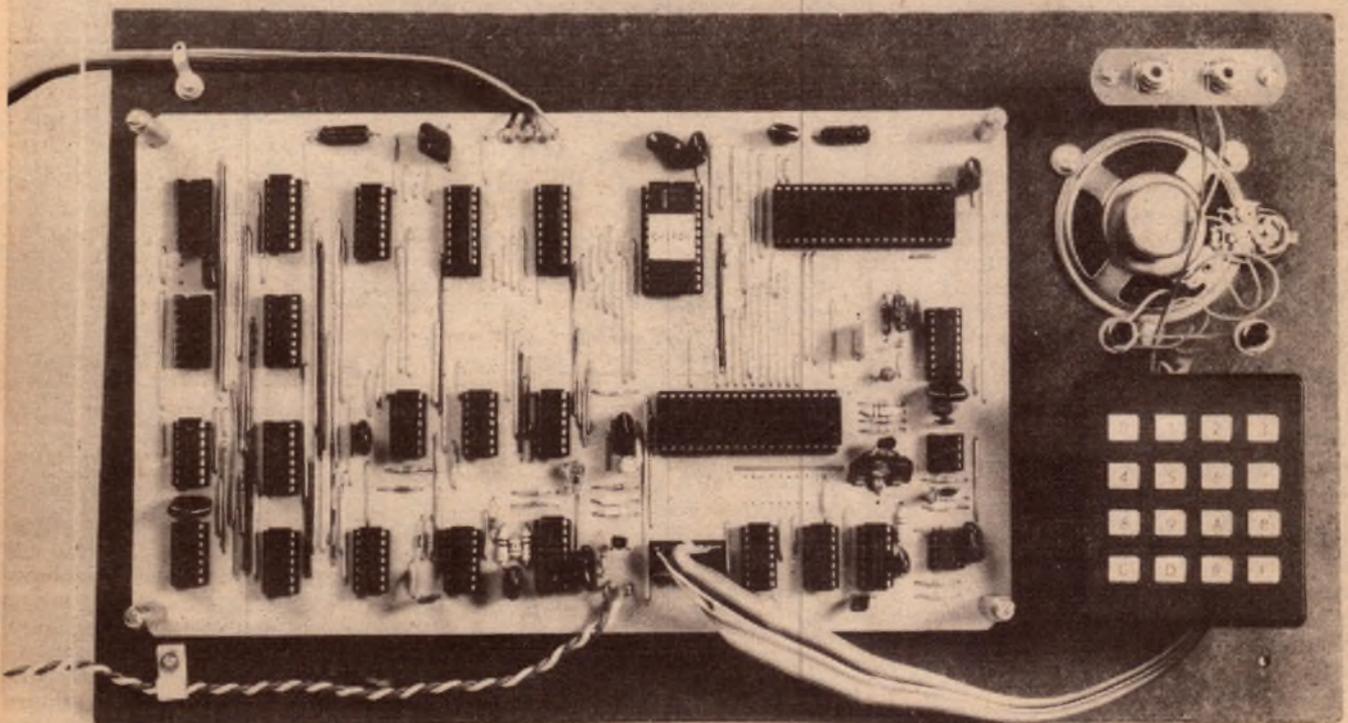Our prototype was built on a hardboard base with a perspex cover to protect and show off the PC board.




COMPUTER COMPONENTS


6800 DESIGNER BOARDS MODULES PROTO BOARDS

Ideal for expanding D2 kits:

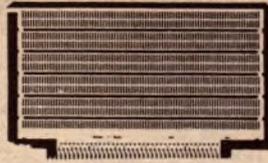STEWART ELECTRONICS
9 SLOT BACKPLANE FOR M6800
● Double sided board
● Solid shield on top
● Active or passive termination
● Provision for 10 bypass caps
● Exorciser and D2 compatible **\$39.00**




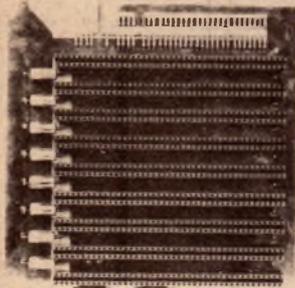M6800 PROTOTYPING BOARD
Suitable for wire + wrap or point to point wiring Drilled to accept IC's with 0.3" 0.4" or 0.6" spacing Any mix.
ALL HOLES PLATED THROUGH
43 x 43 way 0.156" spacing gold plated edge connector
Motorola exorciser and D2 compatible **\$24.50**



LOW COST VDU

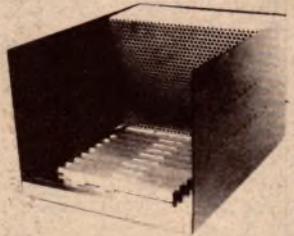VIDEO DISPLAY BOARD
D2—6800 COMPATIBLE
● Electronics Australia Aug 1978
● 16 lines 32 characters
● Memory mapped — software controlled
PCB epoxy glass gold contacts **\$14.50**
KIT complete **\$45.50**



Stewart Motorola D2 Exorciser Compatible
Card Cage with provision for shielded power supply. See EA Feb 1979 for full details shown with our 9 slot mother board fitted
Cage **\$34.50**
Card Guides (per pair) **0.50**

EXTENDER CARD

6800 — D2 — Exorciser Compatible
43 x 43 way double sided fibre glass board
Hard gold plated contacts Gold plated socket **\$24.50**

HOBBY-WRAP TOOL-BW-630

● Battery Operated (size C)
● Weighs ONLY 11oz
● Wraps 30 AWG Wire onto Standard DIP Sockets (0.25inch) Complete with built-in bit and sleeve **\$47.75**
Tax exempt
(Batteries not included)

WIRE-WRAP KIT — WK-2-W

WRAP • STRIP • UNWRAP
● Tool for 30 AWG Wire
● Roll of 50 Ft. White or Blue 30 AWG Wire
● 50 pcs each 1", 2", 3" & 4" lengths — pre-stripped wire. **\$17.50**

WIRE WRAP TOOL WSD-30
WRAP • STRIP • UNWRAP (tax ex) **\$7.80**

WIRE WRAP WIRE — 30 AWG KYNAR SPECIFY COLOUR —
White-Yellow-Red-Green-Orange-Blue-Black 1000 ft **\$18.00**

WIRE DISPENSER — WD-30
● 50 ft roll 30 AWG KYNAR wire wrap wire
● Cuts wire to desired length
● Strips 1" of insulation **\$4.80 ea.**

REPLACEMENT SPOOLS FOR WD-30 Specify blue, yellow white or red **\$2.60 spool**


COMPUTER GRADE CAPACITORS



6.800MFD	16V	\$ 5.00 EA
10.000MFD	16V	7.00 EA
10.000MFD	25V	8.00 EA
15.000MFD	25V	9.50 EA
22.000MFD	25V	10.50 EA
68.000MFD	16V	17.00 EA

DIP PLUGS

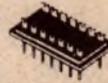Ideal for use with flat ribbon cable or to mount components on.



14 pin **\$0.56** 24 pin **\$0.94**
16 pin **\$0.68**

CERMET SINGLE TURN TRIM POT

Spectral model 63P
ACTUAL SIZE

STOCK VALUES
10, 20, 50, 100, 200, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1M, 2M 1—9 **\$0.85**
10+ Values may be mixed **\$0.76**

COMPUTER COOLING FANS

Popular Muffin fan
Standard size 4.68" square, 110 volt or 240 volt available **\$24.50**



DIP SWITCHES

(On-Off Contacts)
4 positions **\$1.50**
6 positions **\$1.70**
8 positions **\$1.80**
10 positions **\$3.45**



WIRE WRAP IC SOCKETS

Gold plated 3 level wrap
8 PIN 42 24 PIN 1.30
14 PIN 66 28 PIN 1.82
16 PIN 74 40 PIN 1.96
18 PIN 90
20 PIN 1.20
22 PIN 1.20

P.C. EDGE CONNECTORS



\$100 gold plated wirewrap **\$5.50**
\$100 gold plated solder tail **\$4.90**
D2 Motorola bus
43/86 156 gold solder tail **\$7.34**
43/86 156 w/wrap **\$7.95**

We can supply all your edge connector requirements from 2 to 85 pin in both 156 and 1 spacing Please send for price sheet.

10 TURN POTENTIOMETERS

Stock resistance values
10, 25, 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K
Spectral model 534 1/4" shaft
Price 1—9 **\$6.75**
10+ values may be mixed **\$5.75**



CERMET

20 TURN TRIM POT

Spectral Model 43P



ACTUAL SIZE
STOCK VALUES
10, 20, 50, 100, 200, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1M, 2M 1—9 **\$1.10**
Values may be mixed 10+ **\$0.98**

PROTO-CLIP



For power-on/hands off signal tracing Bring IC leads up from PC board surface for last troubleshooting
PC14 4.50 PC24 8.50
PC16 4.75 PC40 13.75

BRIDGE RECTIFIERS

W02 1.5A 200V \$0.50
W04 1.5A 400V \$0.60
KBPC 602 6 Amp 200V \$1.50
KBPC 606 6Amp 600V \$1.75
KBPC 1002 10 Amp 200V \$1.95
KBPC 1004 10 Amp 400V \$2.25
KBPC 3502 35Amp 200V \$2.60
KBPC 3504 35 Amp 400V \$2.95



LOGIC PROBES

CONTINENTAL SPECIALITIES




LP2 1.5 MHz max input **\$24.95**
LP1 10 MHz max input **\$44.95**
LP3 50 MHz max input **\$69.95**
DP1 Digital pulser with autopolarity pulse sensing **\$74.95**

POWER TRANSFORMERS


SPECIALLY DESIGNED FOR MICROCOMPUTERS
* See Feb 1979 EA. for full details
* Good regulation
* Electrostatic shield
* SE 805
8V @ 5A 2x14V @ 1A **\$14.00**
* SE 810
8V @ 10A 2x15V @ 1A **\$19.00**
* 820
8V @ 20A 15V @ 1A 15V @ 3A **\$28.00**

Intersil 3 1/2 DIGIT PANEL METER \$29.95 LCD KIT

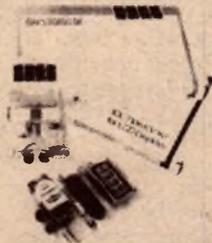BUILD A WORKING DPM IN 1/2 HOUR WITH THESE COMPLETE EVALUATION KITS
Test these new parts for yourself with intersil's low cost prototyping kits complete with A/D converter and LCD display (for the 7106). Kits provide all materials including PC board for a functioning panel meter



Z80 CENTRAL PROCESSING UNIT

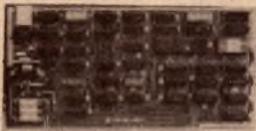

Software:
The Z-80 CPU will accept most existing 8080 software without modification including Assemblers, Debuggers, Disk Operating Systems, Basic and Fortran.
Support:
The Z-80 CPU is fully S-100 compatible and supported by a full range of peripherals from both Ithaca Audio and other vendors.
Features:
● On-board 2708 EPROM
● Power-on-jump to any 4K boundary above 32K-RAM, ROM, or the on-

board 2708.
● Front panel-less operation allowed by on-board run-stop flip-flop and optional generation of MEMORY WRITE
● Selectable wait states on the following cycles: M1 cycle Memory Request cycle On-board ROM cycle Input cycle Output cycle
● Selectable 8080 or Z-80 1/0 addressing modes.
● DMA Grant tri-states all signals from processor board.
● 8224 clock generator provides 8080 like 1 and 2 for the S-100 Bus.
PCB with manual \$44.50
Manual only (refundable when board purchased) **\$5.00**
Kit complete with manual 4MHz **\$125.00**
Built and tested 2MHz board **\$175.00**

All prices plus 15% sales tax. Plus freight. Please add sufficient freight. Any excess will be refunded.

STEWART ELECTRONICS

33 SUNHILL ROAD, MT WAVERLEY 3149
Phone (03) 277 0622
Bank Card Accepted.

Mon-Fri 9am-6pm
Sat 9am-12noon

printed board (GND line), your work surface, and yourself. Don't wear nylon pantyhose or rub ebonite rods in your hair while handling MOS!

Apply power once again, and you should notice a short bleep in the speaker and something resembling fig. 2 on the screen. The actual pattern and 4-digit number seen are just random garbage in the RAM at switch-on. Try keying in any 4 hex digits. This number should then appear on the screen, and if so, your computer is, in all probability, fully operational. See how many 4-letter words you can make from the hex digits: A,B,C,D,E and F. If your system fails to display the above information (after resetting), see how many 4-letter words you can mutter to yourself and then proceed calmly to the section on trouble-shooting.

Once the video generator and processor appear to be working, you can try using the memory-modify command. Hit [RST], then enter 0, 1, 0, 0, the starting address of the display refresh buffer. Now key [FN] followed by [0] to get into "memod". The display window will show a 2-digit number beside the address. This is the contents of location 0100, which can also be seen in binary at the upper LHS of the screen. (A white dot = 1, no dot = 0.) Step through the memory by pressing [FN] repeatedly. Go back to 0100 (hit [RST], 0, 1, 0, 0, [FN], 0). This time, write into the buffer by keying in a pair of hex digits, and another, and another . . . noting the binary pattern formed by each byte.

Notice that as data bytes are deposited into memory, the address flips to the next address, before you see the byte just keyed in. This is a design compromise (not an oversight), but should be of no concern because you're not likely to be looking at the screen anyway, when keying in a program. One eye will be on a listing, the other on the keypad. The data, having been entered, can be verified later by stepping through with the [FN] key.

Getting the feel for it, and want to try a CHIP-8 program? Try the simplest possible! Use memod to enter this data at 0200:

Address	Data	Mnemonic
0200	F0	go to monitor
0201	00	

The instruction F000 does not exist, and will result in a jump back to the monitor (CHIPOS), but first the interpreter clears the screen, as it does at the start of each new program, (unless you start from C002). To run this "program", hit RST, C000, FN, 3 (GO from C000).

Here's something to watch CHIPOS's random number generator at work:

0200	CA3F	VA is random x-coord (00-63)
0202	CB1F	VB is random y-coord (00-31)
0204	A20A	Point to pattern byte (I=20A)
0206	DAB1	Display 1 byte at coords (VA, VB)
0208	1200	Go to loc'n 0200 for next instr'n
020A	8000	DATA: 80hex = 10000000 binary = dot.

Before the programs get too much bigger, you'll want to save them on cassette. If your recorder has line (auxiliary) input and output, you're fortunate because these voltage levels are optimum for use with the DREAM-6800's tape modem. Also it is highly desirable (but not essential) that the recorder's internal speaker not be muted, so that the leader tone can be located by sound. Hence, recorders with only an EXT-SPKR (or earphone) jack should be modified such that insertion of the plug does not result in disconnection of the speaker. If this is awkward, another speaker can always be connected externally.

Do not operate the recorder at high volume when connected to the computer. Voltage levels exceeding 5V peak-peak could damage IC23, but this is improbable at normal listening levels. Further, recorders without an AUX in-

put may require a much lower signal level from the computer, for use with the "MIC" input. This problem is easily solved by inserting a 220k resistor in series with the "TAPE-OUT" line (pin-16). Shielded cable should be used for the tape connections, with the shield wired to pin-13 of the I/O plug.

To test the cassette functions, proceed as follows. Use the "memod" function to create a pattern on the screen, as described earlier. Then define the beginning and ending addresses of the block you want to save, in this case the display buffer page from 0100 to 01FF. For convenience, the ending location PLUS ONE is specified. Hence to dump the display, deposit the following data at 0002:

0002	01	Beginning address MSB
0003	00	Beginning address LSB
0004	02	Ending address (+1) MSB
0005	00	Ending address LSB

HOW WE BUILT OURS:

Since the author did not present a proto-type with his article, we decided to build our own, both to confirm the design and to aid presentation of this attractive system in the magazine. With the latter idea paramount, we decided to mount the PCB on a hardboard base with a perspex cover to protect and show off the unit.

The perspex cover is also used to mount the keyboard, two pushbuttons and the tape interface sockets. This method of construction is easy to build, is very economical and produces an attractive unit.

Readers will note that we have used IC sockets for the ICs on the PCB. We did this as a precaution — if bugs had shown up, we wanted to be able to change ICs with a minimum of work. Nevertheless we are inclined to agree with the author's comments on IC sockets.

The miniature speaker is mounted face down on the hardboard base. Even so we found the loud bleeps it emitted quite annoying, so we muted it with a preset pot, as suggested by the author.

Rather than salvage a keyboard from a calculator or other source, we took the easy but expensive approach of buying a new one. We used a Digitran KL0043 keyboard, which has the buttons connected in a 4 x 4 matrix as required but with a slightly different numbering to that shown on the circuit published last month. However, this

presents no problem.

The keyboard can be purchased from Radio Despatch Service, 869 George Street, Sydney, NSW 2000. Radio Despatch Service have notified us that since the wholesale price of the keyboard is high, they have reduced their own margin to a minimum. Even so, the KL0043 will set you back by \$20.43, including sales tax. Radio Despatch Service also have a ready source of suitable perspex in the form of surplus smoke-tinted record deck covers, at \$2 each.

For the RST and FN pushbuttons we used two good quality momentary contact switches. We didn't bother to label these as they are used so often that it soon becomes second-nature. The FN button is mounted on the right and the RST on the left, immediately above the keyboard.

The major ICs for our unit, with the exception of the CHIPOS EPROM, were supplied by Total Electronics, 155 Willoughby Road, Crows Nest, NSW 2065. Silicon Valley Stores and Applied Technology Pty Ltd, 1a Pattison Avenue, Waitara, NSW 2077 will be able to supply all the IC's, including the CHIPOS (2708) EPROM.

Two other firms have EPROM programming services: A.J.F. Systems & Components Pty Ltd, 29 Devlin Street, Ryde, NSW 2112 and Warburton Franki (Sydney) Pty Ltd, 199 Parramatta Road, Auburn, NSW 2144.

ECONOMIC DIGITAL CONTROL PTY. LTD.

PO Box 817, CROWS NEST, 2065.
SHOWROOM: Cnr. ATCHISON and OXLEY STS,
ST. LEONARDS, SYDNEY.
TEL: 439-1220 439-1773
TELEX: AA27901

COMPONENTS, KITS and EQUIPMENT

We are now dealers for Jade Computer Products Inc. Guaranteed factory prime. Delivery normally ex-stock to 3 weeks. Add 1 week for mail orders. Add 15 percent sales tax to all prices. Add \$3.50 for postage and handling of mail orders. Wholesale enquiries welcome on headed paper. Discount for quantity orders. Send money with order or use Bankcard (send No, expiry date, signature). Send 20c stamp for Catalogues.

Some sample prices.(Retail on one-off basis)

2114 RAMS	\$10.38	8085 CPU chip	\$28
2513 Char Gen. Ucase	\$9.40	63 key ASCII unencoded keyboard	\$40
2708 EPROMS	\$12.50	19 key hexadecimal keypad	\$14
2716 EPROMS (TI)	\$28	TRS-80 16k memory kit installed	\$240
6502 CPU chip	\$10.95	16k Static Ram kit	\$299
8080 CPU chip	\$16	Z80a 4 MHz board kit	\$165
Z80a CPU chip	\$30		

Prices subject to change without notice

MICROCOMPUTER SYSTEMS

Send 20c stamp for our full range of equipment and software

● **COMPUTER WITH 48K RAM, Z80A, 2 x 8" disk drives (480K single density, 960K double density optional); Terminal 9600 baud, 80 x 24, ASCII keyboard plus numeric keypad; Printer upper and lower case, impact, tractor feed; Debtors, Creditors, Payroll, General Ledger, Utilities.**

\$7,700

● **DIABLO PRINTERS**, Axion 801p, Ip.225, Expander printers, extra disk capacity, additional memory, Database packages available. Send for details.

● **WORD PROCESSORS** starting from \$4,600 plus your choice of printer.

● **THE TEACH YOURSELF COMPUTER** soon to be released at \$640 retail. This computer will make all computers under \$3000 obsolete. Send for details.

DREAM 6800

[N.B.: 01FF+1=0200; MSB = Most significant (high-order) byte; LSB = Least significant (low-order) byte.]

Thus, a 256-byte block is defined, from 0100 to 0200, not including the last byte (at 0200). The same block applies to a load or dump. This simple tape format lets you load a file (or part thereof) into any place in RAM, regardless of where it was dumped from, thereby allowing relocation of data or programs.

Having got that, reset the system, start the cassette in RECORD mode and adjust the recording level, and let it run for several seconds to write a "leader" tone (steady 2400 Hz). Then key [FN][2] (dump/save). The screen will be disabled until the dump is complete, because the serial I/O software cannot tolerate the display refresh delays.

To verify the dump, and to test your demodulator, power down the system to destroy RAM contents. Once again, enter the begin and end locations, as above. Set the DEMOD trimpot to mid-position. Rewind and play the tape until the leader tone is heard, then press [FN][1] (load). The display will again black out and should return at the instant the last byte is accepted, hopefully revealing your saved pattern.

If anything goes wrong, first retry the above steps. Then try various recording and playback levels, or try adjusting the DEMOD trimpot (although this should be non-critical in the majority of cases). As a last resort, you might have to check the modem with a CRO, but be suspicious of external troubles first. Also note that it pays to use good quality cassettes.

That concludes the testing procedure. Now you can look forward to entering and saving much larger programs. Be sure to write down the block loading addresses on the cassette index. It's a good idea to always use "standard" size blocks; e.g. 0200-0300 for a small program; 0200-0400 for a medium; and 0080-0400 to dump all usable RAM. Refrain from dumping/loading 0000-0080, because this area is reserved for CHIPOS's scratchpad and stacks.

Just a final note for perfectionists. The width of the first and last dot (on every row) is controlled by the delay network on H64, (120 ohms, 220R, 220 ohms, .0033uF). If the RHS dots are too narrow, first try increasing C to .0047uF. Also, the frequency of the cassette modulator (2400Hz, marking) can be adjusted by the 5.6k resistor. Speaker volume can be reduced with a series resistor or 500 ohm trimpot.

This is the complete listing for the CHIPOS interpreter/monitor program.

```

C000 8D 77 CE 02 00 DF 22 CE 00 5F DF 24 DE 22 EE 00
C010 DF 28 DF 14 BD C0 D0 96 14 84 0F 97 14 8D 21 97
C020 2E DF 2A 96 29 44 44 44 44 8D 15 97 2F CE C0 48
C030 96 28 84 F0 08 08 80 10 24 FA EE 00 AD 00 20 CC
C040 CE 00 2F 08 4A 2A FC A6 00 39 C0 6A C0 A2 C0 AC
C050 C0 BA C0 C1 C0 C8 C0 EE C0 F2 C0 FE C0 CC C0 A7
C060 C0 97 C0 F8 C2 1F C0 D7 C1 5F D6 28 26 25 96 29
C070 81 E0 27 05 81 EE 27 0E 39 4F CE 01 00 A7 00 08
C080 8C 02 00 26 F8 39 30 9E 24 32 97 22 32 97 23 9F
C090 24 35 39 DE 14 6E 00 96 30 5F 9B 15 97 15 D9 14
C0A0 D7 14 DE 14 DF 22 39 DE 14 DF 26 39 30 9E 24 96
C0B0 23 36 96 22 36 9F 24 35 20 E8 96 29 91 2E 27 10
C0C0 39 96 29 91 2E 26 09 39 96 2F 20 F0 96 2F 20 F3
C0D0 DE 22 08 08 DF 22 39 BD C2 97 7D 00 18 27 07 C6
C0E0 A1 D1 29 27 EB 39 C6 9E D1 29 27 D0 20 D5 96 29
C0F0 20 38 96 29 98 2E 20 35 8D 38 94 29 20 2F 96 2E

C100 D6 29 C4 0F 26 02 96 2F 5A 26 02 9A 2F 5A 26 02
C110 94 2F 5A 5A 26 0A 7F 00 3F 9B 2F 24 03 7C 00 3F
C120 5A 26 0A 7F 00 3F 90 2F 25 03 7C 00 3F DE 2A A7
C130 00 39 86 C0 97 2C 7C 00 2D DE 2C 96 00 AB 00 AB
C140 FF 97 0D 39 07 C1 79 0A C1 7D 15 C1 82 18 C1 85
C150 1E C1 89 29 C1 93 33 C1 DE 55 C1 FA 65 C2 04 CE
C160 C1 44 C6 09 A6 00 91 29 27 09 08 08 08 5A 26 F4
C170 7E C3 60 EE 01 96 2E 6E 00 96 20 20 B0 BD C2 C4
C180 20 AB 97 20 39 16 7E C2 E1 5F 9B 27 97 27 D9 26
C190 D7 26 39 CE C1 BC 84 0F 08 08 4A 2A FB EE 00 DF
C1A0 1E CE 00 08 DF 26 C6 05 96 1E 84 E0 A7 04 09 86
C1B0 03 79 00 1F 79 00 1E 4A 26 F7 5A 26 EB 39 F6 DF
C1C0 49 25 F3 9F E7 9F 3E D9 E7 CF F7 CF 24 9F F7 DF
C1D0 E7 DF B7 DF D7 DD F2 4F D6 DD F3 CF 93 4F DE 26
C1E0 C6 64 8D 06 C6 0A 8D 02 C6 01 D7 0E 5F 91 0E 25
C1F0 05 5C 90 0E 20 F7 E7 00 08 39 0F 9F 12 8E 00 2F

C200 DE 26 20 09 0F 9F 12 9E 26 34 CE 00 30 D6 2B C4
C210 0F 32 A7 00 08 7C 00 27 5A 2A F6 9E 12 0E 39 D6
C220 29 7F 00 3F DE 26 86 01 97 1C C4 0F 26 02 C6 10
C230 37 DF 14 A6 00 97 1E 7F 00 1F D6 2E C4 07 27 09
C240 74 00 1E 76 00 1F 5A 26 F5 D6 2E 8D 28 96 1E 8D
C250 15 D6 2E CB 08 8D 1E 96 1F 8D 0B 7C 00 2F DE 14
C260 08 33 5A 26 CB 39 16 E8 00 AA 00 E7 00 11 27 04
C270 86 01 97 3F 39 96 2F 84 1F 48 48 48 C4 3F 54 54
C280 54 1B 97 1D DE 1C 39 C6 F0 CE 80 10 6F 01 E7 00
C290 C6 06 E7 01 6F 00 39 8D EE 7F 00 18 8D 55 E6 00
C2A0 8D 15 97 17 C6 0F 8D E1 E6 00 54 54 54 54 8D 07
C2B0 48 48 98 17 97 17 39 C1 0F 26 02 D7 18 86 FF 4C
C2C0 54 25 FC 39 DF 12 8D BF A6 01 2B 07 48 2A F9 6D
C2D0 00 20 07 8D C2 7D 00 18 26 EC 8D 03 DE 12 39 C6
C2E0 04 D7 21 C6 41 F7 8D 12 7D 00 21 26 FB C6 01 F7
C2F0 80 12 39 8D 00 37 C6 C8 5A 01 26 FC 33 39 CE 80

C300 12 C6 3B E7 01 C6 7F E7 00 A7 01 C6 01 E7 00 39
C310 8D 13 A6 00 2B FC 8D DD C6 09 0D 69 00 46 8D D3
C320 5A 26 F7 20 17 DF 12 CE 80 12 39 8D F8 36 6A 00
C330 C6 0A 8D BF A7 00 0D 46 5A 26 F7 32 DE 12 39 20
C340 83 86 37 8D B9 DE 02 39 8D F7 A6 00 8D DD 08 9C
C350 04 26 F7 20 0B 8D EA 8D B7 A7 00 08 9C 04 26 F7
C360 8E 00 7F CE C3 E9 DF 00 86 3F 8D 92 8D 43 0E 8D
C370 CE 4D 2A 10 8D C9 84 03 27 23 4A 27 D8 4A 27 C8
C380 DE 06 6E 00 8D 0C 97 06 8D 06 97 07 8D 23 20 DF
C390 8D AD 48 48 48 48 97 0F 8D A5 9B 0F 39 8D 12 DE
C3A0 06 8D 25 8D 9A 4D 2B 04 8D E8 A7 00 08 DF 06 20
C3B0 EC 86 10 8D 2B CE 01 C8 86 FF BD C0 7D CE 00 06
C3C0 8D 06 08 8D 03 8D 15 39 A6 00 36 44 44 44 44 8D
C3D0 01 32 DF 12 BD C1 93 C6 05 BD C2 24 86 04 9B 2E
C3E0 97 2E 86 1A 97 2F DE 12 39 7A 00 20 7A 00 21 7D
C3F0 80 12 3B DE 00 6E 00 00 C3 F3 00 80 00 83 C3 60

```

TROUBLE-SHOOTING

In the unlikely event that your computer malfunctions, the cause must be either a constructional error or a faulty component. Therefore, proceed to double check the board. Inspect the solder side with a magnifying glass and if any tracks appear to be touching, scrape between them with a sharp pointed instrument. Remember to ground yourself and the board. Look for disoriented components, and incorrect values. Check that all links are present. From here on, it is assumed that the wiring is correct and that your power supply and video monitor are working properly.

The first step is to get the video display generator up. ICs 1, 2, 3, 4, 7 and 9 should be removed at this stage. First check the clock (IC8). There should be 1MHz square waves at pins 7, 13, and 15, and 2MHz at pin 5 (to VDG). Also check RST (pin 14) is high. If trouble, check that the crystal is oscillating (1MHz sine-wave at pin 2), using a x10 probe on your CRO. If not, try it without the L-C tank circuit (150pF/10uH). If no success, you have a bad crystal, or 6875.

If there appears to be some video output, but you can't get the picture to lock, the trouble is probably in your RF modulator. Try reducing the level of the video input signal to the modulator. Also, beware of harmonics; perhaps you have been trying to tune in to a spurious signal emanating from the thing.

Assuming the presence of a 2MHz clock signal, check for horizontal and vertical sync pulses (4us every 64us, and approx. 300us every 20ms, resp.). If no sync, check counter outputs (ICs 15, 14, 13, in that order). Vertical problems could also be caused by IC 13 not resetting or by a faulty one-shot (IC19b). There's not much else that can go wrong with the VDG itself, except when interacting with the MPU.

Having obtained a rock solid white rectangle display, the next step is to check operation with the processor. With all ICs installed, switch on (and reset) the system again. Press a few hex keys. Are the keystrokes being acknowledged with a bleep, but something incoherent is being displayed? If so, do the following, in order given:—

1. Check the LOAD pulse (IC7, pin 9); should be 500 to 800 nanosec, every 8 dot-clock cycles (4us).
2. Remove ICs 1, 2 and 9 (MPU, ROM, PIA); connect BA (IC11, pin 13) to +5V; proceed to check the DMA address bus (outputs of buffers, IC5, 6). The signals should be the same as the respective inputs. Now remove the +5V connection to BA. The out-

puts should no longer follow the inputs, but "float". If any of the Tristate buffers appear to be faulty, replace it.

3. Re-insert all ICs previously removed. The screen should show RAM contents, usually some kind of vaguely ordered pattern, or random dots. Try grounding WE (IC3, pin 10) momentarily with a jumper lead, a few times, while the system is running. The display should change each

- time. If not, suspect the 4014 (IC7).
4. Finally, the least likely cause of the above symptoms is a bad EPROM.

At this stage, we are assuming that the video is behaving itself, but a processor malfunction is suspected. With all chips on board, press the [RST] key. The speaker should bleep when the key is held down (even if the PIA is at fault), and the RST line (IC8, pin 14) should go LOW momentarily. If not, check the 2.2uF tantalum capacitor and RST wiring. Note that the Reset function is performed by the 6875. If the system does not appear to be resetting, you could have a faulty EPROM, RAM, MPU or PIA!

(Continued on p125)

PARTS LIST

HARDWARE

- 1 PC board, 244 x 142mm
- 1 4.000MHz crystal
- 1 hexadecimal keypad (4 x 4 matrix)
- 2 momentary-contact pushbuttons
- 2 RCA phono sockets
- 1 small loudspeaker
- 1 10uH inductor

SEMICONDUCTORS

- 1 6800 microprocessor
- 1 6821 peripheral interface adaptor
- 1 6875 clock generator
- 1 2708 EPROM (programmed with CHIPOS)
- 2 2114 static RAMs
- 1 4040B CMOS counter/divider
- 1 4014B CMOS static shift register
- 2 74LS04 hex inverter
- 1 74LS08 quad 2-input gate
- 1 74LS10 triple 3-input gate
- 1 74LS11 triple 3-input gate
- 1 74LS20 dual 4-input gate
- 1 7440 dual 4-input buffer
- 1 7474, 74LS74 dual D flipflop
- 2 7493, 74LS93 binary counter
- 1 74121 one-shot multivibrator
- 1 74123 dual one-shot
- 2 74LS367 Tristate buffer
- 1 566 function generator
- 1 741 operational amplifier
- 1 2N3643 NPN transistor
- 1 2N4250 PNP transistor
- 6 1N4148 silicon diodes

IC Sockets

- 2 40 pin
- 1 24 pin
- 2 18 pin
- 3 16 pin
- 1 16 pin DIL plug

CAPACITORS

- 2 10uF/16VW aluminium electrolytic
- 1 10uF/16VW tantalum electrolytic
- 1 2.2uF tantalum electrolytic
- 12 0.1uF polyester or ceramic
- 1 .033uF polyester
- 1 .022uF polyester
- 2 .01uF polyester
- 1 .0033uF polyester
- 1 .001uF polyester
- 2 150pF ceramic
- 1 47pF ceramic or polystyrene

RESISTORS

- (1/4W, 10% tolerance)
- 2 x 22k, 5 x 10k, 1 x 6.8k, 1 x 5.6k, 2 x 4.7k, 5 x 2.2k, 3 x 1.5k, 1 x 1k, 2 x 470 ohms, 2 x 120 ohms, 1 x 75 ohms (or 2 x 150 ohms), 1 x 74 ohms.
- 1 5k trimpot (vertical mounting)

MISCELLANEOUS

Ribbon cable, tipped copper wire, spaghetti sleeving, shielded cable, PC pins, 22g solder, 3 extra DIL plugs and sockets (if required for expansions).

PITT ST. MICROCOMPUTER CENTRE

SOFTWARE FOR TANDY TRS-80

Software 80	
Complete Business System (DISC)	\$495
(Acces. Rec. Acces Pay. Invent. Payroll. Mail List)	
Also various computer games.	
Microsoft	
TRS-80 Fortran (DISC)	\$365.50
Small System Software	
Electric Pencil	\$105.00
Also Disc Monitor, Resident Edit/Assem. etc.	
Pitt St. Centre	
Level II Games Cassette	
Startrek etc.	\$12.00
Level II Instruction	
Cassette in Basic	\$32.00
TAILOR MADE SYSTEMS: SOFTWARE PACKAGES MODIFIED	
A.J.A. Systems & Sunshine Comp. Co.	

LECTURES (1 evening/wk)

Microcomputers 8wks	\$150
Microprocessors 8 wks	\$150
Beginners Basic 4wks	\$80
Consulting services from	\$5.00

HARDWARE

Teletype 43	\$1322.50 Incl. S.T.
Connecting cable for Tandy	\$30.00
Intel 8085 Microprocessor kit	\$230.00 Incl. S.T.

When ordering cassettes specify for CTR41 or CTR80


WRITE TO:

373 PITT ST, SYDNEY 2000.

Phone: 235 7229

TANDY USERS CLUB NEWS LETTER \$10/annum.

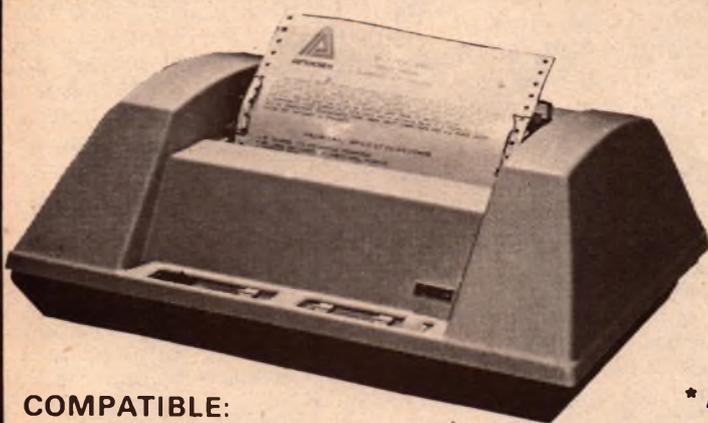WE PROUDLY PRESENT: THE DICK SMITH LINE PRINTER MODEL DP-8000



COMPATIBLE:
WITH ANY CENTRONICS
TYPE PORT: SORCERER/TRS-80 etc

\$6.00 FREIGHT ANYWHERE IN AUSTRALIA

FEATURES:

- * BI DIRECTIONAL PRINTING
 - * 9x7 CHARACTER FORMAT
 - * 241mm STANDARD FAN FOLD COMP. PAPER
 - * UP TO 3 CARBON COPIES & ORIGINAL
 - * 80 COLUMNS SINGLE, 40 DOUBLE WIDTH CHARACTERS
 - * UPPER & LOWER CASE ASCII
 - * AUTO TOP OF FORM
 - * AUTO SKIP OVER PERFORATION
 - * PARALLEL CENTRONICS PORT
 - * RS232 PORT (110-9600 BAUD) SERIAL
 - * 1K BUFFER MEMORY
- * **AVAILABLE EX STOCK THROUGHOUT AUSTRALIA**

CAT.X-1188

\$1298⁰⁰

DICK SMITH ELECTRONICS

PRICES CORRECT AND STOCK AVAILABLE AT PRESS TIME



SYDNEY 439 5311 CANBERRA 80 4944 MELBOURNE 67 9834
BRISBANE 391 6233 ADELAIDE 212 1962 PERTH 328 6944
MAIL ORDERS PO Box 747, CROWS NEST, NSW 2085. Post and packing extra.

551

Cromemco COMPUTER SYSTEMS

TOMORROW'S COMPUTERS NOW



ADAPTIVE ELECTRONICS NOW OFFERS THE SUPERB RANGE OF **CROMEMCO** COMPUTER SYSTEMS, PERIPHERALS AND SOFTWARE. INCLUDING SOFTWARE SUPPORT AND PROFESSIONAL HARDWARE BACK-UP.

SYSTEM THREE FEATURES

- Fast Z 80A microprocessor
- RAM expansion to 512k Bytes
- 2 or 4, 8 inch disc drives
- 21 slot S-100 bus
- Printer interface
- RS-232 or 20mA serial interfaces
- Excellent service access

COMPREHENSIVE SOFTWARE SUPPORT

- Disc operating system (CP/M compatible)
- 16k disc extended BASIC
- Multi-user BASIC
- COBOL compiler
- FORTRAN IV compiler
- Z-80 macro-assembler
- Word processing and Data base management

**AE ADAPTIVE
ELECTRONICS P/L**

77 Beach Rd, SANDRINGHAM, Victoria, Australia 3191
Telephone (03) 598 4422; Telex 35666

Perth Representative: Micro-Data Pty Ltd, 437, Cambridge Street, Wembley, 6014. Telephone (09) 387 3314

A Power Supply for the DREAM 6800 computer

This power supply was designed specifically to meet the power requirements of the DREAM6800 computer published elsewhere in this issue. The supply provides three rails: $\pm 5V$ and $+12V$, each with more than adequate current capability.

by LEO SIMPSON

As part of our presentation of the highly innovative DREAM 6800 computer we decided to produce a suitable power supply. You could call it the "DREAM POWER". The circuit is much the same one originally roughed out by designer Michael Bauer, but we have produced a PC board for it, to make construction easy. After all, why make the computer easy to build but the power supply difficult?

Maximum power requirements (worst case) of the DREAM 6800 are $+5V$ at 1 amp, $-5V$ at 100 milliamps and $+12V$ at 100 milliamps. This is easily and simply provided by a bridge rectifier and transformer with a centre-tapped 30V secondary winding.

The bridge rectifier feeds a 2200 μF /25VW filter capacitor for the two positive supply rails and a 1000 μF /25VW capacitor for the lightly loaded $-5V$ rail. Under normal load conditions, both capacitors will be charged to 20VDC or more. This is necessary for good line regulation of the 12V rail, but means that the voltage drop and thus power dissipation of the two 5V regulators is higher than ideal.

Fortunately, the $-5V$ regulator is lightly loaded, as noted before, and therefore does not dissipate much power. But the $+5V$ regulator dissipates 10 watts or more, which requires an effective heatsink. We settled on this perhaps wasteful compromise because it results in a simple rectifier circuit and uses an economical and readily available transformer.

Power dissipation in the regulators could perhaps be reduced by substituting a transformer with a centre-tapped 24V secondary. This would result in approximately 17VDC across the filter capacitors instead of more than 20VDC. However, this approach might prejudice the line regulation of the 12V regulator in areas where the mains voltage is prone to drop below 240VAC.


While only the $+5V$ regulator is required to supply 1 amp, we have standardised on 1 amp regulators for all three since they are the most readily available. If you are able to obtain 12V

and negative 5V regulators of lower rating at a good price, then by all means use those instead.

All the circuitry for the power supply is accommodated on a small PC board measuring 81 x 90mm and coded 79ups6. The bridge rectifier consists of four 1 amp diodes such as 1N4001 or

similar types. Even though the two filter capacitors are reasonably close to the regulators in terms of conductor length, we have taken the usual precautions to ensure stability of the regulator ICs.


These precautions take the form of 1 μF tantalum capacitors at the input and output of each regulator. An exception to this is the negative 5V regulator, which requires a 2.2 μF tantalum capacitor at its input. In general, the input capacitors are required to prevent high frequency oscillation of the main emitter-follower in the regulator IC, while the output capacitor ensures a low output impedance at

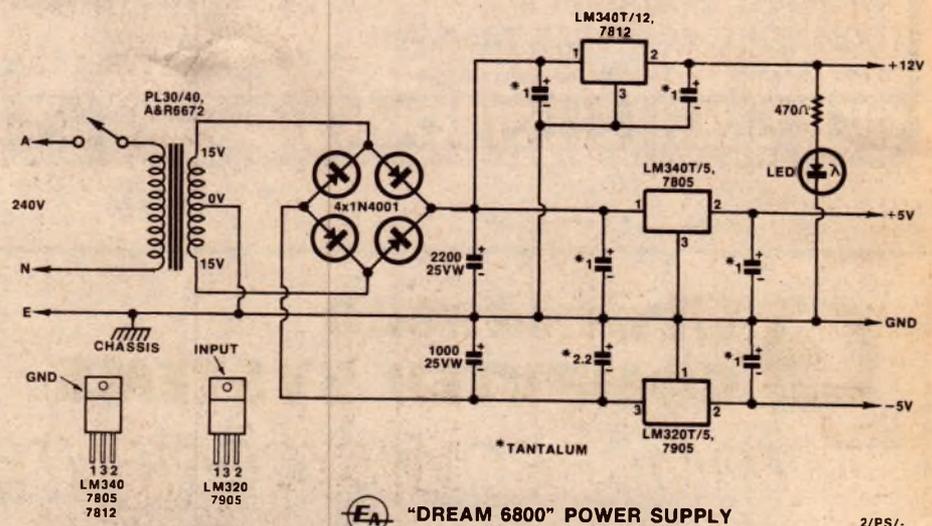

EA "DREAM 6800" POWER SUPPLY

2/PS/-

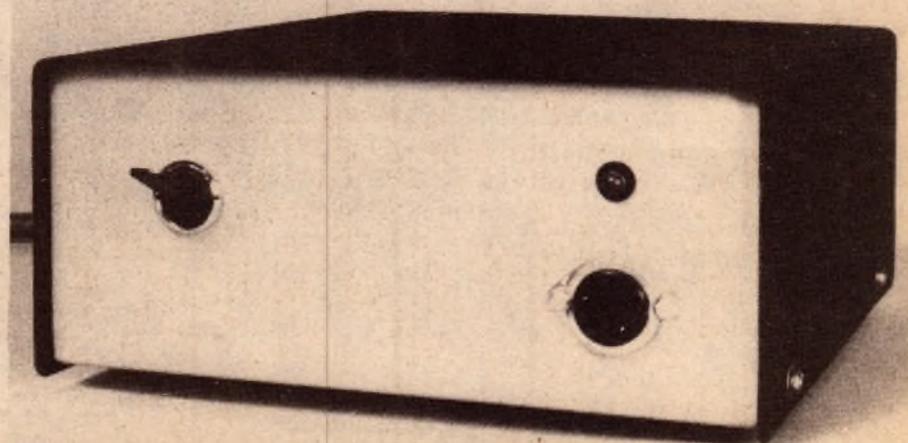This circuit has adequate current ratings for the requirements of the DREAM 6800.



The utilitarian looks of this power supply will not upstage the DREAM 6800 computer.

DREAM POWER SUPPLY

high frequencies.

We used a standard case from Dick Smith Electronics to house the power supply. This has a sturdy steel wrapover cover with ventilation holes, but the U-shaped pan section is made of light-gauge aluminium which is quite flimsy. In addition, it is painted so it is quite inadequate as a heatsink for the +5V regulator. Overall dimensions of the case are 160 x 70 x 184mm (W x H x D).

PARTS LIST

HARDWARE

- 1 case with lid, 160 x 70 x 184mm
- 1 PC board, 81 x 90mm, code 79ups6
- 1 transformer with 30V centre-tapped secondary at 1 amp DC or more; Ferguson PL30/40VA, A&R 6672, DSE M-6672 or similar
- 1 SPST mains toggle switch
- 1 3-way insulated terminal block
- 1 single-sided heatsink, 100 x 50mm, or larger
- 8 PC pins
- 4 Richo PCB supports
- 1 solder lug
- 1 4-pin polarised plug and socket
- 1 Mains cord and plug (preferably one-piece moulded type)
- 1 mains cord clamp

SEMICONDUCTORS

- 4 1N4001 silicon diodes
- 1 LM340T-5.0, regulator uA7805 regulator
- 1 LM340T-12, uA7812 regulator
- 1 LM320T-5.0, uA7905 regulator
- 1 LED and bezel holder

PASSIVE COMPONENTS

- 1 x 2200uF or 2500uF/25VW pigtail electrolytic
- 1 x 1000uF/25VW pigtail electrolytic
- 1 x 2.2uF tantalum electrolytic
- 5 x 1uF tantalum electrolytic
- 1 470 ohm 1/4 or 1/2W resistor

MISCELLANEOUS

Heatshrink tubing, hook-up wire, screws, nuts, lockwashers, solder.

NOTE: See text for possible component substitutions.

To solve the heatsink problem we cut a small window (about 20 x 25mm) in the rear of the case, coinciding with the position of the +5V regulator. This enabled this regulator IC to be bolted directly to a single-sided extruded aluminium heatsink of reasonable size. We did not fit heatsinks to the other regulators.

Note that the lead arrangement on the negative 5V regulator differs from positive regulators: the centre lead and metal flag are connected to the input rather than GND (OV).


Use PC pins on the PC board, to

simplify connections. 8 pins are required.


Several readily available power transformers can be used. We used the Ferguson PL30/40VA. Others which

would fill the bill are the A&R 6672 or the Dick Smith equivalent, M-6672.

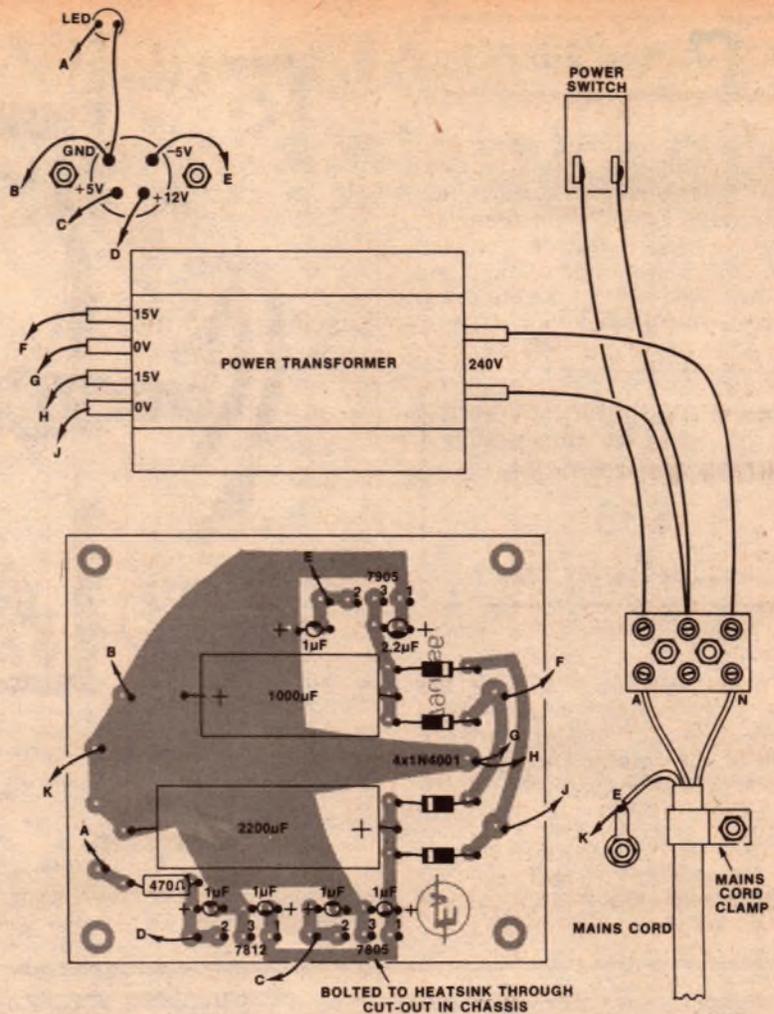Take care with the mains wiring. The three core mains cord should be passed through a grommetted hole in the rear



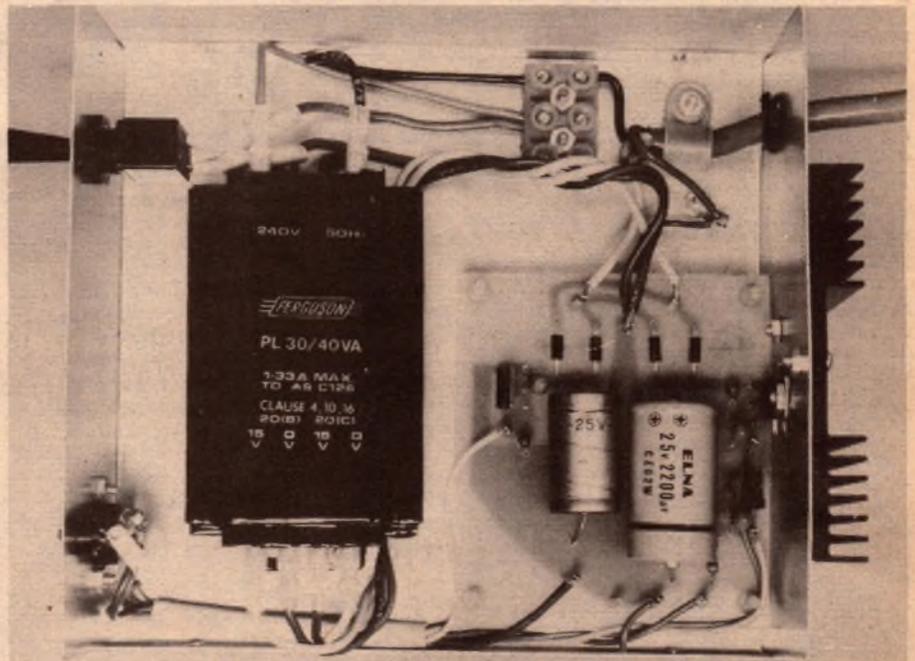Follow this diagram and the photograph below for easy assembly of the power supply.



DREAM POWER SUPPLY

of the case and anchored with a cord clamp. Mechanically terminate and solder the earth wire to a solder lug screwed to the case. Terminate the active and neutral conductors plus the wires to the transformer primary and the mains toggle switch via a three-way insulated terminal block.

We estimate that the current cost of parts for this power supply is approximately

\$38

This includes sales tax.


Make sure that the soldered connections to the mains switch and the transformer primary are insulated with heatshrink tubing or similar material. In the case of the Ferguson transformer, this problem is taken care of by sheathed push-on connections.

We terminated the regulator outputs in a 4-pin polarised socket which is convenient for cable connection. However there is no reason why


separate screw terminals or jack sockets could not be used.

Before the power supply is put into service it is a good idea to check the output voltages. Use a 47 ohm 1W resistor to load the 5V regulators and a

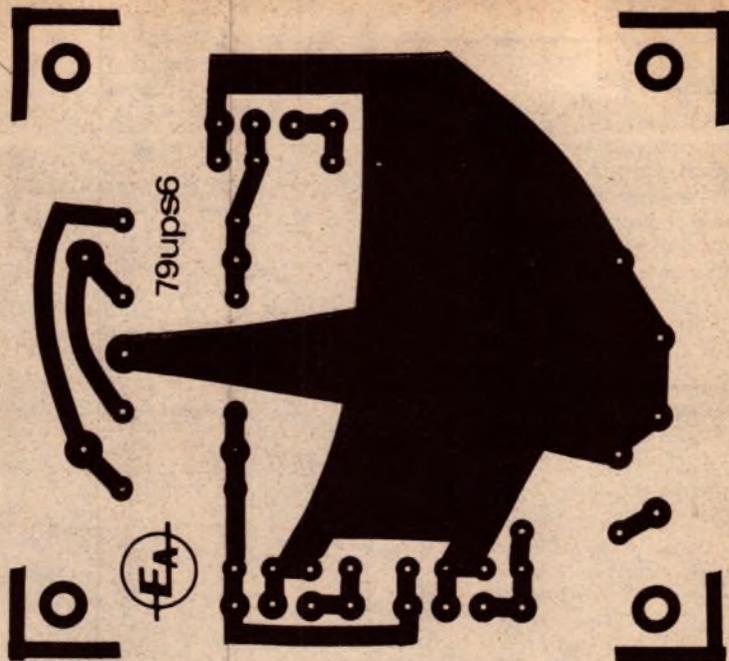100 ohm resistor of 2W rating or more for the 12V regulator. For the 5V regulators the acceptable range of output voltage is 4.75 to 5.25V, while for the 12V regulator the range is 11.4 to 12.6V.



Actual size artwork for the PC board.

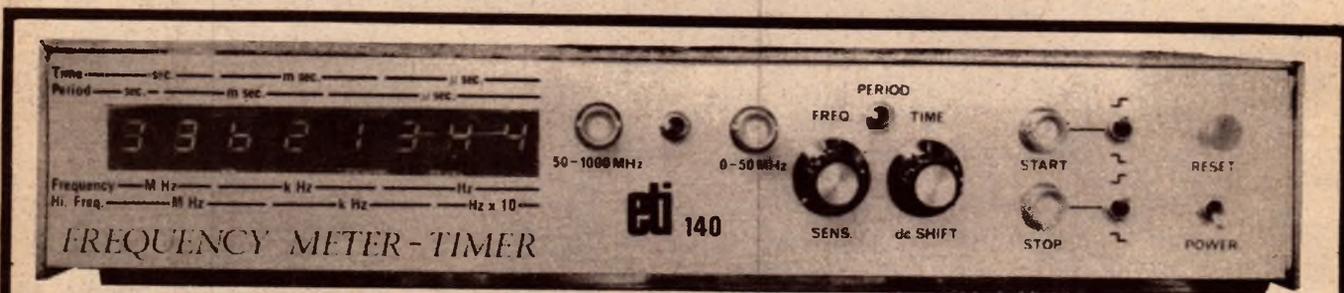

1 GHz DIGITAL FREQUENCY METER KITS

\$179 (\$199 inc. tax) Registered Post \$6; C.O.D. \$1 Extra.

Now features improved displays, and notes based on the hundreds of units built to help you avoid problems. Optional low cost "add-on" high stability oscillator. Details with kits, or upon enquiry. 50 MHz version (without prescaler) \$164 (\$182 inc. tax) plus post. ALL parts are supplied, and all are high quality and guaranteed. Pre-punched chassis with brushed aluminium front panel. Pre-tinned fibreglass P.C. board to ease construction. Can be successfully completed by anyone capable of good quality soldering who follows the instructions. Examine the kit carefully, and if you are not satisfied for any reason, or feel it is too difficult for you, return it in new condition within 10 days of purchase for a full refund. Service, at reasonable rates, is available. Details with kits. Tax free prices are available to manufacturers, educational and government institutions, students presenting the appropriate declaration, and export sales. Insured airmail to N.Z. and P.N.G. \$13. For further information see 'E.T.I.' March 1978, or contact us.

MAIL ORDERS AND ALL ENQUIRIES TO:

J. R. COMPONENTS

P.O. BOX 128 EASTWOOD N.S.W. 2122. PH. (02) 85 3976

COUNTER SALES FROM

JAYCAR PTY LTD, 405 SUSSEX ST, SYDNEY

SPECIFICATIONS ETI - 140

Modes of operation	Frequency, period and time
Range	
Frequency	10Hz - 50MHz
High frequency	50MHz - 1GHz*
Period	0.1µs - 10 sec
Time	1µs - 100 sec
Resolution	
Frequency	1Hz
High frequency	10Hz
Period	0.1µs
Time	1µs
Display	8 digit LED, leading edge blanking
Sensitivity	
Normal input	20 mV
High frequency input	20 mV
Time inputs	0V to +3V level shift
Input impedance	
Normal input	1Meg // 16pF
High frequency input	≈ 75 ohms
Time input	> 10k
Maximum input voltages	
Normal input	70 V ac, 100V dc
High frequency input	200 mV ac, 50V dc
Timing inputs	±100V dc
Crystal frequency	
nominal	4000 kHz
actual	3998.986 kHz
Stability and accuracy	
Frequency	Depends on crystal used and initial adjustment. Over used keeps temperature within 2°C.
Period and time	approx - 0.000125%

* The upper limit of the prescaler has not been checked due to the lack of a signal source but both the preamplifier (OM336) and the divider ICs are specified up to 1GHz.

ROD IRVING

FANTASTIC QUANTITY DISCOUNTS

10	TIP 32B	6.50
10	TIP 31B	6.50
10	FND 357	12.90
10	FND 500	12.90
10	RED LEDS	1.50
100	RED LEDS	13.00
1000	RED LEDS	110.00
10	7805	8.50
10	7812	8.50
10	BC547	1.20
100	BC547	10.00
100	IN4003	6.90
100	IN4004	7.00
10	4016	4.50
100	4016	42.00
6	LUGTAG STRIPS	.05
2	LM309K	3.00
10	GREEN LEDS	2.90
100	GREEN LEDS	25.00
10	YELLOW LEDS	2.90
100	YELLOW LEDS	26.00
10	4011	2.20
10	4001	2.20
10	7400	2.00
10	7410	2.00
10	7490	3.50
10	uA301	3.30
10	723	4.50
	LED CLIPS ea.	.02
100	LED CLIPS	1.50
100	MOLEX PINS	1.80
500	MOLEX PINS	8.50
1000	MOLEX PINS	16.00
20	BD139	9.00
20	BD140	8.00
10	BC548	1.40
10	BC549	1.40
10	BC557	1.80
10	BC558	1.80
10	BC559	1.90
10	74000	3.00
10	2102LP 450nS	15.00
2650	CPU ea	21.50
8080A	CPU ea	11.90
10	555 Timers	2.80
20	555 Timers	5.10
10	741 m DIP	2.80
20	741 m DIP	5.10
10	8 pin DIL	2.30
10	14 pin DIL	2.50
10	16 pin DIL	3.00
100	IN4148	4.00
1000	IN4148	35.00
2708	EPROM ea.	13.25
10 2708	EPROM ea.	125.00
2114	(450nS) ea.	7.50
8	2114 (450nS)	57.00
16	2114 (450nS)	112.00
32 2114	(450nS)	199.00
10	2N3055	7.00
10	SC141D	12.00
10	SC151D	21.00

LARGE ELECTROLYTICS

Lug Mounting Cans

90uF	450V	\$3.90	2500uF	80V	\$5.90
100uF	200V	\$1.90	2500uF	100V	\$8.90
100uF	350V	\$3.70	3300uF	75V	\$4.90
150uF	200V	\$2.50	4000uF	15V	\$2.30
220uF	350V	\$6.90	4000uF	75V	\$6.30
300uF	200V	\$3.50	4700uF	35V	\$2.90
1000uF	63V	2.90	4700uF	100V	\$9.50
1000uF	100V	\$3.70	5600uF	40V	\$1.90
1000uF	160V	\$6.50		PCB	
2500uF	35V	\$2.90	6800uF	50V	\$4.80
2500uF	63V	\$2.60	8000uF	75V	\$7.90

MULTIPLE CAPACITORS

4X22uF	400V	\$2.90	100+50	300V	\$6.90
40+40	350V	\$2.75	150+100		
50+50	350V	\$3.50	+100	315V	\$9.90
40+80	300V	\$4.30	200+60	275V	\$4.90
			200+100	350V	\$7.90

COMPUTER GRADE ELECTROS

2900F	40V	\$5.90	15,000uF	25V	\$10.30
6800uF	16V	\$5.75	22,000uF	25V	\$12.00
10,000uF	16V	\$8.00	22,000uF	40V	\$20.50
10,000uF	26V	\$9.00	27,000uF	35V	\$21.70
10,000uF	40V	\$11.50	68,000uF	16V	\$19.50

SOCKETS

10	8 PIN	\$2.30	100	14 PIN	\$23.00
100	8 PIN	\$20.00	10	16 PIN	\$2.80
10	14 PIN	\$2.50	100	16 PIN	\$25.00

KITS

ETI 480 100W Module	12 volt Electronic Siren Kits
Kit includes Heat Sink Bracket . \$19.75	1. "Whip" \$8.00
ETI 480 50 W Module	2. "Wail" \$8.00
Kit includes Heat Sink Bracket . \$16.00	3. "Flying Saucer" \$8.00
	Horn Speaker to suit \$8.50

ULTRASONIC TRANSDUCERS

as used in ETI 585R/T	40R \$5.95
ultrasonic switch	As a pair \$11.00
40T \$5.95	

SHOP 499, HIGH STREET, NORTHCOTE, VIC. 3070

Open: Mon-Thur 8am-5.30pm; Fri 8am-8pm; Sat 8.30am-12.30pm. Mail Orders: PO Box 135, Northcote, Vic. 3070. Minimum \$1.00 post and pack. Send 40c stamp for free condensed catalogue.

ELECTRONICS

Psst! Want the most complex clock in town?

LED display for your 2650

Interfacing your 2650 Mini Computer to a set of common-cathode LED displays requires only a single IC and a handful of other parts. With such an interface you can have your 2650 perform many number display tasks — including display of the time!

by **DAVID EDWARDS*** *69 Anglo Road, Campsie, NSW 2194

There are many applications where a processor is required to drive a simple numerical display, and this can be achieved in a variety of ways. It is possible to have either a multiplexed or non-multiplexed display, for instance, and one can decode from binary or BCD to seven-segment display format with either hardware or software. The circuit presented here uses hardware for the BCD to seven-segment decoding function, but has the multiplexing of the digits under software control.

A single 4511 CMOS IC is used to convert incoming BCD numbers to seven-segment format, and is connected to bits 0 to 3 inclusive of the "D"

non-extended output port on the 2650 system. Refer to the November 1978 issue for details of how to implement the I/O ports available with the 2650 CPU. Four 470k resistors are used to pull the inputs low, so that the decoder is present to the "0" state if no input signals are connected.

The lamp test (LT) and blanking input (BI) pins are tied permanently high, while the latch enable (LE) pin is tied low. +5V is supplied to the 4511 from the 2650 Mini Computer, and bypassing is provided by a 100uF electrolytic capacitor, in conjunction with a 0.1uF ceramic or polyester capacitor.

A four digit common-cathode LED display is required, and several options

are available here. For the author's prototype, a National Semiconductor multidigit display type number NSB7881 was used. This has four 0.7in digits mounted on a common PCB. Similar units with 0.3in and 0.5in high digits are also available, coded NSB3881 and NSB5881.

A similar unit by Fairchild is available from Dick Smith Electronics, and was advertised in the March 1979 issue, at the very reasonable price of \$4.95. The third alternative is to construct the display from individual seven-segment displays, such as the LT303 or TIL313 devices.

The 7 segment outputs of the 4511 are connected to the commoned segment lines via 82 ohm current limiting resistors. The four common cathode digit lines from the display are driven by BC337 switching transistors. BC548s could be substituted if required. Base signals for the transistors are developed from the remaining four "D" output port bits, bits 4 to 7 inclusive.

As you can see from the photographs, the prototype was constructed on a small piece of Veroboard, and connected to the computer by a short length of rainbow cable. It is not necessary to use a socket for the 4511, just exercise the normal precautions during soldering. Refer to the November 1978 issue for details of wiring the connector to the computer.

The completed display unit can be

*61E00 440 459	
0440 76 40	PPSU 40
0442 75 18	CPSL 18
0444 04 82	LODI, R0 82
0446 F0	WRD, R0
0447 F9 7E	BDRR, R1 0447
0449 04 46	LODI, R0 46
044B F0	WRD, R0
044C F9 7E	BDRR, R1 044C
044E F0 25	LODI, R0 25
0450 F0	WRD, R0
0451 F9 7E	BDRR, R1 0451
0453 04 10	LODI, R0 10
0455 F0	WRD, R0
0456 F9 7E	BDRR, R1 0456
0458 1B 6A	BCTR, UN 0444

Fig. 2: A listing of the small routine written by the author to demonstrate the LED display.


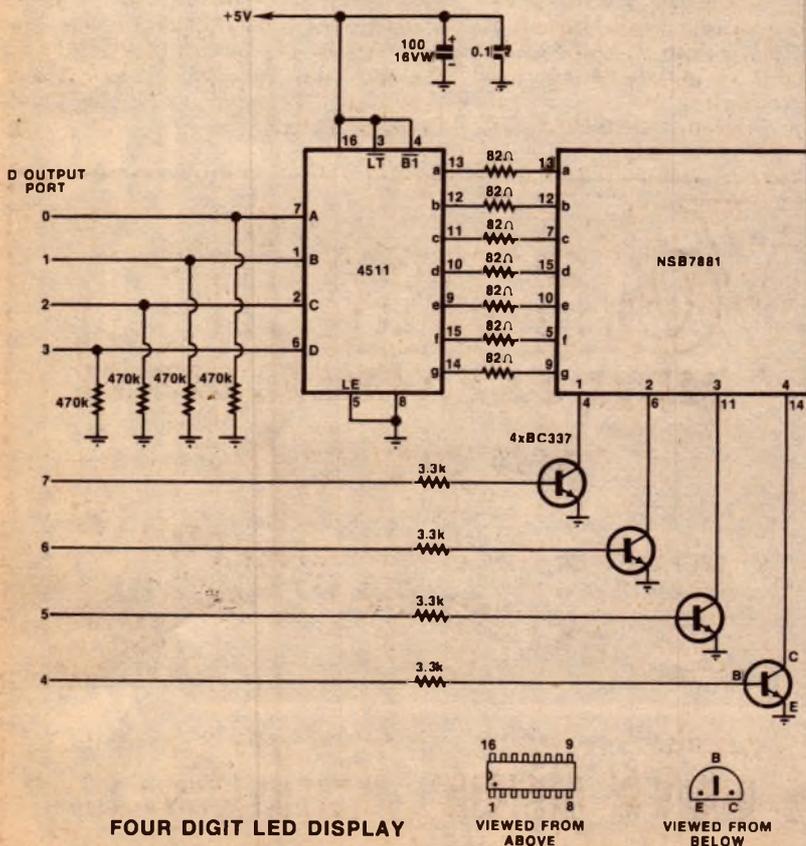
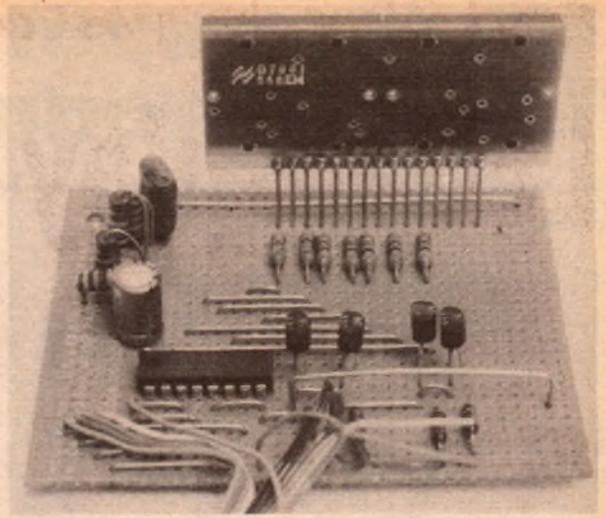


Fig. 1: The circuit for the author's software-driven four digit LED display. It interfaces to the 2650 Mini Computer via the non-extended "D" output port.

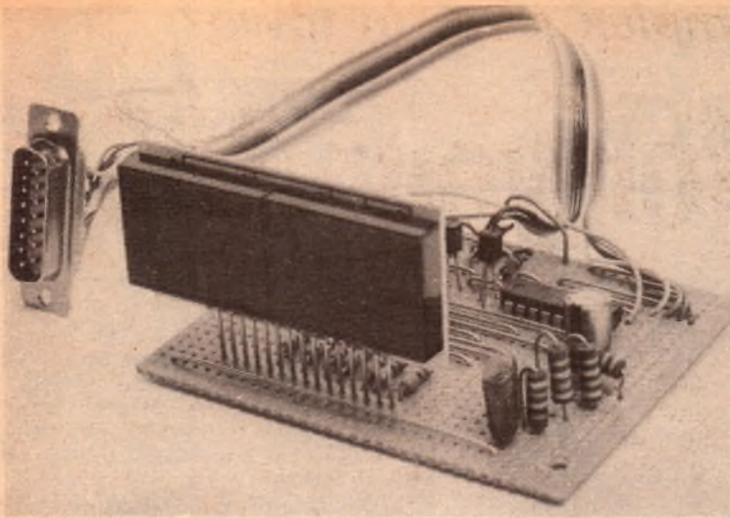

```

0440 76 40 75 18 3F 02 DB 77 08 75 21 08 0C 82 94 C2
0450 E6 60 1A 20 06 00 75 20 04 67 81 94 C1 E5 24 1A
0460 19 05 00 C0 77 10 05 51 06 1D 3B 1D F9 7C FA 7A
0470 75 10 1B 53 04 05 F8 7E C0 C0 1B 68 50 50 50 50
0480 44 0F 17 F0 04 DC F8 7E 17 75 18 01 3B 6E 64 80
0490 3B 71 01 44 0F 64 40 3B 6A 02 3B 60 64 20 3B 63
04A0 02 44 0F 64 10 3B 5C 77 10 C0 17
  
```

The photographs above show two views of the prototype display built by the author on a small piece of Veroboard. The wiring is not critical.

Fig. 3 (left): A HEX LISTING OF THE TIME program, which turns the 2650 and display into a 24-hour clock.

tested before connecting it to the computer. Connect +5V to the board, and observe the display. No numerals should be visible. If any are, switch off, and check the wiring associated with the four transistors. Assuming all is well, use a clip lead to connect the number 4 input bit to +5V. The right-most digit should now read "0", with all other digits off.

By applying +5V to inputs 5, 6 and 7 in turn, you should be able to make the digits read zero in turn. If you want to, you can apply BCD codes to the inputs of the 4511 by pulling the appropriate pins high, and check that the appropriate digits are displayed. However, if you were like the author, you will want to see the computer operate the display, and will not bother to carry out this test.

Fig. 2 is a listing of a small program which will exercise the display. It is completely relocatable, and can be stored anywhere in memory. The first address is the starting address. The program assumes that the display unit is connected to the D output port.

The program repeatedly writes four data bytes to the display, with a small delay between each successive write. The first data byte is X'82, and this displays the numeral 2 in the left most digit of the display. The nybble "8" (binary 1000) turns on this digit, while the nybble "2" is decoded by the 4511 to produce the seven-segment code for the numeral 2.

Similarly, the second data byte (X'46) displays a 6 in the 2nd digit from the left, and so on. The delay between each WRTD instruction, produced by the BDRR, R1 instruction, is necessary in order to provide a glitch free display. Without this delay, all segments of the display tend to glow, due to inherent

circuit delays caused by stray capacitance.

You can change the number displayed by altering the lower four bits of locations X'445, 448, 44F and 454. To turn a selected digit completely off, use a non-BCD number such as X' A to F.

The second program presented here is shown as a hex listing in Fig. 3. It occupies locations X'440 to 4AA inclusive, and is again completely relocatable. It is called TIME, and will make the computer and display unit appear to be a 24 hour clock. It uses the Pipbug routine GNUM to get an initial starting time from the line buffer.

To call the program, type G440 AABB,

where AA is the current time in hours (e.g. 20 if it is 8PM), and BB is the current number of minutes past the hour. Do not press the carriage return key until the current minute has ended; the time displayed will then be correct to the nearest second (provided you press the cr key precisely at the 60 second time).

The program assumes that the CPU oscillator is running at exactly 1MHz. Changing the contents of location X'467 by one will vary the timing by approximately one part in 10,000. If location X'467 is incremented, the clock will slow down. To return to Pipbug, press the reset switch. 2

Verbatim

MINI FLEXIBLE DISKS

MD 525 1-9 \$4-25
10up \$4

SPECIFY SECTORING OR SYSTEM

OFFER EXTENDED INDEFINITELY

DEALER ENQUIRIES WELCOME.

(062) 815011

P&P Incl — add 15% sales tax

THE BYTE SHOP

PO BOX 118, MAWSON, ACT 2607
29 COLBEE CRT PHILLIP

Microcomputer News & Products




Compucolor II now in Australia

Anderson Digital Equipment, representatives for the US Compucolor Corporation, advise that they now have stocks of the new Compucolor II high-performance personal computer system. Features of the system include integral 33cm colour CRT monitor and mini floppy disc drive, 16K or 32K bytes of user RAM, and system software providing extended DISC BASIC in ROM, full colour graphics, disc file handling, RS-232 driver for a printer or modem, and utility programs like a test editor and 8080 assembler. A range of pre-programmed diskettes are available with games, etc.

Options available with the Compucolor II systems include a second mini floppy drive, expanded keyboard and deluxe keyboard. An additional 16K RAM modification is also available to convert the 16K model to 32K. Both models are provided with a 50-pin expansion connector for future expansion.

Price of the 16K Model 4 Compucolor II system is \$1995, with the 32K Model 5 costing \$2395. The additional disc drive is \$495. All prices include import duty and 240V/50Hz conversion.

Further information is available from

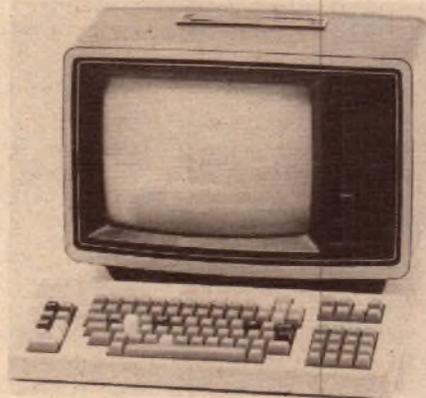

Anderson Digital Equipment Pty Ltd,
P.O. Box 294, Ryde NSW 2112.
Telephone (02) 808 1444.

8K static RAMs

Two new 8K static RAM devices have been released by Mostek, and are available from local Mostek agents Amtron Tyree. The MK4801 and MK 4118 are both organised as 1K x 8 bits, making them very well suited for microcomputer applications. They are both in 24-pin DIL packages with a pinout compatible with existing Mostek ROM and EPROM devices, for further system flexibility.

The MK4801 is a special 100ns device

for high speed cache and buffer memory applications, while the MK 4118 is designed for standard microcomputer applications requiring access times of 120-250ns. Both devices use Mostek's Poly-R N-channel silicon gate technology and are TTL compatible. They feature an optional address latching function.

Further information is available from Amtron Tyree Pty Ltd, 176 Botany Street, Waterloo NSW 2017. Telephone (02) 698 9666.

Club in Geelong . . .

We have been advised that a computer club was formed in Geelong in October, 1978, and is now well established. The Geelong Computer Club meets on the second Thursday of each month at Tybar Engineering, Hampton Street Newtown, Geelong Victoria. The club contact is honorary secretary/treasurer Ian J. Stacey, c/o P.O. Box 93, Geelong 3220, or telephone (052) 22 1455 in business hours.

. . . and in SA

A Users' Group for Tandy TRS-80 users has been started in Adelaide, with meetings held on the first Thursday in the month at the local Tandy store. The contact is Mr R. G. Stephenson, 34-36 Sturt Street, Adelaide SA 5000, or telephone (05) 51 5241. Meetings are not formal, more in the nature of a friendly "get together".

Wire-wrap board

A new wire-wrap board compatible with Motorola Exercisor systems is now available from Pennywise Peripherals. To minimise noise, which can be a problem on such boards, the layout is based on recommendations by Telecom arising from research on "Noise in Digital Systems".

The PCB has the standard Motorola micromodule dimensions of 248 x 153mm and has all holes through-plated for maximum pad anchorage. It has provision for card ejector levers if desired. Either 0.3in or 0.6in spacing DIL packages can be accommodated. The board is priced at \$46.70 plus 15% tax if applicable.

Pennywise Peripherals also advise that its M4-16 16K byte static RAM card is now available in two speeds: 300ns or 450ns. The cards use low-power 2114


16K PROM CARD + PROGRAMMER

FOR LATEST 2K x 8 SINGLE +5V 2716 EPROMS

- For INTEL 2716 & TEXAS 2516 EPROMs
- Runs entirely from +5V
- Execute programs from any PROM
- Program any PROM location in 50ms with a single store instruction
- Write protect switch.
- Motorola Exercisor bus as on D2 Kit
- Compatible with 6800, 8080/5, 6502, 2650, SC/MP etc.
- Two 8K switch addressable blocks.
- PCB plated through with solder resist

NEW PRODUCT

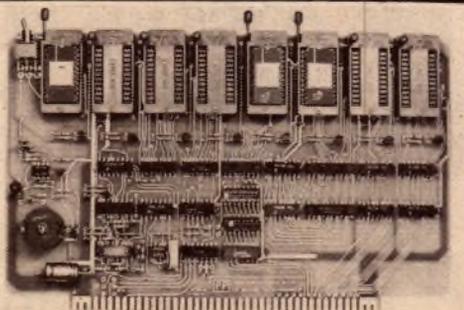16K/32K/64K PROM Card for mixtures of 2708, either 2716, 2732. Has software controlled 4K bank select.



Assembled & tested only
\$197.30 with Low Insertion Force Sockets
\$236.20 with Zero Insertion Force Sockets
 (P&P \$3.00, add 15% if Sales Tax is Applicable)
 SINGLE +5V 2716s available
PRICE ON APPLICATION

Designed & Manufactured in Australia
 19 Suemar St, Mulgrave Vic. 3170.
 (03) 546 0308

PP Pennywise
Peripherals

devices and consume only 1.2A when fully loaded. The firm's 2708 programmer card has also been upgraded, with plated-through holes and solder resist on both sides. An application note is also available explaining how to program triple-supply 2716 EPROMs using this programmer.

Further information is available from Pennywise Peripherals, 19 Suemar Street, Mulgrave, Victoria 3170.

Commodore PET



The Commodore PET desktop computer is to be marketed in Australia by the Business Equipment Division of Hanimex Pty Ltd. It will sell for about \$1500, around the middle of the price range for personal computers now available here. Hanimex is anticipating healthy sales, as 25,000 PET systems were apparently sold in the USA last year. Some 200 applications programs are now available for use on PET systems, written in BASIC; 140 of these are for small business use.

Cromemco dealer

Adaptive Electronics has announced that it is now a dealer for the Cromemco range of microcomputer systems and peripherals. Cromemco offer an advanced range of S-100 microcomputer systems and components based on the Z-80 microprocessor, and suitable for applications in business, education, process control, word processing and scientific or engineering computing. Cromemco systems available range from the small Z-2 system intended for EPROM-based dedicated control applications to the advanced System Three, incorporating up to four 8-inch floppy disc drives and sophisticated disc protection. A wide variety of system and application cards is also available, all to S-100 standards. Recent additions to the range include a 64K byte RAM card, a 32K byte EPROM card with programming facility, and an optically isolated 4-port I/O card for power control.

Further information on the Cromemco range of systems and products is available from Adaptive Electronics Pty Ltd at 77 Beach Road, Sandringham, Victoria 3191.

EIGHT SELF-STUDY COURSES ON CASSETTES

THE TIME-EFFICIENT WAY TO LEARN™

THE COURSES by Dr Rodney Zaks

All courses include 2 to 8 audio cassettes and a special workbook. They can be used at home, in the office or in the car.

THE FASTEST WAY TO LEARN

The lecturer stresses all important points in a systematic way. Reference books are available to study details.

1 — SHORT COURSES (INTRODUCTORY)

Each course lasts 2-5 hours and does not require a computer background. \$39.95 each.

- S1 — MICROPROCESSORS (the hardware)
- S2 — PROGRAMMING MICROPROCESSORS (the software)
- S3 — DESIGNING A SYSTEM (the interconnect)

2 — COMPREHENSIVE COURSES \$59.95 each

- SB1 — MICROPROCESSORS (12 hours)
- SB2 — PROGRAMMING MICROPROCESSORS (10 hours)

3 — SPECIALIZED COURSES \$49.95 each

- SB5 — BIT SLICE (6 hours)
- SB6 — INDUSTRIAL MICROPROCESSOR SYSTEM (4-5 hours)
- SB7 — MICROPROCESSOR INTERFACING TECHNIQUES (6 hours)

REFERENCE TEXTS

C200 — An Introduction to Personal and Business Computing	\$12.40
C201 — Microprocessors	\$14.00
C202 — Programming the 6502	\$15.00
C207 — Microprocessing Interfacing Techniques	\$15.90

THE TRENDCOM INTELLIGENT PRINTER IS HERE. For the Apple, Pet, TRS-80 (level II with interface) and Sorcerer. And affordable! Write for details please state the name of your computer.

THE BASIC HANDBOOK by Dr David Lien, is needed by students and programmers at every level. \$15.70. An excellent book.

BOTTOM SHELF PROGRAMS ON CASSETTE FOR YOUR TRS-80. Write for details.

Postage and handling: \$1.20 per book, double for cassettes.

Note: for cassettes only: 10% discount for schools.

COMPUTERWARE

63 Paisley Street,
Footscray, Vic. 3011.
Telephone: 68 4200.

LOOKY VIDEO

FACSIMILIE TRANSCIEVER NeFAX — 1000 EX F

The instant telephone postman

3, 4, 6 minute per picture

Input: black and white or colour

Output: black and white only

Size A4 paper

\$1,800

(incl. tax)

Bigger and faster machines also available.

WIDE RANGE OF VIDEO EQUIPMENT

Fairchild programmable TV Games only

\$199.00

& Cartridges at

\$17.95 (each)

VHS Recorders (prices on application)

U-MATIC: Reel to reel recorders, etc.

Trade-ins and demo models from \$350

National Giant TV

\$5498

AMATEUR AND VIDEO

TV cameras b/w from \$269.00, colour from \$1,395.00

COMMUNICATIONS RECEIVER DR48 \$469.00

ALSO AVAILABLE A RANGE OF EDUCATIONAL AND FUN GAMES

T.I. CALCULATORS, SOLAR ELECTRICITY

G.E. BATTERIES & CHARGERS

Dubbing and editing from \$10 per hour.

CASH — CARDS — TERMS — LEASING

For further details contact:


Bruce Fisher VK3 YRF/A.T.V. at:

LOOKY VIDEO

418 Bridge Rd,
Richmond, Vic. 3121
(03) 429 5674

All mail to: PO Box 347, Richmond, Vic. 3121.

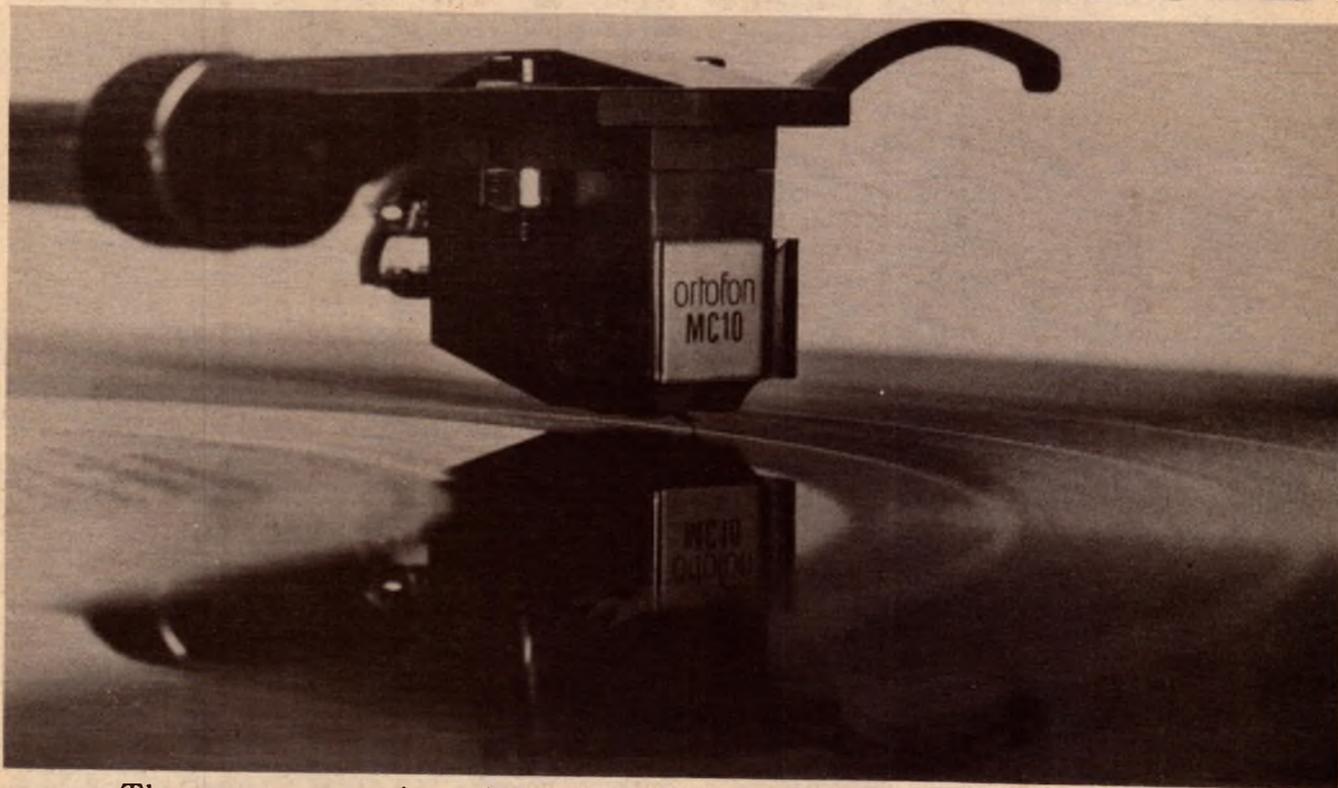A MOVING COIL CARTRIDGE AT A PRICE YOU CAN AFFORD.



The experts agree. A moving coil cartridge reproduces music more accurately than any other design. But such a cartridge represents the tip of a very expensive system. For one thing, the coils have to be painstakingly wound under a microscope. For another, its small output voltage and low inner resistance requires a transformer to boost the signal. So the moving coil cartridge is great. And expensive. Great? Yes. Expensive? No longer.

AN AFFORDABLE MOVING COIL.

Ortofon, the developers of the moving coil design, and the most respected name in quality cartridges, has made it possible to own a moving coil cartridge - the MC 10 - at the price of a good magnetic model.

Your Ortofon dealer is now ready to demonstrate the MC 10 and surprise you with its affordable price.

THE RECORD CUTTERHEAD AND THE MOVING COIL.

A cutterhead uses a moving coil system to inscribe music onto a master record. With a moving coil playback cartridge you "extract" the music in the same way. This direct "unravelling" of the music explains, in part, why the moving coil cartridge reproduces musical sound with unparalleled accuracy.

CHANGE TO A MOVING COIL CARTRIDGE. THE NEW MC 10 FROM ORTOFON.



ortofon accuracy in sound

Distributed by:-
HARMAN AUSTRALIA PTY. LTD.,
P.O. Box 6, BROOKVALE, N.S.W. 2100
Telephone: (02) 939 2922

MA118/78

Especially for the

AUDIOPHILE

by NEVILLE WILLIAMS



Reviewed below are several discs which should be of special interest to dedicated audiophiles. All are direct cut; one is a test and demonstration disc from Ortofon, one is recorded at 45rpm and the other has been acclaimed overseas as one of the best-ever recordings of a concert organ.

First off, and of special interest, is a direct-cut test and demonstration record produced by Ortofon of Sweden. While it would be a handy disc to have in an audio lab, it is primarily intended to be used in the home by the enthusiast who is keen to check the operation of his amplifier system.

ORTOFON PICKUP TEST RECORD. Stereo, direct cut, number 0001. Side 1, tests. Side 2, music from the Concert Hall of the Tivoli Gardens, Copenhagen.

The disc comes in a double-fold jacket, with general notes on the inside face and a separate brochure which explains what the tests are all about.

It is interesting to note from this brochure that Ortofon has been in the audio business for over 60 years, dating from the time when its founders, Axel Petersen and Arnold Poulsen developed what they claim to be the first sound film projection system. The patent rights were sold in America.

In the thirties, the Company developed a line of high quality disc cutting heads utilising the moving coil principle.

In the forties, Ortofon engineers succeeded in reversing the concept to produce the first of a series of moving coil pickups, which were accepted enthusiastically, the world around. Moving coil pickups still feature in the Ortofon range but they have been supplemented by magnetic cartridges and a variety of other associated products.

Now comes the test record produced of course, with Ortofon equipment and utilising the latest direct cut techniques.

Side 1 is devoted entirely to test tracks. Each is separate, making it necessary to move the head manually from track to track. This is something of a nuisance but, without a tape master, and working from instrument set-ups, a continuous direct cut spiral would be fiendishly difficult to arrange, if not impossible!

Track 1, introduced by a gentle

female voice (how agreeable) carries white noise, and is intended to check for correct left/right channel connections, channel balance and channel phasing. In use, it would present no problems for an experienced audiophile.

Track 2 allows the listener to judge whether the overall channel separation is less, equal to, or greater than 20dB, 25dB or 30dB. It uses a broadband signal filtered down to a 316Hz bandwidth and centred on 1kHz. Again relying on the listener's ears, it gives a quite positive indication.

The signal-to-noise ratio of the entire system can be assessed with the next track, which offers white noise in graduated steps down to minus 60dB. The notes warn that the recording system itself tends to mask the difference between -50 and -60dB as also will any turntable rumble, amplifier noise and hum, and general household background.

Track 4 is a silent, unmodulated groove, cut with a locked stylus to ensure freedom from recording amplifier noise. Virtually all noise heard when this groove is played would originate from the playback chain.

Track 5 provides an unusual test, reflecting on the quality of the stylus and cartridge, tracking conditions and linearity within the preamplifier. High frequency tones (20kHz to 7kHz) in pairs 1kHz apart are recorded together and pulsed alternatively with a 1kHz reference tone. If the high frequency tones intermodulate heavily, the resultant will dominate the reference tone to produce a dash-dot (Morse N) signal. If intermodulation is slight, dot-dash (Morse A) will be heard.

CLASSICAL RECORDS

Julian Russell, who prepares our monthly review of classical recordings, was taken ill, involving a stay in hospital. He is now recuperating but, until he is well again, his column will be taken over by Paul Frolich.

Cartridge tracking ability, horizontal and vertical, is probed by a 315Hz signal at various levels in tracks 6 and 7, while 8 and 9 allow the user to check for arm/cartridge resonance. Ortofon engineers nominate 10-12Hz as the range in which the resonance should centre, with the added observation that it should also be well damped.

Contrary to usual practice, the disc provides no frequency runs or bands. Apart from lack of space on the disc, Ortofon engineers may well have reasoned that they can be more of a hindrance than a help in subjectively assessing high quality equipment. At low frequencies, subjective loudness is dominated by standing waves in the room while, at high frequencies, the hearing acuity of the listener becomes a limiting factor.

But, frequency tests notwithstanding, the tracks provided on the Ortofon disc allow the listener to check and adjust his amplifier system in a number of important respects.


Side 2 of the disc is a live, on the spot recording of the Tivoli Symphony Orchestra in the concert hall of Copenhagen's Tivoli Gardens. Featured are a variety of compositions by Christian Lumbye, who was often referred to as "Scandinavia's Strauss". It is pleasant, lilting music, easy on the ear, and with a wide range of instrumental tone colour.

The quality of reproduction is first rate — as it should be. The special Ortofon cutting head and stylus, designed originally for CD-4 quadraphonic, is driven by a 500W amplifier and is within plus and minus 0.5dB of the target response from 10Hz to 26kHz. With microphones covering way beyond this range again, the only artificial restriction was a 6dB per octave filter below 15Hz, to minimise possible sub-audible modulation on the groove.

Ortofon is represented in Australia by Harman Australia Pty Ltd, but the disc can be obtained through Ortofon stockists in all states. The recommended retail price is \$17.00.

Hioki

Dependable Multitesters

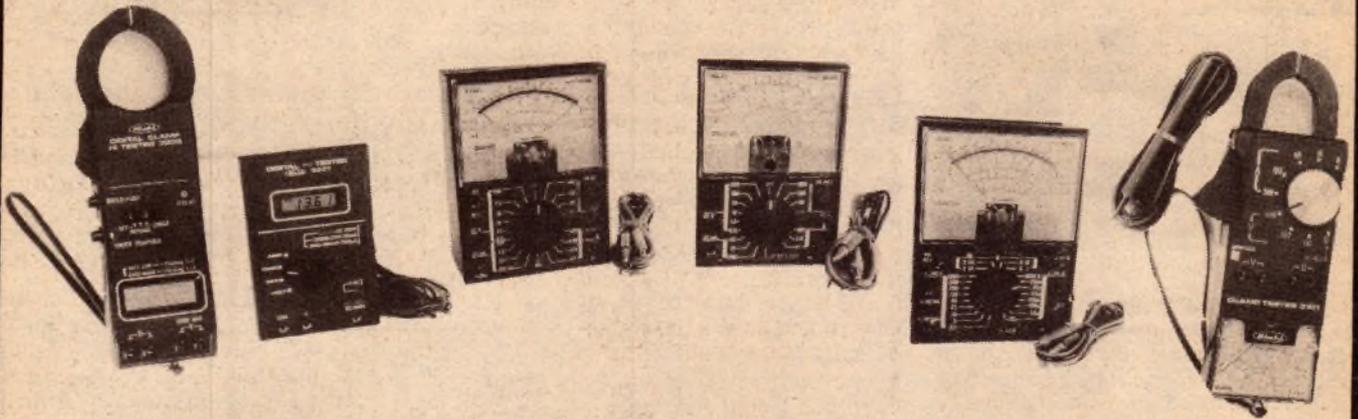

BRIEF SPECIFICATIONS FOR SOME POPULAR MODELS FROM THE EXTENSIVE HIOKI RANGE OF TAUT BAND ANALOGUE AND DIGITAL INSTRUMENTS

SPECIFICATIONS

3001 TESTER FOR APPLIANCES AND GENERAL HOUSEHOLD

0.25/2.5/10/50/250/1000V DC $2k\Omega/V \pm 3\%$
 0.5/10/250mA DC $\pm 3\%$
 10/50/250/1000V AC $2k\Omega/V \pm 3\%$
 3k/30k/300k $\pm 3\%$ F.S. R.C. 26Ω

3002 PRACTICAL COMPACT TESTER

0.5/2.5/10/50/250/1000V DC $20k\Omega/V \pm 3\%$
 50 A/25/250mA $\pm 3\%$
 10/50/250/500/1000V AC $9k\Omega/V \pm 3\%$
 10k/100k/1M $\pm 3\%$ F.S. R.C. 100Ω
 L.F. Output -20 to $+36dB \pm 4\%$

3003 PRACTICAL MEDIUM CLASS TESTER

0.25/2.5/10/50/250/1000V DC $30k\Omega/V \pm 3\%$
 $50\mu A/2.5/25/250mA/10A$ DC $\pm 3\%$
 10/50/250/1000V AC $13.5k\Omega/V \pm 3\%$
 10A AC $\pm 4\%$
 5k/50k/500k/5M $\pm 3\%$ F.S. R.C. 50Ω
 L.F. Output -20 to $+36dB \pm 4\%$

3005 HIGH CLASS TESTER WITH RELAY PROTECTION

0.25/1/2.5/10/50/250/1000V DC $50k\Omega/V \pm 3\%$
 $50\mu A/2.5/5/50/500mA/10A$ DC $\pm 3\%$
 10/50/250/1000V AC $10k\Omega/V \pm 3\%$
 10A AC $\pm 4\%$
 2k/20k/200k/2M $\pm 3\%$ F.S. R.C. 20Ω
 L.F. Output -20 to $+36dB$

3010 HIGH SENSITIVITY ($10\mu A$ OPERATING CURRENT) TESTER WITH RELAY PROTECTION

0.1/1/2.5/10/50/250/500/1000V DC $1000k\Omega/V \pm 3\%$
 10 A/100 $\mu A/1/10/100/500mA/10A$ $\pm 3\%$
 10/50/250/500/1000V AC $10k\Omega/V \pm 3\%$
 10A AC $\pm 4\%$
 2k/200k/2M/20M $\pm 3\%$ F.S. R.C. 20Ω
 L.F. Output -20 to $+36dB$

3011 HIGH CLASS WIDE RANGE TESTER FEATURING ELECTRONIC RELAY PROTECTION

2.5/5/10/25/50/100/250/500/1000V DC $40k\Omega/V \pm 2\%$
 $25\mu A/50\mu A/100\mu A/250/2.5m/25m/250m/2.5A/10A$ DC $\pm 2\%$
 $2.5/5/10/25/50/100/250/500/1000V$ AC $10k\Omega/V \pm 3\%$
 $25\mu A/50\mu A/100\mu A/250\mu A/2.5m/25m/250mA/2.5A/10A$ AC $\pm 3\%$
 3k/30k/300k/3M $\pm 2\%$ F.S. R.C. 20Ω
 L.F. Output -20 to $+36dB$

3205 DIGITAL MULTITESTER SEMI AUTO RANGING WITH FE-LIQUID CRYSTAL DISPLAY AND HIGH ACCURACY

DC V 0-200mV/2000mV/20V/200V/1000V $10M\Omega$
 AC V 0-200mV/2000mV/20V/200V/1000V $10M\Omega$
 Ω 0-200/2000/20k/200k/2M/20M
 DC A 0-200 $\mu A/2000\mu A/20mA/200mA$
 AC A 0-200 $\mu A/2000\mu A/20mA/200mA$

3101 CLAMP TESTER WITH CONVENIENT METER LOCK

6/15/60/150/300A AC $\pm 4\%$
 150/300/600V AC $2k\Omega/V \pm 3\%$
 0-1k Ω (Centre 30Ω) $\pm 3\%$ F.S.

3206 DIGITAL CLAMP TESTER TO 1000A AND FE-LCD FEATURES READING HOLD FACILITY AND SURGE HOLD FOR MOTOR START READINGS. SPECIAL 0-20A RANGE PROVIDES 0.01A RESOLUTION.

AC A 0-19.99 (Push Button) 0-199.9/1000A (Auto)
 Surge Current 0-1000A
 AC V 0-199.9V/1000V (Auto)
 Surge Voltage 0-1000V
 0-199.9/1999 Ω (Auto)

A WIDE RANGE OF OPTIONAL ACCESSORIES ALSO AVAILABLE.

Hioki Multitesters are available through your favourite stockist or electrical wholesaler. If he does not have the model of your choice ask him to order it for you. For further information contact:—



& CO. PTY. LTD.

(Sole Australian Agents)

Melbourne 329 6511;

Sydney 601 6600; Brisbane 52 5231;

Perth 446 6622 Adelaide 46 6411;

DIRECT-CUT CLASSICS IMPRESS

BEETHOVEN. Piano Sonata No 23 in F Minor, Op 57, "Apassionata". Ikuyo Kamiya. Stereo, direct cut, 45rpm. (From M. R. Acoustics, P. O. Box 165, Annerley, Qld 4104. Also from specialty record stores. Price \$19.00)

According to the jacket notes, this recording was made in February 1977, in the Iruma Public Hall (Japan) and using a German Bosendorfer Imperial grand. Produced by the Victor Company of Japan, it was released in America through RCA — an ironic twist because it was RCA who, in the early days of microgroove recording fought to have the industry standardise on 45rpm. In the event, RCA got their way with 7-inch singles and EPs but albums gravitated to 33rpm, with the support of CBS, Decca and others.

With direct cuts, it is not possible to pre-monitor the program for purposes of automatic groove spacing. Because of this restriction JVC engineers point out that the playing time for a 45rpm direct cut is limited to 10 to 12 minutes per side. On the other hand, the higher speed markedly reduces the steepness of transient wavefronts, giving about 5dB of extra "headroom" for transient peaks, for a given level of distortion.

On this disc, side 1 carries Allegro assai and side 2 Andante con moto and Allegro ma non troppo.

The performer may not be well-known to many but is a Japanese woman in her early thirties who has won acclaim in both her own country and in Europe. She displays an impressive amount of physical resource at the keyboard.



Some may note minor stylistic details in the performance, but variance with European traditions but the fact is that JVC and RCA have entrusted her with the program content of a disc that, for its production, required an enormous logistic effort.

As the notes point out, dismantling, transporting, installing and setting up a precision transcription lathe and drive amplifier is a very different proposition from handling even a top quality tape recorder.

As a recording, it is tremendously impressive. As distinct from the purist approach of twin microphones only, JVC engineers used another four in the

body of the auditorium to capture the right amount of ambience. As a result, the piano has a powerful presence but is enriched by ample natural ambience.

The dynamic range is outstanding and absolutely demands a quiet listening room, free from traffic and household noises if you are going to listen through the quiet passages, without ear shattering fortissimos or knob twisting — which would defeat the whole concept!

The beauty of it is that the quiet passages are unspoiled by background or surface noise, while the fortissimos remain completely clean, with hard, biting transients.

This indeed is a show disc that should entertain the ears of any audiophile!

CONCERT ORGAN

MICHAEL MURRAY at the Great Organ in the Methuen Memorial Music Hall. Stereo, direct cut. Telarc 5036B. (From P. C. Stereo, P. O. Box 272, Mt Gravatt, Qld 4122. Also from specialty record stores Price \$19.50 posted).

The organ featured in this album was originally installed in the Boston Music Hall in 1857-63 by E. F. Walcker of Ludwigsburg, Germany. As such, it was the first full concert organ to be installed in the USA. However, despite its

popularity it was removed from the Hall in 1884 to make way for the Boston Symphony Orchestra and was stored for the next 13 years. In 1897 the organ was purchased by E. F. Searles, who built a special hall to house it at Methuen, about 20 miles from Boston city.

The Hall later passed to public ownership and, in 1946, the organ was revised and modernised by the Aeolian-Skinner company. Now with its 84 stops, 115 ranks and 6065 pipes — including a recently added reed chorus — it ranks as one of the fine organs of America.

The featured organist is Michael Murray, pictured as a young man, with an already extensive musical background and currently the Municipal organist of Cleveland. He is credited by one overseas reviewer as having "the fleetest fingers and feet in the business". Certainly, he finds no



SPECIAL THIS MONTH \$195.00 ONLY. FOR FRINGE OR DX

- 1 — Crown Model 24. Rotator 13kg weight loading
Wind loading 70 miles per hr: NORMAL PRICE \$99.00
- 1 — Hills TL4-11 element wideband log periodic NORMAL PRICE \$46.48
- 1 — Kingray 20dB Masthead amplifier
75 & 300 ohm input & output NORMAL PRICE \$74.97
- TOTAL NORMAL PRICE \$220.45**

CB SPECIAL

REPLACE YOUR AERIAL SYSTEMS

- 1 — Belling Lee helical 5ft whip aerial with base
& 12ft lead and plug. NORMAL PRICE \$27.00
- 1 — Ecraft ¼ Ground plane aerial NORMAL PRICE \$37.73
- TOTAL NORMAL PRICE \$64.73**
- SPECIAL PRICE \$40.00**

ROYCE POWER/SWR TWIN METER MODEL 2-098. Range measured 0-10 WATTS, 10-100 WATTS. 2 ranges. SWR Meter 1:1 to 1:3 V.S.W.R. Frequency response 3MHz — 144MHz. THE BEST BUY EVER IN SWR/POWER METER. AN INSTRUMENT NOT A TOY \$19.70

2 ONLY. ME-11X TWIN SWR/POWER METER. Frequency range 3.6-150MHz Max: handling power 1.kw. THE CHEAPEST INSTRUMENT AVAILABLE \$16.00

12" Jumper lead fitted with 50ohm plugs \$2.75

PLEASE INCLUDE POSTAGE WITH ALL ORDERS.
TRADE ENQUIRIES WELCOME.


WE ARE SPECIALISTS 30 years in the antenna business.
Hours — 8am to 5pm. Sat: 9am to 12pm.

ELECTROCRAFT PTY. LTD.
68 WHITING ST., ARTARMON 2064
TELEPHONE: 438-3266

RED POINT

Heatsinks

M-TYPE

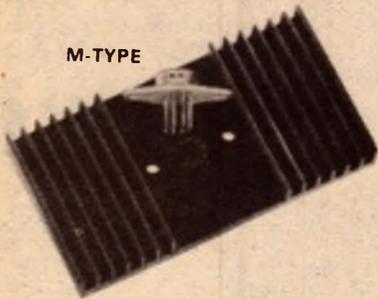


M-Type

For applications including that of printed circuit boards and suitable for external mounting on equipment

Height 0.56" — 14mm
Width 3.69" — 94mm

2M	2" — 51mm
3M	3" — 76mm
4M	4" — 102mm
6M	6" — 152mm

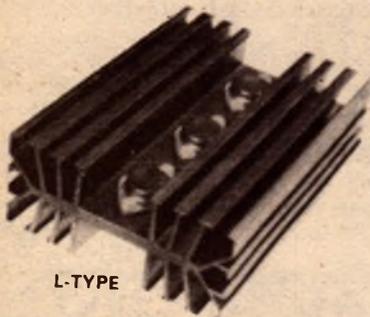

L-TYPE

L-Type

Height 1.97" — 50mm
Width 4.33" — 110mm


2L	2" — 51mm
3L	3" — 76mm
4L	4" — 102mm
6L	6" — 152mm

All D.I.L. packs with 14 pins and most 16 pin packs

DIP 14/8

Size 9 x 28 x 7mm high

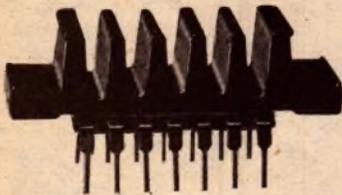Supplied complete with cyanoacrylate adhesive in packs of 50 units



Ex Stock



99 Alexander St, Crows Nest
439 2488

Adelaide 42 6655
Brisbane 277 4311
Canberra 82-3581
80 4654

Newcastle 69 1625
Perth 325 5722
Melbourne 598 9207

Especially for the AUDIOPHILE — continued

difficulty here in coping with a classic-romantic program, with French leanings in a building which, in its interior at least, is rather reminiscent of a segment of a French cathedral:

Tocatta in F-Major, 5th Symphony (Widor) — Meditation from 24 Pieces in Free Style (Vierne) — Final from the First Symphony (Vierne) — Psalm XIX (Marcello) — Claire de Lune (Karg-Elert) — Final Op. 27, No. 7 (Dupre) — Prelude from 24 Pieces in Free Style (Vierne).

The mic. placement is excellent, capturing not only the source sound but the ambience of what is regarded as a particularly appropriate environment for a concert organ.

What is especially noteworthy,

however, is the dynamic range of the recording, from powerful peaks to passages that are so delicate and so remote that you will need a quiet listening room to stay with them. One gets the impression that the team of young men behind this disc — organist, producers and sound engineers — have been keen to emphasise a point. The result is dramatic but it is debateable whether the total dynamic range in a dedicated space like a cathedral or concert hall is appropriate to the practical environment of a domestic listening room.

But arguments aside, this is a fine performance and a dramatic original recording, with clean, noise-free copies produced in Germany.

Birds, animals, homo sapiens — and electronics!

INVESTIGATING MUSIC. A 170-page edited transcript of four ABC radio programs edited by John Merson. Also a cassette containing music illustrations used in the broadcasts. Price for the book \$4.45, for the cassette \$6.45, both including postage from: The Cashier, ABC, GPO Box 487, GPO Sydney 2001



I did not hear this series of four broadcasts myself, but it was reportedly very popular; hence the book and cassette. Anyone who wants to assimilate the information in this form will obviously have to work harder than would be the case when merely listening. However, the important thing is that the information is accessible.

The idea is to read the book, which is set out largely in the form of discussion between panel members, with questions or requests picked out in italics and the responses in normal face. Every here and there are footnotes which suggest resort to the tape to listen to the various sound illustrations.

Wisely, the producers of the tape have included segments of the discussion, such that the tape can be replayed at any time with in-built clues as to what it is all about. The sound excerpts have obviously been collected from a variety of available sources and, besides being in mono, are often indifferent in quality. However, they serve the purpose.

I did not have time to read the book through, but I did read some and scan the rest, while listening to the entire tape.

Contrary to what one might expect, "Investigating Music" is not primarily


concerned with the structure of western music: notes, harmonics, scales, rhythms, etc. It is assumed that the listener is already reasonably conversant with such matters, at least by way of terms and definitions.

The panel — or more correctly, the panels — cover four general aspects: Music, Language and Perception; Social Functions of Music; Music, Class and Culture; Technology and Musical Education.

Under the first heading, considerable attention is paid to the sounds made by birds and animals and their possible connection with the music of man. Section two looks at music in those cultures where it is still closely related to activities, as distinct from whim or entertainment.

Section three investigates the relationship of music and western civilisation and the degree to which each has modified the other. This leads into the fourth and final section which is heavily involved with electronically generated sound. Attention is focussed on the Australian developed "Qasar", which might be described as a computer controlled synthesiser.

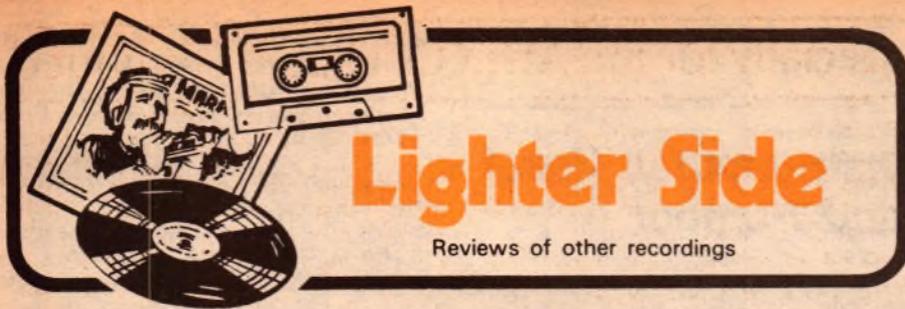As I said earlier, "Investigating Music" is a book/cassette combination that one needs to work at, but the audiophile may well find it an enriching background to his immediate involvement with hifi technology and direct-cut discs or grand pianos and concert organs.



Lighter Side

Reviews of other recordings

Classical organ music from British cathedrals, Kings College

ELGAR: The great First Organ Sonata, and organ music by Bliss, Vaughan Williams, Britten and Malcolm Williamson. Stereo, World Record Club R 04973.

A collection of 20th century organ music by four English composers and "honorary" English composer Malcolm Williamson — born in Sydney. The major work is Elgar's Organ Sonata No. 1 in G major, played by Herbert Sumsion at the organ of Gloucester Cathedral. Bliss is represented by his three Fanfares composed for the wedding of Princess Margaret in 1960; Vaughan Williams by his Three Preludes on Welsh Hymn Tunes; Britten by his Prelude and Fugue on a theme by the Spanish composer Vittoria; and Williamson by his Two Epitaphs for Edith Sitwell.

The organs are all of a high standard, and the organists well known. Christopher Dearnley plays the Bliss fanfares in St. Paul's Cathedral, Robert Joyce the Vaughan Williams preludes in Llandaff Cathedral, Herrick Bunney the Britten prelude and fugue at Edinburgh's St. Giles Cathedral, and Allan Wicks the Williamson epitaphs at Canterbury Cathedral.

Whether or not you enjoy this record will probably depend on the degree to which you can identify with the music. While Elgar is generally not my cup of tea, I found Sumsion's playing of the first sonata gave me new insights into the work, and most enjoyable. Allan Wicks' playing of the Williamson pieces I also found very satisfying, but the other three organists either use a little too heavy registration for my taste or they are not recorded to best advantage.

In short, I would suggest that you listen to this one before making up your mind. (J.R.)

☆ ☆ ☆

ORGAN MUSIC FROM KING'S. Philip Ledger at the organ of King's College, Cambridge. Stereo, World Record Club R 05216.

Philip Ledger was the youngest

Cathedral organist in England when he was appointed to Chelmsford Cathedral in 1961. Since 1974 he has been Director of Music at King's College, where he plays on this recording. The pieces he plays are all well-known and often played, but he brings to them a down-to-earth freshness which makes the recording both interesting and enjoyable.

The first work played is that venerable war-horse, J. S. Bach's Toccata and Fugue in D minor — surely the most often-played and often-badly-

played of all organ works. Yet by skillful registration, sensitive phrasing and careful control of pace, Ledger manages to make it sound remarkably fresh. Quite a contrast against the many "renditions" of this work which sound as if the organist is either worried about missing the last train home, or is solely concerned with demonstrating how fast his fingers can move without leaving his hands!

The remaining pieces are all from the romantic school: a Chorale Prelude by Brahms, Liszt's Prelude and Fugue on B-A-C-H, the second of Vaughan Williams' Three Preludes founded on Welsh Hymn Tunes, Cesar Franck's Choral No. 3 in A minor, Louis Vierne's Berceuse and Widor's "celebrated" Toccata from his Symphony No. 5. In all of them Ledger displays the same skill and sensitivity. The registrations seem just right, and the tempi chosen with great care to bring out the best from each movement.

The recording is of a high standard, too, giving a most satisfying reproduction of the historic King's instrument — parts of which date from 1605.

All in all, then, a most interesting and enjoyable recording of familiar organ works played uncommonly well. (J.R.)

New Devotional Records

GARY S. PAXTON. Terminally Weird But Goodly Right. Stereo, Pax R-2406. (Fram Sacred Productions Australia, 18-26 Canterbury Rd, Heathmont, Vic 3135)

In his own jacket notes, Gary Paxton says that he anticipates that the style of this album will alienate many traditional Christians but, while he regrets this, his prime aim is to communicate with those who, in turn, are alienated by traditional Christian music.

The sound varies from rock, through gimmicked C&W to a soul version of "Blessed Assurance"; Certainly well removed from normal devotional music. Yet the words, set out in full in the double fold jacket, pull no punches in challenging materialistic values:

I'm Anchored In The Rock Of Ages — Lord How'd I Get So Old So Fast? — Mental Pollution — Ode To The Outlaw (That Prison Called Freedom) — Can't See Me Serving Nobody But Jesus — Will There Be Hippies In Heaven? — Blessed Assurance — Progress (Fun Loving Progress) — Fat, Fat Christians — The Clone Affair — The Big A, The Big M.

If your preference is for comfortable, familiar devotional melodies, this is not for you. But if you're prepared to listen to and consider a multi-pronged



challenge to you and your stereotyped group listen to what Gary Paxton has to say! (W.N.W.)

☆ ☆ ☆

COMMUNION — A singalong for God's people in harmony. Stereo, Birdwing BWR-2009. Released in Australia through Spotlight Music Pty Ltd, 262 Pitt St, Sydney 2000).

For decades, chorus singalongs have been a prominent feature of Gospel rallies — originally catchy choruses of actual hymns but, more recently, with an increasing content of new compositions. In fact, they can be as much a problem to keep up with as pop songs!

For example, although there are over 40 excerpts and choruses on the four sides of this singalong medley, the chances are that you won't recognise any or many of them. You needn't worry, however. They follow the usual pattern of being tuneful and varied and the diction is excellent. So also is the quality of the sound off the disc.

They are presented in close harmony by a vocal group, with instrumental

THE LIGHTER SIDE — continued



backing including piano, organ, drums and synthesiser. You can let the group-singalong for you in a quiet, relaxed manner, or turn the volume up and enjoy it that way — or join right in with them!

The disc could suggest new material for your own group singalong activities and, in this connection, a label on the jacket suggests that a book of music and lyrics is available. There is also mention of an open-reel tape and two cassettes which carry the musical accompaniment only. (W.N.W.)

For information on World Record Club albums, contact the club at 605 Camberwell Road, Hartwell, Victoria, 3124. Tel. 29 3636.

Instrumental, Vocal and Humour

THE JAZZ SOUND OF THE DON BURROWS QUARTET. World Record Club stereo WRC RO5193.

I have an original copy of this album some 14 years old which is one of my firm favourites. (Originally it was released on Columbia.) The re-release with WRC is every bit as good and can still be classed as a first class recording. Surface noise is low.

There are nine tracks: Kaffir Song — Love Is For The Very Young — Esa Cara — Slightly Blue — Hard Sock — Rain On Water — De Veras? — Algeciras — Pink Gin. (L.D.S.)

☆ ☆ ☆

SONGS FOR SWINGIN' SELLERS. World Record Club stereo WRC R 05229.

Fans of Peter Sellers, who might be thought of as a Goon who grew older, will be keen to listen to this album. As can be expected of Peter Sellers it is unmitigated nonsense, which is all very clever. Unfortunately, none of it struck me as being particularly funny. Perhaps I should have reviewed it while semi-intoxicated! (L.D.S.)


SHOWBOAT. Music by Jerome Kern, lyrics by Oscar Hammerstein II. Cast recording from the Adelphi Theatre, London. Stereo, World Record Club RO-5022.

Although this recording reached me through the World Record Club catalog, the pressing and jacket appear to be as originally distributed by Columbia. As such, they probably date back to the 1971 era, when the particular show opened in London. It featured Andre Jobin, Cleo Laine, Thomas Carey, Kenneth Nelson and Derek Royle.

The show was acclaimed at the time for its sheer spectacle and the album will be most meaningful to those who have seen this or another production. To those who haven't, the album will have to stand or fall by the numbers which, together, add up to a generous recording time of nearly 50 minutes: Cotton Blossom — Where's The Mate For Me? — Make Believe — Can't Help Lovin' Dat Man — I Might Fall Back On You — Ol' Man River — Queenie's Ballyhoo — At The Fair — Nobody Else But Me — How'd You Like To Spoon With Me? — You Are Love — Bill — Dance Away The Night — Why Do I Love You? — Ol' Man River.


It's a typical cast recording, not perfect but carrying the atmosphere of the stage production. The recording quality is normal and, if you like the music, this will be an opportunity to enjoy it all over again. (W.N.W.)

CASH-MORE ENTERPRISES

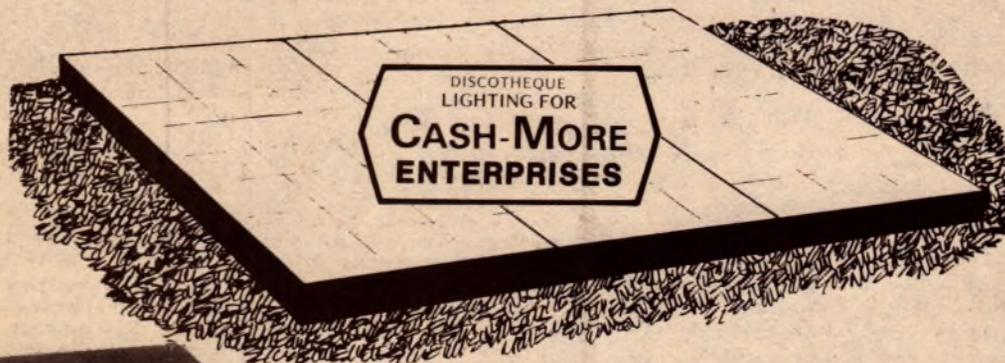

SAC 4 CHASER
4 x 1K OUTPUT
WILL RUN
8-8' x 4' x 6"
MODULES

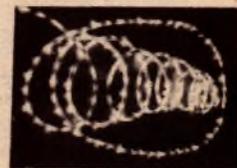ILLUMINATED DANCE FLOORS WHITE ACRYLIC PLEXIGLASS 8' x 4' x 6" MODULAR
ALL SIZES MANUFACTURED TO REQUIREMENTS



ROPELIGHTS
32ft, 4 COLOURS

CASH-MORE ENTERPRISES IMPORTERS, RETAILERS, HIRERS, MANUFACTURERS OF QUALITY SOUND. DISCOTHEQUE + EFFECTS LIGHTING. MIRROR BALLS, STROBES, PROJECTORS, SOUND TO LIGHT CHASERS — AMPLIFIERS — SPEAKERS MICS. ETC.

356 LIVERPOOL RD, ASHFIELD, NSW 2131.

TEL: SYD 798 6782, 798 5647

OPEN SUNDAYS BY APPOINTMENT,
BROCHURES — PRICE LIST BY REQUEST

EDWARD WOODWARD, The Thought Of You. Festival L 36717.

I like Edward Woodward better as a singer of ballads than as the rather unpleasant "Callan" of the TV series.

On this disc he gives us a dozen superbly sung tracks: Can't Smile Without You — Time In A Bottle — You Are Beautiful — The Folks Who Live On The Hill — Smile — The Party's Over — I'm Old Fashioned — Growing Older Feeling Younger — I've Told Every Little Star — Love Look At Us Now — The Very Thought Of You — Evergreen. The backing is provided by an orchestra under the direction of Johnny Arthey.

Quite a few of the tracks have had a fair amount of air-play recently. (NJM)

BEHIND THE SMILE. Marti Caine. Astor Records SPLP1541.

English Marti Caine gained her big show business break on ATV's "New Faces" when her hesitant brand of humour, combined with some fine singing, took her into the winner's league and a triumphant debut at the MGM Grand Hotel in Las Vegas.

Since her success on "New Faces" Marti has had her own series for ATV and a series for BBC television.

"Behind The Smile" is a brilliant "easy-listening" album with some excellent interpretations of recent hit singles: Prelude — Nobody Does It Better — You — A Weekend In New England — Feelin' Single, Seein' Double — I Honestly Love You — Sometimes When We Touch — I've Never Been To Me — If It's Magic — What's The Weather Like Outside — Sweet Music Man — All In Love Is Fair — Lullaby For Myself. (D.H.)

15 THOUGHTS OF BRINSLEY SCHWARZ. Brinsley Schwarz. United Artists L 36713. Festival release.

The 15 songs on this album are taken from various albums through the years 1970-1975, the time span that this British Rock Band stayed together before going their own way.

The collection of songs on this album are: Peace, Love And Understanding — There's A Cloud In My Heart — Nightingale — Hypocrik Funk — Angel — I Like You, I Don't Like You — Rockin' Chair — Shining Brightly — Country Girl — Surrender To The Rhythm — Hooked On The Road — Home In My Hand.

This is an excellent album with a variety of style: country, soul, reggae, rhythm & blues and pop. (D.H.)

UNCLE HARRY LIVES AGAIN

TALES OF MY UNCLE HARRY. Keith Garvey. Dolby System cassette. Also available on LP disc. (\$3.95, \$4.40 posted from: The Cashier, ABC, GPO Box 487, Sydney 2001).

Keith Garvey, as introduced in the cassette folder, is a true son of the Australian outback and a keen admirer of Henry Lawson. For a couple of years he has featured on the ABC radio network and many will be familiar with his series of "Tales of my Uncle Harry". If you are, and you want a sampling of them, this cassette contains about 16, all told.

On the other hand, if you have merely noticed the item in the programs, without ever having listened, what are you going to hear on this cassette? A half-hour of side-splitting humour? Not unless you're in a particularly receptive mood! Playing a tape like this alone in your lounge room is about as sterile an experience as reading one of those old-fashioned books of jokes. Somehow, you need environment and atmosphere to bring them alive.


Having some first-hand knowledge of the country, it is sufficient for me to say that, while Uncle Harry was a past master of the tall tale, the setting of those tales is in tune with the outback as it used to be. The rest is up to you and your mood. (W.N.W.)



Digital Wind Speed and Direction Indicator



KIT ID-1590E—\$125.50

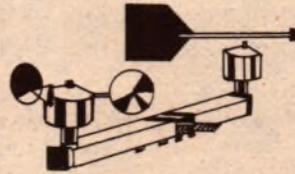

ID-1590E SPECIFICATIONS: Wind Speed: 0-99 in miles per hour, knots or kilometres per hour (choice of two). Response Threshold: 3 mph Accuracy ± 1 digit or ± 10%, whichever is greater. Direction Response Threshold: approx 2 mph. Power Requirement: 240V AC, 50 Hz.

Outstanding accuracy and easy-to-read digital display make this kit a "must" for pilots, boaters—anyone whose activities are affected by the wind. Pick the two readout modes you want from the three available: miles or kilometres per hour, or knots. Switches select mode and front-panel lights show which is in use. Incandescent bulbs mark the 8 principal compass points, providing 16-point resolution. The transmitter boom clamps on to any 1" to 1½" TV aerial mast and connects to the receiver with optional cable.

Digital Indoor / Outdoor Thermometer



KIT ID-1390AE—\$103.50

You'll never have to "gauge-guess" again! This fun-to-build kit monitors indoor / outdoor (or any two temperatures) with a big, bright, ½" high digital readout. The readout includes plus and minus signs as well as indoor and outdoor indicator lights, so you know at a glance which temperature is being monitored. Switches select Fahrenheit or Celsius and let you choose continuous readings of one temperature or alternate readings of both. The 85' of cable included lets you place the temperature sensors just about anywhere for a variety of custom applications—home freezer, hot house, garage, basement, pump house, swimming pool, aquarium, almost any temperature.

ID-1390AE SPECIFICATIONS: Temperature Range: Fahrenheit -40 to +120°. Celsius -40 to +50°. Power Requirement: 240V AC, 50 Hz.

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$..... is enclosed plus \$7.00 for package and post.

Name.....
Address.....
P/code.....

KIT ID-1590E plus one of either:
 IDA-1290-1, 50' Cable—\$16.00
 IDA-1290-2, 100' Cable—\$28.00
 & choose two of: m.p.h.
 k.p.h.
 knots

KIT ID-1390AE

Send to: WF Heathkit Centre
220 Park St, South Melb. 3205. Phone 699-4999.

WF 586/77

AMATEUR RADIO



by Pierce Healy, VK2APQ

Sydney hosts WARC 79 preparatory seminar — special report by Pierce Healy

As a lead-up to WARC 79 — and second only in importance to the conference itself — there have been three preparatory seminars organised by the ITU; one each in Nairobi, Panama, and Sydney. Your correspondent was privileged to attend the Sydney seminar, and reports some highlights of the formal and informal sessions.

WARC 79, which will commence in Geneva Switzerland in September is expected to have 1600 participants from the ITU's 154 members and will last for ten weeks. The agreements reached regarding the radio regulations will apply for the remainder of this century.

The ITU (International Telecommunications Union) organised the preparatory seminars to familiarise the delegates — many of whom will be attending their first radio conference — with the procedures and requirements involved in bringing up-to-date the 1959 regulations. The Sydney seminar hosted 170 representatives from 37 countries.

Being allowed to observe these preparations in progress was a most rewarding experience, and also a most enlightening one. In particular it brought home the sheer magnitude of the task ahead and, in doing so, emphasised that the Amateur Service is, after all, only a tiny part of the total communications scene to be dealt with.

The magnitude of the task was emphasised particularly by some of the documents circulated at the Sydney seminar. One was a report of the CCIR Special Preparatory Meeting held in Geneva during October and November 1978. It consists of over 600 A4 (295mm x 210mm) pages, in reduced typewriter font, and weighing nearly 1.2kg (over 2½lbs).

Its contents range from broadcast band allocations to satellite TV relays; from standard frequency transmissions to analogue and digital transmissions in the GHz bands; from terms and definitions to allocations for power transmission (in GW) by radio waves from solar satellites.

And this was only a preparatory meeting.

In addition, there was similar order of documents generated by the Sydney seminar, mainly in the form of papers

by various delegates. One document alone — A Summary of Discussions (Questions and Answers) — ran to some 60 odd A4 typewritten pages.

The initial session of the seminar was presided over by the Deputy Secretary General ITU, Mr Richard Butler, who welcomed delegates and called for nominations for seminar chairman. Mr E. J. Wilkinson, First Secretary, Radio, Frequency Management, P & T Dept., Australia, was elected to this position.

At the official opening, the seminar was addressed by Mr M. Mili, Secretary General ITU, who referred to WARC 79 and the task it was to perform, and to the technical progress and evolution in the countries themselves since 1959 when there were 96 members of ITU.

Mr A.A. Staley, Minister of Post and Telecommunications in Australia, officially opened the seminar, welcoming the delegates and referring

to Australia's involvement in ITU since 1878 and the emphasis Australia places on the subjects to be discussed at the seminar and the keen desire that WARC 79 should be a success.

Thirty-five papers covering many and varying aspects of radio communication were read and discussed by delegates. These included topics of regional interest, terrestrial and space services and technical advances leading to a more efficient use of the radio frequency spectrum.

The amateur service was represented on the Australian delegation by David Wardlaw, VK3ADW and Michael Owen VK3KI.

A number of delegates from the countries represented, and serving in various capacities, were also amateurs, as were some of the seminar staff personnel.

Apart from formal discussions, the seminar provided an opportunity for a good deal of informal discussion between various countries and services. Naturally the amateur service made most of its opportunities.

A social function for the delegates, hosted by the Wireless Institute of



Physics master at the Burra Community School, Wally Spehr, VK5PD, at the microphone during the contact with VK2BOK. The transceiver is a Kenwood 820 operating into a parasol beam lashed to a playground swing. (Story, p 111.)



a decade of research in HF transceivers brings you the FT-101Z series. Price..FT-101Z \$779. FT-101ZD \$929.

Today's technology, backed by a proud tradition, is yours to enjoy in the all-new FT-101Z (and FT-101ZD) high-performance HF transceiver from YAESU and BAIL. A host of new features are teamed with the FT-101 heritage to bring top dollar value.



Photo shows FT-101ZD transceiver with Digital display. FT-101Z Analog Model (without digital display) available at \$799 and you add the optional extras if desired. (Accepts 901 series acc. e.g. multiscopes, transverter, ant. cplr., etc.)

Rcvr includes variable IF bandwidth with two 8-pole crystal filters and a highly effective all-new NB circuit with front panel blanking level control. Also included are 10 and 20 dB attenuators, and offset tuning for transmit and receive. Trans. section uses two 6146 final tubes with RF neg. feedback. An RF speech processor is built in. Available options include DC-DC converter, cooling fan, dig. display/counter unit (for FT 101Z), hand or desk mic, and CW filter. CW filter may be used in addition to SSB filter in CW mode. Write for our full colour brochure today.

Prices quoted are recommended retail and include 90-day warranty except power valves and semi-conductors. As the authorised Yaesu agent and factory representative since 1963, we provide complete after sales service and spares.

JAS7879-38



Bail Electronic Services, 60 Shannon St., Box Hill Nth, Vic. 3129. Tel. (03) 89 2213
Branches in all States and A.C.T.

FRED BAIL VK3YS
JIM BAIL VK3ABA



HF Mobile FT-7B ... power and performance for the Ham on the move

FT-7B SSB, CW, AM all solid state compact transceiver from Yaesu, 80-10m, 100W peak input.

With all the features of the FT-7, inc. noise blanker, cal., clarifier, semi-break-in CW with sidetone, etc., plus many more:- provision for Digital readout, full coverage on 10M. A.M., Audio peak filter for sharp selectivity and improved S/N ratio on CW, Drive Control, RF attenuator. Sensible

compact shape (W230 x H80 x D320 mm inc. heat sink) so that it easily fits into most modern cars. Handy tilt-up foot for desk use. **FT-7B** price, inc. 28.5-29 crystal, mobile bracket, mic., power cable, English inst. book, connectors, and Bail 90 day warranty, **\$629.**

Options, **YC-7B** ext. dig R.O. can be mounted on dash or steering column for convenient and safe viewing, includes adjustable sunshade, **\$125.** Extra 10M range crystals **\$12** each.

Prices & specs subject to change. All prices inc. S.T. Freight & ins. extra.



Bail Electronic Services, 60 Shannon St., Box Hill Nth, Vic. 3129. Tel. (03) 89 2213
Branches in all States and A.C.T.

Fred Bail VK3YS — Jim Bail VK3ABA

JAS7879 — 35

**TR DIP
METER**



**\$89
SCOOP !**

SCOOP PURCHASE! NORMALLY \$132
Freq Range: 1.5 to 250 MHz in 6 ranges
IDEAL FOR RAPIDLY CHECKING CIR-
CITS AND COMPONENTS IN RECEIVERS,
TRANSMITTERS AND FOR ANTENNA
TUNING.


**PROGRAMMABLE!
VHF-UHF
SCANNING RECEIVER**



**BEARCAT 210 10 CHANNELS
BEARCAT 250 50 CHANNELS**


**12 CHANNEL POCKET
VHF RECEIVER
XTAL LOCKED**

**NICADS,
CHARGER
SUPPLIED
AS
STANDARD**

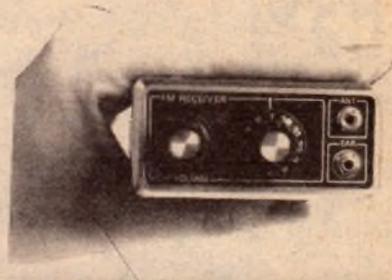


McKay Dymek

Your HF Headquarters

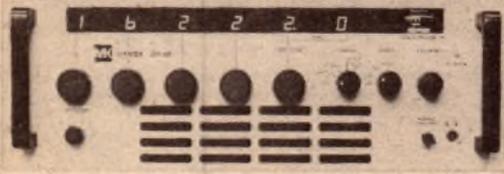

50kHz — 29.7MHz continuous

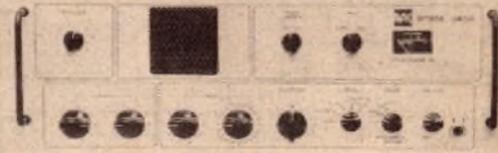

AM SSB CW RTTY

AIRCRAFT RECEIVER



- SCAN OR MANUAL
- 16 CHANNELS
- AC/DC OPERATION (BUILT-IN AC SUPPLY)
- 4 CRYSTALS SUPPLIED
- IDEAL FOR CLUBS, SCHOOLS.



\$199

The VICOM 747 Scanning Receiver is a high quality solid-state monitor designed for the private pilot or flying club to watch the aircraft band frequencies. This compact-sized and rugged construction receiver offers many features over other aircraft receivers. Price \$199 + P&P.

JK01	General purpose audio amp 0.5N	18.00
JK02	Microphone amplifier	19.00
JK03	Sine wave generator 20-20,000 Hz	30.00
JK04	FM Tuner 88-108 MHz	30.00
JK05	27 MHz receiver	33.00
JK06	27 MHz transmitter	29.00
JK08	Light operated relay	20.00
JK09	Siren Kit including speaker	19.00
JK10	Photographic timer	23.00
JK101	Car burglar alarm	55.00
AT465	2 channel lught show	64.00
AT468	4 channel light show	75.00
HF61	Medium wave receiver	19.00
AF300	Audio amplifier 3 watts	25.00
AF340	Audio amplifier 40 watts	35.00
AF380	Audio amplifier 2 watts	14.00
HF395	RF pre-amp 1-225 MHz	6.00
HF385	VHF/UHF receiver pre-amp	30.00
NT300	Lab. power supply 2-30V	110.00
AT347	Electronic Roulette	54.00
AT320	Alt Round AC/DC Regulator	54.00
HF305	Converter 175-105 MHz to 105 MHz	28.00

NEW KITS



FM TRANSMITTER 60-148MHz (model HF65) will run 5w output with a heat sink. Ideal for signal testing or a miniature transmitter which could be received on a standard FM Receiver. \$9 plus \$1 P&P for mail order.

QUALITY FM TUNER. A high quality kit with good sensitivity and low distortion. With this kit all coil-winding is already done for you.
 KIT HF325-2 \$79.00
 KIT HF310 \$49.00 (economy kit)
 STEREO DECODER KIT \$24.00 (model HF330)

COMPLETE WITH COMPREHENSIVE INSTRUCTION BOOKS.
\$1 P&P FOR ALL MAIL ORDER PLEASE!



AMATEUR RADIO DIVISION
 68 Eastern Road
 SOUTH MELBOURNE VIC 3205
 PH (03) 699.6700 Telex AA30566

Sydney	681 3544	Hobart	43 6337
Adelaide	43 7981	Cairns	54 1035
Gold Coast	32 2644	Launceston	44 3882
Canberra	31 6685	Brisbane	38 4480
Melbourne	836 8635	Wellington (N.Z.)	287 946
Perth	321 3047		

AMATEUR RADIO

Australia and the International Amateur Radio Union was held on Saturday evening 31st March.

Apart from generalities, one of the main talking points was the IARU simple low cost direct conversion receiver. A short continuous video tape explaining the amateur radio service was also available for delegates to view at their leisure. Both items created considerable interest.

Away from the seminar environment, several members of the Sydney Chapter Quarter Century Wireless Association were hosts to Richard Butler and Michael Owen, VK3KI, for dinner. The informal discussion on the amateur service and WARC 79 which followed, made the evening a very informative and enjoyable one.

There is no doubt that both the formal and informal discussions helped all the delegates to form a broader view of the problem of equitably sharing the radio frequency spectrum between all services — including the Amateur Service — and all countries. It also emphasised to the amateurs that their allocations are only a very minute portion of the spectrum and only one of a great many subjects on the agenda for WARC 79.

It is ironical in some respects that amateur radio, having been so closely associated in the progress of radio science and communication, finds itself in the situation of having to fight to maintain recognition.

It may be significant however that there was no objection or criticism of the amateur service at the seminar.

Indeed it is thought that many administrations are now, through the unified work of the IARU, more appreciative of the value a responsible amateur service could be. But there is still no room for complacency about WARC 79 decisions.

All amateurs should give their support to their national amateur radio society.

Finally, I would express my appreciation to all associated with the seminar, in particular Mr Richard Butler for his friendly interest and willingness to discuss my inquiries.

SCHOOL DEMONSTRATION

An amateur radio demonstration was given on 5th April 1978 at the Ingleburn High School. The occasion was the "Careers Market Day" held to give final year students first hand information about careers in various trades and professions.

More than 50 information booths and displays were staffed by representatives from manufacturing, banking, legal, health, further

Amateur radio at the Ingleburn High School "Careers Day". Shown holding the microphone is Marcia Robinson, an exchange student from Nebraska, USA, who was able to talk to an amateur in her own country. (See story, this page.)



education, Army, Navy, RAAF, catering, and communication organisations.

Over 2500 boys and girls from schools and colleges in adjacent areas visited the centre.

Amateur radio was demonstrated as a means of gaining knowledge and experience in electronics and communication either as a rewarding hobby or to assist a career in the radio or electronics industry.

Several overseas contacts were made during the day, giving those interested the opportunity to ask questions of the operators and their country. A highlight was Japanese language lessons, given by student operators in Japan.

Many students, whose experience in radio communication was limited to CB activity, were amazed at the courteous and friendly manner among amateurs in various parts of the world, and expressed their desire to upgrade to AOC standard.

The station operators were Pierce Healy, VK2APQ and Athol Tilley, VK2BAD.

This type of public relations activity is recommended as an enjoyable and

rewarding community service.

WIA NEWS

WIA president and amateur representative on the Australian delegation to WARC 79, David Wardlaw VK3ADW, has advised that the Australian submission relating to amateur allocations within Australia recommends that all existing channels be retained in their entirety. In addition, a segment 6.95MHz to 7MHz and small segments around 10MHz, 18MHz and 24MHz have been suggested.

FINANCIAL SUPPORT: The response to the appeal for donations to send the WIA observer to WARC 79 has been very good. Many non-members of the WIA and business organisations have contributed. The outstanding contributions — Eastern and Mountain District Radio Club \$1100; VICOM \$1000; Bail Electronics \$500; Dick Smith Electronics \$500.

These donations together with divisional contributions are acknowledged and will be tabulated in a future issue of the WIA magazine "Amateur Radio".

NSW DIVISION: A special general

RADCOM QUALITY COMPONENT

105 ELDRIDGE ST., BANKSTOWN
PHONE: 709-4706

Air spaced variable capacitors

10pF-25pF-50pF-100pF
250pF ALL AT \$2.50
500pF at \$5.00

All preferred values of capacitors

All preferred values of resistors

PLUGS CONNECTORS AND ACCESSORIES IN STOCK

High voltage fixed capacitors, all types of toggle and wafer switches.

Multi-tapped transformers

0-15v 1 AMP \$5.00
0-15v 2 AMP \$9.30


TRY US FOR THE HARD TO GET COMPONENTS

STOCKIST FOR

silicon valley

THE WAR CONTINUES

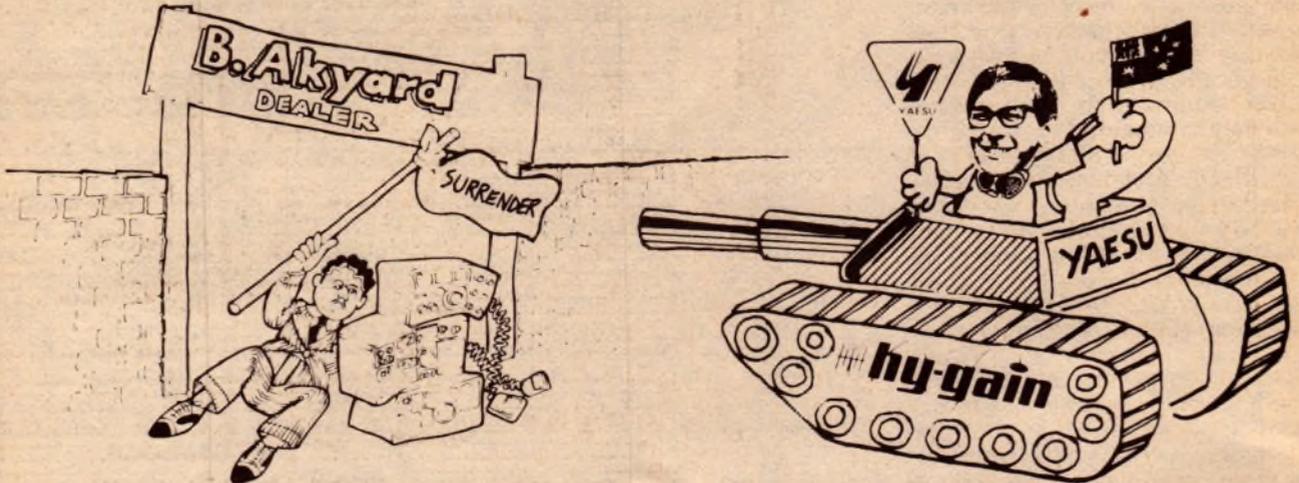THE BATTLE STILL RAGES WITH YAESU — NOW HY-GAIN ANTENNAS HAVE FALLEN TOO!



You must have heard about the Yaesu price war — Dick Smith will better any genuine price offered by anyone on Yaesu products . . . We've received such a tremendous response from the Amateurs of Australia that we've decided to reduce the price of Hy-gain HF antennas. So now you can buy your complete amateur station from Dick at a real bargain price.

YOU REAP THE BENEFIT!

And you'll be buying from a fully Australian owned company — your one stop electronics shop who actively supports amateur radio!

HERE ARE OUR YAESU PRICES:

(and we'll send them anywhere in Australia for just \$6.00 extra — We even lose money on this 'below cost' freight offer!)

FT-101E 80-10m HF transceiver	Cat D-2860	\$789.00	FT-101Z New HF transceiver	Cat D-2862	\$775.00
FT-301 Solid State HF transceiver	Cat D-2870	\$795.00	FT-901D Top class HF transceiver	Cat D-2854	\$1349.00
FT-7 Mobile HF transceiver	Cat D-2866	\$375.00	FT-227RA 2m FM scanning transc.	Cat D-2891	\$379.00
FT-227 2m FM transc with memory	Cat D-2890	\$379.00	CPU-2500 computerised 2m transc.	Cat D-2889	\$549.00
FC-301 Antenna tuning unit	Cat D-2896	\$219.00	FC-901 antenna tuning unit	Cat. D-2855	\$249.00
FL-2100B 1.2kW linear amplifier	Cat D-2546	\$529.00	FL-110 200W linear amplifier	Cat D-2884	\$189.00
FRG-7 Solid State HF Rcvr	Cat D-2850	\$319.00	FRG-7000 Digital HF rcvr	Cat D-2848	\$599.00
FP-301 13 8V/20A supply	Cat D-2872	\$169.00	YC-500S 500MHz Freq Counter	Cat D-2892	\$475.00

We believe that the prices above are better than any supplier in Australia. If you find someone cheaper for the same goods, tell us! For us to better any price, simply show us the advertisement from any Australian company. After checking that they have stocks available at that price we will sell it for a lower price. Offer remains open while present stocks last (approx. \$250,000 worth).

Easy terms available to approved personal applicants on any item priced at \$111.00 or more.

NEW HY-GAIN HF ANTENNA PRICES:

SUPER SPECIAL:

TH6 DXS SLASHED BY \$104.00 TO ONLY

\$295.00

Cat D-4308

WHILE STOCKS LAST

TH3Mk3 BEAM:

Save \$50.00 . . .

\$249.00

Cat D-4306

TH3JR BEAM:

\$20.50 off!

\$199.00

Cat D-4304

18AVT VERTICAL

SAVE \$14.50

\$135.00

Cat D-4302

HY-GAIN VHF ANTENNAS ALSO IN STOCK. ASK OUR PRICE!

IONOSPHERIC PREDICTIONS FOR JUNE

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open. 6.79

meeting called to discuss the proposed sale of Wireless Institute Centre, Crows Nest, and the constitution of the Division, was held on the 23rd March, 1979. The meeting resolved that the incoming council appoint a committee to review the future requirements of the division and the options relating to the sale of the Crows Nest property.

A committee was also appointed to review the constitution and to report its recommendations to a general meeting of the division. This committee consists of Pierce Healy, VK2APQ chairman; Harry Caldecott, VK2DA; Barry White, VK2AAB; Tim Mills, VK2ZTM; Chris Jones, VK2ZDD.

The committee will review the constitution, bearing in mind the views expressed by members on such aspects as the powers of the council, club affiliation, voting rights of members, and proxy votes.

Members wishing to offer suggestions and opinions should do so in writing to the Constitution Review Committee, 14 Atchison Street, Crows Nest 2065.

COUNCIL ELECTIONS: There were only seven nominations received and no ballot was necessary. The nominees were — Phil Card, VK2ZBK; Henry Lundell, VK2ZHE; Ian Mackenzie, VK2ZIM; Tim Mills, VK2ZTM; Fred Parker, VK2NFF; Steven Paul, VK2VHP and Eric Van De Weyer, VK2ZUR. At their first meeting, Fred Parker, VK2NFF was elected president; Phil Card, VK2ZBK and Ian Mackenzie, VK2ZIM vice presidents; Tim Mills, VK2ZTM secretary.

ACT DIVISION: Office bearers elected at the annual meeting held in February, 1979, were: president — Andrew Davis, VK1DA; vice-presidents — Mike Vale, VK1VW and Ron Henderson, VK1RH; secretary — Fred Robertson-Mudie, VK1NAV; treasurer — John Roberts, VK1ZAR; committee members — John Tilley, VK1FT; Bob Chorley, VK1RC and Les Thurbon, VK1NBK.

Meetings are held on the fourth Monday of each month commencing at 7.30 pm at "The Studio" Griffin Centre, Civic, ACT. Visitors are welcome.

SYDNEY SCIENCE MUSEUM OPENING CEREMONY

Unfortunately, printing schedules for the May issue limited our report on the above to a photograph and brief comment. A highlight of the ceremony resulted from the first official "CQ"

14MHz EAST	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR)																							
JOHANNESBURG																							
McMURDO SOUND																							
NEW DELHI																							
NEW YORK																							
RIO DE JANEIRO																							
TOKYO																							
VANCOUVER																							
WELLINGTON																							
WEST AFRICA																							
WEST EUROPE (SR)																							
WEST EUROPE (LR)																							
ADELAIDE TO SYDNEY																							
BRISBANE TO MELBOURNE																							
PERTH																							
SYDNEY																							
DARWIN TO SYDNEY																							
MELBOURNE TO PERTH																							
SYDNEY																							
21MHz GMT	15	16	17	18	19	20	21	22	23	24	01	02	03	04	05	06	07	08	09	10	11	12	13
EAST AUST TO BARBADOS (SR)																							
JOHANNESBURG																							
McMURDO SOUND																							
NEW DELHI																							
NEW YORK																							
RIO DE JANEIRO																							
TOKYO																							
VANCOUVER																							
WELLINGTON																							
WEST AFRICA																							
WEST EUROPE (SR)																							
WEST EUROPE (LR)																							
ADELAIDE TO SYDNEY																							
BRISBANE TO MELBOURNE																							
PERTH																							
SYDNEY																							
DARWIN TO SYDNEY																							
MELBOURNE TO PERTH																							
SYDNEY																							
28MHz EAST	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR)																							
JOHANNESBURG																							
McMURDO SOUND																							
NEW DELHI																							
NEW YORK																							
RIO DE JANEIRO																							
TOKYO																							
VANCOUVER																							
WELLINGTON																							
WEST AFRICA																							
WEST EUROPE (SR)																							
WEST EUROPE (LR)																							
ADELAIDE TO SYDNEY																							
BRISBANE TO MELBOURNE																							
PERTH																							
SYDNEY																							
DARWIN TO SYDNEY																							
MELBOURNE TO PERTH																							
SYDNEY																							

which, quite unsheduled, brought a reply from the Burra Community School, Burra, South Australia, who had set up an amateur station display as part of a school gala day. A letter confirming the contact was received from the physics teacher, Wally Spehr, VK5PD.

"I would like to thank you for such an interesting contact on Friday 23rd March during the opening of the Applied Arts and Science Museum Station, VK2BOK. We were very pleased to be the first station to officially contact the Museum station and to be able to speak with the Federal P&T Minister, Mr Peter Staley.

"The contact certainly gave a boost to our Amateur Radio Display which had been set up as part of the school Gala Day. Those present were impressed with the learning opportunities provided by amateur radio, and the Museum contact really highlighted this. Our principal, Chris McCabe, enjoyed the opportunity to speak with the Museum education officer and to tell him about the Burra Community School and the local district.

"I use my own gear in a portable capacity and transmit from the school's

science laboratory using a parasol beam constructed by the students.

"Our group is run on an informal basis and meets on the first and third Wednesday of each month from 12.50 to 1.20pm CST. We operate... close to 28.560MHz and 14.210MHz and welcome contacts with other stations, particularly other school groups. We have found such contacts to be very educational.

"A few students have expressed an interest in gaining a novice licence and it is hoped that their ambition can be realised.

"Finally, I hope that all goes well with station VK2BOK and look forward to visiting it in the future."

SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to
**THE COURSE SUPERVISOR,
W.I.A.**

14 ATCHISON STREET,
CROWS NEST, NSW 2065

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

SHORTWAVE SCENE



by Arthur Cushen, MBE

Sunspots Force The Use Of Higher Frequencies

With the Sunspot count expected to reach 150 next month, international broadcasters are using the 11 and 13-metre bands in an attempt to provide world-wide coverage. One problem facing broadcasters is that many listeners have receivers which do not cover these two bands.

Due to the increasing Sunspot count, most broadcasters are now using the 13-metre band for an international service, while the 11-metre band is being used for the first time by several countries.

The highest frequency previously used by a broadcasting station was 26150kHz by W4XB Nashville, Tennessee in 1939. This has now been surpassed by the Israel Radio with its use of 29705kHz from 0535-0600 and 1000-1030GMT.

Two new countries recently extended their operation into the 11-metre band. Radio France International is now using the additional frequency of 25820kHz from 1000GMT with a broadcast from Paris, while Radio Nederland is using 25650kHz from its Madagascar transmitter for a broadcast in Dutch 0730-0825GMT. In addition, Israel which uses 25605kHz at 0535GMT, has used this frequency for additional programs in recent weeks. The United States is using five frequencies in the 11-metre band both for the Voice of America and Armed Forces radio programs.

The Armed Forces signal is very good from 2100-0400GMT over the Dixon transmitter on 25620kHz, while the Voice of America at 2200GMT is well received on 25990 and 25096kHz.

Radio South Africa continues to use the 11-metre band and has been noted opening at 1100GMT on 25790kHz. The same program is carried on 21535, and both transmitters are beamed to Central Africa and Europe.

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT. Add 8 hours for WAST, 10 hours for EAST and 12 hours for NZT.



Fritz Greveling, the new compere of DX Juke Box on Radio Nederland.

NEW JUKE BOX COMPERE

Fritz Greveling is the new compere of Radio Nederland's DX Juke Box program. Fritz replaces Dick Speekman who is returning to Australia after being with the program for 4½ years.

Fritz was born on October 10, 1947 and his early radio career was with Lourenco Marques Radio in Mozambique. Later the station changed its name to Radio Five and moved to Johannesburg, South Africa after Mozambique became independent. He later did freelance broadcasting for Swazi Music Radio, working in their recording studios in Johannesburg. He returned to his native Holland in 1976 where he joined the staff of Radio Nederland as a translator and later as host of DX Juke Box.

DX Juke Box is broadcast every Thursday from Radio Nederland studios in Hilversum, Holland and is well received through the relay station at Bonaire in the Caribbean. The program of 30 minutes includes a weekly DX report and DX Juke Box is broadcast at 0750GMT on 9715 and

9770kHz, and repeated at 0850GMT on 9715kHz. There are other transmissions for various parts of the world both from the relay bases at Bonaire and Madagascar, as well as a transmitter at Lopik in Holland.

The DX information comes from four contributors, The first Thursday of each month features Arthur Cushen's Pacific DX report; Jan Turner reports from Sweden on the second Thursday; Glen Hauser from North America on the third Thursday; and Victor Goonetilleke from South East Asia on the fourth Thursday. The first Thursday of the month also includes a propagation report from Maarten Ven Delft, while on the third Thursday there is a handicap aid program from Fritz Mulder.

TESTS FROM BRAZIL

Radio Nacional at Brasilia operated an International Service for several months but this was closed last year with the transmitter being used for an internal service. In recent weeks the station, now using the slogan Radio Bras, has been heard on 15280kHz with English 0200-0300GMT. This is a test transmission and, according to the announcement, will be on the air for 90 days. Depending on the interest in the new program a permanent service could commence. The frequency is subject to interference from KGEI in San Francisco, also using 15280kHz.

The earlier test transmissions from Brasilia were on 11780 and 15240kHz with English at 2200GMT, but this transmission is beamed to North America. The station is giving a new address for reception reports and this is: Radio Nacional Brasilia, c/- International Correspondence Service, Post Office Box 04-0430, Brasilia, Federal District, 70323 Brazil.

RADIO AFGHANISTAN

As well as a verification card, Radio Afghanistan at Kabul gives some background information on the history of broadcasting in that country. In Afghanistan, as in other developing nations, radio reaches the largest number of people, far more than the printing press.

Experimental broadcasting began in Afghanistan as early as 1925, when two small broadcasting transmitters were imported to Kabul. Regular broadcasting began in 1940 with a medium-wave transmitter. Later on, the station was equipped with more medium and short-wave transmitters.

Until 1963, the broadcasting station in Afghanistan was called Radio Kabul, but following continued expansion assumed the name of Radio Afghanistan. Radio Afghanistan verifies reception reports with a card, as long as return postage is enclosed and the report covers the usual details required by an international station.

The present schedule of Radio Afghanistan includes two broadcasts in English: 1400-1430GMT on 4775kHz and 1900-1930GMT on 11895 and 15140kHz. Radio Afghanistan broadcasts for 106 hours on medium-wave, while the External Service is carried for 31 hours 30 minutes each week. The address of the station, is Radio Afghanistan, PO Box 544, Kabul, Afghanistan.

NEW LISTENERS CLUB

The Belgium Radio and Television has commenced a listeners club on its short-wave service, and listeners can join by writing to BRT, PO Box 26, B1000 Brussels. There will be special information bulletins for club members, verification cards, stickers and penants.

The Belgium DX Corner is broadcast on the 2nd and 4th Monday of the month during the English transmission to North America 0015-0100GMT on 11705 and 15190kHz.

NEW ZEALAND SCHEDULE

Radio New Zealand has made some alterations to its schedule for broadcasting to the Pacific, with closedown now being at 1030GMT. The service to Australia continues to be broadcast up to 1215GMT.

Broadcasts to the Pacific are: 1800-2105GMT on 11835kHz; 1800-0625 on 15345; 2115-0815 on 17860; and 0640-1030 on 6105. Broadcasts to Australia are 0830-1215GMT on 11945kHz; and 1045-1215 on 6105. It is expected that this schedule will remain in force up to the last Sunday in October, when there will be a change to daylight time in New Zealand.

NEW MALTA FREQUENCY

Radio Malta, after broadcasting for some months for evening reception in the United Kingdom, now has changed to a morning broadcast which is heard 0700-0800GMT on Saturdays. The frequency used is 9670kHz, and this outlet is noted after the Voice of America closes at 0700GMT. There has been some interference from Radio Australia which is also using the frequency.

The program consists of bright music and a news bulletin at 0705GMT. Requests for reception reports are made during the transmission and these should be sent to Radio Malta, PO Box 82, Valletta, Malta. The station verifies with a letter and also sends a tourist booklet about Malta.

LISTENING BRIEFS EUROPE

BULGARIA: Radio Sofia has changed some frequencies for its English broadcasts and is now heard on 15310kHz 1830-1900GMT to Africa, along with 17825kHz. The broadcast to Europe 1930-2000 is on 9700 and 11720kHz, while the transmission to North America is now carried on 11860kHz 0430-0500GMT.

VATICAN: The Vatican Radio is to continue to use the frequency of 11745kHz with English to Australia 2210-2225GMT.

ASIA

PAKISTAN: Radio Pakistan has been heard with strong signals on 21655kHz.

This frequency replaces 21625kHz, and carries the World Service to the United Kingdom from 0715-1100GMT, and the English slow speed news 1100-1115GMT. Radio Pakistan has dropped 9465kHz and added 15465kHz in parallel with 11675kHz for the broadcast in English to Europe at 1700GMT, with Urdu following at 1730GMT.

TAIWAN: Following the closure of the American Forces Taiwan Network in April, some businessmen in Taipei have set up a broadcasting organisation to continue English language programs in the area. In the past AFTN has broadcast on medium- and short-wave. The new group plans to call the station "International Community Radio" and it should be heard in this part of the world.

OMAN: A verification card which gives the new schedule for Radio Oman has been received by Peter Bunn of Melbourne. The station is operating on 6175kHz 0200-0715GMT and 1400-2015 in Arabic; and on 11890kHz 0900-1100 in English and 1100-1315GMT in Arabic.


AMERICAS

BRAZIL: Radio Continental has been heard with fair signals at 0915GMT after the BBC relay station on Antigua leaves the frequency. The BBC station carries the World Service 0900-0915GMT. Radio Tupi is reported in Sweden Calling DXers as being heard on 15365kHz at around 0015GMT.

BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076
(ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)

B.S.C. TELEX AA36004

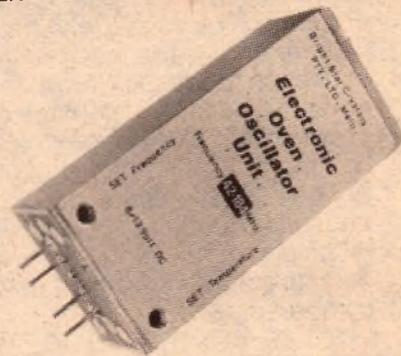

BRIGHT STAR CRYSTALS ARE PLEASED TO ANNOUNCE A NEW RANGE OF ELECTRONIC CRYSTAL OVENS AND OVEN OSCILLATOR UNITS.

DATA SHEETS AVAILABLE ON REQUEST

INTERSTATE AGENTS:

- ROGERS ELECTRONICS
ADELAIDE Phone 42 6666
- HOSE & EQUIPMENT
SYDNEY 666 8144

- DILMOND INSTRUMENTS
HOBART 47 9077

- WESTEST ELECTRONICS
PERTH 337 6393
- FRED HOE & SONS PTY LTD
BRISBANE 277 4311



U.H.F. CB antenna strength loss is no longer a problem.



Philips introduce the battery operated Field Strength Meter which lets you measure the efficiency of your U.H.F. C.B. band antenna. F.S.M. sensitivity is such that measurements are normally made at distances greater than 20 metres from the antenna being monitored or tested. The small detachable quarter wave pick-up antenna is inserted into the INPUT socket on top of the F.S.M. If a remote antenna is required in place of the one provided the feeder from the antenna is connected to the input socket.

The F.S.M. enables day to day checks of transmitted radiated power, comparison of relative gain between antennas, and accurate measurement of radiated power to construct a polar diagram.

An important addition to your U.H.F. C.B. radio operation. For further information contact your local Philips Service Branch on the following telephone numbers, or bring your rig in for a test.

Sydney 736 1233, Newcastle 61 1631, Canberra 95 0321, Melbourne 699 2731, Hobart 28 0121, Brisbane 221 5422, Townsville 79 7422, Adelaide 223 4735, Perth 322 4653.

Specifications of the Philips U.H.F. field strength meter

Frequency Range.....477MHz + 5MHz. Input Impedance...50 Ohms.
 Input Level.....-30dBm (+ 1.5dB) at maximum sensitivity.*
 Scale Calibration.....-10dB to + 1dB, relative to -30dBm input.
 Power Supply.....2 Standard 9V transistor radio batteries.
 Battery Life.....With normal intermittent use - over 150 hours.
 This will be double with long life batteries.


*When the sensitivity control is set at MINIMUM, a further reduction of approximately 10dB is provided. This control is combined with the ON/OFF switch.

(Also illustrated are 2 of the new Watt meters for signal measurement)

Service
Service
Service

PHILIPS

The Australian CB SCENE

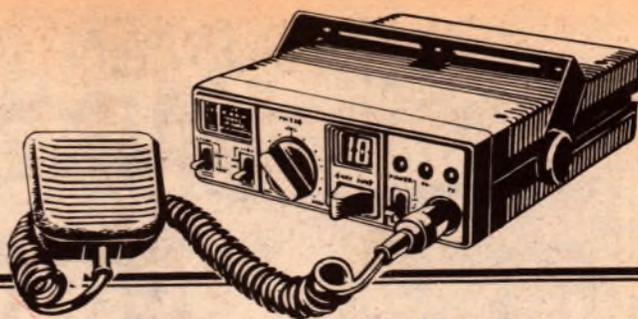

CB: MORE THAN ITS SHARE OF AWKWARD QUESTIONS

Is CB, on balance, a blessing or a menace to the community? Should the 27MHz band be maintained, encouraged or regulated out of existence? How can Australia square its use of 27MHz with world radio planning? Questions like these are indeed awkward.

by NEVILLE WILLIAMS

Citizens Band radio came to Australia in force a couple of years ago, amidst a tremendous barrage of publicity, and supported by a whole range of people from "progressives" through to businessmen who stood to benefit financially.

In the normal way, the authorities would almost certainly have turned CB down flat but they were faced with a virtual fait accompli — tens of thousands of CB transceivers in use and on sale, following years of neglect by successive governments. To use an old phrase, the horses were already well and truly out of the stable!

But victory turned rapidly sour for most of the campaigners. In very short order, CB users made headlines in the daily press for obscenity, larrikinism, standover tactics and other questionable activities. For the most part, the "progressives" dropped it cold. CB ceased to be the "in" thing and importers found themselves with huge stocks, which they had no hope of shifting in short order, even at almost giveaway prices. That problem is still with us.

Importers weren't the only ones to suffer. Knowing that the Government planned to close down CB on 27MHz by July 1, 1982, the Philips organisation developed their uniquely Australian UHF transceiver. Pricewise it should have been able to compete, in a booming market with quality HF imports at the then ruling figures; it was a quite different matter competing against heavily discounted 27MHz imports in a market which had turned sour.

So sour, in fact, that Philips stopped talking about CB altogether and began to woo prospective customers on the basis of "personalised two-way radio"!

This tactic had a quite unforeseen repercussion: the lobby, which had long been keen to see the tariff removed from CB imports seized on it as

evidence that their 27MHz transceivers and the Philips UHF transceiver were not really in competition; the tariff should therefore be removed.

Indeed, in one sense they are not in competition. If a prospective purchaser examines the propagation characteristics of the HF and the UHF bands, makes a deliberate prior choice, and then starts looking for suitable equipment, the two classes are quite distinct.

On the other hand, if the initial decision is to buy a two-way radio of some kind, subject to availability, looks and price, then the two varieties certainly are in competition. At \$300-plus, Philips are already at a disadvantage selling against discounted high quality imports. With less tariff, the gap could only be greater.

Fairly obviously, the Government would like to sustain Philips' local production of a uniquely Australian product with a possible export potential. Equally, they would doubtless like to see a run-down in the stockpile of 27MHz transceivers; the sooner they are sold, the sooner will they cease to be a source of pressure to go on issuing licences for 27MHz. By the same token, if the Government is sincere about closing down 27MHz CB, it can't afford to do anything which will prompt a new wave of imports. In the long term, removal of the tariff might have just that effect.

Although questions like this persist, the authorities must at least have been thankful for a brief period of respite from the emotive side of CB. Towards the end of last year, it dropped out of the news and, while dedicated enthusiasts pursued the hobby as ever, the public at large forgot about it. It was on its way to becoming a routine activity that some followed and most ignored!

Then came a crime which was

headlined in the Sydney press as a "CB Murder". Whether the headline was justified is debatable but suddenly CB was back in the news, in a most un-savoury context.

This was followed in short order by the truckies' strike with its reported dependence on CB radio to organise blockades and supplies. Initially it was seen as part of the bravado; later, as the mood of the public changed, CB became increasingly part of a mischief. Politicians, faced with a highly embarrassing situation, must surely have speculated whether it would have reached the same proportions had not the truckies been able to communicate so effectively via 27MHz CB.

It's hard to say what will happen from here on but I wouldn't be at all surprised to find that these recent events have strengthened the hand of those who would like to see 27MHz CB contained, and finally bottled up in July 1982. CB certainly can't afford a repetition of these recent events: what it needs above all else, is a low profile and improved internal discipline.


Another factor which must be borne in mind is that Australian authorities are going to find it increasingly difficult to legislate for CB, or any other service, as a purely internal matter. More than any previous conference, WARC'79 is going to put the spotlight on each country's use of spectrum space — and CB of the high-powered variety may find itself with far more critics than backers.

A curious news report preceded the recent national liberal Party conference in Perth. It nominated various major matters that would occupy the attention of the conference and, at the end of the list: CB radio! I haven't heard whether it actually came up for discussion but, presumably someone felt that it was politically "awkward" enough to warrant inclusion on the agenda of a national conference!

L. E. CHAPMAN

122 PITT RD, NTH CURL CURL
MAIL ORDERS BOX 156, NSW 2099 TEL.: 93 1848

SUPER SPECIALS FM STEREO TUNER KITS

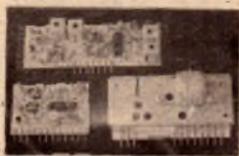

SETS OF 3 MODULES INCLUDE FM TUNER, DECODER & IF/DETECTOR. CIRCUIT DIAG. SUPPLIED. CAN BE USED WITH AMP MODULES


ONLY \$18!



PHILIPS TV TUNER
Transistor
NT3030
NT3032
Colour
\$10 ea

100 Mixed Resistors, all useful.
\$2.00

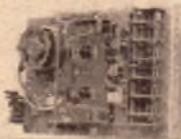Special! 100 mixed capacitors — fresh stock, all useful
\$2.00



VORTEX DECKS

COMPLETE WITH HEADS & CIRCUIT FOR AMPLIFIERS FOR THE DECK.

ONLY \$25!

SPARE ERASE HEADS for above \$2 ea

VU & BALANCE METERS



STEREO VU
\$3



12 Kn 100uA
\$2



BALANCE
\$1

NEW EDITION

FUNDAMENTALS OF SOLID STATE

Fundamentals of SOLID STATE



ONLY
\$3.50
+ 60c
p&p

Fundamentals of Solid State has been reprinted, revised and updated showing how popular it has been. It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised texts very heavy going. It begins with atomic theory, diode types, uni-junction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A glossary of terms and an index complete the book. Fundamentals of Solid State has also been widely adopted in colleges as recommended reading — but it's not just for the student, it's for anyone who wants to know just a little bit more about the operation of semiconductor devices.

Available from:
"Electronics Australia", 57 Regent St, Sydney. **PRICE \$3.50** OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. **PRICE \$4.10.**

Dick offers FANTASTIC Value on Playmaster Kits



YES! Over 500 of these magnificent Playmaster Tuners have been sold. NOW, because of our increased buying power of components we have actually been able to **REDUCE THE PRICE!**

Buy now as the price can only remain at this low price while stocks last.

Reap the benefit of our huge buying power NOW!

NOTE: This special price can only apply to our second production batch of 500 units.

LOWER PRICE

PRICE

AM/FM Stereo

Digital Tuner/Clock

A superb stereo tuner with digital station readout PLUS, at the flick of a switch, a built-in digital clock. AM plus FM/stereo, too. All this in a superb looking, easy-to-build kit with an extremely detailed construction manual. You'll be listening to your Playmaster Tuner in no time! The tuner heart comes as a complete, ready built module. No alignment is necessary.

Take advantage of this special reduced price NOW: we'll even send the kit anywhere in Australia for only \$6.00 extra. That's actually **BELOW COST!**

(Tuner shown with optional wood-grain finish sleeve: it makes your tuner look so good your friends won't believe you built it. **Timber Sleeve: Cat H-3113 @ \$8.50**)

Terms available to approved applicants, personal shoppers only

ONLY 500 UNITS AT THIS PRICE!!

See EA Nov/Dec '78 & Jan '79

SAVE \$30



NOW ONLY \$129⁵⁰

Cat K-3494

DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RE-SELLERS

TECHNICAL GLOSSARY — continued

CRYSTAL: A term with a variety of meanings. In the context of transmitters and receivers it usually refers to an assembly containing a critically ground wafer of quartz, which is resonant at a particular frequency. As far as the crystal is concerned, the resonance is primarily mechanical — the frequency at which it tends naturally to vibrate. When associated with electronic circuitry, the mechanical vibration can be translated into an equivalent electrical oscillation. "Crystals" cut and etched from either natural or artificially grown quartz, and mounted in appropriate holders, are widely used as the frequency determining elements in oscillators, or in filter networks.

CYCLE: In general terms, one complete round of a repetitive event. More specifically, if a train of alternating current (AC) or alternating voltage waves is displayed, one cycle is the plot between any two adjacent but exactly symmetrical points on the display. Most commonly, the start of

a cycle is taken to be the point where the display crosses the median line moving upwards. Thereafter, it moves to an upper peak, back across the median line to a lower peak then back towards the median line. Where it crosses the median line the second time would be the end of the original cycle and the beginning of the next.

DC (DIRECT CURRENT): current which flows in the one direction through a circuit. The amount of current flowing may vary from instant to instant in sympathy with a signal present in the circuit but, if electrons in the circuit always flow in the one direction, the current present is said to be "direct". The current flowing from a battery to a CB transceiver is DC, as also is the current flowing thence to the collectors of the various transistors, even though they are handling signals. When the electrons in a circuit actually reverse direction, particularly in a cyclic way, the current present is said to be "alternating" current or "AC".

DC VOLTAGE: expanding the abbreviation it means literally a "direct-current voltage". This is a most awkward term, which is never used in that form. On the other hand the expressions "DC voltage" or "volts DC" enjoy very wide usage, if only for lack of a better term. The idea is that a DC voltage is one which relates to a direct current. It can be as a voltage (and current) source, or the potential which results when a direct current produces a voltage drop across a resistance. By contrast, an "AC voltage" is one which relates to an alternating current.

DELAYED AGC: (see also Automatic Gain Control). Most modern receivers incorporate a system of automatic gain control (AGC). It involves producing a control voltage which increases as the level of the input signal rises. The control voltage is applied to amplifiers in the RF and IF chain, limiting their gain and tending to keep the level of the signal at the detector fairly constant. With "simple" AGC, the system operates with even the weakest input signals and diminishes their apparent strength quite unnecessarily. With delayed AGC, the operation of the system is inhibited (or "delayed") so that it acts only upon signals above a certain minimum strength. It is a matter of signal and voltage levels; it has nothing to do with time. 🗨

KEYBOARDS



Microcomputer-based Intelligent Keyboard 103SD24-2

- Solid state Hall Effect keys with single chip microcomputer.
- 8-bit CPU, ROM, RAM, I/O and time/event counter with 8-bit USASCII coding in 4 modes.
- Serial & Parallel data outputs.
- 14 relegendable key tops for customer assignment.
- 8 deep FIFO character storage.
- N-key rollover.
- Timed auto repeat for designated keys.
- Repeat key controls repeat for other designated keys.
- Secretary shift and audio feedback drive.
- Pin for pin compatible EPROM capability.
- Single 5V supply.

MOS Encoded Communication Keyboard 53SD5-2

- Hall Effect solid state keys coupled to MOS encoding.
- Familiar Model 33 array.
- USASCII code assignment with 4 modes of operation.
- Two key rollover.
- Quiet operation — only moving part is key plunger.

HONEYWELL PTY. LTD.
863-871 Bourke Street, Waterloo, 2017
Tel: 699 0155

Honeywell MICRO SWITCH

Available from:	Silicon Valley	51 4080	MELBOURNE:	Silicon Valley	52 1339
ADELAIDE:	Silicon Valley	51 4080	NEWCASTLE:	DGE Electronics	69 1625
BRISBANE:	Silicon Valley	52 1339	PERTH:	Micro Controls	325 2444
CANBERRA:	Ortex	82 4994	SYDNEY:	Silicon Valley	439 2965

New Products

Toshiba RT-8340S portable: heart of a system

Without being unduly large or heavy, the new Toshiba RT-8340S stereo radio cassette recorder manages to pack into one portable package a considerable range of entertainment facilities. Toshiba say that it is intended to slot into the market between economy (usually mono) cassette/radios and the much more expensive three-in-ones.

As distinct from the manufacturer's model number RT-8340S, the new receiver carries the name "Bombeat". The word did nothing for this reviewer, although it may have a subtle charm for the under 25's, as one of the target groups! It would certainly have the appropriate visual appeal, with its array of facilities.

As a basic radio, the RT-8340S offers normal broadcast band coverage with in-built ferrite rod antenna, plus two short-wave bands operating from a telescopic rod, which otherwise rests along the top of the cabinet. The short-wave coverage is from 2.3 to 22MHz overall, with separate MHz scales for each band. By way of additional vernier action, a small "fine tune" knob is provided.

The vertical whip antenna also serves the FM band mode and this is in full stereo, with automatic frequency control and a stereo indicator LED. As with AM, a tuning meter at the left-hand end of the dial indicates signal strength, so that accurate stereo FM reception is ensured by observing both the LED and the meter. Tested under typical user conditions on a Sydney suburban home, all the radio facilities performed as expected, with adequate gain and selectivity, good signal/noise ratio and no sign of AGC overload, even on a powerful nearby station.

The receiver is equipped with two inbuilt speakers, of nominally 120mm diameter, and twin amplifiers each rated at a nominal 3.5W.

Of special interest is a switch marked "Stereo — Wide — Space Wide". On stereo program material, pushing the switch through the latter positions produces an obvious broadening of the apparent signal source, out of all proportion to the size of the receiver itself. Without having an opportunity to see the circuit, we tip that the switch introduces high frequency cross-phasing between the channels plus, perhaps, some blending in the normal stereo position. As we said, the effect is obvious, although we also gained the impression that, on other than clean program material, it tended to highlight any noise and distortion.

The cassette facility provided in the RT-8340S is practical but fairly basic. It uses supersonic (50kHz) bias but erasure is by a multi-pole magnet, presumably to conserve current drain when operating from batteries. There is no provision for CRO2 tape and one would assume that the unit has been pre-set for conventional ferric tapes, as far as recording is concerned. Signal/noise ratio is rated at 48dB, wow and flutter at 0.2% and frequency response as 50-12,000Hz, although without dB limits.

Tape controls include the usual Play button, flanked by Rewind and Fast Forward. The last two can be partially



depressed while the recorder is in Play mode, to provide a "review" and "cue" facility. There is a locking type "Pause" button which can be operated without impressing any click on the tape, and a "Record" button which is interlocked with "Play" to provide single button control. The mechanism will switch off automatically at the end of the normal play or record function, but not when fast spooling.

Recording off air is simplicity itself: merely tune the desired program and operate the "Record" function, as per the manufacturer's instructions. The program can be recorded while the receiver is playing at any desired volume, even silent. When using the in-built electret microphones, the loudspeakers are silenced automatically, to prevent acoustic feedback. On test, the record functions operated normally, although, as expected, there was some background from the motor when using the in-built microphones. In both modes, recording level on to the tape is controlled automatically — and effectively.

However, the RT8340S has provision for external microphones, external speakers, headphones, and an auxiliary input which can be used with any signal source having a flat frequency response. In short, apart from being a self-contained portable, the unit has provision for expansion.

Normal operation is from the AC power mains but there is provision for a 12V DC input, and for internal batteries: eight type D cells. The battery drain is about 90mA on radio and 100mA for tape play, both with the volume turned well down. Turning up the volume towards maximum produced peaks of between 500 and 700mA indicating the need for moderation in this mode, in the interest of battery life.


Recommended retail price is \$229. For further details of the RT-8340S and appropriate external microphones, speakers, etc: Toshiba Aust Pty Ltd, PO Box 452, Lane Cove 2066. (W.N.W.)

Plug-in thermostat



A&R Electronics has introduced the Arlec "Thermoplug", a self-contained plug-in thermostat unit designed to provide temperature stabilisation for domestic electric heaters. The unit plugs into a normal power outlet, and itself provides an outlet for the heater. Retailing for around \$18, it incorporates 10A switching contacts and a continuously variable temperature control. Further details from A&R Electronics at 30 Lexton Road, Box Hill, Victoria 3128.

Sensitised laminate

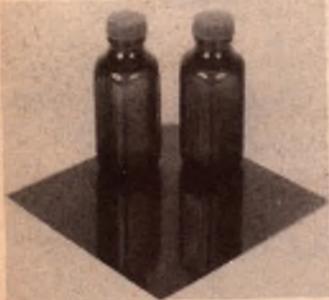

Fibreglass PCB laminate pre-coated with "Riston" negative photo resist is now available in Victoria from All Electronic Components. The laminate is available in both single and double-sided form, and in a number of sizes. Single-sided board is available in 306 x 306mm, 306 x 154mm and 154 x 154mm sizes, while double-sided board is available in 306 x 306mm and 154 x 154mm sizes.

30MHz Trio 'scope for TV

A new 30MHz dual trace oscilloscope designed with video applications in mind has been released by Trio-Kenwood Corporation in Japan. Designated the model CS-1572, the new instrument is especially suitable for servicing and maintenance of CCTV and VTR equipment. Although provided with only a single sweep generator, it has a newly developed video delayed trigger capability which offers video waveform analysis capabilities very similar to those provided by delayed sweep. Triggering can be established at any point within a TV frame, and a desired segment magnified by increasing the sweep rate. Alternate video fields can also be displayed one above the other on the dual traces.

The CS-1572 has 30MHz



bandwidth at 5mV/division sensitivity and 200ns maximum sweep speed. It uses a mesh-type PDA tube for bright, high resolution displays.

Further information on the CS-1572 is available from local Trio agents Parameters Pty Ltd, 68 Alexander St, Crows Nest, NSW 2065.

AEC also has available liquid developer for the resist, etchant and etching kits, trays and instruction sheets for the use of these products.

Prices for the pre-coated laminate range from \$2.70 for the smallest size in single sided form up to \$12.70 for the larger size in double-sided form. Bottles of photo-resist developer are available at 55 cents each.

Further details from All Electronic Components at 118 Lonsdale Street, Melbourne who are the Victorian distributors for these products.

Fibre optic links

Rank Optics has released a new mains-powered duplex fibre-optic data link, designed to meet the needs of multi access computer system users. Electrical interfacing is at TTL levels, via a "D"-type connector. The fibre-optic



connections are made by AMP optical connectors. At a data rate of 10M bits/second the system can be used at distances up to 1.5km with Rank fibre type 250/PCS2/08. Fibre optic cables are available already terminated with AMP connectors for use with the link units.

Further information is available from Dennis Irving, Professional Services Group, Rank Industries Australia Pty Ltd, Melbourne. Telephone (03) 29 3724.

THE SORCERER PERSONAL COMPUTER

ORDER NOW!

Why did Dick Smith take so long to release a personal computer? Because it takes time to make the best selection, that's why! We are proud to be associated with this fine 100% U.S. made product - the EXIDY "Sorcerer" hobby computer. The "Sorcerer" is in fact the most versatile hobby computer available today. Because hobby and business requirements are so enormously varied, the Sorcerer has designed-in flexibility to accommodate both. This means that if you buy the Sorcerer now you won't have a piece of near obsolete equipment on your hands in a year's time!

"THE FIRST HOME COMPUTER WITH THE FLEXIBILITY TO SATISFY THE NEEDS OF ANYONE FROM THE HOUSEWIFE TO THE DEDICATED MICRO ENTHUSIAST."

8k ONLY \$995⁰⁰

Dealers for the products of Dick Smith Electronics



69 1222

ELECTRON 2000

WE SUPPLY THE DICK SMITH PRODUCTS ADVERTISED IN THIS MAGAZINE • 44 Brown Rd. Broadmeadow, 2292

ELECTRONICS Australia, June, 1979

119

**BRASS SHIPS CLOCKS
SMITHS 8 DAY 7 INCH
DIAMETER \$110**

Post A \$175; B \$300; C \$360.

**GENUINE EX ARMY WRIST
WATCHES**

Complete with nylon band \$19.50
Post \$1.10

P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line. **\$39.50**

(2 TELEPHONE SETS)

\$2 Cartage to Rail. Freight payable at nearest attended Railway Station.

RECEIVER No. 210

2-16 M/cs \$65
Transmitter No 11 suits 210 \$35
24 volt Power supply to suit above \$15.
Or complete station with Headphones. Mic. **\$110**

**EX ABC
MAGNETIC RECORDING
TAPES 1/4"**

PROFESSIONAL QUALITY

5" x 600' **\$1.50**
7" x 1200' **\$2.75**
P + P \$1.30
10 1/2" x 2400' \$7.95
P + P A \$1.65 B \$2.75 C \$3.10

**COLLINS INDEPENDENT
SIDEBAND TRANSCEIVER
TRC/75**

Fully synthesised transceiver with am. upper, lower and independent sideband operation. 1KHz steps from 2MHz to 29.999MHz. 1 microvolt sensitivity. 2.5KHz bandwidth ssb. 6KHz bandwidth AM. 1 RW PEP max output. Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc. 400Hz supply. *Ideal for amateur use*
PRICE \$750

**COLLINS SYNTHESISED 1
SB RECEIVER**

TRC/75 receiver section of transceiver specification as above.
PRICE \$400

TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don. 8 perfection condition \$39.50 per drum. \$2.00 cartage to rail freight payable at destination.

**20X to 60X
ZOOM TELESCOPE**

With Tripod. \$115.50.
Post **A\$2.25, B\$4.10, C\$6.10.**

RCA 44BX MICROPHONES

PROFESSIONAL QUALITY \$75
P&P A \$1.80, B \$3.50, C \$4.55,
D \$4.55

AERIAL CAMERAS

WITH 8" FL 3" DIAM. LENS F24 MARK
IV 2.9 LENS STOPS 11, 8, 5.6, 4, 2.9 —
\$65
\$2 cartage to rail freight. Payable to nearest attended railway station.

PENTAC LENSES

3" DIAM 8" FL WITH DIAPHRAGM
STOPS 11, 8, 5.6, 4, 2.9 MOUNTED IN
METAL HOUSING — **\$65**
POST: A \$1.85, B \$3.25, C \$4.10

PRISMS

4" SQUARE FACED RIGHT ANGLE
PRISMS TOP QUALITY EX AIR FORCE
— **\$65**; OR LENS & PRISM FOR \$120
POST A \$1.75, B \$3.00, C \$3.60

SOLENOIDS

200 MA 24 volt 1/8in push movement.
\$2.50 P+P 80c

NIFE CELLS

1.2 volt, fully charged. 4in x 3in x 1in 4
AH. **\$1.50 each P&P 80c**

**ROLA 66 MK 2
TAPE RECORDERS**

Good condition **\$275.00**

ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 5 1/2" diam gunmetal rotating circle. Adjustable elevation and depression. Has top grade 3/4" diam. object lens FL 10" with cross hairs, eyepiece, 1/2" right angle prism — height 10" — weight 3 1/2 kgs. With leather carrying case. Original cost \$300

Our Special only **\$27.50**
P&P A \$2.25 B \$4.00 C \$6.00



**ZOOM SPOTTING
SCOPES**

30 x 30
LENGTH 12 1/2" HEIGHT
10"
WEIGHT 1 3/4 lb
\$32.50

High grade coated lenses
Ideal for pistol and rifle ranges or general viewing. Zooms in from very low to high powers. Complete with tripods.
POST A \$1.75, B \$3.00,
C \$3.60

TELESCOPES

25 x 30 \$13.50
P&P A \$1.30

45 x 40
Length 16in
Height 10in
Weight 2lb
\$49.50

SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8". Only **\$7.95** each, post 60c.

BINOCULARS

PRISMATIC Coated Lenses. Brand new Complete with case

8 x 30	\$36.50		
7 x 50	\$48.95	P&P	
10 x 50	51.00	A	\$1.75
12 x 50	53.00	B	\$3.00
		C	\$3.10

**SMALL CLIP-ON
POCKET TELESCOPE**

15X **\$7.00, P+P 80c**

**3" ASTRONOMICAL
REFLECTOR TELESCOPE**

117X magnification FL 700mm with 5x24mm finder scope and two section hardwood tripod. **\$169.25**
Post **A\$2.25, B\$4.10, C\$6.10**

3000 TYPE RELAYS

P.M.G. 200 ohms — 1,500 ohm
Coils **\$2.50** each P+P 80c

AIRCRAFT INSTRUMENTS

Directional Gyros
AN5735-1 Air Operated **\$35**
Sperry Artificial Horizon
AN5736-1 Air Operated **\$45**
Slip and Turn Indicators
\$17.50
P&P
A \$1.65, B \$2.75, C \$3.10

**SIEMENS
Typing Perforator**

240 Volt Type with Keyboard **\$57.50**

ANEROID BAROMETERS
In brass case, made in London. **\$95**
P&P A **\$1.65**
B **\$2.75**
C **\$3.10**

POSTAGE KEY:

A NSW
B Vic. Qld. SA
C NT Tas
D WA

VALVES

BRAND NEW
6SN7 **\$1.95** 6BM8 **\$1.95**
5U4 **\$1.95** 6GV8 **\$1.95**
EF50 **\$1.50** 6AK5 **\$1.95**
1H6 **\$1.50**
2x2 **\$1.50** 832 **\$5.00**
P+P 80c
6x4 **\$1.95**
VR65 **\$1.50**

**STC HIGH IMPEDANCE
HEADPHONES**

3400 ohms, brand new, only **\$4.95** pair.
P&P A \$1.65 B \$2.75 C \$3.10

**WRIST WATCHES
SWISS JAEGER**

Le Coultre ex RAAF rated one of the world's best in smart chrome case with black dial. Original cost \$250

SPECIAL **\$49.50**
Post **\$1.30**

THEODOLITES

Made by Wilds Microptic, with tripod Model T1, reads down to one minute of ARC **\$750**.
(Usual Price **\$1750**)
Model T2 reads down to one second of ARC **\$1000** (Usual Price **\$3200**)
Freight payable at nearest attended R way Stn

**ZOOM FOCUSING
MICROSCOPES**

Zoom focusing microscopes, 750X battery and mirror illuminated **\$31.75**
Zoom 1200X similar to above **\$47.95**
P&P A \$1.65, B \$2.75, C \$3.10

**TRANSCEIVERS
Ex Army**

No. C45 set 23 to 38MHz with headphones, mic 24V power supply, etc. **\$95.00**
\$1.00 cartage to rail, freight payable at nearest railway station.



**EX-ARMY
TWO-WAY
FM RADIOS**

1.2 WATTS OUTPUT
SUPERHET
PRC9 AND 9A 27 to 39M/HZ
PRC10 AND 10A 38 to 55M/HZ
WITH HANDSET ANTENNA \$25 EA.
UNTESTED
Battery **\$3.95** extra. Harness **\$4.50** extra
\$2 Cartage to Rail. Freight payable nearest attended Railway Station.

**16MM SOUND PROJECTORS
IN GOOD WORKING ORDER**

240 volts operated complete with Speaker and Amplifier.
RCA **\$275**
BELL & HOWELL **\$195**
\$1 Cartage to Rail. Freight payable at nearest attended Railway Station.

**SELSYN MOTORS
MAGSLIP**

RECEIVERS 2" MK2 **\$5.50**
TRANSMITTER 3" MK2 **\$15.00**

Post Packing A \$1.75, B \$2.75, C \$2.75, D \$3.65
P+P: A \$1.75, B \$3.00, C \$3.10

**COMMUNICATIONS
RECEIVER**

COLLINS R — 391/URR
Continuous tuning of range 500 KHz — 32MHz in 32 bands. Receive frequency indicated directly on digital counter type readout to within 300Hz. Selectivity adjustable in six steps. From 100Hz to 16KHz bandwidth. Sensitivity 1 microvolt or better 240 VAC operation — 10 inch rack mount — autotone on eight preset channels available complete with instructions and service manual and tested.
PRICE \$500.

Deitch Bros.
70 OXFORD STREET, SYDNEY 2010

SORRY NO COD

New Products

New fire detection system

A new fire prevention system that detects fire and over-heating in tunnels, conduits, cable ducts, floor voids and other inaccessible areas has been introduced to Australia by Fire Fighting Enterprises (Aust) Ltd.

Alarmline, described as a new concept in continuous line detection in high fire risk, is already in use by BHP at Newcastle and Australian Iron And Steel at Port Kembla.

The system employs sensitised cables which detect over-heating or fire and flash the alarm back to a control unit where appropriate action is taken. Its major uses are in mines, petrochemical plants, heavy industrial works, power

stations, ocean transporters and wheat silo and conveyor complexes where the consequences of over-heating can be catastrophic and surveillance may be restricted.

For further information contact Fire Fighting Enterprises Pty Ltd, 6 Hope St, Ermington, NSW 2115.




Stick-on tracks for fast PC boards

A range of pre-etched, pressure sensitive copper mounting configurations has been released by Bishop Graphics Inc (USA). Called "Quick Circuit", the range consists of various copper patterns electro-deposited on a very thin epoxy-glass substrate. The patterns come predrilled and are designed to mate with 2.54mm grid pre-punched epoxy-glass board to allow fast, easy construction of PC boards.

The adhesive-backed patterns are also useful for the repair of existing PC boards which may have become damaged.

Also recently released by Bishop Graphics is a 200-page publication entitled "The Design & Drafting of Printed Circuits". The book is broken down into 17 chapters, and covers every aspect of PCB design.

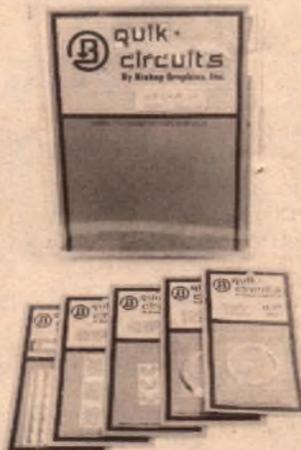Bishop Graphics products are distributed in Australia by Circuit Components (A/Asia) Pty Ltd, 383 Forest Road (PO Box 70), Bexley, NSW 2207.



Scientific desk calculator

Dick Smith Electronics has purchased the entire remaining stock of the Sharp "Compet 1002" LSI programmable scientific desk calculator from the manufacturer, and is offering 500-odd units at the low price of \$49.50.

The calculators are mains powered and have a 10/12 digit fluorescent display. They can operate in either floating-point or scientific notation, and can store and run programs of up to 64 steps.

As supplied they provide the four basic maths functions plus trig and inverse trig functions, hyperbolic functions, common and natural logarithms and antilogarithms, exponentials, square and square root, mean and standard deviation and polar/orthogonal conversion. There is also a "pi" key,

and the ability to use up to eight memory registers (which progressively reduces the program memory capacity).

The units are sturdily made, and seem very good value for money at the price quoted. You might have to be quick, though, with only 500 available.

Further details from DSE stores in most states — see their advert in this issue.



Solid-state recorders

Measuring & Control Equipment Co Pty Ltd has developed a solid-state recorder for recording field data. The recorder employs erasable read only memories (EPROMS) to store data in a non-volatile form.

The memory cartridge can be removed from the recorder and will retain recorded data without the need for backup power. The data is read out by means of a translator (playback) unit, and the memory then erased by exposure to UV light for re-use.

MACE is currently producing two versions of the recorder for hydrological and meteorological use. Enquiries to Measuring & Control Equipment Co Pty Ltd, 5 The Boulevard, Epping 2121.

Australian Film and Television School

is looking for aware, creative men and women dedicated to film and television careers in the area of

SOUND

for the three-year full-time course beginning **March 1980**. The course covers all aspects of **RECORDING, BALANCING and MIXING of DIALOGUE, MUSIC and SOUND EFFECTS.**

Training is also given in **PRODUCTION EDITING** and **CAMERA** techniques with **DIRECTION** as an option in second and third years.

The AFTS is a Commonwealth government authority, located in Sydney. An allowance of \$5000 a year, plus dependants' allowances and assistance with moving to Sydney where required, is paid to students while training.

Applications, which close on WEDNESDAY, JULY 4, must be on the official form, obtainable with all necessary information from


Recruitment Officer, Australian Film and Television School, PO Box 126 NORTH RYDE, NSW 2113. Sydney (02) 887 1666, Melbourne (03) 328 2683



JUST PUBLISHED

A Newnes Project Constructor Series from Newnes-Butterworths

Newnes Constructors Projects books have been specially written for the electronics enthusiast. Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, circuit board layouts are suggested and shopping lists of components drawn up for each project.

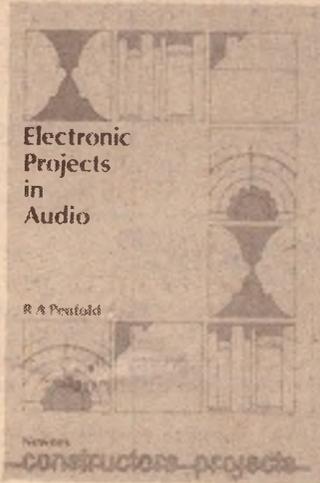

BOOKS IN THIS SERIES:

- Projects in Radio and Electronics — I. R. Sinclair*
- Electronic Projects in Hobbies — F. H. Rayer*
- Electronic Projects in the Home — O. Bishop*
- Electronic Projects in the Car — M. George*
- Electronic Projects in Music — A. J. Flind*
- Electronic Projects in the Workshop — R. A. Penfold*
- Electronic Game Projects — F. G. Rayer*

Order now from your Bookseller or if unavailable, use order form below.

ORDER FORM

Please send me the following books:

.....

Cash Enclosed

Please Bill Me

NAME:

ADDRESS: Postcode:

SIGNATURE: Date:

(Recommended Domestic Retail Prices include postage and are subject to change without notice. This order is subject to acceptance by the Head Office of Butterworths)

MAIL TO

Butterworths

Pty Limited

586 Pacific Highway, Chatswood 2067.





Books & Literature

Security devices

ELECTRONIC SECURITY DEVICES, by R. A. Penfold. Bernard Babani Ltd, London, 1979. Soft covers, 108 x 181mm, 102pp; many diagrams. Price in UK £1.45.

This recent addition to the Babani book range is a practical little volume on burglar alarms, smoke and gas detectors, water and temperature alarms and other security devices. The author is well-known British technical author R. A. Penfold, and he has written with the electronics enthusiast in mind.

The book begins by looking at basic switch activated burglar alarms, the elaboration of these with exit and entry delays, and basic electronic alarm tone generators. It then covers simple infrared detectors, ultrasonic detectors and light detectors, before progressing to other types of security device such as smoke, gas, water and heat detectors.

The practical circuits given are quite simple and straightforward, but at the same time they use CMOS gates and other modern devices. The devices used are also quite readily available in Australia, which should make the book just as valuable here as in the UK.

In short, a worthwhile little book and one which should interest many security-minded hobbyists.

The review copy came direct from the publishers. (J.R.)

Op-amp experiments

THE DESIGN OF OPERATIONAL AMPLIFIER CIRCUITS WITH EXPERIMENTS, by Howard M. Berlin, Bugbook Reference Series volume 4, published by E&L Instruments Inc, Derby, Connecticut, 1977. Soft covers, 152 x 229mm, about 200pp, many diagrams.

Another book in the E&L Instruments' "Bugbook" series, this volume provides a basic introduction to the design and operation of op-amp circuits. As part of the treatment it describes some 35 practical experiments, designed to provide the reader with meaningful experience in using the devices and circuits involved. The author is an electrical engineer with the US Army, and also does technical writing and lecturing.

There are chapters on op-amp basics, linear amplifier circuits, differentiator

and integrator circuits, voltage-current conversion, comparators and rectifiers, generators, active filters, power supply considerations, the Norton op-amp and instrumentation applications.

The approach is direct and down-to-earth, and the text concise. As a result the book seems to be very suitable as either a practical teaching guide for the serious hobbyist or a laboratory text for the college student.

The review copy came from Stewart Electronics, 33 Sunhill Road, Mt Waverley, Victoria 3149. (J.R.)

Simple projects

ELECTRONIC PROJECTS IN THE HOME, by Owen Bishop. Newnes-Butterworth, London, 1979. Soft covers, 135 x 216mm, 88pp; many illustrations. Recommended retail price \$6.00.

One of a series of new Newnes books written for the electronics hobbyist, this one describes 12 small construction projects for use around the home.

Described are a moisture detector, a temperature alarm, an attention flasher, a constant-temperature enclosure for making yoghurt (!), a simple touch switch, a latching touch switch, a delay switch, a door alert, a light-operated switch, a flashing "star" for Christmas trees, a simple process timer and a power pack.

Each of the projects is fairly simple, and suitable for a beginner. They require only a small number of low-cost parts, and the parts are in most cases available in Australia as well as in the UK. The descriptions given are clearly written, and cover not only circuit operation but also physical construction. In short, just about everything a beginner would need to know in order to tackle them with confidence of success.

Not that I think the book will only be of value to the beginner — I suspect that quite a few hobbyists with years of experience behind them will find it of interest. After all, there can be lots of fun and relaxation in building up a few simple projects, particularly if they produce gadgets which are useful around the house.

At the quoted price it seems very good value for money.

The review copy came from the local office of the publisher, but by the time you read this the book should be available at most of the larger book stores. (J.R.)

NEW BOOKS

Just a few of the thousands in stock. Call in or write. Prices subject to fluctuation. Correct at time of going to press

American Radio Relay League



**NEW
1979
EDIT.
NOW
OUT
\$13.95**

AARL Antenna Handbook \$8.00
Coil Winding Calculator: L/C/F Calculator \$4.45

Radio Society Great Britain

Amateur Radio Techniques. Hawker \$9.35
Radio Communication Handbook
Vol. 1 \$21.85
Radio Communication Handbook
Vol. 2 \$18.90

Recent Popular Titles

WORLD RADIO TV HANDBOOK

1979 edition Guide to the World's broadcasting and TV stations NOW OUT \$15.95

Amateur Radio Theory Course — Ameco \$7.80
Beam Antenna Handbook. Orr \$7.00
Best of Creative Computing. Vol. 1 \$12.75
Best of Creative Computing. Vol. 2 \$12.75
Best of Byte Vol. 1 \$15.95
CMOS Cookbook Lancaster \$14.25
Cubical Quad Antennas. Orr \$6.75
Ham & CB Antenna Dimension Charts.
Noll \$3.90
Introduction to Microcomputers. Osborne
Vol. 0 — Beginners Book \$12.55
Vol. 1 — Basic Concepts \$12.55
Vol. 2 Some Real Microprocessors) New Edition
Loose-leaf w/out Binder \$19.00
With Binder \$28.00
Vol. 3 Some Real Support Devices — New Edition
Loose-leaf w/out Binder \$19.00
With Binder \$28.00
Learning Basic Fast. Claude J. DeRossi \$11.95
Microprocessor Interfacing Techniques. Lesea & Zaks \$16.40
Microprocessors from Chips to Systems. Zaks \$16.40
Radio Amateur Antenna Handbook
Orr & Cowan \$9.90
Radio Handbook. Orr. New 20th edition \$26.50
Scelbi Byte Primer. Wadsworth & Helmers \$16.80
Servicing Electronic Organs — Tab \$13.95
Simple Low-Cost Wire Antennas For Radio Amateurs. Orr \$7.00
Truth About CB Antennas. Orr & Cowan \$8.50
Transistor Substitution Handbook
17th Ed \$7.95
TTL Cookbook. Lancaster \$12.70
VHF Handbook for Radio Amateurs.
Brier & Orr \$8.50
World DX Guide — Companion to World
Radio TV Handbook \$9.95
73 Dipole & Long-wire Antennas. Noll \$6.75
73 Vertical Beam & Triangle Antennas \$7.50
1979 Radio Amateur Callbook DX Listings \$19.95
1979 Radio Amateur Callbook US Listings \$19.95
Getting Acquainted with Microcomputers — Frenzel \$11.95
Learning Basic Fast — De Rossi \$11.95
Radio Frequency Testers 77 Instruments you can build — 73 Magazine \$ 7.80
Tune in the World with Ham Radio — ARRL — Complete Kit containing tape cassette, text and workbook \$11.20

MAIL ORDERS BY RETURN

PLEASE ADD 90c per parcel postage (Vic.)
\$1.70 per parcel interstate

TECHNICAL BOOK & MAGAZINE CO.

295-299 Swanston St.,
MELBOURNE 3000
Ph. 663 3951

LANTHUR ELECTRONICS

69 Buchanan Ave, PO Box 162, North Balwyn,
Vic 3104. Ph. 859 4061.

BATTERY SAVER KITS

Will supply dc voltages from 2 to 15. Suitable radios, record players, toys, instruments, etc. You get transformer, rectifier, cap and circuit

One amp size	\$9.25
Plus post Vic	\$1.00
Other	\$2.50
Two amp size	\$12.95
Plus post Vic	\$1.25
Other	\$3.00

BATTERY CHARGER KITS

Will charge 12 volt wet batteries @ 2 amp. You get transformer, rect., ballast resistor and circuit \$10.50
Plus post Vic \$1.00
Other \$2.50

Surplus postage refunded

ELECTRIC MOTOR SPEED CONTROL KITS. Will control brush type ad/dc motors down to stop without loss of torque. Use with hand tools, lathes, potters' wheels, etc. 10 amp, 2400 watt capacity \$10.95
Price includes postage.

LAMP DIMMER KITS

Will control incandescent lamps from full to out. Useful for protection of projection lamps, theatrical, etc. Available with rotary or slider controls. 10 amp, 2400 watt capacity. \$8.95
Price includes postage.

CABINETS. Aluminium suit batt saver kit, 1 amp \$2.95. 2 amp \$3.25. Batt charger kit \$3.25. Speed kits and dimmer kits. Alum \$2.95. Plastic with alum lid. \$1.95.

BILL EDGE ELECTRONIC AGENCIES

115-117 Parramatta Road,
Concord 2137 747 6472.

(corner Lloyd George Ave and Parramatta Rd, Concord)

OPEN SUNDAY (10 am-2 pm) Mon-Fri, 9 am-5.30 pm. Sat 9 am-noon.

PHILIPS SPEAKERS & SPEAKER KITS

DRASTICALLY REDUCED:

AD12K12 12in 3 way kit	\$298.00 Pair
ADBK30 8in 3 way kit	\$199.00 Pair
AD0160/T8 Dome Tweeter	\$12.88 each
AD5060/SQB Mid Range	\$18.88 each
AD8066/W8 Hi Fi Woofer 40w	\$22.50 each
AD12100/W8 12in Hi Fi Woofer 40w	\$63.88 each
ADF500/4500/8 Crossover	\$19.90 each
ADF600/4000/8 Crossover (includes attenuators)	\$57.55 Pair

(OPEN SUNDAY)

PRODUCT RANGE INCLUDES: Sound equipment, automotive accessories, intercoms, kits, test equipment, books, burglar alarm systems, power supplies and transformers, TV aerials and accessories, communication accessories, tools, wires and cables, coils and formers, copper clad board, breadboards, matrix & strip board & accessories, scotchcal, hardware, dimmers & timers, fuses, terminal strips, bezels, plugs and sockets, switches, relays, capacitors, resistors, potentiometers, semiconductors and valves. (Open Sunday)

Some DICK SMITH products available at catalogue prices. As you are dealing direct with owner we are very enthusiastic to give you the best possible service. (Open Sunday)

MAIL ORDER Post \$1 + 5% of order value up to \$80 and thence a flat \$4.00
HEAVY ITEMS SENT FREIGHT ON THROUGH CARRIER

INFORMATION CENTRE

PLAYMASTER TWIN 25: I have discovered a discrepancy between the description of operation and the circuit diagram. You said that a .0022uF capacitor has been fitted from the collector of T10 to 0V to reduce the open loop bandwidth from 500kHz to 40kHz to ensure stability with overall feedback applied. The capacitor however, upon inspection of the PCB, is in fact fitted between the collector of T9, a constant current source, and the 0V line.

I would appreciate it if you would let me know if this is an error or just an unpublished alteration to the circuit. In all other respects I am more than pleased with the performance. (R. A., Melton, Vic.)

● This same query was raised in a letter featured in an article on feedback from readers on the Playmaster Twin 25, featured in September 1976. While the .0022 is physically connected to the collector of T9, it is effectively connected to the collector of T10, by virtue of the 0.1uF capacitor shunting T15. So the .0022 does have the effect of rolling off the high frequency response of T10 and thus, the overall open loop bandwidth of the whole amplifier.

COORDINATED UNIVERSAL TIME: What is Coordinated Universal Time as announced by WWV? Is it just a "Yankee" version of good old Greenwich Mean Time? Several encyclopedias I have referred to fail to answer this. (D. K., Waverley, NSW.)

● Coordinated Universal Time is not a "Yankee" version of Greenwich Mean Time. Indeed, it was arrived at by world agreement and as the name suggests, it is used universally. Because the science of timekeeping is so complex any explanation relating to it must of necessity be somewhat simplified.

In recent times, time measuring techniques have been developed which are many orders more accurate than the traditional method based on observations of the earth's rotation with relation to the sun and more distant stars. There are several time scales, and the one now generally used as a prime basis exploits certain peculiarities of the atom of caesium. After centuries of observations by astronomers, the length of a year, and so a day and, finally, a second has been determined with some accuracy. To fit in with this assessment of the duration of the second, the frequency of the caesium atom has been determined as 9,192,631,770Hz.

This has become the standard of

reference and it is stable to a very high order of accuracy, far beyond that of the earth's rotation, which has a number of variables. But the rotation of the earth on its axis determines our natural day and, because of the variables just mentioned, the yearly average length of the day will also vary slightly and so fall out of precise step with our new frequency standard. In order to avoid any undue accumulation of error between the standard and the average solar day, "leap" seconds are added or subtracted as required from time to time. Generally, these adjustments are made on the first day of January and sometimes at other times agreed to internationally. As a matter of interest, a leap second was added last January and virtually nobody was aware of it.

This adjusted time (by means of leap seconds), to which all civil clocks are set, is called Coordinated Universal Time and is almost the same as the older Greenwich Mean Time.

SPEAKER ENCLOSURES: I would like to design a bass reflex speaker but the information I have is not very suitable. Has "Electronics Australia" published any articles on this? Also, could you supply a formula for vented systems, and for ported systems if possible? The speaker resonance is 44Hz and the volume is 6cu. ft.

On another note, I have an idea on how to damp speaker resonance. It is as follows: (Editorial note: The writer gives a circuit of an R/L/C series network in parallel with the vice coil, plus the calculations showing how the network would shunt the voice coil at the resonant frequency.) Would this idea work? (P. S., Ipswich, Q.)

● Most of the old charts and tables to do with vented (or ported) enclosure design are suspect because they are based only on driver diameter and resonance and ignore a vital factor, namely driver "Q". It was for this reason that many vented (and ported) systems sounded unduly boomy. Furthermore, attempts to eliminate the boom by damping the vent or the enclosure itself was applying the remedy to the wrong place! The correct approach is to start with a driver which has the right diameter, resonance and "Q" so that it can be mated with a convenient enclosure to give the target results. In short, the system needs to be designed as a whole. How to go about it has been worked out by Australian engineer Neville Thiele and his approach has

been adopted worldwide and expanded upon. However, it is an engineering level exercise, which cannot readily be reduced to simple tables or charts, and applied to any over-the-counter driver. We can only suggest that you do th best you can with the driver and data you have and fiddle the performance by trial and error. If you want to damp the driver resonance, pin one or more layers of absorbent material closely over back of the housing so that the rear pressure wave has to pass through it. We would not suggest R/L/C damping across the speaker terminals.

FREQUENCY METER: I have just completed building the new 40MHz Digital Frequency Meter (File 7/F/24,25, August, September 1978) and it is operating very well. One problem, however, is that now I am not sure of the possibilities or applications of such a meter. Could you please send me ideas, particularly on connecting the input of the meter to an amateur transceiver in the best possible way. (B.W., Narooma, NSW).

● We are glad you have been successful with the Digital Frequency Meter. As you become more involved with electronics, whether it be indigital circuitry, audio, or amateur radio, you will find numerous uses for your new instrument. If you wish to measure the transmit frequency of a transmitter the easiest was is to connect a short length of wire to the centre-pin of the input socket and place it close to the antenna or dummy load of the transmitter.

NOTES & ERRATA

5V/10A (MINI-BRUTE) POWER SUPPLY (November 1977, File No 2/PS/43): The 100 ohm resistor between the bases of Tr2 and Tr3 and the output was omitted from the wiring diagram.

MAKING USE OF AUDIO INDICATORS (April 1979, File No. 1/MS/18): The AI254 cannot be substituted for the X50W12A because it is not waterproof; however, the X70W06 can be used. Also there is 15% sales tax on audio indicators; the X70W06 is \$9.78 and the X50W12A is \$15.99. The postage on the latter is \$1.20, the mass being approximately 150 grams.

LOW COST PRINTER FOR MINI SCAMP (April 1979, File No. 2/CC/37): The author has advised that there are two errors in the message sending routine listing. At location X'10 the data field should be 06, not 00; at location X'23 the data should also be 06, in place of 0C as shown.

FASTER DUMPING AND LOADING FOR THE 2650 (April 1979, File No. 8/M/36): The hex listing on page 70 contains an error which is repeated six times. At location X'3E0A and that immediately following, the content of X'9CFE should be changed to 9D00. This should also be done at X'3E25, 3E2C, 3E39, 3E67, 3E78 and 3E9F.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

PROJECT QUERIES: Members of our technical staff are NOT available to discuss individual projects, either in person at our office or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy

answers, undertake special research or discuss design changes.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

DREAM . . . from page 88

Check that the MPU address lines are all HIGH (except A0) when RST is LOW (hold down [RST]). Before trying a new MPU chip, note that any faulty device on the address bus might be holding a bus line LOW (incl. ICs 5, 6).

Assuming the actual reset circuit is operating, but CHIPOS refuses to spring to life (i.e. no 4-digit readout on screen, or no keypad response), the fault is almost certainly in EPROM or RAM, or the associated select logic. Less likely is a bad PIA, but this can be checked. If you have a good display, but no I/O response, check the PIA initialization. After resetting, PBO is HIGH, PB1-PB7 are all LOW, PA0-PA3 HIGH, and PA4-PA7 LOW. When a hex key is pressed, the PAX lines will reverse

momentarily, if CHIPOS and the PIA are both operating.

If you have an acquaintance who is also constructing a DREAM-6800, see if you can arrange to borrow the MPU, RAM, EPROM, and PIA chips. One by one, substitute a chip for one of your own.

In conclusion, it must be said that, provided due care is taken in construction, the probability of success at switch-on is very high. Readers who are contemplating the project, should not be put off by the trouble-shooting section, which was included to help isolate rare, hard-to-find bugs. Problems of a minor nature should be able to be handled by enthusiasts with a moderate amount of experience, with the help of the theory-of-operation section.

(To be continued)


RADIO DESPATCH SERVICE

THE SPECIALIST STORE

869 GEORGE STREET, SYDNEY, NSW 2000. (NEAR HARRIS STREET)
PHONES 211 0816, 211 0191

CS-1560A 130mm DUAL TRACE 15MHz TRIGGERED SWEEP OSCILLOSCOPE

**SPECIAL
\$638.25**

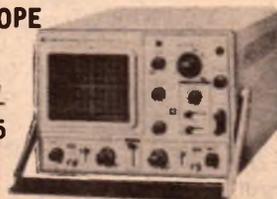


successfully realized with the use of ICs throughout ● A vertical amplifier provides as wide a bandwidth as dc to 15 MHz, as high a sensitivity as 10mV/div and a low input capacitance ● A sweep rate extends from 0.5 usec/div to 0.5 sec/div in 19 ranges. Further TV vertical and horizontal syncs are available for measuring video signals and with its x5 magnified sweep, its range of application is extremely wide ● Very easy X-Y operation of high input sensitivity for Lissajous measurements ● Dimensions: 260(w) x 190(h) x 385(d)mm. Weight 8.4kg

TI 59 CALCULATOR PRICE: \$247.00 plus s/tax
TI PC100 PRINTER PRICE: \$213.57 plus s/tax

**CALCULATORS
TEXAS INSTRUMENTS**

	Excl. S. Tax	Incl. S. Tax
T.I. MBA	73.00	80.95
T.I. Programmer	53.60	59.00
T.I. 5025	73.85	81.76
T.I. 5220	162.10	179.80
T.I. 5100	44.80	49.60
Library Modules	32.00	35.30
Blank Mag Cards	14.63	15.95
TP 30250 (3 Rolls)	11.39	12.50
PC 100A Printer	213.57	236.00
T.I. 5040	114.10	126.33

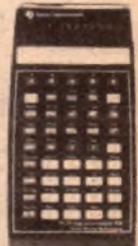

DELIVERY/MAIL ORDER ADVICE
Please allow \$1.00 to cover packing on all orders.
POST: 5 per cent of order value up to \$80 and a flat \$4 over \$80.

OPEN: MON-FRI 8.00 am-5.30 pm

Thursday late night shopping until 8.30 pm, Saturday 8.00 am-11.45 am.

UP to

40% OFF
LAST YEARS PRICES

7400 SERIES TTL

7400	\$0.20	7440	\$0.25	7496	\$0.90
7401	0.20	7442	0.65	7496	1.00
7402	0.20	7446	0.90	74100	1.50
7403	0.20	7447	0.90	74107	0.50
7404	0.25	7448	0.90	74109	0.55
7405	0.25	7450	0.25	74121	0.50
7406	0.40	7451	0.25	74122	0.60
7407	0.40	7453	0.25	74123	0.60
7408	0.25	7454	0.25	74125	0.70
7409	0.25	7460	0.25	74126	0.70
7410	0.20	7470	0.45	74132	1.00
7411	0.28	7472	0.45	74141	1.25
7412	0.28	7473	0.45	74145	1.10
7413	0.40	7474	0.45	74151	0.90
7414	0.60	7475	0.60	74153	0.90
7416	0.50	7476	0.40	74154	1.30
7417	0.50	7480	0.80	74157	0.85
7420	0.28	7482	1.00	74160	1.10
7421	0.30	7483	1.00	74164	1.30
7423	0.35	7485	1.30	74165	1.30
7425	0.35	7486	0.45	74174	1.30
7426	0.35	7489	2.00	74176	1.10
7427	0.35	7490	0.40	74177	1.10
7430	0.25	7491	0.90	74184	2.20
7432	0.35	7492	0.55	74185	2.20
7437	0.35	7493	0.40	74192	1.00
7438	0.35	7494	0.90	74251	1.30

CMOS 4000 SERIES

4000	\$0.25	4020	\$1.30	4050	\$0.50
4001	0.25	4021	1.30	4051	1.00
4002	0.25	4022	1.30	4052	1.00
4006	1.35	4023	0.25	4053	1.00
4007	0.25	4024	0.90	4060	1.50
4008	1.20	4025	0.30	4066	0.75
4009	0.70	4027	0.70	4071	0.35
4010	0.70	4028	0.95	4072	0.35
4011	0.25	4029	1.20	4073	0.35
4012	0.25	4030	0.45	4075	0.35
4013	0.55	4035	1.50	4081	0.35
4014	1.20	4040	1.20	4082	0.35
4015	1.15	4042	1.10	4510	1.30
4016	0.50	4043	1.00	4511	1.30
4017	1.20	4044	1.00	4516	1.30
4018	1.20	4046	1.50	4518	1.30
4019	0.45	4049	0.50	4520	1.30

LOTS MORE — Transistors, Zeners, Capacitors, Switches, etc. Just write for your free CATALOGUE

P&P 70c Minimum — Please allow more for heavier items

LINEAR ELECTRONICS

MAIL ORDER ELECTRONIC COMPONENTS
PO BOX 264 PUNCHBOWL 2196

After-Hours in Adelaide

POSITRONICS

ELECTRONICS COMPONENTS

Monday, Wednesday, Thursday
and Friday to 8 pm.
Saturday and Sunday
afternoons to 5 pm

**13 MCGOWAN ST.
POORAKA, SA**

Marketplace

FOR SALE

FREE YES ABSOLUTELY FREE — pak of semiconductors for the experimenter. Send large S S A E for your pak now! A E Cooling, 6 Trimmer Rd., Elizabeth South, SA 5112

SPEAKER BOXES Hand-made. Excellent acoustically. Write: SHERWOOD ELECTRONICS, PO Sherbrooke 3789

AUSTRALIAN RADIO DX CLUB — Published over 360 pages of DX notes during 1978. The official news source for Radio Australia's DX Programme for over 14 years: 1979 is World DX Youth Year with special introductory membership fee for people under 18 years old. For full details write to PO Box 67 Hightett, Victoria 3190, or PO Box 79 Narrabeen, NSW, enclosing a 20c stamp


DENCO COILS dual purpose red, white, blue, yellow — ranges 1, 2, 3, 4, 5 @ \$3.67 ea. Green coils \$4.00 ea. Transistor coils, ranges 2, 5 — all colours \$3.80 ea. Screening cans 38c. Noval Coil sockets 35c. Hobipak P.O. Box 224, South Carlton, Victoria, 3053 (Room 92B/113 Swanston St, Melbourne)

AUTO TRANSFORMER's 240-110 Volts 6 AMP primary \$22.50 each. Geared motors 1/10 HP 120 RPM 110 Volts, \$8.00 each. Micro switches, 50c each. Pana-Flex Eng 7 Inman Rd, Dee Why, Ph. (02) 98 5848

KEYBOARD KITS — Full Ascii Output (Model 756) only \$63.50. Plus numeric key pads \$10.50 extra. Ph. (03) 347 5513 or send for free literature. Hugh R Martin P.O. Box 65, Nth Carlton, Vic. 3054

NOVICE AMATEUR RADIO STUDY PACKAGES still available. See p108 August 1978 E.A. for review or p66 October 1978 E.A. for details. Also **FULL A.O.C.P. STUDY materials & MORSE CODE TAPES** from 5wpm to 20wpm. Write for free illustrated brochure to Ann Davis, P.O. Box 200, Alderley, QLD 4051

TIME CLOCKS SANGAMO

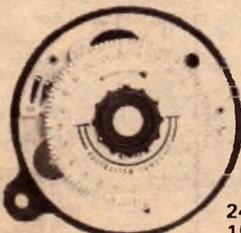

LESS
DAY OMIT
DEVICE
\$13.50

WITH
DAY OMIT
DEVICE
\$16.00

240V 50 cs
15A Contacts

Used tested and guaranteed
PACK & POST N S W \$2.00
Vic & Qld., S.A. \$2.90, W.A. \$3.40

CLOCK DISPOSAL CO.
P.O. Box 147
LINDFIELD, N.S.W. 2070

RADIO SERVICE MANUALS Vol 9 1950 & Vol 12 1953 published by Strand Press, B'bane — Pain (02) 452 5172

WANTED

RIBBON CABLE — 10 way 0.1in centres 0.6mm solid core ideal PCB interconnections — 69c/mtr + 80c pp SAE for sample and bulkrates JATRONICS, PO Box 31 Engadine 2233

OSCILLOSCOPE in working order with 50 mV/DIV vertical sensitivity or better. Contact J. Crago, 37 Bremen St., Hemmant 4174. Ph. (07) 390 5154 A.H.

SUPER 12 WHARFEDALES, Goodmans or other similar quality speakers for cash. Ph. (03) 95 0179

READER SERVICE

SERVICE to most brands JAPANESE. Cassette recorders, car cassettes, Tape Decks, radios, etc. incl. National & JVC. We also repair Electronic digital clock radios, Video Games, both B&W, colour PETER G BROUGHTON, 99 Sussex St (Inr King Street) Sydney, Ph. (02) 29 3845

CORRECTION

Futuretronics advertisement in our May issue inadvertently omitted to carry the number "3" preceding MONTHS WARRANTY

DISPLAY ADVERTISEMENTS IN MARKETPLACE are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm. **CLASSIFIED RATES** \$2 per line per insertion payable in advance. **Minimum two lines.**

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

ADDRESS all classified orders, copy, enquiries, etc., to: The Advertising Manager, **ELECTRONICS Australia**, Box 162, Beaconsfield 2014.

THE "ELECTRONICS AUSTRALIA"

LOG BOOK


**FOR: RADIO AMATEURS
DX LISTENERS
CB OPERATORS** **\$2.95**

From "Electronics Australia", 57-59 Regent St, Sydney OR by mail order from PO Box 163, Beaconsfield 2014. Price includes postage.

ELECTRONICS CENTRE


BARGAIN PRICES • PERSONAL ATTENTION • SLICK MAIL ORDER SERVICE • SATISFACTION •

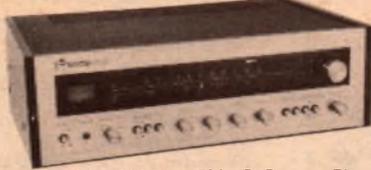RANK ARENA SUPERSONIC AM-FM STEREO RECEIVER/AMPLIFIER



12+12W. 8 ohms. 88-108MHz. FM B/C am. Phono. aux. tape. headphones. Hi/Lo Filters, loudness, muting controls.

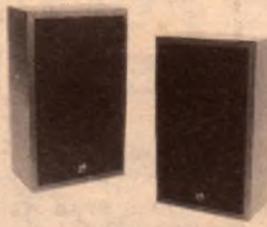\$147.00 PP NSW \$2.75. VQ \$3.75. T SA \$4.75. WA NT \$6.00



RANK ARENA 2-WAY SPEAKER SYSTEM

**LESS THAN
½ PRICE**

8 OHMS 10 watts teak cabinets 18¼" H
11" W 9½" D
Pack & Post NSW **\$2.00** VIC QLD **\$3.50**
SA TAS WA NT **\$5.50**

\$42.00 PAIR



SOUND SYSTEMS SLEEK AND SLENDER CLUBS • SCHOOLS • HALLS • ETC.

Black Vinex Covered Cabinets. Rugged and Attractive
Interboard Lined for Richer Sound. Excellent Frequency Response
8 or 16 ohms. Floor or wall mounting.

3 MODELS WITH 4 HEAVY DUTY SPEAKERS IN EACH
30 WATTS RMS 40 WATT RMS 50 WATT RMS
\$59.00 \$69.00 \$79.00

FREIGHT ROAD, RAIL OR AIR. FON.

GEL-CELL RECHARGEABLE BATTERIES



6 VOLT 1.2AH **\$4.95** EA PP NSW 80c
INTERSTATE \$1.20



12V 1.2AH (Two 6V batteries supplied)
complete with 240V plug-pak charger **\$10.95** PP NSW \$1.75
INTERSTATE \$2.50

Batteries are in fully sealed high impact, moulded case 3" x 7/8" x 2".

C-CORE TRANSFORMERS



LOW NOISE. HI EFFICIENCY

PRIMARY 240V 50Hz
MODEL JT266 0-18V 8A **\$22.95**
MODEL JT235 26.0-26V4A **\$21.95**
MODEL JT248. 10V. 10A **\$22.95**
MODEL JT249 0-15V
8.5-0-8 5V 4A
FOR MICRO PROCESSOR **\$23.95**
MODEL JT274 10V 10A
2 x 12V 1A **\$22.95**
MODEL JT 253A
0-18V 30A PEAK **\$41.95**
P.P. MODEL 253A NSW **\$3.50** V.Q.T.
\$5.50 SA WA NT **\$7.00**
P.P. ALL OTHER MODELS
NSW **\$2.95** V.Q.T. **\$3.75**
WA SA NT **\$5.50**

CLARION CAR SPEAKERS



Twin cone 10W 4 ohms
Air suspension, big magnet.
\$29.95 pair
PP NSW \$1.50. Interstate \$2.25



AWA 12" SPEAKER SPECIAL

MODEL 12UA 30 WATTS RMS
Freq. 35-6000 Hz
15 OHMS **\$17.50**
8 OHMS **\$19.50**
P.P. NSW \$2.00 INTERSTATE \$2.75

AWA-ETONE SPEAKERS

High performance, high power. 30cm.
38cm, 46cm. Send SAE for specs and
extra low prices.

TRANSISTOR PACKS GUARANTEED

Top quality, clearly marked. N.B
Minimum order \$5.00.
BC559, BC549, BC558, BC547,
BC548, BC177, 2N4248, 2N4250,
TT638A, AY1110, BC327/337,
2N3642 TT1002 = BF115, 2SB367,
10 for \$1.40

BD135/136 10 for \$2.50
BD139/140 10 for \$4.95
2SD200 = BU205, 10 for \$12.00.
8UX80, 4 for \$19.00.

I-C PACKS

UA301, UA741, UA709, UA723, 7473,
7450, 7451, 10 for \$1.35
SN7490 10 for \$2.85
LM382N 10 for \$12.50.
P-P NSW 75c. Interstate \$1.25

GEARED MOTOR

240VAC 50Hz 3W



12 RPM. Plenty of torque. With Cam
and N/O N/C microswitch. 36 switch
contacts per min. OA size. 65 x 60 x
35mm.

\$2.50 P+P 50 cents

SOLDERING IRON


Especially for mini components, transistors, IC, extra fine tip, lightweight,
240vac. 15 watt

\$12.95
PP NSW 75c Interstate \$1.25

SERVICE

Moderate charges — Repairs
guaranteed. Radios, Tape
Recorders, Cassettes, Amps.

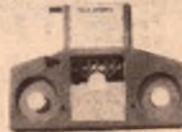• SUPER SCOOP • (LAST OFFER — FACTORY CLOSED) TELESPORTS SUPER 6TV GAMES



COMPLETE KIT \$11.95 INCLUDING AY3-8500 CHIP

• THE ONE WITH THE GUN — AS SEEN ON TV • KIT INCLUDES
FACTORY ASSEMBLED PRINTED CIRCUIT BOARD WITH
TRANSISTORS, RESISTORS, CAPACITORS, I-C, AND OTHER
COMPONENTS PROFESSIONALLY SOLDERED • CABINET •
SPEAKER • GUN • POTS • SWITCHES • KNOBS • CIRCUIT • 4
BAT AND BALL GAMES • 2 BAT/BALL SIZES • 2 ANGLES • 2
SPEEDS • P+P NSW \$1.75. INTERESTATE \$2.75
Refer Nov. 78 EA for Review.

75 ohm COAX CABLE

Dia. 6mm Cap 11pf per 34cm Very
flexible. Annealed, braided copper shield.
Black PVC covered.
50 METRES **\$ 8.00**
100 METRES **\$14.00**
Fon. Road, Rail, Airfreight

REFLEX TRUMPET SPEAKER



Indoor/outdoor, weatherproof. 8 watt. 8
ohms. Size. 110 x 85 x 125mm. Ad-
justable mounting bracket.
\$8.95
PP NSW 75c Interstate \$1.25

CERAMIC STAND-OFF INSULATORS



O/A dim. 75h x 75 x 55mm
\$1.50 ea
2 for **\$2.50**

Egg Insulators, 10 for **\$4.95**,
PP NSW \$1.00. Interstate \$1.60


STEREO RECORD PLAYER



240V 50Hz separate 2-pole motor,
chrome turntable, 6¾" dia. with plastic
mat Chrome tubular pick-up, imbal
mount and rest. Ceramic cartridge
PP NSW \$1.25. Interstate \$1.60.

Don't let your valuable issues go astray

ELECTRONICS AUSTRALIA BINDERS

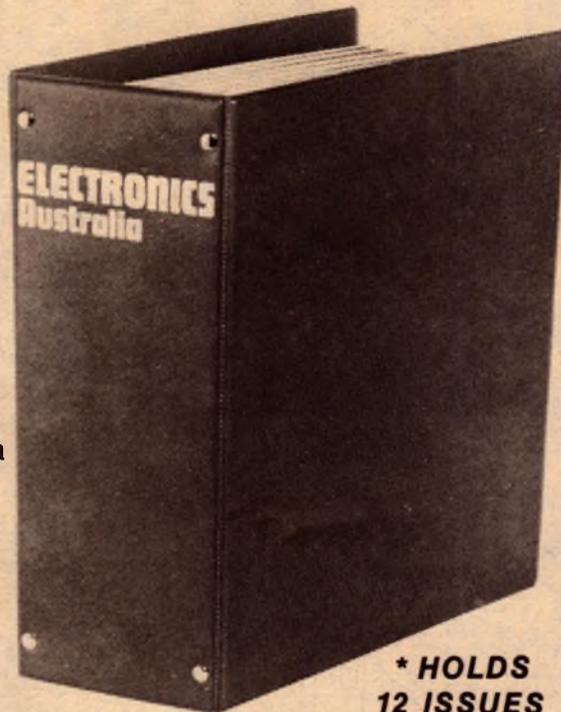

These attractive binders finished in brown plastic with gold lettering will keep your back issues of Electronics Australia neat and tidy.

*** HOLDS 12 ISSUES**

Available from
Electronics Australia,
 57 Regent St, Sydney. PRICE: **\$4.50**
 or by mail order from Electronics
 Australia, P.O. Box 163, Beaconsfield 2014.
 PRICE **\$5.50** NSW; **\$6.50** other states;
 or 6 for: **\$28.00** NSW; **\$30** other states.

*Magazines prior to April 1971 will need to be trimmed to fit binder

ADVERTISING INDEX

ADVERTISER	PAGE
A & R Soanar	74
ASP Microcomputers	80
Ace Radio	127
Adaptive Electronics Pty Ltd	89
Adcola Products	37
All Electronic Components	53
Audo Telex Communications Pty Ltd	36
Audio Egnineers Pty Ltd	30
Australian Film & TV School	121
Australian Hi-Fi Publications Pty Ltd	64, 65
Bail Electronic Services	107
Bright Star Crystals	113
Butterworths Pty Ltd	122
Byte Shop, The	95
C & K Electronics (Aust.) Pty Ltd	9
Cash-More Etrnerprises Inc.	104
Cema (Distributors) Pty Ltd	Insert
Chapman L. E.	116
Classic Radio	63
Clock Disposal Co	126
Color Tubes International	25
Computerware	97
Convoy International Pty Ltd	40
Cunningham R. H. Pty Ltd	34
Davis Ann	126
Deitch Bros	120
Dick Smith Electronic Group	
22, 23, 69, 76, 77, 89, 110, 116	
Dindy Marketing (Aust.) Pty Ltd	26
E. D. & E. Sales Pty Ltd	53
Economic Digital Control Pty Ltd	86
Electrocraft Pty Ltd	101
Electron 2000	119
Electronic Agencies	124
Electronic Calculator Discounts	9
Elmeasco Instruments Pty Ltd	20
General Electronic Services Pty Ltd	102
Hagemeyer (Aust.)	OBC
Harmen Australia Pty Ltd	98
Honeywell	117
Imark Pty Ltd	73
Invictos Trading Co Pty Ltd	43
J. R. Components	92
Lafayette Electronics	79
Lanthur Electronics	124
Linear Electronics	126
Looky Video	97
National Panasonic (Aust.) Pty Ltd	18C
Parameters Pty Ltd	16
Pennywise Peripherals	96
Philips	2, 15, 33, 114
Positronics	126
RCS Radio	55
Radcom Pty Ltd	109
Radio Despatch Service	125
Radio Parts Group	35, 58
Rod Irving Electronics	93
Rowe H. & Co	100
S. M. Electronics	80
Sangster A	88
Scope Laboratories	6
Sigma Data Corporation (A'Asia) Pty Ltd	48
Stanton Magnetics, Inc	28
Stewart Electronics	84
Stotts Technical College	19
TEAC Aust Pty Ltd	38
Tandy International Electronics	46
Tasman Electronics	37
Technical Book & Magazine Co	123
Trio-Kenwood	IFC
Vesco Electronic Supplies	50
Vicom International	27, 108
Video Technics	50
Warburton Franki	70, 105
Wireless Institute of Australia	111

SUBSCRIPTION SERVICE



Subscription Rates
\$18.00 per year within Australia.
\$A21.00 per year elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon with your remittance to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001. Subscription will start with first available issue.

Name
 Address
 Postcode Enclosed is for years

THE JVC RECEIVER.

Every bit as revolutionary as they look, and then some.

In our case, looks are never deceiving. Because all our new DC integrated stereo receivers combine unprecedented, revolutionary styling with unique electronic design features that reflect JVC's more than 50 years' experience in audio development and innovation.

DC Power Amplifier Design

All four new JVC receivers feature DC amplifier circuitry. They offer virtually distortion-free performance (0.03% THD) throughout the entire audible spectrum. As a result, the sound you hear is clearer, cleaner and crisper. In addition, your speakers are protected with the Triple Power Protection circuit and you can monitor output wattage with dual power meters. Choose from 120, 85, 60 and 35 watts/channel.*

SEA all the way

All four receivers offer JVC's exclusive built-in SEA five-zone graphic equalizer for more complete control of



the music spectrum than conventional tone controls. You can attenuate or accentuate any of five separate musical bands, and as an added feature, we've incorporated a special button so that the SEA circuit can be switched to your tape deck.

Pushbutton Source Selectors

A horizontal panel of pushbuttons provides total control over all functions. And brilliantly illuminated LEDs instantly indicate the program source. Professional-type slider controls set volume and balance. Combine all these exclusive features with high sensitivity and tuning precision, thumb control tuning wheel and accurate dual-metering and you'll see just how revolutionary the new JVC DC integrated stereo receivers are. Play one at your JVC dealer soon.

For details on all JVC Hi-Fi Equipment, write to JVC Advisory Service, Box 307, North Ryde, N.S.W. 2113.



Top JR-S401
Left JR-S201 Right JR-S301

JR-S 401 (top), JR-S 201 (bottom left) & JR-S 301 (bottom right)

For pure Hi-Fi entertainment!



the right choice



JR-S501 * @ 8 Ohms, both channels driven from 20Hz-20 KHz, with no more than 0.03% THD.

TECHNICS. THE TOTAL PERFORMANCE RECEIVERS.



Examine the exciting line of Technics receivers. Clean, functional styling and audible quality is evident in each. Total harmonic distortion is extremely low — an incredible 0.04%. You don't have to buy Technics most powerful receiver to get the most sophisticated circuitry. Because every Technics model is direct-coupled OCL (output capacitor-less) this contributes to tight, solid bass response right down to the very low frequencies. You'll discover greater dynamic range in your records due to super-quiet signal-to-noise ratio. And FM reception is outstanding, thanks to phase locked loop IC's, flat delay filters and a frequency response that's both flat and wide.

If sound and performance are your priorities in a receiver, then the Technics range deserves your consideration.

Model	Min. R.M.S. Power per Channel into 8 ohms from 20Hz-20kHz	T.H.D. at Rated Power (Max.)	FM Sensitivity	S/N Ratio
SA-400	45 Watts	0.04%	1.9uV	78db
SA-300	35 Watts	0.04%	1.9uV	78db
SA-200	25 Watts	0.04%	1.9uV	78db

Shown above is Technics receiver model SA-300

For a National Technics catalogue please write to:
Technics Advisory Service, P.O. Box 278, Kensington, N.S.W. 2033.

 **Technics**
hi-fi