

# ELECTRONICS

## AUSTRALIA

VIDEO, HI-FI &  
COMPUTERS

FEBRUARY 1981  
AUST \$1.60\*  
NZ \$1.70

**Special Feature:**

**NEW BREED  
COLOUR  
CAMERAS  
AND VCRs**

**6A BATTERY  
CHARGER**

**DUAL-TRACE  
CRO ADAPTER**

**GUITAR  
FUZZ BOX**



SONY®



# Heavy.

Introducing another Sony only. The MDR series open-air headphones. The smallest, lightest stereo headphones available today. Or tomorrow.

With our lightest at 40 grams, you will barely know you're wearing them. Yet the sound is dynamite.

Through a remarkable new audio breakthrough, our engineers have succeeded in reducing big-headphone technology down to the size of your listening channels.

The MDR series headphones' airy spaciousness delivers absolute clarity through an ultra-small driver

unit that produces more than three times the energy of conventional circuits. And a new high-compliance diaphragm accurately reproduces the 20 to 20,000Hz bandwidth and improves low-range response.



That means you can listen to the heaviest of music for hours. Lightly. And know that you're hearing every nuance of the original recording from deep bass to the highest treble.

Listen to our new MDR series headphones. They're light. And heavy.

STEREO HEADPHONES  
**MDR**

# ELECTRONICS

## AUSTRALIA

Volume 43, No. 2  
February, 1981

**AUSTRALIA'S HIGHEST SELLING ELECTRONICS MAGAZINE**



This easy-to-build Oscilloscope Switch will increase the versatility of your single-trace oscilloscope by providing dual-trace operation. Find out how to build it on p40.



Having trouble with flat batteries? Our new battery charger is capable of charging 6 or 12V batteries at currents up to 6A and features full overload protection. Details p48.

COMING NEXT MONTH — Find out what's coming by turning to p29.

### On the cover

Entertainer Peter Allen cools off as he displays some of the latest National Panasonic video gear. Don't miss our special feature articles on the coming revolution in home video electronics starting on p8. [Photograph courtesy National Panasonic (Aust) Pty Ltd and George Patteson Pty Ltd].

### FEATURES

- SPECIAL: THE COMING ERA IN HOME VIDEO — 1** *New-generation VCRs* . . . . . 8  
**SPECIAL: THE COMING ERA IN HOME VIDEO — 2** *Colour Video Cameras* . . . . . 14  
**GLASS BOTTLES WITH LIGHTS IN THEM** *One man's "wireless" collection* . . . . . 20  
**TWENTY-FIVE YEARS FROM NOW** *A cautious look at the future* . . . . . 22

### HIFI TOPICS AND REVIEWS

- AUDIO/VIDEO ELECTRONICS** *Video Disc: Pioneer wants to be No. 1* . . . . . 31  
**HIFI REVIEW** *Sony PS-X75 automatic turntable* . . . . . 37

### PROJECTS AND CIRCUITS

- BUILD AN OSCILLOSCOPE SWITCH** *Dual-trace facilities for your CRO* . . . . . 40  
**FULLY-PROTECTED 6-AMP BATTERY CHARGER** *For 6 & 12V batteries* . . . . . 48  
**PLAYMASTER MOSFET STEREO AMPLIFIER** *Chassis wiring details* . . . . . 54  
**SIMPLE FUZZ BOX FOR ELECTRIC GUITARS** *Adds interest to your music* . . . . . 64  
**MINISPOT 455KHZ SIGNAL GENERATOR** *For receiver IF alignment* . . . . . 76  
**RS-232C PRINTER INTERFACE FOR THE SYSTEM-80** . . . . . 82

### MICROCOMPUTERS

- TANDY'S TRS-80 POCKET COMPUTER** *An in-depth review* . . . . . 88  
**CURVE-PLOTTING WITH YOUR SORCERER** *High resolution, x & y axes* . . . . . 92  
**COLUMN 80** *Interpreters and compilers explained* . . . . . 121  
**MICROCOMPUTER NEWS & PRODUCTS** *DREAM 6800 expansion kits* . . . . . 122  
**SOFTWARE REVIEW** *Microsoft editor/assembler* . . . . . 136

### AMATEUR RADIO, CB SCENE, DX

- AMATEUR RADIO** *The need for a better public image* . . . . . 97  
**CB SCENE** *CB: each of us has a story to tell* . . . . . 102  
**SHORTWAVE SCENE** *Radio Vemarana heard during Santo rebellion* . . . . . 104

### COLUMNS

- FORUM** *Non-approved transceivers and telephones* . . . . . 26  
**THE SERVICEMAN** *Bolts and washers can drive a serviceman nuts!* . . . . . 70  
**RECORD REVIEWS** *Classical, popular and special interest* . . . . . 113

### DEPARTMENTS

- EDITORIAL 3 — NEWS HIGHLIGHTS 4 — CIRCUIT AND DESIGN IDEAS 74 — LETTERS TO THE EDITOR 94 — NEW PRODUCTS 106 — BOOKS AND LITERATURE 118 — INFORMATION CENTRE 138 — MARKETPLACE 142 — NOTES AND ERRATA NIL**

# LOW COST PORTABLE OSCILLOSCOPES THAT DON'T COMPROMISE ON PERFORMANCE!



**TTM303**  
**15MHz**  
**Mains and Battery Operation**

## TTM303

The TTM Dual Trace Portable Scope Model 303 offers a high sensitivity of 5mV/DIV with DC to 15MHz bandwidth. The 3-inch CRT with 1.5kV regulated accelerating voltage gives a clear bright display.

This Portable Scope operates from standard line voltage (90 to 260V) or from the internal rechargeable Ni-Cad battery, that provides 2 hrs operation before recharging is required. It also operates from any external DC voltages of 11 to 30V, e.g. car batteries, standard 'C' size cells, etc.

## SPECIFICATIONS:

**SENSITIVITY:**- 5mV to 10V/DIV 1-2-5 step with fine control. **BANDWIDTH:**- DC: DC to 15MHz (-3dB). **RISETIME:**- 24nS. **OPERATING MODES:**- CH-A, CH-B and Dual Trace TIME BASE:- 1 $\mu$ sec to 500 mS/DIV with fine control. **EXPANSION:**- x5 at all ranges. **X-Y OPERATION:**- X-Y mode is selected by SWEEP TIME/DIV switch. CH-A: Y axis. CH-B: X axis. **POWER REQUIREMENTS:**- AC: 115/240V DC: 11-30V, 7.2VA. Battery: Ni-Cad Battery (up to 2 hour operation). **SIZE:** 113 (H) x 223 (W) x 298 (D) mm approx. **WEIGHT:**- 4.6kgs.



**BS310S**  
**Mains and Battery Operation**  
**2mV Sensitivity**  
**Add/Subtract Feature**

## APPLICATION BS310S

The dual trace Model BS-310 employs a high brightness 95mm CRT and offers a high sensitivity of 2mV/DIV from DC to 15MHz.

The ADD/SUB feature makes this model ideal for measurement and maintenance of computers and peripherals. This scope is recommended for FLOATING Measurements and FREQUENCY/PHASE Measurement (X-Y mode). Rechargeable battery operation makes it ideal for repairing TVs and other consumer and industrial equipment.

**Now with 95mm  
rectangular  
tube**

## SPECIFICATIONS:

**SENSITIVITY:**- 2mV to 10V/DIV on 12 ranges in 1-2-5 step with fine control. **BANDWIDTH:**- DC: DC to 15MHz (-3dB). **RISETIME:**- 24nS. **OPERATING MODES:**- CH-A, CH-B, DUAL, ADD and CHOP. **TIME BASE:**- 0.5 $\mu$ sec to 0.5sec/DIV in 19 ranges and X-Y in 1-2-5 step with fine control. **MAGNIFIER:**- x5 at all ranges. **X-Y OPERATION:**- X-Y mode is selected by SWEEP TIME/DIV switch CH-A: Y axis. CH-B: X axis. **POWER REQUIREMENTS:**- AC: 115/240V DC: 11-30V, 7.2VA. Battery: Ni-Cad Battery (up to 2 hour operation). **SIZE:**- 113 (H) x 223 (W) x 298 (D)mm. **WEIGHT:**- 4.5kgs (5.5kgs including battery).



**BS610**  
**140mm**  
**No Parallax Display**

## APPLICATION BS610

The BS-610 employs a high brightness 140mm Rectangular CRT with internal graticule assuring easy and accurate observation of waveforms without any parallax.

External DC-Powered operation expands the versatility of this oscilloscope to FLOATING Measurements as well as field operation.

Other features including TV SYNC and HF REJ. make this scope ideal for research and development, production lines or in-the-field service applications from computers to electrical appliances.

## SPECIFICATIONS:

**SENSITIVITY:**- 5mV to 10V/DIV on 11 ranges in 1-2-5 step with fine control. **BANDWIDTH:**- DC: DC to 15MHz (-3dB). **RISETIME:**- 24nS. **OPERATING MODES:**- CH-A CH-B DUAL, ADD and CHOP. **TIME BASE:**- 0.5 $\mu$ sec to 0.5sec/DIV in 19 ranges and X-Y in 1-2-5 step with fine control. **MAGNIFIER:**- x5 at all ranges. **X-Y OPERATION:**- X-Y mode is selected by SWEEP TIME/DIV switch. CH-A: Y axis. CH-B: X axis. **POWER REQUIREMENTS:**- AC: 115/240V DC: 11-30V, 7.2VA. **SIZE:**- 145 (H) x 280 (W) x 369 (D)mm. **WEIGHT:**- 6.7kgs.

**We STOCK PROBES and ACCESSORIES to suit most makes of oscilloscopes to 150MHz. Contact us for competitive prices.**

Available from selected stockists or from:-

PO Box 30, Concord, NSW 2137  
13-15 McDonald St, Mortlake, NSW 2137  
Phone: (02) 736 2888. Telex: 25887

PO Box 107, Mt Waverley, Vic 3149  
21-23 Anthony Drive, Mt Waverley, Vic 3149  
Phone: (03) 233 4044. Telex: 36206

Adelaide: 271 1839, Brisbane: 229 3161, Perth: 398 3362

**ELMEASCO**  
**Instruments Pty. Ltd.**



# Editorial Viewpoint

## A problem at the grass roots level

Up until the late '60s, at least, component and radio factories were to be found, dotted around Australia. For school leavers, they provided a well trodden path into the radio industry.

Having been bitten by the "bug", many lads found their first job as an assembler or a wirer in a nearby radio factory. For some it led nowhere but, for many others, it provided support and background for continued hobby activity, and for study at a private or formal level.

Out of the ranks of assemblers and wirers came generations of well informed enthusiasts, amateur radio operators dedicated to home construction, servicemen, technicians, and quite a few qualified engineers. Those same men formed the backbone of the signals units during World War II.

From that same pool, through the years, has come most of the staff of "Electronics Australia" — men who knew the thrill of winning sound from that first crystal set, and the satisfaction of progressively filling the gaps in their understanding of basic theory. They shared that experience with readers.

But, over the last decade, factory after factory has closed down, to be replaced by bulk stores, crammed with imported goods. As the factories have disappeared, so have the grass roots jobs in electronics — or the bottom rungs of the ladder.

In that 10 years, we have become a nation of electronic consumers. We have more radio sets, more tape decks, more hifi systems, more electronic gadgets of all kinds than ever before. We listen to them, watch them, play with them, communicate through them, use them to work out problems — all with increasing facility but with a lessening perception of how the circuitry inside really functions.

These thoughts were prompted in part by a letter from a reader in Montefiores, NSW, who deplores the current dependence on kits, the attention paid to computers, the premature obsolescence of yesterday's projects, the readiness to discard rather than to fix. "Remember", he says, "that we were kids once, and there are so many more nowadays who need to learn how to use a soldering iron, and what to do from there on!"

Maybe there are, but try to tell the kids that! One of the anomalies we have come up against, in trying to fill recent staff vacancies, is that so many applicants are very familiar with built-up equipment but manifestly ignorant of basic components and circuits.

In short, a new kind of self-taught enthusiast is emerging, who doesn't have much regard for grass roots theory. If the industry is to have an assured supply of technicians, with a basic grounding in theory and practice, it will have to rely increasingly on apprentices and students trained in an organised and formal way.

**Neville Williams**

### EDITOR-IN-CHIEF

Neville Williams  
M.I.R.E.E. (Aust.) (VK2XV)

### TECHNICAL EDITOR

Leo Simpson

### ASSISTANT EDITOR

Greg Swain, B.Sc. (Hons. Sydney)

### TECHNICAL PROJECTS

Ron de Jong, B.E. (Hons. NSW), B.Sc.  
John Clarke, B.E. (Elect., NSWIT)  
Gerald Cohn  
Paul de Noskowski

### GRAPHICS

Robert Flynn

### PRODUCTION

Danny Hooper

### SECRETARIAL

Pam Hilliar

### ADVERTISING MANAGER

Selwyn Sayers

### CIRCULATION MANAGER

Alan Parker

### Registered for posting as a publication — Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

#### Editorial Office

57 Regent St, Sydney 2008.

Phone (02) 699 3622 Telex 25027.

Postal Address: PO Box 163, Beaconsfield 2014.

#### Advertising Offices

Sydney — 57 Regent St, Sydney 2008

Phone (02) 699 3622 Telex 25027

Representative: Narciso (Chit) Pimentel.

Melbourne — 392 Little Collins St, Melbourne

3000 Phone (03) 602 3033

Representative: Janis Wallace.

Adelaide — Charles F. Brown & Associates Ltd, 254 Melbourne St, North Adelaide 5006

Representative: Sandy Shaw (08) 267 4433

Perth — 454 Murray Street, Perth 6000.

Representative: Ashley Croft (09) 21 8217.

#### Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001

Enquiries: Phone (02) 20944, ext 2589

#### Circulation Office

21 Morley Ave, Rosebery, Sydney 2018.

Phone (02) 663 3911

#### Distribution

Distributed in NSW by Sungravure Pty Ltd, 57

Regent St, Sydney; in Victoria by Sungravure Pty

Ltd, 392 Little Collins Street, Melbourne; in South

Australia by Sungravure Pty Ltd, 101-105

Weymouth St, Adelaide; in Western Australia by

Sungravure Pty Ltd, 454 Murray Street, Perth; in

Queensland by Gordon and Gotch (A'asia) Ltd; in

Tasmania by Ingle Distributors, 93 Macquarie St,


Hobart; in New Zealand by Gordon and Gotch

(NZ) Ltd, Adelaide Rd, Wellington.

#### Copyright. All rights reserved.

Devices or arrangements shown in this magazine may embody patents. Information is furnished without responsibility for its ultimate use, or for failure of equipment to operate as expected, or for any damage, loss or injury which may be sustained. Material intended for publication is submitted at the sender's risk and, while care will be taken, responsibility for any possible loss will not be accepted by "Electronics Australia"

\* Recommended and maximum price only.

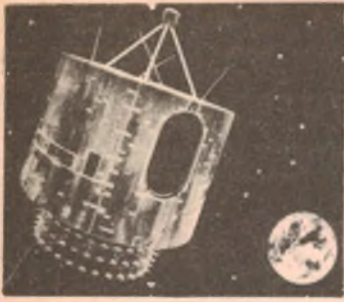

# News Highlights

## Radioactivity & coal-fired power stations

It is not generally realised that coal fired power stations create a significant amount of radioactive pollution. According to David Fishlock, Science Editor of the London Financial Times, (27/11/80) the level is sufficient to justify monitoring in the interest of public health.

(In Australia, tests by the Australian Atomic Energy Commission, at Lucas Heights, NSW, confirm that significant amounts of radioactive waste are released from coal fired power stations. — Ed.)

According to David Fishlock, a study has been made by the National Radiation Protection Board, "watch — dogs" of the public interest in radiation. It is the first to be made in Britain in such depth.

The results show that public exposure from radioactive discharges to the atmosphere from Britain's coal-fired stations is about the same as the discharges to atmosphere from the whole of the nuclear fuel cycle as practised in Britain. The biggest contributor to the nuclear industry's releases, however, is not the nuclear

power stations themselves but the reprocessing plant for spent nuclear fuel at Windscale.

Most minerals contain traces of the two nuclear fuels, uranium, and thorium, both radioactive, and traces of the products of their natural radioactive decay. In the combustion of coal in power stations the gaseous radioactive substances, mainly radon, are discharged into the atmosphere. Also discharged is a small proportion of the solid radioactive material, as dust. Claims and counter-claims have been made by those debating the politics of nuclear energy about whether a nuclear or a coal-fired power station "leaks" more radiation into the atmosphere.

The NRPB study, by Dr William Camplin, makes no attempt to compare directly the leakiness of the two technologies. Neither does it, consider the whole of the coal fuel cycle, from the coal mine to final disposal of the great bulk (99.5%) of the slightly radioactive ash as building material or landfill. Dr Camplin considers only the 0.5% of ash which evades the filters and is emitted from the chimney stack, together with radioactive gases.

Dr Camplin looked into five pathways by which people might pick up radioactivity from a coal-fired power station.

The most complex of these is through the foodchains, which involve movement of the activity into the soil, then into the plant, and then into an animal or directly to man. The contribution from this source dominates the estimate of the individual radioactive dose.

He estimates that the annual committed effective dose equivalent received by a member of a hypothetical critical group would be 23 millirems (230 micro-sieverts). This is less than 5% of the dose equivalent limit, and although conceivably some people in Britain could receive this much, he believes it likely that individual doses would be much lower.

Dr Camplin believes that enough radioactivity is normally emitted by large coal-fired power stations to warrant a program of environmental monitoring in the vicinity of a large power station to measure the true levels of radio-nuclides in animal food products.

## Electronics: problems for auto industry

A "Car of the Future" conference, sponsored by the Australian Automobile Chamber of Commerce, was held in Canberra on November 27 and 28, 1980.

Technical addresses from General Motors Holden, Ford Motor Company of Australia, Robert Bosch Australia Pty Ltd and the Motorola Semi-conductor Group outlined the extent of new technology that will be introduced to vehicles on Australian roads within two-four years.

Particular emphasis was placed on new methods of manufacturing which, in turn, would force entirely new approaches towards servicing and repair of these vehicles.

Earlier the Conference was told that microprocessors and computer control would become commonplace for many vehicle functions in cars manufactured within the next two or three years.

According to the 1979 White Paper on Technological Change in the Retail Motor Industry, Australia's automotive

retail and service repair industries seriously lack the expertise and the trained personnel to deal with technological advances currently being introduced into the world's automobiles.

Of major concern to the Conference participants was the rate of technological change and technical development, which has increased to such a point that current educational institutions and training organisations are unable to cope.

One delegate to the Conference claimed that some colleges were using 30 year old equipment trying to prepare young apprentices to work on new technology, highly complex 1980s motor vehicles.

Emphasis was placed on the need to re-equip technical and further education centres throughout Australia with more staff, better facilities, and more up-to-date teaching equipment.

## AWA, Hughes in joint satellite venture

● **Amalgamated Wireless (Australasia) Limited and Hughes Aircraft, USA** are completing negotiations to form a team which will submit proposals to the Australian Government for the supply of satellite ground terminals. A team of AWA engineers had just returned from the Hughes plant in Los Angeles and has now set up a satellite project office at AWA's North Ryde Division in Sydney. The spokesman said Hughes and AWA must be one of the strongest contenders for the Australian satellite ground terminal system.

## Changes at DSE

● Mr Ike Bain has been appointed Managing Director of the Dick Smith Electronics Group, while Dick Smith remains Executive Chairman. Mr Bain had been General Manager since 1975.

## Predicasts: \$200 billion US market in home electronics by 1995

There's a revolution coming in home electronics according to a recent report released by Predicasts, Inc, the Cleveland-based business information and market research firm.

By 1995, says Predicasts, you'll be able to plan the annual household budget and the week's meals on the computer; get the latest stock reports from the cable TV; play checkers on a hand-held electronic game (and be soundly booed for a bad move; order a coat from a TV catalog; and talk to Ralph on the videophone.

Communications services will be the largest and fastest-growing home

electronics category, according to Predicasts. Predicasts expects CATV to reach 90% of US households by 1995, with some 70% of households on 2-way interactive cable.

Solid growth is also expected for the audio-visual sector. Videodisc players in particular will shoot up a predicted 53% annually, reaching over 7 million units valued at nearly \$1.5 billion.

Personal communications devices will also be an area of rapid technological innovation, while speech synthesis will greatly aid in personalising the home computer. Predicasts holds that a 2-way conver-



Courtesy Predicasts, Inc., Ohio.

sation facility, combined with continued cost reductions, will dramatically further the acceptance of the computer as a "member of the family".

## \$300 fine for breaching copyright

A video engineer was fined a total of \$300 recently for possessing master video cassette copies of major feature films from which other infringing copies could be made.

John Ian Randall, 44, of Macquarie Street, Cromer, pleaded guilty in St James Court of Petty Sessions to five charges involving Stormboy, Rocks, F.I.S.T., and The Taking of Pelham 123.

He also pleaded guilty to a summons charge in similar terms involving The Hunting Party.

The offences, under the Copyright Act, were said to have occurred on February 13, 1980.

Randall was the proprietor of Electronic Instruments, a business carried on at his home.

On February 13 police seized from Randall's home 1300 video cassettes of cinema films and other title material, together with a quantity of documents and video recording equipment.

"The majority of these tapes are feature motion pictures and are subject to copyright with the exception of 56 video cassette tapes - all are of professional quality," Sgt Montford said.

He applied for an order for the forfeiture of 1216 video cassettes of motion pictures and other work which he said were illegal copies of cinema and TV films.

Mr G. Smyth, SM, refused a request that the seized tapes be erased and returned to Randall.

Mr D. Lasky, for Randall, said the tapes could be erased under police supervision.

He said the recording was a hobby and his client had no way benefited commercially.

"He had suffered large economic loss because of the seizure," Mr Lasky added.

## AM stereo: the wrangle continues

The projected AM stereo service for the United States, using the Magnavox system, is still bogged down in legal and technical arguments. As reported in our August 1980 issue, the FCC originally gave the official go-ahead to Magnavox, but this was almost immediately challenged by other trade interests who claimed that the system had technical limitations. This was reported in our October issue.

The latest report comes from the US magazine "Radio-Electronics" for November 1980. It says:

Don't look for AM stereocasting to start any time soon. The best guess now is early 1982 at the soonest, as a result of the bitter controversy that erupted over the FCC's choice of the Magnavox system over four others. After the Commission chose Magnavox, critics

were quick to point out that it generated "pops" at 95% negative modulation. Magnavox retorted that the pops are completely eliminated by special circuitry in the IC designed for the system.

Nevertheless, the Commission took note of the brouhaha over its choice by letting its engineering staff go back and refine and improve the decision-making that led to the choice of Magnavox. The decision will be released and the public will be given the opportunity to comment. That could result in the choice of another system, or in reaffirmation of the system originally chosen - but it means more delay. Although FCC staff sources say the delay could be as short as six months, past experience indicates it's more likely to be a year or more before there is AM stereocasting.

## Laser rangefinder accurate to 5 metres

Shown in the photograph is the LP7 Laser Rangefinder, a British development that is in daily use in Britain's North Sea oilfields for the accurate positioning of oil platforms and drilling barges and with NATO forces for fire control, reconnaissance, and position siting for weapons.

The Rangefinder has a maximum range of 9km with an accuracy of  $\pm 5$  metres regardless of distance. It weighs 2kg and has a built-in rechargeable battery that provides up to 600 measurements before charging. The equipment is housed in a rugged waterproof case and is of modular design to simplify repair and maintenance.

To make a measurement the rangefinder is aimed at the target and the firing button depressed. The range is immediately presented in the left hand



eyepiece as a four digit LED display. The intensity of the display can be adjusted and in order to save power the display is automatically switched off three seconds after each ranging.

Further details from: Lasergage Ltd, Lennig House, Masons Avenue, Croydon, CRO 9XS, England.

# VSI

## THE NUMBER ONE PHILIPS DISTRIBUTOR

### **Why No. 1? Because we**

Have on-line inventory access of over 7,000 semiconductor and passive items.

Have on-line order processing.

Have on-line warehouse printing of despatch docket and invoices.

Will take an order up to 3 p.m. Sydney time and deliver all ex-stock items next day in all capital cities.

Have dedicated hot lines just for Philips products.

Call (02) 438 3960 in Sydney,  
(03) 877 5822 in Melbourne.

And now for a new service!

For the price of a local phone call, dial 00822055 from anywhere in Australia to check your back order status with our Customer Service Department.

(Sydney Customers use 439 4655.)

VSI Electronics (Australia) Pty. Ltd.



**VSI  
ELECTRONICS  
(AUSTRALIA)  
PTY LTD**

**The Distributor offering something unique - Service.**



## Artist draws on television

An artist can "paint" a colour picture or design colour graphics directly onto a television screen using this new micro-processor based device developed in Britain.

Called "Paintbox," it consists of an electronic drawing board called a tablet, a TV monitor and a floppy disc memory. The artist draws directly onto the tablet with a special stylus. Nothing appears on the tablet, but the moving stylus is followed by an electronic marker within the tablet. As its position is digitised and stored the drawing appears simultaneously on the TV screen.

Paintbox offers several advantages

over conventional methods. The user can select a colour by switching a colour chart onto the screen, and touching the corresponding position on the tablet with his stylus. He can call up varying combinations of tone and brightness or alter the width of his stylus line. Paintbox even has an airbrush simulator, which "sprays" coloured dots onto the screen and the user can fill a defined area with colour at the touch of a button.

Originally developed by the Engineering Research Department of the BBC, Paintbox is one of several research projects being offered to British companies for manufacture and sale under licence.



## Britain falling behind in micro industry says report

All is not well with the British chip (microprocessor) industry, according to a report in the London Financial Times (21/11/80). High development costs, lack of technical expertise, supply problems and depressed markets are some of the factors which prevent British companies applying the microprocessor.

These are some of the conclusions of a report on microprocessors in manufactured products published by the Policy Studies Institute.

It says that the Government's present support schemes such as the Microprocessor Applications Project should be continued and extended. The institute believes that Britain's industries face serious risks of falling further behind its major competitors in its application of new technology.

Already the report notes that some of the 90 companies it studied showed signs of falling behind their chief overseas competitors many of which

had the advantage of substantial backing from their own governments.

The report also notes "the problem is not one of keeping in step with other countries but the much more difficult one of catching up from a position of weakness."

The institute also blames manufacturers' decreasing competitiveness on the fact that their products have bad or inappropriate design and specification, poor market research and inadequate after-sales service.

However not all Britain's industries are lagging behind foreign companies. The report says that at one extreme in the toy industry some companies are not only keeping up with world technology but actually setting the pace, but at the other extreme, in electronic games, Britain is well down in the ratings.

The institute says that the Government must be made aware of the fact that "British companies, if left to stand on their own two feet, may not have much chance against heavily supported foreign competitors."

The report claims that many British companies involved in microprocessors believe strongly that they are placed at a significant disadvantage relative to US and Japanese manufacturers because "they get second class treatment from their American suppliers in terms of prices, delivery times, access to the latest technology and help with development."

For this reason the institute felt that the Government's decision to continue to support Inmos, the silicon chip manufacturer set up by the National Enterprise Board, is a "partial but welcome recognition that some action is needed".

## Satellite to rendezvous with Halley's Comet

The go-ahead has been given for a new satellite that will rendezvous in outer space with Halley's Comet, last seen in 1910, and, due to be visible again in 1985/86. The aim is for the satellite to intercept the comet so that instruments on board can obtain new information about the chemical composition of the region surrounding the nucleus and of the comet's famous "tail". It is also hoped to measure the comet's magnetic field.

British Aerospace, under contract to the European Space Agency (ESA), earlier completed a three-month study of the project and reported that a GEOS-type spacecraft could do the job.

ESA's industrial policy committee has now chosen the space centre of British Aerospace at Bristol to develop a satellite based on the design of Europe's first pair of GEOS geostationary scientific satellites.

BAe and ESA will negotiate a contract expected to be worth some \$54 million. This will be shared between a number of European aerospace companies.

The satellite will be named GIOTTO

after Italian painter Giotto di Bondone who observed the comet in 1301. His painting "Adoration of the Magi", completed around 1304, contains one of the first visual impressions of Halley's Comet.

GIOTTO will be launched during a 10-15 day period in mid-July 1985 and intercept the comet in March 1986. Because the time available for observation is only a few hours, the satellite must be highly reliable, as must the prediction of the orbits of both satellite and comet.

The satellite will have an on-board rocket motor that will fire the craft into orbit, while its advanced telecommunications system will transmit instrument readings a distance of nearly 160 million kilometres back to earth.

Illustrating the accuracy required for the rendezvous, British Aerospace says the satellite will have to pass less than 1000 metres from the nucleus — no mean feat when it is realised that the nucleus may be only a few kilometres across.

## Special: the coming era in home video — 1

# New-generation

Video cassette recorders have largely faltered since their introduction in the late 70s, but 1981 looks like being the year in which sales really take off. The reason — a range of new generation VCRs, smaller and lighter, and packed with features to make them attractive to the consumer.

by JOHN FREE

New table-model VCRs of dealer's shelves are notably slimmer, with distinctive, ultramodern styling. And what's inside these new-generation video cassette recorders — microcomputers for programming and switching logic, all-electronic tuners, soft-touch controls, new TV microcircuits — not only trims VCR size and weight to make the new look possible, it also means more reliability and operating flexibility. Competition is bringing last year's high-end features, such as high-speed picture search and slow-speed and frame-by-frame advance, to under- \$1000 models.

These technology advances and features appear in portables, too. Manufacturers have whittled about 2kg off some earlier battery models. Now, with a 5kg portable and lightweight camera, you can tape on the go without straining under heavy gear. One new portable has a home-VCR first: stereo capability that adds an exciting new audio dimension.

The new lightweight portables, in the popular VHS tape format, helped squelch or postpone the expected introductions of two incompatible decks — so-called longitudinal recorders with fixed instead of spinning tape heads. Instead, only one new tape format has appeared, used in a remarkably compact 3kg portable.

### Speed wars

VCR makers are now trying to capture sales by supplying more features at a better price. But until recently, the marketing emphasis was on recording time: "Our models put more programming on a single tape than theirs." Sony's first Betamax, which I tried five years ago, recorded just one hour.

Since then, with intense competition between the VHS and Beta tape formats, manufacturers have steadily boosted recording/playback time by slowing down tape speed. Machines for both formats

can now record the longest movie or football game, so it's a standoff. But judging from the new models I've been trying and others I saw at demonstrations, there's a new kind of speed race — for the fast picture search.

The first speed-play model I tried was JVC's HR-3600. It doubles tape playback speed so you can bypass commercials, visually find a section faster, or actually watch programs in half the time. (A digital circuit prevents Donald-Duck-like pitch changes from doubled audio speed.)

Some of the newer decks have pulled out all the stops on playback speed for picture search. Sony's SL-5800 with BetaScan, for example, can boost tape speed from five to 20 times normal — in forward or reverse — to pinpoint a sequence or zip through commercials. Toshiba's SuperScan in its V-8000 Beta-format deck periodically displays pictures as tape whips by at 40 times normal speed. Audio, of course, is muted at



*Catering to the overseas traveller, Sony's new SL-T7 "Color 3 System" video cassette recorder can play back NTSC and SECAM tapes as well as PAL-recorded programs. An 8-function remote control unit controls picture search and freeze facilities, in addition to the usual functions. (Note: the SL-T7 must be used with a modified receiver to take advantage of all three playback modes).*

# VCRs



Recently released in Australia, National Panasonic's NV-7000 VHS video cassette recorder features 4-hour playback time, Dolby noise reduction, an electronic tuner, a 14-day 8-program timer, variable playback speeds, freeze frame, and a 12-function remote control unit. RRP is \$1500.

these high speeds.

The VHS decks, which load and scan tape differently than Beta-format models do, were initially left behind in the high-speed picture-search race. While catching up, VHS deck makers have stressed the slow-motion, freeze-frame, and frame-by-frame advance features of their machines. RCA's lead 1981 VHS model, the VET250, now has a forward or reverse picture-search feature at nine times normal speed.

## Smart decks

Since microcomputers have crept into your new car, the food processor in your kitchen, and practically everything else, you'd expect to see them in VCR decks, too. In the 1981 models, the computer-on-a-chip handles everything from switching logic (pushing the wrong button won't harm anything) to the complex programming tasks of turning decks on and off automatically, to changing chan-

nels over a two-week period while you're away.

While microcomputers can increase the flexibility of complex equipment such as VCRs, they can also make deck operation more difficult. On its VC-6800, Sharp has a calculator-like keyboard for computer programming and an LCD panel that shows channels, dates, times, or even serves as a four-digit electronic tape counter.

For each channel you want to program in advance, you have to push some 18-odd buttons in an exact sequence. The panel and keys are also used in a complex procedure to fine-tune channels and assign them numbers. While the 6800's computer aids these tasks, its use demands patience and a knack for nimble, careful keyboard programming.

Sharp's 6800 can be programmed to change channels seven times up to one week ahead. This number-of-programs-days-ahead sequence varies widely among the costlier programmables.

What makes this advance programming possible is the all-electronic (non-mechanical) tuners in virtually all new VCRs. Another nice feature is the soft-touch front-panel controls, which operate solenoids to quietly start or stop mechanical sequences.

What about recorded picture quality? Comparing brands, it's very difficult to detect any significant differences. Even in the six-hour VHS mode, where special noise-reduction and enhancement circuits are used, pictures are surprisingly good. Using test patterns, I noted that resolution was slightly worse with Quasar's lightweight VH5300 portable compared with more massive table-top models.

## Versatile portables

"Consumers in the '80s will find a world of use for video and won't want to be limited by a stationary system to just taping and viewing TV programs at home,"

## Hollywood hurries to put movies on video tape

MCA . . . Columbia . . . Paramount . . . Warner . . . Metro-Goldwyn-Mayer . . . 20th Century-Fox.

At times, from the names on exhibit booths, I felt it was a Hollywood convention instead of the annual summer Consumer Electronics Show in Chicago.

The new Hollywood names at the show confirmed that virtually all major motion-picture companies hope to benefit from the sales boom in VCR hardware and software (prerecorded tape). Until this year, distributor booths for adult or X-rated video cassettes dominated the video-tape scene at the show. (Studies indicate that while the sales volume of video pornography remains high, its percentage of total cassette sales is falling steadily.)

Why the new interest in prerecorded-cassette marketing? Hollywood com-

panies and others have noted that VCR-deck sales are climbing steadily to the point where two million will be whirring in homes. If even a small percentage of this home-entertainment market buys its Hollywood favourites on prerecorded cassettes at \$50 to \$100 each, that spells big profits.

Paralleling the explosion of new titles is the steady growth of new distributors and retailers. Stores specialising in video cassettes are popping up in larger cities. Mail-order video-tape clubs are multiplying, too. Some tape stores and nationwide chains such as Fotomat rent video cassettes. Pamphlets I collected at the show indicate there are distributors that specialise in everything from special-interest software, such as *The Two Best World Series Ever*, to such Saturday-afternoon TV staples as *Fort Apache* or

classics such as *Citizen Kane*. One way to locate new sources of video software is to pick up some of the new video magazines.

Perhaps first prize for innovation in VCR-software distribution should go to a Santa Rosa, Calif, cable-TV firm. It plans to send prerecorded software to customers overnight on blank channels. A computerised controller to switch a subscriber's VCR on and off automatically is planned.

One development that may trim prerecorded cassette prices is the high-speed duplicator. Next year, Japan's Matsushita plans to offer a machine that can spew out 12, two, or four-hour VHS cassettes in four minutes. Conventional duplication techniques work on a "real-time" basis, with a master recorder and numerous slave duplication machines.



Flip cards fit over buttons to aid programming the microcomputer in Sharp's VC-6800. LEDs on the deck's tape-remaining selector (left) light up so you can tell if there's enough to finish recording a program.



says Charles Phillips, executive vice-president for Akai America. That's the logic behind Akai's entry into the VHS portable market last year and its improved model this year. Portables are capturing a larger portion of VCR sales.

With a portable, of course, you aren't limited just to battery operation outside. All of the portables can be used with an optional tuner. A portable/tuner system works just like an AC-only, table-top

model. The combination of deck and tuner costs about \$1500, which may prove less expensive than buying an AC-only model and deciding later than you need a portable, too.

Akai's initial VHS portable could capture only two hours of material on a cassette. Its upgraded model, the VP-7350, includes a switch for six-hour recording. The 7kg portable also can record audio in stereo.

The Dolby noise-reduction circuits in the 7350 provide a 51dB signal-to-noise ratio. Akai's 7350 has another unusual feature: a key lock to prevent unauthorised use at a business, or at home by children.

Another new entry in the portable field is the two/four/six-hour VHS 7500 model from Hitachi. It weighs in at 7kg with its battery (compared with another VHS lightweight, Quasar's 5300, and the identical Panasonic PV-3000, which weigh 6kg with batteries). To help shrink the 7500s size, Hitachi used specially designed large-scale-integration (LSI) microcircuits.

The prize for compactness, however, goes to Technicolor's 3kg portable, which uses a new (nonstandard) ¼-inch tape — half as wide as VHS and Beta tape. "It is the first step toward a more comprehensive and versatile group of video products than would have been possible with former technology," said Jack Minor, president of the firm's audio-visual division.

The new portable deck was jointly developed by Funai Electric Trading Company in Japan and Technicolor. "Funai will manufacture the VCR, forerunner of the other related products in the video field," Minor said. "These will include a Technicolor camera and other innovative items to complement the VCR." The additional hardware may be available by the time you read this.

## How to put six hours on a two-hour cassette

Many new VCR's now have a switch that reduces the tape-recording speed enough to put six hours of material on a VHS cassette originally designed for two-hour recordings. (Beta-type decks also have an extra-slow speed for up to five hours of recording.)

Several changes have been made in components and circuits to achieve the extra-long play. The chart (right) shows how some parameters change at various speeds in RCA's Matsushita-built VHS machines. The horizontal segments represent half-inch tape with diagonal recorded tracks. Adjacent tracks (CH1, CH2) represent a single 1/30-second (NTSC) TV picture frame, and are recorded or played back by heads on opposite sides of a spinning drum. (Some new special-effect VHS decks have a second pair of heads offset 90° from the other pair, and some JVC decks use four heads.)

Matsushita's six-hour decks without special effects have narrower heads (30 microns, or  $\mu\text{m}$ ) compared with older two/four-hour VHS machines, which have heads 38 microns wide. As playing time is extended by reducing tape speed, the space between recorded tracks is reduced and even overlaps and erases parts of previously recorded tracks. Signals for adjacent tracks are altered before they're recorded to minimise interference between adjacent signals.

The sync pulses separating the 262-odd TV-picture lines (US NTSC system) on each track, for example, are aligned on adjacent tracks in the two/six-hour modes, minimising the effect of slight mistracking since adjacent tracks have similar picture content. In the four-hour mode, sync pulses can't be aligned, so they're offset slightly

	TRACK	SYNC-PULSE ALIGNMENT	TAPE SPEED
2 HR			1.3 IPS
4 HR			0.65 IPS
6 HR			0.44 IPS


( $\frac{3}{4}$ H). This precise offset causes adjacent interfering signals to cancel each other optically on the screen.

# What do **SCOPE** Irons Do Best?

- 1. Provide intense heating power :**  
The heating concept located right behind the tip provides tremendous heat output to get the iron hot fast; then keeps the temperature under your control to complete every joint faster.
- 3. Put this heating power right at the tip :**  
A perfect iron has its heat source right at the surface of the tip — inefficient irons have their's up the barrel. The Superspeed range generate their heat on the copper tip itself, hence the intense concentration.

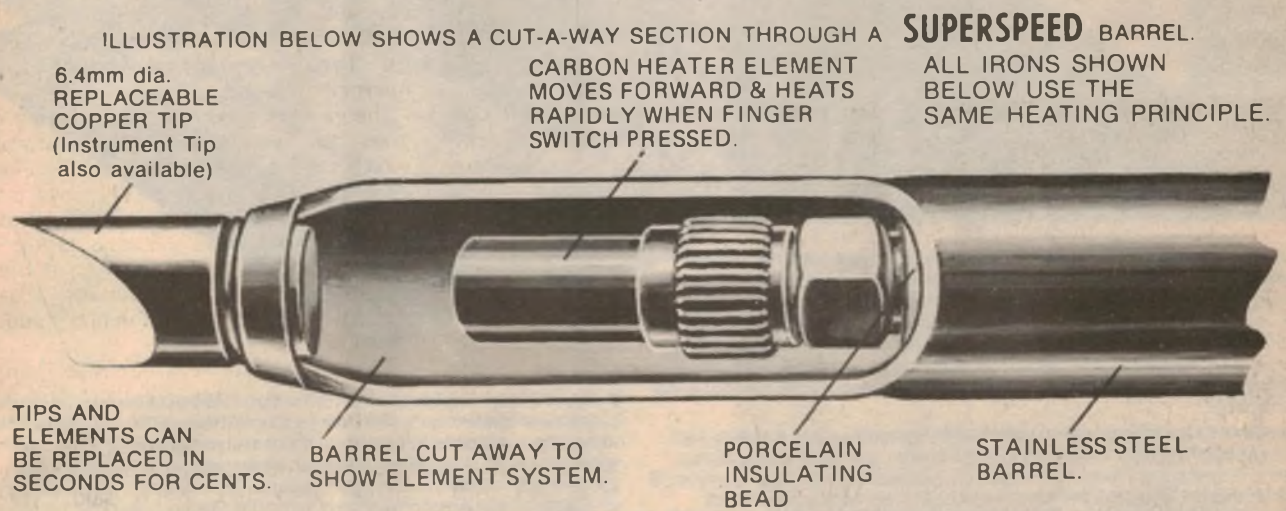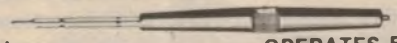

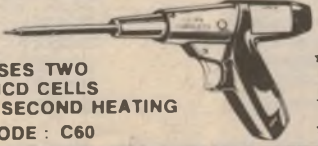
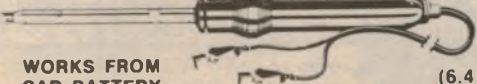
- 2. Let you control the power :**  
Should you encounter a heat sink which would rapidly drain away tip heat (e.g. thick metal or a need for plenty of molten solder) your finger switch provides another burst of heat to keep the copper tip at correct temperature. Normally only heavy irons have this capacity and take a long time to heat — and cool.
- 4. Lets the tip run cool when not actually soldering :**  
The tip stays tinned longer and lasts much longer because the iron switches off when switch released. This feature plus a low heat conductivity stainless steel barrel keeps the handle cooler.

## HOW DO **SCOPE** IRONS HEAT SO FAST?



THE TEMPERATURE IS CONTROLLED BY FINGER OR TRIGGER SWITCH.

### WHICH SCOPE IRONS DO THIS?

<p><b>MINI SUPERSPEED 20-75 WATTS</b> 5 Second Heating</p>  <p>MANUAL TEMPERATURE CONTROL OPERATES FROM SCOPE TRANSFORMER CODE : M.S.</p>	<p><b>SUPERSPEED 150 WATTS</b> 5 Second Heating CODE : S.S.</p>  <p>MANUAL TEMPERATURE CONTROL OPERATES FROM SCOPE TRANSFORMER</p>
<p><b>RECHARGEABLE CORDLESS 60W</b></p>  <p>USES TWO NICD CELLS 6 SECOND HEATING CODE : C60</p> <p>3 RECHARGE ADAPTORS ★ AUTO CIG. LIGHTER ★ 240V. ADAPTOR ★ 3.3V. ADAPTOR</p>	<p><b>12 VOLT HOBBY IRON 200W</b></p>  <p>WORKS FROM CAR BATTERY SAFE EVEN IN WET CONDITIONS CODE : HI</p> <p>(6.4 Metre Lead)</p>

FOR MORE INFORMATION CONTACT :

## SCOPE LABORATORIES

3 WALTON STREET, AIRPORT WEST, 3042 TELEPHONE : (03) 338-1566 TELEX AA38318

N.S.W. : (02) 546-6144, S.A. : (08) 223-2261, Qld. : Brisbane (07) 221-1933, Townsville (077) 71-3448, Rockhampton (079) 27-3370, TAS. : Hobart (002) 34-2811, Launceston (003) 31-5545, W.A. : (09) 381-4155

OVERSEAS DISTRIBUTORS:  
N.Z. : Wellington 85-9578, P.N.G. : Port Moresby 255300/255028/257796, P.N.G. : Lae 422172.

# everyone can learn electronics . . . the effective **Heathkit<sup>®</sup>** way!



**There's never been a better, faster, lower cost way to learn electronics than these Heathkit Programs!** Learning electronics could very well be the most important step you'll ever take, so, naturally, there are many factors to consider in choosing your method of learning. If you're like most people, you don't have the time for conventional learning institutions. The Heathkit Continuing Education Series was conceived to make learning electronics more convenient and affordable for everyone. Thousands of people just like you are finding out what makes Heathkit learning programs so tremendously successful. Simple, easy-to-use and EFFECTIVE!

**Among the many reasons for the wide acceptance of these programs** is their simplicity. Each learning program is simply and logically arranged for easy, step-by-step 'programmed' learning. Progressing at your own established pace, you learn in an unhurried environment free from pressure. No facet of the material is omitted and nothing is assumed. Each program includes everything you need for a high degree of understanding. Audio records (or optional cassettes) reinforce the text material and an optional final examination lets you test your overall comprehension.

**The Continuing Education Programs are economical too.** The first four programs use the same trainer so you can get a complete education in fundamental electronics at substantial savings. The advanced programs, Digital Techniques and Microprocessors, require separate trainers, but they still cost less than competitive courses.

**Get 'Hands-on' experience for a better understanding of electronics.** Learning electronics and being able to apply what you've learned are, of course, the goals you seek to achieve with

the Heathkit Continuing Education Series. For that reason, we have spared no effort in assuring your complete comprehension. Our optional Electronic Trainers, designed for use with each program, perfectly illustrate the Heath approach to learning. These trainers give you actual 'hands-on' experience with electronic components and circuitry. It's an acknowledged fact that you learn best by doing and the trainers let you do exactly that. You get a better grasp of circuit concepts and perform the program projects quicker and easier as well. Solderless connectors on the trainer panel make hookup of the components supplied with the program quick and neat. Built-in power supplies and signal sources provide convenient operation. The trainers are available in both kit and assembled form.

**When you've finished the program,** the trainer still serves as the ideal device for breadboarding circuits of your own design. We highly recommend these trainers as supplements to the Heathkit Individual Learning Programs. A record (or cassette) player is needed to play the audio portion of the material. A VOM for measuring voltages is also needed, and an oscilloscope is required for some of the experiments in the Electronic Circuits and Digital Techniques Programs.

**to find  
out more  
send for your  
FREE CATALOG  
today!**

**Recommended Order**  
The Heathkit Self-Instruction Programs are Designed to let you Progress from DC Electronics to AC Electronics to Semiconductor Devices to Electronic Circuits. These are the Four Basic Programs. For Optional Advanced Study, The Digital Techniques Program Provides the Background for the Microprocessor Program.

There are many courses in the HEATHKIT Continuing Education Program designed to effectively expand your electronic horizons including—

EE 3101	DC Electronics	\$76.00
EE 3102	AC Electronics	\$84.00
EE 3103	Semiconductors	\$84.00
EE 3104	Electronic Circuits	\$99.00
EE 3201	Digital Techniques	\$125.00
EE 3401	Microprocessor Program	\$168.00
ET 3100	Experimenter/Trainer	\$131.00
ET 3200	Electronic Trainer	\$157.00
ET 3400	Computer Trainer	\$347.00



## ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$..... is enclosed plus \$7.00 for package and post.

Name .....

Address ..... P/Code .....

Send to: W. F. Heathkit Centre  
220 Park St., South Melb. 3205. Phone 699 4999.

- EE 3101
- EE 3102
- EE 3103
- EE 3104
- EE 3201
- EE 3401
- ET 3100
- ET 3200
- ET 3400

Please rush me my Free catalog containing full details on the complete range of Heathkit Learning Programs.



Credit Card No:

\_\_\_\_\_

Expiry Date

Signature

# New-generation video cassette recorders



**Compact portable VCR** introduced by Technicolor uses a quarter-inch-wide tape in small (non-standard) cassettes. The 3kg deck records 30 minutes on a cassette. AC adapter (right) contains RF modulator that feeds signals to TV.

**Remote controls** for newer decks handle more and more functions. Slider control for JVC's HR-6700U varies playback speed while another button freezes TV picture. RCA's VET250 control has a button to change channels.

Although the deck can be used with some portable cameras already on the market, special patch cables are needed for each camera.

The portable's battery supplies enough energy for 40 minutes of taping with a camera, and recharges in one hour. The recorder has a freeze-frame capability, slow and fast viewing speeds. Technicolor plans to market its new lightweight through video, camera, and other retail stores.

## LVR's and more

Technicolor's marketing plans for its portable, and the latest 5kg VHS portables from Japan, were bad news for BASF. BASF had started a new factory in California to manufacture its longitudinal video recorder (LVR), which it has been demonstrating at European shows for several years. But the factory has now

been closed down, and a new LVR model from BASF expected at the summer Consumer Electronics Show never appeared.

LVR machines use a fixed head, like audio tape recorders, with the tape pulled at high speed over the head. So-called helical-scan decks now on the market spin the video heads at high speed, but move the tape very slowly. While a 5kg LVR model sounded impressive a few years ago, helicalscan technology has caught up with it. Toshiba also demonstrated a slightly different LVR model last year. While it is planning to market an industrial version of its LVR, the consumer model expected was delayed this year, too. The LVR tape format is temporarily postponed, but its simple-construction and lower-cost advantages will no doubt surface again, probably in the form of advanced super-compact VCR decks.

Although the VHS and Beta formats seem firmly established, at least one other new tape format is on the way. Next year, N. V. Philips may introduce its eight-hour VCR in the US through its Magnavox subsidiary. This high-technology VCR uses a non-standard cassette that records four hours on one tape side; it is then turned over like an audio cassette for four additional hours.

Sony leads the recording-time battle with a cassette-changer mechanism for its decks that provides a 20-hour capability. But Philips reportedly has a changer for its deck that permits 48 hours of recording and playback. The recording-time war may start again in 1981.

Reprinted from "Popular Science" with permission. Copyright © 1980 Times Mirror Magazines, Inc.



## Don't miss this . . .

### 27 DO-IT-YOURSELF PROJECTS FROM "ELECTRONICS AUSTRALIA"

You can't afford to miss out on this exciting new book of popular projects. There's a tachometer, a dwell meter and a CDI unit for your car; a Doppler burglar alarm; a digital clock; a loudspeaker protector; a variable power supply; plus much more. Order your copy now!

Available from "Electronics Australia", PO Box 163 Beaconsfield, NSW 2014. Price \$3.00 plus 70c pack and post. Also from 57-59 Regent St, Sydney.

# Colour Video

Lightweight colour video cameras, available at a price the consumer can afford, will revolutionise home movie making and lend impetus to VCR sales throughout the 80s. Choosing the right camera depends on your budget and the features you want.

by WILLIAM J. HAWKINS

My oldest daughter was to be in a school play. Perfect, I thought, for a video taping.

With the J. C. Penney system I was using, I could tape the entire hour long show on one \$13 video cassette. Not bad, considering that an hour's worth of film and processing for my super 8 movie outfit would have cost me about \$150.

It's now all possible because of a new group of lower-priced home video cameras. Sure, colour video cameras have been around for years, but at prices ranging up to \$50,000, they were a little out of reach for amateurs. New home cameras may be a step down in size and video quality, but they are affordable — from \$750 to about \$1500. And even those prices are dramatically offset when you consider the cost of film versus tape. That doesn't include the cost of the videotape recorder you'll need, but it's not like a projector that sits in the closet

for months at a time. You can use it to tape TV shows.

Video cameras take an image and convert it to a colour video signal that can be recorded on any videotape recorder. Since there's no film involved, there's no processing. You get an instant playback right on your TV set. Made a mistake? No problem. Just rewind the tape — as you would on an audio recorder — and try again. Record the same scene over again as many times as you like using the same tape. There's no waste and recording time is limited only by your recorder — up to six hours per cassette on some machines.

Choosing a video camera, however, is not as easy as using one. Price is one consideration, of course, but nearly all makers offer cameras at competitive prices. Picking the right one depends largely on how you'll use it, the features you'd like, and what equipment — if any — you already own. Here's how you sort through the variety of models available.

## Just a camera

Despite their sophistication, video cameras rely heavily on conventional camera optics. Instead of focusing an image on a strip of film, however, the lenses on these cameras focus light on the face of an internal vidicon tube that converts the image to electronic signals.

The lens used will have an effect on the type of recording to can make. Low cost models, for instance, usually have a single focal length, 25mm, f/2 lens. It's a standard lens with good quality, but it is limited — it has no wide-angle or telephoto capabilities.

The "f" number is a measurement of the "speed" of the lens — how much light it can gather. The lower the number, the larger its maximum aperture and the more light on the vidicon tube. An f/1.4 lens, for example, will provide twice the amount of light of an f/2. This means little if you do most of your shooting out-


## Sony's video camera of the future

It's five years away, Sony representatives claim, but the "video movie" is not just a dream — the working prototype shown here is a complete video camera and recorder in one. Each miniature cassette (about the size of a microcassette, but twice as thick) holds up to 20 minutes of tape. Besides its smaller mechanics and electronics, one reason for its compact size is the use of a CCD chip (upper photo, far right) instead of a vidicon to sense a video image. Currently, the camera is placed in a home video editor (lower photo, far right) for playback on a TV screen or home recorder. Future versions may have playback electronics included. The total weight of the unit, including the rechargeable battery pack, is about 2kg.





# Cameras

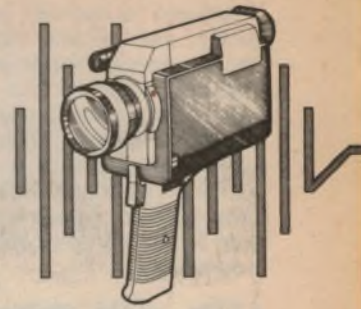

doors in sunlight. But as the light level goes down — say, if you move indoors — an  $f/2$  camera will require additional floodlighting sooner than the 1.4.

Although more expensive cameras do have larger apertures ( $f/1.8$  seems to be about average), the most significant change is in the type of lens you get; it zooms. One twist and you capture the whole family in a wide-angle picture. Another twist and you zoom in for a long telephoto shot. The typical zoom ratio (wide angle to telephoto) is 6:1. Many of these cameras give you macro capabilities: push a button and you can focus on something a few centimetres in front of the lens — a postage stamp will fill the TV screen on playback.

If you're on a limited budget, or not into exotic stamp shots, the standard lens will do fine. And many cameras, such as JVC's economy model, use a standard C-mount for the lens — unscrew the lens and replace it with an upgraded one later if you wish. But if you're a photo fanatic, save a little longer for the better lens — the additional capabilities it offers are worth the wait.

## What you see is what it's got?

In photography, the human head can be decapitated without loss of blood — just a rise in blood pressure for the movie viewers. Properly framing a shot is just as important in video taping. To do it, these new video cameras use one of three methods: optical sighting, through-the-lens, or electronic viewfinding.

The Zenith KC1000, for example, uses the sighting technique. You aim the camera by looking through a pop up viewfinder and lining it up with a front mounted sight atop the camera body. The angle between sets the angle of the camera, properly framing the scene at an average distance. This works fine once you become accustomed to it (and you get plenty of tries since you can erase the video tape and use it again).

The through-the-lens systems (TTL) are



ABOVE & RIGHT: Sony's HVC-2000 Trinitron colour camera and SL-3000 portable VCR are ideal for both indoor and outdoor home movies. The camera features electronic zoom and fade, while SL-3000 VCR lets you record up to three hours of programming.



a step up. Of these — Panasonic's PK-530 is an example — the viewfinder is optically coupled to the front lens, giving you two advantages.

For one, you see precisely what the lens sees — framing becomes simple and error-free. And second, you can manually focus the image as your subjects move. With a telephoto lens, for example, this is a must.


For a film camera, a through-the-lens system is the ultimate. But for video, it's only "next best". Top end cameras use an electronic viewfinder — a tiny 3.8cm black and white picture tube — to show you what's being recorded on tape. You look through a viewfinder equipped with a magnifying lens to see the CRT screen. Framing is simple, focus is precise, and even lighting is taken into account: If you can't see the scene on the CRT, it's not going on tape.

On some cameras, the CRT is mounted inside the rear of the camera body. Others, such as Sharp's QC-35, use an

outboard CRT on one side of the camera. This allows you to move the camera closer to your shoulder for easier handling and better weight distribution. RCA's CC007 uses the same idea, but the CRT will pivot — from left to right side — for minority groups. Being a "lefty", and favouring my left eye for viewing, I found this a definite plus.

The CRT can be used for other things, too. Throw a switch on the Sony HVC-2000, for instance, and you see a display of the video waveform to help you set light levels. And one big advantage of a CRT viewfinder has nothing to do with recording — you can use it to play back a tape, as well. While some scenes just can't be re-enacted — like the night my three year old daughter fell asleep in her bowl of spaghetti — most can. Rewind the tape you just made and play it back through the camera. You see the scene — good or bad — in the viewfinder. If there's a problem, record it again. Great, but there is one catch.

# Cameras

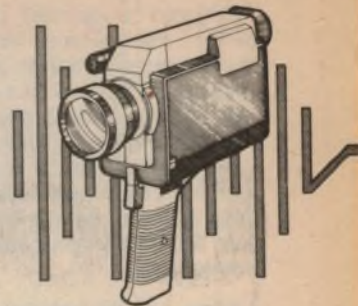

doors in sunlight. But as the light level goes down — say, if you move indoors — an  $f/2$  camera will require additional floodlighting sooner than the 1.4.

Although more expensive cameras do have larger apertures ( $f/1.8$  seems to be about average), the most significant change is in the type of lens you get; it zooms. One twist and you capture the whole family in a wide-angle picture. Another twist and you zoom in for a long telephoto shot. The typical zoom ratio (wide angle to telephoto) is 6:1. Many of these cameras give you macro capabilities: push a button and you can focus on something a few centimetres in front of the lens — a postage stamp will fill the TV screen on playback.

If you're on a limited budget, or not into exotic stamp shots, the standard lens will do fine. And many cameras, such as JVC's economy model, use a standard C-mount for the lens — unscrew the lens and replace it with an upgraded one later if you wish. But if you're a photo fanatic, save a little longer for the better lens — the additional capabilities it offers are worth the wait.

## What you see is what it's got?

In photography, the human head can be decapitated without loss of blood — just a rise in blood pressure for the movie viewers. Properly framing a shot is just as important in video taping. To do it, these new video cameras use one of three methods: optical sighting, through-the-lens, or electronic viewfinding.

The Zenith KC1000, for example, uses the sighting technique. You aim the camera by looking through a pop up viewfinder and lining it up with a front mounted sight atop the camera body. The angle between sets the angle of the camera, properly framing the scene at an average distance. This works fine once you become accustomed to it (and you get plenty of tries since you can erase the video tape and use it again).

The through-the-lens systems (TTL) are



ABOVE & RIGHT: Sony's HVC-2000 Trinitron colour camera and SL-3000 portable VCR are ideal for both indoor and outdoor home movies. The camera features electronic zoom and fade, while SL-3000 VCR lets you record up to three hours of programming.



a step up. Of these — Panasonic's PK-530 is an example — the viewfinder is optically coupled to the front lens, giving you two advantages.

For one, you see precisely what the lens sees — framing becomes simple and error-free. And second, you can manually focus the image as your subjects move. With a telephoto lens, for example, this is a must.

For a film camera, a through-the-lens system is the ultimate. But for video, it's only "next best". Top end cameras use an electronic viewfinder — a tiny 3.8cm black and white picture tube — to show you what's being recorded on tape. You look through a viewfinder equipped with a magnifying lens to see the CRT screen. Framing is simple, focus is precise, and even lighting is taken into account: If you can't see the scene on the CRT, it's not going on tape.

On some cameras, the CRT is mounted inside the rear of the camera body. Others, such as Sharp's QC-35, use an

outboard CRT on one side of the camera. This allows you to move the camera closer to your shoulder for easier handling and better weight distribution. RCA's CC007 uses the same idea, but the CRT will pivot — from left to right side — for minority groups. Being a "lefty", and favouring my left eye for viewing, I found this a definite plus.

The CRT can be used for other things, too. Throw a switch on the Sony HVC-2000, for instance, and you see a display of the video waveform to help you set light levels. And one big advantage of a CRT viewfinder has nothing to do with recording — you can use it to play back a tape, as well. While some scenes just can't be re-enacted — like the night my three year old daughter fell asleep in her bowl of spaghetti — most can. Rewind the tape you just made and play it back through the camera. You see the scene — good or bad — in the viewfinder. If there's a problem, record it again. Great, but there is one catch.

Without a special connector cable (which may or may not be available), most cameras cannot play back a tape unless it's attached to a compatible VCR (usually the same brand). There are exceptions, however, such as Sears' 53811, which has a video IN connection as well as the conventional video OUT for recording. If you're buying a camera only, be sure it is totally compatible with the VCR you're using.

### LEDs, dials, things to try

All video cameras have circuitry that can compensate for a vast range of lighting conditions. But, in extreme changes, additional controls let you help it along.

When our eyes look at the colour white, for instance, we see white, whether it's in bright sunlight or a dimly lit room. To a vidicon tube, however, colour depends upon the colour temperature of the source. A white colour can turn reddish or bluish to the camera, depending upon whether you're shooting outdoors in sunlight or indoors under standard lighting. To compensate for it, all cameras have some sort of tint control (like the colour tint control found on NTSC colour TV receivers). Knowing where to set it is the trick, however.

For many cameras, you simply make a guess at the right setting, based on past experience. (If you're wrong, you can often correct the colour with the tint control on your TV during playback.) But some cameras take guesswork out of it. Push the WHITE BALANCE control on Sanyo's VCC545P camera, for instance, and you can adjust the tint while looking through the electronic viewfinder. Inside, LEDs show you when the colour is correct. The Sears camera gives you a temperature display on a small side meter — aim the camera at a white surface and simply adjust a control until the meter centres.

LEDs play an important role indicating other functions, as well. An underexposure LED, for example, tells you when to add light on a subject or when to readjust the iris to let more light into the lens (some cameras have automatic iris compensation, too). Another LED indicates whether the tape recorder is running or has paused when you press the



RCA's swivel CRT viewfinder allows the camera to be used from either shoulder.



Sanyo's new VCC 545P colour video camera features a built-in electret microphone, an electronic viewfinder, and a horizontal resolution of 250 lines. An AC power adapter (pictured) is included in the RRP of \$1150 (approx).

camera tape-start trigger. Still another LED will show when the portable batteries are low (you've got about five minutes left). All these displays are in the viewfinder — you see the scene you're shooting plus a complete status check in one glimpse.

Depending upon the camera, there are a variety of other special-feature buttons, as well. They're designed to give your tapes a more professional touch. A FADE button, for example, fades into or out of a scene. And a ZOOM button controls a motorised zoom lens for jitter-free movement.

These are fine, but test every feature first, in the store, before you buy. Use a motorised zoom on a camera with a built-in mike, for example, and you may hear the whir of the motor on the sound track during playback. A quick check at the store will tell you.

Naturally, there are other things to check while in the store, too. Weight is one criterion, and the balance of the camera when you're shooting is another. If the camera feels clumsy or heavy, your taping sessions will become a real chore.

Specs? Sure, there are some you can check. Signal-to-noise ratio is one. Noise on a video signal means snow to a picture. The higher the signal-to-noise ratio (expressed in dB), the less snow you should see. Another spec is the horizontal resolution — the larger the number of lines, the better the picture detail. (And it will give you an indication of the vidicon quality — there are many types.)

Some specs become important depending upon how you use the camera. For outdoor portable operation, the lower the power requirement (wattage), the

longer your batteries will last. For indoor use, the lower the minimum lighting spec, the less likely you'll need additional lights on your subject. Audio should also be an important consideration. If you take lots of telephoto shots (or try to tape school plays regularly), an external microphone will help. To use one, however, be sure the camera has an external mike input jack.

### In use

What fascinates me most after using these cameras is how much they've changed me — the instant playback and erase and try again features of video tape make it all fun. I found myself shooting flowers, animals, people I didn't know — all the things I would never consider with three minute super 8.

To be fair, however, super 8 is still more portable than video. Besides the camera, you'll need a portable VCR, fresh batteries, extra tapes, and maybe lights with an extension cord or two. Portable VCR systems do have fantastic advantages for home "movie" takers, but, for now, taking one along on a vacation is like taking your microwave oven along on a cookout.

Despite the portability problem, the results I've gotten from using a video camera have been excellent. And watching home "movies" is no longer a chore. There's no screen or projector to set up — just pop in the tape and turn on the TV. Picture quality is excellent. ☺

Reprinted from "Popular Science" with permission. Copyright © 1980 Times Mirror Magazines, Inc.

# Look to the 'LEADER'

The Function Generator with more flexibility,  
high performance and low cost!

Leader Function Generator LFG-1300—part of the new breed of test instruments from the top international specialists.



Frequency Range from 0.002Hz-2MHz.

Generates Sine, Triangle, Square, Pulse and Saw Tooth Waveforms.

Built-in sweep function with log. and linear sweep.  
Built-in AM modulator.

**LEADER**



Vicom International Pty. Ltd.

68 Eastern Rd.,  
Sth. Melbourne, Vic. 3205  
Phone (03)699 6700

339 Pacific Highway,  
Crows Nest, N.S.W. 2065  
Phone (02)4362766

It won't rust, overheat, drown, rot or crack-up! It just keeps you talking on frequency no matter what the conditions. NIROS 707 is a compact unit for use in the 66-88MHz, 146-174MHz and 420-470MHz bands.

It can be supplied with all types of tone equipment, including a tone

option which allows up to 100 different code numbers.

Its rugged stainless steel construction has been tested in the Danish Research centre for shock, vibration, temperature, water proofing and internal moisture resistance.

Such uncompromising Danish quality ought to cost a fortune. NIROS costs less than at least one other top-selling professional transceiver.

Contact us. We're ready to give you the good word on NIROS now.


## NIROS. It never gives up.



Vicom International Pty. Ltd.

68 Eastern Rd.,  
Sth. Melbourne, Vic. 3205  
Phone (03)699 6700

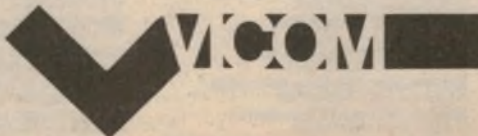339 Pacific Highway,  
Crows Nest, N.S.W. 2065  
Phone (02)4362766



# PARTS FOR NEW KITS

If a kit you want to build is not listed, the parts may be available anyway. Check the Dick Smith Catalogue or call in to your nearest Dick Smith store.

## CRO SWITCH (See EA February)

Complete kit Cat. K-3517 \$69.50  
PCB only Cat. H-8392 \$3.75

SYSTEM 80 RS 232 INTERFACE (see EA February)  
PCB only Cat. H-8391 \$2.25  
All other components in this kit are normal stock lines

## GUITAR FUZZ BOX (See EA February)

PCB only Cat. H-8390 \$2.15  
All other components in this kit are normal stock lines

MINI SPOT 455kHz GENERATOR (See EA February)  
PCB only Cat. H-8389 \$1.75  
Other components in this kit are normal stock lines

## AUTODIM (See EA Jan)

PCB (avail mid Jan) Cat. H-8388 \$3.50  
All other parts are normal stock lines

ETI MOSFET AMPLIFIER MODULE (See ETI January)  
PCB (available mid January) Cat. H-8633 \$9.95  
Power Mosfets (low cost medium power types as above) Cat. Z-1815 \$16.00 pr

## SELECTALOT (See EA December)

PCB Cat. H-8384 \$2.95  
All other components are normal stock lines

## AC MILLIVOLTMETER

PCB Cat. H-8385 \$2.25  
All other components are normal stock lines

SYSTEM 80/TRS80 INTERFACE (See EA Nov)  
PCB Cat. H-8383 \$1.90  
All other components are normal stock lines

PLEASE NOTE: ABOVE PROJECTS AND PRICES ARE SUPPLIED FROM MAGAZINE'S ESTIMATES ONLY

# GET BOOKED!

**Solid State Basics**  
Doug Demaw & Jay Rushgrove. 158 pages.  
Contains a complete beginners course in solid state theory. This is backed up by simple & useful projects that you can build. Illustrated & easy to follow.  
Cat. B-2224 \$6.75

**Solid State Design**  
Wes Hayward & Doug DeMaw. 256 pages.  
Radio amateurs extend your theoretical understanding of solid state devices. You'll be surprised at what you can do by designing circuits: test equipment, transmitters etc etc!  
Cat. B-2211 \$12.00

# You'll save \$\$\$!

**ARRL Electronics Data Book**. 128 pages.  
Edited by Doug DeMaw.  
This book covers math equations, data charts, explanations of technical terms & MUCH MORE! A must for any radio amateur experimenter.  
Cat. B-2203 \$6.75

**Practical Basic Programs**  
Edited by Lon Poole. 175 pages.  
If you are having difficulty in finding a practical application for your computer - look no further. Applications include finance (home budgeting, statistics and many others that could help you save \$\$\$!)  
Cat. B-2344 \$16.50

# HOBBYISTS/EXPERIMENTERS Try this handy PHONE PLUG!

This handy plug is ideal for many experimental applications. Use it for intercom connections, amateur radio projects etc. Hobbyists: buy one for the junk box, you may never know when you need it!  
NOTE: Not approved by Telecom for replacement of standard phone plug.  
Cat. P-5700 \$2.50

**Your First Computer**  
Rodney Zaks. 280 pages.  
Whether you are about to buy a computer or own one already, this book would be a valuable aid. You'll learn the many facets of a computer system - written in everyday language.  
Cat. B-2388 \$8.95

**You just bought a Personal WHAT?** Thomas Dwyer & Margot Critchfield. 340 pages.  
Let your imagination go... think of all the programs you can do with your new computer! This book educated the beginner & gives a structured approach to creative programming. There's even a section on business finance plus a chapter on expanding your computer system.  
Cat. B-2331 \$15.95

# A DREAM COME TRUE! FT902D With the new WARC bands!

**The Dick Smith SUPER CRO AT A SUPER PRICE!**  
OUTPERFORMS CRO'S COSTING MUCH MORE!  
We've sold 100's of these quality 6.5 Meg CRO's. Ideal for technicians, hobbyists, teachers etc.  
● 10mV/DIV SENSITIVITY  
● 10Hz-100kHz SWEEP FREQUENCY  
● INCREDIBLY LOW PRICE!  
Cat. Q-1280 \$199.00

# The Dick Smith SUPER CRO AT A SUPER PRICE!

Most amateurs dream about a rig like this, now the dream is within your reach! All mode digital readout, new WARC bands factory fitted. This superb transceiver represents the absolute state-of-the-art in amateur communications! Don't forget, we offer terms (to approved personal customers) and Bankcard.

# The Kambrook TIME MACHINE

It may be no TARDAS, but Dr Who probably uses one to switch on & off K9 (His robot dog), security lights, electric jugs & frypans, the pool filter etc etc. It can switch on and off any appliance within a 24 hour period - you just set the time!  
Cat. X-1120 \$19.95

# VVR0000MM!! NEW LED TACHO KIT

Get the best from your car's engine. As with a conventional tachometer it displays the engine speed in an analogue form - but with an illuminated row of LEDs! It indicates at a glance what your engine is doing, without having to mentally interpret a numerical display as with a conventional tachometer. YOU DON'T TAKE YOUR EYES OFF THE ROAD! Use with 12V positive or negative earthed systems. Only 3 connections are required and it is easy to build. Complete with instructions.  
Cat. K-3240 \$24.50

# WATCH THIS SPACE AND FIND OUT WHAT YOU MISSED

Each month all of our stores feature an outstanding special which is actually BELOW COST! N B Specials are strictly while store stocks last. Don't miss out!

**LAST MONTH:**  
AM/FM PORTABLE RADIO  
Normally \$22.50; reduced to \$11.95

# ECONOMY CALCULATOR WITH LCD READOUT!

A bargain for pocket or purse. Batteries last for ages. Auto switch off.  
Cat. Q-3025 \$9.95  
Cat. Q-3015 \$19.95

# DON'T GET LOST!!! (This side of the 'Rabbit Proof Fence')

Next time you go holiday in a remote area take one of these with you just in case you get lost! Can tune into a radio station and be able to pinpoint its direction. Makes it ideal for bushwalkers, campers, fishermen etc etc. Has 5 bands: AM/FM/VHF/SW/MARINE. At this price you can't go wrong!  
Cat. D-2820 \$125.00

# YOU AIN'T HEARD NOTHING YET! If you think your hi-fi sounds good, these units will make them sound GREAT!

**EQUALISER**  
Easy to build, easy to fit, easy to use! The Graphic Equaliser can adjust individual bands of frequencies in both channels to make up for system deficiencies, room effects and so on. Build now and save!

**ANALYSER**  
To get the most from an equaliser you need to know where your system deficiencies are. The analyser tells you! So you and up with clear, pure sound! And this superb kit also doubles as a LED level meter: looks good, works really well! Complete with instructions.  
Cat. K-3510

**EITHER UNIT NORMALLY SELLS FOR \$99.50 NOW \$89.50!!!**  
TIMBER SLEEVE SHOWN IS OPTIONAL AT EXTRA COST FOR THAT PROFESSIONAL LOOK: ONLY \$8.50 (Cat. H-3113)

# SAVING \$10.55!

**TALKING COMPUTERS! Acoustic Coupler kit**  
Cat. K-3605 \$75.00

**READY FOR UHF?**  
Specially made for Dick to suit Australian standards. Adjustable decoupling in 2 directions: very important for good UHF reception. Uses standard 300 ohm ribbon.  
Cat. L-4028 \$19.95

**DUSTY DISKS?**  
Do you have valuable diskettes just lying around collecting dust? This library case will protect them from dust, dirt, heat etc. Holds 10 diskettes! Store away or folds into convenient position.  
Cat. X-3515 \$5.95

# THE RATINGS ARE COMING... So why not get the best reception & SAVE!

Don't put up with John Wayne's Ghost appearing or a treasy Raquel Welch on your screen this season! Our antennae will get the bug out of bad reception.  
**Boost that signal...**  
With this mast head amplifier. Use with 75 or 300ohm coax. Gives 18db gain!  
Cat. L-4200 \$39.50  
The big gun for more difficult areas. 75 ohm. Use coax or twinlead. Cat. L-4030 \$54.50

**SAVE \$10.00 ON THIS GREAT PHONE DIALLER!**  
This is the ideal dialler for the experimenter, hobbyist etc. Features push button dialling plus a last number re-call! **WASS49.50**  
NOTE: Although this connects easily to the standard Telecom phone (no soldering required), present regulations do not permit so.  
Cat. X-1175 \$39.50

**CAN'T PUT IT UP? CHECK OUR HUGE RANGE OF TV ACCESSORIES**  
Here are just a few...  
28cm WALLMOUNT \$4.25  
69cm WALLMOUNT \$4.95  
CHIMNEY MOUNT \$9.75  
CABLE PLUGS, SOCKETS, BALUNS. You name it - we got it!

# MAJOR DICK SMITH RE-SELLERS:

- Listed below are re-sellers who stock a large proportion of our range. However, we cannot guarantee that they will have any or all of the items, or at the same prices, as those advertised on these pages.
- ATHERTON, QLD:** Tabilinum Radio Service 2 Jack Street, Phone 812 017
  - BENDIGO, VIC:** Sumner Electronics 95 Mitchell Street, Phone 431 577
  - BLACKHEATH, NSW:** Goodwin Electronics 123 Station Street, Phone 878 379
  - BROKEN HILL, NSW:** Crystal TV Rentals 88 Crystal Street, Phone 687
  - CAIRNS, QLD:** Thompson Instrument Services 78-81 McLeod Street, Phone 512 404
  - COFFS HARBOUR, NSW:** Coffs Harbour Electronics 3 Coffs Harbour Plaza, Park Ave, Phone 525 884
  - DARWIN, NT:** Kent Electronics 42 Stuart Highway, Phone 814 749
  - DURBO, NSW:** Seleka Sound 31 Talbeger Street, Phone 828 879
  - EAST MAITLAND, NSW:** East Maitland Electronics, Car Laws & High Streets, 337 327
  - FAIRY MEADOW, NSW:** Trillogy Wholesale Elect. 40 Princeas Hwy, Phone 821 218
  - GEWALTON, WA:** KD Electronics & Marine 361 Main Terrace, Phone 212 178
  - GOSFORD, NSW:** Tomorrow's Electronics & Hi Fi 88 William Street, Phone 247 248
  - HOBART, TAS:** Aero Electronics 123 Bathurst Street, Phone 348 232
  - KINGSTON, TAS:** Kingston Electronics & Records Channel Cove, Phone 258 027
  - LAUNCESTON, TAS:** Audet Electronics 5a The Quadrant, Phone 317 025
  - LISMORE, NSW:** Ocea Electric Magellan St & Bruzard Hwy, Phone 214 137
  - MACKAY, QLD:** Stevens Electronics 42 Victoria Street, Phone 511 723
  - MARYBOROUGH, QLD:** Keller Electronics 218 Adelaide Street, Phone 214 569
  - MORUYA, NSW:** Coastal Electronics 43 Vulcan Street, Phone 742 545
  - MT GAMBIER, SA:** Hutchasson's Communications 5 Elizabeth Street, Phone 258 404
  - MUSWELLBROOK, NSW:** Silicon Chip Electronics Suite 3, 98 Bridge Street, Phone 43 1098
  - NAMBOUR, QLD:** Nambour Electronic Shop Shop 4 Lawton House, Ann St, Phone 411 804
  - NEWCASTLE, NSW:** Elektron 2000 181 Wharf Road, Phone 282 844
  - ORANGE, NSW:** M&W Electronics 48 McKinnon Street, Phone 828 491
  - ROCKHAMPTON, QLD:** Puruly Electronics 15 East Street, Phone 21 058
  - SOUTHPORT, QLD:** Amateur's Paradise 121 Norang Street, Phone 322 844
  - TANWORTH, NSW:** Sound Components 78 Brisbane Street, Phone 881 383
  - TOOWOOMBA, QLD:** Munis Electronics 18 Neil Street, Phone 328 944
  - TOWNSVILLE, Qld:** Tropical TV 49 Fulham Rd, Vincent Village, Phone 781 421
  - TRARALGON, VIC:** Power N' Sound 147 Argyle Street, Phone 743 838
  - WAGGA, NSW:** Wagga Wholesale Electronics 82 Forayth Street
  - WINDSOR, NSW:** Hawkesbury Electronic Centre 111 George Street, Phone 773 411
  - WOODONGA, VIC:** A & M Electronics 78a High Street, Phone 244 588
  - WYALLA HORRIE, SA:** Mellor Enterprises Shop 2, Forayth Street, Phone 454 764

# WOULD YOU LIKE TO BE A DICK SMITH RE-SELLER?

How would you like to join the hundreds of successful Dick Smith re-sellers, spread right across Australia? If you're interested, why not give our wholesale division a call - Sydney (02) 888 3200 9AM - 5 30PM weekdays. It could be the start of something big.

# LOOKING FOR A LIGHT SHOW?



**EA CHASER**

Add life to your next party with this incredible Light Chaser. Features include reverse/forward chasing, variable flash rate control plus an invert/normal switch. This switch can make 2 lights appear to move instead of 1 at a time. The versatility is increased with 'auto reverse & inverse' functions. This automatically inverts or reverses the display at any rate. All this makes it a worthwhile project that will save you \$55 and give hours of entertainment.

**\$69<sup>50</sup>**

Cat. K-3145



**EA MUSI-COLOR**

Turn your music into a coloured light show. This unit will accept an audio input from almost any amplifier and uses the information to control 3 channels of colour. Both the MusiColor and the Light Chaser are easy to build and come with detailed instructions. Makes it ideal for parties, discos, rock bands/concerts etc.

**\$59<sup>50</sup>**

Cat. K-3140

# BARGAIN COMPUTER TAPES!

We've made a HUGE SCOOP PURCHASE of world renowned Memorex computer cassettes for computer recording is also ideal for recording notes etc (no drop outs)! These are professional quality (we've used them in our \$25,000 computerised photo-type setter and they're perfect!) These tapes are selling for less than HALF our normal computer cassette price - and they're much longer! Hurry - this is definitely a once-only offer. Buy now & save a fortune!



**SIMILAR TAPES SELL FOR \$12.00 EACH!**

**OUR PRICE: 95¢!!!**

Cat. X-350

## TEST IT! TRANSISTOR TESTER KIT



This one tests bipolar transistors, diodes, FETs and even SCR's & PUT's. It's a low cost and practical instrument simple enough for a beginner to build. Ideal also for the serviceman. A valuable piece of test equipment you can't afford to miss! Cat. K-3052

**\$15<sup>00</sup> WAS \$19.95!**

## BEAUT MINI ORGAN



Have hours of fun with this easy to build mini organ kit. Microprocessor technology provides versatility including tremolo & variable depth plus 2 switchable voices. Comes complete with speaker & instructions (batteries & case not supplied). Cat. K-3430


**WAS \$29.50! NOW \$19<sup>50</sup>**

## IT'S HERE! THE ALL NEW PLAYMASTER MOSFET AMP

**SEE PAGE 57 FOR FULL DETAILS!**
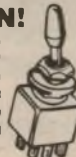
## TOGGLE SWITCH BARGAIN!

A DPDT mini toggle switch for only \$1.25! Contacts are rated at 125V 10A (but great for 240V at lower current). As used in just about every EA & ETI project. Normally \$2.50 each but our bulk buying power enables us to slash the price. YOU REAP THE BENEFIT!! Cat. S-1168



**WAS \$2.50! NOW \$1<sup>25</sup>**

## LEDS AND LADDERS GAME



One of our most popular kits of the past was the intriguing 'LEDS & LADDERS' game described in EA 1975. Now EA have come up with another version which is easier to build and play. Can you climb out of the well without being plummeted down again?

**AND NOW FOR THE BEST NEWS:** This kit is actually \$1.00 cheaper than it was in 1976 - despite 4 years of inflation! **WAS \$16.75 in '76 NOW ONLY \$15<sup>75</sup>**

Cat. K-3390

## NEW NEW NEW NEW NEW MINI SOLDERING IRON

This is the perfect iron for working on computer boards or any other detailed area. Comes with spare copper tip and heats up in seconds! The voltage is low so it is safer to work in these 'delicate areas'. Connect up to a car cigarette lighter plug (Cat. P-1875 @ 70¢) and you can repair things in the car!

**\$6<sup>95</sup>**



**COMING SOON!**

Cat. T-1920

**TRANSFORMER TO SUIT:** Cat. M-2155 multtap **\$4<sup>00</sup>**

**SPARE TIPS:**

**\$1<sup>50</sup>  
\$1<sup>50</sup>**

Conical Cat. T-1921  
Wedge Cat. T-1922

## MEASURE IT WITH A DICK SMITH PANEL METER

The MU range are of high quality with a full scale accuracy better than 2%!

0-1mA - 120ohms	0-2010	<b>\$8<sup>50</sup></b>
0-50uA - 1400ohms	0-2020	<b>\$8<sup>50</sup></b>
0-5A DC - 3ohm (shunt)	0-2030	<b>\$8<sup>50</sup></b>
020V DC - 100ohm	0-2040	<b>\$8<sup>50</sup></b>




Dimensions: 100mm(w)x82mm(h)  
MILLIAMPERES 1ma-120ohms 0-2080 **\$12<sup>50</sup>**  
MICROAMPERES 100uA-1400ohms 0-2070 **\$12<sup>50</sup>**

**SAVE EVEN MORE ON BULK PURCHASES!**
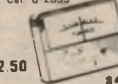
## TUNER PANEL METERS

As used in the famous Playmaster Tuner kit, these meters provide many uses for the hobbyist etc. Attractive finish. Cat. Q-2095



**\$2<sup>00</sup> \$3<sup>00</sup>**

**WERE \$4.95 EACH!**

## RESISTANCE SUBSTITUTION WHEEL

Convenient size with large easy to read value selection that enables you to select values from 5 ohms to 1M ohm in 36 steps! Complete with leads and insulated crocodile clips. Fantastic for the experimenter, designer, hobbyist & serviceman. Buy a few & save hours of soldering!




**\$5<sup>95</sup>**

Cat. Q-1410
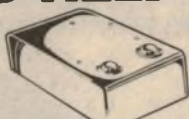
## CAR COSTS BEATING YOU? CDI COULD HELP

Thousands of happy motorists are saving money with CDI. You could join them! A Capacitor Discharge Ignition System could do any - or all - of these in your car:

- Increase spark energy giving better fuel combustion
- Help dirty or fouled plugs to fire - increasing time between plug changes
- Increase points life by lowering current through them - so car stays in tune longer
- Give better cold and hot starts by maintaining firing voltage during cranking
- Help in wet weather driving



**COMPLETE KIT:**

**SAVE! WAS \$32<sup>50</sup> NOW: \$25<sup>00</sup>!**

Cat. K-3280

## FUN WAY INTO ELECTRONICS

### FUNWAY 1

It has to be the best way to learn electronics! The unique breadboard wiring system is simple, safe & a lot of fun. There are 20 exciting projects to build including the famous Beer Powered Radio!


**B-2600 72 pages \$4<sup>95</sup>**

### FUNWAY 2

Once you've enjoyed Funway Volume 1, why not step up to volume 2! Features 20 practical projects. There is full information on how to solder PLUS a guide to using your multimeter. Learn how to make PCB's. PLUS MUCH MUCH MORE! You'll have fun learning & building these projects & using them for a worthwhile purpose.

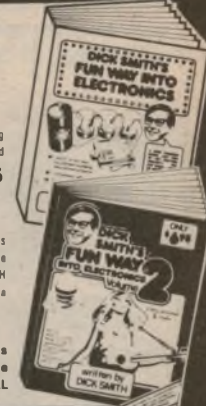**B-2605 128 pages \$6<sup>95</sup>**

**TEACHERS:** Funway into Electronics has enormous educational benefits. Why not ask about our incredible discounts for bulk orders (10 copies or more) YOU'LL SAVE A BUNDLE!



## 3 INPUT AUDIO MIXER KIT



K-3492

**\$35<sup>00</sup> WAS \$49.50!**

Specially designed for the home recording enthusiast, this unit has more features than others selling for over \$100! Features autotune from one channel to another for voice over music dubbing plus full bass and treble control. Also has 3 inputs with gain controls plus a master control! Complete with instructions

## SPEAK UP! TELEPHONE AMP

Now you can let everyone hear that telephone message! This telephone amplifier has a sucker that attaches to the telephone. When someone calls, just switch on the unit to hear the caller loud and clear!



**COMING SOON! \$12<sup>50</sup>**

Cat. X-1174

## Build these simple kits & save \$\$\$!

### CONTINUITY TESTER

Checks the continuity of electrical circuits & components. Also gives an indication of continuity over a resistance range from zero to many thousands of ohms! Simple to build, it provides a valuable tool for the hobbyist when fault finding in projects. **\$4<sup>00</sup>** (not illustrated) Cat. K-2041

### 2 OCTAVE ORGAN

Utilise your ingenuity! cheap and simple to assemble this monophonic organ is tuneable, covering a full 2 octaves and ranging from C262-C1047Hz at 12 notes per octave. Ideal for the budding musician. Keyboard materials not supplied - you can use your own ingenuity! Cat. K-2072 (not illustrated) **\$8<sup>50</sup>**

**NOTE:** Instruction book is required to build these kits: Cat. B-3852 @ \$4.75

# DICK SMITH ELECTRONICS


## BUYING BY MAIL?

ORDER VALUE:	P&P
\$5 (min) to \$9.99	\$1.00
\$10.00 to \$24.99	\$2.00
\$25.00 to \$49.99	\$3.00
\$50.00 to \$99.99	\$4.00
\$100 or more	\$5.00

**NOTE:** These charges apply to goods sent by post to Australia only. Large and bulky items cannot be sent by post. If you prefer, we will dispatch your order by Comair Road Freight to anywhere in Australia for only \$8.00 - that's below what it costs us! Large and bulky items are normally sent by Comair unless you specify differently (eg by rail or air - you pay freight on delivery)
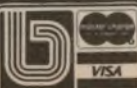
## COMPUTER HOTLINE

Want to know more about our computers? Or maybe you're having problems and need advice. For friendly, helpful information on System 80 or Sorcerer computers, or on any of our peripherals, phone our Computer Hotline: **Monday - Friday, 9 - 5.30 on Sydney (02) 888 2002**



<b>NSW</b>	145 Parramatta Rd	<b>AUBURN</b>	648 0558
	613 Princes Hwy	<b>BLAKEHURST</b>	546 7744
	818 George St	<b>BROADWAY</b>	211 3777
	531 Pittwater Rd	<b>BROOKVALE</b>	93 0441
	147 Hume Hwy	<b>CHULLORA</b>	642 8922
	162 Pacific Hwy	<b>GORE HILL</b>	439 5311
	30 Grossa Street	<b>PARRAMATTA</b>	683 1133
	125 York Street	<b>SYDNEY</b>	290 3377
	263 Keira Street	<b>WOLLONGONG</b>	28 3800

<b>ACT</b>	96 Gladstone St	<b>FYSHWICK</b>	80 6944
<b>QLD</b>	166 Logan Road	<b>BURANDA</b>	391 6233
	824 Gympia Rd	<b>CHERMSIDE</b>	59 6255
<b>SA</b>	60 Wright Street	<b>ADELAIDE</b>	212 1962
<b>VIC</b>	399 Lonsdale St	<b>MELBOURNE</b>	67 9834
	656 Bridge Road	<b>RICHMOND</b>	428 1614
	Dandenong Rd	<b>SPRINGVALE</b>	Open soon
<b>WA</b>	414 William St	<b>PERTH</b>	328 6944

**DICK SMITH MAIL ORDER CENTRE:**

PO Box 321, North Ryde NSW 2113. Phone (02) 888 3200

SERVICE CENTRE: LANE COVE & WATERLOO ROS, NORTH RYDE NSW 2113.

PHONE (02) 888 3200. HOURS 9AM TO 5PM, MONDAY TO FRIDAY ONLY.

**SHOP HOURS:** 9AM TO 5.30PM MONDAY TO FRIDAY; NOON SATURDAY (Brisbane stores half hour earlier). Some stores are open on late shopping nights; please phone your local store to check before coming in!

# Glass bottles with lights in them

Readers of "The Serviceman" column in "Electronics Australia" over the years will have noticed valves disappearing from his case histories as solid state devices have displaced them. To one retired radio serviceman, however, those "funny glass bottles with lights in them" still remain an absorbing interest.

by **BEN FURBY**

Keith McIlraith, now 70 years old and in retirement in the city of Christchurch in New Zealand's South Island, still has the Browning Drake kitset receiver he bought as a boy and assembled – and over 100 other valve radio receivers as well. He remembers using the Browning Drake to listen to the radio coverage of the first attempt to fly the Tasman on January 10, 1928, by fliers Moncrieff and Hood in a Ryan monoplane. Wellington's leading station stayed on the air until 2am that night, but the fate of the fliers is unknown to this date.

Possibly they overflew New Zealand in the darkness, or crashed in dense bush in

some remote spot. In New Zealand the latter idea is still considered, and there is still interest in the possible discovery of the Ryan's wreckage, after 52 years.


In New Zealand, radio servicemen are licensed by the Electricity Registration Board, and after working for a while in a shop, Keith McIlraith turned his hobby into a career and qualified as a radio serviceman. In the town of Ashburton, 80km south of Christchurch, he operated his own business with considerable success until retirement – and collected radios as a matter of personal interest.

In retirement, the collection has become a major interest for him. Besides restoring the electronic componentry to operating order, cabinets often need ma-


ior refurbishing: replacement of sections or veneers, and varnishing and repolishing to restore the former glory of these pre-television receivers. In many of the sets repaired, the restoration of major parts of the cabinets has been done so well that the work is barely noticeable.

Few Australian receivers were sold in New Zealand prior to World War II, and as local manufacture grew, the engineering tended to follow mostly USA radio practice. The post World War II shortage of US dollars created an opportunity for other manufacturers which Philips, always an active marketer and manufacturer in New Zealand, was quick to exploit. Philips' aggressive post-war marketing saw American valve types replaced by Philips equivalents and the widespread use of the European valve type code. AWA, also active in New Zealand, but more as a component supplier and a source of equipment, such as broadcasting transmitters, has always been prominent in New Zealand electronics.

Visiting Keith McIlraith's collection of

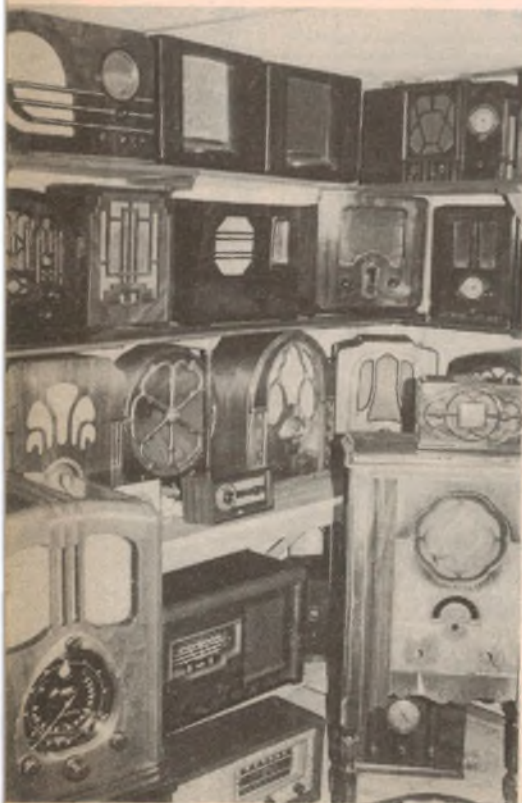

ABOVE: Keith McIlraith holds a radio receiver he made about 1925. It used two 01A valves and a crystal detector, and gave good reception on headphones. Other receivers in this photo and the photo at left include: 1923-24 Crossley (USA) 5-valve; 1931 Philco (USA); 1929 Philips 4-valve; Astor (Aust.) 5-valve; 1935 Cromwell (NZ) 5-valve; 1934 Stewart Warner (USA) 5-valve; 1932 Decca (UK) 4-valve; 1936 Stromberg Carlson (Aust.) 5-valve; and a 1938 Columbus (NZ) 7-valve.

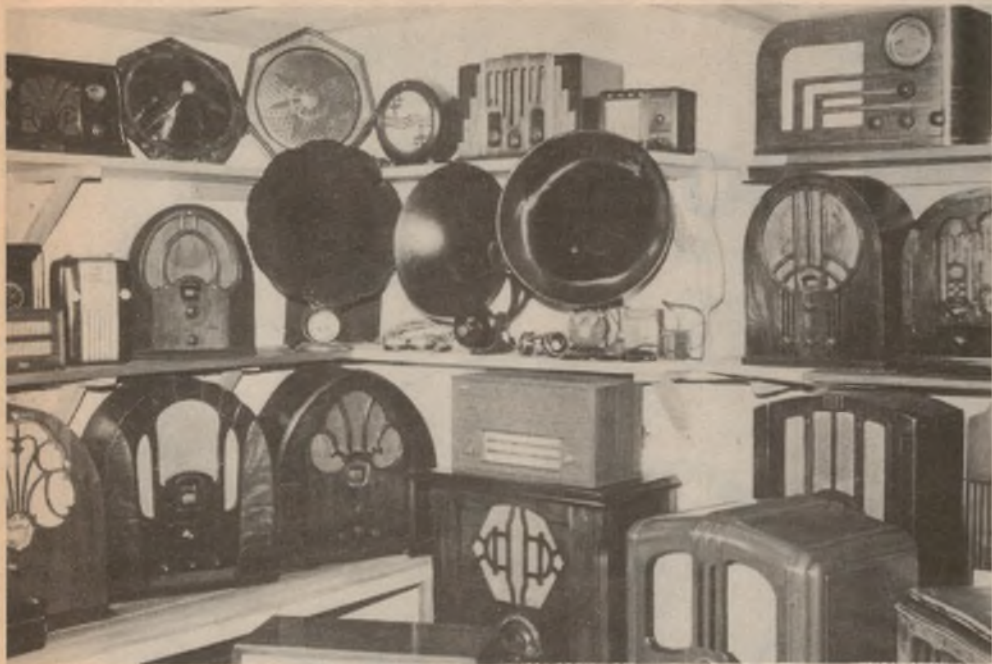

*Some of our older readers will recognise at least some of the brands in Keith McIlraith's collection. Famous makes include Zenith (USA), Philips, HMV, Air King (USA), Culbransen (NZ), Burndept (UK), Amplion (UK), Philco (USA), Atwater-Kent (USA), Stewart Warner (USA), Radiola (Aust) and Astor (Aust).*

radios is a true walk down Memory Lane: names of manufacturers, once famous in radio and "wireless", are recalled by those with many years' association with the industry. The lineup of receivers also reminds us that Australia and New Zealand once had many competent radio manufacturers who built an efficient local industry that contributed considerably to those nation's efforts during World War II.

**THERES NOTHING NEW  
UNDER THE SUN,  
BUT IF THERE IS  
WE'VE GOT IT**



**NEW FROM SOUNDOUT  
DISCOTHEQUES FROM \$650.**

Speaker enclosures from \$150.

Featuring the excellent BD55 Belt drive turntables — turntables and mixers also available separately. Light chasers include the compact Saturn four chaser with snake light attachment made to Australian Energy Authority standards. Colorgram 44 Light Control systems, snake lights, projectors with effects including panoramic rotators and dynagraph units giving inexpensive Laser effects, lighted dance floors, wooden dance floors, space beacons, strobes, infinity panels, Cash-moramic projector panels, mirror balls — oval and round, 12 to 36 inch. Pyrotechnic smoke effects. Bubble machines.



OUR BAND GEAR boasts Frunt, PA guitar and bass amplifiers, Soundout 200 mixer amp heads and slave amps, stands, Bands, please note that we have rehearsal rooms with or without gear, and an excellent film studio with full Cyclarma, for film clips for when you really make the big time!



For further information please call us on (02) 798 5647 or (02) 797 7022. You'll love our ASS (after sale service). Interstate buyers — we'll pay the surface freight.

**CASH-MORE  
ENTERPRISES**

**354-356 LIVERPOOL RD,  
ASHFIELD, SYDNEY**



# Twenty-five years from now



By W. M. WEBSTER

Technological change in home entertainment electronics, energy generation, and transportation will proceed more slowly over the next 25 years. But more importantly, sociological and economic pressures will play an increasing role in the selective development of technologies in these areas.

My assignment is to speculate about the world of 2005 – the end of the second 25 years of the *RCA Engineer*. To prepare myself for this assignment, I dug out a speech made by General Sarnoff in 1956 predicting some things about the world of 1976. This speech was one of the things that made me swear off making predictions.

In fairness, however, General Sarnoff was quite accurate in areas that he knew a lot about, such as television. I will learn from this and limit my comments to two areas: electronics with emphasis on the consumer, and energy including transportation. The main problem is in deciding what is likely to happen out of the many things that are or may become technically possible. In any event, it is unlikely that I'll worry much in 2005 about my accuracy – so here goes.

## Electronics

Network and broadcast TV will still be with us. But television executives will emphasise news, interview and talk shows, and other formats that depend on immediacy. Also, alternative methods of delivering entertainment, such as pay TV and video disc, will partly displace broadcasting.

Low-cost digital technology will displace analog methods for most video signal processing but not for most transmission to the home. Digital transmission, however, will distribute signals via ground networks and satellites to broadcasters and cable operators.

The digital audio disc based on video disc technology will have a medium-sized market. But the audio disc will be less popular than the video disc, since most people will prefer good sound plus the picture.

Nearly every home in urban and suburban America will be connected to cable. And the cable will be two-way, with the upstream direction used for signalling and for low-speed data transmission. Access to channels carrying pay TV will be allowed or denied on a per-program, per-subscriber basis. Cable also will provide the main access to the services and databanks being market-tested today in Europe, Japan and the US. I think that the broadcast version of these services (similar in concept to RCAs "Homefax") will be introduced in the 1980s.

The systems which give telephone access to many different sources, but at a lower data rate, will be available in the

1980s, too. By 2005, these systems will be largely replaced by a switched system using the TV cable to achieve both the variety and the high data rate. This could be a connection supplied by the telephone companies. However, I think that the economics favour the development via cable. Distribution of these data services together with broadcast TV and pay TV, particularly of live shows such as sports, will share about equally the cable capacity.

With such widespread use of cable and the existing diversity of the broadcast system, I don't see a need in the US for direct broadcast from satellite to home. Although the technology will certainly be available, not enough homes will be without cable or be able to pay for the direct broadcast system. Direct transmission from satellite to home will be a reality in many other countries, however. Where the government owns the broadcasting system and particularly where no other system has yet been built (as in some Third World countries), the economics are quite different and will favour direct transmission from satellites.

A video disc with double the resolution in both the horizontal and vertical directions will be introduced in the mid-1990s. This high-resolution video disc will use an encoding technique that will permit compatibility with older players. Cable TV and probably broadcast TV will follow this lead. And, of course, the pictures will be displayed on a large, flat panel.

I have not put a computer in every home in 2005. Terminals with some intelligence will access the services and data I mentioned earlier. Some people will have fairly sophisticated terminals but I doubt it will be a mass market.

A great deal of intelligence, however, will be built into other things in our homes and autos. Appliances will be under microprocessor control. Discriminating switches will turn on lights, for example, only after sensing the simultaneous presence of darkness and a person. Room thermostats will operate similarly.

## Energy and Transportation

By the year 2005, we will have had a war over energy or we will have learned to live with reality. In the first case, it would likely escalate to World War III and all predictions are off.

I believe that US energy needs will be somewhat reduced in 2005 – perhaps by as much as 15 percent of today's usage. More efficient climate control and more efficient transportation, both developed because of rising costs, will be mainly responsible for the reduction.

Use of passive solar heating, better insulation and efficient energy management will be economic realities by 1995. Photovoltaic solar cells will supply about 10 percent of our electrical needs in 2005. Nuclear power plants will supply 30 percent and the rest will be generated mostly by coal. None of these sources will be cheap.

There will be new oil and gas found, and liquid fuels will be developed from coal and alcohol. The energy packing-density of liquid fuels will increasingly reserve them for transportation. Gas, both natural and synthetic, will increasingly be used for residential heating because of the in-place delivery system.

The American public will not give up the automobile and the independence it provides. Mass transportation will continue to be used by commuters and for long-distance travel between large cities. Although the railroad system will have to be improved and rebuilt to deliver coal, the consequences will be some shift from roads to rails for goods but not for people. Instead, the autos of 2005 will be two- and four-passenger vehicles (for smaller families) of very lightweight but high-strength construction. The structural concepts used in aircraft construction will be adapted and plastics will replace steel. A comfortable two-passenger car with an empty weight of 550kg will get 30km/l. The difference between city and highway mileage will decrease because microprocessor-controlled stoplights connected in networks will phase themselves to the traffic needs.

I expect that the rate of technological change in the next 25 years will be slower in these areas than it was in the past 25 years. But one cannot anticipate



**Bill Webster**, Vice President, RCA Laboratories, is responsible for directing RCAs central research organisation, located at the David Sarnoff Research Center, Princeton, New Jersey. He is also responsible for direction of technical programs at Laboratories RCA Ltd in Zurich, Switzerland; RCA Research Laboratories Inc in Tokyo, Japan; and RCAs Solid State Technology Center in Somerville, New Jersey.

A leader in the field of solid-state physics, Dr Webster joined RCA Laboratories in 1946 and made numerous contributions to tube and transistor developments. From 1954 to 1959, he was Manager of Advanced Development for the RCA Semiconductor and Materials Division. He returned to RCA Laboratories as Director of the Electronic Research Laboratory in 1959. He was appointed Staff Vice President, Materials and Device Research, in 1966 and has been in charge of RCA Laboratories since 1968. He was elected to his present position of Corporate Vice President in 1969.

major inventions such as the transistor which completely revolutionised our world and made today's computer technology possible. While other such revolutionary inventions are probable in the next 25 years, we engineers will have plenty to do to develop the technologies we already know about and to put them into profitable use.

## Conclusion

In order to keep all predictors humble, let me remind you of the technical innovations of the past 25 years. In addition to the integrated circuit, solid-state memories and the microprocessor mentioned earlier, there were the Salk vaccine, manned space flight, lasers, microsurgery, the heart transplant, the "Pill", and permanent-pressed clothes. Some of these were perhaps predicted in 1955. But, I don't remember.

Copyright © 1980 RCA Corporation.

## Sensitized Copper Board Riston 3000 Coated

(Fibreglass Base)

	Single	Double
36 x 24	\$45.00	\$57.00
24 x 18	\$22.50	\$30.00
18 x 12	\$12.50	\$16.00
12 x 12	\$ 8.00	\$10.75

OTHER SIZES ON APPLICATION

Developer \$4.25 litre  
Concentrate (1 = 4) \$9.50 litre

All plus 15% ST & Freight if applicable

**BPF**

## Colour Computer

Full business and games capability.  
Console Monitor Power Supply.  
\$865 + ST if applicable.

**KALEX**

101 Burgundy St,  
Heidelberg 3084  
(03) 458 2978  
Telex AA 37678

and at MELTON (03) 743 1011

ELECTRONIC COMPONENTS & ACCESSORIES

**LOOKY**

## VIDEO

Shop: 418 Bridge Road, Richmond, Vic.  
Mail: PO Box 347, Richmond, 3121, Vic.

### HOLIDAY SPECIALS

- 8K Expansion kits \$79.00 (\$120.00)
- Assembled and tested \$94.00 (\$135.00)
- U14 Word Processor \$39.00 (\$99.00)

### OSI HARDWARE FOR OHIO COMPUTERS

Superboard II	\$395.00
Sil Covers/VDU Stands (plastic)	\$18.95
RF Modulators 5/9V	\$19.95
EPROM with single Key Basic and Cursor control	\$49.95

### OSI SOFTWARE FOR OHIO COMPUTERS

Over 100 titles for C1P/SII, C2/4P, enquire Categories are: Games, Education, Business, Text, Instructions (Modifications), and Utilities.  
K.2. Catalogues. Brief description of all programs, free hints. New enlarged version, \$3.50, PLUS \$1.00 P&P.

Example of titles:	
G33 Grand Prix	\$9.95
G37 Nuclear Sub (2 tapes) Adventure	\$18.95
U19 Cursor/Editor C2/4	\$11.95
U20 Mini-Assembler	\$9.95
U24 Sound Effects	\$9.95
I25 RTTY for C1P	\$16.95

Now available blank digital tapes  
C10 \$1.85 ea. Less for lots of 10 or 100.

Mail orders allow postage on Software 1 or 2 \$1.00,  
3-5 \$1.50, 6-9 \$2.00, 10 or more items \$2.50

All prices INCLUDE sales tax.  
Prices subject to change without notice.



# Australia's first under \$300 COMPUTER...

**\$295**  
INCL. ZX80 BASIC  
MANUAL



Remember — all prices shown include sales tax, postage and packing.  
N.B. Your Sinclair ZX80 may qualify as a business expense.

## sinclair ZX80 - British made.

Until now, building your own computer could cost you around \$600 — and still leave you with only a bare board for your trouble. The Sinclair ZX80 changes all that. For just \$295 you get **everything** you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more. The ZX80 is programmed in BASIC and you could use it for anything from chess to running a power station.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual. The unique Sinclair BASIC interpreter: offers remarkable programming advantages — unique 'one touch' key word entry. The ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST etc) have their own

single key entry. Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately, preventing entry of long and complicated programs with faults only to discover them when you run.


Excellent string handling capability — takes up to 26 string variables of any length. All strings can undergo all rational tests (e.g. comparison). The ZX80 also has string input to request a line of text; strings do **not** need to be dimensioned. Up to 26 single dimension arrays. FOR/NEXT loops nested up to 26. Variable names of any length. BASIC language also handles full Boolean arithmetic, conditional expressions, etc.

Exceptionally powerful edit facilities, allows modification of existing program lines. **Randomise function**, useful for games and secret codes. **Timer under program control**. PEEK and

POKE enable entry of machine code instructions,USR causes jump to a user's machine language sub-routine. **High resolution graphics** with 22 standard graphic symbols. The Sinclair teach-yourself-BASIC manual 96 page book free with every kit.

**Fewer chips, compact design, volume production means MORE POWER FOR YOUR DOLLAR!** The ZX80 owes its low price to its remarkable design; the whole system is packed onto fewer, newer more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

ORDER FORM: SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD. 308 High St., Kew 3101, Vic. Tel. 861 6224			
Quantity	Item	Item Price	Total
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price incl. ZX80 BASIC manual, excl. mains adaptor.	\$295.00	
	Mains Adaptor(s) (600Ma at 9V DC nominal unregulated).	\$16.00	
	Memory Expansion Board(s) takes up to 3K bytes.	\$ 28.50	
	RAM Memory chips — standard 1/2K bytes capacity	\$ 10.00	
	Sinclair ZX80 Manual(s) free with every ZX80 computer.	\$ 15.00	
I enclose cheque/Bankcard/Diners Club/Amex		TOTAL	
<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>			
Name _____		EAI	
Address _____		Postcode _____	

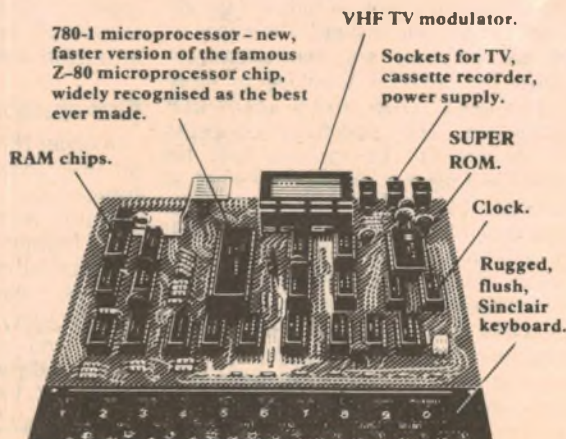


# ZX80

COMING SOON
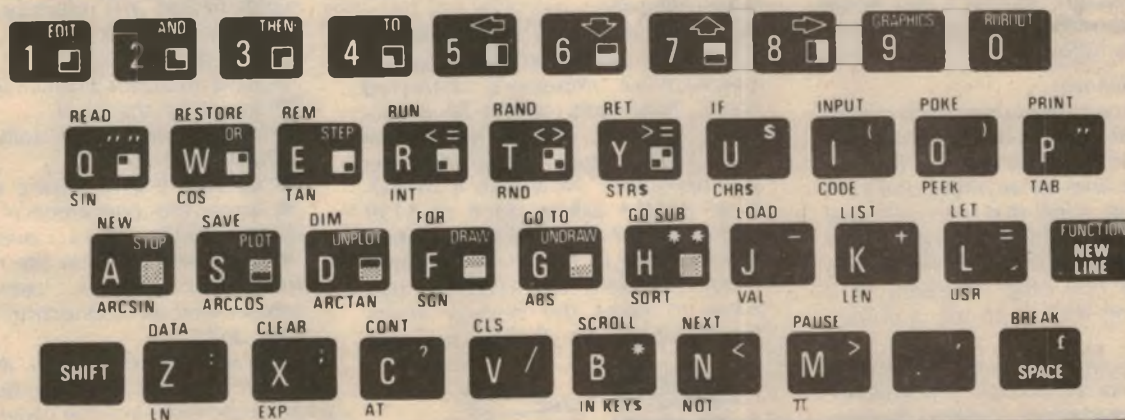
# 8K BASIC ROM

Fantastic new options for **SINCLAIR ZX80**



## THE CHIP

a drop-in replacement for the existing 4K BASIC ROM, comes with a new keyboard template and a supplementary operating manual. Designed for high-level, full facility computing.

### KEY FEATURES INCLUDE —

- Full floating-point arithmetic to 9-digit accuracy.
- Logs, trig, and their inverse functions, graph plotting facility.
- Animated displays using PAUSE n.
- Full set of string-handling facilities.
- n dimensional arrays, cassette LOAD and save with named programmes.

### AND ZX80 16K-BYTE RAM PACK

Complete module designed to provide massive add-on memory capacity.

The 16K-BYTE RAM pack can be used for program storage or as a database. Yet it costs up to half the price of competitive additional memory.

Measuring 3 in × 3 in × 1.25 in approx., the RAM pack plugs into the existing expansion port on the rear of the Sinclair ZX80 via an edge connector. No additional power supply is needed.

**SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.**

308-312 High Street, Kew, Vic., 3101. Tel. 861 6224.



# FORUM

Conducted by Neville Williams

## Non-approved transceivers and telephones — Moral problem or administrative mess?

A reader from Berowra, NSW is genuinely worried because he feels that "Electronics Australia" has been guilty of supporting double standards. Perhaps other readers have felt the same way and it may be helpful to publish his letter in full and examine the problems which he sets out.

First off, we don't resent the letter and we are not about to try to shoot the writer down in flames. The points he raises are quite legitimate and warrant a reasoned answer — even if it isn't in the terms that he might have expected. His letter runs as follows:

Dear Mr Williams,

I read several publications each month (including EA), and am normally not one to write to any of their editors. There is always a first time for anything, and I am writing in the hope that you will deal with my comments through your "Forum" column, as it is my belief that EA (and at least one other magazine, ETI) are condoning what is, to me, a double standard.

Whilst you probably are quite within your rights not to accept responsibility for advertising content, I believe that you do have the power to influence some of your major advertisers on the content of their advertisements. I list below four examples of what I call "double standard" advertising.

- (1) At least two separate suppliers are advertising a push-button telephone dialling system and have been for some time. They carefully state that they are not approved for use by Telecom, however, they fit perfectly (no soldering required). One supplier obviously has sold all his original stock because he is now boasting a new bulk buy to reduce the price.
- (2) The next example is the "Cutie Phone", which "although it easily replaces the standard Telecom phone, present regulations forbid them to be used for this purpose". I wonder what other purpose the average purchaser would have in

mind! I understand that it even comes with a wall plug, which means that "Blind Freddie" could substitute it for his current phone, albeit illegally.

- (3) The third example is a 40 channel CB radio, advertised as a "scoop purchase of importer's distressed stock. These sets cannot be licenced in Australia, but are brand new and ideal for parts or amateur experimentation." Now who is he kidding! At the asking price of \$139 and the offer of a 100% guarantee, who is going to buy them for parts? I can only view this as encouragement to enter the field of illegal broadcasting. To further make a



(Cartoon adapted from "Interface" newsletter, Sigma Data Corporation).

mockery of the situation, I seem to recall that this advertiser was one of the most vocal exponents of legalising CB in Australia! Now he seems to have changed his direction!

- (4) Back onto the telephone again — a cordless phone and I really find it hard to believe my eyes on this one! "21st century technology is all around us and yet you still rent a telephone that has hardly changed since the days of Alexander Graham Bell. It is now possible with the Dick Smith X1178 cordless phone to:

- have freedom from trailing wires
- use it by the pool
- receive and send calls from a remote location
- operate it as a paging system
- enjoy the convenience of push-button dialling, etc . . . even though this unit will work on the Australian telephone system . . . users will be prosecuted for connection or use of this unit."

I suppose that covers you, Mr Advertiser, but it would be interesting to see what happened if anyone caught using it decided to join the supplier as co-defendant!

With apologies for the length of this letter, I now come to the role of yours and other magazines in this charade.

Whilst realising that you need advertisers, I personally believe that you have the right and ability to discourage this kind of advertising. This may be a hot potato for you, however, I strongly recommend that you, who I believe to have very high moral values, should tackle it head on.

I would be interested to hear, or read, your views on this subject. Other than that, I believe you have an excellent magazine, even though it sometimes goes over my head in some respects.

C.R. (Berowra, NSW).

C.R. mentions hot potatoes. This figure of speech is one that I find it difficult to exploit. If he would agree to swap the potato for a stone, I could proceed to

the remark that, in turning over the particular stone, he has uncovered a whole nest of worms — very mature worms at that!

In fact, the dilemma of which he speaks is not peculiar to the present; past events are very relevant to current attitudes, both in the business world and within our own administration.

One gets rather tired of making futile gestures; or, in the Australian idiom "of being the mug!"

I cast my mind back to the pre-war era when the Postmaster-General's Department maintained a very tight control over transmitting activities in Australia. They were able to do this, because their supervisory staff could cope with the limited number of would-be "pirates" in the community. Significantly, if you wanted a transmitter in those days, you built it yourself!

Their task was complicated, after the war, by the number of people who emerged from the services with an interest in radio and first-hand experience in the everyday use of transceivers.

However, the Radio Branch carried on much as before, sagely vetting applications for new services, inspecting equipment, conducting examinations and issuing new licences. For would-be "pirates" they had one message, based on the Wireless Telegraphy Act of 1905: the mere possession of equipment capable of transmitting radio signals could render one liable to prosecution.

Unhappily for the Department, another arm of the Federal Government was busily engaged in a quite different activity: getting rid of the military equipment that it no longer needed. And, of course, it included truckloads of surplus transmitters and transceivers. They were knocked down at auction to dealers from all over Australia, in the certain knowledge that they would be re-sold to the public.

And they certainly were — stacked to the ceiling in every second disposals store in the land.

## ADVERTISING DILEMMA

I can't remember all the details now but the question arose as to whether we should or should not accept advertisements for ex-disposals transmitters. As a group of licensed amateurs, we were inclined to say no but the sheer futility of the situation was overwhelming.

On the one side, the Radio Branch was preaching "Thou shalt not . . .". On the other, the Defence Department of the same Federal Government was selling off thousands of transmitters and transceivers, most of them in working order, many of them new.

To pretend it wasn't happening would have made King Canute look like a sage. It would have earned us only ridicule from dealers anxious to advertise and from readers keen to know what the Government was unloading next, on to a

market starved for bits and pieces by several years of war.

When disposals transmitter advertisements did begin to appear in our magazine, it was without hassle and without challenge — a complete anticlimax to our own internal hang-ups:

- Brand new AT5 transmitter . . . 140kc to 20 megs . . . with crystal and aerial coupling unit, circuit and instruction book . . . £27.10.0.

- New command transmitter . . . 5.3 to 7 megs . . . with valves and crystal . . . £9.10.0.

- Collins autotune ART 13 transmitters . . . with valves . . . £85.

So it went on for years, with successive governments, ministers and administrators aware of the anomaly but either unwilling or unable to do anything about it.

Ultimately, the equipment, the advertisers and the problem faded into history, with just a little of it still lingering in clearance houses like Deitch Brothers.

## AND SO TO CB . . .

It was against that background that we watched the situation develop in relation to CB equipment. During 1976, 27MHz transceivers began to pour into Australia in far greater numbers than were needed to meet the demands of licensed amateurs and industrial users.

Not relishing the idea of 27MHz CB spawning in this country, the Radio Branch of the PMG Department made some attempt to control the situation by demanding that retailers keep records of purchasers. But, with no restraint whatever at the point of entry, it was like trying to stem a flood with a bucket! The Radio Branch itself couldn't keep up and the record system lapsed.

In the editorial for January 1977 our then editor Jamieson Rowe said "due to lack of co-ordination between Government departments, we already have a de facto CB service, albeit an illegal one."

And, once again, we found ourselves in the middle. Importers were being issued with licences to bring in any number of American standard transceivers, which were then being advertised, displayed and sold to the public, without restraint and presumably legally.

It just happened to be illegal to use them! How utterly ridiculous. And how completely reminiscent of post 1950.

In due course, the Citizens Radio Service was formalised and, overnight, "pirates" and illegal (to use) equipment had the chance to become legit. But, because of internal industrial action, the Radio Branch found itself unable to process all the applications and, for weeks on end, operators and stockists alike found themselves suspended halfway between piracy and long-sought respectability.

Ultimately, it was sorted out but still nothing was done about blocking the activities of those who trade in unaccep-

## printed circuits

- Accurately machine printed etched
- Phenolic & fibreglass-gold tin plated
- EA R & H ET Philips Mullard available
- Specials to your drawing
- POSTAGE small 80c large \$1.10

ETI 1500	9.00	ETI 572	3.50	EA80MG9	2.80
80MV11	2.80	90LS12	3.20	80RAM12	5.50
ETI 476	4.00	247	2.80	ETI476	4.00
255	2.80	80DC10	4.80	80TRS11	2.80
80LBRI2	2.80	80BM10	2.80	80AW10	3.00
80TC12	2.80	80TM8B	2.80	80ST10B	2.80
80ST10A	4.50	327	2.80	EA80TM8A	5.00
568	2.80	ETI457	3.00	ETI47	3.00
ETI475	4.00	80B7	2.50	ETI326	2.80
80LPG9	3.50	250	2.50	80DM9	4.50
80TR9	3.50	80LL7	2.80	564	10.50
ETI 1324	3.50	80LL7	2.80	80M07	3.00
80PC7	3.00	80CH7	4.80	80M07	3.00
563	2.80	467	4.00	565	3.50
80PP7B	2.50	80PP7A	5.00	149	2.80
80G6	4.80	578	2.50	80RF5	2.80
80D6	3.00	78AF2	3.00	636	16.00
80PA6	12.00	77CB12	2.60	ET58820	10.00
80BB3	2.80	ET135	3.00	78EK3	3.30
454	3.00	80H56	2.80	781A2	2.60
80AW4	4.00	325	2.50	ET716	4.00
80C14	2.80	80PC4	3.00	ET245	2.50
466	6.00	562	3.30	78S3	2.60
80AU3	3.00	453	2.80	77PH12	2.60
264	2.50	566A	2.50	80PG6	5.00
322	2.80	80GPS3	2.80	80HLA5	2.50
80S1	2.50	496	5.00	80TV8	3.30
ET560	2.80	496G	6.50	566B	3.00
ET151	2.50	80CM3A	3.20	80F3	2.80
79D10	2.80	561	2.80	ET152	2.80
79T11	2.80	80GA3B	3.20	726	8.00
ET262	2.50	79SB10	2.80	80CM3B	2.80
ET150	2.80	ET452	4.50	455	3.00
79PG9	3.00	80SA3	4.50	80GA3A	5.00
ET573	2.80	79EB12	2.80	ET474	2.80
79QM9	3.00	ET270	2.80	ET321	3.50
79RR8	4.20	ET261	2.50	79FE11	2.80
79BT9	2.60	ETI46	2.50	79PC12	2.50
79AC9	3.50	79MD9	2.80	ET263	2.50
ET576	4.20	ET577	2.80	ET260	2.50
ET730	3.50	79PS10	2.80	79PS11	2.50
ET252	3.00	79SF10	2.50	ET606	3.00
79WF8	3.20	79TT7	2.60	ET473	3.50
79PS6	2.80	79SF9	2.60	79R18	2.80
ET451	2.50	ET574	2.80	79A19abc	4.20
6800	8.50	ET814	2.80	79W9	2.80
79UPS6	2.50	79SR8	2.80	ET731	3.00
ET144	3.50	79UT8	3.00	ET575	2.50
79R05	3.00	79RF6	3.50	ET725	3.50
77E02A	3.50	ET472	3.00	79TRF5	2.50
ET320	2.50	79C17	4.80	79M8	2.80
ET595	2.80	79SA5	8.00	ET148	2.50
491	4.50	ET254	2.50	ET724	2.50
79PS3	2.60	79EQ2C	2.50	79KB7	2.80
79P1B	2.80	ET249	2.80	ET651	4.50
79C1A	3.00	ET253	4.20	ET471	5.50
142B	4.00	559	3.80	79EQ2B	4.00
79S1	4.50	78Se3	4.00	ET594	2.50
79IT2	5.00	79P1A	2.80	ET470	3.20
78S12A	5.50	558	2.50	79A3	3.00
78N10	2.60	142A	8.00	721	3.00
78DT10C	2.50	79W3	2.60	79PB2	3.20
ET813	3.50	78SB12	3.00	78C1B	2.80
ET812	2.80	781M12	3.00	557	3.00
ET556	6.00	78C11	3.10	79UP1	5.00
78BB9	3.50	78DT10B	2.80	79C1	2.60
650B	2.60	ET143	2.80	78S12B	2.50
718	2.60	ET593	3.20	78UP10	7.00
590B	8.00	78DB11	2.80	78DT10D	2.50
78E09	2.50	555	4.00	78DT10A	6.50
ET391A	2.50	650A	4.00	ET141	4.20
ET591C	2.50	553	3.00	ET490	2.80
				78UP9	6.00

ALL SILICON 30/60W PA PORT AMP  
6 1/2"W x 8 1/2"D x 3 1/4"H 12 — 16V, two inputs 5 & 100mV. 125, 250, 500 ohm output only. No. 763A  
\$70 ea. 240V operation \$33 extra. Freight collect.

COILS and IF's All \$2.50 ea plus post 60c  
3/4"W x 3/4"D x 2"H

MAIL cheque or money order  
(add postage) direct to —

## RCS radio pty ltd

651 FOREST RD BEXLEY  
NSW 2207 587 3491

# MR BUSINESSMAN!

here at last from DICK SMITH is a

## STOCK CONTROL & PRICING SYSTEM

especially designed  
for Australian  
conditions

program suits  
DICK SMITH  
SYSTEM 80  
micro computer



No, not just another software package imported from overseas, but one that has been written (at great expense) by Australians for Australian businesses

In fact it has been modelled closely on the Stock Control and Pricing System used so successfully by Dick Smith Electronics.

The original system runs on an IBM computer costing more than \$50,000 — but you can have the same benefits for less than one tenth of this cost (yes, for both the computer hardware and the software!)

While you're in one of our stores why not check out the many features of the System 80 and its peripherals?

You, and your business can benefit from this amazing system for less than you think!

### HERE ARE JUST SOME OF ITS OUTSTANDING FEATURES

Cat X-3750

- Capacity for up to 1200 stock lines!
- Machine-language sorting for FAST operation!
- Ability to print out price lists as well as stock status reports and other listings (all dated!)
- Fast stock and financial status reports on the screen!
- Simple "menu-driven" operation — no special training required!
- Prints out stock count sheets for stocktaking, then gives you a printed analysis of all discrepancies!
- Special Australian Sales Tax feature (optional)!
- Easily expandable — so you're not forced to change to another system as your business expands!

# \$275!

(Program & Data Disks with comprehensive User Manual)

The full Dick Smith business computer system includes computer, monitor, disk-drives, expansion interface, large memory, cables, etc. — costs just \$3,480.00. So with SCAP you can have a superb operating system for well under \$4,000!!!

**DICK SMITH**  
Electronics



SEE OUR OTHER ADS FOR  
FULL ADDRESS DETAILS

table (to the P&T Dept) transceivers, antennas, "after-burners". This, despite the fact that there could no longer be an excuse that they were meant for use by licensed amateur station operators.

Which brings us to the present.

I rang Dick Smith personally and put to him C.R.'s question: How could you, as a one-time champion of legalised CB, now be offering 40-channel transceivers which do not meet the specs laid down by the Department of Communications?

He waxed eloquent in the manner of someone who has generated strong convictions. I summarise:

**SAYS DICK SMITH:**

- *Yes, I support legalised CB and I've tried to do the right thing.*
- *I've made endless representations to Melbourne and Canberra seeking practical support for legitimate traders who want to adhere to the Australian standards.*
- *I've received endless undertakings but they have all come to nothing. I simply don't believe them any more!*
- *With 40-channel (and more) equipment available from job lots, sales of legitimate 18-channel CB have fallen to a dribble. It's cost us something like \$300,000 to back an administration which won't back itself.*
- *That kind of money affects jobs and staffing levels.*
- *It wouldn't be so bad if we got any credit for our stand, but we don't. Customers abuse our staff for not matching what they can buy somewhere else.*
- *Yes, we reversed our policy, and those are the reasons why.*

**AND TELEPHONES?**

The position in regard to non-departmental telephones and cordless telephones is a further extension of the same theme.

I came up against it personally when the subject was taken up by ABC television. They had been alerted to the anomaly of specialist shops in Sydney legally importing and selling telephones which the public were not supposed to connect to Telecom lines.

Seeking background on the subject, one of their reporters rang me (He's an editor; he's not involved; he ought to know what's going on!)

I filled in the broad background and made an on-camera statement. They also went off and talked to the retailers concerned, to a local manufacturer of "legitimate" equipment and to a representative of the P&T Department.

The report received nationwide exposure and comment. That was, maybe, a year ago and the subject was duly reintroduced. The retailers went on importing and selling their verboten phones

and Dick Smith went on being conservative. And here I add one more neologism in the style of the others:

- *The same with extension telephones. We were continually asked for them and abused for not stocking them. I got sick of being the mug!*

Nor is Dick Smith the only doubter.

During last year, our CB correspondent Jan Christensen included a "hot tip" in her notes, straight from the lips of the then Minister for Posts and Telegraphs, Mr Tony Staley. His department was preparing to come down "boots and all" on those who were selling unacceptable equipment — 40-channel (and more) CB, high power finals, cordless telephones, etc.

I crossed it out, partly because there was too much copy for the space available, and partly because I didn't believe it would happen anyway!

And, of course, it didn't. There was a general election, Tony Staley did not renominate and we're back at square one.

Perhaps the new Minister, Mr Ian Sinclair, may elect to "have a go" but then he has a few other morsels on his plate, like the status of the Australian Broadcasting Tribunal, multicultural radio and television, satellites, and so on.

**THE "MORAL" ASPECT**

C.R. rounds off his letter with a reference to morals, particularly as pertaining to this magazine and its Editor-in-Chief.

If morals are meant to relate, in this case, to an overall respect for, and observance of the law, I do confess to some difficulty in generating an unambiguous response to an administrative mess that has existed for at least 30 years.

As far as the Dick Smith advertisements were concerned, as quoted, the purchaser "victims" would obviously have been informed — and willing!

C.R. invites us to tackle the problem head on, presumably in the fond belief that we could pull advertisers into line with a particular point of view. Or, even if we did, that it would have the slightest effect on the vendors or the purchasers who never as much as see the magazine!


If anyone has to tackle the job head on, it must be the Government itself. Then and then only is it likely to become C.R.'s "hot potato". It's too big a job for "Electronics Australia", or any other single enterprise.

One final word: I am not being political in making the foregoing statements. During the 30 odd years to which I have referred, Governments and ministers of many persuasions have been in office.

But the "Too Hard" basket has remained blissfully undisturbed!


# Coming Next Month\*
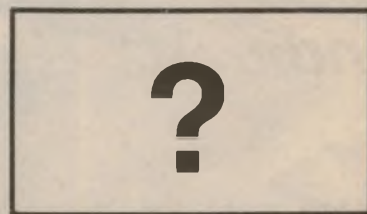
## Graphic Analyser with Colour Bar-Graph Display



*We're so excited about this project that we did not even have time to have it photographed. Which is probably just as well really, because a small black and white photograph hardly does it justice. This analyser gives a dramatic multi-colour bar-graph display of your room or hi-fi system response, via your colour TV set. You can also use it to give a dynamic ten-band display of program signals. It is low in cost and easy to build.*

## Playmaster Guitar Amplifier

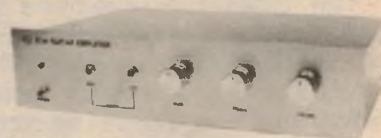

*An easy-to-build guitar amplifier for practice or performances at small venues. Power output is 35 watts into a 4 ohm loudspeaker system and it all goes together in just a few hours.*

*\*Our planning for this issue is well advanced but circumstances may change the final content. However, we will make every attempt to include the articles mentioned here.*



# The moving coil replacement from Stanton Magnetics... the revolutionary 980LZS!




Now from the company to whom the professionals look for setting standards in audio equipment comes a spectacular new cartridge concept. A low impedance pickup that offers all the advantages of a moving magnet cartridge without the disadvantages of the moving coil pickup. At the same time it offers exceedingly fast rise time—less than 10 micro seconds—resulting in dramatic new crispness in sound reproduction—a new “openness” surpassing that of even the best of moving coil designs. The 980LZS incorporates very low dynamic tip mass (0.2 mg.) with extremely high compliance for superb tracking. It tracks the most demanding of the new so called “test” digitally mastered and direct cut recordings with ease and smoothness at 1 gram  $\pm 10\%$ .

The 980LZS features the famous Stereohedron™ stylus and a lightweight samarium cobalt super magnet. The output can be connected either into the moving coil input of a modern receiver's preamps or can be used with a preamp, whose output is fed into the conventional phono input.

For “moving coil” audiophiles the 980LZS offers a new standard of consistency and reliability while maintaining all the sound characteristics even the most critical moving coil advocates demand. For moving magnet advocates the 980LZS provides one

more level of sound experience while maintaining all the great sound characteristics of cleanliness and frequency response long associated with fine moving magnet assemblies.

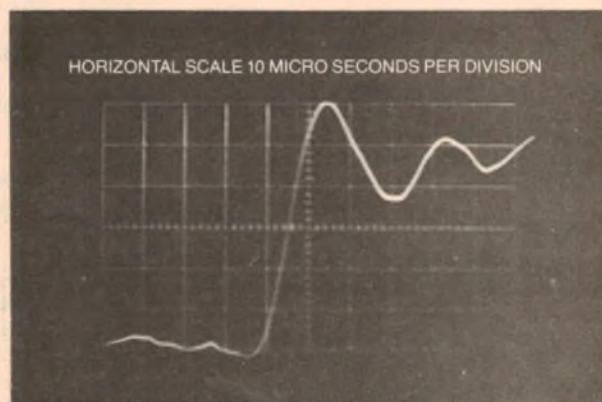From Stanton... The Choice of The Professionals.



Actual unretouched oscilloscope photograph showing rise time of 980LZS using CBS STR112 record.



## STANTON


THE CHOICE OF THE PROFESSIONALS™

IMPORTERS AND EXPORTERS OF AUDIO EQUIPMENT



**SOUNDEX** PTY. LTD.

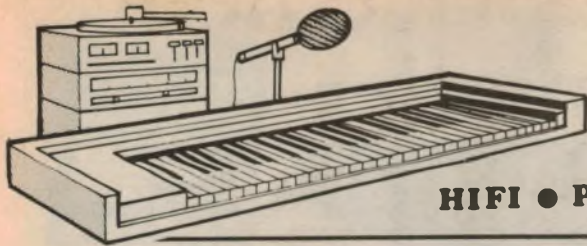Head Office: 156 Railway Pde., Leederville, Western Australia, 6007. Telephone: 381 2930. Telex: AA 93241 ANSB. LRP.  
NSW Office: 7 Jordan Rd., Wahroonga, 2076. Telephone: 487 2543.



# AUDIO - VIDEO ELECTRONICS

HIFI • PROFESSIONAL AUDIO • ENTERTAINMENT

## VIDEO DISC: Pioneer wants to be number one!

While most other companies seem content to let the video disc follow somewhere back in the wake of the new season's video cassette decks, Pioneer have taken a different approach. They are talking disc here and now and have already reached agreement with GMH whereby their video disc equipment will provide the essential audio/visual link between GMH and their Australia-wide network of dealerships and service centres.

The Pioneer/GMH announcement comes hard on the heels of another from the National Library of Australia in Canberra, indicating that they had installed what they believed was Australia's first video disc service which "allows film workers, researchers and others to view American films by plugging a video disc machine into a specially adapted television set".

Mr Ray Edmondson, Director of the Library's film section, said that the equipment installed was an MCA Discovision player using the laser principle — the only one currently on sale in the United States. The players are not normally available in Australia but Pioneer Elec-

*GMH's new Pioneer/Rank Arena Video Centre uses 30cm laser discs which play for 30 minutes per side. One disc can carry as much material as twelve 4 to 5-minute film cartridges, as used in the now obsolete GMH "Mini Theatre".*



### VIDEO DISCS FIFTY YEARS AGO . . .

While practical commercial video discs belong undoubtedly to the 80s, the concept of recording television signals on disc is by no means new. Ten years ago, Decca and Telefunken developed a video disc with about a 10-minute playing time, which went on sale in Germany for a brief period.

But even Decca and Telefunken had been anticipated by John Logie Baird in England by about 40 years.

Baird had demonstrated his primitive mechanical-scan television to engineers in 1924, and exhibited it to the public in 1925 in Selfridges store in Oxford St, London. The signals were broadcast in 1926 and Selfridges opened a TV sales section in 1928. It was during the period 1926/8 that Baird first concentrated on video disc recording.

Since his low definition television signals required a bandwidth of only 13kHz, Baird realised that, with care, they might be accommodated on a standard 78rpm record. He patented the method in October 1926.

How to record picture and sound on the one disc posed a problem but Baird suggested that the most practical scheme would be to use side-by-side concentric grooves, played by a dual pickup. In fact, he seems to have concentrated on single groove recordings carrying picture information only.

Perhaps sound wasn't really all that important for the disc that went on public sale in Selfridges in 1935. Presumed to be a copy of one of Baird's 1928 test cuts, it carried 10 drawings on glass depicting the faces of Marconi, Harry Lauder, Stanley Baldwin and a number of other people who can no longer be identified.

Those 10, flickering, silent images are a long way from today's full colour television but they represent a notable piece of electronics history.

tronics, the local distributors for MCA Discovision, had co-operated in obtaining a player for the Library.

According to Mr Edmondson "the Library's machine is a sophisticated industrial model, which has a built-in microcomputer enabling it to do such things as freeze frames and fast search film for particular frames."

Amongst the initial batch of features in the Library's disc collection is Fellini's "Cassanova", "To Kill A Mockingbird", "The Great Waldo Pepper" and the original "Frankenstein".

While the Library player was more or less a one-off installation, the arrangement between pioneer and GMH is on a much larger scale. According to Robin Macdonald, Publicity/Promotions Officer for Pioneer, "it makes Australia the first country outside North America to install laser video disc equipment in any numbers — a major breakthrough . . ."

Replacing the now obsolete GMH "mini theatre", the purpose of the new system is to communicate the latest training, sales and service skills, and product information, without having to take



Pioneer's industrial Laser Disc Player with remote control (left) and two typical MCA Discovision feature movie albums.

staff out of their normal dealerships to attend regional and Head Office seminars.

The GMH Video Centre, as the new system is called, consists of a Discovision 7820 laser disc player, produced by Universal Pioneer Corporation, a TV monitor and an optional Pioneer sound system. It is housed in a special cabinet constructed by Rokor, Pioneer's manufacturing subsidiary.

The 7820 video disc player features fast visual scanning in forward and reverse modes, single frame display and what Pioneer describe as "chapter search", an invaluable aid for educational and office use in the future. The player can reproduce a normal movie or access any of 54,000 distinct frames on one side of a 30cm disc. To find and display a nominated frame takes a maximum of five seconds.

Because General Motors in the United States and Canada has taken up the Video Centre concept on a huge scale — to a total of 11,500 units — GMH in Australia should have access to a vast amount of general software.

However, they have also arranged to produce software in Australia, through AAV, to the master video tape stage. It will be shipped to Discovision Associates in America, where video and audio will be transferred to the laser disc.

The entire system operates to NTSC standards. However, it is to be displayed here on an Australian sourced Rank Arena receiver/monitor, which has been adapted to operate from either NTSC or normal broadcast PAL video.

The Video Centre is to be supplied, installed and serviced by Pioneer Electronics. The package price to GMH dealers stands at "under \$4000", and installation is planned for May, this year.

While projects like this serve to focus early attention on Philips/MCA Discovision, they also tend to draw attention to editorial opinion expressed some months ago in the Japanese English-language journal JEI. They expressed the view that the laser system is well suited for industrial applications but less so to the consumer market. Here, the capacitance systems of RCA and JVC would appear to have the advantage, on the basis of

simplicity and economy.

Les Black, Managing Director of Pioneer Electronics Australia rejects this view outright. He maintains that the multi features of the Discovision system and the complete freedom from disc and "stylus" wear will more than offset the price advantage of the two competing systems.

Discovision retails at present, at a little over \$700 but developments in the pipeline will bring this figure down markedly, without sacrificing performance.

As far as Pioneer Australia is concern-


ed, they were saying in October last that they expected to be the first company in Australia to market the video disc system. They were also tipping a delay of about 12 months for PAL system equipment to become available.

The more recent press release announcing the GMH Video Centre still maintains: "domestic release is tentatively set for 1981".

Pioneer are obviously still hopeful of being number one in the marketplace.

To some degree, this will depend heavily on the availability and supply of video disc players and software designed
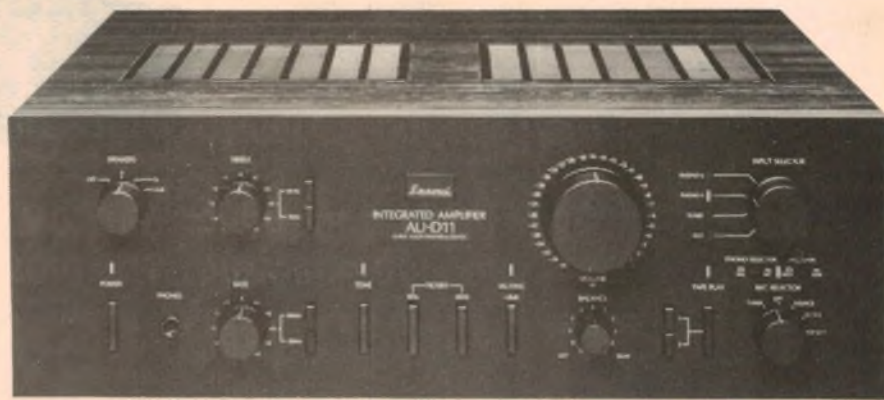
## FROM SANSUI: Feedback plus "feedforward"



Sansui's latest contribution to the struggle for ultimate performance in hifi amplifiers is found in their new models AU-D9 and AU-D11. In addition to the normal negative feedback provisions, Sansui engineers have applied what they describe as "Super feedforward" to the power stage. Although patented in 1928, the method has rarely been used in commercial amplifiers. Basically, it involves sensing the distortion content being produced by the output stage, processing it through a separate small supplementary stage and applying it independently to the load. The aim is not just to reduce distortion (as by negative feedback) but to cancel it altogether. Sansui claim that it can cope with all forms of distortion, including switching distortion; this being the case, it removes the point from current debate about class of operation: class-B, class-A, etc.

The AU-D11, as pictured above, offers 120W min. per channel into 8 ohms, both channels, 10-20kHz, with a THD of 0.005% max. Actual response (-3dB) is DC to 300kHz. Dimensions are 445 x 163 x 443 (mm, W, H, D) and weight 14.5kg. The AU-D9 offers 95W min per channel, being slightly less deep and about 1kg lighter. Both have the same panel layout and offer a full range of user facilities. (Our information came direct from Japan. In Australia: Vanfi Aust Pty Ltd, 162 Albert Rd, South Melbourne, 3205. Phone (03) 690 6200.

# Sony's inseparable separates.

Sony's new ST-J55 tuner and TA-F55 amplifier come in elegant matching designs. Separately, they're

straight signal processing circuit construction, revolutionary Heat Pipe, and Pulse Power Supply, providing



outstanding. Together, they're out on their own, both in appearance and performance.

The J-55's tuner is frequency synthesized and quartz locked. A neat line of feather-touch switches gives a choice of Memory, Auto, or manual tuning.

The J55's incredible electronic MNOS memory tuning lets you preset your 8 favourite AM/FM stations - including reception adjustments like muting or mode pre-set.

The other half of the team, the 65W F55 Amplifier, features an electronic motor driven volume control,

extremely clean and noise-free sound quality.

The F55 operates with almost any type of MC and MM cartridge; has gold-plated phono jacks, oxygen-free copper wiring, metallized film resistors and polypropylene capacitors.

You won't find better engineering than these. Not even from Sony.

# SONY®

# RARE ADDITIONS FROM MARANTZ. SUPERIOR FM TUNERS.



**Rare:** very valuable.

**Additions:** the things added.

**Marantz:** a range of ultra-high performance FM Tuners which blend state-of-the-art engineering with operational versatility.

The name Marantz guarantees your choice from a superior range of AM/FM Stereo Tuners, guarantees exceptional quality and, with the advent of more FM stations, Marantz guarantees your total listening pleasure.

## **MARANTZ ST500 AM/FM STEREO COMPUTUNER**

Sleek, slimline and microprocessor controlled — tune and recall stations with amazing speed and precision. The Computuner features state-of-the-art, quartz-locked, drift free frequency synthesised tuning with 7AM and 7FM memory presets. The LED signal strength display doubles as a multipath indicator and the Wide and Narrow IF Selector enables the switching of a tuning bandwidth best suited to reception area conditions.

## **MARANTZ ST600 AM/FM STEREO TUNER**

This model incorporates a built-in oscilloscope that affords the most precise means possible to determine optimum reception, even from weak or distant stations. The functions of the oscilloscope extend well beyond those of conventional tuner meters.

## **MARANTZ ST400 AM/FM STEREO TUNER**

A large, fuss-free Vacuum Fluorescent readout clearly displays the selected frequency and Electronic Gyro-Touch with Servo-Lock guarantees drift-free, razor-sharp tuning every time. Uncompromising quality through and through.

## **MARANTZ ST300 AM/FM STEREO TUNER**

Consistent with all quality Marantz tuners, the ST300 features MOSFET FM front end and Phase Lock Loop demodulator for superlative performance — low distortion, extremely linear operation and wide dynamic range. Illuminated dial cursor, LED function indicators and Gyro-Touch tuning make the ST300 an exceptionally sophisticated buy at a modest price.

Your Marantz stockist will be pleased to demonstrate the complete range of Marantz tuners. If you see your hi-fi as an investment and, if you demand critical performance standards as well as the best value for money, listen to the future.

Listen to Marantz.

**marantz**  
Now you're listening.

Distributed by: MARANTZ (AUST) PTY LTD  
32 Cross Street Brookvale, N.S.W. 2100  
Telephone: (02) 939 1900 Telex AA 24121  
Melbourne (03) 329 7655 Brisbane (07) 48 8882  
Adelaide (08) 223 2699 Perth (09) 328 3874

## AUDIO-VIDEO ELECTRONICS — continued

to work with PAL receivers.

The first round for system supremacy will be fought in the US and Japanese arenas, where NTSC reigns supreme. The mass markets in Europe, Australia and elsewhere will attract attention from the various manufacturers only when they can afford to divert some of their manufacturing potential to the production of PAL standard equipment.

This could conceivably give Philips and possibly other European manufacturers a head start in the PAL markets.

However, reports from Japan have drawn attention to another factor which could vitally influence public preference in longer term — success or failure in producing good quality recordings, substantially free from noise and dropouts.

Pioneer President Yozo Ishizuko claims that his company has had considerable success in this area and may, in fact, be leading the World.

Their discs are made from PMMA (Poly Methyl Meta Acrylate resin) sometimes referred to as resin-glass, by reason of its high transparency.

At a video disc test plant at Pioneer's Kofu factory at Yamanashi Prefecture, discs are produced by injection moulding at a temperature of 200°C. One of the prime aims is to so control the entire process that the discs which emerge will be free from inherent stress and warp.

### PHILIPS, SONY DISCS


In the Netherlands, according to the same report, Philips also use acrylate resin but subjected to photo polymerisation by ultra-violet radiation. This modifies the molecular structure and produces a very hard disc. The method is technically difficult, however, and Philips are reportedly studying the Pioneer approach.

Sony also produce optical video discs, but they appear to be relying more on conventional pressing techniques, using vinyl chloride.

For double-sided optical discs, the biscuits have to be metallised, then cemented together. According to Pioneer, the techniques for moulding and metallising discs, and for cementing them together all exist and need only to be refined; new equipment for mass production is under development. "The opinion that optical video disc is difficult to produce is groundless".

On the other hand, production of the capacitance type disc is much closer to established audio techniques. They use vinyl chloride, rendered conductive by the inclusion of carbon black; RCA reputedly treats the surface also with a silicone oil, to ensure smoothness and low friction.

The art of producing a top quality

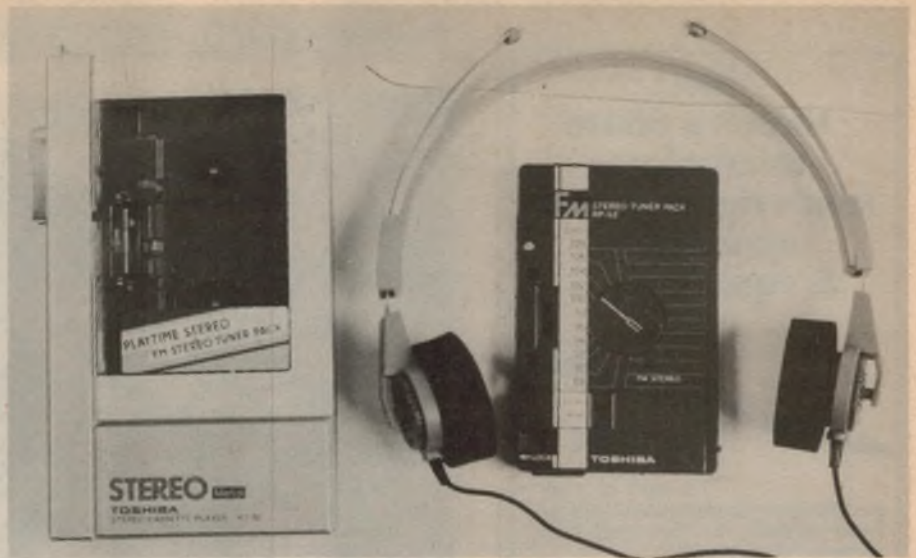

Left, the KT-S2 player, with lightweight headphones and, between them, the FM stereo tuner.

## Personal stereo cassette/radio

During the month, we were able to have a closer look at the Toshiba KT-S2 stereo cassette/radio player pictured in our January issue. Measuring 88.5(W) x 155(H) x 31.5(D)mm, and weighing 455g with batteries, it is intended primarily for personal portable wear, using stereo headphones. No provision is made for a loudspeaker, either internal or external.

The KT-S2 is a player only, with no recording facilities, its prime role being to reproduce prerecorded cassettes. This it does very well indeed, with ample loudness and excellent tonal balance.

Provision is made to compensate for normal ferric or other tape, and there is a hi/lo tone switch. There is provision for cue (fast forward) or review (fast rewind) and auto-stop which will cut off the supply at the end of a normal play over-run.

A novel feature of the KT-S2 is the provision and use of an in-built microphone, which might otherwise serve for recording. In the KT-S2, pressing the appropriate button mutes the normal music signal somewhat and turns on the microphone. The user can thereby be involved in a conversation, without having to remove the headphones.

The headphones, by the way, are very light and comfortable and offer a good sound, as judged by their use in this unit. However, they are fitted with a miniature plug rather than the more usual 6mm type.

But the really novel feature about the KT-S2 is that it comes complete with an FM stereo tuner, styled to insert in place of a cassette. Connections are established automatically, but there is no provision for an external antenna. A tiny (too tiny?) thumbwheel allows the user to tune right across the normal FM band and there is even a built-in light to indicate a stereo transmission.

In use, the lack of an antenna renders the tuner somewhat sensitive to attitude and location and hiss can be a problem on some stations in some locations. Fortunately, the tuner carries a tiny mono-stereo switch and this is likely to get a fair amount of use.

Operation is from four internal "AA" cells, but there is provision for operation from an external 6V DC supply. Battery life is quoted as three hours (approx) for tape replay or 11 hours for radio. This assumes a modest listening level, however, not the 40mW+40mW of which the unit is capable.

The KT-S2 comes in a package with headphones, FM-stereo tuner, carrybags for player and tuner, carrying strap, instruction booklet and warranty card.

We understand that an AM tuner has been designed which can be used instead of the FM tuner which comes with the unit.

For further information: Toshiba Aust Pty Ltd, 16 Mars Rd, Lane Cove NSW 2066. Phone (02) 328 2055.

capacitance disc (CED or VHD) rests heavily on the use of the smallest possible carbon particles and, for these, prime patents are held by Azko in the Netherlands. In a joint venture, Azko and Lion have been producing the carbon for about 12 months at the Yokkaichi fac-

tory of Japan EC.

The product merges well with vinyl chloride and makes very little difference to its moulding qualities.

President Toshihiko Yamashita, of the Matsushita Industrial Co Ltd, a major competitor for the optical system, says

**fact:**  
**there's a Shure**  
**microphone**  
**that's right for your**  
**application**  
**& equipment...**



**SM81**

First of the new breed of high-performance, studio-quality unidirectional condensers—technically state-of-the-art, exceptionally rugged and superb sound.



**SM59**

You've seen it on TV musical shows where sound quality is a must. Unidirectional, dynamic with exceptionally flat response, extremely low handling noise, mellow, smooth, and accurate sound.



**SM58**

The most widely used "on-stage" hand-held dynamic cardioid microphone—the world standard noted for its distinctive, crisp sound.



**UNIDYNE® III**

The world-famous UNIDYNE® III family offers top value per dollar. Uniform cardioid pattern helps control off-axis coloration, background noise, and feedback.



**SM61**

Omnidirectional dynamic. Outstanding low handling noise. Handsome, smooth looks with new VERA-FLEX® dent-resistant grille—a favorite on-camera mic with soundmen and entertainers.

**AUDIO ENGINEERS P/L**

342 Kent Street,  
 SYDNEY 2000 N.S.W.

AE 149/TP




With so much hifi equipment coming, nowadays, from Japanese sources, it is appropriate to be reminded that a beleaguered but esteemed group of manufacturers in Britain are carrying on the traditions of earlier days. This picture, from the British Information Service, shows a Linn Sondeck LP12 single-speed turntable being tested at the factory of Linn Products Ltd, 235 Drakemire Drive, Castlemilk, Glasgow G45 9SZ, Scotland.

that the major groups are all trying desperately to optimise techniques for the mass production of video discs.

He states, as a conviction, that the group which gains the advantage in producing quality pressings will be the one which enjoys ultimate success in the battle of the video discs.

**SANYO AUSTRALIA PTY LTD** are offering a 5-year warranty on their ambitious "Plus 35" hifi system. It includes a Q40 fully automatic direct-drive turntable with quartz-locked PLL servo motor.

The tuner is the "Plus" T35 unit, as pictured below. For the amplifier, Sanyo have chosen the class-A DC model A-35, featuring hi and lo filters, loudness, two tape dubbing switches, and 12-point LED bar graph with range switching. Rated power output is 50W per channel. The cassette deck is Sanyo's model D62, with metal tape compatibility, two-colour fluorescent peak-hold output indicators and the AMSS track search system. Recommended retail price of the system is \$1776, with loudspeakers and mounting rack extra. [Sanyo Aust Pty Ltd, 225 Miller St, North Sydney 2060.]

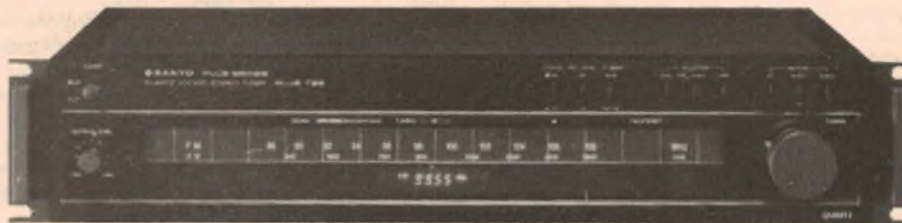

The T35, pictured above, belongs to Sanyo's new "Plus Series" of tuners. It offers both digital and analog frequency display, operating in conjunction with a sampling quartz locked tuning system. Also provided is a bar-graph signal strength indicator, plus another for centre tuning. As an aid to recording, the tuner provides a reference tone matched to 50% modulation from an FM transmitter. Other features include wide/narrow IF band selection and two-level FM muting. Recommended retail price is \$399. Details from G. Boucher, Sanyo Aust Pty Ltd, 225 Miller St, North Sydney 2060. Phone (02) 436 1122.

**"Concertmate"**  
— a new  
rhythm  
unit  
from  
Tandy




Unlike most other rhythm units, Tandy's new "Concertmate" has its own battery supply and its own in-built amplifier and loudspeaker. It can therefore be used as is, or connected to an external loudspeaker or amplifier. In its simplest role, the Concertmate can be used as a metronome with controllable sound level and tempo, and LED visual timing indicator. But it also offers eight distinctive rhythms, including latin, bossa, rock, foxtrot and waltz. It offers also, the sound of five musical instruments: bass drum, clave, cymbal, snare drum and high hat. Measuring 28 x 7 x 20cm, the Concertmate operates from 6 C-type cells, or from an external DC supply. As catalog item 42-2103, it is available from Tandy stores and outlets for \$89.95.

**CONCEPT AUDIO PTY LTD** have a cassette head demagnetiser which is marketed under the name "Whistle Stop". Manufactured by Robins Industries in the USA, it looks like a standard cassette but, inside, it contains a special oscillator circuit and batteries to operate it. The idea is to plug the Whistle Stop into a cassette deck, switch the deck on and set it in the "Play" mode. This automatically activates the oscillator, which initially produces a signal at about 60Hz. During the next six seconds approximately, the oscillator frequency slides up the range to beyond audibility. In so doing, the sound can be monitored through the loudspeaker, indicating that the Whistle Stop is doing its job. At low frequencies the magnetising current through the head is quite high but it diminishes to a negligible value as the frequency drifts higher. The Whistle Stop


retails for \$19.95. [Concept Audio Pty Ltd, 22 Wattle Rd, Brookvale NSW 2100. Phone (02) 938 3700].

**R. H. CUNNINGHAM PTY LTD** are producing a small news sheet intended to keep audio professionals and dedicated sound enthusiasts up to date in lines being handled by the Company. To be put on the mailing list, apply through PO Box 4533, Melbourne 3001. Announced in the issue to hand is a new pair of headphones from Sennheiser, type HD222. They are lightweight, with soft cushions and gentle headband pressure. Rated response is 20Hz to 20kHz, impedance 600 ohms and nominal sound pressure level 94dB. Also announced is the Soundex Stereo PPM 400, a twin peak program meter, with in-built ppm amplifiers, illuminated meter movements and mains power supply.

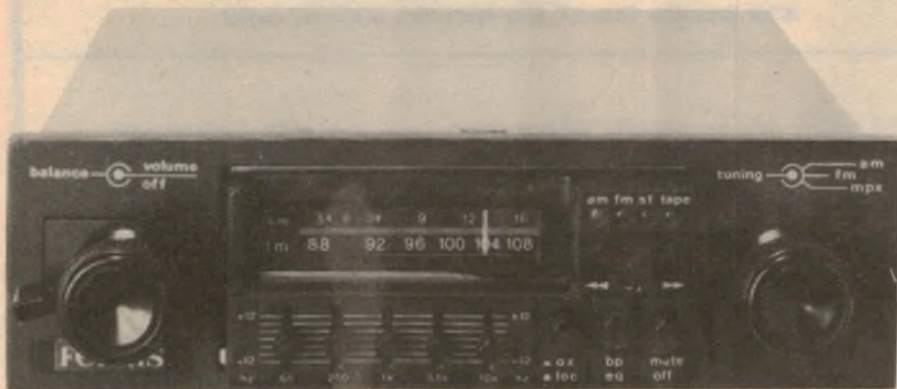


Compact for what it is, the Ferris JMPA 3020 is nevertheless big on facilities and performance. It offers AM/FM-stereo radio with muting and local/DX switch, and stereo cassette with auto stop and lock-in fast forward and reverse. It has volume and balance controls and a 5-level graphic equaliser with a range of  $\pm 12$ dB. Frequency response is quoted as from 50Hz to 12kHz. The price is \$250 approx. For details: J. Manneken, Ferris Audio Products, 353 Victoria St, Brunswick, Vic 3055. Phone (03) 387 3844.

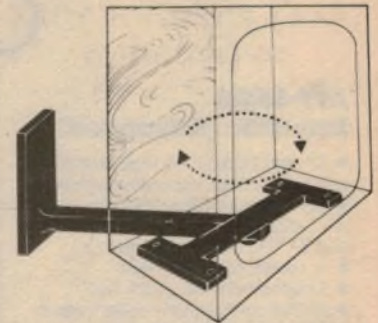
**Piv·telli**  
MULTI-DIRECTIONAL AUDIO/VISUAL  
BRACKETS



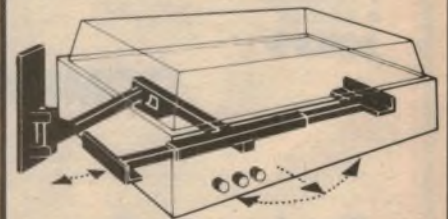- 5 different models available.
- Holds anything from 195 mm to 1204 mm in width (7" to 4').
- Holds up to 110 kilograms in weight.



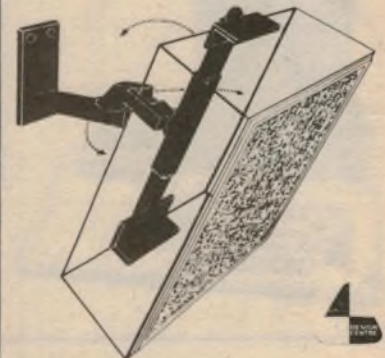- Available with horizontal pivot and vertical tilt.
- Saves valuable floor space.
- Complete with all necessary fixings.
- Solid high grade steel, finished in matt black or gloss white.



**NOW AVAILABLE IN AUSTRALIA**

Please send me free brochure/price list

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

**ASSOCIATED STEEL EQUIPMENT P/L**  
Sole agent in Australia  
11 Horscroft Place,  
Moerabbin, Victoria, 3189  
Phone (03) 555 9921

Perth: Gibson Benness Ind. 323 8686  
Adelaide: Orion Distributors 332 3777



# SCHOOL'S IN CALCULATORS

## APF-8602 Scientific (Advanced)

- 12 Digit Display - 8 Digit Mantissa with sign, 2 Digit exponent with sign.
- Scientific Functions: Sin, Cos, Tan,  $\text{Sin}^{-1}$ ,  $\text{Cos}^{-1}$ ,  $\text{Tan}^{-1}$ ,  $e^x$ ,  $10^x$ , Log, L,  $Y^x$ ,  $X^2$ ,  $\sqrt{x}$ ,  $1/X$ , DMS to degree,  $\pi$
- 2 Levels of parenthesis
- Degree/radians/grads key
- Statistical Functions: mean value, variance, standard deviation
- Normal Distribution
- Permutations & Combinations
- Polar-Rect
- Deg/Rad/Grad Conversions
- Hyperbolics
- Factorial

**\$29.95**



## LOTS MORE MODELS

*12 months guarantee  
Sales tax exemption for students*

*Trade enquiries welcome.*



## APF 2303 Metric Converter

- Wallet & Batteries included
- Metric - Imperial - US
- Length
- Area
- Volumes
- Temperature

**\$19.95**

## COMPUTER WITH COLOUR MONITOR

3 MONTHS GUARANTEE

### The Imagination Machine



## APF APF APF APF

**IM-1** Your Life Will Never Be The Same - Two great achievements - a powerful state-of-the-art personal computer and a thrilling home entertainment centre in one single package

- User-programmable in BASIC
- With loads of pre-programmed software for educational entertainment and home and personal management
- Features - 9K RAM, 14K ROM
- 53 key typewriter-style keyboard
- 32 characters x 16 line screen format
- Alpha numerics in three colour modes with up to eight colours
- Built-in sound synthesizer with a range of three octaves including flats and sharps
- Six function built-in cassette tape deck
- Two game-style hand-held controllers
- Unique shift key for "BASIC keywords"
- Expandable for floppy disk, printers memory and more.

**\$995** inc colour monitor. Tax paid.

### APF ELECTRONICS (AUSTRALIA) PTY LTD

TRADE ENQUIRIES WELCOME.

435 Bourke Street, Melbourne. (03) 67 6412.

#### DISTRIBUTED BY:

**VICTORIA:** CALCULATOR SUPERMARKET, 435 Bourke St, Melbourne  
RADIO PARTS GROUP, 562 Spencer St, West Melbourne  
1103 Dandenong Road, E. Malvern  
KALEXTRONICS, 101 Burgundy St, Heidelberg  
Shop 11, Melton Shopping Centre, Western Highway, Melton  
SELECTED CHEMWAY CHEMISTS

Ph: (03) 67 6412  
Ph: (03) 329 7888  
Ph: (03) 211 8122  
Ph: (03) 458 2976  
Ph: (03) 743 1011  
Ph: (03) 547 9011

**NSW:** (Metro) AUSTRALIAN ELECTRONIC INDUSTRIES, 1-3 Sydenham Road, Brookvale  
(Country) AVIOLOGISTICS PTY LTD, 1 Carter Rd, Brookvale

Ph: (02) 938 4243  
Ph: (02) 929 4011

**QLD:** CUSTOMER COMPUTER SERVICES, 41 Diamond Ave, Kallangur

Ph: (07) 204 4995

**SA:** GRANVILLE DISTRIBUTORS, 2B Gordon St, Glenelg

Ph: (08) 295 4779

#### NT, WA &

**TAS:** APF ELECTRONICS AUST PTY LTD

Ph: (03) 602 4092



# HIFI REVIEW

## Sony PS-X75 automatic turntable

Sony's top-of-the-line record player is the PS-X75, an automatic unit whose turntable is driven by a crystal controlled direct-drive motor. A unique feature is the Biotracer tonearm in which the horizontal and vertical movements of the tonearm are servo-controlled — under microprocessor command — by "linear motors" which are fed information from sensors incorporated in the arm.

At least two of what Sony call "linear motors" appear to be solenoids in which the drive current is varied in an analog manner to give smooth control of the tonearm's movements. The application of solenoids for this purpose appears to be an excellent idea as no friction is incurred, the only slight penalty being a minor increase in mass.

As a matter of interest a similar system has been in use for many years on most of the disc recording lathes located around the world. In this case the application is for control of the vertical movement of the cutterhead such that the depth of cut — and hence groove width — is subject to automated dynamic control according to program level and frequency, as well as providing for remote manual control.

Three motors are incorporated in the Biotracer arm; one for horizontal motion, one for vertical and the other for lifting the tonearm from its (lowered) playing position to its upper (safe) setting. Inverse feedback for the servo amplifiers is derived from moving-magnet sensors which provide electronic damping of solenoid deflections.

Complete electronic control of the horizontal and vertical movements of the Biotracer tonearm allow Sony to provide full remote facilities for the following functions:

- Tonearm raise and lower
- Lateral positioning of the tonearm
- Stylus tracking force
- Anti-skating bias. In practice a separate control is not provided, the bias being obtained as a function of the variable (stylus) tracking force control.

In common with several other state-of-the-art record players, the controls are mounted in a straight line along the front edge of the deck such that even with the clear perspex lid closed, operation is unhindered.

At the extreme left of the control strip is the mains OFF-ON pushbutton. All other controls are grouped together,

reading from left to right:

- Motor OFF-ON pushbutton
- Tonearm traverse "left" pushbutton
- Tonearm traverse "right" pushbutton
- Tonearm raise/lower pushbutton
- Display window
- Turntable speed selector pushbutton
- Repeat play pushbutton
- STOP pushbutton
- START pushbutton
- Stylus tracking force adjustment knob


from its rest, traversing to the outer edge of the record (where the lead-in groove is) and gently lowering the cartridge onto the surface of the record.

When the tonearm has reached the lead-out groove, the arm lift solenoid raises the arm, after which the horizontal motor returns the arm to its rest, with the turntable being brought to rest within approximately one-third of a revolution, through the microprocessor controlling an electromagnetic brake.

After coming to rest the brake is released so that the turntable may be easily rotated by hand for cueing purposes.

Should one wish to cease play before the end of a record, press the STOP pushbutton and the tonearm is lifted from the record and returned to its rest, with the turntable being halted as previously.

If it is desired to repeat-play a side,

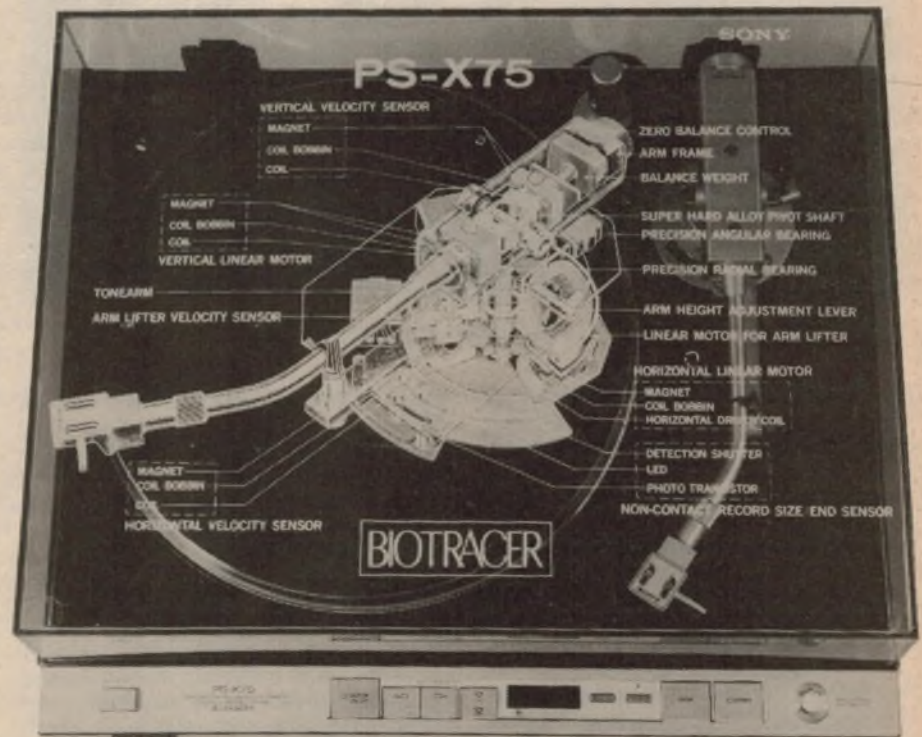

The Sony PS-X75 has all controls mounted outside the lid. Our review sample had a transparent overlay which gave a see-through view of the Biotracer arm.

Playing a record is simplicity itself. Place the record on the turntable, select turntable speed, press the START pushbutton and the motor will start in addition to the Biotracer arm lifting away

press the REPEAT pushbutton. Repeat-play continues until such time as either the REPEAT pushbutton is pressed a second time or the STOP button is actuated.

## SONY PS-X75 TURNTABLE

Manual play is equally easy. In this case, after selecting turntable speed bring the tonearm to the desired position over the record by pressing the traverse "left" pushbutton. Should overshoot occur, one presses the traverse "right" pushbutton to return the arm to the desired position. Thence press MOTOR (ON) and tonearm "lower". The PS-X75 unit will respond to the commands irrespective of which of these two pushbuttons is pressed first.

This is a nice feature since it enables

and a further two seconds for the arm to lower.

To speed up the operation the arm may be moved by hand, which is no handicap when time is at a premium. However, unless the tonearm has previously been lowered electronically in the normal way, it is not possible to lower it by hand.

At the right rear of the turntable is a pillar light which is beamed through plastic prisms on the turntable mat to phototransistors mounted underneath

certainly cannot be considered oversized. In fact it feels just about "right". The mains cable is two-core as the unit is double-insulated, being identified as such by the international "double-square" symbol. The RCA phono plugs are gold plated — a quality touch.

The stylus tracking force is adjustable from the control panel by means of a knob with a scale calibrated in 0.1g increments from zero to 3.0 grams. After initial setting — of which more anon — the accuracy of this remote control appears to be within  $\pm 0.1g$ .

We found great difficulty in accurately setting the initial tonearm balance according to the supplied instructions. The suggested method is to balance the arm by means of the counterweight at zero tracking force. Unfortunately our subjective judgment of "balance" was such that we rarely achieved results closer than  $\pm 0.25g$ , and on occasion incurred an error as high as 0.5g.

But with the aid of a stylus pressure gauge we arrived at a method whereby we would preset the stylus force to, say, 1.0g, and then adjust the counterweight so that the actual stylus force was indeed 1.0g. Having done this we found that the calibration accuracy of the remote stylus force control was within  $\pm 0.1g$  over its range — an excellent performance. To any intending purchasers of the PS-X75 we would therefore suggest the acquisition of a stylus pressure gauge so as to accurately set the stylus force.

The counterweight control knob requires approximately 360° rotation to change the effective stylus force by one gram. This provides good vernier control for adjustment but unfortunately it is all too easy to inadvertently upset this setting as no locking mechanism is incorporated, nor is this control "detented" which would be another way of overcoming the problem.


In normal usage it may be that one's fingers do not stray to this area of the tonearm, but in inspecting and testing we found that we knocked this control out of adjustment on several occasions.

As supplied, the PS-X75 is fitted with a Sony XL-25A cartridge which has a  $0.3 \times 0.8$  mil elliptical diamond stylus. We measured the inductance of each winding and found it to be 530mH, which is about average for today's moving magnet cartridges.

Whilst the suggested tracking force lies within the range from 1.0 to 2.5g, Sony recommends operation at 1.5g for optimum performance. At this pressure the XL-25A handled the +12dB drum test track on the W & G 25/2434 test disc but the tracking force had to be increased to 2.5g in order to track the +16dB test track.

Frequency response of the cartridge was flat within  $\pm 2.5dB$  from 20Hz to 20KHz. Channel separation was 30dB at 1KHz, falling to 20dB at 10KHz and remained essentially the same right up to 20KHz.

(Continued on page 142)

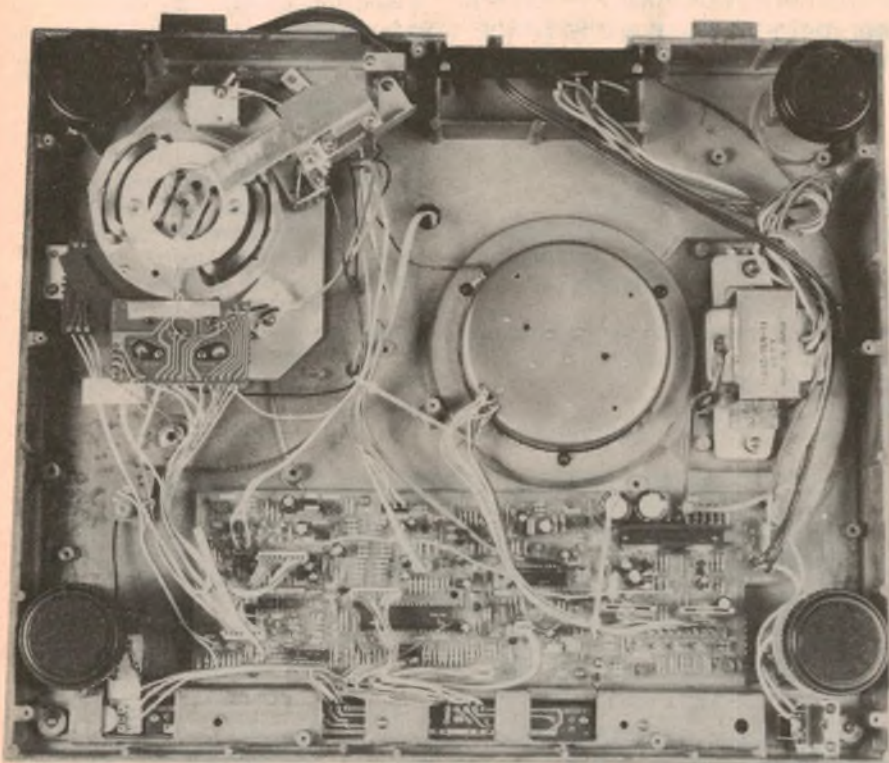

Inside the chassis of the Sony PS-X75. Note the microprocessor on the PC board.

the operator to give priority to mode according to his requirements viz, if searching for an item of music he would probably press MOTOR followed by tonearm "lower", but if he were cueing a track for, say, recording to cassette he could first lower the arm, cue the start of the track by moving the turntable backwards and forwards, and then simultaneously start (turntable) motor and cassette recorder.

The latter operation is assisted by the fact that the turntable only requires one-half revolution to accelerate to normal speed at 33 $\frac{1}{3}$ rpm, and just over three-quarters of a revolution at 45rpm.

Relatively quick as the turntable startup may be, at times one feels just a little frustrated by the time taken for the motors to both swivel and raise/lower the tonearm. It takes about five seconds for the tonearm to traverse from its armrest to a point halfway across a record,

the turntable. This photo sensor system detects the size of record on the turntable for automatic positioning of the tonearm at start of play. If no record is on the turntable, the tonearm will not descend, but will return to its armrest with the turntable being stopped.

Sony describe the turntable drive system as direct-drive, crystal lock, magnedisc servo control system with the motor being brushless and slotless (probably an ac induction motor). Speed accuracy appears to be excellent, certainly better than the  $\pm 0.02\%$  to which we normally measure. Sony claim a speed accuracy of  $\pm 0.003\%$ . Wow and flutter measured just under 0.1%. Whilst just perceptible on constant tones, wow and flutter was not noticeable on normal music recordings.

Width of the PS-X75 is 480mm, depth is 420mm and height is 165mm. Although by no means the smallest in its class, it

# NOT ALL OF THE BEST SPEAKERS ARE IN POLITICS.

But many of them depend on our speakers to make themselves heard. Because we're specialists in the manufacture of loudspeakers for just about any application — P.A. systems, car stereo, hi-fidelity, radio, TV and communications.

Whatever your loudspeaker requirements are the specialists at Magnavox can help.

Just send in the attached coupon for details of our complete range or contact your nearest Magnavox distributor.

Qld. R.A. Venn Pty. Ltd. 67 Doggett Street, Fortitude Valley Qld. 4006  
Ph: 525421. N.S.W. Standard Components Pty. Ltd. 10 Hill Street, Leichhardt  
N.S.W. 2040 Ph: 6606066. VIC TV Tuner Service Pty. Ltd. 469 St. Georges  
Road, Thornbury Vic. 3071 Ph: 446179. S.A. Gladiola Company 11 Laurel  
Avenue, Linden Park S.A. 5065 Ph: 513700. Protronics Pty. Ltd. 180 Wright  
Street, Adelaide S.A. 5000 Ph: 2123111. W.A. Everett International Pty. Ltd.  
17 Northwood Street, West Leederville  
W.A. 6007 Ph: 3815500.

**MAGNAVOX**

Australia Pty. Ltd.




To: Magnavox Australia Pty. Ltd. PO Box M345. Sydney Mail Exchange. N.S.W. 2012.  
Please send me information on Magnavox  High fidelity range  General purpose range.

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

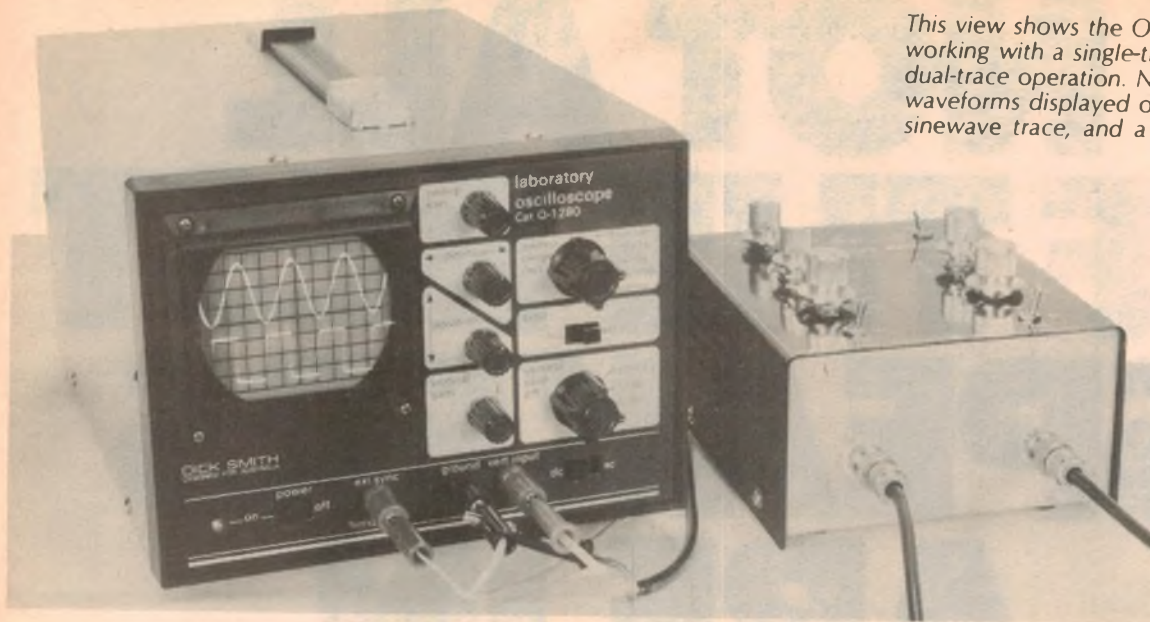This view shows the Oscilloscope Switch working with a single-trace CRO to provide dual-trace operation. Note the two waveforms displayed on the CRT: an upper sinewave trace, and a squarewave.



Add dual-trace facilities to your CRO with this

# Oscilloscope Switch

Dubbed the Oscilloscope Switch, this easy-to-build instrument will increase the versatility of your single-trace oscilloscope by providing dual-trace operation. It features switched attenuators, sync selection, AC or DC coupling and selectable chop rates.

by IAN POGSON

The oscilloscope is without doubt the most useful and versatile instrument we have for observing, measuring and analysing electrical signals. However, if an oscilloscope has only single trace capability, this limits its usefulness to a considerable degree.

Where two signals must be monitored simultaneously the single trace instrument can still be used in some cases but the operator needs more skill in interpreting the resultant display. For example, phase and frequency differences between two signals may be measured using the technique known as Lissajous figures. This involves feeding the two signals to the horizontal and vertical amplifiers of the oscilloscope, and is described in many textbooks.

There are other methods whereby a single trace oscilloscope can be used to compare different signals but they too require extra skill on the part of the operator.

By far the easiest way to monitor two signals simultaneously is to observe them on a dual trace oscilloscope.

Note the term "dual trace" rather than "dual beam". There are very few true double beam oscilloscopes these days, and even the more expensive ones usually use the dual trace system. In the dual trace oscilloscope, a single gun CRT is employed and the beam is switched rapidly between the two signals to give two traces which sweep across the tube face at the same speed.

Essentially, what our Oscilloscope Switch does is convert a normal single trace oscilloscope to dual trace operation, thereby greatly extending its versatility.

As an example, when testing an amplifier one can compare input and output signals and note any phase shifts or distortion. When testing a stereo amplifier, comparisons can be made of signals in both channels and crosstalk may also be observed directly.

One might also use a dual trace oscilloscope for checking a transmitter — comparing the modulation envelope with the modulating signal. At the other end of the line, one can observe detec-


tion or demodulation in a radio receiver.

In digital circuitry, the dual trace oscilloscope really becomes indispensable for observing timing relationships between different pulse trains and seeing logic at work!

There are actually two modes of operation by which a dual trace display can be produced on a single trace oscilloscope. One is the "chopped" mode, the other is the "alternate" mode. In the chopped mode, the electron beam is switched rapidly between the two signals at a rate considerably higher than the frequency of the signals being observed.

In effect, what happens is that a square wave is applied to the vertical amplifier of the oscilloscope. At the same time, the signals to be displayed are superimposed on the square wave — one signal on the upper part of the waveform and the other signal on the lower part of the waveform. The vertical sections of the waveform become invisible, provided the rise and fall times of the square wave are fast enough.

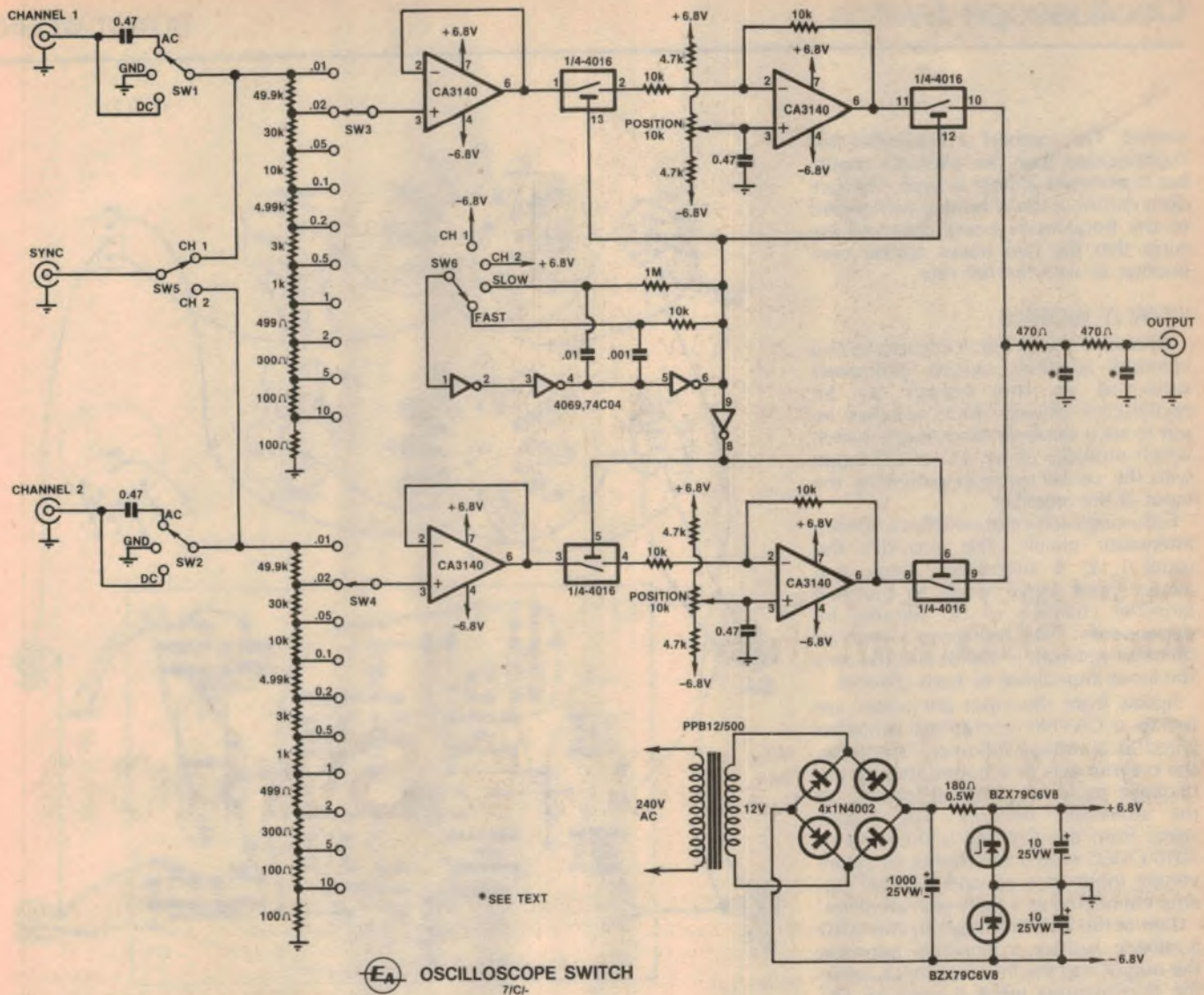The "chopped up" nature of the two apparent traces seems to disappear for two reasons. One is that each waveform develops visual continuity due to its "row of little dashes" nature. The other is that the switching frequency of the square wave is deliberately arranged not to be harmonically related to the signals being displayed. For this reason, the



**EA** OSCILLOSCOPE SWITCH  
71C1

The circuit consists of two identical amplifier channels alternately switched to the output by an oscillator.

dashes effectively "move" along the traces rather than remain stationary.

This, combined with the visual persistence of the tube phosphor and the human eye, makes the two traces appear continuous.

In situations where high frequencies are to be measured however, the chopped trace mode cannot be used. The main reason is that the chopping rate is limited by the bandwidth of the oscilloscope, so that the "chopped" nature of the traces tends to become more apparent when viewing high frequency signals. In these situations, the "alternate" mode of dual trace operation is used.

In this mode, a square wave of lower frequency than those being displayed is applied to the oscilloscope vertical amplifier. The square wave is locked to half the timebase frequency and again has the signals to be displayed superimposed on the upper and lower sections of the waveform. However, in this case the beam traces the upper half of the

square wave (and one signal) in one complete sweep and the lower half of the square wave (with the other signal) on the successive sweep. Hence the "alternate" operation.

Thus, in the alternate mode, the two traces are produced successively and persistence effects in the tube phosphor and the human eyes make it seem as though there are two separate and simultaneous traces.

Most dual trace oscilloscopes have both chopped and alternate trace operation, with the mode automatically selected by the timebase switch (chopped for low speeds and alternate for high). On the more flexible instruments the user has the option of selecting the mode of operation himself.

Our new Oscilloscope Switch has a fast chop rate of 65kHz, but to provide the alternate mode would involve gaining access to the timebase circuitry of the oscilloscope to be used with the switch. As an alternative (no pun intended!) we have provided a slow chop rate (74Hz)

## SPECIFICATION

**Bandwidth (-3dB):**  
DC coupled — DC to 1MHz  
AC coupled — Approx 10Hz to 1MHz

**Input impedance:**  
100kΩ shunted by ≤ 30pF

**Trigger source:**  
Channel 1 triggered by Channel 1 signal; Channel 2 triggered by Channel 2 signal

**Maximum input voltages (attenuator set to .01):**  
DC — ±4V; AC — 3V RMS

**DC blocking on AC input:**  
±250V (DC + peak AC)

**Output DC level shift: ±2V**

**Chop frequencies:**  
Slow — 74Hz; Fast — 65kHz

instead. This method is somewhat less sophisticated than the alternate mode, but it performs almost as well. The random nature of the chopping with regard to the frequencies being observed ensures that the two traces appear continuous, as with the fast rate.

## HOW IT WORKS

Refer now the circuit. It consists of two identical amplifier circuits alternately switched to the output by an oscilloscope driving CMOS switches. Input is via a three-position toggle switch which provides either AC or DC input, with the centre position grounding the input of the amplifier.

Following each input switch is a 10-step attenuator circuit. This provides the usual 1, 2, 5 attenuation steps, and allows input signal levels to the two amplifier channels to be adjusted independently. Total resistance of each attenuator network is 100k $\Omega$  and this sets the input impedance to each channel.


Signals from the input attenuator are fed to a CA3140 operational amplifier wired as a voltage follower. Essentially, the op-amp acts as a buffer, its high impedance providing minimal loading on the attenuator network. The output signal from the CA3140 is then fed to 4016 CMOS switch and thence to the inverting input of a second CA3140 op-amp connected as a unity gain amplifier.

Gain of the amplifier is set by the 10k $\Omega$  feedback resistor connected between the output and the inverting input, while the non-inverting input is used for DC position adjustment. A voltage divider consisting of a 10k $\Omega$  potentiometer and two 4.7k $\Omega$  resistors is connected across the positive supply rails. By adjusting the pot, the user can set the reference voltage on the non-inverting input (pin 3) according to requirements.


Output signals from the unity gain amplifier are fed to a second CMOS switch whose control electrode is wired in parallel with the first. (Some readers may be wondering why we have included CMOS switches on the inputs to the unity gain amplifiers. Why switch the inputs as well as the outputs? We tried the circuitry both with and without the first set of CMOS switches and found that the circuit depicted worked best and minimised output transients.)

Switching transients are further reduced by a two section RC filter wired between the output switches and the output socket. This circuit is something of a compromise between bandwidth and transient suppression, and is open to experimentation by individual constructors. More about this later on.

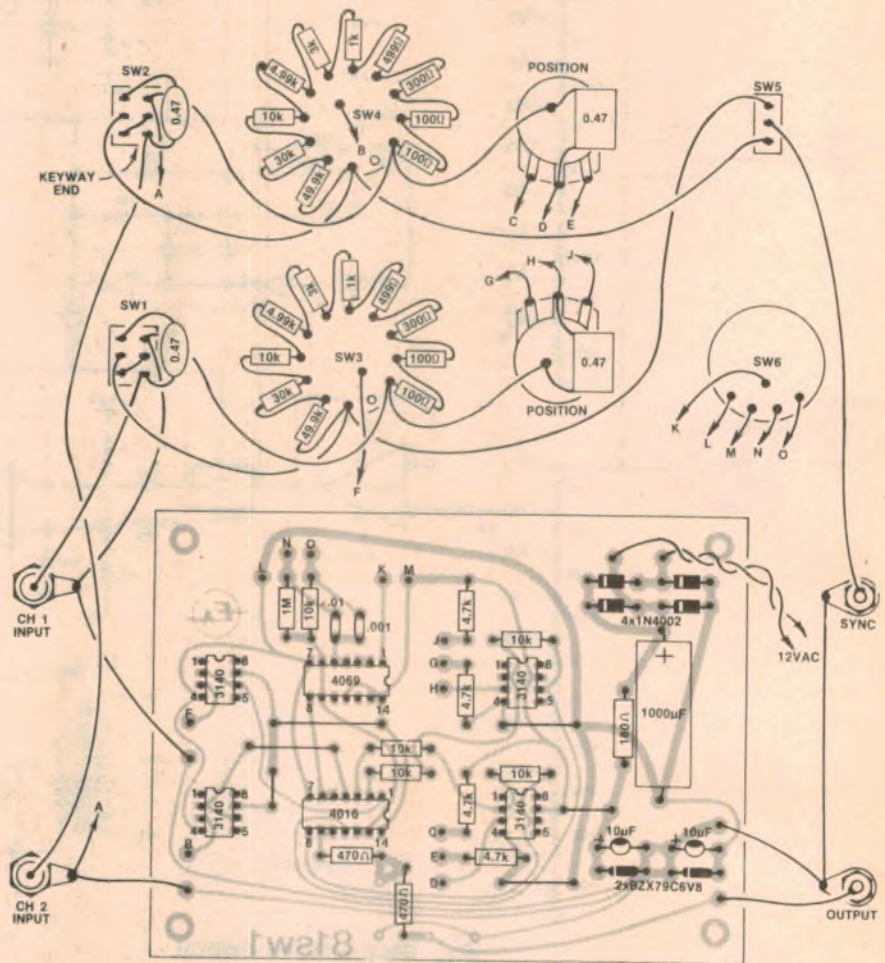
The switching oscillator consists of three sections of a 4069 (74C04) hex in-



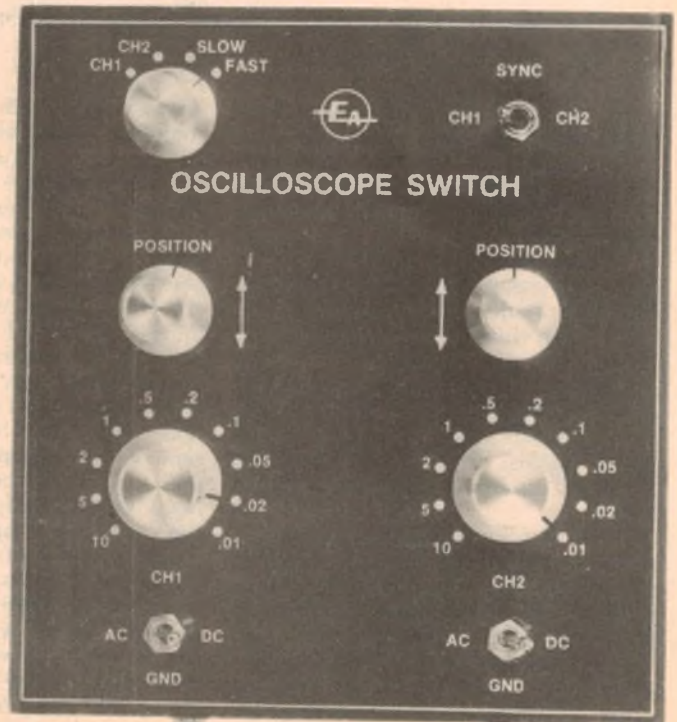ABOVE: the wiring diagram for the Oscilloscope Switch. Note that the resistors on the attenuator switches must be 2% types.



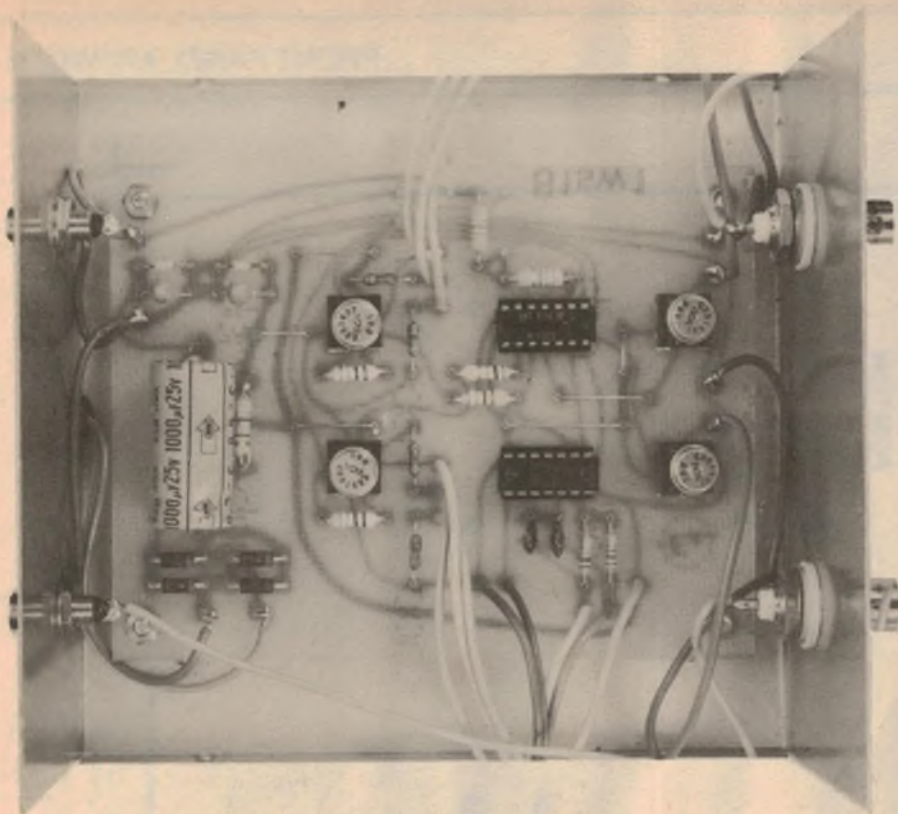RIGHT: the completed prototype. As well as providing dual-trace operation, it also provides a calibrated attenuator for a CRO which doesn't already have this feature.



View inside the prototype showing the assembled PCB. Observe the precautions listed in the text regarding the CMOS ICs, and don't forget the wire links.

## PARTS LIST

- 1 metal case, 150 x 76 x 134mm
- 1 Scotchcal front panel, 134 x 150mm
- 1 printed circuit board, 81sw1, 124 x 93mm
- 1 single-pole 4-position rotary switch (see text)
- 2 single-pole 12-position rotary switches (see text)
- 2 2-pole 3-position miniature toggle switches
- 1 SPDT miniature toggle switch
- 2 10k $\Omega$  linear potentiometers
- 5 knobs to suit front panel
- 1 12VAC plugpack transformer
- 4 8-pin DIL sockets (optional)
- 2 14-pin DIL sockets (optional)
- 2 single hole mounting RCA sockets
- 1 rubber grommet
- 2 insulated BNC sockets (see text)

### SEMICONDUCTORS

- 4 1N4002 or similar power diodes
- 2 BZX796C6V8 zener diodes
- 4 CA3140 op-amps
- 1 4069 or 74C04 hex inverter
- 1 4016 or 4066 quad bilateral switch

### RESISTORS (1/2W, 5% unless stated)

- 1 x 1M $\Omega$ , 5 x 10k $\Omega$ , 4 x 4.7k $\Omega$ , 2 x 470 $\Omega$ , 1 x 180 $\Omega$  1/2W

### RESISTORS (1/4W, 2%)

- 2 x 49.9k $\Omega$ , 2 x 30k $\Omega$ , 2 x 10k $\Omega$ , 2 x 4.99k $\Omega$ , 2 x 3k $\Omega$ , 2 x 1k $\Omega$ , 2 x 499 $\Omega$ , 2 x 300 $\Omega$ , 4 x 100 $\Omega$

### CAPACITORS

- 1 1000 $\mu$ F 25W axial lead electrolytic
- 2 10 $\mu$ F 25VW tantalum
- 4 0.47 $\mu$ F 250V metallised polyester (greencap)
- 1 .01 $\mu$ F greencap
- 1 .001 $\mu$ F greencap
- 1 47pF ceramic (see text)

### MISCELLANEOUS

Screws, nuts, hookup wire, PC stakes, solder etc.

**NOTE:** Ratings are those used on the prototype. Components with higher ratings may generally be used providing they are physically compatible. Components with lower ratings may also be used in some cases, provided the ratings are not exceeded.


verter arranged in standard three-gate configuration. It has two switched output frequencies selected by switch SW6 to provide the fast and slow chop rates (65kHz and 74Hz). A fourth section of the hex inverter is used to give a second output (at pin 8) which is 180° out of phase with pin 6.

With this arrangement, the oscillator output at pin 6 controls the CMOS switches in Channel 1 while the inverted output from pin 8 controls the switches in Channel 2.

The remaining two switch positions on SW6 switch the oscillator off so that the user can select either channel for display. For example, in the CH 1 position, pin 1 of the 4069 is pulled low, thus forcing pin 6 high and activating the CMOS switches in Channel 1. In the CH 2 position, pins 1 and 8 of the 4069 go high and the Channel 2 trace is displayed.

When viewing the signal traces, the oscilloscope timebase frequency must be synchronised directly from one of the two input signals – the one desired to be kept stationary. In our circuit, sync signals are derived directly from the wipers of the input switches (SW1 and SW2) and are selected by switch SW5.

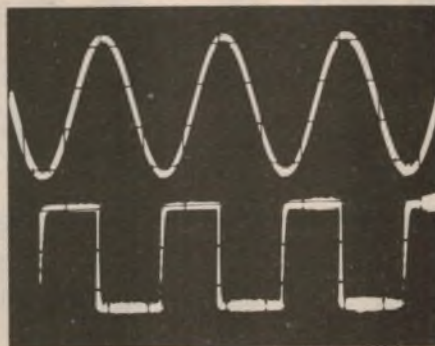In practice, this means that the oscilloscope should be set for external synchronisation of the timebase (Ext Sync) and the external sync terminal connected to the sync terminal on the Oscilloscope Switch. SW5 then allows the user to synchronise to either Channel 1 or Channel 2.



A typical display produced by the Oscilloscope Switch. The small breaks in the traces are the graticule lines.

The power supply is derived from a nominal 12V AC which may be obtained from a plugpack or any other suitable transformer. The 12V AC is fed to a bridge rectifier using four 1N4002 (or similar) power diodes, and the rectified output filtered by a 1000 $\mu$ F 25VW electrolytic capacitor. The filtered DC output is then split and regulated by two BZX79/C6V8 zener diodes to give the plus and minus 6.8V supply rails.

## CONSTRUCTION


We built our Oscilloscope Switch into a standard metal case measuring 150 x 76 x 134mm. Construction is straightforward, with most components mounted on a small printed circuit board (PCB)

measuring 124 x 93mm and coded 81sw1. A Scotchcal label provides an attractive finish to the completed instrument.

Both the PCB and the Scotchcal label should be available through the usual retail outlets by the time this article appears in print. A list of potential suppliers is published on the last page of the magazine.

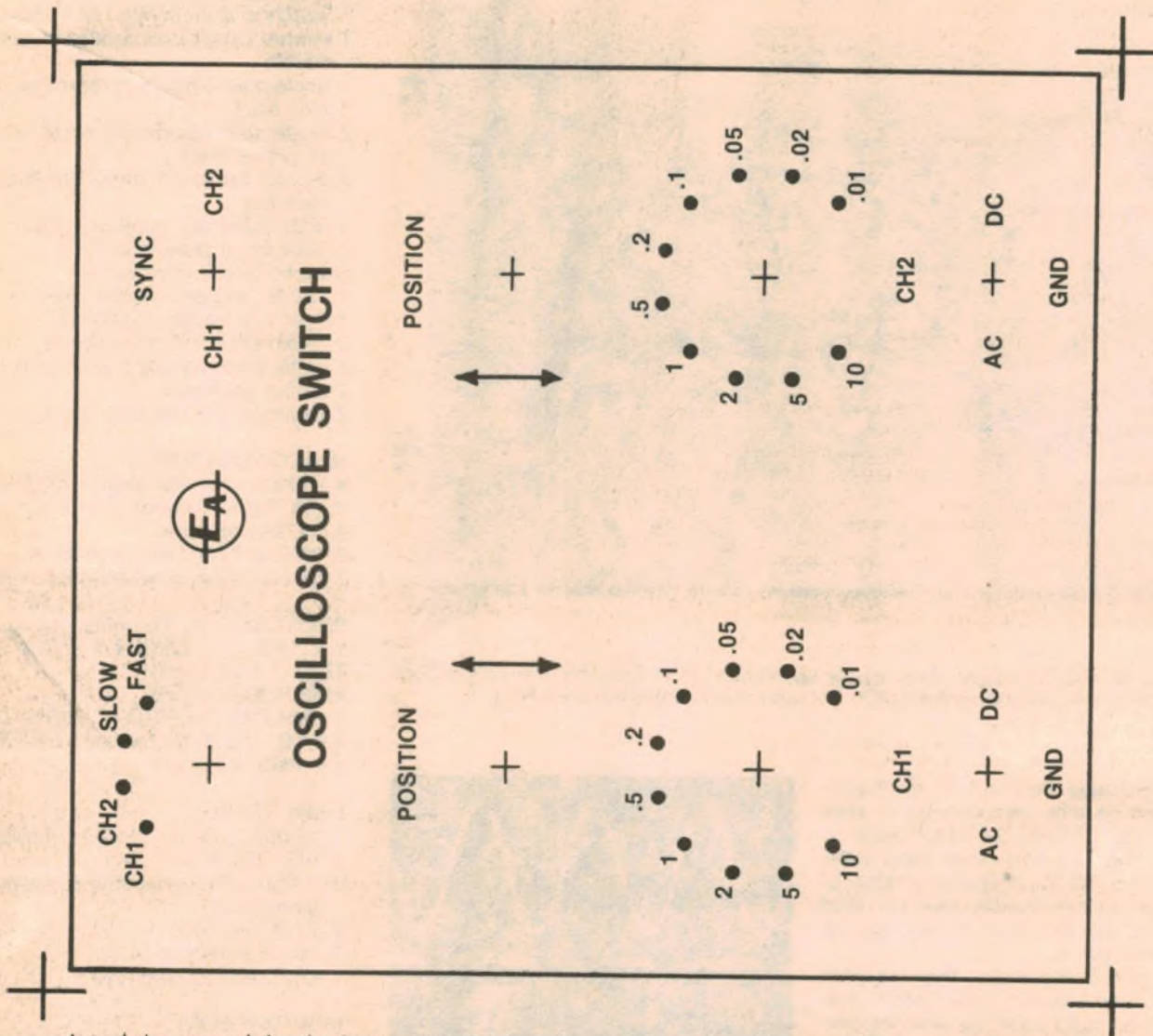Commence construction by assembling the PC board. Follow the accompanying wiring diagram carefully and make





Actual size artwork for the front panel. Finished "Scotchcal" panels will be available from retail outlets.

sure that all polarised components are correctly oriented. Don't forget to install the six wire links, and leave the CMOS ICs (4016, 4069) till last. We used IC sockets in the prototype and readers may care to do the same.

If you do elect to solder the ICs into circuit, then the following precautions should be observed for the CMOS devices: avoid handling the pins; earth the barrel of your soldering iron to the earth track on the PC board using a clip lead; and solder the supply pins (pins 7 and 14) first.

The use of PC stakes is recommended to facilitate external connections to the PCB.

Once the PCB assembly is complete, the case can be drilled to accept the two RCA sockets, the BNC input sockets, and the rubber grommet through which the power supply leads pass. This done, the PCB can be mounted in the case using machine nuts and screws and the wiring

to the sockets completed.

The next step is to fix the Scotchcal label to the case lid and drill the holes for the various front panel controls. However, if you are using a case similar to that used for the prototype, you may find that the Scotchcal panel will not adhere properly due to the rough nature of the painted finish. The solution is to augment the adhesive on the panel with rubber cement such as Bostik or similar material.

Now mount the front panel controls and complete the wiring according to the diagram. Note that the two potentiometers should be oriented so that their lugs face each other, and that the resistors fitted to the attenuator switches must be 2% close tolerance types (or better).

Some readers may think that some of the resistor values specified for the attenuator network are a little strange, eg 49.9k $\Omega$ , 4.99k $\Omega$  and 499 $\Omega$ . The explana-

tion is quite simple — these are the close tolerance preferred values and are so close to the required values of 50k $\Omega$ , 5k $\Omega$  and 500 $\Omega$  that it really doesn't matter! If you have difficulty in obtaining some values, then the 49.9k $\Omega$  resistor can be replaced by two parallel 100k $\Omega$  resistors, the 30k $\Omega$  resistor can be replaced by two series 15k $\Omega$  resistors, and so on.

A few other comments on components may also prove helpful. First, although a single-pole 4-position switch

We estimate that the current cost of parts for this project is approximately

**\$60.00**

This includes sales tax but does not include a plugpack.

# PLAYMASTER MOSFET STEREO AMPLIFIER

Performance of prototype:

POWER OUTPUT	One channel	Both channels
4 ohms	64W (72W)	45W (60W)
8 ohms	50W (56W)	42W (50W)
16 ohms	37W (38W)	31W (31W)

## FREQUENCY RESPONSE

Phono inputs	RIAA equalisation within 1dB from 30Hz to 20kHz
High level inputs	25Hz to 20kHz $\pm$ 1dB

## CHANNEL SEPARATION

(with respect to 50W) 10kHz	-40dB
1kHz	-47dB
100kHz	-50dB

## INPUT SENSITIVITY

Phono at 1kHz	2mV	56k
Overload at 1kHz	120mV	
High level inputs	190mV	36k (minimum)

## HUM & NOISE

Phono (with respect to 10mV)	73dB (75dB) unweighted with typical cartridge
Other inputs	80dB (82dB) unweighted with inputs open circuit

## TOTAL HARMONIC DISTORTION

At full power with both channels operating from 25 to 20kHz: less than 0.2%  
Typically less than 0.05% at normal listening levels



## TOPE CONTROLS

Bass	+12, -13dB at 50Hz
Treble	$\pm$ 10dB at 10kHz

## DAMPING FACTOR

at 1kHz	> 50
at 30Hz	> 50

## STABILITY

Unconditional  
(Figures in brackets refer to the performance with the Ferguson PF 4361/1 transformer.)

PCB \$9.90

Output transistors

Front panel \$11.00

- Complete kit of parts ..... \$159.00 ea
- Front panel ..... \$11.00 ea
- PCB 80Sa 10 to suit ..... \$9.90 ea
- Mosfets to suit 2Sk133 ..... \$8.95 ea
- Mosfets to suit 2SJ48 ..... \$8.95 ea

## KITS

## KITS

## KITS

## KITS

## KITS

## KITS

## KITS

Kit for Exidy Sorcerer EPROM Programmer to be released in August EA Kit price including Scotchcal Front Panel ..... \$75.00

### TV PATTERN GENERATOR

Kit of parts as featured in EA JUNE 1980, Dot, Greyscale, Crosshatch, Raster, Check

COMPLETE KIT (including Scotchcal front panel) ..... \$48.49

KIT WITHOUT BOX ..... \$36.90

### EPROM PROGRAMMER KIT

Kit of parts as featured in EA JULY 1980 Programs 2708, 2716 & 2532 Usw with TRS 80, Sorcerer & Compucolour Kit does not include connector from the programmer to computer

COMPLETE KIT (inc Scotchcal Front Panel) ..... \$72.49

KIT WITHOUT CASE ..... \$59.99

### DIGITAL PANEL CAPACITANCE METER

Kit of parts as featured in EA MARCH 1980  
Four Digits. Extremely popular

COMPLETE KIT (inc Scotchcal Front Panel) ..... \$52.49

KIT WITHOUT CASE ..... \$39.99

### TV CRO ADAPTOR KIT (EA MAY 1980)

COMPLETE KIT (Inc Scotchcal Front Panel)

(without power adaptor) ..... \$29.00

### POWER ADAPTORS TO SUIT

1 240V to 6/7.5/9V ..... \$ 9.50

2 240V to 9V ..... \$ 5.95

## KITS

### ETI SERIES 4000 60W STEREO AMP KIT

Complete Kit Rack Mounting Case ..... \$199.00

Woodgrain Sided Case ..... \$189.00

### PARTS AVAILABLE SEPARATELY

Front Panel ..... \$10.90

Rack Mounting Case ..... \$55.00

Wooden Sided Case ..... \$49.00

ETI 471 PREAMP KIT of parts ..... \$45.00

ETI 472 PS KIT of parts ..... \$47.00

(without transformer) ..... \$24.00

ETI 470 60W Kit of parts ..... \$26.50

(without heatsink) ..... \$23.00

ETI 480 50W KIT of parts ..... \$17.50

ETI 480 100W KIT of parts ..... \$22.50

ETI 084 Car Alarm KIT ..... \$11.50

EA TV CRO ADAPTER KIT ..... \$29.00

EA 300W POWER AMP MODULE ..... \$63.50

ETI 466 300W PA MODULE ..... \$63.50

EA DIGITAL CAPACITANCE METER KIT (EA

March 1980) ..... \$52.99

AUTOCHIME KIT ..... \$29.75

### MK3 Drill Speed Control

..... \$13.50

CAPACITOR DISCHARGE IGNITION ..... \$32.50

MUSICOLOR MK3 KIT ..... \$69.50

DISCO STROBE KIT ..... \$34.50

LEDS & LADDERS (EA August) ..... \$15.75

ETI 149 Two Tone Generator ..... \$34.90

ETI 563 Nicad Fast Charger ..... \$54.90

DREAM 6802 KIT ..... \$109.00

Power Supply TO Suit ..... \$29.50

Hex Keypad ..... \$24.90

ETI 568 Sound or Light Operated Flash Trig-

ger ..... \$25.90

ETI 147 ELECTRONIC DUMMY LOAD KIT ..... \$99.00

SERIES 3000 "MINI" STEREO AMP KIT ..... \$79.90

ETI 561 Metal DETECTOR KIT ..... \$32.50

PLAYMASTER 40+40 AMP KIT ..... \$129.00

PLAYMASTER AM/FM TUNER KIT ..... \$129.00

PLAYMASTER GRAPHIC EQUAL ..... \$99.50

PLAYMASTER GRAPH ANALY KIT ..... \$99.50

EA 79SF9 Sound Flash Trigger ..... \$15.00

ETI 585H Ultra Sonic RX ..... \$15.95

ETI 585T Ultra Sonic TX ..... \$8.95

ETI 576 ELECTROMYOGRAM KIT ..... \$89.00

### ETI Digital Clock ETI 564

At last a clock display that can

be read at a distance;

Kit of parts

..... \$79.50

### ETI 262 House Alarm

Kit of parts only

..... \$15.90

### New EA Light Chaser

Kit \$64.95

Includes Case plus Kit of parts.

### LEDS and Ladders

EA August 80

Great game for winter nights.

Kit of parts \$18.00

Scotchcal Front Panel

to suit 3-25

### ETI Digital Car Tacho

ETI 324 . . . Kit of parts

..... \$29.95

### EA Power Saver

August EA, an interesting approach to power savings. Kit of parts

..... \$32.50

### ETI147 OCT 80 ELECTRONIC LOAD

Kit parts

..... \$75.00

### ETI327 TURN HAZARD UNIT

Kit parts

..... \$22.00

### EA DIGITAL ENGINE ANALYSER

Oct 80 80TM8a/10 kit parts inc front panel

..... \$44.95

### EA CAR BATT VOLTAGE MON

Oct EA kit parts

..... \$6.50

### EA BIPOLAR TRAIN CONTROLLER

Nov 80 kit parts

..... \$26.00

### EA DIGITAL STORAGE CRO

Adapter Nov 80 kit parts

..... \$78.00

### EA LIGHT BEAM RELAY NOV 80

Kit of parts


..... \$13.00

### EA RS232 PRINTER INTERFACE

Nov 80 kit parts

..... \$15.00

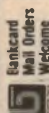Please note we attempt to have all kits available to our customers. Provided of course we have the required information from the mags in time. Where a component is unavailable we may use a substitute or credit this cost so as to prevent delay.



Please debit my Bankcard.

Bankcard No. ....

Expiry Date ....

Name .....

Signature .....

Post & Pack \$2.50 small kits, heavier kits add extra postage

Prices subject to change without notice. Send 60c and SAE for free catalogues.

MAIL ORDERS: PO Box 135, Northcote, Vic 3070. Minimum pack and post \$1.00.

Phone (03) 489 8131.


# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE, VICTORIA. Ph (03) 489 8131



# HITACHI OSCILLOSCOPES

## 2 YEAR WARRANTY

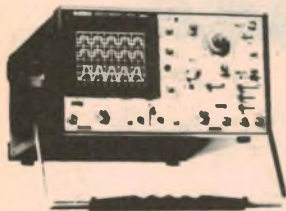

### V550 50 MHz \$1,795

Professional quality oscilloscope with many unique usable features: 50 MHz Dual Trace, Third Trace Trigger View, 1 mV/Div. Sensitivity, Delayed Sweep, X10 Sweep Magnification. Equivalent Oscilloscopes cost 100s of dollars more. Supplied under contract to the A.B.C.



### V302 30 MHz \$955

Dual Trace 30 MHz 1 mV Sensitivity per division. Built in delay line plus many other features. Ideal for general purpose, transceiver and TV service, and digital use. The only 30 MHz 1 mV oscilloscope available for less than \$1,000. In use by the CSIRO.



### V152 15 MHz \$572

Dual Trace 15 MHz, 1 mV Sensitivity, XY operation, TV sync separator circuit. Sweep times magnifier (10 times) Trace rotation Z Axio Input. Excellent value for money. Supplied to many Government Departments and National TV Service Companies.

\* New low price \*



Hitachi new generation oscilloscopes are unequalled for reliability, operating ease, technical features and value for money. You can confidently buy HITACHI Test Instruments for year after year of trouble-free use.

Prices + S/Tax 15%. Subject to change. FOT Sydney.

#### HITACHI AVAILABLE FROM:-

N.S.W. Radio Dispatch Service, David Reid Electronics, Standard Components, Emtronics, D.G.E. Systems Newcastle.  
Vic. Ellistronics, G.B. Telespares, David Reid Electronics, ECQ Electronics, J. H. Magrath & Co. Pty. Ltd.  
Qld. Audiotronics, ECQ Electronics, St. Lucia Electronics.  
S.A. Bee Jay Electronics.  
W.A. Reserve Electronics.  
Tas. George Harvey Electric Launceston and Hobart

## Standard Components Pty. Ltd. "STOCKISTS IN ALL STATES"

10 Hill St., Leichhardt N.S.W. 660-6066

## RADIO DESPATCH SERVICE

869 George St, Sydney 2000 Near Harris St.

Phone 211 0816, 211 0191

### FEBRUARY SPECIALS

- 1 "M/Sound" Cartridge Head Cleaner ..... ea 70c
- 2 Ralmar SDH-7D Stereo Headphones \$8.95
- 3 "M/Sound" M-92 Music Centre Care Kit ..... \$8.80
- 4 Oval Speaker 6" x 4" 15 ohm ..... \$2.50
- 5 Sansei 12V Red Led Bezel ..... ea \$1.00
- 6 EP-1 T/Radio 3.5mm Earpiece ..... ea 55c
- EP-2 T/Radio 2.5mm Earpiece ..... ea 55c
- 7 ACV-27 CB Antenna Converter ..... \$9.90
- 8 EP-1/A TV/Radio Long Cord 3.5mm Earpiece ..... ea 70c
- EP-2/A TV/Radio Long Cord 2.5mm Earpiece ..... ea 70c
- 9 E-Z Circuit Drawing Aids for Projects and Printed Circuit Design etc
- 10 Ni-Cad Rechargeable AA Penlite Cell ..... ea \$1.75
- 11 Cassette Recording Tapes, C-45, C-60, C-90, and C-120 — range available
- 12 Inspect our range of Instrument Boxes in — Alum, Diecast, Plastic etc — wide range carried.

### BUY TEXAS CALCULATORS

	Excl ST	Incl ST
TI 30 SP	20.00	22.10
TI 1750	16.40	18.15
TI BAII	40.97	45.35
TI 50	36.40	40.30
TI 55	55.35	59.00
TI Programmable 58C	132.00	149.00
TI Programmable 59	265.00	299.90
PC 100C Printer	210.00	237.00
Specialty Packettes	8.00	9.00
Library Modules	30.50	34.50

### COMPUTER COOLING FANS

Muffin 240V	\$28.75
Sprite 240V	\$30.76

### 14 New Electronic Learning Aids by Texas Instruments

- A Speak and Math Grades 1-6 ..... \$73.68 \$81.57
- B Speak and Read for Beginners ..... \$81.96 \$90.74
- 15 See us first for components to build projects etc, Resistors, Capacitors, Transistors and Diodes — extensive range carried.

All PC Boards for EA & ETI Projects Front panels for some 1979 and 1980 EA & ETI projects. Black or silver background by the Scotchcal System.



Hirose and Ansley Ribbon Cable Connectors fitted same day.

### CANNON AUDIO CONNECTORS

We are distributors for Canon plugs and sockets.



### MAIL ORDER CUSTOMERS

Packing charge	\$1.00
Postage Local min	\$1.00
Postage Interstate min	\$1.50

OPEN: Mon-Fri 8am to 5.30pm. Thursday night late shopping till 8.30pm. Saturday 8am to 11.45 am.

has been specified in the parts list, we actually used a 3-pole 4-position unit. The latter type is more readily available, and does not appear to be any more expensive. Also, 2-pole 3-position miniature toggle switches are specified in the parts list, but only one pole of each switch is used in the circuit. Again, the 2-pole types are more readily available.

Insulated BNC sockets were fitted to the prototype since we wished to use probes with BNC plugs. Many constructors will no doubt prefer to do the same, although other types of sockets may be used if you so wish. Whatever type of input socket you do decide to use, it should be insulated from chassis to keep channel crosstalk to a minimum.

We used RCA sockets for the sync and output sockets.

With respect to ICs, it is worth noting that type 4069 is identical with type 74C04, while type 4016 may be replaced with type 4066. The CA3140 op-amps used were in the TO-5 style package, although standard 8-pin DIL packages may be used instead. Either type can be plugged into the 8-pin DIL socket.

We mentioned earlier that the RC filter on the output was open to some experimentation. We found that a 47pF capacitor fitted between the two resistors was sufficient, the capacitance of the output cable substituting for the second capacitor. Admittedly, this did reduce the bandwidth of the system somewhat, but it also significantly reduced the switching transients.

We also found on the prototype that we could dispense with the 47pF capacitor, provided the output cable capacitance was of the order of 80pF.

## FINAL TESTING

With the construction of the Oscilloscope Switch now complete we are in a position to test and set it up for use. We suggest that you go through the following procedure:

- Set SW1 and SW2 to "AC", SW3 and SW4 to ".01", and SW6 to "FAST";
- Set both "POSITION" potentiometers to mid-position;
- Connect the output cable to the input socket of the oscilloscope and the sync lead to the external sync input of the oscilloscope;
- Switch on the oscilloscope, set it to DC input, and adjust the trace to the centre of the screen.

Now switch on the Oscilloscope Switch. Two traces should now appear on the screen, and these should move vertically with adjustment of the two position controls. If the movement of the traces is restricted, the gain control of the oscilloscope is set too low. Advance

the gain control until the trace can be moved over the full range of the screen.

From here on, it is simply a matter of getting used to the operation of the Oscilloscope Switch. In general, you will find that fast chop will be best for viewing low frequency signals, while slow chop will be best for high frequencies.


The way in which the input switches are used will soon become obvious. Selection of "AC" or "DC" depends on whether the DC component of the signal is to be taken into consideration, while the "GND" position grounds the input circuit without grounding the input signal. The latter facility is useful for setting the trace so that DC signal levels can be measured.

We settled for an input impedance of 100k $\Omega$  rather than 1M $\Omega$ . A 1M $\Omega$  attenuator would require some elaborate frequency compensation, whereas 100k $\Omega$  could be used without any compensation and with only a relatively

small effect on the losses of high frequency components. However, there are some losses and to keep these to a minimum we suggest that wherever possible the attenuator should be set to ".01" when viewing frequencies above about 500kHz.

Finally, the Oscilloscope Switch provides the bonus of a calibrated attenuator for a CRO which doesn't already have this feature. Assuming that you have a CRO with a sensitivity of 10mV/div or better, the procedure is to set the attenuator switch on the Oscilloscope Switch to "1" and feed in a suitable AC reference voltage say 5V p-p. (An unabashed plug: the EA Voltage Reference, described in June 1976 and January 1977, is ideal for this purpose.)

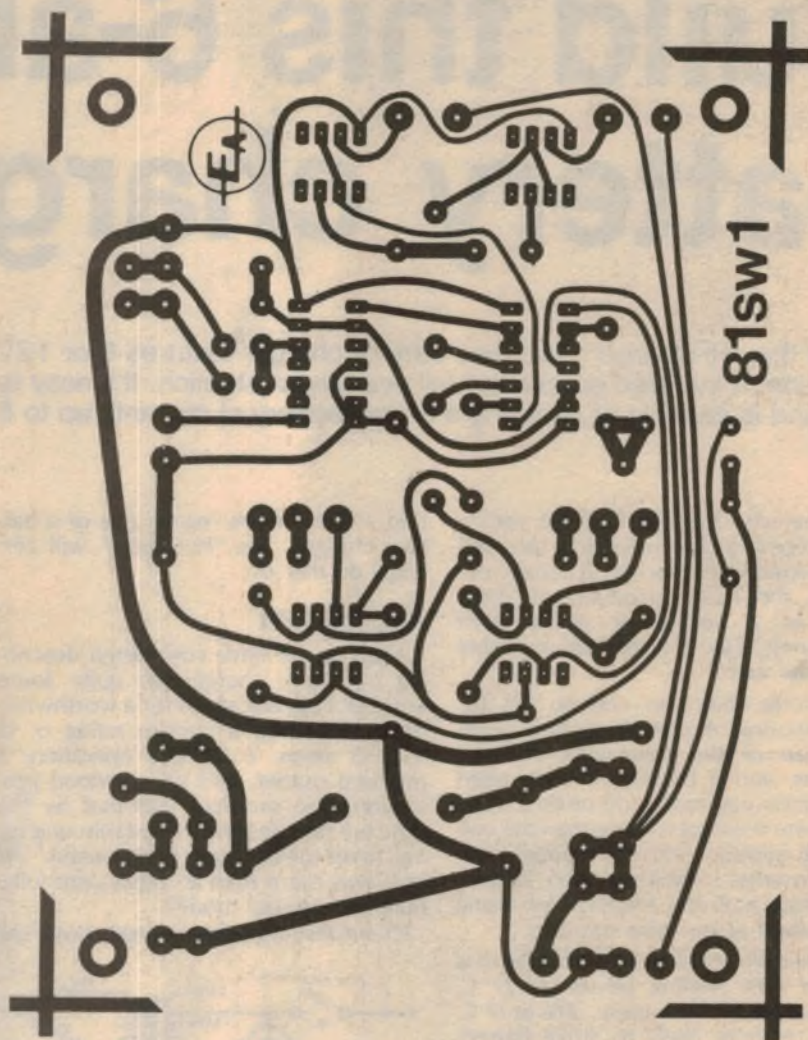Now all you have to do is adjust the sensitivity of your CRO to give a reading of 1V/div. The result — a calibrated attenuator capable of switching from 10mV/div sensitivity down to 10V/div sensitivity!



Actual size reproduction of the printed circuit board pattern.

New design features full overload protection

# Build this 6-amp battery charger

Called the "Hi-Charge", this new battery charger features 6 or 12V operation, a metered output and full overload protection. It's easy to build and is capable of charging a typical battery at currents up to 6 amps.

by GREG SWAIN

Anyone who has been caught with a flat battery in a car knows only too well how frustrating this can be. It usually occurs at the most inconvenient time, often as a result of one's own carelessness. Ever left the parking lights on in your car?

Of course, batteries can go flat for other reasons. A combination of short runs, use of the headlights and accessories, and a battery that has seen better days may easily add up to a situation where the load is more than the battery can supply. And quite apart from these external conditions, the battery itself aggravates the situation by being less efficient at low temperatures.

For example, a half-charged battery has typically 60% starting power at 27°C, which could fall to a mere 30% at 0°C. So you're more likely to strike battery trouble in winter, when the battery is least efficient and when much greater use is made of lights and other accessories. Also, to some extent, the starter motor will draw more current in cold weather because the engine is harder to crank.

For all these reasons, well-prepared motorists like to keep a battery charger in the garage, either to get their car back on the road when the worst happens or, better still, to prevent trouble occurring when the likelihood can be foreseen. Unfortunately, most of us get caught "with our pants down" — a flat battery, no battery charger and a 2½ hour wait for a service van. The battery charger design presented here is your chance to correct this situation.

Boating enthusiasts and caravanners are even more likely to be interested in our new battery charger. Boats and caravans tend to be used at irregular intervals and batteries left idle in a partially charged state or "flat" tend to deteriorate. Ideally, these batteries should be kept in a fully charged condi-

tion, which means regular use of a battery charger. The "Hi-Charge" will certainly do this job.

## THE DESIGN


Actually, we have considered describing a battery charger for quite some time. Our specifications for a worthwhile design included a current rating of at least 5 amps, 6 or 12V operation, a metered output, and full overload protection. The problem was that by the time we had designed a suitable unit using over-the-counter components, its cost was more than an equivalent fully-built commercial model!

It's surprising just how quickly costs can

Australia", complete with circuit and wiring diagrams and full constructional details.

The result of our joint efforts is this fully-protected 6-amp battery charger which we have christened the "Hi-Charge". (A&R refer to it simply as the PS518 Charger Kit.) At around \$58 it is substantially cheaper than the Arlec Charger 8 which has similar specifications, but is sold fully assembled.

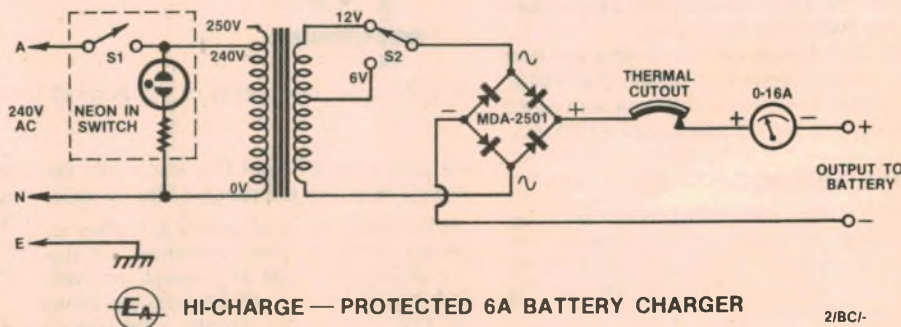The Hi-Charge conforms with all the specifications listed above and in addition, features a current rating of around 6 amps. This is where the Hi-Charge scores over the \$25-30 battery chargers that you may have seen in discount stores



The circuit consists of a transformer driving a bridge rectifier. A bi-metal thermal cutout provides protection in the event of overload.


escalate by the time one mounts a suitable transformer inside a case and then proceeds to add a high power bridge rectifier, a meter, switches, output cables, and other sundry items of hardware!

Our approach was to put the problem to A&R Electronics Pty Ltd who, among other things, manufacture a range of commercial battery chargers. Could they design a kit using off-the-shelf components that the hobbyist could assemble at favourable cost? In return, we would feature the article in "Electronics

and motor accessory shops. The latter only have a continuous current rating of 1-2A, hardly sufficient to get you moving quickly when you do get a flat battery.

By comparison, the Hi-Charge should be able to "pump" enough charge into the battery to get you going within a period of 15 or 20 minutes (as opposed to a wait of some hours). So the extra money for the heavier duty unit is well worthwhile.

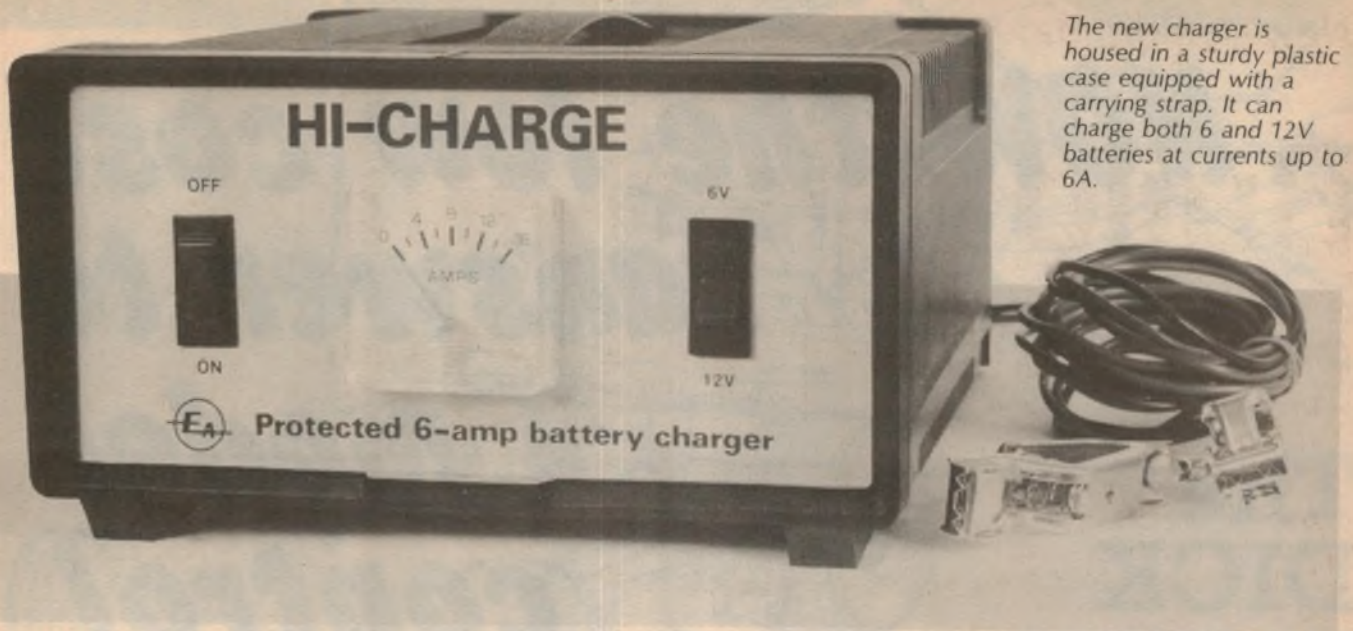Refer now to the circuit. It's really very simple and consists of a transformer driving a bridge rectifier. The transformer



The new charger is housed in a sturdy plastic case equipped with a carrying strap. It can charge both 6 and 12V batteries at currents up to 6A.

has a nominal output voltage of 14.3V with a tap at 8.4V, and these are selected by switch S2 to provide for 12V and 6V operation respectively.

S1 switches the mains active and features a built-in neon indicator to give visual indication of mains on or off. Note that a 250V tap is provided on the primary side of the transformer in addition to the usual 240V AC connection. This 250V AC connection should be used in areas where the mains voltage is consistently above 240V, eg in Western Australia.

Overload protection is provided by a bi-metal thermal cutout wired in series with the positive output. While at first sight this method may seem rather crude it is actually very effective and has several advantages over electronic systems, including low cost, simplicity and reliability. It provides protection in the event of overload due to reverse battery connection, output short circuits and incorrect selection of charging voltage.

Essentially, the thermal cutout monitors the output current, although not in the same way as an electronic protection circuit. It works as follows: as current flows through the cutout, it heats the bi-metal strip, the degree of heating depending upon the current level. If the output current exceeds a certain level, the temperature of the bi-metal strip will rise, the strip will bend, and the load will be disconnected.

The thermal cutout will then cycle on and off every few seconds until the fault condition is removed.

Selection of the thermal overload point is critical, since the cutout must be able to hold the rated current in high ambient temperatures but still react quickly enough to fault currents to protect the transformer and the bridge rectifier. In the Hi-Charge, the thermal cutout operates at about 7 amps.

The two presspahn barriers fitted to the transformer serve to separate the primary and secondary wiring areas inside the charger. They are an important safety feature – in fact, if construction is carried out according to this article, the resulting charger will substantially comply with the requirements of Australian Standard C126.

A 0-16A meter movement, also connected in series with the positive output rail, is used to monitor the charging current. A&R are the first to admit that the meter supplied is not a high quality unit, but one that has been selected on the basis of ruggedness and low cost. In this application it is perfectly adequate, although readings should be taken as an approximate guide only.


As it stands, the circuit is capable of charging a typical battery at 6A, depending on the state of discharge of the battery, its age and condition, and the mains

voltage. Charging current is determined by the resistance of the circuit, which is the sum of the internal resistances of the charger and the battery, and by the difference between peak value of the rectified secondary voltage and the battery voltage. Hence a 10% change in mains supply voltage will produce a much greater than 10% change in charging current.

When the charger is connected to a flat battery, the charging current will initially be quite high due to the marked voltage difference between the two. The charging current automatically tapers off as the battery voltage approaches the charger voltage.
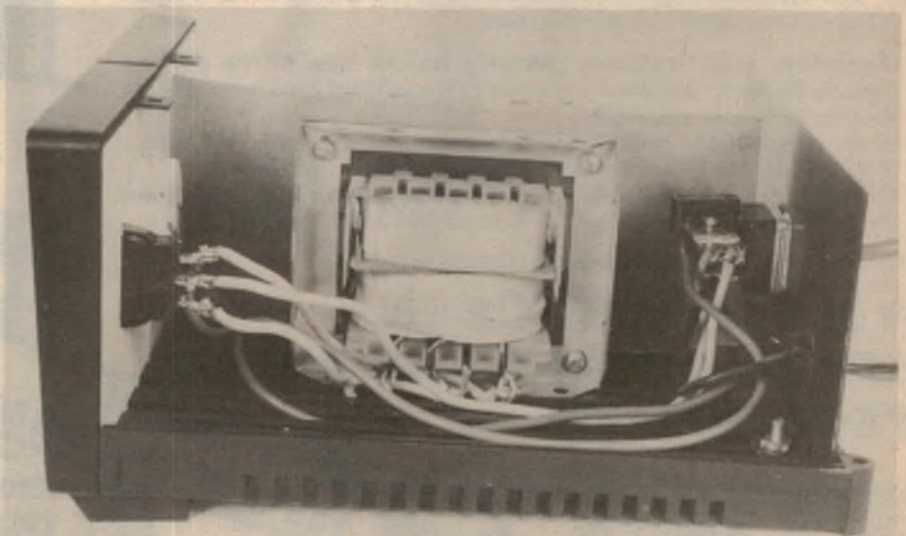
## CONSTRUCTION

A&R's kit for the Hi-Charge is supplied complete to the last nut and bolt. All the constructor needs is a soldering iron, solder and a few simple tools to assem-



View inside the unit showing the wiring on the secondary side of the transformer. The bridge rectifier is mounted in the centre of the rear panel (right).

# NOW the low cost answer to model control

## The DICK SMITH three channel digital proportional radio control



Imagine! A fully digital proportional 3 channel radio control system for under \$100.00! Compare elsewhere at \$150 and more . . . This outstanding system features three individually controlled channels, with 'trim' offset controls. Two channels are joystick controlled, the third a slider control (ideal for throttle, etc.)

- Complete with receiver, battery holder and three servos (spare battery holders and servos available so you aren't tied to just one model!)
- Ideal for models of all types: boats, planes, vehicles, etc.
- Top range transmitter and ultra-sensitive receiver
- Crystals are changeable for different operating frequencies
- Requires 10 pen light cells. Cat. S-3003: 22 cents each

GET INTO RADIO CONTROL MODELS NOW!

### A MASTERPIECE IN STATE-OF-THE-ART RADIO TECHNOLOGY

Complete with transmitter; receiver; battery holder; 3 servos

**DICK BREAKS \$100 BARRIER**

**only \$99**

Cat. X-1230

P&P \$4

**DIRECT IMPORT YOU REAP THE BENEFIT!**

**DICK SMITH Electronics**



**SEE OUR OTHER ADS FOR FULL ADDRESS DETAILS**

**New design features full overload protection**

# Build this 6-amp battery charger

Called the "Hi-Charge", this new battery charger features 6 or 12V operation, a metered output and full overload protection. It's easy to build and is capable of charging a typical battery at currents up to 6 amps.

by GREG SWAIN

Anyone who has been caught with a flat battery in a car knows only too well how frustrating this can be. It usually occurs at the most inconvenient time, often as a result of one's own carelessness. Ever left the parking lights on in your car?

Of course, batteries can go flat for other reasons. A combination of short runs, use of the headlights and accessories, and a battery that has seen better days may easily add up to a situation where the load is more than the battery can supply. And quite apart from these external conditions, the battery itself aggravates the situation by being less efficient at low temperatures.

For example, a half-charged battery has typically 60% starting power at 27°C, which could fall to a mere 30% at 0°C. So you're more likely to strike battery trouble in winter, when the battery is least efficient and when much greater use is made of lights and other accessories. Also, to some extent, the starter motor will draw more current in cold weather because the engine is harder to crank.

For all these reasons, well-prepared motorists like to keep a battery charger in the garage, either to get their car back on the road when the worst happens or, better still, to prevent trouble occurring when the likelihood can be foreseen. Unfortunately, most of us get caught "with our pants down" — a flat battery, no battery charger and a 2½ hour wait for a service van. The battery charger design presented here is your chance to correct this situation.

Boating enthusiasts and caravanners are even more likely to be interested in our new battery charger. Boats and caravans tend to be used at irregular intervals and batteries left idle in a partially charged state or "flat" tend to deteriorate. Ideally, these batteries should be kept in a fully charged condi-

tion, which means regular use of a battery charger. The "Hi-Charge" will certainly do this job.

## THE DESIGN


Actually, we have considered describing a battery charger for quite some time. Our specifications for a worthwhile design included a current rating of at least 5 amps, 6 or 12V operation, a metered output, and full overload protection. The problem was that by the time we had designed a suitable unit using over-the-counter components, its cost was more than an equivalent fully-built commercial model!

It's surprising just how quickly costs can

Australia", complete with circuit and wiring diagrams and full constructional details.

The result of our joint efforts is this fully-protected 6-amp battery charger which we have christened the "Hi-Charge". (A&R refer to it simply as the PS518 Charger Kit.) At around \$58 it is substantially cheaper than the Arlec Charger 8 which has similar specifications, but is sold fully assembled.

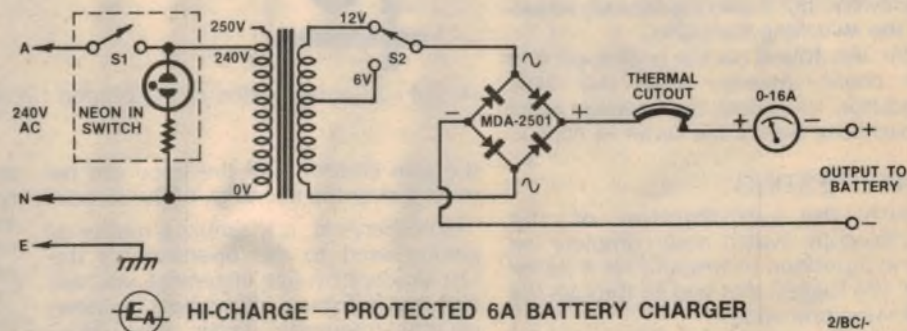The Hi-Charge conforms with all the specifications listed above and in addition, features a current rating of around 6 amps. This is where the Hi-Charge scores over the \$25-30 battery chargers that you may have seen in discount stores



The circuit consists of a transformer driving a bridge rectifier. A bi-metal thermal cutout provides protection in the event of overload.

escalate by the time one mounts a suitable transformer inside a case and then proceeds to add a high power bridge rectifier, a meter, switches, output cables, and other sundry items of hardware!

Our approach was to put the problem to A&R Electronics Pty Ltd who, among other things, manufacture a range of commercial battery chargers. Could they design a kit using off-the-shelf components that the hobbyist could assemble at favourable cost? In return, we would feature the article in "Electronics

and motor accessory shops. The latter only have a continuous current rating of 1-2A, hardly sufficient to get you moving quickly when you do get a flat battery.

By comparison, the Hi-Charge should be able to "pump" enough charge into the battery to get you going within a period of 15 or 20 minutes (as opposed to a wait of some hours). So the extra money for the heavier duty unit is well worthwhile.

Refer now to the circuit. It's really very simple and consists of a transformer driving a bridge rectifier. The transformer



has been specified in the parts list, we actually used a 3-pole 4-position unit. The latter type is more readily available, and does not appear to be any more expensive. Also, 2-pole 3-position miniature toggle switches are specified in the parts list, but only one pole of each switch is used in the circuit. Again, the 2-pole types are more readily available.

Insulated BNC sockets were fitted to the prototype since we wished to use probes with BNC plugs. Many constructors will no doubt prefer to do the same, although other types of sockets may be used if you so wish. Whatever type of input socket you do decide to use, it should be insulated from chassis to keep channel crosstalk to a minimum.

We used RCA sockets for the sync and output sockets.

With respect to ICs, it is worth noting that type 4069 is identical with type 74C04, while type 4016 may be replaced with type 4066. The CA3140 op-amps used were in the TO-5 style package, although standard 8-pin DIL packages may be used instead. Either type can be plugged into the 8-pin DIL socket.

We mentioned earlier that the RC filter on the output was open to some experimentation. We found that a 47pF capacitor fitted between the two resistors was sufficient, the capacitance of the output cable substituting for the second capacitor. Admittedly, this did reduce the bandwidth of the system somewhat, but it also significantly reduced the switching transients.

We also found on the prototype that we could dispense with the 47pF capacitor, provided the output cable capacitance was of the order of 80pF.

## FINAL TESTING

With the construction of the Oscilloscope Switch now complete we are in a position to test and set it up for use. We suggest that you go through the following procedure:

- Set SW1 and SW2 to "AC", SW3 and SW4 to ".01", and SW6 to "FAST";
- Set both "POSITION" potentiometers to mid-position;
- Connect the output cable to the input socket of the oscilloscope and the sync lead to the external sync input of the oscilloscope;
- Switch on the oscilloscope, set it to DC input, and adjust the trace to the centre of the screen.

Now switch on the Oscilloscope Switch. Two traces should now appear on the screen, and these should move vertically with adjustment of the two position controls. If the movement of the traces is restricted, the gain control of the oscilloscope is set too low. Advance

the gain control until the trace can be moved over the full range of the screen.

From here on, it is simply a matter of getting used to the operation of the Oscilloscope Switch. In general, you will find that fast chop will be best for viewing low frequency signals, while slow chop will be best for high frequencies.


The way in which the input switches are used will soon become obvious. Selection of "AC" or "DC" depends on whether the DC component of the signal is to be taken into consideration, while the "GND" position grounds the input circuit without grounding the input signal. The latter facility is useful for setting the trace so that DC signal levels can be measured.

We settled for an input impedance of 100k $\Omega$  rather than 1M $\Omega$ . A 1M $\Omega$  attenuator would require some elaborate frequency compensation, whereas 100k $\Omega$  could be used without any compensation and with only a relatively


small effect on the losses of high frequency components. However, there are some losses and to keep these to a minimum we suggest that wherever possible the attenuator should be set to ".01" when viewing frequencies above about 500kHz.

Finally, the Oscilloscope Switch provides the bonus of a calibrated attenuator for a CRO which doesn't already have this feature. Assuming that you have a CRO with a sensitivity of 10mV/div or better, the procedure is to set the attenuator switch on the Oscilloscope Switch to "1" and feed in a suitable AC reference voltage say 5V p-p. (An unabashed plug: the EA Voltage Reference, described in June 1976 and January 1977, is ideal for this purpose.)

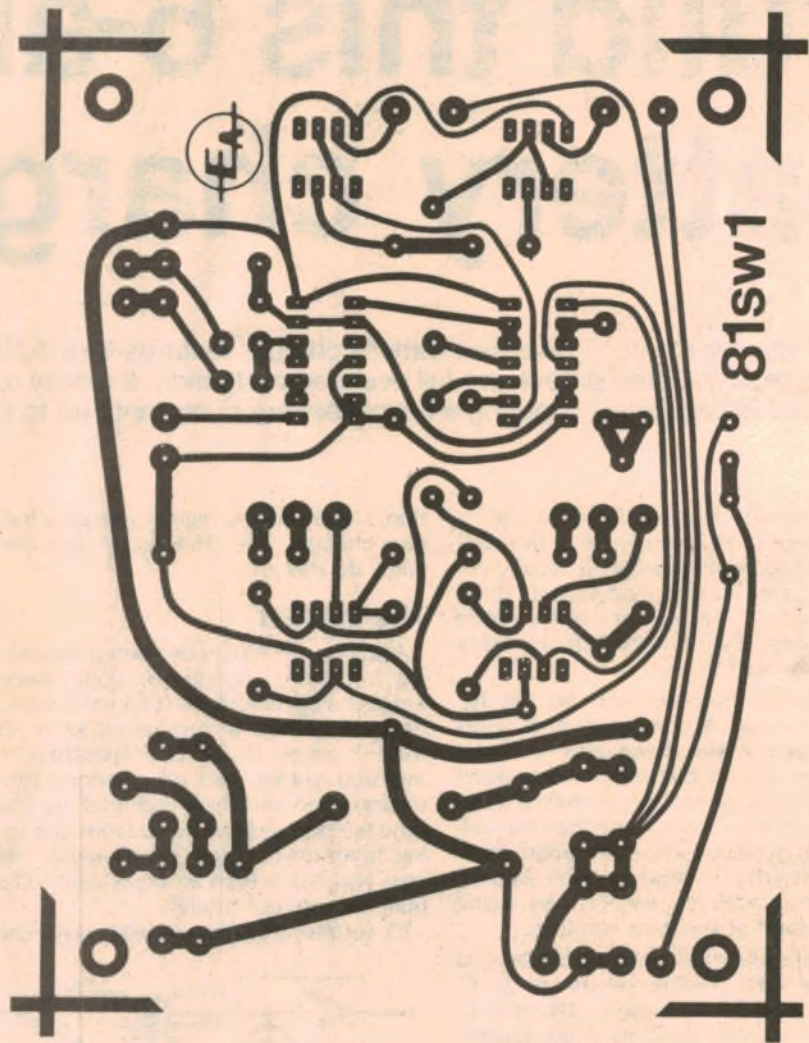Now all you have to do is adjust the sensitivity of your CRO to give a reading of 1V/div. The result — a calibrated attenuator capable of switching from 10mV/div sensitivity down to 10V/div sensitivity!



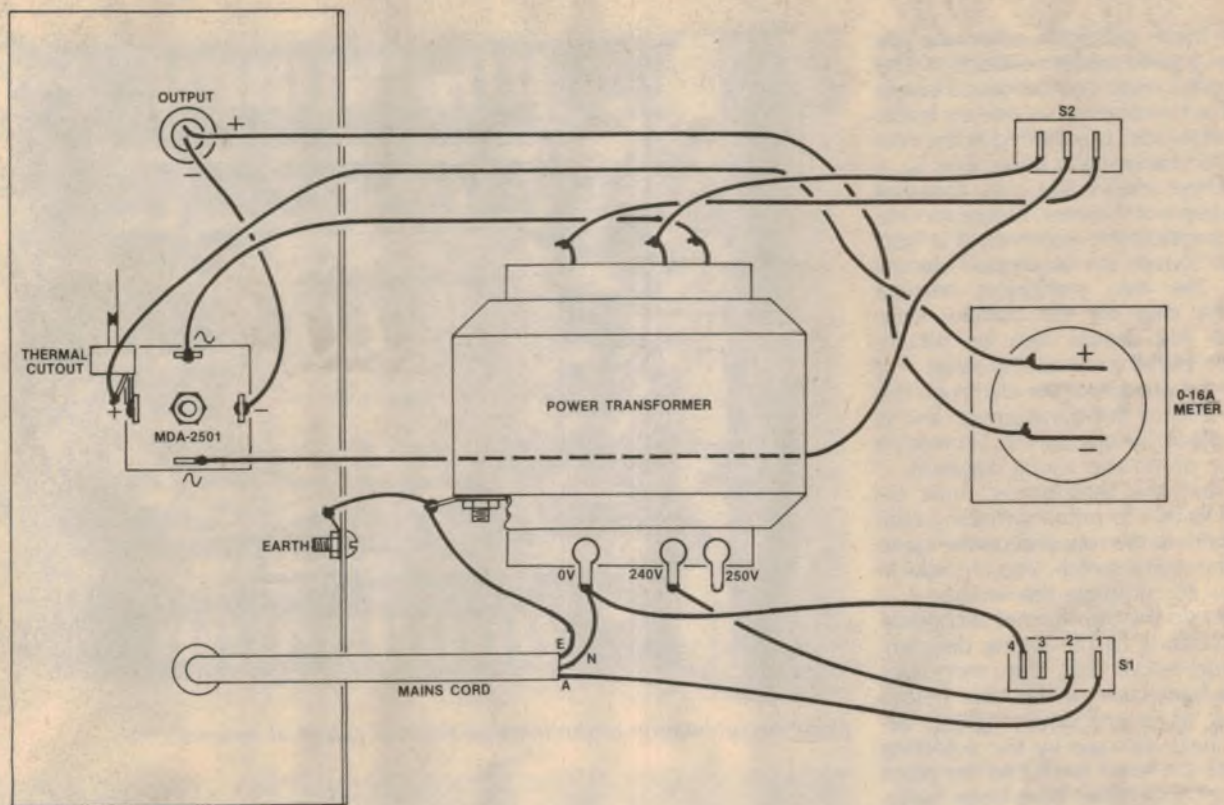Actual size reproduction of the printed circuit board pattern.



Follow this diagram carefully when wiring up the battery charger. Note that the transformer is NOT centre-tapped and don't forget to fit the presspahn barriers.

ble the unit. A handsome silk-screened front panel with dark blue printing on a light blue background provides a really professional finish.

Commence construction by fitting the two switches and the meter to the front panel. You will need to do some work on the back of the panel with a small file in order to get the switches and the meter to fit properly, as they were originally designed to suit a somewhat thinner panel. Make sure that you mount the mains switch — the one with the neon indicator — so that the number one terminal is at the top.

The front panel is supplied with holes of the correct size to suit the meter and switches. Similarly, the rear panel is supplied with holes to accept the "Gripit" grommets for the power and output cords, but not with the rectifier and earth screw mounting holes. You will have to drill these yourself.

The next step is to drill a  $\frac{1}{32}$ in hole exactly in the centre of the rear panel for the bridge rectifier, together with a  $\frac{1}{8}$ in hole in the foot of the panel for the earth screw. The latter should be carefully positioned so that, with the rear panel bolted in position, the head of the screw fits naturally into one of the channels running along the length of the base. A solder lug and a shakeproof washer complete the earth screw assembly.

Smear a thin layer of heatsink compound on the underside of the bridge rectifier and bolt it to the rear panel using a  $\frac{1}{32} \times \frac{3}{4}$ in machine screw and nut. (Note: A&R specifies screw sizes in Imperial units.) Use a serrated shakeproof washer under the nut on the bridge rectifier side. The rectifier should be oriented so that its positive terminal is at the top.

This done, the rear panel can be bolted into position ready to commence wiring. All leads are supplied precut to the correct length, stripped and tinned, so it is important to use the right lead in the right place. Do not shorten any of the leads supplied while wiring the kit.

Begin by connecting the 250mm long yellow wire between the centre terminal of the voltage selector switch and one of the AC input terminals on the bridge rectifier, as shown in the wiring diagram. Arrange the wire so that it runs naturally down one of the channels in the case. The other yellow wires are soldered to the two remaining lugs on the voltage selector switch ( $2 \times 130$ mm) and to the remaining AC input terminal on the bridge rectifier (170mm), ready for connection to the power transformer secondaries.

Next, pass the two output leads through the appropriate hole in the rear

panel and solder the red lead to one of the meter terminals (see wiring diagram) and the black lead to the negative terminal of the bridge rectifier. Both output leads are then clamped using the smaller of the two Gripit grommets.

Use a pair of bull-nosed pliers to install the grommet, and leave plenty of slack in the leads inside the case so that they are not subject to strain.

The thermal cutout is soldered to the positive terminal of the bridge rectifier with its contacts facing upwards. Orient the device as shown in the photograph and avoid handling the bi-metal strip, as this can alter the thermal cutout point significantly. The cutout point can be "tweaked" later on, if need be, by varying the exact point of connection to the rectifier terminal.

(For example, to increase the cutout point, solder the thermal cutout closer to the end of the rectifier terminal; to lower the cutout point, move the device closer to the rectifier body. The more heat the thermal cutout receives from the rectifier, the lower the cutout point will be.)

With the thermal cutout mounted in position, connect the 300mm red wire between its remaining terminal and the remaining terminal on the meter. Don't forget to scrape the enamel off the ends of the heavy gauge copper leads that

form the meter terminals, otherwise you won't get a good solder connection. The same applies when you get round to wiring up the transformer secondary leads.

The transformer is mounted in the centre of the chassis base using four  $\frac{5}{32} \times \frac{1}{2}$ in machine screws and nuts, together with shakeproof washers. Before mounting the transformer, however, it is necessary to loosen the lamination clamps and fit the two presspahn barriers under the clap on the primary side. An earth lug should also be attached to the transformer at this stage – it goes on the outside of the clamp on the primary side of the transformer, and is held in place by one of the lamination bolts (see photo and wiring diagram).

Note that the transformer must be oriented so that its primary winding connections are at the top, and on the same side of the mains switch. You are now in a position to complete the wiring.


Connect up the transformer secondary leads according to the wiring diagram. We recommend that the secondary leads be bent clear of the case before soldering, as a precaution against accidental heat damage by the soldering iron. Tuck the leads back into the place when the connections have been made.

Important: the transformer is NOT centre-tapped. Instead, the tap is off-centre to allow for the effect of the two diode drops in the rectifier bridge. Make sure that you wire your unit up exactly according to our wiring diagram, otherwise the charging voltage on the 6V range will be too low.


Utilux connectors are used to make all connections to the mains switch, and these are supplied already fitted to their appropriate leads. A&R really have made the job easy! The sequence of wiring is as follows: connect the white lead between the transformer neutral (0V) connection and the No. 4 terminal on switch S1; connect the red lead between the transformer 240V connection (250V in WA) and the No. 2 terminal on switch S1; connect the short length of tinned copper wire supplied between the rear panel and transformer earth lugs.

The mains cord is the last item to be wired into circuit. Pass the leads through the hole in the rear panel, and connect the active lead (brown, with the Utilux connector) to the No. 1 terminal on the mains switch. The neutral (blue) and earth (green and yellow) leads are then terminated according to the wiring diagram, ie, to the neutral connection on the transformer and to the transformer earth lug respectively.

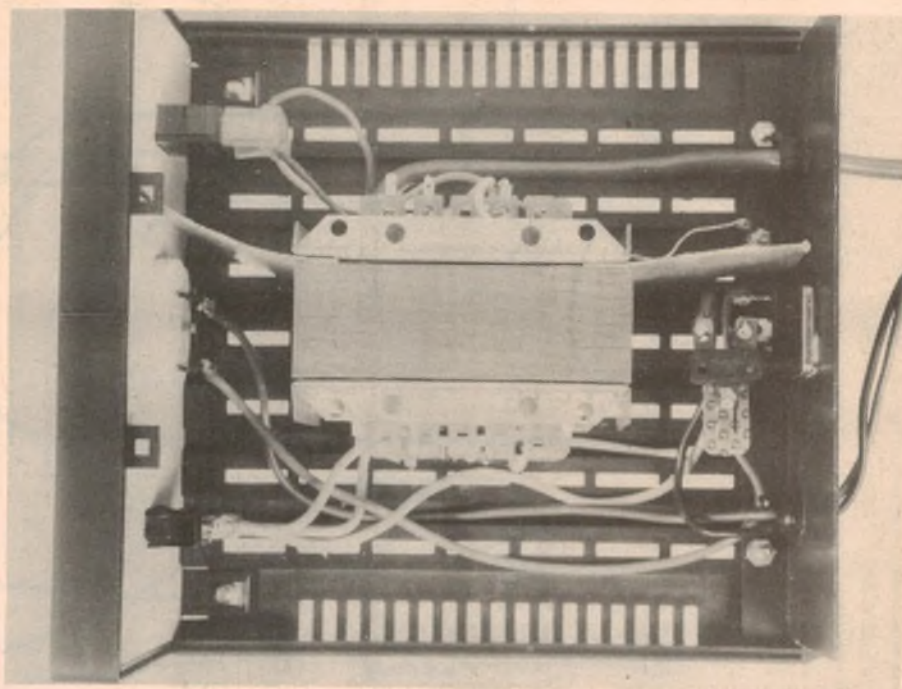Use the large grommet to securely clamp the mains cord to the rear panel. Again, use a pair of bull-nosed pliers to install the grommet and leave plenty of slack in the leads.



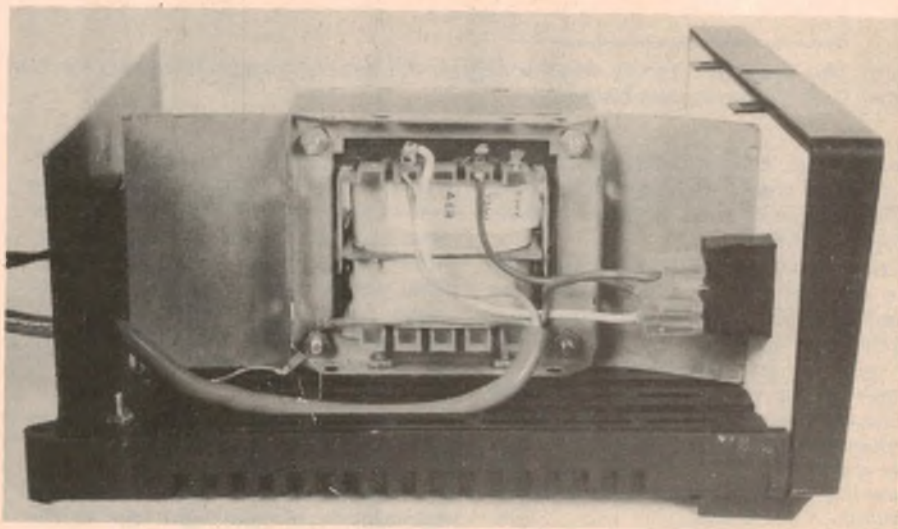Note the orientation of the bi-metal thermal cutout at centre-right.



This view shows the mains wiring to switch S1 and the transformer primary.

Before going further, carefully check your wiring against the wiring diagram. Assuming that all is well, fasten down the lid of the case using the two self-tapping screws provided, slip the front panel bezel into position, and tighten the two securing screws located under the unit behind the front panel.

Finally, a few words of warning. Never cause a spark or use a naked flame near a lead-acid battery – you could cause an explosion if you do. Lead-acid batteries generate hydrogen gas as a by-product and, as readers will know, hydrogen is highly inflammable.

When using the charger, always make

the connections to the battery first, before plugging the charger into the mains and operating the mains switch. We also recommend that the vent caps on the battery be left in place, and that the battery be disconnected from the car electrics. Take care to ensure that you connect the battery the right way round – the red (positive) lead from the charger goes to the positive terminal on the battery, the black lead to the negative terminal.

Stocks of the A&R Hi-Charge battery charger kit should be available from most components suppliers by the time you read this article.

# AT LAST! A SENSIBLE ALTERNATIVE TO TANDY AND DICK SMITH...

# ALTRONICS


THE ONE STOP ELECTRONICS SHOP AND AUSTRALIA WIDE MAIL ORDER SPECIALISTS!

## All about ALTRONICS Same Day Red Hot Service

- MAIL DELIVERIES PERTH TO EAST COAST ARE FAST, FAST, FAST - TYPICAL AS FAST AS FROM SAY BONDI TO NORTH RYDE OR RICHMOND TO FOOTSCRAY.
- WE DESPATCH SAME DAY OF RECEIPT OF ORDER - SHORTS ARE ADVISED BY AIRCARD SAME DAY WITH ETA IN STORE.
- ADDITIONAL MAIL COSTS THROUGH SPLIT DELIVERIES OR BACKORDERS ARE PAID BY US.

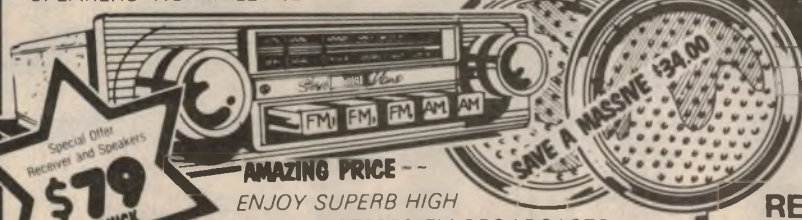**TRY US NOW!**

RECEIVER NORMALLY \$89 **HUGE SAVINGS**  
SPEAKERS NORMALLY \$24



Special Offer Receiver and Speakers  
**\$79**  
BE QUICK

**AMAZING PRICE --**  
ENJOY SUPERB HIGH FIDELITY STEREO FM BROADCASTS  
**NOW! HUGE 7 WATTS RMS POWER EACH CHANNEL**  
HIGHLY SENSITIVE IC CIRCUITRY ● QUALITY ALTRONICS IMPORT

**STOP PRESS!**  
MONO AM, FM Version (same specs.) only  
Great replace - **\$49.95**  
ment for your old worn out radio!

**1¢ Each!!**  
Look at This...  
**RESISTORS CRAZY**  
All values—10ohm-10Meg  
PRIME SPEC CARBON FILM  
5 WATT PACK'S OF 100 EACH VALUE \$1.00 PK  
25 WATT PACK'S OF 200 EACH VALUE \$2.00 PK



**\$12.95** complete units.  
**16 Drawer Parts Cabinets**  
● Stackable  
● Clear view drawers  
● Size 300 (w) x 180 (h) x 144 (d) mm

**GET THE 'LED' OUT FELLAS!**  
Look at this... red leds from 7¢ each  
You'll SAVE dollars here!!

3mm Red	1.9	10-99	100 up
5mm Red	16'	10'	7'
5mm Green	28'	20'	15'
5mm Yellow	55'	25'	25'
5mm Orange	34'	30'	22'

From 7¢ each  
DON'T WAIT! They'll walk out at these prices!  
Retangular Too!  
Red & Green 30¢ each  
10 up 20¢ each

**250mm DIAM. SPEAKER GRILL**  
QUALITY AUSTRALIAN MADE.  
10up \$1.75 EACH  
**Twin cone spkr.**  
10up \$7.00 Save 50%  
**GREAT FOR EXTENSION SPEAKERS PA'S BACKGROUND MUSIC!**  
Hear them for yourself and you'll be sold.  
Buy several while they last! Great frequency range 30HZ-15 KHZ

**PANEL METERS**  
MU45 Panel Meters  
Normally \$12.50 Now \$10.00  
Smart Appearance Tool!  
MU4 Series only \$7.50  
VU Only \$7.95

**MU-45 MU-65**  
0-1MA M1 0-1MA M6  
0-5A M2 0-100UA M7  
0-30V M3  
0-500A M4  
VU M5  
Overall - 58 (w) x 52 (h) mm  
Hole Req - 45 mm  
Overall - 100 (w) x 82 (h) mm  
Hole Req - 63 mm

**NEW!**  
**ONLY \$39.95 EA.**  
5 up \$35.00 ea

**JUMBO'S, DC'10s, CESSNAS**  
LISTEN TO THEM ALL  
Direct Import  
This Incredible AM/VHF RADIO POWERFUL SOLID STATE RECEIVER covers aircraft and 2 ways bands, together with your favourite AM stations

**MINI PCB RELAY**  
● 12 V DC operation  
● 225 OHM coil resistance  
● Signal change over 15 P.D. 1 contact  
● Handle up to massive 2 AMPS @ 24 V DC or 100 V AC  
● Mounts directly on to PCB  
1's 10's 25 up  
\$1.50 \$1.20 \$1.00

**TRANSFORMERS - THE BARGAIN OF 1981 and SEC APPROVED.**  
2851 240/12.6 CT 150MA \$2.95  
2155 240/6.3-15V Multitap 1 amp \$3.95  
6672 240/15-30V Multitap 1 amp \$5.95  
**WHY RISK USING UNAPPROVED TRANSFORMERS AND PAY THROUGH THE NOSE TO BOOT?**

**BUILD A STACK - SAVE A STACK.**  
With 48.3 cm (19") rack mounting boxes, glorious anodised black finish, side vented.  
**TEACHERS MAY DO IT IN CLASS BUT ELECTRONICS BUFFS DO IT IN A JIFFY!!**

**DIODES AT SILLY PRICES STREWTH!**

IN 914	1.9	10 up
IN 4002	4c	3c
IN 4004	6c	5c
IN 4007	7c	6c
IN 5404	14c	13c
IN 5408	30x	25c
	35c	30c

**INCREDIBLE OFFER**

**This is a Screamer!**  
**MAD PRICE!**  
Soldering iron stand  
Heavy, durable, comes with sponge...

**PRICE BREAKTHROUGH ON DIRECT IMPORT SWITCHES**

MINIATURE TOGGLE	1.9	10 up	25 up
S1010 S P D T 125V/3A	1.45	1.25	1.15
S1020 D P D T 125V/3A	1.65	1.50	1.40
STANDARD TOGGLE			
S1040 S P S T 125V/3A	.95	.75	.65
S1050 D P D T 125V/3A	1.25	1.00	.90
PUSH BUTTON			
S1060 Push to Make Mini	.40	.30	.25
S1070 Push to Break Mini	.45	.35	.25
S1080 Push to make 250V/3a	1.40	1.20	1.00
S1090 Push on Push off 250V/3A	1.60	1.40	1.25

Now the old zippy box is obsolete... Altronics leads the way with this radical New PCB SNAP IN JIFFY BOX.  
Can be used as vertical slide-in too.  
4 handy sizes. Will take 250V PC boards perfectly!  
(as featured in E.A. DEC issue)  
The savings in screws, spacers, mounts - Labour will pay for the box.  
**FRONS!**  
HO101-UB1 1.75  
HO102-UB2 2.75  
HO103-UB3 1.35  
HO105-UB5 1.00  
**DE-SOLDERING WICK**  
Easy to use solder wick on easy to hold spool!  
**Save 30% ONLY \$1.50**

**THIS IS WHAT THEY SAID ABOUT US**  
GEOFF WOOD RADIO DESPATCH SYDNEY, N S W  
"I can get stock from Altronics in Perth faster than from Sydney suburbs"  
JOCK ELLIS, ELLISTRONICS, MELBOURNE, VICTORIA  
"Fantastic delivery - Order after 1 close Friday and the goods arrive Monday everytime"

**VEROTYPE STRIP BOARD**  
\$3.50 10 up \$3.00 25 up  
Quality silver plated \$4.50 ea  
copper strip board.  
Dimensions: 95 (w) x 304 (l) x 2.54 Pitch (1 inch)

**Mail Order P AND P CHARGES**

\$1 - \$10	\$1.00
\$11 - \$25	\$2.00
\$25 - \$99	\$3.00
\$100 up	\$4.00


**WANTED! DYNAMIC DEALERS for S.A. - Q'LD - TAS AND MAJOR COUNTRY AREAS IN ALL STATES**  
PHONE JACK O'DONNELL NOW 381 7233

**RUSH YOUR MAIL ORDER TO US NOW!**

**ALTRONICS**  
105 Stirling Street, Perth.W.A. 6000  
PHONE: 09 328 1599 TELEX: 94186 Altron  
JUST POSSIBLY AUSTRALIA'S FASTEST MAIL ORDER SERVICE

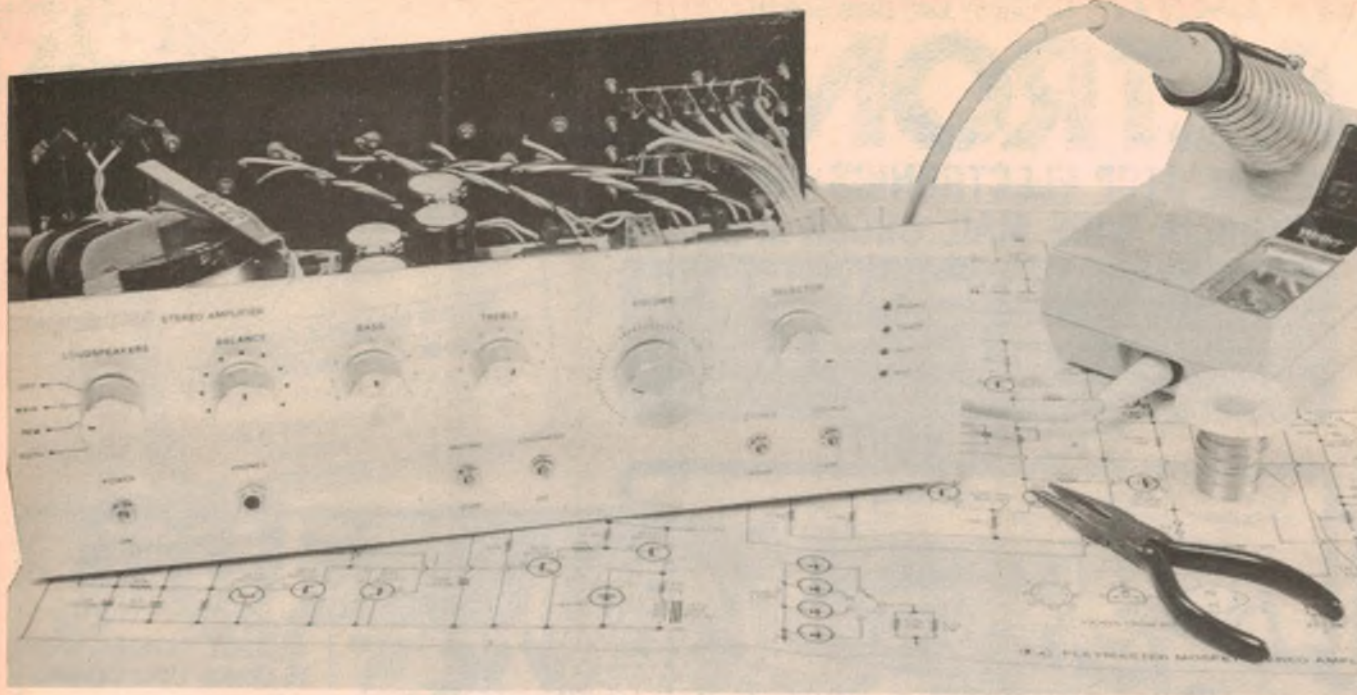**SPECIAL OFFER! JAN/FEB... ALL MAIL ORDERS P&P Only \$1.00**

**Established Major Resellers**  
VIC.  
ELLISTRONICS (03) 602 3282  
N.S.W.  
RADIO DESPATCH (02) 211 0816  
PREPAK (02) 569 9797



# Playmaster Mosfet Stereo Amplifier

In this third and final article on the Playmaster Mosfet Stereo amplifier, we complete the details of construction, detail a number of options and give a trouble-shooting procedure.

By LEO SIMPSON

Several points concerning the PC board remain to be discussed before we can proceed to the chassis assembly.

Some holes on the PC board layout provided last month appear to be unused. However, only two of these, behind the relay are actually unused. We can account for all the others. Those adjacent to terminal 41 on the PCB should be used for loudspeaker (earth) returns. And those underneath the reservoir capacitors are provided for the additional securing lead on each 2500 $\mu$ F capacitor.

Similarly, alternative mounting holes are provided under the trimpots for standard upright types. We used Bourns ten-turn trimpots because they are less critical to adjust and less likely to be knocked out of adjustment by clumsy handling of the PC board. Regardless of which type of trimpot is used, you will have to use a small screwdriver with an insulated shaft to make the adjustments.

Two tasks remain in the assembly of

the PC board. First, install a length of figure-8 shielded cable between the balance control connections and the power amplifier input connections, pins 1, 2, 3 and 34, 35, 36 and 37, respectively. This cable is shown on the chassis wiring diagram and should be routed as shown in the chassis photographs.

Finally, solder a 100 $\Omega$ /5W resistor across each pair of fuseholders on the PC board (the fuses should not be installed). These resistors perform two functions during setting up of the amplifier. First, they provide a convenient means of monitoring the quiescent current of the amplifier output stages. Second, they provide safe current limiting in the event of a circuit fault in the amplifier.

With the circuit board complete, go over it very carefully to check that all components are correctly installed as far as their values and polarity are concerned. Do the same on the copper side of the board, checking that each and every solder joint is good. That done, put the


board aside and start work on the chassis.

A first step in the chassis assembly is to check, as far as possible, that all holes are correctly placed and of correct size. For example, you can check that all controls and switches actually fit in their respective holes and that the transformer mounting holes are correct. Check too, that the dress front panel holes line up with those on the chassis. The idea behind these checks at this point is to drill and debur any required holes now rather than later when metal swarf may find its way into potentiometers or other components.

Start by mounting the smaller hardware first, such as the RCA phono input panels and the spring-loaded loudspeaker terminals. Note that a number of solder lugs are attached at the same time as these panels. The chassis wiring diagram shows where these are located.

Swap one pair of red and black terminal covers on each spring loaded terminal panel so that the red terminals are in the centre of each panel. The idea behind this is to minimise the possibility of damaging shorts between the output leads.

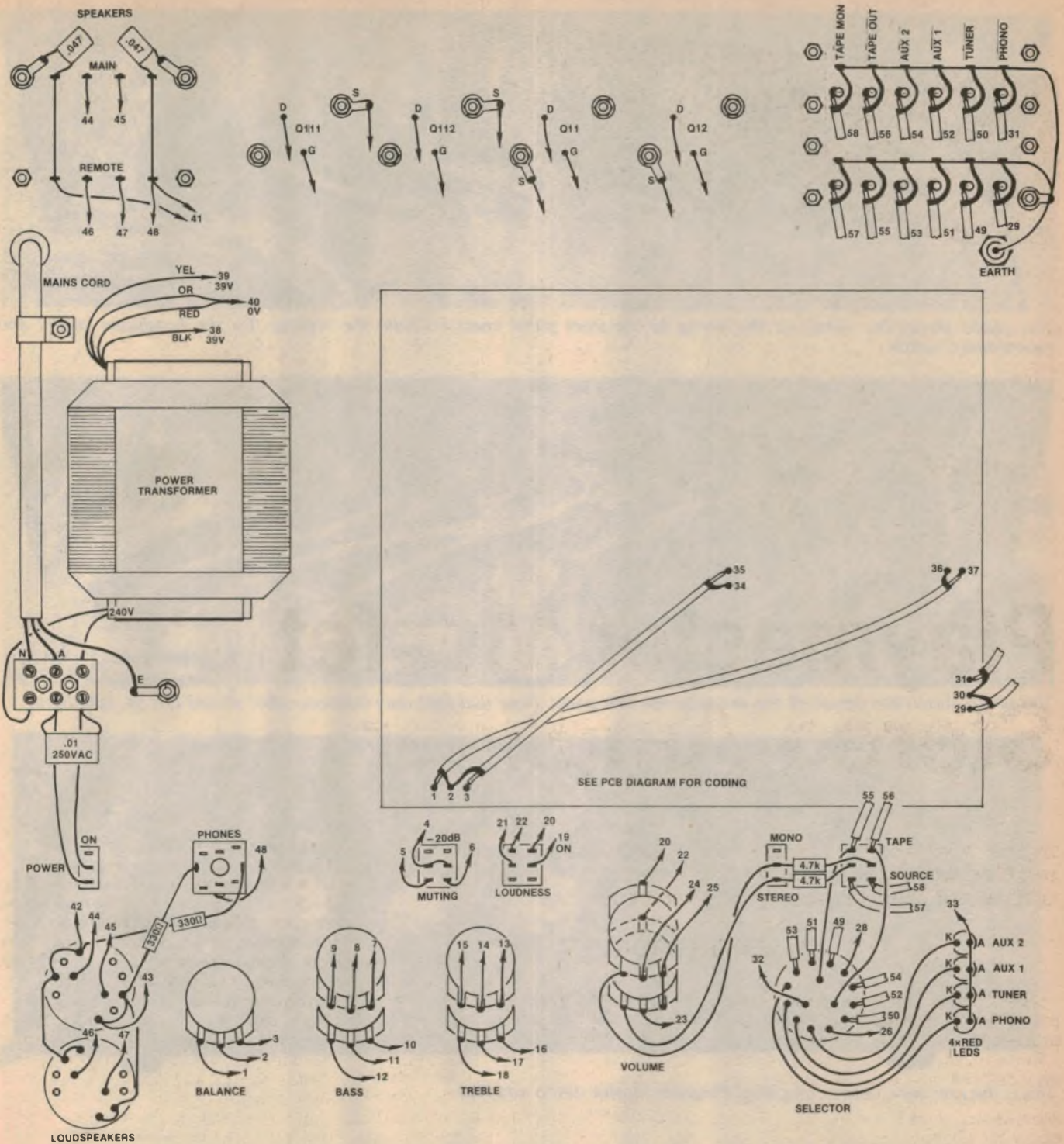A binding post terminal should be installed just below the phono inputs to



Use this diagram, in conjunction with the circuit and PCB component diagram, to complete the amplifier wiring.

provide an earthing point for those turntables which have a separate earth lead for the tone arm.

Do not mount the dress front panel until the amplifier has been completely checked out and is working satisfactorily. By leaving the dress panel until all other work has been completed you avoid the possibility of scratches on the panel.

Cut the shafts of the potentiometers and rotary switches to a length about 11 or 12mm, before they are installed in the chassis. Note that each of these controls should be spaced away from the inside


of the chassis by the thickness of one nut so that, when the dress panel is finally installed, the potentiometer and switch bushes do not protrude unduly.

The loudspeaker switch is a 4-pole, 4-position type. At present, two types are available: One is a Lorlin type RA, distributed by C&K Electronics (Aust) Pty Ltd and available from most parts suppliers; the other is from Dick Smith Electronics. The switches may employ make-before-break or break-before-make contacts — it is not critical. Neither switch is intended to switch heavy currents


although they can both carry the relatively high currents involved.

The headphone socket can be a non-switching type instead of the switching type which we used (because we had it on hand). The 330Ω resistors to the headphone socket are wired directly between the relevant terminals on the speaker switch and the socket itself. These resistors should be ½W or 1W types, to avoid the possibility of overheating when listening at high levels to the headphones.


The headphone socket should be in-

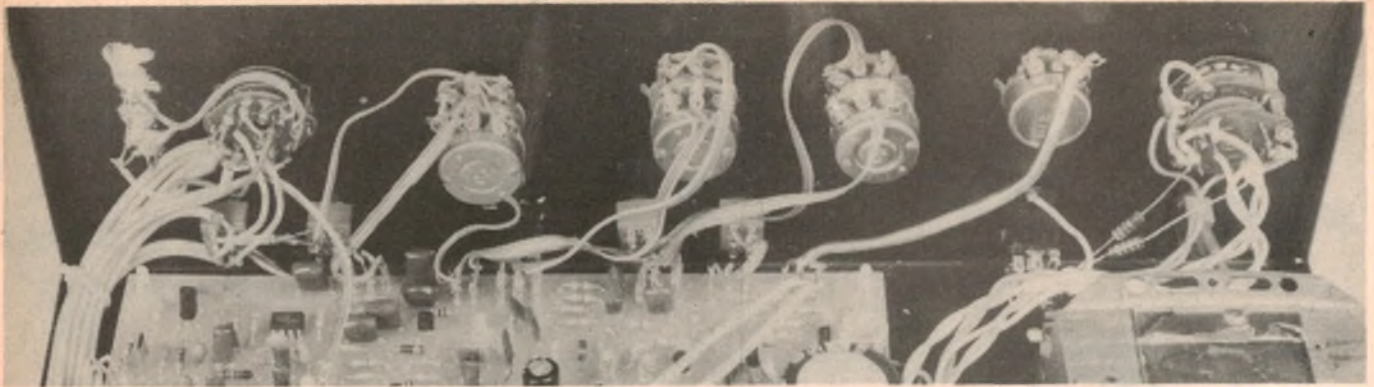

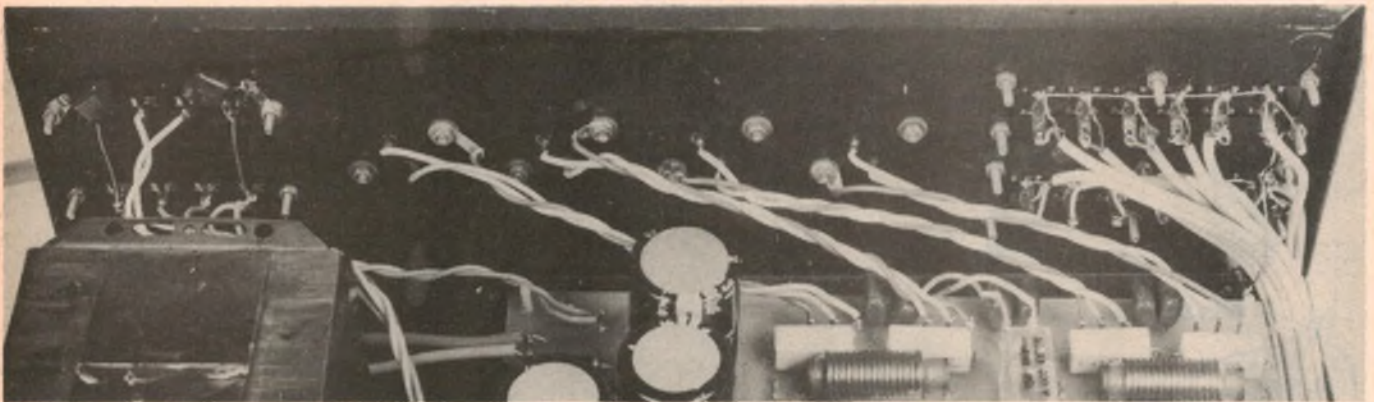*This photo shows the details of the wiring to the front panel controls. Note the resistors for the headphonestyle socket and mono/stereo switch.*



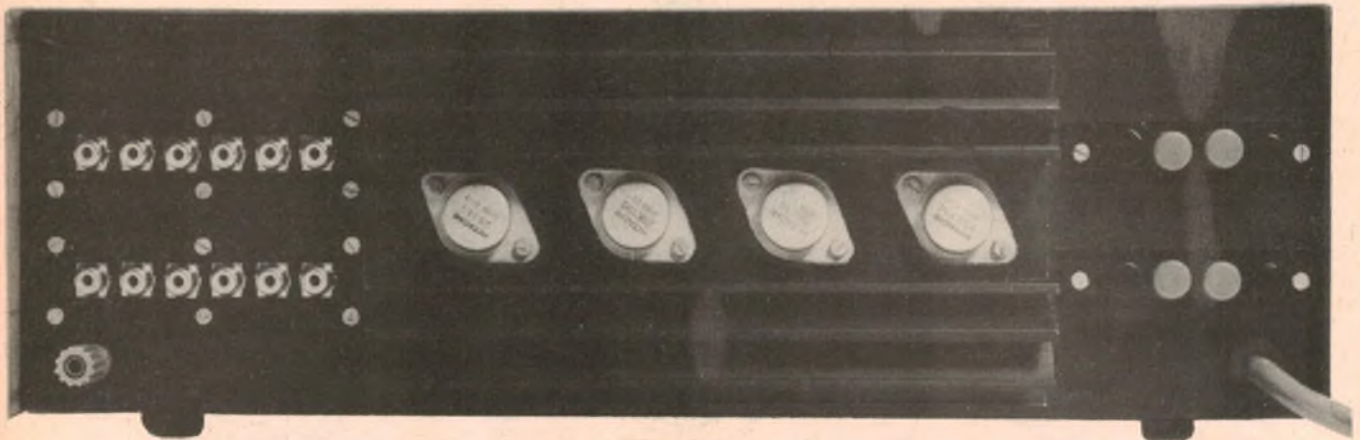*This photo shows the details of the wiring to the rear panel. Note that light-duty rainbow cable should not be used here.*



*This is the rear view of the completed Playaster Mosfet stereo amplifier.*

insulated from chassis and a separate earth return run back to the loudspeaker terminal panel (shown as connection 48 on the chassis wiring diagram). Insulate the headphonestyle socket using two fibre washers and insulating tape. Alternatively, you can make your own washers out of suitable plastic sheet. The insulation tape is wound around the bush of the socket where it passes through the chassis and, ultimately, through the front panel.

When the headphonestyle socket is mounted and connected, check that it is, in fact, insulated from chassis by using a multimeter switched to one of the high resistance ranges.

Similarly, the  $4.7\text{K}\Omega$  resistors between the Tape Monitor and Stereo-Mono switches are wired directly between the switches themselves. In this case, the resistors should be sleeved with spaghetti or Nylax tubing to prevent the likelihood of shorts.

The output transistor heatsink is secured to the chassis via the various mounting screws of the TO-3 output transistor packages. Once again, you should carefully examine the heatsink to ensure that all holes line up exactly with the corresponding holes in the chassis. Also make sure that the transistor mounting surfaces are flush and free of any metal swarf or burrs.

The Mosfet output transistors are mounted in the same way as conventional bipolar transistors having TO-3 cases. Use mica washers and insulating bushes to isolate the transistors from heatsink and chassis, as depicted in the diagram on page 61.


Note that the Mosfet output transistors do not have the connections you might expect if you are familiar with bipolar power transistors. The Source is in fact connected to the transistor case rather than the Drain, as you might expect. Take great care not to transpose the Gate and Drain connections otherwise you are sure to end up with damaged transistors.

you can have all the features of expensive commercial amps at a fraction of their price.

**YES!**  
Contains the genuine components specified by Electronics Australia. Beware of other kits with non-standard parts: especially the transformer!

... when you build the  
**Playmaster Mosfet Amp**

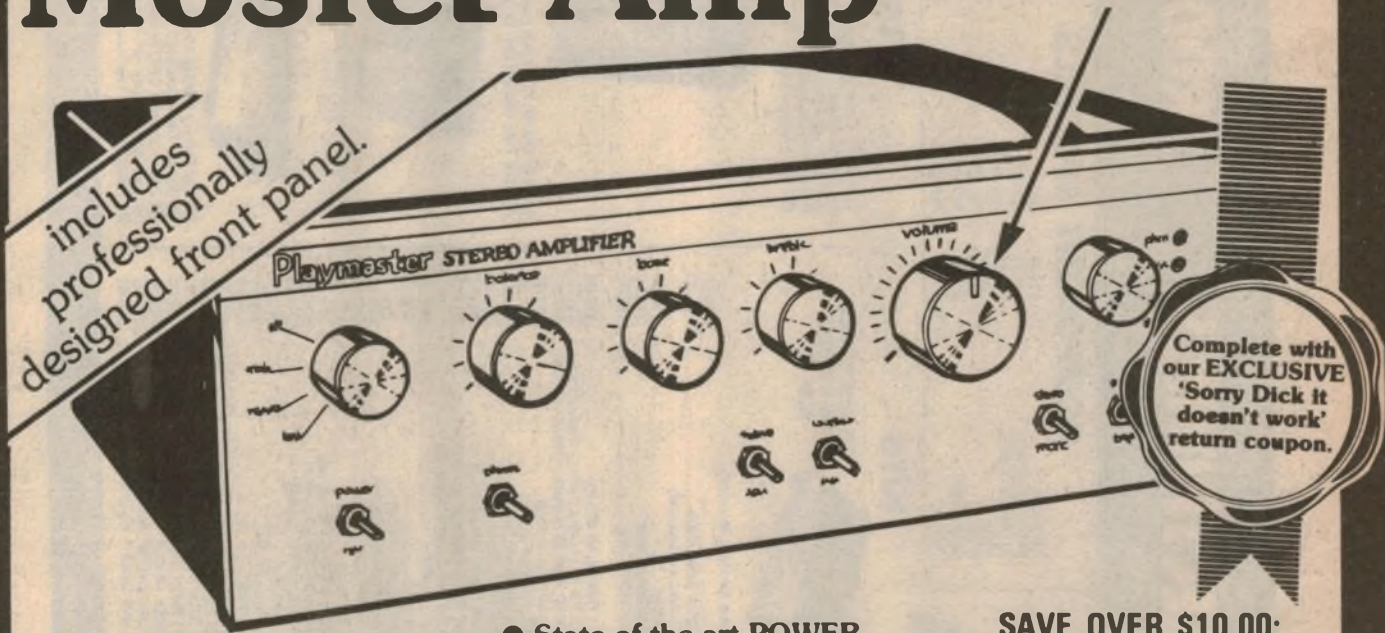**MAGNIFICENT!**  
EVEN A NEW RANGE OF MAGNIFICENT PRO-QUALITY KNOBS - JUST FOR THIS AMP!



This is it: the new Playmaster Power Mosfet Stereo Amplifier, as described in the current issue of Electronics Australia. It's the latest in the incredibly successful series of Playmaster amplifiers (over 10,000 Twin 25's & Forty/Forty's built!) but this one really has everything:

- State-of-the-art POWER MOSFETS!
- Low-noise FET input preamps!
- Over 50 watts per channel!
- Speaker switching plus loudness & muting controls!
- And a brand new professional styling!
- Complete with our famous step-by-step instruction manual!

**SAVE OVER \$10.00:**  
This kit **INCLUDES** the optional loudspeaker protector circuitry: **AT NO EXTRA CHARGE**

**\$159<sup>00</sup>**

Cat. K-3610

**DICK SMITH**  
Electronics



**SEE OUR OTHER ADS FOR FULL ADDRESS DETAILS**



# ROD IRVING ELECTRONICS

425 HIGH-STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131

# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131

## NEW PRODUCTS

### WELLER TEMPERATURE CONTROLLED STATION WTCPN Series

Product Description: A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The soldering pencil is made of a special alloy, providing a long maximum life temperature is employed. Energy producing temperature sensitive components are used to provide accurate temperature and automatic temperature control. The soldering pencil features a stainless steel heater construction, a non-scorching silicon rubber cord and a 3mm diameter to 6mm diameter with a choice of 10 temperatures of 600 degrees F to 735 degrees C.

A redesigned transformer case features an impact resistant nylon for durability and protection against accidental damage. A quick connect/disconnect plug for the soldering pencil allows easy storage. It has a 3-wire safety line, plus an improved off-on switch with a 3-wire power cord. The soldering iron is normally provided with a PTA-2-11, 6mm diameter, 700 degree F/370 degrees C tip.

**POWER UNIT**  
 Power Input 240 volts 50Hz 60 Watts In. 0 Transformer Output voltage—24 volts (full load) Power Unit size—115mm x 197.2mm x 86mm, 2 metres, 3 wire power cord.  
 Weight—50 grams (NW cord) a frequency time (from 100 degree F stop) W/PAT 19 sec.  
 Please note our size price distributors for all Weller quality products.

### RISTON PRE-COATED PRINTED CIRCUIT BOARD

Available ex stock in handy sizes. Write for information and prices. Single and double sided available. Tax exempt prices available through Ritronics Wholesale (03) 489-7099.

### CLARE ASCII ENCODED KEYBOARDS

SPECIAL \$165.00 inc. tax  
 Model C70/MGP microprocessor controlled.

AT LAST A FULLY BUILT POWERFUL COMPUTER FOR THE SERIOUS PROGRAMMER

Australia's first under \$300 COMPUTER... **\$295**

THE BEST VALUE

## COMPONENT SPECIALS

4116RAMS	\$ 5.00	10 for \$ 2.90
2114RAMS (450NS)	\$ 3.30	10 for \$ 5.50
2114RAMS (300NS)	\$ 3.90	10 for \$ 5.50
1000UP	\$ 2.95 ea	10 for \$11.00
2732	\$22.00	10 for \$ 1.40
2708EPROMS	\$ 6.90	100 for \$11.00
741S	10 for \$ 2.50	

## KITS



ETI SERIES 4000 60W STEREO AMP KIT

Complete Kit Rack Mounting Case	\$189.00
Woodgrain Sided Case	\$189.00
Parts Available Separately	
Front Panel	\$10.90
Rack Mounting Case	\$55.00
Wooden Sided Case	\$49.00

ETI 471 Preamp kit of parts	\$10.90
ETI 472 PS kit of parts (without transformer)	\$24.00
ETI 470 60 Watt kit of parts (without heatsink)	\$23.00
ETI 480 50W kit of parts	\$17.50
ETI 480 100W kit of parts	\$22.50
ETI 084 Car Alarm kit	\$11.50
EA TV CRO Adaptor kit	\$29.00
EA 300W Power Amp Module	\$63.50
EA 466 300W Power Amp Module	\$63.50
EA Digital Capacitance Meter Kit (EA March 1980)	\$59.99
Autoclimb kit	\$29.75
MK3 Drill Speed Control	\$13.50
Capacitor Discharge Ignition	\$32.50
Musicolor MK3 Kit	\$69.50
Disco Strobo kit	\$34.50
Leads and Ladders (EA August)	\$15.75
ETI 149 Two-Tone Generator	\$34.90
ETI 563 Nicad Fast Charger	\$54.90
Dream 6802 kit	\$109.00
Power Supply to Suit	\$29.50
Hex Keypad	\$24.90
ETI 568 Sound or Light Operated Flash Trigger	\$25.90
ETI 147 Electronic Dummy Load kit	\$99.00
Series 3000 'Mini' Stereo Amp kit	\$79.90
ETI 561 Metal Detector kit	\$32.50
Playmaster 40 plus 40 Amp kit	\$129.00
Playmaster AM/FM tuner kit	\$129.00
Playmaster Graphic Equaliser	\$99.50

## KITS

Playmaster Graphic Analyser kit	\$99.50
EA 79SF9 Sound Flash Trigger	\$15.00
ETI 565R Ultra Sonic RX	\$15.95
ETI 565T Ultra Sonic TX	\$8.95
ETI 576 Electromyogram kit	\$89.00



ETI 147 Oct 80 Electronic Load kit parts \$75.00  
 ETI 327 Turn Hazard Unit kit parts \$22.00



EA Digital Engine Analyser Oct 80 80TMBal/10 Kit parts inc. front panel \$44.95



EA Car Battery Voltage Monitor Oct EA kit parts \$6.50  
 EA Bipolar Train Controller Nov 80 kit parts \$26.00  
 EA Digital Storage CRO Adaptor Nov 80 kit parts \$79.00  
 EA Light Beam Relay Nov 80 kit of parts \$13.00  
 EA RS232 Printer Interface Nov 80 kit parts \$15.00

## SPECIALS


TRIO CRO'S NOW IN STOCK (write for full product range and price list)

\$555.00 plus tax.



TRIO

Simplified circuitry improved performance and dependability have been successfully realized with the use of ICs throughout the TRIO range. The TRIO range includes a high DC to 15 MHz, as high a sensitivity as 10 mV/div, and a sweep rate of 0.5 sec/div to 15 MHz. A sweep rate extends from 0.5 μsec/div to 0.5 sec/div in 19 ranges. Further, TV vertical and horizontal sync are available. The TRIO range includes a high input impedance, sweep, is a range of applications. The TRIO range includes a Y-sensitivity of high input sensitivity for Lassolous measure-ments. Dimensions: 260(W) x 190(H) x 385(D) mm. Weight: 8.8 kg

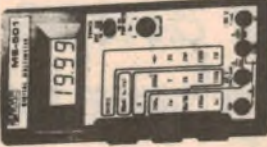

Soar Model 501A  
 4 digit LARGE LCD DISPLAY  
 Send for spec. \$79.00  
 Add \$3 P&P and certified mail.


## INTERASIL LCD 3 1/2-DIGIT PANEL METER KITS. INTERASIL ICL7106 \$34.50

Build a working DPM in 1/2 hour with these complete evaluation kits. Test these new parts for yourself with Interasil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter. ICL7106EV(LCD).



SUPER SPECIAL COMPUTER COOLING FANS 4 INCH \$18.50

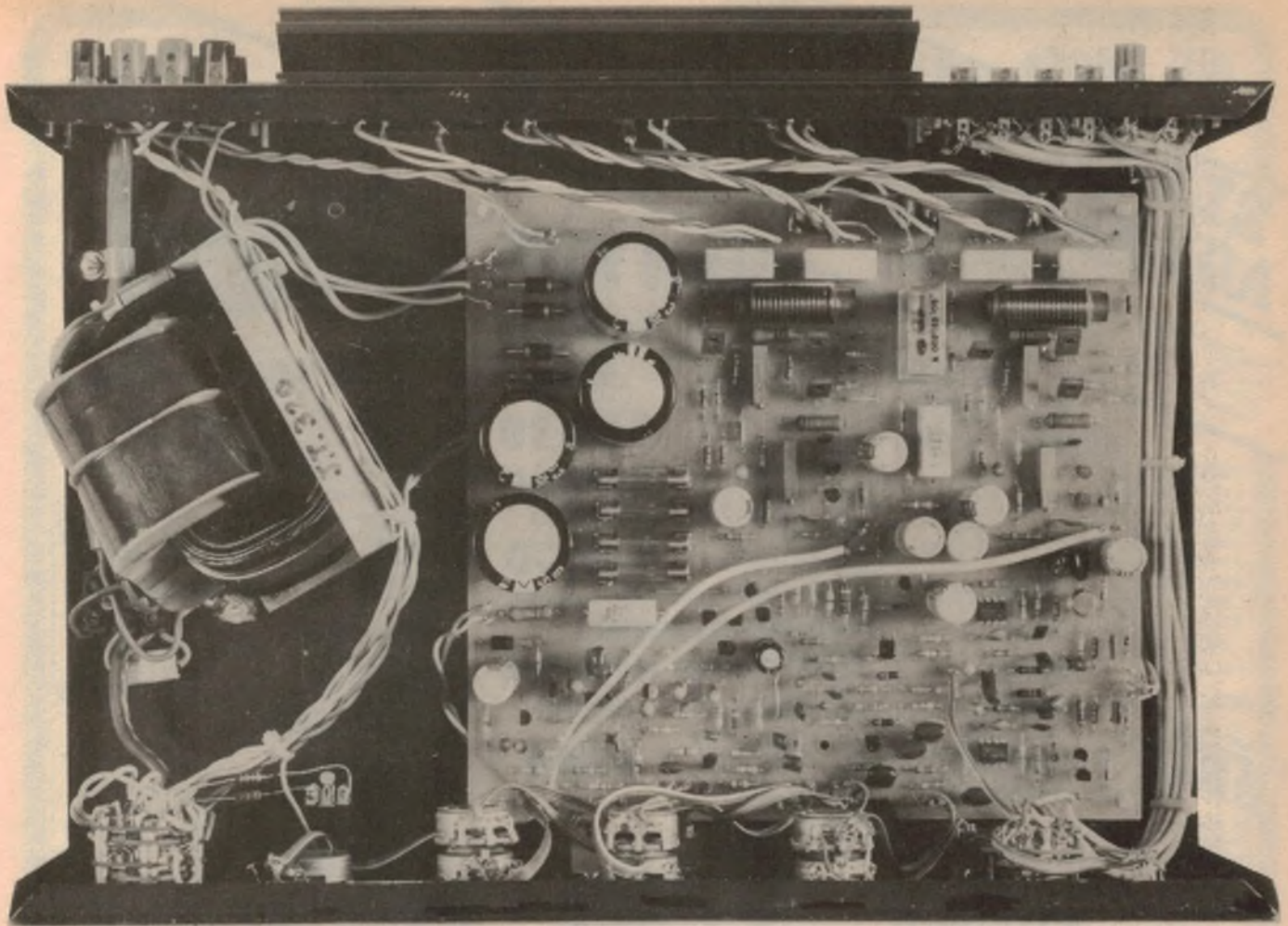For heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. Minimum pack and post \$1.00. Bankcard Mail Orders welcome.



*This photo shows how the wiring from the Speaker Selector to the Speaker terminals is attached to the C-core transformer.*

The mains cord should be passed through a grommetted hole in the rear of the chassis and anchored with a cord clamp. Terminate the mains active (brown or red) and neutral (blue or black) wires to the insulated terminal block and solder the earth (green or green with yellow stripe) wire to a solder lug near the transformer.

The mains switch has a  $0.01\mu\text{F}$  interference suppression capacitor wired across it, at the insulated terminal block. Keep the leads to this capacitor reasonably short and sleeve them if necessary with Nylex and spaghetti to prevent them from contacting the chassis (or the user). This interference suppression capacitor must be rated for 250VAC operation. This means that it must either be a metallised paper or dual dielectric (paper plus polyethylene terephthalate) type rated at 250VAC, a metallised polypropylene type with a rating of 250VAC or 1kV or 1600VDC or a ceramic disc capacitor rated at 2kV or higher.

Do not use polyester or polypropylene capacitors rated at 630VDC or 220VAC. They could be a potential fire hazard.

Mount the transformer as shown in the photographs and chassis wiring diagram. Note that the Jones C-core transformer

has an odd orientation, to minimise hum. Whichever transformer is used, the primary connections should be near the on/off switch while the secondary connections are to the rear.

Wiring from the input sockets to the Selector and associated switches can now be installed, with the shields all terminated to the common earth "bus" around the input sockets. This bus is soldered to a solder lug retained by the input panel mounting screw close to the binding post terminal. The cable shields are not terminated at the Selector switch. The cable shields for the phono input are terminated at the PC board, when it is installed. Note that the phono input cable must be run first, before that for the tuner and auxiliary inputs.

Cut and dress the input cables so that they lie together neatly, as in the photographs. Use three cable ties to hold the cables in position.

Flat ribbon cable can now be run from each potentiometer section, and from the associated toggle switches. Each cable should be of an appropriate length and stripped and tinned at the free end, ready for termination to the PC board.

By way of explanation, flat ribbon cable usually comes in 10 strand form — just peel off as many strands as needed

and cut to length.

On the loudspeaker terminal panels, connect the two outside earth connections together with 16-gauge tinned copper wire and then install two  $.047\mu\text{F}$  capacitors from the "earths" to solder lugs on the chassis. These capacitors must not be omitted as they help maintain amplifier stability and suppress mains-radiated interference.

Now you can mount the PC board into the chassis. Terminate the transformer secondary wires directly to the PC board (do not use PC pins for these three connections) and then mount the PC board using six Richco plastic supports. Both the board and chassis should be drilled for these supports.

Make all connections exactly as shown in the chassis wiring diagram. Do not use ribbon cable to make the connections to the Mosfet output transistors or the loudspeakers — it does not have sufficient current rating. Instead, use conventional hook-up wire such as  $10 \times 0.2\text{mm}$  or heavier.

Connecting leads to the output transistors should be kept as short as possible and twisted together for neatness. Keep these leads away from the input socket panels, or instability could result.

If you are using the Jones C-core

Bill Edge's

# ELECTRONIC AGENCIES

bankcard welcome here  
115-117 Parramatta Road Concord 2137  
(Corner Parramatta Rd & Lloyd George Ave)  
Tel. 745 3077 (two lines)

\$1.00 All heavy or bulky items  
\$2.00 (over 20kg) sent 'Freight-on'  
\$3.00 through carrier. Bankcard  
\$4.00 welcome—by mail, phone or  
\$5.50 over the counter.

MAIL CHARGES  
\$5-\$9.99  
\$10-\$24.99  
\$25-\$49.99  
\$50-\$99.99  
\$100 or more

what else do we carry?  
HARDWARE \* TOOLS \* SEMIS  
VALVES \* HI-FI \* KITS \* PA EQUIPMENT  
MIKES \* SPEAKERS \* BOOKS

TRADING HOURS  
9am—5.30pm  
Mon-Fri  
9am—noon  
Saturday  
10am—2pm  
Sunday

## Superb ETI 4000 speaker kits

The ETI 4000 series speakers have set new standards in kit speaker design and performance. The kits can be purchased as drivers and crossovers only—you make your own cabinets; or you can buy a complete kit with cabinets

ETI 4000/2 3 WAY INC. CABINETS **\$510** pair  
ETI 4000/1 4 WAY INC. CABINETS **\$709** pair  
ETI 4000/2 3 way **\$370** pair  
ETI 4000/1 4 way **\$469** pair

## NEW windscreen wiper delay kit

A complete kit of parts including case, front panel and hardware to make a 4 speed delay unit. Easy to build, easy to install.

See EA Sept '79

ONLY

**\$19.95**



## "Selectalott"

Why bother thinking up numbers when this great little kit can do it for you? 40 LEDs tells you what to pick. Who knows? You could even win! Great conversation piece (also useful for picking dishes in Chinese restaurants!)



**\$22.95**

## ph meter

3 1/2 digit display, easy to build pH meter. Ideal for pool or fish tank water testing, or lab use.

**\$99.50**

with solutions

## drill speed control

Simple to build kit gives complete control over the speed of your universal 240V AC brush type drill.

**\$13.50**

## 300 Watt Amp

Famous EA designed 300 watt power amp module. All you need is a power supply and case for a complete 300 watt power amp. Has many uses—PA, stage, hi-fi, irritating neighbours, etc.

**\$85**

Bill Edge (on the left) and Bruce Routley, Manager, personally guarantee you the best in friendly, efficient service when you buy from Electronic Agencies.

## NEW KITS

### Fuzzbox

No self-respecting guitarist since Jimi would be caught dead without a fuzz box. This great new design from EA solves all the old noise problems—and you'll save a packet by building it yourself.

**\$19.50**

### 'Le Gong' doorbell kit

**\$15.00**

Why spend a fortune on a doorbell when this great new kit can do the job simply, cheaply and pleasantly (or use it to replace that passe 'ding-dong' job you've got now!) (pushbutton not included) See EA Feb '81

### Toroidal powered Playmaster amplifier

The acclaimed Playmaster series of amplifiers now has a 50 watt per channel model with MOSFET outputs giving incredibly low distortion—and our kit has an exclusive TOROIDAL transformer for lower hum and improved performance.

MOSFET

**\$159**



## NEW oscilloscope switch kit

Convert your single trace CRO to dual trace with this simple to build kit. Kit includes  
\*12V plugpack  
\*IC sockets  
\*Fibreglass PCB  
\*Metal front panel  
\*All hardware  
Complete kit



**ONLY \$65.00**

See EA Feb '81

## Special offer!

FANTASTIC!

## DICK SMITH 6.5MHz CRO

The Dick Smith CRO is ideal for the hobbyist's workbench—now you can own the CRO and the superb dual trace adaptor kit and SAVE MONEY! BUY BOTH TOGETHER



if purchase separately

FOR ONLY **\$249** save **\$16** **\$199**

## FREE! software with the SYSTEM 80



16K RAM

**\$750**

to \$20 value

You all know about the famous System 80 computer. But did you know that if you buy your System 80 from Electronic Agencies you get up to \$20 worth of software free? That's right—\$20 worth of software to get your System 80 up and running straight away!


NEW lower price

## SAVE \$10 MUSICOLOR

Yes! the famous Musicolor 3—now reduced to \$10 below normal price. Complete kit with deluxe metalwork and front panel!

NOW ONLY **\$59.90**

## Engine Analyser kit

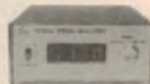

**\$53.50**

Keep your car in tune and save fuel. This unit measures RPM, dwell and battery voltage on any 4, 6 or 8 cylinder petrol engine. Complete kit

## Light & sound flash kit

Take spectacular action photos. Suits any flash unit—fully variable sensitivity & delay. See ETI Oct



**\$26.95**

## wideband receiver kit

Four ranges from broadcast to 30MHz. Complete kit (see EA Nov 1980 for details) only:



**\$65.00**

## six hour turnaround on mail orders

If the goods are in stock your order will be at the Post Office within six hours. Can any of our competitors beat that?



## PLAYMASTER MOSFET STEREO AMPLIFIER

transformer do not dress and bind the loudspeaker wiring permanently at this stage. You will have to find the optimum wiring dress in a procedure we will outline later.

With all the wiring complete, double-check all your work to ensure that no mistakes have been made. You are now almost at the stage where power can be applied. Set the trimpots associated with the power amplifier inputs to midpoint and the trimpots for quiescent current adjustment (between the collectors of Q9 and Q10) to minimum resistance. Do not connect loudspeakers or dummy loads at this stage. Disconnect the power amplifier inputs at pins 35 and 37 on the PC board.

Now apply power and measure the supply voltages which are shown on the circuit diagram. Note that these are approximate only. Now check that the amplifier output voltages, at the junction of the  $0.56\Omega/5W$  resistors in each channel, are close to 0V. That being the case, you can set the quiescent current. This is done by measuring the voltage across one of the  $100\Omega/5W$  resistors installed across the fuseholder clips.

Adjust the appropriate trimpot to obtain 7.0 volts across the resistor, coinciding with a quiescent current of 70 milliamps. Later checks of this voltage will probably show that the current drifts but provided it stays within about  $\pm 10mA$  or so there is no cause for worry.

Note that it is immaterial whether you measure the voltage across the  $100\Omega$  resistor in the positive or negative supply rails to each power amplifier — the reading will be the same. Just make sure that you measure the voltage across one of the appropriate resistors, dependent on which channel you are adjusting. Looking at the PC board from the front, the two fuseholders for the righthand power amplifier are closest to the front, with that closest being in the negative supply rail.

The quiescent output voltage at the output of the power amplifiers should preferably be adjusted with the aid of an accurate digital multimeter which has polarity indication, so that the voltage can be adjusted to within a few millivolts of 0V. Failing that, a conventional multimeter switched to the lowest available DC voltage range will do the job, although the final setting will probably not be as good. (Note that, in theory, greater sensitivity could be obtained from a conventional multimeter when switched to the lowest available current range, eg,  $50\mu A$ , but the strong possibility of inadvertently damaging the meter movement makes it inadvisable!)


This adjustment is fairly touchy in nature but it should be possible to set the quiescent output voltage to within

$\pm 5mV$  of 0V. The trimpots in question are the ones associated with Q6 and Q7 in each channel.

Now connect loudspeakers and the connections on the PC board at pins 35 and 37. With the volume control set fully anti-clockwise, listen closely to the loudspeakers for any extraneous hum and noise. With typical loudspeakers and in a quiet room, the noise level should be very low. Turning up the volume control should not increase the noise level markedly, except in the case of the phono input which should have a magnetic cartridge connected (or be short-circuited) for minimum noise output.

As noted previously, it is possible to optimise the loudspeaker wiring "dress" for minimum hum output, if the C-core transformer has been used. Reference to the relevant chassis photo will show that the loudspeaker wiring is bound into a

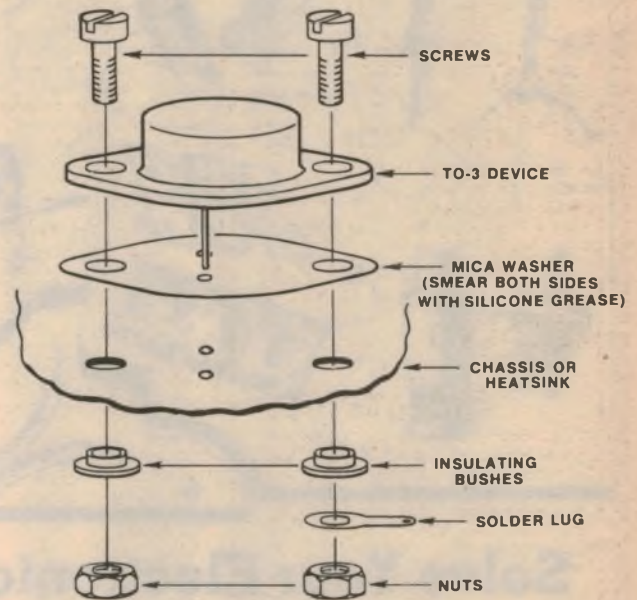*This diagram shows the method of mounting the power transistors.*



cable form with ties and attached to the topmost edge of the transformer clamp (with a suitable adhesive). The best position for this cable form can be found by monitoring the residual hum output from both channels by using a pair of stereo headphones (the more sensitive, the better).

Those who have access to an audio oscillator will be able to orient the tone control potentiometers accurately so that when set to zero they are flat. For the treble control the "flat" position is very close to the mechanical centre of the resistance element but for the bass control, the flat setting is closer to "2".

If these checks are okay, turn off the power and wait until the reservoir capacitors discharge, as indicated by one of the LEDs. Now install the 2A fuses and you are in business. Select program source and listen to your heart's content.

Providing that all these checks are to your satisfaction, you may then install the front panel.

For those who have been unlucky enough to be unable to obtain correct operation, we sympathise with you and now provide some notes on troubleshooting.

Trouble-shooting in the power amplifiers should be performed with the  $100\Omega/5W$  resistors wired across the fuseholders in place of the 2-amp fuses. If a fault is present which causes heavy current drain, the resistors will get very hot but they will generally prevent damage to the output stage. This means that you can work on the amplifier without worrying about burning up expensive output devices.


Even so, you should take care while trouble-shooting. The total DC voltage in the power amplifiers is 100 volts or so, which can give you a nasty belt! By the same token, avoid touching the output transistor cases when the amplifier is delivering high power.

Tabulated below are the voltages at all the key points in the circuit. These were

taken with the amplifier under no-signal conditions, with volume control at minimum setting, tone controls and balance control centred and with 240VAC input. Note that small changes in the mains voltage will cause equivalent changes in the power amplifier voltages while in the preamplifier, normal component tolerances will cause voltage changes of up to  $\pm 10\%$ .

First, we will assume that the positive and negative supply rails are operational. If the negative or positive 15V rails are less than 1V, the likely cause is a short-circuit or reverse-connected zener diode. On the other hand, if these supplies are substantially higher than 15V, then it is likely that the associated zener diode is open circuit. Note that the 15V rails are actually slightly less, at about +13.9 and -14.4V.
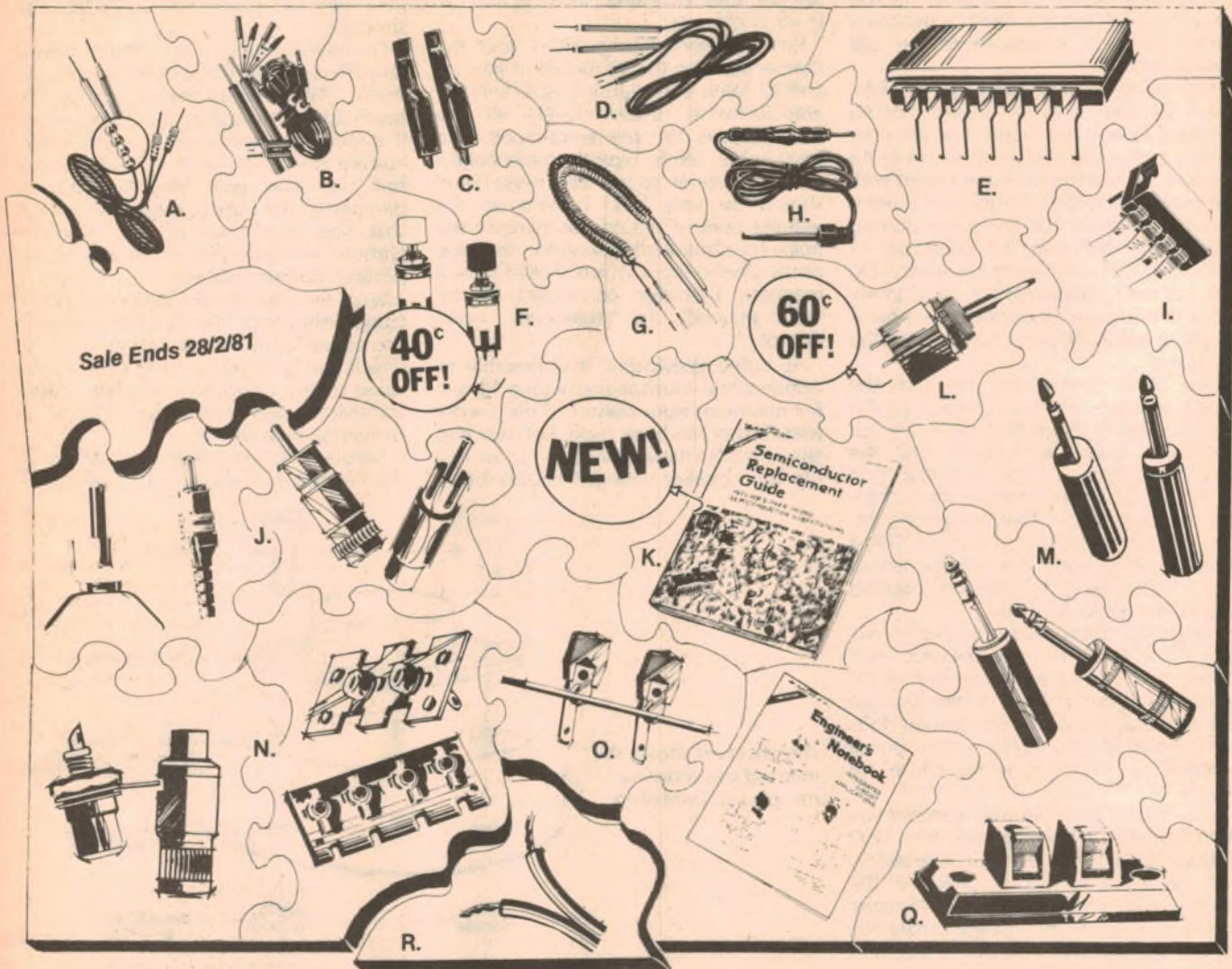
# TANDY PUTS THE PIECES TOGETHER FOR YOU!



## Solve Your Electronics Parts Puzzle At Tandy!

We make it easy with our quality range, advice and year-round low prices!

Whether you're a do-it-yourselfer or a professional, Tandy's got the biggest range of parts in Australia. Let Tandy put you in the picture.

- A. "Flexi" Test Leads. 1.5m.  
278-740 ..... Pair/2.69
- B. 11-Pc. Test Lead set. 270-332 . . . 6.95
- C. Insulated Alligator Clips.  
270-354 ..... Pair/1.99
- D. 127 cm Banana Plug/Test leads.  
278-746 ..... Pair/3.39
- E. Phase-Locked Loops from only  
..... 2.99

- F. Pushbutton Switches from only  
Regular Retail Price 2.59 ..... 2.19
- G. Coiled Cord Test Leads.  
278-750 ..... Pair/3.99
- H. Mini-Clip Test Leads. 5.7cm.  
278-1160 ..... Pair/3.99
- I. Op-Amps from ..... 1.09
- J. Quality Audio Plugs, assorted  
packages from ..... 1.59
- K. Semiconductor Handbook.  
276-4004 ..... 2.99
- L. Lever Switches. Big range from  
Regular Retail Price 2.99 ..... 2.39

**Australia's Parts Place!**

- M. Phone Plugs as low as 1.29 (Pkg. of 2)
- N. Quality Phono Jacks from only  
..... 1.19
- O. Pushbutton Terminals. 274-315 ..... 1.39
- P. Engineers' Notebook. 276-5001 ... 2.49
- Q. Spring-Lever Terminals.  
274-621 ..... 1.49
- R. 2-Conductor Speaker Wire.

Description	Gauge	Mtr	Cat No.	Ea
Miniature Clear	24 Solid	23	278-1509	4.99
Medium Clear	22 Stranded	30	278-1385	5.59
Standard Clear	20 Stranded	23	278-1388	6.39
Low Loss Clear	18 Stranded	9.1	278-1602	4.49
Low Loss Clear	18 Stranded	18	278-008	7.19
Standard Brown	20 Stranded	30	278-1387	6.99
Heavy-Duty Brown	16 Stranded	9.1	278-1263	4.99
Heavy Duty Brown	16 Stranded	30	278-1384	12.95

Available at all Tandy Stores and Participating Dealers Around Australia or Mail Order Department, P.O. Box 229, Rydalmere, N.S.W. 2116

# TANDY ELECTRONICS

## PLAYMASTER MOSFET STEREO AMPLIFIER

	emitter	base	collector
Q 1	-0.57	-0.015	1.2
Q 2	-0.57	-0.015	1.2
Q 3	6.6	7.2	13.9
Q 4	0.68	1.3	7.5
Q 5	6.8	7.5	13.9
Q 6	0.75	0.15	-47.9
Q 7	0.75	0.15	-47.9
Q 8	-48.6	-47.9	-20.1
Q 9	-48.6	-47.9	-0.5
Q10	48.9	48.3	0.6
Q13	0.0	0.0	0.2
Q14	0.68	0.2	0.0
Q15	0.0	0.0	0.68
Q16	0.0	0.68	0.26
Q17	51.0	50.4	50.9

These are the key voltage readings in the circuit of the new amplifier.

These voltage readings were taken with a digital multimeter having an input impedance of 10 megohms. Readers should note that loading effects of conventional multimeters with a sensitivity of 20,000 ohms per volt will prevent accurate voltage measurements from being taken around Q1 and Q2, and at the bases of Q3 and Q4. The voltages given at the bases and emitters of Q6 and Q7 are notional only and will depend on the matching between the transistors and the setting of the balance trim pots.

A difficulty in using voltage measurements to diagnose faults in amplifier circuits is that negative feedback can often cause the fault conditions to be "reflected" throughout all stages. Worse still, negative feedback may enable an amplifier with a faulty transistor to produce very-close-to-correct operating conditions in all stages. Still, careful analysis of the operating voltages can often give a clue to where the fault lies.

A useful point to remember is that all conducting transistors will have a base-emitter voltage drop of 0.6 to 0.75V. It is also useful to remember that if one channel is fully operational, it can serve as a basis for comparison with the faulty channel.

Trouble-shooting in the power amplifiers should be done with the amplifier inputs at pin 35 and 37 on the PC board disconnected.

If the amplifier output voltages cannot be set to zero, check the base-emitter voltages of Q6 and Q7 (0.6V) and their collector voltages — approximately -48V and equal. If no fault is evident here, continue voltage checks through the stages of the amplifier. If the voltages around Q8, 9 and 10 are wildly askew, check that you have not inadvertently swapped Q10 with Q8 or Q9.

If the amplifier offset voltage is close to zero and the 100Ω protective resistors are dissipating excessive voltage it is likely that the amplifier is oscillating super-

sonically or drawing excessive quiescent current. Check that the gate connections to Q11 and Q12 are okay. If no variation of the quiescent current can be obtained by varying the appropriate trim pot, try shorting the gates of Q11 and Q12 together. This should drop the quiescent current to zero. If not, one of the Mosfets is probably faulty. If so, the relevant trim pot wiper is probably open-circuit.

Instability in the power amplifiers in the form of supersonic oscillation could be due to the following causes: faulty RLC network in the output stage; faulty 100μF bypass capacitors; open-circuit 100pF capacitor associated with Q8; poor lead dress associated with Q11 and Q12 or with the loudspeaker wiring.

Faulty or open-circuit capacitors can generally be checked by bridging with a capacitor of equivalent value.

Trouble-shooting in the preamplifiers follows similar procedures to those used in the power amplifiers. Remember to leave the 100Ω protective resistors in circuit just in case you drop a meter prod on the PC board or a similar untoward event occurs.

Note that while the output voltage at pin 6 of the TL071 op amps is nominally zero, it can be as high as ±200mV, dependent upon the matching of Q1 and Q2 and the match of the input stage transistors in the TL071. If the output offset is higher than this figure, it is likely that Q1, Q2 or the TL071 op amp is faulty. Do not fall for the trap of forgetting that the op amps are orientated in different directions. You were warned previously!

If any transistors are removed from the circuit as suspect, it is handy to be able to check them with the aid of a multimeter. The range which is usually appropriate is "R × 100 ohms". First check the transistor from collector to emitter in both directions. Each measurement should produce a high resistance reading. Similarly, check the base-emitter and base-collector junctions. These should give high readings in one direction and low readings in the other.

Excessive hum in the amplifier may be a problem caused by some of the abnormal operating conditions already described, or by incorrect layout. But the latter should not occur if the wiring diagrams have been followed explicitly.

### ERRATA:

A number of errors have come to light in the parts list for this project, published last month on page 47. In the list of capacitors, delete the 2 x 33μF/50VW electrolytics, and one 47μF non-polarised electrolytic. In the list of resistors, add one 15kΩ/¼W and change the 4 x 0.47Ω/5W to 0.56Ω.



### AP SERIES OMNI-PURPOSE LOUDSPEAKER



#### AP-Series

The world's most appreciated indoor/outdoor loudspeakers, 15 or 30 Watts. Choice of 8 or 45 Ohms, or Built-in Vari-Tap control-centre for line matching. Sensitivity as microphone: -20dBm.

### WT SERIES MUSIC SPEAKERS



### AUSTRALIA'S LEADING SOUND EXPERTS

### AUDIO TELEX COMMUNICATIONS PTY. LTD.

Sydney  
P.O. Box 421,  
1 Little Street,  
Parramatta, 2150  
Phone: 633 4344  
Telex: 22251

Melbourne  
P.O. Box 468  
7 Essex Road,  
Mt. Waverley, 3149  
Phone: 277 5311

Brisbane  
P.O. Box 44  
394 Montague Road,  
West End 4101  
Phone: 44 6328

Adelaide  
Werner Industries  
Unit 5, 28 Gray St.,  
Kilkenny, 5009  
Phone: 268 2801

Perth  
Electro Acoustic Co.  
55 Frobisher Street,  
Osborne Park, 6017  
Phone: 444 8688

Add interest to your music with this

# Simple fuzz box for electric guitars

Feel like some fuzz on your guitar? What is fuzz anyhow? Does it have anything to do with policemen? These and other hairy questions are answered in this article which shows you how to make a fuzz box for your electric guitar.

by PHILIP WATSON

We first described a fuzz box back in August 1967 (File No. 1/GA/10) and it proved extremely popular. So much so, that we were recently inspired to take a fresh look at the original design, with the aim of simplifying construction. As a result it now uses a PC board and employs CMOS switching to circumvent a shortage of suitable mechanical switches as used in the original.

For those who may be a little hazy as to just what a fuzz box is, or how it works, let us recapitulate from the original article.

A fuzz box is a piece of circuitry introduced into the guitar amplifier chain to deliberately distort the waveform. It produces a sound which is "buzzy" by nature, not unlike that from a heavily overloaded amplifier or from a loudspeaker whose voice coil is fouling in the magnet gap. In fact, the similarity of fuzz to overload is no accident, because a fuzz box deliberately simulates or introduces an overload condition.

By nature, the waveform from an electric guitar ranges from the reasonably

sinoidal to one carrying mainly consonant harmonics – depending on playing technique and the position of the pickup coils in use. A fuzz box squares up, or otherwise distorts the waveform envelope, adding multiple harmonics as it does so, and also adding further dissonant frequencies by intermodulation of those actually being fed in from the pickup coil. The naturally "round" tone of a guitar therefore takes on a strident quality.

Just how a fuzz box treats the wave envelope passing through it depends largely on the circuitry involved. Straight clipping circuits, for example, square off the tops of the waveform, so that predominantly sinoidal waves begin to look quite square on a CRO. As might be expected, the sharper the corners, the wider the spectrum of the harmonics so generated.

In actual fact, most guitarists tend to regard squared waves as too conservative in terms of fuzz, particularly when generated from substantially pure waveforms; a squared sine wave has a

rather pleasant "woodwind" quality and is anything but strident. Again, while a broad spectrum of harmonics may be generated in the first instance by simple clipping, those above about 4kHz don't count for much in the average guitar situation.

The kind of guitar fuzz which is likely to have greater impact is that in which there is a concentration of spurious harmonics within the normal musical range of a guitar system – that is, up to about 3kHz. Aurally, the requirement seems to be met best by circuitry which tends not just to clip waveforms, but to generate waves with generous overshoot at either or both ends of the plateau.

In short, fuzz is a gimmick intended primarily to add stridency to single tones or, at most, simple chords. It should not be used with complex chords and needs to be switched out before such chords are attempted.

The method we have used to produce fuzz is to pass the guitar signal through a small transistor amplifier whose operating conditions can be modified to operate in overload mode from direct guitar signals.


The characteristics of our fuzz box may be summed up as follows:

(1) Completely self-contained, connecting between an individual guitar and its normal input jack to the main amplifier. It should operate with almost any typical guitar system.

(2) Output on "normal" and "fuzz" is at substantially the same level and, in both modes, the unit contributes a small amount of gain.

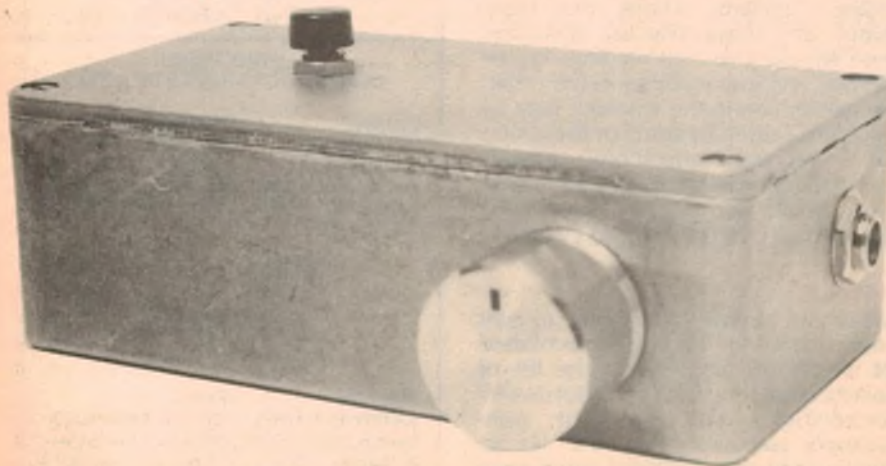(3) In addition to the normal fuzz footswitch, a control allows the degree of fuzz to be varied as required.

As can be seen from the circuit diagram, the device consists of, basically, two DC coupled transistors operating as



We estimate that the current cost of parts for this project is approximately


**\$19**

including sales tax.


Why make it beautiful if you're only going to tread on it?



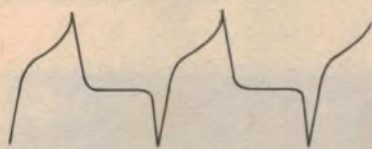
MIN. FUZZ 30mV RMS INPUT, 120mV P-P OUTPUT



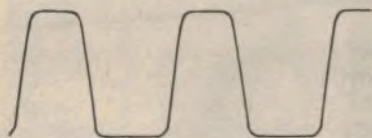MAX. FUZZ 30mV RMS INPUT, 360mV P-P OUTPUT



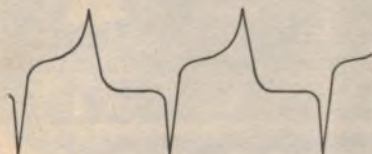MIN. FUZZ 60mV RMS INPUT, 120mV P-P OUTPUT



MAX. FUZZ 60mV RMS INPUT, 520mV P-P OUTPUT


Shown above are typical waveforms from the unit. As can be seen, the "fuzz" at minimum is amplitude dependent but at higher levels of distortion the waveform is determined mainly by the "fuzz-control" setting.

an amplifier in the guitar line. By means of three CMOS switches (4016) the operating conditions can be changed from a simple distortion-free mode, to a high distortion mode, but with the degree of distortion variable over a useful range.

To understand how this is done, imagine that two of the switches — pins 3,4,5 and 10,11,12 — are closed and the third one — 1,2,13 — is open. Under these conditions the load for the first transistor is made up from the 15k $\Omega$  and 680k $\Omega$  resistors. This, with the forward bias applied, is sufficient to bring the stage near to current saturation. Because the second transistor base is DC coupled to the first collector, the second transistor will simultaneously be held to near cut-off.

When a sinoidal signal is applied to the first transistor base, the base will be driven alternately positive and negative. On the positive swing of the input signal the transistor will be driven into complete saturation, limiting the collector's voltage swing and resulting in a clipped signal peak at the collector.

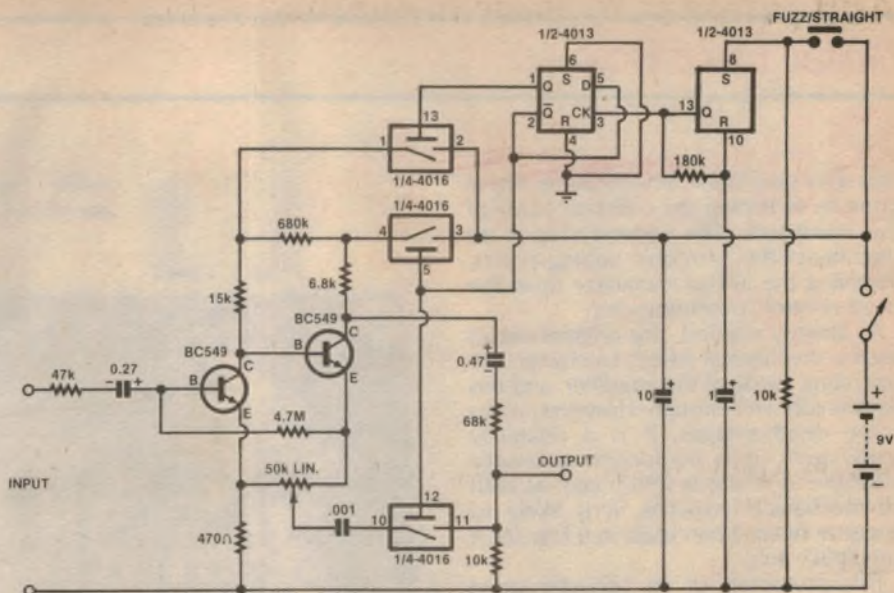On the other hand, the quiescent voltage across the load is sufficient to allow a full and unclipped collector voltage swing on the other half-cycle of the signal. The resulting waveform at the first collector is therefore a sinusoid with a clipped negative peak.




FUZZ-BOX

VIEWED FROM BELOW

1/GA1-

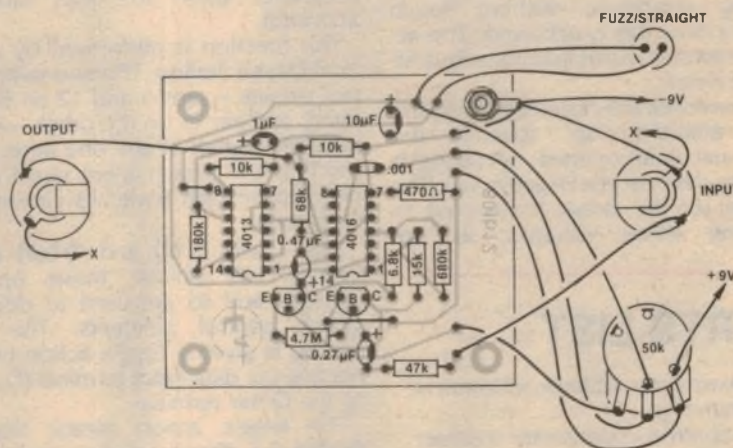The circuit consists of two DC coupled transistors operating as an amplifier in the guitar line. It is designed to deliberately introduce distortion.



This wiring diagram shows the PC board as viewed from the component side. Observe the usual precautions when soldering in the CMOS ICs (see text).

Now for the other transistor. The unaffected signal peak at the first collector will drive the second transistor into a complete cut-off, thereby delivering a signal at the output which has both peaks clipped.

The actual gain through the fuzz unit is largely a function of the output divider, the 10k $\Omega$  and 68k $\Omega$  resistors being chosen to give a small amount of gain in both modes, actually about 1.5 times.

However, as we have already pointed out, waves which are merely squared produce rather modest fuzz, and further elaboration of the distortion circuitry is called for, at least for the more extreme effects.

Looking again at the circuit, a distorted signal appears also at the emitter of the second transistor and, by adding the higher frequency components from this

distorted and out-of-phase waveform to the output from the collector circuit, the end result is a large spike above the trailing edge of the initial squared, output waveform.

By using a potentiometer as the emitter load for the second transistor, it is possible to vary the basic fuzz shape to one with the superimposed spike, as already mentioned.

This explanation assumes that the output from the guitar will be sufficient to overdrive the transistors, but this will normally be the case **provided the guitar is operated with its own volume control fairly well advanced.**

When the CMOS switch positions are reversed, ie, the 1,2,13 section is closed, and 3,4,5 and 10,11,12 are open, two things happen. Firstly, the operating condition of the transistors is changed so



# Guitar Fuzz Box


that they give linear amplification; this is done by switching the collector loads of the transistors. The second step is to disconnect the harmonic adding circuit, involving the  $.001\mu\text{F}$  capacitor from the "fuzz control" potentiometer.

As already implied, the original circuit used a mechanical switch to change the operating mode of the amplifier, and this did the job well enough. However, it has some disadvantages. It is a relatively costly item, it is no longer as readily available as it was in 1967, and, as with all mechanical switches, it is likely to become noisy when used in a low level circuit like this.

This prompted us to consider using CMOS switches. By this means we reduce the fuzz switching function to a single pair of contacts, and these are no longer directly in the signal path.

In our circuit explanation so far we have simply assumed that the three 4016 bilateral switches have been open or closed, as required for a particular operating condition, without much regard for how this is achieved. The actual operation is worth looking at in a little more detail.

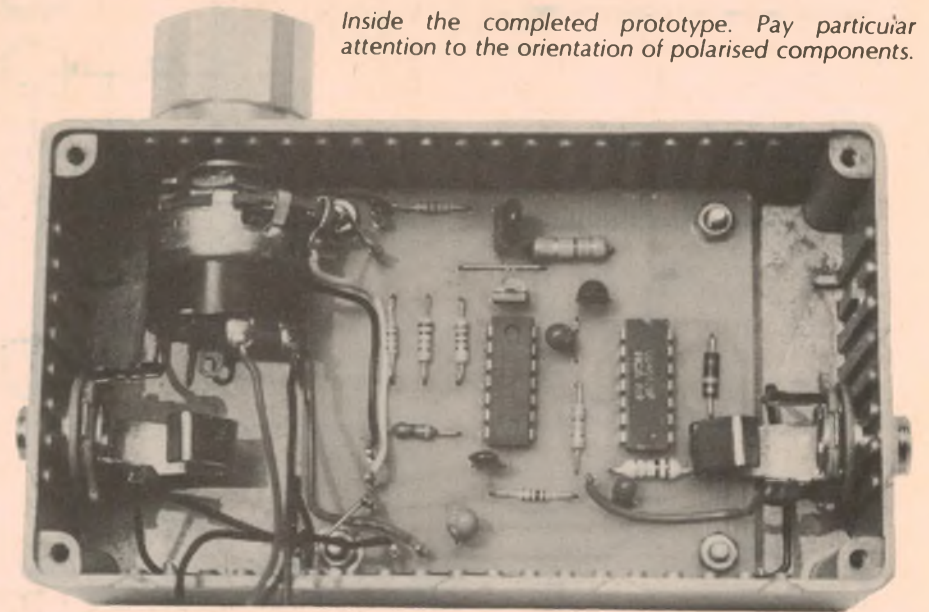These switches are closed by taking the control element "up" towards the positive rail, and opened by taking it "down" to deck, or the negative rail. The remainder of the circuit is devoted to generating these voltages, as ap-



Inside the completed prototype. Pay particular attention to the orientation of polarised components.

propriate, when the foot switch is activated.

This function is performed by a 4013 dual-D type flipflop. The two switch control circuits — pins 5 and 12 on the one hand, and pin 13 on the other — require opposite signals at any one time. When pin 13 is low (switch open), pins 5 and 12 need to be high (switches closed), and vice versa.

Pins 1 and 2 (Q and Q-bar) of the flipflop will deliver these opposite voltages and so are used to drive the switch control elements. The same flipflop is given a toggle action by connecting the data input terminal (D, pin 5) to the Q-bar terminal.

The toggle action means that the flipflop will change its state each time a

positive pulse is fed to the clock terminal (pin 3) and, in theory, such a positive pulse could come directly from the positive rail via the footswitch (with suitable current limiting).

In practice, bounce in the mechanical contacts would inevitably result in more than one pulse being generated, giving an unreliable end result. For this reason the second flipflop is used as a de-bounce circuit, the  $180\text{k}\Omega$  resistor and the  $1\mu\text{F}$  capacitor providing the necessary time constant.

Thus, although the footswitch is only a simple momentary-make switch, it is made to function, as far as the user is concerned, in the same manner as the original mechanical switch, ie, in a "push on-push off" mode. Each time the switch

## PARTS LIST

- 1 Diecast box, 122mm x 66mm x 40mm
- 1 Pressbutton momentary contact switch
- 2 6.5 panel sockets
- 1 9V battery (Type 216 or similar)
- 1 Connector to suit battery
- 1 Aluminium knob, 25mm dia
- 1  $50\text{k}\Omega$  linear potentiometer with switch
- 2 BC549 NPN transistors
- 1 4013 dual-D type flipflop
- 1 4016 quad bilateral switch
- 1 PC board, code 80fb12

### CAPACITORS


1 x  $10\mu\text{F}$  tantalum, 1 x  $1\mu\text{F}$  tantalum, 1 x  $0.47\mu\text{F}$  tantalum, 1 x  $0.27\mu\text{F}$  tantalum, 1 x  $.001\mu\text{F}$  green cap.

### RESISTORS ( $\frac{1}{4}$ or $\frac{1}{2}\text{W}$ , 5% tolerance)

1 x  $4.7\text{M}\Omega$ , 1 x  $680\text{k}\Omega$ , 1 x  $180\text{k}\Omega$ , 1 x  $68\text{k}\Omega$ , 1 x  $47\text{k}\Omega$ , 1 x  $15\text{k}\Omega$ , 2 x  $10\text{k}\Omega$ , 1 x  $6.8\text{k}\Omega$ , 1 x  $470\Omega$
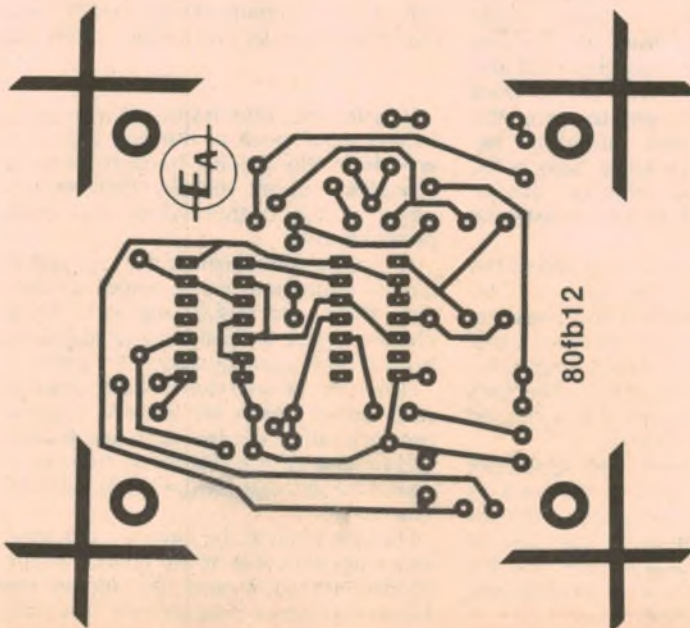
### MISCELLANEOUS

4 mounting screws, nuts, and spacers.  
Hookup wire, solder, etc.



At left is an actual size reproduction of the artwork for the PC board.

is pressed, even briefly, the operating conditions are changed.

**CONSTRUCTION**

So much for how it works. Construction is simplified by the use of a printed circuit board (80fb12). This should be readily available from the same source as the other components.

Points to watch during assembly of the board include the polarity of electrolytic capacitors, correct interpretation of transistor lead connections, and correct orientation of the ICs. In regard to the latter, some makers provide a groove at one end, as shown on the component diagram, and some identify pin No. 1 by means of a small dot moulded on the top of the package.

Another point about these ICs concerns soldering precautions. Being CMOS devices, they are more sensitive to stray voltages than some other types. A good precaution is to connect the barrel of the soldering iron to the negative rail of the board, and to solder the two supply pins — pins 7 and 14 in this case — before other pins are soldered.

The complete circuit is housed in a small diecast box measuring 122mm (L) x 66mm (W) x 40mm (D). Input and output sockets are mounted at opposite ends of the box, the footswitch on the lid, and the fuzz control/on-off switch on the side. The board is mounted in the bottom of the box, using four screws with suitable nuts and spacers to lift the board clear of the metal surface.

And that's about all there is to it. It is a relatively simple circuit, with little to go wrong. If built with reasonable care and with due regard to the simple precautions we have mentioned, it should go first time.

Coming soon . . .



**25W Guitar Amplifier**

Based on a well-proven power amplifier design, this new 25W guitar amplifier features both tone controls and a tremolo facility. It's easy to build, and should only cost about \$80. Watch for it soon!

**Ideal for practice or for use at home**



**“HOW TO TURN ELECTRONIC THEORY INTO PRACTICE AND MAKE IT PAY...”**

“If you understand and enjoy radio and electronics and want to extend your knowledge and experience, then we at Stott's can help you.

Stott's have home-study courses for complete beginners in Radio theory and basic Electronics through to the standards needed to maintain and service Colour Television.

Anyone who has these skills at their fingertips can make it pay by turning a fascinating hobby into a lucrative part or full time profession.”

*Athol H. Kelly*

Athol H. Kelly B Com (Hons) A A S A F C I S  
Principal Stott's Technical Correspondence College



**Stotts**



The name to trust in correspondence education.

TECHNICAL CORRESPONDENCE COLLEGE

- Melbourne, 159 Flinders Lane, 3000 Tel: 63 6212
- Sydney, 383 George Street, 2000 Tel: 29 2445
- Brisbane, 290 Adelaide Street, 4000 Tel: 31 1627
- Adelaide, 85 Pine Street, 5000 Tel: 223 3700
- W Perth, 25 Richardson Street, 6005 Tel: 322 5481
- Hobart, 1st Fl, 29 Argyle Street, 7000, Tel: 34 2399
- Singapore, P.O. Box 3396, Singapore 1.

Please send me free, and without obligation, full details of the following courses.

**The Stott's range of courses in Electronics is**

- Intro. to Electronics
- Digital Electronics for Technicians/ Servicemen
- Microprocessors
- AM Radio Receivers
- Radio/TV Servicing
- Colour Television
- Radio for Amateurs
- Amateur and Novice Radio Operators Certs
- Electrical Mechanics

A full range of Hobby and Business courses also available

ALA/ST1929/EA2-81

\_\_\_\_\_  
(PLEASE PRINT)

MR MRS MISS \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Stott's undertake that no sales counsellor will visit you

**BSR**WORLD'S LARGEST MANUFACTURER  
RECORD CHANGERS/PLAYERSMODEL  
P-208**BELT DRIVE STEREO PLAYER**Mechanism, cartridge only.  
Pack and post NSW \$4.50. V. SA  
\$67.50 T. Q. \$5.50.  
W. A. NT. \$6.50.Mounted in walnut cabinet, with  
perspex dust cover, hinges.  
P-P NSW \$6.50 INTERSTATE  
\$8.50. **\$117.50**

Specs. 240VAC 50Hz, auto or manual operation • Plays 17, 25, 30cm (7, 10, 12in) records • 33 and 45 rpm, adjustable counter weight and stylus pressure • cueing lever • Bias compensator and anti skate control • Big platter with mat • RCA audio plugs and cable, 3-core power cable and plug • High quality ADC magnetic cartridge • Diamond Stylus • Cut-out Template, instruction book •

Pro Model P-200. (specs. as above) **\$105.00**or mounted in walnut cabinet with perspex cover **\$137.50**P-P NSW \$4.50  
INTERSTATE \$6.00P-P NSW \$6.50  
INTERSTATE \$8.50● **NEW BSR STEREO RECORD PLAYER** ●  
● **MANUAL OPERATION** ●Model P-207 • 240V AC, 50Hz • Auto-Stop  
• S-Shape tone arm • Ceramic cartridge, dia-  
mond stylus • 33-45rpm • Plays 17, 25,  
30cm (7, 10, 12in) records • Cue lever •  
Template for cut-out • operating instructions**\$49.95** NSW 4.50. V. SA. T. Q. \$5.50. WA.  
NT. \$6.50.● **ALSO BSR STEREO COMBINATION  
CHANGER/PLAYERS** ●**Model C198.** 4-pole motor, S-shape tone arm, fitted with ceramic cartridge, **\$55.00.** Fitted with magnetic cartridge **\$65.00.****Model C197.** 2-pole motor, straight tone arm, fitted with ceramic cartridge, **\$47.50**

P&amp;P: NSW \$3.00; V. SA, Q \$4.00; TAS, WA, NT \$5.00

With all the wanted facilities • Auto or manual operation • Cueing lever • Bias compensator • Adjustable stylus pressure • 33, 45, 78rpm • Plays 7, 10, 12in records • Separate changer and player spindles • Operating instructions • Template for cut-out • Big 28cm turntable • Diamond stylus • 240V AC 50Hz.

**PA REFLEX HORN SPEAKERS**A1 Quality Weatherproof  
8 Ohms 150Hz — 13kHz6" 10 WATT \$21.95 8" 15 WATT \$25.50  
8" x 5" 15 WATT \$26.50 12" 25 WATT \$44.50

Pack and Post NSW \$1.50. Interstate \$2.50.

**SUPER  
SCOOP****PASSIVE RADIATOR HI FI  
SPEAKER SYSTEM**Excellent frequency response from the 8 ohm 15 watt  
200mm (8") woofer and tweeter with cross-over • modern  
styling sturdy walnut cabinet • 445H, 280 W, 178 DMM.**\$69.95** Pack and Post NSW \$2.75  
V. Q, SA, T \$3.75  
WA, NT, \$5.50  
Pair**1 MA. FSD PANEL METER****\$1.75  
EACH****2  
For  
\$3**

38 M/M SQ. V-U SCALE, PP 90c.

● **CERAMIC EGG  
INSULATORS** ●HIGH GLAZE • TOP QUALITY •  
32 x 22mm**10 FOR \$8.95**PP NSW \$1.50, INTERSTATE  
\$2.75.● **SLIDE POTS** ●Brand net stock, 35mm travel  
1K lin. 10K lin. 200k lin.**20 MIXED \$2.50**

PP NSW \$1.50. INTERSTATE \$2.50

● **ELECTROLYTIC** ●2200uF 63VDCW  
Chassis mounting, plastic  
encapsulated  
45 x 35mm**10 for \$6.50**PP NSW \$1.50, INTERSTATE \$2.50  
4700uF 35V AXIAL LEADS  
10 for \$17.50 PP \$1.50**A.C.E.**  
**RADIO**


136 VICTORIA

**ELE****BARGAIN PRICES • PERSONAL ATTENTION •****PLAYMASTER MOSFET**● **50 WATTS**● **LATEST TECHNOLOGY** ●**OR \$197 FOR THE FULLY CONSTRUCTED**Ref. Dec. 80, Jan, Feb 81 EA for full particulars. Add  
pack and postage: NSW \$4.50; V. Q. T. SA \$5.50;**3 DRAWER CASSETTE STORAGE CABINET****HOLDS  
36 TAPES**  
(12 IN EACH DRAWER)Modern woodgrain  
plastic, smooth sliding drawers, designed for single or multi stacking.**\$15.95** PP NSW \$2.50  
INTERSTATE \$3.50**ETONE  
12" SPEAKER  
SPECIAL****GUARANTEED TOP QUALITY  
BRAND NEW BARGAIN**Please indicate ohms required with  
order.\* Rugged diecast frame.  
8 and 15 ohms available.  
**12" Woofer, 30 Watts RMS.**  
Resonance 65Hz.  
Freq. response 50-8000Hz.**\$21.00 each or 2 for \$37.95****12" Twin Cone, 30 Watts RMS.**  
Resonance 65Hz.  
Freq respon 50-15kHz.**\$22.00 each or 2 for \$39.95**

Speaker	NSW	Interstate
Pack 1	\$2.00	\$2.75
Post 2	\$2.75	\$3.75

**ETONE  
HIGH POWER  
SPEAKERS****EXTENSIVE RANGE AT  
FACTORY PRICES****MODEL 231:** 12" 60W guitar, bass,  
organ, reson. 60Hz, freq.  
40-7000Hz **\$49****MODEL 236:** 12" twin cone, acoustic  
instruments, vocal, pa, 60W, reson.  
60Hz, freq. 40-12000 Hz **\$58****MODEL 241:** 12" 80W guitar, bass,  
organ, reson. 60Hz, freq.  
40-7000Hz **\$63****MODEL 246:** 12" twin cone, 80W,  
reson 60Hz, freq. 40-12500Hz **\$66****MODEL 451:** 15" 100W, bass guitar,  
organ, reson. 60Hz, freq.  
50-5000Hz **\$99****MODEL 801:** 15" 200W, reson.  
30Hz, freq. 30-5000Hz **\$169****MODEL 805:** 15" 250W, reson.  
30Hz, freq. 30-2000Hz **\$180**All prices plus freight. Models 231  
through 451 available 8 or 16 ohms.  
Models 801, 805. Available 4-8 or  
16 ohms.**CERAMIC  
INSULATORS  
HIGH GLAZE**High power stand-off (illustrated)  
110mm high, flange dia 95mm **\$4.50**  
(with hardware) PP NSW \$1,  
interstate \$1.50. Stand-off • Above  
chassis MT 75mm high, mounting  
hole centres 55mm **\$2.50.** PP NSW  
75c. Interstate \$1.25.**34cm B/W TV  
PICTURE TUBE**Type A34-99, 110 deflection.  
12V 75MA Fil, K cut-off 30-60V  
Focus 0-400V, HT 300V, EHT  
12KV.**BRAND NEW STOCK****\$17.50** INCLUDING PACK & POST  
ANYWHERE IN AUST.

RD. MARRICKVILLE, NSW 2204  
PHONE 51 3845

PROUD TO BE  
AUSTRALIAN 

# CTRONICS CENTRE

SLICK MAIL ORDER SERVICE • SATISFACTION

## STEREO AMPLIFIER

PER CHANNEL •

CORE TRANSFORMER •



COMPLETE  
KIT  
TOP QUALITY  
COMPONENTS

**\$159**

## THOROUGHLY TESTED AMPLIFIER

WA. NT \$7.50 and we do offer a 12 months PARTS  
and LABOUR WARRANTY.

### SELF CLEANING SOLDER SUCKER

VASTLY IMPROVED NEW MODELS •

All metal construction, other than teflon nozzle. Powerful suction •  
Lightweight handheld •

MINIATURE MODEL  
STANDARD MODEL

150 x 15MM  
IDEAL FOR I-Cs  
**\$10.95** PP 90c

185 x 20MM  
GENERAL PURPOSE  
**\$14.95** PP 90c

EX COMPUTER • PMG  
TV GAMES • POKER  
MACHINE •  
ETC, P-C BOARDS •

Crammed full of useful components •  
ICs • transistors etc. etc.  
4 MIXED BOARDS

**\$7.50** PP NSW \$2.50  
INTERSTATE \$3.50

### HEAVY DUTY CHASSIS and COVER

- Can be 19" rack mounted
- Fully ventilated
- Top quality ex-PMG

485W x 155D x 120H mm  
**\$7.50** PP NSW \$3.50  
Interstate \$5.50

### HEAT SINK •

- Double sided Cooling Fins
- A1 quality ex-PMG
- 134x110x58mm
- Drilled to suit T03

**\$3.50** PP NSW 90c  
INTERSTATE \$1.50

### EX-PMG POWER TRANSFORMERS

- EXCELLENT QUALITY  
GUARANTEED
- SIZE 115 x 95 x 90mm
- PRIMARY 0-200, 210, 220, 230  
240, 250VAC, 50Hz

Type No 1: 0-110V 2A secondary  
Type No 2: 55-0-55V 2A secondary  
Type No 3: 48, 30, 20 - 0 - 20, 30,  
48V, 2A, sec.

**\$13.95 ea** PP NSW \$2.75  
INTERSTATE \$3.75

### A1 QUALITY FIBREGLASS P-C BOARD

BRAND NEW BOARD FRACTION OF  
NORMAL PRICE 1.5MM SINGLE  
SIDED.

405 x 310mm **\$2.85 ea** PP75c  
or 3 for **\$7** PP NSW \$2

Interstate \$2.75  
360 x 80 or 245 x 110mm 90c  
ea PP75c

or 3 for **\$2** PP NSW \$1.50  
Interstate **\$2.25**

### STC • 20 BRAND NEW LEVER SWITCHES •

- Mounted on slim line panel 500 x  
40mm. Fits 19" rack.
- Audio applications.
- Model trains, etc, etc.
- Two types

Type No. 1, DPDT spring return in  
one direction.  
Type No. 2 DPST.

**\$17.50 ea.** PP NSW \$2.50  
Interstate \$3.50

### ATTENTION!! STEREO FM TUNER BUILDERS

Fully constructed front end complete with coils • Variable tuning  
condensator, 3:1 gear ratio, 2 gang AM, 3 gang FM • High freq amp with 2  
RF stages • 3 transistors FET input varactor diode (AFC) • Reception  
band 87.5-108.5MHz • IF freq 10.7 MHz • Input imp 300 ohms • Supply  
12V at 10mA • In fully shielded metal box 74W x 70D x 42H mm • Circuit  
included • Top quality unit guaranteed •


**\$19.95** P&P NSW \$1.50; INTERSTATE \$2.00

### VARICAP VHF FRONT END TUNER •

2 Bands 46.25 — 107.75MHz, 1F freq. 33.4MHz and 138.25 —  
221.75MHz 1F freq. 38.9MHz Imp. 75 ohms, 3 transistors, 10 diodes,  
PCB in fully shielded box. 90 x 88 x 20mm. Operating voltage, 0.3 — 28V,  
tech data, circuit included.

**\$19.95** PP \$1.50

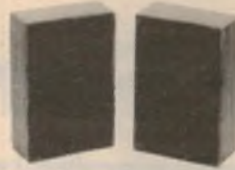FACTORY SCOOP • ½ PRICE BARGAIN  
• BRAND NEW A1 QUALITY • 8"(20cm) 2-WAY  
SPEAKER SYSTEM • 8 OHMS • 10 WATTS •



**\$42** PAIR

ATTRACTIVE WALNUT CABINET:  
52H x 30W x 14½D cm

P&P NSW \$3.00, SA, V. Q \$4.00  
TAS, NT, WA \$5.50

### C-CORE TRANSFORMERS

PRIMARY 240V, 50Hz CONT. RATING  
LOW NOISE • HIGH EFFICIENCY •

• ALL THE ONE PRICE •



MODEL	SEC.V.	AMPS	
JT 266	0-18V	8A	<b>\$26.95 ea</b>
JT 235	26-0-26V	2A	Pack and Post NSW \$2.95;
JT 248	0-10V	10A	V. Q. SA. T. \$3.75
JT 249	8.5-0-8.5V	4A	WA. NT \$5.50
	& 15VCT	1A	JT320 36-0-36V 2A
JT 274	0-9.5V	10A	
	& 2x0-12V	1A	

### DOUBLE C-CORE TRANSFORMER — HEAVY DUTY

PRIMARY 240VAC 50Hz  
SECONDARY 0-18V; 12.5A cont. 30A PEAK.

**\$49.95** PP NSW \$4.50; V. Q. SA. T. \$6; WA. NT \$7.50.

### HEAVY DUTY NI-CAD RECHARGEABLE BATTERIES STANDARD TORCH SIZES

SIZE	AH	PRICE	ea pp
D	4	\$6.55	75c
C	2	\$5.00	75c
C	1.8	\$4.50	75c
Sub C	1.2	\$3.95	75c

1.2v



FAMOUS BRANDS  
Top quality guaranteed.  
Used by many Govt Depts

• BULK BUY AND SAVE •

SIZE D 4 for ..... \$25  
SIZE C 1.8AH 4 for ..... \$16  
SIZE C 2.AH 4 for ..... \$18.50  
Sub C 1.2AH 4 for ..... \$14.80

SIZE AA .5AH 10 for ..... \$17.75

PP NSW \$1.75 INTERSTATE \$3.60

### BLOWER MOTOR •

By Plannair Ltd to Admiralty specs.  
115/230VAC, 50/60 Hz 1PH fully  
sealed.

### AXAIL FLOW 60CFM

Size 210 x 115mm mounting flange  
each end. Mechanically quite ideal for  
high power elect gear, home,  
workshop, factory.

**\$17.50** PP NSW \$2.50  
V. SA. Q. T. \$4  
WA. NT. \$5

### ! COOL IT !

### CEILING FAN MOTOR \$14.50

200-240VAC 50Hz,  
3 types  
55 watt for 36" blades  
75 watt for 48" blades  
90 watt for 56" blades



### SPEED CONTROLLER INCLUDED

PP NSW \$4.50; V. SA, T, Q \$6.50  
WA, NT \$7.50

### EMITAPE

816-2400N EMI PROFESSIONAL  
RECORDING TAPE

¼" x  
2400FT



10½"  
Metal  
Spool

**\$17.50** PP NSW \$1.50  
Interstate \$2.50

LIMITED STOCK

### ALARM SIREN •

12VDC WARBLER TONE 100dB/1M  
8 watts output  
indoor/outdoor  
for home, car,  
boat, caravan etc

**\$18.50**  
P&P NSW \$1.50; INTERSTATE  
\$2.50


### GEARED MOTOR 240VAC 50Hz 3W \$2.50

P&P 50c  
5 RPM Plenty of torque With Cam and  
N/O N/C microswitch 15 switch  
contacts per min OA size 65 x 60 x  
35mm  
Refer Dec 79 EA New Products  
Review


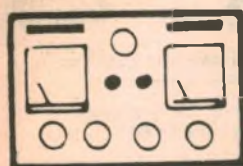
### SERVICE

Moderate charges — Repairs  
guaranteed. Radios, Tape Re-  
corders, Cassettes, Amps.



# The Serviceman

## Bolts and washers can drive a serviceman nuts!

Intermittent faults in TV sets and other domestic appliances have a high nuisance value, and can often prove expensive, but have you ever considered the effect of similar faults in professional computers? And if you imagine that these elite devices are above that sort of thing, you have another think coming.

This is not a story from my own workbench, but comes from one of my regular readers – “from the early days of Radio and Hobbies” – who is now a Senior Technical Officer (electronics) in charge of computers in a large research establishment. He is Mr B. J. of Victoria, and this is how he tells it. I quote:

This story is written to show that multi-thousand dollar computer installations are just as prone to curly faults, originating from poor quality control, as are their cheaper domestic cousins such as the colour TV sets, etc.

As a senior technical officer in charge of a large research laboratory it is part of my function to maintain a large computer system which handles real-time data from several medically orientated research units. As the real-time data is the result of weeks of experimental preparation, and is quite often not repeatable, breakdowns of any kind are bad news. But intermittent faults, involving repeated crashing of the system, are a prescription for instant ulcers!

This particularly applies in our situation as, due to the high cost of contract servicing, we opted to do all our own maintenance. Looking back six years to those first couple of years when our theoretical knowledge was good (due to in-house courses run by the computer manufacturer) but our practical knowledge of the system was zero, I wonder how we survived – particularly when we encountered the type of fault I am about to describe.

There is one law of electronics that I have discovered after 25 years of fixing all forms of devices, from radios to computers, and it is not found in any text book. It is that electronic devices, if they break down in their warranty period, invariably develop intermittent faults. Moreover, the fault magically disappears when the service technician walks

through the door, to reappear a year later when the warranty has expired!

Our system followed this pattern religiously with several mysterious crashes during the warranty period. Upon restarting, the system would run perfectly. No fault would be found by the service representative, who would run all the appropriate diagnostics, drink our coffee, and disappear.


This sort of fault in a large system is a servicing nightmare; it can be anything from a glitch in a power supply – of which there are a dozen or so – to a memory or CPU fault. As the system works perfectly when restarted, and the fault that caused it might have lasted for only microseconds, finding and repairing it usually involved a series of inspired guesses and sheer hard work.

It was late one week when our programmer came to tell me that the system had crashed again. I gave a groan, thinking that it was going to be

the usual tale of chasing a phantom, but the programmer almost cheerfully told me that as he was standing in front of the computer all the panel lights on one disk unit lit up to twice their normal brightness before expiring. At the same time a small cloud of smoke came out of the cabinet, and he made even time to the power switch to shut the system down.

I spent the next hour stripping all the metalwork off the disk unit and giving it a close visual inspection. Nothing was immediately obvious and all the fuses were still intact, so setting up a DVM to take some voltage readings, I asked the programmer to switch the system on and to be ready to switch it off quickly if needed. On these particular disk units all the power supply leads emerge from a common point, which makes voltage checking easy, and a quick run around the various pins confirmed what I already suspected; that the –15V supply which, among other things, supplied the voltage for the front panel lights, was non-existent.

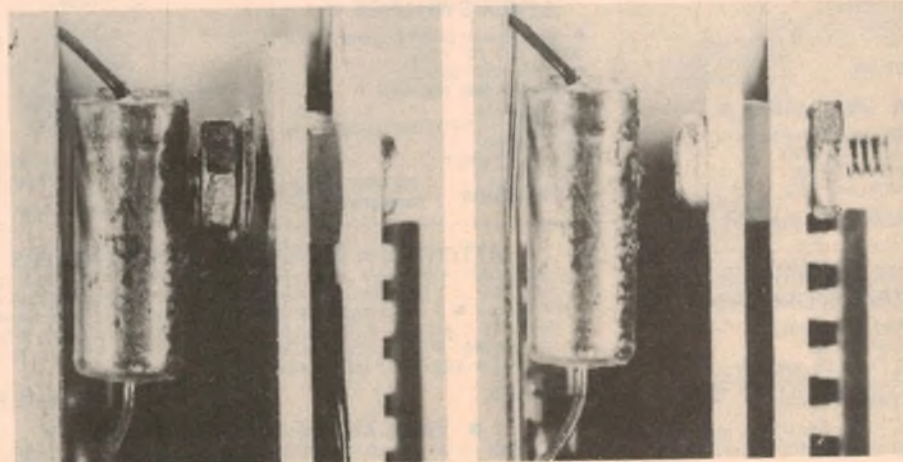As the lights were so bright before failing, I had the unhappy prospect that the supply had failed in a catastrophic manner and applied the full unregulated voltage to the –15V rail. This thought



An intermittent fault, before and after. On the left, an assembly bolt has bitten into the body of an electrolytic capacitor, with a loose washer to provide an intermittent path to the copper pattern. On the right, as the bolt should have been.

did not fill me with a lot of joy, as the -15V supply ran to dozens of amps and transistors scattered over several boards, and the possibility of damage to some of these was extremely high.

Putting an ohmmeter across the rail showed a dead short to earth. Fortunately, on this model disk store, all the logic and servo control boards can be unplugged, so I promptly yanked the whole lot. The short remained - which didn't surprise me, as the power supply was left in circuit.

The power supply is a fairly standard circuit consisting of a series transistor and associated voltage reference circuitry, with a full wave rectifier and meaty transformer supplying it. The one surprising feature for a supply in equipment of this price is the fact that it has no over-voltage protection - creating a potentially disastrous situation.

## SUPPLY, A MESS!

Some quick checks confirmed that the supply was a real mess. The bridge rectifier and series regulator transistor were both shorted and several tracks on the printed circuit board were melted and charred, which explained the smoke. The next day was spent rebuilding the supply and then, with the -15V rail disconnected, checking to see if it gave the correct voltage when switched on.

Now came the hard part; finding the reason for the failure in the first place, which I suspected was a dead short on the -15V rail. This was not easy as the over-voltage could have shorted out a dozen components which would mask the original short.

There was nothing for it but to laboriously pull boards and isolate blocks of the circuit and that's what I did, finding in the process several shorted components. It was when I reached the last two boards that I found the reason for all my troubles and also the cause of the intermittent crashes.

The last two boards consisted of the head amp board and the main servo control board. As soon as I moved the servo board the ohmmeter, which I had permanently connected across the -15V rail, showed that the short had gone. Wiggling the board a bit more caused the short to reappear.

It did not take very long before all lay revealed. As intermittent faults go, it was the most unusual one I have struck and in nature was very much like a time bomb that had been built in at manufacture.

The photographs show how the two boards are mounted vertically, with the servo board on the left and the head amp board on the right. The head amp actually involves two boards; the head amp board proper and a ground-plane board bolted to it. The metal ground-plane faces the adjacent servo board.

During the manufacture one of the bolts had been inserted the wrong way,

leaving the sharp end of the bolt protruding. If it had been any of the other three bolts it would not have mattered, but the end of this particular bolt happened to be opposite the body of an electrolytic capacitor decoupling the -15V supply to the servo board. This meant that when the head board was inserted the bolt end gouged into the body of the capacitor (see photo), raising the bolt to -15 volts.

The really interesting part of the fault is yet to come. As well as being inserted the wrong way, the nut on the bolt had obviously not been tightened and the washer underneath the nut was free to move along the bolt, although constrained to some extent by the roughness of the threads.

The bolt head was anchored against an etched section of the board, so there was no path to earth there. Similarly, the body of the bolt was smaller in diameter than the hole drilled through the earthed backplane, so no short occurred here.

It was the washer that was the time fuse. It must have been at the nut end during initial testing and for the first few months of service in our labs. Vibration from the disk unit eventually shook it the fraction of a millimetre required to form a bridge between the earthed ground-plane and the bolt at -15 volts.

The intermittent crashes had obviously been caused by the washer touching the groundplane for a few milliseconds and the resulting glitch in the -15V supply crashing the disk. Eventually the washer must have touched solidly and welded onto the groundplane, causing the havoc previously described.

Reversing the bolt and plugging the boards back in was all that was needed to finish the repair. All told, this fault had caused a multi-thousand dollar computer installation to be down for several days with the result that a whole research unit had ground to a halt, all because somebody on an assembly line had reversed the installation of a 1-cent bolt.

## IN RETROSPECT . . .

Well, that's Mr B.J.'s story and I must confess to being just as shocked as he obviously was to find such an example of quality control - or lack of it! - in a piece of equipment of this standing.

After all, we have been conditioned to believe that these devices are only one small step behind the ultimate in man's achievement; space hardware. Which reminds me of what one of the astronauts was reputed to have replied, when asked what he thought about while sitting on top of a rocket waiting to be blasted into space.

"I think," he said, "about the hundreds of thousands of individual components on which a successful launch depends - all supplied by the lowest bidder!"

In a lighter vein, here is a rather unusual technical problem my amateur friend presented to me recently. It in-

**CQ electronics**  
and get your components  
SHOP 9 TOWN CENTRE 95 REGENT STREET  
30 CAMPBELL STREET CENTRAL RAILWAY  
blacktown. Sydney.  
621 5809 698 8079

## SCHOOLS, MANUFACTURERS, RETAILERS

Note we have a large stocks of the following items.

### SLIDE POTS

#### SINGLE GANG 45mm

50k LOG	}	ONLY \$15.00/100
2k LIN		
10k LIN		
100k LIN		

#### DUAL GANG

5k LIN A	}	ONLY \$20.00/100
100k LIN B		
250k LIN B		
500k LIN B		
2M LOG (200K TAP)		

### CERAMIC CAPACITORS

12pF - V	}	ONLY \$2.00/100
15pF - V		
100pF - 500V		
220pF - 1KV		
270pF - 500V		
330pF - 1KV		
470pF - 2KV		
680pF - 3KV		
1000pF - 50V		
.02mF - 500V		

### TRANSISTORS

SE 7055 (BF 336) CRT DRIVERS  
ONLY \$20.00/100

### WIRE

1000M rolls of 1/.061"  
ONLY \$20.00 PER ROLL  
Limited colours and stocks left.  
P&P extra \$2.00 per roll.

### PLASTIC PRINTED CIRCUIT BOARD PILLARS

3mm 0 x 10mm separation  
ONLY \$3.00/100

### ALLIGATOR CLIPS

Black & Red. App. 40mm long  
ONLY \$7.00/100

### PLASTIC TRANSISTOR COVERS

For TO 3 type transistors  
ONLY \$12.00/100

### LAMPS

6.3V 200mA fly leads  
ONLY \$3.00/100

### CASTORS FOR SPEAKERS ETC

40mm dia. ball type sets of 4  
25 sets for \$100.00

### CERAMIC INSULATOR BEADS

3mm dia x 6mm long  
ONLY \$1.00/100

### ELECTROLYTIC CAPACITORS

100MF 250V PC type Siemens Brand  
only \$20.00/100

### FREE CHUCK WITH EVERY


EMCO - UNIMAT 3 LATHE

ONLY \$450.00 P&P EXTRA \$10.00

Capacitors and resistors, integrated circuits,  
Wires and cables, semiconductors, fuses, knobs,  
Radio and TV valves, plugs and sockets, pots,  
Manufacturers of PC boards and disco lighting.  
Prices subject to change without notice.  
Back and postage within Australia \$100  
02-621 5809 CQ ELECTRONICS  
30 CAMPBELL ST  
BLACKTOWN 2148  
WRITE

# MAINSCAP

**250v  
A.C.**

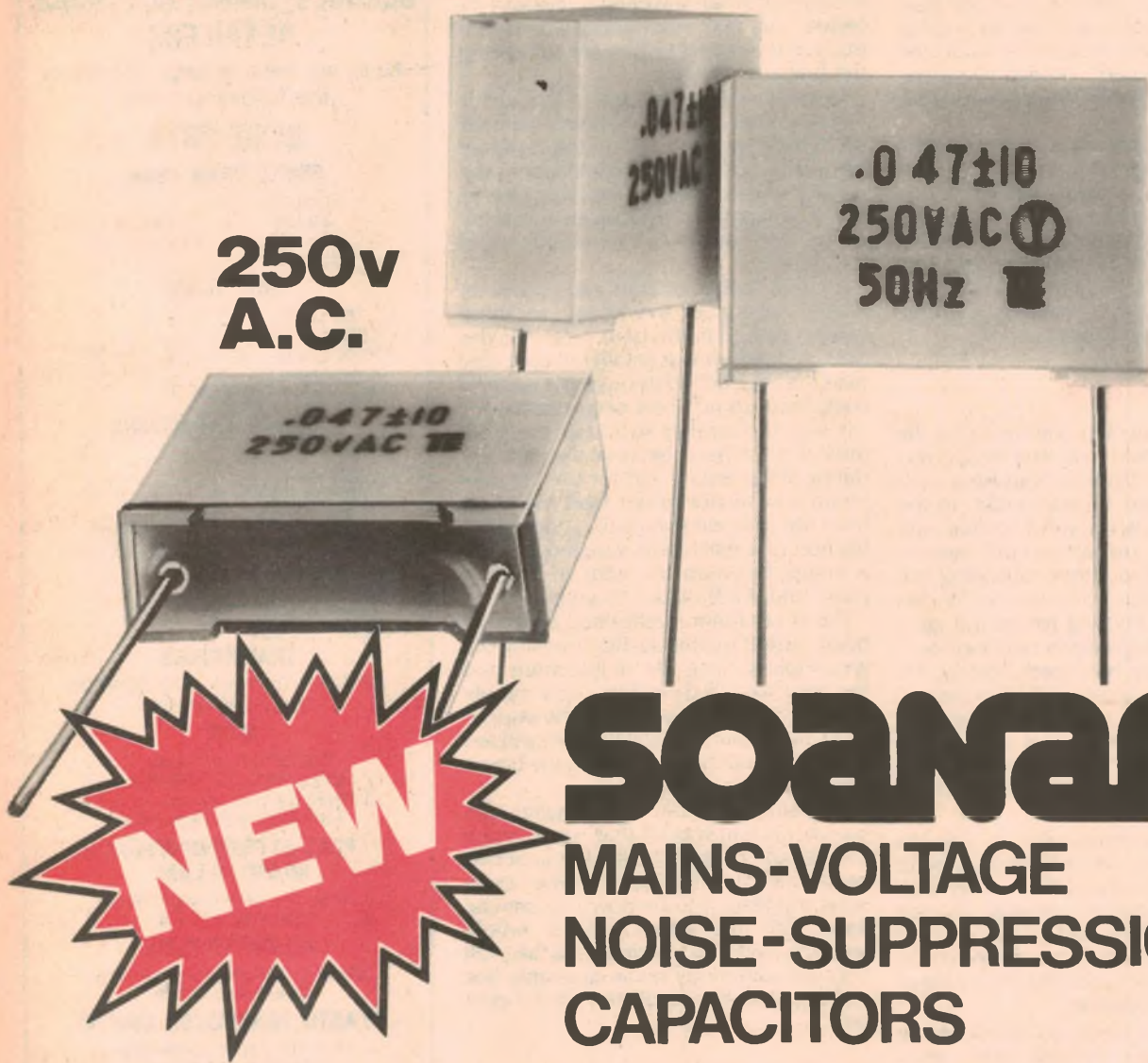

**NEW**

## **SOANAR** MAINS-VOLTAGE NOISE-SUPPRESSION CAPACITORS

Specifically designed for noise suppression in 250V AC circuits these capacitors have been approved by the NSW energy authority to Australian standards C100-1972, and C3145-1979 (CS1630N) for class Y applications.

Using metallised Polyethylene Terephthalate film and fully encapsulated in epoxy resin the mainscap is completely sealed against moisture and humidity ingress and has self-healing characteristics for pulse operations.

- **ELECTRICALLY APPROVED**
- **IMMEDIATE AVAILABILITY**
- **HIGHEST STANDARD**
- **LOWEST PRICE**

**STOCK RANGE**  $\pm$  10% tolerance.

250V 50HZ working

Capacitance .01, .022, .033, .047, .1, .22, .47  $\mu$ F.

Other values, flying leads and delta configurations are available on an indent basis.

**CALL US. WE CAN SAVE YOU A MINT**



## **SOANAR**

**Soanar Electronics Pty Ltd**

A member of the A & R Soanar Electronics Group  
30 Lexton Road, Box Hill, Vic., 3128. Australia

VICTORIA: 89 0661

QUEENSLAND: 52 5421

N.S.W. 789 6733

WEST. AUST. 381 9522

STH. AUST: 51 6981

TASMANIA: 31 6533

volved a typical low-cost 5W, 27MHz transceiver, which he had been modifying for 28MHz on behalf of his local WICEN group. (Refer March 1980 notes.)

He walked into my shop late one afternoon, dumped the aforementioned piece of equipment on the counter and, looking me straight in the eye announced, deadpan, "This has a microphonic valve in it." Now he is one of the old school, who is more at home with valves than with solid-state devices, but the expression on his face told me that this was no slip of the tongue; he was deliberately baiting me.

"What do you mean, a microphonic valve?"

"Well, that's the only way I can describe it. It's just like a microphonic valve, and I thought you might like to see it. You might even like to pass it on to that Serviceman bloke."

That was another dig, because he knows full well that I write these notes, but I decided to humour him. After all, there could be a story in it. So we took it into the workshop, hooked it up to a power supply and switched on. Nothing much happened, except the speaker gave forth the usual background hiss.

My friend leaned over and tapped the top of the case gently with his knuckle. "Boing" said the speaker.

build up again. In a few seconds the whole thing had taken off, and was wailing like a PA system run amok.

Suddenly my friend wasn't looking so smug anymore. "Crikey, it's never been as bad as that before." Like me, he was obviously beginning to worry that the output transistors might be damaged by such a gross overload and he reached for the volume control/on-off switch. To our mutual surprise, turning the volume down did nothing to stop the racket; only the switch had any effect.

By now, of course, I was hooked; I just had to find out what was wrong. I removed the top cover and found myself looking at the component side of a printed board. Armed with the butt end of an alignment tool, I switched on again and tapped the board gently. Everything happened as before, except that it all seemed to be that much more sensitive.

I had hoped that, by decreasing the vigour of my tapping, I would eventually find which part of the board was most sensitive, thus pinpointing the general area, at least. But it was hopeless; every part of the board seemed equally sensitive and I eventually gave up.

As an alternative, I tried exerting gentle pressure on each component, pushing it this way and that, hoping that I might find a dry joint or something similar. I didn't seem to be getting anywhere this way either, until I pushed the top end of a vertically mounted resistor. The speaker gave a pronounced click as I did so and, when I tapped the board again, the microphoney had vanished.


Taking a closer look at the board, I could see what had happened. The resistor was mounted hard alongside a vertically mounted trim pot and one, or both, had been bent slightly towards the other. As a result, the bare pigtail from the top of the resistor had been resting gently against the carbon track of the pot.

The set-up must have been very similar to the crude carbon microphones I used to make as a youngster; a carbon rod, from a discarded dry cell, was sharpened at both ends and supported between two more rods, vertically mounted, with recesses drilled to take the pointed ends.

Elaborate claims were made for such devices, including one that would enable you to hear an ant walking! All I can say is that the ants in my backyard must have worn rubber soled shoes because, even when I managed to coax one or two on to the sounding board of the device, I never detected any footsteps.

In fact, the devices were so touchy as to be almost useless in any role, including the reproduction of speech. Still we had a lot of fun building them.

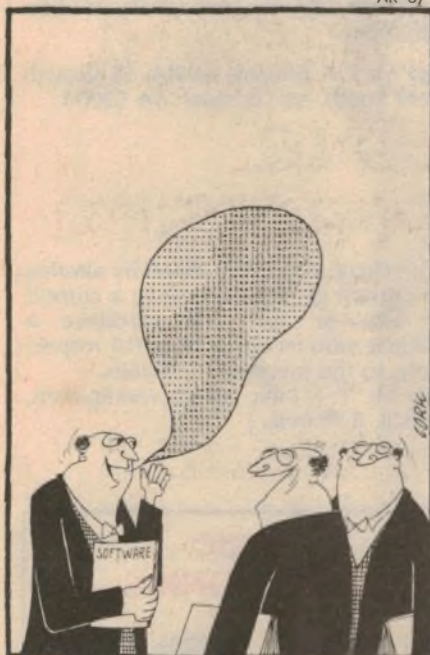But, come to think of it, my friend's "microphonic valve" might just have been sensitive enough to pick up Archie Ant's fairy footsteps.



"There," said my friend smugly, "what's that if it isn't a microphonic valve?" And I had to admit that that was exactly what it sounded like.

"Try the channel selector switch."

I did, clicking the switch through several positions. "Boing, boing, boing-gggg" went the speaker, with the last "boing" showing a marked reluctance to die away. In fact it didn't, but started to

**NEW RELEASE**

**GW TEST EQUIPMENT**



**GOS-955**  
**130mm**  
**Oscilloscope**

Bandwidth — DC - 6.5 MHz  
Sensitivity — mV/div.  
Sweep Frequency — 10HZ to 100KZ in 4 ranges.  
Calibration — 50MVP-P 1KHZ square wave.  
**\$275.00**



**GAG 808A**  
**Sine & Square Wave**

Frequency Range: 10HZ - 1MHZ  
Frequency Accuracy ± (3% + 1HZ)  
Distortion — less than 1%  
(Sine Wave 400HZ to 20KHZ)  
**\$189.00**



**GVT-706A**  
**High Sensitivity**  
**AC Millivolt Meter**

RMS Scale — IMV — 300V in 12 ranges  
DBM Scale — 60DBN + 50DB in 12 ranges  
Frequency — input impedance — 1Meg  
**\$169.00**

**R. F. Attenuators**



<b>GAT 069</b> 0-69DB in 6 steps 0-250MHz <b>\$69.50</b>	<b>GAT 872</b> 0-72DB in 8 steps 0-250MHz <b>\$74.50</b>
---	---

**DISTRIBUTED BY:**



**RADIO PARTS GROUP**

562 Spencer St,  
West Melbourne  
(03) 329 7888

1103 Dandenong Road,  
East Malvern  
(03) 211 8122



# CIRCUIT & DESIGN IDEAS


We invite readers to submit circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. Sources of material must be acknowledged and will be paid for if used. As these items have not necessarily been tested in our laboratory, responsibility cannot be accepted.

## Auto-start for 12-230V AC inverter

Where the output of an inverter is to be used some distance from the battery and inverter, there is the problem of the "no load" current. This is a particular problem with intermittent use. The circuit shown is an addition I have made to the 12-230V Inverter as described in February, 1979. The circuit has been devised so that the inverter will only operate when a load is switched across the AC output. The idea could be useful in low energy solar powered installations where the inverter may make AC available at several locations.

The AC terminals of the bridge rectifiers are connected to the circuit, whereas the DC terminals are short-circuited, to form AC zeners. A bias is then developed across bridge "B" through a 22k resistor from the 12V supply. When a load is switched across the AC output, this bias is fed round via the transformer winding and diode, to the base of the BC108. This is sufficient to turn on the BC108 and pull in the relay.

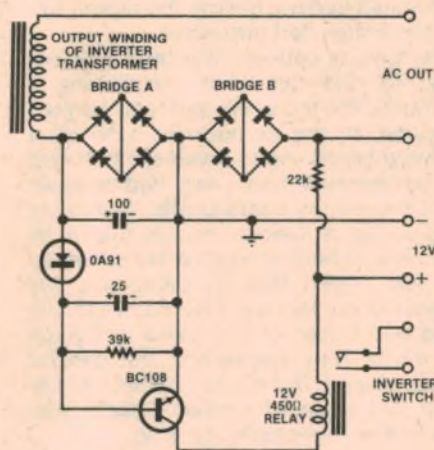The 100 $\mu$ F capacitor cancels the effective capacitance of long AC lines and



prevents "lock on". The 25 $\mu$ F capacitor prevents the relay from chattering and dropping out as the inverter starts. The diode is necessary as the AC component tends to take over the hold in once the inverter starts. The full load power loss through the two bridges is about 1%. There is a fraction of a second delay in


the start and stop but this is no problem. The standing current is under 1mA.

The relay contacts must be heavy enough with a self-oscillating type of circuit to break the main 12V supply. Otherwise, the rest of the components are not critical and may be substituted for similar types. The diode should be germanium as this will pass on more of the available bias. The bridge rectifiers need to carry the maximum output current of the inverter but they can be low voltage types as they are not seeing any high voltage peaks. The neutral end of the output transformer is not directly earthed but it is connected to earth via bridge "A". There is only a little over one volt difference between the two points, so this should not be a problem.

I have built the 12-230V Inverter, as well as several self-oscillating ones and this circuit has been successfully used on both types.

(By Mr J. A. Sheard, VK5JA, 53 Crouch Street South, Mt Gambier, SA 5290.)
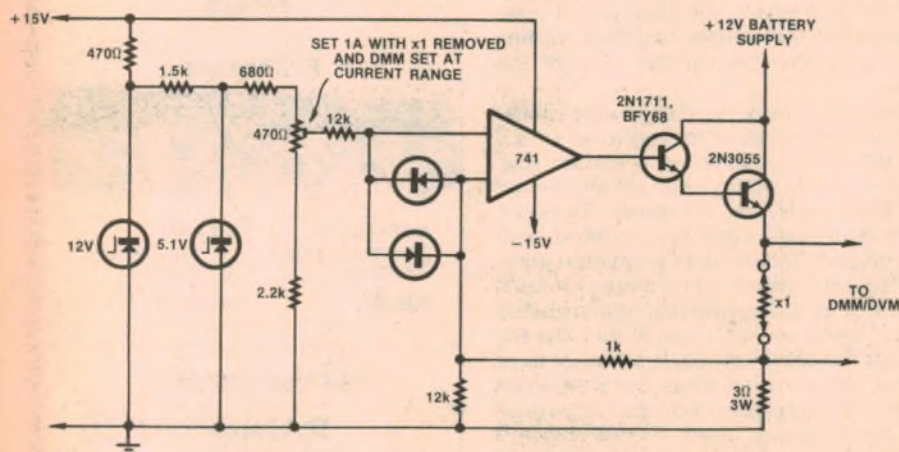
## Add milliohms measurement to your digital multimeter



Most digital voltmeters and digital multimeters do not incorporate a milliohms range in their design. This circuit attachment extends the range of any DVM or DMM to measure low resistance, such as RF chokes of transmitters, motor and transformer windings

etc, without any modifications to the instrument itself.

The circuit basically is a constant current generator of 1A. The voltage across the unknown resistance measured in millivolts can therefore be read as milliohms directly.

The circuit can be modified by altering the current generator to drive a current of 0.1A or 10A and introduce a multiplication factor of 10 or 0.1 respectively, to the measured millivolts.

[By Mr. T. J. John, B-15/6, Modipuram, Meerut. (UP) India.]

## BASIC ELECTRONICS

Basic Electronics begins with the electron, introduces and explains components and circuit concepts, and progresses through radio, audio techniques, servicing, test instruments, etc.

Available from:  
"Electronics Australia", 57 Regent St, Sydney.  
PRICE \$3.50 OR by mail order from  
"Electronics Australia", PO Box 163,  
Beaconsfield 2014. PRICE \$4.20.



# Minispot 455kHz signal generator

Basic  
Electronics



Here is a handy little device for broadcast and shortwave receiver alignment. It is the Minispot. It generates a fixed 455kHz RF signal modulated at 500Hz.

by JOHN CLARKE

A problem which many enthusiasts encounter is that, having completed building a broadcast or shortwave receiver, they have no equipment to provide accurate IF alignment.

Very poor performance can result from lack of, or inaccurate alignment, but, on the other hand, the experimenter who makes only a few projects may hesitate to invest a lot of money, or time, in acquiring a full size service oscillator or signal generator.

Alignment of IF systems is aimed at satisfying two requirements: (a) ensuring that all tuned circuits in the IF systems are tuned to the same frequency and (b) that the frequency to which they are tuned is the correct one.

Failure to satisfy requirement (a) will result in degraded sensitivity and selectivity. Failure to satisfy (b) can result in spurious heterodynes or whistles in certain localities, as well as failure of the tuning system to track accurately with the dial calibrations, particularly in the centre of the dial.

The simplest approach to receiver alignment is "by ear." Using broadcast signals at appropriate positions on the band, the various tuned circuits are adjusted to produce maximum output from the loudspeaker.

While this approach has the advantage of simplicity and will undoubtedly result

in some improvement, it leaves a lot to be desired.

It cannot ensure that the IF system's tuned circuits are tuned to a specific frequency, only that they are all tuned to approximately the same frequency. This is only approximate, because we are depending on the ear to tell us when the maximum signal level has been reached.

The ear is notoriously insensitive to small changes in signal level (less than 3dB) so that each adjustment could conceivably be in error by, say, 2dB. If there are six adjustments to make there is room for a possible total error of 12dB — a very significant amount. While the error will usually be less than this in practice, it may still be significant.

The more usual approach calls for the use of an oscillator (or signal generator) and an output meter. The generator should be capable of generating RF signals, suitably modulated, at the IF used by the receiver, at frequencies at each end of the broadcast band, and in similar positions on the short-wave band or bands, where these are featured.

In use, the generator is connected so as to feed signals into the appropriate part of the receiver, while the output meter is connected to the output circuit feeding the loudspeaker.

The generator is modulated with a steady tone — rather than music or

speech as from a broadcast station — and this is registered as a fixed level on the output meter. As various adjustments are optimised (peaked), the meter will swing up the scale to maximum reading, giving a far more accurate indication than can the ear.

While most multimeters can serve as an output meter, it is the generator which most experimenters find hard to provide. Indeed, a generator to satisfy all the requirements we have just enumerated would be a relatively costly instrument.

However, if we accept the compromise that the IF system is the one most needing adjustment by this method, and that the other adjustments can be made "by ear" without serious error, then a very much simpler and cheaper device will serve our purpose.

More precisely, we can settle for a simple, low cost, single frequency oscillator, preset to the popular 455kHz IF, and intended to do no more than provide alignment facilities for the IF channel.

Rather than implementing the oscillator with an LC circuit, a very good alternative is to use a ceramic filter element. This provides a cheap and reliable alternative 455kHz oscillator when used in the feedback loop of a high frequency amplifier. The stability of this arrangement is close to that of a crystal based oscillator but without the additional associated cost.

Considering the comparative cost and the inherent stability, we feel sure that the alignment generator described here would be a worthwhile device to have. It will fill the need for an inexpensive but reliable source of modulated 455kHz signal suitable for IF alignment of broadcast and shortwave receivers.

*The PC board should be housed in a metal case to prevent stray radiation.*



We estimate that the current cost of components for this project including battery and suitable case is

**\$9.00**

This includes sales tax.

The circuit is also quite easy to modulate. The modulating tone is generated by a free-running bistable multivibrator operating in the vicinity of 500Hz.

It modulates the RF oscillator by varying the supply voltage fed from the junction of the two resistors forming the collector load of one of the multivibrator transistors. The two resistors function as a voltage divider to control the depth of modulation.

As can be seen, the Minispot circuit is quite simple and consists of three low cost transistors, seven resistors, six capacitors and the ceramic filter. Two of these transistors are used in the multivibrator and the other in the 455kHz oscillator. The two capacitors in series with the ceramic filter set the frequency to close to 455kHz. AC coupling is provided for the RF output by way of a

## PARTS LIST

- 1 PC board coded 80if12, 67 x 39mm
- 1 metal case to suit
- 1 9V, 216 battery
- 1 clip connector to suit battery
- 1 RCA panel socket
- 1 RCA plug
- 1 Murata type SFB455A ceramic filter

### SEMICONDUCTORS

- 3 BC548 NPN transistors

### RESISTORS (1/4W 10%)

- 1 x 100k, 2 x 47k, 1 x 3.3k, 1 x 1.5k,
- 1 x 1k, 1 x 470 ohms

### CAPACITORS

- 1 0.22uF metallised polyester
- 2 .047uF metallised polyester
- 2 68pF NPO ceramic disc
- 1 27pF ceramic disc

*NOTE: Ratings are those used on the prototype. Components with higher ratings may be used providing they are physically compatible.*

27pF capacitor.

Construction of the Minispot is relatively simple and could be finished within an hour or so. Start by mounting the components on the printed circuit board coded 80if12 and measuring 67 x 39mm. No particular order is necessary in placing the components.

No problems should be encountered in housing the device. A metal housing must be used, however, to prevent direct radiation from the multivibrator coupling into the audio stages of a receiver.

Any small metal box can be used, such as a general purpose aluminium box measuring 100 x 30 x 54mm (W x H x D) or larger or a box can be fashioned from some scrap aluminium or tin plate.

## One-Second Desoldering

# with SODER-WICK



1. Hold Soder-Wick on termination with hot soldering tip. Wicking action soaks up solder.

2. Remove tip and braid. Termination is left clean and free of solder.



Soder-Wick is a specially treated copper braid which soaks up molten solder like a sponge. Desolders a P.C. pad in a second or so: acts as a heat sink to protect circuits and components.

*From your Components supplier or ring:*

### Royston Electronics

(02) 709 5293 (07) 391 8011  
 (03) 543 5122 (08) 42 6655  
 (002) 34 2233 (09) 381 5500

SW-3


## AMPLIFIED ANTENNA FOR VHF-UHF-TELEVISION-FM-AM-RADIO

### TC 10

10 element\*. For use in primary reception areas.


	FG(dB)	FB(dB)	AA(Degrees)
TC10/B4	To be advised when frequencies allocated.		
TC10/B5	10.6	24.1	20

### MARINE TV ANTENNAS

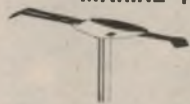

Ultra compact 82-channel TV antennas provide perfect colour and black and white reception in most viewing areas.

Sensor antennas have elegant modern styling which blends with the decor of any home setting. Compact unobtrusive design makes it ideal for homes, camper trailers, mobile homes, cruisers, houseboats and yachts.



## ELECTROCRAFT, PTY LTD

68 Whiting Street, Artarmon NSW. Telephone 438-4308 ext. 6 or 438-3266 ext. 6  
 30 years in the antenna business. Hours: 8am to 5pm  
**PRICES SUBJECT TO ALTERATION WITHOUT NOTICE.**  
**WE ARE SPECIALISTS OFF STREET PARKING**

# If you program microprocessors, these sheets are for you

Writing microprocessor programs on blank or plain ruled paper is messy and time consuming. To make the job easier, Electronics Australia has produced these custom-designed programming sheets for use with virtually any microprocessor system. The sheets feature columns for a 4-digit address, up to six digits of instruction code or data, labels, mnemonics, and comments. There is space for 46 lines per sheet, and the sheets are provided with space for program title, date and sheet number. They are also punched for filing in a standard ring binder. All for less than 5 cents per sheet, posted!

**PRICED AT \$2.00 FOR 50 SHEETS**  
**(plus 40c for postage anywhere in Australia for as long as stocks last)**

Available only from Electronics Australia,  
 57 Regent St., Sydney (P.O. Box 163, Beaconsfield, NSW 2014)




# A pro doesn't wrestle on stage.



We've all seen the artist who seems to spend half his time on stage wrestling with the mike stand adjustment. It doesn't look good. And it doesn't make for a good performance, either.

The problem is that a lot of stands are only fit for growing peas. A really good stand—one of Cunningham's—is precision built with fast, sure-grip adjustment clamps. It's solidly based, sturdily built to take the punishment of roadwork or hasty studio changes.

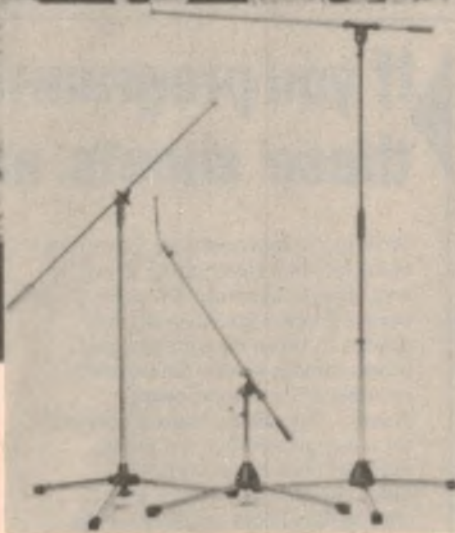The boom arms stay where they're put, and the whole stand collapses down to the minimum possible space.



CUNNINGHAM MICROPHONE STANDS

R. H. Cunningham import some of the world's finest audio products—like Sennheiser microphones and headphones; radio mikes; voice synthesiser; loudspeakers—and more. Post this coupon for our Professional Audio Products Catalogue—free.

Name .....

Address .....

Are you a Musician/Engineer/ Educator/  
Broadcaster/ Hi Fi Enthusiast/Other:

B&B/RH135/EA

From Germany, Cunningham bring you stands for every kind of use. And they have every conceivable accessory—all the way to a clip-on ashtray.

If you take your music seriously, you've got to look into the Cunningham stands. Sure they cost more than the amateur-hour stands. But then your public has paid to see a performance—not a wrestling match.

**R.H. Cunningham**  
PTY.LTD.

Audio equipment for professionals  
146 Roden Street, West Melbourne, 3003.  
4-8 Waters Road, Neutral Bay, N.S.W., 2089.

## Build the Minispot

A small on/off switch should be installed within the box and connected in series with the battery lead. The PC board has provision for two mounting screws on opposite corners and it should be raised from the base with bushes to prevent shorting.

An RCA phono panel socket can provide for the RF output on the case and the output connecting lead made from two pieces of hookup wire soldered into an RCA plug. Connect the opposite ends to alligator clips or probe clips.

Finally the battery can be connected to the PC board with leads and a suitable clip and the circuit is ready to be used.

The Minispot can be used to align the IF amplifier section of receivers equipped with 455kHz IFs, with or without a ferrite antenna.

In the solid state receivers, the most common input point is the base of the mixer, or mixer-oscillator stage. The tuning capacitor should be set for minimum capacitance to avoid any undue loading on the generator signal.

At the mixer input, coupling can be made through a twisted pair of insulated wires, the amount of wire and twisting controlling the capacity (and hence the RF level) between them. The RF level can be reduced by simply unwinding the twisted pair.

In any alignment procedure, the presence of an AGC (Automatic Gain Control) system presents a minor problem.


Virtually all sets are fitted with AGC systems, the purpose being to maintain, as nearly as possible, a constant audio output regardless of whether the received signal is weak or strong. This they do very well (though not perfectly) but, fairly obviously, this action is undesirable during alignment, since it tends to mask the effectiveness of each adjustment as it is made.

Fortunately, most AGC systems are deliberately designed to have a threshold level below which they do not operate (delayed AGC). This is to ensure maximum sensitivity to weak signals.

We can take advantage of this during alignment, by deliberately keeping the input from the generator at the lowest possible level, at the same time keeping the gain of the receiver at the highest level. As various adjustments increase the sensitivity of the receiver, the input should be reduced by a like amount.

Almost any multimeter having the usual AC ranges can be used as an output meter. Connection can be readily made across the loudspeaker terminals.

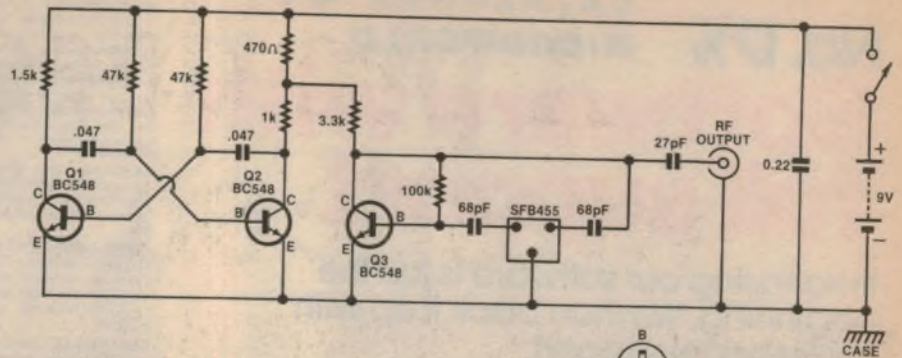With the Minispot connected to the receiver, adjust each IF transformer core for maximum indication on the output meter, reducing the RF input level as





MINISPOT

VIEWED FROM BELOW

710/1-

ABOVE: A multivibrator (Q1 and Q2), an RF amplifier (Q3) and a ceramic filter make up this simple circuit. It generates a 455kHz RF signal modulated at 500Hz.

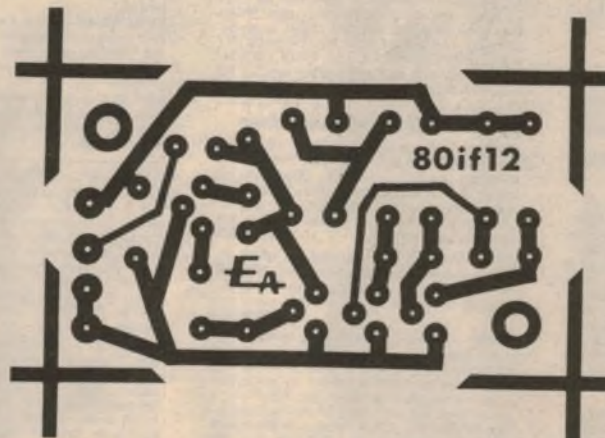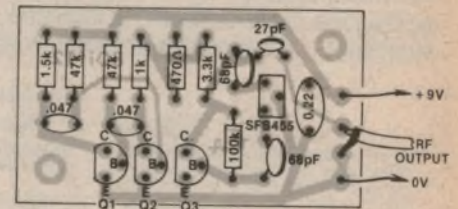RIGHT: This wiring diagram shows the PC board from the component side.



At left is an actual size reproduction of the PC board.

necessary for the reasons outlined previously.

The cores should be adjusted so that their physical positions are at the outside of each coil in the IF transformers, NOT towards the inner area through the coils.

All the foregoing methods of connection have assumed that the user has ready access to any part of the receiver; a situation which would normally apply where a receiver had just been constructed but not yet fitted to its case. However, if we wish to work on a complete receiver, it may not be convenient to remove it from its case.

As already discussed, the output meter can be connected to the loudspeaker terminals, which are generally accessible. However, the input to the mixer stage may not always be so easy to get at, particularly in very small receivers. In this case it is usually possible to feed the signal in through the antenna terminal where fitted, or by coupling to the ferrite rod antenna.

The "Minispot" can be coupled to a ferrite antenna either by laying its output lead across the coil on the rod, or forming an induction loop by connecting the two clips on the output leads together. The lead or loop should be spaced away

from the rod so as to control the output as mentioned earlier.

After peaking the IF transformers, turn off the Minispot. Find a broadcast station at the low end of the dial and adjust the oscillator coil core to place the station at its correct dial position. Tune a station at the top end of the dial and adjust the oscillator trimmer to place it at its correct marking. Repeat the procedure until the two ends are correctly placed.

Find a weak station at the top end of the dial and adjust the aerial trimmer for maximum volume from the speaker. Return to the low end of the dial to a weak station and adjust the position of the coil on the ferrite rod, or the aerial coil's core for maximum audio level. Repeat the procedure until no further change is detected.

As a final note, although the frequency of the Minispot will run close to 455kHz, the operating frequency can be set to an "exact" 455kHz with the aid of a frequency meter. By adjusting the values of the 68pF capacitors in series with the ceramic filter frequency changes can be made. In general, though, without adjustment the Minispot will operate to within 1kHz of 455kHz.

No. 17 1/2

CATALOGUE \$1  
MICROWORLD

# Software with full support

Purchasing our software is just the beginning. We then back it up with professional support:

- Subscription to "LIFELINES" for automatic notifications of revisions!
- Update service for software and documentation!
- Telephone Hotline!
- Overseas software export service!

*Genuine CP/M for Apple II Available now!*

System	Version	Price
CP/M* FLOPPY DISK OPERATING SYSTEM—Digital Research's operating system configured for many popular micro-computers and disk systems.	2 x	349/NA
Apple II*		
SoftCard* with Z80		
Microsoft BASIC version 5 with high resolution graphics		
North Star Single Density	2 x	170/25
North Star Double/Quad	2 x	170/25
Durango F-85	2 x	170/25
iCOM Micro-Disk 2411	1.4	145/25
iCOM 3712 for MITS 88-2510 Console	1.4	170/25*
iCOM 3712 for 3PIS/MITS SIO		
Rev non-zero console	1.4	170/25*
iCOM 3812	1.4	170/25*
iCOM 4511/Perlec D3000	2 x	375/25*
Mis 3202/Altair 8800	1.4	145/25
Heath H8 H17	1.4	145/25
Heath H89	1.4	145/25
Heath H89 by Magnolia	2 x	250/25
Ohio Scientific C3	2 x	200/25
Onyx CB001 Standard	2 x	250/25
Onyx CB001 Enhanced	2 x	330/25
TRS-80 Model I	1.4	145/25
TRS-80 Model II	2 x	250/25
TRS-80 Model III - Corvus Processor Technology Helios II	1.4	145/25
Intel MDS Single Density	2 x	170/25
Intel MDS Double Density	2 x	170/25
Micropolis Mod I	2 x	200/25
Micropolis Mod II	2 x	200/25
Mostek MDX STD Bus System	2 x	350/25**
Ohio Scientific C3-C	2 x	250/25
iCOM 3812	2 x	225/25
iCOM 4511/Perlec D3000	2 x	375/25*

The following configurations are scheduled for release soon:  
North Star Double/Quad Corvus 2 x 250/25  
Ohio Scientific C3-C 2 x 250/25  
iCOM 3812 2 x 225/25  
iCOM 4511/Perlec D3000 2 x 375/25\*

Software consists of the operating system, text editor, assembler, debugger and other utilities for file management and system maintenance. Complete set of Digital Research's documentation and additional implementation notes included. Systems marked \* and \*\* include firmware on 2708 and 2716. Systems marked \* include 5440 media charge. Systems marked \* require the special \* versions of software in this catalog. Includes hardware addition to allow our standard versions of software to run under it.

**Z80 DEVELOPMENT PACKAGE**—Consists of: (1) disk file line editor with global inter and intra-line facilities; (2) Z80 relocating assembler, Zilog/Mostek mnemonics, conditional assembly and cross reference table capabilities; (3) linking loader producing absolute Intel hex disk file. \$95/\$20

**ZDT**—Z80 Monitor Debugger to break and examine registers with standard Zilog/Mostek mnemonic disassembly displays \$35 when ordered with Z80 Development Package \$50/\$10

**AVOCET SYSTEMS**

**XASM-68**—Non-macro cross-assembler with nested conditionals and full range of pseudo operations. Assembles from standard Motorola MC6800 mnemonics to Intel hex \$200/\$25

**XASM-65**—As XASM-68 for MOS Technology MCS-6500 series mnemonics \$200/\$25

**XASM-48**—As XASM-68 for Intel MCS-48 and UPI-41 families \$200/\$25

**XASM-18**—As XASM-68 for RCA 1802 \$200/\$25

**DISTEL**—Disk based disassembler to Intel 8080 or TDL/Xitan Z80 source code, listing and cross reference files. Intel or TDL/Xitan pseudo ops optional. Runs on 8080 \$65/\$10

**DISELOG**—As DISTEL to Zilog/Mostek mnemonic files \$65/\$10

**SMAL/80** Structured Macro Assembler Language—Package of powerful general purpose text macro processor and SMAL structured language compiler. SMAL is an assembler language with IF-THEN-ELSE, LOOP REPEAT-WHILE, DO-END, BEGIN-END constructs. Not compatible with CP/M version 2 or greater \$75/\$15

**PHOENIX SOFTWARE ASSOCIATES**

**PASM\***—Z80 macro assembler, Intel/TDL mnemonics. Generates Intel hex format or relocatable code in either TDL Object Module format or PSA Relocatable Binary Module format. Supports text insertion conditional branching within macros, recursive macro calls and parameter passing \$129/\$25

**EDIT**—Character oriented text file editor. Includes macro definition capabilities. Handles insertion, deletion, searching, block move, etc. for files of any length. Does not require a CRT \$129/\$25

**PLINK\***—Two pass disk-to-disk linkage editor/loader which can produce re-entrant, ROMable code. Can link programs that are larger than available memory for execution targeted on another machine. Full library capabilities. Input can be PSA Relocatable Binary Module, TDL Object Module or Microsoft REL files. Output can be a COM file, Intel hex file, TDL Object Module or PSA Relocatable file \$129/\$25

**BUG\*** and **BUG\***—Z80 interactive machine level debugging tools for program development. BUG has full symbolic trace and interactive assembly (mnemonics compatible with PASM). Dynamic breakpoints and conditional traps while tracing (even through ROM!). muBUG is a subset of BUG and is used in memory limited situations \$129/\$25

**DIGITAL RESEARCH**

**MP/M**—Installed for single density MDS-800 Multi-processing derivative of the CP/M operating system. Manual includes CP/M/MZ documentation \$300/\$50

**MAC**—8080 Macro assembler. Full Intel macro definitions. Pseudo Ops include RPC, IRP, REPT, TITLE, PAGE, and MACLIB. Produces absolute hex output plus symbolic label file for use by SID and ZSID (see below) \$120/\$15

**SID**—8080 Symbolic debugger. Full trace, pass count and breakpoint program testing. Has backtrace and histogram utilities. When used with MAC, provides full symbolic display of memory labels and equated values \$105/\$15

**ZSID**—Z80 Symbolic debugger with all features of SID \$130/\$15

**TEX**—Text output formatter to create paginated page-numbered and justified copy. Output can be directed to printer or disk \$105/\$15

**DESPOOL**—Utility program to permit simultaneous printing from text files while executing other programs \$80/\$10

**tiny C**—Interactive interpretive system for teaching structured programming techniques. Manual includes full source listings \$105/\$50

**BDS C COMPILER**—Supports structures, unions, 2 dimensional arrays, pointers, recursion and overlays. Features optimized code generator, variable sized buffers for file I/O, and capability to produce ROMable code. Includes macro package to enable user to produce linkable modules with MAC (see under Digital Research). Floating point functions, full run-time package and machine code library sources provided. Linker, library manager and textbook included. Compiler lacks initializers, statics, floats and longs \$145/\$25

**WHITESMITHS C COMPILER**—The ultimate in systems software tools. Produces faster code than a pseudo-code Pascal with more extensive facilities. Conforms to the full UNIX Version 7 C language, described by Kernighan and Ritchie, and makes available over 75 functions for performing I/O, string manipulation and storage allocation. Linkable to Microsoft REL files. Requires 60K CP/M \$630/\$30

**MICROSOFT**

**BASIC-80**—Disk Extended BASIC, ANSI compatible with long variable names, WHILE/WEND chaining, variable length file records. MBASIC version 4.51 also included on disk \$325/\$25

**BASIC COMPILER**—Language compatible with BASIC-80 and 3-10 times faster execution. Produces standard Microsoft relocatable binary output. Includes MACRO-80. Also linkable to FORTRAN 80 or COBOL-80 code modules \$350/\$25

**FORTRAN-80**—ANSI 66 (except for COM-PLEx) plus many extensions. Includes relocatable object compiler, linking loader, library with manager. Also includes MACRO-80 (see below) \$425/\$25

**COBOL-80**—Level 1 ANSI '74 standard plus most of Level 2. Full sequential, relative, and indexed file support with variable file names. Powerful interactive, formatted screen handling with ACCEPT and DISPLAY verbs. Program segmentation for execution of programs larger than memory and CHAIN command with parameter passing. Full support of CP/M version 2 files. Includes MACRO-80 (see above), linking loader and relocatable library manager. Requires 48K CP/M \$700/\$25

**MACRO-80**—8080/Z80 Macro Assembler. Intel and Zilog mnemonics supported. Relocatable linkable output. Loader, Library Manager and Cross Reference List utilities \$149/\$15

**XMACRO-86**—8086 cross assembler. All Macro and utility features of MACRO-80 package. Mnemonics slightly modified from Intel ASM86. Compatibility data sheet available \$275/\$25

**EDIT-80**—Very fast random access text editor for text with or without line numbers. Global and intra-line commands supported. File compare utility included \$89/\$15

**PASCAL/M\***—Compiles enhanced Standard Pascal to compressed efficient Pcode. Totally CP/M compatible. Random access files. Both 16 and 32 bit integers. Runtime error recovery. Convenient STRINGS, OTHERWISE clause on CASE. Comprehensive manual (90 pp. indexed). SEGMENT provides overlay structure. IMPORT, EXPORT and untyped files for arbitrary I/O. Requires 56K CP/M. Specify 1) 8080 CP/M, 2) Z80 CP/M or 3) Cromemco CDS \$175/\$20

**PASCAL/Z**—Z80 native code PASCAL compiler. Produces optimized, ROMable re-entrant code. All interfacing to CP/M is through the support library. The package includes compiler, relocating assembler and linker, and source for all library modules. Variant records, strings and direct I/O are supported. Requires 56K CP/M \$395/\$25

**PASCAL/MT**—Subset of standard PASCAL. Generates ROMable 8080 machine code. Symbolic debugger included. Supports interrupt procedures, CP/M file I/O and assembly language interface. Real variables can be BCD, software floating point, or AMD 9511 hardware floating point. Includes strings enumerations and record data types. Manual explains BASIC-PASCAL conversion. Requires 32K \$250/\$30

**APL/V80**—Concise and powerful language for application software development. Complex programming problems are reduced to simple expressions in APL. Features include up to 27K active workspace, shared variables, arrays of up to 8 dimensions, disk workspace and copy object library. The system also supports auxiliary processors for interfacing I/O ports. Requires 48K CP/M and serial APL printing terminal or CRT \$500/\$30

**ALGOL-60**—Powerful block-structured language compiler featuring economical run-time dynamic allocation of memory. Very compact (24K total RAM) system implementing almost all Algol 60 report features plus many powerful extensions including string handling, direct disk address I/O etc. \$199/\$20

**CBASIC-2** Disk Extended BASIC—Non-interactive BASIC with pseudo-code compiler and run-time interpreter. Supports full file control chaining, integer and extended precision variables, etc. Versions of CRUN for CP/M versions 1.4 and 2.x included on disk \$120/\$15

**MICRO FOCUS**

**STANDARD CIS COBOL**—ANSI '74 COBOL standard compiler fully validated by U.S. Navy tests to ANSI level 1. Supports many features to level 2 including dynamic loading of COBOL modules and a full ISAM file facility. Also, program segmentation, interactive debug and powerful interactive extensions to support protected and unprotected CRT screen formatting from COBOL programs used with any dumb terminal \$850/\$50

**FORMS 2**—CRT screen editor. Output is COBOL data descriptions for copying into CIS COBOL programs. Automatically creates a query and update program of indexed files using CRT protected and unprotected screen formats. No programming experience needed. Output program directly compiled by STANDARD CIS COBOL \$200/\$20

**NEVADA COBOL**—Subset of ANSI-74. Features fast compilation and execution with small object modules. Has extended arithmetic with 48 digit accuracy. Extended I/O includes random access files and sequential files of both fixed and variable length records, and interactive accept/display verbs. Good error messages and debugging facilities enhance program development. Requires a 32K CP/M system \$149/\$25

**EIDOS SYSTEMS**

**KBASIC**—Microsoft Disk Extended BASIC version 4.51 integrated with KISS Multi-Keyed Index Sequential and Direct Access file management as 9 additional BASIC commands. KISS included as relocatable modules linkable to FORTRAN-80, COBOL-80, and BASIC COMPILER. Specify CP/M version 1.4 or 2.x when ordering. Requires 48K CP/M \$585/\$45. To licensed users of Microsoft BASIC-80 (MBASIC) \$435/\$45

**XYBASIC** Interactive Process Control BASIC—Full disk BASIC features plus unique commands to handle byte rotate and shift and to test and set bits. Available in several versions:  
Integer ROM squared \$350/\$25  
Integer CP/M \$350/\$25  
Extended ROM squared \$450/\$25  
Extended CP/M \$450/\$25  
Extended Disk CP/M \$550/\$25  
Integer CP/M Run Time Compiler \$350/\$25  
Extended CP/M Run Time Compiler \$450/\$25

**RECLAIM**—A utility to validate media under CP/M. Program tests a diskette or hard disk surface for errors, reserving the imperfections in invisible files, and permitting continued usage of the remainder. Essential for any hard disk. Requires CP/M version 2 \$80/\$5

**BASIC UTILITY DISK**—Consists of: (1) CRUNCH-14—Compacting utility to reduce the size and increase the speed of programs in Microsoft BASIC 4.51, BASIC-80 and TRS-80 BASIC. (2) DPFUN—Double precision subroutines for computing nineteen transcendental functions including square root, natural log, log base 10, sine, arc sine, hyperbolic sine, hyperbolic arc sine, etc. Furnished in source on diskette and documentation \$50/\$35

**STRING/80**—Character string handling plus routines for direct CP/M BIOS calls for FORTRAN and other compatible Microsoft languages. The utility library contains routines that enable programs to chain to a COM file, retrieve command line parameters and search file directories with full wild card facilities. Supplied as linkable modules in Microsoft format \$95/\$20

**STRING/80** source code available separately \$295/NA

**THE STRING BIT**—FORTRAN character string handling. Routines to find, fill, pack, move, separate, concatenate and compare character strings. This package completely eliminates the problems associated with character string handling in FORTRAN. Supplied with source \$65/\$15

**VSORT**—Versatile sort/merge system for fixed length records with fixed or variable length fields. VSORT can be used as a stand-alone package or loaded and called as a subroutine from CBASIC-2. When used as a subroutine, VSORT maximizes the use of buffer space by saving the TPA on disk and restoring it on completion of sorting. Records may be up to 255 bytes long with a maximum of 5 fields. Upper-lower case translation and numeric fields supported \$175/\$20

**CPM/374X**—Has full range of functions to create or re-name an IBM 3741 volume, display directory information and edit the data set contents. Provides full file transfer facilities between 3741 volume data sets and CP/M files \$195/\$10

**System Maintenance**

Diagnostics I	\$60/\$15
Accounting (CBASIC2)	
AP/AR	\$200/\$20
General Ledger	\$200/\$20
Text Processing	
TFS	\$85/\$20
Source listing	\$250
Mailing List	
Super-M-List	\$75/\$10
Utilities	\$50
Programming Languages	
FORTH	\$150/\$25
Tiny pascal	\$85/\$10
Software Security	
I Encode/Decode	\$50/\$15
II Encode/Decode	\$100/\$15
Intercomputer	
Communications	\$110/\$15

**T/MAKER** - Powerful new tool for preparing management reports with tabular data. Makes financial modeling projects easy. Do you want a weekly profitability report? Set up the table and compute. Just change the sales figures for next week and compute. You have a new report! T/MAKER includes a full screen editor for setting up tables which pages left, right, up and down. Compute includes standard arithmetic, percents, exponents, common transcendental functions, averages, maxima, minima, projections, etc. Requires 48K CP/M CBASIC-2. CRT Terminal with addressable cursor positioning. \$275/\$25

**MAGIC WAND** - Word processing system with simple easy to use full screen text editor and powerful print processor. Editor has all standard editing functions including text insert and delete, global search and replace, block move and library files for boiler plate text. Print processor formatting commands include automatic margins, pagination, headings & footings, centered and justified text. Also prints with true proportional spacing, merges with data files for automatic form letters and performs run-time conditional testing for varied output. Requires 32K CP/M and CRT terminal with addressable cursor. \$395/\$40

**ANALYST** - Customized data entry and reporting system. User specifies up to 75 data items per record. Interactive data entry, retrieval, and update facility makes information management easy. Sophisticated report generator provides customized reports using selected records with multiple level breakpoints for summarization. Requires a disk sort utility such as OSORT SUPER-SORT or VSORT. \$250/\$15

**STRUCTURED MICROPROCESSOR PROGRAMMING** - By the authors of SMAL/80. Covers structured programming, the 8080/8085 instruction set and the SMAL/80 language. \$20

**ACCOUNTS PAYABLE & ACCOUNTS RECEIVABLE-CBASIC** book by Osborne/McGraw-Hill. \$20

**GENERAL LEDGER-CBASIC** book by Osborne/McGraw-Hill. \$20

**PAYROLL WITH COST ACCOUNTING-CBASIC** book by Osborne/McGraw-Hill. \$20

**BSTAM** - Utility to link one computer to another also equipped with BSTAM. Allows file transfers at full data speed (no conversion to hex), with CRC block control check for very reliable error detection and automatic retry. We use it! It's great! Full wildcard expansion to send \*.COM, etc. 9600 baud with wire 300 baud with phone connection. Both ends need one Standard and 8 versions can talk to one another. This software requires a knowledge of assembler language for installation. \$150/\$10

**TEXTWRITER III** - Text formatter to justify and paginate letters and other documents. Special features include insertion of text during execution from other disk files or console, permitting recipe documents to be created from linked fragments on other files. Has facilities for sorted index, table of contents and footnote insertions. Ideal for contracts, manuals, etc. Now compatible with Electric Pencil\* and Word-Star\* prepared files. \$125/\$20

**LETTERRIGHT** - Program to create, edit and type letters or other documents. Has facilities to enter, display, delete and move text with good video screen presentation. Integrates with NAD for form letter mailings. \$200/\$25

**MEDITECH PROFESSIONAL ACCOUNTING SYSTEMS:**  
1800 patients on 5 1/4 disk  
8000 patients on 8" disk.  
Developed in Australia  
Statements individual or continuous; receipts;  
RACGP records system;  
management reporting;  
patient recall;  
credit control;  
word processing;  
accounts payable;  
payroll; stock control;  
cost accounting;  
general ledger.  
Complete systems . . . \$9950  
Program alone from . . . \$1500  
OEM & dealers welcome.

**BTMS** - Intelligent terminal program for CP/M systems. Permits communication between micros and mainframes. Sends character data files to remote computers under complete control. System can record character data sent from remote computer systems and data banks. Includes programs to EXPAND and COMPRESS binary files for transmission. This software requires a knowledge of assembler language for installation. \$200/\$25

**DATEBOOK** - Program to manage time just like an office appointment book but using the speed and memory of a computer. Keeps track of three appointment schedules (three dental chairs, three attorneys, etc.) at once. Appointments consist of name, reason for the appointment, the date and time, and the length of the appointment. System can be quickly customized for the individual user. Many helpful features for making, changing, finding, and reporting appointments. Requires 48K CP/M and 180K bytes diskette storage. Not available for Apple CP/M. Specify 8080 CP/M, Z80 CP/M or Cromemco CDOS. \$295/\$25

**NAD** - Name and Address selection system. Interactive mail list creation and maintenance program with output as full reports with reference data or restricted information for mail labels. System for extraction and transfer of selected records to create new files. \$100/\$20

**NORTH STAR 64K QUAD** . . . \$4300  
**SUPERBRAIN 64K QUAD** . . . \$4604  
**DAISYWHEEL PRINTER** . . . \$1995  
**DAISYWHEEL TERMINAL** . . . \$2415  
**MICRODOT 8" QUAD** . . . \$5500  
**MEASUREMENT SYSTEMS S100**  
**SECOND GENERATION BOARDS**

**WHATSIT?** - Interactive data-base system using associative tags to retrieve information by subject. Hashing and random access used for fast response. Requires CBASIC-2. \$175/\$25

**PEACHTREE SOFTWARE**  
General accounting software for small businesses. Each product can be used alone or with automatic posting to the general ledger. Supplied in source for Microsoft BASIC 4.51.

**QSORT** - Fast sort/merge program for files with fixed record length, variable field length information. Up to five ascending or descending keys. Full back-up of input files created. \$100/\$20

**HEAD CLEANING DISKETTE** - Cleans the drive Read/Write head in 30 seconds. Diskette absorbs loose oxide particles, fingerprints, and other foreign particles that might hinder the performance of the drive head. Lasts at least 3 months with daily use. Specify 5" or 8" Single sided \$20 each/\$55 for 3 Double sided \$25 each/\$65 for 3

**SELECTOR III-C2** - Data Base Processor to create and maintain multi-key data bases. Prints formatted sorted reports with numerical summaries or mailing labels. Comes with sample applications including Sales Activity, Inventory, Payables, Receivables, Check Register, and Client/Patient Appointments, etc. Requires CBASIC-2. Supplied in source. \$295/\$20

**GENERAL LEDGER** \$530/\$40  
**ACCOUNTS PAYABLE** \$530/\$40  
**ACCOUNTS RECEIVABLE** \$530/\$40  
**PAYROLL** \$530/\$40  
**INVENTORY** \$660/\$40

**DC 300 Data Cartridges** Specify 450 XL or 300 certified Pack of 5. \$100

**PASCAL USER MANUAL AND REPORT** - By Jensen and Wirth. The standard textbook on the language. Recommended for use by Pascal/Z Pascal/M and Pascal/MT users. \$12

**GLECTOR** - General Ledger option to SELECTOR III-C2. Interactive system provides for customized COA. Unique chart of transaction types insure proper double entry book keeping. Generates balance sheets, P&L statements and journals. Two year record allows for statement of changes in financial position report. Supplied in source. Requires SELECTOR III-C2. CBASIC-2 and 56K system. \$350/\$25

**Other application products supplied in source for Microsoft BASIC 4.51**

**FLIPPY DISK KIT** - Template and instructions to modify single sided 5 1/4" diskettes for use of second side in single sided drives. \$12.50

**DMA**  
**CBS** - Configurable Business System is a comprehensive set of programs for defining custom data files and application systems without using a programming language such as BASIC, FORTRAN, etc. Multiple key fields for each data file are supported. Set-up program customizes system to user's CRT and printer. Provides fast and easy interactive data entry and retrieval with transaction processing. Report generator program does complex calculations with stored and derived data, record selection with multiple criteria, and custom forms. Sample inventory and mailing list systems included. No support language required. \$395/\$40

**MAILING ADDRESS PROPERTY MANAGEMENT** \$530/\$40 \$925/\$40

**FLOPPY SAVER** - Protection for center holes for 5" and 8" floppy disks. Only 1 needed per diskette. Kit contains centering post, pressure tool and tough 7 mil mylar reinforcing rings for 25 diskettes.

**MICROPRO**  
**SUPER-SORT I** - Sort, merge, extract utility as absolute executable program or linkable module in Microsoft format. Sorts fixed or variable records with data in binary, BCD, Packed Decimal, EBCDIC, ASCII, floating & fixed point, exponential, field justified, etc. Even variable number of fields per record! \$225/\$25

**SUPER-SORT II** - Above available as absolute program only. \$175/\$25

**SUPER-SORT III** - As II without SELECT/EXCLUDE. \$125/\$25

**DATASTAR** - Professional forms control entry and display system for key-to-disk data capture. Menu driven with built-in learning aids. Input field verification by length, mask, attribute (i.e. upper case, lower case, numeric, auto-dup, etc.) Built-in arithmetic capabilities using keyed data, constant and derived values. Visual feedback for ease of forms design. Files compatible with CP/M, MP/M supported languages. Requires 32K CP/M. \$350/\$35

**GRAHAM-DORIAN SOFTWARE SYSTEMS**  
Comprehensive accounting software written in CBASIC-2 and supplied in source code. Each software package can be used as a stand-alone system or integrated with the General Ledger for automatic posting to ledger accounts. Requires CBASIC-2.

**GENERAL LEDGER** \$805/\$40  
**ACCOUNTS PAYABLE** \$805/\$40  
**ACCOUNTS RECEIVABLE** \$805/\$40  
**INVENTORY SYSTEM** \$555/\$40  
**JOB COSTING** \$805/\$40  
**APARTMENT MANAGEMENT** \$805/\$40  
**CASH REGISTER** \$805/\$40

**INTERCOR** See ISC Intecolor  
**INTEL MDS** Single Density \$2  
**INTEL MDS** Double Density \$5  
**INTERC SUPERBRAIN DOS 0.5 2 X** \$7  
**INTERC SUPERBRAIN DOS 3 X** \$K  
**ISC Intecolor 8063/8360/8963** \$1  
**Kontron PSI-80** \$6  
**Meca 5"** \$6  
**Micromation** (Except TRS 80 below) \$1  
**Micropolis Mod I** \$1  
**Micropolis Mod II** \$2  
**MIT S 3200/3202** \$1  
**Morrow Disc** \$1  
**Mosiek** \$1  
**MSD 5"** \$C  
**North Star Single Density** \$1  
**North Star Double/Quad** \$2  
**Nyiac Single Density** \$3  
**Nyiac Micropolis Mod II** \$2  
**Ohio Scientific C3** \$3  
**Onyx C801** \$7  
**Parlec PCC 2000** \$1  
**Processor Technology Helios II** \$2  
**Quay 500** \$R  
**Quay 520** \$R  
**RAIR Single Density** \$R

**POSTMASTER** - A comprehensive package for mail list maintenance that is completely menu driven. Features include keyed record extraction and label production. A form letter program is included which provides neat letters on single sheet or continuous forms. Includes NAD file translator. Requires CBASIC-2. \$150/\$20

**FLIPPY SAVER** - Protection for center holes for 5" and 8" floppy disks. Only 1 needed per diskette. Kit contains centering post, pressure tool and tough 7 mil mylar reinforcing rings for 25 diskettes.

**STRUCTURED SYSTEMS GROUP**  
Complete interactive accounting software for business. Each product can be used stand-alone or with automatic posting to the general ledger. Each product is thoroughly tested and very well documented.

**PASCAL USER MANUAL AND REPORT** - By Jensen and Wirth. The standard textbook on the language. Recommended for use by Pascal/Z Pascal/M and Pascal/MT users. \$12

**WORD-STAR** - Menu driven visual word processing system for use with standard terminals. Text formatting performed on screen. Facilities for text pagination, page number, justify, center and underscore. User can print one document while simultaneously editing a second. Edit facilities include global search and replace. Read/Write to other text files. Block move, etc. Requires CRT terminal with addressable cursor positioning. \$445/\$40

**WORD-STAR-MAIL-MERGE** - As above with option for production mailing of personalized documents with mail lists from DATASTAR or NAD. \$575/\$40

**WORD-MASTER Text Editor** - In one mode has supersel of CP/M's ED commands including global searching and replacing, forwards and backwards in file in video mode, provides full screen editor for users with serial addressable cursor terminal. \$145/\$25

**GENERAL LEDGER** \$820/\$40  
**ACCOUNTS RECEIVABLE** \$820/\$40  
**ACCOUNTS PAYABLE** \$820/\$40  
**PAYROLL** \$820/\$40  
**INVENTORY CONTROL** \$820/\$40

## Ordering Information

**MEDIA FORMAT ORDERING CODES**  
When ordering, please specify format code

**LIFEBOT ASSOCIATES MEDIA FORMATS LIST.** Diskette, cartridge disk and cartridge tape format codes to be specified when ordering software for listed computer or disk systems. All software products have specific requirements in terms of hardware or software support, such as MPU type, memory size, support operating system or language.

Computer system	Format Code	Computer system	Format Code	Computer system	Format Code
Ailair 8800 Disk	See MITS 3200	COM 4511 5444 Cartridge	D1	RAIR Double Density	RE
Allos	A1*	CP/M 1.4	D1#	Research Machines 8	A1
Apple - SallCard 13 Sector	RC	COM 4511 5444 Cartridge	D1#	Research Machines 5"	RH
Apple - SallCard 16 Sector	RR	CP/M 2.2	D2	REX	Q3
AVL Eagle	RB	IMS 5000	RA	Sanco 7000 5"	RO
BASF System 7100	RD	IMS 8000	A1*	SD Systems 8	A1*
Blackhawk Single Density	Q3	IMSAI VDP-40	R4**	SD Systems 5"	R3
Blackhawk Micropolis Mod II	Q2	IMSAI VDP-42	R4**	Sorcerer	See Exidy Sorcerer
CDS Versatile 3B	O1	IMSAI VDP-44	R5**	Spacebyte	A1
CDS Versatile 4	O2	IMSAI VDP-80	A1**	SuperBrain	See Intecolor
COMPAL 80	O2	Intecolor	See ISC Intecolor	Target	A1*
Cromemco System 3	A1*	Intel MDS Single Density	A2	TEI 5"	R3
Cromemco Z2D	R6	Intel MDS Double Density	A5	TEI 8"	A1*
CSN BACKUP (Ipa)	T1	Intecolor SuperBrain DOS 0.5 1	R7	Thinkartoy	See Morrow Discus
Delta	A1*	Intecolor SuperBrain DOS 0.5 2 X	RJ	TRS 80 Model I 5"	R2
Digi-Log Microlam II	RD	Intecolor SuperBrain DOS 3 X	RF	TRS 80 Model I - FEC Freedom	RM
Digital Microsystems	A1*	ISC Intecolor 8063/8360/8963	A1	TRS 80 Model I - Micromation	A4*
Discus	See Morrow Discus	Kontron PSI-80	\$6	TRS 80 Model I - Omikron 5"	RM
Durango F-85	RL	Meca 5"	\$6	TRS 80 Model I - Omikron 8"	A1
Dynabyte DB8/2	R1	Micromation	(Except TRS 80 below)	TRS 80 Model I - Shuttleboard 8"	A1
Dynabyte DB8/4	A1*	(Except TRS 80 below)	A1*	TRS 80 Model II	A1*
Exidy Sorcerer	Lifeboat CP/M	Micropolis Mod I	Q1	VDP-40/42/44-80	See IMSAI
Exidy Sorcerer	Exidy CP/M	Micropolis Mod II	Q2	Vector Graphic	Q2
Health H8 H17/H27	P4	MIT S 3200/3202	B1	Vector IZ	Q2
Health H89	Lifeboat CP/M	Morrow Disc	\$1	Versatile	See CDS Versatile
Health H89	Magnolia CP/M	Mosiek	A1	Vista V80 5"	Single Density P5
Helios II	See Processor Technology	MSD 5"	\$C	Vista V200 5"	Double Density P6
Horizon	See North Star	North Star Single Density	P1	Zenith 285	Litebot CP/M P4
COM 2411 Micro Floppy	R3	North Star Double/Quad	P2	Zenith 289	Magnolia CP/M P7
COM 3712	A1	Nyiac Single Density	Q3		
COM 3812	A1*	Nyiac Micropolis Mod II	Q2		

Prices reflect distribution on 8 single density diskettes. If a format is requested which requires additional diskettes, a surcharge of \$8 per additional diskette will be added.

Prices FOB New York. Shipping, handling and C.O.D. charges extra.

Manual cost applicable against price of subsequent software purchase.

The sale of each proprietary software package conveys a license for use on one system only.

\* Single Side Single Density disks are supplied for use with Double Density and Double Side soft sector format systems.

\*\* IMSAI formats are single density with directory offset of zero.

# A media surcharge of \$25 for orders on tape formats T1 and T2 and of \$100 for orders on disk formats D1 and D2 will be added.

The list of available formats is subject to change without notice. In case of uncertainty call to confirm the format code for any particular equipment.



## LIFELINES NEWSLETTER FROM LIFEBOT

LIFELINES is the first step in software support for the serious microcomputer user. Each issue reports new revisions together with information on the purpose for each such release, be it for correction of bugs or the addition of features and facilities.

Feature Articles! New Software! Product Comparisons! Info on CP/M Users Group!

**SUBSCRIPTION INFORMATION:**  
\$18 for twelve issues. U.S. Canada and Mexico \$40 for twelve issues. all other countries. \$2.50 for each back issue. U.S. Canada and Mexico.





# RS-232C printer interface for the System-80

We published a design for a simple serial interface in the November 1980 issue that was suitable for use with the TRS-80 computer. This month we present a modified form of the same interface which is suitable for use with the System-80 computer. The driver software for this unit differs in quite a number of respects to that published in the last article.

by GERALD COHN

The hardware difference lies in the power supply circuitry. Instead of having a convenient power source as is the case with the TRS-80, we had to incorporate a power supply into the design of the new interface unit. The power supply uses the Ferguson 12V AC plugpack, allowing the rest of the interface to fit into the same size case as the previous design.

The 12V AC from the plugpack is half-wave rectified to provide a positive and a negative supply, both of which are smoothed with 1000 $\mu$ F capacitors. Following the smoothing capacitors we have two zener diode regulators providing  $\pm$ 9 volt supplies.

Apart from the power supply there was only one other minor change to be made to the circuit. The reference level for the inverting input of the 741 had to be changed to cope with the different levels at the output of the System-80 cassette interface. Instead of being centred around 400mV, the output waveform is in fact centred around a level of 200mV, with the peak-to-peak swing of the signal being a mere 300mV. The diode used in the previous design has now been replaced with a 150 $\Omega$  resistor.

All the other changes involved the software driver for the interface. There are several differences between the two machines making it necessary to have different software drivers for each. The most noticeable difference is the inbuilt


cassette recorder in the System-80. Because of this, it was necessary to use the second cassette port to output the serial data stream, but this was not without its problems.

One problem is the necessity to switch the relay for the second cassette unit. The data stream as well as the motor control is switched by the relay, instead of just the motor as is the case with the Tandy machine.

The control of the relay is performed with two output instructions. An in-depth description of how this is achieved can be found in the Column 80 article in the November 1980 issue.

To allow for the switching time of the relay, a timing loop has been included.

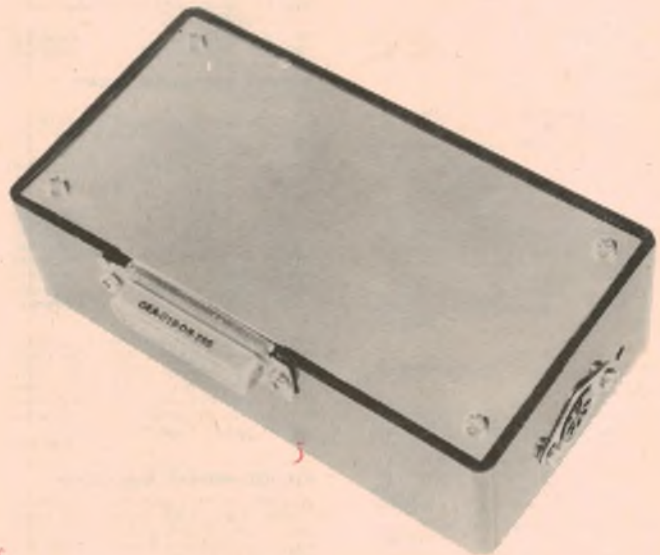*The completed serial interface is mounted in a utility box with a DIN socket for the cassette recorder and an RS-232C socket for the printer.*



## FOR THE GOURMET



### COMMODORE COMPUTERS

The range starts with the PET (illustrated) at under \$1,000 for personal use, through to complete business systems. We have a wide range of software covering Business, Education, Application and Entertainment.

## OUR BREAD & BUTTER LINES

### TRIO TEST INSTRUMENTS

CS-1560All \$660 complete

Other lines include:

B & K Test Gear  
TRENDCOM Printers  
PLESSEY & ETONE Speakers  
MOTOROLA Tweeters  
MOTOROLA KSN 1001A  
KSN 1025A



\$13.00 ea  
\$25.00 ea

Prices include delivery

## THIS MONTH'S SPECIAL

### ICOM IC 2A

2 Meter (Amateur Band)  
FM Handheld Synthesized  
Transceiver. Compact size  
with high performance.  
800 channel, 15 Watt,  
1.5 Watt or 5 Watt with  
optional battery pack.  
Charger is included.



**EDIBLE ELECTRONICS**

50 PARK STREET, ABBOTSFORD, 3067. P.O. BOX 1053, NTH RICHMOND, 3121. PHONE: (03) 41 5708.

This allows the contacts to settle before the data stream is initiated. It should be noted at this point that the printer driver routine is called up for each character that is sent to the printer. Keeping this in mind, it can be seen that the timing loop is included in the transmission of each and every character.

This has the effect of slowing the printing operation, but this only becomes significant at higher baud rates. (The bit rate is not affected by this timing loop since the baud rate is software generated in another part of the driver routine.)


The other software changes involved the values for the zero and one codes. In the TRS-80 version these were FC01 and FC00 respectively, but they have now been changed to FC05 and FC04. This sets bit 3 of port FE high, thus keeping

the relay enabled for the data transmission.

That just about wraps up the changes to the software. The new machine language driver is just a little longer than the one for the TRS-80, and more RAM must be reserved as a result. The new initialisation values for the top of RAM are given in Table 1. These values are entered when the machine is first switched on, and the message READY? appears. Enter the value that corresponds to the amount of free RAM that is available in your particular system.

The rest of the initialisation with the BASIC program is exactly the same as that described in the November 1980 issue, and is reproduced below.

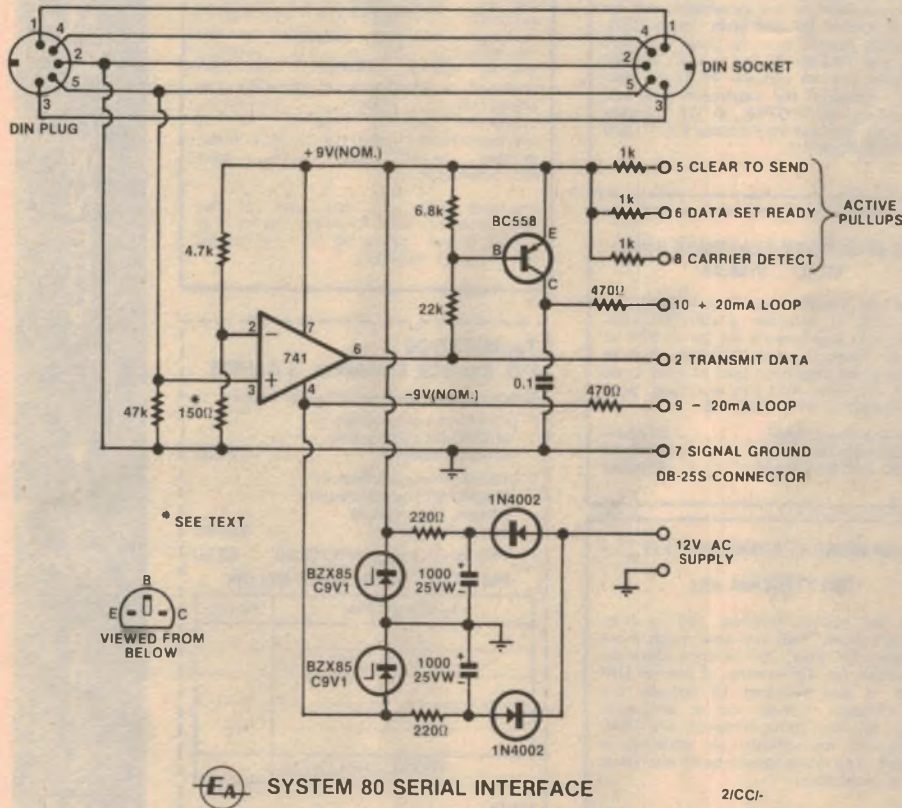When either the LPRINT or LLIST commands are now used, the vector in the



This circuit is similar to the November 1980 version apart from the power supply.

## PARTS LIST

- 1 printed circuit board 100 x 52mm (81SP1)
- 1 plastic utility case 130 x 69 x 42mm
- 1 5-pin DIN socket (180°)
- 1 5-pin DIN plug (180°)
- 1 12V AC plugpack Ferguson type PPB 12/500
- 1 DB25S connector
- 2 x 1000µF/25VW electrolytic capacitors
- 1 x 0.1µF metallised polyester capacitor

### RESISTORS

- 1 x 47k, 1 x 22k, 1 x 6.8k, 1 x 4.7k, 3 x 1k, 2 x 470Ω, 2 x 220Ω, 1 x 150Ω

### SEMICONDUCTORS

- 1 x 741 operational amplifier IC (8-pin)
- 1 x BC558 PNP transistor
- 2 x BZX85/C9V1 or similar 9V/1W zener diode
- 2 x 1N4002

### MISCELLANEOUS

- Screw, nuts, solder, hookup wire etc.



## COMMODORE AND MICROPRO DESIGN JOIN FORCES!

MicroPro Design is now able to offer the Commodore microcomputer systems at prices you can afford! We specialise in the design and manufacture of custom microcomputer equipment and have turned our efforts to the CBM and PET.

Besides having the full range of standard Commodore products available, we can offer interfaces to allow virtually any piece of equipment to be connected to the CBM through the IEEE 488 bus.

You can now also use our MicroCon general purpose microcomputer as a slave to the CBM. This allows you to connect A/D, D/A converters, digital inputs and digital outputs for industrial control, monitoring and data acquisition. Programs for the MicroCon can be created in the CBM and loaded down the IEEE 488 bus into the MicroCon for execution.

A few of the current devices now available for use with CBM and PET:

IEEE488 - RS232 Interface	\$350.00
IEEE488 - Centronics Interface	\$250.00
IEEE488 - Diablo (Ricoh, Qume)	\$420.00
IEEE488 - Microcon Interface	\$200.00
CITOH Printer (80 COL, 125 CPS)	\$970.00
Diablo WP Printer (with interface)	\$3,500.00

**Above prices include all cables and connectors where applicable but do not include sales tax. (Dealer enquiries invited.)**

**Write or call for prices on all the Commodore equipment.**



**MicroPro Design Pty. Ltd.**

PO BOX 153, NORTH SYDNEY, NEW SOUTH WALES, 2060, AUSTRALIA.  
SUITE 205, WENTWORTH HOUSE,  
6-8 CLARKE ST., CROWS NEST,  
NSW, 2065. PHONE: (02) 438 1220.

# CAN YOU AFFORD NOT TO SUBSCRIBE TO MICRO-80?

MICRO-80 is a monthly magazine dedicated to users of SYSTEM 80 and TRS-80 microcomputers. Owned and produced entirely in Australia, each issue of MICRO-80 contains at least six programs, articles, useful hints and answers to readers' problems; all designed to help YOU get the most out of your SYSTEM 80 or TRS-80. Since MICRO-80's first issue in December 1979, we have published over 80 major pieces of software and 10 hardware projects. Most of the programs and articles are written by our readers to whom we pay publication fees thus enabling them to make their hobby pay. MICRO-80 readers can save money by buying Tandy products at 10% discount from an authorised dealer — for details see any issue of MICRO-80. Our sister business, MICRO-80 PRODUCTS, sells Australian designed and produced software and high quality, imported goods at low, sensible prices. We repeat, if you own a SYSTEM 80 or TRS-80.

**CAN YOU AFFORD NOT TO SUBSCRIBE TO MICRO-80? . . . . . 12 month subscription delivered to your door, only \$25.00**

**CASSETTE EDITION only \$60.00 for 12 months**

If you do not have enough time at the keyboard to type in the program listings which are published in MICRO-80 each month, then you need a cassette subscription. As well as MICRO-80 magazine, you receive a cassette each month containing all the programs listed in the magazine.

## SPECIAL OFFER TO ALL NEW SUBSCRIBERS TO MICRO-80

A FREE cassette containing 6 programs (3 Level I + 3 Level II), together with complete documentation, will be sent to every new subscriber to MICRO-80.

Suspicious of mail order? Then send \$2.50 for a single copy of MICRO-80 and see for yourself that this is the magazine for you!

### 77 TRACK DISK DRIVES DOUBLE YOUR CAPACITY

**DD-7S . . . . . \$775**

Micropolis Floppy Disk, 77 Track, 100% larger capacity than most mini-floppy drives, complete with cable, power supply, chassis, and includes NEWDOS '80.

**DD-7 . . . . . \$649**

Same as above but no cable or Newdos '80.

**DC-4 . . . . . \$45**

4 drive connector cable.

### MPI DISK DRIVES

MPI is the second biggest manufacturer of mini floppy disk drives in the world. They produce a family of high quality 5 1/4" drives with super-fast track-to-track access times (5ms!)

**40 TRACK SINGLE HEAD . . . . . \$339**

**40 TRACK DUAL HEAD . . . . . \$449**

**80 TRACK SINGLE HEAD . . . . . \$499**

**80 TRACK DUAL HEAD . . . . . \$599**

Dual head drives use both sides of the disk and occupy two drive positions — it is like having two drives for little more than the price of one!

Prices quoted are for bare drives. Add \$10 per drive for a cabinet and \$30 per drive for a power supply.

### DISKETTES FOR TRS-80

**NASHUA 40 track single side . . . \$4.50 ea**

**VERBATIM 40 track double side. . \$5.90 ea**

**VERBATIM 77 track single side . . \$5.90 ea**

### THE FABULOUS NEWDOS 80 IN STOCK NOW!

**ND-80 . . . . . \$149**

The disk operating system that gives:

- New basic commands that support variable record lengths up to 4095 bytes long.
- Mix or match disk drives — supports any number of tracks from 18 to 80. Use 35, 40 or 77 track 5 1/4" mini disk drives or 8" disk drives, or any combination.
- A security boot-up for basic or machine code programs. User never sees "Dos-ready" or "Ready" and cannot "break" clear screen or issue any direct basic statement including "List". . . . . and much, much more

### EXATRON STRINGY FLOPPY

**\$352.50 incl p&p**

15 times faster than cassette, infinitely more reliable. Completely under computer control, the stringy floppy is easier to use than disks and is a very much cheaper alternative. Will save and load any L2/16K software. Special software also available.

**Wafers for Stringy Floppy  
\$3.50 ea. Any Size**

### SYSPAND 80 FOR THE SYSTEM 80 \$119.00

SYSPAND 80 is a self-contained module which connects to the expansion port on your SYSTEM 80 and gives you a CENTRONICS parallel port to drive a printer PLUS the TRS-80 40 line bus. SYSPAND 80 allows you to connect all Tandy peripheral, including the expansion interface, disk drives, MICROTEK MT-32 memory expansion unit and the fabulous EXATRON STRINGY FLOPPY.

### TRS-80 MEMORY EXPANSION UNIT MT-32 . . . \$149.00

The MT-32 is manufactured by MICROTEK Inc., USA. It provides a CENTRONICS printer port and sockets for up to 32K of dynamic RAM. It comes complete, ready to plug into the expansion port of your Level II 16K machine. (Will also work with your SYSTEM 80 via SYSPAND 80).

**MT-32A without RAM . . . . . \$149.00**

**MT-32B with 16K RAM . . . . . \$208.00**

**MT-32C with 32K RAM . . . . . \$262.00**

### 16K MEMORY EXPANSION KIT.

**ONLY \$59 incl. p&p**

These are prime, branded, 200 ns (yes, 200 ns!) chips. You will pay much more elsewhere for slow, 350 ns chips. Ours are guaranteed for 12 months. A pair of DIP shunts is also required to upgrade the CPU memory — these cost an additional \$4.00. All kits come complete with full, step-by-step instructions, no soldering is required. You don't have to be an electronic type to instal them.

### DISK DRIVE HEAD CLEANING DISKETTES

**\$29.00 plus \$1.20 p & p**

Disk drives are expensive and so are diskettes. As with any magnetic recording device, a disk drive works better and lasts longer if the head is cleaned regularly. In the past, the problem has been, how do you clean the head without pulling the mechanism apart and running the risk of damaging delicate parts. 3M's have come to our rescue with SCOTCH BRAND, non-abrasive, head cleaning diskettes which thoroughly clean the head in seconds. The cleaning action is less abrasive than an ordinary diskette and no residue is left behind.

MICRO-80 has converted the new OLIVETTI ET-121 DAISY WHEEL typewriter to work with the TRS-80 and SYSTEM 80 or any other microcomputer with a Centronics parallel port (RS 232 serial interface available shortly). The ET-121 typewriter is renowned for its high quality, fast speed (17 c.p.s.), quietness and reliability. MICRO-80 is renowned for its knowledge of the TRS-80/SYSTEM 80 and its sensible pricing policy. Together, we have produced a dual-purpose machine:— an attractive, modern, correcting typewriter which doubles as a correspondence quality Daisy-wheel printer when used with your micro-computer.

How good is it? — This part of our advertisement was typeset using an ET-121 driven by a TRS-80. Write and ask for full details.

**To: MICRO-80  
P.O. Box 213, Goodwood, S.A. 5034**

Please rush me the items checked below:


- 12 month subscription to MICRO-80 and my free software cassette . . . . . \$24.00
- 12 month subscription to MICRO-80 and the cassette edition, plus my free software cassette . . . . . \$60.00
- The latest issue of MICRO-80 . . . . . \$2.50
- PLUS THE ITEMS LISTED BELOW**

DESCRIPTION	PRICE
TOTAL ENCLOSED	

Name .....

Address .....

Post Code .....

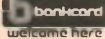 No  
welcome here

Please debit my Bankcard \$ .....

Expiry date .....

Signature .....

EA

**MICRO 80  
PRODUCTS**

(08) 272 0966

284 GOODWOOD ROAD,

CLARENCE PARK, ADELAIDE

TRS 80 and SYSTEM 80 OWNERS TRS 80 and SYSTEM 80 OWNERS

### AUSTRALIAN SOFTWARE

We have a wide range of Australian software available. Send for a free catalogue

## PRINTER INTERFACE

device control block will point to the new driver residing at the top of RAM.

TABLE 1

Memory Size	Last Location	Enter
4K	20479	20350
16K	32767	32640
32K	49151	49020
48K	65535	65410

After a short delay while the machine language program is loading, the computer will respond with:

BAUD RATE?

Answer this question with one of the values listed below. Check your printer manual for the correct baud rate to be used.

110	450	2400
150	600	4800
300	1200	9600

After the baud rate has been entered the computer will respond with:

ADD LF AFTER CR (Y/N)?

BASIC transmits carriage returns after each line of text, but does not transmit the line feed character. If your printer requires a line feed character to advance the paper, answer Y. If you are using a Centronics or a Selectric, answer N, since these printers automatically advance the paper when a carriage return is executed. If you are not sure, consult the printer's manual.

Having answered the last question the computer will respond with:

NUMBER OF NULLS (0-127)?



Some printers require null characters after each carriage return to allow time for carriage travel. If your printer requires these nulls, answer with the desired number, otherwise type 0.

After this question is answered, control returns back to BASIC and the READY message will appear. You are now ready to load and run any of your BASIC software.

The entire circuit with the exception of the plugpack transformer is accommodated on a printed circuit board (PCB) measuring 100 x 52mm and coded 81sp1.



Construction is simple, requiring about an hour of your time. Start the assembly of the PCB by placing the four wire links onto the board and soldering these into place. Follow these up with the resistors and the diodes. Next solder the transistor and the IC into place, leaving the two filter capacitors until last.

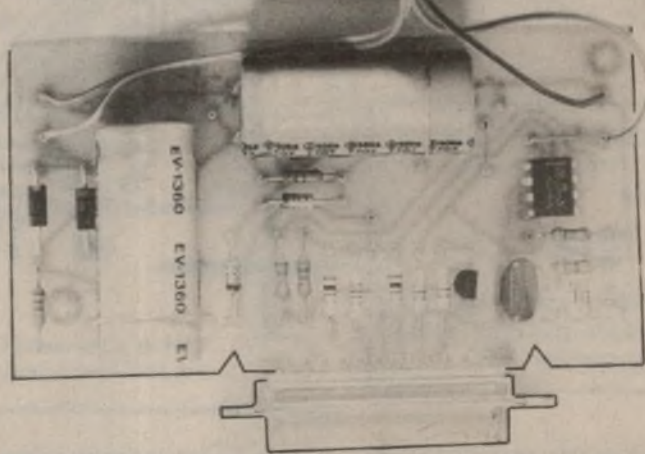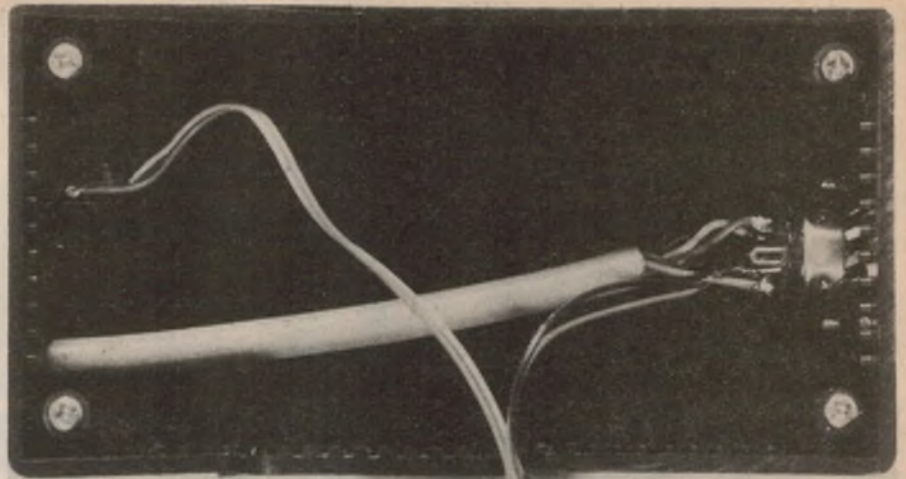The value of the 150Ω resistor may have to be juggled a little depending on the signal levels at the output of the cassette interface in the computer. The value of 150Ω proved quite satisfactory with several System-80's on which the interface was tried, and should work on almost all others. If the signal level is



Notches are cut into one side of the PCB to allow clearance for the socket screws.

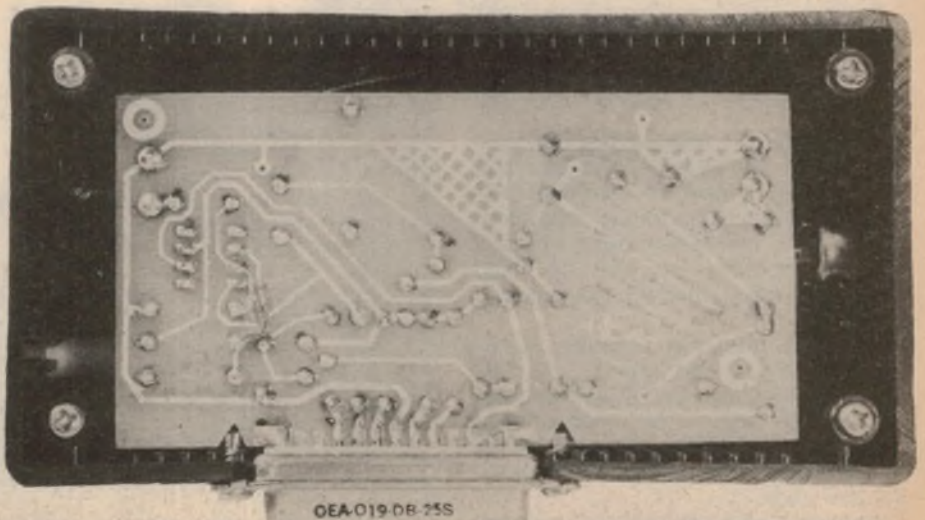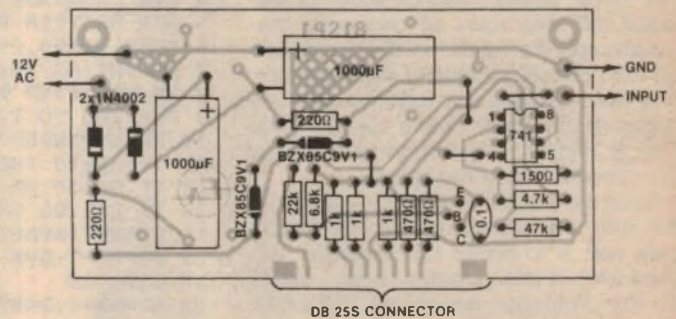Assembly of the PCB is simple. The photo below shows the PCB mounted in the case, supported by the 25-pin socket.



## RS-232C PRINTER INTERFACE

lower than 300mV superimposed on a DC level of 200 to 300mV then you will need to decrease the value of this resistor. The converse is true for higher levels.

The photograph of the PCB shows that we have used PC mounting electrolytics, but provision has been made for pigtail types in case these happen to be more readily available. If you use PC mounting types, then you will need to place a retaining loop around the end of the capacitor, which is then soldered to the board. The last component to be soldered to the board is the DB-25 connector.

We estimate that the cost of parts for this project is approximately

**\$15**

This includes sales tax but does not include the cost of the plugback transformer.

Before you solder the connector to the board, make sure that the side containing 13 terminals is the one on the copper side of the board. The PCB slides in between the two rows of connector terminals, and the tracks on the board line up with the solder tails of the terminals. The two outside pads have been made larger so that more solder can be used. This provides a rigid support between the connector and the board.

Once the board is complete, place it to the side and start preparing the plastic case that is to house the interface. We used one of the popular "zippy" boxes for the prototype, measuring 130 x 69 x 42mm.

The first thing to be done is to make the cutout for the 25-pin connector. Note that the connector is not in the centre of the board, but slightly off to one side.


Three holes are required for the 5-pin DIN socket, the power connector and the cable entry from the computer. We have provided a pin-for-pin equivalent socket in the interface housing so that a cassette recorder can still be used without having to take the interface out of circuit.


The cable from the computer is terminated on one end with a 5-pin DIN plug while the other end is fed through a hole in the case of the interface and soldered to the DIN socket. Make sure that there is a pin-for-pin match between the two ends.

We used a plug and socket to connect

the plug pack to the interfaced unit but this could be hardwired if desired. Now all that remains to be done is to make the connection between the interface board and the computer cable, mount

the board in the box, after checking everything thoroughly, and trying it out. As mentioned before, the procedure for using this version of the printer interface is exactly the same as that described in the November 1980 issue.

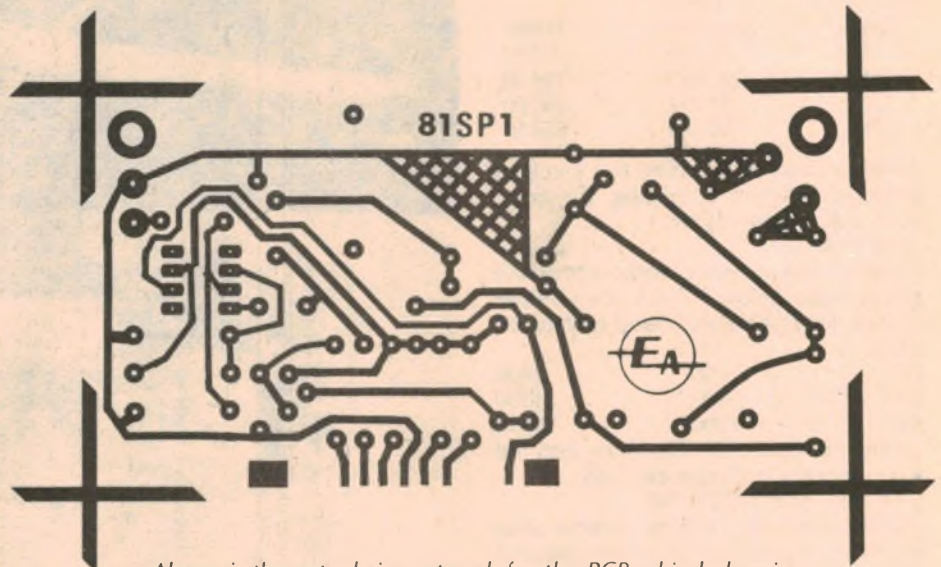There you have it, a simple low cost interface between your System-80 and a serial printer. Have fun. 



Above is the actual size artwork for the PCB while below is the software listing.

```
1 REM BASIC PROGRAM FOR INITIALIZING SYSTEM 80 RS-232 PRINTER
2 REM INTERFACE. THIS PROGRAM REQUIRES THAT AT LEAST 125 BYTES
3 REM BE RESERVED AT THE TOP OF RAM SPACE FOR THE MACHINE
4 REM LANGUAGE DRIVER ROUTINE.
5 REM WRITTEN BY GERALD COHN - 11/11/1980
6 POKE 16553,255:CLS:INPUT"ENTER MEMORY SIZE";MS:MS=MS+1
7 HB=INT(MS/256):LB=MS-256*HB:POKE 16422,HB:POKE 16423,HB
8 IF MS>32767 THEN MS=MS-65536
9 FOR I=0 TO 123:READ D:POKE MS+I,D:NEXT I
10 PRINT:INPUT"BAUD RATE";B:BR=1
11 IF B=110 THEN 19
12 IF B=150 OR B=300 OR B=450 OR B=600 THEN 15
13 IF B=1200 OR B=2400 OR B=4800 OR B=9600 THEN 17
14 PRINT"INVALID SELECTION":PRINT:GOTO 10
15 BR=BR+1:B=B-150:IF B<>0 THEN 15
16 GOTO 19
17 BR=BR+1:B=B/2:IF B<>600 THEN 17
18 BR=BR+4
19 FOR I=1 TO BR:READ D:NEXT I
20 DH=INT(D/256):DL=D-256*DH
21 POKE MS+42,DL:POKE MS+43,DH
22 POKE MS+84,DL:POKE MS+85,DH
23 POKE MS+94,DL:POKE MS+95,DH
24 PRINT:INPUT"ADD LF AFTER CR (Y/N)";QS
25 IF QS="Y" THEN 28
26 IF QS<>"N" THEN 24
27 FOR I=1 TO 4:POKE MS+67+I,0:NEXT I
28 PRINT:INPUT"NUMBER OF NULLS (0-127)";N
29 IF N<0 OR N>127 THEN 28
30 POKE MS+60,INT(N+1):CLS:END
31 DATA 243,62,255,211,254,229,33,255,1,43,62,4,211,255,124
32 DATA 181,32,247,225,121,254,13,40,3,254,32,216,245,229,197
33 DATA 6,9,55,245,245,33,5,252,205,33,2,33,222,0,43,124,181
34 DATA 32,251,241,31,245,48,19,33,4,252,24,19,14,2,175,13
35 DATA 40,2,24,219,62,10,24,215,24,47,198,0,33,5,252,205
36 DATA 33,2,0,0,33,222,0,43,124,181,32,251,16,212,17,222,0
37 DATA 203,74,40,11,33,4,252,205,33,2,27,122,179,32,251,241
38 DATA 241,254,13,40,198,183,40,197,193,225,241,201,615
39 DATA 450,222,146,108,51,23,8,1
```

# OGURA PRINTER

## RO-136E



### Basic Specifications:

- Printing speed 120CPS bidirectional
- Character size 7 (length) × 9 (width) (Standard)
- Character type ASCII 128 characters
- Character spacing 128 (136E) or 64 (80E) special characters can be added as an optional feature
- Line spacing 10 characters/inch
- Form width 6 or 8 lines/inch (switchable)
- Copies 5-15 inches (136E)
- Paper feed speed 5-9 inches (80E)
- Paper feed mechanism Tractor feed (continuous form)
- Data input A slip may also be used
- Power 8 bit parallel Centronics compatible RS-232C I/F.
- Inked ribbon TTY 20mA current loop I/F. A variety of specifications can be applied by controlling the interface.

### Graphic Data RO-136G

The printer can print graphic data by controlling printing on a dot basis of up to 960 dots across the page.  
Speed — 80CPS.

## New Dot Printer Featuring Low Cost, High Performance, and Versatility

The OGURA RO series incorporating a microcomputer, is a low-price, high-performance serial dot printer featuring high reliability and a variety of applications.

It can be used in combination with a microcomputer, a small-scale computer, or as a CRT hardcopy device.

"Ogura RO Series" aims at dispersion of printers.

# SME OLYMPIA PRINTER

Why would you want a golfball when you can now have something quieter, faster and less tiring?

The new generation electric typewriter is here! And it doesn't have a golfball. Olympia Whisperdisc. A super-quiet fully electronic typewriter with a simple, trouble-free typing disc to give you an almost perfect image.

A self corrector lets you remove up to eight characters by pressing a single key. The disc can be changed in seconds to a different typeface. The low profile keyboard reduces strain. And, being electronic, Whisperdisc is virtually trouble-free.

SME can now supply the ES100 Typewriter fitted with RS232C Serial Interface. This unit is known as a ES100P, it can interface to all standard computers via a 25-way 'D' connector.

Please contact SME for more information.

\$1950.00




Send 66¢ in stamps for COMPUTER PRINTOUT CATALOGUE for more details.

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST) DEALER ENQUIRIES WELCOME.

Prices and specs. subject to change without notice.

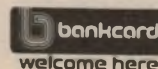All prices tax free, for retail prices add 15 per cent.



Give name, number, expiry date and signature for mail order sales.

# Tandy TRS-80 pocket computer

Just released simultaneously in the USA and Australia, the Radio Shack/Tandy TRS80 Pocket Computer is aptly hailed as a breakthrough but it is almost concealed at the end of their catalogue. It certainly marks a great step forward in microcomputers — with the emphasis on the micro. At its price of \$250 it invites comparison with Sinclair's ZX80 and the UK Compukit, neither of which can compete with the TRS80 in terms of portability. Indeed there is a real risk of losing the TRS80 under a sheet of paper when writing a program.

by R. V. Taylor

The basic unit is just 175 × 70 × 18mm and weighs 240g. The keyboard is of the "QWERTY" variety with a numeric pad at its right side; the 24-character liquid crystal display is placed above the keyboard along the unit's major axis. The 37 alpha keys are pitched at 11mm between centres in four rows, at 7.5mm between centres, while the 20 numeric keys are on the same centres laterally but in columns at 9mm between centres. All keys have a light but definite feel, except the "ON" key, which is set lower than the others and requires positive pressure to operate it. The keytops are clearly marked (SHIFT and CLEAR are also colour-coded) but the shifted symbols, such as colon and semi-colon, are engraved on the panel and are not so easily read. The shifted Y is a Yen sign (indicating the source of the device) though it is not marked on the panel.

The "ALL RESET" switch (operated by means of a stylus, through a hole in the back of the case) is the only off-keyboard control.

A nine-pin socket in the left hand end of the case, provided with a detachable cover, allows connection to the optional Cassette Interface, into which the basic unit may be fitted. This Cassette Interface then encloses the rear and two adjacent sides of the TRS80, making the overall dimensions 210 × 90 × 22mm and the cost \$50 more. The Cassette Interface introduces no extra controls, but requires three AA size batteries, and has a built-in connector with a suitable lead and plug to fit a tape recorder.

The recommended mercury batteries (four in series) form the TRS80 power supply, and are fitted in a plastic holder reached by removing the rear cover of the unit's case. This is retained by four recessed screws, but with a battery life

of 300 hours (100 hours if silver zinc cells are used) this is no handicap. Power consumption is .011W alone and .013W with the Cassette Interface connected.

The simplified block diagram shows the major components and the interface connections. The two CPU's share the bidirectional 4-bit data bus and are gated onto the 8-bit section of the address bus by their "busy" lines. The two remaining address lines of CPU1 access the RAM while those of CPU2 are used for I/O control. The CPU's Read/Write lines are gated onto the RAM/Write line. RAM is comprised of the three Display chips (128 bytes each) and the three RAM

chips (512 bytes each).

CPU1 is mounted on the keyboard PCB and looks after the keyboard while CPU2 is mounted on the arithmetic PCB and deals with arithmetic routines. Other functions of the CPU's include the following:

CPU1  
Interpreter  
Manual operations  
Power control  
Clock control


CPU2  
Display processing  
Input buffer  
Character generation  
Cassette routines  
Buzzer control


Most functions require both CPU's to act together but the details are not relevant to this review.

One section of a 4011 CMOS chip provides the crystal oscillator giving a clock frequency of 256kHz which is rather slow but adequate for the unit's requirements.

Note that the CPU2 cassette routines include generation and decoding of the 2 and 4kHz tones. The Cassette Interface is more of a conditioning and control

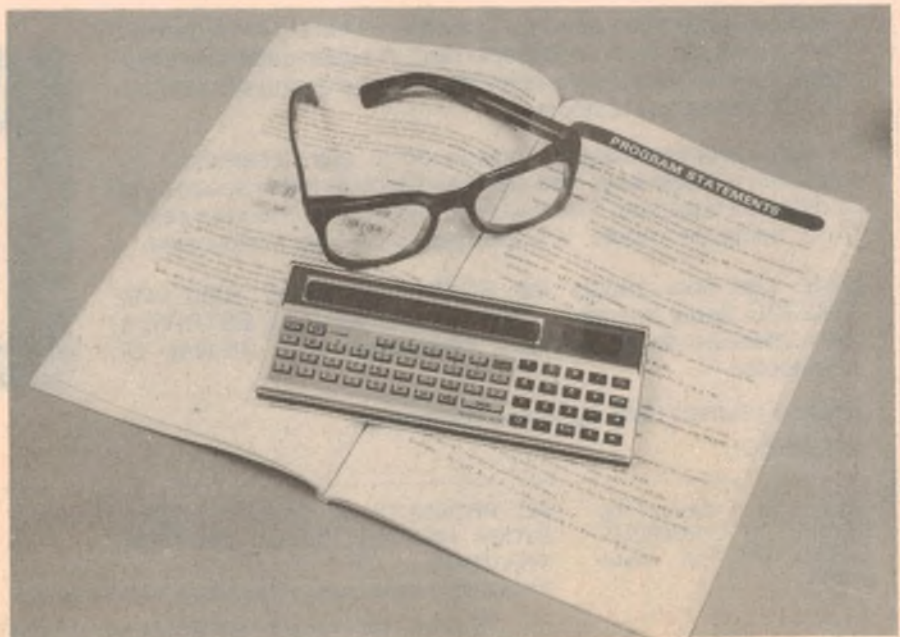*Emphasising its small size, the TRS80 is dwarfed by its companion software manual.*



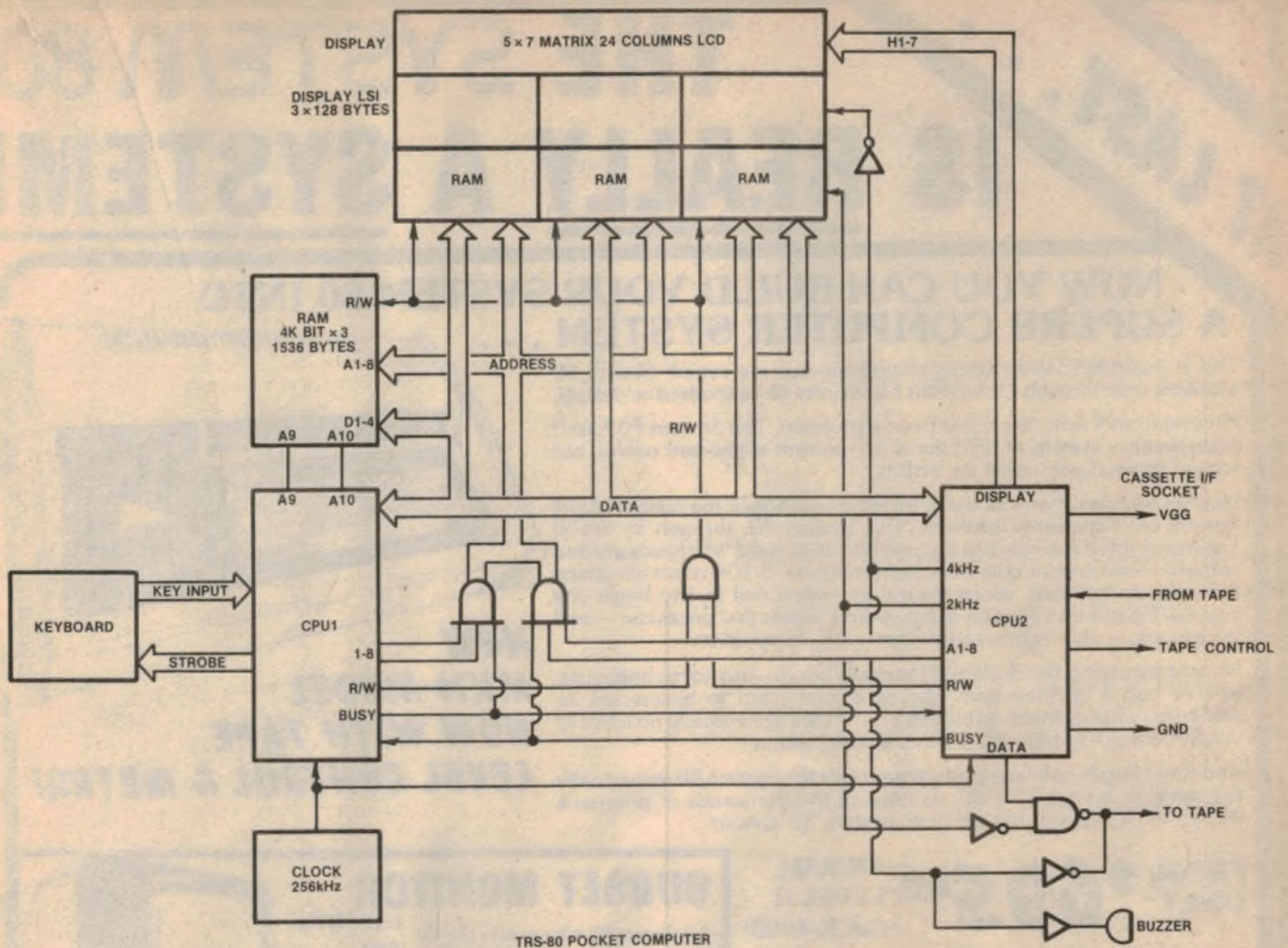

unit, providing also tape motor control and muting, rather than acting as a modem. This makes for most reliable CSAVE and CLOAD operations and allows CLOAD Verification. The Cassette Interface batteries are used only for operation of the relay controlling the tape motor, the remaining power requirements of .002W being supplied from the TRS80.

Documentation is vital for a device of this complexity, so examination of the manual is mandatory. The 122 page Tandy manual weighs more than the microcomputer itself and is generally clear and well set out. The traditional quick reference card tucks into the soft pocket carrying case. Two overlays are provided against assignment of user definable (reservable) keys.

The manual provides an overview of the computer, followed by sections on manual and programmed calculations before going into programming the machine in BASIC. Some knowledge of BASIC is assumed but most of the text could be followed without prior experience — in fact, as the machine uses a shortened form it may be better to start from scratch. (Continued on page 112)

For program storage, the TRS80 and cassette interface mate to drive the recommended Minisette-9 (shown upside-down).





**AT LAST...**

# THE SYSTEM 80 IS REALLY A SYSTEM!

## NOW YOU CAN BUILD YOUR SYSTEM 80 INTO A SUPERB COMPUTER SYSTEM...


This is Australia's fastest selling microcomputer: the superb System 80 available only through Dick Smith Electronics (& authorised re-sellers).

However, until now, there has been a problem. The System 80 hasn't really been a system at all. Like a car without a tow-bar: useful, but limited in what you could do with it.

Now all that has changed: we're proud to announce the release of the System 80 Expansion Interface. The System 80, through its S-100 expansion interface, now has the potential to be used with hardware and software devices from over 200 manufacturers. S-100 is fast becoming the industry standard, which means you aren't tied to any single one supplier for add-ons. A single supply source means that prices can — and usually are — sky-high because there is no competition.

So now we expect the System 80 to really boom — not just to hobbyists, who've had it all their own way until now — but to businesses, to students, to housewives, to industry... There are virtually no limits to the System 80 system. All it takes is imagination.

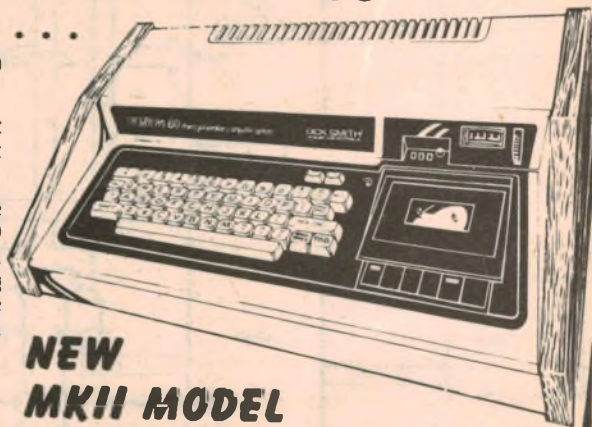And don't forget: software requirements for the System 80 are virtually the same as for the TRS-80: so most of the thousands of programs written for it will also run on your System 80 system!



**NEW MKII MODEL NOW WITH TAPE LEVEL CONTROL & METER!**

**FROM ONLY \$695<sup>00</sup> (4K RAM, LEVEL II Cat X-4003)**

**16K RAM, LEVEL II MODEL (Cat X-4005) \$750<sup>00</sup>**

### BUDGET MONITOR

The System 80 will run with any TV set: but in case you need a monitor, check this one out! P 5 This monitor will also work with most other microcomputers. Compare our prices and **SAVE!**

**USE WITH ANY COMPUTER!**

**\$149<sup>50</sup>**  
Cat X-1196



## NEW SYSTEM 80 SOFTWARE —

### FOR FUN & EDUCATION

Here are five recently released software tapes for the System 80 (also suitable for the TRS-80 Level II). They're fun to play and they're educational, too.

#### X-3688 "DEATH TRAP"


In this fast-moving realtime graphics game you have to control the motion of a constantly-moving point on the video screen and avoid randomly-appearing "mines" until an "escape window" appears. You can't cross your own trail, or hit the sides of the screen either. If you escape, you get further tries — only it gets tougher! Has sound effects. Requires 16K.



**\$9.95**
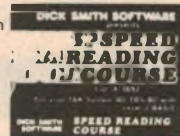
#### X-3692 "SPEED READING COURSE"

A set of programs supplied on two cassettes, designed to help readers of all-ages to improve their reading skills. The programs have been developed from the West Australian Reading Development Scheme. Requires 16K.



**\$19.95**

#### X-3694 "LEARNING FUN 1: SCURVE INVADERS"

Combines basic maths drill with the ever-popular "Space Invaders" game. Before being able to take each shot the player feeds in the "correct data". Sound effects, three levels of difficulty. Requires 16K.



**\$9.95**

#### X-3696 "LEARNING FUN 2: HANGMAN/CONCENTRATION"

Two programs. Hangman is complete with animated graphics "man" getting hung. The words chosen by either the program or a second player. Concentration: two players or teams have to match prizes behind numbers on the screen, then try to guess the mystery food word. Requires 16K.



**\$9.95**

#### X-3698 "LEARNING FUN 3: ALPHABET COUNTDOWN/RHYME TIME"

In Countdown sets of words taken at random from a large group must be placed in alphabetic order. Rhyme Time displays a series of unfinished rhymes, and the player has to type in the missing word from the clues given in the rhyme itself. Requires 16K.




**\$9.95**
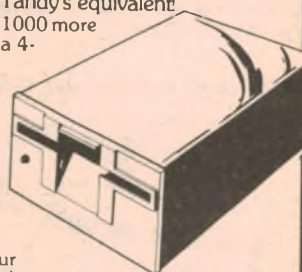
## BARGAIN PRICED MINI DISK DRIVE

\$200 less than Tandy's equivalent! You'd pay over \$1000 more from Tandy for a 4-drive system!

This incredible drive is world-famous Pertec brand; offers higher capacity than Tandy drive and will work with System 80 or TRS-80. Ask for more info at your nearest Dick Smith store!



X-3230

**\$379**

## DISK PRICES TUMBLE!

Unbelievable prices for either hard or soft sector mini diskettes. Suit virtually all disk drives available. Buy from Dick and save a fortune!

Hard Sector (X-3505)  
Soft Sector (X-3510)

Trade enquiries welcome

**WERE \$5.95 EA! NOW:**  
1 - 10: \$4.95  
10 - 100: \$3.95  
100 UP: \$3.50

## ITOH 8300P BUDGET PRINTER

For budget printing, you can't go past this one! Uses standard tractor-feed paper, gives high quality print from its 7x5 dot matrix. Up to 240mm paper, prints 125 chars/sec. For either System 80 or TRS-80. Cat X-3255.

40/80/132 CHAR/LINE

Uses Printer interface  
and cable below

**\$970**



FAN-FORM COMPUTER PAPER  
TO SUIT ABOVE PRINTER 2000 SHEETS.

Cat X-1189

**\$35.00**

## LETTER QUALITY DAISY WHEEL PRINTER

For top quality print, try this: it's over \$300 cheaper than Tandy's daisy-wheel, and is capable of proportional printing! Limited stocks

Takes standard  
stationery!



Cat X-3265

**\$1995<sup>00</sup>**

## PROGRAM CASSETTES

Popular C-10 computer cassettes (just the right size for programs!) with computer-quality tape. Suitable for all 'compact cassette' type units (which everyone uses!) Cat X-3500

**\$1<sup>95</sup>**



## SAVE A FORTUNE ON MEMORY IC'S

Were almost \$100 more twelve months ago! Fast 250nS 4116 RAMs, for upgrading your 4K or 8K to 16K, 16K to 32K or 32K to 48K. 8 IC's in pack. With full instr. Cat X-1186

**\$59<sup>95</sup>**



Also available individually:  
Cat Z-9310 \$7.90 ea.

## DON'T NEED FULL S-100 EXPANSION?

Use this parallel printer interface if you don't need full S-100 expansion. Save a bundle! Uses similar connecting cable to S-100 interface

**\$49<sup>50</sup>**

## PRINTER CABLE

Cat X-4013



Fitted with edge connector at one end. 57N-36 plug at other: suits virtually all Centronics-type printers. Use with either S-100 interface or parallel printer interface.

**\$39<sup>50</sup>**

Cat X-4014

## SOUND OFF

Add sound to your System 80 programs! Includes amp, programs and full instructions. You can add sound to existing programs too! Also suits TRS-80.

**\$19<sup>50</sup>**

Cat X-3648



## MICROSOFT™ EDITOR/ASSEMBLER PLUS!

Editing, assembling & debugging power you've never had before! Equivalent of Tandy's Editor/assembler and T-bug products but in one package and at less than half the price! And it's far more powerful! Suits System 80 & TRS-80




**\$39<sup>95</sup>**

Cat X-3680

## LIGHT PEN BARGAIN!

The best value around. Gives your System 80 or TRS-80 an eye. Easy to use, has simple programs

**\$9<sup>95</sup>**

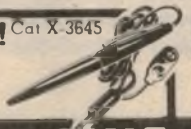

## COMPUTER HOT LINE . . .

Want to know more about our computers? Or are you having troubles? We've set up a special computer hot line just to help you out. Call between 9AM & 5PM on Sydney (area code 02)

**888 2002**

## SOFTWARE for System 80 or TRS-80

GAMES AND EDUCATIONAL SOFTWARE  
CURRENTLY AVAILABLE

### TIME TREK

**\$17.95**

You're boldly going where no man has gone before. Mind you, those pesky Klingons attack you from time to time, so you'll need fast reflexes as well as sharp wits. Nine levels of difficulty. Cat X-3650

### STIMULATING SIMULATIONS

**\$17.95**

No less than 10 different games, all fascinating and original: Art Auction, Forest Fire, Minister Chase, Nautical Navigation, Lost Treasure, Business Management, Gone Fishing, Rare Birds, Space Flight and Diamond Thief. Cat X-3652

### ELECTRIC PAINTBRUSH

**\$17.95**

This is a special machine language graphics interpreter program which lets you program dazzling graphics displays using simple high-level commands. Easy - and fun! Cat X-3654

### BRIDGE CHALLENGER

**\$17.95**

Keen on Bridge? This game never gets tired of playing with you. Ideal for practising and improving your level of play - whether you're an expert or just a beginner. Needs a 16K machine. Cat X-3656

### MICROCHESS

**\$22.50**

Think you're a wizz at chess? This program will put you to the test! But think out your moves carefully: the computer is out to beat you! One of the top selling chess programs in the USA. Cat X-3658

### BLOCKADE

**\$17.95**

You'll need fast reflexes and good coordination for this one. It's written in machine language, so it can give really high speed graphics. Try to force your opponent into a collision with a moving wall, without running into a wall yourself! Cat X-3659

### PUNTER'S DREAM

**\$12.50**

Place your bets, please the race is about to start! Study the form of the various horses before placing your bets. Then the race is on! The program looks after the betting accounts of up to nine punters, and can even cream off a percentage for the house! You get a realistic simulation of racetrack probabilities. Use it for fun, or to improve your strategies! Needs a 16K machine. Cat X-3660

### BANDITO

**\$14.95**

Like playing the one-arm bandits down at the club? Here's one you can play seated at your friendly System 80! Tell the machine how much you want to spend, and it will feed it through. Watch the handle go down, the reels spin, and your money go! Then experience that familiar thrill when you hit a jackpot. Needs a 16K machine. Cat X-3661

### MATHS/SPELLING

**\$9.95**

Here's a great way to coach spelling and maths: imagine how much more interesting the lessons are if the computer is giving the problems! Help stamp out illiteracy and poor spelling - this great program can help you do it! Cat X-3662

### AIRMAIL PILOT

**\$12.95**

You're back in the early days of aviation. You must get the mail through in the shortest possible time. Your cloth-covered bi-plane must take you through unpredictable winds and electrical storms - can you make it? Cat X-3663

### INTERLUDE

**\$22.50**

This is the adults-only game for your computer. After the kids have gone to sleep, let the computer give you ideas for the rest of the night! It comes with a comprehensive instruction manual! (Note: this program is NOT available to any person under 18 years of age). Do not purchase this program if you are easily offended. Needs a 16K machine. Cat X-3665

### SIMUTEK 1

**\$17.95**

Not just one, but FIVE superb space fantasy games. Includes Graphic Trek 2000 (try to dock the Enterprise with the space station without being shot down!), Invasion Warg (protect the Earth), Star Wars (get in to the Death Star, plant a Bomb and get out again!), Space Target (a battle game) and Saucers (an action graphics game). Complete with instruction book. Needs 16K. Cat X-3685

### POKER PETE

**\$15.95**

Like a game of poker? He's a pretty shrewd player - hard to beat, although it can be done. Has really intriguing graphics, needs 16K machine. Cat X-3664

## NOW AVAILABLE SYSTEM 80 TECHNICAL MANUAL

48 pages of data, technical information, service data, minor modifications, etc. etc. Great for technically minded people with their own computer.

**\$14<sup>95</sup>**

Cat. B-6210



# DICK SMITH ELECTRONICS



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS

Basic program gives high resolution  
plus X and Y-axes

# Curve-Plotting with your Sorcerer

This function plotting program for the Exidy Sorcerer takes advantage of the computer's user-definable graphics feature to produce a high resolution display of any single-variable function. The function and the domain over which it will be plotted can be defined by the user, and the final display is most impressive.

by DANIEL WONG


The program will plot any single variable function with a high degree of resolution, and can be run on any Sorcerer computer. It produces a display which is almost continuous, without the "stair-case" effect seen in lower resolution plotting programs. The X and Y-axes and their corresponding minimum and maximum values are also depicted.

To run the program the user only has to define the function to be plotted in statement 10 and the domain of the X-axis in statement 20. XI is the minimum value that X can take, and XA is the maximum value. As listed here the program will plot the function  $X=\text{SIN}(X)$  between the limits  $X=0$  and  $X=6.3$  (in radians in this case).

Note line 1225, which confines the

possible positions of the plotted points between the values of  $-3968$  and  $-2049$ , which are the limits of the screen RAM of the Sorcerer (in decimal). Poking data into memory locations outside these limits can have strange results, and may cause the programs to crash. Adding this simple test to any program that manipulates the screen RAM can save many hours of de-bugging.

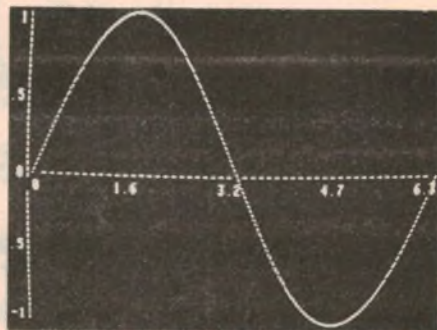Any single variable function can be plotted.  $X=\text{TAN}(X)$  gives interesting results, as does  $X=\text{EXP}(X)$ . Remember that when you define a new function to be plotted it will also be necessary to change the limits of the X-axis. The program will automatically scale the plot to make best use of the available screen area.



Above is a typical plot from the program listed on the opposite page.

Users of the Sorcerer will be aware of the potential of the machine's user definable graphics and memory mapped display. Theoretically the combination of these two features results in a display with a resolution of  $512 \times 240$  dots. The catch is that the programming for high resolution is quite complex. The subroutine from line 1020 to line 1245 in this program shows what must be done. Study of this routine will provide valuable hints to anyone interested in fully exploiting the Sorcerer's high resolution capabilities.

## ELECTRONICS AUSTRALIA HANDBOOKS



**FUNDAMENTALS OF SOLID STATE** is in its second printing, showing how popular it has been. It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works, but without the maths and abstract theory.



**BASIC ELECTRONICS**, now in its fifth edition, is almost certainly the most widely used manual on electronic fundamentals in Australia. It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. If you've always wanted to become involved in electronics, but have been scared off by the mysteries involved, let Basic Electronics explain them to you.

Available from "Electronics Australia", PO Box 163 Beaconsfield, NSW 2014. Price \$3.50 each plus 70c pack and post. Also from 57-59 Regent St, Sydney.


```

10 DEF FNY(X)=SIN(X)
20 XI=0:XA=0.3
90 DIM BK(24),X1(7),Y1(7)
100 GOSUB 900
101 PRINT CHR$(12)
102 IF Y1=YA AND Y1<0 THEN 128
104 IF Y1=YA AND Y1>0 THEN 126
110 IF Y1=0 OR (Y1>0 AND YA>0) THEN 140
111 IF YA=0 OR (Y1<0 AND YA<0) THEN 131
120 XX=INT(ABS(Y1)*25/(YA-Y1))
124 GOTO 150
126 Y1=0:YA=2*YA:GOTO 140
128 YA=0:Y1=2*Y1
131 XX=24:GOTO 150
140 XX=-1
150 FOR I=0 TO 50
160 H=I-64*XX-2227
170 POKE H,45
180 NEXT I
230 IF XI=0 OR (XI>0 AND XA>0) THEN 260
231 IF XA=0 OR (XI<0 AND XA<0) THEN 251
240 YX=INT(ABS(XI)*51/(XA-XI))
250 GOTO 270
251 YX=50:GOTO 270
260 YX=-1
270 FOR J=0 TO 24
280 H=YX-64*J-2227
290 POKE H,124
295 NEXT J
300 GOSUB 1020
301 AA=XI:BB=1:XX=XX-1:GOSUB 350
302 AA=INT(2.5*(XA-XI)+0.5)/10+XI:BB=13:GOSUB 350
303 AA=INT(5*(XA-XI)+0.5)/10+XI:BB=26:GOSUB 350
304 AA=INT(7.5*(XA-XI)+0.5)/10+XI:BB=39:GOSUB 350
305 AA=XI:BB=51:GOSUB 350
310 AA=YI:BB=YX:XX=0:GOSUB 350
321 AA=INT(2.5*(YA-YI)+0.5)/10+YI:XX=6:GOSUB 350
322 AA=INT(5*(YA-YI)+0.5)/10+YI:XX=12:GOSUB 350
323 AA=INT(7.5*(YA-YI)+0.5)/10+YI:XX=18:GOSUB 350
330 AA=YA:XX=24:GOSUB 350
335 END
350 CC$=STR$(AA)
360 XL=LEN(CC$)
370 FOR I=1 TO XL
380 DD=ASC(RIGHT$(CC$,I))
390 H=BB-I-64*XX-2227
400 POKE H,DD
410 NEXT I
420 RETURN
900 PRINT CHR$(12)
905 PRINT "Calculation in progress. Please wait!"
910 DIM Y2(50)
915 FOR J=0 TO 50
920 X=J*(XA-XI)/50
925 Y2(J)=FNY(X+XI)
930 IF J=0 THEN 985
935 K=J-1
940 FOR I=0 TO K
945 IF Y2(J)>=Y2(I) THEN 980
950 C=Y2(I):D=Y2(J)
955 FOR L=I TO K
960 A=Y2(L+1):Y2(L+1)=C:C=A
965 NEXT L
970 Y2(I)=D
975 GOTO 985
980 NEXT I
985 NEXT J
990 YI=INT(Y2(0))
995 YA=INT(Y2(50)+0.5)
996 RETURN
1020 P=1024:Q=128
1030 FOR K=-1024 TO -1:POKE K,0:NEXT K
1040 FOR I=0 TO 50
1050 A=I*8:B=I*8+7
1060 FOR J=A TO B
1070 C=J-A
1080 X=J*(XA-XI)/408
1090 YY=FNY(X+XI)-YI
1100 Y=INT(YY*200/(YA-YI)+0.5)
1110 BK(C)=INT(Y/8)
1120 IF C=0 THEN 1160
1130 D=C-1
1140 IF BK(C)=BK(D) THEN 1160
1150 P=P-8:Q=Q+1
1160 X1(C)=J-8*INT(J/8)
1170 Y1(C)=Y-8*INT(Y/8)
1180 E=2*(7-X1(C))
1190 F=7-P-Y1(C)
1191 IF F>=0 THEN 1245
1200 G=E+PELK(F)
1210 POKL F,G
1220 H=I-64*BK(C)-2227
1225 IF H<-3968 OR H>-2049 THEN 1235
1230 POKE H,Q
1235 NEXT J
1240 P=P-8:Q=Q+1
1242 NEXT I
1245 RETURN

```

# RCA

## RCA COSMAC VIP COMPUTERS

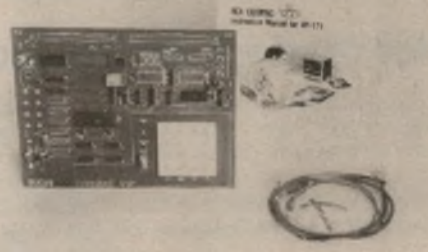

### \$139 ASSEMBLED\* TESTED AND GUARANTEED

Build a computer system one board at a time! Start at this very low price and expand as you learn up to COLOUR and FULL BASIC

#### FEATURES . . .

- RCA 1802 Microprocessor
  - ROM Operating System
  - 1k Bytes of Static RAM. Expandable to 4k on card, off-card to 32k, and with more select logic to 64k
  - Video Output to monitor, or via an RF Modulator to a TV
  - CHIP-8 Interpreter Language or Machine Language programmable. CHIP-8 has you programming the very first night!
  - Cassette Interface — 100 bytes/sec!
  - Audio Tone Generator
  - Hexadecimal Keypad
  - Single 5 Volt operation
  - Instruction Manual, with games, schematics, CHIP-8 and much more
  - 7-day Money-Back Guarantee
  - 3-month Parts and Labour Guarantee
  - Thousands sold in USA
  - Ideal for low cost control applications
- \* User need only connect cables (supplied), a power pack, regulator and modulator (optional) and an 8 ohm speaker (supplied).

#### OPTIONAL ACCESSORIES . . .

User Guide — Additional information for the beginner and the newcomer to CHIP-8 Recommended.  
Expansion Kit — Extra RAM, and full expansion facilities allowing the use of the following —

Memory (RAM) Boards	EPROM Board
Sound Generator — 256 note	EPROM Programmer
Stereo Music Synthesiser	Auxiliary keypads
Quadrasonic Expander Board	Tiny BASIC (Integer)
ASCII/Numeric keyboard	Floating Decimal Point BASIC (16k!)

Colour Board (PAL) and Interactive Data Terminal — Coming Soon!  
Software — the US User Group has already gathered hundreds of programmes, applications and hardware ideas.  
Several books have been published, in addition to RCA's own manuals.  
Phone Cash-On-Delivery (ie. collect at PO) orders accepted.  
Tax Exempt Price of VPIII for students, colleges, schools, etc — \$126.  
Other prices as listed.  
Units are ex-stock Cut out or copy coupon.

( ) VPIII Microcomputer	\$139.00	\$ . . . . .
( ) Power Pack and Regulator	\$10.00	\$ . . . . .
( ) User Guide Manual	\$5.00	\$ . . . . .
( ) RF Modulator Kit	\$5.00	\$ . . . . .
( ) Post Pack Insurance - Cash Orders	\$3.00	\$ . . . . .
( ) Post Pack Insurance - COD Orders	\$5.00	\$ . . . . .
( ) Priority Paid Mail (Optional Extra)	\$2.00	\$ . . . . .
	<b>TOTAL:</b>	<b>\$ . . . . .</b>

Name \_\_\_\_\_ Signature \_\_\_\_\_  
Address \_\_\_\_\_ Postcode \_\_\_\_\_  
Phone Nos: Home \_\_\_\_\_ Work \_\_\_\_\_  
I understand that this order is subject to a 7-day Money-Back Guarantee.  
EA2/B1

**J. R. COMPONENTS PTY LTD**  
PO Box 128, Eastwood, NSW 2122  
Ph (02) 85 3385



# Letters to the editor

## We'll let readers be the judge Pt. 2

Thank you for publishing my letter in your December issue. May I now clear up for you one or two statements in that letter.

Firstly, I fully agree with you that Dick Smith kits are not the responsibility of EA.

Secondly, I wasn't accusing EA or DSE of deliberate conspiracy. I was, however, taking your "Information Centre" to task for lack of technical thought in its reply to a reader's problem. Nothing was said about this in your reply.

My assumption that EA and DSE have a close association is based on the fact that "Column 80" is written by a DSE employee, and the original article for the "Playmaster AM/FM Stereo Tuner Clock" stated that the project was done in association with DSE. Lastly, the first errata that appeared for the project concerned itself with DSE kits, the change required for the AM/FM mono/stereo switch.

I also stated that I have been an EA reader for 20 years; that should imply that I hold your magazine in good standing. And as far as DSE is concerned, although I have had some problems with these kits due to missing parts etc, they have been very helpful and therefore, no complaints.

You must surely agree that as you design for a public which has varying degrees of technical expertise, your "Information Centre" must be accurate, and a bit of thought put into answers to the readers queries. I would venture to say that if one reader puts in a query, there could be a number of other people having the same problem, who would also use that information for their own projects. You would never find out about these people.

Take the case of JS, say 10 other readers had the same problem and saw that uninformative reply. They took the advice to try and fix their tuners, then they would have parted with \$18 each. Tell me who is out of pocket when they find they still have the same problem?

In my case I knew of about a dozen people with that problem whilst I was in Sydney and a couple since I have lived down here. Two of these people had already bought new chips and, of course, still had the problem.

I've only talked about one case, but if that is representative of the replies given by the "Information Centre" it won't be an isolated case.

I don't intend to start a series of letters to aim criticism at your magazine, I'm far too busy in my own activities for that. But I think a bit of thought in your "Information Centre" pages would keep EA to the high standard that we are used to.

M. Rogerson,  
Werribee, Vic.

**COMMENT: As with the rest of the magazine, we take a great deal of care in preparing answers for the Information Centre. However, can you imagine the difficulty of trying to troubleshoot a problem which you have not personally experienced? We are often in this position - trying to diagnose and cure faults with sometimes very vague information supplied by readers, and without the benefit of having the faulty project in front of us to check our suggestions.**

**We do our best to help readers who have problems with our projects, but we do not claim to be infallible. Certainly, we did not expect that after 18 months on the market the AM/FM tuner kit would suddenly be sold with wrong instructions regarding the transistor leads.**

**Finally, we would like to inform you that it is strict editorial policy that we admit to all mistakes and publish corrections in the first available issue. How else could we maintain credibility with our readers?**

## Support for EA & AC wiring rules

Having read the letter from your disgruntled correspondent (M.R.) in the December 1980 issue of EA, I feel constrained to write a note in your support. Not, I guess that you need it, or you would long ago have fallen by the wayside.

In a long time in electronics (40 years approacheth) and having subscribed to about 0.7 cubic metres of EA, RT&H, & R & H (I have some 33 years of them), I cannot recall ever having seen your support given to a questionable practice of any kind. Further, it has only been on the rarest of occasions I can recall the odd technical boo boo, and no one could have been quicker than your journal in correcting such points in a subsequent issue, once the matter has been realised. Enough of that . . .

On the same page as the letter referred

to above is one from Mr Stephen of the Energy Authority of NSW. It does bring up a point that leaves some measure of concern in my mind. The several articles that you print on projects involving work on the AC power system - the "Light Dimmer" being one such - can lead experimenters into a dubious zone. As with NSW, all states have fairly rigid "hands off the AC mains" rules.

I would be the first to compliment you on the safety comments you invariably add to such projects - rather more than other journals are apt to offer. However, apart from the very real points made by Mr Stephen, I suspect that there are one or two other matters also not generally realised - such as that unauthorised modifications to wiring may void the building fire insurance.

Equally real can be the effect on the RF Spectrum - you have reasonably well discussed this in "Forum", EA October issue. Again, the unwanted side effects from DC generated - vide the amendment to AS100 - by miscellaneous appliances are rather more relevant than the slightly abbreviated comment, with some added levity, that graced "Forum" in the June 1980 issue. Having had some little experience in this area, the "tip-of-the-iceberg" syndrome is again with us.

Brian Byrne,  
Indooroopilly, Qld.

## Robots & unemployment

Dear Professor Blatt,

May I venture to compliment you on your interesting and thoughtful article in Electronics Australia, December 1980, on the effects of technology on unemployment. I heartily agree with your views.

Although, to a minimal extent, people are already paid a living allowance, eg family allowances or the dole, I should like to see the introduction of a points system for living allowances. In such a points system, there would be points for getting born, for educational level reached, for looking after the young, old or helpless, for providing goods or services for others, for undertaking management duties, for providing professional services, for teaching, for work in science, engineering and art, and indeed in any activity which contributes to the quality of life.

The living allowance for minimum points should provide a full life within the capabilities of the particular individual, eg a baby or handicapped person. Those individuals who choose to advance and do work of the highest quality should receive the highest points and the highest living allowance.

All money, or tokens, paid for goods and services, including receipts from exports, would be paid into a regional, national or even world living allowance

fund from which would be disbursed the various allowances.

At the start of such a scheme, everyone would at least retain their present income and the scheme would evolve fully and slowly as generations of people grew up and died.

What a Utopian dream to set against the present omens of disaster! But surely, the massive human brain was not evolved for the purpose of its own destruction, but rather for the perfection of the species.

G. J. Winsbury,  
Heathcote, NSW.

## NSW was not first!

I would like to point out to Ron de Jong a small, but important, error in his "Selectalott" article (December 1980), where he states "... Lotto is played only in NSW, with a similar game called Tattslotto in Victoria ..."

It should read: "Tattslotto is played in Victoria, with a similar game called Lotto in NSW".

Here, NSW must concede, they were not first!

M. J. Robinson,  
Barkers Creek RSD, Vic.

## Suppliers for the battery charger



Attached herewith is a list of suppliers who will be stocking the PS518 Battery Charger Kit described in the current issue of "Electronics Australia" (Editor's Note: see p48):

VICTORIA: Kalextronics Pty Ltd; Stewart Electronics Pty Ltd; Davred Wholesalers Pty Ltd; Ellistronics Pty Ltd; Truscott Electronics; Radio Parts Pty Ltd; Magrath's Pty Ltd.

NSW: Electronic Agencies; George Brown Pty Ltd; Browntronics Pty Ltd; Martin De Launay Pty Ltd; Davred Pty Ltd; Sheridan Electronics; Radio Despatch Service; D. J. Coulter Wholesale (Newcastle); Electronic Components (Canberra).

SA: Ktronics Pty Ltd; Gerard & Goodman Pty Ltd; Protronics Pty Ltd; M. S. McLeod Pty Ltd.

QLD: Audiotronics; Belsound Pty Ltd; GEC (Aust) Pty Ltd; Gayrad Pty Ltd; Lighting & Electrical; Rapco Auto Parts; Traders A.G.S.

WA: Alltronics Pty Ltd; Atkins Carlyle Pty Ltd.

W. Bryer, Advertising Manager,  
A&R Electronics Pty Ltd,  
Box Hill, Vic.

## ELECTRONICS AUSTRALIA

# projects & circuits

Number 2

### AUDIO PROJECTS

LOUDSPEAKER PROTECTOR FOR HI-FI SYSTEMS .....	12
DIGITAL METRONOME WITH ACCENTED BEAT .....	22
REMOTE TV HEADPHONES .....	29
TOROID FILTER CUTS RADIO, TV BREAKTHROUGH .....	37
SIMPLE MIXER FOR PICK-UP AND MICROPHONE .....	42
UNIVERSAL HEADPHONE UNIT .....	65
ACTIVE FILTER UNIT FOR CROSSOVER NETWORKS .....	78
VOICE-OPERATED RELAY .....	87

### POWER SUPPLIES AND POWER CONTROL

SPEED CONTROL FOR ELECTRIC DRILLS .....	15
FULLY PROTECTED, REGULATED POWER SUPPLY .....	58
MOODLIGHTING WITH THE VARILIGHT MK 2 .....	62

### AUTOMOTIVE PROJECTS

A CONTROL UNIT FOR INTERMITTENT WIPER ACTION .....	6
AN UPGRADED CAPACITOR DISCHARGE IGNITION SYSTEM .....	18
A DWELL METER FOR ENGINE TUNE-UPS .....	26
TACHO FOR TUNE-UPS .....	46
A TRAFFICATOR REPEATER FOR CARAVANS AND TRAILERS .....	70

### CB PROJECTS

POWERMATE: 13.8V SUPPLY FOR TRANSCEIVERS .....	10
PREAMPLIFIER FOR 27MHz .....	54
SHORT-WAVE CONVERTER FOR THE 27MHz BAND .....	73

### MISCELLANEOUS

10GHz RADAR BURGLAR ALARM .....	2
MODEL TRAIN CONTROL WITH SIMULATED INERTIA .....	32
MULTI-BAND VERTICAL AERIAL .....	45
AN ELECTRONIC ROULETTE WHEEL .....	49
AN IN-CIRCUIT TRANSISTOR TESTER .....	68
MODULAR DIGITAL CLOCK .....	82
NOVEL "LEDS AND LADDERS" GAME .....	90
SIMPLE PROXIMITY SWITCH FOR A NOVEL DOOR CHIME .....	94

### CIRCUIT & DESIGN IDEAS

HEE-HAW SIREN FOR TOYS .....	36
MODEL TRAIN SIGNALLING SYSTEM .....	48
MICROPHONE PREAMPLIFIER .....	67
TEMPERATURE ACTUATED SWITCH .....	81
WATER LEVEL ALARM .....	89
2-PHASE CMOS CLOCK OSCILLATOR .....	93
ECONOMICAL CRYSTAL OVEN .....	96

Available from "Electronics Australia", 57 Regent St, Sydney.  
PRICE \$3.00 OR by mail order from "Electronics Australia", PO  
Box 163, Beaconsfield 2014. PRICE \$3.70.

# TWICE THE FUN

## WITH DICK SMITH FUN WAY INTO ELECTRONICS Vol.1 & Vol.2



Cat. B-2600

**\$4.95**



Cat. B-2605

**\$6.95**

Post and packing: \$1 per book.

For the absolute beginner this book is a must. 20 projects from a beer powered radio to a continuity tester, all built without the need to solder. The unique 'breadboard' method of construction enables you to follow the circuit via the wires and because every project is battery powered they are perfectly safe! Learn electronics the FUN WAY.

**Kits for Fun Way 1.** For projects 1-10 all the parts to build any one of the projects, including breadboard. Cat. K-2600 @ \$6.90. For projects 11-20 Cat. K-2610 (this is used in conjunction with Kit 1) @ \$7.50. Buy the book and both kits for only \$17.50 Cat. K-2615 and save \$1.85 on the individual prices!

**Our 7 day money back guarantee means you can not loose.** If you're not completely happy with either book, you may return the book in its original condition within 7 days for a full refund of the purchase price. What could be fairer?

### FUN WAY TWO KITS: EASY, SAFE & ECONOMICAL!

#### MULTI-PURPOSE LED FLASHER .... \$2.75

A really simple kit that can be used as a warning device, electronic jewellery, etc. Cat K-2621

#### DING DONG DOORBELL \$4.00

Welcome visitors to your home with this integrated circuit doorbell! Cat K-2622

#### MORSE CODE TRAINER \$4.00

This simple oscillator circuit lets you learn Morse code the easy way! Cat K-2623

#### UNIVERSAL TIMER \$5.00

Use it as an egg timer, a dark-room timer, etc: in fact, it's got a lot of applications! Cat K-2624

#### ELECTRONIC DICE .... \$4.75

Throwing a dice is old hat: do it electronically! Simple circuit has other uses too. Cat K-2625

#### MONOPHONIC ORGAN \$7.50

Easy to build, and easy to play! And it even has 'vibrato' - just like the big ones! Cat K-2626

#### POCKET TRANSISTOR RADIO \$7.50

Simple to build, and it's nice and small. Listening is so much more fun! Cat K-2627

#### TOUCH SWITCH \$4.90

One touch on, next touch off - or 'on while touched'! Dozens of uses in the home. Cat K-2628

#### MOSQUITO REPELLER \$4.50

Don't get eaten by mozzies scare them away electronically. Take it anywhere. Cat K-2629

#### SIMPLE AMPLIFIER \$6.00

A useful little amplifier for all those projects needing audio amplification. Cat K-2630

#### WIRELESS MIC. \$6.50

A tiny transmitter that can be received on any FM receiver. A great little kit! Cat K-2631

#### LIGHT ACTIVATED SWITCH \$4.90

Highly useful for alarms, night light switches, etc etc. Sensitive and reliable. Cat K-2632

#### METAL/PIPE LOCATOR \$6.00

A simple BFO circuit you can use to find metals, pipes, wiring, etc - maybe gold! Cat K-2633

#### SOUND ACTIVATED SWITCH \$6.50

Picks up sound waves and trips a relay. Use as a telephone bell extender, too. Cat K-2634

#### HOME/CAR BURGLAR ALARM \$6.00

Learn how burglar alarms work when you install your own! For home or car. Cat K-2635

#### ELECTRONIC SIREN \$4.50

Great for alarm use - or where any warning is required. Good for kids toys, too! Cat K-2636

#### LED LEVEL DISPLAY \$8.50

This fascinating project shows you the audio level of any amplifier. Cat K-2637

#### INTERCOM UNIT \$8.50

Communicate! Build this intercom and talk between rooms, etc. Cat K-2638

#### LED COUNTER MODULE \$7.50

Learn how digital circuits work by building a counter. Count slot car laps, etc. Cat K-2639

#### SHORTWAVE RECEIVER \$6.50

Listen in to the exciting world of shortwave radio: amateurs, foreign countries! Cat K-2640

# DICK SMITH ELECTRONICS



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS

# AMATEUR RADIO



by Pierce Healy, VK2APQ

## Amateur radio — and the need for a better public image

A good public image is a virtual necessity for almost any organisation, and particularly so for one which is under continual official and public scrutiny. Failure to project an accurate image may well contribute to the eventual demise of such an organisation.

This observation applies particularly to amateur radio, which owes its existence largely to its past history of contributions to the art and science of radio communication, and to its service to the community in times of emergency. But it is not sufficient that we provide these services, we must see to it that the public know what we have done, what we are doing, and what we can do.

Amateur radio is unique in many ways. One is that, in spite of its amateur status, it provided the foundations for today's commercial radio communications; local, international, entertainment etc. Yet it remains a hobby type activity to be enjoyed from home, from portable locations, from one's vehicle, and involving a wide range of techniques. Quite outstanding claims, but factual nevertheless.

That is an approach that can be used when introducing the general public to amateur radio. This opinion has been reinforced by my association with the amateur radio demonstration station, VK2BQK, at the Museum of Applied Arts and Sciences Museum Sydney, since its inception in December 1978. It was highlighted when, just prior to the 1980 festive season, I was asked questions by a visitor to the Museum.

This visitor, with a teenage family, had come upon the station during an unplanned visit caused by inclement weather on a weekend outing. He expressed amazement at the achievements, services given in emergencies, and the fact that the potential of amateur radio was not more fully publicised, adding that he also had a background of community activities. In fact, the only remarks about amateur radio that stirred in his memory were derogatory insinuations made about "ham" operators in the news media. But he now realised that these

reports had been made by persons without any knowledge of amateur radio and with a mental fixation that all wrong doers on the air are amateur radio operators.

Another point that visitors are interested in is the international aspect of amateur radio and the national amateur radio societies rather than the parochial type radio clubs.

It is on these themes that the Wireless Institute of Australia should actively publicise amateur radio.

It has been suggested that, with the expansion of community radio, the opportunity exists for the WIA to publicise the Amateur Service; let the outstanding status of amateur radio be made public.

Within these notes are instances where amateurs are providing community services that receive little or no publicity through everyday news media.

### A NEW BOOKLET

For those amateurs who wish to hold more fulfilling QSOs with the many Japanese amateurs on the bands, a booklet has been published by Westlakes Radio Club. Titled "QSO JA NOW", by Paul Rodenhuis, VK2AHB, it sets out a basic QSO in Japanese (Roman text) in an easily followed manner.

Commencing with the basics of equipment, signal reports, etc, it progresses through weather, counting, time, personal details, job, and other points of general conversation.

A companion cassette tape assists with the pronunciation of the Japanese words and phrases in the booklet. The aim is to promote more QSOs between Australian and Japanese amateurs, beyond the usual English stereotype.

The cost of the booklet is \$2.95; including the cassette tape \$4.95.

Available from Westlakes Radio Club, PO Box 1, Teralba, NSW 2284.

The author, Paul Rodenhuis, VK2AHB, speaks Japanese fluently. He recently spent a month touring Japan as guest of a wide cross section of Japanese amateurs. As an amateur his keen interest is RTTY, and he is currently secretary of the Australian National Amateur Radio Teleprinter Society.

The booklet could also have an educational aid value to students.

### RADIOTELETYPE NEWS

How many give a thought to the voluntary effort that goes into producing regular news bulletins? Particularly those broadcast on behalf of your own or other amateur radio societies. Well, here are some statistics about the Australian National Amateur Radio Teleprinter Society RTTY broadcasts in Sydney. These are made through VK2TTY each Sunday at 0030 UTC on 7045kHz and 14090kHz; 21095kHz at 0130 UTC and 3545kHz at 0930 UTC. Relays are made on 146.6MHz at 0030 UTC and 0930 UTC.

News bulletin number 166 was broadcast on December 21, 1980. In just over three years one and a half million words have been transmitted, involving 1142 metres of paper; 5425 metres of paper tape; 43 ribbons, and 525kWh of power from the AC mains.

Time occupied in collecting, correlating, editing, and producing tapes, and transmitting these bulletins by the originating and relay stations cannot, with any degree of reasonable accuracy, be even estimated.

Nevertheless, these statistics are worthy of consideration and appreciation by those who enjoy this news service. The service also has a large overseas audience and co-operates with the American Radio Relay League and British Amateur Radio Telegraph Group teletype news services.

If interested in radioteletype contact the Secretary, ANARTS, PO Box 860, Crows Nest, NSW 2065.



# AMATEUR RADIO

A visitor to Australia during December 1980 - January 1981, was Mal Westwood, 9M2MW from Penang, Malaysia. During his trip he visited amateurs in Western Australia, New South Wales, South Australia and Victoria, discussing radioteletype activities and equipment with amateurs, and visiting their stations. While in Sydney, stations visited included VK2SG, VK2ABH and VK2APQ.

Mal was the first amateur in Malaysia to be active on RTTY.

## NAVY WEEK - TASMANIA

This story comes from Ted Beard, VK7EB, of Hobart. Ted is a member of the Royal Naval Amateur Radio Society (RNARS), and his story tells how amateur radio participated in Navy Week celebrations during November 1980. It is another example of community service amateur radio can provide.

"What has Navy Week to do with amateur radio? Generally speaking nothing. But for the training ship TS Derwent and the RANR Cadets in Hobart, Tasmania, quite a lot.

"For as long as I can remember (before WW II) units of the RAN have sailed up

the Derwent River and entertained the locals during Navy Week.

"This year Lieut Cdr Max Webb, skipper of the TS Derwent, received a signal advising that, as units of the RAN had been deployed to other areas, no units of the fleet would be visiting Hobart for Navy Week. RANR Cadets were therefore requested to assist HMAS Huron, the Navy Depot, to entertain the public on Sunday, November 2, 1980.

"One bright news item was that Lieut Cdr Ron Coleman and crew of TS York, from Georgetown, northern Tasmania, were visiting TS Derwent for the weekend. Ron was to be commanding officer and, being an ex-wartime bunting tosser (visual signals - flags, semaphore, and light), this raised my hopes somewhat, as I was in charge of communications at TS Derwent.

"A program of activities for the cadets was evolved by Sub Lieut Ron Smith. Four watches were formed and classes held in navigation, firefighting, sailing, and rifle shooting. All activities were on a rotational basis.

"HMAS Huon's work boat was used to give rides to visitors. Naval Cadet Signaman D. Lacey maintained contact with his opposite number R. Scholes at TS Derwent with an aldis signalling lamp and an HF walkie talkie as alternative back up.

"Earlier I had installed an IG 701 amateur transceiver in the communications room to establish contact with

VK6DV, VK6TO and ZL1AHK, all members of the RNARS. We also made contact with the American Naval Base at Guantanamo Bay in Cuba.

"At 6.30pm (0730 UTC) on a pre-arranged schedule, contact was made with G3ASM in Stockton-on-Tees in England. A lengthy contact ensued in which members of the ship's company participated. All concerned, including Hank, G3ASM, enjoyed the experience.

"Other stations worked included VK2BVH, VK2BWQ and VK2APQ.

"In conclusion the skipper has asked me to extend an invitation to any RANR cadets to visit TS Derwent should they visit Hobart. Parades are held on Friday nights and sailing and other activities every Saturday."

## NORTH QUEENSLAND CONVENTION

Preparations are already well in hand for the fourth biennial North Queensland Convention to be held by the Townsville Amateur Radio Club over the weekend September 26-27, 1981.

This will be a gathering of amateur radio operators and enthusiasts not only from Australia but also from overseas. As far as it is known, the convention will be the first planned to use the new international airport facility at present being constructed at Townsville.

The convention has already attracted the interest of several amateur radio operators from South America and it is also hoped that a number will arrive from Japan and USA.

Not only will there be activities and displays for amateurs and computer hobbyists, there will also be items of interest for other members of the family. Accommodation will be available at the venue over the weekend. For those wishing to stay longer, there are a number of high class hotels, motels, or caravan parks.

For further information contact - The Publicity Officer, Townsville Amateur Radio Club, PO Box 964, Townsville, Qld 4810.

## WIA NEWS

Federal Executive of the Wireless Institute of Australia have agreed that the Worked All VK Call Areas (WAVKCA) award should be opened for Australian amateurs from January 1, 1981, for contacts made on or after that date.

The rules of this award will be suitably amended, and will require a total of 77 contacts to qualify.

The contacts are to be made up as follows: Ten on at least three bands for each call area VK2 to VK7 inclusive; five on two bands for VK1 and VK8 call areas; four in three territories in VK9 call areas; and three in two locations of the VK0 call area.

A separate award will not be available for any particular mode; proof of contact by production of QSL cards for contacts claimed.

## BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076  
(ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)

INTERSTATE AGENTS  
ROGERS ELECTRONICS  
ADELAIDE PHONE 42 6666  
J E WATERS PTY LTD  
SYDNEY PHONE 666 8144



BSC TELEX AA36004

## WATCH CRYSTALS




## SPECIFICATIONS

1. Nominal Frequency	32.768KHz
2. Frequency Tolerance	±30ppm/28° ±1°C
3. Drive Level	1μW max
4. Series Resistance	31.0k ohms max
5. Q Factor	40000 min
6. Parabolic Curvature Constant	Less than -0.04pp m/°C (Refer Fib. 1)
7. Turnover Temperature	28.0°C ± 5°C
8. Capacitance Ratio	700 max
9. Storage temperature Range	-30°C ~ +80°C
10. Operating Temperature Range	-10°C ~ +60°C
11. Aging rate	Less than ± 5ppm/year
12. Shock	Less than 5ppm for 50cm Hammer Shock Test
13. Package size.	

DILMOND INSTRUMENTS  
HOBART PHONE 47 9077  
FRED HOE & SONS PTY LTD  
BRISBANE PHONE 277 4311  
WEST TEST ELECTRONICS  
PERTH PHONE 337 6393

This Service Monitor sets the standards for what a Communications Test Set Needs to be!

# FM/AM-1000S

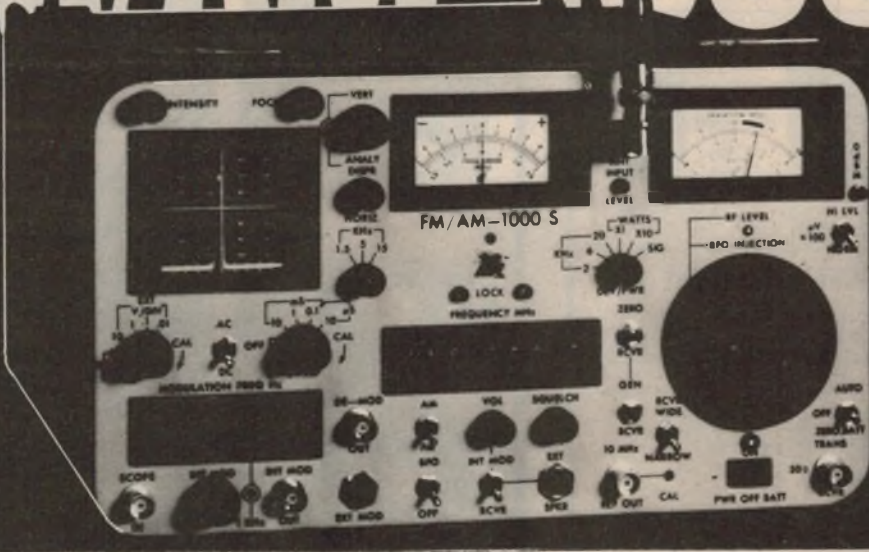

**We gave you the features you needed and the performance you expected to get the job done... on the bench and on the go!**

The FM/AM-1000S is a compact, light weight, completely portable test set which is easily and efficiently used with no sacrifice in versatility. Its ruggedly constructed circuits are housed in a deep-drawn, heavy gauge metal case, allowing it to withstand the rigors of portable operation as well as being a highly functional bench instrument.


As a generator, the FM/AM-1000S features continuous frequency coverage from 100 Hz to 1 GHz, AM or FM modulation, internal variable audio tone generator, 1000 Hz fixed tone generator, and 0 dBm RF output level into 50 ohms.

Automatic switching to monitor mode occurs at 100 MW, allowing measurement of transmitter frequency, FM deviation or 9% AM modulation, and RF power throughout the operating range of the test set.


A sensitive receiver allows measuring the characteristics of radiated signals, including SSB and DSB. The Beat Frequency Oscillator features variable injection level and is phase-locked to the master oscillator for precise suppressed carrier frequency measurement. The 15 kHz Narrow IF selectivity allows monitoring a desired signal within 25 kHz of adjacent channel interference without difficulty.

The Oscilloscope/Spectrum Analyzer operates simultaneously with all other indicators to provide detailed analysis of monitored signals. The 70 dB dynamic range of the analyzer is equal to that of many individual analyzers.

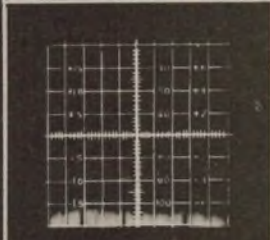
**Features... Performance... Portability.** The FM/AM-1000S Communications Service Monitor has them all — plus it's priced below comparable, competitive test equipment. Call the distributor in your area today for a demonstration. Let us prove it!



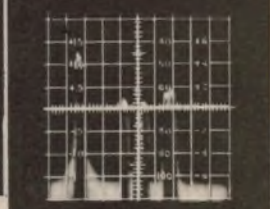**WIDE DISPERSION:**  
Analyzer sweeps  $\pm 3$  MHz from selected frequency (30 MHz span)



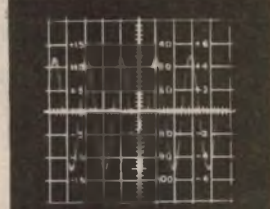**NARROW DISPERSION:**  
Analyzer sweeps  $\pm 0.5$  MHz from selected frequency (1 MHz span)



**OSCILLOSCOPE:**  
Oscilloscope features DC to 1 MHz frequency response




**Vicom International Pty. Ltd.**

68 Eastern Road,  
South Melbourne, Vic. 3205  
Phone (03)6996700

339 Pacific Highway,  
Crows Nest, NSW. 2065  
Phone (02)4362766

N.Z. (Wellington) 287946

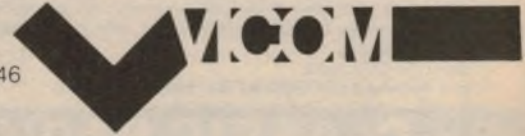

## SPECIAL PURCHASES

### NEW PLESSEY-FOSTER & AWA HI-FI SPEAKER SYSTEMS POWER RATING 50 WATTS RMS FREQUENCY RANGE 30 to 18000 CYCLES

This HI-FI speaker system uses the top of the range Foster C00F05 8" woofer which is a free edge cone speaker with a resonant frequency of 27 cycles and a 2" voice coil, weight 3577G (magnet weight 607G) Two AWA 4" tweeters with ceramic magnet & curve-linear cones are supplied also crossover components, grille cloth, innabond lining & cabinet plans. (Cabinet not supplied.)

**\$59.00**

(List price was over \$100)  
Post & packing NT & NSW \$3.50 per kit  
Qld, Vic \$5.50; SA, WA \$8.00 per kit  
Foster C00F05 8" woofer max power  
80W available as separate unit at \$47.50 +  
post & pack as kit.



### RANK-ARENA 2 WAY SPEAKER

- 10 Watts RMS
- 8 ohm impedance
- 8" woofer with tweeter
- Supplied with leads and plugs
- Teak finish

**\$42.00  
PER PAIR**



A similar system available in walnut finish. Dimensions 18"H, 11"W, 9 1/2"D. Freight extra per rail air or road transport.

### GARRARD CC10A RECORD CHANGER

**\$20.00**

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template and instructions. Post & packaging NSW \$2.50. Int \$3.50.

### SPEAKER GRILLE FABRIC AT 1/2 PRICE

AVAILABLE IN LIGHT & MID BROWNS. WIDTH 54"

**\$4.80** Per YARD. Post & Pack \$1.75.  
Send two 20c stamps for samples.

### NEW EMI RECORDING TAPE

HIFI LOW NOISE  
At less than 1/2 list price  
HDP12 5" reel 1,200ft  
double play 2.95 4 for **\$10.00**.  
PP \$2.00



### EMI SUPER C90 CASSETTES

8 for \$10, P&P \$2.00



### NEW STANDARD BSR RECORD CHANGERS MODEL C129R

**\$36.00**

Fully automatic turntable plays up to six records automatically and single records automatically or manually as required. 11" turntable. Cue & pause control. Record speeds 33 1/3, 45 and 78 rev/min. Finished in black with silver trim. Player and changer spindles supplied. Fitted with ceramic cartridge. Post & packing extra. NSW \$2.70; Vic, Qld, SA \$3.70; WA \$4.70 (registered post \$2 extra if required). Spare cartridge and stylus for above \$4.50 (list price \$10.00).

### NEW AWA HI-FI SPEAKER KITS 8" 2 WAY 3 SPEAKER SYSTEMS

AT LESS THAN 1/2 LIST PRICE

POWER RATING, 20 WATTS RMS. IMPEDANCE 8 OHMS Frequency range 46 TO 18,000 CYCLES

Supplied in kit form (less cabinet) each kit comprises: One AWA 8WAC 8in bass unit, two AWA 4MBC 4in tweeters with ceramic magnets & curve-linear cones, crossover components, grille cloth, innabond lining and cabinet plans.

CABINETS AVAILABLE

Post & packing extra: NSW \$2.50; Interstate \$3.50.

**\$20**



PER KIT

## CLASSIC RADIO

245 PARRAMATTA RD., HABERFIELD 2045

PHONES 798-7145, 798-6507

# PRECISION FANS

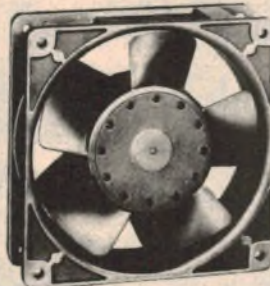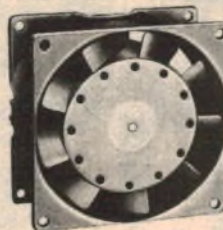

## THE SUPER GROUP

### Range of application:

Fans for cooling, ventilation and de-aeration of electrical and electronic units and systems as:

electronic data processing system with all external units needed for this system, automatic booking machines, business machines, measuring instruments, appliances of the wireless engineering, photo copying equipment, acoustic instruments, high frequency generators, clean air cabinets, lift cages, welding equipment, motors and generators (additional ventilation).

## INSTANT COMPONENT SERVICE

marketing  
division of

**STC-CANNON** COMPONENTS  
PTY LTD

248 Wickham Rd, Moorabbin, Victoria, 3189

ADELAIDE: 268 7088

BRISBANE: 44 6667

MELBOURNE: 555 9566

SYDNEY: 693 1666

# AMATEUR RADIO

## VICTORIAN CONVENTION

The Victorian Division WIA will hold a convention on February 28 and March 1, 1981, at the Latrobe University, Glen College, Bundoora, Victoria. Activities: Friday evening, social starting at 8pm. Saturday evening, convention dinner. Master of ceremonies: Harold Hepburn, VK3AFQ, plus guest speakers.

Saturday and Sunday: Trade, industry, and educational display, amateur TV demonstration, swap and trade table, book sales, and competitions, including equipment and field events.

For further information contact. The Secretary, Victorian Division, WIA, 412 Brunswick St, Fitzroy, Victoria, 3065. Phone: (03) 417 3535.

## RADIO CLUB NEWS

### WESTERN AUSTRALIAN VHF GROUP:

During a holiday weekend in October 1980 an expedition was organised by members of the WA Repeater Group to Mount Toolbrunup. The purpose was to set up the group's channel 8 portable repeater, VK6REE. Mount Toolbrunup is in the Stirling Ranges, in the south west corner of WA, and is 1100 metres high. The climb took 2½ hours, carrying all the equipment, including two car batteries.

Setting up the station took about one hour. The repeater, cavity filters, batteries, and other bits and pieces were installed in a small cave from where the coaxial cable was fed inside a six metre high aluminium tube mast to the base of a Ringo antenna.

The moment the repeater was switched on signals were heard from all over the countryside. During the afternoon several of the party went mobile to test the coverage.

"The range of the repeater had to be heard to be believed. The experience of using a 2-watt handheld to talk to

anyone within a circle of 160 kilometres was quite incredible."

The mobile coverage was also quite phenomenal; one contact was maintained over a distance of 300km. The repeater was heard in Perth and one brief contact was made. Stations in Bunbury were also worked.

Whether a permanent repeater can be installed on Mount Toolbrunup, which is located in a National Park, is being investigated by the WA repeater group.

(Extract from the WA VHF Group Bulletin Nov 1980).

### CENTRAL COAST AMATEUR RADIO CLUB:

Final preparations are being made by the committee for the Club's 24th annual field day to be held at the Gosford Showground on Sunday, February 22, 1981. Program details were given in last month's issue of these notes. Make it a family weekend on the beautiful central coast of NSW.

A group of seven students attending the classes at the clubrooms, Kariong, will be sitting for the amateur licence examination held by the Department of Communications, in March 1981.

### WAGGA AMATEUR RADIO CLUB:

In answer to a request from the Wagga FM Community Radio Co-op, members of WARC helped in the painting and restoration of the Co-op's tower at the top of Williams Hill. Although it was estimated that it would take two weekends, the task was completed on the first. A community service that was greatly appreciated.

### WESTLAKES RADIO CLUB:

Novice licence, computer, and construction classes conducted by the WRC will commence during the first week in February, 1981. Details of the classes and other club activities may be obtained by writing to the Secretary, WRC, Box 1 PO, Teralba, 2284 or call at the club rooms in York Street, Teralba, NSW. Telephone (049) 58 1588. Club station VK2ATZ is net control on Thursday evenings at

8.30pm on 29475kHz or 3565kHz and Sunday 11.45am on 1912.5kHz.

### TOWNSVILLE AMATEUR RADIO CLUB:

At the annual general meeting the following officers were elected for 1981.

Roger Cordukes, VK4CD – president; Bill Sebbens, VK4XZ and Peter Renton, VK4PV – vice-presidents; Bob Mann, VK4ZFX – secretary; Ken Telford, VK4ZOC – treasurer.

The retiring president Bill Sebbens, VK4XZ complemented all those who assisted in club activities during his term of office. Included were the class instructors, led by Ross Wilken, VK4ZZW, for their efforts in helping more than 20 members to obtain either an amateur licence or upgraded to higher qualifications.

The report closed with the thought that there is a need to promote the image of amateur radio, possibly through the avenue of community service type exercises.

The TARC club station is VK4WIT and a repeater, VK4RAT, two-metre channel 6700. Postal address, PO Box 964, Townsville, Qld 4810.

### ILLAWARRA AMATEUR RADIO SOCIETY:

On the weekend March 28-29, 1981, members of IARS will be joining in the activities commemorating Laurence Hargrave's work as a pioneer in aviation, Displays of Hargrave's work, kite flying, etc, are expected to be well attended.

The club station VK2AMW will operate from the site of the celebrations during the whole weekend and at the same time inaugurate the Lawrence Hargrave Award.

Keep the dates clear and watch for further details of the award.

### SOUTH WEST AMATEUR RADIO SOCIETY:

This society, centred generally on the Riverina-Murrumbidgee irrigation areas in southern New South Wales, holds quarterly meetings and invites all amateurs in southern NSW and Northern Victoria to attend.

Regular weekly nets are held on Wednesdays at 2030 hours during daylight saving period and 2000 hours EST on 3610kHz. The call sign is VK2DEI.

For further information write to the Secretary SWARS, Sid Ward, VK2SW, C/o PO Box 71, Koorlinga, NSW 3650.

Radio clubs and other organisations, as well as individual amateur operators, are invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown

TADIRAN

# The Fail-Safe 10-Yr Lithium Batteries

BY TADIRAN ISRAEL ELECTRONICS

Power CMOS with single cell.  
Nominal Voltage 3.4V per cell.

TECNICO ELECTRONICS

P.O. Box 50, Lane Cove, N.S.W. 2066. Tel. (02) 427 3444  
P.O. Box 520, Clayton, Vic. 3168. Tel. (03) 544 7833

## SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to  
**THE COURSE SUPERVISOR,  
W.I.A.**

P.O. BOX 123,  
ST. LEONARDS, NSW 2066

# The Australian CB SCENE



## CB: each of us has a story to tell

CB isn't a single entity. You can't point to something or someone and say "There, that's what CB is all about." CB is made up of ordinary everyday people like you and I. We all have our own reasons for turning our rigs on, and for turning them off as well. Each of us came to CB in our own way and each of us has a story to tell.

I have been sitting here at the typewriter for the past hour or so wondering what on earth I can talk to you about this month. There has been nothing really exciting going on, and all seems quiet as far as "the Department" is concerned. It is hoped that by the time the next issue of EA arrives we will have heard more on the results of the CBRS inquiry, but at the moment there is a definite lull as far as news is concerned.

I've got an idea — let's try to organise a contest! The editor will probably scream blue murder, but I'll take my chances.

Here's what I'm thinking . . . CB isn't a single entity. You can't point to something or someone and say "There, that's what CB is all about." CB is made up of ordinary everyday people like you and me and we all have our own reasons for turning our rigs on, and for turning them off as well. Each of us came to CB in our own way and each of us has a story to tell. Some may be happy stories, some sad — but each story is different. I would like very much to hear your story, and I am sure other readers would too.

Let's try to find out what brings a person to buy a CB set? Even more importantly, what is a person looking for when he or she picks up the mike and starts talking to a complete stranger? Do they ever find what they are looking for?

This column is called "Australian CB Scene". CB is made up of people, isn't it? What better purpose could some of the space in the column be put to than using it as a forum for you to tell us why you became a CB operator? I would like very much to hear your story and I am sure other readers would too.

Realistically speaking, one always achieves better reader participation in something like this if there is a prize at the end of it. Perhaps a CB rig for the best story?

As I said, this is just an idea at the moment, and it depends on a few things if it is going to get off the ground: a name for the competition, a sponsor who is willing to put up a good prize, and the blessings of my editor (not necessarily in that order).

I tell you what. Leave it with me for a month or so and I'll see what I can organise. If I can get the support I need at my end (I know I can count on yours), then we could really have something here.

**UHF CB:** At the moment we have three brands competing for the UHF market: Philips, Sawtron and Apollo. I have only seldom used UHF, and therefore am in no position to talk about it to any great degree. However, I would like to, and intend approaching the companies concerned in an effort to obtain a set from each to be used over a trial period, giving my own personal view (from an operator's stance) each month.

My technical knowledge is limited, so I won't be going into all sorts of details. I will simply give my impressions of each one as an average CB operator. If the companies are prepared for that sort of testing, then you can look forward to reading about these sets in future issues.

### SOME UNEXPECTED READERS

I have received mail from some strange and far distant places over the past year or so — the popularity of EA sees it going everywhere. However, I must admit that I was exceedingly touched to find out that the boys who are "guests of Her Majesty" have been reading my column. Some of them have not only taken the time and trouble to write to me, but have also sent me a Christmas card. The guys are using their time to learn more

about electronics and have undertaken appropriate technical courses. I would like to send a special "Hi" to Noel, Jim, Shane and all their mates. Thanks for the letters and cards, and best of luck.

Speaking of the places in which my articles turn up . . . I was, to say the least, surprised when Ross Ramsay of the Department of Communications flashed a copy of one of them during the Convention. He commented that I say nice things about him. Well, that's not hard to do, because he really is a nice man. He has a good head start because he is a Queenslander!

Seriously though, I am confident that we can expect a really fair hearing from the Department with Ross in there as First Assistant Secretary. I know that the National Director of the NCRA is pleased



NCRA national assembly meeting: Jan holding her NCRA-South Pacific Radio Special Recognition Award.

with the swifter flow of communications from the Department these days.

**NCRA CONVENTION:** I still can't get over my being presented with a special trophy at the NCRA Convention last November. I look at it and wonder "Why me?" Which reminds me — I must throw a huge bouquet of flowers to Terry Watkin, the National Director of the

NCRA who has worked (to the detriment of other aspects of his life) to improve the CBRS, in particular the 27MHz side. Thanks, Terry.

## MAIL BAG

**COMBINED CB MEETING:** Our roving reporter, Ken Upton, has been at it again. I tell you, it's hard to keep a good man down!

Ken, as you all know by now, is the Omega One. There was a Combined CB Meeting (Ken tells us) at the Liverpool (NSW) Town Hall on November 28 and the Omega Club was represented by Ken, Gary, Steve, Eric and John. The guest speakers were: Mr John Kerin, MLA for Werriwa; Mr Bill Storer, Deputy State Superintendent (NSW) Department of Communications; and Mr Alfred Reipano from the Licencing Branch (DOC).

I gather from what Ken has written that many club representatives left the meeting feeling that more than a few of their questions had not been adequately answered. On the question of an easy-to-follow booklet of rules and regulations relating to CB, Bill Storer even suggested that the NCRA prepare a suitable draught copy and submit it to the Minister!

In spite of its apparently limited success, I would like to congratulate the people who organised the meeting and thank those who took the trouble to attend.

**FOUNDATION FESTIVAL:** The Paramatta Foundation Festival last November saw the Omega club put on its Radio Display for the second consecutive year. The members worked until around mid-night getting everything set up, and excessive SWR caused a few headaches until finally solved.

Members Dave and Steve are also full call amateurs, and attracted a lot of interest with their Kenwood transceivers. CB sets on display ranged from 100mW hand-helds up to the large base station setups. Sam Voron turned up with his shoulder pack, and apparently caused a bit of a stir with it.

Special thanks must go to Walter Roldoy (Omega 9) and Eric Gee (Omega 19) for all their efforts. All in all it seems to have been a worthwhile exercise in public relations by the Omega club. Well done!

Well that's about it for this month. If you have any news please write to me at PO Box 406, Fortitude Valley, Queensland 4006.

Jan Christensen

### FUNDAMENTALS OF SOLID STATE

Available from "Electronics Australia," 57 Regent St, Sydney. **PRICE \$3.50** OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. **PRICE \$4.20.**

# MICROPROCESSORS & PERSONAL COMPUTERS



Microprocessors and personal computers, little more than a dream a few years ago, are now changing the face of electronics. This book introduces the basic concepts, describes a selection of microprocessor and personal computer systems, and details a build-it-yourself computer designed especially for beginners.

## GENERAL

THE PERSONAL COMPUTER REVOLUTION .....	2
MICROPROCESSORS: THE BASIC CONCEPTS .....	14
PLOT BIORHYTHMS WITH YOUR TRS-80 .....	67
UNDERSTANDING BASIC PT 1 .....	80
UNDERSTANDING BASIC PT 2 .....	83
GIVE YOUR COMPUTER AN RS-232C INTERFACE .....	110

## MICROPROCESSORS

INTEL 8080A & SDK-80 EVALUATION KIT .....	20
INTEL 8085 & SDK-85 SYSTEM DESIGN KIT .....	24
MOTOROLA 6800 & MEK6800D2 EVALUATION KIT .....	26
MOTOROLA 6802D3 EVALUATION KIT .....	30
NATIONAL SEMICONDUCTOR SC/MP CHIP & EVALUATION KIT .....	32
SIGNETICS 2650 CHIP & EVALUATION SYSTEMS .....	36
FAIRCHILD F8 & F8 DESIGN EVALUATION KIT .....	40
MOSTEK F8 & MOSTEK EVALUATION KIT .....	43
SIGNETICS 8X300 & EVALUATION KIT .....	46
NATIONAL SEMICONDUCTOR PACE & DEVELOPMENT SYSTEM .....	48
TEXAS INSTRUMENTS TM990/189 TRAINING SYSTEM .....	50

## PERSONAL COMPUTERS

TANDY ELECTRONICS TRS-80 PERSONAL COMPUTER .....	10
EXIDY SORCERER PERSONAL COMPUTER SYSTEM .....	58
HEATH H8 HOME COMPUTER SYSTEM .....	60
HEATH H11 16-BIT MINICOMPUTER KIT .....	62
COMPUCOLOR II PERSONAL COMPUTER SYSTEM .....	64

## MISCELLANEOUS EQUIPMENT

E & M ELECTRONICS CASSETTE INTERFACE KIT .....	45
PARATRONICS MODEL 100A LOGIC ANALYSER .....	70
PARATRONICS MODEL 10 TRIGGER EXPANDER .....	72
LEAR SIEGLER ADM-3 VIDEO TERMINAL KIT .....	74
TAPE READER KIT FOR HOBBY COMPUTERS .....	76
SIGNETICS INSTRUCTOR 50 TRAINING SYSTEM .....	78

## DREAM 6800 COMPUTER

INTRODUCTION TO THE DREAM 6800 .....	86
BUILDING THE DREAM 6800 COMPUTER .....	93
INTERESTING PROGRAMS FOR THE DREAM 6800 .....	98
CHIP-8 PROGRAMMING FOR THE DREAM 6800 .....	103
DREAM 6800 POWER SUPPLY .....	107

Available from "Electronics Australia", 57 Regent St. Sydney. **PRICE \$5.00** OR buy mail order from "Electronics Australia". PO Box 163, Beaconsfield 2014. **PRICE \$5.70.**

# SHORTWAVE SCENE



by Arthur Cushen, MBE

## Radio Vemarana heard during Santo Rebellion

During July 1980, a station called Radio Vemarana operated on Espiritu Santo in the New Hebrides. The station operated during the height of the so-called "bow and arrow" rebellion on Santo, and was widely heard throughout the South Pacific.

During July, 1980 broadcasts from Radio Vemarana were widely reported in Australia and New Zealand, and continuous listening gave a picture of a conflict between a Government in Vila and the rebellion on Espiritu Santo. Broadcasts were heard every morning on 3522kHz and during most of the transmissions there was severe jamming from the British forces who did their best to block the signal to listeners outside the area. During August the station moved to 3577kHz but later returned to its old frequency before it was finally put off the air.

The facts about the station are contained in a recent letter from the announcer of Radio Vemarana — now living in Australia. Radio Vemarana was thought to be a new name for the old Radio Tanafo which was operated by Jimmy Stevens for many years. Tanafo was the headquarters of Jimmy Stevens and was situated 25km from Luganville, the capital of Santo. This was never the location of Radio Vemarana, which transmitted from around Luganville. During July the operating power was 350W, but in August it was raised to 1000W.

### BRAZIL ADDS FREQUENCIES

Radio Nacional Brazilia has added a second transmitter for its service to Europe and North America in English. The transmission to Europe at 1900UTC is now broadcast on 15125 and 17180kHz; the North American service at 0200UTC is carried on 15290 and 17830kHz; and the broadcast to Africa at 2100 continues on 15280kHz. The two new frequencies are both in the 16m band and are using the power of 250kW. The station is requesting reception reports and

these should be sent to: Radio Bras, International Service, PO Box 04-0340 Brazilia Federal District, Brazil.

### YUGOSLAVIA'S NEW VOICE

In the next two years, Radio Yugoslavia will provide a new service for Australian migrants who have been trying to hear broadcasts from Belgrade. Transmissions at the moment are being received on 9620kHz with English at 1830 and 2000UTC, but under difficult reception conditions.

The plans announced indicate that four new transmitters of 500kW will be used by Radio Yugoslavia, with broadcasts beamed to Asia, Africa, North and South America and Australia. The transmitters are to be constructed in Yugoslavia and most of the equipment will be supplied by local manufacturers, except for some antenna components which will be imported. A BBC Monitoring Service report states that the External Service of Radio Yugoslavia will then broadcast in nine languages.

### MAJOR TIME CHANGES

The Soviet Union has announced that major changes in time zones across the country will be made later this year in order to bring some areas into the International Time Zone which was created in 1931, but rejected by some Soviet States. This year the Soviet Union will observe summer time from April 1 to October 1. Clocks will be put forward by one hour. On October 1 when most of the Soviet Union will return to standard time, the areas which did not observe the 1931 agreement will remain on daylight time thus bringing them into line with the correct time zone. The BBC Monitoring Service reports that this change will cover relatively small areas of the Soviet Union. During the period April 1-October 1, when Moscow will be observing daylight time, it will be four hours ahead of UTC.

### VOICE OF GREECE

New frequencies are being used by the Voice of Greece in Athens for transmissions in Greek and English to Australia. The broadcast from 0900-0950UTC from Athens is carried on 9640 and 15405kHz and this transmission is in Greek and English. The broadcast 2100-2150 in Greek is on 9640, 11730 and 15405kHz, while a further transmission 2200-2250 is on 9640kHz only. A broadcast to Japan in English 1000-1050UTC is carried on 11845 and 15405kHz. The frequency of 9640kHz at 0900UTC is blocked by the BBC World Service up to 0915UTC while 15405kHz, though on a clear frequency, is received at low signal level. The schedule is valid up to March 1, 1981.

### LESOTHO ON 11720kHz

The new 50kW Lesotho transmitters have previously been reported on 4800kHz and now 11720kHz has been observed opening at 0458UTC. The transmitters are used by the BBC World Service with news in English at 0500UTC, then a program in French to Africa at 0530UTC. At 0600UTC the BBC News Desk feature is presented and at 0630 a further broadcast in French has been observed. The new frequency provides fair reception in this area and is presumed to be the first used by the BBC of the new Lesotho relay station for high frequency broadcasting in Southern Africa from the new site. In the past, the Lesotho transmitter was heard on 4800kHz and around 1800UTC, but carrying local programming.

### NIGERIA'S HIGHER POWER

A new high powered 300kW transmitter has been heard on 17800kHz broadcasting the External Service from Lagos on a test basis. John Mainland of Wellington, NZ first reported this transmission when test announcements were heard between 0700-0800UTC. Recently the frequency has been used to relay the Voice of Nigeria to North Africa but reference to the frequency of 15120kHz only made in the broadcast.

Observations show that there is a full world news bulletin at 0630UTC and on Friday, at 0700, mail from listeners is answered. At 0730UTC Nigerian local news is broadcast and the English

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill NZ. All times are UTC (GMT). Add eight hours for WAST, 10 hours for EAST and 12 hours for NZT. In areas observing daylight saving time, add a further hour.

# SHORTWAVE SCENE

transmission ends at 0800 when the broadcast continues in French.

This transmitter has given good reception in southern New Zealand and parts of Australia at this time, with the only interference being from Paris, France also using 17800kHz, but with a much weaker signal level. The address for reports is Federal Radio Corporation of Nigeria, Broadcasting House, Ikoyi Lagos, Nigeria.

## STRONGER IRAQI SIGNALS

The Iraqi Government recently signed a contract for the installation of high-powered medium and shortwave transmitters. Current plans call for 16 shortwave transmitters, each of 500kW, and two 1 megawatt medium-wave transmitters. The French company which has been awarded the contract plans to start installation shortly.

In the continuing conflict between Iran and Iraq it has become obvious that Radio Teheran in Iran is winning the propaganda war and so Iraq is attempting to improve its signals throughout the Middle East area and the world in general. The Iraqi could, however, be curtailed due to economic difficulties as a result of the recent fighting.

## INTERESTING KOREAN SIGNAL

Broadcasts in English are being received from the Voice of Korean Unification, with English transmissions 1430-1500UTC. The transmission is carried on two shortwave frequencies, 4120 and 4557kHz, and on medium-wave on 1053kHz. A transmission at 2230-2300UTC is broadcast only on 1053 and 4557kHz. The broadcasts call for the unification of North and South Korea and though the station announces as Seoul it is obvious that the broadcast originates from Pyongyang in North Korea.

## KTWR CHANGES

Frequency changes at KTWR Agana Guam have been numerous and at the present time the popular "DX Listeners' Log" is now carried on the new frequency of 9510kHz on Friday at 1445GMT. Some of the other changes include: 1430-1600UTC 11895kHz; 2159-0130 17800kHz; 0458-0700 15160kHz; and 1359-1429 15320. The transmission 2045-2129UTC in Russian is now on 11945kHz.

The English transmissions continue to be received 0000-0140UTC on 17770kHz and 0745-0930 on 11840kHz. DX Listeners' Log is heard on these transmissions on Thursdays at 0100 and Fridays at 0915UTC. Reports on reception are appreciated by KTWR, Box CC, Agana, Guam 96910.

## KOREAN CHANGES

Radio Korea in Seoul has made some changes in times and frequencies for its English broadcast, though the transmission best received in New Zealand continues to be 9750kHz at 1000UTC. Other transmissions noted are at 0230UTC on 15570, and 11810kHz; 0800UTC on 9870, 11810 and 15570kHz; and 1230 on 7550 and 11830kHz. Another transmission well received is 2130-2230UTC on 15375kHz but there is some interference for the first 30 minutes from Cairo, Egypt broadcasting in English. Radio Korea now has a DX Program during their Friday transmissions.

## NEW US STATIONS

A radio station owner in New Orleans, Joseph M. Costello III, who owns five radio stations in the area, has been granted a licence for a shortwave commercial broadcasting station. The licence for the new station was granted on the basis of a law passed in 1948 stating that the United States government does not have a monopoly on shortwave broadcasting. The FCC (Federal Communications Commission) therefore reluctantly granted the application and the station is expected to beam shortwave broadcasts to Canada and Europe. This will be the

first international commercial station to operate in the United States since WNYW ceased transmission some years ago and was taken over by WYFR.

The FCC has also granted a licence to the Billy Graham Organisation to establish a shortwave broadcasting station on Hawaii.

## ENGLISH FROM PATAGONIA

An English announcement has been heard from Radio Patagonia operating on 6080kHz from 0930UTC. The station has a series of descending chimes then there is a full identification in Spanish. This is followed by another set of chimes and a short announcement of station details in Spanish, followed by further chimes and then the English announcement. The English announcement indicates that listeners are tuned to Radio Patagonia in Coyhaique, Chile broadcasting on medium-wave on CD97 on 970kHz and on shortwave on 6080kHz. The station has already confirmed reception of reports to broadcasts heard in New Zealand.

A verification card and a fact sheet in Spanish about the area has been received. The card shows an ice scene at the Sar, Rafael Lagoon. The principal city in the region is Coyhaique, which has a population of some 30,000.

## LISTENING BRIEFS

### EUROPE

**ROMANIA:** Radio Bucharest broadcasts to Africa in English 0530-0600UTC and is heard on 17790kHz. The transmission is also carried on 11840 and 15235kHz. The second broadcast 1730-1800UTC is on 11805, 15340 and 17720kHz, but only the first frequency is audible as 15340 is blocked by Kuwait and 17720kHz by WINB.

**VATICAN:** The Vatican Radio European language transmission opens at 0630UTC on 11715kHz, as Switzerland leaves the frequency. The opening announcements are in four languages and the same broadcast is noted on 6210kHz. At 0635UTC Mass is broadcast.

**NORWAY:** Oslo is using 11920kHz for the transmission to North America 0500-0630UTC. This frequency carries English on Monday 0600-0630UTC, but the last 30 minutes of the transmission suffers interference from Radio Moscow.

**BELGIUM:** Brussels is using a new frequency for English to North America - 11700kHz has replaced the old frequency of 15385kHz 0015-0100UTC. A further channel, 15175kHz, carries the same program. The broadcast from Brussels to Africa at 1000UTC is now heard on the new frequency of 21625kHz, replacing 21465. An additional frequency, 26050kHz, carries the same program.

### ASIA

**IRAN:** The Home Service of Radio Iran

in Teheran, after operating on 15315kHz, has moved to 11745kHz. Transmission opens at 0315UTC with an interval signal and broadcasts commence at 0330UTC. The new frequency of 11745kHz is not so well received, as it is also used by Radio Moscow for a transmission in Spanish to Latin America.

**PAKISTAN:** Radio Pakistan has been heard by Geoff Cosier, reporting in "DX Post", as carrying Home Service programs on 7091kHz at 1303UTC, while another frequency 7375 was heard at the same time with a program in English. Another frequency, 7120kHz, has been heard to closing at 1415UTC, but suffers severe interference from Radio Peking.

### AMERICAS

**COSTA RICA:** Radio Noticias in Costa Rica opens with a guitar interval signal at 0855UTC and identification in Spanish at 0900. Signals on 9615kHz suffer light interference from a Russian transmission on the same channel, reports Simon Tuck of Adelaide in "DX Post".

**PERU:** Radio America in Lima now seems to be operating 24 hours a day on a Saturday, and is heard round 0700UTC on Sunday on 9510kHz. This signal causes severe interference to the BBC World Service from the Antigua relay base, although Radio America is heard clearly after 0915UTC when they use the slogan "American Radio" and feature popular American music.





# NEW PRODUCTS

## Hitachi V-352 35MHz Dual Trace Oscilloscope

Hitachi have recently introduced two more oscilloscopes to their range of medium priced CROs. The V202 and V352 are both dual-trace CROs with 20MHz and 35MHz bandwidths respectively and include such features as 1mV/div sensitivity and x10 sweep magnifier.

Dimensions of both CROs are 275 × 190 × 400mm (D × H × W) and weight is 8.5kg. A large carry handle is provided which also functions as a tilting bail. The CRT has a rectangular screen with a blue phosphor and measures 94 × 75mm.

An internal graticule is divided into 10 vertical and eight horizontal divisions, each 9.4mm. It is worth mentioning here that internal graticules, ie, graticules etched on the inside of the CRT tube, are relatively recent innovations in the medium priced CRO market. The major advantage of this feature is that "parallax" error is eliminated, so the signal on the screen can be accurately compared against the graticule from any viewing angle.

In appearance the new Hitachi CROs are almost exactly the same as other models in the series. All of the usual features expected in medium range CROs are provided. Input attenuators for both channels are calibrated from 5mV to 5V in 1-2-5 steps plus there is a separate variable adjustment of gain with an indented calibrate position.

Unlike many similar CROs, however, the Hitachi V-202 and V-352 also provide a x5 vertical gain feature which results in an input sensitivity of 1mV/div. This high sensitivity is very useful for observing low level audio or analog signals etc.

Time base calibration is in 19 steps in 1-2-5 sequence from .2µs to .2s, and a separate variable sweep speed control has an indented calibrate position. Hitachi also provides a x10 sweep magnifier rather than the usual x5. The increased resolution is very useful for examining high frequency waveforms or complex waveforms such as video signals.

The Model 352 which we reviewed has a quoted bandwidth (ie, -3dB point) of 35MHz and we were able to verify that this was certainly correct. The ultimate frequency limit of a CRO however, is imposed by the triggering circuitry and the maximum writing speed of the CRO tube. In the case of the Hitachi 352 we

found it still maintained triggering up to 100MHz and even gave a useable display using the x10 sweep magnifier.

Accuracy of both the time and voltage axis is quoted as ±3% and ±5% on the x5 vertical gain of x10 sweep magnifiers. Using a DFM to check the time scale we found it was accurate to within 0.5% for .1ms/div and above but the accuracy

*We found that the Hitachi V-352 gave a useable display of signals up to as high as 100MHz.*


decreased to 2% at higher sweep speeds and with the x10 sweep magnifier. Measurements on the voltage axis with a DMM indicated a typical accuracy of better than 3% either with or without the x5 vertical gain.

Vertical amplifier input impedance was 1MΩ shunted with 30pF, though with the probes fitted, the input impedance at the probe was 1MΩ shunted by 150pF on the 1:1 position and 10MΩ shunted by 20pF on the 10:1 position.

Additional controls include the usual FOCUS, INTENSITY, SCALE ILLUMINATION, AC/GND/DC input switches, trigger level, trigger source and mode, and display mode. The trigger modes available are auto, normal and TV+ and

TV-, with the latter modes particularly useful for syncing on the vertical sync pulse of a TV signal. Display modes are CH1, CH2 (X-Y), DUAL, ADD, DIFF plus an X-Y display can be obtained by switching to CH2 (X-Y) and switching the timebase to X-Y. This procedure is actually slightly more complex than other CROs which simply require the time base to be set to X-Y to give Lissajous displays.

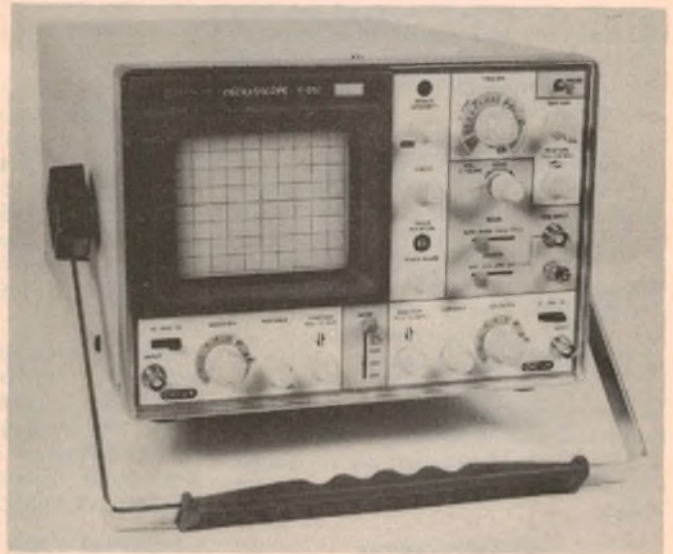The X-Y mode is useful for phase measurements of audio equipment and control systems, but of course the accuracy of the phase measurement depends on the relative phase shifts of the amplifiers. The Model V-352 exhibited virtually no phase error below



10kHz but we did note a slight error as the frequency was increased to 20kHz though well within the quoted accuracy of 3 degrees from DC to 50kHz.

Another feature not always found in medium priced CROs is electronic trace rotation. The trace rotation control is a recessed screw driver adjustment on the front panel which can be used to compensate for any inclination of the trace caused by external magnetic fields. Electronic trace rotation rather than actual rotation of the tube assembly is of course necessary because of the internal graticule, but this is still a very convenient feature for accurate observations on the time or voltage axis.


Interestingly, the actual trace rotation

is performed by a small coil on axis with the tube and the trace rotation control is a potentiometer which can be set anywhere between +12V and -12V effectively generating a magnetic bias field along the axis of the tube. When correctly adjusted the bias field just cancels out the component of the earth's magnetic field along the tube. Note that components of the external field in other directions merely shift the trace vertically or horizontally.

One feature which is not evident from the front panel is the inbuilt signal delay line which permits the leading edge of fast transient waveforms to be observed.

As you can see from the photograph, the front panel layout is clean and uncluttered with the various controls grouped together according to function. Note that the variable gain and sweep adjustments are not concentric with the input attenuator and timebase switch as is the case on other CROs.

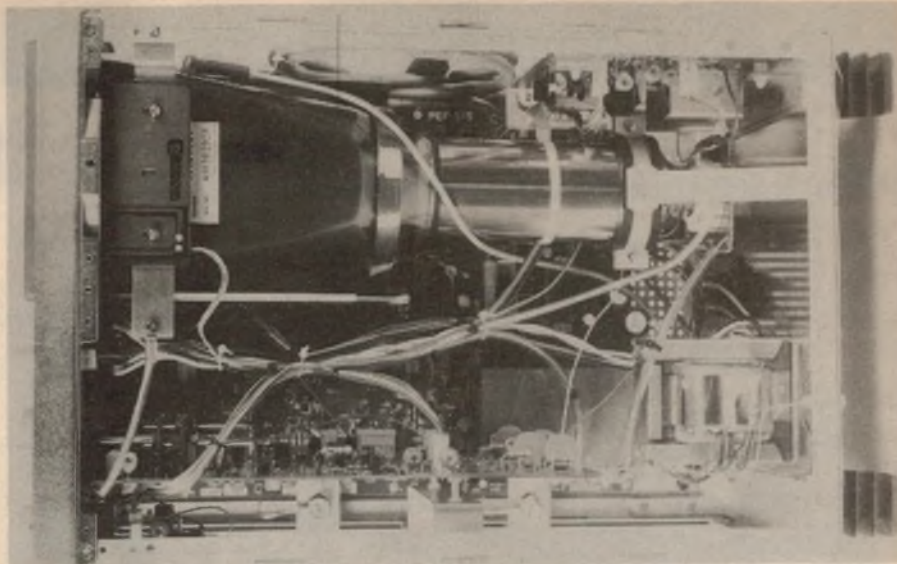A comprehensive operation manual is supplied with the CRO and it provides useful information on making various measurements such as phase, risetimes, frequency etc plus there is a complete circuit diagram of the CRO.



The interior of the Hitachi V-352. The trace rotation coil on the tube can be clearly seen.

Our overall impression is that the V-352 is competitively priced and offers quite a few important features not found in similar CROs. The recommended retail price of the V-352 is \$1059 plus

sales tax of \$119.13 and the retail price of the V-202 is \$665 plus \$74.81 sales tax. Probes are not included in this price but 1:1/10:1 probes can be purchased for \$44.50 each, including sales tax. (RdJ)


## FM Tuner kit from L. E. Chapman

An FM stereo tuner kit for less than \$20 must be one of the best electronics buys you can make in 1981. L. E. Chapman, of 122 Pitt Road, North Curl Curl, NSW has such a kit which is based on three printed circuit modules. All three modules are supplied fully assembled and aligned.

The RF module is fully shielded and uses a gear-driven solid-dielectric tuning gang to cover the whole FM band. It has provision for 300Ω balanced and 75Ω unbalanced antenna connections, together with AFC (automatic frequency control).

The IF and demodulator module employs the wellknown (and current) Philips TCA420A IF amplifier IC. As well as providing the required gain at 10.7MHz plus audio demodulation, this module also provides the AFC voltage for the RF module, the mono/stereo control voltage for the following multiplex decoder module and an output to drive a signal strength meter.

The stereo decoder module is also based on a Philips IC, the TCA290A. The module uses the standard Philips circuit for the TCA290A, which is claimed to yield separation between channels of better than 40dB at 1kHz with typical harmonic distortion of 0.2%. The module also drives a stereo LED indicator and has a pair of transistor preamplifiers to boost the left and right channels to the required level. 19kHz and 38kHz rejection (from the circuit used) is claimed by Philips to be typically 30dB and 40dB respectively.

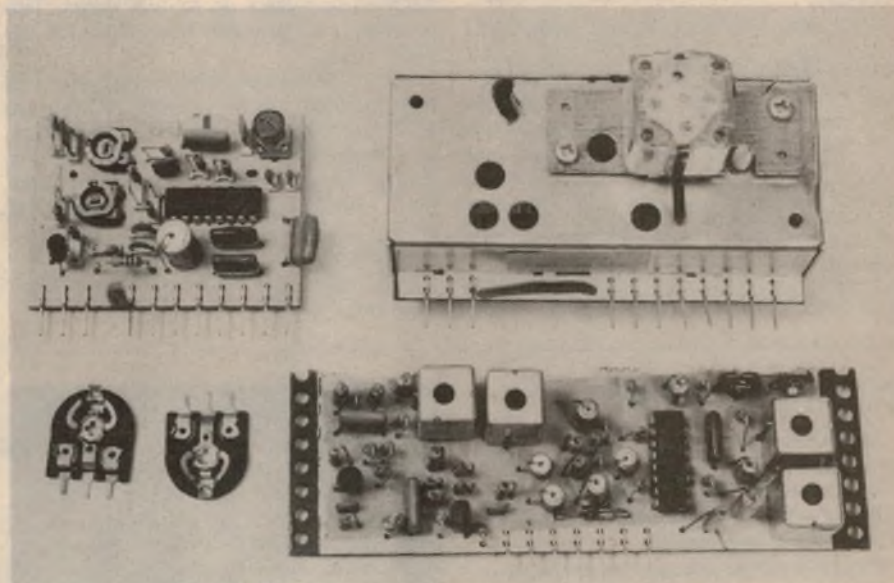

The three modules will run from a 12 to 15V regulated circuit and we have heard of at least one system being successfully used in a car.

Also included in the kit are two trim pots and two photostat pages of circuit information which shows how to connect the modules together to obtain a working tuner. The complete circuit requires a handful of resistors and capacitors, two switches, a LED, a signal strength meter movement and the power supply already mentioned.

Price of the kit which comprises the three modules, two trim pots and the circuit information is \$18 plus \$1.00 for postage and packing where required. Mail orders should be addressed to L. E. Chapman, Box 156, PO Dee Why, NSW 2099.

**NEW PRODUCTS  
CONTINUED ►**

## New Products

### PROGRAMMABLE SCANNING RECEIVER



GFS Electronic Imports has announced the release of an updated version of the already extremely popular J.I.L. SX-200 HF/VHF/UHF programmable scanning receiver.

The new SX-200 features wide-band coverage (26-88, 108-180 and 380-514MHz), encompassing the 27MHz and UHF CB bands, the 10m, 6m, 2m and 70cm amateur bands, the Australian low and high VHF commercial two-way bands, VHF satellite and the UHF commercial two-way band, as well as the aircraft band. Both AM and FM frequencies are covered on all bands. Other features include a three mode squelch control that can be used to stop the set locking

on spurious or carrier only signals; a digital clock and squelch output for use in triggering a tape recorder or some other auxiliary equipment; and memory back-up that lasts up to two years. The receiver can operate from 12V DC or 240V AC.

Main differences when compared to the previous model include redesigned RF, IF and audio boards to give specification improvements in areas such as sensitivity, image rejection ratio and adjacent channel rejection. The expected selling price is \$489 including sales tax.

Additional information from GFS Electronic Imports, 15 McKeon Rd, Mitcham, Victoria 3132.

### DC-DC Converters

Scientific Electronics, designers and manufacturers of a wide range of high performance power supplies, has released a new series of Eurocard compatible 25W DC-DC converters.

The converters utilise a DIN 41612 connector and occupy only 300mm of rack width. Although they have been primarily designed for Eurocard rack systems, their small size (100 x 160 x 30mm) makes them ideal for a wide range of power supply applications.

The units are rated at 25W continuous operation at 60°C ambient temperature and input voltage range is 40-60V DC with efficiency greater than 75%. Two output voltages are available: 5V and 12V.

Input and output noise voltages are both below 50mV p-p DC to 20MHz and



the input ripple current is less than 20mA p-p.

The units feature overvoltage and short circuit protection, 0.2% total line and load regulation, synchronisation facility, input voltage transient protection, input reverse polarity protection and 50kHz switching.

For further information contact Scientific Electronics, 6 Holloway Drive, Bayswater 3153.

### DOT MATRIX DISPLAYS



Warburton Franki has released details of the SM-810-002, the second in a series of 5 by 7 dot matrix display systems from the Display Systems Division of Beckman Instruments, Arizona.

Like its predecessor, the 40-character SM-810-001, it is microcomputer controlled and can be used in process control or instrumentation applications, as well as for a variety of other OEM designs.

The SM-810-002 features a 130° viewing angle for its field of 20 12.5cm high characters. All of the operational features are the same as those of the 001; however, the larger characters of the 002 appear brighter and are easier to read.

Both display systems have the ability to blink a continuous field of characters that includes 96 standard ASCII symbols, as well as two non-standard symbols — the degree sign and the Greek letter, "Mu".

The new display system accommodates left-to-right data entry. Mounted on one PC board, smaller than a cigarette carton, it incorporates a custom-masked microcontroller with 1K of ROM. Refresh rate is 94Hz.

The microcomputer also keeps track of character position and intercepts the control codes for backspace, carriage return, initialise, scroll, blank, unblank, blink and position functions. This built-in intelligence simplifies the setup of special messages: an operator can completely blank, and then unblank the display to generate a message immediately. He can also scroll a message from right to left.

For further information contact your local Warburton Franki office.

### MAINS INLET FILTERS

Rifa, distributors for the Bulgin range of products, has released a new series of 3-pole mains inlet connectors and combined interference filter units.


These new units are designed to protect digital and analog instruments from mains-borne voltage transients, and comply with the requirements of IEC 320, CEE22 and BS4491.

All filtering components are enclosed in a tin plated steel case which provides

# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE VICTORIA. Ph. (03) 489 8131.

## NEW PRODUCTS

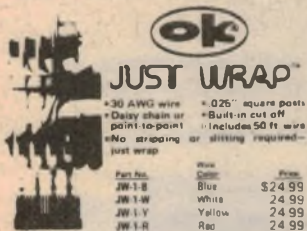

**OK JUST WRAP**

\*30 AWG wire      \*0.25" square posts  
 \*Delay strain or      \*Built-in cut off  
 point-to-point      \*Includes 50 ft wire  
 \*No strapping or      \*Slitting required -  
 just wrap

Part No.	Wire Colour	Price
JW1-B	Blue	\$24.99
JW1-W	White	24.99
JW1-Y	Yellow	24.99
JW1-R	Red	24.99

## JUST WRAP Replacement Wire

Part No.	Color	50 ft. roll	Price
R-JW-B	Blue	50 ft. roll	\$4.99
R-JW-W	White	50 ft. roll	4.99
R-JW-Y	Yellow	50 ft. roll	4.99
R-JW-R	Red	50 ft. roll	4.99

## SCOTCHCAL FRONT PANELS FOR ETI & EA PROJECTS

ETI 452 Guitar Practice Amp Series 4000 Any colour	\$4.80
MOVING Coil Pre Amp	\$12.50
577 Power Supply	\$2.00
455 Loud speaker protector	\$2.00
Variable power supply	\$2.70
Linear ohmmer	\$2.50
Muscle activity meter scale	\$1.40
ETI 576 Electromyogram	\$2.80
561 Metal Detector	\$2.50
EA Capacitance meter	\$3.50
EA Flash exposure meter	\$4.25
EA Sound triggered flash	\$3.50
EA Slave flash	\$1.20
EA Playmaster graphic analyser	\$8.50
EA Metal Detector 79md9	\$3.90
EA Pulse generator	\$4.80
EA Square wave oscillator	\$2.50
EA RF Z Bridge	\$3.25
EA Thyristor tester	\$2.40
EA Quartz frequency ref	\$2.70
EA Multi monitor	\$1.90
EA Experimenters Supply	\$2.80
EA Quiz master	\$3.70
EA Variable wiper delay	\$1.10
EA Playmate stereo Amp	\$4.50

ALL FRONT PANELS AVAILABLE FROM DAY OF RELEASE OF MAGAZINES WHEN ORDERING FRONT PANELS. SPECIFY COLOUR OF LETTERING FIRST. THEN COLOUR OF BACKGROUND.

## KITS

### TV PATTERN GENERATOR

Kit of parts as featured in Electronics Australia June, 1980. Dot, Greyscale, Crosshatch, Raster Check

Complete Kit	\$48.49
Kit without case	\$36.90
Pack and post	\$2.50

## EPROM PROGRAMMER KIT

Kit of parts as featured in Electronics Australia July, 1980 Programs 2708, 2716 and 2532. Use with TRS80, Sorcerer, and Compucolor. Kit does not include connector from the programmer to computer.

Complete Kit	\$72.49
Kit without case	\$59.99
Pack and post	\$2.50

## DIG CAPACITANCE METER

Kit of parts featured in Electronics Australia March, 1980. Four digits.

Complete Kit	\$52.49
Kit without case	\$39.99
Pack and post	\$2.50

## COMPONENTS

4116 RAMS	\$5.00
2114 RAMS	3.30
2708 EPROM	6.90
741 s 10 up	2.50
555 s 10 up	2.90
BD139 10 up	5.50
BD140 10 up	5.50
SC141D 10 up	11.00
SC151D 10 up	21.10
RED LEDS 10 up	1.40
RED LEDS 100 up	11.00
YELLOW LEDS 10 up	2.30
8 PIN I/C SKTS 10 up	2.00
BC548	0.15 ea
BC549	0.19 ea
MJ802	3.60
6.800/50V CAPS (LUG)	4.50
5.600/40V CAPS (PCB)	1.90

## KITS & CIRCUIT BOARDS

### ETI SERIES 4000 AMP

● Complete Kit	\$199.00
● Quality front panel to suit above	10.90
● ETI 470 kit of parts	22.50
● ETI 480 kit of parts 100w (incl. bracket)	19.75
● ETI 470 PS kit of parts (includes relay, not transformer)	19.50
● Transformer to suit	22.90
● ETI 471 pre-amp	45.50
● ETI 585R ultra sonic RX	15.95
● ETI 585T ultra sonic TX	8.95
● EA 7.9 SF9 sound flash trigger	15.00
● All parts available for DREAM computer project	
● P.C.B.'s (all quality fibreglass boards)	
ETI 574 disco strobe	2.80
ETI 549A metal detector	2.75
DREAM circuit board	10.90



SCHUGART SA 400  
5in Minifloppy Drive

\$399.00 Tax Inc  
\$347.00 ex

RITRON COMPUTER GRADE P/S  
+5V reg 10a 16V unreg @ 1A  
KIT \$79.95 inc  
Built and tested \$99.50

ETI636 MOTHERBOARD  
7 Slot Motherboard \$77.00  
Built and Tested \$95.00  
ACTIVELY TERMINATED

### INTERSIL LCD \$34.50 3 1/2 DIGIT PANEL METER KITS

Build a working DPM in 1/2-hour with these complete evaluation kits. Test these new parts for yourself with Intersil's low cost prototyping kits complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter ICL7106EV (LCD).

## COMPUTER COMPONENTS

Attention Sorcerer & TRS 80 owners. Memory expansion kits available. We also offer full service on the popular computer projects and systems.

**SPECIAL 4116 RAM OFFER**  
8 OFF PRIME SPEC 4116 I/Cs \$39.00  
16 4116s for \$78.00

**STATIC RAM KIT 16K S-100**  
2114 \$3.30; 2716 \$11.00; 2708 \$6.90

## DIP PLUGS

Ideal for use with flat ribbon cable or to mount components on

14 pin	\$0.80
16 pin	\$0.90



24 pin \$1.20

## COMPUTER COOLING FANS

Muffin fan 4 1/2" square

110V	\$39.50
240V	\$26.50

Range of larger fans available. Send for details.

## POWER TRANSFORMERS

SPECIALLY DESIGNED FOR MICROCOMPUTERS

- Good regulation electrostatic shield
- RI 810 8V @ 10A x 15V @ 1A \$24.50
- RI 820 8V @ 20A 15V @ 1A 15V @ 3A \$35.50

## 20 TURN CERMET TRIM POT



## SPECTROL 43P ACTUAL SIZE

STOCK RESISTANCE VALUES  
10R, 20R, 50R, 100R, 200R, 500R, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1M, 2M

1-9	\$1.40
10-99	\$1.30
100	\$1.20

Values may be mixed.

## Hexadecimal Keypad

\$24.50/each



19-key pad includes 1-10 keys ABCDEF and 2 optional keys and a shift key.

Ideal for dream project

## MULTIDIALS



Dials to suit 10 T Pots

Model 21 1.8" dia	\$16.50
Model 16 9" dia	\$12.50
Model 18 1" x 1.75" dia	\$20.60

## cermet single TURN TRIM POT

Spectral model 63P  
ACTUAL SIZE

STOCK VALUES  
10R, 20R, 50R, 100R, 200R, 500R, 1K, 2K, 5K, 10K, 20K, 50K, 200K, 500K, 1M, 2M

1-9	\$1.00
10-99	0.90
100	0.80

Values may be mixed

## P.C. EDGE CONNECTORS



S100 gold plated wire wrap	\$6.90
S100 solder tail	\$6.50
D2 Motorola bus	
43/B6 solder tail	\$6.34
43/B6 gold plated wire wrap	\$7.40

## DREAM

ELECTRONIC AUSTRALIA MICROCOMPUTER PROJECT  
Kit for main board (including programme 2708) \$109.00  
Also available re designed 6802 PCB \$11.90

PCB (fibre glass) only	\$10.90
2708 programmed	\$15.50
Key Pad 19 keys	\$24.50
Kit (less key pad)	\$94.00
PCB for power supply	\$3.50

## 10 TURN POTENTIOMETERS

Stock resistance values

50R, 100R, 200R, 500R, 1K, 2K, 5K, 10K, 20K, 50K, 100K	
Spectral model 534 1/4" shaft	
Price 1-9	\$8.50
10 + values may be mixed	\$7.90

HEAVIER ITEMS ADD ADDITIONAL POSTAGE EXTRA HEAVY ITEMS SENT COMET FREIGHT ON PRICES SUBJECT TO CHANGE WITHOUT NOTICE. SEND 60c & SAE FOR FREE CATALOGUE MAIL ORDERS: PO BOX 135, NORTHCOTE, VIC 3070. MIN PACK & POST \$1.00 PRICES CURRENT UNTIL MARCH 7 1981

# DIABLO AND SORD COMPUTER SYSTEMS

Write or phone today for full details or an obligation free proposal



XEROX  
DIABLO 3000



DIABLO 3200

Your alternatives are — buy hardware and so called "standard" software with -----??

OR

Buy a system with all programs tailored to your exact requirements, fully installed and supported on your premises by professional programmers and totally guaranteed.

There is only one way to go — our way if you are serious about your business.



M223  
MARK III

M203 MARK III

NEW SORD MODELS

## 5 ABSOLUTELY SUPERB SYSTEMS FOR THE BUSINESSMAN

- SORD M203 MARK III AND M223 MARK III — 5" SYSTEMS.
- DIABLO 3000 — 8" SYSTEM ● DIABLO 3100 WITH BUILT-IN HARD DISK
- DIABLO 3200 EXPANDIBLE TO MULTIPLE SCREENS, PRINTERS, ETC.

# HEWLETT-PACKARD CALCULATORS:

Free package and postage by registered mail anywhere in Australia.

THE GREATEST CALCULATOR  
MONEY CAN BUY!  
— THE HP41C SYSTEM —



CARDREADER

PRINTER

MEMORY  
MODULES

- HP41C — over 400 steps, up to 64 data registers (continuous) \$374 (\$336)
- The 41C has 4 interface ports for:
  - Extra RAM, Pre-Programmed ROMS's, Card Reader, Optical Wand and Printer/Plotter.
- Card Reader \$273 (\$245)
- Printer/Plotter \$489 (\$439)
- Extra memory modules each with capacity of basic 41C \$56.40 (\$49.10)
- Plus 16 application pacs (plug-in modules) \$56.40 (\$49.10) each.
- 24 solution books \$15.70 (\$13.60) each.
- Optical Wand \$158.60 (\$142.50)
- 40 Magnetic Cards \$25.10 (\$21.80)
- 120 Magnetic Cards \$56.40 (\$49.10)
- 6 rolls therm. paper \$7.50 (\$6.50)
- calc. rechargeable batteries \$48.50 (\$43.60)
- Calc. adaptor \$18.20 (\$16.40)

MAGNETIC CARDS

OPTICAL WAND

- HP31E Scientific \$66.00 (\$59.00)
- HP32E Advanced Scientific Statistical \$91.50 (\$82.00)
- HP33E Advanced Scientific Programmable, 49 steps \$117 (\$105)
- HP97 Card Programmable, printing 224 steps \$953 (\$857)

### CONTINUOUS MEMORY

- HP34C Scientific Programmable, 210 steps \$192.50 (\$173)
  - HP33C Scientific Programmable, 49 steps \$155 (\$139)
- Plus business machines.

Price in brackets excluding sales tax.



Copy and complete  
Please debit my Bankcard \$  
No. Expiry Date  
Signature  
Name  
Address

## CALCULATOR AND COMPUTER DISTRIBUTORS


INCORPORATING EXCLUSIVE CALCULATORS & COMPUTERS  
and ELECTRONIC CALCULATOR DISCOUNTS

PHONE (02) 624-8849

MAIL ENQUIRIES:  
PO BOX 106, BAULKHAM HILLS  
2153
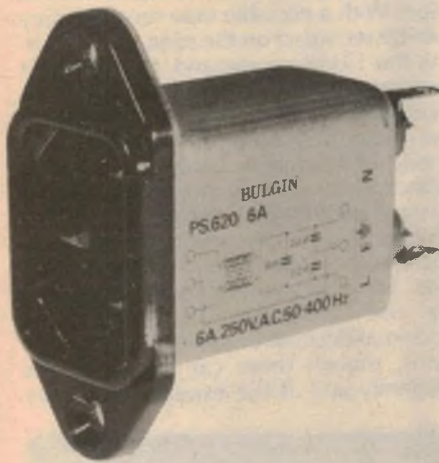
## New Products


electromagnetic screening. The total earth leakage current is less than 0.35mA, as required by the general safety regulations in Europe and the UK.



There are four units in the series, the PS620 3 amp, PS620 6 amp, PS620 10 amp and the PS621 6 amp.

For further information contact Rifa Pty Ltd, 202 Bell Street, Preston, Victoria 3072.

## MINIATURE RELAYS

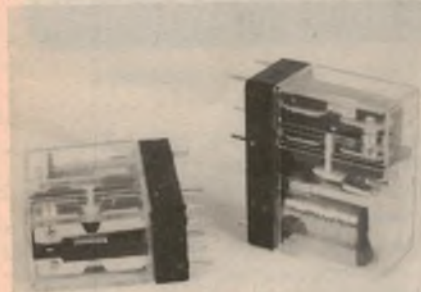

One of the latest miniature relays to appear on the Australian market is the Fujitsu miniature high power relay, FBR600 series. Available in two basic types, FBR610 (SPDT) and FBR620 (DPDT) they can be supplied with coils to suit DC supply voltages of 5, 6, 9, 12, 18, 24, and 60V.

These relays are directly interchangeable with other miniature relays on the market, such as Pye, Varley, etc, and have been approved by the State Electricity Commission of Victoria and Telecom. They also carry international approvals, VDE, UL, and CSA.


The contacts are of silver alloy and for the FBR610 are rated at 10A carrying current and 10A making/breaking current at up to 30V DC and 240V AC. The FBR620 is rated at 5A for the same voltage ratings. Initial contact resistance is given

as 100mΩ at 6V DC, 1A.

Coil dissipation is 0.5W for both models, while contact operate time is given as 8ms and release time as 2.5ms.

These relays will be available from a number of retail outlets, and further information can be obtained from IRH Components Pty Ltd, 53 Garema Circuit, PO Box 265, Kingsgrove, NSW 2208. Phone (02) 750 6444.

## CONDUCTIVE WRIST STRAP

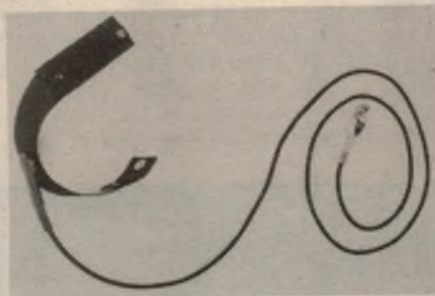

Royston Electronics has introduced a conductive wrist strap that meets military specifications for quick release and resistance to line voltages from accidental contact. Conductive wrist straps are used to prevent static electricity damage to microcircuits while radar, avionics, computer and other equipment is undergoing repair, maintenance or inspection in base stations or the field.

The CP401A grounding strap has a wrist attachment of "Velcro" hook-and-loop tape that separates with a slight pull and prevents a worker from breaking the grounding wire by inadvertently leaving the work area while still wearing the strap.

The wrist strap is made of conductive polyester ribbon for permanent conductivity, but with built-in resistance to protect the wearer against possible line voltages.

The wrist strap and ground wire are joined by a standard snap fastener. An extra snap fastener provides a convenient connection for grounding electric tools, bench covers or other items that must be grounded.

Further information from: Royston Electronics, 27 Normanby Rd, Notting Hill, Victoria 3149.

## KIKUSUI OSCILLOSCOPES

Kikusui of Japan has recently released two new oscilloscopes: the models 5650 and 5531.

The Kikusui model 5650 is a 50MHz dual-channel oscilloscope with dual time base. The sensitivity of the vertical



amplifier is 5mV/div at full bandwidth with the capability of 1mV/div per division sensitivity at a restricted bandwidth of 10MHz. Waveform magnification with calibrated sweep delay is standard.

Other facilities include alternate timebase, alternate trigger, 500kHz chop frequency, auto level (lock) circuit, one touch trigger delay, variable hold off and one touch XY operation.


The Kikusui model 5531 is a dual-channel 35MHz oscilloscope offering 5mV/div sensitivity at 35MHz with a Y magnifier on both channels giving 1mV/div at 15MHz bandwidth.

The 5531 has two timebases, giving sweep modes of A, A intensified and B. The instrument also incorporates an uncalibrated trigger delay.

Among other features are alternate chop (200kHz), one touch trigger delay, variable hold off, one touch XY operation, internal graticule and a high brightness CRT.

For further information contact The Dindima Group Pty Ltd, PO Box 106, Vermont, Victoria 3133.

## SUPPRESSION CAPS

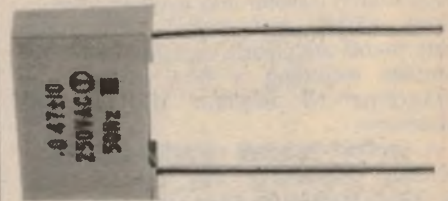

Soanar Electronics Pty Ltd has announced the introduction of the "Mainscap" suppression capacitor. Specifically designed for 250V AC circuits, this capacitor has been approved by the Energy Authority of NSW to Australian Standard ASC100-1972 and AS3145-1979 (CS1630N) for Class Y applications.

Using metallised polyethylene terephthalate film and fully encapsulated in epoxy resin, the Mainscap is fully sealed against moisture and humidity ingress and has self-healing characteristics for pulse operations.

The stock range is .01μF, .022μF, .033μF, .047μF, .1μF, .22μF and .47μF and the tolerance 10%. Other values, flying leads and delta configurations are available on an indent basis.

For full specifications and data contact Soanar Electronics Pty Ltd, 30 Lexton Road, Box Hill, Victoria 3128.

The Manual Calculations section covers direct execution of calculations using the device as a "scientific" calculator and is followed by a section on Programmed Calculations. Well illustrated with examples, this section is also the start of a BASIC primer (despite the suggestion that BASIC manuals be studied first). The section includes discussion on the organisation of the available memory and simple instructions on editing and debugging.

Under the heading of "Variables", the use of available memory is further discussed. The use of strings and indirect addressing is dealt with together with input and recall of contents. However, this section does not make clear one limitation - the fact that a character (alpha or numeric) can be sorted as a string ie, in a character variable, but if a digit, cannot be read from that string and processed as a numeric value. This makes handling of (for example) hex characters difficult (but by no means impossible).

The next sections, "Program Statements" and "Command Statements", really get down to BASIC, covering: LET, INPUT, PRINT, PAUSE (a 0.85 second PRINT), USING, GOTO, IF, GOSUB, RETURN, FOR & NEXT, STOP, END, BEEP (self-explanatory and a handy device when used with the PAUSE statement as one could miss a brief display) CLEAR, AREAD (a limited READ instruction) and REM as program statements.

The Command Statements are RUN, DEBUG, CONT, LIST, NEW, MEM, CSAVE, CLOAD, CLOAD?, CHAIN (a tape-search transfer and execute instruction), PRINT and INPUT. All these statements are clearly explained with examples including a flow chart, and diagrams to explain the CHAIN statement.

A section headed "RESERVABLE key" follows explaining the use of the RESERVE MODE to allow the call-up of short programs or functions by means of a single key. Keyboard Overlays are provided to allow marking of the designated keys (the bottom two rows of the keyboard).

The last section in the manual lists the Error Codes and explains the methods of indicating and clearing errors.

Appendices cover specifications, battery replacement, Cassette Interface Connection and Operation (including a CLOAD 1 Statement not previously mentioned) and end with "Some Sample Users' Programs".

**OPERATION**

As a manual calculator, having 10 digits and exponent range -99 to +99, the TRS80 is a powerful device. With the reservable keys programmed and its built-in functions, few extra keystrokes are needed for quite complex calcula-


tions, even when comparing the TRS80 with larger dedicated calculators.

The recall facility and the moveable cursor with edit keys (DELETE and INSERT) make its use as a calculator more versatile than one would expect. Functions directly available are SIN, COS, TAN (and their inverse functions), natural and common logarithms, EXP (natural antilog, e<sup>x</sup>), square root and powers; Gradians (100g=90°) - Degree/minute/second - Decimal degree - Radian angular modes or conversions may be specified; Integers, Absolute values and signs may be extracted. The basic four functions (+, -, \*, /) have keys in the numeric pad, but / and \* replace the last two, as for any other computer.

Fixed (A-Z) and variable (27-204) memories are available in the Manual mode. Strings may also be used in this

to be easily read. The PAUSE statement allows automatic display of information a line at a time (24 columns only - not much of a limitation) and should be used with the BEEP tone to avoid being taken by surprise by the first item.

The available 1.9K of RAM allows quite long (say 100 step) programs to be written while "in the field" and retained in memory until they can be transferred to tape. With a portable tape recorder they can be recorded on the spot, as well. Using the CHAIN command, much longer programs, broken into stages, can be executed, though the lack of an immediate print out may limit the need for this mode of operation. Long tapes can be searched for data or programs without manual supervision, making up for the limited RAM. The shortage of string manipulations mentioned earlier may be felt, for example, by those who wish to use programs involving hexadecimal/decimal or other base conversions, though these can be done less elegantly and at the expense of brevity

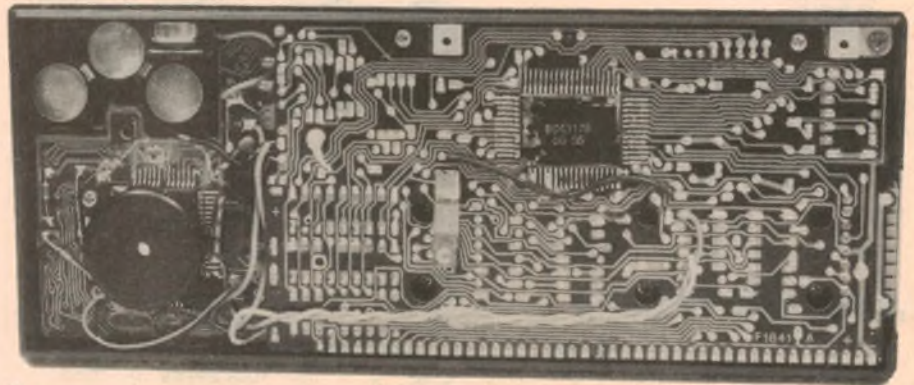

The back of the TRS80 can be removed to reveal the circuitry and batteries.

mode, but none of the usual BASIC string manipulations (LEN\$, MID\$, LEFT\$ etc) are provided in any mode. The logical operators (<=, >=, =, etc) and AND (\*) and OR (+) can be used, returning "1" when expressions are true and "0" when false.

The 80-character buffer, the 15 levels of parenthesis and the 24-column display (columns 25-80 are not accessible in this mode except when recalling calculations) make the TRS80 a match for any advanced calculator. Add to the foregoing the advantages of programming in BASIC and there is no doubt that this device is a breakthrough.

Treating the TRS80 as a computer, the limited display is a handicap only to those users who require graphics. The line and cursor controls (up, down rolling, Left, Right at two speeds) with the LIST and RUN statements, allow quick access to any part of a program. The Reserve mode can be used to effectively expand the keyboard and add subroutines quickly. From the physical point of view, the keyboard is not so small that the average finger(s) cannot make entries accurately, and the 9.5mm high display characters are large enough

with the TRS80. The limit of seven characters to a string can also be circumvented with a little thought and at the same price.

Operations of the TRS80 with the Cassette Interface and almost any tape recorder is simple, and few problems with levels are likely, thanks to the effective signal processing and muting system. The built-in tone monitor is useful though 4kHz can be irritating to nearby uninvolved parties.

As for the TRS80 "Pocket BASIC", there is little cause for complaints apart from those already noted; it is simple and efficient, and with four levels of subroutines and four levels of FOR-NEXT statements allowed, it has plenty of potential for most users. Software in tape form will shortly be available.

Inevitably, with the present rate of progress in this field, the TRS80 will have competition before long, but that is no argument against this excellent genuine microcomputer. Supported by Tandy service and with the example of the large amount of both soft and hardware developed for the original TRS80, it is likely to generate a very large following.



## Sound safe.

Agfa SUPERFERRO—the sound safe—will record and store your music safe in sound, ready for when you want it. And we mean all the music. The outstanding performance of Agfa SUPERFERRO is achieved through the use of a particular form of ferric oxide particle that is uniform in shape and size. The second factor is an Agfa technique that enables more particles to be deposited per sq. mm of tape, with each particle separated and in line to eliminate cross-over interference.

The advanced technology of the SUPERFERRO tape results in five big improvements:

1. Reduced background noise.
2. Better maximum output level.
3. Improved dynamic range.
4. Improved high frequency output level.

5. Reduced harmonic distortion. In addition, Agfa SUPERFERRO cassettes feature a special mechanism for improved running properties.

Agfa SUPERFERRO—the sound safe you can bank on for outstanding performance.



\*Registered trademark of AGFA-GEVAERT Antwerp/Leverkusen.





## Digital IC Probe & Logic Pulser

### PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

- Automatic threshold resetting • DE to > 60 MHZ
- Compatible with all logic families 4-15 VDC • 10Nsec. pulse response
- Supply O.V.P. to  $\pm 70$  VDC • 120 K  $\Omega$  impedance
- No switches/no calibration • Automatic pulse stretching to 50 Msec
- Open circuit detection • Automatic resetting memory
- Range extended to 15-25 VDC with optional PA-1 adapter

### PLS-1 LOGIC PULSER

The PLS-1 logic pulser will superimpose a dynamic pulse train (20 pps) or a single pulse onto the circuit node under test. There is no need to unsolder pins or cut printed-circuit traces even when these nodes are being clamped by digital outputs.

PLS-1 is a multi-mode, high current pulse generator packaged in a hand-held shirt pocket portable instrument. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic state. Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed, a single high-going or low-going pulse of 2 $\mu$  sec wide is delivered to the circuit node under test. Pulse polarity is automatic: high nodes are pulsed low and low nodes are pulsed high. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

- High input impedance (off state) 1 meg ohm • Multi mode-single pulses or pulse trains
- Low output impedance (active state) 2 ohms • Automatic polarity sensing
- Output pulse width 2  $\mu$ sec nominal • Automatic current limiting; 7 amps nominal
- Input over voltage protection +50 volts • Automatically programmed output level
- Finger tip push button actuated • Circuit powered
- Power lead reversal protection • No adjustments required
- Multi-family RTL, DTL, TTL, CMOS, MOS and Microprocessors

PRB 1	DIGITAL LOGIC PROBE	PA 1	HIGH VOLTAGE ADAPTER
PC 1	POWER CORD, Alligator Clips	PT 2	REPLACEMENT PROBE TIP (2)
PC 2	POWER CORD, Micro Hooks	PLS 1	LOGIC PULSER

## AMPEC ELECTRONICS PTY. LTD.

1 Wellington St, Rozelle, 2039. PO Box 132, Rozelle 2039. Ph (02) 818-1166.

Available from: NSW Radio Despatch Service, 211 0191 David Reid Electronics, 29-6601. Electronics (Distributors) 636-6052. Martin De Launay, 29-5834. Applied Technology, 487-2711. VIC: Stewart Electronics, 534-3733. Ellistronics, 602-3282. John Pearce, 528-5240. Ritronics, 489-8131. QLD: N.S. Electronics, 36-5061.

WA: Reserve Electronics, 275-2377. Taimac, 328-1988.



REVIEWS OF RECENT

# Records & Tapes

CLASSICAL ● POPULAR ● SPECIAL INTEREST

## BERG, STRAVINSKY — “A must for all violinists”

**BERG — Violin Concerto.**

**STRAVINSKY — Violin Concerto in D. Itzhak Perlman (violin) with the Boston Symphony Orchestra conducted by Seiji Ozawa. DGG Stereo Disc 2531 110.**

Here is an excellent example of the divergent lines avant garde music took during the early years of this century. Berg, a Schonberg colleague mentioned in the last issue (Pierrot Lunaire) was blessed with such a strong lyrical gift that even the ultra rigid disciplines of the serial method most of the time retained something very like the ghost of a melody.

Indeed, he is the only one of the Second Vienna School to win — and retain — some popular acceptance. His violin Concerto appears regularly on scores of concert platforms and has been recorded many times. The same applies to his operas *Wozzeck* and *Lulu*. There are other works of his in the regular musician's repertoire.

I think I can explain the popularity of the Violin Concerto because it emphasises rather more than usual the solo part — but without spotlighting it. This tends to make it sound like real music! It also has repetitive bars, forbidden in strict serialism.

You'll find the same wizardry in his operas of which *Wozzeck*, at least, has an absorbing dramatic libretto. When you get used to the concerto idiom I expect you will enjoy a deeply moving experience when listening to it. Indeed, I find that it tends to make the Stravinsky concerto on the reverse side sound almost facetious.

Stravinsky took a very different path. A pupil of Rimsky-Korsakoff he had a marvellous sense of orchestral scoring. He also brought with him a charming sense of romantic melody exhibited in his early works — the opera, *The Nightingale*, the ballets *The Firebird* and *Petrouchka*. This, plus a peerless sense of complicated rhythms, many of which might well be described as primitive, as in *The Rite of Spring*.

He then went on to a period of neo-classicism and also enjoyed putting his own stamp on music from the baroque and rococo periods. He did, well towards the end of his industrious life, turn briefly to serialism (*Agon*) but died before disclosing what this might have led to.

Both of these concerti were composed in the early 1930s and the Stravinsky is typical of his writing during this period.

The first movement, for instance, is jaunty with an overtone of mockery. The writing for both the solo part and orchestra is always wonderfully clean and incisive. Here and there during the work there is a hint of the garrulity of the baroque period; yet other parts of it are puzzlingly reminiscent of William Walton's post-Facade period. Bach also seems to keep a paternal eye on the way things are going.

The general impression of the whole

work is that of a man struggling to get out of a well-worn romantic cloak.

All this refers to the solo part and perhaps Stravinsky's significance during this period was in his treatment of the orchestra. It goes along its own way, seemingly ignoring the soloist most of the time. The Finale is a kind of *moto perpetuo* movement — a la baroque — but with characteristic syncopation.

I can find nothing but the highest praise for Perlman's performances of both these immensely difficult works. He displays seemingly endless technical resources, and is completely in sympathy with the intentions of both composers. And the same must be said of the Boston Symphony's support under Ozawa.

The album is a must for all violinists and anyone else interested in this interesting period of musical development. (J.R.)

## RESPIGHI: Pines, fountains and festivals

**RESPIGHI — Pines of Rome. Fountains of Rome and Feste Romane. Boston Symphony Orchestra conducted by Seiji Ozawa. DGG issued in Australia to members of the World Record Club. Stereo 2530 890.**

This Respighi disc is not a re-issue but a new recording of considerable merit. These picturesque but not great works were all the rage in the early '30s and their popularity has continued undiminished, with recordings being virtually uncountable.

Such a statement is strangely at variance with the welcome they received from the music critics in two Sydney daily papers, attributing to them blatant cacophony. This was in the '30s, when the ABC was beginning what might be called Sydney's musical education.

Today, of course, these three works sound quite mellifluous. They still make pleasing listening, especially when con-

ductors capture their spirit as Ozawa does here.

After the jaunty *Pines of the Villa Borghese* comes the contrasting mystery of the *Pines near a catacomb*. This is truly ghostly music, despite its unexpected but well prepared climax.

The *Janiculum Pines* really aroused the venom of the critics of the time, because the composer had had the impudence to include in his score a 78 recording of a nightingale singing. The producers perforce used the equipment of the day, so that it was pretty well inaudible; but nowadays, with our improved techniques, it is perfectly balanced into the score.

The suite concludes with the *Pines lin-*



ing the Appian Way and, with a little imagination, the march used calls up visions of a Roman legion of some 2000 years ago.

The Fountains is my favourite among the three suites and they gush and glitter as picturesquely as ever. The fluid scoring of the Triton Fountain is something every student of orchestration should study.

I Like Roman Festivals least of the three pieces, even though the work is admirably played by a huge orchestra and recorded with outstanding depth and detail. Altogether, a pleasant reminder of times past. (J.R.)

☆ ☆ ☆

**DVORAK — Cello Concerto in D Minor. Paul Tortellier (cello) and the London Symphony Orchestra conducted by Andre Previn. World Record Club Stereo R 06352.**

Great cellist though he is, Tortellier faces stiff competition from others in his recording of perhaps the finest cello concerto ever written. There is, of course, the famous Rostropovitch record, and one I am particularly fond of but recently deleted by Gaudron, to name only two of many.

But quoting these is not to be taken as disparaging this excellent recording under review. Tortellier is undoubtedly one of the finest present-day performers of this glamorous work. But I am afraid that on the day he recorded it he was not at his best; nor, for that matter, was Previn and his orchestra. And I have heard the London Symphony better recorded too.

I must stress, however, that the disc's shortcomings are all very slight and that they'd probably pass unnoticed by those who do not love the concerto as much as I do.

Perhaps some of these blemishes are due to the prominence of the cello part, beautifully played though it is. As a result, Dvorak's lovely orchestral scoring loses some of its exquisite detail. For instance, the clarinet is badly served in the enchanting slow movement. The only woodwind soloist to be given his deserts is the delightful flautist. In the Finale the clarinet is recorded much below average.

As an accompanist, Previn can usually be relied upon to be exceptionally sympathetic to his soloist but I'm not so sure about him this time, especially as an interpreter/collaborator. Here and there are passages where soloist and conductor do not seem of one mind. These, blemishes again, are slight, because Previn is much too fine a musician to pass any glaring faults. The same might be said of Tortellier.

Despite all that I have written, it is a great buy at the price it is offered to members. There is a fill, too — an enchanting bit of trivia, a Rondo in G Minor I have never heard before and which is deliciously played by soloist and orchestra. (J.R.)

## MUSIC UNDER THE MICROSCOPE

“... potentially valuable”

### GUIDE TO UNDERSTANDING MUSIC.

Produced for Stereo Review magazine by David Randolph. Four record boxed set, stereo C4-10384. [From MR Acoustics, PO Box 165, Annerley, Qld 4103. Phone (07) 48 7598. \$36.00]

I have been consciously dodging this review since receiving the last batch of records from MR Acoustics — this for one simple reason: it takes quite a while to listen to both sides of four LP records! But let me hasten to add that, for many, it will be a potentially rewarding experience.

David Randolph is a prominent choral conductor, broadcaster and lecturer on the New York scene, and author of the book “This is Music”.


Carefully, painstakingly, he examines the nature and structure of music, illustrating every point with excerpts — most of them tantalisingly brief — drawn mainly from nominated classical recordings. Here is a brief rundown of the topics, referenced to the sides:

1 — Rhythm, melody, harmony; 2 — The Textures of Music; 3 — Sense and Sensation in Music; 4 — How Music is Unified; 5 — Form in Music; 6 — Words and Music; 7 — Can Music Tell A Story or Paint a Picture?; 8 — Interpretation of Music.

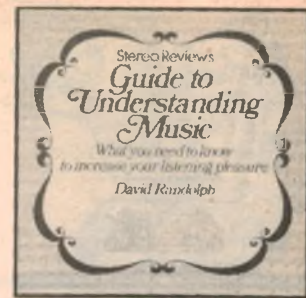**LISZT: Complete Hungarian Rhapsodies. Hungarian Rhapsodies Nos. 1-19; Polonaise from “Eugen Onegin” of Tchaikovsky; Illustration No. 2 from “Le Prophete” of Meyerbeer; Waltz from “Faust” of Gounod; Reminiscences de “Norma” of Bellini. Michele Campanella, piano. Philips Box of four stereo discs 6999 084.**



As far as I know, the only other pianists to record the whole of Liszt's 19 Rhapsodies in recent decades were Louis Kentner (a true Liszt specialist) and Philippe Entremont, a good all-rounder, whose principal work has concentrated on Ravel and Debussy. Others, with Alfred Brendel in the lead, have studied



Accompanying the set is a brochure which introduces the author/narrator and provides background to the recordings. It also contains a full list of the recorded excerpts used to illustrate the text.

Who could benefit from this quite ambitious presentation? Certainly music teachers in classroom situations. By following through the various topics and allowing time for discussion and further examples, there is material here for quite a few periods.

In a less formal situation, the presentation is adequately clear and self-sufficient for home listening, even at a group level. It could introduce the structural aspects of music to the uninitiated who may not, as yet, have thought much about it.

And it could also help those who have developed a warm response to various works and composers, without quite understanding why.

The narration is good, as is the dubbing and panel work, and the recording itself well up to standard. A potentially valuable addition to any collection. (W.N.W.)

these works lovingly without, however, recording more than a discreet selection from the whole set.

Michele Campanella, now in his early thirties, has distinguished himself in many competitions, both in Italy and elsewhere and is getting fairly well known in Europe. He plays these works very well indeed and certainly has no technical problems; what leaves me less than enthusiastic is his musical approach: there is a tendency to exaggerate rhythms, to lapse into hoppity-hop at the least provocation. But what really bothers me is a patent lack of excitement and personal involvement; he can play the pieces, but it seems a chore rather than a labour of love.

As the heading makes clear, Philips have thrown in an extra disc of operatic paraphrases and these are certainly welcome as demonstrations of the artist's ability to become involved, and not just technically. If you want all the rhapsodies together and cannot find (or afford) the Kentner set, get this by all means; however, be prepared for odd disappointing moments musically and also for the fact that some of the lowest bass notes lack clarity — possibly due to the piano used in recording. (P.F.)

**BRUCKNER — Symphony No. 7. Berlin Philharmonic Orchestra conducted by Herbert von Karajan.**  
**WAGNER — Siegfried Idyll. Selected members of the same orchestra under Karajan. DGG Stereo recording issued in Australia to members of the World Record Club. R-06377-8. Two Discs.**

If you have patience, you will hear some fine melodies in this mostly slow moving symphony. Myself, I'm temperamentally unsuited to so much nobility. You will also hear much peerless playing by the Berlin Philharmonic exploited to its limit by Karajan. The work itself is full of spacious landscaping.

You will also enjoy an Adagio movement, a tribute to Bruckner's adored Wagner that, for me, makes the whole of the rest of the work well worthwhile. The Scherzo, fails to give much sense of fun but is rescued from monotony by

Karajan's enchanting pointing of the rhythm.

Though some might prefer it a little more pointed I thought it fitted perfectly into Karajan's overall plan of the work. And he also finds just the right difference in tempo in the Trio.

Another fact worthy of attention is Karajan's more forceful accenting of the Finale which goes far to explain his more delicate treatment of the Scherzo. Under his direction the symphony, already broad, takes on still broader proportions. Long, sometimes very long melodies unwind majestically till the final peremptory ending.

The fill is Wagner's Siegfried Idyll which Karajan handles as tenderly as he might his first born. Taking the splendour of the playing for granted there is, in the sleeve notes, an interesting explanation of Wagner's mysterious dedication of the work which reads: "Triebtschen Idyll, with Fidi's bird-song and Orange Sunrise, presented as a Symphonic Birthday

pleasant listening experience to those who have yet to make its intimate acquaintance.

The handsome double-fold jacket carries full notes on the musicians, the recording process, and the work itself, including the sonnets which traditionally accompanied the score and which established the connection between the music and the thought patterns which prompted it. (W.N.W.)

Greeting to his Cosima by her Richard, 1970". Well, Triebtschen was the name of the Wagner house near Lake Lucerne. Fidi was the young Siegfried recently born by Cosima, and the Orange Sunrise was the colour of the wallpaper beside Cosima's bedroom. Again, it may refer to the Berlin Zoo, where the two swore eternal fidelity to one another back in 1863!

☆ ☆ ☆  
**HITS FROM BERLIN. 1927-1931. Jack Hylton and His Dance Band. Mono, World Record Club WRC R-06658.**

This is a real turn-the-clock-back effort, recalling the period 1927-1931, when a conscious effort was being made in Europe to heal the wounds of World War I. In this generous collection of 16 recordings, Jack Hylton is playing numbers attributable to German composers. A few of the English titles are:

When Day Is Done — I Kiss Your Hand  
 Madame — When The White Lilacs Bloom Again — O Maiden, My Maiden — Falling In Love Again — White Horse Inn (selection) — Today I Feel So Happy.

Along with the detailed jacket notes, each track is dated (Aug '27 to Sept '31), and the changing personnel of the band is noted. Archive material indeed.

The first track "When Day Is Done" opens to such a brisk tempo that one gets an instant recall of the frantic dance routines of the day. Notable, too, is what passed for appropriate vocals: I'll say no more!

The  
4



## Seasons . . .

**VIVALDI — The Four Seasons. Gerard Schwarz and the Los Angeles Chamber Orchestra. Elmar Oliveira, violin. Digital-master stereo, DMS Delos DMS 3007. (From PC Stereo, PO Box 272, Mt Gravatt, Qld 4122. Phone 07 343 1612).**

Here is yet another release on the Delos label, which attempts nothing spectacular, but which succeeds in capturing clean, intimate orchestral sound, sometimes quite vigorous, sometimes fading through whisper-quietness into silence.

Gerard Schwarz may be better known to some as the virtuoso trumpeter who featured on a couple of recent Telarc digital discs, but he also happens to be prominent in the rising generation of American conductors.

Elmar Oliveira is also a notable young musician, the first American to win the Gold Medal in the Tchaikovsky International violin competition in Moscow, and seen by many as a likely successor to the passing generation of violin greats.

The backing chamber orchestra was founded by Neville Marriner and is now under the directorship of Gerard Schwarz.


The sound is clean, intimate and virile; it should appeal to those who are familiar with the work and provide a



## VIDEO TECHNICS

THE CAROUSEL CENTER, SHOP 17 & 18, 530 OXFORD ST. BOND JUNCTION  
 P.O. BOX 50, BOND JUNCTION, BOND JUNCTION NSW 2022 TEL 387 2555  
 3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE,  
 BRISBANE 4064 PH 36 1257

## UNIVERSAL CAPABILITIES

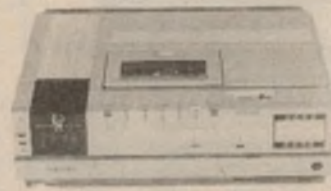

## VIDEO SYSTEMS

These National and Sony video recorders fitted with appropriate receivers can record and play PAL and SECAM and play NTSC.

There is no limit to what you can see.

Now you can play tapes from the US, France, as well as Australia.

In fact from anywhere in the world.

FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA

## RECORDS & TAPES — continued

Technically, the frequency response of the recordings is very limited but the sound is clean and substantially noise-free. An album for those interested in a slice of musical history. (W.N.W.)


☆☆☆

**JAZZ ULTIMATE.** Bobby Hackett & Jack Teagarden. Stereo, World Record Club WRC-R 06766.

From an original Capitol recording, made in New York in September 1957, this club re-release still makes excellent listening.

It features Bobby Hackett on trumpet and Jack Teagarden on trombone — both jazz masters of their respective instruments. They are backed by a formidable team: Gene Schroeder, Peanuts Hucko, Billy Bauer, Ernie Carceres, Buzzy Drootin and Jack Lesberg.

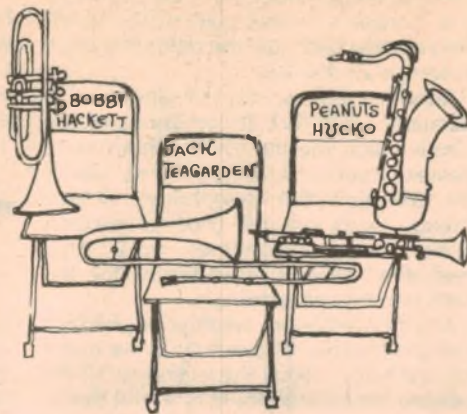There are 11 tracks in all: Indiana — Oh Baby — It's Wonderful — I Found A New Baby — Sunday — Baby, Won't You Please Come Home — Everybody Loves My Baby — Mama's Gone, Good Bye —



'Way Down Yonder In New Orleans — 55th And Broadway — 'S Wonderful.

"Just about anybody can enjoy the music on this album" say the jacket notes and that's probably not too far from the truth. It's a happy uncluttered sound, with Hackett and Teagarden working their way through freewheeling improvisation. (W.N.W.)

☆☆☆

**BLACK RUSSIAN.** Black Russian. Motown M7942. Astor Records.

Three immensely talented young Russian musicians (1 female and 2 males) known as Black Russian defected from Russia to the US in 1976. They are the first Soviet rock musicians ever to sign with an American recording company, and this is their debut album.

The sound is unique, reflecting the group's background in classical music, as well as the influence of rhythm and blues, rock and jazz.

The group wrote, arranged and produced all of the following eight tracks: More Together — Cause I Love You — Love's Enough — Leave Me Now — Mystified — New York City — Life Is Too Short — Emptiness.

An exciting debut album with clear vocals backed with fine musical arrangements. (D.H.)

☆☆☆

**IRONS IN THE FIRE.** Teena Marie. Motown G8997. Astor Records.

This is Teena Marie's third album for Motown Records and is virtually the imaginative creation of one person, with Teena writing the songs, handling their rhythm arrangements and overseeing the ultimate musical outcome.

The eight tracks on the album are: I Need Your Lovin' — Young Love — First Class Love — Irons In The Fire — Chains — You Make Love Like Springtime — Tune In Tomorrow — You Make Love Like Springtime (Reprise).

This is a refreshing album containing tracks of rhythm and blues and sentimental ballads.

The recording quality is also of a very high standard. (D.H.)

☆☆☆

**JADE HURLEY.** Festival Records. Stereo L37023.

Twelve tracks with a distinctive country flavour make up this excellent disc from Jade Hurley. Jade had a hand in writing

**NOW — AVAILABLE DIRECT**

### SOLAR-POWER ALARM WATCHES

**"5 YEAR" SOLAR BATTERY POWER**

**BEEP! BEEP!!**

**WITH 12/24 HOUR SYSTEM**

**\$135**

**\$85**

**WATERPROOF TO 100FT.**

YES — This is the latest "Superior Quality" Super Slim "Solar-power" Alarm Chronograph — Displays 12 Functions WITH 1/10 sec. Lap-Time, Stop-Watch, 12/24 Hour Selectable System, AND Loud Daily Alarm. Waterproof to 100ft, Shockproof, 100% Stainless Steel, Mineral Glass, Instructions, 2 Year Guarantee.

Send name & address for your . . .

**FREE** FULL DETAIL COLOUR PHOTOS OF RANGE TO:..

**QUARTX INTERNATIONAL**

G.P.O. BOX J666, FORREST PLACE, PERTH. W.A. 6001.

**TRADE ENQUIRIES WELCOME**

## Recent devotional releases

**THE BEST OF B. J. THOMAS.** Myrrh MSB-6653. (From Word Records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135.)

Ten tracks with predominantly ballad style form a showcase for the vocal talents of B. J. Thomas on this enjoyable record from the "Word" stable. While the sleeve does not carry the lyrics, the singer's diction is so good that this is not too much of a problem.

The tracks are: Without A Doubt — Storybook Realities — Home Where I Belong — I Want To Be More Like Jesus — Happy Man — What A Difference You've Made — He's The Hand On My Shoulder — Jesus On My Mind — You Gave Me Love — Faith Of A Little Child.

All are songs of simple faith, well worth listening to. (N.J.M.)

☆☆☆

**TAKE IT EASY.** Chuck Girard. Stereo, Good News Records GNR 8108 (From Word Records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135).

Chuck Girard's latest release is a pleasant mixture of rock and ballad styles with an excellent backing group. There are ten titles:

Chuck Girard — rock and ballad



Take A Hand — Love Is Alive — Little People — Full Immersion Ocean Water Baptism By The Sea — Without Your Love — Our Lives Are In Your Hands — His Word Is Still His Promise — Song For A Christian Wedding — Wings Of Mercy — All I Want.

The "Song For A Christian Wedding" is worthy of attention, particularly when so many marriages seem to last only a short while. The record is a release from Myrrh records, a division of "Word" Records who seem to have most of the leading Gospel musicians under contract. (N.J.M.)

many of the songs himself, and he is backed by a competent group on guitar, banjo, percussion, bass and various keyboard instruments. As with other country music, two themes are prevalent on this album — love and going home.

The tracks are: For The Last Time — You Can Make Me Smile — Takin' The Country Road Home — Lady — Paradise — The Devil In Me (Is In Love With The Angel In You) — Hey Mr Lazy — Listen To The Singer Listen To His Song — I Want You To Spend Tonight With Me — I'm Goin' Back Where I Belong — I Write The Words And I Sing The Song — You Are The Reason.

Don't worry if the track titles are unfamiliar. The words are printed on the jacket if you fancy a sing-a-long. Recording quality is well up to standard. (G.S.)

☆ ☆ ☆

**THE SECRET POLICEMAN'S BALL. Stereo, Island L-37253. Festival release.**

This new album is a recording of a show put on, at no charge, by a bevy of Britain's "superstar comedians" in aid of Amnesty International. Included are such names as John Cleese, Peter Cook, Billy Connolly, Mike Balin, Terry Jones, Rowan Atkinson, John Fortune and Eleanor Bron.

The humour is Goon style, brilliantly written and performed.

But . . . on the cover is the warning: "This album contains language which may be considered offensive".

## Carlo Curley at the Alexandra Palace

**AN ADVENTURE IN SOUND.** Carlo Curley plays the Allen Digital Organ at Alexandra Palace, London. Stereo, Chalfont STG 77021. (From Allen Organs Aust, 32 Woodhouse Rd, Doncaster East, Vic 3109. Tel (03) 842 3465. \$8.00 + \$1.30 P&P Melbourne, \$1.60 P&P elsewhere.)

If the sound at Holy Redeemer Church (reviewed last month) was big, here it is enormous. What else would you expect of an organ similar to Carlo Curley's own touring instrument: 5 tons in weight, 4 manuals, 164 stops and 380 loudspeakers?

All this set up in the Alexandra Palace, with its 7-second reverberation period. Not that this is any great hassle, as far as the recording is concerned. The venue had been the scene of two major seasons, more than a dozen full-scale recitals, and a hugely successful BBC television special.

The more is the pity. Performers of this calibre don't need to rely on four letter words and double entendre to win laughs. What is does is merely alienate a segment of listeners who would otherwise want to share the show with their friends.

And that includes this reviewer. (W.N.W.)



In the jacket notes, Jerome E. Ruzicka refers to Carlo Curley's one-time flamboyant style but there is no doubting his sheer ability as he presents seven of his own favourite items and encores: Toccata and Fugue in D minor (J. S. Bach); Fantasia in F minor (W. A. Mozart); Toccata from Symphony No. 5 (Widor); Fugue a la Gigue (J. S. Bach); Trumpet Voluntary in D major (J. Clarke); Scherzando (C. Pierre); Finale from Symphony No. 5 (Widor). Considering the reverberation and (at times) the huge sound and bass content, the definition is very good indeed and the recording very clean. Full marks must go to those in charge of the technicalities.

Interestingly, however, there is reference in the jacket notes to a digital version of the same performance. It does not appear to be available at present in Australia but, if it does ever show up, it should be a "bottler" (translated: very impressive). (W.N.W.)

CASSETTE  
SPECIALS  
C90

Price per box  
of 10

OPUS UD \$19.00

AMPEX 20/20 \$21.30

AMPEX GRAND  
MASTER I \$36.00

**Mail order charges:**

Up to 20: \$2.75

20 to 50: \$3.50

Over 50: \$5.00

## PHILIPS LOUDSPEAKERS

### PROFESSIONALLY DESIGNED SPEAKER KITS

If you are in the market for a \$2000 set of speakers with only a few hundred dollars in your pocket, we could have just what you want. The ETI 4000 Series Speakers — using Philips Drivers — compare very favourably with speakers costing twice to three times as much. If you are on a really tight budget you could consider the Philips AD12K12 kit — a 70 watts r.m.s. per channel 12" 3-way system — which you assemble completely in about 2 hours. A steal at under \$300 per pair. You can buy all components with or without boxes, any way you like. We have both the ETI 4000-I and II on display, as well as other Philips Kits. Come in for an audition, or write for further information.



northpoint hi-fi

100 Miller St, North Sydney.  
Ph 922-7780.



# Books & Literature

## CP/M disc-operating system explained

**THE CP/M HANDBOOK with MP/M, by Rodnay Zaks. Published by Sybex, USA, 1980. Soft covers, 136mm x 214mm, 321 pages. Illustrated with photos, sample user input and computer outputs. Price \$18.40.**

Firstly we should explain for the uninitiated, that CP/M is a disk operating system designed by Digital Research Corporation, various versions of which have been written for such microcomputers as the Cromemco, PET, APPLE, TRS-80, NORTHSTAR, in fact most of the popular computers. Unlike the resident monitors of most computers though, it is not stored in ROM and hence must be bootstrap loaded from the disk each time the computer is turned on – just as is done on all large computers and minicomputers.

The term "bootstrap loaded" refers to a small program which is actually part of CP/M but which is always resident in the computer. When power is first applied the computer automatically executes this bootstrap program, which then loads the entire CP/M operating system – in effect, the CP/M cpu loads itself by its bootstraps.

The advantage of CP/M is that since it runs on most computer systems the user can work on any of these systems without having to learn a new "language" for each one. It is also a powerful operating system offering a vast range of software such as an assembler, editor, debugger and extensive file handling commands to rename, erase and save files, etc.

The CP/M handbook covers all these topics well and should provide an excellent supplement to the standard manuals. The subject is discussed in an evolutionary manner starting from turning the power switch on, all the way to editing and saving programs. Technical terms are clearly explained and there is a vast amount of computer dialogue to illustrate how the computer responds to various commands.

Contents of the book are as follows: Introduction to CP/M, CP/M and MP/M facilities, Handling files with PIP, Using the Editor, Inside CP/M, Reference guide to CP/M and MP/M commands and programs, Practical hints, the future. There are also extensive appendices tabulating ED and CP/M commands, PIP keywords, HEX conversion tables etc.

The thorough coverage of all levels of CP/M and MP/M and in particular the easy clear style in which the book is written could make it invaluable to the CP/M user.

We obtained our review copy from McGills Authorised Newsagency, 187-193 Elizabeth St, Melbourne. (R.deJ.)

## Antenna Catalogue

**HI-Q COMPLETE AERIAL CATALOGUE. Stiff paper cover, 44 pages, 242mm x 180mm illustrated.**

In some ways a companion volume to their "TV and FM Aerial Installations", Hi-Q have now released a catalogue of antennas which they have available for purchase and installation by home handymen. Included in the catalogue was a "Hobbyist" price list and order form.

Most of the antennas illustrated are manufactured by Hi-Q but models by other manufacturers are also included.

Catalogue sections cover TV aerials, caravan systems, aerial spares and accessories, installation components, cable, plugs & sockets & switches, baluns & splitters, outlets & filters, amplifiers and rotators.

A covering letter says that a range of "Channel 0" antennas is available, although not mentioned in the catalogue. If required, information on Channel 0 antennas should be requested.

The catalogue is available from Hi-Q Aerials, 69 Maitland Rd, Islington, NSW 2296. Phone Newcastle 61 5317. (W.N.W.)

## BASIC Programming

**DICK SMITH'S EASY WAY TO PROGRAMMING IN BASIC; by John and Judy Deane. Stiff paper covers, 85 pages plus appendices, 297 x 212mm, illustrated. Published by Dick Smith Electronics Pty Ltd. Price \$9.95.**

The System 80 distributed in Australia by Dick Smith Electronics is a highly competitive alternative to the Tandy TRS-80. It is very largely software compatible with the TRS-80, and therefore supports

a rather powerful BASIC interpreter. To help solve some of the mysteries of the BASIC language, and to assist those people who have not had any contact with computers, Dick Smith Electronics have released this book.

Written along the same lines as the Sorcerer manual (by the same authors), it provides an entertaining introduction to computer programming using the BASIC language.

The opening chapter starts by showing the user how to connect the system to the power and how to hook the monitor (or TV set) to the system. This is done in a step-by-step fashion, and the way in which it is written immediately tends to give the newcomer confidence.

In the chapters that follow, the reader is introduced to the basics of stored program writing and execution, dealing with two or three commands or statements at a time. The graphics capabilities are also discussed in detail. This comes in handy when writing your own games programs.

At the end of each of the chapters there is a summary of the points covered. Each chapter also contains one or two exercises involving the BASIC statements or commands covered. The answers to these exercises are to be found in Appendix C, at the back of the book.

Altogether the book is well written, and should fulfil its intended task in introducing the concepts of programming. It should also prove a valuable aid to those with more programming experience since it is a great refresher course as well.

Our review copy came from Dick Smith Electronics, and copies should be available from all Dick Smith outlets by the time this appears in print. (G.C.)

## Your First Computer

**YOUR FIRST COMPUTER, A guide to business and personal computing, by Rodnay Zaks. Soft covers, 258 pages, 140mm x 217mm. Published by Sybex Inc, USA, 2nd edition 1980. Price \$13.20.**

The author, Rodnay Zaks, has written quite a few books on microcomputers, and his considerable experience in this field is reflected in the contents of this book. If you are just starting in microcomputers or if you already have a "system" then this book should be invaluable.

It starts off with a futuristic discussion on the uses of microcomputers giving the reader a clear perspective of what can be done with a computer system. This is followed by chapters on using the system, basic definitions, how the system works, programming the computer, from Basic to Cobol, business computing, selecting a system, the peripherals and many more plus appendices on logic elements, the binary number system and disk file structures.

Virtually every aspect of microcom-

puters is covered, with many technical terms such as floppy disks, interpreter, breakpoints etc, clearly explained. The operation of micros and peripherals such as UARTs, CRTs, printers, ROMs, is also discussed on a basic level. If you are after a system then the chapter on "selecting a system" could be useful. It contains an extensive listing of the various micros available, with photographs and brief technical details.

Also of interest is the chapter on "programming your computer" which discusses the various languages used on micros, eg BASIC, APL, FORTRAN, PASCAL, COBOL. Program examples in each language are given along with a discussion of programming features and their advantages and disadvantages in various applications.

The extensive coverage of microcomputers and associated topics in an easy to understand manner makes this book ideal for the beginner and we have no hesitation in recommending it.

Our review copy came from McGills Authorised Newsagency Pty Ltd, 187 Elizabeth St, Melbourne, 3000. (R.de.)

## Electrical Principles

**ELECTRICAL & ELECTRONIC PRINCIPLES** by S. A. Knight. Soft covers, 151 pages, 185mm x 246mm, illustrated with circuit diagrams, waveforms. Published by Newnes Butterworths, England, 1980. Price \$11.50.

There are numbers of other books in the same series which are all written for the English electronic certificate course. The material in this book basically covers passive circuits, viz resistors, capacitors, inductors, transformers and electrical machines at a fairly elementary level and includes a large number of worked examples plus self test questions.

Chapter 1 starts with a discussion of Norton and Thevenin equivalent circuits and then goes on in chapter 2 with a discussion of DC transients, ie, simple R-C and L-R circuits and exponential charge/discharge waveforms. In the next two chapters the response of RC, LR and LCR circuits to AC is studied with a clear explanation of phase, impedance, power factor, reactive power, and resonance.

Transformer principles are the subject of chapter 5, though the discussion is limited, with nothing more "meaty" than turns ratio and a qualitative treatment of transformer losses. Following chapters are titled: three-phase circuits, electrical machines, the induction motor, methods of measurement and the final section provides answers to the self-test problems in the previous chapters.

All in all the author treats each subject in a clear, easy-to-follow manner making this book ideal for technical college courses or for the beginner who is interested in learning basic theory.

Our review copy came from the publishers, Butterworths, 586 Pacific Highway, Chatswood, NSW 2067. (Rdl)

# NEW BOOKS

## NEW — NEW — NEW

Latest editions of some of the most popular books on the subject:

The Radio Amateur's Handbook — ARRL 1981 Edition Just out!! A must for the Radio Amateur and Professional	\$14.95
R S G B Handbook Volume 1	\$21.85
R S G B Handbook Volume 2	\$18.90
Reference Data for Radio Engineers (New Edition) I.T.T.	\$39.95
Radio Handbook (William Orr) 21st Edition	\$27.75
Australian Amateur Operator's Handbook — Postal & Telecommunications Department	\$3.60
Practical Antennas for the Radio Amateur (Scelbi)	\$12.95

## Adam Osborne Books

The 8086 Book — Rector	\$18.00
Z8000 Assembly Language Programming — Leventhal	\$15.00
Introduction to Microcomputers. Osborne Vol. 0 — Beginners Book	\$11.50
Vol. 1 — Basic Concepts 2nd ed	\$15.00
Vol. 2 Some Real Microprocessors — New Edition. Loose-leaf w/out Binder With Binder	\$19.00 \$28.00
Vol. 3 Some Real Support Devices — New Edition. Looseleaf w/out Binder With Binder	\$19.00 \$28.00
6800 Programming for Logic Design	\$13.50
8080 Programming for Logic Design	\$12.55
Z80 Programming for Logic Design	\$13.50
Z80 Assembly Language Programming	\$13.80
6800 Assembly Language Programming	\$15.00
8080A/8085 Assembly Language Programming	\$15.00
6502 Assembly Language Programming — Leventhal	\$15.00
8088 1/0 Process handbook — includes 8289 Bus Arbiter	\$7.15
Pet and the IEEE 488 Bus (GP1B) — Fisher & Jensen	\$18.00
Pet/CBM personal computer guide—Donahue & Enger	\$18.00

## New Books from T.A.B.

Complete Handbook of Robotics — Safford, Jr	\$9.95
Master IC Cookbook — Hallmark	\$12.50
Antenna Construction for Ham, CB & SWL	\$7.50
Beginners Guide to Computers & Microprocessors with Projects	\$8.50
Master Handbook of 1001 Practical Electronic Circuits	\$12.50
Master Handbook of 1001 More Practical Electronic Circuits	\$15.95
Towers' International Transistor Selector	\$8.50
How to Build Your Own Working Robot	\$8.50
Pet — DaCosta	\$8.50
The Active Filter Handbook — Tedeschi	\$8.50
Complete Handbook of Radio Receivers — Carr	\$10.95
Complete Handbook of Radio Transmitters — Carr	\$10.95

## American Radio Relay League

A.R.R.L. Antenna Handbook	\$8.30
The Radio Amateur's License Manual	\$6.80
FM & Repeater for the Radio Amateur	\$8.80
Single Sideband for the Radio Amateur	\$7.20
Ham Radio Operating Guide	\$7.20
Electronic Data Book	\$7.20
Solid State Design for the Radio Amateur	\$9.80
Tune in the world with ham radio — includes Text, Tape Cassette & Workbook Complete box set	\$10.50
A.R.R.L. Antenna Anthology	\$6.80

## Microprocessor Books

The Basic Handbook — Lien	\$17.95
Learning Basic Fast — DeRossi	\$10.95
6502 — Applications Book — Zaks (Sybex)	\$18.20
6502 — Software Design — Scanlon	\$14.20
TRS-80 BASIC — A self-teaching Guide — Albrecht Inman & Zamora	\$12.55
TRS-80 Interfacing Book I — Titus	\$11.95
Microprocessor Interfacing Techniques Zaks & Lesea Sybex	\$16.95

Just a few of the thousands in stock Call in or write. Prices subject to fluctuation Correct at time of going to press.

If the book you require is not listed below, it can be ordered from us.

Practical Microcomputer Programming The M6800 — Weller	\$36.55
Some common basic programs for the pet — Cassette	\$18.00
Some common basic programs for the TRS-80 — Cassette	\$18.00
Basic programming primer — Waite & Pardee	\$12.70
Computers & computing — Australian Yearbook 1980 ETI	\$4.95
Introduction to low resolution graphics — (Scelbi)	\$12.95
Microcomputer interfacing with the 8255 PP1 chip — Goldsbrough	\$12.70
6502 software gourmet guide & cookbook — (Scelbi)	\$14.25
8080/8085 software design book 1 — Titus, etc	\$12.35
8080/8085 software design book 2 — Titus, etc	\$14.20
TEA an 8080/8085 co-resident/assembler — Titus	\$11.50
Z-80 microcomputer design projects — Barden	\$17.80
Z-80 microcomputer handbook — Barden	\$12.70
Z-80 microcomputer programming & interfacing book 1 — Nichols etc	\$15.60
Book 2 — Nichols etc	\$17.80

## Howard W. Sams Books

TTL Cookbook (Lancaster)	\$13.60
TV Typewriter Cookbook (Lancaster)	\$14.20
The Cheap Video Cookbook (Lancaster)	\$7.95
Active Filter Cookbook (Lancaster)	\$17.95
Transistor Substitution Handbook	\$7.95
TTL Cookbook — Lancaster	\$13.60
IC Op Amp Cookbook — Jung — New 2nd Edition	\$19.95

## Pianos, Organs etc.

The Art of Organ Building — Audsley Volume II	\$17.50
The Organ — Its Evolution, Principles of Construction and Use — Sumner	\$29.95
The Cinema Organ — Reginald Foort	\$9.30
The Reed Organ: Its Design and Construction — Milne	\$6.00
Piano Servicing Tuning & Rebuilding Arthur Reblitz	\$19.15
Player Piano Treasury — Harvey Roehl	\$20.00
Harpichord design and construction — Kern	\$25.00

## Other Titles

How to Build a Small Budget Recording Studio From Scratch with 12 tested designs — Everest	10.95
Practical Guide for Concert Sound — Hell	\$13.35
Tilt — The Pinball Book — Tolbert Home	6.95
Maintenance. History. Hot Tips	6.95
Questions & Answers for the Novice Licence — Westlake Radio	\$5.95
Electric Guitar Amplifier Handbook — Darr	\$15.00
Motorola CMOS Data Book	\$10.00
73 Dipole and Long-wire Antennas (Edward M. Noll)	\$6.75
73 Vertical, Beam and Triangle Antennas	\$7.80
Basic Television — Principles and Servicing — 4th Edn (Bernard Grob)	\$18.75
Amateur Radio Operating Manual Eckersley	\$13.30
The World in My Ears — Cushen	\$15.95
SCR Manual — Including Triacs and other Thyristors 6th Edition	\$4.65
Beam Antenna Handbook — New 5th Edition (William I. Orr & Stuart D. Cowan)	\$5.95
Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan)	\$5.95
All about Cubical Quad Antennas —	\$5.70
Amateur Radio Theory Course — Ameco	\$8.00
Electronic Projects for Musicians — Anderson (Guitar Player Pubs)	\$9.95
Ham & CB Antenna Dimension Charts Noll	\$3.20
Metal Detecting In Australia — Webster	\$4.50

MAIL ORDERS BY RETURN

PLEASE ADD 90c per parcel postage (Vic)  
\$1.70 per parcel interstate

TECHNICAL BOOK & MAGAZINE CO.

295-299 Swanston St., MELBOURNE 3000. Ph. 663 3951.



The Rolls  
Royce of  
personal  
computers



or the basis  
for a  
fine  
business  
system

# Yet the Sorcerer will still cost you less!

Looking for a really serious small computer? Feature for feature, dollar for dollar, the Sorcerer is way out in front. When you've finished playing with the others, move up to the Sorcerer.

**Features:**

- Up to 48K RAM on board — with full S-100 expansion for a huge number of peripherals, etc.
- User-definable graphics and full upper & lower case character set as standard; also special character set.
- Plug-in ROM PACS™ give you instant changeover for special applications: Word processing, software development, etc. Or your own custom programs, using the EPROM PAC.
- Numeric keypad as well as full 63 key ASCII set.
- Centronics-type printer interface & RS-232C communications port built-in as STANDARD!

**FROM ONLY \$1340**

Credit terms available to approved applicants

Cat. X-3000 8k Memory <b>\$1340</b>	Cat. X-3001 16k Memory <b>\$1395</b>
P&P \$5.50 per unit	

## look at our prices for peripherals

### Video Monitor



**Suits Sorcerer, Tandy TRS-80, Apple etc.**

Why waste money on overpriced monitors? This unit has large 30cm diag screen plus it simply connects to your computer via an RCA socket. 240V AC or 12V DC operation.

**\$149<sup>50</sup>** X-1196  
P&P \$5.50

### S-100 Expansion Unit



**Use other manufacturer's peripherals with your Sorcerer & S-100**

For the serious computer owner. Contains powerful computer power supply plus buffer/interface circuit to protect the computer in case of damage to the S-100. Plus many more benefits.

**\$575** X-3010  
P&P \$5.50

### Floppy disc drives



Need more storage? Floppies are the way to go. Quality Micropolis disk drives added on to your system can give up to 1260K bytes capacity!

Start with the Micropolis 1043 — it comes with the controller board to plug into your S-100 expansion unit. This gives you 315K.

If you want more capacity, use the Micropolis 1023 drive: it uses the 1043 controller board, so it's cheaper — much cheaper (\$600 to be precise!) You can add up to three 1023 drives, bringing your total capacity to over one and a quarter megabytes! Compare the cost of our 1.26M system with others — and be pleasantly surprised

X-3205 \$1350.00 X-3208 \$750.00

### Sorcerer ROMPACS™



Just plug them in — they instantly re-program the Sorcerer for specific uses. No problems!

#### WORD PROCESSOR PAC™

Want professional quality Word processing at a fraction of the cost of commercial systems? Your Sorcerer, Word Processor Pac™ and our daisy-wheel printer — and you're there!  
Cat. X-3085 \$275.00

#### DEVELOPMENT PAC™

If you're serious about developing your own software, this is a MUST! It turns the Sorcerer into a powerful, dedicated development system for Z-80 assembly language programming  
Cat. X-3090 \$139.50

#### EPROM PAC™

The Sorcerer is ideal for dedicated uses: this PAC allows an EPROM to be used to control the computer. Ideal for all types of control systems, etc.  
Cat. X-3095 \$75.00

# DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



# Column 80

by JAMIESON ROWE

Technical Director,  
Dick Smith Electronics

## Interpreters and Compilers Explained

Do you know the basic difference between an interpreter and a compiler, and the relative advantages of each? This month we take a look at these two important types of "systems software" program, and explain how they are used.

You can't go very far with computers of any size before you come across the terms "interpreter" and "compiler". Often newcomers find them quite puzzling, yet they tend to be used with gay abandon (often interchangeably and wrongly) to describe all sorts of software utility programs. So this month I'm going to try and clarify these terms for you.

As you may have already gathered, interpreters and compilers are basically **programs** designed to **translate** from one type of computer programming language into another. Generally, both terms are used to describe programs which are designed to translate from a "high level" or "problem-orientated" language like BASIC or FORTRAN, etc, into the computer's own "machine language" or binary code — the form which all programs must ultimately take before they can be "run".

It may seem a strange idea that we would write our programs for the computer in one "language", then use another program to get the computer itself to translate our new programs into the actual "language" which they must be in before it can "understand" and run them. Sounds a roundabout way of doing things, doesn't it? Yet it makes a lot of sense.

The main reason for doing it is that the computer's own machine language is basically just a string of binary numbers — each number a "code" signifying a particular type of elementary operation. This "language" may be fine for computers, but for we humans it is a very tedious and intricate form in which to try and write programs.

It is far easier and faster for us to write our programs in a more abstract and human-orientated form, and then get the computer itself to translate them into its own precise and fine-detail strings of binary codes. Unlike a human translator it doesn't have to "understand" what it is translating; it just follows rigid and clearly-defined rules of translation previously set down (by a human programmer). And being a computer, it can do the job of translation both faster and

more accurately than could we humans — once a human has written the translation program to tell it how to do so, of course!

Well, so much for translation programs in general. Now for the differences between interpreters and compilers. Each type of translation program works in a rather different way.

Basically, a **compiler** is designed to be loaded into the computer and run by itself. Under its control the computer accepts your high-level program as "input data", works out the equivalent string of machine-language code, and delivers this as the "object code" version of your program. This may then be fed into the computer at any time, again by itself, to run like any other machine language program.

With a compiler, then, the actual translation of your program into object code is performed by the computer as a distinct operation, quite separate from its being executed. But with an interpreter, the two functions are "interleaved" and tend to be fused into a single complex task.

An **interpreter** is designed to be present in the computer's memory along with your high-level program, and to do its translation of the program "on the run". Instead of translating the program as a whole into machine code, it translates it a line at a time, and executes the equivalent machine code for each line before attempting to translate the next. So with an interpreter a full machine-code translation of your complete program never exists at any single time; its parts are produced and run in rapid succession.

What are the relative merits of the two? Well, because a compiler produces a full machine-code translation of your program, which subsequently runs by itself, your program can run at the full operating speed of the computer. The same high-level program can never run as fast with an interpreter, as the interpreter has to translate it afresh each time the program is "run". The computer obviously can't both translate and execute

it in the same time as it would normally take to run it! So compilers have a speed advantage.

A compiler also allows you to run longer high-level programs, because your translated program ultimately runs in the computer by itself. In contrast, with an interpreter your program has to have the interpreter alongside it in memory, to translate it and "hold its hand" during execution. So for a given amount of computer memory, the space available for your program has to be "what's left" after that required by the interpreter.

Does a compiler have any disadvantage? Yes, and quite a serious one. Because a compiler translates your program quite separately from its execution, it doesn't allow you to work in "real time". You have to write the program first in the high-level language (generally using a text editor program), then use the compiler to translate it, and then load in the resulting object code version to see how — or even if — it runs.

If there are problems, either in the logic or the syntax (even a misspelt command word, or a comma in the wrong place), you have to go back to your original program, change it, translate it again using the compiler, then feed the new revised object code it again for another try. Even with a modest-sized program this can be a tedious and irritating business; with a big and complex program it can be a nightmare!

Here's where an interpreter pulls ahead, despite its relative limitations in terms of absolute speed and program size, because it allows you to work in "real time". As soon as you have written your program using its inbuilt text editor, you can tell the interpreter to "run" it. If there are any problems, these will become apparent in fairly short order. You can then "break" in, modify the program in memory, and "run" it again, solving the bugs as you go along.

In practice, this proves a tremendous advantage in terms of programming convenience and speed. This is why just about all of the current generation of microcomputers are provided with a BASIC interpreter, which is generally resident in ROM so that it is "ready to go" as soon as you turn the machine on.


What about the compiler "hare" — does it always lose out against the friendly interpreter "tortoise"? No, not really;

(Continued on page 142)

# Microcomputer News & Products



## DREAM 6800 EXPANSION KITS FROM JR

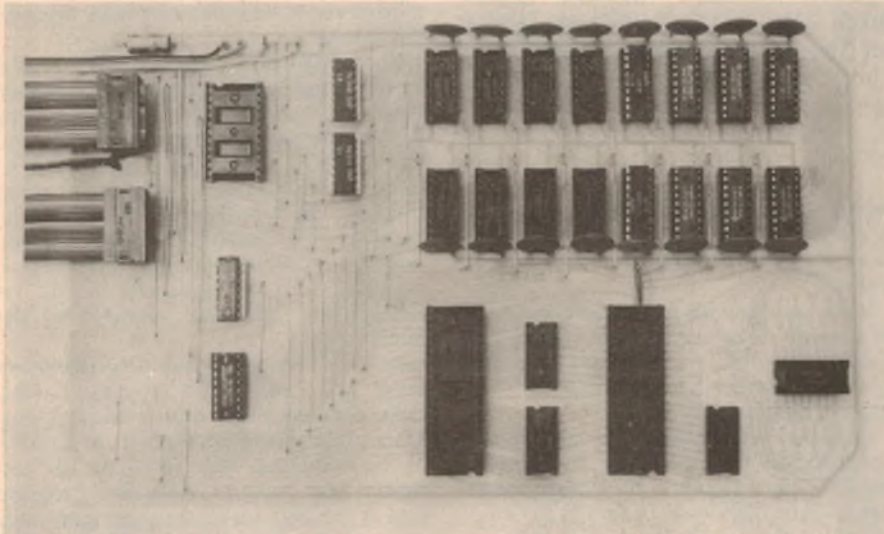

Designed for the DREAM 6800 and 6802 a 4K Expansion Kit, consisting of a DREAM-sized fibreglass printed circuit board containing a 4k RAM (the 1K on the DREAM board is transferred to this board making 5K in total) with sockets, address buffers, select logic, connectors and instructions is now available for \$99 (or \$59 without RAM).

A more sophisticated kit has — in addition to the features of the 4K kit — provision for 8K RAM, two PIAs, one EPROM and drive transistors for off-card optocouplers.

The PC board is intended to be mounted above or below the DREAM board. Connection is made via a short length of ribbon cable with plugs. If the

unit is mounted in a box, ventilation must be provided. The amount of current drawn depends on which brand of RAM is used, and how many IC's are installed. Worst case current drain is just under 2 amps.

Enquiries should be directed to J. R. Components Pty Ltd, PO Box 128, Eastwood, NSW, 2122.

## PROGRAMMED EPROM FOR DREAM 6800

Dreamsoft has introduced a software package on EPROM which is intended for use with the J. R. Components DREAM 6800 Expansion Kit. It provides 2K of programs which can generate text displays with variable delays, reverse video and scrolling. Waits for external key inputs may also be programmed. All these can be strung together to form repeating messages, advertising displays, titles or education aids.

Standard ASCII code is used to display the full 64 character subset on a 5 x 3 dot matrix. Inexpensive hard copy is available as a bonus for users with Baudot teletypes, whilst improved tape load, dump and verify routines are included which avoid the need to insert the start and finish addresses with the monitor program.

Details of user-callable subroutines are provided. The EPROM is supplied complete with commented listing and instructions for installation on the J. R. printed circuit board. Dreamsoft price this EPROM at \$30, with further information being available from Dreamsoft, PO Box 139, Mitcham, VIC, 3132.

## ATTENTION

QUEENSLAND APPLE & NORTHSTAR  
OWNERS AND PURCHASERS

*Computer Country Pty. Ltd.*

338 Queen St. Melbourne  
(03) 329 7533

*is proud to announce the grand opening of its affiliate*

### COMPUTER CITY

600 OLD CLEVELAND ROAD  
CAMP HILL (BRISBANE)  
(07) 398 6433

**CALL NOW FOR GREAT SPECIAL DEALS AT BOTH STORES**


## “WHISPERDISC” CHARACTER PRINTER



A medium speed serial printer that prints “letter quality” via a daisy wheel

Micronews continued p125 
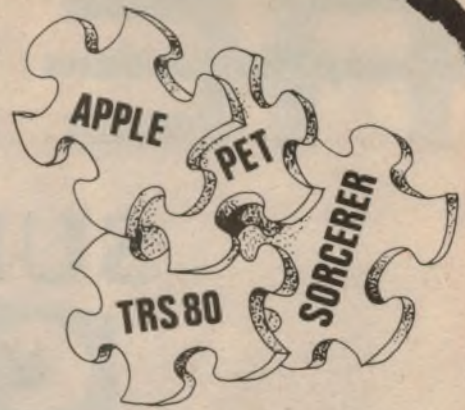
# Puzzled? Which computer to buy? The solution . . .



At Applied Technology we do things a little differently. Our market research has shown that a lot of people buy their first computer mainly to learn the basic concepts involved. Once they have mastered the basic principles only then can they effectively apply the computer to carry out their specific requirements.

We believe that a first computer must start small and be expandable and at the same time be supported with enough documentation and examples so that a user can master both hardware and software concepts at his own pace. Unless you can get "hands on" experience and actually make a computer actually do something like switch on a relay or play a musical tune you will find mastering the microcomputer a difficult, time consuming battle.

With this in mind we have designed a series of computer boards each with a specific function and yet fully compatible with each other. You can have fun and build each from kits (or buy them assembled and tested) and when a board is ready to go, plug it into the S100 BUSS (the hobby standard!) and you are ready to explore the fascinating world of the microcomputer. Some users of our Z80 system have already developed sufficient expertise to set up their own business writing software and designing industrial control systems. You could easily do the same!

## \$399 INSTRUCTOR 80

An ideal starting point and a powerful self-contained computer on two S100 cards. The kit includes DGZ80 CPU (with on-board ROM and RAM and adequate I/O for most applications), the DG640 VDU (64 character/line display

with upper and lower case and graphics facility), a full feature RCA keyboard, 3 slot motherboard with edge connectors. The kit comes with complete manuals, a step by step programming course and sample programs to run. All you need to do is connect a simple power supply and a monitor/modified TV to complete the unit. Our exclusive warranty service and technical backup are readily available.

## ADD ON S100 CARDS AND PERIPHERAL EQUIPMENT

The Instructor 80 can be readily expanded using cards from our wide range of S100 boards. You can, for example add 16K or more of reliable static memory using our AT16K RAM boards or add fine detail graphics/programmed screen characters and connect joy stick controls with the TCT PCG (see ET1 July 1980). A full set of hardware is available to house your S100 computer system and if required we have just developed a professional quality 12" monitor with an easy-on-the-eye green phosphor and resolution to cater for up to 132 characters/line! A full range of peripheral equipment including printers and high capacity floppy discs is available as your needs arise.

## SOFTWARE SUPPORT

The Z80 is probably the most popular 8 Bit microprocessor in the world and has an abundant software base including business packages, word processing and languages such as CP/M, PASCAL, FORTRAN, FORTH. We have developed cassette based programs including Microworld Basic, Microworld Editor/Assembler, Utility Package and many exciting and challenging games. Courses

in microprocessor applications and programming are run regularly. Please enquire for more details.

## PRICE LIST

DGZ80 S100 CPU Kit	\$199.00
Assembled	\$249.00.
DG640 S100 VDU Kit	\$149.00.
Assembled	\$159.00
DGOS Operating System in 5Volt EPROM	\$40.00
AT16K Memory Module	
Assembled	\$199.00
TCT 16K Static RAM Kit	\$209.00
Assembled	\$229.00
TCT PCG Kit	\$140.00
USCI Cassette Interface	
Assembled	\$25.50
JC100 9 Slot Motherboard	\$49.50
JC200 Card Cage	\$49.50.
JC300 Power Supply	\$69.50
JC400 Desk Mount Cabinet	\$69.50
Clare C70 Keyboard	\$165.00
NT300 Hires Monitor	\$230.00
<b>Software now available on cassette tape (DGOS format)</b>	
Microworld Z80 Basic 2.1T Package	\$25.00
Microworld Editor/Assembler Package	\$35.00
Utility Tape 1	\$14.75
Battle Games (Target Trek)	\$14.75
Competitive Games	\$14.75
Learning and Challenging Games	\$14.75
Chess (suitable for PCG only)	\$5.00
Experimenters Pack 1 (Stac Timer)	\$17.50
Experimenters Pack 2 (Music Generation)	\$17.50
Experimenters Pack 3 (I/O Controller)	\$17.50



**APPLIED  
TECHNOLOGY  
PTY. LTD.**

### MAIL ORDERS TO:

PO Box 311, Hornsby 2077.

Please add \$2.00 per order towards cost of post and packing.


### AND NOW AT GOSFORD -

1 Debenham Road, West Gosford (behind the Pizza Hut) 043.24 2711
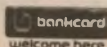
### OFFICE/SHOWROOM

1a Pattison Avenue, Waitara 2077.

Hours: 9-5 Monday to Saturday  
Telephone: 487 2711



Note: All prices include sales tax and are subject to change without notice.

AT007

# **AE ADAPTIVE** **ELECTRONICS P/L**

## **SUPPLIERS of** **Cromemco** **TO AUSTRALIA**

Our product range includes:

- **Cromemco computers and peripherals**
- **Printers & V.D.U.'s**
- **Highly supported range of business software**
- **Tandon mini disk drives**
- **Persci dual 8" drives**
- **I.M.I. Winchester 11 & 22 M. Byte drives**
- **Adaptabox instrument cases**
- **Word processing software**

## **WE ARE MOVING**

Our new address will be.  
418 St. Kilda Road  
**MELBOURNE**

Telephone (03) 267 6800      Telex AA32565

## Microcomputer News & Products

has just been released by Olympia. Called the "WHISPERDISC", it will accept forms up to 381mm wide and prints at 20 characters per second.

Eight different typefaces are available, and it can make up to four copies.

In announcing the release, Mr Mike Connell, the Olympia national sales manager, states that the first contract for delivery of the new printer has been signed with Rudi Hoess of Electronic Concepts Pty Ltd, the Australian distributor for Apple computers.

The ES100 SP "Whisperdisc" can be used by most users of mini or microcomputers where they can access a standard RS232 interface. Priced at \$2550 it is available from Olympia International, 59-61 Dickson Ave, Artarmon, NSW, 2064.

### MENSA HAVE FINDEX

Mensa Computers Pty Ltd of 454 St Kilda Rd, Melbourne has just released the Findex portable business microcomputer, measuring 444 x 546 x 210mm with a mass of only 14kg.


Features of the Findex include an expanded keyboard with 72 keys, a lightweight gas plasma flat display panel, built-in mini-floppy diskette drive, 128k bytes of bubble memory (expandable to 2 megabytes) and built-in printer using forms 228mm wide.

The CPU utilises the Zilog Z-80 microprocessor functioning on a clock frequency of 2.5MHz, with the option of specifying a frequency of 4MHz. Serial, parallel and S-100 Buss interface is stan-

dard. Audio-cassette recorder jacks and built-in modem acoustic coupler are optional.

Peripherals include standard floppy and large hard disk drives, printers and other computers. Communication may be asynchronous, synchronous or bisynchronous.

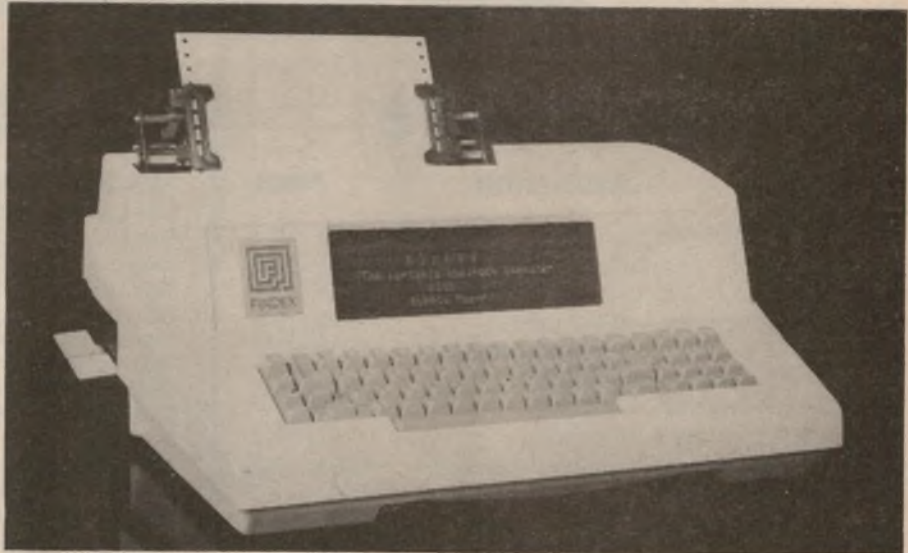Mensa Computers can also supply larger systems such as the Industrial Micro Systems Series 8000 and the Opal range of equipment.



More Micronews p127 →

## K&L Computing Systems introduces the feature packed Archives Business Computer.

This highly versatile desk top unit provides high technology at a competitive price. Suitable for handling all the day by day business requirements, its features include:

- An extremely fast Z80 4MHZ Processor
- CP/M Operating System
- S100 Expansion Bus
- 64K RAM Standard
- 744K Bytes Disk Storage (Expandable)
- 25 Line x 80 col. Display

Available with word processor and complete accounting package, or software can be written to customer's specifications.

Also, see K&L's range of Apple II Plus Computers, floppy disk drives, video monitors, interfaces and expansion options.

- Language card with compilers for Pascal and Fortran
- Z80 Softcard with micro-soft basic compiler and CP/M
- DOS 3.3 upgrade kits (143K Bytes per disk)
- Paper Tiger printer with graphics

**Qume Sprint 5 and Ricoh RP 1600 Printer**, top quality Daisy wheel printers ideal for word processing applications, at a highly competitive price.

Office Hours:  
Weekdays 9 to 5  
or by  
appointment.




**COMPUTING SYSTEMS**

385-387 BRIDGE ROAD,

RICHMOND, 3121. TEL: (VIC.) 429 2122

KLR 003

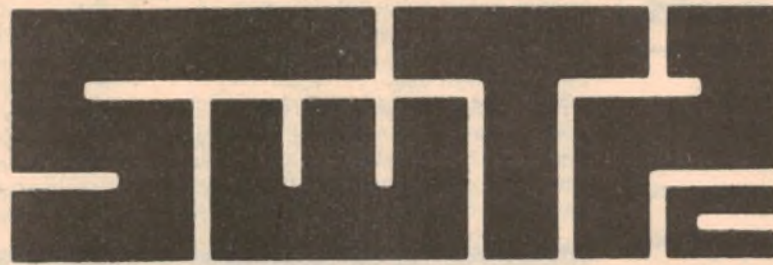

## HARDWARE

KIT	DESCRIPTION	PRICE
S/O9	6809 Computer w/128K Memory	\$3350.00
/O9	6809 Computer w/56K Memory	\$1660.00
69/A	6809 Computer w/8K Memory	\$760.00
PP132	characters 6540 printer	\$2350.00
S/OO	S/O9 W/O Proces/Mem card	\$560.00
DT-80	Terminal w/monitor	P.O.A.
8209	Terminal w/monitor	\$1050.00
8212	Terminal w/monitor	\$1175.80
DMF2	Disk System w/2.5m Capacity	\$2650.00
CDS-1	Winchester Hard Disk System	\$4835.00
SP-3	Daisy Wheel Printer (QUME)	\$3295.00
SP-5	Daisy Wheel Printer (QUME)	\$3515.00
PR-40	Alphanumeric Printer	\$275.00
MP-O9	6809 Processor Board Kit	\$192.50
MP-O9A	6809 Proces/Board (Assem)	\$225.00
D5-2	double side/double density 720KB	\$1395.00
3809	128K Memory Expansion for S/O9	\$2305.00
MP-32	32K Memory (assembled)	\$715.00
MP-16	16K Memory (assembled)	\$440.00
MP-8A	8K Memory (assembled)	\$258.50
MP-8M	8K Memory kit	\$220.00
MP-LA	Parallel Interface	\$45.00
MP-L2	Dual Parallel Interface	\$110.00
MP-N	Calculator Interface	\$65.00
MP-P	Power Supply	\$66.00
MP-QP	Circuit Board for SP-3 (assembled)	\$78.00
MP-R	Eprom Programmer	\$65.00
MP-S	Serial Interface	\$45.00
MP-SA	Serial Interface (Assembled)	\$66.00
MP-S2	Dual Serial Interface	\$110.00
MP-SX	Serial interface Expansion	\$27.50
MP-T	Interrupt Timer	\$52.25
MP-WP	IBM Selectric Interface	\$66.00
S-32	Universal Static Memory Card	\$115.00
MP-O9b	Processor Circuit Board	\$27.50
MP-8Mb	8K Memory Circuit Board	\$27.50
DMF2b	Controller Board for DMF2	\$434.50
DT52	double track density 1-9MB	\$1850.00

PRICES SUBJECT TO ALTERATION  
 EXPORT PRICES UPON APPLICATION  
 ALL HARDWARE PRICES PLUS 15% ST WHERE APPLICABLE

## SOFTWARE

ASMO9	Optimizing Assembler (5" or 8")	\$110.00
Flex O9	ver. 2.6:5 w/manual	\$38.50
Flex O9	ver. 2.6:5 w/o manual	\$11.00
Inventory	Program	\$110.00
Mail List	Program	\$110.00
Word processing	Editor & Text processor	\$165.00
Word Processing	Editor	\$110.00
Text processor		\$66.00
SP-O9-2	Text Editing System	\$38.50
SP-O9-3	Mnemonic Assembler	\$44.00
SP-O9-4	Basic	\$71.50
SP-O9-5	Debug Package	\$82.50
SP-O9-6	Extended Basic	\$110.00
SP-O9-7	Standard Precompiler	\$55.00
SP-O9-8	Extended Precompiler	\$55.00
UniFLEX	Multi-tasking BASIC	\$150.00
SP-O9-10	Sort/merge	\$82.50
SP-O9-11		\$66.00
* UniFLEX:- Multi-user and Multi-tasking		\$495.00

### SWTPC BUSINESS SOFTWARE: ACCOUNTS RECEIVABLE, GENERAL LEDGER, INVENTORY, PAYROLL, MAIL LIST AND MANY OTHERS.

#### FLEX for the EXORciser™

Runs on a Motorola EXORciser with EXORdisk™ II or III. Requires no hardware modifications with the possible exception of memory re-addressing. Uses the same boot as MDOS™.

#### FLEX Support Software

Extended BASIC  
 Standard BASIC  
 6809 Diagnostics Package  
 Text Processing System  
 Sort/Merge  
 68000 Cross Assembler  
 6809 Cross Assembler  
 6809 FLEX Utilities  
 6800 FLEX Utilities  
 6809 Debug Package  
 6800 Debug Package  
 FLEX for SWTPc  
 UniFLEX:- Multi-user and Multi-tasking




## SOUTH WEST TECHNICAL PRODUCT CORPORATION

(COVERING AUSTRALASIA)

7a BURTON STREET, DARLINGHURST, N.S.W. 2010.

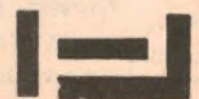P.O. BOX 380 DARLINGHURST N.S.W. 2010. PHONE (02) 357 5111



## Microcomputer News & Products

### NEW TELEPRINTER PRINTS RED AND BLACK



A new matrix print head for printing true lower case descenders and the capability of red and black printing are options now offered with the Tally T-1612 1200 Baud Printer terminal. Tally reports the new nine needle printhead design allows teleprinter users to have true APL capability. Underlining and lower case descenders are printed without sacrificing printer speed. The T-1612 prints bi-directionally at 160 characters per second and slews to the next print position at 48ips.

The black and red ribbon option allows the user to employ the same shift principle as a typewriter to achieve two colour printing. The option is useful in accounting applications for signalling debits or to highlight numbers, or for interactive communications whereby answers and requests can be colour differentiated. Also, the Tally T-1612 terminal has double wide character printing and with the added function of red printing, the user can highlight portions of text.

Tally reports that the addition of these two options to an already highly versatile machine makes the T-1612 the most flexible teleprinter available. The T-1612 offered with 42 standard programmable functions, lists among its many options a Short Form Quick Tear device for saving forms costs and an Auto Front Feed device for handling cut forms.

For further information contact the Warburton Franki office in the capital city of your State.

### LOW-COST ROMLESS Z8 MICROCOMPUTER

A new member of Zilog's Z8 single-chip family that omits mask-programmed read-only program memory (ROM) and instead offers the user alternative combinations of input/output lines and bus compatibilities, has been announced by Zilog.

The ROMless Z8681, compatible with the Z8000 microprocessor's peripheral circuits offers an alternative to multi-chip solutions in such high-performance applications as smart terminals, printers and controller with specialized I/O requirements.

"Although these applications can be addressed by the mask-programmed Z8 with this internal ROM," said a Zilog spokesman, "the new ROMless version has a lower price, inherently greater flexibility, and no minimum quantity requirement. These benefits are expected to broaden the Z8's applicability to a wide

Micronews continued p128



**\$ THE LOGIC**

SHOP PTY.LTD.

### 5% BELOW LIST ON ALL STOCK

#### COMPUCOLOR II

Ex  
Stock



features:

Up to 32K User RAM  
Eight-colour display  
32 lines of 64 char.  
5" Mini Disk Drive  
40 Tracks, 48 TPI

#### TELEVIDEO TVI-912

Ex  
Stock



features:

24 lines  
80 char. per line  
Transmission rates 75-19,200 Bd.  
96 char. ASCII Upper & Lower Case  
12" Monitor

#### MICROLINE 80 PRINTER

Ex  
Stock



features:

80 char. per sec.  
80 and 132 char. per line  
9x7 DOT MATRIX character or  
graphics printing.

#### PLUG COMPATIBLE TO TRS-80

(TRS-80 is a regd. trade name of  
The Tandy Corp.).

**SPECIAL**  
5 1/4 DISKETTS  
\$3.95 EACH (INC. TAX)

**\$ THE LOGIC** SHOP PTY.LTD.

212 HIGH ST. PRAHRAN,  
VIC 3181. TEL (03) 51 1950  
91 REGENT ST. CHIPPENDALE,  
NSW 2008. TEL (02) 699 4919  
SHOP 16 CIVIC ARCADE,  
ADELAIDE ST. BRISBANE QLD  
TEL (07) 312330



## Microcomputer News & Products

range of designs in which it can be used to reduce chip count and power requirements."

A complete microcomputer, the Z8681 contains 124 bytes of on-chip RAM, up to 24 I/O lines, two eight-bit counter/timers for real-time control applications, a UART for serial communications, six levels of interrupts, and an on-chip oscillator. An expandable bus interfaces up to 62K bytes each of external program memory and external data memory.

Under program control, the Z8681 can be tailored to the specific needs of the user. It can be configured as a traditional microprocessor that manages up to 124K bytes of external memory, or as a parallel-processing element in a system with other processors and peripheral controllers linked by Zilog's Z-Bus Component Interconnect. In all configurations, a large number of pins remain available for I/O purposes.

Housed in a 40-pin dual-in-line package, the Z8681 requires a typical current of 150 milliamps from a +5 volt power supply.

Enquiries should be directed to Zap Systems Pty Ltd, PO Box 22, St Leonards, NSW, 2065.

# TANDY

## COMPATIBLE

Printers, Expansion Units,  
Disc Drive, Software.


**DIRECT FROM  
THE U.S.**

Write for our Catalogue

**COMPUTER IMPORTS  
PTY. LTD.**

**P.O. BOX 7, PORT ADELAIDE,  
S.A., 5015  
PHONE (08) 26 88065**
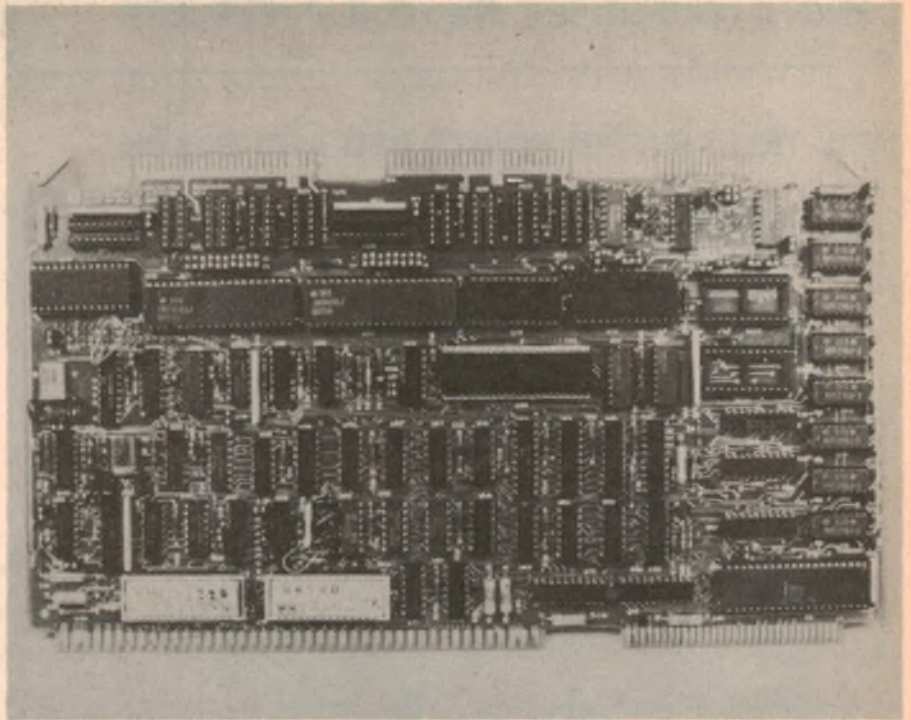
## NATIONAL RELEASE SINGLE-BOARD COMPUTER



The BLC-80/316, a single board computer featuring dual-port RAM, is now available from National Semiconductor Corporation. Ideal for any system involving multiprocessing, dual-port RAM allows access of the onboard RAM by not only the on-board CPU, but by any board that can take control of the bus. In board-intensive systems, dual-port RAM potentially reduces system cost by eliminating the need for a RAM expansion board, as well as saving time by reducing the number of bus accesses.

ROM/RAM "shadowing" capability under software control is also provided on the BLC-80/316, allowing ROM to "disappear" and be replaced by system RAM, creating the environment that CP/M was designed to run under. The BLC-80/316 uses a Z-80A CPU, which features an exceptionally fast, 3.69 MHz execution speed.

Supported by the BLC-8930 firmware monitor, the BLC-80/316 also features 9 levels of vectored interrupts, 48 programmable I/O lines, 3 programmable counter/timers, as well as full compatibility with the industry standard BLC/SBC Series/80 family of microcomputer products. Onboard arbitration logic is also included, providing transparent bus arbitration for multiple CPUs.

Enquiries to NS Electronics, PO Box 89, Bayswater, Vic 3153. Editor's Note: CP/M is a registered trademark of Digital Research.

**MICRONEWS  
CONTINUED** →

## System-80 and TRS-80 Users

**10 × Quality Verbatim Diskettes  
in Plastic Filing Box . . . . \$49.95**

Gold edge connectors × 3 . . . . . \$34.00  
Suppressor Plugs, ea . . . . . \$7.00  
Modem (ex PMG) . . . . . \$150 plus freight

**SPECIAL** the famous NEWDOS+ with 3.0 Super Zap  
and Book TRS-80 Disk &  
Other Mysteries . . . . . \$106

Prices include S/T where applicable

**Complete Business System (Tandy Basic)**  
Osborne/McGraw Hill

System Text books: Accts Pay/Rec . . . . .	\$ 20
General Ledger . . . . .	20
Programs: Creditors . . . . .	90
Debtors . . . . .	90
General Ledger . . . . .	90
+ Cash Book . . . . .	50
Invoicing . . . . .	90

All linked together: \$400 (save \$50)  
(ie, enter data once/automatic posting)

Send for free list of over 100 Programmes




**PITT ST MICROCOMPUTERS**

BOX A344 SYDNEY SOUTH, PITT ST SYDNEY 2000  
Office Hrs: 10am-6pm, Mon-Fri; Ph: (02) 569 8228



# E-X-P-A-N-D YOUR SYSTEM 80

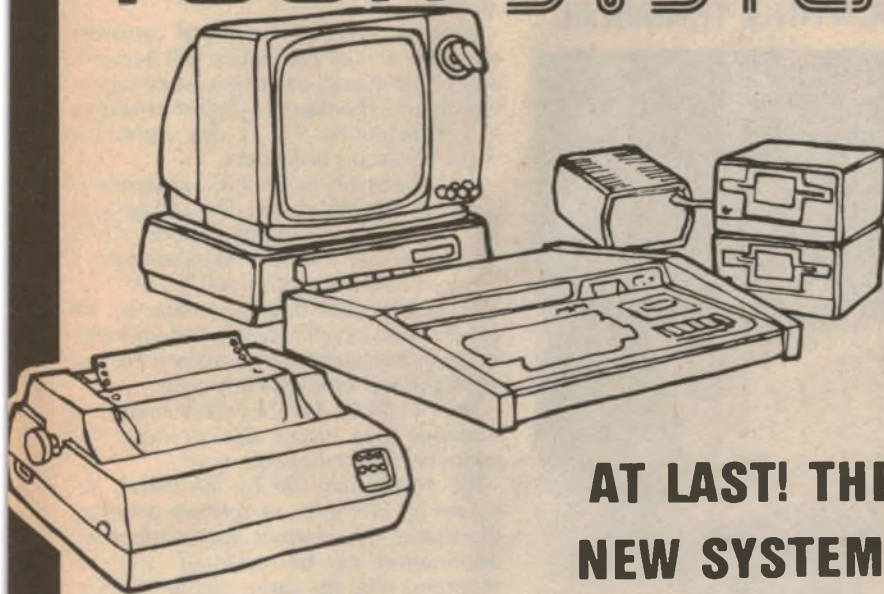

## AT LAST! THE NEW SYSTEM 80

Here's what  
it can do for your System 80:

## S-100 EXPANSION INTERFACE

- Give you a standard Centronics parallel printer port. (Suits most printers including our Dot Matrix (X-3255) and Daisy Wheel (X-3265) printers.
- Give you an RS-232C port with full 'handshaking' logic for connection to modems, etc.
- Give you the option of fitting extra memory: fit a RAM CARD with another 16K or 32K (available separately) — plus you can still fit another S-100 add-on board.
- Give you a floppy disk controller (up to four drives) with external data separator for improved reliability
- Gives you the ability to use a cheap teleprinter instead of a parallel printer. Save a bundle!
- Gives you S-100 compatibility: so you can use many of the peripherals from hundreds of manufacturers: why be tied to one source of supply?

**AND IT'S \$\$\$\$ CHEAPER THAN TANDY!**

Apart from the massive savings on the computer itself, our expansion unit is over \$119 less than Tandy's (theirs is \$618.95 including RS-232C interface). And it offers you much more!

Sent anywhere in Australia for \$6  
Below cost!

Cat X-4010

**ONLY  
\$499<sup>00</sup>**

Terms available to  
approved applicants

### 16K RAM CARDS TO SUIT S-100 INTERFACE

Comes with 16K fitted; with room for another 16K. You can have a 48K computer!  
And the savings can be massive!

Card (including 16K RAM) (Tandy charge \$220.00!)	<b>X-4016 \$199.00</b>
Second 16K RAM (Tandy charge \$220.00!)	<b>X-1186 \$59.95</b>

## IF ALL YOU WANT IS A PRINTER INTERFACE . . .

We've got this economical parallel interface allowing you to run any Centronics-type printer direct from the System-80 — no expansion interface needed. And again, the price is a big saving over Tandy's!



Printer Interface:  
Cat X-4013

**\$49<sup>50</sup>**



Connecting Cable:  
(suits Printer Interface  
or S-100 Interface)

**\$39<sup>50</sup>**

Cat X-4014

**DICK SMITH  
Electronics**



**SEE OUR OTHER ADS FOR  
FULL ADDRESS DETAILS**

## Microcomputer News & Products

### HP INTRODUCES POWERFUL PRINTING TERMINAL



The new terminal also appears to be the first to offer eight user-definable softkeys. The softkeys, and a programmable RETURN key, make it possible to tailor the terminal to individual applications.

soft carrying case, the HP 2675A can be transported easily from one location to another.

The integrated thermal printer operates at 120 characters per second, and prints quietly to fit into an office environment. The thermal printer produces a high-resolution 7 x 11 dot matrix for sharp character definition.

With the ability to print 132 columns of data on 21.6cm paper, the printer can deliver full-size computer reports. At 40 characters per line, the expanded print mode is useful for titles and labels.

A standard line-drawing character set can be used to print forms. And underlined and framed characters make it easy to highlight and emphasize reports.

The HP 2675A comes with built-in dual cartridge tape drives able to store 320 kilobytes per removable tape.

File access may be by file name, absolute file number, or relative position. Updatable tape format allows recorded information to be updated and re-recorded over the same section of tape.

Search/rewind is done at 228cm per second, while read/write is 56cm per second.

For further information contact Hewlett-Packard Pty Ltd, 31-41 Joseph St, VIC, 3130.

A portable terminal featuring high-speed thermal printing, national keyboards, and integrated mass storage has been introduced by Hewlett-Packard.

The new HP 2675A is the first terminal in its class to offer selectable columns per line and enhanced characters on a quiet thermal printer.

### STOCK CONTROL AND PRICING SYSTEM

Dick Smith has released a Stock Control and Pricing system program ("SCAP")

Micronews continued p133

# SORCERER?

SOFTWARE?  
DISKS?  
SOFTWARE?  
CP/M?  
SOFTWARE?  
SPELLBINDER?  
SOFTWARE?  
PRINTERS?  
SOFTWARE?  
WORD  
PROCESSORS?  
SOFTWARE?  
PERIPHERALS?  
TAPE?  
S-100?  
SOFTWARE!  
BASIC  
UPGRADES!

*Software Source*

PO BOX 364  
EDGECLIFF 2027  
(02) 33 4536

Phone or write for  
**FREE CATALOGUE**

# Synertek

A Honeywell Company

#### TICK ITEMS OF INTEREST

- Static RAMS
- EPROMS
- Custom ROMS
- SYM-1 Single Board Computer
- Keyboard terminals, KTM-2 & KTM-2/80
- 8K BAS-1 & 8K RAE-1 Resident Assembler Editor for SYM-1 ROM Resident
- $\mu$ P Computer Module, Super-Jolt
- 6500 Micro's & peripheral IC's
- Low cost/low quantity custom LSI's
- Industrial systems engineering

Please send information on items ticked. My application is:

- HOBBY
- INDUSTRIAL
- PROFESSIONAL

Name: .....

Company: .....

Address: .....

Post Code ..... Phone: .....



### ROYEL MICRO SYSTEMS PTY. LTD.

VIC: 27 Normanby Rd., Notting Hill, 3149. Phone 543 5122  
NSW: 15/59 Moxon Rd., Punchbowl, 2196. Phone 709 5293

SRC100A



# MENSA COMPUTERS

Suite 3, 454 St. Kilda Road, Melbourne, 3004. Telephone: (03) 26-5683, 26-6150.

## FINDEX, The Real Computer



### THE WORLD'S FIRST PORTABLE MICROCOMPUTER Battery or mains operated

RAM 48K to 2 megabytes, bubble memory to 2MB, gas plasma display, optional audio, printer, mass storage mini floppys to 800K bytes, hard disk to 195 megabytes, acoustic coupler, S-100 bus, battery optional, CPU with real time clock. For dynamic businessmen on the move. Ideal for real estate agents, insurance brokers and accountants.



Powerful, multi-purpose microcomputer systems.

## BUSINESS SYSTEMS

Priced competitively from as low as \$45.00 p.w. lease cost including sales tax and software.

### TYPICAL APPLICATIONS

Debtors ledger and statements, creditors ledger and remittances, general ledger and trial balance, order entry/invoicing, sales analysis, payroll/wages, enquiry, word processing, mailing, record keeping, ledger card, doctors office, real estate, agency accounting, hotel/motel accounting, branch office accounting, Facilities management consulting, Software and computer sales, Computer data preparation.

**INTRODUCING**

## MENSA G.F. 1000

### BASIC SPECIFICATIONS

CPU 8080 and Z80 operating at 4MHZ. 64K bytes Dynamic RAM expandable to 2MB with Bank select allowing multi user. Texas Instruments 810 Printer. Over 2MB total 4 drives on-line storage bytes of unformatted data on two double density drives. Optional external hard disk storage can be connected using the optional S-100 Bus. Floppy Disk.

### WINCHESTER DISK


26MB of Winchester Disk complete with controller and easy backup. Disk has special capacity to only back up files accessed during the last period. Disk operating system CP/M.

### OPTIONAL SOFTWARE

FORTRAN, COBOL, BASIC.

Application packages. Extensive software development tools are available from leading software vendors, including software for the following applications: payroll, accounts receivable, accounts payable, inventory control, general ledger and word processing. All modules mounted to base. CRT in a rigid aluminium frame. Disk Drive assemblies are mounted into special brackets for ease of servicing.

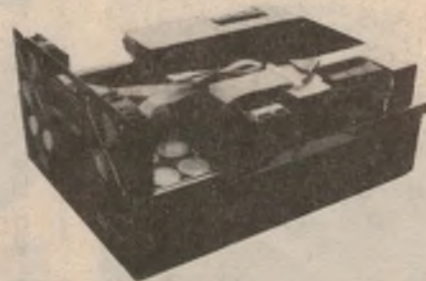Mensa computers provide a service network throughout Australia at major service centre locations to minimise response time to service calls. To ensure that equipment will operate at peak performance, engineers and technicians are trained to ensure the highest possible standard of service.





MAIL ORDER  
TO  
AUSTRALIA

32 Lloyd Avenue, Sydney 2000,  
(02) 908 2235; Telex AA20149

Our company's aim is to supply throughout Australia personal computers at Australia's lowest prices, these prices being possible by the traditional savings of mail order marketing.

Our office is open 9 to 5 weekdays and also 7 to 10pm Monday through Thursday so that our Australia-wide clients can use STD when it's cheap (after 9pm save 60% on your call).

**Service** — We provide full service, equal to any in the business, on all our lines. We support fully the manufacturer's warranty and provide complete after warranty service (we give this undertaking in writing on our invoice).

**Delivery** (door to door)

- Customer collection (or arrangement) from our premises.
- Arranged by us, the charges being:
  - one Apple —
 

— NSW	\$24	— Perth	\$33
— Melb, Bris, Adel	\$22	— WA	\$42
— Vic, Qld, SA	\$31	— Tas	\$34
  - Items marked so † — \$11 anywhere in Australia.
- Smaller items by certified post, the charges being less than \$11.

**ALL CHARGES INCLUDE INSURANCE TO THEIR FULL VALUE**

**Payments** — (1) Personal cheque — allow time to clear.  
(2) Bank cheque or Cash.  
(3) COD but add 15% to the bill.

**A receipt will be immediately issued for all moneys received.**

If you desire the protection of a written contract between us we can issue you with a pro forma invoice.

## APPLE DISCOUNTED

You've seen our opening prices, now consider our increased range

— and still at good price reductions.

	Tax Free	Tax Paid	Save* (approx)
16k Apple II plus	\$1,220	\$1,403	\$192
16k Apple II plus +16k	1,280	1,472	276
16k Apple II plus +32k	1,340	1,541	351
† Disc II with controller (3.3)	630	725	35
† Disc II only	476	547	78
† Pascal language system	433	498	72
High speed serial comm card	175	201	29
Parallel comm card	193	222	28
PAL colour card	158	181	21
Graphics Tablet	744	856	122
Apple Controller	700	700	100
Apple Cashier	306	306	44
Visicalc	175	175	25
CCS Database Management	132	132	18
"General" 12" B&W monitor	127	146	21
"Dick Smith" 12" B&W monitor	114	130	20
"Sanyo" 12" green screen monitor	297	342	49
Z80 Microsoft card	333	383	53

(we can supply all Microsoft's products)

\* Based on the tax paid Sydney Computerland price list effective 16/7/1980.

**Printers:** We carry the Paper Tiger, Dick Smith's daisy wheel, Sanders 12/7 and most likely can get any other you want — expect a discount of up to 10%.

**Diskettes:** Verbatim, BASF, Memorex 5 1/4" soft sector, \$40 per box of 10 including postage

**Prices subject to change and exclude delivery charges.**

**Pledge.** Any orders that we cannot supply from stock we will specify a dispatch date on your receipt. Failure to dispatch by this date will require us to immediately issue a full refund unless instructed otherwise by the customer.



# Cromemco


Tomorrow's computers now

Cromemco offers you a wide choice in high-capability computers with outstanding features such as high speed, many card slots to allow for broad system expansion, wide card support, fast memory and our much-admired Cromemco software.


Further, Cromemco computers are of a rugged, all-metal construction that immediately tells you these computers are built to be dependable and long-lived.
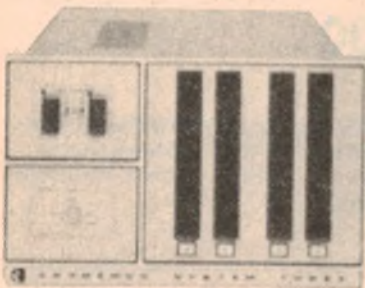
### OBSOLESCENCE INSURANCE

The nature of their construction also promises versatility and long life. Built with easily-accessible card slots, these computers can be configured to meet the needs of an almost endless variety of applications.



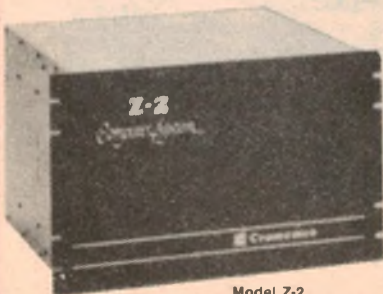**SYSTEM THREE**  
Two to four disks Up to 512  
Kilobytes of RAM/ROM Up to 4.8  
Megabytes of disk.



**Model Z-2**  
Up to 512 Kilobytes of RAM/ROM



**SYSTEM ZERO**  
WITH ODF  
Two Disks  
Up to 512 Kilobytes  
of RAM/ROM  
780 Kilobytes of  
disk storage.

- |                        |                                 |
|------------------------|---------------------------------|
| NEW ★ LISP             | NEW ★ SELF-TEST DIAGNOSTICS     |
| NEW ★ RPG 11           | NEW ★ HIGH RES COLOUR GRAPHICS  |
| NEW ★ CROMIX (UNIX)    | NEW ★ INTELLIGENT I/O PROCESSOR |
| NEW ★ REPORT GENERATOR | NEW ★ SDI GRAPHIC SOFTWARE      |
|                        | NEW ★ BUSINESS SOFTWARE         |

Available from —

3 BANK STREET, SOUTH MELBOURNE, VICTORIA, AUSTRALIA, 3205.  
TELEPHONE (03) 690 2284. TELEX 30458. INSYST.



**Model Z-2B**  
11 Megabytes of hard disk  
storage. Up to 512 Kilobytes of  
RAM/ROM 780 Kilobytes of floppy disk storage.



**System Two**  
Up to 512 Kilobytes of RAM/ROM  
780 Kilobytes of disk storage.

## Microcomputer News & Products

that has been written in Australia for Australian small businesses. It has been written to run on the Dick Smith System-80 computer (and it can be easily adapted to run on a Model 1 TRS-80, with Level II BASIC).

Developed from Dick Smith's own company stock control and pricing system, SCAP can control and manage up to 1200 stock lines. It is easy to drive, using "menus" on the video screen, and can be customised with the user's own company name. It also provides the option of taking Australian Sales Tax into account (or not) when working out gross profit margins, etc.

As well as providing on-screen information in seconds, SCAP can print out a variety of reports, including two different types of price list, five different types of stock status listing, fully itemised sales docket posting reports, and stock count sheets and stocktake analyses (for stocktaking). The last two of these are Dick Smith developments.

One of the other features of SCAP is a machine-language sorting routine which makes item sorting more than three

times faster than with competing programs. It also features special item status "flag" codes.

SCAP comes on two mini-floppy disks (a Program disk and a Sample Data disk), together with a comprehensive User Manual. The complete software package sells for \$275.00.

In order to run SCAP the following minimum hardware configuration is required: (a) a System-80 computer with video monitor and expansion unit, and a total of 32K of user RAM memory; (b) two 40-track floppy disk drives with power supply and daisy-chain cable; (c) a printer capable of printing 132 columns, with matching cable. Current price of this hardware package from Dick Smith Electronics is \$3480.00, including sales tax.

This new software product is available from Dick Smith branches and resellers in each state.

### THREE COMPUTING COURSES FROM RADIO UNIVERSITY

The University of NSW has announced that its educational radio station - VL2UV Radio University - will be con-

Micronews continued p134 →

### The BEST DISKETTES IN THE WORLD



Your Computer files are too important to trust to less than the best. A detected diskette error can be expensive. An undetected error can be disastrous. Solve your diskette problems. DYSAN diskettes are 100% surface tested and are recognised throughout the industry as the best. Put quality on your side - Order some DYSAN diskettes today. Our prices are competitive.

Price inc. tax

DYSAN 5" Soft-sector      Each \$7.70  
(for APPLE II,              Box of 10 \$75.00  
TRS-80, SUPERBRAIN,  
and most others)

Enquire for other types and quantities.  
Orders sent within 24 hours. Please include cheque with order and state type of computer.

### SYSTEM SOLUTIONS

28 Palmerston St,  
BERWICK Vic 3806  
Tel (03) 707 2851



## MICROCOMPUTER PRODUCTS

130 Military Road, Guildford,  
NSW 2161. Phone (02) 632-6301,  
(02) 632-4966. Telex AA25958.

### ANNOUNCING

## THE NEW 1981 AED COMPUTER CATALOGUE.

- ★ BUSINESS SYSTEMS, DEVELOPMENT SYSTEMS, HOME & HOBBY COMPUTERS.
- ★ PRINTERS, MONITORS, KEYBOARDS, HARD & FLOPPY DISKS
- ★ 5100 CARDS - ASSEMBLED AND KITS
- ★ PARTS, TOOLS, BOOKS & MAGAZINES

★ FREE

CALL AT THE SHOWROOM 9 TILL 6 MONDAY TO SATURDAY  
OR SEND A4 SIZED S.A.E.

#### • WE ARE S100 SPECIALISTS

If you are computing, interested in hardware or software, if you are a businessman, an engineer, educator, student or hobbyist - see us before you make any rash decisions you will regret!

#### • COMING SOON - PROGRAMMING COURSES - CALL FOR DETAILS •

Trading hours Mon-Sat 9AM to 6PM.

See previous ads in EA and ETI.

## Microcomputer News & Products

ducting courses on Fortran IV Programming, Microprocessor Fundamentals and Pascal Programming; each commencing in March. Readers in other parts of Australasia will be interested to learn that the lectures will be available on audio cassettes, following conclusion of the broadcasts.

- The course on Fortran IV Programming will be in two parts, with the lecturer being Professor J. M. Blatt, Professor of Applied Mathematics at UNSW.

The language taught by Professor Blatt is USA Standard Basic Fortran IV, which is available on most computers, and suffices for nearly all practical applications. "The course will enable students to write programs on many computers," he says, "not only the one on which they have been taught."

Professor Blatt's radio lectures will be broadcast at 9pm on Mondays, with repeats at 9pm on Fridays over Radio University's station VL2UV. Television sessions and seminars will take place on Tuesday evenings.

- The two-part course on Microprocessor Fundamentals was first

offered in 1980 and proved so popular that Radio University decided to repeat it in 1981. Dr David Mee of the School of Electrical Engineering and Computer Science is the lecturer for the course.

This course requires no more than a basic understanding of electronic circuits and simple logic networks. Only general experience of computing is necessary. "By the end of part 1 students will have reached a level where they can understand simple programming and application of microprocessors," says Dr Mee. "In part 2, I go into further hardware and software problems encountered in microprocessor systems, and look at typical evaluation modules. I will then demonstrate how to design, develop and debug a simple microprocessor project."

Dr Mee will broadcast 10 lectures for each part of the course at 8pm on Wednesdays, with repeats at 9pm on Thursdays. There will also be one television segment to each part, and Dr Mee will conduct three evening tutorials at the University.

- The course on Pascal is also in two parts, with the lecturer being Ken Robinson of the Department of Computer Science.

Pascal is today's most sophisticated structured programming language. It provides extra capabilities that boost performance and cut development time for almost all computer projects.

Ken Robinson has structured the course so that it can be followed by beginners with no previous computing experience.

Part 1 of the course consists of six radio lectures, to be broadcast by Mr Robinson at 7pm on Mondays with repeats at 8pm on Fridays over Radio University's station VL2UV. In addition, Mr Robinson will use two television programs on Tuesday evenings for programming demonstrations, and conduct three attended seminars at the University of New South Wales.

Fees range from \$42 to \$56 dependent on Course selected. The audio cassettes are priced at \$7 per cassette (ie, approx \$150 per Course).

Radio University transmits on 1750kHz just off the regular broadcast band, and can be picked up in the Sydney area on a radio adjusted to receive this frequency. Instructions on how to modify a radio are sent out to enrolled students, or they can buy a transistor set already modified for \$8 from Radio University. Television University transmits on 631MHz to four viewing centres in the Sydney Metropolitan area.

Further information on these and other radio, television and tape courses can be obtained from the Division of Postgraduate Extension Studies, University of New South Wales, telephone (02) 662 2691.

## IS YOUR PET™ A DUMB ANIMAL?

If you are having problems with debugging programs on your Commodore PET/CBM™ Micro-Computer, perhaps a Programmers Toolkit™ will help. The Toolkit™ consists of several extra BASIC commands which are implemented on a ROM chip which plugs into one of the spare sockets in your computer. These commands are: -

<b>AUTO</b>	- Automatic Line Numbering.	<b>STEP</b>	- Execute one line at a time.
<b>DELETE</b>	- Delete program lines in range.	<b>OFF</b>	- Turn TRACE/STEP off.
<b>RENUMBER</b>	- Renumber program lines.	<b>FIND</b>	- Find all occurrences of instructions, variable names or strings.
<b>DUMP</b>	- Dump contents of all variables.	<b>HELP</b>	- Highlight reason for error.
<b>TRACE</b>	- Display last 6 line numbers executed.	<b>BYE</b>	- Disable Toolkit (BASIC 4.0 only)

Toolkits are available for all PET/CBM™ models including the new 8000 Series. Prices are as follows:- (When ordering, please describe your machine and any memory or operating system upgrades).

TK 4.0 - for all PET/CBMs™ with BASIC 4.0 Operating System	\$69.00
TK 160 - for all PET/CBMs™ with BASIC 2.0 Operating System	\$69.00
TK 80P - for original BASIC 1.0 Operating System (Old Roms)	\$80.50

We have many other products for owners of Commodore Machines. Books in stock are:

PET Revealed - Explains the inner workings of your PET/CBM™	\$30.00
Library of PET Sub-Routines - Stacks of useful sub-routines for sorting, etc	\$30.00
PET/CBM Personal Computer Guide - Covers all things the Manuals don't	\$17.00
PET and the IEEE - How to use the PET/CBM™ as an IEEE488 Bus Controller	\$17.00
6502 Assembly Language Programming - Excellent book with many examples	\$16.00
Hands on BASIC with A PET - Beginners guide to programming the PET/CBM™	\$18.00

All prices include Sales Tax. Please add \$1.00 per item ordered for postage/packaging within Victoria and \$2.00 per item for interstate orders. Bankcard orders welcome. Please quote card number and expiry date.



MICROCOMPUTER SYSTEMS DESIGNERS

**B. S. MICROCOMP,**

4th Floor,  
561 Bourke Street,  
MELBOURNE, 3000.

**Tel: 614-1433/614-1551**

## Microsoft Editor/Assembler reviewed

Microsoft Inc have recently released a new version of their EDTASM editor/assembler, suitable for use with both the System 80 and TRS-80 computers. Apart from the editor and assembler there is also a powerful debugging monitor called Z-BUG. All of this adds up to a very versatile software development package.

We will look at the package by examining each of the modules in turn, starting with the editor, then proceeding to the assembler and finally the Z-BUG monitor.

The editor is easy to use and is also very versatile due to its extremely good editing facilities. The input format is the same as most other text editors in that it starts with the statement number in the extreme left hand column, followed by the label field, the op-code field, the operand field and finally the comment field. Each of the fields are separated by a fixed number of tab stops which helps to keep text in a neat orderly fashion.

When the editor is first called up, the command to insert text (I) is given, followed by the starting statement number and then the increment between the statement numbers. The actual format is \*I100, 10 where the \* is the command mode prompt. The 100 specifies that the first statement number will be 100, while the increment between lines will be 10. This is very useful when it comes to adding additional lines of text between existing lines.

There is also a line renumber function that allows the user to renumber the statement lines. A situation that often occurs is that a few lines of text have to be inserted somewhere but the numbering of the lines won't allow this. This is where the renumber function comes in to play.

Another handy function is a set of positioning commands that allow the user to locate a particular block of text in the edit buffer. The editor always maintains a pointer to the current line of the edit buffer. Two special symbols are used to position the pointer to the beginning or the end of the edit buffer. It is also possible to do a line-for-line search using the up and down cursor controls.

It is possible to print out either the entire contents of the edit buffer, or just a particular block which can be specified in the format of the print (P) command.

Another very useful feature is the ability to move specified blocks of text around to any location within the edit buffer. When a move is made, the text is placed into the new location while the

text at the original location is automatically deleted. This is a very powerful and time-saving feature.

It is also possible to copy a block of text from one part of the buffer to another, but keeping the original source intact. This is great if you need a routine two or three times in the one program but don't want to go to the trouble of defining a macro (an often used subroutine).

That just about completes the summary of the major features of the editor and as can be seen, it is quite powerful.

Having prepared the source code with the aid of the editor, we are ready to move onto the assembler. This has the capability to assemble directly into memory and enables the use of macros. Other powerful features of the assembler include a function that allows the suppression of certain portions of the assembled code when printed out. It is possible, for example, to suppress the object code in a printout, symbol tables, printing of macros, or the entire program listing. This allows proprietary codes to be suppressed and therefore aids in the protection of software.

The assembler supports a good range of pseudo-ops, including the definition of single bytes, 16-bit words and also the definition of messages. The latter is extremely useful when text is to be incorporated into the program.

The assembler will also evaluate expressions such as DEFB \$-TABLE where \$ is the current value of the program counter and TABLE is a label in another part of the program. This expression is being used to find the size of a data table relative to the current value of the program counter. All four arithmetic operations are supported.

One thing that the assembler does not appear to support is the ability to specify GLOBAL symbols and there does not appear to be any facility to link programs together. I may be wrong about this but the documentation that accompanies the software makes no mention of these facilities.

The last major feature of the assembler is conditional assembly. The user can specify a certain set of conditions under

which the assembly is to take place, and only when all conditions have been met will the assembler do its work. A very powerful and useful feature.

Now we come to the Z-BUG debugging tool. This allows the writing and editing of the source code, the assembling of the program, and then the debugging to be done without the need to load all these utilities separately. They are all loaded in together, and since they are all resident, the problems associated with debugging and modification are largely overcome.

Z-BUG will allow memory locations to be displayed and modified in hexadecimal, decimal or octal. This is a great help if you are working with 8080 code which is to run on the Z-80. Another useful feature is symbolic debugging. This relies on the editor buffer remaining intact since it references the label field in the source code. In this mode the user specifies a label and then proceeds to debug the program with the output showing the label and the corresponding offset into the program. This is a very powerful debugging mode that also allows modification of any memory location at any time.

With Z-BUG it is also possible to display and modify any of the registers and their contents. All registers and contents can be displayed simultaneously if desired.

Other features that Z-BUG supports are breakpointing, with a total of eight breakpoints being allowed, and a most important function, single-step execution. To use this function, the user enters the execution address and then presses @. The instruction at the execution address is then acted upon. Further use of the @ key will continue the execution of the program.

If the editor buffer is still intact, it is possible to specify a label as the execution address. This is a good way of testing subroutines etc.

A final note regarding Z-BUG. Although Z-BUG is loaded together with the editor/assembler, there is a stand alone version of Z-BUG on the reverse side of the cassette. This proves handy when the services of the editor/assembler are not required.

In summary, this is an excellent software development package which represents good value for money. It is highly recommended. The retail price is \$39.95.

The review sample came from Dick Smith Electronics, Cnr Lane Cove and Waterloo Roads, North Ryde, 2113. Phone (02) 888 3200 (G.C.)



# THE NDK S-4000 PRINTER

For all bulk word processing applications where reliability, speed and sustained print quality are of prime importance.

The NDK S-4000 is supplied with a heavy duty 16-wire head producing single pass high quality 17 x 16 matrix characters at 75 characters/second for word processing quality and 150-200 characters/second for drafts.

Four fonts (dot matrix, word processing, super/subscript and Katakana) are supplied as standard. Typical scientific, mathematical and currency symbols are included as standard. The fonts can be intermixed as bold faced, enlarged (5 CPI, 17 x 23 matrix), reduced (12 CPI) or normal (10 CPI). Other fonts can be specified by the user. Each dot on the 16 x 16 matrix can be programmed by the host computer to produce special graphic effects (such as letterheads and trade marks). Full page graphics is possible by controlling ten wires of the printer head and executing half-line feeds. The special graphic patterns can be printed at the rate of 900 dot columns/second at a resolution of 4.7 dots/mm (120 dots per inch) both horizontally and vertically. A horizontal dot resolution of 240 dots per inch can be produced using half dot timing.

Superscripts and subscripts are produced by the superposition method enabling complicated mathematical formulae to be produced quickly and easily. The subscripts and superscripts are half normal size and the printing pitch is half that of the PICA.

## PRICE

The following come as **standard** and are **included** in the price shown:

- |  |  |
|--|--|
| A. Parallel or RS232c Serial (which includes ETX/ACK and X-ON/X-OFF protocols) | E. Variable pitch (10 CPI, 11.7 CPI and 5 CPI)       |
| B. Front or rear paper feed  | F. Soundproofed contoured casing                     |
| C. Adjustable tractors   | G. Ease of maintenance (only 3 major sub-assemblies) |
| D. 2 x Form Control Loops & 2 Ribbons  | H. 6 months' warranty                                |

**PRINTER (excluding sales tax) ... \$3,190.00**

JOHN F. ROSE COMPUTER SERVICES PTY LTD IS THE SOLE AUSTRALIAN DISTRIBUTOR FOR THE NDK RANGE OF PRINTERS.

# OPAL COMPUTER SYSTEMS

The OPAL 1000c is an 8-slot S-100 system conforming to the new IEEE standards. An NNC Electronics Z80a 4MHz CPU card with 2 RS232c serial and 3 + 8 bit bi-directional, fully buffered parallel ports is used in conjunction with the California Computer Services Disk Controller. One serial port has been initialised as a printer port. An additional I/O board with 2 serial and 3 parallel ports is provided for communications with peripherals and other systems.

Memory is provided by a 4MHz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable.

Disk drives are 2 x 8in Shugart SA801R running at double density (480k/drive).

The system is mounted in an attractive pressed aluminium housing with a cast front panel fitted with reset button and key operated on/off switch.

The operating system software is CP/M version 2.2. An extensive monitor is included.

Full test utilities for the CPU, disk drives, memory, terminal and printer are available.

**PRICE ... \$4,775.00 (excludes sales tax)**

# BSTAM

BSTAM is a commercially orientated telecommunications facility for transmitting and receiving CP/M files over telephone lines. Files may be sent between two CP/M computers using a short wire.

BSTAM will transmit and receive **any CP/M** file. There is no limit on the size of the file. In addition to this, all data is transmitted exactly as it is stored on disk. For example, if a byte of data is 'X'FF', it is sent as 1 byte and not as 2 ASCII F's. By doing this, data is transmitted at maximum line speed.

BSTAM includes the following features:

1. ERROR CHECKING
  - Framing Errors
  - Overrun Errors      Parity Errors
  - BCC Errors (Block Control Check - CRC type)
  - Auto Block Resend      Lost Data Errors
  - Mid Block Resend      Exception Errors
  - Length Errors      Time Out Errors
  - BCB errors (Block control Byte Counter)
2. GROUP FILE TRANSMISSION AND RECEPTION
  - Transmit A: \* \*      Receive A:
  - Transmit B: \* .BAS      Receive B:
3. USER INTERFACE FOR UART/USART CHIP

## New Features

BSTAM now has a new extended receive mode. In this mode BSTAM will wait to receive more files until a Control C is entered on the receiving console. In addition, BSTAM has further enhanced recovery features when data errors are detected.

## Hardware and Software requirements

- \* 16k RAM
- \* 1CRT (running at least 4800 baud)
- \* 1 disk drive
- \* CPU 8080/Z80 or 8085
- \* Asynchronous modem that will support at least 300 baud:
  - Full duplex option
  - Originate or Answer option      RS-232 option
- \* SIO interface (UART/USART chip)
  - 300 baud strapping      Header strapped at terminal end
- \* CP/M or some derivative
- \* RECEIVE.COM (BSTAM)
- \* TRANSMIT.COM (BSTAM)

On short wire connections, the baud rate may be set at 9600 baud.

**PRICE ... \$150.00**

## BSTMS

**BSTMS** was designed for the use of CP/M computers to connect the host computer (IBM, Honeywell, Univac, etc) for time sharing. **BSTMS is a high level TTY emulator.** The main difference between BSTMS and a real TTY is its ability to send and receive files. As you know, a human operator cannot enter data at 30 chrs/sec. This is what BSTMS does very nicely. Also BSTMS can echo all Host input to your list device.

BSTMS is divided into separate parts. First there is the terminal mode and second the file mode. The terminal mode is used to run your CP/M computer as if it was a TTY. While in the terminal mode, you may change between half and full duplex at any time just by keying a command to BSTMS. After doing whatever you have to do in CP/M, you may return to BSTMS and start off in the host computer. Also BSTMS has been connected to all types of CBBSS and ABBSS. BSTMS may also connect to another CP/M system as its host computer.

While BSTMS is in file mode, you may send or receive a file to the host computer. When sending a file, BSTMS will expand all Control Is into multiple spaces to align on columns of 8. BSTMS may also transmit binary files. There are two programs used to send and receive binary files. The first is DCOMPRES.COM. This program will convert any binary file into an ASCII file. The second program is COMPRES.COM. This program will convert any DCOMPRESSED file into a binary file.

The minimum requirements in the computer hardware and software are:

1. CP/M operating system or compatible
2. 24k user memory space when transmitting a file. All received files must fit into the available memory. (See BSTAM.)
3. 1 disk drive
4. 1 CRT running at least 4800 baud.
5. CPU: Z80, 8080, 8085
6. Asynchronous modem that will support at least 300 baud
- a. Full duplex option
- b. Originate option
- c. RS-232 option
7. SIO interface - Any USART/UART chip
  - a. 300 baud strapping
  - b. Header strapped at terminal end
8. Installation of BSTMS may require knowledge of assembler language programming. Installed using the same technique as BSTAM.

**PRICE ... \$200.00**

## LIFELINES

**Lifelines** is a monthly software newsletter published by Lifeboat Associates.

Although Lifelines contains features and columns dealing with new software products on the market, product comparisons, the CP/M Users Group and other items of general interest, the principal role of the periodical is to provide timely notice to owners about their software. Each month, new revisions are reported, together with information on the purpose for each such release, be it for the correction of "bugs" or the addition of features and facilities.

The software products distributed by Lifeboat Associates are frequently both complex and costly. We recommend that all serious users of software should take out subscriptions to Lifelines, ensuring that they are automatically informed about the current state of their software tools and thus get full value for their purchase.

### Subscription Costs

- \$36.00 for 12 issues. Price includes postage for anywhere in Australia.
  - \$5.00 each for back issues. Price includes postage for anywhere in Australia.
- All orders must be prepaid.

**CATALOGUES: \$1.00 FOR HARDWARE DETAILS AND SOFTWARE SUMMARY**

**\$5.00 FOR OUR FULL 140 PAGE SOFTWARE OMNIBUS**


**PRICES INCLUDE POSTAGE IN AUSTRALIA**

# JOHN F. ROSE

## COMPUTER SERVICES PTY. LTD.

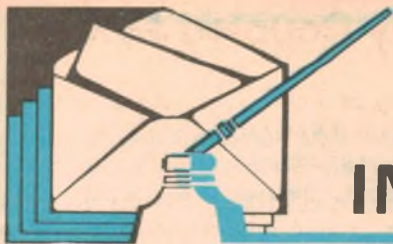33-35 ATCHISON STREET, ST. LEONARDS, N.S.W., 2065, AUSTRALIA  
TELEPHONE: (02) 439 1220 TELEEX: AA 27901

PRICES AND  
SPECIFICATIONS  
SUBJECT TO  
CHANGE WITHOUT  
NOTICE



## INFORMATION CENTRE

**BASS GUITAR:** I am about to buy a bass guitar and I would like to make my own bass amplifier and speaker box. I have looked in your latest publications, but I could not find anything suitable for a bass amplifier. I was wondering if you could send me some plans of amplifiers suitable for a bass amplifier (over 100 watts) at a reasonable cost, less than \$150. Also could you supply plans for a good speaker box and cross over for a large woofer speaker. (D. P., Melbourne.)

● Although we have not published a complete guitar amplifier in recent times which is suitable for your purposes, the Playmaster 300W amplifier as described in the June and July issues of 1980 would be suitable for the power amplifier and in conjunction with the guitar preamplifier as described in the October 1968 issue would constitute a powerful but inexpensive bass guitar amplifier.

An article entitled Loudspeaker Systems for Electric Guitars was published in September 1968, and although a little dated, will still apply when using modern loudspeakers. It would be advisable to observe the manufacturers power ratings though. These articles are available through our information service at \$3 per article, which includes postage.

**BURGLAR ALARMS:** Ten or 12 years ago, after an article appeared in your magazine, we corresponded about burglar alarms for private homes. I contributed an article, which was published, in which the relay was activated by a transistor only if a burglary was attempted. This system had the advantage over normally activated relay circuits in that the current consumption of the circuit was considerably reduced.

I regret that since those days, due to pressure of other interests, I have been unable to indulge myself in the very interesting subject of electronics and hence am out of date on the subject.

I may say that at a later date an attempt was made to burglarise my home. The alarm was activated, and the would-be burglar fled, leaving open a window. A woman neighbour telephoned the local police station and reported the ringing of the alarm bells in my home. The reply she received was "The batteries will soon run down and then the bells will stop ringing". No police came to my home to check on the alarm.

I took up this dereliction of duty with Police Headquarters and an enquiry was instituted. I was informed that; "Appropriate action was taken". However, knowing the police department as I do, I imagine this statement meant that nothing was done!

As probably you are aware, the State Government has decreed that from January 1 next burglar alarms must be fitted with a device which automatically switches off the alarm after the alarm has been ringing for 10 minutes. I am of the opinion that this period is too short and should be extended to half an hour. However, the Government has spoken.

I do not possess the knowledge necessary to install in my alarm circuit the device needed to switch off the alarm after it has been sounding for 10 minutes. Therefore I wish to enquire whether you would provide me with the necessary information. Of course it may be that you have already published in your excellent magazine this information. (K.G., Castlecrag, NSW).

● Unfortunately, we have not published a circuit which would meet your requirements although it would be a fairly simple design. We will consider publication of an up-to-date burglar alarm while bearing in mind that quite a few commercial burglar alarms are available at reasonable prices.

**PH METER:** Would you please ask your readers if any of them have a circuit diagram for a PH meter, and also a circuit diagram for a b&w TV tube tester and rejuvenator. I will be happy to reimburse anyone who can help me for stationery and stamps etc. (L. R. Mansbridge, 41 Wharf St, Tuncurry, NSW 2428).

● Request granted L. M. We have published your full name and address so that readers may contact you directly.

**REMOTE CONTROL:** I have recently constructed the Stereo Infra-Red Remote Control Unit (October 1979).

The unit works well and has a high sensitivity. The one problem I have encountered is that every time the volume is changed, both up or down via the remote control, there is a great "thump" through the speakers.

The unit is connected between the pre-amp and power amp in my system. I wonder if this is a common fault, and if so what could be done to overcome it (P. S., Mount Isa, Qld).

● The problem you are having with "thumps" when the volume level is changed could be due to the metal shield around the audio stage, IC2, not functioning. Another possible fault is due

## UTC — Co-ordinated Universal Time

**UTC and GMT:** Recently I heard Radio Canada International say that as from May 4, 1980 they would drop GMT (Greenwich Mean Time) and use UTC. In the August 1980 issue of Electronics Australia I read that the World Administrative Radio Conference had decided to do likewise. Is this a bit of one-upmanship on the part of UTC people, as the time is the same and the reference co-ordinate is the same? It appears that only the name is changed. I understand that UTC is more accurate than GMT but surely this accuracy is academic and is only useful to space travel and the like. It will be of insignificant use in radio broadcasting. Finally, how does Co-ordinated Universal Time come to be UTC, rather than CUT? (H. C., Nowra, NSW).

● The tendency in timekeeping worldwide is to standardise its terminology. GMT is for all practical purposes the same as UTC. However, the

art of timekeeping has made enormous strides in the past few decades and as various errors and situations have been uncovered, different titles have been given to various time scales to cope with these errors. Incidentally, the errors generally arise from irregularities in the rotation of the earth. As recently as 1972, a time scale, was agreed internationally, based on atomic time and arranged so that it would stay as closely as possible to mean solar time. This scale is designated UTC, Co-ordinated Universal Time. Any accumulated errors are corrected periodically by adding or subtracting a "leap" second as required. The Bureau International de l'Heure, in Paris, acts as an international co-ordinating body for timekeeping services. We suspect that the discrepancy between UTC and "CUT" has occurred in its translation from the French. GMT is considered to be the same as mean solar time and so there would be some small discrepancies between GMT and UTC.

to the changing DC output voltage of IC2a and IC2b caused by the biasing currents drawn by the op amps, via the attenuator resistors. Perhaps the 4136 device you are using is marginal in which case you could try replacing it with another 4136 or with the BI-FET equivalent, the Texas Instruments TL075. This has an extremely low input bias current of 7nA hence it should not suffer from this problem.

**DELTAHET MARK 2 RECEIVER:** In Electronics Australia for February, March, April and May, 1971, you described the Deltahet Mark 2 Communications Receiver. I wish to know if you are going to rejuvenate it, incorporate a printed circuit board and a five digit frequency meter. If so, when? (G. W., East Burwood, Vic).

● We regret to advise you that we have no plans at present to update the Deltahet Mark 2 Receiver.

**DIGITAL CAPACITANCE METER:** Having constructed your digital capacitance meter (March, 1980) and found it to be a tremendous help to me on the work bench, I was wondering if it would be possible to add inductance ranges to it, as may be done with some analog meters. If this is impractical would it be possible to feature a project on this subject in a forthcoming issue, as I am sure many readers would be very interested in building one using the same digital format. (J. H., Windsor Gardens, SA.)

● Unfortunately the digital capacitance meter could not be adapted to measure inductance but we may consider a combined capacitance/inductance meter as a possible project.

**TV ANTENNA:** I was wondering if there are any back issues dealing with TV antennas suitable for country areas? As I have an engineering shop, the manufacture of an antenna presents no problem. I merely require a design. (D.A.B., Beverly Hills, NSW.)

● As most enthusiasts prefer not to get involved in complex mechanical construction, it is many years since we published a TV antenna project. However, we published three articles in 1965 which may be of interest to you. They were "Fringe Area TV Reception" (6/ATV/8) in September, 1965, "Log Periodic Dipole Antennas" Pt 1 (6/ATV/9) in December, 1965 and Pt 2 (6/ATV/10) in January, 1966. Whilst the two later articles deal in depth with the design of antennas, the first articles looks at fringe area TV reception and the methods of overcoming the problems involved, and serves as an excellent introduction. We can supply photocopies of each of these articles at our usual price of \$3 each (ie \$9 the set).

## More on the Acoustically Coupled Modem

**ACOUSTICALLY-COUPLED MODEM:** I have read your magazine over many years and have always found it interesting and stimulating, particularly in this electronic age.

I was very interested in your article in September 1980 on the Acoustically Coupled Modem for joining up terminals or for home computers over telephone lines. However, now that you have whetted our appetites, there is one problem many of us will be faced with. No doubt most of us have had experience with BASIC and understand this part reasonably well.

When it comes to the sort of programming requirements to get these connections to work through the modems, however, many will be as lost as I am. What about a nice helpful article on the requirements for this and perhaps even a few program hints to get things working? (R. G., Glen Iris, Vic).

● We understand your problem although we would assume that most personal computers would have instructions in the manual on how to use the serial ports. If your computer is one that does not have a serial port, such as the Tandy TRS-80 or Dick Smith System-80, you will need a parallel-to-serial adapter or use the serial interface system and program described in our November 1980 issue (File No. 2/CC/56). In general, the PEEK and POKE instructions are used

**EPROM PROGRAMMER:** Your EPROM Programmer project (EA July 1980) was most timely and I am now procuring the necessary components to have this project built.

My problem is this! I'm currently developing a program that runs in excess of 8K and may possibly exceed 16K. How then can I utilise the EPROM programmer to burn and run programs in excess of 8K?

I guess that an EPROM card similar to the S-100 bus 16K EPROM card would be required, but I'm not sure of this.

I would greatly appreciate any assistance that you can provide. Perhaps other EA readers have a similar problem. (R. S., Wagga, NSW.)

● The EPROM programmer which we described in July 1980 can only program or read the contents of one ROM at a time. Hence it is possible to burn as many ROMs as you like but not all at once. One other point to be noted is that the programmer is not memory mapped so it cannot run the program in a ROM. This can only be accomplished by plugging the programmed ROMs into ROM sockets provided on the computer or a plug in EPROM board as you have mentioned.

to send and receive data via the serial port and thus via the Modem.

**ACOUSTICALLY COUPLED MODEM:** Your project in the September issue entitled "An Acoustically Coupled Modem for Computers" appears to be very interesting. Whilst your Acoustic Coupler project is half-duplex in the form in which it was published, it would seem to me to be fairly easy to construct as an answer-only or originate-only device simply by certain substitutions of components on the receive side or transmit side as appropriate.

Such a device would be eminently useful to me and possibly other users. Would you seriously consider publishing the component values required to transmit and receive 980/1180Hz. (G. D., Sydney NSW.)

● To change the transmit and receive frequencies of the Modem from 1650/1850Hz to 980/1180Hz: On the transmitter the .01uF and .0068uF capacitors on IC4 and IC5 are changed to .0168 (.01 in parallel with .0068) and .01 respectively. On the receiver the 1.5kHz high-pass filter will need to be reduced to a 500Hz high-pass filter by using a .016uF capacitor for the .0068uF and .0082uF for the .0047uF capacitor. Also the .033uF on IC7 connecting pin 9 to pin 1 should be changed to .056uF for a centre frequency of 1080Hz.

**PLAYMASTER 760 ORGAN:** I am interested in building the Playmaster 760 Organ as described in March, April, May, June and August, 1976. Would it be possible for me to build such an organ without any previous experience? Unfortunately, I do not have all of the series of articles, so could you send such plans to me if they exist in such a form I could understand? What is a "polyphonic" keyboard? I am also interested in the Auto Rhythm Unit by David Edwards. Could this be incorporated into the organ? Would such an organ be suitable for a rock band? (G. B., Yanco, NSW.)

● We would hesitate to encourage you to embark on such an ambitious project without any previous experience. We can supply copies of the original articles for \$3 each. A polyphonic keyboard is one where multiple notes may be played at the one time. The Auto Rhythm Unit could conceivably be added to the Playmaster 760 Organ but again we must emphasise that this would require at least some previous experience in the construction of electronics projects. Finally, we doubt that the organ in question would be suitable for rock band work, as it was designed more for use with classical music in mind.

## RESISTORS

150 ohm, 5W	20c
10 ohm, 5W	20c
47 ohm, 5W	20c
12 ohm, 3W	20c
2.5 ohm, 3W	20c
33 ohm, 3W	20c
8 ohm, 10W	25c
4000 ohm, 10W	25c
100 ohm, 5W	20c
330 ohm, 10W	25c
220 ohm, 5W	20c
5 ohm, 5W	20c
220 ohm, 10W	25c
950 ohm, 20W	20c
115 ohm, 5W	20c
10 ohm, 5W	20c
1k ohm, 5W	20c
5000 ohm, 5W	20c
6.8k ohm, 3W	25c
3300 ohm, 10W	25c
6800 ohm, 10W	25c
1500 ohm DUAL 21W	50c
50 ohm, 5W	20c
330 ohm, 5W	20c
1k ohm, 5W	20c
820 ohm, 5W	20c
12 ohm, 10W	25c
470 ohm, 7W	20c
4700 ohm, 4.5W	20c
5000 ohm, 10W	25c
8.2 ohm	5W
3.3K	7W
1 ohm	5W
10K	7W
2.5 ohm	3W

## CAPACITORS

0.0039uF, 1500V	20c ea
6N8, 1500V	20c ea
0.0068uF, 1500V	20c ea
1200PF, 400V	10 for \$1
0.068uF, 400V	5 for \$1
2200PF, 630V	10 for \$1
0.47uF, 250V	10 for \$1
0.10uF, 400V	5 for \$1
0.082uF, 160V	10 for \$1
26k, 250V	10 for \$1
0.041uF, 400V	10 for \$1
0.033uF, 250V	5 for \$1
0.027uF, 100V	20 for \$1
220uF, 10V	10 for \$1
1uF, 350V	10 for \$1
470uF, 40V	5 for \$1
1000uF, 16V	10 for \$1
2.2uF, 200V	10 for \$1
0.047uF, 1500V	50c
47uF, 25V	4 for \$1
680uF, 40V	50c
22K, 100V	20c
330uF, 25V	25c
2.2uF, 200V	30c
470uF, 40V	50c
680uF, 35V	50c
0.015uF, 250V	25c
2500uF, 35V	\$1
1uF, 100V	25c
1000uF, 16V	50c
220uF, 16V	50c
2000uF, 63V	\$1
0.47uF, 400V	50c
680K, 250V	25c
0.12, 250V	25c
15NF, 250	10c
120K, 250V	20
10uF, 315V	25c
0.056, 250V	10c

### Slide Pots

250K-50K	3 for \$1
Dual 500K	3 for \$1
1 Meg	3 for \$1
2 Meg	3 for \$1
Including Fancy Gold Knobs	
25K dual	2 for \$1

### SPECIAL

100 mixed resistors, all useful	\$2
100 mixed capacitors, fresh stock	\$2

### AUDIO LEADS

3.5m to 3.5m, 7ft	75c
3.5m to 6.5m, 7ft	75c
6.5, 7ft	50c

### MICRO SWITCH

5A, 250V AC	75c ea
-------------	--------

### TUNING CAPS

2 and 3 gang	\$1 ea
Min 2 gang	50c

### FUSES

0.5A, 2A, 3.25	10 for \$1
In line fuse holders	30c
RCA jack plugs and sockets	40c pair
1A, 10 for	\$1

# L. E. CHAPMAN

122 PITT ROAD, NTH CURL CURL.  
MAIL ORDERS: BOX 156, DEE WHY, NSW. 2099.  
TELEPHONE 93-1848.

## SPECIAL TRANSISTORS

AD161-162	\$2.50 pr
BSC 901A	\$1.50 ea
BC 548	10 for \$1
AD 149	\$3 pr

## ELECTROS

470uF, 25V	5 for \$1
400uF, 10V	5 for \$1
47uF, 63V	5 for \$1
350uF, 16V	2 for \$1
27uF, 160V	5 for \$1
25uF, 63V	10 for \$1
22uF, 160V	10 for \$1
47uF, 16V	5 for \$1
47uF, 200V	5 for \$1
220uF, 10V	10 for \$1
68uF, 16V	10 for \$1
2500uF, 63V	2 for \$1
100MFD, 350V chassis mount	\$1

- Telescopic aerials, \$1.50
- Top quality, low impedance microphones, \$3.50
- 6 inch ferrite rods, 75c
- Rainbow lead, 5 strand, 20c per metre
- Line output transformers, 600 ohm, to 15 ohm, 20 watts, \$5
- Line output transformers, 1200 to 3/ohm, 5 watt, \$1
- Power supply units, filtered, 240 to 20 volt, \$12
- 240 to 15 volt transformers, \$3.50

Power leads 240 volt, suit most tape recorders, radios, etc \$1 each.

TV Stick Rectifiers 20SC, \$1.00.

Phillips Colour TV Convergence Boards, \$3 each

455KC IF Transformers for valve radios, \$1 each. Also aerial and OSC coils, 75 cents each

## POTS ROTARY

1/2 Meg	30c
1 Meg	30c
100K	30c
100K Switch	50c
50K Double Pole Switch	50c
7.500	30c
10K Switch	50c
250K	30c
50K	30c
20K	30c
10K Min Pots	25c
50/Ohm	50c
1/2 or 1 Meg Switch	50c
1/2 1 meg dual Concentric tapped at 100K	\$1
2 meg ganged double pole switch	\$1
1.5 meg dual ganged	50c
2 meg ganged log	\$1
1 meg dual ganged	\$1
1/2 meg dual ganged LIN	75c
25K, 50K dual ganged Concentric double switch	\$1
200K single line	30c

HOR Drive 3021 transformers for colour TV \$2  
TV Colour Convergence Units 11270 44 x 6 \$3

### PILOT LIGHTS

Screw in 6.3V	10 for \$1.50
24V	10 for \$1.00
Pilot light holders	\$1.50

- Car radio suppressors, 3 for \$1
- 3 position slide switch, 50c
- Toggle switches, 25c
- 2 position push button switch, 50c
- 6 position push button switch, \$1
- 4 position push button switch, 75c
- Transistor ear plugs & leads, 3 for \$1
- In-line fuse holders, 4 for \$1
- 4 pole 2 position rotary switches, 50c

Pick up Cartridges BSR universal type Ceramic Stereo.....\$5  
Audio Technica AT6 diamond stylus stereo.....\$12

## DIODES

OA 626	4 for \$1.00
OA 662	4 for \$1.00
EM 410C	4 for \$1.00
DS 150A	50c
DSY 130YO	50c
OA 636	50c
HR 15	50c
Diodes BYX 55, 600	30c
BY 188	30c

## STEREO AMPLIFIER SOLID STATE 5 watts RMS per Channel \$25



PP NSW	\$1.50
Interstate	\$2.50
WA TAS	\$3.50

Special: 100 mixed capacitors, fresh stock, all useful. \$2.00

## SPEAKER SPECIALS

15 ohm 4" — 2 for \$2.
5x3 15 ohm 2 for \$2
6x9 15 ohm \$5 each
5x7 15 ohm \$4 each
8x4 15 ohm \$4 each
6x4 15 ohm \$3 each

## SUPER SPECIAL

GRAMOPHONE motor and pickup 3 speed stereo balanced arm

240 volt \$9.75

PP NSW \$1.50

Interstate \$2.75

WA \$4



\$250 WA \$3.50

Miniature speaker and drive output transformers \$1 pr

Special mixed tag strips 10 for \$1

## 24V MOTORS

Reversible

Only \$2.50 ea.




## SPEAKER SYSTEMS



Incl one 6 x 4 speaker, 5W RMS, \$4.75 ea  
P&P: NSW \$1.80, Interstate \$2.80, WA \$4  
(For singles or pairs.)

## TV TUNER VALVE TYPE

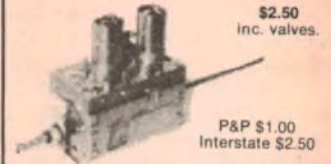

\$2.50  
inc. valves.

P&P \$1.00  
Interstate \$2.50

## SUPER SPECIALS FM STEREO TUNER KITS



Sets of 3 modules include FM tuner, decoder and IF detector. Circuit diagram supplied. Can be used with amp modules.

ONLY \$22  
P&P \$1.00

## TRANSISTORS

2N3055	\$1.20
SE1002	4 for \$1
BF459	50
B544 DE6	50
C106 F1	50
TIP 110	50
608EK	4 for \$1
BCS54813	10 for \$1
2SB186	50
2SA101	50
BD263	50
BSB405	50
2SB77	50
2SB303	50
AC187	50

## VU & BALANCE METERS

STEREO VU \$3.00



12Kn 100uA \$2.00

## PHILIPS TV TUNERS

Transistor NT3024, NT3032, Colour — P&P \$1.



\$10 ea.

**TRANSISTOR-ASSISTED IGNITION:** I have built the Transistor-assisted Ignition Kit and installed it in an HJ Holden van. I have only experienced one problem with it, that is, severe electrical interference with the car radio. Capacitors and suppression leads are fitted to the engine, and while running on the standard ignition there is minimal interference. I have checked the whole unit and it seems satisfactory to me. Your advice would be much appreciated. Secondly, I believe that a diagram of an In-circuit Transistor Tester once appeared in your magazine. Could you kindly tell me in which year/month it was published? (D.W.B., Gordonvale, Qld.)

● We assume that you are referring to the Transistor-assisted Ignition System described in our December, 1979 issue. Interference problems usually arise in one of these three areas:—

1. Radiation from the negative return to ground of the electronic unit. Keep this lead short and well away from the vehicle's own antenna. Sometimes it helps to return this lead direct to the engine block rather than the body/chassis of the vehicle.

2. Inadequately earthed case of the Transistor-assisted Unit. Generally, it is better to earth the case separately from the unit's own ground return, and to earth to one of its own mounting screws.

3. Radiation from the additional (length of) lead between (the CB terminal of) the coil and the electronic unit. Keep this lead as short as practicable, and well away from the vehicle's antenna.

Re your other query on the in-circuit transistor tester — this project was published in our April, 1977 issue (File No. 7/VT/13).

**TV SET ENGINE SCOPE:** Since reading the article on the TV CRO adapter in the May, 1980 issue of EA, I was wondering if it would be possible to use this project as an auto ignition analyser. I already have an ignition scope, but I find it difficult to interpret the waveforms on the small screen, in particular when there are six or eight traces being displayed. Also, have you considered featuring a negative ion generator project. It seems to me from what I have read on the subject that these devices are very similar to the television EHT circuits and should therefore not be beyond the capabilities of the home constructors. (W. W., St Marys, NSW.)

● While it may be possible to use the principle of the TV/CRO Adapter, considerable difficulties arise if many waveforms need to be displayed simultaneously. Another problem is that the TV/CRO Adapter has no sync facility whereby the display can be locked.

And while it is possibly true that television EHT circuits do produce negative ions, they also tend to produce ozone. In

## Want something? Read this!

"Electronics Australia" provides the following services:

**PHOTOSTAT COPIES:** \$3 per project, or \$3 per part where a project spreads over multiple issues (price includes postage). Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

**CHASSIS DIAGRAMS:** for the few projects which require a custom metal chassis (as distinct from standard cases) dyeline plans showing dimensions are normally available. \$3 including postage.

**PC BOARD PATTERNS:** High contrast, actual size transparencies. \$3, including postage. Please specify positive or negative.

**PROJECT QUERIES:** Members of our technical staff are not normally available to discuss individual projects, either in person at our office or by telephone.

**REPLIES BY POST:** Limited to advice concerning projects published within the last three years. Charge \$3. We cannot provide lengthy answers.

undertake special research or discuss design changes. Nor can we provide any information on commercial equipment.

**OTHER QUERIES:** Technical queries outside the scope of "Replies by Post" and/or submitted without fee may be answered in these pages, at the discretion of the Editor.

**COMPONENTS:** We do not sell electronic components. Prices and specifications should be sought from advertisers or agents.

**BACK ISSUES:** Available only until our stocks are exhausted. Within six months of publication, face value. Seven months and older, if available, \$2 (includes storage fee). Post and packing 70c per issue extra.

**REMITTANCES:** Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

**ADDRESS:** All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

practice, while negative ion generators may use simpler circuits, it is very difficult to avoid production of ozone which is undesirable. We have no plans to publish a design for such a device.

**TV-CRO ADAPTER:** My son is experiencing considerable difficulty in getting a project to work. It is the TV-CRO adaptor on page 42 of the May 1980 edition of Electronics Australia. I have had it examined by a radio mechanic who reports as follows: "tracing the circuit through with a CRO, all is working correctly as though the project should work. A logic probe was used, all appears OK."

"A frequency meter revealed that the horizontal oscillator is running at 10 times its correct frequency, and the vertical oscillator runs at twice its correct frequency, there is no way the sync circuit can line up the trace with these conditions appearing."

If there was an error it would normally be corrected in a later issue but my son says a friend of his made the project which appears to work OK. As we are completely confounded I thought we'd write to you to seek your advice on how to get the ingenious device working. (E. N., ACT).

● The correct frequencies for the vertical and horizontal oscillators, IC7 and IC6, are 50Hz and 15625Hz respectively. These frequencies can be adjusted over quite a large range by adjusting the 100k trimpot connected to pin 7 of IC7 and the 100k potentiometer connected to pin 7 of IC6. If you are still unable to obtain the correct operating frequency the capacitors in each oscillator can be changed, although this should not be necessary.

The horizontal oscillator capacitor is a .001 $\mu$ F connected to pin 2 and 6 of IC6, while the vertical oscillator capacitor is 0.1 $\mu$ F and is connected to pin 2 and 6 of IC7. Increasing the values of either capacitor will decrease the horizontal or vertical frequency and decreasing them would increase the frequency.

Note however that even if these frequencies were not correct you should get some sort of signal display on the TV screen.

**ELECTRODYNAMIC LOUDSPEAKER:** I recently discovered an old speaker which seems to be in good condition. It is a Rola model F12 2500 $\Omega$  with a transformer mounted on it. The transformer has 7000 printed on it but nothing else. What I wish to know is how can this speaker be used with an amplifier which requires 8 $\Omega$  and if it is worthwhile to do so. Having no permanent magnet on it and four input wires I assume it is an electro-magnet sort of arrangement. Is this correct? (R. C., Seymour, Vic).

● You have found a component which is truly obsolete. It is an electrodynamic loudspeaker which has a separate magnet winding intended to be energised from the high tension rectifier of a typical valve radio of the mid-thirties to early forties. In fact, the magnet winding functioned as a filter choke for the high voltage supply.

To use it these days you would need a power supply capable of supplying around 150 volts DC at up to 60 or 70 milliamps. It would be cheaper to use the speaker for a non-electronic purpose such as a door-stop.

# MARKETPLACE

## FOR SALE

**DREAM 6800** "How To Get The Most Out Of Your Dreams". A comprehensive breakdown of CHIP 8 instructions together with some Machine Code programs as an aid in using your DREAMS \$10.

**DREAM SOFTWARE** Random Tatstlotto Selection \$3, Naughts & Crosses \$3, TV Drawing Pad \$3, Memory Modify/Display routine in machine code \$5. Send cheque/money order to T. Huett, PO Box 520, Woodridge 4114.

**AMIDON CORES** — Large range of ferromagnetic cores for all receiver and transmitter applications. Send large SASE for data/price list to: RJ & US Imports, Box 157, Mortdale, NSW 2223.

**LEVEL TRANSMITTER, LAB INSTRUMENT.** 10kHz — 10MHz, Wandel & Goltzmann appears usable as sig. gen. \$80. Tape reader "Tally" suit computers, \$60 AC output at 1A, \$70 Melb 458 2580.

**OTHELLO:** Challenge your Level II System — 80/TRS — 80 to this intriguing game of strategy. For tape & listing send \$5 to G. Lawrence Box 191, Heidelberg, Vic 3084.

**CB & HAM DISPOSAL SALE** AM fr \$39 SSB fr \$109 Rigs all types coming in daily PARK DISPOSALS 32 Park St, Sydney 2000. Ph (02) 264 7515.

**LEARN THE EASY WAY** Cassettes, Basic Electronics, Communications, Basic Astronomy, Radio Astronomy. \$6 each. \$1 P&P Wallace, PO Box 363, Wauchope, NSW 2466.

**PRINTED CIRCUIT BOARDS** made to customers own layout. Enquiries, cost etc, write PO Box 272, Edgecliff, NSW 2027 or Telephone (02) 358 6342, Sydney.

**TRS — RACING SYSTEM** level 1K. Let your computer select winners! Full documentation, program tape, certified data tape. Send \$45 cheque money order to Softsell, Box 1173, Dubbo, NSW 2830.

**QUALITY CASSETTE SOFTWARE** for OSI CHALLENGERS. Write for full details to Computer Cottage, Box 455 Charters Towers 4820.

**KT9500 2650** with CBUB/PIPBUG 150, 1 and 2MHz crystals \$5. 78up10 with 6K Ram \$50. EA cassette interface \$15. 79up1 Eprom burner \$15. D Murphy, Flat 1/24 Chatsworth Rd, Greenslopes, Qld.

**GREEN SCREENS.** Microcomputer owner, operators, enthusiasts, no more blood shot eyes, no more eye strain, no more eye fatigue. With our easy to install Green Screens, no drilling or screwing. TRS-80 Early VDU (Squarish) \$11.99 TRS-80 Later VDU \$14.99 With some ingenuity can fit almost any 30cm (12") VDU. Enquiries welcome for any other sizes, discount for quantity (please state). Give your computer the professional look! Send your cheque or money order (sorry no COD) to "Experienced Technical Services Pty Limited", Box 114, PO Merewether, NSW 2291.

## CLUBS

**CALLING ALL SHORTWAVE DXERS,** see what the Australian Radio DX Club has to offer you. Special membership fee for people under 18. New member kit upon joining Australian DX News averages over 25 pages each month. Latest news on Shortwave, Mediumwave & Utility Dxing. For full details write to ARDXC including a 22c stamp to PO Box 79 Narrabeen, NSW 2101 mentioning this ad.

**SHORTWAVE LISTENERS & DXERS:** "Southern Cross DX Club incorporated", GPO Box 336, Adelaide, South Australia 5001, is Australia's national friendly DX Club! 1st year subscription (incl \$2 joining fee) is \$10. Students under 18 & pensioners pay \$8. Write for full detail of membership and a FREE copy of our monthly publication with latest news & tips from Amateur & broadcast band to: Grantley Williams, 19 Wicklow Av, Athelstone (Adelaide), SA 5076

**DISPLAY ADVERTS IN MARKETPLACE** are available in sizes from a minimum of 2cm x 1 col rated at \$12 per col cm.

**Please state classification:** For Sale, Wanted, Reader Service, Position Vacant, Position Wanted, Business For Sale, etc . . .

**CLASSIFIED RATES** \$3 per line per insertion payable in advance. Minimum two lines.

**CLOSING DATE** is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

**ADDRESS** all classified orders, copy, enquiries, etc. to: The Advertising Manager, **ELECTRONICS AUSTRALIA**, Box 162, Beaconsfield 2014.

## FOR HIRE

**MICROCOMPUTERS FOR RENTAL.** Commodore PETs (8k) at \$25 per week (minimum period 1 week). Software tapes and manuals included, plus BASIC instruction course and book. David B. Bates Microcomputer Consultant, Ph (02) 630 8652.

## COLUMN 80 from P121

compilers still have their place, particularly where it is most important that a program runs at the maximum possible speed.

In fact compilers shouldn't really be regarded as an alternative to interpreters. They can be used to complement one another. You can use an interpreter to develop your program and get it fully debugged, then turn to a compiler to produce the final "full speed" version.

Needless to say, to do this you have to have a compiler which matches the interpreter you are using. Unfortunately as yet there aren't too many compiler equivalents to the popular BASIC interpreters, but with luck these will appear soon.

## SONY PS-X75 from P38

Waveform of sine and square waves was commensurate with those obtained from upper-middle price range cartridges.

Sound quality of the XL-25A was good, although a minority of buyers may wish to acquire another headshell and instal a more expensive cartridge.

In summary, we really could not fault the operation of this record player — it operates silently and treats records gently. It is a unit which can certainly take its place in the top echelon of automatic turntables.

Recommended retail price of the Sony PS-X75 is \$649. Further information can be obtained from high fidelity retailers or from Sony (Australia) Pty Ltd, 453-463 Kent St, Sydney, NSW, 2000.

## EA Magazine Holders



The binders and magazine holders are available over the counter from Electronics Australia, 57 Regent Street, Sydney, NSW — Price: \$5.10 binders, \$4.50 holders.

Mail orders should be sent to Electronics Australia, PO Box 163, Beaconsfield, NSW 2014

Prices including postage are:

Holders: \$5.40 NSW; \$5.50 other states; or six for \$28.30 NSW, \$30.40 other states, A\$32NZ.

Binders: \$6.20 NSW; \$7.90 other states; or six for \$32 NSW, \$34 other states, A\$36.60 NZ.

<p><b>BRASS SHIPS CLOCKS</b> SMITHS 8 DAY 7 INCH DIAMETER \$110</p> <p>Post A \$175; B \$300; C \$360.</p>	<p><b>SOLENOIDS</b> 200 MA 24 volt. 1/8in push movement. \$2.50 P+P 80c</p> <p><b>NIFE CELLS</b> 1.2 volt, fully charged, 4in x 3in x 1in 4 AH \$1.50 each P&amp;P 80c.</p>	<p><b>POSTAGE KEY:</b> A NSW B Vic Qld. SA Tas C NT D WA</p>	<p><b>WRIST WATCHES</b> <b>SWISS JAEGER</b></p> <p>Le Coultre ex RAAF rated one of the world's best in smart chrome case with black dial. Original cost \$250</p> <p><b>SPECIAL \$49.50</b> Post \$1.30</p>
<p><b>GENUINE EX ARMY WRIST WATCHES</b> Complete with nylon band \$19.50 Post \$1.10</p>	<p><b>CENTRE DRILLS</b> 15/64 x 15/64 Carbon steel \$4.00 doz. Post 60c</p>	<p><b>VALVES</b> <b>BRAND NEW</b> 6SN7 \$1.95 6BM8 \$1.95 5U4 \$1.95 6GV8 \$1.95 EF50 \$1.50 6AK5 \$1.95 1H6 \$1.50 2x2 \$1.50 832 \$5.00 P+P 80c</p> <p>6x4 \$1.95 VR65 \$1.50</p>	<p><b>PRISMATIC TELESCOPES</b></p> <p>15 x 50 Ex RAN — black enamelled brass. Length 16". weight 5kg Price \$39.50</p> <p>\$2 cartage to rail, freight payable at nearest attended railway station</p>
<p><b>CHASSIS PUNCH SET</b> For perfect holes in metal Cuts holes 3/8" 1/2" 5/8" 1" 1 1/8" With tapered reamer size 3-14mm <b>\$37.95</b> P + P A \$1.95 B \$3.25 C \$3.65 D \$3.65</p>	<p><b>ARTILLERY DIAL SIGHTS MK2</b> Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 5 1/2" diam gunmetal rotating circle. Ad- justable elevation and depression. Has top grade 1/2" diam object lens. F.L. 10" with cross hairs, eyepiece, 1/2" right angle prism — height 10" — weight 3 1/2kgs. With leather carrying case. Original cost \$300 Our Special only \$27.50 P&amp;P A \$2.25 B \$4.00 C \$6.00</p>	<p><b>STC HIGH IMPEDANCE HEADPHONES</b></p> <p>3400 ohms, brand new, only \$5.95 pair. P&amp;P A \$1.65 B \$2.75 C \$3.10</p>	<p><b>ZOOM FOCUSING MICROSCOPES</b></p> <p>Zoom focusing microscopes battery and mirror illuminated 750 x \$31.75 1200 x \$47.95 P&amp;P A \$1.65, B \$2.75 C \$3.10</p>
<p><b>RECEIVER No. 210</b> 2-16 M/cs \$75 Transmitter No. 11 suits 210 \$35 24 volt Power supply to suit above \$15. Or complete station with Headphones. Mic \$110.</p>	<p><b>ZOOM SPOTTING SCOPES</b></p> <p>30 x 30 LENGTH 12 1/2", HEIGHT 10" WEIGHT 1 3/4 lb <b>\$32.50</b></p> <p>High grade coated lenses Ideal for pistol and rifle ranges or general viewing. Zooms in from very low to high powers. Complete with tripods. POST A \$1.75 B \$3.00 C \$3.60</p>	<p><b>TELESCOPES</b> 25 x 30 \$13.50 P&amp;P A \$1.30</p>	<p><b>DIRECTOR LEVELS</b></p> <p>Ex Army No 9 with azimuth horizontal circle and vertical adjustment suits all types of levelling in leather case <b>\$95</b> P + P A \$1.75 B \$3 C \$3.60.</p>
<p><b>EX ABC MAGNETIC RECORDING TAPES 1/4"</b></p> <p><b>PROFESSIONAL QUALITY</b> 5" x 600 \$1.50 7" x 1200 \$2.75 P + P \$1.30 10 1/2" x 2400 \$7.95 P + P A \$1.65 B \$2.75 C \$3.10</p>	<p><b>SPY TELESCOPES</b> 8 x 17 mag size of a rifle cartridge ex- tends to 8" Only \$8.95 each, post 60c</p>	<p><b>CONDENSER LENS</b> 2 1/2" diam 2" FL \$1.50 each or \$2.50 per pair P&amp;P 80c</p>	<p><b>CLINOMETER MK6 0° TO 45°</b></p> <p>Precision calibrations set in solid gunmetal frame spring ratchet ad- justment. Approx size 7" x 6". Complete in wooden case <b>\$37.50</b> P + P A \$2.15, B \$3.85, C \$4.85, D \$4.85</p>
<p><b>COLLINS INDEPENDENT SIDE BAND TRANSCEIVER TRC/75</b></p> <p>Fully synthesised transceiver with am- upper, lower and independent sideband operation, 1KHz steps from 2MHz to 29.999MHz 1 microvolt sensitivity, 2.5KHz bandwidth ssb 6KHz bandwidth AM 1 RW PEP max output. Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc. 400Hz supply Ideal for amateur use. <b>PRICE \$750</b></p>	<p><b>AIRCRAFT INSTRUMENTS</b> Directional Gyros AN5735-1 Air Operated. <b>\$35</b> Slip and Turn Indicators <b>\$17.50</b> P&amp;P A \$1.65, B \$2.75 C \$3.10</p>	<p><b>IMPELLER PUMPS</b> New gunmetal body, Stainless Steel Shaft, Neoprene Impeller Up to 15ft Lift, suitable for almost any type of liquid Self priming Ideal boat bilge pump, sul- lage drains, etc. Approx size 8" x 5" 3/4" \$35.75, 1/2" \$61.00, 1/4" \$68.60. P+P A \$1.95, B \$3.50, C \$4.60</p>	<p><b>ROLA 77 MK 3 PROFESSIONAL TAPE RECORDERS</b></p> <p>Ex ABC In Good Working Condition 7 1/2 and 15 IPS Original Price \$2,500 Special \$650</p>
<p><b>COLLINS SYNTHESISED 1 SB RECEIVER</b></p> <p>TRC/75 receiver section of transceiver specification as above <b>PRICE \$400</b></p>	<p><b>SMALL CLIP-ON POCKET TELESCOPE</b> 15X \$7.00. P+P 80c</p>	<p><b>Liquid filled compass</b></p> <p>With magnified lens sight and degree reader. Only \$7.95 each Post \$1.30</p>	<p><b>16MM SOUND PROJECTORS IN GOOD WORKING ORDER</b></p> <p>BELL &amp; HOWELL \$250 \$1 Cartage to Rail Freight payable at nearest attended Railway Station.</p>
<p><b>TELEPHONE WIRE</b> 1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$45.00 per drum. \$5.00 cartage to rail freight payable at destination.</p>	<p><b>THEODOLITE</b> Kern Suisse Switzerland DK2 Two minute can be estimated down to one minute. Tested in good working order. \$750.00</p>	<p><b>POLARITY &amp; CURRENT CHECKER</b></p> <p>3 volt to 400 volt Simple leads and prods quickly determines positive or negative with illuminated indicators, also checks AC current and intensity, fully insulated only \$4.95, pp \$1.30</p>	<p><b>SELSYN MOTORS MAGSLIP</b></p>
<p><b>3" ASTRONOMICAL REFLECTOR TELESCOPE</b></p> <p>117 X MAGNIFICATION FL 700MM WITH 5 X 24MM FINDER SCOPE AND TWO SECTION HARDWOOD TRIPOD. <b>\$169.25</b> P&amp;P A \$2.25 B \$4.10 C \$6.10</p>	<p><b>BINOCULARS</b> PRISMATIC Coated Lenses. Brand new Complete with case. 8 x 30 \$42.00 7 x 50 \$48.95 P&amp;P 10 x 50 \$51.00 A \$1.75 12 x 50 \$53.00 B \$3.00 20 x 50 \$65.00 C \$3.10 20 x 65 \$130.00 8x to 17x Zoom \$150</p>	<p><b>MACHETES, genuine ex-army, brand new with bakelite handle and canvas scabbard, only \$8.</b></p> <p>P&amp;P A \$1.55 C \$3.10 B \$2.75</p>	<p><b>TRANSMITTER 3" MK2 \$17.50</b> Post Packing A \$1.75, B \$3.00, C \$3.10</p>
<p><b>AERIAL CAMERAS</b> WITH 8" FL 3" DIAM. LENS F24 MARK IV 2.9 LENS STOPS 11, 8, 5.6, 4, 2.9 — \$75 \$2 cartage to rail freight. Payable to nearest attended railway station</p>	<p><b>MAGNESIUM DRY CELL BATTERIES</b> Suits PRC25 and dozens of other uses. 15 volts long life. Only \$1.50 each P &amp; P A \$1.35, B \$2.75 C \$3.60.</p>	<p><b>ANEROID BAROMETERS</b> In brass case, made in London. \$39.50 P&amp;P A \$1.65 B \$2.75 C \$3.10</p>	<p><b>TAPE RECORDERS</b></p> <p>Rola 66 professional tape recorders (ex ABC) in good working order \$200. \$2.00 cartage to rail freight payable at nearest attended railway station.</p>
<p><b>NIBBLING TOOL</b> Cuts sheet metal like a punch and die up to 18 G.A. Cuts Trims Notches \$14.95 P + P \$1.45</p>			

**Deitch Bros.**  
70 OXFORD STREET, SYDNEY 2010

SOBRY NO COD





## MICROPROCESSORS & PERSONAL COMPUTERS

**Order your copy now!**

Microprocessors and personal computers, little more than a dream a few years ago, are now changing the face of electronics. This book introduces the basic concepts, describes a selection of microprocessor and personal computer systems, and details a build-it-yourself computer designed especially for beginners.

Available from "Electronics Australia", 57 Regent St. Sydney. **PRICE \$5.00** OR buy mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. **PRICE \$5.70.**

### ELECTRONICS AUSTRALIA

#### PRINTED CIRCUIT BOARDS AND FRONT PANELS

Some readers have indicated problems obtaining PC boards and front panels for projects. Many of our advertisers sell these items and advertisements in the magazine should be carefully checked in the first instance. Failing satisfaction from this source, the following is a list of firms to which we supply PC and front panel artwork. Some may sell direct, others may only be prepared to nominate sources from which their products can be obtained.

#### N.S.W.

Applied Technology Pty Ltd,  
1a Pattison Avenue,  
Waitara, NSW 2077.

Dick Smith Electronics,  
PO Box 321,  
North Ryde, NSW 2113.

Electronic Agencies,  
115-117 Parramatta Road,  
Concord, NSW 2137.

RCS Radio Pty Ltd,  
651 Forest Road,  
Bexley, NSW 2207.

Radio Despatch Service,  
869 George Street,  
Sydney, NSW 2000.

#### VIC.

Kalextronics,  
4 Burgundy Plaza,  
101 Burgundy Street,  
Heidelberg, Vic. 3084

Rod Irving Electronics,  
425 High Street,  
Northcote, Vic. 3070.

#### S.A.

James Phototronics,  
522 Grange Road,  
Fulham Gardens, 5024.

#### W.A.

Jemal products,  
8/120 Briggs Street,  
Welshpool, WA 6106.

#### TAS.

D & H Electronics,  
108 Campbell Street,  
Hobart, Tas. 7000.

#### N.Z.

E. H. Earl Ltd,  
PO Box 834,  
Wellington, NZ.

Marday Services,  
PO Box 19 189,  
Avondale,  
Auckland, NZ.

Mini Tech Manufacturing Co Ltd,  
PO Box 9194,  
Newmarket, NZ.

Printed Circuits Limited,  
PO Box 4248,  
Christchurch, NZ.

### ADVERTISING INDEX

A & R Soanar	72
Acoustic Electronic Developments Pty Ltd	133
Ace Radio	68, 69
Adaptive Electronics	124
Agfa Gevaert Ltd	facing 112
Altronic Distributors Pty Ltd	53
Ampec Electronics Pty Ltd	facing 113
Applied Technology	123
Associated Steel Equipment	35
Audio Engineers Pty Ltd	34
Audio Telex Communications Pty Ltd	63
BS Microcomp	134
Bright Star Crystals	98
CQ Electronics	71
Caporale, J.F.	116
Cash-More Enterprises	21
Cema (Distributors) Pty Ltd	6
Chapman, L.E.	140
Classic Radio	100
Computer Country Pty Ltd	122
Computer Imports Pty Ltd	128
Cunningham, R. H.	78
Deitch Bros	143
Dick Smith Electronic Group	18, 19, 28, 50, 57, 90
Dick Smith Electronic Group	91, 96, 120, 129
Direct Computer Retail	132
Edible Electronics	82
Electrocount Pty Ltd	36
Electrocraft Pty Ltd	77
Electronic Agencies	60
Electronic Calculator Discounts	110
Elmeasco Instruments Pty Ltd	2
Hagemeyer (Aust)	IBC
Instant Component Service	100
Instant Software	80
Informative Systems	132
JR Components	93
John F Rose Computer Service Pty Ltd	136, 137
K & L Computing Systems	125
Kalextronics	23
Logic Shop, The	127
Looky Video	23
Magnavox Australia Pty Ltd	39
Marantz (Aust.) Pty Ltd	facing 33
Mensa Computers Pty Ltd	131
Micro 80	84
Micro Pro Designs	83
Microdot	81
Northpoint Hi-Fi	117
Paris Radio Electronics	126
Pitt Street Microcomputer Centre	128
RCS Radio	27
Radio Despatch Service	46
Radio Parts Group	73
Rod Irving Electronics	45, 58, 75, 109
Rothmans of Pall Mall (Aust.) Ltd	OBC
Royel Microsystems Pty Ltd	130
Roysten Electronics	77
SM Electronics	87
Sinclair Equipment	24, 25
Scope Laboratories	11
Software Source	130
Sony (Aust.) Pty Ltd	IFC, facing 32
Standard Components Pty Ltd	46
Stanton Magnetics Inc.	30
Stotts Technical College	67
Systems Solutions	133
Tandy Electronics	62
Technical Book & Magazine Co.	119
Technico Electronics	101
Vicom International	17, 99
Video Technics	115
Warburton Franki	12
Wireless Institute of Australia	101

## SUBSCRIPTION SERVICE



**ELECTRONICS  
Australia**

#### Subscription Rates

**\$21.00 per year  
within Australia  
\$25.00 per year  
elsewhere.**

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon with your remittance to Electronics Australia Subscription Dept. John Fairfax & Sons Ltd. GPO Box 506 Sydney 2001. Subscription will start with first available issue.

Name . . . . .  
Address . . . . .  
Postcode . . . . . Enclosed is . . . . . for . . . . . years

# UNTIL WE DEVELOPED THE STEREO GROOVE, HI-FI WAS PRETTY HO-HUM!



The world of hi-fi owes a lot to the original and continuing innovation of JVC. Few companies, if any, have done as much to help turn records and record-players into the virtual musical instruments they are today . . . or to lead the way in developing so many *firsts* in the more recent concepts of sound amplifiers, cassette decks and computer-designed speaker

systems. Hi-fi, as we know it today, had its beginnings in 1956, with JVC's development of the 45°/45° groove for stereo records. The fact that this system still remains as the world standard is, in itself, outstanding testimony to the technology of JVC. The development revolutionised not only the record-making industry, in which we've been involved since 1930; it also paved the way for enormous advancement in the design and engineering of record-playing equipment. Now, hi-fi has expanded to



R-S77. Super-A FM/AM Stereo receiver

embrace a wealth of highly-sophisticated electronic equipment; and it's not surprising that JVC has continued to play a leading role in so much of its development.



HR-3660 EA. VHS Colour Video Cassette recorder

## THAT WASN'T OUR ONLY FIRST, EITHER.

We also pioneered Japan's television industry, introducing their first TV receiver just over 40 years ago. A more recent innovation is VHS, the home video recording system now gaining world-wide acceptance as *the* system for such equipment. In the course of staying ahead, we've introduced a number of world *firsts* of radical importance: the Quartz Lock turntable is one of them.

## THE QUARTZ LOCK TURNTABLE. MANY TIMES MORE ACCURATE.

It stands to reason that if your equipment is at the top end of the range, then your turntable must be capable of comparable performance. Only Quartz Lock ensures this, tying the speed of the turntable to the unvarying pulse of the atom, and providing a level of accuracy far in excess of conventional turntables.



## MORE MILESTONES IN HI-FI.

To match the superb quality of Quartz Lock, we produced the S.E.A. graphic equalizer system. Then we refined it to such a degree it even compensates for the effect your furniture has on sound when it leaves the speakers! To expand the capabilities of tape, we designed ANRS and



SEA-80. Stereo Graphic Equalizer

Super ANRS — automatic noise reduction systems which not only reduce distortion and 'hiss' but actually extend the dynamic range of the tape. Similarly, with speakers: at JVC we employ computers in their design to help provide the ultimate in sound reproduction.

## AND NOW, SUPER-A.

In its own way, as significant a hi-fi development as the stereo groove. Imagine an amplifier which combines the *best* features of the two recognised amplifier classes (A and B) . . . an amp which combines the *efficiency* of one with the *low distortion* of the other. Some engineers said it couldn't be done; but not those at JVC. Enter the Super-A amplifier . . . the *latest JVC first!*

Distributed and Serviced by . . .

**HAGEMEYER**



the right choice

## THE FUTURE.

It's already with us. For instance, we were so far ahead in the new metal tape technology that our cassette decks were metal-compatible before the tapes were generally available. And now there's the JVC Electro-Dynamic Servo Tonearm, damping tonearm resonance by means of a purely electronic system and two 'thinking' linear motors. Who was it who dubbed JVC, 'the innovators'?

SETTING THE PAGE IN MODERN SMOKING

# PETER STUYVESANT EXTRA MILD

THE  
INTERNATIONAL  
PASSPORT  
TO SMOKING  
PLEASURE



Peter Stuyvesant Extra Mild has what  
mild smokers the world over want right now.  
Mild choice tobaccos. Miracle Filter.  
King Size. So much more to enjoy!

LIGHT UP A STUYVESANT—YOU'LL BE SO GLAD YOU DID