

Australia's Top Selling Electronics Magazine

Registered by Australia Post —
publication No. NBP 0240

Electronics Australia

June 1985

Aust \$2.60

NZ \$3.50



■ RALLY COMPUTER

Slot car timer/lap counter

High-voltage
insulation
tester

Multi-band
trapped
antenna

Bridge adaptor
for amplifiers

REVIEWS:

Mitsubishi DP-205 CD player
Kenwood 780 cassette deck

The one you can't afford not to own!

AQUARIUS™

The REAL computer that starts from under \$100! You'd love to learn about computers? But thought all you could buy for your money were a few boring games. Now, we are the EXCLUSIVE Australian distributors of the new Aquarius. Not the "Claytons" computer but the perfect beginner's computer which gives you the opportunity to see what a real computer does.

Learn how to RUN YOUR OWN PROGRAMS in the Basic language! PLAY GAMES! Organise your HOUSEHOLD FILES! And much much more!

Simply connect the Aquarius to any colour TV and it's ready to teach and entertain the whole family. There's something for everyone. And what's more, you won't outgrow the Aquarius! As you need to

learn more, the Aquarius offers a huge range of add-ons that will take you into the world of electronic wizardry once offered only by the BIG ones.

With a full moving-key keyboard Aquarius is truly EASY to USE. Microsoft BASIC computer language is built right in! The easy-to-read manual and simplified instruction cards make learning a snap.

CREATE your own VISUAL EFFECTS with 16 colours and 256 built-in characters or design your own sound effects! Once you start to expand your Aquarius with the huge software and hardware range you'll find endless uses and possibilities for your system. With it's own mini expander, data recorder, memory expansion cartridges and thermal printer you'll soon wonder what the Great

Computer Secret was all about!

FANTASTIC SOFTWARE RANGE

With more than two dozen fantastic games and educational programs available now and many being developed to add to the range shortly, there's just no end to the versatility of Aquarius. Software cartridges just plug into your Aquarius and you're ready for work or play. All software programs are available separately so you can purchase only those which interest you.

AQUARIUS with built in 2K memory (expandable to 34K) and its long list of expansion units and software is the REAL computer for the price of a TOY!

1. MINI EXPANDER

Adds versatility to your AQUARIUS. Game playing is easier and more exciting with 2 detachable hand controllers and additional sound channels. Also has 2 cartridge ports so you can plug in your expanded memory cartridge into one even while you're using software in the other.

Cat X-6005 **\$69**

2. DATA RECORDER

Save your own program or utilise one of the many great software programs available on cassette with this great value unit.

Cat X-6010 **\$49**

3. MEMORY EXPANSION CARTRIDGES

16K or 32K memory cartridges give you far greater flexibility by giving your computer a much larger memory. For more advanced programming.

16K Cartridge Cat X-6015 **\$69**

32K Cartridge Cat X-6020 **\$129**

4. THERMAL PRINTER

Ideal for documenting programs, keeping records or printing charts and records. You'll probably never again see one at this price!

Cat X-6025 **\$129**

Paper roll to suit. Cat X-6026 **\$350**

Aquarius Colour Computer

Cat X-6000

**Fantastic
Value
ONLY**

\$99





Dick Smith Electronics Pty Ltd

COMPUTERSTOP



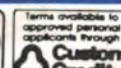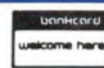Your one stop computer shop at your nearest Dick Smith Electronics centre.



A-923

THIS MONTH'S COVER

Good navigation is vital for rallying. Our new Rally Computer has all the features of a well-known commercial unit, yet can be built for a fraction of the cost. Build it and you won't get bushed — see page 42. (Photo Greg McBean).

Electronics Australia

Volume 47, No. 6

June 1985

Features

- 16 THE X-RAY SPECTROMETER *How it works*
- 98 EA CROSSWORD PUZZLE *And the solution for May*
- 110 OBITUARY *Bill Moore, VK2HZ*
- 119 COMING NEXT MONTH *Infrared remote control*
- 120 50 AND 25 YEARS AGO *Hot movies, television violence*

Hifi, Video and Reviews

- 24 BAFFLES, BOFFLES, BOXES AND VENTS *The whys & wherefores*
- 36 HIFI REVIEW *Mitsubishi DP-205 compact disc player*
- 38 HIFI REVIEW *Kenwood KX-780 3-head cassette deck*

Projects and Circuits

- 42 BUILD THIS RALLY COMPUTER *Three road counters plus a clock*
- 62 TIMER/LAP COUNTER FOR SLOT CARS *For fun or competition*
- 74 HIGH VOLTAGE INSULATION TESTER *Checks for leakage*
- 82 CIRCUIT AND DESIGN IDEAS *Zener/diode tester*
- 86 BRIDGE ADAPTOR FOR STEREO AMPLIFIERS *Low cost, easy to build*
- 90 OP AMPS EXPLAINED PT.15 *Power supply requirements*
- 100 AN ANTENNA FOR THOSE OTHER BANDS *Easy to build and erect*

Personal Computers

- 112 DAISYWRITER PRINTER REVIEW *Has graphics capability*

Columns

- 30 FORUM *RSI: real or imaginary?*
- 52 THE SERVICEMAN *Revamping a motel TV system*
- 114 RECORD REVIEWS *Classical, popular & special interest*

Departments

- | | |
|--------------------------|------------------------|
| 3 EDITORIAL | 104 NEW PRODUCTS |
| 6 NEWS HIGHLIGHTS | 122 INFORMATION CENTRE |
| 12 LETTERS TO THE EDITOR | 126 MARKETPLACE |
| 102 BOOKS AND LITERATURE | 124 NOTES AND ERRATA |

Rally computer for cars



This Rally Computer boasts three independent road counters and a quartz clock. Best of all, it's easy to build and use. Details page 42.

What's coming

1000V Megohm Meter: featuring an inbuilt transistor inverter, our new Megohm Meter tests at 1000V and covers the range from 2M Ω to 2000M Ω . It is particularly handy for checking electrical wiring. See also page 119.

High voltage insulation tester



Build this high voltage insulation tester and check for insulation breakdown at 500V DC. It tests for 10G Ω insulation resistance and gives a much more realistic indication than a multimeter. Construction begins on page 74.

||||| Plus/4 |||||

Introducing Software That Comes With Its Own Built-In Computer



Word processing, electronic spreadsheet, graphic plotting and file management certainly need no introduction.

But a computer that has them all built-in certainly does.

Especially for under \$600*.

You could easily say the built-in software alone is worth a lot more than the price.

But then again you could easily say the Commodore PLUS/4 computer alone is worth a lot more than the price. With 64K of memory, 60K fully usable, full size typewriter keyboard, four separate cursor keys, high resolution colour graphics, extended BASIC, split screen and windowing capabilities.

Turn on the power and judge for yourself. Write and edit letters, reports, papers and novels with the built-in wordprocessor. Do the books, the budgets, the projections, profit/loss

statements with the built-in spreadsheet. Draw circles, boxes, complex shapes, images and combine them with text with the graphics program. Collect, store, organize and retrieve information such as mailing lists, inventories, personal files, business files and recipes with the file management program.

Go from one program to another at the touch of a key. For not only are they built into the computer, they're built into each other. So, for example, in one document, you can go from words to numbers to graphs to names and addresses. In just a matter of moments.

The Commodore PLUS/4. The first new computer that doesn't have one new thing about it. It has four.

For further information contact your nearest Commodore Dealer.

*Recommended retail price

commodore
COMPUTER

Keeping up with you.

Commodore Business Machines Pty. Ltd. New South Wales: (02) 427 4888
Victoria/Tasmania/South Australia: (03) 429 9855 Western Australia: (09) 389 1266 Queensland/Northern Territory: (07) 393 0300

BMS/CC365

EDITOR

Leo Simpson
B. Bus. (NSWIT)

ASSISTANT EDITOR

Greg Swain, B.Sc. (Hons. Sydney)

EDITORIAL CONSULTANT

Neville Williams
F.I.R.E.E. (Aust.) (VK2XV)

TECHNICAL STAFF

John Clarke, B. E. (Elect. NSWIT)
Colin Dawson
Robert Flynn
Andrew Levido
Louise Upton, B.A. (Hons. Sydney)

ADVERTISING PRODUCTION

Danny Hooper

ART DIRECTOR

Brian Jones

SECRETARIAL

Christine Millar

ADVERTISING MANAGER

Selwyn Sayers

MANAGING EDITOR

Jamieson Rowe

PUBLISHER

Michael Hannan

Editorial and Advertising Office 140 Joynton Avenue (PO Box 227), Waterloo, NSW 2017. Phone: (02) 663 9999. Advertising Sales Manager. Sel Sayers. Representative: John Oliver.

Melbourne: 23rd Floor, 150 Lonsdale Street, Melbourne, Vic 3000. Phone (03) 662 1222. Representative: Laurie Gross.

Adelaide: Charles F. Brown & Assoc. Phone (08) 332 7711. Representative: Sandy Shaw.

Brisbane: Media Services Pty Ltd, 4 Adelaide Terrace, Brisbane 4000. Phone (07) 229 6033. Representative: Fred Maybury.

Perth: Adrep, 62 Wickham Street, East Perth, WA 6000. Phone (09) 325 6395. Representative: Cliff R. Thomas.


Distribution: Distributed by Gordon and Gotch Limited, Sydney.

Registered by Australia Post — publication No. NBP0240. ISSN 0313-0150

Printed by Magazine Printers Pty Ltd, Regent Street, Chippendale and Masterprint Pty Ltd, Dubbo, NSW for The Federal Publishing Company Pty Ltd.

*Recommended and maximum price only.

Copyright. All rights reserved.

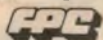

Editorial Viewpoint



by Leo Simpson

Star Wars: pie in the sky!

So the Europeans gave the elbow to President Reagan's Star Wars concept, or to give it its official name, "Strategic Defence Initiative". Not surprising, really, since the Europeans seem to have less money to throw around than the Americans. But just because the Europeans have poured cold water on the scheme and refuse to be involved does not mean that we have heard the last of it.

There seem to be two main drawbacks to the Star Wars concept. The first is doubt about its practicability. This has several aspects. For example, to be completely effective, the system has to be able to log on to hundreds of missiles (in an all-or-nothing attack this is what would happen) and destroy all of them while they are still in the stratosphere. If it misses just a few multi-warhead missiles, then the system will have failed miserably and we will all be up the creek.

Destroying the missiles is a bit of a problem too, because an enormous amount of laser power has to be focussed onto the moving target to disrupt its electronic guidance systems or otherwise render it unusable. The necessary laser energy may well be available from earth-based power stations or nuclear powered satellites, but the defence against this form of missile damage may be as simple as a coat of reflective paint!

The other drawback is that even if the system does prove to be completely effective in destroying missiles in an all-out attack, there is a strong possibility that the Russians may simply build up other means of attack such as nuclear submarines and cruise missiles. Whatever happens, it is likely to lead to yet another round in the weapons build-up.

Such arguments about practicality unfortunately don't have much effect in stopping this sort of weapons development. A weapon doesn't have to be practical in order to be eventually developed into a potent system. A prime example of this was the hydrogen bomb which certainly was not practical in its original concept. It was crazy. In effect, Edward Teller and his crew had to build a 12-ton refrigeration plant in order to make the first bomb work. Naturally, the whole plant was vapourised along with the bomb! But that was the sort of trouble the scientists were prepared to take to prove the concept.

If you think that sort of thinking is not in vogue today, some 30 years after the hydrogen bomb was developed, think again. Edward Teller is still around and has been one of the defence advisers to President Reagan.

The real danger about the Star Wars concept is that it could indeed be developed into an effective system. The past record of the USA shows that. As such, it may tempt the USA into thinking that it could win a nuclear conflict. Or the Russians may think that is what the USA perceives. And that is an extremely dangerous situation for all of us.

The really sad part about the Star Wars concept is not that it is an outlandish scheme devised by some extremist politicians and generals, but that there are plenty of scientists and engineers around who are willing to do their best to make it work. They won't be making the world any safer or better, for any of us.

You'll save a fortune with

DSE KITS



FANTASTIC! \$439

Playmaster series 200 Hi fi Mosfet Amplifier

This is the one you've been waiting for. The all-new Playmaster Series 200 Integrated Amplifier is almost certainly the best build-it-yourself design to be published anywhere in the world! Feature for feature, dollar for dollar, it more than stacks up against the 'big names' in hi fi - with the big price tags to match.

And it has features that aren't even found on many of the 'names'. Features like electronic input switching. Circuitry to handle just about every input imaginable: moving magnet, moving coil, CD player, hi fi VCR, cassette, tuner, etc etc etc. Plus, of course, incredible 'headroom' with 100 watts per channel output power. And much, much more!

And don't forget the exclusive Dick Smith Electronics kit features:
 • Solder-masked and silk-screened PCB to help eliminate errors.
 • Power transformer with factory-wound low voltage winding (why wind by hand?).
 • Special step-by-step construction manual • complete with our 'Sorry Dick, it doesn't work' repair service.
 • PLUS our exclusive satisfaction guarantee: you can return the kit within 7 days if you think construction is beyond you!

Cat K-3516

4 Sector Home Alarm

Once upon a time, we had a kit for a simple alarm. Then everyone started asking for an all bells and whistles kit. So we brought out the EA 8 sector alarm kit. Now it seems everyone wants a simpler kit again!!!

Here it is: designed by Dick Smith Electronics Research and Development division to suit the requirements of the majority of users.

- Features instant or delayed inputs
- Wire-out-proof system - suitable for all types of sensors
- LED sector and control state indication
- Adjustable entry, exit and alarm periods

Short form kit - suits 'building in' to whatever you like!

Easy to build - and could save your property!
 Cat K-3254



Short form kit
 Does not include case


\$49

UHF Power Amplifier

\$129

Now a power amplifier for UHF AMATEUR AND CB radio. A very healthy 25 watts output from virtually any UHF input (from around 300mW or so.) And that could make the difference between being heard and...

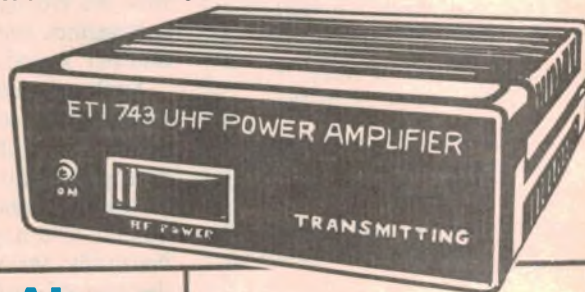The amplifier kit is complete to the last nut and bolt - including the same deluxe case used in our UHF amateur transceiver, and its matching power supply. So now you can build a matching amplifier too! Cat K-6314



Mixer Preamp

Designed to suit the 300W amp kit, this mixer preamp has 4 inputs with an impedance of 100K - suitable for most microphones, guitars, etc. Ideal also for use with 50W (K-3400) and 100W (K-3442) power amp modules. This unit provides bass, treble and presence control. Instructions supplied.

Short form kit: no case, transformer or power supply.
 Cat K-3035

\$32⁹⁵

VCR Theft Alarm



WAS \$54.95

Don't let your VCR become the most talked about item behind the pub! Build this neat little kit and it will scream its head off if anyone tries to make off with your pride and joy! Cat K-3423

NOW ONLY **\$29⁹⁵**



LED TACHO

Don't spend a fortune buying a tachometer - build your own and save! Displays engine speed in an analogue form in an illuminated row of LED's. Instructions included - a great kit! Cat K-3240

\$24⁵⁰

When you build it yourself!

Earn a Fortune!

(or a few cents)

Build the Busker Amp

Easy-to-build general purpose microphone/guitar preamp & power amplifier, ready to build into a speaker case for a go-anywhere mini pal!

Ideal for the budding buskers in the family. Also fantastic for displays, fetes, rallies, etc.

Includes components, speaker but we leave the case to you (if you want to use away from power point you'll also need a 12V gell cell.
Cat S-3320

Short form kit
Does not include case



Cat K-3446

\$79⁹⁵

Stereo Enhancer

Here's a great kit for those on a space budget! If your listening area is not exactly stereo quality, the stereo enhancer will 'widen' the sound to make it sound like it's almost designed that way!

Complete kit, including special abs case together with instructions make this one a beauty to put together - and even more of a delight to use.

As described in ETI, March 1985.
Cat K-3419



\$79⁹⁵

VCR Sound Processor



Unless you're lucky enough to have one of the new hi fi videos, the sound from your VCR is probably pretty pedestrian! Now you can give it a lift with this VCR Sound Processor!

It includes an effective stereo simulator circuit, a 5 band graphic equaliser to make up for the crook audio and your (probably!) equally crook listening room plus noise filtering to get rid of tape hiss and other unwanted high frequency noise. Cat K-3422

\$49⁹⁵



Speed Controller


A completely new circuit offering unbelievable smooth control and torque - even at very low rpm. Yes, it's even better than the previous model! New design includes 'in line' plugs and sockets for extra convenience. Suits virtually all 'universal' (brush type) motors.
Cat K-3084

\$21⁹⁵

Ultrasonic Movement Detector

The problem with 99% of car alarms is that they cannot prevent the thief who breaks a window and reaches in for the goodies. While this kit won't prevent the window being broken, it will protect your property inside the car. Silent ultrasonic rays detect any movement and trigger the main alarm systems. Cat K-3251

\$19⁹⁵

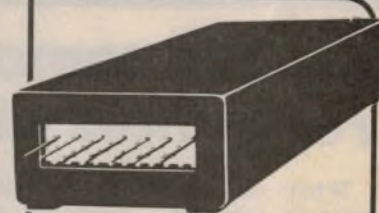

Negative Ion Generator

You've heard all about Negative Ion Generators and their benefits, now buy the kit and find out what it's all about. Many commercial units run from the mains, but our kit is safe - it runs on 12V DC, which also means that you can put one in your car! Kit includes exclusive Dick Smith emitter head, power pack and tough moulded plastic case.
Cat K-3335

\$42⁵⁰

Stereo TV Decoder

TV sound can be very high quality - especially now it's being transmitted in stereo. But 99.9% of TV sets can't take advantage of this because they're only equipped for mono sound. And 99.9% of people aren't willing to get rid of a perfectly good colour telly just to get stereo sound!

Especially when a new stereo colour TV can set you back the best part of a tidy bit! Here's the Dick Smith Electronics-low-cost-solution.
Cat K-6325




\$249

DICK SMITH ELECTRONICS

PTY LTD

See page 84
for store addresses

News Highlights

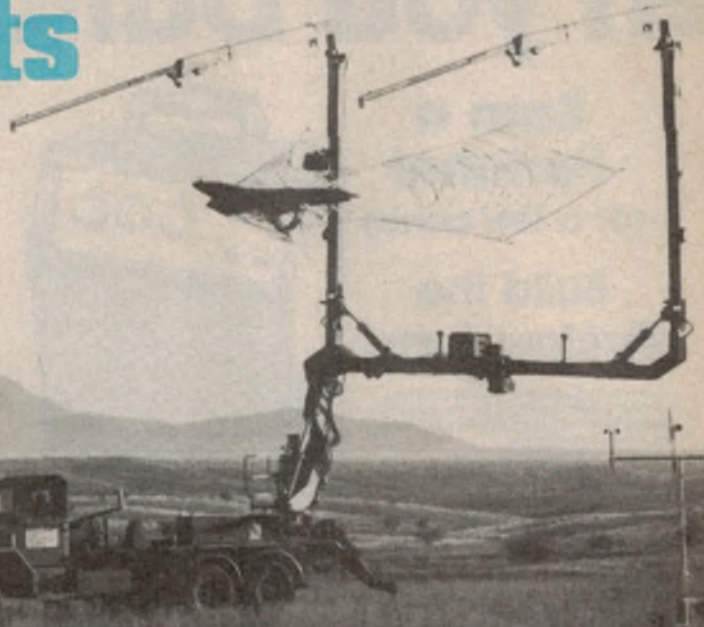

Aquila remotely piloted reconnaissance vehicle

What can the military have in common with radio controlled model aircraft enthusiasts? The answer lies in remotely piloted vehicles (RPVs) which can be used to reconnoitre areas which would be far too dangerous for manned aircraft.

One such RPV is the American Aquila (Latin for "eagle") which has been developed by the Lockheed Missiles and Space company of California. It is constructed of fibreglass, is about 2m in length with a wingspan of about 4m, and weighs in at approximately 100kg. Its

two-stroke 19.4kW engine drives a two-blade propeller, giving the Aquila a cruising speed of 150km/h and a maximum speed, in level flight, of 200km/hour. Maximum endurance is approximately three hours.

Both its body and engine size make it difficult to detect. Because of its small size, it reflects smaller radar signal levels, it is harder to spot visually and it is much quieter than conventional aircraft.

The Aquila has been designed as a recoverable vehicle. It is launched using an hydraulic catapult set on a five-tonne

truck, and recovered by flying the vehicle into a vertical ribbon-barrier braking system.

Guidance and control are vital for the success of the RPV. The Aquila carries an on-board navigation computer and an inertial package for accurate navigation and control of the vehicle. The navigation system is linked to a ground-based tracking system which periodically updates the RPV's position, thus allowing for accurate target location.

The craft contains a fully controllable video camera and the image is continuously transmitted over a secure data link to the ground control station. This provides information about possible targets, such as enemy weapon systems.

— Brian Dance.

Australia to lobby for BMAC satellite standard

Australia will be at the meeting of the International Radio Consultative Committee (CCIR) which will make recommendations on world satellite transmission standards later this year.

The CCIR as a regulatory body will be considering a major report on satellite television transmission systems. The BMAC system, which has been chosen by Australia for satellite broadcasting, forms a prominent part of this report.

Having adopted BMAC, Australia

is naturally keen to see the standard taken up by other countries as well. Work done by the Department of Communications in assessing a number of systems will give Australia a strong argument to present to the CCIR in November.

AWA extends microcircuit design capabilities

Amalgamated Wireless (Australasia) Limited has made an important software exchange

agreement with RCA. Along with this comes over \$1.5 million worth of new design equipment.

For AWA, the agreement signals a major advance in the company's microcircuit design capabilities. The software will enable engineers to simulate a circuit's electrical performance, thus reducing initial design errors and shortening lead times.

AWA is confident that custom digital integrated circuits represent a strong growth area within Australia. The RCA agreement, which also makes its CMOS digital circuit design and simulation tools available, is an important step for this growth.

Electronic ear-tags for cattle

The management of Australia's beef cattle industry could be greatly improved by using electronic means to identify livestock, according to researchers at several Australian universities.

The project, which is funded by the Australian Meat and Livestock Corporation, arose because of the need to improve traditional methods of identification.

Dr Michael Yerbury, of Sydney University's Physics Department, is contributing to the development of a "light gun" which triggers an electronic tag attached to the animal's ear.

The light gun produces a high-intensity infrared beam lasting 100 microseconds. This switches on the electronic tag which in turn sends back radio waves that are picked up by a receiver attached to the gun, decoded and displayed on a small screen. The

animal can be identified from a distance of 30 metres.

Once an animal is identified, information about it can be called up on a hand-held microcomputer or new information added to the record. This information can then be transferred to the main computer system.

The combined university research team were set certain goals in developing prototypes. The mechanism had to be robust and secure; it had to last over the life of an animal (10 years); and it had to be relatively cheap (\$2 per tag was the original target).

Two approaches have been considered: attachment to the ear and implantation under the skin of an electronic device. The latter is less developed and perhaps holds some interesting prospects for those who can imagine the possibilities of 1984-style social control.



Business Brief

Soundring Pty Ltd (PO Box 154, Cammeray, NSW 2062) has been appointed sole Australian distributor for Lenco Switzerland. Lenco manufactures a range of hifi and video equipment, including turntables, record cleaning kits, and a video enhancer.


Australia needs a silicon foundry

A senior executive from the IBM corporation said that the Federal Government should give serious thought to funding a silicon chip foundry for university educational and academic research. The executive, Dr Juri Matisoo, was visiting Australia recently to review activities at the Joint Microelectronics Research Centres (JMRCs) at the University of New South Wales and the Royal Melbourne Institute of Technology. Dr Matisoo said that Australia would suffer for the lack of such a facility.

Dr Matisoo is the director of semiconductor sciences at IBM's Yorktown Heights research centre in the US. He believes that "the people who do the research here do some excellent work, but one area which is not particularly well equipped is a facility to handle the fabrication and development of technology for integrated circuits.

"I think this is one area which the Australian Government might support. It could be done so that it becomes a national resource", he said. The cost of setting up a silicon foundry would be between \$10 and \$50 million, depending on the requirements. "Because it's too expensive for an individual university, one might consider that the appropriate place for that funding to come from would be the Government," Dr Matisoo said.

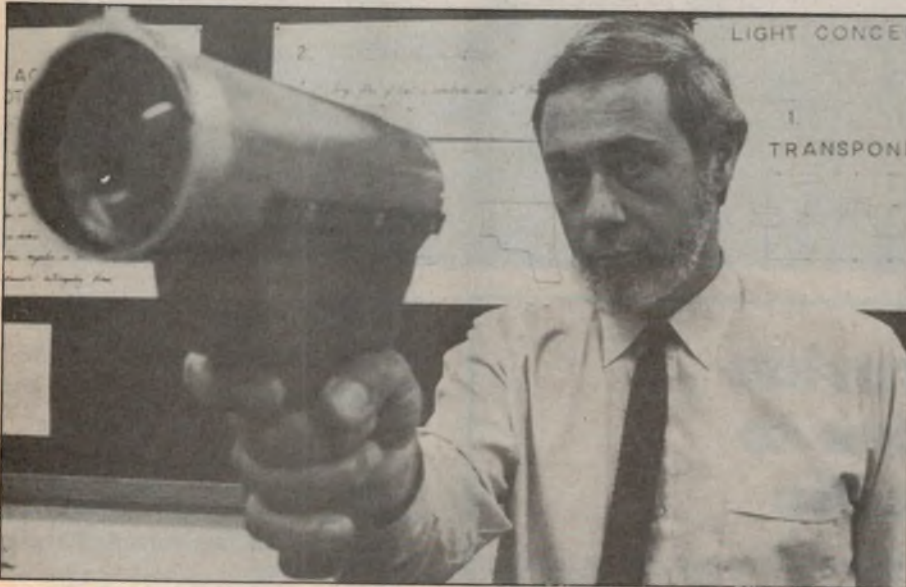At present, the research team at the University of New South Wales is involved in the development of silicon solar cells and research into chips for high speed data transmission equipment for Telecom.



The infrared light gun developed by a combined university research team.

Megabit-chip from IBM

International Business Machines Corporation has announced the development of a new extremely small, fast one-million-bit computer memory chip.

The chip is designed to operate at a speed of 80 nanoseconds (billionths of a second). Initial samples have operated as fast as 60 nanoseconds. With dimensions of 5.5 millimetres by 10.5 millimetres, the new chip is among the fastest and densest megabit chips reported anywhere. It is significantly smaller and

faster than the megabit chip announced by IBM last year.

The new megabit chip stores four times as much information in just slightly more space than that used by the 256,000-bit chip now in volume production at IBM. IBM announced last September that it is using the 256K-bit chip in the 3880 disk storage controller and in the 4381 model group 3 computer system.

Both of IBM's megabit chip designs have been fabricated on existing production lines. Perfect chips, in which every one of the 1,048,576 memory cells operates as intended, have been fabricated on each of these lines.

Solar power at work in the coalfields

In Victoria, the State Electricity Commission has introduced solar power into two of its three open-cut coal mines. Solar cell panels supplied by Amtex Electronics are being used to power laser levelling systems at the Loy Yang and Yallourn mines.

The solar panels are mounted in units on trailers and supply power equivalent to five 12V car batteries per two panel unit. The units are used to charge batteries which in turn power the levelling devices. These guide the dredgers during coalface cutting operations.

The panels were introduced as a solution to the problem of batteries constantly going flat on the job.

One of the battery units powered by Amtex Electronics solar cell panels.



Aussat may provide satellite services to south-west Pacific

A proposal by Aussat Pty Ltd to modify its third satellite to give it the potential to provide communications facilities for countries in the south-west Pacific, including New Zealand, has been approved by the Australian Government.

According to an announcement by the Minister for Communications, Mr Michael Duffy, the question of what services would be provided, and when, were matters for the countries themselves, in consultation with Aussat.

The design modification would allow three transponders to be switched to cover the south-west Pacific.

Depending on overall customer demand, the third Aussat satellite could be launched as early as mid-1986.

Originally it was expected that Aussat's capacity to serve the south-west Pacific would have been part of the second generation of Aussat satellites, timed for the early 1990s.

Mr Duffy said it was traditional for Australia to co-operate with South Pacific nations in telecommunications matters and the Aussat decision demonstrated its willingness to continue to do so. It was possible that Australian industry could benefit from the provision of such services.

Apart from NZ, countries that could avail themselves of the potential offered by the Government's decision included Fiji, Western Samoa, Tonga, Vanuatu, the Solomons, Papua New Guinea, the Cook Islands, Kiribati, Tuvalu, Federated States of Micronesia, Nauru, Tokalau and Niue.

NASA antenna for University of Tasmania

The 26-metre antenna located at the Orroral Valley Tracking Station has been donated to the University of Tasmania, according to the Department of Science and Technology.

The antenna had been used to track a variety of US spacecraft, including Skylab and the Space Shuttle. It will now be used by the University's Physics Department as part of its teaching and research activities.

One of its planned uses is in conjunction with the Australia Telescope, now under construction for Australia's bicentenary. According to researchers, the addition of the new 26m antenna at Hobart will significantly improve the performance of this telescope.

The antenna will also be available for Very Long Baseline Interferometry in conjunction with other suitable instruments. This will assist in geodynamics and geophysical research by obtaining more accurate measurements of the Earth's surface.

AT LAST!

A BUDGET PRICED 19 INCH RACK SYSTEM

ZIP-RACK 19A is the basic rack system for your 19 inch rack mounting equipment, kits & PCB sub-racks.

ATTRACTIVE
ANODISED
ALUMINIUM
FINISH

STANDARD
FRONT FACE
MOUNTING
FORMAT

FAST
EASY
KIT
ASSEMBLY

THREE
STANDARD
RACK SIZES




Advance Australia

*ZIP-RACK 19 IS
DESIGNED AND
MANUFACTURED
IN AUSTRALIA*

BY

AUTOTRON AUSTRALIA

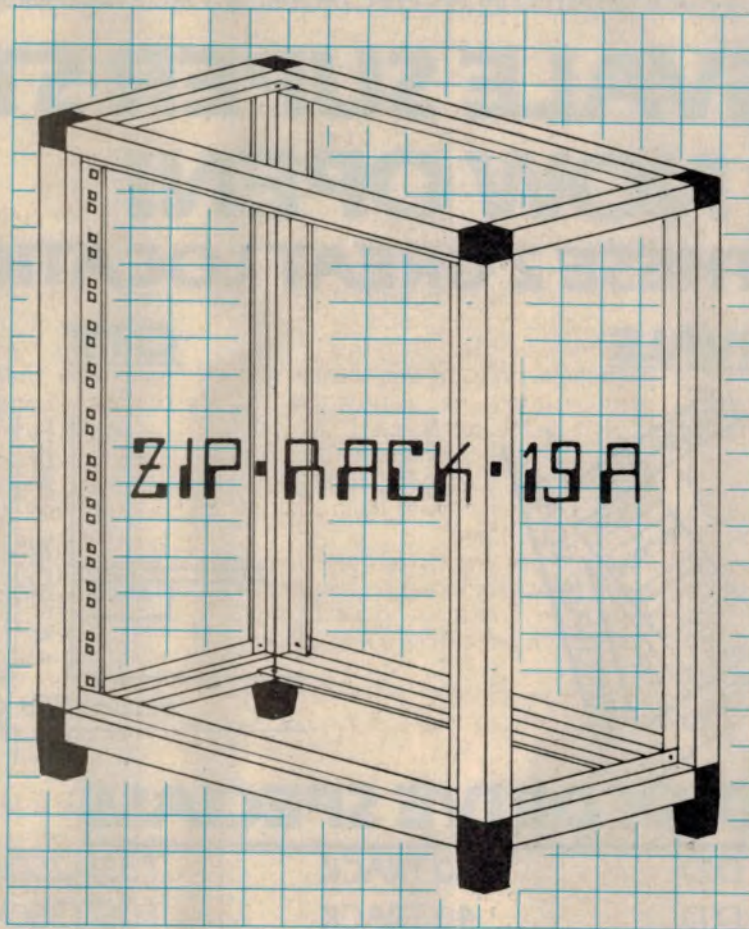PO Box 202,
Glen Waverley, 3150,
Victoria, Australia.
Telex 38433
Telephone (03) 763 6423



SIZE	KIT No.
6 RU	19-111
12 RU	19-112
18 RU	19-113

1 Rack Unit (RU) Panel
is 44.5 mm high (1 $\frac{3}{4}$ in.)
ALL RACKS ARE
358 mm DEEP.

KIT CONTENTS

- ★ 12 Frame Sections
- ★ 4 Top Corners
- ★ 4 Lower Corners
- ★ 12 Clip-in M6 Nuts*
- ★ 12 M6 Screws*
- ★ 1 Pack of 'Pop'
Rivets
- ★ 1 P&N Drill
- ★ Simple, easy to
follow instructions

* For equipment mounting

ASSEMBLY

Tools required: Small rubber mallet; electric hand drill; hand rivet tool. Twelve lengths of hollow extrusion are interlocked using eight plastic corner pieces. The plastic corners are inserted into the hollow sections using a small rubber mallet. This assembly is then made permanent by drilling and pop riveting each corner with drill (3.2 dia.) & pop rivets supplied with kit. No spanners, screws, nuts or washers. Just a clean fast fit.

NSW: CONTACT YOUR LOCAL JAYCAR STORE
FOR THEIR CUSTOMISED ZIP-RACK 19J

VIC: ACTIVE ELECTRONICS: MELBOURNE (03) 602-3282
SPRINGVALE (03) 547-1046

W.A.: ATKINS CARLYLE: (09) 321-0101

LOCAL & OVERSEAS DISTRIBUTORS ENQUIRIES WELCOME



ACTIVE ELECTRONICS


289 LATROBE STREET, MELBOURNE 3000 PH. (03) 602 3499
887 SPRINGVALE ROAD, SPRINGVALE 3171 PH. (03) 547 1046

8.30am - 5.30pm MON-THURS 8.30am - 8.00pm FRIDAYS 9am-12noon SATURDAY
ALL YOU HAVE EVER WANTED IN AN ELECTRONIC STORE - AND MORE!

SPRINGVALE SUPER STORE NOW OPEN!


CHECK THESE 2 GREAT LOCATIONS

SPRINGVALE

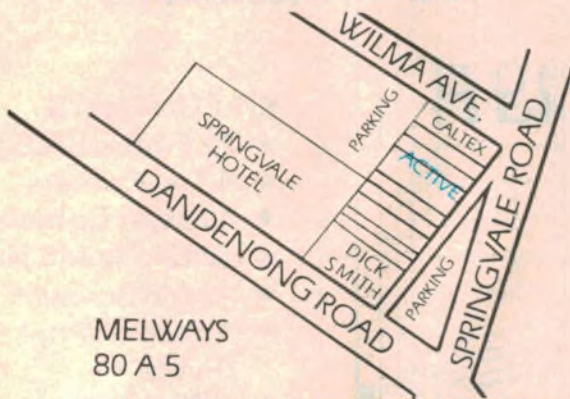

MELWAYS
80 A 5

CITY

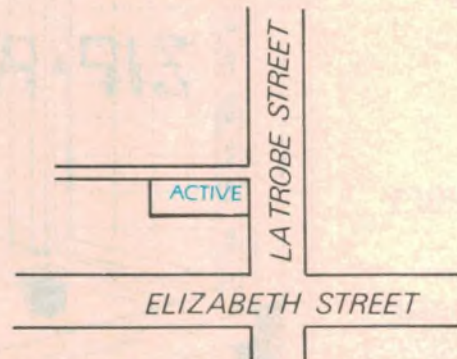

DISK DRIVE SPECIALS

CHINON 3 1/2"	S.S.D.D	40 TRACK	F351 (250K)	\$149
CHINON 5 1/4"	S.S.D.D	40 TRACK	F051 (250K)	\$149
CHINON 5 1/4"	D.S.D.D	40 TRACK	F052 (500K)	\$195
MITSUBISHI 5 1/4"	D.S.D.D	40 TRACK	M4851 (500K)	\$215
MITSUBISHI 5 1/4"		80 TRACK	M4853 1 MEG	\$260
MITSUBISHI 5 1/4"	D.S.H.D	77 TRACK	M4854 1.6 MEG	\$350
MITSUBISHI 5 1/4"	D.S.H.D	77 TRACK	M4855 2 MEG	\$385



MAIL ORDER
HOT LINE

(03) 671312



\$1-\$9.99	\$1.50	\$100-\$199	\$5.00
\$10-\$24.99	\$2.00	\$200-\$499	7.50
\$25-\$49.99	\$3.00	\$500 plus	\$10.00
\$50-\$99.99	\$3.50		

MAIL ORDERS LA TROBE ST. STORE ONLY



ACTIVE ELECTRONICS

289 LATROBE STREET, MELBOURNE 3000 PH. (03) 602 3499
887 SPRINGVALE ROAD, SPRINGVALE 3171 PH. (03) 547 1046

8.30am - 5.30pm MON-THURS 8.30am - 8.00pm FRIDAYS 9am-12noon SATURDAY
ALL YOU HAVE EVER WANTED IN AN ELECTRONIC STORE - AND MORE!

NOW AVAILABLE DO IT YOURSELF BURGLAR ALARM KIT.



COMES IN CARRYING CASE.

\$399



AUSTRALIAN MADE

PROTECTS YOUR HOME,
OFFICE & FACTORY.

TOP BRAND MITSUBISHI MONITORS



GREEN
NV1290 x

\$210

AMBER
NV1290 x

\$215

CHECK OUR SEMICONDUCTOR PRICES - YOU WON'T DO BETTER (JUST PART OF OUR LARGE IN-STORE RANGE)



ACTIVE - JUST ABOUT EVERYTHING ELECTRONIC



Letters to the editor

More on engineers

I have been reading the correspondence you have received on your August '84 editorial. I do not remember this particular editorial as I retain — for a while — only those issues which have a particular interest to me. Had I retained them all since R & H days there would be no room in the garage for my car!

It is apparent that your "applicants" were required (among other things) to explain the working of a "superhet" (?). In my view any electrical engineer who could not answer that one is not worth any consideration — irrespective of what the other questions were!

I am not altogether sure that your comparison to mechanical engineers (re two stroke engines) is valid. Nevertheless I have no sympathy with such people as Mr P. Stewart, who rubbished you on that account.

**B. M. Ferguson,
Glenroy, Vic.**

In praise of Electronics Australia

I have only been reading your magazine for five months so I am a newcomer to the ranks of your readership. You may rest assured that I will be a faithful reader for many years to come. I am very impressed with the high standard of the articles, reviews, projects and general news which appear in your magazine.

Omissions from stations list

I wish to draw attention to a number of broadcasting stations not included in your list in the March 1985 edition.

These are the community radio stations for the print handicapped and include 2RPH in Sydney and 3RPH Melbourne, both on 1629KHz. I understand that Brisbane and Hobart have similar stations.

According to a spokesperson at 3RPH all have been on air for more

I have read with great interest the correspondence on the subject of engineers. I have found it particularly enlightening as I am a first year electronics engineering student at RMIT. You have again given me much to think about as I begin my formal education in electronics engineering.

**P. Campbell,
Hawthorn, Vic.**

Still more on engineers

As one who has both qualified and earned a living as an electronics technician and engineer, may I offer the following toward your debate.

Integrated circuit technology enables technicians to develop sophisticated electronic modules for discrete functions. However, it requires an experienced engineer to successfully integrate discrete modules into reliable operational systems.

Ignorant, lazy engineers are no more numerous than similarly disposed technicians. Arrogant engineers and technicians are the greatest problem. Fortunately, they are not numerous.

As with politicians, a nation gets the engineers it deserves and regrettably Australia is doing badly. It is training, on a pro-rata basis, fewer engineers (in all disciplines) than most European and some Asian countries, eg, Japan, South Korea, Taiwan and Singapore. The situation is even worse when one considers that nearly 20% of engineering

than 12 months. At least one large daily newspaper publishes a complete program for 3RPH and it can also be obtained in braille from 3RPH.

**R. Ridgway,
Frankston, Vic**

The omissions are unfortunate but the list was compiled using the latest available information from the Department of Communications. In fact we even made a point of phoning the DOC to ask for an update just before publication. Thanks for bringing the omissions to our attention.

places in our tertiary institutions are occupied by assisted overseas students.

Considering the nation depends upon graduate engineers, one can start feeling concerned about our prospects of sustaining economic growth at a desirable rate. Engineering is the greatest employment multiplier in any economy.

For the answer to our national neglect of the profession, your readers may care to check the backgrounds of the 100 top leaders in business, public service, industry and politics; "Whose Who" will do as a reference. With few exceptions they will be found to have qualifications in accounting, economics, law, medicine or psychology. Engineering is not fashionable amongst the upwardly mobile.

One of the sad features of engineering training in Australia is the general lack of preparation for the management role. Far too often we find good professional engineers becoming amateur managers following promotion.

**K. B. Flynn,
Aranda, ACT**

Breakdown voltage test jig

I refer to the February 1985 issue, page 70. Mr Dance states that the voltmeter reads the zener "breakdown" voltage. Wrong! The voltmeter is shown across the "junction under test" and VR1 (1k Ω). The meter should be across the junction under test.

Mr Dance's explanation as to how his circuit works is also somewhat muddled. This is due to his fairly obvious belief that current flows into his circuit out of the positive rail. His statement that Q2 current "robs Q1 of base current" is positively juvenile.

In fact Q1 cannot pass any current at all unless its emitter is negative with respect to its base (leakage current of both transistors, particularly Q2 Ico, is disregarded). The emitter of Q1 is, indeed, connected to the negative rail via the mA meter, the junction, the voltmeter and VR1. So, provided the "junction" is not open-circuited, Q1 will conduct.

With the junction fused (shorted) the voltmeter merely reads the voltage across VR1. With an open junction, the only current flowing in Q1 is through the voltmeter. There is no voltage across VR1 and thus no Q2 current.

Assuming a normal junction, there are two basic ways of explaining Mr Dance's circuit. The simplest method is to regard Q2 as a variable resistance in series with R1.

(a) with Q2 a "high R" (zero base

Much more on engineers

I have been reading the engineers' debate, and I agree that it has been a bit one-sided. There have been far more engineers sticking up for each other than those defending your point of view. Although I am only a hobbyist and have no technical qualifications, I am no dumbo and I can see your point of view.

Thank God doctors don't have the same point of view as those engineers. Can you imagine a doctor, or for that matter a nurse, suddenly stopping in the middle of the operation to have a few hours study so he can brush up on what he is not sure about.

Given that background, I sat down again and tried to answer the five questions you asked your applicants. I could answer Question 1 on the superhet receiver fully, and without any problems. Question 2 on the complementary symmetry amplifier was a different matter. While I can answer in general terms, it's obvious that I don't have the depth of knowledge to answer it properly.

For Question 3, I could give a reasonable explanation of how a phase lock loop works, but I would be lost on the fine detail of designing the filters and selecting the loop constants. Similarly, I could describe the Schmitt trigger in Question 4, but I had to think for a long time before I realised what you meant by a three gate oscillator.

In Question 5, I could describe how a multiplex seven-segment display works, and give its advantages. However, I couldn't say for certain why LCDs are not multiplexed.

On the face of it, and in view of your remarks, I wouldn't qualify for a job with *Electronics Australia*, and I shouldn't be calling myself an engineer. So why can't I answer your five questions? Perhaps, more importantly, why couldn't your applicants answer the questions?

Firstly, I think you made an unwarranted assumption in your editorial. You said that by selecting recently qualified engineers, or those part way through their courses, you would be hiring people who are right on top of the latest developments in technology. The only engineers who have that sort of knowledge are those

who have been working for some years in the particular technology.

As other writers have pointed out, the student has a very big work load, and can't afford the time to learn about any new technology to great depth. In addition, course content is set well before the start of each year, usually in conjunction with other bodies, so it is unlikely that the syllabus will be changed during a year to include material on new technologies. It's more often the case that a new technology has been introduced, and in regular commercial use, well before it appears in a course.

Secondly comes the question "What sort of engineer do you really need?" — Note that I said what do you need, not what did you advertise for. Do you need a hobbyist, a graduate engineer or an experienced engineer? Anyone who believes that the three are interchangeable, or that a graduate engineer has the knowledge and experience to design many of your projects and produce a satisfactory result quickly and economically is in for a nasty shock.

I remember applying for a position a couple of years after graduating, only to be told by the selection committee that I was only a journeyman, and that they were looking for a master mechanic. They were quite right of course. Graduation means that you have absorbed sufficient information to be able to convince the examiners to let you loose into the world. But that is only the first phase of an engineer's training. The next, and most important phase is to learn how to apply the knowledge already gained to practical problems.

This is perhaps the most important phase in an engineer's training, and can make or break his future career. In fact it is so important that learned Institutions such as the IEE (UK) used to insist that it be carried out under the direct supervision and guidance of one of their qualified members. The Australian Institutions were not so demanding, but still regard it as a critical portion of the training. That is why they have had the two classes of membership, "Graduate" and "Member".

It is unrealistic to expect an undergraduate, or a recent graduate to carry out design work quickly and efficiently. Remember that they are still learning, and if there is no experienced engineer to guide them, they are going to

learn by making mistakes.

Perhaps what you really need is to employ an experienced engineer. That means one who gained his experience in those fields you want to write about. He should also be able to design equipment that can be put together from average commercially available components, and still meet the design specifications without having to specially select one transistor or other component from a batch. He should know about printed circuit layout, and in particular, the layout rules for power supply rails for digital circuits. He must know how to design a piece of equipment that will work the first time without a lot of cut and try. He must know how to design test points into a circuit, and how to go about cost efficient designs.

Certainly such an engineer will cost you much more per hour than an undergraduate or recent graduate. But he will also produce much more per hour than the other two, and the overall cost per job will be less, with fewer missed deadlines. In fact you will end up saving money.

Now, why couldn't I answer all your questions? Simple. In all my years of experience, I have never had to design or make a detailed assessment of the design for a complementary symmetry amplifier, a phase-lock loop, nor a liquid crystal display. With so much else to learn, I haven't had time to study any of these in detail. I would be surprised if many of your applicants would have had the time or opportunity to gain the practical experience needed to answer your questions confidently. As for the average reader of EA, how long has it been since you published sufficiently detailed articles to allow them to answer your five questions properly?

Finally, you ask what is wrong with engineers that they don't take an active interest in electronics. Why should they? How many professionals do you know in other professions that take an active interest outside office hours, and whose work is the same as their hobby? Why shouldn't engineers go home and relax, take up sport, read about other topics, or enjoy being with their families. What is so special about electronics that engineers should devote their whole life to it?

**A. M. Fowler, MIE Aust,
North Balwyn, Vic.**

voltage), Q1's forward base voltage and collector current will both be high.

(b) with Q2 a "low R" (maximum available positive Q2 base voltage), Q1 forward base voltage and collector current will both be low.

There are other considerations, caused

by varying Q1 current varying the VR1 voltage. Quite probably it's enough to say that Mr Dance's circuit reminds me of a dog chasing its own tail.

With the voltmeter connected across the junction the reading might at some point remain steady. This could be


assumed to be the zener voltage (irrespective of current change).

There is a better way and I enclose a circuit of my own zener/diode tester (to be published).

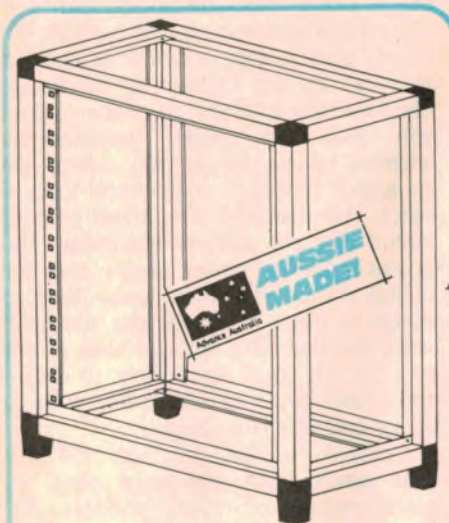**B. M. Ferguson,
Glenroy, Vic**

JAYCAR - YOUR No.1 STORE FOR GREAT

Because of the devalued Australian Dollar we have sourced some Aussie manufactured items that are outstanding value for money! Check the "Aussie Made" logo in our ads for locally made goods at great prices! Remember! Aussie made goods means your precious dollar stays here!



AT LAST! An Economical RACK CABINET MOUNTING SYSTEM!!

This fully Australian-made product we believe will become one of our hottest selling items!

It has taken an Aussie manufacturer to come up with the world's first low cost rack mounting system especially for the budget-conscious home constructor!

The rack mounting system basically consists of specially designed aluminium extruded frames. Moulded plastic corner and feet pieces connect the extrusions together to form a rigid frame. No spanners, screwdrivers are needed but the use of a rubber or wooden mallet is advised to securely fit together the self-aligning pieces. When assembled the frame can be further strengthened with pop rivets. The system is supplied in knocked-down (kit) form to keep costs and freight down. Assembly takes around 20 minutes and instructions are supplied. In keeping with the low-cost philosophy, side and top panels are not included. Any reasonably competent reader should be able to fashion wooden or metal panels to suit. (Edge finish is not necessary as the panels recess into the frame.) Jaycar will have special side panel sets available shortly however. Please watch our ads for further details.

THE RACK IS AVAILABLE IN 3 SIZES 6, 12 and 18 rack unit

(One rack unit is 44.5mm or 1 3/4")

Each kit comprises: ★ 12 frame pieces, including 2 pieces with pre-punched holes for front panel mounting. Natural anodised finish. (You can use the rack back-to-front to mount non-standard racks). ★ 4 top corners (black) ★ 4 bottom corners (black) ★ 4 x clip-in M-6 nuts (for mounting your equipment) ★ 4 x M-6 Phillips head mounting screws ★ easy to follow instructions

But the best part about this exciting concept is **THE PRICE!**

ONLY

Cat. HR-5310 **6 RACK FRAME \$ 99**
Cat. HR-5320 **12 RACK FRAME \$ 119**
Cat. HR-5330 **18 RACK FRAME \$ 139**

Extra M-6 captive nuts (Pack of 12)

Cat. HP-0640 **\$4.95**

Extra M-6 x 16mm plated Phillips head mounting screws (pack of 12)

Cat. HP-0645 **\$2.95**

AVTEK MULTIMODEMS

State-of-the-art multimodem - has the following data standards CCITT V.21 & V.23, BELL 103 & 202. Data rates 300, 600 & 1200 BPS. Backward channel 75 BPS in conjunction with 1200 BPS. Computer interface CCITT V.24 (RS232C). Power requirements 240V AC 3 watts. Talk to the world with this fine Multimodem. Cat. XC-4820

INCLUDES PHONE

\$349.00

MiniModem

★ 300 Baud full duplex ★ Answer/originate ★ Plugs straight in (hardware phone) ★ Superior VLSI chip performance (identical to Multimodem) ★ Telecom approval C64/37/1173. Cat. XC-4825

ONLY \$199.00
INCLUDES PHONE

FREE CATALOGUE

Ask for a FREE COPY of our 1985 Engineering Catalogue or send large SAE with 50¢ stamp

JAYCAR JVE-1 VIDEO DETAIL ENHANCER

(For technical details see page 15 of our catalogue or send SAE) This is made in Australia exclusively for Jaycar. It was designed at a well-known Australian University. It was designed with Australian standard video systems in mind and beats the pants off some expensive imports!

(Power adaptor Cat. MP-3020 only \$9.95 extra)

Cat. AV-6501 **ONLY \$69.95**



1/4" (6mm) BRASS Clearance Spacers

Bulk packs - from as low as 6¢ each!

We are pleased to announce that we are having these MADE IN AUSTRALIA. They are high quality, natural brass finish and will allow a 4BA screw to pass through with clearance. They are 1/4" dia as well!

YOU CAN BUY THEM FROM US IN PACKS OF:

8 Cat. HP-0860 **\$ 0.95**
100 Cat. HP-0870 **\$ 8.50**
500 Cat. HP-0871 **\$30.00**

MAIL ORDER HOTLINE

To save you time (and therefore money) we have installed a special HOTLINE direct to the inner workings of our mail order dept. This saves you from going through our Head Office switchboard! If you wish to place an order, enquire about an order or simply check for more information, call:

(02) 646 1300

GREAT NEW PRODUCTS!!!

Our ongoing product development brings you unique new products every month!

RCA PLUGS - Yellow and white covers. They match red and black for identification of stereo input/output leads



	1-9	10+
Cat. PP-0240 RED	\$0.45	\$0.40
Cat. PP-0242 BLACK	\$0.45	\$0.40
Cat. PP-0243 YELLOW	\$0.45	\$0.40
Cat. PP-0244 WHITE	\$0.45	\$0.40

5 pin DIN plug 270° spread of pins. These plugs are used in computer and some video applications. Shielded backshell.



	1-9	10+
Cat. PP-0305	\$0.90	\$0.82

Electricity Authority Approved Fuseholder! At Last! A 3AG 240V 10A fuseholder that is approved but at a reasonable price! (Approval No. CS2929) Ideal for manufacturers.

Cat. SZ-2025 **ONLY \$3.95**



Blue Strobe Flasher 12V This unit has a magnetic base and is fitted with 4 metres of cable terminating in a cigarette lighter plug. Ideal for car alarms or fitted to a siren cover to bring visual attention to a theft.



Cat. LA-5105

ONLY \$32.50

NEW! Longer TV plug-to-socket Fly leads (75 ohm)

Cat. AV-6580 1.8 metre Plug-to-Plug	\$3.20
Cat. AV-6582 1.8 metre Plug-to-Socket	\$3.45
Cat. AV-6584 4.5 metre Plug-to-Plug	\$4.95
NEW! Cat. AV-6585 4.5 metre Plug-to-Socket	\$5.95
Cat. AV-6586 10 metre Plug-to-Plug	\$9.75
NEW! Cat. AV-6587 10 metre Plug-to-Socket	\$10.95



Coaxial Cable Joiner Now you can join 3C2V, RG59, RG58, 5C2V coaxial cables together WITHOUT SOLDER with this nifty cable joiner!

Cat. PS-0618 **ONLY \$1.50**



Solderless BNC line plug This enables you to terminate coax in the field without a soldering iron! Reliable screw connection withstands flexing.

Cat. PP-0652 **ONLY \$2.75**



At Last! A car 12V cigarette lighter SOCKET! A panel mount source of 12V for cars, boats, planes. You even can plug a cigarette lighter into it!

Cat. PS-2002 **ONLY \$4.50**



NEW! Gel-cell Battery Charger Specifically for charging Gel-cells with 1/4" quick connect tabs on them. 240V AC to 12V DC @ 300mA ensures fast charge!

Cat. MB-3506 **ONLY \$10.95**

MOTOROLA

PIEZO TWEETER BARGAIN!

Quite frankly we were staggered when an importer came to us with his dilemma. We couldn't believe our ears when we were told the price of the genuine US-made Motorola brand KSN-1071 high performance tweeter. "With such a strong US dollar," they said the price we offer to you is far below our current replacement cost. This HI-FI high power tweeter is a surface mount, controlled dispersion line source unit that is fitted with its own grille panels. The use of high temperature materials in its construction enables it to be used in automotive applications. Two piezo elements provide a wide (90°) dispersion horizontally with a narrow 30° dispersion vertically. Sensitivity is 98dB @ 2.8V @ 1/2m. Frequency response easily goes out to 40kHz but this can be limited with external passive components if necessary. A comprehensive data sheet is supplied, which includes frequency response graph, specs, mounting details etc. The KSN-1071 normally sells for a very reasonable \$24.00 each (pre devaluation). While stocks last, this unit is available from Jaycar for the ridiculously low price of **\$12.95 each!** That's right! A high quality, high power HI-FI tweeter for a pittance! HURRY!

Cat. CT-1918

ONLY \$12.95 each



PRODUCTS AT GREAT PRICES!!

SCOOP PURCHASE! GENUINE SIEMENS

Universal voltage tester with LED indicator
The Siemens "UNISPANN" voltage probe has been around for some time now. You can determine the presence of AC or DC voltages safely anywhere with this quality probe. It will even tell you which AC mains conductor is active and works from 6-500V AC or DC. It also shows DC polarity.
Normally these units are very expensive but a Jaycar SCOOP PURCHASE brings them to you at a great price!
WHILE STOCKS LAST - AN INCREDIBLE BARGAIN
Cat. QT-2220



TELEPHONE EXTENSION LEADS

Our purchasing guy is a "bunny" and now we've got them coming out of our ears! **SAVE HEAPS** while we are in this dilemma!

- | | | | |
|---------|------------------|----------------|-----------------|
| YT-6010 | 5m Ext. lead | \$9.95 | SAVE \$5 |
| YT-6012 | 10m Ext. lead | \$12.95 | SAVE \$7 |
| YT-6013 | 15m wind up reel | \$12.95 | SAVE \$7 |
| YT-6014 | 20m wind up reel | \$14.95 | SAVE \$8 |

☆ SAVE HEAPS ☆



BLANK PCB - BARGAIN OF THE CENTURY

We have secured massive stocks of high quality copper-clad PCB material. In both single and double sided versions. Jaycar has NEVER had the opportunity to sell material at anything NEAR this price before. We suggest that you stock up NOW as we doubt that we will EVER be able to repeat this bargain again.

OFFER 1

Blank, single sided board. Phenolic base. Dimensions approximately 350mm (14") x 330mm (13")
Limit 2 sheets per customer
Cat. HP-9508

May Only \$3.95
(Normally \$6.95) **SAVE \$3.00**

OFFER 2

Blank, single sided board. Fibreglass base. Dimensions 350 x 330mm
Cat. HP-9510

May Only \$4.95
(Normally \$8.95) **SAVE \$4.00**

OFFER 3

Blank, double sided board. Fibreglass base. Dimensions 300mm (12") x 300mm (12")
Limit 4 sheets/customer
Cat. HP-9520

May Only \$6.95
(Normally \$12.95) **SAVE \$6.00**

Note that the normal price is based on 300mm square sheets and not this larger size - an even greater saving!

FM TRANSMITTER MODULE

FEATURES:

- ★ Ultra low noise output (-60dB or better attainable with suitable tuner)
- ★ Excellent frequency stability
- ★ NOT a kit - ready for immediate use
- ★ Connections required: (A) Power supply or battery (B) Antenna (C) Audio input
- ★ Full instructions supplied
- ★ Suits any application where a stable low noise FM link is required

SPECIFICATIONS:

- Frequency 88 - 108MHz
- Useable range - 50 metres
- Supply - 6 to 9V @ 20mA
- Input sensitivity adjustable max 30mV
- Pre-emphasis - 50us standard
- Dimensions 90 x 22 x 15mm (approx)

Cat. DT-5450

NEW! BY POPULAR DEMAND! Commercial Ultrasonic Pest Repeller

Everything that we have said about the VermineX domestic unit except that it is for commercial applications!
★ Sturdy metal cabinet
★ 3 selectable pitch and loudness settings to optimise for particular problems
★ Low power consumption
★ 14 day satisfaction guarantee
★ Includes AC mains adaptor
Cat. VS-5510

ONLY \$159.00



ULTRASONIC PEST REPELLER

Which of these do you need to get rid of? Mice, blowflies, birds, spiders, bats, rats, cockroaches, flies, moths or fleas? The VermineX ultrasonic insect/pest repeller creates a sonic environment which is totally hostile to the creatures mentioned.

HOW DOES IT WORK?

The environment is relatively devoid of ultrasonic sounds. Evolution has not had a compelling reason to protect non-acoustic sensory mechanisms from ultrasonic stimulation. By subjecting an insect or rodent to a high level ultrasonic soundwave of a particular pattern the creature begins to behave in a typical fashion. The pest becomes disoriented, lethargic and bewildered. The natural reaction is to escape from the sound-affected area. The sonic pattern is the secret and this pattern is a combination of scores of frequencies mixed together. The pattern was developed by Professor J.L. Stewart - the man who invented the Bionic ear. It works!

Like us, you would be skeptical at first that this would work. Our first reaction was "If they are so good why haven't I heard about them before?" or "Surely a product like this - if it was any good - would have been around years ago." There have been ultrasonic repellents around but none of them have the patented soundwave pattern of the VermineX. We have on our file, many letters of testimony to the fact that the VermineX is effective. The letters are from Australian Universities, Animal Husbandry research institutions, commercial Piggeries, restaurants etc. Many of them had several pest problems! Your pest problems may not be as bad but it may still be a nuisance, which is why the domestic VermineX was developed. We are so confident of the VermineX units' effectiveness, we make the following offer:

Buy the VermineX from us and use it for up to 14 days (21 days for mail order customers). If you are not happy with the product after using it as directed return it to us in a clean, original condition and we will refund your money in full! (Less post/packing). What have you got to lose? The VermineX covers an area of 2000 sq ft (uninterrupted) and is not cheap. But if the idea of dangerous chemicals, sprays, baits etc worries you it's a great solution. It is supplied with a 240V plug pack but can be battery powered.
Cat. VS-5500

WHAT HAVE YOU GOT TO LOSE EXCEPT THE BUGS!

\$79.00

INFRA RED MOVEMENT DETECTOR

- Built-in test lamp
- Tamper switch included
- Alarm output SPST 30V DC @ 1A

- 12V DC powered
- Small 4 1/2" x 2" x 1 1/2"
- Double sensor
- Computerised OC to lower failure rate

MULTIMETER "PIN PLUGS" to EZ HOOKS

- Great multimeter probes that will fit the 2mm diameter pin tip sockets of your multimeter (NOT "banana" type sockets)
Cat. WT-5314

Normally \$3.95/set
this month \$1.50

WHACKO! Only 430 available. Hurry!



ONLY \$59.95



UV EPROM ERASER

Erase your EPROMs quickly and safely. This unit is the cost-effective solution to your problems. It will erase up to 9 x 24 pin devices in complete safety, in about 40 minutes for 9 chips (less for less chips).

- ★ Erase up to 9 chips at a time
- ★ Chip drawer has conductive foam pad
- ★ Mains powered
- ★ High UV intensity at chip surface ensures thorough erase
- ★ Engineered to prevent UV exposure
- ★ Long life UV tube
- ★ Dimensions 217 x 80 x 68mm
- ★ Weight 670 grams

Cat. XE-4950

ONLY \$89.50



Incorporating ELECTRONIC AGENCIES
NUMBER 1 FOR KITS

MAIL ORDER HOTLINE (02) 646 1300

N.S.W. SHOWROOMS

SYDNEY: 117 York Street. Tel: (02) 267 1614
CARLINGFORD: Cnr. Carlingford & Pennant Hills Road. Tel: (02) 872 4444
CONCORD: 115/117 Parramatta Road. Tel: (02) 745 3077
HURSTVILLE: 121 Forest Road. Tel: (02) 570 7000
GORE HILL: 198/192 Pacific Highway (Cnr. Bellevue Avenue) 439 4799

QUEENSLAND

BURANDA: 144 Logan Road. Tel: (07) 393 0777

MAIL ORDERS: P.O. Box 480, AUBURN 2144. Tel: (02) 643 2000

HEAD OFFICE: 7/9 Rawson Street, AUBURN 2144.

Tel: (02) 643 2000 Telex: 72293

SHOP HOURS

Carlingford, Hurstville & Gore Hill
Mon-Fri 9am - 5:30pm; Thurs 8:30pm; Sat 12pm
Sydney
Mon-Fri 8:30am - 5:30pm; Thurs 8:30pm; Sat 4pm
Concord
Mon-Fri 9am - 5:30pm; Sat 4pm

POST & PACKING

\$5 - \$9.99	\$1.50
\$10 - \$24.99	\$3.20
\$25 - \$49.99	\$4.50
\$50 - \$99.99	\$6.50
\$100 - \$199	\$8.00
Over \$199	\$10.00

COMET ROAD FREIGHT ANYWHERE IN AUSTRALIA ONLY \$12



**MAIL ORDER VIA
YOUR PHONE**

A look at the x-ray spectrometer

One of the most invaluable instruments ever developed for the mining industry is the x-ray spectrometer. Here we take a look at how the instrument works.

by A. B. HOLLEBON

In the eyes of many people the main use of x-rays is for medical purposes, such as the examination of broken bones, or for engineering purposes such as the examination of welds in high pressure pipelines. However, this form of radiation is also very widely used to investigate the composition and structure of materials and even the very structure of atoms and molecules themselves.

One of the most widely used of these techniques is x-ray fluorescence spectrometry in which a powerful beam of x-rays is used to excite a sample of material and so cause it to emit fluorescent x-rays of its own. An examination of the wavelengths and intensities of this emitted radiation then allows a complete chemical analysis of

the sample to be made without in any way altering or destroying the original sample.

How it works

The complete instrument consists of several separate stages, each performing separate tasks under the control of a central programming unit.

The first step in the process is the generation of a powerful x-ray beam which is used to excite the sample. This is followed by a system which splits the radiation emitted by the sample into individual wavelengths. In the majority of instruments these wavelengths are then measured one at a time by a single measuring system. The results are then printed out directly or may be fed to a computer for further processing

depending on the type of work being carried out.

X-rays to excite the sample are generated in a conventional x-ray tube. This is essentially a large vacuum tube diode. The filament is heated by a current from a transformer in order to emit a copious supply of electrons, and a potential of up to about 100,000V is applied across the tube in order to accelerate the electrons towards the anode. When these electrons collide with the anode they suffer a very rapid deceleration and give up part of their energy in the form of x-rays.

These x-rays then pass out of the tube through the thin beryllium window. Only a very small part of the energy of the electrons appears as x-rays and the remainder appears as heat in the anode. As much as two or three kilowatts of heat may be generated in this way and this heat has to be removed by circulating water through the anode.

The sample to be analysed is placed as close as possible to the x-ray tube window so that the maximum possible radiation intensity illuminates the surface of the sample. Under these conditions the sample emits x-rays of its own and this radiation is passed on to the spectrometer for separation and measurement.

Secondary x-rays

Every atom in the sample consists of a central nucleus which is positively charged, surrounded by a number of negatively charged electrons which move in fixed orbits or energy levels, as shown in Fig. 1. When an x-ray quantum collides with an atom it is capable, under certain conditions, of raising an electron from its normal orbit to one of a higher level.

However an atom in this state is unstable and the electron quickly falls back to its original level. As it does it releases the extra energy which it had in the higher orbit in the form of an x-ray quantum. The wavelength of this quantum is inversely proportional to the amount of energy released.

The Quantum Theory

The basis of the quantum theory was laid down by the German physicist Max Karl Ernst Planck in 1900. The theory indicates that radiation from a body travels in the form of "energy packets" called quanta or photons. These quanta possess the properties of both wave motions and of particles, and the energy of one quantum is equal to its frequency multiplied by a number known as Planck's constant.

When energy is emitted or absorbed by a body, the total amount of energy involved is always a whole number of quanta. It is impossible to have a process which involves fractions of one quantum.

In the case of the x-ray spectrometer described in the accompanying article, the first part of the instrument which splits the radiation into its individual wavelengths makes use of the wave-like properties of the x-ray quanta. However in the measurement part of the instrument, the operation of the counters makes the quanta appear to behave as particles. The apparent discrepancy between these two types of behaviour is resolved if the quantum is pictured as a small "packet" of waves travelling as a distinct entity.

The energy levels in the atom are different for every chemical element and, therefore, an examination of the wavelengths in the radiation emitted by the sample indicates which elements are present in that sample. Also the total amount of radiation of a particular wavelength leaving the sample is proportional to the percentage of that element in the sample. It is therefore possible to identify which elements are present, and to estimate their concentrations, by identifying the wavelengths and measuring their intensities.

A typical x-ray spectrometer therefore consists of an x-ray tube to excite the sample, a system to separate the emitted radiation into individual wavelengths, and a system to measure the intensity of the wavelengths. Such an instrument is known as a wavelength dispersive spectrometer. An alternative approach, known as energy dispersion, separates the x-ray quanta on the basis of their energy. However the wavelength dispersive method is the most widely used and is the type described in this article.

Wavelength dispersion

The wavelength dispersion system depends on the properties of crystals and the fact that the atoms in any crystal are arranged in a regular pattern. For our purpose these atoms may be pictured as being arranged in a series of layers lying parallel to the surface. If a beam of x-rays is allowed to fall on to the surface of the crystal it will be reflected in a manner somewhat similar to the reflection of a beam of light. This means that the reflected beam will leave the crystal at the same angle that the incident beam met it as shown in Fig. 2.


However only a small fraction of the original beam is reflected at the surface of the crystal. The remainder penetrates the crystal and is reflected at the various layers of the atoms within the crystal. The beam leaving the crystal is therefore the combined reflections from all the crystal layers. If all of these reflected waves are in phase their effect will be additive and a strong beam will result. On the other hand if they are out of phase, cancellation will occur and there will be no reflected beam.

For a given x-ray wavelength and a given crystal, reflection occurs only at particular angles and these angles are predictable by means of the Bragg equation.

$$n\lambda = 2d \sin \theta$$

where n may be any whole number, λ is the wavelength, d is the distance between the atomic layers in the crystal and θ is the angle at which the x-ray beam meets the crystal.

The complete spectrometer is

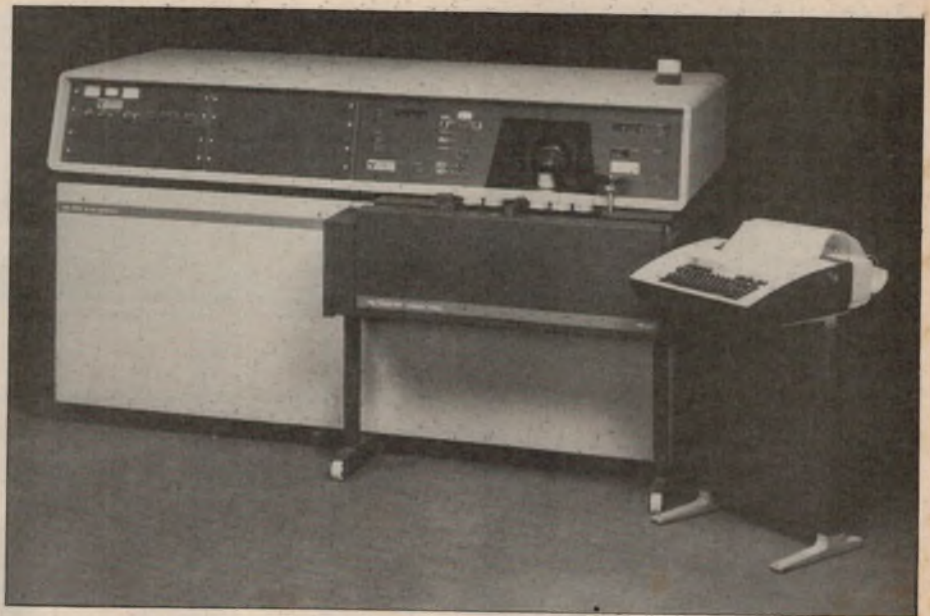

A Philips PW1400 spectrometer fitted with an automatic 6-position sample loader and output printer.

therefore arranged as shown in Fig. 3. Fluorescent radiation leaving the sample passes through the primary collimator which consists of a series of closely spaced parallel metallic plates. This collimator produces a parallel x-ray beam which is then allowed to fall on the crystal. In order to examine the whole range of wavelengths which may be present, the crystal is slowly rotated so that the angle θ is gradually increased.

Reflected radiation leaving the crystal passes through the secondary collimator and then enters the detector. In order to meet the requirements of the Bragg equation and to satisfy the requirement that the incident and reflected beams are at the same angle with respect to the crystal, the secondary collimator and the detector must be moved at twice the angular velocity of the crystal.

If this motion is continuous and the

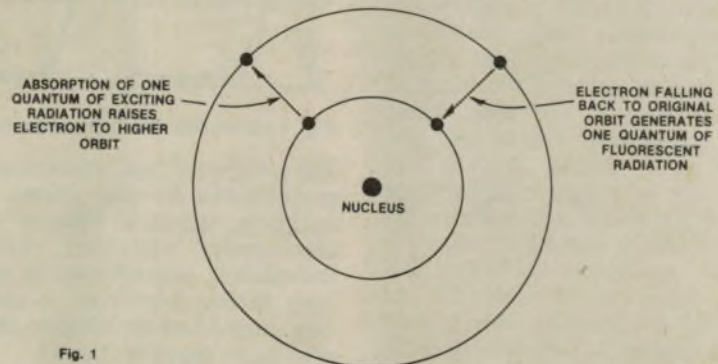


Fig. 1

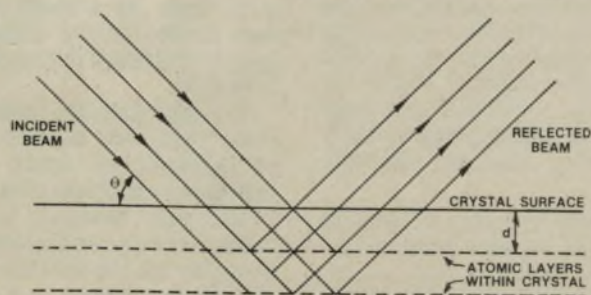


Fig. 2

X-ray spectroscopy

output of the detector is fed to a strip chart recorder, the record will be as shown in Fig. 4. Each peak represents a single wavelength present in the fluorescent radiation from the sample, and the heights of the various peaks indicate the concentration of elements in the sample.

X-ray detectors

The range of x-ray wavelengths that needs to be covered by a modern wavelength dispersive spectrometer is very wide and it is difficult to construct a single detector which is capable of covering the whole range. It is therefore common practice to use two separate detectors in tandem. The first detector is a flow proportional counter, capable of detecting the longer wavelengths only. This counter is transparent to all shorter wavelengths and it is possible to place a scintillation counter behind it which is able to detect these shorter wavelengths.

The flow proportional counter is used to measure the radiation from the lighter chemical elements, and this radiation has such a low penetrating power that it is unable to pass through air. For the measurement of these light elements it is therefore necessary to place the whole of the spectrometer, including the flow counter, inside a vacuum chamber.

This counter is similar in construction to the more familiar Geiger counter, as shown in Fig. 5. The body of the counter is made of metal and has two windows located on its front and back. These windows are covered with a very thin sheet of Mylar plastic. A very fine tungsten wire is stretched tightly along the axis of the counter and is electrically insulated from the body. The counter is filled with a mixture of argon and methane gas and a potential of 1500-2000V is applied to the central wire. The counter is then connected to an amplifier as shown in the simplified diagram in Fig. 6.

In order to detect the very long wavelengths the Mylar window has to be extremely thin, otherwise these low energy x-ray quanta would never reach the interior of the counter. These thin windows are not completely gas proof and gas has to be supplied continuously to the counter to make up for these losses.

When an x-ray quantum of suitable energy enters the counter it has a high probability of colliding with a gas molecule. When this happens the energy of the quantum is used up in forming ionised gas atoms within the counter.

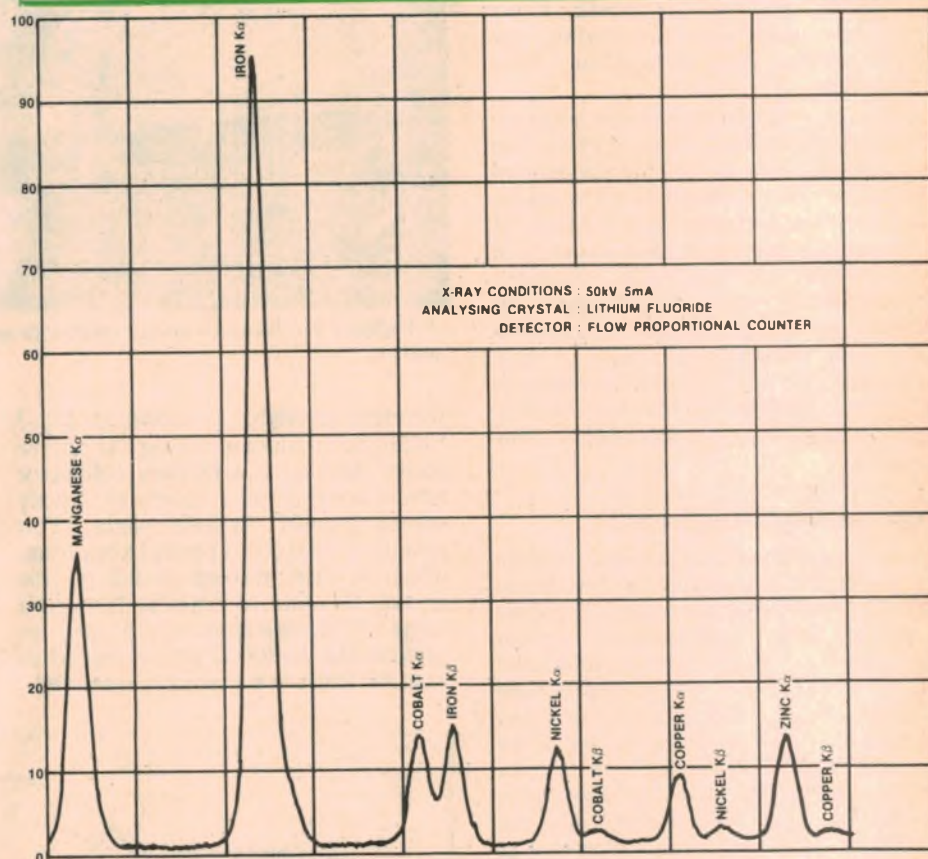
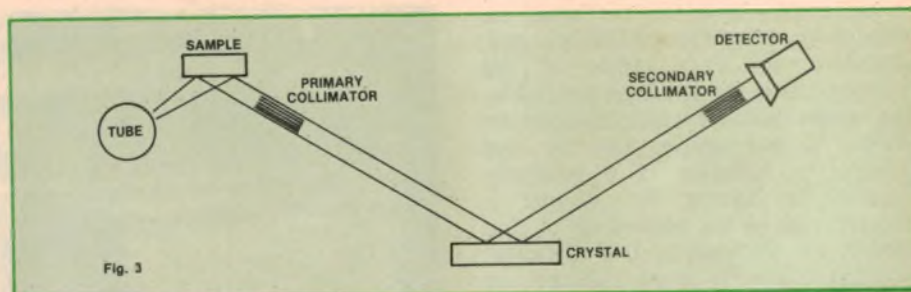


Fig. 4 shows the record from the strip chart recorder.

The number of ions produced is directly proportional to the energy of the incoming quantum. Because they are electrically charged, these ions immediately migrate towards either the body of the counter or to the central wire, depending on whether they carry positive or negative charges.

As these ions move they pick up speed and eventually have enough energy to ionise other gas atoms as they collide with them. As a result the number of ions formed by the original collision is greatly multiplied due to these secondary collisions.

Provided that the counter is operated under the correct conditions, the number of negative ions which arrive at the central wire is proportional to the energy of the x-ray quantum. Since all of the collected charge on the central wire must flow through the load resistor, a negative going pulse appears at the input to the amplifier for every quantum of radiation absorbed by the counter.

Scintillation counter

Any radiation which is not absorbed by the flow proportional counter passes out through the rear window and enters the scintillation counter. This counter is designed to detect more energetic quanta than the flow counter and so does not require such a thin and frail window. In most cases the window is made of a thin layer of beryllium, and its main purpose is to admit x-rays while blocking visible light.

After passing through the window, the x-ray quanta enter a specially activated sodium iodide crystal. This crystal converts the energy of the incoming quanta into individual pulses of visible light, which are sensed by a photomultiplier tube. Amplification of the pulses occurs in the photomultiplier and, in a similar manner to the flow counter, the output pulses from the load resistor are proportional to the energy of the original quanta.

Practical use of the x-ray spectrometer

Fully automatic x-ray fluorescence spectrometers have been in use in industry for about 25 years and are now an indispensable tool particularly in the mining, metallurgical and cement industries. In many cases they have almost completely displaced the older classical methods of chemical analysis with a significant reduction in both labour costs and the time taken to complete the work.

Instruments available at the present time can handle elements from atomic number nine (fluorine) up to atomic number 92 (uranium) at concentrations ranging from less than one part per million right up to 100%. These instruments are fully automatic in operation with all operating parameters being adjusted by an internal programming unit as the analysis proceeds from the determination of one element to the next.

Before commencing an x-ray analysis it is usually necessary to carry out some form of sample preparation before the sample is presented to the instrument. In the case of a metallic sample this usually consists of a grinding or machining procedure in order to produce a flat surface which is free of any surface contamination which may have been present on the original sample.

In the case of mineral samples the situation is usually more complex since the sample may consist of several separate mineral species present as discrete particles. It is usually necessary to reduce these irregularities in the sample and this may be done either by very fine grinding or by fusing the sample with a material such as lithium borate. This destroys the original crystal

structure of the material and converts it into an amorphous glass.

The melt is poured onto a cold surface to solidify and the resulting glass disc may then be loaded into the instrument. However, in some cases segregation of the various elements occurs during solidification and it is then necessary to grind the disc to a fine powder and form it into a briquette before the analysis can be carried out. In order to further reduce the effect of any non-uniformity in the sample, some instruments continuously rotate the sample during measurement.

Modern instruments usually provide some form of automatic sample handling. The prepared samples are loaded into specially designed trays and each tray carries a card to provide identification of the samples and the required analysis program for those particular samples. The tray is then loaded into the spectrometer and the analysis proceeds automatically without further intervention by the operator.

The degree of excitation of the various elements in the sample by the primary beam from the x-ray tube depends on the wavelengths present in the primary beam. The main factor controlling these wavelengths is the material from which the tube anode is made since the emitted radiation consists of the characteristic wavelengths of the anode material plus "white" radiation which is spread over a fairly wide range of wavelengths. The anode material is therefore chosen to provide the optimum excitation for the elements of interest in the sample.

A further point which must be

considered is that a small amount of the primary radiation from the x-ray tube finds its way through to the detectors. Consequently, if say a chromium anode tube is used then a chromium peak will be present in the spectrum even if there is no chromium in the sample. However, it is possible to insert a suitable filter into the primary beam to remove the unwanted characteristic radiation and so enable measurements to be made of the same element as that used in the tube anode.

In cases where it is required to analyse for elements covering a wide wavelength range, it is not practical to use a single crystal for wavelength dispersion due to the limitations imposed by the Bragg equation:

$$n\lambda = 2d\sin\theta$$

Since $\sin\theta$ has a maximum value of 1.0 it is necessary to use a crystal which has a "d" spacing of not less than half of the wavelength to be measured if first order reflection ($n = 1$) is to be used. Most instruments therefore are fitted with more than one crystal arranged in a suitable turret which allows them to be brought into use automatically as required during the course of the analysis.

The measurement is carried out by sending the pulses leaving the pulse height analyser directly to a pulse counting system. Counts are accumulated either for a fixed time or the time taken to accumulate a fixed number of counts is measured. A further option in some instruments is to make a direct measurement of the ratio of the count rates obtained from the unknown sample and from a previously analysed reference sample.

Signal processing

The output of both types of counter contains a certain amount of unwanted electronic noise in addition to the required pulses. Under normal conditions the noise pulses have lower peak amplitudes than the real signal and so can be removed by passing the output through a discriminator circuit which allows only those pulses greater than a pre-selected amplitude to pass.

A second problem which must be overcome, particularly with the lighter chemical elements, is that two or more wavelengths may be found at the same angle of the analysing crystal. This occurs when the term n in the Bragg equation has a value of 2 or 3 in place of the usual value of 1. Under these conditions the corresponding wavelength

is one half or one third of the required value. However since both types of counter produce output pulses which are proportional to the energy of the incoming quanta, the pulses arising from these so-called second or third order reflections are two or three times as large as the required pulses.

In order to overcome this problem the simple discriminator is replaced by a full pulse height analyser. This unit will pass only those pulses which fall in a particular range of pulse heights. As a result it is able to reject both low level noise pulses and pulses due to higher order reflections, and only pulses from the required element will appear at its output.

Since the pulse heights increase in a regular manner from the lighter to the



The sample changer provides fast automatic loading of samples into the spectrometer.

X-ray spectroscopy



A mixture of analytical and reference samples can be analysed in a preset sequence.

heavier elements it is necessary to alter the settings of the pulse height analyser for each new element which is to be measured. These changes are usually made automatically by the instrument on the basis of a preset program.

Pulse counting


The pulses leaving either the discriminator or the pulse height analyser may be handled in two different ways. In the first method the pulse stream is sent to a pulse rate metering circuit which produces a DC signal whose amplitude is proportional to the rate at which pulses are supplied to it.

If the analysing crystal and detector system is moved at a constant angular velocity and the output of the count rate meter circuit is fed to a strip chart

recorder, a recording of the type shown in Fig. 4 will result. This allows identification to be made of the elements in the sample from the position of the individual peaks, and a rough estimate of their concentrations to be made from the height of the peaks.

However the instrument is more commonly used for routine chemical analysis where the elements present are known in advance and a precise estimate of their concentrations is required. In this case the analysing crystal and detector system is moved directly to the angles corresponding to the elements to be measured and held at each of these angles while a measurement is made.

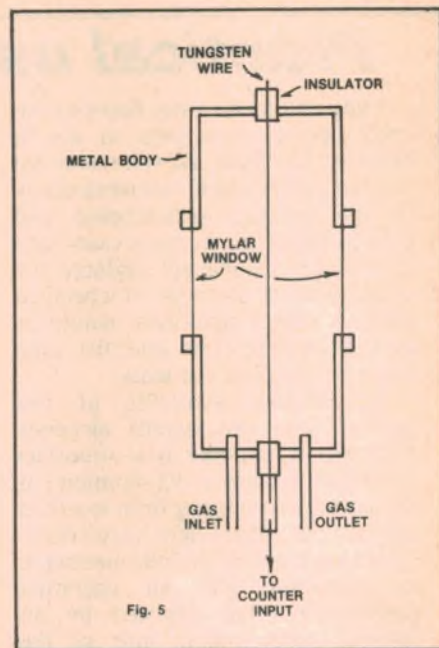The measurement is carried out by feeding the pulses from either the discriminator or the pulse height




analyser directly to a pulse counter. The pulses may either be counted for a fixed time or until the sample has received a fixed dose of x-rays. If the second method is used a small separate system is used to produce a stream of pulses whose rate is proportional to the output of the x-ray tube. This pulse stream is fed to a separate (reference) counter.

Both counters are set to zero at the start of the measurement and both are then allowed to run until the reference counter reaches a pre-selected number. At this time the analytical counter is automatically stopped and the accumulated total is printed out. This method is relatively insensitive to variations in the output of the x-ray tube and produces the most precise results. On the other hand, if counting is carried out for a fixed time, a very high stability in the x-ray source is required if reproducible results are to be obtained.

Final processing

In most cases results obtained from the instrument are not able to be used directly due to several interfering factors which are always present. The most serious of these effects is the fact that every element in the sample interferes to a greater or lesser extent with the measurement of every other element. This interference is of a complex nature due mainly to absorption by the interfering element of both the exciting beam of x-rays and of the fluorescent radiation which is generated in the sample.

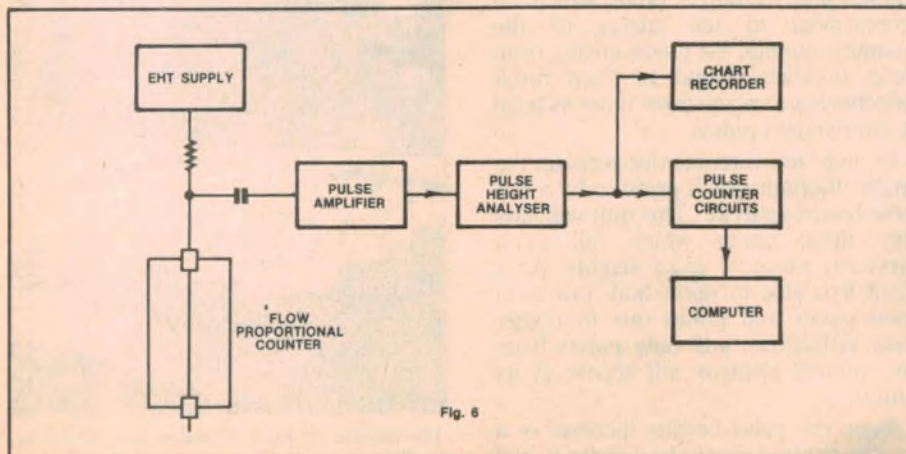These interferences can be corrected by means of a computer which is an integral part of the instrument. All the required settings for the operations are carried out automatically.



IC17106	18.50	74H106	2.50	74LS180	1.00	MM58174	19.50	SC152D	6.90	MRF455	37.00	VN88A	3.95	74148	2.00	FD1771	18.00	78L05	1.20
IC17110	19.50	74H108	2.50	74LS181	80	MM58303	7.00	C103YY	.90	MRF475	7.70	25C372	1.95	74150	1.50	FD1791	(8878)	78L12	7.30
IC17117	21.50	74H110	4.00	74LS182	1.50	MM58309	14.50	C103B	.90	MRF803	19.50	25C495	2.95	74151	2.00	FD1793	(8877)	78L24	1.20
IC17611	6.90	74H114	1.10	74LS183	1.50	MM58348	1.50	C106B	4.00	MRF841	49.00	25C710D	1.95	74154	1.75	FD1793	(8877)	LM309K	1.20
IC17612	6.90	74H183	7.90	74LS184	60	LM0002	9.50	C122D	2.50	MRF901	3.75	25C800F	1.95	74155	2.00	FD1795	39.00	LM324C	1.90
IC17660	5.90			74LS185	1.00	LH0024CH	9.50	C122E	2.95	MRF901	3.75	25C915A	1.95	74157	1.00	WD1681	29.50	LM317K	4.50
IC17663	4.90	74C		74LS186	2.55	LH0070	9.50	C268D	8.50	MRF131	1.90	25C945A	1.95	74158	1.00	WD1681	29.50	LM317HV	9.50
IC17664	4.90	74C00	.50	74LS187	8.50	LH0071	9.50	C268E	8.50	MRF131	1.90	25C945A	1.95	74159	1.00	WD1681	29.50	LM317Z	7.50
ICM7211	12.50	74C02	.60	74LS173	.90	LO161	1.50	2N2646	1.20	TIP31A	70	25C1018	4.95	74160	1.00	WD1933	59.00	LM3500	1.50
ICM7216A	48.50	74C04	.80	74LS174	.90	LO162	2.90	2N2647	2.50	TIP31C	70	25C1018	4.95	74161	1.00	WD1933	59.00	LM3500	1.50
ICM7218A	48.50	74C10	.80	74LS175	.90	LO163	2.90	2N2647	2.50	TIP31C	70	25C1018	4.95	74162	1.00	WD1933	59.00	LM3500	1.50
ICM7219A	44.50	74C14	1.40	74LS190	1.50	LO172	2.30	TRANS		TIP32B	70	25C1096	2.95	74163	1.40	WD1933	59.00	LM3500	1.50
ICM7217A	48.50	74C20	.80	74LS191	1.20	LO173	3.20	AC125	1.20	TIP41C	1.50	25C1217	2.95	74164	1.20	WD1933	59.00	LM3500	1.50
ICM7220	18.50	74C32	.80	74LS192	1.20	LO174	4.90	AC126	1.20	TIP42A	1.40	25C1306	6.30	74166	1.00	WD1933	59.00	LM3500	1.50
ICM7221A	18.50	74C42	1.90	74LS194	1.20	LO182	2.50	AC127	1.20	TIP42C	1.50	25C1419	2.95	74167	2.20	WD1933	59.00	LM3500	1.50
ICM7224A	74C48	2.50	74LS195	.90	LO183	2.90	AC187	1.50	TIP50	2.20	25C1449	1.95	74174	1.45	WD1933	59.00	LM3500	1.50	
ICM7226A	74C74	1.40	74LS196	.90	LO184	3.45	AC188	1.50	TIP53	2.50	25C1874	1.95	74175	1.45	WD1933	59.00	LM3500	1.50	
ICM7227A	48.50	74C78	1.90	74LS221	2.00	TCA220	9.50	AD189	3.40	TIP111	1.50	25D288	2.95	74177	1.45	WD1933	59.00	LM3500	1.50
ICM7271A	19.50	74C83	2.30	74LS240	1.90	TCA280	1.50	AD189	3.40	TIP116	1.50	25D288	2.95	74178	2.15	WD1933	59.00	LM3500	1.50
ICM7213A	15.50	74C85	2.30	74LS241	1.90	TDA1024	2.80	AF118	2.90	TIP117	1.50	25D288	2.95	74179	2.15	WD1933	59.00	LM3500	1.50
ICM7240	7.50	74C90	1.90	74LS242	1.90	T2205P	3.90	AF127	1.50	TIP120	1.50	25K45	3.95	74180	1.20	WD1933	59.00	LM3500	1.50
ICM7250	7.90	74C95	2.00	74LS244	1.90	UAA170	5.95	BC107	50	TIP121	1.50	25K45	3.95	74181	1.20	WD1933	59.00	LM3500	1.50
ICM7555	2.75	74C107	8.50	74LS248	1.50	UAA180	3.75	BC108	50	TIP122	1.50	25K45	3.95	74182	1.20	WD1933	59.00	LM3500	1.50
ICM7556	2.95	74C154	9.90	74LS249	1.60	LM301H	1.50	BC178	60	TIP125	1.50	25K45	3.95	74183	1.20	WD1933	59.00	LM3500	1.50
74500	60	74C160	1.90	74LS251	1.50	LM302H	6.50	BC179	60	TIP125	1.50	25K45	3.95	74184	1.20	WD1933	59.00	LM3500	1.50
74502	1.00	74C151	1.90	74LS252	1.20	LM307CM	1.00	BC212	40	TIP127	1.50	25K45	3.95	74185	1.20	WD1933	59.00	LM3500	1.50
74504	1.00	74C157	1.90	74LS258	1.50	LM308H	1.90	BC320	40	TIP127	1.50	25K45	3.95	74186	1.20	WD1933	59.00	LM3500	1.50
74505	1.50	74C160	1.90	74LS266	1.20	LM310M	3.20	BC327	40	TIP127	1.50	25K45	3.95	74187	1.20	WD1933	59.00	LM3500	1.50
74506	1.50	74C161	1.90	74LS273	1.95	LM310M	3.20	BC327	40	TIP127	1.50	25K45	3.95	74188	1.20	WD1933	59.00	LM3500	1.50
74510	1.00	74C167	1.90	74LS275	6.80	LM311	1.00	BC338	40	TIP127	1.50	25K45	3.95	74189	1.20	WD1933	59.00	LM3500	1.50
74511	1.00	74C167	1.90	74LS275	6.80	LM311	1.00	BC338	40	TIP127	1.50	25K45	3.95	74190	1.20	WD1933	59.00	LM3500	1.50
74515	1.60	74C181	1.90	74LS283	1.90	LM317K	4.50	BC348	40	TIP127	1.50	25K45	3.95	74191	1.20	WD1933	59.00	LM3500	1.50
74520	1.20	74C192	2.00	74LS290	1.50	LM318	4.90	BC349	40	TIP127	1.50	25K45	3.95	74192	1.20	WD1933	59.00	LM3500	1.50
74522	1.50	74C163	2.00	74LS293	1.90	LM322	1.00	BC354	40	TIP127	1.50	25K45	3.95	74193	1.20	WD1933	59.00	LM3500	1.50
74530	1.00	74C164	2.50	74LS295	1.75	LM325	4.50	BC358	40	TIP127	1.50	25K45	3.95	74194	1.20	WD1933	59.00	LM3500	1.50
74532	1.00	74C185	2.50	74LS297	6.50	LM326	4.50	BC357	40	TIP127	1.50	25K45	3.95	74195	1.20	WD1933	59.00	LM3500	1.50
74537	1.70	74C174	1.90	74LS299	1.20	LM329D	9.00	BC358	40	TIP127	1.50	25K45	3.95	74196	1.20	WD1933	59.00	LM3500	1.50
74538	1.70	74C175	1.90	74LS320	3.95	LM335Z	2.20	BC359	40	TIP127	1.50	25K45	3.95	74197	1.20	WD1933	59.00	LM3500	1.50
74540	1.20	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74198	1.20	WD1933	59.00	LM3500	1.50
74541	8.00	74C192	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74199	1.20	WD1933	59.00	LM3500	1.50
74544	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74200	1.20	WD1933	59.00	LM3500	1.50
74545	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74201	1.20	WD1933	59.00	LM3500	1.50
74546	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74202	1.20	WD1933	59.00	LM3500	1.50
74547	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74203	1.20	WD1933	59.00	LM3500	1.50
74548	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74204	1.20	WD1933	59.00	LM3500	1.50
74549	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74205	1.20	WD1933	59.00	LM3500	1.50
74550	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74206	1.20	WD1933	59.00	LM3500	1.50
74551	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74207	1.20	WD1933	59.00	LM3500	1.50
74552	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74208	1.20	WD1933	59.00	LM3500	1.50
74553	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74209	1.20	WD1933	59.00	LM3500	1.50
74554	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74210	1.20	WD1933	59.00	LM3500	1.50
74555	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74211	1.20	WD1933	59.00	LM3500	1.50
74556	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74212	1.20	WD1933	59.00	LM3500	1.50
74557	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74213	1.20	WD1933	59.00	LM3500	1.50
74558	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74214	1.20	WD1933	59.00	LM3500	1.50
74559	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74215	1.20	WD1933	59.00	LM3500	1.50
74560	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74216	1.20	WD1933	59.00	LM3500	1.50
74561	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74217	1.20	WD1933	59.00	LM3500	1.50
74562	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74218	1.20	WD1933	59.00	LM3500	1.50
74563	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74219	1.20	WD1933	59.00	LM3500	1.50
74564	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74220	1.20	WD1933	59.00	LM3500	1.50
74565	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74221	1.20	WD1933	59.00	LM3500	1.50
74566	1.60	74C193	2.00	74LS323	3.95	LM338 2.5V		BC450	50	TIP127	1.50	25K45	3.95	74222					

We've got the kits at

LATEST KITS!



MULTI SECTOR ALARM STATION

Protect your home from intruders with this up-to-the-minute burglar alarm system, it's easy to build, costs less than equivalent commercial units, and features eight separate units, individual sector control, battery back up and self-test facility.

Specifications:

- Eight sectors with LED status indication.
- Two delayed entry sectors.
- Variable exit, entry and alarm time settings: entry delay variable between 10 and 75 seconds; exit delay variable between 5 and 45 seconds; alarm time variable between 1 and 15 minutes.
- Resistive loop sensing suits both normally open and normally closed alarm sensors.
- Battery back-up with in-built charger circuit.
- Built-in siren driver.

Complete kit including deluxe prepunched metal work and electronics for only...

Cat. K85900 \$119



LOW BATTERY VOLTAGE INDICATOR

Knowing your batteries are about to give up on you could save many an embarrassing situation. This simple low cost project will give you early warning of power failure, and makes a handy beginner's project.

(ETI 280, March '85)

Cat. K42800 \$7.95



PARALLEL PRINTER SWITCH

Tired of plug swapping when ever you want to change from one printer to another? This low-cost project should suit you down to the ground. It lets you have two Centronics-type printers connected up permanently, so that you can select one or the other at the flick of a switch.

(ETI 666, Feb '85)

Cat. 46660 \$69.95



STEREO ENHANCER

The best thing about stereo is that it sounds good! The greatest stereo hi-fi system loses its magnificence if the effect is so narrow you can't hear it. This project lets you cheat on being cheated and creates an enhanced stereo effect with a small unit which attaches to your amp.

(ETI 1405, ETI, MAR '85)

Cat. K54050 \$79.50



MICROBEE ENHANCER 1

This brand new, totally amazing expansion unit for the Microbee owners/users! Most expansion units up to this time offered at best only one or other features, and this made it impossible to run, say, complex sound effects mingled with speech. The Enhancer 1 will do all this and much more as well. It is quite amazing how much has been shoe-horned into this compact unit. The Enhancer 1's many powerful features include:

- Two ATARI/COMMODORE/COLECO/SEARS type joystick inputs
- Two TRS COLOR COMPUTER type joystick inputs
- Allows the connection of Touch Pads, Paddles, Proportional Joysticks, Trakball Mice, temperature sensors, lights level sensors, transducers, etc. etc!
- A 4 voice music/sound effects synthesizer
- A real time clock
- Unlimited vocabulary speech synthesizer (option)
- Parallel printer interface (option)
- A built-in speaker with volume control

Listings of all necessary routines for use:

- An impressive demonstration program package
- Compatible to all Microbees
- All units carry a 90 day warranty and servicing is also available
- Digital recording and playback of speech and sound
- An 8 channel analog to digital converter with variable voltage or variable resistance type analog inputs and also user selectable resolution from 1 to 9 bits
- A digital to analog converter with selectable resolution from 1-8 bits
- Allows automatic data acquisition and logging
- 5 digital input lines, 4 digital output lines
- A voice input channel
- A 40 pin experimental socket with all 8 analog inputs, 5 digital inputs, 4 digital outputs, 3.58 MHz buffered clock, sound output (so that you can play the sound effects through your HI FI), 3 high resolution voltage comparators, DAC output etc.

The amazing Microbee Enhancer is available exclusively from Rod Irving Electronics.

Cat. \$149

Complete kit including deluxe prepunched metal work and electronics for only...

Cat. K42800 \$7.95

Knowing your batteries are about to give up on you could save many an embarrassing situation. This simple low cost project will give you early warning of power failure, and makes a handy beginner's project.

(ETI 280, March '85)

Cat. K42800 \$7.95

The amazing Microbee Enhancer is available exclusively from Rod Irving Electronics.

Cat. \$149

TALKING ELECTRONICS KITS!

HEADLIGHT REMINDERS Cat. K80022 \$12.90

IC POCKET RADIOS Cat. K80023 \$10.80

LED DICE Cat. K80024 \$9.05

LED ZEPLINS Cat. K80025 \$7.85

LIGHT THE LED Cat. K80026 \$4.60

LOGIC DESIGNER (with PC) Cat. K80027 \$20.90

LOGIC PROBES Cat. K80028 \$11.55

LOGIC DESIGNER (without PC) Cat. K80029 \$17.60

LOTTO SELECTORS Cat. K80030 \$16.50

BLACK JACK

Cat. K80001 \$11.00

CAPACITANCE METER Cat. K80002 \$6.25

CLOCKS (Incl. PCB) Cat. K80003 \$22.80

CLOCKS without PCB Cat. K80004 \$19.50

COMBINATION LOCKS Cat. K80005 \$7.50

COUNTER MODULE Cat. K80006 \$21.70

7 SEGMENT DISPLAY Cat. K80007 \$11.40

CUBE PUZZLE Cat. K80008 \$17.90

DIGI CHASER Cat. K80009 \$17.40

DIODE TESTER Cat. K80010 \$3.30

KEN'S DUAL PSU. Cat. K80011 \$11.80

DUAL TRACKING PSU. Cat. K80012 \$18.90

8x8 DISPLAY Cat. K80013 \$22.80

DUAL TRACKING PSU. (without PCB) Cat. K80014 \$15.60

EGG TIMER Cat. K80015 \$8.30

8W AMPLIFIER Cat. K80016 \$9.70

EXPERIMENTER BOARD Cat. K80017 \$14.30

EXPERIMETER DECK Cat. K80018 \$17.55

HANGMAN with PC Cat. K80019 \$12.50

FM BUGS Cat. K80020 \$6.80

HANGMAN with no PC Cat. K80021 \$9.20

PROGRAMMABLE COUNTER Cat. K80041 \$11.80

AUTO RESET Cat. K80042 \$9.70

QUICK DRAW Cat. K80043 \$3.90

RAM STACKS Cat. K80044 \$9.70

RELAY DRIVER BOARD Cat. K80045 \$28.40

ROULED Cat. K80046 \$8.50

SQUARE WAVE OSCILLATOR Cat. K80047 \$4.70

STEREO MINI MIXER Cat. K80048 \$23.10

STEREO PRE AMPS Cat. K80049 \$13.20

SIMPLICITY AMPS Cat. K80050 \$6.80

STEREO VU METERS (no PC) Cat. K80051 \$10.70

TRAIN SIGNALS Cat. K80052 \$7.70

STEREO VU METER (with PC) Cat. K80053 \$14.00

TOUCH PUZZLE Cat. K80054 \$6.25

TRAIN THROTTLE MK11 Cat. K80055 \$4.30

TREMOLO Cat. K80056 \$3.80

TEC 1A Cat. K80057 \$95.00

STAGE-1 KIT Cat. K80058 \$89.95

SERIES 5000 PRICES SLASHED!

By directly importing and a more technically orientated organisation, ROD IRVING ELECTRONICS can bring you these products at lower prices than their competitors. Enjoy the many other advantages of RIE Series 5000 kits such as "Super Finish" front panels at no extra cost, top quality components supplied throughout. Over 1,000 Sold.

For those who haven't that time and want a quality hi-fi, we also sell the Series 5000 kits Assembled and Tested.



POWER AMPLIFIER

WHY YOU SHOULD BUY A "ROD IRVING ELECTRONICS" SERIES 5000 POWER AMPLIFIER.

- ★ 1% Metal Film resistors are used where possible.
- ★ Aluminium case as per the original article.
- ★ All components are top quality
- ★ Over 1000 of these kits now sold.
- ★ Super Finish front panel supplied at no extra cost.

Please note that the "Superb Quality" Heatsink for the Power Amplifier was designed and developed by ROD IRVING ELECTRONICS and is being supplied to other kit suppliers.

SPECIFICATIONS: 150 W RMS into 4 ohms
 PPOWER OUTPUT: 100 W RMS into 8 ohms (±55 V SUPPLY)
 FREQUENCY RESPONSE: 8 Hz to 20 KHz +0, -0.4 dB 2.8 Hz to 65 KHz -0.3 dB NOTE: These figures are determined solely by passive filters
 INPUT SENSITIVITY: 1 V RMS for 100 W output
 HUM: 100 dB below full output (flat)
 NOISE: 11.6 dB below full output (flat, 20 KHz bandwidth)
 2nd HARMONIC DISTORTION: <0.001% at 1 KHz (0.0007% on Prototypes) at 100 W output using a ±55 V SUPPLY rated at 4A continuous <0.003% at 10 KHz and 100 W
 3rd HARMONIC DISTORTION: <0.0003% for all frequencies less than 10 KHz and all powers below clipping
 TOTAL HARMONIC DISTORTION: Determined by 2nd Harmonic Distortion (see above)
 INTERMODULATION DISTORTION: 0.003% at 100 W (50 Hz and 7 KHz mixed 4:1)
 STABILITY: Unconditional

Cat. K44771. Assembled and Tested \$499



PREAMPLIFIER

THE ADVANTAGES OF BUYING A "ROD IRVING ELECTRONICS" SERIES 5000 PREAMPLIFIER KIT ARE:

- ★ 1% Metal Film Resistors are supplied
- ★ 14 Metres of Low Capacitance Shielded Cable are supplied (a bit extra in case of mistakes).
- ★ English "Lorlin" switches are supplied (no substitutes here).
- ★ Specially imported black anodised aluminium knobs.

Available Assembled and Tested. (We believe that dollar for dollar there is not a commercial unit available that sounds as good.)

SPECIFICATIONS:
 FREQUENCY RESPONSE: High-level input: 15 Hz-130 KHz +0, -1 dB Low-Level input - conforms to RIAA equalisation ±0.2 dB
 DISTORTION: 1 KHz <0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation)
 S/N NOISE: High-Level input, master full, with respect to 300 mV input signal at full output (1.2 V) >92 dB flat >100 dB A-weighted MM input, master full, with respect to full output (1.2 V) at 5 mV input 50 ohms source resistance connected >86 dB flat 92 dB A-weighted MC input, master full, with respect to full output (1.2 V) and 200 uV input signal >71 dB flat >75 dB A-weighted

Cat. K44791. Assembled and Tested \$599



THIRD OCTAVE GRAPHIC EQUALIZER


SPECIFICATIONS:
 BANDS: 28 Bands from 31.5 Hz to 16 KHz.
 NOISE: <0.008 mV, sliders at 0, gain at 0 (-102 dB0).
 20 KHz BANDWIDTH DISTORTION: 0.007% at 300 mV signal, sliders at 0, gain at 0; maximum 0.01%, sliders at minimum.
 FREQUENCY RESPONSE: 12 Hz-105 KHz, +0, -1 dB, all controls flat.

BOOST AND CUT: 14 dB. 1 Unit... \$199

Cat. K44590 2 Units... \$379

POST & PACKING: \$10 per SERIES 5000 KIT.


Rod Irving Electronics!

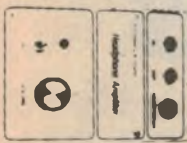

HEADPHONE AMPLIFIER
PRACTICE WITHOUT ANNOYING THE FAMILY!
 If you play any type of electronic instrument this headphone amplifier will surely interest you. It will let you practice for hours without upsetting the household or you can use it to monitor your own instrument in the midst of a rowdy jam session. (EA Feb. 84) 83MA11
 Cat. K83011 **\$28.00**



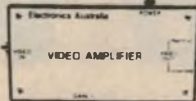LAB SUPPLY
 Fully variable 0-40V current limited 0-5A supply with both voltage and current metering (two ranges: 0-0.5A/0-5A). This employs a conventional series pass regulator, not a switchmode type with its attendant problems, but dissipation is reduced by unique relay switching system switching between taps on the transformer secondary. (ETI May 83) ETI 163
 Cat. K41630 **\$175.00**




VIDEO AMPLIFIER
 Bothered by smeary colours, signal beats and RF interference on your computer display? Throw away that cheap and nasty RF modulator and use a direct video connection instead, it's much better! The Video Amplifier features adjustable gain and provides both normal and inverted outputs. Power is derived from a 12V DC plugback supply. (EA Aug. 83) 83VA8
 Cat. K83081 **\$15.00**



COMPUTER DRIVEN RADIO-TELETYPE TRANSCIVER
 Here's what you've been asking for, a full transmit-receive system for computer driven radio teletype station. The software provides all the latest "whizz-bangs" like split-screen operation, automatically repeating test message, printer output and more. The hardware uses tried and proven techniques. White designed to team with the popular Microbee. Tips are available on interfacing the unit to other computers. (ETI Nov. 84) ETI 755
 Cat. K47550 **\$139.00**



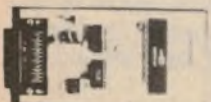
ELECTRONIC MOUSETRAP
 This clever electronic mousetrap disposes of mice instantly and mercifully, without fail, and resets itself automatically. They'll never get away with the cheese again! (ETI Aug. 84) ETI 1524
 Cat. K55240 **\$29.95**




MICROBEE SERIAL-TO-PARALLEL INTERFACE
 Most microcomputers worth owning have an RS232 connector, or port, through which serial communications (input/output) is conducted. It is a convention that, for listing on a printer, the BASIC LIST or LPRINT command assumes a printer is connected to the RS232 port. Problem is, serial interface printers are more expensive than parallel Centronics interface printers. Save money by building this interface. (ETI Jan. 84) ETI 675
 Cat. K46750 **\$59.00**




CAR IGNITION KILLER
 Most car burglar alarms are easily circumvented, but not this cunning "Ignition Killer". This sneaky anti-theft device uses a 555 timer to place an intermittent short circuit across the points. Until disabled by its hidden switch the circuit effectively makes the car undriveable — a sure deterrent to thieves! (EA Feb. 84) 84AU1
 Cat. K84010 **\$16.95**
 (Our kit includes the box!)

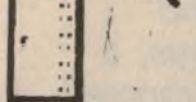

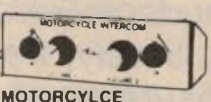
TRANSISTOR TESTER
1000's SOLD
 Have you ever desoldered a suspect transistor, only to find that it checks OK? Trouble-shooting exercises are often hindered by this type of false alarm, but many of them could be avoided with an "in-circuit" component tester, such as the EA Handy Tester. (EA Sept. 83) 83TT8
 Cat. K83080 **\$15.00**



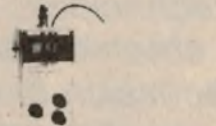
MOTORCYCLE INTERCOM
OVER 300 SOLD!
 Motorcycleing is fun, but the conversation between rider and passenger is usually just not possible. But build this intercom and you can converse with your passenger at any time while you are on the move. There are no "push-to-talk" buttons, adjustable volume and it's easy to build! (EA Feb. 84) 84MC2
 Cat. K804020 **\$45.00**



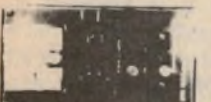
PH METER KIT
 Build this pH meter for the swimming pool season is here again! From swimming pools to fish tanks to gardening, this pH meter has many applications around the home. This unit features a large 3 1/2 digit liquid crystal display and resolution to 0.1 pH units, making it suitable for use in the laboratory as well. (EA Dec. 82) 82PH12
 Cat. K82123 **\$139**



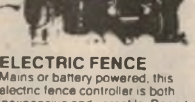LOW OHMS METER
 How many times have you cursed your Multimeter when you had to measure a low-value resistance? Well with the "Low Ohms Meter" you can solve those old problems and in fact measure resistance from 100 Ohms down to 0.005 Ohms. (ETI Nov. 81) ETI 158
 Cat. K41580 **\$34.50**



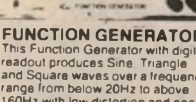
ELECTRIC FENCE
 Mains or battery powered, this electric fence controller is both inexpensive and versatile. Based on an automotive ignition coil, it should prove an adequate deterrent to all manner of livestock. Additionally, its operation conforms to the relevant clauses of Australian SIND 3129. (EA Sept. 82) 82EF9
 Cat. K82092 **\$19.50**



FUNCTION GENERATOR
 This Function Generator with digital readout produces Sine, Triangle and Square waves over a frequency range from below 20Hz to above 160KHz with low distortion and good envelope stability. It has an inbuilt four-digit frequency counter for ease and accuracy of frequency setting. (EA April. 82) 82AQ3A/B
 Cat. K82040 **\$87.50**
 Cat. K82041



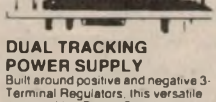
EPROM PROGRAMMER
EPI
 No need for a Micro with EA's great Eprom Programmer suitable for 2716/2758 Eproms. (EA Jan. 82) 82EP1
 Cat. K82013 **\$47.50**
 With Textool Sockets **\$59.95**




DUAL TRACKING POWER SUPPLY
 Built around positive and negative 3-Terminal Regulators, this versatile dual tracking Power Supply can provide voltages up to 2A. In addition the Supply features a fixed +5V 0.3A output and is completely protected against short circuits, overloads and thermal runaway. (EA March 82) 82PS2
 Cat. K82030 **\$87.50**



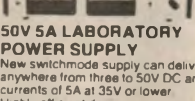PHONE MINDER
 Dubbed the Phone Minder, this handy gadget functions as both a bell extender and paging unit, or it can perform either function separately. (EA Feb. 84) 84TP2
 Cat. K84021 **\$24.00**



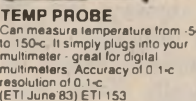50V 5A LABORATORY POWER SUPPLY
 New switchmode supply can deliver anywhere from three to 50V DC and currents of 5A at 35V or lower. Highly efficient design. (EA May June 83) 83PS5
 Cat. K83050 **\$149**



TEMP PROBE
 Can measure temperature from -50 to +150°C. It simply plugs into your multimeter - great for digital multimeters. Accuracy of 0.1°C resolution of 0.1°C. (ETI June 83) ETI 153
 Cat. K41530 **\$24.50**



EFFECTS UNIT
 An "effects unit" that can create phasing, flanging, echo, reverb and vibrato effects. (EA June 83) 83GA6
 Cat. K83060 **\$75.00**




VIDEO ENHANCER
100's SOLD
 Like tone controls in a hi-fi amplifier touch up the signal with this Video Enhancer. (EA Oct. 83) 83VE10
 Cat. K83100 **\$35.00**



SOUND SIMULATOR FOR MODEL TRAINS
 Fancy a diesel sound simulator for your model train layout? This circuit mounts inside the train for added realism and even varies its speed according to the throttle setting. (EA Nov. 84)
 Cat. K84110 **\$18.00**



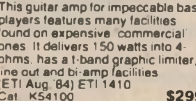
RADIOTELETYPE CONVERTER FOR THE MICROBEE
 Have your computer print the latest news from the international shortwave news service. Just hook up this project between your short wave receivers audio output and the MicroBee parallel port. A simple bit of software does the decoding. Can be hooked up to other computers too. (ETI Apr. 83)
 Cat. K82050 **\$20.00**



150W BASS AMP
 This guitar amp for impeccable bass players features many facilities found on expensive commercial ones. It delivers 150 watts into 4-ohms, has a 1-band graphic limiter, line out and bi-amp facilities. (ETI Aug. 84) ETI 1410
 Cat. K54100 **\$299**



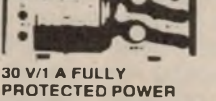EA AM STEREO DECODER
 AM stereo is now broadcast in Australia on an experimental basis. This add-on decoder works with the Motorola C-QUAM system. (EA Oct. 84) 84MS10
 Cat. K84101 **\$24.95**




30V 1A FULLY PROTECTED POWER SUPPLY
 The last power supply we did was the popularly popular ETI-131. This low cost supply features full protection, output variation from 0V to 30V and selectable current limit. Both voltage and current metering is provided. (ETI Dec. 83) ETI 162
 Cat. K41620 **\$52.50**




DIRECTIONAL DOOR MINDER
 Most electronic door minders function by having a beam of light shining across doorway interrupted, but are incapable of detecting whether the light beam is broken by a person entering or leaving the room. This project overcomes that problem with the aid of digital logic. (ETI Nov. 84) ETI 278
 Cat. K42780 **\$29.95**



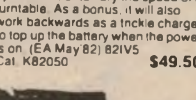
ELECTRIC DUMMY LOAD
 With this unit you can test power supplies at currents up to 15 Amps and voltage up to 60 Volts. It can "sink" up to 200 Watts on a static test and you can modulate the load to perform dynamic tests. (ETI Oct. 80) ETI 147
 Cat. K41470 **\$109**



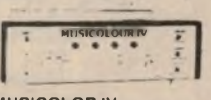40W INVERTER
 This 12 240V inverter can be used to power up mains appliances rated up to 40W or to vary the speed of a turntable. As a bonus, it will also work backwards as a trickle charger to top up the battery when the power is on. (EA May 82) 82IV5
 Cat. K82050 **\$49.50**



MUSICOLOR IV
 Add excitement to parties, card nights and discos with EAs Musicolor IV light show. This is the latest in the famous line of musicolors and it offers features such as four channel "color organ" plus four channel light chaser, front panel LED display, internal microphone, single sensitivity control plus opto-coupled switching for increased safety. (EA Aug. 81) 81MC8
 Cat. K81080 **\$89.00**

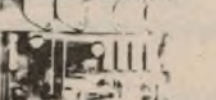

MOSFET POWER AMPLIFIER
 Employing Hiachi Mosfets, this power amplifier features a no compromise design and is rated to deliver 150W RMS maximum and features extremely low harmonic transient and intermodulation distortion. (ETI Jan. 81) ETI 477
 Cat. K44770 **\$69.50**

Remember.... We have over 260 Kits, most of which are in stock!!

WANTED

16-18yrs Shop Assistant(s)

If you're an electronics enthusiast and would like to work in electronics retail, we'd like to hear from you

Phone: Greg Boot (03) 663 6580

ROD IRVING ELECTRONICS
 425 High Street, NORTHCOTE, 3070 VICTORIA, AUSTRALIA
 Phone (03) 489 8866
 TELEX: AA 38897
 48-50 A Beckett Street, MELBOURNE, 3000 VICTORIA, AUSTRALIA
 Ph. (03) 663 6151
Mail Order and correspondence: P.O. BOX 235 NORTHCOTE 3070

MAIL ORDER HOT LINE

(03) 481 1436

POSTAGE RATES

\$11-\$9.99	\$2.00
\$10-\$24.99	\$3.00
\$25-\$49.99	\$4.00
\$50-\$99.99	\$5.00
\$100-\$199	\$7.50
\$200-\$499	\$10.00
\$500 plus	\$12.50

This is for basic postage only. Comet Road freight, bulky and fragile items will be charged at different rates.

Errors and omissions excepted

Baffles, boffles, boxes and vents

by NEVILLE WILLIAMS

While expressing appreciation for articles on current hifi technology, a reader from Parkdale in Victoria has entered a strong plea for a plain language discussion of loudspeakers and enclosures, old and new. Surely, he says, a modern fully sealed enclosure must "strangle" the loudspeaker? And whatever happened to that very sensible concept, the "boffle" box? We do our best to oblige.

In putting his request, correspondent (A.B.) adds: "I guess that my interest owes more to mechanical than to electrical engineering. What I am trying to sort out is the effect of various types of enclosure on the basic pumping action of a loudspeaker."

We'll refer to that concept later, but let's start at the beginning:

When an electrical drive signal is applied to a dynamic (ie, moving coil) loudspeaker, the cone moves back and forth in accordance with the instantaneous polarity, frequency and amplitude of the signal. As the cone moves forward, it creates a layer of compressed air at the front, and rarified air at the back; as it moves backward, the reverse applies.

The effect of such pressure pulses on the surrounding air can be compared to what happens when something disturbs the water in a still pond: waves can be observed radiating outwards from the source, effectively dispersing and propagating the original energy over a wide area.

Variations in instantaneous pressure produced by a loudspeaker cone in an invisible medium (air) are likewise dispersed and propagated in the form of sound waves.

Directional Effects

The pond analogy applies best to frequencies in the middle of the audio spectrum — from a few hundred to a few thousand Hertz. Over this range, sound

waves are propagated from an unmounted dynamic loudspeaker substantially through the full 360°.

Above about 4.5kHz, however, as the sonic wavelength diminishes and becomes smaller than the frontal dimensions of the cone, propagation from an ordinary dynamic loudspeaker becomes increasingly directional.

Depending, in part, on the size and shape of the cone, sound propagation to the sides diminishes, while that to the rear is shadowed, anyway, by the housing and magnet structure. What remains is predominantly a "beam" of high frequencies typically 20-40° wide along the frontal axis of the cone.

At frequencies below about 600Hz the situation is different again. With the cone moving in a given direction for a progressively longer period during each half-cycle, air under pressure on the one

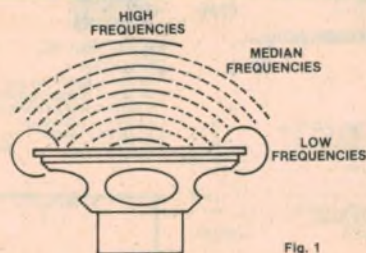


Fig. 1

Fig.1: The sound propagation pattern for an unmounted full-range loudspeaker. Baffling is necessary to prevent low frequency energy from being merely pumped back and forth around the edge of the housing.

side of the cone has time to flow around the edge of the housing to relieve the partial vacuum on the other side.

Instead of propagating a pattern of low frequency sound waves into the surrounding atmosphere, much of the system energy is wasted in simply pushing air back and forth around the edge of the housing.

Fig.1 depicts the sound propagation pattern of a typical full-range dynamic loudspeaker (unmounted) with the highest frequencies projected as a beam, the median frequencies widely dispersed, and the lowest frequencies confined mainly to the immediate vicinity of the cone.

Clearly, if the reproduction is to sound reasonably balanced, it is essential to achieve better propagation at the bass end. This is mainly what the article is all about: "Baffles, boffles, boxes and vents" — and their influence on low frequency response.

Bass Roll-off

In their loudspeaker literature, Philips (and others) describe the direct front-to-back path for bass energy as an "acoustic short-circuit". It becomes evident, they say, at frequencies below that at which the distance from front to back of the cone approximates one half wavelength. (For an unmounted driver, I take it upon myself to suggest a mean distance between points at about half the driver

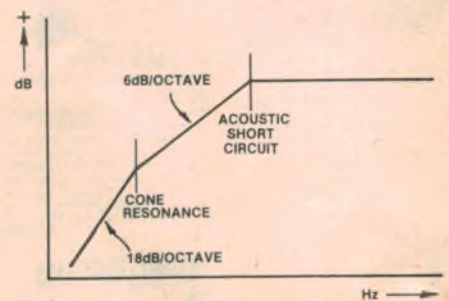


Fig. 2

Fig.2: The low frequency response of an unmounted loudspeaker diminishes at about 6dB/octave in the region of acoustic short-circuit and by a further 12dB/octave below the cone resonance.

radius).

Below this region, the effective response falls at the nominal rate of 6dB/octave, down to the system resonance. Below that again, the slope steepens to 18dB/octave (Fig.2).

It follows that physically large loudspeakers with (normally) a lower cone resonance will exhibit better bass response, unmounted, than their smaller counterparts — something that most will have noticed.

In fact, examples exist in commercial hifi systems and electronic organs of loudspeakers which, for bass response, rely primarily on jumbo size (and sometimes oddly shaped) cones, with only a modest amount of additional cabinet work. But while they may provide an interesting talking point, they can offer, at best, only a partial solution to the basic problem.

Baffling Essential

In the late '20s, the potential for improved bass response was a major reason for the rapid adoption of dynamic loudspeakers. It was accepted, however, that they would need to be mounted on a "baffle" of some sort for the advantage to be realised.

It might take the form of a rigid panel, possibly resting on the floor and/or mounted across a corner, to increase its effective area. Alternatively, the need might be met by an open-back radio cabinet, preferably as large and substantial as possible.

Either way, the basic purpose was to increase the path length between the front and rear of the cone, thereby pushing the region of acoustic short-circuit and low frequency roll-off further down in the range.

However, aspirations at the time were not all that demanding — at least for the mass market. After the moving iron horn and cone loudspeakers of the '20s (Fig.3) any bass seemed like good bass! Besides, other factors had to be considered:

- Supply, reliability and price in a booming, highly competitive market.

- Sensitivity, too, was vital and, in keenly priced, mass-produced models, that meant using a lightweight cone and a relatively short voice coil in a narrow magnetic gap.

- To maintain the voice coil central in the gap, and to keep cone excursions within acceptable limits, suspension systems had to be relatively stiff. As a result, the majority of such loudspeakers ended up with a prominent (high Q) cone resonance, commonly above 70Hz for 30cm models and higher again for their smaller counterparts.

When mounted in typical console radio cabinets, it was not unusual for the low frequency response to meet up with the cone resonance, which would then be

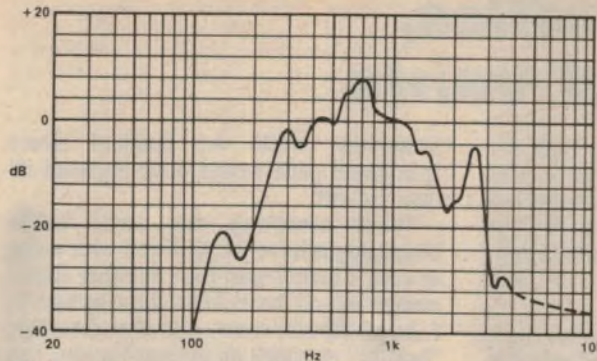


Fig. 3

Fig.3: The frequency response curve of a typical old-time horn loudspeaker — bad enough, without even considering the distortion! It is of little wonder that dynamic loudspeakers took over so rapidly.

heard loud and clear, resulting in the infamous "one-note bass" of the early '30s (Fig.4).

To curb it, designers came to rely on negative feedback in the amplifier to lower the impedance of pentode output stages and to provide a measure of electrical damping on the coil/cone system.

While budget-priced "radio" loudspeakers, with suitable circuitry, may provide acceptable sound for general listening, their potential for use in a high quality sound system is strictly limited, despite claims to the contrary over the years.

In any case, what might have rated as excellent in the days of indifferent signal sources could sound very ordinary in this, the digital era.

Hifi Loudspeakers

With rare exceptions, the starting point for a good loudspeaker system needs to be a high quality driver (or drivers) of which examples have been available since I first entered the industry in the early '30s.

I still look back with a certain anguish to the big full-range American Magnavox and Jensen models that I had to fit to other people's systems but could not afford myself! These were followed by a variety of British and European models, including big-name brands like

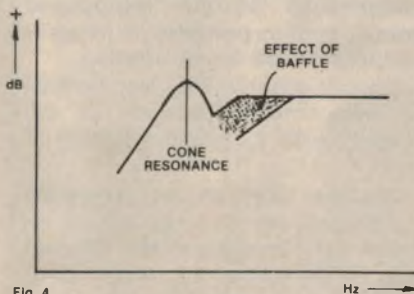


Fig. 4

Fig.4: Fitting a loudspeaker to a baffle pushes the 6dB/octave roll-off further down in the range. The cone resonance can become very prominent, as a result, if it is not sufficiently damped by the associated amplifier.

Goodmans, Wharfedale, Celestion and Philips.

Best described as "general purpose" hifi loudspeakers, they were generously proportioned (30-38cm diameter) with specially moulded (often curvilinear) cones, long travel voice coils and suspension, and a large magnet structure to ensure high sensitivity and good electrical damping with (commonly) power triode output stages. Their bass resonance was down around 45Hz but so well damped and so broad that it was usually difficult to pick by ear.

They certainly sounded impressive in a deluxe console or, less commonly, on a large suitably styled baffle made from heavy timber or, in the Wharfedale manner, from plywood layers filled with dry sand.

Extended Bass

But still not satisfied, individual enthusiasts and a generation of dedicated English hifi manufacturers aspired to a still further downward extension of the bass response, requiring the means to more effectively contain or control back radiation from the cone.

One logical — but not very practical — answer was to create an "infinite" baffle by mounting the loudspeaker: (1) in a dividing wall; (2) in the door of a capacious cupboard; (3) in the opening of a disused chimney, or (4) through the ceiling.

Apart from structural implications, however, other matters had to be considered like noise from the rear of the loudspeaker, unequal air pressure on the respective sides of the cone — and hungry rodents!

To quote Gilbert Briggs of Wharfedale: "Moral: don't use the mouse's living room as a speaker enclosure!"

So the tantalising problem remained: to devise an enclosure that would be self-contained, of practical dimensions and construction, and able to contain or control low frequency radiation from the rear of the cone; this — to use A.B.'s term — without "strangling" the loudspeaker!

Baffles, boffles, boxes and vents

(What should be added was that, for the most part, the effort was concentrated around general purpose hifi loudspeakers which, as a class, did not lend themselves to being crammed into "practical" sized enclosures of any description!)

The obvious starting point was a rigid, completely sealed box, still misguidedly described by some as an "infinite" baffle. While it may indeed have "contained" back radiation from the cone, it was (and still is) anything but "infinite" in its effect on cone behaviour.

In particular, the body of air trapped behind the cone, alternatively compressed and rarified by cone movement, acts as a supplementary spring, tending to restore the cone to its median position. It has the effect of raising both the frequency and the "Q" of the cone resonance, being particularly apparent with large loudspeakers in unduly small enclosures.

In the mono era, some enthusiasts nevertheless found it practicable to accommodate a "general purpose" hifi loudspeaker in a single large enclosure — 250 litres (9 cu ft) or more — tolerating a modest 5-10Hz rise in the bass resonance and restraining the "Q", if necessary, by partially filling or padding the enclosure.

Smaller Boxes?

But, especially with the arrival of stereo, 250-litre enclosures were out of the question for most enthusiasts. Nor did they relish the idea of small sealed enclosures, with their potentially traumatic effect on the resonance of typical loudspeakers, padding and filling notwithstanding.

The "boffle" box, mentioned by correspondent A.B., represented one of many attempts to get around the dilemma. I forget the finer details but we actually had a pair of them bracketed to the wall of the EA lab at one stage, for on-the-spot audio testing.

As I recall, they were about 45-50cm cubes, open at the back. But, behind the 30cm loudspeakers, was a succession of caneite panels and spacers, with a circular hole in each panel, progressively smaller towards the back.

The idea was that the panels would intercept and absorb middle and high frequency radiation from the rear of the cone and thus minimise standing waves in the box. This they probably did but, at the vital lower frequencies, their contribution would have been something of a gamble.

Air partly trapped behind the cone could still have affected its resonant

frequency, while the residual direct front/back path would have imposed its own roll-off.

While accepting that some boffle boxes might have worked well with some drivers, I feel certain that, in other cases, results would have been very ordinary. Like jumbo size cones, mentioned earlier, "boffles" provided an interesting idea but not a fundamental solution to the basic problem.

Among other approaches, popular at the time, was the acoustic labyrinth — an enclosure with internal partitions which formed a convolute path for the back radiation to a separate outlet port.

The object was to achieve an approximate half-cycle phase delay through the labyrinth at selected low frequencies, such that output from the port would reinforce direct radiation from the cone in the normal roll-off region.

Unfortunately, a suitably long acoustic path of sufficient cross-section to work well with a large loudspeaker can itself be quite large. If shortened, it will reinforce the wrong frequencies. If narrowed, or filled with fibrous material, it may raise the resonant frequency of the cone and achieve little else.

Much the same remarks apply to folded horn enclosures. If well executed (as by Paul Klipsch in the '40s) they can be very good, even if rather large and

Linear Phase Loudspeakers

In these systems, the treble, mid and low frequency drivers are mounted on the front panel in such a way as to equalise, as far as possible, the distance from each cone to a listener seated in the optimum listening area. The purpose is to maintain the correct phase relationship between the frequency components of the reproduced sound, both to preserve its integrity and to optimise stereo imaging.

Special attention may also be paid to the dividing network in the system, with the same objective in view.

The measures can be shown on instruments to have an effect on phase and waveshape but whether the difference is significant subjectively is open to argument.

Either way, linear phase design does not modify the need to pay full attention to basic requirements for proper bass response.

expensive. But, if scaled down in an effort to conserve space and cost, they become eminently forgettable!

Forgettable, too are many other examples of the enclosure maker's art from the immediate pre-and post-war period, based on earlier work, hunches, observation, enthusiasm — and an imperfect understanding of the principles involved! Prominent in this group is an array of smallish, highly "doctored" vented systems, yet to be discussed.

Most such creations are the product of an era in which those involved started out with a particular loudspeaker (or system) thereafter attempting, by empirical methods, to produce an enclosure to suit it. The inevitable result has been misinformation and confusion.

The Modern Approach

The present-day approach to hifi loudspeaker and enclosure design is reminiscent of the old adage: "If you can't beat 'em, join 'em!"

Instead of acquiring independently an ostensibly high performance loudspeaker (or system) and then trying — possibly against the odds — to devise an enclosure to go with it, the loudspeaker (or bass driver) and enclosure are chosen and/or designed, from the outset, to complement each other.

The concept is not new but, over the past 20-odd years, mathematical analysis and computer programs have emphasised its advantages, transforming what was once a rather tedious and empirical procedure into an exact science.

For a given loudspeaker, it is now possible to predict system performance for a range of enclosure dimensions. Or, given certain enclosure specifications, a design can be derived for a complementary driver. Yet again, for a certain performance target, the options for both driver and enclosure can be explored to discover the most practical combination — before any hardware is produced.

Computer aided design has focused mainly on fully sealed and on reflex (ie, vented) systems, both of which combine relative ease of construction with a wide range of options in terms of size, cost and performance.

Both can be presented as simple, rectangular boxes housing either a single full-range loudspeaker or a complete multi-way system with a dedicated bass driver. Alternatively, they can be constructed in a variety of shapes, provided the correct volume is retained.

Sealed Systems

In the case of fully sealed systems, the basic concept is to plan for a loudspeaker (or a bass driver) with a deliberately soft

ULTRA

THE NEW MUSICAL CHALLENGE FROM

SHURE®



MODEL 300

FREE YOURSELF
FROM THE
EXPERIENCES
AND BONDAGE
OF THE PAST



MODEL 500

ULTRA PRESENTS

THE NEW ESOTERIC HAND CRAFTED CARTRIDGES

SPECIFICATIONS

SPECIFICATIONS	ULTRA 500	ULTRA 400	ULTRA 300
Frequency Response	10 to 35kHz	10 to 30kHz	10 to 22kHz
Total Effective Mass	0.165mg	0.190mg	0.300mg
Dynamic Vertical Stylus Compliance	20µcm/dyne	14µcm/dyne	11µcm/dyne
Trackability @ 1.2g force in cm/sec peak recorded velocity	400Hz 42cm/sec 1kHz 65cm/sec 5kHz 100cm/sec 10kHz 75cm/sec	29cm/sec 51cm/sec 76cm/sec 64cm/sec	28cm/sec 38cm/sec 50cm/sec 44cm/sec
Channel Balance	within 1dB	within 1dB	within 1.5dB
Channel Separation (minimum)			
@ 1kHz	27dB	27dB	25dB
@ 10kHz	20dB	17dB	17dB
Optimum Tip Tracking Force	1.2g	1.2g	1.2g
Optimum Total Tone Arm Force (Dynamic Stabiliser Operating)	1.7g	1.7g	1.7g
Force Exerted by Dynamic Stabiliser	0.5g	0.5g	0.5g
Optimum Load	47kΩ//250pF	47kΩ//200 to 300pF	47kΩ//200 to 300pF
Output @ 1kHz, 5cm/sec peak recorded velocity	3.2mV	4.0mV	3.5mV
Inductance (typical @ 1kHz)	330mH	360mH	360mH
dc Resistance (typical)	815Ω	1kΩ	1kΩ
Net Weight	9.3g	4.5g	4.5g
Replacement Stylus	ULTRA 500S	ULTRA 400S	ULTRA 300S

TAKE IT FOR A SPIN
AND BRING YOUR
RECORDS TO LIFE

AUDIO ENGINEERS
342 KENT STREET,
SYDNEY

PH: (02) 29 6731



MODEL 400

C commodore 64
VIC-20
sinclair SPECTRUM



with our Speech Synthesisers from Currah. No software needs to be loaded, just plug the synthesiser onto your computer and it's ready to talk, using the sound on your TV.

An infinite vocabulary is achieved through use of allophones or sound syllables. These look just like they sound and are very easy to enter into your programmes. The Microspeech and Speech 64 have "speechware" available — synthesiser compatible software from commercial suppliers. Full instructions are provided for endless fun and education.

Speech 64 for Commodore 64 **\$69.00**
 Chatterbox for Vic 20 **\$66.50**
 Microspeech for Sinclair Spectrum **\$62.00**

Phone or send sae for FREE brochure — specify computer type.



Australian distributor:

dolphin computers

99 Reserve Road,
 ARTARMON, NSW 2064

Telephone: (02) 438-4933
 Telex: AA20677

At discerning computer shops or mail order from Dolphin. Airmail (software) \$11.00 per mail \$2.50, or via courier \$6.00. Enclose cheque/money order/Bankcard details. All prices include sales tax. All products guaranteed.

****Dealer enquiries welcome****

BUILD YOUR OWN SPEAKERS

The superb DYNAUDIO and SCAN-SPEAK drivers from Denmark are now available in Australia. These loudspeaker drivers are used by many superior brand named speakers, some of which sell for up to \$13,000 per pair. Here is your chance to design and build your own top speakers. If you prefer, you can use the designs and crossover networks we have available. All specifications are available on request, including 'Thiele & Small' parameters for design of bassreflex cabinets.



TRADE AND OEM
 INQUIRIES WELCOME.

Sole Australian Distributor:

SCAN AUDIO Pty. Ltd.
 P.O. Box 242, Hawthorn, 3122.
 Ph. (03) 819 5352

Baffles, boffles, boxes and vents

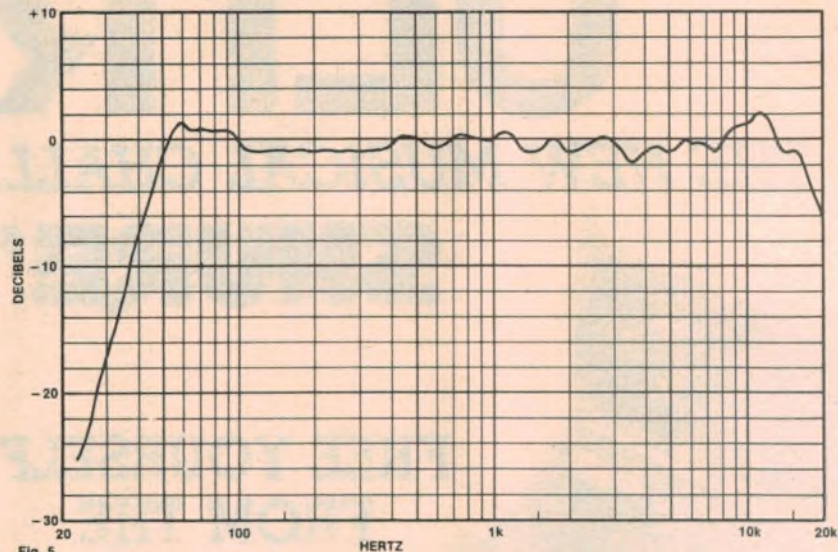


Fig. 5

Fig.5: The frequency response curve of a full-scale domestic loudspeaker system using Philips drivers and a Philips designed sealed enclosure. It could readily cope with low-end bass boost.

(compliant) suspension and a deliberately low cone resonance, typically below 30Hz.

Such a driver would be liable to damage by excessive cone excursion, if used on a flat baffle, in an open-back cabinet or an over-large sealed enclosure. But, by mounting it in a suitably small enclosure, the "stiffness" of the entrapped air supplements that of the mechanical suspension, affording greater protection from overdrive and raising the resonance to a still low but convenient frequency.

Instead of the enclosure "strangling" the loudspeaker, as was formerly the case, it becomes an essential part of the suspension. As well, it completely "contains" the back radiation, thereby solving the basic problem.

By way of example, a large, 3-way loudspeaker system marketed by Philips for commercial or home construction, includes a 30cm bass driver having a cone resonance, unmounted, of 20Hz. Installed in the recommended fully sealed 100-litre (3.6 cu ft) enclosure, the bass resonance rises to about 50Hz, giving full output at that frequency and a useful response extending to below 30Hz (Fig.5). Rated power handling capacity for the system is 100W.

At a more modest level, commercial sealed enclosures range downward in size to small "bookshelf" dimensions, often with a surprising performance for their size. They use proportionately smaller drivers, with a long travel voice coil to permit high output, relying heavily on the entrapped air to cushion the cone against excessive travel.

However, small wide-range fully sealed systems are, by nature,

comparatively insensitive, requiring more drive than their larger counterparts to produce an adequate level of sound in the listening room. Fortunately, this seldom poses a problem with modern solid state amplifiers.

One other point warrants repetition from page 100 of the February issue: If a sealed enclosure has been optimally designed to complement a particular driver, it is unwise to arbitrarily increase the enclosure volume with the idea of gaining extra bass response. The resonance of the system may indeed be moved to a lower frequency but the "Q" of the system could also be lowered (Fig. 6), causing the response curve to droop, with a marginal loss, rather than a gain in useful response.

Reflex Enclosures

Reflex (or vented) enclosures are a derivative of the historic Helmholtz

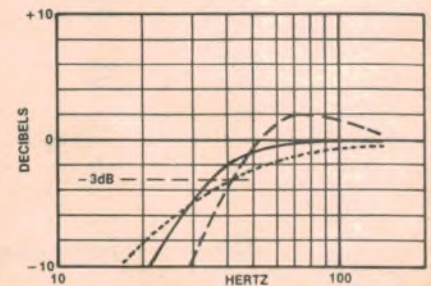


Fig. 6

Fig.6: The solid curve shows the bass response of a critically designed sealed enclosure. A too-small enclosure produces an undesirable peak (dashed) but too large causes the curve to droop (dotted).

Multidirectional Loudspeakers

Conventional stereo loudspeakers project sound towards the listener and are frequently judged on their ability to create a sharp stereo image.

Multidirectional loudspeakers, on the other hand, are designed to project middle and high frequencies in a variety of directions, often deliberately bouncing the sound off adjacent and rear walls.

The claim is that it is subjectively more natural, pleasant and relaxing to be surrounded by sound than to have it "squirted" at the listener from two sonically obvious sources.

It is largely a matter of individual preference but one thing is certain: an array of small loudspeakers to disperse middle and high frequencies does not obviate the need for adequate provision for the bass end.

resonator, involving an otherwise airtight cabinet, with a vent or tubular port, plus a mounting hole for a loudspeaker.

The volume of the enclosure and the dimensions of the vent are normally chosen such that a mutual acoustic resonance occurs at a frequency approximating the bass resonance of the loudspeaker. In this region, energy from the rear of the cone emerges from the vent, shifted sufficiently in phase to reinforce direct radiation from the front of the cone.

Effectively, the reflex system achieves a similar end result to the acoustic labyrinth — without the partitions. And, because it uses rather than suppresses energy from the rear of the cone, it offers

somewhat greater acoustic efficiency than the fully sealed system, particularly in the bass region.

One of the all-time champions of the method, Gilbert Briggs of Wharfedale, had this to say:

"From the point of view of size, cost and ease of construction, the vented enclosure seems to pay the highest dividends in terms of bass output, provided vent resonances below about 50Hz are adhered to. A higher resonance frequency may be obnoxious."

The vented system worked well for Briggs because, in his day, Wharfedale was mainly concerned with large loudspeakers in large enclosures and resonances generally in the under-50Hz region. What he and his contemporaries didn't fully realise was that then-current design guidelines did not take into account factors that were vital to compact systems.

So, when compact reflex systems began to appear on the market, the bass characteristics of some were indeed sufficiently "obnoxious" to earn them a reputation as boom boxes!

In an attempt to curb objectionable resonance effects, designers resorted to a variety of measures, including internal partitions or curtains, padding, filling and acoustic filters across the vent. Sometimes they helped; sometimes they didn't.

It was left to an Australian engineer, Neville Thiele, and others, to perform a detailed mathematical analysis of the reflex system. It has since been translated into computer programs, making it possible to predict accurately the performance of various driver/enclosure/vent combinations and to give the "thumbs down" to basically unsuitable drivers or to impractical specifications.

The work has also rendered obsolete

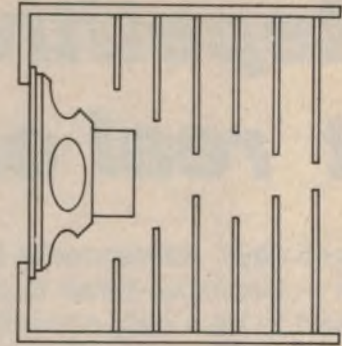



Fig.7: the "boffle" box used a succession of canite panels and spacers, with a circular hole in each panel, progressively smaller towards the back. The panels were designed to minimise standing waves in the box.

most articles on the subject from the '50s and '60s, along with ideas for "doctoring" systems that were probably ill-conceived in the first place!

But, equally, it has made it possible for companies with engineering know-how to design and/or manufacture a range of vented systems based on proven technology rather than "guesstimation".

The one lament is probably that modern reflex enclosure design can not be reduced to a few simple tables and graphs, for use by non-technical hobbyists. If you want to build a reflex system, base it on a proven design from a reliable source.

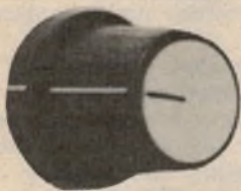How do reflex and fully sealed systems compare in terms of performance? In general, reflex systems should have the advantage in terms of efficiency, particularly over the bass region, but they are probably less practical for very small enclosures. Both have strong support, however, and our advice is simply to invest in the system which seems best to meet your needs, be it sealed or vented!



CLIFF K9 KNOBS

Quality Nylon, Matt Black Finish, 20x19mm ϕ w/coloured cap — red, black, white, green, yellow, grey, orange or blue.

	1 +	100 @
Push Fix	.50	.37
Push Fix w/Mark Line	.55	.43
Screw Fix	.70	.57
Screw Fix w/Mark Line	.80	.63



CLIFF PCB SPACERS

Nylon w/centre flat section that can be gripped while fixing. Fixing by size 6 or 8 self-tapper or $\frac{1}{16}$ in ϕ rivet into each end.

	1 +	100 +
Length	.09	.065
$\frac{1}{2}$ in	.10	.072
$\frac{3}{4}$ in	.11	.08
1in	.16	.126



CLIFF TO3 INSULATOR PAD

Simply mount on the under side of the heatsink to insulate fixing screws and device pins — speeds mounting.

1 + .16; 100 + .13



CLIFF S2 SERIES 6.5mm SOCKETS

Quality nylon (earth isolated) with break (B), single (S) or make (M) contacts. Contact material is nickel-silver alloy. Colours — white, black, red, grey.

	1 +	100 +
S2 SNB Mono	.60	.47
S2 BNB Mono	.60	.47
S2 MNM Mono	.60	.47
S2 BBB Stereo	.78	.65
S2 SSS Stereo	.63	.48
S2 MMM Stereo	.78	.65

DELSOUND

Australian Distributor for Cliff

PTY LTD, 1 Wickham Terrace (cnr Wharf St), Brisbane

Ph: (07) 229 6155. Telex: AA44442

Repetitive Strain Injury: is it real or imaginary?

These days, references in the media to RSI — Repetitive Strain Injury — seem almost to be a daily occurrence. For some people, RSI supposedly spells the end of a promising career; to others, the whole idea is a load of hogwash. Who's right and who's wrong or does the truth lie somewhere in between.



FORUM

Conducted by Neville Williams

When concern about possible computer operator ailments first surfaced some years ago, RSI had not been dignified by a special name. It was just one aspect of broadly based and rather emotional staff opposition to the introduction of computer keyboard technology into the workplace.

Some saw the technology as a threat to their existing personal expertise; others were more concerned with its likely impact on job opportunities generally. Still others were ready enough to accept advanced technology — provided they could negotiate an award to cover new skills, new hazards, and anything else they could dream up!

Some indulged in rather free-wheeling speculation about the possible ill effects of spending long hours in front of a display screen. Might not the TV-style scanned image cause eyestrain and/or produce mental tension of an obscure kind?

Again, something as highly visual and electronic as a display screen must surely generate rays of a sort and these might have an effect on anything from libido to genes!

More practically, there were claims that the kind of environment that had sufficed for typists and stenographers for decades was totally unsuitable for electronic keyboard operators. Room layout, lighting and posture all needed to be re-thought before the new equipment was introduced!

On the other side of the table, computer manufacturers, computer vendors and prospective purchasers were busily working out appropriate rebuttals.

In all this, fact was often so obscured by fiction and by industrial politics that I, along with a lot of others in the technical fraternity, tended to treat much of the debate with the proverbial "grain of salt".

Then, in a stroke of pure genius, someone invented a collective term —

complete with initials—for the potential physiological effects of working for long periods at a computer style keyboard; they christened it RSI, short for Repetitive Strain Injury.

In very short order, keyboard operators across the country were claiming that they had had to give up work because of RSI, or were currently suffering from its effects, or were being exposed to its ravages.

It was reminiscent of the one-time debate surrounding those vague, alleged visitations from outer space. Initially, people merely professed to having seen a disparate array of mysterious lights, flying saucers, and unearthly aircraft manned by little green men. But, almost overnight, all such phenomena were dignified and unified by a new, collective name: UFOs or Unidentified Flying Objects!

But, as with "UFOs", the term RSI also provided a convenient focus for the sceptics. There were plenty of them, but it would be difficult to imagine one more outspoken than Dr Denis P. Mackey, of Lindisfarne, Tasmania, author of a letter to the Editor, published in the Sydney Morning Herald on February 21, last. Under the title "RSI a joke", he says:

"A form of mass hysteria is moving through the Australian Public Service in the guise of repetitive strain injury (RSI).

"This 'disease' was invented two years ago as a bit of a joke so that work shy people could have an excuse for a 'sickie'. RSI represented no more than sore muscles or joints following repetitive use or overuse, as any tired housewife can confirm.

"RSI was invented as a diagnostic entity to support a hoax. All the aches and pains of everyday life have been translated into RSI and floated to a gullible community as a workers' compensation claim, to see which sector will take the bait."

From the standpoint of the medical

profession, Dr Mackey admits to a certain amusement, as public servants "line up by the droves to claim compensation for their overworked muscles." He concludes:

"It must be embarrassing for the Commonwealth Health Department, which controls all medical statistics, to observe that there are more cases of this disease in its own ranks than in any other Government department."

While few sceptics have expressed themselves quite as forcibly as Dr Mackey, there has certainly been widespread reservation about this ostensibly "new", potentially crippling disease. What about all the woman who worked for years in traditional typing pools? Why hadn't they become victims of RSI?

Perhaps many did, without some cumulative work-related disability ever having been diagnosed — or accepted — as such.

The same question could doubtless be pursued about women machinists in clothing factories or other process workers doing tedious repetitive handwork, often under makeshift conditions.

Accepted wisdom is to point out that typists, for example, normally break their keyboard routine at frequent intervals to handle paper and documents, thereby changing posture and bringing other muscles into play. This may not happen to anything like the same extent with, say, a word processor, where the activity involves fewer muscles for longer periods — possibly resulting in RSI.

A very old problem:

As it turned out, Dr Mackey's letter to the Sydney Morning Herald prompted three letters from other readers, all coincidentally having to do with old-time Morse Code operators.

Referring to RSI (and more particularly to Tenosynovitis or Carpal tunnel syndrome), J. W. Dargan of

Greenwich, NSW (Mar 4, '85) pointed out that the basic problem surfaced at least 50 years ago in connection with a primitive forerunner of modern "electric" communication devices: the Morse Code key. I quote:

"The same over-use of movements of small amplitude and low force by the tips of the fingers resulted in pain and rigidity of the wrist, which in turn destroyed the flexibility necessary for forming Morse signals at high speed. In those days it didn't have a medical name, and was known graphically as 'glass arm'!"

When that happened, according to the writer, the operator had no alternative but to learn to send with the other hand and, failing that, with the palm or even the wrist. Then unable, any longer, to send code, the operator simply lost his job, with little or no thought of sick pay or compensation.

By way of further comment (SMH March 8, '85) Mr Alf Baker confirmed the difficulties faced by old-time Morse Code operators, who were vital to Railway Department communications in country areas, before the installation of telephones. The glass arm problem was alleviated by development of the "pendograph", which allowed the operator to send code messages by using the thumb and forefinger in a lateral movement.

In the same issue, Dr M. Raphael of Mosman, NSW, also refers to the problems of Morse Code operators early in the century but says that over-use syndromes have been reported under various names in many industries over at least 300 years!

Morse Code operators, he said, ultimately had their shifts reduced. It seems only logical that, in addition to ergonomically designed work stations, present-day employees should receive proper consideration in regard to shifts, rest pauses, exercises, etc, in order to forestall trouble of a similar nature.

(In fact, this practice is now mandatory in some computer intensive government departments.)

Musicians as well!

More or less coincident with the foregoing debate in the Sydney Morning Herald, a news item in the Sydney Daily Telegraph quoted a report from Victoria, to do with professional musicians. The curiously worded introduction made it sound as if RSI was really an infectious disease, to be passed on and caught like the flu:

"The disease that was once thought only to inflict keyboard operators in the typing pool is also sweeping through symphony orchestras."

The item goes on to say that Mr Hunter Fry, the scientific convenor of

Distortion on orchestral strings

I would like to comment on your article "Why the distortion on orchestral strings?" in the February issue of "Electronics Australia". It has been a pet study (or hate) of mine over many years.

First let me say that the distortion is on the master tapes but becomes more apparent through each processing stage. (You can certainly hear it if you play back the master lacquer.)

But, significantly, it is often discernable also at the original performance. By way of illustration, let me recount something that happened to me in the days of mono reproduction.

At the time, I used to hold musical evenings in my home where a number of guests would come and simply sit in silence, listening to the reproduced music. One such guest was a prominent artist in Melbourne, who learned his craft painting model and stage scenery at La Scala in Milan, often to the sound of great orchestras rehearsing in the background.

At one of our evenings, he noticed "fizz" on the strings and described it as distortion, ostensibly in the recording. Later, we happened to attend an opera together and, during the performance, he became quite agitated. I learned later that he was trying to tell me how he had become aware of the very same "distortion" at this live performance. So it is a fact.

Now for my theory: You have noted, as I have, that it only occurs with some sound sources: vocal, strings — and some brass, you will find.

Further observation seems to

indicate that it only occurs where the artist has to select the pitch of the instrument while playing — no definite finger hole. Flutes in unison do not seem to exhibit the effect.

It appears to me that, in sounding the required notes, individual members of the group are all ever so slightly "off key" and that this causes a large conglomeration of harmonics. The louder the playing (or singing) the more noticeable the effect.

One might reasonably argue that, if enough harmonics are generated, the wave envelope would start to "square off":

So we have a problem to start with — it sounds distorted "live" — but this is progressively compounded by the difficulty which the unnaturally complicated waveform presents to the microphones and to the rest of the system, both recording and playback. Phase problems with multiple microphones certainly do not help!

Yes, I have heard the effect on some compact discs. And, yes, the skill of the musicians is important. For example: try as I may, I could not hear it during a performance by the Israel Orchestra during their last visit here.

To sum up:

- (1) "Distortion" is frequently present in the live performance.*
- (2) It happens only with choral groups and some instruments and depends to a degree on the skill of the performers.*
- (3) It becomes more noticeable with each recording stage, particularly if great care is not taken with levels and any application of treble boost.*

*Harry Mauger
(Mordialloc, Vic.)*

the Victorian Arts Medical Society, has surveyed six symphony orchestras during the past year, on the lookout for signs of RSI amongst the players.

Reportedly, he found evidence of the problem in 50% of the players. About 7% were ranked as having a "Grade Five" condition, suggesting that they would not be able to continue playing for much longer.

The report put the blame for RSI on bad posture and constant practice, and foreshadowed the time when orchestra members might "down tools" every half hour for an RSI break!

When I read that, I immediately rang Julian Russell, well known for his record reviews in this magazine. In his younger days, Julian was a professional concert and orchestral pianist, and later a

conductor. He has been in and around orchestras and musicians, worldwide, for most of his long life.

What were his reactions to the Victorian report?

In effect, they were substantially parallel to those of Dr Mackey, as quoted earlier, but expressed in somewhat less polite terms!

Any good teacher, he said, would place strong emphasis on posture and a professional musician who chose to ignore such advice would be likely to suffer the consequences in the way of plain, old-fashioned aches and pains.

Said Julian: unlike electronic keyboard operators, musicians do not, for the most part, just use their fingers. There is, or can be, considerable incidental

Electronics Australia

SPECIAL LIMITED OFFER

Save ^{Over} \$10.00!!

SUBSCRIBE NOW...



As Australia's top-selling electronics magazine, Electronics Australia brings you reviews of the latest HI-FI and VIDEO equipment, exciting and easy-to-build DO-IT-YOURSELF PROJECTS, news of the LATEST PRODUCTS and regular columns. Be sure to get your copy every month.

...AND RECEIVE 12 issues for the price of 8!!

That's just \$20.80 for 12 issues!

OR BETTER STILL...

If you subscribe now for 2 years you will take advantage of this special offer AND guard against price rises until 1987!!

That's just \$41.60 for 2 years!

TAKE ADVANTAGE OF US.

SUBSCRIBE AT 1/3 OFF THE NORMAL NEWS-STAND PRICE...

YOU'LL SAVE OVER \$10.00!!

ORDER NOW. IT'S EASY — HERE'S ALL YOU DO...

Tick

Please accept \$20.80 being payment for a one year subscription to Electronics Australia.

Name: _____

Address: _____

Postcode: _____

No stamp required if posted in Australia.

MAIL FREE TO: Freepost No. 4,
The Federal Publishing Company Pty. Ltd.,
PO Box 227,
WATERLOO. NSW. 2017.

Please allow up to 6 weeks for delivery of your first issue.
Offer valid until 30/9/85

OR

Please accept \$41.60 being payment for a 2 year subscription to Electronics Australia.

Tick payment you select:

Bankcard Mastercard American Express

Card No.

Expiry Date: _____

OR

Cheque/money order payable to Federal Publishing Company Pty. Ltd.

Signature: _____

(Unsigned orders cannot be accepted.)

Forum — continued

movement of other muscles.

As a professional pianist, he would customarily have spent many hours each day practicing, followed by an evening performance, and he never experienced any suggestion of so-called repetitive strain injury. Nor, could he remember other musicians complaining about it.

"It's the same old syndrome. Invent a new ailment and there's an immediate rush of people claiming to have it!"

In retrospect, I guess I should have asked Julian whether he could remember musicians being troubled by rheumatism or arthritis — or, at least, by complaints so described. RSI by any other name hurts just the same!

To this point I have deliberately kept my options open — but I haven't quite finished. The fact is that I had a personal reason for raising the matter in the first place.

My own experience

As a professional technical writer I, too, worked for decades in front of a typewriter, without any notable complications, apart from quite predictable fatigue. In retirement, however, I have effectively pensioned off the aging Adler and, nowadays, write virtually everything on a word processor.

As often happens in a domestic situation, the new equipment was shuffled around a good deal, until it finally ended up on a separate small table — appropriately tidy and set up ready for immediate use.

Some time later, I became aware of mild but niggling arm and shoulder pain which, on the wrong side of retirement, can give some cause for concern. But then I noticed that the pains became most apparent after some hours at the word processor. Why so, after years in front of a typewriter keyboard?

I was using the processor because it encouraged longer periods of concentration, with fewer distractions, resulting in much higher productivity. But, in so doing, it largely obviated the need for physical movement, other than to do with the keyboard.

Then I realised that, during those longer periods of concentration, my elbows were thrust quite heavily into the padded arms of the office style chair, with a significant amount of body weight literally hanging from my shoulders. No wonder the arm and shoulder muscles were protesting. It seemed very much a matter of posture.

A call to a doctor friend proved most enlightening. He is associated, by the way, with a large company which

SORRY, Mr KODAK!

The inadvertent omission of a few words from a paragraph in "Forum" (March '85, page 30) completely changed its sense, to the disadvantage of Kodachrome film. The actual printout from the Author's word processor reads as follows:

But, closer to home, when comparing notes with a photographer friend, I had a look at a collection of 35mm slides which I had either taken personally or bought during the EA-organised "Technitour" to Osaka for EXPO '70. My own Kodachrome slides were still in good shape but many of the bought slides had taken on hues ranging from a prevailing blue, through, reddish-purple to a faded all-over orange — in the latter case, a complete write-off.

operates a great many keyboards.

"Do you recognise the symptoms?"

"I certainly do. They're classical. Where do you have the processor?"

"On an ordinary small table.

"It'll be too high. The keyboard should be down near your knees, not up near your chest! Cut a few inches off the legs!"

"What about the arms on the chair?"

"Put them right down, if you can, or take them right off!"

"Anything else?"

"Yes. Set the screen at a comfortable viewing height and make sure that it's not reflecting glare from windows or lights.

"Thanks for your observations. I think I might say something about this in the magazine.

"By all means do. Impress on your computer-nut readers the vital importance of posture and lighting when spending long periods at a keyboard. If they don't, they could run into aches and pains — no matter by what name you call them!"

Frankly, that sounds to me like good

advice, particularly for private users, isolated from imposed work practice discipline.

By its very nature, a computer style keyboard encourages prolonged concentration, particularly in the role of a word processor. There is little need for incidental body movement: No need to reach for new sheets of paper or to arrange completed sheets as the job progresses. No need to search for a rubber or correction fluid, or to get up and walk away in disgust when something has to be re-typed or re-arranged.

You just tap a few extra keys and carry right on!

The combination of that kind of concentration with poor posture and/or poor lighting can cause exactly the kind of aches, pains and eyestrain that one would expect. Whether tenosynovitis or carpal tunnel syndrome lurks just around the corner is not quite so clear but at least we should take note of problems that are immediately obvious.

Distortion on strings

In February last, I raised the matter of the "edginess" or "zizz" that often characterises the sound of massed strings or massed voices. It is commonly blamed on the recording and replay equipment but I suggested that, if you listen carefully, it can often be discerned at a live performance.

Could it be that the sheer complexity of harmonics from multiple sound sources, all slightly and randomly off tune, is interpreted by the ear as noise and therefore as "distortion"?

Some may have regarded it as a rather "way out" suggestion and I was naturally most interested to receive a letter of support from a long-time friend, Harry Mauger (pronounced 'major'). Before his retirement, Harry was chief recording engineer for Astor Records in Melbourne and he speaks from a wealth of practical experience.

I suggest you read his letter on the preceding page and compare his observations with the original article in February.

"So next time you go to a concert, don't just sit there enjoying the music. Keep an ear out for the "distortion"! ☺

BASIC ELECTRONICS

For the beginner, or for the hobbyist as a reference book and almost certainly the most widely used manual on basic electronics in Australia.

It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. Begins with the electron, introduces and explains components and circuit concepts, details the construction of simple receivers. Separate chapters on test instruments, servicing amateur radio, audio techniques, stereo sound reproduction.

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017. PRICE \$4.50. Or by mail order: send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017. PRICE \$5.40.

Are your ears as the

"The CD-44 is most probably the 'sharpest' and most marketable CD player introduced by the Marantz company. Its major attributes extend beyond the realm of price as the designers have aimed at providing a sophisticated performance which does not appear to be limited by price.

The frequency accuracy of the player proved to be outstanding. The consequent frequency deviation was only a paltry 0.1Hz for the 20kHz reference signal. The frequency linearity was 20Hz to 20kHz \pm 2dB. That sort of accuracy is not likely to be improved upon by any other player.

This sort of performance would be raved about by other manufacturers and their P.R. personnel as state of the art performance."

Louis Challis. "Electronics Today International". May 1985.



STAN CURTIS' RIGHT EAR.

STAN CURTIS' LEFT EAR.

"By contrast, the Marantz player produced a sound which was smoother,

not so forward or bright, and infinitely more musically convincing.

Many recordings played on the Marantz exhibited that very important characteristic of a good reproducing system – the sound didn't obviously emanate from two loudspeakers.

Obviously at this level we are not talking about a standard of reproduction that was poor, but of a difference in absolute performance which made the Marantz preferable."

Stan Curtis. "Hi-Fi for Pleasure."



DAVID PRAKE'S RIGHT EAR.

DAVID PRAKE'S LEFT EAR.

"I have been surprised by the quite audible difference between CD players and have already stated a preference for the sound of the Marantz machine in terms of its handling of "ambience" and its sheer unfatiguing listenability.

Other players I've heard in direct comparisons have shown a bright veiling effect with more up-front presentation and a fatiguing quality.

ears as good experts?

How much of this is down to the quality of the analogue audio circuitry in the players in question, and how much to the 14 versus 16 bit systems, I'd hate to guess."

David Praker. "Hi-Fi Answers," U.K. "Ironically, after all the opulent, lavish and wholly enjoyable CD launches of the past four years, it was in these very low key surroundings that I can truly say I first heard the potential of this system.

To my ears and those of our Technical Editor, Dave Berriman, it was the most convincing and encouraging demonstration to date.

But why should little Marantz get it right where the others have failed? It certainly encouraged many who had come to despair of CD ever attaining the heights claimed for it."

David Praker. "Practical Hi-Fi," U.K.



MARTIN COLLOMS' RIGHT EAR

MARTIN COLLOMS' LEFT EAR

"Marantz U.K. managed to lend me a CD player for just a few hours.


To my ears and in my system the CD player provided a standard of home replay as good as I have ever used.

It was found that during the sessions the sound level was very high, in fact to the limit of the system, and yet the sound itself did not appear loud.

This is a very good sign, a feature familiar to me from my collection of copy master tapes. Moreover, in certain respects, the sample programme bettered my master tapes.

Judging from the advance sample, the Marantz CD has a very bright future."

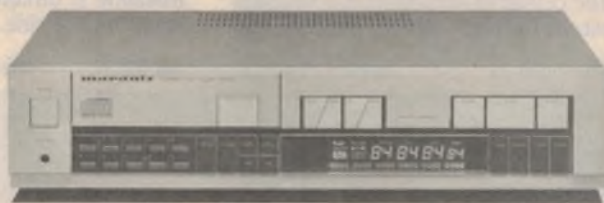Martin Colloms. "Hi-Fi for Pleasure," U.K.



For further information contact: Marantz (Australia) Pty. Limited. Incorporated in NSW. 19 Chard Road, Brookvale, NSW, 2100.

Telephone (02) 939 1900 or your nearest Marantz dealer.

marantz®

Mitsubishi DP-205 compact disc player

One of the less familiar names in the hifi market is Mitsubishi. They have been building fine audio equipment for many years and they have a compact disc player, the DP-205. This is a full-featured machine which has infrared remote control.

While Mitsubishi has been producing hifi equipment for quite a few years now, they have not had a high profile on the Australian market. Maybe this will change with the release of their compact disc player.

The Mitsubishi DP-205 is a fairly large machine for a CD player although it has a low profile. It has a conventional front-drawer disc loading system and is finished in the most popular hifi colour: black. Dimensions of the unit are 424mm wide, 300mm deep and 79mm high. Weight of the unit is 5.4kg.

The front panel presentation of the DP-205 consists mostly of tinted perspex which has been screen-printed in white for the control legends. Happily, all the control labelling is easily readable, even in relatively dim lighting.

In the centre of the panel is a vacuum fluorescent display which indicates all

the disc track, index and time information. The visibility of this display is good, both under dim and bright room lighting.

The DP-205 has an unusual array of pushbutton controls on the front panel which do not immediately strike a familiar chord with the user. But it also has an infrared (IR) control and it seems fairly clear that the makers intend the machine to be controlled with this rather than via the front panel buttons.

The IR control has the usual Play, Pause, Stop, Fast Forward and Reverse buttons, plus others for repeat, Open/Close, Display, Program, and forward and reverse skipping by track or index selection. The IR control has an effective range of between three and four metres, depending on whether the machine is directly in front of the user, or off to the side.

On the far righthand side of the front panel of the machine is the headphone socket and accompanying volume control. This is a natty little knob which is normally flush with the front panel and which, when slightly depressed, springs out by a centimetre or so, to allow the user to adjust it.


Removing the cover of the unit reveals a spacious chassis with a surprisingly large disc mechanism. The laser pickup is also a fairly large assembly which linearly traverses the underside of the disc.

On the righthand side of the chassis are two large printed circuit boards which are stacked face to face. Access to the lower board is gained simply by unlatching two nylon clips on the upper board and rotating it over to one side. Our photo shows the copper side of the top board so that the only components visible are two resistors tacked across some IC pins and a 60-pin surface-mounting integrated circuit.

Japanese products are appearing with more and more surface-mounting components these days. Beside the one just mentioned there is another mounted on the other printed board which has no less than 70 pins at about 0.7mm spacing.

In other respects the internal details of

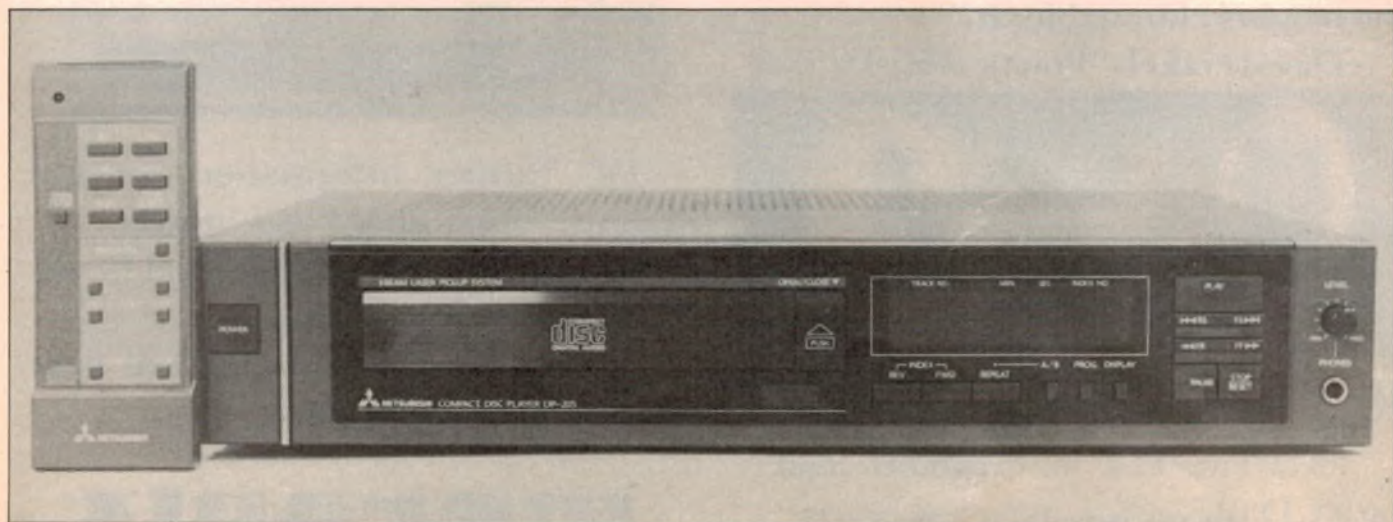The Mitsubishi DP-205 is supplied complete with an infrared remote control. The unit is large for a CD player.



the DP-205 are more or less standard and require little further comment.

The rear panel of the unit is bare except for a pair of gold-plated RCA sockets. The unit is double-insulated and is fitted with a sheathed two-core mains flex and standard Australian 2-pin mains plug.

As with most other compact disc machines, the Mitsubishi DP-205 has transport screws which must be removed before it can be put into use. Just why these are necessary is beyond this reviewer, as the act of screwing the transport suspension down removes any possibility of lessening the shock damage to the laser pickup.

When power is applied, the only sign that the unit is alive is the tiny "colon" indication on the fluorescent display. If it wasn't for this, the machine would look completely inert.


From there on, the machine is fairly standard in its operation although it is more convenient to use the remote control than the front panel buttons.

Loading a disc causes "Disc" to be displayed, plus the number of tracks and the total playing time. Pushing the Play button then causes the machine to start and to display the elapsed time. It is possible to program the unit to play the tracks in random order and to repeat musical phrases, complete tracks or the whole disc. Learning how to do all this is not easy, however, as the controls are not self-explanatory and the 8-page manual is not at all clear.

As with most Japanese machines, the DP-205 uses conventional 16-bit digital-to-analog conversion and sampling at 44.1kHz.

Performance

As usual, we put the Mitsubishi through the full battery of tests to assess its performance. Frequency response was very flat, being at 0dB from 20Hz all the way up to 15kHz. At 18kHz, it was 0.2dB down and 0.4dB down at 20kHz. The level discrepancy between channels, more usually expressed as "channel balance", was exactly 0.5dB over the whole range, with the right channel being the lower in level.

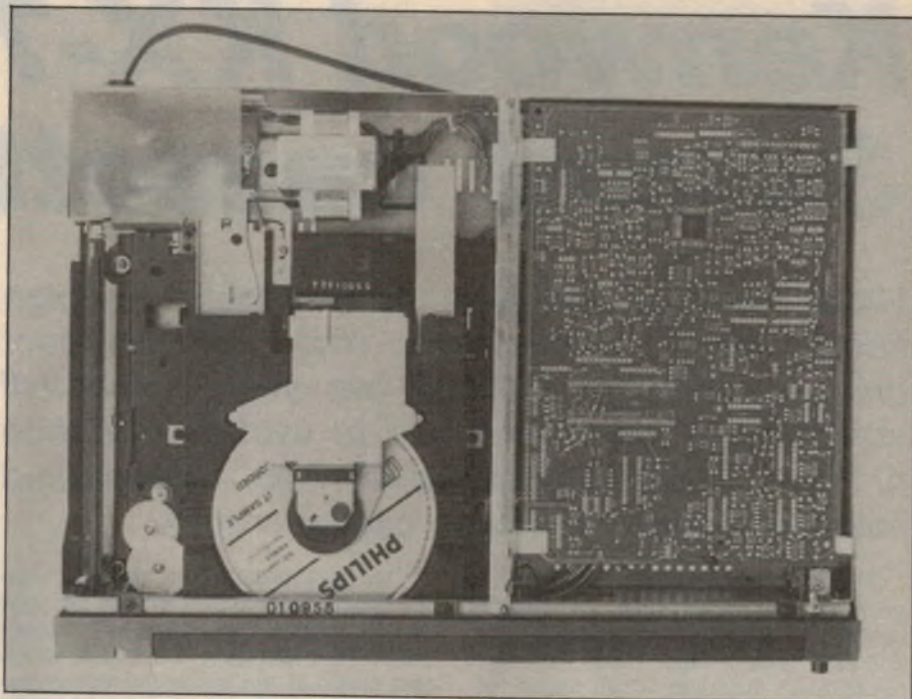

The DP-205 features two PCBs stacked face to face and a surprisingly large disc mechanism. Two surface mounting components are used in the design.

Separation between channels was good, at close to 90dB over the whole range of frequencies. When you compare the figures for separation between channels for CD players and other hifi equipment, it is astounding just how good they are.

Figures for harmonic distortion were also very good, at typically between .004 and .005%, rising to just over .01% at 20kHz. Intermodulation at 0dB for a 400Hz + 7kHz signal was .007%.

Results for the linearity tests were also good, showing an error of 1dB (only 0.5dB in the right channel) at the -80dB level and 4dB error at the -90dB level.

Signal to noise ratio figures were -97.5dB with emphasis and -94dB without emphasis. Both results are good.

Where the machine was not so good was in its tracking and error correction. On the Philips No 4A defect disc, the DP-205 would not track the 800µm dot (which simulates quite a large defect) and at other times on the same disc there was a regular "ticking" noise, indicating that the error correction was in the muting

mode. And on our badly scratched sample disc, which is something of a torture test for CD players, there were some tracks the machine could not play at all.

As far as susceptibility to shock and vibration was concerned, the DP-205 was also not quite up to the standard we have come to expect from CD players in general. In normal circumstances though this should not be a big problem since it is not customary to jolt the player while it is working.

In all other respects, the Mitsubishi turns in a fine performance and should give many years of listener satisfaction. Naturally, it sounds superb.

Recommended retail price of the Mitsubishi DP-205 is \$859.00, including the infrared remote control. For further information on the Mitsubishi range of products contact the Australian distributors, AWA-Thorn Consumer Products Pty Ltd, 348 Victoria Road, Rydalmere, NSW 2116 or interstate branches. (L.D.S.)

Specifications

Sampling frequency	44.1kHz
Digital-to-analog conv	16-bit linear
Frequency response	5 — 20,000Hz ±0.5dB
Dynamic range	Better than 94dB
Harmonic distortion	0.003% (at 1kHz, 0dB)

Channel separation	Better than 94dB (at 1kHz)
Wow and flutter	Below measurable limits
Line output level	2V (0dB, into 50kΩ load)
Headphone output level	22mW (0dB, into 8Ω load)
Power consumption	19W
Weight	5.4kg
Dimensions	424 x 79 x 300mm (W x H x D)

Kenwood KX-780

3-head cassette deck

While most of the new developments in high fidelity seem to have taken place with compact disc players over the last two years, other hifi components have continued to evolve. Evidence of this is the new Kenwood KX-780, a three-head microprocessor controlled cassette deck.

The first cassette decks to employ a microprocessor used them to provide optimum bias and equalisation for different types of tape. These were top-of-the-range machines which aimed for the very best of performance, more or less regardless of cost.

By contrast, this new medium range machine from Kenwood employs a microprocessor to control the mechanical functions of the deck, plus some of the fancy user features. In total, the microprocessor provides the electronic tape counter, transport control, line muting (depending on the mode of operation) and such features as re-record/standby, fast forward and reverse skip plus memory rewind and replay.

If all these features were to be provided using conventional circuitry and mechanics, the resulting machine would be a great deal more complex and more costly.

The microprocessor is not used to optimise bias. Kenwood have provided a manual bias control which, provided the user settles on just a few tape types, can give very good results.

The Kenwood KX-780 is a three-head machine with Dolby B and C noise reduction systems.

One good point about having a user-adjustable bias control is that the bias can be optimised according to the user's particular preference. A criticism which was aimed at the earlier microprocessor machines mentioned above is that the machines seemed to be programmed to optimise bias at the expense of distortion. In other words, they have a good frequency response but quite high harmonic distortion, especially at the higher signal levels. The user had no option but to live with this compromise for there was no way of overriding the machine's internal program.

From our point of view then, the concept of a user-adjustable bias control is better than having the microprocessor do it.

The Kenwood KX-780 is quite an imposing machine to look at, both as far as its overall dimensions are concerned and its general style. It does not have a large array of user controls but those it has have been arranged and labelled so as to give it a "technical look". This is not meant as a criticism as such, as we quite liked the looks of the unit. At any rate it

makes a change from the antiseptic styling of some European hifi equipment which seems to go too far in the opposite direction.

Overall dimensions of the KX-780 are 440mm wide, 111mm high and 322mm deep. Weight is 4.8kg.

Features

The KX-780's cassette compartment has a large, clear plastic door which is very gently released by the Eject button. This is accomplished by a miniature version of a pneumatic door closer.

The unit has three heads and is compatible with all three tape types including metal tape.

In the centre of the front panel are the transport control buttons. They are not buttons actually, more like a "bent membrane". They have very little travel and operate as if they each have a microswitch behind them. Above these are three slide switches which select timer operation, tape type and noise reduction: Dolby B or C. To the right of these is the counter reset, and below it, the bias control knob. To the right again is the large vertical signal level meter panel which employs red LEDs.

At the far righthand side are the recording level controls, monitor switch, microphone sockets, headphone socket and combined headphone/line output level control.

The rear panel is bare except for the RCA input and output sockets and the two pin socket for the AC mains power input. The machine appears to be



In a class of it's own...

KENWOOD KX-780B 3 head monitor cassette deck




- KENWOOD's KX-780 High Quality Cassette Tape Deck utilises a dual combination 3-head design for recording and playback which enables both the source and recorded sound to be monitored independently.
- Tape bias can be fine tuned by a variable control even during recording should this be required.
- Dolby B & C noise reduction effects can be monitored whilst recording by the operator, via discrete circuitry.
- Microprocessor control facilities include a 100 count automatic REW or FF, play, rewind-play, re-record standby, counter zero stop and auto-recording mute zero signal 4 record spacer.
- The KENWOOD KX-780 is an outstanding deck by any standards, even compared with "luxury" 3-head models or half speed recording decks.

 **KENWOOD**

GASTK2558



MITSUBISHI AUDIO SYSTEMS

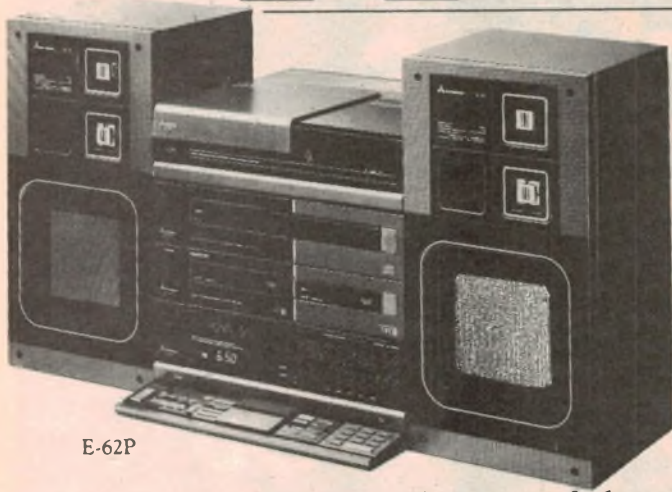

E-62P



L-70

The brilliance of three diamond performance!

Mitsubishi "Commander" infra-red control AM/FM Stereo Audio System Model E-62P. Built-in Compact Disc Twin cassette tape deck 35 watts per channel FTC rms Linear tracking, fully automatic turntable Infra-red, detachable "Commander" control Programmable recording and playback.

Mitsubishi 7 Cassette programmed AM/FM Stereo Autochanger Audio System Model L-70 will play up to seven pre-loaded cassettes, either side, in any order. Provides random selection, or programmable selection from both sides of seven tapes Fully automatic linear-tracking turntable Stable AM/FM stereo tuner 2-way bass-reflex speaker system.

Distributed and guaranteed throughout Australia by **AWA-THORN CONSUMER PRODUCTS PTY. LTD.** (Incorporated in N.S.W.)

OUTSTANDING PERFORMANCE ... at safer temperatures!



Choose an approved soldering iron that best suits your needs.

- Adcola 'Standard'**: for hobbyists and general soldering.
- Royel 'Duotemp'**: push-button temperature control.
- Royel 'Thermatic'**: electronic feedback temperature control.
 - Light weight, cool handles.
 - No transformer required, plug in to 240V.
 - Correct heat for Printed Wiring Boards.
 - Many tip profiles available for all models.

ADCOLA ROYEL


provides protection against thermal damage to modern circuitry.

**ASK YOUR NEAREST
ELECTRONICS PARTS
SUPPLIER!**

Chosen by
**AUSTRALIAN MILITARY SERVICES
& LEADING MANUFACTURERS
WORLDWIDE!**

MHL 3035R

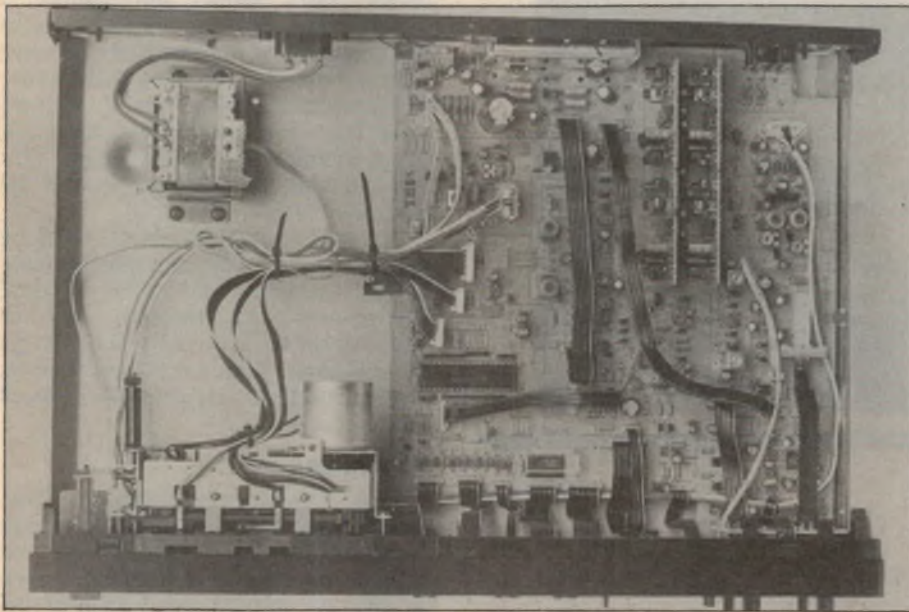VIC: (03) 543 5122 ■ N.S.W.: (02) 709 5293 ■ QLD: (07) 277 4311 ■ S.A.: (08) 212 5999 ■ W.A.: (09) 381 5500 ■ TAS: (002) 34 2233



The large integrated circuit on the PC board is the microprocessor which provides many of the user functions.

double-insulated but lays no claim to being so.

Chassis features

The transport mechanism of the KX-780 is powered by a single motor, with two solenoids employed for changing the transport mode. The record and play heads are separate but occupy the volume of the normal record/play head in a conventional two-head machine. A single capstan is employed and it has a reasonably large flywheel.

More than half the chassis area is occupied by the main printed circuit board which carries the microprocessor control circuitry and the audio circuitry. The microprocessor is a 40-pin device with internal ROM (read only memory) and inbuilt oscillator.

Four Dolby processor ICs are used, for B and C noise reduction. There is also a largish vertical board, for the circuitry associated with front panel controls, the tape counter and the LED signal level meters.

Another point of interest is the relatively large number of ribbon cables employed in the unit. These are mostly soldered into place rather than using sockets. It appears the entire electronics component of the deck is manufactured as one large PC board and then sections are snapped off (with cables in place) to provide all the ancillary boards.

At the rear of the chassis, all on its own, is the transformer which is fitted with a copper strap (for hum leakage). This transformer is energised

while ever the unit is connected to the mains, and the power switch operates in the secondary winding. This is a common enough practice with synthesised FM/AM stereo tuners but is unusual in cassette decks. The reason for doing it in this machine is to enable a somewhat simpler power switch than is usual. In double-insulated equipment it is usual to have a well insulated push-on/push-off switch mounted toward the rear of the chassis, near the power transformer, and actuated by a long plastic rod. In the KX-780, this has been dispensed with in favour of a switch with lower ratings, mounted off the front panel.

Performance

Testing any cassette deck is not easy these days as there are three types of tape to contend with, ferric, chrome and metal, and on this deck there is the added complication of having two noise reduction systems to contend with. Add in bias adjustments and you have an almost infinite number of variables. To make some sense of this we decided to do the tests of the selected tape types with three different bias levels: minimum, normal (halfway setting) and maximum.

As might have been expected, the differences wrought by the changes in bias level were mainly apparent at frequencies above 15kHz with the major difference being the corner frequency, beyond which the response took a sudden plunge. Distortion figures were

continued on page 126

THE ULTIMATE IN AUDIO
& VIDEO CARE FROM

LENCO SWITZERLAND

HERE IS ONLY ONE
SELECTION OF LENCO'S
WORLD FAMOUS PROGRAM:

LENCOCLEAN L

The revolutionary wet-play record care system: The number one record cleaning product in Europe!



LENCOCLEAN L

Other record care products clean records, but they do nothing to reduce the tremendous friction and heat of several hundred degrees produced at the contact points between the stylus and the record groove.

LENCOCLEAN works by simultaneous mechanical cleaning of the record in front of the needle and moistening of the record with a rapidly evaporating fluid which leaves no residue.

LENCOCLEAN

- GREATLY REDUCES NOISE AND DISTORTION.
- GREATLY INCREASES LIFESPAN OF BOTH RECORD AND STYLUS BY AT LEAST 50%.
- CLEANS GROOVE JUST AHEAD OF STYLUS AND NEUTRALISES GRANULAR DUST.
- DISCHARGES ELECTRO STATIC CHARGING WITHOUT LEAVING ANY RESIDUE.
- ELIMINATES THE CONSTANT CLEANING OF STYLUS.
- REDUCES SKATING FORCE.

For more details of this or any great Lenco product ring or write to:

SOUNDRING PTY LTD

2/514 Miller Street,
Camberay, NSW 2062

Tel: (02) 92 1990, (02) 929 6672.
Telex: AA26539

DEALERS ENQUIRIES WELCOME!!



Presentation

The Rally Computer is built into two plastic cases which are connected together by a multiway cable. One case contains most of the electronic circuitry and is mounted out-of-sight, either under the dashboard or under one of the front seats. The second case is the control unit and is mounted on the dashboard. This unit contains the LED display and the control switches.

To measure the distance travelled by the vehicle, a magnet and coil assembly is used to monitor driveshaft rotation. Alternatively, the magnets may be mounted on an undriven wheel. In this way, distance measurement inaccuracies due to wheelspin and slides are reduced to a minimum.

Functions

Three Road functions and one Time function are available on the Rally Computer and are selected by the function switches located directly below the display. A LED above each of the ROAD 1, ROAD 2, ROAD 3 and TIME switches indicates which function is currently displayed.

All of the Road counters have 10-metre resolution on the final digit and will display up to 1999.99km before automatically returning to zero. As already mentioned, they operate independently of each other and can be set to count either up or down. Alternatively, a counter may be placed on Hold, in which case no further distance counting occurs.

This independent operation makes the unit extremely versatile. For example, one counter may be on hold while another counts up and the third counts down.

Similarly, the Time function can be set to count either up or down, or set to Hold. An alarm sounds when the count reaches zero for any of the Road or Time functions. All these features may seem complicated but you soon become familiar with them after a short period.

Controls

To the right of the display and function switches are the various control switches; DIMming, END, ENTER, CLearR/1, HOLD, SET, -, + and CALibration.

Note that all the switches, with the exception of DIM, END and ENTER, are also marked with a number from 0 to 9. These are used in conjunction with the ENTER switch to program the function counters and CALibration memory.

When the ENTER switch is pressed, the accompanying LED lights to indicate that the other switches are now numeral switches. The display is then cleared

Rally Computer

PART 1

Rallying is a popular motor sport in Australia. This easy-to-build Rally Computer features three separate distance counters, 10-metre resolution and a quartz clock. The clock and counters can be independently set to count up or down and an alarm sounds when any count reaches zero.

by JOHN CLARKE

Since publication of the EA Car Computer in July, August and September 1982, we have had many requests for a rally computer. As rally enthusiasts have discovered, commercial rally computers are quite expensive. This unit provides similar features to a well-known commercial unit, but can be built for a fraction of the cost.

Rally events are a gruelling test of driving and navigation abilities. Success relies heavily on teamwork and on having the right equipment. A suitably prepared vehicle is a good starting point but accurate navigation is also a vital ingredient.

By using this Rally Computer, the navigator can very effectively locate various points along the rally course. Three independent up/down counters provide the vital distance information

with 10-metre resolution, while a 12-hour clock enables checkpoint times to be measured to the nearest second.

Alternatively, the clock can be used as a stopwatch or as a down counter which can start from any time up to 19 hours 59 minutes and 59 seconds.

All information is displayed on a bright 5-digit LED readout. Naturally, the computer will retain all data when switched off after the rally event so that important information can be recalled. This is also an important feature for overnight stops or if the car is temporarily disabled during the event.

All the above features are packed into a unit that's very easy to use. After all, what good is a rally computer that's too complicated to use when you're sideways in the dirt at 120km/h?

ready for entering numbers into the function or CALibration memories. As each numeral switch is pressed, the number is entered on the display. After completion of the entry, the END key is pressed to store the entered number into the selected function. At the same time, all switches are returned to their normal functions.

The SET switch controls the HOLD, CLR/1, - and + switches. When pressed, the SET LED lights to indicate this mode of control. For example, let's say that we want to clear the contents of the ROAD 2 counter. The switch sequence is ROAD 2, SET, CLR/1. At the completion of the sequence, the display will show 0.00 and the SET LED will extinguish.

The CLR/1 switch can also be used to zero the ROAD 1 counter when the SET LED is off. This allows the rally navigator to quickly clear this counter without using the SET control switch. To further aid the navigator, CLR/1 also has a remote hand-held switch facility.

To alter the + (up), - (down) or HOLD status of a function, just press the SET switch and one of these switches. Once again the SET LED will extinguish when the alteration is completed. The left hand digit of the display will indicate a "+" for an up counting function, a "-" for a down counting function and a combined "+" and "-" for a HOLD.

The process of altering the function status by using the extra SET switch ensures that the functions are not altered inadvertently during the gruelling mental strain of rally navigation. You must use the SET switch before the status is altered. To escape from SET without altering the function status just press END.


The CALibration switch provides access to the distance calibration number. This number represents the distance travelled by the vehicle between each pulse from the distance sensor. We'll tell you more about this feature in the second article next month.

The final switch on the front panel is the DIMming switch. Its function is self-evident — it simply allows the user to switch between two levels of display brightness. The bright setting is suitable for daylight use and the dim setting is designed for night-time driving.

The circuit

A microprocessor takes care of most of the complex functions of the Rally Computer. This is basically an integrated circuit which can be programmed to manipulate data and control or respond to external hardware in the manner requested by the program.

In this case, the microprocessor

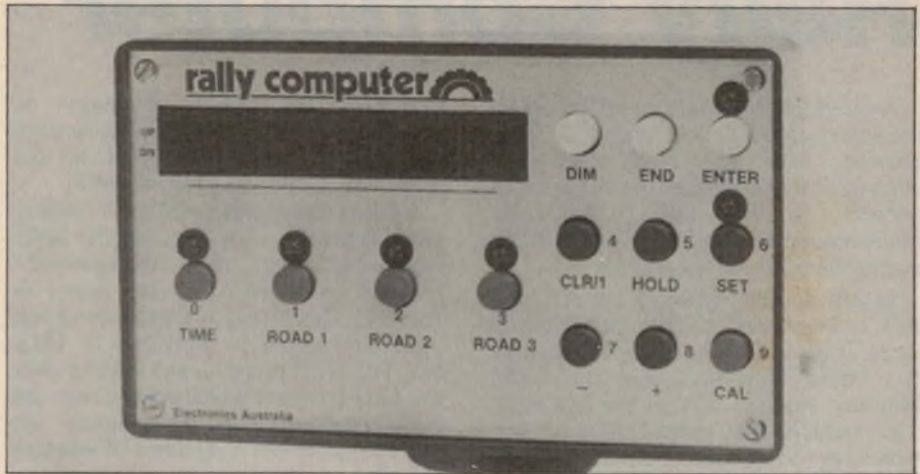

The control unit is designed for dashboard mounting and is easy to operate.

controls the display and responds to the switch and distance sensor inputs. It also carries out the addition and subtraction functions and performs the various other duties as required.

Refer now to the circuit. IC1 is the microprocessor which is a Motorola 6802 8-bit CPU. It can perform all the instructions of the well-known 6800 microprocessor and contains 128 bytes of RAM which can be used for data storage when running a program. The first 32 bytes is separately powered, to enable important information to be retained when power to the remainder of the CPU is switched off.

A 3.58MHz crystal supplies a stable clock reference for the CPU and this is divided internally by four to give an 895kHz clock (or E) pulse on pin 37. Note that there is a trimmer capacitor on pin 39 of the crystal oscillator input to IC1. This allows the crystal oscillator frequency to be precisely adjusted for accurate time keeping on the Rally Computer clock.

IC2 is a Peripheral Interface Adaptor (PIA) and is used to control all the external hardware under the direction of the CPU. It comprises two 8-bit ports (PA0 to PA7 and PB0 to PB7) which can be programmed as inputs or outputs. Two extra control lines on each of these ports, CA1 and CA2 and CB1 and CB2 respectively, are also available. The CA1 and CB1 lines are inputs, while CA2 and CB2 can be programmed as either inputs or outputs.

PA0 to PA7 are used to drive the display segments via 7404 TTL inverters (IC9 and IC10) and 33Ω current limiting resistors. The inverters buffer the outputs of the PIA "A" port and provide the high current necessary for driving the display LEDs.

PB2 to PB7 are used to drive the display digit transistors (Q3 — Q8), while

PB0 and PB1 scan the front panel switches. PB0 and PB1 are thus programmed as inputs while PB2 to PB7 are outputs. Inverters IC8a-f buffer the PB2-7 lines while the 390Ω resistors limit the transistor base currents.

The display consists of six common anode display digits. The most significant digit is actually an overflow digit and displays +, -, 1 and decimal point. The remainder of the displays are standard 7-segment types with decimal point. The separate LEDs which indicate the four functions, the SET and ENTER modes connect to unused segments on the display.

Note that the cathodes of each display are connected to the corresponding cathodes of the adjacent displays, while the display anodes connect to their respective digit driver transistors. This form of connection allows the display to be multiplex driven.

With multiplexing, only one digit is on at any given time. In this design, the PIA "A" lines drive the display cathodes while the PIA "B" lines switch the displays in sequence. Because the digits are switched at a 1kHz rate, the eye perceives a continuous flicker-free display.

The switches are scanned in matrix form via the multiplexed PIA "B" lines. If a switch is closed, a high will be read by either the PB0 or PB1 input. The program then decodes which switch has been pressed and acts accordingly by displaying the necessary function, modifying the function status or entering a number.

IC3 is a 2K byte Electrically Programmable Read Only Memory (EPROM) which holds the Rally Computer program. This is a non-volatile memory, which means that the memory will remain stored even with the power off.

Rally Computer

A common 8-bit data bus (D0 — D7) interconnects IC1, IC2 and IC3. This provides two way read and write communication between the devices. An address bus from A0 to A10 also interconnects IC1 and IC3 and is used to access the EPROM locations.

Simple address decoding for IC2 and IC3 is performed by the two NAND gates, IC6c and IC6d. IC3 is accessed by IC1 when both A14 and the Valid Memory Address (VMA) line are high. This switches the output of IC6d low which, in turn, forces G-bar of IC3 low. The VMA indicates a valid address on the bus. The EPROM locations are from hexadecimal memory address 6000 to 67FF.

All the registers of the PIA (IC2) are accessible by high/low combinations of RS0 and RS1 (pins 35 and 36), which are connected to A0 and A1 respectively. The Chip-select lines — CS0, CS1 and CS2-bar — are connected to G-bar of IC3, Vcc and the output of IC6c respectively. When A15 and the VMA go high, CS2-bar goes low and, provided IC3 is not selected with a high A14, IC2 is selected. IC2 is accessed using addresses from hexadecimal 8004 to 8007.

Interrupts

Three levels of programming are used in the Rally Computer. These are the RESET, Non Maskable Interrupt (NMI) and the Interrupt Request (IRQ). The

initiation of these programs is determined by the voltage levels, or edge triggering in the case of NMI, on the respective pins of IC1 (40, 4 and 6).

Each of these programs has a priority level. When first switched on, the Rally Computer runs the "background" program initiated by the power-on RESET. This program continues to run until interrupted by NMI-bar or IRQ-bar. The NMI program has priority over the IRQ program which means that the NMI program runs immediately the NMI-bar goes low, regardless of whether the IRQ program was running or not.

The NMI program is used to control the display multiplexing and to update the data on the display. The multiplexing rate is set by Schmitt trigger oscillator IC5c, which is gated via NAND gate IC6b. As a result, the NMI-bar interrupt is disabled until CB2 of IC2 goes high. This occurs during the RESET program and after the PIA has been initialised.

The IRQ performs two functions and is interrupted when either a time pulse or distance pulse occurs. So that the processor can determine which of the two inputs actually caused the interrupt (after all the processor only has one IRQ-bar pin), it is necessary to send these signals via the PIA. The PIA sets flag bits within the registers which correspond to the input that caused the interrupt. The hardware outputs of IC2 — IRQA-bar and IRQB-bar — then interrupt the IRQ-bar of IC1.

Whenever negative edges occur at CA1 or CB1, IRQ-bar of IC1 goes low to serve the interrupt. The IRQ-bar line will then only go high after all the interrupt flags within the PIA registers are cleared.

The time interrupt is derived from division of the 895kHz E clock signal from IC1. IC6a inverts the E clock signal and applies it to the input of IC7 which is designed to divide a standard 3.58MHz crystal oscillator signal down to 60Hz. However, since the E clock is actually one quarter the crystal frequency, the output from IC7 is only 15Hz. This signal is connected to CA1 of the PIA.


Whenever there is a time IRQ, the clock function program of the Rally Computer is accessed. This means that the clock alters by one second every fifteenth pulse.

The distance interrupt input is CB1 of the PIA. This collects its pulses from the distance sensor via IC5b and transistor Q2.

An induced voltage is developed in the distance sensor coil each time the rotating magnet assembly passes the coil. This signal is rectified by diode D4, filtered and amplified by Q2. Finally, the distance signal is squared up using Schmitt trigger inverter IC5b.

Each time there is a distance IRQ, the distance function of the Rally Computer is accessed. It checks whether the distance counter is to be incremented, decremented or left unchanged and acts accordingly.

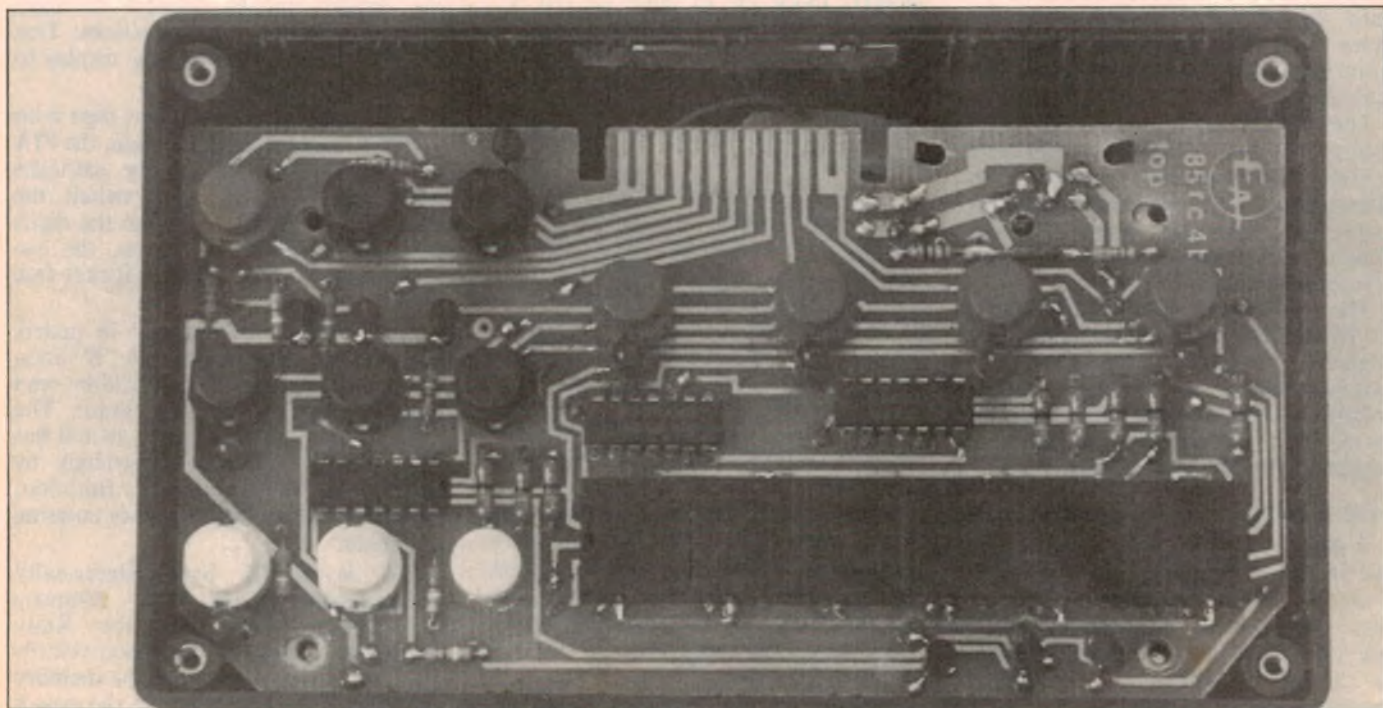Whenever one of the distance counters or the clock counts down to zero, the CA2 output of IC2 goes momentarily low and triggers a 555 timer, IC11. This timer provides a high



View inside the control unit showing how the LEDs and pushbutton switches are mounted (construction details next month).

The Latest from Yaesu!



Economy 70cm
Value & reliability - with the latest in features! That's the new FT-703 hand held. Tiny size: but what a performer: even has VOX with optional headset! Cat D-3508

\$479



New 2m mobiles, Too!
Want economy? Try the new FT207R. Want power? Try the new FT207RH. You get the choice - up to an amazing 45W output (Yaesu's new duct-flow cooling makes it all possible!) Both have 10 memories, dual VFO's plus all the new goodies that make 2 metres fun again!

FT207R (25/3W) Cat D-3515	\$699
FT207RH (45/5W) Cat D-3517	\$649




Mobile 70cm
Full 10 watts output on 70: two 4-bit microprocessors make everything so easy!
And it's small enough to go anywhere. Features a brilliant display for extra road safety - and with fast/slow band scanning, it's great, mate!
Cat D-3505

\$449



Push-Button 70cm
Real performance in a hand-held. Push-button keypad gives you real control; add the battery pack you want for the output you want!
Cat D-3509
10.8V Battery Pack Cat D-3506 **\$79**
12V Battery Pack Cat D-3507 **\$89**

\$499 Battery Not Inc.



FRV-8800 VHF Frequency Conv
Fits right inside case - complete with its own telescopic antenna. Frequency range 118-174MHz
Cat D-2823 **\$149**

FRA-7700 Active Antenna
Great for flat dwellers! No need for an outside antenna and preamp will pull in stations you didn't think possible!
Cat D-2845 **\$89.50**

FRT-770 Antenna Coupler
Ensures best performance from all types of antennas. A must if your antenna is not low impedance.
Cat D-2843 **\$95**

FRG-8800 DC Kit
Allows operation of your FRG-8800 on 12V DC. Great for field operation, monitoring, etc.
Cat D-2822 **\$2.50**

FRG-8800: All band all mode
And all singing, all dancing. Amazing performance in Yaesu's new masterpiece, the FRG-8800 receiver. Choice of two models, both featuring the very latest in receiver technology.

- 150kHz-30MHz coverage (FRG-8800)
- Fully CAT compatible (computer aided transceiver)
- Provision for VHF converter inside the receiver!
- 10 memory channels inbuilt (nothing more to buy!)

And much, much more. Ask for a free FRG-8800 brochure at your nearest Dick Smith Electronics store.

FRG-8800 (150kHz-30MHz)
Cat D- 2820 **\$799**

FRG-8800SW (2MHz-30MHz)
Cat D -2821 **\$749**
VHF converter to suit (118-174MHz)
Cat D-2823 **\$149**



2M/70cm FT2700RH
Versatility: both hands in a set so small you wouldn't believe it! Full duplexing, twin VFO's, ten memories...whatever you want, the 2700 has got!
And it even speaks to you: add the optional voice synthesiser and it actually tells you which frequency you're on. Hows that!!!

- 25 watts continuous on both bands
- two 4 bit CPU's for complete control
- Amazingly tiny size: just 150 x 168 x 50!!!

Cat D-3515 **\$945**

The best from



All these items available from your nearest Dick Smith Store.


Radio Despatch Service

ESTABLISHED 1934

SPECIALS

TOOLS:

Phillips & Allan key wrench sets.	NOW: \$1.50
6 pce. Jewellers screwdriver sets.	\$1.00
Long nose pliers.	\$2.50
Miniature precision tool kits.	\$1.00
Side cutting pliers 6"	\$2.00
Automatic wire strippers.	\$6.00

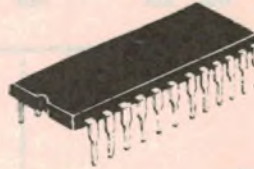

Our Sydney store stocks EVERY PC Board printed in "Electronics Australia" and "Electronics Today International". Over 1100 Boards in stock. Front Panels to order.

Computer Connectors

D Type connectors
Centronix connectors
Transition sockets
Transition holders
Solder
IDC

SWITCHES:

Rotary wafer switches.
Miniature push button (N/O, N/C)
Heavy duty toggles
Sliders — all over 75% off.

EXCESS 4000 SERIES

4011	40c
4012	45c
4019	70c
4027	60c
4066	45c
4069	40c

CONNECTORS:

Edge-Board-mount with feet \$2.50

X-L-R from 2-6 pin
RS232 Type — solder & IDC

I.C. in Stock

74 Series
74 LS Series
74 C Series
C Mos 4000
Linear
Intersil
I.C. Sockets
74HC.

ELECTRONIC CONTROL SECURITY SYSTEM

\$72⁹⁵



Push button. Accessories available.



V-212

\$690

1 only



We also stock:

Electrolube Cleaning & Lubricating Products.
Quality Computer Ribbon Cable to 50 way.

MAIL ORDER ACCEPTED: Now \$4.00 NSW



3 YEAR WARRANTY

70 SERIES WITH ANALOG & DIGITAL DISPLAY



Prices quoted include tax. We reserve the right to alter prices quoted without notice.


YES! WE HAVE MAIL AND PHONE ORDERS AND USE BANKCARD, MASTERCARD AND AGC FINANCE. OR VISIT OUR STORE.

We are closed on Public Holidays

Radio Despatch Service

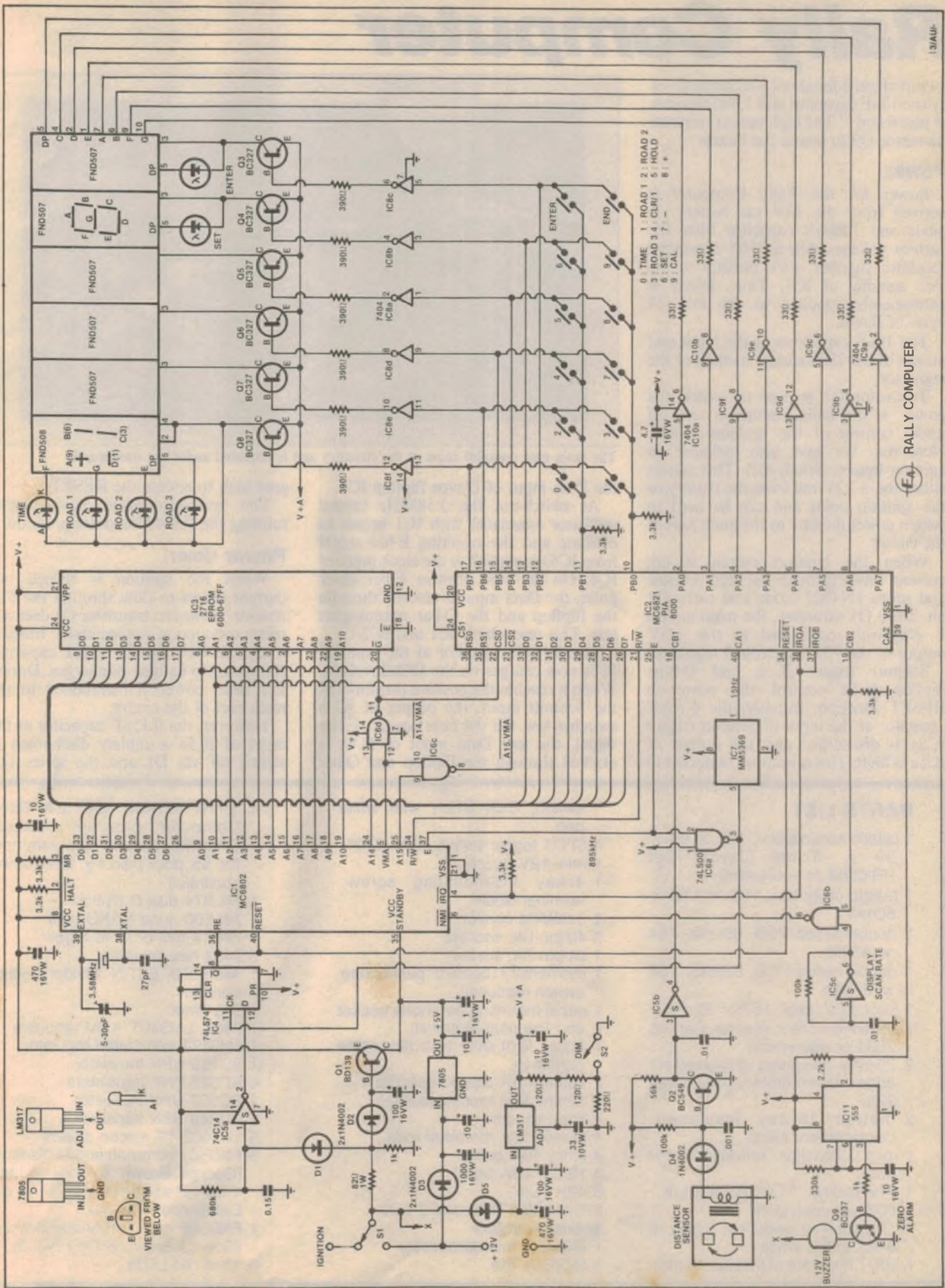869 GEORGE STREET SYDNEY 2000
TELEPHONES 211 0744 • 211 0816





RALLY COMPUTER

Rally Computer

output at pin 3 for about 3 seconds, as set by the $10\mu\text{F}$ capacitor and $330\text{k}\Omega$ resistor at pins 6 and 7. The high output turns on transistor Q9 to sound the buzzer.

Power


Power for the Rally Computer is derived from the 12V car battery. A diode and $1000\mu\text{F}$ capacitor filter the battery voltage while a 7805 3-terminal regulator supplies +5V directly to the Vcc standby of IC1. Thus, power is permanently supplied to the first 32 bytes of RAM.

The $10\mu\text{F}$ capacitors at the input and output of the 7805 ensure stability of the regulator.

Transistor Q1 is used to switch the power to the main circuit on and off under control of the ignition switch. Note that we have also included an ignition bypass switch (S1). This selects either the +12V rail from the battery or the ignition input and can be used to switch power directly to the main part of the circuit.

When the ignition switch is on, current flows through the 82Ω resistor and series 1N4002 diode and turns Q1 on. Since Q1 saturates, the main circuit is effectively connected to the +5V output of the 7805 3-terminal regulator.

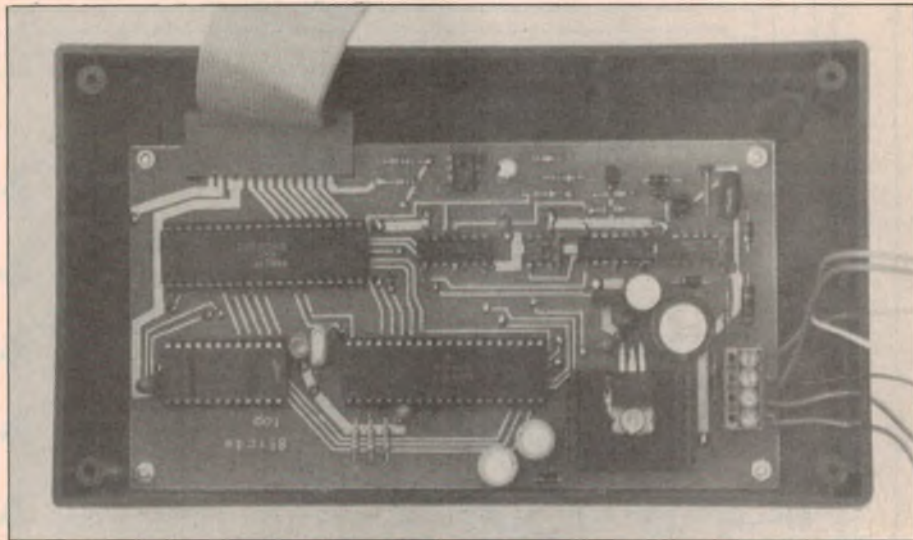Schmitt trigger IC5a and D-type flipflop IC5a control the power-on RESET function. Initially, the $0.15\mu\text{F}$ capacitor at the input of Schmitt trigger IC5a is discharged and the output of IC5a is high. This output is connected to



The main case contains most of the circuitry and is mounted under the dashboard.

the Data input of D-type flipflop IC4.

At switch-on, the 3.58MHz crystal oscillator associated with IC1 begins to oscillate and the resulting E-bar signal from IC6a is applied to the clock input of IC4. On the first positive E-bar clock pulse, the Data input is clocked through the flipflop and the Q-bar output goes low. This resets both IC1 and IC2.

The $0.15\mu\text{F}$ capacitor at the input of IC5a now charges via the $680\text{k}\Omega$ resistor. When it reaches the positive threshold of the Schmitt input, the output of IC5a switches low. On the next positive E-bar signal, the low Data input of IC4a is clocked through the flipflop and Q-bar

goes high to release the RESET.

The microprocessor now begins running the Rally Computer program.

Power down

When the ignition is turned off, current ceases to flow through the 82Ω resistor. However, transistor Q1 does not cease conduction immediately. Instead, it remains on while the $100\mu\text{F}$ capacitor connected to its base discharges. During this time, power is maintained to the main part of the circuit.

However, the $0.15\mu\text{F}$ capacitor at the input of IC5a is rapidly discharged at switch off via D1 and the series $1\text{k}\Omega$

PARTS LIST

- | | | |
|--|---|--|
| 1 plastic console box, 161 × 96 × 39 × 57mm (Jaycar Cat HB-6203 or equivalent) | 1 switch, C&K 8161, with white cap | 1 2716 EPROM with EA Rally Computer program (erased EPROMs can be programmed for \$5 post paid by <i>Electronics Australia</i>) |
| 1 plastic utility box, 195 × 113 × 60mm | 1 SPDT toggle switch, C&K 7101 | 1 74LS74 dual-D flipflop |
| 1 double sided PCB, 85rc4a, 164 × 87mm | 1 mini 12V buzzer | 1 74LS00 quad NAND gate |
| 1 double sided PCB, 85rc4b, 154 × 82mm | 1 4-way PC-mounting screw terminal block | 1 74C14 hex Schmitt trigger |
| 1 Scotchcal label, 157 × 92mm | 1 3.58MHz crystal | 3 7404 hex inverters |
| 1 distance sensor (Jaycar Cat XC 2034 or equivalent) | 2 40-pin DIL sockets | 1 MM5369 EST/N divider, 60Hz version |
| 2 26-way insulation displacement edge connectors, Amphenol 225F | 1 24-pin DIL socket | 1 555 timer |
| 2 metres 26-way insulation displacement cable | 1 momentary contact pushbutton switch (optional) | 1 7805, LM340T +5V regulator |
| 1 mini U heatsink, Altronics Cat H 0502 | 1 panel mounting earphone socket and line plug (optional) | 1 LM317T adjustable regulator |
| 1 Thermalloy TO-220 heatsink, 6038 or equivalent | 1 metre light duty twin flex cable (optional) | 1 BD139 NPN transistor |
| 12 Isostat key switches, 5 red, 5 black and 2 white | 2 25mm 4BA tapped spacers | 6 BC327 PNP transistors |
| 1 SPDT alternate action pushbutton | 2 12mm 4BA tapped spacers | 1 BC337 NPN transistor |
| | 4 6mm spacers | 1 BC549 NPN transistor |
| | 4 15mm 4BA threaded rods | 5 1N4002 1A silicon diodes |
| | 4 6mm 4BA bolts | 5 FND507 common anode displays (George Brown & Co Pty Ltd, 174 Parramatta Road, Camperdown 2050) |
| | 4 12mm 4BA bolts | 1 FND508 common anode display (George Brown & Co Pty Ltd) |
| | 8 4BA nuts | 6 3mm red LEDs |
| | 2 6mm 6BA bolts and 2 nuts | |
| | Semiconductors | |
| | 1 MC6802 microprocessor | |
| | 1 MC6821 PIA | |

resistor to ground. This sets the output of IC5a high and thus Q-bar of IC4 goes low on the next positive E-bar clock pulse to again reset IC1.

This power down sequence ensures that memory in the first 32 bytes of RAM is not corrupted at this critical stage.

As well as controlling power to the main circuit, the ignition switch also switches power to the LM317 regulator which supplies the display driver transistors (Q3 — Q8).

A 1N4002 diode and 470 μ F capacitor filter the battery voltage to the input of the LM317, while the 100 μ F and 10 μ F capacitors at the input and output of the regulator ensure stability. The output voltage of the regulator is set by the 120 Ω and 220 Ω resistors connected between the output and adjust terminals and ground.

Since about 1.25V is applied between the OUT and ADJ terminals, around 10.5mA flows through the associated 120 Ω resistor. This current also flows through the 120 Ω and 220 Ω resistors connected between ADJ and ground. With both these resistors in circuit, the ADJ terminal is jacked up by 3.4V above ground. This produces +4.65V at the output.

When the 220 Ω resistor is shorted by the DIM switch, the output is about +2.5V. The DIM switch thus controls the voltage applied to the displays and consequently sets the display brightness.

That concludes the circuit description. Next month, we shall describe the construction and give the installation details.

Capacitors

- 1 1000 μ F/16VW PC electrolytic
- 2 470 μ F/16VW PC electrolytic
- 2 100 μ F/16VW PC electrolytic
- 1 33 μ F/16VW PC electrolytic
- 5 10 μ F/16VW PC electrolytic
- 1 4.7 μ F/16VW PC electrolytic
- 1 1 μ F/16VW PC electrolytic
- 1 0.15 μ F metallised polyester
- 2 .01 μ F metallised polyester
- 1 .001 μ F metallised polyester
- 1 27pF miniature ceramic
- 1 5.2-30pF D series Murata trimmer (green), Altronics Cat. R 4007

Resistors (1/4W, 5%)

- 1 \times 680k Ω , 1 \times 330k Ω , 2 \times 100k Ω , 1 \times 56k Ω , 5 \times 3.3k Ω , 1 \times 2.2k Ω , 2 \times 1k Ω , 6 \times 390 Ω , 1 \times 220 Ω , 2 \times 120 Ω , 1 \times 82 Ω 1W, 8 \times 33 Ω

Miscellaneous

Hook-up wire, solder, machine screws and nuts, washers, etc.

INTERESTED IN ELECTRONICS? THEN WHY NOT TURN YOUR HOBBY INTO A CAREER?



Alan Mulraney, Stott's Graduate, in his workshop.


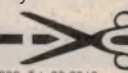
In this fast-changing electronic world people with interest and training are going to be in demand. Turn your interest into a lucrative career in any one of the following fields:

**Computers • Industrial Controls • Medicine
Radio Communications • Domestic Radio & Television**

Electronics plays an important role in these and many other fields. With a Stott's Home Study Course, training is easy, and will prepare you for a career in the manufacture, installation, commissioning, sales or servicing of electronic equipment.

You'll have experienced, professional instructors who will guide you through an integrated theory/practical program. They'll give you individual attention and advice, and prompt replies to all test assignments and queries. And best of all, you'll study at your own pace, in your own home.

Send the coupon today. It may be the smartest move of your life.

Stotts
CORRESPONDENCE COLLEGE

The name to trust in correspondence education.

**Please send me free, and without obligation,
full details of the following courses:**

(PLEASE PRINT)

MR. MRS. MISS _____ AGE _____

ADDRESS _____

POSTCODE _____

Stott's undertake that no sales counsellor will visit you.

Melbourne, 140 Flinders Street, 3000. Tel: 63 6212

Sydney, 383 George Street, 2000. Tel: 29 2445

Brisbane, 65 Mary Street, 4000. Tel: 221 3972

Adelaide, 226 Pulteney Street, 5000. Tel: 322 3700

W. Perth, 25 Richardson Street, 6005. Tel: 322 5481

Hobart, 150 Collins Street, 7000. Tel: 34 2399

New Zealand, Box No. 30 990, Lower Hutt. Tel: 676 592

**The Stott's range of courses
in Electronics is:**

- Intro to Electronics
- Digital Electronics for Technicians/Servicemen
- Microprocessors
- Radio Receivers
- Radio/TV Servicing
- Colour Television

ALA/ST5303/EA6R5

We've got the lot, at

COMPONENTS!



SIP RESISTORS
Standard values

1-9	10+
6 Pin	50¢ 40¢
8 Pin	60¢ 50¢
10 Pin	65¢ 60¢



RELAYS
Massive 3A connectors

1-9	10+	100+
S.P.D.T. S14060		
\$1.20	\$1.10	\$0.90
D.P.D.T. S14061		
\$1.50	\$1.40	\$1.20



NEW SWITCHES

1-9	10+
SPDT Cat. S11040	
\$1.50	\$1.40
DPDT Cat. S11042	
\$1.60	\$1.50



QUALITY MOMENTARY (RED BODY)
SPDT Cat. S11050

1-9	10+
DPDT Cat. S11052	
\$1.50	\$1.40
\$1.95	\$1.75




DIP SWITCHES

1-9	10+
2 Way	\$1.50 \$1.10
4 Way	\$1.60 \$1.20
5 Way	\$1.70 \$1.30
7 Way	\$1.80 \$1.40
8 Way	\$1.90 \$1.50



FUSE SPECIAL 3AG
Two values, 3 Amp and 1 Amp

1-99	100-999	1000+
8¢ each	6¢ each	5¢ each
STOCK UP NOW		

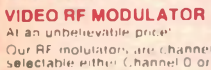

VIDEO RF MODULATOR
At an unbelievable price!
Our RF modulators are channel selectable either Channel 0 or Channel 1

1-9	10+
at S16040	
\$4.95	\$3.95



PRIME SPEC RED LEDS
We bought 100,000 so you can reap the benefits!
Cat. Z10150

1-9	10-99	100+
\$0.10	\$0.09	\$0.08



ENCLOSED ROTARY SWITCHES AT SPECIAL PRICES!!

1-9	10+
\$1.20	\$1.00



CRYSTALS SPECIALS
Prime Specs. We just have too many in stock!

3.5795 MHz	14.318 MHz
4.00 MHz	18.00 MHz
4.1934 MHz	20.0 MHz

All \$2.50 each!
10 or more \$2 each!



CONNECTORS!


SOLDER CENTRONICS PLUGS
Unreal price for absolute top quality. Normally \$14.95 (Our opposition charge up to \$19.95)

1-9	10+	100+
\$6.50	\$5.95	\$4.95




36 WAY CENTRONICS CRIMP PLUG
Cat. P12200

1-9	10-99	100+
\$7.95	\$7.50	\$7.25

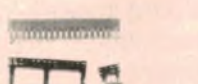

IC SOCKETS (LOW PROFILE) How cheap can they go??

1+	10+	100+	1000+
8 Pin Cat.			
15c	14c	12c	09c
14 Pin Cat.			
16 Pin Cat.	15c	14c	10c
17c	16c	15c	11c
18 Pin Cat.			
18c	17c	16c	13c
20 Pin Cat.	29c	28c	26c
24 Pin Cat.	35c	33c	28c
40 Pin Cat.	45c	40c	35c

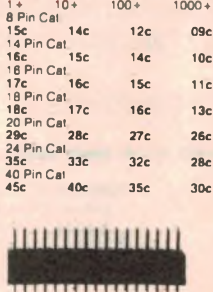

UNPROTECTED HEADERS
Dual in Line 2.54mm

1-9	10+	
10 Way Cat. P12240	\$1.95	\$1.75
16 Way Cat. P12246	\$2.95	\$2.65
20 Way Cat. P12250	\$3.25	\$2.95
26 Way Cat. P12256	\$3.75	\$3.40
30 Way Cat. P12260	\$3.95	\$3.55
34 Way Cat. P12264	\$4.95	\$4.50
40 Way Cat. P12270	\$5.25	\$4.75
50 Way Cat. P12275	\$5.95	\$5.35


CASES!



PROFESSIONAL SERIES RACK MOUNTING CABINETS
These beautifully crafted rack cabinet boxes will give your equipment a real 1st class appearance.

- All aluminium construction
- Removable top and bottom panels
- All dimensioning conforms to the International Standard
- Natural or black finish
- Ventilated lid
- Deluxe brushed finish anodised front panel.

1-4	5+
H10401 Natural	\$48.50 \$43.50
H10402 Natural	\$55.50 \$49.50
H10403 Natural	\$62.50 \$55.50
H10411 Black	\$49.50 \$43.50
H10412 Black	\$55.50 \$49.50
H10413 Black	\$62.50 \$55.50

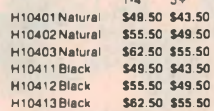

ECONOMY 19" RACK CASE
Tremendous Value! Dimensions W 480 x H 134 x D 250mm
Cat. H10400


1-9	10+
\$34.95	\$29.50



NEW SLOPING CASES
Plastic with metal front panel available in two sizes

Cat. H10450	190x120mm	\$9.95
Cat. H10455	256x185mm	\$17.95

(measurements are approx. only)

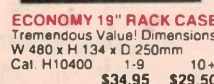

TOOLS OF TRADE!

DIGITAL MULTIMETER YFE YF1100 FEATURES

- Large easy to read 3 1/2 digit display
- Facilities for transistor and diode testing
- Clearly laid out front panel
- 10A DC AC range
- Priced to undersell all others

Cat. Q16025	\$69.50
-------------	---------



LOGIC PROBE 3800A
Features 20MHz memory TTL/CMOS operation. Normally \$29.50
Cat. Q11272

1-9	10+
\$23.50	\$19.50



UNIVERSAL SOLDERING IRON STAND
Cat. T11302

\$5.95 slashed to \$3.95




TRANSISTOR NIPPERS
Normally \$7.95! This Month
Cat. T12070

\$6.95




MICRO NIPPERS
Normally \$9.95 This Month
Cat. T12050

\$6.95

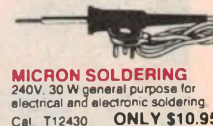

MICRON SOLDERING
240V, 30W general purpose for electrical and electronic soldering
Cat. T12430

ONLY \$10.95

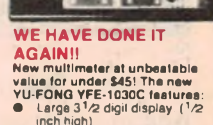

WE HAVE DONE IT AGAIN!
New multimeter at unbeatable value for under \$45! The new YU-FONG YFE-1030C features:

- Large 3 1/2 digit display (1/2 inch high)
- Autopolarity "±" display for Negative input
- High over-load protection for all ranges
- Over-load display highest figure "1" or "-1" alone glows
- Power consumption 20mW approx.

Cat. T12430	\$49.95
-------------	---------



IC'S GALORE!

4116	1-9	10+
\$1.80	\$1.70	\$3.25
4164	\$2.25	\$2.95
2716	\$5.90	\$5.50
2732	\$6.25	\$5.95
2764	\$8.25	\$7.95
27128	\$12.50	\$11.50
6116	\$5.50	\$5.15
41256	\$14.50	\$12.50



RECHARGEABLE 12V GELL BATTERIES
Leakproof and in 3 convenient sizes, these long service life batteries are ideal for burglar systems, emergency lighting or as a computer backup power supply. Ideal for many power needs.

Cat. S15029	12V 1.2 AH	\$17.95
Cat. S15031	12V 2.6 AH	\$39.50
Cat. S15031	12V 4.5 AH	\$49.95



NICAD BATTERIES
Save on carbon batteries with these Apollon Nickel cadmiums. Rechargeable up to 1000 times!

1-9	10+	
Cat. S15020	AA500	\$2.45
Cat. S15021	C1.8 AH	\$2.25
Cat. S15022	D4 AH	\$4.95
\$7.95	\$6.95	

HARDWARE!



BRAND NEW FANS
Not noisy pullouts! Stacks of uses in power amps, computers, hotspot cooling etc. Anywhere you need plenty of air.

240V 49dB	Cat. T12461	\$10.95
115V 49dB	Cat. T12463	\$10.95
240V 3 1/2"	Cat. T12465	\$10.95
115V 3 1/2"	Cat. T12467	\$10.95

10 Fans (mixed) less 10%



BULK CABLE 100M ROLLS

Cat. W11222	3C2V75 OHM	\$22.00
Cat. W11224	5C2V75 OHM	\$35.00
Cat. W11219	4 Core Shielded	\$49.00



PANEL METER BARGAINS!
250ua Sensitivity Panel cut out 36 x 16mm. Mounting hole centres at 49mm
Cat. Q10400

normally \$4.50	NOW \$3.95
-----------------	------------



TELEVISION ACCESSORIES!


250ua Sensitivity centre "O" very useful for balanced circuit and applications needing a centre "O" or null indication
Cat. Q10405

normally \$4.95	NOW \$3.95
-----------------	------------




HYBRID SPLITTERS

2 Way	\$3.95
4 Way	\$5.95

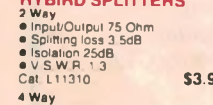

300 OHM COUPLERS
Suitable for UHF, VHF and FM

2 Set	\$2.85
4 Set	\$4.90

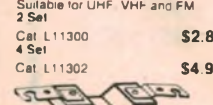


UHF/VHF OUTDOOR MATCHING TRANSFORMER
75/300 Ohm. Waterproof type
Cat. L11020

\$3.75



UHF/VHF/FM ANTENNA
Frequency: VHF 48.216 MHz (Ch 1-12)
UHF 536.764 MHz (Ch 25-62)
Impedance: 75/300 (200) Ohm
Element: VHF 4, UHF 9
Gain (dB): VHF 4-6 UHF 4-8
Cat. L11014

\$39.50

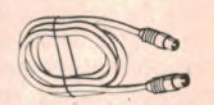

CONNECTOR CORDS
For TV/VTX (using cord 3C-2V)
2.5m long

Male to Female	\$2.95
Male to Female	\$2.95



CO-AXIAL CONNECTORS
Socket to socket

L12260	\$0.75
Plug to plug	\$0.75
L12259	\$0.75
Plug to socket	\$0.75
Cat. L12761	\$0.75

CIRCUIT EQUIPMENT!




S100 PROTOBOARDS
SAVE \$20

Horizontal Bus	\$19.50
Cat. H19125	
Vertical Bus	\$19.50
Cat. H19130	
Pad Per Hole	\$19.50
Cat. H19135	



NEGATIVE & POSITIVE CIRCUIT RESIST
Make your own presensitized PC Boards. POSITIVE PHOTO RESIST using 1-1 tapes and pads on clear film for one off or prototypes. Resist: 50ml bottle for approx. 1500 sq cm of pcb.
Cat. P85500

\$6.95

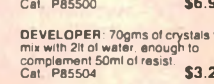


DEVELOPER: 70gms of crystals to mix with 2fl of water, enough to complement 50ml of resist.
Cat. P85504

\$3.25



NEGATIVE PHOTO RESIST for using normal negative PCB images. Resist. 50ml bottle for approx. 1500 sq cm of pcb.
Cat. P85508

\$5.45

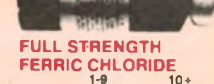

ETCHANT: 400gms of crystals to mix with 1 to 1 1/2 lts of HOT water.
Cat. P85512

\$3.25

Rod Irving Electronics! *

*If not, then very nearly!

SECURITY EQUIPMENT!



LOCAL BURGLAR ALARM CONTROL PANEL

The odds against you are climbing and prevention is better than cure!

- Adjustable exit/entry time delay and alarm time (avoids unnecessary noise pollution)
- Provision for battery back-up.
- Temper switch
- Optional outputs: Sirens bells, floodlights, automatic diallers, tape recordings, closed circuit TV, etc.
- Accepts N.C. and N.O. detectors such as infrared, microwave ultrasonic wireless vibration sensor, magnetic switch, door mat, smoke detector, glass breakage sensor, panic button etc.

Cat. S15051 \$99.95



ULTRASONIC BURGLAR ALARM

- Easy to install
- Connect with magnetic switch, infrared detector, etc.
- Equip with horn/speaker, lockswitch, flashlight, closed circuit TV, etc.
- Rechargeable battery circuit with recharge indicator L.E.D.
- N.O. and N.C. circuit breakdown indicator
- Low dry battery indicator

Cat. S15052 \$89.95



MINIATURE BUZZER

5-15V White or black
Cat. A15062 1-9 \$1.95 10+ \$1.75



HORN CRAZY!!

BW, aluminium or plastic.
Normally \$9.50
Aluminium Cat. C12015
Plastic Cat. C12010
1-9 \$6.50 10+ \$5.95



ULTRASONIC MOTION DETECTOR

A compact design that can be used with virtually any alarm system which has an input for N.C. or N.O. external sensor. Coverage is approximately 110 degree angle and up to 8 metres. Comes with detailed instructions.
Cat. S15033 \$39.95



MOUNTING BRACKET

For above Ultrasound Alarm and features ball pivot for horizontal and vertical adjustment.
Cat. S15042 \$11.95

VIDEO ACCESSORIES!



TDK VIDEO TAPES AT BARGAIN PRICES!

VHS:	E60	\$12.50
	E120	\$12.50
	E180	\$11.80
	E240	\$22.40
BETA:	L250	\$13.50
	L500	\$14.40
	L750	\$17.50



VDK1 VIDEO DUBBING KIT

For European and Japanese machines.
Contains:
Audio/Video 6 pin DIN plug to 6 pin DIN plug 1.5 metres
Audio/Video 6 pin DIN socket to (a) Video RCA plug (b) Audio 5 pin DIN plug (Both 16cm in length)
Video 1 each plug adaptor (PA21) RCA socket to PL259 plug (PA23) RCA socket to BNC plug
Audio 5 pin DIN socket to 2 RCA plugs 18cm length 2 plug adaptors (PA60) RCA socket to 3 5mm phone plug
Cat. \$16.95

AUDIO PRODUCTS!



P.A. SPEAKERS

Low dual cone wide range, 200mm (8in.) Ideal for public address, background music, etc. Tremendous Value at these prices!
Cat. C12000 1-9 \$5.95 10+ \$4.95



Would you like a quality sound system in your car? ...at an affordable price?!!

Rod Irving Electronics now sell quality Ferrari sound systems (A brand everyone knows and trusts.) Prices start from a very affordable \$55.95. Feel free to call in for a personal demonstration at either of our two stores.

FERRIS 1600: AM/FM Manual Car Radio. Integrated Circuit. Automatic Dual Polarity.

FERRIS JM 700: AM/FM/MPX Radio/Auto Reverse Cassette Stereo with Lock-in F/Forward and LOC/DX Switch. Output 7 Watts per Channel. Balance and Tone Controls. Overall Dimensions: 162(W)x114(D)x44mm(H).

FERRIS JMPA 600B: Auto Reverse Stereo Cassette Player with AM/FM/MPX Electronic Scanning, Digital Radio and Digital 12 Hour Clock. 12 Station Memory Metal/Normal Tape Switch. 8W/8W Max. Local/DX Switch. FM Interference Absorption Circuit. Base and Treble Control.

FERRIS FA 100a: 10 Level Graphic Equaliser Amplifier with LED read-out on L & R Channels. Fader Control. 20W/20W 4 speaker Wiring.

FERRIS FA 104: High Power Module, up to four times your volume, suits all Ferrari Power Sets and most other Car Stereo Units with Normal IC Output.


FERRIS F7 55X: Flush Mount 4-8 Ohms 50z. Dual Cone. 5 Watts NOM. 10 Watts Max. Mesh Grille.

FERRIS TR1-510: "Super Power Deluxe" Flush Mount 4 Ohm 10oz. Triaxial Three Way 6 1/2 inch Diameter. Mesh Grille 40 Watts Max.



ELECTRONIC CASSETTE DEMAGNETISER

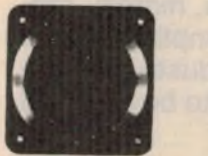Save \$2. Rec. retail \$19.95
Cat. A1006 NOW \$17.95



PHILIPS SPEAKERS

You don't have to "imagine" Philips quality at these prices!
Cat. C12030 AD01610 T8 \$12.95

Cat. C12040 AD02160 SQ8 \$34.95

Cat. C12045 AD70620 MB \$49.00

Cat. C12050 AD12550 W8 \$79.00

JOYSTICKS!



CENTRE RETURN JOYSTICK


Features 2x150K pots, long shaft 40mm with 25mm control ball.
Bonus adjustable offset feature on pots.
Cat. X156371-9 10+ \$9.95 \$8.95



JOYSTICK FOR APPLE

Ideal for games or word processing. Fits most 6502 "compatible" computers.
Cat. C14200 \$27.95

COMPUTER ACCESSORIES!

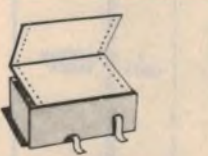

COMPUTER PAPER

Top quality at a very affordable price!
Blotk 11 x 9 1/2" 2,000 sheet, quality 60 gsm bond paper.
Cat. C21001 \$29.50



RITRON (ZETA) DATASHEET

For data loading and saving this Micron Datasheet suits most home computers and features tape counter, monitor function for audio verification and side volume control for output level.
Cat. C14900 \$29.95



RITRON 2

Stylish swivel base monitor, available in amber or green.
1-9 10+
Green Cat. X14500 100+ \$215 \$205
Amber Cat. X14500 \$219 \$205



RITRON MULTI PURPOSE MODEM

Our New RITRON Multi Purpose Modem has arrived and has all the standards you require. Just check the Ritron's features:
● CCITT V21 300 Baud Full duplex
● CCITT V23 1200/75
● Bell 103 300 Full duplex
● Bell 202 1200 Half duplex
● Auto answer, auto disconnect
● Telecom Approval No. C84-371134
\$399



RITEMAN INFO RUNNER

An exciting new printer from the experts "Riteman". This compact stylish printer performs like printers twice its price and size. 120 C.P.S. dot resolution graphics, tractor/injection feed, 10" paper.
\$459



M4851

Slimline 5 1/4" disk drive. Double sided, double density 500K unformatted, 40 tracks/side. Steel band drive system.
Cat. C11901 \$199
Case & Power Supply to suit
Cat. X11011 \$89



TELECOMMUNICATION PLUG TO 2 SOCKETS.

Ideal for modem connections.
Cat. Y16014 \$12.95



READY MADE CABLES

Serial to Serial
Cat. P19011 \$18.95
Parallel centronics to centronics
Cat. P19013 \$23.95



IBM COMPATIBLE COMPUTER

\$2,450
Including Tax!

*IBM is a registered trademark.

CHEAP DISKS!



DISKS GALORE!!

All prices for boxes of 10.
Single disks 10% extra.
SPECIALS!

MD525-01 S/S D/D Cat. C12501 \$29.50
MD550-1 D/S D/D Cat. C12504 \$39.50

Head Cleaners

C12551 S' Head Cleaner \$10.50
C12651 B' Head Cleaner \$11.50

VALUE LIFE

C12421 S/S D/D \$22.95
C12425 D/S D/D \$29.95

8" Verbatim

C12800 FD32-1000 S/S/D/D \$39.50
C12801 FD32-8000 S/S/D/D \$48.50
C12802 FD32-9000 S/S/D/D \$49.50
C12803 FD34-1000 S/S/D/D \$49.50
C12804 FD34-8000 S/S/D/D \$55.50
C12805 FD10-4008 D/S/D/D \$59.50
C12806 FD10-4015 D/S/D/D \$64.50
C12807 FD10-4026 D/S/D/D \$64.50
C12808 FF32-2000 D/D/D \$69.00
C12809 FF34-2000 S/D/D/D \$69.00
C12810 DD32-4000 D/S/D/D \$52.50
C12811 DD34-4001 D/S/D/D \$52.50
C12812 DD34-4008 D/S/D/D \$54.50
C12813 DD34-4015 D/D/D \$54.50
C12814 DD34-4026 D/S/D/D \$54.50

5 1/4" Verbatim Disks

5 year DataLife guarantee
MD525-01 \$29.50 (S/S D/D) C12501
MD525-10 \$39.50 (S/D D/D 10 Sect. 40 Tracks) C12502
MD525-16 \$39.50 (S/S D/D 16 Sect. 40 Tracks) C12503
MD550-01 \$39.50 (D/S D/D) C12504
MD550-01 \$49.50 (D/S D/D 10 Sect. 40 Tracks) C12505
MD550-16 \$49.50 (D/S D/D 16 Sect. 40 Tracks) C12506
MD577-01 \$49.50 (S/S D/D Soft Sect. 80 Tracks) C12507
MD577-10 \$59.50 (S/S D/D 10 Sect. 80 Tracks) C12508
MD577-16 \$59.50 (S/S D/D 16 Sect. 80 Tracks) C12509
MD557-01 \$59.50 (D/S D/D Soft Sect. 80 Tracks) C12510
MD557-16 \$59.50 (D/S D/D 16 Sect. 80 Tracks) C12511



XIDEX DISKS

1-9 10+
Box of 10 S.S. D.D. Cat. C12401 \$34.50 \$29.50
Box of 10 D.S. D/D Cat. C12410 \$44.50 \$39.50



DISK STORAGE BOXES

Efficient and practical, these disk storage boxes protect your disks from being damaged or lost.
50" Features smoked plastic cover with provision for a lock. High impact ABS plastic base.

Cat. C16025 \$26.50
50" Features smoked plastic cover. Divided into 10 sections, each fan elevates the disks for easy identification and access.
Cat. C16050 \$34.50



BLANK DATA CASSETTES

Brings out the best in any micro!
Cat. D11141
1-9 \$1.50 10-99 \$1.40 100+ \$1.20



SWIVEL BASE

Makes life easier, normally \$29.50
Cat. D11100 \$27.50

PUBLICATIONS!



Inside CP/M \$41.95

by David E. Cortesi

The Complete Home

Video Book Vol. 2 \$25.95

The Robotics Primer \$17.95

by Robert A. Ullrich



ROD IRVING ELECTRONICS
425 High Street,
NORTHCOTE, 3070
VICTORIA, AUSTRALIA
Phone (03) 489 8866
TELEX: AA 38897
48-50 A Beckett Street,
MELBOURNE, 3000
VICTORIA, AUSTRALIA
Ph. (03) 663 6151
Mail Order and
correspondance:
P.O. BOX 235
NORTHCOTE 3070

MAIL ORDER HOT LINE




(03) 481 1436


POSTAGE RATES

\$1-\$99.99	\$2.00
\$10-\$24.99	\$3.00
\$25-\$49.99	\$4.00
\$50-\$99.99	\$5.00
\$100-\$199	\$7.50
\$200-\$499	\$10.00
\$500 plus	\$12.50

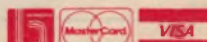This is for basic postage only. Comet Road freight, bulky and fragile items will be charged at different rates.



Errors and omissions excepted

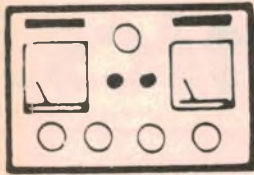

First aid for a motel TV system

One area of television in which day-to-day expertise appears to have lagged behind the available technology is that of antenna distribution systems as used in blocks of home units, motels, etc. The butchery approach by electricians attempting such installations is well known, but, even within the industry, where those concerned should know better, there appears to be a woeful amount of ignorance and a slap-happy approach.

These comments were prompted by a story from my colleague on the NSW south coast, involving the TV system in a local motel and the various problems which can occur in such a situation. For any reader likely to be similarly involved there are several lessons to be learned. This is the story as he told it to me.

The motel in this story is one of a large chain operated by the one company — a matter of some importance as far as administration is concerned — and, in its original form, had been built before there was any TV available in the area. As it stands today it consists of a central block, which is the original building, having 22

units, office, dining room, kitchen, manager's quarters, etc, laid out in a rectangular arrangement enclosing a courtyard or quadrangle.

About 50 metres from the central block, in different directions, are two additional blocks of 10 units each, referred to as the western block and the southern block. Both these blocks were added later, first one and then the other as business increased, and are connected to the central block by covered walkways.

A natural result of all these factors was that the TV distribution system had been installed after the central block had

been built and whoever had done the job had run all the coax externally. I can't really blame him for this because it would have been a prohibitively expensive job to run it in the roof and wall in the conventional way. The roof is a low pitched style of corrugated fibro cement, and large sections of it would have had to be removed.

The two later blocks were a better proposition. The western block is well above ground level, providing easy access under the floor, while the southern block was apparently wired when it was built. This had been done with 300Ω ribbon for the early monochrome sets.

In fact, one of the first jobs I did for the motel, some 10 years ago when they first called me in, was to rewire this block with coax to accommodate colour sets. And that produced the first of many surprises. Apart from the need to change the cable there was the problem that there was little or no signal in several units, a condition which apparently had prevailed since the system was first installed.


The reason wasn't hard to find. Removing the wall mounted outlet plates in the offending units revealed the simple fact that there was no ribbon behind them. In short, they had never been connected. Just why the contractor had done this, or why the management had allowed him to get away with it, is one of those mysteries lost in time.

In rewiring this block I was forced to run the cable along the front wall, just above path level, but below floor and entrance step level. It was then looped through the wall to each outlet plate.

As for the central block, the weather had taken its toll. Even at that time the outer covering of the coax was beginning to crack and break away, allowing moisture to enter and generally degrade performance. In one case, in order to cut down the length of cable with consequent losses, the coax had been run across the roof above the fibro.

But these weren't the only problems. Countless technicians, electricians, and do-it-yourself types had all had a go at the system over the years, with the result that it was now a real patch job. And, while I continued to do what I could to

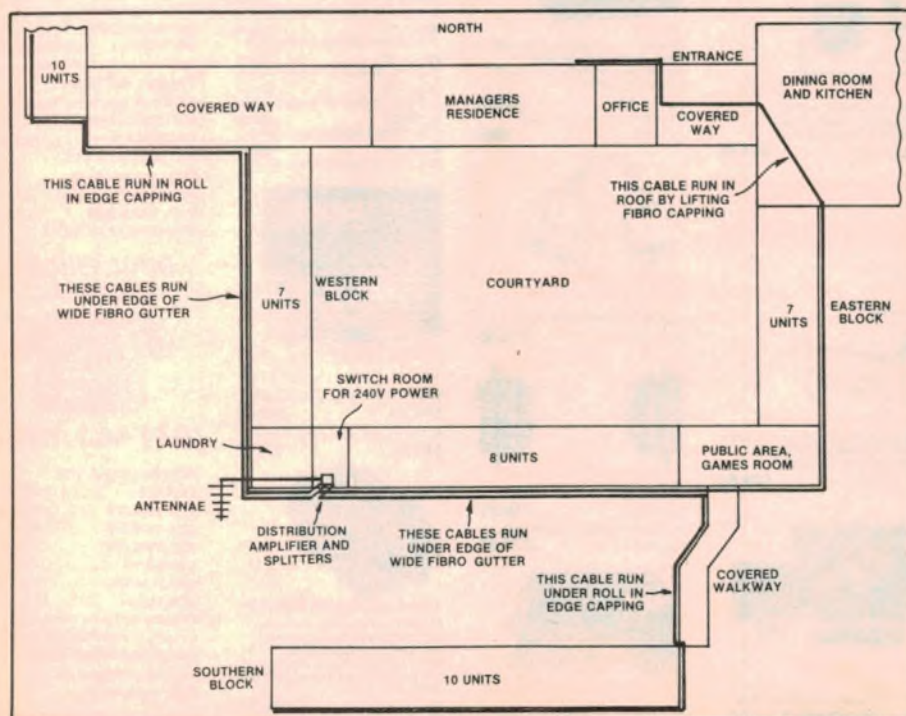Below: this diagram shows the path of the cable to each section of the motel.



keep the system working this was becoming more and more difficult and I kept advising those in charge that, sooner or later, the whole system would have to be overhauled and largely re-wired.

But getting any action was difficult. The fact that it was only one unit in a large chain meant that decisions of this kind were outside the scope of the local manager, who could only make recommendations to head office. And, to make matters worse, the managers were changed from time to time. I would just get a manager on-side and convince him that the work needed to be done when he would be shifted somewhere else and I would have to start all over again with a new manager.

Ultimately, it was the system itself which forced the issue. It simply reached the stage where the performance was quite unacceptable and I was forced to adopt the attitude that it was just not possible to go on patching it any further. So the then manager was finally given the go-ahead to get a quote for a major re-wire job.

And so I set to work to assess what would be needed. In addition to the coax, the antenna system itself had also reached the end of its life, having succumbed to the salt atmosphere of the coastal district. The distribution amplifiers were also suspect. They had been mounted on the outside of the building, under the eaves, where they were exposed to the weather. Again, damp salt atmosphere had taken its toll.

A further complication involved the western block. At some time in its history some technician had decided to divorce this block from the rest of the system and provide it with its own antenna and distribution amplifier. This wasn't necessarily a bad concept, but the actual installation had fallen down on several points.

First, there is the matter of signal strength in this area. The only reliable signals are those on channels nine and 11 from translators near Moruya and, taking into account the strength of the translators, the distance involved, and the terrain, the level at the motel site is nothing spectacular. Adequate signals are available, but one has to search for them.

In this case the antenna the technician had chosen, and its position, had resulted in about $500\mu\text{V}$ of signal. In my experience, the minimum signal to aim for, whether for a single set, or to be fed to a distribution amplifier, is $1000\mu\text{V}$ (1mV) to ensure noise free pictures. Below this figure there is a serious risk of some noise which no amount of subsequent amplification will correct. On the contrary, the noise will be amplified along with the signal, and added to any

noise generated in the amplifier.

But, even if this signal had been adequate, his subsequent treatment of it was not. He fed it into a small distribution amplifier having about 10dB gain; this to serve 10 sets. Now there is just no way that such a signal could do the job, as a few simple calculations would have revealed, had he bothered to make them.

Distribution systems

Which brings me to the point where it may help the reader if we look at the whole concept of distribution systems of this kind and the basis of their design and operation. The most basic requirement in any situation involving more than one set connected to one antenna — and of which most readers would be aware — is the need to isolate each set from its neighbours.

A major reason is the need to prevent any local oscillator re-radiation from any one set from interfering with any other set. It is also necessary to ensure that branch runs of cable are either (ideally) always terminated by a set or dummy load or, at least, adequately isolated from the rest of the system.

As many a do-it-yourselfer and electrician has discovered, an unterminated run of cable, connected to an existing antenna system, can play havoc with the signals. If the length of such a run should happen to equal an odd number of quarter wavelengths, at a particular channel frequency, it will act as a short circuit at that frequency, with disastrous results to the signal strength.

In practical terms there are two commonly used devices to provide the necessary isolation between sets; splitters and "T"s. Typical splitters split the signal equally either two ways or four ways, allowing this number of sets to operate from the one antenna. A two-way splitter will normally cause about 3.5dB loss in each outlet, at VHF, and a four-way unit about 7dB. They will provide between 25 and 30dB of isolation at VHF and slightly less at UHF.

They are intended mainly for domestic installations, or perhaps small showroom displays, and it goes without saying that the incoming signal must be strong enough to withstand the losses involved and still provide each set with an adequate signal. They can also be used in reverse as combiners; ie, to feed two antennas — VHF and UHF — to one set.

The "T" is a completely different device. As its name might imply, it is designed to provide a branch off a main run of cable, the main run being through the horizontal portion of the "T" and the branch via the vertical portion. Unlike the splitter, the losses via the two outlets

Looking to purchase instruments

We are stockists of Hitachi, Fluke, Trio, Goodwill, Maguro, Aaron and Kikusui: so if you're in the market for an oscilloscope, think of David Reid.

20 MHz KIKUSUI COS5020

\$697.00

+ 20% Sales Tax
INCLUDING TWO PROBES
AND DUST COVER



(Vertical Axis), 1-2-5 sequence, 10 range: Sensitivity, 5mV/DIV - 5V/DIV, (within $\pm 3\%$); Frequency response, DC (AC 10Hz) - 20MHz (-3dB, 8DIV); Operation mode, CH1, CH2, DUAL, ADD, X-Y (DUAL automatic switching ALT and CHOP); (Horizontal Axis), 1-2-5 sequence, 20 ranges. Sweep time, 0.2 μ sec - 0.5sec/DIV (within $\pm 3\%$); (with 10 \times MAG.), 20sec - 50msec/DIV (within $\pm 5\%$).

40 MHz KIKUSUI COS5041

\$1167.00

+ 20% Sales Tax
INCLUDING TWO PROBES
AND DUST COVER



(Vertical Axis), 1-2-5 sequence, 10 range: Sensitivity, 5mV/DIV - 5V/DIV, (within $\pm 3\%$); Frequency response, DC (AC 10Hz) - 40MHz (-3dB, 8DIV); Operation mode, CH1, CH2, DUAL, ADD, X-Y (DUAL automatic switching ALT and CHOP); (Horizontal Axis), (A: Main sweep, B: Delayed sweep); Sweep time, 1-2-5 sequence, A: 20 ranges B: 11 ranges; A: 0.2 μ sec - 0.5 sec/DIV (within $\pm 3\%$); B: 0.2 μ sec - 0.5 sec/DIV (within $\pm 3\%$); (with 10 \times MAG.), A: 20n sec - 50m sec/DIV (with $\pm 5\%$); B: 20n sec - 50m sec/DIV (with $\pm 5\%$).

ESCORT MULTIMETERS

EDM 1105

\$75.00

• 3 1/2 digits • Six functions: DCV, ACV, DCA, ACA, OHM, Diode Testing
• 0.8% basic DC accuracy

EDM 1116

\$100.00

• New model complete with transistor and capacitor tester

EDM 1125

\$108.00

• 3 1/2 digits • Seven functions: DCV, ACV, DCA, ACA, OHM, Diode Testing, Audible Continuity
• 0.25% basic DC accuracy

EDM 1135

\$140.00

• 3 1/2 digits • Eight functions: DCV, ACV, DCA, ACA, OHM, Diode Testing, Audible Continuity
• 0.1% basic DC accuracy

EDM 1346

\$225.00

• 4 1/2 digits • Eight functions: DCV, ACV, DCA, ACA, OHM, Audible Continuity Testing, Diode Testing, Data Hold
• 0.05% basic DC accuracy


All multimeters + 20% Sales Tax

GAG-808A AUDIO GENERATOR

\$203.00

Covers 10Hz to 1MHz

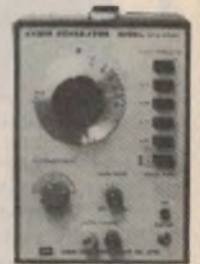• 20V p-p open circuit output • Sine and Square wave outputs • External sync • 600 ohm output impedance



ALL PRICES SHOWN DO NOT INCLUDE SALES TAX. ADD 20%

These are just a few of the many 100's of up-to-date Electronic items on display at:



DAVID REID ELECTRONICS LIMITED

127 York Street, Sydney, 2000
or Telephone (02) 267 1385

NICHOLSON ELECTRONICS

ELECTRONIC ENGINEERS

TRADE SERVICES

Philips Tuner ECL2060 Exchange or Repair	\$10.00
Other Varicap Tuners (Repair Only)	\$14.00
Philips Mini Turret Tuner (Repair Only)	\$12.00
I.F. Alignment Service Modules or TV	\$16.00

MODULES

Philips U Series (K9/K11) Repaired	\$16.00
Philips Power Supplies K9/K11 Repaired	\$32.00

AWA THORN

4KA Exchange Modules	
Power Scan	\$30.00
Small Signal	\$30.00
Vertical Module	\$20.00
Convergence Yoke	\$25.00
Convergence Handset	\$25.00

THORN 3504 EXCHANGE MODULES

Power Supply	\$30.00
Scan Module	\$30.00
I.F.	\$20.00
R.G.B.	\$20.00
Chroma	\$18.00
Vertical Sound	\$20.00
Convergence	\$20.00

HMV 212 MODULES (Repaired only at present)

S/M Power Supply	\$30.00
IF/SND	\$26.00
Horizontal Timebase	\$30.00
Luminance	\$20.00
Chroma	\$20.00
Vertical	\$20.00
Convergence	\$25.00

Custom Designed Test Equipment (1 week delay on all items).



TEST TUNER VHF/UHF—Isolated Output. Eliminates Tuner in any TV Internal Power Supply **\$58.00**

Line Output Switch Mode Power Supply Tester Analyst. Clips in place of Line Output Transistors or chopper. Reads Drive, BT, Shorts, Pulse, Width, without Destroying expensive Transistors. **\$60.00.**

High Voltage Regulated Supply. Variable to 120 Volts/1 AMP folds down when overloaded **\$120.**

Solid State Leakage Tester. Measures Leakage to 150 megohms Ideal for Testing Leakage in Transistor diodes Triacs Thyristors, etc. **\$46.00.**

Car Burglar Alarm. Includes Flashing Dashlight-Key Switch Door-boot and Bonnet Switches, 10 seconds delay on doors, Instant on Boot and Bonnet. Flashes Lights — Beeps Horn. **\$70.00.**

Other Test Equipment still being developed. Colour Bar Generator — Signal Strength meter-Sweet and marker Generator — UHF Down Converter. Enquiries welcome.

BU126 chopper Transistors **\$2.50** or **\$2.00** 10up. BC548 BC558 General Purpose **14c 5up, 12c 10up** 2N3055-60v 10A POWER **16c 5up, 14c 10up.**

3 MONTHS WARRANTY ON ALL WORK AND TEST EQUIPMENT

Prices do not include Freight Charges.

30 BRANDE STREET, BELMORE, SYDNEY, NSW 2192

(02) 759 8359

MAIL ORDERS WELCOME



PICTURE TUBE TESTER REJUVENATOR. Tests-Emission-Heater Cathode Shorts. Rejuvenate and removes cathode grid shorts. Includes 3 sockets and universal lead allowing almost any tube to be tested. **\$99.00**

SHORTED TURNS TESTER — Fits in toolcase. Includes 9v battery. Test for shorted turns in yokes L.O.P.Tx and other inductors. . . . **\$36.00**



ZENER DIODE TESTER — Direct readout of Zener voltages from 2v to 100v in two ranges. Internal power supply. **\$42.00**

VCR ALARM — Fits inside the VCR. Emits loud hee haw sound if the unit is lifted. Includes module — Mini Key switch. Ceramic transducer and 9v battery. **\$36.00**



The Serviceman

are, quite deliberately, not equal. The "through loss" is kept as low as possible, while the "side loss", which is also the isolation figure, is kept as high as possible. Typical values would range from 0.2dB through loss for 30dB isolation, to 1.5dB for 12dB isolation.

As can be seen, the two losses are related; the higher the side loss, or isolation, the lower the through loss. Where a large number of "T"s are used in a long run it is customary to use high side loss units at the beginning of the run, to minimise the through losses and to avoid possible overload of the sets, and progressively lower side loss units towards the end of the run.

Fairly obviously the side losses have to be allowed for by providing a high level signal on the through run, taking into account the worst case situation at the end of the run where the combined through losses, plus cable losses, can be significant. Supplying the necessary signal level is the function of the distribution amplifier and its selection depends on the signal level into it from the antenna, and the calculated losses along the line to the last TV set.

So much for the potted theory. Harking back to the 500 μ V signal into the 10dB amplifier it is obvious that, with a minimum isolation figure of 20dB at the first "T", the signal to the set is going to be 10dB down on the antenna level, or about 160 μ V — a hopelessly inadequate level. The results were exactly as one would expect; tons of snow and frequent colour drop-out, particularly at the end of the line.

I suspect that this technician had fallen into a common trap which seems to have thrown a lot of technicians. The amplifier he used is described as a "high power" unit, a possibly confusing term but one which is intended to mean that they are capable of delivering a distortion-free high level output — as high as 1.5V in some models — suitable for driving very large systems with potentially high losses. This voltage output would be given in the specifications.

The confusion appears to arise because some technicians assume that the amplifier will deliver this level automatically whereas, of course, it will only do so if the input level is high enough. In the example given (10dB or three times voltage gain) the amplifier would need over 300mV input to deliver 1V out.

Such signal levels could be encountered in favourable city or suburban locations and such an output might be desirable for a very large

installation; ie, several hundred outlets. Which is a far cry from the meagre 500 μ V available in this case. Looking at it another way, the person concerned appeared to be unable to differentiate between the unit's gain — perhaps because it is quoted in dB — and its maximum output level.

But this wasn't the only boo-boo this character had made. I subsequently retrieved this amplifier for use as part of the high gain amplifier system I had planned. In the process of pulling it out I removed the outlet plate in the first unit to make some checks and, while handling the connections, copped an almighty wallop.

A check with the meter revealed something like 120V of AC across the outlet, and a further check revealed that the three-pin plug on the amplifier power cord had been incorrectly wired. Don't ask me to go into detail; I was too shocked — in every sense of the word — to work out the exact mechanism by which I was able to measure 120V, a rather puzzling value in itself, across the outlet.

But it was one of those classic mixups of active, neutral and earth leads which so often prove fatal. Fairly obviously I was not in direct contact with the mains, but rather via some form of leakage path made possible by the wiring mixup. I simply reefed the wires out of the plug and re-wired it correctly.

The new system

This, then, was the set-up I encountered when I was given the go-ahead to rebuild the whole system, and I had to decide the best way to tackle it. I started out by assuming that I could get a 1mV signal using a suitable antenna in a practical location. This was a reasonable assumption, based on field strength measurements I had made during previous service calls, and was subsequently confirmed by more exact measurements.

Assuming this figure could be achieved, I made a few rough calculations and began to evolve a plan. The idea was to provide one distribution amplifier system having about 45dB gain — more about this in detail in a moment — and from this to split the signal into four legs, each leg supplying about one quarter of the total sets. More exactly, I planned to use two legs for the central block and one leg each for the western and southern blocks.

The actual amplifier system was to be made up from two amplifiers; a new 40dB unit and the 10dB unit originally used in the western block. The idea was

to connect the two amplifiers in line, with a small attenuator, about 5dB, between them. Not only did I not really need the full extra 10dB, but I had to consider that the two amplifiers connected directly together might prove unstable or that the output of one might overload the other.

Output from the amplifier would then go to a two-way splitter, the outputs of which would then each go to two more two-way splitters, giving four outputs in all. (Yes, a single four-way splitter would have done the same job, but I had a small surplus of two-way units on hand.) Allowing a theoretical loss of 3.5dB for each splitter, the total loss to each leg would be at least 7dB. For safety I added a couple of dB to my calculations.

On this basis each line would be running at +36dB over 1mV at its beginning. From this must be subtracted cable losses and the runs to the western and southern blocks would each involve about 100m of cable to the first "T". Good quality cable has a loss of about 2dB per 30m, at 200MHz, so each of these runs would involve about 6dB loss. Thus we would have a 30dB signal at the first "T" and would have to select suitable "T" values to ensure adequate signal at the last set.

A good compromise seemed to be a mixture of 26dB isolation (0.3dB through loss) and 20dB isolation (0.5dB through loss) "T" units. In addition to the through losses there will be cable losses between each "T" and these could run to 0.5dB each, or a total loss of up to 1dB per "T". A typical arrangement would be to use 26dB isolation units for the first five "T"s and 20dB units for the remainder. This would provide a +4dB level at the first set, falling to +1dB at the last set.

Well that's the kind of rough estimate needed to determine if the whole concept is at least in the ball park. Some of the figures used are estimates, but have been slanted on the conservative side. In any case, published loss figures for components, cables, etc, should always be treated with some reserve, while even minor components, such as plugs and sockets, introduce some loss.

Practical requirements

So much for the theory. The first practical requirement was to find a better place to house the distribution amplifiers, splitters, etc, where they would be protected from the weather and reasonably close to the antenna. The switch room for distribution of 240V power seemed to be an ideal spot and prompted me to make my first field strength readings in this area.

Fortunately, luck seemed to smile on me. At a convenient corner of the

The Serviceman

building, close by the switch room, I was able to score a little over 1mV from a reasonably high gain antenna. So I went ahead and installed this part of the system; the antenna, distribution amplifiers, splitters, etc, and confirmed that I had the calculated signal on all four outlets. (For obvious reasons I planned to do as much work as possible before disturbing the existing system, and then to cut over in sections, as convenient.)

The next problem was how best to run the cables. The original wiring in the central block had been alongside the outside walls, about half a metre above ground level. While a convenient level as far as the outlets were concerned, I was looking for some way to run them that would not only conceal them, but also protect them from the weather and physical damage.

On the other hand, getting into the roof would prove far too expensive so I had to find some other solution. Again I had a lucky break. The gutters were of fibro cement supported on the fascia board by metal hangers in the conventional way. However, at the back of the gutter the transition from vertical to horizontal was markedly rounded, while the metal hanger was a sharp angle.

The result was a large gap between the gutter and the bracket; quite large enough to take at least two cables. Granted, the job of feeding the cables through each hanger was a trifle tedious, but it made a first class job and was well worth the effort. I left a loop of cable at each intended "T" point, large enough to go under the fascia board and permit mounting the "T" on the back of the fascia, high up where it would be well protected from the weather.

But that was only part of the cable story. While the gutters solved the problem around the main block, I still had to get the cables to the southern and western blocks. The covered walkways provided the obvious path but, again, I was anxious to conceal and protect it as much as possible.

The walkway roofs were flat and of corrugated iron running lengthways. Both walkways had a slight natural slope and drainage was into an end gutter and, in one case, into a central box as well. The roofs were finished along each edge with rolled edge capping and I found it was fairly easy to remove the nails from the lower edge of this capping and then slip the cable up into the rolled section. It thus served as a very effective protective conduit and, although the job was a little tedious, the end result was well worthwhile.

Using these techniques I first ran two cables from the switch room along the southern side of the building to the corner, then along the western side. One of these was to serve the seven units on the western side, while the other was continued along the covered walkway to the western block, down the wall of this block under a convenient cover strip, and along the underside to serve the 10 units.

Then I ran two more cables along the southern side of the main block, in the opposite direction. One of these was then taken along the covered walkway, to serve the 10 units in the southern block. The other run was destined to serve the eight units on the southern side of the main block, the games room, seven units on the eastern side, the dining room, the office, and the manager's residence.

This was a long run, and certainly the most complex. It was plain sailing as far as the dining room but then, to get to the office and residence, it was necessary to go around the dining room, which would add some 60 metres to the cable path, or take a short cut across the roof.

This latter arrangement was what had been done before and there was a very strong temptation to do it again, provided I could find a way to get most of the cable out of the weather. In fact, I found a way. The manner in which the building had been constructed, at various stages, meant that the dining room roof had a valley in it between the end of the units and the beginning of the covered way to the office.

I was able to run the cable in the valley, then tuck it under the fibro sheets where they overhung the valley. This brought me to the pitched roof running the length of the northern side and the solution here was to remove the fibro ridge capping and lay the cable on top of the ridge pole. It was a tricky job in one sense because the fibro was old and brittle but, by carefully undoing the screws and exercising reasonable care, the whole job was completed without breaking one piece of fibro.

This brought me to the office and manager's residence and completed the main cable runs. At this stage I decided to concentrate on the western block which had been running on its own antenna, although it had been restricted to a few units ever since I had removed the amplifier. Fortunately, this was during a slack period.

Because the cable was to run under the floor, with only short runs up to the outlet plates, I elected to use what are called loop plates. These are actually a "T" network built on to an outlet plate and the cable is looped into the plate, hence the name. This means using more

cable and, if running down from a ceiling, may be unacceptable if losses must be kept to a minimum. In this case the extra length was negligible.

That much done I fired the system up and checked the field strength at each outlet. Everything worked out at least as well as I had expected with well over a millivolt of signal at all outlets. So that was one block up and running.

Next in line was the southern block. As I mentioned at the beginning this had already been re-wired some years ago and, apart from some tidying up, mainly involving worn or damaged outlet plates, was ready to go. And, once again, I finished up with well over 1mV of signal at all outlets. So that was two sections on line.

So now I was ready to tackle the central block, in many ways the biggest part of the exercise. But at this point the manager intervened. It appeared that he had just been advised by head office that the whole of the block was to be given a major refurbish; new electrical fittings, and wiring where necessary, new bathroom fittings, plumbing, etc, painting, new furniture — in short, a major overhaul from the shell up.

In the circumstances, the manager felt that it would be pointless for me to wire cable into the units with the risk that, at best, it might be damaged or, at worst, ripped out. All of which seemed perfectly logical and I was happy enough to suspend operations. According to the manager, it was anticipated that it would take about six months, by the time everything was organised and the work completed.

So it was agreed that he would contact me when the job was done.

Well, that's my friend's story so far. I'm afraid we will have to leave it there for this month, due to space limitations. (The Editor gets awful twitchy if my copy runs over its allotted length.) I'll continue the story, and in many ways the best part of it, next month.

TETIA Fault of the Month

National TC2631

Symptoms: North-south barrel distortion. East-west correction works perfectly but set has no adjustments for N-S correction.

Cause: Fault is caused by drift in pincushion correction circuit values. Adjust by reducing value of R456 (560 ohm 1 watt). This circuit is almost the same as the Korting 5507 which has an adjuster at this location.

This information is supplied by courtesy of the Tasmanian branch of The Electronic Technicians' Institute of Australia. Contributions should be sent to J. Lawler, 16 Adina St, Geilston Bay, 7015.

ALTRONICS COMPONENTS

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ Stereo Mixers at Low Import Price

ATTENTION—Social Clubs, Schools, Churches, Disco Operators, Entertainers, Hotels, Night Clubs and sporting Bodies. With Altronics low prices—here is your opportunity to install one of these outstanding sound control mixers. Both models include microphone "Soundover" facility—making either ideal for live entertainment use.

Stereo Audio Mixer



A 2550
\$125.00

240V Mains
Operated


This brilliant little mixing console is absolutely packed with features. Allows blending of Microphone, two Phono inputs and either two Tape or Turner inputs • Right and left VU meters • Separate Bass and Treble controls • 5 slide level controls • Fader control between Phono pickups for professional cueing • Headphone monitor switch • Talkover facility.

SPECIFICATIONS:

• Input Mic 0.5mV 600 Ohms Phono 3mV 50K Ohms Tape/Tuner 150mV 100K Ohms • Output 250mV • Frequency Response 20Hz to 20KHz (plus or minus 1db) • Tone Control (Treble) 10KHz (plus or minus 12db) • Tone Control (Bass) 100Hz (plus or minus 12db) • Distortion Less than 0.07% • S/N Ratio More than 60db • Headphone Impedance 4—6 Ohms • Dimensions 318 (L) x 217 (W) x 85 (H)

Pro-Quality Stereo Mixing Console

240V Mains
Operated

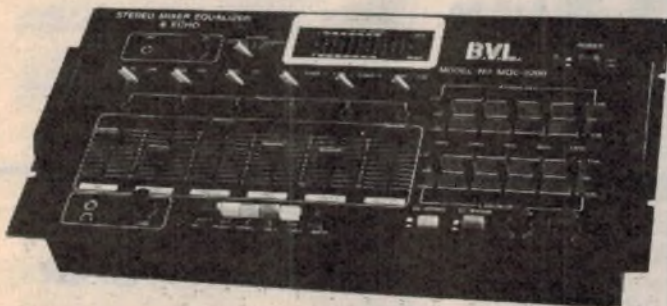

AMAZING VALUE

A 2570 \$399.00

Our sophisticated 'NEW' Audio Mixing Console is ideal for 'live' recording • PA mixing • Fantastic Tape recordings • Even Stereo/Mono VCR recording. A truly professional deck that features separate R/L 5 band graphic equalisers • Echo and Peak LED level indicators • Talkover facility • Separate H/Phone level control • Patch switch bank • Individual microphone, Phono 1 Phono 2, Aux/Line 1, Aux/Line 2, and Master slide level controls. — Blend up to two magnetic or crystal turntables, two tape decks or tuners and two microphones all at once!!

SPECIFICATIONS:

• Input Mic 1—0.5mV 600 Ohms Mic 2—0.5mV 600 Ohms Mic 2—0.5mV 600 Ohms (low imp.) 2.5mV 10K Ohms (low imp.) Phono 1 & 2 (Mag) 3mV 50K Ohms Phono 1 & 2 (Cry) 150mV 100K Ohms Tape/Tuner 1 & 2 150mV 100K Ohms • Equaliser 5 frequency bands—60Hz, 250Hz, 1KHz, 4KHz, 12KHz—Boost Cut range—plus or minus 12db @ Centre frequency. • Output 1.5V/0.775V (Selectable) • Frequency Response 20Hz to 20KHz plus or minus 1db • Distortion Less than 0.05% • S/N Ratio More than 50db • Headphone Impedance 4—16 Ohms • Echo B.B.D. System • Delay Time 30—200mS • Echo Repeat Control • Delay Time Control • Dimensions 480 (L) x 240 (W) x 110 (H)



Build These Great EA Projects

Save a bundle on the price you would otherwise pay for a commercial equivalent.

FREQUENCY COUNTER

Measures to 50MHz (to 500MHz with optional Prescaler).

Why Pay up to \$500 For Commercial Units?



UNBELIEVABLE 0.005% ACCURACY

• Frequency and Period measurement to 500MHz (with optional prescaler) • High Input sensitivity. Professional unit at a fraction of the cost of built up units. • IC sockets provided throughout • Low age rate 10,000MHz XTAL • Quality ABS plastic case with deluxe front panel • Specified LSI.

- K 2500 \$129.50
- K 2501 **PRESCALER** \$29.50
- K 2502 **DECIMAL POINT** \$9.50

FUNCTION GENERATOR

With Digital Display sine, triangle and square wave outputs 15Hz—250KHz.



K 2505 \$89.50

The most essential piece of test gear (second only to a good multimeter) on any hobbyist's bench is some kind of audio signal generator.

A truly versatile unit at a bargain price.

• 4 digit frequency readout (eliminates tiresome dial calibration) — typical accuracy +2% • 3 overlapping ranges x1, x10, x100 • 600 Ohm Nominal Output — continuously variable 3mV — 2.5V P-P • Distortion—sinewave: less than 0.7% @ 1KHz • Linearity—triangle wave: better than 1% • 1KHz • Squarewave rise time— 6V/uS maximum output • Amplitude stability— better than 0.1db on all ranges.

With the exception of the display all components mount on a single PCB making this kit suitable for all constructors.

DIGITAL CAPACITANCE METER

Measures 1 pf to 99.99 uf in 3 ranges



K 2521 \$59.00

This superb Test Instrument Kit now compliments our top selling Digital Frequency Counter and Function Generator Project Kit Electronics Australia Project. Measures capacitance of both polarized and non-polarized capacitors from 1 picofarad to 99.99 microfarads in 3 ranges. Check values of unmarked capacitors, especially those little trimmers that are never coded. Select precise values for filters and timing networks with ease.

EXCLUSIVE TO ALTRONICS

Each Kit includes precision measured capacitors for accurate calibration of each range.

FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007

FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007

ALTRONICS

COMPONENTS

★ **Quality Electronic Products at Import Prices.**

- ★ **Phone Your Order Toll Free 008 999 007**
- ★ **Next Day Delivery to Every Capital City and Suburbs**
24—48 Hours later to Country Areas
- ★ **Technical and Competent Staff for Helpful Advice.**

FOR NEXT DAY JETSERVICE DELIVERY

FOR NEXT DAY JETSERVICE DELIVERY

VINYL BINDER

Holds 12 magazines, each on a spring out wire rod. Just the shot for each year's set of Electronics Australia, ETI or any of your favourite magazine.

Suits all A4 size publications (275 x 210). Very smart Royal Blue colour with beautiful gold embossing.

B 9999.....\$5.50
THIS MONTH
\$5.00
4 or more \$4.50 ea.



UTILITY PARTS CASE

Featuring a clear plastic lid so you can tell contents at a glance. Simple slide lock, 48 partition combinations. Very sturdy ABS plastic. A must for the Technical, Handyman, Hobbyist, Collector.



H 0449
\$17.95

NEW

Metal Film Resistor Pack
150 Pcs
Computer Selected

R 3505 **\$5.95**



Other Pack Bargains
All computer selected values mix
All \$5.95 Per Pack

- R 3501 Carbon film resistors .25W PK 300
- R 3510 Greencap Capacitors PK 50 pcs
- R 3515 Ceramic Capacitors PK 100 pcs
- R 3520 PC Mount Electrolytics PK 40 pcs

MICROWAVE OVEN LEAK DETECTOR



Completely passive project receives microwaves via an antenna which develops a voltage across a detector diode driving the meter. Monitor your microwave oven with this easy to build kit. All components mount on single PCB including the meter.

K1724.....(still only) **\$14.50**

These Prices will rise by up to 30% with next shipment
(prices quoted are definitely for current stock only - phone now to reserve your order)

NICAD RECHARGEABLE BATTERIES

Premium Grade—good for up to 1000 recharges.
AA Size charge at 45-50MA
C Size charge at 160-180MA
AA Size 500 MAH
C Size 1.8 AH



S 5020	AA	1-9	10-99	100+
S 5022	C	2.45	2.00	1.80
		5.95	5.40	4.98

SEALED LEAD ACID

As used in security systems, battery backup for computers etc Premium grade long life (typically in excess of 5 years). Easy to charge.



S 5065	12V	1.2AH	ea.	5 Up
S 5067	12V	2.7AH	19.95	16.98
S 5069	12V	4.5AH	24.95	19.98
			34.95	26.95

16 WAY PARTS DRAWER SET

See through acrylic parts drawer. Slide-in Ident. card fronted drawers. Ident. cards supplied. Value Plus!



H 0440

\$19.50

4up

\$17.95

High Definition Computer Monitor

There are a number of low cost 'Hobbyist' monitors around these days at prices unheard of a year or so ago. However, they all suffer from poor to medium definition or resolution—hence eye strain becomes a real headache. The situation has all changed with the 1985 release of the superb Micron Series 3. Non glare, naturally, and screen character resolution well worthy of mating up with top end personal or professional computers.

NEW Micron Series 3




D 1115 Green Non Glare
\$179

• 1050 lines resolution at centre screen • 22MHz bandwidth • Video input impedance switch allows networking use • Incredible—repeat—Incredible—Resolution
SPECIFICATION:
Screen—Green phosphor Front Controls—Power on/off, character brightness/intensity, display centering Rear controls—Background intensity, vertical and horizontal adjustment etc. Input Impedance—Switch 75/10K
Bandwidth—10Hz-22MHz Resolution—1050 lines minimum at centre screen

PANBRAKE SHEET METAL BENDER

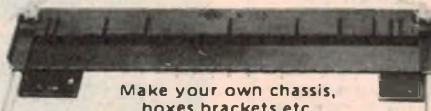Our Panbrake Sheetmetal bender continues to be one of our most popular tools. Just the shot for making up heatsinks, brackets, chassis etc.



Make your own chassis, boxes brackets etc.
Unique slotted upper clamping bar allows complex corner bends etc.

Handles up to 16 gauge metal and up to 445mm wide.

T 2400 Direct import price! **\$89.95**

IMPORT SCOOP

Quality Commonwealth Computer Fan 80MM - 240V

★ Super quiet ★ Sealed sleeve bearings for long life ★ Sturdy die cast frame ★ Operating range—10 deg C to + 70 C



SUPERB QUALITY SLIMLINE GRAPHIC EQUALISER / AMPLIFIER



Incredibly compact 22H x 145W x 132D. 7 Key 30W / 30W Led Level meters/Qual. Japan Marf. Freq. Response 20HZ-30KHZ... C 9132

ONLY \$55

CAT F 1020

\$12

4 or More

\$11

Amazing Value

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007

And 1985's Top Project



BENCH TOP POWER SUPPLY

3—30V to 1 amp Max. with variable current limit.



Electronics Australia have released this superb new supply kit in our very attractive H 0480 instrument case—thus complementing the Frequency Counter, Function Generator projects etc.

FEATURES:

- * Output variable between 3 and 30V
- * Short circuit Protection
- * Full 1 Amp output over entire voltage range
- * Load switching
- * Current limiting fully variable—twin selectable ranges. * Dual Scale Meter
- * Separate earth terminal provided
- * Housed in our Deluxe "ABS" Instrument case

SPECIFICATIONS:

- * Output Voltage — 3 to 30 Volts
- * Output Current — 0 to 1 Amp (fully variable)
- * Load Regulation — Better than 0.2% from 0 to full load
- * Output Ripple — Less than 2mV RMS

Fantastic Value

K 3210 \$55.00

EA'S LABORATORY POWER SUPPLY

3—50 Volt at up to 5 Amps


Single Printed Circuit Board construction - dead easy to build.

EXCLUSIVE TO ALTRONICS:

- * Deluxe instrument case.
- * Attractive silk screened front panel.
- * Fully drilled and punched chassis - no holes to drill.
- * Front panel supplied to accommodate K 3325 option if required.
- * Heatsink tubing supplied for critical component termination.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

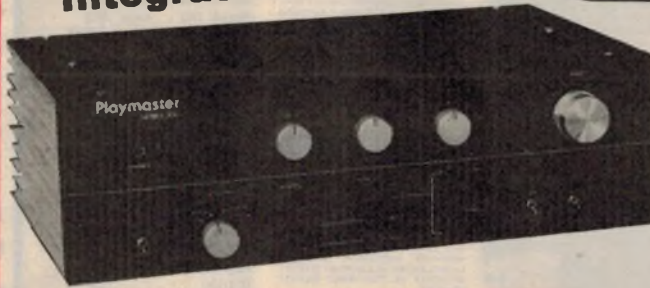Build this Fantastic New Kit NO COMPROMISE DESIGN Ultra Fidelity Series 200 Mosfet Integrated Amplifier



K 5030
complete kit

\$399

Incredible Value

WARNING Readers Please Note

This excellent design specifies a number of important components which cannot be substituted without affecting overall performance. The Altronics Kit is based 100% on the Electronics Australia Design. Beware of Kits offered by suppliers who do not conform to EA's Design.

No Audiophile will now dispute that the top end High Fidelity Amplifiers are all Mosfet design. The reasons Mosfet output transistors deserve such acclaim are many and various—like incredibly fast response time (therefore even the most complex violin note will be reproduced with purity and realism that borders on "perfection") and of course with Mosfets thermal runaway is a thing of the past. Another handy characteristic of Mosfets is "self shutdown" when grossly over driven insufficiently heatsunk etc. So Leo Simpson and the Team set out many moons ago to create the ultimate in a fully integrated stereo amplifier

ENGINEERING CONCEPT

The original October 1984 release date came and went with no end in sight as to the mechanical format of the Amplifier. The initial bench tests were so outstanding it soon dawned on the EA Team that there would be potentially 10's of 1000's of Hi Fi buffs dying to get their clutches on such an amp especially at the surprisingly low cost of the "Bits" or projected Kit set cost. However, as most of these potential owners would be relatively "Green" at Electronics construction—the EA Engineers have placed virtually all the components on a single (rather large) printed circuit board i.e. anyone with a reasonable "beginners" comprehension, and prepared to carefully study the instructions, should have little difficulty in building this project. Naturally for experienced Electronics enthusiasts—the task will be straightforward.

The end result borders on perfection and will last you a lifetime.

FEATURES:

This brilliantly designed stereo amplifier will equal or better just about any integrated commercial amp regardless of price. It is a no-compromise design capable of delivering 100 watts per channel at very low distortion. Four basic stereo inputs are provided for both moving magnet and moving coil cartridges. Also three high level stereo inputs are provided for compact disc players, AM/FM tuner and auxiliary input which could be from a stereo TV tuner or Hi Fi VCR. Input facilities are also provided for two stereo cassette decks and full monitoring facilities are available for either deck plus dubbing from Deck 1 to Deck 2 or vice versa.

- Full CMOS Analog switching (soft touch)
- Twist Type speaker lead binding posts supplied.
- De-thump muting In-built.
- All Hi-Spec low noise IC's used.
- Incredibly accurate RIAA equalisation.
- No control wiring whatsoever.
- Led indication of switch status (On/Off)
- All components mount on the PCB, even pots and sockets.
- Super efficient Toroidal Transformer—Low Hum.
- Uses Hitachi Mosfet Power devices.
- In-built over drive protection.
- Centre detents on Bass, Treble and Balance controls; multiple detents on volume control.
- Heavy Duty Heatsinks.

SPECIFICATIONS:

Power Output: 100W RMS into 8 Ohms (per channel)
 Freq. Response: 8Hz to 20KHz +0 -0.3db
 2.8Hz to 65KHz +0 -1db
 Input Sensitivity: 0.775mV for full power

Hum: -100db below full output
 S/N Ratio: 94db flat -100db A-weighted
 Distortion: 0.01% @ 1KHz
 Stability: Unconditional

GO ANYWHERE 12—240V POWER

This great inverter kit enables you to power 240V AC appliances from a 12V DC power source. Tremendous for camping, fishing etc. Install into your car, Boat or Caravan.

300 WATT INVERTER

K 6750 \$199.50

\$10 DELIVERY AUSTRALIA WIDE

A fully regulated and overload protected design, featuring XTAL locked frequency use to power HiFi, TV sets, even electric drills for short time periods.

MANY OF THESE KITS ARE NOW IN USE FOR EMERGENCY LIGHTING PURPOSES.

ALTRONICS KIT FEATURES:

- * Plated edge connector and PCB buss
- * Low age rate XTAL
- * Sockets for all IC's
- * High Efficiency Transformer
- * Pre punched and screen printed chassis
- * High current switching relay supplied



(EA June '82)



K 3300 \$139.50

SPECIFICATIONS:

- * Output Voltage = 3-50 volts
- * Output current up to 5 amps (max. 175W)
- * Floating outputs isolated from ground.
- * Ripple less than 90mV p p at Max.

Auxiliary + /-12V Option

K 3302 \$12.50

BANKCARD HOLDER—PHONE ALTRONICS TOLL FREE 008 • 999 • 007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007 FOR NEXT DAY JETSERVICE DELIVERY

FOR NEXT DAY JETSERVICE DELIVERY

FOR NEXT DAY JETSERVICE DELIVERY

SEMICONDUCTOR DATA BOOKS

MOTOROLA SEMICONDUCTOR

MOTOROLA CMOS DATA

A comprehensive reference covering 4024 CMOS ICs, along with specially devices such as LCD drivers, telephone and general communication ICs, and industrial control 882 pages. Essential in all spheres of electronics.

B 1105 \$12.95

SCHOTTKY TTL DATA

Essential reference for the enthusiast and engineer alike. Designing, building and servicing digital circuitry is an absorbing pastime. Data for the LS, ALS and FAST families along with design considerations and circuit characteristics are logically presented in this manual, making it quick and easy to use.

B 1100 \$11.95

MOTOROLA MEMORY DATA

An absolute must for the microprocessor buff! This is the latest reprint of Motorola's famous memory data manual and includes the latest specifications and design application data on TTL, RAM, TTL PROM, MECL, MOS, MOS DYNAMIC RAM, MOS STATIC RAM, MOS EPROM, MOS EEPROM, and MOS ROM. Worth many dollars more.

B 1113 \$11.95

LINEAR & INTERFACE DATA

Popular data manual. At last readily available. Includes a data design procedure and equivalent listings for 1000's of devices under headings OF AMPS, VOLTAGE REGULATORS, CONSUMER CIRCUITS (e.g. TV automotive power), HIGH FREQUENCY CIRCUITS, and SPECIAL PURPOSE CIRCUITS. Gives data, design procedures and equivalent listings for MEMORY MICROPROCESSOR SUPPORT LINE DRIVERS/RECEIVERS, TELEPHONE COMPARATORS, VOLTAGE REFERENCE AND DATA CONVERSION DEVICES. Includes comprehensive selector guide.

B 1114 \$22.95

MOTOROLA MECL DATA

Emitter Collector Logic (ECL) is today's latest form of digital logic providing the most direct way of improving system performance. This previously hard to get manual provides data on the 10KH, 10K and 10L families, MECL memory and PLL CHIPS.

B 1100 \$11.95

MOTOROLA POWER DATA

Motorola are the undisputed world leader in power transistors. Renowned for their low cost and reliability. Book includes a 9 page selection guide, application notes and data sheets for over 700 devices. 388 pages.

B 1101 \$19.95

MOTOROLA MASTER SELECTION GUIDE

The most useful book ever printed. Covers MOS ICs listed by function. LINEAR ICs listed by function. INTERFACE ICs listed by function. LSJ memory, TTL ICs, power products, SCR's diodes, transistors listed by application and ratings. RF, small signal and op-amp devices listed by application and ratings. Essential data given for all devices. Terrific value.

B 1104 \$7.95

MOTOROLA OPTO DATA

Handy reference provides data and application notes on opto couplers, infrared LEDs, photo transistors and a complete chapter on fibre optics, a communications system which is fast gaining usage world wide. Very Educational.

B 1118 \$11.95

MOTOROLA 8-BIT MICROPROCESSORS AND PERIPHERALS

This manual covers all aspects of Motorola's microprocessor microcomputer and peripheral components. A clearly written manual providing all the data necessary to design and build a working computer system from scratch. 100's of circuit examples, flow charts, truth tables and programme routines.

B 1125 \$16.95



NATIONAL SEMICONDUCTOR

INTERFACE

This data book provides complete specifications for a variety of transmission line drivers/receivers, peripheral power drivers and level translators/buffers. Product selection guides list applications information and operating features. Memory dynamic memory microprocessor, data communications and disk support products are also covered in the data book. The interface appendix section contains cross reference guides, the programmable logic section describes the technology, design and gives application suggestions.

Pages: 1520 Year: 1983

B 1005 \$13.50

5 Up \$12.00

DATA CONVERSION ACQUISITION DATABASE

The 1984 edition of the Data Conversion/Acquisition Database is one of the most comprehensive in the industry. It contains specifications for high technology conversion products in the analog signal path both preceding and following the conversion process. Combining high volume production capability with leading edge technology such as thin film resistors, laser trimming and advanced micro CMOS and bipolar processing, has helped develop products best suited to your design needs.

Pages: 1232 Year: 1984

B 1007 \$13.50

5 Up \$12.00

LINEAR DATABASE

The 1982 edition of the National Semiconductor Linear Database is the only comprehensive reference available. It presents approximately 2000 pages of specifications for our high-technology linear products. Applications, descriptions, features and diagrams in this database include detailed sections for Voltage Regulators, Op Amps, Voltage Comparators, A to D, D to A Converters, Industrial Blocks and Audio and TV Circuits. The database also features advanced telecommunication devices and speech synthesis (DIGITAL TALKER) plus other non-state-of-the-art linear products offering performance, economy, quality and reliability.

Pages: 1952 Year: 1982

B 1010 \$15.00

5 Up \$14.00

LINEAR SUPPLEMENT

The 1984 Linear supplement provides the most recent information on National's new linear products. This supplement also provides a comprehensive index published in the Master Database. New products designed are indicated by an Asterisk and in bold type. Revised data sheets are listed in both National's supplement database system allows you to make product selections of their latest product offerings.

Pages: 566 Year: 1984

B 1011 \$7.50

5 Up \$6.50

LOGIC DATABASE

National's new Logic Database covers five of the most popular TTL (54/74) Schottky (54S/74S), low power (54H/74H) and low power (54L/74L). The Logic Database is especially organized for quick and easy referencing - offers two complete functional indices and selection guides for one SSI and one MSI devices. In addition, it includes over 100 connection diagrams and test waveforms to help speed the design cycle. All in all it's probably the most comprehensive collection of practical information ever assembled on such a broad line of practical components.

Pages: 550 Year: 1981

B 1015 \$11.00

5 Up \$10.00

MOS MEMORY DATABASE

The 1984 MOS Memory Database is a comprehensive collection of information on advanced, high-density memory products covering the spectrum of this mainstream semiconductor component category. National Semiconductor has an array of advanced technology processes for applying memory design and development. These range from high-density tripoly process used in the most advanced RAMs, the small-geometry silicon gate, oxide-isolated micro-CMOS technology which is now being applied to high-performance memory devices for the first time.

Pages: 256 Year: 1984

B 1025 \$7.50

5 Up \$6.50

HYBRID PRODUCTS DATABASE

The Hybrid Products Database is the only National Semiconductor publication that contains complete information on all our hybrid semiconductor products. Included are precision thin film and thick film products which provide the user with standard functions from operational amplifiers to converters with capabilities beyond those of current monolithic technology. Product selection guides and an application section are also included.

Pages: 792 Year: 1982

B 1045 \$9.95

5 Up \$9.25

TRANSISTOR DATABASE

National Semiconductor has added many new transistors and product families since publication of the last database. Many have already been widely acclaimed by users. In addition to small-signal, power, bipolar and field effect transistors that have been the mainstay of our catalog, there is a section for multiple-field-effect transistors. More part numbers will be added as market needs dictate. To keep current on all new National transistors, please contact your National sales representative or franchised distributor and ask to be placed on the customer mailing list.

Pages: 558 Year: 1982

B 1050 \$9.95

5 Up \$9.25

CMOS DATABASE - 1984

The CMOS Database contains the industry's most comprehensive collection of high-performance CMOS products available. Our early commitment to micro-CMOS technology has made possible the development of a broad spectrum of advanced devices that will simplify your design and assure state-of-the-art systems. Micro CMOS technology describes National's array of small-geometry, silicon gate, oxide-isolated processes used to build the product in this book. Using N- or P-well substrates and multiple-layer metal or polysilicon-interconnect structures, micro-CMOS processes feature sizes of 3.0, 2.0 or 1.5 microns, with submicron feature sizes in development.

Pages: 1520 Year: 1984

B 1030 \$13.50

5 Up \$12.00

VOLTAGE REGULATOR HANDBOOK

With the variety of fixed and variable regulator technology currently available, the 336 page Voltage Regulator Handbook becomes a must for the selection of three terminal and dual tracking components that meet the system requirement while utilizing the most cost effective approach. Beginning with product selection procedure and a data sheet summary, the text continues with easily accessible information about booster, precision power transformer and filter specifications, test methods, manufacturers' cross reference, and extended use applications for National's regulators.

Pages: 336 Year: 1982

B 1055 \$9.95

5 Up \$9.25

STATE OF THE ART TOROID POWER TRANSFORMERS

For the same price as your common garden heavy, bulky, buzzing laminated iron (any old iron at that!) transformer you can now design in a superb Toroid Power Transformer from Altronics.

4 MODELS TO CHOOSE FROM ALL WITH 240V PRIMARY



NEW FOR 85'

Why a Toroid?

- Smaller size and weight to meet modern "Slimline" requirements.
- Low electrically induced noise demanded by compact equipment.
- High efficiency enabling conservative rating whilst maintaining size advantages.
- Lower operating temperature.
- Simple, quick single bolt mounting.

CAT.No.	SEC V	VA	PARL SEC	SER SEC	I	EA	10UP
M 3050	12V + 12V	160	13.2A	6.6A	45.00	43.50	
M 3060	25V + 25V	160	6.4A	3.2A	45.00	43.50	
M 3070	35V + 35V	160	4.6A	2.3A	45.00	43.50	
M 3100	40V + 40V	300	7.5A	3.75A	55.00	52.50	

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroids offer in size, weight, lower radiated field and, thanks to Altronics - Low Price.

DIMENSIONS

Diameter 110mm
Height 42mm (160VA Models)
42mm (300VA Models)
Leads 200mm length

Made in UK Quality

Highly Recommended For:

- Audio Amplifiers • Power Supplies
- Microprocessor/computer equipment

MANUFACTURERS AND BULK USERS PLEASE CONTACT OUR WHOLESALE DEPT. FOR BULK QUANTITY RATES.

MOTOROLA BONUS OFFER

SET OF 9 TITLES

B 9995 \$99.00

SAVE \$30

NATIONAL SEMI BONUS OFFER


SET OF 10 TITLES

B 9996 \$89.00

SAVE \$22

Home Telephone Extension Cords and Adaptors

PRICES RISE 25% NEXT MONTH

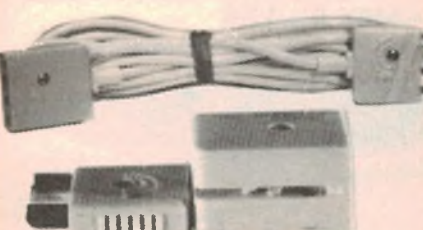

Now you can have your Telephone in the backyard or just on the other side of the lounge room with these nifty telephone leads. Double Adaptor allow two phones into the one line. Ideal for cordless phones etc.

P 0990 5 Metre extn. lead \$14.95

P 0992 10 Metre extn. lead \$17.50

P 0995 Phone Dble Adpt. \$12.50

NEW ALTRONICS PRODUCT

LOW COST MULTIPURPOSE POWER TRANSFORMER

240V to 9, 12, 15, 18, 21, 24 volts at 60VA (60W) High grade silicon steel laminations (Sorry we could not do a Toroid at this price).

Our Multitap 1 amp and 2 amp Transformers have proved so popular we decided to release a big brother. Made right here in Australia. Use of high grade Silicon steel has enabled surprisingly compact dimensions (70mm x 70mm x 58mm High)

Outputs Two Simple Secondaries, each with just one tap, permit an amazing range of outputs i.e.

Voltage	Current	Centre Tap
3	6.6A	No
6	6.6A	Yes
9	6.6A	No
12	5A	No
15	4A	No
18	3.3A	Yes
21	2.9A	No
24	2.5A	Yes

And the best new is the Low Price - Just \$22.50 Cat. M 2165

An exclusive Altronics Design Why didn't we think of it years ago!!

BANKCARD HOLDERS - PHONE ALTRONICS TOLL FREE 008 • 999 • 007

BANKCARD HOLDERS - PHONE ALTRONICS TOLL FREE 008 • 999 • 007

STATE OF THE ART

The Avtek MultiModem

a breakthrough in low cost modem design Using state-of-the-art VLSI integrated circuitry, the Avtek MultiModem provides the highest standards of reliability for data communications on public phone lines. Digital signal processing is used to achieve functions normally requiring analogue filters.



MULTIMODEM NEVER REQUIRES ADJUSTMENT

MULTIMODEM WORKS RELIABLY ON LINES WHERE OTHER MODEMS CAN'T FUNCTION Its digital filters are much sharper than on conventional modems. Line interference is screened out. You get error free data transfer, even on very noisy lines.

MULTISTANDARD OPERATION CCITT and Bell Duplex and Half Duplex
AUTO ANSWER OPTION (MODEL D 1205) Autoanswer is the ability of your computer/modem to receive when the phone rings. Some computer/software combinations do this. MultiModem offers the alternative for computers without this facility—hardware autoanswer. Leave your computer waiting for information.

TEST FUNCTIONS

DIG: This function enables the user to test the modem's operation over a line, testing both modem and line
ANL: Provides testing of computer, software, cabling and modem.

SPECIFICATIONS

Data
Standards: CCITT V.21 & V.23 Bell 103 & 22
Data Rates: 300, 600 & 1200 BPS
Backward Channel: 75 BPS in conjunction with 1200 BPS
Computer Interface: CCITT V.24 (RS232C)
Power Requirements: 240 VAC Power drain—3 watts

TWO MODELS
D 1200 (Standard) **\$349.00**
D 1205 with auto answer **\$389.00**

BLOOD PRESSURE & HEART RATE MONITOR
Why Risk Unnecessary Heart Attack?

A simple (take the reading yourself) periodic check of your blood pressure and pulse provides an "inward look" into a vital aspect of your bodily health. Heart disease strikes down many people in their early 40's (or even 30's). The tragedy remains that had such victims been alerted, remedial medical, physical and dietary action could have been prescribed to avoid illness and in many cases restore full bodily health.



A Superb Gift for the dedicated fitness enthusiast **Absolutely essential** for those over 40 and concerned with their health, or on Fitness Therapy. Use this **easy to operate** Monitor to measure your pulse (or heart rate) and Blood Pressure.


DON'T PAY \$150
X 3055

Now Only \$89

Remember high blood pressure is in itself symptomless and the usual forerunner to future chronic heart disease. **Features** include "error" display warning of incorrect use. Handbook supplied will enable anyone in your family to be fully conversant with this monitor in minutes. Easy to read display of Systolic and Diastolic Blood Pressure and Pulse Rate.

PROFESSIONAL SERIES RACK CABINETS

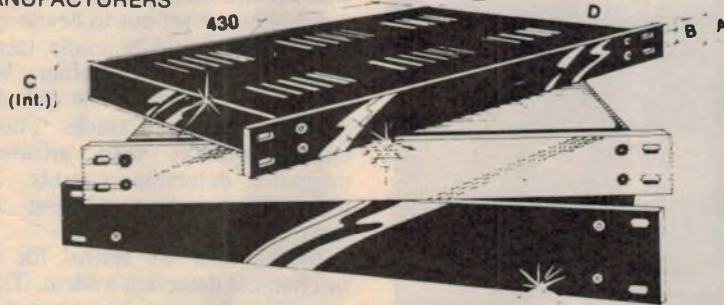NOW YOUR PREAMPS, AMPS, CONTROL MODULES MONITOR PANELS ETC. CAN LOOK EVERY BIT AS GOOD AS TECHNICS, NAKAMICHI AND OTHER TOP MANUFACTURERS



FEATURES:—• These beautifully crafted rack cabinet boxes will give your equipment a real 1st class appearance • Aluminium construction with removable top and bottom steel cover panels • All dimensioning conforms to the International Standard • Natural or Black finish • Ventilated lid • Deluxe finish front panel • Individually cartoned • Supplied in Flat Pack Form—Easily assembled in minutes—**Side Elevations:**—• D= 254mm C (Internal Chassis Height) • B (Mounting Bolt Centres).

SIX NATURAL AND BLACK FINISH MODELS

The Black or Natural finish cabinets are each available in 44mm, 88mm or 132mm high models. Mounting hole centres conform exactly to international Racking Specifications both vertically and horizontally.

Cat. No.	Finish	A	B	C	ea.	5+
H 0401	Natural	44	34	38	\$49.50	\$47.50
H 0402	Natural	88	57	82	\$59.50	\$56.00
H 0403	Natural	132	89	126	\$64.75	\$61.50
H 0411	Black	44	34	38	\$49.50	\$47.50
H 0412	Black	88	57	82	\$59.50	\$56.00
H 0413	Black	132	89	126	\$64.75	\$61.50

ALTRONICS COMPONENTS

105 STIRLING STREET, PERTH
FOR INSTANT SERVICE
PHONE ORDER TOLL FREE
008 999 007
PERTH METRO AND A/HRS
ORDERING SERVICE
(09) 328 1599

ALL MAIL ORDERS
Box 8280, Stirling St Perth WA 6000

PACKING AND DELIVERY CHARGE \$3.00 DELIVERY AUSTRALIA WIDE -We process your order the day received and despatch via Australia Post. Allow approx. 7 days from day you post order to when you receive goods. Weight limited 10Kgs.

\$5.00 OVERNIGHT JETSERVICE - We process your order the day received and despatch via overnight jetservice Courier for delivery next day. Country areas please allow additional 24-48 hours. Weight limit 3Kgs.

\$10.00 HEAVY HEAVY SERVICE - All orders of 10kgs, or more must travel Express Road - Please allow 7 days for delivery.

INSURANCE — As with virtually every other Australian supplier, we send goods at consignees risk. Should you require comprehensive insurance cover against loss or damage please add 1% to order value (minimum charge \$1) When phone ordering please request "insurance".

TOLL FREE PHONE ORDER - Bankcard Holders can phone order toll free up to 6pm Eastern Standard Time. Remember with our **Overnight Jetservice** we deliver next day.

ALTRONICS RESELLERS
Wanted in all Areas of Australia—Phone Steve Wroblewski on (09) 381 7233 for Details

NSW	QUEENSLAND	VICTORIA
CITY David Reid Electronics ... 267 1385 Jaycar ... 267 1614	CITY Desound P/L ... 2296155 Jaycar ... 393 0777	CITY Active ... 602 3498 All Electronic Components ... 662 3508 MaGraths Electronics ... 347 1122
SUBURBAN CARLINGFORD Jaycar ... 872 4444	FORTITUDE VALLEY McGraths Electronics ... 832 3944 St Lucia Electronics ... 523547	SUBURBAN BENTLEIGH Absolute Electronics ... 557 3971
CONCORD Jaycar ... 745 3077	PADDINGTON Jacques Electronics ... 369 8594	BOX HILL SOUTH Eastern Communications 288 3107
GORE HILL Jaycar ... 439 4799	SALISBURY Coloursure Wholesale 2753188	CHELTENHAM Tatung Electronics ... 550 2386
HURSTVILLE Jaycar ... 570 7000	SLACKS CREEK David Hall Electronics ... 2088808	DONCASTER Chipstone Electronics ... 84 2868
LEWISHAM PrePac Electronics ... 569 9770	TOOWONG ECO Technics ... 3710879	FOOTSCRAY Acron Electronics ... 689 1911
ORCONTRY Webb's Electronics ... 25 4066	COUNTRY CAIRNS Thompson Instrument Services ... 512404	SOUTH CROYDON Truscott Electronics ... 723 3660
BATHURST The Electronics Shop ... 31 4421	BUNDABERG PM Electronics ... 728 272	COUNTRY BENDIGO K.C. Johnson ... 41 1411
BROKEN HILL Crystal TV ... 4803	GLADSTONE Purley Electronics 724321	MORWELL The Electronic Centre ... 34 6133
COFFS HARBOUR Coils Harbour Electronics ... 52 5684	NAMBOUR Nambour Electronics ... 411604	ROBINVALE John Mason Electronics ... 26 3643
GOSFORD Tomorrows Electronics ... 24 7246	PALM BEACH The Electronic Centre ... 341248	SHEPPARTON GV Electronics 21 8866
KURRI KURRI Kurri Electronics 37 2141	ROCKHAMPTON Centre Purley Electronics 21058	
NEWCASTLE D.G.E. Systems ... 69 1625	TOOWOOMBA Hunts Electronics 329877	
GEORGE BROWN & COMPANY ... 69 6399	TOWNSVILLE Solax ... 722015	
NOWRA Southern Communications 21 4011		
ORANGE MW Electronics 626 491		
PORT MACQUARIE Hall of Electronics ... 83 7440	SA CITY Force Electronic 212 2672 Protronics ... 2123111 Garra & Goodman 223222	WA COUNTRY ALBANY BP Electronics ... 41 2681 ESPERANCE Esperance Communications 71 3344
RAYMOND TERRACE Albatac Electronics ... 87 3419	SUBURBAN BRIGHTON Vector Electronics ... 78 4277	GERALDTON K.B. Electronics & Marine ... 21 2176
RICHMOND Landlink Communications 65 4622	CHRISTIES BEACH Force Electronics ... 382 3366	KALGOORLIE Today's Electronics ... 21 2777
TENTERFIELD Nathan Ross ... 36 2204	PROSPECT Electronics ... 269 4744	MANDURAH Kenronics ... 35 3227
TOKLEY TES Electronics ... 96 4144	REYNELLA Force Electronics ... 381 2824	WYALKATCHEM D & J Pease ... 81 1132
WINDANG Madjenk Electronics ... 96 5066	COUNTRY MT GAMBIER South East Electronics ... 250 034	
WINDSOR M & E Electronics Communications 77 5935	PT LINCOLN West Coast Elect Supplies ... 82 5802	
WOLLONGONG Nereta Electronics ... 27 1620	WHYALLA Eye Electronics ... 46 4764	
WYALLA Eye Electronics ... 28 4400	TASMANIA HOBART D & I Agencies ... 34 7877 George Harvey ... 342233	NT DARWIN Ventronics ... 81 3491 ALICE SPRINGS Accom Electronics ... 52 1713 Farmer Electronics ... 52 2967
	ACT CITY Electronic Components ... 80 4654 Scientronics ... 54 8334	
	LAUNGESTON George Harvey ... 31 6533	
	LEGANA Frans Beech Electronics ... 301379	

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007 FOR NEXT DAY JETSERVICE DELIVERY

BANKCARD HOLDERS—PHONE ALTRONICS TOLL FREE 008 • 999 • 007 FOR NEXT DAY JETSERVICE DELIVERY

Pit yourself against the clock!

Timer/lap counter for slot cars

Slot car enthusiasts know that electronic timing equipment adds considerably to the atmosphere of a "meet". With commercial timing gear expensive and scarce, we decided that there was a definite need for a "do-it-yourself" project. So here it is — the EA Slot Car Timer and Lap Counter.

by COLIN DAWSON

The completed project has every desirable feature: drag race style "Christmas tree" starting lights, a presettable lap counter (it counts down from the preset to zero) and, of course, an electronic stopwatch with .01s accuracy.

The Christmas tree lights consist of six LEDs in a column. When a start is initiated, the lights count down from the top with one LED at a time illuminated. When the bottom LED is illuminated, the competitor is free to start and the

stopwatch begins timing. Should the competitor jump the start, the LEDs will stop counting down. A new start can only be initiated by resetting the circuit.

As with most forms of racing, the stopwatch is started simultaneously with the start signal, not when the competitor actually starts. Obviously, fast reflexes in starting are an advantage.

Each time the car crosses the start/finish line, the stopwatch display is frozen for about half of a second so that the progressive time can be read. When

timing resumes, the total time including the 0.5s delay is included. The timer stops when the lap count is "00".

The lap counter can be preset to any number from one to 99. After resetting, the preset number is indicated. This decrements every time the car completes a lap.

To keep costs within reasonable bounds and simplify the construction, we have adapted a hand-held electronic stopwatch to take care of the timing. This can be used as a control unit and is linked to the main circuit by a 7-way rainbow cable. Resetting, as well as manual start/stop, can be performed by the stopwatch. In this case, only the start LEDs and lap counter display would need to be mounted in view of the competitors.

The basic circuit described here can monitor one track but, by duplicating the circuit, another track can be monitored. Only a single connection between boards need be made to synchronise them.


By far the most time consuming part of the design was the detection circuitry, although this would not be immediately apparent from the circuit diagram. The pick-up, after all, is a simple track mounted contact. Unfortunately, this was not the first scheme we tried.


Initially, we set out to devise a pickup system that could be easily transferred from one track to another. We also wanted it to be compatible with different makes and sizes of tracks. This led to experimentation with infrared and magnetic detection circuits. Unfortunately, neither system proved sufficiently reliable.

In the end, we settled for a semi-mechanical detection system. The input circuitry relies on the brushes of the car shorting a wire contact to the positive rail of the track. For our prototype, only about 3mm of the wire is exposed. This protrudes through the joint between track segments and is isolated from the positive rail with insulation tape.

To date, this scheme has proven to be completely reliable. In view of its simplicity and ease of installation, we don't think the lack of portability is a serious limitation.

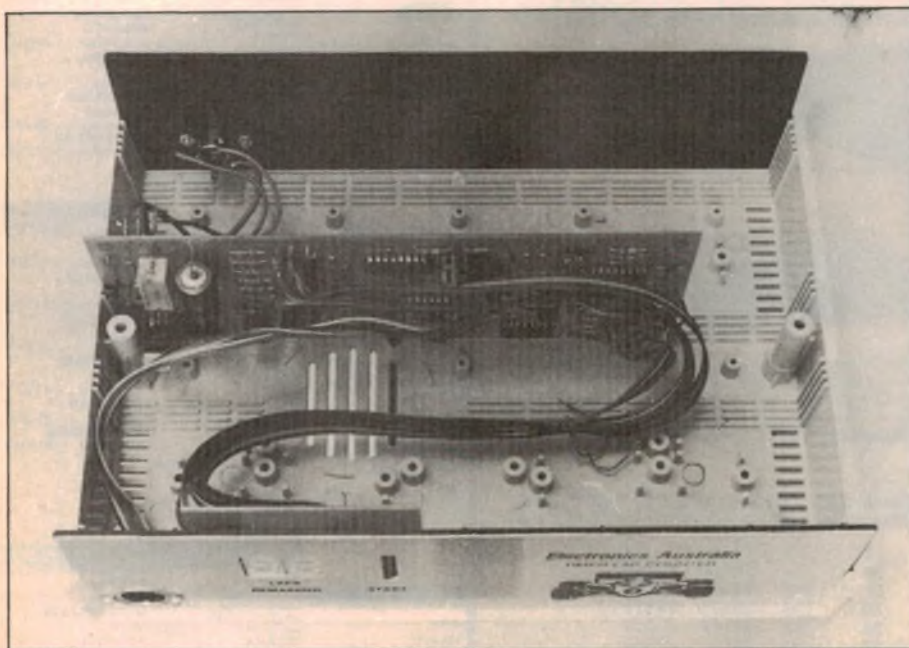This view inside the prototype shows an early version of the PCB.



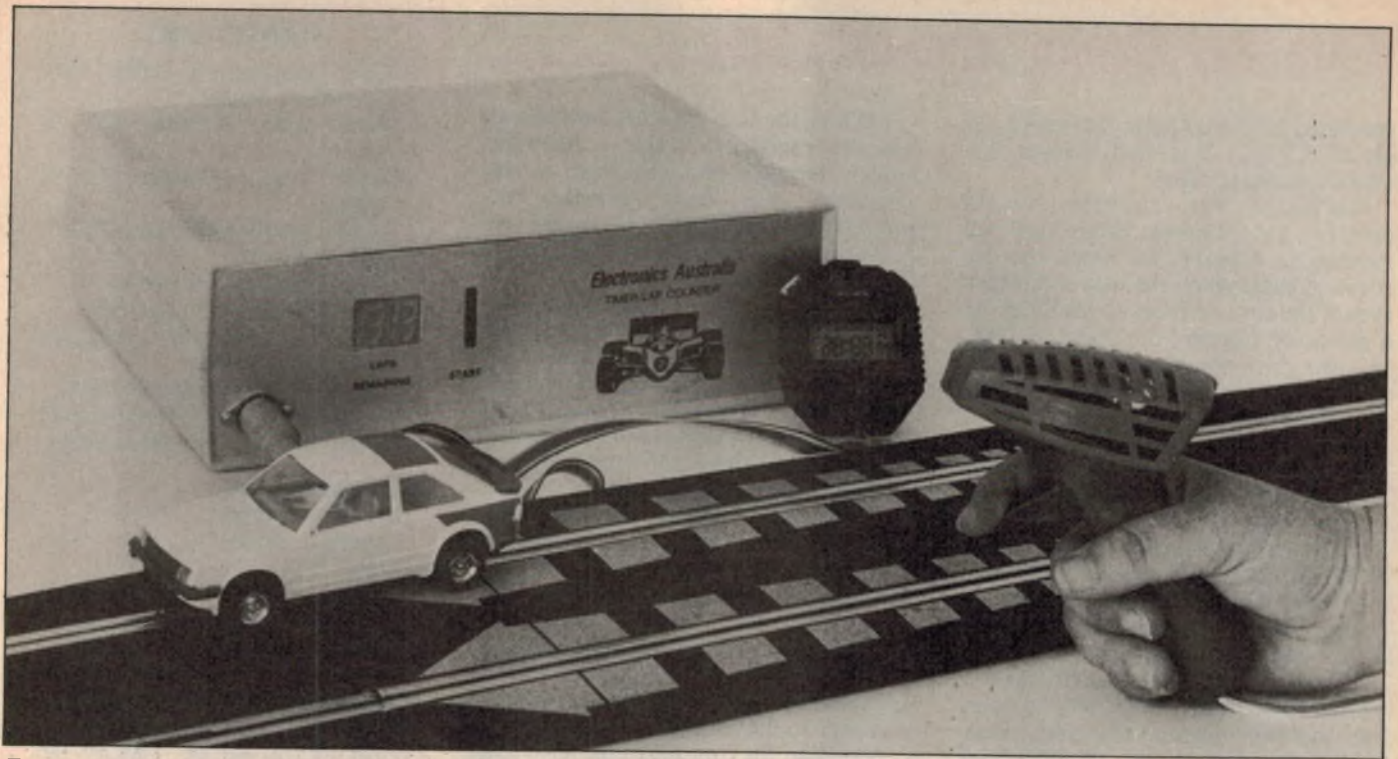

The unit features starting lights, a presettable lap counter and a modified stopwatch for timing.

From the electrical point of view, it would have been preferable to mount the contact on the negative rail of the track. This rail is permanently connected to the power supply, whereas the positive rail is intermittently disconnected through the hand controller. However, the construction of the track we used (Scalextric) was more suited to positive rail mounting of the contact.

Circuit description

It is essential to consider the circuit in terms of its various "blocks" to make any headway with the description. It will quickly become apparent, however, that the connections between blocks are manifold and devious!

Detection is performed by Q1, a BC337 NPN transistor. In addition to providing greater immunity to voltage spikes than an IC detector, the transistor can also be triggered from a lower voltage. This ensures reliable detection. Even if the car coasts across the finish line, the motor will generate sufficient voltage for triggering. In fact, pushing the car over the finish line by hand will trigger the detection circuitry.

IC1b and IC1c operate as a latch, with the latch condition maintained by D5. When Q1 turns on, the output of IC1c latches high and will remain so until reset by D2.

The start lights are controlled by IC2, a 4017 decade counter. When the Reset switch is pressed, IC2 returns to its "0" count (ie, pin 3 high). This turns on the first LED. When the Reset switch is released, IC2 begins counting "down"

with each of the outputs from 1 to 5 going high in turn.

Clock signals for IC2 are generated by Schmitt trigger oscillator IC1d, which has a frequency of about 2Hz.

In order for IC2 to continue counting, its clock enable pin (13) must be low. There are two conditions which can defeat this condition: the "5" output of IC2 can go high, taking pin 13 high by means of D7; or the start pulse can be latched, taking pin 13 high by means of D6. In the latter case, IC2 will stop counting before the last LED has been illuminated. This corresponds to an illegal start.

Diodes D3 and D4 form an AND gate. When both pin 1 of IC2 and pin 2 of

IC1a are high, the AND gate output is high. This corresponds to a car crossing the pickup after the count down sequence is completed. Since the car will be moving when it crosses the pickup, a brief pulse will be generated at the output of the AND gate.

The pulses generated at the AND gate are used for both the lap count and stopwatch functions. Consider first the lap count circuit — its operation is rather more straightforward.

The lap count display has two digits, each driven by a 4511 decoder/driver IC. IC6 drives the least significant digit and IC8 the most significant. Each of these ICs has a 4-bit binary coded decimal input which is decoded and used to drive the respective displays.

The input code is generated by two 4029 presettable counter ICs. In this case, the preset number is the number of laps to be raced. This is set by two small screwdriver adjustable binary coded decimal switches. These two switches can either be mounted on the PCB and left at some setting or mounted on the front panel so that they can be easily adjusted. When the preset enable pin (1) is taken high, the output code is the same as the preset input code. This number is latched so that it continues to be displayed after the preset enable goes low.

Clock pulses are fed into the clock input (pin 15) of IC7 which drives IC6 and the least significant digit. Because the 4029s have been configured to count down in this circuit (pin 10 tied low), IC7 decrements each time a pulse is



View showing the stopwatch with the modified Reset switch and race in progress LED.

Timer/lap counter

generated by the detector. The carry-out pin of IC7 (pin 7) is used to clock IC9 (most significant digit).

Normally, the counters would continue to decrement after they had reached 0. Clearly, we want the lap count to cease when the race is finished, even if the car continues to circulate. As a means of stopping the count at "00", the two carry-out pins of the counters are ANDed and used to enable clocking via the enable pin.

The carry out pins are normally high, going low only when the minimum count (for decrement mode) has been reached. The carry out pins of IC7 and IC9 are fed to a common point through D17 and D18 respectively. This point goes low only when the "00" count is reached and is fed back to the clock input of IC7 (pin 15) through D15.

Since the clock signals are fed to IC7 via a 100k Ω resistor, the ANDed carry outs can easily prevent any clock pulses from registering at pin 15 once both carry outs go low.

The clock pulses for IC7 are not taken directly from the input AND. Instead, the input pulses are processed in IC5 before being supplied to the rest of the circuit. The stopwatch part of the circuit will need to be considered in conjunction with IC5.

The stopwatch

The actual stopwatch used in our prototype came from Dick Smith Electronics, but it appears to be very similar to other types. It has three button switches — the middle switch selects the mode, the right hand switch is Stop/Start for the stopwatch mode, and the left hand switch is Reset for the stopwatch. These buttons also perform other tasks which are irrelevant to this circuit (eg, time and calendar setting).

Pressing the Reset button before the timer has been stopped gives a lap time. This causes the display to freeze. When it resumes the correct elapsed time is indicated. To operate the stopwatch as required by this circuit, the sequence must be: Start, Reset, another Reset 0.5s later (the display freeze time), Stop, and then finally the Reset to 0 pulse. All of these pulses must originate from the track mounted detector.

The stopwatch is connected to the main circuit via a 7-way rainbow cable. This permits the Stop and Reset to be controlled externally. Since the stopwatch has only a single battery as its power supply, the +12V rail of the main circuit can not be used for the control pulses. To overcome this problem a 4016 quad bilateral switch (IC4) is included in the circuit.

Each of the four switches function as low power solid state relays — when the control terminal is taken high, a low resistance path exists between two input/output terminals. There are no polarity requirements for the input/output signal.

In this circuit, 12V control signals are used to control the 1.5V switch voltage of the stopwatch. The Stop button of the stopwatch can be left in place — there is no problem if it is wired in parallel with IC4c. In fact, this will allow starting and stopping of the stopwatch to be performed manually if desired.

The Reset switch of the stopwatch must, however, be rewired. It is essential that both the main circuit and the stopwatch receive reset pulses at the same time. The simplest method of achieving this is to fit a new switch and run two wires to the main circuit. When the main circuit is reset, a reset pulse is also sent to the stopwatch via IC4d.

Note that the control pin for IC4d (pin 5) is connected via a 10k Ω resistor to diodes D10 and 11. These two diodes form an OR gate for the "1" and "8" outputs of IC5 (a 4017 decade counter). The 10k Ω resistor ensures that the OR output can easily be defeated by other control functions.

IC5 is reset each time a pulse is delivered from the track pickup. After each reset, it cycles through to the "9" count and, because the "9" output (pin 11) is connected to the clock enable (pin 13), waits until another reset pulse is delivered. While cycling, both the "1" and "8" outputs (pins 2 and 9) will momentarily go high, providing two pulses at the OR gate output.

The duration of each pulse is one clock cycle. In this case the clock (IC1f) operates at about 12Hz. The two OR pulses are separated by seven clock pulses which is about 0.5s.

The "9" output of IC5 (pin 11) is also connected to the reset pin (15) via D12. At the end of the cycle, the "9" output will be high and D12 reverse biased. In this state, a reset pulse fed to pin 15 will reset IC5.

As soon as the reset is effective, the "9" output goes low. D12 is now forward biased and pulls pin 15 low, thus preventing any further reset pulses from resetting IC5. This prevents multiple counting due to contact bounce at the pickup — only the first pulse registers. Any other pulses occurring before IC5 finishes counting (just over 0.5s) will be ignored.

The clock signal for the lap counting circuit is taken from the "1" output of IC5. This is connected via a 100k Ω resistor to the clock input (pin 15) of IC7.

PARTS LIST

- 1 LCD stopwatch (DSE Cat. Y-1041 or similar)
- 1 PCB, code 85ms6a, 205 × 75mm
- 1 PCB, code 85ms6b, 70 × 75mm
- 1 plastic instrument case, 260 × 190 × 80mm
- 1 7-pin DIN plug and socket
- 1 3-pin DIN plug and socket
- 1 SPST momentary contact pushbutton switch
- 2 rotary BCD decade switches
- 3 metres of 8-way rainbow cable
- 1 metre of 2-core shielded cable

Semiconductors

- 16 1N914 diodes
- 1 1N4001 diode
- 6 red LEDs
- 1 green LED
- 7 BC337 NPN transistors
- 1 7812 12V regulator
- 2 7-segment common cathode displays (Stanley NKR163, Fairchild FND500 etc)
- 1 74C14 or 40106 CMOS hex Schmitt inverter
- 2 4017 decade counters
- 1 4093 Schmitt input quad NAND gate
- 1 4016 quad bilateral switch
- 2 4029 presettable up/down counters
- 2 4511 BCD to 7-segment decoder/drivers

Capacitors

- 1 470 μ F 35VW PC electrolytic
- 1 4.7 μ F 15VW PC electrolytic
- 1 1 μ F 15V tantalum
- 2 0.1 μ F metallized polyester (greencap)
- 1 .082 μ F greencap
- 1 .047 μ F greencap

Resistors (0.25W, 5%)


- 1 × 2.2M Ω , 5 × 1M Ω , 14 × 100k Ω , 10 × 10k Ω , 19 × 1k Ω , 6 × 470 Ω .


Miscellaneous

- Machine screws and nuts, 6mm spacers (optional), hookup wire etc.

Whilst the reset pulses for IC5 are obviously derived from the pickup, they are not in fact coupled in directly. The first reset pulse must be ignored — we do not want the lap count to decrement as the car crosses the start line for the first time. Thus, we need a circuit that ignores the first pulse but registers all subsequent pulses.

This circuit is provided by IC1e, IC4b, IC3c and IC3b. IC4b (a CMOS switch) latches the first pulse, with pin 10 going high and the latch condition maintained

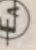 **TIMER/LAP COUNTER**

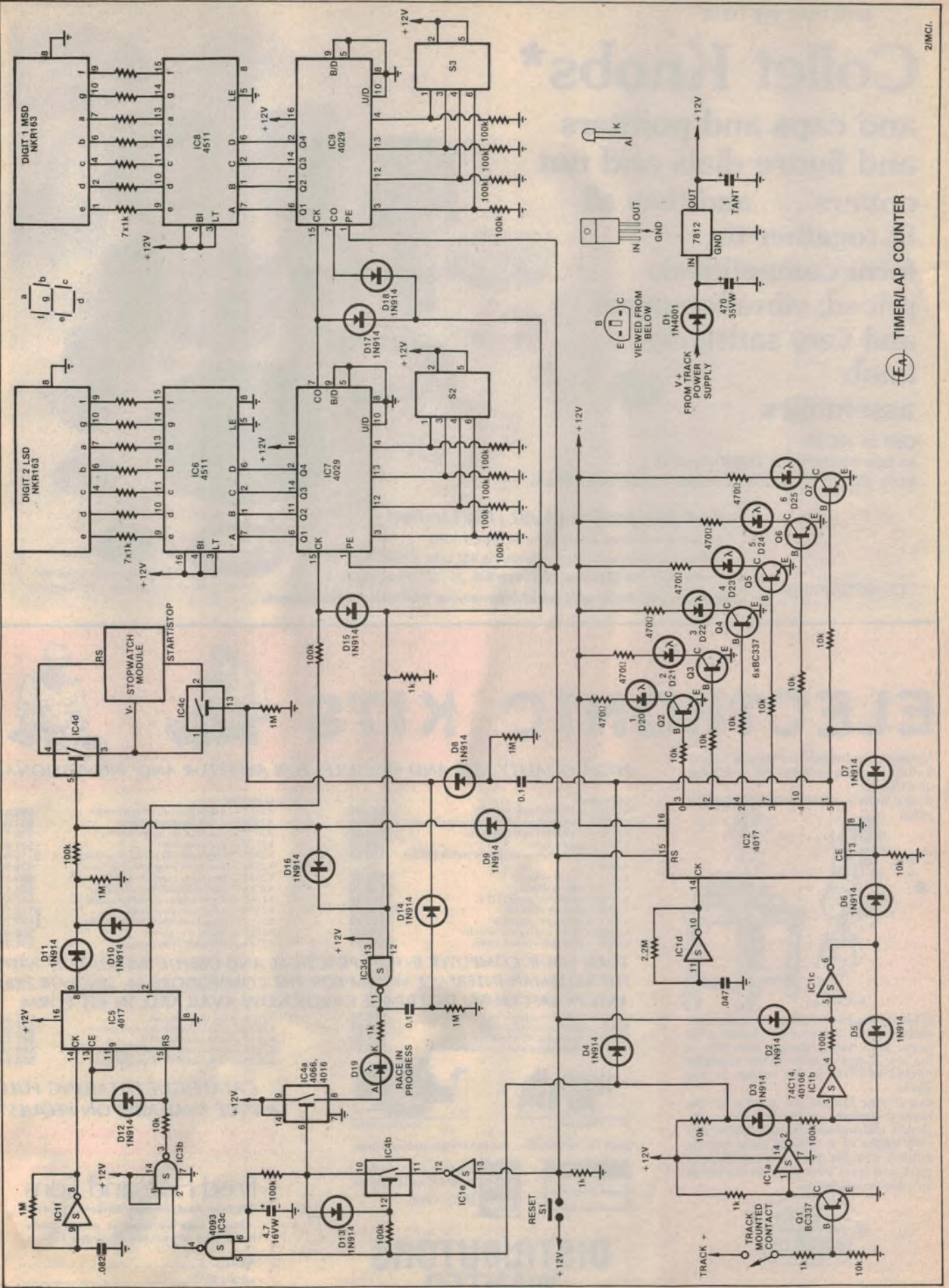

.. and now we have

Collet Knobs*

and caps and pointers
and figure dials and nut
covers . . . and they all
fit together to
form competitively
priced, vibration-proof
and very satisfying
knob
assemblies

Call us NOW!
to talk about your requirements . . .
from single to O.E.M. custom made quantities.



COMPONENTS

C&K Electronics (Aust.) Pty Limited

Office 2/6 McFarlane Street Merrylands NSW 2160
PO Box 101 Merrylands 2160 Telephone 682 3144 Telex AA23404
Agents Melb 598 2333/Adel. 269 2544/Bris. 36 1277/Perth 458 7111

Bringing you the excellence of International Professional components



* Manufactured by
SIFAM LTD England

VELLEMAN

ELECTRONIC KITS

Installing an Industrial Process Timer?
Building your own Amp, FM Oscillator
or whatever?
THEN DON'T LET THIS HAPPEN TO YOU!



Whether you're a beginner, an advanced enthusiast or a tradesman looking for better than hobby quality, with 90% of the low-budget kits currently available **FRUSTRATION** is the name of the game.

But if you hunger for quality of the highest regimen, together with lucidly simple instruction manuals, throw out your bagful of cheap parts with its untried designs that frequently don't work and feast your eyes on the bill of fare presented here:-



FRED HOE and SONS Pty. Ltd.
246 EVANS ROAD SALISBURY BRISBANE, 4107
TELEPHONE (07)277 4311 TELEX 42319



HIGH QUALITY KITS AND MODULES FOR AMATEUR AND PROFESSIONAL

Light effects:	
K1874 — 4 channel running light	\$43.01
K2588 — 3 channel sound to light with pre-amp	\$50.49
K2590 — 7 channel light computer	\$74.80
K2601 — strobe light	\$29.92
K2602 — 4 channel running light and modulator	\$50.49
Audio:	
K611 — 7 watt amplifier	\$20.57
K1771 — FM oscillator	\$18.70
K1798 — stereo VU using LED's	\$41.14
K1804 — 60 watt amplifier	\$46.75
K2572 — stereo pre-amplifier	\$23.28
K2582 — stereo audio input selector	\$39.27
K2606 — LED audio power meter	\$35.53

Controllers:	
K2557 — 3 digit precision thermometer	\$59.84
K2574 — 4 digit up/down counter	\$91.00
K2577 — universal AC motor control	\$29.12
K2579 — start/stop timer	\$21.84
K2585 — code-lock 140 x 6 digit numbers	\$115.94
K2594 — zero cross programmable timer	\$29.92
K2623 — lab power supply 0-24V DC @ 1A	\$69.19
K2565 — auto slide/cassette controller	\$27.12
K2567 — 20cm display, common anode	\$47.69
K2584 — 4 digit precision timer	\$118.30
K2591 — programmable control module	\$109.20
K2625 — digital rev counter	\$50.96
K2595 — precision timer module	\$91.00

TURN YOUR COMPUTER INTO A PRACTICAL AND USEFUL INSTRUMENT WITH THE VELLEMAN INTERFACE SYSTEM FOR THE COMMODORE 64, SINCLAIR ZX81 AND ZX SPECTRUM. INTERFACE CARDS NOW AVAILABLE IN KIT FORM

K2629 — CMOS real time clock and RAM	\$70.98
K2615 — motherboard for ZX81	\$60.97
K2616 — motherboard for ZX Spectrum	\$61.88
K2628 — motherboard for Commodore 64	\$73.71




LIGHT COMPUTER



START/STOP TIMER

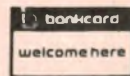*SALES TAX INCLUDED. Add \$3.50 Freight charge per order.



BANKCARD AND
AMERICAN EXPRESS
WELCOME

CATALOGUE DETAILING FULL
RANGE AVAILABLE ON REQUEST

CUT OUT AND MAIL TODAY!

Fred Hoe and Sons

246 Evans Road, Salisbury, Brisbane, Qld. 4107

Please send me name of nearest dealer
and a copy of your new illustrated booklet.

NAME _____

ADDRESS _____

POST CODE _____

DISTRIBUTORS WANTED

Timer/lap counter

by D13. This logic level is fed to pin 6 of NAND gate IC3c, but only after a delay of about 0.5s as set by the associated RC delay network (100kΩ and 4.7μF).

In order for IC3c to deliver a pulse, both of its inputs must go high. Pin 5 goes high whenever the detector delivers a pulse but pin 6, as we have just seen, does not go high until 0.5s after the first pulse. By this means, the first detector pulse is ignored while all subsequent pulses are gated through to the output (pin 4).

IC3b inverts the output of IC3c to obtain the correct logic sense for resetting IC5.

To reset the pulse discrimination circuitry, pin 11 of IC4b must be pulsed low. This pulse is derived by using IC1e to invert the positive going pulse from the Reset switch.

One last characteristic of the stopwatch Reset circuit should be mentioned. In the event of any resetting pulses being supplied by IC4d after a Stop pulse has been delivered by IC4c, the stopwatch would immediately reset to 0. This may not be desirable — a car may perform a victory lap after the race and this should not reset the timer.

For this reason, D16 is connected between the lap counter AND circuit (D17 and D18) and the control pin of IC4d (pin 5). When the AND output is low (both counters at 0), D16 is forward biased and blocks any further reset pulses to pin 5.

Let's briefly sum up the functions described thus far. First, a starting cue is provided by a column of six LEDs. When the last of these is illuminated, the competitor is free to start.

When the car crosses the starting line for the first time, a pulse is generated and a latch is toggled. If this occurs before the last LED illuminates, the start is

aborted (ie, the LEDs stop). If the start is legal, the start pulse toggles another latch which, after a 0.5s time delay, toggles a third latch which enables the lap counting circuitry.

Each subsequent pulse is converted to a double pulse (IC5) and interfaced to the Reset control of the stopwatch. When the lap count reaches 0, both lap counting and lap timing are inhibited.

Stop/start control

Let's move on now and discuss the Stop/Start control for the stopwatch. Fortunately, both the stop and start pulses are generated by relatively simple means.


The start pulse is delivered when the "5" (final) count of IC2 is reached. This positive transition is differentiated by a 0.1μF capacitor and 100kΩ resistor. It is then coupled to the control pin (pin 13) of IC4c via diode D8.

A stop pulse is provided when the ANDed carry out of the 4029 counters changes state. At the completion of the race, this output goes low and is inverted by IC3d. The resulting positive going stop pulse is again differentiated and coupled to pin 13 of IC4c via D14.


D8 and D14 serve to isolate the stop and start circuits from each other.

In addition to providing the stop pulse, IC3d also drives the cathode of LED D19. The anode of D19 is driven through an inverter (IC4a) from the pulse discriminator latch (IC4b). In this way, the LED is illuminated whenever there is a race in progress. It comes on after the car crosses the start line (not when the timer starts) and is extinguished when the lap count reaches 0.

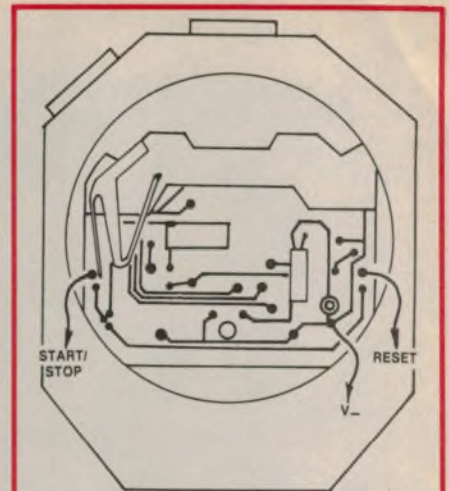Power for the circuit is derived from the track power supply and regulated to +12V using a 7812 3-terminal regulator.



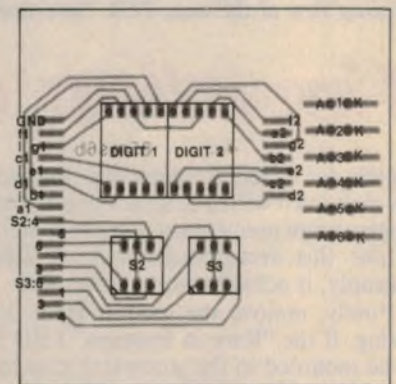This diagram shows the wiring connections to the stopwatch module. Additional leads are run to the LED and Reset switch.




Parts layout for the display PCB (S2 and S3 optional on this board, see text).


With the Scalextric set we used, the power pack includes a full wave rectifier but no filtering. The nominal voltage is 12V (RMS), but the actual voltage is closer to 25V peak with no load.

Construction

With the stopwatch we used, it was impractical to use the existing Reset

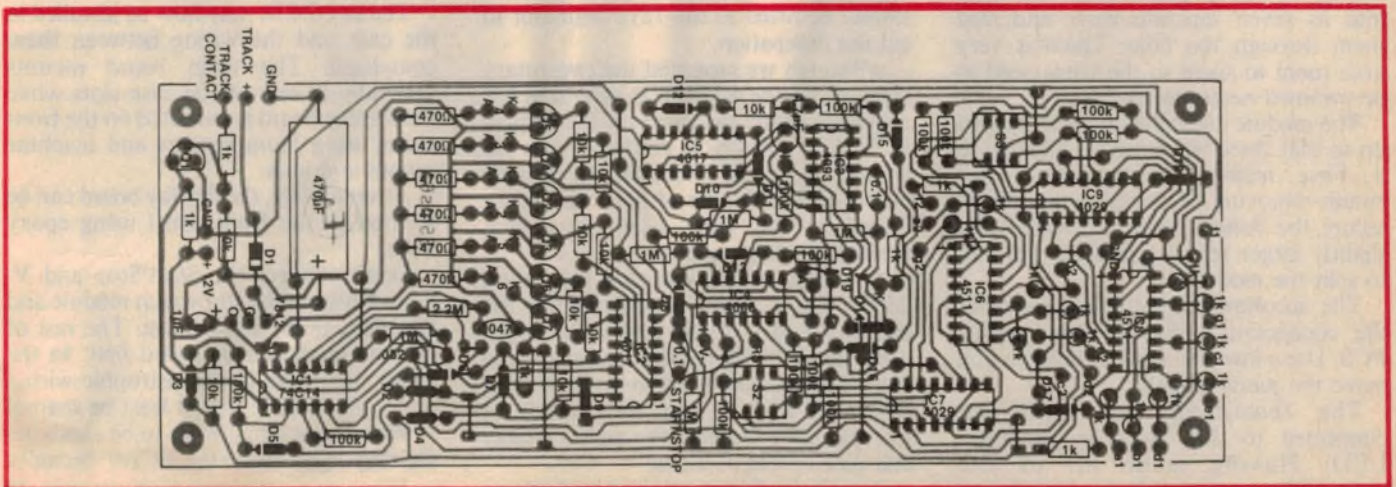Below: parts layout for the main PCB. Take care when installing the semiconductors and electrolytic capacitors.



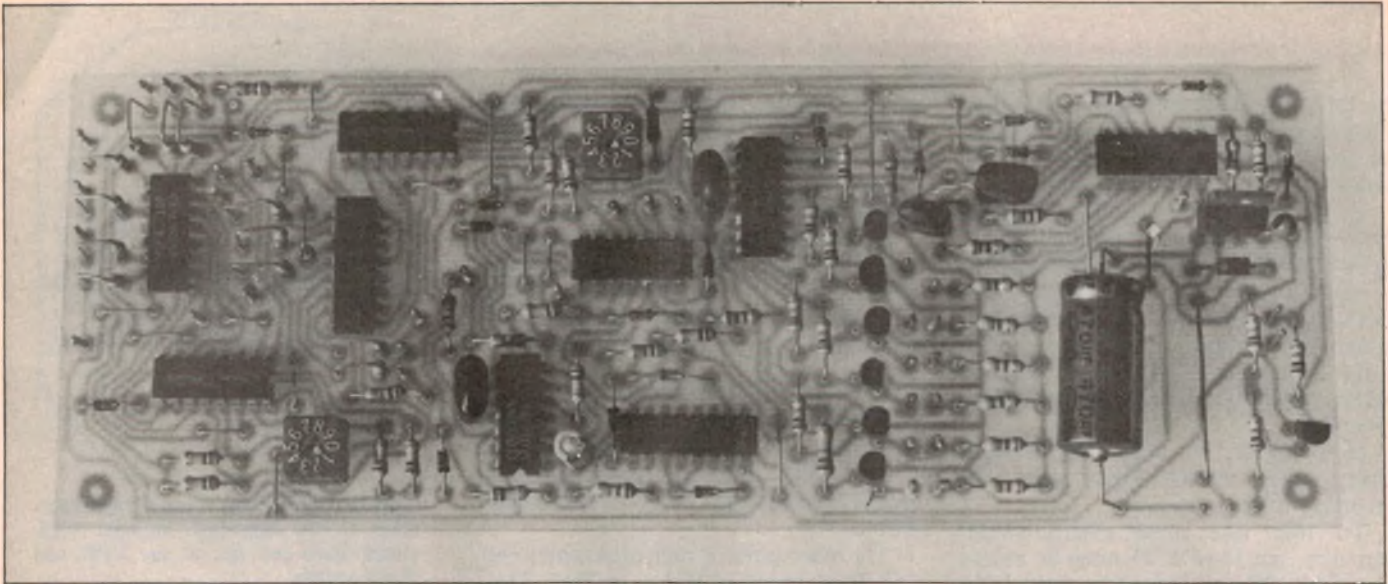

Close-up view of the main PCB. Note that the final version differs slightly from this prototype.

Timer/lap counter

switch for external switching. Instead, we replaced it with a compact single pole, single throw momentary contact switch. Whilst this arrangement looks a little ungainly, it actually works quite well.

Firstly, remove the module from the casing. If the "Race in Progress" LED is to be mounted in the stopwatch case (as ours was), drill the hole now. This done, remove the Reset button and drill two small holes through which to feed the leads for the new Reset switch.

The switch we used was of the type intended for PCB mounting. We chose it because of its low profile. Once the leads were soldered to it, we used super glue to hold the switch in place.

A 1-metre length of 7-way rainbow cable is used to connect the stopwatch module (and Reset switch) to the main PCB. The access hole for the cable is drilled in the bottom of the case and should be about 3mm. Split the cable into its seven separate wires and feed them through the hole. There is very little room to spare so the wires need to be trimmed neatly to length.

The module itself must now be opened up so that three wires can be soldered to it. First, remove the battery — this entails removing two small screws which secure the battery holder. Another two slightly larger screws are then removed to split the module.

The accompanying diagram indicates the connection points on the module PCB. Use a low power soldering iron and make the joints quickly.

The remaining two leads are connected to the "Race in Progress" LED. Having made all of the connections, re-assemble the module and

check that the back cover of the case can still be fitted. The other end of the rainbow cable is terminated in a DIN socket connector.

PCB assembly

Two printed circuit boards take care of the circuit assembly. These are coded 85ms6a (205 × 75mm) and 85ms6b (70 × 75mm). The larger board accommodates all the ICs while the smaller board carries the 7-segment displays and the six Start LEDs.


The main board can be assembled first. No particular order need be followed but we suggest that the 16 wire links be installed first and the ICs left until last. We used PC stakes to terminate the external wiring connections.

Note carefully the orientation of the semiconductors and the electrolytic capacitors. A small aluminium heatsink should be fitted to the 7812 regulator to aid the dissipation.

Although we mounted the two rotary switches on the main PCB, provision has also been made for them on the display PCB. The choice is yours. If you do choose to mount them on the display board, then a couple of holes should be drilled in the front panel to permit screwdriver adjustment.

A plastic instrument case measuring 260 × 190 × 80mm is used to house the circuitry and is fitted with a Scotchcal dress label. A 7-pin DIN socket on the front panel accepts the stopwatch plug connector while a 3-pin DIN socket on the rear panel accepts the power supply and pick-up connections.

Attach the Scotchcal label to the front

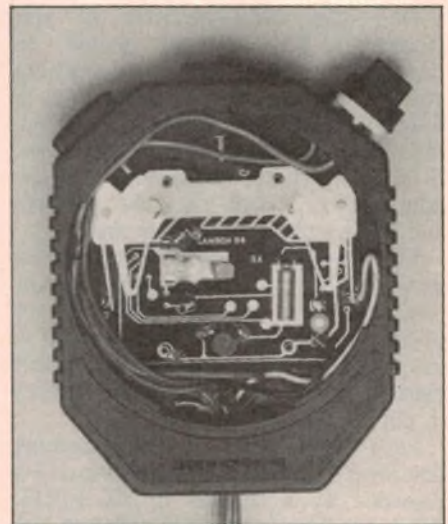

View inside the modified stopwatch. Compare this with the wiring diagram on page 67.

panel, then drill and cut the necessary holes for the displays and the DIN socket. The rear panel DIN socket can also be mounted at this stage.

The two PCBs may now be installed in the case and the wiring between them completed. The main board mounts vertically in one of the case slots while the display board is mounted on the front panel using 6mm spacers and machine screws and nuts.

Alternatively, the display board can be secured to the front panel using epoxy resin.

Don't connect the Start/Stop and V-wires between the stopwatch module and the main PCB at this stage. The rest of the circuit should be tested first. In the event that there is a catastrophic wiring error, the module will at least be spared!

Where two circuits are to be used, the starting light oscillator (IC1d) becomes

continued on page 70

Bert bought bargain bubbles. Bye-Bye, Bert.


Poor Bert. He saved a few cents on bargain air bubble packaging. And wound up costing the company big dollars in returned, damaged goods. Trouble was he looked only at price. Not at his product. He got the right price, but settled for the wrong bubbles. And loss of cushioning thickness did him in.

He should have chosen AirCap[®], the barrier-sealed bubble packaging material from RHEEM Sealed Air Products. AirCap's barrier seal retains air to prevent cushion thickness loss. And provides the best cushioning protection possible at affordable prices.

Don't be a Bert. For the right packaging, at the right price, make the right choice. Insist on AirCap[®], available in rolls, slit rolls, perforated rolls, cut to size pads and bubble bags to suit your packaging requirements.




RHEEM AUSTRALIA LIMITED
Incorporated in Victoria


Sealed Air Products 

Our Products Protect Your Products[®].

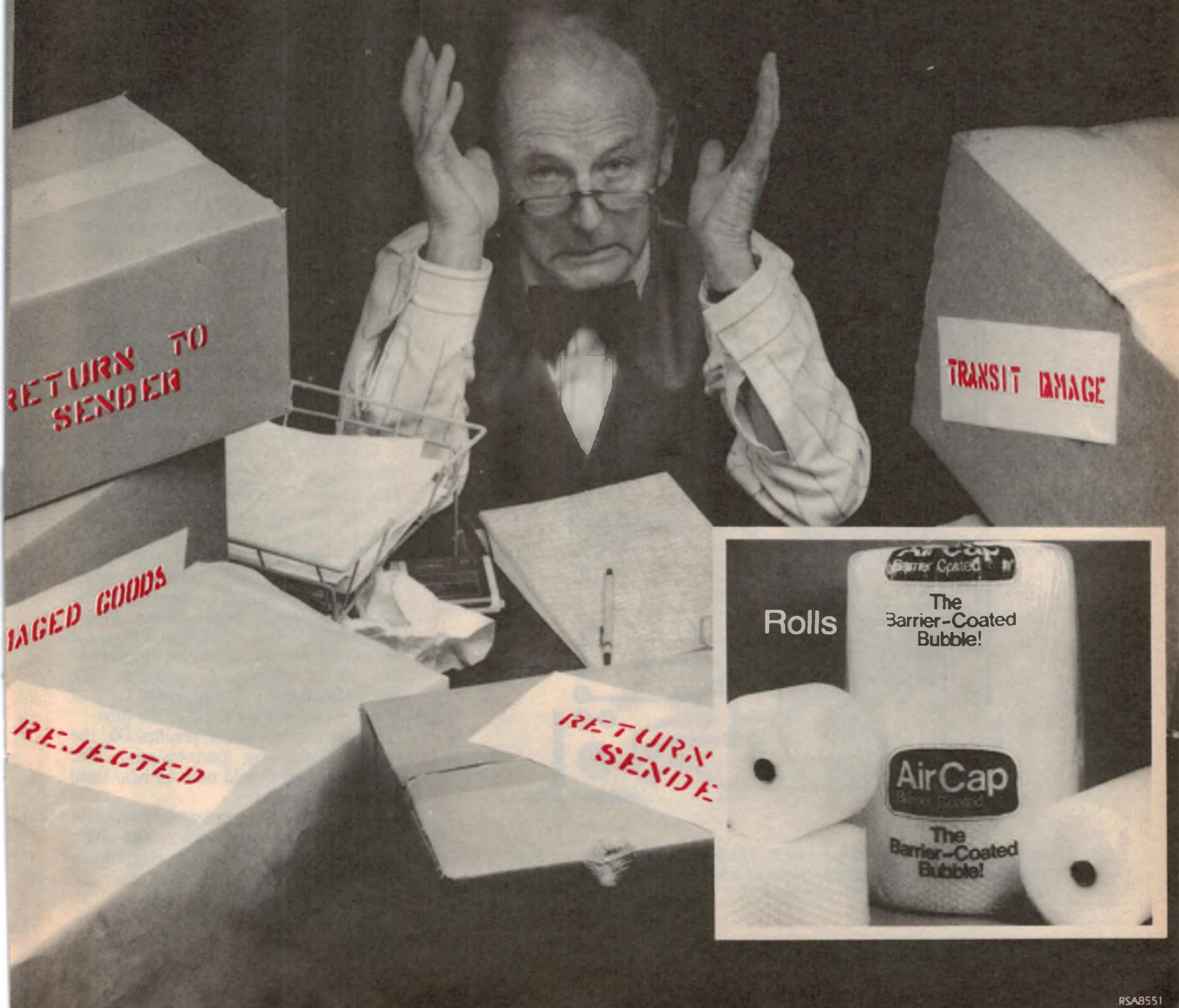3 Burrows Road, Alexandria, NSW 2015
Phone: Sydney (02) 519 4211. Melbourne (03) 579 4366
Brisbane (07) 277 2133. Adelaide (08) 45 7633
Perth (09) 458 4877



Timer/lap counter

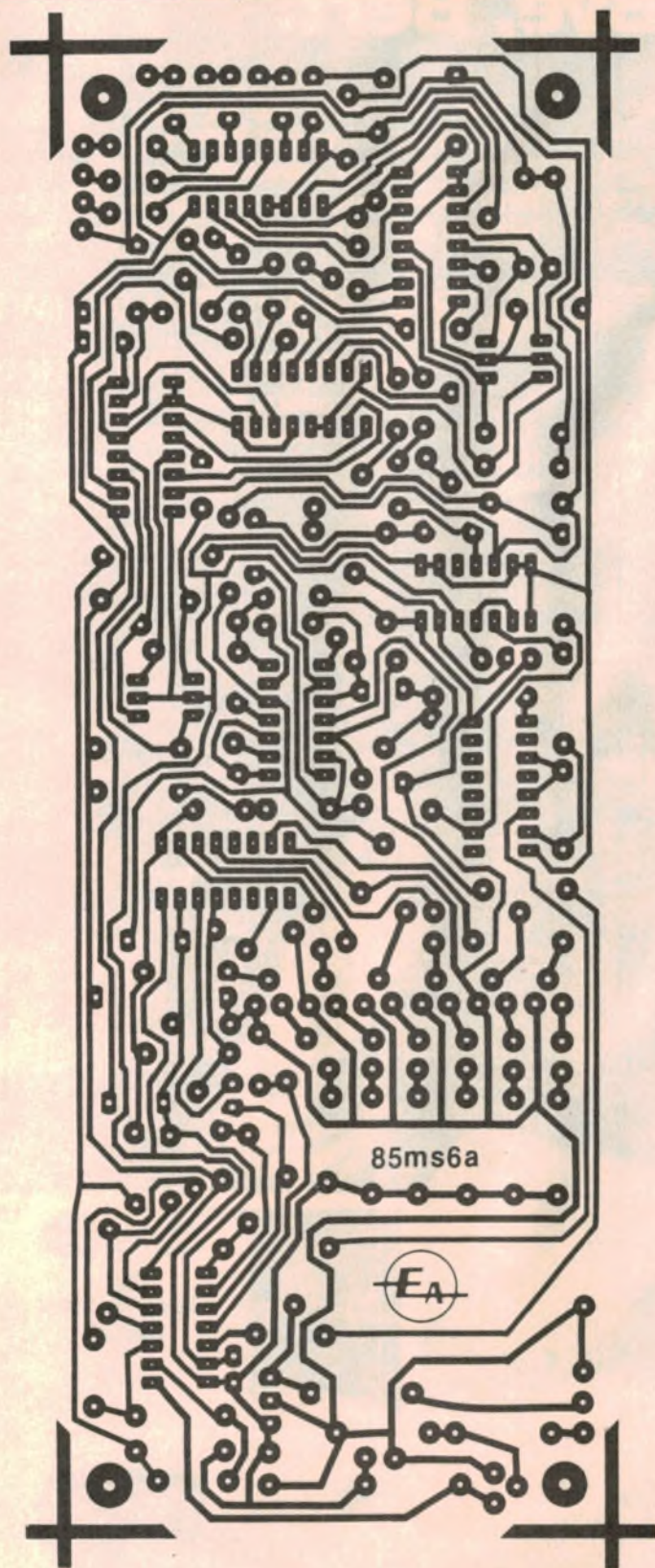

Actual size artwork for the main PCB. The front panel artwork has been omitted due to space limitations. Finished artworks can be obtained from Electronics Australia for \$3 post paid.

redundant for the second circuit. Whilst we are not suggesting that one sixth of IC1 can be omitted from the circuit, the associated $2.2M\Omega$ resistor and $.047\mu F$ capacitor most certainly can be. Link 1 must also be omitted from the slave board.

The two boards are then slaved together by installing a connection between Link 1 on the master board and pin 15 of IC2 on the slave board (this is available at one of the Link 1 mounting holes). Note that the input of IC1d (pin 11) on the slave board should be soldered to the adjacent pin 12. It would otherwise be left floating, leaving IC1d prone to spurious oscillations.

Testing

Check first of all that the regulator is in fact regulating to +12V. If the output voltage is only about 2V, the regulator is probably installed backwards. If the output voltage is more than 12.5V, the regulator is either defective or the PCB has a bridge between the copper tracks.

Assuming that you've made first base, plug in the stopwatch connector and try operating the Reset switch. The first start LED should be illuminated while the switch is held down and the countdown sequence should begin as soon as it is released. The preset number should be indicated on the lap counter display after resetting.

Next, set the preset to a low 2-digit number (eg, 11), press the Reset button and short the pickup to the Vin terminal. The "Race in Progress" LED should illuminate. Now momentarily short the pickup to the Vin terminal at about 1s intervals — the lap counter should now decrement by one on each occasion.

When the lap count reaches 00, the "Race in Progress" LED should extinguish. If this checks out, switch off and connect the Start/Stop and V- leads to the 7-pin DIN socket.

Make sure that the timer is set to the stopwatch mode and is reset. Now, when the start countdown is completed, the stopwatch should begin timing. When the pick up is first shorted to Vin, there should be no change to the stopwatch. On each subsequent occasion, the stopwatch display should freeze for half a second to indicate the elapsed time.

When the lap count reaches 00, the timer should stop (permanently). The indicated time should now be held until the circuit is reset.

Note that the stopwatch connector should be unplugged when the main circuit is switched off. If this is not done, the stopwatch controls may be permanently activated, leading to premature battery failure.

Troubleshooting

Fault: no count down on starting LEDs.

Check: is the clock (IC1d) for IC2 working? The correct frequency is 12Hz. Is pin 13 of IC2 (clock enable) low after resetting? Is pin 15 (reset) low when the reset switch is released?

Fault: stopwatch does not start when countdown is finished.


Check: remove the base resistor for Q7. If fault persists, check that the 1M Ω pulldown resistor on pin 13 of IC4c is the correct value. Otherwise, check the wiring to the stopwatch module. If OK, replace the base resistor. If the base resistor is the problem, replace it with a higher value eg 22k Ω .

Fault: stopwatch does not stop counting after each lap.

Check: does pin 10 of IC4b latch high after the car starts? If not, does its pin 12 go high when the pickup is shorted to Vin? Does a pulse arrive at pin 15 of IC5 after each lap? Is the clock (IC1f) for IC5 working? A 30Hz clock signal should be present at pin 14. Is pin 5 of IC4d normally low? — it should be.

Fault: "Race in Progress" LED does not work.

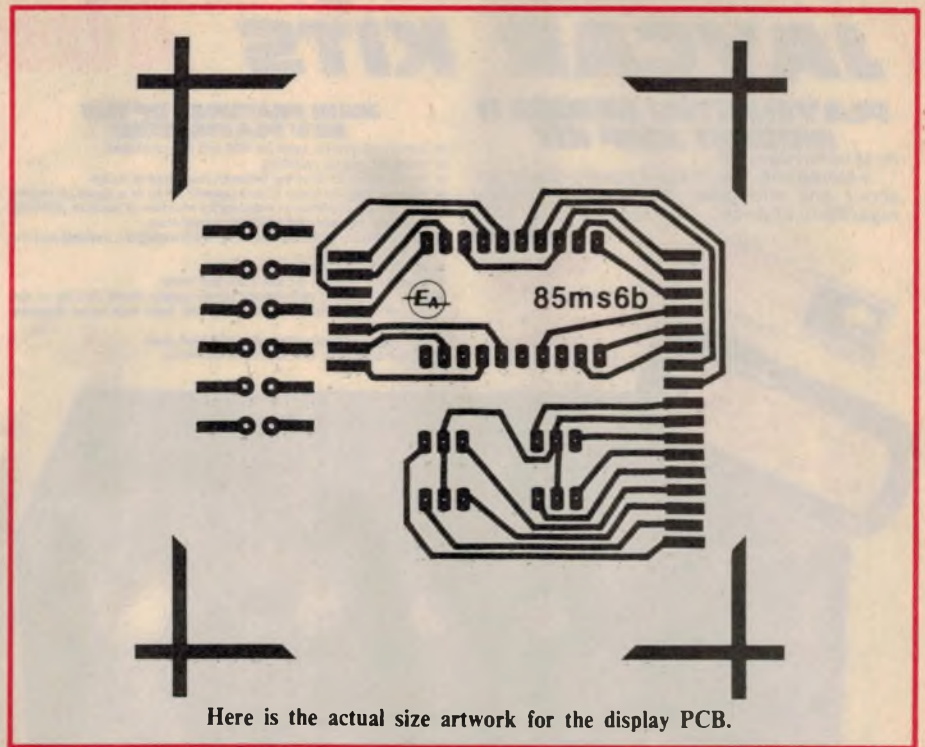Check: Pin 12 of IC3d must be low after resetting and before the car begins



Here is the actual size artwork for the display PCB.

racing. If it isn't, make sure that the counter ICs have a high carry out (pin 7). Pin 8 of IC4a should be low after the start — if not check IC4b as per above.

Fault: lap count displays do not indicate the preset numbers or do not illuminate.

Check: carefully check that the various control pins of ICs 6, 7, 8 and 9 are tied either high or low as per the circuit diagram. Look for unsoldered pins or solder bridges. Try running a razor between non-connected adjacent pads. ☺

AUDIO TELEX

OUR TX100 HAS VOX!

No its not a disease, its voice operated muting on channel four — and that's just one of the many new features of our TX series PA amplifiers.

TX100
4 mic inputs
2 aux inputs

Others include:-

- Rack or table mounting
- AC/DC operation
- VU meter
- Tape recorder input output
- 600ohm output



And a price which is lower than most ordinary amplifiers.

SYDNEY
P.O. Box 421,
1 Little Street,
PARRAMATTA 2150
Phone: 633 4344

MELBOURNE
P.O. Box 468,
7 Essex Road,
MT WAVERLEY 3149
Phone: 277 5311

BRISBANE
P.O. 871,
42 Commercial Road,
FORTITUDE VALLEY 4006
Phone: 852 1312

Werner Electronic Industries Pty. Ltd.,
P.O. Box 111, WELLAND SA 5007
37A Humphries Tce., KILKENNY 5009
Phone: 268 2766

Electro Acoustic Co. Pty. Ltd.,
55 Frobisher Street,
OSBORNE PARK WA. 6017
Phone: 444 8688

JAYCAR KITS AUSSIE MADE

PLAYMASTER SERIES II MOSFET AMP KIT

Ref. EA Jan/Feb/March 1985

"... a stereo amplifier that will equal or better just about any integrated commercial amplifier, regardless of price". - Leo Simpson, Editor of EA, February 1985.

MAIN FEATURES OF THE NEW PLAYMASTER

- ★ Switchable phono input for MM and MC cartridges
- ★ Electronic signal switching
- ★ Full facilities for dubbing between two cassette decks
- ★ Monitor loop for either of two cassette decks or a signal processor
- ★ Click action pushbutton switches for selection of sources, dubbing and tape monitor with LED status indicators.
- ★ Centre detents on bass, treble and balance controls, multiple detents on volume control
- ★ Heavy duty heatsinks
- ★ Power transformer for low hum and noise
- ★ Easy to build - all parts except power supply mount directly on the two printed circuit boards; wiring has been kept to an absolute minimum
- ★ 100 watts RMS per channel into 8 ohm load
- ★ Less than 0.01% total harmonic distortion

MOTORCYCLE INTERCOM

Ref. EA February 1984

What a great kit! This full duplex unit enables you to talk to your pinion passenger whilst driving with your helmets on! Powered by the bikes battery - you can both talk at the same time if you wish as there are no switches to activate. The Jaycar kit includes the special headphone inserts and all parts
Cat. KA-1533

ONLY \$39.95



MUSICOLOR IV

Ref. EA August 1981

The ultimate lighting controller. Combines a four channel sound-to-light effect with a four channel chaser.

- Front panel LED display
- 4 different chaser patterns
- Auto and manual reverse chase
- Sound triggered chase
- Inbuilt electret microphone
- Safe, opto-isolated circuitry

Cat. KA-1010

ONLY \$99.90



GREAT NEW KITS FROM ETI Modem Kit

Ref. ETI May 1985

This brilliant new design is a price breakthrough. Never has a modem with such SOPHISTICATED FEATURES been offered at such an incredibly low price. Now you can have no excuse to gain the tremendous benefits that a modem will offer viz:

- ★ Access to huge data banks
- ★ Networking
- ★ Telecommunications
- ★ Electronic shopping
- ★ Software exchange
- ★ And much more

Cat. KE-4695

ETI 699

This ETI kit is a full modem with facilities similar to units costing hundreds of dollars more. It even includes a Telecom approved push button telephone! Now is your chance to use your electronic skills in your new hobby and save a fortune over ready built.

You can obtain this modem kit (which includes a telephone for us humans) for the incredibly low introductory price of only \$149. That's right! \$149, inc. case, down to the last nut and bolt. But hurry! Stocks of the critical modem chip are very low and will severely limit kit supply.

ONLY \$139

8 SECTOR BURGLAR ALARM

Ref. EA Jan/Feb 1985

Why buy a commercially made up unit for more when you can buy this kit and SAVE money! A unique feature of this kit is the fact that you can wire N/O and N/C alarm sensors ON THE SAME LINE.

- ☆ 8 sectors ☆ 2 delayed entry sectors ☆ Steel box ☆ Includes battery and siren driver in the price ☆ Variable exit and entry delays.

Cat. KA-1560

\$139.00

BRAND NEW KIT FROM JAYCAR



BUSKER AMPLIFIER

Ref. EA February 1985

Fantastic portable amplifier kit for low-level P.A., Buskers or for practice.

- ★ Battery or mains operation
- ★ Full control - bass, treble and volume
- ★ 2 inputs (low and high)
- ★ 17 WATTS RMS output
- ★ Gel battery automatically recharged when mains used.

★ INTRODUCTORY PRICE ☆

All electronics including GEL battery, 8" speaker, metal chassis etc.
Cat. KA-1592

ONLY \$125
PRE-CUT WOODEN CABINET to suite Cat. KA-1593

ONLY \$30.00
BUY BOTH AND PAY ONLY
\$149.00
A FURTHER SAVING


EPROM COPIER/PROGRAMMER

Ref. EA December 1984

This unit enables you to program 2716 & 2732 EPROMs and copy 2708, 2716 & 2732's. It is easy to make and works well. The Jaycar kit includes all PCB components (inc. ZIF sockets) and panel.
Cat. KA-1557



ONLY \$69.00

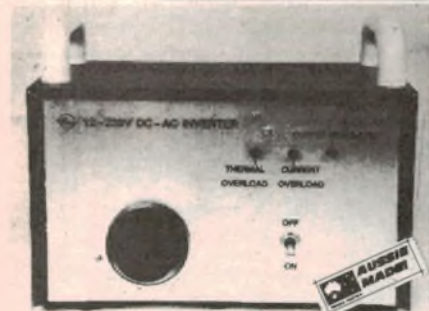

12/230V - 300 WATT INVERTER

This unit provides up to 300VA of power at 235V from an ordinary car battery. It is ideal as a standby AC power supply. The output voltage is regulated and gives a precise 50Hz. The kit also has current limiting with ultimate thermal shutdown.

The Jaycar kit features quality conservatively rated components and is complete down to the case and front panel.
Ref. EA June 1982

Cat. KA-1574

\$195.00

NEW!

ETI ECONOMY HOUSE/CAR ALARM MODULE

Ref. ETI May 1985

This low cost full feature module can form the basis of a sophisticated anti-theft system!

ETI 1527

Cat. KE-4698

\$24.95

- YOU SAVE MONEY! ★ ★ ★

ETI 153 TEMPERATURE PROBE FOR MULTIMETERS - Ref: ETI June 1983


This simple add-on project extends the functions of your multimeter to the measurement of temperature. It is particularly suited to digital multimeters. It can be used to measure temperature over the range from -55°C to +150°C with an accuracy of 0.5°C or better. The Jaycar kit includes the Jiffy case and Scotchcal panel. The AD590 is supplied but not the probe case which is in fact the plastic case of a BIC biro.

Cat. KE-4033 **ONLY \$19.50**

Microwave Leak Detector

Ref: ETI 724 - If you own a microwave oven, your peace of mind is worth the price of this kit. Extremely simple and foolproof to build and use. Gives a positive indication of the security of your oven's seal.

Cat. KE-4013 **ONLY \$14.95**

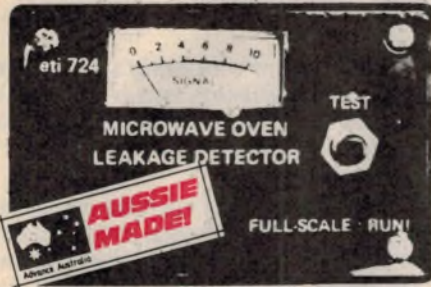

VOCAL CANCELLER - Ref: EA April 1982

Do you think you can sing? How would you like to be the lead singer in a famous rock (or any) band? You can cancel out the lead singer from almost any stereo record and substitute your own voice or musical instrument. Complete kit including case.

Cat. KA-1430 **ONLY \$19.50**

4164-150ns DRAM 64K x 1 INCREDIBLE SPECIAL SALE

We have made a scoop purchase of National Semiconductor brand new prime spec 64K DRAM. At the prices shown below we expect many manufacturers to buy so hurry! Quantities naturally are limited. **PLEASE NOTE** that these prices INCLUDE 20% sales tax which the hobbyist MUST PAY so don't be misled by offers that may appear cheaper!

Cat. Z2-8420

NEW LOWER PRICES

1-9		
\$4.00		
10-24		
\$3.80		
25-99	100-249	250+
\$3.25	\$2.95	\$2.80

3C-2V 75 Ohm COAX - 7 metres??

Seven metres? Well this is a pack of 7 metres of high quality coax cable. Why seven metres is beyond us except that it was thought to be the most asked for length and why not therefore prepack it? The bean counters got their sums wrong because it did not sell! 7 unterminated metres would normally cost \$3.50. Jaycar has a fair quantity of these fairly useful lengths for only \$2.00 which amounts to a substantial saving!



Cat. HP-1360

ONLY \$2.00/7 metres

FREE CATALOGUE

Ask for a FREE COPY of our 1985 Engineering Catalogue or send large SAE with 50¢ stamp

"RAILMASTER" Pulse-Power Train Controller



Ref: EA September 1984

"We feel that it is the best controller available, regardless of cost" - John Clarke or Leo Simpson (or both) Sept '84

This is a state-of-the-art train controller offering tremendous features:

- Variable simulated inertia
- Full short circuit protection including both audible and visual indicators
- Power and track monitor indicators
- Adequate power for double and triple heading of locos
- Fixed 12V DC and 15V AC power for lighting and accessories
- Optional walk-around throttle

The Jaycar kit includes realistic Scotchcal front panel and the special console case only available from us. The large paddle switches have been specially imported just for this kit. We believe that you will be delighted with this unit.

Cat. KA-1560 **ONLY \$79.95**



Optional Walk-around controller

Cat. KA-1559

ONLY \$9.95

Diesel Sound Simulator

Ref: EA November 1984

This project mounts inside a model train (i.e. goods wagon) and produces a noise similar to a diesel locomotive. The speed varies according to the throttle action for added realism. All parts supplied.

Cat. KA-1561 **ONLY \$19.95**

Steam Sound Simulator

Ref: EA December 1984

Build this realistic steam sound simulator for your model train layout. It features an Infra-Red optical switch to synchronise the 'chuffs' to the wheel rotation. Like the KA-1561 this unit picks up its power from the railway tracks. All specified components supplied including 32 ohm headphone type transducer.

Cat. KA-1562 **ONLY \$15.95**



JUNE SPECIAL!

Electronic Crossover Kit

(Ref: EA November 1984)

NEW SHORT FORM KIT!

You can NOW build this desirable project for a lot less! There have been requests for a version of this kit that can be built into other equipment. This is it!

The kit contains PCB and all board components etc. The box (inc. front panel) and selector switches are not supplied but everything else! Special price for June only

Cat. KA-1571

ONLY \$79.00

SQUEAKY CLEAN MAINS

FILTERS - Two fantastic low cost models MS-4010 will supply up to 4 appliances. Each 240V socket is isolated from the other. i.e. interference from disc drives is de-coupled from the CPU power supply etc. It will supply up to 4 outlets with a total load of 6 amps (unswitched).

Cat. MS-4010

ONLY \$125.00

Single 10 amp line socket type filter (unswitched).

Cat. MS-4012

ONLY \$34.95



TWO PLUGPACK AND DC CONVERTOR BARGAINS!

Plug Pack This unit will give a DC output of 1½, 3 or 4½ V @ 250mA (max). A switch on the back of the unit changes the voltage. It is also supplied with a 1.6m cord, polarity reversing plug and midway connecting plug. We have over 500 of them. This voltage range is fairly useless except for small transistor radios, calculators etc. At this price however, it's worth having one or two for the inevitable occasion when such a power source is required.

Cat. MP-3002

ONLY \$2.95

You could pay over \$10 elsewhere!



DC Converter This unit plugs into your car cigarette lighter socket and will provide up to 300mA at 6 and 9V DC. Ideal to power the Ghetto Blaster in your car! We only have just over 200 so hurry!

Cat. MP-3015

Normally sell for around \$10. This month \$4.95 - 1/2 price!!



Incorporating ELECTRONIC AGENCIES

NUMBER 1 FOR KITS

MAIL ORDER HOTLINE (02) 646 1300

N.S.W. SHOWROOMS

SYDNEY: 117 York Street Tel: (02) 267 1614
 CARLINGFORD: Cnr Carlingford & Pennant Hills Road Tel: (02) 872 4444
 CONCORD: 115/117 Parramatta Road Tel: (02) 745 3077
 HURSTVILLE: 121 Forest Road Tel: (02) 570 7000
 GORE HILL: 188/192 Pacific Highway (Cnr Bellevue Avenue) 439 4799

QUEENSLAND

BURANDA: 144 Logan Road Tel: (07) 393 0777

MAIL ORDERS: P.O. Box 480, AUBURN 2144 Tel: (02) 643 2000

HEAD OFFICE: 7/9 Rawson Street, AUBURN 2144

Tel: (02) 643 2000 Telex: 72293

SHOP HOURS

Carlingford, Hurstville & Gore Hill	\$5 - \$9.99	\$10.00
Mon-Fri 9am - 5:30pm, Thurs 8:30pm, Sat 12pm	\$10 - \$24.99	\$32.20
Sydney	\$25 - \$49.99	\$45.50
Mon-Fri 8:30am - 5:30pm, Thurs 8:30pm, Sat 4pm	\$50 - \$99.99	\$65.50
Concord	\$100 - \$198	\$80.00
Mon-Fri 9am - 5:30pm, Sat 4pm	Over \$199	\$100.00

COMET ROAD FREIGHT ANYWHERE IN AUSTRALIA ONLY \$12



MAIL ORDER VIA YOUR PHONE

'est components for leakage

High voltage insulation tester

Everyone knows how to do a simple insulation test on mains wiring, appliances and components using the ohms ranges on a multimeter, but this is only a go/no-go test. To do it properly you need our Insulation Tester which has an internal 500V supply.

by **ANDREW LEVIDO**



The problem with using a multimeter to perform insulation tests is that it only tests at 1.5V DC. Very few components operate at this very low voltage so it really is not valid.


Consider a mains operated appliance. It may easily give an open circuit reading when tested between the active leads and the frame. But plug in to the mains and you have a different kettle of fish altogether. The peak voltage of the 240VAC mains is 340 volts which increases the chances of insulation breakdown enormously. Add to that the strong possibility of spike voltages rising on top of the mains voltage and you can see why mains operated appliances have to have such good insulation.

The same arguments apply when testing transformers, capacitors, high voltage semiconductors and other components, so there is a real need for a convenient self-contained insulation tester which can test at a voltage at least as high as that which will be present in the circuit under normal operating conditions. The voltages most commonly used in tests of this kind are 500V and 1000V.

A further disadvantage of the majority of multimeters is their lack of resolution when measuring large resistances. Most multimeters simply read infinity (open circuit) when the resistance is above a few tens of megohms. There are meters especially designed to measure large resistances at high voltages and these are often referred to as a "Megger". Many people use the word "Megger" as a generic term but it is actually a trade-name. While we intend to describe a similar Megohm Meter in the near future, we considered that a simpler tester would also be worthwhile.

We selected 500V as the most suitable test voltage, since it provides a reasonable margin over the typical mains voltages present in electronic equipment, while keeping the design of the inverter as simple as possible.

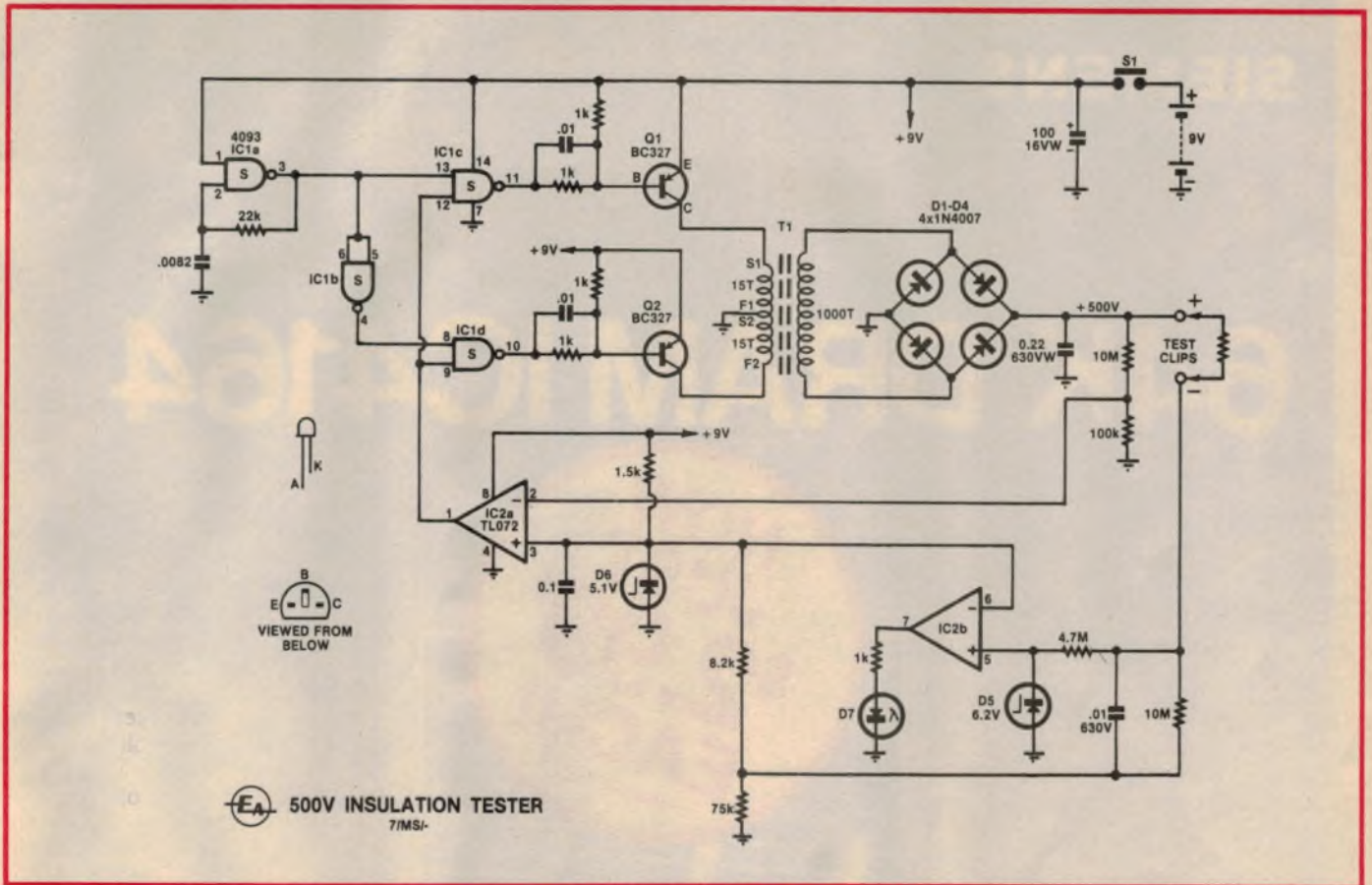Having decided on this, it remained to select a threshold value of resistance



A feedback-controlled inverter is used to generate 500V DC from a 9V battery.

which would be considered suitable. One tester published in this magazine some years ago used the value of one thousand Megohms which seems quite a high figure. However, these days it is possible to test for a much higher figure which is closer to the ratings of typical components.

Accordingly, we selected a value of 10,000 Megohms or, in today's parlance, 10 Gigohms. That's a lot of ohms in anybody's language. At a test voltage of 500V, an insulation resistance of 10 Gigohms will have a leakage current of nanoamps.

At this point it would be a good idea to have a look at how the tester is used in practice. Consider a typical mains powered project as published in this magazine. The mains cable enters through a grommet in the back panel, and is terminated at a barrier strip. From this point the mains wiring is routed to the primary of the transformer, perhaps via a switch and possibly a fuse as well. The chassis is earthed.

There are any number of points at which the mains may break down to the chassis under fault conditions, so an insulation test should be made. One of the test leads is clipped to the chassis, and the other to one of the mains conductors. The test button is pressed, and the indicator LED mounted on the

front panel of the tester is observed. If the LED glows continuously, the insulation between the mains and the chassis is suspect. If the LED flashes briefly and then goes out, then the insulation resistance is higher than 10GΩ, and hence the insulation between the mains and chassis can be considered adequate.

Further, the Insulation Tester can be used to provide indication of leakage in capacitors and other components. Naturally, the tester can only give an indication that capacitor leakage current is less than 50nA, however this gives a fair indication of the condition of the capacitor. Large value capacitors will take a considerable time to charge up to the full 500V because of the high series resistance of the tester, so be sure to allow for this before discarding a capacitor as leaky.

How it works

The heart of the 500V Insulation Tester is an inverter to generate the 500V supply from the 9V battery. A feedback-controlled inverter was selected because it gives a much improved regulation of the output voltage and much lower current drain at no load.

In a previous tester of this type (Capacitor Insulation Tester, EA November 1971), a self-excited inverter

was used. When we tried an inverter of this type again, we found that the current drain when there was no load was undesirably high for a single 216 type 9V battery. This problem did not arise with our previous circuit because it employed a much larger battery. Unfortunately, such batteries are no longer available.

We therefore settled on the driven inverter shown in the accompanying circuit diagram, based on a quad NAND Schmitt trigger, IC1. One gate, IC1a, is connected as a Schmitt trigger oscillator with a square wave output and a nominal frequency of 5kHz.

The oscillator works as follows. Consider the initial condition whereby the capacitor has no voltage across it. This means that pin 2 of IC1a will be low and the output, pin 3, will be high. The capacitor therefore begins charging up via the 22kΩ resistor and will continue to do so until it reaches the positive threshold of the input. When this happens the output at pin 3 will switch to low and the capacitor will begin discharging via the 22kΩ resistor. It continues to do so until the voltage at pin 2 drops to the negative threshold of the input which causes pin 3 to switch high and begin the cycle again.

The result is a square wave at pin 3 and a sawtooth waveform at pin 2.

SIEMENS

64K DRAM IC4164

**NOW
JUST
\$2.99*
EACH!**
While stocks last.



180,000 Components for Peanuts!

Siemens, a world leader in high technology electronic components is even better known for relentless quality control. And now Siemens is offering memory I.C.'s at a lower price.

Both 128 and 256 refresh cycle I.C. memory parts are available immediately.

Each 16 pin dual in line package delivers 180,000 components – mostly transistors and capacitors – in its silicon chip. That's more than 600 components for less than 1 cent!

Siemens Ltd.
544 Church Street, Richmond, Vic. 3121.
Telephone: 420 7318 Sydney 436 8730

Siemens Memory I.C.'s. High quality. New low price.

*Minimum order of 100 + pieces, plus sales tax if applicable.

Cash sales facilities available for non account customers.

A6/85

Insulation tester

The square wave signal is fed via the other three gates of IC1, to the bases of transistors Q1 and Q2. IC1c and IC1d have two of their inputs connected together and are used to gate the drive signals to Q1 and Q2 off or on, depending on whether the inverter voltage is above or below a determined reference level. IC1b is used as an inverter to obtain a complementary signal to that from pin 3 of the IC1a, the oscillator. IC1c and IC1d gate the complementary signals from pins 3 and 4, in response to a control signal from pin 1 of IC2a.

Transistors Q1 and Q2 are driven from the outputs of IC1c and IC1d via 1k Ω current-limiting resistors. Since transistors driven via such large-value resistors tend to be rather slow in their switching action, .01 μ F capacitors are connected across the 1k Ω resistors to provide a "speed-up action". 1k Ω resistors are also connected between the bases of the transistors and the positive rail to ensure that the transistors switch off properly.

Q1 and Q2 drive the inverter transformer primary winding. Because Q1 and Q2 are driven out of phase, the supply voltage will be applied alternately to each half of the primary. When one transistor turns on, it will apply the full 9V to one half of the primary winding. By transformer action, this will apply 9V across the other half of the primary winding. This means that the opposing transistor has 18V appearing across it.

So each half-primary winding sees a waveform of 18V peak-to-peak and the total primary winding sees a voltage of 18V RMS. This is stepped up by the transformer turns ratio (1000:30) to obtain 600V peak to peak across the secondary. When rectified and filtered, this gives a DC voltage of 600V.

But we don't want 600V. We want 500V, so we turn off the inverter every time the DC output voltage rises by a small margin over 500V. This is accomplished in the following way.


A voltage divider consisting of a 10M Ω and a 100k Ω resistor is connected across the DC supply to sample the

output voltage. The divider produces 5.1V at the input of IC2a when the DC output voltage is 515V.


This sampled voltage is compared with the zener diode voltage applied to pin 3 of comparator IC2a. Now whenever the sample voltage at pin 2 rises by the smallest smidgin above 5.1V, IC2a switches its output, pin 1, low. This turns gates IC1c and IC1d off and removes the drive from both transistors. The output voltage will now drop until the voltage at pin 2 of IC2a is sufficient to let its output go high again and enable the oscillator.

Thus, the nominal output voltage of the inverter is maintained at around 510V or so, depending on the resistor and zener diode tolerances.

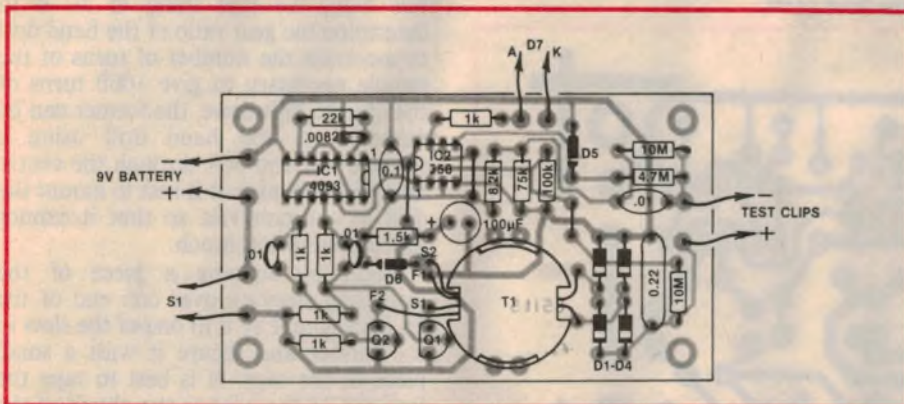The +500V is connected to one of the test terminals, while the other terminal is connected to a 4.6V reference via a 10M Ω resistor. For a resistance of 10G Ω across the test terminals, a current of 50nA will flow through the 10M Ω resistor. This will produce a voltage of



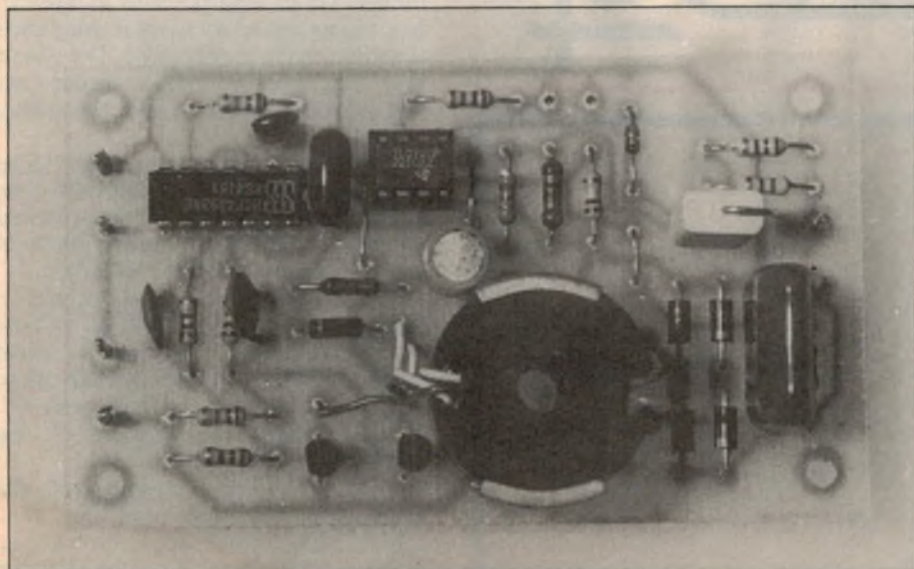Above is the parts layout and wiring diagram while below is a view of the assembled PCB. Take care with component orientation.



Parts List

- 1 PCB, code 85it5, 54 x 95mm
- 1 plastic case, 130 x 68 x 41mm
- 1 Scotchcal label
- 1 SPST momentary pushbutton switch
- 1 FX2240 potcore with former and mounting clip
- 1 9V battery clip
- 1 5mm LED clip
- 1 figure-8 cable clamp grommet
- 2 alligator clips
- 8 PC pins
- 2.5 metres 26 B&S enamelled copper wire
- 50 metres 36 B&S enamelled copper wire
- 4 5mm spacers

Semiconductors

- 1 4093 quad Schmitt NAND
- 1 TL062, TL072, LF352 dual Fet-input op amp
- 2 BC327 PNP transistors
- 1 5.1V 400mW zener diode
- 1 6.2V zener diode
- 1 red LED
- 4 IN4007 diodes

Capacitors

- 1 100 μ F 16VW PC electrolytic
- 1 0.22 μ F 630V metallised polyester
- 1 0.1 μ F 100V metallised polyester
- 2 .01 μ F ceramic
- 1 .01 μ F 630V metallised polyester
- 1 .0082 μ F 100V metallised polyester

Resistors (0.25W, 5%)

- 2 x 10M Ω , 1 x 4.7M Ω , 1 x 100k Ω ,
- 1 x 75k Ω , 1 x 22k Ω , 1 x 8.2k Ω ,
- 1 x 1.5k Ω , 5 x 1k Ω

Miscellaneous

- Machine screws and nuts, hookup wire, figure-8 cable, solder etc.

Insulation tester

0.5V across the resistor. It is this voltage that is monitored by IC2b to determine if the resistance between the test terminals is lower or higher than the threshold value.

The 4.6V reference for the negative test terminal, and thus for pin 5 of IC2b, is set by the voltage divider resistors (8.2k Ω and 75k Ω) connected across the 5.1V zener diode.

If the current through the 10M Ω resistor exceeds 50nA, the voltage developed across it will be more than 0.5V and the non-inverting input of IC2b, pin 5, will be raised above the inverting input, pin 6, which is held at 5.1V by the zener diode. When that happens, the LED will glow.

We had to use a Fet-input operational amplifier for IC2 because IC2b must have a very low input bias current in order to work properly in this circuit. Typical Fet-input op amps have an input bias current of around 50 picoamps at room temperature so this condition is easily met.

A .01 μ F capacitor is connected across the 10M Ω sensing resistor to prevent the LED from flashing due to the variation of the 500V supply as the inverter is turned on and off. This capacitor requires a rating in excess of 500V in order to withstand the full voltage of the test circuit when there is a short circuit between the test clips.

Op amp IC2b, however, could not withstand such a high input voltage, even for the briefest interval. For this reason, the 4.7M Ω resistor and zener diode D5 have been included. D5 limits the maximum voltage applied to the non-inverting input, pin 5, to 6.2V while the 4.7M Ω resistor keeps the current flowing through the diode to a low level, even if the test terminals are short circuited. The output of IC2b drives the indicator LED via a 1k Ω current limit resistor.

The LED will light when the voltage across the 10M Ω sensing resistor exceeds 0.5V. This will occur only when the current through the sensing resistor reaches the value corresponding to a

resistance of 10G Ω or less between the test terminals. For resistance greater than this value, the LED will flash briefly while whatever capacitance exists across the test terminals is charged and then will be extinguished.

The whole circuit, as mentioned earlier, is powered from a single type 216 9V battery. The battery is connected to the circuit via a momentary pushbutton switch, SI.

Construction

Construction of the 500V Insulation Tester is, for the most part, very simple. Winding the potcore is probably the most difficult, and certainly the most tedious, job. It is best to do this first. Apart from the core assembly itself, and the wire, you will need some ordinary adhesive tape, some 50mm pieces of thin insulating sleeving (we used insulation which we stripped off some scraps of telephone cable) and a certain amount of patience.

The 1000 turn secondary is wound first. This can be done by hand if necessary, although we used a hand drill to make the job easier. If you are doing it this way, the first thing to do is to determine the gear ratio of the hand drill to ascertain the number of turns of the handle necessary to give 1000 turns of the chuck. This done, the former can be mounted in the hand drill using a suitable nut and bolt through the centre hole of the former. It is best to mount the drill in a bench vice so that it cannot move around too much.



Begin by slipping a piece of the insulating sleeving over one end of the 36 B&S wire. Lay it in one of the slots in the former and secure it with a small piece of the tape. It is best to tape the free end of the wire to the chuck of the drill to prevent it getting in the way. Carefully wind 1000 turns onto the former. Try to wind as evenly as possible, but it is not necessary to try to wind each turn next to the previous one. The wire is very thin, and breaking it means that you will have to start again, so be very careful.


When the 1000 turns have been wound on the former, slip another piece of sleeving over the end of the wire and secure the winding with a few layers of tape. This completes the secondary.

The primary is bifilar-wound; that is, two wires are wound together, as one. Divide the 26 B&S wire into two equal lengths. Sleeve both ends of both wires, and label the two starts S1 and S2. Similarly, label the finishes of the respective wires F1 and F2.

Wind 15 turns, finishing off the windings at the same place that they started. Move the sleeving up to the core, and trim off any excess wire. Wind a few

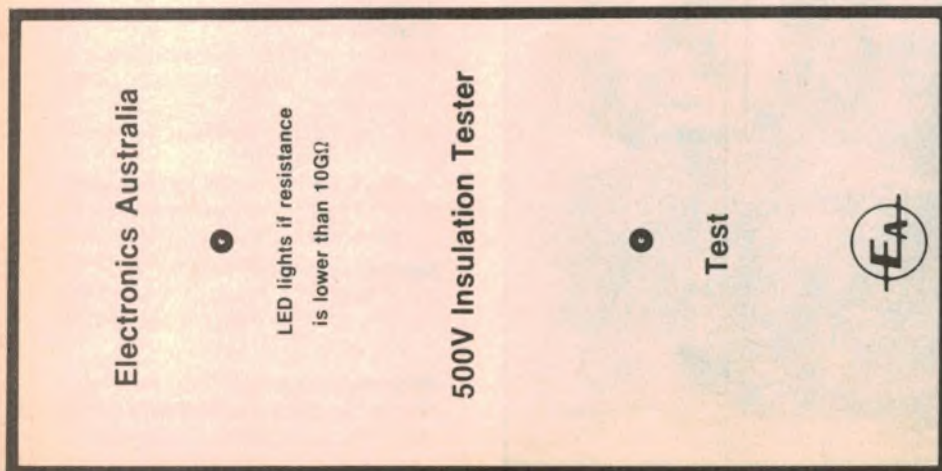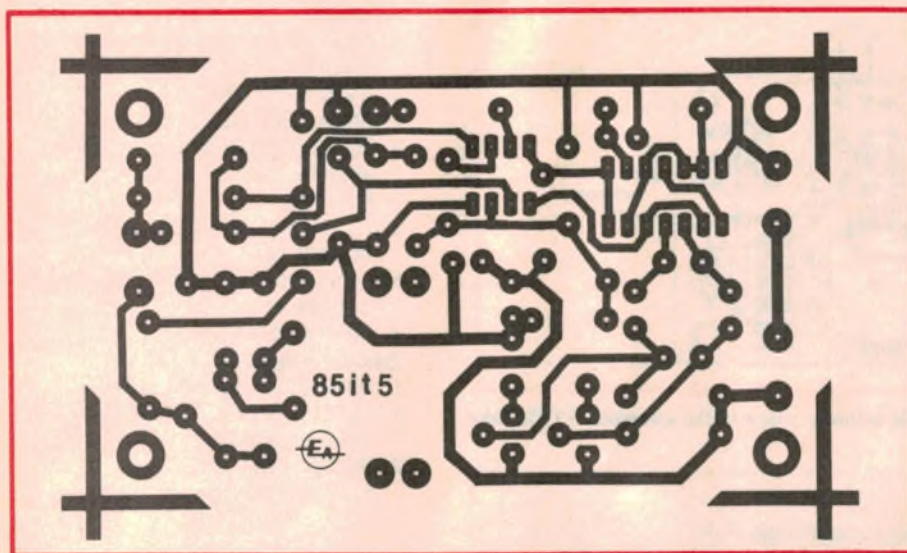Below are actual size artworks for the PCB and the front panel.



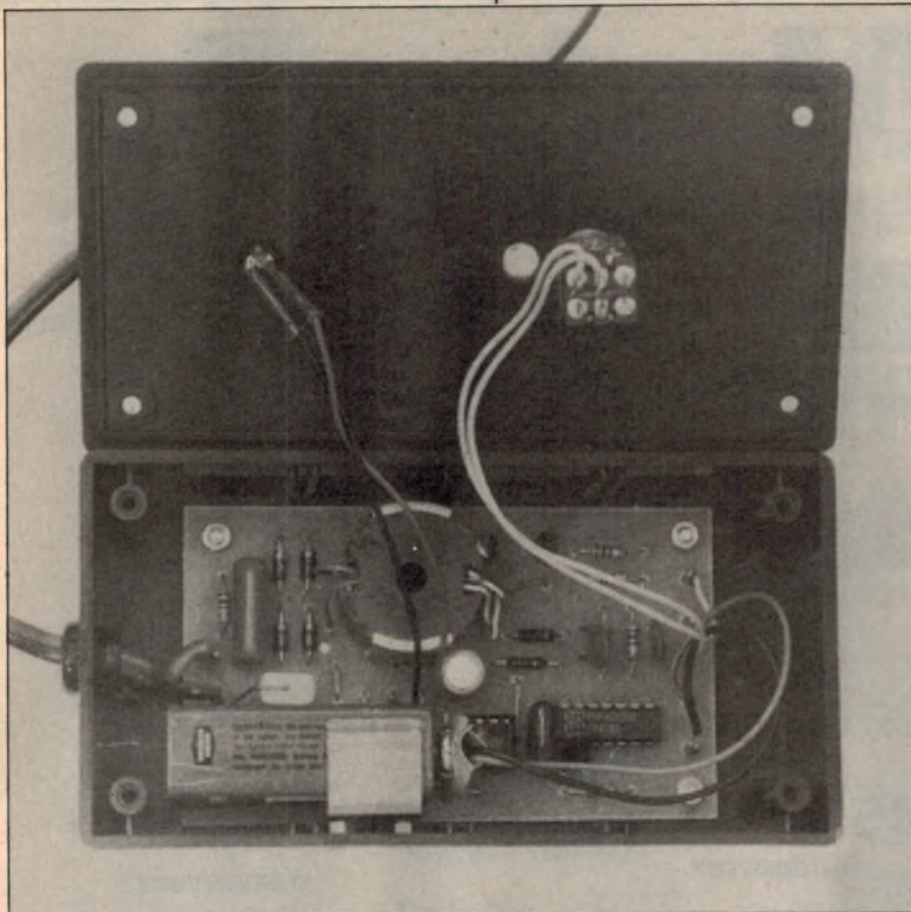

View inside the completed insulation tester. Use 240VAC cable for the test leads.

more layers of tape over the whole former and trim the wires back to about 25mm long. Strip and tin the last 5mm or so of all the windings.

The potcore can now be assembled, ready for mounting on the printed circuit board (PCB).

The ideal op amp for this circuit is the Texas Instruments TL062 which has a current drain of 0.5 milliamps. However, we recognise that this can sometimes be difficult to obtain and so the TL072 or LF352 can be substituted without any other changes. The difference will be slightly higher total current drain.

The PCB measures 54×95mm and is

coded 85it5. Begin by mounting the PC pins, the two wire links and the low profile components such as resistors and diodes. This done, mount the other semiconductors taking due care with their orientation. Mounting the capacitors and the potcore completes the printed circuit board. Note that the primary wires of the transformer must be connected to the printed circuit board as shown on the component overlay, or the inverter will not function.

The next job involves the preparation of the plastic case. Apply the Scotchcal label to the front panel and use this as a drilling template for the LED and switch


holes. Both of these were ¼-inch for the LED clip and switch that we used. Using a very sharp blade, carefully cut away the Scotchcal panel where it covers the lid mounting holes. A further hole must be drilled in the end of the box for the test leads. We used a cord clamp grommet.

Mount the PCB in the bottom of the box, using 6BA machine screws and nuts. Use a 5mm spacer under each corner of the board to raise it off the bottom. We used a clip for the 9V battery, but this is not strictly necessary; a piece of double sided sticky tape would do the job equally well. Next, mount the front panel hardware and wire this to the appropriate pins on the PCB. Do the same for the battery clip and test leads.

Use a good quality 240VAC-rated twin-lead for the test leads, since any leakage between them will be measured as well. We soldered insulated alligator clips to the ends of the leads to facilitate connection to the device under test.

To test the unit, simply push the test button and observe the LED. If all is well, it should flash briefly and the inverter should make a faint sound. Try pushing the button with the test leads shorted — the LED should light. We found that by firmly grasping the insulation of both alligator clips we could get the LED to light, showing just how high a leakage resistance is 10 Gighms. Note that this may not work if the humidity is very low or if the insulation covering the clips is particularly good.

Finally, here is a word of warning. Although the high voltage produced by this instrument is itself quite safe because it is delivered from a high impedance source, the unit can deliver a substantial bite. Be careful. If it is used to charge large value capacitors, these then become dangerous and could deliver a very severe electric shock (possibly fatal). For this reason, you should carefully discharge capacitors after they are tested, as they can remain charged to a high voltage for a long time afterwards, just waiting to a shock the unwary.

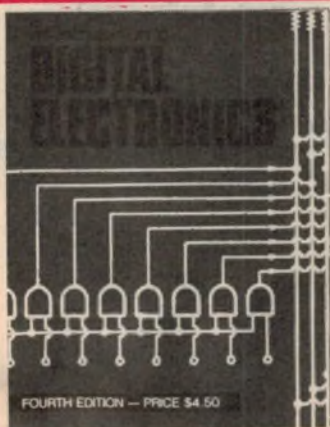

AN INTRODUCTION TO DIGITAL ELECTRONICS

Every day, more and more electronic equipment is "going digital". Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and An Introduction to Digital Electronics can give you that grounding. Tens of thousands of people — engineers, technicians, students and hobbyists — have used the previous editions of this book to find out what the digital revolution is all about.

Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017, **PRICE \$4.50** OR by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017, **PRICE \$5.40**.



IDC SOCKETS

1-9	10+
P12100 10 Pin Socket	1.95 1.75
P12101 16 Pin Socket	2.25 2.05
P12102 20 Pin Socket	2.45 2.25
P12104 26 Pin Socket	2.65 2.45
P12106 34 Pin Socket	2.75 2.55
P12108 40 Pin Socket	2.95 2.75
P12110 50 Pin Socket	3.50 2.95

Plus 20% Sales Tax where applicable

IDC CONNECTORS

1-9	100+
P12114 14 Pin Dip Plug	0.60 0.50
P12116 16 Pin Dip Plug	0.65 0.55

Plus 20% tax where applicable



CARD EDGE CONNECTORS

Edge Connectors to Disk Drives Etc	
1-9	10+
P12060 10 Way Card Edge Con	2.95 2.50
P12062 20 Way Card Edge Con	3.25 2.75
P12064 26 Way Card Edge Con	3.55 2.95
P12066 34 Way Card Edge Con	3.95 3.50
P12068 40 Way Card Edge Con	4.50 3.90
P12070 50 Way Card Edge Con	5.50 4.50

Plus 20% Sales Tax where applicable



UNPROTECTED HEADERS STRIP HEADERS

Dual in Line 2.54mm	
1-9	10+
P12240 10 Way Unprot Header	1.25 1.10
P12246 16 Way Unprot Header	1.35 1.20
P12250 20 Way Unprot Header	1.45 1.25
P12256 26 Way Unprot Header	1.50 1.40
P12260 30 Way Unprot Header	1.75 1.65
P12264 34 Way Unprot Header	1.95 1.75
P12270 40 Way Unprot Header	2.25 1.95
P12275 50 Way Unprot Header	2.75 2.50
P12280 60 Way Unprot Header	2.95 2.75

Plus 20% Sales Tax where applicable

R.A HEADERS

1-9	10+
P12241 R A 10Way Unprot Head	1.45 1.30
P12247 R A 16Way Unprot Head	1.55 1.40
P12251 R A 20Way Unprot Head	1.65 1.45
P12257 R A 26Way Unprot Head	1.70 1.50
P12261 R A 30Way Unprot Head	1.95 1.85
P12265 R A 34Way Unprot Head	2.15 1.95
P12271 R A 40Way Unprot Head	2.45 2.15
P12276 R A 50Way Unprot Head	2.95 2.70
P12281 R A 60Way Unprot Head	3.15 2.95

Plus 20% Sales Tax where applicable



COMPUTER CONNECTORS

Cat No.	Description	1-99	100+	1000+
P10900	DB25 Plug	1.30	1.20	1.00
P10901	DB25 Socket	1.40	1.30	1.20
P12210	Centronics Solder	3.50	3.15	3.00
P12200	Centronics Crimp	6.00	5.50	5.00
P10880	DB9 Plug	1.30	1.20	0.90
P10881	DB9 Socket	1.40	1.30	1.00
P10890	DB15 Plug	1.30	1.20	0.90
P10891	DB15 Socket	1.40	1.30	1.00
P10902	DB25 Cover	80	75	70

Plus 20% tax where applicable



PANEL METERS

1-9	10+	
Q10500	MU450-1mA	5.95 5.75
Q10502	MU450-0-50uA	5.95 5.75
Q10504	MU450-0-100uA	5.95 5.75
Q10505	MU450-0-50uA	5.95 5.75
Q10510	MU450-0-5A	5.95 5.75
Q10518	MU450-0-1A	5.95 5.75
Q10520	MU450-0-20V	5.95 5.75

Plus 20% tax where applicable



NICADS

Cat No.	1-99	100+
S15020	AA	1.50 1.50
S15021	C1 8AH	3.25 2.90
S15022	D 4 0AH	5.90 5.50

Plus 20% tax where applicable



SEALED LEAD ACID BATTERY 12V 1.2 AH

S15061	1-9	10.99	100+
	12.50	11.00	10.50



75OHM COAX CABLE

Cat No.	100M	500M	1000M
W11222	3C2V	18.00	17.00 16.00
W11224	5C2V	23.00	22.00 21.00

(5C2V WHITE OR BLACK)
100M ROLLS
LINE LOSS PER 100' (33M 200MHZ)
W11222 6.2dB (Approx)
W11224 3.9dB (Approx)
Plus 20% tax where applicable



DIGITAL MULTIMETER YFE YF1100

- Large easy to read 3 1/2 digit display
 - Facilities for transistor and diode testing
 - Clearly laid out front panel
 - 10A DC AC range
 - Priced to undersell the others
- | | | |
|--------|-------|-------|
| YF1100 | 1-99 | 100+ |
| | 59.50 | 57.50 |
- Plus 20% tax where applicable



IBM ADD ON HARD DISK

- 10 Mbyte
 - Seagate hard disk
 - Hard disk controller by Xebec
- | | |
|-------------|--------|
| Cat. X20010 | \$1295 |
|-------------|--------|
- Plus 20% tax where applicable



RELAYS

Massive 3A connectors			
1-9	10+	100+	
S.P.D.T. Cat. S14060	\$1.20	\$1.10	\$0.90
D.P.D.T. Cat. S14061	\$1.50	\$1.40	\$1.20



HORN SPEAKERS

Cat No.	1-99	100+
C12010	5" Plastic 8W Max	4.80 4.70
C12015	5" Metal 8W Max	4.70 4.30
C12012	12V Siren	8.50 8.00

Plus 20% tax where applicable



SOLDERING IRON STANDS

Cat No.	1-99	100+
T113023	3.25	3.00

Plus 7 1/2% tax where applicable



CANNON TYPE AUDIO CONNECTORS

We've sold 1000's because of their great value!!

3 Pin Line male Cat. P10960	1.60	1.50
3 Pin Chas male Cat. P10962	1.70	1.60
3 Pin line female Cat. P10964	2.10	1.80
3 Pin Chas FMe Cat. P10966	2.50	1.90

Plus 20% Sales Tax where applicable

TRANSISTOR

1-99	100+
2S149	3.90 3.70
2S134	3.90 3.70

Plus 20% tax where applicable




ADD ON DISK DRIVES FOR 6502 SYSTEM

1-9	10
\$195	\$189

SIP RESISTORS

Standard values.	
1-9	10+
6 Pin	0.50 0.40
8 Pin	0.60 0.50
10 Pin	0.65 0.60

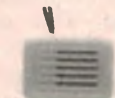

MINITURE BUZZER

5-15V White or black	
Cat. A15062	1.99 100+
	0.90 0.80

Plus 20% tax where applicable

RCA INSULATING SOCKETS

Cat No.	Desc	1-99	100+
P10232	2Way	0.25	0.21
P10234	4Way	0.45	0.40
P10236	6Way	0.75	0.60

Plus 32 1/2% tax where applicable

RCA CHASSIS MOUNT METAL

Cat No.	1-99	100+
P10231	0.16	0.13

Plus 32 1/2% tax where applicable

MONITORS

Cat No.	1-3	4+
X14500	Ritron 1 Green	\$140.00 \$135.00
X14502	Ritron 1 Amber	\$145.00 \$140.00

WHILE STOCKS LAST
Plus 20% tax where applicable



RITRON II

Swivel base monitor in stylish case.

1-9	10+
Green Cat. X14506	\$169 \$159
Amber Cat. X14508	\$179 \$169

Plus 20% tax where applicable



FANS

240V	4 1/2"	10.50	10+	100+
240V	3 1/2"	10.50	10.00	8.00
115V	4 1/2"	10.50	10.00	8.00
115V	3 1/2"	10.50	10.00	8.00

Plus 20% tax where applicable

VOLTAGE REGULATORS

7805uC	45	100+	1000+
7805KC	1.50	1.40	1.20
7812uC	45	44	43
7815KC	1.50	1.40	1.20
7818uC	50	49	48
7818KC	1.50	1.40	1.20
7905uC	50	46	44
7912uC	50	46	44
uA323KC	4.50	3.90	3.75
78H12	7.00	6.00	5.90
78HGKC	7.50	6.50	6.00
79HGKC	16.50	16.00	14.00
78P05	11.50	11.00	10.50
78P12	14.00	13.50	13.00

Plus 20% tax where applicable

RESISTORS

- 1/4 WATT E12 CARBON BULK
 - PACKED \$5.25/1000
 - TAPED AND BOXED \$5.25/1000
 - \$5.00/1000 10K LOTS
 - 1/4 METAL FILM TAPED AND BOXED
 - \$13.00/1000 \$12.00/1000/10K LOT
 - SUPPLY E24 VALUE
- Plus 32 1/2% tax where applicable



NEW SWITCHES

SPDT Cat. S11040	10-99	100+
DPDT Cat. S11042	1.00	.95
	1.20	1.00


Plus 20% Sales Tax where applicable



ENCLOSED ROTARY SWITCHES AT SPECIAL PRICES!!

1-9	10+	100
1.20		1.00

Plus 20% Sales Tax where applicable

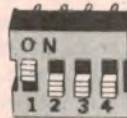

DIP SWITCHES

10+	100+	
S13402 2 Way	70 65	60
S13404 4 Way	80 75	70
S13405 5 Way	90 85	80
S13407 7 Way	1.10 1.00	.95

20% Sales Tax where applicable



QUALITY MOMENTARY (RED BODY)

SPDT Cat. S11050	10-99	100+
DPDT Cat. S11052	1.00	.90
	1.20	1.00

Plus 20% Sales Tax where applicable



ECONOMY TOGGLE SWITCHES

Unbelievable Value!

10-99	100+
S11010 (SPDT)	0.70 0.60
S11020 (DPDT)	0.90 0.80

Plus 20% Sales Tax where applicable

Circuit & Design Ideas

Interesting circuit ideas from readers and technical literature. While this material has been checked as far as possible for feasibility, the circuits have not been built and tested by us. As a consequence, we cannot accept responsibility, enter into correspondence or provide constructional details.

Infrared remote keyboard

In March, an infrared data link was described in these pages. This month the entire remote keyboard is presented. The keyboard is powered by a rechargeable battery, and has provision for hardwire operation as well as infrared operation.

The heart of the remote keyboard is IC1, an MM57499 serial keyboard interface. This chip scans a 96 key keyboard and outputs ASCII data serially. This chip has many functions built in, and the reader is referred to the National Semiconductor applications notes for further details.

The clock input for the keyboard interface is obtained from the three gate oscillator formed by IC3a, IC3b and IC3c. This oscillator is designed to run at a frequency of 895kHz and trimpot VR1

is included to trim the frequency to this value.

IC2, an 8-bit parallel out shift register is used to display the status word generated by the keyboard encoder. This feature could be omitted if desired. D1, the 100kΩ resistor and the 0.1μF capacitor form a power on reset network.

The serial data appears at pin 24 of the MM57499. Transistor Q2 drives the optocoupler IC4, which provides isolation between the keyboard and the computer when the two are connected directly.

The data is also used to modulate the infrared transmitter, published in March. The only difference between the circuit presented in March and this one is the network containing D20, D21, the 100kΩ resistor and the 1μF capacitor. This network provides a turn on delay to the 100kHz oscillator to prevent the turn


on glitch produced by the MM57499 being transmitted.

The power supply for the remote keyboard is based around 4 C-sized Nicad cells. These are connected via a fuse and an on/off switch to the circuitry. No regulation is required since all ICs are MOS types. Q1 and associated components form a "battery OK" indicator. The voltage level at which the LED extinguishes can be adjusted by means of trimpot VR2.

The prototype used a Jameco 62 key keyboard — those keys that are not required are simply left open circuit. The keyboard and electronics were housed in a sloping front keyboard case, with the infrared LEDs mounted along the top edge, so that as much of the LED body as possible is protruding through the case.

A. Sinton,
Taupo, New Zealand.

\$30

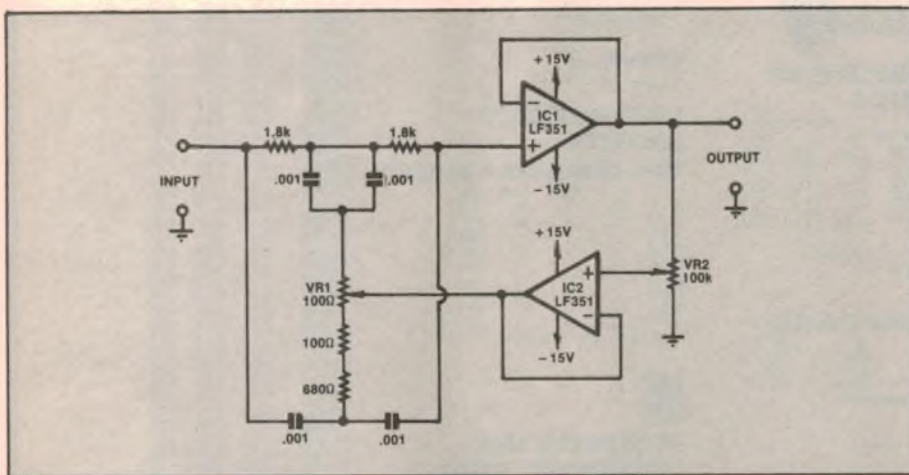

88kHz notch filter for CD players

This notch filter was developed in the EA lab for use when testing compact disc players which use the oversampling technique. These machines have a residual output signal at 88.2kHz which, although well out of the audio band, masks the noise and distortion signals, making them unmeasurable.

The filter is used between the CD player output and the input of the distortion measuring equipment. There are two controls to be adjusted: VR1, which allows the notch to be tuned over a small range; and VR2, which allows


the Q of the circuit to be set.

The circuit is a standard active twin-T filter with component values selected such that the notch is centred at the desired frequency. Ideally, close tolerance components should be used in the circuit.

Total harmonic distortion of the circuit is around .005% at 1kHz and 2V RMS, remaining below .01% right up to 80kHz. While this is not sufficiently low to enable definitive measurements of CD player distortion, the circuit does allow signal-to-noise ratio and separation between channels to be determined.

A. Levido,
Electronics Australia.

Hee-haw siren using piezo buzzer

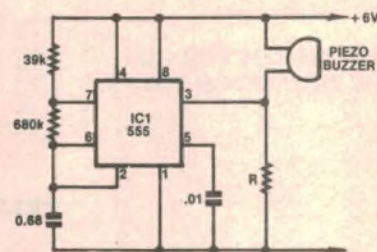


Most small piezoelectric buzzers change pitch and intensity with supply voltage, and hence current. This can be put to good effect to produce a simple hee-haw siren sound, either as an alarm or for model use.

A 555 timer wired as an astable is used to pulse the buzzer in the normal way as shown in the circuit diagram. The difference here is that resistor R is added to bleed a small current through the buzzer when it would otherwise be silent. A suggested starting value for R is 39Ω, but this may need to be varied somewhat in individual cases. Alternatively, a 6.3V 150mA pilot lamp could replace R to give a visual backup to the sound effect.

Using the components shown, the pulse rate frequency of the 555 is 1.5Hz.

D. Bolton,
Mt Waverley, Vic.

\$15

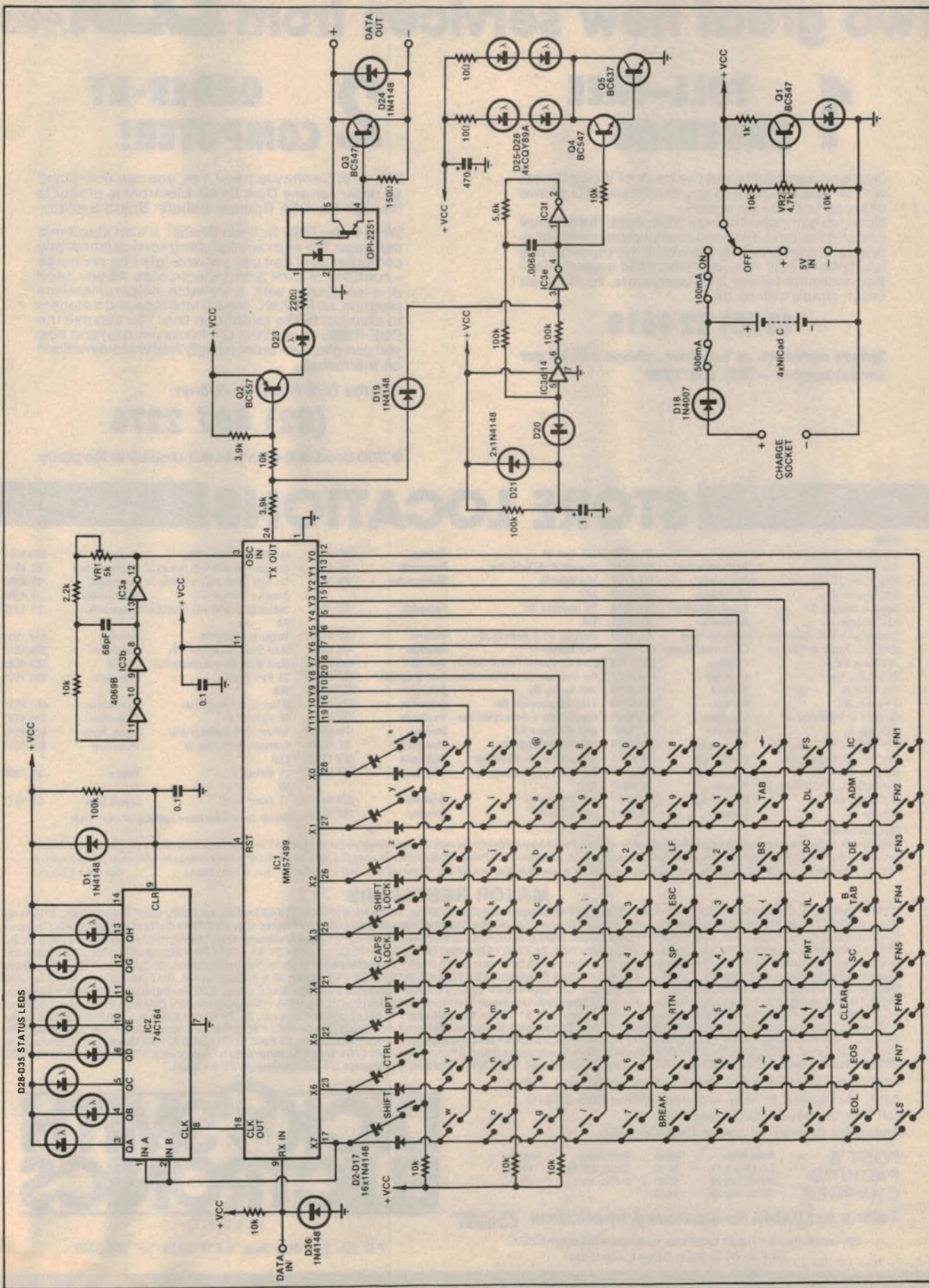

Two great new services from **DSX** PRESS

1 TOLL-FREE ORDERING

Just because you're out the back of Woop Woop, why should you have to pay exorbitant STD phone charges to place an order? Now you can order through DSXpress: the original and still the best electronics mail order supplier in Australia (and probably the world!) for the price of a local phone call. Yes, we've installed a special toll-free orderline for our STD customers. To place an order, simply call us on

(008) 22 6610

Sydney customers or enquiries, please call on our normal number - (02) 888 3200

2 ORDER-BY COMPUTER!

The 21st Century is here! Yes, you can now place an order for any Dick Smith Electronics products through the DSE Remote Bulletin Board System.

What is the DSE Bulletin Board? It's an electronic message, file and data handling service which any computer user can use - absolutely free of charge - courtesy of Dick Smith Electronics. All you need is a computer with a suitable communications program, an RS232C (serial) interface and a modem to connect to the telephone line. You can call the DSE RBBS at any time (24 hours per day) and now you can place an order (simply follow the directions on the menu).

Call the DSE RBBS on Sydney

(02) 887 2276

● 300 baud ● 8 data bits ● 1 stop bit ● No parity

STORE LOCATIONS

NSW

Cnr Swift & Young Sts.
T55 Terrace Level
Shop 1, 65-75 Main St
613 Princess Hwy
Oxford & Adelaide Sts
531 Pittwater Rd
Campbelltown Mall, Queen St
Shop 235, Archer St Entrance
147 Hume Hwy
162 Pacific Hwy
315 Mann St
4 Florence St
Elizabeth Dr & Bathurst St
450 High St
173 Maitland Rd, Tighes Hill
Lane Cove & Waterloo Rds
George & Smith Sts
The Gateway, High & Henry Sts
818 George St
6 Bridge St

Albury 21 8399
Bankstown Sq. 707 4888
Blacktown 671 7722
Blakehurst 546 7744
Bondi Junction 387 1444
Brookvale 93 0441
Campbelltown 27 2199
Chatswood Chase 411 1955
Chullara 642 8922
Gore Hill 439 5311
Gosford 25 0235
Hornsby 477 6633
Liverpool 600 9888
Maitland 33 7866
Newcastle 61 1896
North Ryde 88 3855
Parramatta 689 2188
Penrith 32 3400
Railway Sq 211 3777
Sydney 27 5051

125 York St
Brisbane St & Kable Ave
263 Keira St
ACT
96 Gladstone St
VIC
Creswick Rd & Webster St
145 McCrae St
Shop 46, Box Hill Central, Main St
Cnr Hawthorn Rd & Nepean Hwy
260 Sydney Rd
1150 Mt Alexander Rd
Nepean Hwy & Ross Smith Ave
205 Melbourne Rd
291-293 Elizabeth St
Bridge Rd & The Boulevarde
Springvale & Dandenong Rds
QLD
293 Adelaide St
166 Logan Rd

Sydney 267 9111
Tamworth 66 1961
Wollongong 28 3800
Fyshwick 80 4944
Ballerat 31 5433
Bendigo 43 0388
Box Hill 890 0699
East Brighton 592 2366
Coburg 383 4455
Essendon 379 7444
Frankston 783 9144
Geelong 78 6766
Melbourne 67 8834
Richmond 428 1614
Springvale 547 0522
Brisbane 229 9377
Buranda 391 6233

Gympie & Hamilton Rds
Cnr Queen Elizabeth Dr & Bernard St
Cnr Gold Coast Hwy & Welch St
Bowen & Ruthven Sts
Ingham Rd & Cowley St West End
SA
Wright & Market Sts
Main South & Flagstaff Rds
Main North Rd & Darlington St
24 Park Terrace
WA
Wharf St & Albany Hwy
66 Adelaide St
William St & Robinson Ave
Centreway Acde, Hay St
TAS
25 Barrack St
NT
17 Stuart Hwy

Chermside 359 6255
Rockhampton 27 9644
Southport 32 9863
Toowoomba 38 4300
Townsville 72 5722
Adelaide 212 1962
Darlington 298 8977
Enfield 260 6088
Salisbury 281 1593
Cannington 451 8666
Fremantle 335 9733
North Perth 328 6944
Perth City 321 6357
Hobart 31 0800
Stuart Park 81 1977

Watch for a new store opening in your area!

Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days, or unforeseen circumstances might hold up shipments so that advertised lines are not in the stores by the time the advert appears. And very occasionally, an error might slip through our checks and appear in the advert (after all, we're human too!) Please don't blame the store manager or staff, they cannot solve a dock strike on the other side of the world, nor fix an error that's appeared in print. If you're about to drive across town to pick up an advertised line, why not play it safe and give them a call first, just in case! Thanks. Dick Smith Electronics

MAJOR RESELLERS


NSW: • **Ballina:** A. Cummings & Co. 91-93 River St 86 2284 • **Bathurst:** Electronic Shop, 74 Bentick Street, 31 4421 • **Bowral:** Barry Gash Electronics, 370 Bong Bong St 61 2577 • **Broken Hill:** Hobbies & Electronics, 37 Oxide St 88 4098 • **Charlestown:** Newtronics 131 Pacific Hwy 43 9600 • **Coffs Harbour:** Coffs Harbour Electronics, 3 Coffs Plaza, Park Ave. 52 5684 • **Deniliquin:** Deni Electronics, 220 Cressy St, 81 3672 • **East Maitland:** East Maitland Electronics, 99 High St, 33 7327 • **Gosford:** Tomorrows Electronics & HiFi, 68 William St, 24 7246 • **Lismore:** Decro 3A/6-18 Carrington St, 21 4137 • **Port Macquarie:** Hall of Electronics, Horton Centre, Horton St, 83 7440 • **Orange:** Fyfe Electronics 173 Summer St, 62 6491 • **Tweed Heads:** Stuarts Electronic Sales, Sh 3, 4 Stuart St. • **Swansea:** Swansea Electronics, 184 High St, 71 1674 • **Wagga:** Phillips Electronics 82 Forsyth St, 21 6558 • **Windsor:** M & E Electronics, Sh 7, Mc Ewans Arcade, 206 George St, 77 5935 • **VIC:** • **Hamilton:** John Thompson & Co, 138-148 Gray St, 72 2000 • **Echuca:** Webster Electronics, 220 Packeham St 82 2956 • **Mildura:** McWilliams Electronics 110A Langtree Ave, 23 6410 • **Morwell:** Morewell Electronics, 95 George St, 34 6133 • **Shepparton:** GV Electronics Centre 100 High St, 21 8866 • **QLD:** • **Atherton:** Maatens Music Centre 55 Main St, 91 1208 • **Bundaberg:** PM Electronics, Takalvan St, 72 8272 • **Cairns:** Electronic World Shop 27 K-mart Westcourt Plaza, 518 555 • **Gladstone:** Purely Electronics Shop Cnr Hebert & Auckland Sts 72 4321 • **Mackay:** Stevens Electronics, 42 Victoria St, 51 1723 • **Maryborough:** Keller Electronics, 218 Adelaide St, 21 4559 • **Rockhampton:** Purely Electronics, 15 East St, 21 058 • **SA:** • **Mt Gambier:** Hutchessons Communications, 5 Elizabeth St, 25 6404 • **Whyalla:** Eyre Electronics Shop 2 Forsythe St, 45 4764 • **WA:** • **Albany:** Micro Electronics 133 Lockyer Ave 41 3432 • **TAS:** • **Launceston:** Advanced Electronics 5A The Quadrant, 34 1399 • **NT:** • **Darwin:** Ventronics 24-26 Kavanagh St, 81 3491

DSXpress Order Service Order with your Bankcard, Mastercard or Viscard. Just phone 008 22610 toll free for fast 24 hour despatch!
Enquiries: By mail, or phone (02)888 3200.

POST & PACKING CHARGES

Order Value	Charge	Order Value	Charge
\$ 5.00-\$ 9.99	\$2.00	\$50.00-\$99.99	\$6.00
\$10.00-\$24.99	\$3.50	\$100 or more	\$8.00
\$25.00-\$49.99	\$4.50		

Terms available to approved applicants

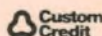

SA Customers: Credit facilities available through C.C.C.
722 King William Street, Adelaide



PTY LTD

P.O. Box 321, North Ryde, N.S.W. 2113. Tel: 888 3200

Circuit & Design Ideas

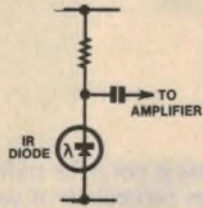


Fig. 1

Infrared diode amplifier

A problem which often occurs with modulated infrared beam systems is that of detector diode saturation under conditions of high ambient light. Saturation of the diode results in poor gain. Any attempt to reduce the effect by lowering the value of the series resistor results in decreased sensitivity to the wanted signal. This problem is basically a result of the simple bias system that is usually used (Fig. 1).

Some years ago, the front end stage shown in Fig. 2 was designed for a VDU optical touch pad system. The system had to cope with a wide variation in ambient light conditions, including indirect sunlight and fluorescent lighting. The beam was modulated at 3kHz.

The diode is reverse biased at 3V by

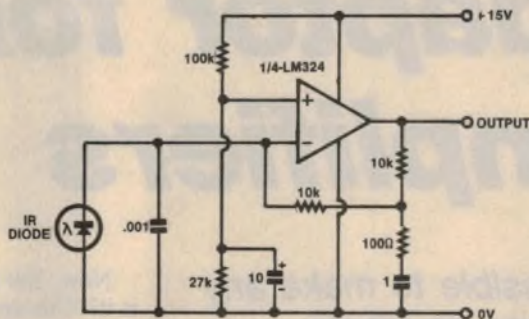


Fig. 2

100kΩ and 27kΩ resistors in conjunction with the two 10kΩ feedback resistors. The two 10kΩ resistors provide current feedback under high ambient light conditions, providing the high dynamic range of the unit.

Frequency response of the amplifier is set by the 100Ω resistor and 1µF capacitor which roll off the response below 1kHz. This gives a reasonable degree of attenuation at 50Hz and 100Hz, which is necessary to avoid interference from room lighting. The amplifier has maximum gain at about 5kHz, just above the modulating frequency. High frequency rolloff is determined by the natural response of the op amp.

The .001µF capacitor provides protection from RF interference while the 10µF capacitor attenuates supply noise at the bias divider.


G. R. Grey,
Christchurch, NZ.

\$20

CRO adaptor for RMS measurements

A simple voltage divider adaptor can be used to allow a CRO to indicate directly the RMS value of a sine wave input. It consists simply of an appropriate value resistor in series with the input resistance of the CRO.

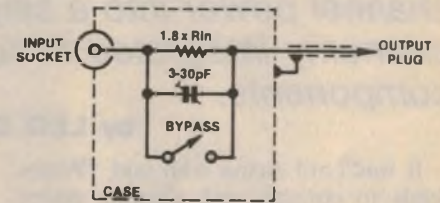In the case of the usual 1MΩ input impedance, a 1.8MΩ resistor is used in parallel with a 3-30pF trimmer capacitor. A bypass switch could be included to restore the peak-to-peak reading when necessary. For CROs with R_{in} other than 1MΩ, simply use a total adaptor resistance of $1.8 \times R_{in}$.



The components should be mounted in a small earthed metal case and the output brought out on a short length of coax fitted with the appropriate plug. The input is terminated on a suitable socket mounted on the case.

The trimmer capacitor should be adjusted, with a square wave input to the adaptor, to restore the "squareness" of the signal. Once set for a particular CRO, it should need no further adjustment. Since many CROs have a vertical calibration accuracy of not better than 10%, resistors of 5% tolerance should suffice for most applications.

D. Bolton,
Mt Waverley, Vic.

\$10




SOLAREX



PO BOX 204 Chester Hill 2162 NSW
Phone 644 5055

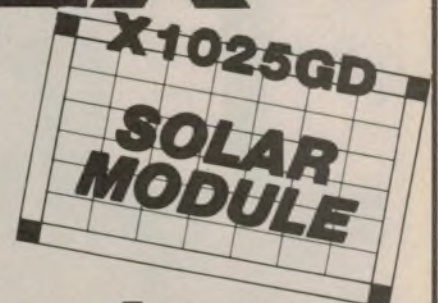9.2 watts .6 amp 14 volts

Marine quality go anywhere top \$ for watt
value plus our standard 5yr warranty
dim 456mm x 300mm wt 2.4kg



ONLY \$220

For those who seek more power

Bridge adaptor for stereo amplifiers

With this simple circuit it is possible to make any stereo amplifier deliver four times its single channel power into a single load. It uses just one economy integrated circuit and a few other components.


by LEO SIMPSON

It was Lord Acton who said, "Power tends to corrupt, and absolute power corrupts absolutely. Great men are almost always bad men". However, since he lived last century, he couldn't have been thinking of audio power. As far as the average audio enthusiast is concerned, "Power is good and more power is better". The only way in which corruption may enter is if you scheme and rob to get it. If you are a power hungry audiophile, it is not necessary to be a tea-leaf to get it. Many of us have stereo amplifiers which we don't use any longer. We may have bought a new system and the old amp has been

relegated to the storeroom.


Often those older amplifiers have little wrong with them, particularly as far as the power amplifiers are concerned. They may have nois phono inputs, the volume control may be scratchy or the whole unit may look on the dowdy side. But if the amplifier has a rating of, say, 50 watts per channel (into 8-ohm loads), it is not to be overlooked. Fifty watts is not such a large rating these days but by adding this simple circuit we are about to present, it could be turned into a powerful mono amplifier capable of delivering 200 watts into an 8-ohm loudspeaker.

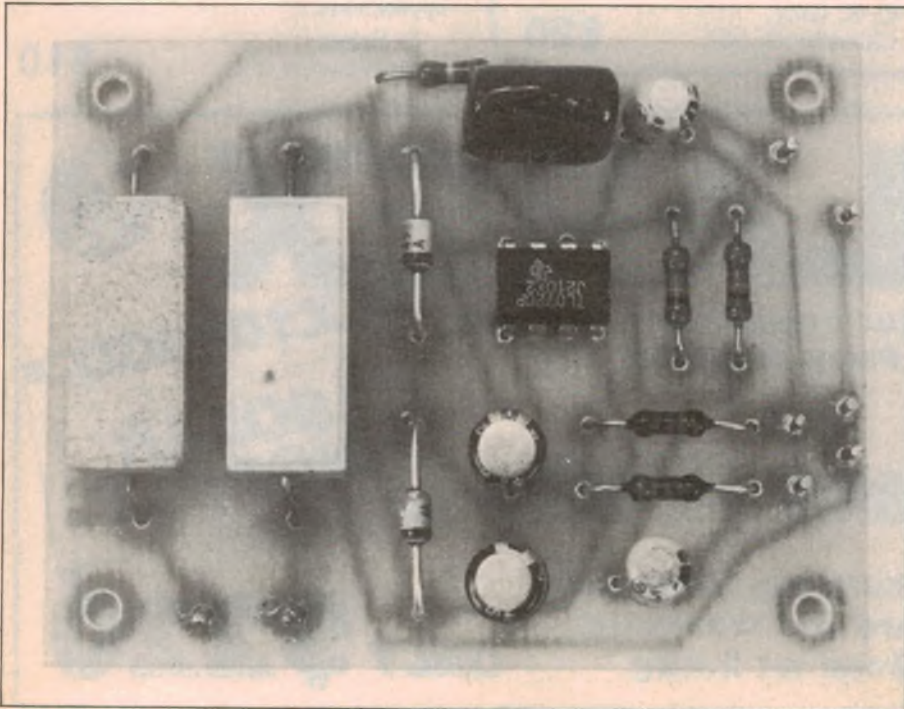Below is a larger than lifesize photo of the assembled PC board.



Now, 200 watts is not to be sniffed at, is it? This applies particularly if you are an impecunious type. Two hundred watt amplifiers are not cheap.

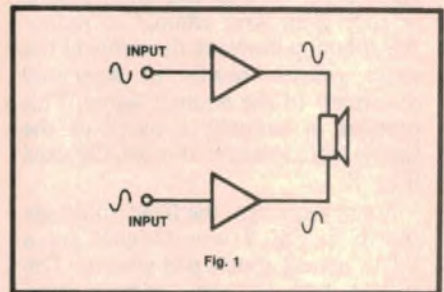The way to get this high power is to connect both channels of the amplifier so that they both drive the loudspeaker, in push-pull. In other words, the loudspeaker is connected across the active outputs of the two amplifiers, with no connection to ground. Fig.1 shows the general concept.



In the normal course of events, if two amplifiers were connected in this way and both were fed the same input signal, virtually no sound would be heard in the loudspeaker. Any sound heard from the loudspeaker would represent the slight difference in gains between the two power amplifiers. If the two power amplifiers were absolutely identical in every respect, ie, in gain, frequency response, phase response, distortion and so on, then absolutely nothing would be heard from the loudspeaker.

But if we were to feed one power amplifier with a signal which was identical to the signal in the other channel but reversed in phase, we would get an entirely different result. Each amplifier would work in the way it was intended, delivering a substantial signal from its output terminal. If we examined each output with an oscilloscope we would find the same signal at each end of the loudspeaker, which is not surprising.

If we then were to measure the signal applied across the loudspeaker, we would find that it would be the sum of the amplifier outputs. So if each amplifier was delivering 20 volts RMS, the voltage for 50 watts into an 8-ohm load, we

would find a total of 40 volts across the loudspeaker. And by doubling the voltage, we get four times the power! All that, just by reversing the phase of one channel. Two hundred watts!


This concept is called "bridged mode" and power amplifiers operated in this way are said to be "bridged".

Well, the concept is great as far as you, the power hungry audiophile is concerned, but what does it mean to the amplifier? Is it going to be quite happy doing far more than you ever thought possible? You could say, "Who cares?" After all, it is not a beast of burden. It is inanimate. But there are ramifications which we should consider.

Think about what happens when each power amplifier drives the loudspeaker. If it delivers eight volts RMS to an 8-ohm loudspeaker in the normal course of events, we would expect one ampere of current to flow. But since there is an amplifier at the other end of the speaker also applying eight volts, the resultant current is two amps. So as far as each amplifier is concerned, it does not "see" an 8-ohm loudspeaker; it "sees" a 4-ohm loudspeaker. Hmm. For a given output voltage, twice the current flows. That is why we get twice as much power from each amplifier.

What this means is that we cannot extend the concept indefinitely. We cannot look at the ratings and say, "Ahah, this amplifier gives, say, 90 watts, into 4-ohms, with both channels driven, therefore I can get 360 watts in bridge mode". That isn't possible, unless the amplifier can safely handle 2-ohm loads at full power. That is what it would be required to do. Many amplifiers would blow their output transistors under this treatment and even the most rugged could be expected to blow their fuses.

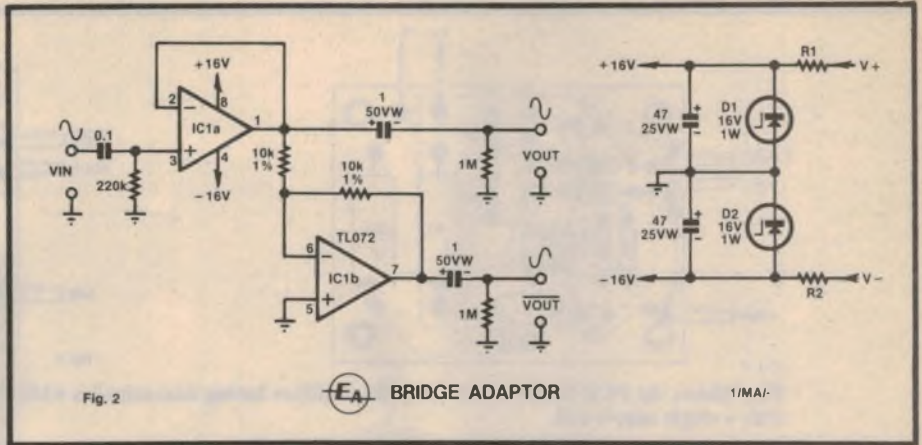There is another proviso too. Since each power amplifier driving an 8-ohm loudspeaker in bridge mode sees a 4-ohm load, a more accurate guide to the power we can expect is provided by the 4-ohm ratings. Most amplifiers are not able to deliver twice the power you expect into 8-ohms. For example, if an amplifier is



IC1a is a non-inverting voltage follower while IC1b functions as a unity gain inverter.

Specifications

Input impedance	220kΩ
Output impedance	< 1kΩ
Gain	unity
Maximum input and output	> 8V RMS
Frequency response	10Hz to 300kHz ±1dB
Harmonic Distortion	< .001% @ 8V RMS
Signal/noise ratio	-104dB with respect to 1V RMS and with 1kΩ source impedance

rated to deliver 50 watts into 8-ohms, it might only deliver 90 or less watts into 4-ohm loads. This is because of inevitable losses in the power stages themselves and less than perfect regulation in the amplifier's power supplies. (Many amplifiers have fairly poorly regulated power supplies and so they do not deliver much more power into 4-ohm loads than they do into 8-ohm loads.)


Such a stereo amplifier (delivering 90 watts into a 4-ohm load) can only be expected to deliver 180 watts into an 8-ohm load when operating in the bridged mode. Still, while it is not the full 200 watts it is still a very worthwhile increase. And the power capability on musical peaks can be expected to be a little above the continuous power. So a closer guide to the full power output of a stereo amplifier in bridge mode, into

8-ohm loads, is "double the rated power output into 4-ohm loads".

The circuit

Now let us have a look at the circuit of the Bridge Adaptor in Fig.2. It really is dead simple; just a pair of op amps in a single IC package. We used a TL072 dual Fet-input op amp which has good noise and distortion performance, and is cheap and readily available.

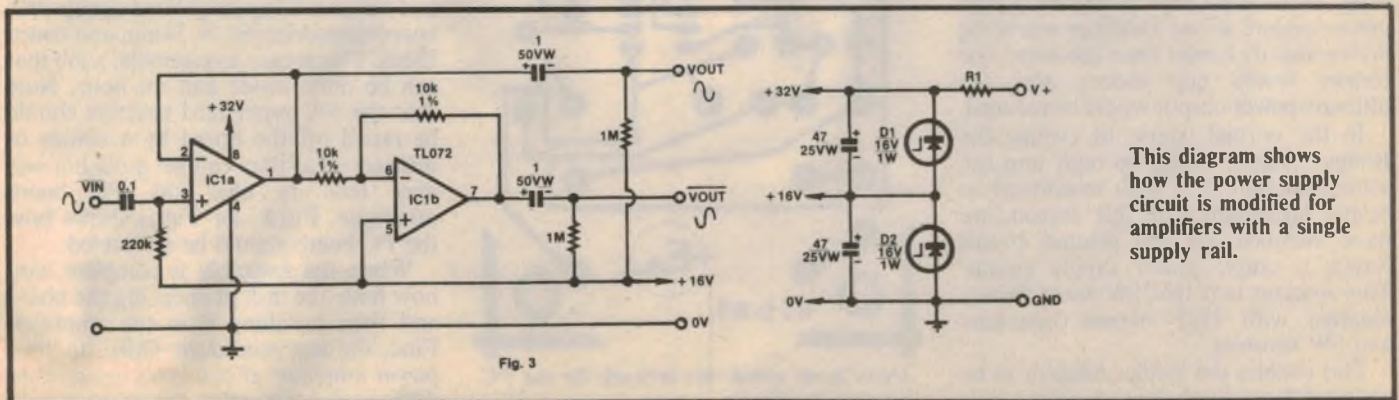The first op amp, IC1a, is connected as a non-inverting voltage follower stage. Since it has its output connected directly to its inverting input, it has 100% negative feedback applied around it. This results in the op amp having unity gain which is why it is called a "voltage follower"; any input signal is reproduced exactly at the output. IC1a also has a very low output impedance as a result of



This diagram shows how the power supply circuit is modified for amplifiers with a single supply rail.

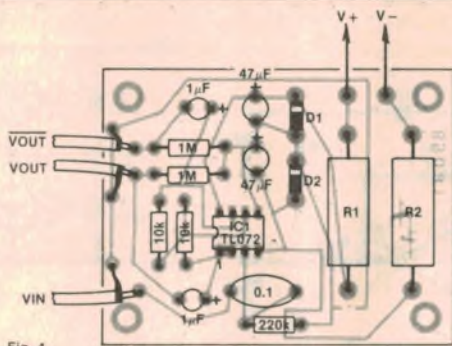


Fig. 4

Fig.4 shows the PCB layout to be used with amplifiers having dual supplies while Fig.5 shows the layout for amplifiers with a single supply rail.

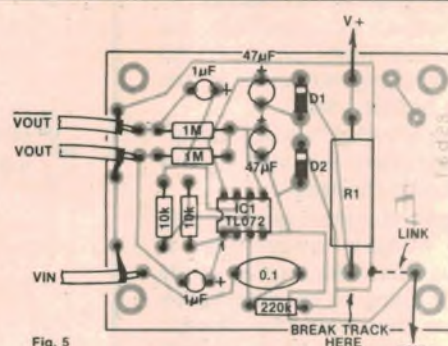


Fig. 5

Bridge adaptor

the 100% feedback, and a high input impedance, which is set by the 220kΩ resistor at pin 3. This means that it performs well as a buffer stage.

The output of IC1a is fed in two directions. The first is to one of the circuit outputs, via a 1μF capacitor. The other is to the input of IC1b. This op amp is set up as a unity gain inverter, so that its output signal will have exactly the same amplitude as the input but reversed in phase by 180°.

We have used relatively low value input and feedback resistors (10kΩ) for IC1b, to ensure low noise output. After all, we want the Bridge Adaptor to have as low a noise and distortion output as possible, to avoid degrading the performance of the amplifiers as much as possible. The accompanying specification panel shows that we have achieved that aim.

Note also that we have specified 1% tolerance resistors for IC1b. This is to ensure that the gain of this stage is as close to unity as possible. The reasoning behind this is to make sure that the amplitudes of the two output signals from the Bridge Adaptor are almost exactly equal. This ensures that the following power amplifiers "see" the same load value and will ultimately "clip" at the same time, giving maximum power output. If one amplifier was to be driven slightly harder than the other, the former would clip sooner and the ultimate power output would be reduced.

In the normal course of events, the Bridge Adaptor would be built into the stereo amplifier you wish to convert to bridge operation. For this reason, we have included, on the printed circuit board, a simple power supply circuit. This employs two 16V/1W zener diodes, together with 47μF bypass capacitors and 5W resistors.

This enables the Bridge Adaptor to be powered from the balanced supply rails

TABLE 1

Dual supplies


Voltage range	R1, R2
20 to 45V	470Ω/5W
45 to 72V	1.2kΩ/5W
70 to 100V	5.6kΩ/5W

Single supply

Voltage range	R1
40 to 60V	470Ω/5W

of most solid-state amplifiers. It will be necessary to select the zener feed resistors to suit the amplifier supply rails. Table 1 shows values and power ratings for a range of supply voltages.

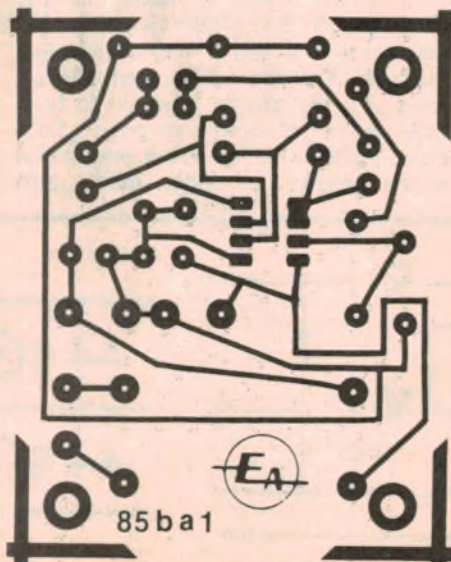If the stereo amplifier proposed for conversion has output coupling capacitors and therefore a single supply rail, it will be necessary to modify the power supply circuit, as shown in Fig.3. This involves the use of a single feed



Above is an actual size artwork for the PC board (code 85ba1).

resistor and connection of the negative supply point to the printed circuit board earth connection. It will also be necessary to modify the printed circuit layout slightly, as shown in Fig.5.

Before you can construct the Bridge Adaptor, you will have to discover what are the voltages of the main DC supply rails in your amplifier. If you have the amplifier service manual, this is easy. Look at the circuit of the power amplifiers and check the value of the supplies feeding the power output stages. These are usually the highest DC voltages within the unit. That done, check the recommended value of feed resistors in Table 1, and you can start construction.

If you don't have access to the amplifier's service manual, you will have to measure the supply rails. You will need a multimeter switched to the 100V DC range. Now check the voltages across the main electrolytic filter capacitors. These will usually have a value of 1000μF or considerably more, in most cases. And be careful now when measuring the two supply rails. Remember that one will be reversed in polarity to the other and it will be necessary to reverse the leads to your multimeter when measuring the negative supply rail.

Construction

As noted above, the Bridge Adaptor is laid out on a compact printed circuit (PC) board measuring 69 × 54mm and coded 85ba1. This is easy to assemble, a job that can be done inside half an hour. Note that the 5W zener feed resistors should be raised off the board by a couple of millimetres as they can get quite hot and may tend to char the PC board otherwise. Fig.4 (or Fig.5) shows how the PC board should be assembled.

When the assembly is complete, you now have the task of checking the board and then installing it in the amplifier. First, the test procedure: Open up your power amplifier, if you have not already done so, and identify the main supply

filter capacitors. You will have to run the supply leads to the Bridge Adaptor directly from these filter capacitors. Do not run the supply leads from the main output transistor collectors of the power amplifiers. That would be asking for trouble and may result in unstable amplifier operation.

Temporarily run positive and negative supply leads from the stereo amplifier to the Bridge Adaptor. You will need an earth lead too. This can be run from one of the power amplifier input earths.

Now turn on the power and measure the voltages across the two zener diodes. They both should be within $\pm 0.5V$ of 16V. Check also that the 16V supplies are present at the IC: +16V at pin 8 and -16V at pin 4. Now check that the output voltage of each op amp is very close to zero, ie, pin 1 and pin 7 should be no more than +100mV DC.

Now you have to select a position

PARTS LIST

- 1 PC board, 69 x 54mm, coded 85ba1
- 1 TL072, LF352 dual Fet-input op amp IC
- 2 16V/1W zener diodes
- 1 0.1 μ F/100VW metallised polyester capacitor (greencap)
- 2 1 μ F/50VW PC-mounting electrolytic capacitors
- 2 47 μ F/25VW PC-mounting electrolytic capacitors

Resistors

2 x 1M Ω , 2 x 220k Ω , 2 x 10k Ω 1%, 2 x 1.2k Ω /5W wirewound or as selected from Table 1 (see text)

Miscellaneous

8 PC pins, PC board mounting hardware, hook-up wire, shielded cable, RCA panel-mount socket (optional)

within the stereo amplifier to install the Bridge Amplifier board. It should be kept away from the amplifier output stages and the power transformer. At the same time, do not place its input and output leads too close to sensitive phono input stages. Within all these restraints, it should be possible to find a suitable spot. If not, it may be worthwhile to consider installing the Bridge Adaptor inside a metal or plastic box on the rear panel of the amplifier.

When you have mounted the PC board in position in the amplifier, you can run the supply leads mentioned earlier. Do not run a separate earth lead as this function will be performed by one of the shielded cables carrying the output signal. Note that it will be necessary to disconnect the existing power amplifier inputs.

Electronics is going digital.

This book can help YOU go right along with it:

Electronic equipment now plays an important role in almost every field of human endeavour and every day, more and more electronic equipment is "going digital".


Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and *An Introduction to Digital Electronics* can give you that grounding. Tens of thousands of people — engineers, technicians, students and hobbyists — have used the previous editions of this book to find out what the digital revolution is all about.

The new fourth edition has been updated and expanded, to make it of even greater value.

You don't need any previous knowledge of digital electronics — the book starts you right from scratch, and covers all the basic concepts you need.

PRICE **\$4.50**

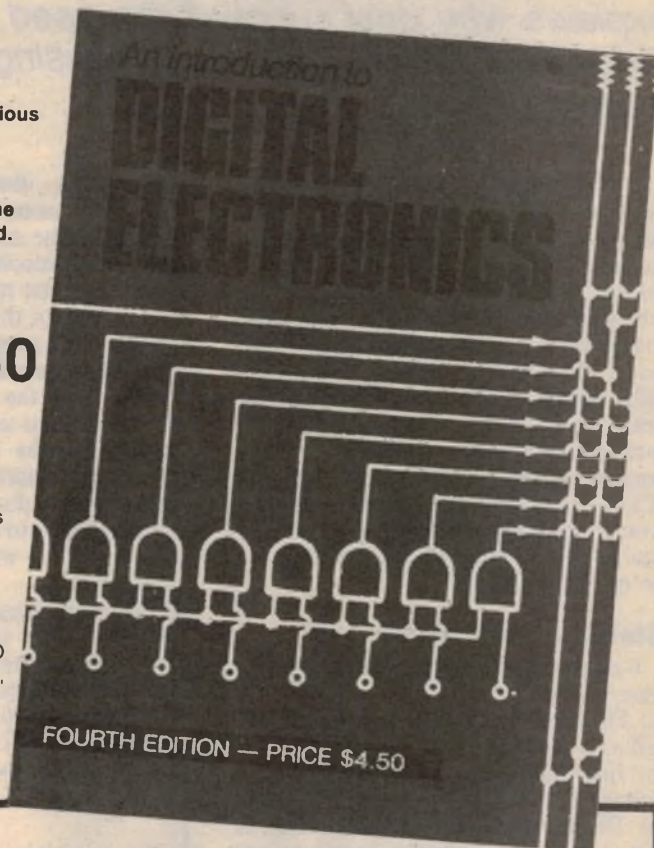
Available from "Electronics Australia", 140 Joynton Avenue, Waterloo, Sydney, 2017, PRICE \$4.50. Or by mail order: Send cheque to "Electronics Australia", PO Box 227, Waterloo, 2017, PRICE \$5.40.



Here are the chapter headings:

- | | |
|--------------------------------|------------------------------|
| 1. Signals, circuits and logic | 12. Basic readout devices |
| 2. Basic logic elements | 13. Multiplexing |
| 3. Logic circuit "families" | 14. Binary arithmetic |
| 4. Logic convention and laws | 15. Arithmetic circuits |
| 5. Logic design: theory | 16. Timing & Control |
| 6. Logic design: practice | 17. Memory: RAMS |
| 7. Numbers, data & codes | 18. ROMs & PROMs |
| 8. The flipflop family | 19. CCD's & magnetic bubbles |
| 9. Flipflops in registers | 20. D-to-A Converters |
| 10. Flipflops in counters | 21. A-to-D Converters |
| 11. Encoding and decoding | Glossary of terms, Index |

OP AMPS Explained

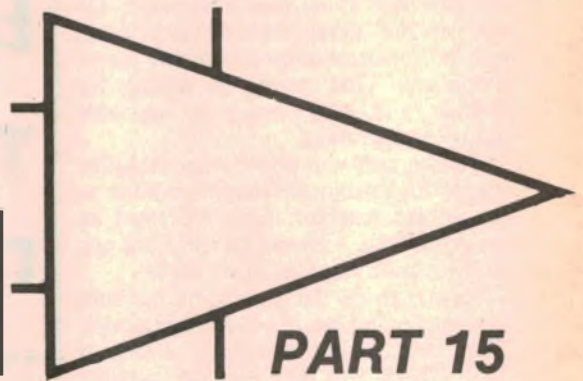

This chapter discusses the power supply requirements of operational amplifiers and explains why dual supplies are used. Also discussed are decoupling, bypassing and power supply rejection.

All operational amplifiers, being active circuits, need some form of power supply. Various names traditionally used include "supply", "power supply", "power source", "bus" and "rail", all of which mean exactly the same thing. The first three are obvious, but "bus" (from Latin "omnibus" = "for all") and "rail" refer directly to the conductor line we draw on circuit diagrams, for example marked +15V. Such conductors may connect power to many amplifier stages, ICs or transistors and "rail" is a hangover from valve days when a bare copper bar was used so that stages could be clipped on or off in testing.

Standard practices

Common drawing practices, to save time, include:

(a) Drawing the actual power supply, the rail and connections as Fig. 1(a).
 (b) Just drawing blocks, marked with a voltage, to indicate supply, as Fig. 1(b).
 (c) The drawing of only a straight line, as Fig. 1(c) to indicate the supply rail or bus, leaving the details of the necessary power supply itself somewhere in your imagination.

(d) Drawing nothing at all of the power system, on the assumption that you know that power supplies must exist and you will even be familiar with the correct pins of the IC for the connections. Fig. 1(d) illustrates this drawing shorthand practice, mostly reserved for integrated circuits, mostly reserved for integrated circuits. Many 8-pin linear ICs use pin 7 for positive supply and pin 4 for negative, but beware, this is by no means universal and you must check the data sheets if uncertain.

Fig. 1(b) illustrates an essential connection sometimes overlooked by beginners. The centre connection of the dual power supplies **must** be connected to the zero line and ground and also to the low side of the source voltage.

Each op amp design requires an appropriate supply voltage, taking into consideration the load to be driven and the components used. For example, if we want ± 5 volts output swing from a stage, any supply voltage somewhat higher would do, eg, ± 9 V, ± 12 V or ± 15 V. Which to choose? It's a matter of convenience, within the following constraints:

- Supply voltage usually must exceed required output voltage.
- Supply voltage must not exceed the op amp ratings. For example, for National's LM101A the supplies must not exceed ± 22 V. For the LM301A, the

limit is ± 18 V while for the Analog Devices 171K module op amp the limit is 150 volts.


(c) Every circuit has an absolute minimum supply voltage, below which operation is not guaranteed. For example contrast the older type 302 IC which required a supply greater than 12 volts with National's type LM4250 which will work happily on ± 1 V

Dual supplies

A question which has vexed electronic enthusiasts for years is "Do we really need dual voltage supplies to run our circuits?" And older enthusiasts may object that years ago they never used more than a single power supply for their valve circuits. So why now? Looking objectively at the question it boils down to this:

- Do you want your amplifier to be DC-coupled?
- If so, do you want input and output to swing across zero, ie, positive to negative and back?
- When input and output are both zero volts, do you simultaneously want low output impedance?

A "yes" to all three questions means that you must use dual supplies, one

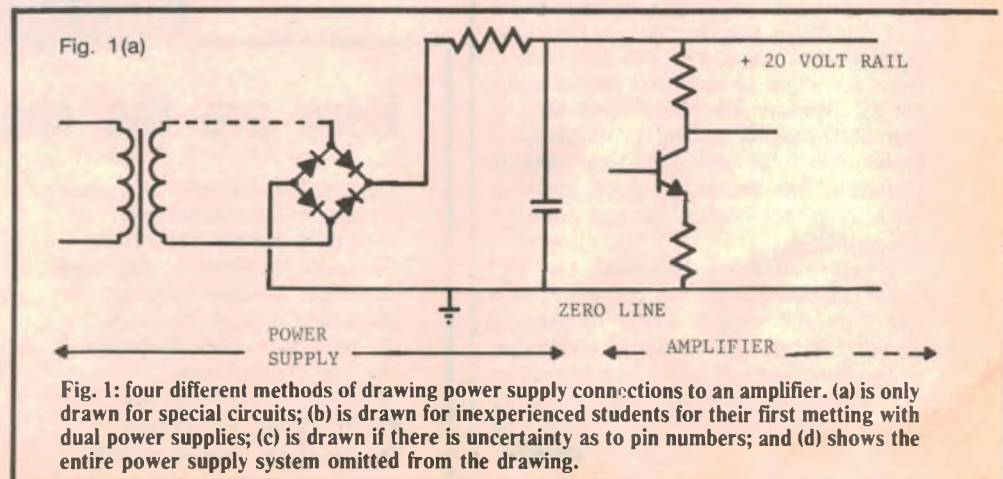

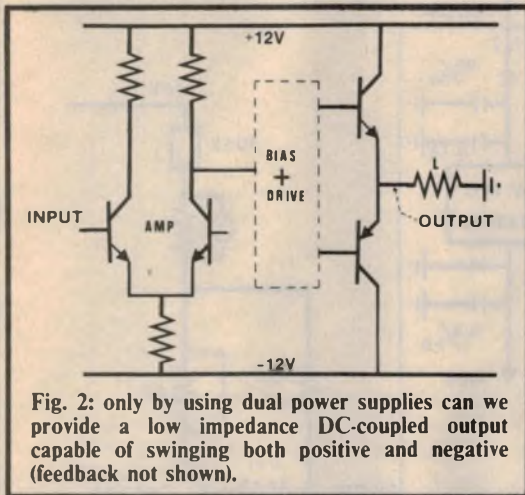


Fig. 2: only by using dual power supplies can we provide a low impedance DC-coupled output capable of swinging both positive and negative (feedback not shown).

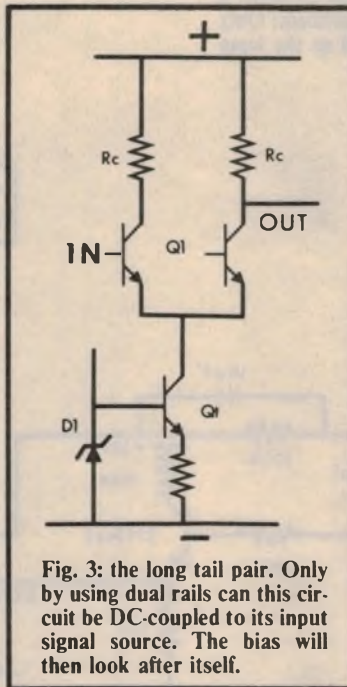


Fig. 3: the long tail pair. Only by using dual rails can this circuit be DC-coupled to its input signal source. The bias will then look after itself.

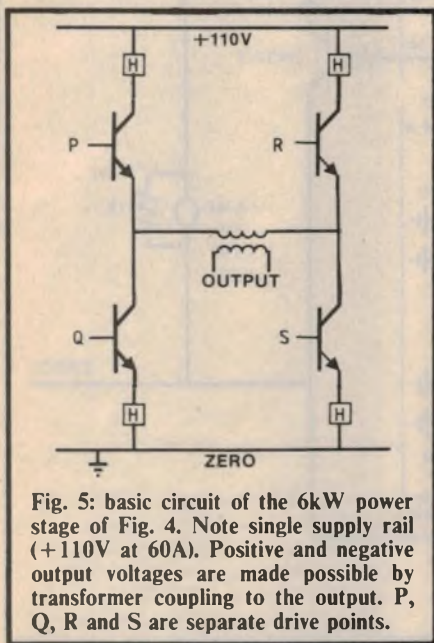


Fig. 5: basic circuit of the 6kW power stage of Fig. 4. Note single supply rail (+110V at 60A). Positive and negative output voltages are made possible by transformer coupling to the output. P, Q, R and S are separate drive points.

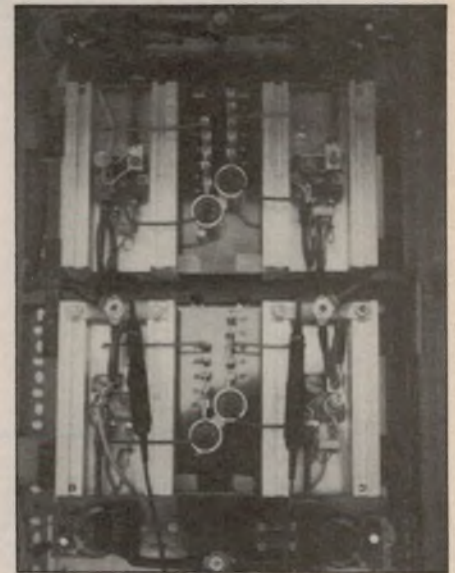


Fig. 4: this 6kW power output stage operates happily from a single power supply. Four NPN transistors are used, as shown in Fig. 5. (Photo courtesy P. Wolfs, Capricornia Institute, Rockhampton.)

necessary? Consider Fig. 2, a fundamental op amp circuit of an IC and its "innards" in a phase reversing or inverting op amp configuration. Only by using positive and negative supplies can this circuit fulfil each of the three conditions above.

We observe that:

- (1) The circuit is DC-coupled.
- (2) Input may be positive, zero or negative and always the output will obey the gain equation:

$V_{out} \text{ approx} = -(R_f/R_i) V_{in}$
 provided the voltage at pin 2 and the output pin 6 are within limits (always some margin within the supply rail voltages). Except for the class-B output transistors every NPN base is always considerably more positive than its emitter and less positive than its collector, so such transistors remain in linear conduction and have gain at all

times. The same applies for all PNPs, with reverse polarities of course. Therefore the open loop gain G remains high for all such inputs, including zero.

It follows that the closed loop gain T continues to obey the well known equation:

$$T = V_{out}/V_{in} = G/(1 + GH) = -(R_f/R_i)(G/(1 + G + (R_f/R_i)))$$

Furthermore, the system remains operating as a negative feedback amplifier meaning that the output impedance Z_o is given, as in earlier episodes of this tale, by the natural output impedance of emitter followers (perhaps 100Ω) divided by the feedback factor $(1 + GH)$. Now if $G = 100,000$ and $H = 1/10$ then:


$$T \text{ approx} = 10$$

$$Z_o = 100\Omega / (1 + (100,000(1/10))) = 10m\Omega$$

This low output impedance is valid

positive and one negative. They do not have to be the same voltage but they usually are for convenience.

Why is it so that twin supplies are

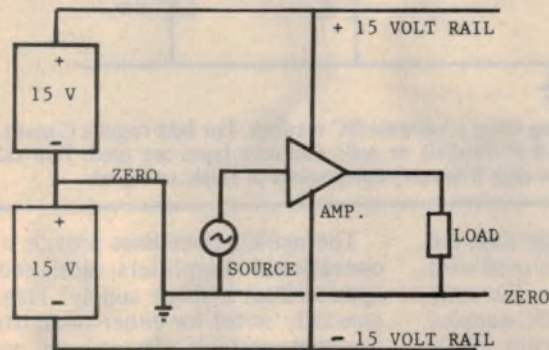

POWER SUPPLY
 Fig. 1(b) AMPLIFIER

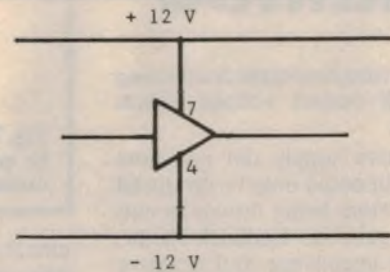


Fig. 1(c)


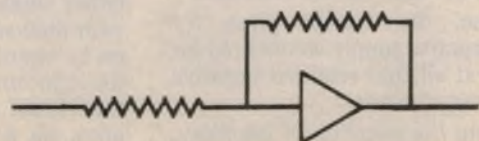


Fig. 1(d)

Fig. 6: this DC-coupled power op amp is used to drive a heating lamp for a high-precision scientific experiment. Only one 6V DC high-current power supply is used as the lamp does not require negative voltages.

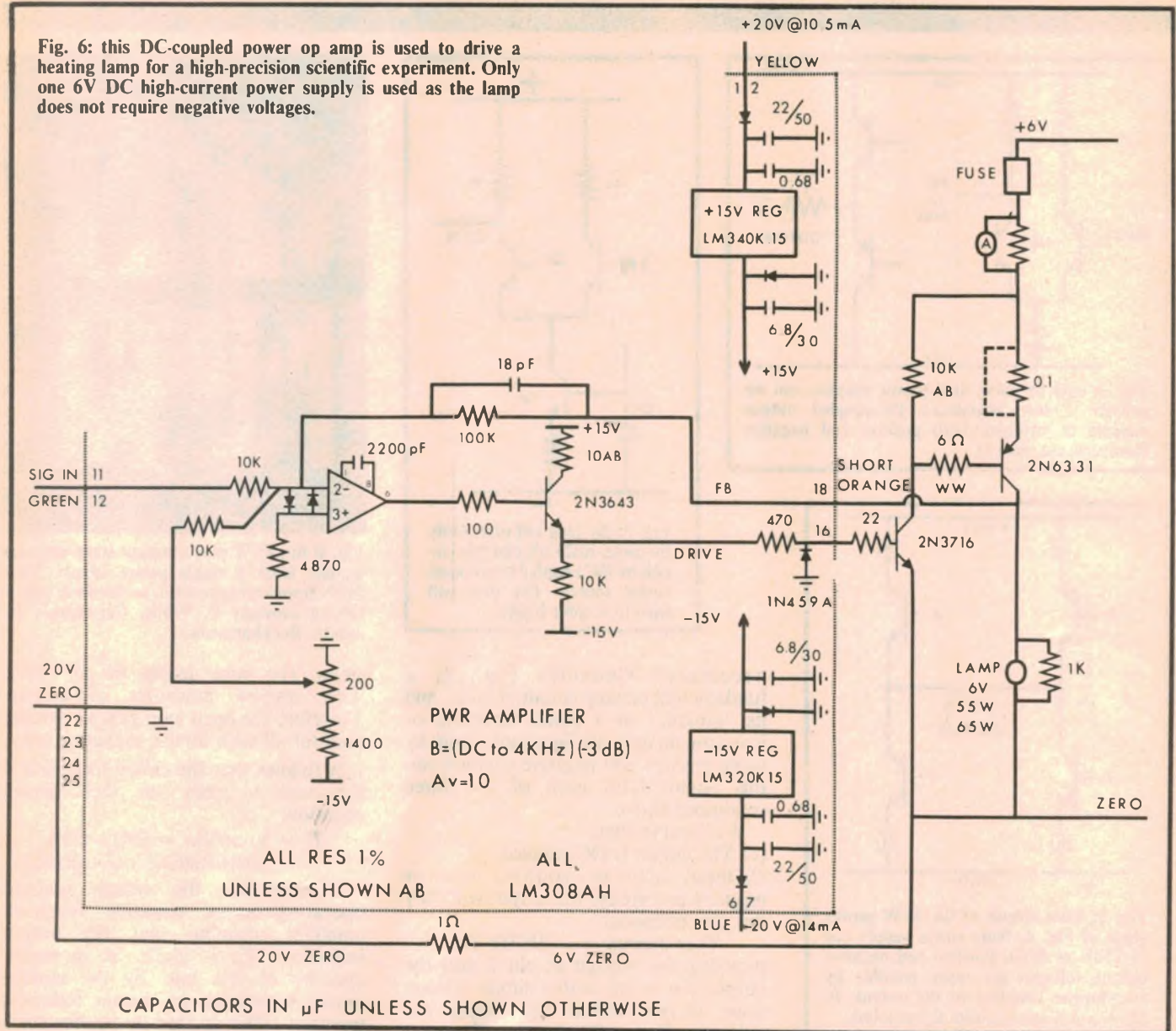


OP AMPS Explained

because all transistors remain conducting to produce all output voltage values including zero.

If the negative supply did not exist then zero output could only be produced by some transistors being driven to cut-off, hence no gain, no feedback factor, no low output impedance and negative voltage output could not be achieved.

Of course, the reasons given for needing a negative supply would hold for any circuit at all that required negative voltage output at times.

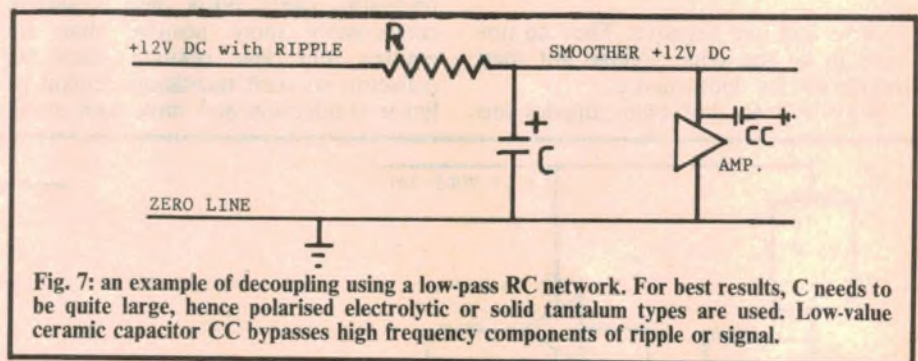Apart from the question of necessity, dual supplies allow wider choice of



circuit. For example the simple long tail pair depicted in Fig. 3, can be used with either single or dual supplies. But only with dual supplies can it be DC-coupled (at its input) to the outside world. While the input may swing positive or negative, the virtual earth point x automatically takes on a voltage level exactly "one junction voltage" below the input.

The market place does provide a few operational amplifiers designed to operate from a single supply. They are especially suited for either small battery operated portable devices, or mobile equipment working directly from your car's single 12 volt battery. Examples are Motorola's LM158-258-358 and LM2904.

WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ...


WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ... WOOD FOR CHIPS ...

NOW STOCKING PRODUCTS FROM OKI INDUSTRIES

IF YOU'RE INTO WIRE WRAP THEN TALK TO US!

Why Cut? Why Strip? Why Slit? Why Don't you JUST WRAP?

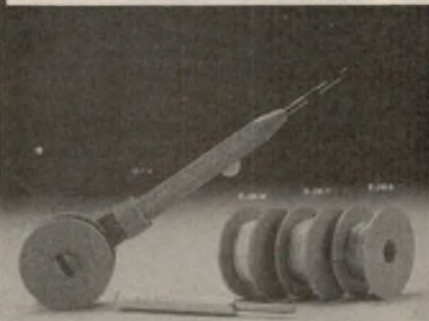A really handy little tool for 30AWG wire and 0.025" (0.63mm) square posts. Does daisy chains or point to point. No slitting, no stripping. Built-in cut off. And it's so easy to load the wire. The really convenient way to do your wrapping since it's all in the one tool **\$44.50**



Reels of wire to suit 50 feet. Blue, white, yellow or red. **\$4.25** a reel.

Hobbyist Wire Wrap Tool suits 30AWG wires and 0.025" posts. Wraps, strips and unwraps **\$23.75**.

OKI IC HANDLING EQUIPMENT

Are you wasting time and raising your blood pressure trying to force 40 mis-aligned IC pins into their respective holes simultaneously? Are you levering IC's out with a screwdriver and bending all the legs? Save time and do the job properly with OKI tools.



These tools are essential for CMOS and other sensitive IC's since they have provision for an earthing strap. Double



8.30 to 5 Monday to Friday, 8.30 to 12 Sat
Mail Orders add \$3.00 to cover postal charges.
Next day delivery in Sydney add \$5.00

All prices INCLUDE sales tax.
Tax exemption certificates accepted if line value exceeds \$10.00

OPEN FRAME, LOW PROFILE IC SOCKETS

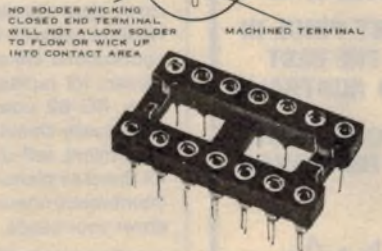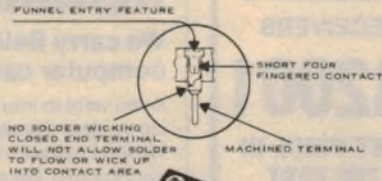

Highest quality glass filled polyester with MACHINED contacts. Four finger GOLD PLATED contact. Terminals are tin plated for easy soldering. Open frame ensures good cooling, easy cleaning and checking. Available in 8 to 40 pin configurations. 8 pin **\$6c**, 14 pin **98c**, 16 in **\$1.12**, 18 pin **\$1.26**, 20 pin **\$1.40**, 24 pin **\$1.68**, 28 pin **\$1.96**, 40 pin **\$2.80**.



SINGLE IN LINE SOCKETS AND ADAPTORS

SIP sockets feature four finger GOLD PLATED beryllium copper contacts with tin plated brass terminals. 20 pin strip can be easily snapped apart to form shorter lengths. Maintains spacing when mounted end to end or end to side. Socket strip **\$2.50**. Adaptor strip **\$2.00**.

chrome plated for good static dissipation. Heavy duty precision construction. Buy them individually or save a few bucks with the complete set -

MOS1416 14-16pin MOS. CMOS Safe Inserter features easy one-hand operation. **\$11.15**

MOS2428 24-28 pin MOS. CMOS Safe Inserter similar to MOS1416 **\$25.12**

MOS40 36-40 pin Safe Inserter. Also aligns bent pins. A twist of the handle and they all line up to the proper spacing. Then locate the tool over the socket, push the plunger for instant accurate insertion. **\$27.86**

EX-1 Extractor is ideal for hobbyist or lab use. One piece spring steel construction extracts all IC's from 8 to 40 pin. (No earth strap facility) **\$5.50**
EX-2 CMOS Safe Extractor for 28 to 40 pin IC's. Easy one-hand operation **\$27.86**.

If you use a lot of IC's get the complete kit of all five tools for **\$94.86** and save a few dollars

TRUE RMS



ONLY \$225.00 ex tax (\$258.75 inc tax)

• 4½ digits • 8 functions Vdc, Vac, Adc, Aac, Ohms, Audible Continuity, Diode test, Data Hold • 0.05% basic accuracy **EDM1346**

DC Voltage	
Range	• 200mV, 2V, 20V, 200V, 1000V
Resolution	• 10uV, 100uV, 1mV, 10mV, 100mV
Accuracy	• 200mV - 1000V ± (0.05%rdg + 3dgt)
AC Voltage: (True RMS AC coupled 10% to 100% of range)	
Range	• 200mV, 2V, 20V, 200V, 750V
Resolution	• 10uV, 100uV, 1mV, 10mV, 100mV
Accuracy	• 200mV - 200V @45Hz - 1KHz ± (0.5%rdg + 2dgt) @1KHz - 2KHz ± (1.2%rdg + 3dgt) @2KHz - 5KHz ± (5.0%rdg + 4dgt) (200V @2KHz - 5KHz not specified) 750V @45Hz - 1KHz ± (1.0%rdg + 2dgt)

DC Current	
Range	• 2mA, 20mA, 200mA, 2A, 10A
Resolution	• 100nA, 1uA, 10uA, 100uA, 1mA
Accuracy	• 2mA - 200mA ± (0.3%rdg + 3dgt) 2A - 10A ± (0.75%rdg + 3dgt)
AC Current: (True RMS AC coupled 10% to 100% of range)	
Range	• 2mA, 20mA, 200mA, 2A, 10A
Resolution	• 100nA, 1uA, 10uA, 100uA, 1mA
Accuracy	• 2mA @45Hz - 400Hz ± (2.5%rdg + 2dgt) 20mA - 200mA @45Hz - 400Hz ± (0.75%rdg + 2dgt) @400Hz - 1KHz ± (0.75%rdg + 3dgt) 2A - 10A @45Hz - 500Hz ± (1.2%rdg + 2dgt)

Resistance	
Range	• 200Ω, 2KΩ, 20KΩ, 200KΩ, 2MΩ, 20MΩ
Resolution	• 0.01Ω, 0.1Ω, 1Ω, 10Ω, 100Ω, 1KΩ
Accuracy	• 200Ω ± (0.2%rdg + 5dgt) + 0.04Ω 2KΩ - 200KΩ ± (0.1%rdg + 3dgt) 2MΩ ± (0.15%rdg + 3dgt) 20MΩ ± (0.5%rdg + 3dgt)

TALK TO GEOFF ABOUT YOUR INSTRUMENT NEEDS



GEOFF WOOD ELECTRONICS PTY LTD

Incorporated in N.S.W.
656A Darling St, Rozelle 2039
(One door from National Street)
Tel: **810 6845**



specialising in electronic components for the professional and hobbyist.

SCAN AUSTRALIA

WITH WORLD'S BEST SCANNING RECEIVERS



AR2001

FOR THE BEST PRICE IN TOWN. FOR THE BEST SCANNER IN AUSTRALIA

WORLD'S FIRST CONTINUOUS COVERAGE
THREE MODE COMMUNICATIONS RECEIVER
& SCANNER

Features

- 25-550 MHz Continuous
- NBFM — For Communications
- WBFM — For BC8TV monitoring
- AM For Air Band
- 20 CH Memory
- Clock Priority CH

\$559
+S10 POST

POCKET SIZE SCANNER SC-4000

NO COMPROMISE PROGRAMMABLE
HAND-HELD SCANNER THAT
EVERYBODY CAN AFFORD!

FEATURES:

- 160 MEMORY CHANNELS
- 9 BAND — POLICE, GOVERNMENT, MILITARY, LAND MOBILE, CB, AMATEUR, RADIO TELEPHONE ETC
- OVER 45,000 CHANNELS
- UNIQUE SPLIT PROGRAMMING SYSTEM
- AUTOMATIC FREQ. STORAGE
- PRIORITY CHANNEL
- 100 MSPA AV
- PROG SCAN/SEARCH RATE
- 24 HOUR CLOCK AND MANY OTHER FEATURES

SPECIFICATIONS:

- FREQ. RANGE: 26-28MHz, 68-88MHz, 138-176MHz; 380-512 MHz
- SENSITIVITY: 0.5µV-1µV depending on band
- SCAN RATE: 16 CH/SEC
- AUDIO OUTPUT: 0.5W

COMES COMPLETE WITH NICAD BATTERY, CHARGER AND ANTENNA

ONLY

SPECIAL
\$379
+S10 POST



NEW Personal 2-way radio here at last!

"EMTRON ACE"

A QUALITY 40-CH HIGH POWER UHF CB HAND-HELD TRANSCIVER ● DESIGNED FOR AUSTRALIA
DOC APPROVED

FEATURES:

- 40 CHANNEL OPERATION
- HIGH (2.0W) LOW (0.5W) RF OUTPUT
- OFFSET FOR REPEATER OPERATION
- NICAD RECHARGEABLE BATTERIES
- ILLUMINATED DIAL FOR NIGHT OPERATION
- SMALL IN SIZE — BIG IN PERFORMANCE

APPLICATIONS:

- FARMING
- FISHING, BOATING, HUNTING, BUSHWALKING
- BUSH FIRE CONTROL
- AG SHOWS
- SECURITY
- CONSTRUCTION SITES
- CAR RALLIES
- CROWD CONTROL AND MANY OTHERS

- OPTIONS:**
- 3W NICAD
 - SP MIKE
 - 3/4 WHIP
 - STAND-IN CHARGER
 - DRY CELL PACK
 - DC/DC CONVERTER AND MANY MORE

ONLY
\$399
TAX FREE

DEALER INQUIRIES WELCOME

Cut your computer installation time.

We carry Belden®...the most comprehensive line of computer cable available.

If you want to move data a few feet or a few miles, we can help you get clean, clear signals regardless of how difficult the operating environment. We have cable for local area networks plus plant and office interconnect applications. We also stock Belden's Bit-Driver™ line drivers and multiplexers for replacing short-haul phone lines with long-term savings. Plus, RG-62 coax, twin-ax from 78 to 200 ohms, Datalene™ and individually shielded pair cables. Ask for them in Belden's time-saving, convenient, self-dispensing UNREEL® packages. Many are also in stock for direct air plenum installations. Plus, we carry fiber optic cable for total interference immunity. You won't find a more complete line anywhere to cover your needs.



There is no equal.

ACME® ACME ELECTRONICS
(Hardie Trading Ltd. Inc. in Vic.)

SPEED DATA. Datalene™ data cable.

Belden® Datalene is the answer to your high-speed data transmission requirements. Datalene insulated cables offer lower capacitance and signal dissipation so you can send distortion-free data at higher speeds and for longer distances. It's crush-resistant, lightweight and has a temperature range of -40°C to +80°C. We have this high-performance Belden product—plus a huge selection of other Belden data transmission cables—in stock, ready for delivery. Just give us a call.

There is no equal.

ACME® ACME ELECTRONICS
(Hardie Trading Ltd. Inc. in Vic.)



EMTRONICS

Retail Division of EMONA ELECTRONICS P/L

All Mail to: PO Box K21, Haymarket, NSW 2000
Ph: (02) 211 0531 Ph: (02) 211 0988
94 Wentworth Ave, Sydney, 2000.

VIC. 205 Middleborough Rd, Box Hill 3128. Tel: 890 0900
N.S.W. 120 Beaconsfield St, Auburn 2144. Tel: 648 2255
QLD. 62 Doggett St, Fortitude Valley 4006. Tel: 854 1911
A.C.T. Electronic Components Tel: 80 4654
S.A. Neil Muller P/L Tel: 272 8011
W.A. J. G. Thomas & Assoc. Tel: 272 7122
TAS. W. P. Martin P/L Tel: 34 2811 Hobart, 31 5545 Laun.

OP AMPS Explained

Over the last few months we have considered high power operational amplifiers, many of which are internally DC-coupled but capacitor coupled to the outside world, quite successfully using a single large power supply. If that doesn't scotch the false rumour that "a single supply circuit is necessarily small" consider Figs. 4 and 5, a 6 kilowatt output stage consisting of four NPN transistors, Motorola type MJ10101, in a bridge configuration, transformer coupled to the load and operating from a single 110 volt DC supply.

Yet another fable needs to be laid to rest. Some users of professional electronics believe that to be a high

precision circuit dual power supplies are necessary. As illustrated in Fig. 6 this is not true. Here a single 6 volt 50 amp supply provides power for the output stage of a highly stable feedback control system. The load on the system is a 6 volt 11 amp tungsten filament quartz-iodine lamp used to apply heat via a lens to a small region of a scientific experiment, to control temperature. The control system is in fact a high gain power operational amplifier, successfully controlling the temperature of that small region to an accuracy of $\pm 0.25^\circ\text{C}$ (Ref. 1). Although low current $\pm 15\text{V}$ supplies are also employed, only one high current 6 volt supply is used, as lamps don't need current in both directions.

For many low power circuits such as filters, tone controls and preamplifiers, dual power supplies do give greater design flexibility in that whole sections can be DC-coupled. Where only one DC supply is available, it is possible to use a DC-to-DC converter, to derive dual output voltages at ± 12 volts or ± 15 volts

as desired. Such converters can be constructed or purchased, eg, Analog Devices Modular DC/DC converter model 964 will give ± 15 volts at 33mA, all derived from one 12 volt car battery. Or the model 953 could supply larger output current, 150mA. If in building your computer you have plenty of 5V DC logic power supply available but want a few milliamps at $\pm 12\text{V}$ for an analog-to-digital converter, then you could use the model 960 which gives $\pm 12\text{V}$ DC output supply when powered by your computer's +5V logic supply rail. These converter modules are also useful in providing zero line isolation for specialised input isolation amplifiers.

Other manufacturers also make such products. In general they convert the DC supply input to square wave AC by transistor choppers, operating at about 22kHz (to make it inaudible), transform up as necessary, rectify, filter and possibly regulate to provide smooth output. Multiple transformer windings can easily provide multiple outputs.

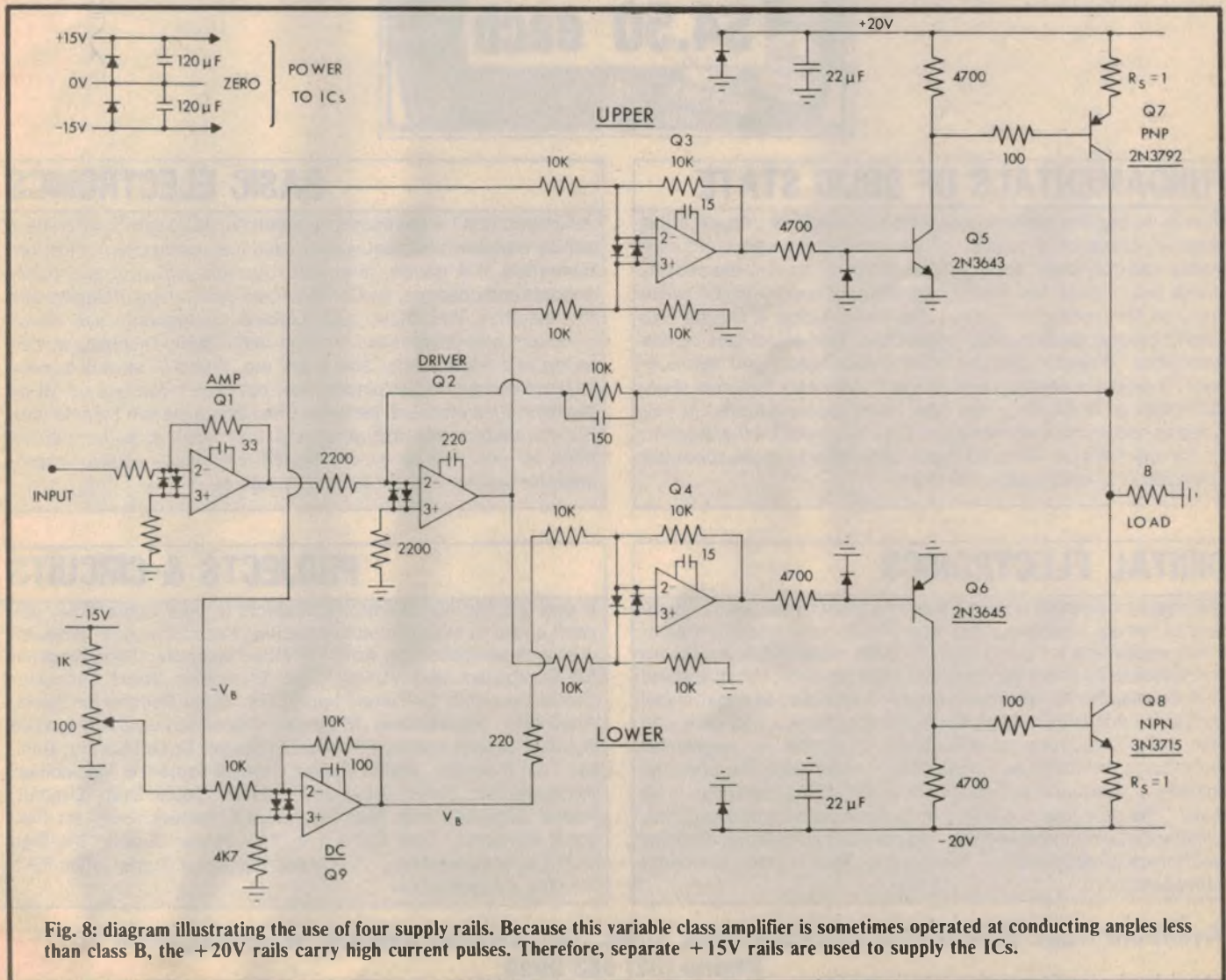


Fig. 8: diagram illustrating the use of four supply rails. Because this variable class amplifier is sometimes operated at conducting angles less than class B, the +20V rails carry high current pulses. Therefore, separate +15V rails are used to supply the ICs.

ELECTRONICS AUSTRALIA HANDBOOKS

Are you an
enthusiast?
A student?
A hobbyist? Or
a complete
beginner?



Whatever your
interest in
electronics,
we've a book
to suit
your needs!

FUNDAMENTALS OF SOLID STATE

Now in its second reprinting — which shows how popular it has been! It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised tests heavy going. It begins with atomic theory, diode types, unijunction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A glossary of terms and an index complete the book. Fundamentals of Solid State has also been widely adopted in colleges as recommended reading — but it's not just for the student, it's for anyone who wants to know just a little bit more about the operation of semiconductor devices.

BASIC ELECTRONICS

As a basic text for the electronics enthusiast, Basic Electronics is almost certainly the most widely used manual on electronics fundamentals in Australia. It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. It begins with the electron, introduces and explains components and circuit concepts and progresses through radio, audio techniques, servicing test instruments, television, etc. If you've always wanted to become involved in electronics, but have been scared off by the mysteries involved, let Basic Electronics explain them to you. Easy-to-understand diagrams and text make this the perfect book for you. We've even included five simple electronic projects for you to try your hand at building!

DIGITAL ELECTRONICS

Electronic equipment now plays an important role in almost every field of human endeavour and every day, more and more electronic equipment is "going digital". Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and Introduction to Digital Electronics can give you that grounding. Tens of thousands of people — engineers, technicians, students and hobbyists — have used the previous editions of this book to find out what the digital revolution is all about. The new fourth edition has been updated and expanded, to make it of even greater value. No previous knowledge of digital electronics is necessary — the book covers all basic concepts from scratch.

PROJECTS & CIRCUITS

If you like building electronic projects in your spare time, you can't afford to miss out on this exciting book of popular projects. Just look what's inside! **Audio & Video projects:** Video Amplifier for Computers and VCRs; Video Enhancer; Vocal Cancellor; Stereo Simulator for Tuners and VCRs; Guitar Booster for Stereo Amplifiers. **Automotive Projects:** Transistor-assisted Ignition System; Breath Tester; Low Fuel Indicator; Speed Sentry; Audible Turn Indicator. **Mains Power Control Projects:** Musicolour; Photographic Timer; Driveway Sentry; Touch-lamp Dimmer. **Power Supplies and Test Equipment:** Battery Saver for Personal Portables; Dual Tacking $\pm 22V$ Power Supply; $3\frac{1}{2}$ -Digit LCD Capacitance Meter; In-Circuit Transistor Tester. Plus EA's 10-year project index!

Available from: Electronics Australia Book Sales, 140 Joynton Avenue, Waterloo, NSW 2017.
Phone (02) 663 9999.

OP AMPS Explained

Specifications

Designers need to know how accurate the power supply must be for successful operation of their circuits. Will your circuit perform correctly if the nominal ± 15 volt supply actually is producing ± 14.9 volts, or ± 16 volts, or even $+15.1$ volts/ -14.8 volts? Will you notice anything untoward if the $+12$ V rail has some 50Hz or even 100Hz ripple (hum) superimposed upon it due to insufficient filtering or poor regulation. Supplies derived from the mains **always** have some residual ripple at 100Hz (from full wave rectification). But how much can be tolerated by your circuit? More correctly, how much can be rejected by your circuit. This is an important specification of every op amp. You will generally find figures quoted in Integrated Circuit data sheets as "Supply Voltage Sensitivity" or "Power Supply Rejection Ratio" (PSRR).

This denotes the ratio of the ripple or change measured in the amplifier output due to a ripple or change existing in the supply rail. Most integrated circuit op amps are designed with such excellent balance and such constant current active

load and tail impedances that quite large voltage variations occurring in the supply produce only tiny changes in the output, which are unnoticed in many applications. If 100mV ripple in the supply only produces 10 microvolt ripple in the amplifier's output, then we say the power supply rejection ratio is equal to 10,000 to 1, or 80dB. Data books quote PSRR for the 101A-201A-301A series op amps as typically 96dB, an excellent figure. The LM108A-208A-308A series is quoted higher still at typically 110dB. As a little mains ripple in the supply rails produces no noticeable effect on reasonable size signals, these integrated circuits can be used on unregulated rails (supplies which are simply rectified and filtered). But if you are dealing in microvolt size signals, you will need to use ICs having such high rail rejection ratios and use regulated supplies to reduce supply ripple to a very low figure.

Occasionally you will see (Ref. 2) supply rail rejection properties of an amplifier fully specified by stating the ratio measured for changes made in the positive or negative rails separately at DC and a range of frequencies.

Decoupling

Ripple superimposed on DC rails can be reduced by decoupling the supplies as shown in Fig. 7 where capacitor C is chosen quite large, and is generally an electrolytic type. A rule-of-thumb used by some designers is to choose C equal to

$10\mu\text{F}$ per milliamp of load current. If you cannot sufficiently reduce supply ripple by decoupling, then you need one of the many voltage regulation methods available. A second, quite separate, use of decoupling has as its purpose the removal of signals from the supply rails.

Large output stages, especially those in class B, will draw varying currents and cause voltage variations in the supply at signal frequency. If early low level stages do not have sufficient supply rejection ratio at signal frequency, such signals will appear in the early stages to be amplified and promptly fed to the output stage. The effect can be cumulative, resulting in positive feedback and instability. The amplifier uses the common power supply as a positive feedback loop. The cure is more effective decoupling of power rails and the use of early stages having a greater power supply rejection ratio.

Alternatively, voltage regulators can be used to supply low voltage rails for early stages, taking the power needed from output stage rails or, as a further variation, use separate power supplies for the early stages, ie, use four separate supplies, such as in Fig. 8. (Refs 3, 4)

Also we observe that the lower the output impedance of the power supply itself, the less is the above problem (hint — next month's topic).

High frequency bypassing

In every amplifier it is wise to decouple or at least bypass the positive and the negative rail for every stage as a

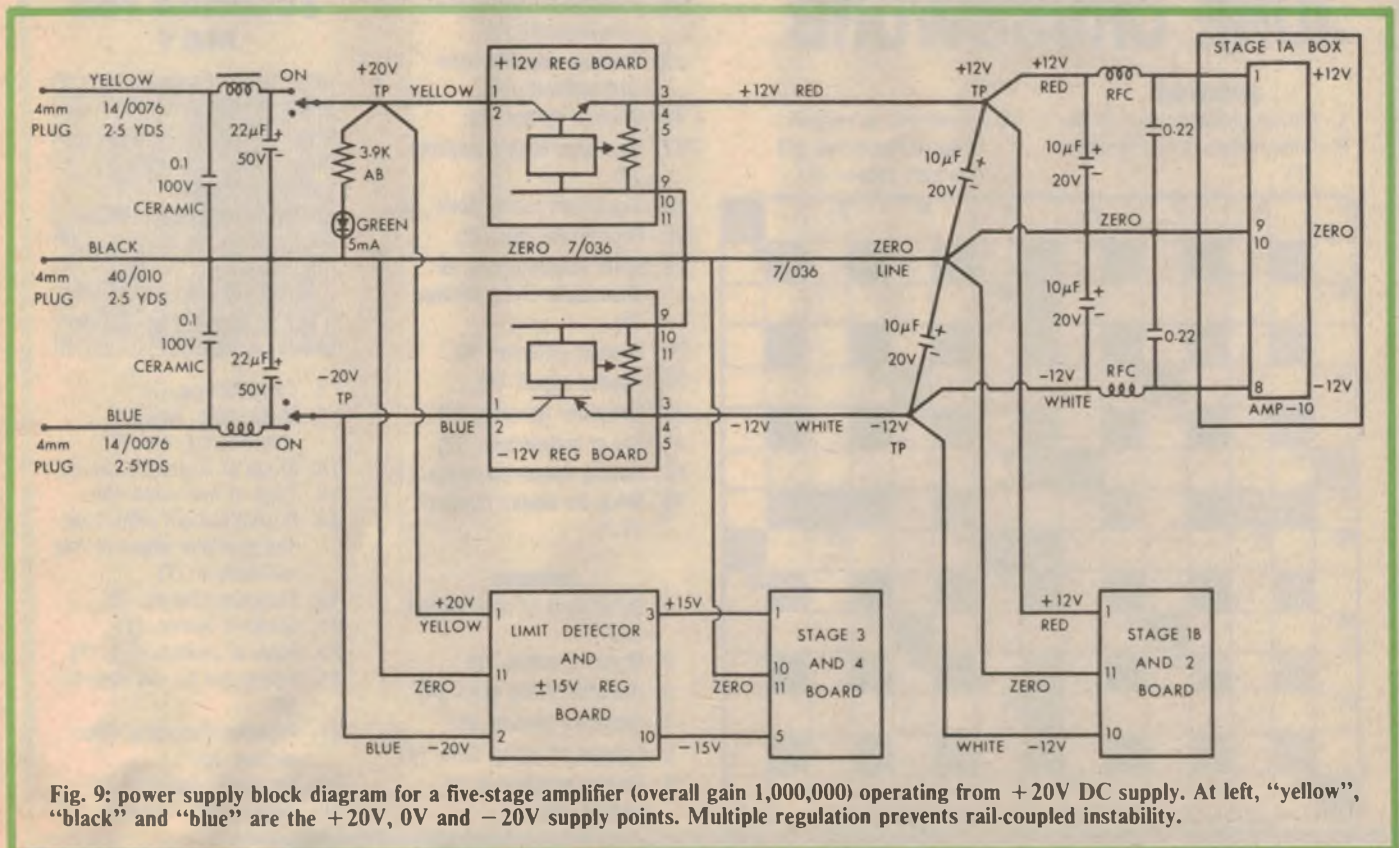


Fig. 9: power supply block diagram for a five-stage amplifier (overall gain 1,000,000) operating from $+20$ V DC supply. At left, "yellow", "black" and "blue" are the $+20$ V, 0V and -20 V supply points. Multiple regulation prevents rail-coupled instability.

OP AMPS Explained

precaution against high frequency rail-coupled feedback. Ceramic capacitors of 0.01 μ F to 0.1 μ F should be used, for sufficient bypassing at high frequencies. These are in addition to the larger electrolytic or tantalum types used to bypass the low frequencies, as electrolytic capacitors do not work at high frequencies.

The reason why every IC should have its own ceramic bypass capacitors close by is that even a short section of supply rail conductor has some inductance (at high frequencies) which prevents ceramic capacitors at one stage being effective in bypassing adjacent stages. Some designers may regard the above prescription as somewhat too strict and on occasion get away with less. Generally the more stages used and the higher the overall gain, the more necessity to be generous with bypassing.

A stage example is shown in Fig. 7. For very high closed loop gain systems to operate from a common power source, great care must be taken to prevent rail-coupled instability. Fig. 9 shows the supply arrangement used for an amplifier

which has closed loop gain of 1 million and bandwidth of 0.1Hz to 50kHz.

Drift

We define "drift" as a very slow change in an amplifier's operating voltage levels caused by temperature changes. The importance of this factor multiplies enormously as soon as a few stages are DC-coupled, because the second stage thinks the drift in the first stage's output voltage is a valid part of the signal to be amplified. Further stages compound the problem.

If the first stage has too low a supply rail rejection ratio (measured at DC) or should its supply rail voltages drift in value too much, then that stage's output voltage will drift excessively. We note that: (a) No stage has infinite supply rail rejection ratio; (b) Some voltage drift exists in every power supply and (c) Whether the resulting amplifier's output drift is acceptable or not depends on how much DC-coupled gain follows and the final user requirements.

If changes in DC level of the source voltages are a vital part of the input signal to be amplified, then your amplifier just has to be DC-coupled throughout. You have no choice. Many such situations occur in industry and science. Examples include position, force or level transducers and load cells in control systems. Should your input signal

be small, say 20 microvolts, you have a real problem. You may find it difficult to produce a first stage amplifier and associated power supplies so stable that the drift in the output voltage of that stage is small enough compared to the wanted signal excursions.

It can be done! As we saw in part 4 (June '84) of this series, a combination of careful amplifier design, choice of IC having high rail rejection, and very low drift power supplies can successfully produce DC-coupled linear amplifiers having gains of 50,000 or more. The exact value of the power supplies' voltage is not very important, but the value must not change any more than a few microvolts per hour.

Just how to design such stable power supplies we must leave till next month's episode. Bye!


References

1. Maher B. "System for accurately measuring a cutaneous thermal stimulus", Proc IREE(Aust) Vol 41 No. 4 Dec 1980 p 146.
2. Maher J.B. "A system of electronic equipment for neuropharmacological research", ME thesis UNSW p 40, 42.
3. Williamson DTN. "High Quality Amplifier, New Version", W. W. London Nov 1949.
4. Maher B. "A Novel Bias design for complementary amplifiers", JEEE(Aust) Vol 4 No 3 Sept 1984 p 216.

JUNE CROSSWORD

ACROSS

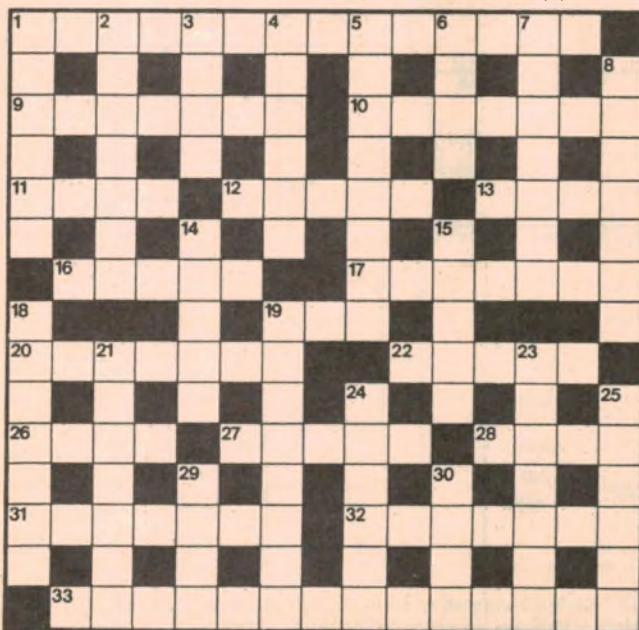1. Carrier characteristic. (5-9)
9. Components of hifi systems. (7)
10. Pertaining to certain charged particles. (7)
11. Program repeat. (4)




12. Example of successful interference? (5)
13. Possible speaker cone arrangement. (4)
16. Without defect. (5)
17. Discharge tube accessory. (7)
19. Significant replay point. (3)
20. Regenerate data. (7)
22. What electronics is for thousands of EA readers. (5)
26. Type of antenna. (4)
27. Applied signal. (5)
28. Computer operator. (4)
31. Set of instructions. (7)
32. Having advanced phase. (7)
33. What do diodes restrict? (7,7)

DOWN

1. By-product of rectification. (6)
2. Stylus material. (7)
3. Radiotelephony term. (4)
4. Blank TV picture. (6)
5. Convert to digital form. (8)
6. Final instruction in 31 across. (4)

SOLUTION FOR MAY

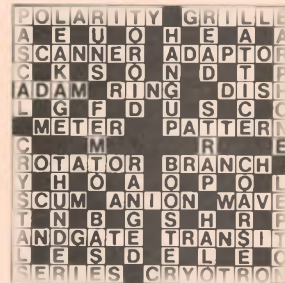

7. Carry charge. (7)
8. Mass, time, energy, capacitance, etc. (7)
14. Stage of IC production. (5)
15. Type of transistor. (5)
18. Project pattern printed on the previous pages of this publication. (7)
19. Frequency bands. (8)
21. Death of device. (7)
23. Form of multiplexing. (7)
24. Addressed by the system? (6)
25. Possible state of a video picture. (6)
29. Terminal condition? (4)
30. Current cat's whisker! (4)

NOW MOHAMMED NEED NOT GO TO THE MOUNTAIN...

Imagine! A computer that's powerful enough to run your business . . . yet small enough to take home with you. That's the Bondwell 14 Portable. It has all you need to run a business – yet costs a fraction of the price of other computers. That's why it's the success story of 1985!



Cat X-9000

In just a few short months, the Bondwell 14 portable has become our largest selling business computer. It offers performance and reliability far exceeding its low price tag. Even first glance will tell you that the Bondwell 14 portable is no ordinary computer!

You'll see:

- 128K RAM on board!
- Twin 360K disk drives!
- 220mm amber-screen monitor!
- Twin RS-232 serial ports!
- Centronics parallel port!
- External video monitor port!
- Ergonomically designed adjustable keyboard!
- PLUS a package of famous Micropro 'Star' series software valued at over \$1200: Wordstar word processing, Calcstar spreadsheet, Datastar information handling and Reportstar report preparation. AND if that's not enough, a host of CP/M utilities including a speech synthesiser! Yes, this is all included FREE with your Bondwell 14 portable.

And just in case your business needs other specialised software, you have one of the biggest 'libraries' in the world at your disposal: the Bondwell 14 portable operates under the world-standard CP/M system. (And it's the latest, most powerful version - Vs 3.0.)

With the huge number of programs written for this system, you'll find the one you require. And the Bondwell 14 portable will read disk files from many other computers – including the IBM PC (& compatibles), Osborne, Kaypro and Spectravideo!

Weighing in at just 12kg and measuring just a little larger than an electric typewriter, the Bondwell 14 is truly portable. Take your Bondwell 14 to where the job is: Mohammed need no longer go to the mountain.

Your business survival depends on your making the correct decisions. Decide on the Bondwell 14 portable. And survive!

Want to know more? Call in to your nearest Dick Smith Electronics Computerstop for a test drive. Ask for a copy of the Bondwell 14 brochure. And then get your own Bondwell 14!

Bondwell Computers: exclusive to Dick Smith Electronics.

ALL THIS FOR ONLY

\$2495


Or \$247 deposit and \$19.85 weekly over 48 months to approved purchasers.

Dick Smith Electronics Pty Ltd

COMPUTERSTOP



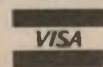Your one stop computer shop at your nearest Dick Smith Electronics centre.



A964/A966RT585

An antenna for those other bands

This simple trapped antenna offers good performance on the 80, 40, 30, 17 and 12 metre bands. It uses readily available materials and is easy to build and erect.

by BRIAN J. WARMAN, VK5BI

Most amateurs sometime or other get around to putting up a beam for the HF bands; ie, for 10, 15, and 20 metres. In the past a simple Windom, G5RV, or a couple of dipoles on 40 and 80 metres would suffice for the remaining popular amateur frequencies.

WARC '83 changed all that. If we dismiss a log periodic beam as too large, not having enough gain and too expensive (especially if you have a perfectly adequate tri-bander up there on the tower), there are still five bands to be catered for. These are 80, 40, 30, 17, and 12 metres.

A compromise antenna may be erected of course; perhaps a G5RV, made to work by the use of an antenna tuner. Such an antenna will work, and many amateurs may be heard using such antennas, particularly on 30 metres. However, if you want DX, a resonant antenna erected as high as possible must be your aim.

I have constructed such an antenna using coaxial traps. There have been a number of very fine articles dealing with design and construction of such traps and I commend them to the reader. My antenna has a total length of just over 12 metres each side; ie, just slightly longer than a full sized dipole on 40 metres.

The first step in constructing this antenna will be to obtain a one-metre length of 32mm poly pipe. This is the white pipe used for irrigation and may be obtained from all hardware stores. If you have any doubts about the dielectric qualities of the material obtained you may perform a simple test by putting a piece in a microwave oven for one minute. There should be no reaction.

A 10-metre length of RG-58U coaxial cable will be required. The dimensions given for the traps in this article will be correct only when used with this cable.

Cut the trap material as follows:

Band	Length of coax (mm)	Length of former (mm)
40m	1800	110
30m	1330	90
17m	830	70
12m	710	70

Once the formers have been cut to length, drill three holes in each as follows: one 5mm hole, 25mm from one end, which is to secure the beginning of the coaxial coil; and two 2mm holes 10mm from each end. These are to attach the antenna wires to the trap and should be in line.

Strip 75mm of jacket off each end of the length of coax followed by 50mm off the centre conductor. I have found the neatest way of finishing off the braid is to part the strands near the jacket and then fish the centre conductor out through this hole. In this way, the weaving remains intact and makes for a very neat finish. Push one end of the coax through the 5mm hole at the end of the former until 5mm of the jacket is inside. Wind the coax to form a coil on the former then mark a hole at the finish to allow 5mm of jacket to be pushed inside to finish the coil. Pull the remaining coax through this hole. You will now have approximately 70mm of coax inside the former at each end.

Solder the centre conductor from one end of the coil to the braid at the other end. Fig. 1 shows the general idea but note that the connection will be inside the former, not on the outside as shown. (The figure has been drawn this way for clarity.) The remaining braid connects to the element coming from the feedpoint (centre) of the antenna, while the remaining inner conductor goes to the next element.


I sealed the ends of the coaxial cable using CRC Lectra Shield (tradename) — you may care to use silicone.

The antenna may now be assembled, using the following element lengths:


12 metres	2 x 260cm
17 metres	2 x 22cm
30 metres	2 x 244cm
40 metres	2 x 144cm
80 metres	2 x 545cm

When cutting the element lengths, allowance must be made for terminating the element to the former. I allowed about 30mm extra, thus allowing for the wire to pass through the 2mm hole in the former, to be passed back, and then twisted around the element.

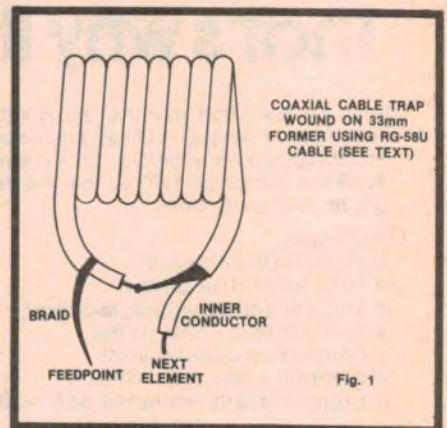I used a balun to terminate RG-58U coax feeder to the feed point. An advantage of using a balun is in the reduction of radiation on the coax (with consequent TVI reduction) and also a



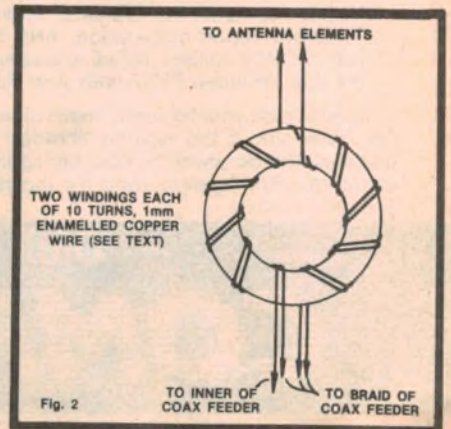
Connect the traps as shown in this diagram.



Here are the winding details for the balun.



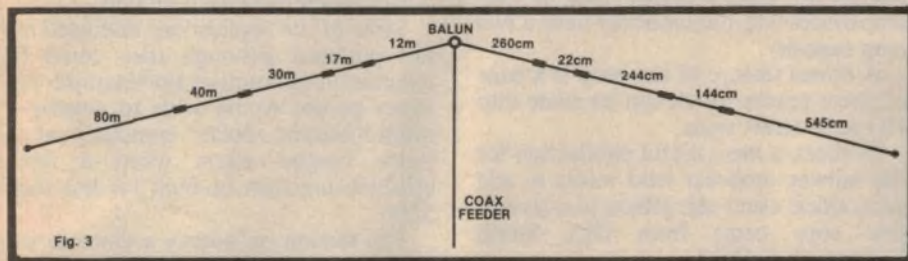The coaxial traps can be clearly seen in this photograph of the author's antenna.



This diagram shows the assembly details. The element lengths are shown on the right while the corresponding bands are shown on the left.

more uniform radiation pattern from the antenna.

Fig. 2 shows the winding details for the balun. There are two windings of 10 turns each but note that one of the windings is split; ie, it consists of five turns each side of centre. The balun core dimensions are not all that critical — I used cores with an outside diameter of about 40mm.

Amidon ferrite rings suitable for balun construction may be obtained from the suppliers listed at the end of the article, or ready made baluns purchased from the remaining source.

The balun should be mounted in a plastic box to protect it from the weather. Entry holes for the coax feeder cable and for connections to the antenna elements should be sealed with silicone.

The two 260cm (24.9MHz) elements are soldered to the balun at the centre of the antenna then passed through the holes in the 12-metre traps and soldered to the coaxial cable forming the trap. The 17-metre element is then attached to the other end of the trap and so on. Fig. 3 shows the assembly details. Do not use excessive heat on the centre conductor of the coaxial trap when soldering.

The length of the 80-metre element resonated my antenna at 3.6MHz. This resonant frequency will be attained with the antenna in the air and clear of obstructions. The resonance may be affected if the antenna is not in the clear. Adding and subtracting lengths to this

element will not affect other bands.

For those who wish to have all traps spot on frequency, the following procedure may be adopted. Before drilling the second 5mm hole to terminate the coil winding, temporarily connect the inner conductor at one end to the braid at the other end. The coax can now be held in position on the coil former and tested for resonance using a dip oscillator.

I resonated the traps at the following frequencies:

40 metres	7.1MHz
30 metres	10.1MHz
17 metres	18.1MHz
12 metres	24.9MHz

Similarly, if you wish to be sure the element lengths are exact for your requirement, each section may be tuned before the next one is attached. I did this using an antenna noise bridge. If such an instrument is unavailable, trim the lengths for best SWR.

Footnote: Amidon cores are available from: Ian J. Truscott Electronics, Croydon, Victoria 3136; and R.J. and U.S. Imports, PO Box 157, Mortdale, NSW 2223. Ready made baluns are available from K. Bruce Smith, 110 Rosemead Rd, Hornsby, NSW 2077.

References

- (1) "Tapping the Mysteries of Trapped Antennas", Gary E. O'Neil N3GO, Ham Radio Magazine, October 1981.
- (2) "A Two-band Half Sloper Antenna", Gary Myers, QST, June 1980.

PHILIPS

IS YOUR CURRENT POSITION PROVIDING THE REWARDS AND SATISFACTION THAT YOU REQUIRE?

Philips are world wide leaders in the design and manufacture of electronic products and have operations in all capital cities and major regional centres throughout Australia employing more than 4000 employees.

As a result of our continual advancements in high technology equipment and increasing sales we are continually searching for experienced and qualified technical staff for our operations throughout the country.

Our product range is extremely diverse, ranging from consumer products such as Natural Colour Stereo T.V. receivers, Laser Video and Audio players and the latest in Video Recorders and cameras to our Professional Range of products such as Micro Processor Controlled 2-way Radio Equipment, Data Communications Information Equipment, Micro Processor based PABX/Traffic Controllers and Defence Systems.

To service and design this exceptional range of products we believe that it is important to employ the right technical staff. Therefore we are interested in receiving applications from Technicians and Electrical Engineers in all fields of electronics for our operations in all major capital cities.

Essentially, applicants will have had some form of tertiary technical training, whether they be a degree or trade qualifications. However, the most important quality we seek in our technical staff is **EXPERIENCE**.

As can be appreciated, experience is closely attuned to the type of products the person is involved with, but as a guide the persons we are seeking should have had experience in any of the following areas:

- The servicing and design of 2-way radio equipment both UHF and VHF in digital and analogue circuitry;
- In servicing Electronic Office Equipment and Financial Systems including Electronic Funds Transfer using digital logic;
- The design, installation and servicing of microprocessor based PABX communication systems.

As would be expected, wages and conditions are excellent and staff benefits include superannuation after a qualifying period.

If you have had experience in any of the above areas, forward a detailed resume, outlining in full your qualifications and experience, also highlighting your particular area of interest to:



Mr. C.N. Westacott,
Personnel Manager,

PHILIPS
COMMUNICATION SYSTEMS
25-27 Paul Street North Ryde
NSW AUSTRALIA. 2113



PHILIPS — We want you to have the best

Books & Literature

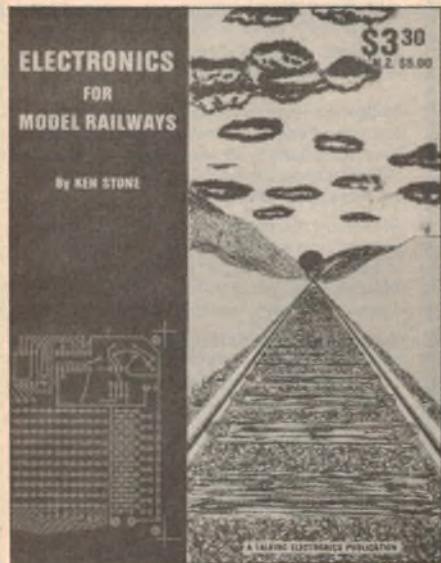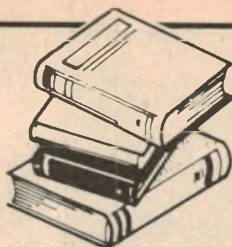

Model railway electronics

ELECTRONICS FOR MODEL RAILWAYS: by Ken Stone. Published 1984 by Talking Electronics, Melbourne. Soft covers, 210 × 275mm, 73 pages, illustrated with diagrams and photographs, ISBN 160884-40-16K. Recommended retail price \$3.30.

As any model railway enthusiast can attest, there is a dearth of books on the subject of railway modelling and particularly on the electronics side of it. So the arrival of this Australian publication is likely to be very welcome.

The content of this small text is strictly at a hobby level and would be well within the grasp of most railway modellers. All the circuits are simple and easy to build, with readily available components.

The list of circuits comprises the following: Warning lamp flasher unit, capacitor discharge unit (for point motors), scale fluorescent lamps (flickering), air horn, power supply, remote relay unit, pedestrian crossing, light chasers and shop displays, level crossing flasher, crossing boom control, light sequencer, throttle and train detectors.

There is also a brief introduction on the use of computers and a section on three-coloured LEDs which are most useful in railway modelling.

All the circuits appear to be workable although several show some lack of theoretical knowledge on the part of the author. One example of this is in the power supply which specifies the use of parallel-connected one-amp diodes in a bridge rectifier to gain a two amp current capacity. Since any diode in a bridge rectifier conducts for only half the total conduction time, a bridge made of one-amp diodes will automatically have a two amp capacity.

A bonus feature of the book is a page of street names which can be made into HO scale street signs.

In short, a most useful publication for the railway modeller who wants to add economical electronic effects to a layout. Our copy came from Dick Smith Electronics (L.D.S.)



Interfacing the IBM PC

THE IBM PC CONNECTION: by James W. Coffron. Published 1984 by Sybex Inc, Berkeley, California. Soft covers, 177 × 227mm, 264 pages, illustrated with diagrams. ISBN 0-89588-127-6. Recommended price \$24.95.

This book is aimed at the user of an IBM Personal Computer or IBM compatible who wants to use his machine for more than just running

programs. It discusses the use of an IBM PC to operate as a home security system and a home temperature control, adding voice synthesis, digital-to-analog conversion and analog-to-digital conversion.

Much of the discussion revolves around a proprietary input/output board available in the USA (but not necessarily in Australia) however the reader would not have to be a prospective buyer of this unit to benefit from reading the book.

There is also an assumption that the reader will be willing to solder ICs and other components into printed boards. Whether many IBM PC owners are wont to do this is a moot point.

Perhaps the most useful feature of the book are the short programs in Basic which accompany each section.

Some of the applications discussed are not practical although they could be regarded as instructive. For example, not many people would wish to employ a multi-thousand dollar computer as a home burglar alarm when a more effective unit can be built for less than \$200.

The section on adding a voice to the IBM is based on using the Votrax chip. This is available in Australia but is not cheap or easy to obtain.

The book can be regarded as helpful as there is not much information published on this subject but whether it will encourage users to interface their machine to the "outside world" is another matter. (L.D.S.)

Z80 machine code programming

AN INTRODUCTIN TO Z80 MACHINE CODE: by R. A. & J. W. Penfold. Published 1984 by Bernard Babani (publishing) Ltd, London, UK. Soft covers, 110 × 178mm, 132 pages, illustrated with tables and lists. ISBN 0-85934-127-5. Recommended retail price \$6.75.

Here is a useful little text for those people with a Sinclair Spectrum or ZX81, or an Amstrad CPC464 or anyone with a need to be familiar with Z80 machine code programming. It gives a brief but well written introduction to assembly language, which mentions such topics as binary coded decimal, hexadecimal, stacks and flags.

There is a chapter each on addressing modes, on the Z80 instruction set, on storing and execution and on input/output characteristics of the Z80 CTC (counter/timer circuit). There is also a chapter of sample routines in machine code for the above mentioned computers. (L.D.S.)

at the leading edge

SHARP 25 line x 80 CHARACTER/GRAPHICS LCD

Liquid Crystal Displays take one step closer to emulating the attributes of the C.R.T. with Sharp's **LM64004G**. Its **640x200 dot** capacity will give word processing and spreadsheet capabilities to laptop and portable computers and increased graphics flexibility to instrumentation and monitoring equipment. The LM64004G is supported by the Sharp **LR3692 L.S.I. controller**.

MEGAVALT LAUNCHES 330 AND 660 MEGABYTE WINCHESTERS

An average seek time of **18 ms** puts these **8" hard disks** in a high performance class normally the preserve of 14" and "washing machine" storage units. OEMs and mainframe installers can look forward to big savings right across the board. Cost, weight, power drain and size are way down on these **SMD** and **SCSI** interfaced devices.

FLOPPY INTERFACE TAPE STREAMER BACKS UP 10 MBYTE

Configured like two 5Mbyte floppy drives **Interdyne's ID1010** provides a rapid and economical back up for the most popular hard disk configurations. **Track access is totally electronic** overcoming offset problems associated with the head positioning mechanism used in most streamers.

REDUCTIONS ALL ROUND ON MINISCRIBE HARD DISKS

Miniscribe follows the release of their low power, half height **3212 10MByte** Winchester with a **25MByte** model designated the **3425**. Average access time for both units has been reduced to **88 msec**, putting them among the fastest stepper positioned drives commercially available.



daneva australia Pty Ltd

64-66 Bay Road Sandringham Victoria 3191
Australia PO Box 114 Sandringham 3191
Telephone (03) 598 5622 Telex AA34439

Sydney: E&M Electronics (02) 51 5880
Adelaide: DC Electronics (08) 223 6946
Brisbane: Baltec (07) 369 5900

New Products...

Product reviews, releases & services

GUC-2010 100MHz frequency counter

The GUC-2010 Universal Counter made by the Goodwill Instrument Company certainly lives up to its name. This versatile piece of test gear performs a multitude of timing and counting functions, and is priced well within the reach of the serious hobbyist.

by ANDREW LEVIDO

The GUC-2010 is built into a grey plastic case measuring 237mm x 85mm x 284mm (W x D x H) which includes a tilting bail. The front panel is dark grey with white lettering and orange detailing. An 8-digit LED display occupies the upper half of the right hand side of the front panel, with the control buttons and indicator LEDs set out below this. At the left of the front panel are the two BNC input sockets.

There are six control buttons in all: a mains power switch, a reset switch, a gating time select switch, a function select switch, a range switch and an input attenuator switch. The mains power switch requires no explanation, but the others are worth a closer look.

The input attenuator works only on the main (A) input and attenuates the input signal by a factor of 10 when it is in circuit. Pushing the switch once removes this attenuation when measuring low level signals. Pushing it again restores the attenuation.

A range button is provided to switch an extra divider into the input circuit to facilitate measurements of high frequency waveforms. Dividers are switched into both the main (A) input channel and the secondary (B) input simultaneously.

The required function is selected by means of the function button and indicated by a row of six LEDs. Pushing the button repeatedly steps the counter through all the available functions. There are six possible functions: Frequency, Period, Time Interval, Frequency Ratio, Totalise and Check.

Frequency and Period are self-explanatory while the Totalise function

is similar to Frequency except that the user controls the gating time. Thus, the meter actually counts the number of input pulses. This is quite a useful feature.

The above three functions require the use of only one input (the A input), while Frequency Ratio and Time Interval measurements require the use of both the A and B inputs. In the Frequency Ratio mode, the display shows the quantity of F1/F2 where F1 is the A input and F2 the B input. This function is especially useful in determining the frequency ratio of harmonically related signals.

The Time Interval measurement function displays the time interval between negative transitions of the signals applied to the inputs. The signal at input A provides the start input, while

that at input B provides the stop input.

The next pushbutton on the front panel is the Gating time control. This works in a similar manner to the Function control in that pushing the button repeatedly steps through the available options. There are four gating times available, each indicated by a separate LED: .01s, 0.1s, 1s and 10s.

Incidentally, each time either the Function or Gating time switches are pressed the counter emits a short "beep" (this tone is different for each switch). We found this quite annoying during regular use. Had the instrument been ours, the piezo transducer would have been disabled in very short order!

Finally, there is a Reset switch which is used in the Totalise mode to reset the count to zero.

Construction

Opening the case of the GUC-2010 reveals a large printed circuit board covering the whole of the bottom of the chassis. On this board are all the components except the digital display and the LEDs — these have their own board mounted at right angles to the main board.

Construction appears to be of a high standard and most components are readily available types. This, combined with the fact that there is a circuit diagram in the instruction manual, should simplify servicing should it ever be needed. Goodwill are one of the few manufacturers of test gear who consistently include a circuit diagram with their equipment.

One thing we did notice is that the mains fuse is located on the PC board which means that the case will have to be opened whenever the fuse blows. However, there is little chance of the fuse blowing in normal circumstances, so this is no real drawback.

So how does the GUC-2010 perform?



The Goodwill GUC-2010 frequency counter covers the range from 5Hz to 100MHz.

Brief Specifications

Frequency measurements (channel A only)

Range 5Hz to 100MHz
Gating times 10ms, 0.1s, 1s, 10s
Resolution 100Hz, 10Hz, 1Hz, 0.1Hz
Accuracy Timebase accuracy + 1 digit

Period measurements (channel A only)

Range 0.04 μ s to 10s
Resolution 0.1ns to 0.1 μ s (10MHz range), 0.01ns to 0.01 μ s (100MHz range)
Accuracy Timebase accuracy + trigger error + 1 digit

Frequency ratio (channels A and B)

Range CH A: 5Hz to 100MHz
 CH B: 5Hz to 25MHz
Accuracy 1 digit of CH A + trigger error of CH B

General

Input sensitivity CH A: 20mV to 100MHz
 CH B: 20mV to 25MHz
Input impedance 1M Ω shunted by less than 30pF
Max input voltage 250V DC + AC peak, 150V RMS to 1kHz, 5V RMS to 100MHz

We found that the unit took a little getting used to. The controls tend to be somewhat confusing at first and the instruction manual does not help much. While this did tend to slow us down, it was not an insurmountable obstacle and, after a period of fiddling, we quickly mastered the controls.

Taking readings is quite simple and requires little thought on the part of the operator. The decimal point moves as different ranges and gating times are

selected and two LEDs indicate whether the display is reading in kHz or μ s. An additional LED lights if there is a display overflow. The only point which we found that we had to watch was that it was easy to forget that the divide by 10 circuit had been switched on.

Sensitivity was quite adequate for most uses (see specifications panel) and performance on the Frequency Ratio and Time Interval modes was good. As a frequency and period meter the device

also performed well, but the usefulness of the self check facility is a little doubtful.

When this function is selected the frequency meter measures the frequency of its own 10MHz reference oscillator. This is meaningless as far as accuracy is concerned since all frequency measurements are made with respect to this oscillator. Even if the oscillator is significantly off frequency the display will read 10000.000kHz.

Unfortunately, this test function does not test the input stages of the meter either, the 10MHz signal being injected directly into the converter chip. So this function does nothing except check that the converter IC is working — a correct test result does not mean that the entire circuit is OK.

In conclusion, the Goodwill GUC-2010 Universal Counter represents fair value for money. It is a versatile counter with very respectable specifications and good performance. It requires a little time to get used to but the display provides an unambiguous readout of the measured quantity.

The Goodwill GUC-2010 Universal Counter is supplied complete with a mains cord, spare fuses, two test leads and an instruction manual. It is available from Geoff Wood Electronics, 656A Darling St, Rozelle, NSW 2039. Phone (02) 810-6845. Price is \$634.80 (including tax).

Variable volume piezo buzzer

Piezo buzzers normally operate with fixed volume but the new KPE 960 from IRH has provision to vary the sound output. This is achieved by means of a knurled knob which is rotated to increase the hole dimensions at the front of the buzzer.

According to IRH, the KPE 960 is ideal for applications where a high sound pressure is required. Its small size, low cost and variable sound pressure make it particularly suitable for the security industry.

With the acoustic volume control "open", the sound pressure level at 100cm is a claimed 95dB minimum (12V supply). This sound pressure is reduced by 15dB with the control in the closed position.

The KPE 960 can operate from any DC source between 1.5 and 16V DC. The resonant frequency is 2.5kHz and current consumption is 3.5 - 70mA, dependent on voltage.

IRH Components, 53 Garema Circuit, Kingsgrove 2208. Phone (02) 750 6444.



IRH's KPE 960 variable volume piezo buzzer.


Videophone for security systems

DESIGNED FOR installation in apartment complexes etc, this videophone system allows homeowners to view visitors before permitting access to the building. Main features include a 10cm monochrome screen, a wide angle lens with built-in lighting lamps, and a two-way intercom. For further information contact Electron Alarm Supplies, 225 Ramsay Rd, Haberfield, NSW 2045. Phone (02) 799 4745.



The control centre features a 10cm screen.

New Products...

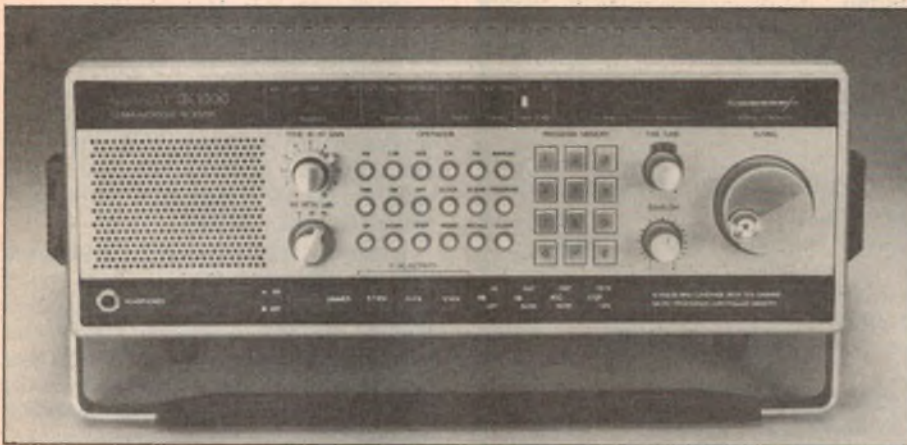

Bearcat DX1000 communications receiver

Featuring microprocessor control, the Bearcat DX1000 communications receiver covers 10kHz to 30MHz continuously. It has PLL synthesized tuning, 10 memory channels and automatic band scanning.

In addition to indicating the frequency with a resolution of 1kHz, the digital display doubles as a two time zone 24-hour clock. By utilizing the internal

clock, the DX1000 can be programmed to record up to five different broadcasts on any frequency and in any mode.

An IF bandwidth selection control is provided to help separate high powered stations on adjacent frequencies. Receiving modes are AM, LSB, USB, CW and FM.


Further information is available from all Dick Smith stores.

Gold-plated RCA plugs & sockets

Looking for some high quality RCA plugs and sockets? These fancy units from Arista Electronics feature screw locking and gold plating to ensure reliable contact. An integral cable entry spring provides protection against cable breakage.

The sockets are single hole chassis-mounting types and are supplied with nylon insulating washers.

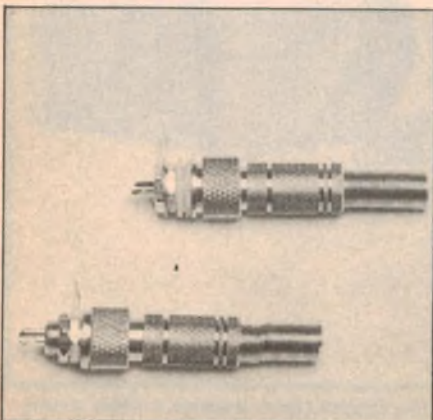Arista Electronics Pty Ltd, 39 Jones St, Ultimo, 2007. Phone (02) 648 3488.



New products for Z8000 family

The George Brown Electronics Group has released several new products in the Z8000 range. They are: the Z8065 Burst Error Processor, the Z8068 Data Ciphering Processor, the Z8090 Universal Peripheral Controller (UPC) with 2K ROM, the Z8094 Prototyping Device with EPROM/RAM interface, and the Z8530 Serial Communications Controller.

The George Brown Electronics Group, 174 Parramatta Rd, Camperdown 2050. Phone (02) 519 5855.

High density bubble memory

Recently released by IRH, the Fujitsu FBC504M4M series high-density memory cards have an interface compatible with the IEEE796 multibus. Main features include the DMA controller equivalent of the 8527 selectable 8 or 16-bit bus, built-in power supply protection circuitry (+5V rail required) and four levels of memory expansion from 128K to 512K. The memory can be further expanded to

Low cost EPROM eraser

Erasing the contents of EPROMs can now be carried out quickly and safely with the Ango Eprom Eraser from Jaycar Electronics. The unit can erase up to nine 24-pin devices in around 40 minutes.

The Ango Eprom Eraser uses a high intensity UV tube operating at 2540 angstroms to ensure reliable chip erasure. This is mounted inside a moulded plastic case which prevents leakage of the UV light. A slide out drawer with a conductive foam pad accepts the EPROMs.

According to Jaycar, the tube life is rated at 3000 hours. The unit features mains operation, measures 80 x 217 x 70mm (W x D x H) and retails for \$79.50.

Jaycar Pty Ltd, PO Box 480, Auburn, NSW 2144. Phone (02) 643 2000.



4MB if required.

Also available from IRH components are the Bubble Memory Module series types FBM-M128TA and FBM-M128TC. The modules consist of a bubble memory device and peripheral linear ICs mounted on the same package. All the components use TTL level I/O.

IRH Components, 53 Garema Circuit, Kingsgrove, NSW 2208. Phone (02) 750 6444.

ELECTRONICS GALORE

100's OF OTHER BARGAINS FOR CALLERS

'OPEN SESAME' TO A 1001 STUPENDOUS BARGAINS

Scoop Purchase

LAST FEW

JVC Battery Charger/Power Supply

Combined battery charger and fully regulated power supply unit (Model AA-P41EA)
Input: 240VAC 50Hz
Output: 12VDC 2.3A



Has built in over-charge prevention and automatic change over from nicad to power supply.

Ideal for use as a computer power supply


All brand new and cartoned with instruction book. Normally around \$150 but from us a silly

only **\$60** plus P&P certified post \$8.00

LAST CLEARANCE OF TECCOR DEVICES

Prices below Trade


SCR EC106A1	100v 6A	Sensitive Gate	TO220	\$1.00
SCR Q4015H	400v 15A	Non Sens Gate	1/2" stud	\$2.00
SCR S4020L	200v 20A	Non Sens Gate	TO220	\$1.25
SCR T10601	200v 4A	Sensitive Gate	TO220	\$1.00
Triac Q4025H	400v 25A	Gated Triac	1/2" Stud	\$3.00
Triac Q4001L	400v 1.6A	Gated Triac	TO220	\$1.00
Triac Q6025H	600v 25A	Gated Triac	1/2" Stud	\$3.50

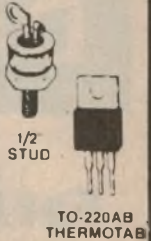

CLEARANCE OF BRAND NEW UNUSED TOP GRADE COMPUTER ELECTRO'S

SPRAGUE & PHILIPS types . . .

10,000mfd 40v	\$ 6.50
14,000 mfd 25v	\$ 5.50
14,000 mfd 40v	\$ 9.00
39,000 mfd 30v	\$13.00
47,000 mfd 25v	\$19.00
120,000 mfd 15v	\$15.00

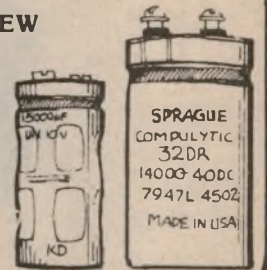

Microswitch Bargain

Top quality Cherry brand. 15A/250VAC rating. Normally open contact with lever.

only **65c**
10 for **\$5.50**

150 ohm/25W Wire Wound Rheostat

Going at absolutely giveaway prices for New Year. Ceramic body, 1/4" shaft. Perfect for speaker attenuators, power supplies etc.

only **\$1.00**

SUPERIOR SINGLE STRAND HOOK-UP WIRE

300 metres of 3-way FLAT RIBBON CABLE in Yellow, Green & Orange. PVC covered, rating 1000 Volts

ONLY **\$30** per Roll

Give away specials Limited stocks only

2764 8Kx8 EPROM was \$13.00 now **\$8.00**
6116-P3 150nS Static RAM was \$9.95 now **\$5.50**

Money Savers

A14A Glass Diodes 100V 1A 10 for \$1
A15A Glass Diodes 100A 3A 10 for \$1.50

IN914 (IN4148) Diodes 100 for \$2.50
IN4004 Diodes 50 for \$2.50

BC548 Transistors 10 for \$1.40
BC549 Transistors 10 for 90c
BC559 Transistors 10 for 90c

BC547 Transistors 10 for 90c
BC557 Transistors 10 for 90c
BC332 Transistors 10 for 90c

BC109/BC337 Transistors 10 of each (20) \$3.00

TIP29B Transistors 10 for \$3.50
4001A CMOS 10 for \$1.50
4020A CMOS 10 for \$2.50


Crystal 6MHz \$2.50 each
Crystal 32.768 Clock Xtal \$1.25
4433 619KHz Colorburst \$2.00

The Ultimate joystick for the VIC-20 and Atari

The incredible Pointmaster is truly the finest Joystick on the market and will add incredibly to your enjoyment of video computer games.

Just look:

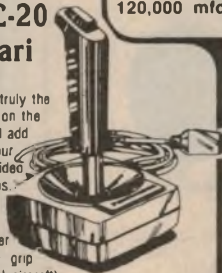- High speed thumb trigger
- Unique hand grip (as on actual aircraft)
- Self centring
- Long 150cm cord.




\$32.95

300V/150A Stud Rectifiers below wholesale

ASTOUNDING SAVINGS on these 300V rectifiers. 300V forward or reverse voltage (please specify). All brand new current stock.

only **\$7.50**

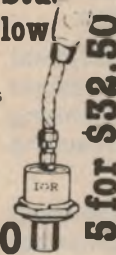

5 for **\$32.50**

2500uF/63V Elna Electros at 1/3 Normal Cost

63mm High (inc connector x 35mm wide. Can type with mounting clip. Going for a song!!

\$1.75 10up **\$1.50**



BARGAIN PACS

1 **Component Pacs.** 1 1/2kg's of useful components, including switches, capacitors, slide pots, relays, tagstrips resistors etc. Worth at least \$20 Yours for only. **\$6**

2 **Fuse Pacs.** 50 assorted 3A & 2AG glass fuses in fast-acting & slow blow, all useful values. Normally 25c each. Our special price only **\$6**

3 **Relay Pac.** 30 assorted types from 12 to 48 volts. Cradle, mini and mercury wetted etc. \$60 value for only \$10. Limited stocks. Only Rush your order NOW. **\$10**

4 **Disk Ceramic Pac.** 60 assorted values. From 10pf to 1uF. 100 to 630V. Here's value for money. \$6 value for only **\$3**

5 **Polyester Capacitor Pac.** 60 assorted types from 001uF to .22uF 100V. Only **\$6**

6 **Electrolytic Pac.** 55 assorted high grade electros. Radial and Axial types. 2.2uF to 470uF 10 to 25V. \$10 value for only **\$5**

7 **1% Resistor Pac.** High grade Takman 1/4 watt type. 300 mixed types that would normally cost you around \$22, but for only a measly. **\$12**

8 **Connector Lead Pac.** Look what you get here. Talk about value. 1 x 5 pin DIN plug to 4 x 6.5mm Mono Plugs. 1 ditto to 1 x 3.5mm plug 2 x 6.5mm line socket to 1 x 6.5mm stereo plug 1 x 3.5mm plug to 1 x RCA Line Socket. **4 for \$5**

Monolithic Cap Pac. Now here's value. Mini Bypass caps manufactured by Emcon USA. 50 assorted from 12pf to 270 pf 100V in radial and axial. Worth at least \$15. Our special price. **\$7**

Miniature 'Jones' connectors

8 way plug with top entry cover plus 8 way chassis socket with bracket. Very difficult connector to find at this price.

only **\$2.00** pr.



SHERIDAN

ELECTRONICS PTY LTD

164-166 Redfern Street, Redfern, NSW 2016
Phone (02) 699 5922, 699 6912

Mail Orders to: PO Box 229 Redfern NSW 2016

Mail Charges:
\$5.00-\$9.99 \$3.50
\$10.00-\$24.99 \$4.00
\$25.00-\$44.99 \$6.00
\$50.00-\$99.99 \$7.00
\$100 and over \$8.00
Large and overweight items sent Skyroad Freight Forward


Trading Hours:
Mon-Fri 9am-5:30pm
Thurs 9am-7pm
Saturday 9-12pm
Note: We accept Bankcard and American Express. However we cannot provide quantity discounts

on credit card purchases or account orders. Minimum for account orders is \$50.00. Minimum order is \$10.00 exclusive of postage and packing.

All prices include sales tax.

MASTER THE DARK ARTS

With Heimann
Far Infra-Red Detectors

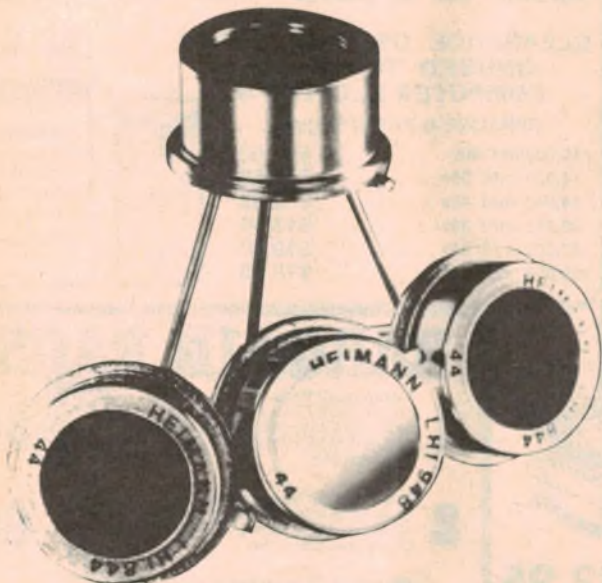

These devices are Pyro-Electric cells with built in Mosfet Pre-Amplifiers and single or differential elements for maximum background rejection.

These detectors are used as human body heat sensors for security systems, temperature measurement, flame detectors, locating overheated wiring and equipment and many other unusual and exciting applications.

We have excellent engineering bulletins which show typical circuits for these versatile, economical devices.


**Promark
Electronics** PTY.
LTD.
(inc N.S.W.)

SYDNEY
02-439 6477

MELBOURNE
03-878 1255

TOLL FREE
008-22 6226

New Products...

VHF marine transceiver



◀ *JUST RELEASED* by Dick Smith Electronics, this hand-held VHF marine transceiver features diode programming for frequency selection without the need of additional crystals. The D 1404 covers the marine frequency band from 156MHz to 162MHz, has switchable 0.5W/2.5W output power and comes complete with a NiCd battery. For further information, contact your nearest Dick Smith store.

LMC669 CMOS auto-zero circuit

National Semiconductor has introduced an auto zero circuit that automatically and continuously corrects the offset voltage of an operational amplifier or any other linear circuitry.

The LMC669 is intended for designers who need more precision than they normally get out of an op amp. It is available in two versions. The 8-pin package is a stripped-down circuit while the 16-pin version offers extra features such as a reset mode, start-up circuitry and precision comparator functions.

National Semiconductor (Aust) Pty Ltd, 23 Cleg St, Artarmon, NSW 2064. Phone (02) 439 6455.

Sealed batteries from Chloride

Chloride has launched a comprehensive range of rechargeable batteries using RE (recombination electrolyte) technology. The new Exide Powerstore batteries provide primary or standby power in neat, clean packages that resemble building blocks more than they do rechargeable batteries.

Indeed, the Powerstore batteries can be treated like building blocks. Containing no free electrolyte, the batteries can be stacked side or end on, or even upside down if necessary. There is no gassing on charging, no water loss and no need for topping up.


Ten batteries comprise the Powerstore range and deliver voltages ranging from 2V at 5.8Ah to 12V at 240Ah. The batteries are ideal for portable equipment and as standby power packs in computers, cash registers, security alarms, and telecommunications.

Chloride Systems Division, 55 Bryant St, Padstow, NSW 2211.



New rack system

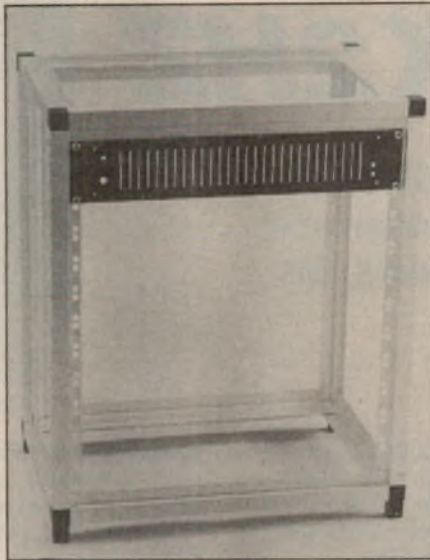Autotron Australia have released a new concept in 19-inch racking systems called Zip-Rack. Based on an exclusive aluminium extrusion together with specially tooled interlocking plastic corner pieces, Zip Rack is supplied in kit form with all necessary items for frame assembly.



These include blank panels, recessed bins, floor and bench mounting brackets, Eurocard bins and cassettes, PCB card panels, dust covers, cable support bars and roller castors.

Zip-Rack is available in two standard depths, 358mm and 500mm, and five standard rack heights. The entire Zip-Rack system has been designed and manufactured in Australia.

Zip-Rack frames can be supplied unanodised which enables end users to anodise to their own colour choice or to use an alternative finish. Further product information is available from Autotron Australia, PO Box 202, Glen Waverley, 3150. Phone (03) 763 6423.


A consumer version of the Zip-Rack range will be available in three sizes from all Jaycar Electronics stores. See advertisement on page 14.

The Exide Powerhouse batteries are ideal for portable equipment.



SEE THE LIGHT

With Heimann Light Dependent Resistors

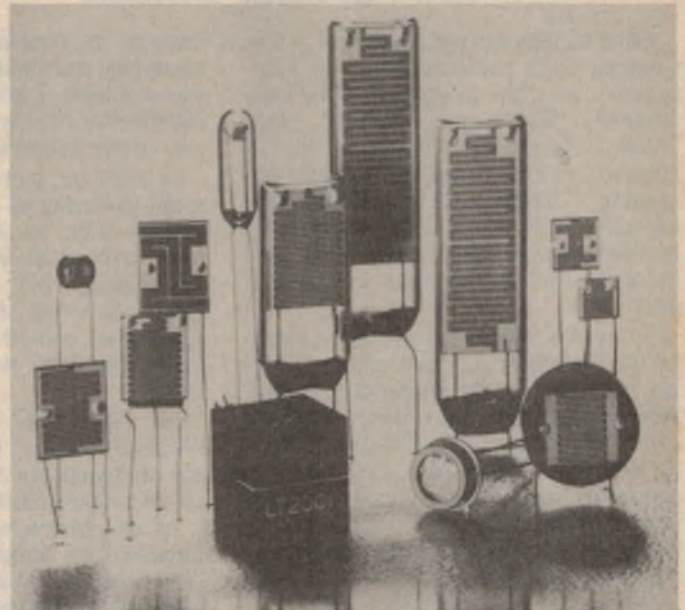

These highly sensitive detectors feature broad spectral response, wide resistance change and very low power dissipation. These unique features make them suitable for a wide range of applications in street lamp switching, dimmers, exposure meters, active filters and volume controls. A wide range of encapsulations is available to suit industrial and commercial use.

Comprehensive data is available now.


Promark
Electronics PTY. LTD.
(inc N.S.W.)

SYDNEY
02-439 6477

MELBOURNE
03-878 1255

TOLL FREE
008-22 6226

Obituary to Bill Moore, VK2HZ

Well known radio amateur William (Bill) McInnes Moore, VK2HZ, passed away at his Springwood home on March 28, 1985. For many years, his amateur radio notes were a part of this magazine.

by PHILIP WATSON

Older readers will remember Bill as the amateur notes contributor to the fore-runners of this magazine; "Wireless Weekly", "Radio and Hobbies", and "Radio Television and Hobbies". In the latter years these appeared under the heading "Amateur Bands with Bill Moore". It was a long association, commencing in 1933 and, with the exception of the war years, continuing until 1963.

Bill was born in 1911 at Crows Nest, NSW, the eldest of three children. He was educated at the Suspension Bridge Primary School, and a junior technical school where he obtained his Intermediate Certificate. A tertiary education had been planned but his father's death when Bill was 19 meant that he became the sole support of his mother, brother, and sister.

Having obtained his Junior Technical School Certificate he joined Metropolitan Water Sewerage & Drainage Board as an apprentice fitter and turner. He remained with the Board until he retired, 42 years later, as Chief Inspector, Testing and Inspection.

During his early teens Bill developed an avid interest in the then relatively new technology of wireless and in 1929, he joined the Wireless Institute of Australia. He obtained his amateur licence in July 1931 and in 1934 was elected federal president of the WIA, a position he held until 1938.

This interest in radio, which started purely as a hobby, was to assume a major importance in the years ahead. It not only aided him in his primary career — he conducted radio communication experiments for the Board in 1936 — but became the basis of his career in the RAAF with the outbreak of war.

Bill was a typical old-school amateur, brought up in an era when specialised amateur components were scarce and expensive, and the money to buy them even more limited. So Bill, along with

most of his contemporaries, learned to improvise and make do with whatever was available. Little did anyone realise the role this hard won experience was to play in the nation's war effort.

In 1934 Bill met Doreen Ashton at a social gathering at Wollongong. Fifteen months later, on April 13, 1935, they were married at St Michael's Church, Wollongong. Bill and Doreen would have celebrated their 50th wedding anniversary just 10 days after his death. Their son John was born in August, 1936.

In 1938 Bill joined the RAAF Wireless Reserve. On the outbreak of war on September 3, 1939 he was called up, and commenced duties on September 6, as an aircrew wireless operator. He embarked for Singapore on August 10, 1940 where he was attached to No. 8 Squadron in Northern Malaya. Early in 1941 he was seconded to the Royal Air Force and attached to their pioneering radar installation and maintenance unit.

Bill was responsible for the erection of radar stations throughout Northern Malaya. In April 1941 he was commissioned as a Pilot Officer and, in October, promoted to Flying Officer. As the Japanese advanced, he was responsible for destroying the radar stations he had installed. Still attached to the RAF, he was evacuated from Singapore to Java in February 1942. He was captured in March and held for three-and-a-half years in eight different prisoner-of-war camps. He returned home on September 30, 1945.

But it was while he was a prisoner of war that Bill's technical expertise and courage were to be fully demonstrated. Bill's exploits have been mentioned in a number of books covering the Singapore campaign and the Java prisoner of war camps. Typical is a quotation from "Saga of Achievement", by Group Captain D. R. Hall (retired).

"In March, 1942, all Air Force



Bill Moore, VK2HZ.

personnel remaining in Southern Java were assembled at Tasik aerodrome, prior to being moved as prisoners of war to barracks in Batavia. Flying Officer W. M. Moore, an RAAF radar officer, removed some command receiving equipment from Kittyhawk aircraft, a number of which were scattered about the aerodrome, either in a new or crashed condition. This receiving equipment was then smuggled into the camp in Batavia, where it was modified for operation from torch batteries.

"The radio was concealed in a hole in the floor of the barracks, formed by removing two tiles and excavating earth and replacing the tiles in position to give the impression of an undisturbed floor. While operating the set after dark, a tile was removed and an aerial was run up and connected to a wire strung across the room and used to support a mosquito net.

"Headphones were removed from the hole and Moore received the news bulletins from All India Radio, Delhi. Later, bulletins were received from the ABC and the BBC. Next morning the news bulletins were passed to a senior officer, who secretly disseminated the news to other prisoners of war.

"When batteries became scarce, small transformers were manufactured and the unit was rebuilt to fit into the bottom of two standard issue water bottles. A false bottom was installed in each water bottle to allow four inches of water and space below for the parts of the radio. This radio was used for 18 months, carried from camp to camp, and survived numerous searches by Japanese guards.

"In 1944 all water bottles held by prisoners of war were seized by the Japanese for use by native troops, so a new place of concealment had to be found for the radio. The final receiver was built into the heels of a pair of wooden clogs, which were standard footwear for prisoners of war. It was with this receiver that news was received

of the atomic bomb and the capitulation of the Japanese."

This was not only an extremely ingenious operation; it was also a very dangerous one. The Japanese would have taken less than kindly to the exercise and, had it been discovered, punishment would almost certainly have been severe. For this ingenious and courageous action Bill earned a "Mention in Despatches" and received an Oakleaf Emblem.

After the war Bill slipped quietly back into civilian life, resuming his job with the Water Board, his amateur activities, and his role as amateur correspondent for "Radio and Hobbies". Bill and Doreen had two more children; a daughter Lucile born in 1946 but who survived only a few days, and Bill born in 1949.

He continued to be actively interested in the WIA and was state president of the NSW Division for 1947 and 1948. In 1958 he was instrumental in forming the Blue Mountains Branch of the WIA and was secretary for its first decade and president for another four years until 1972.

Bill was a cheerful, quiet, unassuming bloke. Significantly, very few people outside his family and immediate friends knew of his colourful exploits as a POW; he was content to simply pick up where he had left off. While his original amateur interest had been on the HF bands he moved with the times and became a keen VHF operator, particularly on six metres. His quiet voice was instantly recognisable, and he was always ready to offer a word of advice or encouragement to those who needed it.

He was an active member of Legacy, and assisted many war widows through financial and personal crises over the years. He also played an active role in the local RSL sub-branch and, first as treasurer and then as president, helped pull it through a period of crisis.

And so, while it is primarily as an amateur that readers of this magazine will remember Bill, we should also think of him as a devoted family man, a brave soldier, and a community-minded individual ever ready to help those less fortunate than himself. Bill wouldn't have put it that way, but that is how others saw him.

Both amateur radio, and the community at large are the poorer for Bill's passing. He is survived by his wife Doreen, his brother John, and his sons John and Bill, to whom we extend our sincere sympathy. (PGW)

(Much of the above material, particularly the facts and dates of Bill's war service, were kindly supplied by his sons John and Bill, which we gratefully acknowledge.)

Jaycar

ELECTRONICS

JAYCAR

20% OFF

EVERYTHING


SALE

That's right! A last minute frantic sale before June stocktake. You can take **20%** off the current price of every item (even current June Specials in this magazine), but ONLY until:

Sorry! No deposits and no back-orders. Normal post and packing charges apply.

- remember, **20% off EVERYTHING!**

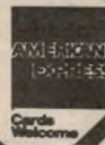Cash, Bankcard, American Express, Visa or Mastercard.



JAYCAR MAIL ORDER CENTRE
Orders to: **P.O. Box 480, AUBURN 2144**
OR any Jaycar store!
ONLY WHILE STOCKS LAST

MAIL ORDER HOT LINE

(02) 646 1300

The Daisywriter computer printer

For most computer applications there are only two choices of printer: Dot-matrix for speed and graphic capability or Daisywheel for letter quality. The Daisywriter reviewed here blurs that simple generalisation by being able to produce graphics output and by being quite fast, especially on columnar data.

by LEO SIMPSON

While there are now a number of relatively cheap Daisywheel printers on the market, the person or business who is interested in a new printer should consider those higher up the scale before making a purchase. One such printer which deserves consideration is the Daisywriter, made by the US firm, Computers International Inc. It offers the letter quality printout of a typical Daisywheel printer but incorporates many additional features to justify its higher price.

Certainly, it is quite an imposing unit compared to lower-priced Daisywheel and Dot-matrix printers. It is quite heavy too. Overall dimensions are 614mm wide, including the platen knobs, 374mm deep, not including the protruding data plug, and 260mm high with the standard single sheet plastic support. If a sheet feeder is used, it becomes more bulky again. Weight is 16kg.

The unit has a rugged but stylish plastic case in what now appears to be the mandatory off-white colour used by the IBM PC. If you're going to use this printer right next to an IBM though, you will need a large desk.

The basic printer mechanism is the same as used in the Brother HR-1 printer and EM-2 electronic typewriter. One of the interesting features of the mechanism is the linear induction motor used to propel the print-wheel and ribbon cartridge assembly along the platen. The linear motor consists of a fixed heavy steel rectangular section bar with a series

of tiny slots milled across its underside. A coil assembly, supported underneath the bar and attached to the printer head and ribbon carrier assembly, induces the travelling field into the bar. Power to the linear motor, printwheel motor and solenoid are carried via two flexible

How a Daisywheel printer works

For those not familiar with this sort of printer, they are similar in principle to the children's typewriters of many years ago. These had a printwheel containing all the characters. It was rotated by hand until the appropriate character was in place and then a single lever was struck to print it. The modern Daisywheel is about 75mm in diameter and has up to 96 "petals", each carrying one print character. It is rapidly rotated to select each character in accordance with the standard ASCII (American National Standard Code for Information Interchange) code. When each character is in position, a solenoid-driven hammer thumps the petal and ribbon onto the paper, printing it out.

The petals are rather fragile and easily broken off so a recent refinement in the Daisywriter model under review is the printwheel cassette which protects the wheel from damage during handling.

printed circuit cables.

Two user features which are sure to appeal are the fact that it uses the same ribbon cartridge as the IBM Selectric typewriter (which should always be readily available) and the easily loaded print-wheel which is protected in an integral see-through plastic cassette. Changing print-wheels while partway through a print-run is dead easy: just lift the plastic top-cover of the printer, press a grey lever near the print solenoid and the printwheel is simply lifted out. Drop the new wheel in, push the lever back, lower the top-cover and printing can resume. It can all take place in a few seconds.

The 96-character print-wheels are available in 25 languages and 25 font styles with printing pitch (dependent on the selected wheel) of 10, 12 or 15 characters to the inch. The print-wheels are rated for a minimum of 25 million impressions. That is equivalent to about 4000 1000-word documents.

The reason that the Daisywriter is claimed to have such a high print throughput is that it has no less than four Z-80 microprocessors. Three of these are used to control the page movement, to allow the machine to perform vector and dot graphics, since it can print 120 dots per inch (dpi) horizontally and 48 dpi vertically. The fourth processor is used to look ahead at data in the buffer, to anticipate white space, such as margins, tab stops, extra line spacing and so on. When these occur, the printer accelerates through the empty space, at an effective speed of 200cps, resulting in a significant increase in printing speed.

Printer buffer

The incorporation of a printer buffer also increases the printing speed, as well as freeing single-task computers such as the IBM PC for other jobs while printing is in progress. The maximum buffer capacity for the Daisywriter is 48K which sounds like a lot but long reports or articles can soon gobble it up. For example, the article on the Bridge



The Daisywheel printer offers a wide range of features, including subscript and superscript commands, bold or shadow printing and underlining. It is good value for money.

Adaptor on page 86 of this issue is about 2800 words and occupied just over 15K as a Wordstar file. On that basis, a 9500 word report would just about fill the buffer. Still, the Daisywriter would take about three-quarters of an hour to print out such a report. This is a long time for the computer to be tied up, which would be the case if the machine did not have such a large buffer.

However, the printer buffer does not always allow you to go on with other tasks. The problem is the noise of the printer itself, although this is not out of the ordinary as far as Daisywheel machines go. The first time I printed out a file and almost immediately got the message on screen telling me that as far as the computer was concerned, printing was finished. I thought, "beauty, I can get on with something else." But with the printer still belting through the text which had been loaded with such alacrity into its buffer, I could hardly hear myself think. I could not use the computer effectively. To make really effective use of the printer buffer, you would have to install the printer in another room or in a noise-proof enclosure.

It is also possible to reprint the contents of the printer buffer, using either a routine involving the Ready/Test and Top-of-Form buttons on the control panel or under software control. The buffer can be automatically reprinted up to 255 times under software control, which could be a handy feature where multiple original copies of documents are required.

The Daisywriter has a variety of

hardware and software settings. Controls on the front panel let the user select default settings for line spacing, page length (up to 109 lines) and pitch (10, 12 or 15, to suit the selected print-wheel).

By way of explanation, default settings are those employed by the printer unless instructed under software control to do otherwise. For example, under software control, it is possible to set page length up to 255 lines.

In addition, 24 DIP switches, hidden behind a small door, give the user control over a host of parameters. The switches select for continuous or single sheet feed paper, six or eight lines per inch, 16 different languages, baud rate, printer interface, auto line feed and eight different protocols. These allow the unit to emulate printers by NEC, Diablo, Qume, Centronics and IBM, as well as three different Daisywriter protocols.

The Daisywriter has subscript and superscript commands, as well as underlining, bold or shadow printing, and selection of black or red ribbon. Of course, to use these features your word-processing program must either already be capable of doing these by expecting an appropriate printer emulation provided by the Daisywriter, or by having the appropriate routines "patched in".

Most printers have only one interface, either serial or parallel, with one alternative interface usually available as an option. The Daisywriter is fitted with four: Centronics eight-bit parallel, IEEE-488, RS-232C and 20mA current loop. For the serial modes, bit rates are automatically selected from 50 to 19,200

baud, or selectable by front panel DIP switch or software.

Speed

The makers of Daisywriter point out that specs for printer speed in characters per second (cps) do not necessarily bear any relationship to actual throughput. On short documents I found the Daisywriter was comparable in speed to some nominally much faster dot-matrix printers, as it was when printing columnar data such as the table and spec panel of the Bridge Adaptor article referred to earlier. In fact, the manufacturers state that on this sort of printout the effective throughput of the Daisywriter can be as high as 40 cps.

It was only on long documents that the Daisywriter was noticeably slower than a typical dot matrix unit, but even so it was reasonable, at about 20 cps.

While I did not try it, the Daisywriter can also be used to plot charts and graphs. It does this by using selected petals (such as the "full stop") on the Daisywheel and by effectively moving the paper around to accomplish drawing. This would be very intriguing to watch but it would probably lead to premature wear on the selected Daisywheel petals.

Cut-sheet feeder

The Daisywheel has two optional-sheet feeders, one of which is suitable only for A4 or smaller paper sizes (Easifeed 230) or the other which is able to handle wide paper sizes (Easifeed 235). Both are available with a paper-out sensor. I tried the former model. I found it a little fiddly to set up as it has quite a lot of mechanical adjustments. Once set up though, using the helpful instruction booklet, it seemed to be quite reliable.

I should also note that the instruction book for the printer itself is very comprehensive and has helpful print exercises, plus good explanations of the error modes (indicated by a beeper) and control panel procedures. The section on the software commands is long and comprehensive.

Conclusion

The Daisywriter is an impressive product which would enable the best results to be obtained from most word-processors. Its overall quality and range of features make it good value for money.

Price of the Daisywriter with 48K buffer, universal interface and interface cable (available to suit a large range of computers) is \$1986 including sales tax. When supplied with the Easifeed 230 the price is \$2220 or \$2140 with the optional tractor feed mechanism.

For further information, contact PSI Daisywriter Products, 1-3 Atchison St, St Leonards, NSW 2065. Phone (02) 439 8086. (L.D.S.)

REVIEWS OF RECENT Records & Tapes

CLASSICAL • POPULAR • SPECIAL INTEREST



RAVEL & CHAUSSON

Piano Trio in A Minor. Piano Trio in G Minor. Beaux Arts Trio. Philips Digital Disc 411-141/1.

The first thing about this record to strike one is the nice broad tone of the piano, unlike the usual sharpish sound of a French instrument — at any rate those of an earlier generation. The next thing is the digital range which is much too wide for chamber music. A normal fortissimo means a whispered pianissimo.

(Permit me here the aside that the latest compact discs are showing a peculiarity in their sales. The makers' haste to establish a big market by putting out a torrent of mostly reprocessed issues has resulted in many new CD discs being offered by retailers at considerably less than the recommended price.) But back to the review.

The first movement of the Trio has hints of Ravel's justifiably popular quartet and also his *Daphnis and Chloe* which was composed soon after. But the Trio is a mature work built on a strong formal chassis. Yet with all its many merits I do not find it among one of Ravel's most attractive compositions. The second movement is dainty with a strangely lurching gait strongly reminiscent of one of the movements in *Daphnis and Chloe*. Uneven bar lines are much in evidence.

Everywhere the piano is dominant often too much so. It is not until the third movement that the pianist's low notes start to disappear into silence with the cello following it. The music is an adaption of a Malayan poem ingeniously transcribed. And here the round-noted piano shows up to full advantage. Towards the end of the movement with a normal dynamic gain setting there is much ear-stringing.

There are fountains of notes in the attractive, fast finale with the piano sometimes having things much too much its way.

The Chausson, composed a quarter of a century before the Ravel, reminds one of what happened to music in that comparatively short time. It reminds us that Chausson was strongly influenced by his teacher, Cesar Franck. The first movement is all very tuneful and elegant. The second is a dainty scherzo.



The third movement features a most beautiful cello solo though the piano again gets more than its full share of the production. Indeed the pianist adopts the air of a bully in some passages. But after many tries the music finally enters silence at the end of the movement.

The Finale follows, nicely flowing and fresh-minded. The piano again acts as soloist, leaving only scraps for the other players. Cyclic form — a la Franck is again dominant. By this time I had grown so fed up with the pianist that I felt inclined to tell him to shut-up. It is fitting that the picture on the record sleeve shows a gigantic piano keyboard with three tiny tail-suited musicians sitting on it. Throughout the trio the piano is either much too forwardly recorded or else played by an insensitive artist. I prefer to think the former. (J.R.)

WAGNER

Lohengrin. Complete opera. Peter Hofmann (tenor), Karen Armstrong (soprano) Leif Roar (baritone), Elizabeth Connell (mezzo-soprano) and others with the Bayreuth Festival Chorus and orchestra conducted by Woldemar Nelson. Five digitally recorded discs, CBS Masterworks 78503.

I like *Lohengrin* less than every other Wagnerian stage work except *Rienzi*. Wagner wrote it with an eye to instant popularity. He was at the time comfortably ensconced in a regular job in a provincial German opera house and decided he liked it that way. But his subconscious must have made him

uncomfortable by recalling thoughts of work that remained to him in developing music drama, and facing up to the gigantic task of getting on with the architecture of *The Ring*.

Removal from his sinecure was urgent. That is the only plausible explanation for his dangerous friendship with the anarchist Bakunin which led to his flight from Germany to Switzerland to avoid arrest by German police. There he settled down to the composition of *The Ring*, in which opera took an entirely new direction.

Lohengrin has a ridiculously sentimental story even by operatic standards. A knight in shining armour arrives in the nick of time to save a maiden in distress and after a romantic interlude is forced to desert her, to her dismay and death. During the evening he sings sentimental songs to a big bird and subdues two evil plotters before returning to his mysterious country of origin.

The opera is often tuneful but without true dramatic significance. The plot makes frequent references to the Holy Grail — the cup or bowl out of which Christ drank at the Last Supper. Indeed the sugary prologue depicts the Grail's descent to earth and its return to heaven. To Wagner's atheistic mind it was like some large object that comes down to earth, arrives to the accompaniment of a couple of cymbal crashes and takes off again like a miraculous yo-yo.

This lip service to piety occurs often in the hypocritical course of the opera. All the ingredients of popularity are there, arias sprinkled throughout, an exciting prelude to the third act and a wedding march still used in Christian wedding ceremonies. To even as convinced a Wagnerian as myself it is much too much.

The present recording was made live in Bayreuth in 1981 and the sound is good with only inconsiderable evidence of an audience's presence. Orchestra and choir are fine and the balance admirable. There is also, alas, the too wide dynamic range of digital recording that makes "pps" inaudible and "ffs" unbearable.

The soloists are less rewarding. The heroine, Karen Armstrong emits a pump-like vibrato reminiscent of an Eastern European soprano and the tenor, Peter Hofmann, matches her in

unsteadiness of production. There are many audiences to whom the magic of Wagner's name makes the work tolerable, but they need generosity to accommodate the poor standard of the soloists while still having the rest of the production first rate enough to compensate.

MOZART

**Piano Concerto in B Flat Major, K. 450
Piano Concerto in D Major, K. 451.
Murray Perahia (piano) with the English
Chamber Orchestra CBS Masterworks
Digital Disc D37824.**

There is an alternative issue by Ashjenzay which differs widely in its reading. Each has its own attractions. That I prefer the Perahia should in no way effect your choice. To make things easier I recommend both.

Perahia gives a transfixing classical performance of both sonatas. In the K. 450 Mozart frees the woodwind to give it its own important personality, though it is perhaps thematically ever so slightly inferior to its successor. Every bar of both concertos holds the attention. The relative importance of each performance is always questionable, the two differ so much from each other.

DEBUSSY & RAVEL

**String Quartet in G Minor. String
Quartet in F Major.
The Melos Quartet DGG Analog Disc
2531 203.**



This is an elegant beautifully balanced performance of both quartets. What I write about the Debussy, despite its superlatives, might well be suited to the Ravel.

The first movement of the Debussy is freely expressed but never gusty. The players' firm tone is immaculately reproduced. It slows down the tiniest bit sentimentally in the middle but quite without banality. And the ensemble is everywhere beautifully balanced.

The ensuing movement with its sharp pizzicatos is delightfully crisp and the following violin legato melody is taken pianissimo, instead of self-assertingly forte. Its high pitch gives it the necessary delicious prominence. The players' continuing unanimity proceeds uninterrupted. The rest of the work goes on in the same persuasive fashion. The listener need do nothing but relax and enjoy it.

A notable performance recorded in analog with a splendid dynamic range — full but never exaggerated, and exactly right for chamber music.

In the Ravel see above for the recording and performance. Do not judge the worth of this issue by the shortness of the notice. After having lauded its perfection what else is left to say?

“MESSIAH” ON CD

**Handel, Messiah: Favourite choruses
and arias. The Atlanta Symphony
Orchestra and Chamber Chorus, with
Layton James, harpsichord. Conducted
by Robert Shaw. Telarc compact disc
CD-80103. [From P. C. Stereo Pty Ltd,
PO Box 272, Mt Gravatt, Qld 4122.
Phone (07) 343 1612]**

Although this review appears rather belatedly, I first heard this disc, very appropriately, on Easter Sunday, when the events that inspired it were fresh in mind.

Booklet notes point out that, circa 1730/40, Handel's fortunes had fallen to a low ebb in London, especially with the failure of the Composer's Italian opera company. In consequence, he had turned to writing oratorios, in English, for stage rather than church presentation, using a mix of recitatives, arias, choruses and instrumental items.

“Messiah”, his ninth “commercial” oratorio, was written in just over three weeks and taken to Dublin for presentation, although Handel deliberately delayed the first performance for six months, anticipating (correctly) a build-up in public interest. Dubliners received it with great enthusiasm, but it took 10 years or more before gaining popularity in London.

As originally conceived, “Messiah” called for 40 singers and 40 instruments but, over the years, the number of performers has risen, on occasions, to hundreds and even thousands, providing a devotional, if not a musical “spectacular”.

For this recording, Robert Shaw uses resources of more Handellian proportions, better able to provide clarity of sound: 40 instruments, organ and 60 voices. Included are Karen Erickson and Syliva McNair (soprano). Alfreda



Hodgson (contralto), Jon Humphrey (tenor) and Richard Stilwell (baritone) — all American singers of note.

Telarc indicates in the notes that the complete work is available on two-set CD and LP albums but this single disc contains 22 “favourite choruses and arias”, edited unobtrusively into a composite 60-minute performance that certainly captures the traditional spirit of the work.

Helpfully, the scripture texts which form the basis of each item are listed in the notes.

The sound quality is generally excellent, although with just a touch of edginess on some of the more complex vocal passages. But my hunch is that those who buy this disc will do so for the content rather than ultimate technical perfection. (W.N.W.)

TRUMPET CONCERTOS

**Classical Trumpet Concertos. Ludwig
Guttler, with the Neues Bachisches
Collegium Musicum Leipzig, conducted
by Max Pommer. Compact disc,
Capriccio 10010 [From P. C. Stereo Pty
Ltd, PO Box 272, Mt Gravatt, Qld
4122. Phone (07) 343 1612]**

Digitally recorded in Leipzig in 1981, this recital was released last year on compact disc by Capriccio — a label relatively new to Australia. It carries trumpet concertos by Leopold Mozart, Johann Melchior Molter, “Anonymous” (an unidentified contemporary) and Joseph Haydn.

Composed in 1762, Mozart's “Concerto for trumpet, two Horns, Strings and Basso continuo in D-major” contains two movements totalling 11'12”. Consistent with trumpets and the baroque writing of the period, it is pitched almost entirely in the clarino (high) register, posing considerable difficulty for the soloist, even without the “singing” quality and specified slurs, which the work demands.

KALEX

UV MATERIALS

- Riston™ PCB
- 3M Scotchcal
- 3M INT

UV PROCESSING EQUIPMENT

KALEX LIGHT BOX

- Autoreset Timer
- 2 Level Exposure
- Timing Light
- Instant Light Up
- Safety Micro Switch
- Exposure to 22In x 11In

\$435.00 + ST
DELIVERED

KALEX "PORTU-VEE"

- UV Light Box
- Fully Portable
- Exposure to 10In x 6In

\$175.00 + ST
DELIVERED

KALEX ETCH TANK

- Two Compartment
- Heater
- Recirculation (by Magnetic Pump)
- Two Level Rack
- Lid

\$595.00 + ST
DELIVERED

RISTON 3000 PCB MATERIAL

SIZE INCHES	SINGLE SIDED	DOUBLE SIDED
36 x 24	49.50	62.70
24 x 18	24.75	33.00
18 x 12	13.75	17.60
12 x 12	8.80	11.80
12 x 6	6.00	6.45



plus sales tax if applicable.

KALEX

40 Wallis Ave.
East Ivanhoe 3079
Telex AA 37678
MELTON
(03) 497 3422

ELECTRONIC COMPONENTS & ACCESSORIES
● SPECIALIST SCHOOL SUPPLIERS

Records & Tapes

"Concerto for Trumpet, Violin, Strings and Basso continuo in E-flat major" (12' 30") has three movements: allegro, andante, allegro. While the composer is unknown, it typifies various mid 18th century compositions and, presumably in Guttler's view, "proceeds with good breeding and charm."

Molter's "Concerto No. 1 for Trumpet, Strings, and Basso continuo in D-major" (9' 13") also has three movements and would appear to have been composed in the mid 1740s, following the composer's return to Mannheim from Rome. Certainly, the Italian influence is evident.

As distinct from the three earlier concertos, Haydn's "Concerto for Trumpet and Orchestra in E-flat Major" (15' 12") took advantage of Weidinger's then new and improved trumpet, with its extended useable range, particularly in the lower register. With it came the demand and the opportunity for playing skills of quite a different kind: nimbleness and, as in the Adagio, the opportunity to

convey real emotion.

Curiously, the work was neglected after Haydn's death but was revived by the noted British trumpeter George Eskdale in the late 1920s. A version for the modern valve trumpet has become one of the most popular works ever for a brass instrument. It certainly provides a fitting — and a welcome — climax after the earlier emphasis on clarino baroque.

Ludwig Gutler, by the way, is currently professor at the Academy of Music in Dresden, has travelled as soloist with the Bach Orchestra and the Berlin Chamber Orchestra and, since 1969, has been resident trumpet soloist with the Dresden Philharmonic.

Manufactured by Sanyo in Japan, the recording itself provides clean, well balanced sound, with the trumpet always in the spotlight. It is not — nor should it be — an audio spectacular but it will appeal to those partial to small or chamber groups and, of course, to anyone interested in solo orchestral trumpet. (W.N.W.)

MORE OLD/NEW JAZZ

The *Legendary Jazzmen, Vol. 4*. Digitally re-mastered stereo and simulated stereo LP, double album. RCA VJL-20425.

Such has been the reception accorded the earlier three volumes in the "Legendary Jazzmen" series, that RCA have now released volume 4, a double-album set. And it certainly doesn't let the series down, despite the mounting problem of locating further suitable (and available) originals from the archives and from private record collections.

As with the earlier re-mastered old-time jazz recordings, reviewed in these columns during the past few months, the man responsible for the technical — and musical — resurrection of this latest set is broadcaster and recording engineer Robert Parker. With the aid of a Packburn de-noiser to get rid of surface clicks, skilful panel work to recapture the original dynamic range, a reverb unit, an Orban Parasound stereo synthesiser and a Sony digital recorder, he creates a new master and recordings which would almost certainly sound far better than even pristine pressings of the day.

And they are startlingly good. "Sugar" (side 3, track 1) featuring Adrian Rollini on sax, was recorded in 1927 but it certainly doesn't sound that way; and much the same remark applies to other tracks from the same era.

For orderly presentation, the contents

of the volume, amounting to 30 tracks in all, are arranged and presented under four headings: The Brass, The Reeds, The Rhythm and The Arrangers.

About half the tracks come from '78s from the late '20s and '30s, with the odd tape in stereo from the '60s. Others in between are from unidentified originals but all have had the "Parker" treatment, ensuring a surprising consistency in balance from track to track.

The personnel involved are listed for each item; in addition, there are biographies and, in most cases, pictures of the featured artists. With so many tracks, it is not practical to list the titles but few would be likely to question the joint judgment of recordist Robert Parker and producer Ron Wills.

Well worth the purchase price if you're into jazz! (W.N.W.)



COUNTRY GOSPEL

Just a closer walk. Alan Hawking. Stereo LP album, RCA Victor VPL1-0473.

With his brother Russell, since deceased, Alan Hawking made his debut on disc in 1955, featuring the Hawking Brothers. About the same time, he was a member of the "Trailblazers", an early Melbourne concert group. Since then, he has performed at venues ranging from the Sydney Opera to the Grand Ole Opry (USA), has toured with top-line American artists, and twice represented Australia at the International Show of the American Country Music Association at Nashville.

As might be expected, this whole album is presented in simple, relaxed, country style, with lead vocal, harmony, drums, bass, guitars, harp and banjo.

What is surprising is that, apart from some high harmony by Jane Hawking on one track, everything from the

arrangements to the vocals and instrumental support was provided by Alan Hawking himself, using multi-recording.

There are 12 tracks, all with Gospel themes well known on the C&W scene: Just a Closer Walk — It Is No Secret — The Three Bells — One Day at a Time — The Old Rugged Cross — Amazing Grace (instrumental) — How Great Thou Art — Just For Today — Scarlet Ribbons — In His Hands — Where I'm Going — Gospel Train (instrumental).

The whole presentation is notably tuneful and restful, with excellent diction and with a lot of potential appeal to anyone who just likes to relax and listen to this sort of middle-age Gospel music. Even if you do doze a little, the final track "Gospel Train" will wake you up again with a spot of very adept one-man blue-grass rhythm.

The technical quality is good and I'd be surprised if Alan Hawking didn't make quite a few new friends with this one. (W.N.W.)

ROCK DEVOTIONAL

MetroBand Live. Directed By Thurlow Spurr. Stereo LP album, Light LS-5842. (From Word Records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135. Phone (03) 729 3777).



Whatever other claims to fame the MetroChurch (Edmond, Oklahoma, USA) may have, they can certainly be proud of the church band, featured on this album. "It is equally at home", says the jacket, "playing Count Basie style Big Band, Pete Fountain New Orleans Dixieland, or a reasonable facsimile of a Salvation Army street band."

In this "live" concert performance, they set out in a very professional manner to demonstrate that the claim is justified. Listening to the solos in a couple of the tracks, I was reminded of a Sydney jazz trumpeter friend who

explained to me one day that: "you lose your job if anyone, during your solo, gets to recognise the melody!"

In a wide variety of arrangements, some by members of the band, they present eleven tracks based mainly on traditional hymns:

I Go to the Rock — Leaning on the Everlasting Arms — He Lives — Jesus Saves — We Will Stand — When the Roll is Called up Yonder — There is Power — When We All Get to Heaven — Love Lifted Me — Victory in Jesus — Jesus Medley.

The sound quality is excellent and the album should appeal strongly to anyone interested in orchestral gospel arrangements. I'm not quite so sure about the elderly lady whom the compere imagines might be discovered, late at night, enjoying these grand old hymns of the church. Unless she's been raised on a diet of big band dixieland, she mightn't even recognise some of them!

But, for what it is, it's good (W.N.W.)

"BIG BAND" GOSPEL

Straight Ahead. Amy Grant. Stereo LP album, Myrrh SPCN-7-01-675706-4. (From Word records Aust, 18-26 Canterbury Rd, Heathmont, Vic 3135. Phone (03) 729 3777.)

This is very much an album for the "now" generation, or at least for that section of it that's turned on by the sound of Gospel rock music. One generation on, and churchgoers tend to be less enamoured by rock rhythm,

"SO WHAT'S NEW IN CRS?"

...THE ANSWER IS IN THE PALM OF YOUR HAND

Now you don't have to leave your communications behind when you leave your vehicle. The ICOM IC-40 is a compact 40 channel UHF CRS field proven hand held, with optional 3 Watts output power, the same as many

mobile radios.

The IC-40 is perfect for jobs on the land, water or business.

Contact your local dealer for a demonstration of the most advanced CRS portable available in Australia.



Please post to:

ICOM AUSTRALIA PTY. LTD.
7 DUKE STREET WINDSOR 3182.
VICTORIA.

Name _____

Address _____

City _____ Postcode _____

or phone ICOM on (03)51 2284

 **ICOM**
The World System

IC0012

Records & Tapes

especially as delivered by over-powered amplifiers and accompanied by lyrics, identified as "devotional" mainly by the title!

These remarks are not meant to detract in any way from the evident talent or the dedication of Amy Brown and the musicians supporting her in this new album. They are very capable and undoubtedly very sincere but, as I said, their music will appeal primarily to the younger generation of Gospel record buyers.

Diction is about average for this kind of performance but, to forestall any doubts on this score, the inner jacket carries the lyrics in full, plus the credits for each track. Amy Grant's name appears several times against words and/or music — a further indication of her talents.

The track titles: Where Do You Hide Your Heart? — Jehovah — Angels — Straight Ahead — Thy Word — It's Not a Song — Open Arms — Doubly Good to You — Tomorrow — The Now and the Not Yet.

The sound quality of the album is well up to standard and, if Amy Grant happens to be your pin-up favourite among Gospel vocalists, you will find a signed, eye-catching full-colour portrait inside, to go with the music! (W.N.W.)

FLAWLESS FLUTE

In the Pink. James Galway and Henry Mancini, with the National Philharmonic Orchestra. Stereo LP, Starcall SFL1-0117. Distributed by RCA.

One might be excused for concluding that, as a musician and entertainer, James Galway can't put a foot wrong — or maybe, can't put a lip wrong! Whether faced with a classical or a popular program, he always manages to live up to expectations.

This disc is no exception and will certainly not disappoint James Galway's many fans.

It opens with the jaunty "Pink Panther" theme, followed by "Maggie's Theme", the latter marked by Galway's superbly controlled sound. At the other extreme is the dazzling virtuosity displayed in "Speedy Gonzales". "Pennywhistle Jig" and "Pie in the Face Polka" provide their own brands of rhythm, while "Baby Elephant Walk" is different again, played on a penny-whistle!

Other track titles include: Breakfast at Tiffany's — Crazy World — "Thorn Birds" Theme — Two For the Road — "The Molly Maguires" Theme — Mancini/Mercer Medley — Cameo for Flute.



Henry Mancini, composer (or joint composer) arranger and conductor provides a backing that complements but never competes with Galway's flute. The technical quality is excellent and, all told, it adds up to a very tuneful and listenable album. Recommended (W.N.W.)

VOCAL DUO

Only You. Renee & Renato. Stereo LP album, Starcall SFL10111. (Distributed by RCA).

As with their earlier recording "Just One" (reviewed by GS in March '84) this latest album is again virtually devoid of jacket notes. Yes, it was recorded in Hollywood in 1984 for the Hollywood label and is distributed by Starcall/RCA — but the orchestra, chorus and conductor receive not a mention.

From the names, accents and a couple of pleasant but modest cover pictures, one might conclude that Renee is English, with a touch of French. Renato presumably has an Italian background and a penchant for the Italian operatic style, which he uses to good effect.

Undoubtedly, the European touch adds its own appeal to this further album of middle-of-the-road romantic songs, rounded off by what is probably a "message" track: "Jesus Loves Us All". The remaining titles are:

Volare — Come Prima — Love Letters — Anniversary Waltz — Blue Serenade — Only You — Save Your Love — Falling in Love — If Love Is Not the Reason — I Wanna Give You Love.

Technically, the sound is good and, overall, the album should have a ready appeal to those who prefer middle of the road popular music (W.N.W.)

Ian J. Truscott's **ELECTRONIC WORLD**

MORE & MORE

People are discovering us each week. Both the home enthusiast through to the small manufacturer.

★ ★ ★

Motorola and national data books, wima capacitors, vero and riston printed circuit boards. Amidon toroids

Components for the hobbyist and radio amateur.

COMPONENTS • TOOLS • KITS

In any quantity, buy one, or one thousand, we're happy to oblige

SCHOOLS • CLUBS • ETC.

For all your electronic needs, see us.


Inquire about our bulk discount deals

Save yourself a trip to the city — come to

30 LACEY STREET CROYDON OR PHONE (03) 723 3860/723 3094


Mail orders welcome.

PCB TRANSFORMERS

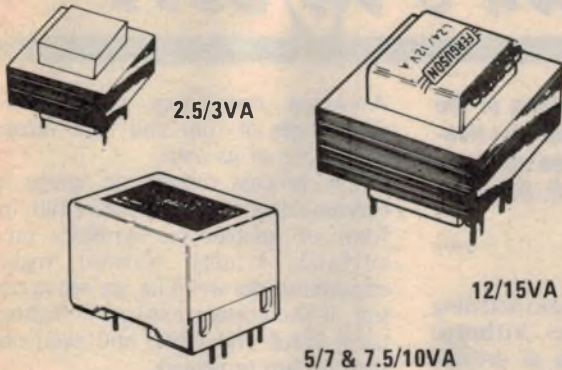


- Manufactured to AS3126 and Telecom approved
- Suit standard PCB grids and simplify construction

POWER TRANSFORMERS

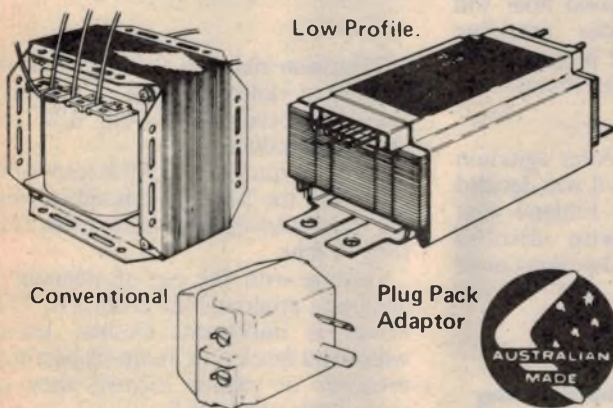

- Wide range of secondary voltages from 1.5V to 115V
- Stock range has ratings up to 1000VA
- Special types for microprocessors, 115V etc

AUDIO TRANSFORMERS

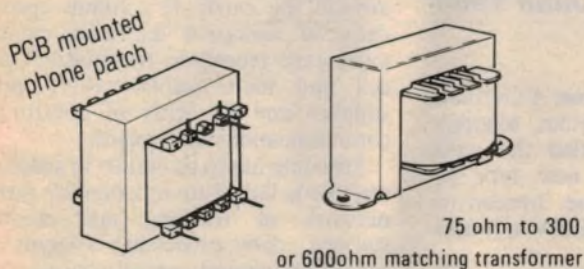

- Line and Matching transformers up to 150W
 - Power transformers for high power amplifiers
 - Transistor drivers
 - Special 'C' core transformers
- Ask for MAL VK2BMS or DOUG VK2BPX

TALK TO FERGUSON - THE AUSTRALIAN COMPANY
WITH NEARLY 50 YEARS EXPERIENCE OF MANUFACTURING
IN AUSTRALIA FOR AUSTRALIAN CONDITIONS

Ferguson Transformers Pty. Ltd.
331 High Street, Chatswood 2067. Tel: (02) 407-0261.
Telex: AA25728. Melbourne: (03) 561-6699.

FERGUSON

Next month in Electronics Australia



Megohm Meter

Featuring an in-built transistor inverter power supply, this Megohm Meter tests at 1000V and covers the range from 2MΩ to 2000MΩ. It is particularly handy for checking electrical wiring. Details in July *Electronics Australia*.

Infrared Remote Control

Next month, we intend to describe an infrared remote control for the Dick Smith Teletext Decoder. It requires very few extra parts, is easy to build and duplicates all the control keys on the original wired unit.

Surface Mounted Components

Don't miss our exclusive article on surface mounted technology. Our article looks at the various component types and describes how they are mounted onto PC boards.

Hifi Reviews

We take a look at the Luxman L-215 stereo amplifier and the Spectrum V1.2 loudspeaker system.

**Although these articles have been prepared for publication, circumstances may change the final content.*

50 and 25 years ago...

"Electronics Australia" is one of the longest running technical publications in the world. We started as "Wireless Weekly" in August 1922 and became "Radio and Hobbies in Australia" in April 1939. The title was changed to "Radio, Television and Hobbies" in February 1955 and finally, to "Electronics Australia" in April 1965. Below we feature some items from past issues.



June 1935

Perfect silence impossible: The impossibility of producing perfect silence has been demonstrated recently by engineers at the General Electric Company.

The engineers constructed a small box-like room inside one of the laboratories. The floors, ceilings and walls of the inner room were suspended on springs. This room was then padded inside and out with sound absorbing materials.

When the room was completed, a sensitive meter placed inside it detected sounds averaging about 14dB.

Egg lark: Engineers at station WOR, New Jersey, found a lark in a nearby meadow which had built a nest in a discarded coil of wires; while the 50kW transmitter was working, the lark went about other business, leaving the eggs unattended.

The eggs hatched out all right because while the transmitter was working, the coil picked up just enough heat to keep the eggs warm, which may be just a lark, as may the bit about other larks who tried the same thing but selected coils with too much wire in them, so that the eggs were cooked.

Television standards: There appears to be a great deal of uneasiness in the trade in London regarding television. Whilst every manufacturer is hastily reassuring his clients that present day sets will still be of use three or four years hence, there is a feeling that this is more a hope than a statement of fact.

The BBC is at the moment in a state of change, their 38 line transmissions are coming to a close in the very near future. Germany works on the 180 line picture and English authorities will either go to this or increase the lineage to 240.

Radio in every room: A radio listening installation on a scale hitherto unattempted in Australia is at present being placed in the new building of the Hotel Australia.

By means of an AWA system of centralised radio reception, programs from eight Sydney metropolitan stations will be available to guests in every room. A radio room on the second floor will accommodate the master receiving apparatus from which the programs will be distributed to the guests' rooms.

Musicians redundant: After agitation by unemployed musicians it was decided by the Government of Finland that restaurant owners who dismiss orchestras and install loudspeakers must pay a fixed monthly sum to the Musicians' Union.



June 1960

Car engine without pistons: A German company making motorcycles, scooters and Prinz cars has startled the auto world with an entirely new type of internal combustion engine. Instead of pistons that shuttle up and down, it uses a tricky three lobed rotor.

A cross between the ordinary internal combustion engine and a turbine, it promises twice the power from the same weight and size as conventional engines.

The potent package is a rotary gasoline engine, an engineering will-o'-the-wisp that has eluded inventors for generations. It has apparently been captured at last by the NSU Werke.

Hot movies: A new thermoplastic recording process developed recently in the General Electric laboratories in

America combines most of the advantages of film and tape recording with some of its own.

The process records an image on a thermoplastic layer on tape or film in the form of microscopic wrinkles on the surface. Under normal lighting conditions, the wrinkles are not apparent but, if the correct method of lighting is used, black and white and even colour pictures are projected.

The film consists of three layers. The thickest layer is the base material, which is about as thick as conventional movie films. Over this is coated a layer of conducting plastic, and finally the low melting point thermoplastic layer.

Television violence: Rules to limit the amount of violence shown on television have been codified by the BBC and issued to producers.

A large number of American series offered to the BBC are refused as being too brutal. Accepted cuts are made from time to time.

Dealing with the use of weapons in children's programs the code says: "The choice is important. Coshes, knives, whips and bottles are more suspect than revolvers or swords because they are more easily available."

Weather satellite: The United States weather satellite "Tiros" constitutes what is probably the most elaborate electronics package yet sent into orbit around the earth. It contains specially designed miniature television cameras, video tape recorders, transmitters, solar cell and rechargeable battery power supplies and an array of control and communications equipment.

Speeding along its course in space, the satellite is linked to an extensive ground network of tracking and receiving stations, data processing systems and programming and control centres.

Colour TV camera: A new EMI colour camera uses three vidicon tubes and an optical system — several times more efficient than relay lens systems — which has been designed so that the maximum amount of light falls on the photo-conductive surfaces of the vidicon.

The versatile design makes the system suitable for broadcasting and telecine transmissions, as well as for use in industry and medicine.

COMPUTER BOARDS

THE NEW ZRT-80 KIT

CRT TERMINAL BOARD!

A LOW COST Z-80 BASED SINGLE BOARD THAT ONLY NEEDS AN ASCII KEYBOARD, POWER SUPPLY AND VIDEO MONITOR TO MAKE A COMPLETE CRT TERMINAL USE AS A COMPUTER CONSOLE, OR WITH A MODEM OR USE WITH ANY OF THE PHONE-LINE COMPUTER SERVICES.

FEATURES:

- Uses a Z80A and 6845 CRT Controller for powerful video capabilities.
- RS232 at 16 BAUD Rates from 75 to 19,200.
- 24 x 80 standard format (60 Hz)
- Optional formats form 24 x 80 (50 Hz) to 64 lines x 96 characters (60 Hz).
- Higher density formats require up to 3 additional 2K x 8 6116 RAMS. Uses N S INS 8250 BAUD Rate Gen. and USART combo IC.
- 3 Terminal Emulation Modes which are Dip Switch selectable. These include the LSI-ADM3A The Heath H 19 and the Beehive.
- Composite or Split Video.
- Any polarity of video or sync.
- Inverse Video Capability.
- Small Size: 6.5 x 9 inches.

BLANK PCB WITH 2716 CHAR. ROM. \$159

2732 MON. ROM. \$299

ZRT-80 WITH 8 INCH SOURCE DISK \$299
SOURCE DISKETTE - ADD \$20
SET OF 2 CRYSTALS - ADD \$12

LS100

256K S100 SOLID STATE DISK STATE DISK SIMULATOR

CALLED THE "LIGHT-SPEED 100" BECAUSE IT OFFERS AN OUTSTANDING INCREASE IN YOUR COMPUTER'S PERFORMANCE WHEN COMPARED TO A MECHANICAL FLOPPY DISK DRIVE.

FEATURES:

- 256K on board, using +5V 64K DRAMS.
- Uses new Intel 8203-1 LSI Memory Controller.
- Requires only 4 Dip Switch. Selectable I/O Ports.
- Runs on 8080 or Z80 S100 machines.
- Up to 8 LS-100 boards can be run together for 2 Meg. of On Line Solid State Disk Storage.
- Provisions for Battery back-up.
- Software to mate the LS-100 to your CP/M 2.2 DOS is supplied.
- The LS-100 provides an increase in speed of up to 7 to 10 times on Disk Intensive Software.

Full 256K Kit Including Tax \$799



THE LITTLE BIG BOARD

FEATURES:

- Z80A CPU (4 MHz)
- 65,536 bytes of RAM
- Two RS232C I/O ports
- Battery back up realtime clock and calendar.
- Up to four, 8 inch or 5.25 inch double sided double density or single density floppy disk drives
- Full STD Bus
- Designed for CP/M MP/M and CP/NET systems

Cat # (including tax) \$459



6809 "UNIBOARD" NEW SINGLE BOARD COMPUTER KIT!

Many software professionals feel that the 6809 features probably the most powerful instruction set available today on ANY 8 bit micro. Now, at last, all that immense computing power is available at a truly unbelievably low price.

CHECK THE FEATURES!!!

- 64K RAM using 4116 RAMS
- 6809E Motorola CPU
- Double Density Floppy Disk Controller for either 5 1/4 or 8 inch drives. Uses WD1793.
- On board 80 x 24 video for a low cost console. Uses 2716 Char. Gen. Programmable Formats. Uses 6845 CRT Controller.
- ASCII Keyboard parallel input interface (6522).
- Serial I/O (6551) for RS232C or 20 MA loop.
- Centronics compatible parallel printer interface (6522).
- Bus expansion interface with DMA Channel (6844).
- Dual timer for real clock application.
- Powerful on board system monitor (2732). Features commands such as Go To, Alter, Fill, Move, Display, or Test Memory. Also Read and Write Sectors, Boot Normal, Unknown, and General Fix.
- PC board is double sided, plated through solder masked, 11 x 11 1/2 inch.
- Includes the powerful 3rd generation Motorola 6809 Processor ideal for colleges, O.E.M.'s, industrial and scientific uses!

BLACK PC BOARD WITH PAL'S AND TWO EPROMS \$199

5 1/4 OR 8 INCH SOURCE DISKETTE ADD \$25

plus tax

COMPLETE KIT FULLY SOCKETED, ALL OPTIONS ARE STANDARD, NO EXTRAS TO BUY \$599

including tax

Please allow 4 weeks for delivery

YOUR CHOICE OF POPULAR DISK OPERATING SYSTEMS

FLEX 1m from TSC Cat \$359

OS9 1m from Microwave Cat \$459

(Please specify 5 1/4 or 8 inch)



THE ORIGINAL BIG BOARD 1 COMPUTER KIT!

FEATURING:

- 64K RAM. Uses industry standard 4116 RAM. All 64K is available to the user, our VIDEO and EPROM sections do not make holes in system RAM. Very special care was taken in the RAM entry PC layout to eliminate potential noise and glitches.
- Z-80 CPU. Running at 2.5 MHz, handles all 4116 RAM refresh and supports Mode 2 INTERRUPTS. Fully buffered and runs 8080 software.
- BASIC I/O. Consists of separate parallel port (Z80 P10) for use with an ASCII encoded Keyboard for input. Output would be on the 80 x 24 Video Display.
- 24 x 80 CHARACTER VIDEO. With a crisp, flicker-free display that looks extremely sharp even on small monitors. Hardware scroll and full cursor control. Composite video or split video and sync. Character set is supplied on a 2716 style ROM, making customized fonts easy. Sync pulses can be any desired length or polarity. Video may be inverted or true. 5 x 7 Matrix, upper and lower case.
- FLOPPY DISK CONTROLLER. Uses WD 1771 controller chip with a TTL Data Separator for enhanced reliability. IBM 3740 compatible. Supports up to four 8 inch disk drives. Directly compatible with standard Shugart drives such as the SA800 or SA801. Drives can be configured for remote AC off/on. Runs CP/M 2.2.
- PFM 3.3 ZK SYSTEM MONITOR. The real power of the Big Board lies in its PFM 3.3 on board monitor. PFM commands include Dump Memory, Boot CP/M, Copy Exam, Fill Memory, Test Memory, Go To, Read and Write I/O ports, Disk Read (Drive Track Sector), and Search PFM. Copies one of the four 2716 EPROM locations provided.
- FULLY SOCKETED.

Ideal for OEM Industrial Business, Scientific, Colleges etc.

Cat # K41001 including tax \$379

OPTIONS AVAILABLE:

- CP/M 2.2 FOR BIG BOARD \$269
- TWO PORT PARALLEL I/O \$19
- SERIAL I/O \$35
- REAL TIME CLOCK \$15
- DOUBLE DENSITY ADAPTOR BOARD \$225
- BIOS DISK \$25



RITRON MULTI PURPOSE MODEM

We goofed with the multi modems you wanted, because we were unable to get supplies, however we now have something better and at the same price! Our New RITRON Multi Purpose Modem has arrived and has all the standards you require. Just check the Ritrone's features!

- CCITT V21 300 Buad Full duplex
- CCITT V23 1200/75
- Bell 103 300 Full duplex
- Bell 202 1200 Half duplex
- Auto answer, auto disconnect
- Telecom Approval No. C84/37/1134


A better modem for the same price!

\$399

★ ★ ★ ★ ★ ★ ★ ★
We stock a full range of computer connectors!
★ ★ ★ ★ ★ ★ ★ ★

IC SPECIALS

	1-9	10+
8085	4.95	4.00
8155	4.95	4.00
8156	4.95	4.00
8212	1.95	1.75
8224	2.95	2.50
8226	2.50	2.00
8253	4.50	4.00
8255	4.50	3.95
8257	4.95	4.00
8259	4.95	4.00
8279	4.95	4.00

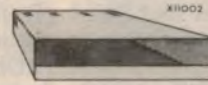

COMPUTER AND DISK DRIVE CASES AND POWER SUPPLIES


5 1/4" DRIVES

1 x 5 1/4" Slimline Drive Case	
X11001 Bare Case	\$49
X11011 Case and Pwr Supply	\$89
2 x 5 1/4" Slimline Drive Case	
X11001 Bare Case	\$69
X11012 Case & Pwr Supply	\$139
1 x 5 1/4" Standard Drive Case	
X11003 Bare Case	\$39
X11013 Case and Pwr Supply	\$89
2 x 5 1/4" Standard Drive Case	
X11004 Bare Case	\$59
X11014 Case & Pwr Supply	\$129


8" DRIVES

1 x 8" Standard or 2 x 8" Slimline, and computer Case (BB1)	
X11006 Bare Case	\$99
X11016 Case & Pwr Supply	\$395
2 x 8" Slimline Drives and Computer Case (BB1 and BB2 etc)	
X11007 Bare Case	\$145
X11017 Case & Pwr Supply	\$395
1 x 8" Slimline Drive Case	
X11020 Bare Case	\$95
X11022 Case & Pwr Supply	\$149
Dual 8" Slimline Drive Case	
X11025 Bare Case	\$99
X11026 Case & Pwr Supply	\$245
1 x 8" Standard Drive Case	
X11009 Bare Case	\$99
X11019 Case & Pwr Supply	\$139
5" Hard Disk Drive Case	
X11030 Bare Case	\$139
X11032 with Pwr Sup & Fan	\$475
5" Dual Slimline	
Room for BB2 etc. under drives	
X11005 Bare Case	\$149
X11015 Case & Pwr Supply	\$399

Errors and Omissions Excepted

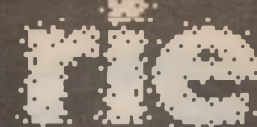

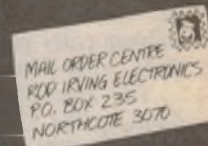Rod Irving Electronics
425 High Street,
NORTHCOTE, 3070
VICTORIA, AUSTRALIA
Phone (03) 489 8866
TELEX: AA 38897
48-50 A Beckett Street,
MELBOURNE, 3000
VICTORIA, AUSTRALIA
Ph. (03) 663 6151
Mail Order and
correspondence:
P.O. BOX 235
NORTHCOTE 3070



or phone ...

MAIL ORDER HOT LINE



(03) 481 1436



POSTAGE RATES

\$1-\$9.99	\$2.00
\$10-\$24.99	...	\$3.00
\$25-\$49.99	...	\$4.00
\$50-\$99.99	...	\$5.00
\$100-\$199	\$7.50
\$200-\$499	...	\$10.00
\$500 plus	...	\$12.50

This is for basic postage only, Comet Road freight, bulky and fragile items will be charged at different rates.

Certified Post for orders over \$100 included "free"! Registered Post for orders over \$200 included "free"! Account orders from schools, Government Departments, Public Co., gratefully accepted. (Min. order of \$20).



CICADA 300
• 300 baud
• Provides full 12V bipolar output signal
• Direct connect modem
• Full duplex operation (Phone not included)
Cat # X19101 \$180

NEW FOR BB II!
Menu driven EPROM programming software, will program 2716, 2732, 2764.
\$49

BIG BOARD II OVER 1,000 SOLD!

Jim Ferguson designer of the "Big Board" distributed by Digital Research Computers, produced this stunning computer "Big Board II".

FEATURES

- 4 MHz Z80 CPU AND PERIPHERALS CHIPS. The Ferguson computer runs at 4MHz. Its monitor code is learn, uses Mode 2 interrupts and makes good use of the Z80 A DMA chip.
- 64K RAM + 4K STATIC CRT RAM. 24K (EPROM OR STATIC RAM). "Big Board II" has the three memory banks the first memory bank has eight 4164 RAMs that provide 60K of user space and 4K of monitor space. The second memory bank has two 2K and 8 5RAMs for the memory mapped CRT display and space for six 2732s or 2K x 8 static RAMS, or pin compatible (EPROMs). The third memory bank is for RAM or ROM added to the board via the STD bus. Whether bought as a bare board a full kit or assembled and tested, it comes with a 450nS2732A EPROM containing the monitor.
- MULTIPLE DENSITY CONTROLLER FOR 5 1/4" FLOPPY DISKS. The "Big Board II" computer has a multiple density disk controller, it can use 1793 or 8877 controller chips. The board has two connectors for disk signal with 34 pins for 5 1/4" drives, the other with 50 pins for 8" drives.
- VASTLY IMPROVED CRT DISPLAY. The "Big Board II" computer uses a 6845S CRT controller and 8002 Video Attributes controller to produce a display that will rival the display of quality terminals. Characters are formed by a 5 x 7 dot matrix on 15.75 kHz monitors and a 7 x 9 dot matrix on 15.75 kHz monitors. The display is user programmable with the default display 24 lines of 80 characters.
- STD BUS CONNECTOR. "Big Board II" brings its bus signals to a convenient place on the PC board where users can solder a STD socket; bus cards can be plugged directly into it, and it can as well be connected by bus cable to industry standard card cages.
- A Z80 A S1010 = TWO ASYNCHRONOUS/SYNCHRONOUS SERIAL PORTS.
- TWO Z80A CTCS = EIGHT PROGRAMMABLE COUNTERS/TIMERS. The "Big Board II" has two Z80 A CTCS. One is used to clock data into and out of the Z80 A CTCS. One is used to clock data into and out of the Z80 A S1010, while the other is for systems and application use.
- PROGRAMMING CIRCUITRY AND SOFTWARE. The "Big Board II" computer has circuitry and drivers for programming 2716s, 2732As, or pin compatible (EPROMs). (Software \$25 extra).
- CP/M CAPABILITY. CP/M with Russell Smith's CBIOS for the "Big Board II" is available for the "Big Board II" (plus tax) \$230. The CBIO5 5" or 8" is avail. separately.

Cat # K41015


NOW \$595

(plus tax)

Less 10% for 3 or more!

Assembled and Tested \$849

(plus tax)

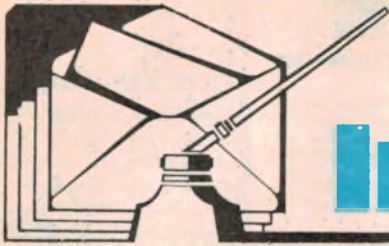

Information centre

Substitute transistors for Playmaster 136

A few years ago, I constructed the Playmaster 136 amplifier (EA Dec 1972). It worked extremely well and I subsequently passed it on to one of my sons, while I went on to bigger things.

The amplifier has now developed a fault in the left output transistors, viz AY8171 and AY9171. The problem is that I cannot obtain these transistors anywhere, and nobody apparently can give me the equivalents. Can you help?

Recently, I also built the stereo synthesiser published in EA in December 1982. The 470pF capacitor across switch S3 had been devalued by the kit supplier from the 2kV specified to 1kV. On completion of the unit, a dreadful mains hum was present and the LED indicator light refused to go out. Needless to say it was the 470pF 1kV which was at fault.

My problem is that I cannot find the correct capacitor at the various outlets although I have tried.

I am looking forward to building your

latest Playmaster Series 200, and I hope that I can purchase a kit exactly as you specify. (R.H., Carlingford, NSW).

● We suggest that you use a TIP318 for the AY8171 and a TIP328 for the AY9171. These TO-126 style transistors can be bolted directly to the top of the heatsinks and their emitter and base leads bent at right angles so that they pass through the appropriate holes.

As far as the stereo synthesiser is concerned, we are surprised that the 1kV capacitor should fail. We suggest that you contact George Brown & Co Pty Ltd, 174 Parramatta Rd, Camperdown, NSW 2050. Phone (02) 519 5855.

Problem with tacho/dwell meter

I would appreciate any advice you can give me on these problems to do with the Tacho/Dwell Meter (EA, July 1983).

(1) The kit purchased from Jaycar did not include a voltage dependent resistor (VDR). The result of an enquiry to Jaycar was inconclusive and they had no

VDR for sale. Dick Smith had two VDRs for sale. One was too large to fit in the case; I bought and fitted the smaller.

When the meter was switched to tacho mode and connected between the negative end of the coil and chassis earth, the engine stopped (possibly the resistance of the VDR with 5.5V across it went too low and virtually shorted the coil to earth). The VDR has since been removed. Can you tell me:

(a) the type number of the correct VDR; or

(b) the type number of an acceptable alternative; or

(c) the characteristics of an acceptable type and where to buy it.

(2) When used to measure resistance on the 20 Ω range, the readings change in a random manner at intervals of about one second. A typical series of readings would be, when measuring a 10% resistor: 09.7, 10.1, 09.8, 10.2 etc. The soldered joints appear to be satisfactory, there are no bridges between tracks, diodes D5 and D6 have been checked (with an ohmmeter), and the thermistor appears to be satisfactory (it measured 1.06k Ω at room temperature, about 23°C) and the range resistors appear to be satisfactory.

As I have previously built the Capacitance Meter (EA, March 1982) and the 3½ Digit Multimeter (EA, March 1983), and both worked from the start, I would appreciate any advice you could give me. (T.C., Bexley North, NSW).

● An examination of previous tacho circuits published in EA shows that none have used a VDR and it is not really necessary. The circuit should work without it.

As far as the problem of measuring resistance is concerned, we suggest that you check that the four position slide switch has low contact resistance, as this can affect the readings.

Infrared remote control

I have built the Stereo Infrared Remote Control (EA, October 1979) which has been working well for 12 months. Recently, I decided to make the modification which appeared on page 116 of the January 1980 issue.

I have found that the "up", "down"

Multi-sector burglar alarm

I recently built your Home Burglar Alarm (EA, January 1985) but encountered a few problems with the siren driver circuit. I would be glad for any advice you could give me.

The problems occur when the silent alarm switch is closed. With no load connected, the unit goes through the alarm and reset cycle correctly if triggered. However, after 10 seconds (the exit delay) the unit triggers again.

With a load connected, the alarm resets almost immediately and the siren gives a short "BLAT". When the test button is pressed the same result occurs — a short "BLAT" and also a flash of the sector LEDs.

The alarm LED remains steady when the silent alarm switch is open; when closed, it pulsates.

The circuit was tested with IC10 removed — IC7d and IC11a worked correctly.

IC10 appears in different places in the text as a 4001 and a 4011. A 4011 was used, although a 4001 was tried

but without the desired results. The wiring diagram seems to conflict with the circuit diagram and I have altered the wiring. (K.H., Boya, WA).

● Firstly, the changes you have made to the wiring diagram are quite in order. The pin marked 32 on the printed circuit board was included due to an oversight, and should be ignored. The corrections that you have made to the wiring to S11 and S12 are necessary if the type of switches that you use have the common contacts in the centre rather than at one edge as in those used in the prototype.

IC10 should be a 4011. The parts list is correct but the circuit diagram is in error.

The problem that you have appears to be related to IC7, because it is common to both the alarm and the delay circuits. Check all the solder joints around this IC and associated components, watching out for short circuits in particular. Pay close attention to pins 2 and 3 of IC7 since the problem only occurs when S10 is closed.

Electronics Australia Reader Service

"Electronics Australia" provides the following services:

PHOTOSTAT COPIES: \$3 per project, or \$6 where a project spreads over multiple issues (price includes postage). Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries. We reserve the right to supply complete back issues instead of photostats, where these are available.

CHASSIS DIAGRAMS: For the few projects which require a custom metal chassis (as distinct from standard cases) dyeline plans showing dimensions are normally available. \$3 including postage.

PC BOARD PATTERNS: High contrast, actual size transparencies: \$3, including postage. Please specify positive or negative.

PROJECT QUERIES: Members of our technical staff are not normally available to discuss individual projects, either in person at our office, or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the last three years.

Charge \$3. We cannot provide lengthy answers, undertake special research, or discuss design changes. Nor can we provide any information on commercial equipment.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" or submitted without fee may be answered in the "Information Centre" pages, at the discretion of the Editor.

COMPONENTS: We do not sell electronic components. Prices and specifications should be sought from advertisers or agents.

BACK ISSUES: Available only until our stocks are exhausted: \$3 (includes post and packing and storage fee).

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 227, Waterloo, 2017.

and "off" work very reliably from over 10 metres away. However, to switch on, I have to move to about one metre away and press the "up" button on the remote as many as five or 10 times, with a relay click now and then until it finally stays on.

I replaced the 10k Ω resistor on the base of the modified circuit with different values. I settled on 100 Ω which gives me back the range, but now it goes straight to the second last or last maximum volume position (which to say the least is a bit startling to the unaware).

Can you give me some ideas on how to make this part more reliable? (M.K., Carlingford, NSW).

● First, we suggest that you restore the circuit to its original condition. If the circuit still fails to operate correctly, then it seems likely that one of the ICs has been damaged. Try IC5 and IC6.

It should not be necessary to reduce the 10k Ω resistor to the base of the BD263 Darlington transistor. Try replacing this component also.

Le Gong doorbell

I have built two Le Gong units (EA, March 81) and both have been triggered when switching on household lights or when using the ceiling fan speed controller. Both units have been run by inbuilt batteries, with no connection whatsoever to the AC mains. Can you suggest a cure?

I have been a reader of your journal since the old Wireless Weekly days of 1928 and have spent many happy years building many different projects including the 50W Mosfet Playmaster Stereo Amplifier (EA, Dec 1980). Now, at 72 years of age, I still like to tinker. (J.D., Tweed Heads, NSW).

● We suggest that you try bypassing the pushbutton leads with a 0.1 μ F capacitor. In addition, to keep interference to a minimum, we suggest that the leads be twisted together.

Interference to AM radio

Since moving into my new home some two years ago, I have experienced a very annoying "buzz" on the AM receivers around the house and parts of the backyard. It comes about when either of our Rank television sets are switched on, appearing about every 15kHz on the AM receivers.

Is there any way to cure this wretched problem. (M.M., Rye, Vic).

● Your radio is picking up the 15,625kHz harmonics generated by the line output stage of each TV receiver. The best way around this problem is to

use an external aerial for the radio, with a shielded lead-in. This external aerial should be mounted as far away from the TV receivers as possible.

Help wanted for scanner project

After looking around at various scanners, transceivers and CB rigs, I have decided to build my own. Although heavily into electronics, I lack the expertise necessary to devise my own plan. Can you help me? (A.M., Campsie, NSW).

● There is no way you could build a scanner with special features for less than the cost of a commercial unit. And the amount of design work necessary for the microprocessor and RF circuitry does not bear thinking about. No, we certainly cannot help on that one.

Looking for a CRO

I am a beginner come average hobbyist in electronics and I am looking to buy a CRO (say 10MHz or less) without too many features (single trace, z input, not very old and reliable) at about \$150. I am not looking for a kit but a second hand oscilloscope or new one (up to \$200).

Could you please advise me where and how I may purchase one as I have tried the newspaper classifieds, your EA Marketplace and cannot find any for sale. Many of the electronics stores have been tried (such as David Reid and Jaycar) but without success. (E. Misoyannis, 42 Haines Ave, Carlingford, NSW 2118).

● We have printed your full name and address so that any reader with a suitable CRO can contact you directly.

Waterlogged solar fountain

I have two problems that you may like to tackle in your Information Centre. First, I made up the Solar Fountain, putting in much time and effort to dig and cement a pond, and mount a fountain etc. The pump became waterlogged within two weeks of operation, so we fitted a second pump only to have a repeat performance. Is there any cure?

My second problem is with the Touch Lamp Dimmer (April, 1983). I made up two of these units. The first one works well but I placed the second one in a bedlamp with lots of metal for the touchplate and on humid days I have to remove the globe to stop the lamp from going through a continuous cycle. Can you help? (W.F., Carnarvon, WA).

● We have not heard of the problem with the Solar Fountain pump before and can only suggest that you take the matter up with the retailer concerned. The sensitivity of the Touch Lamp Dimmer can be reduced by reducing the 1M Ω resistor on pin 15. Try substituting a 470k Ω resistor initially, but be prepared to use a lower value if required.

Sub-woofer amplifier

After reading many reviews in your magazine I purchased a 100W Sub-Woofers Amplifier kit (EA, July 1982). I bought it about three months ago and have never been able to get it running.

I was very careful in constructing the amplifier but I was unable to get zero voltage at the output. I have installed the 5W 220 Ω resistors across the fuse clips, the +50V rails are correct, and I was

able to obtain 13V across the 220Ω resistors.

Now each Mosfet has about 14-16mV across each 0.56Ω/5W resistor. It is impossible to adjust the trimpot (VR2) to obtain zero voltage at the amplifier output — I always get about 40V.

I went right through the amplifier and replaced the trimpots and all transistors except for the Mosfets. The problem remains, even when the Mosfets are not connected.

Later on a friend had a look at it and found that the input signal got as far as the Q1 transistor, so the filter works well but that's all. I have spent a great deal of time on this thing and I hope that you can suggest something besides the garbage tin. (B.P., Coogee, NSW).

● Having read through your description of the symptoms, it is not possible to say what is wrong with the amplifier. Indeed it is possible that there is nothing wrong at all since the output stage appears to be biased correctly. Are you measuring the output voltage as depicted on the circuit diagram, ie, between the output and 0V terminals? The voltage here should be close to zero volts.

Trouble with Teletext Decoder

I have been trying unsuccessfully to get the Teletext Decoder working.

Basically it does not like going into the teletext mode. The self-starting crystal oscillator usually won't, but if it does start, Data and Clock signals come out of the VIP SAA5030 and into the TAC SAA5040 correctly; so too does the

information from the remote control. During this time, a normal TV picture usually appears. Occasionally, for no apparent reason it will decide to function.

The picture has half good information and half corrupt (this is when L2 is tuned to the best possible position). When this happens, all the functions of the handset appear to function. Sometimes even pages can be selected, although they are still 50% corrupt. Occasionally, selection between television and teletext works normally but, more often, once television is pressed, it is impossible to get back into the teletext mode.

When the unit has been running for five minutes, the SAA5030 VIP gets too hot to touch. After 20 minutes, you can smell the heat of the plastic. This occurs in either mode. The 5V and 12V rails are correct.

The PO line functions as described — high for TV and low whenever a Teletext picture is displayed.

The decoder is totally incapable of displaying the large headers used on the index eg: MAGAZINE ONE, MAGAZINE TWO. The space where they should be is filled with seemingly random garbage as: "gggf Ggjj5 og ggggggggggg8".

I really would appreciate any help or advice. (A.N., Campbell, ACT).

● We feel that the problems you are experiencing are all due to one of two things: either the signal which you are applying to the decoder is of insufficient amplitude or the signal source is not tuned correctly. It must be stressed that the Teletext Decoder requires the TV station to be tuned spot on. The video waveform should have an amplitude of

between one and two volts peak to peak.

Since the clock generated in the SAA5030 is phase locked to the clock signal recovered from the incoming teletext data, insufficient level or mistuning could easily prevent this clock from running correctly. This clock then controls all the timing throughout the circuit, accounting for the problems that you are experiencing with the controls.

Once you have resolved the problems with the input to the circuit we feel that good results will be obtained after the setting up procedure has been followed. The SAA5030 does get quite hot under normal conditions.

Notes & Errata

HOME BURGLAR ALARM (February 1985, 3/MS/113): the leads to LED D33 are shown transposed on the wiring diagram on page 59. Similarly, the leads to switches S3 and S4 have also been transposed. Three pins marked "32" are shown instead of two — the one on the printed circuit board should be ignored.

The wiring for switches S11 and S12 is correct for the switches that we used. These switches have the common contact at one end rather than at the centre as with most popular types. The short length of wire soldered between these switches must connect to the common of the switches, so the wiring must be altered if centre common switches are to be used.

Finally, if the alarm time is longer than specified, reduce the 4.7μF timing capacitor on pin 5 of IC7c. If the alarm sounds soon after you have left the house, then the exit delay should be made longer.

NEW PRODUCT




\$1545

FROM CASHMORE'S WE INTRODUCE THE
PIXEL 25 x 25 MATRIX-ZONER
(COMPUTER CHASER)

OVER 50 INBUILT PATTERNS 100 WATTS PER CHANNEL.
STANDARD (TO 1000 WATTS PER CHANNEL) COMPUTERIZED PATTERNS TO SUIT YOUR APPLICATION.

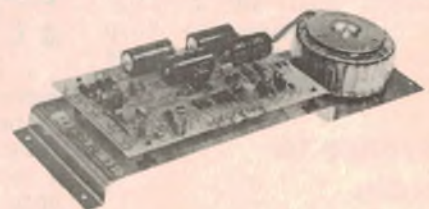★ FREEZE SWITCH ★ 3 TIMING SPEEDS ★ MANUAL CHASE
★ STEP BY STEP ★ MORE FACILITIES THAN PULSAR AT HALF COST AND AUSTRALIAN MADE ★ REMOTE CONTROL MODELS AVAILABLE.



200 WATTS MUSIC POWER CHASSIS AMPLIFIER

FROM \$160

COMPLETE KITS NOW AVAILABLE COMPLETE WITH 2 POWER AMPS, 2 VU METERS, 19" RACK MOUNTING, CASE, etc.

COST PER KIT \$430

CASHMORE SOUND SYSTEMS PTY. LTD.

354 LIVERPOOL RD, ASHFIELD. Telephone (02) 798 6782. Telex AA74549

HIRE, SALES, INSTALLATION OF DISCO LIGHTING, SOUND SYSTEMS, REHEARSAL STUDIOS AVAILABLE

L.E. CHAPMAN

122 PITT ROAD, NTH CURL CURL.
MAIL ORDERS: BOX 156, DEE WHY, NSW. 2099.
TELEPHONE 93-1848.

SUPER SPECIAL BSR GRAMO MOTOR AND PICKUP 240V

3 speed 33-45-78 includes
cartridge and
stylus turnover



\$12
P&P NSW \$2.75
INTERSTATE \$4.20
WA, NT \$5.20

SUPER SPECIAL FM STEREO KITS



Sets of 3 modules includes FM tuner decoder
and if detector Circuit diagram supplied.

ONLY \$22 PP \$1.60

Send stamped envelope for copy of Elec-
tronics Australia magazine review of the units.

SPECIAL BALANCE METERS CENTRE ZERO

\$2



PP
\$1

6P VALVE SOCKETS

9 pin 25c — 7 pin 25c — octal 25c

SPECIAL DUAL VU METERS



\$3

PP
\$1

SPARK GAPS

10 for \$1

THERMISTERS

4 for \$1

DIODES BY 406

10 for \$1

455KC IF Trans
for valve radios
\$1 each
OS coils
75c each

CAR RADIO
Suppressors
5 for \$1

SPECIAL

Chrome 1/4 shaft push-on knobs 10 for \$1.
Usual price 60c to 80c each

IC SOCKETS

24 pin 35c
28 pin 40c
18 pin 25c

Slide pot
knobs
10 for \$1

TRANSISTORS AD161-162 \$1 pair
100 mixed Capacitors, fresh stock, all
handy values \$2 AD149 \$2 pair
100 mixed resistors, handy values \$2

STICK RECTIFIERS

TV 20-SC \$1 each

VALVES

EF86	\$4.00	VT128 955	\$5	652	\$3
12AX7	\$4.00	CV423	\$4	7V4	\$4
12AU6	\$4.00	879	\$4	6CM5	\$6
12AX7	\$4.00	EM84	\$5	6CU5	\$5
6BM8	\$3.00	VR101-102/28054	IL4	\$4	
6BL8	\$3.00	IC4	\$5	6BW7	\$4
6BQ5	\$4.00	EL37	\$12	6AT6	\$4
6K8	\$10.00	IDB	\$4	6BA8	\$4
6K7	\$7.00	41	\$6	6CW8	\$5
5AS4	\$4.00	42	\$6	6BD6	\$4
6VE	\$10.00	6B7	\$6	6AM6	\$4
6AL3	\$4.00	80	\$6	6BF5	\$4
6GV8	\$4.00	6F6	\$10	00V03	\$6
6SA7	\$5.00	6BK6	\$4	12AV6	\$4
6Y3	\$4.00	6BD7	\$5	12AN7	\$5
6BE6	\$5.00	6HG8	\$5	12AO5	\$6
6BH5	\$5.00	6AX4	\$5	IA3	\$4
IT4	\$2.00	6D06	\$6	6AD8	\$5
6AV6	\$3.00	6CW7	\$3	6CW5	\$5
10B	\$4.00	IC7	\$5	2E26	\$7
VT121 955	\$5.00	IM6	\$5	5V4	\$6
ECH33	\$7.00	IM5	\$5	5V4	\$6
6CBVT163G	3.00	6EH7	\$4	2525	\$4
VT86	\$5.00	6DX8	\$4	6BK7	\$5
6H6	\$4.00	6AW8	\$5	30AE3	\$5
6V4	\$5.00	6W6	\$5	6B7	\$5
6U7	\$7.00	6V9	\$5	30A	\$4
IS2	\$3	6EJ7	\$4	6C8	\$4
6V4	\$3	6ES8	\$4	VT86	\$4
6AQ5	\$6	6BH8	\$5	6BD6	\$5
6BU8	\$4	6C08	\$5	12BY7	\$4
6N3	\$3	IX2	\$4	6B26	\$4
6X9	\$5				

SPECIAL

12 mixed switches \$4 PP \$1.40 not a
lucky dip, c wot u get! P.P. \$1.60

POTS ROTARY

1/2 Meg	50c	10K Switch	50c
1 Meg	50c	250K	30c
100K	30c	50K	30c
100K Switch	50c	20K	30c
50K Double Pole Switch	50c	10K Min Pots	25c
7 500	30c	50K/ohm	50c

Extra Pots 1/2mg LIN 50c
1 Meg log switch \$1
1/2 1 meg dual Concentric tapped at 100K \$1
2 meg ganged double pole switch \$1
1 5 meg dual ganged 50c 2 meg ganged log \$1
1 meg dual ganged \$1 1/2 meg dual ganged LIN 75c
25K 50K dual ganged Concentric
double switch \$1
100K dual ganged linear pots 75c
200K single line 30c 10K sub min log pots 50c
20K wire wound 75c 250K ganged pots 75c
dual log 10K 75c 25K in ganged pots 75c

SUPER SPEAKER SPECIAL

15/ohm 2 1/4 inch four for \$1 P.P. \$1.60

MICRO SWITCHES

5A 250V 50 cents

SLIDE POTS

1/2 meg dual	\$1	1K dual	\$1
1 meg dual	\$1	50K single	50c
2 meg dual	\$1	250K single	50c
25K dual	\$1	10K single	50c
250K dual	\$1	2 meg single	50c

TOUCH MICRO SWITCHES

As used in front control panels in colour TV
sets.

4 FOR \$1

SPEAKER

2-way crossover
networks

30 WATTS RMS \$2

CRYSTALS for colour TV \$1 each

AM FM TUNING CAPACITORS

\$7



4 PIN SPEAKER SOCKETS

4 for \$1

FERRITE RODS

Bin x 1/4in with coils \$1.50

TELESCOPIC AERIALS

Opens up to 38 inches \$1.50

PICKUP CARTRIDGES

Ceramic BSR Turnover Stylus universal type \$5

TOGGLE SWITCHES

4 FOR \$1



Capacitors ELECTROS

2500 16V	4 for \$1	22 UF 16V	10 for \$1
220 16V	4 for \$1	330 UF 63V	each 50c
1000 UF 50V	each \$1	1MFD 50V	10 for \$1
1000 UF 63V	each \$1	33 UF 10V	10 for \$1
22 UF 160V	3 for \$1	1MFD 50V	10 for \$1
1000 UF 16V	each 50c	33 UF 10V	10 for \$1
63 UF 25V	5 for \$1	0.0039 1500V	
47 UF 63V	each 50c	8 MFD 350 V	each 50c
47 UF 160V	3 for \$1	6N8 1500V	each 50c
47 UF 25V	4 for \$1	220 UF 35V	4 for \$1
40 UF 25V	5 for \$1	1000 UF 25V	each 50c
47 UF 40V	3 for \$1	680 UF 50V	each 50c
47 UF 10V	10 for \$1	22 UF	10 for \$1
100 UF 25V	5 for \$1	100 UF 6.3V	10 for \$1
25 UF 25V	10 for \$1	330 UF 25V	3 for \$1
47 UF 16V	5 for \$1	2000mfd 25V chassis	mount \$1
220 UF 50V	each 50c	50mfd 400V chassis	mount \$1
47 UF 200V	each 50c	Dual 75mfd 65V 20mfd	450V chassis mount \$1
1000 UF 10V	4 for \$1		
2 2 UF 200V	4 for \$1		

SPECIAL SHIELDED CABLE SINGLE STRAND

25 meters for **\$2.50**

SUPER SPECIAL

ICs new packed in original tubes.
20 mixed popular types for **\$2** P.P. \$1 anywhere
in Australia.

CONTACT SWITCHES

EBM3320 4 for \$1

SPEAKER SPECIALS

5x4 4/ohm	\$4
5x7 7 watts RMS in 8 or 15/ohm	\$4.50
6x4 in 8 or 15/ohm	3.50
9x6 10 watts RMS in 8 or 15/ohm	\$6
8x4 7 watts RMS in 8 or 15/ohm	\$4.50
6 inch single cone 15/ohm	\$4

Colour convergence coils
Delta 11270 \$5

Hor Drive Transformer for Colour TV —
3021, 39/6 \$3

DIN PLUG SOCKETS

4 FOR \$1.00

POWER TRANSFORMERS

240V 285 ASIDE 3.5 60 MIL \$10
PP NSW \$2.75 INTERSTATE \$4.50

POWER TRANSFORMERS

240V 30V 12V 2 AMP \$12
PP NSW \$2.75 INTERSTATE \$4.50

Transistor TV Tuner

MSP 46300-5
11 volt

\$10

p.p. \$1.40



4 POSITION PUSHBUTTON SWITCH

\$1.00



SUPER
SPECIAL

BSR BELT DRIVE

Record player 2 speed 33 and 45 RPM 11
inch turntable pickup arm counter balanced
cuing facility Ceramic cartridge
diamond stylus works off 240V
9V or 12V. **\$39**
P.P. \$5.50

SPECIAL WORLD FAMOUS

PIEZO LOW IMPEDANCE MICRO PHONE

RRP
\$42



NOW
\$10

HOR OS COILS

for B & W TV sets \$1

SUPER SPECIAL SPEAKER SYSTEM

3 WAY
30 WATTS
RMS EACH
SPEAKER

\$58 pair

SIZE 19 1/2 by 13 1/2 by 13

PP NSW \$6 INTERSTATE \$9 WA NT \$14

POWER TRANSFORMERS

240V pair 25V taps

260V

117V \$10

MUTING SWITCHES

EBM209 4 for \$1



Minituning capacitors 50c
Sub mini 75c

Infra Red Audio Transmitter

for colour TV
3102 108-30301



\$7



Video Det & AFT

3102 108-58741



SPECIAL! TRANSISTOR EAR PIECES

with plugs & leads — top
quality in sealed plastic packets

4 for \$1

3.5 to 3.5MM 7ft
6.5 to 3.5MM 7ft
6.5 Single ended

\$1
50c

FOR SALE

ANTIQUE RADIOS: Collection for sale. Range from 1925 to 1939. Included are spare valves of any description, spare parts and circuits, old radio manuals and books. Max Gistingier, 41 Willmington St. Newmarket 4051.

SUPER 80 USERS: We have the largest range of super 80 hardware/software. For catalogue send SSAE to Matrix Software, PO Box 291, Kensington 2033.

AMIDON FERROMAGNETIC CORES: Large range for all receiver and transmitter applications. For data and price list send 105X220 SASE to: R.J. & U.S. Imports, PO Box 157, Mortdale, NSW 2223. NSW: Geoff Wood Electronics, Rozelle. VIC: Truscott Electronics, Croydon. WA: Willis Trading Co., Perth.

RCS RADIO PTY. LTD.

Established 1933
IS THE ONLY COMPANY
WHICH MANUFACTURES AND
SELLS EVERY PCB & FRONT PANEL
published in EA and ETI
651 Forest Road Bexley 2207
AUSTRALIA
RING (02) 587 3491 FOR INSTANT PRICES
24-HOUR TURNAROUND SERVICE

STEREO-VIDEO-SECAM-NTSC-RGB

ST182 Universal Stereo Decoder
(converts mono TV to stereo reception) . . . \$125
VA1 Video/Audio input module (suitable
for hot chassis) \$115
SM1 Secam Transcoder (converts PAL
TV for Secam reception) \$95
RGB85 Universal RGB input module
(suitable for TTL or linear RGB) \$95

NTSC-decoder in preparation. Prices include P & P
LIBRATRONIX
6 Woodcrest Pl, Cherrybrook, NSW 2120.
Phone (02) 875 1858.

WANTED

MICROPHONES: From early broadcast studios. Also 16 inch transcription discs and acetates, for collector. Perth (09) 279 1234. 85 Parker Street, Bassendean 6054, WA.

QLD FOR PRIVATE SALE

HIGHLY RESPECTED ELECTRONICS BUSINESS

RETAIL AND SERVICE

TV - HI FI - CAR SOUND - RADIO - CB

In top 8 U.H.F. outlets in Australia. Established 9 years in progressive modern town. One hour drive to coast. Excellent turnover and nett income \$38,350 + S.A.V.

PH A/H (079) 92 1125

DO YOU WANT TO BE A RADIO AMATEUR?

The Wireless Institute of Australia, established in 1910 to further the interests of Amateur Radio, conducts a Correspondence Course for the A.O.C.P. and L.A.O.C.P. Examinations conducted by the Department of Communications. Throughout the Course, your papers are checked and commented upon to lead you to a successful conclusion.

For further information, write to:

THE COURSE SUPERVISOR W.I.A. (N.S.W. DIVISION)

P.O. Box 1066
PARRAMATTA, N.S.W. 2150.

DISPLAY ADVERTS IN MARKETPLACE are available in sizes from a minimum of 2cm X 1 col rated at \$15 for a col cm. Ad sizes may be increased up to a maximum of 10 col cms.

CLASSIFIED RATES \$3.60 for 40 letters or part thereof per insertion payable in advance. Minimum 80 letters.

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

EXCEPTIONAL OPPORTUNITY

TECHNICAL SALES - ELECTRONICS & COMMUNICATIONS

If you are a good technician working with RF, audio telecommunications or allied systems, with a yearning to make a career in technical sales, then this could be your opportunity.

We are looking for a person with initiative, drive and technical ability, who feels at ease meeting new faces and is capable of influencing people. As a part of a small team of highly motivated professionals you will receive on the job training in all aspects of systems sales engineering, including immediate exposure to field work under supervision.

It will be expected of you to progress steadily towards your objective of a successful technical sales career.

A competitive salary package is offered, including performance based incentive, car or allowance. For details and interview appointment, please contact Mr Jim Weir on 858 8458 or AH 871 8346.

F.F.E. SERVICES PTY LTD,

6 HOPE STREET,
ERMINGTON 2115.

BLACKTOWN NEXT TO TELECOM OFFICE

Electronic Components
PC Boards, Computer Repairs
OPEN MONDAY TO SATURDAY
(02) 621 5809

30 Campbell St BLACKTOWN NSW
CQ ELECTRONICS

48 HOUR PCB SERVICE

Single Sided 7c per cm²
Double Sided 10c per cm²

(Minimum 100cm²)

DRILLING (0.8mm) 2.5c per hole
Send artworks on film or transparency P&P \$2.50

WDELECTRONICS

PO Box 341 Riverstone, NSW 2765
Phone (045) 73 6097

Kenwood KX-780 cassette deck . . . from p41

not markedly affected by the bias changes which indicates that the machine is pretty well set up to begin with.

By far the best performance was obtained with metal tape, TDK MA C-60 (one of Kenwood's recommended types). At a recording level of -20VU, the -3dB point of the frequency response was 19kHz without Dolby, 16kHz with Dolby B and 15kHz with Dolby C.

At -10VU, and Dolby out, the frequency response was only 6.5dB down at 20kHz, for a medium bias setting. Signal-to-noise ratio was 50.5dB without Dolby, 56dB with Dolby B and 58dB with Dolby C. All signal to noise ratio figures are unweighted. At 0VU, harmonic distortion was around 1.5%, an excellent result. By pushing the maximum signal level a little over 0VU, a dynamic range in excess of 60dB is easily achieved.

With Nakamichi SC tape, the 20VU frequency response was 3dB down at 19kHz, without Dolby. With Dolby B, it was 17.4kHz and with Dolby C, 18kHz. At -10VU, the frequency response was 10dB down at 10kHz, although only 0.3dB down at 15kHz, again for a medium bias setting. Signal-to-noise ratio was 49.5dB with Dolby out, 54dB with Dolby B and 56dB with Dolby C. Harmonic distortion at 0VU and 1kHz was around 1.6% again, a very good result overall.

With Ferric tape, (DM Magnetics) the
continued on page 128

ELECTRONICS CENTRE

BSR STEREPHONIC RECORD CHANGER

(BE QUICK — THEY ARE ALMOST EXTINGT)

Latest Model • 240VAC 50HZ • Auto/Manual Operation • 3-Speeds • Big Platter • Cue Lever • Magnetic Cartridge • 2 Spindles • Instructions • 4 Pole Motor •



\$79.95 P-P NSW \$5.50
Q, V, SA, T \$7.50; WA, NT \$9.50

HIGH POWER HORN SIREN WITH PROGRAMMABLE TIMER



TOP QUALITY • WEATHERPROOF • 5 1/2" DIA • 12VDC 10W • WARBLER TONE • OUTPUT 105dB @ 1M • ADJUSTABLE FROM 30 SECONDS TO 5 MINUTES • INBUILT

ONLY \$33.95 P-P NSW \$3 INTERSTATE \$4.50

STANDARD MODEL (NO TIMER) \$20.95 PLUS P-P

★ GOOD PRICE • GOOD QUALITY ★ ALARM CONTROL MODULE

Designed for — Home, Office, Factory, Warehouse installation — allows soundless entry and exit • N/O for heat, smoke vibration, and N/C for doors, windows • Exit delay approx 20 sec. • 10 second closed circuit delayed alarm • Instant alarm for open circuit • Auto-reset 1 min • Drives 8 ohm horn speaker • 12VDC • 2MA when armed.



\$39.95 P-P NSW \$2.50 INTERSTATE \$3.50

ROTATING FLASHING RED DISTRESS BEACON 12 VOLT 2A



Ideal for Car, Truck, Boat. Also Disco.

\$12.95 P-P NSW \$2.50 INTERSTATE \$3.50

SILVER PLATED VARIABLE CAPACITOR



150pf AIR SPACED 1" x 1/4" DIA SHAFT. CERAMIC INSULATION

\$6.50 P-P \$1.35

WE BUY

50 WATT RMS SPEAKERS


FOR **\$39.95** PAIR OR \$22.50 EA.

ETONE FACTORY SCOOP.

30cm 8 Ohm Hi-Fi Woofer. Rugged Top Quality with Warranty. Foam Surround. 3.5cm V.C. Hefty Ferrite Magnet. Freq. Response. 35-4500 Hz.

P-P NSW for one, \$4.50. Interstate \$6.90. P-P NSW for two, \$6.50. Interstate \$8.50

TUNING CAPACITOR

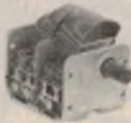

\$5.75

P-P NSW \$2.00 INTERSTATE \$2.75

3 gang, 60pF, 200pF AND 415pF. IDEAL for A.T.U., etc. Top quality Ball bearings. 55X45X40mm.

TEXAS TIL 139



Source and Sensor Assembly • Gallium arsenide LED and PNP silicone photo transistor • Can be PCB mounted.

P-P \$2

75c EACH 10 FOR \$6.00

DIODES

IN 4004, 400 pIV 1 AMP IN 5404, 400 PIV 3 AMP

50 FOR \$2.50 50 FOR \$7.50

M9775 650 PIV 3 AMP

50 FOR \$9.50

P-P NSW \$1.35. INTERSTATE \$1.70

CRYSTAL 3.579545 MHz. Mini Solder in.

95c

P-P 75c

2SD200 = BU205 TRANSISTOR

NPN VCBO VCE 300V 750V 3 AMPS

4 FOR \$3.75 P-P NSW \$1.35 INTERSTATE \$1.70

MJE 350 TRANSISTORS

PNP. 300V .5A

10 FOR \$3.50

ETONE SPEAKER SPECIALS

GENUINE FACTORY PRICES

Rugged top quality Aust made brand new bargains — all with factory warranty

Model	Size	Cone Type	V/Coil	Reson Hz	Freq Hz	Watts Rms	Price Ea or 2 for
4310	38cm	Straight surround	8 or 15 Ohms	45	40-6000	60	\$79.95 or \$155.00
4510	38cm	Straight surround	8 or 15 Ohms	45	40-6000	100	\$99.95 or \$195.00
4350	38cm	Hi-Fi	8 or 15 Ohms	30	30-4000	120	\$79.95 or \$155.00

30cm PRO MODELS CAST ALUMINIUM FRAME DESIGN FOR (HI POWER)

Model	Cone Type	V/Coil	Reson Hz	Freq Hz	Watts Rms	Price Ea or 2 for
235	Hi Fi Woofer	8 or 15 Ohms	30	30-5000	120	\$ 88.95 or \$169.00
239	Hi Fi Twin Cone	8 or 15 Ohms	30	30-12000	120	\$ 95.50 or \$181.50
245	Hi Fi Woofer	8 or 15 Ohms	30	30-5000	150	\$111.00 or \$216.00
249	Hi Fi Twin Cone	8 or 15 Ohms	30	30-12000	150	\$117.50 or \$223.00
265	Bass Guitar etc	8 or 15 Ohms	50	40-8000	150	\$168.00 or \$320.00
266	Disco etc	8 or 15 Ohms	50	40-14000	150	\$175.00 or \$332.00
231	Disco etc	8 or 15 Ohms	65	50-8000	60	\$ 75.50 or \$143.00
236	Twin Cone Disco	8 or 15 Ohms	65	50-14000	60	\$ 90.00 or \$170.00
241	P.A. etc	8 or 15 Ohms	65	50-8000	80	\$ 94.50 or \$180.00
246	Twin Cone P.A.	8 or 15 Ohms	65	50-15000	80	\$ 99.50 or \$190.00

PACK AND POST: FOR ONE 30cm SPK, NSW \$5. VIC \$7. SA Q T \$9. WA NT \$10.50. PACK AND POST: FOR TWO 30cm SPK, NSW \$7.50. VIC \$10. SA Q T \$12. WA NT \$14. PACK AND POST: FOR ONE 38cm SPK, NSW \$6. VIC \$8.50. SA Q T \$10. WA NT \$12.50. PACK AND POST: FOR TWO 38cm SPK, NSW \$8.50. VIC \$11. SA Q T \$20. WA NT \$22.50.

FOR REGISTERED POST, ADD AN EXTRA \$3.65 TO PACK & POST CHARGE.

A AND R POWER TRANSFORMER

Primary Tapped from 200v to 250v 50Hz.

Secondary 0-20, 30, 48v 2.5 Amps.

Size 95 x 80 x 85mm

\$9.95 P-P NSW \$5.50 INTERSTATE \$7.50

PLASTIC BOX



\$1.25
P-P 75c

117 x 63 x 35mm

STURDY — you can actually stand on them — 2 colours — grey and white
BACK PLATE INCLUDED

**SPECIAL SOUVENIR
EDITION**



**TOP VALUE
AT ONLY
\$3.95
NZ\$4.50**

A TRULY NOSTALGIC TRIP INTO AUSTRALIA'S WIRELESS PAST

AT YOUR NEWSAGENT NOW

THE FEDERAL PUBLISHING COMPANY

PO BOX 227, WATERLOO 2017

Kenwood KX-780 cassette deck...from p126

-20VU frequency response was 3dB down at 17kHz with and without Dolby B, and at around 19kHz with Dolby C, although note that the overall response was a good deal lumpier than with the previous two tapes.

At -10VU, the response at 20kHz was -9dB down and distortion at 0VU was 3.1%. All these figures for Ferric tape were taken with minimum bias setting, which gave the best overall results.

Separation between channels was -39.5dB at 100Hz, -40dB at 1kHz and -38dB at 10kHz. These are good results.

In fact, the overall results from this machine were very good and demonstrate just how far the cassette medium has evolved. There are few points worth complaining about, although the accuracy and resolution of the LED signal level could be improved.

In use, the unit performs very well and produces very good quality recordings.

Recommended retail price of the Kenwood KX-780 is \$679.00. For further information on the Kenwood range of products, contact Trio-Kenwood (Australia) Pty Ltd, 4E Woodcock Place, Lane Cove, NSW 2066. (L.D.S.)

ADVERTISING INDEX

ADVERTISER	PAGE
Ace Radio	127
ACME Electronics	94
Active Electronics	10, 11
Altronics	57, 58, 59, 60, 61
Audio Engineers	27
Audio Telex Communications	71
Autotron Australia	9
AWA Thorn	40
Cashmore Sound Systems	124
C&K Electronics	66
Chapman L. E.	125
Commodore Computers	2
CQ Electronics	126
Daneva Australia	103
David Reid Electronics	53
Delsound	29
Dick Smith Electronics	IFC, 4, 5, 45, 84, 99
Dolphin Computers	28
Electronic World	118
Electronics Australia	32, 89, 96, 119
Elmeasco	IBC
Emtronics	94
Federal Publishing	128
Ferguson Transformers	119
F.F.E. Services	126
Fred Hoe & Sons	66
Geoff Wood Electronics	93
Gordon Girdler	126
ICOM	117
Jaycar Electronics	14, 15, 72, 73, 111
JWD Electronics	126
Kalextronics	116
Len Wallis	Insert
Libratronics	126
Marantz Australia	34, 35
Nicholson Electronics	54
Parameters	OBC
Promark Electronics	108, 109
Radio Despatch Service	46
Rheem Australia	69
RCS Radio	126
Rod Irving Electronics	21, 22, 23, 50, 51 80, 81, 121
Royston Electronics	40
Philips	101
Scan Audio	28
Sheridan Electronics	107
Solarex	85
Siemens Ltd	76
Sounding	41
Stotts Correspondence College	49
Trio Kenwood	39
Wireless Institute of Australia	126

FROM HOBBYIST TO PROFESSIONAL - FLUKE MUST BE YOUR FIRST MULTIMETER CHOICE FOR FEATURES, QUALITY AND VALUE



**FLUKE MULTIMETERS
CARRY A ONE YEAR
MINIMUM WARRANTY
AND ARE BACKED BY
COMPREHENSIVE SPARE
PARTS, CALIBRATION
AND SERVICE**

1 8050A

- 4½ digit bench portable • 0.03% basic accuracy • 10uV, 10nA, 10mohm sensitivity
- True RMS to 50kHz • dB with 16 reference impedances • Relative reference for comparing values • Mains/Battery option

8010A 8012A (similar to 8050A)

- 8010A has 10A range and true RMS • 8012A has low ohms (0.001ohm resolution) • Both have conductance • Mains/Battery option

2 8020B

- 3½ digit • 0.1% basic accuracy • Eight functions including conductance
- Continuity beeper

3 8021B 8022B

- 3½ digit • 0.25% basic accuracy • Diode test • Continuity beeper (8021B only)

4 8024B

- 3½ digit • 0.1% basic accuracy
- 11 functions including temperature with K type thermocouples • Peak hold on voltage and current • Logic detection and continuity testing • Audible and visible indicators

5 8026B

- 3½ digit • 0.1% basic accuracy • True RMS to 10kHz • Conductance to 10,000Mohm
- Diode test and continuity beeper

6 8062A

- 4½ digit • 0.05% basic accuracy • Similar to 8060A without counter and dB • Relative reference • True RMS to 30kHz

7 8060A

- 4½ digit • 0.05% basic accuracy • True RMS to 100kHz • Frequency counter to 200kHz • dB and relative dB • Microprocessor self diagnostics • Relative reference for comparing values • Direct resistance to 300Mohm

**LOW COST 70 SERIES
WITH ANALOG & DIGITAL
DISPLAY**

**3 YEAR
WARRANTY**

8 73

- 3200 count display • 32 segment bar graph
- 18 ranges • Automatic power down
- 10A current range • Autorange • 0.7% basic accuracy • 2000 hour battery life

75

- All the features of the 73 plus:
- Audible continuity tester • Autorange/Range hold • 0.5% basic accuracy • Low mA range

77

- All the features of the 75 plus:
- Touch Hold function • 0.3% basic accuracy • Multipurpose protective holster

**ACCESSORIES INCREASE
THE VERSATILITY OF
YOUR FLUKE
MULTIMETER**

An extremely wide range of accessories is available for your Fluke multimeter.

SOLD & SERVICED IN AUSTRALIA BY

ELMEASCO
Instruments Pty. Ltd.

Elmeasco Instruments Pty Ltd - incorporated in N.S.W.
NEW SOUTH WALES
15 Macdonald Street,
MORTLAKE
P.O. Box 30, CONCORD
NSW 2137
Tel: (02) 736 2888
Telex: AA25887

VICTORIA
12 Maroondah Highway,
RINGWOOD
P.O. Box 623, RINGWOOD
VIC 3134
Tel: (03) 879 2322
Telex: AA36206 ELMVIC

QUEENSLAND
243 Milton Road,
MILTON
P.O. Box 2360, BRISBANE
QLD 4001
Tel: (07) 369 8688
Telex: AA44062

SOUTH AUSTRALIA
99 King William Street,
UNLEY
P.O. Box 1240, ADELAIDE
SA 5001
Tel: (08) 271 1839
Telex: AA88160

WESTERN AUSTRALIA
20 Barcomb Way,
GOSNELLS
P.O. Box 95, GOSNELLS
WA 6110
Tel: (09) 398 3362

One system per engineer.
Now you can afford to work with it.
You can't afford to work without it.



The engineering community has addressed productivity through computing on two fronts: CAE and the personal computer.

In just a few years, CAE has grown dynamically to provide extensive functionality to the electrical design engineer.

For example, the Daisy LOGICIAN was introduced in 1981 as a stand-alone engineering workstation. Since then, the LOGICIAN has grown in performance and functionality to replace many mainframe design automation systems.

Meanwhile, the engineering community has quietly selected the IBM PC as the workhorse for general purpose engineering support.

There isn't room or need for two different computers on the engineer's desk.

**daisy**
SYSTEMS CORP.

Daisy's Personal LOGICIAN packages the workhorse PC, logic entry and CAE network access.

One desk, one computer. One low price.

The benefits are significant.

Because of the compatibility of the processors and architecture of the Daisy and IBM systems, we provide you an affordable, highly integrated personal engineering workstation with enormous price/performance and functionality benefits.

You get the most system for your money, and for your desk space.

You get Daisy's commitment to delivering the competitive edge in CAE productivity. And you ride with the IBM standard as the functionality of the personal computer is advanced.

If you have been waiting for a CAE solution that fulfills the need of your entire engineering department...your wait is over.

The technology is available. Your investment is protected.

The Personal LOGICIAN is the entry level workstation of the Daisy integrated CAE range. Other products include:

LOGICIAN. The cornerstone of Daisy CAE

The industry's best selling, best proven CAE workstation, providing full CAE functionality for design entry and design verification – and included in every high-level Daisy system.

MegaLOGICIAN and PMX. For total system simulation.

Accuracy and simulation acceleration combine to deliver reliable verifications at *interactive* speed.

The PMX (Physical Modeling Extension) allows system designers to incorporate complex devices and subsystems as part of entire system simulations.

GATEMASTER. The standard semicustom workstation.

The system for optimal semicustom design and *correct by construction* layout. With more design libraries on line than any other system, GATEMASTER puts semicustom technology within the reach of any design engineer.

CHIPMASTER. Next-generation mask layout.

Integration of CAE and CAD in a single system. Performance acceleration means layout now runs at interactive speeds, in a windowed working environment. Plus: Power and capacity for VLSI circuits of any size, any technology.

For full details of the Daisy product range, contact your nearest Parameters office today.

SYDNEY:

41 Herbert St, Artarmon, N.S.W.
P.O. Box 573, Artarmon, N.S.W. 2064
Phone (02) 439 3288 Telex AA25021

MELBOURNE:

1064 Centre Road, Oakleigh South
Private Bag No. 1, Oakleigh South 3167
Phone (03) 575 0222. Telex AA33012

**PARAMETERS** PTY LTD
PERFECTION IN MEASUREMENT