

**SPECIAL 148-PAGE ANNUAL DIGEST!**

**WIN ONE  
OF TWO H-P LOGIC  
ANALYSERS WORTH \$5500!**

NDD

# Electronics

**AUSTRALIA** WITH Professional Electronics & ETI

JANUARY 1996 \$5.50  
NZ \$7.30 incl GST



**PC DRIVEN  
ANALYSER FOR  
EGO SENSORS  
CHECKS MODERN  
CAR ENGINES...**

**LOW COST  
CONTROLLER  
FOR DUAL 12V  
BATTERIES**

**BEYOND THE  
INTERNET:  
OTHER ON-LINE  
SERVICES**

**AUST SYSTEM  
'UNTWINKLES'  
THE STARS...**

**EASY TO USE  
METER TESTS  
ELECTRO 'ESR'**



# No Other DMM Compares!

The Metrix MX56 is, without question, one of the world's finest digital multimeters. The best of the ASYC II Series, it has the best accuracy (50,000 count/ $\pm 0.025\%$ ), a built-in counter, displays True RMS AC (and AC+DC) voltage as resistive power or dB (impedance selectable), mains disturbance indication and much, much more. The ASYC II Series has been designed to provide IEC1010 category safety for the user with separate battery compartment, leads that won't accidentally be disconnected, 600V fuses, metal oxide varistors, holster and sealed cases, double insulated (IP677) and waterproof to 10m.



## High Accuracy, High Resolution

50,000 Counts (all models) and 0.025% basic accuracy

## Mains Disturbance Indicator

Indicates the presence of spikes or noise on the line, enabling the user or technician to determine if more sophisticated monitoring equipment is needed.

## True RMS (AC or AC+DC)

For accurate measurements of non-sinusoidal waves, the ASYC II series displays True RMS readings for AC or AC+DC.

## Display Vac as dB or Resistive Power

The meter performs the dB or power calculation and you select load impedance from  $1\Omega$  to  $9999\Omega$  in  $1\Omega$  steps.

## Resolution down to 0.01 microamps

You can measure currents from hundredths of a microamp to half an amp without changing the jack or switch position with electronic auto-ranging.

## High Accuracy Temperature Measurement

By simply adding a Metrix PT100 or PT1000 Temperature Probe directly into the meter's jacks, measurements to  $800^{\circ}\text{C}$ , with an accuracy of  $1^{\circ}\text{C}$  over the entire range can be made easily.

## Traceability & Calibration

Each ASYC II DMM is provided with a Declaration of Conformity and Test Report for traceability to national and international standards. Re-calibration is digital via a serial interface without opening the meter and takes just 7 minutes in our NATA Cal. Lab!

## Performance Choices

	MX53	MX54	MX55	MX56
Basic Accuracy (%)	0.1	0.05	0.025	0.025
T RMS Bandwidth (kHz)	30	100	100	100
Min/Max/Average		yes		yes
Event Counter				yes
Disturbance Indicator		yes		yes
dB		yes	yes	yes
Resistive Power				yes
Temperature		yes		
50mA Accuracy (%)	0.2	0.05	0.05	0.05

All ASYC II meters have a 3-year replacement guarantee (If it fails - you get a brand new meter!).


Prices start at \$470.

Get the full specs now!

Freecall 1800 623 350    Freefax 1800 067 263

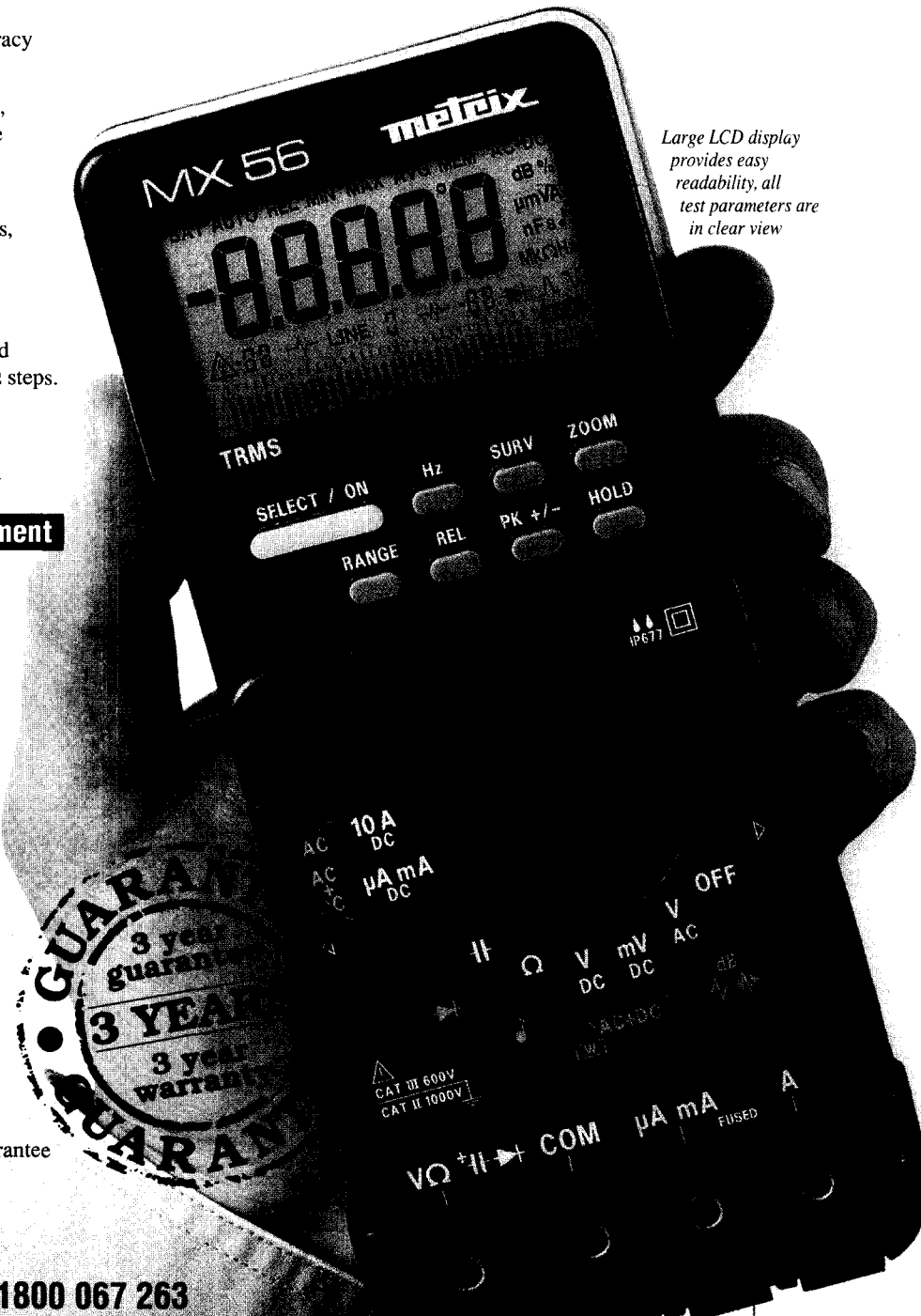**50,000 COUNTS,  $\pm 0.025\%$  ACCURACY.**

Metrix patented "SECUR X" concept keeps leads from accidental disconnection.



Large LCD display provides easy readability, all test parameters are in clear view

**NILSEN TECHNOLOGIES**

Any prices are ex tax

**NILSEN**  
Engineering solutions for tomorrow

READER INFO NO. 1


# Electronics

Volume 58, No.1  
January 1996

**AUSTRALIA** with Professional Electronics & ETI


AUSTRALIA'S LARGEST SELLING ELECTRONICS MAGAZINE — ESTABLISHED IN 1922

## Low cost ESR meter

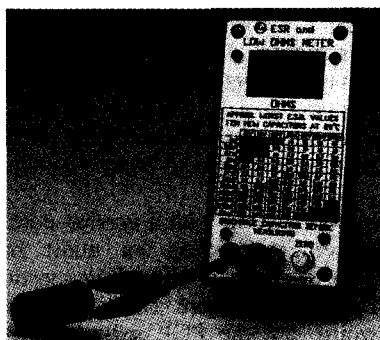

Although electrolytic capacitors can cause a lot of trouble when they dry out and develop a high equivalent series resistance, you can't really check them with a DMM or capacitance meter. But Bob Parker's new ESR Meter design checks them easily — see his article starting on page 76.

## Untwinkling the stars...

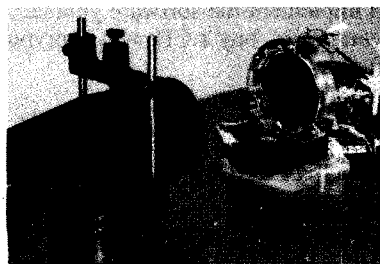

Scientists at the Anglo-Australian Telescope and Sydney Uni have developed new 'adaptive optics' systems, like this 'rubber mirror', to correct star images for distortion from the Earth's atmosphere. Geoff McNamara explains how it's done — see page 26.

## On the cover

EA project designer Graham Cattley checks out his new PC-driven EGO Sensor Analyser on the oxygen sensor of a late-model Toyota Camry. As you can see, it provides a lot of very handy diagnostic information — at much lower cost than comparable commercial analysers. (See page 60.) Photo by Phil Aynsley.

## Video and Audio

- 8 TECHNOLOGY LEAP IN NEW VAF SPEAKERS *Impressive performance!*
- 12 THE CHALLIS REPORT *The Bose 'Auditioner' and 100 years of acoustics*
- 18 WHAT'S NEW IN VIDEO & AUDIO *Home THX audio system from Jamo*

## Features

- 6 MOFFAT'S MADHOUSE *A major eruption of hyperbabble...*
- 20 UNTWINKLING THE STARS *Adaptive optics at the Anglo-Aust Telescope*
- 24 UNSW OPTO-ELECTRONICS RESEARCH *Impressive results achieved*
- 26 QUOIN RIDGE: THE SMA'S 'BIG EARS' *Monitoring station in Tasmania*
- 30 ONLINE, BUT NOT ON YOUR OWN *CompuServe and the other services*
- 34 WHEN I THINK BACK... *Dr Ernest Benson — a brilliant career (1)*
- 53 SEMI DATA ON A CD-ROM *D.A.T.A.'s Parametric Access Library*
- 104 ANNUAL INDEX FOR VOLUME 57 *All main articles, reviews and columns*

## Projects and Technical

- 44 THE SERVICEMAN *How long does it take to forget a fault?*
- 48 EXPERIMENTING WITH ELECTRONICS *Never too much experimenting!*
- 58 CIRCUIT & DESIGN IDEAS *Dual train controller, auto 12V battery charger*
- 60 PC DRIVEN EGO SENSOR ANALYSER - 1 *Really tells what's going on...*
- 66 SMART DUAL 12V BATTERY MANAGER - 1 *For RV's, caravans etc*
- 76 ESR & LOW RESISTANCE METER *At last: check those dubious electrolytics!*
- 82 REMOTE VOLUME CONTROL - 2 *Assembling it and putting it to use*
- 90 DSE 'DISCOVERY SERIES' KIT: *A low cost stereo preamp or mixer*
- 108 VINTAGE RADIO *The ancestors of electronics — 1*

## Columns and Comments

- 4 LETTERS TO THE EDITOR *Encryption & PGP, interesting error in CDI*
- 5 EDITORIAL VIEWPOINT *Reactions to our story on the L2 cache RAM scam*
- 40 FORUM *Why doesn't EA publish more microcontroller-based projects?*
- 99 SHORTWAVE LISTENING *Indonesia Radio's checkered history*
- 100 INFORMATION CENTRE *Windows 95, new life forms and 'synchros'...*

## Departments

- |                           |                            |
|---------------------------|----------------------------|
| 39 BOOK REVIEWS           | 146 DIRECTORY OF SUPPLIERS |
| 112 MARKETPLACE           | 146 ADVERTISING INDEX      |
| 114 EA HISTORY, CROSSWORD | 131 EA SUBSCRIPTIONS OFFER |

## Professional Electronics

- 118 NEWS HIGHLIGHTS *Sony releases 'Interactive PlayStation' with 32-bit CPU*
- 120 HAMEG'S MODULAR INSTRUMENT SYSTEM *Flexible and cost effective*
- 122 POST TEST CARD FOR IBM PC'S *Design uses an EPLD device*
- 126 HIGH QUALITY 'MULTIMEDIA' SPEAKERS *We review the Active 75's...*
- 128 SOLID STATE UPDATE *24-bit sigma-delta ADC: combined photodiode-amp*
- 132 NEW PRODUCTS *Our annual expanded coverage of the latest releases*
- 136 SPOTLIGHT ON SOFTWARE *Harris Technologies' Basbox 5.1*
- 140 SILICON VALLEY NEWSLETTER *US chip market to grow by 26% in 1996*
- 142 COMPUTER NEWS & NEW PRODUCTS *'Smart' sound card, more*

**MANAGING EDITOR**  
Jamieson Rowe, B.A., B.Sc., SMIREE, VK2ZLO

**PRODUCTION EDITOR**  
Milli Godden-Jones

**TECHNICAL EDITOR**  
Rob Evans

**PROJECT DESIGNER/WRITER**  
Graham Cattley

**CONTRIBUTORS**  
Louis Challis

Arthur Cushen, MBE

Peter Lankshear

Jim Lawler, MTETIA

Tom Moffat, VK7TM

Peter Phillips, B.Ed., Dip Ed., ECC

Nick de Vries, MIAME, AMSAE

Neville Williams, FIREE, VK2XV

**COVER DESIGNER**  
Clive Davis

**ADVERTISING PRODUCTION**

Anthony Macarounas; phone (02) 353 0740

**PRODUCTION**

Ray Eirth

**CIRCULATION MANAGER**

Michael Prior

**PUBLISHER**

Michael Hannan

**ADVERTISING MANAGER**

Selwyn Sayers. Phone (02) 353 0734;

fax (02) 353 0613

**SECRETARY**

Ana Maria Zamora

**HEAD OFFICE - EDITORIAL**

PO Box 199, Alexandria 2015.

180 Bourke Road, Alexandria 2015.

Phone (02) 353 0620; fax (02) 353 0513

**Subscriptions Enquiries:**

phone (02) 353 9992

**Book Shop Enquiries:** phone (02) 353 9944

**Reader Services:** phone (02) 353 0620

**Bulletin Board:** phone (02) 353 0627

**INTERSTATE ADVERTISING OFFICES**

**MELBOURNE:** 504 Princes Highway, Noble Park, 3174. Phone (03) 9213 3222; fax (03) 9701 1534. Pilar Misa.

**BRISBANE:** 26 Chermide Street, Newstead 4006. Phone (07) 3854 1119; fax (07) 3252 3692. Graham Smith.

**ADELAIDE:** 98 Jervois Street, Torrensville, 5031. Phone (08) 3352 8666; fax (08) 352 6033. Kerryn Delaney.

**PERTH:** Allen & Associates, 54 Havelock Street, West Perth, 6005. Phone (09) 321 2998; fax (09) 321 2940. Tony Allen

**ELECTRONICS AUSTRALIA** is published by Federal Publishing Company, a division of Eastern Suburbs Newspapers Partnership, which is owned by General Newspapers Pty Ltd.

**A.C.N.000 117 322,**

Double Bay Newspapers Pty Ltd.

**A.C.N.000 237 598** and

Brehmer Fairfax Pty Ltd.

**A.C.N.008 629 767,**

180 Bourke Road, Alexandria, NSW 2015.

Copyright © 1995 by Federal Publishing Company, Sydney. All rights reserved. No part of this publication may be reproduced in any way without written permission from the Publisher or the Managing Editor.

Printed by Macquarie Print, 51 - 59 Wheelers Lane, Dubbo 2830. Phone (068) 843 444.


Distributed by Newsagents Direct Distribution Pty Ltd, 150 Bourke Road, Alexandria 2015; phone (02) 353 9911.

**ISSN 1036-0212**

\*Recommended and maximum Australian retail price.

The Australian Publication emblem on the front of this magazine is there to signify that the editorial content in this publication is largely produced and edited in Australia, and that most of the advertisements herein are the products and services available within Australia.

# LETTERS TO THE EDITOR

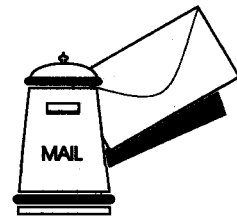

## LF field risk?

After the ABC-TV's Four Corners program, exploring the potential hazards associated with RF-electromagnetic fields, and following Editorial Viewpoint (September '95), I now dare to air a concern I've carried with me for some time, in regard to the low frequency electromagnetic exposures some hearing impaired persons and others are subjected to.

A very satisfying system for some deaf persons to hear the audio part from TV-programs, is the use of a 'loop system', consisting of an independent 20 watt amplifier which receives a signal from the audio output of a TV or video recorder. The output from this amplifier is fed to a multi-core wire, fixed around a room. An induction coil fitted in many types of hearing aids (T-switch), produces a perfect reception of TV/radio sound to the person with a hearing aid, which is not hindering other people. The room however, is now subject to an electromagnetic field.

My concern is the fact that this kind of radiation has, as far as I know, never been investigated and my question is, if you, or any of our readers can throw a light on this subject, in particular about ways to measure and establish acceptable levels of electromagnetic radiation.

**Pieter Engelsman,  
Calliope, Qld.**

## Encryption, PGP

I wish to make some comments regarding PGP and encryption technology as mentioned in Moffat's Madhouse (October 1995 issue). Firstly, the instructions given for getting PGP over the Internet are illegal — Australian users must obtain the international version of PGP, not the version meant for people inside the US.

The US government classifies encryption technology as a munition, and therefore subjects it to export restriction which PGP (in addition to many other software packages) has to live with. The history of encryption technology (PGP is no exception) is a very political and legal one.

Secondly, there are many uses for

encryption technology which are often overlooked:

- Detecting tampering of documents when they are thrown around the 'net';
- Restricting document access to a group of people who the sender wants;
- Providing additional security even if a hacker manages to break into one of your computers;
- In conjunction with a version control system, providing an audit trail whose validity is difficult to question;
- Data compression! This might seem weird, but the PGP software has a compression algorithm built into it, to make it difficult to guess what the original text is. If the person trying to crack the document knew that the document begins with 'Once upon a time' it makes it much quicker to 'crack' a document.

Finally, if you wanted to hide your tracks just buy an encryption book (paying cash and wearing your best disguise) and implement the software yourself, or if you prefer, buy a CD with encryption software on it.

**Andrew Cassin,  
Newport, Vic.**

## Vic Harris story

Thank you for the articles by Neville Williams on my late father, Vic Harris, of High Fidelity Products.

Since my father ran a business, some of his clientele can be described as simply being his customers, but many became personal friends like members of a club. He had an impeccable sense of business ethics and treated his clientele with great respect and caring.

Not many would know of some of our future plans. His wife, my mother was expected by many not to survive the past four years. Being nine years older than my father, even she expected that the long term, future plans would not include her. Proposed accommodation projects, and goals were being assembled over the past 15 years. My husband, Ray Tierney, is an industrial designer. Vic and he were working jointly on two development

projects. Ray hopes to be able to complete them, but admits that he will have a difficult time without him.

Vic's client list to some degree became part of his reason for existence. To the best of his ability, he told me, he would endeavour to survive, and outlive his equipment. The old turntable that he helped my husband install in an antique cabinet for me 20 years ago, has had almost daily use. Over this time, a new stylus, a clean and oil, and a new belt, is all that it needed. I am told that excluding catastrophic failure such as lightning, car accidents, floods and fire, his equipment rarely needs repair so I can't blame him for not being able to outlast it.

I now would very much like to find someone to make use of the stock of spare parts he has left, to provide a repair service for as long as possible. A side benefit to this person would be the absolute assured sale of any equipment which could be assembled out of some of the spare parts.

**Mrs Julia Tierney,**  
Leura, Blue Mountains, NSW.

### Interesting error

The item by Manfred Schmidt in CDI November 1995 entitled '24V - 12V converter for trailers' contains an interesting technical error. Mr Schmidt has determined that a 50% duty cycle for the switching MOSFET is appropriate for half voltage output, where the correct ratio should be only 25%. A doubling of supply voltage from 12 to 24 leads to four times power into a resistive load, requiring a 25% duty cycle to correct.

At 50% duty cycle a normal DC meter will show 12 volts from a 24 volt supply which no doubt Mr Schmidt has found. This is misleading as the RMS value is much higher at 17 volts. The RMS value of voltages or currents must be used wherever the heating effect is of interest, as is the case with lamps.


At 25% duty cycle, the RMS value is 12V and the average only 6V, which is what a normal DC meter will show.

A change in R1 from 47k to 18k will bring the ratio to 25%.

**Philip Allison,**  
Summer Hill, NSW.

Letters published in this column express the opinions of the correspondents concerned, and do not necessarily reflect the opinions or policies of the staff or publisher of Electronics Australia. We reserve the right to edit letters which are very long or potentially defamatory.

# EDITORIAL VIEWPOINT

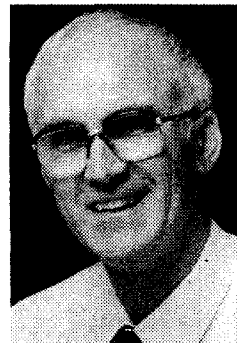

## Reactions to our story on the L2 cache RAM scam...

Judging by the response from readers, our article in the October issue on the 'Cache RAM Scam' really hit the spot. A surprising number of readers have written in, faxed or left a message on the BBS to thank us for uncovering this nasty scam — and unfortunately many have also reported that when they'd checked their own computer, the tests revealed they too had been caught. I gather that quite a few dealers around the country (and also in New Zealand) have been hit with claims for a replacement or refund, and the relevant State and Federal authorities have also been alerted.

What really amazed me, though, was some of the responses that people have reported getting from their dealers. A common reaction, when confronted about a faulty machine, was to pour scorn on the *EA* article and deny that the scam was possible — even when the user had done the tests, and these clearly showed that the machine *they'd* supplied had the fake RAMs and doctored BIOS!

Another common response, from other dealers, was even more incredible. This was to say "That's nothing new — everyone in the industry knows it's been going on for quite a while!"

I don't know about you, but I find this one even more disturbing than the first. If people 'in the industry' have indeed been well aware of the scam for quite a while, why on earth didn't they raise the alarm, and warn both the public and the authorities?

Goodness only knows how many unsuspecting customers have unknowingly bought computers fitted with these fake cache RAMs, because people 'in the industry' knew what some of their colleagues were doing, but kept quiet. By not raising the alarm, these people were virtually acting as accomplices to the crime — even if they've never knowingly sold a faulty machine themselves.

Every industry has its share of unscrupulous and dishonest operators, of course, but surely in any mature and reputable industry the honest people are keen to have the 'rotten apples' kicked out, so they don't ruin the reputation of everyone else. It's clear that the personal computer industry still has a long way to go in this direction, before it will be able to inspire much customer confidence.

By the way, thanks to Tom Moffat and the Internet we've been able to track down a shareware program called CACHECHK.EXE, written by a gentleman from Illinois called Ray Van Tassle. Like AMIDIAG it too seems to be able to tell if there's really any L2 cache RAM present, and can also check memory accessing speed with and without the cache operating. It's now available on our BBS complete with documentation file, in the compressed file CACHCHK2.ZIP.

So if you suspect your machine, this program can provide another testing tool. For the best results, though, boot your machine straight from a DOS 'system' floppy disk (i.e., with no memory manager or network driver enabled) before checking — otherwise you can get some strange results.

*Jim Rowe*

# TECHNOLOGY LEAP IN NEW VAF SPEAKERS

Although its 'DC Series' of locally designed and manufactured kit loudspeaker systems has been very well received by the hifi industry, South Australian firm VAF Research has now gone one better again. Its new Ultra-DC range achieves even more impressive performance, largely by taking advantage of an innovative new 'physical low pass filtering' technology developed by VAF's founder and chief designer Philip Vafiadis.

by **JIM ROWE** and **ROB EVANS**

There's no holding back SA loudspeaker system designer Philip Vafiadis and his firm VAF Research, it seems. Not content with the considerable success achieved by their 'DC Series II' kit hifi speaker systems, they've now come up with a range of 'Ultra DC Series' models, delivering even more impressive performance for only a small premium in cost. And although they aren't intended to replace the existing DC Series II systems (which remain current), the performance/cost ratio delivered by the new models must inevitably have an impact on these — as well as the systems from quite a few other makers.

VAF's DC Series II models were released early last year, you may recall. Louis Challis gave the DC-7 MkII a very favourable review in our April 1995 issue, while we gave an overview of the series as a whole in the May issue. Basically we found them most impressive, with a performance that compared very well with commercial systems costing considerably more. This made them of great potential interest to anyone wanting to achieve 'audiophile' performance on a restricted budget.

It's therefore not surprising that since

their release, the DC Series II models have apparently been very popular — not only in the Australian market, but overseas as well. Significant numbers have now been sold to Singapore, while a large US distributor is launching them into the North American market this month. VAF's reputation and success, as a designer and manufacturer of high quality but affordable hifi speaker systems is steadily growing.

But Philip Vafiadis is not one to rest on his laurels. In fact like all of the best speaker designers he admits (somewhat reluctantly) that his work is driven more by an ongoing 'passion' for improved sound reproduction, rather than a desire to be a successful business entrepreneur. He has been pursuing the goal of 'an even better speaker system' ever since he was back in his teens, and his success to date doesn't seem to have changed that quest.

Even before the DC Series II went into full production, it seems, he was working on another idea — a way to achieve a much smoother overall performance from any speaker system, by using what he describes as 'physical low pass filtering'. After a lot of testing and analysis


this has now been achieved, and the results turned out to be so impressive that VAF has patents pending on the technology involved.

Although the new physical low pass filtering technology can actually be applied to sound sources other than loudspeakers, and also to speakers other than the popular moving-coil/cone variety, it's mainly in this area that it has been tested to date. And it was because the technology allowed such a significant improvement to be achieved in the performance of their existing bass/midrange drivers that VAF decided to come out with the new Ultra system models, based on it.


Although Mr Vafiadis is understandably somewhat cautious about revealing much detail of the technology, until they have full patent protection, he has explained the basic concept to us in general terms and as applied to a loudspeaker. Essentially it involves a special tapered cylindrical structure extending from the front of the centre magnet pole-piece, on the axis of the voice coil and cone. The protrusion is currently machined from acetal plastic, selected for its acoustic properties.

At the far end of the protrusion is attached a larger-diameter cap of the same (or a different) material, with a carefully designed shape and profile. Typically it may be a disc with a diameter around 50% of the effective cone piston diameter. The rear surface of the cap is also covered with acoustically absorbent felt.

By careful design of this structure, VAF has been able to make it act as a selective low-pass acoustic filter, acting upon the sound energy generated by the speaker. It has virtually no effect at lower frequencies, but begins

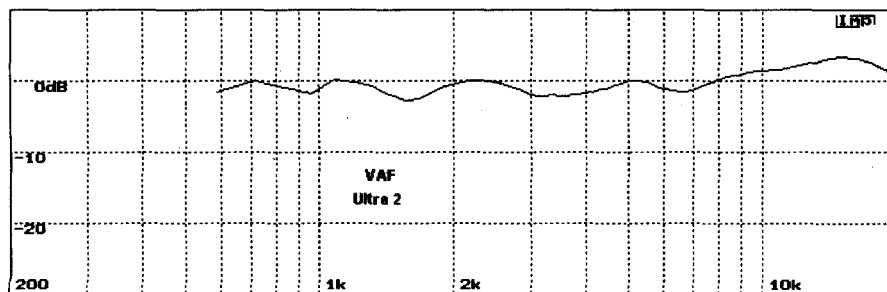

**Fig. 1: Our measured frequency response for the Ultra 2, above 600Hz. Although there are a few minor variations, it is much smoother than the DC-2 model.**

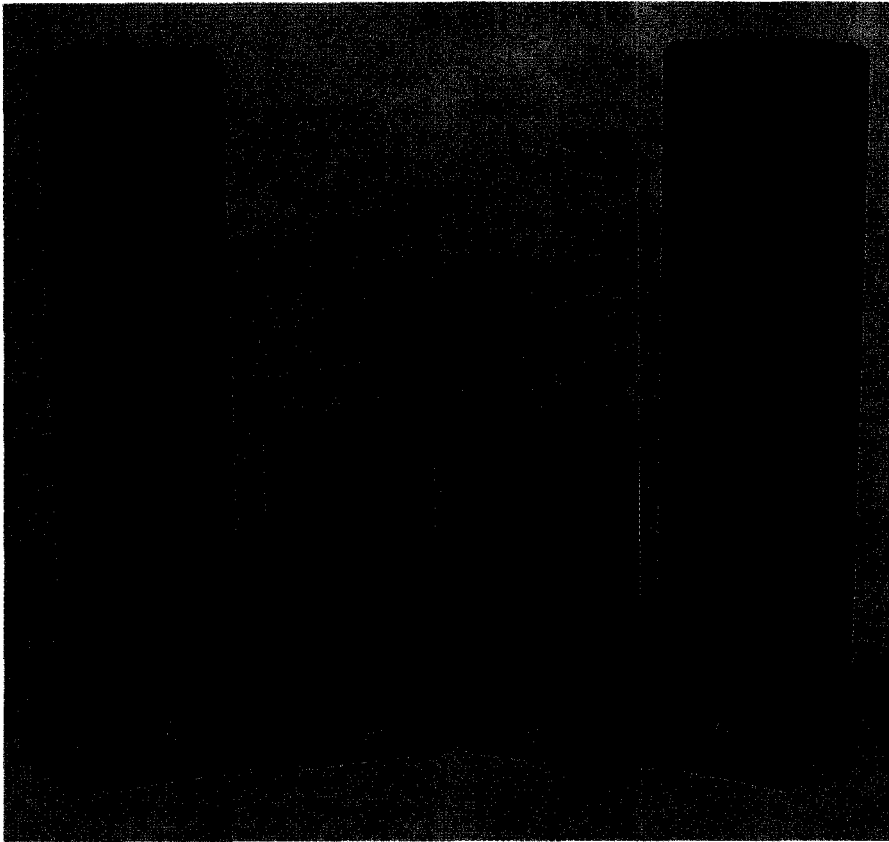

to absorb more and more of the energy once the system's acoustic 'corner frequency' is reached.

But how can this be used to improve the overall performance of a speaker system? Well, all loudspeaker cones — even those in the most elaborate and expensive drivers — tend to 'break up' and develop high-order resonant modes of vibration at higher frequencies. This introduces all manner of peaks and dips in a driver's high-end response, along with various kinds of distortion. That's why, for the best results, it's necessary to use two or more drivers to cover the complete audio spectrum. In theory at least this allows each driver to handle only the frequencies where it operates correctly as a 'piston' — with an electrical filter or 'crossover' network dividing the bands of signal frequencies among them.

The problem is that the design of a crossover network always tends to involve fairly significant compromises. Separating the bands of frequencies effectively can require a complex circuit, and the more complex the circuit the harder it is to stop it from introducing distortion, phase shifts and spurious responses of its own.

A 'two-way' system with only two drivers (woofer and tweeter) tends to involve fewer of these compromises than one with three drivers, but still

isn't easy. Very careful selection of drivers, together with a lot of skill and experience is needed to achieve a smooth overall response, combined with low distortion.

The 'crossover' region is particularly critical, because for best results the output of the woofer needs to be reduced rapidly as soon as its cone begins to depart from correct 'piston' operation. At the same time, the output from the tweeter must be increased at the same rate, and with as little relative phase shift as possible, if the overall response is to remain smooth and 'clean'. With many woofer and tweeter combinations this can be almost impossible to achieve.

VAF's physical low pass filter technology can help in this situation, in a number of ways. Its effect is fairly complex, but one function is to achieve some

of the necessary roll-off of the woofer output at high frequencies *acoustically*, which allows the electrical crossover network to be simplified. It provides an additional means of controlling not only crossover frequency, but also the driver's Q in the crossover region.

By providing additional damping and suppression of higher-order resonances in the woofer cone, it can also extend the useful range of the woofer and bring it 'closer' to the optimum range of the tweeter — reducing the demands on the crossover network and also making it less of a compromise. The nett result is a simpler network, fewer phase shift problems, a smoother response in the transition region and lower distortion.


Now let's look at two of the new Ultra DC Series systems, to see how VAF has been able to take advantage of this new technology.

## The Ultra 2

The Ultra 2 is a compact two-way system intended for use in high quality audio systems where accuracy and realism are required at comfortable listening levels, on a limited budget. It is also very suitable for use in the 'surround' channels of very high quality home cinema systems.

Measuring only 400 x 268 x 180mm overall, each Ultra 2 enclosure uses a VAF proprietary 130mm woofer fitted with the new physical low pass filter technology, teamed with a proprietary 'double chamber' 25mm precision ground metal dome tweeter fitted with VAF's Hypersoft damping. The enclosures themselves are filled with what VAF describes as 'second generation Special Hypersoft' damping foam, claimed to offer improved control of internal reflections and further optimise low-end response.

The simplified electrical crossover network in the Ultra 2 features resin-bound air cored 1% tolerance inductors wound from very heavy gauge wire, and close tolerance capacitors and resistors. It is claimed to provide sophisticated

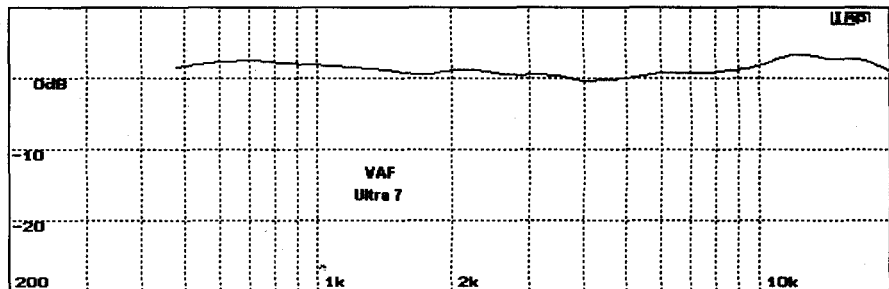

**Fig.2: The measured frequency response for the Ultra 7, above 500Hz. As you can see, it is remarkably smooth and well balanced.**

# Technology Leaps in New VAF Speakers

shaping of frequency, phase and impedance characteristics.

The rated frequency response of the Ultra 2 system is 45Hz - 20kHz  $\pm$ 2dB, with a phase response  $\pm$ 35° above 200Hz. Nominal impedance is 8Ω, with a sensitivity of 87dB/W/m. Recommended amplifier power is 20 - 75W per channel.

Note that although the overall dimensions of the Ultra 2 enclosures are roughly the same as those for the corresponding DC-2 Series II, the aspect ratios have been adjusted to make them less 'narrow looking'. They also have a different finish and trim, with moulded top caps and bases (available in a range of colours and finishes), and full wrap-around 'socks' of acoustically transparent cloth. The trim can apparently be changed quite easily at any time, if desired.

The quoted introductory price of the Ultra 2 system (two enclosures) is \$599 for the kit version, and \$699 for the fully assembled and tested version.

## The Ultra 7

Like the existing DC-7 MkII, the Ultra 7 system consists of two floor-standing enclosures, each a two-way system which teams two of VAF's proprietary 130mm woofers (in this case fitted with the new physical LP filter technology) with a single 25mm precision ground metal dome tweeter. The Ultra 7 is intended for use in high quality audio and home cinema systems, and offers easy loading for compatibility with a wide range of amplifiers.


The Ultra 7 system enclosures are again broadly similar in overall size to the corresponding DC-7 Series II system, although the proportions have again been adjusted to make the new enclosures less narrow looking and more stable — they measure 900 x 268 x 180mm (H x D x W). They also use the new trim system.

The enclosures of the Ultra 7 system are again filled with improved Special Hypersoft damping foam, but feature an angled internal bracing system which combines with the damping foam to function as a tapered, closed-end lossy transmission line for better control of internal reflections. The electrical crossover network again uses 1% tolerance resin-bound air cored inductors wound from heavy gauge wire, and close tolerance resistors and capacitors.

Rated frequency response of the Ultra 7 system is 40Hz - 20kHz  $\pm$ 2dB, with

a phase response of  $\pm$ 35° above 200Hz. The nominal electrical impedance is again 8Ω, while the sensitivity has been increased (compared with the DC-7 MkII) to 91.5dB/W/m. Recommended amplifier power rating is 20 - 100W per channel.

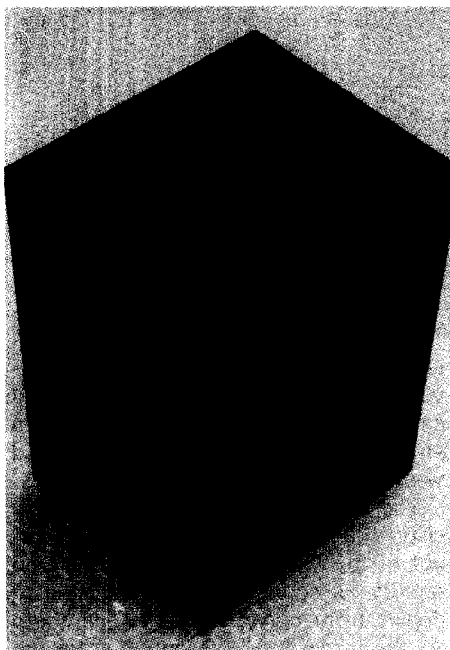The quoted introductory price for the Ultra 7 system (two enclosures) is \$799 for the kit version, or \$999 fully assembled and tested. These prices are only \$50 above those for the existing DC-7 MkII system, although Philip Vafiadis stresses that they probably won't be able to hold them at this level for long.



**A close up view of one of VAF's new models, showing the 'physical low pass filter' device in the centre of the woofer driver. It simplifies crossover network design, and also extends the woofer's effective frequency range.**

## What we found

When VAF very kindly provided sample Ultra 2 and Ultra 7 systems for our evaluation, the first thing we were interested in testing was the frequency response in the critical middle and higher frequency region — the area where any benefits from the physical LP filter technology would be most apparent. And we certainly weren't disappointed.

Tested with our IMP system, the smaller Ultra 2 system turned out to have a very smooth and balanced response. As you can see from the plot (Fig.1), it was within  $\pm$ 3dB from

600Hz to above 20kHz, with no worrying anomalies at all. A very nice response, in fact.

When it came to measuring the response of the Ultra 7 system, though, the results were even more impressive. In fact it proved to be remarkably smooth, as you can see (Fig.2), with only gentle deviations and well within  $\pm$ 2dB from below 500Hz to above 20kHz. Frankly this is the smoothest mid/high end response from a speaker system that we've ever measured, and it shows a very clear improvement over the DC-7 MkII, which does exhibit a small but noticeable 6dB dip at 3kHz in the crossover region.

The other thing we noticed straight away with the Ultra 7 system was its increased sensitivity over the DC-7 MkII. Over the middle frequency range in particular, it's at least 2dB more sensitive than the DC-7 — presumably another benefit of the physical LP filter technology. As well as making the system more suitable for use with modest-power amplifiers, it also tends to give the Ultra 7 better overall balance (the DC-7 MkII is slightly 'top heavy').

We also tried measuring the low-end response of both systems, using both IMP and LMS. This isn't nearly as easy as measuring the middle and high-end response, of course, and like many other 'indoor' measuring setups ours isn't capable of giving truly clear-cut and unambiguous results. However both systems gave a very good account of themselves, with the Ultra 2 quite consistently showing a gentle sag of about 4.5dB around 200-300Hz, a small peak around 90Hz and a slow rolloff below that — with very useful output down to about 45Hz, which is impressive for a system of this size. The Ultra 7 seemed to have much the same performance, although with a more pronounced dip (about 6dB) around 150-200Hz, again a small peak at 90Hz and a slower low end rolloff — with useful output down to about 40Hz.

We can't be positive that the apparent 'dip and peak' were not at least partly due to measuring artifacts, though, especially with the Ultra 7. Getting a reliable measure of the bass performance of this kind of bass reflex system, with two drivers, is not easy.

We also measured the electrical impedance of the two systems, as you can see from Fig.3. Both appear to have less variation than the corresponding DC Series MkII models, with the Ultra 2 (solid line) remaining in the range 8 -



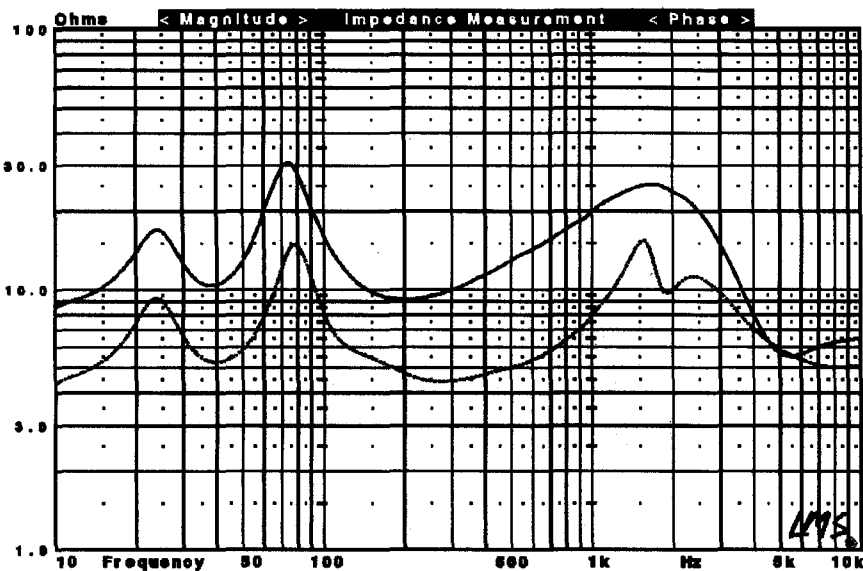


Fig.3: The measured impedance plots for the Ultra 2 (solid, top curve) and Ultra 7 (dotted, lower curve). Both vary less than the corresponding DC models.

30Ω over most of the spectrum and only dipping to about 5.5Ω briefly at about 5.5kHz.

The Ultra 7 has a minimum of 4.5Ω at about 300Hz and maxima of around 15Ω at 80Hz and 1500Hz. Although the curve looks a little odd in the crossover area, there's nothing there that should cause any concern. In fact both systems should be remarkably 'amplifier friendly'.

### Listening tests

For our listening tests, in a typical 'domestic lounge room' environment, we first tried the smaller Ultra 2 system. This gave a very nice account of itself, with a particularly smooth and balanced sound on virtually every kind of programme material. Its bass response was most impressive, for such a small system, and the improved middle register now mates well with the quite exceptional high-end performance of VAF's dome tweeter. The transient response was very clean, and we couldn't really detect any audible distortion.

Not surprisingly, though, the Ultra 7 system was even more impressive, with an exceptionally smooth and 'transparent' sound on every kind of material we tried — solo vocal and full choral works, string/brass/wind instrumental, full orchestral and so on. We were particularly impressed with the stability of its stereo imaging — a good indicator of the absence of 'funnies' in the dispersion and/or phase response, especially in the mid range. The sound was also very well balanced, with no real evidence of that dip-and-peak that seemed to be present in the measured bass response...

The transient response also seemed to be exceptionally clean and accurate, and again we couldn't detect any audible distortion.

The existing DC-7 MkII system is already an excellent performer, so the new Ultra 7 with its much smoother mid range and better overall balance can now


only be described as *exceptional*.

By the way, we also liked the new styling of the Ultra models, with their more balanced aspect ratio and tidy wrap-around grille cloth trim. However some hifi enthusiasts may find them a little frustrating, as you can no longer 'unclip' the grilles to display the drivers.

In short, then, and judging from these two sample systems, VAF seems to have achieved quite a significant breakthrough with its new physical LP filter technology and the Ultra Series it has made possible. Both the Ultra 2 and Ultra 7 systems show significant advances over the corresponding models in the DC Series MkII range, and are now very nice loudspeaker systems indeed.

Even more than before, they surely represent an excellent choice for anyone seeking to achieve 'audiophile' performance on a restricted budget. In fact from our experience, you'd have to spend considerably more to achieve even comparable performance.

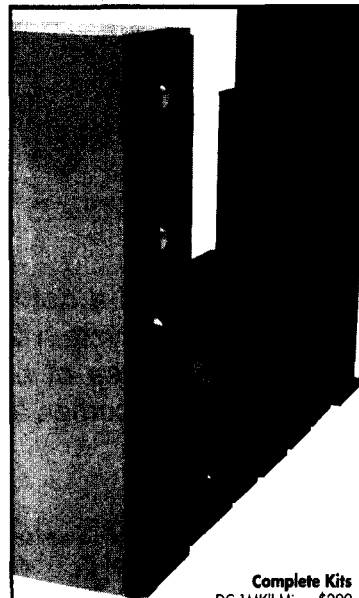Further information on any of the VAF Ultra Series models is available from VAF Research at 291 Churchill Road, Prospect 5082 (or PO Box 380, Greenacres 5086); phone (08) 269 4446, or fax (08) 269 4460. ♦



## The Best

THE '95-'96  
**SOUND AND**  
*image*  
AWARDS

Winning an "Audio system of the year Award" at the '95-'96 Sound & Image Awards, VAF loudspeakers are arguably the finest in their price range in Australia today.

For instance, *Electronics Australia's* evaluation of the new Ultra 7 speaker system, stated; "...this is the smoothest mid/high end response from a speaker system that we've ever measured."

Whether your interest is home theatre or superior quality sound only, all VAF loudspeakers offer natural and tonally accurate responses, 'walk in' sound stages, realistic dynamics and low distortion at all frequencies.

VAF loudspeakers have already received five 'best buy' reviews to date and are used by professionals such as the ABC. All VAF loudspeakers are available only directly from VAF in kit form or fully assembled. To find out what all the fuss is about, phone **Free call 1800 818 882**. Finish your own symphony!

#### Complete Kits

- DC-1MKII Micro \$299
  - Ultra DC-1 MKII must be heard to be believed \$349
  - DC-2MKII compact monitor used by the ABC \$499
  - Ultra DC-2 compact sound at its best \$599
  - DC-5MKII compact point source array \$605
  - DC-6MKII centre channel \$349
  - DC-7MKII compact floor standing \$749
  - Ultra DC-7 truly exceptional \$799
  - DC-9MKII large 5 driver array \$995
  - Signature I-51 no compromise compact \$1698
  - Signature I-66 absolute accuracy \$3799
  - IB-3 micro servo active subwoofer \$999\*
  - IB-6 compact servo active subwoofer \$1499\*
  - IB-X no compromise subwoofer \$1999\*
- (\*available only fully assembled)


**VAF**  
RESEARCH

VAF Research Pty Ltd  
291 Churchill Road Prospect  
South Australia 5082  
Ph 08 269 4446 Fax 08 269 4460

READER INFO NO. 2

# Video & Audio: The Challis Report
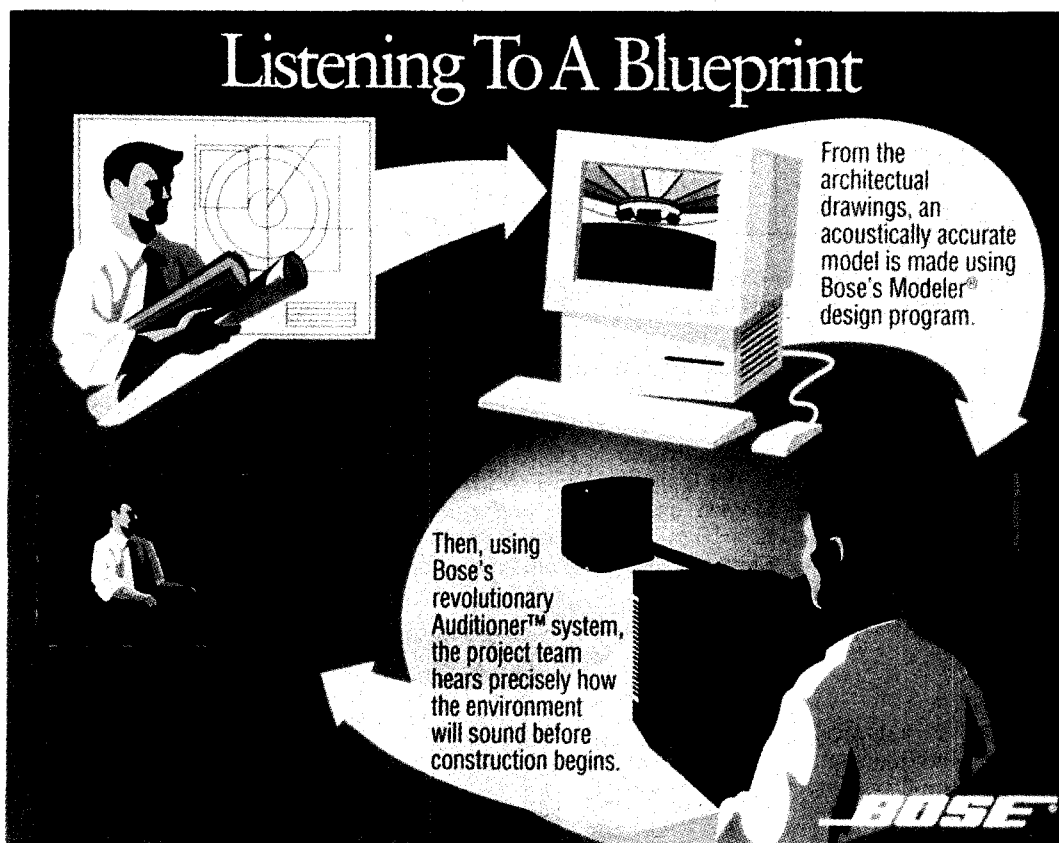
## The Bose 'Auditioner', and 100 Years of Applied Acoustics



This month, Louis Challis had the opportunity to attend a demonstration of Bose Corporation's new Auditioner, a computer modelling and simulation system for auditoria and other acoustical environments. Acoustical engineering is his primary area of expertise, of course, and he was struck by the significance of this development — which comes almost exactly 100 years after the 'birth' of the modern science of applied acoustics...

Imagine a scene a century ago, in which a young, brilliant and resourceful university lecturer stood inside a newly completed lecture theatre which had proved to be virtually unusable, because of the persistence of the sound whenever a lecturer attempted to address his classes. The lecturer was Wallace Clement Sabine. The year was 1895, and the time at which this scene occurred was typically between 2.00am and 4.00am, five nights per week.

Sabine, with one assistant, would stand in the lecture theatre and perform strange measurements involving a series of organ pipes, a stop watch, and with just his

ears as the instrumental detector to assist him during those ungodly hours. The location of the measurements was the Fogg Art Museum's lecture theatre, at Harvard University.

When I first read Sabine's collected papers on acoustics in 1966, I too had been performing somewhat similar measurements at 2.00am. Whilst Sabine was forced to perform his measurements to avoid the noise of tramcars, my unwanted source of noise was overflying aircraft at Rockdale, in southern Sydney.

When I read about Sabine's work, I experienced a feeling of 'deja vu'.

Thereafter, apart from both of us being involved in acoustical measurements, all similarity ends.

Sabine's intrepid research work resulted in a new and exciting technology. Sabine was the father of modern acoustics, and the theories and principles which he developed impinge on each of us, and our lives, on a daily basis.

Sabine accepted the challenge of the task he was given with zeal. Whilst a lesser man might have been satisfied with 'partial correction of the problem', Sabine broadened the task to include two other lecture theatres which displayed similar problems.

More significantly, realising the need for additional data, Sabine also chose to include a constant temperature room located at the Jefferson Physical Laboratory and another lecture room which displayed 'tolerable acoustics', into the array of rooms whose performance characteristics he measured.

It is only when one compares Sabine's equipment with that which almost any acoustician would use today to analyse similar problems, that one begins to understand the paucity of the resources that Sabine brought to bear at that time.

Sabine used four organ pipes (with solenoid activated switches), a constant pressure air supply, a stop watch, and his ears. Yes, he used his ears as the detector to identify when the reverberant sound energy in each of the rooms decayed to the point of 'inaudibility'.

It is only when you read what Sabine wrote about his studies, and extend that reading to encompass what other contemporaries wrote about his work, that you realise how great and rare an ability he displayed.

His greatest strength lay in that, having examined a complicated situation in which he correctly identified the problems, he was able to develop practical solutions. Those solutions in turn ultimately opened the door to both his, and subsequently our understanding of the fundamental principles involved.

Sabine immediately recognised the importance of good hearing, as well as the need to be able to both identify, and preserve the frequency balance in such environments. His understanding of the need to exclude extraneous noise from the rooms in which he performed his evaluations was extremely perceptive. His understanding of the importance of maintaining an appropriate signal to noise ratio for his test signals ultimately proved to be the most critical factor in his studies. In the absence of all of those elements, he would never have been able to perform valid measurements.


Now Sabine was not just a good physicist — more significantly, he was the first architectural acoustician who was able to logically apply scientific principles to his design studies. His pioneering work was immediately recognised in Boston.

In 1900, he was commissioned to assist the architects in the design of the new Boston Music Hall. For those of you who have not been to Boston, or have not read books like Beranek's *Music, Acoustics and Architecture*, you would be unaware that the Boston Music Hall is acclaimed as being one of the best concert halls in the world.

In the first half of this century, between 1900 and 1950, architectural acoustics came of age. We not only saw the development of sound level meters with A, B and C-weighting networks, but also saw the development of octave band analysers, level recorders, amplifiers, loudspeakers, electronic oscillators, and even cathode-ray oscilloscopes.

During that 50 year period were founded the three major companies which dominated the field during the next 50 years.

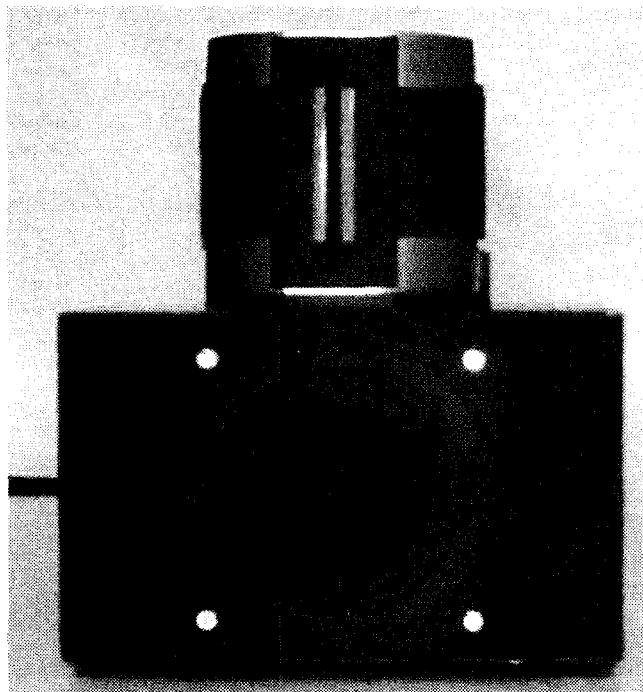Those companies were in order of creation and importance, General Radio and



**When Louis Challis himself was modelling the acoustics of the new Parliament House in Canberra, he used this 'scaled down' speaker system to generate sounds at 10 times normal frequencies. It covered 1-80kHz, +/-6dB.**

Hewlett-Packard in the USA, and Briel & Kjaer in Denmark.

If one excludes Sabine's momentous work between 1895 and 1900, the second world war, nearly 50 years later, provided more impetus for applied acoustical research than any other single factor during that 100 year period. The war (and the subsequent creation of the United Nations) resulted in the creation of many illustrious firms, the most notable of which was Bolt Beranek & Newman, who were also located in Boston.

During the second half of the century, from 1950 to the present, the study of acoustics came of age. More significantly, the commercial, educational and environmental facets of acoustics suddenly assumed a prominence that would have even staggered Wallace Clement Sabine. During the first half of this century, Sabine pioneered the technique for carrying out two dimensional acoustical modelling.

During the second half of this century, three dimensional modelling using carefully scaled models of auditoria and important buildings, gained technical prominence — particularly in the period 1950 to 1980. Important auditoria like the Concert Hall and Opera Hall at Sydney's Opera House, made use of scale model testing. The evaluation procedures were both slow and tedious. More significantly, they were fraught with innumerable technical problems.

The underlying principle was based on scaling the test frequencies used (as well as the absorption coefficients), to match the scaling factor of the model constructed. Thus by way of example, if you chose a model whose dimensions were 1/10th of those of the proposed chamber, your test frequencies would be scaled up by a factor of 10:1. Even though there were innumerable problems and frequent pitfalls involved in performing an analysis of a future building with an acoustical scale model, it offered the only effective and analytical procedure available at the time.

Relatively few acoustical engineers ever get the chance to undertake a scale modelling program for a major auditorium. I guess I am one of the more fortunate ones, as I was given the opportunity when I was appointed as the acoustical engineer for the New Parliament House, Canberra.

Titles are fine, however when a monumental project is dished up with unrealistic deadlines, the pleasure and the excitement soon turns into a monumental headache. The client insisted that the architectural studies and the refinements of the acoustical design had to be completed

within three months.

## New approach

Faced with what appeared to be an insuperable problem, I set aside the then 'current practice' and its related measurement technology, and in effect invented a new way of performing acoustical modelling. I described it as 'computer controlled acoustical scale modelling'. Whilst other acousticians and engineers used tape loops and multi-speed tape recorders to laboriously re-analyse their scaled acoustical data, I decided that approach was 'strictly for the birds'. The time required to extract the critical data by that approach, was anywhere from one to five days for each different variant of the model.

The approach that I adopted would probably now be described as being close to the 'cutting edge' of new technology, circa 1981. I decided to build a 576KB digital memory, which provided

392K of 12-bit resolution data storage. With a 400kHz sampling frequency I could store approximately one second of acoustical data.

I could then expand that data to 1/10th of the original sampling speed, and still achieve a commendable frequency resolution — i.e., a nominal 18kHz bandwidth in the reduced speed mode.

I set out to use the digital memory with a new Hewlett-Packard computer. That computer was already capable of controlling a new digital one-third-octave band real time analyser. With the addition of a spark source which was modified to accept computer control, I believed I would be able to use the real time analyser's proprietary software to analyse the characteristics of the 1/10th scale acoustical model.

## Minutes, rather than days

What this system offered us was the ability to analyse the characteristics of the model in a few minutes, rather than in a few days. More importantly, it provided us with the mechanism for processing the data, and simultaneously printing the graphed 'report ready' output onto a matching HP digital plotter.

Whilst I can now afford to gloss over the myriad of problems which we experienced in commissioning the system, it is still noteworthy that all the modelling studies were completed within the restrictive three-month period, and the 'fast track' design process was neither impeded nor prejudiced by our efforts at that time.

Relatively few people realised that I was neither satisfied, nor content to just perform testing and present the client with the results. I realised that the multitude of graphs and tables would have no real significance or meaning to most of those who would read it.

I felt that further refinements in the testing procedure were essential. I believed that those refinements should provide the client with an appropriate impression of the quality of sound for each model variant evaluated.

The approach I adopted was to record the voice of a staff member whilst he read the text of an act of parliament. That signal was then scaled up in speed/frequency by a factor of 10 using a Kudelski Nagra IVSJ instrumentation recorder, and replayed into the model.

In order to reproduce the re-scaled sound, I constructed an unusual two-way loudspeaker, using a Philips mid-range driver and a Technics Leaf tweeter (Type 10TH 1000).

With an appropriate crossover network, the miniature speaker system was capable of faithfully reproducing the scaled frequencies to cover the range from 1kHz to 80kHz, +/-6dB.

The sound produced in the model was

then recorded with a miniature Bruel & Kjaer 1/4" microphone, type 4136, and its signal was then recorded by the digital memory.

The final step involved replaying the sound at 1/10th the recorded speed onto a cassette recorder, for the client's subsequent audition.

During each stage of the modelling program the reproduced speech from the modelled loudspeaker was recorded at various critical points within the model. When the client and the architects ultimately heard the tape recordings, they were able to assess the quality of the sound, and give their approval for the design concept.

At the time, I considered this approach to be a technical break-through. In the ensuing period, I would now describe it as

either the cost or the complexity of the tasks which I had successfully completed during that decade. The Yamaha acoustical analysis programs displayed an exciting innovative perception of the technical issues involved, and gave that company a decided advantage when offering their proprietary hardware for evaluating the performance characteristics of various new auditoria in Japan.

Yamaha decided not to market their software, and the advantage was strictly 'in-house'. Around about the same time I learnt that a Norwegian group had developed a software package which achieved similar results, which anybody with enough money could purchase. The complete package proved to be far too expensive, and very few people were prepared to purchase it.



**Danny Neuman, one of Louis Challis' associates, shown adjusting a microphone inside the 1/10th scale model for the Representatives Chamber of new Parliament House, during the acoustic modelling.**

just another milestone in the development of acoustical philosophy and technology.

## Gives perspective

You may wonder why I bother to account my distant past, in the midst of what started out to be a conventional technical review. Well frankly, it provides a historical perspective for the main subject of this article.

In 1989, following the successful completion of New Parliament House in Canberra, I decided to visit the Yamaha Acoustics Laboratory in Hamamatsu, Japan. To my surprise, I discovered that a team of dedicated acoustical engineers had recently developed a computer modelling procedure for large auditoria. That program could analyse auditoria without the need to construct a scale model and generate

## Enter Bose...

Enter centre stage Bose Corporation, who were aware of what Yamaha and the Norwegians had developed. More importantly, they learned through the 'grapevine' that at least two of their most prestigious competitors were developing similar programs. The year was 1986, and Bose decided to develop a program which they ended up calling the Bose 'Modeller Design Program' (MDP).

Unlike their competitors, who started out with the idea that their programs were marketable, Bose started out with the diametrically opposite viewpoint. The Bose concept was that the MDP should be available to assist any, or all prospective professional users.


Unlike the competing programs, its most important feature was its fundamental and

straightforward ability to graphically model any room or space. Each surface of that space could be sub-divided into areas, with acoustical characteristics conforming to those from which it would be constructed, or which would be added to it after construction.

To further simplify that task, the program already contained a database with a wide range of conventional, reflective and absorptive materials.

Having drawn the plan and each of the elevations of walls or views of the ceiling of your modelled space, you would then select the materials. By nominating the sound absorption characteristics of each sub-surface on that wall, floor or ceiling, the program would then compute the following characteristics:

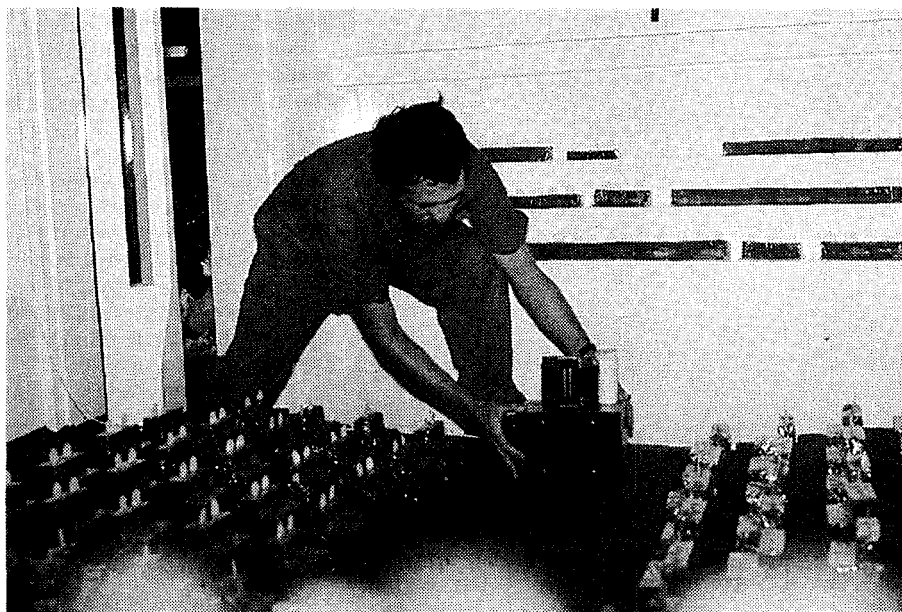1. Reverberation time.
2. Speech transmission indices, including an array of different parameters.



**Another view of Mr Neuman in the model, this time positioning the special scaled down speaker system used to generate test signals at 10 times normal frequencies. It used a Philips mid-range driver and Technics leaf tweeter.**

3. The sound pressure level and point response for sound generated by a nominated single loudspeaker, or an array of specific loudspeakers positioned anywhere within that space, for any nominated listener position within that space.

4. The sound intensity plot for one or more arrays of loudspeakers positioned at any location or locations, within that space.

The only catch with the original MDP versions, and all subsequent versions up to 4.0, was the paucity of data on loudspeakers from competing manufacturers. Obviously, if one were to nominate one or more combinations of loudspeakers, and particularly if they were Electro-Voice, Altec Lansing or JBL speakers, you would need accurate, extensive and appropriate data for the computer modelling to be useful.

With the right data, you could rapidly determine (acoustically model) the frequency response of nominated loudspeakers at any point in any room.

The early version of the MDP proved to be extremely 'user friendly'. Bose chose to use an Apple Macintosh computer in preference to a DOS based computer. That of course was no accident. At that time (and even now) the Apple Macintosh based software and hardware, are generally superior for graphical analysis of this type, when compared with the competing DOS or Windows based software and hardware.

At the time of the initial release of its MDP, Bose had relatively few PA type loudspeakers which were 'fit for purpose'. As a result, Bose had qualms about incorporating design data for their competitor's products. By the same token, it's equally possible that the competitors may well have had similar qualms about providing all

the relevant data on their loudspeakers, to an up and coming competitor.

In the ensuing period, it would appear that two issues wrought changes in Bose's original philosophy. The first appears to have been the result of their competitor's reticence in providing Bose with explicit and accurate performance data on their products. The second, and I suspect the equally compelling factor, was Bose's subsequent reluctance to provide data on products which were not of their manufacture.

Even when taking into account the inaccuracies that could devolve from inappropriate specification of absorptive materials, and misapplication of the data provided, the early MDP proved to be reasonably accurate and convenient. Subsequent versions proved to be substantially better, as

user feedback resulted in the development of new features, and new or enhanced 'user-friendly' routines.

Anybody who used Version 4.1 or 4.2 would have to acknowledge that the speed with which a problem could be analysed, shamed any other conventional computational or computer based procedure available to them.

In the early 1990s, a number of Bose's competitors had also developed competing computer software intended for basically the same purpose. A number of those manufacturers started to aggressively market and/or distribute those programs. In 1991 and 1992, I evaluated two competing programs. I soon formed the view that the Bose MDP was considerably easier to master, as it provided both the graphical and tabular results in a format which was easier to digest.

Bose received copious feedback from a multitude of engineers and technicians who regularly used its MDP. They accepted the comments and criticism and proceeded to substantially improve and modify the program's format. Alas, during this period, they progressively dropped references and data on competing products as soon as comparable Bose products became available.

By mid 1989, Bose's top management reassessed their marketing strategy for professional loudspeakers. They decided to become a major player in the global supply of PA systems. They all agreed that the MDP gave them a distinct marketing edge with design engineers, during the critical phase when components were being selected for a system.

They also acknowledged that the MDP gave them no perceived advantage with the technically untrained architect or facility manager, let alone the developer who was frequently providing the cash. The key marketing issue foremost in their minds, was what could or should they do to convince the vacillating purchaser(s), that the system being proposed by Bose, was clearly the best.

## New R&D project

At that point they set up a new research team of five senior engineers, and a number of peripheral engineers with the task of developing the 'Auditioner Audio Demonstration' system.

The key people in the group were Dr Beckman, who was responsible for developing the algorithms in the software; Chris Ickler, a senior physicist and project manager; and Ken Jacobs, who provided the conceptual vision and who ultimately developed the 'schematic block diagram' on which the system was ultimately based.

The Bose 'Auditioner R&D group' were a skilled group of electronic experts in audio-engineering who broadened their skills to encompass architectural acoustics, and related aspects of speech transmission. Ken Jacobs' proposals must have been viewed

## THE CHALLIS REPORT

as being audacious, and even possibly speculative by the rest of the team's members.

The magnitude of the task must have been somewhat daunting, since what they were trying to do was model all the physical, directional and acoustical characteristics of PA systems, whilst simultaneously replicating all the relevant architectural features of spaces in which the speakers would be placed. The program had to be able to provide the flexibility to position the loudspeakers anywhere within that space. It also had to provide the flexibility to position a listener at any other point within that space, and then modify the resulting sound field at that point to conform to what the listener would actually hear.

During its development, the Auditor system underwent a number of dramatic changes. The first developmental system was monstrous in size, encompassing racks of equipment, in much the same way that the original Yamaha DSP processor (which now only requires one LSI chip) required two full 19" racks of equipment.

### Australian DSP


The refinements in the design were materially assisted by Bose's adoption of the Australian Lake DSP system, as a fundamental component. Bose are full of praise for the Lake DSP system. They acknowledge that without it, the Auditor system would not be nearly as good. As I subsequently learned, the Lake DSP card and the associated special LSI chips perform a number of critical functions.

The DSP card provides special filters, and generates full bandwidth signals with a 'latency' of 1.5 seconds. The acoustical signal is provided from an external source which may be a CD player, tape or even a person speaking into a microphone. The Auditor program and its DSP processor convert that signal into a two-dimensional signal which replicates a three-dimensional space.

Not just any three-dimensional space, mind you, but the space that has been modelled with a revised Bose 'Modeller' software routine which contains a number of critical refinements — which as yet, have not been incorporated into the basic Modeller program.

Bose were less than forthright in providing information as to what those changes might be. They were unwilling to describe the program in more detail, nor to give any clues which might end up assisting their competition.

They were prepared to describe in general terms how an engineer by the name of Morton Jorgenson was given the task of authenticating the accuracy and realism of the dynamic response of the Auditor system. He apparently spent three or four months in assessing the dynamic response with impulse conversion tests, and inter-comparing with live A-B testing the Auditor system in five different sized rooms, where he also evaluated the total

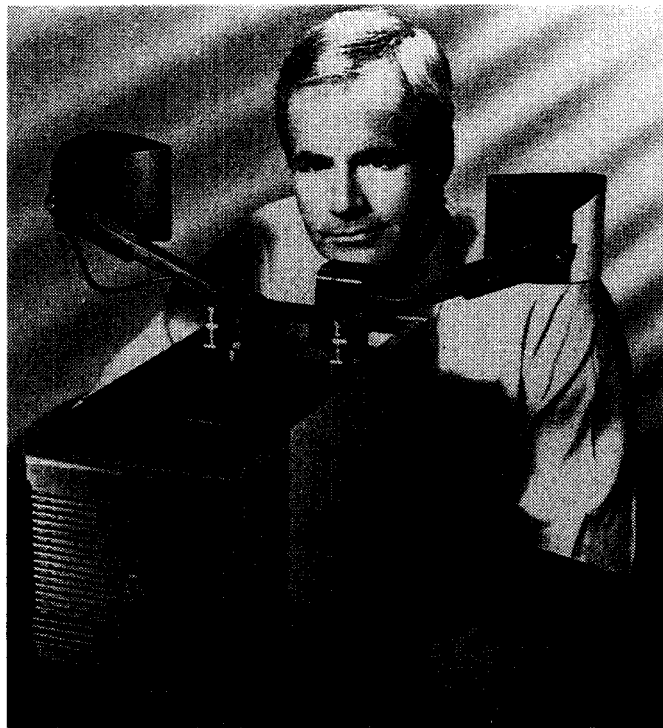

**The Bose Auditor system uses this active speaker setup to create an accurate simulation of the sound which will be audible at any desired location inside the acoustic environment being modelled by the computer.**

system and room. The five rooms had reverberation times ranging from a low of one second to a high of 4.5 seconds.

He also evaluated loudspeakers with 'Qs' or directional factors ranging between 4-27. These tests were conducted with central clusters and distributed speaker arrays, and made extensive use of the intelligibility tests of the American Standard ASA S.3.2:1989 — which is similar to AS2822-1985, 'Acoustics, Methods of Assessing and Predicting Speech Privacy and Speech Intelligibility'.

Those of you who are familiar with the speech transmission or speech intelligibility indices would be aware that for a PA system or speech communication system to be classified as 'good', normally requires an STI index of approximately 0.6 or better. The Auditor allows you to compute that STI index, and to audibly assess its impact on speech or music transmission.

As the Auditor system developed it became smaller, and with the availability of faster and (less expensive) Apple computers, the flexibility of the system improved immeasurably.

It became possible to rapidly change speaker selections, speakers positions, directional pointing angles, and equally importantly the acoustical characteristics of a room, to assess the quality of sound at any position of one's choice. As both a design and marketing tool, the Auditor system has immense potential for Bose, as well as for its clients.

Sixty Bose Auditor systems were constructed to satisfy the firm's current requirements, and 60 separate dedicated groups of operators were trained to use those systems. Obviously, if the wrong information were to be fed in, then the output would be simply a case of GIGO (garbage in, garbage out).

With so much at stake both professionally and financially, Bose were not willing to allocate Auditor systems to any regional or marketing office, except where a competent operator had been trained to use it.

These systems were distributed world-wide for evaluation purposes, and Australia received two for local use, with two additional systems for use in the near east. In order to be able to optimally use the system, the operator needed to understand the electronic as well as acoustical and electro-acoustic theory, all of which are of fundamental importance.

### The Auditor

The Bose Auditor Audio Demonstration unit consists of a modestly sized box in which amplifiers and a sub-woofer have been incorporated. At one end is a chin rest on which the listener places his chin. On both sides of the chin rest, a small tweeter extends on an arm pointing towards the listener's head.

The Auditor box is connected to the computer which is normally positioned on the table where the demonstration is performed. The computer is capable of displaying a wide range of information, the most significant examples of which are plan or two-dimensional perspective views of what you would be able to see in the modelled space from the selected position at which you are listening.

The computer provides the ability to select a number of different positions at the

## THE CHALLIS REPORT

touch of a button on the keyboard (or through the use of the mouse). It is able to alter any one of the significant dimensional, positional or acoustical parameters with prior preparation, so as to provide rapid A-B comparisons. Those comparisons frequently encompass changes of speaker configuration or directivity, or even the listener's position, at a single key stroke.

Bose Australia have recently used the Auditor to model the quality of sound of various PA options for dozens of different auditoria and sporting venues. At the time of my visit to their office, they demonstrated pre-prepared data for St Andrews Cathedral in Canberra.

Now as it happens, I have visited St Andrews Cathedral on a number of occasions. I am familiar with its visual attributes, and sadly, with its acoustical liabilities. I was able to compare the modelled sound quality for a single centrally positioned speaker array, with my memories and clear recollections of the poor sound propagation within that worthy cathedral. The demonstration allowed me to position my ears at many locations within the cathedral.

I was impressed by what I would describe as the realism of the modelled sound. I was equally impressed by the convenience with which I could re-position myself in that acoustical model, to assess the reproduced sound quality as well as its speech intelligibility, with the similarity of sound that I had previously heard in the cathedral.

The Bose Auditor is a bold and exciting milestone. It epitomises just how far acoustical theory and practical applied research and development have progressed, in a tad less than the 100 years since Wallace Clement Sabine initiated his exciting first steps in practical applied acoustics.

Bose Corporation are to be commended for what they have achieved in terms of a practical synthesis of wide ranging computer controlled DSP technology with fundamental psycho-acoustic principles. This development constitutes another impressive milestone in the continuous quest for superior technology which provides us with new and more effective design and evaluation tools.

Whilst neither you nor I will be here in the year 2095, it would be indeed a wonderful exercise in crystal ball gazing, to guess just how far or fast this technology will develop in the next century.

### Suggested further reading:

1. Sabine, Wallace C. *Collected Papers on Acoustics*. Dover Publications, New York 1964.
2. Beranek, L.L. *Music, Acoustics & Architecture*. John Wiley & Sons, New York 1962. ♦

## AUDIOPHILES!

NEW PRODUCTS FOR 1995/96 NEW valve TESTER to test valves for balance, noise & distortion. Service available for \$2.00/valve. Brand new and New old stock valves including Sovtek's 12AX7WXT, 6922, Mullard 12AT7 with gold pins, Svetlana 6550WB and many more. New Hybrid and All valve Triode. Integrated Amplifiers in preparation. Kit Digital to Analogue Converter.

Other products include: Kimber Caps and cables, MIT Caps, Cerafine Caps, Holco resistors, High Quality Valves, ALPS Pots, and many others.

1995/96 Product Catalogue in preparation, send \$1.00 stamp to reserve catalogue. PHONE & FAX: (03) 9807 1263

**CONTAN AUDIO**  
37 WADHAM PARADE  
MT. WAVERLEY, VICTORIA 3149

READER INFO NO. 3



## LEGACY

*still needs your help*

## SPEAKER PARTS DIRECT

ALL THE LATEST **vifa** DRIVERS AT THE BEST PRICES

<u>Vifa Tweeters and Midrange drivers:</u>		Was	Now		Was	Now	
D19TD-05-06	1/4" soft dome tweeter	\$55	\$25	M22WR-09-06	8" coated cone, cast frame	\$199	\$143
D19AD-05-06	1/4" metal dome tweeter	\$88	\$39	M26WR-09-08	10" coated cone, cast frame	\$229	\$179
D25TF-55-06	1" soft dome tweeter	\$74	\$36	M30WO-09-08	Top 12" woofer, cast frame	\$348	\$163
D25AG-35-06	1" metal dome tweeter	\$114	\$55	<u>Vifa Car Audio speakers and accessories:</u>			
D25SF-04-06	1" soft dome shielded tweet.	\$98	\$48	A20WG-00-08	8" two-way coaxial car speaker	\$199	\$99
D26TG-35-06	1" double chamber tweeter	\$114	\$39	D26NC-05-06	1" neodymium soft dome tweeter	\$99	\$59
H25TG-35-06	1" soft dome horn tweeter	\$114	\$46	Flush mount cup or mounting wedge for D26NC			
H26TG-35-06	1" fabric dome horn tweeter	\$119	\$67	<u>Peerless Speaker Drivers:</u>			
H10ND-39-08	4" coated cone midrange	\$99	\$55	811582	1" soft dome tweeter	\$45	\$26
H13MH-08-08	5" coated "Rolls Royce" mid	\$119	\$87	811827	1" wide Angle soft dome tweeter	\$69	\$36
D75MX-31-08	3" soft dome midrange	\$129	\$99	821214	2" high quality dome midrange	\$139	\$75
<u>Woofers with long life rubber surrounds:</u>		Was	Now	831622	8" efficient high quality polycone woofer	\$149	\$75
C13WG-08-08	5" coated woofer - a legend!	\$99	\$49	831680	6.5" high quality polycone woofer	\$148	\$69
H135G-09-16	5" shielded wool, cast frame	\$148	\$68	831531	10" polycone woofer	\$169	\$89
P13WG-00-08	5" polycone woofer, cast	\$128	\$63	831676	10" high quality paper cone woofer	\$249	\$99
P17WG-00-08	6.5" polycone woofer	\$128	\$49	831857	12" CC line polycone woofer	\$298	\$161
P17WJ-00-08	6.5" polycone woofer, cast	\$158	\$68	<u>Dynaudio Drivers:</u>			
H18W0-09-08	6.5" air dried cone, cast frame	\$149	\$119	Dynaudio 17W-75XL	17 cm woofer, 12 Ohms	\$248	\$125
				Dynaudio 24W-75	24 cm woofer, 4 Ohms	\$238	\$120

Call or fax for free price list on all our drivers, crossovers, coils, Solen capacitors and other speaker parts. Or send \$10 cheque, money order or fax with credit card details for our data book with engineering specs on every VIFA, PEERLESS AND DYNAUDIO driver we sell. (Price includes air mail postage). Bulk buyers of any VIFA driver listed here or not: We are still much cheaper than anyone!


### HOW TO ORDER:

- Phone order with your Bankcard, Mastercard or Visa.
- Fax or post your order with your credit card details - or Post a money order or bank cheque.
- Delivery charge: \$10 per order Australia wide. Please allow one week for delivery.
- Some items are limited - stock available only until sold. Order now!

**SCAN AUDIO PTY LTD, P.O. BOX 242 HAWTHORN VIC 3122**  
PHONE: 03-9429 2199 FAX: 03-9429 9309

READER INFO NO. 4

# What's New in VIDEO and AUDIO

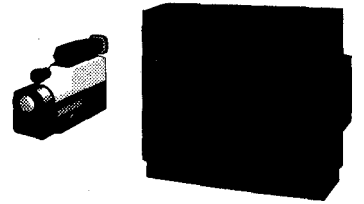

## Compact, well priced mini hifi system

Kenwood Electronics claims its new UD-213 mini system is 'big on entertainment', but conservatively priced with an RRP of \$649. Finished in brilliant 'crystal cut' translucent black, the

UD-213 mini offers the same quality finish as its higher priced stablemate minis. It provides a two channel (2 x 40W) stereo amplifier, five-band spectrum analyser, graphic equaliser, double cassette deck, CD player, AM/FM stereo tuner, two way speaker system and infra red remote controller. Also inbuilt is


Kenwood's ASP or Acoustic Signal Processor, designed to recreate the ambience of an arena, jazz club or stadium.

The UD-213 employs a dual two way speaker system employing 130mm (5") woofer/mid drivers and 50mm (2") dome tweeters for extended high frequency response. The UD-213 is covered by a two year warranty and is available at selected Kenwood dealers.

For further information circle 271 on the reader service coupon or contact Kenwood on (02) 746 1888.
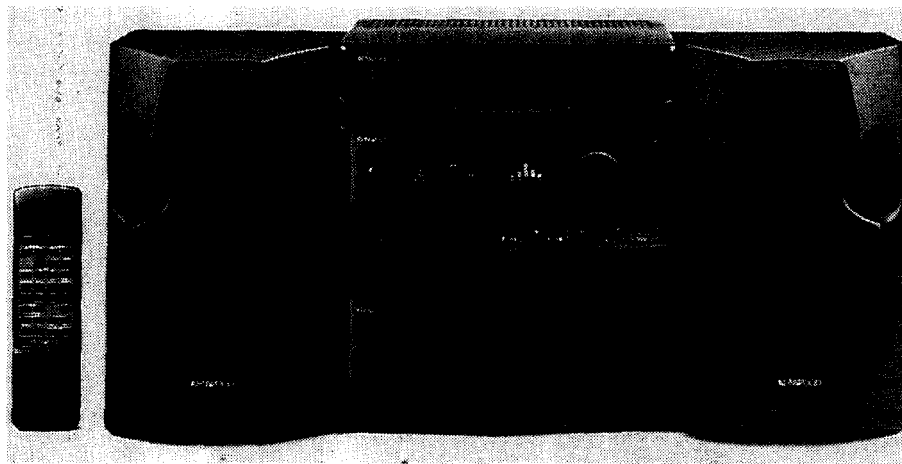
## Smallest six disc car CD changer

Sony has come up with what is claimed as the world's smallest car CD changes — so small it will fit in the glove box. It says the CDX-T60 is set to revolutionise the car CD market, by abolishing the traditional boot mounted CD stackers and replacing them with a compact and convenient piece of car audio equipment.



## Home THX audio system from Jamo

In the beginning of 1994, Danish loudspeaker manufacturer Jamo A/S obtained a Home THX Audio System licence from Lucasfilm Ltd. Now Jamo has announced its first Home THX Audio System.

The Home THX standard lays down a number of highly detailed and stringent specifications regarding frequency response, dynamic range and dispersion pattern to ensure that the sound from a Home THX Audio System comes as close as possible to the sound heard by the film makers in their studios.

Like most other manufacturers of Home THX certified left, centre and right front loudspeakers, Jamo has employed a vertical array design in order to meet the dispersion pattern criteria of Lucasfilm Ltd. But here the similarity ends.

For the vital front loudspeakers, Jamo has developed a special combination of two 5" woofers, two 3" midrange units with polypropylene cones, plus a 1" textile dome tweeter. These units and the



computer optimised crossover network deliver a linear and extended frequency response that is also suitable for ordinary stereo sound reproduction.

The subwoofer features a 12" Peerless driver from Denmark with a front firing bass reflex port for easier room placement. To ensure optimum sound localisation, really thunderous bass, and meet the THX specifications, the use of two subwoofers is necessary.

Jamo's left and right surround loudspeakers for the Home THX Audio System are designed as dual two way

dipoles, each featuring two 4" polypropylene cone woofers and two 1" textile dome tweeters. In spite of the compact dimensions of the enclosures, these surround loudspeakers deliver a linear sound pressure level all the way down to 125Hz. Retailing below \$8000, the system is said to be very competitive in the market place.

Further information is available by circling 272 on the reader service card or by contacting Scan Audio, of 52 Crown Street, Richmond 3121; phone (03) 429 2199.



Measuring only 225mm by 158mm, the CDX-T60 is small enough to fit neatly under front car seats or in the consoles or glove boxes of most vehicles.

The system features a 110 Disc Custom File memory, which allows the user to apply an eight-digit character name to their CDs for easy identification. The appropriate name of the disc will then automatically appear on the head unit. This means less time fiddling with controls and more time spent concentrating on the road.

The CDX-T60 has been designed to interact with all other Sony car audio equipment with CD control capability. Other features include a 1-bit D/A converter and eight times oversampling digital filter. A five-step angle adjustment allows for vertical, horizontal, suspended and inclined installation.

The CDX-T60 has a suggested retail price of \$849.

### SlimVision camcorder has 10cm LCD monitor

Panasonic's New SlimVision NV-V10A camcorder has a 10cm (4") colour LCD monitor for video shooting and viewing recorded scenes with the recorded sound. The LCD is claimed to be 56% larger than any other camcorder model on the market.

The V10 also has a conventional black and white viewfinder for users who prefer this more conventional filming method but prefer to watch the scenes filmed back on the LCD colour screen.

Despite the inclusion of the colour screen, the V10 is a slim and compact unit which is easily held in one hand.

The screen swings out from the left side for easy viewing during shooting and playback and folds neatly away when not required. It is also ideal for extreme low angle or overhead shots, because it can be turned upwards and downwards for a total of 180°. The LCD screen has a special non-glare, silica particle surface coating making it fingerprint resistant and stain proof. The surface coating also greatly reduces glare from strong light sources, making it simple to view in outdoor situations.

The V10 also comes equipped with a wide angle lens, combined with variable speed 10X power zoom. The wide angle setting corresponds to a 35mm wide angle lens of a standard SLR (Single Lens Reflex) photo camera.

Excellent indoor shooting is possible with the low light setting, which can film in lighting as low as 0.6 lux. The camera can also be set on full Auto, Manual, Sports or Portrait for special

filming situations. The Panasonic NV-V10A video camera is available from leading electrical retailers for an RRP of \$2399.

### Samsung releases 'World Best' TV

Samsung Electronics has launched its 'World Best' colour TV, a 68cm model selling for around \$2800. Featuring what is claimed to be the world's flattest screen, best reception and greatest built in surround sound system, World Best is the most advanced set Samsung has released into the Australian market. The ultra-flat CRT (2.5R) used in the set is claimed to produce a most realistic picture and to reduce picture distortion and eyestrain. The set also offers a two tuner Picture in Picture feature, which allows watching two shows at once - one on the main screen and the other on a choice of four sub-screens.

Another feature of the set is described as a Low Noise Amplifier — 'the first in the world', which is said to ensure high quality pictures and sound, even in a weak signal area.

For spacious sound, Samsung has used a Twin Turbo Double Woofer speaker system with six speakers. And for sound to suit the occasion, the set's digital surround sound system provides a choice of concert, stadium or mono mode depending on the program and the atmosphere it creates.

World Best comes with a three year warranty, free installation to an existing aerial and person-to-person instruction with an optional television check-up in the last year of warranty.




### Compact speakers from Yamaha

In the S15 and S55 Compact Speaker Systems, Yamaha claims to have combined the best in compact speaker performance, high power handling, design and affordability. The mount anywhere speakers are ideal for a wide range of around the home applications, as well as commercial installations.

Both models feature a two way design for clean, accurate sound over a wide frequency range — up to 40kHz in the high end, where reproduction of upper harmonic components is critical to natural musical performance. Yamaha's original Waveguide Horn design further improves high frequency performance and dispersion by generating a virtually ideal spherical wavefront.

Although small, these advance speaker systems handle a surprising amount of power and possess a very efficient design. The S15, which is available in both black and white finishes, is comfortable with up to 80W continuous power output, and has a recommended retail price of \$399. Its sensitivity is rated at 88dB/W/m. The S55, which comes in black finish, retails for \$699 and will handle 140W.

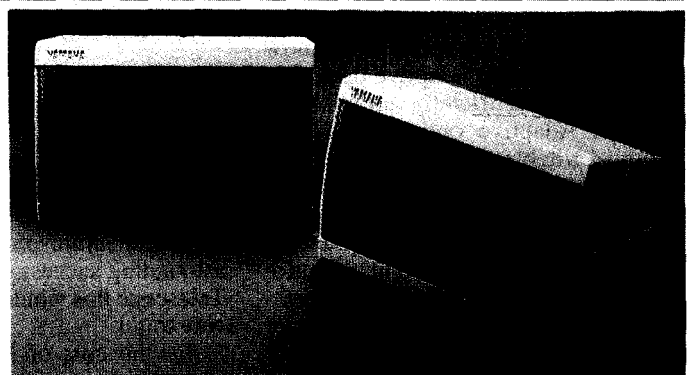Their efficiency is around 90dB/W/m, which means a big sound from a compact box. Additionally, with the escalating demand for home theatre, the S55 speakers feature full mag-



netic shielding, so they can be used in close proximity to TV sets without picture distortion.

Free angle wall or ceiling mount brackets let you set the speakers at any angle for optimum sound and coverage. Stand mounting is also possible, meaning that temporary or permanent installation can be easily accomplished in any listening environment.

For further information circle 273 on the reader service coupon or contact Consumer Electronics Division, Yamaha Music Australia, on (03) 9699 2388 or 1800 805 413. ♦

## ***Adaptive optics at the Anglo-Australian Telescope:***

# **UNTWINKLING THE STARS...**

Scientists working at the Anglo-Australian Telescope at Siding Springs in northern NSW and at Sydney University have developed 'adaptive optics' systems capable of correcting for the optical distortion introduced by the Earth's atmosphere. Already in operation is a 'tip-tilt' mirror system to stabilise the image position, while a 'rubber mirror' system to sharpen the images is to follow

by **GEOFF McNAMARA**

Twinkle twinkle, little star  
How I wonder what you are...


To most people, these famous lines are the beginning of a children's poem. To the astronomer, they're a lament of how difficult it is to study the Universe from Earth. While astronomers indeed wonder about the distant stars and galaxies, the twinkling mentioned in the poem blurs their view.

Stars twinkle in the night sky because their light is distorted, or blurred, by the Earth's atmosphere. While the stars look sharp and bright to the naked eye, to modern astronomers using state-of-the-art telescopes it's like standing on the edge of a swimming pool trying to read a copy of *Electronics Australia* at the bottom of the water. You can make out the big headline letters, but the really interesting stuff is just plain blurry.

After centuries of having to wait for those special nights when the air is really steady — or more realistically simply putting up with whatever clear night they get — astronomers are now experimenting with 'adaptive optics' in an attempt at artificially untwinkling the stars. Adaptive optics involves a system of tiltable and deformable mirrors that counteract the effects of the Earth's atmosphere.

One such adaptive optics system is being developed for the Anglo-Australian Telescope (AAT) in northern New South Wales, by a team of scientists and technicians from the Anglo-Australian Observatory and Sydney University.

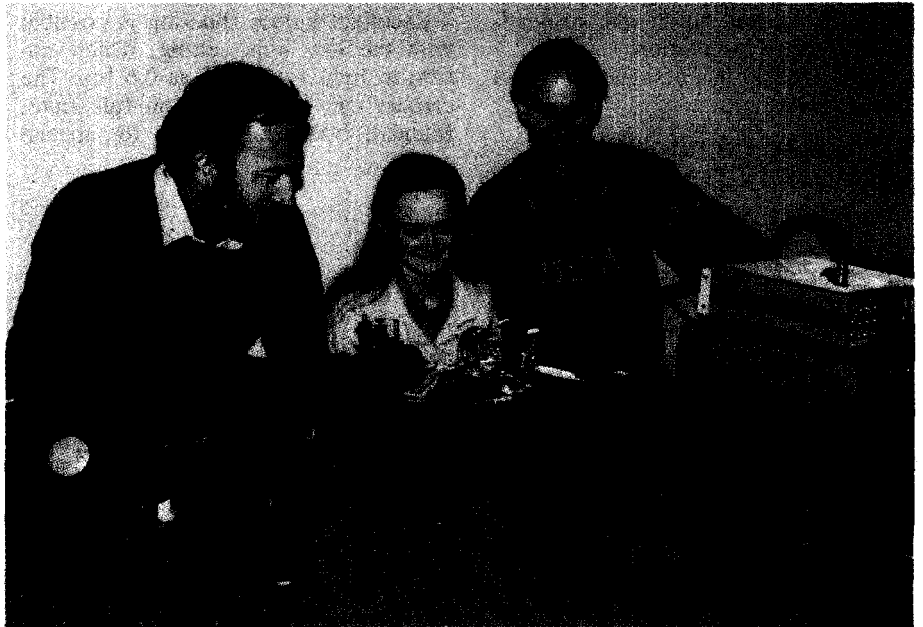As well as blurring a star's image, the atmosphere moves it around in an unpredictable manner. This random motion causes the image to dance around in the field of view of the telescope. Like a nervous bartender trying to fill a stationary glass, some of the light inevitably spills outside the aperture of any instrument attached to the telescope. With the



***Researchers John O'Byrne, Julia Bryant and Pal Fekete (left to right) examining an experimental adaptive optics set up at Sydney University.***

incredible faintness of some of the objects astronomers observe, every photon counts!

The ideal solution is to send telescopes into space, well above Earth's turbulent atmosphere, and with the astounding success of the Hubble Space Telescope this would definitely seem the way to go.

But the cost of building a telescope like Hubble, putting it in orbit and maintaining it, are enormous. Even if the funds to build more of these orbiting observatories could be found, astronomers like to swap and change the instruments attached to their telescopes on a regular, sometimes nightly basis. This is something that just can't be done with space-based telescopes like Hubble, which have a set compliment of instruments that can only be changed

during major servicing missions, timed years apart.

So, stranded on the ground, astronomers came up with adaptive optics. The idea was first proposed over 40 years ago, but the technology to realise the idea has only recently become available. While the new generation of large telescopes is being fitted with adaptive optics systems to maximise their performance, several existing instruments are being retro-fitted. Such is the case with the 3.9 metre Anglo-Australian Telescope.

By today's standards, the AAT is in an odd place. The largest telescope in Australia, and arguably one of the finest and most efficient in the world, the AAT sits on what passes for a high peak in Australia: the 1200-metre Siding Spring Mountain in northern New South Wales.

Modern telescopes of the AAT's calibre are built on much higher mountains, well above most of the Earth's atmosphere. For example, the telescopes on Mauna Kea in Hawaii peer at the Universe from a height of 4205 metres above the surrounding ocean. So, while Siding Spring is one of the darkest sites in the world, it's blanketed by much of the Earth's atmosphere. The result is that on some nights the atmospheric stability, or 'seeing' as astronomers call it, is less than ideal.


Despite this handicap, the AAT is famous for the high accuracy of its optics, and the efficiency and cleverness of the staff and visiting astronomers who work there. Continuing in this tradition, the AAO and Sydney University scientists have developed an adaptive optics system for the AAT that will further increase its already world-renowned capabilities.

Leading the project is John O'Byrne, a physics lecturer at Sydney University, who became interested in adaptive optics four years ago. At first, he says, he simply had "an interest in playing the game". But an Australian Research Council grant of \$170,000 in 1994, and a second grant of \$330,000 a year later, enabled O'Byrne to assemble both the equipment and the people to do some serious work in the field.


He had two objectives in mind: "Produce a system that would enhance the observing efficiency of the AAT, and explore how effective adaptive optics was going to be at the AAT site."

### How it's done

So how *do* you untwinkle the stars?

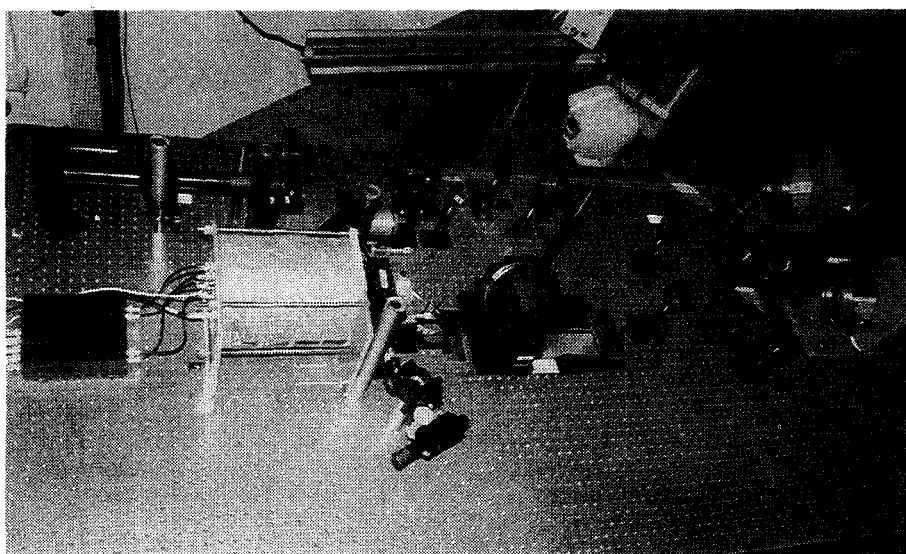

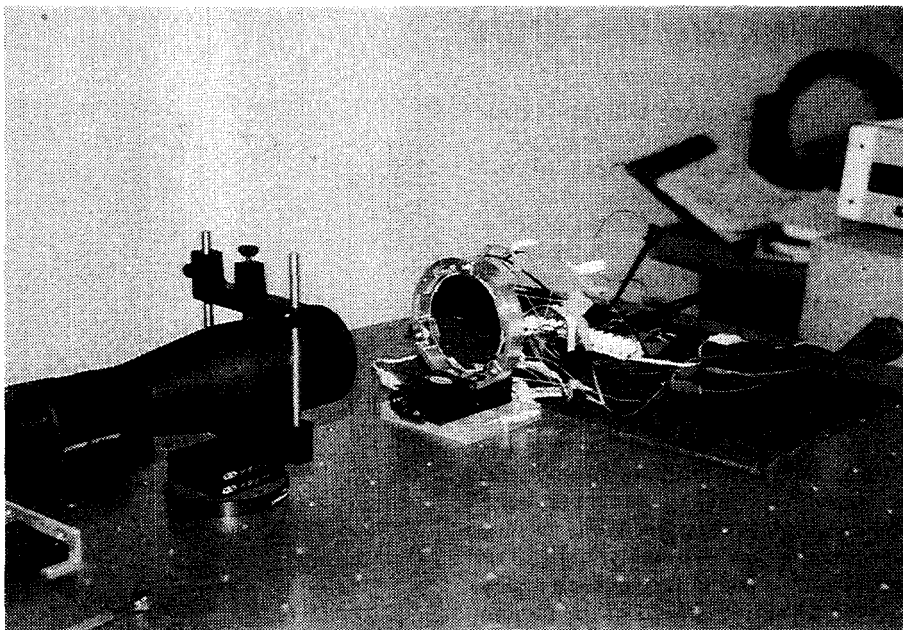**The 'tip/tilt' image centring setup on the test bench at the Anglo-Australian Telescope Facility at Siding Springs. The large silver object at left is the quad sensor assembly.**



**A close up view of the 'rubber mirror' set up, on the optical test bench at Sydney University.**

The principle behind adaptive optics is straightforward, even if the actual techniques aren't.

A special mirror called a beam splitter intersects the beam of light produced by the telescope. Some of the light is sent to sensors that measure the location and amount of distortion in the image, while the remainder goes on to the science instrument. Before the light encounters the sensors, it's manipulated by special mirrors that correct for the effects of the atmosphere.

One of these special mirrors is called a 'tip-tilt' mirror. Its purpose is to re-centre an image which has been shifted by

the atmosphere. As the image 'zigs', the mirror 'zags' and keeps the image in the middle of the field of view — ensuring all of the light makes it into the instrument. The shifting of the image is by far the more important factor to be corrected by adaptive optics.

In order to detect the location of the image in the field of view, the beam from the telescope is divided into four by a series of prisms called a 'pyramid'. The light from each of the four quadrants is focussed onto one of four photomultiplier tubes, which count the number of photons in each of the quadrants.

If the image isn't perfectly centred on the field of view, more light will be detected by one or more of the photomultiplier tubes. A computer measures this discrepancy and commands the tip-tilt mirror to redirect the light more evenly onto each tube.

"Essentially what the computer wants to do is even up the number of photon counts in each quadrant", said Julia Bryant, a post-graduate student who joined O'Byrne's project two years ago. "The mirror is mounted on four piezoelectric 'pistons'. By varying the voltage to the pistons, the mirror is tilted to redirect the beam."

The use of a tip-tilt mirror offers astronomers an added bonus. "The tip-tilt mirror nominally corrects for seeing, but it also corrects for telescope pointing", according to Bryant. "Even though we're using a telescope like the AAT (which is renowned for its pointing accuracy), there are minute drifts in positioning throughout an observing

# Untwinkling the Stars

run. The tip-tilt mirror will correct for that as well."

To counteract the blurring of the image, adaptive optics uses a deformable mirror, sometimes called a 'rubber mirror'. Unlike ordinary astronomical mirrors, deformable mirrors flex and bend in discrete places on their surfaces.

You can make a crude deformable mirror from any shiny, flexible material such as aluminium foil. By gently bending the foil, you can create a distorted image of everything around you. In adaptive optics, however, the demands on the accuracy of the surface deformation are extremely high. The rubber mirror has to flex in such a way that the distorting effects of the atmosphere are counteracted precisely, so a sharply focussed and distortion-free image is produced.

The rubber mirror is made from two wafers of piezoelectric material, that sandwich a layer of electrodes. The computer varies the voltage applied to each electrode, which in turn flexes the segment of piezoelectric mirror directly above it. The end result is that whatever the atmosphere does to the image, the rubber mirror does the reverse.

The computer decides which segment of the mirror is to be distorted, and by how much, based on the amount of dis-



Another view of the 'tip/tilt' optical assembly at Siding Springs. The two blue objects are the off-axis paraboloid mirrors.


tortion of the image. This distortion is once again measured by counting the number of photons in each segment. The light from the telescope is subdivided by an array of tiny lenses that focus the light from discrete segments onto optical fibres.

The fibres carry the light to a collection of avalanche photodiodes, that once more play the photon-counting game. The computer analyses the intensity of the light coming from each segment and determines the distribution of photons. Once again, it's the computer's job to even up the score — something Bryant describes as a "computing nightmare, but it can be done."

The astonishing thing about adaptive optics, however, is the speed with which all this occurs. Even a casual glance at the night sky reveals just how quickly stars twinkle.

To keep up with the atmosphere, an adaptive optics system has to perform the necessary measurements, calculations and mirror adjustments a thousand times every second.

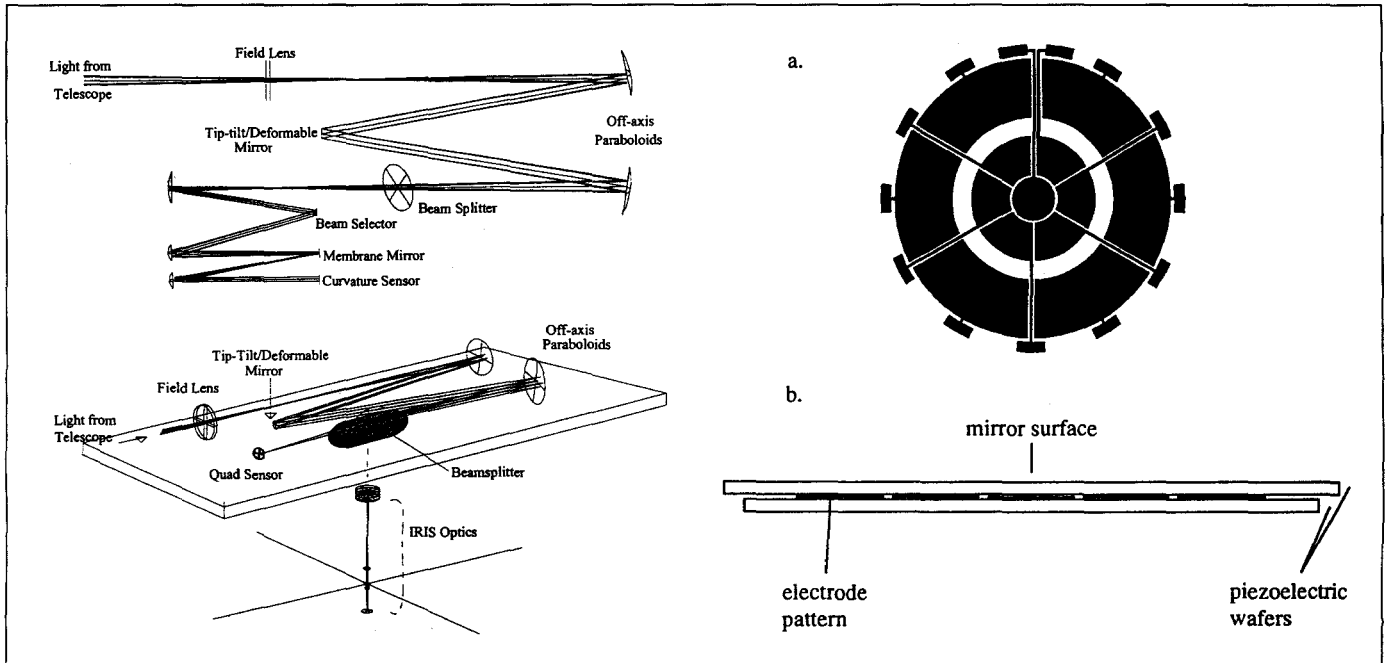To be able to do all this, however, an adaptive optics system needs a bright enough guide star in the field of view, to feed the sensor. "The problem with most systems is that they're attempting to produce a very high level of correction by using a sensor that's divided



The diagram at left shows the 'tip/tilt' adaptive optics assembly used for image centring, with the plan view at top and a perspective view below it. At right is shown the construction of the piezo-actuated 'rubber mirror' used to clean up the images themselves.

into a whole lot of little bits", explained O'Byrne. "But each little bit needs to be supplied with light. You've got a finite amount of light coming through the telescope (from the reference star), so the more ways you sub-divide it the fewer photons each segment ends up with. The result is that the sensitivity tends to be awful."

For a sensor on a 4-metre telescope you can achieve tremendous results by having hundreds of segments — if you can find a comparison star in the field of view that's bright enough to feed the sensor enough photons. Each segment in the sensor receives only a small portion of the total amount of light, "...about as much as you'd get out of a 10cm telescope", explained O'Byrne. "The rest of your telescope is feeding other bits of the sensor." On top of that, the system is making corrections a thousand times a second. "You rapidly run out of photons!" said O'Byrne.

The problem is worsened by a shortage of suitable reference stars. Even a casual glance at the night sky will show you there are fewer bright stars than faint ones. The same is true for telescopes like the AAT, which peer deeper into the night but have correspondingly smaller fields of view. The result is it's rare to have a bright enough reference star in the same field of view as the object you want to study.

### Make your own reference?

One solution to the problem is to make your own reference 'star'. By sending a laser down the business end of a telescope, the optics of the instrument work in reverse and project a beam of light into the sky.

The laser light reacts with the atmosphere to create an artificial star image, that the telescope can then monitor. Since the beam is travelling through the very stuff the system is designed to correct for — air — it's distorted in exactly the same way as the incoming light from the distant stars. By using this method, the adaptive optics system basically has a reference star wherever it looks.

There are problems with this, however, such as the fact that such a laser can have serious detrimental effects on anyone looking out of a plane window, should it cross over the beam of the telescope. Then there are other astronomers using telescopes nearby — your artificial reference star is fine for you, but it's basically just another form of light pollution for your colleagues.

Faced with a shortage of bright guide stars, O'Byrne has decided to follow a different path to other adap-

tive optics projects. "We keep the number of segments low," he said. By using a rubber mirror with fewer segments, 13 in this case, more light can be analysed by the sensor.

While this means the correction for the blurring of the atmosphere may be less effective than a system with hundreds of segments, it leaves more light for each segment's sensor — allowing astronomers to use fainter reference stars. "That gives us much better coverage of the sky, simply because there are more faint stars to look at", said O'Byrne.

Eventually, the tip-tilt and deformable mirror requirements will be combined. By mounting the deformable mirror onto the four piezoelectric 'pistons', the scientists hope both processes can be handled at once — which cuts out one of the mirrors and so reduces loss of light.

So far, all adaptive optics systems, including the AAT's, are working in the infrared rather than the optical. The reason is simple: the demands placed on the system by infrared are much lower. "It would be great to be able to do good adaptive optics in the optical, but nobody is really claiming very much success in that respect at the moment", said O'Byrne. "We're all going for the infrared."

The beam splitter used by the system therefore has to be highly reflective at infrared wavelengths, but transparent to visible light. This means that most of the infrared collected by the telescope can be passed on to the tip-tilt/deformable mirror and then on to the science instrument, while the optical is siphoned off and sent to the sensors.

"For a long time, the AAT has been one of the largest telescopes in the world. That's now changing, with the new generation of 10 metre class telescopes", says O'Byrne. "If the AAT is going to survive as a front-line facility, it will have to carve itself an appropriate niche. One of the things it should be doing is improving efficiency by the use of adaptive optics."


The tip-tilt mirror phase of the adaptive optics system became operational in October 1995, while the deformable mirror will follow in 1996. When the system is operating it will sharpen the vision of an already superb optical instrument.

In closing, I would like to extend special thanks to John O'Byrne and Julia Bryant, for their assistance in preparing this article.

(Geoff McNamara is a freelance astronomy writer and Associate Editor for *Sky & Space magazine*.) ♦
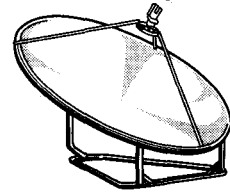
# YOU CAN NOW AFFORD YOUR OWN SATELLITE TV SYSTEM

For many years you have probably looked at satellite TV systems and thought "one day"



Your own K-band system from only:

**\$995**

### HERE'S WHAT YOU GET:

- Prime focus dish configured to your location.
- Super low noise LNB/feedhorn.
- 25m low loss coaxial cable.
- DYNALINK 50 channel stereo satellite receiver, with remote control. Pre-programmed to Optus frequencies.
- Pointing co-ordinates for your location.

### BEWARE OF IMITATORS

**Direct Importer: AV-COMM PTY. LTD.**

PO BOX 225, Balgowlah NSW 2093  
Tel: (02) 9949 7417 Fax: (02) 9949 7095

Ask about our regular newsletters and Customer BBS. Send coupon for your free info pack, listing all items and prices.

YES GARRY, please send me more information on K-band satellite systems.

Name: \_\_\_\_\_

Address: \_\_\_\_\_

P'code: \_\_\_\_\_

Phone: \_\_\_\_\_

ACN 002 174 478

READER INFO NO. 5

## ***Australian achievements in optical communications:***

# **IMPRESSIVE RESULTS BY UNSW OPTO RESEARCHERS**

Researchers at the University of NSW's School of Electrical Engineering, led by Professor Pak Chu (Head of Optical Communications), have achieved impressive results in three key areas of relevance to the future of optical communications direct to the home and office. The developments include a low-cost optical waveguide on a glass wafer, an on-chip mirror to swing a light stream 90° into a photodiode, and a low cost optical demultiplexer.

Researchers in NSW's School of Electrical Engineering have devised a simple method of making an optical waveguide on a glass wafer.

An optical waveguide is a device which guides a beam of light along a defined path, similar to the way a wire guides an electrical current. Inexpensive optical waveguides will be essential to the economics of delivering communications carried by optical fibre to the home.

Michael Bazylenko, a PhD student working with Professor Pak Chu, and Dr Mark Gross, a postdoctoral researcher in the school, have shown that they can make an optical waveguide by focusing an ultraviolet laser beam onto a wafer of silica (pure glass) that had been doped with a small amount of germanium, a semiconductor element similar to silicon.

The new waveguide thus becomes another device by which photons are steadily supplanting electrons as the means for transmitting and processing information.

It also becomes the latest of several potentially valuable devices that have been developed by electrical engineers at UNSW working with the Optical Fibre Technology centre at the University of Sydney, the Optical Sciences Centres at the Australian National University and Siemens Ltd.

All are members of the Australian Photonics Cooperative Research Centre.

Professor Chu said that the new process was less expensive than previous methods that required the silica wafers to be impregnated with hydrogen for up to two weeks, before they could be treated with a process that was less accurate than the new method.

"With our process," said Professor



***Professor Pak Chu (in front) with Ruo Fei Peng, a Laboratory Assistant working for UNSW's Optical Communication Group, shown keeping an eye on the production of a twin core optical fibre. (Photo courtesy Uniken.)***

Chu, "we can construct a waveguide that is only eight microns (millionths of a metre) wide, and about 12 microns deep. This means a beam of light or a stream of photons, whatever you wish to call it, can be directed very accurately into optical or electronic devices."

Another advantage of the new process is that parts of the waveguide can be erased by running the laser over the parts of the wafer that need to be altered.


Among the many possible applications of the new waveguide could be a simple-to-record device, similar to a CD-ROM but able to be rewritten.

Professor Chu said that his group was not yet certain why their process achieved the results it did. Part of the process had to do with placing the 5cm

doped silica wafers under a compressive stress while they were illuminated with the UV laser.

'Doping' is a term for implanting small amounts of a foreign material into a host material, to alter its behaviour. The host material is usually a semiconductor, often silicon, and doping induces changes in the semiconductor that can be exploited by makers of computer chips and photovoltaic cells.

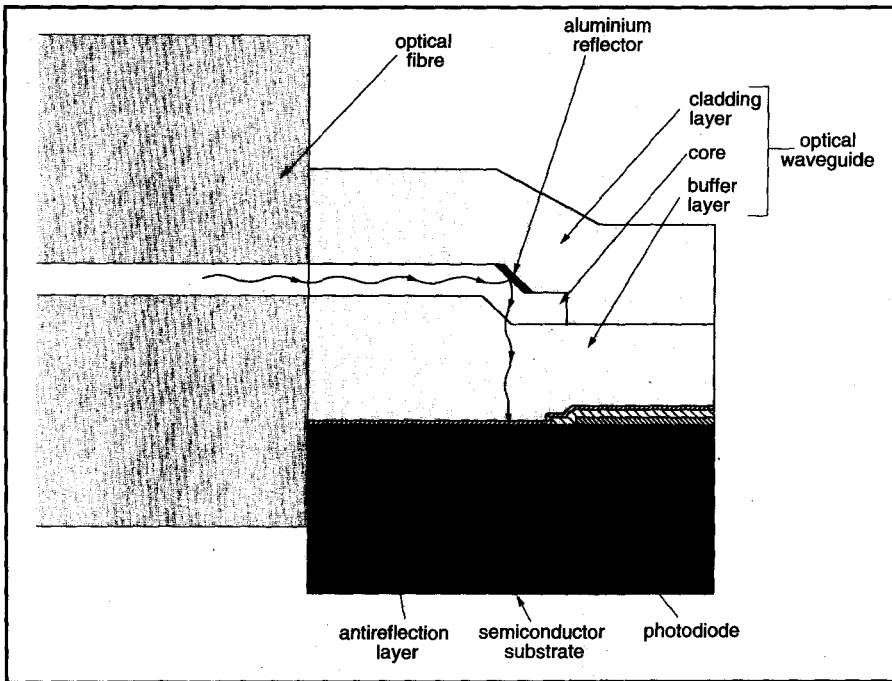Researchers are now using doping techniques to create changes in silica and other materials that influence the behaviour of light in the materials. In this case, a process known as plasma enhanced chemical vapour deposition (PECVD) is used to dope the silica.



**A diagram of the on-chip mirror developed by the UNSW researchers, to reflect light through 90° for coupling into a photodiode. (Courtesy Optical Communications Group, UNSW.)**

Professor Chu said that two advantages of the new process were that it induced a change in the refractive index of the silica almost three times as large as had been achieved by other processes, and that the change was negative whereas other processes produced a positive charge. The negative change — reduction of the speed of light in the waveguide — could be

expected to lead to other novel approaches, he said.

### **A built-in mirror**

A device to reflect light signals from an optical fibre through 90°, so they can enter a photodiode, has also been developed by the above researchers and Erik Gauja, a professional officer in the School of Electrical Engineering.

The advantage of the UNSW device is that it can be made economically at the relatively low temperature of 300°C. Optical devices have been made at temperatures of 1000 - 1200°C and these prevented the integration of electronic components into the optical chip. The low temperature technique developed by the UNSW group is a crucial step for the manufacture of a monolithic opto-electronic chip required in future communication systems.

Again, a PECVD technique is used to deposit a highly reflective layer of aluminium at 45° to the light carrying core of the optical fibre, after a special technique has been used to produce a flat reflecting surface at the required 45° angle.

The device has been tested and as it can be made using only standard semiconductor fabrication techniques, it is amenable to low cost mass production.

The projection was supported by the ARC and ATERB, the Australian Telecommunications and Electronics Research Board.


### **Inexpensive demultiplexer**

The third device produced in UNSW's School of Electrical Engineering could become an essential item in every home or office linked to optical fibre for phone, TV and other data services coming down the information superhighway.

The device is a demultiplexer, that will be necessary to separate the two optical signals that have been selected to bring all the above information to consumers.


Professor Chu explained that the device, which is only one centimetre long containing two identical cores, was attached to the optical fibre carrying different signals at 1.3 and 1.55 micron wavelengths. By a quirk of physics and much hard labour by the research group, one of the incoming signals has been persuaded to jump across from one core to the other. From this point, both optical fibres unload their now separated signals into two photodetectors, which convert the optical signal into an electrical signal that is then processed in the usual way by the telephone, television or other receiver.

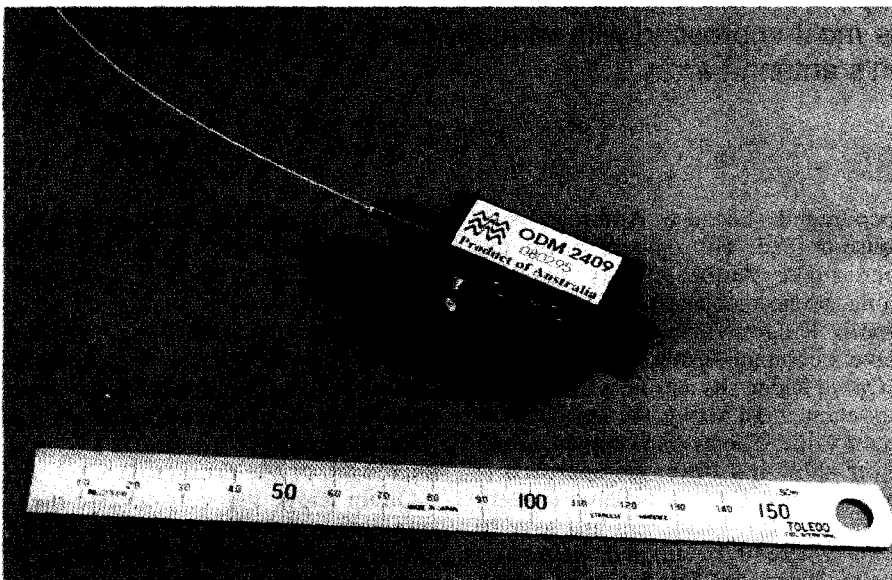"The optical isolation between these two channels is larger than 30 decibels optical, or 60dB electrical. No other demultiplexer can achieve such good separation but, more importantly, the cost of this device is very low because of the unique qualities of the twin core



**This demultiplexer, pictured with optical fibre attached, could become the link between the home and the optical communications highway. Inside the 5cm package only about 1cm of twin core optical fibre is needed to separate two streams of light signals. (Photo courtesy Optical Communications Group, NSW).**

*Continued on page 38*

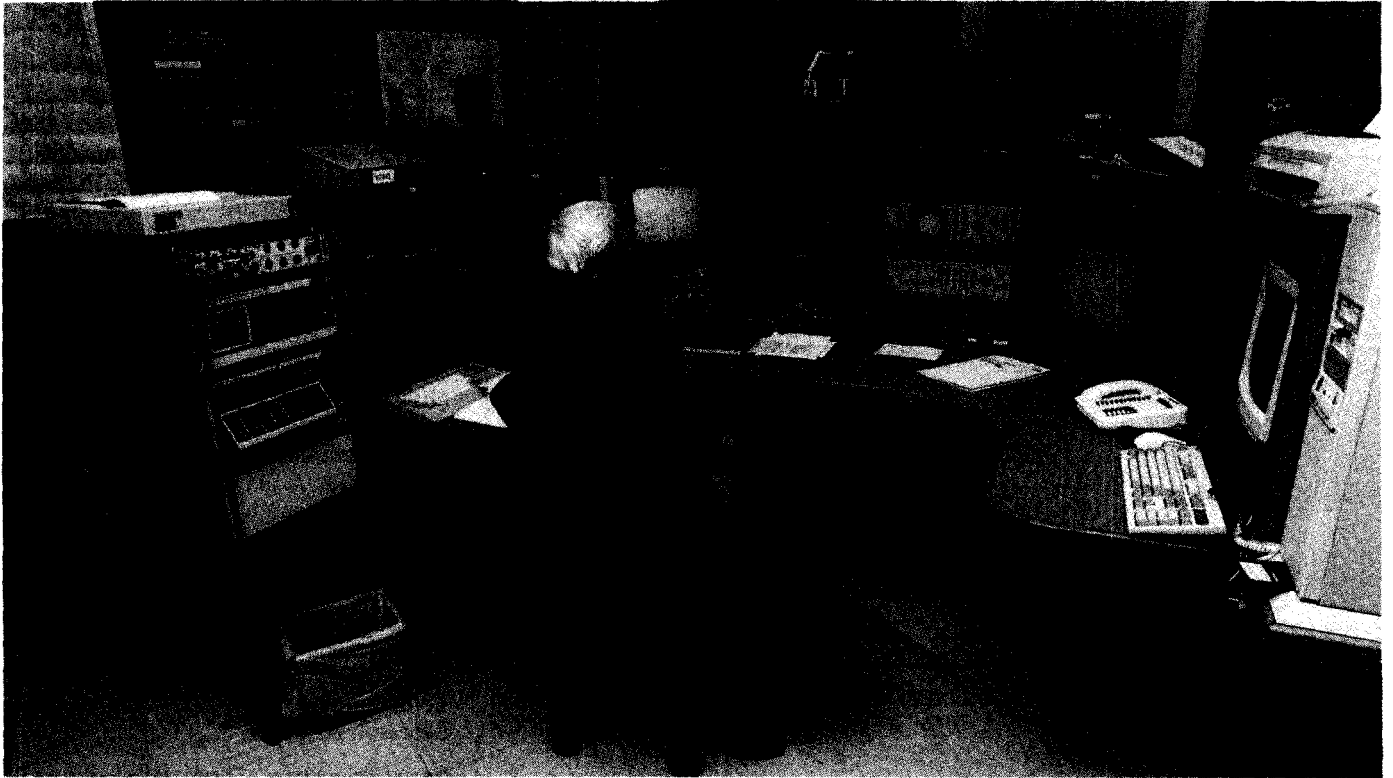

# QUOIN RIDGE: SMA'S BIG EARS IN TASMANIA

Just before he left for the USA, Tom Moffat paid a visit to a part of Tasmania that few people have had the opportunity to visit — the Spectrum Management Authority's very important HF monitoring station at Quoin Ridge. He was most impressed with what he found, and especially with the reception possible using the station's antenna array...

by TOM MOFFAT

How would you like to have a radio receiving site so quiet that the only allowable approach to it would be on horseback — cars would be banned. Well, that's the first impression you get when you arrive at Quoin Ridge, the Spectrum Management Authority's super-quiet monitoring station near Hobart. Standing there in the parking bay is a horse. But he's not really for transport; a small jeep is parked nearby for that purpose.

The horse's name is Ambrose, and he's pretty good mates with Dave Thorne, Officer in Charge at Quoin Ridge. Ambrose doesn't just stop at the door; given half a chance he kicks the screen door open and steps inside. This behaviour isn't really

encouraged, because Ambrose isn't house-trained. His owners down the road make Ambrose stay outside, alone. So he spends a lot of his time at Quoin Ridge, for warmth and for Dave's companionship.

Quoin Ridge sits astride a flat-topped mountain, high above the surrounding countryside. The average person would never know it's there; the approach is by a dirt track off an isolated country lane. There's no sign; you just have to know where it is. Invited visitors to Quoin Ridge are faxed a map which reveals all, but for someone to just stumble upon the station would be very unlikely. Should that happen there are gates and early warning systems all along the road.

Given reasonable conditions, the receiving equipment at Quoin Ridge can hear just about any HF signal radiated anywhere in the world, and get a pretty good idea where it is coming from and how strong it is. The site radio noise level is  $-120\text{dBm}$ , so it can hear signals that would only be a dream in a suburban setting. ( $-120\text{dBm}$  is .001 of a microwatt, or one nanowatt!)

Quoin Ridge has very precise measurement capability, making it the only monitoring station in Australia to meet the strict ITU (International Telecommunications Union) standards. The number of similar stations in the world can be counted on the fingers on one hand.

Quoin Ridge has two primary pur-



poses: tracking down interfering signals, and making very precise frequency and strength measurements on selected signals. Although it's mainly concerned with HF signals, the station can receive on any frequency between 3kHz and 1.5GHz. All modes are covered, from AM and FM right down to decoding individual channels on a multi-channel radioteletype system. So *nothing* can escape its attention...

Its radio-quiet status is what makes Quoin Ridge so important. Being high on a mountain (442 metres), the station is well isolated from ignition noise. The nearest above-ground power line is over 1km away; power is brought to the station via a shielded underground conduit. Since the site is flat, there is plenty of space — over 40 hectares — to install the gigantic antenna systems.

## Two main antennas

For HF receiving there are two main antennas. The biggest is centred on a 32 metre tower. Eighteen wires radiate out 150 metres in all directions, to three-metre towers at their far ends. Each pair of these wires forms a vee antenna, making nine in all spaced 40° apart. Each wire is terminated at the far end with a 470 ohm resistor, and thence to an underground return wire back to the main tower.

Each pair of vee-wires connects to a



470 ohm balanced winding of a ferrite transformer. The other winding, 50 ohms unbalanced, goes to a piece of low-loss 50 ohm coax running back to the station. So the output of the whole antenna system is nine runs of coax, each representing a different direction of reception.

Back at the station, each of the nine vees feeds into a wideband distribution amplifier with 10 outputs, so each 'direction' can be sent off to 10 different receivers, simultaneously if need be, with total isolation between the receivers. The distribution amps are made of VHF power transistors of the type used in mobile radio transceivers; the idea is to provide extreme dynamic range, so a received signal can produce as much as 20 volts at the antenna terminals without causing intermodulation with other signals.

Each receiving location thus has a feed from each of the nine vee antennas, and the operator can select which direction to receive from by turning a large 10-position switch marked in degrees — 10, 50, 90, etc. The array of vee's has a frequency range of 100kHz to 30MHz.

The other HF receiving antenna is basically a large upside-down discone, supported by four telephone poles and a network of wires broken apart with strain insulators. This antenna has been built to a very stringent ITU standard, so its sensitivity is known and carefully calibrated.

The cone can thus be used for direct

**Left:** The 'far end' of one leg of the vee array. The central tower is 150m away. **Right:** The 'upside down' discone, which forms the ITU FSI array.



**Quoin Ridge OIC Dave Thorne shows a spectrum analyser display of a 16 channel radio teletype signal. All channels are idle except for the one in the middle, which looks 'furry' with modulation.**

field-strength measurements; if a spectrum analyser, for instance, shows something at a level of -130dB, then that's what the true incoming level is.

The output of the cone antenna goes to another wideband distribution amplifier, and it's distributed throughout the Quoin Ridge station just like the nine HF vee's. The cone comes up as position 10 on each antenna selector switch.

## HF transmitters

There is a further cone-type antenna, a Collins Low Angle multi-cone array, which is used primarily for transmitting in the range of 2-25MHz. The station has


two all-mode HF transmitters of 200 and 1000 watts, which can be used for regulatory purposes such as asking a suspected unlicensed station to identify itself. The transmitters are also useful in distress or disaster situations.

Although officially an HF station, Quoin Ridge also has VHF/UHF capabilities covering such services as marine, police, CB radio, and small boating. This is for southern Tasmanian use only, extending out to 100km or so.


The receivers within the Quoin Ridge station are enough to make any short-wave listener drool with envy. The one most used at the moment is an Icom R-9000, considered the king of all communications receivers. It, however, is


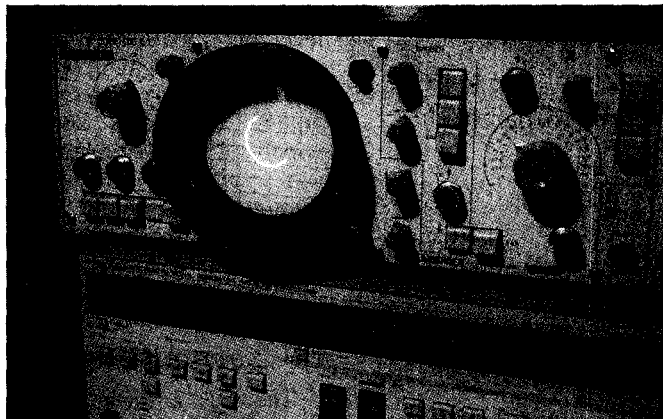
## Quoin Ridge: SMA's Big Ears in Tasmania



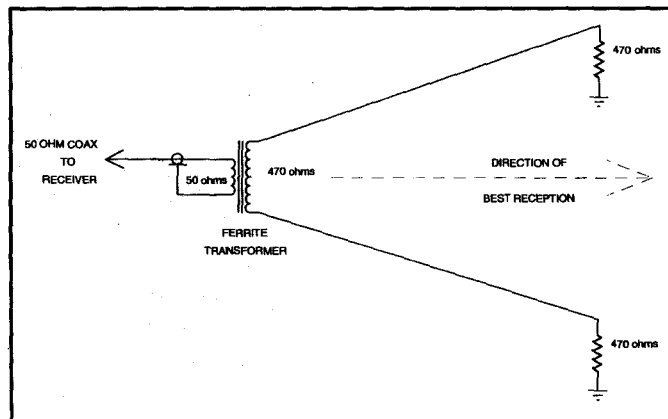**Above: Frequency measurement display of the VNG 2500kHz transmitter. The half circle display on the CRO is stationary, so VNG is on frequency. Right: How the 'Vee' antennas are used.**



'under evaluation' and will probably be replaced with something else equally flash at a later date. The SMA is swapping them around, to try to find the 'best' communications receiver available in Australia.

Just above the R-9000 sits an Icom R-71A, the same one I use for my own development work. They're joined in the main console by a rather yummy-looking Racal model. There is a secondary operating position in another room, also serviced with the 10 antenna feeds, and still more antennas go into a lab area.

### Tracking 'em down

The day I visited Quoin Ridge there was a big Australia-wide operation under way to find the source of some interference affecting a world-wide aviation channel on 13.306MHz. This

channel is used extensively by air traffic controllers in Perth, to communicate with aircraft flying to Singapore, Cocos Island and other parts of Asia. The channel was getting so messed up that the air traffic controllers finally issued a 'Critical Service Failure Notification' and the SMA swung into action.

Every hour on the hour, a woman's voice came up on 13.306MHz SSB and said, in Mandarin, "THIS IS JUHAI. THIS IS JUHAI". And a few moments later, again in Mandarin, "NOTHING, GOODBYE". This occurred like clockwork, and later increased to every half-hour. The response was always "nothing", never "something", and it sounded very much like a test of some service that might later expand its operation to obliterate 13.306MHz completely.


Australia operates an interesting

direction-finding network called Jackal. This consists of three 'blockhouse' stations at Perth, Brisbane and Darwin, in addition to Quoin Ridge. The blockhouses are simple concrete huts containing remotely-controlled direction finding equipment, working from 1-30MHz. Because of their three-point wide physical separation, the stations can do triangulation fixes near Australia with deadly accuracy (watch out drug runners!) and with excellent accuracy further afield.

The blockhouses are normally operated by SMA staff in their home cities, but is also possible to telephone the huts directly from Quoin Ridge to take control of them. Although Quoin Ridge coordinates interference searches, in the case of JUHAI, most of the work was done by SMA staff in Perth. It was they who organised bearings to the



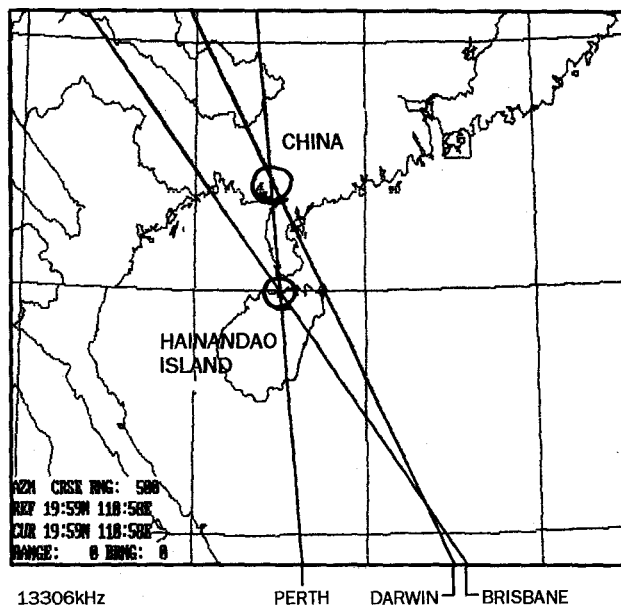**Left: Dave and Ambrose — best mates at Quoin Ridge. Right: Computer printout of the direction finding 'fix' on the 'Juhai' signals.**



JUHAI transmitters from all three stations and then faxed the results to Quoin Ridge, where a computer system is set up to use observed headings to pinpoint the interfering signal.

The JUHAI transmitter worked out at two locations. One was at the city of Haikou on the Chinese island of Hainandao. The other was on the Chinese mainland, about 200km north of Hainandao, near the city of Zhanjiang. Two location indications could have been due to several causes; perhaps there were actually two transmitters, or the one transmitter could be moving from one location to the other, or maybe there was just some screwy propagation.

Still, China was proved to be the culprit one way or the other. Once all the evidence is finalised, the SMA will write up a 'harmful interference complaint' and give it to the Chinese authorities. Dave Thorne says it's entirely possible the authorities themselves don't know about the JUHAI transmitter. They are members of the ITU, so he is confident China will cooperate to have the offending station removed.

## Frequency measurement


Quoin Ridge can measure the frequency of any signal it can hear, with the result based on a Rubidium frequency standard with an accuracy of 1 part in  $10^{12}$ . Frequency measurement over an HF path is difficult, however, because of the fading and phase changes that cause the observed frequency to jump around.

So digital methods are out, and analog methods are in. Quoin Ridge uses a simple oscilloscope coupled to the human eyeball to determine the frequency. The CRO is nothing more than an X-Y display, with a 1kHz sine wave applied to both the vertical and horizontal plates with a 90° phase shift between them. The result is a circle displayed on the screen, caused by the electron beam going round and round 1000 times a second.

To make a frequency measurement, an HF receiver is first tuned to the station in question. Then a signal generator, tuned 1kHz higher or lower, is mixed with the incoming signal to produce a 1kHz beat note. The audio thus developed is used to *intensity modulate* the oscilloscope's electron beam, such that peaks on the audio intensify the display and valleys on the audio cut the beam off. With the beam going round and round 1000 times a second, the display becomes a

half-circle, with one half intensified and the other half cut off.

Should there be some difference other than 1kHz between the incoming signal and the local signal generator, the whole oscilloscope display will rotate one way or another. The operator then adjusts the signal generator frequency to make the display stop spinning, and notes the signal generator's frequency less the 1kHz offset. Both the 1kHz tone going to the oscilloscope's deflection plates, and the signal generator output frequency, are locked

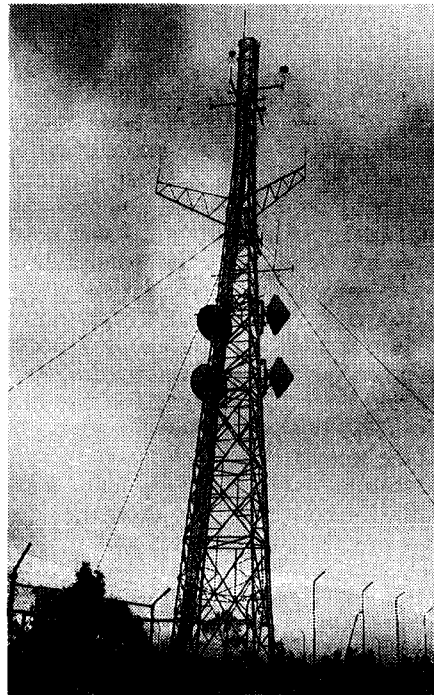

**VHF and UHF antennas at Quoin Ridge. The dishes are part of an Army microwave relay link.**

to the station's Rubidium frequency standard. So the measurement result is traceable to that standard as well.

This all sounds easy in theory, but in practice most HF signals are knocked around by phase delays and multipath propagation and their own modulation. The result is an oscilloscope display that gyrates wildly, and a certain amount of human interpretation is required to establish when the display actually stops spinning. That's why they have *people*, instead of machines, as frequency monitors.

The photo shows a frequency measurement being made on the Australian time and frequency station VNG on 2.5MHz. It was chosen because during the day its signal is solid as a rock in Hobart — almost ground-wave performance with no fading or phase changes at all. This was the only station that

would hold still long enough to get a good photograph. VNG staff will be pleased to know that they are correctly on frequency — 2500.00000kHz plus the 1.00000kHz offset.

## Valves rule!

That made you sit up and take notice, didn't it? But my visit to Quoin Ridge showed me something in practice that many of us old-timers have suspected for a long time. Maybe we're about to start some more squabbling in the Forum column...

After our 'official' business was finished, Dave Thorne took me into the lab — where sitting on the workbench was an elderly GEC receiver type BTR400K, a 1970 model built on a REAL chassis with REAL valves poking out all over it.

"Listen to this!", Dave said, and he twisted the tuning dial. Up popped a low frequency air navigation beacon identifying in morse code FLI — Flinders Island. "But you ain't seen nothing yet!", he said, and tuned it again. This time we got an airport at Sale in Victoria, and then Essendon, and then — Sydney! In the middle of the day, no less, on frequencies around 200kHz, and just about noise-free.

Admittedly that thumping big directional vee antenna had a lot to do with it. But then we went back to the main operating console and fired up the R-9000 receiver on the same frequencies. Yes, we heard the stations, but this time they were accompanied by various shrieks and whistles and buzzes, obviously caused by local broadcast stations.

In short, that old GEC boat-anchor KILLED the latest Icom in the intermod stakes...

That little demonstration led to a discussion of what Dave Thorne would really like to see as the main station receiver. A brand-new valve design, with tracked tuning in the front end, would be ideal. But if valves are a no-no, then perhaps something based on VHF power FET's as used in the antenna distribution amplifiers, as the front-end amplifier at least.

But is a 'modern' valve receiver impossible? They used to say that about hi-fi, didn't they. But now valve-based amplifiers are the latest thing, highly sought after by the audio elite.

Maybe, just maybe, someone like Icom or Yaesu or Kenwood could drag an old valve-receiver engineer and give him one more moment of glory. It would make a lot of people extremely happy, especially Dave Thorne! ♦

# ONLINE, BUT NOT ON YOUR OWN..

All of the media hype on the Internet has tended to distract attention away from commercial online information services, like the long-established CompuServe and Apple's new eWorld service. Here's a look at what's available on these services — which nowadays also provide links to both the Net and its GUI domain, the World Wide Web.

by **BARRIE SMITH**

If you're close to the point of screaming at the sight of another story on — wait for it — the Internet, relax. This one is about other online services.

Like many, I jumped into online communication with little more than a modem, a service provider account and a disk of comms shareware — most of which was useless.

Getting my Net connection up and running, I began to see what all the fuss was about. But, sook that I am, after getting my fingers wet with the UNIX commands, I soon developed a deep and brooding aversion to any form of command line instruction — DOS included. But that comes from many years of GUI (graphical user interface) navigation on the Mac.

Then I tried CompuServe, now a veteran of some 25 years. Soon after, Apple's eWorld service appeared, which I embraced with gusto. What with my Ozemail provider account, CompuServe and Apple's slice of online, I was now triply literate in online communication!

The weight of services now truly across my aching back, it was fortuitous that a sudden influx of writing commissions appeared on my desktop; I could now not only pay for the services, but finally use them for research on the stories.

Getting myself in deep with both, I soon found two things: there was much of use to me; and it was easily accessible.

But with CompuServe I discovered it

can be costly, unless you know where you are going. However, compared to swamping around on the Internet, digging into the commercial services for information turned out to be relatively quick, accurate and satisfying.

## CompuServe

This service is well developed and comprehensive. It is also very American in attitude and content — aside from a useful European slant, with some sites in French and German plus a UK component.


## Here's an overview:

News, sports and weather are served well, from such press agencies as Australian Associated Press, Reuters and UPI as well as the main English newspapers (excluding Murdoch's), plus German and French press agencies. Editable text from these sites can be downloaded with little fuss — provided you follow through with each service's proclaimed copyright policy.

An interesting site is the Bettmann photo archives, with an amazingly wide catalog of images, begun in 1933 and now totalling 17 million images — from cave paintings to current news shots. Small (roughly 100-200KB) files that will print to A5 size on a 300dpi printer, they are available for personal use only.

Another is Archive Photos, holding 20 million images of all varieties. Again, downloading of small image representations is allowed 'for personal use'. Like a shot of Claudia Schiffer in a black tee shirt?

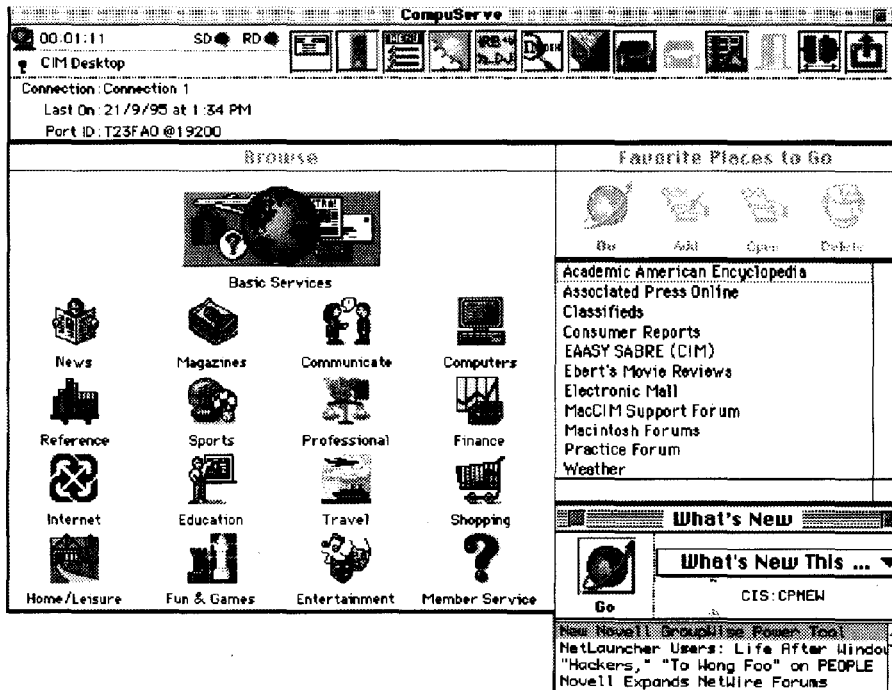Magazines in all forms get a heavy run: naturally computer titles feature (*PC Week*, *PC World*, etc), as well as *Fortune*, *Rolling Stone*, *New Yorker*, etc. Unless you keep exhaustive files of major world titles going back many years you will find, as I have, access to these publications useful in tracking



**CompuServe's main window which appears at log on. The service claims to have 29,000 Australian subscribers.**

down specific articles and their publication dates. The interactivity is an attractive feature, allowing subscribers to make direct input to a publication.

Computer vendors operate major support and information sites: Lotus, Novell, Microsoft, IBM and Apple are all there, as well as dozens of others. With the current cost of telephone help to sort out hardware and software problems, you can expect to see this area grow. Major US publisher Ziff-Davis operate six sites; one is in French, another in German, while still another can be accessed to download shareware for both PC and Mac enthusiasts.

If you really want to move around, an unusual location on the CompuServe 'network' is operated by Magellan Geographix. Here maps can be selected and downloaded. Your basic online charge covers you for downloads of 'Basic Maps' of any area on any of the seven continents. Fire up the mouse and you can download limited resolution GIF images — with the usual copyright restrictions.

If you feel the need for a higher quality, vector-based (in Postscript) graphic map, you may find what you want in the site's MGDigital Atlas. The cost can be anywhere between US\$50 - 400. Cheap they are not, but the advantage is that the map image files are editable and in layers.

Movies feature heavily on CompuServe. Less than four hours after the 1995 Oscar awards night concluded,

The screenshot shows a CompuServe terminal window with a title bar 'CompuServe' and a system clock '00:09:21'. The window title is 'Bettmann Archive Forum'. Below the title bar, there are several icons and a menu bar with options: Info, Abstract, Mark, View, Retrieve, Delete. The main content area displays a table of files with columns for Filename, Title, Submitted, Size, and Accesses.

Filename	Title	Submitted	Size	Accesses
TVRITC.GIF	Christina Riccio in "Seven Year Itch"	3/6/95	156.5K	522
ENESB2.GIF	Evelyn Nesbit	21/4/95	157.5K	67
ENESB1.GIF	Evelyn Nesbit	21/4/95	122.5K	158
DCASS2.GIF	David Cassidy & Susan Dey	21/4/95	157K	43
DCASS1.GIF	Teen Idol David Cassidy	21/4/95	163K	33
CAPTEN.GIF	Captain & Tennille	21/4/95	173K	33
STRSAL.GIF	Sally Struthers	8/3/95	151.5K	82
STRLLF.GIF	"All in the Family" cast	8/3/95	186.5K	52
JEBELM.GIF	French star Jean-Paul Belmondo	23/2/95	102K	44
DOTTIE.GIF	Stripper Carol Doda	9/2/95	197.5K	864
BIKCON.GIF	Ft. Lauderdale Bikini contest	9/2/95	115.5K	1409
ANGARY.GIF	Silent-era beauty Anita Garvin	9/2/95	142.5K	31
SKYSLR.GIF	Sophie Loren in a sexy outfit	4/2/95	174.5K	578
STJHTP.GIF	Actress Jill St. John	4/2/95	90.5K	222
ST&BON.GIF	Rock stars Bono & Sting	4/2/95	177.5K	92
SEYBDC.GIF	A seductive Jane Seymour	4/2/95	143.5K	697
POVDCN.GIF	Debbie Downer... with doves	4/2/95	136.5K	707

**One of the strengths of CompuServe is a wide choice of photo files. But copyright latitude is a moot point...**

some 38 stories were filed in the Reuters Variety news area — along with 40 GIF and JPEG graphics and clips from the winning movies. Enough to keep any Hollywood buff buoyant for a few months! Naturally, downloading megabyte-heavy movie files could lead to long hours at the PC — and a hefty CompuServe charge on your credit card.

Online reference is becoming a useful tool for those with a pauper's library, or

a slothful approach to dropping in at the local library. The main encyclopaedia on CompuServe (and eWorld) is Grolier's — adequate, but certainly no Britannica in depth!

Professional forums are CompuServe's strength. I have had many happy hours poking around in my area of interest — broadcasting — and was mischievously delighted to pick up a thread of messages about excessive head wear in SP Betacam recorders.

Apparently, Sony changed the head formulation without telling anyone (except its own tape manufacturing facility); the result was that other tape companies were caught flat footed — and Betacam owners with worn heads — until 3M entered the fray and marketed a new tape!

### Online navigation


Navigation around the CompuServe service is fuss free. The initial graphic menu window is the starting point. Double clicking on any icon will move you into the area you want. But once past the pretty picture facade it's text driven all the way. The contents listings are depicted in long menus, supported by textual explanations. Moving to a site directly is very simple; a typed command GO BETTMANN will take you directly to the Bettmann Archive; GO UK PAPERS moves you into an area where you can peruse recent editions of *The Daily Telegraph*, *The Guardian*, etc.

The screenshot shows the 'Welcome, AustPR8!' window of the Apple eWorld service. The left side features a 3D isometric cityscape facade with various buildings and icons. The right side contains a text menu with several items, each with a small icon and a title.

- STARSHIP SOCIAL HOUR.** Stroll down to Ten Forward Lounge in Synergy Center at 7 PT. Selena plays bartender & talk is of -all- the generations.
- GOT A LEARNING DISABILITY?** At least 19% of Americans have got one. Join us as we help one another cope. 7 pm PT, at The Water Cooler.
- EXPERT HOMEWORK HELPI!** Go to the head of the class with the boost you get from CyberStudy's booknotes, help files & Study Smarter tips.
- MANAGING NEWSGROUPS.** Don't let messages pile up! The eWorld Weekly News Power User Tip from Roger EAC tells you how to take charge.

**Apple eWorld's main window. The graphics facade goes three menus deep, then text takes over.**

# Online, But Not on Your Own...

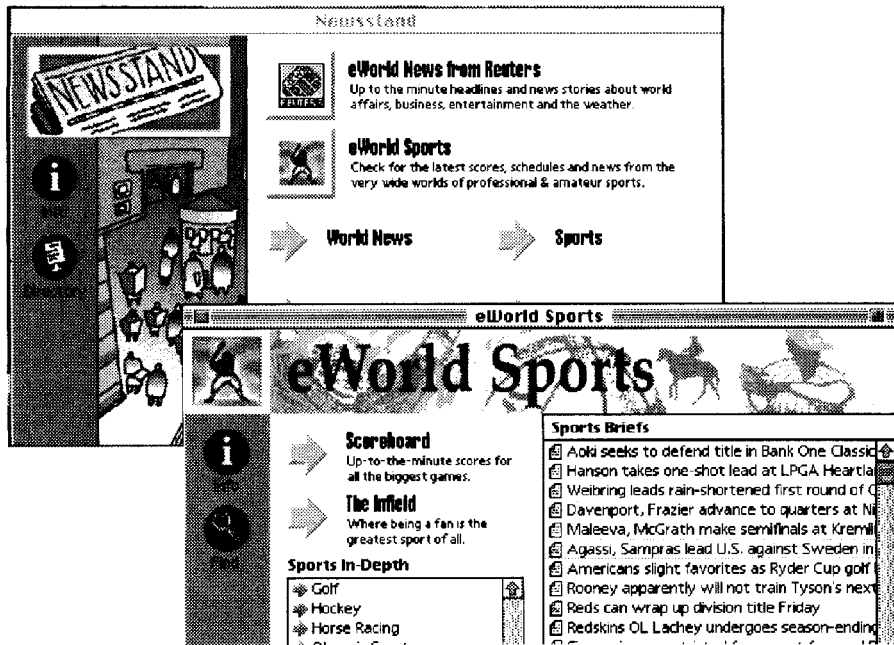

The eWorld 'Newsstand' graphics window. The penalty for such visuals is download time.

In this GUI facade, backed up by textual navigation, CompuServe differs considerably from eWorld, which carries graphics for three or four layers more until text begins. As a result, the former is considerably faster...

Member support is another strength. Once you're connected, and if you still feel out of your depth, you can tap into customer service in a quest for help in getting around. Or you can make billing enquiries, send a message back to base, etc, etc — all at no charge. CompuServe still sees the need to stuff subscribers' letterboxes with all sorts of paper publications in support — as well as a magazine, mailed each month.

CompuServe now also offers gateways to the World Wide Web and the rest of the Internet.

Despite a tip of the mouse towards kids in a few forums, CompuServe is a business/professional service that will fill many needs. But mind those extras!

## Apple's eWorld

A cow of a name to type, with its initial lower case character, this service is the one to watch — until Microsoft's Network can display its strengths.

In many ways eWorld is complementary to CompuServe. Unfortunately, it may be a little too late on scene to garner any more substantial and attractive content.

The situation of various companies soaking up content to make a commer-

cial online service viable and appealing has great similarities to the plight of local Pay TV operators, scrambling to sign up programme providers.

Apple have targetted their core market as 'consumer/home' and SOHO (small or home office) users. For some, eWorld will be a little too 'Mum and Dad', but the promise of Australian content will surely attract many subscribers.

The access software I tried before writing this story was in version 1.1, a little slicker, definitely more 'graphicy' than the launch version.

I have been a subscriber twice over the last six months or so, and each time found much of interest to me. But then my interests are fairly catholic; what eWorld does lack is information rich, professional content.


The much described eWorld 'town square' greets you on connection, complete with muted traffic sounds.

The current version features 10 sites, to lead you into its byways: News Stands, Marketplace, Arts & Leisure Pavilion, Learning Centre, Computer Centre, Business & Finance Plaza, Community Centre, Info Booth, eMail Centre — and the Internet ramp.

Concerning the latter, I was happy to find a special World Wide Web browser can be downloaded — with no connect charge.

I'm afraid you will find one or two of the eWorld sites a little too US-orientated, particularly the Learning Centre, complete with US college admissions info. But imagine its usefulness with a fully loaded Australian educational content!

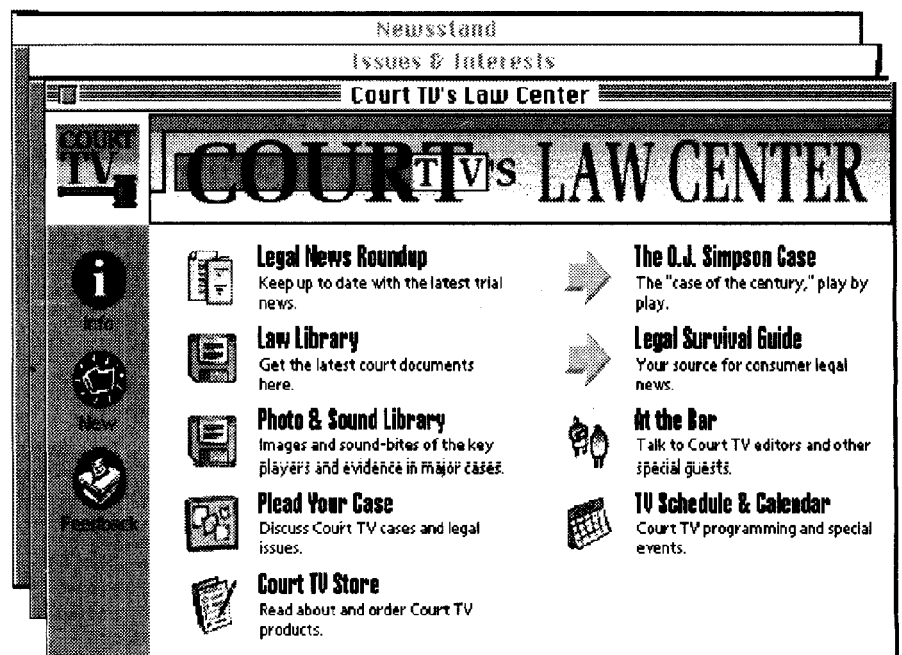There are some highly interesting projects for student level browsers. Some niceties on this spot relate to historical dates and images of personalities, all of which text and graphics you can down-



The eWorld 'Court TV Law Center' site, which was especially popular during the O.J. Simpson trial.

load; these don't appear to carry copy-right burdens.

Another site that caught my eye was the Arts Pavilion, appealing for the movie or arts buff — but not the place where you can find handy tips on SP Betacam!


If you have children, eWorld (and possibly CompuServe to a degree) could be 'ultra safe' services to leave the kids to roam freely; the company claims the service is 'G' rated.

No porn — maybe the occasional nude, but little that will frighten the average parent. Just make sure the kids can't get your credit card details — or watch out for them scavenging around the beguiling shopping malls sprinkled around the service.

However, if you are researching a book on an arcane scientific subject, perhaps eWorld is a little too prosaic.

One irritating facet of eWorld is the highly polished graphic interface. While it is, admittedly, pleasing to click on dialog buttons on ultra decorative windows, the pain in the behind comes from the time the system takes to download each graphic — anything up to 30 seconds per window. But, once loaded, the graphics headers are stored in your eWorld folder.

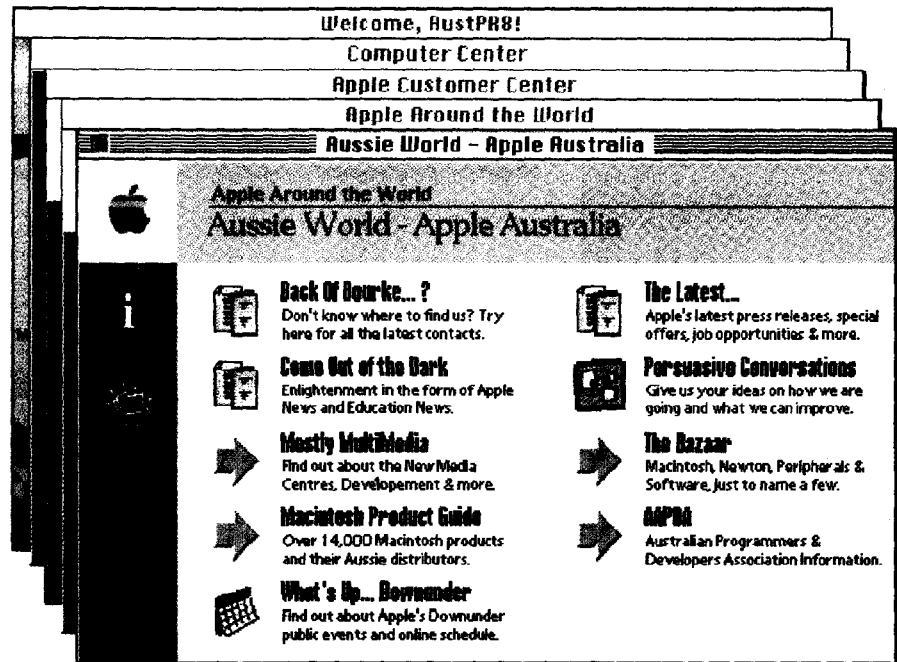I have to admit I'm a sucker for eWorld; it reminds me of those 500-page US magazines we used to get (before paper costs soared), replete with long articles and an advertising content of somewhere near 70%. Great to roam



The Australian sites currently available on eWorld. The company hopes to expand this area.

around in — and, in truth, eWorld is a delight to roam around in, with return visits repaying you with new delights at every mouse button click.

### Conclusion

I am faced with the choice: CompuServe, eWorld, or my basic Internet service provider (which happens to be Ozemail). I like both of the commercial services very much; eWorld has much appeal and, if it grows in con-

tent over the next few months, it may well be my ultimate choice. But then I'm a Mac user — and there is much for devotees of the Apple Corp product.

Now that both commercial services offer a ramp onto the Internet, it means I could well do without my original service provider!

In closing, I would like thank Peter Sandys and Mike Fuller of eWorld and Subra Venkat of CompuServe for their help in compiling this story. ♦

### CompuServe

CompuServe began as a computer time sharing service, in an effort to make an insurance office computer available for the use of down-at-heel programmers in out of hours 'downtime'.

Now the world's largest commercial online service, CompuServe has 3.2 million members — around 29,000 of which are in Australia.

The service is believed to be the market leader in terms of breadth of content. Its traditional users have been from the business sector, but now being discovered by SOHO and individual members.

In CompuServe's formative years no hardware or software was found capable of allowing it to do what it desired so it built its own. Using host machines based on VAX, it created its own operating system and also built its own network equipment.

Several dozen mainframe computers are used, plus a myriad of other host

machines for special purposes, like a dedicated WinCIM (Windows CompuServe Information Manager) download machine.

Regarding censorship: it is against company operating rules to post any obscene material on the service. Forum operators will generally remove obscene material and warn the offending person not to do it again. Repeat occurrences will result in forum lock-outs or loss of membership.

Australian content: aside from AAP, there are a number of other local content providers, and the company encourages people with ideas for their content to contact them.

### eWorld

Currently 115,000 subscribers (as this article closed) are on eWorld globally. The base in the US uses Stratus servers with HP UNIX systems as mail servers.

Occasionally I had trouble logging on, due to traffic. I did find the slow download

times at 9600b/s a bit annoying — how about 20 minutes for a megabyte! But Apple say they will soon lift this to a higher speed.


By the end of 1995, a Windows/DOS version of the comms software was scheduled to be available — which will be of some delight to the PC crowd.

One big advantage of Apple Australia being on eWorld is that you can hit them with questions and download system software without needing to overload the Pacific carrier.
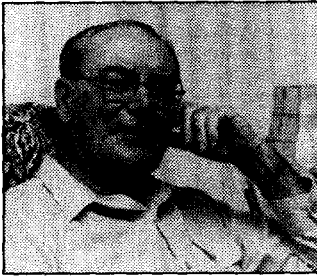
### Comparisons

Both services have a useful 'intelligent agent' feature, which can make daily downloads from the world's press on any subject of your choice.

In the US, there are over half a dozen commercial services. CompuServe is the leader. eWorld is now global and soon will be PC compatible. The question is, will either survive the arrival of an all-singing, all-dancing Microsoft Network?



# When I Think Back...

by Neville Williams

## ***Dr Ernest Benson: A brilliant career in electronics, academic and practical - 1***

Such is the history of electronics that most of its pioneers became involved at an elementary level and gained expertise mainly by practical experience. But a few, like the late Dr Ernest Benson, concentrated first on gaining an initial foundation in physics, maths and electrical engineering — resulting in an exceptional appreciation of both the theory and the practice of electronic equipment design.

Having known 'Ern' or 'Ernie' Benson as a personal friend over many years, it was a shock to hear of his death and to read the notice in the *SMH* a couple of days later:

BENSON, John Ernest — August 2, 1989 (suddenly) at home (D.Sc.ENG) loved husband of Mavis ....

Ern had been an esteemed member of the Institution of Radio & Electronics Engineers (Aust), and an obituary was published in the *IREE Monitor* for March 1990, contributed by his fellow engineer, Neville Thiele. It was reprinted, with due acknowledgement, in the July 1990 issue of this magazine.

Then why this belated instalment of 'When I Think Back', in January 1996? Mainly because the memory of Ern Benson lives on, and embraces far more than could be conveyed in a one-page obituary. There were episodes in his career that I can personally recall and, with the passage of time, it is now possible to merge them with the published obituary, without embarrassment or conflict with the personal recollections of his family.

So here is the story of the Ernest Benson who will be remembered by many old-timers in the electronics industry, and by another quite separate group affiliated with the Anglican Church of Australia. Much of the information, and most of the illustrations have been made available by his wife Mavis and with the cooperation of his sons, both of whom are medical practitioners.

John Ernest Benson was born in Ryde, Sydney, on March 7, 1911, the only son of John Ernest and Lilian Benson. His father was an orchardist and property owner, as were his grandfather and great-grandfather. So it was that Ernest junior spent his boyhood in a farming environment, with cows to be milked, a horse and sulky, fuel stove and grate, and kerosene lamps. The family had to wait patiently for the gas to be connected — and even longer for electricity!

Come Sunday and the Benson family

would put on their 'Sunday best' and head off to St John's Anglican Church at North Ryde, where his father was Sunday School Superintendent. Young Ernest attended St John's until the age of 12, when he linked up with the larger Anglican church of St Anne at Ryde.

At a personal level, this provided a link when we met in later life. My parents also attended church each week in their Sunday best; my father too was Superintendent of the 'bush' Sunday School in Bargo, and I had been one of



**Fig.1: A young John Ernest Benson poses on the family pony with his 'kid' sister Ruth Lilian, his junior by 15 months. They grew up in the 'bush' that once encompassed Sydney.**



the kids. To the 'sceptics', we were both accepted as incurable 'wowsers'!

### The 'bushie' fringe

If Ern's rural background seems inconsistent with his suburban address, one must allow for the fact that Ryde at the time was very much on the city fringe. Beyond it lay what was then Sydney's 'food bowl' — a pattern of rolling hills, orchards, market gardens, dairies, poultry farms, family farms and timber mills, punctuated by tracts of native bushland as yet uncleared.

Ern's years at the Ryde public school would appear to have been a mixed bag, with a teacher problem costing him an extra year. However, when he finally sat for what we then called the 'QC' (Qualifying Certificate), he gained admission to the Sydney Technical High School in Albion St, Paddington. This was in 1925.

It was a tedious return journey from his home each day by foot, train and tram, but it was obviously the right kind of school for his temperament. He appears to have skipped second year and sat for his Leaving Certificate in 1928, earning a Teachers' College Scholarship deferrable over five years. For extra measure, a University Exhibition entitled him to be enrolled in the Faculty of Engineering, commencing in 1929.

This he took up, but after two years of Engineering, he transferred to Science and graduated with a B.Sc. in 1932, continuing his studies to completion in November 1933.

From December 1933 to February 1934 he did Honours Research under Dr Geoffrey Builder and Dr David Martin, in the Radio Research Board in the Electrical Engineering School. His Honours Thesis was titled 'The Cathode Ray Oscilloscope in Radio Research'.

Ern Benson graduated Bachelor of Engineering in Electrical Engineering (B.E.) with First Class Honours, in 1934. Ironically, all this study in Ern's home was done under gaslight, presumably from one of the original coal gas conversion plants that sup-



**Fig.2: An old 'Box Brownie' photo of a live steam scale model of the 'Flying Scotsman' loco — An early indication that Ern Benson had an aptitude for practical work as well as 'book learning'. Ern Benson is at right.**

plied Sydney. The electricity mains did not reach the Benson home in Arthur St, Ryde until 1939!

### Professional hobbyist?

To this point, one might be excused for assuming that the former 'farm lad' had gravitated into the compleat academic — preoccupied by 'why so' rather than 'how to'. But in fact, while pursuing his very successful studies at 'Tech High' he had joined a school hobbies

club and built a small slide-valve steam engine. (I can relate to that because at one stage in my own rural boyhood, my ultimate acquisition had been a miniature steam engine, fired by methylated spirits. It would spin the flywheel like a top but, unlike Ern's home made slide-valver, it lacked the power needed to drive separate models.)

This done, Ern joined forces with a school friend, Ken Nicholls and set about the construction of a 'Flying Scotsman' loco, live steam and scaled for a 2" track. It was completed during his early university years and necessitated the installation of a suitable track in the backyard of the family home 'Mascotte', in Arthur Street. The project culminated in a 'grand opening' attended by Ken Nicholls and C.A. ('Sammy') Coulson, their one-time metalwork teacher from Tech High.


I knew none of this until I read the notes supplied by Mrs Mavis Benson. But it helped explain why I had come to regard Ern as a very practical engineer, ready to come up with ideas but no less prepared to back them up with practical examples. More about this later.

As it happened, 1934 — the year that Ern gained his honours degree — was a carry-over from the 'great depression' and appropriate vacancies were few and far between. He accordingly decided to take up the deferred teachers college scholarship, which was still valid — and emerged with a 2A Certificate from the Dept of Education, a Dip.Ed. from the University of Sydney and a letter from the Director of Education commending him for 'a meritorious college career'!

### Classroom or lab?

Ernest did his practical teaching at Sydney Technical High, his old school, and duly received notice of his appointment to the High School at Lithgow, a mining town and rail centre on the western fringe of the NSW Blue Mountains.

However he apparently had mixed feelings about a teaching career and was still pondering the situation when he received a

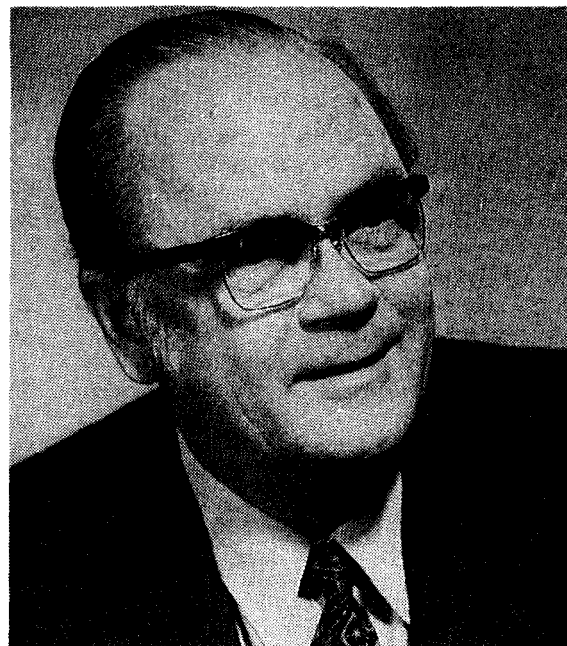

**Fig.3: The Ern Benson that we knew at IREE meetings and other trade functions — and often plied with technical questions. Like fellow engineer Fritz Langford-Smith, he was also very active in Anglican Church affairs — from Sunday School teacher to a member of synod.**



**Fig.4:** From EA files, AWA Research Lab staff in the 'good old days'. (L-R, standing): C.A. Saxby; G.R. Walters; J.E. Benson; H.A. Ross. (Seated): F. Maynard; R.M. Huey; Dr G.Builder; H.J. Brown; D.M. Sutherland.

call from his former mentor, Dr Builder. Dr B. himself had accepted a position with the Research Laboratory at AWA in Ashfield, and needing qualified support staff, had remembered young Ernest Benson. I gather that it didn't take young Ern long to make up his mind! This was in 1934.

At the time, there was considerable debate about the need for more accurate frequency control of AM broadcasting stations. In the early days of broadcasting, many transmitters used tuneable L/C master oscillators, adjusted to the best ability of 'techs' and inspectors — often without precision frequency meters! Listeners would notice aberrations and would protest *en masse* to the PMG Dept when ostensibly isolated stations appeared to edge too close to an adjacent channel.

The Government accordingly decided that all broadcasting stations should convert to crystal frequency control, thereby motivating AWA to document the problem and develop expertise in the production of precision crystals and crystal oscillators. This was at a time when crystalline quartz had to be sliced in certain planes, cut into rectangular wafers, then manually ground and/or etched to a critical thickness until each individual wafer exhibited a natural piezoelectric oscillation at a nominated frequency, when mounted in a suitably designed plug-in crystal holder.

It was a tedious task, with each crystal a one-off product, priced accordingly. How different from the present-day scene when tiny, precision crystals are used by the thousand in tuners and transmitters, and by the tens of thousands in accurate timepieces, ranging from ornate clocks to — almost literally — 'two bob' watches!

### All about crystals

So it was that in December 1934, Ern Benson found himself in Dr Builder's Research Lab charged with the responsibility of clarifying the needs of broadcasters and the appropriate response of AWA in terms of advice and equipment. For several weeks, he spent long evenings in the lab listening to broadcast stations and tabulating the frequencies on which they were actually transmitting.

This led to ongoing work on crystals and their applications, culminating in a paper prepared for the IRE World Radio Convention (Sydney, 1938) entitled 'Precision Frequency Control Equipment using Quartz Crystals' by Dr Geoffrey Builder and J.E. Benson.

Unfortunately, although listed, the paper does not appear in my bound copy of the *Convention Proceedings* and I was denied a first-hand account of the work to that point. I gather, however, that Builder and Benson investigated various modes of vibration in quartz

crystals and their further applications in remotely controlled receivers.

By 1945 Ern Benson had written some 10 further papers on these subjects, which were submitted to the Sydney University for an M.E. degree. This he gained with First Class Honours and the University Medal.

Ern was a natural writer and for the same reasons would no doubt have emerged as an outstanding teacher had he chosen that career. He had a natural ability to sense how best to introduce a given subject, and the sequence in which new and interdependent facts should be presented.

Almost as a matter of course he became the Editor of the *AWA Technical Review*, issued by the Research Laboratory and circulated to technical professionals in the local electronics industry and to contacts overseas. In a sense, it was a companion publication to *Radiotronics* and its related publications, devoted to valve applications under the guidance of Fritz Langford-Smith, a fellow professional engineer/author. Sourced from the same holding company, both publications did much to reinforce the image of AWA as a research organisation as well as being a manufacturer and a merchant!

### A notable tribute

In his obituary (*EA* July 1990, p.16) Neville Thiele records that Ern Benson edited *AWA Technical Review* for 27 years, until he retired from AWA in 1975.

Referring to one of Ern's papers published in the IRE (Aust) *Proceedings* on the colorimetric principles of television (July-Aug, 1951) Neville Thiele modestly describes it as a 'lifelong model for at least one young author, for writing a technical paper'.

Meanwhile, at a personal level, I myself had joined AWA in 1936 and became a small cog in what was then a very large wheel. In the A.W. Valve Co. lab, I/we were only metres from where Ern Benson worked in the cottage-size 'Research' or 'Standards Lab' — call it what you will.

But we might as well have been in another world. We in the AWA lab reported for duty at the same time as most others in the Ashfield complex, arrived in the same buses or competed for parking places in the adjoining streets. We knocked off about the same time each evening and poured out through the same gates, scanned by the

same uniformed security staff.

The research lab team, on the other hand, seemed to 'do their own thing', giving the impression that they were answerable to Head Office in the city rather than being an integral part of the organisation at Ashfield. Over the years, they came and went, as if by remote control.

Shortly after starting work at AWV, my attention was drawn to someone who had just pulled up in his car in the drive outside the Research Lab. "That's Ern Benson", I was told. "He's been specialising in quartz crystals".

Ern was conspicuous, not for his face or figure, but for the fact that the upper half of his torso was protruding from a 'Baby Austin' car. As I remember, it was classified officially as the 'Austin Seven', having a tiny seven horsepower motor. At the time it was the smallest — and lightest? — mass produced car on the road. Some called it the 'motorised pram'...

### Memorable vehicle


From then on, Ern Benson and/or his car became a familiar sight to me in the environs of the Ashfield complex. He seemed almost to relish the contrast between his tiny two-seater and the 'Gee Whiz' vehicles used by some of his peers. One, I remember, drove a French Delarge, weighing allegedly three tons! (Was my mind playing tricks when the name Don Connolly flashed before me?)

I mentioned Ernest and his Baby Austin to his wife Mavis, and suggested that he seemed almost to be making a statement of some kind. Said she: "I'm not sure about that, but he certainly continued to drive the Austin Seven until the mid-fifties. He reckoned he had the last laugh during the war with his Austin 'beetle', when motorists were rationed to a few gallons a month". She continued:

"Ernest used to drive his beetle to university, much to the good-natured amusement of this fellow students. On one occasion he came out of lectures, to find it on top of the steps of the P.N.R. building!" She didn't finish the story, but went one better by finding a picture of the original 'Ern-mobile', photographed outside their home with an exact duplicate owned by a friend.

Ernest's work with crystals led to a paper prepared in association with Ms Edna Dash entitled 'A Compact Piezoelectric Chronometer'. Despite the adjective 'compact' the finished clock used a standard 19" (48cm) wide panel, just on 1-metre high.

In its day it was a revolutionary con-

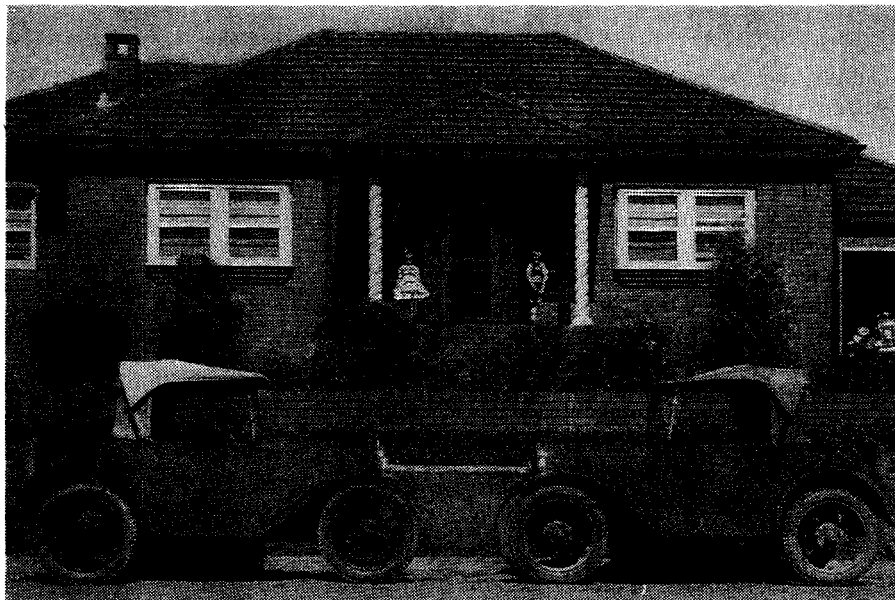

**Fig.5: Two identical 'baby' Austin Sevens, the one on the right being the one which carried Ernest Benson to university and to work at Ashfield up to the mid 1950's. During the war years, they would make a little petrol go a long way!**

cept, but such has been the progress with solid-state technology that I am wearing on my wrist an el-cheapo digital watch which my wife bought for me when I entered hospital over 12 months ago. It is waterproof, runs from an inbuilt cell, displays the year and date on demand, shows the time — which is still spot-on after 14 months — and it cost around 10 dollars. (Not worth pinching!)

### Christmas chimes

That Ern Benson did not have a one-track mind became evident in 1940, when worshippers heading for the Christmas Morning service at St Anne's Anglican Church at Ryde were amazed to be greeted by the sound of a carillon, emanating from the normally mute stone tower.

It transpired that the Rector (Mr Stubbin) and Ernest Benson had 'got their heads together' and set up a public address system in the tower, fed from an amplifier, a phono pickup and a selection of records carrying chime music. To both rector and congregation, the sound brought just the right atmosphere to the occasion.

Then in 1943, the parishioners made a presentation to Mr Stubbins to commemorate the 21st anniversary of his induction as Rector of Ryde. He, in turn, handed the cheque back to the Church wardens to be used towards the purchase of a set of orchestral chimes.

It fell to the lot of Ern Benson to translate the gesture into a reality, beginning with the purchase of a set of tubular bell chimes from the Premier

Drum Co (UK), suitable for keyboard operation. Ernest himself devised the mechanism and constructed the keyboard in memory of his mother, Ethel Benson. A fellow parishioner, Mr L. Vincent constructed the console.

Electronic pickup from the tubular bells and an amplifier feeding loudspeakers in the tower completed the installation. The loudspeakers were AWA public address flared horns, fitted with multiple drivers. The installation was dedicated on February 27, 1944 by Archbishop Howard Mowll.

AWA subsequently commercialised the design and installed an electronic chime carillon in about 25 churches, including Lithgow, Singleton, Scone, Hurstville, St Matthew's at Manly, and the Roman Catholic church at Darlinghurst. One was even shipped to Bombay in India. An AWA model was also installed in St Anne's, and the Benson original was presented by the Church to the Cathedral of the Holy Spirit at Todoma in the Diocese of Tanganyika — half a world away.

### Special occasions

At a professional level, the Chime Carillon was played at the Melbourne Town Hall by Professor Bernard Heinze. Also by Professor D.R. Peart, Professor of Music at Sydney University, from an installation in the AWA tower atop their Head Office building at 45 York St, Sydney; the occasion was the birth of Prince Charles. How time passes!

Broadcast on short wave over Radio

## WHEN I THINK BACK

Australia, the Melbourne performance was heard by Garth Major of the Antarctic Research Expedition on Macquarie Island. Reception was verified by cable to the AWA Melbourne office.

Commercial production of the carillon has since been terminated by AWA by reason of reorganisation and rising labour cost. The installation at St Anne's in Ryde is still functional. It was silent for a while for lack of an experienced player, but the role has since been filled — again — by Mavis Benson on Sunday mornings, in memory of her husband.

A practical advantage of the electronic carillon, she says, is that, unlike their traditional counterpart, the loudness can be moderated — out of consideration for neighbours who may want to sleep in on Sunday mornings! The observation reminded me of an alleged conversation between two neighbours in an unspecified English village:

"Beautiful bells aren't they?"


"Sorry — I can't hear you!"

"I said: the bells are beautiful — so much a part of the English tradition."

"I'm afraid it's no use. I can't hear you for those (adjectival) bells!"

### Taste of the future

I round off this first instalment with a reference to the first occasion on which I walked into the Epping Baptist Church, reportedly the largest Baptist

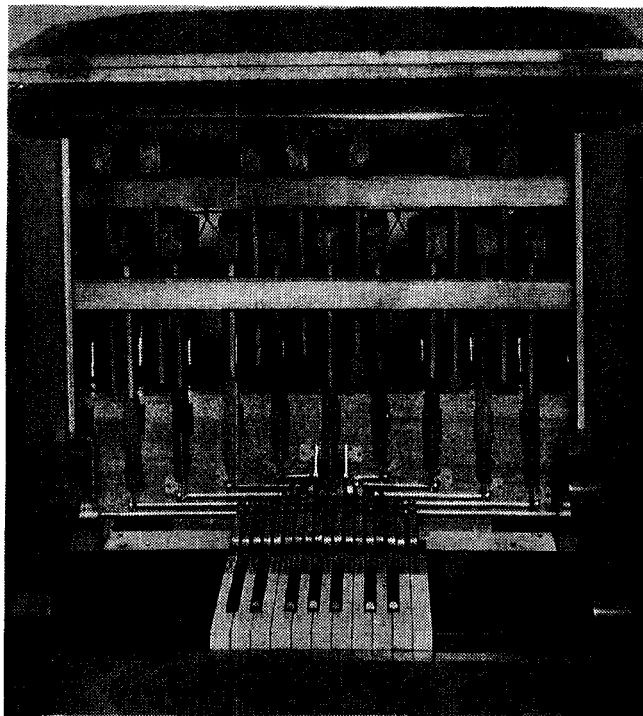

**Fig.6: The 'works' of Ern Benson's keyboard carillon installed and still operating at St Anne's Anglican Church in Ryde, NSW — played by his widow, Mavis. The design was commercialised by AWA.**

church in Australia. It was full to the doors, but I was immediately impressed by the effectiveness of the PA system. It was crystal clear, with not a hint of feedback and with the voice appearing to come from the rostrum area.

A quick glance around revealed only one sound source — an oddly shaped enclosure bracketed into the area where the front wall merged with the ridge of the peaked ceiling. It was fairly large, but too far above the normal line of sight to be intrusive.

A tall narrow fret down the inner face of the enclosure betrayed the presence of (probably) four fairly large loudspeakers; it was clearly intended to project its wedge-shaped sound column towards the audience in the rear section of the auditorium.

Underneath, the sloping base of the enclosure carried a second, shorter column, focussed on the forward pews. Down below the enclosure was the platform carrying the pulpit and supplementary microphones, clear of the wedges of sound emitted by the columns above.

Textbooks tell us that human senses indicate to us the source of sound in the horizontal plane — left/right and front/back. We are much less sensitive in the vertical plane. The congregation at Epping Baptist simply accepted that the sound was coming from where the action was; they had no urge to quibble that the preacher was 'doing his thing'

50 feet in the air.

At the end of proceedings, I remarked to a church officer that "Whoever specified the PA system knew what he was doing!" His reply: "He's a local man from St Anne's at Ryde. You might know him — Ernest Benson."

Yes, Ernest Benson certainly *did* know what he was doing. He was to mastermind sound systems in some of the most important buildings in Sydney and Canberra!

*(To be continued) ♦*

## Impressive Results by UNSW Opto Researchers

*Continued from page 25*

fibre we have developed. Also, integration of the demultiplexing and photodetection devices into a single package makes the unit very robust," Professor Chu said.

"If every home in Australia is going to be wired with optical fibre, it is not difficult to see the huge market for this device," he added.

As the principal investigator for the project, which received \$1.28 million in GIRD funding, Professor Chu is looking for a commercial developer for the device, which, he estimates,

could be manufactured for about \$100.

Professor Chu said that the demultiplexer was robust enough for wide-spread application.

It is now ready for commercial production and Professor Chu welcomes inquiries.

Siemens has decided not to commercialise the product, due to the company's specialising in electronic (as opposed to photonic) technology and to a perceived bout concerning the speed with which 'fibre to the home' technology may be taken up by Australian markets.


In this project, Siemens paid for

John Arkwright to work with the group. Professor Chu said that the link through Mr Arkwright to Siemens had been invaluable in defining Siemens' requirements and directing the focus of the research — which had produced numerous benefits for Siemens.

This project followed the highly successful project on twin core fibre optical switches supported financially by Siemens and led by Professor Chu and Professor Allan Snyder of the ANU.

*(Reprinted from Uniken, by permission). ♦*

# NEW BOOKS

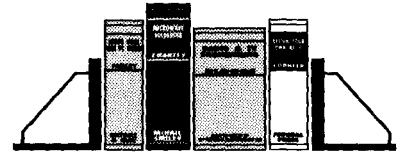

## Scope primer

**FAST SERVICING WITH OSCILLOSCOPES**, by M.C. Sharma. Published by BPB Publications, 1994. Soft covers, 234 x 180mm, 176 pages. ISBN 81-7029-409-6. RRP \$19.95.

Another economy textbook from New Delhi (India) publisher BPB, this time an introductory book on the operation and use of modern scopes. The author says his aim has been to enable the scope user to use it more intelligently, and get the maximum out of it as a tool.

There are 17 main chapters, which start with scope basics and take the reader through the various sections of the instrument and how they work. Then follow chapters on probes, measurement techniques, troubleshooting, storage scopes, using a scope in conjunction with a counter, and choosing an instrument. A couple of appendices deal with scope performance parameters and measurement, and typical specifications.

Where particular instruments are discussed, there's a fairly strong emphasis on the particular instruments available in India. However apart from that, there's a great deal of general material that applies just as much over here. In fact on the whole, the book gives a very good basic introduction to the operation of scopes and how they're used.

I couldn't find any typo's, and there are plenty of neatly drawn diagrams — although only a few rather murky half-tone pictures. If you're after a helpful but inexpensive introduction to scopes, though, it's well worth considering.

The review copy came from Jaycar Electronics, which stocks it as Cat No. BM-2488. (J.R.)

## DIY monitoring

**HOW TO BUILD EARTHQUAKE, WEATHER AND SOLAR FLARE MONITORS**, by Gary G. Giusti. Published by Tab Books, 1995. Soft covers, 190 x 235mm, 290 pages. ISBN 0-07-025209-2. RRP \$39.95.

This is a book about build-it-yourself equipment to monitor natural phenomena like lightning strikes, solar disturbances and earthquakes. The author is billed as a National Weather Service (US) spotter and longtime student of earthquakes and weather phenomena.

The book is divided into three parts, each with a number of chapters. The first part describes modular circuits and is a 'basics' section, aimed at beginners to electronics. Included are designs for a basic seismometer (with sensors), a seismic-flare receiver, a number of valve circuits (TRF radio, audio amplifier, geo-monitor) and some power supply circuits. At all times the author keeps the focus on monitoring natural phenomena, rather than just electronics.

The second, or advanced part includes details of a BFO seismic detector, a magnetic disturbance detector, a very simple ULF/VLF radio and an inductive energy field monitor. This part includes two chapters about earthquakes, mainly based around the United States.

The third part, called 'Maverick observations, theories and tools' details some case studies and theories, along with constructional details for some more equipment. It includes a Geiger counter, an interferometer and how to adapt a digital multimeter as the display for some of the projects in the book.

The appendices includes a list of basic

electrical laws, US standard electrical symbols, component colour codes, very brief data on some popular ICs and components and a list of reference books.

In summary, there are over 40 projects to build. The most expensive project is costed at US\$75, but most less than US\$25. The book doesn't aim to teach electronics, but many of the projects are suitable for beginners.

The writing style is rather old fashioned, but is friendly and easy to read. The review copy came from McGraw-Hill Australia, of PO Box 239, Roseville 2069. (P.P.)

## Caravan electrics

**DAVE JEANES' COMPLETE GUIDE TO CARAVAN ELECTRICS**, by Dave Jeanes. Published by Dave Jeanes, 1995. Plastic comb binding, 210 x 150mm, 88 pages. ISBN 0-646-21344-X. RRP \$15 including P&P.




A handy little 'practical manual' from Australian author Dave Jeanes, whose earlier books *Marine Electronics Workshop Manual* and *Journey Around Australia* have been very popular. Mr Jeanes has also contributed various articles to *EA*, in the past.

The idea of this new book is to give non-technical caravan owners enough practical knowledge of electricity, low voltage circuits and electrical appliances to be able to tackle mods, additions and of course emergency repairs, when trouble strikes in isolated locations.

There are 12 chapters, which start off with basic electrical concepts and gradually progress through wiring, lighting and batteries to the various appliances — including fridges, TV and radio receivers, mobile radio and phones. There's lots of good practical information, which should make it of considerable value to those for whom it's written.


Mr Jeanes has written and published the whole thing on a PC using Microsoft Word and Publisher, and although some of the diagrams are a little basic, they're generally quite clear. Overall it seems good value for money.

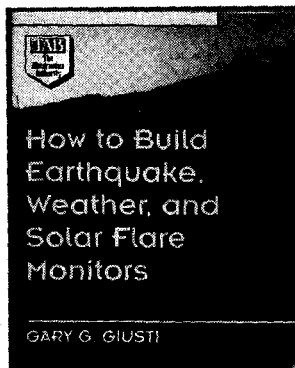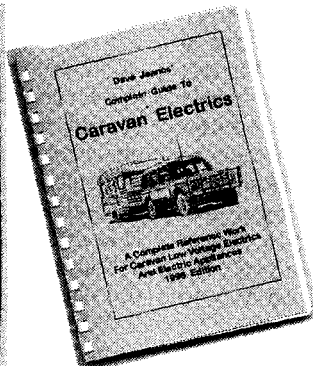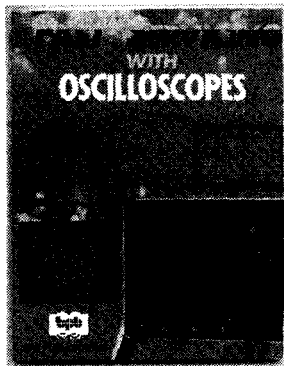Copies are available at the price given above directly from Dave Jeanes Books, PO Box 77, Tugun 4224; phone (075) 988 642. (J.R.) ♦



# FORUM

Conducted by Jim Rowe

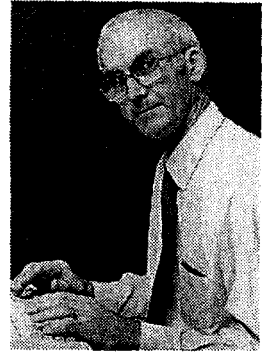

## Why doesn't EA publish more micro-based projects — with full source code?

We're going to tackle a different, timely but also quite thorny subject this month: the question of whether or not magazines like *EA* should publish more construction project designs based on microcontrollers and similar chips containing 'firmware'. After all, say the pro-micro enthusiasts, this technology represents the real future of electronics. There's also the related question of whether we should always include the full source code listing for any firmware involved in such projects, to allow readers to learn more about its operation...

This is a subject that I've been concerned about myself for some time now, and I imagine that it's been exercising the minds of quite a few other electronics magazine editors as well. With microcontrollers and other programmable devices becoming more and more common in commercial electronics equipment, shouldn't we be publishing more construction projects using these same devices, so that our readers can learn more about them?

Unfortunately it's not quite as simple as that — I only wish it were. In fact it's one of those subjects that tends to open up all sorts of complex issues, as I'll try to explain.

Because these projects are based largely on firmware, or 'software in silicon', the conventional hardware side of the project often tends to become little more than a few unexciting-looking chips on a small board. The really 'interesting' part is the code buried inside the programmable chip — i.e., how the programmer managed to get the chip to 'perform the appropriate tricks'.

What this means, for a start, is that we're now talking about a different *kind* of electronics project from the traditional type. One where the interest and satisfaction (for readers and those who build the project) must come from understanding the code used to make the chip do the required job, rather than from understanding how the various components work together, to make a circuit which achieves a similar result.

Now I'm not saying that this makes such a firmware-based electronics project any less appropriate, or less worthy of publication than a traditional hardware-based one. Bearing in mind the

directions in which electronics is moving — inexorably — that's clearly not the case. In fact you can easily argue that firmware-based projects are now more appropriate than the traditional type.

But they're clearly rather *different*. So different, in fact, that some readers and electronics DIY enthusiasts have indicated to us that they don't find them of much interest. They see them as exercises in programming rather than in building a piece of electronics, and they don't find this as satisfying. "Why don't you give us as many interesting little electronics projects as you used to?" they ask, "instead of these things based on yet-another-@#%\$\*~-programmed-micro?"

Another complicating aspect of the situation is that for magazines like *EA*, which still try to develop as many DIY projects as we can 'in house', these firmware-based projects always seem to take a lot longer to develop than the traditional variety. This means that essentially, they cost us more to develop...

Not only that, but when they are finished and we want to publish them, we then have to find ways to ensure that pre-programmed chips will be available, for the benefit of people who don't have their own programming equipment. As many people nowadays like to be able to buy a complete kit for any project they build, this often means talking at least one of the major kit suppliers into organising a chip-programming operation. This is something that understandably they're often not all that keen to do — it adds to the cost of producing kits, and if the kits don't sell, the programmed chips may not be easy to use for any other project.

What happens in a year or two's time,

too — when the firm or firms who have originally agreed to do the programming may have decided not to program any more, because of reduced demand? Such a project can become 'too hard to build' much faster than one based purely on hardware...

Even publishing the firmware's source code listing in the magazine can be a problem, because it can take up a lot of space — often generating complaints that we're filling up our pages with 'boring computer programs'.

### Other complications

On the other hand if we publish a project submitted by a contributor, using a programmed micro, there can be *other* complications. Because the firmware has often involved the author/designer in a great deal of work, they understandably want to get a reasonable return on this 'investment'. Often this means either that they want us to pay a lot more money than usual for the publishing rights (which would make them too expensive for us to pay), or that they want to retain the copyright for their firmware — and either sell the programmed micros themselves, as the sole supplier, or require a licence fee from any kit supplier who wants to make use of the firmware.

Needless to say, either of the latter options tend to make the projects less attractive to the main kit suppliers, who generally won't touch them. So both readers and advertisers tend to be rather less than enthusiastic, about such projects...

Starting to see what a complex subject this can be?

Actually the foregoing is all by way of a preamble, to two letters from readers



that turned up recently, dealing with different aspects of this subject. One is a complaint from a reader, asking why we don't publish more source code listings, while the other comes from an engineer/designer who had offered me a number of micro-based projects, and was understandably a little disappointed when I was only lukewarm in my response. When they both turned up in rapid succession, I decided that it was time we explored the subject here...

The first came from Mr Steven Pass, of Huntingdale in Victoria, who had this to say:

*I have been reading various electronics periodicals for about 15 years, both local and international publications. In the last couple of years, I have noticed a disturbing trend, particularly in locally produced publications, from an educational to a profit driven content.*

*Many projects are now being based on microcontrollers, which is good to see. However virtually none of them include source listings, or the ability to download the listings, because the project writer has retained the copyright, etc. This forces the reader who is interested in building the project to purchase a pre-programmed device, and occa-*

*sionally the PCB. Nothing is therefore learnt about microcontroller programming or its internal operations.*

*"The writer has put considerable time and effort into the project", I hear you say. True, however isn't that why you paid for the article in the first place? Didn't you pay for the rights to publish their work? Why should they, or even you, the publisher, monopolise the market for that project?*

*I used to see detailed listings and examples for all of the 'hi tech' projects. This is where electronics enthusiasts really learned their skills. Now we have to send off for a device where all of the hard work has been done, and we gain no new skills at all.*

*Why then, do other overseas publications continue to give their readers source listings, or at least the ability to download it from somewhere? They, obviously, are education driven. They actually want their readers to learn more from a project than just assembling projects onto a PCB and connecting switches and LEDs.*

*A few local attempts at educating the readers was made in the past, with microcontroller development kits, but these were never followed up. Why?*

*With the increasing trend towards microcontroller based projects, why don't projects include the skills taught by the development kits?*

*I now find myself only purchasing your publication for 'The Serviceman', feature articles and the occasional non-microcontroller based projects. I sincerely hope this situation changes soon.*

Thank you for taking the trouble to write about your concerns, Mr Pass. I can appreciate your general position, too — no-one can learn much from plugging in a pre-programmed 'black box' chip, if the code inside is kept secret. However some of your specific criticisms do seem a bit unfair, and perhaps based on either unrealistic or incorrect deductions.

For example you imply that magazines like EA have somehow changed from once being purely 'educational', to now being purely driven by profit. That's not true, of course — like all commercially published magazines, we've always had to make at least some profit in order to survive. What has changed, in recent years, is that nowadays we have a much harder battle in order to even survive.

All around the world, traditional elec-

tronics magazines like *EA* have been finding things tougher. Circulations seem to have been slowly falling, while at the same time advertising revenues have stagnated due to tightening economies in many of the developing countries like Australia. Paper costs have also been rising, quite dramatically. Nowadays we also have to compete on the news stands against an enormous range of other publications — including electronics magazines from overseas, and umpteen different computer magazines. All competing for the attention of our traditional readers, who seem to be fewer in number than they were. So survival isn't nearly as assured as it might once have been, and we simply can't afford to ignore this aspect.

Despite this increased pressure, though, we haven't forgotten or deliberately dropped our traditional role in helping readers learn about developing technology — after all, this is one of the reasons why people have wanted to read this type of magazine, and we wouldn't want to do anything that would make them lose interest in us. As I mentioned earlier, the problem has been that satisfying all of these requirements is simply not easy.

As you can see, Mr Pass also assumes that with contributed projects involving firmware, we should simply be prepared to pay the designer for all rights — so that we can publish and/or make available the complete source code, etc. Well, this might be feasible for overseas magazines with considerably larger paid circulations and better advertising support than we have here, but I can assure you that if we tried to do this, we'd need to charge rather more for *EA* than we do now...

I wonder if Mr Pass would be prepared to pay considerably more for the magazine, in order to make this possible? Even if he is, I'd doubt if many readers would be that generous. My guess is that we'd lose quite a few readers, and consequently we'd have even more 'challenges' than at present.

I'm sorry, Mr Pass, but I don't think there are any simple answers.

### Designer's viewpoint

But let's look now at the second letter, which came by e-mail from Mr John Olsen of Whitireia in New Zealand. I gather that Mr Olsen is a lecturer in electronics at the local college, and he first sent me a letter asking about my possi-

ble interest in some microcontroller-based projects he had developed. Because of the complications with this kind of project, my reply was somewhat less than wildly enthusiastic, even though the projects themselves sounded quite interesting in themselves. I explained some of the drawbacks of publishing too many of these projects, and mentioned some of the criticisms we have received.

Mr Olsen was quite understanding, and sent back a letter with the following very interesting comments:

*Thank you for your reply. It sounds to me from the fax you mention that you might at least have a possible topic for your forum pages. On that basis I thought you might be interested in some of my thoughts for and against programmable chips in general.*

*Firstly I believe that programmable chips, especially microcontrollers, are going to be more and more important in future. Suppliers tell me that they are selling these chips more and more. Many of them are going in instead of standard TTL and CMOS chips.*

*If this is the way that the industry is heading, then it follows that standard logic chips are going to get less common. This means that in the long run you are going to get more and more limited in the projects you can offer. I see this as part of the same trend that has taken us from octal valves, through the miniature tubes, into transistors, and on to integrated circuits. I haven't been around for the whole of this process, but I recall some of the arguments when changes were occurring. While I enjoy the odd bit of vintage radio etc, I'd hate to see the whole magazine drop into a time warp...*

*Remember back when integrated circuits were going to make home construction impossible? Well, we're still here.*

*On the other hand, I can understand a potential constructor being wary of a project which contains a chip which may be difficult to replace, and which he/she does not understand the contents of. However, this is not unique to programmable chips. I have been put off by projects containing special function chips which are not readily available in New Zealand, although they may be in Oz. Not all manufacturers are as well represented in both countries.*

*The point about publishing software and firmware is a pretty valid one. I have certainly been aided by the example software from application notes that I have been able to get hold of. Perhaps the article should contain a*

*fully documented listing — or else it should be freely available, e.g., from your bulletin board.*

*The down side is that unless you are really interested, an assembly code listing is pretty deadly stuff. The computer magazines all breathed a sigh of relief when the march of technology rendered it unnecessary to publish listings.*

*Another aspect is that the writer of the software would have to surrender all rights, as once it is published there is no effective way of limiting its use, to say non-commercial use. This would mean that the payment to the writer would have to cover all rights, and would have to be a fair return for the effort put in.*

*I would not have any particular problem with selling rights in that way, but would point out that the designer does put in a larger effort with this type of design. The user reaps the benefit of a project which for a given outcome is easier to assemble. This would leave it to you to negotiate arrangements for kit manufacturers, who could program their own or arrange to have it done, and it would be just a part of whatever arrangements you already have with kit manufacturers.*

*It might in fact be easier for them to program a standard blank part which could feature in several projects, than to locate a brand XYZ special function chip which is only available from one place (and they just ceased production...). Electrically erasable chips are especially nice for this situation, as excess stocks can be erased and reused in another kit. But even one-time programmable chips should only be programmed at the latest time practical.*

*An advantage of publishing the listings would be that the adventurous reader could modify the design. (I sometimes wonder how many designs are built exactly as published. Going by some that I have been asked to help get going at times, not very many!)*

*Incidentally one objection to programmable chips is the cost of the programmer and software. This is not as bad as it seems. There are two approaches. One is to buy a kit for a particular family of devices. The kit for the SGS-Thomson ST6 devices is around the NZ\$250 mark, complete with software and sample devices. This is not an impossible sum for a keen enthusiast who wants to be able to do design work. The project for the 68705 chips described in your magazine seems to be good value too.*

*The other approach is to splash out a*



bit and buy a universal programmer. These are more expensive but will program a much wider variety of chips. I have a universal programmer myself at home. The difficulty is that you will still need software for the particular families of chips you want to program. There is some software available as shareware or public domain. It is also possible with PAL chips to do the equivalent of hand assembly. (Perhaps that would make a good article :-). Phillips used to provide a form in their databooks for doing just that. This means that you start with a logical design — e.g., symbolic diagram or equations, and figure out which fuses in the PAL need to be blown to create that design.

Also not everyone needs a programmer. The ordinary constructor only needs access to programmed chips. Perhaps it could be like the printed circuit boards, where some manufacturers of boards can provide boards for any EA (or ETI) design for years back. I would actually program any chip for which I have the source code, for a half dozen tinnies for a one-off, and a very negotiable price around \$1 each for large quantities. (Plus the price of the blank chip, of course!)

From your magazine's point of view, I suspect that microcontrollers are more practical than PALs, partly because programmer kits are more readily available. The software is also fairly available too.

My experience is that the chip manufacturers, or at least the agents, are only too happy for you to have the software, as the only possible reason to want it is to create a demand for their chips. They seem to think their mission is to sell chips, not disks. Some of the PAL software seems to be more commercial.

Fortunately microcontrollers are better suited for the kind of project you would mostly be interested in. PALs only come into their own where really high speed complex logic is needed.

It would be reasonable for you to limit the range of programmable parts you were prepared to consider to those that you know are readily available, and that the kit suppliers could cope with. This might include standard EPROMs and a few of the microcontrollers for which programming kits are available readily.

One thing that really appeals to me about the whole design process using programmable chips is its flexibility. If something isn't quite working right, just tweak the code a little. With simulators and emulators, you can try out the

design before committing yourself too far. If the printed circuit layout proves difficult, you can change the pinout (to varying degrees depending on the type of chip). Also the printed circuit layout tends to be less complex, so you may get away with a single-sided board instead of double.

Thank you for those comments, Mr Olsen. I for one found them very interesting, and I imagine other readers will do so as well.

You may well be right, that the change from 'hard wired' chips to the programmable variety is merely another stage in the ongoing evolution of electronics, which began with thermionic valves. Perhaps that means we will find a way to adapt to this next stage, and one that will keep everybody happy...

### Different implications

It's interesting, too, that you agree there's rather more effort in developing a microcontroller-based design than one based purely on hardware. As I read this part of your letter, it occurred to me that this is an aspect with different implications when you're designing equipment for commercial production, compared with designs for publication in a magazine like EA.

When you're designing something for commercial production, the additional effort involved in writing and debugging the firmware is of less importance, because it's a 'one time only' factor that can be balanced against the expected savings in production costs — or if you like, the additional profits from selling the end product. But when a design is to be published, that balancing can't be achieved as the magazine merely publishes the design and doesn't receive any revenue from the production and sale of the equipment concerned. The additional development cost simply makes the design a more expensive one, compared with one based purely on hardware.

It's true, of course, that the firmware-based design may be easier for the constructors to put together and get going. If we're able to publish the source code, they'd also be able to learn a lot about up-to-date technology. But that brings us back to one of those questions raised earlier: how many readers would be prepared to pay more for their magazine, in order to compensate the publisher for the additional investment?

Roughly about the same number of readers as those who'd be prepared to invest in their own programming setup for microcontroller chips, I suspect...

### What it all means

Well then, let's see what can we conclude so far about this rather complex situation. I guess it's pretty clear that we're going to have to publish more of these firmware-based designs in the future, as that's the way electronics is headed. We've already published a number of them, of course — most of them from contributors.

At the same time, we're obviously going to have to try harder to obtain permission from the designers of these projects, to allow us to either publish their source code in the magazine, or at least make it available to interested readers via either the BBS or floppy disk. How many designers of these projects are going to allow this, without wanting additional money, I'm not sure; but we'll try.

Even if they do, I'm not sure how many source code listings we're going to be able to print in the magazine itself. As John Olsen points out himself, they can be pretty boring unless you're really interested — and they often tend to take a good deal of space. Perhaps readers like Steven Pass will be prepared to settle for them being available via the BBS, or by sending in a formatted floppy and having us run off a copy, for the usual 'nominal fee' to cover postage, etc.

I'm not sure exactly what we can do about the availability of pre-programmed chips, for those who can't program their own. We don't really have the staff or facilities to do this ourselves, and often the major kit suppliers don't want to be bothered. We might be forced to continue the arrangement that has been used with many of the designs published to date, whereby we ask the author/designer to make pre-programmed chips available for a reasonable fee.


But what do other readers think — is there a better way of handling this situation? What do the rest of you think about projects involving firmware? Please write, fax or leave a message on the BBS to let me know what you think. ♦

### EA's READER SERVICE BBS

As part of its service to readers, *Electronics Australia* operates a Reader Information Service Bulletin Board System (BBS), which makes available a wide range of useful information for convenient access and rapid downloading.

The BBS is ANSI compatible and is currently operational for virtually 24 hours a day, seven days a week, on (02) 353 0627. Use any speed to 28.8kb/s.

# THE SERVICEMAN

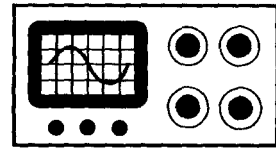

## The VCR with a mind of its own, and how long does it take to forget a fault?

Among the stories I have for you this month is the tale of a VCR which produced the most weird fault symptoms I've ever heard of — especially as they kept on changing. There's also yet another story of problems caused by dry joints on PC boards, and finally an embarrassing admission: I've just spent about 90 minutes rediscovering a fault I tracked down seven years ago, in the self-same set!

Most stories used in these pages have a distinct beginning, middle and end. That is, we open with a description of the symptoms, develop the story with the search for the cause of the trouble, then wrap it up with a discussion on why the fault caused the particular problem.

This is all very neat and satisfying as far as these 'finished' jobs are concerned. But there are a number of interesting tales that just peter out in the middle — no satisfactory answer is ever found. In these cases the appliance is either junked or used within the limitations imposed by whatever fault is still present.

The following story is one of these. It comes from contributor Gus Harvey, of Taringa in Queensland. I'll let Gus describe his problems first,

then see if we can work out a likely end to his story:


*I have a 1982 or 83 model National NV 777 VCR, which apart from replacement of some mechanical parts, has required no servicing and is still producing good recordings. However late last year it developed some strange electronic behaviour which I cannot explain, and I hope you may be able to throw some light on it.*

*With the machine in the normal 'standby' mode, when the On button is pressed the LCD counter remained blank but all other functions were operative. I assumed that this was due to the failure of the supply rail to the LCD.*

*I dismantled the machine, but by the time I had opened out all the boards to get to the power supply and do some checking, the LCD was again operating normally. Nevertheless, I traced out the 5V rail with a multimeter, paying particular attention to contacts in the inter-board plugs and sockets, wiggling and twisting circuit boards, and squirting freezer spray into strategic places. There was simply no way I could make the circuit misbehave.*

*I also checked with a CRO for adequate filtering, bearing in mind the possible condition of 12 year old electrolytics, and your article in the November 94 issue.*

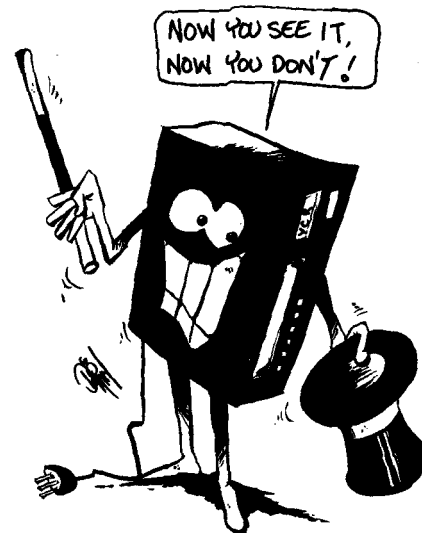*So I put the machine back into service, but after a couple of weeks the fault recurred. As it wasn't convenient to take the machine out of service at that time, I continued to use it. But several days later, while in the standby mode, I noticed some faint bits of other characters flickering on the LCD. Pressing the ON button brought the LCD to full display, but*



*now none of the control buttons would work!*


*So it was back to the workbench, and a repeat of the former performance. By the time I got the cover off and the set re-energised, everything was working normally. And it stayed that way — despite my attempts to bash it, freeze it or heat it into its failure mode, all of this over a period of several days.*

*In fact, it seemed that merely disconnecting it from the mains for a few minutes was enough to cure the fault.*

*Since then there has been another mutation of the fault. After the VCR has been in standby mode for a couple of weeks, with normal record and playback of about six hours per week, pressing cue or review buttons causes the machine to stop. However, it will respond to a subsequent press of the play button. This fault can also be*
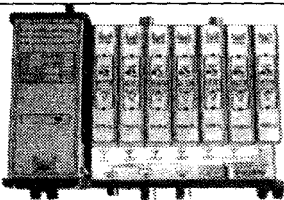
## Equalize..

..up to seven TV channels with 42dB UHF gain, inputs for Sat. and FM, and auto. level measure for around \$350 plus tax. New Alcad 905C.



Peter C. Lacey Services Pty. Ltd.  
80 Dandenong Rd. Frankston VIC. 3199  
Tel: (03) 9783 2388 Fax: (03) 9783 5767

cured by disconnecting from the mains for a short time.

I have adopted the practice of simply pulling out the mains plug whenever the VCR is not required, and in this manner it has been working perfectly for a couple of months. I realise that I am taking the easy way out, but I have only a superficial knowledge of VCRs and microprocessors, etc., and am not competent to probe any deeper. However, I tell the story so that others may find it of some academic interest.

Well, Gus, that is as strange a set of symptoms as any I have heard of. At first reading, I thought it sounded a bit like a faulty Mode Switch, then I changed my mind to a faulty microprocessor, then to something else and finally gave up. I really don't have any theory that would account for all the symptoms.

At one point the problem looked like a dry joint or loose connection. But that wouldn't be cured by simply turning the power off for a few moments. A bad mode switch would introduce mechanical problems — the machine would be unlikely to work normally for record and playback. A faulty display driver might account for the LCD problems, but not for the control lock-out.

I don't know, Gus. I can't answer your question — does any reader have a clue? Gus and I would both like to hear from you.

## Happier ending

Now we turn to a New Zealand contributor, for a story with a happier ending. It comes from Graham Cheer of Tauranga. Graham tells a story about dry joints on early PCBs, and the long and frustrating search for one particular joint:

*I have been in the electronics service business since the early 1960s, and have a collection of service stories from the non-TV/VCR bench that you may find of interest.*

*The first story dates back to about 1973, when I was working for the then NZ distributor of Canon cameras and calculators. I was servicing the calculators, which were using DTL (the forerunner of TTL) and diode/resistor logic.*

*As you can imagine, these desktop calculators were quite complex, especially as the logic chips were all NAND gates only and the more complex models had seven or eight plug-in PCBs with about 30 to 40 ICs per board.*

*One of the problems these PCBs suffered from was dry joints on the through pins, which connected the top*

*and bottom tracks of the double-sided boards. Whenever one of these units came in with an intermittent fault, we would remove the offending board and resolder all the through pins at top and bottom. This would usually fix the problem.*

*I had one particular unit which came back for the same intermittent fault a number of times, and it was always proved to be the same board. So I had to get stuck into this one with the oscilloscope to try to find the cause, as resoldering had not solved the problem.*

*I found that the problem was still to do with a faulty connection, as one pin of an IC had an intermittent 'fuzzy' signal when it should have been a clean logic type of signal. To trace the source of the problem, I had to follow the track*



*on the PCB to where I eventually came to a through pin.*

*On looking at the top side of the PCB, I found the pin came up underneath an IC. This we had never encountered before, and it was the only place where a pin appeared under an IC in all the models we serviced.*

*I removed the IC and found the pin barely protruding through the board and with an obvious dry joint on its surface. I pushed the pin further through and resoldered it, then reinstalled the IC, now sitting just a little higher than usual.*

*The calculator worked perfectly after that, and we didn't see it again. Needless to say, from then on whenever that model came in with intermittent problems, we made sure to resolder that hidden pin top and bottom!*

*I have found that working on these early model calculators has left me in a position of being able to get into microprocessors without too much difficulty. I have gained a good knowledge of adder circuits and how they function, and also the concept of subtracting, multiplying and dividing by doing addition only.*

*It is also interesting to think back just 20 years and how digital electronics has progressed. The old Canon calculators could easily fit into their own equivalent of 'Vintage Radio'.*

*Two things that come to mind are the complexity of the JK flip-flop, being made from two NAND gates with associated resistors, capacitors and diodes. The second item was a mechanical 'shift register' memory. It used an electro-mechanical delay line, like the reverb units used in guitar amps.*

*You may remember that these consisted of a piece of steel spring set into vibration at one end by a coil, the vibration travelling to the other end and being sensed by a pickup coil. As you can imagine, in digital memory service, any tap on the case would completely corrupt the data in the system!*

*Thanks for that little item, Graham. I can quite imagine the confusion that hidden through-pin must have caused. Come to think of it, I recall a number of early English colour TVs with double-sided boards and problems with dry joints. Who knows, maybe a number of those finished on the tip, due solely to hidden through-pins...*

*As far as the 'Spring Memory' is concerned, I've never heard of anything like it. I could imagine that it would work, but in a shaky island like New Zealand, I reckon the data would be corrupted more often than not! (All right — I'm sorry!)*


*Graham mentioned that he was submitting several stories. I am holding the others until later — they are too good to splash out all at once. Thanks, Graham.*

## Lapse of memory

Now for a story from my own workshop.

How long does it take to forget a particular TV fault? I happen to know, because I have just looked it up on a customer record. It takes just seven years and twelve days!

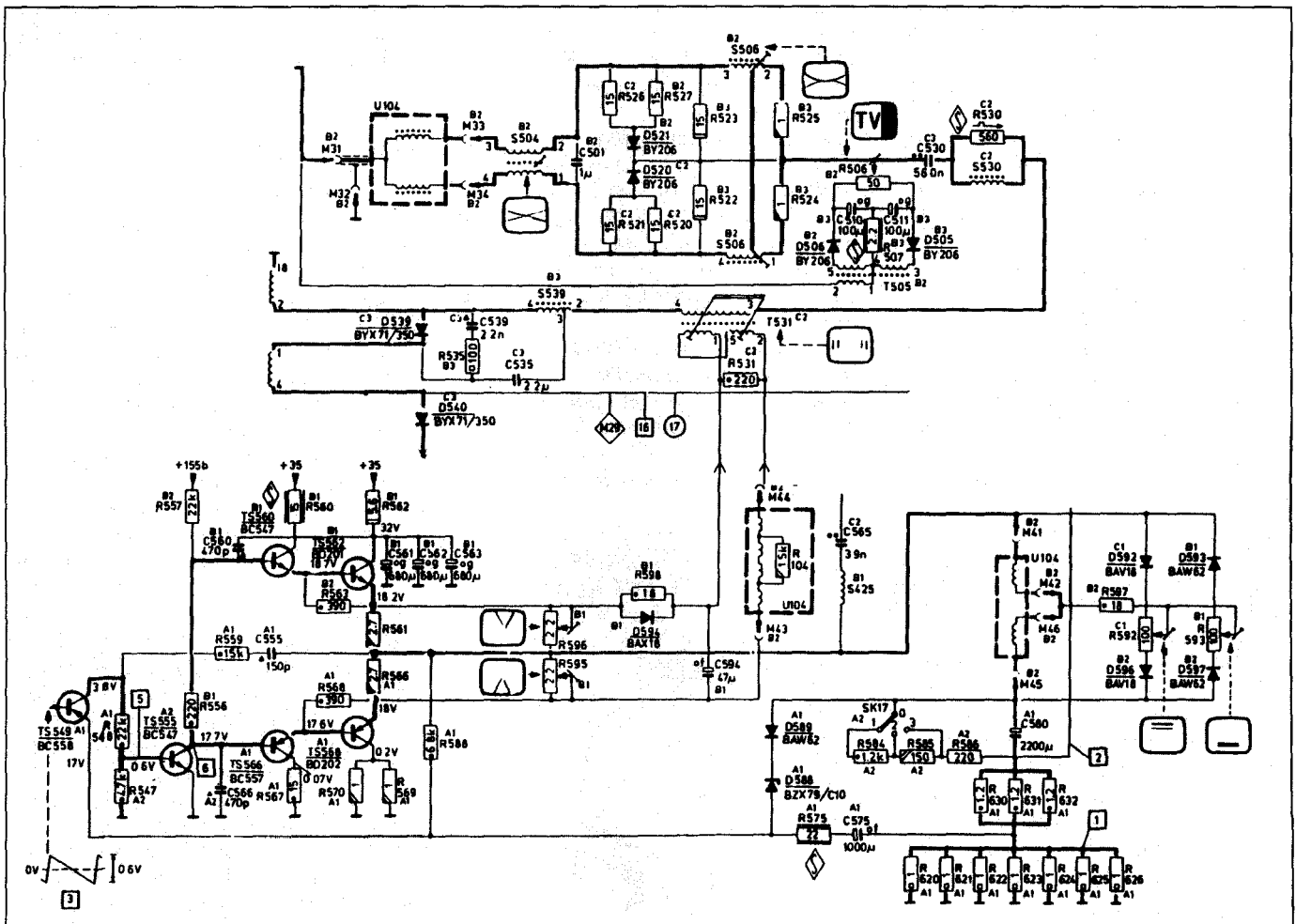I spent an hour and a half today re-discovering a fault that I first spent an hour and a half discovering just over seven years ago. And the frustrating thing about it is that the details were all there all the time on the customer record — I just didn't recognise it.



**An extract from the circuit for a Philips K11 colour TV, showing the vertical sweep circuitry — the area in which our Serviceman finally found the cause of the set's poor height and width, in exactly the same place as it was the last time!**

The set was a Philips model KL257, fitted with a K11A-1 chassis. It was a very early model, released soon after colour TV began in 1975. It was very similar to the K9 chassis, but was never that common in my neck of the woods. I'm much more familiar with the K9, but I've still seen enough of the K11A to be reasonably confident with the circuit.

It's just that these days, I seem to allow myself to get sidetracked by irrelevant symptoms.

The set came in with the complaint that it had a very narrow picture, about three centimetres wide across the centre of the screen. Now, by my interpretation of the word 'narrow', it means 'not wide' and I expected to see a narrow picture, up and down the screen. In turn, this suggests a limited range of causes, mostly centring around an open circuit yoke or dry jointed yoke connections.

When I got the set on the bench and switched on, I was immediately greeted by a blurred horizontal line, stretching about three quarters of the way across the screen. So the problem was really a form of vertical collapse, not horizontal as the client's description had first suggested!

Between the client's phone call and his presentation of the faulty set on my bench, I had had about 45 minutes to consider what might be the problem. In that time, I had more or less convinced myself that it was going to be a horizontal scan problem and had mentally listed all the components that I was going to test. So imagine my chagrin when the set finally arrived and presented a vertical scan problem!

Anyway, I swallowed my disappointment and accepted that the fault was not as the customer initially described it. It wasn't all that difficult to re-align my thinking, to accept the

more accurate description provided by my eyes.

The only problem presented by the set in front of me was that both the height and width were less than normal. The blurred line that I was looking at was only three quarters of the width of the screen. And of course, the height was only seven eighths of the available screen height!

My previous experiences of 'low height' were usually accompanied by normal width, so the present symptoms were confusing to say the least. Then, they were coupled with a very fuzzy image to add yet another symptom to the list. It wasn't easy to decide which one to tackle first!

The easiest to check was the fuzzy pic, since it looked like a focus problem and the focus control was easily accessible. A quick twiddle on the focus pot shaft soon proved that the control wasn't working, and that usually means an

open circuit focus resistor. A common fault, and easy to repair. Now I had a pin-sharp, but still narrow and low picture on screen. One down, two to go...

For some reason I decided that the narrow pic should be the next problem to tackle, on the basis that whatever was causing the lack of width might also be causing the lack of height. In retrospect, I know this was the wrong order of approach, but I had the feeling that I might be looking for a low supply voltage and this could affect both width and height.

So I spent well over half an hour looking for a low or missing voltage.

However, rather than low or missing voltages, all that I found were somewhat *high* voltages. Everywhere, the rails measured some 10% higher than they should have done.

Of course, when you think about it, this is not so unusual. Both the line output and vertical output stages were running at less than full power — so the current drain must have been low, and consequently the voltage was high.

As I said, I spent a lot of time looking for a fault that wasn't there. So I turned to the vertical circuits and began looking for a cause for the low height.

An oscilloscope check proved that there was a healthy sawtooth input at the base of TS549, the first vertical driver transistor. After that the waveform disappeared. With the scope's vertical gain turned right up, there were traces of vertical pulses on the other transistors, but nothing resembling a sawtooth.

All the transistors checked out OK, as did the voltages on bases and emitters; which implied that the transistors were turned on, and that all the relevant resistors were doing their jobs. That left only the capacitors to check, and since I have no faith in electros in vertical circuits, I attacked these items first off.

The vertical amplifier is direct coupled, so there are no electros in the signal path.

However, there are three important caps hanging off the collector of the top output transistor. They are C561, C562 and C563, each of 680uF. These have an important filtering duty on the supply to the output transistors and although it is unusual for all three to fail together, it is not unknown. So out they came and in with three new ones. But all to no avail...

Next, I turned my attention to the deflection yoke, its coupling capacitor C580, and the network of resistors R630/631/632 and R620 to 626 inclu-

sive. The capacitor has been known to fail, so it was removed and thoroughly checked for capacity and leakage. It got a clean bill of health.

The resistors were not so easy to check since their purpose is to form a very low resistance (0.4 ohms in series with 0.142 ohms) voltage divider at the earthy end of the coupling capacitor. As far as I could tell, after allowing for the resistance of the meter leads, the network totalled about half an ohm which looked about right.

Then I realised that I had seen a similar fault in this part of another K11 some time ago. It was also a vertical collapse and was caused by the failure of the two diodes D588 and D589. As I recall, one went short circuit and the other open circuit. Could this be the cause here, I wondered?

The only difficulty in checking the theory was finding the diodes. They are tiny glass encapsulated items, in this case hidden under a thin layer of dust. I eventually found them, but the effort was a waste of time — they were both perfect. So where to now?

At this point I had the first bright idea I'd had all day. I decided to look at the equivalent part of a K9 circuit. If you remember, I said earlier that I have more experience with the K9 and my circuit diagrams are covered with notes about faults I have picked up over the years. And that's where I found the solution.

On the K9 diagram I had drawn a ring about C573 and noted 'No height'. C573 is a 1000uF electro that comes off the K9 equivalent of the resistor network mentioned above. Its purpose is to supply a feedback pulse, via an amplifier, to the input of the vertical stage.

In the K11, the same purpose is served by C575, although this one does not need an amplifier as in the K9. It took longer to find the capacitor (funny how Philips components are never where you'd expect them to be) than it did to remove and test it. But the effort was worthwhile, since its 1000uF had degenerated to something less than 10uF.

A new capacitor cured the 'low height' problem, and at the same time took the picture out to the full width of the screen. The lack of width was probably a result of interaction between horizontal and vertical signals in the pin-cushion correction circuits.

But now we come to the nub of this whole sorry story.

I keep a card index of all my customers, with brief details of each job I

do for them. In this case, as I wrote 'no height, C575 o/c' on the card, my eye caught the figures C575 on the same card, about seven or eight lines higher.

On reading that entry in more detail, I found that I had done this very same job, on this very same set, just seven years and 12 days earlier! When I looked again at the dud capacitor, I saw that it was a different brand to all the others in the set — which seemed to confirm that it had, indeed, been changed sometime earlier.

My excuse for missing the vital clue on the card is that I only keep these records to cover myself during the warranty period. If a customer comes back next week and says "It's broken down again. You didn't fix it properly!", I can refer to exactly what the fault was and what I have done to repair it. After a month or two the information is more or less irrelevant.

So I had no reason to read the card before I tackled the set. It wasn't until I had finished the job that the opportunity arose to see the previous record. Perhaps I'll have to change my habits.

Anyway, my K11 circuit diagram now has a ring around C575 and a note similar to the one on the K9 sheet. Trouble is, I'll probably never again see another K11 in this particular condition!

I mentioned at the beginning that it takes seven years to forget a particular fault. It might also be noted that it takes seven years for an electro to drop dead!

That's all for this month. I have a good selection of stories for next month, so don't go away! ♦

## VIDEO AND TV FAULTS Made Easy

Fault libraries for Australian  
TV & VIDEO'S are available as

Manuals \$165 (inc. postage)  
Inc. both TV & VIDEO


Program for IBM compatibles  
\$160 (inc. postage)

TECHNICAL APPLICATIONS  
P.O. Box 137 KENMORE Q. 4069  
FAX / PHONE (07) 3378 1064

READER INFO NO. 7

# Experimenting with Electronics

by DARREN YATES, B. Sc.

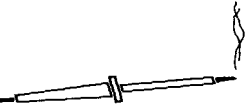

## Too much experimenting is barely enough!

Experimentation is the basis of any advance in circuit design. It's also the basis of our initial understanding as well. This month we answer a reader's query, discuss pulse-width modulation (PWM) and continue on with our look at op amp circuits.

It's always good to hear from readers who are out there experimenting and actually building circuits, and when it comes to experimenting, I like to borrow a well-known phrase from H.G. Nelson: "too much is barely enough". This month, I received a letter from B.F. of Morphett Vale in South Australia, who posed an interesting design question.

Briefly, B.F. wanted to control some 6V globes so that when a switch was flicked on, the globes would brighten up over a period of three to five seconds and when it was flicked off, they'd dim over the same period. I've also had another point raised from a reader who wanted more explanation in the circuits, so I'll try my best to answer both.

B.F. had tried using some AC circuit theory, using zero crossing detectors and other circuits, but found that the project was becoming too complicated. A crude but practical answer to his problems is the circuit shown in Fig.1. It's a low voltage auto-dimmer using some of the switching theory we've covered in previous issues, and it should work quite well.

In answering B.F.'s question, I decided to use this DC-based switching circuit solution rather than trying to control an AC mains-frequency voltage.

While this circuit is primarily designed to control light globes, it could also be used as the basis of an auto-throttle for a model railway layout as well.

AC voltage control is a tricky area which would be difficult to handle in a short answer. While I hope to cover this topic at some stage, to cover it now would require a lot of new territory and topics we haven't covered yet.

Looking at the circuit in Fig.1, it's based around a common LM358 dual

op-amp IC, with IC1a hooked up as a triangle wave oscillator and IC1b as a simple comparator.

Last month, we introduced the circuit of the squarewave oscillator and we're using that same circuit configuration here. What I didn't mention is that there is also a triangle waveform of sorts available from this circuit — provided you're careful. If you connected up a cathode ray oscilloscope — we'll call it a CRO (pronounced 'crow') from now on — across the capacitor, you'll see that you end up with a ramping voltage as the capacitor charges and discharges.

The signal across the capacitor can be used for other circuits, provided you only have a high impedance load connected to it. Using too low an impedance will cause the frequency of the circuit to change, and in extreme cases, stop the circuit from oscillating altogether.

### Droopy, but OK

A perfect triangle waveform has linear or straight edges, but because of the

way this particular circuit works, the peaks of the waveform droop a little. Now the reason for this lies in the way the capacitor is charged up. If we look just at the oscillator in Fig.1, the capacitor is charged and discharged through the output of IC1a via a resistor. Let's consider the capacitor's progress as it charges up.

With the output high, current flows through the 10kΩ resistor and 0.1μF capacitor and it begins to charge up. As it charges up, it develops a voltage across it. And as it develops this voltage, the voltage across the resistor reduces accordingly. Since the resistance is fixed, a drop in voltage causes a drop in current though the resistor and consequently, the capacitor as well. The drop now means that the capacitor doesn't charge up as quickly and the voltage across it rises more slowly, causing a droop in the ramp.

In order for the ramp to be straight or 'linear', the capacitor must charge and discharge with a constant current. As we've just seen, the current isn't con-

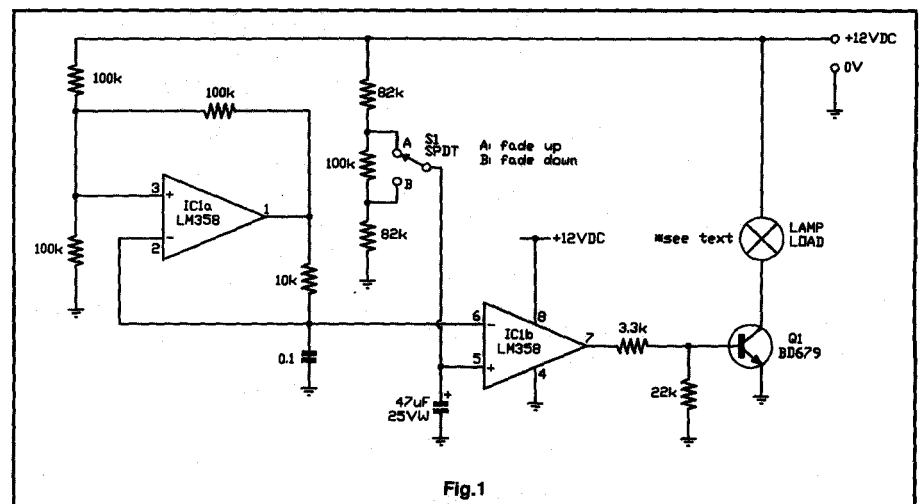


Fig.1

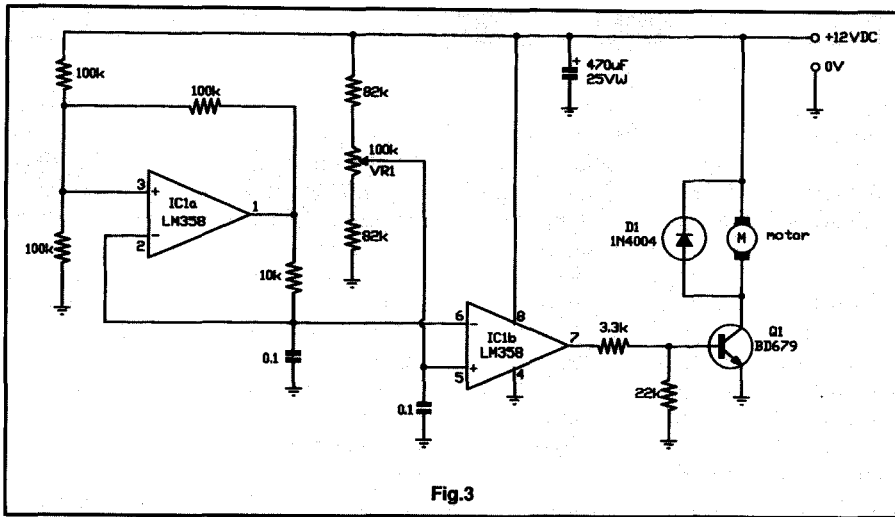


Fig.3

stant, and this happens when it's both charging and discharging, so the output is not linear. But for the purpose of this circuit, which is simply to fade and brighten some lights, it's more than adequate.

In some cases, this imperfect signal may well be 'perfect' for a particular application, so it's worth remembering because it's much cheaper to make than a proper linear ramp generator. However, it must be said that there are applications where linearity is important and we'll look at how to achieve this in a latter issue.

Looking back at Fig.1, the ramp signal from IC1a is connected to the inverting input of IC1b, and this is configured as a comparator. On the other input, we have a simple resistor/capacitor arrangement controlled by a switch. This is a single-pole double-throw (SPDT) switch, which will control the lights. With the switch in the 'A' position, the capacitor charges up and in the 'B' position, the capacitor discharges.

With the way the oscillator is biased, the absolute DC voltage level of the ramp signal is approximately 4V to 8V. The resistor network connected to the switch is designed to ensure that when we want the lamps to fade out, they go fully out and vice versa.

With the switch in position A, the maximum voltage on pin 3 of IC1b is around 8.5V and the minimum in position B is 3.5V. Because these voltages are just outside the range of the ramp signal, IC1b's output will remain fully high and low at these extremities and the lamps fully on or off. But because

they're only just outside, you should still find that you get a fairly smooth fade in and out. The 47µF capacitor with the resistors selected gives a time constant of roughly the correct order of

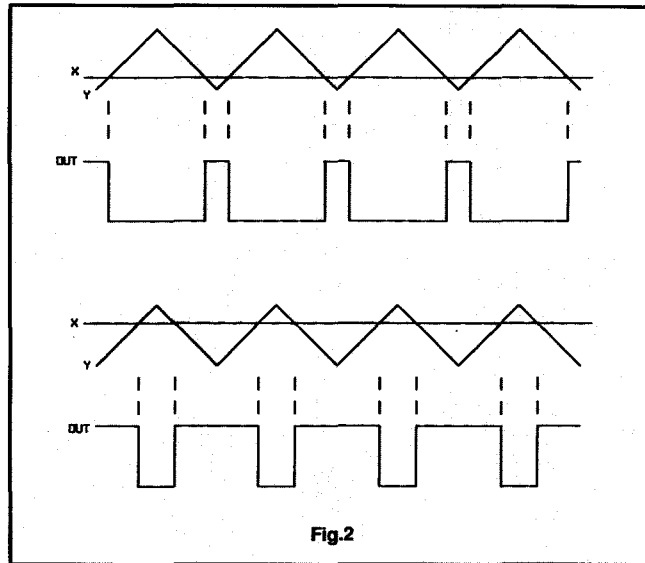


Fig.2

magnitude, producing a delay of around four seconds from lights on to lights off.

Again, we use the imperfect ramping voltage from this capacitor to control the

output of the comparator. And the output we end up with is known as a *pulse-width modulated* or 'PWM' waveform. In practice, this means that if the switch is in position A, the output of IC1b will start from ground, then gradually progress from a narrow positive pulse waveform, move through to a squarewave, to a narrow negative-pulse waveform and finally to a high steady voltage. When the switch is turned off, the same thing will happen but in reverse order.

### How PWM works

Fig.2 shows how this works a little more clearly. Pulse-width modulation is the process whereby a control voltage is used to vary the pulse width of a waveform. It can be a positive response — i.e., a low voltage produces a narrow positive-going pulse and a large voltage a wide positive-going pulse — or it can be negative, i.e. vice versa.

The method we're using, of a triangle waveform fed into a comparator, is one of the simplest and easiest methods to understand. There are other more complicated methods to produce signals with higher degrees of linearity, but they're not needed here.

Let's take a look at how the comparator produces the PWM signal, using the example of where the control signal X on the non-inverting input is a steady but low DC voltage, and the triangle waveform is applied to the other input Y. (Upper graphs in Fig.2.) As the triangle waveform starts out on its rise, the inverting input is lower than the non-inverting input, which forces the output high; but once the ramp output rises above the control input, the output falls low. Over time, the inverting input voltage is high-

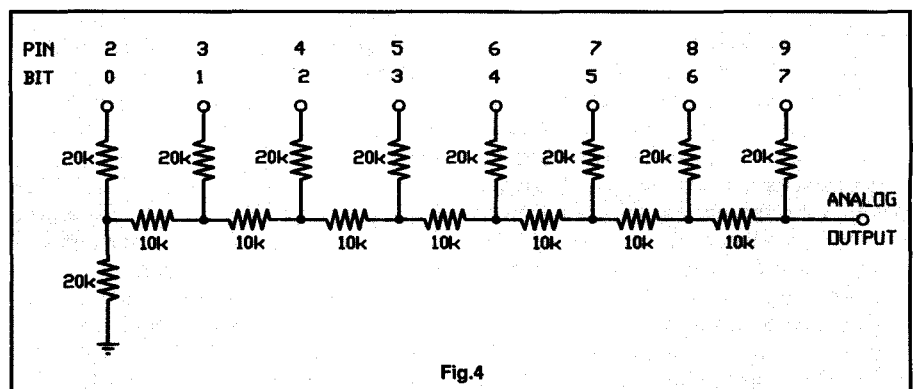


Fig.4

er in magnitude than the other and so the output remains low for a longer period of time.

If we now go to a higher DC voltage on the control input X (lower graphs), the output is now higher for longer than it is low, because the X input is higher in voltage than the Y input for a greater proportion of the time.

Now why use PWM in the first place? Well, it happens to lead in nicely to our current area of exploration; but more importantly, it can be done cheaply as well as wasting as little power as possible.

One important feature with PWM is that the frequency remains fixed — that is, the time of each high-and-low cycle adds up to the same total.

Back to the circuit, the output from IC1b is then fed into the power transistor Q1. Now while this transistor can switch on and off quickly, the light globes have a much slower response and more importantly, our eyes have an even slower response to switching light sources. So much so, that with a frequency of 2kHz our eyes can't see the difference. The globes will produce a dull glow with a low pulse width and a bright glow with a higher pulse width waveform.

The major benefit of using PWM here is that the transistor is simply used as a fast-acting switch. As a result it only has to dissipate relatively low amounts of power. This means that it produces less heat and requires only a small heatsink to keep it happy.

## Drill controller

As I mentioned earlier, PWM is used to control motors as well, and one of the obvious uses is as a drill speed controller. In a previous column, we looked at a transistorised version which used a pot to vary the current ratio in a two-transistor oscillator. We can also use the same circuitry that answered B.F.'s problem to control a motor.

The updated circuit is shown in Fig.3. Note the addition of the protection diode across the motor. This is to protect the

output transistor from the motor's inductive effects. Each time the transistor is switched off, the voltage at the collector can rise to several times higher than the supply voltage. The motor in reality is simply a large coil of wire, which tries to maintain the same energy level once the current though it has been stopped.

This causes the voltage to rise rapidly and without proper protection, this voltage could damage the output transistor. Once the voltage rises to 0.7V above the supply voltage, diode D1 conducts and

frequency control circuitry. Instead, it simply provides a voltage level to the circuit. This may not seem like a big deal, but it enables us to use anything that can generate a voltage to control the circuit. This can include a digital to analog converter driven from just about any computer. You could use, say, the printer port of an IBM PC, convert it to an analog DC voltage and get the computer to control the motor speed.

There are two interesting things to note about this. Firstly, you can use any IBM PC (so dust off that old XT) and secondly, you can use it to control your model railway or just about any motorised circuit.

Digital to analog conversion is a big topic, but by using the parallel printer port, most of the circuitry is already provided. All you need to do is to add a resistor array shown in Fig.4, to convert the 8-bit digital code into a DC voltage.

Later in this series we'll look more closely at the printer port, which provides a rich source of both outputs and inputs for our circuits. It's by far the easiest solution for interfacing circuits with the PC, without having to design special expansion slot boards or worry about blowing up expensive motherboards. We'll also show you some simple BASIC code to program the port.

But for the meantime, this circuit uses what's called an 'R-2R ladder' arrangement, since the resistors to each of

the PC's port pins is twice that of the interconnecting resistors. Each bit provides twice as much voltage as the previous one, with bit 7 providing half the maximum possible DC voltage.

Note also that the switch and 100kΩ resistor have been replaced with a 100kΩ pot which now acts as a speed control. The overall effect is the same as before, ensuring that we obtain both maximum and minimum speeds at the extremes of the control. The 47μF capacitor has also been replaced with a 0.1μF capacitor, which simply removes noise from the control signal.

The main difference between this circuit and the transistor equivalent we published a few issues back is that the control pot is not part of the active fre-

quency control circuitry. Instead, it simply provides a voltage level to the circuit. This may not seem like a big deal, but it enables us to use anything that can generate a voltage to control the circuit. This can include a digital to analog converter driven from just about any computer. You could use, say, the printer port of an IBM PC, convert it to an analog DC voltage and get the computer to control the motor speed.

## Multi-LED display

LEDs are great for giving visual indication of a voltage state, but what if you need to detect different levels? Op-amps, particularly the very-common LM324, make very good comparators and by stringing a few up together we can actually detect five different voltage levels using just four op-amps.

The circuit for the five-LED voltage monitor is shown in Fig.5. This circuit is

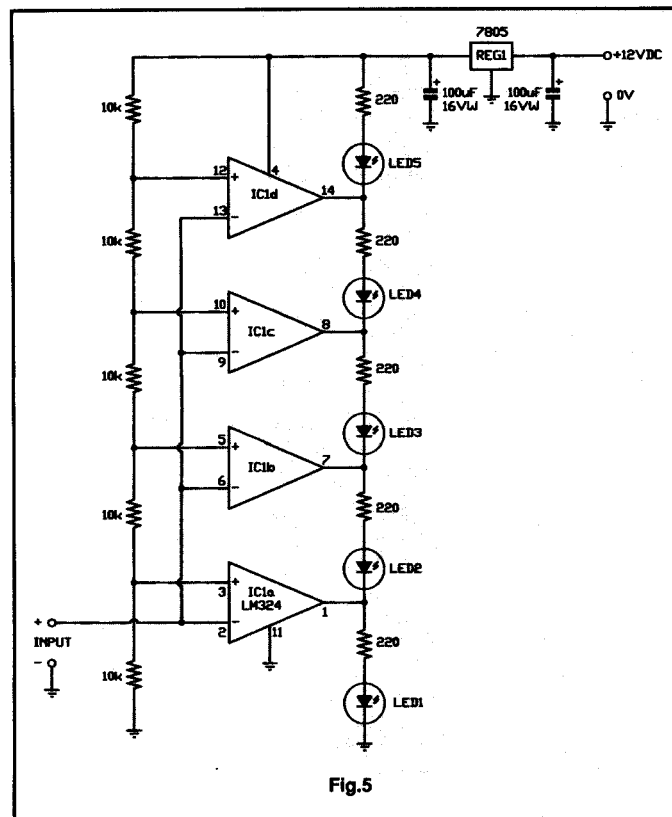


Fig.5



quite convenient to build, since all of the op-amps required come from a single IC package. As you can see, all of the inverting inputs are wired together, giving each input the same look at the input voltage. Their non-inverting inputs are distributed along a resistor divider chain made up of five 10kΩ resistors, with the top of the chain connected to the output of a 5V regulator.

Using a bit of mathematics, you can deduce that each junction is 1V higher up the ladder i.e., IC1a sits at 1V, IC1b at 2V, IC1c 3V and IC1d at 4V. The outputs are each connected head-to-tail with a 220Ω current limiting resistor and a red LED. Let's run through it and see how it works.

With the input voltage less than 1V, the inverting input of IC1a is lower than the inverting input so the output is high. But it's also lower for the three remaining op-amps, so their outputs are high too. This means that only LED1 has a voltage across it, so it alone lights up.

As the input voltage rises to between 1 and 2 volts, the inverting input of IC1a is now higher than its non-inverting input so the output of IC1a falls low and LED1 turns off. The other three op-amps still have the non-inverting input higher than the input voltage so their outputs remain high.

But now we have a voltage difference between the output of IC1b and IC1a, which lights LED2. Note that the current flow is out from IC1b to the output of IC1a. Because the output voltage of IC1a is near ground, it's a low-impedance path to ground which can take the current from the LED.

Hopefully you can see that this process continues up the chain until finally the input voltage rises above 4V. At this point, all of the outputs are low since the input voltage is higher than all of the resistor tap-off points. But now the last LED switches on, because of the voltage difference between the supply rail and the low output of IC1d.

There are a couple of benefits to this circuit. Firstly, we can show five states with only four op-amps; secondly, only one LED is on at any one time and thirdly, because only one LED is on, the current consumption is lower than a parallel LED configuration, where all LED cathodes are connected to ground.

Note that since all resistors in the chain are equal in value, each LED represents a linear progression — i.e., equal steps of 1V. By changing the resistor values, you can also change the type of progression you get as well as determine at which voltage points the LEDs swap

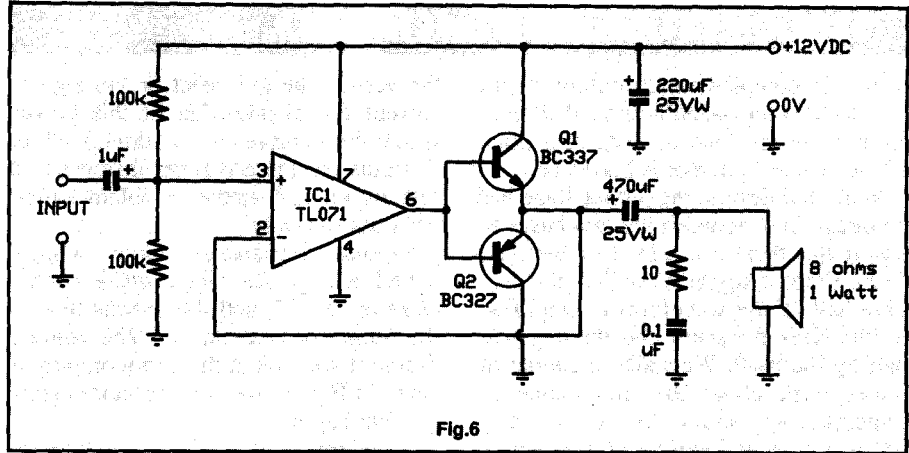


Fig.6

from one to the other. Too much experimenting...

### Simple audio amp

Some op-amps also have the makings for some tiny but useful audio power amplifiers. Some — not all. While op-amps can be used as both comparators and op-amps, comparators can only be used for comparators. So don't connect up an LM339 or LM393 as an audio amplifier and expect it to work terribly well.

There are also some other op-amps that don't make very good amplifiers and a couple of these are the LM358 dual op-amp IC and its quad cousin, the LM324. These two devices suffer from crossover distortion unless you connect up a fairly heavy load to them. With such a load (around 600 ohms) the op-amp internally switches from Class B (which creates the distortion) to Class A, which has much less distortion but you use up quite a bit more current in the process.

Be that as it may, there are plenty of

low cost op-amps which are suitable. Good examples are any of the TL07X range, and National Semiconductor's LF347/351/353 types.

Fig.6 shows a simple audio amplifier which uses the bare minimum of components but can still thump a watt into an 8Ω load at 12V. The most interesting thing about this amplifier is that both bases of the output transistors are tied together. Now normally this would result in enough crossover distortion to make anything sound like 'heavy metal' music(?) — but in this circuit the output transistors are connected up as part of the negative feedback loop.

By using this technique, the crossover distortion is reduced by a factor equal to the open loop gain of the op-amp. Since the open loop gain of most op-amps is in the order of 10,000 and up, the crossover distortion becomes tiny indeed.

### Crossover distortion

For those who haven't come across this term before, crossover distortion

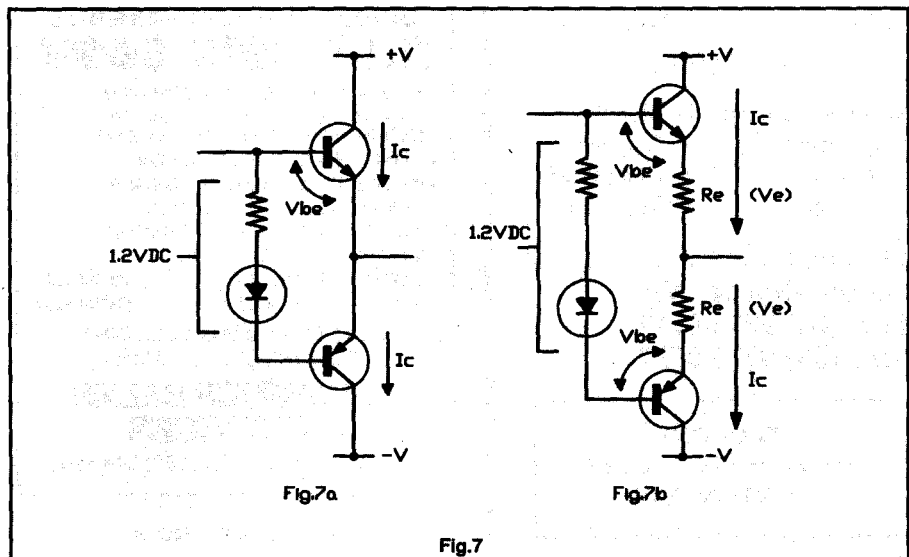


Fig.7

## EXPERIMENTING WITH ELECTRONICS

occurs in complementary output stages (i.e., those where an NPN and a PNP transistor drive the loudspeaker), at a point where neither transistor is biased on.

In normal design, the output stage has a voltage bias between the two bases to ensure that there is a 1.2V drop between them. When a signal is applied, the positive half of the waveform is amplified by the NPN transistor and the negative half by the PNP. We spoke a couple of issues back about the importance of remembering about the 0.6V drop between base and emitter of a transistor — and this is one of those times. You can almost think of it as an offset that we must overcome before we produce any output signal.

When the waveform is at its peaks, both positive and negative, we're alright — the transistors are switched on pretty hard and the signal is amplified. But in the grey area around the halfway-mark, we can run into crossover distortion.

This occurs when there is insufficient bias current to turn on either transistor, as the signal swings or 'crosses over' from one half of its waveform to the other. When you consider the 0.6V drop across both transistors, there is a region of 1.2V where we get no output signal regardless of what the input signal is doing.

In most amplifiers, this is taken care of by setting up a fixed 1.2V drop between the bases so that they're always just on the verge of conducting. (By 'on

the verge', the quiescent or 'no signal' current for an amplifier of this power should be no more than 8-10mA.) While this cuts out the crossover distortion, it sets us up for another problem called 'thermal runaway'.

Bipolar transistors have what's called a *negative temperature coefficient* or 'NTC', and this means that as the transistor heats up, its Vbe voltage drops. If we look at the common output stage in Fig.7a, we can see more clearly what happens.

If we apply too much bias voltage at the bases, the transistors are conducting continuously. This causes the transistor to heat up.

The heat build-up causes the transistors to conduct a little more current, because of the way their Vbe's fall. This produces a little more heat and a little more current and then before you know it, wafts of smoke are gently climbing from the charred remains...

Fig.7b shows the simple remedy — two low value resistors 'Re'. By including these in the emitter legs of each side, we all but remove the problem. Here's how it works.

As the transistor heats up, the Vbe drops and it begins to conduct more current; but now we have the resistors in place, we now have an extra voltage drop across them. This pushes the emitter voltage up.

As the base voltage remains the same, the transistor shuts down slightly, cool-

ing the transistor down and dropping the current. The drop in current also drops the voltage across the resistors. This allows the transistors to turn on a little more.

All this happens quite quickly, and the circuit reaches an equilibrium state where there is sufficient current flowing but not too much.

Now while all that is interesting and very important, if we go back to our amplifier of Fig.6 based on an op-amp, it's all done automatically. The op-amp sets up the biasing needs of the output stage so that the crossover distortion is reduced to just about nothing, as well as taking care of the thermal runaway problem. This makes this circuit one of the more difficult to blow up, and its tiny component count makes it nice and quick to build.

Hopefully some readers will remember that the four-transistor amplifier we presented some months back didn't use these protection resistors. That's because if you keep the base voltage drop between the two transistors to less than 1.2V, and you can ensure that the supply voltage doesn't rise above the stated level, you can get away without them. But it's a bit like walking a tight rope without the safety net below...

Next month, we'll continue with some more op-amp circuits. ♦

(Darren Yates is Chief Engineering Officer with R.A.T. Electronics, of PO Box 641, Penrith NSW 2750.)

### LINK TECHNOLOGIES ELECTRONIC COMPONENT BROKERS

#### SHOWROOM NOW OPEN TO PUBLIC

- Semiconductors    ■ Modules
- Capacitors        ■ Displays
- Relays             ■ Connectors
- Sensors            ■ Resistors

548 Frankston Dandenong Rd  
Carrum Downs VIC 3201  
Tel: (03) 9775 0717  
Fax: (03) 9775 0727

**WANTED**  
SURPLUS ELECTRONIC  
COMPONENTS

READER INFO NO. 8

## VIDEO SURVEILLANCE D.I.Y. SETS \$699

- SENSOR INPUTS & AUDIBLE ALARM
  - SENSOR VIDEO TRACING FUNCTION
  - EXPANDABLE UP TO FOUR CAMERAS
  - 10 INCH HI-RESOLUTION SCREEN
  - INTEL MICROPROCESSOR CONTROL
  - VCR VID/AUDIO INPUT OUTPUT
  - TWO WAY AUDIO COMMUNICATION
  - SINGLE 5mm PLUG IN CABLE
- ADDITIONAL CAMERAS            FROM \$225  
TINY CAMERA MODULES        FROM \$159

CIRCLE CARD FOR FULL INFO  
(DISCOUNTS UP TO 37.5%)

### ALL THINGS SALES & SERVICES

Ph (09) 349 9413 Fax: (09) 344 5905

READER INFO NO. 9

### Construction Plans and Rotor Magnet Kits Shipped Worldwide Since 1987



Don't let the experts rule your life — build your own brushless, low revving power generator — from scratch! Let's be realistic, unless you own a slave, the only way to get a long-lasting generator for a windmill, water turbine or steam engine with a decent output at low revs, without costing a small fortune, is to build it yourself.

Contact Al Forbes, Ph: 64 9 818 8967  
anytime, Fax 64 9 818 8890 or Todd-Forbes  
Publishing, PO Box 3919, Auckland, New  
Zealand, for a free brochure on the  
Homebuilt Dynamo.

READER INFO NO. 10

# SEMICONDUCTOR DEVICE DATA ON A CD-ROM

Hinton Information Services now has available the D.A.T.A Parametric Access Library, a CD-ROM version of D.A.T.A.'s comprehensive database of integrated and discrete semiconductor devices. It's designed to meet the needs of designers, purchasing officers, and repair and maintenance technicians.

On a single CD-ROM disc, the new D.A.T.A. Parametric Access Library lists and provides data for over 1.25 million active and discontinued ICs and discrete semiconductor devices, from more than 1000 different manufacturers. The database on the disc provides part numbers, generic numbers, manufacturers, distributors, pinout connections and package outline in addition to function, fabrication technology, supply voltage and parameters such as maximum frequency, propagation delay, temperature range, etc.

For discrete devices there are four database categories: diodes, transistors, thyristors and optoelectronics. According to the manufacturer there's data on over 380,000 diodes; 232,000 transistors; 145,000 thyristors and 92,000 optoelectronic devices.

Similarly there are six categories for IC's: linear, digital, interface, memory, microprocessors and programmable logic. Again there's said to be data on over 60,000 linear devices; 85,000 digital devices; 69,000 interface devices; 107,000 memory devices; 31,000 microprocessors and 11,000 programmable logic devices.

In addition to providing current device information, the system also covers discontinued devices dating back to 1956 — which should make it very useful for repair and upgrade operations. Over 1100 manufacturers are listed, both active and inactive.

The CD-ROM is accompanied by software on a 3.5" or 5.25" floppy disk, to provide fast and convenient searching of the database by generic type number, specific part number, device category, function, manufacturer or distributor. There's also a 'quick inquiry' mode, and searching can be refined by using up to 25 specific parameter values. Some search modes also allow 'wild card' or 'starts with' searching.

Although most of the information in the database appears to be in alphanumeric form, the device package outlines

are in high resolution graphics images. Search results are displayed in 'browseable spreadsheet' format, and allow you to highlight devices meeting selected criteria.

Other features of the D.A.T.A. P/A/L disc include utilities to allow the user to customise the screen colours, set the program up to suit a particular printer, and optimise settings.

Hardware requirements are DOS 3.1 or higher, 2MB of RAM, 5MB of free hard disk space and a CD-ROM drive. A 486 or better processor is recommended. Although intended for use on a single PC, the software is optionally available in a form compatible with any PC LAN and the database can apparently be installed on a network server CD-ROM providing the network has CD-ROM management software.


The Parametric Access Library CD-ROM is sold as an annual subscription, where the annual subscription covers

one disc and is currently priced at \$1500. When your subscription has ended, the software apparently flashes a message on your screen to remind you that renewal is due.

According to the manufacturer, 'if you choose not to renew, your D.A.T.A. P/A/L will eventually discontinue itself'. It's unclear whether this means that superseded discs cannot be used for reference to data on discontinued devices, or that the database merely becomes obsolete with the passage of time.

Purchase of a subscription to the CD-ROM also entitles the user to order hard copies of manufacturers' data sheets, for a price of \$12 per data sheet up to 10 pages, and \$1 per page thereafter.

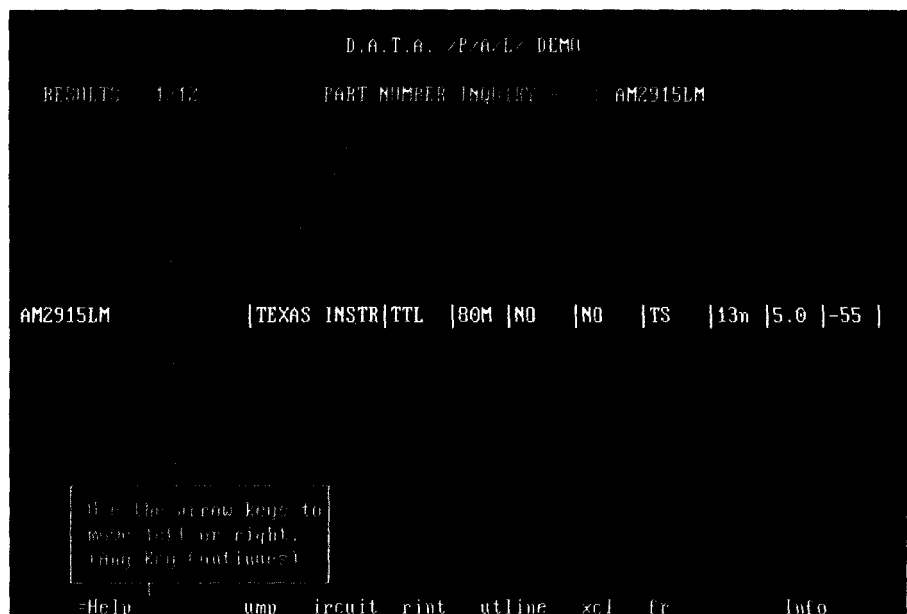Further information on the D.A.T.A. Parametric Access Library is available from Hinton Information Services, Locked Bag 7, Eastwood 2122; phone (02) 804 6022 or fax (02) 804 7434. ♦



**This screen dump from a demonstration version of the D.A.T.A. Parametric Access Library gives a good idea of the 'browseable spreadsheet' format used by the software to display device data.**

# DICK SMITH ELECTRONICS

## All You Need Is Right Here!

**NEW**


**Range  
Of Knobs  
in a variety  
of colours**



- Cat P-7126 15mm Push Fit Miniature Knob, Black \$0.85
- Cat P-7130 16mm Push Fit Miniature Knob, Red \$1.00
- Cat P-7132 16mm Push Fit Miniature Knob, Green \$1.00
- Cat P-7134 16mm Push Fit Miniature Knob, Yellow \$1.00
- Cat P-7136 16mm Push Fit Miniature Knob, White \$1.00
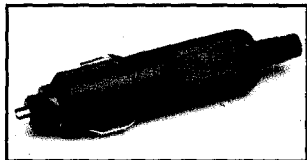
### Lighter Socket Plug

With in-built fuseholder, 5A fuse and "Power On" LED indicator.  
**\$395**  
Cat P-1684



### Universal Camcorder Charger

Power supply and battery refresher suits most 8mm and VHS-C video cameras. Specially designed to safely recharge your camcorder batteries. Operates from car cigarette lighter socket or optional AC/DC adaptor. Refresh function provides 100% full charge. Normal and quick charge facilities.  
Cat M-9499

**\$3995**


**SCOOP  
PURCHASE!**



**HURRY LIMITED STOCKS!**

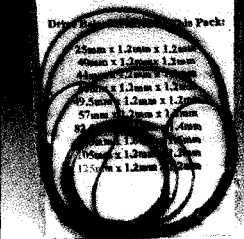**NEW**

**Assorted Audio Drive Belts  
Pkt 10**  
ELECTRONIC PARTS FOR THE  
PROFESSIONAL & ENTHUSIAST



**Audio Drive Belts  
Comes in  
packs of 10  
Assorted sizes**

- Sizes include:
- 25mm x 1.2mm x 1.2mm
  - 40mm x 1.2mm x 1.2mm
  - 44mm x 1.2mm x 1.2mm
  - 46mm x 1.2mm x 1.2mm
  - 49.5mm x 1.2mm x 1.2mm
  - 57mm x 1.2mm x 1.2mm
  - 82.5mm x 1.4mm x 1.4mm
  - 100mm x 1.6mm x 1.6mm
  - 105mm x 1.2mm x 1.2mm
  - 125mm x 1.2mm x 1.2mm

Cat H-6015

**\$495**

### Motorised Potentiometer


50k ohms log.  
Dual ganged.

Note: Pot is supplied with spline shaft and not straight solid shaft as illustrated.

Cat R-7830

**\$1895**

**NEW**

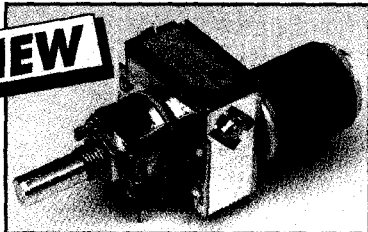

### Pressure Mat


Great as a customer warning in shops, or general home security, this pressure mat is almost impossible to detect under carpets or rugs. When an intruder steps on it, it triggers the alarm. With N.O. (Normally Open) contacts, it suits most systems.

Cat L-5270

**\$2695**

**NOW AVAILABLE**

**NOW AVAILABLE**

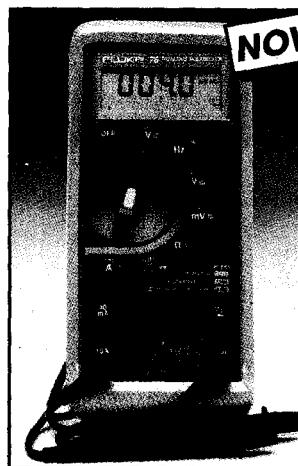

### Fluke 76 True RMS DMM

This true-RMS Digital Multimeter is ideal for detecting peaking, nulling or trending with its fast, 63-segment analog bar graph, 4000-count digital display and 40 times per second update rate - as fast as the eye can see. Also, the frequency counter shows frequency while simultaneously showing AC voltage levels on the analog bar graph! Other great features include 10A, 40mA, TouchHold, Audible Continuity/Diode Test and Auto Range/Range Hold.

Cat Q-1608

**FLUKE**

**\$479**

On display at the following stores:

• York Street • Cannington • Brisbane City • Adelaide City • Bourke Street • Darwin • North Ryde • Hobart

May also be ordered from your nearest Dick Smith Electronics Store

**Don't forget your  
copy of BENCHMARK!  
Now available FREE  
in your nearest store.**

# Try Your Hand At These!

## DISCOVERY SERIES




**NEW**

### Four Channel Infrared Remote Control

Build your own handy infrared remote control! It includes a small transmitter that can be constructed to fit in your hand, and a receiver with five outputs, all of which can directly drive relays. Both the transmitter and receiver have a selectable security code to prevent false triggering and operation by other transmitters. Kit comes complete with all components and PCBs which are solder masked and silk screened.

Cat K-2810

**\$3995**

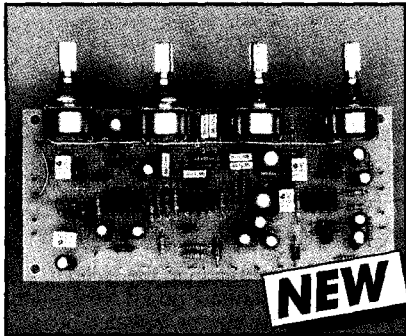

**NEW**

### Stereo Pre-Amp

This compact high quality module makes it possible to upgrade your bare power amplifiers into a complete audio system by adding volume, bass, treble and balance controls. The circuit is stereo with an extra input to both channels that can be used for either multi-channel mixing or gain control applications. Supplied with components, hardware and silk-screened, solder masked PCB.

Cat K-2811



**\$3450**

### With Bonus! DSE Soldering Station

Make a permanent and reliable connection! Features a fully variable temperature control from around 200 degrees to 500 degrees Celsius. With temperature meter and is approved by the Energy Authority. Comes complete with a lightweight iron fitted with a silicon non-burning cable, iron holder and cleaning sponge.

Cat T-2000

**\$159**

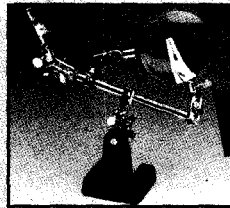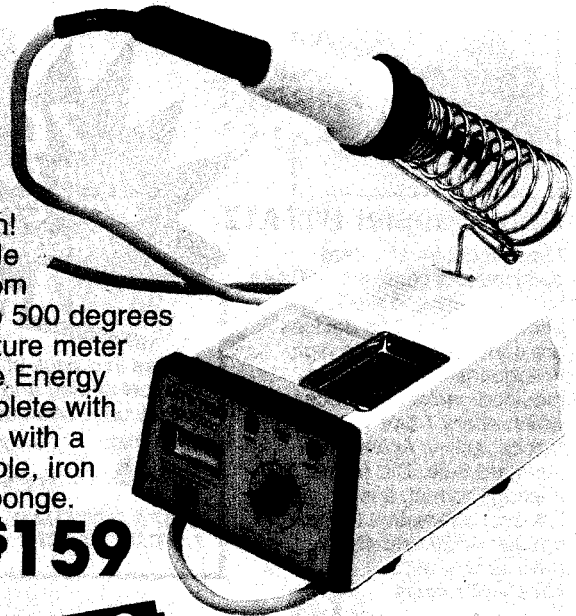

**BONUS**

### Helping Hands With Magnifier

Makes working on PCBs much easier!

Cat T-5715



### Hobby Tool Kit 28 Pcs With Case

A convenient collection of tools complete with a foam-lined plastic storage case. Includes 9-piece Hex Nut drivers and quality reversible ratchet handle, 6-piece Jewellers screwdrivers, sidecutters, pliers, plus 10-piece assorted screwdriver bits.

Cat T-4610

**\$2995**

**SAVE \$10**

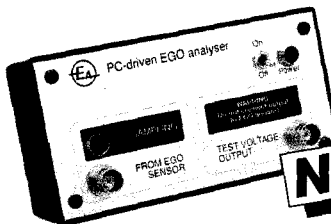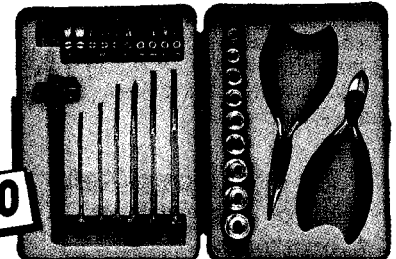

**NEW**

### PC Driven EGO Analyser

This low-cost analyser is designed to monitor your car's engine performance by examining the Exhaust Gas Oxygen sensor (EGO sensor) directly. Supplied with software, the results will be displayed on your PC. Project is complete with all components, hardware, PCB, pre-punched silk-screened front panel, case and software.

Cat K-4214

**EA** Jan '96

**\$4995**

### ESR & Low OHM Meter

Measures the equivalent series resistance (ESR) which is often difficult to check with capacitance meters, so if you need to measure very low values of resistance, this project can save you lots of time and aggravation. Kit is supplied with all components, hardware, PCB, case and pre-punched silk-screened front panel.

Cat K-7204

**\$5995**

**NEW**

**EA** Jan '96



Availability: Our kits consist of many different parts from numerous suppliers. Whilst we have consulted closely with them and are satisfied with their ability to supply, sometimes problems can arise in obtaining all of the parts. This means there is a slight chance that availability may be delayed. Rainchecks are available, however, if you'd like to check beforehand, don't hesitate to contact your local store.

# Put These To Use!



**SCOOP PURCHASE!**

## Opto-Coupler H11A1Z

These industry-standard optoisolators consist of a GaAs Infrared LED and a silicon phototransistor. The devices are constructed with a high voltage insulation, double-moulded packaging process which offers 7.5kV withstand test capability. Available in standard 6-pin DIL plastic package format, it is a low-cost alternative to the popular 4N28 and 4N25 devices in a wide variety of circuits.

Cat Z-4810

**\$125**

## 12VDC Lighter Socket Extension Lead

This will be handy! With in-built fuseholder, 5A fuse, safety "Power On" LED indicator, dust & moisture-proof socket cap. Also includes 1-metre coiled cable that extends to approximately 2.8 metres.

Cat P-1681



**NEW**

**\$12.95**

## 1.25 GHz Hand-Held Digital Frequency Counter

Ideal for measuring radio frequency transmissions and servicing stereos, videos, computers and cordless phones. This incredibly easy-to-use 10Hz to 1.25 GHz frequency counter has an 8-digit LCD display, data hold, relative management and data record (min, max & average). There's also selectable resolution, period measurement and more. Comes complete with telescopic antenna and BNC to alligator-clip test leads.

Cat Q-1322

**\$199**



**SAVE \$50**

**70% Less Than Regular 1/4 Watt Carbon Film Resistor Prices**

**NEW**


## 1/4 WATT CARBON FILM RESISTORS

Comes in a pack of 300+. Mixed values. With preformed and precut leads - the extra work's been done for you!

Cat R-7022

**\$445**

**THAT'S LESS THAN 1.5 CENTS EACH!**

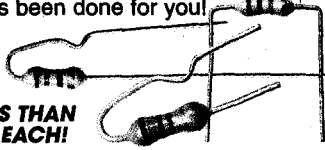


**NEW**

## Miniature Toggle Switch

DP3T, 240V 2A. Momentary both sides, centre off. With blue toggle cap.

Cat P-7689

**\$4.95**

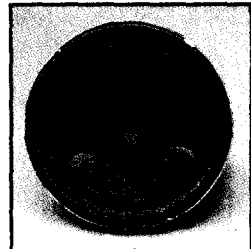

**SCOOP PURCHASE!**

## Mini Speaker

At 8 Ohm and 0.2 W, it's just 38 mm.

Cat C-2209

**\$1.95**



**NEW**

## Apple Night Eyes Night Viewer

Designed for terrain urban viewing and orientation in the twilight, the Apple Nighteyes can be used by tourists, hunters, guard services for sea navigation and other tasks at night. The viewer makes it possible to observe in the natural night-sky background light as well as in the moon and stella light. Complete with a removable laser illuminator allows observation in total darkness. Also comes with soft carry case and shoulder strap. Nighteyes uses 2 x "AA"-batteries.

Cat L-8150

**12 MONTH WARRANTY \$999**

Available in selected stores only.

May be ordered if unavailable at your store.

### MAJOR DICK SMITH ELECTRONICS AUTHORISED STOCKISTS:


NSW: •Batemans Bay 725 030 •Bathurst 323 933 •Bowral 611 861 •Broken Hill 884 098 •Cootamundra 422 561 •Deniliquin 813 672 •Dubbo 828 711 •Goulburn 221 288 •Grafton 421 911 •Griffith 624 534 •Kempsey 631 134 •Leeton 532 800 •Moree 522 091 •Mudgee 723 895 •Murwillumbah 723 684 •Parkes 623 366 •Richmond 784 101 •Tuncurry 545 006 •Windsor 776 722 •Young 821 279 VIC: •Ararat 522 345 •Bairnsdale 525 677 •Benalla 622 710 •Colac 312 847 •Echuca 822 956 •Hamilton 72 2865 •Horsham 824 680 •Morwell 339 458 •Rosebud 822 225 •Shepparton 219 497 •Swan Hill 329 303 •Warragul 234 255 •Warrnambool 615 111 •Wonthaggi 721 411 QLD: •Ayr 831 566 •Boonah (0754) 632 606 •Bundaberg 521 785 •Caloundra (0754) 918 533 •Gympie (0754) 836 677 •Ingham 763 188 •Innisfail 612 014 •Kingaroy 625 777 •Mackay 511 723 •Maryborough 214 559 •Mossman 982 200 •Mt. Isa 433 475 •Pialba 283 749 TAS: Burnie 319 222 •Devonport 248 322 SA: •Whyalla 454 764 WA: •Albany 412 077 •Bunbury 216 222 •Busselton 542 991 •Geraldton 211 278 •Mandurah 581 4940 •Margaret River 573 888  
Stores Across Australia & New Zealand

# Time To Stock Up!

## WIA HAM Radio Callbook 1996

Lists call signs, names and address information for all the licensed amateur radio operators in Australia.  
Cat B-2338

**\$15**

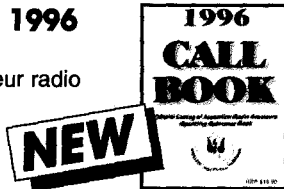

**NEW**

## Packet: Speed, More Speed & Applications

For packet enthusiasts interested in medium to high speed packet systems or applications that go beyond BBSs and Packet Cluster. Includes projects, special topics & references.  
Cat B-2410

**\$26<sup>95</sup>**

**NEW**



## Free Keyboard Template Microsoft Office Short Cuts Pack

All the Short Cuts Guide Books to the Microsoft Office program, plus a **FREE** keyboard template to Microsoft Office. Great for those who need memory joggers.  
Cat B-8130

**\$29<sup>95</sup>**

**NEW**



## Passport To Worldband Radio, 1996

What's on shortwave radio, the best and worst radios, how to get the most from your shortwave radio and more!  
Cat B-2057

**\$34<sup>95</sup>**

**NEW**



## Antennas & Techniques For Low-Band DXing

An in-depth treatment of antennas and operating strategies you need to span the continents on 40, 80 and 160 meters. Operating tips, antenna designs and software.  
Cat B-2110

**\$39<sup>95</sup>**

**NEW**



## Troubleshooting And Repairing VCRs 3rd Edition

With step-by-step details on home VCR maintenance and troubleshooting power supplies and logic circuitry problems.  
Cat B-1640

**\$54<sup>95</sup>**

**NEW**



## With CD-ROM Upgrading & Repairing PCs 5th Edition

Scott Mueller's latest updated work is now more comprehensive than ever. It covers the Pentium Family and Intel Licensed processors. Contains a CD-ROM with a wealth of helpful information.  
Cat B-6189

**\$79<sup>95</sup>**

**NEW**



## Precision Knife Set

This 13-piece Precision Knife Set comes with three quality (varying size) knife handles and 10 spare blades in a variety of shapes and sizes. Comes in a handy plastic storage case.  
Cat T-3618

**SAVE \$4**

**\$12<sup>95</sup>**



## Transformer 7.5 - 42.5 V @ 60 VA

Power Rating: 60VA  
Output Windings: 0 - 10 - 17.5V @ 1.4A  
0 - 17.5V @ 1.4V  
0 - 7.5V @ 1.4A  
Terminations: Solder lugs  
Dimensions: 65(h) x 79(w) x 70(d)mm



**\$19<sup>50</sup>**

**SAVE 30%**

Cat M-6676



**This magazine is now on sale at all of our New Zealand stores!**

## PHONE, FAX & MAILORDER SERVICE

**AUSTRALIA: Outside Sydney: FREE Call (1800) 263 922  
Sydney and Enquiries - (02) 9937 3366**

**Fax: (02) 805 1986 or write to**

Dick Smith Electronics, Mail Orders, Reply Paid 160  
PO Box 321 NORTH RYDE NSW 2113

**NEW ZEALAND: Phone: (09) 480 8049 or (09) 480 3331**

**Fax: (0800) 800 290 or write to**

Dick Smith Electronics, Mail Orders Division, Private Bag 102-903  
North Shore Mail Centre, Auckland

All major Credit Cards accepted. Overnight Courier Available.

NSW • Albury 21 8399 • Bankstown Square 707 4888 • Blacktown 671 7722 • Bondi 387 1444 • Brookvale 9905 0441 • Burwood 744 7299 • Campbelltown 27 2199 • Chatswood 411 1955 • Chullora 642 8922 • Gore Hill 439 5311 • Gosford 25 0235 • Hornsby 477 6633 • Hurstville 580 8622 • Kotara 56 2092 • Liverpool 600 9888 • Maitland 33 7866 • Miranda 525 2722 • Newcastle 61 1896 • North Ryde 9937 3355 • North Sydney (Greenwood Plaza) 9964 9468 • Orange 618 400 • Parramatta 689 2188 • Railway Square 211 3777 • Penrith (047) 32 3400 • Sydney City York St 267 9111 & Mid City Centre 221 0000 • Tamworth 66 1711 • Wollongong 28 3800 ACT • Belconnen (06) 253 1785 • Fyshwick 280 4944 VIC • Ballarat 31 5433 • Bendigo 43 0388 • Box Hill 9890 0699 • Coburg 9383 4455 • Dandenong 9794 9377 • East Brighton 9592 2366 • Essendon 9379 7444 • Frankston 9783 9144 • Geelong 232 711 • Highpoint 9318 6300 • Melbourne City Strand Central Arcade 9663 5320 & 246 Bourke St 9639 0396 • Richmond 9428 1614 • Ringwood 9879 5338 • Springvale 9547 0522 QLD • Alderley 3356 3733 • Booval 3282 6200 • Brisbane City 3229 9377 • Buranda 3391 6233 • Cairns 311 515 • Capalaba 3245 2870 • Cherside 3359 6255 • Indooroopilly 3878 4944 • Maroochydore 791 800 • Mermaid Beach 5578 5600 • Rockhampton 27 9644 • Southport 5532 9863 • Toowoomba 38 4300 • Townsville 72 5722 • Underwood 3341 0844 SA • Adelaide City Pulteney St 232 1200 & Myer Centre 231 7775 • Elizabeth 255 6099 • Enfield 260 6088 • St Marys 277 8977 • Westlakes 235 1244 WA • Balcatta 240 1911 • Cannington 451 8666 • Fremantle 335 9733 • Perth City 481 3261 • Midland 250 1460 • Northbridge 328 6944 TAS • Glenorchy 732 176 • Hobart 31 0800 • Launceston 344 555 NT • Darwin 81 1977

\* STORES IN RED ARE OPEN SUNDAYS. STORES ACROSS AUSTRALIA AND NEW ZEALAND

# Circuit & Design Ideas

Interesting circuit ideas from readers and technical literature. While this material has been checked as far as possible for feasibility, the circuits have not been built and tested by us. We therefore cannot accept responsibility, enter into correspondence or provide further information.


## Protected 50Ω pad, 50dB pad

When working with communications transceivers, it's usual to connect a 6dB 50Ω pad between a signal generator and the receiver. This ensures both pieces of equipment see a termination of 50 ohms, which might not otherwise be the case.

There are a number of possible configurations for a 50Ω pad, but I've found those shown here to be the most useful. A special advantage of these circuits is that 100mA fuses come in two types, which happen to have a resistance of 16Ω or 36Ω. Using these in the circuits gives protection as well as the right resistance.

For HF transceivers it is sometimes convenient to use a 50dB pad to give an output point as a convenient means of monitoring — for instance, with an oscilloscope for a two-tone envelope check, or with a frequency counter to measure frequency. As well, it's possible to feed a signal from a signal generator into the receiver with no fear of damage should the transmitter be keyed.

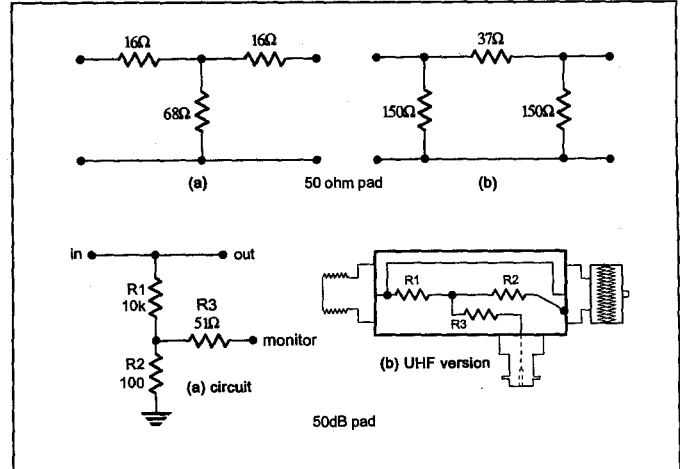The pad I use for this is shown in the circuit, along with a simple way to build it. The case is the smallest diecast box available, with a male and a female panel mount connector on



the ends. Two 100Ω resistors in parallel will do if you can't get a 51Ω resistor.

David Jackson  
Papua, New Guinea.


\$35

## Simple logic probe

This simple logic probe can detect low, high and floating logic levels, single short pulses and pulse trains. When the probe is connected to a logic 0, transistor Q1 is off and LED2 is also off. If the probe tip is connected to an open-circuit (floating), the small current from pin 4 of IC1 will keep the transistor on slightly, causing LED2 to glow dimly. A logic 1 at the probe will cause enough base current to make Q1 turn on fully, lighting LED2 to full brightness.

LED1 is on only when the monostable of IC1 is triggered, which occurs with a negative-going pulse (logic 1 to logic 0) at pin 4. For a single pulse, there is only one transition and therefore one flash from LED1. A pulse train will continually retrigger the monostable and the LED will keep flashing. The brightness of LED1 will increase with the frequency of the pulse train.

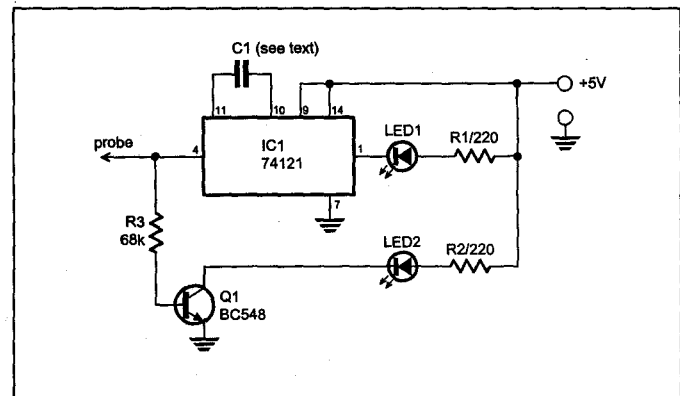The value of R3 will probably need to be determined by trial, and should be such that LED2 glows dimly for an open-circuit



at the probe tip. The value of C1 is determined by noting if a single pulse causes a suitable flash from LED1.

Andrew Chin,  
Heidelberg, Vic.

\$35

## EVER THOUGHT OF WRITING FOR EA?

Have you developed the circuit of the century, or a really great design, and would like to tell others about it?

Now is your chance to get your achievements to the largest number of colleagues and fellow enthusiasts, and make some money.

If you're not sure just how to write your article, ring our

office on (02) 353 0620 and ask for a copy of our writer's guide notes.

Just send your contribution to:

The Managing Editor,  
Electronics Australia,  
PO Box 199,  
Alexandria, NSW..2015.




## Dual train controller

This circuit lets you independently vary the speed of two model trains on the one track. The only modification required to each engine is the addition of two diodes. The principle of the circuit is very simple — one train responds to positive going pulses, while the other responds to negative going pulses. To vary the speed, the mark-space ratio of each set of pulses is changed independently.

In the circuit, IC1 (multivibrator type 4047) is wired as an astable, with an operating frequency set by R1 and C1. Its output is coupled to two monostables, IC2 and IC3. Mono IC3 responds to the positive-going edge of the signal from IC1, causing its output to go high for a time set by RV2 in conjunction with R3 and C3. The larger the value of RV2 the longer the pulse width, and the faster train #1 runs.

The timing component values for IC3 have been chosen so the maximum duration of its output pulse is slightly less than half the period of oscillation of IC1. The output pulse at pin 10 of IC3 is coupled to the non-inverting amplifier and power stage formed by Q1 and Q2, and then by D1 to the motor of train #1.

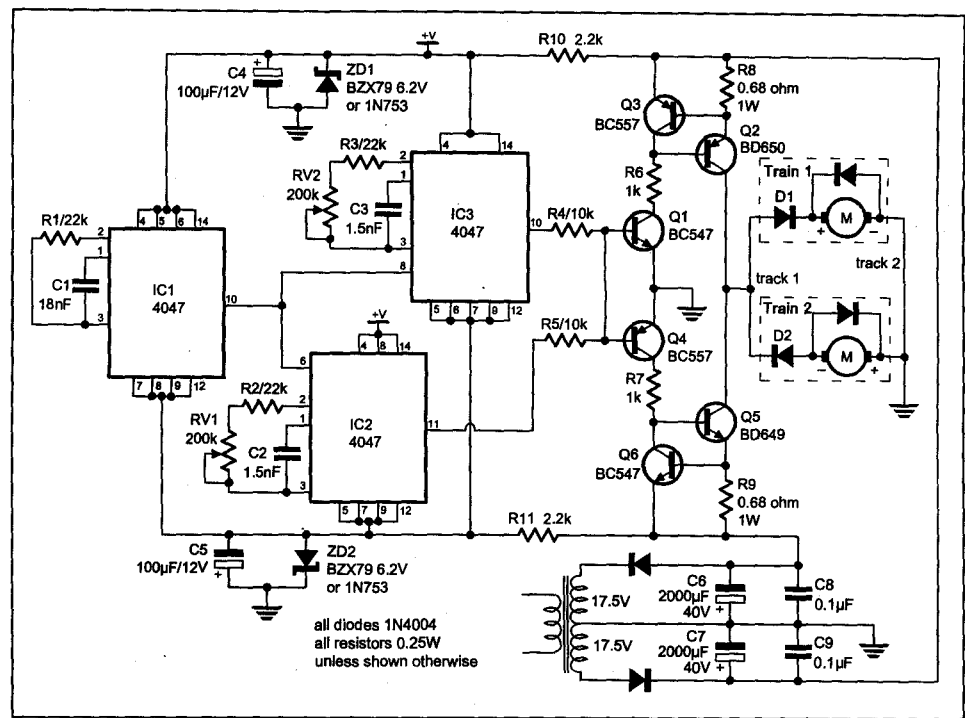Similarly the negative-going edge from IC1 causes the output of IC2 to go



low, for a duration set by RV1, R2 and C2. The larger the value of RV1 the longer the pulse width, and the faster train #2 runs. The output pulse at pin 11 of IC2 is coupled to the non-inverting amplifier and power stage formed by Q4 and Q5, and then by D2 to the motor of train #2.

Output current limiting is provided by

Q3 and Q6 and is set by R4 and R5 to about 900mA. The output transistors should be mounted on a heatsink. For 12V trains, you could use the suggested power supply or a centre-tapped power supply of 48V DC, with a suitable current capacity.

Les Kerr  
Beacon Hill, NSW.

\$45

## 12V battery charger

This circuit is designed to charge a 12V lead-acid battery (gel etc). Charge current to the battery is via IC1, Q1, R7 and D4. The value of the charge current is set by R7, although in the circuit as shown, regulator IC1 has a practical limit of 1A or so.

IC1 is a 555 timer that drives LED1 and LED2 and also supplies base current to Q1 via D3. The battery voltage is


sensed via RV2 and controls the operation of IC2. When the battery voltage is below a preset value, the output of IC2 is high. As a result, LED2 (red) is on and charge current flows to the battery. As the battery voltage increases, a point is reached when the output of IC2 switches low, turning on LED1 (green) and switching off charge current to the battery. The battery voltage now falls slightly, causing the output of IC2 to

switch high, restoring charge current and turning on the red LED. This cycle continues while power is applied, giving pulses of charge current to the battery. The width of the charge pulses get smaller as the battery reaches full charge. Temperature compensation is provided by ZD1 and D2, which ideally should be mounted close the battery being charged to sense any increase in temperature of the battery. This circuit gives a voltage of around 4.7V to pin 5 of IC2.

To adjust the charger, first ensure the DC supply to the circuit is 16V. With the charger not connected to a battery, adjust RV1 to give 5.4V at pin 6 of IC2, and adjust RV2 for 2.8V at pin 2. The green LED should be on. Now connect a fully charged 12V battery (12.5 to 12.6V) to the charger. Readjust RV1 for 4.7V at pin 6 and RV2 for 2.4V at pin 2. The red and green LEDs should both be on, indicating the charger is regulating the current to the battery.

Allied Electronics,  
Kingsford, NSW.

\$45

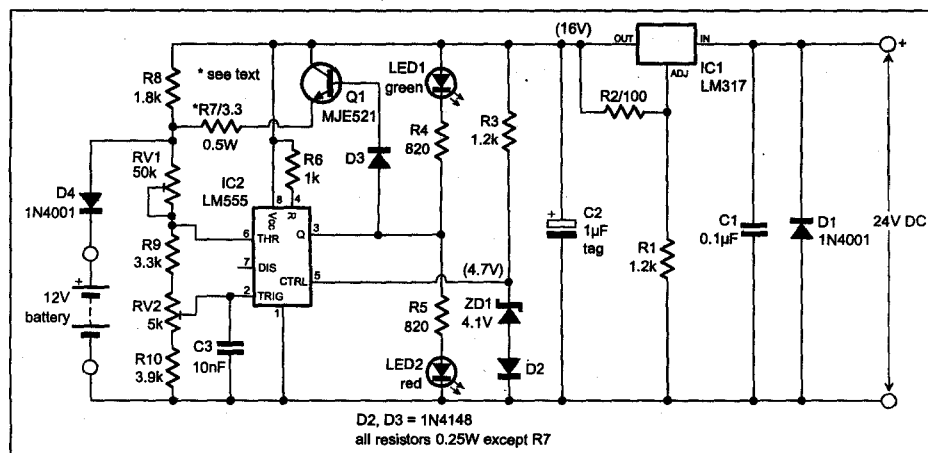

D2, D3 = 1N4148  
all resistors 0.25W except R7

## Construction project:

# PC-DRIVEN EGO SENSOR ANALYSER - 1

With car engine management systems becoming more and more sophisticated (and complex), it is getting increasingly difficult to find out what's happening 'under the hood'. This low cost analyser, combined with any IBM PC and some special software can provide a large amount of information on your car's performance.

by GRAHAM CATTLEY

Look under the bonnet of almost any modern car, and you will find that a disturbingly large proportion of the engine's operation is controlled by a microcontroller — otherwise known as an Engine Control Unit (or ECU).

The ECU monitors, through a large number of sensors, almost every aspect of the engine's operation, and is responsible for keeping tabs on (and compensating for) the many different factors that affect the engine's overall performance.

If you don't have several thousand dollars to spend on specialised engine monitoring systems, you can find it difficult to analyse your car's performance — important, particularly when things like catalytic converters require the engine to be running within very narrow margins in order to operate effectively. To this end we have designed a simple, low cost device to monitor the engine and display the results on an ordinary IBM PC (or clone).

The PC driven EGO analyser monitors the output from the engine's Exhaust Gas Oxygen (EGO) sensor, and provides a scope-type graphical display of its output voltage. This is a great improvement on existing designs (which display the sensor's voltage using a row of LEDs), as the computer can not only display the sensor's output waveform, but also perform many complex calculations to give you such details as:

- The percentage of oxygen in the car's exhaust (indicating the amount of wasted or unburned fuel);
- Whether (or when) the engine is running too rich or too lean;
- The engine's Air/Fuel Ratio (AFR), and consequently its Lambda (more about this later).

By examining the waveform, you can even tell how 'tightly' the ECU is controlling the engine. Quite an impressive amount of data from one little sensor!


All of this information is updated in 'real time' — taking a lot of the guesswork out of tune-ups, as the results are immediately apparent.

Also, with a bit of extra work on the software side of things, we have managed to get the computer to drive the analyser in 'reverse' so that instead of reading a voltage coming in from the sensor, the analyser can produce a software selectable DC output voltage in the

same range. This voltage can be fed in to the ECU *instead* of the EGO sensor's signal, allowing you to check the operation of the ECU and associated fuel injection systems with a 'simulated' EGO sensor.

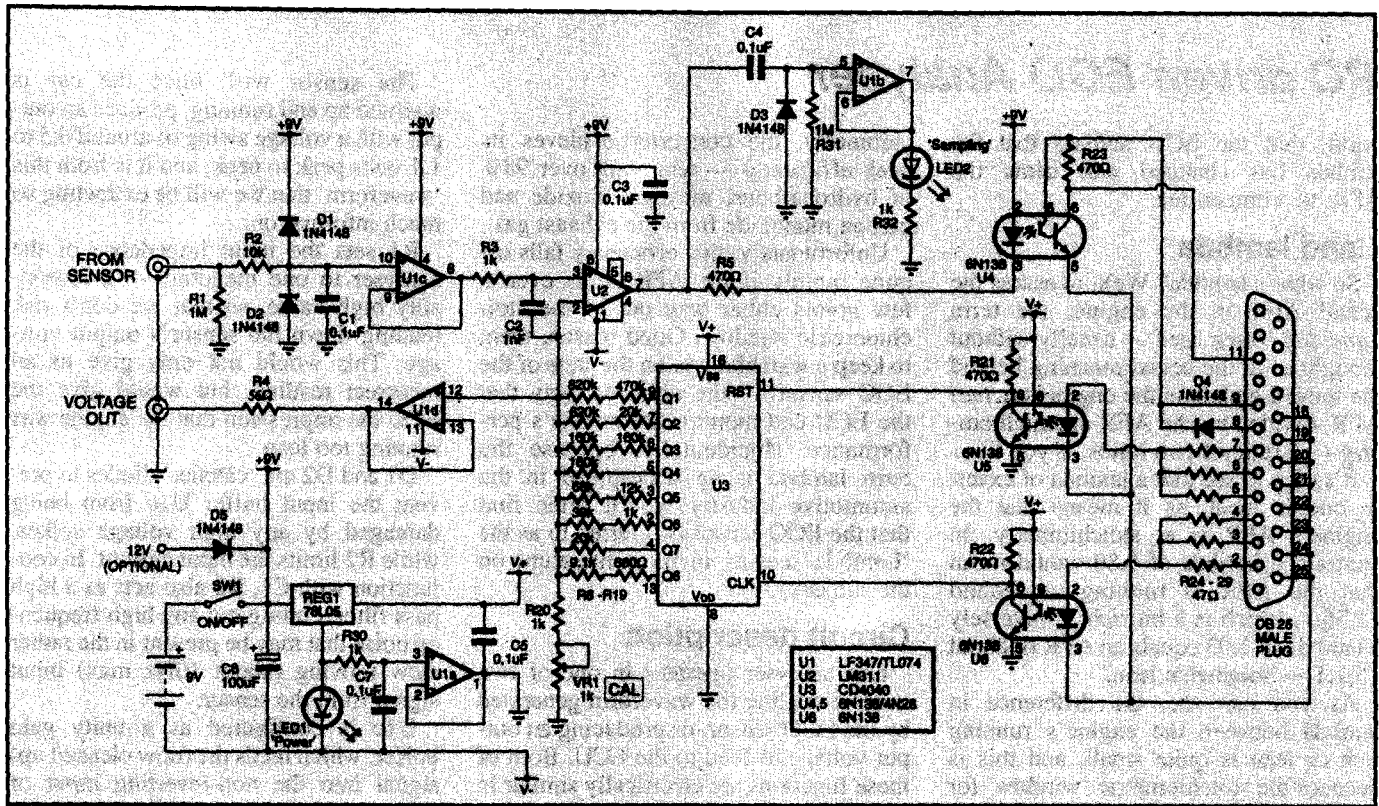The selection between reading in a voltage and outputting one is done under software control — in fact, the only hardware control on the device is the on/off switch! Also, much effort has been put into the software to make it as user-friendly as possible, as well as making it able to run on almost any system.





U3, a CMOS binary counter, the output of which is fed to high speed comparator U2, forms a simple digital to analog converter which is also fed with the EGO sensor's signal via U1c. Opto-isolators provide complete isolation between the analyser and the computer.

## EGO sensor?

The ECU receives input from a multitude of sensors distributed throughout the car. Of these, perhaps one of the most important is the EGO, or Exhaust Gas Oxygen sensor, located as you might expect in the exhaust manifold of the engine. The correct functioning of this sensor is of paramount importance to the correct operation of the engine management system.

As its name would suggest, the EGO sensor produces a voltage that is inversely proportional to the percentage of oxygen remaining in the engine's exhaust gas. As this residual oxygen level is a direct indicator of the engine's efficiency in burning the fuel (petrol), the EGO sensor therefore plays a crucial part in the engine's AFR closed-loop feedback control system. It needs to be functioning properly in order for the engine both to give its best fuel economy, and to achieve the correct pollution control of exhaust gases.

One problem comes about when the EGO sensor becomes contaminated with carbon or other residues in the exhaust gas.

This causes the sensor to become slow or 'lazy' in responding to changes in the exhaust's oxygen content, and this

is consequently reflected in the engine's performance.

Looking at the screen shot (Fig.1) you can see that the sensor's output voltage is not, as you might expect, maintained at a steady, constant level. This is because the sensor is part of a closed loop control system, whereby the ECU detects a change in the voltage coming from the sensor, and so changes the width of the pulses used to switch on the engine's fuel injectors.

In just a few hundred milliseconds or so (depending on the speed of the engine), the sensor detects the change in the AFR (or rather the change in the residual oxygen percentage, which amounts to the same thing), and consequently changes its output voltage accordingly.

Because of the inherent lag in this closed-loop system, due to the time taken for the exhaust gas to pass from the cylinders down to the sensor, as well as the distinctly non-linear AFR/voltage curve (see Fig.2), the sensor's output voltage swings fairly smartly between an upper and lower value. This means that the engine is running alternately rich and lean every second or so, which evens out to give the engine's average AFR.

By monitoring the sensor's varying output voltage, and by seeing how many times it crosses its own average voltage, we can see how fast the loop-response of the system is. The number of these crossings is averaged out over a 10-second period, with 20 to 40 'cross counts' every 10 seconds considered quite reasonable for high engine speeds.

## Stoichiometry...

Of course the whole point of this feedback system is to maintain the AFR at some ideal level. And for petrol, this ideal air/fuel ratio is 14.7:1. A mixture of 14.7 parts air to one part fuel (by volume) is the best mixture to keep the engine running at its optimum level, in terms of maximum efficiency in converting the fuel into energy, and the lowest pollution.

This ideal ratio is known as the *stoichiometric* point, and the ECU strives to keep the engine running at stoichiometry. The way that it does this is to try and keep the sensor's average voltage at the magic value of 0.45 volts.

This is one nice thing about EGO sensors — when the AFR is exactly 14.7:1, the usual sensor will produce an output voltage of 0.45V, and it is when the voltage swings past this

# PC driven EGO Analyser

point, that the ECU realises that the lambda has changed and trims the AFR to compensate.

## ...and lambda

So what's lambda? Well, to assess the actual AFR in the engine, the term *Lambda* is often used — usually without thought as to the actual meaning behind the term. Lambda is the engine's *actual* AFR, divided by the AFR at stoichiometry — a ratio of two ratios, if you like.

It's easy to see that a lambda of exactly one is ideal, as it means that the engine's AFR is at stoichiometry. In contrast, a lambda of 0.80 would mean that the AFR is running at around 11.76:1, which is a bit rich. Conversely a lambda of 1.03 equals an AFR of about 15.1:1 — somewhat lean.

As you can see, the difference in lambda between the engine's running rich or lean is quite small, and this is because the stoichiometric 'window' for optimum operation is itself quite narrow, ranging from 14.65:1 to 14.75:1.

Keeping the AFR within this range is not just for the engine's benefit, however, as the catalytic converter mounted in the exhaust system has a very narrow range over which it will operate. A quick look at Fig.3 will show you that at stoi-

chiometry, the converter achieves its peak efficiency — removing over 98% of hydrocarbons, nitrogen dioxide and carbon monoxide from the exhaust gas.

Unfortunately, this efficiency falls off quite rapidly if the AFR shifts even a few points either way out of the stoichiometric window. Good reason, then, to keep a watchful eye on the state of the EGO sensor — the only real way that the ECU can monitor the engine's performance. (Incidentally, because the term lambda is so widespread in the automotive industry, you'll often find that the EGO sensor is referred to as the 'Lambda sensor' in most literature on the subject.)

## Circuit description

Our analyser operates in one of two modes: reading the waveform generated by the EGO sensor, or producing an output voltage to feed to the ECU. Both of these functions are electrically similar in operation, the only real difference being in how the software 'drives' the circuit to perform each function.

To start with, we'll assume that we are reading in a waveform from a reasonably healthy EGO sensor, and that it is connected to the sensor input (labelled 'From Sensor' in the circuit diagram).

The sensor will, once the car is warmed up and running, produce an output with a voltage swing of around 0.5 to 1.1 volts peak to peak, and it is from this 'waveform' that we will be extracting so much information.

R1 sets the input impedance of the analyser to one megohm — a reasonably high value, so that we don't risk loading down the sensor's output voltage. This would not only give us an incorrect reading, but would give the ECU the impression that the engine was running too lean.

D1 and D2 are 'catcher' diodes to prevent the input buffer U1c from being damaged by any high voltage spikes, while R2 limits the input current. In conjunction with C1, R2 also acts as a high pass filter, cutting out any high frequency noise that may be present in the rather slow moving (about 10Hz max) input signal from the sensor.

U1c is configured as a unity gain buffer, which feeds the (now cleaned up) signal into the non-inverting input of high speed comparator U2.


That's about it for the analog part of the circuit. The rest of the circuit is driven by the computer and is, as you might expect, digital. To explain this part of the circuit, we are best off starting with the signals generated by the computer on the parallel port, and to explain these properly, we will have to dig a bit deeper — into the operation of the software itself.

When configured to read in (or 'sample') the sensor's output voltage, the software starts off by writing the value C7 hex to the computer's parallel port address. This is converted into a reset pulse, synchronising the hardware with the software so that everybody starts off on the right foot.

After a few milliseconds (the exact time will depend upon the speed of your computer), the software writes the values FF and then F8 (hex) to the port in quick succession, and then has a quick look to see if the port's BUSY line has gone low. The software does this write-check routine a total of 255 times for each individual sample, which is why that particular part of the program was written in machine code — anything else would be too slow!

## The real world

Okay, now that we know what the software is doing, we can get back to the 'real world' of electronics. Of course, each time a value is written to the port address in software, its binary equivalent

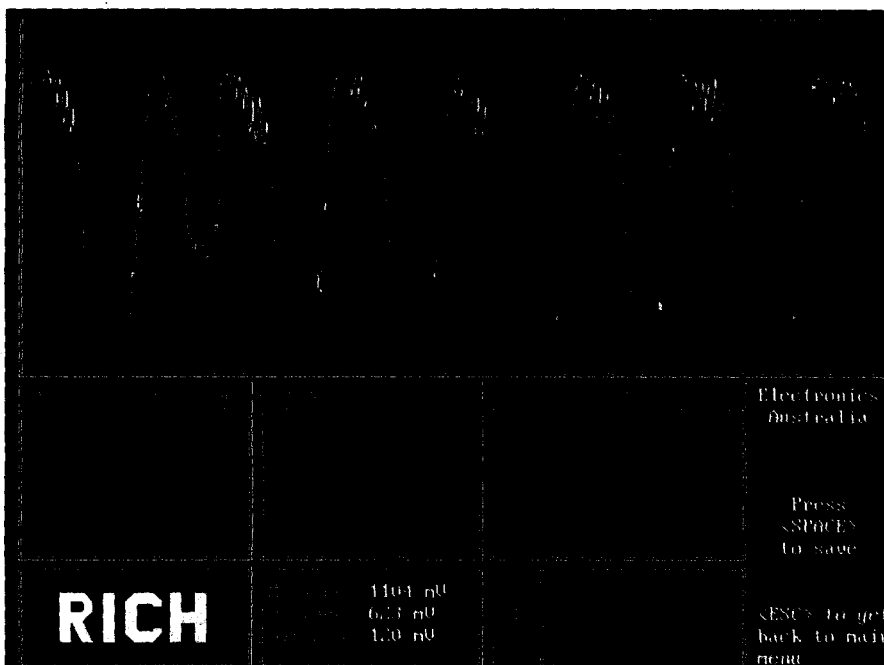

**Fig.1: A screen shot from the analyser, clearly showing in the top half the waveform produced by the EGO sensor, while the bottom half displays all of the calculated readings. Note that this reading was taken while the car was accelerating, accounting for higher than normal lambda.**

lent is produced on pins 2 to 9 of the computer's parallel port, and consequently appears at the DB25 plug on the right hand side of the circuit diagram.

If you look at the binary equivalent of the reset value that appears on the port at the start of each sample, (11000111), you'll see that the three zeros match up with the current limiting resistors R24, R25 and R26. These three resistors tie together to drive the optocoupler U5, with the ground return connected to pins 18-25 on the parallel port.

We have decided to use optocouplers to interface between the computer and the analyser for a couple of reasons; one is so that you can plug and unplug the analyser from the computer at any time — even when the computer and analyser are turned on. The other (and more important) reason is to electrically protect the computer from any voltage surges that may occur in the car's electrical system. The optocouplers serve to provide complete electrical isolation between the computer and the rest of the world.

Getting back to our resistors though, as they have a logic low applied to them (through bits 4 to 6), the optocoupler will be turned off. As a result, the RESET line of the binary counter U3 is pulled high through R21, and counter chip U3 resets — bringing all of the Q outputs low.

A similar thing happens when the values FF and F8 are sent out from the

## PARTS LIST

### Resistors

All 1% 1/4 watt:	
R1,31	1M
R2	10k
R3,16,30,32	1k
R4	56 ohms
R5,21,22,23	470 ohms
R6	820k
R7	470k
R8	620k
R9,17	20k
R10,11,12	160k
R13	68k
R14	12k
R15	39k
R18	9.1k
R19	680 ohms
R20	1.5k
R24,25,26,27,28,29	47 ohms
VR1	10k horizontal mini trimpot

### Capacitors

C1,3,4,5,7	0.1uF 100VW MKT
C2	10nF 100VW MKT
C6	100uF 16VW RB electrolytic

### Semiconductors

U1	LF347/TL074 quad op-amp
U2	LM311 high speed comparator
U3	4040 14-stage binary counter
U6	6N138 high speed optocoupler
U4,5	6N138 or 4N28 optocoupler
D1,2,3,4	1N914/1N4148 small signal diode
REG1	78L05 low power 5V voltage regulator
LED1,2	5mm red LED with bezel

### Miscellaneous



PCB 57 x 103mm, coded 96ego1; UB3 medium jiffy box, 130 x 77 x 40mm; 2 x BNC panel mount sockets; 2m x 12-way data cable; 30cm single core shielded cable; hookup wire; DB25 male plug; 9V battery clip; SPDT toggle switch; 19 x PC pins; nylon tie for cable clamp; 3 x 15mm 6BA bolts; 6 x 6BA nuts; 3 x 5mm spac-

computer, only this time it is U5 that gets switched. (The hex values FF and F8 are binary 11111111 and 11111000 respectively.) As you can see, bits 4, 5 and 6 remain high, preventing the counter from resetting, while bits 1, 2 and 3 toggle high/low, this time clocking the counter.

Resistors R6 to R19, along with R20 and VR1 comprise a resistor 'ladder' driven by the counter's outputs, and as a result of the counting action of U3, this simple 'digital to analog converter' (DAC) produces a rising staircase or

ramp voltage on the inverting input of U2. This voltage is trimmed via VR1 so that after 255 counts, the voltage peak is at 1.28 volts. With the port toggling away at around 15 to 30kHz (again, depending on the speed of your computer), a few quick jabs at your calculator will tell you that the ramp's frequency is around 58 to 117Hz — quite fast compared with the rather slow moving signal coming from the sensor.

Looking back now at comparator U2, you can see that its output will flip high whenever the ramp voltage from the

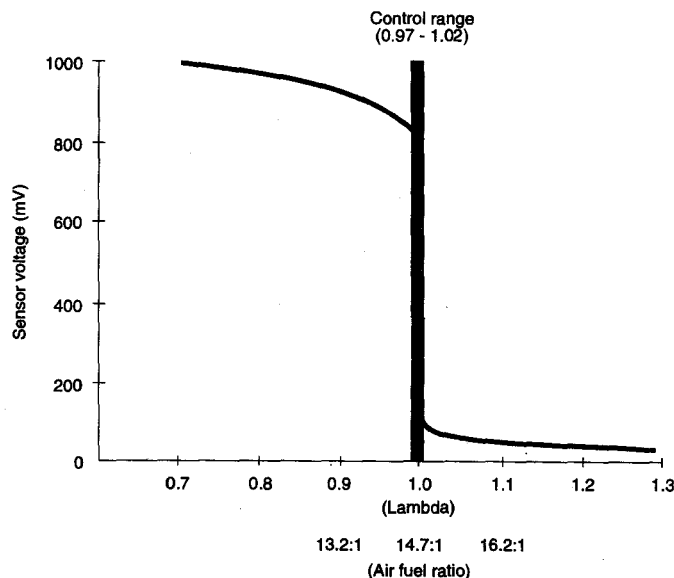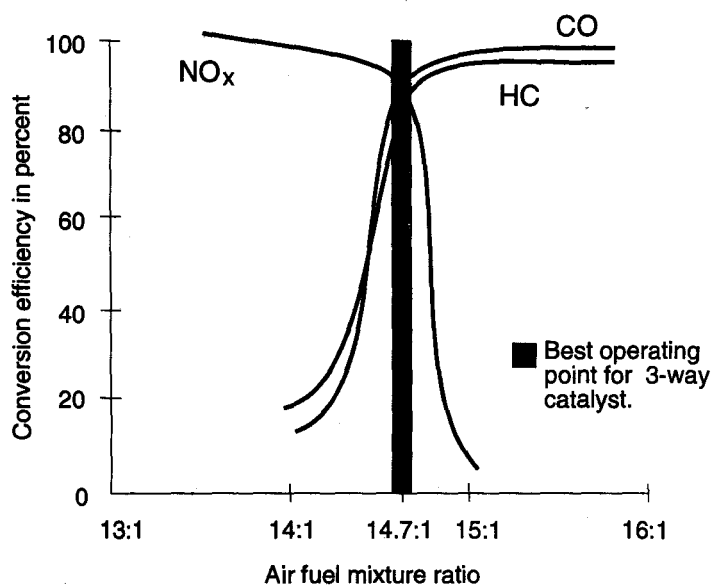

**Fig.2 (left)** This graph shows how the EGO sensor's output voltage swings severely as the air/fuel ratio moves through stoichiometry. Under normal conditions, the engine runs in the narrow range of .97 - 1.02 lambda, shown here in grey. **Fig.3 (Right):** Catalytic converters operate within a very narrow 'window' which is centred around the ideal AFR of 14.7:1. The ECU keeps tight control over the engine in order for the converter to remove up to 98% of carbon monoxide, hydrocarbons and oxides of nitrogen.

## Dead PCs? Lost Data?

### Unidentified Faults?

PC Maintenance and repair and Data Retrieval is one of the fastest growing and most lucrative businesses in the world!

Whether you want to

Profit from offering a service which is simple to provide when you have the right tools

Profit from selling superior tools at unbeatable prices

Save the high costs of repairs to your own equipment

# FIX IT FAST!

Phone (07)3279 5551

Fax (07)3279 4494

### Rescue

Retrieves data from dead disks - even physically damaged disks! Recover any file type automatically from any drive regardless of format.

### Trouble Shooter

PC Diagnostics that really finds the bugs! Bypasses operating systems for guaranteed results even on dead PCs.

### Pocket Post -

The most feature packed Power-on Self-Test card in the world!

### Alert Card

Test for and Monitor power and temperature fluctuations on PCs and Networks

### LAN Designer

The first network design software that automates the design and installation of the most complex network. Makes network installation fast, easy, inexpensive!

### Discovery Card

The ONLY product to guarantee detection of actual usage of any IRQ or DMA channel in any IBM compatible PC

### Skylight

Windows trouble-shooting utility written in Windows. Reports information the way Windows sees it.

Special prices for Computer Technicians.

Dealers Wanted

## Objectives

Master Australian Distributors  
1 Bellambi Place, Westlake QLD 4074

## PC driven EGO Analyser

resistor ladder exceeds the voltage coming from the sensor. This high drives the optocoupler U4, which relays the signal through to the BUSY line (pin 11 on the parallel port). In this way the computer can determine the sensor's output voltage at any time, by counting the number of times it needs to toggle the port before a BUSY signal is generated by the analyser.

### Power supplies

To be technical, there are two power supplies in this project — the more obvious one based around REG1, and another used to power optocoupler U4. This latter one is simply pins 8 and 9 of the parallel port, which are set through software so that they are permanently high.

Small signal diode D4 prevents any damage to the port, in case the analyser is plugged into the computer before the software has had time to set both of these bits high (if one were high and the other low, the two outputs would 'fight' each other, possibly overloading the outputs).

The power supply for the rest of the circuit is based around the low power three-terminal regulator REG1. This is a 5V device, but due to the 1.8V voltage drop from the 'Power' LED in its common line, the regulator puts out 6.8V relative to battery negative. Note that battery negative is not ground, as is usually the case, because here we are using U1a as a buffer to provide a ground that tracks exactly 5V below the regulator's output, giving a stable 5V supply for the binary counter U3 — necessary if we want to keep our ramp voltage stable.

The rest of the circuitry is somewhat less critical in its power requirements, and so is run straight off the battery, taking the load off the regulator.

As we are calling the output of U1a ground, battery negative by definition, becomes a minus voltage and is thus used to power the negative supplies of U1 and U2. Speaking of batteries, don't be tempted to power the circuit directly from the vehicle's own 12V battery, since this would effectively short out this 'induced' negative supply rail. However you could connect to some kind of huskier external battery via a flying lead and set of alligator clips — in which case we suggest that you include the diode D5 (not mounted on the PCB), to protect the analyser against accidental reverse polarity.

U1b, used to light the 'Sampling'

LED, gets its input through C4 from the output of the comparator U2. This output will be toggling high/low with a mark-space ratio dependent on the input voltage to the analyser. C4 serves to block DC and pass only the 'AC' pulses as U2's output changes state. These pulses are then buffered by U1b, driving LED2 with a signal that is pulse-width modulated with the EGO sensor's output.

### The other mode

As stated above, the analyser can operate in one of two modes, either reading in a voltage from the EGO sensor, or producing a voltage to feed into the Engine Control Unit instead of the EGO sensor's output. We've only covered the 'reading in' or sampling side of things so far, so we'll move on to the other mode — voltage production.

Surprisingly, this involves the addition of only two extra components, U1d and R4 (actually, that's one and a quarter components, but we aren't going to be picky, are we?).

The way it works is quite simple. All that happens is that the software (now in 'generate voltage' mode) produces a reset pulse, as it did before, and then proceeds to clock U3 a specific number of times, depending on the voltage to be generated.

As the maximum count of U3 is 255; and this corresponds to a voltage of 1.28 volts, it is a simple matter for the software to clock the counter  $255/1.28V = 199$  times per volt. This equates to 5.0mV per count, so that if an output of, say, 0.55 volts was required, the software would clock the counter a total of 110 times.

The required voltage appears as before on the end of the resistor ladder R6-19 and this is buffered by U1d which provides a relatively low output impedance, with the maximum output current limited to 20mA by R4.

Well, that's about all we have room for this month. Next month we will be covering the construction, testing and calibration of the analyser, along with some information on how to interpret its readings. If you're after more info on EGO sensors, our Automotive Electronics series makes very informative reading — particularly the January 1994 and last month's December 1993 issues, which cover the operation of the sensor in greater detail than can be afforded here.

(To be continued) ♦



## Construction project:

# SMART DUAL 12V BATTERY CONTROLLER - 1

This auxiliary battery manager takes full advantage of a dual battery setup's capabilities, by controlling when and how the 'auxiliary' battery is connected to the electrical system. It's fully automatic, will cost you far less than an equivalent commercial unit, and is particularly suited to the new breed of deep-cycle auxiliary batteries.

by **ROB EVANS**

Those familiar with the way dual battery systems are used in (mainly) recreational vehicles will no doubt appreciate the added safety and convenience this arrangement has to offer. The main advantage is that with an auxiliary battery powering any 'non-essential' accessories such as a refrigerator during an overnight stop, the four wheel drive vehicle (4WD), boat or camper's main battery is preserved for starting the engine in the morning.

This certainly beats being stranded in the middle of the Simpson desert in your 4WD, because the ever-important beer fridge has exhausted the vehicle's main, and *only* battery during the night...

Since a dual setup's auxiliary battery needs to be isolated during stops, but connected to the main 12V system for charging while the engine is running, there needs to be some switching system involved — and preferably an automatic one. In practice, there are a number of ways this can be done, and these vary substantially in cost and complexity.

The most common switching arrangements are based on a very heavy-duty relay — typically rated at between 20 and 100 amps — that has its contacts wired between the main and auxiliary battery terminals, and is energised via a switch on the vehicle's instrument panel or from an automatic control line. The relay itself is a fairly specialised and expensive device, with silver-coated contacts for longevity and very large bolt-type connectors, and is mostly sold through 4WD and marine accessory shops.


The manual switch method of engaging the relay has obvious pitfalls, as it relies on the correct action from the

operator, but the various automatic arrangements can work well. Regardless of the control method though, the relay is often switching very high currents and will suffer from the associated contact arcing. This in turn tends to cause the contacts to burn and eventually fail (despite the use of silver), and in extreme cases, can induce large voltage spikes in the main electrical system — a cause for concern with today's sophisticated engine management systems...

In the light of this then, some form of semiconductor switching is clearly the way to go, and commercial manufacturers offer a number of solid state switching units, as well as those based on heavy-duty relays. These range from


units that provide the required isolation by placing a high-powered *diode* in series with each battery — with the associated problems of forward voltage drop — to quite sophisticated management systems using switching MOSFETs, some of them quite costly.

As you've no doubt gathered, we have followed this latter path with the design of our own new auxiliary battery manager, which uses high-current switching MOSFETs and a relatively elaborate (but not expensive) control circuit. The MOSFETs have a rated drain-to-source current of around 50 amps, and an effective 'on' resistance of just 30 milliohms. To bolster the manager's current capability, we've elected to

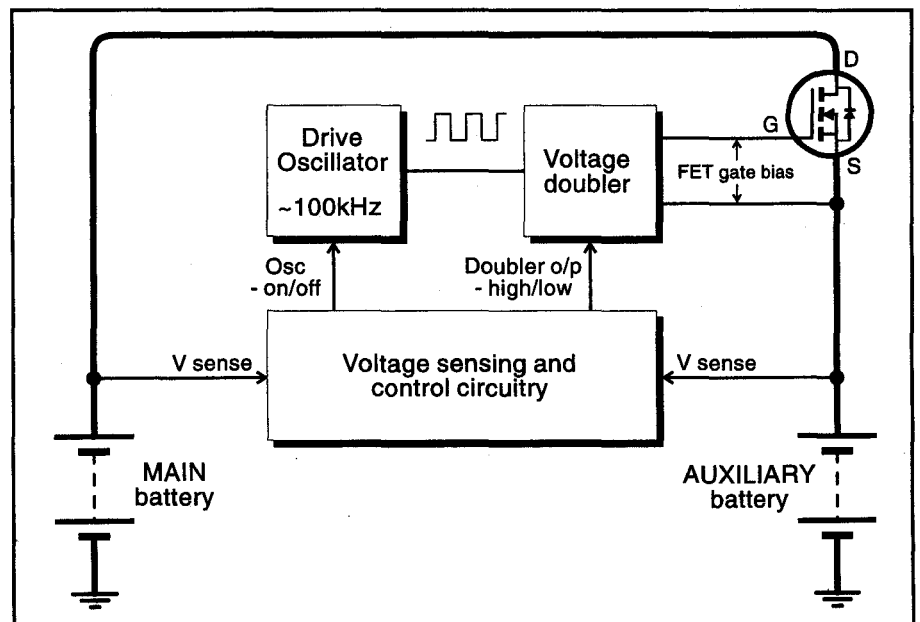

**Fig.1: The basic block diagram of the battery manager. The control circuit only allows the MOSFET to pass charging current when both batteries are in a suitable state.**



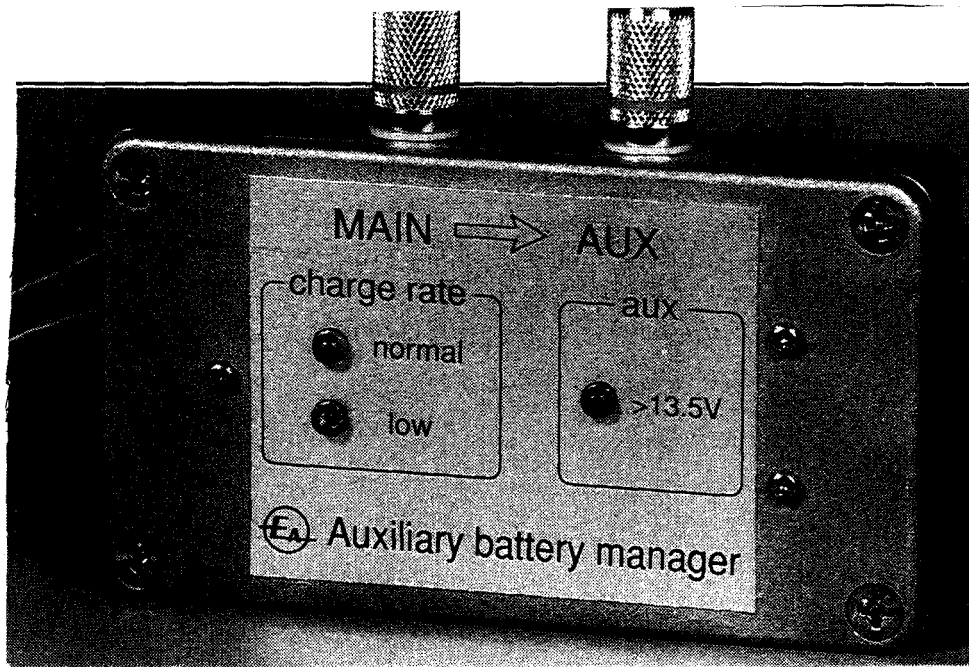

use two of these devices in parallel.

The circuitry used to control the MOSFETs senses the state of both the main and auxiliary batteries, and as a result will only connect the two directly together when conditions are appropriate. Namely, this is when the ignition system is active, the main battery has been fully charged, and the auxiliary battery has a reasonable terminal voltage.

This last condition has been included to protect the internals of a fully *discharged* auxiliary battery, because the new deep-cycle types in particular can be damaged by a large and sudden inrush of charging current. As this would be the case if the fully charged main battery is directly connected to a discharged auxiliary unit, the battery manager will not allow full current to pass until it senses that the auxiliary battery is at least partially charged.

In practice, the circuit allows an exhausted auxiliary battery to charge at two or three amps, then applies full charging current when its terminal voltage has reached about 10 volts. In this way the circuit helps to extend the working life of an auxiliary battery (which will often have a high replacement cost), and offers a degree of overload protection.

And to help you keep tabs on both the battery manager activity and the state of the electrical/charging system, we have also included a number of LED indicators on the front of the unit, as you can see from the associated photographs. Note that this includes an 'AUX>13.5V' LED, which will illuminate when the auxiliary battery has returned to a healthy state of charge.

So there we have our new auxiliary

battery manager. It's relatively inexpensive to construct, thanks to the use of common, low-cost components; can be installed without interfering with the existing wiring, and automatically charges the auxiliary battery in a 'sympathetic' manner. Plus of course, it provides the basic isolation needed to preserve the main battery for starting purposes.

### The overall design

The block diagram in Fig.1 shows the basic arrangement of the Battery Manager's circuit, where the high current charging path between the main and auxiliary batteries (via the MOSFET) is indicated by a heavy line, and the three low power control sections are shown in the centre area.

Here, the 'brains' of the circuit, the *voltage sensing and control* block, continuously monitors the voltage level of both the main and auxiliary batteries via their respective *V sense* lines, then uses this information to control the conduction of the MOSFETs (only one shown) via the remaining *Drive oscillator* and *Voltage doubler* blocks.

When enabled, the (nominally) 100kHz squarewave output from the oscillator drives the 'floating' voltage doubler circuit, which has its output connected between the MOSFET gate and source pins as shown in the diagram. The applied gate bias therefore has a DC level that's close to the peak-to-peak voltage of the incoming squarewave — around 12V — which comfortably exceeds the 8 - 10V bias level needed to switch the MOSFET into full conduction. In absolute terms then, the voltage at the MOSFET gate will be at the level produced by the voltage dou-

bler stage *plus* the terminal voltage of the auxiliary battery (say, 12V and 13V respectively, or a total of 25V).

Note, however, that the MOSFET is only switched into full conduction when both the oscillator and voltage doubler are fully enabled by the control circuitry, and this will only occur when the unit has sensed that both batteries are in a suitable condition for full charge current to flow.

If the main battery has a terminal voltage of less than 13.5 volts on the other hand, the control circuit will shut off the drive oscillator via the 'Osc — on/off' line, thereby removing the MOSFET's gate bias and preventing any current flow to the auxiliary battery. Thus the battery manager will only attempt to charge the auxiliary battery when it has sensed that the main battery has reached an acceptable state of charge (above 13.5V), as mentioned earlier.

Once this condition is satisfied the enabled oscillator then supplies AC energy to the voltage multiplier, which will in turn apply either a *full* or *reduced* bias level to the MOSFET gate, as determined by the state of the 'Doubler o/p — high/low' control line from the voltage sensing circuit. If the circuit senses that the auxiliary battery's terminal voltage is above 10.5V — and is therefore ready to accept a full current charge — the voltage doubler is switched to a high output level, which will then apply full gate bias to the MOSFET to turn it hard on.

Conversely, if the auxiliary battery is in a relatively poor state of charge (less than 10.5V) and full charging current should not be applied, the control circuitry will switch the voltage doubler to its low output level, causing the MOSFET to only 'partially' conduct. In practice, this bias level will be around 3V DC, resulting in a charge current of about two amps. This is adjustable via a trimpot mounted inside the battery manager.

So there we have the broad outline of the auxiliary battery manager's operation, as shown in the block diagram of Fig.1. Note that there are actually two MOSFETs wired in parallel in the final circuit, so as to increase the unit's current capacity.

Also as depicted in Fig.1, these devices have an internal protection diode connected the drain and source pins. While this means that 'reverse' current *can* flow between the auxiliary and main batteries, this is not really a problem in practice — we'll discuss this aspect in more detail at a later point...

# Smart Dual 12V Battery Controller - 1

## Circuit description

Referring now to the battery manager's full schematic diagram, you can see that the layout roughly matches that of the block diagram in Fig.1. The drive oscillator is based on IC1a, the voltage doubler is formed around D2 and D3, while IC1b and IC1c perform the main voltage sensing and control functions as described above.


In detail, the main battery voltage is sensed by the comparator circuit based on IC1b, which monitors the terminal voltage via the divider chain formed by R9 to R11, then compares this to a 5V reference supplied by the 78L05 voltage regulator IC3. The values chosen for R9 to R11 (and R15) mean that when the source voltage rises to 13.5V, there is 5V present at IC1b's non-inverting input (pin 9) and the comparator will change state. This in turn allows the output at pin 14 to rise to a high level via pullup resistor R13.

At this point it's worth noting that the LM339 quad comparator used here for IC1 is of the *open-collector* type, and therefore needs a pullup resistor to achieve a high output level. In the above case R13 is connected to the 'IGN' supply rail. This rail is directly connected to the vehicle's ignition circuit and will therefore be at a 12V level (or close to that of the main battery voltage) when the engine is running. As this rail supplies virtually all of the battery manager's circuitry, the unit will therefore be disabled when the vehicle engine is shut down.

Thanks to the hysteresis effect produced by positive feedback resistor R12, the IC1b comparator will then remain in the above condition (output high) until the input voltage from the main battery drops to around 12.5V. At this point the voltage at IC1b's non-inverting input has fallen *below* the 5V reference at the inverting input, and the comparator's output will return to a low level.

In order to disable the drive oscillator when the main battery is at less than 13.5V, the comparator's output is connected directly to the oscillator circuit via diode D1, at IC1a's inverting input. A low level at the comparator's output will therefore forward bias D1 and hold IC1a's inverting input at near ground potential, which disables the oscillator and forces its output (pin 13) to a high level.

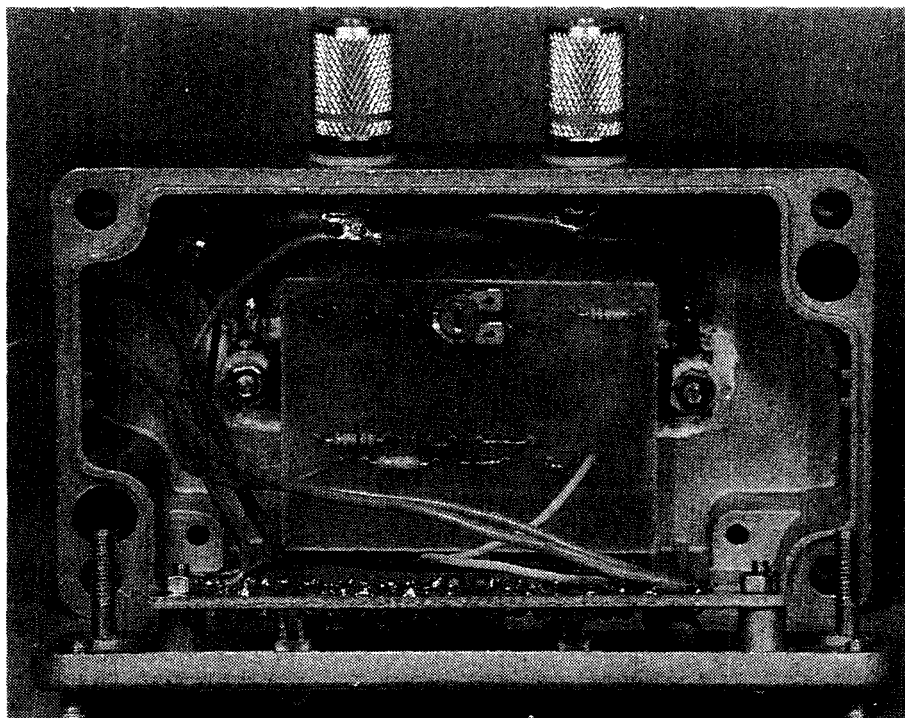Conversely, a high level at the comparator output (pin 14) will reverse bias



**Two high current MOSFETs are used to control the current between the MAIN and AUX terminals — they provide support for the small 'drive' PCB, and use the bottom of the case as a heatsink.**

D1 and remove its loading effect on the RC network at pin 10, allowing the oscillator to run freely.

The oscillator itself is a fairly simple RC arrangement, where the biasing network composed of R1 to R3 provides both hysteresis and positive feedback for IC1a, and the values for R4 and C1 have been selected for an oscillator frequency of around 100kHz. Note that in this case the opamp's pullup resistor (R5) is tied to the main battery supply rather than the more usual IGN supply line, as this guarantees that the oscillator output swings between 0V and the main battery's terminal voltage.

The aim here is to make sure that the input to the voltage doubler — and hence the drive voltage to the MOSFET gates — is at the highest possible level, and not at the mercy of the IGN supply line which can fall due to the loading of the vehicle's accessories. If the voltage on the ignition line drops by a significant degree, the proportional fall in the MOSFET gate drive voltage may cause their power dissipation to rise sharply, as they may no longer be *fully* biased on. In this situation, the MOSFETs could overheat or even self-destruct...


So while tying the oscillator's pullup resistor to the main battery rather than

ignition line neatly solves this problem, it does increase the leakage current from the main battery when the battery manager is disabled — that is, when the vehicle is not in use.

However as the current path to ground via R5 is via high value resistors (R3, R4 and so on), the 'wasted' battery energy is extremely low. In fact, the bleed current will be less than 200uA, which is much less than the likely self-discharge current of a typical lead-acid automotive battery.

The squarewave energy from the oscillator output is next passed to the voltage doubler stage, which is composed of capacitors C2 and C3, and signal diodes D2 and D3. The resulting DC output developed across C3 and bleed resistor R6 is then applied between the MOSFET gate and source via R7 and RV1. Note that at this stage LED1 to LED3 and R8 are not influencing the circuit (optocoupler IC2 is 'off'), so full drive voltage (say 12VDC) is applied to the MOSFETs, which will turn hard on and pass full charging current to the auxiliary battery via 'resistor' RL (which is actually the output lead). More about this component later on.

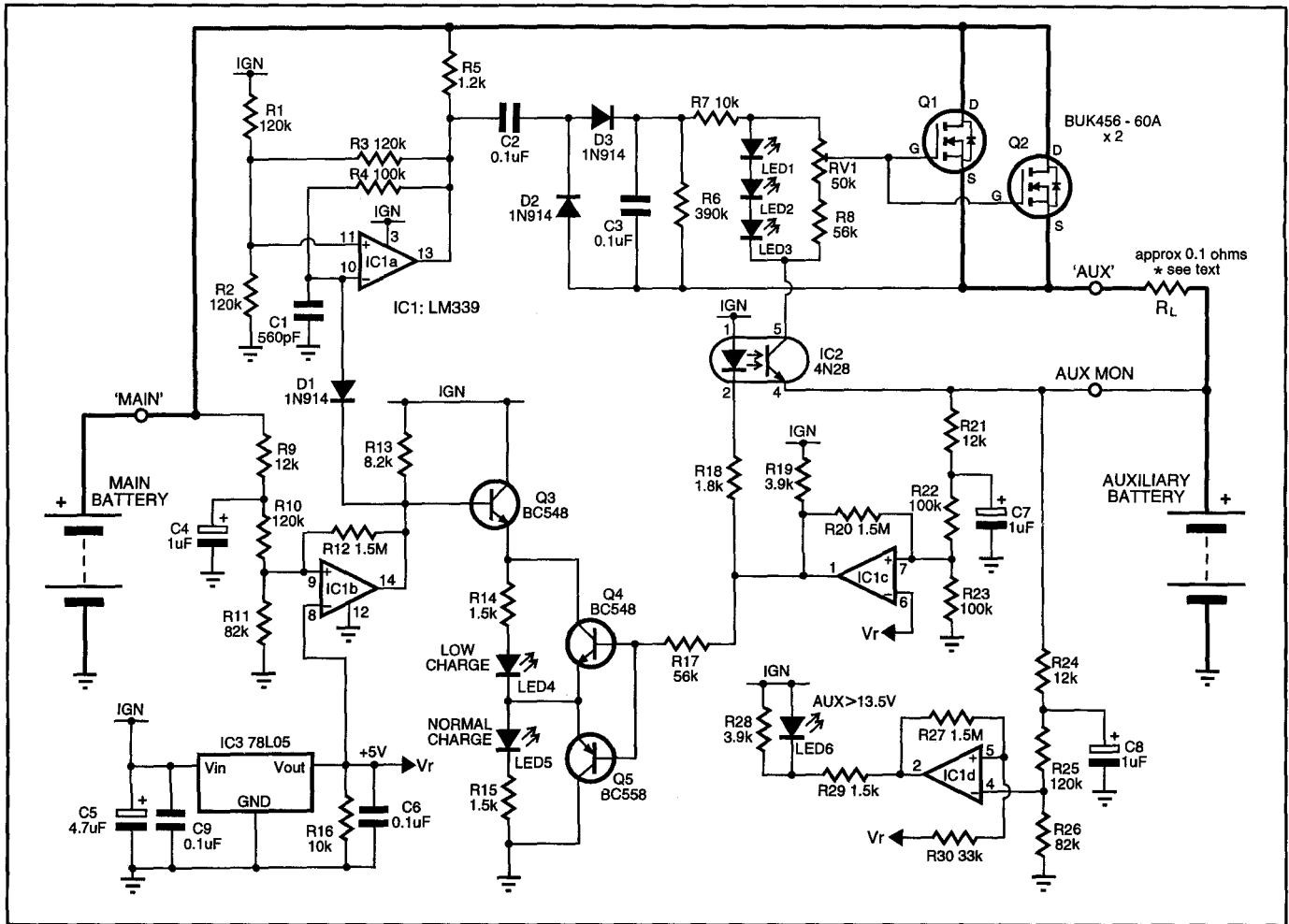The terminal voltage of the auxiliary battery is monitored by the comparator



The overall schematic diagram for the manager. As you can see, the layout roughly matches that of Fig.1, so the various sections are easy to locate.

circuit based on IC1c, which is identical to the one used to sense the main battery voltage (IC1b), except for the value of the resistor at the bottom of the sensing divider chain, R23. With this arrangement, IC1c's output (pin 1) will be at a high level when the auxiliary battery voltage has risen above 10.5V, and will then fall to 0V if the battery then drops below about 11.5V — as before, the circuit is essentially a non-inverting comparator with a hysteresis of about 1V.

When the auxiliary battery is below 10.5V and should not receive a full current charge, the resulting low level at the output of IC1c will energise the optocoupler's internal LED (pin 1 and 2 of IC2) via limiting resistor R18. This will in turn bias IC2's internal NPN transistor fully on (at pins 4 and 5), and connect both R8 and the cathode of LED3 directly to the auxiliary battery's positive terminal, via the 'AUX MON' connection.

Ignoring RL for the moment then, you can see that as R8 and the LED3's

cathode are now connected to the MOSFET source pins, the level from the voltage doubler (across R6) is now applied to a voltage limiting circuit formed by dropping resistor R7 and the LED string (LED1 to LED3). The nominal 12V level from the voltage doubler is consequently reduced to about 4.5V across the LEDs (about 1.5V per LED), then 'trimmed' below this level by preset potentiometer RV1.

As the trimpot's wiper is connected to the MOSFET gates and therefore sets the final drive voltage when IC2 is activated, this adjustment is used to preset the 'low' charging current. In practice, about 3V of MOSFET gate bias will reduce the output current (into the auxiliary battery) to about two amps.

The story doesn't quite end there however, since the effect of the inline 'resistor' RL will slightly modify (in fact, improve) the behaviour of this part of the circuit, by acting as a source resistor for the MOSFETs.

As you would expect from a source or emitter resistor, RL provides a

degree of DC negative feedback for Q1 and Q2, and therefore stabilises the output current for a given MOSFET gate bias voltage.

Note that the gate voltage generated across the LED string is referenced to the auxiliary battery side of RL, via IC2.

In effect then, the circuit behaves as a constant current source, when switched into the 'low' current mode.

Any increase in the nominal output current will cause a proportional rise in the voltage across RL, which in turn reduces the actual gate-to-source voltage applied to the MOSFETs. The MOSFETs will then shut down slightly, which compensates for the original increase in output current. However, note that since RL is a very low value and therefore provides only a small degree of negative feedback, the arrangement is somewhat less than a perfect constant current source. It's more than adequate for this application though, and the current varies by only a relatively small amount.

At this stage it's worth considering the

# Smart Dual 12V Battery Controller - 1

other main effect of the output lead resistance (RL), which comes into play when the unit is in the 'normal' charge rate mode, where the MOSFETs are biased hard on (with IC2 inactive). Under these conditions RL simply limits the maximum current that can flow into the auxiliary battery, so as to protect the vehicle's electrical system, the battery manager's MOSFETs, and the auxiliary battery itself.

Note that in practice the battery manager only switches into the high (normal) current mode when the auxiliary battery has reached a terminal voltage of about 10.5V, so if we assume that the main battery is at say 14V, there will be around 3.5V across RL. If the lead has an inherent resistance of 0.1Ω then, the maximum charging current is restricted to about 35 amps.

Since the auxiliary battery is not fully charged at this point however, its own internal resistance will generally limit the charging current to a somewhat lower figure.

## LED indicators

The remaining parts of the battery manager's circuit are mostly used to drive the front panel status LEDs, which indicate the current rate of charge (normal/low) and whether the auxiliary battery has reached a 'charged' condition (>13.5V).

As you can see from the schematic, the output of the main battery voltage monitor at pin 14 of IC1b also drives emitter follower Q3, which will provide a voltage source for the charge rate indicator circuit (LED4, LED5, Q4 and Q5) when the comparator output is at a high level — that is, when the main battery has risen above 13.5V and charging is enabled.

Then if the auxiliary battery is below 10.5V and a low charge current is flowing, the low level at the output of IC1c (pin 1) will be passed to the junction of LED4 and LED5 via emitter follower Q5 and isolating resistor R17. The 'low charge' indicator LED4 is therefore energised, via limiting resistor R14.

Conversely, when the auxiliary battery's terminal voltage has risen above 10.5V and the output of IC1c is high, emitter follower Q4 passes the high level to the junction of LED4 and LED5, thereby energising the 'normal charge' indicator LED5 via R15.

And as you would expect, when charging is *not* enabled (the main battery has not yet reached 13.5V) Q3's emitter

will be low, which prevents either LED from illuminating regardless of the state of the auxiliary comparator IC1c.

The remaining comparator circuit based on IC1d monitors the state of the auxiliary battery in much the same way as IC1c, and drives the 'AUX >13.5V' indicator LED6 via limiting resistor R29.

In this case however, the circuit is set up as an inverting comparator, where the voltage reference Vr is applied to the non-inverting input (pin 5) via R30, and the sensing voltage divider (R24 to R26) feeds the inverting input at pin 4. Since the voltage divider values match those used with the main battery comparator

(IC1b), IC1c's output will go low when the auxiliary battery has reached about 13.5V, therefore energising LED6.

Other minor parts of the circuit include the 78L05 low power voltage regulator IC3, which is used as a 5V reference for the comparator circuits, plus a number of passive 'housekeeping' components.

These include the IGN supply and regulator bypass capacitors C5, C6 and C9, and additional comparator pullup resistors R19 and R28 which ensure that IC2 and LED6 (respectively) are fully off when their matching comparator outputs are high.

Lastly, C4 is included to act as a low-pass filter in conjunction with R9, so that high frequency or transient interference from the main battery line cannot reach comparator IC1b. C7 performs the same function with R24, for the auxiliary comparator IC1c.

## Internal MOSFET diodes

As you can see from the heavy current path shown in the battery manager's schematic, the MOSFET internal protection diodes will allow a 'reverse' current to flow if the auxiliary battery's terminal voltage is significantly higher than that of the main battery. While this is obviously not the case during normal charging operations, there can be circumstances where the auxiliary battery is fully charged yet the main battery's voltage has fallen due a high current load — such as the vehicle's starter motor.

If the auxiliary battery can deliver a high current (most deep cycle batteries can't, by the way), then the MOSFET diode current is only really limited by the connecting lead resistance RL, and may rise to a high level — say 60 amps. This in turn means that the MOSFETs will dissipate around 30 watts each, thanks to the 1V drop across the diodes. If this current were present for an extended period, the MOSFETs would become rather hot and bothered due to the modest heatsinking capability of the diecast box.

Note that the MOSFETs dissipate less than 10W during normal charging operations.

While we were initially a little concerned about the above scenario, and considered a number of circuit configurations that would provide full two-way isolation between the batteries (by the use of a high-current relay), we found that the additional expense and circuit

## PARTS LIST

### Resistors

(All 1/4W 5%)	
R1-3,10,25	120k
R4,22,23	100k
R5	1.2k
R6	390k
R7,16	10k
R8,17	56k
R9,21,24	12k
R11,26	82k
R12,20,27	1.5M
R13	8.2k
R14,15,29	1.5k
R18	1.8k
R19,28	3.9k
R30	33k
RV1	50k miniature horizontal trimpot

### Capacitors

C1	560p ceramic
C2,3,6,9	0.1uF monolithic
C4,7,8	1uF 25V tantalum
C5	4.7uF 25V tantalum

### Semiconductors

IC1	LM339 quad comparator
IC2	4N28 opto-isolator
IC3	78L05 mini 5V regulator
Q1,2	BUK456-60A power MOSFET
Q3,4	BC548 NPN transistor
Q5	BC558 PNP transistor
LED1-3	3mm red LED
LED4	5mm red LED
LED5	5mm orange LED
LED6	5mm green LED

### Miscellaneous

Diecast aluminium box (waterproof if possible) 115mm x 65mm x 35mm; 2 x heavy-duty terminal posts; 2 x medium-duty solder lugs; PCB, coded 96bm1a (85 x 40mm); PCB coded 96bm1b (55 x 40mm); 2 x BUK456-60A mounting kits; heavy and light duty hookup wire, tinned copper wire, nuts, bolts, etc.

complexity of the alternatives was difficult to justify.

And as the condition would only occur if (a) the auxiliary battery was of the high current type, (b) the load was applied for an extended period (unlikely with a vehicle's starter motor), and (c) the main battery voltage dropped substantially under load (indicating a less than healthy battery), we reasoned that there was not too much cause for concern.

Of course, we'd have to add that it's extreme folly to set off in your 4WD, camper or car/caravan combination with an unhealthy main battery — or for that matter, a vehicle that's difficult to start and needs to be cranked for an extended period.

Under normal circumstances, the potential for reverse current flow could be considered as somewhat of an advantage in a dual battery system, since any excess charge in the auxiliary battery will be automatically passed to the main battery via the MOSFET diodes. This in turn ensures that the main battery is always in the best possible state of charge for the conditions at the time, and can therefore crank the engine into life.

That's all we have room for this month. In the second and final article, we'll cover the construction, testing and installation aspects of the battery manager. ♦

## EML-2M

### EPROM EMULATOR



The EML-2M ROM/RAM Emulator allows two different ROM's or SRAMS to be emulated from 64Kb to 1Mb, or 1 ROM or SRAM up to 2Mb. EML-2M is an easy to use and economical development tool suitable for general firmware development. It saves EPROM

consumption and cuts time wasted in repetitive programming and erasing. The software provided can quickly download files in either HEX or BINARY format to the emulator. A full screen editor enables modification in HEX or ASCII format.

- Can emulate 4Mb to 8Mb after expansion.
- RESET/HALT can be activated on the target board
- Comes with disassemblers



**BALTEC**  
SYSTEMS PTY LTD

26 Mayneview St  
Milton Qld 4064  
Ph: (07) 3369 5900  
Fax: (07) 3369 5257  
Freecall: 1800 818 097

READER INFO NO. 13


**Save Time! Save \$\$\$'s... Save Clients!**

# IDENTIFY PC PROBLEMS FAST!

## with Tech Star Diagnostics

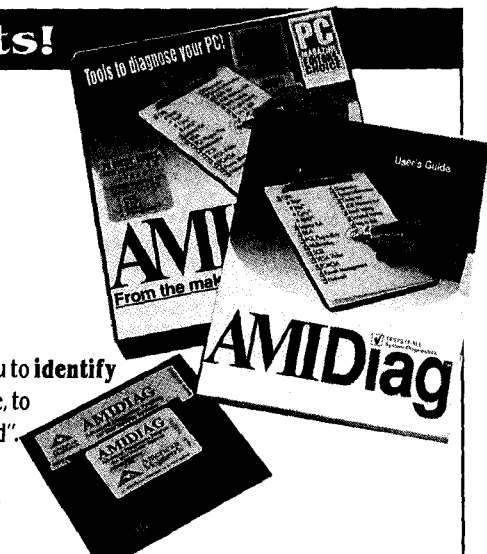**Mini P.O.S.T. from \$95**

Tech Star International has an advanced range of PC Diagnostics that allows you to identify and troubleshoot PC problems FAST. Everything from single component failure, to IRQ & DMA conflicts to chip level diagnosis of systems that appear to be "dead". This is the most comprehensive range of PC diagnostics available in Australia with products for the novice user through to professional hardware technicians.



### POCKET P.O.S.T.

A fast and efficient diagnostic board which allows you to explore a PC's BIOS even when the PC appears dead and DOS is not available.

- Easy to use. Simply plug the Pocket P.O.S.T. board in and read the error codes displayed on the built-in hexadecimal LED display
- Comprehensive reference manual provides you with an immediate diagnosis and course of action
- Imagine the time and frustration you could save

### AMIDIAG

From the makers of the world famous AMIBIOS comes a first class diagnostic tool for all users. AMIDIAG, winner of the prestigious PC Magazine Editor's Choice award, provides all of the testing and system information you need for complete maintenance of your PC. Not only does AMIDIAG check your system board, memory and cache, but it also provides complete testing and support for VESA, PCI and EISA bus. As well as system information on your operating environment including IRQ and DMA addressing.

### PC CHECK

Technicians' No. 1 choice for reliably testing PC hardware.

- Identifies system configuration and set up immediately
- Professional tests and tools for effortless fault diagnosis and system burn-in
- Independent Operating System for true hardware diagnosis without interference from DOS
- Includes testing facilities for external cache and intelligent multimedia testing

## TECH STAR INTERNATIONAL

PTY. LTD. ACN: 054 575 030  
Specialist Technology Suppliers  
**PO Box 259 Paddington Q 4064**  
Telephone: (07) 3367 1444    Facsimile: (07) 3367 1331  
Brisbane:

**State Distribution Opportunities Available**

READER INFO NO. 14

**ROD IRVING ELECTRONICS PTY. LTD.**  
 YOUR FIRST CHOICE IN QUALITY ELECTRONICS A.C.N. 005 428 437 ESTABLISHED SINCE 1977

ERRORS & OMISSIONS EXCEPTED. PRICES CHANGE WITHOUT NOTICE.  
 WINDOWS IS A REGISTERED TRADEMARK OF MICROSOFT CORPORATION IN THE U.S. AND OTHER COUNTRIES.

**SYQUEST PRODUCT RANGE ROUND-UP -**

FOR EVEN MORE AFFORDABLE BACKUP AND FILES EXCHANGE BETWEEN COMPUTERS



**FREE PACK & POST FOR ORDERS WORTH \$25 OR MORE & UNDER \$3K - OFFER VALID ONLY UNTIL 31ST JANUARY 1996.**

HERE'S A VERY ECONOMICAL WAY TO BACKUP FILES AND TRANSFER INFORMATION...

**INDUSTRY STANDARD**

**3.5" HIGH PERFORMANCE REMOVABLE CARTRIDGE HARD DISK DRIVE.**

**FEATURES INCLUDE:**

- ANSI ATA interface (IDE SCSI available as option) provides 14.5msec access time
- Offers primary and secondary storage in one drive.
- 64K intelligent read "Look Ahead" caching buffer.
- Data transfer rate at the host interface up to 4.0MB per second
- Data transfer rate from the head / media interface is up to 2.3 MB per second.
- Programmable power modes - sleep, stand-by idle and active
- 20,000 cartridge insertion cycles
- 100,000 start/stop cycles
- Ergonomic engineering for reliable and easy cartridge loading and unloading
- 100,000 hours MTBE with 100% duty cycle
- On-the Fly error correction
- 1-7 RLL modulation recording for maximum read window margins.
- Removable storage advantages - including unlimited capacity and off-line storage, data transportability, system sharing, data security and fast backup.

The 3.5" SQ3105 drive is designed for all laptop/desktop computers.

Our 3.5" drives provide universal interchangeability through the use of an embedded servo system and adaptive read channel, while including comprehensive self-diagnostic capabilities and programmable power-saving modes.

**AS USED BY**

- Printers • Draughtsman • Architects • CAD Users
- Bureaus • Typesetting Bureaus • DTP-based design studio • Advertising Agencies • Computer-based Graphic Artist & others who has the need to exchange data quickly and easily.

Printing companies take note- these are the same removable media that you could be paying \$250.00 or more for. We will call at your place of business to advise for free. Call 543 2166. Ask for Kevin Glenton.



**WHILE STOCK LASTS!**

	Tax Inc.	Tax Ex.
105MB Cartridge C11880..... (Compatible with the 270MB Removable Drive)	\$119.00	\$99.00
270MB Removable Cartridge C11888.....	\$129.00	\$105.00
270MB Removable Drive Mechanism IDE C11854.....	\$599.00	\$531.00
(Read and writes 105MB cartridge format) SPECIAL PRICE .	\$519.00	\$425.00
270MB Removable Drive Mechanism SCSI C11856..	\$599.00	\$531.00
SPECIAL PRICE .	\$519.00	\$475.00



**NEW EPSON EPL-5500 LASER PRINTER**

The EPL-5500 is EPSON's new generation of laser printers. This ultra-compact personal laser offers 600 dpi print quality at a speedy 6 pages per minute. It includes EPSON's Bi-Resolution Improvement Technology (BIRITech)- for crisp and smooth text and graphics- and EPSON's Microgrey Technology (EMGTech) for improved greyscale printing. This printer is powered by a 22.5 Mhz SPARClike RISC processor

**Features:**

- PCL5e emulation
  - 1 MB RAM (expandable to 32 MB using industry standard SIMM's)
  - Image Optimum memory management system
  - Bi-directional parallel interface
  - 22 resident scalable fonts
  - Toner saving mode
  - Power saving feature
  - First print in less than 20 seconds
  - 150 sheet input tray
- Options:**
- 250 sheet optional input tray
  - Optional interfaces including buffered parallel, ethernet, LocalTalk, serial, Coax and Twinx

**C92350**  
**\$1225**  
 TAX EX.  
**\$1495**  
 TAX INC.

**JUST RELEASED!! NO PICTURE AVAILABLE**

**12 MONTHS WARRANTY**

PLEASE SEND ALL MAIL ORDERS TO:  
**MAIL ORDER DEPARTMENT,**  
**ROD IRVING ELECTRONICS PTY. LTD.**  
**LOCKED BAG 620, ROSEBANK MDC,**  
**CLAYTON SOUTH, VIC 3169.**

**MELBOURNE:** 48 A'BECKETT ST. MELBOURNE 3000  
 • Ph. (03) 9663 6151 • Fax. (03) 9639 1641  
 • Mon-Thurs: 9.00-5.30pm • Fri: 9.00-8.00pm • Sat: 9.00-1.00pm

**VERMONT:** 190 ROOKS RD. VERMONT 3133  
 • Ph. (03) 9874 8888 • Fax. (03) 9874 2288  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm

**DAKLEIGH:** 240C HUNTINGDALE RD. DAKLEIGH 3166  
 • Ph. (03) 9562 8939 • Fax. (03) 9562 8940  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm

**NORTHCOTE:** 423 HIGH ST. NORTHCOTE 3070  
 • Ph. (03) 9489 8866 • Fax. (03) 9489 8131  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm

**BOX HILL:** 1031 MAROONDAH HWY. BOX HILL 3128  
 • Ph. (03) 9899 6033 • Fax. (03) 9899 0156  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-3.00pm

**CLAYTON:** 56 RENVER RD. CLAYTON 3168  
 • Ph. (03) 9543 7877 • Fax. (03) 9543 8295  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-12.00pm

**BLUESTAR COMPUTERS:** 271 MAROONDAH HWY. RINGWOOD 3134  
 • Ph. (03) 9870 1800 • Fax. (03) 9879 3027  
 • Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm

**SYDNEY:** 74 PARRAMATTA RD. STANMORE 2048  
 • Ph. (02) 519 3888 • Fax. (02) 516 5024  
 • Mon-Thri: 9.00-5.30pm • Sat: 9.00-1.00pm

**ADELAIDE:** 241-243 WRIGHT ST. ADELAIDE 5000  
 • Ph. (08) 211 7273 • Fax. (08) 211 7273  
 • Mon-Thurs: 9.00-5.30pm • Fri: 9.00-8.30pm • Sat: 9.00-5.00pm • Sun: 10.00-4.00pm

**LATEST CPU PRICE**

intel CPU	AMD CPU	CYRIX CPU
486DX2-66 OverDrive Chip ... \$189	486DX4-100 NEW! ... \$179	
486DX4-100 OverDrive Chip \$269	486DX4-120 NEW! ... \$249	
PENTIUM 60MHz ..... \$199		
PENTIUM 75MHz ..... \$319		
PENTIUM 90MHz ..... \$469	486DX2-66 3.3V ..... \$69	
PENTIUM 100MHz ..... \$499	486DX2-66 5V ..... \$79	
PENTIUM 120MHz ..... \$799	486DX2-80 3.3V ..... \$89	
PENTIUM 133MHz ..... \$999	486DX2-80 5V ..... \$99	
	486DX4-100 ..... \$119	

AVAILABLE ON ORDER THROUGH OUR STORES OR BY MAIL ORDER

**COMPUTER CARDS - HUGE RANGE!!**

CAT NO.	DESCRIPTIONS	PRICE
X18075	1Meg 16bit VGA	\$159
X18196	Trident 9440 AGI VGA	\$169
X18004	IDE/SPG	\$39
X18005	High Speed I/O	\$59.95
X18013	IDE	\$29
X17072	ADAPTEC SCSI 16bit 1522A	\$189
X18161	*16bit ETHERNET NE2000 BNC	\$69
X18165	16bit ETHERNET RJ45 + BNC	\$79
X18169	16bit NE2000 +	\$119
X18159	Ethernet 10 base T Connector	\$119
X18151	S.P.G.	\$25
X18190	Printer 2-Port Sict Lpt 1-2 Card	\$39
X18191	Printer Port Sict Lpt 1-2-3 Card	\$49
X18141	High Speed Serial Card 1-Port 16550	\$49.95
X18041	High Speed Serial Card 2-Port 16550AFN	\$69
X18143	High Speed Serial Card 4-Port 16550AFN	\$189
x18157	S.P.G with 16550 UART CHIP	\$44.95
X18019	Games Card	\$19
X14260	SMART GAMES Cont	\$39.95
C18177	CD ROM Controller	\$45
	2.88 FDD Controller Card	\$125

Specifications subject to changes. \*X18161 without Boot Rom.

**VESA LOCAL BUS**

X17078	VESA SCSI IDE FLOPPY MULTI I/O ..	\$249
X18002	VESA MULTI I/O ..	\$39
X18099	VESA 1 Meg TRIDENT 9400 ..	\$129
X18100	VESA CIRRU5 5428 ..	\$139
X18184	VESA PARADISE Bahamas 1Meg ..	\$349
X18186	VESA IDE Cache Cont ..	\$349
X17071	VESA SCSI 2, IDE, Floppy, Multi I/O	\$299
X18087	VESA WD Accelerator Video Card ..	\$209
X18167	VESA VGA S3 Accelerator ..	\$169
X18185	VESA ET-4000 TSENG LABS ..	\$199
X18149	VESA CLOUD9 VGA 2 MEG ..	\$449
X18047	VESA IDE ENHANCED MULTI I/O ..	\$119
X18182	VESA CACHED IDE MULTI I/O ..	\$280

**PCI**

X17900	PCI 1M VGA TRIDENT 9440 ..	\$149
X18179	PCI IDE CONTROLLER ..	\$39
X18206	PCI VGA STEALTH 1MEG DRAM ..	\$279
X18207	PCI VGA STEALTH 2MEG DRAM ..	\$349
X18208	PCI VGA STEALTH 2MEG VRAM ..	\$529
X18209	PCI VGA STEALTH 4MEG VRAM ..	\$999
X18183	PCI VGA CIRRU5 LOGIC 5430 ..	\$175
X18510	FULL - DUPLEX PCI ETHERNET ..	\$149
X18514	FULL - DUPLEX ISA ETHERNET ..	\$99

**NEW PCI/ISA 486 MOTHERBOARD**

**XJ8508 \$209**

Support all members of 486 family, and features a WRITE Back/WRITE THROUGH secondary cache memory from 256K in size. Support PCI local bus architecture, ISA bus architecture and integrate a High Performance PCI IDE Controller on-board. Support Dark Green Function (SMM mode of SMI-CPU).

**CPU:** • Intel 80486SX/DX/DX2/SL Enhanced 25/33/50/66 MHz  
 • Intel 80486DX4 75/100MHz • AMD486DX/DX2/DX4 40/66/80/100MHz • Cyrix Cx486DX/DX2 40/50MHz • UMC U55 33MHz SIMM module. **System Memory:** • 4 x 72pin SIMM module • flexible memory size from 2MB to 128MB Cache  
 • Support 0/128/256/512KB secondary cache on board with either Write Back or Write through mode. **On-board IDE:** • Support 4 IDE Device and Enhanced IDE Function. **I/O Bus Slots:** • 32-bit PCI Local Bus slot x 3 • 8-bit XT Bus slot x 1 • 16-bit AT Bus slot x 3. **Board Size** - 220 x 220mm

**FREE PACK & POST / FREE PACK & POST / FREE PACK & POST**

**ROD IRVING ELECTRONICS PTY. LTD.**  
 YOUR FIRST CHOICE IN QUALITY ELECTRONICS. A.C.N. 005 428 437  
**ROD'S HOTLINE 1-800-33-5757**  
 MAIL ORDER LOCAL CALLS (03) 9543 7877

## COMPUTER FANS SUPA SPECIAL!

COMPUTER SERVICEMAN - KEEP A SELECTION OF THESE FANS IN YOUR TOOLBOX!

**CLEAR COMPUTER FAN** FOR POWER SUPPLY REPLACEMENT

**500 only left, be quick!**

12V DC 80MM (3.15") ROTARY DC FAN- 12V 0.11A  
 T12469 **\$19.95** 1-9 10-99 **\$9.95 \$8.95**

## QUALITY FANS

Suitable for power amps, computers, hotspot cooling etc. Anywhere you need plenty of air!



QUANTITY: 1-9 10-99  
 • 240V 4 5/8" T12464 \$14.95 \$12.95  
 • 240V 4 5/8" T12466 \$14.95 \$12.95  
 • 115V 3 1/2" T12467 \$14.95 \$12.95

## PENTIUM COMPUTER FAN

Suit 90MHz cpus  
 H10612 **\$24.95**



## PENTIUM COMPUTER FAN

For 60/66MHz cpus  
 H10613 **\$24.95**

## COMPUTER FAN

The easy way to cool your CPU

H10611 1-9 10+  
**\$14.95** \$12.95 \$10.95  
**GREAT PRICE!!**



## STEAM ENGINE

GREAT EXECUTIVE STRESS RELIEF DEVICE. YES YOU CAN ACTUALLY BLOW OFF STEAM WITH THIS!



**\$129** **WAS \$139**  
**A95000**  
 YES! STEAM ("DONKEY") ENGINE- CAT No. A95000. Every child should have one of these. Great for mom and dad to play with as well. • Easy to operate • Runs on Methylated Spirits • Steam engine produces sufficient horsepower to run other mechanical toy apparatus. • Easy to maintain, simply oil the appropriate parts. • Operating instructions included

## FLASHING LED

Flashing 12VDC LED alarm indicator. Small 5mm LED size in bezel housing.

• Hole size: 7mm  
 • Max panel thickness: 4mm

S15087  
**\$4.95**



CHEAP PROTECTION FOR YOUR CAR. EASY TO INSTALL AND WIRE UP.

## SECURITY TORX DRIVER SET

Tool set with ratcheted handle and multiple bits. Supplied with security torx drivers and standard sized attachments. Total of 29 pcs.

- Ratchet handle
- Bit holder
- Socket adaptor
- 8 star bits T8/T9/T10/T15/T20/T30/T40
- 4 slotted bits 4/5/6 & 7mm
- 2 hex bits H3/H4
- 7 hexagonal sockets 4/5/6/7/8/9 & 10mm

T12177  
**\$29.95**


Contains 29 pieces & the handle to get torx bits



Illustration of bits is only indicative of comparative sizes and is not true to actual size.
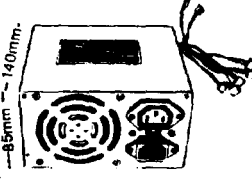
## 200W POWER SUPPLY


Come with flying leads. OUTPUT: 220W INPUT AC REQUIREMENTS: High range 180-265VAC Monomant 100-240VAC



X11104  
 1-9 10+  
**\$59.95 \$49.95**

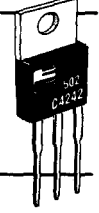
## SWITCHMODE POWER SUPPLY TRANSISTORS

2SC4242 T90764  
**IN STOCK!** 1-9 10+  
**\$7.95 \$6.95**


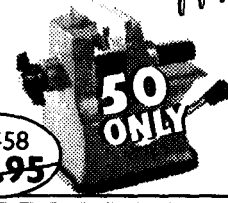
## MINI VISE

For hobbyist or craftsman. Keep one in your workshop for those little jobs!



**\$7.95** T12458 **\$9.95**

## NEW 6 TOOLS IN 1

## HOT-SOL SERVICE KIT

A multifunctional tool holder that can be used for:

- Soldering (up to 400°C)
- Heat Shrinking
- Repairing
- Cutting
- Torch (up to 1300°C)

T12660  
**\$29.95**

Runs on standard butane gas lighter fuel. Up to 60 minutes continuous use. 5 tips included.



## MULTIMEDIA SPEAKERS

### 120W SPEAKERS

#### NEW AMPLIFIED STEREO SPEAKERS FOR YOUR MULTIMEDIA SYSTEMS:

A whopping 120W set of speakers- magnetically shielded stereo speakers with plug & play feature. 120 Watt with • 4" woofer speakers • 2" tweeter speakers • Magnetically shielded • Frequency response: 20 - 20K Hz • Impedance: 4 ohm • Build-in power booster • PC and Macintosh compatible • Bass/treble/volume control • Dimension: 220 (H) x 140 (W) x 180 (D) mm • Cord length: 6' to source.



C10181  
**\$109.95**

ERROR & OMISSION EXCEPTED. PRICES CHANGE WITHOUT NOTICE.

## DISK BOXES

- C16020 5.25" HOLDS 100 DISKS \$5.95 HIGH IMPACT PLASTIC
- C16040 5.24" HOLDS 40 DISKS \$4.95 4 dividers with tag holders
- C16046 3.5" HOLDS 90 DISKS \$8.95 Strong lock for security

## GAS SOLDERING KIT

A multi-purpose unit that is available in this model as a gas soldering iron tool with solder tips. Can also be used as a: • Blow Torch • Hot Knife • Polyform Cutter or a Flat Flame depending on model purchased.



T12661  
**\$24.95**  
 MORE VALUE FOR MONEY PRODUCT!

## 50 WATT AMPLIFIED COMPUTER SPEAKER

Magnetically shielded speakers for monitor, drive an disc protection.

OVAL SPEAKER 50 x 90mm  
 Power Output: 50 watt P.M.P.O.  
 Frequency resp: 20 - 20K Hz

Speaker Impedance: 4 ohm  
 Cord length: 6' to source  
 Power on/off  
 Volume control  
 Dimension: 198 (H) x 75 (W) x 95 (D) mm



C10182  
**\$59.95**

**FREE PACK & POST FOR ORDERS WORTH \$25 OR MORE & UNDER 3KG- OFFER VALID ONLY UNTIL 31ST JANUARY 1996.**

**FREE PACK & POST FREE PACK & POST FREE PACK & POST**

**FREE PACK & POST FREE PACK & POST FREE PACK & POST**

**FREE PACK & POST FREE PACK & POST FREE PACK & POST**

**ROD IRVING ELECTRONICS PTY. LTD.**  
 YOUR FIRST CHOICE IN QUALITY ELECTRONICS A.C.N. 005 428 437 ESTABLISHED SINCE 1977

**ROD'S HOTLINE**  
 1 800 33 5757 MAIL ORDER LOCAL CALLS (03) 9543 7877

**REMOVABLE CARTRIDGE ZIP DRIVES**

WITH ACCESS SPEED OF 13.5MS, WHICH IS ALMOST ON PAR WITH TODAY'S HARD DISK DRIVES SPEED, "ZIPPY" ACCESS TO DATA HAVE NEVER BEEN SO QUICK AND EASY! AS FAST AS A HARD DISK DRIVE.

This is the most powerful and efficient peripheral you can buy to compliment your computer system. EZ135 Drives combine the speed and reliability of hard drives to enable you to store and retrieve files lightning fast, with the removability of a floppy to ensure you'll never run out of space. EZ135 Drives are for people who want to:

- Let family and friends use their own cartridges for personal storage
- Let kids have their own space for games and homework
- Store and run entire Multimedia presentations
- Work with large graphics and sound files
- Download and save pictures and sound from computer network without clogging up their computers
- Keep private files off their computers, but easily accessible
- Free up their hard drives without using complicated compression software, or virtual memory
- Exchange files with other EZ135 users
- Stop using endless floppy libraries ....and much more!

IDE (Internal) C11878 .....	\$395
SCSI II (External) C11876 .....	\$449
135MB cartridge C11890	
1-9 ....\$49 10+ ....\$42.95	

**SYQUEST EZ135 DRIVES**

**EASY TO USE - SAVE ON THOUSANDS OF FLOPPIES!**

**SPECIFICATIONS:**

Interface:	ATA/IDE
Capacity:	135MB (formatted)
Average Seek Time:	13.5msec
Data Transfer Rate:	
Burst	4.0MB/sec
Sustained Max	2.4MB/sec
Reliability and Maintenance:	
MTBF	200,000 hours (P. O. H)
Preventative Maintenance:	None
Dimensions:	254 (H) x 101 (W) x 150 (L) mm
Weight:	425gm
Warranty:	
Drive	2 years
Cartridge	5 years

**LATEST KITS RANGE**

-For our complete range of kits see pages 175-184 of our 1995-96 annual catalogue. If you don't own one, fill in the coupon below and we will send you a free copy. The latest kits project update is also published in our monthly magazine- "Communicate!". If you are not on our subscription list, just write to us and enclose \$12 for one years' subscription.

**LOW COST MICRO-BASED ESR & LOW OHMS METER**

**K10730 \$44.95**



If you repair switch-mode supplies, TV receivers, computer monitors, vintage radios, or similar equipment, and/or if you need to measure very low values of resistance, this project can save you lots of time and aggravation. It measures an aspect of electrolytic capacitors performance which is very important, but normally very difficult to check: the equivalent series resistance, or "ESR" EA JAN '96

**PC DRIVEN EGO SENSOR ANALYSER**

**K10735 \$39.45**

NO PICTURE AVAILABLE AT TIME OF PUBLICATION

With car engine management systems becoming more and more sophisticated (and complex), it is getting increasingly difficult to find out what's happening "under the hood". This low cost analyser, combined with any IBM PC and some special software can provide a large amount of information on your car's performance. EA JAN'96

**ENGINE IMMOBILISER**

**K10720 \$35.95**



This circuit will immobilise your car if a thief tries to start it. Fit it to your car as cheap insurance. If a thief tries to steal your car, the engine will repeatedly stall and he will move to easier pickings. SC Dec'95

**SMART DUAL 12V BATTERY CONTROLLER**

**K10740 \$59.95**




ASSEMBLED & TESTED \$99.95

This auxiliary battery manager takes full advantage of a dual battery setup's capabilities, by controlling when and how the "auxiliary" battery is connected to the electrical system. It's fully automatic, will cost you far less than an equivalent commercial unit, and is particularly suited to the new breed of deep-cycle auxiliary batteries EA JAN'96

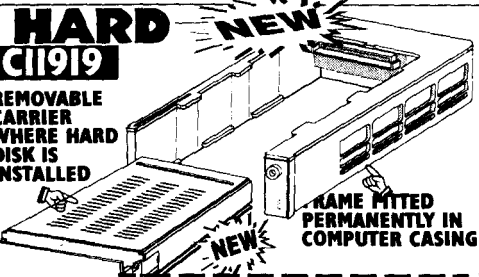**REMOVABLE HARD DISK DRIVE CARRIER**

A great idea that answers the prayers of many network managers in organisations that are constantly in need of exchanging data between internal departments. Faster even than attempting huge amount of data transfer across network! Simply remove the hard drive carrier holding the required hard drive and then simply insert it into the computer system that needs to access the same data. Very much like the removable cartridge drives system, but capable of holding as much data as the hard drive's capacity-which can be anything from 540mbytes to Gigabytes!



**IF YOU ARE CONSTANTLY EXCHANGING HUGE AMOUNT OF DATA BETWEEN COMPUTERS- YOU NEED ONE OF THIS!**

**IDEAL FOR HOME/WORK OFFICE SITUATIONS**

- Data security- simply remove the disk and lock it away
- Multiple operating systems
- Requires 1 5/4" drive mounting bay
- Suitable for IDE hard drives only

**NOTE:**

- Computer must be turned off to insert/remove or change hard disk
- System CMOS must be set if using drives with different geometry


**JUST LOOK AT THIS PRICE- SUCH A GREAT IDEA SHOULD BE WORTH MUCH MORE..**

**Complete Kit including:**  
**Removable Carrier & Frame...\$99**

Note: Only available as a complete kit at the moment

**GEIGER COUNTER**

**K10715 \$169.95**



Are you concerned by the Nuclear tests in the Pacific and China? Worried about a possible increase in the amount of background radiation? Then check it out with this Geiger counter. It will detect alpha, beta and gamma radiation and has an audible output SC Oct'95

Geiger Tube available at \$119.00

**LOW COST FIVE BAND EQUALISER**

**K10725 \$32.95**



Live up your keyboard, guitar or music system with this 5-band equaliser. It only uses a few low cost parts and will enable you to "customise" the sound of your system just by twiddling a few knobs. SC Dec'95

**Jumbo 350**



**Protect Your Business. Streamline Your Office.**

- Safeguard Your Business. Protect Your Data Against Accidental Deletion, Theft, Fire, Floods...
- By Performing Regular Tape Backups
- Save Disk Space - Move Seldomly Used Files to Tape
- Archive Business and Personal Records
- Transfer Large Files Between Offices

**EASY TO USE SUPPORT SOFTWARE:**

- Includes Powerful, Easy To Use Software: Colorado\* Backup For DOS, Colorado Backup For Windows Lite\* Data Compression\* Menu Or Command Line Operation\* Point And Click Mouse Support\* Supports Most Popular Networks (Novell\* NetWare\*, NetWare Lite\* and LANtastic\* Certified)

**OTHER MODELS:**

X20250 700MB TapeDrive .....	\$499
X20254 1400MB Tape Drive ...	\$799

**Minicartridges and Options Sold Separately**

X20248 350MB Tape Cartridge	\$49.95	\$45.00
X20252 700MB Tape Cartridge	\$69.95	\$59.95
X20256 1400MB Tape Cartridge	\$89.95	\$79.95

**Compatibility and Performance Features:**

- Up To 340 Megabyte Capacity Using Data Compression and 425" Tape
- Typical 100 MB Backup In About 20 Minutes
- Auto-configuring Installation
- User Defined Backup and Restore, Compare and Error Reporting

**350MB Tape Drive**

**X20246 \$349**

**NEW LOWER PRICE \$299**

**FREE PACK & POST FOR ORDERS WORTH \$25 OR MORE & UNDER 3KG- OFFER VALID UNTIL 31ST JANUARY 1996.**

ERRORS & OMISSION EXCEPTED. PRICES CHANGE WITHOUT NOTICE

**ROD IRVING ELECTRONICS FREE CATALOGUE**

YOUR FIRST CHOICE IN QUALITY ELECTRONICS ERRORS & OMISSION EXCEPTED PRICES CHANGE WITHOUT NOTICE

**MAIL ORDER COUPON**

Please send me the following items:  
 IF NOT ENOUGH SPACE PLEASE ATTACH SEPARATE LIST

**SEND TO:**  
**FREE POST**  
 ROD IRVING ELECTRONICS P/L  
 REPLY PAID 8888,  
 BAG 620,  
 CLAYTON SOUTH, 3169.  
 TOLL FREE: 1-800 33 5757

Name: .....

Address: .....

..... P/Code: .....

Phone: ..... Date: .....

B/CARD  VISA CARD  AMEX  DINERS TOTALS.....

Signature: ..... Exp. Date: .....

**NORMAL PACKAGE & POSTAGE:**

\$1-\$9.95	\$3.00	\$50-\$99.95	\$6.00
\$10-\$24.95	\$3.50	\$100-\$199	\$7.00
\$25-\$49.95	\$4.00	\$200+	FREE

The rates shown here apply to Australia Post Surface Mail within Australia only. Orders above 5kg or containing fragile parts will be sent by road freight at our discretion and charged to you. EANP/96



## RITRON QUAD SYSTEM

**UPGRADE TO POWER MULTIMEDIA COMPUTING TODAY!**

Choosing the right system configuration has never been so easy - simply match your needs & budget to the choices here and you are well on the way to exploring the world of multimedia. Each & every system is powerful in its own rights and will handle today's complex & software applications quite easily.

**INCLUDE 7 FREE CD SOFTWARE TITLES:**  
Microsoft- Works/Money/Encarta '95/Dangerous Creatures/Golf & CD Sampler and Yellow & White Pages Phone Disc. • **20 Mbytes FREE SHAREWARE GAMES.**



**4x QUAD-SPEED CD-ROM DRIVE**

- Quad-Speed CD-ROM drive • 4 MEG RAM • 850 MEG H.D.D. • 1 MEG Video Card • 14" SVGA N.I. Mon.=1024 x 768mm 0.28mm D.P. • 1.44 3.5" F.D.D.
- Ritron Mouse Pad • Mouse & Joystick • 101 Keyboard • 16-bit Sound Card • Magnetic Shielded Spkr
- Workgroups for Windows 3.11 or Windows 95

**4 YEAR PARTS & LABOUR WARRANTY (FIRST 2 YEAR ON-SITE) MELB MET AREA 4 HOUR FREE TRAINING COURSE**

CPU CHOICES	TAX EX	TAX INC
DX2-66 .....	\$1599	\$1799
DX2-80 .....	\$1629	\$1829
DX4-100 .....	\$1650	\$1890
Pentium™ 60 .....	\$1625	\$1865
Pentium™ 75 .....	\$1820	\$2100
Pentium™ 90 .....	\$1990	\$2190
Pentium™ 100 .....	\$2190	\$2290
Pentium™ 120 .....	\$2290	\$2510
Pentium™ 133 .....	\$2540	\$2990

With HEX-SPEED CD-ROM DRIVE... \$250 extra FREE HOME DELIVERY & SETUP- MELBOURNE METRO AREA ONLY

## RITRON QUAD SYSTEM PRO

**UPGRADE TO POWER MULTIMEDIA COMPUTING TODAY!**

This range of great systems offer higher performance levels with 8 Meg of RAM, a huge 1 GIG hard disk drive and the Quad-Speed CD-ROM drive. Video or animation files will play more smoothly than ever before, off this CD-ROM drive. Internet connection is child's play with these powerful systems.

**INCLUDE 7 FREE CD SOFTWARE TITLES:**  
Microsoft- Works/Money/Encarta '95/Dangerous Creatures/Golf & CD Sampler and Yellow & White Pages Phone Disc. • **20 Mbytes FREE SHAREWARE GAMES.**



**4x QUAD-SPEED CD-ROM DRIVE**

- Quad-Speed CD-ROM drive • 8 MEG RAM • 1 GIG Hard Disk Drive • 1 MEG Video Card • 14" SVGA N.I. Monitor- 1024 x 768mm 0.28mm Dot Pitch • 1.44 3.5" F.D.D. • Ritron Mouse Pad • Mouse & Joystick • 101 High Quality Keyboard • 16-bit Sound Card • Magnetically Shielded Speakers • Workgroups for Windows 3.11 or Windows 95

**4 YEAR PARTS & LABOUR WARRANTY (FIRST 2 YEAR ON-SITE) MELB MET AREA 4 HOUR FREE TRAINING COURSE**

CPU CHOICES	TAX EX	TAX INC
DX2-66 .....	\$1749	\$2019
DX2-80 .....	\$1799	\$2049
DX4-100 .....	\$1860	\$2140
Pentium™ 60 .....	\$1860	\$2100
Pentium™ 75 .....	\$2080	\$2390
Pentium™ 90 .....	\$2290	\$2590
Pentium™ 100 .....	\$2390	\$2720
Pentium™ 120 .....	\$2495	\$2810
Pentium™ 133 .....	\$2690	\$3120

With HEX-SPEED CD-ROM DRIVE... \$250 extra FREE HOME DELIVERY & SETUP- MELBOURNE METRO AREA ONLY

### SOUND BLASTER VALUE I6/6X-17

**HEX SPEED**  
X17340  
**\$519**

Combines SBBlaster 16 Value with the Creative Hex Speed, Photo-CD compatible, Multi Session, CD-ROM drive & includes SBS30 stereo speakers plus 17 CDs software titles.

### SB PERFORMANCE CD32/6X

**HEX SPEED**  
X17342  
**\$639**

Combines SBBlaster 32 Plug and Play compliant audio card with the latest Creative Hex speed CD-ROM drive. Includes CS100 stereo speakers, Telex microphone and bundled with 23 software titles.

**Removable Cartridge ZIPPY DRIVE**  
"zippy" 13.5ms access speed-135MB cheap storage & backup. As fast as a hard drive  
**\$395**

**SYQUEST EZ135 4MB/SEC DRIVES**  
EASY TO USE  
**ON DISPLAY AT OUR CITY STORE**

### UPGRADES & PERIPHERALS FOR YOUR SYSTEMS

#### MULTIMEDIA UPGRADE KIT

Upgrading to multimedia has never been so easy - simply follow the installation instructions. All CD-ROM drives versions are Kodak PhotoCD™ compatible. Includes the same 16-bit Sound Card, Stereo Speakers and great Software titles: Microsoft-Encarta'95/Works/Money/Golf/Dangerous Creatures & CD Sampler which previews over 55 MS titles, has 8 Windows games.

Dual-Speed Version .....	\$329
Quad-Speed Version .....	\$369
Hex-Speed Version .....	\$599

**CD ROM DRIVES**

DUAL-SPEED CD ROM DRIVE	
IDE INTERFACE .....	\$149
PANASONIC QUAD-SPEED CD ROM DRIVE IDE INTERFACE .....	\$249
PANASONIC 502J Panasonic Interface .....	\$169
NEW HEX-SPEED CD ROM DRIVE .....	\$399

**MEMORY**

	1-9	25+	100+
30 PIN SIMM			
1M x 9-70 With Parity	\$65	\$63	\$57
4M x 9-70 With Parity	\$215	\$209	\$189
72 PIN SIMM FOR PENTIUM™ Processor M.B.			
4M X 8-70 No Parity	\$215	\$209	\$189
4M X 9-70 With Parity	\$235	\$239	\$229
8M X 9-70 No Parity	\$419	\$389	\$369
16M X 8-70 No Parity	\$809	\$799	\$769
16M X 9-70 With Parity	\$899	\$879	

**Windows 95**

Upgrade ACAD 3-H .....	\$95
Upgrade 3-H .....	\$135
Upgrade CD .....	\$135
Full 3-H .....	\$269
Full ACAD 3-H .....	\$179

**FLOPPY DISK DRIVES**

1.44 F.D.D. ....	\$55.00
1.2MB F.D.D. ....	\$89.00

#### SUPA MOTHERBOARD UPGRADES

486DX2-66# L B No Cache .....	\$199
486DX2-66#256K Cache L.B .....	\$259
486DX2-80#256K Cache L.B NEW! .....	\$279
486DX4-100#256K Cache L.B NEW! .....	\$299
PENTIUM™ 60MHz/256K VESA/PCI .....	\$299
PENTIUM™ 75MHz/256K VESA/PCI/ISA NEW! .....	\$599
PENTIUM™ 90MHz/PCI/ISA .....	\$729
PENTIUM™ 100MHz/PCI/ISA .....	\$799
PENTIUM™ 120MHz/PCI/ISA .....	\$899
PENTIUM™ 133MHz/PCI/ISA .....	\$1199

#### HARD DRIVES VOICE COIL IDE HD

Capacity	Av. Access	Tax Inc.	Tax Ex.
260M	16ms	\$244	\$200
420M	12ms	\$293	\$240
540M	12ms	\$398	\$345
640M	12ms	\$318	\$260
850M	11ms	\$341	\$280
1.08GB	12ms	\$391	\$320
1.27GB	10ms	\$476	\$390
1.27GB WESTERN DIGITAL	10ms	\$509	\$409
1 GB SCSI HD	10ms	\$561	\$460
1.6GB WESTERN DIGITAL	10ms	\$610	\$500

#### NEW MONITOR RANGE

- 14" Interlaced 1024x768 (0.28mm Dot pitch) ..... \$349
- 15" XGA Digital MPRII 1280x1024 ..... \$599
- 17" XGA Digital MPRII 1280x1024 ..... \$999
- 17" XGA Digital MPRII 1600x1280 (0.26mm Dot Pitch) ..... \$1395
- NEW! 20" XGA Digital MPRII ..... \$1999

**VERBATIM DISKS**

PLASTIC BOXES		CARDBOARD BOXES			
DESC.	1-9	10+	DESC.	1-9	10+
3 1/2 DS/DD	\$18.95	\$17.95	3 1/2 DS/DD	\$19.95	\$16.95
3 1/2 DS/HD	\$22.95	\$19.95	3 1/2 DS/HD	\$19.95	\$17.95
5 1/4 DS/DD	\$12.95	\$10.95	5 1/4 DS/DD	\$11.95	\$10.95
5 1/4 DS/HD	\$16.95	\$14.95	5 1/4 DS/HD	\$14.95	\$13.95

### RITRON COMPUTER SYSTEMS

**NOW WITH 540 MB H.D.D.**

CPU TYPE	TAX EX	TAX INC
486DX2-66 .....	\$983	\$1199
486DX2-80 .....	\$1065	\$1299
486DX4-100 .....	\$1099	\$1340
Pentium™ 60* .....	\$1099	\$1341
Pentium™ 75* .....	\$1395	\$1699
Pentium™ 90* .....	\$1535	\$1872
Pentium™ 100* .....	\$1720	\$2098
Pentium™ 120 .....	\$1890	\$2305
Pentium™ 133 .....	\$2050	\$2501

External 250K Cache  
**4 YEAR PARTS & LABOUR WARRANTY**

All systems include: 4 MEG RAM \$40 MEG H.D.D. GREAT VALUE! • 1.44 MEG 3.5 FDD • Mini or Baby AT casing • 2 SPG Ports • 101 Keyboard • 3 Slots VESA Local Bus Motherboard • 14" SUPER VGA (1024 X 768) (0.28" DOT PITCH) Colour Monitor • VLB 1MB VGA Cards are supplied in 486 machines AT NO EXTRA COST (Up to 1280 x 1024) Pentium systems now come with PCI Cards and should be bought with 8MB of RAM

**FREE 3 HOUR TRAINING COURSE (MELB. ONLY) FOR ALL COMPUTER SYSTEMS INCLUDING MULTIMEDIA SYSTEMS**

### Intel™ OverDrive™ Processors

**Upgrade to Intel™ OverDrive™ processor power Now! Speed up all your software!**

OverDrive processors accelerate all applications running under MS-DOS, Windows, OS/2 & UNIX.

486DX2-66 OverDrive .....	\$189
486DX4-100 OverDrive .....	\$269

### NEW MOTHERBOARDS

**OPTI895 GREEN PC Mainboard .....** \$199  
DX2-66 CPU installed ..... \$229  
DX2-80 CPU installed ..... \$249  
DX4-100 CPU installed ..... \$289

With 4 x 72 pin SIMM sockets 256K REAL CACHE

### 80486 GREEN Mainboard .....

**80486 GREEN Mainboard .....** \$139  
DX2-66 CPU installed ..... \$189  
DX2-80 CPU installed ..... \$209  
DX4-100 CPU installed ..... \$229

With 2 x 72 pin & 4 x 30 pin SIMM sockets

### LAPLINK CABLES

Connect two computer with these cables and transfer files quickly or "play" games such as DOOM, HERETICS, etc. interactively! (\*Serial version only)

Parallel DB25 M/M 2 Metre.....\$9.50  
Serial DB9 F/F & DB25 25 pin.....\$12.50

### EPSON PRINTERS-NEW LOWER PRICES!

LQ300 264 Cps Draft, 9 pin dot matrix .....	\$249
With colour option .....	\$349
LQ300 216 Cps Draft, 24 pin dot matrix .....	\$429
With colour option .....	\$529
Stylus Pro 720dpi full colour A4 NEW! .....	\$1399
Stylus Pro XL 720dpi full colour A3 NEW! .....	\$2899
Stylus 820 720x360dpi b/w A4 NEW! .....	\$419
Stylus Colour IIs 720x360dpi full colour A4 NEW! .....	\$569
Stylus Colour II 720x720dpi full colour A4 NEW! .....	\$729
EPL 9000 600dpi, 8ppm, laser, A3NEW! .....	\$3499

### MICROSOFT SIDEWINDER 3D PRO

• Digital tracking joystick • Works with Windows or DOS-based game • Precise & swift response • Bundled with MechWarrior 2 CD-ROM ver. the hottest game in town!

**Great Value! WOW! WHAT A RIPPER OF A JOYSTICK!**

**\$125**

### THE ROD IRVING ELECTRONICS

FOR THE SERIOUS COMPUTER USER A.C.N. 005 428 431  
ESTABLISHED SINCE 1977. 100% AUSTRALIAN OWNED. ALWAYS AHEAD WITH THE LATEST TECHNOLOGY & PRODUCTS.  
HEAD OFFICE: 56 Renner Rd Clayton, Victoria, 3168 Ph: (03) 9543 7877  
MELB: 48 A'Beckett St. City. Ph: (03) 9663 6151. Fax: (03) 9639 1641 Computers: (03) 9639 1640  
VERMONT: 190 Rooks Rd. Ph: (03) 9874 8888. Fax: (03) 9874 2288  
OAKLEIGH: 240C Huntingdale Rd. Ph: (03) 9562 8939. Fax: (03) 9562 8940  
NORTHCOLE: 423 High St. Ph: (03) 9489 8866. Fax: (03) 9489 8131  
BOX HILL: 1031 Maroondah Hwy. Ph: (03) 9899 6033. Fax: (03) 9899 0156  
ADELAIDE: 241-243 Wright St. Ph: (08) 211 7200. Fax: (08) 211 7273  
SYDNEY: 74 Parramatta Rd. Stanmore. Ph: (02) 519 3888. Fax: (02) 516 5024

BLUESTAR COMPUTERS: 271 Maroondah Hwy. Ringwood Ph: (03) 9870 1800  
Fax: (03) 9879 3027 TRADING HOURS: Mon-Fri 9am - 5.30pm. Sat 9am - 1pm

City store open till 8pm on Fridays. Box Hill store open till 3pm on Saturdays.  
Tax Exempt sales: RITRONICS WHOLESALE Ph: (03) 9543 2166 Fax: (03) 9543 2648  
RIE BULLETIN BOARD Ph: (03) 9562 7877 For Specials, info & Shareware  
E-MAIL: rie @ozemail.com.au  
MAIL ORDER: Ph: (03) 9543 7877 Fax: (03) 9543 8295  
Mail Order Hotline 1-800 33 5757

Pentium™ OverDrive™ & Intel486™ are registered trademarks of the Intel Corporation EAGGJ96

## Construction Project:

# LOW COST MICRO-BASED ESR & LOW OHMS METER

If you repair switch-mode power supplies, TV receivers, computer monitors, vintage radios, or similar equipment, and/or if you need to measure very low values of resistance, this project can save you lots of time and aggravation — as it has for me. It measures an aspect of electrolytic capacitor performance which is very important, but normally very difficult to check: the equivalent series resistance, or 'ESR'.

by **BOB PARKER**

Some wise person once said, "The reliability of any piece of electronic equipment is inversely proportional to the number of electrolytic capacitors in it", and I doubt that many service technicians would disagree!

Especially now that switch-mode power supplies (SMPSs) have been commonly used in domestic VCRs and TVs, etc for a decade or so, one of the most likely components to fail is the humble electrolytic.

The symptoms can be as diverse as a VCR's playback picture swimming in tiny dots, up to SMPSs mysteriously self destructing.

As a service technician myself (though I'd prefer to be a full-time designer!), I was just about tearing my hair out because of the difficulty in determining which electros were faulty and which ones were still OK, in SMPSs and other equipment. I wanted to be able to check electros in circuit, with the power safely disconnected.

Why not use a readily available capacitance meter? Because when electros go faulty, they normally don't lose their capacitance significantly (as many technicians assume they do). Rather their equivalent series resistance (ESR) 'goes through the roof'. Capacitance meters don't tell you this; about the best they can do is give a low reading if the electro is nearly open circuit.

### About ESR...

So what exactly is an electrolytic's equivalent series resistance?

Electrolytics depend on a water based electrolyte, soaked into a strip of porous material between the aluminium foil plates, to complete the 'outer' electrical

connection to the aluminium oxide dielectric coating on the anode foil.


The electrolyte has electrical resistance which, along with the (negligible) resistance of the connecting leads and aluminium foil plates, forms the capacitor's equivalent series resistance.

Normally the ESR has a very low value, which stays that way for many years unless the rubber seal is defective. Then the electrolyte's water component gradually dries out and the ESR creeps

up with time. The electro gradually acts more and more like a capacitor with its own internal series resistor...
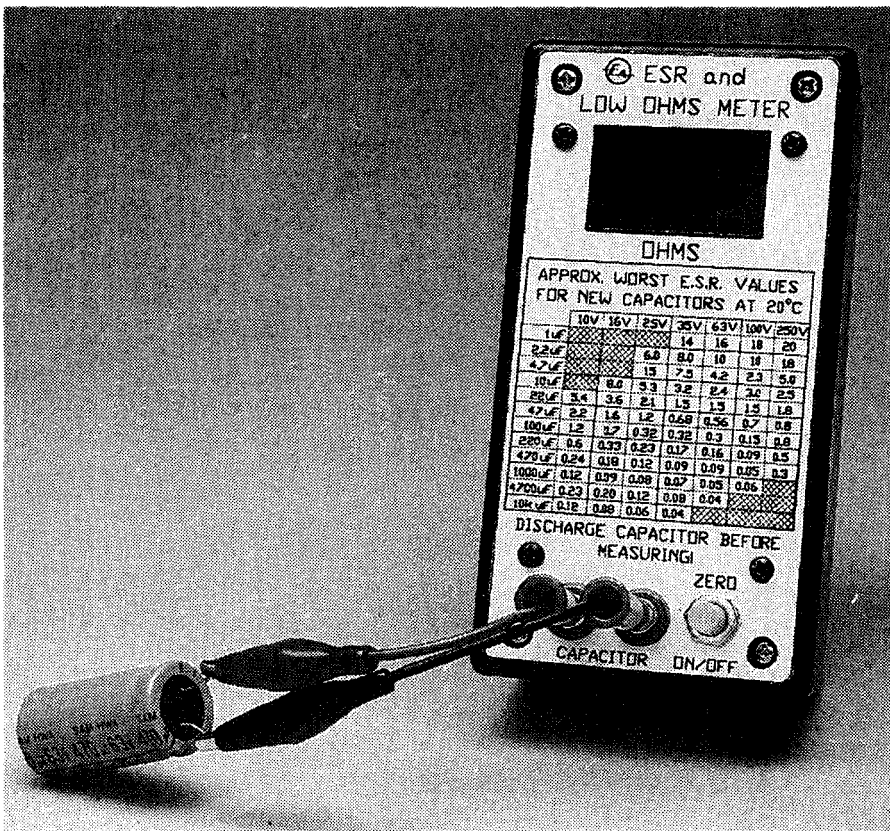
### Heat makes it worse

If an electro is subjected to high temperatures, especially from heat generated internally as a result of large ripple currents, the electrolyte will start to decompose and the dielectric may deteriorate — and the ESR will increase far more rapidly.



To make things worse, as the ESR increases, so does the internal heating caused by ripple current. This can lead to an upward spiral in the capacitor's core temperature, followed by complete failure — sometimes even explosive!

The service life of electros is approximately halved for every 10°C increase in temperature and, surprisingly, many are designed for a reliable operating life of only a few thousand hours at their maximum rated temperature and ripple current. (A year is only 8766 hours!)

Switch-mode power supplies place quite severe stresses on filter capacitors. Because of their compact construction, temperatures are high (that's why your PC's power supply is equipped with a fan), and the capacitors have to endure large ripple currents.

### Micro-based ESR meter

Necessity is supposed to be 'the mother of invention', but desperation works even better and I designed this ESR meter from scratch. It's based on a versatile Zilog Z86E0408 microcontroller — which already has two voltage comparators and two flexible counter/timers built in, greatly simplifying the rest of the circuit. A micro also allows the easy incorporation of some 'user friendly' features...

This instrument has three ESR ranges, with full scale readings to 0.99Ω, 9.9Ω and 99Ω respectively. The range is automatically selected by the micro, so your hands are free to hold the test leads. The accuracy of the prototypes was better than +/-5% of displayed reading, +/-1 digit. A single '-' on the left-hand display indicates a reading above 99Ω.

The readout is on two 0.5" (13mm) seven-segment LED displays, plus two 3mm decimal point LEDs which are needed because the display decimal points are on the wrong side for this application. If you forget to turn the power off, the micro will do it for you when the displayed reading has remained the same for two minutes. This feature can be disabled for uninterrupted operation from a 9V plugpack.

When the battery voltage is nearly too low for the circuit's

5V regulator to function correctly, the Z86 reduces the power to the LED displays and flashes a 'b' on the right-hand one in the 'off-scale' condition, to warn you to look for a new battery.

### Meter operation

There's a single pushbutton, which has three functions: one press turns the power on, and another press will switch it off again if the measured resistance is 1Ω or more.

A push of the button with the leads shorted together will cause their resistance value to be subtracted from all subsequent readings, as long it's less than 1Ω.

Before making a measurement on an electrolytic, first discharge it. I find a 100Ω 5W resistor does this well. Then connect the test leads — either way around. If your capacitor is still in circuit (with the power OFF!), you're likely to get quite an accurate reading, because it

should be the component with by far the lowest high-frequency impedance.

The circuit's test signal has a peak open-circuit voltage of 600mV (maximum 100mV peak at full-scale reading), so it won't make diodes or transistors conduct and cause measurement errors. Compare the reading you get with the front panel table, to get an idea of whether the electro's ESR is about normal or significantly above it.

The table's approximate 'worst ESR' figures were taken from the Nippon Chemi-Con Aluminum Electrolytic Capacitors Catalog Number 4, as 100kHz impedance figures for their 'SXE', 'SXG' and 'LXA' capacitor series. They agree pretty closely with my own measurements of many new electros of assorted brands, styles, sizes and ages.

From my actual faultfinding experience with the prototypes, an electro's ESR needs to be many times the table value before it's likely to cause trouble.

### Low ohms uses

The instrument is very handy for measuring low values of resistance, too. But note that because it makes an AC measurement, it can't give a sensible indication of the DC resistance of inductive components, such as transformer windings or chokes.


I've used it to 'roll my own' low value resistors, by measuring off the required number of (milli) ohms of DSE catalog number W-3200 resistance wire, which I then formed into a spiral by wrapping it around a drill shank.

It can also locate short circuits on PC boards, by measuring actual track resistances. If the reading increases as you probe further along the track, you know you're going in the wrong direction!

You could also use it to confirm solid continuity of mains lead earth conductors, etc, etc...
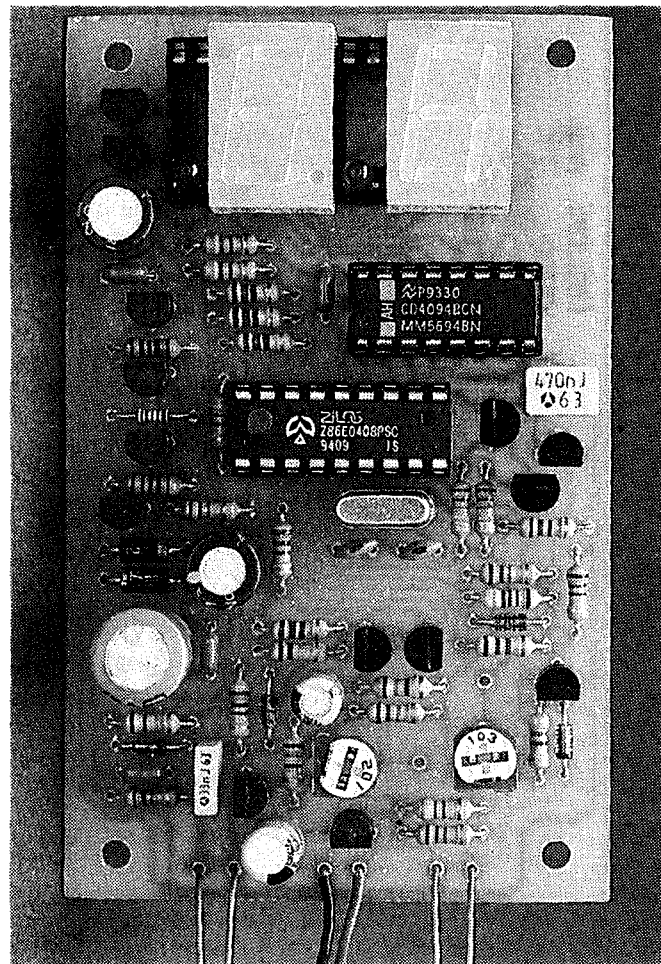
### What NOT to do

There are a few minor points to keep in mind, when using the meter. First, it can't identify leaky or



**A close up view of the ESR meter PCB, showing the position and orientation of all the parts — except the test lead jacks, push button and battery. Note that the LED displays and decimal point LEDs are mounted via a 28-pin IC socket.**

# Micro-based ESR and Low Ohms Meter


short-circuited capacitors — that's what the resistance ranges of normal multimeters are for! Also, avoid using self-retracting 'curly' test leads, because their inductance can cause small measurement errors.

Lastly, don't use the meter right next to an operating TV set or computer monitor — the high amplitude pulses radiated by the horizontal output stage can be picked up by the test leads and cause unstable readings.

## The circuit

Now let's have a brief look at how it all works, by reference to the schematic.

A push of the button switches on

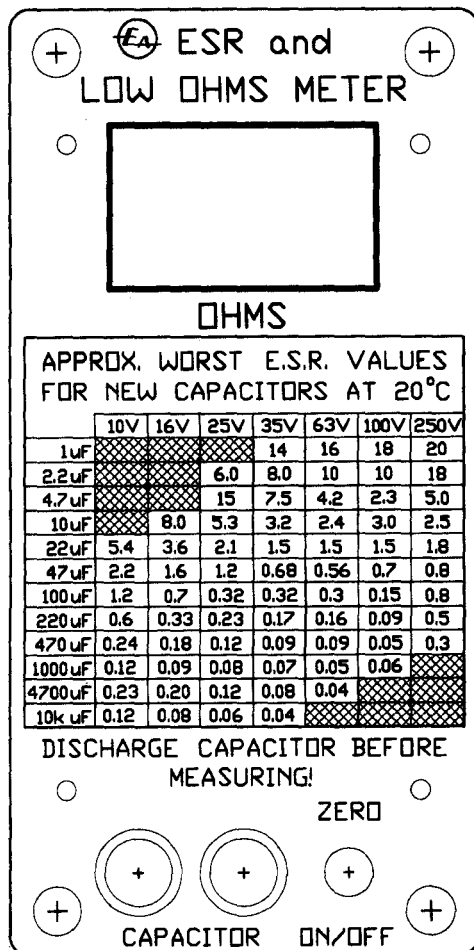

Bob Parker's artwork for the front panel of his ESR Meter. There's only one control — the pushbutton, which doubles as both the ON/OFF switch and the control to get the inbuilt micro to compensate for test lead resistance. To make the meter easy to use, he has included a table of expected maximum ESR values for the most common values of electrolytic capacitor.

Q1, supplying +9V to IC1, the 5V regulator. Once the Z86E0408 microcontroller ('Z86' for short) starts up, it forward biases Q2. This holds Q1 on, maintaining the 5V supply after you release the button.

The displays are driven by IC3, an eight bit serial-in parallel-out shift register. IC3's outputs are connected to both seven segment displays and the decimal point LEDs in parallel. Cathode driver transistors Q12 and Q13 are configured so that only one display and its decimal point LED can illuminate at a time, under control of the Z86's pin 18.

Every 5ms the Z86 serially updates the segment and decimal point data in IC3, and swaps displays; at this speed it appears both displays are continuously illuminated.

The Z86 starts a measurement by grounding its pin 4, switching on current mirror transistors Q9 and Q10 and causing C10 to begin charging at a constant rate. Under control of its firmware, the Z86 drives Q3, 4 or 5 to apply short current pulses of 0.5, 5 or 50mA, via C5/6, to the capacitor being tested.

The resulting voltage pulses, proportional to the electro's ESR, are amplified by Q7 and Q8 (no relation to the one in the Persian Gulf!), and compared with C10's voltage. Q6 functions as a ground reference switch.

A simple time measurement allows the Z86 to determine the amplitude of the voltage pulses and so the capacitor's ESR. At the end of each measurement, Q11 is used to discharge C10. Then the Z86 subtracts the test lead resistance (if it's been zeroed), and displays the value.

Now for the 'frills'...

**Battery voltage check:** The Z86 regularly allows C10 to charge to 2V. If the battery voltage sample on VR1's wiper (fed in via pin 9) drops below this 2V level, the 'battery low' warning condition is triggered.

**Protection:** Sooner or later this meter will find itself connected to an unexpectedly charged capacitor (or worse), so some protection has been built in. D3, D4, D5 and D6 are strategically placed to prevent destructive voltages from finding their way back to the microcontroller; D4 also limits the test voltage to 0.6V peak.

**The rest:** When the Z86 detects the button is pushed while measuring a resistance of one ohm or more, it switches off Q2 and displays ques-

tions marks until your finger leaves the button. Then Q1 switches off the battery supply.

Crystal XTAL1, C11 and C12 complete the Z86's clock oscillator, which provides the timing for all the meter's operations.

## Construction

As EA's photos show, every component except the pushbutton is mounted on a 57 x 95mm (2.25" x 3.75") PCB board, coded 96ESR1.

Before fitting any components to the PCB, first illuminate its component side with a bright light, and examine the copper side carefully for fine track breaks and especially whiskers or bridges — particularly where tracks pass between IC socket pads. If necessary, drill the corner mounting holes to accept 3mm screws, and enlarge the trimpot mounting holes if they're too small.

If you're planning to run the ESR & Low Ohms Meter from a 9V plugpack, leave R25 (47k) off the PCB. This will disable the two minute automatic switchoff function, and also the low battery warning...

When you're soldering the components to the PCB, using the overlay diagram as a guide, bear in mind that the PCB is tightly packed and the solder pads are small. The last thing this circuit needs is solder bridges and bad joints — so please use decent 0.71mm or similar fine diameter solder!

Begin installing the components, starting with the lowest-height ones (resistors and diodes), and working your way up to the tall ones. Note that the displays and LEDs are mounted on a 28-pin IC socket, not soldered directly to the PCB!


It's a good idea to double-check, especially at the beginning, that you're putting each component's leads into its correct holes. They're rather closely-spaced...

Take care with the orientation of the polarised components, and make sure the different transistor types and IC1 all go in their correct places. Don't install the socketed parts just yet, though.

When everything's on the PCB, once again illuminate it from the top, and check for and correct any solder bridges or other problems.
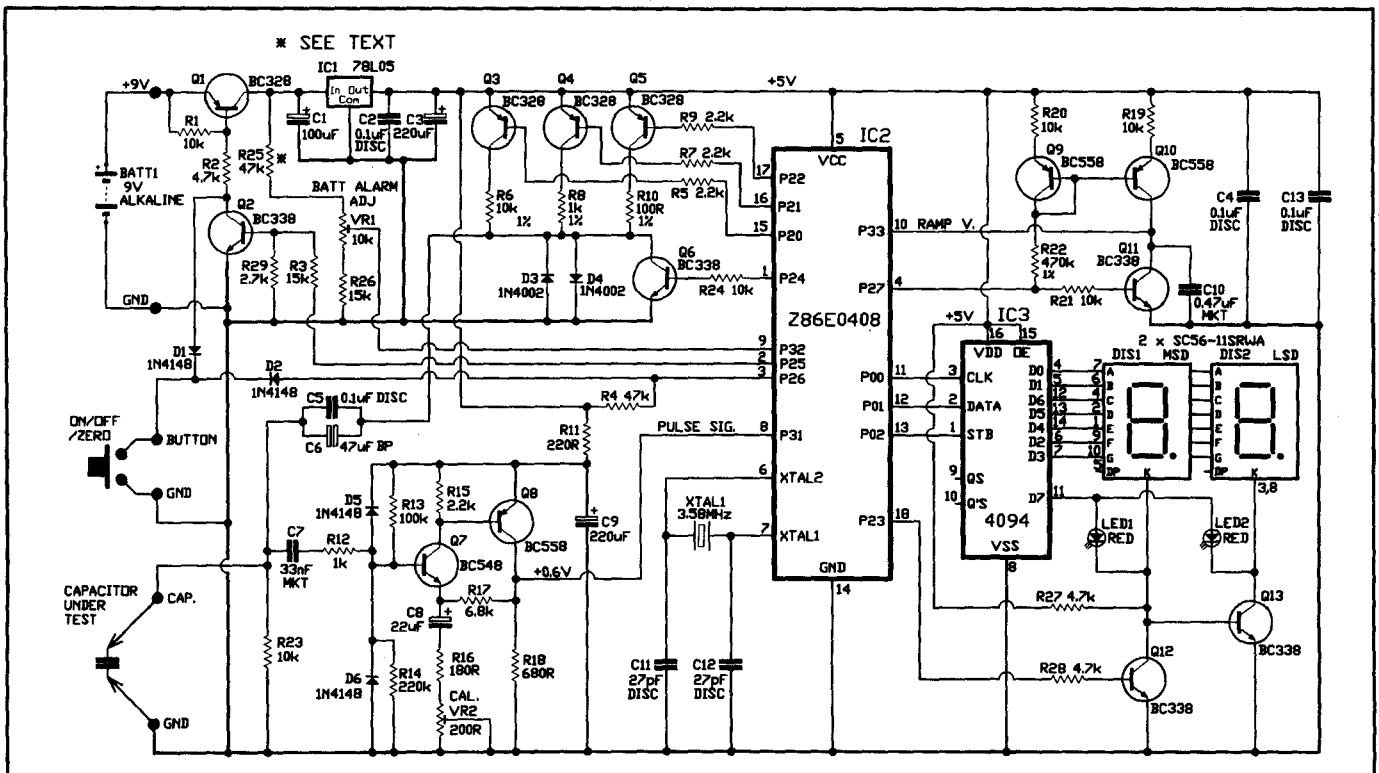
## Making a display

Next study the display area in the photo of the PCB. Then, keeping the cathode (short) leads of the decimal point LEDs to the right, cut the leads down to about 9mm long. Use long-nose pliers to 'dog-leg' the leads about 3mm



*The schematic may look a little complicated, but the circuit is actually quite elegant. Everything is under the control of IC2, a low cost microcontroller. As well as auto ranging, it also compensates for test lead resistance.*

from the ends, so the LEDs will be about level with the bottom of the seven-segment displays when installed.

Push the LEDs into their places in the 28-pin socket, followed by the seven-segment displays themselves, ensuring their decimal points are at the bottom, and they are properly seated.

### First test

Solder the battery snap leads to their pads, making certain their polarity is correct, and solder long component lead offcuts to the 'capacitor' and 'button' pads. Temporarily solder the pushbutton to the ends of its leads, then turn VR1 fully clockwise, and set VR2 to mid-range.

Using alligator clip leads or similar, connect a variable DC power supply set for 9V (and preferably with about 50mA current limiting) to the battery snap terminals.

Make sure the positive lead goes to the clip, and the negative to the stud. You can use another battery snap to make the connection, but remember that its black lead will be the positive one!



Hold the button down and check that pin 5 of IC2's socket and pin 16 of IC3's socket have +5V on them, relative to the power supply negative.

If they have, discharge any static electricity by touching something earthed, then install IC2 and IC3 in

their sockets and double-check their orientation.

Push the button for a second or so,

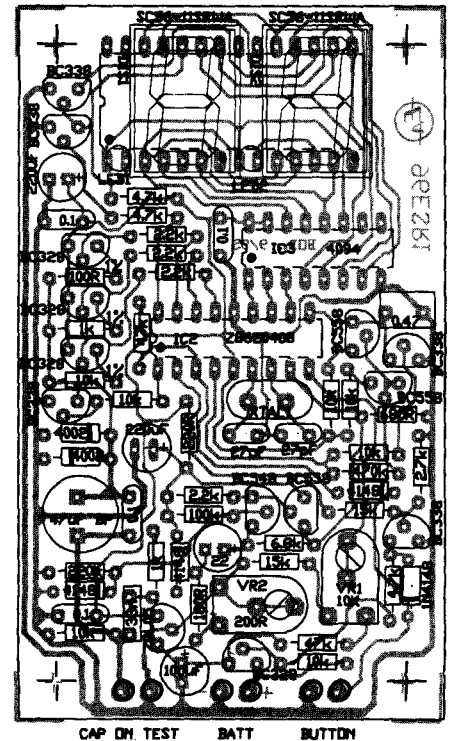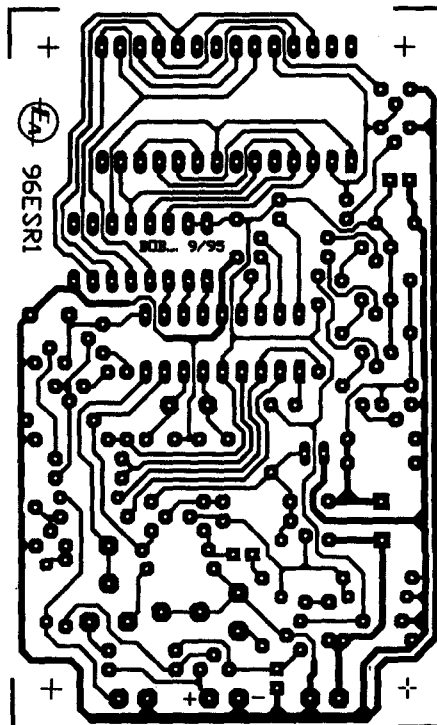and you should see 'EA' flash on the displays for a moment, followed by a single '-' on the left-hand one. If not,



*At left is the PCB pattern for the meter, reproduced actual size as usual for those who wish to etch their own boards. At right is the PCB overlay diagram, showing where everything goes. Use it in conjunction with the photo when you are assembling your own board, to ensure that you get everything in the right place.*

# Micro-based ESR and Low Ohms Meter

carefully recheck the PCB and its soldering and component placement, until you find the problem.

Now short the 'capacitor' leads, and the display should indicate a resistance of around .03 ohms. Push the button again and this should change to '.00', possibly with the least significant digit hesitating between 0 and 1.

## Calibration

Connect a resistor of known accuracy of around 68 to 82 ohms to the 'capacitor' leads, and adjust VR2 for a correct reading. Now try a resistor in the range of 1 to 9 ohms, and check that the meter reads close to the correct value.

**Battery Warning:** Skip this bit if you disabled the automatic switch-off function by leaving R25 off the PCB.

Leaving the 'capacitor' leads separated, turn the power supply voltage down to 7.0V, preferably confirmed by a digital voltmeter. Slowly turn VR1 *anticlockwise* until the display brightness suddenly drops noticeably, and a 'b' begins flashing on the right-hand display.

Push the button again and the displays should switch off. Wind the power supply back up to 9V, switch the ESR meter back on by pushing the button, and recheck that the battery warning triggers when you drop the supply to 7.0V.

## General assembly

Now you only need to install the completed electronics in the box. If you're using a Dynamark front panel, get a photocopy of its pattern then use it as a template to mark out the holes you'll need to drill, ream and file in the lid.

Use an 'X-acto' or similar hobby knife to cut out the holes in the Dynamark panel, then after removing its backing, carefully align and stick it to the box's lid. Mount the button and banana sockets as shown in the photos, then position a suitably-sized piece of filter material under the display window — holding it in place with a drop of contact adhesive or similar on each side.

Now bolt the PCB to the lid, using 25mm x 3mm screws and 15mm tubular spacers (or a similar scheme). You might need some washers as extra spacers, if the display filter material is a bit thick...

Finally solder the 'capacitor' and 'pushbutton' leads in place and connect a 9V alkaline battery, which can be held snugly against the bottom of the box by

## PARTS LIST

### Resistors

All 0.25W 5% unless noted:

R1,19,20,21,23,24	10k
R2,27,28	4.7k
R3,26	15k
R4,25	47k
R5,7,9,15	2.2k
R6	10k 1% metal film
R8	1k 1% metal film
R10	100 ohms 1% metal film
R11	220 ohms
R12	1k
R13	100k
R14	220k
R16	180 ohms
R17	6.8k
R18	680 ohms
R22	470k 1% metal film
R29	2.7k
VR1	10k hor. trimpot
VR2	200 ohm hor. trimpot

### Capacitors

C1	100uF 16VW RB electrolytic
C2,4,5,13	0.1uF 50VW disc/monolithic
C3,9	220uF 16VW RB electrolytic
C6	47uF 50VW bipolar RB electrolytic
C7	33nF 63VW MKT
C8	22uF 16VW RB electrolytic
C10	0.47uF 63VW MKT
C11,12	27pF 50V NPO disc ceramic

### Semiconductors

D1,2,5,6	1N4148 etc signal diode
D3,4	1N4002 etc power diode
Q1,3,4,5	BC328 PNP transistor
Q2,6,11,12,13	BC338 NPN transistor
Q7	BC548 NPN transistor
Q8,9,10	BC558 PNP transistor
IC1	78L05 voltage regulator
IC2	Z86E0408 microcontroller (with custom firmware)
IC3	4094 CMOS shift register
DIS1,2	Seven-segment LED displays (see text)
LED1,2	3mm LEDs (see text)

### Miscellaneous

XTAL1	3.58MHz crystal, HC-49/U case
BATT1	9V alkaline battery
One each 16,18, 28-pin IC sockets; '216' type battery snap lead; plastic utility box, type UB3; PC board, 95 x 57mm, code 96ESR1; push-on momentary pushbutton switch; two x 4mm banana sockets; Dynamark dress plate; 4 x 15mm tubular spacers; 4 x 3mm machine screws 25mm long, plus nuts; piece of foam plastic (see text); two non-curling test leads with 4mm banana plugs; display filter material (see text); 0.71mm solder, etc.	

a piece of thick foam plastic under the PCB. Alternately, you can bring the lead from a 9V plugpack into the box via a suitable grommetted hole.

Now screw the lid down, plug in some probe (or clip) leads, and prepare for a future of easy identification of faulty electrolytics, and low resistance measurements!

## Uncommon parts

Nearly all the components in this project are common stock types, but it was unavoidable that a few special bits and pieces would be needed...

The Zilog Z86E0408 microcontrollers containing this project's firmware will be supplied with kits and will also be available separately, along with the PCBs and Dynamark front dress plates, from RCS Radio Pty Ltd, of 651 Forest Rd, Bexley NSW; phone (02) 587 3491). RCS will also have a detailed version of this article available on a 3.5" floppy, as 96ESR1.DOC.

Because of the need to conserve battery power, the 0.5" seven segment LED displays and 3mm LEDs stocked by most suppliers are too dim in this circuit to read easily under normal room lighting.

The orange 13.2mm displays and 3mm LEDs (catalog numbers Z-4151

and Z-4083 respectively from Dick Smith Electronics) are reasonable, if you can find a thin piece of orange-tinted plastic to use as a display window. (One side from a box of orange-flavoured 'Tic Tacs' is suitable!)

I recommend ultra high efficiency 'super red' Kingbright SC56-11SRWA 14.2mm displays and L-934HD 3mm LEDs, as shown in the photos. These perform brilliantly (pun intended!), and will also be available from RCS Radio.

Rockby Electronics, of 261 Huntingdale Rd, Huntingdale Victoria; phone (03) 9562 8559 stock pieces of excellent non-reflective red filter material (catalog number D1555), which can be cut down to make a display window for the Kingbright displays and LEDs.

## Acknowledgements

In closing I'd like to thank Keith Anderson, Managing Director of Adilam Electronics Pty Ltd (who stock a wide range of high-grade electrolytic capacitors), for eagerly providing lots of technical information including the front-panel ESR figures. This has been of great help in preparing this article.

Thanks also to Wayne Scicluna for building, evaluating and thoroughly testing the prototype units shown in the photos! ♦

**Big price drop!**  
**486DX4-100**  
 motherboard  
 including CPU!!

Features:  
 - 256K cache.  
 - 4 x 30 pin and  
 2 x 72 pin SIM  
 sockets.

**\$225**

**3.5" 1.44M**  
**DISKETTES**



**\$5.50**

*Life-time*  
 PRE-FORMATTED *Warranty!!*

Buy in bulk and  
 save even more .....

**10+ \$5.00**  
**100+ \$4.75**

Prices based on box of 10 diskettes.

**Electronic Components**


We carry a large range of electronic components such as semiconductors, passive components, plugs & sockets, service equipment.....

For full listing of our product range, please send \$2.00 for our price list on computer diskette. Alternatively, you may request a free copy with your purchase.

To receive our wholesale price list on diskette, please send your business card.

Price list supplied on MS-DOS format 1.44M HD disks.

**Pentium-100 Multimedia System**

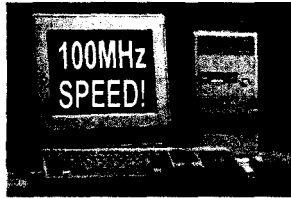

**8M RAM FREE** DELIVERY & SETUP.\*  
**1G HDD FREE** 1 YEAR ON-SITE WARRANTY.\*  
**Quad-speed CD-ROM FREE** 2 YEAR PARTS & UNLIMITED LABOUR WARRANTY.

\* Limited to Melbourne metropolitan areas. Conditions apply.

**Configuration:** 256K cache, 3 x PCI bus slots, 8M RAM, 1G IDE HDD, 1.44M FDD, onboard enhanced IDE controller, onboard 2 x 16550 UART serial ports and 1 x parallel, 1M PCI-bus SVGA card, 14" non-interfaced monitor, joystick, Quad speed CD-ROM drive, SB16 PnP sound card, speakers, MS Ergo mouse & pad, enhanced 101 keyboard, choice of either desk-top or mini-tower case, and 5 Microsoft CD titles.

Available with your choice of either MS-DOS 6.22 & Win. for Workgroups 3.11 or Windows '95 at no extra cost!!

Pentium-120 upgrade option .... \$100  
 Pentium-133 upgrade option .... \$375  
 15" N.I. / dig. monitor upgrade .. \$120

**\$2795**



**THE ELECTRONIC & COMPUTER SUPPLIERS**

HEAD OFFICE / MAIL ORDERS:  
 305 Latrobe Street, Melbourne, Vic. 3000  
 Phone:(03)9602-3499 Fax:(03)9642-8551  
 Melbourne suburb:  
 Cnr. Blackburn & Wellington Rds., Clayton, Vic. 3168  
 Phone:(03)9562-9501 Fax:(03)9562-9261  
 SHOP HOURS: Mon.-Thurs. 8:30-5:30 Fri. 8:30-8:00 Sat. 9:00-1:30  
 ADELAIDE: 223-2225 BRISBANE: 229-4086 DARWIN: 814-0770 SYDNEY: 262-3093

**POSTAGE RATES:**  
 \$1.00 ~ \$9.99 ... \$3.75  
 \$10.00 ~ \$24.99 ... \$4.00  
 \$25.00 ~ \$49.99 ... \$4.95  
 \$50.00 ~ \$99.99 ... \$6.50  
 \$100.00 ~ \$199.99 ... \$7.50  
 \$200.00+ FREE

**Freight charges:**  
 Melbourne metro. .... \$7.00  
 Road Freight ..... \$12.00  
 Overnight Air Freight .... \$12.00  
 Above rates are minimum charge applicable to packages of up to 3Kg. Please enquire for larger items such as computer systems. Insurance extra.

N.B. Above rates apply to small packages only. Bulky or fragile items will only be sent by road or air freight. Insurance extra.

N.B. Normal prices charged unless ad prices quoted. Errors & omissions excepted. Prices & specifications subject to change without notice.

Tax exempt orders: TECS Imports P/L, 1st. Flr. 289 Latrobe St, Melb., Vic. 3000  
 Phone:(03)9670-6474 Fax:(03)9670-6006

Free Call  
 Mail Order  
 Hotline!!  
**(1800)335-901**

**SIM converters are here!**

Convert 4 of your 30pin SIMs into a single 72pin SIM. Very handy when you are upgrading from an old motherboard to a new one.

**\$19**

**Need more memory to run Windows '95?**  
**30pin SIM**

1M ..... \$59  
 4M ..... \$210

**72pin SIM**

4M no parity ..... \$215  
 4M with parity ..... \$265  
 8M no parity ..... \$425  
 8M with parity ..... \$545  
 16M no parity ..... \$820  
 16M with parity ..... \$995

**FLOPPY DISK DRIVES**

1.44M 3.5" \$49  
 1.2M 5.25" \$75

**Bargain price on multimedia kit!**

You no longer have any excuse for not having a CD-ROM drive and a sound card in your computer.




**Includes:**

- Panasonic 562J double speed CD-ROM drive.
- 16-bit sound card.
- pair of speakers.

**\$195**

Quad speed CD-ROM drive upgrade option for only \$125 extra!!

**Sony Trinitron monitors**

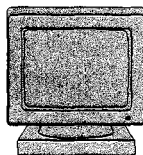

We have a range of these superb monitors on display at our new City store. Come in and take a look for yourself the clarity and the flatness of these fine monitors.

**Intelligent Digital Multiscan**

The CPU and ASIC chips determine the graphic controller's video frequency, quickly calculate the waveforms required to compensate for geometric distortion, and then generate the screen image accordingly thereby eliminating nearly all distortion.

**15SF 17SF 20SF**

**\$799 \$1950 \$3925**

**Pentium CPU and motherboard**

These days, more and more games and other software require a very fast processor to handle the complex graphics. Even the 486 machines are no match for some these fancy programs. You need the power of the Pentium processor.

All motherboard features PCI bus, 256K cache, Triton chipset, and "Plug & Play" BIOS.

Pentium-75 \$575  
 Pentium-90 \$725  
 Pentium-100 \$799  
 Pentium-120 \$925  
 Pentium-133 \$1190

## Construction Project:

# REMOTE VOLUME CONTROL - 2

In this second article describing the remote volume control project for hifi systems, etc., we present full details of how to build it, set it up and get it going. The PCB design is very flexible, allowing the project to be either built into an existing amplifier or as a separate self-contained unit linked in via the 'tape loop' connectors.

by PETER PHILLIPS


Last month we described the circuit details of this versatile project. As you've seen from Part 1, the project has two main applications: as a remote controlled volume system or a controller for relay operated loads. Therefore the circuit and the PCB design is in three sections, with the decoder section common to the other two.

Recapping briefly, the decoder section has two output terminals, A and B. There are three possible output conditions, depending on whether a transmitter key is pressed — and if so, which of the two keys.

When there's no transmission, these terminals are effectively open circuit, or floating. If the UP key on the transmitter is pressed, the 12V DC supply is switched to terminal A, and terminal B is left floating. Pressing the DOWN key causes terminal B to be switched to ground potential, leaving terminal A floating.

In other words, the output of the decoder is rather like that of a three-state logic IC, in that it can source or sink current, or remain open circuit. When the motor PCB is connected to the decoder, terminals A and B are joined and the motorised potentiometer rotates according to the three possible states of the output.

When the relay PCB is connected,

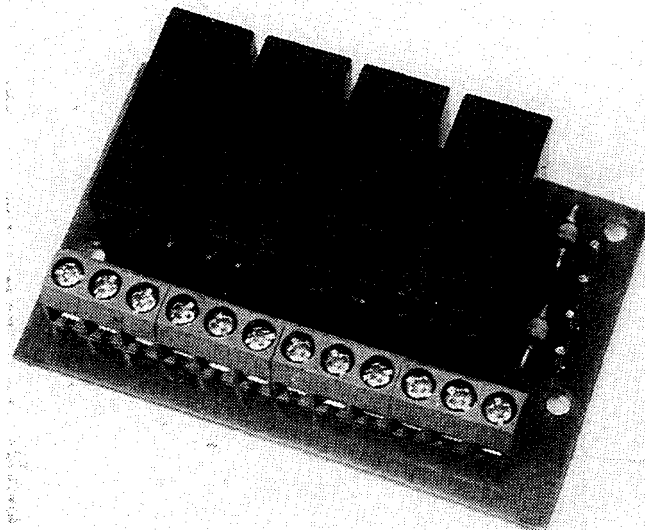

*This photo shows the relay PCB. Connections to the relay contacts can be through a terminal block, or soldered directly to the PCB pads.*

terminals A and B are separate. When terminal A is active (+12V), relays 1 and 2 operate. When terminal B is active (0V), relays 3 and 4 operate. As described last month, it's not possible for both terminals to be active at the same time (unless there's a fault).


Now here's how to build it all...

decoder PCB, whether they are separated or not.

Construction of the whole thing is relatively straightforward, and the supplied PCB is silk-screened with the component layout. Start by installing the links, or if you intend using them, by fitting IC sockets in place.

Next solder the resistors, capacitors and diodes, checking for correct polarity of the latter two. Now fit the transistors, making sure not to accidentally mix them up. There are three different types of transistors that all look the same.

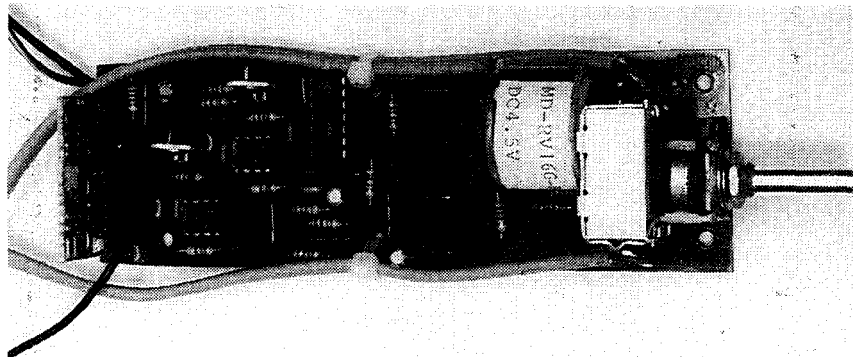The motorised pot assembly solders directly to the PCB, and the



*This is a close up of the decoder and motor PCBs. The receiver PCB is at the end of the decoder PCB. Note the links joining the two PCBs.*




motor wires connect either directly to the pads labelled R (for red wire) and B (for black wire) on the decoder PCB, or if the boards are separated, to the loop terminals on the motor PCB. This allows the motor wires to be terminated, with longer leads completing the connection back to the decoder PCB.

The audio connections are through shielded cable with RCA connectors. The prototype has leads fitted with RCA plugs to allow the volume control to be connected in the tape monitor loop of an amplifier. Anchor these leads with plastic ties.

The relay PCB has four relays and two diodes, so its construction is very simple. A terminal strip like that in the prototype can be soldered to the PCB for connections to the relay contacts. This is really only necessary if the board is going to be used in a variety of applications. Otherwise just solder the connections directly to the PCB.

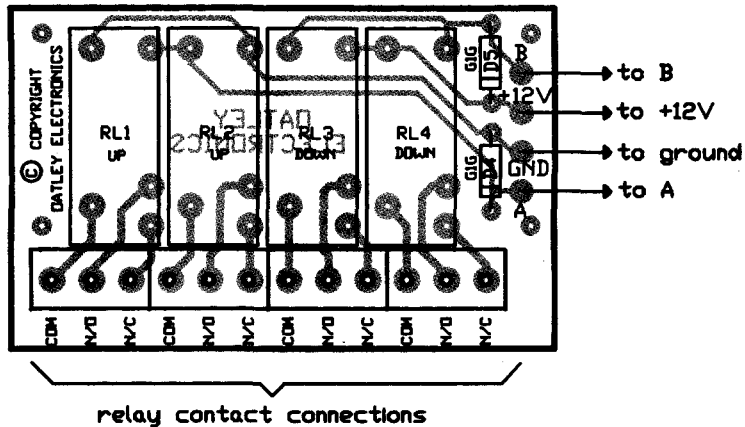Finally, fit the UHF receiver module and the ICs. The UHF receiver module is mounted so its component side faces in. Before soldering it in place, fit a terminal post made from a piece of tinned copper wire to the test point for the receiver, to make things easier during adjustment. Also connect a 300mm length of insulated



**This is the layout for the relay PCB. Because terminals A and B are joined on the motor PCB, don't include the motor PCB when using this one.**

hookup wire as an antenna.

The power supply is specified at 12V, but can be 10V DC or so. The main thing is that the supply is DC and able to supply around 200mA. We used a plug-pack, but any DC supply will do.

### Transmitter mods

Before the system can be tested, there are four modifications to make to the supplied transmitter. Incidentally, although the transmitter comes with a 9V battery, it is most unlikely that the battery will be any good.


It will possibly read 9V when open circuit, but this will drop significantly under load. Using it with the transmitter will make adjustments almost impossible. So fit another known-good battery before doing any adjustments.

The modifications you have to make are marked on the circuit (Part 1 - Fig.1) and are:

1. Remove the coil former and its ferrite core from the inductor. This will leave two exposed loops of wire, which form the inductor. Try not to distort the position of the loops of wire when the former and core are removed.
2. Remove C5 and replace it with a trimmer capacitor. This capacitor is the one right next to the inductor, running parallel with the inductor.
3. Replace R8, a 220k resistor with a 10k resistor. This resistor is next to the UP pushbutton, parallel with three other resistors all fitted between the two pushbuttons.
4. Replace R7 with a 10uH inductor. The resistor is to the right of the UP pushbutton, almost in line with the two-turn inductor, and at the top-right edge of the PCB.
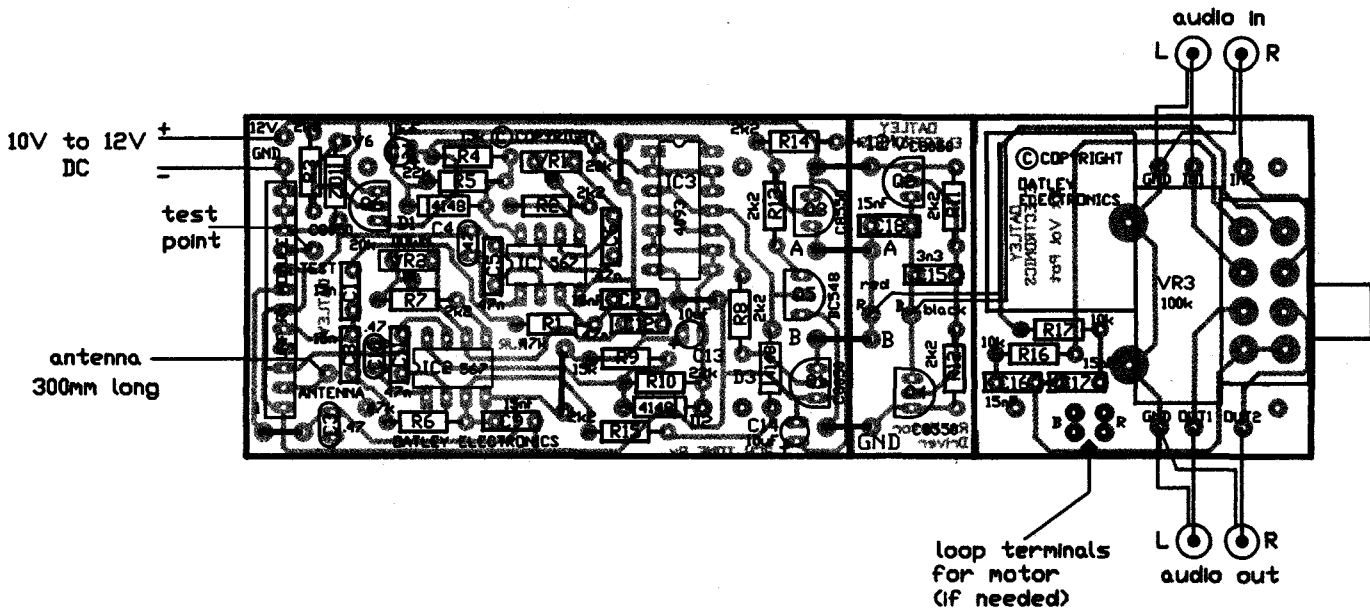
### Adjustments

There are a number of adjustments to do to get the unit working over the best range. These are: the transmitting frequency of the handheld transmitter, the frequencies of the UP and DOWN tones in the transmitter, and the free running frequencies of IC1 (UP tone decoder)



**This layout is for the decoder and the motor PCB. The boards can be separated and connected by lengths of wire to suit. In this case, connect the motor wires to the loop terminals, with extra leads from the terminals to the decoder PCB. Otherwise connect as shown here.**

## Remote Volume Control - 2

and IC2 (DOWN tone decoder). We'll describe two ways of doing these, one for those with an oscilloscope and one for those who have limited equipment.

The first adjustment is the transmitting frequency. If you have a 'scope, connect it to the test pin of the UHF receiver module. Otherwise, connect a voltmeter set to its low voltage AC range. The output voltage at this pin will be around 1V on a typical multimeter. If you don't have a voltmeter, connect a set of headphones or the input of an audio amplifier to the test terminal.

Hold the transmitter about one metre from the receiver, and press either button. Using a non-metallic screwdriver, adjust the trimmer capacitor to get the highest output at the test point. Trim the adjustment by moving the transmitter further away from the receiver and again peaking the adjustment.


For those with an oscilloscope or a frequency counter, monitor the frequency at the test point of the receiver and set the UP tone frequency to 2.2kHz by adjusting the transmitter trimpot nearest the battery. Then adjust the DOWN tone frequency to around 2.8kHz with the other trimpot. These frequencies don't have to be accurate, but you should get both frequencies so they are about 600Hz apart.

Then connect the oscilloscope to pin 5 of IC1 to monitor its free running frequency. Adjust this frequency with VR1 to about that of the UP tone frequency (2.2kHz). Fine tune it by pressing the transmitter UP button and setting VR1 so this tone remains the same when the incoming tone is received. You should also be able to confirm that the output of IC1 (pin 8) goes low when the two tones are within about 100Hz of each other.

Repeat this for IC2, this time for the DOWN tone frequency (2.8kHz). Again confirm that the output of IC2 goes low when the frequencies are about the same. Obviously the output of IC1 should not be affected by the DOWN frequency and the UP frequency should not affect the output of IC2.

If you don't have an oscilloscope, you can do all of this quite easily with an audio amplifier or even a set of high impedance headphones. Unfortunately, these days most headphones are low impedance, so unless you have the right sort, use an audio amplifier. The procedure is rather similar to that already described, except now you listen to, rather than watch, the signals.

Start by connecting an audio amplifier

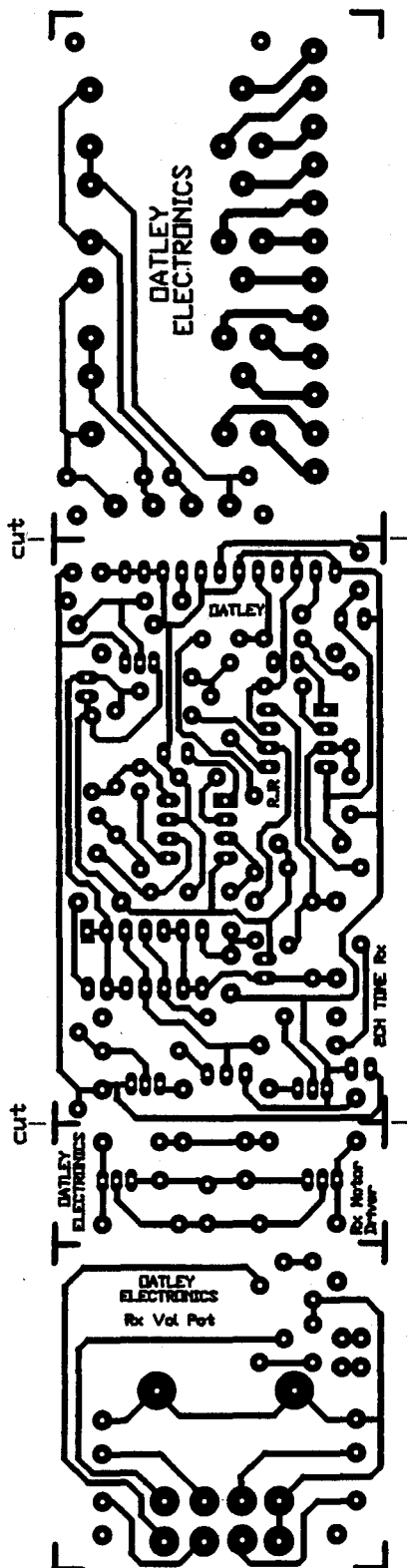

*This is the artwork of the complete PCB, showing where the board can be cut. It's reproduced full size for those who want to make their own. Commercially the design is copyright to Oatley Electronics.*

to pin 5 of IC1 so you can listen to the free running frequency of IC1. Compare this frequency to that at pin 5 of IC2, and adjust VR1 and VR2 so the frequency from IC1 is markedly lower than that from IC2.

Now press the UP key of the transmitter and listen to the tone it produces by connecting the audio amplifier to the test terminal of the UHF receiver. Adjust the transmitter trimpot for this tone (the one nearest the battery) until the tone is about the same as that from pin 5 of IC1. Fine tune this setting by adjusting the trimpot so the frequency at pin 5 hardly changes when the UP key is pressed. When this setting is correct, the output of IC1 (pin 8) should go to zero volts when the UP key is pressed.

Repeat this for IC2. That is, compare the transmitted frequency (at the test terminal of the receiver) to the free running frequency of IC2 and adjust the transmitter trimpot for this tone (the one alongside the DOWN key) until the tone is about the same as that from pin 5 of IC2. Again confirm that the output of IC2 (pin 8) goes to zero volts when the DOWN key is pressed.

If you find IC1 responds to both the UP or DOWN keys, you haven't got the frequencies of the transmitter tones set so they are far enough apart. To fix this, adjust either trimpot in the transmitter to increase the difference in the frequencies, and repeat the adjustments already described.

If you have no equipment except a multimeter, you'll have to do the adjustments by trial and error. It really doesn't matter what the frequencies of the two transmitted tones are, providing they are sufficiently different. You could start by leaving the transmitter trimpots where they are set, and keep adjusting VR1 and VR2 until IC1 and IC2 respond properly. Remember you have to set the transmitting frequency (with the trimmer capacitor) first. This can be done as already described, or you can use a set of low impedance headphones connected to the test terminal of the receiver module. However you can't use these headphones to listen to the tones at IC1 and IC2, as the headphones will change the frequency.

### Connecting it up

The volume control could be fitted in place of an existing control, providing there's room in the equipment. You might also be able to derive a suitable DC supply from the equipment. Otherwise, for an audio amplifier, connect the volume control in the tape mon-

## PARTS LIST

### Resistors

All 1/4W, 5% unless otherwise stated:

R1,R6	47k
R2,R3,R7,R8,R11-15	2.2k
R4,R9	15k
R5,R10	22k
R16,R17	10k
VR1,VR2	20k
VR3	100k log, motorised dual gang

### Capacitors

C1,C2,C8,C9,C16-18	15nF ceramic
C3,C4,C10	0.47 monolithic
C15	3.3nF ceramic
C7,C13,C14	10uF electrolytic
C5,C6,C11,C12	47nF ceramic

### Semiconductors

D1-3	1N4148 signal diodes
D4,D5	G1G, 400V 1A diode
ZD1	5.6V 400mW zener
Q1,Q2,Q6	C8050 NPN transistor
Q3,Q4	C8550 PNP transistor
Q5	BC548 NPN transistor
IC1,IC2	LM567 tone decoder
IC3	4093 quad Schmitt NAND

### Miscellaneous

PCB, 205mm x 44mm; UHF receiver module; UHF transmitter with 2.5pF trimmer capacitor, 10k resistor and 2.2uH inductor as replacement parts; plastic case 50 x 90 x 160mm; 4 x SPDT 12V relays; 240V-12V DC/200mA plug pack, knob, stereo shielded lead with RCA connectors.

A kit of parts for this project is available from Oatley Electronics, phone (02) 579 4985. Postal address (mail orders): PO Box 89, Oatley West NSW 2223.

Complete volume control kit, includes everything in the parts list except plugpack (and relays).....\$69

Complete relay control kit, includes everything in the parts list except plugpack (and motorised pot).....\$55

Suitable plugpack.....\$12  
Individual parts are also available, although there's a limit of two transmitters per kit. Phone for details.  
Packing and postage charges \$3 to \$5 per order.

Please note that the PCB artwork for the project is copyright to Oatley Electronics, and cannot be sold by other companies.

itor loop of the amplifier. Because it has a value of 100k, the volume control won't significantly load the output from most audio equipment (like the output of a CD player, VCR or tape player). This means you could connect the volume control between the output of a piece of audio gear and the input of the amplifier. The disadvantage here is that the remote volume will only work for that piece of equipment.

As the photo in Part 1 shows, the prototype was mounted inside a black plastic case, with a hole drilled in the end for the potentiometer shaft. A large control knob is needed so you can see its position from a distance. You might even fit a 3mm LED to the knob, making its position even easier to see.

### Relay operation

The relay section is for operating an external load, typically a motor. The relay contacts are rated at 8A 250V, although the PCB is not designed for 240V applications. Any load within the contact rating can be connected to the relays, but we advise that you only use low voltage equipment with the relays.

If you want to control mains equipment, use these relays to switch additional relays that in turn switch the mains. This keeps all mains wiring well away from the PCB.

There are lots of cheap and effective ways of building a simple motorised

actuator. For example, a 12V DC windscreen wiper motor has incredible torque and might suit a simple panning mechanism for a security camera or antenna rotator.

An efficient, quiet, powerful and readily available example is a Volkswagen windscreen wiper motor. These have a permanent magnet field, and take around 2A under a reasonable load. There are 6V and 12V versions, but try for the 12V version. A typical price from a car wrecker is around \$10.

Applications using this motor could include remote controlled curtains, an antenna or satellite dish rotator, a motorised flow valve and so on. When combined with a lead screw (available from most hardware shops as a threaded shaft), you could build a simple actuator arm.

To do this, run a threaded nut onto the shaft (make sure it runs smoothly along the shaft), and connect the shaft to the motor, so it's turned by the motor. Drill and tap a hole through the nut so a lever can be attached to the nut. The lever can be pivoted, or arranged to push or pull the load.

This type of actuator will have considerable power, and could be used to open a gate, door, flap and so on.

Other uses for the system will probably come to you, as this is really one of the most versatile remote control type projects we've presented for some time. ♦

**HINTON**  
INFORMATION SERVICES

Up-to-date Information for  
Design & Repair

### D.A.T.A. BOOKS & CD-ROM

- Integrated Circuits & Semiconductors
- Parametric Access Library on CD-ROM

### IHS CD-ROM

IC/Discrete Parameter Database  
CD-ROM contains over 1,500,000 devices and their parameters, Australian distributors, device pinout information and many more features.

FREE-CALL 1 800 062 299

FREE-FAX 1 800 817 716

...for a FREE catalogue & price list.

IHS AUSTRALIA Pty Limited ACN 059 947 410

Trading as: Hinton Information Services  
Locked Bag 7, Eastwood NSW 2122

## KITS KITS KITS KITS

The following kits which were developed by TOM MOFFAT are now available exclusively from:

**ACTIVE**  
electronics

GPO Box 1022  
Hobart 7000

Listening Post Wesat @ \$109

Listening Post II @ \$89

Pocket Packet @ \$89

PH 002 310 111 FAX 002 343 073

# SOLAR PANEL

## warehouse

manufacturers / wholesale / retail

Huge range of panels  
Crystal or amorphous from  
10 mA to 5000 mA. Mega  
panels, 30% extra power  
Free delivery this month over \$50

### SolarCorp

259 Broadway BROADWAY ph 02 5664340

# JANUARY DEALS FROM JAYCAR

## 1 Amp AA NICADS!!!

Yes, that's correct. They do exist, and we've got them at very low prices.

- AA 1.2V 1A/HR ~~Cat. \$4.75ea~~ **\$4.75ea**
- AA 1.2V 1A/HR with solder tags ~~Cat. \$5.00ea~~ **\$5.00ea**
- NICKEL METAL HYDRIDES ARE ALSO AVAILABLE
- AA 1.2V 1.1A/HR ~~Cat. \$5.95ea~~ **\$5.95ea**
- AA 1.2V 1.1A/HR with solder tags ~~Cat. \$6.25ea~~ **\$6.25ea**



**NEW**

JAYCAR ELECTRONICS IS NOW A

## QUALITY ENDORSED COMPANY!

Our Purchasing Dept, Warehouse, Wholesale Sales and Kit Department are now Quality Assured to AS9002.

Quality System

Quality Endorsed Company AS9002

### 30W RMS X 2

**NEW**

Power Amplifier

Supply voltage: 12-24VDC (12V) - Output: 30W x 2


Channel separation: 20dB

Distortion: 0.1%

Frequency response: 20Hz to 20kHz

Dimensions: 100 x 100 x 25mm

Cat. AR-1710 ~~\$43.95~~ **\$35.00**

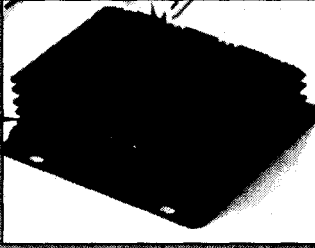


## PROGRAMMABLE REMOTE CONTROL

This remote control will "learn" the functions of other remotes. If your TV / stereo coffee table has a row of remotes, you can actually retire them all and just use this one. Also ideal if one of your remotes is "on the way out". Before it dies, buy one of these and it will learn the functions. Brand name replacement remote controls cost a fortune.

- Specs:** •Memory capacity: 150 commands
- Memory hold without batteries: About 8 minutes
- Suitable equipment: Most brands of infra red remote controllers for audio/video devices
- Effective range: 8 metres
- Power source: 4 x AAA batteries (not supplied)
- 187(L) x 64(W) x 15(D)mm

Cat. AR-1710 **\$43.95**

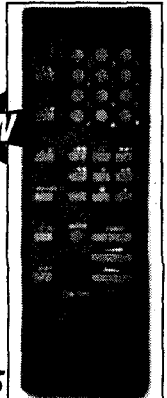

### CAR AMPLIFIER

**NEW**

30W RMS X 2

Power Amplifier

Supply voltage: 12-24VDC (12V) - Output: 30W x 2

Channel separation: 20dB

Distortion: 0.1%

Frequency response: 20Hz to 20kHz

Dimensions: 100 x 100 x 25mm

Cat. AR-1710 ~~\$43.95~~ **\$35.00**



## LASER POINTER

If you need to point out objects or details that are out of reach, then you need a laser pointer. Up until now you have had to pay around \$140, but not at Jaycar. Laser Pointer is small and easy to hold, and has a push on switch for operation. Requires 2 x AAA batteries. Supplied in a plastic case for storage. Specifications: •wavelength - 670nm at 50 metres, 650nm at 150 metres, 630nm at 300 metres •size - 140 x 18 x 15mm. Class 2 laser product. Do not store into beam.

Cat. ST-3100 **\$89.50**



### Jaycar 2.5 Amp 24 to 12 Volt Reducer

**NEW**

Converts 24V to 12V

Supply voltage: 24VDC - Output: 2.5A

Dimensions: 100 x 100 x 25mm

Cat. MP-3050 ~~\$49.95~~ **NOW \$39.95**



## Planetary Gear Box Set

Automatic transmissions in cars use planetary gear clusters. They are simple, compact and strong. This gear set made in Japan by TAMIYA is sensational. Why? Firstly you can configure the gearbox to 8 different reduction rates 4:1, 5:1, 16:1, 20:1, 25:1, 80:1, 100:1 and 400:1. A genuine MABUCHI RC-260 3VDC motor is included! (at 400:1 the gearbox gives a massive 15kg/cm of torque!) Typically Japanese, it is thorough. Absolutely everything is supplied including tubes of lubricating grease, mounting feet, two drive attachment cranks and a beat brass double female coupling to connect to other (drive) shafts. You will love this product! •Measures 100mm long x 28mm(dia of body), height including mounting feet 38mm. Steel output shaft 4mm dia •Can be ganged for up to (max) 160,000:1 •Moulded out of sturdy ABS plastic

Cat. YG-2720 **\$39.95**



### Jaycar 7.5 Amp 24 to 12 Volt Reducer

**NEW**

Converts 24V to 12V

Supply voltage: 24VDC - Output: 7.5A

Dimensions: 100 x 100 x 25mm

Cat. MP-3060 ~~\$92.50~~ **NOW \$69.95**





JAYCAR NOW OPEN IN PERTH
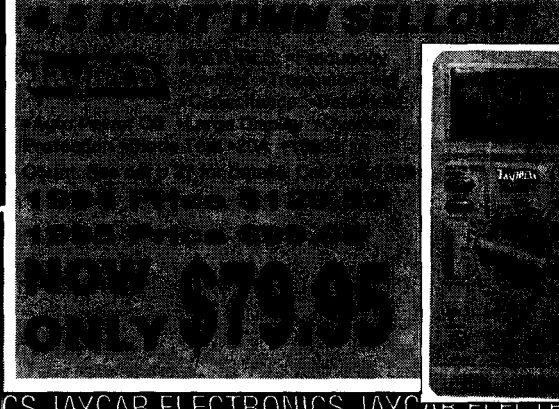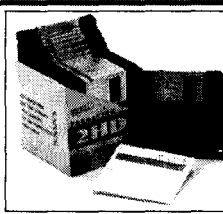
## CHEAP DISKS!!!

**NEW** Save even more on 3.5" HD IBM formatted disks. 100% error free and includes user labels. CAT XC-4740




Don't pay \$19.95 **Pkt 25 Only \$13.95**



## Save on Breadboard for January

See catalogue page 130 for full details.

Cat	Description	Normally	Jan	Save
PB-8810	Distribution strip 100 hole	\$4.25	\$2.95	\$1.30
PB-8812	Terminal strip 630 hole	\$13.50	\$9.95	\$3.55
PB-8814	830 tie points	\$18.95	\$13.95	\$5.00
PB-8816	1660 tie points on plate	\$44.95	\$34.95	\$10.00
PB-8818	2420 tie points on plate	\$56.95	\$46.95	\$10.00
PB-8820	3220 tie points on plate	\$75.00	\$62.00	\$13.00

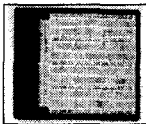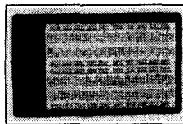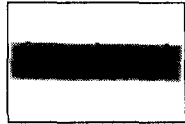

## SAVE ON CROS

25MHZ

CRO \$749  
2 PROBES \$79  
\$828



QC-1900

Jan Pay \$699

50MHZ

CRO \$1195  
2 PROBES \$79  
\$1274



QC-1910

Jan Pay \$1095

## Cable For 2 Disk Drives

This lead has one 3.55" floppy disk drive plug to 2 x 3.5" drive power sockets.


Cat. PL-0753

**\$5.95**


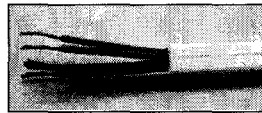
## 6 Core Phone Cable Sellout

SAVE A FORTUNE!  
Our new cable is Austel approved.



This stuff isn't. Limited quantity only. Austel approved cable is 0.75¢ metre or \$48 roll


This cable is **0.40¢** metre or **\$28** roll  
Cat. WB-1603

## MAJIC EAR

Majic Ear is an amazing aid to hearing that sits comfortably behind your ear and magnifies sound with superb clarity.

If you have trouble hearing the TV, listening to the radio etc than Majic Ear will help. There is also 3 different earpieces so you can be assured of a perfect fit. There is an adjustable volume control and an on/off switch. Complete with battery and a spare. Don't put up with trouble hearing!!! Cat. QM-7230

Cat Price \$29.50 **NOW \$19.50**

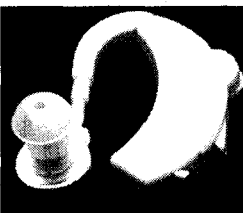

## UNIDEN Cordless Phone Sellout!!!


We have a very small quantity of these phones left. See catalogue page 106 for full details.

**CAT PRICE \$229**

**Sellout**

**Price \$189**

**SAVE \$40** Cat. YT-7040

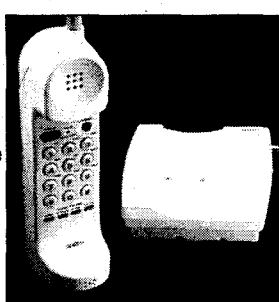

## Ammonium Persulphate Bucket

Save a fortune. 2.5kg bucket.


**CAT PRICE \$29.95**

**Now**

**\$22.95**

**SAVE \$7**

Cat. NC-4256

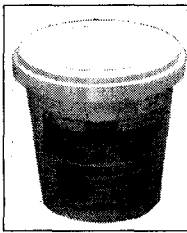

## DOLBY PRO LOGIC CENTRE SPEAKER KIT BARGAIN

Kit includes:

- 2 x 5" shielded woofers Cat CW-2102 Value \$79.90
- 1 x 1" shielded dome tweeter Cat CW-2006 \$16.95
- 1 x crossover network Cat CX-2613 \$8.50
- 1 x set box plans / wiring details \$105.35

**Only \$89** **SAVE OVER \$16** Cat. CS-2500



## LED Display

**Bargain**

LTS313AR /LT303 common cathode 0.3". Peak wavelength 700, IFMA10 .1V(VDC)650 Cat. ZD-1803

**CAT PRICE \$2 EACH**  
**Jan 10 for \$10**



## TELEPHONE EXTENSION LEAD

This lead has a 15 metre length of telephone cable with a U.S. 4 pin plug on each end. Also supplied are two adaptors. One accepts the U.S. plug and converts it to an Australian plug.

The other adaptor is from the U.S. plug to and Australian socket. So you can have any combination of U.S. plug to Aust plug, U.S. plug to U.S. plug or U.S. plug to Aust socket all 15 metres long. Adaptors cost \$6.50 each and the lead is \$12.95. That's over \$25 value. Austel approved.

Cat. YT-6050 **Cat Price \$13.95 JAN \$9.95**



## 12V 16W TWIN TUBE FLURO LIGHT

This fluro light runs off your 12V car power and plugs into the cigarette lighter. It has a magnetic base, so its easily attached to a van, and you can have one or both tubes on. Also ideal for lighting sheds, or houses without 240 volts.

Cat. ST-3025 **only \$24.95**




**GIFT VOUCHERS AVAILABLE**
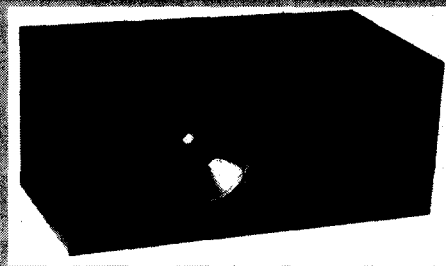
# SAVE ON VIFA JV80 - SUBWOOFER

QUOTE FROM  
ROB EVANS IN  
ELECTRONICS  
AUSTRALIA  
MAGAZINE.

"The JV80 performed extremely well in both our subjective and objective tests, and really did demon-strate how a refined driver such as the Vifa M22WR can deliver the goods in a correctly tuned enclosure"



AS REVIEWED IN ELECTRONICS AUST. JUNE 95

The driver has an impedance of 6 ohms, so could also be used in a car situation. The power handling is very large, for such a small driver being 150 watts nominal (RMS) a long term max rating of 300 watts (on for one minute, pause for two minutes) and a short term max power of 500 watts (on for one second, pause for one minute). We also recommend you use a polyswitch RXE300 Cat RN3472 \$10.95. To simplify, any amplifier between 30 and 200 watts can be used. Look at our new Subwoofer Amplifier Kit.

The enclosure is very small with a volume of 35 litres and only 600 x 270 x 300(Dimm). The cabinet is supplied prebuilt and is made from MDF in blackwood veneer. Grill is supplied with speaker cloth mounted.

## SPEAKER ONLY

VIFA M22WR 8" Cat. CW-2115

Normally \$199.50

**Jan Price \$179.50 ea**

**SAVE \$20**

## SUBWOOFER KIT

INCLUDES: •VIFA M22WR DRIVER •

PREBUILT CABINET •POLYSWITCH

Catalogue Price \$349.45

**Jan Price \$299**

**SAVE ALMOST \$50**



ROAD FREIGHT ANYWHERE IN AUSTRALIA \$14. INSURANCE \$3


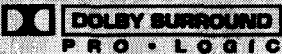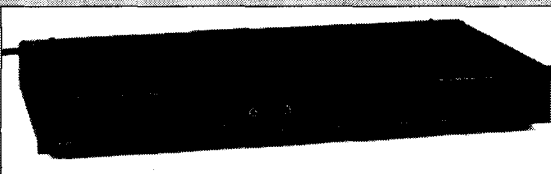
## DOLBY PRO LOGIC SURROUND SOUND DECODER & EFFECTS KIT

REF: SC Nov/Dec 95

You don't have to go to the cinema for big movie sound - you can get it right here with this genuine Dolby Pro Logic Decoder kit! This new design features inbuilt power amplifiers to drive the centre and surround channels and an effects selection for unencoded sources providing adjustable delay between the front and rear surround channels. Housed inside a custom rack-style case, other features include auto noise sequencer for balance setup, sub woofer output, adjustable delay from 15mS to 30mS and a 2 digit front panel delay display. This design has been fully approved AND tested by Dolby Laboratories in the USA. Kit is complete with punched and screened steel chassis, toroidal transformer, microprocessor and all specified electronic components as per the Silicon Chip article.



Cat. KC-5200

**ONLY \$379.00**

ONLY AVAILABLE FROM JAYCAR

## DOLBY PRO LOGIC KIT FOR UNDER



**\$200**



Yes, you can now buy the Dolby Pro Logic short form kit (KC-5175) and the enclosure kit (KC-5176) for \$199.


**SAVE \$40**

**\$199.00**
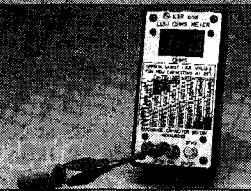
## NEW KITS ESR & Low Ohms Meter Kit

REFER: EA JANUARY 1996

If you need bench mode power supplies, TV receivers, computer monitors, vintage radios, audio power amplifiers etc then you owe it to yourself to give this project serious consideration. It measures an aspect of electrolytic capacitor performance which is VERY IMPORTANT BUT NORMALLY VERY DIFFICULT TO CHECK the equivalent series resistance, or "ESR". A standard capacitance meter won't help too much in finding faulty electrolytics as an electro normally doesn't lose its capacitance - as many techs assume they do (see EA January 1996 for a full explanation). The ESR value is displayed on two 7 segment LED displays, and a chart printed on the front of the case for easy referencing. Kit is complete with case, silkscreened front panel, PCB, pre-programmed microprocessor plus all electronic components. DV battery required.




Cat. KA-1769

**\$69.50**
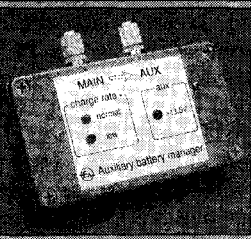
## Smart Dual 12V Battery Controller Kit For 4WDers

REFER: EA JANUARY 1996

The main advantage of an auxiliary battery powering any "non-essential" accessories such as a refrigerator during an overnight stop, is that the main battery is preserved for starting the engine in the morning. This kit will automatically isolate the auxiliary battery during stops, but connect it to the main 12V system for charging while the engine is running. The circuit is housed inside a robust weatherproof diecast case that could be mounted inside the engine bay. Case, PCB, heavy duty battery binding posts plus all electronic components included.



Cat. KA-1782


**\$44.95**

## Save On Super Flat OFC Speaker Cable

Ideal for cars and houses, and can be laid under carpets - its only 2mm high. 7 x 48/0.1mm. See 1995 cat P156 for full details. Cat. WB-1738

**CAT PRICE \$5.95 METRE**


**Jan \$3.95m or \$350/100m roll**

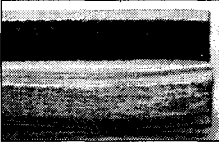

## IC Specials

LIMITED QUANTITIES AVAILABLE

		WAS	FOR JANUARY
2732A	EPROM	ZZ8459 \$11.95	<b>\$8.95</b>
27128	EPROM	ZZ8468 \$11.95	<b>\$7.95</b>
27C128	EPROM	ZZ8469 \$9.95	<b>\$6.95</b>
27256	EPROM	ZZ8470 \$11.95	<b>\$7.95</b>
27C512	EPROM	ZZ8474 \$11.95	<b>\$7.95</b>
D41264C	RAM	ZZ8520 \$8.95	<b>\$4.95</b>
P8086-2	5mhz CPU	ZZ8510 NA	<b>5 for \$5</b>
SN75477P	Dual Driver	ZK8865 NA	<b>10 for \$4</b>
4116 USED RAM		ZZ8419 NA	<b>20 for \$5</b>

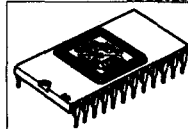

## Woofer Stopper Kit Sellout

Stop that dog barking. At the press of a button this kit emits a high level supersonic tone that lasts for about 9 minutes. See 1995 catalogue P18 for full details. Cat. KC-5133

**CAT PRICE \$59.50**

**SAVE \$20**

**Now \$39.50**




## Electric Fence Kit Sellout

We have sold thousands of this kit over the years. See 1995 catalogue P22 for full details.

**CAT PRICE \$64.95**

**Sellout \$47.95**

**SAVE \$17** Cat. KA-1660

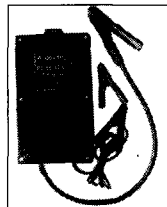

## TURN YOUR SURPLUS STOCK INTO CASH!!!

JAYCAR WILL PURCHASE YOUR SURPLUS STOCKS OF COMPONENTS AND EQUIPMENT. WE ARE CONTINUALLY ON THE LOOKOUT FOR SOURCES OF PRIME QUALITY MERCHANDISE. CALL MARK HARRIS OR BRUCE ROUTLEY NOW ON (02) 743 5222



### HEAD OFFICE

8-10 LEEDS ST RHODES 2138  
PHONE: (02) 743 5222  
FAX: (02) 743 2066

Quality System

Quality Endorsed Company

### WHOLESALE

PHONE: (02) 743 5222  
ORDERS: 1800 620 169  
FAX: (02) 743 3070

### MAIL ORDERS

PO BOX 185 CONCORD 2137  
ROAD FREIGHT ANYWHERE  
IN AUST (up to 20kg) \$14.00

### MAIL ORDER - PHONE

FREE CALL - ORDERS ONLY  
(1800) 022 888  
HOTLINE (02) 743 6144



### ADELAIDE SA

• 194 Wright St (Cnr. Selby St) • Ph: (08) 231 7355  
• Fax: (08) 231 7314 • Mon/Fri: 9-5.30 • Fri: 8.30 • Sat: 9-4pm  
• 144 Logan Rd • Ph: (07) 3393 0777 • Fax: (07) 3393 0045  
• Mon/Fri: 9-5.30 • Thurs: 8.30 • Sat: 9-4pm

### BURANDA QLD

### CANBERRA ACT

• 11 Kembla St. Fyshwick • Ph: (06) 239 1801  
• Fax: (06) 239 1821 • Mon/Fri: 9-5.30 • Sat: 9-1pm  
• 266 Sydney Rd • Ph: (03) 9384 1811 • Fax: (03) 9384 0061  
• Mon/Fri: 9-5.30 • Fri: 8.30 • Sat: 9-4pm

### COBURG VIC

### MELBOURNE CITY

• Shop 2, 45 A Beckett St • Ph: (03) 9663 2030 • Fax: 9663 1198  
• Mon/Fri: 8.30-5.30 • Fri: 8.30 • Sat: 8.30-4 • Sun: 10-4pm  
• 887-889 Springvale Rd Mulgrave. Nr Cnr. Dandenong Rd  
• Ph: (03) 9547 1022 • Fax: (03) 9547 1046  
• Mon/Fri: 9-5.30 • Fri: 8.30 • Sat: 9-4pm

### SPRINGVALE VIC

### SYDNEY CITY

• 129 York St • Ph: (02) 267 1614 • Fax: (02) 267 1951  
• Mon/Fri: 8.30-6pm • Thurs: 8.30pm • Sat: 9-4pm

### BANKSTOWN

• 363 Hume Hwy Cnr Meredith St • Ph: (02) 709 2822 • Fax: (02) 709 2007 • Mon/Fri: 9-5.30 • Thurs: 8.30pm • Sat: 9-4 • Sun: 10-4pm

### GORE HILL

• 188 Pacific Hwy (Cnr. Bellevue Ave) • Ph: (02) 439 4799 • Fax: (02) 439 4895 • Mon/Fri: 9-5.30 • Thurs: 8.30 • Sat: 9-4 • Sun: 10-4

### NEWCASTLE

• 830 Hunter St. (Cnr Stewart Ave) • Ph: (049) 653 799  
• Fax: (049) 653 796 • Mon/Fri: 9-5.30 • Sat: 9-4pm

### PARRAMATTA

• 355 Church St. (Cnr Victoria Rd) • Ph: (02) 683 3377 • Fax: (02) 683 3628 • Mon/Fri: 9-5.30 • Thurs: 8.30pm • Sat: 9-4 • Sun: 10-4pm

### PENRITH

• 199 High St • Ph: (047) 21 8337 • Fax: (047) 21 8935  
• Mon/Fri: 9-5.30 • Thurs: 8.30 • Sat: 9-4pm • Sun: 10-4pm

### PERTH

• 326 Newcastle St Northbridge • Ph: (08) 328 8252  
• Fax: (08) 328 8982 • Mon/Fri: 9-5.30 • Sat: 9-4

### RHODES

• 8-10 Leeds St • Ph: (02) 743 5222 • Fax: (02) 743 2066  
• Mon/Fri: 9-5.30



POST & PACKING

\$10 to \$24.99=\$4.00

\$25 to \$49.99=\$5.00

\$50 to \$99.99=\$7.00

OVER \$100=\$8.00

## DSE 'Discovery Series' Construction Project:

# A LOW COST STEREO PREAMP

The latest release in the Discovery Series of learning kit projects from Dick Smith Electronics is this low cost and compact stereo preamp module, which provides all four of the usual control facilities: volume, bass and treble tone controls, and channel balance. It can be combined with a suitable stereo power amp to make a complete hifi system, but can also be easily adapted for use as a simple stereo mixer for recording, etc. The kit for the module is available from DSE's stores as K-2811, priced at \$34.50.

This compact high quality audio module makes it possible to upgrade your basic power amplifiers into a complete audio system, by adding volume, bass, treble and balance controls. The circuit is stereo, with an extra input to both channels that can be used for either multi channel mixing or gain control applications.

Suitable audio sources include CD players, tuners, VCR's, tape players or similar, but the gain can be easily increased to use low level sources like microphones or record players. Application circuits are provided to show how mixing, balanced inputs and other useful configurations can be implemented.

The module is small, measuring only 122 x 56mm, and has the four dual control pots mounted directly on the PCB board. The complete assembly is light enough to allow it to be supported solely by the controls, although if you prefer mounting posts can be used.

Power for the module can be from single supplies within the range 9V to 36V, or from dual supplies within the range

SPECIFICATIONS	
<b>Supply voltage:</b>	9V to 36V
Single supply	+/-4.5V to +/-18V
Dual supply with optional regulators	+/-7V to +/-40V
<b>Supply current:</b>	18 to 25mA typical
<b>Frequency response:</b>	4Hz to 80kHz (controls centred)
<b>Tone control range:</b>	
Bass	+/-18dB at 20Hz
Treble	+/-18dB at 20kHz
Crosstalk:	-86dB at 1kHz, 1V RMS out
<b>S/N ratio:</b>	100dB A weighted (1kHz, 1k $\Omega$ source, 1V out)
<b>Voltage gain:</b>	3.5V/V (11dB)
<b>Input impedance:</b>	40k $\Omega$ (approx)
<b>Output impedance:</b>	100 $\Omega$ (approx)

+/-4.5V to +/-18V. By adding two optional components to the PCB, dual supplies up to +/-40V can be used.

### Circuit description

The stereo audio signal passes through three stages, each stage using one LM833 dual audio operational amplifier IC. For each of these IC's, one of its op-amps is used by the left channel and the other by the right channel. Despite the two channels sharing the same IC pack-



ages like this, the crosstalk within the IC is typically very low, at only -120dB.

Although the following description refers only to left channel components, it can be applied equally to the corresponding components in the right channel, since both channels are identical. Use of the extra inputs will be described later, and for the basic circuit are left disconnected.

**Stage 1:** The first stage uses op-amp IC1a. The main purpose of this stage is to act as a buffer, between the volume control and the stage two tone controls.

Without this buffer the response of the tone controls would be effected by the impedance of the source and by the volume control setting.

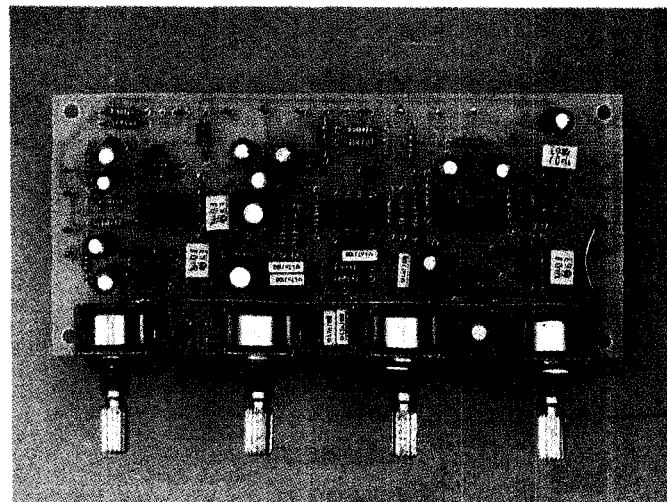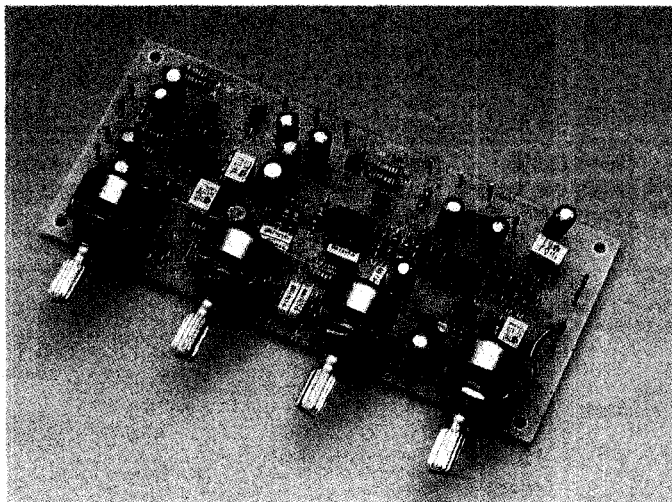The second function of this stage is to set the overall gain of the circuit, the last two stages having approximately unity gain. Putting most of the gain in the first stage gives a better overall signal to noise ratio than if the later stages provided the gain. The magnitude of the gain is determined by the values of resis-



Both of these views of the new module show it wired as a stereo preamp with volume, bass, treble and balance controls.



tors R2 and R3, according to the following formula:

$$\text{stage 1 gain} = (R2+R3)/R2 \\ = 3.5V/V \text{ (11dB)}$$

If the gain needs to be changed, the best way is to reduce the value of resistor R2 for more gain, or increase it for less gain.

The high end of the frequency response is rolled off by capacitor C3, to ensure the stability of IC1a and attenuate any unwanted ultrasonic frequencies.

Capacitor C1 prevents the op-amp's DC input current (which flows out of the inputs) from flowing through the sliding contact of volume control VR1, the bias path being provided instead by fixed resistor R1 to the bias supply rail. Capacitor C2 gives the stage unity DC gain, which is necessary with single supply operation, by blocking a DC path through R2.


**Stage 2:** This stage, using op-amp IC2a, is a version of the Baxandall active tone control. Active tone controls are those which have the control elements as part of the feedback loop of an amplifier, in this case the negative feedback loop. This type of tone control offers advantages over the passive variety: they are symmetrical about the axis in cut and boost operation, they have very low THD (total harmonic distortion), and the range of component values is small.

The gain of this stage at any frequency is equal to the ratio of the feedback impedance between pins 6 and 7, and the impedance between pin 6 and the input to the stage. So when the tone controls are both set to their middle positions, the gain of the stage at all frequencies is unity. This also tends to be its gain at mid frequencies (i.e., around 1kHz).

With the bass control VR3 set to maximum boost, the gain of the stage at low frequencies can be calculated by considering C5, C6 and C7 to be open circuit, and is equivalent to the maximum bass boost, given by the following formula:  
 maximum bass boost =  $(R8+VR3)/R7 = 10$  (20dB)

Because of the symmetry of the feedback circuit, the maximum bass cut is simply equal to the reciprocal of this value, which is 0.1 or -20dB.

Conversely, with the treble control VR2 set to maximum boost, the gain of the stage at high frequencies is calculated by considering C5, C6 and C7 to be short circuits — as their reactance will be very low. The bass and treble networks are now in parallel, and the gain

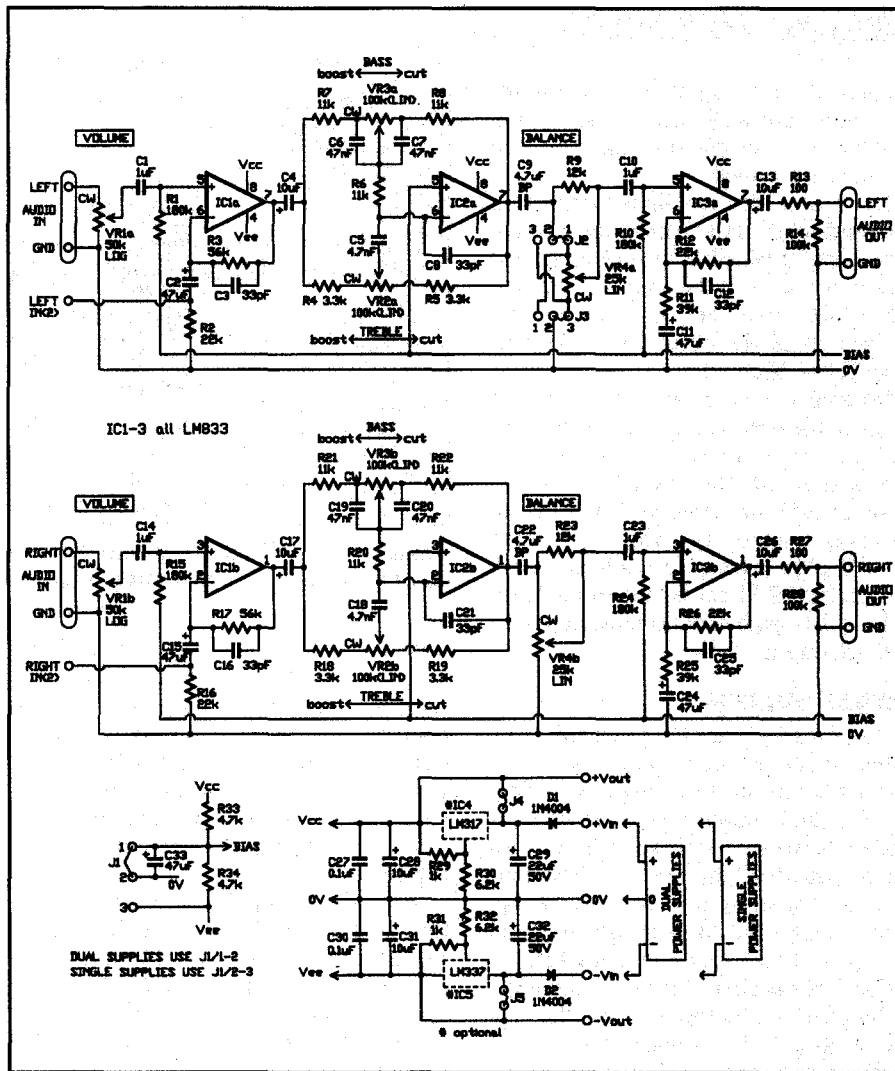

**Fig.1: The schematic for the preamp module when connected as a standard stereo preamp with volume, bass, treble and balance controls. It's very flexible however, and can be wired in a variety of other configurations.**

of the stage/maximum treble boost is given by the more complicated formula:  
 maximum treble boost =  $(R4+3R)/(VR2+R5)/R4/(VR2+R5+3R)$   
 which simplifies to  $= 8.3$  (18dB)  
 where  $R = R6 = R7 = R8$ .

As before, the circuit is symmetrical and so the maximum treble cut is 0.12, or -18dB.

One component of the feedback loop that has been ignored until now is capacitor C8. This capacitor contributes to the desired rolloff at supersonic frequencies, without affecting the tone control action significantly. It also ensures that the stage remains stable under all conditions.

The signal input to this stage is coupled via capacitor C4, a DC blocking capacitor. The output coupling capacitor C9 is a bipolar type because the polarity of the voltage across it changes, depend-

ing on whether single or dual power supplies are used.

**Stage 3:** This stage, using IC3a, acts as a buffer between the balance control and the output load.

Balance control VR4 is simply a stereo volume control with the pot for the left channel connected in reverse. With the control centred, both pots give the same attenuation and so the two channels are balanced. With the control fully anticlockwise, the left channel has maximum gain and the right channel is off and vice-versa for the fully clockwise position.

Resistor R9 connected across the top end of both balance pots serves to decrease their attenuation and seems to enhance the 'feel' of the control. A more common type of balance control uses a single pot wired across both channels with the sliding contact earthed. This

# Stereo Preamp

method, while being simpler, can introduce more crosstalk due to the sliding contact not completely earthing the potentiometer track.

The reason for the links connecting both ends of the left channel balance pot is to make it possible to reverse it, and hence to use it as the 'master' volume control in mixer applications. In that configuration, the normal volume control VR1 is disabled.

Op-amp IC3 is given a small amount of gain, determined by the values of R11 and R12, to compensate for the attenuation of the balance control. Resistor R13 in series with the output prevents instability from occurring when highly capacitive loads are used, and resistor R14 across the output provides a DC path around capacitor C13 to discharge it.

## Power supply

The preamp can be powered from either single or dual power supplies, selected by means of a single wire strap J1. For dual supplies J1 must be connected between terminals 1-2 and for single supplies between 2-3. The purpose of this strap is to bias all the op-amp outputs at a voltage midway between the two supply rail voltages.

For dual supplies, this bias is automatically provided by the 0V from the supply, so strap J1/1-2 connects the bias rail to 0V. Single supplies however, do not have this half-rail potential available, so resistors R33 and R34 provide the bias. Also, with single supplies the Vee and 0V rails are now connected together by J1/2-3, to make the negative rail the common ground.

Diodes D1 and D2 protect against

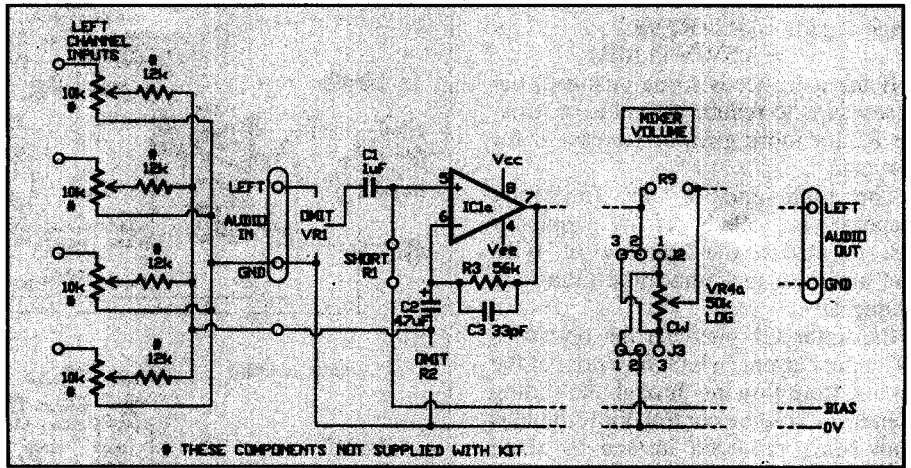


Fig.2: How the module is wired in order to turn it into a four channel mixer. IC1a becomes an active mixer stage, with VR4 becoming the volume control.

reversed polarity and capacitors C27-32 provide filtering. For dual supplies with voltages greater than +/-18V, PCB connections are available for inserting optional voltage regulators IC4 and IC5. These devices allow input voltages up to +/-40V to be used, and also offer the advantage of removing power supply noise.

With single supplies there is no use for negative regulator IC5, which can be replaced by wire strap J5. Similarly there is no need for diode D2, which can also be replaced by a wire strap.

When the regulators are used, voltages Vcc and Vee are determined by the values of resistors R29, R30 and R31, R32 respectively according to the following formula:

$$V_{cc} = 1.25 * (R_{29} + R_{30}) / R_{29} = 9V \text{ (with values supplied)}$$

For the regulators to function properly, their input voltage must be at least

2.5V greater than their output voltage. So, with the regulated voltages set to +/-9V the supply voltages must be at least +/-12V.

If IC4 and IC5 are not used, then straps J4 and J5 must be inserted in their place, and resistors R29-32 can either be left in, or removed to reduce power consumption.

As well as the three power input terminals +Vin/0V/-Vin, three power output terminals +Vout/0V/-Vout have been provided. These can be used to provide a regulated supply to other PCB's (when IC4 and IC5 are used), instead of installing regulators on each board.

## Creating a mixer

Fig.2 shows how the module can be configured as a stereo mixer. This example shows four channels, but more can be added if needed.

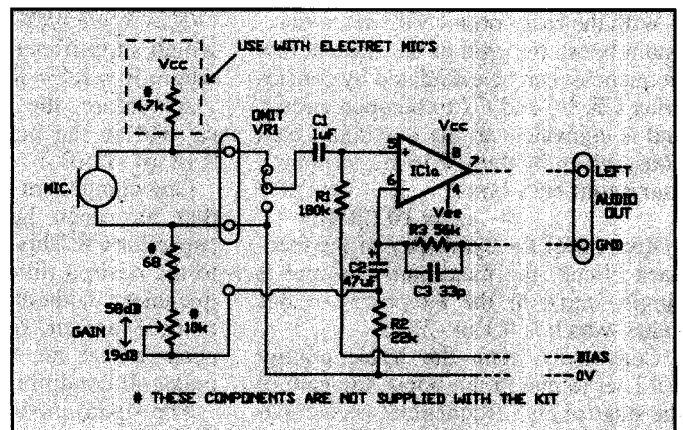
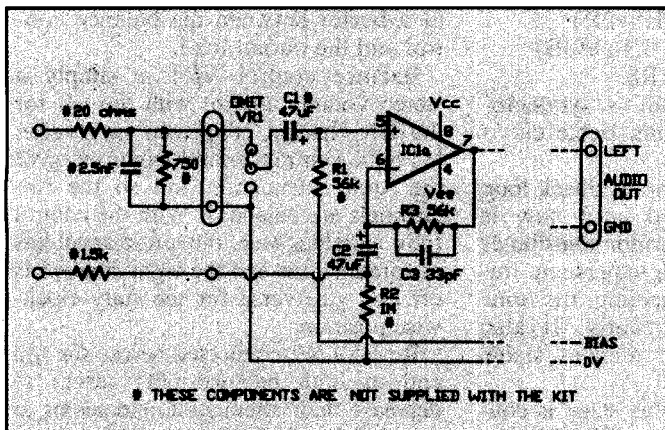


Fig.3 (left): How the module input stage is configured in order to provide a balanced microphone input. Note that VR1 is omitted. Fig.4 (right): For improved signal to noise ratio with microphones, the input stage can be configured to provide an active (negative feedback) volume control.

In this configuration the normal volume control VR1 is removed, the non-inverting (+) input of IC1 is connected directly to ground by replacing R1 with a strap, and R2 is left out. The extra input now becomes a 'virtual earth', which means that signal currents from a number of sources can flow into it without the sources interfering with one another.

The gain for each mixer input is given by the value of R3 (56k) divided by the value of the resistor in series with the input concerned (12k). With the values shown, the gain is 56k/12k, or 4.7. Potentiometer VR4 can be converted from a balance control to a master volume control by moving strap J2 to position 2-3 and strap J3 to 1-2. Also if desired, the 25k linear pot normally used for VR4 can be replaced by the 50k log pot that was VR1.

### Balanced input

Fig.3 shows how the extra input can be used to create a balanced microphone preamplifier.

In this configuration the volume control is again removed and replaced by a strap. Capacitor C1 is replaced by a 47uF electrolytic capacitor (the same as C2), R1 is replaced by 56k and R2 is replaced by 1M. Four external components have to be added as shown, including a 2.5nF capacitor which can be made of a 1nF/MKT in parallel with a 1.5nF/MKT.

This circuit can be called a *subtract-*

PARTS LIST			
<b>Resistors</b>			
1/4W 1% metal film unless otherwise stated:			
			<b>Colour Code</b>
			<b>4 band</b> <b>5 band</b>
R1,10,15,24	180k	brn-gry-yel-brn	brn-gry-blk-org-brn
R2,12,16,26	22k	red-red-org-brn	red-red-blk-red-brn
R3,17	56k	grn-blu-org-brn	grn-blu-blk-red-brn
R4,5,18,19	3.3k	org-org-red-brn	org-org-blk-brn-brn
R6-8,20-22	11k	brn-brn-org-brn	brn-brn-blk-red-brn
R9,23	12k	brn-red-org-brn	brn-red-blk-red-brn
R11,25	39k	org-whit-org-brn	org-whit-blk-red-brn
R13,27	100	brn-blk-brn-brn	brn-blk-blk-blk-brn
R14,28	100k	brn-blk-yel-brn	brn-blk-blk-org-brn
R29,31	1k	brn-blk-red-brn	brn-blk-blk-brn-brn
R30,32	6.2k	blu-red-red-brn	blu-red-blk-brn-brn
R33,34	4.7k	yel-vio-red-brn	yel-vio-blk-brn-brn
<b>Potentiometers</b>			
VR1	50k	log dual gang 16mm PCB mtg	
VR2,3	100k	lin dual gang 16mm PCB mtg	
VR4	25k	lin dual gang 16mm PCB mtg	
<b>Capacitors</b>			
C1,10,14,23	1uF	63VW MKT	
C2,11,15,24,33	47uF	25VW RB electrolytic	
C3,8,12,16,21,25	33pF	50VW NPO ceramic	
C4,13,17,26,28,31	10uF	25VW RB electrolytic	
C5,18	4.7nF	100VW MKT (.0047, 4700, 472)	
C6,7,19,20	47nF	100VW MKT (.047, 473)	
C9,22	4.7uF	50VW bipolar electrolytic	
C29,32	22uF	50VW RB electrolytic	
C27,30	0.1uF	50VW ceramic (100nF,104)	
<b>Semiconductors</b>			
IC1-3	LM833 dual op-amp		
D1,2	1N4004 power diode		
<b>Miscellaneous</b>			
PCB, 122 x 56mm code ZA1211; PCB terminal pins.			

ing amplifier, because it only amplifies the difference between the two input signals. It does this by amplifying the individual inputs with the same gain but 180° out of phase. As well as the gain


characteristics, it is important that both inputs have the same impedance to ground, so that noise tends to be picked up identically at both inputs and is therefore cancelled.

Ignoring component tolerances, the circuit in Fig.3 is balanced except at frequencies below about 10Hz. Capacitors C1 and C2 cause an imbalance at very low frequencies which is minimised, but not cancelled, by making them the same value. In any case, the gain rolloff at low frequencies compensates for the imbalance. To optimise the balance at low frequencies, the two inputs can be tied together and connected to a noise source while trimming the two series input resistors for minimum output.

For optimum balance at high frequencies, the 2.5nF capacitor across the non-inverting input should be an MKT type and may have to be trimmed in value due to wide capacitance tolerances. Also, capacitor C3 could be replaced with a more stable polystyrene type.
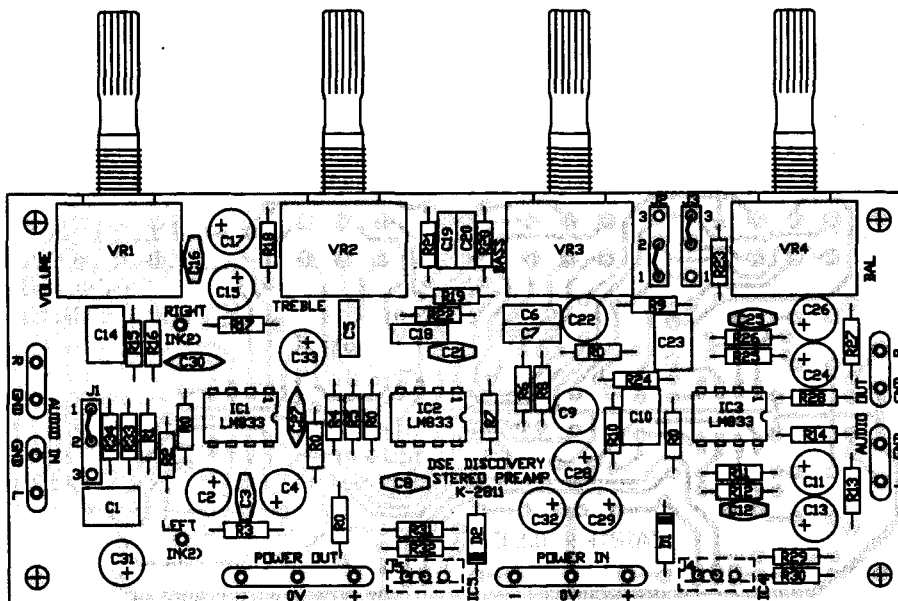
### Active gain control

When using the kit as an unbalanced microphone or phono preamplifier, there are two methods that can be used to achieve the necessary increase in gain. Firstly, resistor R2 can simply be



Use this overlay diagram as a guide if you are wiring up the module in its basic stereo preamp configuration, together with the photos on page 90. Note that the metal frames of the potentiometers are connected to signal ground.

**JACQUES**  
AUDIO • VIDEO

**DIGITAL INTERCOM  
SYSTEMS & AUDIO  
VISUAL EQUIPMENT**

- Correctional Centres
- Police Stations
- Hospitals
- Schools
- Hotels/Motels/Resorts
- Lecture Theatres
- Board Rooms
- Video Conferencing

▲ MANUFACTURERS ▲ DISTRIBUTORS  
▲ SYSTEM ENGINEERS

**PHONE (07) 3844 1103  
FAX (07) 3844 1078**

**JACQUES ELECTRONICS PTY LTD  
268 Montague Road  
West End Q 4101**

READER INFO NO. 19

**NEW KITS FOR  
EA PROJECTS**

**FROM DICK SMITH ELECTRONICS:**

**ESR-Low Ohms Meter** (January 1996): The DSE kit is complete with case, pre-punched and silk screened front panel, and tinted perspex filter. It includes pre-programmed micro, all specified components and test leads with clips. Cat. No. K-7404, it is priced at \$59.50.

**PC-Driven EGO Analyser** (Jan/Feb 1996): The DSE kit is complete with case, pre-punched and silk screened front panel, all specified components, cable/connectors for the printer port cable, and software on a 3.5" disk. Cat. No. K-4214, it is priced at \$49.95.

**FROM JAYCAR ELECTRONICS:**

**Dual 12V Battery Manager** (Jan/Feb 1996): The Jaycar kit is complete with case, PCBs and all specified components. Cat. No. KA-1782, it is priced at \$44.95.

**ESR-Low Ohms Meter** (January 1996): The Jaycar kit is complete with case, silk screened front panel, pre-programmed micro and all specified components, and test leads with clips. Cat. No. KA-1783, it is priced at \$69.50.

**PC-Driven EGO Analyser** (Jan/Feb 1996): The Jaycar kit is complete with case, silk screened front panel, all specified components and cable/connectors for the printer port cable. Cat. No. KA-1781, it is priced at \$37.95.

*NOTE: This information is published in good faith, as supplied by the firms concerned and as a service to readers. Electronics Australia cannot accept responsibility for errors or omissions.*

**Stereo Preamp**

**TABLE 1: Wire links**

The function of the various wire links are described in the text, but the following table gives a summary:

Link Function	Insert Link	Omit Link
Dual power supplies	J1/1-2	J1/2-3
Single power supplies	J1/2-3	J1/1-2
Basic preamp (Fig.1)	J2/1-2	J2/2-3
	J3/2-3	J3/1-2
	J2/2-3	J2/1-2
Mixer (Fig.2)	J3/1-2	J3/2-3
IC4 option not installed	J4	
IC5 option not installed	J5	
IC4 installed		J4
IC5 installed		J5

replaced by a smaller value, typically in the order of 100 ohms depending on the input signal level, and use VR1 to control the signal level. Alternatively, the active gain control configuration shown in Fig.4 can be used.

In this configuration VR1 is removed and replaced with a strap, and the full signal level from the source appears at the non-inverting (+) input of the opamp. An external series resistor and potentiometer are then connected in parallel with R2 to control the gain of the opamp, rather than by attenuating the input signal level. This method typically results in a higher signal to noise ratio than with the passive volume control.

**Construction**

To mount the components on the PCB, start with the low profile components first and then work your way up to the taller components.

To place the components, look at the overlay diagram which shows how the components and wire links actually appear on the PCB. Read the label of the component, e.g. C5, from the overlay and then look up the description next to that label in the parts list. For example, C5 is an MKT type capacitor and has the value 4.7nF, so it may be marked either 4.7nF, .0047uF, 4700pF or 472 (i.e.  $47 \times 10^2$  pF).

Occasionally one of the supplied capacitors may be marked with a voltage rating greater than that shown in the parts list, which is acceptable as long as it fits on the PCB. If the voltage rating is less than that shown in the parts list, then advice should be sought unless the discrepancy is explained in the errata section at the end of the instructions.

Begin construction by installing the resistors. Resistors have their values marked on them as a colour code, which is given in the parts list. The last band of

the colour code gives the tolerance value, and is the colour band furthest from the others. Resistors are non-polarised and can be mounted in either direction, but it is good practice to mount them with their colour codes all in the same direction so that it is easier to read the values later. Some of the resistors are labelled R0 on the overlay. These are actually wire links built like resistors and have a single black band in the centre. They are used in place of wire links wherever possible because they are easier to insert and look neater.

At this stage it is also probably a good idea to work out which wire links need to be inserted. Refer to Table 1 if you're not sure which to install or leave out.

The remaining components are installed as follows.

**Diodes:** These have a band on them close to one end and must be mounted in the direction shown on the overlay.

**IC's 1-3:** These have an eight pin DIL (dual in-line) package, with a dot or notch at the end near pin 1. The overlay shows at which end the notch should be. The IC pins count anticlockwise from this notch or dot, looking at the top of the package.

**Ceramic and MKT capacitors:** These two types of capacitors are non-polar, and can be mounted in either direction.

**Electrolytic capacitors:** All of these except for C9 and C22 are polarised types which will have a negative (-) or (+) sign printed on them — normally the (-) lead is marked. On the overlay the position of the positive lead is marked. C9 and C22 are bipolar and can be mounted in either direction.

Finally, the PCB pins can be inserted for making connections to the PCB. They are normally inserted through the top of the PCB with the short end passing through the PCB.

With the assembly of the board complete, carefully check all of your soldering. Look especially for dry solder joints, and solder bridges shorting tracks together.

**Connecting it up**

To connect sockets or switches to the inputs of the preamp, always use shielded cable if the connections are more than a few centimetres long. The output connections are not as sensitive to picking up noise, but should also be shielded.

The power wiring does not have to be shielded, but should be kept away from the signal wiring. The 0V power wiring should be run separately from the input/output ground wiring. ♦

# Pantech For High Quality

## 3200 Count "Pen" DMM Has Analog Bargraph

- Easy read-out with 3200 count display and analog bargraph
- Auto and manual range selection
- DC/AC Volt to 600 V, Resistance to 30 M $\Omega$
- Auto-power-off, Data hold mode, Fast continuity beeper
- Rugged construction with high-impact thermoplastic case
- Standard pitch input jacks
- Basic accuracy:  $\pm 0.7\%$  rdg + 2 dgt

PANTEC 3210 **\$119** ex tax  
(\$145 inc tax)



## 4000 Count TRMS DMM Provides 42 Segment Curved Bargraph

- Auto/manual range selection
- True RMS, Vdc to 1000 V, Vac to 750 V, AC/DC current up to 10 A
- Frequency counter up to 1 MHz, Capacitance measurements
- Adapter measurements, Resistance up to 40 M $\Omega$ , Diode continuity test
- Water resistant/fire retardant case, Auto-power-off
- Data hold mode/relative mode, Min/max hold function, Memory store/recall
- Input impedance 10 M $\Omega$
- Basic accuracy:  $\pm 0.1\%$  rdg + 2dgt

PANTEC 2820RMS **\$325** ex tax  
(\$396 inc tax)



## 3200 Count Economy DMM With 65 Segment Curved Bargraph

- Auto/manual range selection
- Vdc to 1000 V, Vac to 750 V
- Aac/dc to 10 A, Ohms to 30 M $\Omega$
- Auto-power-off
- Water spray protected, dust proof IP 64
- Data hold and delay hold modes
- Basic accuracy:  $\pm 0.5\%$  rdg + 2dgt

All Meters Have  
**FREE Case  
And/Or Holster**

PANTEC 2710 **\$160** ex tax  
(\$195 inc tax)



## AC/DC TRMS 1000A Clamp With Multifunctions


- Large 4000 counts display and analog bargraph
- Aac/dc to 700 A, True RMS for AC current/voltage
- AC Volt up to 750 V, DC Volt up to 1000 V
- Resistance to 40 M $\Omega$ , Frequency to 4000 kHz
- Data hold, Peak hold, Max hold functions
- Zero Adjustment / Relative Reading, Auto/manual ranging
- Clamp opening 46 mm
- AC Current Accuracy:  $\pm 2\%$  rdg + 5 dgt
- Basic DC Volts Accuracy:  $\pm 0.75\%$  + 2dgt

PANTEC 6410RMS **\$398** ex tax  
(\$485 inc tax)


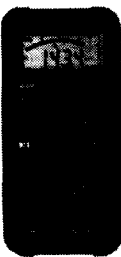
## Low Cost 4000 Count TRMS DMM With 40 Segment Curved Bargraph

- Water spray protected and dustproof to IP 64
- Auto/manual range selection
- True RMS, Vdc to 1000 V, Vac to 750 V, AC/DC current up to 10 A
- Resistance up to 30 M $\Omega$
- Auto-power-off, Diode/continuity test
- Data hold and delay hold modes
- Basic accuracy:  $\pm 0.5\%$  rdg + 2 dgt



PANTEC 2720RMS **\$195** ex tax  
(\$237 inc tax)

## 4000 Count DMM with 42 Segment Curved Bargraph

- Auto/manual range selection, Auto-power-off
- Vdc to 1000 V, Vac to 750 V, AC/DC current up to 10 A
- Frequency counter up to 1 MHz, Capacitance & Adapter measurements
- Data hold mode/relative mode, Min/max hold function
- Memory store and recall functions
- Water resistant and fire retardant case
- Basic accuracy:  $\pm 0.4\%$  rdg + 2dgt

PANTEC 2810 **\$265** ex tax  
(\$323 inc tax)



## 600 A Digital Clamp Meter With 4000 Counts

- Easy read-out LCD display, Manual range
- Data Hold, Peak Hold
- AC current to 600 A, AC and DC Volt to 600 V
- Ohmmeter and continuity check
- Diode test
- Clamp opening 32 mm
- Aac accuracy:  $\pm 1.5\%$  rdg + 4 dgt
- Vdc accuracy:  $\pm 1\%$  rdg  $\pm 1$  dgt

PANTEC 6220 **\$140** ex tax  
(\$170 inc tax)



Full range of accessories, probes, test leads, holsters, carry cases etc available. Many other DMMs available - call us with your requirements.

Ask for NEW 1996 Catalogue. Available FREE!

# OBIAT PTY LTD

129 Queen Street, Beaconsfield.

P.O.Box 37 Beaconsfield NSW 2014

Tel : (02) 698 4111 Fax : (02) 699 9170

Call for the name of your local stockist



FIRST NEW LOOK ISSUE your computer

# YOUR computer

WHAT TO BUY HOW TO USE IT

DECEMBER 1995 \$8.40\*  
NZ \$9.70 (air Express Edition Inc GST)  
NDD

More than 200  
Australian PCs listed

# BUYERS GUIDE

Find your solution  
see page 115

## WORD PROCESSORS

Make your words work

5 of the best on test



Your Computer is Australia's only computer magazine written for small business and home users.


Our editorial is locally written and is slanted with a 'hands on' approach for those who believe in PCs as a tool to increase business efficiency and productivity. As it says on our cover we've been Helping PC users since 1981.

To subscribe to *Your Computer* magazine phone TOLL FREE 1800 800 933 - Sydney residents phone (02) 353 9992 - and have your credit card details ready. Or send your name, address and phone number, with your payment of \$55 for 12 issues (cheque, credit card details or money order) to: Federal Publishing, Subscriptions Department, Reply Paid No. 3, PO Box 199, Alexandria, NSW 2015 (no stamp required) or fax (02) 353 0967.

your  
**computer**  
on sale now

# ALTRONICS COMPONENTS

ALTRONICS Fax Order Line: (09) 328 3487

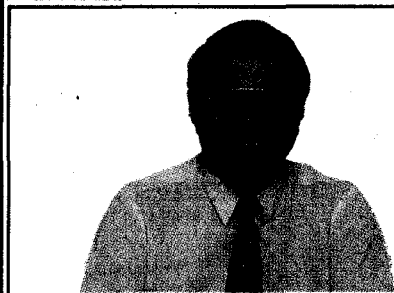

## ALTRONICS

**For Ultra Quick delivery.**  
 Phone Order on 1-800 999 007. Jetservice  
 Delivery - next day all capital cities and suburbs,  
 please add 24 - 48 hours for country clients.

Regards, Jack O'Donnell, Managing Director

### EPROM Emulator Kit

(See EA Dec '95) This EPROM emulator allows you to do away with EPROM's whilst in the prototyping stage of product development. The emulator is connected to a spare parallel port on your computer and also the 'target' board. The EPROM file (that is normally downloaded into the EPROM), is then transferred into the emulator by copying the file to the parallel port. This process saves repetitively "blowing" new EPROM's with each modification to the program. Emulates 2764, 27128, 27256 and 27512 EPROM's.


K 9530 **Just \$149**

### Signal Comparator Kit

(See EA Aug '93) If you have ever tried to fix a circuit without a circuit diagram you will know how frustrating it can be. If you have an operational unit this can ease the pain but still, difficulties can be incurred. This kit could help. It can compare two circuits point to point and will indicate any difference between them.

K 2563 Normally \$39<sup>95</sup>,

**This Month Only \$29**

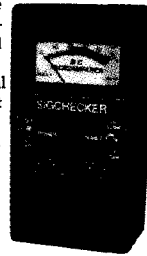

### Digital Storage C.R.O. Adaptor Kit for P.C.'s

(See EA Jan '93) This great kit enables a P.C. user to capture a waveform and zoom in to segments of interest then save them to disc. The unit has 32K of storage memory and a sampling rate of over 600K samples per second. Input level of up to 2.5 Volt. Full sampling rate between 15K s/s to over 600K s/s. Input impedance of 1M ohm.

K 2805 Normally \$63<sup>50</sup>,

**This Month Only \$55**

K 2812 PC 3.5" Disk Software to Suit \$29.95

### 5 Band Graphic Equaliser Kit **NEW**

(See SC Dec '95) Liven up your keyboard, guitar or music system with this 5 band graphic equaliser. It uses only a few low cost parts and parts and will vastly improve the versatility of your sound system. Bands are centred at 63Hz, 250Hz, 1kHz, 4kHz and 16kHz, with a ±12dB boost/cut adjustable level on each band. Requires +15V power supply (not included).

K 5305 **\$39.95**

### PC Based EPROM Programmer Kit

(See EA Sept '93) This is a great new kit for programming EPROM's from 2716 to 27256. Compares favourably against commercial units costing \$\$\$ more. This kit puts you in the driving seat for under \$100. It is flexible enough to be able to program 12.5, 21 and 25V EPROMs/EEPROMs.

K 9525 **\$97.50**

K 9526 3.5" PC Software to Suit \$19.95

### 50W Mosfet Amp Module Kit

This great module features moderate power output at low harmonic distortion. Simple to build and compact in size this unit makes a great replacement module for your old Hi-Fi or buy two and make your own stereo amplifier. Requires ±50V DC supply.

**Power Output:** .....50W into 8Ω  
**Freq. Response:** .....25Hz-20kHz, ±1dB  
**Input Sensitivity:** .....1V RMS  
**T.H.D.:** .....0.05%

K 5115 **\$54.95**

### Ignition Killer Kit

(See SC Dec '95) There are many ways of theft prevention for your vehicle. Disabling the ignition is perhaps one of the better methods, as it can totally immobilise the car. This ignition killer will help prevent your car from being stolen by producing erratic behaviour in the ignition system. The thief will suspect a problem with the car and leave it.

K 4380 **\$29.95**

### Digital Announcement Recorder Kit

(See EA Feb '95) This kit is an extremely flexible microprocessor controlled eight channel digital voice recorder. Requires no battery back up for memory. Will record up to 8 different messages, with a total time up to 16 seconds. Each message can be individually triggered. Features chime function, an on-board 2 watt amplifier, negative or positive trigger, once only or recycling announcement function etc.

K 9580 **\$109**

### Impedance Meter Kit

Measuring a transformer with a standard ohm meter will not give accurate results because it is measuring with a DC signal, not AC. This invaluable unit is fantastic for checking transformers and speaker impedances. For those people dealing in PA equipment, the built in tone generator enables an entire PA system to be checked before the amplifiers are connected. Uses one 9 Volt battery. (Not supplied). Three ranges enable accurate measurement of 2 - 20,000 ohms. Accuracy mid range typically ±5%.

K 2550 Kit Version **\$99**

K 2551 Fully Built & Tested Version **\$159**

### High Efficiency Fluoro Inverter Kit

(See SC Nov '93) Ideal for camping, fixing cars etc. This circuit will drive a standard 40 Watt fluoro tube from a 12 volt source. Being a fluoro light, it draws less current than an incandescent globe. Features flicker free starting/running, reverse polarity protection and faulty tube protection. Globe and housing not included. Requires 11 to 14V DC power source. Suitable for 18, 20, 36 and 40W globes. Low EMF radiation.

K 6370 **\$69.00**

*Ideal for Camping.  
 Farmers. Fixing cars etc.*

### Auxiliary Battery Manager

(See EA Jan '96) Ideal for those who have a car with a second battery. This circuit will monitor the voltage of the second battery and if it drops below a set point it will disconnect the second battery from the main battery. This prevents the second battery from being drained and allows the main battery to be recharged. The circuit is controlled by a microprocessor and will also monitor the voltage of the main battery and will disconnect it if it drops below a set point. Also, the circuit will monitor the voltage of the main battery and will disconnect it if it drops below a set point.

K 4330 **\$49.95**

Add Incredible Bass to Your Hi-Fi or Home Theatre System!

ALTRONICS

ALTRONICS

ALTRONICS

ALTRONICS

ALTRONICS

ALTRONICS

ALTRONICS

**1-800 999 007 PERTH (09) 328 1599**

# OVERNIGHT DELIVERY

## The Powerhouse 600W & 1200W Inverters

(See EA Feb '92) These Power Inverters will provide all your power requirements from a heavy duty 12 or 24V battery. Using the latest Mosfet output stage and toroidal transformer the inverters are both efficient and will deliver high surge currents. The Powerhouse has been designed not only for rugged operation but for ease of construction. The kits come to you in a fully drilled, pre punched chassis complete with silk screened front panel. Assembly of the kit is simplified as the majority of components mount on a single PCB. Thus virtually eliminating all external terminations. Suitable for use in camping, boating, fishing, mining, farming, remote settlements etc.

**Now with Improved Circuitry!**

K 6776 12V Input, 600W Kit Version **\$535**  
K 6778 24V Input, 600W Kit Version

K 6796 1200W Kit Version **\$799**  
K 6798 1200W Kit Version

## At Last - An Accurate Digital LCR Meter


In the past multimeters including inductance and capacitance ranges have been relatively mediocre in their performance. This new model will measure inductance, capacitance and AC resistance with great accuracy! Ideally suited for speaker crossover design and transformer/coil manufacture.

Supplied complete with two sets of leads and inbuilt sockets for direct measurement of inductors, capacitors or resistors. Includes integral bench stand.

**Resistance Ranges:** .....20, 200, 2k, 20k, 200k, 2M, 20M  
**Capacitance Ranges:** .....200pF, 2nF, 20nF, 200nF, 2µF, 20µF, 200µF

**Inductance Ranges:** 2mH, 20mH, 200mH, 2H, 20H, 200H  
**Accuracy:** .....Better than 5%

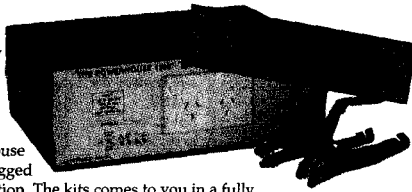Q 1010 Normally \$199, Now Only **\$149**



**Get 240V from Your 12V or 24V Car/Boat/Truck Battery!**  
Ideal for Camping, Boating, Farming etc.

## PCB Spacers

We are massively over-stocked with incorrectly supplied PCB spacers - incorrect because they have an odd UNC4/40 thread. Although perfectly fine with the correct bolt, we are unable to sell them separately. So out they go at never to be repeated prices. All are quality heavy duty nickel plated brass.

All are supplied in packs of 100 spacers with 200 6mm bolts.

HX1391 10mm Spacer **\$7.50**  
HX1394 15mm Spacer **\$10**  
HX1397 25mm Spacer **\$15**

**Massive Savings on Regular Prices. Save Up to 60%**

## Famous Labtech 20MHz Dual Trace Oscilloscope

This model is a dual trace, 20MHz oscilloscope with a high brightness CRT. The vertical amplifiers have high sensitivity of 5mV/div and a frequency characteristic response with a smooth roll off exceeding 20MHz. The TV sync. signal operator circuit is provided to ensure stable observation of video signals. Triggering is obtained by sampling the AC wave form, external waveform or internally generated trigger.

Q 1015 Normally **\$729.00**


**This Month Only \$649**

Q 0175 Cro Probes to Suit **\$39.95** Each

## Polypropylene Speakers

These fantastic speakers are ideal replacement speakers or for your own speaker design. The lightweight plastic cones offer levels of performance above that of conventional cardboard cones. The cone is more rigid and does not "break-up" (flex) as much as its counterparts.

	Watts RMS	Watts Max	Normally	This Month
C 3055 6.5" Woofer/Midrange	30W	50W	\$29.95	\$22.50
C 3060 8" Woofer	60W	100W	\$59.95	\$44.95
C 3065 10" Woofer	60W	100W	\$79.95	\$59.95
C 3070 12" Woofer	100W	150W	\$99.00	\$73.95
C 3075 15" Woofer	120W	200W	\$139.95	\$104.95

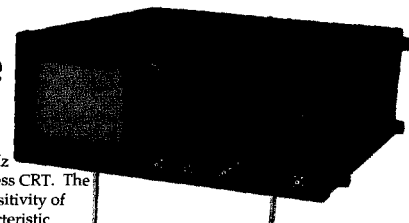

**Now With Component Test Function! Now Over 2000 in service throughout Australia including many 100's in Universities, Research Establishments and Industry**



**Save 25%**

Call Us on (09) 328 3487  
Microtonics for Full Specifications.


## High Performance 2 Way Flush Mount Ceiling Speaker System

Designed to be installed into ceilings or walls, this slim profile attractive speaker system/grill assembly will compliment any sound system. Installation is simplified by use of mounting frame (which could be installed during construction) which the speaker assembly attaches to. Full mounting kit supplied, including fixing screws. Employs a 165mm (6.5") latex covered driver and a high efficiency polymylar tweeter coupled with a high quality crossover. The grill and exposed surround can be painted to match existing decor.

**Specifications:** • Impedance: 8 Ohm • Power Input: 30W RMS • Frequency Response: 50Hz - 20kHz • Colour: Ivory White • Dimensions: ~306L x 220W x 86H mm

C 0884 Normally **\$250 Per Pair**,

**This Month Only \$199 Per Pair**

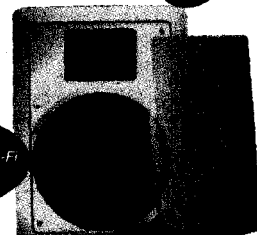

**Save Over \$50 a Pair**

Ideal for Home Theater Surround Sound or Hi-Fi Extension Speakers!

## True RMS Digital Multimeter with RS-232

Supplied with high quality hard carry case and silicon test leads. This 3.75 digit 4000 count digital multimeter would have to be one of the best meters we have seen. Features include menu driven functions (no complicated instructions to remember), large backlit display, timer function, 20 amp current scale and many more. Other Features: • RS-232 Mode • True RMS mode • Large display includes main and sub displays with bargraph • 10 Location memory • Stop watch/pre-settable count down timer • Minimum, maximum, average and relative modes • Double measurement • Capacitance and inductance measurement • Temperature mode (C and F) • Pulse signal generator for logic and audible testing etc. • Continuity and diode test • Logic test • Auto power "off" and "keep on" mode • 20A current range • Warning buzzer sounds when leads are incorrectly inserted in the 20A current mode • Back lit display • Data hold and run mode • Low battery indication • Overload protection • Safety design in compliance with UL 1244 and VDE 0411


### Specifications & Ranges Available:

DC Volt: .....300mV, 4V, 40V, 400V, 1000V  
AC Volt: .....4V, 40V, 400V, 750V  
DC Current: .....400µA, 400mA, 20A  
AC Current: .....400µA, 400mA, 20A  
Frequency: .....10kHz, 100kHz, 1MHz, 10MHz  
Resistance: 400Ω, 4kΩ, 40kΩ, 400kΩ, 4MΩ, 40MΩ  
Capacitance: .....100µF  
Inductance: .....100H  
Temperature: .....17 - 1093 C (0 - 2000 F)  
Display: .....3.75 digit, 4000 count LCD

Q 1098 **\$299**

Q 1092 K Type Temperature Probe to Suit \$22.00

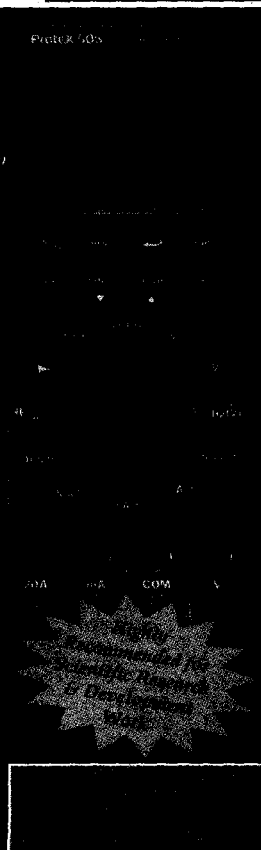Q 1093 Protective Carry Hoister to Suit \$13.50



These Timers Are Made by the Same Manufacturer as Those Sold by Major Hardware Stores & Supermarkets!

**This Month Save 30%**



**ALTRONICS Fax Order Line: (09) 328 3487**

**1-800 999 007**

**PERTH (09) 328 1599**

# ALTRONICS COMPONENTS


ALTRONICS Fax Order Line: (09) 328 3487

## Multi-Function Remote Car Alarm

S 5205 **\$199**

This amazing model features just about everything you could imagine. Multi-function key ring remote control will arm and disarm alarm (and activate central locking if fitted), panic and even open the boot (if actuator fitted). Other features include starter inhibitor, valet mode, central locking interface, flashes car indicators when tripped, auto reset, user programmable options plus much more. Also includes two spare electric outputs which are operated by the key ring remote control, these can be used to chirp the horn, turn on the car headlights or a myriad of other functions! Can be configured to automatically re-arm if a door is not opened within 22 seconds after disarming (avoids accidental disarming). Full battery backup siren includes built-in batteries, charging circuit, siren and key on/off switch.

**Features:** • Supplied complete with two miniature remote controls • Remote arming and disarming • Super Loud 127dB siren • Remote panic function • Full battery backup and tamper proof siren • Child proofing and anti intrusion alert while driving • User selectable exit delay and automatic re-arming • User selectable arming/disarming chirp • User selectable auto arming • Starter disable • Valet mode can be activated by remote or glove box switch • Automatic shunt of any defective entry zone • Turns on interior lights for 20 seconds when alarm is disarmed • Alarm memory indicates which zone (1-3) triggered • 60 second siren with auto reset • Two colour LED status indicator • Can be interfaced with central locking (where fitted) • 3 extra channels on remote to control other vehicle features such as boot release, etc.

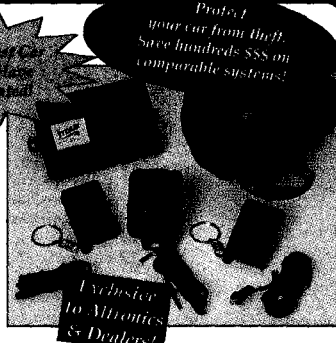

**Protect your car from theft. Save hundreds \$\$\$ on comparable systems!**

**Exhibitor to Altronics & Dealers!**


## 14,400bps Internal Fax/Modem with Internet Access Software

Connect to the information super-highway on the Internet and explore the world!

Using the latest in digital signal processing, this internal fax/modem will give you years of service. Supplied with WinFax Lite for Windows, and DosFax Lite for DOS, this software will let you send/receive faxes direct from your PC. Features 5 year warranty. Austel approved.

\* Service charges apply.

D 1650 **\$199**

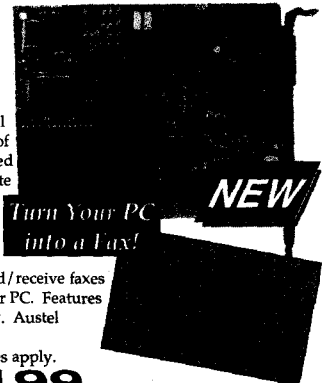

Turn Your PC into a Fax!

**NEW**

**Protect Your Home This Summer. Thieves Don't Take Holidays!**

**Amazing Bonus Package**  
Over \$100 Value of Installation Accessories Including Cable, Strobe & Siren Free with Each Alarm System Purchase!

**WARNING**  
ALTRONICS SURVEILLANCE ALARM SYSTEM FITTED HERE

## ALTRONICS

**Standard Delivery & Packing Charge:** \$4.00 to 500gms, \$5.50 500gms-1 kg, \$8.00 1kg-5kg. Where possible we process your order the day received and despatch via Australia Post. Allow approx 9 days from day you post order to when you receive goods.

**Overnight Jet-service:** Up to 3kg is \$9.50, 3kg to 5kg is \$18.00—We will process your order the day received (if placed before 2.00PM WST) and despatched for delivery the next day. Country areas please allow an additional 24-48 hours.



**Heavy Service:** All orders of 10kgs or more must travel Express Road—Please allow up to 7 days for delivery. \$12.00 to 10kgs. \$15.00 over 10kgs. **Insurance:** As with virtually every other Australian

supplier, we send goods at consignee's risk. Should you require insurance cover against loss or damage please add \$1.00 per \$100 of order value (minimum charge \$1). When phone ordering please request "Insurance". Altronics Resellers: Chances are there is an Altronics Reseller right near you—check this list or phone us for details of the nearest dealer. Blue Ribbon Dealers are highlighted with a ●. These dealers generally carry a comprehensive range of Altronics products and kits or will order any required item for you.

### WA - COUNTRY

<b>ALBANY</b>	BP Electronics ● (098) 412681	Micro Electronics (098) 412077
<b>BUNBURY</b>	Micro Electronics (097) 216222	Marks Music (097) 523522
<b>BUSSELTON</b>	Esperance Comm. (090) 713344	Golden Mile Electronics (090) 215212
<b>ESPERANCE</b>	Ivan Tomek Electronics (091) 732531	TV Joe's (09) 5271806
<b>KALGOORLIE</b>	All Electronic Comp. (03) 96623506	TECS ● (03) 96706474
<b>PORT HEDLAND</b>	Talking Electronics (03) 95842386	TECS ● (03) 95629501
<b>ROCKINGHAM</b>	Truscott Electronics ● (03) 97233860	G.B. Telespares (03) 93266035
<b>VIC - CITY</b>	Preston Electronics ● (03) 94840191	

### COUNTRY

<b>BALLARAT</b>	Ballarat Electronics (053) 311947
<b>BENDIGO</b>	Sumner Electronics (054) 431977
<b>MILDURA</b>	Truscott Electronics ● (050) 238138
<b>SHEPPARTON</b>	Andrew Guyatt Elect. (058) 219497
<b>QLD - CITY</b>	
<b>NEWSTEAD</b>	Delsound PL ● (07) 38396155
<b>WEST END</b>	E.C.Q. (07) 32541153
<b>WOODRIDGE</b>	B.A.S. Audiophonics (07) 38447566
<b>COUNTRY</b>	David Hall Elect. ● (07) 38082777
<b>GLADSTONE</b>	Gladstone Elect. Services (079) 724459
<b>MAROOCHYDORE</b>	Mals Electronics ● (074) 436119
<b>TOWNSVILLE</b>	Super Solex ● (077) 724466
<b>TAS</b>	
<b>HOBART</b>	G.H.E. Electronics ● (002) 342233
<b>LAUNCESTON</b>	G.H.E. Electronics ● (003) 316533

### NT ALICE SPRINGS KATHERINE SA - CITY

<b>BRIGHTON</b>	Farmer Electronics (089) 522388
<b>COL LIGHT GDNS</b>	Logicware (089) 723030
<b>ENFIELD</b>	Aztronics ● (08) 2126212
<b>FINDON</b>	Force Electronics ● (08) 2125505
<b>HOLDEN HILL</b>	Force Electronics ● (08) 3770512
<b>KENSINGTON PK</b>	Force Electronics ● (08) 3743346
<b>LONGDALE</b>	Aztronics ● (08) 3496340
<b>SALISBURY</b>	Force Electronics ● (08) 3471188
<b>NSW - CITY</b>	Force Electronics ● (08) 2617088
<b>SMITHFIELD</b>	Force Electronics ● (08) 3322299
<b>COUNTRY</b>	Force Electronics ● (08) 3260901
<b>COFFS HARBOUR</b>	Force Electronics ● (08) 2830755
<b>NEWCASTLE</b>	David Reid Elect. ● (02) 2671385
<b>WOLLONGONG</b>	Chantronics (02) 6097218
<b>WOLLONGONG</b>	Coffs Harbour Elect. (066) 525684
	Novocastrian Elect. Supplies (049) 621358
	Vilec Distributors (049) 566792
	Newtek Electronics ● (042) 271620
	Vimcom Electronics (042) 284400

**1-800 999 007 PERTH (09) 328 1599**



# SHORTWAVE LISTENING

with Arthur Cushen, MBE

## Indonesia Radio's checkered history

Indonesia, with its population of 200 million, has many hundreds of radio stations. But when we look back at the history of broadcasting, we find that it was originally a Dutch colony, and the Dutch were the pioneers of radio in what was then the Dutch East Indies.

A company known as NIROM: Netherland Indies Broadcasting Company Ltd, was founded in the late 1930's and operated several stations in Batavia, Bandoeng and Surabaya. However the true pioneers were perhaps the various wireless societies set up by radio amateurs to broadcast to the local population. These were heard up to the Japanese occupation in 1942.

By June 1942, the Japanese had overrun the former Dutch East Indies and taken control of radio services. We then began to hear new voices on the band. Later Radio Batavia started to use the higher frequency bands and commenced broadcasts in English — full of propaganda with the Japanese war news, lists of prisoners of war and civilian internees. They also had a special lunchtime broadcast to Australia and New Zealand from Batavia, using 18,135kHz for this transmission at 0130GMT.

By 1946 two broadcasting systems were in operation: Radio Batavia, operated by the Dutch in Batavia and the Voice of Free Indonesia in Jogjakarta under the control of the emerging Indonesian Government. The latter was the founding of Radio Republik Indonesia.

The conflict dragged on, as a transfer of power from the Dutch to a new Indonesian Government was in discussion in 1947 and this took place in 1949 under Sukarno. In 1966, further radio activity was noted, with a student radio on the air and Radio Andir was heard.

According to a Radio Nederland programme looking at radio in Indonesia, there are now 647 private broadcasting stations as well as the network of the Radio Republik Indonesian RRI stations spread throughout Indonesia. All stations relay the news on the hour from Jakarta, and this is familiar to shortwave listeners for the preceding 'Song of the Coconut Island' before the news.

Reception of the Indonesian External Service with its high powered transmitters is noted with sign-on at 2300UTC on 9525 and 9680kHz and these frequencies are still in use at 1100UTC. Many RRI stations can also be received on the lower frequency bands with Tanjung, Karanga on 3395kHz and Jakarta on 4777kHz being well received around 1300UTC.

### Media Network Milestone

This month Radio Nederland's Media Network programme will celebrate 30 years of my contribution to it — which when I first broadcast in January 1966, was called DX Jukebox. In those days it was a programme of some shortwave listener news and the hits of the moment, and was compered by Harry

Van Gelder. The programme started in 1959 and it was designed to also help people build receivers and give more technical information, realising the difficulties of shortwave listeners worldwide in obtaining that type of information.

In 1966 in the broadcast on the first Thursday of the month, my contribution was carried. At that time, there were three other correspondents coming from South Africa, Holland and Sweden. In those days my broadcasts were recorded at Radio New Zealand studios in Invercargill, along with my programme for our own shortwave service which started in 1960. The two programmes were put together at the one sitting, using, of course, a braille script.

The Radio Nederland programme was recorded two weeks in advance as it was airmailed to the Hilversum studios, then put together and broadcast. In 1968, when the relay station in Bonaire was opened it was recorded a month in advance so that the material could be sent to Hilversum, the programme put together and airmailed down to the transmitter at Bonaire.

Harry Van Gelder carried the session into the 1970's and following his retirement there were several other comperes. Jonathan Marks joined the staff of Radio Nederland in 1980 and later the programme was re-titled Media Network, and in recent years, it has been voted the most popular communications programme on shortwave. Radio Nederland then pioneered the use of the telephone for reports and for the past few years, my contribution has been telephoned on a Tuesday morning to Hilversum for broadcast on a Thursday evening.

Media Network has now evolved into a communication type feature and there are only two overseas correspondents with regular input, Victor Goonetilleke and myself. The two sessions for reception in the South Pacific are at 0752UTC on 9720 and 11,895kHz; and 0952 and 7260, 9720 and 9810kHz. ♦

## AROUND THE WORLD

**BANGLADESH:** Radio Bangladesh signs on in English at 1229UTC, with news broadcast at 1230 on 7185kHz.

**BULGARIA:** Sofia has been well received in English at 0500 - 0600UTC on 7480kHz and 9700. Both frequencies have been heard in the South Pacific.

**GERMANY:** Deutsche Welle transmits in English to Oceania at 0900 - 0950 on 6160kHz, 7380, 11,715, 17,780, 17,820 and 21,680kHz; 2100 - 2150 on 6185kHz, 9670, 9765 and 11,785kHz.

**NETHERLANDS:** Radio Nederland has English to the Pacific at 0730 - 0825 on 9720kHz and 11,895kHz; 0830 - 0925 on 9720kHz and 13,700kHz; 0930 - 1025 on 9720kHz, 7250 and 9810kHz; and 1030 - 1125 on 7250kHz and 9810kHz. The broadcasts on 9720kHz and 11,895kHz originate from Bonaire. All other transmissions are from the Commonwealth of Independent States.

Radio Nederland is using a transmitter in Russia for a broadcast in English noted at 1830 to 2030, on 4945kHz. Reception has been very good during this period and the transmission is beamed to Central and South Africa.

**PALAU:** KHBN, The Voice of Hope, 9965kHz after testing has been heard with an extended schedule, and English at 0730, Chinese at 0800

and still operating at 1800UTC. The station has two other frequencies, 9730kHz and 9985kHz, listed for use by new transmitters.

**PHILIPPINES:** FEBC, Manila has been heard on 11,635kHz opening at 0930 with news and feature programmes at 0940UTC. The address for reception reports is PO Box 1, Valenzuela 0560, Metro Manila, Philippines.

**SAIPAN:** KHBI, Christian Science to the South Pacific broadcasts from 0800 - 1000 on 13,615kHz; 1000 - 1100 on 13,625; 1100 - 1200 on 9425; 1200 - 1300 on 13,625; 1800 - 1900 on 9355; 2100 - 2200 on 13,840; and 2300 - 2400 on 13,625kHz.

**SWEDEN:** Stockholm broadcasts in English to Australia 1230 - 1300 on 9835kHz, 13,740 and 15,240kHz. Also heard 0130 - 0200 on 7120kHz to this area.

**TURKEY:** The Voice of Turkey has English broadcasts 0400 - 0500 on 7190kHz, 9560 and 9685kHz. The station uses five new 500kW transmitters for the Voice of Turkey broadcasts.

**USA:** WGTC, PO Box 1131, Copperhill, Tenn, 37517, USA heard on 9475 at 0400UTC with English and Spanish announcements. Signals are still heard at 0500 but at 0600 the station is blocked by HCJB. This is a new 50kW gospel station. ♦

*This item was contributed by Arthur Cushen, 212 Earn Street, Invercargill, New Zealand who would be pleased to supply additional information on medium and shortwave listening. All times are quoted in UTC (GMT) which is 11 hours behind Australian Eastern Daylight Time and 13 hours behind New Zealand Daylight Time. ♦*



# INFORMATION CENTRE

by PETER PHILLIPS

## Windows 95, new lifeforms and 'synchros'...

I'm devoting the column this month to two unrelated topics: computers and synchros. We haven't described synchros here at all before, and we've never devoted much of the column to computers and the problems people have with them. So I trust you'll find both topics interesting, even if you are not 'into' either. Incidentally, I'm out of What?? questions again. Can anyone help please?

You might not have seen a recent and rather remarkable SBS program in a series called the 'Seven Wonders of the World', which featured a man who was (I think) the director of a US company involved in the development of artificial thought. He talked about his work, about computers and the future, and threw in some quite profound beliefs.

Perhaps the most profound was his view that man and computer were destined to combine into a new, much higher order being — which would place today's man at about the relationship monkeys presently are to us. This new being, according to the program, would be God.

The segment featuring this man lasted about 10 minutes, and he went on to say that future computers and the supporting technology would be so sophisticated that no one person would be able to understand it. He further suggested that eventually parts of future computing systems (the computer itself perhaps) would be just a black box that no one would need to understand, like knowing why two plus two equals four.

It's hard to dismiss these opinions when you consider that computers are evolving at an ever increasing-rate and, unlike any previous technology, computers help in their own evolution. Furthermore, in the last few years we have seen millions of computers join together all over the world through a communications system (the Internet and so on) that is expanding as fast as the need arises. It only takes the right software to make these computers interact, perhaps like a large electronic brain.

Now consider the way computers have developed. Babbage is generally accredited with inventing the concept of the computer in 1831, and Boole in 1854 pioneered a new way of thinking, called

digital logic. In the late 1940s the first generation of electronic computers appeared, followed some 10 years later by second generation, all solid state computers. Third generation computers were developed in the '60s, but until the '70s these computers were mainly the tools of large industry and government, because of their expense.

Then came the microprocessor during the '70s, followed by 8-bit personal

and in keeping with our computer theme for this month, we'll move to a discussion about the most publicised software ever written.


## Windows 95

As an electronics magazine, we would be remiss if we failed to keep you abreast of the major happenings in the computer world. One of the more recent happenings is Windows 95, described by some as Microsoft's answer to the graphical interface of the Apple Macintosh.

The story I'm going to relate about Windows 95 is not a reassuring one, but one that does have a happy ending. I'm describing it because it might give you some answers if you have problems installing Windows 95. It goes like this...

Last August, I described a computer crash I experienced at the time. Although traumatic, I learnt a lesson from the experience, including how important my computer is to me, and the need for backups. So when I decided to install Windows 95, I had tape backups of everything, and I'd even installed another hard disk, especially for the new program. This disk had no other software on it, and offered 'virgin territory' for Win 95.

Because of conflicting reports, I opted for a dual system, with Windows 3.1 on my old drive and the new system on the new drive. I installed from a CD ROM, choosing a custom installation and responding to the various questions during the installation. And after about 20 minutes, there it was — Windows 95. I was pleased that the installation had gone thus far with no problems, so I spent the next half an hour looking around the all-new graphical interface, that somehow reminded me of how my

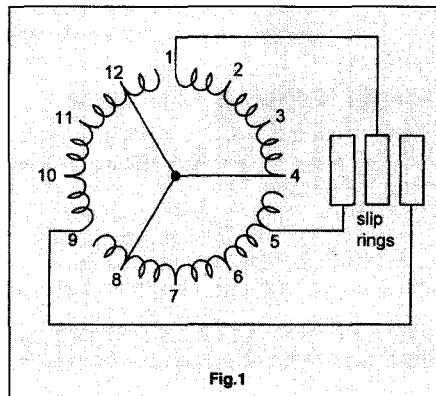

computers towards the end of the '70s. In other words, it took from 1831 to the late 1970s to get computers into our homes. Now ponder the developments that have occurred with computers since say 1980 to 1996, a period of 16 years.

Even if the rate of change of computer development stays constant, where will computers have taken us in another 16 years? But given that the rate of change of computer development is itself increasing, then it seems we can look forward to huge technological improvements in half this time. So by 2020 or so, who knows where we will be. Perhaps the predicted computer-human creation will be a reality, with consequences we can only wonder at...

I'll leave you to think over that one,

Apple IIGS (remember the IIGS?) looked in 1986.

I was soon to discover, however, that all was not as it should be. According to others, the program should have read my old WIN.INI file during installation and set itself up to run at least some of my existing Windows-based programs. I fiddled about for a while, finally concluding that I would need to re-install my programs to make them run under Win 95.

As this month's deadline was fast approaching, I decided to leave Windows 95 alone, and return to Windows 3.1. I then found to my horror that although Windows 3.1 ran — albeit very slowly — very few of my programs would now run under it, giving the message 'not enough memory'. I won't go into all the details; suffice it to say that my computer was now dysfunctional in a big way!

The first and most obvious thing was to use the 'uninstall' facility of Windows 95. Unfortunately, for some reason it had not made the necessary files to allow this, despite having made (at my request) a boot disk. I'm sure nothing I had done had prevented it making the required uninstall files.

I then tried finding what Windows 95 had done to my system. It seems the program is very intrusive, and gets into almost everything, even DOS. A few phone calls to other users confirmed that the simplest way out of the mess was to restore my hard disk from the tape backups.

So, after several more hours of restoring from tape, I felt confident all would be well. But no! In fact, things were now worse than before, as Windows 3.1 would not even boot. Instead the computer would hang, halfway during loading.

As you can imagine, I couldn't understand why my system wasn't working. I had even reformatted my drive to get rid of any possible remainders of Windows 95. It threw into doubt the whole principle of making backups.

I'll spare you my feelings and instead give you the happy ending, which came from Robert Priestly, a regular contributor to the magazine. Robert has had a lot of experience getting people out of trouble following a Windows 95 installation,

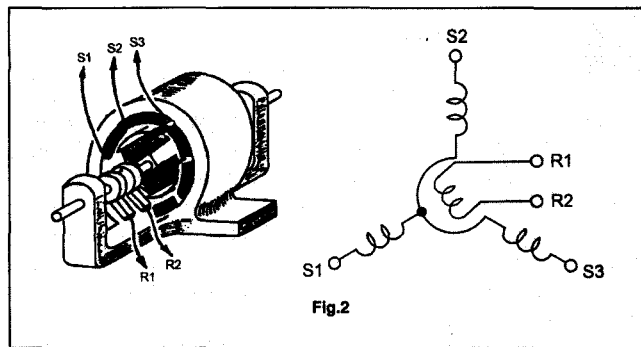


Fig. 2

and believes the best way is to start with a totally new computer system.

All I had to do was boot from a floppy, go to the C: prompt, and enter the command fdisk<space>/MBR (rewrite the master boot record). I had to do this twice and thereafter all was well. It seems the master boot record on my C drive had been altered (I have to assume by Windows 95), and this was stopping everything from working.

It's possible you've never heard of this DOS command, or even used it. But there it is, and one worth knowing. Incidentally, Robert and all the other people I spoke to agree that Windows 95 is excellent, but I guess it will be some time before I try it again.

### And OS/2...

While we're on the subject of GUIs and computers, here's a letter from a reader who read my comments on the IBM Aptiva in November.

*I read with interest about your adventure with the IBM Aptiva. A couple of years ago a friend and I decided (independently) to try out OS/2 — he got the full system and I chose OS/2 for Windows (claimed at the time to run Windows better than Windows itself).*

*Mine never did get installed, as it continually gave up at I think disk 5, out of a total of 20 3.5" disks. Although I could have had the disks replaced, I decided not to continue with the idea. So I was faced with removing what had been installed. That was when my troubles*

*started, as some of the files were hidden and when found, refused to allow the attributes to be changed to delete them. And while they were there, all I could get was the maddening OS/2 logo.*

*My friend meanwhile completed his installation, but decided that OS/2 was not his cup of tea, and had similar experiences trying to remove the last of the files.*

*In the end we both had to re-partition and re-format our hard disks, and in my case I'm sure OS/2 had written to the scratch area of the CMOS BIOS to pre-empt some of the services to itself. I removed the on-board battery briefly, and then had to re-enter all the usual BIOS information. Finally I had to re-install ALL my programs from scratch.*

*Incidentally, you describe the Aptiva as 'incompatible'. Can an IBM computer be other than compatible? I'm sure IBM would hold the view that since they engineered the original PC architecture, AND wrote the original code for the CMOS BIOS, they have a right to consider all 'clones' as interlopers, and completely incompatible with the IBM ethic. (Even if they use a BIOS licensed by IBM!)*

*Perhaps we should all say a prayer of thanks for Bill Gates? And hooray for Windows! (Bob Abel, Condobolin, NSW)*

I know the feeling about having to start all over again, Bob, and I'm sure there's quite a few readers empathically nodding. You're right about it being unfair to call the IBM Aptiva incompatible, but it's certainly different from the so-called IBM compatibles. But as it happens there's more to say about this unfortunate computer, although it's probably nothing to do with it being an Aptiva.

### Disk drive problem

Not long after I wrote about the Aptiva, its owner accidentally introduced a virus into it — called EXEBUG, I think. This virus could not be removed by the McAfee software recommended by the IBM help desk, so my friend decided to ask a computer-literate work colleague to help. This person was familiar with OS/2 and he was able to painlessly remove the virus, and OS/2 with it.

But later another problem

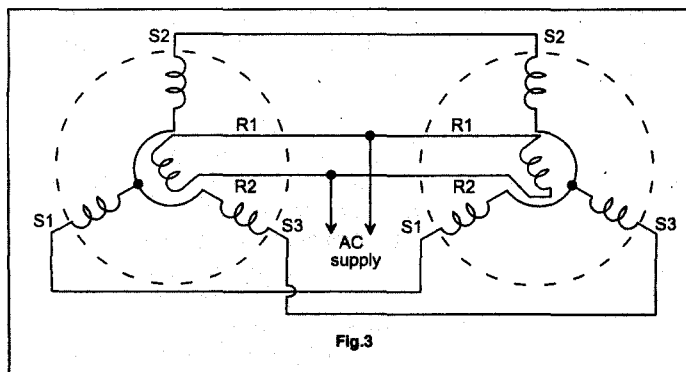


Fig. 3

emerged. For unknown reasons, the single 3.5" floppy drive in the Aptiva now won't read the directory of anything other than the first disk it reads after power-up. That is, replacing the first disk with another gives a display of the same directory as the first. Trying to install software that comes on more than one disk is therefore impossible.

The solution? Who knows! At the time of writing, it seems all that can be done is to restore the Aptiva back to how it was shipped, so the IBM help desk can figure it out. This means my friend will get OS/2 back again, along with losing everything he has installed. Is it the remains of the virus, the complexity of OS/2 and the Aptiva causing the problem, or the well known gremlin? I'll keep you posted.

## GPO problem

The next letter is computer related in a rather strange way. I'll let you read the letter first, then I'll make a few comments.

First, congratulations to EA for the great BBS you have set up. You may be interested in a strange problem I am having, and maybe a reader can help me with a solution.

The story needs a bit of background. I use quite a lot of computers, and also repair many for other people. This is the main way I earn my living, and it's all done at home. I usually have two or three computers set up at a time, doing a burn-in.

I therefore have a room set aside for this, and when the house was built this room was fitted with three double power points (GPOs), along with a telephone line (for a modem). The problem, which you may not believe possible, is with one of the power points.

With modern computers the power supply has a mains input which is connected to a GPO, and a fused mains output for a monitor. This allows a single switch to operate both the computer and the monitor.

So what's wrong? With one particular power point, when I turn the computer's power switch on the monitor comes on, but the computer doesn't! About three seconds later the LED display on the front of the computer flashes. However if I turn the computer on then off, wait for the flash, and turn it on when the display flashes, the system will come up

beautifully!

One computer I was using on this power point had this problem on other GPOs as well, but after replacing its power supply it was fine on all other GPOs except the one in question.

I have used three computers (and four different computer power supplies) on this power point and each one has the same problem. The solution is fairly simple — run an extension lead from another GPO.

It seems strange that a GPO would sort of (?) work, is fine for using transformer type power supplies, but not switch mode designs. Any suggestions? (Conrad Smith, Berowra NSW.)

Thanks for your letter, Conrad, which came to me via the BBS. Anyone who likes to send their letters this way is most welcome.

I suggest you check the wiring to the offending GPO. It might be that the earth and neutral wires are reversed. This will usually make the GPO appear to work properly, but is really quite dan-

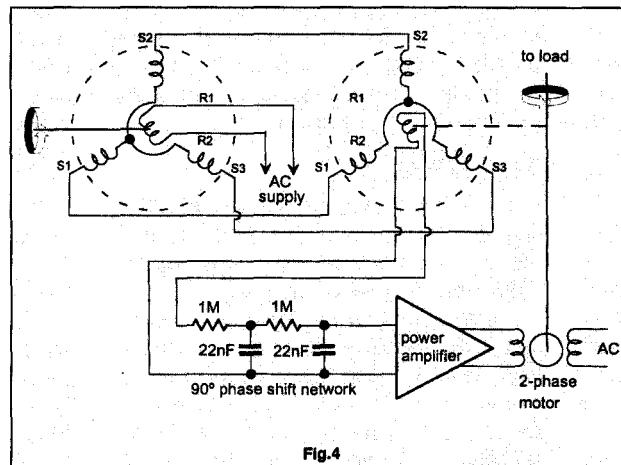


Fig.4

gerous. I have no idea if this could cause the symptoms you describe, but I'm starting to give up on computer related problems. Other than that, I can only throw the question over to our readers.

And now, I'm want to take you back to April 1964, when computers were almost unheard of, a hifi system cost around \$400 and synchros were readily available through disposal stores.

## Synchros

In October '95, I included a letter from a reader wanting a system that would allow the position of a remotely mounted weather vane to be indicated by a pointer on a compass face. He did not want a digital solution, just a simple analog method. I proposed a pair of synchros (also known as selsyns), but admitted to being hazy about these almost forgotten but simple devices.

Since then I've received a number of letters about them, and I have also found an article on the subject written by Jim Rowe in the April 1964 edition of this magazine (then called Radio & Hobbies). I'll present two letters first, as they both offer practical suggestions, then refer to Jim's article to give you a precis of how synchros work:

Your inclusion of a letter from G. Kinnear in October's Information Centre reminded me that I've been collecting material for some years on the very devices you recommend as a solution to Mr Kinnear's problem. Unfortunately, suitable units may be hard to find or even recognise.

The terms magflip, selsyn and synchro all refer to the same device, and yes, they do work over 360°. However while these devices have a three phase stator, they don't need an external three phase supply.

The way they work is quite elegant. The transmitter and receiver have a similar construction, and many were made

in a standard housing of about 50mm diameter. Each unit has a three phase stationary winding and a two pole rotor.

When the rotors of both units are energised with the same AC supply, the induced voltage in the stator of the transmitter will cause currents to flow in the stator of the receiver. The rotor in the receiver will then align itself to agree with the position of the rotor in the transmitter.

So all we need are two synchros, a low voltage AC supply for the rotors, and five wires between the two units. A typical supply voltage is 30 to 50V AC,

but the units I have are so nicely made they work at a much lower voltage. Old military units may have been designed for a 400Hz supply. The ARRL Antenna Handbook of a few years ago has useful information about how to get by with just four wires and a simple 400Hz supply.

The difficult part is finding a pair of suitable units. To my knowledge, they were used in meteorological instruments and radar heads. However suitable equipment may be closer at hand, in the form of a car alternator. Perhaps your magazine has the resources to try my idea.

First get a pair of alternators and remove the diode packs. Next connect the two stator networks together and apply a low voltage AC to the (paralleled) rotors. I think you'll find that moving the rotor of one causes the rotor

of the other to move in an identical way.

My fear is that as the rotor has more than two poles, the two units will have more than one lock position. Maybe the extra pole pieces could be cut off with an angle grinder. Also the stator windings might have a field pattern differing from those of a standard synchro. (John Hill, Wellington, NZ.)

Thanks for your comments John, and in particular for suggesting a car alternator as a synchro. It's certainly worth a try, if you happen to have two (I assume identical) car alternators and a suitable AC supply.

Here's a few lines from another reader, who opens his letter in a rather unique way...

*Damn you, you have disturbed my brain. I have had to resurrect KNOWLEDGE buried for at least 18 years and up to 50 years.*

*I suggest that any pair of universal motors can be modified to operate as repeater motors. These are in many household appliances like vacuum cleaners and blenders. Other possible sources are 12V car fans and windscreen wiper motors like those in Volkswagens.*

*The number of coils is not important provided the same coil segments are connected to each other. Only three segments need to be used as take-off points as shown in Fig.1. The idea is:*

*Open circuit the armature winding at three points and join segments 4, 8 and 12 (or equivalents on your motor). Fit slip rings to the shaft and connect segments 1, 5 and 9 (or equivalent). Do this with two motors and you have two synchros. (L.M. Cross, Newtown NSW.)*

I think you've left out one step, Mr Cross: the field coils. In your idea, it seems the three phase stator normally found in a synchro is now the rotor, so the two pole rotor of a normal synchro must now be replaced with a two pole stator in your 'inverted' design. Most universal motors have a two pole stator anyway, so the design is complete.

My only other comment concerns the suggested Volkswagen windscreen wiper motor. As these usually have a permanent magnet field, it could not be used in this application.

Now let's look at what Jim Rowe had to say about synchros in 1964, when they were in much wider use:


## About synchros

First is the name. Selsyn is a trade name from General Electric Company, and other names like Autosyn and mag slip seemed to also be proprietary terms. The most general term is synchro,

which I'll use here.

A basic synchro and its internal circuit is shown in Fig.2. The sketch of the synchro (from the April '64 article) is illustrative only, and commercial units look much more elegant. In a typical system, one synchro is called the transmitter and the other the receiver. It seems there is little difference between these and they can be used in either role.

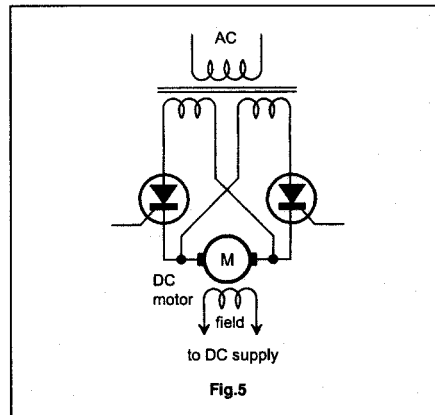If two such devices are connected as in Fig.3, turning the rotor of either



machine will cause the rotor of the other to align itself to agree exactly with the first. However there is no power gain, so this simple system is only useful for low torque applications, such as that required by Mr Kinnear.

An arrangement that gives power gain is in Fig.4. As before, the stator windings of both synchros are joined, but the rotor winding of the receiver is now fed to a 90° phase shift network, which connects to a power amplifier. This amplifier feeds one winding of a two-phase AC motor, the other fed from an AC supply.

The receiver's rotor is mechanically coupled to the load, so it's turned with the load by the extra motor. When the position of this rotor agrees with that of the transmitter, there is no error voltage and the system is stable.

An interesting point is that a DC motor can be used as the load turning motor, as in Fig.5. The amplifier circuit shown is an adaptation of the original, which uses thyratrons (a gas-filled valve, rather like an SCR).

The trigger pulses to the SCRs are 180° out of phase, from a previous amplifying stage. The field winding of the DC motor is supplied by an external DC supply, perhaps from another winding on the transformer, via a rectifier bridge.

Jim's article goes on to say that synchros make an excellent alternator, perhaps to produce a signal source, or even a small amount of power. This gives

support to John's suggestion of using an alternator as a synchro.

There's much more, including a description of differential synchros. I'll leave it there however, as this brief summary covers the main points of the article. Reprints of the full article are available through our Reader Service if you want more information.

## What??

Here's a non-mathematical question. It comes from Bryan Maher, a regular contributor to our What?? segment. Bryan writes:

Electrons can exhibit positive or negative mass. In contrast, most physical objects like golf balls, people and cars have a positive mass, which means their inertia resists acceleration. Such objects tend to hold back when pushed. But if something has a negative mass, it would react to acceleration by instantly moving quickly ahead when pushed. The question is, what large size mechanical object that we are all familiar with exhibits an apparent negative mass?

## Answer to December's What??

The answer is 75km. The mathematical solution is: on the first flight, the bird flies 50 x 60/80km, the trains go 50 x 20/80 km = 12.5km, and the trains are now 50 x (2 x 12.5) = 25km apart. For the second flight, the bird flies 25 x 60/80km, the trains go 25 x 20/80 = 6.25km and the trains are now 25 - (2 x 6.25) = 12.5km apart. For the third flight, the bird flies 12.5 x 60/80km, the trains go 12.5 x 20/80km = 3.125km and the trains are now 12.5 - (2 x 3.125) = 6.25km apart. For the fourth flight the bird flies 6.25 x 60/80km.

The total distance covered by the bird in four flights is:  $D(4) = (50 \times 60/80) + (25 \times 60/80) + (12.5 \times 60/80) + (6.25 \times 60/80)$ . This equals  $(50 \times 60/80)(1 + 0.5 + 0.25 + 0.125)$ km. The second set of brackets contains a geometric series, and the formula for the sum of the first n terms is:

$S(n) = a(1 - r^n)/(1 - r)$ , where a is the first term, in this case 1, and r is the common ratio, in this case 0.5. For an infinite series, n is infinity, so as  $a = 1$  and  $0.5$  raised to infinity = 0, the formula reduces to  $S(\text{infinity}) = 1/(1 - 0.5) = 2$ . So, the total distance flown by the bird is  $D(\text{infinity}) = (50 \times 60 \times 2)/80 = 75$ km.

A more lateral way to approach the problem is: each train has moved 25km when they meet. At 20km/h this takes 1.25 hours. The bird flying at 60km/h for 1.25 hours travels 75km. ♦

# INDEX FOR VOLUME 57

January 1995 to December 1995

## AUTOMOTIVE ELECTRONICS

An Australian designed and built engine management system: Injec's EMI	Jan	p 48
Emona's EM-606 handheld engine analyser	Mar	p 89
Using a scope for vehicle faultfinding — 1	Apr	p 93
Using a scope for vehicle faultfinding — 2	Jun	p 20
Using a scope for vehicle faultfinding — 3	Jul	p 95
Vetronix's Mastertech analyser	Aug	p 44
OTC's 'Vision' diagnostic tool	Sept	p 94
The ABS braking system and how it works	Oct	p 30
Catalysers, lean burn and the oxygen sensor	Dec	p 14

## BOOK REVIEWS

Complete Guide to Troubleshooting & Repairing Consumer Electronics Without a Schematic	Jan	p 29
Circuit Designer's Companion	Jan	p 29
McGraw-Hill Circuit Encyclopedia & Troubleshooting Guide	Jan	p 29
Electronics Theory and Practice	Feb	p 93
Inside Spice: Overcoming the Obstacles of Circuit Simulation	Feb	p 93
Crystal Sets 'N Such	Feb	p 93
Simplified Design of Linear Power Supplies	Mar	p 35
Electric Motors and Control Techniques	Mar	p 35
Radio Receiver Projects You Can Build	Mar	p 35
Official Hayes Modem Communications Companion	Apr	p 24
Audio Recording & Reproduction	Apr	p 24
Understanding and Servicing CD Players	Apr	p 24
Automotive Electronics Handbook	May	p 16
Passport to World Band Radio 1994	May	p 16
Comprehensive Radio Valve Guide	May	p 16
TV Faults & Video Faults	Jun	p 82
Advanced Microprocessors	Jun	p 82
Simplified Design of Switching Power Supplies	Jul	p 16
The Alarm, Sensor & Security Circuit Cookbook	Jul	p 16
Test Equipment	Jul	p 16
The Novice Operators Theory Handbook	Aug	p 18
Amplifiers, Waveform Generators & Other Low Cost Projects	Aug	p 18
Digital Logic Design	Aug	p 18
The Cellular Radio Handbook	Sept	p 45

Auto Audio: Choosing, Installing & Maintaining Car Stereo Systems	Sept	p 45
The Tube Preamp Cookbook	Sept	p 45
Interactive Television: A Comprehensive Guide for Multimedia Technologists	Oct	p 18
Build Your Own Low Cost Data Acquisition & Display Devices	Oct	p 18
The Story of the Key	Oct	p 18
The Benchtop Electronics Reference Manual	Nov	p 18
Modern TTL Circuits Manual	Nov	p 18
Satellite and Cable TV	Nov	p 18
Electronic Instrument Handbook	Dec	p 18
Tuning in to RF Scanning	Dec	p 18
Audio & HiFi Handbook	Dec	p 18

## CIRCUIT & DESIGN IDEAS

Simple shed alarm	Jan	p 66
DVM milliohm adaptor	Jan	p 66
Energy auditor	Jan	p 67
Efficient linear power supply	Jan	p 67
Dual polarity supply	Feb	p 80
LED display driver	Feb	p 80
DTMF decoder	Feb	p 81
Piezo screamer	Feb	p 81
TRF radio	Feb	p 81
NiCad cell tester	Mar	p 56
Cable tester	Mar	p 56
Voltage and continuity tester for cars	Mar	p 57
Current limiting switch	Mar	p 57
Karaoke converter	Apr	p 56
Fridge cooler	Apr	p 56
In-circuit transistor tester	Apr	p 57
Light & sound trigger mods	Apr	p 57
Switch mode battery charger	May	p 50
Solar night light	May	p 51
First event indicator	May	p 51
Etching PCBs	May	p 51
Oil temperature indicator	Jun	p 50
Stable 100kHz source	Jun	p 51
Flashing beacon	Jun	p 51
Energy monitor	Jun	p 51
Wideband current feedback amplifier	Jul	p 50
Silent phone bell	Jul	p 50
Water purity tester	Jul	p 51
Falling bomb simulator	Jul	p 51
Energy saver	Aug	p 66
Brake fluid alarm	Aug	p 66
NiCad charger	Aug	p 67
Micropower LED flasher	Aug	p 67
Expanded scale meter	Sept	p 56
Variable timer	Sept	p 56
Fan speed controller	Sept	p 57
Solar panel booster	Sept	p 57
Phone ring indicator	Sept	p 57
Tap on connections	Oct	p 66
Engraving pen	Oct	p 66
Capacitance meter	Oct	p 67

Simple inductance meter	Oct	p 67
Simple computer interface	Nov	p 56
Inductive load controller	Nov	p 56
Multi-flash adaptor for cameras	Nov	p 57
24V-12V converter for trailers	Nov	p 57
Personal emergency alarm	Dec	p 56
Charging 12V NiCads from a 12V battery	Dec	p 57
Microwave HV diode tester	Dec	p 57
Reaction timer	Dec	p 57

## CONSTRUCTION PROJECTS

Stereo TV sound receiver	Jan	p 56
DSE Four sound siren generator	Jan	p 68
Dry cell & NiCad battery charger	Jan	p 70
Valve preamp for audiophiles - 2	Jan	p 80
Digital pulse generator using an EPLD - 2	Jan	p 92
Solid state audio recorder	Feb	p 56
DSE 10Hz - 100kHz function generator	Feb	p 64
Stereo TV sound receiver - 2	Feb	p 68
Automatic house number	Feb	p 82
PC-based serial protocol analyser	Feb	p 110
Mains appliance remote controller - 1	Mar	p 48
DSE Audio link using optical fibre	Mar	p 58
Calibrated RF detector probe	Mar	p 62
Putting the VMAC recorder to work	Mar	p 68
DSE 38-LED roulette wheel	Apr	p 48
Playmaster 300W subwoofer amp - 1	Apr	p 58
Minispot 2 AM/FM alignment source	Apr	p 68
Digital trigger adaptor for scopes	Apr	p 80
Smart door minder	May	p 56
Mains appliance controller - 2	May	p 60
Surround sound decoder	May	p 68
ACS decoder in a Digitor A-4199	May	p 74
Playmaster 300W subwoofer amp - 2	May	p 82
DSE parallel port interface for PCs	Jun	p 54
CFL & fluoro lamp inverter	Jun	p 60
Single chip chess computer	Jun	p 68
PC-based 68705K1 programmer	Jun	p 104
Crystal locked 5MHz VNG receiver	Jul	p 56
PC driven electrocardiogram	Jul	p 56
'Postage stamp' micro flasher	Jul	p 71
DSE mini stereo amplifier module	Jul	p 89
Flexitimer Mk2 - 1	Aug	p 56
Parallel port breakout box	Aug	p 68
DSE 1.5A regulated power supply	Aug	p 78
PC controlled sweep analyser	Sept	p 58
Flexitimer Mk2 - 2	Sept	p 70
LED battery voltage indicator	Sept	p 76

DSE multi-timer module	Oct	p 56
Induction loop TV headphones	Oct	p 68
PC controlled sweep analyser-2	Oct	p 76
DSE xenon tube flashing beacon	Nov	p 58
Model train controller	Nov	p 62
'Watchdog' timer card for PCs	Nov	p 76
Power supply module	Nov	p 98
Using the PIC16C84 single chip micro - 1	Nov	p 122
Active antenna for HF reception	Dec	p 58
DSE four channel IR remote control system	Dec	p 64
Remote volume control - 1	Dec	p 74
Dual power supply module	Dec	p 82

### EXPERIMENTING WITH ELECTRONICS

Switching regulators	Jan	p 86
Playing games with the 4060	Feb	p 90
An easy to build AM radio	Mar	p 72
'COB' sound generators	Apr	p 72
The many uses for diodes	May	p 48
Putting transistors to work - 1	Jun	p 91
Putting transistors to work - 2	Jul	p 39
Interesting transistor circuits	Aug	p 48
Simple circuits are often the best	Sept	p 82
Operational amplifiers unplugged	Nov	p 72

### FEATURES

Receiver Improvers: How Good Are They?	Jan	p 20
Calling All Spacecraft!	Jan	p 24
HST Searching for Planets on Other Stars	Jan	p 32
Apple's Quicktake Digital Camera	Feb	p 16
The World's Biggest Telescope	Feb	p 18
High Tech in a Modern Cinema	Feb	p 18
CSIRO's Multi-beam Satellite Antenna	Feb	p 18
Victoria's Schools Linked by Satellite	Feb	p 32
Out Beyond the Sound Cards	Feb	p 48
Putting a 'Spin' on Radio Stars	Mar	p 14
Lite and Safer Flight in Space	Mar	p 18
The Digital Printing Revolution	Mar	p 26
Pocket Packet goes TCP/IP	Mar	p 76
Recharging dry cells	Mar	p 82
'Interactive' Takes Centre Stage at CES	Apr	p 8
What's Inside the New 'Smart' Cards	Apr	p 20
Teaching Electronics at Home	Apr	p 23
Spying on the Sun	Apr	p 26
VAF Upgrades its Speaker Kits	May	p 8
Megabytes and F-Stops	May	p 26
DSP Revisited: The Next Generation	May	p 44
Big Screen 3D TV Needs No Glasses	Jun	p 26
Compact VIFA Subwoofer Kit	Jun	p 28
Upgrading Your PC with a 'Multimedia' Kit	Jun	p 12
Introduction to Basic Electricity	Jun	p 32
Mini Stereo Amp for Computers	Jul	p 63
The Search for Life Among the Stars	Jul	p 18
And Now, Live from China - 1	Jul	p 26

PCMCIA: Pretty Puny Peripherals	Jul	p 30
And Now, Live from China - 2	Aug	p 14
The Beginning of our Future in Space	Aug	p 26
Understanding the IRIS Codes	Aug	p 112
High Quality VIFA Two-Way Speakers	Sept	p 30
Formulas for Fantastic Faxing	Sept	p 14
'2dF' Nears Completion	Sept	p 20
And Now, Live from China - 3	Sept	p 26
DIY Faultfinding and Repair	Sept	p 46
Voyage of the Beagle	Sept	p 110
SMPTE '95	Oct	p 6
Warning: Some Cache RAMs Aren't	Oct	p 20
The Wide World of WWV	Oct	p 26
The Pianodisc	Nov	p 14
Observing the Violent Universe	Nov	p 26
Digital 'Piggyback' Security Monitoring	Nov	p 32
Fluoro Lamps and the Risk of Skin Cancer	Nov	p 36
Griffith Uni IAP powers ahead	Nov	p 84
Nikola Tesla: Creative Genius or Crackpot?	Dec	p 20
Biggest Radio Telescope Ever!	Dec	p 26
First Encounters with the Internet	Dec	p 28

### FORUM

Who should determine whether your service technician has sufficient qualifications?	Jan	p 34
TETIA and qualifications for service technicians: the debate continues	Feb	p 40
Problems playing CDs, soldering safety and connecting MOSFETs backwards	Mar	p 36
Australia's mains voltage, and why can't you use a CD player on a plane?	Apr	p 40
Qualifications for service technicians: the topic that simply will not die	May	p 34
The fury of some radio amateurs, when their wallets are threatened	Jun	p 40
More on banned CD's in planes, and do CD's have rumble?	Jul	p 34
Should Morse still be mandatory for a full amateur radio licence?	Aug	p 34
Responses to that letter about problems in NZ's industry...	Sept	p 40
The project we developed, but legally can't tell you how to build	Oct	p 40
DIY projects and the PSTN: interesting responses from Austel	Nov	p 20
CDPs on aircraft, rumble on CDs, and imports vs local manufacturing	Dec	p 40

### INFORMATION CENTRE

Troubleshooting problems, cleaning fluids and more on

that resistor-ladder 'What?'	Jan	p 104
Fuses, baluns and electrically charged rain...	Feb	p 94
Double takes and lateral thinking...	Mar	p 100
EA's new BBS explained	Apr	p 86
'Braid breaker' baluns, compact fluoro's and frypans	May	p 92
Party pieces, magnetics and high voltage capacitors	Jun	p 84
Insect repellers, repair hints and more...	Jul	p 92
Computer crashes, 'braid breakers' and more...	Aug	p 92
Suspect testing methods, ultra-sonic pest repellers	Sept	p 86
Sausage powered clock, and motorbike CDI	Oct	p 92
When supposedly compatible things aren't...	Nov	p 108
Baud and bits/second, braid breakers and insults...	Dec	p 84

### MOFFAT'S MADHOUSE

What's in a name, Tom asks - and also recalls US radio announcer 'Wolf Man Jack'	Jan	p 30
Reflections on the 'Quackintosh'	Feb	p 14
Our 'right' to privacy	Mar	p 24
E-mail, J-mail and gobbledygook	Apr	p 32
The man who is NOT America's richest person	May	p 30
A little slice of heaven, in Denver	Jun	p 24
The Dog goes all modern and electronic	Jul	p 6
Gridlock on the Information Superhighway	Aug	p 6
My, my — it's really Sci-fi!	Sept	p 6
Moments of memorable mischief	Oct	p 24
The sounds of silence...	Nov	p 6
It's all in the mind...	Dec	p 6

### NOTES & ERRATA

PC Interface for DSE's Teletext Decoder (June 1993)	Feb	p 97
Versatile 40V/3A Lab Power Supply (December 1993 and January 1994)	Feb	p 97
Versatile Solid State Audio Recorder (February 1995)	Mar	p 40
Low cost 1GHz counter (April 1993)	Mar	p 40
IMP Loudspeaker Testing System (July, August and September 1994)	Mar	p 103
Shoestring Stereo Amplifier (December 1994)	Apr	p 62
Versatile Multiple Announcement Recorder (February 1995)	Apr	p 89
Low Cost Inductance Adaptor (December 1994)	May	p 87
Experimenting with Electronics (April 1995)	Jun	p 32
EPROM Programmer (September/October 1993)	Jun	p 32
Shoestring Stereo Amplifier (December 1994)	Jun	p 32
Water Purity Tester (CDI - July 1995)	Sept	p 87

# Index January 1995 to December 1995

PC Driven Electrocardiogram	Sept p 87
Playmaster 300W Subwoofer Amp (April 1995)	Sept p 87
Stereo TV Sound Receiver (April 1995)	Sept p 87
Economy Surround Sound Decoder (May 1995)	Sept p 87
Power Transistor Tester (May 1988)	Sept p 87
Parallel Port Break-out Box (August 1995)	Oct p 87
Playmaster 300W Subwoofer Amp (April/May 1995)	Nov p 114
New improved Flexitimer Mk2 (September 1995)	Dec p 43
PC controlled Sweep Analyser (September 1995)	Dec p 43
Model Train Controller (November 1995)	Dec p 43
LED Battery Voltage Indicator (September 1995)	Dec p 43

## REVIEWS

Onkyo's TX-SV919THX A/V System	Jan p 11
The Promax GV-698 TV Signal and Pattern Generator	Jan p 126
NC Easy Connect Plus Line Sharer	Mar p 116
New Video Test Gear from Tek	Mar p 110
The Superfuser	Apr p 110
Software based Logic Analyser	Apr p 114
The Greencell Battery Regenerator	May p 32
Fluke's Enhanced 'Series II' Scopemeters	Jun p 112
HP's 54620A Logic Analyser	Jun p 116
'Super Mini' VIFA two way speakers	Jul p 78
IR Remote Control Tester	Jul p 108
PC-based 'Scope, Meter, Data Logger	Jul p 116
The Genius Cordless Mouse	Aug p 82
Fluke's new 5500A Calibrator	Aug p 104
Tek Handheld DSO samples at 500MS/s	Sept p 116
The Unaohm EP-315A TV-Satellite field strength meter	Oct p 104
'Discovery Card' — resolves IRQ and DMA conflicts	Oct p 120
AMIDiag diagnostic software	Nov p 90
5mW Laser Pointer	Nov p 120
EPROM emulator kit	Dec p 116
Jaycar DMM's	Dec p 119
Sony's 15SF digital multi-scan monitor	Dec p 122

## SHORTWAVE LISTENING

Interesting summer listening: 'number stations' finally identified and located	Jan p 103
More interesting listening	Feb p 85
Radio Canada celebrates 50 years	Mar p 98
Vanuatu installs new equipment	Apr p 35
How to verify that difficult station	May p 91

BBC monitors the world for news	Jun p 83
Time and frequency reference stations popular	Aug p 91
Relay bases closer to the audience	Sept p 93
France plans expansion at Radio Tahiti	Oct p 83
Russian broadcasts decrease: Moscow's new role	Nov p 66
Belgian broadcasts from Africa	Dec p 91

## SPOTLIGHT ON SOFTWARE

Intusoft's ICAP/4 Windows Jobsheet 2000	Jan p 140
Protel's Advanced Schematic 2.2, Adv. PCB 2.6	May p 120
Designer 4.1: Technical Edition	Jul p 112
Micrografx's Picture Publisher V. 5.0	Sept p 122
Spectra Plus V3.0 Pro Edition	Dec p 106

## THE CHALLIS REPORT

A look at the CSIRO's development of the A4 digital audio processor chip	Jan p 14
Accusound's 'Phase Zero' loudspeaker system	Feb p 8
The Alpine Electronics Ai-Net car hifi system	Mar p 8
VAF's DC-7 Mk2 loudspeaker system	Apr p 14
The Vivid 3D Plus ambient sound enhancer	May p 12
Akai's impressive VS-G2100 'Intelligent' VCR	Jun p 8
The Bose LSM5 'Lifestyle' Music System	Jul p 10
Sony's new MDM-111 Mini Disc Data Drive	Aug p 10
The Harman/Kardon TD420 'Pro' Cassette Deck	Sept p 10
The Philips FW17 'Monster Micro' compact stereo	Oct p 12
The Sony SBM-1 'Super Bit Map' audio DAC	Nov p 10
Yamaha's CDC-755 five disc CD changer	Dec p 10

## THE SERVICEMAN

'The Tape Duplicator from Hell' — they don't make them like that any more!	Jan p 42
The Sanyo CTV that I almost put an axe through!	Feb p 44
"Oh — you might like to fix the TV, if you get bored!"	Mar p 42
The polarity of VW car batteries, and servicing tip risks	Apr p 44
The problems caused by uninformed pot twiddling!	May p 40
The car that produced wow and flutter in cassette players!	Jun p 46
The failure alarm that sometimes made the system fail!	Jul p 42

The Sanyo that wouldn't change channels any more...	Aug p 40
What do you do when a CTV has reached its 'use by' date?	Sept p 22
The sinister case of the 'exploding' microwave ovens	Oct p 46
Customers: where WOULD we servicemen be without them?	Nov p 46
Wrestling with some decidedly unfriendly audio and video equipment	Dec p 46

## VINTAGE RADIO

How Astor radios were made - Douglas Bolton describes Astor's production lines	Jan p 108
Good advice for vintage set buyers: 'Caveat Emptor'	Feb p 98
A quiz on vintage radio servicing	Mar p 94
A miniature Eddystone receiver - the 870A	Apr p 100
Restoring a monster Columbia 1930 TRF receiver	May p 100
Rewinding old power transformers	Jun p 74
Revisiting the Philips 'Theatrette' receiver	Jul p 82
The excellence of Hammarlund components and receivers	Aug p 84
The Hammarlund 'Super Pro' receivers	Sept p 34
Vintage electronic music: the Theremin	Oct p 84
AC mains heated valves and how they came into use	Nov p 100
Who really DID invent the Superheterodyne?	Dec p 92

## WHEN I THINK BACK

Archie Caswell: serviceman, radio ham and modest hero in Japanese POW camps	Jan p 38
Archie Caswell: radio dealer and modest hero — 2	Feb p 34
Readers have their say on Archie Caswell, H.K.Love	Mar p 30
Readers have their say — 2: what are 'collectables'?	Apr p 36
Donald Macdonald and Radiovision	May p 20
A.C.E Radio and the post-war disposals stores	Jun p 34
Readers think back - maintaining old radars	Jul p 20
Max Byer - well made audio recording equipment	Aug p 20
The car radio industry: a career for Vic Humphrey!	Sept p 34
Victor Harris: sought perfection from analog discs	Oct p 34
Victor Harris: top performance from analog discs - 2	Nov p 40
World War II: 'Funny-peculiar' things happened in radio, 50 years ago!	Dec p 34



Want to get more in-depth with the 'how',  
'why' and where in the world of Music,  
recording, Multimedia and more? Read

AUSTRALIAN

# DIGITAL

MUSIC, RECORDING, MULTIMEDIA

WIN A STUDIOMASTER STAR SERIES CONSOLE

AUSTRALIAN  
**DIGITAL**  
MUSIC • RECORDING • MULTIMEDIA

1995 Issue No. 8 \$6.95 with CD (NZ \$8.00 inc. GST)

NO PART OF THIS DISC MAY BE REPRODUCED IN ANY FORM WITHOUT THE WRITTEN CONSENT OF THE COPYRIGHT OWNERS. THIS MIXED-MAKE MULTI-PLATFORM COMPACT DISC IS ISSUED WITH AUSTRALIAN DIGITAL MAGAZINE. NOT FOR RESALE.

**DIGITAL**  
MUSIC • RECORDING • MULTIMEDIA

**CD MISSING?  
ASK YOUR NEWSAGENT!  
BEWARE!**

Don't play track #1 on CD audio player  
(it's software only) — play all  
other tracks on it, though!

**KORG VIRTUAL SYNTHESIS**  
Now & the future...

digidesign®

AKAI 92000 & E-mu 164 samples

Print Post Approved by 2952073 01441


9 31296 124401

To subscribe to *Australian Digital* magazine phone TOLL FREE 1800 800 933 - Sydney residents phone (02) 353 9992 - and have your credit card details ready. Or send your name, address and phone number, with your payment of \$35.00 for 6 issues (cheque, credit card details or money order) to: Federal Publishing, Subscriptions Department, Reply Paid No. 3, PO Box 199, ALEXANDRIA NSW 2015 (no stamp required) or fax (02) 353 0967.

**ON SALE AT YOUR NEWSAGENTS NOW**

# Vintage Radio

by PETER LANKSHEAR

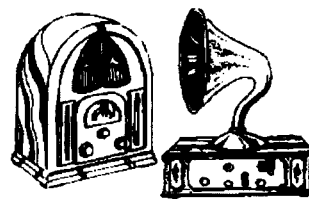

## Ancestral Electronics — 1

1995 was a significant year in the history of electronics, as it was the centennial of the young Marconi's taking the generation and detection of Hertzian waves out of the laboratory to experiment in their practical use. But so far, there has been remarkably little commemoration of his achievements, from which grew one of the greatest engineering sciences. Here's a look at the existing technology that Marconi was able to build upon.


This coming year continues the Marconi anniversary, as it was during 1896 that he made his first application for a patent, and gave public demonstrations in Britain of transmission and reception of wireless telegraph signals.

I suspect that one reason for the lack of fanfare is that no exact date can be put on the occasion when Marconi was actually fired up with the idea of using electromagnetic radiation for communication. Nor on his experiments which made the transition from repeating the investigations of scientists such as Hertz and Lodge, to the realisation of a practical system of wireless telegraphy.

Marconi is generally credited as being the first to create a working system that evolved into a commercial operation, building on the findings of previous research. As Oliver Lodge is reported to have remarked, "We all knew about the egg; but Marconi showed us how to stand it on its end".

We know too that initially Tesla in America, and Popov in Russia were probably ahead of Marconi with their development work, but did not have the same business acumen or backing. Marconi had a head start by having the foresight to be born into an affluent family, with very influential connections in both Italy and Britain. In 19th-century society this provided invaluable advantages in achieving recognition.

Electronics engineering is sometimes thought of as having its birth in the wireless telegraph, but in reality its roots go back more than half a century previous-

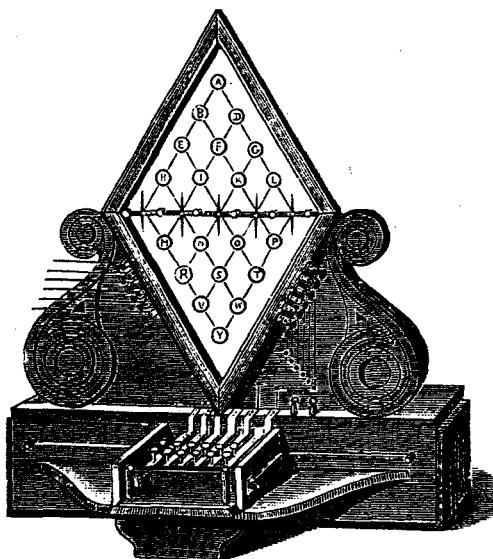

**Fig. 1: The first electric telegraph in commercial operation was the five needle Cooke and Wheatstone, of 1837. Any one letter of 20 could be selected by the deflection of two needles, controlled by the keys at the base of the instrument. Note the six line wires at the left of the face.**

ly to the invention of the electric telegraph — which by the middle of the 19th century was already well established world wide, with an advanced technology, and together with the railway had an enormous economic and social impact. In America especially, the study and collection of telegraph instruments is regarded as an important aspect of vintage electronics, all the more significant as the telegraph is now virtually extinct.

Although the value of Marconi's achievements should not be underesti-


mated in any way, it is important to realise that he worked with an existing technology. In fact, his early equipment was essentially that of a basic electric telegraph, along with simple equipment to generate and respond to radio frequency radiations. His main object was to provide a wireless connection between conventional telegraph instruments. Had he first needed to have developed the telegraph instruments as well, his work would have been considerably more difficult.

### Earlier origins

The origins of the electric telegraph go back a long way. In 1753, a correspondent in *The Scots Magazine* suggested electrifying wires to attract pieces of paper with letters or words printed on them or to ring bells. This was obviously not a practical system, but an indication of the early realisation that the ability of electricity to travel instantaneously through a long conductor could be used to convey intelligence.

In 1809 in Germany, Samuel Sommering demonstrated over a distance of 600 metres a telegraph which had an electrolyte filled glass vial for each letter of the alphabet. Bubbles of gas indicated the required letters. The system might have worked, but with a wire for each character, constructing connecting cables of any length would have provided a daunting obstacle. The signalling speed would also have been very slow.

Andre Ampere, whose name is immortalised in the unit of current, in

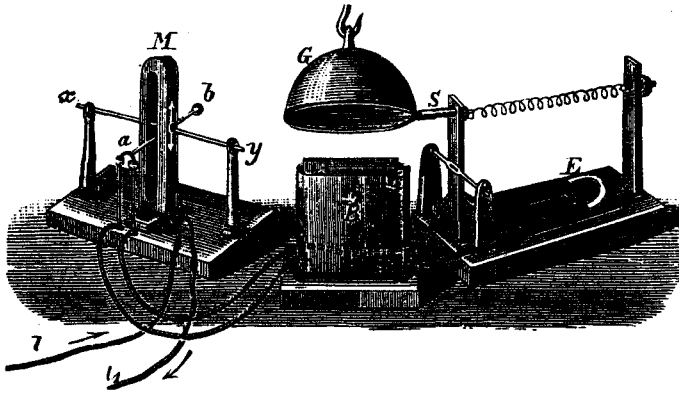


**Fig.2:** To obtain sufficient current to operate the needle telegraph alarm bell, Wheatstone invented the first relay. A galvanometer coil M surrounded a magnetised needle carrying a pair of contacts a. When the needle was deflected, the contacts touched the surface of some mercury in the two little cups, completing the circuit of the battery B and the electro magnet E. This activated the bell striker S.

1820 came up with a much more workable method by suggesting the use of galvanometers.


A galvanometer is essentially a compass needle deflected by currents flowing in a surrounding coil of wire, and is the ancestor of moving iron and moving coil meters. Ampere proposed using one instrument for each character, but again the logistics of constructing such a system ruled it out.

In one of those coincidences of the type that has happened several times in the history of electronics, in 1837 no fewer than three independent inventors announced workable systems. Carl Von Steinheil in Germany demonstrated a single galvanometer system which relied on a code using combinations of left and right deflections of the needle.

It is unclear as to what extent, if ever, that Steinheil's system was used, but he

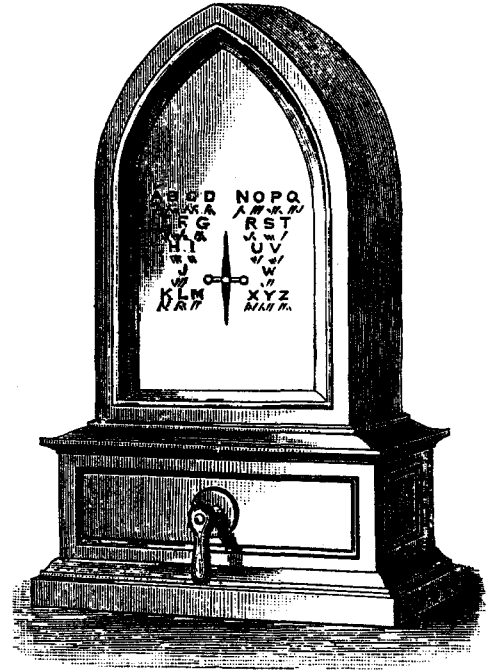

**Fig.3:** Cooke and Wheatstone's telegraph was ultimately simplified to a single needle, controlled by the handle in the base. It was often used with a form of the Morse code, with left deflections equalling dots and right deflections dashes.

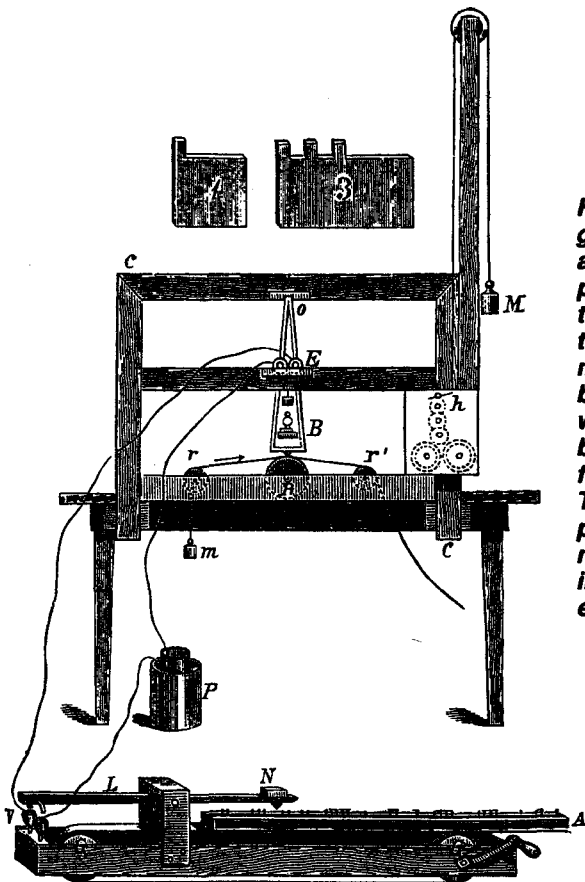


**Fig.4:** The first Morse telegraph. Although it bore no apparent resemblance, it possessed all the essentials of the practical system that remained in use for more than a century. At the bottom is the transmitter, in which level L was actuated by teeth on movable type fixed in the carrying strip A. There were nine different patterns, to provide the necessary number of teeth; in the drawing, 1 and 3 are examples.

did make the invaluable discovery that the earth can be used as a conductor of virtually zero resistance. This useful property halved the amount of wire and battery power that would otherwise have been required for telegraph circuits.


In England Charles Wheatstone, (later knighted for his many engineering achievements) teamed up with William Cooke to construct the first successfully operational electric telegraph. Again, this was based on the galvanometer, and over the years it went through at least three developments. Wheatstone made several important contributions to the telegraph, and one of his greatest, the relay, came from his work with the needle telegraph. Another of major importance, the principle of which is still important today, was the introduction of the Christie Bridge, often called the Wheatstone Bridge.

Cooke and Wheatstone's first system of telegraphy used a row of four and then five needles. By deflecting two needles at a time, any one of 20 characters arranged in a diamond shaped grid could be selected. This system was installed over a distance of 2.5km between two London & Northwestern Railway stations and in 1840, the Great Western Railway installed a line 63km long. This

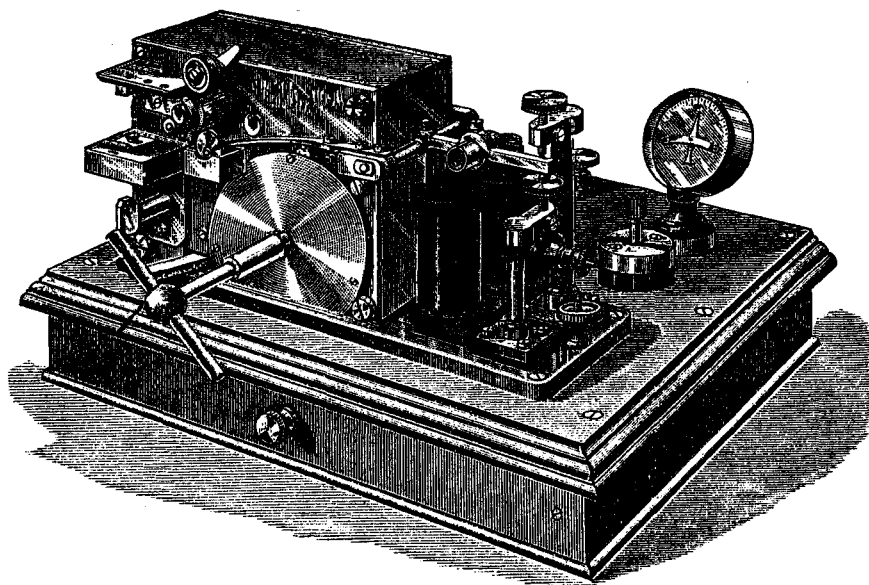

**Fig.5: The Morse register, recorder or inker was developed directly by Alfred Vail, from Samuel Morse's picture frame receiver. Operators found that they could read the messages by listening to the sound of the armature hitting the limiting screws, and so the sounder was developed.**

## ALPHABET AND NUMERALS.

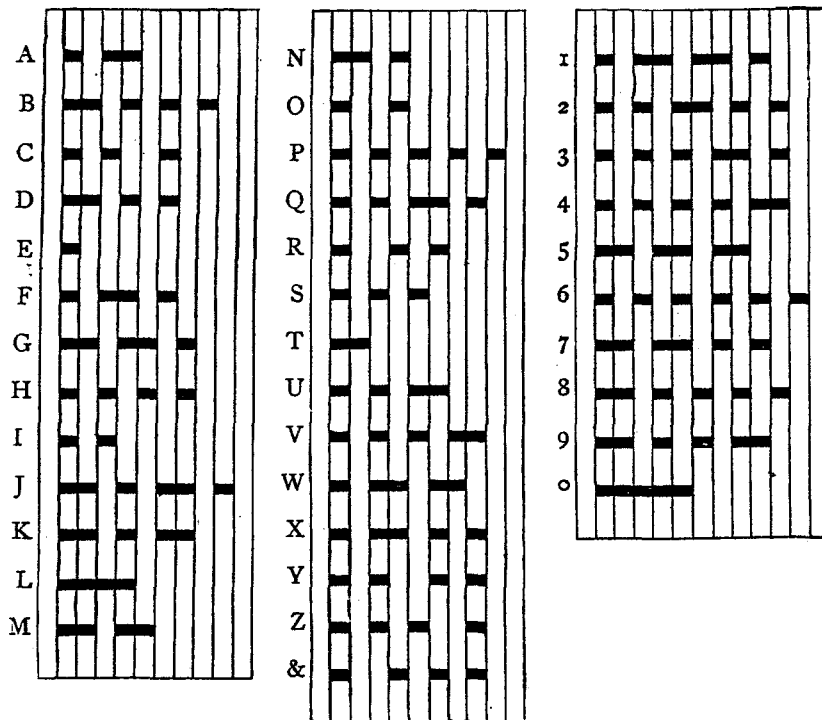

**Vail's adaptation of the Morse code, which became known as Continental or American Morse. With two different lengths of dash and long spaces within some letters, it was a difficult code to master. American and Canadian landline operators refused to adopt the more familiar International Morse code, although it was used by their radio counterparts.**

became quite a wonder, and the public was charged a shilling to watch it in operation.

This original Wheatstone and Cooke telegraph was successful, but it required five or six wires between stations, and needed two operators — one reading and the other writing down the messages. The restricted signalling speed also meant that it was soon superseded. Single-needle and double-needle adaptations were used quite extensively in England, and for communication between signal boxes, these instruments survived on some railway systems into the second half of this century.

### Artist's obsession

The third system announced in 1837 was to revolutionise communications and dominate telegraphy well into the 20th century. This was of course the telegraph invented by portrait painter Samuel Morse, who although he knew little about electricity, was inspired to overcome enormous difficulties to do so. He received invaluable practical assistance from Alfred Vail, who has not always been given due credit, and the two eventually entered a partnership. Morse ran into problems in operating his receiver over long connecting wires, and enlisted the aid of Professor Henry, who explained the importance of sufficient ampere-turns on an electromagnet.

Previous systems had worked by some method of pointing to or indicating individual characters, but the genius of the Morse telegraph was that it used instead a binary code which could be used to represent an unlimited number of characters.

Initially, the Morse transmitter used nine different patterns of movable lead type, adapted from the printing industry. Instead of a typeface, each had a number of notches corresponding to the code pulses representing one of the numbers 0 to 9. For transmitting messages these 'types' were mounted on a bar, which was moved under a lever fitted with a set of contacts.

The prototype Morse receiver, which was built on a frame from a painter's canvas, consisted of an arm or pendulum actuated by an electromagnet. A pencil fastened to the end of the pendulum was in contact with a moving paper tape. Pulses from the transmitter caused lateral deflections of the pendulum, whose movements were registered on the tape as a serrated line from which the transmitted numbers could be read. These

were then interpreted with the aid of a code book. For example, the sentence 'SUCCESSFUL ATTEMPTS WITH TELEGRAPH' was transmitted as 215, 36, 2 and 58.

### Vail's Morse code

Alfred Vail now took over, and as a skilled and gifted technician, he refined the equipment to the stage where Congress could be persuaded to grant an appropriation for a line between Washington and Baltimore. The first message was sent on May 24, 1844 with the project hailed as a triumph.

For sending, Vail discarded the movable type and substituted the familiar manually operated key, while the ungainly receiver was transformed into the 'Register' which embossed or marked the paper tape by the vertical motion of a stylus or inked wheel. Of even greater significance was Vail's revision of the code, which now represented each character directly and did not need a code book.

There were seven elements in the new Morse code, with the basic unit of time the *dot*. The other elements were the short dash = two units; the long dash = four units; the space between elements of a letter = one unit; the letter space = two units; the word space = three units; and finally the sentence space was six units.

Readers familiar with the International Morse code will know that dashes are today three times the length of a dot, and may be puzzled by the reference to the long dash. The fact is that there were *two* Morse codes. Vail's original code, known generally as 'American Morse', was used exclusively on the extensive landline systems of the US and Canada. As can be seen from the table, it is more complex and demands greater skill than International Morse, and with some letters containing a double space, ambiguities were possible. For example, EE could be confused with O.

Within a few years, Morse himself campaigned for the adoption of a simpler code; but the operators refused to give up American Morse, which, according to some authorities, was faster than the International code. Eventually, the short dash was lengthened to three units, and, until teleprinters, computers and fax machines made the telegraph extinct, American Morse remained the standard code for North American landlines.

Elsewhere in the world, the International Morse code had become standard. This presented a problem as marine radio became established, requir-

ing American radio operators, including amateurs, to use the International code. One outcome was that operators dealing with both line and radio telegraphy had to become 'bilingual'. It appears too that at one stage, the US Navy used yet another code.

### Birth of the Sounder

The Morse register provided a permanent record on a paper tape, and for this reason was favoured by Marconi for his early equipment. But deciphering the marks on the paper was time consuming and operators soon learned to read the messages, as they were received, from the sound of the armature lever striking the limiting stops. A similar practice was developed by operators of the needle telegraphs, with the added advantage that a second person was not needed to transcribe the messages.

It was only a short step from this to the development of the most familiar of all telegraph instruments, the Morse sounder — but a fuller description of this will have to wait until next month. As well we will recount some of the story of Australia's own heroic enterprise, the Overland Telegraph, and look at some of the complex technology involved in Morse telegraphy.

As an example of this complexity, I will leave you with a question that could be a candidate for one of Peter Phillips' 'What?' puzzles: 100 years ago, how could four messages be sent simultaneously and independently over one wire, using DC technology only? Time sharing and diodes were not used. Look for the answer next month... ♦

## RESURRECTION RADIO

### VALVE EQUIPMENT SPECIALISTS

Repairs to valve radios, guitar and audio amplifiers

#### Books for holiday reading:

Golden Age of Radio in the Home .....	\$42.95
More Golden Age of Radio .....	\$49.95
Old Time Radios Restoration & Repair .....	\$36.95
70 Years of Radio Tubes and Valves .....	\$42.95
Crystal Sets 'n' Such .....	\$19.95
In Marconi's Footsteps .....	\$49.95
The Compleat Talking Machine .....	\$39.95
An Approach to Audio Frequency Design .....	\$39.95
The Audio Designer's Tube Register .....	\$36.95

Send SSAE for Catalogue

Visit our Showroom at

242 Chapel Street (PO Box 2029)  
PRAHRAN, VIC 3181

Tel (03) 9510 4486 Fax (03) 9529 5639

READER INFO NO. 21

# ROCOM

## ELECTRONIC COMPONENTS

### COMPONENT SALE

#### INTERGRATED CIRCUITS

4028	BCD-to-Decimal Decoder	\$0.20
4029	4-Bit Preset. Up Down Count.	\$0.20
4093	Quad 2-Input NAND Schmitt Trig	\$0.25
4164B-12	D/RAM 64K x 1	\$0.30
4503	Hex 3-State Buffer	\$0.25
4536	Programmable Timer	\$0.20
74123N	Retri. Monostable Multiv.	\$0.25
74HC04N	Hex Inverter	\$0.20
74HC21B1	Dual 4-Input AND Gate	\$0.20
74HC4051AP	8-Ch. Ana. Multi/De.Plexer	\$0.30
74HCT153	Dual 4-Input Multiplexer	\$0.20
74LS138N	1-of-Decoder/Demultiplexer	\$0.25
74LS151	8-Input Multiplexer	\$0.20
74LS125	Quad Buffer, Low Enable, 3-State	\$0.20
74LS123	Dual Retrigr. Monostable Multivib.	\$0.20
74LS157	Quad 2-Input M/plexer, Non-Invert.	\$0.20
74LS173	4-Bit D Register, 3-State	\$0.20
74LS257	Quad 2-Input M/plex, N/Invert, 3-St.	\$0.20
74LS20	Dual 4-Input NAND Gate	\$0.20
74LS241	Octal Bus/Line Driver, 3-State	\$0.20
LF353N	Wide B/wld. D/JFET Inp. O/Amp.	\$0.40
LM339N	Low Pwr Low Offset Volt. Q/Comp.	\$0.25
SN75492	Display Driver	\$0.30
LM386N-1	Low Voltage Audio Pwr Amp.	\$0.30

#### CRYSTALS

4.0MHz	H123	\$0.80
11MHz	H123	\$0.40
3.5795MHz	H123	\$0.70
13.1072MHz	H123	\$0.25

#### TRANSISTORS -SCR'S

BC547B	NPN 45V 0.1A 500mW TO-92	\$0.07
BD291	NPN 45V 6A 60W TO-126	\$0.15
BD292	PNP 45V 6A 60W TO-126	\$0.15
TIP3055	NPN 100V 15A SOT-93 POWER	\$0.60
TIP2955	PNP 100V 15A SOT-93 POWER	\$0.60
BC558	PNP 30V 0.1A 0.5W TO-92 G/P.	\$0.05
BC559	PNP 30V 0.1A 0.5W TO-92 G/P.	\$0.05
MPSA93	PNP 200V 500mA 625mW TO-92	\$0.10
MPSA42	NPN 300V 0.5A TO-92	\$0.10
PN2222	NPN 40V 0.8A TO-18 G/PURP.	\$0.05
C106D	4A 400V 200µA-IGT (SCR)	\$0.40

#### DIODES

RG1B	100V 1A Fast	\$0.10
122108	100V 30A Fast (stud)	\$0.40
	EQUIV. TO: 1N3910	

STOCK IS SUBJECT TO PRIOR SALE.

#### ROCOM ELECTRONIC COMPONENTS

261 Huntingdale Rd HUNTINGDALE VIC. 3166

P.O BOX 142 HUNTINGDALE VIC 3166

PH. 03 9548 9229 FAX. 03 9562 8772

READER INFO NO. 22



## FOR SALE

**Fully approved 12V DC 1 Amp "plugpacks":** Buy direct from importer. \$10 + sales tax. Many other models available. Call AV-COMM Pty Ltd (02) 9949 7417/9948 2667 or fax (02) 9949 7095.

**UK magazine ETI:** is currently running a series of articles on a PIC Basic Interpreter that will support 10/18 I/O lines and 2K/8K Eeprom. Larger versions under construction. Programs a Micro in Basic from the serial port of your PC. To get a free copy of the \*FULL\* Win 3.1/95 Dev System, Manual, and hardware pricing, send me a \$2 coin and I'll send it on my Promo disk to you. Don McKenzie 29 Ellesmere Cres, Tullamarine VIC 3043. (03) 9338 6286.

**"The homebuilt dynamo":** (construction plans), brushless electric generator, 1000 watt DC at 740 RPM. A\$85 postpaid airmail from Al Forbes, Box 3919-EA, Auckland, New Zealand. phone 0011 649 818 8967 anytime. Philips Ferroxdure rotor magnets (3700 gauss) kit now available cut to size and magnetised. Fax: 64 9 818 8890.

**Unusual books:** Electronic devices, fireworks, locksmithing, radar invisibility, surveillance, self-protection, unusual chemistry and more. For a complete catalogue, send 95 cents in stamps to: VECTOR PRESS, Dept E, PO Box 434 Brighton SA 5048.

**Amidon Ferromagnetic Cores:** For all RF applications. Send business size SASE for data/price to RJ&US Imports, Box 431, Kiama NSW 2533. Agencies at Geoff Wood Electronics, Sydney; Webb Electronics, Albany; Assoc TV Service, Hobart; Truscotts Electronic World, Melbourne and Mildura; Alpha Tango Products, Perth.

**Rain Brain 8 Stat. Sprinkler Kit:** Top quality kit has temp. and rain switch I/Ps, 3 week cycles. Heaps of other features! Call Mantis Micro Products, 38 Garnet St. Niddrie, 3042 P/F/A (03) 9337 1917.

**HC11's and IC's http:**  
//worf.albanyis.com.au/bob/home.html.

**2SJ162 & 2SK1058 FET's:** also Toroid transformers to suit EA Pro-Series Amps. FETS \$10 ea. (03) 9704 2960.

**Business for sale:** Electronic service and repair business for sale in the fastest growing inland city in NSW. Plenty of fresh air, sunshine & country hospitality. At present servicing mainly audio gear, specialising in car audio. Service agent for regular, wide custom base. Plenty of room to expand in premises and business, including into retail. Good lease available. This business is offered for genuine urgent sale due to the owners ill health. Price \$45,000 WIWO. Enquiries phone (068) 841 158.

**Current Monitor CM100:** As seen in Sept. EA. Unique instrument for the design and service of anything mains powered. Measures from 1mA to 20 Amp true rms on 3.5 digit LED display. BNC output DC to 100kHz fully isolated. Amps/KVA switch. In stock at \$395 plus p+p. Phil Allison (02) 799 8242.

**Voice Scramblers:** Combined encoder/decoder modules. Sum radios etc. \$49 incl. post & pack. Accurate Electronics. Ph: 018 600 006 for details.

**Educational Electronic Kits:** Easy to build Good quality. Up to date technology. Cheap. Guar to work. Wide selection. TEACHER LESSON PLANS. Send \$2 stamp for catalogue/price list or log onto BBS FREE for full kit details. DIY Electronics 22 McGregor St, Numarkah. VIC 3636 Ph/Fax (058) 621 915 Ph/Fax/BBS (058) 62 3303. E-mail laurie.c@cni.com.au .

**C Compilers:** Dunfield compilers are now even better value. Everything you need to develop C and ASM software for 68HC08, 6809, 68HC11, 68HC16, 8051/52, 8080/85, 8086 or 8096: \$140.00 each. Macro Cross Assemblers for these CPUs. All compilers, XASMs and monitors: \$400. 8051/52 or 80C320 Simulator (fast): \$70. Demo Disk: Free. All prices +\$5 p&p. GRANTRONICS Pty Ltd, PO Box 275, Wentworthville. 2145. Ph/ Fax (02) 631 1236.

## CLEARANCE SALE BE QUICK! LIMITED QUANTITIES

### \* NEW ITEMS:

Video/Audio TV Modulator	\$10
LNFBs	\$150
Video Phone Intercom	\$400
Microwave Movement Detector	\$40
Cordless Stereo Headphone	\$50
BETA Video Tapes	\$6
40 Watt 12-230vac Inverters	\$40

### \* USED ITEMS

Vectorscope Tektronix	\$400
A3 Flatbed Plotter	\$250
Video Camera B&W & Colour	\$50
YEW Voltage-Standard	\$300

16mm Projectors etc. Ask for List  
Ph: (09) 349 9413 Fax: (09) 344 5905.

### \$159 Tiny 2/3 matchbox size video

**camera modules:** Over 20 types from 32x32x15mm Low light & IR sensitive. IR LEDs 50mW from 50¢. UNIQUE Vid/Audio TV MODULATOR/MIXER/ANT AMPLIFIER plug in series with coax display record on TV/VCR \$30. Ask for CCTV info & price list. ASS Ph: (09) 349 9413 Fax: (09) 344 5905.

**Cheap Microcontroller System:** 8MHz Z80. Program from IBM, no Eeprom needed. 32k RAM batt backed. Up to 128 I/O. Can run stand alone. Software = Text Ed/Simulator/Compiler/Dumper/Reader/Z80 Subs/Heif. Min XT/PC & EGA. Software & circuit \$20. (Components not incl. - cost \$70). Send \$20 to: J&N Moxham, 23 Arizona Tce, Glenalta SA 5052.

## ADVERTISING RATES FOR THIS PAGE

### SMALL ADS:

The minimum acceptable size of two centimetres x one column costs only \$70. Other ads up to a maximum of 10 centimetres are rated at \$40 per centimetre.

### CLASSIFIEDS:

\$6 per 40 letters. Just count the letters, divide by 40, and multiply by \$6.

ROUND UP TO THE NEAREST MULTIPLE OF \$6  
MINIMUM CHARGE \$12

### CLOSING DATE:







Ads may be accepted up to the 10th of the month, two months prior to issue date.

### PAYMENT:

Payment must be in advance by cheque, money order or credit card, include your name, address, and credit card details. Faxes accepted. Payment should be sent with your advertisement to:

THE ADVERTISING  
PRODUCTION MANAGER  
ELECTRONICS AUSTRALIA,  
P.O. BOX 199,  
ALEXANDRIA,  
NSW 2015

PHONE (02) 353 0740 • FAX (02) 353 0997

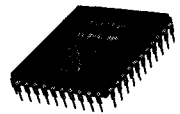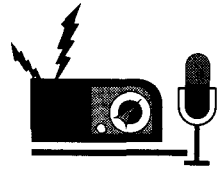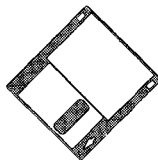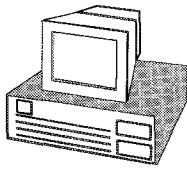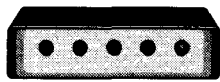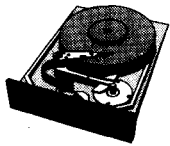

## FOR SALE

**Clearance Sale:** PC-based Analog Interface unit kit. Parallel port powered. 8 bit ADC/DAC. C/Pascal/Basic drivers supplied. Complete kit now only \$55. Short form kit, PCB & software only \$25. Advanced R&D Solutions. 12 Copeland Road Lethbridge Park 2770. (02) 628 1223.

### Eddystone 940 Communications

**Receiver:** in very good working condition \$250 ono (02) 331 3965.

**Eprom Programmer:** For your PC, model MP271, 2716-27512 eproms, suitable for Philips and Codan comm. software, as new \$250.00 Ph: 903) 803 6590.

### Marconi TF868A Universal Bridge:

\$295 • Hewlett Packard 606A RF Signal Generator \$295 • EEL Unigalvo type 20 Galvanometer model \$639. (06) 299 3218.


**Microcraft presents:** Dunfield (DDS) products are now available exstock at a new low price, please ask for our catalogue. Micro C, the affordable 'C' compiler for embedded applications. Versions for 8051/52, 8086, 8096, 68HC08, 6809, 68HC11 or 68HC16 \$139.95 each + \$3 p&h • Now on special is the SDK a package of ALL the DDS 'C' compilers for \$399 + \$6 p&h • EMILY52 is a PC based 8051/52 high speed simulator \$69.95 + \$3 p&h • DDS demo disks \$7 + \$3 p&h • VHS VIDEO from the USA (PAL) 'CNC X-Y-Z using car alternators' (uses car alternators as cheap power stepper motors!) \$49.95 + \$6 p+h (includes diagrams) • Device programming EPROMs/PALs etc from \$1.50 • Fixed price electronic design and PCB layout • Credit cards accepted • All goods sent certified mail • Call Bob for more details MICROCRAFT PO Box 514 Concord NSW. 2137 (02) 744 5440 or Fax (02) 744 9280.

### ELECTRONIC DESIGN-MANUFACTURE

Complete Electronic Design to Production Service.  
PCB Assembly and Product Assembly.  
PCB Design & Manufacture, Prototyping.  
Redesign/Modify Existing Equipment.  
Service to Electronic Equipment.

**ELECTRONIC FORMATION SERVICES**  
PO BOX 1407, WEST MELTON, VIC 3337  
PH/FAX (03) 9747 0800

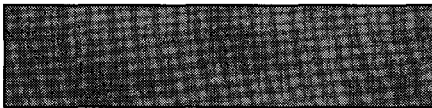**Satellite Dishes:** International reception of Intelsat, Panamsat, Gorizont, Rimsat. Warehouse sale - 4.6m Dish & pole \$1499, LNB \$50, feed \$75. All accessories available. Videosat, 2/28 Salisbury Rd. Hornsby. (02) 482 3100 8.30-5.00 M-F.



ABCDE  
FGHIJK  
L NO  
PQR T  
UVWX  
YZ

Ignore it and it won't  
go away.

**MS**  
Multiple Sclerosis.

## WANTED

**Any early valve hi-fi:** Quad, Leak Garrard 301/401, SME, Ortofon, KT66, KT88, 300B or similar. Cash paid (074) 491 601.

**Manual or circuit diagram:** for Vinten base radio type BR20 (receiver/modulator section). Copy costs gladly paid. Call Brian, (03) 809 2079.

**Experienced video-tv tech required:** for the beautiful Atherton tablelands in North Qld. Above award for the right person, must have a sense of humour. Ph: Nick Chapman (070) 913 858 (W). (070) 965 546 (H).

**Wanted:** Circuit for Conway Masteranger model \$639. (06) 299 3218.

**PCB + Schematic Software**  
DOS and Windows  
From \$160  
107A Burbridge Rd  
Hilton 5033 Australia  
Don Alan Electronics Ph: (08) 433957 Fax: (08) 2345339

**Printed Circuit Board Manufacture**  
We manufacture high quality PCBs at prices so low, that it's not worth making yourself!  
INSTANT PCB'S  
PO BOX 448 AVALON 2107  
PH: (02) 974 1189 FAX: (02) 974 5491

**KIT REPAIRS - R & D, prototyping, repairs to electronic equipment, all kits repaired**  
**CAMPAD ELECTRONICS**  
26 KEITH STREET CAPALABA, Q. 4157  
Phone (07) 3245 2008

**TORTECH PTY LTD**  
TOROIDAL TRANSFORMERS  
Design and Manufacture  
Approved to AS3108 - 1990 & U.L. Standards  
Tel: (02) 642 6003 Fax: (02) 642 6127

**Phoenix Radio**  
AT LAST IT'S NOW AVAILABLE  
Manufactured in Australia By Phoenix Radio  
UNIVERSAL BATTERY ELIMINATOR  
'A', 'B' and 'C' Power Supply.  
Suitable for a wide range of battery powered receivers from the 1920's to the 1950's.  
This single unit will operate most multiple battery, portable and vibrator powered receivers.  
A MUST FOR ALL VINTAGE WIRELESS ENTHUSIASTS.  
Send S.A.E. for information & specifications or contact Phoenix Radio on (08) 537 0397 Post: P.O. Box 140, Milang SA 5256.  
Circuit design by Peter Lankshear (EA Vintage Radio)

# 50 and 25 years ago...

'Electronics Australia' is one of the longest running technical publications in the world. We started as 'Wireless Weekly' in August 1922 and became 'Radio and Hobbies in Australia' in April 1939. The title was changed to 'Radio, Television and Hobbies' in February 1955 and finally, to 'Electronics Australia' in April 1965. Below we feature some items from past issues.

## January 1946

**Television, sound on one channel:** A radio development demonstrated at Cambridge seems likely to restore British television to the leadership it enjoyed until the war started, when the diversion of technicians to other work, enabled America to win ascendancy.

The Pye Radio Company has evolved a new system marking a major advance in transmission and reception. This makes possible the use of a single instead of a double transmitting unit as hitherto used, and similarly combines into one the vision and sound receivers.

Television pictures are broadcast in lines, picked up at the rate of 10,000 a second by a 'scanning point'.

At the end of each line there is a tiny

pause before the 'scanning point' goes back to start a new line.

Pye technicians have discovered a means of broadcasting a sound 'snapshot' during that pause.

Guests who saw the system operating report that reproduction of both sound and vision is superior to the older system of dual transmission.

## January 1971

**Million volt electron microscope:** The first commercial million volt electron microscope to be built in Europe is now installed at the UK Atomic Energy Authority at Harwell. It will be used in studies of neutron radiation damage in reactor materials and in their non-nuclear program.

The high voltage makes it possible to

obtain sharp images from thick specimens. This, combined with the large specimen space available, enables a wide variety of experiments such as heating and tensile testing to be performed within the microscope while the specimen is under observation.

**High efficiency klystron:** An electrostatic depressed collector developed by the General Electric Company in the USA has increased the efficiency of a high power broadcast klystron from 45% to 67% according to Dr Theodore G. Mihran, a physicist at the company's research and development centre.

Developed for space applications, the high efficiency klystron may help make possible communications satellites for direct and simultaneous nationwide television broadcasting, Dr Mihran said.

By virtue of its increased efficiency, the tube's heat rejection system and the satellite's solar cells can be reduced; the former by two to three times, and the latter by more than a third. The combination of increased efficiency and size reduction is expected to permit smaller communication satellites with less power needed for launching. ♦

# EA CROSSWORD

## ACROSS

1. Research facility. (10)
5. Collections of items for assembly. (4)
9. Flexible ring. (7)
11. Equipment carried on a mission. (7)
12. Items for bundling wires. (4)
13. Sound with vibrations. (5)
14. Laser guided weapon. (4)
17. Successful composer, ---- Lloyd Webber. (6)
18. Gradual introduction of a signal. (4-2)

20. Brand of mobile phone. (1,1,1)
22. Electronic system replacing cash. (6)
24. Manufacturer of CB radios. (6)
28. Section of a communication network. (4)
29. Gauge, in mm, of small videotape. (5)
30. Rock group with current choice? (1,1,1,1)
33. Purpose of most video games. (7)
34. Section of mains wiring. (7)
35. Telephone tone. (4)
36. Wave frequency generator. (10)


## SOLUTION TO DECEMBER 1995

```

GENERATE OPAMPS
R O O I L E W
I O N P A I R S H U T T L E
D I M O O G E D
B A C K D I A L S P O L E
I A E D A F R N
A D D I N G U T I L I S E
S T B E O N
W I R E T A P G A R B L E
P N R L P T L W
L I K E A L P H A B A S S
A J B A O K C R
N E E D L E S T R I C K L E
A T U T O T E
R A S T E R I N T E R V A L
    
```

## DOWN

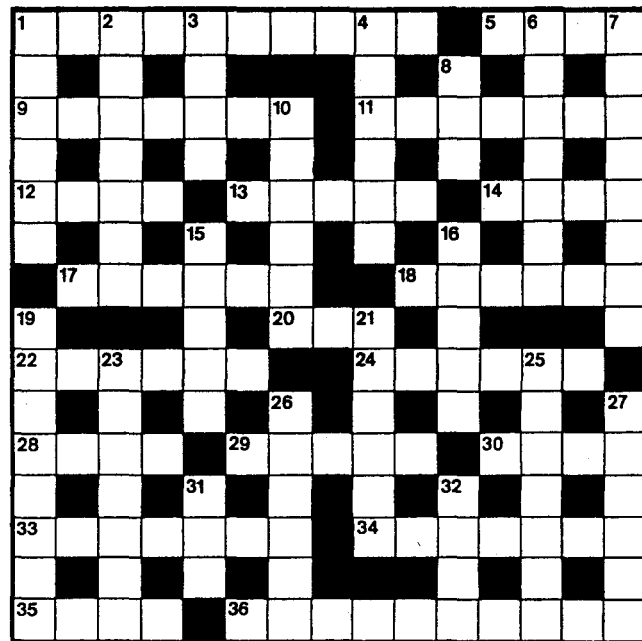1. Items activated in security systems. (6)
2. Type of logical system. (7)
3. Memories. (4)
4. Residual wave. (6)
6. Mineral located with magnetometer. (4,3)
7. Part of SSB transmission. (4,4)
8. Light-sensitive organ. (3)



10. Said of operated power switch. (6)
15. Inert gas. (5)
16. Australian Antarctic research station. (5)
19. Said of mobile phone network. (8)
21. EA's shortwave columnist, Arthur ----. (6)
23. Voltage. (7)
25. Passage taken from composition. (7)
26. Audible alarms. (6)
27. Directionless physical quantity. (6)
31. Unit of illumination. (3)
32. Type of scale used in balancing conditions. (4)



Electronics Australia's

# Professional Electronics

S ♦ U ♦ P ♦ P ♦ L ♦ E ♦ M ♦ E ♦ N ♦ T

**PRODUCT REVIEWS:**  
HAMEG'S MODULAR SYSTEM  
8000 TEST INSTRUMENTS,  
IMPROVED ACTIVE SPEAKERS  
FOR MULTIMEDIA PC'S,  
BASSBOX 5.1 CAD SOFTWARE



WITH THE NEW PROFLINE 2000 THE EMISSIONS TEST SYSTEM FROM HAMEG  
NOW HAS A 100% ULTRA-PURE AC POWER SOURCE WITH A BUILT-IN  
ANALYSER TO CHECK FOR COMPLIANCE TO IEC 1000-4 AND IEC 1000-3

# NEWS HIGHLIGHTS

## CYBEC WINS VIC PREMIER'S AWARD

Melbourne based Cybec, which produces the highly regarded computer virus protection program VET, has been awarded the Victorian Premier's Award for outstanding technological development. The Award was presented by Premier Jeff Kennett to Cybec founder Roger Riordan, at the recent Telstra and Victorian Government Small Business Awards evening.

Founded six years ago, Cybec has also received independent acclaim for VET by the highly regarded virus publication *Virus Bulletin*, which gave it a 98% rating — ahead of McAfee's Viruscan, Virus Buster, Central Point Anti-Virus, F-Prot, IMB Anti-Virus, Microsoft Anti-Virus and Norton's Anti-Virus.

Major Australian users of VET include the Commonwealth Bank of Australia, Westpac Banking Corp, NSW and Victorian TAFEs, and BHP. (Smaller users include *Electronics Australia!*)

## IREE LINKUP TO HONOUR MARCONI

On December 12, 1901, on Signal Hill in St John's Newfoundland, Guglielmo Marconi received a signal (the Morse letter 'S') transmitted from Poldhu in Cornwall (UK) — the first demonstration of long distance radio communications. To commemorate the centenary of his first transmission in December 1895, the IREE Society Hobart Local Area Committee has planned a 'multimedia' linkup between Hobart and St John's during its annual Radio Foundation Day Dinner, on December 12, 1995.

The main planned linkup is via HF radio, where Richard Rogers VK7RO will have attempted to make a Morse contact on 7018kHz with radio station VO1AA operated by the Society of Newfoundland Radio Amateurs, in

Cabot Tower on Signal Hill — close to the longest possible transmission path on Earth. In addition it was planned to be on contact with St John's via the

Peter Jensen VK2AQJ, who has contributed to *EA*, is an architect, town planner and long-time radio amateur with a deep interest in radio history. In his book he describes both the work carried out by Marconi and the more important places in which it was carried out, linking the narrative together with his own experiences in visiting them. A section at the rear explains how he made replicas of some of the more important early radio equipment, and gives sufficient information to allow the reader to make their own.

All books which received the Book Awards are apparently reviewed in the December 1995 issue of *Scientific American*.


## COMPUTER SHOW SUB WINNER

Winner of the 12-month free subscription to *Electronics Australia* at the recent Brisbane Computer Show was Mr Phillip Kay, of Abstract Lighting in Deception Bay, Queensland. Our congratulations to Mr Kay, and we hope he finds the issues of interest and value.
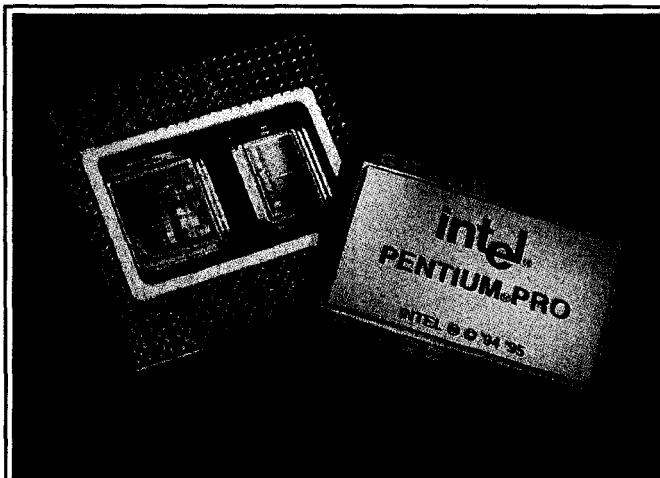
## CD-I PLAYBACK BOARD FOR PC'S

Philips is shortly planning to introduce a plug-in board for IBM-compatible PCs, which allows the playback of all CD-i, Video CD, CD Audio, Photo CD and Digital Video titles. The board effectively converts the PC into a fully functional and user friendly CD-i/Video CD player.

Since the board performs all of the necessary multimedia functions independently of the CPU, it can be used in machines with CPUs between a 386SX/16MHz and a Pentium with the same image quality and speed. All CD-i titles run directly from the CD and do not use hard disk space or system memory. MPEG quality Digital Video, Video CD and CD-i Digital Video titles are



Intel's new Pentium Pro processor chip itself measures around 13mm sq., but is packaged together with a 256K or 512K Level 2 cache memory chip measuring almost as much. Both are made using 0.6 micron technology, and operate from three volts. The power dissipation is around 30 watts!

Internet, by email and also using the real time, interactive 'talk' Unix program. Links via normal and cellular phones were also planned.

Organiser of the event was IREE Vice President and Councillor David Edwards, a former *EA* staff member now working for the CSIRO Division of Oceanography. As this issue went to press before the event, we are unable to report on its success. However we'll try to give details next month.

## JENSEN BOOK WINS AWARD

Australian author Peter Rolf Jensen's book *In Marconi's Footsteps: Early Radio*, published by Kangaroo Press, has won one of the 1995 Scientific American Young Readers Book Awards. The awards are newly established by the highly regarded US journal *Scientific American*, and are designed to recognise outstanding achievements in communicating scientific or technical topics to a youthful audience.

provided in theatre-quality images.

The CD-i/PC board also comes with an IDE CD-ROM drive interface.

Philips has also developed a CD-i based Internet access package, which allows users with a CD-i player and colour TV receiver to gain convenient access to the Internet and World Wide Web. The CD-Online package contains an CD-i disc and a 14.4kb/s modem, and the disc software allows automated login to the nearest Internet access provider. CD-Online also maintains a set of WWW home pages, offering user support information and hypertext links to other net sites.


## FREE EMC NEWSLETTER

Schaffner's free EMC world 12-page newsletter is distributed every three months and covers many important EMC issues that are relevant to the new mandatory standards being introduced by many countries around the globe.

A valuable feature is the centre lift out guide to Electromagnetic Immunity Standards — 'Standards UPDATE' which lists the types of EMC test, the relevant IEC test number and a brief description of the test parameters.

Other issues commonly covered are EMC instrument calibration/certification, new products, testing short cuts, world EMC news events and seminars, and application notes.

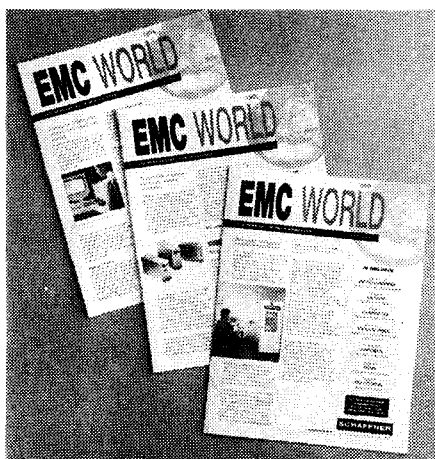For further information circle 230 on the reader service coupon or contact



Westinghouse Industrial Products, Locked Bag 6, South Melbourne 3205; phone (03) 9676 8888.

## CHURCHILL TRUST INVITES APPLICATIONS

Each year the Winston Churchill Memorial Trust awards a number of individual Australians with Churchill Fellowships, which fund approximately three months of overseas travel for study purposes. In 1996 the Trust will be financing the study trips of some 86 Australians in this way.

Applications are now invited for the 1997 Churchill Fellowships, which are open to all Australian residents. Most require no academic or other formal qualifications, as merit is the primary test.

For further information and applications forms, send a stamped and self-addressed 24 x 12cm envelope to:

Application Forms,  
The Winston Churchill Memorial Trust,  
218 Northbourne Avenue,  
Braddon, ACT 2612.

Applications and references close on February 29, 1996.

## US STUDY LINKS LF FIELDS & CANCER

A report prepared for the US National Council on Radiation Protection by a committee of leading experts in electromagnetic fields has recommended that safety limits for exposure to low frequency fields should be lowered to a level 5000 times smaller than the currently accepted international limits. The report was funded by the US Environmental Protection Agency.

Chairman of the committee was Professor Ross Adey, an Australian neurologist at the Veterans Affairs Medical Center in Loma Linda, California. Professor Adey is reported in *New Scientist* as saying that there is now "a powerful body of impressive evidence" to show that very low exposure to EMF's has subtle, long term effects on human health. "The sensitivity of the brain and its mechanisms to these fields is the key to understanding this issue", he added.

The safety limit recommended in the


## SONY RELEASES INTERACTIVE 'PLAYSTATION'

Sony Computer Entertainment has launched in Australia its long awaited 32-bit, CD based video games/entertainment system, the PlayStation. The company says PlayStation has the power to provide realtime action, 3D graphics and CD quality stereo sound, and is expected to emulate the huge success of Sony Walkman 24 years ago.

"Sony is widely recognised as a leader in entertainment technology, having invented CD-ROM, co-invented the audio CD and was the first with innovative products like the Walkman, Trinitron television, Camcorder and Discman. This trail of innovation now leads directly to PlayStation, which aims to shape the future of interactive home entertainment," said Michael Ephraim, General Manager of Sony Computer Entertainment in Australia.

"Hundreds of millions of dollars have been injected into the six year development of PlayStation, which makes it as important as the launch of the Sony Walkman in 1972. The investment in PlayStation demonstrates how serious Sony is to grow, and establish global leadership of the interactive home entertainment market."

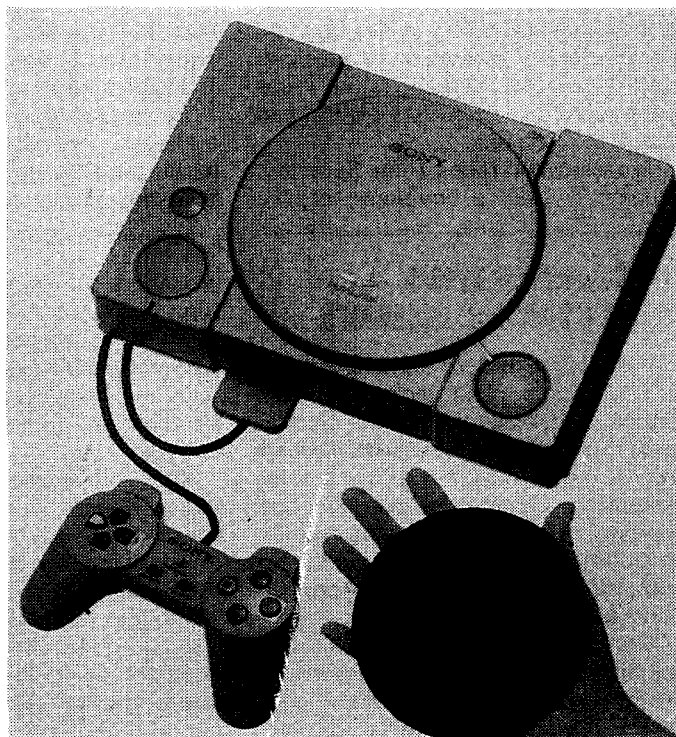Retailing for \$695, the PlayStation is packaged with a sample disc of new game clips and playable demos. It employs a 32-bit RISC processor (the first time a RISC chip has been used in a games machine), runs at 500MIPS (millions of instructions per second), juggles 1.5 million polygons per second and is JPEG compatible for full motion video sequences.



## NEWS HIGHLIGHTS

report is 0.2 microteslas, whereas that currently recommended by the World Health Organisation is 1000uT. The field around many current domestic appliances exceeds 0.2uT at distances of less than 300mm, while the field beneath many high voltage transmission lines is typically between 8 and 40uT depending upon the voltage level.

### VIRTUAL ELECTRON MICROSCOPE LAB


For more than a decade, scientists have travelled to Berkeley in California to use the unique high voltage electron microscope at Ernest Orlando Lawrence Berkeley National Laboratory. Now the Berkeley Lab is taking the facility to the user.

No, the three-story-tall microscope (the most powerful in the USA) has not been put on wheels. Rather, the Laboratory has created a set of interactive, online computing tools that will allow scientists to manipulate the instrument, conduct experiments, and view images from their own offices, via the Internet.

In-situ electron microscopy — inducing and observing changes to a sample in the microscope — had never been done remotely until a demonstration by Berkeley Lab scientists last August.

The presentation, during the Microscopy Society of America's annual international meeting in Kansas City, caused a minor sensation, so much so that a repeat demonstration was demanded by scientists who had missed the first one.

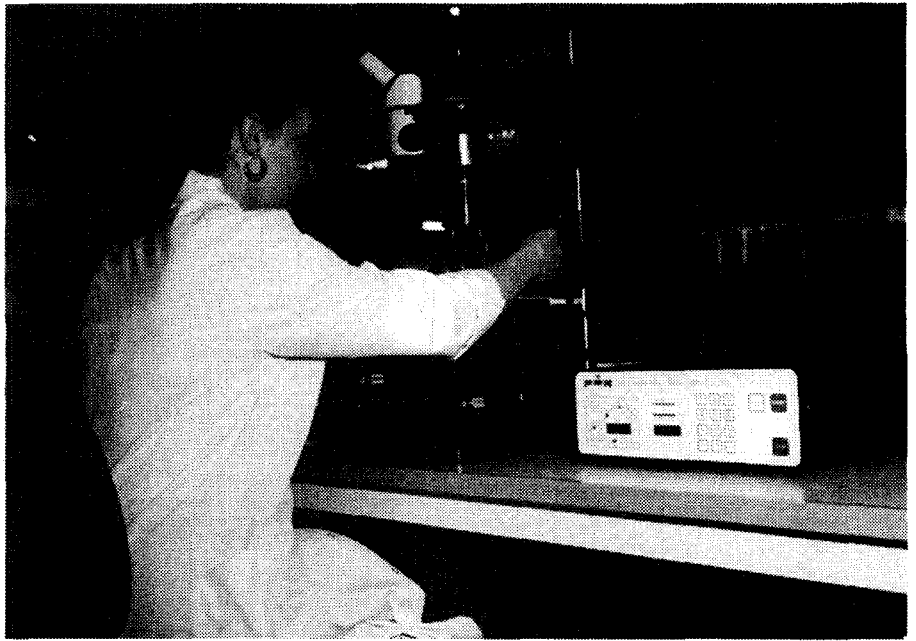Two thousand miles from Berkeley, researchers used a computer to take



**UK company PDR Microelectronics has announced the sale of its one thousandth focused infra-red (FIR) SMT repair system, since it introduced this technology in 1986. The machine was purchased by Fujitsu Telecommunications Europe Ltd.**

control of the microscope, heat an advanced alloy specimen, and observe the ensuing progression of structural changes on the computer monitor.

The team bringing the electron microscope online is led by computer scientist Bahram Parvin and Michael O'Keefe, the deputy head of the lab's National Center for Electron Microscopy. Other team members include John Taylor, Brian Crowley, Doug Owen, Ken Westmacott, Bill Johnston, and Uli Dahmen.

To make remote control of the microscope possible, Parvin's team is automating onsite the positioning and focusing of the microscope. This is

being made possible through the development of advanced computer vision algorithms.

Experimenters at remote locations will be able to 'drive' the microscope. They will be able to change magnification, scan the sample, alter its orientation, and trigger a range of experimental conditions. Collaborators will do this through a computing environment that includes the necessary video-conferencing tools.

A short movie demonstrating computer vision tracking of DNA can be seen on the World Wide Web at the address of [http://www-itg.lbl.gov/ITG.hm.pg.docs/VISION/DNA\\_track.mpg](http://www-itg.lbl.gov/ITG.hm.pg.docs/VISION/DNA_track.mpg).

### COCHLEAR-SIEMENS FORM HEARING ALLIANCE

Australia's Cochlear Limited, a leader in Cochlear implant technology, has formed a collaboration with German based Siemens Audiologische Technik GmbH, the world's leading hearing instruments company. Under the new agreement the companies will evaluate possibilities to cooperate in marketing, sales, distribution and R&D projects which have mutual benefit.

"Our global agreement demonstrates that Siemens is expanding its horizon, to better service hearing impaired customers", according to Brad Carlisle,

Managing Director of Brisbane based Rexton, the Australian hearing technology arm of Siemens. "For example, Siemens has formed over 20 joint ventures in China alone, so we can help Cochlear into the world's biggest potential market."

"The collaboration with Siemens will help Cochlear re-enforce our preeminence in cochlear implant technology", says Albert Sorrell, general manager, Asia Pacific region, Cochlear Limited. "With the recent approval of cochlear implants for the severely hearing impaired, this collaboration can help us reach, and grow, this newest segment of our business".

Among specific areas in which Cochlear and Siemens will collaborate are the development and communication of a joint marketing positioning strategy and joint participation in congresses, workshops and presentations. In the R&D area, the companies plan to work on joint research projects leading to the development of new and improved products and technologies.

Cochlear Limited has offices located throughout the world which provide comprehensive service and support. It is the world leader in multi-channel cochlear implant technology and manufactures the Nucleus 22 Channel Cochlear Implant System.

## FLUKE METER SAFETY RECALL

Philips Scientific & Industrial is advising owners of certain models of Fluke digital multimeters to return the meters for a safety modification. The Fluke meters concerned were manufactured after July 1994 and can be identified with the model numbers 70, 73, 75, 77, 21 and 23, with serial numbers in the range from 60990000 to 6375200.

A malfunction may arise in the affected units when used to measure 400V DC or greater. The meter may go into a lock-up state and indicate a reading of (or near) zero.

The safety modification involves the installation of a special capacitor, and Philips Scientific & Industrial is offering a free calibration for those affected meters which are returned for the modification. Multimeters that have the modification made will be marked with the letter 'R' near the serial number.

Telephone enquiries on this modification are being handled by Paul Tamone at Philips Scientific & Industrial on (02) 888 0491.

## PHILIPS RELEASES CD-ERASABLE SPECS

Philips Electronics has distributed the proposed specifications for an erasable Compact Disc format, indicating significant progress in enabling companies to bring CD-Erasable products to market in 1996.

The release of the specifications came just five months after 10 major manufacturers — IBM, Ricoh, Hewlett-Packard, Mitsubishi Chemical Company (MCC), Mitsumi Electric Co., Matsushita Kotobuki Industries (MKE), Sony, 3M, Olympus and Philips announced their support for the development of an erasable CD format for data applications.

With a data capacity of up to 680MB

per disc, CD-Erasable provides additional benefits to application environments currently served by CD-Recordable products.

CD-Recordable discs provide more permanent data storage, while CD-Erasable allows data to be updated and disc space to be reused. CD-E drives will be capable of reading all existing CD formats. They can also write and read CD-Recordable media and, of course, these products will be able to read, write and overwrite CD-Erasable discs.

## FIRST COMMERCIAL SCALE POWER PLANT

What is claimed to be the first commercial scale solar power station in New South Wales has begun operation in Nimbin. Called the Sunpower Project, the 10 kilowatt facility is said to represent a significant milestone in the development of a new Australian industry which will allow customers to choose environmentally sensitive electricity for their power requirements.

Solar generated electricity from the Sunpower Project will be available for sale to North Coast residents from early in 1996. Mr Greg Don, the Retail Sales Manager with NorthPower said that as demand for solar generated electricity grew, the Sunpower Project would be expanded and other projects initiated. NorthPower distributes electricity from mid north coast and far north coast of New South Wales to the Queensland border and west to Bourke.

Opened by Mr Harry Woods, MP on behalf of Federal Industry Science and Technology Minister Senator Peter Cook, the Sunpower Project is the result of a two year research and development project undertaken by a consortium which includes Essex Electrical Pty Ltd, Hundell Corporation, NorthPower, the Department of Primary Industry and Energy and the Electricity Association of NSW.

## TECH-RENTALS NOW ISO 9002 CERTIFIED

Tech-Rentals has implemented a quality management system certified by Lloyd's Register Quality Assurance (LRQA), meeting the ISO 9002:1994 standard.

The standard assures customers of an efficient and reliable management system, designed to ensure consistent levels of customer service.

A major goal of the company is to maintain a high level of flexibility and service in meeting customer needs, which in the rental market are often urgent.

At the same time the planning of the quality system has involved a complete review of Tech-Rentals' calibration procedures and facilities. This has been a major task given the rental inventory size of 900 different instrument models and over 7000 assets.

Managing Director Paul Jindra stated "Tech-Rentals had its foundations 20 years ago as a third party service company. The adoption of the ISO 9002 for our quality system is a logical step in continuing to meet our customers' needs for quality products both in the instrumentation and computer fields."

## AUST. FIRE ALERT SYSTEM FOR TELSTRA

Telstra has installed a world recognised, Australian designed fire alert system to ensure the security of its telecommunications network.

"We need the earliest indication of a possible fire, particularly as new technology such as fibre optics and electronic switches have enabled us to concentrate more and more telephone traffic into a single cable and switching area", Telstra's National Fire Co-ordinator, Mr Rod Sinclair. "If a fire was to occur now, it would affect many more people and businesses than it would have just 10 years ago," he added.

Telstra has selected an Australian designed early system called VESDA. "By using VESDA technology we can detect a potential fire during the pre-combustion period and act on the threat before it progresses further," Mr Sinclair said.

With the telecommunications cable tunnels, some of which are located 30m beneath the roadway, the VESDA. "By using VESDA technology we can detect a potential fire during the pre-combustion period and act on the threat before it progresses further." Mr Sinclair added. ♦

## NEWS BRIEFS

- **TGE** has been appointed as the Australian distributor for the Data Guard Electronics range of uninterruptable power supplies.
- Glenn Ward has been appointed product marketing manager of electronic test and measurement instruments for **Nilsen Technologies**.
- The 12th international computer expo **Computer '96** will be held at the Hong Kong Convention and Exhibition Centre, May 15-18 1996. For details phone (852) 2865 2633.
- Kenwood Electronics has appointed **Nilsen Technologies** as the exclusive distributor for Kenwood test and measurement instruments in Australia.
- Mr Ron Spithill, managing director of **Alcatel Australia**, has been appointed to the Board of the worldwide Alcatel group's telecommunications operations. This is the first time an Australian has held such a position.
- **Amber Broadcast** has been appointed as the exclusive distributor for Pro-Bel signal switcher, routing and signal management products.

## Product Review:

# HAMEG'S MODULAR INSTRUMENT SYSTEM

Almost 10 years ago, European test instrument maker Hameg introduced its innovative and cost effective Modular System 8000, which has been very popular. Here we take a 'hands on' look at the system, which Hameg has steadily expanded...

by JIM ROWE

With its headquarters in Frankfurt, Germany, Hameg has been designing and manufacturing high quality, but 'down to earth' and competitively priced test equipment for over 30 years. Nowadays it has R&D and manufacturing facilities not only in Germany, but in France and the USA as well, and also sales offices in Spain, the UK and Hong Kong — together with distributors in other countries (like Kenelec in Australia), this has allowed the company to build up a substantial international business and reputation — albeit in a fairly low key fashion.

Currently its main range of instruments includes both analog and digital scopes, spectrum analysers, system multimeters and counters, function and RF generators, and a GPS-based time and frequency standard. There's also the Modular System 8000, an innovative range of relatively low cost instruments based on a compact two-slot 'mainframe' and a range of plug-in functional modules.

Since its introduction by Hameg about eight years ago, the Modular System 8000 has apparently been very well received — with over 100,000 units sold worldwide to date. And the range of modules has steadily expanded, to the point where there are now some 12 plug-in modules ranging from a 4.5-digit DMM to a semiconductor device curve tracer.

There's also a 'blank' module, for users who want to build their own custom module for use in the system.

The foundation of the system is the HM8001-2 mainframe unit, which is a sturdy case assembly measuring 285 x 365 x 75mm (W x D x H) — virtually the same external dimensions as Hameg's HM8100 series of system-level instruments. In contrast with the latter instruments, though, the front section of the HM8001-2 case is largely

empty, with two 'full height/half width' cavities to accept a pair of the instrument modules.

At the rear of the case is a built-in dual power supply, with 22-way edge connectors in the rear wall of each cavity to supply power to the modules. Although the two power supplies share a common power transformer they are otherwise quite independent, delivering electrically isolated power for each of the two module 'slots'. Each supply provides 8V AC at up to 0.5A, regulated 5V DC at up to 1A, and two separate regulated DC sources capable of delivering up to 20V at 0.5A.

An ingenious linking system allows each 22-way connector to be set up for 'programming' that slot's two adjustable DC regulators for any of six supply voltages, from 5.2V to 20V — or even disabled, so that the basic AC voltage from that transformer winding is fed directly to the module. This means that any module can configure the power supply system to suit its particular needs.

The power supply is rated for a total loading of 36W, and since most of the plug-in modules draw no more than 11W, the supply has more than enough capacity. The only exception is the HM8040-2 Triple Power Supply module, which can draw up to 25W when fully loaded. Because of this, Hameg specifies that only one HM8040-2 module can be plugged into any particular mainframe module at a time, to prevent overloading. However a power supply module can be combined with any other module in the same mainframe, as the total loading will be no more than the rated 36W.

Another innovative aspect of the HM8001-2 mainframe is its power switch, which is located inside the rear power supply to avoid running mains wiring alongside the module slots.

However to provide convenient front-panel control, the switch actuator is 'extended' forward via a 2mm rod inside the mainframe's centre partition, and provided with a narrow but easy to operate red 'pushbutton' — just visible in the photo, in the centre of the front-panel divider. An elegant solution!

The regulator chips for the mainframe power supplies are provided with husky finned heatsinks, mounted on the rear of the case along with the fused IEC mains plug and 230V/115V mains voltage selector. The case itself is provided with mounting feet, with the two front feet also fitted with tilting extensions for benchtop use.

## The modules

As mentioned earlier, there are currently 12 different plug-in modules in the Modular System 8000 range. Here are brief details of each:

**HM8011-3 Digital Multimeter:** This is a 4.5-digit manual ranging instrument (maximum indication 19999), with a basic DC accuracy of 0.05%. It provides a total of 28 ranges, with a maximum resolution of 10uV, 10nA and 10mW. Other features include true RMS AC measurements (up to a crest factor of seven), and current measurements up to 20A DC or AC, short term (10A continuous). Indication is via LED readouts.

**HM8014 Milliohm Meter:** This is designed to measure low resistances accurately, from 0.1mW to 20kW. Four-wire measurements are possible using an plug-in Kelvin probe set (included). It has a 3.5-digit LED readout, five manual ranges, a diode test function and an audible continuity indicator.

**HM8018 L-C Meter:** This provides for accurate digital measurement of inductance and capacitance, via a 3.5-digit LED readout. There are 24 manually selected ranges, measuring inductance from 200uH to 200H, equivalent series

resistance (inductors) from 20 $\Omega$  to 200k $\Omega$ , capacitance from 200pF to 200 $\mu$ F and equivalent shunt conductance (capacitors) from 20 $\mu$ S to 200mS. Three test frequencies are used for the various measurement ranges (160Hz, 1.6kHz and 16kHz), and the maximum readout resolution is 0.1pF, 0.1 $\mu$ H, 10mW and 0.01 $\mu$ S. The basic rated accuracy is 0.5%.

**HM8021-3 Universal Counter:** This module provides a complete multi-mode counter with a frequency range from DC to 1.6GHz. Input channel A covers from DC to 150MHz with 1M/40pF input impedance, while channel C covers from 100MHz to 1.6GHz with nominal 50 $\Omega$  input impedance. Input sensitivity is 20mV, and the LED readout provides eight digits plus exponent. The TXCO timebase has a rated stability of  $5 \times 10^7$ .

**HM8026 Wow & Flutter Meter:** This module was developed for the measurement of speed drift, wow and flutter in analog magnetic recorders and record turntables. It can use crystal-controlled test signals of either 3000Hz or 3150Hz, and provides a three-digit LED readout with a of 0.001% for wow and flutter, or 0.01% for speed drift. Results are calculated using the two-sigma technique.

**HM8027 Distortion Meter:** Measures total harmonic distortion in the audio range, between 20Hz and 20kHz in three bands. A three-digit LED readout pro-

vides a maximum resolution of 0.01%. The 'fine tuning' for fundamental nulling is automatic, and there is an output for monitoring the residual components on a scope.

**HM8030-5 Function Generator:** A versatile signal source for testing and experimentation, capable of generating sine, square or triangular waveforms over the frequency range 0.05Hz - 5MHz in eight decade ranges. Output frequency is displayed on a four-digit LED readout, and output voltage (maximum 10V into 50 $\Omega$ ) is adjustable over a 60dB range via switched and variable output attenuators. The module can also perform frequency sweeping over a 100:1 range.

**HM8032 Sinewave Generator:** Based on a Wein bridge RC oscillator, this module covers from 20Hz to 20MHz with a distortion of less than 0.2% below 500kHz and an output flatness of less than 0.2dB. Output frequency is displayed on a four-digit LED readout. Both 600 $\Omega$  and 50 $\Omega$  outputs, with a maximum output voltage of 1.5V RMS into 50 $\Omega$ ; output level is adjustable over a 60dB range via switched and variable output attenuators.

**HM8035 Pulse Generator:** This module produces pulses with less than 3ns rise/fall time, over a frequency range from 2Hz to 20MHz plus manual one-shot mode. Pulse width is continuously

adjustable from 20ns to 200ms, with a LED indicator to warn when width exceeds repetition period. Two separate main outputs have independently adjustable polarity and amplitude (0.8 - 5Vp-p) into 50 $\Omega$ , with a trigger output also provided (leading by 10ns).

**HM8037 Low Distortion Generator:** A high quality audio sinewave generator providing highly stable signals adjustable in frequency between 5Hz and 50kHz, with THD less than 0.01%. Output frequency is displayed on a three-digit LED readout, while output level (maximum over 1.5V RMS into 600 $\Omega$ ) is adjustable over a 60dB range via switched and variable attenuators.

**HM8040-2 Triple Power Supply:** A compact variable supply with digital metering, for laboratory testing and educational work. Three independent, fully floating DC supplies: one nominally fixed at 5V/1A (actually adjustable +/- 0.5V), while the other two are separately adjustable 0 - 20V at 0.5A, with adjustable current limiting. Each of the two variable supplies has a three-digit LED readout, switchable between output voltage and current. All outputs can be connected in series if required.

**HM8042 Curve Tracer:** This micro-processor-based module converts any oscilloscope with X-Y display capability into a system capable of displaying the characteristic curves of semiconductor devices such as diodes, transistors, FETs and thyristors. Provides on-screen display of up to five curves, with cursors for parameter value readout and auto calculation of dynamic parameters. Offers three collector/drain voltage ranges (2V, 10V and 40V); three collector/drain current ranges (2mA, 20mA and 200mA); and three power ranges (40mW, 400mW and 4W).

## What we found

Thanks to Hameg's Australian distributor Kenelec, we were able to examine and try out an HM8001-2 mainframe unit with a total of four sample modules: an HM8018 L-C Meter, an HM8027 Distortion Meter, an HM8032 Sinewave Generator and an HM8035 Pulse Generator.

We were very impressed with the overall 'build quality' of both the mainframe unit and the modules. They were nicely made, and also revealed that a good deal of thought and planning had gone into both the electrical and mechanical aspects of their design. For example while both mainframe and

*Continued on page 137*



## Construction Project:

# A POST test card for IBM PCs

When you're trying to track down strange faults in a PC, you can save a lot of time and trouble by using a 'POST Card' to display the codes generated by the PC's own inbuilt Power-On Self Test routine. This article describes how to build your own low cost POST card using an Altera EPM7032 EPLD device.

by DAVID N. WARREN-SMITH, CPENG

Some readers of my article on the Altera system, published in the December 1994 issue of *Electronics Australia* may have acquired a free copy of Altera's First Step evaluation software. A neat project that is within the capabilities of this software is a POST test card for IBM compatible PCs, as presented here.


Similar cards have been described in overseas electronics magazines, as listed in the references at the end of this article. In this article I will give enough detail, including the complete source code, for the electronics enthusiast to construct their own POST test card, using Altera's low cost EPM7032 device.

This device can be compiled with Altera's First Step software and consequently any one with a copy of this software and a compatible programmer can start experimenting with this device.

The First Step software runs in MS Windows and provides an integrated environment consisting of a text editor, a compiler and a hierarchy manager.

To use the software you first enter the source code with First Step's text editor, then you set the project name to the name of the source code file, which generates a .ini file, and then you call up the compiler which generates a report file (.rpt) and a programmer (.pof) file amongst others. The .pof and .ini files are required by the programmer hardware to program the device.

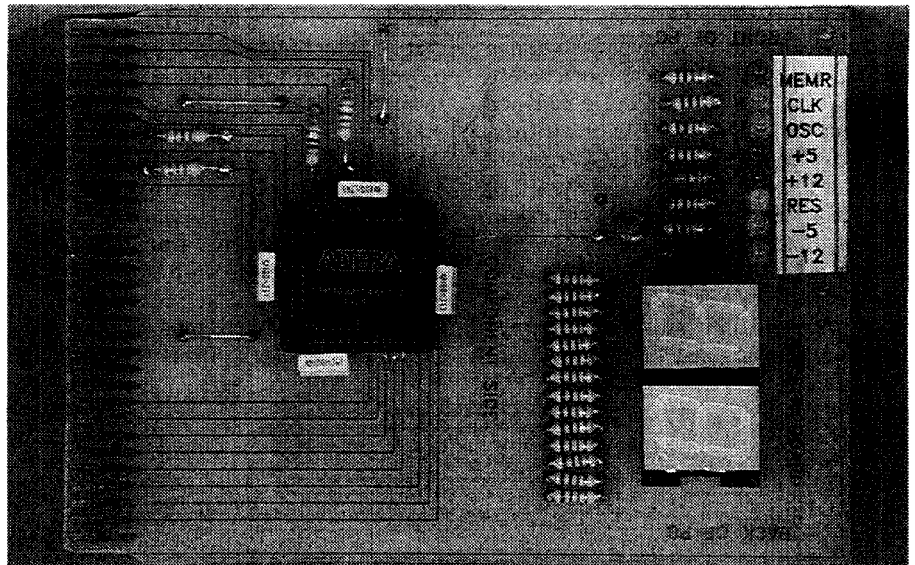If you don't have a copy of First Step you can get your own copy from the Bulletin Board Service operated by Veltek Australia, Altera's Australian distributor.



The numbers for Veltek's BBS are (03) 888 7776 in Melbourne and (02) 713 7278 in Sydney. Be prepared to download a fairly large file.

**If you would like to construct the project but do not have access to a programmer, I am prepared to supply a programmed 7032 device at a nominal charge for the service. My phone number and address are given in the source code listing later in the article.**

A computer club friend of mine, Eric Patching, and myself have built ourselves these test cards. Eric came across an article in one of the UK electronics magazines (see references) for a PC POST (Power On Self Test) test card.


The idea of the test card is that if you have an old AT type PC motherboard which may have stopped working, you plug the POST test card into the motherboard and power up. The test card has

a two digit seven-segment LED display which displays a two digit hexadecimal number. As the PC goes through its POST testing routine it writes a number at a specified I/O address prior to each test — which is read, stored and displayed by the test card. The PC halts if a test fails.

If the POST test does not run through fully, the last number showing represents the last test run and hence the fault. You look up the number in a chart to find out the cause of the fault. The test card does not require a video or other card in the PC.

The test card in the original magazine article<sup>1</sup> required three PAL chips and Eric asked me where he could get them. I pointed out that I could program the whole requirement into a single EPM7032 device. Eric made up the printed circuit cards for us



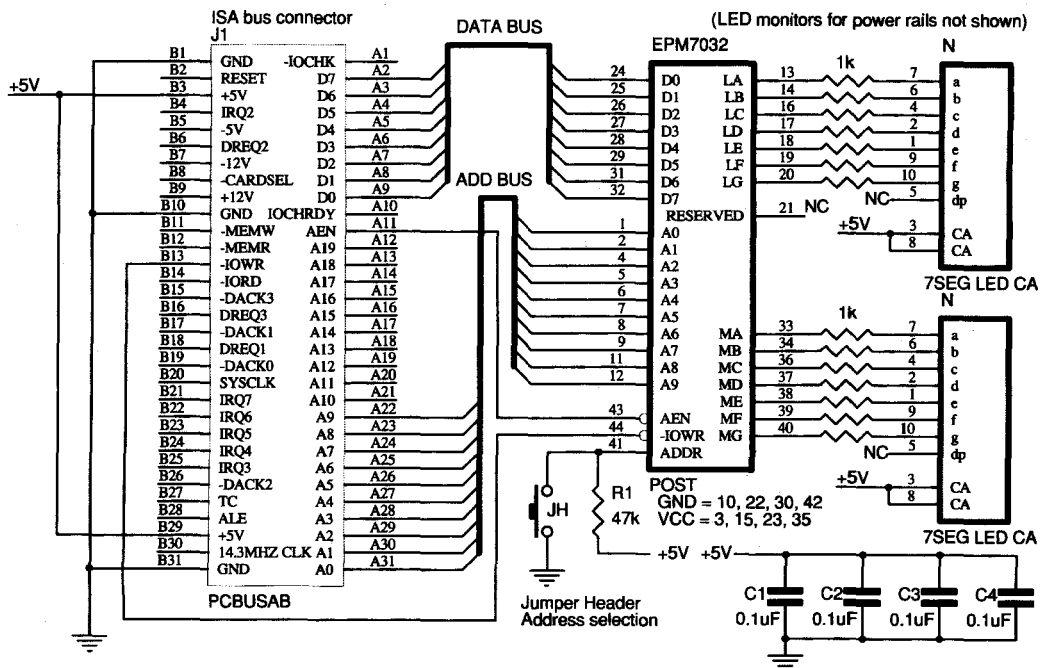

**Fig.1: The schematic for the POST card. As you can see, it's surprisingly simple, thanks to the use of a pre-programmed EPLD device. The only other components needed are a pair of seven segment displays, some LEDs and a handful of resistors and capacitors.**

and I provided the 7032 devices. We duly got together when a card was ready to test and we found it to be fully operational.

I think this is a plus for the Altera 7000 devices, considering the ease with which they provided a one-chip solution. The 7032 device directly interfaces with the ISA bus and directly drives the seven-segment common anode LED displays quite happily through current limiting resistors.

In another magazine article<sup>2</sup> describing a POST test card, the author has used

eight discrete small-scale ICs to achieve the same result.

In yet another article<sup>3</sup> the author has used four ICs including two GAL chips, but this article has made provision for six possible addresses for the diagnostic address, for different BIOS versions.


This article is also the most comprehensive of the three articles and lists available commercial hardware and software for PC diagnostics.

The test card that Eric and I have constructed gives a selection of the two

most common addresses. It could probably be modified to give all six addresses, but we haven't tried this.

For deciphering the codes that come up in the POST test any of the articles listed give details.

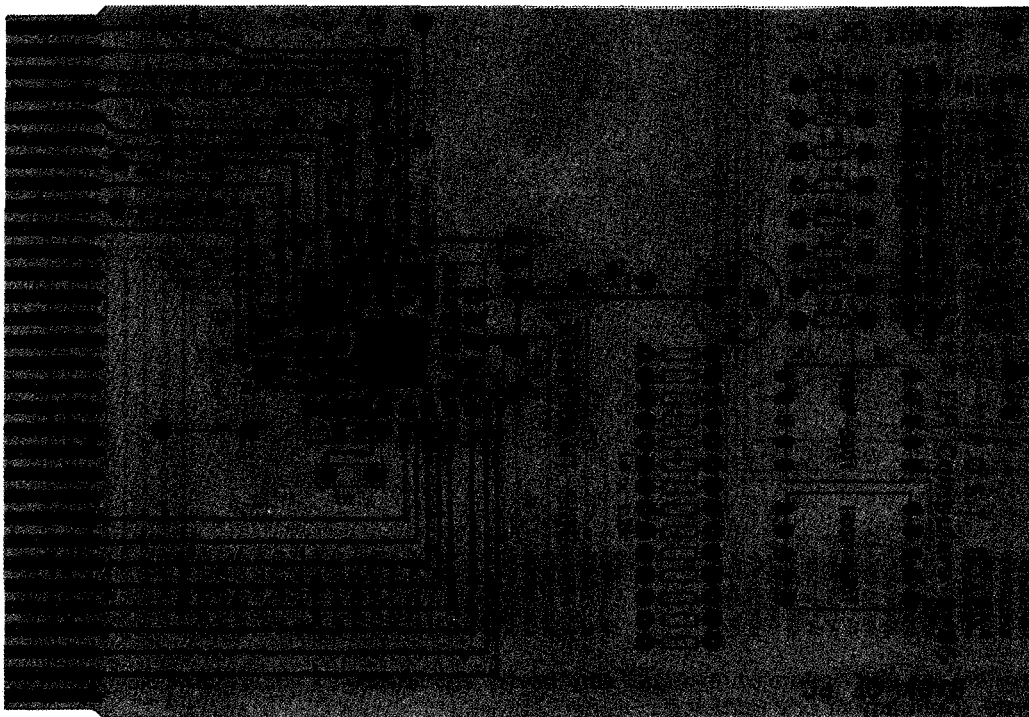There is a shareware program called Post Code Master (PCM) that provides quick look up for both POST codes and BEEP codes through a software program. It should be possible to get a copy of this program off a bulletin Board such as that operated by *Electronics Australia*. I found a copy on the 'SIM-



**Use this overlay diagram when you are wiring up your own POST card. The small three pin jumper header with the A and X labels is used to configure the card for use in AT or XT machines respectively.**

# A POST test card for IBM PCs

	0 = a,b,c,d,e,f 1 = b,c 2 = a,b,d,e,g 3 = a,b,c,d,g 4 = b,c,f,g 5 = a,c,d,f,g 6 = a,c,d,e,f,g 7 = a,b,c 8 = a,b,c,d,e,f,g 9 = a,b,c,d,f,g A = a,b,c,e,f,g B = c,d,e,f,g C = a,d,e,f D = b,c,d,e,g E = a,d,e,f,g F = a,e,f,g	a = 1,4,B,D b = 5,6,B,C,E,F c = 2,C,E,F d = 1,4,7,A,F e = 1,3,4,5,7,9, f = 1,2,3,7,D g = 0,1,7,C
--	--	--

Fig.4: How the decoding for the seven segment displays is derived. The actual decoding is performed in the author's program, of course.

TEL for DOS' CD-ROM, in the miscellaneous info section.

## Circuit description

The schematic of Fig.1 shows the basic circuit, which as you can see is very straightforward. It consists main-

ly of the 7032 and the seven-segment display devices plus current limiting resistors and decoupling capacitors.

Usually provision is made on POST cards for LEDs to monitor the supply rails and other key signals. These are also provided here, although they



have not been shown on the schematic. The LEDs monitor MEMR, CLK, OSC and RES, along with +5V, +12V, -5V and -12V.

Decoupling capacitors are placed near the four supply points on the PLCC socket. The jumper header makes provision for two addresses, one of which is 80H for the AT bus. The other is 60H, which according to reference 3 is for the XT bus.

The PCB design produced by Eric Patching is shown in Fig.2. As you can see, it is double sided, as cards have to be in order to connect to the contacts on both sides of the PC expansion bus sockets. The PCB wiring/overlay diagram is also shown (Fig.3), and using this along with the photograph should make assembly of the board very straightforward.
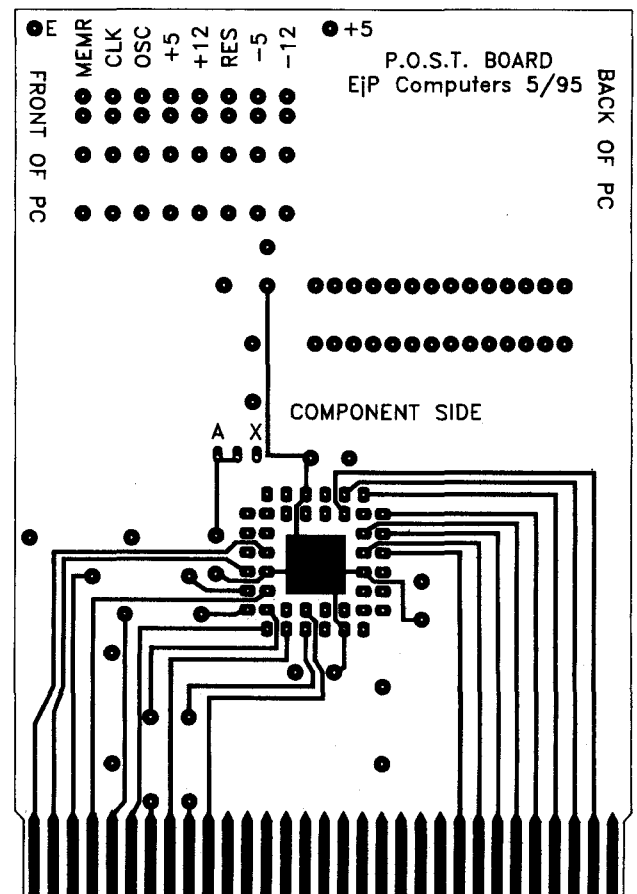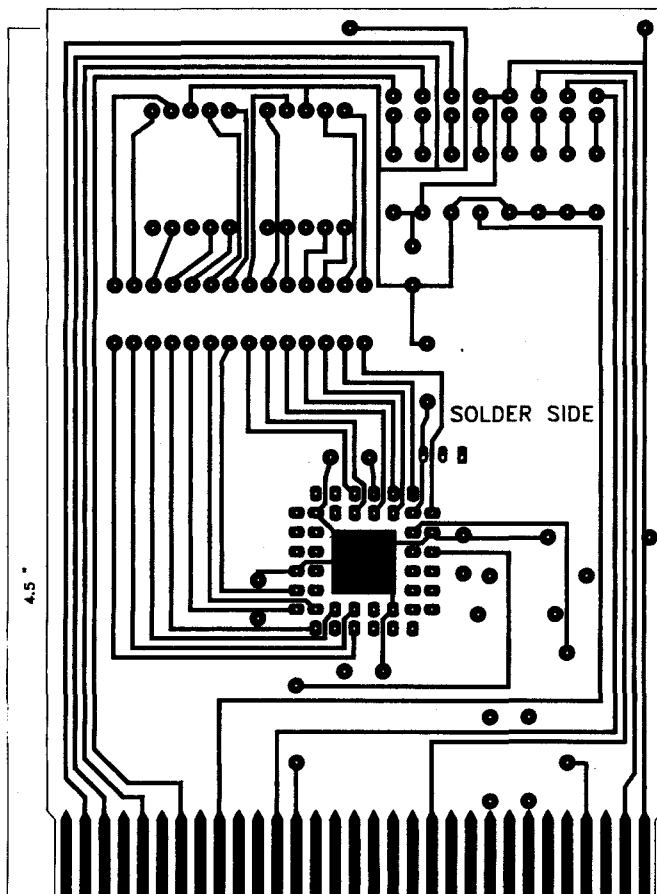
## EPLD source code

For those who would like to program their own EPLD device, the source code I have developed is shown in the box. It is commented to help in understanding it.



Here are the etching patterns for the top and bottom of the POST card board, reproduced as usual actual size for those who like to etch their own boards. (Courtesy of Eric Patching.)

## Source code for the POST EPM7032

Title "POST test card for PCs";

% File name: POST1.TDF

Started: 6 December 1994

Updated: 29 April 1995 (ADDR for selecting address added.)

Concept from: Electronics Today International, October 1994 Page: 22 - 27.

Coded by David N. Warren-Smith of Digital Logic Systems, South

Australia. PO Box 647, Elizabeth, SA 5112, Phone: (08) 255 2953

%

FUNCTION LATCH (D, ENA) RETURNS (Q);

DESIGN IS POST1

BEGIN

DEVICE IS EPM7032LC44-15T

BEGIN % This section assigns signals to the pins on the socket %

```
A0      @ 1      : INPUT ;
A1      @ 2      : INPUT ;
A2      @ 4      : INPUT ;
A3      @ 5      : INPUT ;
A4      @ 6      : INPUT ;
A5      @ 7      : INPUT ;
A6      @ 8      : INPUT ;
A7      @ 9      : INPUT ;
A8      @ 11     : INPUT ;
A9      @ 12     : INPUT ;
D0      @ 24     : INPUT ;
D1      @ 25     : INPUT ;
D2      @ 26     : INPUT ;
D3      @ 27     : INPUT ;
D4      @ 28     : INPUT ;
D5      @ 29     : INPUT ;
D6      @ 31     : INPUT ;
D7      @ 32     : INPUT ;
ADDR    @ 41     : INPUT ;
NALE    % or AEN % @ 43 : INPUT ;
NIOW    @ 44     : INPUT ;
LA      @ 13     : OUTPUT;
LB      @ 14     : OUTPUT;
LC      @ 16     : OUTPUT;
LD      @ 17     : OUTPUT;
LE      @ 18     : OUTPUT;
LF      @ 19     : OUTPUT;
LG      @ 20     : OUTPUT;
MA      @ 33     : OUTPUT;
MB      @ 34     : OUTPUT;
MC      @ 36     : OUTPUT;
MD      @ 37     : OUTPUT;
ME      @ 38     : OUTPUT;
MF      @ 39     : OUTPUT;
MG      @ 40     : OUTPUT;
```

END;

END;

SUBDESIGN POST1

( % This section is for declaration of inputs and outputs %

```
A[9..0] : INPUT; % Address inputs %
D[7..0] : INPUT; % Data bus inputs %
ADDR,   % Address select input %
NALE, NIOW : INPUT; % Address latch enable, IO write signal %
LA, LB, LC, LD, LE, LF, LG : OUTPUT; % 7 segment outputs for LS digit %
```

MA, MB, MC, MD, ME, MF, MG : OUTPUT; % 7 segment outputs for MS digit %

VARIABLE % This section is for declaration of internal variables %

LL[6..0] : LATCH; % A=0, B=1 ... G=6 %

LM[6..0] : LATCH; % Latches for POST data word %

STROBE : LCELL; % Internal address select %

BEGIN % This section is for logic equations %

% With ADDR = High address is 80H for the AT bus,

with ADDR = Low address is 60H for the XT bus %

STROBE = (A[9..0] == H"080") & !NALE & !NIOW & ADDR % Address 80H %

# (A[9..0] == H"060") & !NALE & !NIOW & !ADDR; % Address 60H %

% Insert the required second address in place of H"060" if different %

LL[.].ena = STROBE;

LM[.].ena = STROBE;

% The code on the data bus is translated to 7 segment code and stored  
in 7 latches for each digit %

LL0.d = !D3&!D2&!D1&D0 # !D3&D2&!D1&D0 # D3&!D2&D1&D0  
# D3&D2&!D1&D0;

LL1.d = !D3&D2&!D1&D0 # !D3&D2&D1&!D0 # D3&!D2&D1&D0  
# D3&D2&D1&!D0 # D3&D2&D1;

LL2.d = !D3&!D2&D1&!D0 # D3&D2&!D1&D0 # D3&D2&D1;

LL3.d = !D3&!D2&!D1&D0 # !D3&D2&!D1&D0 # D3&!D2&D1&!D0  
# D2&D1&D0;

LL4.d = !D3&!D2&D0 # !D3&D2&!D1 # !D3&D2&D1&D0 # D3&!D2&!D1&D0;

LL5.d = !D3&!D2&D1 # !D3&!D2&D0 # !D3&D2&D1&D0 # D3&D2&!D1&D0;

LL6.d = !D3&!D2&!D1 # !D3&D2&D1&D0 # D3&D2&!D1&D0;

LM0.d = !D7&!D6&!D5&D4 # !D7&D6&!D5&D4 # D7&!D6&D5&D4  
# D7&D6&!D5&D4;

LM1.d = !D7&D6&!D5&D4 # !D7&D6&D5&!D4 # D7&!D6&D5&D4  
# D7&D6&D5&!D4 # D7&D6&D5;

LM2.d = !D7&!D6&D5&!D4 # D7&D6&!D5&D4 # D7&D6&D5;

LM3.d = !D7&!D6&!D5&D4 # !D7&D6&!D5&D4 # D7&!D6&D5&!D4  
# D6&D5&D4;

LM4.d = !D7&!D6&D4 # !D7&D6&!D5 # !D7&D6&D5&D4 # D7&!D6&!D5&D4;

LM5.d = !D7&!D6&D5 # !D7&!D6&D4 # !D7&D6&D5&D4 # D7&D6&!D5&D4;

LM6.d = !D7&!D6&!D5 # !D7&D6&D5&D4 # D7&D6&!D5&!D4;

% Output logic (active low) is driven directly from the latches%

LA = LL0.q; % Least significant digit of POST code %

LB = LL1.q;

LC = LL2.q;

LD = LL3.q;

LE = LL4.q;

LF = LL5.q;

LG = LL6.q;

MA = LM0.q; % Most significant digit of POST code %

MB = LM1.q;

MC = LM2.q;

MD = LM3.q;

ME = LM4.q;

MF = LM5.q;

MG = LM6.q;

END;

### The author's source code listing for his program for the EPM7032 EPLD device in the POST card..

The logic consists of an address decoder, logic for decoding the seven segment display segments and two sets of latches for storing the segment data.

The segment outputs are driven directly from the latches. The decoding for the segments is derived in the diagram of Fig.4. Details of how to interpret the logic equations were given in

the examples in my Pulse Generator article in the January 1995 issue of EA.

### Using the card

When using the card, it should be noted that placing the card in the motherboard slot the wrong way around will result in +/-12 volts and -5 volts from the supply rails being applied directly to

the address inputs on the 7032 device. This would very likely damage the 7032 device. Hence, warnings should be placed on the card and due care taken in inserting it.

A further debt is owed to the authors of the original ETI article for a BASIC program (POSTTEST.BAS) that will

*Continued on page 127*

## Multimedia upgrade review:

# High quality multimedia speakers

If you'd like more 'punch' in the sound from your PC's multimedia applications and games, this set of self-powered shielded speakers from Rod Irving Electronics may be just the shot. They offer volume, bass and treble controls, use vented enclosures to extend the low-end response, and are a genuine two-way speaker system featuring both bass and treble drivers.

by **ROB EVANS**

When it comes to reproducing the more demanding sound effects or musical passages from games and other PC applications, the typical set of low cost multimedia speakers really do fall rather short of the mark. More often than not they have a very small driver in an equally small enclosure, and as a result, tend to turn explosions into muted 'blurts' and segments of potentially emotive music into a series of lightweight tinkles — needless to say, the desired effect becomes somewhat lost...

While changing over to a larger set of speakers can relieve the situation to some degree, the sound card itself can then impose a further limitation on the sound quality though its very limited output power capability. With a typical figure of just a few hundred milliwatts, most cards have little hope of extracting the full potential from larger and better speakers.

Perhaps the only real way to get the full impact from your PC sound then, is to upgrade both the amplifying system *and* speakers. While a retired hifi system can do the job at a pinch, the speakers would have to be placed some distance from the computer monitor due to their lack of magnetic shielding. You would also need to buy or construct an adaptor cable that can connect the output of PC's sound card to the hifi amp input. All in all it's a fairly bulky and inelegant way to beef up the sound from your PC, albeit a potentially low cost one.

Of course the other approach to the problem is to purchase a set of higher-performance speakers that are specifically designed for multimedia applica-


tions, such as the 'Active 75' units featured here. With an integrated (that is, built-in) amplifier system, full magnetic shielding and relatively robust drivers, this system appears to address all of the above limitations in one hit.

The Active 75's are based on a set of molded high-impact plastic speaker enclosures that house what appears to be an 85mm woofer and 20mm tweeter, plus a 25mm port tube.

As you can see from the photo, the enclosures have a very neat and functional appearance thanks to the integrated speaker grills, rounded corners and a tapered vent tube, and would not look out of place alongside most

contemporary PCs. For the record, the overall cabinet dimensions are approximately 225 x 140 x 185mm (H x W x D).

In order to have a just a single set of volume, bass and treble controls, the Active 75's stereo amplifier is held in one of the enclosures, while the other acts as a conventional (passive) speaker. The amplifier connections are accessed via a recess in the rear of the enclosure, where RCA-style connectors are used for the stereo input signal from the sound card and the single speaker output to the other enclosure — which in turn has just one RCA connector, as you would expect.

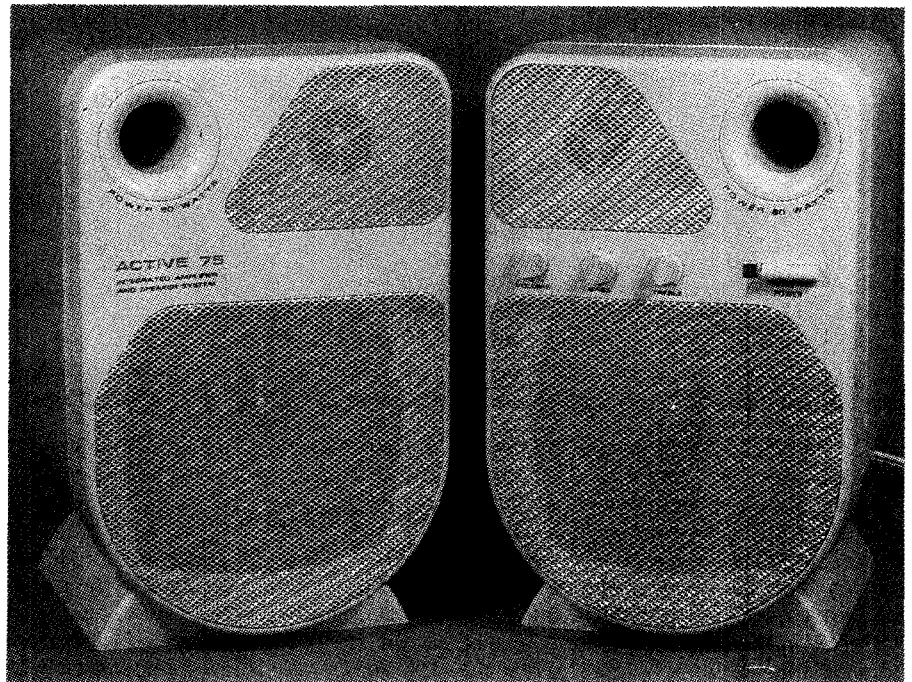


## A POST test card for IBM PCs

Continued from page 125
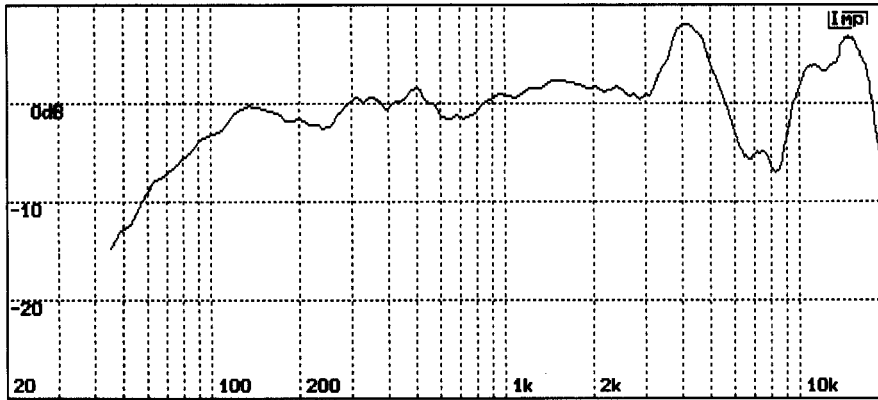
### Software for this project

The POSTTEST.BAS program which can be used to test this project is available on the EA Computer BBS, in the EA Project Software area. Also available on the BBS in the Useful Utilities area is the PCM105.ZIP shareware utility, which provides a lot of information on the PC's Power-On Self Test routine and its diagnostic codes.

The phone number of the EA BBS is (02) 353 0627.



The frequency response plot for the Active 75's, as measured with our IMP loudspeaker testing system.

### Sound check

The Active 75's are supplied with an RCA-to-RCA speaker lead to interconnect the two enclosures, plus a stereo input lead which is terminated in a 3.5mm stereo plug to suit most sound cards and portable music systems. Unfortunately though, while the connection process was very straightforward, we initially found that there was no response from the system at all, when power was first applied — even the power 'on' indicator next to the push-button power switch was dead.

Seizing the opportunity to take a look inside, we disassembled the 'amplifier' enclosure and soon found that the main PCB had been dislodged from its mountings (or perhaps installed incorrectly), and was badly cracked as a result. Fortunately, it was a fairly simple matter to repair the associated broken PCB tracks — which had effectively disconnected a couple of the unit's main power supply lines — and 'revive' the amplifier.

We're confident that this damage was an isolated case, and judging by the quality of construction inside the units we feel sure that other Active 75's will perform as expected.

By the way we also checked out the effectiveness of the driver's magnetic shielding, and found that unlike a number of other so-called multimedia or 'monitor friendly' speakers, these units caused no perceivable discolouration or distortion in our test monitor's screen.

When connected to a clean signal source such as an FM radio or CD player we found that the Active 75's delivered an impressive performance, and were able to produce surprisingly high volume levels without obvious

stress. The bass response was pleasantly extended — implying that the vented enclosures are well matched to the woofers — and the treble response was similarly extended, but somewhat harsh (in hifi terms) in the upper midrange area.

Investigation with our IMP loudspeaker testing setup confirmed that the system exhibits a sizable peak in the response at around 4kHz, quickly followed by a broad dip in the 7kHz region, which would certainly account for the somewhat strident midrange performance (see Fig.1). This is probably a side effect of the enclosure's very simple crossover network (one capacitor), which appears to have introduced a degree of phase addition and cancellation between the acoustic output of the bass and treble drivers.

In practice though, we noted that when the Active 75's are operating in a typical setup (with a PC or portable CD player) the subjective performance is vastly superior to that of typical compact speakers — particularly if the treble control is slightly backed off. So if your PC has a 16-bit sound card and you have access to the latest generation of sound-orientated games, you should find that the Active 75's add a new dimension to your enjoyment.

And while really can't take the '80 watts PMPO' power figure offered by the manufacturer very seriously, we would guess that the unit's internal amps are rated somewhere between 5 and 10 watts RMS, which should be more than enough to disturb the entire household...

The Active 75's are currently priced at \$129, and are available from Rod Irving Electronics stores around Australia — their mail order hotline is 1800 33 5757. ♦

thoroughly test the card. That article should be referred to for details. Possibly a copy of the BASIC program may become available on *Electronics Australia's* BBS.

To use POSTTEST, you simply run it using QB45 and note that all the correct numbers appear on the seven-segment display. You will need a floppy disk and video in the PC as well as the POST test card to run the test program. You will of course have to leave the lid off the PC in order to see the results.


You might want to test the card in a machine that is known to be working properly, before trying it on a faulty motherboard.

The information given here should be sufficient for anyone interested to make up one of these POST test cards using the 7032 device and so to experience the future of digital electronics. The libraries of Universities and TAFE colleges as well as public libraries are usually available to the public to look for the references.

### References

1. The magazine articles which gave us the idea for the POST test card were in the October and November 1994 issues of *ETI* (Electronics Today International), written by Stephen Smith and A.R. Jardine.
2. Another POST test card was described in *Computer Craft* for November 1993, written by Paul E. Yost.
3. Yet another, but comprehensive article on POST test cards appeared in *Elektor Electronics* for January 1995, written by M. Rathjen.
4. An informative article on POST was published in *PC Magazine* for Feb 13, 1990, entitled 'Tutor — The First 30 Seconds' and written by Jeff Prosis. ♦

# Solid State Update

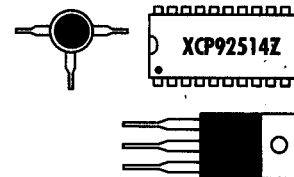

KEEPING YOU INFORMED ON THE LATEST DEVELOPMENTS IN SEMICONDUCTOR TECHNOLOGY

## 24-bit sigma delta ADC

Harris Semiconductor has announced the HI7190, a sigma-delta ADC.

Its 2.9uV peak-to-peak noise translates to 23.5-bit effective resolution. The device has 16-bit accuracy and is suited for process controls, commercial scales, instrumentation and medical applica-

tions. The serial interface is compatible with SPI, QSPI, MicroWire and Intel standards and supports three wire interface to most MPUs.


The converter features 0.0015% full scale integral non-linearity (INL) over the temperature range of -40°C to +85°C. Its differential analog inputs

are programmable for unipolar (ground referenced) or bipolar (plus and minus) operation. Noise rejection at 50/60Hz is better than -120dB when the notch filter is programmed to a sub-harmonic of 50/60Hz.

A patent pending auto-calibrate function helps maintain 16-bit accuracy over temperature. This innovative function compensates for first and second order errors caused by differences in non-linearity between the negative and positive regions of the transfer function, differences that are typical of all switched capacitor charge-balanced modulators.

Conversion rates of 10 to 2000Hz (10MHz crystal) or one to 200Hz (1MHz crystal) and gains of 1, 2, 4, 8, 16, 32, 64 and 128 can be programmed. The on-board programmable-gain instrumentation amplifier has gain options of 1, 2, 4 and 8, and on-board processing provides further gain in the digital domain.

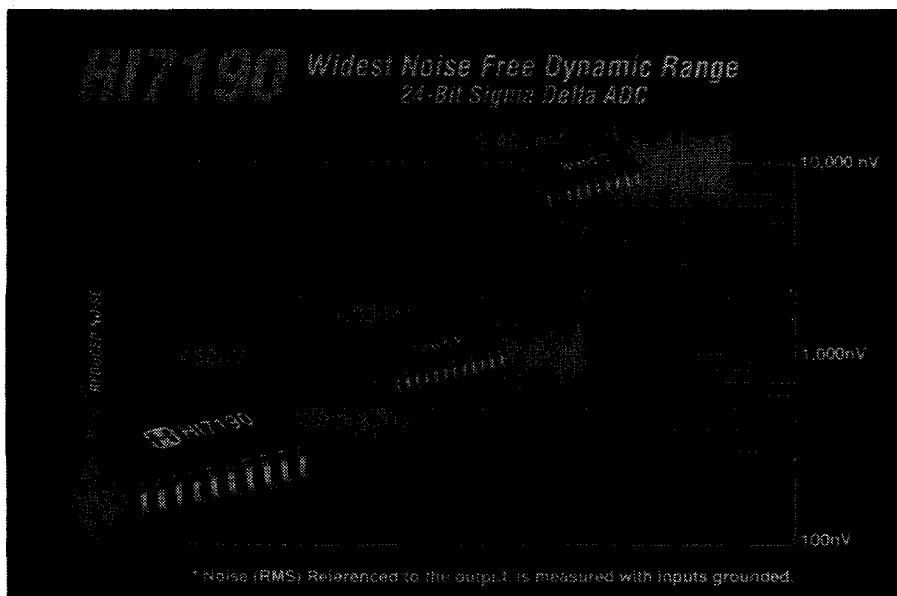For further information circle 272 on the reader service coupon or contact Avnet VSI Electronics, 6-8 Lyon Park Road, North Ryde 2113; phone (02) 878 1299.



## 5A flyback power converter


National Semiconductor has expanded its Simple Switcher power converter family with the introduction of two new 5A flyback power converters, called the LM2587 and LM2588.

Both devices feature increased power (5A switch current versus 3A) over previous Simple Switcher power converters, and 65V switch voltage rating. New, higher frequency operation allows smaller external magnetic components and capacitors, reducing the required printed circuit board area. The LM2587 operates at 100kHz while the LM2588 allows frequency adjustment between 100kHz and 200kHz with one external resistor.

Other advantages of the LM2588 include synchronisation to a common frequency (so devices can be connected in parallel), and an on-off pin for external turn-off reduces quiescent current to 60uA.

Both ICs are designed for flyback, forward and step-up (boost) switching converter applications, and are available in 3.3V, 5V, 12V and adjustable output voltage versions. Both also offer current-mode operation for improved transient response, line regulation and current limit. Protecting the power switch are current and thermal limiting circuits and an under voltage lockout circuit for fail safe operation. A soft-start feature reduces in-rush current during start up.

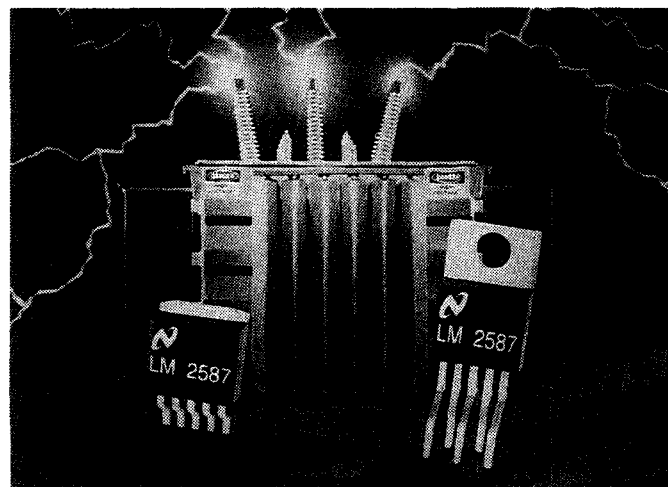The new flyback power converters are supported by



'Switchers made Simple' version 4.0 design software, which provides a complete design solution including schematics, components lists and vendor information. Both ICs are available in a TO-220 package or TO-263 surface mount package.

For further information circle 270 on the reader service coupon or contact National Semiconductor, Business Park Drive, Monash Business Park, Notting Hill; phone (03) 558 9999.

## Combined photodiode-amp

The new OPT101-R photodiode/amplifier IC from Burr Brown is packaged in red moulded plastic to provide optical filtering. The device combines a high performance photodiode, micro-power transimpedance amplifier and a 1M $\Omega$  feedback resistor on a single monolithic IC.


The Red plastic package provides selective response to wavelengths greater than 570nm, making it ideal for applications using red or infrared illumination. The device is suited to a wide range of light sensing applications including smoke detectors, position and proximity sensors, medical and laboratory instrumentation. Optical filtering improves performance by reducing response to ambient light sources. Clear plastic versions are also available for applications requiring wider spectral response.

The sensor's output voltage increases linearly with light intensity. Power supply current is 120uA and single supply operation extends from 2.7V to 36V. It can also operate from dual supplies. An internal 7.5mV output pedestal voltage assures linear operation down to zero light with a single supply. Other key specifications include bandwidth of 14kHz, and photodiode responsivity of 0.45A/W at 650nm.

The integrated combination of photodiode and amplifier eliminates the problems commonly encountered with discrete designs, such as leakage current errors, noise pickup and gain peaking. The 2.29 x 2.29mm photodiode is operated in photo-

conductive mode for best linearity and low dark current. It is available in 8-pin DIP, 5-pin vertically mounted SIP, and 8-lead surface mount packages.

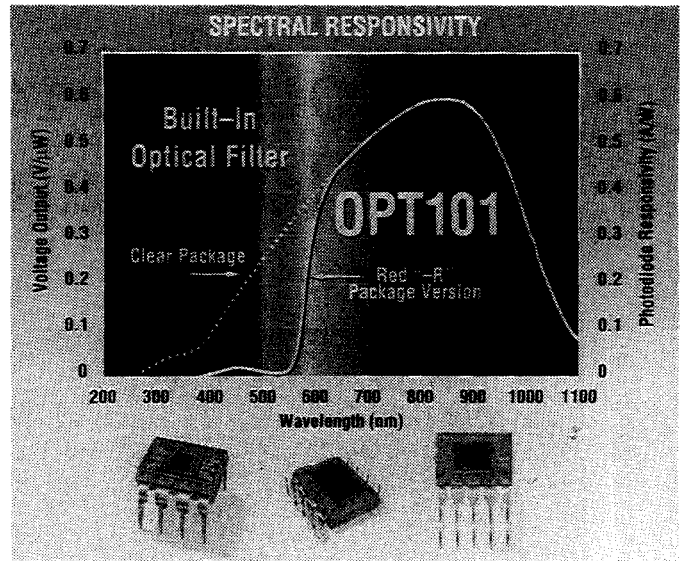For further information circle 273 on the reader service coupon or contact Kenelec, 2 Apollo Court, Blackburn 3130; phone (03) 878 2700.



## CCD image signal processor

A high integrated sensor processor that performs all the analog functions necessary for CCD sensor operation has been introduced by National Semiconductor. The device, called LM9800, is compatible with grey scale and colour CCD sensors used in sheet-fed and flatbed scanners.


The LM9800 features 8-bit resolution

and operates at a 2.5 million pixel/second conversion rate. It removes errors from and digitises a linear CCD pixel stream, while generating all the necessary clock signals to drive the CCD. An internal configuration register sets CCD and sampling timing to maximise performance and simplify the design.

Functions include correlated double sampling for black level and offset compensation resulting in minimum noise and offset error; 8-bit analog-to-

digital conversion; and pixel-by-pixel gain adjust that maximises the dynamic range and resolution, even on 'weak' pixels. The LM9800 is available in a 52-lead plastic leaded chip carrier (PLCC). A 52-pin thin quad flat pack (TQFP) package is also available.

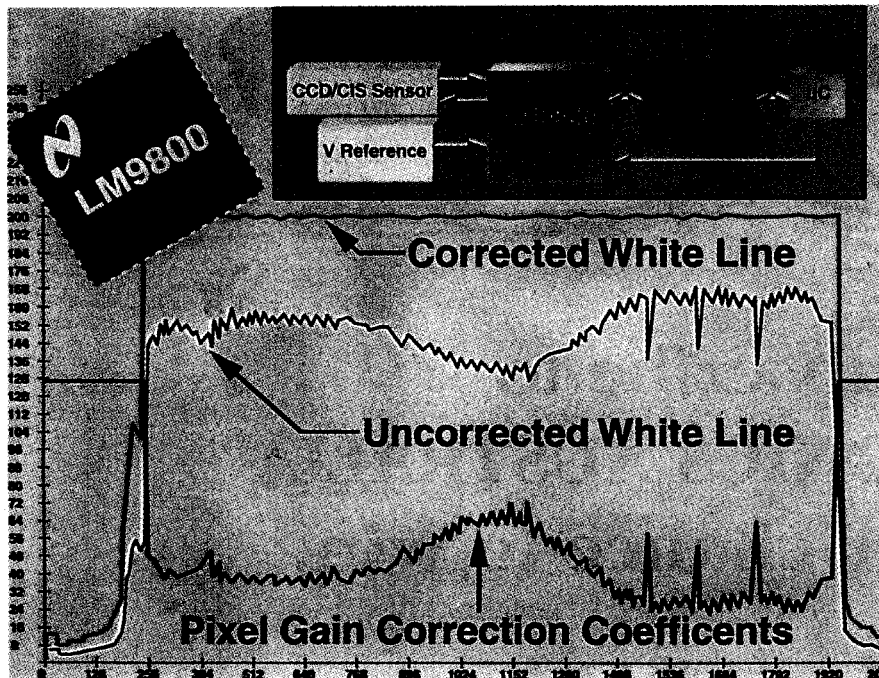For further information circle 275 on the reader service coupon or contact National Semiconductor, Business Park Drive Monash Business Park, Notting Hill; phone (03) 558 9999. ♦



Feels like a scope.

Sets up like a scope.

Displays like a scope.

Could it really be a  
logic analyser?



Subscribe to  
"ELECTRONICS AUSTRALIA"  
for your chance to win.

 HEWLETT®  
PACKARD



## Two lucky subscribers will each win a Hewlett-Packard 54620A Logic Analyser, valued at \$5557.

Sixteen channels of 500MSa/s logic analysis in a box that drives like a scope may seem impossible. Until you see the HP 54620A logic analyser.

The HP 54620A will change your attitude about trouble shooting. Its range of triggering allows you to match the complexity of your problem. The high-speed display system shows you unstable signals. And because of its remarkably rapid update rate and instantaneous feedback, you can operate this with a simple twist of a knob.

The HP 54620A - a logic analyser that really is as easy to use as your scope.

To be in the draw to win a HP 54620A, simply subscribe or extend your existing subscription to Electronics Australia. We'll deliver 12 issues straight to your door for only \$55 (which includes postage and handling) - that's a saving of more than 15% off the cover price.

**12 Issues only \$55.00**

To subscribe by phone, call TOLL FREE 1800 800 933. Sydney residents call (02) 353 9992 and have your credit card details handy.

Alternatively, simply fill out the subscription card attached and send with your payment to:

Federal Publishing • Subscriptions Department  
Reply Paid No 3 • PO Box 199  
Alexandria NSW 2015

For further information on the HP 54620A, call the Hewlett-Packard Customer Information Centre on 13 1347 (Australia Wide) and ask for extension 2902.

# HURRY! OFFER ENDS 23RD JANUARY, 1996.

CONDITIONS OF ENTRY: 1. The competition is open to Australian residents authorising a new or renewed subscription to Electronics Australia before last mail on 23.01.96. Entries received after closing date will not be included. Employees of the Hannan Group, Hewlett Packard, their subsidiaries and families are not eligible to enter. 2. South Australian residents need not purchase a subscription to enter once by submitting their name, address and phone number to: Electronics Australia/ Hewlett Packard Competition, PO Box 199, Alexandria, NSW 2015. 3. Prizes are not transferable or exchangeable and may not be converted to cash. 4. The judge's decision is final and no correspondence will be entered into. 5. Description of the competition and instructions on how to enter form a part of the competition. 6. The competition commences 20.09.95 and closes last mail on 23.01.96. 7. The draw will take place in Sydney on 02.02.96 as 11am and the winners will be announced in a later issue of Electronics Australia and notified by mail. 8. The prize is: 2 X Hewlett Packard HP 54620A Logic Analysers, valued at \$5557 each. Total prize value is \$11,114. 9. Subscriptions are not refundable. 10. The promoter is the Federal Publishing Company Pty. Ltd., 180 Bourke Rd, Alexandria NSW 2015. Permit No. TC75/4138 issued under the Lotteries and Art Union Act 1901/Vic. Permit No. 95/1393 issued on 09/08/95; ACT permit no. TP95/1668 issued under the Lotteries Act 1964; NT permit no. 95/1404.

# NEW PRODUCTS


## COMPONENTS

### Infrared receiver IC


Dick Smith Electronics has added an integrated optical receiver 'subsystem' to its range of optoelectronic devices, as catalog number Z-1954. Housed in a compact three-pin plastic package incorporating a 'biradial' lens and filter, the device includes an IR receiver diode, amplifier, limiter, bandpass filter and demodulator.

As the output from the device is a demodulated digital signal that's identical to that transmitted, it provides a convenient and inexpensive alternative to traditional discrete receiver front ends in IR remote control systems. It has a high sensitivity and a nominal range of eight metres, operates from a 5V supply, and drives its output low in response to infrared energy modulated at 38kHz.

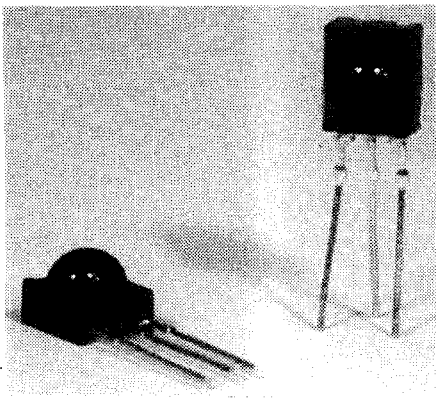The Z-1954 infrared receiver IC is priced at \$9.95 and is available at all Dick Smith Electronics stores.



### Very small 8kV relay

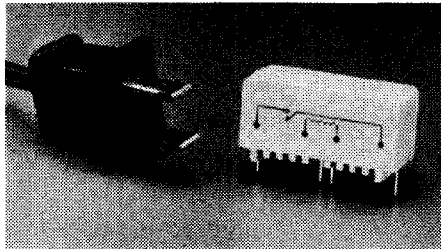

Kilovac Corporation has added a new power switching relay to its line of vacuum sealed, high voltage and RF power reed relays. Kilovac's new S02JTA is claimed to be the smallest 8000 volt relay in the industry (35 x 12.7 x 19mm).

The in-line PC pin connections provide close side by side mounting. Power handling for the new relay is 2A continuously at up to 8kV and the relay can power switch over 200 watts. The S02JTA is available in form A, SPST-NO with a choice of 5V, 12V or 24V DC coils.

For further information contact Kilovac, PO Box 4422, Santa Barbara, CA, USA 93140.

### Spring terminal pack

In response to suggestions from its customers, Dick Smith Electronics has released a low cost pack of 'spring terminals' for the highly successful Fun Way into Electronics Series 1 kits. The spring terminals are designed to augment the small screws originally used to mount components and perform connections in the Funway 1 kits, allowing the various circuits to be wired up faster and more easily, and with less damage to

component leads. This results in longer component life, and less need to replace parts with continued use of the kits.

The terminal springs are made from stainless steel wire so that they will not corrode or oxidise. The quantity of 28 springs supplied is sufficient to make the connections for all circuits described in the Funway 1 manual. Each spring is formed at one end to allow easy attachment to the moulded plastic base, using the original terminal screws.

The K-2602 Spring Pack is priced at only \$2.95 and is available from all Dick Smith Electronics retail outlets.

### Switch caps

MEC has introduced a new series of 'Combi-Caps' for UNIMEC switches. The caps are available in round, rectangular, and square styles.

The three cap styles can be ordered in any of seven colours. The square cap is also available in a transparent clear which accepts interchangeable legends. A bezel can be ordered with the square cap to give a finished look to front panel cutouts and all caps can be printed with standard legends and graphics, or with custom markings.

Switch ratings are 250mA at 120V for




### 10.4" colour active matrix LCD

The LDH102T-20 is a new colour active matrix LCD from Flat Panel Display Co. It consists of an AM LCD, an integrated adjustable backlight and module electronics.

The module electronics enables simple interfacing with commercially available VGA chipsets such as those from Cirrus Logic, Western Digital and Chips & Technologies. It can display 4096, 256K or 16.7 million colours depending on user selection, has low power consumption, is thin, compact, light weight and has a fast response. The display has an integrated high efficiency, single tube CCFT backlight for a brighter display.

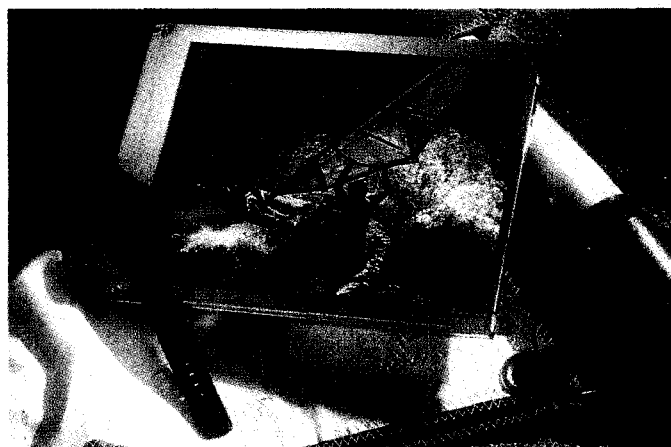For further information circle 233 on the reader service coupon or contact Amtex Electronics, PO Box 285, Chatswood 2057; phone (02) 805 0844.



silver contact material (gold optional). Mechanical life is 1.5 million cycles for momentary and 500,000 cycles for maintained switches. The new caps are also available for high temperature UNIMEC switches which provide 10 million cycles for momentary and five million cycles for alternate action switches. All UNIMEC switches are sealed to IP54 standards, are splash-proof and dust resistant.

For further information circle 231 on the reader service coupon or contact Associated Controls, 29 Smith Street, Hillsdale 2036; phone (02) 311 3255.

## 20A power relay

The Omron G4A relay is a miniature single pole relay capable of 80A surge current and 20A switching current, making it ideal for motor switching. The relay is available in 5V, 12V and 24V DC ratings, has highly noise resistive insulation materials and has the option of PCB terminals or #250 tab/PCB terminals.

For further information circle 232 on the reader service coupon or contact DGE Systems, 103 Broadmeadow Road, Broadmeadow 2292; phone (049) 61 3311.

## CONSUMER/BUSINESS EQUIPMENT

### Pocket sized fax machine and organiser

The Handifax 1000 is a 256K electronic personal organiser and fax machine in one.

Not much bigger than a family size block of chocolate, the product is used in conjunction with a standard touch tone telephone or analog mobile phone.

To use it, type the message you want to fax into the organiser, place the handset of the telephone (or mobile phone) on the acoustic coupler speaker and microphone, dial the fax machine you are calling and press SEND.

The Handifax 1000 can communicate with any standard fax machine at speeds up to 9600b/s. It can hold up to 120 faxable pages and its auto dialling facility overcomes the need to manually dial numbers or access codes. It includes built in fax cover pages and the ability to customise fax headers, standard orders, invoices and any kind of fax you regularly send.

Its 256K memory allows the device to double as a powerful personal organiser, capable of storing more than 3500 entries. It has a built in programmable

alarm, and can store access codes, extensions, credit card numbers, daily schedules and appointment times.

Included is an integrated calculator in standard keypad format which doubles as a telephone pad for easy phone and fax number entry. An optional PC interface allows users to back up and store information on any standard IBM compatible PC.

The Handifax 1000 is available at all Dick Smith Electronics stores for \$699.

### Personal fax, TAM, phone and copier

The Panasonic SuperPhone is a dedicated personal fax machine designed for home use. It combines a telephone, facsimile, answering machine and copier all in one compact unit.

It is designed to replace an existing



telephone and answering machine. The UF-S1 can determine whether an incoming call is a fax or phone call and switches accordingly. By using digital memory instead of a tape for the answering machine, messages can be accessed instantly and the flash memory protects messages in the event of a power failure.

The unit includes a timer alarm as a useful reminder for deadlines, or appointments. It also has a help function which prints out a copy of the operation guide listing all the major functions.

When sending fax messages the SuperPhone has 64 level halftone output for sending photographs or drawings, and a built in 25 page memory for storing incoming documents when the machine is out of paper.

Included is a copy function with an enlarge ability. For telephone operation, up to 15 frequently called telephone numbers can be programmed into memory and the machine can be configured to recognise private calls, while others

will automatically record on the answering machine.

The SuperPhone is available from electrical retailers and communication specialists for a recommended retail price of \$799.

For further information contact Panasonic's Customer Care Centre on 132 600.

## VHF/UHF FM handhelds

Kenwood has released two new handheld VHF/UHF FM portable transceivers, the TK-250 and TK-350. (West Australian Kenwood dealer Mobile Masters has won a large tender with the WA Police, involving a three year contract to supply TK-350 handhelds and provide service support.)

The TK-250 operates on frequencies from 150 - 174MHz and the TK-350 is available in four models covering 403MHz to 510MHz. Designed for the harshest environment, both units comply with selected criteria from MIL 810C/180D and 810E methods and procedures. Both units offer 150 channel capacity, four character LCD display, multiple scanning operation, and a selection of built in features including QT/DQT squelch, two tone decoding and DTMF decoding.

Other features of both models include 'busy channel lockout' that prevents transmit if another user or talk group is on the air, and a timer than can be programmed between three and 300 seconds to guard against misuse or accidental key presses. A tri-coloured LED gives four status indications for transmit, channel busy, selective call alert and low battery.

For further information circle 234 on the reader service coupon or contact Kenwood, 8 Figtree Drive, Homebush 2140; phone (02) 746 1888.

## POWER SUPPLIES

### Solar power for mobile phones

A new company called Southern Cross Solar has been formed to handle the Australian and New Zealand distribution rights to a new product called Solar Life solar batteries. The company is based in Hobart Tasmania.

Managing director Jon Grunseth believes the new batteries will revolutionise the mobile phone market. The nickel-metal hydride solar batteries have been specifically designed for mobile phones, and are a new technology developed by Bell Sound in the US.

## NEW PRODUCTS

The batteries can be charged by simply placing them in the sun, from a pocket size solar panel, from an AC power adaptor (two hours), or from a 12V car cigarette lighter. As an IC controller chip continually monitors charging and discharging to eliminate memory effect problems, the battery can be charged while in use, and automatic shut off circuitry prevents the battery overheating.

For further information phone Southern Cross Solar on 1800 636 758.

### 240V AC inverter for test equipment

A new accessory for use with the HP Basic Instruments range draws operating power from the cigarette lighter of a car, or from an external 12 volt battery. The HP 34397A DC-to-AC inverter makes it possible to use instruments on a portable calibration cart that travels throughout a plant, to make measurements at remote locations where no AC line is available, and to keep instruments powered and ready to use while in transit between sites.

Specifications include an input voltage range of 10.5 to 15 volts, output voltage of (standard) 115V AC 60Hz,  $\pm 0.06\text{Hz}$  or (option 0E3) 230V AC 50Hz,  $\pm 0.05\text{Hz}$ . The output range is 100 watts continuous or 200 watts for five minutes. The output waveform is a quasi-sine wave.


The inverter costs \$260 and is supplied with a manual in English, French and German and a set of battery clip leads. The 230 volt option comes with an IEC-to-IEC power cord to connect the instrument to the inverter.

For further information contact Hewlett-Packard's Customer Information Centre on 13 1347, extension 2902.
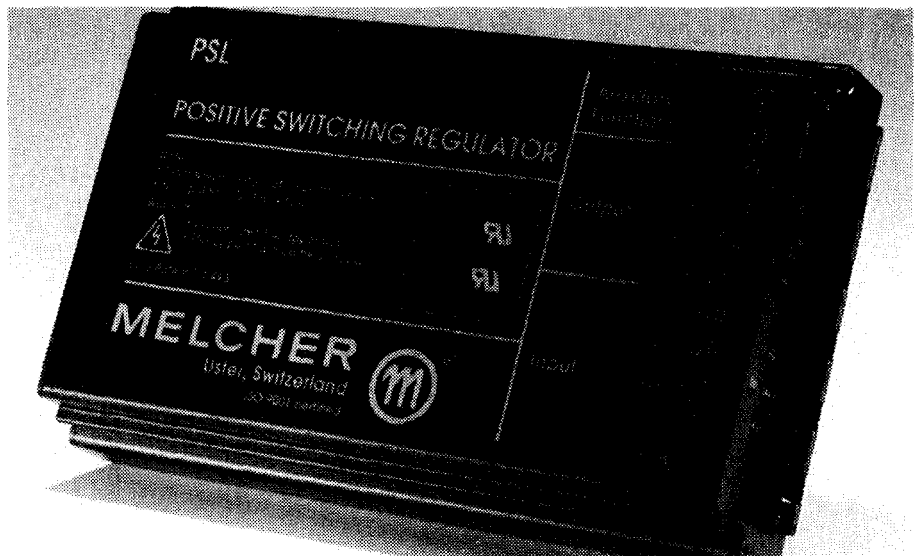
### Switching regulators

Power supply manufacturer Melcher has announced the new PSL family of switching regulators. With outputs from 5V/12A to 36V/6A and wide input voltage ranges, the products are available in three grades to suit rugged, industrial and benign environments. Housed in a 19" Eurocassette format aluminium extruded case, the units can also be chassis mounted, with an overall profile of 36.5mm.

The three grades allow users to select input, temperature ranges and immunity to environmental conditions to suit specific applications. For example, 'rugged' units are fully rated to 71°C, with input



voltage ranges up to 144V DC for powering directly from unregulated sources (e.g., traction batteries) and are well suited to portable/vehicle based systems. 'Benign' grade units are rated to 50°C and have input ranges up to 60V DC. Such units can be powered from a more

stabilised source (e.g., 24/36V DC bus), and are suited to telecoms, and commercial grade applications.

For further information circle 239 on the reader service coupon or contact Scientific Devices, 2 Jacks Road, South Oakleigh 3167; phone (03) 9579 3622

## TEST EQUIPMENT


### Tek DSOs double performance

Tektronix has doubled the performance of its TDS300 series digital oscilloscopes, with no increase in price. Announced are three new models:

100MHz (TDS340), 200MHz (TDS360) and 400MHz (TDS380).

The scopes are basic troubleshooting instruments targeted primarily for the education, design, service and repair markets. The digital capability of the series allows users to store set-ups and waveforms and perform 21 different automatic measurements.

The upgraded scopes now include fast

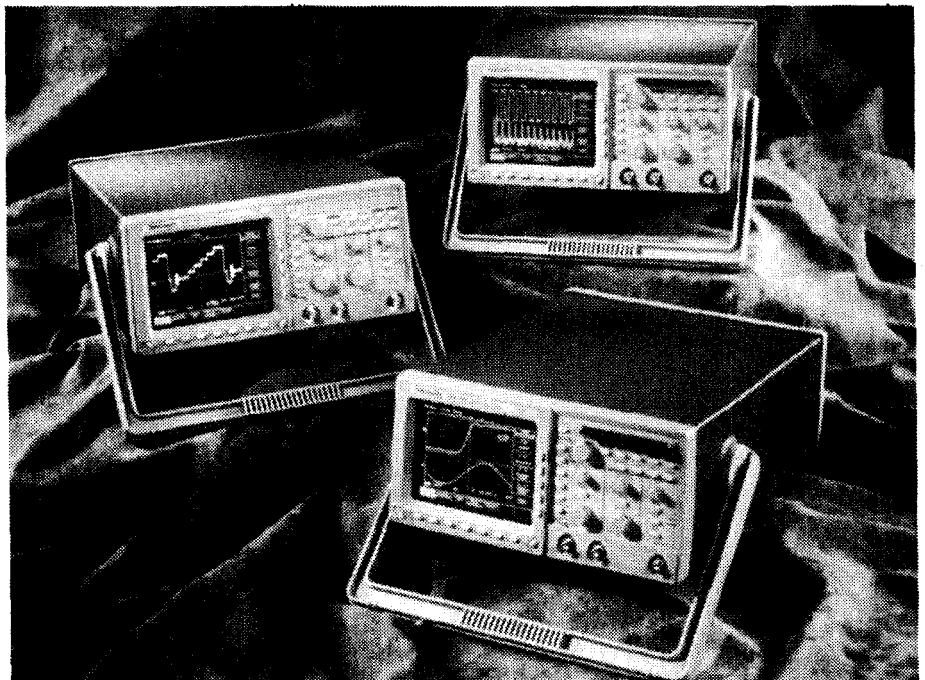

fourier transform (FFT) capability, which is useful for analysing harmonic content of signals.


They also feature Tektronix' patented digital real-time (DRT) oversampling technology, claimed to dramatically reduce aliasing and allow single shot waveform capture at the instrument's full bandwidth.

The TDS340's two channels digitise at a rate of 500 megasamples per second, the TDS360 at one gigasample per second and the TDS380 at two gigasamples per second.

A 3.5" DOS compatible floppy disk drive is built into the TDS360 and 380 models, for storing reference waveforms, saving waveforms and setups, and importing and exporting waveform values into application programs.

The suggested retail price for the TDS340 is \$3700; the TDS360 is \$5200 and the TDS380 is \$6800. Each comes with a three year warranty. A communication option is available for I/O to GPIB, RS-232 and Centronics type interfaces and VGA monitor output.

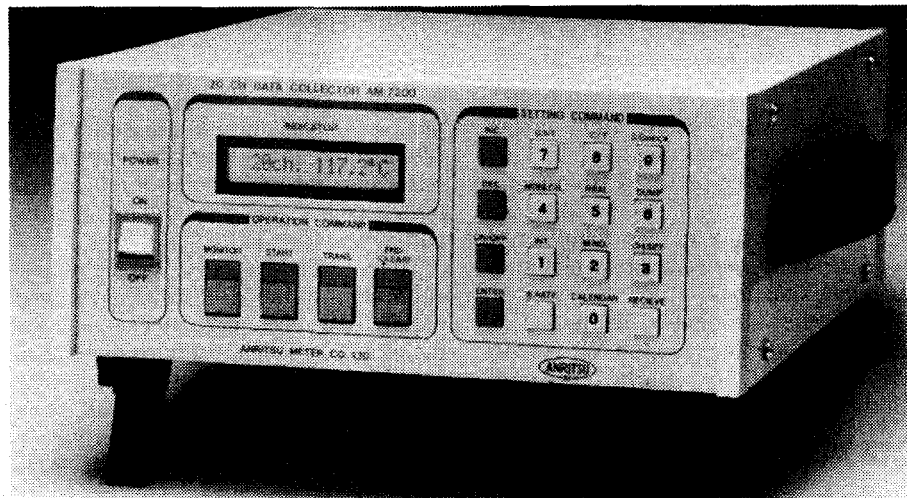For further information circle 240 on the reader service coupon or contact Tektronix Australia, 80 Waterloo Road, North Ryde 2113; phone (02) 878 9000.



### Fast 20 channel data collector


The AM-7200 high speed multi-channel data collection Anritsu incorporates a precision A/D converter, a CMOS microprocessor and a large capacity memory. Multi-purpose system upgrades are possible through communication with external devices through the RS-232C interface.

Many functions are concentrated in the compact unit and temperature ranges can be monitored from -200°C

to +1200°C (type K or type E thermocouple).

The instrument features self-calibration for zero and full scale compensation. Linearisation and calculation of the temperature data over the 20 channels is achieved at intervals of 0.5 sec. Setting parameters include calendar (year, month, day, hour and minute), interval timer, machine number setting up to four digits, channel selection, real time RS-232C output, memory data output, baud rate, memory dump to display, 0.1° to 1° resolution, °C/°F selection, sensor
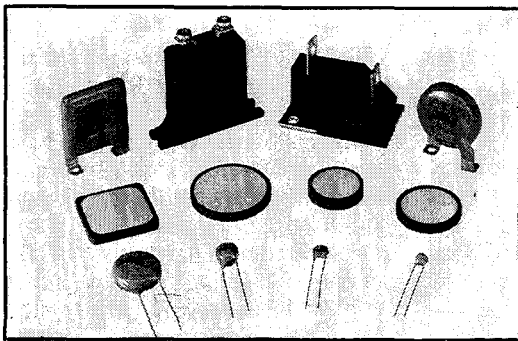
## METAL OXIDE VARISTORS **Iskra** VARISTOR Co



- Element diameters of 5; 7; 10; 14; 20; 25; 32 & 40 mm
- Voltage range (1mA) from 18 to 1800 V
- Surge current (8/20us) up to 40 kA
- Energy absorption (2 ms) up to 1200 J
- Operating temperature without derating - 40 to +80°C
- Available in tape & reel and ammo packaging
- UL recognition #1449, file E103662


**Fastron** Ph (03) 794 5566  
TECHNOLOGIES PTY. LTD. Fax (03) 794 6670

AGENTS IN ALL STATES & NZ

READER INFO NO. 23
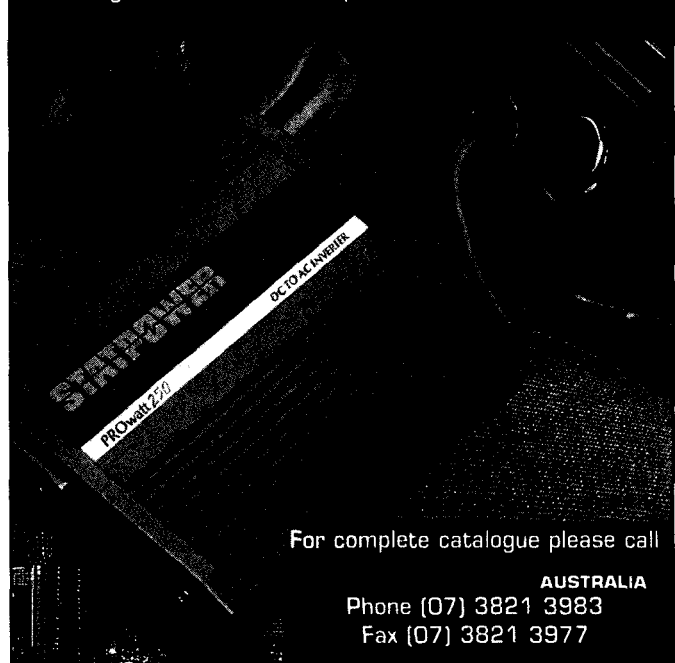
### WHAT HAPPENS IF YOUR POWER FAILS?

Converts office support battery power into business 240 volts AC. Runs all your computers, overheads, lighting, recording and test equipment. Plug it into your car cigarette lighter and run mobile phone batteries, VCR's, etc.



For complete catalogue please call

AUSTRALIA  
Phone (07) 3821 3983  
Fax (07) 3821 3977

READER INFO NO. 24


## NEW PRODUCTS

check, parameter setting from instrument keypad or host computer.

The unit can be powered from mains AC, 12V DC or from battery. Cases can be supplied for use in high temperature ovens or warm showers for special measurement situations.

For further information circle 241 on the reader service coupon or contact Electromark, 36 Barry Avenue, Mortdale 2223; phone (02) 533 3322.

### CDMA mobile phone tester

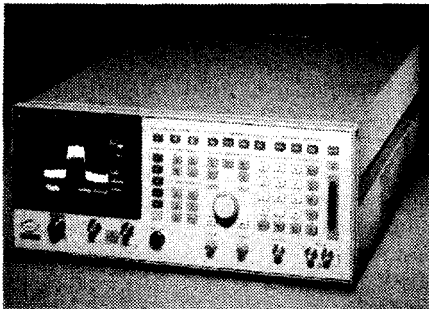

Hewlett-Packard has released a test set that uses one instrument to perform automated testing of the digital DMA and analog FM sections of dual-mode mobile phones.

The HP8924C test set simulates base-station operation to make an array of automated measurements in manufacturing or high level service environments. The instrument has two independent, intermediate frequency (IF) demodulators: one that recovers real time data bits for link maintenance and receiver measurements, and one that

performs transmitter measurements. Manufacturers can perform simultaneous evaluation of frame error rate, transmitter power and modulation quality, cutting test time in half.

To test a CDMA phone, the technician connects it to the HP-8924C, enters the required RF channel number, waits for the mobile to acquire service and presses the instrument's call button. The tester makes a CDMA phone call, verifies receivers, the instrument displays a pass/fail indication based on the measured frame error rate.

A full complement of CDMA transmitter tests is performed automatically by the instrument, including high speed, digital signal processing based power measurement from 0.1mW to 6W and accurate channel power measurement from 0dBm to -50dBm. When making CDMA receiver measurements, the tester compares the received 9.6kb/s data to the transmitted 9.6kb/s pseudo-random data and performs a bit-by-bit comparison to calculate the true frame error rate.

For further information phone Hewlett-Packard's Customer Information Centre on 13 1347, extension 2902.

### Troubleshooting workstation

Huntron Instruments of USA has announced the new ProTrack generation of programmable troubleshooting instruments, which link the company's analog signature analysis technique (ASA) with a number of new software and hardware tools.

The new product family, which introduces the concept of a personal troubleshooting workstation, is based on a modular approach. It allows users to put together customised systems, ranging from simple benchtop troubleshooting units to fully automated board testers using robotic probers.

Windows based software and programmable test ranges allow the system to handle complex boards, including through hole or surface mount assemblies incorporating mixed technology components.

The basic unit in the ProTrack family is the ProTrack 1 model 10; a benchtop unit for applications where a computer interface is not needed.

The interface is added in the model 20, which can be used in conjunction with the ProTrack Scanner 1 to scan up


to 128 pins at a time, and make real-time comparisons between boards.

The model 20 can be interfaced with a personal computer running Huntron's Workstation for Windows automatic test software to form a troubleshooting workstation.

Test information can be transferred between computer or locations, and component databases can be stored or rearranged. Up to 10 individual models can be stored for each component. Test results can be viewed immediately and test data can be printed out or stored for archive purposes.

For further information circle 239 on the reader service coupon or contact Metromatics, PO Box 314, New Farm 4005; phone (07) 335 8155.

### Comb generator, RF calibrator

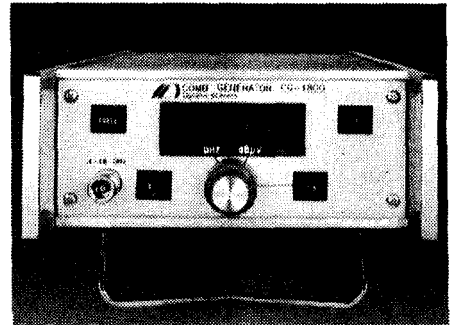

The DSI-IG-1800 solid state RF comb generator from Dynamic Sciences covers the frequency range of 100MHz to 18GHz, and is suitable as a calibration source for RF measurement systems and receivers.

The instrument is claimed to be a precise, accurate and inexpensive signal source with the stability of a temperature stabilised crystal oscillator. It has a coherent comb line space of 100MHz, an output levelling function and is suitable for laboratory or field application. All controls can be remotely operated by the IEEE-488 bus allowing control over frequency, levelling and signal amplitude. The instrument features front panel indicators for repetition rate and amplitude. The impulse generator is supplied calibrated in dBuV (referenced to 50 ohms) with a maximum output of 70dBuV and an 81dB attenuator with 1dB steps.

For further information circle 216 on the reader service coupon or contact Dynamic Sciences Australia, 614 Hawthorne Road, East Brighton 3187; phone (03) 9596 0155.

## ASPAC AUSTRALIA

**Wholesale Distributors of  
Quality Electronic Components**  
SPECIALISING IN:

- Liquid Crystal Display Modules.  
Digital Character & Graphic types.  
Character Type Range: TN, STN 8Ch x 2Ln to 40Ch x 4Ln. LED, EL or CFL Back Light.  
Graphic Dot Matrix Range: STN 122 x 32 Dots to 256 x 128 with Touch Screen
- LED Products  
Complete range of LED Lamp Products.  
Standard 3 & 5mm, Blue, Super Bright.  
Bi-Colour, Full Colour, Flashing & Rectangular.  
Seven Segment & Alphanumeric Displays.  
Dot Matrix Modules 30mm to 100mm.
- Electronic Enclosures  
Comprehensive range of Quality Desk Top, Hand Held, Wall Mount and Instrument Cases.
- Product Information:  
QLD. Tel: 07 3288 9036 Fax: 07 3294 0750  
VIC. Tel: 03 9465 1895 Fax: 03 9465 1895

READER INFO NO. 25

## TOOLS

### 'Pistol' screwdriver, olive picker

Scope Laboratories has announced a number of new hand tools for the electronics service industry. Included is an ergonomically designed pistol grip screwdriver that includes three slotted and two Phillips head bits, normally stored in the handle.

The drive has a reversible ratchet function and is a compact 120mm in length.

Another is the 'olive picker', a tool originally designed to lift olives from a narrow jar. This tool has been adapted to recover dropped parts from inside equipment. Its three spring loaded fingers expand to 15mm.

To help locate dropped parts, or to inspect impossible to see places, Scope has also available a 30mm inspection mirror that is adjustable to any angle. A 55mm mirror is also available, featuring a telescopic handle.

For further information circle 245 on the reader service coupon or contact Scope Laboratories, PO Box 63, Niddrie 3042; phone (03) 9338 1566. ♦

## Hameg's Modular Instrument System

Continued from page 121

modules are light in weight and fabricated from fairly light gauge metal and plastic parts, they are carefully designed and structured to achieve a high order of strength and durability.

Incidentally although the mainframe unit appeared to have been made in Germany, all of the sample modules had been made at Hameg's factory in France.

Overall the operation of the various plug-in modules was very straightforward and intuitive, with the controls arranged logically and the LED readouts stable and unambiguous — leaving little need to refer to the user manuals.

The measured performance of the modules also compared very well with their rated specs, and were generally well inside them — suggesting that in most cases the specs are quite conservative.

By the way, the quoted prices of the Modular System 8000 components seem very reasonable. The mainframe


unit is priced at \$470, while the plug-in modules range from \$480 for the HM8040-2 Triple Power Supply, up to \$985 for the HM8042 Curve Tracer. The prices for the HM8027 Distortion Meter and HM8032 Sinewave Generator are both \$590, for example, while the HM8018 LC Meter is \$645 and the HM8035 \$880.

These prices are all exclusive of sales tax, but include a two year warranty by the manufacturer.

On the whole, then, our impression of Hameg's Modular System 8000 is that it is a very well thought out and nicely executed family of medium level, cost-effective test instruments. Considering how infrequently some of the more specialised test instruments tend to be used, this approach should therefore have a lot of appeal for both individuals and smaller labs.

Further information on these and other instruments in the Hameg range is available from Kenelec at 2 Apollo Court, Blackburn 3130; phone (03) 9878 2700 or fax (03) 9878 0824. ♦

25% Discount for  
AUTOTRAX Users

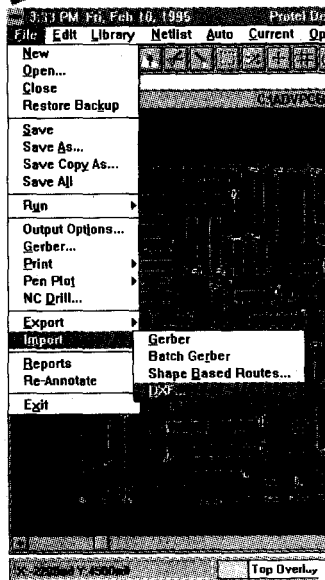

### Protel Design System for Windows


- Schematic Entry
- PCB Design
- Autorouting
- Autoplace
- Simulation interfaces
- FPGA and EPLD support



For more information phone

Toll Free  
1800 030 949

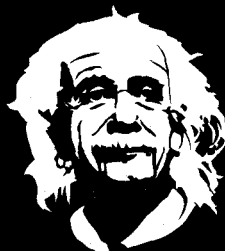Protel Technology  
Technopark Dowsings Point 7010 Tasmania



$$E = mc^2$$


## HI-TECH C

for embedded systems.

The world's best C cross compilers.  
Available for most popular chips.

HI-TECH Software  
Ph. (07) 300 5011  
Fax (07) 300 5246  
PO Box 103 ALDERLEY  
QLD 4051.

# SPOTLIGHT ON SOFTWARE

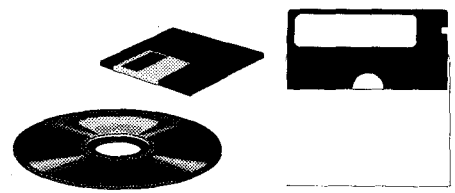

## BassBox 5.1

Using the Windows 3.1 environment, Harris Technologies' *BassBox* program helps you design a wide range of low-frequency loudspeaker enclosures, including the increasingly popular double- and triple-chamber bandpass configurations. It has a built-in database of around 1300 drivers, can plot up to six variables for each design, and offers a number of useful utilities such as an integrated port/vent calculator.

by ROB EVANS

Those interested in loudspeaker enclosure design are probably aware of how the related CAD (Computer Aided Design) software can make the job of developing a speaker system a much easier, and arguably less error prone process.

With the ability to quickly design, evaluate and then 'fine tune' a speaker system *before* building the enclosure, a comprehensive loudspeaker design program can save you a considerable amount of time and effort when developing a suitable cabinet for a given driver.

As it happens, we've been using the DOS-based LEAP (Loudspeaker Enclosure Analysis Program) system for several years now at EA, and have certainly been impressed with the accuracy of its design tools and performance simulations. With LEAP, the actual prototype enclosure tends to perform very close to the program's predictions, and usually just needs a little fine tuning.

While the current version of LEAP carries a fairly hefty price tag — as you would expect from what's now a very 'professional' CAD package — an array of quite competitively-priced loudspeaker design programs have surfaced since its inception back in 1988. These range from inexpensive 'shareware' packages written by speaker design enthusiasts, through to very comprehensive programs such as the Australian developed CALSOD system from AudioSoft in Melbourne (which is also the distributor of BassBox).

You can download a couple of examples of the low cost shareware

alternatives from the EA Reader Services BBS, by the way — see SDES12.ZIP and BOXPLO.ZIP.

Harris Technologies' *BassBox* appears to take a quite effective middle path in the features/price balance, by concentrating on low-frequency (bass) enclosures only, and leaving the equally complex area of high-frequency driver and crossover network analysis to other dedicated programs — hence the *Bassbox* tag.

Thanks to this somewhat more specialised approach, BassBox 5.1 is able to offer a very comprehensive set of analysis routines and utilities for bass cabinet/driver combinations. In practice this is of course the core of any loudspeaker design.


BassBox 5.1 requires a '386 or better machine with at least 4MB of system RAM, and Windows 3.1 (or later) installed. It is supplied on two 1.44MB 3.5" diskettes and requires approximately 7.5MB of free hard disk space — a fairly 'lean' program, by today's standards — and is quite reasonably priced at \$189.

When it comes to features though, you could hardly summarise the program's capabilities as lightweight. They include:

- The ability to use drivers from the built-in database, or those entered from Thiele-Small or electro-mechanical ('BL' etc) data.
- Automatically derived 'optimum' enclosures for sealed and vented designs, which can also be used as a starting point for new designs.
- Definable degrees of box damping (Q) and acoustic fill material.

- Custom 'passive' radiator designs, plus 'extended bass' alignments for vented cabinets.
- Vented boxes can be designed with multiple ports, which can have almost any shape.
- Multiple woofer designs include 'standard', 'push-pull' and 'compound' (*isobaric*, or face-to-face) arrangements.
- Modelling for both fourth- and sixth-order bandpass (multi-chamber) box designs.
- Response plots for amplitude ('normalised' and at 2.83V), maximum acoustic power, voice coil impedance, phase change and group delay.
- An interior acoustic response plot (from a room or automobile interior) can be impressed on a design's amplitude response plot.
- Designs can be loaded and saved, plus all data and plots printed out under control of Windows — and therefore to any supported printer.
- A box dimension calculator which includes a range of pre-defined shapes, which can be applied to the overall box or internal sub-cabinets, or subtracted from the enclosure to allow for space occupied by speakers and braces.
- A vent dimension calculator for round, rectangular or undefined shape ports, which automatically derives the correct vent size for the selected cabinet's tuning.
- A speaker parameter calculator, that also guides you through the driver testing process (bench



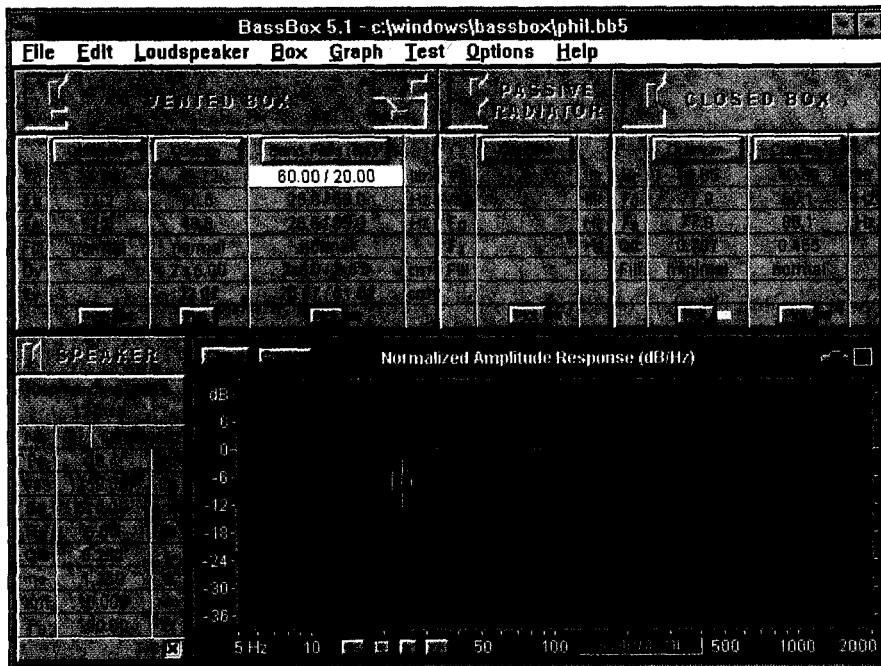

**BassBox's main analysis and plotting screen. The red curve shows the response for the program's suggested 'optimum' vented enclosure, while the blue plot is the projected response for a trial bandpass design featuring compound-mounted drivers. As you can see from the highlighted design near the top of the screen the bandpass enclosure has a 60 litre rear chamber and a 20 litre front chamber.**

- oscillator and multimeter required).
- Response plot data files can be imported from several popular loudspeaker measurement systems, including IMP.
- High resolution screen (1024 x 768 pixels) compatibility, which can simultaneously show four response plots along with the standard control panels.

As you can see BassBox offers a pretty impressive list of features and analysis 'tools', and all of these appear to be of practical use when designing bass enclosures, rather than just adding 'bells and whistles' to impress the user.

The impression of a well thought out and nicely 'focused' program is further reinforced by the 115-page manual supplied with the software, which is refreshingly lucid and uses a range of sample screen shots, response plots and diagrams at pertinent points through the text.

### Trying it out

Our review copy of BassBox 5.1 included an additional version 5.15 update disk, which was duly installed after the main program was up and running.

There was no obvious change in the operation of BassBox after this

was loaded, so we can only assume that version 5.15 is largely a 'bug fix' upgrade.

Thanks to the familiar nature of the Windows operating environment and the quite intuitive layout of the BassBox screens and labels, we had little difficulty in working our way through the program's features. It was interesting to note that despite the range of detailed analysis routines available in BassBox it could be used at a quite low level. After typing in just the basic parameters for a driver (Fo, Qts and Vas), we were able to design a suitable vented cabinet in short order.

This sort of 'quick and dirty' design procedure appears to be quite practical in BassBox, due to the way it can interpolate a limited range of input data, and automatically offer the user an 'optimum' design for the current driver. This can then be fine-tuned to suit your needs, using the Box Designer and other BassBox tools. As you would expect of course, the final results will be more accurate if a complete set of driver parameters are used during this procedure.

When it comes to fine tuning an enclosure design we were particularly impressed with BassBox's Box Designer section, which automatically provides a quick 'preview'

response plot when any parameter has been changed.

While the small preview screen makes no pretences as to its accuracy — there aren't any vertical or horizontal scales — it allows to user to immediately judge the results of a change, without the need for a full analysis and plotting cycle. With this arrangement, you can quickly 'home in' on the desired result, then return to the main screen and plotting routine to confirm your design's performance.

Virtually all other aspects of BassBox were similarly well thought out and easy to use. The program's screens and functions operate in a quite intuitive manner, so we had little need to consult the user manual or on-line help system while completing a number of test designs. In short, we were very impressed with BassBox's operation and user interface.

The only problem we *did* come across was the way BassBox responded when the computer had used almost all of its system resources — or in effect, had ran out of 'horsepower'. This came to light when using a fairly modest '386-based machine, where the program would labour for some time and then fatally crash as it attempted access the built-in speaker database, or print to a Postscript printer.

Since the above machine's configuration is the *minimum* recommended by the program's literature though, we can't really regard this as an overall criticism of BassBox, which rockets along smoothly on more potent machines. In practice, though, we would recommend that you run BassBox on a '486 (or better) computer that's equipped with at least 4MB of system RAM.

As a complete design package for bass enclosures then, we can highly recommend BassBox as a very 'user-friendly' but surprisingly powerful CAD system.

With the ability to deal with compound-mounted speakers in both double and triple-chamber bandpass enclosures, it's very much in tune with the latest trends in loudspeaker design. And with a \$189 price tag, it may well be within the reach of many non-professional users.

BassBox 5.1 is available from Audiosoft at 128 Oriel Road, West Heidelberg, Melbourne 3081; fax (03) 9497 4441.

They are also offering both BassBox and CALSOD 1.30 in a bundle for \$249, which sounds like a very interesting deal indeed... ♦

# Silicon Valley NEWSLETTER



## Chip market to grow 26% in 1996

The worldwide computer chip market is predicted to achieve a fifth year of better than 25% growth in 1996 and will continue to grow at an average of 21.3 percent through 1998, according to the Semiconductor Industry Association in a forecast presented at the group's 19th annual forecast dinner. Global semiconductor sales were predicted to have risen 43.7% to US\$146.4 billion in 1995.

According to the World Semiconductor Trade Statistics (WSTS), the industry statistics organisation within the SIA, the global semiconductor market will grow by more than 26% in 1996 to US\$185.1 billion. Chip sales will climb another 18.1% in 1997 to US\$218.6 billion, and 19.6% in 1998 to US\$261.5 billion.

The memory chip market will be leading the way in 1996 with an estimated 40% increase. Worldwide sales of microprocessors and other micro products will grow 22.4% in 1996 to US\$41.2 billion.

Geographically, Japan will remain the second largest regional market at US\$47.7 billion in 1996, with a 17.8% growth rate. The European market will rise 26.6% next year to US\$36.2 billion, according to the trade group.

"Perhaps we are in fact entering the Golden Age of the electronics industry, where the products spawned by our industry are revolutionising society and the way we live, work and play — thus triggering a period of sustained high growth", said Ray Stata, Analog Devices chairman and chief executive officer, who delivered the forecast address at the SIA dinner.

Not surprisingly, the mood among the 1000 chip executives attending the SIA's annual forecast and awards dinner was festive. With four years of booming chip demand behind them and perhaps a decade or more of healthy growth ahead, there was little need to be overly serious at what the event's MC, Fred Hoar, called "one of Silicon Valley's great annual geek fests."

Few seemed bothered that the SIA

appears to have fallen back on an old habit of miscalculating the growth of its own industry. Last year the SIA forecast growth of 15% for 1995, off a bit from the 44% real growth.

Ray Stata said "The forecasts were off, but the actual results were good and it looks like 1996 will be more of the same."

## SIA honours IC inventor Jack Kilby

In an announcement laced with irony, 72-year-old Jack Kilby was honoured at the annual SIA dinner as recipient of the Robert N. Noyce award for pioneering the semiconductor industry — and, by extension, the information age.

In 1958, as an engineer for Texas Instruments, Kilby invented the integrated circuit. Almost simultaneously, Noyce made a similar discovery at Fairchild Camera & Instruments in Mountain View.

TI and Fairchild fought huge PR and legal battles in the 1960s, over whether Kilby or Noyce deserved the title of inventor of the integrated circuit. Noyce died in 1990 and the award was created in his name to honour excellence in the semiconductor industry. The integrated circuit, of course has become 'the plankton in the food chain of a trillion dollar electronics industry', said Pat Weber, vice chairman of TI, who called Kilby "a gentle giant who changed the world".

In accepting the award, Kilby said he is personally very pleased to see the impact his invention has had on the world and on the US\$150 billion market it has created. "It's been exciting to watch", he said.

## Korean DRAM exports booming

Meanwhile, in South Korea, the country's three largest chip makers announced that heavy demand for DRAM memories had sent their exports of semiconductors soaring during the first 10 months of 1995.

Officials for Samsung, LG Group, and Hyundai said the chip export boom was

likely to continue throughout 1996, because of demand for memory-hungry multimedia software requiring powerful PCs. The top three Korean chip makers said their exports had risen about 60% to a combined US\$10.7 billion in the first 10 months of the year, and could reach US\$18 billion in 1996. The chip exports accounted for more than a tenth of South Korea's total exports of US\$101.94 billion.

## Two of Intel's rivals to merge

In a surprise move that could put some pressure on Intel in the microprocessor market, Advanced Micro Devices announced it has agreed to merge with competitor Nexgen, in an effort for the two companies to compete more effectively with Intel in the multi-billion dollar PC processor market. Under the terms of the all-stock deal, valued at US\$865 million, AMD will buy Nexgen of Milpitas and produce Nexgen's Pentium and Pentium Pro-compatible 586 and 686 processors.

AMD and Nexgen executives said they have concluded that to be successful in their struggle against market-dominating Intel, they must combine their respective strengths in processor design and manufacturing.

AMD chief Jerry Sanders III said it was clear that his company could not compete on its own against the "vast resources of Intel", which he said spends seven times as much on chip factories and has a market value greater than that of General Motors.

"It is with tremendous pleasure that I make this announcement," said Atiq Raza, CEO of Nexgen since 1991. "The combination creates an opportunity as hasn't been seen before."

Following the merger, AMD will abandon its K6 processor development program and manufacture Nexgen's 686 chip at its state-of-the-art factory in Austin, Texas. However, Sanders said AMD will go forward with its much-delayed K5 chip, which is due out next summer. Once those projects are finished, AMD and Nexgen will combine

their design resources to launch future generations of chips.

"Our goal is 30% of the market (about 30 million chips) by 1998", Sanders said. "We think this is a major event in the chronology of the PC industry."

Analysts said that while AMD has done a good job increasing manufacturing capacity to challenge Intel, it has been slow in bringing its new K-5 Pentium clone to market. Meanwhile, Nexgen has designs on par with Intel, but didn't have the manufacturing capability.

Sanders said AMD will operate Nexgen as a subsidiary and will keep all its employees. He said Raza will serve as chief technology officer of AMD and become a corporate vice president as well as retain his titles as top executive of Nexgen.

In addition, Vinod Dham, Nexgen's chief operating officer and former Intel Pentium designer, will serve as head of the combined company's processor design teams for the sixth and seventh-generation chips.

## Cirrus to invest \$2 billion in fab

Cirrus Logic, the world's first fabless semiconductor company with sales in excess of a billion dollars, has announced plans to invest some US\$2 billion over the next five years in a variety of joint chip foundry projects that will ensure the Fremont-based company a steady supply of its popular multimedia and communications components. Cirrus also announced the financial results for its most recent quarter, showing a sales increase of 57% and profits surging 166%.

For the second quarter of its fiscal 1996, Cirrus said profits jumped to US\$33.0 million, from \$12.4 million in the same period a year earlier. Sales grew to US\$317.8 million from \$202.2 million.

Among the alliances announced by Cirrus is a joint venture with IBM to spend an additional US\$195 million during the next 18 months for new production lines at an IBM facility in upstate New York.

Cirrus said it has also formed a new joint venture with AT&T's microelectronics group to start production in 1997 at an AT&T facility in Orlando, Florida. Cirrus will own 40% of the unnamed joint venture, while AT&T will hold 60%.

Cirrus will also invest US\$90 million in the formation of a new company in Taiwan called United Silicon Inc.,

which will have the financial backing of both Cirrus, along with United Microelectronics Corp. of Taiwan and two other US chip companies whose names have not yet been made public.

Finally, Cirrus plans an expanded relationship with Taiwan Semiconductor Manufacturing Co., a foundry, calling for Cirrus to lend TSMC



**At the recent Dataquest Semiconductor 1995 Conference, Sematech chip research consortium chief operating officer Jim Owens predicted that the world chip market could reach the magical trillion dollar mark as early as 2005, or 2008 at the latest. He also predicted that the industry may well achieve these huge increases in sales volume without any of the traditional 'boom or bust' cycles.**

about US\$120 million during the next three years.

## Motorola joins DRAM alliance

Motorola has moved to become a major player in the high-stakes DRAM memory chip business by joining the three-continent DRAM alliance of IBM, Siemens and Toshiba. The alliance has

successfully developed a production-ready 64Mb DRAM, a fully functional 256Mb DRAM and is hoping to bring an even more advanced 1Gb memory device to market.

"The existing alliance clearly is one of the most powerful and successful in the industry. It's a premier team of the world's best scientists and engineers", said Dr Michael Attardo, general manager of IBM's Microelectronics Division. "We are proud of our successes. We relish the future and all of its possibilities. We welcome Motorola as the newest member of the team."

"Motorola's enthusiastic participation in this alliance underscores our commitment to provide our customers with the most advanced memory technology," said Tommy George, president of Motorola's Semiconductor Product Sector.

## National, Eveready to make new batteries


With the use of portable computers and communications devices in ever more critical business applications, National Semiconductor and the Energizer Power Systems division of Eveready Battery said they have agreed to respond to the demand for batteries that offer longer-lasting charges and require much less time to recharge. Together, the two companies said they hope to develop new intelligent battery solutions for rechargeable nickel-based battery chemistries.

The two companies have worked together on various battery projects since May 1994, particularly on charge-control and fuel gauge design. The new agreement expands the cooperative venture and sets the stage for integrating a wide range of battery chemistries from Energizer Power Systems with a series of new integrated circuits from National Semiconductor. The systems will encompass a variety of controls for intelligent battery-power packs including charge control, fuel gauging and protection circuits.

"The demand for longer battery life and shorter charge cycles has taken on a new urgency due to the increased use of portable equipment in critical business applications", said Mark Levi, National's vice president of analog marketing.

"Although battery types and their behaviour are changing rapidly to meet the needs of new portable product designs, the basic electronic solutions under joint development are adaptable across the board." ♦

# Computer News and New Products

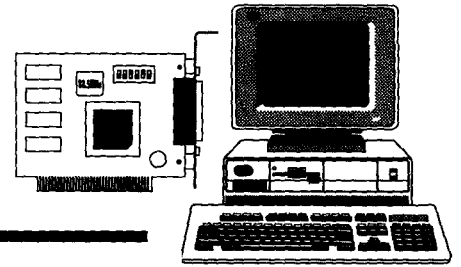

## 80C51XA development system

Ashling Microsystems, under an agreement with Philips Semiconductors, introduced the Ultra-51XA microprocessor development system for the new Philips 16-bit 80C51XA microcontroller.

The system provides a complete development environment for the Philips XA microcontroller family, hosted under Windows. It includes an in-circuit emulator operating at clock speeds up to 50MHz, 'Pathfinder for Windows', source level debugger and SEA-XA real time performance analysis system for XA applications.

A uniform user interface supports editing, C-compiling, assembling, linking, simulation, in-circuit emulation, performance analysis, code coverage measurement, software validation reporting and EPROM/EEPROM programming.

After debugging a 80C51XA microcontroller program with the Pathfinder for Windows debugger, the designer can immediately return to the WinIDEAS editor, at the appropriate line in the source file, to change the source program. With a single keystroke, WinIDEAS re-compiles and re-links the

program, downloads it to the in-circuit emulator and resumes debugging at the same line in the source file.

For further information circle 161 on the reader service coupon or contact Metromatics, PO Box 315, New Farm 4005; phone (07) 3358 5155.

## Smart sound card

The MA594 is an intelligent 16-bit



sound card that combines recording and playback with control functions. It is compatible with Microsoft's WAV audio file format which has been adopted by virtually all PC-based sound cards, including Soundblaster. Fourteen sampling frequencies are available, including standard multimedia frequencies of 11, 22 and 44kHz. Five data formats are supported: 16-bit linear PCM, A-Law and u-Law PCM, 8-bit linear PCM and IMA ADPCM.

On-board sound memory supports EPROM and Flash devices. An optional MA502 adaptor enables playback from one or two PCMCIA memory cards. With two 40MB Flash cards, maximum playback time is over two hours with a 5kHz audio bandwidth. The I/O includes Line In/Out ports, microphone and speaker lines, serial port, 16 parallel lines and IC bus interface.

The on-board control software (VPM) includes routines to compress (2:1) 16-bit linear PCM files to an A-Law format and to program sound files from PC disk into Flash memory cards. The VPM software allows over 4000 audio segments or phrases to be linked, to provide complex announcements.

An optional embedded assembler (VPMASM) is available for custom control software development. User

## 'Multimedia' computer case


Rod Irving Electronics is now stocking a 'Multimedia' computer case, which has inbuilt stereo loudspeakers to save desk space and provide a tidier system than when the usual separate speaker boxes are used.

The case measures 360 x 400 x 135mm (W x D x H), and in addition to the inbuilt speakers also includes both a 200W switchmode power supply and a compact stereo amplifier with an output of 2 x 10W.

The amplifier provides both treble and bass tone controls as well as a volume control, all conveniently accessible from the front of the case. At the rear are mic and auxiliary audio inputs, and optional external speaker sockets.

Other features of the computer case include a three digit seven-segment LED speed/status display, three front control buttons (power, reset and turbo) and three status LEDs (HDD, turbo and power).

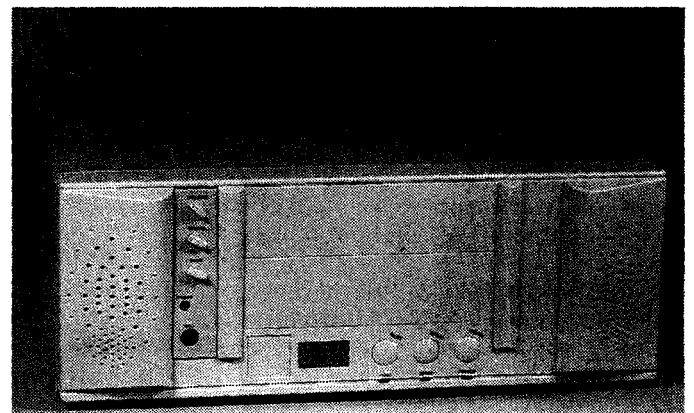It also features eight push-out rear card slots, provision for mounting a 3.5" HDD and up to two 5.25" or CD-ROM drives,



a slide-on top with five rear screws and all motherboard and expansion card mounting hardware.

Priced at only \$149.65, the Multimedia Computer Case has the catalog number X11084 and available from all RIE sales outlets.

control software can also be written in an on-board proprietary programming language (Voice) which is optimised for applications needing simultaneous voice output and control functions.

For further information circle 162 on the reader service coupon or contact Microcontrol (Australia), PO Box 1020, Pymble 2073; phone (02) 449 1546.

### 486 CPU card has on-board VGA controller

Aeon Technology's new SBC-450 is a half-size all-in-one single board 486 computer with an on-board VGA CRT/flat panel controller. The SBC-450 is fully PC/AT compatible.

The on-board VL-bus VGA CRT/flat panel controller uses the C&T 65545 chipset and supports resolutions up to 1024 x 768 in 16 colours or 800 x 600 in 256 colours.

The on-board features include two high speed RS-232 serial ports with 16C550 UARTs, one bi-directional parallel port, and an IDE hard drive controller and a floppy controller. If program execution is halted by a program bug or EMI, the board's 15 stage watchdog timer can automatically reset the CPU or generate an interrupt.

The unit provides two 72-pin SIMM sockets for on-board DRAM, of up to 64MB. Industry standard PC/104 modules can be added to meet system requirements.

For further information circle 163 on the reader service coupon or contact Amtex Electronics, PO Box 285, Chatswood 2057; phone (02) 805 0844.

### Power system management


Testing and Certification Australia has introduced Polylogger II — the successor to the Polylogger used by power authorities throughout Australasia.

Polylogger II provides simultaneous

three phase voltage and current logging and computer analysis in a Windows environment. The new instrument offers measurement of real and apparent power, power factor and energy; quality of supply analysis features including logging of power surges and sags; increased memory; and multi-voltage capability.

The unit is designed to carry out load and voltage surveys, load balancing, voltage complaint investigations, and energy auditing.

Features of the software include

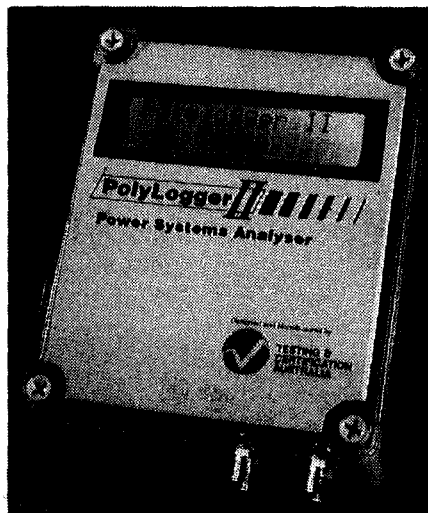

mouse operation, direct colour printing of graphs, zoom and compression of graphs, statistical analysis and comprehensive help.

For further information circle 164 on the reader service coupon or contact Testing and Certification Australia, 14 Nelson Street, Chatswood 2067; phone (02) 411 5180.

### Data acquisition in Excel

Iotech has released DaqViewXL, a Windows 3.1 and Windows95 compatible data acquisition and display application that seamlessly integrates into Microsoft Excel spreadsheet software.

DaqViewXL is the first entry in Iotech's new series of products designed as 'software components' that can be launched and operated from inside a 'home' application such as Excel.

DaqViewXL enables users to set up data acquisition applications from within Microsoft Excel without programming, and provides graphical access to all the functions of Iotech's parallel port based DaqBook, plug-in DaqBoard or DaqPCMCIA card data acquisition products.

DaqViewXL permits hardware configuration for range, trigger condition, sampling rate and signal conditioning via a graphical interface that eliminates all programming.

It also provides a strip-chart recorder-like display that can be opened with Excel to view acquired data in real time. DaqViewXL's installation results in the addition of a new tool bar in Excel, providing access to all of DaqViewXL's features from within Excel.


For further information circle 165 on the reader service coupon or contact Scientific Devices Australia, 2 Jacks Road, South Oakleigh 3167; phone (03) 9579 3622.

### Low cost version of Visual Designer

Intelligent Instrumentation has announced a low cost version of the Visual Designer Application Generator Software (PCI-20908S-1) for students, colleges, universities and other academic institutions.

Visual Designer is a Windows-based application generator for PC-based data acquisition and control. It allows users to develop custom applications by drawing block diagrams (FlowGrams) of their applications rather than coding the applications with a programming language. Customisable displays include
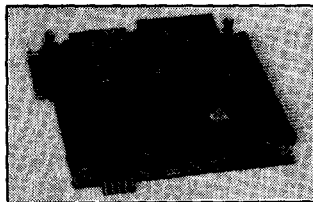
## Australian Computers & Peripherals from JED... Call for data sheets.



### Australia's own PC/104 computers.

The photo to the left shows the JED PC540 single board computer for embedded scientific and industrial applications.

This 3.6" by 3.8" board uses Intel's 80C188EB processor. A second board, the PC541 has

a V51 processor for full XT PC compatibility, with F/Disk, IDE & LPT. Each board has two serial ports (one RS485), a Xilinx gate array with lots of digital I/O, RTC, EEPROM. Program them with the \$179 Pacific C. Both support ROMDOS in FLASH. They cost \$350 to \$450 each.

### JED Microprocessors Pty. Ltd


Office 7, 5/7 Chandler Road, Boronia, Vic., 3155. Phone: (03)9 762 3588 Fax: (03)9 762 5499

**\$125 PROM Eraser, complete with timer**

**\$300 PC PROM Programmer.**
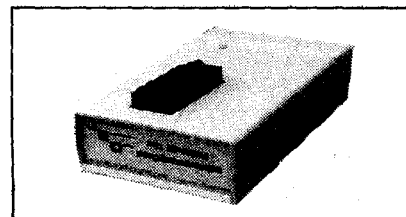
### Need to programme PROMs from your PC?

This little box simply plugs into your PC or Laptop's parallel printer port and reads, writes and edits PROMs from 64Kb to 8Mb. It does it quickly without needing any plug in cards.



(Sales tax exempt prices)

## COMPUTER NEWS AND NEW PRODUCTS

plots, instrument panels and control panels. The software supports a variety of GPIB (IEEE-488) instruments and serial devices.

For further information circle 166 on the reader service coupon or contact Kenelec, 2 Apollo Court, Blackburn 3130; phone (008) 335 245.

### 68HC11 in-circuit emulator

Technology Affair has released the G5 probe for the WICE 68HC11 low

cost in-circuit emulator, further extending the support to the 68HC11G5, 68HC711G5 and 68HC11G7 family of Motorola devices.

The system provides real time emulation for the Motorola 68HC11 family, in both expanded and single chip modes, at speeds up to 20MHz.

It supports symbolic debugging for a wide range of assemblers and C compilers, and incorporates hardware breakpoints with break on address, address

range, memory read and memory write.

The emulator communicates with a host PC via a standard RS-232 COM port at 115.2Kb/s, allowing fast uploading and downloading of files in Motorola S-record, Intel hex and Tektronix hex formats.

The host PC software supplied with the emulator provides a windowed user interface that monitors user selectable memory locations, stack locations, CPU registers and breakpoint configurations.

It incorporates standard features like single stepping, breakpoints, on-line symbolic assembler and disassembler, fast file downloading, logic analyser trigger output, EEPROM erasing and programming, plus a range of commands for searching, displaying and modifying memory and CPU registers.

It also includes advanced features like peripheral simulation, which allows the target software to use the host PC as a peripheral device, for simulating target hardware in real time during software development.

For further information circle 167 on the reader service coupon or contact Technology Affair, 57 Wessex Street, Carine 6020; phone (09) 246 4810.




## PC Breeze II

"PCBreeze really is a breeze."

Herman Nacinovich, ETI review "It's a Breeze" Jan. 1990.

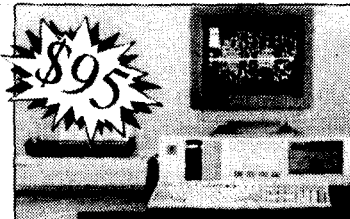The First Truly Affordable  
Software for Printed Circuit  
Board Artwork  
Easy to Use and Learn  
Pop up Menus and  
Mouse support  
50 mil (1.27 mm) Grid  
Variety of Pad and Line sizes  
Interactive and Netlist  
Autorouting Text  
and Component Overlay



### Hardware Supported

448K IBM PC/XT/AT/PS2 or compatible  
CGA, EGA, VGA & Hercules graphics  
HP-GL, DM-PL, PostScript devices  
Epson FX/LQ type dot matrix printers  
Microsoft Mouse or compatible device



**KEPIC Pty Ltd**

4 Steinbeck Place Spearwood 6163

Western Australia



Phone/ Fax: (09) 418 5512





Free shipping within Australasia  
Available direct from above address

READER INFO NO. 29
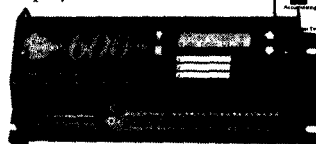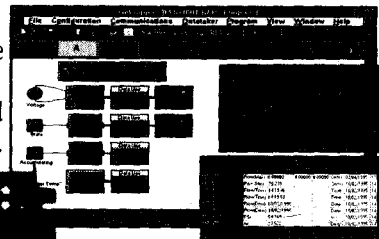
## Point-and-click data logging

Simply point and click to set up a data logging schedule using DeLogger, the new Windows™ programming and display software for Datataker.



DeLogger will not only program your logger, but give you real-time trend plots and tables.

Data logging with Datataker really is this simple.

Just connect thermocouples, RTDs, strain gauges, load, flow, level, pressure, meteorological, ... in fact, any sensor you like. No add-on cards. No signal conditioning. No complex programming.

Datataker does it all in a stand-alone logger that's compatible with all computers. Notebooks to mainframes.

Datatakers are available with one to hundreds of channels. Alarms, calculations and a full range of statistical functions are standard.

To find out how simple data logging can be, call the data acquisition experts ...



**DATA ELECTRONICS**  
Phone (03) 9764 8600  
(02) 9971 7994

ACN 006 134 863 AD-038-AD

## Solid state relay board

Procon Technology has released an externally mounted solid state relay output board. Manufactured in Australia, the PC-IO-LH2 board has been designed for operation in the most arduous conditions.

The boards are mounted externally and can be operated through any IBM-PC bi-directionally parallel printer adaptor interface (many PCs, notebooks and industrial PC/104 computers have compatible interfaces). The PC-BD-IO interface card is recommended for guaranteed operations and full expansion capability.

Three DIP switches select each board's address, allowing up to eight cards to be daisy chained with a single 25 way cable providing expansion up to 120 outputs. The 16 single pole single throw solid state relays are each rated at 120mA at 350V DC or peak AC.

The relay outputs can be used to control lamps, solenoids, motor contactors, and other high voltage equipment. They can also be used to switch low current analog or digital signals. Each output provides 3750V RMS isolation from the other, and from the computer circuitry, providing maximum immunity to electrical noise and maximum flexibility in the system's design.

The relays have current limiting and over temperature circuitry, enabling them to pass FCC 86.302 and other regulator voltage surge requirements, when the over-voltage protection option is used. Ideal for telecom use, they employ a low current limit suited for ground fault applications.

For further information circle 168 on the reader service coupon or contact Procon Technology, PO Box 655, Mount Waverley 3149; phone (03) 9807 5660. ♦



# SPEAKERS

## NEW SHEILDED DRIVERS

FOR

**SURROUND** Sound and **COMPUTER** Multimedia

**ME Technologies**  
(an ME Sound Pty Ltd subsidiary)  
 Post Office Box 50,  
 Dyers Crossing NSW 2429


Phone: 065 50 2254

065 50 2200

Fax: 065 50 2341

Email: [me@midcoast.com.au](mailto:me@midcoast.com.au)

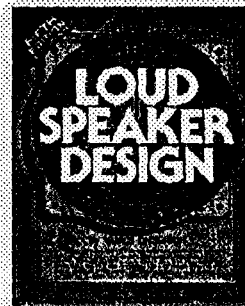Internet: <http://www.midcoast.com.au/bus/me>



WE ALSO STOCK A  
 LARGE RANGE OF  
**SPEAKER DESIGN**  
**BOOKS,**  
**AUDIO ANALYSIS**  
**SOFTWARE**  
**AND CAPACITORS**

READER INFO NO. 31

# Word Bus

**The software you need**      **The service you love**

The **only** anti-virus software supplied under contract to the entire Queensland Government.

The **only** anti-virus software chosen by the Commonwealth Government for inclusion in contract PE64.

Now detects and removes all Word Macro viruses.

Over 16,000 users in Defence - where security is paramount. Over 300,000 Australian users.

When you need anti-virus, call us for some friendly help...

Leprechaun Software  
 Tel +61 7 3823 1300  
 Fax +61 7 3823 1233

READER INFO NO. 32

## EA DIRECTORY OF SUPPLIERS

Which of our many advertisers are most likely to be able to sell you that special component, instrument, kit or tool? It's not always easy to decide, because they can't advertise all of their product lines each month. Also, some are wholesalers and don't sell to the public. The table below is published as a special service to EA readers, as a guide to the main products sold by our retail advertisers. For address information see the advertisements in this or other recent issues.

Supplier	State	A	B	C	D	E	F	G
Altronics	WA	.	.	.	.	.	.	.
Dick Smith Electronics	ALL	.	.	.	.	.	.	.
Emona Instruments	NSW	.	.	.	.	.	.	.
Geoff Wood Electronics	NSW	.	.	.	.	.	.	.
Jaycar Electronics	Eastern	.	.	.	.	.	.	.
Kalex	VIC	.	.	.	.	.	.	.
RCS Radio	NSW	.	.	.	.	.	.	.
Rod Irving Electronics	Eastern	.	.	.	.	.	.	.
Scientific Devices	VIC	.	.	.	.	.	.	.
TECS	VIC	.	.	.	.	.	.	.

### KEY TO CODING

A	Kits and modules	D	Components
B	Tools	E	IC chips and semiconductors
C	PC boards and supplies	F	Test and measuring instruments
		G	Reference books

Note that the above list is based on our understanding of the products sold by the firms concerned. If there are any errors or omissions, please let us know.

## Electronics Australia Reader Services

**SUBSCRIPTIONS:** All subscription enquiries should be directed to: Subscriptions Department, Federal Publishing Company, P.O. Box 199, Alexandria 2015; phone (02) 353 9992.

**BACK ISSUES:** Available only until stocks are exhausted. Price A\$7.50 which includes postage within Australia only. **OVERSEAS READERS SHOULD ADD A FURTHER A\$2.50 FOR EVERY BACK ISSUE REQUIRED.**

**PHOTOCOPIES:** When back issues are exhausted, photocopies of articles can be supplied. Price \$7.50 per project or \$15 where a project spreads over several issues.

**PCB PATTERNS:** High contrast, actual size transparencies for PCBs and front panels are available. Price is \$5 for boards up to 100sq.cm, \$10 for larger boards. Please specify negatives or positives.

**PROJECT QUERIES:** Advice on projects is limited to postal correspondence only and to projects less than five years old. Price \$7.50. Please note that we cannot undertake special research or advise on project modifications. **Members of our technical staff are not available to discuss technical problems by telephone.**

**OTHER QUERIES:** Technical queries outside the scope of 'Replies by Post', or submitted without fee, may be answered in the 'Information Centre' pages at the discretion of the Editor.

**READER SERVICES BULLETIN BOARD:** (02) 353 0627, 24 hour access.

**PAYMENT:** Must be negotiable in Australia and payable to Electronics Australia. Send cheque, money order or credit card number (American Express, Bankcard, Mastercard or Visa card), name and address (see form).

**ADDRESS:** Send all correspondence to: The Secretary, Electronics Australia, P.O. Box 199, Alexandria NSW 2015; phone (02) 353 0620.

**PLEASE NOTE THAT WE ARE UNABLE TO SUPPLY BACK ISSUES, PHOTOCOPIES OR PCB ARTWORK OVER THE COUNTER.**

Name:.....

Address:.....

State:.....Postcode:.....

Back issues:.....

Photocopies:.....

Amount: A\$.....  
Signature:.....(Unsigned orders cannot be accepted.)

Method of Payment: (Please circle correct method.) Credit card / Cheque / Money order.

Credit cards accepted:

Mastercard, American Express, Visa Bankcard (please circle applicable card).

Expiry date:.....

## ADVERTISING INDEX

Active Electronics	85
Allthings Sales & Services	52
Altronics	96-98
Aspac Australia	136
AV-COMM	23
Bainbridge Marine	135
Baltec Systems	71
Campad Electronics	112/113
Contan Audio	17
Data Electronics	144
Dick Smith Electronics	54-57
Don Alan Electronics	112/113
EA subscriptions offer	131
Electronic Formation Service	112/113
Fastron Australia	135
FPC Marketing	95
Geoff Wood Electronics	65
Hewlett-Packard Australia	130
Hinton Information Service	85
Hi-Tech Software	137
Icom Australia	OBC
Instant PCBs	112/113
Jacques Electronics	94
Jaycar Electronics	86-89
JED Microprocessors	143
Keptic	144
Leprechaun Software	145
Link Technologies	52
Memory International	129
ME Technologies	145
Nilsen Technologies	IFC
Oatley Electronics	IBC
Obiat	95
Objectives	64
Peter Lacey Services	44
Phoenix Radio	112/113
Protel Technology	137
Resurrection Radio	111
Recom Elect. Components	111
Rod Irving Electronics	72-75
Scan Audio	17
Solar Corporation	85
hStar International	71
TECS Wholesale	81
Todd-Forbes Publishing	52
Tortech	112/113
VAF Research	11

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.



## UNIVERSAL IR REMOTE

**NEW** LEARNING UNIVERSAL IR REMOTES replace up to 8 dedicated units: **\$45**

## KITS

### 1-CH UHF FOR CENTRAL LOCKING

Our single channel UHF receiver kit has been updated to provide provision for central locking!! Key chain Tx has SAW resonator, see SC Dec 92. Compact receiver has pre-built UHF receiver module, and has provision for two extra relays for vehicle central locking function. Kit comes with two relays. **\$36** Additional relays for central locking **\$3** ea. I-Ch Tx kit **\$18**

**LOW COST 1-2 CHANNEL UHF REMOTE CONTROL** compact keying transmitter kit, 1/2 million codes, receiver has 2A relay contact output, PCB and all components kit. 1 channel Tx kit **\$11**, 2 channel Tx kit **\$18** Rx kit **\$22** extra components for 2 channel Rx operation (extra decoder IC and relay) **\$6**

**ECG** Solder masked and silk screened PCB and software on 3.5" disk only (See EA July 95) **\$10**

**MASTHEAD AMPLIFIER** High performance low-noise masthead amplifier covers VHF-FM-UHF and is based on a MAR-6 IC. Includes two PCBs, all on-board components. For a limited time we will include a suitable plugpack to power the amplifier from mains for a total price of: **\$25**

**FM TRANSMITTER MK3 KIT** 200m range, has a pre-wound RF coil. 6V at 20mA PCB 46 x 33mm **\$18**

**SPEAKER SIREN** Uses driver circuit from our Protect Anything Alarm kit, gives 95dB sound pressure of irritating sound. **BARGAIN \$12.**

**PLASMA BALL KIT:** PCB and components kit, needs any 240V light bulb **ON SPECIAL \$20.** Gassed, but faulty laser tubes that give a bright red display with this kit: **\$10**

## MORE ITEMS & KITS

Poll our **(02) 579 3955** fax number to find out how to get our item and kit lists. **MANY MANY MORE ITEMS AND KITS THAN THOSE LISTED HERE!** Ask for these lists to be sent with your next order.

## STEREO SPEAKER KIT

Total of four speakers to make two 2-way speakers. Quality European cloth surround bass - midrange speakers, used in upmarket stereo televisions, rectangular, 80 x 200mm. Tweeters are good quality cone types, 85mm square. Two woofers & two tweeters. **\$16**

## HF FLUORO BALLASTS

European, slimline HF fluorescent lamp ballasts: flicker-free start, better efficiency, no flicker, no strobing effect, no buzz, much reduced RF interference. Some include a dimming option (with external 100k pot or 0-10V DC source). Some use a separate filter choke (supplied, 16x4x3.2cm). Wattage ratings from 16 to 150W. Price **\$20 to \$26.**

## BATTERY CHARGER

This simple kit combines a 12 hour mechanical timer to set the charge period and an easy-to-build hard-wired constant current. Resistors supplied so you set the required current. Can be powered from your existing charger or any suitable DC supply. Great for gel cells. **\$12**

## MOTOR CONTROL

**COMPUTER CONTROLLED STEPPER MOTOR DRIVER KIT** drives two stepper motors: 4, 5, 6 or 8-wire stepper motors from an IBM computer parallel port. Needs a separate power supply for motors. Includes software on a 3.5" disk, detailed manual, circuit diagrams & descriptions. Great low cost educational kit. With two stepper motors (you select type) **\$44** Without stepper motors **\$32**

**MOTOR SPEED CONTROLLER PCB** Simple circuit controls small DC motors up to 2A. Adjustable duty cycle from 0 to 100% **\$11.** For larger motors, use BUZ11A MOSFET **\$3**

## WE'RE ON THE WEB

We now share a web site with DIY Electronics. See & download our latest catalog & other info. Over 300 kits. Send e-mail orders. Explore! <http://www.hk.super.net/~diykit>

## LASERS

**HELIUM-NEON** 633nm red laser tubes from new and near new equipment. Suitable for light shows: Output power in the range of 2.5 to 7.5mW. Includes our 12V Universal Laser power supply MkIV. (No problems with our new transformers.) **ON SPECIAL** at a reduced price of **\$80** for a 2.5-4mW tube and supply. **\$130** for a 40-7.5mW tube and supply.

**COMPACT LASER POINTER** 5mW/670nm in 75 x 42 x 18mm plastic case with key chain. Uses 2 1.5V N batteries (included). **\$80**

**AIR-COOLED ARGONS** Used 30-100mW argon-ion head blue/green output. Includes details of power supply and other information: head only. **\$250 to \$350** (depends on hours of use)

**VISIBLE LASER DIODE KIT** 5mW 670nm visible laser diode and collimating lens, with housing and APC driver kit EA 9/94 **SPECIAL \$40** Suitable case and battery holder (as in EA 11/95): **\$5**

**VISIBLE LASER DIODE MODULES** Industrial quality 5mW/670nm laser diode modules. Overall dimensions: 11mm dia x 40mm long. Have APC driver built in and need about 50mA from a 3-6V supply. **\$55** 12 x 43mm version in aluminium case, better optics **\$65**

## GEIGER COUNTER

Ready made Geiger counter detects dangerous Beta and Gamma rays. Audible and visual (LED) output, tube unplugs from main unit. Can be connected to a computer (serial port). Powered from separate 12-14V AC or DC supply. **\$75**

## MISCELLANEOUS


**MAGNETIC CARD READERS** will read virtually any card **\$75**

**PELLIER DEVICES** Solid state, can be used to make a thermoelectric cooler - heater. Basic info included. 12V-4.4A **\$25**

Two thermal cut-out switches and a 12V DC fan to suit **\$10**
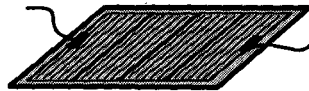
## 12V-2.5W SOLAR PANEL

US amorphous glass solar panels only need terminating and weather proofing. Includes clips and backing glass. Very easy to complete. Size: 305x228mm, Voc 18-20V, Isc 250mA. **SPECIAL \$20** ea, 4 for **\$60.**



Efficient switching regulator kit also available: suits 12-24V batteries, 0.1-1.6A panels, **\$27.** Also available, simple, efficient shunt regulator kit **\$5**

## CCD CAMERA-VCR SECURITY SYSTEM

Ready made PIR detector module and learning remote control combination can trigger any domestic IR remote controlled VCR to **RECORD** human activity within a 6m range with an 180° view. Starts VCR recording at first movement and ceases recording a few minutes after the last movement has stopped. Just like commercial CCD-video recording systems costing \$1000's!! No connection needed to your existing VCR. IR detector module, control kit, IR learning remote control and instructions **\$90** or **\$65** when purchased with our CCD camera. Previous CCD camera purchasers can claim reduced price with proof of purchase.

**TINY PCB CCD CAMERA** with auto iris lens, 0.1lux 320k pixels, IR responsive, has 6 IR LEDs on PCB, almost matchbox size! **\$180**

**IR ILLUMINATOR** Has 42 high-output 880nm IR LEDs (30mW @ 100mA ea). Operates from 10-15V DC, current adj range 5-600mA. Suits our CCD camera: **\$40**

**VHF MODULATOR** for CH7-11, to connect CCD camera to a TV set. Operates TV if modulator within 50cm of the antenna. No wires! **\$12**

**SOUND FOR CCD CAMERA** High gain audio amp, electret mic, speaker **\$10**

## DOT MATRIX LCDs

New Hitachi LM215 400 X 128 dot matrix LCDs in an attractive housing. Driver ICs fitted but needs external controller. Effective display size 65 x 235mm. **\$25** ea. or 3 for **\$60**

## LENSES

**PROJECTION LENS** Brand new, precision angled projection lens. Overall size 210x136mm. High-impact Lexan housing with focal length adjustment. When disassembled yields three 4" diameter lenses convex-concave, convex-convex, concave. Very limited quantity. **\$35**

**TOMINON HIGH POWER LENS** These 230mm (1:4.5) lens have never been used. Contain 6 coated glass lenses, symmetric, in black aluminium case. Scale range from 1:10 to 1:1 to 10:1. Applications include high quality image projection at macro scales, and large format portrait photography **\$45**

## VEHICLE COMPUTER

Originally for bicycles, these suit any moving vehicle with wheels! 9-function computer with speed, average speed, maximum speed, distance, odometer, timer, scan, freeze frame memory, and a clock. Microprocessor circuitry can be adapted to work with almost any wheel diameter. Divide the wheel diameter in millimeters by 6.8232, and program the result into the computer. **\$32**

## 3.5 DIGIT LCD METER

**NEW** Panel meter, 200mV, 1999 count, 9-12V @ 1mA, 0.5% accuracy, auto polarity & over-range indication, 13mm char height. 100MΩ I/P, 68 x 44mm. **\$27**

## PC-CONTROLLED SWITCH

Control up to 4 appliances with this 4-channel programmable driver for high-power relays. Can be controlled via the parallel or serial port of a computer (has opto-isolators). Includes software, 2 assembled and tested PCBs, four 10A relays. **\$92**

## NIGHT VISION

**IR 'TANK SET'** Components for a very responsive IR night viewer. Construction is up to you. New IR tube as used in older style military tank viewers. Needs IR illumination, very sensitive, even responds to 940nm LED illumination. Kit includes our miniature night viewer power supply and instructions. **\$80**

**INTENSIFIED NIGHT VIEWER** Parts to make a 3-stage first generation night scope that gives good vision in starlight! Includes a 3-stage fibre optically-coupled image intensifier tube, EHT power supply kit which operates from 6 to 12V, and sufficient plastics to make a monocular 'scope. 25mm version **\$270**, 40mm version **\$300**. Also available, a quality Peak brand Iox 'plalupe' as an eyepiece **\$18**. See SC Sept. 94.

# OATLEY ELECTRONICS

PO Box 89, Oatley NSW 2223

Phone (02) 579 4985

Fax (02) 570 7910 or 579 3955

orders by email: [oatley@world.net](mailto:oatley@world.net)

major cards accepted with phone and fax orders

P&P most orders Aust \$6.

ICOM

Count on us!



## **Any port in a storm, but don't rely on just any radio.**

Reliable communication at sea is assured with the Icom VHF Marine Transceiver range.

Choose from our heavy duty handhelds with optional low security scramblers ...there's the IC-M10; the IC-M15, waterproof up to a depth of 1 metre for 30 minutes; and the IC-GM1500, approved by the Australian Maritime Safety Authority for GMDSS (Global Maritime Distress and Safety System) use. Or the quality and reliability of our mobiles ...the IC-M58 or IC-M126DSC, both with digital SELCALL capabilities and scrambler facilities.

To get the full story talk to the marine communications experts at Icom or your nearest Icom dealer.

Call free on 1800 338 915 or write to Icom Australia Pty. Ltd.

7 Duke St Windsor Victoria 3181 P.O. Box 1162

Ph: (03) 9529 7582. Fax: (03) 9529 8485. A.C.N. 006 092 575