

TEST AMP BEHAVIOR WITH A REACTIVE LOAD BOX

# audio **X**PRESS

THE AUDIO TECHNOLOGY AUTHORITY

AUGUST 2003

US \$7.00 Canada \$10.00

Continuing *Audio Electronics*, *Glass Audio* & *Speaker Builder*

QUALITY  
AM Sound  
with a **TUBE**  
**RECEIVER**

Building a  
**BETTER HORN**

a **SURE FIX** for  
**DYNACO TUNERS**


Restoring  
**CLASSIC** tweeters

An **ITALIAN**  
version  
of **THOR**

design YOUR OWN  
transmission line

TIME-DELAY  
circuit for  
SYSTEM CONTROL

www.audioXpress.com

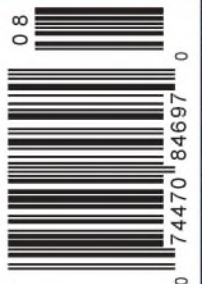

0 74470 84697 0



# Over the Top

Music performance and craftsmanship that exceed your expectation in every way

## Compass DANCER SERIES

### Compass DANCER SERIES DESIGN HIGHLIGHTS:

- Carbon-paper woofer cone
- Silk-fabric soft dome tweeter; Ceramic type on some models
- Innovative magnet flux design with corrective copper elements on all drivers, resulting in significantly reduced third and second harmonic distortions
- Cast aluminum driver frame
- Hand picked, matched-pair drivers on all models
- Phase coherent crossover designed by world renown master of speaker design, built with components of the highest quality and thoroughly tested with digital-based measuring equipment
- Massive, sonically dead front baffle which places drivers in a fine-tuned physical arrangement
- Multi-chamber reinforced cabinet with solid wood side panels, handcrafted to the highest furniture grade

### Behind the Scene

Dr. Joseph D'Appolito has been working as consultant for Usher Audio since early 2001. A world renown authority in audio and acoustics, Dr. D'Appolito holds B.S.E., S.M.E.E., E.I. and Ph.D. degrees from MIT, MIT and the University of Massachusetts, and has published over 20 journal and conference papers. His most popular and industrial focus child, however, has to be the MIT loudspeaker geometry, commonly known as the "D'Appolito Configuration," which is now used by dozens of manufacturers throughout Europe and North America.

Dr. D'Appolito designs crossovers, specifies cabinet design, and tests prototype drivers for Usher Audio, all done in his private lab in Boulder, Colorado. Although consulting to a couple of other companies, Dr. D'Appolito especially enjoys working with Usher Audio and always finds the tremendous value Usher Audio places upon a delightful response to today's High End audio world.

With an abundance of original concepts in loudspeaker design, backed by thirty years experience in manufacturing and fortified with an eye for fashion and unparalleled attention to detail, is USHER the ideal original design manufacturer you've always been looking for? Find out the answer today by talking to an USHER representative.

## USHER

USHER AUDIO TECHNOLOGY

67, Kai-Fong Street, Sec. 1, Taipei 100, Taiwan

Tel: 886 2 23816299 Fax: 886 2 23711053

Web site: [www.usheraudio.com](http://www.usheraudio.com) E-mail: [usher@ms11.hinet.net](mailto:usher@ms11.hinet.net)



# The Process of Design.

## DRIVERS:

- ▶ ATC
- ▶ AUDAX
- ▶ AUDIO TECHNOLOGY
- ▶ ETON
- ▶ FOSTEX
- ▶ ILLUSION AUDIO
- ▶ LPG
- ▶ MAX FIDELITY
- ▶ MOREL
- ▶ PEERLESS
- ▶ SCAN-SPEAK
- ▶ SEAS
- ▶ VIFA
- ▶ VISATON
- ▶ VOLT

## COMPONENTS:

BOLEN HEPTA-LITZ AND STANDARD INDUCTORS AND CAPACITORS - THE CHOICE OF MANY HIGH-END SPEAKER MANUFACTURERS.

## HARDWARE:

POWER RESISTORS, L-PADS, CABLE, ABSORBING AND DAMPING MATERIALS, GOLD SPEAKER TERMINALS, GOLD BANANA PLUGS AND BINDING POSTS, GRILL FASTENERS, PORT TUBES AND TRIM RINGS, PAN HEAD SCREWS, SPIKES AND TEE NUTS WITH ALLEN HEAD BOLTS AND PLenty MORE...

CUSTOM COMPUTER AIDED CROSSOVER AND CABINET DESIGN

HOW TO BOOKS



When designing a loudspeaker, the initial driver considerations and final driver choice can make or break a project. To ensure your success - you want the most complete information and specifications at your finger tips - the Solen catalog.

Order the **FREE** Solen catalog and CD - containing a wide selection of quality drivers - with complete manufacturer's spec sheets, as well as applications in detail on woofers, with predicted response in different sealed and vented enclosures. It is a valuable resource that will bring out the possibilities in your designs.

## Order the **FREE** Solen CD Catalog.

Forward your request by phone, fax, mail or email - or fill in the online request form at [solen.ca](http://solen.ca).



Name:	_____
Address:	_____ _____
State/Prov:	_____
Zip/Postal Code:	_____
Country:	_____
Tel:	_____
Email:	_____



**SOLENE INC.**

4470 Avenue Thibault  
St-Hubert, QC J3Y 7T9  
Canada

Tel: 450.656.2789


Fax: 450.443.4948

Email: [solen@solen.ca](mailto:solen@solen.ca)

Web: <http://www.solen.ca>

# ***Never Build Another Speaker Cabinet***

*Sit back and enjoy the music*

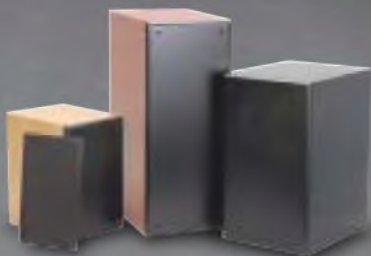

*Premium quality finished cabinets available in three real wood veneer finishes and six different sizes. Baffles are removable and blank providing limitless possibilities for custom loudspeaker designs. Complete with grills, hardware, and veneered backs.*

*To see our complete line of finished cabinets go to [www.partsexpress.com/cabinets](http://www.partsexpress.com/cabinets)*

Parts Express 725 Pleasant Valley Dr., Springboro, OH 45066-1158 Phone: 1-800-338-0531 ♦ FAX: 937/743-1677 E-Mail: [sales@partsexpress.com](mailto:sales@partsexpress.com)

**Source Code: AXM**


# Transformers & Enclosures
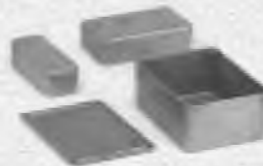
## *In Stock...*



**Torodial Power:**  
13 sizes (15 - 1500 VA)  
6 VAC - 240 VAC

**"Classic" Tube Output:**  
Single Ended (up to 75 watts),  
Push-Pull and Potted (up to 280 watts)



**Enclosures:**  
Aluminum & Steel Chassis,  
Diecast Aluminum, Plastic  
and Rack Mount

**Filament & Low Voltage**  
**Power Transformers:**  
Open & Enclosed

**"Classic"**  
**High Voltage Transformers:**  
Plate, Plate/Filament Combo  
& Filter Chokes (Open & Enclosed)



**Contact us for free catalogs & a list of stocking distributors**



# HAMMOND MANUFACTURING™

256 Sonwil Dr. - Cheektowaga, NY 14225 USA  
Phone: (716) 651-0086 Fax: (716) 651-0726



394 Edinburgh Rd., N. - Guelph, Ontario N1H 1E5 Canada  
Phone: (519) 822-2980 Fax: (519) 822-0715

**[www.hammondmfg.com](http://www.hammondmfg.com)**

### FEATURES

#### A SIMPLE, HIGH QUALITY AM TUBE RECEIVER

Tune in to clean, quality sound with this easy-to-build tube-based AM receiver.

By Scott K. Reynolds..... 6

#### EXTENDING THE 30" TRACTRIX HORN

Experience the high-efficiency sound of horn loudspeakers with this detailed construction project.

By Robert Roggeveen.....20

#### IMPROVING DYNACO'S FM-5 AND AF-6 TUNERS

Here's a modification to the power supply to enhance the performance of your Dynaco tuner.

By Daniel Dufresne .....28

#### ALPHA TRANSMISSION LINES

An interesting look at transmission-line construction, with details on how to build your own unit.

By Rick Schultz .....34

#### SYSTEM POWER CONTROL

Here's a simple circuit to control the on/off sequence of your audio system.

By Frank S. Thomas III .....46

#### BUILD A REACTIVE LOAD

Audio constructors will enjoy building this simple load box design to test power amps.

By Dick Crawford.....48

#### CARE AND MAINTENANCE OF DUKANE IONOVAC TWEETERS

Here's a guide to restoring classic high-frequency speakers, which include no moving parts . . . only the air itself.

By Daniel Schoo .....50



page 34



page 20

audioXpress (US ISSN 0004-7546) is published monthly, at \$34.95 per year, \$58.95 for two years; Canada add \$12 per year; overseas rates \$59.95 per year, \$110 for two years; by Audio Amateur Inc., Edward T. Dell, Jr., President, at 306 Union St., PO Box 876, Peterborough, NH 03458-0876. Periodicals postage paid at Peterborough, NH, and additional mailing offices.

POSTMASTER: Send address changes to: audioXpress, PO Box 876, Peterborough, NH 03458-0876.



page 6

## THE STAFF

Editor and Publisher  
Edward T. Dell, Jr.

Regular Contributors

<b>Eric Barbour</b>	<b>Erno Borbely</b>
<b>Robert Bullock</b>	<b>Richard Campbell</b>
<b>Joseph D'Appolito</b>	<b>Vance Dickason</b>
<b>Bill Fitzmaurice</b>	<b>Gary Galo</b>
<b>Charles Hansen</b>	<b>G.R. Koonce</b>
<b>Nelson Pass</b>	<b>Richard Pierce</b>
<b>Reg Williamson</b>	

Vice President  
Karen Hebert

<b>Dennis Brisson</b>	Assistant Publisher
<b>Marianne Conway</b>	Editorial Assistant
<b>Amity Palmer</b>	Editorial Assistant
<b>Tina Hoppock</b>	Graphics Director
<b>Amy Wyman</b>	Production Assistant
<b>Laurel Humphrey</b>	Marketing Director
<b>Kelly Bennett</b>	Customer Service

Advertising Department

*Strategic Media Marketing*  
1187 Washington St.  
Gloucester, MA 01930

**Peter Wostrel**  
Phone: 978.281.7708  
Fax: 978.283.4372  
E-mail: peterw1@gjs.net

**Nancy Vernazzaro**  
Advertising/Account Coordinator

## DEPARTMENTS

### SHOWCASE

An Italian THOR  
*By Atto Rinaldo*.....58

### XPRESS MAIL

Readers speak out .....62

### NEW CHIPS ON THE BLOCK

AKM AK4395 and AK4554  
*By Charles Hansen*.....72

## IN EVERY ISSUE

### CLASSIFIEDS

Audio-related items for  
sale or wanted ..... 70

**AD INDEX** ..... 71

### YARD SALE

Free classifieds  
for subscribers ..... 71



page 50



page 58

Articles and letters identified with the following symbols:



### LEGAL NOTICE

Each design published in *audioXpress* is the intellectual property of its author and is offered to readers for their personal use only. Any commercial use of such ideas or designs without prior written permission is an infringement of the copyright protection of the work of each contributing author.

### SUBSCRIPTION/CUSTOMER SERVICE INQUIRIES

A one-year subscription costs \$34.95; a two year subscription costs \$58.95. Canada please add \$12 per year. Overseas rate is \$59.95 for one year; \$110 for two years. To subscribe, renew or change address write to the Customer Service Department (PO Box 876, Peterborough, NH 03458-0876) or telephone toll-free (US/Canada only) 888-924-9465 or (603) 924-9464 or FAX (603) 924-9467. E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com). Or online at [www.audioXpress.com](http://www.audioXpress.com)

For gift subscriptions please include gift recipient's name and your own, with remittance. A gift card will be sent.

### EDITORIAL INQUIRIES

Send editorial correspondence and manuscripts to *audioXpress*, Editorial Dept., PO Box 876, Peterborough, NH 03458-0876. E-mail: [editorial@audioXpress.com](mailto:editorial@audioXpress.com). No responsibility is assumed for unsolicited manuscripts. Include a self-addressed envelope with return postage. The staff **will not** answer technical queries by telephone.

### CLASSIFIEDS & WEB LISTINGS

Contact Nancy Vernazzaro, Advertising Department, *audioXpress*, PO Box 876, Peterborough, NH 03458, 603-924-7292, FAX 603-924-6230, E-mail [nancy@audioXpress.com](mailto:nancy@audioXpress.com).

Printed in the USA Copyright © 2003 by Audio Amateur Corporation. All rights reserved.

*The peculiar evil of silencing the expression of an opinion is, that it is robbing the human race; posterity as well as the existing generation; those who dissent from the opinion, still more than those who hold it.*

JOHN STUART MILL



●●● Pleasure just knows no compromises



enjoy  
**your**  
hifi

Every WBT product has been designed and refined for trouble free reliability and superior sonic performance. The formula is simple: develop innovative designs and build them with the finest materials.

**WBT**

801-621-1500 • [www.wbtusa.com](http://www.wbtusa.com)



# 330


## AUDIO GRADE™ POWER CONNECTOR



Triple plated contacts



Adaptable cord clamp insert

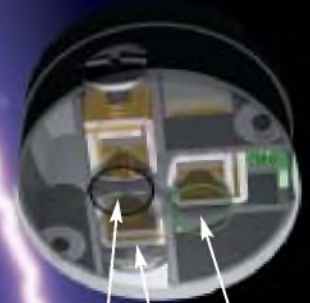

Terminal funnels and holes

The construction of the 330 is built-to-last and features an elegant polycarbonate rear housing available in either black or clear with a durable Nylon-Tough front housing. Additionally, there is a dust seal to protect the wiring chamber. Marked with "Audio Grade™" and Blue Star™.

# WATTGATE™

801-621-1501 • [www.wattgate.com](http://www.wattgate.com)



# A Simple, High Quality AM Tube Receiver

You, too, can re-discover how good AM radio can sound when it is done right. **By Scott K. Reynolds**

**T**his construction project began when I read a letter from Vince Roberts in the February 2001 issue.<sup>1</sup> Mr. Roberts requested an article on an AM tuner using vacuum tubes, and reading his letter inspired me to build one. I tried to come up with a design that would be easy for the home constructor to build and also give good audio quality. Both of these goals meant that I had to keep the radio frequency (RF) circuits as simple as possible, but a large, efficient antenna more than compensated for the low RF gain and resulted in a receiver that has surprisingly good sensitivity.


My wife was at first skeptical of this project, but in the end she liked the



**PHOTO 1:** Front view of the radio receiver. The RF circuits are on the left, with tubes V1 and V2 at the left rear.

radio so much that I had to move it from my workshop into the study. My wife is a National Public Radio (NPR) enthusiast, and we live in a fringe reception area where the local NPR AM station (WNYC) usually comes in with a

fair amount of static and noise. To even my surprise, this new AM receiver brings in WNYC with consistently lower noise than any other radio in the house, and it has a rich and detailed sound the other radios lack. It made my

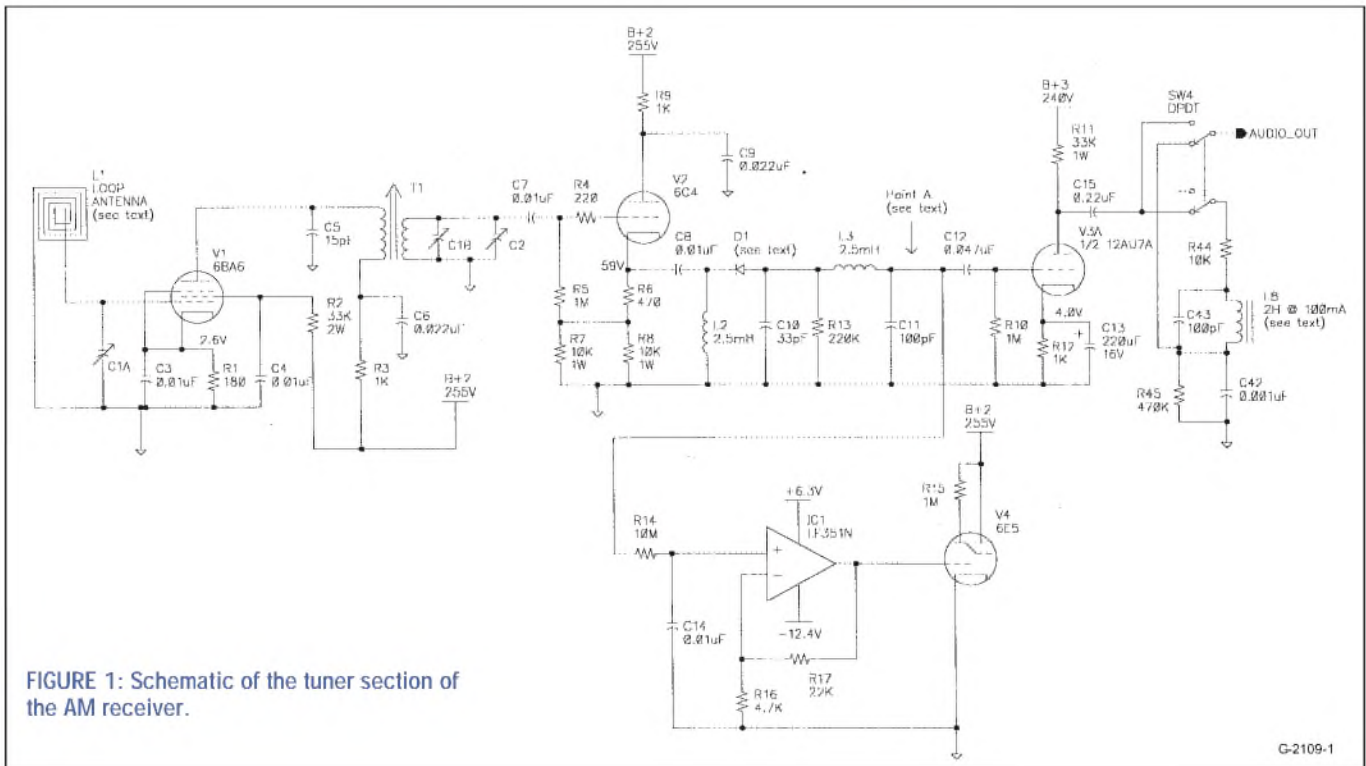


**FIGURE 1:** Schematic of the tuner section of the AM receiver.

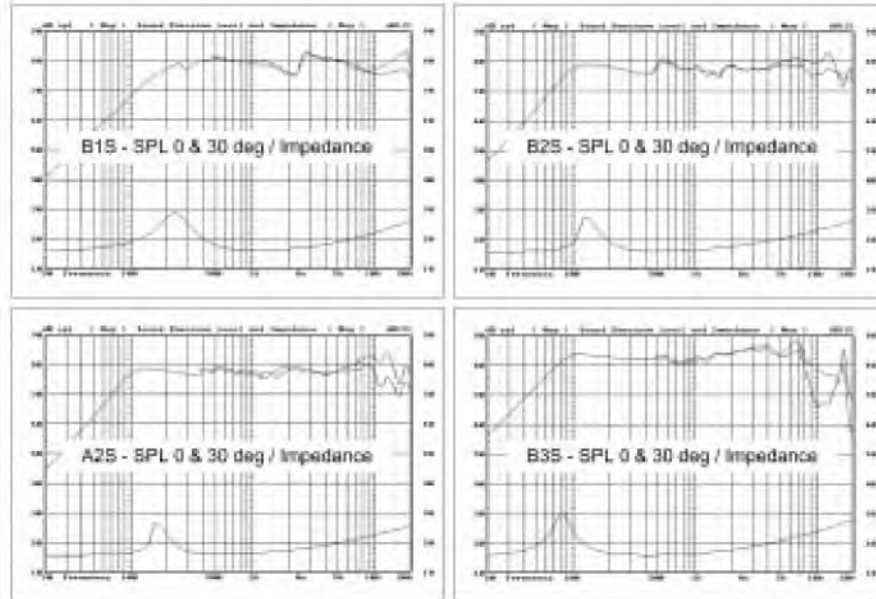G-2109-1

**HI-VI RESEARCH®**  
you can hear the difference

The new *compact* drivers  
full range and midrange woofers



B15



A25



B25



B35

- Aluminum-magnesium cone — an improvement over pure aluminum cone technology
- 100% shielded magnet system - home theater/computer ready
- Optimized T/S parameters for more flexible cabinet design



[www.svenskespeaker.com](http://www.svenskespeaker.com)  
[www.dulcet.com](http://www.dulcet.com)

Distributed by  
**Parts Express**  
Tel: 1-800-338-0531  
[www.parts-express.com](http://www.parts-express.com)

**HI-VI RESEARCH(USA)**

Svenske Speaker Systems, Inc. 2050 Corporate Place, Suite C-103, Monterey Park, CA 91754 USA Tel: (626) 861-0000 Fax: (626) 861-0057 e-mail: [janis@svenske.com](mailto:janis@svenske.com)

**HI-VI RESEARCH(HongKong)**

Hongo (Holdings) Ltd. Flat 1706, China-Venue, Three, Shun Tak Centre, 168-200 Connaught Road, Saiyap Wan, Hong Kong. Tel: (852) 2587-4728 Fax: (852) 2587-8788 e-mail: [hongo@svenske.com](mailto:hongo@svenske.com)

**HI-VI RESEARCH(China)**

HI-VI RESEARCH ELECTRONIC CO., LTD. Fuxing Building, 31st / FL, Exit Tower, 163 HuangPu Ave, Guangzhou, Guangdong, China. Tel: (86) 20 34919991 Fax: (86) 20-85211260 e-mail: [yao@dulcet.com](mailto:yao@dulcet.com)

©2000 Svenske Speaker Systems, Inc. HI-VI RESEARCH and the Sveno logo are registered trademarks of Svenske Speaker Systems, Inc. or its subsidiaries in the United States and other countries. All rights reserved.



about the complexity of the RF circuitry and the difficulty that the home constructor might have in aligning a newly

built radio (aligning several stages in a newly built superheterodyne radio is more confusing than re-aligning an already working radio). I was also concerned about the difficulty of finding parts, especially the tube-compatible IF transformers, since I don't think they are being manufactured anymore. Antique Electronic Supply has a few surplus IF transformers, but it's difficult to know how long they'll be available. I considered winding my own transformers, but I decided to follow Mr. Roberts' advice to "start simple."

A TRF receiver offered a simpler alternative . . . if I could get the required RF gain in a single stage. Multiple-stage TRF receivers aren't so simple anymore, because of the problem of aligning multiple-tuned stages and having them track together over the band as the receiver is tuned. A high gain, multi-stage TRF receiver can be unstable due to unintended feedback.

Finally, TRF receivers suffer

from variations in gain and selectivity as you tune from one end of the band to another, a problem which becomes worse as the number of stages increases. Back in the 1920s and '30s, designers came up with elaborate solutions to these problems, but I didn't want anything elaborate.

### ANTENNA REQUIREMENTS

Having decided on a single-stage TRF design, I wanted to get the most performance I could out of it, and the antenna (component L1 in Fig. 1) seemed like the best place to start. I decided to build the largest loop antenna that would still be practical to receive as much RF signal as I could (without setting up an outdoor antenna). An amateur can readily build a better antenna than a manufacturer can, not having the same sort of space, shipping, or manufacturing limitations.

The RF signal received by a loop antenna is proportional to both the number of turns and the area, so it would seem that you want a large loop area and lots of turns. But in order for the antenna to resonate with the 365pF tun-

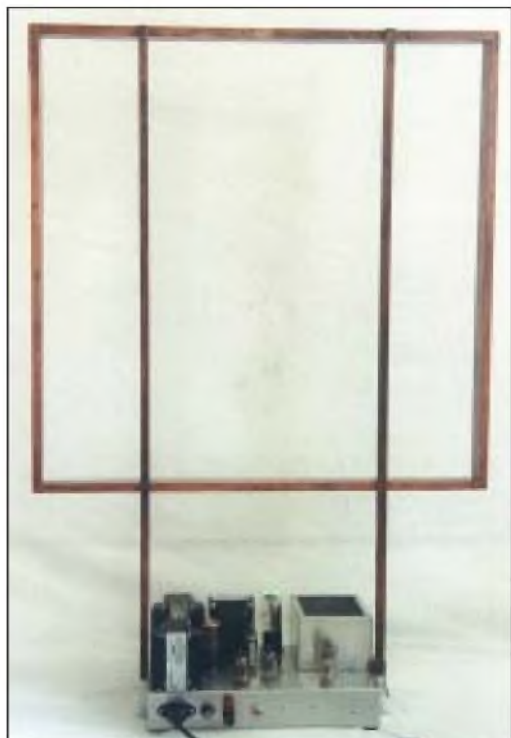



PHOTO 3: Distant rear view of the radio, showing the construction of the antenna L1.

## HiFi Digital Amplification, that simply works, and sounds... GREAT!


### ZAPpulse 2.0

SIMPLE!


Power Supply Connection

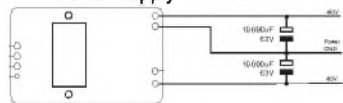

Input/Output Connection RCA

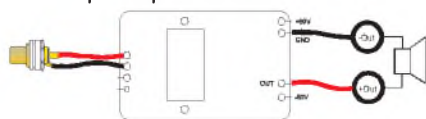

Input/Output Connection XLR

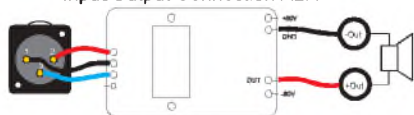

Audio Power Amplifier using New advanced Technology to produce 400 Watt RMS (4 Ohms) on a Credit Card size Footprint !



Available as a ready to play audio appliance, or modules for DIY projects. Almost no heat sinking is called for, a thin steel sheet metal floor of the enclosure will do! Build as mono blocks, stereo, 5 ch, 7 ch in one enclosure. 200 W/8 400W/4 650W/2 RMS cont. pwr. 5 - 150.000 Hz +/- 3dB THD 0.02%@10W Damping Factor 130 Max. Current 62 Amp.



Predator SE 2 x 250 Watts RMS

Efficiency ~ 96% = environment friendly



Predator SE 250 Watts RMS in 8 Ohms Stereo Power Amplifier US\$ 1999.00  
DIY Modules US\$ 199.00  
SE Version w/Black Gate VK as shown: US\$ 269.00

## L C Audio Technology

USA: **DIYCABLE** ● 153 Mountain Home Road ● Port Angeles WA98362 ● Washington ● tel 360-452-9373 [www.diycable.com](http://www.diycable.com)  
Great Britain: **Audio Atmosphere** ● 29 Drake Avenue ● Penkridge ● Stafford ST19 5UA ● tel 0 1785 711232 [www.audioatmosphere.co.uk](http://www.audioatmosphere.co.uk)  
Australia: **Soundlabs Group Pty.** ● POBox 307 ● Surry Hills NSW 2010 ● tel 02 9660 1228 [www.soundlabsgroup.com](http://www.soundlabsgroup.com)  
Scandinavia: **L C Audio Technology** ● Christiansgade 1 ● DK7500 Holstebro ● tel +45 97410863 [www.lcaudio.com](http://www.lcaudio.com)

ing capacitor C1A over the entire AM broadcast band (540–1600kHz), you are constrained to make the loop's inductance 238 $\mu$ H. The loop's inductance is approximately proportional to the square of the number of turns and the square root of the loop area, so selecting the antenna size gave me an interesting mathematical and experimental problem to solve.

I settled on a 24"  $\times$  24" (61cm  $\times$  61cm) square wooden frame, with nine turns of AWG 22 enameled magnet wire wound around the outside, with the turns spaced 1/8" (3.18mm) apart. The spacing is important in order to minimize the self-capacitance of the antenna. If the self-capacitance is too high, the antenna cannot be tuned over the entire AM band.

My radio tunes from 560 to 1570kHz, which should be adequate for most readers. But some of you may wish to receive a station in the extended AM band from 1600 to 1700kHz (these are mostly low-power local stations, the most interesting kind). To do that, you'll need to take a turn (or half a turn) off L1, which may prevent you from getting stations below 600kHz. You can also tap L1 to make changing

the number of turns easy.

For the antenna to tune the entire 540–1700kHz extended AM band without changing taps appears to require a smaller loop area, but, of course, that results in a less efficient antenna and a less sensitive receiver. The size of the antenna I chose is just one of those inevitable engineering compromises. I'll give more details on antenna construction and setup later.

## CIRCUIT DESCRIPTION

The main tuning capacitor C1 is a dual-ganged 365pF air-variable capacitor, which used to be standard in AM radios. But these air-variable capacitors are becoming harder to find. RF Parts Co. and Antique Electronic Supply both have suitable parts. The fine-tuning capacitor C2, which is a 33pF air variable, is more readily available. But it can be tough to find one with a shaft for a knob (most



PHOTO 4: Underside view of the chassis. The RF wiring is at the right rear.

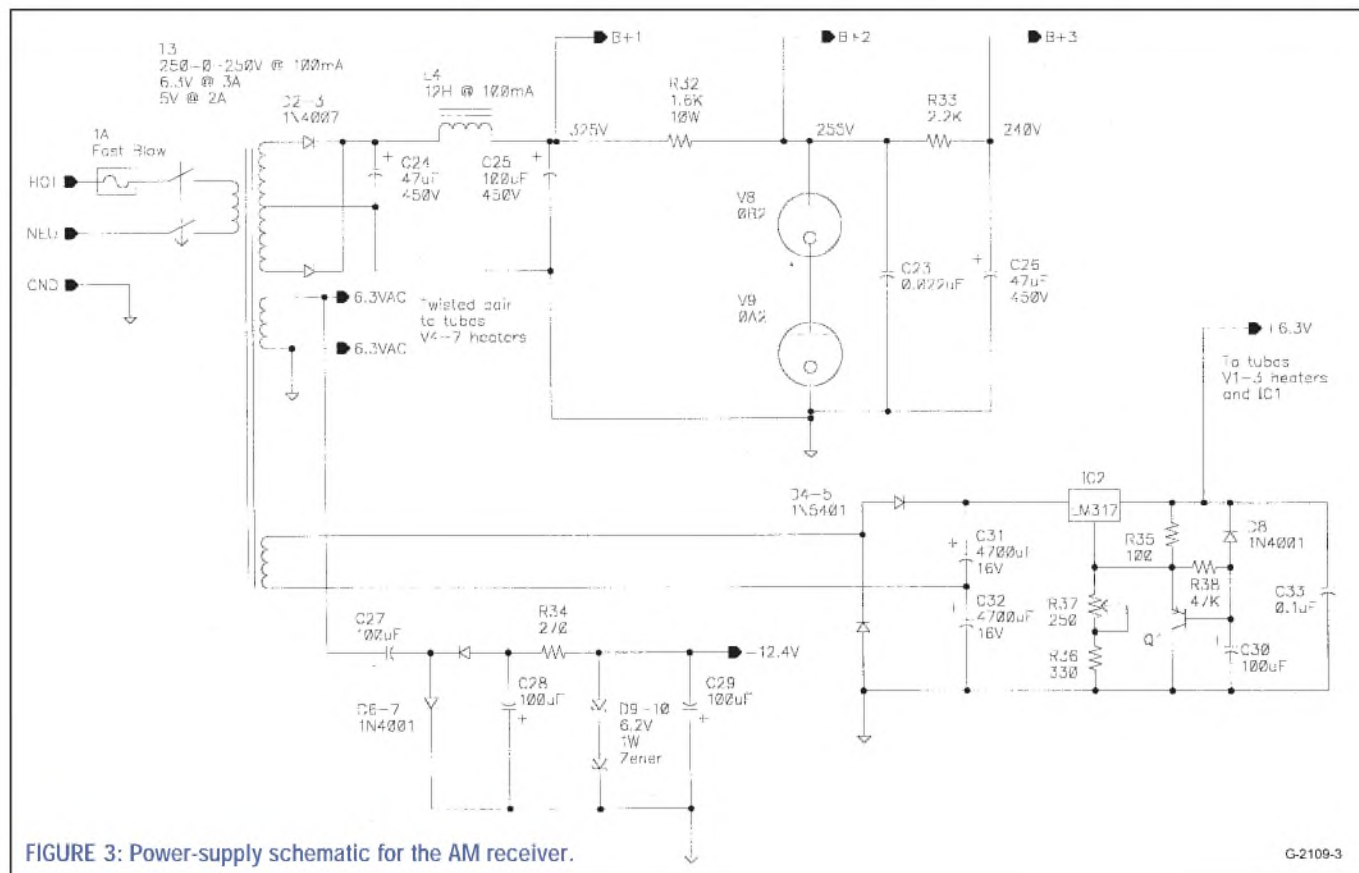


FIGURE 3: Power-supply schematic for the AM receiver.

have slots for screwdriver adjustment). Mine came from RF Parts Co.

All of the RF gain in the receiver (20–30dB) comes from remote-cutoff pentode V1, a 6BA6 or 5749/6BA6W. The quiescent cathode current in V1 is set to a relatively high 14.4mA by the value of R1. The high bias current is used to maximize the transconductance of V1, giving high gain and low noise. Raising the value of R1 lowers the transconductance and the gain, so you could achieve RF gain control by inserting a variable resistor in series with R1. I'll give more details on this later.

The output of V1 is transformer coupled to the detector circuit by T1, a slug-tuned RF transformer. T1 is Antique Electronic Supply part number P-C70-RF (I'm not aware that these RF transformers are available from any other source, but they aren't surplus, so they should continue to be available).

T1 is designed so that the primary circuit should resonate at a frequency below the AM band, but if the associated circuit does not have enough capacitance, some additional capacitance needs to be added to reduce the prima-

ry resonant frequency. That is the purpose of C5, a 15pF dipped mica capacitor. The secondary of T1 resonates with C1B and C2, forming a second tuned circuit at the same frequency as the L1-C1A combination. Because of its large physical size, the antenna L1 has more self-capacitance than the secondary of T1, so you need to add the additional fine-tuning capacitor C2 in order to make the two tuned circuits track properly over the AM band.

The detector circuit is a classic diode envelope detector used in countless AM radios. To get high sensitivity, use a 1N34A (or 1N60A) germanium point-contact diode (D1), which is often used in crystal radios and is 10–100 times more sensitive than a vacuum tube diode. These germanium diodes also have the advantage of being more linear than a vacuum tube diode at the low RF signal levels found in this receiver. Note that a standard silicon diode will not work for D1.

A cathode follower (V2) isolates the diode detector from the second tuned circuit, thereby preventing the diode from loading the tuned circuit and pre-

serving high selectivity. Tube V2 (a 6C4 or 6100/6C4WA) is biased at a fairly high 10.8mA to give high transconductance. A cathode follower can be unstable at high frequencies when it has a capacitive load and a tuned circuit at the grid, which is the situation in Fig. 1. Grid stopper R4 prevents any such instability. You should install it immediately adjacent to the tube socket.

The output of the diode detector goes through a low-pass pi-section filter consisting of C10, L3, and C11, which removes the residual RF carrier. This filter has an audio bandwidth of about 6.6kHz, which is adequate for AM signals. You can increase the audio bandwidth by reducing the values of C10 and C11, if you want to experiment. With the RF carrier removed, the remaining signal at point "A" on the schematic (Fig. 1) consists of the audio signal and a negative DC component (there is also some second harmonic distortion). Capacitor C12 blocks the DC component and passes the audio to V3A, the first audio amplifier stage.

The amplitude of the DC component is proportional to the strength of the RF

## Maximum Performance



### *The ExactPower™ EP15A allows audio and video equipment to operate at peak performance by providing clean, non-current-limited AC power.*

Clean AC power allows audio and video components to perform better. The cleaner and more perfect the power, the better the sound and the better the picture. The improvements you experience are immediate and astounding.

The ExactPower EP15A is a single box that performs seven essential corrections, creating the most perfect AC power available for your audio and video products. Other products on the market do one or two or, at most, three corrections. Even in combination, these products are totally outperformed by the EP15A. Because it does multiple, essential corrections for the



Typical AC is distorted



ExactPower corrected AC

cleanest, purest power, only the EP15A can provide maximum high performance and increased longevity from your audio and video components. All units are available in silver or black, are rack-mountable, and feature surge protection that can handle current peaks up to 25,000 amps.

Our products are smaller, lighter, cooler, more efficient, more technologically advanced, and far more affordable than you'll find elsewhere. Add to that our proven track record of reliability and you will see that ExactPower offers the finest choice in power processing/management products.

The ExactPower EP15A uses a unique, patented *subcycle AC voltage regulator* that provides a constant 120 volts ( $\pm 0.5\%$ ) in addition to *instantaneous waveform correction*. It also provides up to 1800 watts *without any current limitation*. In fact, the EP15A actually utilizes *current storage* which avoids any energy starvation-related artifacts from corrupting the power conditioning process. The EP15A is the most accurate, most efficient, most affordable, most flexible, and most adaptable power processing/management solution available.

For the absolute ultimate in power conditioning, couple the EP15A with our high performance SP15A Symmetrical Power unit providing balanced current and digital filtration, plus a host of other features.

Visit our website to find out additional options and technical details on our full line of power processing/management products that can dramatically improve your audio and video systems' performance.

Atlantis Power Quality Systems, Inc.

9411 Winnetka Avenue, Chatsworth, California 91311

SALES & INFORMATION (866) 392-2822 • (866) EXACT AC  
TECH SUPPORT (800) 773-7977 U.S. only • (818) 886-5364 outside U.S.  
FAX (818) 886-0504 • WEB [www.exactpower.com](http://www.exactpower.com)

**EXACTPOWER**  
THE CORRECT SOLUTION FOR CLEAN AC POWER

signal, which makes it useful for operating a tuning indicator. In my area, the strongest RF signals produce about  $-1.5\text{V}$  at point "A." But the 6E5 tuning indicator tube that Mr. Roberts requested requires about  $-8\text{V}$  for complete eye closure.

Therefore, the DC component is amplified by IC1, an LF351N JFET input op amp configured for a non-inverting gain of 5.6. An op amp with a JFET input is essential in order to provide high enough input impedance so as not to load the diode detector circuit. A standard 741 op amp will not work here.

I think the 6E5 tube is quite attractive, but it is becoming rare and expensive. You could also use a 10V full-scale analog meter movement at the output of IC1, or a 1mA meter with a  $10\text{k}\Omega$  series resistor.

Keep in mind that the output of IC1 swings from zero to about  $-8\text{V}$ , so wire the meter with the correct polarity. You cannot wire an analog meter directly to point "A" on the schematic because it will load the diode detector. Digital meters will not work for tuning because their response is not continuous. Some sort of tuning indication is essential for both alignment and normal operation,

so don't be tempted to omit it.

### AUDIO FILTER

Components R44–R45, L8, and C42–C43 in Fig. 1 make up a passive low-pass filter that I added to the output of the tuner to eliminate (or reduce) the annoying 10kHz squeal that AM radios sometimes produce in an environment crowded with many stations. This 10kHz squeal arises because AM stations are spaced 10kHz apart, and along with the desired station you may also be receiving a weak, distant station 10kHz higher or lower in frequency (other local stations are usually 30kHz apart). The two signals "beat" together in the receiver to produce a 10kHz tone, and the only solution is to filter it out. This problem is less noticeable on a modern superheterodyne receiver because the IF filters are so highly selective, giving the receiver less bandwidth.

The filter has a  $-3\text{dB}$  point at approximately 5.5kHz, and it is down more than 15dB at 10kHz. A tiny filter choke (L8) acts as an audio choke to produce an LC filter. Capacitor C43 resonates with L8 at 10kHz to produce a sharp cutoff characteristic. The filter is designed to work best with load imped-

ances between  $50\text{k}\Omega$  and  $100\text{k}\Omega$  (here it sees  $470\text{k}\Omega$  in parallel with the  $100\text{k}\Omega$  potentiometer R18, or about  $82\text{k}\Omega$ ).

I don't recommend replacing L8 (a Hammond part #154M), because other filter chokes may have different audio characteristics. I added a switch (SW4) to bypass the filter when it isn't needed, since I didn't want to unnecessarily reduce the wide bandwidth that my receiver has. You can build the tuner without the filter by eliminating R44–R45, L8, C42–C43, and SW4, taking the audio output directly from coupling capacitor C15.

### AUDIO POWER AMPLIFIER

The output of V3A or the audio filter is coupled into the audio power amplifier (Fig. 2) through selector switch SW1. I decided to add an auxiliary input to the power amplifier so that I could plug in my FM tuner or CD player (or any line level audio signal). The power amplifier is a simple, classic design that many readers will have seen before. Tube V3B is an input amplifier, and V5 is a "long-tailed" phase splitter. A pair of push-pull 6V6s produces about 9W of audio power.

One slightly unusual feature is that the 6V6s have separate cathode bias re-

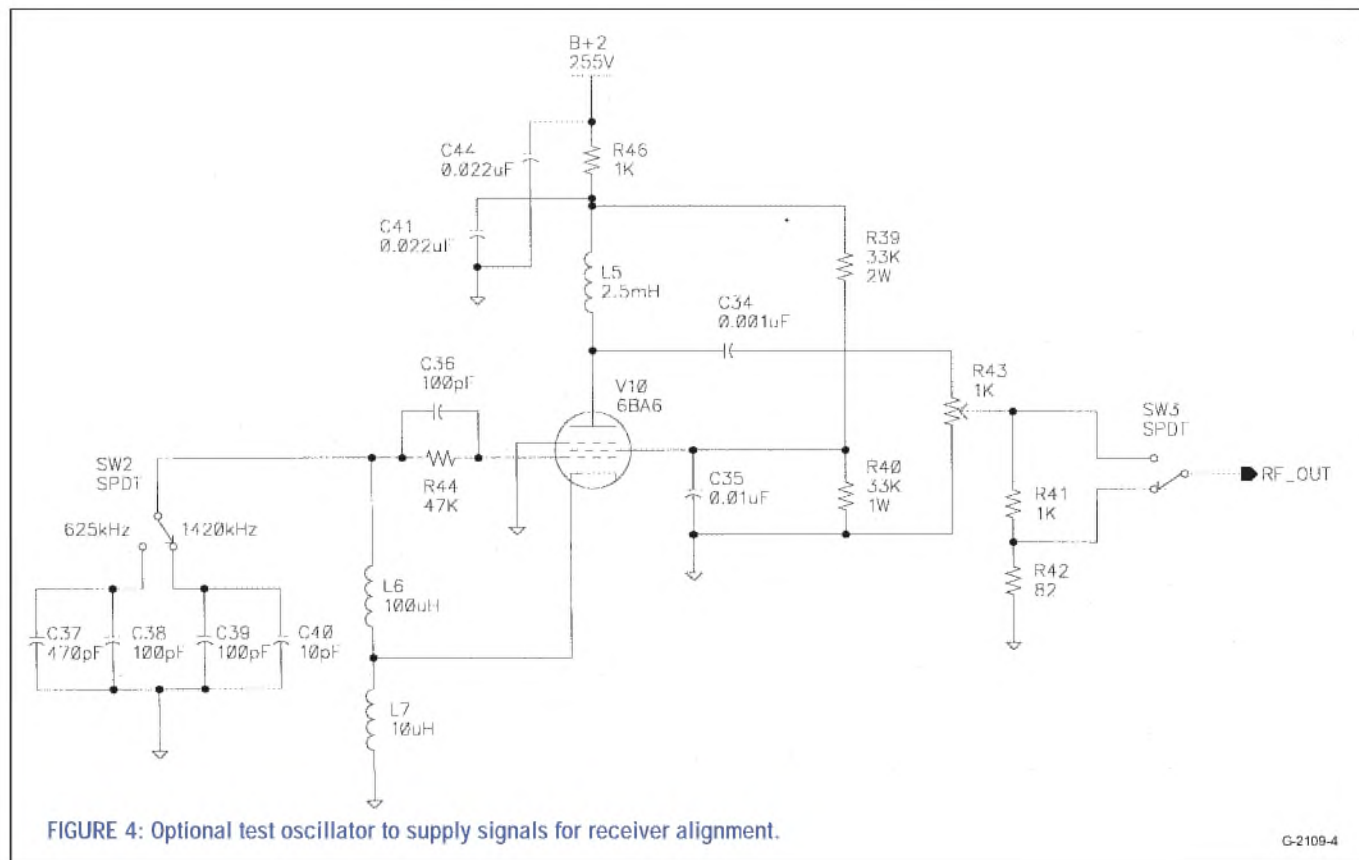



FIGURE 4: Optional test oscillator to supply signals for receiver alignment.

G-2109-4


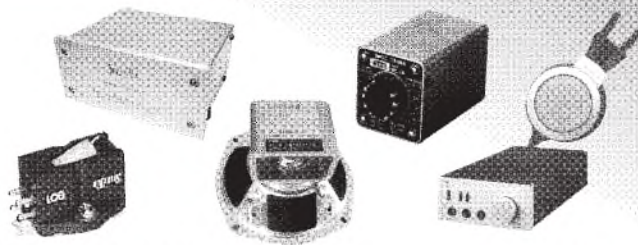
# Look!!

Click <http://www.eifl.co.jp>  
or send e-mail to [info@eifl.co.jp](mailto:info@eifl.co.jp)  
for more products information



## ■ Cartridge

Model	Price (US\$)	Postage (Air Economy)	
Denon DL-102 (MONO)	150	Area I \$18	China, Korea, Hong Kong, Taiwan
Denon DL-103 (STEREO)	200	Area II \$22	Singapore, Malaysia, Indonesia
Denon DL-103R (STEREO)	250	Area III \$27	North America, Oceania, Europe
Denon DL-103 PRO (STEREO)	350		
Shelter Model 501 II (CROWN JEWEL REFERENCE)	750	Area IV \$34	Africa, South America
Shelter Model 901 (CROWN JEWEL SE)	1,400	These Area I ~ IV are for all products except book.	

## ■ Japanese Audio Book

Postage \$15

Title	Price (US \$)
Attractive Tube Amps Vol. 1&2 (Isamu Asano)	30 each
The Joy of Vintage Tube Amps 1&2 (Tadaatsu Atarashi)	30 each NEW
Direct & Indirect Tube Amps (Kiyokazu Matsunami)	40 NEW
SE Amps by Transmitting Tubes (Kouichi Shishido)	50
The Remembrance of Sound Post (Susumu Sakuma)	30
Classic Valve (Hisashi Ohtsuka)	40
MJ Selected 300B Amps (MJ)	30
Top-Sounding Vintage Power Tubes (Stereo Sound)	30
Output Trans of The World (Stereo Sound)	30
20TH CENTURY OF AUDIO (Stereo Sound)	30
Vintage Speaker Units (Stereo Sound)	30 NEW
Tube Amp Craft Guide (MJ)	30

## ■ MC STEP UP TRANS

Model	Specifications			Price (US\$)	Postage**
	Pri. Imp(Ω)	Sec. Imp(kΩ)	Response		
Shelter Model 411	3~15	47	20Hz~50kHz	980	Area I \$25 Area II \$30 Area III \$40 Area IV \$50
Jensen JE-34K-DX	3	47	20Hz~20kHz	550	
Peerless 4722	38	50	20Hz~20kHz	300	

## ■ STAX

Model	Price(US\$)
OMEGA II System(SR-007+SRM-007t)	Ask
SRS-5050 System W MK II	
SRS-4040 Signature System II	
SRS-3030 Classic System II	
SRS-2020 Basic System II	
SR-001 MK2(S-001 MK II +SRM-001)	

## ■ Speaker

\*\*Air Economy

Model	Specifications					Price* (US\$)	Postage** (US\$)			
	D(cm)	Ω	Response	db	w		I	II	III	IV
Fostex FE208 Σ	20	8	45Hz~20kHz	96.5	100	296	62	74	120	156
Fostex FE168 Σ	16	8	60Hz~20kHz	94	80	236	42	50	73	98

\*Price is for a pair \*\*Air Economy

## ■ TANGO TRANS (ISO) (40models are available now)

Model	Specifications				Price (US\$)	Postage** (US\$)			
	W	Pri. Imp(kΩ)	Freq Response	Application		I	II	III	IV
XE-20S (SE OPT)	20	2.5, 3.5, 5	20Hz~90kHz	300B,50,2A3	396	47	56	84	113
U-808 (SE OPT)	25	2, 2.5, 3.5, 5	20Hz~65kHz	6L6,50,2A3	242	42	50	73	98
XE-60-5 (PP OPT)	60	5	4Hz~80kHz	300B,KT-88,EL34	620	62	74	115	156
FX-40-5 (PP OPT)	40	5	4Hz~80kHz	2A3,EL34,6L6	320	47	56	84	113
FC-30-3.5S (SE OPT) [XE-60-3.5S]	30	3.5	20Hz~100kHz	300B,50,PX-25	620	62	74	115	156
FC-30-10S (SE OPT) [XE-60-10SNF]	30	10	30Hz~50kHz	211,845	620	62	74	115	156
X-10SF [X-10S]	40	10W/SG Tap	20Hz~55kHz	211,845	1160	90	110	180	251
NC-14 (Interstage)	—	[1+1 : 1+1] 5	25Hz~40kHz	[30mA] 6V6 (T)	264	30	40	50	70
NC-16 (Interstage)	—	[1+1 : 2+2] 7	25Hz~20kHz	[15mA] 6SN7	264	30	40	50	70
NC-20F (NC-20) (Interstage)	—	[1 : 1] 5	18Hz~80kHz	[30mA] 6V6 (T)	640	42	50	73	98
NP-126 (Pre Out)	—	20,10	20Hz~30kHz	[10mA] 6SN7	264	30	40	50	70

Price is for a Pair

## ■ TAMURA TRANS (All models are available)

\*\* Air Economy

Model	Price (US\$)	Postage** (US\$)
F-7002 (Permalloy)	10	3.5
F-7003 (Permalloy)	10	5
F-2013	40	10
F-5002 (Amorphous)	8	3

Price is for a Pair

\*\* Air Economy

**E·I·F·L**  
EIFL Corporation

1-8, Fujimi 2-chome, Sayama City, Saitama Pref. 350-1306 JAPAN.  
Phone: +81-(0)42-956-1178 FAX: +81-(0)42-950-1667  
E-mail: [info@eifl.co.jp](mailto:info@eifl.co.jp)  
Wire Transfer: MIZUHO BANK, SWIFT No. MHBKJPJT a/c # 294-9100866



Card Charge 6%

sistors. I did this to accommodate mismatched tubes. With a single cathode resistor, one tube can hog most of the bias current if the 6V6s are badly mismatched. With separate resistors, you can plug in any two working 6V6s and achieve satisfactory performance.

A 10W Hammond output transformer (type 1608) couples the push-pull 6V6s to the speaker. About 15dB of negative feedback is applied from the speaker output to the cathode circuit of V3B. Note that the output transformer T2 is shown wired for an 8Ω speaker. If you opt to wire it for 4Ω, then R31 should be about 750Ω instead of 1000Ω.

If you wire it for a 16Ω speaker, then R31 should be about 1.5kΩ.

## POWER SUPPLY

The power supply is shown in Fig. 3. A conventional full-wave rectifier and pi-section filter supplies 325V for the power amplifier stages (B+1). Gaseous regulator tubes V8 and V9 produce a shunt-regulated 255V supply for the RF stages (B+2).

I regulated this supply to provide low AC ripple as well as a stable operating point for tubes V1 and V2, so that line voltage and temperature fluctuations wouldn't detune the radio. A regulated

supply is probably not essential, however, as long as B+2 is in the 240–270V range. An RC decoupling filter produces 240V for the low-level audio amplifier stages (B+3).

The 6.3V secondary on T3 supplies heater power for tubes V4–V7. Note that one side of the 6.3V winding is grounded. However, you should run twisted pairs for the AC heater wiring instead of running a single wire and grounding one side of each tube's heater at the socket. Running twisted pairs prevents AC heater current from flowing through the ground connection, thereby eliminating a source of 60Hz hum.

**TABLE 1**  
**COMPOSITE PARTS LIST FOR FIGS. 1–4**

C1	Dual ganged 365pF air variable tuning capacitor (RF Parts Co. Part #10295 or Antique Electronic Supply Part #C-V365-X3 or equivalent)	Q1	2N2907A or equivalent, PNP silicon bipolar transistor
C2	33pF air variable tuning capacitor (RF Parts Co. Part #074-033 or equivalent)	R1	180Ω, ½W, 5%
C3, C4, C7, C8, C35	0.01μF, 500V, disc ceramic	R2, R39	33kΩ, 2W, 5%
C5	15pF, 500V, dipped mica, 5%	R3, R9, R12, R20, R31, R41, R46	1kΩ, ½W, 5%
C6, C9, C23, C41, C44	0.022μF, 500V, disc ceramic	R4	220Ω, ½W, 5%
C10	33pF, 100V, dipped mica, 5%	R5, R10, R15, R24, R25	1MΩ, ½W, 5%
C11, C36, C38, C39, C43	100pF, 100V, dipped mica, 5%	R6	470Ω, ½W, 5%
C12	0.047μF, 100V, film	R7, R8	10kΩ, ½W, 5%
C13, C16	220μF, 16V, electrolytic	R11	33kΩ, ½W, 5%
C14	0.01μF, 50V, film	R13, R27, R28	220kΩ, ½W, 5%
C15	0.22μF, 400V, film	R14	10MΩ, ½W, 5%
C17–C19	0.1μF, 400V, film	R16	4.7kΩ, ½W, 5%
C20, C21	470μF, 35V, electrolytic	R17	22kΩ, ½W, 5%
C22	4700pF, 100V, film or dipped mica	R18	100kΩ audio taper potentiometer
C24, C26	47μF, 450V, electrolytic	R19, R35	100Ω, ½W, 5%
C25	100μF, 450V, electrolytic	R21, R22	51kΩ, 1W, 5%
C27–C30	100μF, 25V, electrolytic	R23	62kΩ, 1W, 5%
C31, C32	4700μF, 16V, electrolytic	R26	22kΩ, 2W, 5%
C33	0.1μF, 100V, film	R29, R30	750Ω, 3W, 5%
C34	0.001μF, 500V, disc ceramic	R32	1.6kΩ, 10W, 5%, wirewound
C37	470pF, 100V, dipped mica, 5%	R33	2.2kΩ, ½W, 5%
C40	10pF, 100V, dipped mica, 5%	R34	270Ω, ½W, 5%
C42	0.001μF, 100V, film	R36	330Ω, ½W, 5%
D1	Germanium point-contact diode, 1N34A, or 1N60A, or equivalent. Available from Antique Electronic Supply, RF Parts Co., or All Electronics.	R37	250Ω trimmer
D2, D3	1N4007, 1000V, 1A rectifier diode	R38, R44	47kΩ, ½W, 5%
D4, D5	1N5401, 100V, 3A rectifier diode	R40	33kΩ, 1W, 5%
D6–D8	1N4001, 50V, 1A rectifier diode	R42	82Ω, ½W, 5%
D9, D10	1N4735A, 6.2V, 1W zener diode	R43	1kΩ linear taper potentiometer
IC1	LF351N, JFET input op amp	R45	470kΩ, ½W, 5%
IC2	LM317T, adjustable voltage regulator (mount this part on a heatsink or on the chassis, using a thermally conductive, electrically insulating gasket)	SW1–SW3	Single-pole double-throw toggle switch
L1	Nine turns of AWG22 enameled magnet wire, spaced ⅛" (3.18mm) apart, wound on the outside of a 24" × 24" (61cm × 61cm) square wooden frame. See text.	SW4	Double-pole double-throw toggle switch
L2, L3, L5	2.5mH RF choke, Hammond part #1535B or equivalent.	T1	540-1600kHz slug-tuned RF transformer (Antique Electronic Supply part #PC-70-RF)
L4	Filter choke, 12H @ 100mA, Hammond part #193B or equivalent.	T2	10W audio output transformer, 8000Ω plate-to-plate primary with ultralinear taps, 4–16Ω secondary (Hammond part #1608 or equivalent.)
L6	100μH molded RF inductor, 10%, Dale Vishay type IM2 or equivalent. Mouser part #70-IM2-100	T3	Power transformer, 250-0-250V @ 100mA, 6.3V @ 3A, 5V @ 2A (Hammond part #270CBX or equivalent.)
L7	10μH molded RF inductor, 10%, Dale-Vishay type IM2 or equivalent. Mouser part #70-IM2-10	V1, V10	6BA6 or 5749/6BA6W
L8	Filter choke, 2H @ 100mA, Hammond part #154M. (Be careful about using a substitute for this choke, since other chokes may have different audio characteristics. See text.)	V2	6C4 or 6100/6C4WA
		V3, V5	12AU7A or 5814A
		V4	6E5 tuning indicator tube (or substitute an analog meter movement)
		V6, V7	6V6 or 6V6GT or 6V6GTA
		V8	0B2 gaseous regulator tube
		V9	0A2 gaseous regulator tube

I included a 6.3V DC heater supply for tubes VI-V3 to produce a completely hum-free radio. A voltage doubler produces about 11V DC from the 5V heater winding on T3, and a standard slow turn-on regulator circuit using an LM317T produces a practically ripple-free 6.3V DC. The LM317T needs a heatsink, which I provided by bolting the tab to a piece of aluminum angle stock, which, in turn, is bolted to the chassis. A thermally conductive washer provides electrical isolation.

Op-amp IC1 requires positive and negative supply rails. The positive rail is from the 6.3V DC heater supply, and a -12.4V DC supply rail is provided by a half-wave voltage doubler using one side of the 6.3V AC heater winding. The voltage doubler supplies approximately -16V, which is regulated down to -12.4V using a couple of 6.2V zener diodes.

Power transformer T3 is heavily loaded, although not overloaded. After prolonged operation, the surface temperature of T3 reaches 50-55°C. Most power transformers are rated for a 60°C temperature rise from ambient, so the temperature of T3 is not a problem, but you should allow for good ventilation as shown in the open design of *Photos 1-3*.

### CONSTRUCTION

I began construction of my radio with antenna L1. I built a 24" x 24" wooden frame using 1/2" x 1 1/8" clear pine trim stock (*Photos 1-3*). For the upright sup-

ports I used 1/2" x 1/2" clear pine trim stock cut to 36" lengths. You should assemble the frame without metal hardware. I used small nails to hold the frame together while the glue dried, and then I removed the nails.

I maintained the 3/8" center-to-center spacing of the turns by cutting slots with a hacksaw in the four outside corners of the frame, starting 1/4" from the edge of the wood. This leaves room for ten slots in the 1 1/8" wide trim stock. Prior to winding the antenna, I stained the pine frame, then applied a coat of polyurethane.

I wound the nine turns of L1 with as much tension as I could by hand, and when I finished the wire was fairly taut. I ran the wires from the two ends of L1 down opposite sides of one of the upright supports. You should do this or something similar in order to keep the wires separate and minimize their mutual capacitance. Do not twist the wires together. You can hold the turns in place with spots of quick-setting epoxy at several locations along each side.

After the epoxy dried, I gave the entire assembly another coat of polyurethane to hold the turns perma-



## Chelmer Valve Company Ltd

The Stables, Baddow Park, Great Baddow, Chelmsford  
Essex, CM2 7SY, England.

email: [sales@chelmervalue.com](mailto:sales@chelmervalue.com) \*\* tel. 44 1245 241 300 fax. 44 1245 241 309 \*\* [www.chelmervalue.com](http://www.chelmervalue.com)

### for High Quality Audio Tubes

Everybody in the audio tube business knows that the justly famous brand names of yesteryear like Brimar, GEC, Mullard, RCA, Telefunken etc. etc. are scarce and often quite expensive. Although we supply all major brands as available (and we have many in stock) our policy is to offer a range of tubes, all new and mostly of current manufacture, the best we can find from factories around the world, which we process to suit audio applications. The result - CVC PREMIUM Brand. Our special processing includes selection for **low noise, hum & microphony** on pre-amp tubes and controlled **burn-in** on power tubes to improve stability avoid tubes with weaknesses etc.

***** A selection of CVC PREMIUM Audio Tubes *****			
PRE-AMP TUBE	POWER TUBES	POWER TUBES cont.	RECTIFIERS cont.
ECC81 5.90	EL34G 8.30	6L6/ 5881 WXT 9.00	5Y3GT 4.80
ECC82 5.90	EL34 (JJ) 8.50	6V6GT 5.50	5Z4GT 5.80
ECC83 5.90	EL34(Large Dia) 11.00	6080 11.50	<b>SOCKETS ETC.</b>
ECC85 6.60	EL84 5.50	6146B 11.00	B9A (Ch or PCB) 1.60
ECC88 5.70	EL509/519 13.00	6336A 48.00	Ditto, Gold Pl. 3.00
ECF82 5.50	E84L/7189 7.50	6550WA/WB 15.00	Octal (Ch or PCB) 1.80
ECL82 6.00	KT66 11.00	7581A 12.00	Ditto, Gold Pl. 4.20
ECL86 6.30	KT66R 22.50	807 10.70	UX4 (4-Pin) 3.60
EF86 6.00	KT77 13.20	811A 11.80	Ditto, Gold Pl. 5.50
E80F Gold Pin 11.00	KT88 13.50	812A 31.00	4 Pin Jumbo 10.00
E81CC Gold 8.00	KT88 (Special) 17.00	845 (New des) 33.50	Ditto, Gold Pl. 13.00
E82CC Gold 9.00	KT88 (GL Type) 30.00	<b>RECTIFIERS</b>	5 Pin (For 807) 3.30
E83CC Gold 8.50	PL509/519 9.90	EZ80 5.10	7 Pin (For 6C33C) 4.70
E88CC Gold 8.80	2A3 (4 pin) 15.50	EZ81 6.00	9 Pin (For EL509) 5.00
6EU7 7.00	2A3 (8 Pin) 17.50	GZ32 15.50	Screen can B9A 2.20
6SL7GT 8.90	211 23.00	GZ33 15.50	Ditto, Gold Pl. 4.30
6SN7GT 5.30	300B 45.00	GZ34 7.20	Top Con. (For 807) 1.70
6922 6.40	6C33C-B 25.00	GZ37 15.50	Ditto, (For EL509) 2.00
7025 7.00	6L6GC 7.60	5U4G 6.30	Retainer (For 5881) 2.20
	6L6WGC/5881 8.90	5V4GT 5.00	

***** And a few 'Other Brands', inc. rare types *****			
5R4GY <i>Fivre/GE</i> 8.50	6SL7GT <i>STC</i> 13.00	13E1 <i>STC</i> 100.00	6550C <i>Svetlana</i> 18.00
5R4WGY <i>Chatham</i> 10.50	6SN7GT <i>Brimar</i> 13.00	211/VT4C <i>GE</i> 120.00	6146B <i>GE</i> 18.50
5Y3WGT <i>Sylv.</i> 6.50	12AT7WA <i>Mullard</i> 6.00	300B <i>JJ</i> 56.00	A2900 <i>GEC</i> 15.00
6AS7GT <i>Sylv.</i> 12.00	12AU7 <i>Mullard</i> 12.50	300B <i>Svetlana</i> 80.00	E88CC <i>Mullard</i> 14.60
6AU6WC <i>Sylv.</i> 5.10	12AY7 <i>GE / RCA</i> 8.40	300B <i>WE</i> 195.00	F2a <i>Siemens</i> 145.00
6B4G <i>Sylv.</i> 27.00	12AZ7 <i>West'h.</i> 8.00	805 <i>USA</i> 52.00	KT66 <i>GEC</i> 69.00
6BW6 <i>Brimar</i> 5.40	12BH7A <i>RCA</i> 14.00	5842A <i>GEC</i> 15.00	KT88 <i>JJ</i> 17.40
6BX7GT <i>GE / RCA</i> 9.00	12BY7A <i>GE</i> 9.50	6080 <i>Telef.</i> 13.30	KT88 <i>Svetlana</i> 35.00
6CG7/6FQ7 8.50	12E1 <i>STC</i> 12.50	6550A <i>GE</i> 31.50	PX25 <i>KR</i> 128.00

ALL PRICES IN U. K. POUNDS £

Please note extras: carriage charge (£3.00 in U.K.) & in EEC VAT (17.50%). When ordering please state if matching required (add £1.00 per tube) . Payment by credit card (VISA, AMEX etc.) or TRANSFER or CHEQUE (UK only). FAX email or POST your ORDER for immediate attention - We will send PROFORMA INVOICE if required. MILLIONS OF OTHER TUBES & SEMICONDUCTORS IN STOCK!

\*\* Valve Amplifiers sound better still with CVC PREMIUM Valves! \*\*

PRICE VALIDITY TO END APRIL 2002 - ASK ABOUT ANY TYPES NOT ON THIS LIST

### TABLE 2 PARTS SUPPLIERS

#### ANTIQUE ELECTRONIC SUPPLY

(480) 820-5411  
[www.tubesandmore.com](http://www.tubesandmore.com)  
RF transformer T1, Hammond components, tubes, air variable capacitors

#### RF PARTS CO.

(800) 737-2787  
[www.rfparts.com](http://www.rfparts.com)  
Air variable capacitors, 6E5 tube, germanium diode

#### MOUSER ELECTRONICS

(800) 346-6873  
[www.mouser.com](http://www.mouser.com)  
Inductors, capacitors, semiconductors, metal chassis

#### ALL ELECTRONICS

(800) 826-5432  
[www.allelectronics.com](http://www.allelectronics.com)  
Germanium diode, various surplus items

#### JAMECO ELECTRONICS

(800) 831-4242  
[www.jameco.com](http://www.jameco.com)  
ClaroStat conductive plastic potentiometer, capacitors, resistors, semiconductors

nently in place. You should wait, however, until you have aligned and tested your radio before using the epoxy or polyurethane, in case you need to change the number of turns on L1. You can hold the turns temporarily in place by using tape.

Loop antennas are directional, and maximum signal pickup is obtained when the signal arrives in the plane of the antenna. Conversely, there is a null in the signal pickup when the signal direction is perpendicular to the plane of the antenna. I bolted the antenna upright supports to the radio chassis in my receiver, so I need to rotate the entire chassis for best reception. But you may choose to build your radio so that the antenna itself rotates.

Assemble the radio itself on a 12" × 8" × 2" aluminum chassis. You should definitely use a metal chassis to obtain a low impedance RF ground. From *Photo 1*, you can see the RF circuitry is on the left-hand side of the chassis, with tubes V1 and V2 at the left rear.

The main tuning capacitor C1 mounts on top of the chassis inside a 3" × 4" × 5" aluminum box. The box provides a ground shield around C1, protects it mechanically, and keeps dust from accumulating between the plates. The power-supply transformer T3 and choke L4 are at the right front of the chassis, and output transformer T2 is at the right rear.

Proper grounding is essential in any RF or audio circuit, and having both on the same chassis as the power supply complicates matters. You should keep all RF grounds short (less than ½") and make them directly to a solder/ground lug bolted to the chassis. Make grounds for audio tube V3 in the same way.

Isolate the ground for the auxiliary audio input jack from the chassis with a nylon washer and run a wire to the same ground lug that R18 and R19 connect to. You should make all grounds for the power supply and audio power amplifier (tubes V5–V7) to an AWG 14 (or larger) copper bus wire, which connects to the chassis at a single point, preferably at the same ground lug that R18 and R19 connect to. Connect the ground wire in the AC power cord directly to a ground lug.

For best operation of the radio (as well as for safety reasons), the radio

needs a grounded three-wire line cord. If you live in an older house and your electrical system is ungrounded, you'll need to provide an alternate ground for the chassis. The *Radio Amateur's Handbook* describes safe and effective ways of doing this.<sup>5</sup>

Keep wiring for the RF circuitry as short as possible—ideally ½" or less—but I have found that it was not always practical to do this. *Photo 4* shows an underside view of the chassis, with my RF wiring in the right rear. The wires leading to capacitors C1 and C2 and antenna L1 are the longest ones. I kept these wires away from the chassis and away from other wires and components in order to minimize stray capacitance.

### SETUP AND ALIGNMENT

To set up and align your receiver, you'll need a high input impedance (10MΩ) vacuum tube voltmeter (VTVM) or digital multimeter (DMM). You'll also need an RF signal generator to provide test signals at the low and high ends of the AM band (approximately 600 and 1400kHz). An oscilloscope is not necessary, but one can be very helpful in troubleshooting.

If you don't have an RF signal generator, you can build the circuit of *Fig. 4* to supply the test signals. This circuit is a Hartley oscillator built with a spare 6BA6 tube and using the radio's own B+ and heater supplies (remove one of the radio's 6V6 tubes while you power this oscillator from the radio's supply rails, to avoid overloading the power supply).

To prevent direct pickup of the oscillator signal, you should provide shielding by building the oscillator in its own separate metal minibox. If you build the oscillator with close tolerance components as specified, the test signals should be within 7.5% of 625kHz and 1420kHz. If you have an accurately calibrated oscilloscope, you can check the output frequencies to be sure they're correct. If not, you must trust that the oscillator is within tolerance.

When you first power-on the receiver, check the supply voltages to be sure they are correct (±10%) as shown in *Fig. 3*. Adjust trimmer R37 to set the DC heater supply to 6.3V. Also check the voltages at selected points in *Figs. 1* and *2*, which should be within about 10% of the values indicated.

Specifically, the 6V6 cathodes should be at 22V, the V5 cathode at 92V, the V3B cathode at 3.3V, the V3A cathode should be at 4.0V, the V2 cathode at 59V, and the V1 cathode at 2.6V. If these voltages are all approximately correct, all of the tubes in the receiver are probably wired properly. If not, look for a wiring error associated with the respective tube.

To align the receiver, connect either your RF signal generator or the circuit of *Fig. 4* to the ungrounded side of antenna L1 through a 100kΩ resistor (put the resistor on the receiver side of the wire or cable you use). If your tuning capacitor C1 has trimmer capacitors, adjust the trimmers for minimum capacity (fully out). Attach your VTVM to point "A" on *Fig. 1*, and set C2 to its half-meshed position. Apply a ~600kHz signal and tune C1 for the maximum negative voltage, which corresponds to maximum eye closure on V4.

You may need to turn down the signal generator level to avoid overlapping the lighted portions of the eye. Conversely, you may need to turn up the signal generator to see any indication on V4. When correctly tuned, C1 should be almost completely meshed. Be careful to avoid tuning to a second harmonic of the signal generator at 1200–1250kHz.

Using a hexagonal adjustment tool (available from Radio Shack as part of a color TV alignment tool kit), adjust the slug on T1 for maximum eye closure. Then readjust C1 for maximum eye closure, then adjust C2, then T1. Continue adjusting these three in sequence until the eye closes no further. You may need to turn down the signal generator as you approach alignment. Temporarily mark the position of C2.

Apply a ~1400kHz signal and adjust C1 for maximum eye closure, then adjust C2. Alternately adjust C1 and C2 until the eye closes no further, and temporarily mark the position of C2. Make sure that maximum eye closure is obtained before C2 is fully meshed. If maximum eye closure is obtained only with C2 fully meshed, you'll need to add some additional capacitance in parallel with C2.

Try adding a 10pF dipped mica in parallel, then repeat the alignment procedure. But I doubt that you'll need any additional capacitance if you used a 33pF trimmer for C2. Assuming C2 is

not fully meshed, alignment is complete. In my radio, C2 is at about one-third meshed at the low end of the AM band and at two-thirds meshed at the high end.

### OPERATION

At this point you should be able to receive many AM radio stations. Tune the radio using C1, then adjust C2 as a fine-tuning control. A little practice will make this easy. Using radio stations as markers, you can determine the tuning range of your receiver.

If you find that you cannot tune to the top end of the AM band, you can remove either a full turn or half turn from L1. Conversely, if you cannot tune to the low end of the AM band, try adding a full or half turn to L1. You'll need to realign the receiver if you change the number of turns on L1. As I mentioned earlier, tapping L1 is one method to extend the tuning range of the receiver, but the need to realign when the taps are changed limits the practicality of this approach.

Once you've settled on the number of turns for L1 and made your final alignment of the receiver, you can make a calibrated dial for C1, and perhaps for C2 as well. I simply affixed a piece of paper to the aluminum chassis behind the knob for C1 and marked my favorite stations on it. But you could easily come up with a more professional-looking dial.

You'll find that the receiver has more gain and greater selectivity at the low end of the AM band than at the high end, but this does not seem to be a serious problem in practice. The reason for this variation is found in transformer T1. Since the primary of this transformer needs to be resonated at a frequency below the AM band, the effective load on V1 varies as a function of frequency, and hence the gain varies.

It is also possible to wind a transformer with a primary that is resonated above the AM band. In fact, that was the more common approach back in the early days of radio. But that only reverses the problem, moving the high gain end of the band to the top.

This variation in gain and selectivity due to the coupling transformers is one of the limitations of a TRF receiver. I find the gain and selectivity more than

adequate across the entire band. But if your favorite station is weak and near the top end of the band, you may find the gain or selectivity inadequate. I think that is unlikely, but you'll only find out for certain by building a prototype.

As I mentioned, the strongest RF signals in my location produce about -1.5V at point "A" in Fig. 1, and I set the gain of IC1 to produce full eye closure for this signal level. You may find that you have stronger or weaker signals, and you can adjust the value of R17 to increase or decrease the gain of IC1 and keep the tuning eye in a useful

range. If you live in an area with a very strong AM station, you may get more than -3V at point "A," which is about the largest signal that the audio amplifier V3A can handle without distortion.

If that is the case, you have two options for handling the large signals. One option is to use a 1MΩ potentiometer in place of R10 to allow you to attenuate the audio signal (connect the wiper to the grid of V3A). The second option is to add an RF gain control by placing a variable resistor in series with R1. Connect one end of a 5kΩ potentiometer to ground, and connect

## Over 2,000 Tube Types for All Applications

RECEIVING • SPECIAL PURPOSE • POWER • INDUSTRIAL • ANTIQUE

★ Highest Quality from the World's Most Popular Manufacturers ★

TYPE	TYPE	TYPE	TYPE
3A3C	6EJ7	12A27A	811A
5AR4	6GH8A	12BA6	812A
5R4GY	6GJ7	12BE6	813
5U4G	6HA5	12BH7A	2050/2050A
5Y3GT	6J5	15CW5	5749/6BA6W
6AJ8	6J7	17JZ8	5814A
6AL5	6JZ8	30AE3	5881
6AQ5	6K7	33GY7A	5965
6AU6	6SA7	35W4	6146A/B
6AX5GT	6SG7	38HE7	6350
6BA6	6SJ7	50C5	6463
6BE6	6SK7	6267	
6BH6	6SN7GTB	6973	
6BL8	6SQ7	7025A	
6CA4	6U8A	7189A	
6CA7	6X4	7581A	
6CG3	6X5GT	KT88	
6CX8	6X8	2D21/EN91	
6CW5	12AT7	85A2/0G3	
6DL5	12AU6	108C1/0B2	
6DQ6B	12AU7	150C4/0A2	
6DR7	12AV6	572B	
6DX8	12AV7	805	
6EA8	12AX7A	807	
6EH7	12AY7	810	

### VOLUME DISCOUNTS

Solid State Replacements as low as \$4.00

Write or call for complete tube range, price list and accessories catalog.



International ©




International Components Corporation

175 Marcus Blvd., Hauppauge, NY 11788 • N.Y. State 631-952-9595 • FAX 631-952-9597

Call TOLL FREE 800-645-9154

www.icc107.com

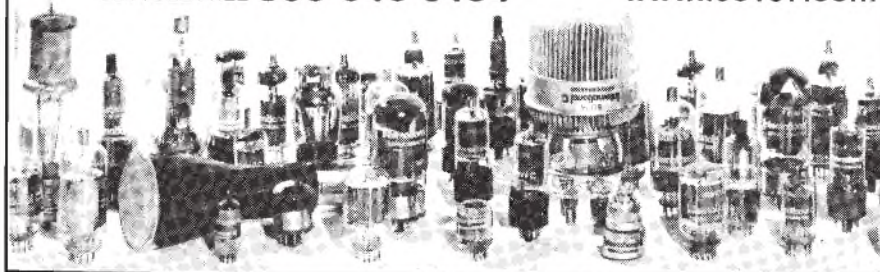

both the wiper and the other end of the potentiometer to the previously grounded end of R1. When the potentiometer is set for zero resistance, the circuit will work as it does now. As the resistance is increased, the gain of V1 is reduced.

If you do add this RF gain control, you should use a high-quality potentiometer, because DC current flows through it at all times, and standard carbon pots quickly become noisy under such conditions. You'll also want to make sure that the potentiometer has almost exactly zero resistance when it is set to one end of its rotation. I recommend a Clarostat or similar conductive plastic potentiometer. Avoid wirewound potentiometers because they are inductive. You can also use a switch to select resistors of different values for R1.

#### AUDIO QUALITY

To get the best audio performance from this receiver, I recommend a high-quality speaker, although it need not be expensive. Most AM radios have poor speakers. I use a Madisound "Sledgeling," a small two-way bookshelf speaker. The audio quality you get will also depend on the RF signal strength and how much RF interference there is in your location, and both of these factors can vary from day to day.

Finally, the audio quality you get depends on the quality of the signal that the radio station itself transmits. Almost all radio stations (AM and FM) use some sort of signal processing to increase the average modulation percentage of their signal. This puts more power into the sidebands and increases the effective amount of power that the station is transmitting, making the station sound louder by increasing the signal-to-noise ratio.

There is nothing really wrong with this, but it obviously impacts audio quality, and if it is overdone the quality can be poor. Stations also sometimes

indulge in equalization, effectively turning up the bass and treble controls whether you like it or not. I find that WNYC and other NPR stations broadcast high-quality signals.

#### CONCLUSIONS

There are several options for building your radio. Obviously, you can build the entire receiver as shown in *Figs. 1-3*, as I did. You could also use the AM tuner as part of your audio system and omit the power amplifier circuitry in *Fig. 2*. In this case the power transformer T2 and filter choke L4 can both be smaller (a 50mA current rating would be sufficient). If you just want to experiment, you could build the tuner circuitry in *Fig. 1* and power it from one or more bench power supplies, but you should still use a metal chassis.

An AM receiver may seem like an anachronism in these days of radio programs streamed over the Internet, but it has brought pleasure to me and to my wife. Perhaps the apparent anachronism is part of the pleasure. In spite of the radio's simplicity, it is the most sensitive radio in the house. The large an-

Buy low. Sell hi-fi.

www.AUDIOGON.com  
HIGH END AUDIO MARKETPLACE

# A Matter of Coincidence

Recorded by Brian H. Preston



A wonderful collection of music recorded using a crossed cardioid microphone technique. This technique enables impressive stereo sound reproduction in keeping with Blumlein's original theory. Selections have been chosen to include a variety of sounds including vocal, chamber ensemble, organ, and jazz band. The music is engaging and the soundstage heard from this technique is remarkable. As well as being entertaining, this CD will also make an excellent test disc for your audio system. 2003.

Sh. wt: 1 lb.

**CDBP1 \$14.95\***

\*Shipping add \$4.00 in US, \$5.00 in Canada, \$7.00, all other surface, \$11.25 all other air.

To order call 1-888-924-9465  
or order on-line at [www.audioXpress.com](http://www.audioXpress.com)!

Old Colony Sound Laboratory, P.O. Box 876 Dept. X2, Peterborough, NH 03458-0876 USA • Toll-Free: 888-924-9465  
Phone: 603-924-9464 • Fax: 603-924-9467 • [www.audioXpress.com](http://www.audioXpress.com) • E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)

tenna and a sensitive detector are the keys to its RF performance.

On recent winter evenings, my wife and I have listened to a French language station from Montreal, which is over 300 miles away. It is certainly possible to build a more sensitive receiver using the superheterodyne approach, but I doubt you'll be able to beat the audio quality of this receiver. It is not CD quality, of course, nor even FM quality, but I think I can promise something much better than you've come to expect from AM radio. I think you will be most pleased with it. ❖

### REFERENCES

1. Vince Roberts, "Letters," *audioXpress*, February 2001, p. 81.
2. My favorite regenerative receiver appeared on p. 210 of the 1944 *Radio Amateur's Handbook*, although this reference is now practically unobtainable.
3. The invention of the superheterodyne was the work of Edwin Howard Armstrong, who also invented FM. See *Man of High Fidelity* by Lawrence Lessing, Bantam Books, Chapter 7, 1969.
4. *The ARRL Handbook for Radio Amateurs*, ISBN #0-87259-186-7, p. 17.18, 2000.
5. *The ARRL Handbook for Radio Amateurs*, ISBN #0-87259-186-7, p. 9.3, 2000.

**From Audio Kits**  
to all types of electronic  
parts... we are **THE Audio**  
**Electronic Supply Source.**



Receive a **FREE Catalog**

**AUDIO**  
ELECTRONIC SUPPLY

1020 Goodworth Drive  
Apex, NC 27539  
919.355.0014 (voice)  
919.355.0013 (fax)

Visit us online for the latest Audio Electronic Supply Catalog at:  
[www.superamp.com](http://www.superamp.com) ■ [www.audioelectronicsupply.com](http://www.audioelectronicsupply.com) ■ [www.sixpacs.com](http://www.sixpacs.com)

# LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES & SEMICONDUCTORS AND I.C.S.

1 MAYO ROAD, CROYDON, SURREY, ENGLAND CR0 2QP  
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

PHONE  
44-208-684-1166

E-MAIL: LANGREX@AOL.COM

FAX  
44-208-684-3056

## A SELECTION OF OUR STOCKS OF NEW ORIGINAL VALVES/TUBES MANY OTHER BRANDS AVAILABLE

STANDARD TYPES			AMERICAN TYPES			SPECIAL QUALITY TYPES		
ECC81	RFT	3.00	5R4GY	RCA	7.50	A2900/CV6091	G.E.C.	17.50
ECC82	RFT	6.00	5U4GB	SYLVANIA	15.00	E82CC	SIEMENS	7.50
ECC83	RFT	8.00	5Y3WGT	SYLVANIA	5.00	E83CC	TESLA	7.50
ECC83	EI	4.00	6BX7GT	GE	7.50	E88CC G. PIN	TESLA	8.50
ECC85	RFT	5.00	6FQ7	EI	5.00	E188CC	MULLARD	20.00
ECC88	BRIMAR	6.00	6L6GC	SYLVANIA	20.00	ECC81/6201	G.E.	5.00
ECC88	MULLARD	10.00	6L6WGB	SYLVANIA	15.00	ECC81/CV4024	MULLARD	6.00
ECL82	MULLARD	5.00	6SL7GT	USA	7.50	ECC81/M8162	MULLARD	7.50
ECL86	TUNGSRAM	10.00	6SN7GT	USA	7.50	ECC81/6201 G. PIN	MULLARD	10.00
EF86	USSR	5.00	6V6GT	BRIMAR	7.50	ECC82/CV4003	MULLARD	15.00
EF86	MULLARD	15.00	12AX7WA	SYLVANIA	7.50	ECC82/M8136	MULLARD	17.50
EL34	EI	6.00	12BH7	BRIMAR	12.00	ECC83/CV4004	MULLARD	40.00
EL37	MULLARD	30.00	12BY7A	G.E.	7.00			
EL84	USSR	3.00	211/VT4C	G.E.	85.00			
EL509	MULLARD	10.00	807	HYTRON	7.50			
EL519	EI	7.50	5687WB	ECG	6.00			
EZ80	MULLARD	5.00	6072A	G.E.	10.00	B7G	CHASSIS	0.60
EZ81	MULLARD	10.00	6080	G.E.	10.00	B9A	CHASSIS	1.00
GZ32	MULLARD	25.00	6146B	RCA	10.00	OCTAL	CHASSIS	1.00
GZ33/37	MULLARD	20.00	6922	G.E.	15.00	OCTAL	MAZDA	2.00
PL509	MULLARD	10.00	6973	E.C.G.	6.00	LOCTAL	B8G CHASSIS	2.50
UCH81	MULLARD	3.00	7308	RCA	15.00			
UCL82	MULLARD	2.00	SV6550C	SYLVANIA	5.00			
				SVETLANA	20.00			

### SCREENING CANS

ALL SIZES 1.00

### MANY OTHER BRANDS AVAILABLE

These are a selection from our stock of over 6,000 types. Please call or FAX for an immediate quotation on any types not listed. We are one of the largest distributors of valves in the UK. Same day dispatch. Visa/Mastercard acceptable. Air Post/ Packing (Please Enquire). Obsolete types are our speciality.

# Extending the 30" Tractrix Horn

This author shows you how to lengthen his horn design to increase its compatibility with other drivers.

By Robert Roggeveen

**A** large mouth concrete axisymmetrical tractrix horn with a small throat is likely made up of two sections: the neck and the bell (*Photo 1*). The reason is twofold: weight and manufacture technique as a result of gravity. The neck is the length from the throat to roughly halfway along the axis toward the mouth. The bell is the rest of the expansion to the terminus mouth flair.

This article describes how to make an extension to the tractrix horn described in "Build Your Own Axisymmetric Tractrix Horn" (*aX* Sept. '02, p. 28); in particular, to the 30" diameter mouth with  $9\frac{5}{8}$ " throat (*Photo 2*) that was mated 1:1 to a 12" EV. (I misstated the diameter as 36" in the article. It really measures 30". Sorry for the mistake.)

## STRETCHING THE NECK

Applying theory, you determine that the lower cutoff of a 15" radius mouth is 150Hz. By lengthening the neck along the tractrix curve path and thus effectively narrowing the throat's diameter, you can mate this large horn to various other drivers needing a smaller throat. I chose a  $2\frac{5}{8}$ " diameter throat.

This neck section has two wooden plates—one for the driver and one to connect with the bell section. Use  $\frac{3}{4}$ " marine plywood for the plates. In between the two plates is concrete, molded to follow the tractrix curve. The mold is built up of sections of disks, each with a radius of 15" made into several cones and stacked on top of one another. Because of the nearly vertical shape, you also need a retention mold to keep the mortar from falling off, which is what sets this project apart from the first.

You must transpose the bell's eight mounting holes accurately to the connecting plate, so when you fasten it the inner circles match up smoothly and the tapers are facing the same direction. Ideally, these two wooden rings are made by joining two  $\frac{3}{4}$ " plywood disks of 15" diameter, cutting the inner throat circle and mounting holes for the driver (12" EV), at once. But I decided on a different process.

## MAKING CONNECTION

I used a test bolt, cut short to  $\frac{3}{4}$ " with a dull point ground on one end. Once you have inserted and screwed it into one of the eight T-nuts in the bell's throat plate, with the ground tip reaching slightly above the plate surface plane, lift the connecting plate, align the center holes by lifting and shifting, and then lower it. Once it is aligned, press lightly where the bolt is inserted. This leaves an indent that marks the spot to be drilled out, slightly oversized relative to the  $\frac{1}{4}$ " hex bolt used to connect the two plates.

Remove and insert the test bolt into the T-nut at 125° to the first, again slightly raised above the plane. Insert a hex bolt through the hole drilled in the connecting plate and into the first T-nut. Since that hex bolt allows the connecting plate to move slightly, align the inner circles and press down gently where the test bolt is inserted, leaving an indent which you will again drill out. Repeat this sequence for all T-nuts, each time placing more hex bolts through the added drilled-out holes in the connecting plate.

The connecting plate (*Photo 3*) looks like a  $\frac{3}{4}$ " thick flat round washer with a

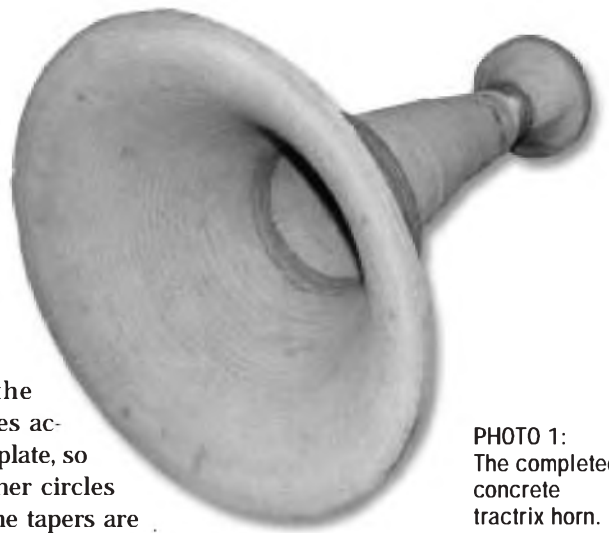


PHOTO 1: The completed concrete tractrix horn.

15" outer diameter and  $9\frac{5}{8}$ " tapered inner diameter. The slant of the taper is about 70° to the surface plane. There are eight  $\frac{1}{16}$ " diameter holes equidistantly placed on a virtual circle corresponding to the T-nuts embedded in the bell's throat plate, roughly in the center of the flat washer's ring area.

This virtual circle produces two areas on the flat connecting plate: an inner surface from the  $9\frac{5}{8}$ " diameter hole to the virtual circle and an outer surface from the outer circumference to the virtual circle. The inner surface gives the image of what is roughly the



PHOTO 2: Horn extension inner mold and connecting plate.



cross section of the concrete horn wall at the connecting plate, revealing a 1¼" thickness.

Thirty-two drywall fasteners are screwed equidistant onto this inner surface area of the connecting plate: 1½", 2", and 2½" in length at a 17° angle with the axis of the horn, slightly more steep compared to the 20° inward slant of the inner ring. These are drawn as far into the predrilled holes and placed in a sine rhythm: 2½, 2, 1½, 2, 2½, 2, 1½, 2

sequence. All slant inward with the contour of the horn's neck. If they reach outward into the open, then you've applied them to the wrong side of the wooden ring. Think of all these screws as anchor rods embedded in the concrete, holding the wooden ring to it.

The eight mounting holes in the connecting plate are fitted with the following ensemble: a hex bolt, a washer, two spacers, and a nut (*Photo 4*). This arrangement is necessary because once

the mortar is applied enough space needs to be left so that you can turn the hex bolt with a ⅝" socket. The height of the tube spacer is ±1½"—cut from ½" inner diameter, clear plastic hose (⅜" thick) that I had on hand. The other spacer is a cylindrical form to stabilize the tube spacer from the inside. Except for painting the connecting plate with bonding agent, it is ready for assembly.

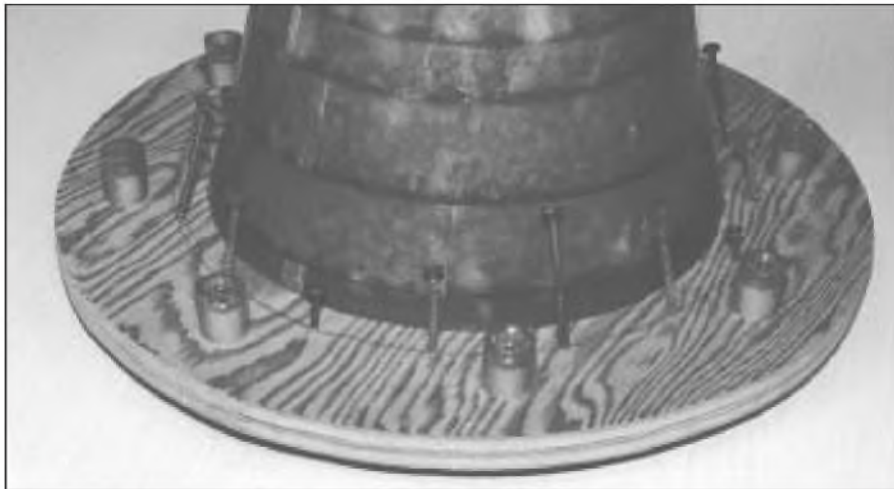


PHOTO 3: Close-up of connecting plate with fasteners.

#### CONSTRUCTION AND ASSEMBLY

Knowing the area of the inner circle in the connecting plate, you can deduce the circumference. Because the inner circle is cut under a slant, use the larger of the two circumferences. Like the bell, you will make the neck of 30" diameter paper disks sections. From a 30" diameter paper disk mark a section with the circumference length slightly longer, by about 1", than the total length of the inner circle circumference of the connecting plate.

In addition, use a protractor to draw a circle with a 7" radius in the center of the 30" disk. For later sections, as they become smaller, use a 9 to 10" radius. Cut out what looks like a washer sec-

## The Ultimate Acoustic Analysis System.

*For real-time testing of  
Audio System performance!*

- 1/12th Octave Real-Time Analyzer (RTA)
  - Energy-Time Graph (ETG) with octave & 1/2 octave band filters
  - Sound Pressure Level Meter
- Speaker Distortion Meter (THD+N)
  - Signal to Noise Ratio
  - Speaker Polarity Test
- Integrated Audio Signal Generator
- Handheld, Portable, Battery Operated
- Serial Data Download and Report Software



Powerful • Portable • Affordable

# SENCORE

1-800-736-2673 • [sencore.com](http://sencore.com) • e-mail [sales@sencore.com](mailto:sales@sencore.com)

Subscribe To The **SENCORE** News at [www.sencore.com](http://www.sencore.com)

tion. Mating the linear edges of the section with two paper clips will produce a truncated cone. For a thorough explanation of how to make cones and the tractrix curve for these concrete horns, read the aX Sept. '02 article.

Slip the connecting plate over the cone. It should not slide off at the bottom. If it gets hung up with more than ¼" remaining under the plate, adjust the paper overlap. It helps to mark several radial lines on the paper section to keep the cone properly aligned when you make adjustments. Cut the excess, if any, to leave a ¼" glue strip.

This is the initial cone. Before gluing it, copy this paper section on the left-over section of the 30" diameter disk you just worked with. You can cut about four or more cone sections from the same disk. Each cone is ½" less in circumference than the previous one. So, following the initial cone, the second cone is ½" less in circumference length, the third is 1" less than the initial circumference length, the fourth is 1½" less than the initial circumference length, and so forth.

All cones stacked up produce a shallow axisymmetrical tractrix curve of the neck of the horn along its 24" length. Prepare the stacked cones with epoxy for a sturdy and water-repellent mold. It is now ready for assembly.

The outer retainer mold has a base cone that fits outside the 32 screws and just inside the eight mounting holes of the connecting plate (Photo 5). For the retainer mold a larger diameter paper disk is used to make the cones. They have at this distance along the axis a greater base circumference. I estimated 48" diameter and worked with sections of that size. The shape of the outer retainer mold is not critical and is built up in four sections (Photo 6).

Working with cones of 6¼" in height allows for adequate though tight space to work mortar into the void formed by the inner tractrix mold and the outer retainer mold. Once the base cone has been established, the second cone will fit over the base cone at its very top (Photo 7), producing an overlap of just ¼". The third cone overlaps the second cone's top ¼". And the fourth overlaps the third (Photo 8).

Whereas building the tractrix curve mold cones are stacked on one another

leaving only a small conical area exposed at the bottom of the previously placed cone, the building of the outer mold is one where stacking cones leaves the vast majority exposed, overlapping only ¼" or small conical area at the top of the previously placed cone.

#### COVERED WITH MUD

Consider the substantial dry weight of the concrete. The 30" bell weighs 63 lb. The extension weighs 40 lb. This outer set of cones does not have the integral strength of the inner tractrix mold. Furthermore, the cones of the outer mold are not glued to each other, so you need to reinforce them with lateral rings perpendicular to the cone surface extend-

ing outward (Photo 6). Cut paper rings and glue them with epoxy onto the outer surface of the individual outer mold cones. Paint the cones on the inside with epoxy to strengthen them and make them water-repellent.

In addition, applying mortar causes the outer cones to move upward relative to the inner mold! To counteract this force, you may choose to apply tabs to the base outer mold, held in place by the eight hex bolt ensembles. I did not have these tabs in place, causing the mold to move ½" upward when I worked the mortar into the gap.

Take the prepared connection plate with its screws, bolts, and spacers in place, and fit it into position onto the

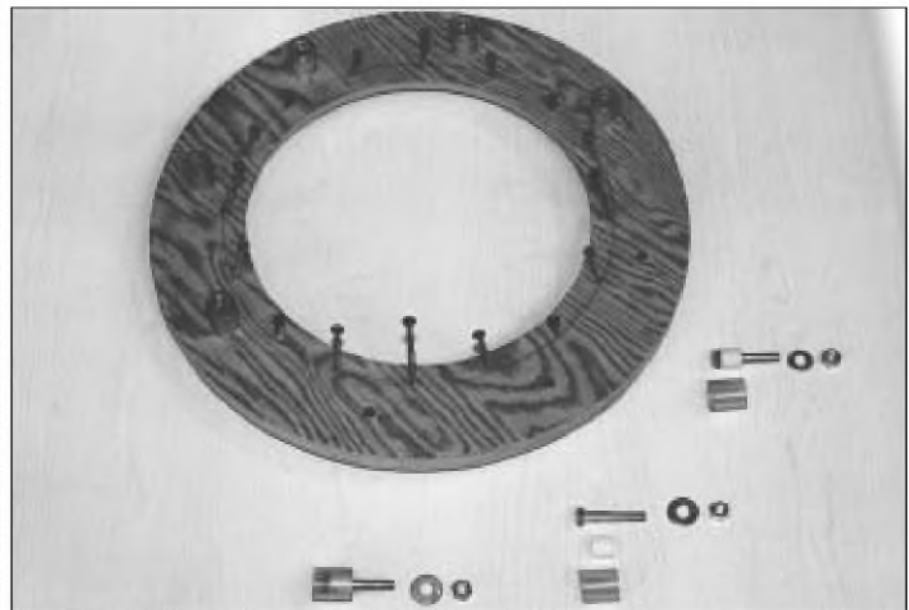


PHOTO 4: Bolt mounting and casting spacer sequence.



PHOTO 5: Fitting the base retainer mold sections, reinforced by a second ring.

epoxied tractrix inner mold, at the base. Just prior to applying mortar, paint the inner surface area and screws on the connecting plate with a bonding agent. Note the outer mold cones with the paper reinforcement rings mounted. These are painted with epoxy on the inside. A 1/4" plywood disk 6" in diameter with a 2 1/8" circular hole in the middle flattens the mortar level at the throat, once applied.

Start by applying mortar into the narrow upright wall void formed by the outer base cone tractrix and tamping and thoroughly working the mud around the screws at the base and all along the neck upward in a spiral motion. Stack the four outer mold cones sequentially as you build up the mortar to form the outer retainer mold. The greater the height, the more precarious it is to work the mortar. The height of

each cone just barely worked. I used a palette knife to shove mud into what is essentially a curved slot, poking and mixing, laying and pressing fairly swiftly, moving around the perimeter. After building up the first 5 1/2" of horn wall, place the second outer cone, overlapping the first by 1/4".

Measuring, marking, cutting, and gluing paper are all quite important, just as with the inner tractrix mold. Good accurate craftsmanship pays off. Once you toss a portion of mud into the wall void, work it right away, keep the layering manageable, and don't forget where you just were. Some of this kind of work is done by feel, as if blindfolded (Photo 9).



PHOTO 6: Retainer mold cone sections.

### FINISHING TOUCHES

At the very upper part of the neck, at the throat, use the wooden level ring to produce an even plane. It helps to have marked the inner mold at the 2 1/8" diameter level. I overapplied mortar, compressing the concrete slightly down to the proper mark. Stick six tack nails into the mortar near the throat on the outside perpendicular to the outer

## Quieter than a computer mouse.

auto

home

marine

aero

industrial

studio

Zeronoize knows what it takes to enjoy the finest sound quality possible and with Cascade Audio Engineering's sound control products you're bound to feel the music!

CAE offers the most advanced dampers, barriers, absorbers, diffusers, traps and baffles available in the industry.

You'll be amazed how easy it is to restore lost midbass and achieve levels of sonic accuracy never thought possible.

Visit [www.zeronoize.com](http://www.zeronoize.com) today and view our complete selection of VBLOK sound control products.

Zeronoize.com, silence at the tip of your fingers.

### Deflex PowerPads

These amazing speaker tuning pads will eliminate speaker backwave once and for all! Install them behind any speaker where a parallel wall exists to fragment speaker backwave and eliminate standing waves within a loudspeaker enclosure. Install a pair and discover accuracy, smooth response and realize a dramatic improvement in sound quality.

sizes: 5" 7" 9" 13"



### VBIX

VBIX vibration damping compound works well when brushed onto the inside surfaces of a loudspeaker enclosure. When cured, the impedance mismatch created can improve output 1 to 1.5 db!

sizes: 1qt 1g 5g



61580 American Lane Suite #3

Bend, Oregon, 97702

[www.zeronoize.com](http://www.zeronoize.com)

[info@zeronoize.com](mailto:info@zeronoize.com)

mold surface, pricking through the paper cone. Let it dry.

Install the driver mounting plate with T-nuts embedded in the 3/4" marine plywood as needed. My prototype included 12 to test the Siare, Pyle, and JBL drivers. Prepare the plate with anchor screws. Place a paper ribbon around the perimeter of the plate to produce a dam to keep the mortar from spilling off the surface of the plate.

Break the concrete extension out of both molds. Let it dry some more. If there are no voids you did a most excellent job. Even if there are some big neglected spots where the mud was not mixed in well you can fill mortar in later to repair these blemishes (Photo 10). It is essential, however, to have the inside surface finished as smooth as possible for the sound wave to propagate properly. The final horn surface is finished with a paste used to seal bathroom tile grout.

Place the throat end of the concrete extension on a piece of cardboard (Photo 11). It may be thin walled, so be careful. The best defense against brittle mud is a good mixture and adequate

curing time, three to four days. Check how it looks. Does it stay upright or lean? This is why it was important that the throat was tapped level.

#### BONDING THE DRIVER PLATE

With the hole centered, T-nuts embedded, wax plugs inserted, and screws and paper edge sticking up, place the concrete throat onto the wooden throat. Mix mortar and paint the plate side facing the concrete and the concrete on the outside of the horn about 4" up with

bonding agent. Place the horn, accurately aligning the throat opening.

Apply the mix in manageable steps, working it around the screws using up and down movements with a palette knife, a dowel, or a piece of wood. Tamp and stir, applying the mix around and up the neck. Before the mortar hardens, you can finish off the top surface in a number of different ways: leave it rough, smooth it, or cut patterns or letters into it. Let it dry. After a day remove the paper dam.



PHOTO 7: Assembling the horn mold pieces ready for casting, a dry run.



PHOTO 8: Overlapping cones in place, a dry run.



PHOTO 9: Forming the concrete mold.

Now IN THE  
**6th**  
EDITION



- More Pages
- More Graphs
- More References
- Brand New Chapters
- Explanations of New Technology

BKAA60  
\$39.95

Order Your Copy  
**TODAY**  
by calling

**1-888-924-9465**

or order on-line at  
[www.audioXpress.com](http://www.audioXpress.com)

Shipping and handling add \$7.25, Canada add \$11.00

Overseas surface mail add \$10.25, air mail add \$22.25.

Old Colony Sound Laboratory, PO Box 876  
Dept. X3, Peterborough, NH 03458-0876 USA  
Phone: 603-924-9464 Fax: 603-924-9467  
E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)

When the concrete has cured and it appears solid, fill in gross, moderate, and minor blemishes as needed on the inside and on the outside of the horn. Fix the substantial blemishes

with mortar mix. Let it dry and finally cover all of the horn inside with a finishing patch material. A smooth surface, with no air leaks, is important. Use a narrow palette knife to strike off



PHOTO 10: Patch up any blemishes on your concrete shell.



PHOTO 11: Aligning the wooden and concrete throats.



## One Groove

## Five Signals

## PERFECTLY ALIGNED

KAB introduces Groove Tuning™ A new concept that lets you mix the five signals of a mono groove for the best sound possible.

Learn More Online


**KAB**

Preserving The Sounds Of A Lifetime

[www.kabusa.com](http://www.kabusa.com)
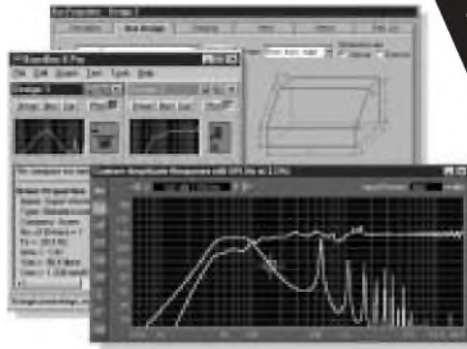
### Design speaker boxes with BassBox Pro


Design speaker boxes for any space: car, truck, van, home hi-fi, home theater, pro sound, studio, stage, PA and musical instruments. Import acoustic measurements. For example, the response of a car can be imported to simulate the in-car response.



\$129  
plus S&H
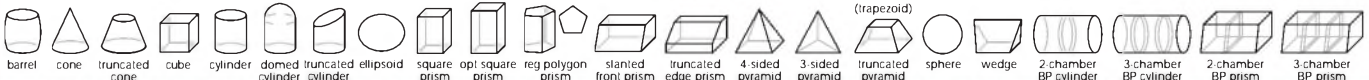
#### Sophisticated Driver Modeling and Advanced Box Design

- Multiple drivers with isobaric, push-pull and bessel options. • 3 dual voice coil wiring options. • "Expert Mode" dynamically analyzes driver parameters. • Design closed, vented, bandpass and passive radiator boxes. • "Suggest" feature provides fast box design. • All box types account for leakage losses and internal absorption.
- Advanced vent calculation. • Bandpass boxes can be single or double-tuned with 2 or 3 chambers. • 22 box shapes (shown below). • Open up to 10 designs at one time.
- Analyze small-signal performance with: Normalized Amplitude Response, Impedance, Phase and Group Delay graphs. • Analyze large-signal performance with: Custom Amplitude Response, Max Acoustic Power, Max Electric Input Power, Cone Displacement and Vent Air Velocity graphs. • Includes a helpful "Design Wizard" for beginners.



### Need help with your speaker designs? BassBox Pro & X-over Pro can help!



Harris Tech Pro software for Microsoft® Windows can help you quickly create professional speaker designs. Our software is easy to use with features like "Welcome" windows, context-sensitive "balloon" help, extensive online manuals with tutorials and beautifully illustrated printed manuals. We include the world's largest driver database with the parameters for many thousands of drivers.


For more information please visit our internet website at:  
[www.ht-audio.com](http://www.ht-audio.com)

Tel: 269-641-5924  
Fax: 269-641-5738  
sales@ht-audio.com

Harris Technologies, Inc.  
P.O. Box 622  
Edwardsburg, MI  
49112-0622  
U.S.A.
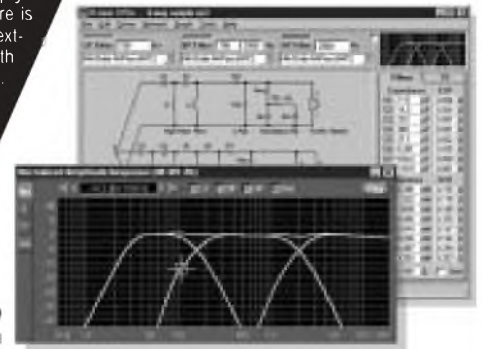
### Design crossovers with X-over Pro

Design 2-way and 3-way passive crossover networks, high-pass, band-pass or low-pass filters, impedance equalization, L-pads and series or parallel notch filters. Its Thiele-Small model provides professional results without complex testing.



\$99  
plus S&H

#### Passive Crossover Filters and Scalable Driver Modeling

- 1st, 2nd, 3rd and 4th-order "ladder" filter topologies. • Parallel crossover topology. • 2-way crossovers offer Bessel, Butterworth, Chebyshev, Gaussian, Legendre, Linear-Phase and Linkwitz-Riley filters. • 3-way crossovers offer All-Pass Crossover (APC) and Constant-Power Crossover (CPC) filters. X-over Pro's capabilities scale to fit the amount of driver data. • A crossover, filter or L-pad can be designed with just the nominal impedance of each driver. • With full Thiele-Small parameters, impedance equalization can be designed and the performance graphed.
- Graphs include: Normalized Amplitude Response, Impedance, Phase & Group Delay.
- Graphs can include the full speaker response including the box. • Estimate component resistance (ESR & DCR). • Calculate the resistance of parallel or series components.

any excess humps or bumps. Sand the area.

### CONCLUSION

This extension project pushed the limits a bit. All mold materials, although fortified with epoxy, are made of paper, so weight plays a major part. The mortar casting is most exciting and anxiety provoking, as about 40 lb of mortar is controlled in paper. To see the paper stand up to such tensions is quite amazing.

I used two layers of cotton duck material, such as from old jeans, to make a gasket to fit between the neck and the bell. Stitch the two at the edges and make eyelets for the bolts. The inside diameter should be flush with the wooden rings. Connect the extension to the bell with eight hex bolts.

Now this is a formidable tractrix horn approximation. It has a 2 1/8" throat, 30" mouth, is 37" in length, and weighs 100 lb. The weaknesses are that the horn is slightly foreshortened relative to the ideal, and it is heavy. Strengths are firmness, high decibels in the band-pass, on-axis circular propagation of the sound-wave front, sound presence,

and punch at a relatively far distance.

Table 1 contains 11 response tests I conducted on six different configura-

tions so far. I performed the tests in an open field with salal, huckleberry, cedar, and fir at the perimeter 70' or

TABLE 1

TEST:	1	2	3	4	5	6	7	8	9	10	11
HERTZ	dB	dB	dB	dB	dB	dB	dB	dB	dB	dB	dB
61			50	66	56	54		56	62	67	
127	65	76	55	75	79	74	54	78	78	79	
251	73	84	67	80	89	86	71	91	90	92	92
499	92	85	81	94	95	93	82	95	95	91	92
997	92	93	85	88	93	92	86	93	88	90	103
1999	89	90	84	69	88	83	83	85	76	88	97
4001	83	86	86	81	86	80	84	84	75	76	92
7993	76	66	85	64	72	73	83	80	64	67	73
10007	80		76		77	78	66	73			70
12503	56		61		54	63	65	58			
16001			61			60	64				
Throat (in. dia.)	2.12	2.12	4.25	2.12	2.12	2.12	2.12	2.12	2.12	9.37	1.5
Mouth (in. dia.)	12	9.25	18	30	30	30	30	30	30	30	30
Length (inches)	8.75	26	10	37	37	37	37	37	37	11	45
Gap (inches)	—	—	1/2	—	—	—	1/2	—	—	—	—
Back vol (quarts)	—	—	—	—	—	—	—	2	2	—	—
f <sub>c</sub> (Hz)	358	458	238	150	150	150	150	150	150	150	150
Drivers:						Test:					
JBL 104H-2						1, 2, 5, 8					
SIARE 16-VR						3, 6, 7, 11					
PYLE W6C200F						4, 9					
EV 12L						10					

VACUUM TUBES • TRANSFORMERS • PUBLICATIONS • SIGNAL PROCESSORS • TUNERS • CD PLAYERS • NOS TUBES • GUITAR AMPS • SOFTWARE

## They'll Find YOU in the World Tube Directory!

Showcase your products in the established tube audio industry sourcebook. Now in its 10th year!

- Target thousands of active buyers who are convinced that vacuum tube components offer superior sound reproduction.
- Used throughout the year by audiophiles, DIY enthusiasts, musicians, technicians, dealers and others, to locate tubes, gear, parts, and related accessories.

Call TODAY to reserve ad space and to register for a free company listing.

**Bonus!** Order by 9/1/03 to get a FREE online ad AND (with a 1/2 page or larger) a FREE classified ad in *audioXpress* for three issues!

CONTACT PUBLISHERS REP: Peter Wusiel • Strategic Media Marketing  
 ph: 978-281-7708 • fax: 603-924-6230 • e-mail: peterw1@gls.net

2004 ANNUAL EDITION—SPACE CLOSING, 10/1/03 MAILED 11/20/03

Want to reach even more tube audio enthusiasts?  
 Advertise right here in **audio PRESS** magazine.



PO Box 876  
 305 Union Street  
 Peterborough, NH  
 03458-0876 USA

POWER AMPS • MIXERS • CONNECTORS • CHASSIS • MIKE PREAMPS • CABLES

KITS • GUITAR EFFECTS • CIRCUIT DESIGNS • TUBE MIXERS • POWER SUPPLIES • KNOS

DIRECT BOXES • HI-FI AMPLIFIERS • COMPRESSORS/LIMITERS • CAPACITORS • CROSSOVERS • REVERB UNITS • PHONO STAGES • SWITCHES

more away from all sides. It was a sunny, fall afternoon (*Photo 12*).

Although designed as a tractrix contour propagation, the extension mimics an exponential expansion fairly closely. So I tested it as such (test #2): 2 1/8" throat, 9 1/4" mouth, and 26" long!

For the test I used a CBS test CD (Old Colony) and played on an unmodified CDB 560 Magnavox CD player. The tube amp is a 145 Leslie, taken from a tone

cabinet. I measured with a Radio Shack digital sound level meter (33-2055) on-axis at 1m. Signal potential is held at 2.71V.

This extension project spurred me on to experiment further. Test 11 is of a horn incorporating an additional 6" extension narrowing the throat from 2.12 to 1.5" in diameter. I may report on this later. In the meantime, enjoy building and listening to horns. ❖



PHOTO 12: The author tests his finished product.

## Lundahl Transformers in the U.S.

**K&K Audio** is now selling the premier European audio transformers in the U.S.

High quality C-core transformers and chokes using silicon iron, mumetal, and amorphous cores.

- Power output transformers – SE or PP
- Interstage transformers – SE or PP
- Line output transformers – SE, PP, and parallel feed
- Input transformers – MC or line
- Audio chokes
- Power transformers
- Power supply chokes

High End Audio Kits using Lundahl Transformers

- MC Phono Step-up Unit
- Phono Preamplifier
- Line Stage Preamplifier
- Microphone Preamplifier

For more information on our products and services please contact us at:

[www.kandkaudio.com](http://www.kandkaudio.com)

info@kandkaudio.com voice/fax 919 387-0911

### GRANDMOS The SMART amplifier

## 2 Audiophile Masterpieces for the DIYer

### TRIPHON The ULTIMATE crossover system



- ✓ Probably, the nearest approach to :  
"A STRAIGHT WIRE WITH GAIN".
- ✓ High end 2 x 100 WRMS / 8 ohms MOS-FET amplifier.
- ✓ SILVER plated PTFE / fiberglass printed circuit boards.
- ✓ SILVER plated connections.
- ✓ Military grade components.
- ✓ Only J-FET and MOS-FET audio transistors.
- ✓ NO CAPACITOR in the sound path \*.
- ✓ Minimum wiring and easy construction.
- ✓ Outstanding performances.
- ✓ Absolute Transparency and Sound.
- ✓ Extremely reliable.
- ✓ Steady performances over years.

\* : under certain conditions

To complete the GRANDMOS (or any good quality amplifier) we have designed the TRIPHON system :

- ✓ Musically neutral and transparent.
- ✓ 3-way electronic crossover.
- ✓ 6 or 12 dB/octave slope (true LINNKWITZ-RILEY filter).
- ✓ 4-channel Class A minimalist MOS-FET amplifier for MID and HIGH frequencies.
- ✓ Choice of cut-off frequency.
- ✓ PTFE / fiberglass printed circuit boards.
- ✓ Fully discrete component technology.
- ✓ SILVER plated connections.
- ✓ Minimal wiring.

by  
**Selectronic**  
INSISTANTIA TELETECHNIE

[www.selectronic.fr](http://www.selectronic.fr)

Phone : + 33 - 328 550 328 - Fax : +33 - 328 550 329  
BP 513 59022 LILLE - FRANCE

>> Detailed information on [www.selectronic.fr](http://www.selectronic.fr) or by e-mail to : [selectrocom@selectronic.fr](mailto:selectrocom@selectronic.fr) <<



# Improving Dynaco's FM-5 and AF-6 Tuners

Discover how to add IC voltage regulators to either a Dynaco model FM-5 or model AF-6 tuner, and also correct the low-frequency drop in the demodulated signal of the early model FM-5. **By Daniel Dufresne**

A few years ago a friend gave me a Dynaco FM-5 FM tuner, which I cleaned up and tried. The unit worked and provided mono audio output, but no stereo output. I replaced the stereo decoder IC Q205, a Motorola MC1307P, with an NTE Electronics Inc. NTE722, and I realigned it. It worked fine and I installed it in my dining room, along with a Dynaco SCA-80 integrated amplifier and two Dynaco A-25 speakers, a true classic all-Dynaco system. I know this sound system is more than 30 years old in design and production, but it works and has escaped the landfill.

Later, I noticed that if I turned on the tuner and immediately changed station tuning, after about five or so minutes it would start muting occasionally. After ten more minutes, it would mute permanently. All I needed to do was to retune slightly and it would stay properly tuned and not mute until I turned it off.

I told myself that I probably had been inattentive when I initially aligned it and I needed to realign it. Then I thought that no misalignment would cause this, but drift would show these types of symptoms. Could the power-supply voltage drift and cause the rest to drift, too? I do not have the equipment to check the RF or IF circuits for drift, but I sure can check the power supply.

## VERSIONS

My FM-5 is the early model with PC-20 and PC-21 printed wire boards (PWBs). There is a later FM-5 version with a different set of boards, PC-25 and PC-26, which are the same ones used in the AF-6. The information in this article can be used for all versions. The AF-6

has a different front end and an added assembly, PC-27, to take care of the AM tuning and demodulating functions.

## REFERENCED DOCUMENTS

I checked back issues of *The Audio Amateur* for any information on Dynaco tuners or FM tuners in general. "Upgrade your FM-5"<sup>1</sup> is a two-page article on improving sonic qualities. There is a "Kit Report"<sup>2</sup> on the VSM Audio, MPX-2 phase-locked loop stereo demodulator using an KB4437 IC, designed for replacing the stereo decoder circuit with an improved IC-based stereo decoder. This was followed by a letter<sup>3</sup> that describes experiments done on this kit and other notes on stereo adjustment for the FM-5.

Finally, I found an article, "Upgrading your FM tuner,"<sup>4</sup> on general modifications. It shows how to add signal

buffers on audio outputs and certain internal nodes where there are some notable improvements. There is a section on adding a regulated power supply, tuning indicator, and a muting comparator. The regulator is based on the Raytheon RC4195-TK IC, which is a fixed dual 15V positive and negative circuit. Raytheon sold the rights for this IC to Fairchild Semiconductor, but I could not


find it on their website.

The Motorola MC-1468 and the National Semiconductor LM325 are equivalents. The LM325 will be obsolete shortly. I could not find the MC1468 on the On Semiconductor website.

I found nothing on drift or erratic muting behavior either in the literature or on the web. I did find the schematic for the FM-5 with PC-25 and PC-26 and tuner alignment information at these addresses: [http://home.indy.net/\\_gregdunn/dynaco/components/FM5/align.html](http://home.indy.net/_gregdunn/dynaco/components/FM5/align.html), and <http://members.home.net/dunn.greg/fm5/schem.jpg>. (Hint: go to these addresses and save both the tuning procedure and the schematics on your computer for safekeeping, in case this site disappears.)
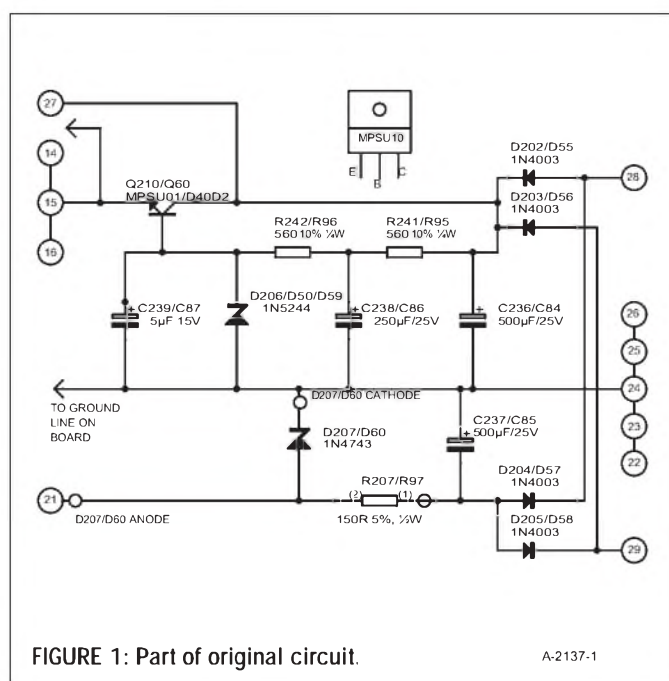
## JUST MAYBE

Having put forth the hypothesis that supply drift was the cause of the misbehavior, I needed to investigate. This means some measurements and some experiments. I also needed an explanation for drift. Even if the FM-5 is an all-





semiconductor tuner, thermal drift is everywhere—in resistors, diodes, and transistors alike. Check some data books, and you will see. You need to determine and evaluate how big and how important its impact may be on circuit performance.

I looked at the tuner's schematic and noticed that it uses a simple shunt zener diode for the negative supply and an amplified zener for the positive supply (Fig. 1). The parts identifications refer to FM-5 both PC-21 and PC-26 in that order, except for D206/D50/D59, which is for FM-5 PC-21/FM-5 PC-26/AF-6 PC-26. The numbered circles represent the PWB eyelets used for interconnections. I brought the tuner to my test bench and did some measurements. The results are in Tables 1–5.

### ORIGINAL CIRCUIT DESCRIPTIONS (PART REFERENCES ARE FOR FM-5 PC-21 VERSION.)

All the power for this tuner comes from a single power transformer with dual secondary. One winding powers the panel lamps; the other has a center tap and powers all the electronics. A full-wave rectifier bridge made from four discrete diodes, D202–D205, charges up two capacitors, C236 and C237, to provide the two raw DC voltages, positive and negative. A two-stage low-pass filter, made from R241 and C238 and R242 and C239, respectively, powers zener diode D206, which connects to the pass tran-

sistor's, Q210, base. The collector connects to the raw positive supply. The emitter is the output terminal.

The negative supply is made of a series-limiting resistor, R207, and a shunt zener diode, D207. These two circuits provide a positive supply of 13.6V and a negative supply of –13.6V.

### POWER-SUPPLY MEASUREMENTS ON ORIGINAL CIRCUIT

The raw positive supply is typically 18.8V with about 1.2V peak-to-peak ripple. The raw negative supply is 22.6V with 250mV peak-to-peak ripple. All these values can vary according to the supply line voltage value.

The positive supply loads are: RF front end only, 16.7mA–18.3mA; PC-20 and front end, 63.7mA–65.6mA; and total positive supply load between 93.7mA and 97.4mA. The two lamps, “tuned” and “stereo,” are powered from the raw DC and consume about 36mA each. The negative supply load is 9.6mA–10.2mA (into PC-20) and 9.7mA–10.4mA (total).

I measured the warm-up drift, which caused the positive supply to change by 0.3V after three hours. Power-line regulation showed a 0.3V change for a 105V to 130V input change range. I told myself that for the tuner's cost and year of design, it is reasonable to use simple zener voltage regulator circuits.

Integrated regulators cost very little these days and could improve the per-

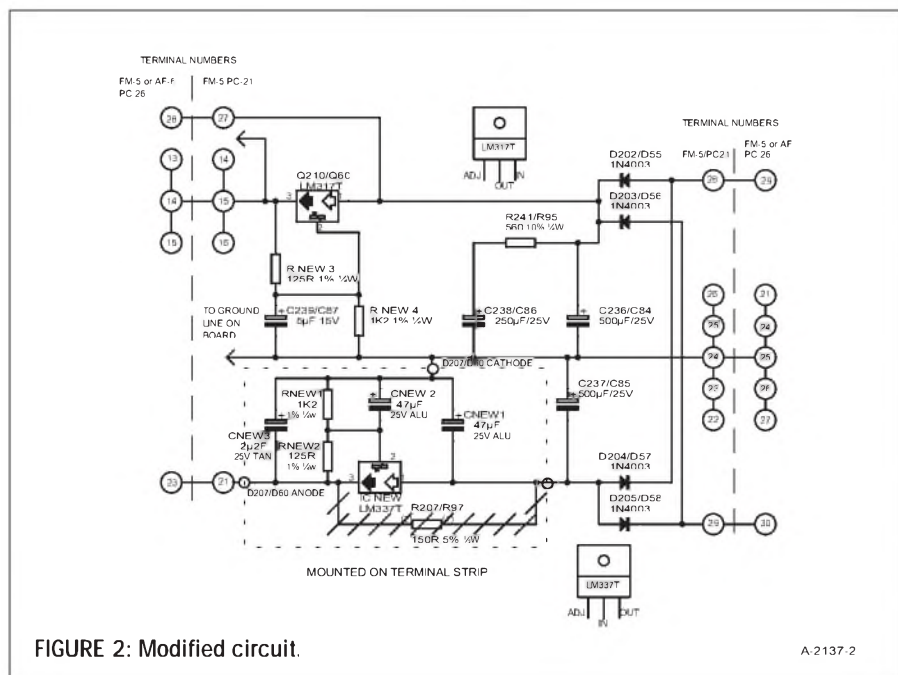


FIGURE 2: Modified circuit.

A-2137-2

## silver flute

Madisound is pleased to introduce this new line of Wool fiber cone woofers from Silver Flute. These drivers feature:

- Wool fiber cones
- Cast frames
- Rubber surrounds
- Economical pricing

We currently offer these speakers in three sizes, 5", 6.5" and 8". The 5" and 6.5" are also available shielded. We will continue to expand the line to include a 10" and 12" version and 4 ohm versions of all drivers.


### W14RC25

Fs 43.5 Hz  
Qts 0.35  
Vas 18.9 ltrs  
X-max 3.5mm  
Sens. 87.5dB  
Price \$14.25


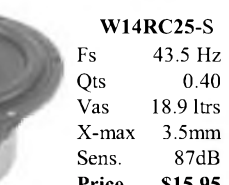
### W14RC25-S

Fs 43.5 Hz  
Qts 0.40  
Vas 18.9 ltrs  
X-max 3.5mm  
Sens. 87dB  
Price \$15.95




### W17RC38

Fs 40.5 Hz  
Qts 0.29  
Vas 28.2 ltrs  
X-max 5mm  
Sens. 89dB  
Price \$19.40


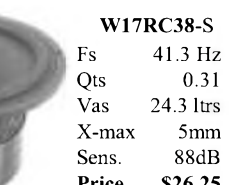
### W17RC38-S

Fs 41.3 Hz  
Qts 0.31  
Vas 24.3 ltrs  
X-max 5mm  
Sens. 88dB  
Price \$26.25



### W20RC38

Fs 30.8 Hz  
Qts 0.23  
Vas 83.3 ltrs  
X-max 5mm  
Sens. 91dB  
Price \$26.60



MADISOUND SPEAKER COMPONENTS, INC.  
8608 UNIVERSITY GREEN  
P.O. BOX 44283  
MADISON, WI 53744-4283 U.S.A.  
TEL 608-831-3433 FAX 608-831-3771  
e-mail info@madisound.com  
Web Page http://www.madisound.com

formance of this tuner's power supply. I decided to replace both the positive and the negative regulator circuits with IC regulators. *Figure 2* shows the schematic of the new voltage regulator section. Whether this change would eliminate the observed drift and improve measured or audible sonic performance remained to be seen.

Should your tuner have a power-supply failure, you might also consider these modifications, which add little cost and take two to three hours to execute. The modified circuit performance along with the original circuit measurements are in *Tables 1-5*.

### NEW REGULATOR CIRCUIT DESCRIPTION

The positive voltage regulator IC is an LM317T, which is adjustable simply by selecting the appropriate resistor values. The first resistor is connected between the regulator output and the regulator adjust terminal. I chose a 124Ω value because the regulator reference voltage is nominally 1.25V. This choice makes the rest of the calculations quite simple.

Also, the regulator needs a minimum of about 10mA to work properly, and this low resistor value provides such a load. To get 13.2V you need the second resistor connected between the adjust terminal and ground to be 1k2. It will have approximately 12V across its terminals. The adjust pin is bypassed to ground with a 5μF capacitor (C239 or C87) to improve the ripple rejection.

The negative voltage regulator circuit is the same as for the positive, but

with two more capacitors: one on the input and one on the output. Both capacitors improve and ensure regulator stability because of the added wire resistance and inductance.

### CAUTION! GLASS INSIDE

When working inside the tuner, try to stay away from the two tubular dial lamps, Dynaco part number 526008, which are located at both ends of the tuning scale. The bulbs look like longish fuses, 1.625" long by 0.25" in diameter.

The lamp bulbs are somewhat fragile; they break easily at the glass to terminal junction. The terminals break away from the glass body and you are left with a short piece of wire protruding from the body; that is, if you are lucky. If not, there is no wire left attached to the body for you to try to reattach.

New bulbs are difficult to find. If you know where to find replacement lamps for these, please contact *audioXpress* with the manufacturer's name, address, part number, price, and distributors.

**TABLE 3**  
**POSITIVE SUPPLY, HUM AND NOISE MEASUREMENTS**

	ORIGINAL CIRCUIT	LM317	IMPROVEMENT
Measurement bandwidth	mV, AC	mV, AC	dB
22.4Hz to 22.4kHz	0.85	0.049	24.7
Plus "A" weighting	0.64	0.019	30.5

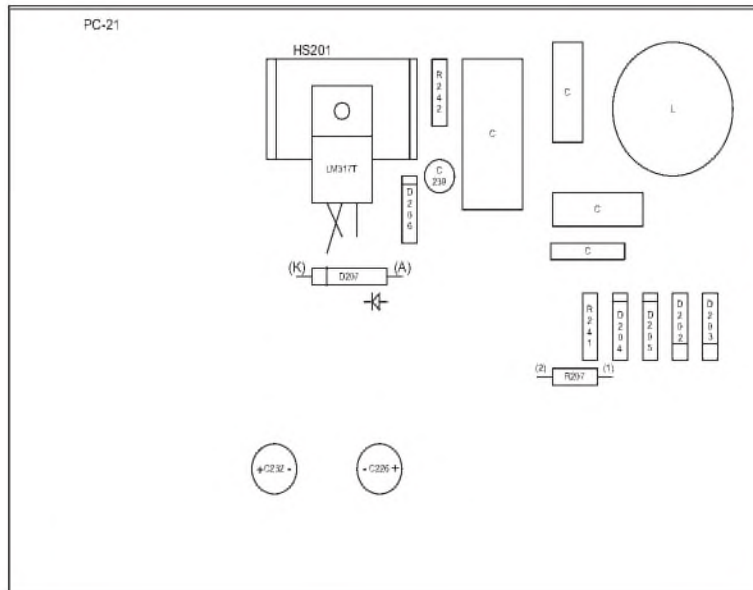


FIGURE 3: Principal parts placement on PC-21.

A-2137-3

**TABLE 1**  
**POSITIVE SUPPLY, DRIFT MEASUREMENTS**

	ORIGINAL CIRCUIT VOLTS, DC	LM317 VOLTS, DC
Initial	12.88	13.2023
After 3 hours	13.18	13.2112
Total drift	0.3	0.0089

**TABLE 2**  
**POSITIVE SUPPLY, LINE REGULATION MEASUREMENTS**

LINE VOLTAGE VOLTS, AC	ORIGINAL CIRCUIT VOLTS, DC	LM317 VOLTS, DC
105	12.80	13.1959
120	13.09	13.2009
130	13.12	13.2059
Regulation	0.32	0.010

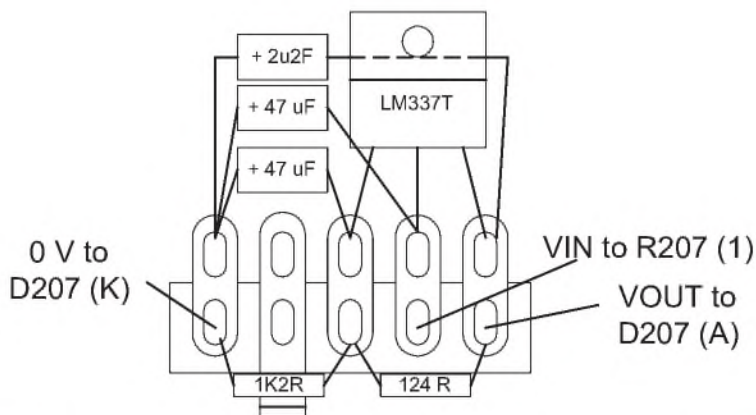


FIGURE 4: A guide for parts placement.

A-2137-4

## POWER-SUPPLY MODIFICATIONS

Safety first. DANGER! High voltage.

The area you will be working on is near the supply line power connections at either 120V or 240V AC. Do not work alone with high voltage present. When taking measurements always unplug, connect your test equipment, plug in, measure, and then unplug.

To proceed, unplug the unit and remove the top cover. Remove the two front-most back panel mounting screws and loosen the rear ones so you can fold back the rear panel. This way you can access the circuits, but the rear

panel stays attached and the wires will not be strained and break.

If your tuner's power supply is working, connect your voltmeter to the positive supply, plug in, and turn on. Measure the supply voltage after about 20

minutes warm-up and record. The value should be about 13.2V to 13.6V. Unplug and repeat for the negative supply. Record the negative supply value.

Do not be tempted to raise the supply

**TABLE 4**  
**NEGATIVE SUPPLY DRIFT**  
**MEASUREMENTS**

	ORIGINAL CIRCUIT VOLTS, DC	LM337 VOLTS, DC
Initial	NA	-13.2147
After 3 hours	NA	-13.2183
Total drift	NA	0.0036

**TABLE 5**  
**NEGATIVE SUPPLY, LINE**  
**REGULATION MEASUREMENTS**

LINE VOLTAGE VOLTS, AC	ORIGINAL CIRCUIT VOLTS, DC	LM337 VOLTS, DC
105	-13.13	-13.2156
120	-13.33	-13.2174
130	-13.44	-13.2187
Regulation	0.31	0.0031

## FM-5 FIX

While researching for this project, I read the initial FM-5 test reports from both *Popular Electronics* and *High Fidelity* magazines, reprinted by Dynaco. I noticed that the frequency-response graph showed a noticeable amplitude drop at the low end, -3dB at 30Hz or 40Hz relative to the 1kHz level. I decided to investigate.

The measurements I made confirmed the drop at 30Hz. Possible culprits are C219, C220, C229, C235, C225, and C231. I bypassed each of these with a capacitor ten times larger in value and measured. I found no measurable improvements.

Then I noticed C226 and C232. Computations show these to be the real source for the drop. I paralleled each with a 47 $\mu$ F 25V aluminum electrolytic capacitor and measured. The 30Hz drop was gone.

Figure 5 shows the simulation results of the amplifier circuit with different values for capacitor C226. The values used are 5 $\mu$ F (bottom left curve) and 47 $\mu$ F (top left curve). The PC-25 and PC-26 assemblies used in the later version FM-5 and the AF-6 have a different circuit and, as far as I can tell, do not suffer from this low-frequency drop.

Some will say that FM regulations limit the low end to 50Hz, but I suspect some stations are able to provide better low-frequency response than this.

To modify, unplug the tuner, locate C226 and C232. Connect the new 47 $\mu$ F in parallel observing proper polarity. Do not go above 47 $\mu$ F in value for the added capacitors. I do not know whether there is noise below 20Hz in this tuner, and I would not like to find out.

Figures 5 and 6 show simulated and measured low-frequency response, respectively. Distortion at 1V output is about 0.01% at 1kHz.

I reassembled the unit, and it works much better. Improvements are like onions, one layer at a time.

# Alpha Transmission Lines

This author challenges some of the mystery and myth by using TSPs in transmission-line design. **By Rick Schultz**

**Q**uarter-wave loudspeaker designs are mystical and mythical creations from the ancient past of loudspeaker design. They go back at least to Voigt's tubes (1934) and Olney's Acoustic Labyrinth (1936), about ten years after the invention of voice-coil drivers. Much later (1965), Bailey stuffed the entire pipe and called it a transmission-line.

Over the years, some people have built successful quarter-wave systems, but many more have failed. It is now possible to build a reliable  $\alpha$ -transmission line derived from any driver's Thiele/Small parameters (TSPs). To get past the myths and mysticism, let's

look outside the lines.

This design system takes some mystery out of transmission line (TL) construction. Later, I will cover how transmission line myth has hampered past designs. Even with this design system, the art of speaker building remains. You may decide to add or remove some stuffing as you listen to your  $\alpha$ -TL. You may choose to build a longer or shorter  $\alpha$ -TL for comparison.

## TL DEFINED

A quarter-wave loudspeaker is a broad group of designs that rely on pipe resonance frequency to assist the driver's output. For example, when you blow across the top of an empty bottle, the bottle hums. If the bottle is partly filled, the hum sounds different.

The common element of quarter-wave design is a long narrow pipe, which is closed at one end and has an opening at the opposite end, just like the bottle. A driver is placed at or near the closed end. Most are stuffed with loose fibers.

Pipes and bottles with one end closed have unique resonant properties. An unstuffed pipe resonates at a frequency directly related to pipe length. A pipe of a certain length is often referred to by its quarter-wave frequency. For convenience, I label the pipe frequency  $f\theta$ . This resonance frequency is at the speed of sound divided by four times the length. I write

this as  $f\theta = c/4l = 13560/(4 \times \text{inches})$ .

Simply, if a closed pipe is 100" long, its first resonance occurs at  $13560/(4 \times 100) = 34\text{Hz}$ . Interestingly, a 34Hz sound has the wavelength of 400". The 100" pipe is one-quarter of the 34Hz wavelength. Hence the name quarter-wave loudspeaker. (See the sidebar for more.)

## TL DESIGN


This article focuses on transmission line design (*Fig. 1*). TLs are special quarter-wave systems. Specific TL properties are:

- Driver attached to the closed end of the pipe
- Opposite end of the pipe is completely open
- Internal stuffing fills the entire length
- Pipe is straight and not tapered
- Q-neutralized impedance curve
- Critically damped, transient perfect driver response

In an  $\alpha$ -TL, the driver is critically damped every time. I have run many simulations, and driver rolloff is usually near 10dB per octave. Group delay is consistently quick and smooth. Traditional TLs perform very much like a  $Q_B = 0.5$  acoustic suspension sealed box. Shorter  $\alpha$ -TLs are also critically damped with great group delay, but offer additional low-frequency output.  $\alpha$ -TLs are just as easy to build as a sealed box.

Here are the steps to design an  $\alpha$ -TL for your driver.

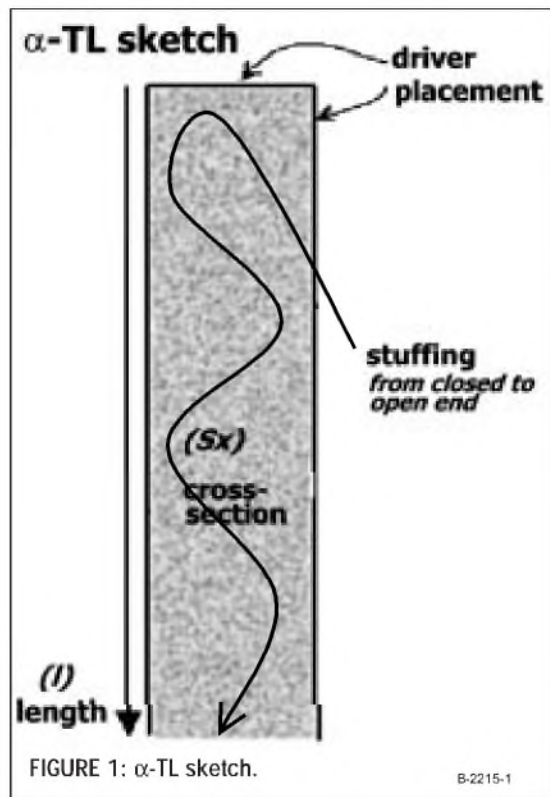1. Choose the pipe frequency  $f\theta$  (between  $f_G$  and two times  $f_G$ ).
2. Decide whether you will use fiberglass stuffing, polyester, or AcoustaStuf.
3. Refer to *Fig. 2* or *Fig. 3* to read pipe length from the curve marked "length inches" line and left axis.



4. Refer to *Fig. 2* or *Fig. 3* to read stuffing density from the stuffing density line and right axis.
5. Refer to *Fig. 4* or *Fig. 5* to read the value of  $Z$ , at the same  $f\theta$  used in steps 3 and 4.
6. Calculate  $\alpha$  equals  $\sqrt{1 + (f\theta/f_S Q_{TS})}$ . Be careful to take the square root.
7. Cross-section area ( $S_x$ ) equals  $Z \times f_S \times f\theta \times V_{AS} / (10,000 \times \alpha)$ .  $V_{AS}$  must be in cubic inches.
8. Material needed equals length times cross-section times density.

Start by reviewing TSPs of the driver—any driver works. Important TSPs in this design system are resonance frequency ( $f_S$ ), quality ratio ( $Q_{TS}$ ), and equivalent volume ( $V_{AS}$ ). One of my

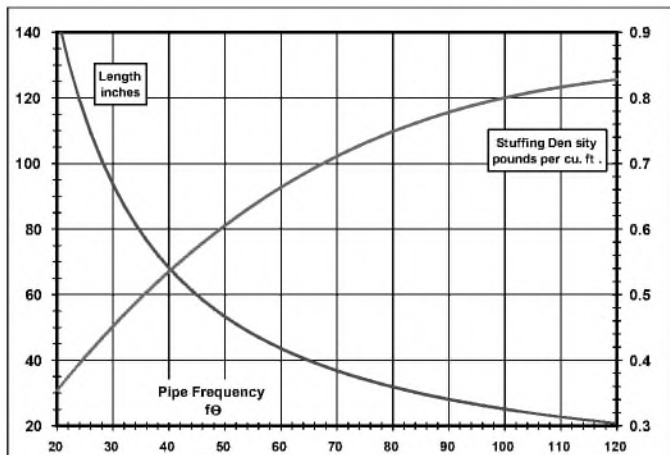


FIGURE 2:  $\alpha$ -transmission line length and stuffing density—fiberglass. After you decide which pipe frequency  $f\theta$  you want to use for your project, use the length line to read the proper length. The length is in inches on the left axis. At the same  $f\theta$ , read the fiberglass stuffing density and the recommended stuffing amount on the right axis. Stuffing is given in pounds per cubic foot. To convert to metric units: inches divided by 39.35 equals meters. Pounds per cubic foot times 16 equals grams per liter.

B-2215-2

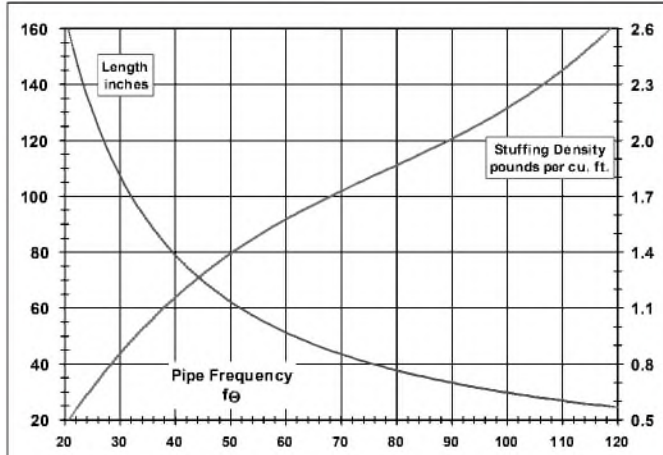


FIGURE 3:  $\alpha$ -transmission line length and stuffing density—polyester, cotton, AcoustaStuf. After you decide which pipe frequency  $f\theta$  you want to use for your project, use the length line to read the proper length. The length is in inches on the left axis. At the same  $f\theta$ , read the fiberglass stuffing density and the recommended stuffing amount on the right axis. Stuffing is given in pounds per cubic foot. To convert to metric units: inches divided by 39.35 equals meters. Pounds per cubic foot times 16 equals grams per liter.

B-2215-3

Origin Live Recreating the Original Sound
www.originlive.com



**KIT TURNTABLES**

"...this vinyl front end had my jaw dropping...it sounds like the door with the wobble and transparency of the music it was making... Overall a deeply impressive deal...without value for money... component quality is superb and the build process is a doozy."  
Hi-Fi World

"One of the most enjoyable and musically involving turntables I have ever heard regardless of make or reputation."  
Audiophile

Now you can own a professionally built, high performance turntable at a fraction of the normal cost. All DL turntable kits are supplied in 2 different specifications:

A Standard Kit of Parts to enable you to build your own plinth at **\$395**

-The Complete Non-suspended Standard Kit offered with a pre-finished & finished plinth at **\$465**

-The Complete Ultra Kit comes in two options. The Ultra Kit Classic offering a truly high end suspended sub-chassis turntable with beautifully finished finished solid wood plinth. The Ultra Kit Modern offers the performance of the Ultra Kit Classic combined with the modern day skeletal styling.

Both options available at **\$715**



**TURBOCHARGING YOUR REGA ARM**

"Wasting less than total dynamic"  
Hi-Fi World

If you are the proud owner of any Rega tonearm, you are now in the enviable position to transform its performance into the league of super arms with our modifications. The DL structural modification at \$105 will enable your Rega to perform at a level exceeding that of arms costing over \$1500!! High performance rewinding with high grade Itz wire is also offered at an additional \$95 and external rewinding is \$95 further increasing the performance.

"I have to say the Rega modifications turn this humble arm into a real quiet killer. Gone is the rather grey, sterile sound of the cooking Rega. Instead, tonal colour is fresh, dynamics have great speed and impact, and the sound stage is huge."  
Hi-Fi World on structural modification

With Hi-Fi gave this modification 3/3

Structural Modification - **\$105**  
Internal Rewinding - **\$95**  
External Rewinding - **\$95**

For arm modifications we normally return your arm in 2 - 3 days



**UNIVERSAL TURNTABLE MOTOR KIT**

"It's value is nothing short of tremendous."  
Listener Magazine

"The single most important upgrade you can ever make to any record deck concerns the motor drive...nothing can prepare you for the shock of yung DC. In a word, gabsmacking."  
Cassman (Sound Magazine)

"...if you are thinking of upgrading your system... the DL DC Motor Kit should be high on your list for consideration."  
DJ Radio

Wherever your current turntable, the results in upgrading to our DC motor & PS unit are simply astounding. Designed as a drop in replacement for almost all turntables, the DL upgrade kit offers vast improvements to all versions of Linn, as well as: Rega, Systemdeck, Roksan, Rock, Grade, Michale, VPI, Clearaudio, Acoustic Signature, etc. The kit consists of a high grade DC motor, aluminium electronic control box and offboard power supply. All this provides an extremely cost effective route to truly high-end audio and is significantly superior in performance to PS upgrades at four times the price.

DL Power Supply & Motor Kit - **\$425**

Origin Live, Unit 5, 362b Spring Road, Sholing, Southampton, SO19 2PB, UK  
Tel/Fax: +44 02380 578877 www.originlive.com email: originlive@originlive.com

personal favorites is Jordan's JX92S (about \$120). From Jordan's website at <http://www.ejjordan.co.uk/92S.html>,  $f_S$  is 45,  $Q_{TS}$  is 0.40, and  $V_{AS}$  is 15.28 ltr.

Notice whether  $V_{AS}$  is measured in liters (l), in cubic feet (ft<sup>3</sup>), or in cubic inches (in<sup>3</sup>).  $V_{AS}$  must be in in<sup>3</sup> to get proper results in my equation. If  $V_{AS}$  is in liters, multiply by 61.02 to convert to in<sup>3</sup>. If  $V_{AS}$  is in cubic feet, multiply by 1728 to get in<sup>3</sup>. For this driver,  $V_{AS}$  is 932 in<sup>3</sup>.

Going through the steps:

1. I choose to set pipe  $f\Theta = 80$ .

2. I will use fiberglass stuffing. I prefer the size and sound of fiberglass pipes, but polyester or AcoustaStuf is much easier to work with. I need to use *Figs. 2* and *4* for the next steps.

3. Referring to *Fig. 2*, my pipe must be 32".

4. Refer to *Fig. 2*; the recommended stuffing density is at least 0.75 lb per cubic foot.

5. Refer to *Fig. 4*; the value of  $Z$  at 80 is 0.34.

6.  $\alpha$  equals  $\sqrt{1 + (80/(45 \times 0.40))} = \sqrt{5.44} = 2.33$ .

7. Cross-section area ( $S_x$ ) =  $0.34 \times 45 \times$

$80 \times 932 / (10,000 \times 2.33) = 49 \text{ in}^2$ .

8. Material =  $32 \times 49 / 1728 \times 0.75 = 0.68 \text{ lb}$  or 11 oz. I need to divide by 1728 to convert in<sup>3</sup> to ft<sup>3</sup>.

About 32" is a very reasonable speaker height. If the  $f\Theta$  you want to use requires a long pipe, there is more to follow about shorter TLs. The cross-section of this pipe is about 49 in<sup>2</sup>. Cross-section shape of your TL is up to you. For the JX92S, cross-section could be a 7" square, an 8" diameter circle, or a 9 × 5½" "golden ratio" rectangle.

Although you may consider this Jor-

## QUARTER-WAVE LOUSPEAKERS

Quarter-wave systems are a group of loudspeakers that rely upon the resonance of a pipe. The fundamental resonance of a quarter-wave pipe is based on the length of the pipe. I refer to this resonance frequency as  $f\Theta$ .

The closed pipe frequency is expressed mathematically as  $f\Theta = c / (4 \times \text{length})$ , where  $c$  is the speed of sound. This is the same equation used to calculate one-quarter wavelength of a certain frequency. If length is in meters, speed of sound is 342m/s. If length is in inches, speed of sound is 13560 inches/sec. A pipe 42" long resonates at 80Hz, the fundamental.


Unfortunately, bare pipes also resonate at odd multiples of  $f\Theta$  (three times  $f\Theta$ , five times  $f\Theta$ , and so on, which I refer to as  $3\Theta$ ,  $5\Theta$ ,  $7\Theta$ , . . .) The 80Hz pipe will also resonate at 240Hz, 400Hz, 560Hz . . . the harmonics. These extra harmonics are unpleasant and destroy the valuable sounds a loudspeaker is meant to deliver. Quarter-wave systems rely on stuffing to control unwanted resonances at  $3\Theta$ ,  $5\Theta$ ,  $7\Theta$ , and beyond.

**Tapered Quarter-Wave Tube (TQWT)**—The first quarter-wave system published was the Voigt (pronounced vote) Patent 447,749 submitted Oct. 17, 1934. In it he lays claim to a wide variety of quarter-wave schemes. However, nowhere does he mention fibrous stuffing. Without it, his pipes undoubtedly produce a series of unpleasant harmonics. His tapered design (*Fig. 3*) and folded tapered design (*Fig. 4*) have an ongoing cult-like following. Today, stuffing is always used in the tapered pipes.

Voigt describes his pipes as "closed at one end and excited by means of a loudspeaker diaphragm . . . [the] length just under one quarter of the lowest frequency at which efficient working is desired, the diameter being about 1/3 or 1/4 the length, and the tube being closed at the one end." (Paul Gustav Adolphus Helmuth Voigt, Patent Specification 447,749, Application date: Oct 17, 1934.) His quarter-wave pipes place the driver on the closed end or on a side immediately adjacent to the closed end. He points out "in practice it is desirable to taper the bass chamber slightly . . ." TQWT is commonly referred to as the "Voigt pipe."

**Acoustic Labyrinth**—"It consists essentially of an absorbent walled conduit having one end coupled tightly to the back of the loudspeaker cone and the other end open. This conduit is in effect folded within the interior of the cabinet."<sup>3</sup> The photo accompanying Olney's article shows a pipe folded into three sections within a furniture-styled cabinet of that time. He places the driver at the closed end and the open end is near the floor.

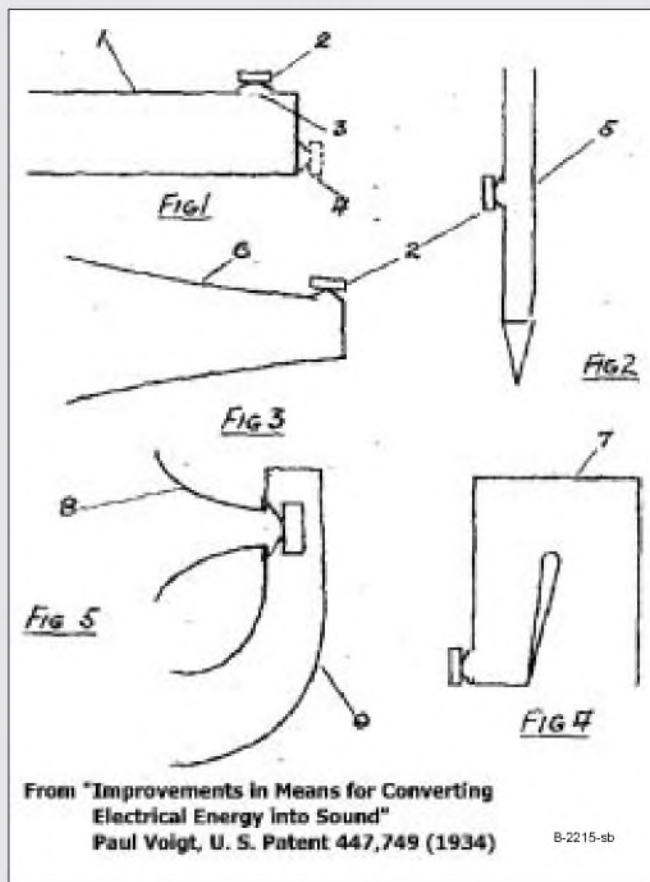Although no dimensions are given, the pipe appears to be several feet long and perhaps a half-foot square in cross-section. One side of the pipe is lined with thick felt, perhaps 2" or 3" thick.



From "Improvements in Means for Converting Electrical Energy into Sound" Paul Voigt, U. S. Patent 447,749 (1934)

B-2215-sb

"However, by lining the tube with material whose sound absorption rises suitably with frequency, we can suppress entirely these higher resonances . . ." Just two years after Voigt's pipes, Olney understood the importance of absorbent lining to suppress the  $3\Theta$ ,  $5\Theta$ , and other harmonics.

**Transmission Line**—A long pipe with parallel sides, stuffed the entire length. Bailey writes more about the transmission line in 1972<sup>4</sup>, "Radiation from the back of the driver cone flows down a pipe filled with a low-density sound-absorbing material. Fibrous absorbents such as loose wool, cotton wool, and kapok can be used." He also notes "[t]he effect of wool filling in the pipe is to slow down the wave relative to its velocity in free air." Stuffing not only attenuates the rear wave but also slows the speed of sound within the tangle.

dan JX92S example a large box, the amount of room it takes up on your floor is not that big, just 7 × 7" plus the width of your wood. α-TLs have a very reasonable "footprint" compared to a corresponding sealed box. Going

through the eight steps has given three critical bits of information: length, cross-section, and stuffing amount. Now you can build the α-TL. The sidebar describes construction. See Fig. 6 for results of this 80Hz α-TL.

Since this is your first view of an α-TL, I need to point out some features in Fig. 6. Driver rolloff is near 9dB per octave. I have run many simulations, and the α-TL driver is critically damped every time. Though not on the graph,

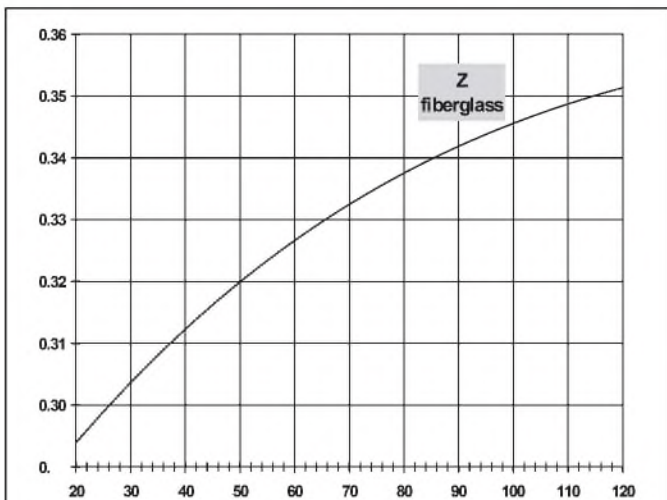


FIGURE 4: α-transmission line Z value—fiberglass. The Z value is needed to determine the cross-section area. Using the same pipe frequency, read the Z value from the curve. Use Z in this equation to set proper cross-section:  $S_x$  equals  $Z \times f_s \times f\theta \times V_{AS} / (10,000 \times \alpha)$ , where  $\alpha$  equals  $\sqrt{1 + (f\theta/f_s \times Q_{TS})}$ . The shape of the cross-section is up to you.

B-2215-4

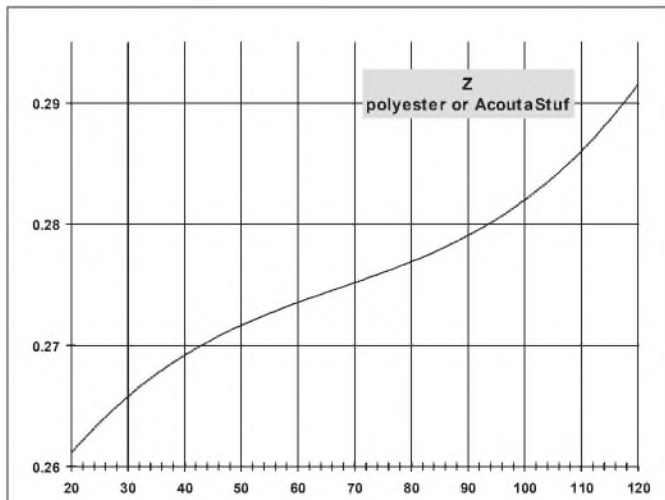


FIGURE 5: α-transmission line Z value—polyester, cotton, AcoustaStuf. The Z value is needed to determine the cross-section area. Using the same pipe frequency, read the Z value from the curve. Use Z in this equation to set proper cross-section:  $S_x$  equals  $Z \times f_s \times f\theta \times V_{AS} / (10,000 \times \alpha)$ , where  $\alpha$  equals  $\sqrt{1 + (f\theta/f_s \times Q_{TS})}$ . The shape of the cross-section is up to you.

B-2215-5

# Hi-Fi Do Inc.

## BUY & SELL

OVER A  
MILLION  
HITS/WEEK

USED AMPLIFIERS, SPEAKERS, PLAYERS, BOOKS, ACCESSORIES etc.

[www.hifido.co.jp](http://www.hifido.co.jp)

OSAKA(Overseas Dept.): 4-6-10 NIPPONBASHI NANIWA-KU OSAKA JAPAN  
TOKYO: TOKUHARA BLD 5-5-7 SOTOKANDA CHIYODA-KU TOKYO JAPAN  
NAGOYA: 3-11-30 OOSU NAKA-KU NAGOYA JAPAN

PHONE 816-4396-7611 FAX 816-4396-7621

Get Hi-Fi Do's Free Online Newsletter >>> [www.hifido.co.jp/logtop.html](http://www.hifido.co.jp/logtop.html)

group delay is consistently quick and smooth, normally between 4 and 6ms.

Notice how flat the impedance curve is in Fig. 6.  $\alpha$ -TL impedance curves are noticeably flatter than the driver's free-air curve. Impedance curves of  $\alpha$ -TLs are much flatter than the curve of the driver in a sealed box or bass reflex. If you like tube amps, this is an attractive property of  $\alpha$ -TLs.

Lastly, output from the opening adds about 3dB to the low-frequency response of the driver. The low-frequency cutoff of the driver alone is at 93Hz. The opening output extends cutoff to 66Hz, one-half octave.

### TRADITIONAL TL

Reviewing TL properties: they have straight sides; they are not tapered. The driver is always at the closed end of a TL. At the open end, the entire cross-section is open. Stuffing is uniformly packed along the entire length of the pipe, from closed end right to the open end. Traditional TLs have one additional, unique property:

- Pipe frequency  $f\Theta$  is set near  $f_S$

Let's examine a traditional TL, using the same JX92S for this example. The only prerequisite for making a traditional TL is setting  $f\Theta$  equal to  $f_S$ . For the JX92S,  $f\Theta = f_S = 45$ . Using fiberglass stuffing as before, Fig. 2 shows the tra-

ditional JX92S TL is 60" tall, while proper packing is just 0.57 #/ft<sup>3</sup>. Doing the rest of the math, cross-section is 17 in<sup>2</sup>, and 5.4 oz of fiberglass is needed to stuff the pipe.

Figure 7 shows the performance for this pipe. Notice the small output from the opening (dashed line). At 200Hz, opening sound is -21dB compared to the driver. That is 1/128 as quiet as the driver—very quiet. These traditional TLs attenuate the opening very effectively. They do not support and augment the driver. This confronts a TL myth. Lighter stuffing alone does little to improve bass response of the system.

As one other example of this, see Fig. 8 of a traditional TL using the Peerless 2732, which is critically damped. At 200Hz, opening output is -26dB, or 1/400 driver output. Also notice how flat the impedance curve is for this traditional TL. Unfortunately, there is little

low frequency support even though  $f\Theta = f_S = 34$ .

### STUFFING

Attenuation of the pipe depends on 1) stuffing density, 2) material, and 3) pipe length—not very profound! Tight packing means more fibers are encountered by the resonant sound waves. Longer pipes mean more fibers are encountered. Fibers of the material have their own unique diameter. Fiberglass is much finer than polyester or AcoustaStuf, has more fibers per unit volume, and is much more effective at suppressing pipe output.

In the first draft of this article, I presumed there was no standard density of stuffing. In his landmark article<sup>1</sup>, George Augspurger provided recommended stuffing amounts appropriate for special TL geometries "but not for simple, straight pipes."

TABLE 1

Using the Jordan JX92S, pipe resonance may be set at any frequency. This table shows cabinet size and stuffing for three resonances and two materials. Results for these values are compared in Figs. 9 and 11, Figs. 10 and 12.

JORDAN JX92S F $\Theta$ VARIATIONS	LENGTH	DENSITY #/FT <sup>3</sup>	CROSS-SECTION	OUNCES OF MATERIAL
<b>FIBERGLASS STUFFING</b>				
45Hz ( $f_S$ )	60 in	0.57	32 in <sup>2</sup>	10.2 oz
63Hz (1.4 $f_S$ )	41 in	0.68	41 in <sup>2</sup>	10.7 oz
90Hz (2 $f_S$ )	28 in	0.78	53 in <sup>2</sup>	10.8 oz
<b>POLYESTER STUFFING</b>				
45Hz ( $f_S$ )	70 in	1.28	27 in <sup>2</sup>	23 oz
63Hz (1.4 $f_S$ )	49 in	1.63	35 in <sup>2</sup>	26 oz
90Hz (2 $f_S$ )	34 in	2.01	45 in <sup>2</sup>	28 oz

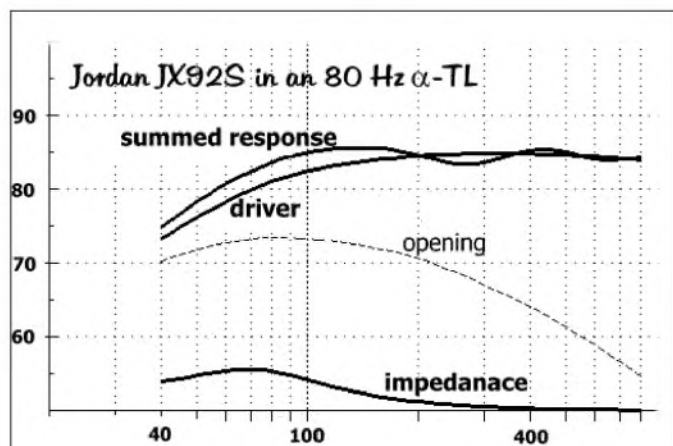


FIGURE 6: Response and impedance curves of the Jordan JX92S in an  $\alpha$ -TL. This pipe is designed at 80Hz. Notice the broad flat impedance curve centered at about 70Hz. The sound produced by the driver is the bold line. As you follow it from midrange down to low frequencies, the slope is -6dB per octave. This indicates critical damping. Critically damped systems have excellent transient response. This is described as "clean" or "tight" sound. See the text for a brief discussion of the "summed response" curve. B-2215-6

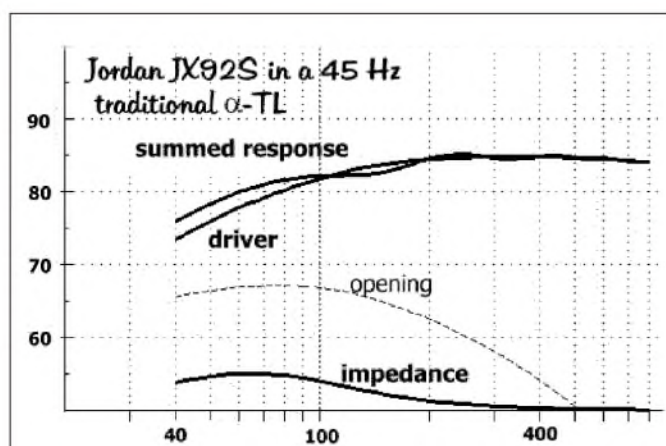


FIGURE 7: Traditional  $\alpha$ -TL response. The pipe is constructed so pipe resonance is the same as the JX92S resonance 45Hz and stuffed with fiberglass. Compared to Fig. 6, the impedance curve has a similar shape but is centered at 64Hz. Driver response is identical. However, the longer pipe with lighter stuffing has less opening output than the 80Hz pipe in Fig. 6. In the past, it was assumed a longer pipe produces more bass. In fact, longer pipes are quieter at low frequency than short pipes. B-2215-7



As I reworked this piece, I looked at the right amount of stuffing for a given straight pipe frequency. It does not matter what driver  $f_s$ ,  $Q_{TS}$ , or  $V_{AS}$  is. It does not matter how wide or slim the pipe is. The density of stuffing depends only upon  $f\Theta$ . When determining the right

density, I looked for about a 1.0dB dip at the  $3\Theta$  resonance and less than 0.5 lift beyond  $3\Theta$ . As I re-read his article, I realized Augspurger used this same standard.

Voice-coil drivers show more variation than this. When cabinet output meets this standard, the  $\alpha$ -TL cabinet of

fers less coloration than the driver itself. That is quite a bold statement. My point is the driver is rarely uniformly flat through midrange.  $\alpha$ -TL cabinets show less variation than the driver itself, but this is not the first time this claim has been made.

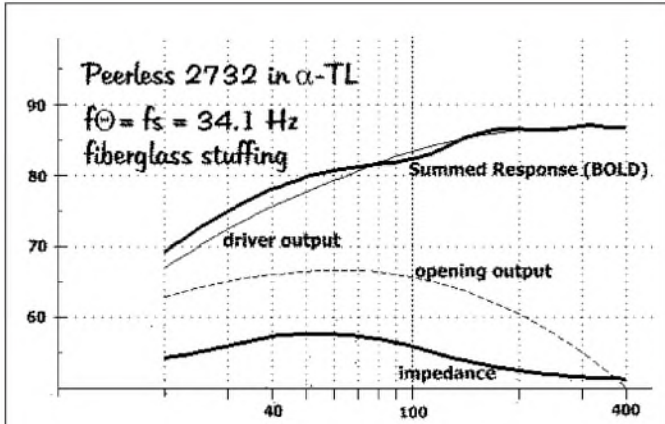


FIGURE 8: Traditional  $\alpha$ -TL using the Peerless 2732. This graph is another example of how quiet long pipes are. The pipe frequency is the same as driver resonance, which is 34Hz. Summed response quiets noticeably below 125Hz. The shelving of response between 50 and 110 is largely due to the  $3\Theta$  resonance. When  $3\Theta$  resonance is better controlled, the shelf would be smoothed out. (Thanks to Peerless, who provided these drivers for an earlier, failed project.)

B-2215-8

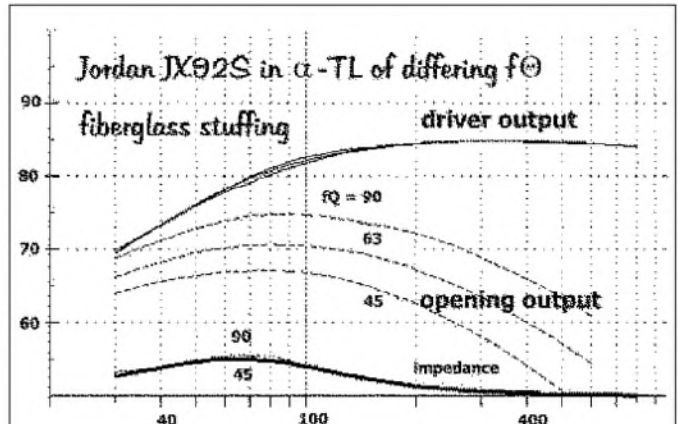


FIGURE 9:  $\alpha$ -TL summed pipe responses—fiberglass. The fine lines on this graph are the combined output of the driver and opening seen in Fig. 11. This sums the amplitude and phase of the sounds and assumes the driver and opening are the same distance from the ear. The flattest response comes from the 63Hz pipe. High and low spots in the summed curves are due to phase differences between the driver and opening.

B-2215-9

**the authority on hi-fi DIY**

Subscribe to **eConnexion**, a monthly email newsletter featuring the latest happenings at pcX - including great specials, clearance items & new product introductions.

Also our online catalog is expanding quickly.

**PARTS CONNEXION**

**1-866-681-9602 www.partsconneXion.com**  
 Tel: 905-681-9602 Fax: 905-631-5777 info@partsconneXion.com

Visa, MasterCard, American Express (+2%), Paypal (+2%), BidPay, Money Order/Bank Draft/Cashier's Check, Personal Check (after clearance)

**2885 Sherwood Heights Drive, Unit #72, Oakville, Ontario, CANADA L6J 7H1**

IMPORTANT NOTE: No "on-site/walk-in" business at this time. However, pick-up orders can be arranged by appointment only. Call for details.

"Listening tests proved that the [TL] cabinet had a 'cleaner' sound than the bass reflex type, the effect of the line being very noticeable in its lack of coloration on speech. Transient response was definitely better on the line speaker, the sound being more 'tight' and natural. "The final subjective tests were very good. The sound quality is effortless

## CONSTRUCTION

The first part of this Jordan JX92S project involves cutting the sides. To keep this project simple, I built a square cross-section. Start with four boards 31 7/8" long (Photo 1). MDF is the best to work with. I used 3/4" material for most of my projects because it doesn't

split as easily and provides enough surface for adhesive. The inner dimension of the Jordan JX92S project is 7" square. I cut the boards a little wider than 7 3/4". This photo shows the driver opening layout.



PHOTO 1: All sides of this project are the same. Since the material is 3/4" thick, the side boards are just over 7 3/4". The driver needs an opening of radius 2 1/4".

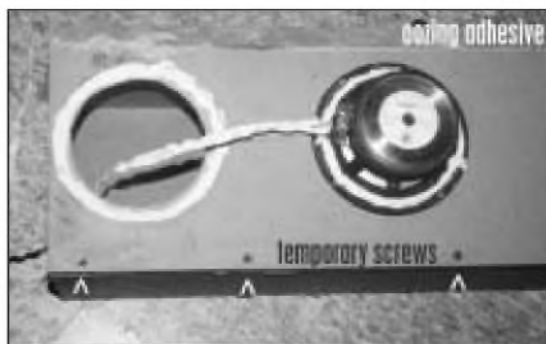


PHOTO 4: Assembled sides are held together with construction adhesive and temporary screws. The adhesive fills in gaps. The screws are removed the next day.



PHOTO 2: The chamfering bit used to widen the inside of the opening. Resting on the router is the flush trim bit used after assembly.

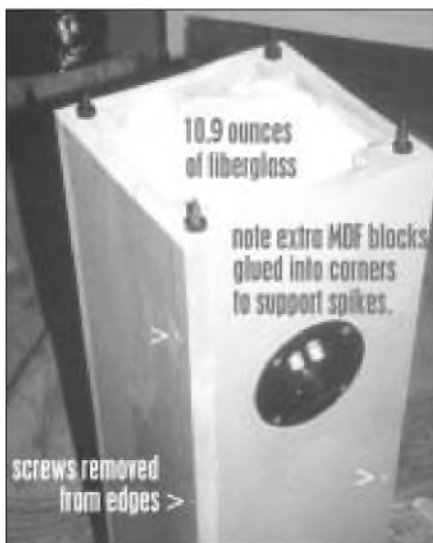


PHOTO 5: Bottom of the assembled cabinet. Extra blocks are added at the corners to receive the spikes. The round black object is the speaker wire d-cup.



PHOTO 3: The face board with opening cut out.



PHOTO 6: The finished  $\alpha$ -TL featuring Jordan's JX92S. Since I had wallpaper available, which matches the living room walls, I tried a different "finish."

Before assembling the sides, I cut the driver opening. It is 4½" diameter. I don't have a nice router jig, so I cut the opening free-hand. I used a plastic lid from a coffee can as my compass, which was very stable and made a perfect circle. I cut the hole using my saber saw, but I didn't get a perfect circle (Photo 2). If the driver doesn't fit, you can cut a little more from the hole. Often, I simply tilt the jig saw a little and just knock off the rim until it fits.

To me, the most important cabinet detail for smaller drivers is chamfering the rear of the hole. Chamfer is a 45° bevel cut. This is critical if you use thick material, which can obstruct airflow between the hole and basket, thus altering all the TSPs. Also, sound ricochets off a square-cut hole wall producing awful reflections back onto the cone.

The chamfering bit (Photo 3) allows free airflow from the rear of the driver and fewer reflection problems. Resting on the router is an edge trim bit (about \$18). It is used later to square off and straighten the cabinet edges. A carbide edge trim bit will last for a few projects.

The sides are butt-joined and held temporarily with drywall screws. I pre-drilled the face but not the side and applied a continuous bead of Liquid Nails construction adhesive to one board. When I drove the screw straight into the material, I noticed some splitting of the side. I needed to reset some screws so I drove them on an angle without a pilot hole. This produced much less splitting, so I plan to use this angling technique in the future.

I used the Liquid Nails to glue four ¾" × ¾" × 2½" blocks at the bottom inside corners. I ran some Latex caulk around the driver and the opening (Photo 4) and pressed the driver firmly into the caulk so it oozed out the front and rear. I installed four drywall

screws along each edge. I was careful so I didn't over tighten them and strip the MDF, and let the assembly cure overnight.

The next day I removed the screws. With a utility knife I trimmed away the cured adhesive and caulk (Photo 5). Because I cut the MDF a little wider than needed, I trimmed the long MDF edges with the bit shown in Photo 2. The edges were straight and sharp.

At the end near the driver, I lined the inside of the cabinet with fiberglass ceiling tile, which was very effective at reducing midrange and treble reflections. I installed 10.6 oz of fiberglass throughout the cabinet. I cut the top MDF a little big, not quite 8 in<sup>2</sup>, attaching it with Liquid Nails and pressing it into place. I didn't bother with screws. Later, I trimmed this with the router just as I did on the long edges. I installed four spikes at the bottom corners to keep the cabinet off the ground. These spikes were essential to detailed imaging.

I used a different cabinet covering on the project (Photo 6), having some wallpaper left over from our living room. My first attempt with this pre-pasted paper did not work. To wallpaper an MDF cabinet, first seal the wood with wallpaper primer (also called sizing). Apply wallpaper adhesive to the paper and the cabinet. Clay adhesive is the best. Place the paper centered on the front and wrap around both sides.

I pre-cut the driver hole in the wallpaper and I think that was a good idea. Wipe out air bubbles with a soft rag or brush. Apply pieces to the sides and wrap to the back. Trim the rear, top, and bottom with a razor-sharp tool. Lastly, apply the top piece and trim. Wallpaper is very forgiving and covers minor imperfections such as unfilled screw holes.

and natural. At first hearing the bass sounds deficient but extended tests show that this is not so, it is merely that one has been conditioned to hear resonant bass."<sup>2</sup>

I must caution that every driver has its own properties. Some are better than others in an α-TL. If you notice some irregularity in the midrange, simply install a little more stuffing. You can remove a bit of stuffing to see whether you can get a little more low end. α-TL construction is still an art. This α-TL design system gives you a very good head start on your project.

You are encouraged to vary the amount of stuffing until you attain the sound quality you prefer. Heavier stuffing brings the system closer to the  $Q_B = 0.5$  acoustic suspension. Packing lighter than my recommended density allows more reinforcement and cancellation, producing uneven response.

The curves in Figs. 9 and 10 are the sum of phase and amplitude of the driver and opening. The sum ignores floor lift, the 2-3dB additional amplitude, because the opening is at the floor. The model assumes driver and opening are equidistant from the ear. However, the driver is often placed near ear level while the opening is farther away at floor level. Room reflections and ceil-

ing height are ignored in the graphs.

For these reasons, I do not fully accept summed response above 120Hz.

The only way to tell whether your combination of stuffing material, density, length, and driver pleases you is to

## Accuracy, Stability, Repeatability

Will your microphones be accurate tomorrow?



Next Week? Next Year? After baking them in the car???

**ACO Pacific Microphones will!**

Manufactured to meet IEC, ANSI and ASA standards.  
Stainless and Titanium Diaphragms, Quartz insulators

Aged at 150°C.

Try that with a "calibrated" consumer electret mic!

**ACO Pacific, Inc.**

2604 Read Ave., Belmont, CA 94002

Tel: (650) 595-8588 FAX: (650) 591-2891 e-mail [acopac@acopacific.com](mailto:acopac@acopacific.com)

**ACOustics Begins With ACO™**

build an  $\alpha$ -TL and listen to one in your room. Give the system some time and add stuffing to suit your taste.

### f $\Theta$ —PIPE FREQUENCY

TL myth assumes you can lower system response by building a longer pipe; pushing f $\Theta$  lower must extend bass performance. This myth started 65 years ago when Voigt set “length just under one quarter of the lowest frequency at which efficient working is desired.” He does not relate quarter-wave pipe frequency to driver resonance. Instead, he related it to whatever frequency “is desired.”

Speaker builders have assumed just building a longer pipe will extend response. In fact, building a lower f $\Theta$  pipe just quiets it. Longer TLs perform much

worse than shorter TLs. The lower limit for pipe frequency should be f $\Theta$  equals f $_S$ . I recommend going no lower, any longer.

Shorter pipes produce +2 to +4dB additional bass through low frequency rolloff. This lift continues to near two times f $\Theta$ . Shorter  $\alpha$ -TL achieves results similar to Augspurger’s special geometries. As he comments on his geometries, he observes, “The efficiency matches that of an equivalent closed-box system; however, pipe output contributes 2–3dB in the low frequency range. . . . the net result is a corresponding increase in maximum output.”

Augspurger also says, “. . . In contrast to a basic cylindrical pipe, at

least four alternative geometries allow lighter damping, which results in higher efficiency.” In fact, straight pipes can perform nearly as well as his geometries. The secret is higher f $\Theta$  and tighter stuffing.

Let’s consider different pipe frequencies and their performance. I will use frequencies f $\Theta$  = f $_S$ , 1.4f $_S$ , and 2f $_S$  for contrast. Using the Jordan JX92S, the three pipe frequencies are 45, 63, and 90Hz. Table 1 contains the cabinet dimensions using fiberglass and polyester. Fiberglass results are in Figs. 11 and 9; polyester results are in Figs. 12 and 10.

In Figs. 11 and 12, driver response is

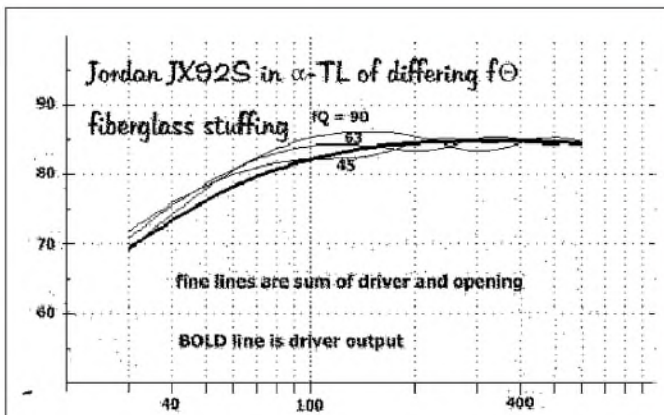


FIGURE 10:  $\alpha$ -TL summed pipe responses—polyester. The fine lines on this graph are the combined output of the driver and opening seen in Fig. 12. This sums the amplitude and phase of the sounds and assumes the driver and opening are the same distance from the ear. These summed responses are very similar to the fiberglass results in Fig. 9.

B-2215-10

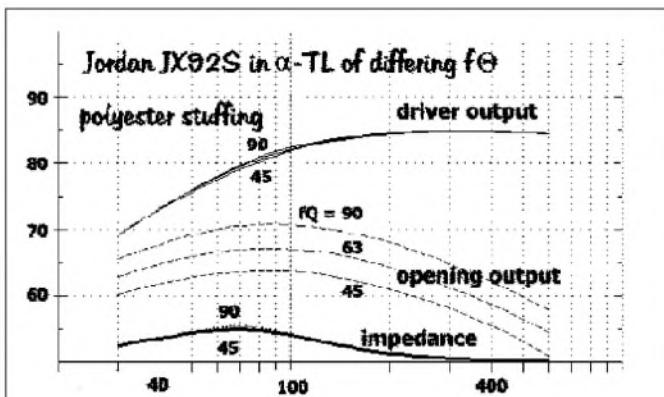


FIGURE 11: Comparison of three fiberglass stuffed  $\alpha$ -TLs at different pipe resonances. Impedance is the same for all three pipes, driver output is virtually identical. The only difference is opening output. The longer lower pipes are clearly quieter. I recommend building no lower, any longer.

B-2215-11

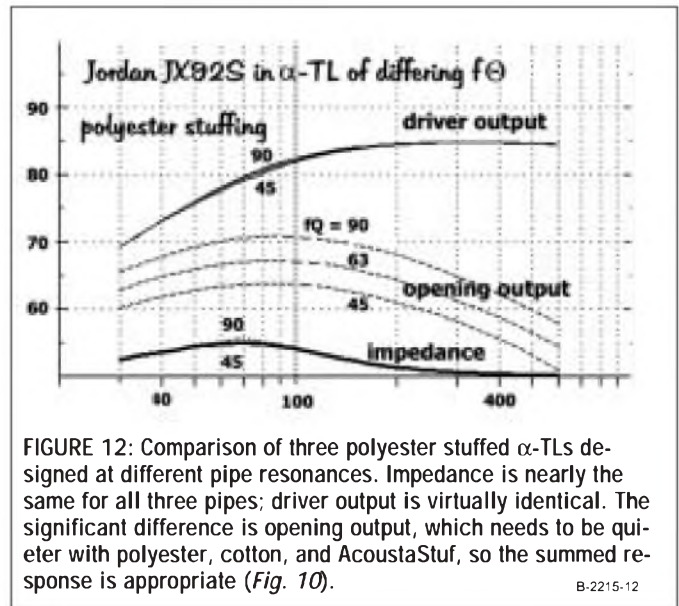


FIGURE 12: Comparison of three polyester stuffed  $\alpha$ -TLs designed at different pipe resonances. Impedance is nearly the same for all three pipes; driver output is virtually identical. The significant difference is opening output, which needs to be quieter with polyester, cotton, and AcoustaStuf, so the summed response is appropriate (Fig. 10).

B-2215-12

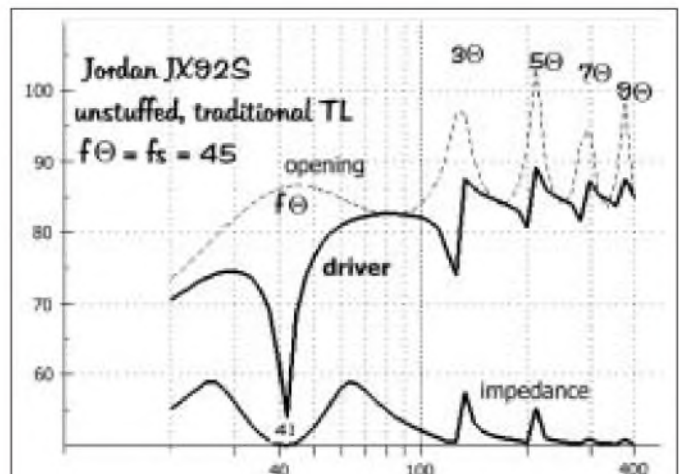


FIGURE 13: Unstuffed traditional  $\alpha$ -TL response. The Jordan JX92S in an empty 45Hz pipe shows typical results. Augspurger’s program makes numerous calculations and connects the points on the curves. The result is some clipping of the 3 $\Theta$  and 7 $\Theta$  harmonics. If this pipe was actually tested, the 3 $\Theta$  and 7 $\Theta$  peaks would be closer to the location of the labels. Notice the impedance anomalies at each harmonic. Also, opening resonance is at 45Hz but the driver is completely quiet, dead at 41Hz.

B-2215-13

virtually the same—critically damped. Impedance curves are quite flat and practically the same. The only noticeable difference is opening output. The shortest pipe gets closest to driver output. However, there can be a lot of lift into midrange. I recommend choosing  $f\theta$  to be 1.2 to 1.6 times driver  $f_S$ .

Since length, density, and stuffing vary, cutoff is difficult to predict accurately. Cutoff is at least as good as the  $Q_B = 0.5$  AS and may be as much as one-half octave lower, especially if  $f\theta$  is 1.2 to 1.6 times  $f_S$ . These pipes also avoid excessive midrange lift. Not bad considering the cabinet is smaller than a traditional TL.

### IMPEDANCE

Pipe frequency is the primary reason the impedance curve flattens. There is a down side. Unstuffed TLs do not resonate at only  $f\theta$ . They have acoustic and electric harmonics at odd multiples of  $f\theta$  at  $3\theta$ ,  $5\theta$ ,  $7\theta$ , and so on.

Figure 13 shows these ugly peaks for an un-stuffed traditional 45Hz pipe using the JX92S. These are unbearable and must be suppressed. The only solution is stuffing, which is vital to deaden acoustic and electric irregularities produced by pipe harmonics.

The basic impedance curve for the JX92S on a large flat board is curve A in Fig. 14. This curve is centered at 45Hz, so we say  $f_S = 45$ . The broadness of the curve determines  $Q_{TS}$ , which is 0.40 for this driver.

Next, look at curve C, which is very irregular. It is the curve of the JX92S in an unstuffed traditional TL of  $f\theta = f_S = 45$ . I set the cross-section based on my  $\alpha$ -TL model. But this curve is more regular than it seems.

One important detail to notice is the first two peaks. If you consider the first two peaks alone, the curve looks like an exquisitely tuned bass reflex design. Amplitude is the same for these two peaks. An improperly tuned pipe exhibits unbalanced peaks.

The next important observation is the location of the peaks at 27 and 64Hz. These are important because  $f_S = 45$  is very near the (geometric) center frequency of these two points; that is,  $\sqrt{(27 \times 64)} = 41$ . Unstuffed  $\alpha$ -TLs always display this centering. The center frequency is normally about 10% lower than  $f_S$ .

The third peak is near 135, the next near 225, another near 315, and again near 405. These impedance peaks represent the  $3\theta$ ,  $5\theta$ ,  $7\theta$ , and  $9\theta$  pipe harmonics. As these resonances quiet at higher frequencies, the impedance peaks flatten. Actual harmonics are normally just below the predicted harmonics.

Finally, curve B is for the traditional stuffed  $\alpha$ -TL. Notice the broad smooth curve. Although the  $\alpha$ -TL is tuned to 45Hz, the impedance peak is not at  $f\theta = f_S = 45$ . Stuffing deadens the first peak. Stuffing also deadens the pipe harmonics. The only remaining peak is at 64Hz, the same as the second unstuffed peak. Because the graph is on a logarithmic scale, this peak is only about 40% of the driver

on a board.

So, it is pipe frequency that damps driver resonance; then stuffing damps pipe resonances. Proper pipe length and stuffing produce a flat impedance curve, phase unity, excellent transient response, and quick, uniform group delay. As  $f\theta$  moves away from  $f_S$ , cross-section adjusts so  $Q_{TS}$  is nearly neutralized in all  $\alpha$ -TLs.

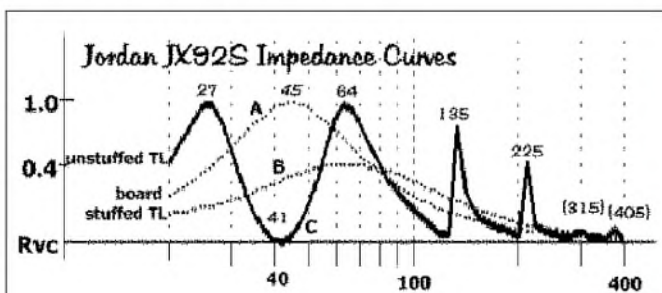



FIGURE 14: Comparison of unstuffed and stuffed traditional  $\alpha$ -TLs. Line A is the impedance of the JX92S on a flat board. Line B shows the driver in a stuffed traditional  $\alpha$ -TL. Line C is the wild impedance of an unstuffed pipe. Stuffing deadens all but one of the unstuffed peaks. The only remaining peak is located at the second unstuffed peak at 64Hz. Because the graph is on a logarithmic scale, this peak is only about 40% of the driver on a board. Figure 14 holds the key to improving the  $\alpha$ -TL. Low frequency response can be extended when the first and second peaks are developed and the third peak is subdued.

B-2215-14

From the developers of IMP and Liberty Audiosuite...
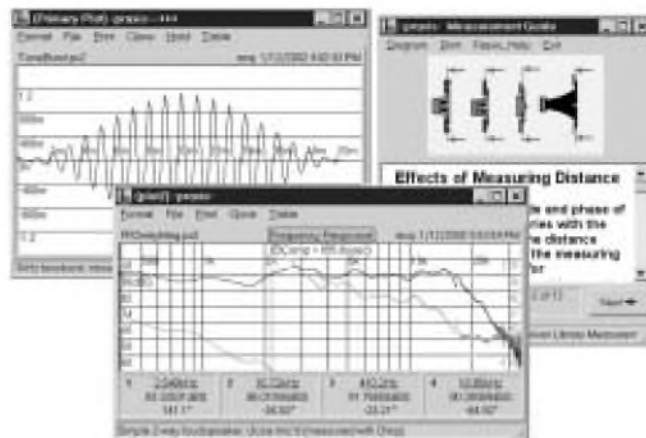
## -praxis-

Full Featured, customizable measurement system for loudspeakers, transducers, electronics, room acoustics, and vibrational systems.



Compatible with laptops and PCs and a wide variety of soundcards running under 32 bit Windows operating systems. Features built-in measurement guides for easy operation. Samples to 24-bit and 192kHz.

For more information please visit us at [www.libinst.com](http://www.libinst.com)

Liberty Instruments, Inc.  
P.O. Box 1454, West Chester, OH 45071 USA  
Phone/Fax 513-755-0252 [carolst@one.net](mailto:carolst@one.net)

## ALPHA . . .

Those of you interested in engineering loudspeakers may have noticed a loudspeaker mystery unveiled here. Speaker builders are accustomed to  $\alpha$  associated to acoustic suspension cabinet volume. In all quarter-wave systems,  $\alpha$  is length dependent. More accurately, it is dependent upon the  $f\theta:f_sQ_{TS}$  ratio. The  $\alpha$ -ratio was the ultimate mystery in TSP-based TL design.

Properly designed quarter-wave systems neutralize the driver resonant peak defined by  $f_s$  and  $Q_{TS}$ .  $\alpha$ -TLs compensate or flatten the driver's electrical resonance peak. When you look at the  $\alpha$  formula, note what happens when  $f\theta$  is set equal to  $f_s$ . Then  $\alpha = \sqrt{1 + (f_s/(f_sQ_{TS}))}$  or  $\sqrt{1 + (1/Q_{TS})}$ .  $\alpha$  is related to the inverse of  $Q_{TS}$ . This explains the flattened impedance curve at driver resonance.

Chat, browse, bid, buy, sell  
or simply click 'til it hurts.

www.AUDIOGON.com  
HIGH END AUDIO MARKETPLACE

To get the flattest possible impedance curve, simply set  $f\theta = f_s/Q_{TS}$ . This does not ensure extended low frequency; it only produces the flattest impedance. To get both the best response and impedance, select a driver whose  $Q_{TS}$  is between 0.5 and 1.0. Still, many people prefer the sound of low  $Q_{TS}$  drivers (below 0.4) in their TLs. This design works for all speakers no matter what  $Q_{TS}$  the driver has.

This article and design is subject to full copyright and patent protection. There is no restriction, of course, on private individuals making an  $\alpha$ -TL for their own pleasure. These are the (proprietary) mathematical equations for the curves on Figs. 2 and 4, Figs. 3 and 5. These equations are reliable for pipe  $f\theta$  up to 120Hz. Beyond that, other factors influence results.

$$L_f = 3816(f\theta^{-1.09})$$

$$D_f = 0.0000002 f\theta^3 - 0.00009f\theta^2 + 0.014f\theta + 0.11$$

$$Z_f = 0.00000008f\theta^3 - 0.00002f\theta^2 + 0.0023f\theta + 0.25$$

$$L_p = 4014(f\theta^{-1.06})$$

$$D_p = 0.000003f\theta^3 - 0.0007 f\theta^2 + 0.068f\theta -$$

0.64

$$Z_p = 0.00000005f\theta^3 - 0.000009f\theta^2 + 0.0008f\theta + 0.25$$

## . . . AND OMEGA

Mr. Augspurger provided the technical review of this article. I deeply appreciate his interest and support. He comments, "Four things I learned from reading the revised manuscript: (a) A simple quarter-wave damped pipe is as easy to build as a closed box, but can provide certain performance advantages. (b) With straight pipe geometry, enclosure volume may not be all that important . . . it doesn't make much difference whether the pipe is 8 in<sup>2</sup> or 10 in<sup>2</sup>. (c) The quarter-wave pipe frequency does not have to match the speaker's free-air resonance. For best performance, it should not. (d) To get more bass, make the pipe fatter, not longer. I agree with all four assertions." He also agrees with my assertion that there is a specific stuffing density dependent upon pipe  $f\theta$  and material only.

Impedance curves can be manipulated by cabinet modifications. The second peak is moved near  $f_s$  and the third

# Hi-Fi News Analogue Test LP—The Producer's Cut from Hi-Fi News

This audiophile-quality pressing of 180gm virgin vinyl features updated and expanded tracks from the original test LP (LP1 from 1996). It provides everything you need to get the best from your turntable, tonearm, and cartridge. The universal alignment protractor is included to allow set up of all sizes and types of arms to a high degree of accuracy. John Crabbe's article on arm/cartridge alignment and copious sleeve notes will provide extensive information for setting up and testing your LP turntable system. Sh. wt: 2 lbs.

LP2 .....\$42.95\*

\*Shipping and handling add \$7.00 US  
Canada add \$8.50, \$9.25 Other sur-  
face \$16.75 Other air.

To order call 1-888-924-9465  
or order on-line at [www.audioXpress.com](http://www.audioXpress.com)!

Old Colony Sound Laboratory, P.O. Box 876 Dept. X3, Peterborough, NH 03458-0876 USA • Toll-Free: 888-924-9465  
Phone: 603-924-9464 • Fax: 603-924-9467 • [www.audioXpress.com](http://www.audioXpress.com) • E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)

peak is deadened by the cabinet and not the stuffing. Simple modifications to  $\alpha$ -TL cabinet design and stuffing lead to a different TSP-based design—the  $\Omega$ -quarter wave reflex. ❖

### ACKNOWLEDGMENTS

I am deeply indebted to G. L. Augspurger, who generously provided his software. Using it has allowed great progress in pursuing my hobby. The graphs in this article are produced by his program.

For more on quarter-wave design, see the best QW site on the planet at <http://www.t-linespeakers.org/index.html>. Dave Dlugos runs the site and has been very supportive of my design ideas. This article will be posted there after publication.


Martin J. King has been very encouraging as we corresponded about stuffing, TLs, TQWTs, and exolinear design. Visit his informative site at <http://www.quarter-wave.com>

### REFERENCES

1. G. L. Augspurger, "Transmission Lines Update, Part 3: Pipe Geometry and Optimized Alignments," *SB* 4/00.
2. Dr. A. R. Bailey, "A Non-resonant Loudspeaker Enclosure Design," *Wireless World*, October 1965.
3. Benjamin Olney, "The Acoustic Labyrinth," *Electronics*, April 1937.
4. A. R. Bailey, "The Transmission-line Loudspeaker Enclosure," *Wireless World*, May 1972.
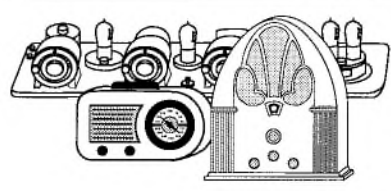
## FREE SAMPLE

IF YOU BUY,  
SELL, OR COLLECT  
OLD RADIOS, YOU NEED...



# ANTIQUE RADIO CLASSIFIED

Antique Radio's Largest Monthly Magazine  
100 Page Issues!

Classifieds - Ads for Parts & Services - Articles  
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,  
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...  
*Free 20-word ad each month for subscribers.*

Subscriptions: **\$19.95 for 6-month trial.**  
**\$39.49 for 1 year (\$57.95 for 1st Class Mail).**  
*Call or write for foreign rates.*

### Collector's Price Guide books by Bunis:


**Antique Radios, 4th Ed. 8500 prices, 400 color photos ..... \$18.95**  
**Transistor Radios, 2nd Ed. 2900 prices, 375 color photos ..... \$16.95**  
*Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.*



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741  
Phone: (978) 371-0512 — Fax: (978) 371-7129



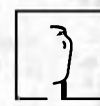Web: [www.antiqueradio.com](http://www.antiqueradio.com) — E-mail: [ARC@antiqueradio.com](mailto:ARC@antiqueradio.com)



Welborne Labs

Online

*More than just a resistor & capacitor store.....checkout what's new at the Labs:*

Our new **ULTRAPATH bp** tube linestage is the first battery powered all-tube preamp **kit** to hit the market. Based on Jack Elliano's original Ultrathath circuit and utilizing the 6GM8/ECC86 tube which was developed solely for automotive applications, the **ULTRAPATH bp** sports several interesting design features:

- Unique Ultrathath Circuitry
- Dual-Mono Design
- Independently Switched Sources and their Grounds
- Transformer Coupled Output w/xtra Headphone Tap
- Low Voltage Battery Supply: 24V B+ w/6V Filament
- A large selection of options and add-ons



**Our Basic Kit Version is just \$695 Complete! The Ultimate Version (pictured) is \$1250.**

[www.welbornelabs.com](http://www.welbornelabs.com)

tel: 303-470-6585

- - We Ship World Wide - -

# System Power Control

Try this circuit to control the power to your audio system.

By Frank S. Thomas III

After installing a new preamp in my system, I experienced audible, but not dangerous, thumps upon turn-on and turn-off. The preamp incorporates tightly regulated power supplies, while the power amps incorporate the usual capacitor input filter power supply. Neither of the power amps—a Hafler DH200, highly modified, nor the new Hsu subwoofer amp—had ever caused any turn-on or turn-off artifacts. The problem was in the preamp power supply.

I decided to solve the problem with a power control unit, even though another solution is to simply manually switch the power amp(s) on after switching on the preamp; and switching the power amp(s) off before the preamp. Most of the time I remember this unusual sequence, but other members of my family do not. I determined that a time delay of five seconds was enough to allow the preamp power supply to stabilize before switching the power

amps on or off.

However, this imposed an unusual requirement. I know of no reasonably priced time-delay devices that turn on in one sequence and turn off in the opposite sequence. You could make a logic system work, but I am not very skilled in designing such circuits.

Furthermore, the power levels would require both voltage and current translation from the logic circuit levels. So I decided to combine a simple time-delay device with appropriate switching to control the three AC outlets. After several attempts, I developed the circuit shown in Fig. 1.

## CIRCUIT OPERATION

The time-delay device is an ancient Amperite thermal relay (TD) with a nominal five-second delay at turn-on, a slightly longer delay at turn-off, and a 115V AC heater. However, I didn't want to switch the AC to the power amps through the Amperite relay contacts. In this design, the TD powers a

transformer/rectifier circuit to energize a power relay, which you can select to match the current requirements of the main power amps. You may use another type of TD, provided it has sufficient delay both at turn-on and turn-off.

There are two additional requirements for this circuit to work properly. The first is that the main switch must be a DPDT type. One pole supplies AC to the TD relay heater, while the second supplies AC to the relay contact/transformer/rectifier/power relay. They can't be combined into one switch contact or the circuit will "lock up" and won't turn off, due to the hold-in action of the preamp power circuit from the power relay.

The second requirement is that the preamp power must be maintained until the TD relay drops out. Remember, the preamp turns on first and turns off last. This is accomplished by providing AC from the main switch for turn-on and from one of the power relay contacts to maintain AC until the TD times out.

I designed this circuit to power my system. The preamp, which appeared in *Stereophile* magazine, November 1991, as "Aunt Corey's Homemade Buffered Passive Preamp," is a homemade almost passive unit made popular by Corey Greenberg. It is powered by a separate, very robust, power supply described by Gary Galo in *The Audio Amateur* 4/90. It is housed in a surplus PAT-5 chassis, with a custom smoked glass front panel, and gold knobs from an earlier Dynakit. It incorporates a separate headphone amplifier from Headroom.

Two main amplifiers are used: a Hafler DH-200, much modified, driving biwired Vandersteen 2Ci main speakers, and a stock Hsu Research driving a single Hsu TN1220H0 subwoofer. Source components are a Marantz CD-

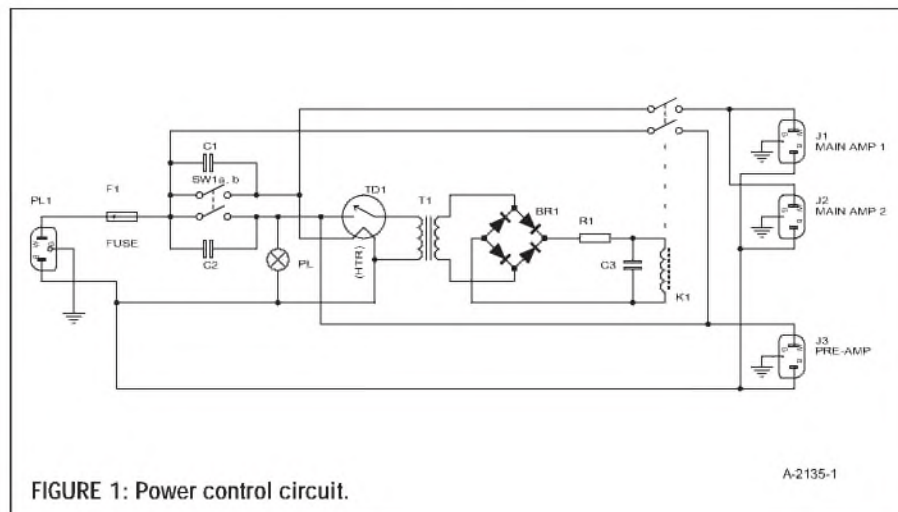


FIGURE 1: Power control circuit.

A-2135-1



63 CD player, with digital output to a separate Assemblage DAC-2 digital processor. The FM tuner is a Dyna FM-5 rebuilt into a Super Tuner Two by Frank Van Alstine. Interconnects are homemade using Mogami cable. Future plans include a new equipment cabinet and new speaker cables.

#### ABOUT THE COMPONENTS

The main fuse is a compromise between adequate capacity to carry the main amp currents and protection of the start-up system elements. I used a 20A fuse, which provides little protection in the event of a failure of T1, BR1, or the K1 relay coil. In over 50 years I have never had a failure of this type of component. Nevertheless, you can add a second fuse to protect these components just before the TD1 switch contact, but after the junction point which feeds the preamp receptacle. This fuse can be in the range of 1–2A.

The DPST switch is a 20A toggle style. This may be difficult to find, so other styles or a common two-pole household wall switch rated for 20A will work just as well. C1 and C2 are 0.01 $\mu$ F, 1000V disc capacitors, which are connected to the line and should be so rated for this application. PL1 is a neon pilot light rated for 115V, but an LED with dropping resistor would work just as well. TD1 is an Amperite octal base time-delay relay with a 115V heater and a five-second time delay. The contact rating is 3A.

T1 is a small, 12.6V secondary transformer. A current rating of 300mA is sufficient for the power relay I used, so a Radio Shack 273-1385 or 273-1365 will be more than adequate. However, if you decide to use one or more heavy-duty relays, you may need to substitute a Radio Shack 273-1352. BR1 is a 100V, 1A bridge rectifier. A Radio Shack 276-1161 is suitable.

To provide current limiting to the power relay, R1 is a 150 $\Omega$ , 2W resistor. You will need to adjust the resistor value to suit both the transformer output voltage and the power relay coil current. C3 is a 100 $\mu$ F, 50V electrolytic. K1 is a Radio Shack 275-218, DPDT with 10A contact rating.

The coil current in the current catalog is 130mA at 12.6V; however, the one I used was listed at 75mA, which

sized the power rating for R1. It is a plug-in style, but I mounted it upside down and soldered wires directly to the lugs. As I discussed earlier, if your main amplifiers require more current capability, a 20A DPDT relay with a 12.6V coil is available from Radio Shack Unlimited, as part number RSU 12131496.

I did not include RFI/EMI filtering since each of my components includes it, and the power control is fed from a filtered AC supply. The two major options are the TD and the power relay. You can use a different TD, provided it has sufficient turn-on and turn-off time delays. Also, you can eliminate the transformer/rectifier-power relay if the TD relay has sufficient current capability, and has separate switch contacts to supply the main amp power separately from the preamp power, just as the power relay does in this design.

The power relay I used has a 12V DC coil, because I didn't want any AC buzz from a 115V AC coil, but you could experiment with it and eliminate the transformer/rectifier. Ideally, the power relay could be a 3PDT so each power amp could be fed from a separate contact. The DPDT I used has 10A contacts and could be considered marginal. Other relays are available from Radio Shack with 3PDT, 10A contacts and DPDT, 20A contacts by special order. If overkill is to your liking, RS also has 30, 40, and 70A contact relays, but they are SPST.


The resistor is used to control the power relay coil current, and its value will depend on the selected relay and the transformer/rectifier output. The capacitor simply provides some ripple smoothing. Obviously, the main fuse, power switch, and pilot light are selected to provide sufficient capacity. The capacitors across the power switch may not be necessary, but I like to use them. I built the unit in a 4 × 5 × 6" mini-box, but if some of the options are chosen, a smaller box could be adequate.

The unit has been in my system now for about two years and is working just fine. Readers with any feedback or alternative bright ideas can reach me at franktren@sbcglobal.net. ❖
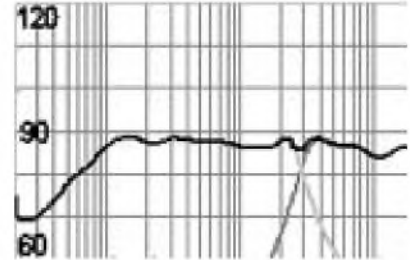
## ADIRE AUDIO

A new video-shielded, **The KIT51** quality minimonitor kit:

The latest HT kit from Adire Audio. Using our own AV5 5.25" woofer and the Audax TM025F1 tweeter, the KIT51 is a smooth performer! Video shielded with strong bass down to 80 Hz in a 5.3 liter cabinet.



The KIT51 uses a 6th order xover at 3 kHz, and has an 8 Ohm impedance. Everything but the cabinet is included: drivers, xover parts, mounting hardware for just \$199/pr.

FR: 80 Hz—20 kHz,  $\pm$ 3 dB

IMP: 8 Ohms Nominal

SPL: 87 dB @ 2.83 Vrms

SIZE: 9"W, 12"H, 6"D

COST: **\$199/PR COMPLETE**

Adire Audio carries a full range of kits, products, and services for the DIYer. Please contact us at:

**WWW.ADIREAUDIO.COM**  
PHONE: 425-778-WOOF (9663)

## DO YOU HAVE SURPLUS STOCK OF SPEAKERS?

- US & European drivers & tweeters preferred
- Quantities from 500 to large quantities
- Prompt payment
- Contact us with details



Electus Distribution  
Sydney, Australia

email:

mreynolds@electusdistribution.com.au

Fax: 61 2 9741 8500

www.electusdistribution.com.au

**ELECTUS**  
**DISTRIBUTION**

# Build a Reactive Load

This author builds a reactive load to test the behavior of his amp designs. **By Dick Crawford**

**O**n page 66 of the May 2002 issue of *audioXpress*, Dennis Colin writes:

“We all know how reactive most speakers are, but consider how profoundly this exacerbates amp(lifier) distortion: you have a wildly-gyrating elliptical load-line plunging the output circuitry into all kinds of normally uncharted regions (sounds figurative but is literal here). The ‘wild gyrations’ are from the vast multitude of simultaneous musical tones exciting the usual speaker impedance variations (magnitude and phase) across the audio band.”

This struck a chord, as I’ve sometimes wondered how my amplifier designs would behave using a reactive load. I decided to design and build a reactive load . . . but what kind? Mr. Colin advises both inductive and capacitive loads at 4 and 8Ω, and at 30 and 60° phase angle, for several different frequencies. This would represent a closet-full of reactive loads, and my closets are already full of audio junk.

So I decided to build the worst-case reactive load: inductive and capacitive at 60° over a range of audio frequencies. I chose 4Ω for this design. I found that I could combine a resistive load, an inductive load, and a capacitive load all in one unit (*Fig. 1*).

## COMPONENTS

The resistive load is the heart of this design, with additional circuits representing the inductive and capacitive segments. Since the 4Ω resistive load is in series with the other loads, the load on

the amplifier is never less than 4Ω. This is only fair, as some amplifiers (even good ones) do not like loads of much less than 4Ω.

The inductive load is about 3mH, which could be a big subwoofer. The capacitive load is about 1μF, which could be an electrostatic driver. The finished box (*Photo 1*) has binding post (banana plug) connectors, with the usual 3/4" spacing, with one common binding post (black) and three binding posts (red) being the inductive, resistive, and capacitive connections.

Because I did not want the components to add measurable distortion, I used air core inductors, metallized polypropylene capacitors, and wire-wound resistors for this design. If you have some other preferred components, please use them. Just remember Crawford’s edict, which says that all parts have some distortion.


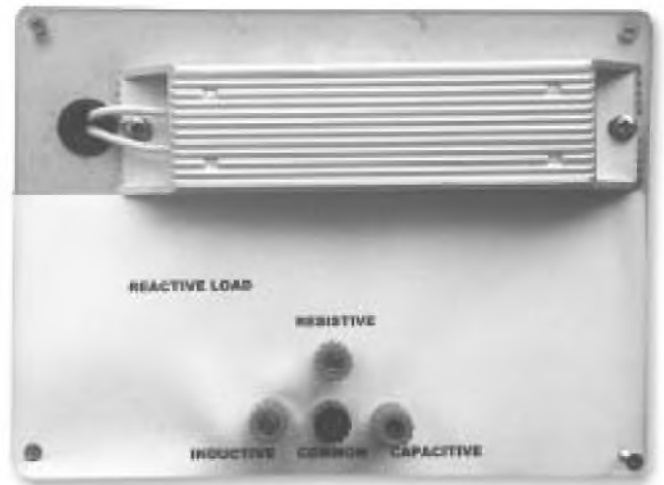


PHOTO 1: The finished box.
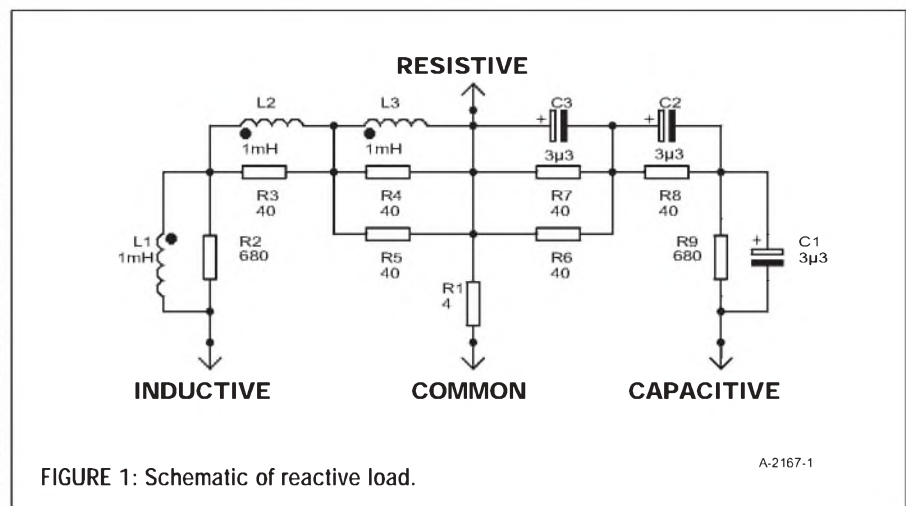
## PERFORMANCE

My goal was reactive loads of 60° (±10°). *Figure 2* shows the measured reactive loads. The inductive load achieves specifications above about 500Hz. The capacitive load is within specification above 200Hz. The lower frequency limits were a compromise, as I wanted reactive loads that would resemble real-world loudspeakers, and I wanted to limit the number and size of the components needed.

As an amplifier designer I can attest that reactive loads usually have their worst influences above 1kHz. The total harmonic distortion (THD) introduced by the reactive loads measures less than 0.01%. It’s probably much less, but



this is the limit of my present measurements.

### POWER RATINGS

The power dissipation of this load box is limited by the 4Ω, 100W resistor. For higher power you need a more robust

4Ω resistor, and for power levels above 200W I recommend more robust inductors, as well. I selected the capacitors and other resistors in the parts list to tolerate an amplifier output of at least 40V RMS, or a nominal 400W. Heatsinks for the 4Ω resistor may be

required for safety reasons, as my calculations show that even at 100W this design will become hot. I mounted the 4Ω resistor on top of the box to improve the cooling due to airflow. Both of the reactive loads have lower power dissipation than the resistive load.

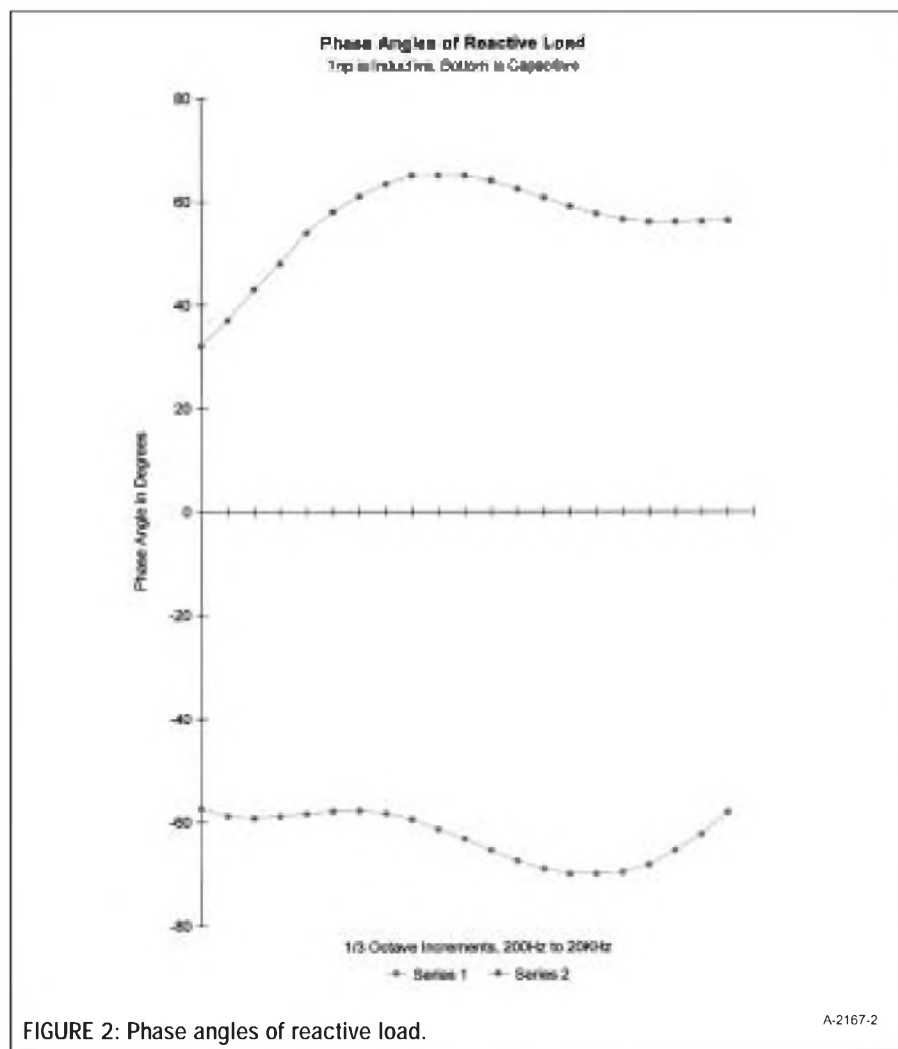


FIGURE 2: Phase angles of reactive load.

**TABLE 1  
REACTIVE LOAD PARTS LIST FOR SINGLE CHANNEL AT 100W**

		COST
<b>CAPACITORS:</b>		
C1-C3	3.3μF/250V, 5%, 027-420, 3 @ \$1.77	\$5.31
<b>INDUCTORS:</b>		
L1-L3	1mH, 2%, 300W, 266-826, 3 @ \$5	\$15
<b>RESISTORS:</b>		
R1	4Ω, non-inductive, 100W, 019-015, 1 @ \$11.50	\$11.50
R2, R9	680Ω, 10%, 5W, 2 @ \$0.19	\$0.38
R3-R8	40Ω, 10%, 20W, 6 @ \$0.55	\$3.30
<b>HARDWARE:</b>		
<b>CONNECTORS:</b>		
B1-B3	Red binding post (banana), 090-485, 3 @ \$0.95	\$2.85
B4	Black binding post (banana), 090-480, 1 @ \$0.95	\$0.95
Chassis	Radio Shack project box, 8 × 6 × 3", 270-1809, 1 @ \$6.99	\$6.99
		<b>Total: \$46.28</b>

Components from Parts Express, unless otherwise noted

### DESIGN OPTIONS

What about 8Ω loads, or 2Ω loads, or whatever? The general rule is that if the load impedance is doubled, then all the inductors and resistors of Fig. 1 are doubled, and all the capacitors are halved. Of course, the "versa is vice."

### CONSTRUCTION

I built my unit in a Radio Shack project box. All of the other parts are from Parts Express (Table 1). I mounted the 4Ω resistor to the outside of the metal top using 8/32 hardware. The other parts are mounted to the inside of the metal top using silicone rubber glue.

I glued the inductors so that they are perpendicular to the aluminum top—close to, and parallel to, the sides of the plastic enclosure. This gives good separation of the inductors and reduces eddy currents in the top. I also glued the 40Ω, 20W resistors to the inside of the top cover.

There is no printed circuit board, as I made the connections by wrapping the component leads around each other and applied lots of solder. I drilled several 1/4" ventilation holes in the plastic enclosure.

### RESULTS

I measured the total harmonic distortion (THD)—at 2.83V RMS—of one of my newer amplifier designs using this load box. As compared to the resistive load, the THD increased moderately for the inductive load, and just about doubled for the capacitive load. The results for the intermodulation tests that Mr. Colin recommends might be different.

### CONCLUSION

There is no doubt that reactive loads are harder for an amplifier to handle than resistive loads, and so it is instructive to test power amplifiers with this reactive load box. This design is simple, the cost moderate, the size is reasonable, and it's easy to use. ❖



# Care and Maintenance of DuKane Ionovac Tweeters

Discover how these unique speakers operate . . . and how you can bring them back to life. **By Daniel Schoo**

**T**he DuKane Ionovac (*Photo 1*) is distinctive among speakers in that it operates on a principle very different from the usual mechanical transducer with moving parts. In the Ionovac there are no parts of the speaker that move. The sound is produced by the interaction of air with high temperature plasma contained inside an open-ended quartz tube.

## HOW IT WORKS

The system is based on a radio frequency oscillator operating at about 27MHz. The audio signal applied to the oscillator modulates the amplitude of this radio frequency signal. The RF signal from the oscillator is greatly increased in voltage by a coil very similar to a Tesla coil. The output of this coil connects to a small pointed electrode inserted into the quartz tube. Energy from the high-voltage RF signal radiates from a sharp point on the end of the electrode and forms a plasma inside a small chamber in the quartz tube.

As the amplitude of the audio signal increases and decreases, so does the amplitude of the RF energy. This, in turn, causes the size of the plasma field to increase and decrease in direct proportion to the audio. As it does, it com-

presses and rarefies the air in the chamber causing compression waves. These waves exit the end of the tube and are coupled to the inlet of a horn. The waves travel down the horn and exit into the room as sound.

The application of this simple concept is closer to a perfect speaker than just about any other means. With no moving parts, mechanical inertia and resonances are minimized.

While it is a very good speaker, it is far from perfect. Nonlinearities in the modulation of the 27MHz RF and colorations added by the transformer that couples the audio into the oscillator, called the modulation transformer, alter the frequency response and add distortion. These effects are relatively small compared to the typical voice coil or electrostatic type of speaker with the inherent mechanical drawbacks each has.

Also, because of physical limitations, the lower end of the frequency response is limited to about 1.5 to 2kHz. Frequency response above this extends well into the ultrasonic range and is limited mostly by the modulation transformer.

There are two sections to the Ionovac speaker connected together by a four-conductor cable and ground strap: the power supply (*Photo 2*) and the oscillator/horn assembly. The power supply contains the components that convert the 120V AC power to the DC supply voltages necessary to operate the oscillator. The power supply is a voltage doubler type with no power transformer. The main supply is 310V DC for the plate of the oscillator tube and 150V DC for the screen grid.

Two other parts complete the power supply. A small 120V to 6.3V filament transformer supplies power to operate the heater in the oscillator tube. A modulation transformer couples the low impedance signal coming from the audio amplifier into the screen grid of the oscillator tube. The modulation transformer also provides ground isolation

## ABOUT THE AUTHOR

Daniel Schoo's interest in antique radios and related equipment began at a young age. He collected radios and learned to repair them growing up in the mid 1950s and 1960s. After graduating from college in 1973 with a Bachelor's degree in Electronics Engineering Technology, he accepted a position at the Fermi National Accelerator Laboratory, a national laboratory for research in high-energy physics, where he continues to work. His interests cover many facets of electronics and antique radio technology.

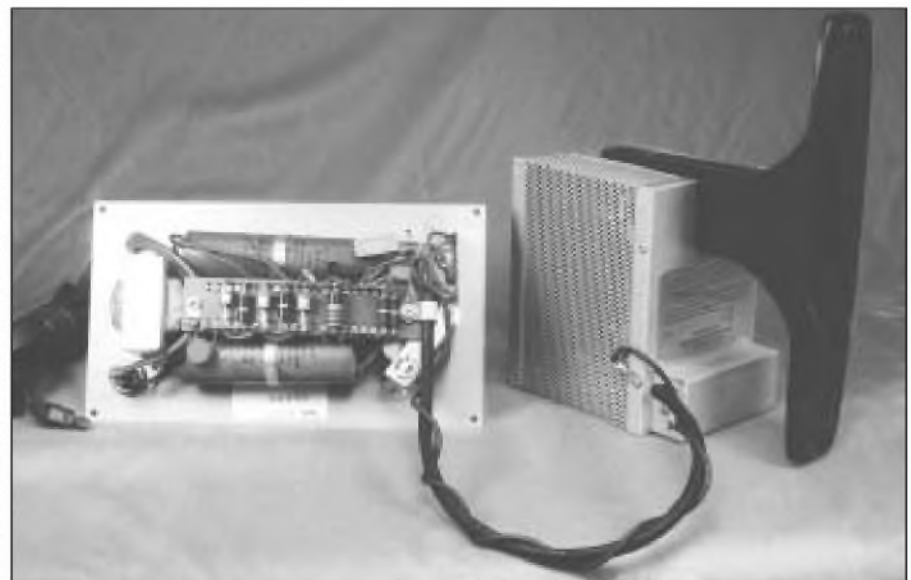


PHOTO 1: Overall view of the complete speaker system.

of the 120V AC power line and blocks the 150V DC screen bias voltage from appearing at the audio input terminals of the Ionovac. These components are all mounted on an open-face metal plate and tied together using a set of terminal strips.

The oscillator/horn assembly contains the oscillator tube and related components, the high voltage coil, the electrode/quartz cell (Photos 3 and 4), and the horn, all mounted in a shielded aluminum box (Photo 5).

### REGULAR MAINTENANCE

The biggest problem in using Ionovac speakers is maintenance. The construction of the Ionovac is much more complex than a magnetic or electrostatic speaker. With consumable components involved, more can go wrong.

When a critical component fails, the speaker is useless until you replace the part. The electrode is consumed during operation and the quartz tube becomes encrusted with dirt and oxidation products of contaminants in the air and electrode residue. A small screen inside the inlet of the horn also becomes clogged with dust and oxidized byproducts. Eventually the tip of the electrode burns away, and the speaker functions poorly or ceases to function. The vacuum tube becomes weak and other components fail.

DuKane guaranteed a minimum lifetime of 1200 hours for the cell. When it did need replacement, DuKane sold a kit containing an electrode and a quartz tube called a "cell replacement kit" part number 438-37, which you

could buy for a few dollars. The kit included instructions on how to remove the old cell and install the new one.

When the electrode went bad and the quartz became fouled, installing a cell kit would restore the operation. This assembly is sometimes called a "crystal," but that term is not used in any of the DuKane documentation. Many years ago DuKane discontinued supplying Ionovac parts, which are now very scarce. Fortunately, very few of the components prone to failure are absolutely irreplaceable.

First and foremost in operating failures is the electrode. When you first turn on the speaker, the oscillator tube takes some time to warm up before it starts. When the oscillator starts, you hear a slight click and see a blue-violet glow down inside the throat of the horn (Photo 6). The glow initially is unstable and sometimes takes a minute or so to fill in and settle down as it reaches operating temperature.

After it settles down, the glow should be perfectly round and even in intensity over the entire end of the tip of the electrode except for a small brighter spot in the exact center. Some electrodes on startup emit a buzzing or squealing sound as the tip heats up and the unstable plasma pulsates. DuKane called this effect "singing," which is a normal part of startup.

With a new electrode installed, the plasma can be uneven and produce these effects as it breaks in but should clear up within about the first 15 minutes of operation. If the plasma does not fill in evenly or continues to make

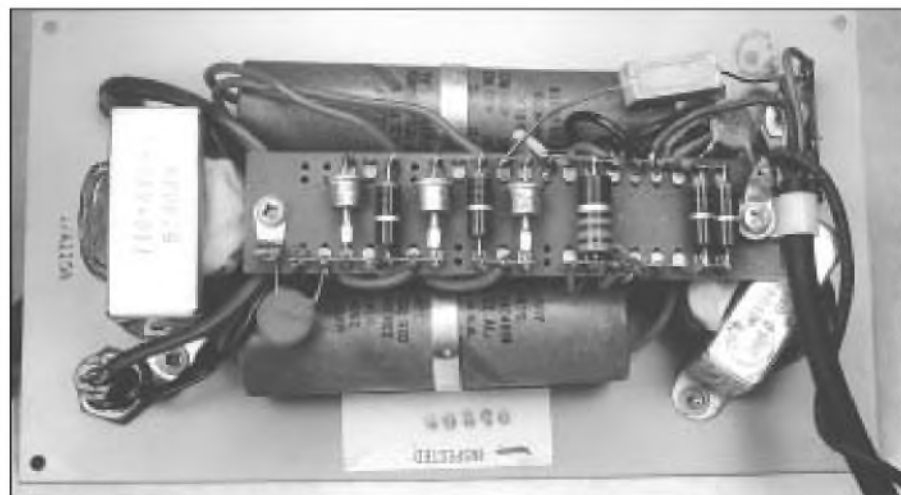


PHOTO 2: The power supply is a simple circuit. The transformer on the left is the filament transformer and the one on the right is the modulation transformer.

# ALL ELECTRONICS CORPORATION

## Li-Ion Prismatic Cell

3.7 Volt, 1400 mAh rechargeable lithium-ion cell. Made by Panasonic, the prismatic cell is 1.94" x 1.32" x 0.4" thick. Lithium-ion cells have a very flat discharge curve providing a very stable power output. Further, they don't suffer from the "memory" effect and don't need to be fully discharged before recharging. The cells have been prepped with a small custom circuit that adds approximately another 0.2" to the length of the cell. The circuit can be removed. It was designed to provide spark protection, over-charge protection, filtering and to identify the charger used with the cell. A schematic of the circuit and specs for the cell are available on our website. **CAT# BTE-45**




**\$5.50**  
each

**10 for \$5.00 each**  
**200 for \$4.00 each**

**SHOP OUR ONLINE STORE**  
[www.allelectronics.com](http://www.allelectronics.com)

## Electroluminescent Strip

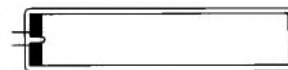

5" x 1" electroluminescent strip. Ivory in off-state. Glows green when energized by 120 Vac or inverter. For backlighting control panels, special-effects lighting, models etc. Solderable pins extend 0.2" beyond end of panel.

**CAT# EL-5**

**\$3.50**  
each

**20 for \$3.25 each**  
**100 for \$2.50 each**

## 12 Vdc 1.25 AMP Power Supply

DVE # DSA-0151-12  
2.1mm I.D. coax power plug.  
Center positive. UL, CSA.

**CAT # PS-1215**

**\$7.25**  
each



**10 for \$6.95 each • 100 for \$6.50 each**

**ORDER TOLL FREE**  
**1-800-826-5432**

**CHARGE ORDERS to Visa, Mastercard,**  
**American Express or Discover**

TERMS: NO MINIMUM ORDER Shipping and handling for the 48 continental U.S.A. \$6.00 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include local state sales tax. Quantities Limited NO COD Prices subject to change without notice.

**CALL, WRITE**  
**FAX or E-MAIL**  
for our **FREE**  
**96 Page**  
**CATALOG**  
Outside the U.S.A.  
send \$3.00 postage.

**MAIL ORDERS TO:**  
**ALL ELECTRONICS**  
**CORPORATION**  
P.O. Box 567  
Van Nuys, CA 91408  
FAX (818)781-2653

**e-mail [allcorp@allcorp.com](mailto:allcorp@allcorp.com)**

any sounds of its own, you should remove the electrode and quartz and examine them for damage, wear, and fouling. If the electrode is bad, you must replace it. Other than individual private stocks, there are no sources to buy new electrodes. This does not mean that you cannot replace them; they can be specially made if you have the production documentation.

You should take special care when removing an electrode. Never grasp the lead wire and pull on it to retract the ceramic retaining bar. This will overstress the bar and possibly snap it in half.

The retaining bar is made of a machinable glass-bonded mica ceramic called Supramica™. I have made replacement retainers out of Macor™ machinable glass ceramic that work equally well. Machinable ceramics are relatively expensive, and the fabrication of replacement retainers as well as electrodes is beyond the scope of this article.

Grasp the two ends of the bar between the thumb and forefinger of one

hand. Hook the connecting wire with your middle finger and apply a slight tension to it so that the cup remains seated in the retaining bar as you retract it. Pull straight back on the bar until the connecting cup just clears the end of the electrode (Photo 7). If the cell starts to come out with the connecting cup, push it back into place with a small wood stick and hold it until the cup is clear. Place the bar below the cell and slowly allow it to return to a forward position underneath. Remove the electrode and quartz for service. Replace the electrode and quartz and place the ceramic retaining bar back in position (Photo 8) in reverse order of removal.

### ELECTRODE LORE

DuKane has long since discarded its original documents on the electrode. Even though the DuKane documents are gone, much is known about the electrode material and dimensions. The DuKane electrode (Photo 9) was made

of a metal alloy very similar in composition to type 416 stainless steel. The manufacturer started with a rod of material drawn down to .162" in diameter and turned down this raw stock to form the tip and shank ends and then cut it to length. After machining and finishing, the electrode was heat-treated to impart hardness.

Within limits the specific material is not as important as the dimensions and heat conductivity. Alloys that are hard are better than softer ones. Those having a good resistance to the effects of heat and corrosion along with a moderate heat conductivity make good choices for electrode service. Aluminum and other soft metals are totally unsuitable

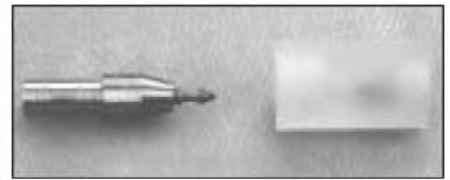


PHOTO 3: Close-up view of an electrode and cell.

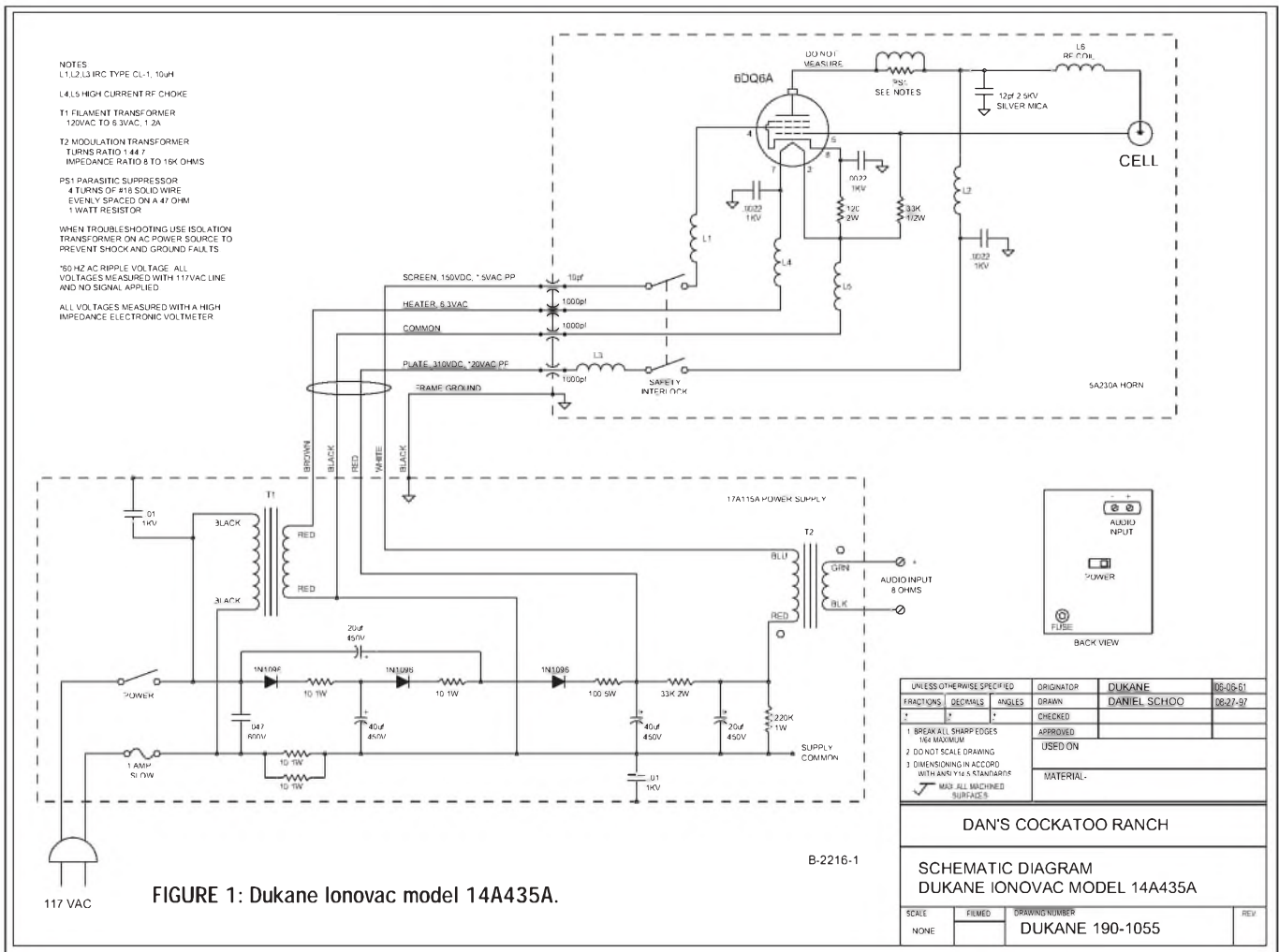


FIGURE 1: Dukane Ionovac model 14A435A.

for electrode material.

The inventor's original plasma speaker designs used platinum electrodes. Platinum is a good material but totally unsuitable for mass production



PHOTO 4: Electrode inserted in a cell. The second electrode is for reference to illustrate the relative position of the parts of the electrode inside the cell.

because of the prohibitively high cost. Replacement electrodes have been made from various metals and alloys. The material used determines the operating temperature, the durability, and lifetime of the electrode.

Several of the stainless steel and nickel alloys are good candidates for electrodes. Type 304 is a commonly available stainless alloy that is relatively easy to machine and has a moderate life comparable to that of the factory originals. High-temperature space-age alloys such as Inconel™ would also probably work very well.

Tungsten and tungsten alloys make

outstanding electrode materials. Tungsten is extremely hard and resistant to heat. It can last almost indefinitely but is very difficult to shape due to its hardness.

Another disadvantage of tungsten is its heat conductivity. High tip temperatures are important for proper operation. Tungsten has superior heat conductivity, and because of this, tungsten electrodes can take a little more time to reach operating temperature than nickel or chromium alloy electrodes.

Claims that the surface must be absolutely smooth and flawless are not accurate. I have deliberately made electrodes with a slightly rough surface, and they worked as well in tests as highly polished samples. The proof of this is evidenced by the fact that no matter what the finish is when first installed, the electrodes soon become pitted and burned in service, and they continue to function satisfactorily.

#### QUARTZ CLEANING

Another cause of failure is fouling of the quartz tube. When replacement parts were available, you could discard and replace the electrode and quartz tube with a new set. Today, because this is nearly impossible, you must reuse the quartz.

Fortunately, the quartz is relatively sturdy and will outlast several electrodes. Dirt and deposits from the high plasma temperatures build up on the inside of the plasma chamber and can

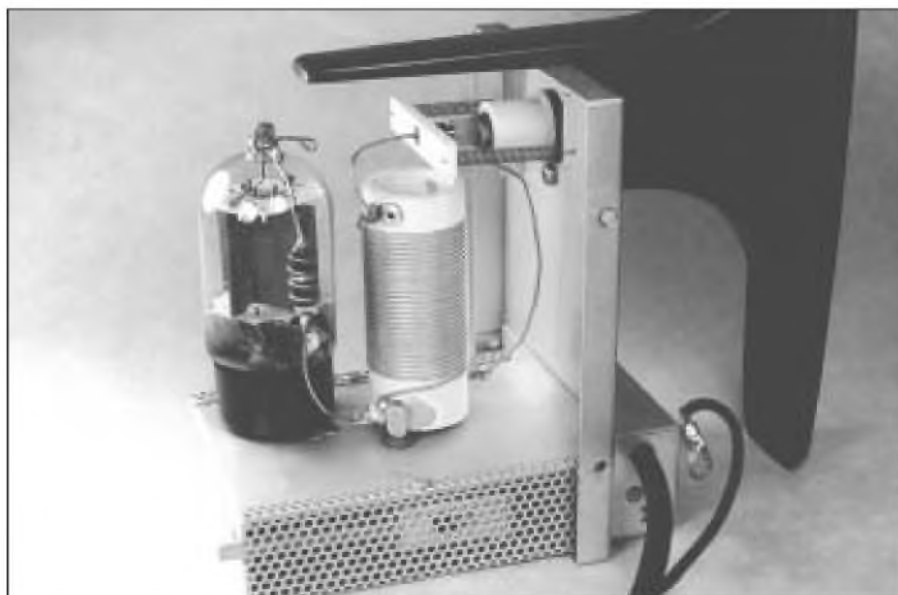


PHOTO 5: The speaker section with the protective cover removed. Note the small tab in the lower left corner of the chassis. This is the actuator for the interlock switch that disconnects the supply voltages when the cover is removed.



**JENA KITS!**



18 & 22 gauge Ultra-Wire  
for your projects




Marinco 320 I.E.C.  
Deep Immersion CRYO

All I.E.C. and NEMA terminations available.



CRYO-Hubbell Duplex



Speak-Easy Cables

Our expensive ultra high-end products have earned us a "Formula 1" status. Surprising to some, we also offer very affordable and DIY products steeped in the same design philosophy.

Our authentic liquid nitrogen cryogenic immersion techniques are definitive state of the art.

Our DIY components offer the ultimate performance at popular prices, all immersion CRYO treated.

DIY interconnect and speaker cable kits  
RCA and XLR cable and panel components  
AC power parts - wide assortment



**See our website**

**JENA LABS**  
www.jenalabs.com

# Toroids for Audio



## Tube Output

Toroidal transformers for tube output applications. Plus related products.

Standard Series (push-pull)

Single-ended

Specialist Range

Special Designs

Power Transformers

Chokes

Chassis for Tube Amplifiers

PCB for 70W & 100W Amps

Book by Vanderveen

## Electrostatic

Step-up toroidal transformers for Electrostatic loudspeaker applications.

## Solid State Power

Low noise, low inrush  
500 to 2000VA fully  
encapsulated power  
transformers.

## Standard Power

A broad range of high  
quality, approved,  
toroidal transformers.  
Designed for general  
purpose applications.  
From 15 to 1500VA.



**PLITRON**  
MANUFACTURING INC

8-601 Magnetic Drive  
Toronto, ON M3J 3J2  
Canada

416-667-9914

FAX 667-8928

**1-800-PLITRON**  
(1-800-754-8766)

[www.plitron.com](http://www.plitron.com)

obstruct the opening. As long as the quartz tube is not broken, cracked, or has no serious pitting, you can clean it and place it back in service. If it is damaged beyond use, there is no alternative at this time to hunting down an old stock replacement at great difficulty and, no doubt, great expense. I have tried several powerful solvents and acids to remove the crud inside the quartz tube, but have found no chemical method that will remove the deposits effectively.

The best method turns out to be the simplest. Gently scraping the inner surface of the quartz tube will remove nearly all of the built-up deposits. A scraper having a very hard surface works best because it will not rub off onto the rough surface of the quartz.

I have used the blunt end of a num-

ber 68 solid carbide drill bit to clean off the surface. A very gentle scraping, one stroke at a time, in and out all the way around the inside surface removes nearly all of the deposits. Do not gouge or attempt to use force, which can damage the surface of the quartz. Better to leave some crud on the quartz than to damage it. Perfect cleanliness is not necessary, but remove as much of the deposit as you can.

After the scraping, gently swab out with a cotton swab soaked with a mild detergent solution and rinse in distilled water to remove the remaining loose dirt. Following a thorough air drying, the quartz tube is ready to use. Never apply force to push anything down through the opening of the quartz, which can be easily cracked and broken.

The screen inside the entrance of the

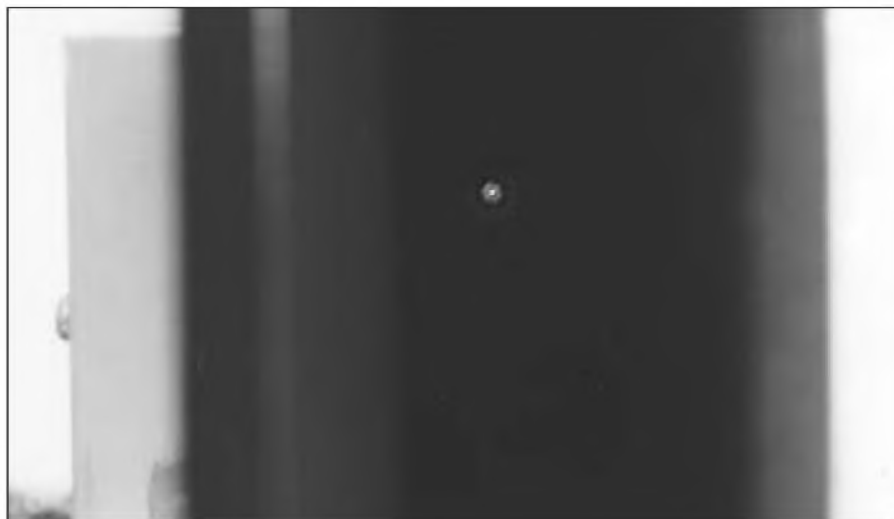


PHOTO 6: A normal plasma pattern. Note the even circular glow with a brighter point in the center. The crosshatch distortion is due to the mesh screen located just in front of the cell in the throat of the horn.



PHOTO 7: The correct way to hold the ceramic bar for removal of the cell components.



horn also collects dirt, which can obstruct the opening. Remove the cell from the horn, then give the horn a gentle blast of air down the throat from a canned air duster. This will frequently remove the accumulated dirt. If this does not remove all of it, very gently rub the screen with a long cotton swab to help loosen the dirt. Be careful not to apply much pressure to the screen, which is very thin and can be damaged easily by too much force.

#### ELECTRODE CARE

When an electrode becomes worn with use, it can cause the plasma to become unstable or irregular. The end of the tip becomes burned and pitted, wearing

back during normal operation. Difficult or incomplete ignition, buzzing, squealing, or snapping noises can result from this. New electrodes tend to do this before they are broken in, but this should clear in a short time. You can sometimes clean used electrodes that have not been completely consumed and put them back into service.

Grasping the tip in a folded-over piece of medium-grade Scotchbrite™ and rotating it is a good way to burnish and remove deposits. If that isn't sufficient, gently clean the tip with 600-grit sandpaper to help restore proper function. Place the paper on a hard, flat surface and gently rub the tip of the electrode forward and backward on the

paper at an angle that puts most or all of the flat side of the tip against the paper. Rotate the shank of the electrode between your thumb and forefinger as you rub it on the paper so that you get even coverage. Just a few strokes are enough.

Removal of large amounts of material or sanding out deeper pits will shorten what life, if any, is left. If the end is burned off flat, wipe the paper a few times across the end to clean it, too. The idea is not to remove much base material but only some of the crust that forms and smooth out the larger deformations.

#### COMPONENT FAILURES

Electrical failures in the associated electronics are common. I will describe several types of failures that happen and what you can do to repair them.

#### Oscillator Tube Plate Cap

Every single Ionovac I have seen has had the plate cap clip on the oscillator tube badly corroded and overheated. The original construction used a plate cap clip composed of two half sections

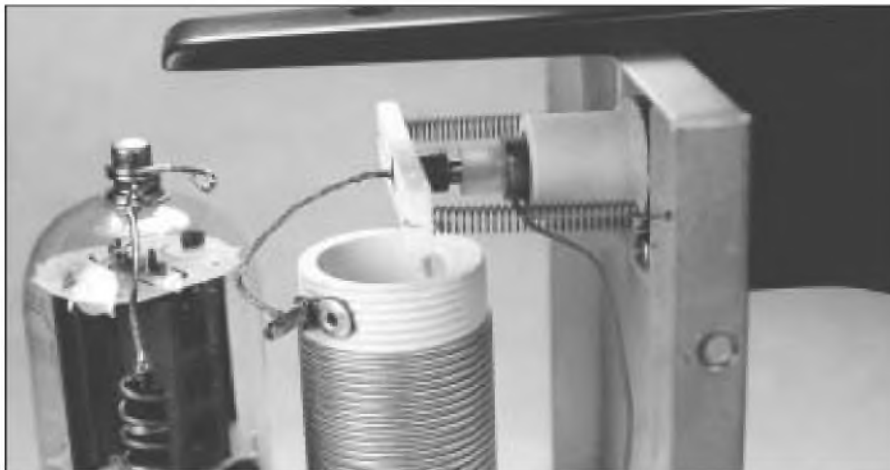


PHOTO 8: Close-up view of the cell mounting assembly. Note the electrode and quartz cell being held in place by the spring-loaded ceramic retaining bar. The bar holds a metal cup pressed against the back end of the electrode. A flexible braided wire attached to the cup connects it to the high voltage coil. Surrounding the cell is a metal sleeve isolated from ground. A wire attached to the sleeve connects it to the oscillator circuit.

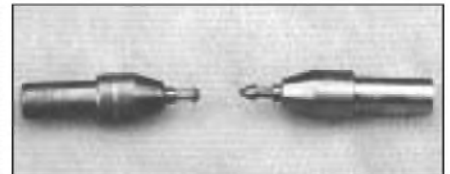


PHOTO 9: Comparison between a new electrode on the right and a used electrode on the left. Note the difference in the length and the sharpness of the points.

# thetubestore.com

Your online source for name brand audio tubes

- Over 1000 types available online
- Perfect Pair matched power tubes
- Capacitors and sockets

Order online at [thetubestore.com](http://thetubestore.com)

or call toll free **1-877-570-0979**



held together by a rivet. The lead wire was put through the hole in the rivet and soldered.

After years of use the rivet corrodes and loses electrical connection with the contact parts. The rivet heats up and becomes progressively worse. Replacement of the plate cap connector is mandatory on all units. I have used the spiral spring clip type with good results.

### Power Supply Cable

The connecting cable between the power supply and the oscillator/horn is insulated with a rubber jacket. With age the rubber becomes hard and cracked. With any movement the rubber breaks off the wires exposing them. Replacement with a new four-conductor #18 cable will solve this problem. The original cable is Belden type 8454 and is still available.

You must take great care when unsoldering the old wire and resoldering the new wire to the feedthrough capacitors in the oscillator/horn assembly. Overheating can melt the solder in the feedthrough causing the center lead to slip out of position. Excessive stress on

the capacitor lead can break the insulating sleeve.

### Feedthrough Capacitors

Feedthrough capacitors can become broken or arced over if the speaker is subjected to large overloads. I repaired one speaker—part of a DuKane column system—that had the woofer blown out by seriously overdriving it. The associated Ionovac tweeter had an arced-over feedthrough capacitor in the oscillator/horn that carried the screen bias and audio signal. It had blackened areas on it where the arcing had burned the metallization.

To prevent damage to the speaker, the absolute maximum audio input voltage should never exceed 2.16V RMS sine wave or 3V peak. Replacement is the only repair for an arced feedthrough. There are two values of feedthrough capacitors—10pF for the oscillator screen grid and 1000pF for the two heater leads and the plate supply. Replacement capacitors are still available from manufacturers on special order.

### Modulation Transformer

Modulation transformers can also become damaged by the stress of being overdriven. They can develop turn-to-turn shorts in the primary or secondary. This will cause the speaker to work at greatly lower volume levels, add distortion, or fail to operate at all. In one speaker I worked on, the modulation transformer had developed a primary to secondary short. This allowed a current path from the power supply back to earth ground through the audio amplifier.

The speaker first blew its fuse. The owner replaced the fuse with one of a substantially higher rating. This, of course, prevented the fuse from blowing again but resulted in all of the DC power supply components and modulation transformer going up in smoke! When I first examined it, I found the modulation transformer and all of the power supply resistors were badly charred.

Replacement of the modulation transformer is not too difficult. Any good-quality audio transformer of a comparable physical size and impedance ratio will work. If only one speaker in a stereo pair needs repair, it is advisable to also replace the transformer in the other side

so that any differences between the old transformer and the new one will be matched in the other channel.

When replacing the transformer, be sure to maintain the original phase polarity, which will guarantee that the speaker will match the phase of its mate and any other speakers in the system. I have marked the schematic diagram (*Fig. 1*) with the phase of the original modulation transformer to use as a guide for replacement.

### Power Supply

The power supply is fairly reliable. Solid-state rectifiers have a very long service life. Only an overload is likely to cause a problem.

At this time all of the Ionovacs are at least 40 years old. The electrolytic capacitors are the most likely components to fail because of advancing age. To date I have not had to replace any electrolytics in an Ionovac, but I'm sure there are some that need it. There are two dual section electrolytics used in the Ionovac. If they need replacement, use four single types having the same values as the old ones.

The other components, such as rectifier diodes and resistors, are all commonly available parts. The original type diodes are no longer available, but modern ones can replace them. A set of 1N4005 silicon diodes will work well in this application.

### Filament Transformer

Filament transformers rarely fail. If a good tube fails to light, check the tube socket for bad connections. Measure the filament circuit with an ohmmeter and verify that the heater RF chokes are not open. If the filament transformer has gone bad, you can easily replace it with any transformer of a comparable physical size and rating.

### WORDS OF CAUTION

The voltages used in this device can be dangerous and possibly lethal if not handled correctly. Certain components such as the cell and the 6DQ6A tube become extremely hot during operation, so you must allow them to cool before doing any work. Remove all power completely from the Ionovac by unplugging it.

You should never bypass the interlock switch on the oscillator cage. Dangerous voltages are inside and present a serious shock and electrocution hazard. If you are not familiar with electronic devices, do not attempt to do the work yourself. Get help from a qualified technician.



### DIAMOND GROOVE

- Analogue Productions
- Audio Fidelity
- Cisco Music
- Classic Records
- Mosaic Records
- Simply Vinyl
- Speakers Corner
- Sundazed

Many other non-audiophile labels  
Over 1,200 new vinyl titles in stock

[www.diamondgroove.com](http://www.diamondgroove.com)

1-877-DGROOVE

[info@diamondgroove.com](mailto:info@diamondgroove.com)

the whole sound of vinyl  
for Canada and the world

## Oscillator Tube

A weak tube will fail to oscillate or give only poor performance. If the cell is in good condition and the power supply voltages are normal, then you can suspect a bad tube. Substitution with a known good tube is the best test for a bad one.

Replacing the tube easily solves tube

### REPLACEMENT PARTS

#### Feedthrough capacitors:

Tusonix type 357-001-X5U 100M, 10pF, screen grid  
Tusonix type 357-001-X5U 102M, 1000pF,  
heater and plate

#### DuKane Ionovac modulation transformer:

Turns ratio 1:44.7

Primary impedance 8Ω

Secondary impedance 16,000Ω

Primary DC resistance 2Ω

Secondary DC resistance 519Ω

Frequency response: 30Hz–20,000Hz, +1, –0.5dB

Power rating: 5W

Suggested substitutes:

Thordarson/Meissner 24S74, 70.7V line to voice coil,  
using the .310W tap

Stancor A-8105, 70.7V line to voice coil, using the  
.310W tap

The closest substitute available for the DuKane modulation transformer is a 70.7V line to voice-coil transformer. Use the 8Ω speaker winding as the audio input and the .310W tap on the 70.7V line winding as the output to the oscillator screen. Except for slight variations in frequency response, the two listed transformers are an exact match for the original.

#### Filament transformer:

Primary 120V AC

Secondary 6.3V AC at 1.2A

Magnatek/Triad type F-14X

Stancor P-6134 (center tap is unused)

#### Tube source:

##### Antique Electronic Supply

6221 S. Maple Ave.

Tempe, AZ 85283

(602) 820-5411

failure. The original tube is an RCA type 6DQ6A, which is not in demand for audio work and was primarily used as a horizontal output amplifier in black and white television sets. You can purchase them for no more than a few dollars from a number of tube suppliers.

## Oscillator Components

Overdriving the speaker can damage components in the oscillator circuit. A failed tube can also cause trouble. These parts are readily available, so you can easily replace them. Overheating because of the bad plate cap clip can also damage plate resistors.

### IMPORTANT SPECIFICATIONS\*

#### Sound output:

.75V RMS continuous sine-wave input = 95dB at 1.5' on horn center axis

#### Frequency response:

±3dB from 3500Hz–30kHz

#### Operating input impedance:

At 200Hz = 5.1Ω

From 1kHz–20kHz = 8Ω +0, –0.8Ω

At 30kHz = 6.30Ω

#### Non-operating input impedance:

At 200Hz = 8.6Ω

At 5kHz = 182.6Ω

At 20kHz = 43.7Ω

#### Input voltage into 8Ω:

0.75V RMS sine wave/1.06V peak = recommended for maximum undistorted output

1.50V RMS sine wave/2.12V peak = 50% modulation

1.75V RMS sine wave/2.47V peak = maximum input without parasitic oscillation

2.16V RMS sine wave/3.05V peak = 100% modulation, absolute maximum input voltage

\*Ratings given are for a typical speaker with a new electrode. Your speakers may vary due to the individual characteristics of the oscillator tube and/or cell condition.

The capacitors in the oscillator section are common types except the 12pF 2500V silver mica. Fortunately, these are very reliable and seldom fail. I have seen one become intermittent, which caused the oscillator to start only once in a while. Silver mica capacitors at this capacity and voltage are very difficult to find. Since the measured voltage across this capacitor never exceeds 850V, I substituted one rated at 12pF at 1000V and had no problems.

The RF chokes in the oscillator are very unlikely to fail. If they do, you can replace them with modern parts that are designed for RF suppression and have about the same inductance. The values are not critical since the chokes are used only to suppress the RF from getting out of the oscillator cage and radiating into the air from the interconnecting power supply cables. ❖

### REFERENCES

1. "Introducing the Ionovac," *Popular Electronics*, May 1961, pp. 56, 57, 117.
2. U.S. Patent #2,768,246, October 23, 1956 granted to Siegfried Klein.
3. General Instruction Manual—Model DuK-5 (14A430) Ionovac, DuKane Corporation PN 400-1141 (undated).
4. Specifications and Instructions (Tentative) Model T-3500 Ionovac, Electro-Voice PN 53518, December 13, 1957.
5. "The Lonophone Loudspeaker," Roger Russell, web document <http://www.sundial.net/~rogerr/ionovac.htm> (undated).
6. Installation Instructions Ionovac Cell Kit 438-37, DuKane Corporation PN 400-1184 (undated).
7. Schematic diagram, Ionovac Model 14A435A, DuKane Corporation Drawing #190-1055, June 6, 1961.

# ZALYTRON

**YOUR ONE STOP SPEAKER  
AND SPEAKER COMPONENTS CENTER**

**Check our web site [www.zalytron.com](http://www.zalytron.com)  
for cutting edge technology in the  
Speaker Industry. Need we say more?**

**Call, Write, Fax or email for our latest catalog**

Mailed FREE in the USA. Canada \$5 P&H, Worldwide \$10 P&H

### ZALYTRON INDUSTRIES CORP.

469 JERICHO TURNPIKE, MINEOLA, N.Y. 11501  
TEL. (516) 747-3515 • FAX (516) 294-1943  
[www.zalytron.com](http://www.zalytron.com) • email [zalytron@juno.com](mailto:zalytron@juno.com)

Our warehouse is open for pick-up 10 AM to 6 PM daily, Saturday 10 AM to 5 PM • UPS orders shipped same day • Minimum order \$50.00

# Showcase

## An Italian THOR

I'd like to share with *audioXpress* readers my piece of work devoted to restyling THOR towers (Photo 1). The Joe D'Appolito project has been described in the *audioXpress* May 2002 issue, and a detailed, step-by-step do-it-yourself construction description has been published by Edward T. Dell, Jr. (Sept. 2002).

The following is my version of this project which departs from previous



PHOTO 1: Overall towers view. You can see the provision made to accept the grille frame once ready. I'm thinking of using thin material similar to ladies' elastic stockings.

### ABOUT THE AUTHOR

Atto Rinaldo is an active retiree after 32 years at IBM, where he experienced various job responsibilities in the US and other parts of the world. He received a radio techniques diploma 45 years ago. Vacuum tubes were the technology used at that time, and he has loved them since. Transistors were just born; he had never heard about integrated circuits. Joining IBM in the late '60s, he has seen vacuum tube computers phasing out just about that time. When transistors and ICs took over, he said to himself that one day he would play with tubes again. He did.



PHOTO 2: A view of the cosmetic panel. The grooves give the tower a "slim" look.

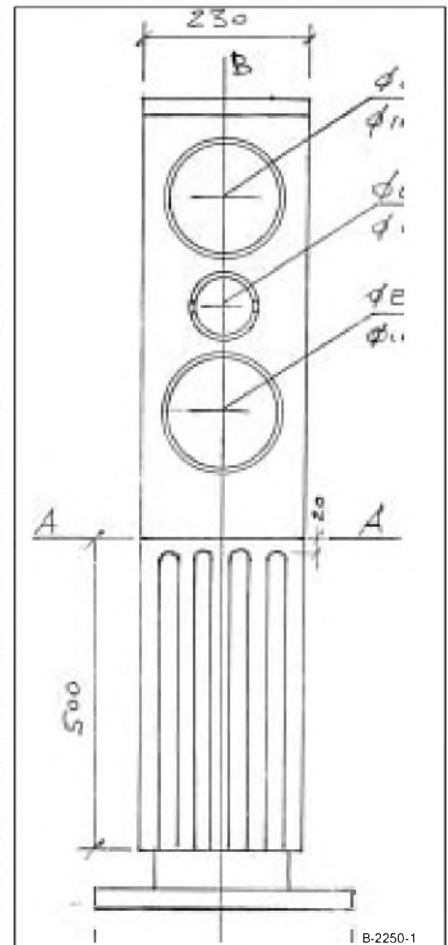


FIGURE 1: This is the original sketch that was selected as "the best" after debating different solutions with a couple of friends.



PHOTO 3: My friend Siro at work while refining a speaker's hole. MDF dust was his worst enemy.

ones in the area of external design. As it turned out, I was so delighted by what I had done that I wanted to share my experience with *audioXpress* readers.

While maintaining the exact specifications of all internal measurements—in order not to alter the quality/performance—I wanted to give this project a better look that its superb sound quality deserves. I thought that the following could be improved over previous projects/prototypes:

1. The bulky base. It needed restyling. Removing it would have given the



PHOTO 4: "T-nuts" used to reliably install the speakers.

2. The front view was too "dull." It required some work to make it more attractive.
3. Missing grille. I believed it needed one in order to protect the speakers from accidental touching.

With that in mind, I prepared a few sketches, and, with the help of some friends, who looked at the different options, I decided to proceed with the version depicted in *Fig. 1*.

The changes include the following:

- The base has been restyled.
- The addition of an "aesthetic" panel on the bottom half of the tower (*Photo 2*).
- Provisions made to allow installation of a grille.

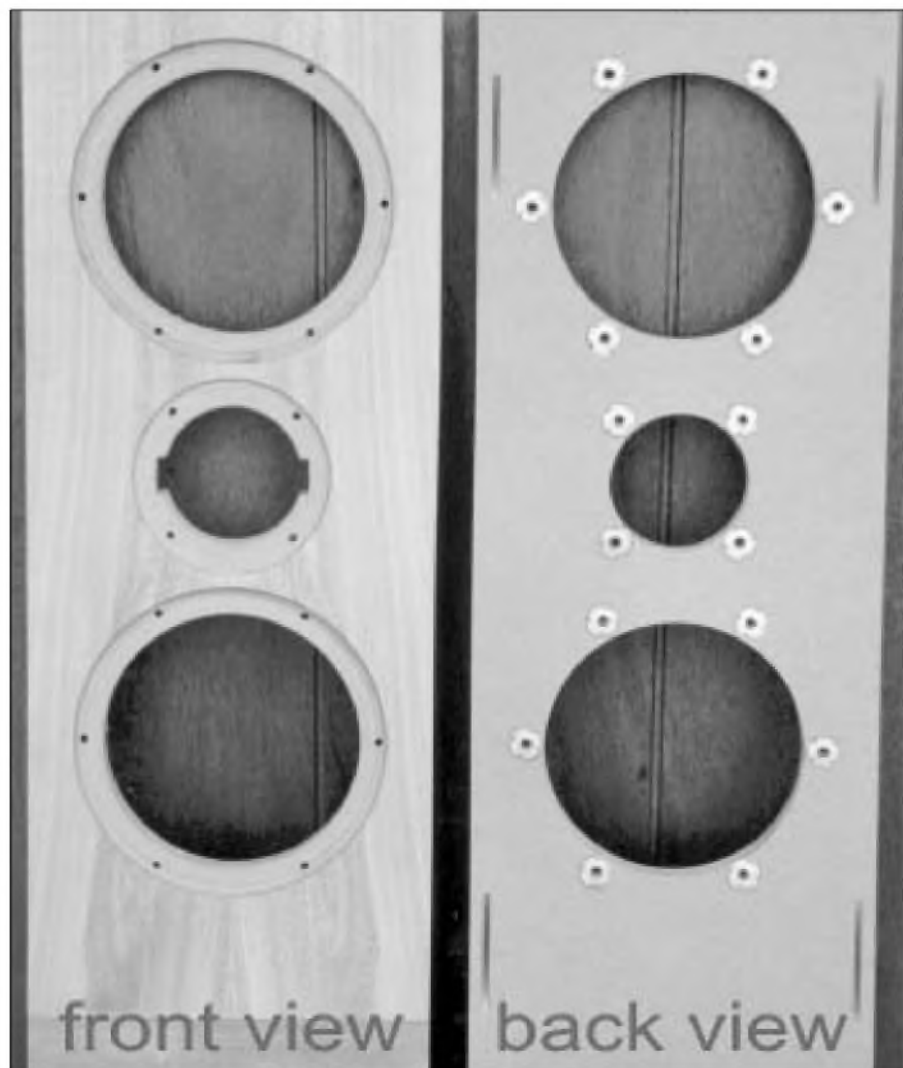


PHOTO 5: "T-nuts" are solidly mounted on the back side of the front panel.

## Electronic Crossovers

Tube  
Solid State

### Line Level Passive Crossovers

### Custom Solutions

We can customize our crossovers to your specific needs. We can add notch filters, baffle step compensation, etc....

*All available as kit*

*Free Catalog:*

Marchand Electronics Inc.

PO Box 473

Webster, NY 14580

Phone (585) 872 0980

FAX (585) 872 1960

info@marchandelec.com

www.marchandelec.com

# LAST

## Record Preservative



Hear Ye – Hear Ye

# LAST®

THE LAST FACTORY

2015 RESEARCH DRIVE

LIVERMORE, CA 94550-3803

925-449-9449 • FAX 925-447-0662

www.lastfactory.com

Drawing a sketch was the easiest part, because building a high-quality THOR TL is not an easy task at all. With the help of my friend Siro (*Photo 3*), a professional joiner, I had most of the work done in his highly qualified joinery. He performed each step with extreme ease; however, he complained about the use of MDF, which, in spite of his dust collector system, seemed to produce dust all over. The sequence of photos, better than my words, give you



PHOTO 6: A view of the base. You can see the wires coming through the panel before sealing the hole with silicon glue. Also visible are the golden speaker's terminals.

an idea of the process and changes.

I would like to comment on the solution I've taken to prepare the holes to fix the speakers.

Since MDF isn't any good at retaining screws—especially if you must remove them a few times—I've implemented the solution of inserting, on the back side of the front panel, a number of "T-nuts" (*Photos 4 and 5*), which gives you the opportunity to remove the screws as many times as you want.

All major parts were assembled using "biscuits" and waterproof glue, as required.

The base contains the crossover (*Photos 6 and 7*) mounted on an aluminum plate which is screwed to the



PHOTO 7: Crossover view before installing onto the base.

I congratulate reader Atto Rinaldo on a beautiful realization of Joe D'Appolito's THOR design using the quite impressive SEAS drivers. His base is certainly an improvement in appearance. The changes to add a grille have some hazards, however.

As Joe has often observed in his many reviews, *any* grille will change the character of the sound. Whether this is for the better or worse is not clear. It could add some amount of diffraction to the sound character both by the top and lower offsets for the grille, as well as the inner edges of the grille frame. His outer edges of the front panel also do not appear to be rounded, another diffraction issue.

The decorative fluting in the lower front section is elegant, but is another variable whose sonic effects are not known. My much plainer design was chosen for purely acoustic reasons, and, since I live alone, I am the only one it needs to please. My visitors have, so far, been so awed by the sound, and they have not commented on the lack of front panel elegance. I was also anxious to strictly follow the designer's prototype.


The Madisound version of the THOR cabinetry also adds a grille to the box. Reader Rinaldo's crossover differs from mine in that bi-wiring is not possible in his. My tweeters and bass drivers are driven by separate amplifiers, theoretically reducing IM distortion.

I fully intended to use threaded brass inserts for mounting the THOR drivers with machine screws, but had not as yet devised a way to position them accurately. Readers may notice that in my Froy project in the March 2003 issue, I finally managed to successfully use the brass insert/machine screw combination to mount the SEAS hardware. Reader Rinaldo's solution is excellent and widely used by most speaker builders.—E.T.D.

Sure we have middlemen.  
FedEx & UPS, to name a couple.

www.AUDIOGON.com  
HIGH END AUDIO MARKETPLACE
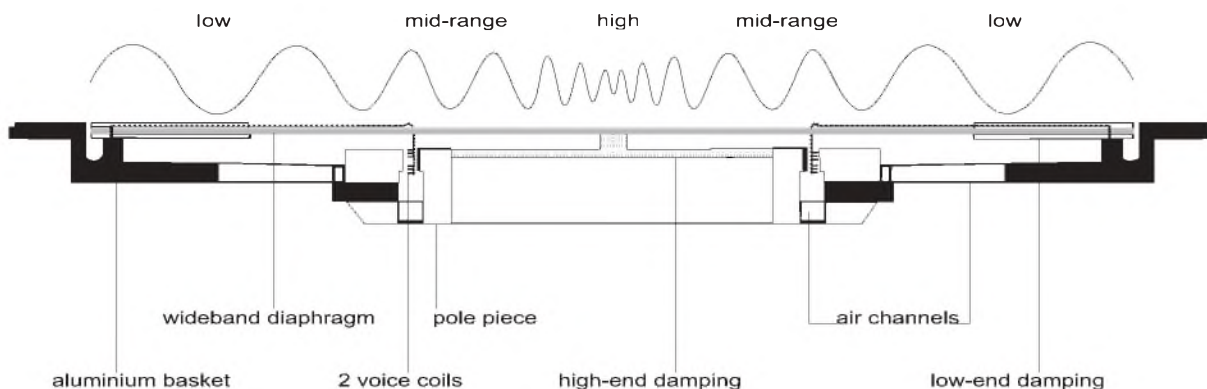
## MANGER Bending wave transducer "Natural accuracy"



E-Speakers.com

Los Angeles, California. 818 907-8942 / www.e-speakers.com

bottom of the base itself. The base is attached to the tower with four screws to the bottom side of the "corners," once

the filling material has been properly put in place. To allow the screws to firmly hold the base in place, the corners were made of 1.5" marine multi-layer wood instead of MDF.

Of course, the varnishing on the veneering took place just after the final assembly. I selected a walnut color to match the furniture of the house. Installing the speakers was the last step.

Finally, it was time to hook them up to my 90 lb 8 × EL34 25W power amplifier driven by a PST 200 pre-amp—both selfmade, vacuum tube tech—and listen to the splendid voice of Amanda McBrown on her LP direct disc recording. *audioXpress* experts have described the exceptional sound quality of THOR TL. They were right on. This is an outstanding piece of audio equipment. Audiophiles who do not have them or have not listened to them, do not know what they're missing.

Thanks, Joe, this is really a great project (*Photos 8 and 9*).

Atto Rinaldo  
Tambre, Italy

PHOTO 8: After all that work, an homage to Joe D'Appolito, "thumbs-up."



PHOTO 9: Final version of THOR with grille. On the left, a black version for a friend who fell in love with the sound.

## PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878  
Reno, NV 89510

[www.passdiy.com](http://www.passdiy.com)

### NEW INTEGRATED STEREO TUBE AMP KIT \$139.95\*



**ALL TUBE DESIGN RIVALS SOUND  
OF \$1000 HIGH END AMPLIFIERS**

**Power Output: 8 Watts per channel**

**Frequency Response: 20 10 20,000 Hz**

**Distortion: Less than 1% at 1 Watt**

**Input Impedance: 100K Ohms**

**Output Impedance: 8 Ohms**

**Minimum Input: 0.5 V for full output**

Uses type 11MS8 tubes included in kit with circuit board, base board and all parts, including transformers, power-cord, etc. and easy to follow assembly instructions.

• **Assembled and tested \$169.95.**

**Add \$10 for shipping and handling.**

**Order K-012M from:**

S-5 ELECTRONICS • 1625 TWIN ACRES

CHANDLER, AZ 85249

Phone: 480-895-2521 • Fax: 480-895-4164

[www.s5electronics.com](http://www.s5electronics.com)

# Xpress Mail

## DAVID HAFLER

David Hafler, 84, who devoted his life to perfecting home high-fidelity sound components, died in Philadelphia on May 25 of complications of Parkinson's disease. A life-long resident of the Philadelphia area, Mr. Hafler also owned homes in Boca Raton, Fla., and London. Naturally, all of his homes were filled with music from quality sound systems he designed, said his daughter Joan Cole. He didn't watch television, she added.

Born and raised in West Philadelphia, Mr. Hafler graduated from West Philadelphia High School in 1936, and received his degree in mathematics from the University of Pennsylvania in 1940. His life changed after the Japanese invaded Pearl Harbor. Mr. Hafler quickly married his high school sweetheart, Gertrude Schwinger, and he enlisted in the Coast Guard, which made him an officer.

Both were very good moves. The couple remained inseparable until her death in 2001. During the war, while serving as communications specialist in the Caribbean, Mr. Hafler was exposed to the notion that sound could be reproduced faithfully. After the war, Mr. Hafler worked for A.J. Wood, a market-research firm in Philadelphia, until his love for music spurred him to design easy-to-assemble electronic sound equipment for consumers.

In 1950, Mr. Hafler founded Acrosound in Roxborough, which built and sold audio transformers. It was his next venture, Dynaco, which he founded in 1954 in West Philadelphia, that set the standard for home music systems. Dynaco manufactured and sold amplifiers as build-it-yourself kits.

Mr. Hafler sold Dynaco to Tyco in 1968 and served as an adviser until 1971. One year later, he founded another company, David Hafler Co., manufacturer of inexpensive kits and preassembled hi-fi gear. Mr. Hafler sold the firm in the early 1990s to Rockford Corp. of Tempe, Ariz. In 1984, he was named to the Audio Hall of Fame. One of his products, the classic Dynaco Mk. II 50W amplifier,

was part of the media display in the Smithsonian's Museum of American History in Washington in the 1990s.

Another of Mr. Hafler's interests was collecting rare chess sets, which he was able to do because his business took him all over the world. Mr. Hafler's 240 beautiful and historic chess sets from across the globe were described by Sarah Coffin, specialist in chess collections and consultant to Sotheby's auction house in New York City, as "one of the finest collections of chess sets in the world." "The theme of my father's life was that if he couldn't be a top player, he could be a top manufacturer or collector," Cole said. "He loved music. But he couldn't play well enough to play professionally. So he manufactured the best sound equipment possible. He also loved to play chess, but he wasn't a world-class player. So he became a world-class collector."

In addition to his daughter Joan, Mr. Hafler is survived by daughter Diane Marinoff; a son, Eric; five grandchildren; and two great-grandsons.

*(Reprinted with permission from The Philadelphia Inquirer, by Gayle Ronan Sims.)*

## PHONO CARTRIDGES

My thanks to Ray Futrell for "doing the math" for the moving-magnet (MM) cartridges that most of us use to play LP records ("The LP Terminator," Jan '03 aX, p. 8). The most surprising result of Mr. Futrell's analysis is that following the manufacturer's recommendations in terminating the cartridge virtually guarantees sound that is shrill and unpleasant. This has been precisely my experience and explains why, for about 20 years, I have avoided moving-magnet cartridges altogether.

Because of its tendency to accentuate surface noise, the MM cartridge has been the largest contributor to the demise of the LP record. Mr. Futrell's research suggests that any MM cartridge (with the possible exception of the Grado and certain oddball car-

tridges from Stanton and GE) loaded with more than about 100pF of capacitance is going to have a peak in the high-frequency response that will grossly magnify this noise.

In practice, all installations will have more than 100pF worth of shunt capacitance. The lowest-capacitance interconnect cables I am aware of—solid-conductor steel-cored quadraphonic cables from the '70s—have a capacitance all by themselves of about 100pF. The question then arises, for whom were these cartridges designed?

As I recall, in the case of the Shure, the answer at the time was to manipulate the standard 47k termination resistance. Some authorities recommended dropping the input resistance by around 30–50% and adding shunt capacitance. This would produce a gradually rising hi-frequency response that could have been partially neutralized by the tone controls.

My first instinct was to question Mr. Futrell's results because they do not take into consideration the mechanical response of the cantilever, but I recalled a frequency-response measurement made in the '70s on my cartridge of the time, an ADC XLM, showing a 3dB peak around 19kHz. This suggests that the output, at least at the higher frequencies, is indeed dominated by electrical resonance.

This was far from an uncommon practice—millions of cassette decks resonated their playback heads in order to extend high-frequency response. The difference between the phono cartridge and the tape head is that the maximum frequency ever seen by a tape head is limited by its gap width; there is no such limit in a phono cartridge, and in fact, ultrasonic pulses are commonly generated by minute imperfections in the surface of the typical record. The cartridge, in response, rings like a Chinese gong, generating a pulse train every time it hits the tiniest piece of debris. This effectively stretches the width of the pulse, which is equivalent to lowering its frequency. I believe this is the mechanism responsible for accentuating the surface noise.



It is a mind-opening experience to play an LP record that has very high levels of surface noise with a cartridge employing a crystal or ceramic element. The quality of reproduction might not be very high, but the surface noise seems to vanish almost completely! Since the principal objection to the LP has been excessive surface noise, it appears that the venerable LP has been getting a bum rap.

To hell with frequency response! We need further study of the MM cartridge in the time, rather than the frequency, domain. This is largely unexplored ground. It may be possible to damp these resonances, or to raise them sufficiently so that they have negligible effect within the audio band by lowering the Q of the cartridge, fiddling with the load resistance, and/or further reducing the shunt capacitance of the typical installation. Perhaps some sort of magnetic rather than electrical damping would be more effective.

I have long used only moving-coil (MC) cartridges in my system. These cartridges have output well into the mid-ultrasonic range, but rarely cause serious problems because they are (or should be) heavily damped. The noise output is therefore directly proportional to the disturbance.

Resonance, in fact, is a dirty word to me. I find that even small amounts of ringing in my cartridge produces large amounts of glare, vagueness of image, loss of detail, and listener fatigue. Fortunately, ringing in moving-coil cartridges can be very effectively controlled by adjusting the load resistor.

In contrast to MM cartridges, the proper load resistance of MC cartridges has been very poorly specified, where it is specified at all. A case in point is the old Dynavector 10A. This high-output cartridge was designed to be a plug-in replacement for a MM unit, and so it was—as far as output voltage was concerned. The cartridge, when connected to the standard 47k resistance, had a nasty, spitty high-frequency response that could be completely tamed by dropping the load resistance to around 100Ω or so (I think). It became my favorite cartridge for years.

In general, the proper way to determine the load for an MC cartridge is to clip in a test resistor and listen to the re-

sults. The sound will become deeper, richer, and more refined as you lower the resistance until the image suddenly collapses. The optimum load is perhaps twice the value that causes the image to collapse. Not very scientific, but with only a little practice, you will be able to find the perfect load for any MC cartridge in a matter of minutes. Hope this helps.

Bob McIntyre  
Toledo, Ohio

Raymond Futrell responds:

*Thank you for the comments on the article. I was surprised after "doing the math" and did not believe the results at first. The calculated capacity values are what you would expect for an RF circuit, not an audio circuit. However, two other engineers couldn't find a mistake in the math, so that meant either Shure or the filter theory was wrong. The Leach preamp experiment clearly demonstrated the sonic benefits of low shunt capacity. Reduce the shunt capacity and hear the music.*

*Reducing the shunt capacity decreases the Q and increases the bandwidth,  $\omega_c$ , because*

# JFETS

ULTRA LOW NOISE  
LS843 - 3nV/Hz typ

TIGHT MATCHING  
LS843 - 1 mV max

- ◇ N & P Channel
- ◇ Duals & Singles
- ◇ Custom Screening
- ◇ Spice Model Library
- ◇ Die, SMT, Thru-Hole
- ◇ No Order Minimum

Second Source for Domestic  
& Foreign JFETS & Bipolars  
Full Service U.S. Manufacturer  
of Specialty Linear Products

## LINEAR SYSTEMS

4042 Clipper Court  
Fremont, CA 94538  
510-490-9160/510-353-0261 (Fax)  
E-mail: Sales@Linearsystems.com  
WWW.LINEARSYSTEMS.COM

**Supplier  
Of High  
Quality  
Speaker  
Kits &  
Components  
For The Audio  
Enthusiast**



**SELENIUM**  
LOUDSPEAKERS

vifa scan-speak

Cabasse

B&C SPEAKERS

ACCUTON

VERSA-TRONICS INC.

**AEON**

FOCAL

RAVEN

LEAP Components & Accessories

Pioneer

115 S. Victory Blvd.  
Burbank, CA 91502  
Vox 818-846-9921  
Fax 818-846-1009  
www.speakercity.com



**SPEAKER  
CITY U.S.A.**

McCaughey

Orders Only! 800-595-9924  
Mon-Sat 10am-6pm

**DYNASONIC** the dynamic

**Planar transducers combining**  
 → exceptional sound performance  
 → design challenges offered by **BIC**

**Info:** The Binary Interlaced Coil technology is based on a proprietary diaphragm (Patent pending) of two symmetrical coils of aluminium, printed one into each other on a very thin 12µ high temperature polyimide film, aligned within the dense field of a Neodymium magnetic structure. This double coil configuration, firstly gives the flexibility of use either in series connection for maximum sensitivity or in parallel for increased power capability. Secondly the **BIC** technology with its symmetry can inspire and motivate designers to a variety of applications:

- Direct Digital Loudspeaker
- Crossing over at two frequencies
- Push - Pull Circuitry
- Feedback Optimizing Circuitry
- Other inventive output circuitry such as
 

2 terminal network	4 terminal network
* single coil operation	* two winding transformer
* double coil series	* two winding autotransformer
	* two winding P-Pull

\*available after 05-31-2007

**DYNASONIC LTD** 59, 186 September st., Athens 114 33  
 Greece, www.dynasonic.gr, E-mail: info@dynasonic.gr  
 tel.: 0030-210-68 30 511, fax: 0030-210-82 29 403



**www.audiokits.com**

**build better audio™**

High-end audio kits,  
 enclosures,  
 and  
 DIY accessories  
 available online.

**FREE SHIPPING\***  
Continental US  
 ON  
**EVERYTHING**  
 WE SELL!

Want to know more?  
 Datasheets available  
 for download at

**audiokits.com**  
 Audiophile Euphoria™

\*Certain restrictions apply. See website for details.

Completed kits available. Contact us at 888-863-9482.

$\omega_0 = 1/\sqrt{LC}$  is increased. Reducing the load resistor isn't the best way to lower the Q because it reduces both the Q and the bandwidth,  $\omega_c$ . The rule of thumb is, reduce the capacity to lower Q, increase the resistance to raise Q.

Increasing the bandwidth also reduces pulse stretching, which is proportional to the rise time, which is related to the bandwidth by the formula  $T_r = 7/B$ . Narrower bandwidth means slower rise time, and a pulse is stretched by the addition of the rise and fall times. This may be why wide bandwidth MC cartridges are less affected by record surface imperfections.

There are several ways to reduce the shunt capacity. Minimize the wiring between the cartridge and the preamp input. Keep it short and simple. You can make interconnects out of high impedance (low capacity) coaxial cable. RG-62 has about 13pF/ft of capacity, so you can have a reasonable length of this cable.

A big source of shunt capacity is the Miller effect in the input stage of the preamp. It's reduced by the loop gain, which may be low at high frequencies. An input stage with low Miller effect, such as a cascode, is best. There's a simple capacity cancellation technique that you can use with a differential input stage to reduce Miller effect.

The electrical damping probably has no effect on mechanical resonance because of the weak magnetic coupling between the coils and stylus. Even so, it's still a good idea to damp the cartridge electrical resonant peak and eliminate that problem.

If most MC cartridges are highly overdamped electrically, it seems reasonable that increasing the terminating resistor for a Q of 5 to 7, which provides the flattest and widest frequency response, would also provide the best stereo image. The overdamped frequency response decreases monotonically and is never flat. Also, the lower the Q, the faster the response decreases. This means that a Q less than 5 peaks the low-frequency response, and a Q greater than 7.07 peaks the high-frequency response.

I had always noticed a grainy harshness on some LPs with excessive high-frequency content, especially on vocals. After reading the "LP Terminator" article by Raymond A. Futrell, I decided to run the numbers for my Grado Red to see what kind of load capacitance it required. I found that for a Q of .707 it needed about 100pF to terminate the 45mH inductance sourced by the cartridge.

Unfortunately, the measured capacitance on my phono patch cables is around 220pF. I didn't wish to change these custom-made cables that use twisted pair/braid shielded silver with Teflon dielectric (old Teledyne Thermodynamics instrumentation cable from Boeing Surplus), so I needed to do something else.

I found that lowering the load resistor from 47k to about 32k and running the numbers yields about 110pF load for a Q of .707. After installing the resistor I noticed a not-subtle improvement in the high frequencies. Gone was the grainy hash overlying vocals. Cymbals sounded more natural and transients were sharper, but not fatiguing like before.

In the past I had tried to remedy this by adding more capacitance! I can now see what this must have been doing to the signal by looking at the author's square-wave simulations. All that hash I was hearing was the ringing of the resonant circuit. Since there aren't many test LPs with square waves, I have no way to confirm this, but my ears tell me of great improvement! So, if you have no way of reducing the load capacitance, try lowering the load resistance, which worked for me.

**Kevin Elliot**  
 Elliot Studio Arts  
 Seattle, Wash.

Raymond A. Futrell responds.

Congratulations on solving your problem. With 45mH of cartridge inductance, even several hundred pF of shunt capacity would still result in a very high  $\omega_0$ . In that case, you can reduce the load resistor to reduce the Q. The cartridge electrical frequency response will still exceed the audio bandwidth. With a high inductance cartridge you can't do that. The shunt capacity must be very low or the bandwidth will be less than 20KHz.

Don't reduce the load resistor below about ten times the cartridge resistance. The load resistance and cartridge resistance forms a voltage divider (attenuator), which reduces the signal-to-noise ratio. Lost signal-to-noise ratio cannot be restored by subsequent amplification.

Thank you for printing Raymond Futrell's article "The LP Terminator"! I have long been a proponent of reducing the capacitive loading on modern car-

tridges to a minimal value (see [www.hagtech.com/loading.html](http://www.hagtech.com/loading.html)). It's great to see such confirmation in a respected audio journal. Kudos to Raymond for helping to dispel this myth.

When designing my phono stages, I went to great lengths to keep the input capacitance as low as possible. The tube stages are under 40pF and the op amp stage is under 15pF. These values are far lower than normal and greatly improve treble clarity and transparency. Even cheap cartridges sound surprisingly good with no shrillness.

**Jim Hagerman**  
Honolulu, Hawaii

*Raymond A. Futrell responds:*

*Thank you for the comments. I was unaware of your very informative white paper on the subject of phonograph cartridge loading. Your simulations of various cartridge types clearly show why the proper load is important, even for the low inductance cartridges. With a low input capacity phono preamp such as yours, even a high inductance cartridge can be properly loaded for a maximally flat bandwidth over 20kHz.*

*The proper cartridge loading also makes cheap records sound surprisingly good. I have a budget label record of Baroque music containing lots of brass, percussion, and strings. I initially thought the record had gross distortion. After correcting the cartridge load capacity, the record sounded quite good. Evidently, the restricted bandwidth, frequency peaking, and ringing was causing most of the distortion.*

#### MOSFETS AND BIPOLARS

**K** I thank Doug Self for his reply to my letter (Jan. '03 aX, p. 61) in regard to bipolar vs MOSFET output stages. It looks as though we'll continue to disagree, with Doug remaining in the bipolar camp and me remaining in the MOSFET camp. We both agree that each has its advantages and disadvantages. I must take some exception to a couple of points Doug made.

Doug suggested that the Type II output stage can provide greater turn-off current to the bipolar output transistor at times of high current output. I disagree. A simplified version of a 100W version of the Type II stage is depicted in *Fig. 1*, where Vb1 and Vb2 model the

It is not enough to put oil into a Capacitor to make it musical....

**KRISTALL  
CAP**



Forget about resistive devices for the volume setting. We offer a silver wired transformer approach

**Silver Rock  
Transformer-  
Potentiometer**



It is not enough to use silver wire for a good SE-OPT...

**Silver Rock  
Output transformer**



**There is only one optimum solution  
for a given problem.**

Audio Consulting / 14B chemin des Vignes / 1291 Commugny / Switzerland  
Fax: 00-41-22-960-12-59 / e-mail: [serge.schmidlin@span.ch](mailto:serge.schmidlin@span.ch)  
<http://www.audio-consulting.ch>

## AUDIO TRANSFORMERS

**AMERICA'S PREMIER COIL WINDER**

Engineering • Rewinding • Prototypes

**McINTOSH - MARANTZ - HARMAN-KARDON  
WESTERN ELECTRIC - TRIAD - ACROSOUND  
FISHER - CHICAGO - STANCOR - DYNACO  
LANGEVIN - PEERLESS - FENDER - MARSHALL  
ELECTROSTATIC SPEAKER TRANSFORMERS**

*Williamson Amplifier Transformer Specialist*

**WE DESIGN AND BUILD TRANSFORMERS  
FOR ANY POWER AMPLIFIER TUBE**

**PHONE: [414] 774-6625 FAX: [414] 774-4425**

**AUDIO TRANSFORMERS**

**185 NORTH 85th STREET**

**WAUWATOSA, WI 53226-4601**

**E-mail: [AUTRAN@AOL.com](mailto:AUTRAN@AOL.com)**

**NO CATALOG**

**CUSTOM WORK**

usual bias circuit. One advantage of this stage over the more conventional stage is that the driver emitter followers operate in Class-A—they are never supposed to turn off.

The voltages shown are for the quiescent condition, with 1.5V across R1, setting the driver standing current at 10mA. The current through R1 is the only current that is available to turn off an output transistor. By inspecting the circuit, you can see that the voltage across R1 will always be approximately 1.5V, regardless of the amount of current flow through R2 or R3 into the load, as long as neither Q1 nor Q2 goes into cut-off (which is not supposed to happen).

Consider the situation where 5A is being sourced into the load by Q3, and the circuit is trying to turn off Q3. Emitter resistor R2 will have a drop of 1.65V, but this will not cause an increase across R1. Indeed, it merely produces a greater reverse bias voltage across the already turned-off output transistor Q4. When the driver circuit is working properly in its linear region, R1 will always have about 1.5V across it, and the available turn-off current will only be 10mA.

Doug also stated that the approximate conjugate matching of the exponential Vbe characteristics of the upper and lower bipolar output transistors allows the selection of a bias current that nearly eliminates output stage “gain wobbles” through the crossover region as output current changes. This might be true were it not for the very necessary inclusion of the emitter ballast resistors R2 and R3, which effectively ruin this relationship. In other words, you can’t just “butt” these two characteristics together and be left with any thermal stability. The combination of the emitter’s dynamic characteristic and the series emitter resistor results in a conductance characteristic that increases with increasing current and then asymptotes to the value of the emitter resistance.

The dynamic source characteristic of a MOSFET behaves in almost the same

way: its conductance (gm) increases with increasing current and then asymptotes to the value of Rds-on. What counts in a properly-biased emitter-follower or source-follower output stage is the device transconductance versus current, not device transconductance versus base or gate voltage. The main difference between the bipolar and the MOSFET is that the MOSFET’s transconductance doesn’t approach that of a bipolar until its current is about ten times that of the bipolar. So if you bias the MOSFET output stage at about five to ten times that of a bipolar, you will get a very similar, and equally small, gain wobble through the crossover region. It will, however, be stretched out over a correspondingly larger range of output current swing.

In other words, the quasi Class-A overlap region of the MOSFET output stage is quite a bit larger than that of the bipolar. This is a good thing. It reduces the “suddenness” of the crossover gain wobble and results in softer, lower-order, crossover distortion components.

Of course, as I mentioned in my previous letter, the price to be paid for the MOSFET stage is the significantly higher idle power dissipation. A MOSFET output stage in a 100W amplifier with ±45V rails will dissipate about 45W when biased at 500mA.

It’s true that paralleled MOSFETs

need to be matched to a degree, but I have never found this difficult. Most of the MOSFETs in a batch tend to be like peas in a pod these days. Matching the devices to within 20 percent of current at the bias current value is more than adequate.

Perhaps the manufacturer Doug was referring to was trying to match the old-style Hitachi MOSFETs. It must have been a killer amp if they needed to put 16 devices in parallel! No paralleling of devices is needed for amplifiers up to about 100W at 8Ω. An IRFP240/IRFP9140 pair, at less than \$3 apiece, is plenty adequate for a 100W amplifier given reasonable heatsinking.

Bob Cordell  
Holmdel, N.J.

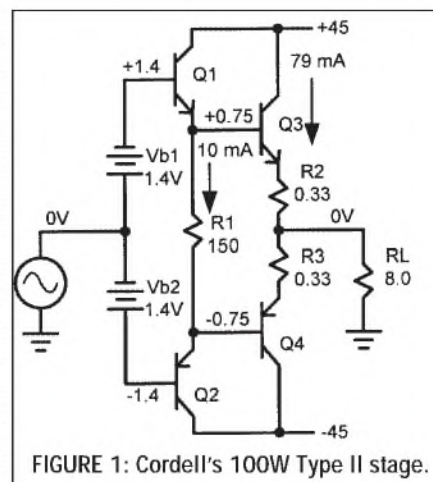


FIGURE 1: Cordell's 100W Type II stage.

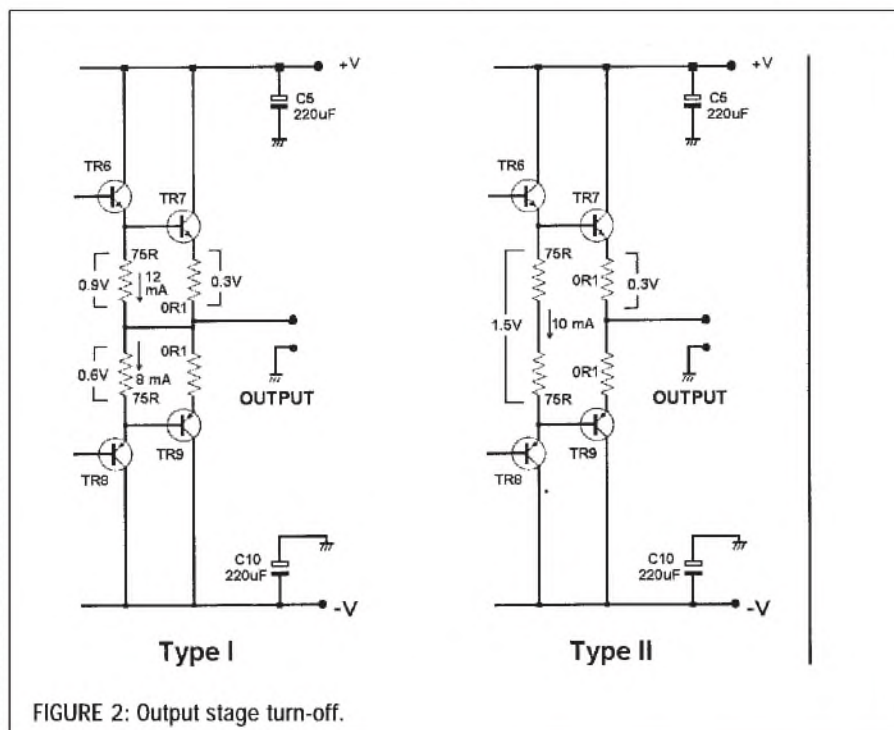


FIGURE 2: Output stage turn-off.

Going once. Going twice.  
Going directly to your house.

www.AUDIOGON.com  
HIGH END AUDIO MARKETPLACE

Douglas Self responds:

1. Turn-off in EF output stages. In the example Bob gives, the upper output device is sourcing 5A, so the lower output device is already well turned off, and the current available to turn it off more is not a very useful quantity. Figure 2 shows the situation in the two types of stage when the lower device is on the point of turning off. I have used the same bias conditions of 1.5V between the driver emitters, and all Vbe drops are assumed to be 0.6V. The driver emitter resistor is split into two 75R resistors for clarity.

In the Type II circuit there is always 1.5V across R1, so the current available for turn-off is always 10mA, as Bob says. However, in the Type I, the extra connection to the output rail means that the 1.5V is no longer equally split across the two 75R resistors. The bottom one can have only 0.6V across it at turn-off, reducing the turn-off current available to 8mA. This is the point I was making.

I would not dream of claiming that this 25% difference in turn-off current is the distinguishing feature between a good and a bad amplifier, or anything like that. In most cases the HF distortion will be composed mostly of crossover products. However, the Type II stage does, in my experience, give slightly lower HF distortion in the 10–20kHz region, by an amount that depends on transistor type and is not very designable. It does, of course, also save a resistor!

2. On FET vs bipolar crossover behavior, I think we do differ.

While I agree with most of what Bob writes, I part company when he says, "if you bias the MOSFET stage at about five to ten times that of a bipolar, you will get a very similar, and equally small, gain wobble through the crossover region." This is not my experience. Both in simulation and real life, I have found that FETs turn on much more abruptly, giving sharp gain changes through the crossover region; looking at the THD residual of mainstream FET amplifiers shows a lumpy residual that fits well with this view. The critical difference appears to be that FETs turn on with something like a square-law, whereas bipolars inherently turn on exponentially, and therefore conduction starts very gradually. Whether this applies to all varieties of FETs under all conditions, I would not like to say.

I quite agree that the more spread out the gain wobble the better, giving lower-order distortion products that are better linearized by negative-feedback. Spreading out the

wobble can be enhanced with bipolars by using low emitter-resistor values—OR1 seems to give quite adequate quiescent stability—or the simple expedient of putting more transistors in parallel. Both techniques increase the quiescent current, which smoothes out the gain wobble. I go into this in some detail in the third edition of the "Audio Power Amplifier Design Handbook" (available from Old Colony Sound Lab, 1-888-924-9465).

## HEATER SUPPLIES

I read with great interest Mark Kelly's article, "Direct Heaters: A Guided Tour." During the past few years I have constructed a couple of single-ended amps using direct heated triodes (DHT). Since the filaments of DHTs carry signal current, the quality of the heater power obviously is of great importance for the sound quality.

I have tried a few different types of regulated DC heater supplies, including some of those presented in the article, and the author confirms my experience. While I may not fully agree with him on the counter-productiveness of current-regulated heater supplies, I really appreciate his article and the experience he shares with us.

Unfortunately, one subject of great interest to me is not mentioned. Because the regulators presented in the article are designed to address differential-mode noise, they are normally ineffective against common-mode noise. Valves may not be very sensitive to differential-mode noise on their heater supplies, but they certainly are sensitive to common-mode noise. Indeed, a DHT filament is as sensitive to common-mode noise as is its grid.

My DHT amps are equipped with series voltage regulated DC heater supplies, but I have added common-mode filtering using series chokes and shunt capacitors. While the sonic results are very pleasing, I am still searching for a regulated heater supply eliminating common-mode noise.

One obvious solution is to try dual voltage regulators connected symmetrically with their ground legs acting "center-tap." This is easy for 2.5V and 10V filament tubes, since 1.25V and 5.0V regulators are readily available. High current regulators for other voltages require more effort and higher



ELECTRA-PRINT  
AUDIO CO.

### S.E. OUTPUT TRANSFORMERS

- \*Primaries to 10K
- \*Power up to 100 watts
- \*-1db 18hz to 40khz typical
- \*Custom designs available

### PUSH-PULL OUTPUTS

- \*Built for triodes
- \*Single output to load

### INTERSTAGE TRANSFORMERS

- \*Full bandwidth, up to 60ma

### LINE OUTPUTS

- \*Full bandwidth, up to 60ma

### POWER TRANSFORMERS

- \*Custom built to your requirements
- \*Power supply design advice

### CHOKES/FILTER and AUDIO

- \*Standard and custom HV filter chokes
- \*High current filament chokes
- \*High inductance audio plate chokes

specification and pricing catalog available  
Visa, MC and Amex

ELECTRA-PRINT AUDIO CO.  
4117 ROXANNE DR., LAS VEGAS, NV 89108  
702-396-4909 FAX 702-396-4910  
EMAIL electraaudio@aol.com

# auricap



**World's finest capacitor,  
Sonically transparent,  
Superior technical  
specifications.**

- Auricap is the best I have tried by a long, long way. Kendrick Power/VP Melbourne Audio Club
- Auricaps are great parts, and represent a significant step forward in capacitor technology and audio-musical performance... Better and cheaper. What more can you ask for? Jamie White-Wolf Cook, Sr. Technical Editor - Positive Feedback Magazine
- If you want absolute transparency, then you must give Auricaps a try. Giorgio Pozzati/INAudio.com

OEM & dealer inquiries invited.  
Call (800) 565-4390  
www.audience-av.com

parts counts, however. The sonic results are excellent.

One other, more direct, solution is to use separate heater supply transformers, with electrostatic screening between their windings, which would stop the noise right at the source. Such transformers seem not very easy to find, though.

I would appreciate it very much if Mark Kelly would share his experience on the importance of common-mode noise rejection in valve heater supplies.

Lennart Jarlevang  
Gothenburg, Sweden

Mark Kelly responds.

Mr. Jarlevang's letter touches on the issue of constant-current sources (CCS), and I have

changed my views on this subject since writing the original article, so I will address this first and then talk about the issues raised in the letter. While I still think that voltage rather than current should be the primary control parameter for v/T heaters—and I still like shunt voltage regulators—I now favor feeding the shunt regulator from a constant-current source. The CCS can be either of the two circuits shown in the article. I have also abandoned the use of the LM431 shunt regulator IC in favor of discrete regulation (Fig. 1)

I agree that common-mode noise is an issue with DHT heaters, but I disagree that his scheme with dual regulators is an effective cure. First, assume that out differential mode regulation is close to an AC shunt between the +ve and -ve heater supplies. In the case of fixed bias v/Ts, one side of the heater supply is grounded, so any common-mode noise must by definition appear on both the +ve and earth line. Noise on the earth line is a grounding issue. With the dual regulation scheme the center point of the regulators is still the earth return, so if the earth line is noisy there would appear to be little advantage.

In the case of cathode biased v/Ts, the heater supply is assumed to be floating, and

common-mode noise is an issue due to the relatively high impedance to ground of the cathode bypass capacitor. In this case the dual regulators are also ineffectual in that they must be referenced to each other, the ground reference for AC is still the cathode bypass capacitor as before

In my experience the best solution to common-mode noise problems is battery supply. I am about to implement this for my 211 heaters (requiring 90 odd kg (200 lb) of batteries) I'll keep you posted how it goes

## HELP WANTED

I am trying to find small PCB mount toroid transformers for some projects. I

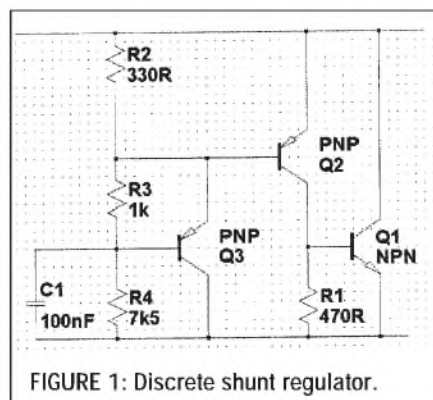


FIGURE 1: Discrete shunt regulator.

Sure, we're an audio center.  
Center of the universe, that is.

www.AUDIOGON.com  
HIGH END AUDIO MARKETPLACE

## Now choose your test microphone when you buy CLIOWin Lite!

CLIOWin Lite is the latest version of the measurement software for the CLIOLite system. Along with the new PCI card version of the PC board and the addition of the Sound Conditioner hardware, this new version is more powerful and flexible, still at an unbeatable price!

To order call 1-888-924-9465 or visit [www.audioXpress.com](http://www.audioXpress.com)!

The system is available with either the calibrated CLIOMIC-01 Lite or the calibrated Mitey Mike II.

Generator & Millivoltmeter  
C & L Meter  
Dual Channel Oscilloscope  
Sinusoidal Response  
Impedance  
Thiele/Small Parameters

Distortion vs. Frequency  
MLS Analysis  
Impulse Response  
Energy Time Curve (ETC)  
1/3 Octave Analysis



Shipping Wt: 6 lbs.

CLIOWin Lite with PCI card, Signal Conditioner and CLIOMIC-01  
KC-CLIOPCIM.....\$699.00

CLIOWin Lite with PCI card, Signal Conditioner, and Mitey Mike II  
KC-CLIOPCIMM.....\$749.00



Old Colony Sound Laboratory, PO Box 876,  
Peterborough, NH 03458-0876 USA  
Phone: 603-924-9464 Fax: 603-924-9467  
E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)

noticed in the Sept. 2002 issue ("DASP 2002," p. 4) there was a small toroid. Is there a company that makes those? What are the specs (gauss, pri/sec V, amp), in case I need to make one?

Greg Morgan  
gemorga@qwest.com

Edward T. Dell responds:

I do not know of a company that provides small toroidal transformers, but some reader may know of such. We have included your e-mail address and ask such readers to let you know. I suspect that such devices fall into the category of custom production. Many companies supply the cores, although I have not checked the US catalogs. The article you cite from our September issue does give adequate instructions for building this particular device, including the part number for the ferrite core from Ferroxcube. I fail to see how, with the correct cores and following the turns count in the parts list, you could go wrong in winding this device yourself.

I saw a review of what looked to be an interesting unit—so interesting that I'd like to find out where to buy one—in a British magazine *HIFI Plus*. It was called the DYNAVECTOR Super Stereo. It seems to be a processor and amp for driving two speakers placed along the side walls in front of the listener and aimed to bounce their direct sound (sort of like a BOSE 901) off the wall behind the front speakers.

The reviewer said that the unit did indeed improve the sound of regular two-channel music, and, while it didn't really produce a home theater surround sound effect with multichannel recordings, it did give an enjoyable sound field—more so than straight stereo without the Dynavector unit. Are any of your readers familiar with this?

Ray Putnam  
putnamrj@juno.com

I am writing from Italy asking for help with a couple of panel loudspeakers that I used for my home hi-fi system years ago. They are Strathern panel loudspeakers, and now I need to replace the sound-absorbent foam in the back of the panels. It is becoming worse and worse, ruined because of the dry air in my

house. I contacted the dealer where I bought the loudspeakers and he said the Strathern factory is closed. Do you know whether this is true, and if so, how I can find a substitute?

Massimo Giuliani  
m.giuliacchi@virgilio.it

Let's hope someone knows of a source for replacement foam for your drivers. Foam generally has a relatively short life both as damping panels or driver surrounds. I would also suggest you look for vendors of insulation material and try various alternatives. Rolls of sheet foam are not usually very expensive, and if you can find a similar thickness, it might be an approximate answer. Modify only one of the drivers and compare sound with the new material to the old.—Ed.

Readers with information on these topics are encouraged to respond directly to the letter writers at the addresses provided.—Eds

## Ready, willing and A VEL



offering an extensive  
range of ready-to-go  
**toroidal transformers**  
to please the ear, but won't  
take you for a ride.

 **Avel Lindberg Inc.**  
47 South End Plaza  
New Milford, CT 06776  
tel: 860-355-4711  
fax: 860-354-8597  
[www.avellindberg.com](http://www.avellindberg.com)

## The British specialists in tube amplifiers and pre-amplifier kits, loudspeaker kits and related publications

Visit our informative website:  
[www.worldaudiodesign.co.uk](http://www.worldaudiodesign.co.uk)  
Enter our HD83 competition on-line



KIT88 integrated amplifier kit



300b PSE monobloc kit



Kel84 integrated amplifier kit



Series II modular pre-amplifier kit

 **World Audio design**

**World Audio Publishing Ltd.**  
12a Spring Gardens.  
Newport Pagnell.  
Milton Keynes.  
MK16 0EE. England

tel/fax: 00 44 1908 218836  
e-mail: [inquiries@worldaudiodesign.co.uk](mailto:inquiries@worldaudiodesign.co.uk)

# Classifieds

## VENDORS

**American Science & Surplus.** Audio, electronic and mechanical components, connectors, wiring, kits, magnets, speakers, tools, hardware, and more! Call for a free catalog: 847-647-0011 or shop [www.sciplus.com](http://www.sciplus.com).

**Principles of Power,** tube audio books, kits, FAQ [www.londonpower.com](http://www.londonpower.com).



**gear racks, media drawers and more**  
Factory direct since 1984  
Free literature (includes audioXpress)  
For Master Designs (800) 421-4883  
[www.rackit.com](http://www.rackit.com)

tubes?  
[www.tubes.it](http://www.tubes.it)

Want the best price/performance kitset audiophile amp on the planet? Need service too? Can't be done? Visit:  
[www.aksaonline.com](http://www.aksaonline.com)



[www.kleintechs.com](http://www.kleintechs.com)  
**ACOUSTIC INTERFACE PADS**  
COMPOSED OF SPACE-AGE POLYMERS  
Improve sound clarity, localize and expand tonal range. Isolate, reduce, and dampen cabinet distortion and vibration. Secure objects and furniture for stability. Eliminate the need for spikes, cushions, mats, floorings and affects any speaker in any kind of surface. Great for center channel speakers. He, wood, and Indium floors. Stops vibration between discs, CD transports. Dealers encouraged!  
p. 901-599-2750 E. 901-422-6228 or [support@kleintechs.com](mailto:support@kleintechs.com)



**Precision Port™**  
Be Different - Sound Better  
CLEANER SOUND  
LESS DISTORTION  
EASY INSTALLATION  
GREATER SOUND PRESSURE LEVELS  
DESIGNED AND MADE IN THE USA  
**Precision Sound Products, Inc.**  
Phone: 815-599-0662  
Fax: 309-279-0359 [www.psp-inc.com](http://www.psp-inc.com)

**Circuit Boards** for Projects, Prototypes or small quantities. From your artwork. Low Rates. No minimum. **Atlas Circuits** 704-735-3943. E-mail: [Atlas@conninc.com](mailto:Atlas@conninc.com)

**WWW.AUDIOELECTRONICSUPPLY.COM**—We are your supply source for all electronic parts—tubes, transformers, capacitors, potentiometers, connectors, and so on, as well as DIY kits and assembled products. Call (919) 355-0014 or e-mail us at [info@audioelectronicsupply.com](mailto:info@audioelectronicsupply.com).


Integrated amp, Headphone amp  
**www.borbelyaudio.com**  
Borbely Audio kits in USA:  
[www.audiokit.com](http://www.audiokit.com)

**www.classifiedaudio.com**  
High end audio.  
Buy it. Sell it. Revel in it.



**Welborne Labs**  
The largest selection of tubes, audio kits, and parts.  
It's all online at  
<http://www.welbornelabs.com>

**FINAL LABORATORY**  
Factory precision amplifiers - custom diameter cables  
DARUMA isolation bearings  
Imported by Venus HI-FI  
[www.venus-hifi.com](http://www.venus-hifi.com)

**THORENS**  
The New Generation  
TD800 Series  
  
See all the new products at  
[www.thorens.com](http://www.thorens.com)  
Distributed by:  
Triam Electronics 608-850-3600 or [www.triamcorp.com](http://www.triamcorp.com)

**FINALLY AFFORDABLE** **\$10 SET OF 4 PLUS FREE SHIPPING** (Continental USA)  
**SILVER PLATED SPADE LUGS**  
All direct plating, no nickel flash. 4/9's pure copper. Designed for 1/4"-5/16" posts and up to 10g wire. Can be crimped and soldered. Also available in gold and bare.  
Email orders only please: [luminous@cavtel.net](mailto:luminous@cavtel.net)  
**LUMINOUS AUDIO TECHNOLOGY**  
High-end cables since '92'  
[www.luminousaudio.com](http://www.luminousaudio.com)

**CERAMIC CABINET** loudspeakers. A sonic revelation! Visit: [www.faradaysound.co.uk](http://www.faradaysound.co.uk)  
Comprehensive DIY information booklet \$15

Low cost PCB layout and electronics design service <http://inyxsolutions.netfirms.com/home.htm>

**Repairs and upgrades for audio equipment.** Let longtime aX contributor and VTV senior editor **Eric Barbour** make your system sound better.  
**METASONIX**, PMB 109, 881 11th St., Lakeport, CA 95453, [synth@metasonix.com](mailto:synth@metasonix.com), (707) 263-5343.

**Sonic Craft** is your high-end speaker source! Accuton, AudioCap, Axon, Alpha-Core, Black-hole 5, Cardas, Goertz, Mills, Sonicap, and kits are on the way! Call 940-689-9800, or see [www.soniccraft.com](http://www.soniccraft.com)

Mic and phono preamps, meters, filters, etc. all US built TDL Technology, Inc. 505-382-3173

**FOR SALE**  
Vishay s102k series super duper quality audio resistors. 33 different values. \$3.00 each. [archaicaudio@webtv.net](mailto:archaicaudio@webtv.net)

**SERVICES**  
**GOT IDEAS? PROTECT NOW, PROFIT LATER!** "PROVISIONAL-PATENT-PENDING" PROTECTION from \$49.99. 1-888-58-PATENT [www.BayAreaIP.com](http://www.BayAreaIP.com) for **FREE INFORMATION.**

**We Want Your Feedback!**  
*audioXpress* encourages reader feedback in the form of letters, queries, and comments.  
Send correspondence to:  
**audioXPRESS**  
Editorial Dept.  
PO Box 876  
Peterborough, NH · 03458-0876  
Phone: (603) 924-9464  
Fax: (603) 924-9467  
Website: [www.audioXpress.com](http://www.audioXpress.com)  
E-mail: [editorial@audioXpress.com](mailto:editorial@audioXpress.com)  
*audioXpress* reserves the right to edit letters for length and clarity. Letters should be brief and to the point.



# Yard Sale

## FOR SALE

Back issues—twenty years of *Audio Amateur*, *Speaker Builder*, *Audio*, *Stereophile*, *Stereo Review*, and *Absolute Sound*, Vols. 1–4. Will trade for amp/preamp. No singles or selected years for sale. FAX Lloyd Street (510) 638-1796 or leave message at (510) 638-1795 between 1:00–3:00PM, California time.

Audiomatica CLIOWIN PC acoustical measurement system with HR-2000 ISA PCB, \$400, eab008@mot.com.

Electronics beginners! Get the book that is easy to read and understand. Go to amazon.com or bn.com, then select Books, search author name "Shanefield," and click on the 5-star Customer Reviews.

### Yard Sale Guidelines

For information on how you can publish your free personal ad in *audioXpress*, visit our website at [www.audioXpress.com](http://www.audioXpress.com).

### Classified Information

To find out how you can order an ad for the classified pages, see our website at [www.audioXpress.com](http://www.audioXpress.com).

## PTFE Insulated Twist-eye Terminal Strips



**Made from the finest materials.**

Lightly tinned 14 gauge OFHC Copper twist-eyes made and inserted by hand into 1/2" virgin PTFE stock.

Perfectly sized for larger audiophile grade components.

Complete with mounting holes and available with 1 to 6 terminals per strip.



[www.grennanaudio.com](http://www.grennanaudio.com)

PMB 302, 8825 W. Olympic Blvd.  
Beverly Hills, CA 90211


## AD INDEX

ADVERTISER	PAGE	ADVERTISER	PAGE	ADVERTISER	PAGE
ACO Pacific Inc .....	41	George Fathauer & Associates .....	61	WBT-USA/Kimber Kable .....	4,5
Adire Audio .....	47	Grennan Audio .....	71	Welborne Labs .....	45
All Electronics .....	51	Hammond Manufacturing .....	1	World Audio Design.....	69
Antique Radio Classified .....	45	Harris Technologies .....	25	Zalytron Industries.....	57
Audience .....	67	Hi Fi Do Inc .....	37		
Audio Amateur Corp.		Int'l Components .....	17	<b>CLASSIFIEDS</b>	
Cliolite .....	68	JENA Labs .....	53	American Science & Surplus.....	70
Matter of Coincidence .....	18	K&K Audio .....	27	Aspen Amplifiers .....	70
Classifieds .....	70	KAB Electro-Acoustics .....	25	Atlas Circuits .....	70
HiFi News Test LP.....	44	Kimber Kable/WBT-USA .....	4,5	Audio Electronic Supply .....	70
<i>Loudspeaker Design Cookbook</i> .....	24	Langrex Supplies.....	19	Bay Area Intellectual group .....	70
<i>World Tube Directory</i>		LC Audio Technology ApS .....	9	Borbely Audio .....	70
advertising opportunites .....	26	Liberty Instruments .....	43	Classified Audio-Video .....	70
Audio Consulting .....	65	Linear Integrated Systems .....	63	Faraday Sound .....	70
Audio Electronic Supply .....	19	Madisound Speakers.....	29	Inyx Solutions .....	70
Audio Transformers .....	65	Marchand Electronics .....	59	Klein Tech Systems.....	70
audioasylum.com .....	31	Origin Live .....	35	Luminous Audio Technology.....	70
Audiogon.com .....	18,44,60,66,68	Parts Connexion .....	39	London Power .....	70
Avel Lindberg Inc.....	69	Parts Express Int'l., Inc. ....	CV4	Metasonix .....	70
Cascade Audio .....	23	Pass Laboratories .....	61	Per Madsen Design.....	70
Chelmer Valve .....	15	Plitron Manufacturing .....	54	Precision Sound Products.....	70
Classified Audio-Video .....	64	Selectronics .....	27	Sonic Craft.....	70
Diamond Groove .....	56	Sencore .....	21	TDL Technology .....	70
Dynasonic Ltd .....	64	Solen, Inc. ....	CV3	Thorens of America .....	70
E-Speakers .....	60	Speaker City USA .....	63	Venus HiFi.....	70
EIFL.....	13	Swans Speakers .....	7	Vintage Hi-Fi .....	70
Electra-Print Audio .....	67	The Last Factory .....	59	Vernon Vogt .....	70
Electus Distribution Pty Ltd .....	47	Thetubestore.com .....	55	Welborne Labs .....	70
Exact Power .....	11	Usher Audio .....	CV2		

# New Chips on the Block

## AKM AK4395 and AK4552 Codec

By Charles Hansen

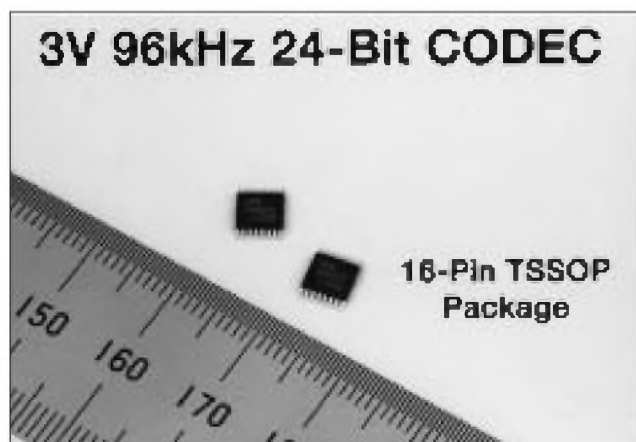

### AKM AK4395

AKM has introduced the AK4395 high-performance digital filter 192kHz 24-bit DAC, aimed at high-end audio systems, including DVD/DVD-audio players, AV amplifiers, and professional audio products. The 28-pin VSOP pin package is pin compatible with the earlier AK4393 and AK4394, to allow easy upgrading for improved performance. The AK4395 adds a 127dB attenuator with 0.5dB resolution, improved 8× digital filter, and lower passband ripple and stopband attenuation.

The analog section provides differential outputs that can drive an AC-coupled 600Ω balanced, or 1kΩ DC-coupled load to +20dBm. A simple balanced low-pass filter is all that is needed to complete a pro-audio interface. The soft mute ramps in 1024 samples between 0dB and full mute for source switching without interruption.

#### Key AK4395 features:

- 128× oversampling: 16-, 20-, and 24-bit audio
- Sampling rate up to 192kHz
- High-performance 24 bit 8× digital filter (slow rolloff option)
- Ripple: 0.0002dB, attenuation: 110dB
- High tolerance to clock jitter using switched capacitor (SC) technology
- Low distortion differential output
- Digital de-emphasis for 32, 44.1, and 48kHz sampling

72 audioXpress 8/03

Channel independent digital volume with soft-transition

Soft mute

THD+N: -100dB

DR, S/N: 120dB

I/F format: MSB justified, 16/20/24 bit LSB justified, I<sup>2</sup>S

Master Clock:

Normal speed: 256fs, 384fs, 512fs, or 768fs

Double speed: 128fs, 192fs, 256fs, or 384fs

Quad speed: 128fs or 192fs

Power supply: 5V DC

TTL level digital I/F

Small package: 28-pin VSOP pin-compatible with AK4393/4

AK4395 pricing \$6.62 US (1k pieces)

### AKM AK4552 CODEC

The AKM AK4552 stereo codec gives designers 96kHz, 24-bit resolution in an ultra-small 16-pin TSSOP package. The device is designed to enhance the performance of portable audio products, electronic musical instruments, and car audio systems, with its wide temperature range of -40 to +85°C, and a combined power consumption of only 60mW for the A/D and DAC.

HPF for DC-offset cancel

Single-ended ADC

• S/(N+D): 89dB @ VA = 3.0V

• Dynamic range, S/N: 97dB @ VA = 3.0V

Single-ended DAC

• Digital de-emphasis for 32kHz, 44.1kHz, and 48kHz sampling

• S/(N+D): 90dB @ VA = 3.0V

• Dynamic range, S/N: 100dB @ VA = 3.0V

Audio I/F format: MSB first, twos complement

• ADC: 24-bit MSB justified, DAC: 24-bit LSB justified

Sampling rate:

• 8kHz to 50kHz (normal speed)

• 50kHz to 100kHz (double speed, double speed monitor)

• 100kHz to 200kHz (quad speed monitor)

Master clock:

256fs, 384fs, 512fs @ normal speed

256fs or 384fs @ double speed

128fs or 192fs @ double speed monitor

64fs, 96fs, 128fs, or 192fs @ quad speed monitor

Power supply: 2.4 to 4.0V

Power dissipation: 42mA

Tamb = -40 to 85°C

Very small package: 16-pin TSSOP

AK4552 pricing \$2.99 US (10k pieces)

AKM Semiconductor, contact Richard Kulavik toll-free at 888-256-7364, or [icinfo@akm.com](mailto:icinfo@akm.com) for info and engineering samples. ♦