

**SPEAKER CABLES: YOUR LIFELINE TO GOOD SOUND**

# audio **X**PRESS

THE AUDIO TECHNOLOGY AUTHORITY

MAY 2004

US \$7.00 Canada \$10.00

Celebrating **35** Years

## Customize your PC with an Internal Amp




### SUPER SYMMETRY:

### Try this Zen Feedback Technique
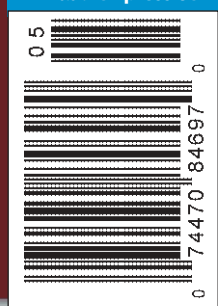
## HOW TO Beat THE High Cost OF Tube Sockets



[www.audioXpress.com](http://www.audioXpress.com)



### Subs and the City: Designing with 8" Drivers



# The performance of SoundString cables brings pure sound direct to you.

As the inventors of Soundstring patented power, speaker and interconnect cables we understand... it's all about the music. With over a century of manufacturing experience we engineered and designed cables with one goal in mind, make your sound system the best it can be.



But don't take our word for it, visit [soundstringcable.com](http://soundstringcable.com) and see what the experts say. Treat your system to the 'Soundstring Connection' and hear the magic.

*Soundstring*  
CABLE TECHNOLOGIES™

*FOR THE PUREST*

SoundString Cable Technologies, LLC  
203-853-9300 Fax 203-853-9304  
[www.soundstringcable.com](http://www.soundstringcable.com)



**NEW !!**

**DH LABS**

**SILVER SONIC™**

HIGH PERFORMANCE AUDIO CABLES


# The Ultimate RCA Connector

## DH Labs "High Copper Alloy"

Virtually all of the RCA Connectors used by today's top cable manufacturers are made from brass. There are a number of different brass alloys, generally featuring a combination of copper (around 60%) and varying amounts of zinc, lead, and even tin. The presence of these other metals greatly reduces the manufacturing cost and conductivity of the resulting alloy.

The conductivity of brass alloys is only about 26% that of pure copper. This loss (almost 75%), directly affects the performance of a terminated cable.

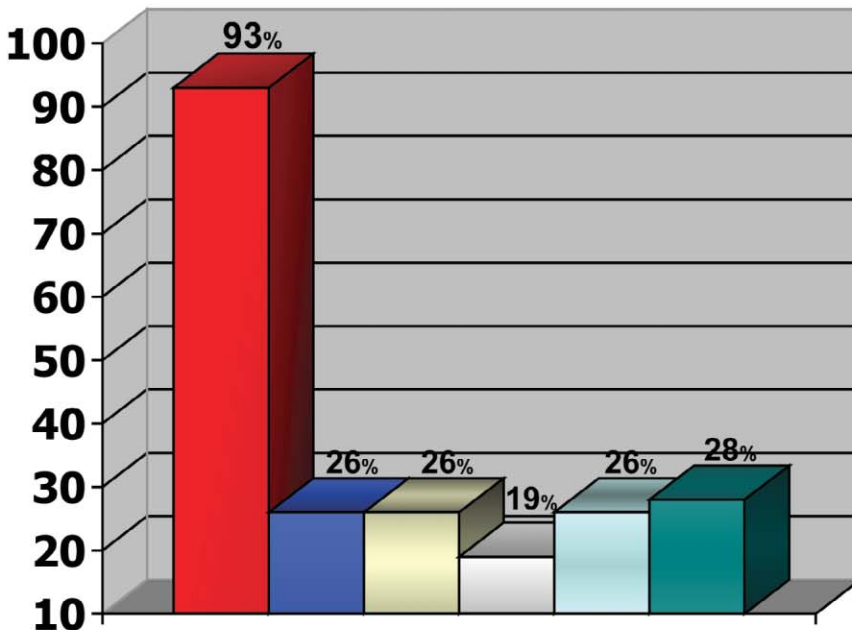Our exclusive **"High Copper Alloy"™** material is sourced from the **U.S.A.** for purity, and composed of more than 99% pure copper. Simply stated, this is the finest connector anyone has ever made....



**Electrical Conductivity (%IACS)**

■	<b>DH LABS HC ALLOY -</b>
	<b>Copper Content - 99.3%</b>
■	<b>WBT 101 TOP LINE -</b>
	<b>Copper Content - 68%*</b>
■	<b>VAMPIRE 807 -</b>
	<b>Copper Content - 63%**</b>
■	<b>VAMPIRE 800C -</b>
	<b>Copper Content - 88%**</b>
■	<b>CARDAS SRCA -</b>
	<b>Copper Content - 62%**</b>
■	<b>WBT 147 MID LINE -</b>
	<b>Copper Content - 52%*</b>

\*Taken from manufacturer's published data  
\*\*Determined by Certified Chemical Analysis

**DH LABS**

612 N. Orange Ave. #A-2  
Jupiter, FL 33458

(561) 745-6406

[www.silversonic.com](http://www.silversonic.com)

HC Alloy is a trademark of DH Labs, Inc.

# Over the Top

Music performance and craftsmanship that exceed your expectation in every way

## Compass DANCER SERIES

### Compass DANCER SERIES DESIGN HIGHLIGHTS:

- Carbon-paper woofer cone
- Silk-fabric soft dome tweeter; Ceramic type on some models
- Innovative magnet flux design with corrective cooper elements on all drivers, resulting in significantly reduced third and second harmonic distortions
- Cast aluminum driver frame
- Hand picked, matched-pair drivers on all models
- Phase coherent crossover designed by world renown master of speaker design, built with components of the highest quality and thoroughly tested with digital-based measuring equipment
- Massive, sonically dead front baffle which places drivers in a time-coherent physical arrangement
- Multi-chamber reinforced cabinet with solid wood side panels, handcrafted to the highest furniture grade

### Behind the Scene

Dr. Joseph D'Appolito has been working as consultant for Usher Audio since early 2000. A world renown authority in audio and acoustics, Dr. D'Appolito holds BEE, SMEE, EE and Ph.D. degrees from RPI, MIT and the University of Massachusetts, and has published over 30 journal and conference papers. His most popular and influential brain child, however, has to be the MTM loudspeaker geometry, commonly known as the "D'Appolito Configuration," which is now used by dozens of manufacturers throughout Europe and North America.

Dr. D'Appolito designs crossover, specifies cabinet design, and tests prototype drivers for Usher Audio, all from his private lab in Boulder, Colorado. Although consulting to a couple of other companies, Dr. D'Appolito especially enjoys working with Usher Audio and always finds the tremendous value Usher Audio products represent a delightful surprise in today's High End audio world.

With an abundance of original concepts in loudspeaker design, backed by thirty years experience in manufacturing and matched with an eye for fashion and unparalleled attention to detail, is USHER the ideal original design manufacturer you've always been looking for? Find out the answer today by talking to an USHER representative.

## USHER

USHER AUDIO TECHNOLOGY

67, Kai-Fong Street, Sec.1, Taipei 100, Taiwan

Tel: 886 2 23816299 Fax: 886 2 23711053

Web site: [www.usheraudio.com](http://www.usheraudio.com) E-mail: [usher@ms11.hinet.net](mailto:usher@ms11.hinet.net)



### FEATURES

#### ZEN VARIATIONS 6: SON OF ZEN GETS XPLOITED

Try this Super-Symmetry (aka X circuit) technique on simple circuits for high performance and noise/distortion cancellation.

By Nelson Pass ..... 8

#### TUBE AUDIO CONSTRUCTION TIPS, PT. 2: SOCKETS

To beat the high cost of tube sockets, follow these handy DIY tips.

By Graham Dicker and Jim Tregellas ..... 14

#### VENTED 8" DRIVER SUBWOOFER, PT. 1

Without breaking your lease, you can enjoy full-bodied musical pleasure with these "apartment" speakers.

By G. R. Koonce and R. O. Wright, Jr. .... 18

#### A BOTTOM OCTAVE COMPENSATOR

Use this simple circuit in a sealed woofer box to accurately extend low-frequency response.

By Dennis Colin ..... 28

#### BUILD A UNIVERSAL PC SOUND AMPLIFIER

This audio veteran from Hungary shows how you can add even more flexibility to your computer setup with this amplifier connection.

By Jenő Keceli ..... 36

#### MINIMAL REACTANCE POWER SUPPLY

For your next audio project, build this power supply and enjoy the clean, sonic results.


By David Davenport ..... 46

### REVIEWS


#### SPEAKER CABLES

Our pair of expert reviewers puts the cables from the leading manufacturers through their paces.

Reviewed by Charles Hansen and Muse Kastanovich ..... 52

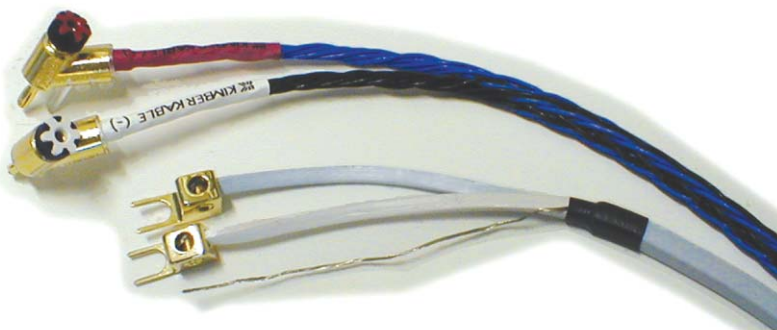

page 52

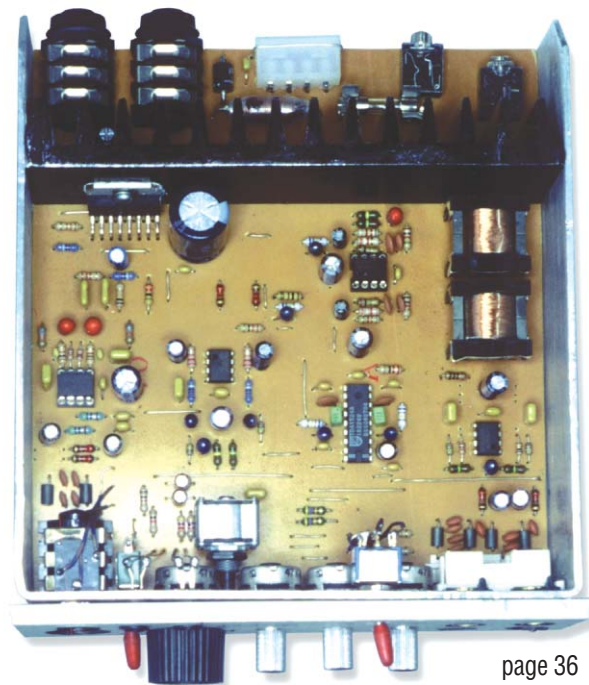

page 36





page 14

## DEPARTMENTS

### OBITUARY


Remembering Ken Wilkinson  
By Reg Williamson ..... 4

### XPRESS MAIL

Readers speak out ..... 63

### AUDIO AID

BNC Jack Positioner  
By Charles Hansen ..... 72

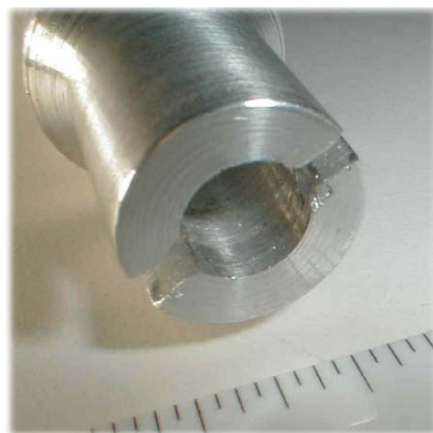

page 72

## IN EVERY ISSUE

### CLASSIFIEDS

Audio-related items for sale or wanted ..... 70

AD INDEX ..... 71

### YARD SALE

Free classifieds for subscribers ..... 71

page 28



## THE STAFF

Editor and Publisher  
Edward T. Dell, Jr.

Regular Contributors

Eric Barbour	Erno Borbely
Joseph D'Appolito	Richard Campbell
Bill Fitzmaurice	Vance Dickason
Charles Hansen	Gary Galo
James Moriyasu	G.R. Koonce
Richard Pierce	Nelson Pass
Reg Williamson	

Vice President  
Karen Hebert

Dennis Brisson	Assistant Publisher
Amity Palmer	Editorial Assistant
Richard Surrette	Editorial Assistant
Tina Hoppock	Graphics Director
Ben Leece	Production Assistant
Laurel Humphrey	Marketing Director
Lora Cunningham	Marketing Assistant
Kelly Bennett	Customer Service
Sharon McClair	Customer Service

### Advertising Department

Strategic Media Marketing  
1187 Washington St.  
Gloucester, MA 01930

### Peter Wostrel

Phone: 978-281-7708  
Fax: 978-283-4372  
E-mail: peter@smmarketing.us

### Nancy Vernazzaro

Advertising/Account Coordinator

*The peculiar evil of  
silencing the expression  
of an opinion is, that it is  
robbing the human race;  
posterity as well as the  
existing generation; those  
who dissent from the  
opinion, still more than  
those who hold it.*

JOHN STUART MILL

**CODE** Articles and letters identified with the following symbols:



solid state



tubes



speakers

### LEGAL NOTICE

Each design published in *audioXpress* is the intellectual property of its author and is offered to readers for their personal use only. Any commercial use of such ideas or designs without prior written permission is an infringement of the copyright protection of the work of each contributing author.

### SUBSCRIPTION/CUSTOMER SERVICE INQUIRIES

A one-year subscription costs \$34.95; a two year subscription costs \$58.95. Canada please add \$12 per year. Overseas rate is \$59.95 for one year; \$110 for two years. To subscribe, renew or change address write to the Customer Service Department (PO Box 876, Peterborough, NH 03458-0876) or telephone toll-free (US/Canada only) 888-924-9465 or (603) 924-9464 or FAX (603) 924-9467. E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com). Or online at [www.audioXpress.com](http://www.audioXpress.com)

For gift subscriptions please include gift recipient's name and your own, with remittance. A gift card will be sent.

### EDITORIAL INQUIRIES

Send editorial correspondence and manuscripts to *audioXpress*, Editorial Dept., PO Box 876, Peterborough, NH 03458-0876. E-mail: [editorial@audioXpress.com](mailto:editorial@audioXpress.com). No responsibility is assumed for unsolicited manuscripts. Include a self-addressed envelope with return postage. The staff **will not** answer technical queries by telephone.

### CLASSIFIEDS & WEB LISTINGS

Contact Nancy Vernazzaro, Advertising Department, *audioXpress*, PO Box 876, Peterborough, NH 03458, 603-924-7292, FAX 603-924-6230, E-mail [nancy@audioXpress.com](mailto:nancy@audioXpress.com).

Printed in the USA. Copyright © 2004 by Audio Amateur Corporation. All rights reserved.



# Remembering Ken Wilkinson

By Reg Williamson

Rarely can one describe someone as a legend in his or her own lifetime, but it would certainly apply to Decca's recording engineer, Ken Wilkinson. Affectionately known as "Wilkie," he was respected by his peers and, even more important, enjoyed the complete trust of the artists he served with his craft. Wilkie began his long career with a small company called World Echo, literally at the dawn of electrical recording in the mid-1920s, and in 1931 he moved to Decca joining the redoubtable Arthur Haddy. It was Haddy's team that developed the well-known Decca "Tree" for stereo, a T-shaped structure holding three omnidirectional Neumann microphones, which Wilkie used extensively.

It had often been said that you could recognize a Wilkie recording

because of the rich balance, favoring to full measure the bottom end of the spectrum, and bringing out the acoustic of his favorite venues. He retired in 1980, just before digital recording began to displace analog. Paradoxically, his skills were recognized more in the US than in the UK, where he won the prestigious National Academy of Recorded Arts and Sciences

Award twice; the first for Berlioz' "Symphonie Fantastique" in 1972 and Ravel's "Bolero" in 1977. He also worked for RCA and for Lyrita.

I spent a day with him about 14 years ago, recording his memories of the many famous artists with whom he had worked, and their idiosyn-



PHOTO 1: Left to Right: Ken Wilkinson, Jimmy Walker (Producer for Lyrita).

crasies. One will suffice. The conductor Stokowki was notorious for wanting to balance his recordings himself. Wilkie smiled, "Of course, maestro. I take it you won't mind if I come out and try my hand at conducting?"

Ken Wilkinson died at age 92 on January 30, 2004. ❖

## LC Audio Technology Inc



A Complete Precision Clock kit is now available for Audio Research CD2!

**The kit is specially designed for AR CD2 and includes all you need:**

Reference Clock (XO3 Ultra High Precision Clock)

Wire Harness specially adapted for CD2

Easy to follow Step by Step Mounting instructions, with photos how to update the CD2 player to the highest sound quality, using modern Low Jitter Clock Technology. **It really Works!**

More Natural Sound - Better Placement in Soundstage - Improved Bass Distinction

Further Information: [www.lcaudio.com](http://www.lcaudio.com)

**NOTE** LC Audio Technology is an independent third party vendor, and has no associations with Audio Research

USA: **DIYCABLE** ● 153 Mountain Home Road ● Port Angeles WA98362 ● Washington ● tel 360-452-9373 [www.diycable.com](http://www.diycable.com)

Australia: **Soundlabs Group Pty.** ● POBox 307 ● Surry Hills NSW 2010 ● tel 02 9660 1228 [www.soundlabsgroup.com](http://www.soundlabsgroup.com)

Scandinavia: **LC Audio Technology Inc** ● Christiansgade 1 ● DK7500 Holstebro ● tel +45 97410863 [www.lcaudio.com](http://www.lcaudio.com)

### LCKlock XO3

The latest in Advanced Low Jitter Clock Technology!



Complete Reference Clock kit with all you need!

Price

Reference Clock kit for Audio Research CD2



**US\$ 399**


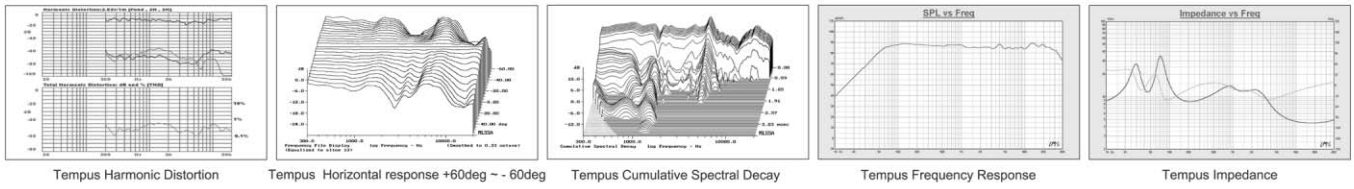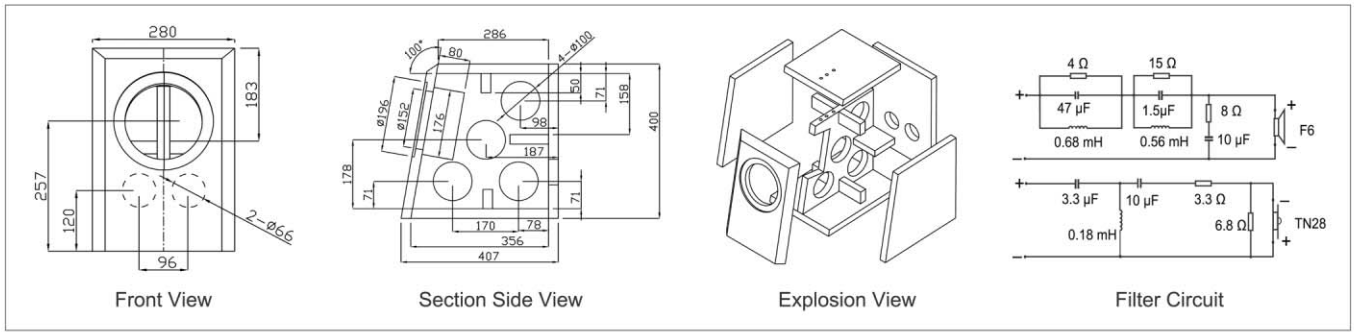
# Swans Tempus Kit



Swans proudly presents their first European-style, independently developed loudspeaker kit. Due to exceptionally high standards for a kit speaker, TEMPUS is a top-level, world-class performer in all regards. German sound magazine KLANG+TON featured the Tempus in the June 2002 issue, commending its excellent acoustic response.



The Tempus project was initially conceived as a private work of the acoustic arts, to be executed independent of all professional affiliations. Despite a lack of traditional marketing and initial editorial commentary, the design has since received wide acclaim in the independent press and has gone on to tremendous commercial success. Tempus' reputation is therefore solely the result of unexpectedly high fidelity from a speaker of its modest origin and cost.

For Tempus' development, Swans agreed to supply premium components for what evolved into a rigorous electro-acoustics design program, executed to the highest European standards. The resulting design's performance was subjected to stringent laboratory confirmation and completely documented in the audio press, including revealing measurements not typical for any loudspeaker much less one of this type. Tempus has since gone on to claim top performance awards from acclaimed KLANG+TON magazine of Germany, during which time Swans cancelled all advertisements and further commentary.

Tempus is now one of Europe's most favored loudspeakers, leaving listeners admiring its naturally musical sound and excellent value. The design is already a classic, destined to sweep the audio world in a fashion similar to its current success.

The new Swans Tempus set includes:

- 2 x 1.1"/28mm Swans TN28 soft-dome tweeters with open-air housing, Neodymium motor, ferrofluid cooling, decompression chamber, integrated grille and German-made silk dome;
- 2 x 6.5"/165mm Swans F-6 shielded high efficiency midbass drivers, with Kevlar/paper curvilinear cone, phasing plug, and alloy basket;
- 2 x completed crossover networks with premium-grade components;
- Two sets heavy input terminals;
- Two pairs internal cable sets;
- Complete manufacturer's instructions.

All Tempus kits are thoroughly pre-tested by Swans and come in matched acoustical sets.

- Price: \$599 with Tempus parts kit only;
- \$999 with Tempus kit and cabinets;
- \$1299 assembled Tempus.



hear different.  
"Tempus"

## SPECIFICATIONS

Frequency Response: 48Hz-20kHz  
 Sensitivity (2.83V/m): 86dB  
 Nominal Impedance: 8 ohms  
 Power Handling: 10-120W  
 Dimensions(HxWxD): 406x286x408 mm

for more info please

Call: (323)-881-0606

SWANS SPEAKER SYSTEMS, INC

2550 Corporate Place, Suite C103  
 Monterey Park CA 91754

www.swanspeaker.com  
 www.theaudioinsider.com



# i m p r o v e d

★ Audio Grade® Power Connectors



350i

350i HC

330i

## TRUE AUDIO GRADE

The performance of WATTGATE™ products relies on fundamental yet superior concepts of engineering. Highly conductive elements (copper and gold) incorporated into high-pressure, large surface area contacts reduces overall resistance which fulfils the goal of improved conductivity. In addition, by implementing new stainless screws into our designs we have now enhanced performance through greater integrity and durability of the connections. Highlighted to the right are some of the important features and technologies incorporated into the WATTGATE™ line of products.

**WATTGATE™** 

Ph: 801-621-1501  
[www.wattgate.com](http://www.wattgate.com)



# nextgen™

The exact solution for  
all digital connections

- the perfect match for all digital audio and video links (75Ω)
- a true wideband RCA type connector
- free from interferences
- with pure copper or silver contacts
- ultra rapid signal transfer



nextgen™ RCA type connector  
WBT-0110

Ph: 801-621-1500  
[www.wbtusa.com](http://www.wbtusa.com)

**WBT**



# Zen Variations 6: Son of Zen Gets Xploited

The Son of Zen amp grows up with the help of this simple Super-Symmetry circuit. **By Nelson Pass**

U.S. Patent #5,376,899 describes an amplifying circuit topology that takes advantage of the character of matched balanced amplifiers that are cross-coupled to provide cancellation of distortion and noise. The result provides high performance with very simple linear circuits and has been dubbed Super-Symmetry—an homage to particle physics—and is also known popularly as the X circuit. Super-Symmetry works by exploiting the complementary characteristics of matched balanced circuits to differentially reject distortion and noise, and applies a small amount of feedback to extend this symmetry, making the distortion and noise even more identical on each half of a balanced amplifying circuit.

In this article I am going to apply this technique to a previous project, the Son of Zen (*Audio Electronics* 2/97), which can also be found at [www.passdiy.com](http://www.passdiy.com)

and whose schematic is shown in *Fig. 1*. Here you see a very simple single-stage balanced differential amplifier without feedback or capacitors. Balanced input signal is presented to the + and - inputs, and a larger version of that balanced signal occurs across the output load.




### WHAT IS SUPER-SYMMETRY?

To best understand Super-Symmetric feedback, consider *Fig. 2*, a simplified version of the Son of Zen (SOZ), where I arbitrarily inject a positive blip representing distortion or noise on the positive output. Because the SOZ amplifier has no feedback of any sort, there is no correction for this

and it appears across the load.

*Figure 3* shows the addition of two symmetric feedback loops to the circuit of *Fig. 2*, consisting of  $1\text{k}\Omega$  resistors in series with the inputs, and  $10\text{k}\Omega$  resistors connecting the input gates of the MOSFETs to the output drains, forming a local feedback loop for each transistor.

If you arbitrarily inject a blip of distortion into the output of Q2 as in *Fig. 2*, note that this blip will also appear (reduced in size) at the gate of Q2, and as a result will also appear as a blip of current coming out of the source of Q2. This current blip drives the source of Q1, and makes the blip appear on the drain of Q1, in phase with the blip on the drain of Q2. To the extent that the sizes and tim-

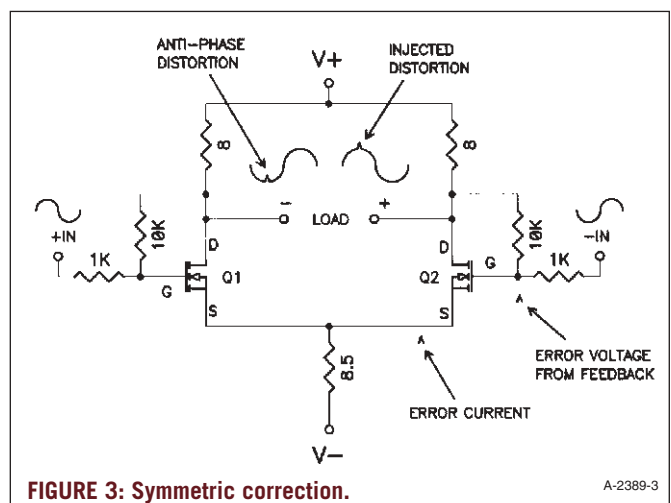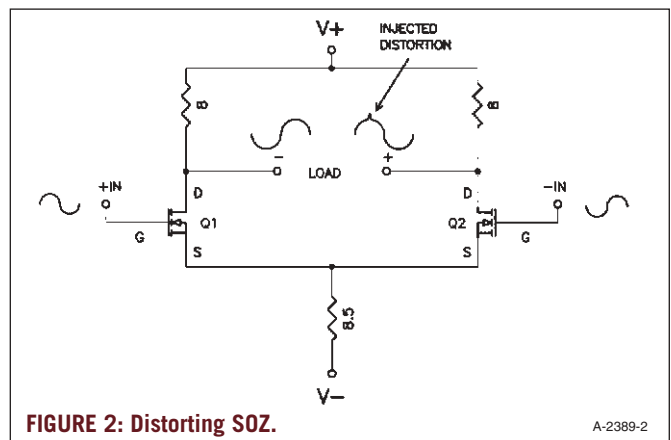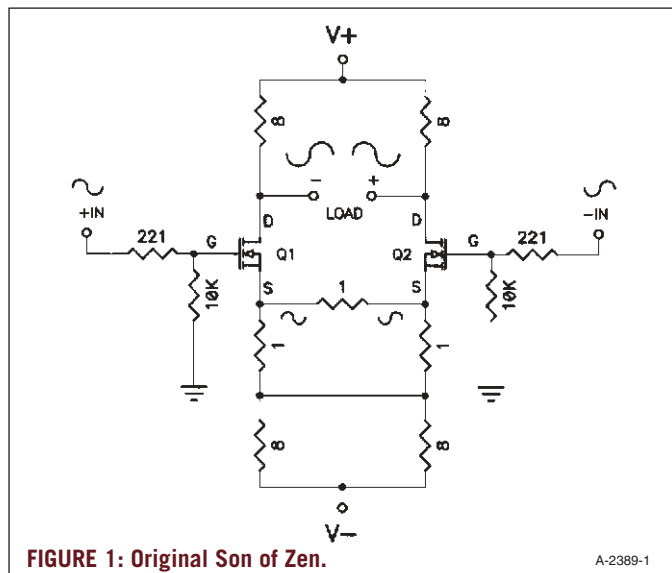



ing of the two blips are identical, they cancel, and are not seen by the load, which is to say they disappear from the standpoint of the loudspeaker.

The unique thing about this arrangement is that the distortion contributed by each half of the amplifier appears nearly equally in phase at both outputs, but the signal appears out of phase at the outputs. So the desired signal is re-

inforced and the undesired noise and distortion is cancelled.

Super-Symmetry is ideally used to obtain high quality performance from very simple circuit topologies, avoiding the high order distortion character and feedback instabilities of complex circuits.

A single-stage circuit such as the SOZ would not actually be expected to see as much improvement as a two-stage circuit because, by its very nature, it does

not correct for the nonlinearities in output current caused by the gate-to-source nonlinearities of the differential pair themselves. This is a fundamental limitation, and of course is true of differential pairs in general.

However, Super-Symmetry does correct the errors in the parts of the circuits that follow them. In a two- or three-gain stage design, the differential pair corrects the errors of the 2nd and 3rd stage, and, of course, any nonlinear-

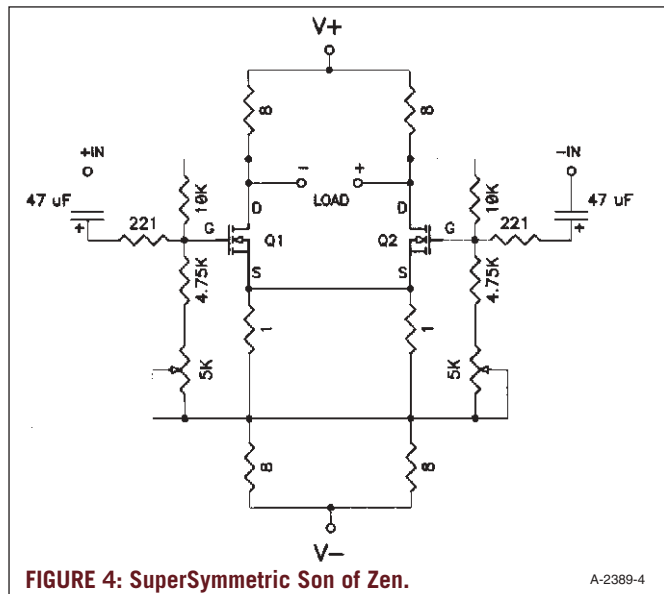


FIGURE 4: SuperSymmetric Son of Zen.

A-2389-4

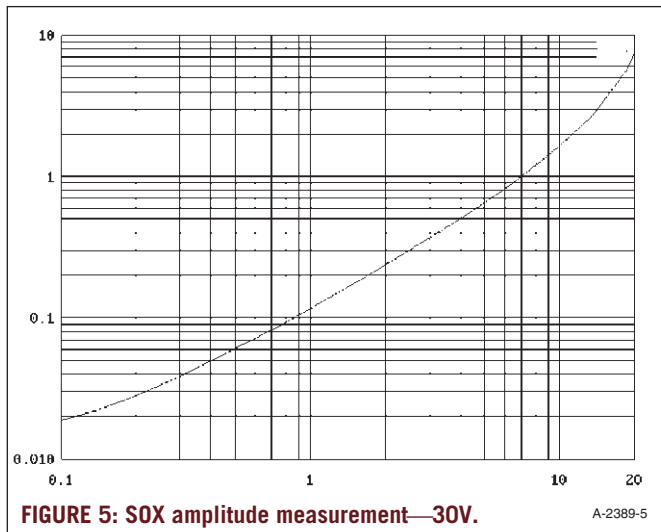


FIGURE 5: SOX amplitude measurement—30V.

A-2389-5

# High Quality Custom Cabinets



Finally a source for the speakers you always wanted the way you want them! Here at P-N-F Inc. we offer our services to the true audiophile. With our cnc routers we can offer a precise cabinet in a variety of shapes that are right on every time. We can assist in the design of the speaker or build from blueprints. With all of our cutting-edge software we can take files from almost any program and convert them into parts. Our vacuum tables allow us to apply real wood veneering with perfect consistency and the best quality, including exotic woods at prices only before available from high-volume cabinet builders. We use our automatic shapers to give all the cabinets we build a locking mitre corner for a stronger and more acoustically sound box. And our state-of-the-art finishing system, consisting of enclosed dust free downdraft spray rooms and short-wave halogen ovens, allows a piano finish in a fraction of the time! There are no minimum quantities. We can run 1 baffle or 1000 pairs and are limited only by your imagination.

P-N-F Inc. 2598 Tuckahoe Rd. Franklinville, NJ 08322 1.877.57.AUDIO

ities in the output voltage contributed by the loudspeaker. Typically a two-gain stage version of this topology can outperform the three or more stages of a conventional amplifier. By gain stages, I generally mean how many transistors there are in series with the signal path, ignoring cascode transistors and counting complementary pairs as a single stage.

As a demonstration of the power of this approach, Pass Labs launched the first "X" amplifier, the X1000, as a 2-stage design with a small amount of feedback, delivering over 1kW with high performance. It has compared well against amplifiers having as many as nine sequential gain stages, and as of this writing is still in production.

The X feedback technique works less well with many gain stages and high open loop gains, mostly because the transit delays through complex circuits can cause a "hall of mirrors" effect,

where the correction comes too late and the distortion bounces back and forth in the circuit. Ordinary feedback amplifiers suffer pretty much the same fate, unless they are deliberately slowed down by frequency compensation.

Why is this important? Because there is a different character of sound attributed to simple linear circuit topologies versus the complex circuits that obtain their performance through the generous use of feedback. It is difficult to produce high power amplifiers with simple circuits, and many previous efforts using many gain stages and high feedback have been described as powerful but musically clinical. Super-Symmetry makes it easier to produce high power amplifiers with the musical characteristic of simple low power amplifiers.





### CONSTRUCTION

Figure 4 shows the actual circuit that I

modified from the original SOZ. All the details of the original project apply to this amp, and I refer you to that article. I removed the 1Ω resistor between the sources of Q1 and Q2, and added two input capacitors of arbitrary value, 1kΩ input and 10kΩ feedback resistors, which set the gain of the circuit. Also, I used 4.75kΩ resistors in series with 5kΩ pots to set the operating point of the MOSFETs precisely for best performance. I will refer to this circuit hereafter as the SOX for brevity.
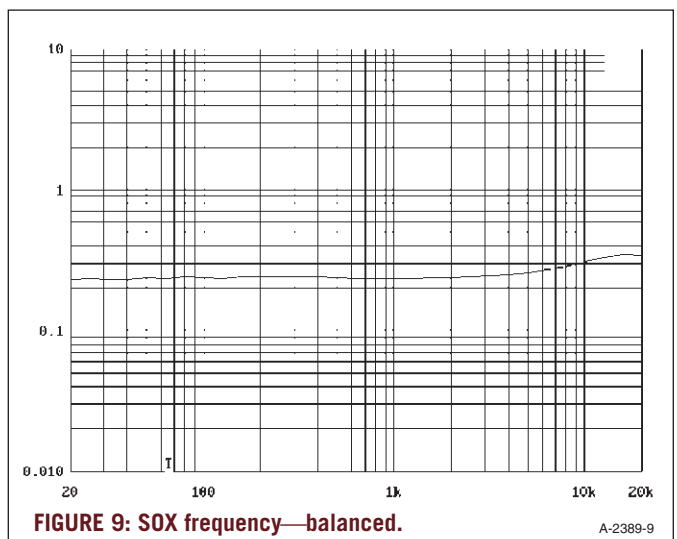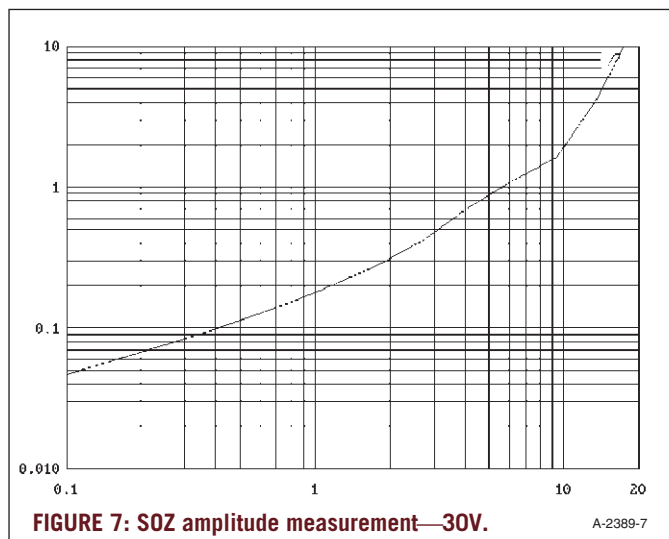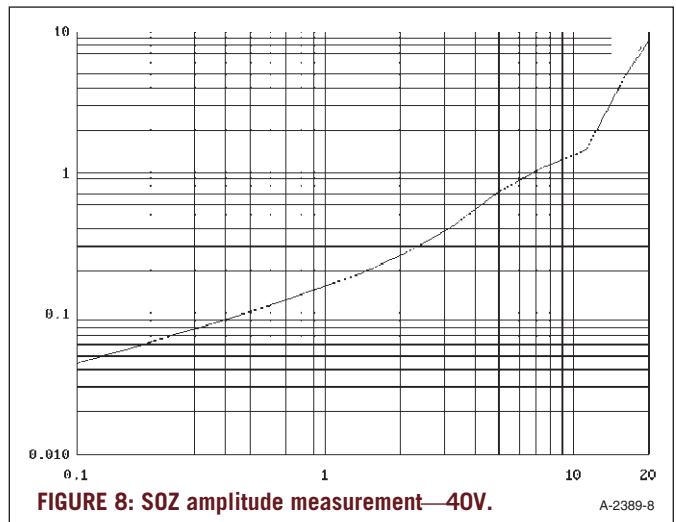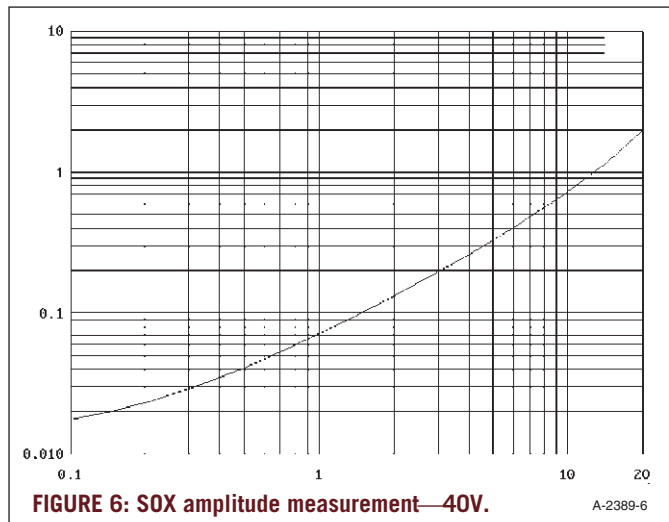
### PERFORMANCE

In order to properly assess the differences between the original SOZ and one with the addition of symmetric feedback, I built a SOZ channel, made the appropriate measurements, and then removed the 1Ω source-to-source resistor and added the feedback elements to form the circuit of Fig. 4. To compare apples to apples, I used the





same supply, the same transistors, an identical layout and test setup, and designed the bias current and gain to be identical. The power supply consisted of a CLC network of 30,000 $\mu$ F, 2mH, and 30,000 $\mu$ F for each rail polarity. Again, you can find other details of the circuit in the original Son of Zen article.

A single stage is the best for tutorial examples, but is not otherwise the most ideal example of the power of Super-Symmetry. Nevertheless, I achieved some interesting and non-intuitive results.

Unless otherwise noted, the curves and data that follow were with an 8 $\Omega$  resistive load, frequencies at 1kHz, output levels at 2W, 600 $\Omega$  balanced source or 50 $\Omega$  single-ended source, and either  $\pm$ 30V at 6A total bias or  $\pm$ 40V at 8A (6A bias means 3A through Q1 and Q2 each).

In the cases where the rails are at  $\pm$ 30V, I set the drain voltages of the SOX circuit on what I judged to be optimal at 8V referenced to ground, which was also about 12.5V drain-source. For the  $\pm$ 40V case, I set the drain voltage at 8.6V DC referenced to ground, which was 13.7V drain-source on the MOSFETs.

As previously noted, the SOZ and SOX gain figures were set about the same, which is close to 12dB with an 8 $\Omega$  load. I set the offset potentiometers to attain the desired drain voltages with a difference of less than 50mV DC, which is then the DC offset experienced by the load. This should be re-adjusted after adequate warm-up, as the character of the MOSFETs drifts with temperature.

First off, I mea-

sured the open loop gain without feedback (and without the 1 $\Omega$  resistor source-source) and achieved a figure of about 20dB. With a 12dB gain after the application of feedback, I calculated 8dB of feedback on the amplifier.

I measured the damping factor, which was about 0.5 (16 $\Omega$  output impedance) for the SOZ and about 3 (2.7 $\Omega$  output impedance) for the SOX—an improvement by a factor of 6 times—more than twice what we would expect with 8dB of feedback—a good example of the power of Super-Symmetry.

The input impedance of the SOZ will be whatever you set the input-ground resistors and the capacitance of the MOSFETs. After the addition of the feedback loops, the SOX input impedance measures approximately 4k $\Omega$  balanced and 2k $\Omega$  unbalanced. This figure is approximate, as it depends somewhat on the MOSFETs and the other settings. It's not a high figure, and it

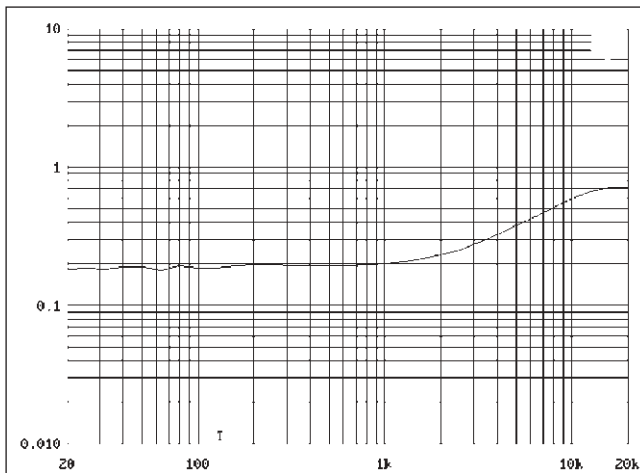


FIGURE 10: SOZ frequency—balanced.

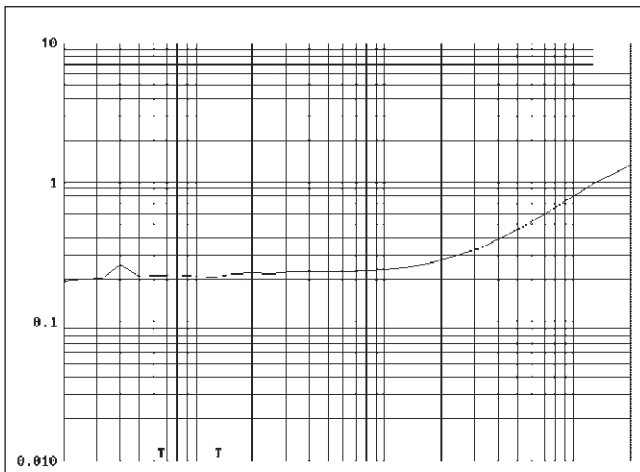


FIGURE 11: SOX frequency—single-ended.



**DRIVERS:**

- ▶ ATC
- ▶ AUDAX
- ▶ ETON
- ▶ FOSTEX
- ▶ LPG
- ▶ MAX FIDELITY
- ▶ MOREL
- ▶ PEERLESS
- ▶ SCAN-SPEAK
- ▶ SEAS
- ▶ SILVER FLUTE
- ▶ VIFA
- ▶ VISATON
- ▶ VOLT

**CUSTOM  
COMPUTER AIDED  
CROSSOVER AND  
CABINET DESIGN**

**SOLEN CAPACITORS  
AND INDUCTORS -  
USED BY THE MOST  
DISCRIMINATING  
LOUDSPEAKER  
MANUFACTURERS.**

**HARDWARE**

**HOW TO BOOKS**

Contact us for the free Solen CDROM Catalog.



**SOLEN**  
4470 Avenue Thibault  
St-Hubert, QC, J3Y 7T9  
Canada  
Tel: 450.656.2759  
Fax: 450.443.4949  
Email: [solen@solen.ca](mailto:solen@solen.ca)  
Web: [www.solen.ca](http://www.solen.ca)

can easily be raised to higher values by increasing the input network values proportionately, but at a cost of higher distortion at high frequencies. Alternatively, you can simply raise the value of the 1kΩ input resistor if you can afford to throw away some gain. In my experience, it will work well with any balanced source, and most single-ended sources, but there are some tube circuits out there that won't like it.

As before, there is no frequency compensation in the amplifier, and I have not encountered a case of instability over the years. It will drive anything—maybe not well, but without oscillation. You can short the outputs as you like, it will not damage the amp. I have not seen significant turn on/off thumps, and I don't expect you to. The amplifier benefits from Vgs matched transistors, but they are not required.

You can refer to the dissipation and power figures from the original SOZ article, and after the modification, the

output power goes slightly higher for a given supply level, as there is no longer the loss across the 1Ω source-source resistor of the differential transistors, but otherwise the curves are very similar.

### DISTORTION VERSUS AMPLITUDE AT 1KHZ, 8Ω

Figure 5 shows the distortion versus amplitude for the SOX circuit using 30V rails and a balanced 600Ω source. From the curves I would call this a 10W amplifier. Figure 6 shows the same for 40V rails, and I would call this a 20W amplifier. For both cases, the overall efficiency is about 3%.

It's pretty clear that the higher voltage and bias of the latter gives marked improvement. In both cases you can see a small improvement over the SOZ, but nothing to write home to mom about. As pointed out earlier, I do not expect improvement in this regard at lower frequencies because for a single-stage amplifier, Super-Symmetric feed-

back does not correct the Vgs versus current distortion of the first differential pair, and that is mostly what you are measuring here.

### DISTORTION VERSUS AMPLITUDE — SINGLE-ENDED SOURCE

The situation alters when the amplifier is driven from a single-ended source (and the minus input of the amplifier is grounded). The curves for the SOX amplifier do not change significantly, but you see that the distortion character for the original SOZ has roughly twice the distortion and begins clipping earlier. Figure 7 shows the 30V supply example of the SOZ, and Fig. 8 shows the 40V example.

### DISTORTION VERSUS FREQUENCY — BALANCED SOURCE

For the SOX circuit you see a slight increase in distortion (about twice) as you approach 20kHz at 2W (Fig. 9), and for the SOZ you see a more dramatic climb

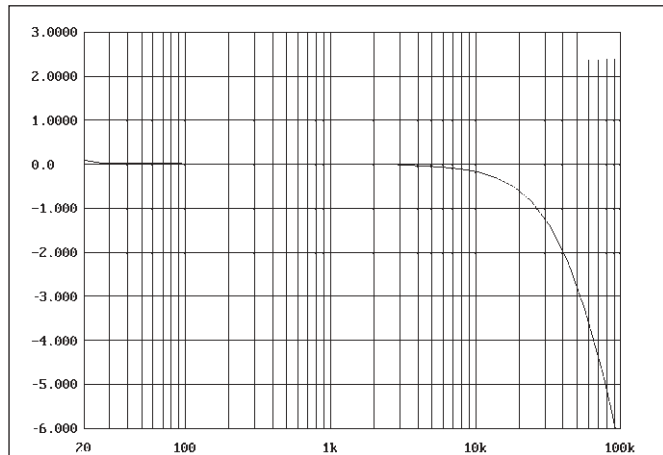


FIGURE 12: SOZ frequency response.

A-2389-12

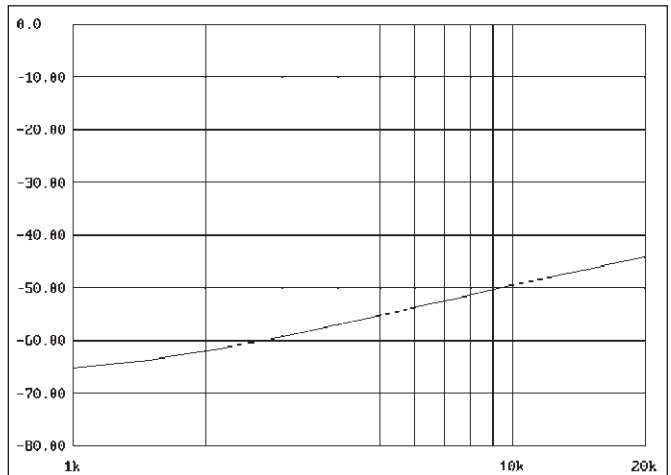


FIGURE 14: SOZ common-mode rejection.

A-2389-14

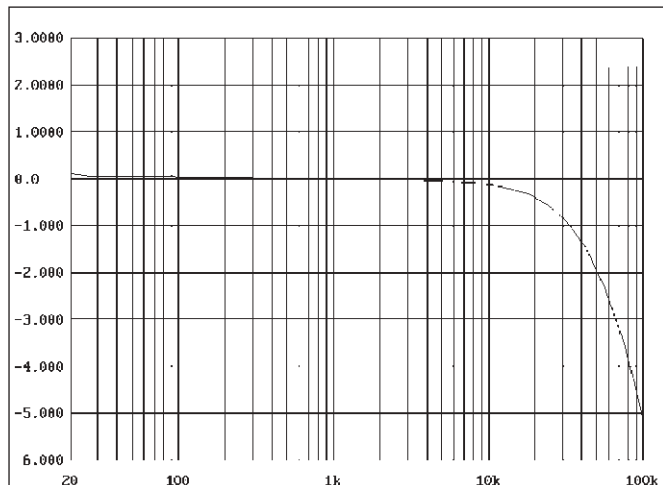


FIGURE 13: SOX frequency response.

A-2389-13

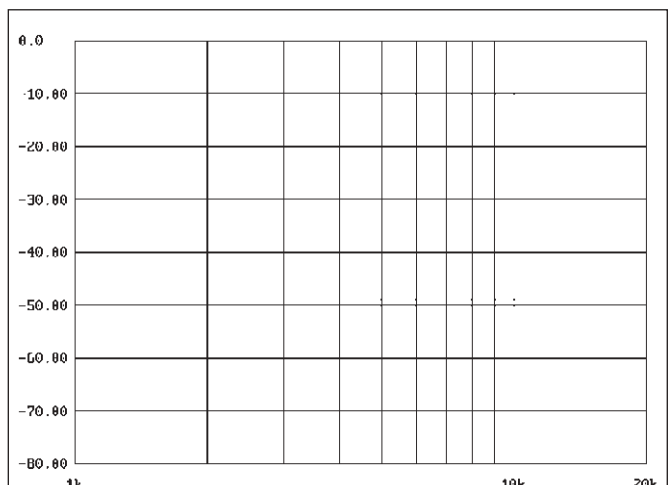


FIGURE 15: SOX common-mode rejection.

A-2389-15



(Fig. 10). I have not explored this difference thoroughly, but I am assuming that the feedback in SOX is removing device distortion outside of the Vgs/current effect, most likely the nonlinearity in capacitances between the drain-source and drain-gate.

### DISTORTION VERSUS FREQUENCY — SINGLE-ENDED SOURCE

Figure 11 shows the increases that occur in distortion versus frequency in SOX when driven by a single-ended source. It goes up quite a bit toward 20kHz, but less than half that of SOZ. You can use balanced sources here, or you can console yourselves in the fact that musical material declines in energy above 5kHz.

### FREQUENCY RESPONSE

The high-frequency rolloffs for both SOZ and SOX do not alter appreciably for different supply voltages and bias currents, but the SOX does come out faster, with a -3dB point at 70kHz versus 50kHz on the SOZ (Figs. 12 and 13). These figures are unaffected by the use of balanced versus unbalanced inputs.

### COMMON-MODE REJECTION

Both circuits show excellent input common-mode rejection (CMRR), the ability to ignore noise appearing the same on both balanced inputs. The SOZ was slightly better (-65dB) at low frequencies, but declined at high frequencies, while the SOX was about -50dB, but constant across the audio band (Figs. 14 and 15).

### LISTENING TESTS

When your output power is 20W with an efficiency of 3%, you tend toward the more efficient type of loudspeakers. Fine, that's what I prefer anyway. I spent some quality time with the SOX and several drivers mounted in the J-Low rear-loaded horns ("The J-Low Project," *audioXpress* Feb. 2004), also at [www.passdiy.com](http://www.passdiy.com). The drivers were the Jordan 92, Manger, Fostex FE208 Sigma, and the Lowther DX55 with the "shower head" phase plug. The Manger and Jordan are not that efficient compared to the Fostex and Lowther, but all are interesting examples of single full-range drivers, particularly when augmented by a bass horn.

I don't want to get into the relative merits of the drivers here (I will elsewhere), but I did compare these to the stock SOZ (actually, the same amps, reconfigured), a pair of balanced Zen Lite (with the three bulbs), and the Aleph 30.

Previously, I had preferred the Aleph 30 on all the drivers except the Jordan, where the Zen Lite ("Zen Variations Part 1," *audioXpress*, March 2002) sounded a little more musical. Part of this is because the other drivers, in spite of their varying efficiency, have larger cone areas and can make more use of the greater power of the Aleph 30. Previously the SOZ sat somewhere in between the other two amps. I rather expected to hear improvement in bottom end control and a more even spectral balance from the SOX. Maybe it's a self-fulfilling prophecy, but that's pretty much what I received.

Compared to the SOZ, there is definitely cleaner bottom and top, and more ability with complex music, particularly orchestral. If it was just a piano or vocal alone, the difference was not as great. I heard a bit better spectral balance in general, and the result was more musical and toe-tapping.

The most interesting experience, where the amplifier seemed outstanding, was with the Lowther on piano, material with dominant vocals and not much else, or string quartets (Philip Glass recordings, as an example). You could kill an evening pretty easily with this if you didn't try to play it too loud or expect deep bottom end.

Compared to the Zen Lite, it depended on the bias conditions. I used a Variac to go between the two 30V and 40V settings, and at the higher bias, it definitely was better than Zen Lite and approached the Aleph 30 for dynamic range, and I would say matched it overall on most material. Unfortunately, at 40V rails and 4A bias per transistor (640W/ch dissipation), it ran hot as hell, and my heatsinking was not up to the job over long periods. As a result, quite a bit of the time was spent at the lower settings.

Alas, the lower setting is slightly inferior, and it's quite easy to get spoiled. This was true of the original SOZ as well, so some things just don't change.

An argument is often made that am-

plifiers like this are wasteful of energy and not environmentally friendly. Well, that's true, but I get more enjoyment out of an amplifier like this than driving a car, which consumes between 10 and 100 times more power. According to my electric bill, for the couple hours I might spend listening each day, an amp like this represents about 2% of my overall consumption. I think I would not leave it on 24 hours a day, though.

To sum up, I am very happy with the results here. If you have already built a Son of Zen, then I certainly recommend that you run out and buy about 10 dollars' worth of parts and upgrade it. If you haven't already built a Son of Zen, stay tuned, and we'll see about raising that efficiency figure real soon.

Nelson Pass, the proprietor of Pass Laboratories and a frequent contributor to *audioXpress*, enjoys creating trouble.

"Aleph," "Super-Symmetry," and "Zen" are trademarks of Pass Laboratories, Inc. ♦

## PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878  
Reno, NV 89510

[www.passdiy.com](http://www.passdiy.com)

# Tube Audio Construction Tips: Part 2: Sockets

This section on tube sockets shows you how you can enjoy audio construction and still keep your bankroll afloat.

By Graham Dicker and Jim Tregellas

In part one of this series, I covered the purchase of tubes for audio projects, and explained my particular interest in using transmitting tubes for SE amplifiers. While the tubes are available at a reasonable price, the sockets represent another problem that can quickly empty a healthy bank balance. Help is available. Here are some ideas I have used in the past to reduce costs.

## TUBE SOCKETS

You can scrounge octal, noval, and seven-pin tube sockets from old black-and-white TV sets. There are many suppliers of new and NOS sockets on the web and advertised in *audioXpress*. The better sockets have ceramic substrates. Some vintage pre-WWII tubes require wafer-type sockets. If you purchase these, ensure that there are no heat marks or carbon tracing in the wafers.

The second most common failure with older sockets is tarnishing (oxidation) and corrosion of the socket pins. High resistance on filament pins can shorten tube life and cause excessive heating at the tube base. If you have discolored heater pins on the socket, beware.

If you have oxidation or tarnishing on tube sockets or NOS components, you can often remove this by soaking the socket or part in a solution of citric acid, which is available at the supermarket. Citric acid, which is used in cooking, is not a strong enough acid to eat away the metal parts, but it does act as a good descaler. After removing the oxidation, I always soak the socket in hot soapy water to remove all traces of the acid.

You can also clean used sockets of flux and surface scale with an old toothbrush and some acetone (paint thinner). You can restore aluminum IF cans by using a wire brush and steel wool, and then anodizing them in a weak solution of sulfuric acid, or caustic soda. Always use rubber gloves and much care when handling any chemical.

When I first started building low-cost amplifiers, I found that one of the most expensive items was the tube socket for transmitting tubes. You

will usually pay around \$50 to \$100 per tube socket for new ones. For the ceramic tubes, especially the 4CX150, 4CX250B, and 4CX350A, you do not need to purchase an expensive air socket. My handy hint here is that you can purchase a standard Locktall socket for around \$5. Be sure to purchase the ones without the mounting shrouds, so as not to impede the airflow over the tube base.

For your audio purposes, you do not need the expensive ones with built-in screen bypass capacitors that sell for \$100. Also, do not purchase the ones intended for grounded grid operation with an internal grid bypass capacitor (*Photo 1*), unless you wish to build a grounded grid audio amplifier. Many years ago, I used a pair of these grounded grid sockets by mistake and had a massive rolloff of high frequencies and poor slew rate in the output stage that drove me nuts for weeks, until the penny dropped. What made life worse was the 15dB of feedback around the stage that was doing really weird things. I tried everything, including a new output transformer.

You can easily form an anode clamp

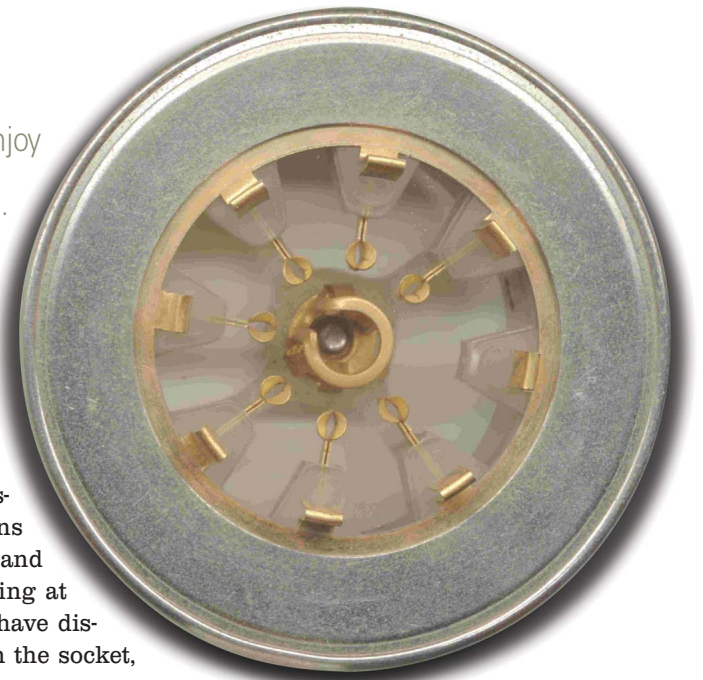


PHOTO 1: SK600 Eimac air socket.


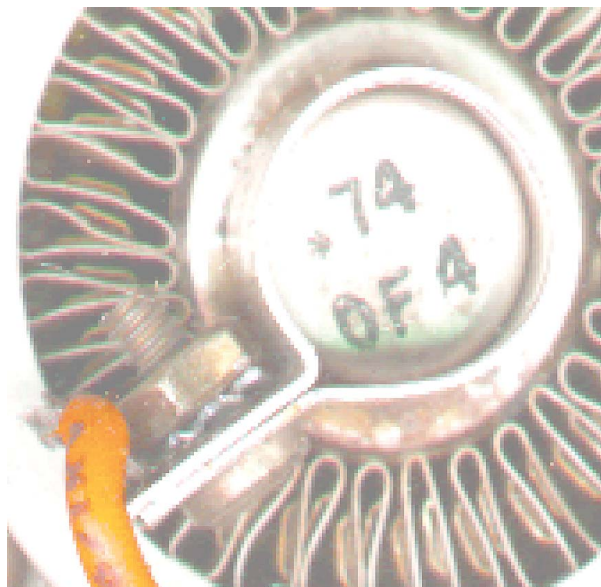


PHOTO 2: Homemade anode clamp.

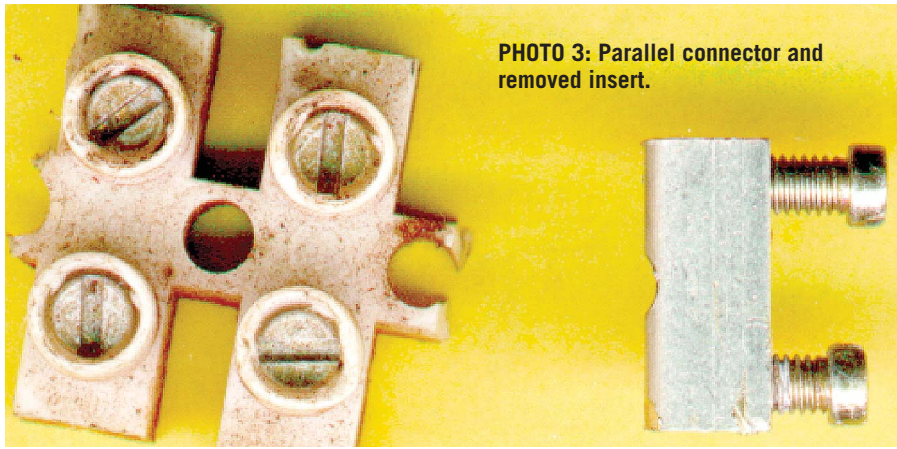



**PHOTO 3: Parallel connector and removed insert.**

ets by purchasing a ceramic bathroom tile, drilling it and mounting parallel connector inserts for the pins (*Photo 3*). Ceramic tiles come in different sorts, textures, colors, and characteristics. I use wall tiles because they are easier to drill than harder floor tiles, and because of the heat resistant properties, not mechanical strength. A single wall tile will yield around 12 ceramic tube sockets. At a cost of around \$1 per tile, that's less than ten cents each socket.

You can cut a standard tile with a tile cutter or a diamond scribe, and then



**PHOTO 4: Socket pin inserts made on a lathe.**

from a short length of aluminum wrapped around a drill bit (*Photo 2*), or you can purchase a radiator hose clamp with equal results. For tubes such as the 6J7 ceramic triode, you can use hose clamps for all of the tube base connectors. I have also used recycled can-type electrolytic capacitor clamps.

### MAKE YOUR OWN

If you are on a really tight budget, why purchase a base at all, when you can make your own? In my cheapskate mode of playing with devices that glow in the dark (tubes), I have often needed a tube base that I did not have in my junk box.

A good trick here is that you can mechanically support your tube using a radiator clamp, then connect to the tube pins using individual Molex crimp connectors. There are many different sizes available. Use the right diameter ones to slip over the tube pins. There is enough grip with these so that they do not fall off. If you wish, you can mount these on a piece of Bakelite or fiberglass substrate by drilling appropriately spaced holes and using ten-minute epoxy to secure them.

For glass tubes such as the 813 or GK-17, the RCA 4-125A, and the Eimac 304TL and others, I make my own sock-

- Speaker level inputs, high-pass satellite outputs
- Line level inputs and outputs
- Auto turn-on
- high-density trim gasket
- 12dB continuously variable crossovers
- 0°/180° phase selector
- Choose from 100W, 250W and 350W RMS models



#### 350 Watt Module

- Motorized control panel with IR remote control

Order #50-6282



#### 250 Watt Module


- Continuously variable 0~180° phase control

Order #50-6281A

#### 100 Watt Module

- Fully enclosed rear housing

Order #50-6265

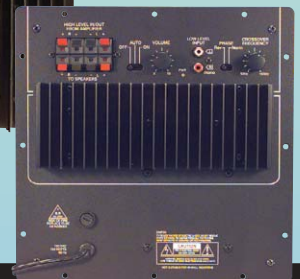

## MCM AUDIO SELECT™ Subwoofer Amplifier Modules



FREE CATALOG

- Over 40,000 products stocked
- Access to over 1.5 million electronic parts and related products
- Superior customer service
- Special offers and discounts
- Quotation team, send us your quotes for quick response
- State-of-the-art automated warehouse

Call toll free

**1-800-543-4330**

or visit

[www.mcminone.com/magazine](http://www.mcminone.com/magazine)

Source Code:

**AE06**



**MCM**

an in one company

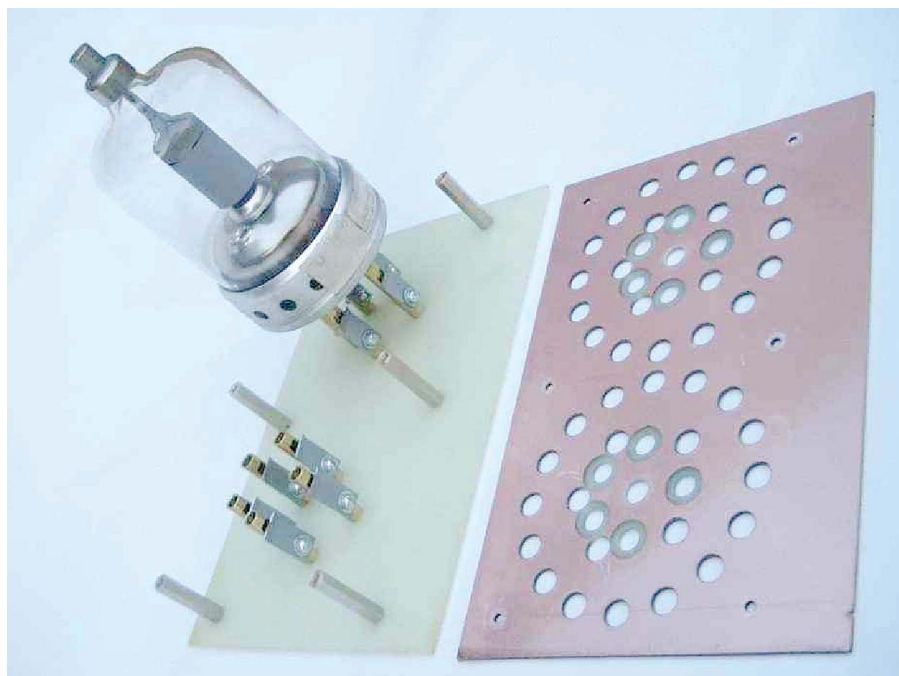


PHOTO 5: Completed 4-125A socket and top ground plane.

sand the sides to remove any edges. The best method that I have found to drill holes is to use a section of masking tape over the area where the hole is to be drilled, and then use a masonry drill bit on low speed. You can easily fabricate a template from some clear Perspex.

Make the connections with Molex crimp connectors, or for the larger tubes, I use brass inserts removed from parallel connectors. These are available in a range of sizes to suit most tube pins. The added advantage is that if the connections are screwed, the tubes do not fall out of the sockets.

The automotive industry makes a range of suitable push-on connectors and bullets which you can also use. Brass connectors are recommended for filament connectors due to the high current requirements. The added advantage is that brass connectors have less oxidation problems over the life of the connector.

Having a good workshop with a lathe makes other solutions possible. As *Photo 4* shows, two possible connector forms evolved, both made from 0.250" diameter brass rod. The first version (shown on the right) simply involved drilling a 4.5mm diameter hole for the tube pin and a 2.5mm hole for the 3mm screw on either end of the rod. I then "necked" the rod to reduce the wall thickness around the pin, splitting the necked section horizontally into four

parts with the lathe chuck stationary and with a very sharp V tool. I mounted the tool in the tool holder, so that it cut at 90° to its normal direction (longitudinally rather than vertically). I then gently squeezed these sections on the finished socket (*Photo 5*) inwards using pliers to give a good springy grasp of the tube pin.

The second connector form on the left is more difficult to make, but gives an extremely firm grasp on the pin. I made the connector by drilling a 4.5mm hole for the tube pin and two 2.5mm holes for the screws, and then milling a double height flat on the socket using a tungsten carbide rotary file in a drill press. I fabricated the spring from 316 stainless steel. Socket pressures are such that the 4-125 filament current presents no problem with this connector. I ended up using this as my preferred socket.

I then mounted the connectors between two pieces of printed circuit board. I drilled the upper one to provide airflow around the tube and to locate the upper parts of the sockets, and drilled the lower one simply to accommodate the sockets and inter PCB spacers. Except for an insulating area around the sockets, I left the copper on the upper PCB, and removed all copper from the lower PCB. I have a very nice custom-made ground plane tube socket for 4-125s complete with built-in air-

flow direction (*Photo 5*).

Having made these sockets, I suggest that brass connectors from trailer light plugs and sockets can work equally well. While it was a long task, the first ceramic socket I ever made used an entire marble color tile as the top of a chassis for the whole amplifier. It looked great, but took ages to drill all of the mounting holes. If you have the budget, I recommend getting them hydra- or laser-cut.

## CHEAP FANS AND COOLING

One of the lowest-cost blowers I have in my workshop for using with ceramic tubes is an old hairdryer, which makes a great centrifugal blower for the 4CX series tubes. I use a short length of Teflon held in place with a rubber band to connect the two together. You can easily make a simple chimney from a small piece of Teflon sheeting rolled into a tube and secured with a rubber band or a radiator hose clamp.

A blown cavity can be fabricated using PVC plumbing fittings and a recycled 36'/minute Panaflow computer fan with equal success. You can also use these fans to cool glass tubes. I prefer to use fans in pairs: one blowing cool air onto the tube, the second to suck out the hot air from the other side. An alternative chimney for tubes is a small ceramic garden pot with holes drilled in the bottom, then placed over the tube to direct a cool airflow. ❖

## SHOW US YOUR STUFF

If you are an audio enthusiast, then you probably have information, tips, and experiences that would be valuable and/or entertaining to *audioXpress* readers. *audioXpress* encourages your feedback and offers you the opportunity to share your knowledge and show off your handiwork. And, we'll pay you a modest stipend for your efforts.

So, put a few bucks in your pocket. But most of all, become an active part of the audiophile community by sending your tips—and any accompanying photographs or artwork—to:

*audioXpress*  
 Editorial Department  
 PO Box 876  
 Peterborough, NH 03458



# Transformers & Enclosures *In Stock...*




## Torodial Power:

13 sizes (15 - 1500 VA)

6 VAC - 240 VAC
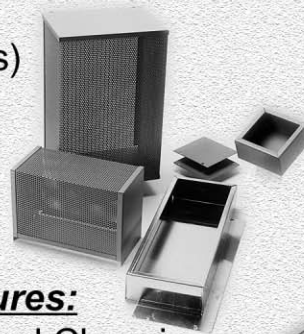
## "Classic" Tube Output:

Single Ended (up to 75 watts),  
Push-Pull and Potted (up to 280 watts)



## Enclosures:

Aluminum & Steel Chassis,  
Diecast Aluminum, Plastic  
and Rack Mount

## Filament & Low Voltage

### Power Transformers:

Open & Enclosed

## "Classic"

### High Voltage Transformers:

Plate, Plate/Filament Combo  
& Filter Chokes (Open & Enclosed)



**Contact us for free catalogs & a list of stocking distributors**



# HAMMOND MANUFACTURING™

256 Sonwil Dr. - Cheektowaga, NY 14225 USA

Phone: (716) 651-0086 Fax: (716) 651-0726

394 Edinburgh Rd., N. - Guelph, Ontario N1H 1E5 Canada

Phone: (519) 822-2960 Fax: (519) 822-0715



**[www.hammondmfg.com](http://www.hammondmfg.com)**

# Vented 8" Driver Subwoofer, Part 1

This article covers the development and construction of physically small subwoofer systems using 8" drivers.

By G.R. Koonce and R.O. Wright, Jr.

**W**hat is an apartment subwoofer? We are talking about small subwoofers that might not get your lease terminated! While they may not play as loudly as larger drivers, they do provide true subwoofer performance. The designs use single voice coil drivers and are intended for use in pairs.

## A DIFFERENT DESIGN APPROACH

You would think development of an 8" driver subwoofer would be as easy as building with a larger driver. This turned out not to be true with the 8" drivers we located.

After development of good 12" and 15" driver subwoofers<sup>1</sup> using the Infinite Box (IB) approach<sup>2</sup>, we had hoped to go the same route with the 8" drivers. While the IB approach provides great-sounding speakers in small enclosures, it produces a higher system  $-3\text{dB}$  frequency ( $f_3$ ) than some other approaches. While measurement showed the 12" IB subwoofer went down to 25Hz, the breadboard 8" driver IBs yielded  $f_3$  limits in the 50 to 80Hz range—clearly not acceptable. The IB approach fails here because of the relatively high  $f_s$  of the 8" subwoofer drivers. Since a given driver will show a similar high  $f_3$  in a closed box, they are not a viable alternate.

The approaches left to achieve a low  $f_3$  while retaining a small enclosure are the passive radiator (PR) and the vented box (VB). If you can obtain small PR units which provide sufficient displacement, the PR technique will enable a smaller enclosure. This is because adding one or more PR units will require less enclosure volume than the duct of the VB.

With a VB design the port delivers most of the system output at low frequency and thus must pass a large air volume. If you decide that a 4" ID port is sufficient, which may be optimistic, you will discover the required port duct length is in the 40" to 60" range. No matter how you coil that up it takes a lot of volume, close to  $\frac{1}{2}\text{ft}^3$ .

We were aware that Al Wooley (of RAW Acoustics) and Bob Reimer (of Creative Sound Solutions) were developing a small PR subwoofer using an 8" driver from TBspeakers. We thus decided to pursue the VB approach and try to solve the "huge vent duct" problem. We hope to publish information on construction and performance of the PR subwoofer in a future issue.

## HOW BIG A VENT DUCT?

Recently published works on the requirements for high-



PHOTO 1: Front view of MCM #55-2421 (#194) driver.

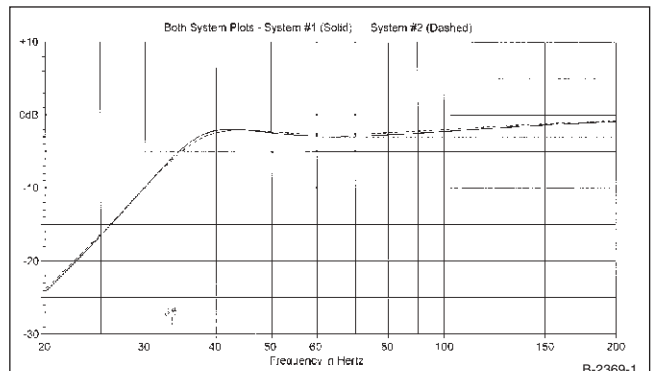


FIGURE 1: Computer VB designs for MCM #55-2421 (#194) driver pair.

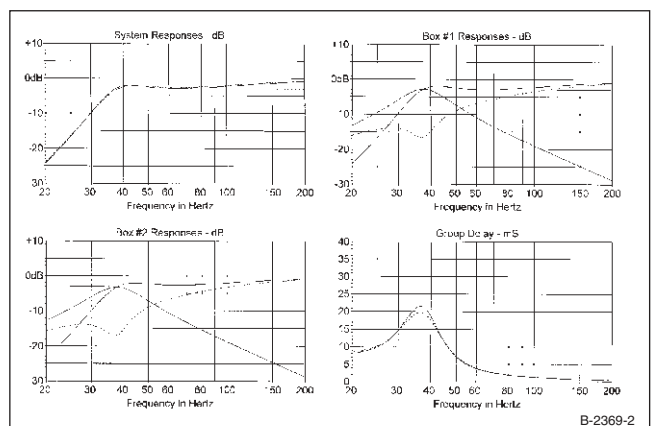


FIGURE 2: Other system performance for MCM #55-2421 (#194) driver pair.



power vent ducts have not been encouraging. Reference 3 looks at the problem in terms of Reynolds numbers. Testing showed that for a 100W power level even a 6" ID vent duct was not sufficient to prevent response shape change with power level. A 100W steady-state input power level is a more severe requirement than our intended application.

Reference 4 is a detailed study of duct shape. It included a chart by Harwood that related maximum SPL to box tuned frequency ( $f_b$ ) for various duct sizes. In our case the #197 driver (identified later) is rated at 84dB/W/m with a 120W power capability, so it could develop 105dB SPL at 1m. From the Harwood chart, at 30Hz, this would require a duct of about 140mm (5.51") diameter.

Reference 5 studied the advantages of having flares at both ends of the duct. It indicated that such flares im-

proved performance by reducing port-generated noise and allowing a given diameter port to be used to a higher power level before it "packed up." This article also pointed out that Precision Sound Products offers kits of the Precision Port™ that contain a flare for each end and a length of pipe you can cut to length. The kits are available in 3" and 4" ID sizes.

Taking a more direct approach, ROW contacted some of his pro-sound field acquaintances. They regularly work the problem of high-power VB designs used at low frequency, but generally with

larger drivers. They reported the following rule-of-thumb for sizing a straight port: If the port diameter is 40% to 50% of the cone diameter you will be OK. David Weems<sup>6</sup> discovered a rule-of-thumb that states the port area should be between 1/7 and 2/3 of the cone area. Converted to a percentage of effective cone diameter, this is 38% to 82%, the minimum being in general agreement with the pro-sound value.

Our drivers have about a 6.5" effective cone diameter, so the 40% to 50% rule indicates a port of from 2.6" to 3.25" diameter would be OK. We worry



PHOTO 2: Back view of MCM #55-2421 (#194) driver.



PHOTO 3: Front view of MA-Audio MA80XE (#196) driver.

## Do you suffer from Audiophilia Nervosa?



**Audio Asylum** - an institution for the care of audiophools.

Audio Asylum is a free and independent resource staffed by a small, volunteer group of audio lunatics. Our mission is to create a unique community for stimulating discussion and helpful interchange without the flame wars and slow load times often found at other sites.

### Here's what inmates have to say:

"This is what the Asylum actually is: USEFUL."

"... the Asylum has taken me to a higher level of knowledge than I ever could have acquired on my own."

"I have saved hundreds...maybe thousands of dollars on equipment through the good advice received here. And not a banner ad in sight!"

"...the best return on your audio dollar will be the Asylum!"

**Get committed today.**



AudioAsylum.com

that these rules-of-thumb may have been developed for woofer and not subwoofer drivers. For a given cone size the subwoofer driver will move a lot more air due to its much larger  $X_{MAX}$ . We decided to design with a port area equivalent to a straight 4" ID pipe (12.57 in<sup>2</sup>) with a fallback to using the area of a 3" ID pipe (7.09 in<sup>2</sup>) with flares added at both ends.

## DRIVER CANDIDATES

We had located and obtained pairs of the following driver types:

1. MCM #55-2421 8"—Our reference #194. See *Table 1* for what catalog data we have on this driver. *Photos 1* and *2* show this driver.
2. MA-Audio MA80XE 8"—Our reference #196. See *Table 1* for catalog data and *Photos 3, 4,* and *5*. This driver is intended for automotive application and has the openings to the rear

of the cone almost vertical to the rim (*Photo 5*). This driver would require major relieving of a thick front panel to allow the rear of the cone to breathe properly. The MA80XE has dual 4Ω voice coils.

3. TBspeakers W8-704C 8"—Our reference #197. See *Table 1* for catalog data and *Photos 6* and *7*. Unit A is serial No. 59 and unit B is serial No. 58.

We ran these drivers at low frequency for over 40 hours at a power level of 2–4W. As noted, we tested the drivers in a small IB breadboard and then measured the T/S parameters. These drivers have large vented magnet structures, making the volume taken from a test box hard to establish, so you should consider the test  $V_{AS}$  values reported as approximations. The #196 (MA Audio) driver had shown poorly in designs based on catalog data and had a shape

making volume estimation very difficult, so we measured only a single unit.

*Table 2* compares catalog and measured data for the #194 (MCM) driver. The two units are fairly consistent; however, they don't match the catalog data very well. First,  $f_s$  is much higher. These are foam surround drivers that might exhibit a drop in fs with additional use. The electrical Q (and thus  $Q_{TS}$ ) is also much higher than specified, which is probably good for a VB application.

Generally the most variable parameter of a driver is the mechanical Q ( $Q_{MS}$ ), a measure of the losses in the suspensions. Surprisingly, this is the parameter that agrees best with the specifications for this driver.

*Table 3* shows the test results of one #196 (MA Audio) driver with the two voice coils connected in series. The catalog rated  $f_s$  (38Hz) was already rather

**TABLE 1  
DATA FOR 8" DRIVERS OBTAINED FOR  
SUBWOOFER CONSIDERATION**

Reference number	194	196	197
Make	MCM	MA-Audio	TBspeakers
Driver	#55-2421	MA80XE	W8-704C
Nominal $Z_{IN}$ (ohms)	4	Dual 4	4
DCR (ohms)	3.4		3.2
Sensitivity (dB/W/M)	87	87.3	84
Rated Power (watts)	120	250	120
Maximum Power (watts)	240	500	230
$X_{MAX}$ (mm — one way)*	16	10	12
Resonance — $f_s$ (Hz)	24.7	38.3	28
Total Q — $Q_{TS}$	0.18	0.31	0.30
Compliance — $V_{AS}$ (ft <sup>3</sup> )	1.39	0.753	0.812
VC Diameter (mm)			50
Force Factor, BL (TM)	13.46		13.35
Magnet Weight (Oz)	47		50
Magnet gap height (mm)	8		8
Moving Mass (G)	64.2		95
Sus. Compliance (M/N)			333
Eff. Piston Diam.(inches)	6.41		6.59


\*We have some question on these Xmax values. The MA80XE specified 20mm for peak-to-peak so 10mm one-way is valid. The other two drivers did not state how Xmax was defined or determined.

**TABLE 2  
CATALOG VERSUS MEASURED DATA FOR  
MCM #55-2421 (#194) DRIVER**


	CATALOG	UNIT A	UNIT B
$f_s$ — Hz	24.7	31.6	30.5
$Q_{ES}$	0.19	0.263	0.265
$Q_{MS}$	12.64	11.98	13.04
$Q_{TS}$	0.18	0.258	0.260
$V_{AS}$ — ft <sup>3</sup>	1.39	0.70	0.85
$V_{AS}$ — L	39.4	19.9	24.2
SPL dB/W/m	87	85.9	85.9

**TABLE 3  
CATALOG VERSUS MEASURED DATA FOR  
MA-AUDIO MA80XE (#196) DRIVER**

	CATALOG	UNIT A
$f_s$ — Hz	38.3	46.9
$Q_{ES}$	0.34	0.47
$Q_{MS}$	4.23	5.88
$Q_{TS}$	0.31	0.44
$V_{AS}$ — ft <sup>3</sup>	0.75	0.41
$V_{AS}$ — L	21.3	11.7
SPL dB/W/m	87.3	85.9

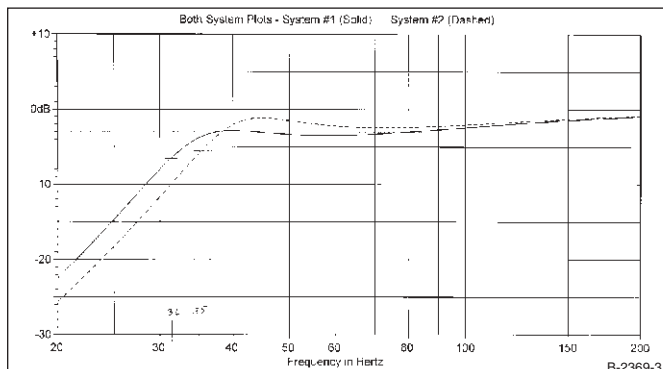

**FIGURE 3: Effects of changing the tuning with MCM driver unit A.**

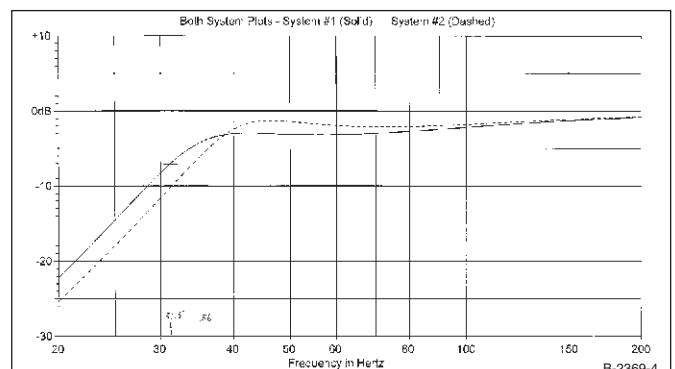

**FIGURE 4: Effects of changing the tuning with MCM driver unit B.**



high, but the real  $f_s$  (47Hz) was much too high for a subwoofer application. Again, this is a foam surround driver, and  $f_s$  may drop a bit more with additional use. Based on the high  $f_s$ , we deleted this driver from further consideration in a small subwoofer application.

Table 4 shows the test results for the #197 (TBspeakers) driver. The two samples match pretty well and are not far from the catalog specification. The low  $f_s$

values agree well with the catalog value and explain why this driver type was the closest to making it in an IB enclosure.

The  $V_{AS}$  measured a bit lower than specified. The electrical  $Q$  (and thus  $Q_{TS}$ ) is considerably higher than specified, which, again, is probably good for a VB application. The SPL, which was already low, computed very low. This testing drop in SPL may be partly due to the lower  $V_{AS}$  (which may be partially

a test problem) and partly to a “weaker” than intended motor as evidenced by the higher electrical  $Q$ .

### SUBWOOFER VENTED BOX DESIGNS

Designing a VB for a subwoofer is a bit different from that for a normal woofer application. First, there is no reason to use a “flat” response alignment. The subwoofer is going to be used only from  $f_3$  up to about 100Hz. This opens up

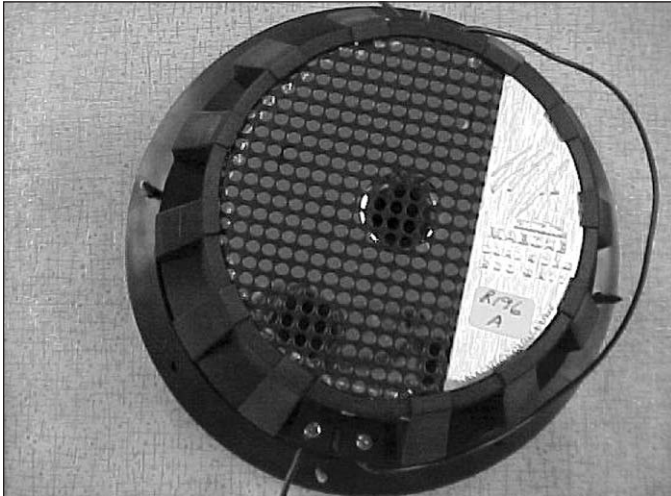



PHOTO 4: Back view of MA-Audio MA80XE (#196) driver.



PHOTO 5: View of MA-Audio MA80XE (#196) driver showing near vertical side openings.
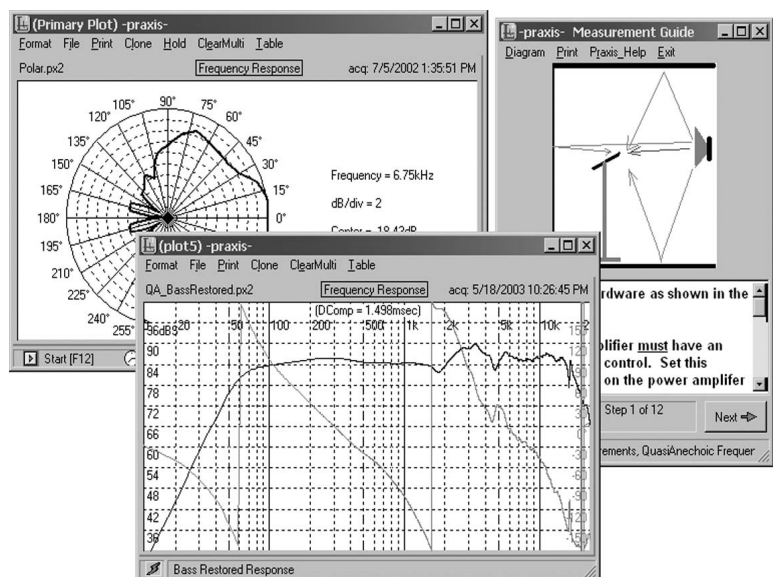
## PRAXIS audio measurement system

- Provides full-featured customizable measurement including loudspeakers, room acoustics, noise surveys, transducers, electronics, vibration testing, PA alignment, and quality control.
- Flexible, portable system advances with the latest 24bit/192kHz soundcard converter technology.
- Latest version always available online.
- Informative website includes technical articles and downloadable demos.
- Friendly small company. No endless voicemail!



[www.libinst.com](http://www.libinst.com)

Liberty Instruments, Inc., P.O. Box 1454, West Chester, OH 45071 USA  
Phone/Fax 513 755 0252, carolst@one.net

alignment possibilities that might not be satisfactory for a woofer design.

We had already established that the vent duct volume was the major problem with the small driver VB subwoofer. For a given duct diameter, the duct length increases slowly as the box size decreases and increases quickly as  $f_B$  (box tuning) decreases. To minimize the duct length, use the largest possible box and the highest possible  $f_B$ . These are not requirements that help you produce a small subwoofer enclosure with a low  $f_3$  cut-off frequency!

We investigated the MCM #55-2421

(#194) and TBspeakers W8-704C (#197) drivers via computer to establish designs of acceptable size and cutoff frequency that had reasonable duct lengths.

### MCM DRIVER

The alignment developed for this driver has a bass response that is "shelved" down from the passband response. While this results in some sensitivity loss, the intent was to keep box volume ( $V_B$ ) and  $f_B$  as high as possible to minimize vent duct length. *Figure 1* shows performance of the VB design for the pair of drivers. The net box volume is  $0.7\text{ft}^3$  and the  $f_B$  is about 37.5Hz.

The performance of the two samples match well in this box containing absorption damping; note  $Q_A$  is set to 10 for a total box Q of 4.8. This alignment's shelved LF response pushes  $f_3$  down to about 34Hz for a loss in sensitivity of perhaps 3dB.

*Figure 2* shows other system results. Note that the port output dominates the system output below 52Hz and the group delay curve looks OK for a sub-

woofer. *Figures 3* and *4* show the effect on the two samples of altering the tuning by  $\pm 2.5\text{Hz}$ . It is clear you can play with the tuning to trade off sensitivity loss for a lower  $f_3$ . Using equations provided by David Weems, based on years of studying duct length in boxes containing damping, the computed length for  $f_B = 38\text{Hz}$  is about 29" for a 4" ID vent duct and about 15½" for a 3" ID vent duct.


### TBSPEAKERS DRIVER

The design software showed that changing net  $V_B$  over the range 0.5 to  $0.9\text{ft}^3$  had almost no effect on the highest  $f_B$  value that could be used with the #197 driver. Since duct length changes rapidly with  $f_B$  and slowly with  $V_B$ , this was not a great help. Again, the designs developed were for damped boxes with  $Q_A = 10$ , total box  $Q = 4.8$ .


We liked the results best with a net  $V_B$  of  $0.8\text{ft}^3$  and  $f_B$  around 32Hz. *Figure 5* shows both driver samples in this design yielding  $f_3$  around 30Hz. Note there is no sensitivity loss with this design, the response showing a dB or two

**TABLE 4**  
**CATALOG VERSUS MEASURED DATA FOR TBspeakers W8-704C (#197) DRIVER**


	CATALOG	UNIT A	UNIT B
$f_s$ — Hz	28	29.8	29.7
$Q_{ES}$	0.30	0.52	0.47
$Q_{MS}$	10.33	11.86	11.78
$Q_{TS}$	0.30	0.50	0.45
$V_{AS}$ — $\text{ft}^3$	0.81	0.61	0.61
$V_{AS}$ — L	23	17.1	17.2
SPL dB/W/m	84	81.2	81.6

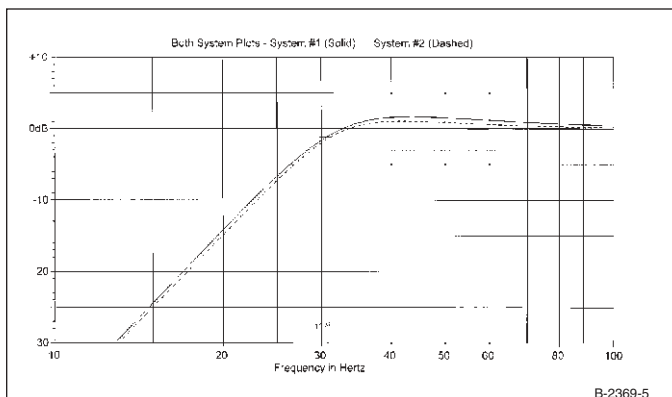


**FIGURE 5: Computer VB designs for TBspeakers W8-704C (#197) driver pair.**

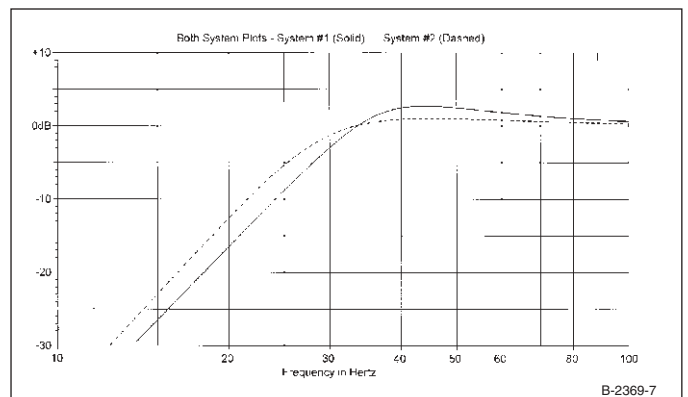

**FIGURE 7: Effects of changing the tuning with TBspeakers driver unit A.**

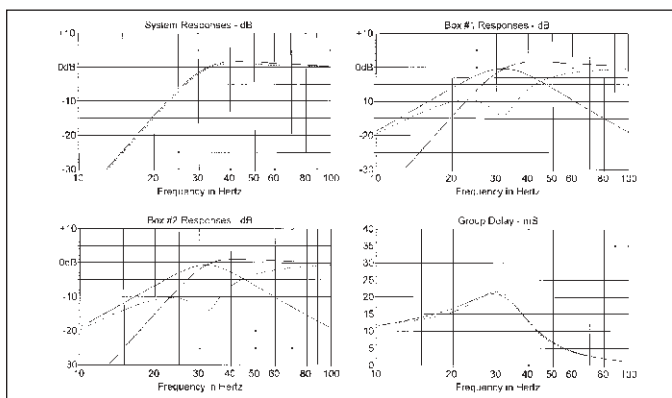

**FIGURE 6: Other system performance for TBspeakers W8-704C (#197) driver pair.**

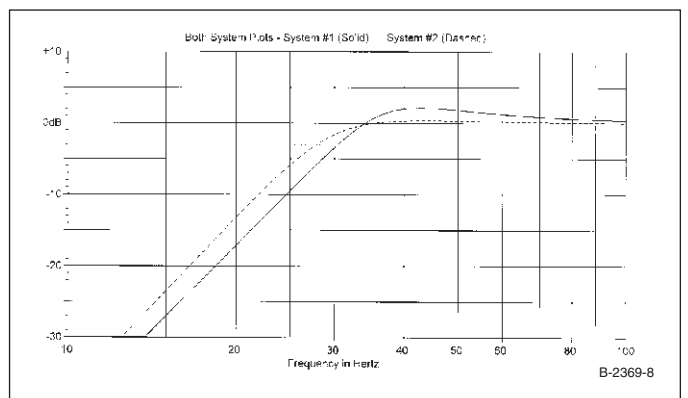

**FIGURE 8: Effects of changing the tuning with TBspeakers driver unit B.**



peaking from 100 down to 40Hz.

Figure 6 shows that the vent output dominates below 45Hz and the group delay looks reasonable. Figures 7 and 8 show that tuning variations from 30 to 35Hz for both samples produce some

shape change with  $f_3$  ranging from about 28 to 30Hz depending on how you define it. The computed duct lengths for this design at  $f_B = 32$ Hz are 36" long for a 4" ID duct and 20" for a 3" ID duct.

We designed and built enclosures for both the MCM #55-2421 (#194) and TBspeakers W8-704C (#197) drivers.

ed useful small subwoofers; however, we thought the more interesting system was that using the TBspeakers W8-704C (#197) driver. The remainder of this article covers that system.

### VERIFYING THE DESIGN

We tested TBspeakers driver unit A in a net test box volume of 0.818ft<sup>3</sup>. Figure 9 shows the input impedance plot indicating  $f_{MIN}$  at 31.5Hz. Figure 10 shows the cone and port near-field



PHOTO 6: Front view of TBspeakers W8-704C (#197) driver.

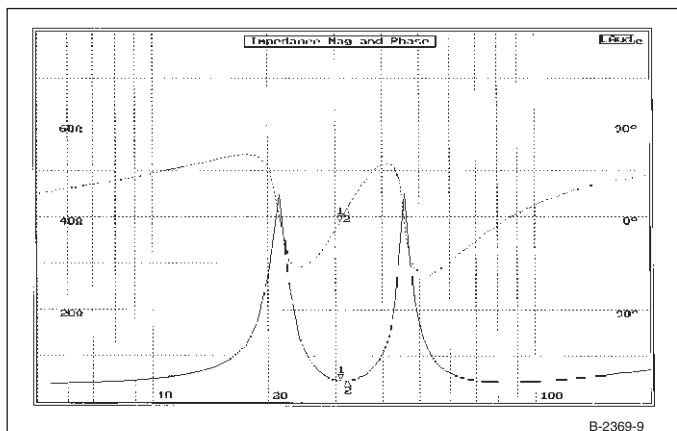


FIGURE 9: Input impedance for test of TBspeakers driver unit A in a VB.

## GRANDMOS

The SMART amplifier



## 2 Audiophile Masterpieces for the DIYer

## TRIPHON

The ULTIMATE crossover system



- ✓ Probably, the nearest approach to :  
"A STRAIGHT WIRE WITH GAIN".
- ✓ High end 2 x 100 W<sub>RMS</sub> / 8 ohms MOS-FET amplifier.
- ✓ SILVER plated PTFE / fiberglass printed circuit boards.
- ✓ SILVER plated connections.
- ✓ Military grade components.
- ✓ Only J-FET and MOS-FET audio transistors.
- ✓ NO CAPACITOR in the sound path\*.
- ✓ Minimum wiring and easy construction.
- ✓ Outstanding performances.
- ✓ Absolute Transparency and Sound.
- ✓ Extremely reliable.
- ✓ Steady performances over years.

\* : under certain conditions

To complete the GRANDMOS (or any good quality amplifier) we have designed the TRIPHON system :

- ✓ Musically neutral and transparent.
- ✓ 3-way electronic crossover.
- ✓ 6 or 12 dB/octave slope (true LINNKWITZ-RILEY filter).
- ✓ 4-channel Class A minimalist MOS-FET amplifier for MID and HIGH frequencies.
- ✓ Choice of cut-off frequency.
- ✓ PTFE / fiberglass printed circuit boards.
- ✓ Fully discrete component technology.
- ✓ SILVER plated connections.
- ✓ Minimal wiring.

by  
**Selectronic**  
L'UNIVERS ELECTRONIQUE

[www.selectronic.fr](http://www.selectronic.fr)

Phone : + 33 - 328 550 328 - Fax : +33 - 328 550 329  
BP 513 59022 LILLE - FRANCE

>> Detailed information on [www.selectronic.fr](http://www.selectronic.fr) or by e-mail to : [selectrocom@selectronic.fr](mailto:selectrocom@selectronic.fr) <<

magnitude responses set to the proper relative level. With  $f_B$  slightly below 30Hz (measured at 29.6Hz on screen), the box is a bit big and tuned a bit low. Note the port dominates the system output below about 43Hz as the design predicted (Fig. 6).

The system response (Fig. 11) is about as predicted up to 80Hz. The response droop above 70Hz is probably built right into the driver. This is a nice-looking response usable from 29Hz to about 100Hz within 3dB. You should keep the upper crossover limit near 100Hz with this driver.

The measured system group delay (Fig. 12) is noise free and thus valid above about 25Hz. This curve is worse than predicted, possibly because the test box is a bit big and tuned a bit low.

## ENCLOSURE DESIGN

This design requires a net box volume of 0.8ft<sup>3</sup> with  $f_B$  near 32Hz. Using 4" ID pipe for the vent gave an estimated length of 36". We tried to implement

such a port using 4" ID PVC thin-wall (drain) pipe. Any box using this port diameter was going to end up bigger than our previous 12" driver IB sub-woofer!

We decided on the fallback approach using 3" ID pipe with end flares. We obtained 3" ID Precision Port™ kits, each of which consists of an external flare that has flange screw holes for mounting, an internal flare, two connecting collars, and a 12" length of 3" ID pipe. All pieces are listed as made of ABS plastic. Photo 8 shows the pieces for a Precision Port™ kit and one kit assembled.

Clearly the straight port kit is not long enough as shipped; we would need to "fold-up" a longer duct. We found that thin-wall 3" ID PVC drain-pipe elbows were somewhat compatible with the flares: The ABS and PVC pipe IDs are the same, but the ODs are different. With a bit of work you can mate the parts to yield a port duct with a smooth inside wall.

Precision Sound Products gives an equation for computing the needed duct length from end to end with the flares. For a net box volume of 0.8ft<sup>3</sup>, you need an overall physical duct length of about 22" for  $f_B = 32$ Hz and 25" for  $f_B = 30$ Hz. We did not know at the time whether their equation factored in damping for the box.

Note that these lengths are a bit longer than those predicted by the Weems equations for a straight 3" pipe in a damped box. Reference 5 had reported that using the flared ends required a duct slightly longer than a straight duct producing the same tuning.

We purchased numerous 3" ID thin-wall (drain) PVC fittings and developed coiled ports of about 25" total length. Two approaches looked reasonable.

One featured the port exit on the box rear with the duct coiled against the bottom of the box right up to the front panel and then part way back toward the rear. The driver would sit



PHOTO 7: Back view of TBspeakers W8-704C (#197) driver.



PHOTO 8: Precision Port™ components.

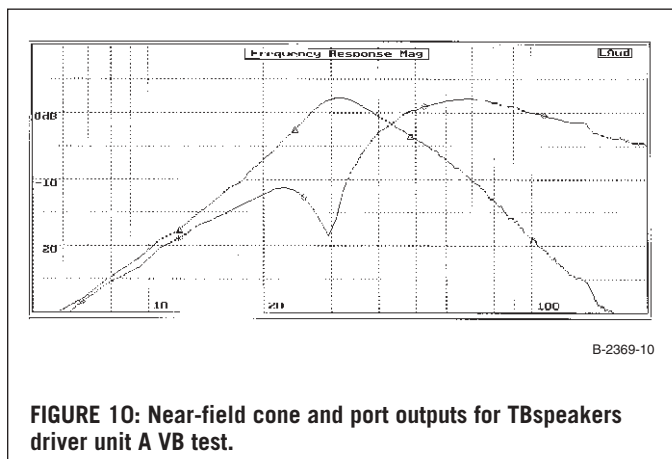


FIGURE 10: Near-field cone and port outputs for TBspeakers driver unit A VB test.

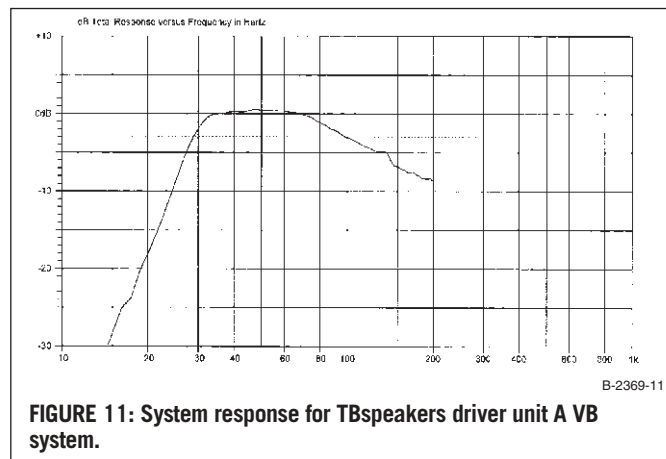


FIGURE 11: System response for TBspeakers driver unit A VB system.



above the duct. The box designed with this approach yielded a net box volume that was somewhat too big (0.87ft<sup>3</sup>) and with overall dimensions of 13" high, 13 1/4" wide and 15 5/8" deep. The net box volume is computed by subtracting the volume lost to the driver and vent duct assembly from the box gross volume.

The second design included the port exit at the side of the box with the duct coiled up behind the driver. The driver would then stand "clear" at the front of the box. With a net box volume of 0.8ft<sup>3</sup> and a 25" total duct length, the external box dimensions were 14" high by 14 3/4" wide by only 12 3/8" deep.

The W8-704C (#197) driver has a very large diameter magnet structure (*Photo 7*), and this box design gives more room for the rear of the cone to breathe. We considered this one to be the better design, so we built it. The duct design was such that it could easily be shortened from 25" to 23", but any further shortening would be a big problem.

## BASIC CONSTRUCTION

The boxes are constructed with 3/4"

thick industrial quality particleboard with appropriate stiffeners added. We believe that heavy, powerful drivers should be tied tightly to a very stiff front panel. We mounted the drivers with 10-24 machine screws into T-nuts. The front panel has stiffeners that tie it to the box corners and walls and that are positioned to retain the T-nuts which do not "bite" well into particleboard. This bracing may seem excessive, but our experience is that producing fast and taut bass requires keeping the driver from moving and the box from "ballooning."

We used yellow glue and 1 5/8" long panel nails to build the box. Where nails passed through a particleboard panel, we drilled a hole with a #51 bit (0.067") to assure that the nail traveled straight into the edge of the mating panel. We set all nails in from outside panels below flush to permit sanding the panel.

The basic building approach was to cut out and fabricate all the major box panels. We then assembled the basic panels, except for the tops, and working through the open top installed most in-

# Look!!

Click <http://www.eifl.co.jp>  
or send e-mail to [info@eifl.co.jp](mailto:info@eifl.co.jp)  
for more products information

- STAX
- SONY (MDR-R10)
- audio-technica
- SHELTER
- KOETSU
- DENON
- TANGO (ISO)
- TAMURA
- HASHIMOTO (SANSUI)
- FOSTEX
- JAPANESE AUDIO BOOK




**E-I-F-L**

EIFL Corporation

1-8, Fujimi 2-chome, Sayama City, Saitama Pref. 350-1306 JAPAN.  
Phone: +81-(0)4-2956-1178 FAX: +81-(0)4-2950-1667  
E-mail: [info@eifl.co.jp](mailto:info@eifl.co.jp)  
Wire Transfer: MIZUHO BANK, SWIFT No. MHBKJPJT a/c # 294-9100866
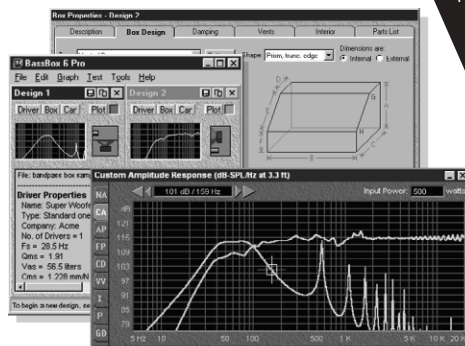
## Design speaker boxes with BassBox Pro

Design speaker boxes for any space: car, truck, van, home hi-fi, home theater, pro sound, studio, stage, PA and musical instruments. Import acoustic measurements. For example, the response of a car can be imported to simulate the in-car response.



\$129 plus S&H

## Need help with your speaker designs? BassBox Pro & X-over Pro can help!



Harris Tech Pro software for Microsoft® Windows can help you quickly create professional speaker designs. Our software is easy to use with features like "Welcome" windows, context-sensitive "balloon" help, extensive online manuals with tutorials and beautifully illustrated printed manuals. We include the world's largest driver database with the parameters for many thousands of drivers.

For more information please visit our internet website at:  
**www.ht-audio.com**


Tel: 269-641-5924  
Fax: 269-641-5738  
sales@ht-audio.com

Harris Technologies, Inc.  
P.O. Box 622  
Edwardsburg, MI  
49112-0622  
U.S.A.

\$99 plus S&H

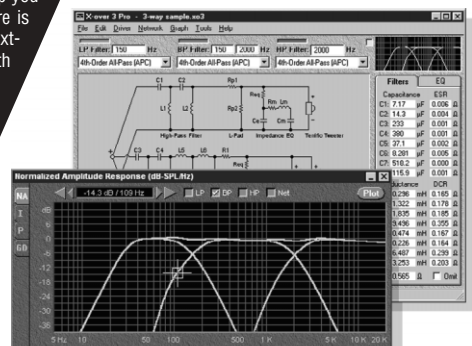
## Design crossovers with X-over Pro

Design 2-way and 3-way passive crossover networks, high-pass, band-pass or low-pass filters, impedance equalization, L-pads and series or parallel notch filters. Its Thiele-Small model provides professional results without complex testing.


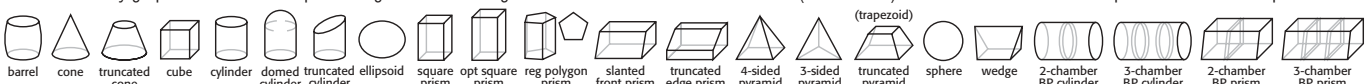
### Sophisticated Driver Modeling and Advanced Box Design

- Multiple drivers with isobaric, push-pull and bessel options. • 3 dual voice coil wiring options. • "Expert Mode" dynamically analyzes driver parameters. • Design closed, vented, bandpass and passive radiator boxes. • "Suggest" feature provides fast box design. • All box types account for leakage losses and internal absorption.
- Advanced vent calculation. • Bandpass boxes can be single or double-tuned with 2 or 3 chambers. • 22 box shapes (shown below). • Open up to 10 designs at one time.
- Analyze small-signal performance with: Normalized Amplitude Response, Impedance, Phase and Group Delay graphs. • Analyze large-signal performance with: Custom Amplitude Response, Max Acoustic Power, Max Electric Input Power, Cone Displacement and Vent Air Velocity graphs. • Includes a helpful "Design Wizard" for beginners.



### Passive Crossover Filters and Scalable Driver Modeling

- 1st, 2nd, 3rd and 4th-order "ladder" filter topologies. • Parallel crossover topology. • 2-way crossovers offer Bessel, Butterworth, Chebyshev, Gaussian, Legendre, Linear-Phase and Linkwitz-Riley filters. • 3-way crossovers offer All-Pass Crossover (APC) and Constant-Power Crossover (CPC) filters. X-over Pro's capabilities scale to fit the amount of driver data. • A crossover, filter or L-pad can be designed with just the nominal impedance of each driver. • With full Thiele-Small parameters, impedance equalization can be designed and the performance graphed.
- Graphs include: Normalized Amplitude Response, Impedance, Phase & Group Delay. • Graphs can include the full speaker response including the box. • Estimate component resistance (ESR & DCR). • Calculate the resistance of parallel or series components.

Copyright © 2002 by Harris Technologies, Inc. All rights reserved worldwide. BassBox is a trademark of Harris Tech. Other trademarks belong to their respective companies. Harris Tech reserves the right to make changes without notice. All prices are in U.S. dollars.

ternal items, including assembly of the vent duct. To provide the absorptive damping included in the design, we covered the walls with a 1" thickness of Owens-Corning (OC) #705 material. You can substitute your favorite VB damping approach.

Finally, we installed the top, cut oversized, and then routed it flush with the side walls. We then installed the stiffeners and damping material associated with the top through the driver hole.

The simple way to build a pair of sub-


woofer boxes is to purchase an industrial-quality particleboard sheet (which is actually 49" by 97") and have the lumberyard cut off two 97" long strips 12½" wide. You can cut the remainder into two reasonable strips for easy handling. Having the sheet cut into three 12½" wide strips provides spare material if you make a cutting mistake. You can cut all major panels for the #197 subs from the 12½" wide strips and fabricate the other pieces from the remaining particleboard.

## FRONT PANEL CONSTRUCTION

To tie the driver securely to the front panel (FP), we mounted it with 1" long 10-24 pan head machine screws and T-nuts. With 8" drivers the clearances become tight. It is critical to position the mounting screw holes so that the screw heads clear the lip on the outer edge of the pressed-metal driver rim. This means pressing the bolt heads into the gasket on the driver's front during installation, but the gaskets seemed to recover just fine. The T-nuts also start to




PHOTO 9: Rear view of front panel with driver mounted.

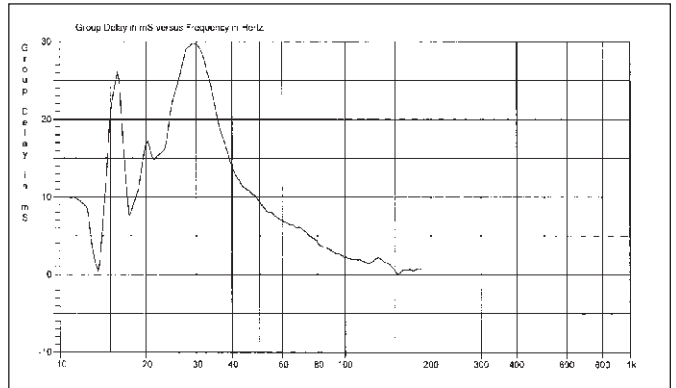

B-2369-12

FIGURE 12: System group delay for TBspeakers driver unit A VB system.

**NEW!** From

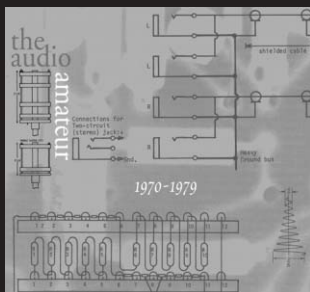

## The Audio Amateur-The 1970s

Now available, the first decade of the parent magazine of *audioXpress*! The entire collection of issues of *The Audio Amateur* from the 1970s is reproduced electronically on CD. Includes issues from 1970, 1972, 1974, and 1978 which are no longer available in printed form. Take a fascinating journey into the first decade of Audio Amateur's rich DIY audio history. You'll find interesting projects for a variety of audio components, interviews with some of the 'founding fathers' of hi-fi, and company visits—including a look at kit giant, Heathkit. The linked indexes will allow you to easily navigate this disc. 2004, CD. Shipping wt: 1 lb.

CDA470S \$39.95

Old Colony Sound Laboratory, PO Box 876,  
Peterborough, NH 03458-0876 USA  
Toll-free: 888-924-9465 Phone: 603-924-9464  
Fax: 603-924-9467  
E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)  
[www.audioXpress.com](http://www.audioXpress.com)

To order call 1-888-924-9465  
or order on-line at [www.audioXpress.com](http://www.audioXpress.com)



intrude into the hole for the driver, but do not hit the driver so this presents no problem.

With high-displacement drivers it is important to relieve the back of the FP so the cone's rear can breathe. The W8-704C (#197) driver throws you a bit of a curve by having six frame ribs and eight mounting holes, so some ribs do not line up with mounting points. The solution was to relieve the driver hole everywhere between the T-nuts.

Our approach to constructing the FP was as follows:

1. Cut a driver-mounting hole of the proper diameter for the intended driver at the correct location on the FP. Note the boxes are built as mirror image pairs in terms of woofer offset from the vertical centerline.
2. Mark the location of the eight mounting screw holes. Orient the drivers so the mounting holes fall on horizontal and vertical lines. Be sure to make the holes on a small enough circle (about 7.7" diameter for our hardware) so the machine screw heads will clear the outer lip of the pressed-metal driver rim. Our 10-24 pan head machine screws had a 0.365" diameter head.
3. Drill a #10 (0.193" diameter) hole at each mounting screw location. This will be snug on a #10 machine screw.
4. Verify that you can install the mounting screws through the driver and FP and secure them with the T-nuts on backwards. Outline the area on the back of the FP covered by each T-nut.
5. Remove the driver and relieve between the T-nut locations. We used a routing bit that cuts at a 45° angle to a depth of 0.430" for both drivers. This depth takes you down to the start of the rear openings in the driver frame.
6. Drill the back of the mounting screw holes to the proper diameter and depth to take the T-nuts. Our T-nuts required a 0.250" hole.
7. Install the T-nuts so all three spikes grab particleboard. We pressed the T-nuts in with a vise after installing a 3/4" long machine screw to assure they stayed aligned with the #10 hole.
8. Verify that you can mount the driver. It is much easier to fix any problem now than when the FP is mounted.

The FP/box stiffeners are designed so that they will retain the T-nuts, but this is not practical on the two T-nuts oriented at 45° on the wide side of the FP. To retain these T-nuts, we installed #6 by 3/8" pan head sheet metal screws next to the T-nut and tightened the screws just enough to retain them.

Photo 9 shows a view of the back of the FP with the driver mounted showing the T-nuts and relieving and demonstrating the offset between frame ribs and mounting points.

Next issue we conclude construction of the subwoofer boxes. ❖

## REFERENCES

1. Koonce, G.R., and Wright, Jr., R.O., "The Infinite Box: Constructing a Subwoofer," *aX*, April 2002, p. 28, and May 2002, p. 42.
2. Koonce, G.R. and Wright, Jr., R.O., "The Infinite Box Concept," *aX*, January 2002, p. 8, and February 2002, p. 38.
3. Raczyński, B., "How Good Is Your Port?," *aX*, Sept. 2001, p. 24.
4. Salvatti, A., Devantier, A., and Button, D. J., "Maximizing Performance From Loudspeaker Ports," *JAES*, Jan/Feb. 2002, Vol. 50, No. 1/2 pp. 19-45.
5. Moriyasu, J., "A Flared Port Study," *aX*, July 2002, p. 28.
6. David Weems, personal communication.

## SOURCES

Creative Sound Solutions, 32-32691 Garibaldi, Abbotsford, BC Canada, 604-504-3954, [www.creativesound.ca](http://www.creativesound.ca)

MCM Electronics, 650 Congress Park Drive, Centerville OH 45459, [www.mcmelectronics.com](http://www.mcmelectronics.com), 937-434-0031

Nuera Acoustic Technology, 6538 Albery Place, Burnaby, BC Canada, V5E-4G2, 604-517-6683, [www.nuera-acoustic.ca](http://www.nuera-acoustic.ca)

Representative in the continental US: 604-805-3867, between 9am and 7pm PST, FAX 604-517-6693 (our source for TBspeakers drivers)

Owens-Corning - For information on obtaining the #705 damping material call the Customer Service Center: 800-328-7617

Parts Express, 725 Pleasant Valley Dr., Springboro, OH 45066-1158, 1-800-338-0531, [www.partsexpress.com](http://www.partsexpress.com)

Precision Sound Products, 815-599-0662, [www.psp-inc.co](http://www.psp-inc.co)

RAW Acoustics, 16756-85 Ave., Surrey, BC Canada, V4N-4W3, 604-576-8951, [www.rawacoustics.ca](http://www.rawacoustics.ca)

Ultimate Sound, 437 W. Grimes Creek Rd., Bayfield, CO 81122, 1-888-900-9687, [www.ultimate-sounds.com](http://www.ultimate-sounds.com) (Our source for MA-Audio drivers)

# Silver Flute

Since we introduced the Silver Flute line of woofers, customer response has been tremendous. These drivers offer a fantastic value.

- Wool fiber cones
- Cast frames
- Rubber surrounds
- Large voice coils

We currently offer these speakers in three sizes, 5", 6.5" and 8". The 5", 6.5" and 8" are available magnetically shielded. We also have 4 ohm versions of the 5", 6.5" and 8" unshielded. We will continue to expand the line to meet your needs.

### W14RC25

Fs 43.5 Hz  
Qts 0.35  
Vas 18.9 ltrs  
X-max 3.5mm  
Sens. 87.5dB  
Price \$15.90



### W14RC25-S

Fs 43.5 Hz  
Qts 0.40  
Vas 18.9 ltrs  
X-max 3.5mm  
Sens. 87dB  
Price \$17.60



### W17RC38

Fs 40.5 Hz  
Qts 0.29  
Vas 28.2 ltrs  
X-max 5mm  
Sens. 89dB  
Price \$22.30



### W17RC38-S

Fs 41.3 Hz  
Qts 0.31  
Vas 24.3 ltrs  
X-max 5mm  
Sens. 88dB  
Price \$27.90



### W20RC38

Fs 30.8 Hz  
Qts 0.23  
Vas 83.3 ltrs  
X-max 5mm  
Sens. 91dB  
Price \$28.35



MADISOUND SPEAKER COMPONENTS, INC.  
8608 UNIVERSITY GREEN  
P.O. BOX 44283  
MADISON, WI 53744-4283 U.S.A.  
TEL: 608-831-3433 FAX: 608-831-3771  
e-mail: [info@madisound.com](mailto:info@madisound.com)  
Web Page: <http://www.madisound.com>

# A Bottom Octave Compensator

This simple equalizer can compensate a typical sealed-box woofer to be anechoically flat to any arbitrary low frequency—20Hz, in the example shown. **By Dennis Colin**

I'm angry and I'm not going to take it! I'm tired of "subwoofers" that are -3dB at 40Hz, or even higher! This is what normal woofers used to do since about 1958, courtesy of the Acoustic Research AR-3 and fellow clones. Now, with a plethora of mini-monitors, albeit of excellent midrange and treble quality, you have "woofers" with an  $f_3$  of 70Hz or so (of course, the biggest joke is "computer subwoofers" that, if lucky, can squeak out a little bit of 60Hz!).

When not listening at the maximum volume your system is capable of, you can equalize most decent sealed woofers to compensate their 12dB/octave (anechoic) rolloff to be flat to 20Hz. Note: Room gain doesn't take effect in typical rooms until below 30Hz. And if the speaker is anechoically flat to 20Hz, a little bit of boost at 20Hz (5dB in my room) is welcome; this helps your hearing rolloff at less than concert-hall volume (Fletcher-Munson, et al.).

There is actually more lowest-octave content in recorded material than is


**Warning! This compensator generates a 12dB/octave rise below the sealed woofer's box frequency (fb), equalizing the woofer's 12dB/octave (2nd order) rolloff slope down to a selectable frequency. Do not use this with vented systems! Besides having twice the rolloff slope, the woofer cone is unrestricted (except by the suspension) below the system rolloff frequency. Applying high power with boosted ultra-low frequencies could easily damage a vented woofer.**

often believed. Besides pipe organs and synthesizers, for example, bass drums and tympani can have significant transient-excited sideband content at and even below 20Hz. You can feel (if not quite hear) this in a concert hall or large club venue; it gives a sense of very deep ambience, like rolling thunder. So why not reproduce it?

## CIRCUIT HISTORY

Figure 1 is just one variant of a circuit

old enough to be called historic. In 1966, my EE professor called it a "2nd order differential equation solver," and that it is (they had vacuum tube op amps then, made by George Philbrick!). Around 1971, while designing the ARP2600 music synthesizer, I presented a paper to the Audio Engineering Society with a title suggested by David Friend of ARP: "The Electrical Design and Musical Applications of a Combination Voltage Controlled Highpass, Bandpass, Lowpass, Band Reject Filter Resonator." (I would have entitled it "A Voltage Controlled Filter," but Dave was the marketing manager!) This circuit used the "new" solid-state op amps, along with analog multipliers for voltage control of

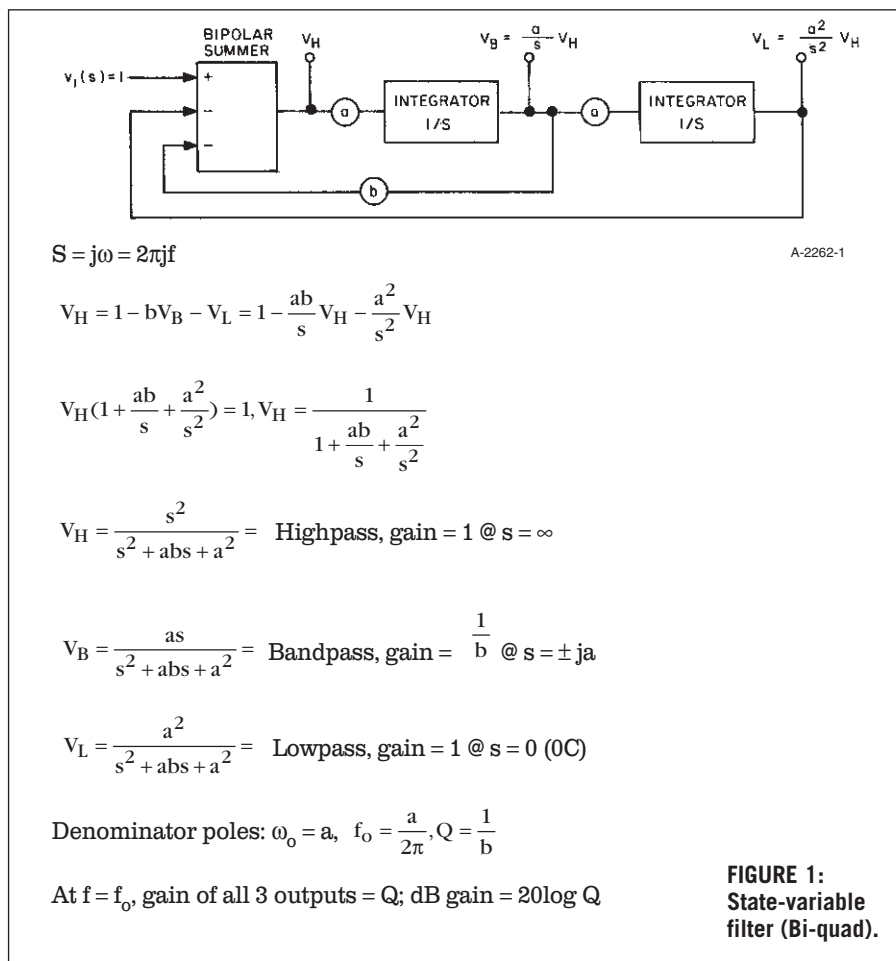



rolloff frequency and Q. ARP made it their module 1047; one was bought by

The Who and used in their song about "We Won't Get Fooled Again."



PHOTO 1: The bottom octave compensator.

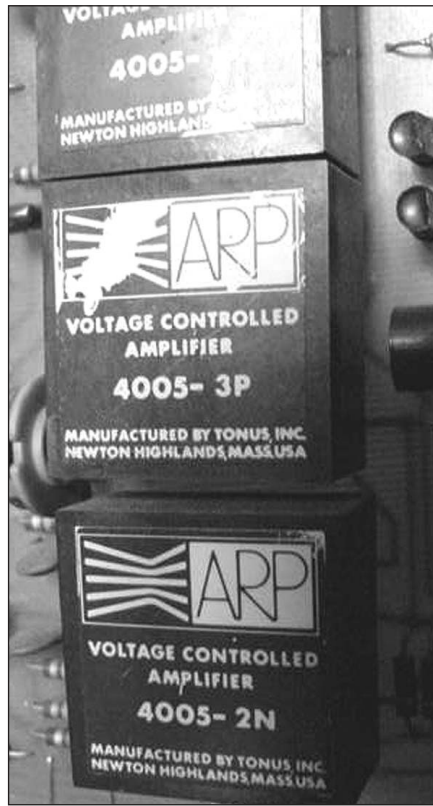


PHOTO 2: Potted all-discrete multipliers.

Photo 1 shows the unit; Photo 2 shows the potted all-discrete multipliers. Photo 3 shows a similar filter I just breadboarded with today's components, using the CA3280 operational transconductance amplifiers to achieve voltage-controlled filter frequency range of 1Hz to 74kHz. Photo 4 shows this filter's notch output used to display the 12.027% THD of a symmetrical triangle waveform.

Today this circuit is often simply called a "Bi-quad." That's because its Laplace transfer function is the ratio of two quadratic polynomials in  $s = j\omega + \sigma$  ( $\omega = 2\pi * \text{frequency}$ ;  $\sigma$  is the damping coefficient). The circuit allows adjustment of all six polynomial coefficients. With variable coefficients, the circuit is sometimes referred to as a "state-variable filter."

### STATE-VARIABLE FILTER— BASIC TOPOLOGY

Figure 1 shows a block diagram configured for independent control of  $f_o$  (rolloff or center frequency) and Q. The input ( $V_1(s)$  in Laplace terminology) is set to 1, which means a flat spectrum



**Welborne Labs**

**Online**

More than just a resistor & capacitor store.....checkout what's new at the Labs:

Our new **ULTRAPATH bp** tube linestage is the first battery powered all-tube preamp kit to hit the market. Based on Jack Elliano's original Ultrath path circuit and utilizing the 6GM8/ECC86 tube which was developed solely for automotive applications, the **ULTRAPATH bp** sports several interesting design features:

- Unique Ultrath path Circuitry
- Dual-Mono Design
- Independently Switched Sources and their Grounds
- Transformer Coupled Output w/xtra Headphone Tap
- Low Voltage Battery Supply: 24V B+ w/6V Filament
- A large selection of options and add-ons



**Our Basic Kit Version is just \$695 Complete! The Ultimate Version (pictured) is \$1250.**

**www.welbornelabs.com**

**tel: 303-470-6585**

-- We Ship World Wide --

unit impulse stimulus. This is fed through a bipolar summer (no, not a psychotic vacation) and a gain coefficient "a" to an integrator (such as an inverting op amp with resistive input and capacitive feedback). Negative feedback is applied back to the input through coefficient "b." This integrator output also feeds a second coefficient "a" and a second integrator, the latter also negatively fed back to the input, but with unity gain coefficient.



The multiple integrator feedback loops produce highpass ( $V_H$ ), bandpass ( $V_B$ ), and lowpass ( $V_L$ ) outputs, all with a common quadratic (2nd order) denominator. Figures 2a, b, and c show decibel versus log frequency (Bode) plots. Note that coefficients "a" determine  $f_0$ , while "b" determines Q. Making "a" and "b" voltage-controllable, as with analog multipliers, allows independent and remote control of  $f_0$  and Q.

### OUTPUT SUMMING


Figure 3 shows that by summing the outputs with adjustable coefficients (H, B, L), the transfer function  $V_0/V_1$  (s) is the ratio of two quadratic polynomials

(biquad). Some of the many available responses are:

1. Highpass, bandpass, or lowpass; when two of the three coefficients "H," "B," "L" are zero.
2. Infinite notch, when "B" = 0.
3. Unity-Gain Allpass (phase shift with flat amplitude), when  $H = L = 1$  and  $B = -1$ .
4. Shelf responses (Figs. 4a, b) when  $H \neq L$ . Various combinations of peaking (at  $f_p$ ) and dipping (at  $f_z$ ) are possible, adjustable by  $Q_p$  and  $Q_z$ , respectively.

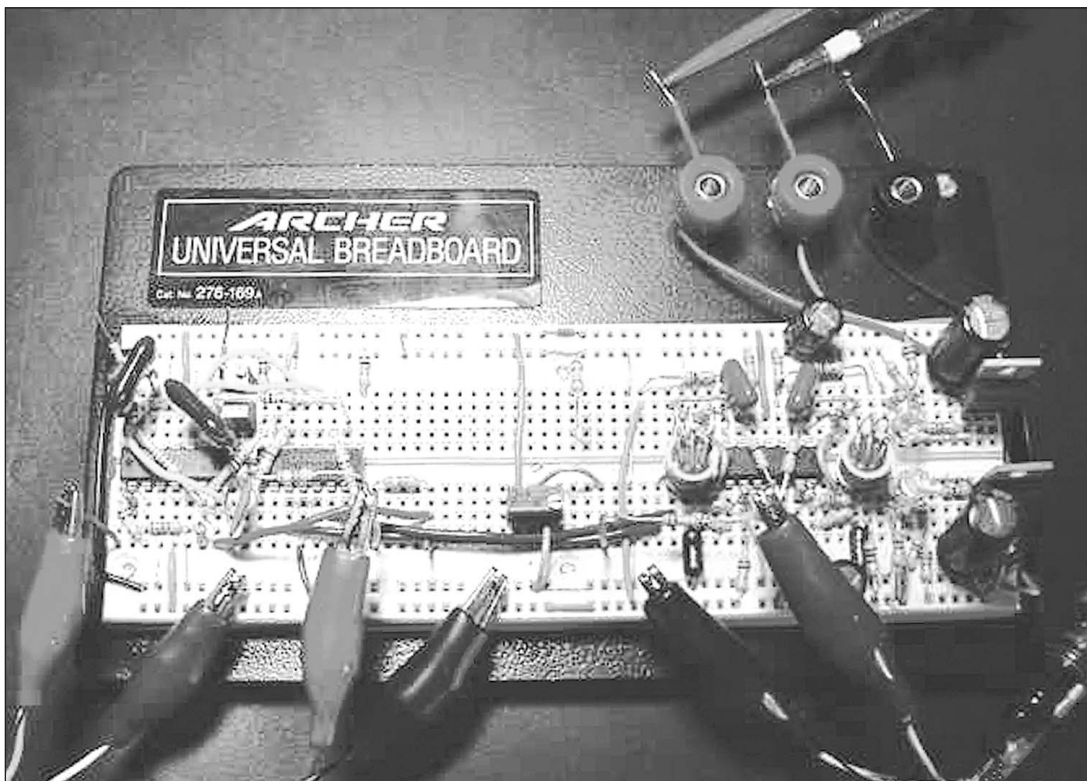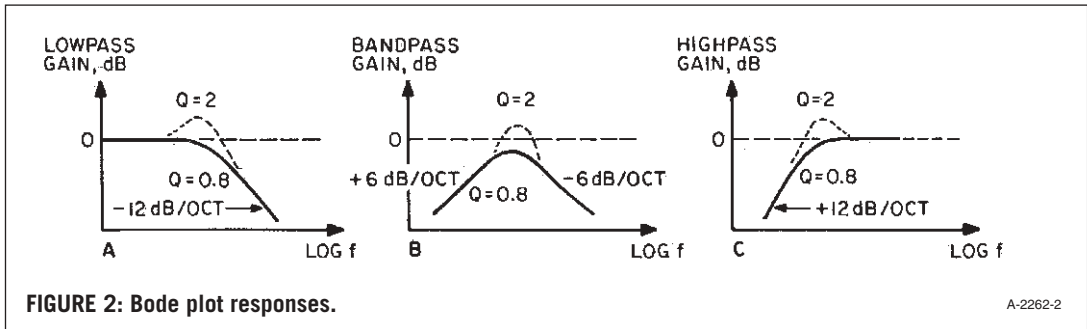

**PHOTO 3: A similar filter breadboarded with today's components.**

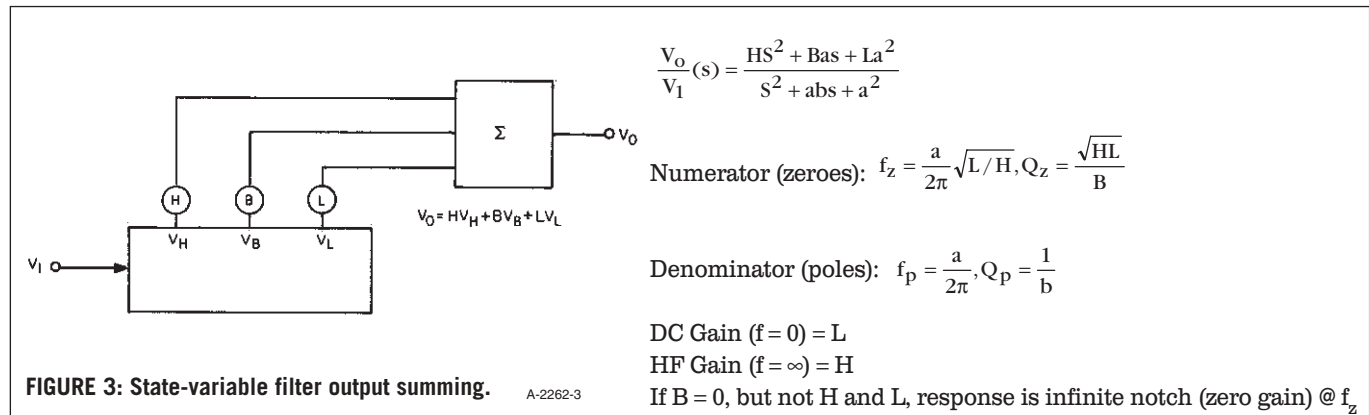



The response type in *Fig. 4a* is used for the sealed-box woofer bass extender (bottom octave compensator) to be described.

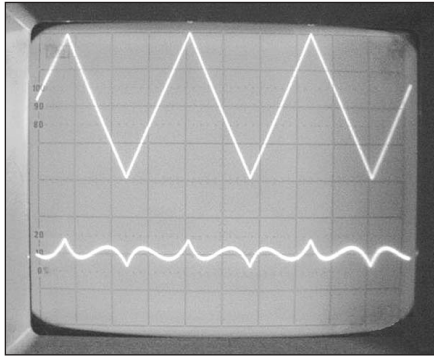


PHOTO 4: Notch output from *Photo 3*.

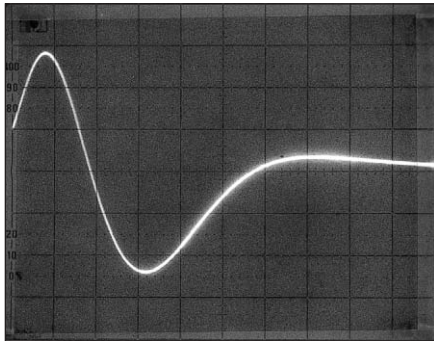


PHOTO 5A: Compensator of *Fig. 5*.

### ADDITIONAL HIGHPASS (HP) ROLLOFFS

In the circuit of *Fig. 5*, C1 and C6 provide a net 2nd order HP rolloff, which,

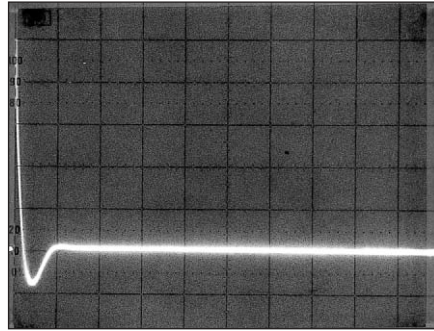


PHOTO 5B: Sealed woofer (simulated)  $f_b = 40.5\text{Hz}$ ,  $f_{-3} = 38\text{Hz}$ ,  $Q_b = 0.75$ .

combined with the *Fig. 4a* response and the woofer rolloff, results in an overall 4th order anechoic LF rolloff response at a subterranean frequency of your

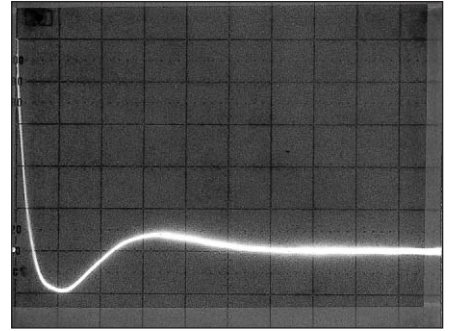


PHOTO 5C: Compensated woofer.

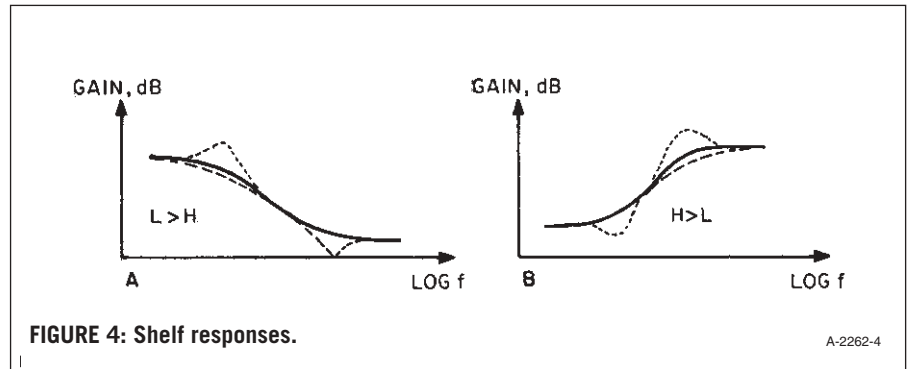


FIGURE 4: Shelf responses.

A-2262-4


# The CLIO system

Turns your PC into the most complete easy-to-use electrical and acoustical measurement system ...

NEW!



The CLIO system PCI

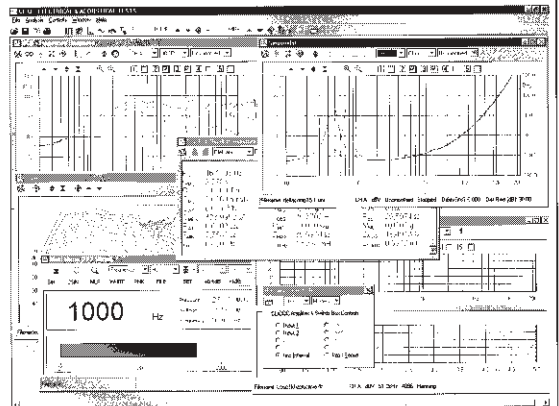

CLIOwin software


The **CLIO** system is a PC-based system for electrical and acoustical measurements. **CLIO** offers several measurement software, related measurement hardware and accessories. **A CLIO system is a complete test instrument**, 100% warranted by **Audiomatica**; all you need is to supply a compatible computer. **No Soundcards involved!**



CLIO is produced by **AUDIOMATICA** and is available also from



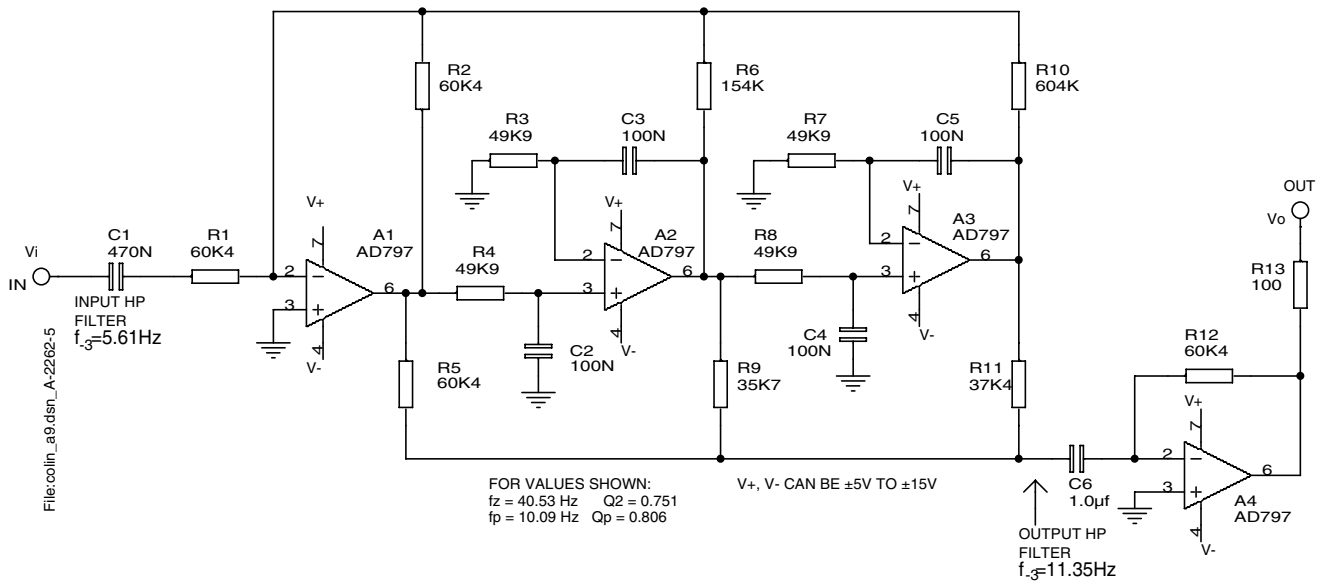[www.cliowin.com](http://www.cliowin.com)  
[www.audiomatica.com](http://www.audiomatica.com)



$$-H = 1 + B \frac{R_H}{R_B} + L \frac{R_H}{R_L}, -H = 1 + \frac{HR_H}{R_B RCS} + \frac{HR_H}{R_L (RCS)^2}$$

$$H[1 + \frac{R_H}{R_B RCS} + \frac{R_H}{R_L (RCS)^2}] = -1, H = \frac{-(RCS)^2}{(RCS)^2 + \frac{R_H}{R_B} RCS + \frac{R_H}{R_L}}$$

$$V_O = \frac{(RCS)^2 + \frac{R_H}{R_{BO}} RCS + \frac{R_H}{R_{LO}}}{(RCS)^2 + \frac{R_H}{R_B} RCS + \frac{R_H}{R_L}}$$

$$\text{Denominator (poles): } \omega_p = \frac{\sqrt{R_H/R_L}}{RC}, f_p = \frac{\sqrt{R_H/R_L}}{2\pi RC}$$

$$Q_p = \frac{R_B}{\sqrt{R_H/R_L}}$$

$$\text{Numerator (zeroes): } \omega_z = \frac{\sqrt{R_H/R_{LO}}}{RC}, f_z = \frac{\sqrt{R_H/R_{LO}}}{2\pi RC}$$

$$Q_z = \frac{R_{BO}}{\sqrt{R_H R_{LO}}}$$

$$Q_z = \frac{R_{BO}}{\sqrt{R_H R_{LO}}}$$

$$@ F = \infty, V_o = 1$$

$$\text{If } A(s) = as^2 + bs + c, \omega_0 = \sqrt{c/a} Q = \frac{\sqrt{ac}}{b}$$

In Fig. 5,  $R_H = R1 = R2 = R5 = R12$   
 $R_B = R6, R_L = R10, R_{BO} = R9, R_{LO} = R11$   
 $R = R3 = R4 = R7 = R8, C = C2 = C3 = C4 = C5$

FIGURE 5: Compensator schematic.

A-2262-5

choosing. Values in Fig. 5 and the following design procedure produce a well-damped roll-off to avoid excessive infrasonic ringing. Figure 6 shows responses for the values in Fig. 5 with a woofer  $f_b = 40.5\text{Hz}$ ,  $Q = 0.750$ .

### PRACTICAL CIRCUIT DESCRIPTION

Figure 5 shows a circuit designed specifically for sealed woofer compensation. It is an active equalizer with unity gain in the flat region above the compensated LF response, to be placed just before the power amp.

A2 and A3 are non-inverting integrators. While these require two

caps each, they avoid the need for additional inverting amps to restore overall positive polarity. R2, 6, and 10 provide the feedback of direct, integrated, and doubly-integrated signals as shown in Fig. 1.

R5, 9, and 11 perform the signal summing shown in Fig. 3; these resistors are inversely proportional to the coefficients H, B, L (Fig. 3), respectively. A4 is an output signal-summing amp. C1 and C6 provide the additional high-pass (HP) rolloffs previously described. Figure 7 is an analysis of this circuit.

### DESIGN PROCEDURE

1. Choose  $R1 = R2 = R5 = R12, R3 = R4 = R7 = R8, C2 = C4 = C5$  (suggested values in Fig. 5).
2. Select  $f_p = \text{LF rolloff of compensated speaker, Hz} \approx \text{compensator peak gain frequency}$ .
3. Set  $R_{10} = R_1 / (2\pi R_3 C_2 f_p)^2$  Note: Component designator numbers in subscripts to avoid math confusion.
4. Choose  $Q_p; Q_p = 0.800$  for response shown.
5. Set  $R_6 = Q_p \sqrt{R_1 R_{10}}$
6. Select  $f_z = \text{start-of-boost frequency, Hz}$ . This is not  $f_3$  of speaker, unless its  $Q = 1/\sqrt{2} = 0.707$ . It is the intersection of the speaker's asymptotic 12dB/octave rolloff slope (straight line on Bode plot) with 0dB speaker reference in its flat region, also called  $f_b$ .
7. Set  $R_{11} = R_1 / (2\pi R_3 C_2 f_z)^2$ .
8. Determine  $Q_z = \text{sealed woofer } Q$ .



9. Set  $R_9 = Q_z \sqrt{R_1 R_{11}}$ .
10. Set input RC rolloff:  $f(\text{in})_{-3} = 1/2\pi R_1 C_1$ .  
Set  $f(\text{in})_{-3} = 0.556f_p$ ;  $C_1 = 0.286/R_1 f_p$  (farads, ohms, Hz).
11. Set output RC rolloff:  $f(\text{out})_{-3} = 1/2\pi R_0 C_6$ , where  $R_0 = R_5, R_9$ , and  $R_{11}$  in parallel; set  $f(\text{out})_{-3} = 1.125f_p$ ;  $C_6 = 0.141/R_0 f_p$  (farads, ohms, Hz).
12. Build it and enjoy bottomless natural bass!

### TRANSIENT RESPONSE TESTS

I looked at square-wave responses using an actual sealed woofer with  $f_b$  (not  $f_{-3}$ ) of 40.5Hz and Q of 0.75, the

same parameters as the circuit of Fig. 5. Responses were much like a passive LCR circuit I also used (to simulate the woofer), but the latter was of course free of room effects (I'm using spectral components below 10Hz!). So I used the LCR circuit for the photos shown.

Photos 5a, b, and c are step responses (a 2.5Hz square wave was used; responses to positive step shown). Time scales are 20mS/division (200mS total span). Photo 1a is of the compensator alone, Photo 1b is the sealed woofer simulator, and Photo 1c is the combination (compensated woofer).

Note that the compensator (Photo 5a) response starts with a positive one division jump (representing the unity-gain HF response), followed by a "swept-frequency" cycle; the latter spectrally "contains" the boosted region in Fig. 6 of about 2.5–40Hz.

The negative-going overshoot in Photo 5b is the minimum-phase consequence of the (simulated) woofer's 2nd order rolloff below 40.5Hz. Note how in Photo 5c the compensator simply and smoothly extends the woofer step response's time scale. This follows from the woofer's  $f_{-3}$  being extended from 38Hz to 14Hz (Fig. 6).

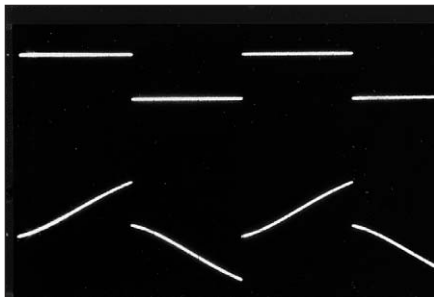


PHOTO 6A: Compensator square-wave response. Upper trace = input, lower trace = output. 40Hz.

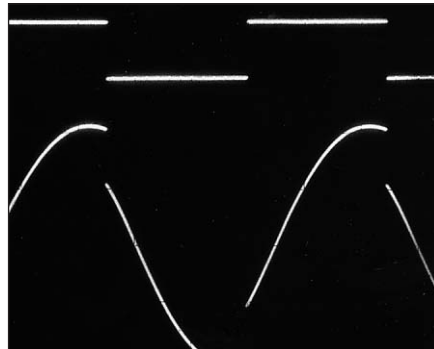


PHOTO 6B: 20Hz.

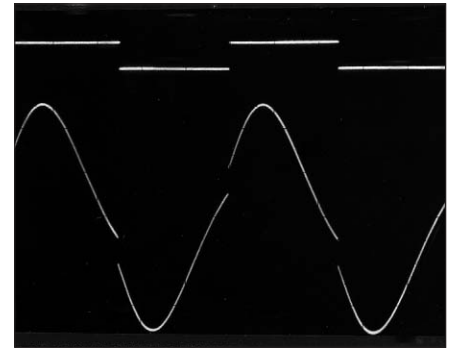


PHOTO 6C: 10Hz.

# SUPERB STEREO SOUND



ACCURATE • CRISP • CLEAN • CLEAR REPRODUCTION  
WITH THE **36D PERFECT PLAYBACK AMPLIFIER**

**ORDER TODAY!**

**www.vasgold.com • 631-686-6122**

Photos 6a, b, and c show the input and output responses of the compensator to a square wave at 40, 20, and 10Hz, respectively. The gains of 11dB at 20Hz and 18dB at 10Hz are evident.

But the proof of good transient response is in the combinational pudding. Photos 7a, b, and c show the woofer responses uncompensated (upper traces) and compensated (lower traces), to a square wave at 40, 20, and 10Hz, respectively. The extension of low-frequency content is clearly evident.

Notice also that no ringing has been added. In fact, the 20 and 40Hz compensated square-wave response shapes have been improved to a nearly ideal exponential decay. And while

the overall frequency response is nearly flat (-1dB) to 20Hz, it's the (minimum) phase shift of the components  $\geq 20$ Hz (due to the  $< 20$ Hz rolloff) that causes the exponential decay, even though the 20Hz square-wave input has no spectral content below 20Hz. A Fourier analysis of the lower Photo 7b waveform would show the square wave's odd harmonic series (20, 60, 100, 140 . . . Hz) with the 20Hz fundamental amplitude 1dB lower than in a perfect square wave, relative to the harmonics.

### COMPENSATOR USAGE

For several years, I've used this type of compensator to extend response to 20Hz, -1dB, with two sealed woofer sys-

tems: (a) an 8" Focal 8K416 (j) in a 0.91ft<sup>3</sup> box;  $f_b = 61$ Hz,  $Q_b = 0.54$ , and (b) a 10" Scan-Speak 25W/8565-01 in a 1.6ft<sup>3</sup> box;  $f_b = 40.5$ Hz,  $Q_b = 0.75$ ,  $f_{-3} = 38$ Hz. Available continuous power is 50W for the 8" Focal, 100W for the 10" Scan-Speak. Some observations:

1. For nearly all music except the deepest pipe organs and exaggerated synthesizer bass, I can drive the amp to clipping; what clips is not the boost-compensated ultra-low bottom octave. Most music doesn't have enough 20-40Hz content for this to clip the amp, even with 18dB boost at 20Hz.

However, much music has sufficient 20-40Hz content to hear and



PHOTO 7A: Woofer square-wave responses. Upper trace = uncompensated, lower trace = compensated. 40Hz.



PHOTO 7B: 20Hz.

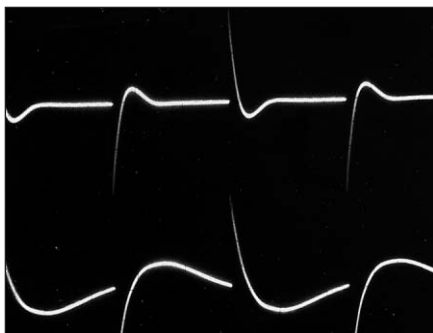


PHOTO 7C: 10Hz.

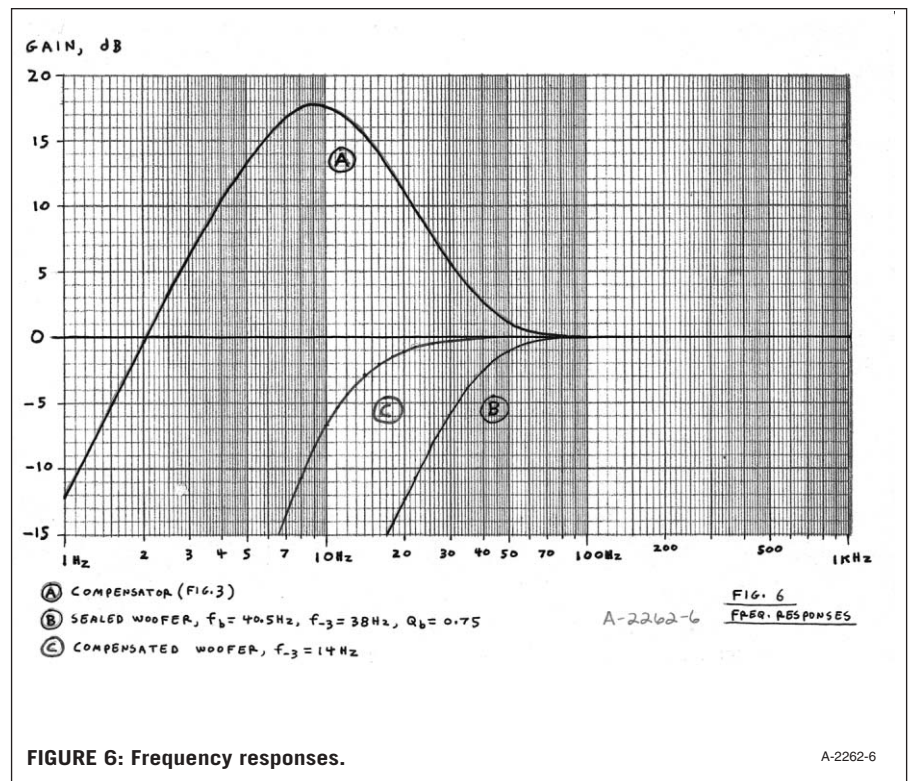


FIGURE 6: Frequency responses.

A-2262-6

### IMPORTANT SPECIFICATIONS

Woofer: Scan-Speak 25W/8565-01. Manufacturer data:  $f_s = 19$ Hz,  $V_{as} = 229$  ltr,  $Q_{TS} = 0.845$

Cabinet: 26"  $\times$  12"  $\times$  12" outside, 3/4" wood

Internal vol. = 1.563ft<sup>3</sup> = 44.26 ltr (not counting driver and brace vol.; negligible)

Center brace panel, 10.5in<sup>2</sup>  $\times$  3/4", 7" round hole.

Damping: three sides, bottom covered with Deflex rubber panels. Loosely filled with Acousta-stuff.

Calculated box parameters (not taking into account cabinet damping and adiabatic-to-isothermal resonance lowering):  $f_b = 47.2$ Hz  $Q_b = 0.845$

Measured box parameters:  $f_b = 40.5$ Hz  $Q_b = 0.75$   $f_{-3dB} = 38$ Hz.

Op Amps: I used TL074 Quad op-amp. For lowest noise and distortion, use Analog Devices AD797—expensive: \$9.48 ea. (Newark)—but very good; Noise = 0.9nV/ $\sqrt$ Hz (open-circuit thermal noise of 50 $\Omega$  resistor!)

THD = -120dB (0.0001%) at 20kHz

Note: Only A1 and A4 pass full-range audio, so you could use AD797 for those, and (dual) TL072 for A2, 3.

Supply voltage: Recommend  $\pm 15$ V, but will work down to  $\pm 6$ V.

feel when accurately compensated for speaker rolloff. Examples include bass drums, tympani, and even some acoustic string bass when close-miked; the latter can produce transient-excited spectral content well below the lowest fundamental (open E string at 41.2Hz). Likewise, but more so, for an electric bass plugged directly into a recording console.

2. Of course, when playing recordings of pipe organs, synthesizers, or any source of sustained ultra-low bass, the amp will certainly clip on these boosted components. But at a reasonably lower-than-full volume, these sources benefit greatly by having flat response to 20Hz. In fact, with satisfactory reproduction of these foundation frequency fundamentals, you don't feel such a need to crank up the juice to approach live music levels.
3. After years of pounding these (high quality) woofers, a pair of each, none has blown nor shown signs of abuse.
4. With anechoic flatness to 20Hz, room gain produces a net acoustic boost at 20Hz. For example, with the 10" Scan-

Speak systems in my 3000 ft<sup>3</sup> living room, 20Hz room gain is about 5dB. I've never found this objectionable, because at lower-than-live levels the ear needs considerable Fletcher-Munson (loudness) compensation at 20Hz. Furthermore, I find that the type of compensation I describe here has none of the boominess, muddiness, nor other colorations rampant in typical "loudness compensation" circuits.

5. I use the 8" Focal systems in my car (see "Real Backseat Bass," *Speaker Builder* 7/98). Here, the cabin (room) gain starts at around the 61Hz  $f_b$  of the woofer, so acoustic response is flat (to  $\approx$  12Hz) without electronic compensation. However, I usually use a compensator that flattens the woofers anechoically to 20Hz. The result is an in-car response boost of about 20dB at 20Hz. Even this doesn't sound boomy or muddy. Perhaps in addition to loudness compensation, such boost is needed to keep up with wind and road noise, which can be very strong at 20Hz.

## CONCLUSION

I have described a simple equalizer circuit that can accurately extend the LF response of any high-quality sealed woofer with straightforward design rules. You can arbitrarily select the compensated (extended) LF rolloff. For high-quality 8" and larger sealed woofers, flat response to 20Hz is practical. But smaller woofers can also be extended within reason (a 4" woofer can be extended perhaps to 40Hz, but not to 20Hz, for example).

One caution: with LP playback and anything less than excellent vibration isolation, or with warped LPs, infrasonic rumble would be greatly amplified with flat-to-20Hz compensation, so you should not use this. But with clean playback sources, and especially with 10" and larger sealed woofers, having flat bass response to 20Hz will add a very satisfying and natural sense of bottomless depth and solid foundation to many recordings. ❖

AdM` Sdk  
Fgd fSTVZ

7j fdSadM` Sdk  
BWA d S` UVZ

A]z;fie`afS` adM` Sdk  
fgd fSTVZ;fieS` kZ] Y Tgfz  
@W`k [ hWfWUZSeeje  
Ua` efgUJa` l\_ SeeHw  
S'g\_ [ g\_ bSfWl\_ ag` f' Yl  
\_afad TVSq` Yel TWel Sd\_ l  
S` Vbai Wlegbbk\_ S]WS` ↑ W  
aXgd fSTVZfZSf agfbWAd\_ e  
S`fZSf ZShWla\_ WTVAdMfz



6[efqTgfW [ fZAGE3 Tk RdS` 7Wfda` [la;` Uz;` \*#( : [Yz Sk=1I Sg` S]Wl;` ' % +) † (" \*Z' " Z(a"" † i i i zcS` Uadbza\_ † VZ S[ fZadVe2 fdS` Uadbza\_



# Build a Universal PC Sound Amplifier

This PC amp delivers  $2 \times 20\text{W}$  power and insulated input for distortion-free sound; volume and tone controls plus standby switch on the front panel; and earphone, PA driver, recorder output, and aux input.

By Jenó Keceli

**Y**ou can only marvel at the advertised gigantic power of PC systems. It is known in professional circles that these figures do not really mirror actual power. Lack of control and connections of these products strongly limit their application. A good solution is to connect an external amplifier to the output of the soundcard. However, this would take too much room on the already cramped computer desk. The number of the various wires would increase and the interference could not always be filtered out.

If you consider these limitations, it becomes clear that it is advantageous to have a high-quality sound amplifier inside the PC box. This article shows how you can build such an amplifier. I will analyze the possible pitfalls and how to overcome them and also refer to the possible changes that can enable the universal implementation of the amplifier.

## PROBLEMS AND SOLUTIONS

You must first consider the output power, which largely depends on the supply voltage. With only 12V at your disposal from the PC power supply, this, similar to that of the car radios, reduces the output power to approximately 4W. If you require higher power output than

### ABOUT THE AUTHOR

Jenó Keceli (of Hungary) is a long-time electronics enthusiast with 40 years of experience. His main fields of interest are designing and building tube and transistor power-amplifiers. He has much experience with sound and disco equipment and has published articles in electro technical journals. He now runs his own firm, where he builds, repairs, and gives advice. Email: keczeli@yahoo.de

this, you need to either increase the supply voltage or apply bridge circuits with two pairs of amplifiers. Increasing the 12V is only possible with a separate DC-

DC converter, which requires room and more components. Furthermore, there is a higher possibility of failure and, in case of non-adequate filtering, it is a source of interference.

Bridging the two pairs of amplifiers is more advisable, and is the solution I have chosen. This way you can also achieve the  $2 \times 20\text{W}$  music power. Anyway, it is not recommended to drive a higher load from the PC power supply, but it is advisable to choose a higher ca-


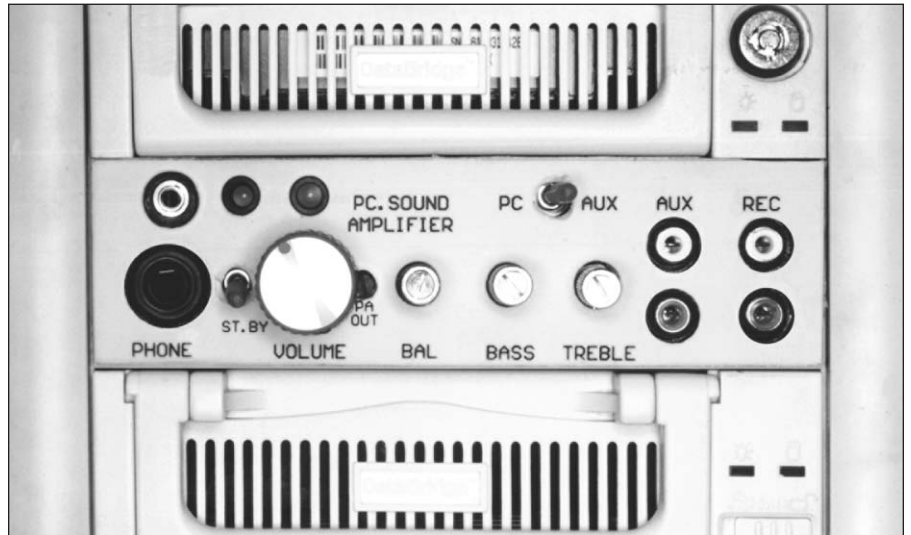


PHOTO 1: Front panel of PC-amp.

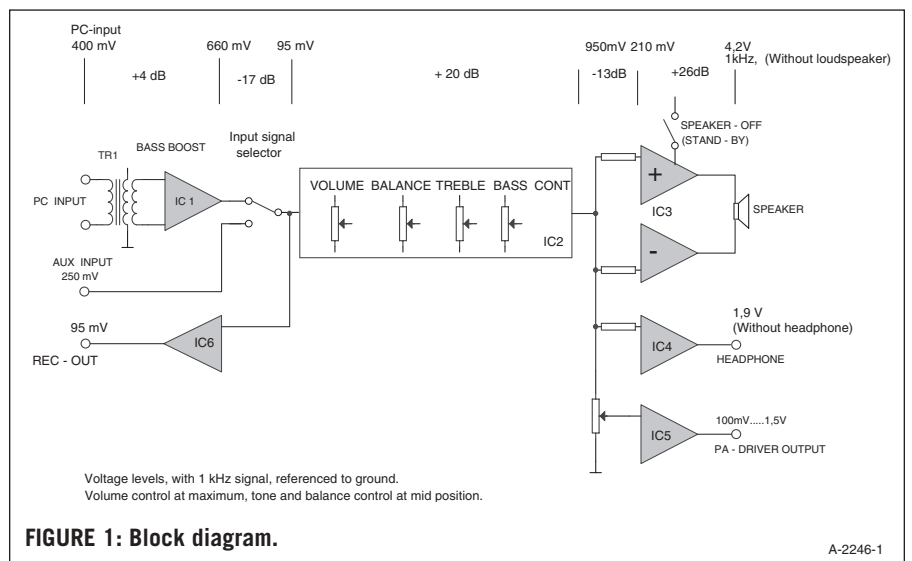

Separate PCB (terminal PCB) in a metal case, that is attached to their PC's back panel.

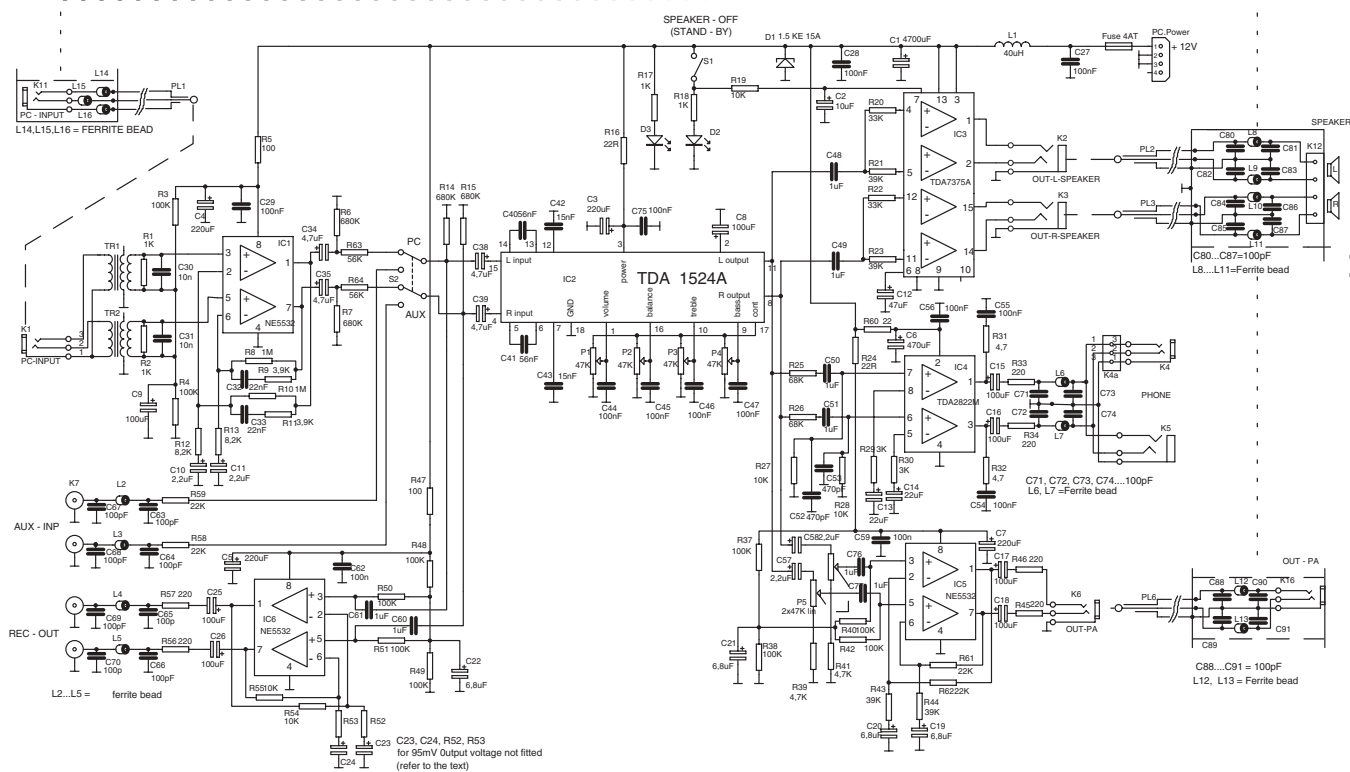


FIGURE 2: Amplifier's detailed schematic (that is attached to the PC's back panel).

A-2246-2

PARTS CONNECTION

VISA MasterCard AMERICAN EXPRESS  
 PAYPAL, BIDPAY, MONEY ORDER/BANK DRAFT/CASHIER'S CHECK

# YOUR DO-IT-YOURSELF TUBE AUDIO SUPERSTORE!

No matter what your requirements are, pcX has what you need. Whether it be vacuum tubes (both newly manufactured, NOS or OS), sockets, transformers, caps, resistors, connectors, hook-up wire, etcetera—we've got a world class selection of all the best brands... and more arriving every month!

toll free order line **1-866-681-9602** US & Canada only.

**www.partsconneXion.com**

Tel: 905-681-9602 Fax: 905-631-5777 info@partsconneXion.com



2885 Sherwood Heights Drive, Unit #72, Oakville, Ontario, CANADA L6J 7H1 • NOTE: No "on-site/walk-in" business at this time.

capacity power supply. Of course, this all depends on the current internal load. In my case, the 12V supply, loaded with 12A, works perfectly. You also must take into consideration the current-consumption of the PC.

In the case of the bridging configuration, two amplifiers (per channel) are applied so that the loudspeaker is not connected to the ground, but to another amplifier that is controlled by a signal of the phase inverter. Hence, from the same supply voltage, you will obtain double output voltage swing and four-fold output power. For this application, you can obtain excellent ICs with two or four internal power amplifiers.

You can guess the second problem, which manifests itself only during the first test. From the loudspeaker, as in

the case of a shortwave radio, the mixture of various peeping sounds disturbs pure musical pleasure. This is caused

**TABLE 1  
TEST RESULTS**

Supply voltage:	+12V from PC	
Current drain	approximately 120mA (standby), approximately 3.5A (full power)	
Output power	2x20W at 4Ω, musical	2x15W (THD 0.5%)
Frequency response	20Hz.....20kHz,	+1....-3dB
PC-input, insulated	400mV	input impedance
		Approximately 600Ω
Aux input	250mV	input impedance 47kΩ
REC output	95mV	from preamplifier
PA-driver output	100mV.....1.5V	
	(approximately -15....+10dB) (adjustable with a screwdriver)	
Power output shorting and overheat protection control		
Headphones output cca. 100mW		
Standby switch, volume (built-in contour), tone and balance control on the front panel.		
Size: front panel 148x42mm (similar to a CD-ROM), depth 175mm		

**PC – AMPLIFIER’S PART LIST**

SCHMATIC REFERENCE DESIGNATOR	PART TYPE VALUE	DESCRIPTION	SCHMATIC REFERENCE DESIGNATOR	PART TYPE VALUE	DESCRIPTION
IC1, IC5, IC6	NE5532		PC-power	Four-way PC power connector,	
IC2	TDA 1524A			PCB-mount, male	
IC3	TDA7375A		PL1, PL6	Phone plug 3.5mm stereo	
IC4	TDA2822M		PL2, PL3	Phone plug stereo ¼"	
D1	1.5 KE 15A	Protection-Suppression Diode	L1	40μH 4A	Inductor Axial
D2	LED red, 5mm		L2-L16	Ferrite bead 5mm	
D3	LED green, 5mm		P1, P2, P3, P4	47k lin, PCB-mounted	Potentiometer
Fuseholder	20x5mm/1"x¼"	PCB fuseholder	P5	2x47k lin, PCB-mounted	Potentiometer
Fuse	4AT	Fuse, glass/ceramic	R1, R2	1k	All resistors are ¼W
TR1, TR2	Audio transformer	600Ω/600Ω (refer to text)	R3, R4	100k	
C1	4700μF/16V	Electrolytic-Radial	R5	100Ω	
C2	10μF/16V	Electrolytic-Radial	R6, R7	680k	
C3, C4, C5	220μF/16V	Electrolytic-Radial	R8, R10	1M	
C6	470μF/16V	Electrolytic-Radial	R9, R11	3.9k	
C7	220μF/16V	Electrolytic-Radial	R12, R13	8.2k	
C8, C9	100μF/16V	Electrolytic-Radial	R14, R15	680k	
C10, C11	2.2μF/16V	Tantalum	R16	22Ω	
C12	47μF/16V	Electrolytic-Radial	R17, R18	1k	
C13, C14	22μF/16V	Electrolytic-Radial	R19	10k	
C15, C16, C17, C18	100μF/16V	Electrolytic-Radial	R20, R22	33k	
C19, 20, 21, 22	6.8μF/16V	Tantalum	R21, R23	39k	
C23, C24	not fitted	refer to the text	R24	22Ω	
C25, C26	100μF/16V	Electrolytic-Radial	R25, R26	68k	
C27, C28, C29	100nF	Ceramic	R27, R28	10k	
C30, C31	10n	Ceramic	R29, R30	3k	
C32, C33	22nF	Ceramic	R31, R32	4.7Ω	
C34, C35, C38, C39	4.7μF/16V	Tantalum	R33, R34	220Ω	
C40, C41	56nF	Ceramic	R37, R38	100k	
C42, C43	15nF	Ceramic	R39, R41	4.7k	
C44, C45, C46, C47	100nF	Ceramic	R40, R42	100k	
C48, C49, C50, C51	1μF	Ceramic/MKS/MKP	R43, R44	39k	
C52, C53	470pF	Ceramic	R45, R46	220Ω	
C54, C55, C56	100nF	Ceramic	R47	100Ω	
C57, C58	2.2μF/16V	Tantalum	R48, R49, R50, R51	100k	
C59	100n	Ceramic	R52, R53	not fitted	(refer to the text)
C60, C61	1μF	Ceramic/MKS/MKP	R54, R55	10k	
C62	100n	Ceramic	R56, R57	220Ω	
C63, C64, C65, C66			R58, R59	22k	
C67, C68, C69, C70	100pF	Ceramic SMD or Disc	R60	22Ω	
C71, C72, C73, C74	100pF	Ceramic SMD or Disc	R61, R62	22k	
C75	100nF	Ceramic	R63, R64	56k	
C76, C77	1μF	Ceramic/MKS/MKP	S1	Subminiature Toggle Switch on-on (panel mounting)	
C80-91	100pF	Ceramic SMD or Disc	S2	Subminiature Toggle Switch 2x on-on (panel mounting)	
K1, K6, K11, K16	Phone-jack, 3.5mm stereo	Socket PCB mounted	Heatsink	140x36x19mm	
K2, K3, K5	Phone-jack ¼" stereo	PCB mounted socket	Al blade	approximately 42x50x2mm	
K4	Phone-jack, 3.5mm stereo	panel mounted	Push-on Knobs	small	3 pieces
K4a	Terminal block	PCB mounted 3 pole	Push-on Knob	average	
K7	4x RCA-jack PCB-mounted socket				
K12	PCB mounted stereo loudspeaker connector				



by high frequency interference generated in the computer. As in our case, with the amplifier installed inside the PC case, these interferences can affect the sound amplifier. The unwanted signals can get in from any undefined source through all the unprotected ways, e.g., the supply voltage, ground connections, with the input signal, or through incomplete screening. The supply voltage and the inputs and outputs should be protected by LC filters. The metal enclosure protects from the external electromagnetic field, but all this is not enough.

You can detect interfering signals that still get into the amplifier on the double ground from the direction of the supply voltage and the input port. It is not possible to prevent them by filters. The only solution that remains is the galvanic separation of the input stage. The test results are shown in Table 1.

#### BLOCK DIAGRAM

Figure 1 shows the complete block diagram. The amplifier's main line consists of the preamplifier (IC1), the tone control (IC2), and the final amplifier

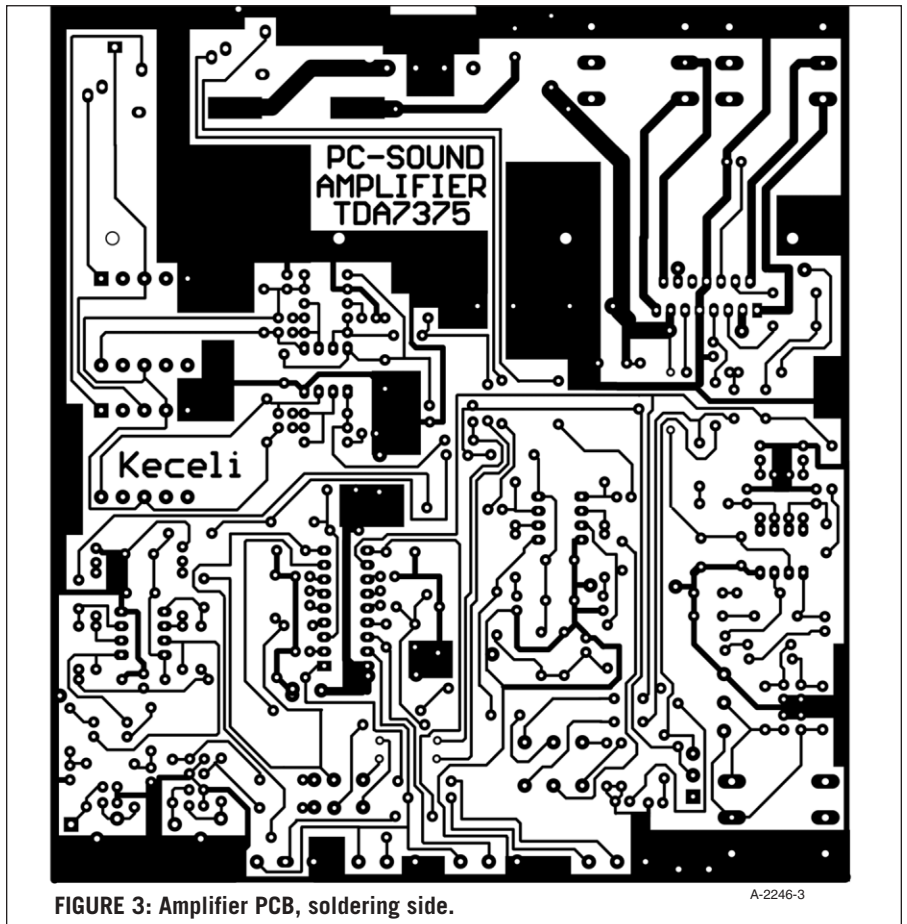


FIGURE 3: Amplifier PCB, soldering side.

A-2246-3

## The Ultimate Acoustic Analysis System.

*For real-time testing of  
Audio System performance!*

- 1/12th Octave Real-Time Analyzer (RTA)
- Energy-Time Graph (ETG) with octave & 1/2 octave band filters
- Sound Pressure Level Meter
- Speaker Distortion Meter (THD+N)
  - Signal to Noise Ratio
  - Speaker Polarity Test
- Integrated Audio Signal Generator
- Handheld, Portable, Battery Operated
- Serial Data Download and Report Software



Powerful • Portable • Affordable

# SENCORE

1-800-736-2673 • [sencore.com](http://sencore.com) • e-mail [sales@sencore.com](mailto:sales@sencore.com)

Subscribe To The SENCORE News at [www.sencore.com](http://www.sencore.com)

(IC3). The gain of the various stages is indicated on the figure. Each stage contains an IC. With these three ICs, the amplifier can already function. However, you need to add further items to build a general-purpose amplifier. The headphone amplifier is implemented with an additional IC (IC4), and there are further two ICs: the IC6 for the REC output, and the IC5 for the PA-driver output. The PC input, the loudspeaker output, and the PA-driver output are on a separate board with individual filters. This board is built in a metal enclosure that is mounted to the back of the PC.

### PRINCIPLES OF OPERATION

Figure 2 shows the amplifier's detailed schematic. The signal goes to the amplifier from the soundcard through the PC input port. This connector, which is on the back of the computer, is fully insulated and fitted on a terminal panel along with the PA-driver output and the loudspeaker connectors. Ferrite beads suppress the interfering signals.

From here, the signal goes to the amplifier through a screened cable and K1 connector (for internal wiring), which is on the amplifier panel. K1 is insulated the same way as the input connector. Full galvanic separations are achieved by the input transformers.

Because this is the sensitive point of the whole system, you must choose a good quality one-to-one transformer, which you can purchase off-the-shelf or make it at home. I used a homemade transformer.

For the sake of a better bass fidelity, I found it advisable to build in a bass correction circuitry. This is the actual pre-

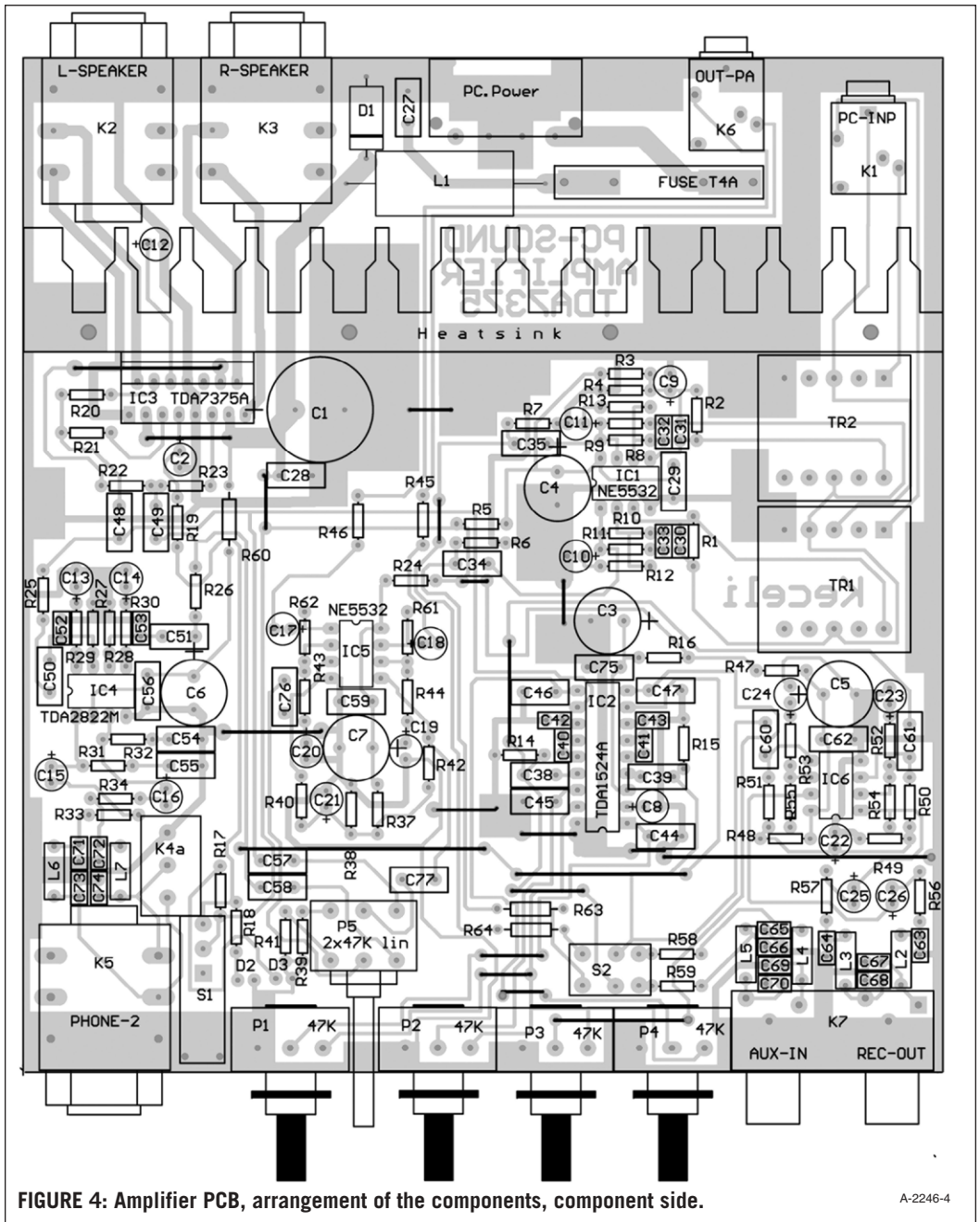


FIGURE 4: Amplifier PCB, arrangement of the components, component side.

A-2246-4

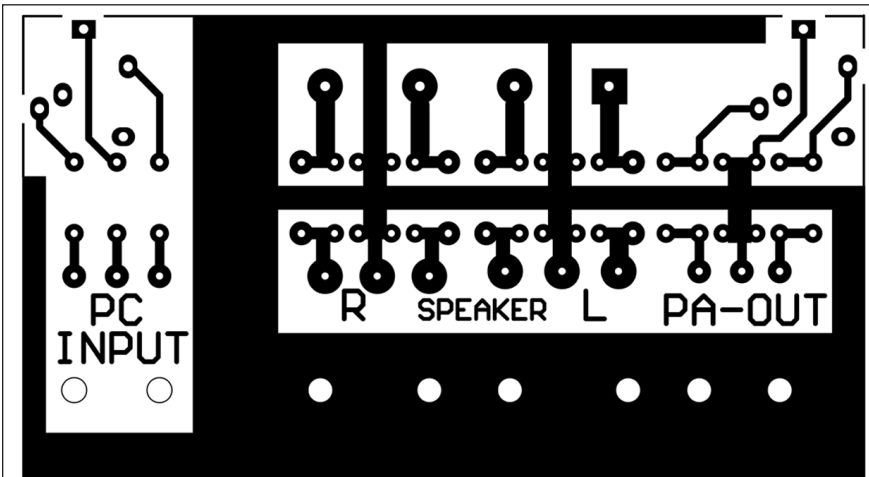


FIGURE 5: Terminal PCB, soldering side.

A-2246-5

amplifier IC1. The solution is a conventional low-noise OP. Its gain is hardly more than one (at 1kHz). R1 and R2 resistors determine the impedance matching, while C30 and C31 set the lower frequency roll-out.

The  $U_{ref}$  produced by the R3/R4 resistors and filtered by the C9 goes through the winding to the input of the amplifier. Bass boost for the compensation of the transformers' bandwidth is ensured by components C32-R9 (C33-R11). The signal from the amplifier goes to the input signal selector through the C34, C35 capacitors and the R63, R64 resistors. The DC null potential is produced by the R6, R7, R14, and R15. This is necessary to prevent the switchover click.

Because the gain of the other stages is quite high, it is the low frequency boost that is more characteristic of the preamplifier. The unnecessary gain is reduced by R63 and R64. If you change R63 and R64, you can alter the input sensitivity. However, increasing the gain is not necessary and can be risky because the amplifier's low-frequency stability may deteriorate.

The AUX input-RCA connector pair is

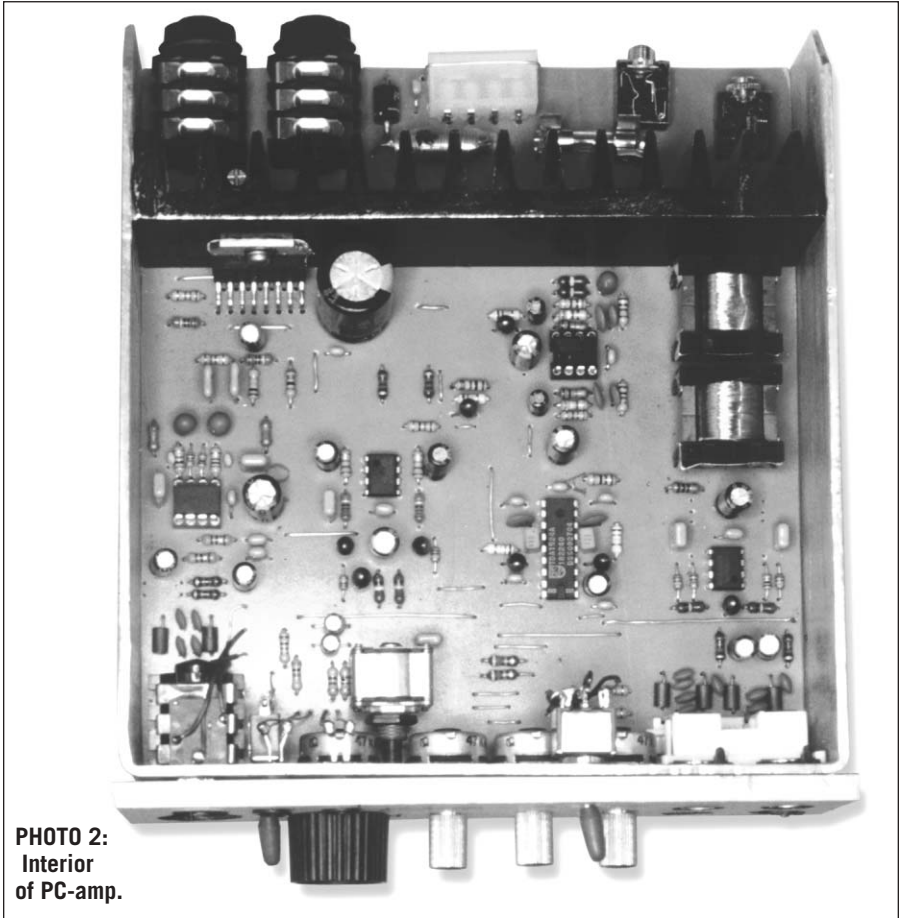


PHOTO 2:  
Interior  
of PC-amp.

# LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES & SEMICONDUCTORS AND I.C.S.

1 MAYO ROAD, CROYDON, SURREY, ENGLAND CR0 2QP

24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

E-MAIL: LANGREX@AOL.COM

FAX

PHONE  
44-208-684-1166

44-208-684-3056

## A SELECTION OF OUR STOCKS OF NEW ORIGINAL VALVES/TUBES MANY OTHER BRANDS AVAILABLE

STANDARD TYPES			AMERICAN TYPES			SPECIAL QUALITY TYPES		
ECC81	RFT	3.00	5R4GY	RCA	7.50	A2900/CV6091	G.E.C.	17.50
ECC82	RFT	6.00	5U4GB	SYLVANIA	15.00	E82CC	SIEMENS	7.50
ECC83	RFT	8.00	5Y3WGT	SYLVANIA	5.00	E83CC	TESLA	7.50
ECC83	EI	4.00	6BX7GT	GE	7.50	E88CC	MULLARD	20.00
ECC85	RFT	10.00	6FQ7	EI	5.00	E88CC G. PIN	TESLA	8.50
ECC88	BRIMAR	6.00	6L6GC	SYLVANIA	20.00	E188CC	MULLARD	20.00
ECC88	MULLARD	10.00	6L6WGB	SYLVANIA	20.00	ECC81/6201	G.E.	5.00
ECL82	MULLARD	5.00	6SL7GT	USA	7.50	ECC81/CV4024	MULLARD	6.00
ECL86	TUNGSRAM	10.00	6SN7GT	USA	7.50	ECC81/M8162	MULLARD	7.50
EF86	USSR	5.00	6V6GT	BRIMAR	7.50	ECC81/6201 G. PIN	MULLARD	10.00
EF86	MULLARD	20.00	12AX7WA	SYLVANIA	7.50	ECC82/CV4003	MULLARD	15.00
EL34	EI	6.00	12BH7	BRIMAR	12.00	ECC82/M8136	MULLARD	17.50
EL36	MULLARD	6.00	12BY7A	G.E.	7.00	ECC83/CV4004	MULLARD	40.00
EL37	MULLARD	30.00	211/VT4C	G.E.	85.00			
EL41	MULLARD	5.00	807	HYTRON	7.50			
EL84	USSR	3.00	5687WB	ECG	6.00	<b>SOCKETS</b>		
EL509	MULLARD	10.00	6072A	G.E.	10.00	B7G	CHASSIS	0.60
EL519	EI	7.50	6080	RCA	10.00	B9A	CHASSIS	1.00
EZ80	MULLARD	5.00	6146B	G.E.	15.00	OCTAL	CHASSIS	1.00
EZ81	MULLARD	10.00	6922	E.C.G.	6.00	OCTAL	MAZDA	2.00
GZ30	MULLARD	5.00	6973	RCA	15.00	LOCTAL	B8G CHASSIS	2.50
GZ32	MULLARD	25.00	7308	SYLVANIA	5.00			
GZ33/37	MULLARD	25.00	SV6550C	SVETLANA	20.00			
PL509	MULLARD	10.00				<b>SCREENING CANS</b>		
						ALL SIZES		1.00

### MANY OTHER BRANDS AVAILABLE

These are a selection from our stock of over 6,000 types. Please call or FAX for an immediate quotation on any types not listed. We are one of the largest distributors of valves in the UK. Same day dispatch. Visa/Mastercard acceptable. Air Post/ Packing (Please Enquire). Obsolete types are our speciality.



installed on the front panel of the amplifier's PCB. Similar to the previous one, these connectors also contain filters made up of ferrite beads and capacitors. These items are fixed to the amplifier panel, near the terminal block.

The resistors R58 and R59 determine the sensitivity of the input. Because the 22k value is calculated for standard value, you can connect an external CD player, tuner, or other signal to it. Input selection is done by a switch, so the signal reaches the tone control stage. The tone control task is

carried out by the IC2. Its gain is 20dB, which you cannot alter.

Besides the bass and treble tone control, you'll also find the volume and balance control here. This is a complex stage; control is carried out by DC levels. From the point of view of construction, this makes the stage less complicated since the RC items of the usual tone control stage are not required and mono potentiometers are sufficient for the control.

The IC2 contains a loudness tone correction stage, as well. This plays an im-

portant role by setting the sound transmission to the sensitivity of the human ear. In our case, this stage is always switched on. You can switch it off for experimenting by grounding the IC2 17 pin by 2.2k.

After setting the frequency response, the signal goes to the power stage through the C48 (C49) capacitors. The power amplifying is carried out by the IC3. For this, I chose an item that requires only a few external components and can still produce good quality (as you have previously amplified the signal properly). Its gain is low.

The gain of the TDA 7375 is fixed at 26dB. I reduced this to 20dB with external components. According to the manufacturer's manual, the inverted and non-inverted inputs of the IC are joint. I separated them by building in ballast resistors (R20, R21, R22, and R23).

As there is a feedback on the inverted input, this input is different from the non-inverted input, so the resistor values are different. I chose the resistor values so that they would receive identical output voltages. The inverted inputs provide phase-shifted signal, which is required for the functioning of the bridge circuit. In this way, no separate phase inverter is needed. In case of an IC with higher gain, the system might not be stable any longer and would make the operation impossible.

As already mentioned, TDA 7375 IC has a standby pin that is connected to the switch on the front panel. Shutting down the whole amplifier is not possible, but you can switch off the loudspeakers with the standby switch.

As the other stages of the amplifier operate independently of this, you can listen to the music through headphones, without external disturbance. K2 and K3 connectors are the loudspeaker connectors on the PCB, but only for internal connection, as the loudspeaker connector K12 is on the back panel on the terminal PCB. Propagation of interfering signals is hindered by a ferrite bead filter.

### OUTPUT STAGE

The amplifier can already function this way, but for the sake of the general-purpose applications, I built in three more ICs. As the PA contains a standby switch and the switching over of the loudspeak-

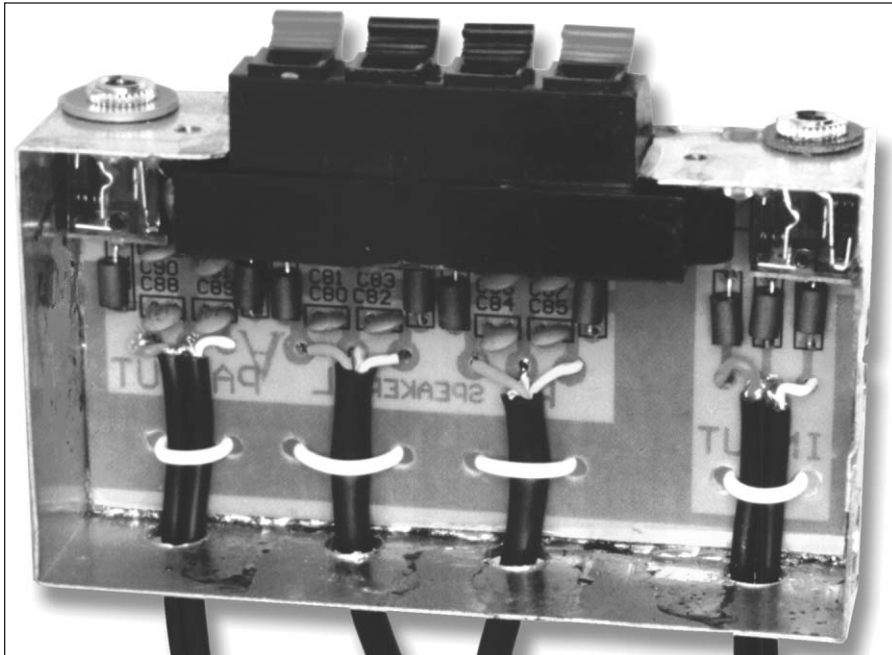


PHOTO 3: Interior of terminal block.

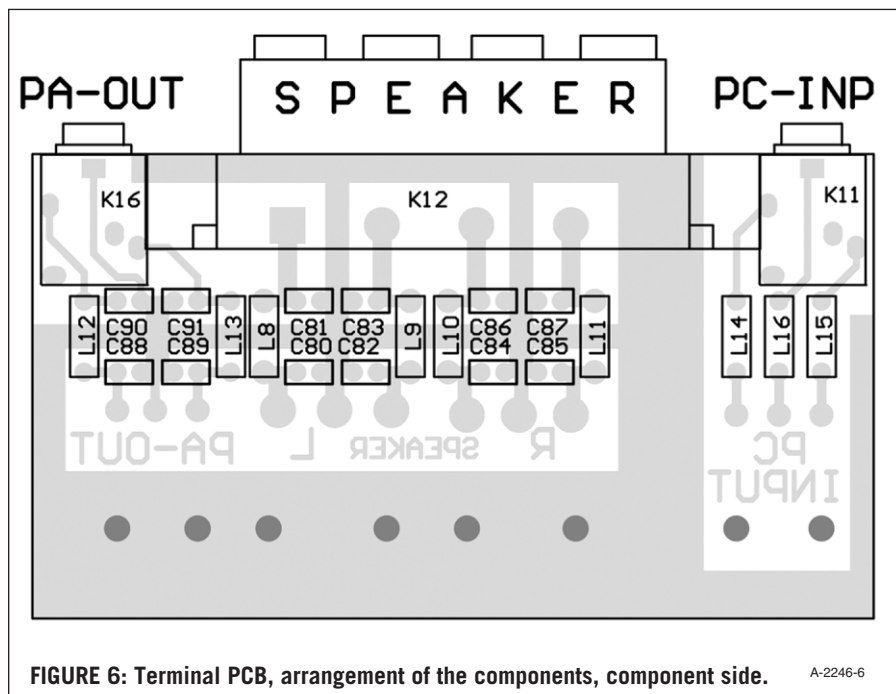


FIGURE 6: Terminal PCB, arrangement of the components, component side. A-2246-6

er output would be more complicated, I constructed a separate amplifier for the headphone output. This is the IC4, TDA 2822, similar to the power amplifier, but

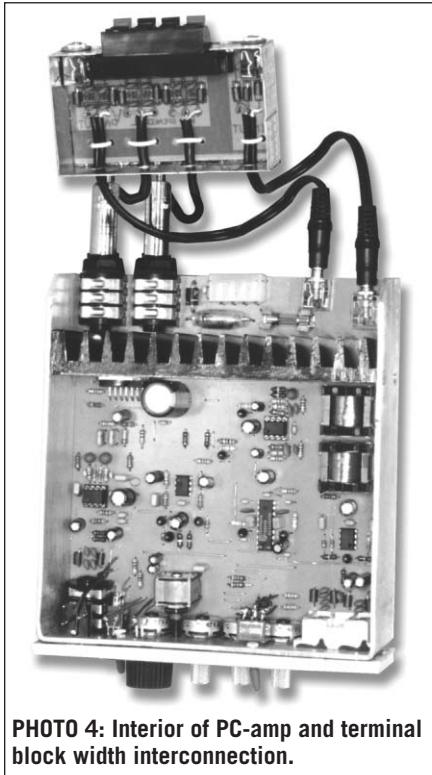


PHOTO 4: Interior of PC-amp and terminal block width interconnection.

with lower power IC.

According to the manufacturer's manuals, the gain is not variable. However, by increasing the negative feedback, I managed to find an optimum solution by reducing the gain using external components and optimizing a reliable state. If the gain is different from the optimum, the amplifier is apt to pop noise. The signal goes to the IC4 through the 68k resistors (R25, R26). This value is usually appropriate for the headphone, but if needed, you can change the value of the resistors.

To avoid pop noise, the previously mentioned IC requires some more external components. I added the C52, C55, and R31 (C53, C54, R32) to it for this purpose. The R33 and R34 capaci-

tors serve as protectors of the IC and of the headphone. The output signal goes through the ferrite bead filters to the connectors mounted on the front panel and the PCB. The smaller connector is mounted above the larger one and is wired to the K4a connector that is on the PCB. This makes the universal connection of headphones possible.

The IC6 gives an output signal from the preamplifier for recording. The circuitry of the stage is conventional. The stage does not need a gain to reach 95mV, it operates only as a buffer amplifier.

Hence the places of the R52, R53, C23, and C24 components are given, but they are not installed. By mounting these components, you can achieve higher

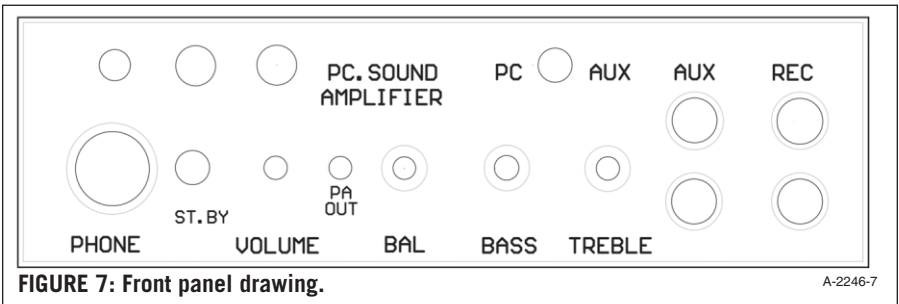


FIGURE 7: Front panel drawing.

A-2246-7

# Hi-Fi Do Inc.

## BUY & SELL

**OVER A  
MILLION  
HITS/WEEK**

**USED AMPLIFIERS, SPEAKERS, PLAYERS, BOOKS, ACCESSORIES etc.**

**www.hifido.co.jp**

OSAKA(Overseas Dept.): 4-6-10 NIPPONBASHI NANIWA-KU OSAKA JAPAN

TOKYO: TOKUHARA BLD 5-5-7 SOTOKANDA CHIYODA-KU TOKYO JAPAN

NAGOYA: 3-11-30 OOSU NAKA-KU NAGOYA JAPAN

**PHONE 816-4396-7611 FAX 816-4396-7621**

Get Hi-Fi Do's Free Online Newsletter >>> [www.hifido.co.jp/logtop.html](http://www.hifido.co.jp/logtop.html)

gain and output level. The output is filtered by the already described ferrite bead filters. The RCA connector pair is on the front panel of the amplifier PCB.

The IC5 is an OP amplifier, as well, with a conventional circuitry. The signal reaches this stage from the tone control IC, which means that it gets the same signal as the PA. The IC has minimal gain, and the output level is adjustable (using a screwdriver) with the P5 that is on the front panel. This output can serve as a PA-driver (or line) output. The K6 connector is on the amplifier PCB and is connected by a cable to the terminal PCB, where you'll find the filters and the K16 connector.

### POWER SUPPLY AND FILTERS

The power supply connector is on the amplifier panel. The D1 diode protects from over-voltage. L1 and C27 act as filters. Furthermore, every IC has its own supply filter, which consists of a 100nF and an electrolytic-capacitor. You need an especially high value electrolytic-capacitor C1 to protect the power amplifier. The filter capacitors are directly beside the ICs. The operation amplifiers

(IC1, IC5, IC6) have an asymmetrical supply, so the production of an  $U_{ref}$  is necessary.

+6V is achieved by the serial connection of two resistors. This voltage is filtered by an electrolytic capacitor and is led through resistors (except for IC1—there it is led through a transformer) to the input of the amplifiers (3.5 pin). The environment is protected by ferrite bead filters (fitted directly next to the connectors) from the high-frequency interference that is radiated by the computer. As the loudspeaker's output, PC-input and the PA-driver output connectors are placed on the computer back panel and are fitted in a separate metal enclosure on a separate PCB (terminal panel).

### CIRCUIT ASSEMBLY

All the active components with the elements belonging to them coupled with the front panel connectors and the operating devices are on the very same PCB (called amplifier panel). This is built in the computer in a vacant driver space. The K1, K2, K3, and K6 connectors placed on the amplifier panel are only

used for internal wiring, because further connectors are provided on the back panel. The loudspeaker connector, the PC input, and the PA-driver output with the ferrite bead filters belonging to them can be found on a separate PCB (terminal PCB) in a metal enclosure that is attached to the PC's back panel.

The amplifier PCB is in a metal box made of a 2mm Al (Aluminum) sheet and enforced with a metallic frame at the front and both sides. The control devices of the front panel are attached to this frame. The heatsink is in the middle of the PCB module to which the already mentioned frame is fixed, so that a closed ring is formed. The front panel connectors with the filters belonging to them are screened by a thin metal sheet. A front panel hides the screws of the Al frame, but this has only an esthetical function.

### ASSEMBLY

Assembly of the amplifier is very simple; no adjustment is required. If you work carefully and avoid mistakes, the amplifier will work at once. You should carry out the tests using an external

## HERE IT IS!

NEW FROM



### TLwrx Version 3.0—Transmission Line Software by G. L. Augspurger, Perception, Inc.

The culmination of years of research into testing and measuring the behavior of transmission line loudspeakers, a software modeling program which accurately predicts the system response of transmission line speakers at the design stage. Including basic performance relationships similar to the Thiele/Small analysis of vented boxes, **TLwrx Version 3.0** provides you with valuable information about expected system response prior to construction.

**TLwrx** is based on extensive research by G. L. Augspurger, longtime technical manager for JBL's professional division and designer of custom loudspeaker monitor installations. Along with the **TLwrx Version 3.0** software, extensive notes, an alignment chart, and Augspurger's three articles describing his research from *Speaker Builder* are included on the CD. 2004, CD. Sh. wt: 1 lb.

**SOF-TLWRX \$129.00**

To order call **1-888-924-9465** or visit **www.audioXpress.com**

**Old Colony Sound Laboratory**, PO Box 876, Peterborough, NH 03458-0876 USA  
**toll-free:** 888-924-9465 **phone:** 603-924-9464 **fax:** 603-924-9467  
**e-mail:** [custserv@audioXpress.com](mailto:custserv@audioXpress.com) [www.audioXpress.com](http://www.audioXpress.com)



power supply and a signal generator. After having mounted the PA-IC3 and the tone control IC2, you can try the first test. The amplifier must function with the AUX input. After this, build in the preamplifier together with the IC1.

The other stages should not cause problems either. (In case one of the peripheral stages is not needed, you can leave it out.) Because of limited space, the smaller headphone connector is not placed on the PCB, but is mounted directly on the front panel. The S2 switch and LED are mounted to the front panel as well.

After having tested what you have built so far, it's time to install the amplifier.

Warning: while installing and connecting inside the PC, you should turn off the unit. Connecting the amplifier to an operating PC might cause a system crash due to the charging current and the high capacity of the C1.

The amplifier might function without ferrite bead filters, but you should still mount the terminal PCB on a vacant space on the back of the PC. You must install the connector K11 isolated from the metal case. The PC input receives the signal through a screened cable from the soundcard. As there is a metal sheet above and below the amplifier, this does not need to be screened separately, but in order to avoid a probable short circuit it is advisable to place an isolating sheet below the amplifier.

## COMPONENTS

**The heatsink**—because I could not find one of appropriate size, I cut a bigger one than I needed. This way I produced the appropriate form. If necessary, you can use a thicker Al sheet.

**The transformer**—the simplest solution is to use a commercial off-the shelf 1:1, 600:600Ω transformer. I made this transformer myself, in this case, on an EF-20 ferrite core of N27 material, (Siemens-Matsushita Cat. # B66311-G90-X127), 2×600 turns ( $\phi=0.1\text{mm}$ ). Between the two windings there is one aligning turn. You ground one of the terminations as screening; No metal screening is needed.

**TDA7375A**, STMicroelectronics, 2×37W dual/quad power amplifier for car radio. Minimal external components. Internally fixed gain (26dB). No

audible pop during standby operations. Protections, output AC/DC short circuit, overrating chip temperature with soft thermal limiter. Supply voltage range 8 to 18V.

**NE5532**, Texas Instruments. Dual low-noise, high-performance operational amplifiers. They feature very low noise, high output-drive capability, low distortion, input-protection diodes, and output short-circuit protection. These operational amplifiers are compensated internally for unity-gain operation. Wide supply-voltage range . . .  $\pm 3\text{V}$  to  $\pm 20\text{V}$ .

**TDA 1524A**, Philips Semiconductors. Stereo-tone/volume control circuit. The device is designed as an active stereo-tone/volume control for car radios, TV receivers, and mains-fed equipment. It includes functions for bass and treble control, volume control with built-in contour (can be switched off), and balance. All these functions can be controlled by DC voltage or by single linear potentiometers. Few external components are neces-

sary. Low noise due to internal gain. Supply voltage 7.5 to 16V. Maximum gain of volume 21dB. The input resistance is a function of the gain of the volume control. At maximum volume it is 10k, and it increases with the reduction of the gain.

**TDA2822M**, SGS-Thomson, Dual low-voltage power amplifier. It is intended for use as dual audio power amplifier in portable cassette players and radios. Supply voltage 1.8 to 15V, output power 300mW at 32R. Closed loop voltage gain 39dB. Input resistance 100k. ♦

If you would like to purchase these PCBs from the author, or are looking for help, you may contact him at

Keceli Jenő  
PF1235, 6701  
Szeged, Hungary  
E-mail: keceli@yahoo.de

## REFERENCES

STMicroelectronics specification publication TDA 7375A, <http://www.st.com>.  
Texas Instruments production data information NE5532, SLOS075G – 11/79, Texas Instruments, PO Box 655303, Dallas, TX 75265.  
Philips Semiconductors product specification TDA 1524A data sheet.  
SGS THOMSON MICROELECTRONICS, TDA2822M applications.  
*ELV Journal* (German) 4/95 PC-Audioverstärker.  
*ELV Journal* (German) 5/99 PC-Audio-Verstärker PCA 200.  
*Elektor* (German) 12/2000 PC-SoundAmp.

# www.mouser.com

300,000+ Electronic Components  
Over 1,000,000 Cross References



New Products,  
New Suppliers,  
New Technologies,  
New Catalog Every 90 Days!

# MOUSER

ELECTRONICS

(800) 346-6873 [www.mouser.com](http://www.mouser.com)

Mouser® and Mouser Electronics® are trademarks of Mouser Electronics, Inc.



# Minimal Reactance Power Supply

The author introduces a new concept for designing a current regulated power supply for your next tube amplifier or preamplifier project.

By David Davenport

I finished developing my SET line stage, and now it was time to produce a power supply. I used a standard choke-input power supply for most of the development that you read about in "Odyssey of a Line Stage" (*audioXpress* 2/03 and 3/03). That supply was okay, but I wanted something special to support the superb sonic qualities of the line stage. If you remember, the line stage ended up as a parafeed design using a constant-current source (CCS).

Thinking about power-supply topologies, I began to wonder whether it needed a choke if the load drew a constant current. This thought opened the door and allowed me to get out of the box of conventional power-supply thinking. The thoughts poured in.

In my experience a CCS was better than a choke as a plate load. Was the CCS an ideal choke? Of course, a CCS doesn't store energy like a choke does, but so what? What if I were to use a CCS in place of a choke in a power supply?



Figure 1 shows the concept with CCS1 in the power supply and CCS2 in the line stage. In this example CCS1 provides a constant 35mA, CCS2 draws a constant 30mA, with the remaining 5mA flowing through the resistor, which is chosen to produce the desired voltage on the output of the power supply. I built a model of the design shown in Fig. 2, and it worked just as I expected.

## CAPACITOR VALUE

My next question was "How big does the input capacitor need to be?" One of the important characteristics of a CCS



PHOTO 1: The completed supply.

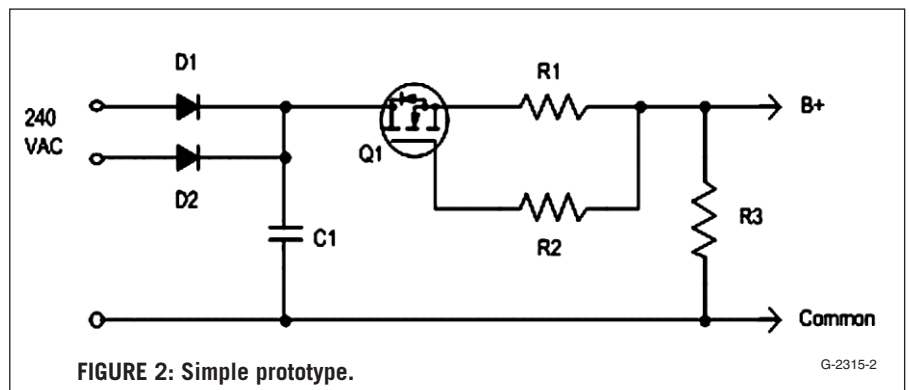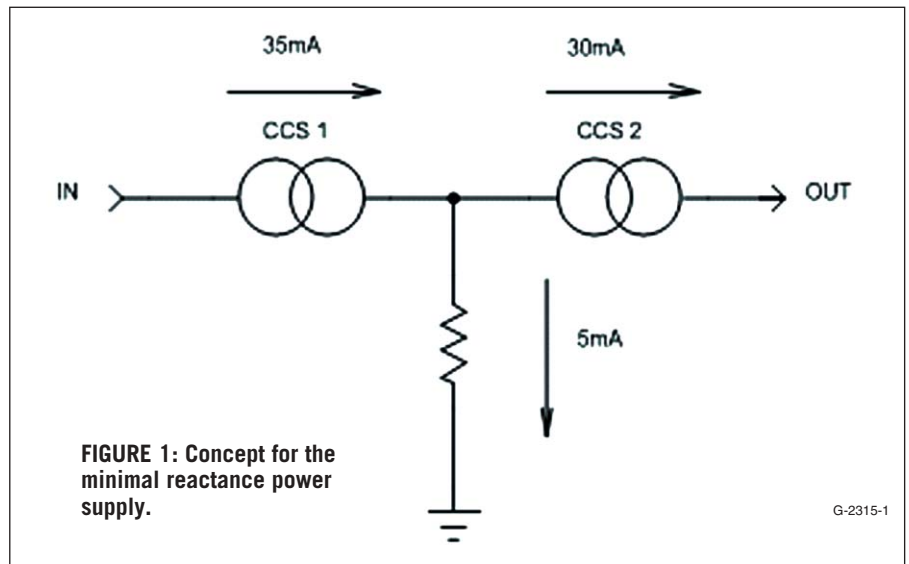

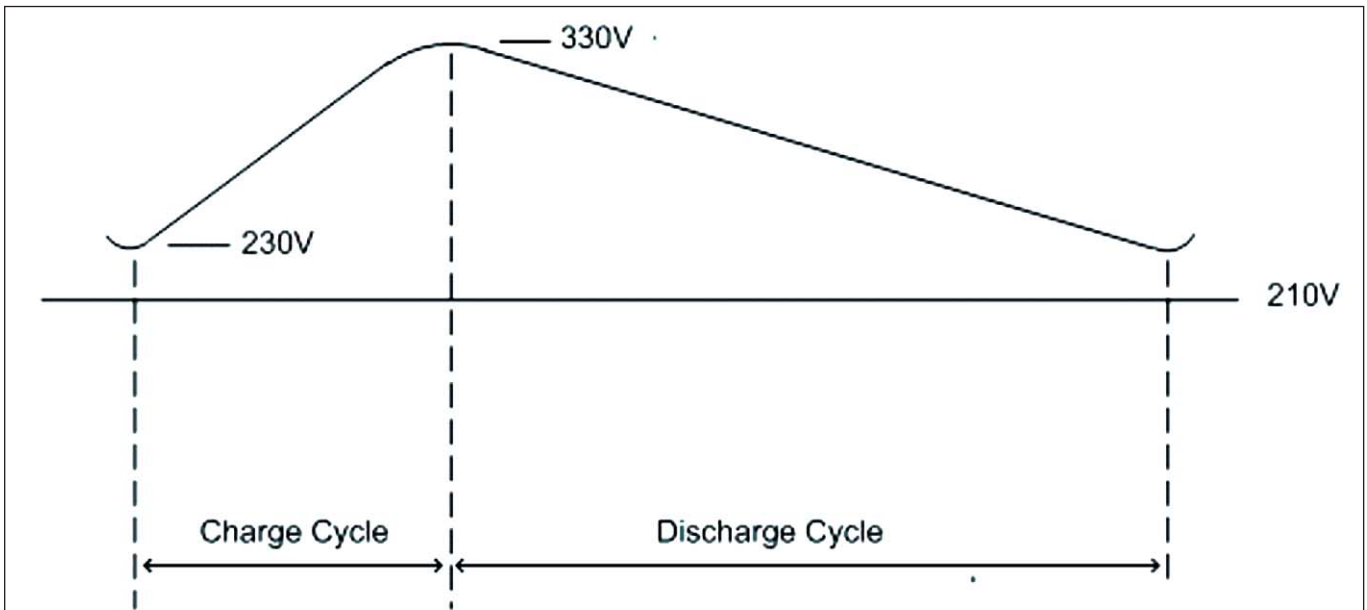


FIGURE 3: Filter capacitor ripple.

G-2315-3

is its power-supply ripple rejection (PSRR). With a very high PSRR, the CCS can tolerate a large ripple on its input; in fact, the amount of ripple is not important as long as the instantaneous voltage stays above a certain value.

In order for the CCS to provide a constant current, there must be sufficient voltage on its input. If the voltage were to drop below this point, the CCS would act like a large resistor and the current would drop as the voltage dropped. It doesn't matter whether the voltage rises above the critical value; the output current remains constant.

Although the DN2450 high-voltage MOSFET I used here needs only a few volts across it to work properly, I conservatively allowed 20V. If I wanted 200V on the output, all I would need to do is keep the input above 220V. I could have a hundred volts of ripple and, as long as the instantaneous voltage stayed above 220V, the CCS would reject all of the ripple. This means that

the input capacitor does not need to be very large at all, perhaps only a couple of microfarads.

But don't you need a large capacitor to store lots of energy to provide for powerful bass and a large crescendo? Nope! Isn't "the more the better" a

good rule for capacitors? Nope! As long as the CCS input voltage stays above the critical value, the output is the same. The current is constant even for those deep bass thumps and large crescendos.

In fact, a large capacitor is not neces-

**From Audio Kits**  
to all types of electronic  
parts...we are *THE* Audio  
Electronic Supply Source.



Receive a FREE Catalog

**AUDIO**  
ELECTRONIC SUPPLY

1020 Goodworth Drive  
Apex, NC 27539  
919.355.0014 (voice)  
919.355.0013 (fax)

**ABOUT THE AUTHOR**

David Davenport has been involved in audio DIY for over 40 years. He retired after 30 years as an engineer with IBM, and then founded his own company, Raleigh Audio, dedicated to exploring the limits of audio electronics and providing the results to OEMs and serious hobbyists. He has written many articles for *audioXpress*, as well as the former Audio Amateur publications, *TAA*, *GA*, and *SB*.

Visit us online for the latest Audio Electronic Supply Catalog at:  
[www.superamp.com](http://www.superamp.com) ■ [www.audioelectronicsupply.com](http://www.audioelectronicsupply.com) ■ [www.sixpacs.com](http://www.sixpacs.com)



Our Samples Are Better Than

**FREE!**



We're so sure you'll love our Square Drive Screws we'll practically pay you to try them. **Return this ad with \$10** and we'll send you our famous "Try-Pack" Sampler of 200 screws (25 each of #8 x 1-3/8, & 1-7/8 Flat Head ProMax®, # 8 x 5/8, 1-1/4, 1-1/2 & 2 Std Flat Head, and #8 x 1-1/4 & 2 Round Washer Head), a driver bit for your drill, our catalog listing 900 types of fasteners, and a coupon for **\$10 off** your first order of \$75 or more! (Limited time offer. Available in USA only.)

"We tried a box of 1-3/4" #8 prelubricated flat heads with nibs from McFeely's, which quickly became our favorite fastener." Speaker-Enclosure Screws, Robert J. Spear and Alexander F. Thornhill, *Speaker Builder*, 2/94

© 2002 McFeely's All Rights Reserved


**McFEELY'S**  
SQUARE DRIVE SCREWS

Box 11169 • Lynchburg • VA • 24506

Call 1-800-443-7937 or FAX 1-800-847-7136
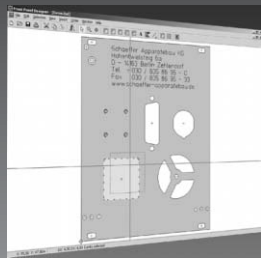
## Front Panels?

Download the free Front Panel Designer to design your front panels in minutes ...



... and order your front panels online and receive them just in time

Unrivalled in price and quality for small orders

[www.frontpanelexpress.com](http://www.frontpanelexpress.com)

sarily a good thing. Take a look at the ripple waveform in *Fig. 3*. During the first part of the cycle, the capacitor charges to the output voltage of the rectifier, while during the second part of the cycle the capacitor discharges until the rectifier voltage again rises to exceed the discharged voltage. As the value of the capacitor increases, the capacitor can store more energy so it loses less voltage during the discharge part of the cycle. As a result, the charge time becomes shorter and the dis-

charge time longer.

With a very large capacitor the discharge time can be minuscule. However, since the capacitor is large, it provides low impedance during this short charge time resulting in a large amplitude current pulse. Thus, the current drawn from the transformer is in the form of very short, high-amplitude current pulses, which cause the transformer to ring like a bell.


A smaller capacitor that draws a wider, lower amplitude current pulse

**TABLE 1**

**PARTS LIST FOR FIGURE 4**

PART	DESCRIPTION	SOURCE
<b>Resistors</b>		
R1, R2	0.5Ω, 5W	Mouser 71-RS5-0.5
R3, R4	0.47Ω, 7W	Mouser 280-PRM7-0.47
R5	120k, ¼W	Mouser 271-120K
R6	100k, ¼W	Mouser 271-100K
R7	100Ω, ¼W	Mouser 271-100
R8	40.2Ω, Caddock MK132	Michael Percy
R9	10k, 5W Mills MRB-5	Michael Percy
R10	40.2k, 12W Mills MRB-12	Michael Percy
R11	5k trimpot	Mouser 72-T93YB-5K
<b>Capacitors</b>		
C1	0.47μF, 300V X-rate	Digi-Key P11120-ND
C2	100nF 50V	Digi-Key P4923-ND
C3	3.6μF, 600V Solen	Michael Percy
C4	1μF, 600V Solen	Michael Percy
C5	100nF, 630V	Mouser 75-MKP1840410634
C6	10nF, 1600V	Mouser 75-MKP1841310134
C7	6800μF, 35V	Digi-Key P6660-ND
C8	1μF, 50V	Digi-Key P5174-ND
C9	220μF, 10V	Digi-Key P10220-ND
<b>Inductors</b>		
L1	CM choke	Digi-Key PLK1007-ND
L2, L3	EMI bead	Digi-Key P9817BK-ND
<b>Diodes</b>		
D1, D2	FRED, DSEI-12	Digi-Key DSEI12-12A-ND
D3	1N4005	Digi-Key 1N4005GICT-ND
D4-D7	SB540	Digi-Key SB540CT-ND
<b>Semiconductors</b>		
Q1	MOSFET, DN2540	K&K Audio
U1	Regulator, LM78M06	Digi-Key NJM78M07FA-ND
U2	Timer, LM555	Digi-Key LM555CNNS-ND
<b>Miscellaneous</b>		
T1	Transformer, Lundahl LL1683	K&K Audio
V1	12×4	Antique Electronics
K1	Relay	Digi-Key PB295-ND
	7-pin tube socket	Antique Electronics
	Heatsink	Digi-Key HS241-ND
	Insulator, heatsink	Digi-Key BER102-ND
	Insulating bushing	Digi-Key 3049K-ND
	4-40 screw & nut	Procure locally
	Mounting hardware	Procure locally

Note: A kit is available from K&K Audio

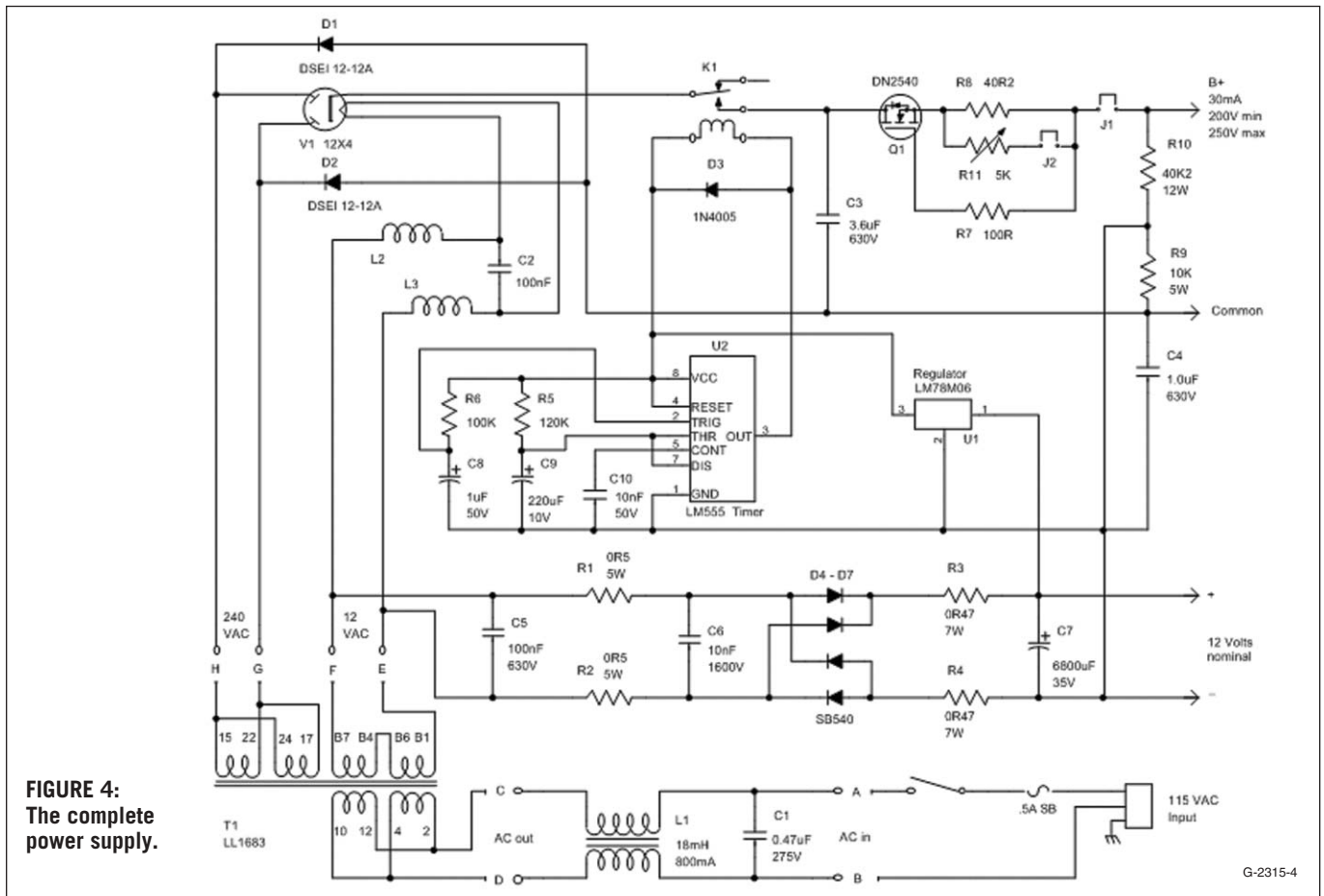

**FIGURE 4:**  
The complete  
power supply.

G-2315-4

has the advantage here. Another benefit of using a small capacitor is that it can be a high-quality film rather than an electrolytic, resulting in even better sonic quality.

The result of all this is a unique supply topology that regulates the current and lets the voltage seek whatever level is needed to provide the required current. Because the design uses as small a capacitor as needed and does not incorporate an inductor, I call it a minimal reactance power supply.

**DESIGN STEPS**

Take these steps to design your own minimal reactance power supply:

1. Determine what current and voltage the external load needs.
2. Calculate the current through the load resistor (R3 in Fig. 2) that will develop the desired output voltage,  $E = IR$ .
3. Calculate the required regulator current. This is the sum of the current through the resistor that you just calculated plus the current required by the external load.

**Supplier  
Of High  
Quality  
Speaker  
Kits &  
Components  
For The Audio  
Enthusiast**

**LEAP™** Components & Accessories  
Crossover Design

**Pioneer**

115 S. Victory Blvd.  
Burbank, CA 91502  
Vox 818-846-9921  
Fax 818-846-1009  
www.speakercity.com

**SPEAKER  
CITY U.S.A.®**

Orders Only! 800-595-9924  
Mon-Sat 10am-6pm

4. Calculate the size of the filter capacitor (C1) needed. For a rule of thumb, I use the formula:  $C = 10 I/V$ , where C is in microfarads, I is the current through the CCS in mA, and V is the peak-to-peak voltage of the input ripple. The top peak is the maximum output of the rectifier,

and the bottom peak is 20V greater than the desired B+ voltage. So, for example, if I wanted 210V B+, 35mA through the CCS, and my rectifier put out 330V, the capacitor needed would be  $C = 10 \times 35/(330-230) = 3.5\mu\text{F}$ . Use the next largest standard value available.

5. Install the capacitor in the C1 location.  
6. R2 is a gate stopper, which will curb any tendency for the CCS to oscillate. The value is not critical; 100Ω should work fine here.  
7. Determine the value for the current sense resistor (R1).

a) Insert a variable resistor into the R1 position.



b) Connect a milliamp meter in series with R1.

c) Connect the actual external load (or a resistor that will draw the same amount of current) to the output of the supply.

d) Apply input power and allow enough time for any tubes to warm up.

e) Adjust R1 for the desired current through the milliamp meter.

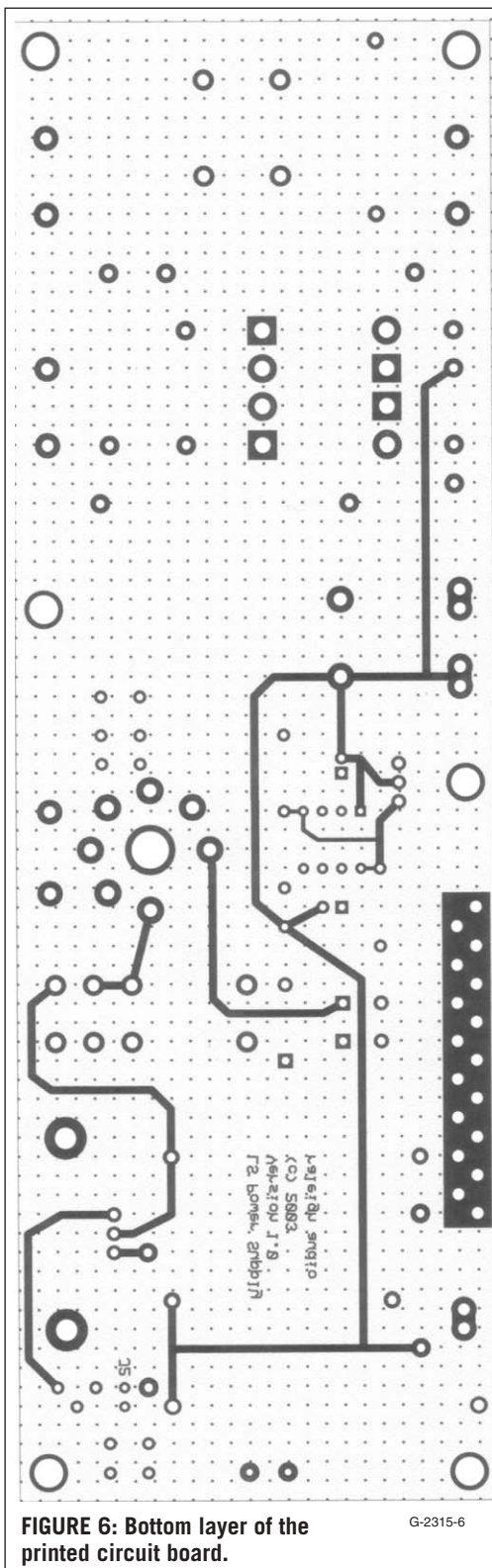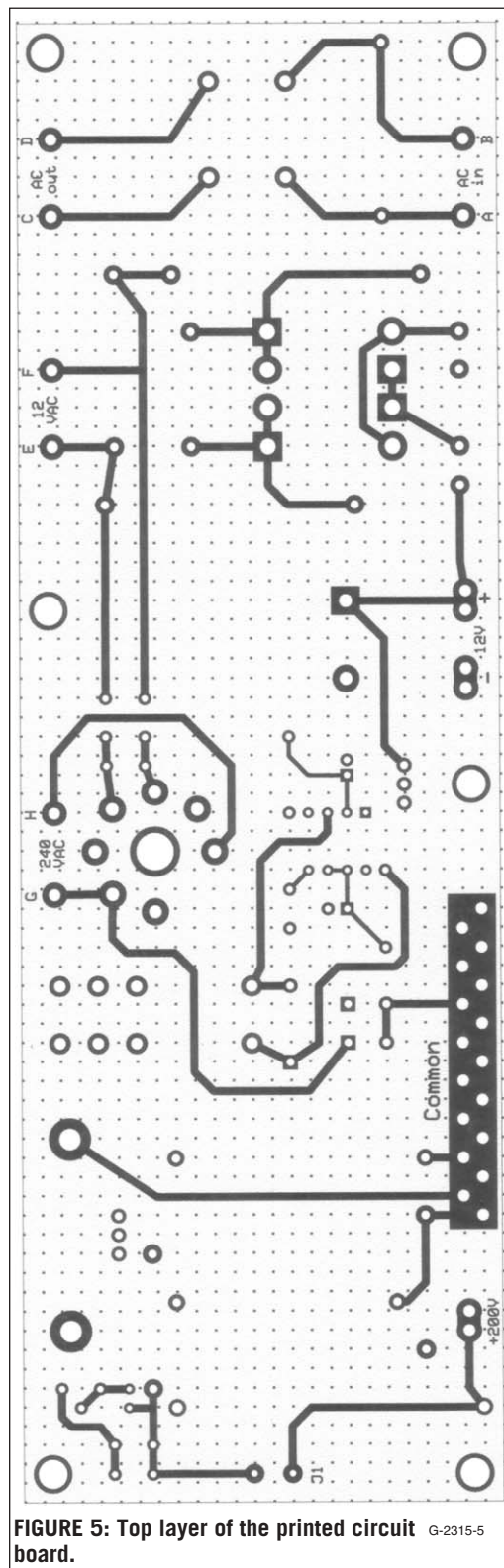f) Check that the residual current through R3 produces the desired voltage.



## SOURCES

Antique Electronic Supply  
6221 S. Maple Ave.  
Tempe, AZ 85283  
480-820-5411  
FAX 480-820-4643

Digi-Key  
PO Box 677  
701 Brooks Ave. S.  
Thief River Falls, MN 56701-0677  
218-681-3380  
FAX 218-681-3380

K&K Audio  
1004 Olive Chapel Rd.  
Apex, NC 27502  
919-387-0911

Michael Percy Audio Products  
11731 Stillwater Creek Rd.  
Nevada City, CA 95959  
530-470-8650  
FAX 530-470-8651

Mouser Electronics  
1000N. Main St.  
Mansfield, TX 76063  
800-346-6873  
FAX 817-804-3899  
sales@mouser.com  
www.mouser.com



If not, adjust the value of R3 or the current through the CCS.

- g) Measure the value of the variable resistor and replace with a fixed resistor.

This is all there is to the basic concept; however, your final design may have some refinements. This supply is transparent, so it is important to use high-quality components. Let me share the complete design of the line stage supply as shown in Fig. 4.

#### FINAL DESIGN

The first thing you will notice is that I have added a power-on-delay timer. Since the supply needs the load to participate in drawing current, it is important that the load be capable of drawing that current. The delay gives the tubes in the line stage a chance to warm up before applying the voltage to them.

Rectifier tube V1, along with diodes D1 and D2, form a hybrid Graetz bridge, which displays the audible characteristics of an all-tube rectifier. Because of the resistance of the tube in series with the solid-state diodes, there is no need

for a reverse recovery spike filter. The 50k output resistor is split to provide a bias to the 12V filament supply. Diodes D4 through D7, together with their associated components, form the 12V supply used to power the timer as well as the line stage filaments.

Common mode choke L1 along with capacitor C1 constitute a power line filter, and the high-quality Lundahl LL1683 is used as a power transformer. Photo 1 shows the completed supply, and printed circuit board layouts are shown in Figs. 5 and 6. The parts list is in Table 1.

Although this power supply is specifically intended to be used with a load that draws a constant current, you could easily adapt it to use with any load. All that you would need is to add a shunt regulator in place of the load resistor. This regulator could incorporate a comparator or be as simple as a single VR tube.

Build a minimal reactance supply for your next audio project, and I believe you will be extremely pleased with the clean, quiet power it supplies and the sonic results it provides. ♦

# Toroids for Audio



#### Tube Output

Toroidal transformers for tube output applications. Plus related products.

Standard Series (push-pull)

Single-ended

Specialist Range

Special Designs

Power Transformers

Chokes

Chassis for Tube Amplifiers

PCB for 70W & 100W Amps

Book by Vanderveen

#### Electrostatic

Step-up toroidal transformers for Electrostatic loudspeaker applications.

#### Solid State Power

Low noise, low inrush  
500 to 2000VA fully encapsulated power transformers.

#### Standard Power

A broad range of high quality, approved, toroidal transformers. Designed for general purpose applications. From 15 to 1500VA.



**PLITRON**  
MANUFACTURING INC

8-601 Magnetic Drive  
Toronto, ON M3J 3J2  
Canada

416-667-9914


FAX 667-8928

**1-800-PLITRON**  
(1-800-754-8766)

**www.plitron.com**
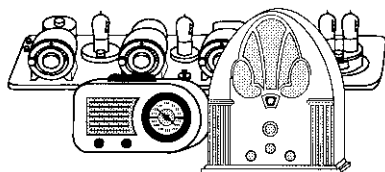
## FREE SAMPLE

IF YOU BUY,  
SELL, OR COLLECT  
OLD RADIOS, YOU NEED...



## ANTIQUE RADIO CLASSIFIED

Antique Radio's Largest Monthly Magazine  
100 Page Issues!

Classifieds - Ads for Parts & Services - Articles  
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,  
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...

Free 20-word ad each month for subscribers.

Subscriptions: \$19.95 for 6-month trial.  
\$39.49 for 1 year (\$57.95 for 1st Class Mail).

Call or write for foreign rates.

#### Collector's Price Guide books by Bunis:

Antique Radios, 4th Ed. 8500 prices, 400 color photos .....\$18.95

Transistor Radios, 2nd Ed. 2900 prices, 375 color photos .....\$16.95

Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741

Phone: (978) 371-0512 — Fax: (978) 371-7129



Web: [www.antiqueradio.com](http://www.antiqueradio.com) — E-mail: [ARC@antiqueradio.com](mailto:ARC@antiqueradio.com)

# Speaker Cables Review

By Charles Hansen and Muse Kastanovich

The parameters of any cable are defined as a combination of electrical resistance, capacitance, and inductance. The DC resistance is a function of conductor length and cross-sectional area. It does not matter whether the total area is composed of a single conductor or multiple conductors.

As the frequency increases, the resistance of a conductor increases due to skin-effect losses. This is the phenomenon by which the alternating current in a conductor concentrates near the surface, increasing the effective resistance. Round conductors show a more pronounced skin effect than thin flat conductors.

## CABLE THEORY

The voltage between two conductors produces an electric field. When an insulator is interposed between the conductors, the molecules of the insulator rotate slightly and produce a field within the insulating material that opposes the applied field. The electric field  $E$  is reduced below the equivalent free space applied field intensity  $E_0$  by a factor equal to the insulating material's dielectric constant relative to free space,  $\epsilon_r$ .

$$E = E_0 / \epsilon_r$$

The lower the dielectric constant of the

insulator, the less the reduction (loss) in the total electric field.

Flat wire cables form parallel plate capacitors. The capacitance can be calculated from:

$$C = (\epsilon_0 \epsilon_r A) / d$$

where  $\epsilon_0$  is the permittivity of free space, and  $\epsilon_r$  is the relative dielectric constant of the insulating material. This varies with material, temperature, and frequency.  $A$  is the area of a plate, and  $d$  is the separation between the plates.

The round wire cables form parallel wire capacitors. You can calculate the capacitance of this arrangement without a ground plane by:

$$C = \pi \epsilon_0 \epsilon_r l / \log_e (d/r)$$

where  $e = 2.718$ ,  $\epsilon_0$  is the permittivity of free space,  $\epsilon_r$  is the relative dielectric constant of the insulating material,  $l$  is the length,  $d$  is the separation between the wires, and  $r$  is the wire radius. Note that  $d$  must be much larger than  $r$ , a condition not always met with speaker cables. Large

gauge, closely spaced round conductors may more closely approximate parallel plate capacitors.

Speaker cables also have the properties of series inductors. You can determine the inductance of two rectangular strips by:

$$L = [0.4l(0.5 \log_e (2dl/(w+h)) + 0.22(w+h)/l)]$$

where  $l \gg w, h$

where  $l$  is the length,  $d$  is the distance between the strips,  $w$  is the width of a strip, and  $h$  is the height of a strip.

To find the inductance for two parallel wires carrying equal and opposite currents, use:

$$L = [0.1 + 0.4 \log_e (d/r)] l$$

where  $(d \gg r)$

where  $d$  is the distance between the



PHOTO 1: Alpha-Core Goertz MI 2.

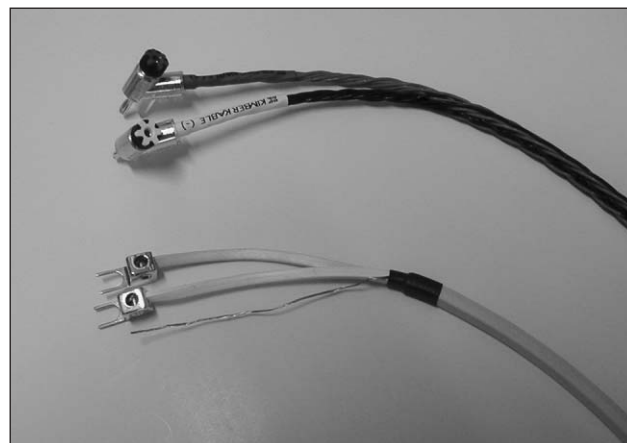


PHOTO 2: Kimber Kable 8TC and Supra 3.4/S.

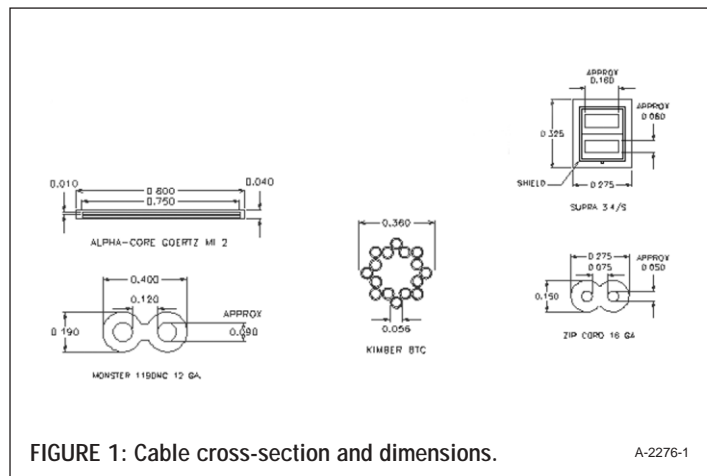


FIGURE 1: Cable cross-section and dimensions.

A-2276-1

wires,  $r$  is the wire radius, and  $l$  is the length.

Thus you can see that the impedance of a speaker cable will vary with frequency as well as the distance between conductors. Capacitance varies in proportion to distance, while inductance varies inversely with distance.

The wire resistance is in series between the amplifier and loudspeaker, and increases with frequency due to skin effect. The skin effect is essentially the same for a conventionally stranded wire as it is for a solid conductor of the same material and the same net cross-sectional area. The skin depth is the depth below the conductor surface where the current density has decreased by  $1/e$ , and for copper at 20kHz it is about 0.5mm (0.02").

Skin effect at 20kHz will increase the resistance by 7% to 34%, depending on the cross section profile. This presents a problem in measuring impedance at higher frequencies. As Bob Pease of National Semiconductor pointed out, when you try to measure pure inductance, you may also measure some of the skin effect. Cable capacitance tends to cancel inductance, so you may confuse inductive phase shift measurements with skin effect.

The cable inductance is also in series between the amplifier and loudspeaker. The inductive reactance in ohms is equal to  $2\pi fL$ . The resistance and reactance do not add arithmetically because the reactance lags resistance by  $-90^\circ$ , so the series impedance is the root-sum-square of the two.

Capacitance has the least effect on the performance of a speaker cable. This is because the cable capacitance is small to begin with and is shunted by the significantly lower amplifier and loudspeaker impedances. Capacitive reactance in ohms is equal to  $1/(2\pi fC)$ . Capacitive reactance leads resistance by  $+90^\circ$ . The shunt capacitance will tend to cancel some of the series inductance as frequency increases.

The complex sum of these L, R, and C components determines the equivalent series impedance of a speaker cable. The phase shift introduced by a cable is proportional to its complex series impedance. The flat wire cables have higher capacitance but lower inductance than the round wire cables.


## CABLE CONSTRUCTION DETAILS

There are seemingly endless processes for constructing speaker cables. The cables provided for testing include a flat-wire type, one with woven wires, one with stranded wire in a rectangular jacket, and one conventional round stranded wire cable. I also added a sample: the infamous 16-gauge zip cord. Test sample lengths varied from 3' to 10'. The 3' lengths may not be long enough for systems with satellites on stands. I used a vernier caliper to measure the dimensions of all the cables. The results are shown in Fig. 1.

The Alpha-Core Goertz MI 2 "T"-series is a bi-wire speaker cable. Each conductor is a  $0.35 \times 0.010$ " solid band of high-purity oxygen-free copper (OFC) surrounded by a 0.005-inch (5 mil)-thick sheath of  $0.8 \times 0.04$ " polyethylene

terephthalate (PET, or polyester, same polymer as Mylar™) insulation. The stiff conductors are placed in close mutual contact inside a 5 mil clear PET jacket. PET has a fairly stable dielectric constant of about 3.2, which decreases about 3% at 1MHz. Polyester film is slightly hygroscopic—it absorbs water by a factor of 0.2% in the presence of high humidity.

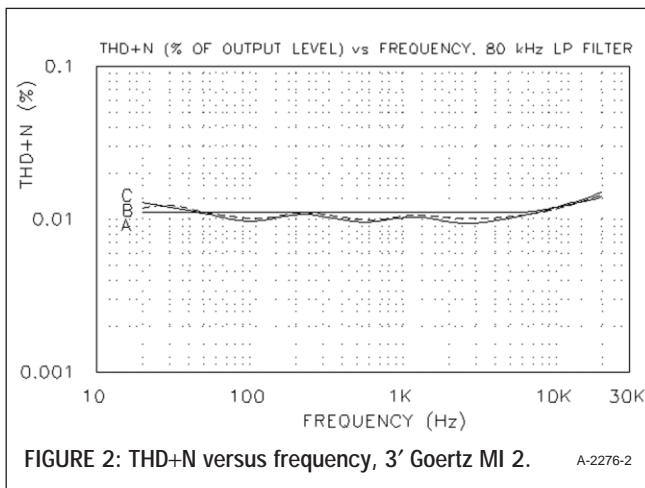The mutual distance between the conductors is 0.003 inches, and the overall cross-section is approximately



# AUDIO TRANSFORMERS

AMERICA'S PREMIER COIL WINDER

Engineering • Rewinding • Prototypes

McINTOSH - MARANTZ - HARMAN-KARDON  
WESTERN ELECTRIC - TRIAD - ACROSOUND  
FISHER - CHICAGO - STANCOR - DYNACO  
LANGEVIN - PEERLESS - FENDER - MARSHALL  
ELECTROSTATIC SPEAKER TRANSFORMERS

*Williamson Amplifier Transformer Specialist*

WE DESIGN AND BUILD TRANSFORMERS

FOR ANY POWER AMPLIFIER TUBE

PHONE: [414] 774-6625 FAX: [414] 774-4425

AUDIO TRANSFORMERS

185 NORTH 85th STREET

WAUWATOSA, WI 53226-4601

E-mail: ATRAN@AOL.com

NO CATALOG

CUSTOM WORK



0.8 by 0.040". The space ratio is close to 50%. The conductor cross-section approximates AWG 10. Rhodium-plated connectors are available to terminate the cable. *Photo 1* shows the amplifier end of the MI 2 cable test sample.

R/C Match Links are provided with the MI 2 cables. The Match Links consist of a pair of Zobel networks, 100nF in series with 10Ω. They are intended to be placed across the speaker terminals in systems with high GBW solid-state amplifiers and loudspeakers with high impedance at high frequencies to prevent oscillation. "Chances are you'll not need these," it says on the package.

The Kimber 8TC consists of 16 individual VariStrand™ PTFE (Teflon™) insulated wires (eight wires for each channel) arranged in a hollow, large format braid. PTFE is the most stable of the dielectric materials, with a low dielectric constant of 2.1. The aggregate wire gauge size is equivalent to two

nine-gauge conductors. The tightly braided configuration and the Teflon™ insulation make these cables a bit stiff.

Various terminations are available: spades, angled and straight banana plugs, even plain ends. The test cables had WBT-0144 angled banana plugs. *Photo 2* shows the Kimber 8TC (top) and the Supra 3.4/S (bottom).

The Supra 3.4/S uses tin-plated copper wire strands arranged in a rectangular cross-section. The slash-S designation identifies the screened ply by which the two main conductors are surrounded by a braided shield with a drain wire at the amplifier end of the cable. This drain wire is intended to be connected to the

amplifier chassis, to limit the EMI radiated from the cables. The shield and the ion-stabilized polyvinyl chloride (PVC) double jacketing make this cable rather stiff. The terminations are Supra Fork XL gold-plated spade plugs.

The conductors in the Monster 1190MC 12-gauge speaker cable are concentric rope lay stranded wire with eight individual helical wound members. The rope lay construction makes this cable very flexible. The insulation material is


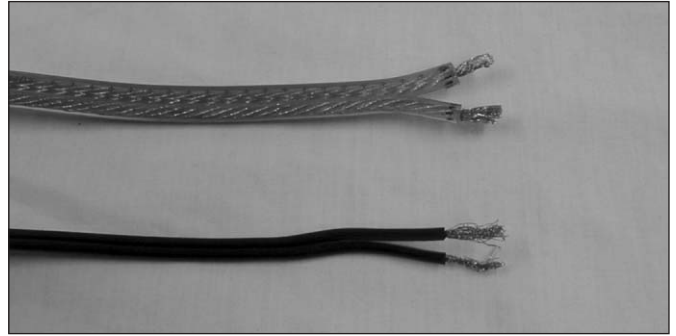
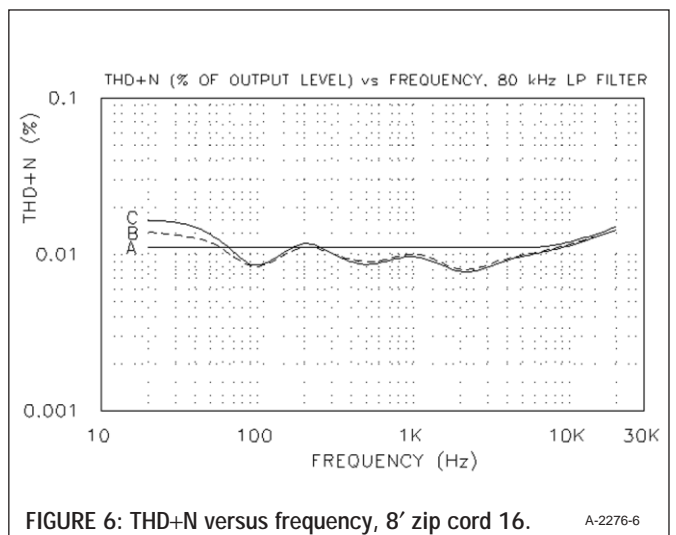
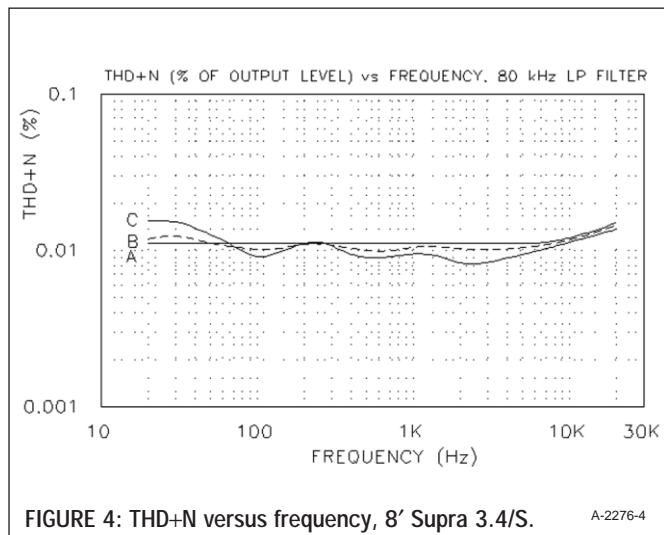
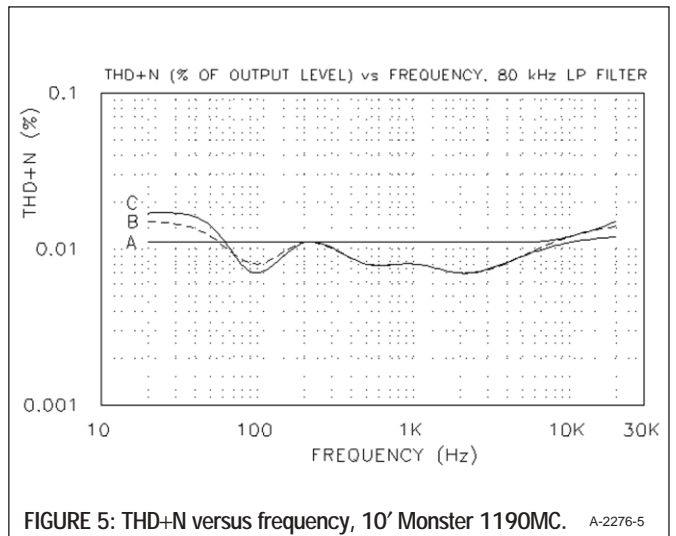


PHOTO 3: Monster 1190MC cable and 16-gauge zip cord.

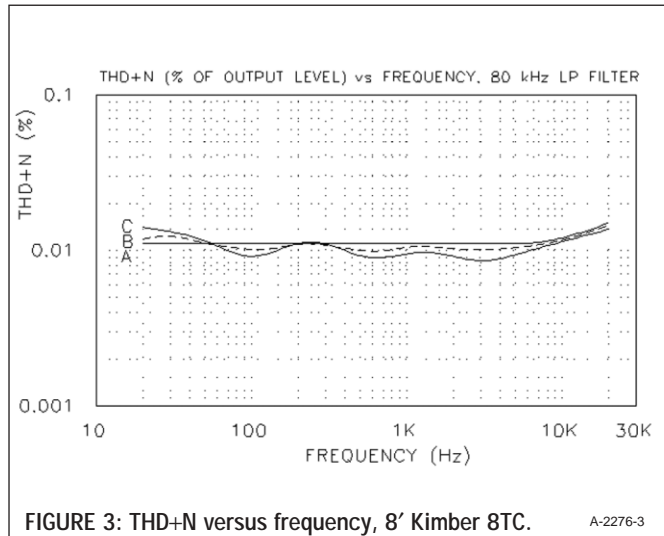

linear polyethylene, which has a stable dielectric constant of about 2.3, changing less than 1% at 1MHz. The 1190MC is Monster's original cable design.

The Radio Shack Megacable and Phoenix Gold cables appear to be similar in construction. My unofficial wire count is that each of the eight helical members contains 33 strands of AWG-37 wire. These individual strands are not insulated, so this construction is not the same as Litz wire<sup>1</sup>. *Photo 3* shows the Monster cable (top) and the zip cord (bottom).

The 16-gauge zip cord is intended for lower current household appliances. My sample consisted of 40 strands of 32-gauge wire, with plain PVC insulation. Ordinary PVC has a rather high dielectric coefficient of 4.7 compared with other polymers. The dielectric coefficient also decreases by 46% at 1MHz.

## MEASUREMENTS

The cable samples vary from three feet to ten feet long. I measured the total capacitance, inductance, and resistance of each sample with two types of digital LCR meters. The HP 4261A performs measurements at 120Hz and 1kHz. The AADE L/C IIB uses a resonance measurement method with a variable frequency signal.

I also measured the DC leakage current of the dielectric using a Keithley 480 picoammeter as a measure of insulation quality. A 12V DC gel cell battery biased the cables. I made all measurements with the samples laid out in a straight line.

The MI 2 is quite stiff, so I needed to clamp it down to hold it flat and straight. Capacitance is measured between the two open circuit conductors (four in the case of the MI 2). The HP 4261A also measures capacitance dissipation factor (DF), which is an expression of the power loss in the dielectric. DF is the ratio of the equivalent series resistance (ESR) to the capacitive reactance (Xc), and is a measure of the insulator's ability to store energy at a given frequency. A lower dissipation factor is better.

The capacitance of the Supra 3.4/S dropped from 944pF to 328pF when I attached the shield drain wire to the guard terminal of the HP 4261A. This is because an adjacent ground plane re-

duces the mutual capacitance. Were the ground plane to be in between the conductors (a Faraday shield), the capacitance drop would be even greater.

Inductance is measured by short-circuiting one end of the cable and connecting the LCR meter to the open end. Resistance is measured the same way, so the L and R per foot is the sum of both conductors. The inductance measurements for the MI 2 were a bit erratic because of the bi-wire pair parallel cables. I ended up shorting the amplifier end, then measuring each of the pairs independently. Then I computed the equivalent parallel inductance  $L_p = L_a * L_b / (L_a + L_b)$ .

This measured inductance of 18nH/ft for the MI 2 turned out to be higher than the

specified 6nH/ft. This caused the calculated characteristic impedance, which is equal to  $\sqrt{L/C}$  and is independent of length, to also be higher than specified.

I also took a 10' length of the flexible Monster 1190MC wire and measured its parameters first as a straight run of cable, and then coiled its full length on the floor in 8" diameter loops. The total capacitance increased by 7% while the

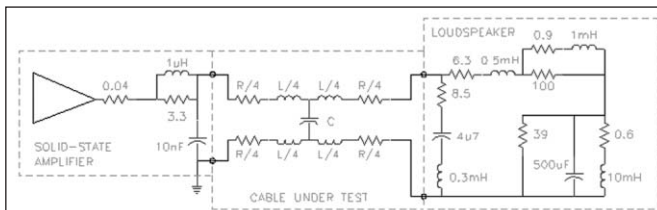


FIGURE 7: Solid-state amplifier system SPICE model.

A-2276-7


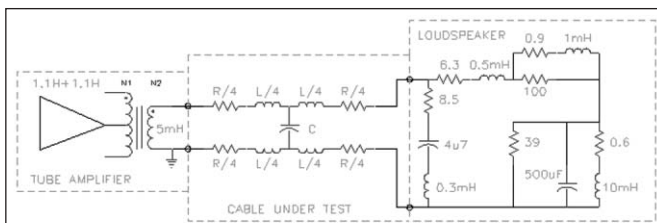


FIGURE 8: Tube amplifier system SPICE model.

A-2276-8

# Test Equipment Depot

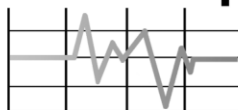

800.996.3837

The source for premium electronic testing equipment

## New & Pre-Owned

- Oscilloscopes
- Power Supplies
- Spectrum Analyzers
- Signal Generators
- Digital Multimeters
- Network Analyzers
- Function Generators
- Impedance Analyzers
- Frequency Counters
- Audio Analyzers



Call now to speak to one of our knowledgeable salespeople or browse our extensive online catalog

[www.testequipmentdepot.com](http://www.testequipmentdepot.com)

- Sales • Repair & Calibration • Rental • Leases • Buy Surplus

inductance remained the same.

The standard 25°C resistance for one-foot pairs of wires is 1.58mΩ for 9-gauge, 2mΩ for 10-gauge, 3.18mΩ for 12-gauge, and 8.03mΩ for 16-gauge.

Using the measured data, I calculated the C, L, and R per foot, the characteristic impedance (Zo), the insulation resistance (Rp), and the cable resonant frequency. Using the physical measurements of the cables, I calculated Rac/Rdc ratio and the effective skin effect resistance at 20kHz. This varied from 107% of the DC resistance (Goertz) to 132% (zip cord). The data is summa-

rized in Table 1.

The Goertz, Kimber, and Supra cables came with characteristic data. I compare this specification data with my measured data in Table 2.

### TESTS

With my audio system warmed up, I first measured the THD+N versus frequency with 2V RMS across an 8Ω resistor connected directly to my Parasound HCA-1000A solid-state amplifier output terminals. Next, I connected each of the test cables in series with the 8Ω resistor and measured the THD+N

at the resistor. There was essentially no difference in the readings with or without the cable. Unfortunately, I did not have a tube power amplifier available for these tests.

I repeated the THD+N vs. frequency test with each cable connected between the amplifier and one of my satellite loudspeakers, an NHT Super-One. I held 2V RMS at the amplifier terminals. Now there was some measurable difference compared to the THD+N that I measured with the 8Ω resistive load alone. The three curves on each graph represent (A) the 8Ω resistive load from

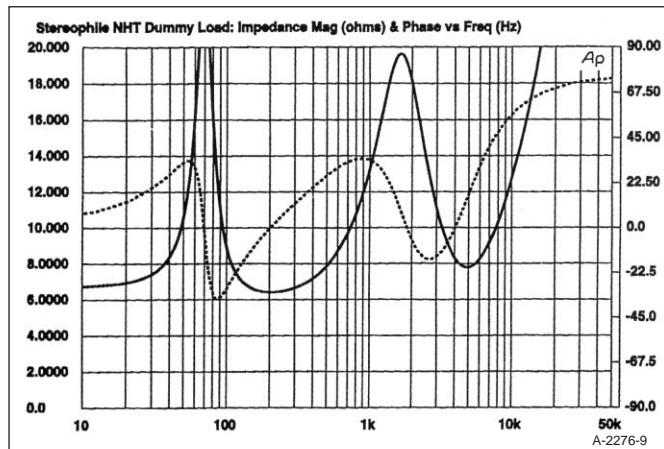


FIGURE 9: Kantor speaker simulator impedance/phase plot.

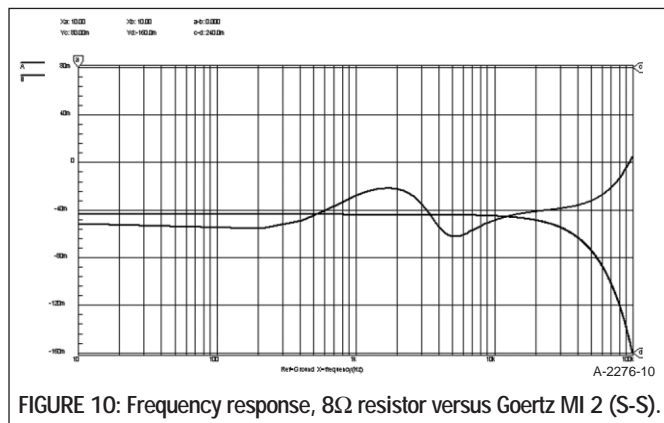


FIGURE 10: Frequency response, 8Ω resistor versus Goertz MI 2 (S-S).

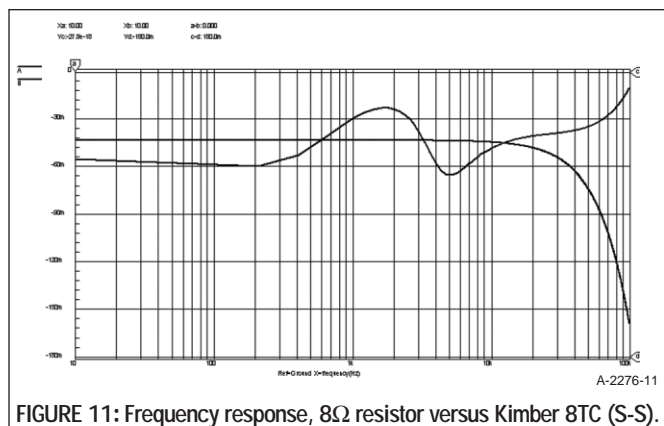


FIGURE 11: Frequency response, 8Ω resistor versus Kimber 8TC (S-S).

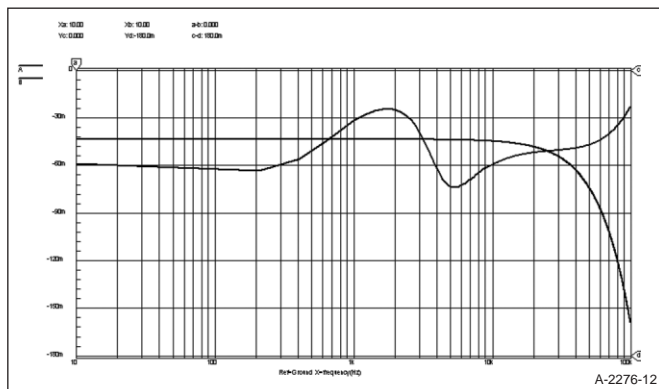


FIGURE 12: Frequency response, 8Ω resistor versus Supra 3.4/S (S-S).

TABLE 1

#### MEASURED AND CALCULATED PARAMETERS

Cable	Goertz (MI 2)	Kimber (8TC)	Supra (3.4/S)	Monster (12)	Zip (16)	Units
Measured C	2,090.0	836.0	944.0	61.7	66.5	pF
Dissipation Factor	0.002	0.001	0.069	0.056	0.063	%
Measured L	54.0	86.0	694.0	580.0	606.0	nH
Measured R	4.80	21.00	27.00	12.00	23.90	mΩ
Length	3	8	8	3	3	ft
AWG equivalent	10	9	12	12	16	
Insulation	PET	TFE	Stabil.PVC	Linear PE	PVC	
Leakage current	0.3	0.6	1.1	1.1	0.7	pA
Rparallel	38.1	190.5	2.4	46.1	38.0	MΩ
C per ft	696.7	104.5	118.0	20.6	22.2	pF/ft
L per ft	18.00	10.75	86.75	193.3	202.0	nH/ft
R per ft	1.60	2.63	3.38	4.00	7.97	mΩ/ft
Characteristic Zo	5.1	10.1	27.1	97.0	95.5	Ω
Lkg per ft.	0.1	0.1	0.1	0.4	0.2	pA
Resonant Frequency	47	59	20	84	79	MHz

TABLE 2

#### MANUFACTURER'S SPECIFICATIONS VERSUS MEASUREMENTS

Parameter	Goertz spec	Goertz measured	Kimber spec	Kimber measured	Supra spec	Supra measured
C per ft	950pF	697pF	100pF	105pF		
L per ft	6.0nH	18nH	50nH	10.8nH	61nH	87nH
R per ft	2.2mΩ	1.60Ω	2.2mΩ	2.63mΩ	1.55mΩ	3.38mΩ
Zo	2.5Ω	5.1Ω				



the initial tests, (B) the THD+N at the amplifier terminals with the cable connected to the speaker, and (C) the THD+N at the speaker terminals.

Figure 2 shows the THD+N versus frequency for the Goertz MI-2, Fig. 3 the Kimber 8TC, Fig. 4 the Supra 3.4/S, Fig. 5 the Monster 1190MC, and Fig. 6 the 16-gauge zip cord. Bear in mind the varying lengths here.

I intended to measure voltage drop and phase shift with each cable installed in one channel of my audio system. However, with 2V RMS at the amplifier terminals, the voltage drop at the speaker end of the worst-performing cable (8' zip cord) was 71mV at 20Hz, 76mV at 211Hz, 37mV at 1kHz, 87mV at 5kHz, and 63mV at 20kHz. At 5kHz this is a -0.4dB loss with a phase shift of 0.3°. The attenuation and phase shift in the 3' lengths of test cable were much smaller. In order to obtain graphical information on comparative 8' lengths, I decided to model the cables as part of an audio system in SPICE.

### SPICE SIMULATIONS

Using the measured parameters, I modeled each cable as part of a SPICE model audio system in order to determine its effect on magnitude and phase. I used both solid-state and tube amp models. The cable models are T-section equivalents based on my actual measurements. The loudspeaker model is the one proposed by Ken Kantor<sup>2</sup> with a nominal impedance of 8Ω.

**Caveat:** SPICE does not model the back-emf of the driver or the many low-level mechanical resonances present in a real loudspeaker. You should consider these simulations comparative rather than absolute.

Figure 7 shows the solid-state system model, based on an NAD-214 amplifier, for which I have the service manual and thus the schematic. The closed-loop output impedance is 0.04Ω at 1kHz, increasing to 0.16Ω at 20kHz.

Figure 8 shows the tube amp system model, based on the high-frequency model proposed by Scott Reynolds<sup>3</sup>. It has an output impedance of about 0.6Ω at 1kHz. Other tube amp SPICE models are available on the web if you want to experiment<sup>4</sup>.

Each amplifier model is set for an open-circuit output voltage of 2V RMS at

1kHz. I ran simulations with an 8Ω resistor directly across the amplifier terminals, and with each cable in series with the loudspeaker model. I used two identical amplifier channels in the simulations to avoid interaction between the 8Ω resistor and the cable/loudspeaker models. The vertical scale is in dB relative to 2V RMS.

The nominal 8Ω speaker impedance has peaks of >20Ω at 70Hz and above 15kHz, 18Ω at 1.5kHz, and reaches down to 6.5Ω at 200Hz. Figure 9 displays the impedance/phase graph.

Figure 10 shows the modeled response of the Goertz MI 2 as a composite (not bi-wired) 8' cable. The top line at 100Hz is the response across the 8Ω resistor directly across the amplifier terminals. The output is a flat -0.043dB over the audio band (1.99V at the resistor), until it drops

due to the increasing impedance of the amplifier's RLC network outside the feedback loop. This network is designed to make the amplifier inherently stable with all speaker loads.

The MI 2 cable shows the peaks and dips as a result of the complex impedance of the loudspeaker model. These excursions vary from -0.021dB at 1.8kHz to -0.062dB at 5.2kHz, representing voltages of 1.996V to 1.986V, respectively, at the speaker terminals. The phase shift at the loudspeaker terminals over the audio band (not shown)

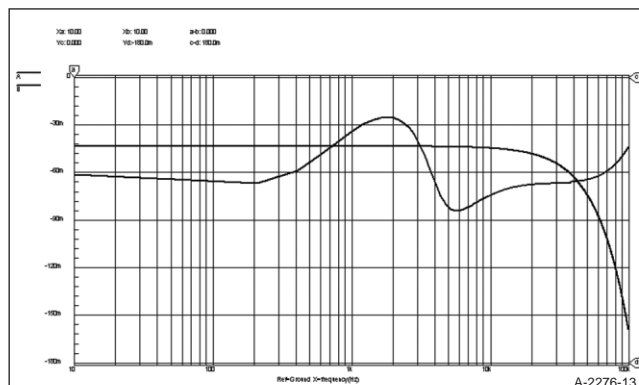


FIGURE 13: Frequency response, 8Ω resistor vs. Monster 1190MC (S-S).

Audio Consulting

# Emotion in Sound

[www.audio-consulting.ch](http://www.audio-consulting.ch)

**GLASPERLENSPIEL** Single ended 300B stereo amplifier featuring SMPS and 4 Silver Rock transformers

**DULCET** 98 dB/w/m efficient Two driver loudspeaker system by Mantra Sound

**ROCK SOLID** Silver wire input transformer solid state amplifier Point-to-point silver wiring

**SILVER ROCK** Silver wire passive transformer-attenuator preamplifier

**SILVER ROCK PHONO** Solid state phono preamplifier with MC silver wire step-up and inductive RIAA equalization

varies from  $+0.099^\circ$  at 639Hz to  $-0.182^\circ$  at 3.5kHz, using the phase shift across the  $8\Omega$  resistor as a  $0^\circ$  reference.

In order to determine phase shift at 20kHz as accurately as possible, I substituted the skin effect resistance for the DC resistance in the cable model. The rise in response above 30kHz is due to the increasing impedance of the loudspeaker, which rises faster than that of the amplifier. Note that if the values of L, R, and C specified by Alpha-Core for the M-1 are used in the cable model, the excursions are  $-0.018\text{dB}$  to  $-0.059\text{dB}$  with the phase shift varying between  $+0.092^\circ$  and  $-0.180^\circ$ . This is a negligible difference.

Figure 11 is the response model for the 8' Kimber 8TC. The peaks and dips as a result of the complex impedance of the loudspeaker model vary from  $-0.023\text{dB}$  to  $-0.065\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+0.111^\circ$  to  $-0.180^\circ$ .

Figure 12 depicts the response model for the 8' Supra 3.4/S. The peaks and dips as a result of the complex impedance of the loudspeaker model vary from  $-0.024\text{dB}$  to  $-0.073\text{dB}$ . The phase shift at the loudspeaker terminals

varies from  $+0.111^\circ$  to  $-0.224^\circ$ .

The next 8' modeled cable is the Monster 1190MC 12 gauge cable. Figure 13 shows the peaks and dips as a result of the complex impedance of the loudspeaker model, which vary from  $-0.025\text{dB}$  to  $-0.084\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+0.107^\circ$  to  $-0.286^\circ$ .

Finally we come to the 16-gauge zip cord (Fig. 14). The peaks and dips as a result of the complex impedance of the loudspeaker model vary from  $-0.032\text{dB}$  to  $-0.098\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+0.150^\circ$  to  $-0.297^\circ$ .

I took the zip cord and loaded it with the  $8\Omega$  resistor rather than the speaker model (Fig. 15). The response across the resistor, which was  $-0.043\text{dB}$  at the amplifier terminals, is  $-0.056\text{dB}$  at the end of the 8' zip cord (bottom trace at 2kHz), with a slightly greater  $-0.062^\circ$  lagging phase shift at 1kHz. Compare this linear response to the rises and dips for that of the cable terminated with the speaker model.

I summarize the SPICE simulation magnitude and phase shift data for the solid-state amplifier models in Table 3.

Figure 16 shows the Goertz MI 2 (L, R, and C as measured) feeding the tube amp model, compared with an  $8\Omega$  resistor at the output terminals of the tube amp. Again, I used two separate amplifier channels to prevent interaction. You can see the greater degree of interaction between the amplifier and the complex impedance of the loudspeaker. The flat portion of the  $8\Omega$  resistor load is down to  $1.862\text{V}$  or  $-0.63\text{dB}$ . The combination of cable and loudspeaker varies from  $-0.041\text{dB}$  at 34kHz to  $-0.694\text{dB}$  at 211Hz. The phase shift at the loudspeaker terminals varies from  $+1.77^\circ$  at 6.5kHz to  $-1.04^\circ$  at 2.8kHz.

The combination of the 8' Kimber 8TC cable and loudspeaker models (Fig. 17) varies from  $-0.041\text{dB}$  to  $-0.700\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+1.80^\circ$  to  $-1.04^\circ$ .

The combination of the 8' Supra 3.4/S cable and loudspeaker models (Fig. 18) varies from  $0.052\text{dB}$  to  $-0.702\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+1.76^\circ$  to  $-1.06^\circ$ .

The combination of the 3' Monster 1190MC cable and loudspeaker (Fig.

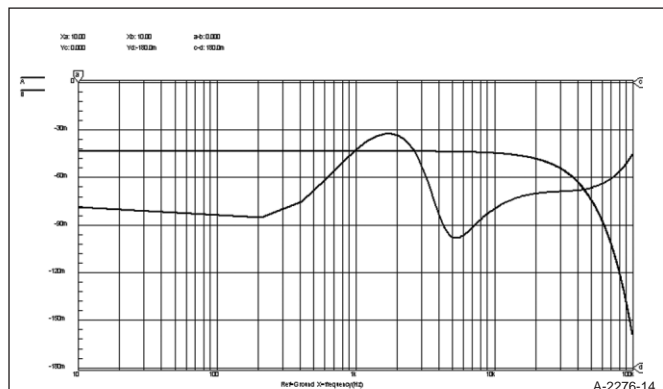


FIGURE 14: Frequency response,  $8\Omega$  resistor versus zip cord 16 (S-S). A-2276-14

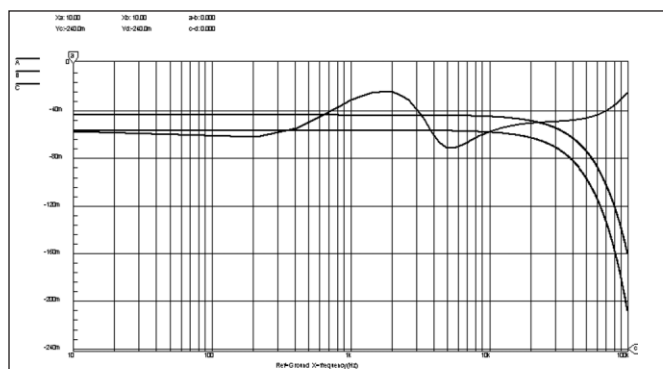


FIGURE 15: Frequency response,  $8\Omega$  resistor versus zip cord 16 with  $8\Omega$  load, speaker load (S-S). A-2276-15

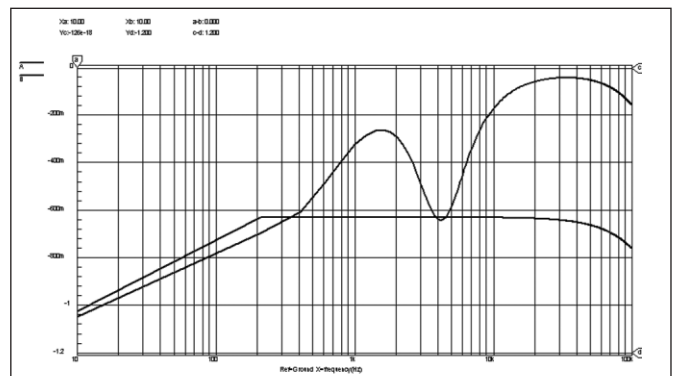


FIGURE 16: Frequency response,  $8\Omega$  resistor versus Goertz MI 2 (tube). A-2276-16

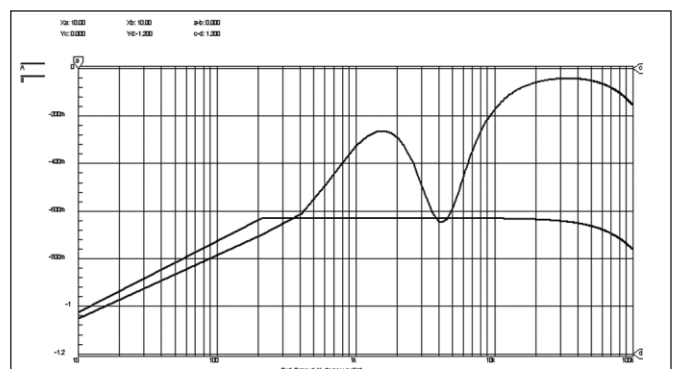


FIGURE 17: Frequency response,  $8\Omega$  resistor versus Kimber 8TC (tube). A-2276-17

19) varies from  $-0.068\text{dB}$  to  $-0.705\text{dB}$ . The phase shift at the loudspeaker terminals varies from  $+1.69^\circ$  to  $-1.10^\circ$ .

Using the 16-gauge zip cord in the same tube amp simulation setting (Fig. 20) shows the response varying from  $-0.070\text{dB}$  to  $-0.720\text{dB}$ . The phase shift varies from  $+1.73^\circ$  to  $-1.12^\circ$ .

The SPICE simulation magnitude and phase shift data for the tube amplifier models are summarized in Table 4.

The increase in skin effect resistance at 20kHz seems to have less consequence than you might imagine. The increase in inductive reactance from 1kHz to 20kHz has a much greater effect on the series impedance than does skin effect. The increase in the RL series impedance component of the six cables from 1kHz to 20kHz is listed in Table 5. Note the much higher percent increases for the last three stranded cables, with their higher inductance. The first two cables have a double advantage due to their geometry: low inductance and low skin effect.

#### CONCLUSIONS . . . SORT OF

Looking at Figs. 2 through 6, you can see the distortion levels decrease in every case at the peaks of the loudspeaker impedance when compared with the essentially flat distortion curve for the  $8\Omega$  resistor. At the high-frequency end of the curve, where you might expect the rising cable impedance to have an effect, the distortion is essentially identical to that of the resistor alone. The more pronounced rise in distortion at the low frequencies, where the cable is essentially a resistor, may be due to woofer distortion in the satellite speaker, whose  $-3\text{dB}$  point is 57Hz.

The distortion excursions are lowest with the short 3' flat wire cable, and highest with the 10' length of Monster cable and 8' length of 16-gauge zip cord. In the mid-range the measured distortion is lowest with the 10' Monster cable than with the other cables, but its low-frequency distortion is also one of the highest. Of the three 8' cables, the Kimber has the lowest overall distortion excursions. This suggests that short lengths of low resistance, low inductance cable are going to be the most accurate.

There is no question that there are also measurable LRC differences be-

tween these three speaker cables. However, the 1kHz impedance of even the 10' length of Monster cable is less

than the  $40\text{m}\Omega$  source impedance of the solid-state amp and far less than the impedances of the tube amp and

TABLE 3

SPICE SIMULATION RESULTS—SOLID-STATE AMPLIFIER

	Goertz MI 2	Kimber 8TC	Supra 3.4/S	Monster 12	Zip 16	Units
min attenuation at Freq =	-0.021	-0.023	-0.024	-0.025	-0.032	dB
max attenuation at Freq =	1.8	1.7	1.7	1.8	1.8	kHz
min phase shift at Freq =	-0.062	-0.065	-0.073	-0.084	-0.098	dB
max phase shift at Freq =	5.2	5.1	5.4	5.8	5.3	kHz
+ phase shift at Freq =	0.099	0.111	0.111	0.107	0.150	degrees
- phase shift at Freq =	639	623	623	631	631	Hz
+ phase shift at Freq =	-0.182	-0.180	-0.224	-0.286	-0.297	degrees
- phase shift at Freq =	3.5	3.3	3.5	3.6	3.5	kHz

TABLE 4

SPICE SIMULATION RESULTS—TUBE AMPLIFIER

Cable:	Goertz MI 2	Kimber 8TC	Supra 3.4/S	Monster 12	Zip16	Units
VT min atten at freq =	-0.041	-0.041	-0.052	-0.068	-0.070	dB
VT max atten at freq =	34	34	34	34	34	kHz
VT max + phase shift at Freq =	-0.694	-0.700	-0.702	-0.705	-0.720	dB
VT max - phase shift at Freq =	211	211	211	211	211	Hz
+ phase shift at Freq =	1.77	1.80	1.76	1.69	1.73	deg
- phase shift at Freq =	6.5	6.4	6.5	6.5	6.5	kHz
+ phase shift at Freq =	-1.04	-1.04	-1.06	-1.10	-1.12	deg
- phase shift at Freq =	2.8	2.8	2.8	2.8	2.8	kHz

## Precision Acoustic Measurements Require Precision Microphones



**PS9200KIT™ \$1650 USD**

A complete IEC and ANSI traceable Type 1 Measurement Microphone System 2 Hz to 40 kHz, 15 dBA to 160 dB SPL  
 \* $\frac{3}{4}$  inch capsule \*4012 Preamp \*PS9200 2 Channel PS  
 \*AC adaptor \*WS1 windscreen \*SC1 die cut storage case.  
 Options: S11E Calibrator; 1 &  $\frac{1}{4}$  inch mics; and Gain for DRA's MLSSA and other board level products.

**ACO Pacific, Inc.**

2604 Reed Ave. Belmont, CA 94002 USA  
 Tel: (650) 595-8588 FAX: (650) 591-2891  
 e-mail: aco\_pac@acopacific.com

**ACOustics Begins With ACO™**



loudspeaker, especially the loudspeaker. Only the 16-gauge zip cord impedance is higher than the solid-state amplifier source impedance. At 20kHz, the zip cord and the long Monster cable impedances are both higher than the solid-state amplifier source impedance. In all cases, the variations in speaker impedance across the audio band result in voltages at the speaker terminals that vary above and below those across the fixed 8Ω load alone.

### CHARACTERISTIC IMPEDANCE

Any transmission line exhibits a certain amount of loss due to the conductor resistance and dielectric leakage current loss in the insulation. Line loss increases when the line termination is not equal to the line characteristic impedance. At frequencies where the transmission line length is an appreciable fraction of the wavelength, a mismatch in line termination from the line's characteristic impedance will produce reflections from the mismatched termination back to the source of the signal. The phase and amplitude of the reflected energy will vary with the degree of mismatch in impedance. The sum of the voltage vectors flowing toward the load is called the incident wave, and the sum of the voltage vectors flowing back to the source is called the reflected wave.

Note that one important consideration here is the ratio of line length  $l$  to wavelength  $\lambda$ . For audio signals, even the longest practical speaker cables are an infinitesimal fraction of the signal wavelength. The wavelength of a 20kHz audio signal, even after accounting for the drop in signal velocity propagation factor due to the cable configuration, is over 39 kilometers.

The flat wire cable characteristic impedance comes closest to the nominal loudspeaker impedance. However, irrespective of the extremely small  $l/\lambda$  ratio, any attempt to match the characteristic impedance of the speaker cable to the system components is also thwarted by the large excursions in speaker impedance over the audio band.

The flat wire cable and the open weave Kimber cable, with their low series inductance and resistance, have lower losses and phase shift than the stranded cables. This is most evident in the simulations with the solid-state amplifier. The closest comparison of the measurable inductance differences between the various cable configurations is with the two 12-gauge cables (Supra 87nH/ft, and Monster 193nH/ft).

Still, the maximum attenuations for the five 8' cable

models differ by less than 0.036dB, and the difference in total phase shift is less than 0.054°. The higher capacitance of the flat wire cable should not cause instability in a well-designed solid-state amplifier. If it does, the problem lies with the amplifier design, not the cable (Goertz does supply those Match Links).

With the tube amp model, the situation is more complicated. Here the interaction of the higher output impedance of the tube amplifier (i.e., lower damping factor) interacts with the complex speaker impedance, producing greater voltage excursions across the loudspeaker than those of the solid-state amplifier. However, the cables just seem to be going along for the ride. There are again negligible differences in the attenuation (0.026dB) or phase shift (0.060°) across the cables, from the amplifier to the speaker terminals, regardless of the cable model used.

Finally, with respect to the differences in insulation materials, there will be a much greater variation in shunt capacitance with the plain PVC zip cord

TABLE 5

#### RL SERIES IMPEDANCE VERSUS FREQUENCY

Cable:	Goertz	Kimber	Supra	Monster	Zip 16
RL impedance at 1kHz	12.8mΩ	21.0mΩ	27.3mΩ	33.4mΩ	64.5mΩ
RL impedance at 20kHz	22.7mΩ	27.0mΩ	94.0mΩ	199mΩ	220mΩ

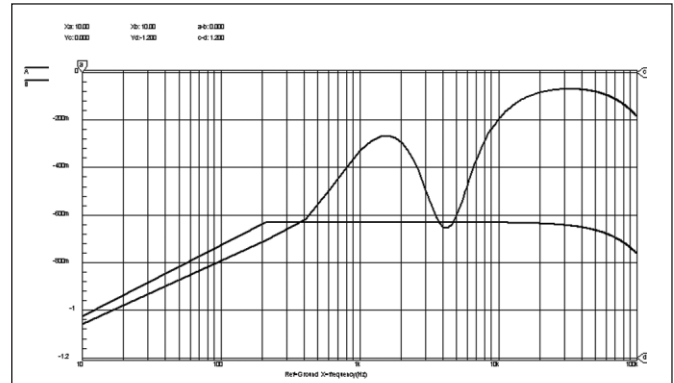


FIGURE 19: Frequency response, 8Ω resistor versus Monster 1190MC (tube).

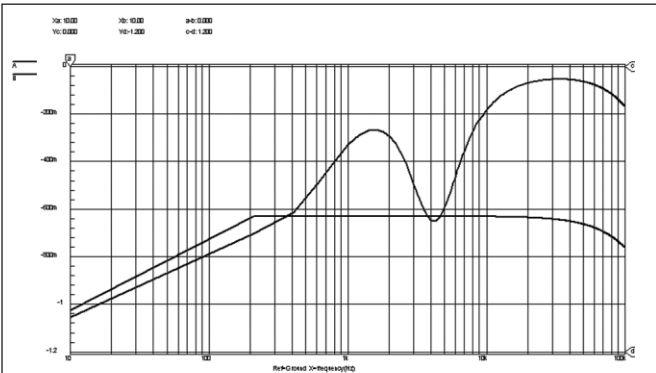


FIGURE 18: Frequency response, 8Ω resistor versus Supra 3.4/S (tube).

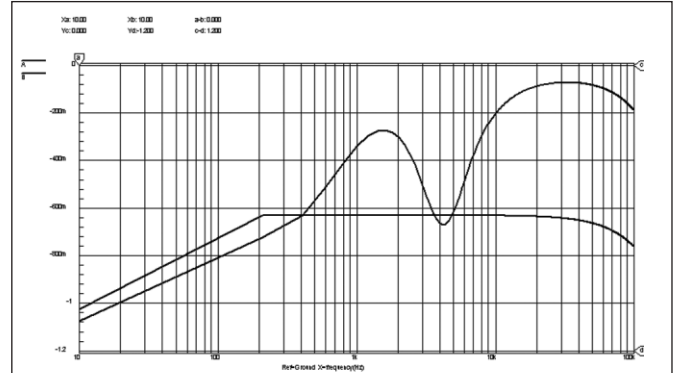


FIGURE 20: Frequency response, 8Ω resistor versus zip cord 16 (tube).

because of its higher dielectric constant and large variation of dielectric constant with frequency and temperature. The highly stable Teflon insulation should give the best electrical performance. All the cables have sufficient insulation thickness to withstand normal handling. ❖

*Manufacturer's response:*

We have found that it is hard to measure inductance in a short cable due to the inevitability of loops at the hook-up point. Also, because all cable interaction is relative to length, we would have proposed testing a more representative run of 10–15 ft. 3 ½ ft. is a very short speaker cable.

We were happy to see in print that "the capacitance of the flat cable should not cause instability in a well-designed solid-state amp." We share the conclusion that if it does, the problem lies with the amplifier, not the cable. Unfortunately a few designers still violate Nyquist's criteria on allowable amount of negative feedback. A good solid-state amp supply should not oscillate.

Ulrik Poulsen  
Alpha-Core, Inc.

First, my compliments on a technically well-carried-out and well-explained test, giv-

**REFERENCES**

1. In order to minimize the skin effect at high frequency, a special stranded wire called Litz wire is employed. Litz wire was designed to minimize the losses in high frequency, high current applications. Litz is an abbreviation for litzendraht, which is German for stranded-wire. Litz wire is composed of separately insulated strands of very fine wire. It is wound so that every strand occupies, to the same extent, every possible position in the cross section of the wire. It is this special construction and the insulated strands that differentiate Litz wire from conventionally stranded wire.

Litz stranding is designed to equalize the flux linkages, and therefore the inductive reactance, of each strand in the wire. This results in the current being distributed evenly among all the strands. Litz wire is typically designed for a specific frequency range. AWG–28 strands may be used for frequencies below 1kHz, while strands as small as AWG–48 are used for frequencies in the megahertz region. The goal of the Litz wire designer is to make the resistance and reactance equal at the design frequency in order to maximize the Q of the cable. Sufficient strands of the selected size are then used to carry the maximum design current.

2. J. Atkinson, "Real-Life Measurements", *Stereophile*, August 1995, Figs. 1, 2. The full text of the original article can be found at [www.stereophile.com/showarchives.cgi?60](http://www.stereophile.com/showarchives.cgi?60).

3. S. Reynold, "Vacuum-Tube Models for SPICE Simulations," *Glass Audio*, Vol. 5, No. 4, 1993.

4. LTSpice and vacuum tube models, [www.duncanamps.com/technical/ltspace.html](http://www.duncanamps.com/technical/ltspace.html).

ing a scientific impression.

Supra Ply is of a sandwich design for low inductance, and we know that even a lower inductance can be achieved with the ribbon design. In fact, we used aluminum tape, flat to flat, for conductors for the measurements of the Ply design concept during the R & D. However, once the theory of low inductance = low transient loss was confirmed, we began working on a user friendly design, which also was a compromise regarding the capacitance not to be too high to risk oscillations in sensitive amplifiers. Furthermore, as we have our own in-house production (different from most produced in China), we made a production friendly solution to ensure value for the money.

The final result was the braided flat conductors of Supra Ply. That was in 1993 when "high-end" speaker cables still were of wide-spaced design. Supra was first with speaker cables in 1976 and first with low-inductance design in 1993.

Tommy Jenving  
President  
Supra

**SOURCES**

Alpha-Core, Inc.  
915 Pembroke Street  
Bridgeport, CT 06608  
(800) 836-5920, (203) 335-6805  
FAX (203) 384-8120  
e-mail: [sales@alphacore.com](mailto:sales@alphacore.com)  
Goertz MI-2 MSRP \$21.50/ft pair single, \$43.00/ft pair bi-wire.

Terminations: Rhodium spades/banana plugs/pins \$48 single, \$63 bi-wire. Silver spades \$58 single, \$85 bi-wire.

Kimber Kable  
2752 South 1900 West  
Ogden, UT 84401  
(801) 625-5530  
e-mail: [info@kimber.com](mailto:info@kimber.com)  
Kimber 8TC MSRP \$420/pair with angled WBT 0645S banana plugs  
Terminations: PostMaster spades, WBT straight or angled bananas

Supra Cables/Jenving Technology AB  
Bastbacka 112-113  
S-459 91 Jlungskile, Sweden  
+46 (0)522-698990  
e-mail: [supra@jenving.se](mailto:supra@jenving.se)  
Supra Ply 3.4/S \$180 2 x 8' with spades  
U.S. distributor: Tonian Labs,  
[www.tonianlabs.com](http://www.tonianlabs.com)

Monster Cable Products  
455 Valley Drive  
Brisbane, CA 94005  
(415) 840-2000  
e-mail: [webmaster@monstercable.com](mailto:webmaster@monstercable.com)  
Monster 1190MC \$1.25/ft without terminations

*Jupiter*  
CONDENSER CO.

COTTON CABLE

*Jupiter*  
CONDENSER CO.

BEESWAX-PAPER-FOIL  
CAPACITORS

[www.jupitercondenser.com](http://www.jupitercondenser.com)  
330-342-9590

**Lundahl Transformers in the U.S.**

**K&K Audio** is now selling the **premier European audio transformers** in the U.S.

**High quality C-core transformers and chokes using silicon iron, mumetal, and amorphous cores.**

- Power output transformers – SE or PP
- Interstage transformers – SE or PP
- Line output transformers – SE, PP, and parallel feed
- Input transformers – MC or line
- Audio chokes
- Power transformers
- Power supply chokes

**High End Audio Kits using Lundahl Transformers**

- MC Phono Step-up Unit
- Phono Preamplifier
- Line Stage Preamplifier
- Microphone Preamplifier

**For more information on our products and services please contact us at:**

[www.kandkaudio.com](http://www.kandkaudio.com)  
[info@kandkaudio.com](mailto:info@kandkaudio.com) voice/fax 919 387-0911

# SPEAKER CABLE LISTENING TESTS

By Muse Kastanovich

Cable is the purist-audiophile's favorite tool for manipulating the frequency balance and other qualities of his/her system. Active equalizers/tone controls are just not transparent-sounding enough for many listeners to be considered as part of a high-quality system. What is left to balance the response and sound of the system in the audiophile's listening room is choice of components, especially cables, which are less expensive than components, and so are easier to switch when you need a change. Cables interact with components to at least some degree, so their sound is always context-sensitive, which is why most outlets allow you to audition them with your own equipment.

For this review I first listened to a selection of high-end cables from the US company Kimber and the Supra company out of Sweden. Both are well-established, reputable audio companies. A comparative study lets you test many different qualities in different models, and also allows the ear to hone in on the exact characteristic sound of individual favorites.

## LISTENING TEST

I listened to the Supra Ply 3.4/S in comparison with my reference Goertz MI 2 Veracity 3' biwire pair. The Supra's treble was just a little grainy, and its transients were a touch rolled off. The midrange and lower treble were more prominent, and the bass sounded rich but a little flabby. The soundstage was more vague than that of the Goertz, and reverb was not as pleasantly noticeable. Overall, the Supra was darker and less involving.

After changing back to the Goertz for more reference listening, I then switched to the Kimber 8TC speaker cables. The Kimber's midrange was a bit less meaty, but the bass was more solid. Dynamics sounded equally good, though transients were not quite as coherent. The soundstage was very vivid, with good depth but not quite as much width. The top octave was not as present nor as clean as with the Goertz, but the treble was more prominent.

## WRAP-UP

I found the Supra Ply 3.4/S was not the best match for my system. It sounded too veiled and soft for me to recommend it as a competitor to the others. However, it is more affordable than the others and may be a decent choice at entry-level. All of the Supra cables have a pastel "ice blue" color jacket that is absolutely delicious to the eye. It's unfortunate that they were not as delicious to my ears, because I really wanted to like them.

I found the Kimber 8TC, which has been available for many years, to still be a good choice in its price range. Its very dynamic, alive, solid sound made me quite happy when I used it to connect my 804s. It is positioned in a medium price range, and you would be hard-pressed to find a better overall value. I recommend taking a listen to this speaker cable, which should match well with many different systems.

## UPGRADE

For about three years, I have been using a bi-wire pair of Goertz MI-2 flat speaker cables, made by Alpha-Core, as the reference wires in my system. So you might imagine I was excited when I heard some months back that they had introduced a new Teflon insulated version called the T-series.

My long-term reference cables are an unterminated (bare-wire ends), 3.5' long, bi-wire pair of Goertz MI-2 Veracity, insulated with a mix of Teflon and polyester terephthalate. Each pair of flat OFC copper foils is sandwiched together to make a ribbon about 3/4" wide and only about 1/16" thick, and has the same conductor cross-section as 10 AWG wire. Of course, there are two ribbons per speaker in a bi-wire setup like mine, though only one is needed per speaker in a normal setup.

The new Goertz MI-2 T-series (\$136) cables reviewed here are

identical to the older version, except that they are 3' long and have only pure Teflon insulation around them. They are also terminated with what Goertz calls integral spaces, though this is not an important difference because the spades are made from the bare copper foil of the wire, meaning they are actually unterminated like my older pair.

## TEST SETUP

My system consisted of a Rotel RDD-980 CD transport and Assemblage DAC-3 D/A processor connected with a Sound & Video Digi-flex Plus BNC cable. Analog interconnects were Kimber Hero unbalanced. Amplification was provided by my home-built STAMINA single-ended MOSFET integrated monoblock amps (based on the Pass Zen/Bride of Zen circuits, output impedance 0.8Ω). Speakers were my modified pair of B&W Matrix 804 (nominal impedance 8Ω, minimum 4Ω).

Alpha-Core included a pair of free R/C Match Links to prevent oscillation in certain amplifiers when using their high capacitance cables. I did not need these with my amps because the ultra simple Zen is rock stable into any impedance.

## LISTENING IMPRESSIONS

The new Goertz T-series MI-2 wires appear identical to my old favorites, except for the color of the translucent insulating jacket. A change of insulating dielectric material can theoretically change the sound, considering that a good portion of the electromagnetic signal travels on the surface of the wire at audio frequencies. Indeed, I was pleasantly surprised by the improvements that greeted me when switching from my old MI-2 cables.

Listening to "Achtung Baby" by U2, I noted the T-series had a slightly brighter sound, and was a little crisper and clearer sounding. Transients sounded a little faster, and there seemed to be a greater number of different layers of sound apparent. Its soundstage was slightly wider, and images were a bit more vivid. The midrange was just a touch recessed, and the bass was deeper. Overall, I preferred the faster, more dynamic sound of the new T-series.

## ASSESSMENT

I very much enjoyed my time with the Goertz MI-2 Veracity T-series flat speaker cables. I found them to be very detailed, transparent, and dynamic sounding. I highly value these main qualities, which make a system sound closer to live music.

I am purchasing the new T-series review samples, which I will use as my new reference. My old reference Goertz wire seemed just too uninvolved after becoming accustomed to what the new ones could do for the music. This is not to say that the "standard version" Goertz wire is no good (it is still being manufactured); on the contrary I still recommend it, but only for systems that are too bright and need a very mellow-sounding wire. For everyone else, the T-series represents a more involving choice that will keep the excitement level high.

## RESPONSE:

*We are disappointed that Muse Kastanovich didn't find the Supra speaker cable to work as needed in his system. In my experience with B&W speakers, while wonderful sounding, they tend to be rolled off on top and wanting more power than less. The Zen amplifier is a respected amplifier, but along with its minimalistic design, the power, in my experience, is less than desirable for that speaker. If the Alpha-Goertz cables are a little brighter on top, that would explain their more desired results in Mr. Kastanovich's review, and given the Supra's flatter response, a less desired result. As with many things in audio, system matching plays a key, and insufficiently acknowledged, role in listening satisfaction.*

*Tony Minasian  
Tonian Labs  
U.S. Distributor (Supra)*



# XpressMail

## ROBERT OAKES JORDAN



Robert Oakes Jordan

The audio world missed the passing of one of its pioneers by several years. I only recently found out that Robert Oakes Jordan passed away in July 1998 during heart surgery. It is not too late to mention some of the accomplishments of Robert Oakes Jordan and Associates.

Bob and James C. Cunningham were the directors of Robert Oakes Jordan and Associates. Jim, a former NBC Radio engineer, is still quite active in the audio world. In the early 1950s, Bob and Jim wrote many technical articles on stereophonic recording techniques in *Audio (Engineering)* magazine and other journals. Their book, *The Sound Of High Fidelity* (Windsor Press), still holds up technically and is a great nostalgia trip.

References to Robert Oakes Jordan and Associates are found in the cover notes of many old LP records and pre-recorded tapes. In the early 1950s, stereophonic sound was just beginning to become practical. In those days, the audiophile buzzword was "high fidelity." The concepts of direction and motion were new and unknown. Robert Oakes Jordan and Associates produced most of the stereo demonstration records for the then new medium of stereo.

Robert Oakes Jordan and Associates set about recording just about any imaginable sound, building the first stereophonic sound-effects library. These recordings were utilized in stereophonic sound demonstrations for

most of the record companies moving into that medium. Their biggest hit was "Sound In The Round," narrated by NBC announcer Tom Mercein.

Sound In The Round was almost universally used to demonstrate both tape-delivered stereo and the later, LP-delivered stereo. As it began with the sounds of a ping-pong game, they probably are responsible for the phrase "ping-pong stereo." Among the companies they produced stereo demos for were Ampex, RCA, Concert-Disc, Allied Radio, and OmegaTape.

Robert Oakes Jordan and Associates also shows up on a number of music record cover notes as consultants for engineering and recording. Bob once told me that in the early 1950s they assisted John Pfeiffer and RCA engineers for recording in Chicago's Orchestra Hall for RCA's first recordings there.

In later years Bob operated a small home-based technical school for young people in his town of Highland Park, Ill. It was sort of a "Mr. Wizard" TV show come home. Young people obtained hands-on technical training in everything from electronics to ceramics.

Mike Stosich  
Esoteric Sound/Rek-O-Kut  
EsotericTT@aol.com

### IONOFANE FIX

Thanks for your very interesting article about the Ionovac in the August issue ("Care and Maintenance of DuKane Ionovac Tweeters," p. 50).

I recently bought an Ionofane 601. It's not working at the moment because of some fault in the power supply that I haven't been able to track down. The electrode is rather worn and blunt—like the one in Photo 9 of your article.

What are the options for electrode replacement for Ionovac owners? Are they available anywhere in the world? Is anyone still making them? Do you know the names of the alloys that were used in the original electrodes?

Jonathan Cook  
brahms1888@yahoo.com

## JFETS

ULTRA LOW NOISE

LS843 - 3nV/Hz typ

TIGHT MATCHING

LS843 - 1 mV max

- ◆ N & P Channel
- ◆ Duals & Singles
- ◆ Custom Screening
- ◆ Spice Model Library
- ◆ Die, SMT, Thru-Hole
- ◆ No Order Minimum

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

**LINEAR SYSTEMS**

4042 Clipper Court  
Fremont, CA 94538

510-490-9160/510-353-0261 (Fax)

E-mail: Sales@Linearsystems.com

WWW.LINEARSYSTEMS.COM

## World-Class Audio Discount Prices



[www.hagtech.com](http://www.hagtech.com)

www.audiokits.com

## Build Better Audio

Distributing select designs of



Celebrating 20 Years of Audio Excellence

### All-FET DAC Class A Headphone Amp

Visit us online at



We accept MasterCard, Visa, Discover and American Express.

## SUNRISE

Faithful Connection  
Sunrise Transformers  
www.us2sunrise.com



Sunrise E.&E., Inc  
tel: 909-598-9136 FAX: 909-468-0307

Daniel Schoo responds:

I have not seen an Ionofane speaker in person—only photographs of them. According to Roger Russell on his Ionofane history web page, the Ionofane is essentially a copy of the Ionovac, which preceded the Ionofane by several years. I can't guarantee that the DuKane cell will fit the Fane speaker, but the likelihood is very good.

There are a number of things you can check in the power supply if the speaker is nonfunctional. I would replace all of the electrolytic capacitors even if they seem to be good. Measure the supply voltages and compare them to the values on the Ionovac schematic. Try installing a known good tube and also don't overlook the oscillator cover interlock switch as a possible problem.

One option for electrode replacement is to check eBay for old stock DuKane cell kits. They show up infrequently and tend to rocket up in bid in the final seconds of the auction.

There is another option: Due to popular demand, new manufactured Ionovac electrodes are now available at [www.ionovac.com](http://www.ionovac.com). They also have cleaning kits with a detailed videotape tutorial on how to disassemble the speaker safely to clean or replace the cell. If the Ionovac electrode doesn't fit the Ionofane cell, you can return it unused for a refund.

The alloy DuKane used for electrodes was essentially type 416 stainless steel as determined by a metallurgical lab analysis on a DuKane electrode. It is reported that Telefunken used an alloy called Kanthal—which is from Kanthal AB of Sweden, a manufacturer of high-temperature metal alloys for heating elements and furnace parts. Like the term "stainless steel," Kanthal refers to a broad product line of high-temperature alloys, so it is unknown just which one was used as electrode stock.

### SERVO SUB

I very much enjoyed Daniel L. Ferguson's article "A Servo Dual Voice Coil Subwoofer" (Nov., p. 18).

Unlike previous similar projects I am aware of, he deals with the mutual induction of the voice-coils.

For example, "Roaring Subwoofer" by Russel Breden (published in *Electronics World*, February 1997), uses two 10" units; distortion at 15Hz is quoted as 2%, without mentioning the corresponding acoustic power. An interesting feature of Russel's design is that in-

stead of differentiating the coil voltage it integrates the incoming signal, "as there is no difference in system performance, either in amplitude or phase response, between differentiating the pick-up signal or integrating the output." This may be applicable to Daniel's design to avoid saturation problems with op amp E.

The second point concerns the current sensing method. Is it really necessary to go through a true differential scheme (op amp A), which could be avoided by connecting the 0.1Ω resistor at the ground side of the driver?

Finally, it would also be helpful for experimenters to know the gain of the power amplifier.

I hope this project will be continued. I suggest two different directions: an enclosure with a 15" driver (the Monacor\* SPH-390TC seems adequate) and, if the servo can be sufficiently bypassed at higher frequencies, a two-way very compact monitor with an 8" unit, which will then also handle the medium range.

Sébastien Veyrin-Forrer  
Saint Chartres  
France

\*Editor's note: Monacor products are not, to my knowledge, available in North America.

Daniel L. Ferguson responds:

Unfortunately, I did not have the benefit of reading "Roaring Subwoofer" prior to writing my initial article. I wish I had. Russel's observation about integrating the incoming signal makes perfect sense. The integral of acceleration is, in fact, velocity. If the sensor voice coil output is fed directly to the servo-summing junction, the system becomes a velocity servo instead of an acceleration servo.

I have experimented with this briefly, and, from what I can remember, stability was improved. I used a low-pass filter to flatten the system response, which acts somewhat like an integrator. However, I could never get the system accuracy obtained using the differentiator method, so I abandoned it. It didn't occur to me to integrate the incoming signal, and I will surely run some experiments on this.

The benefit I would expect is the ability to increase amplifier gain (and system accuracy), since the differentiator shifts the feedback signal 90°. This phase shift should be com-

pletely eliminated using Russel's approach.

I chose the differential amp for current sensing because, initially, I wasn't sure which way to connect the woofer. One direction produces positive feedback and uncontrolled oscillation, the other negative feedback and stability. In seconds, I can reverse the polarity on this part of the circuit by switching leads. It would appear that the configuration you propose could be made to work and thereby eliminate an op amp stage. However, one sure benefit of the differential amp is that it eliminates any DC signal components without resorting to capacitors and their inherent phase shifts, which your proposal does not.

I must add at this point that I'm having second thoughts about using the current sensor at all. The phase shift caused by the differentiator is the problem. The current sensing-circuit measures current ( $i$ ), not the rate of change of current ( $di/dt$ ). Therefore, this signal must be differentiated to mirror the system model.

In my latest experiments, I can obtain the most accurate low-frequency curve tracing without it. However, I do plan to continue to pursue a way to incorporate this, because it has the potential to provide the ultimate in accuracy and stability. The highest amplifier gain I have achieved to date is 10, and this is without current sensing.

I am planning a future project article with a very high-excursion 12" driver. It appears to be a good compromise between box size and output. At this point I have not tamed this beast enough to even consider anything

in the mid-bass frequency range. Current sensing will have to be perfected to operate in this range. Maybe some day.

Thanks for a very insightful letter. You have given me a number of things to consider for future experimentation.

### ACTIVE CROSSOVERS

I have been a long-time subscriber to *Speaker Builder*, *Audio Electronics*, and now *audioXpress* and wish to offer my congratulations on a great magazine. Also, to pass on a comment regarding active crossovers.

I built a three-way system several years ago—satellites with MTM and separate woofer, with monoblock MOSFET amps for each driver and the Butterworth crossover [your own article and design from some years back in *Speaker Builder*]. I neglected to use fuses in the power supplies of the crossovers and had a diode short out, probably due to dirty AC.

The secondary voltage from the crossover power-supply transformer went straight through to the amplifiers and fried the voice coils of each driver in the left channel. Sadly, the 2" sealed back version of the Philips dome midrange took a beating, and these are now out of production. I suggest that any readers using active crossovers might consider fuses!

If any readers know of a supplier for those domes, which can be repaired like a tweeter if I can obtain new

domes/voice coils, I'd appreciate hearing from them. Philips part # AD0211/Sq. [I think Sq stands for Squawker—British for midrange!]

David Mayfield  
maintech@acncanada.net

## DO YOU HAVE SURPLUS STOCK OF SPEAKERS?

- US & European drivers & tweeters preferred
- Quantities from 500 to large quantities
- Prompt payment
- Contact us with details



Electus Distribution  
Sydney, Australia

email:

mreynolds@electusdistribution.com.au

Fax: 61 2 9741 8500

www.electusdistribution.com.au

# ELECTUS DISTRIBUTION


# thetubestore.com

Your online source for name brand audio tubes

- Over 1000 types available online
- Perfect Pair matched power tubes
- Capacitors and sockets

Order online at [thetubestore.com](http://thetubestore.com)

or call toll free **1-877-570-0979**

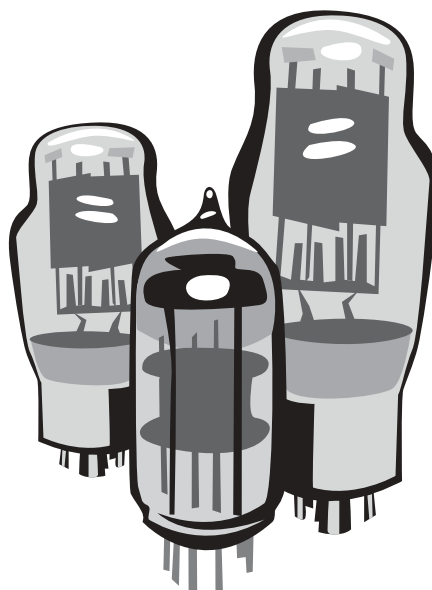




## Quad: The Closest Approach

by Ken Kessler

This much-awaited publication is the life story of Quad, a company started by Peter Walker, who passed away months after the book hit the shelves. Kessler captures the history of Quad through interviews (particularly with Ross Walker and Stan Curtis), reprinted material, and contributions from other industry writers. As a writer for *Hi-Fi News* and *Inside Hi-Fi & A/V*, Kessler takes you through the better part of the 20th Century where the development of high-quality reproduced sound forever changed the audio industry. And although this book contains the history of Quad itself, Peter Walker can now live on through its readers. 2003, 240pp., 12" x 12", hardbound, ISBN 0-9545742-0-6. Sh. wt: 5 lbs.

**BKIA1**

**\$79.99**

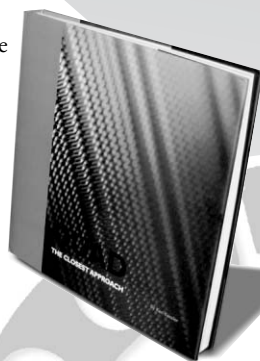

## Paul Wilbur Klipsch: The Life... The Legend

by Maureen Barrett and Michael Klementovich

In the only authorized biography of Klipsch to date, Barrett and Klementovich take you through the lifelong journey of Paul Wilbur Klipsch. Ranging from his experience in World War II to the conception and creation of Klipschorns, to being given the Engineering and Science Hall of Fame Award, you are sure to enjoy living Klipsch's life again in this wonderful rendition. Includes three full photo galleries and diagrams of all twenty-three of Klipsch's patents. 2003, 208 pp., 6 1/4" x 9 1/4", hardbound, ISBN 1-58244-226-6. Sh. wt: 2 lbs.



**BKPW1**

**\$24.95**


## Ribbon Loudspeakers

by Justus V. Verhagen

The first book dedicated to these great-sounding speakers. The author favors ribbons, especially for use at mid- and high-frequencies. They are inexpensive and can be easily constructed with a minimum of tools. The book presents the theory and history of ribbon speakers and includes construction details for building your own ribbon loudspeakers. An extensive resource section is included along with a detailed listing of ribbon loudspeaker patents. 2003, 79pp., 8 1/2" x 11", softbound, ISBN 1-882580-44-3. Sh. wt: 2 lbs.

**BKAA65**

**\$24.95**

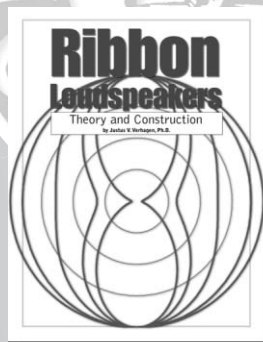

## Premium Home Theater

Design & Construction  
by Earl Geddes

Describes the ins and outs of designing and building a top notch home theater. Written for those familiar with audio and video, but without formal training, *Premium Home Theater* covers all aspects of the subject including topics like—using a PC as a control center; using a low cost PC projector as the video source; designing a small room with the right acoustics; noise control; and more. Contains all the information you need to assemble an unparalleled home theater experience. 2002, 266pp., 7 1/2" x 9", softbound, ISBN 0-9722085-1-8. Sh. wt: 2 lbs.

**BKGL2**

**\$39.95**



Old Colony assumes no responsibility for errors or omissions.

## COMING IN 2004! Speaker Building 201

by Ray Alden

Watch for announcements of this great new book by the author of *Advanced Speaker Designs*. Includes eleven all-new speaker system projects. Pre-publication pricing of \$29.95. Check out [www.audioXpress.com](http://www.audioXpress.com) or *audioXpress* magazine for details!

To order any of these new titles or check out the rest of our books, visit [www.audioXpress.com](http://www.audioXpress.com) or call 1-888-924-9465!

Old Colony Sound Laboratory,  
PO Box 876, Peterborough, NH  
03458-0876 USA  
Toll-free: 888-924-9465  
Phone: 603-924-9464  
Fax: 603-924-9467  
E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)  
[www.audioXpress.com](http://www.audioXpress.com)

## CANTO SIRENA

I enjoyed James Lin's analysis of the differential phono stage in January *audioXpress* ("Canto Sirena, Part 1," p. 32). I built one myself a few years ago, also partly inspired by J.C. Morrison's Siren Song design in *Sound Practices*. I had also read Alan Wright's book.

My design was different in some regards; tubes were 5965 to 6SL7 to 5687 as output. The input stage was cap-coupled to the second stage with low-frequency rolloff below 20Hz. Also, I put the 75 $\mu$ s network first, and the 3180 and 318 $\mu$ s networks were integrated into a direct-coupled cathode-follower output stage formed between the 6SL7 and the 5687.

What I found over time were some odd musical whistlings and phase shifts. These went away when I put a dummy load on the side of the second differential stage that doesn't drive the output tube. This actually balanced that stage and things became more stable and coherent.

James' design may be less troubled by this than mine was due to the less demanding load of the 75 $\mu$ s circuit in this position. Unlike James and J.C., I also made balanced cables from my turntable to my input and therefore had an actual connection to each grid of the input tube from the phono cartridge.

I split the 47k $\Omega$  input load into two 23k $\Omega$  grid resistors on the 5965 input tube. By the way, the 5965 is an excellent low-noise and low-distortion tube for audio with ultra pure nickel in the cathode for computer applications in days of yore. It is very similar in bias conditions to a 12AT7, but slightly lower mu, and has the same base as the 12AX7, 12AT7, 12AU7, and so on. Good luck to all.

John Day  
Austin, Tex.

James Lin responds:

I read Mr. Day's letter with great interest. It sounds as though his design topology differs from mine in that the output stage is a cathode follower rather than a common cathode. In addition, two of the three tubes are different, and the one tube that is common to both—the 6SL7—is used in the second stage instead of the first.

Just from his brief description, there are a number of points of interest. First, the choice of the 5965 input tube. This tube has been used as the third tube in some Conrad-Johnson phono preamps, but is relatively uncommon in audio designs. According to Ludwell Sibley's Tube Lore, it is a computer-rated version of the 12AV7, although the RCA tube manual specifications for the two are somewhat different. From Mr. Day's description, it sounds as though it deserves a wider audience.

Compared to the 6SL7, the 5965 has somewhat lower gain (amplification factor of 47 versus 70), but four-fold higher transconductance, which should mean 6dB less noise—an important consideration for a phono input stage. Its plate resistance is also much lower, about the same as the 6SN7 used in my second stage diff amp.

In a split passive RIAA equalization scheme such as used in my design or Mr. Day's, the best equalization stability is achieved by having the higher impedance 318 and 3180 $\mu$ s network following the higher plate resistance tube, and the lower impedance 75 $\mu$ s network following the lower plate resistance tube. In my design the high plate resistance 6SL7 was the input tube, thus the 318 and 3180 $\mu$ s network came first, whereas in his design the lower plate resistance 5965 is the input stage tube, so the 75 $\mu$ s network should be first, as he has done.

A cathode-follower output has the advantage of lower output impedance, which should make his design less sensitive to choice of output cable. The 5687 tube Mr. Day uses is a medium mu dual triode with about the same low distortion as the 6SN7, but a plate resistance less than half of the 6SN7. It has been used in a number of designs from Audio Note, including some of the most expensive amps ever sold.

The trade-off with a cathode-follower output is lower gain. I would guess that Mr. Day's design is closer to 35–40dB at 1kHz versus 49dB for my design, which is still adequate for moving magnet cartridges. On the other hand, one of my goals was a higher gain to give an output closer to that from my other sources. Of course, the cheapest solution would have been to pad down my other sources at the preamp inputs, but what fun is that?

The use of relatively unfamiliar tubes for audio certainly makes things more interesting. Maybe we'll even find that some of them make better music than the 12AX7 and 6DJ8 tubes we are used to hearing, and

## Electronic Crossovers

Tube

Solid State

## Passive Crossovers

Line level

Speaker level

## Custom Solutions

We can customize our crossovers to your specific needs. We can add notch filters, baffle step compensation, etc....

All available as kit

Free Catalog:

Marchand Electronics Inc.

PO Box 18099

Rochester, NY 14618

Phone (585) 423 0462

FAX (585) 423 9375

info@marchandelec.com

www.marchandelec.com

# auricap



**World's finest capacitor,  
Sonically transparent,  
Superior technical  
specifications.**

- Auricap is the best I have tried by a long, long way.  
Kendrick Pavey/VP Melbourne Audio Club
- Auricaps are great parts, and represent a significant step forward in capacitor technology and audio-musical performance... Better and cheaper. What more can you ask for?  
Jennifer White-Wolf Crock, Sr. Technical Editor - Positive Feedback Magazine
- If you want absolute transparency, then you must give Auricaps a try.  
Giorgio Pozzoli/TINTAudio.com

OEM & dealer inquiries invited.  
Call (800) 565-4390

www.audience-av.com



The audio engineer's hands-on X-over design & speaker voicing tool.

**ATTENTION!**  
Audio professionals, hobbyists, installers and University students/professors.

**The Virtual Crossover BOX™**  
MODEL VCB-100

by **W** Vidsonix  
Audio • Industry



Shipping Wt: 7 lbs.  
K-VCB100 \$249.95

Now includes our exclusive Crossover Design Pocket Slide Tool!

Old Colony Sound Laboratory  
PO Box 876, Dept. LIS2  
Peterborough, NH 03458-0876 USA  
888-924-9465 Fax: 603-924-9467  
E-mail: custserv@audioXpress.com

Call 1-888-924-9465 today or order on-line at [www.audioXpress.com](http://www.audioXpress.com)!




We also design and manufacture home theater, marine, and professional loudspeakers and accessories. Individual drivers, including all Thiele-Small parameters, are also available on our website.

**Vidsonix Design Works**  
28415 Industry Dr. #513, Valencia, CA 91355  
(661)775-2760  
More info at: [www.VIDSONIX.com](http://www.VIDSONIX.com)  
©2004 VIDSONIX. All Rights Reserved

wouldn't that be great?

Incidentally, there is one error in his letter: although I used phono connector inputs, the ground side of the connector is isolated from both chassis and circuit ground—it may not look balanced, but electrically it is. I have balanced cables from my turntable, so the cartridge is directly connected to both grids of the input tube. Morrison shows both balanced and unbalanced connections in his schematic. My schematic shows a balanced connection and the text comments on changes to be made for an unbalanced connection.

In any case, his design sounds very interesting, and I strongly encourage Mr. Day to write it up for publication in audioXpress.

### CAR SPEAKERS

I am searching for speakers, but I am not sure about what size I need for my car, a 1997 Saturn, SC2 Coupe. I cannot figure out what size speakers I need. I looked at the speakers, but they have no markings. Can you please help me?

Richard Abston  
richard.abston@navy.mil

Crutchfield can help you. . . —ETD


### ODE TO A MENTOR

When I moved from New York City down to Florida, I went a year becoming acclimated to a new job and surroundings. I continued reading my hi-fi magazines, but eventually I became lonely for audio DIY friends and longed to meet kindred spirits to talk shop and compare notes with.

It occurred to me that there must be other *Speaker Builder/Audio Amateur* subscribers in my area, so I placed an ad in both magazines inquiring as to whether there were any other like-minded souls out there with whom I could communicate. I received several responses but nothing panned out immediately. I then heard from a fellow by the name of Matt Hamilton. I now consider this to be one of the luckiest days of my life.

As it turned out, Matt is a retired digital electronics engineer who, like me, enjoys tinkering with audio electronics and speakers. And he lives only one mile away from me! We met, became good friends, and have spent many an afternoon together in his garage working on one audio/speaker project or another. Our relationship has been one of teacher/student, with Matt as mentor
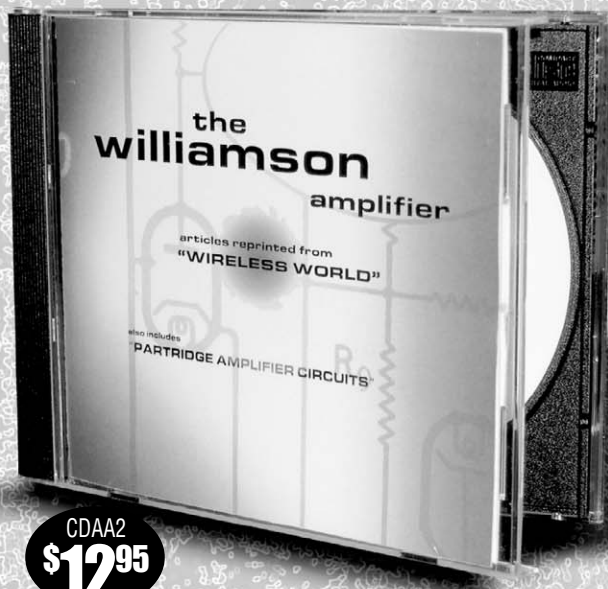
## Now Available on CD From Old Colony Sound Laboratory



### The Williamson Amplifier on CD with Partridge Amplifier Designs

The original booklet (BKAA6) on this famous amplifier has been saved in Adobe Acrobat PDF format along with a 28-page collection of amplifier designs from the Partridge Transformer Company. The "Williamson," long setting the standard for amplifier design and performance, was originally published as a series of articles in *Wireless World*. This collection of articles reproduced by special arrangement is a single resource and important historical document

of D.T.N. Williamson's important work.

Includes more than 40 detailed illustrations, parts lists, and complete construction details. The Partridge collection features 8 amplifier designs and notes on construction. 2004, CD. Sh. wt: 1 lb.

CDAA2

**\$12<sup>95</sup>**

To order call 1-888-924-9465  
or order on-line at [www.audioXpress.com](http://www.audioXpress.com)

Old Colony Sound Laboratory, P.O. Box 876  
Peterborough, NH 03458-0876 USA  
Toll-Free: 888-924-9465 • Phone: 603-924-9464  
Fax: 603-924-9467 • [www.audioXpress.com](http://www.audioXpress.com)  
E-mail: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)





and myself as protégé for the last ten years.

There is so much that I have learned from Matt over the years, so much that I am grateful to him for. He has always been patient, available, and very giving, willing to share his time with me, always ready to answer another one of my curious questions, always ready to go to the blackboard to draw formulas and diagrams in order to help me better understand a subject.

The topic du jour has not been limited to speakers or audio either: Matt is a walking compendium of wide-ranging knowledge in just about any field you can imagine. Needless to say, whenever I have needed help with anything, from broken doorbells to broken swimming pool pumps and anything else you can dream up, he has always been there to answer my questions and lend a hand and pass his knowledge on to me.

The day I met Matt Hamilton was truly a blessed day. Thanks, Matt, for being my friend.

Angel Luis Rivera  
Angel.Rivera@med.va.gov

## MULTITONE TESTING

I enjoyed reading Richard Crawford's article entitled "A 1 PPM IM Distortion Analyzer" in the March 2004 issue (p. 8). This is the kind of article I love to see, and believe it is of great value to the DIY community.

It turns out that the three-tone test that Richard presents, using frequencies of 9.6, 10.4, and 20kHz, is actually the Multitone Intermodulation (MIM) test I originated and presented at the AES convention in November 1979, and subsequently published in the JAES in September 1981. My original test employed frequencies of 9.0, 10.05, and 20kHz to produce IM products at 950 and 1050Hz. I'm flattered that Richard independently came up with virtually the same idea 25 years later!

Richard's measurement floor of somewhat less than 0.0001% is very impressive, and bests my floor of about 0.0002%. Of course, my design was somewhat simpler and used older technology. It used three single op amp Wein Bridge sinewave oscillators for the generator. The analyzer used two third-order 2kHz Butterworth low-pass

filters and a fourth-order 1kHz band-pass filter for the analyzer. Rejection of the test frequencies was more than adequate, as my measurement floor was also dominated by noise.

My MIM measurements tracked THD-20 quite well for a variety of devices, including a power amplifier, with MIM generally lying about 20dB below THD-20. As Richard pointed out, the MIM test is especially important nowadays with digital equipment, where a test whose stimulus and response are both in-band is a necessity.

Bob Cordell  
Holmdel, N.J.

*Richard Crawford responds:*

*My thanks to Mr. Cordell. His original development of the three-tone intermodulation test (MIM) is noteworthy. I recommend the JAES article he mentions, not only for the three-tone test he describes, but also for his discussion of other tests which measure intermodulation. His comparisons of three-tone intermodulation tests and THD-20 (total harmonic distortion at 20kHz) are similar to my own comparisons. A small difference between his instrumentation and mine is that I include a two-tone test to measure third-order nonlinearities.*

## J-LOW HORN DESIGN

The article by Pass and Kruse on building a single driver loudspeaker is very interesting ("The J-Low Project," Feb. '04 aX). However, have they considered transient response effects of a horn that is unloaded on one side? It takes a few cycles for the loading effect of a horn to take effect. In order to keep driver excursion under control for this brief interval, horn designs usually include a small enclosure on the backside of the driver.

Without this loading, the J-Low driver could potentially have extreme transient distortion with cone excursion periodically reaching its physical limits.

Larry Brooks  
larrymb@comcast.net

*Nelson Pass responds:*

*The J-Low horn does have a small enclosure on the backside.* ♦

## Ready, willing and Avel



*offering an extensive  
range of ready-to-go  
toroidal transformers  
to please the ear, but won't  
take you for a ride.*

 **Avel Lindberg Inc.**  
47 South End Plaza  
New Milford, CT 06776  
tel: 860-355-4711  
fax: 860-354-8597  
[www.avellindberg.com](http://www.avellindberg.com)



**ELECTRA-PRINT  
AUDIO CO.**

### S.E. OUTPUT TRANSFORMERS

- \*Primaries to 10K
  - \*Power up to 100 watts
  - \*-1db 18hz to 40khz typical
  - \*Custom designs available
- PUSH-PULL OUTPUTS**

- \*Built for triodes
  - \*Single output to load
- INTERSTAGE TRANSFORMERS**

- \*Full bandwidth, up to 60ma
  - \*Single plate to P-P grids
- LINE OUTPUTS**

- \*Full bandwidth, up to 60ma
- POWER TRANSFORMERS**

- \*Custom built to your requirements
  - \*Power supply design advice
- CHOKES/FILTER and AUDIO**
- \*Standard and custom HV filter chokes
  - \*High current filament chokes
  - \*High inductance audio plate chokes

*specification and pricing catalog available  
Visa, MC and Amex*

**ELECTRA-PRINT AUDIO CO.**  
4117 ROXANNE DR., LAS VEGAS, NV 89108  
702-396-4909 FAX 702-396-4910  
EMAIL [electaudio@aol.com](mailto:electaudio@aol.com)

# Classifieds

## VENDORS

**AUDIOCLASSICS.com** Buys-Sells-Trades-Repairs McIntosh, B&W, Krell, Klipsch, Tannoy, C.J, VPI, Sunfire, Marantz, Levinson, Lexicon & more. **800-321-2834.**

**Principles of Power**, tube audio books, kits, FAQ [www.londonpower.com](http://www.londonpower.com)

**WWW.AUDIOELECTRONICSUPPLY.COM**—We are your supply source for all electronic parts—tubes, transformers, capacitors, poten-

tiometers, connectors, and so on, as well as DIY kits and assembled products. Call **(919) 355-0014** or e-mail us at [info@audioelectronicsupply.com](mailto:info@audioelectronicsupply.com).

These CONCRETE CABINET loudspeakers are a rock-solid Sonic revelation, What HiFi. Buy or build, [www.faradaysound.co.uk](http://www.faradaysound.co.uk)

**2004: OUR 20TH ANNIVERSARY!**

[www.borbelyaudio.com](http://www.borbelyaudio.com)

Borbely Audio kits in USA:

[www.audiokits.com](http://www.audiokits.com)

Borbely Audio kits in Japan:

<http://homepage3.nifty.com/sk-audio/>

**JENA LABS**

Our websites are our information centers for interconnects and cables, AC power solutions, DIY and OEMparts, Immersion Cryo services, and dealer list. [jenalabs.com](http://jenalabs.com) [jenatek.com](http://jenatek.com)

**Rockler Woodworking & Hardware**

Innovative solutions for all your speaker building needs

[www.rockler.com](http://www.rockler.com)

**1-800-403-9736 Free Catalog**

Mic and phono preamps, meters, filters, etc. all US built. **TDL Technology, Inc.**, **505-382-3173**, [www.zianet.com/tld](http://www.zianet.com/tld)



All types of audio tubes. 300B 6DJ8 ECC81 ECC83 KT88 Mullard GEC Sylvania. Discount for large quantity. Billington UK. Tel (0)1403 784961. Fax (0)1403 783519. Email/website [www.bel-tubes.co.uk](http://www.bel-tubes.co.uk)



*FOR THE PUREST*

See our color ad on the front inside cover.

For more information on our Patents and Technologies visit [www.soundstringcable.com](http://www.soundstringcable.com)

[www.southwestelectronics.com](http://www.southwestelectronics.com)

Tubes & Transformers  
Guitar Amp & parts



**gear racks, media drawers and more**

Factory direct since 1984

Free brochure (mention audioXpress)

Per Madsen Design (800) 821-4883

[www.rackittm.com](http://www.rackittm.com)

### Eliminate Vibration Noise Distortion

Changing the Resonant Frequency of the System Will Reduce Undesired Noise that can color sound!


Mass Load and Absorb Top Cabinet Vibration

Gels around small objects and rough surfaces

KTS AIPs Couple and Isolate

Specific Damping 74% Absorption over 60%

Stand, Console Shelves or Support

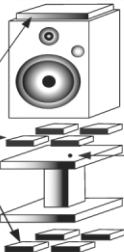

Secures Cabinets/Components to Wood Tile Metal Non-Toxic, Non-Destructive Removable [www.kleintechsys.com](http://www.kleintechsys.com) P. 561-969-2298 email: [support@kleintechsys.com](mailto:support@kleintechsys.com)



**Precision Port™**  
Be Different - Sound Better

CLEANER SOUND  
LESS DISTORTION  
EASY INSTALLATION  
GREATER SOUND PRESSURE LEVELS  
DESIGNED AND MADE IN THE USA

**Precision Sound Products, Inc.**

Phone: 815-599-0662

Fax: 309-279-0359

[www.psp-inc.com](http://www.psp-inc.com)

**TUBES WITH CLASS**

36D Perfect Playback Amplifier

[www.vasgold.com](http://www.vasgold.com)

see our ad in this issue



**Welborne Labs**

The largest selection of tubes, audio kits, and parts.

It's all online at

<http://www.welbornelabs.com>

**SPEAKERBITS**

Foam, cloth and rubber surrounds, spiders, cones, dustcaps, horn diaphragms, world's best voice coils & braid wire. Genuine foam surrounds for Dynaudio, Tannoy, Scan-Speak & more.

Dealers welcome - email for your user ID to access trade prices. We ship worldwide.

[www.speakerbits.com](http://www.speakerbits.com)

**Chassis & Enclosures**

Audiophile Quality



**YAEGER AUDIO**

Breaking Sound Barriers

•[www.yaegeraudio.com](http://www.yaegeraudio.com)•

**ALL ELECTRONICS CORPORATION**

Electronic and Electro-mechanical Devices, Parts and Supplies. Many unique items.

[www.allelectronics.com](http://www.allelectronics.com)

Free 96 page catalog

1-800-826-5432

# Yard Sale

## FOR SALE

Two Orion 225HCCA competition amps/crossover—these car amplifiers are \$175 each or \$300 for the pair; pair of unused Morel MW164 woofers (double magnets, 75mm Hexatech aluminum voice coils, 4Ω), \$100 for pair (originally \$80 each). Call Dean at 720-532-2574 or e-mail deanbrenda@comcast.net.

Curcio Audio CD12V D/A Processor (see curcioaudio.com). Complete working unit with upgrades from stock unit. Three Hammond toroid transformers, pre-regulator for HV. Holco resistors, 20 MIT MultiCaps, low ESR caps, asking \$1300. Also, power amp project for parts—includes two Hammond 167P60 transformers 60VCT 300VA \$100. Contact David at 604 988-6666 or elderton@telus.net.

FRIED C3 two-way TL loaded monitor speaker kit. Two 6.5" bass-mid drivers, two 0.75" Hiquphon dome tweeters. Two upgraded series crossovers, binding posts, mounting hardware, construction manual for cabinets. 90dB/1W, 8Ω. \$75 + shipping. Contact Dan at 317-299-6024, or fastcat95@juno.com.

Horns: short EV tweet horns from Musi-caster PA, approximately 2" x 6" mouth, 6.2Ω DCR voice coils. Longer (7") EV tweet horns, fiberglass oddities, approximately 3" x 14" mouth, 7.5Ω DCR voice coils. Make offer. P.S. Parts: 75W transformer; secondaries are 300-0-300V AC, 6.5V AC, with CT, 250V AC, with 247, 243, and 235 V Taps, \$15 plus shipping. Small

P.S. chokes, ferrite cores: 1.5H, 50mA DC, 35Ω DCR, \$5 ppd. 2H, 15mA DC, 60Ω DCR, \$5 ppd. CORCOM 6EQ1 EMI filters, 6A at 120V AC, fourth-order balance line filter, \$10 ppd. Amps: Altec 1569A mono tube units. Used at V.M.I. for PA. 80W each; rough but complete. \$250 each plus shipping. Tom, PO Box 713, Staunton, VA 24402, 540-886-2634.

Two (one pair) Dynaudio 12" woofers #30W100 in new condition, \$200 OBO, e-mail Rick at bjwmthis@comcast.net.

New, top quality parts collection: chips, diodes, transistors, precision resistors, \$30; rotary panel mount, autotransformer, 8A, 0-130 VRMS, \$28; similar, behemoth autotransformer, 20A, \$55; Large two wire/two prong isolation transformer (guestimate 12A), \$35. Will consider best offers; e-mail Ken at nad512@erols.com.

Parasound HCA-3500 stereo amplifier 500W/channel, like new condition, \$1000 including shipping; Harman Kardon Citation II tube amp 60/60W, extensively modified and upgraded internal and external, documented performance, \$500; pair of Hafler DH220 amplifier modules with power supply, no case, ready to use, \$120 per set (two available). Call or e-mail for details. Joerg 561-881-8112, jzschrnt@aol.com.

Holman Preamp, \$30; DBX 228 NR unit, \$20; DBX 119 NR unit, \$20; Crown IC-150 preamp, \$50; Olson VT FM tuner, \$10; Realist VT receiver STA-30, \$45; Paco VT integrated amp, \$45; Altec 1569A power amp, \$100 each; Proton 1100 preamp, \$50; Leach double barrel 250W/channel circuit boards and all parts, \$125; misc. transf., caps, and so on. Send e-mail for

list of other parts, j-rhurley@webtv.net, or shurley@itsmarta.com.

Bozak Symphony, Altec Lansing horns, drivers JBL-L 100s Crown and Janszen Electrostatics, 301-596-5637.

## WANTED

Heathkit tt1 tube tester for parts—grid current test switch 6550, EL-37, KT66, KT88, 301-596-5637.

Good used moving coil cartridge (Ortofon, Sumiko, or similar), e-mail type and price to j-rhurley@webtv.net or shurley@itsmarta.com.

Kenwood LO7MII or LO5M output/power transistors: 2SA1007A and 2SC2337A. Purchase or source and substitution information would be welcome. Replacement kit 2SA1494 contents and modification information. Johan Granfeldt, 707-829-7072, e-mail: jgranfeldt@att.net.

JBL L250Ti speakers—mint condition for individual in Australia. Shipping within USA need only be to a forwarding agency warehouse in Los Angeles, e-mail WillNan@evansville.net.

Tube Sound Equipment: amps, preamps, tuners, crossovers, tubes, tube testers, horn speakers, all working or not, all old/new. Call 850-314-0321, or e-mail sonnysound@aol.com.

Heathkit stereo power amplifier—good or working condition. Schematic for Precision Fidelity C-8 hybrid preamplifier. George Mueller, mcwill@earthlink.net.

## AD INDEX

ADVERTISER	PAGE	ADVERTISER	PAGE	ADVERTISER	PAGE	ADVERTISER	PAGE
ACO Pacific Inc.	59	Electus Distribution Pty Ltd	65	Parts Express Int'l, Inc.	CV4	<b>CLASSIFIEDS</b>	
Antique Radio Classified	51	Front Panel	48	Pass Laboratories	13	All Electronics	70
Audience	67	Hagerman Technology	63	Plitron Manufacturing	51	Audio Classics LTD	70
Audio Amateur Corp.		Hammond Manufacturing	17	PNF Audio	9	Audio Electronic Supply	70
audioXpress subscription		Harris Technologies	25	Selectronics	23	Billington Expo	70
AAI - 70's on CD	26	Hi Fi Do Inc	43	Sencore	39	Borbely Audio	70
Classifieds	71	Jupiter Condenser	61	Solen, Inc.	11	Faraday Sound	70
New Books	66	K&K Audio	61	Soundstring Cable Technologies	CV2	JENA Labs	70
Sei - TLWRX	44	KAB Electro-Acoustics	72	Speaker City USA	49	Klein Tech	70
Williamson Amplifier on CD	68	Kimber Kable/WBT-USA	6,7	Sunrise E&E Inc	64	London Power	70
Audio Consulting	57	Langrex Supplies	41	Swans Speakers	5	Per Madsen Design	70
Audio Electronic Supply	47	LC Audio Technology ApS	4	Test Equipment Depot	55	Precision Sound Products	70
Audio Transformers	53	Liberty Instruments	21	Thetubestore.com	65	Soundstring Cable Technologies	70
audiomylum.com	19	Linear Integrated Systems	63	Thorens	35	SouthWest Electronics	70
Audiomatica	31	Madisound Speakers	27	Usher Audio	1	Speakerbits	70
Avel Lindberg Inc	69	McFeely's	67	VASGO LTD	33	TDL Technology	70
Classified Audio-Video	64	Mouser Electronics	45	VASGO LTD	68	WBT-USA/ Kimber Kable	70
DH Labs	CV3	MCM Electronics	15	Welborne Labs	29	Yeager Audio	70
EIFL	25	Parts Connexion	37			Welborne Labs	70
Electra Print Audio	69						



# Audio Aid

## BNC Jack Positioner

By Charles Hansen

I make a fair number of projects that use BNC jacks, so I made a tool for aligning the two index pins on the jacks so they are vertical. Not only does this give the finished project a more professional look, it also makes installing and removing test cables easier when the pins are consistently in the same position on a chassis.

Test equipment manufacturers have invested in expensive punches and dies that make chassis holes with flats on one side to make the installation and alignment of jacks, controls, switches, and so on, easy for production assembly. The rest of us must hold the chassis-mounted items in alignment with pliers or wrenches, and hope the components don't rotate out of position as we tighten the retaining nuts. This usu-


ally requires rotating the part slightly out of position and allowing for some small amount of final rotation. Unfortunately, this lack of precision can also scratch the finish of the project.

The thin wall of the BNC jack shell presents added problems. You could apply too much pressure while trying to hold it in alignment and squeeze the shell out of round, or damage the two small alignment pins. I tried modifying a standard BNC plug to make an alignment tool, but its slots are designed to rotate for positive engagement, and installing the plug on an uninstalled jack required holding the jack with pliers, so I was back to the original problem.

The BNC jack installation alignment tool (*Photo 1*) works by means of two straight slots that engage the jack alignment pins. This allows you to hold the jack in its final location on the front of the chassis while you tighten the rear retaining nut. It is fast, easy, and produces accurate results.

was available. A local machine shop can probably make this tool for under \$20, but if you have a drill press and suitable drills, you can make it yourself.

Make sure the aluminum bar is clamped in a perfectly vertical position on the drill press table. Center-punch the aluminum bar and progressively drill the center hole to a final 0.391" ( $\frac{25}{64}$  drill). Then carefully cut a vertical slot across the diameter of the hole,  $\frac{3}{32}$ " wide and  $\frac{3}{8}$ " deep. A standard hacksaw blade makes a slot about 0.05" wide, so you will need to do some additional work with a small flat file to get to  $\frac{3}{32}$ " (0.093"). Break all the sharp edges of the slots and the front of the bar with the small flat file. ❖

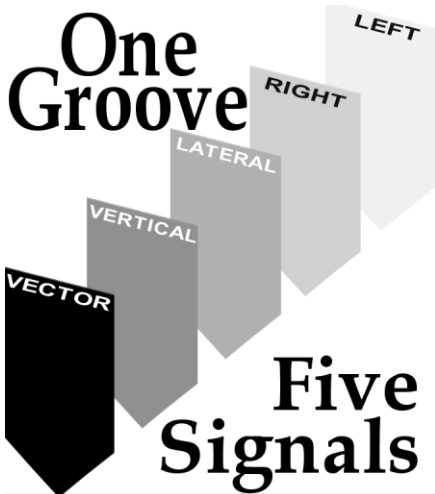

**PERFECTLY ALIGNED**

KAB introduces Groove Tuning™  
A new concept that lets you mix  
the five signals of a mono groove  
for the best sound possible.

Learn More Online

**KAB**

Preserving The Sounds  
Of A Lifetime

[www.kabusa.com](http://www.kabusa.com)

### CONSTRUCTION

*Figure 1* shows the drawing for making the tool, with the minimum dimensions needed for a comfortable grip on the tool while tightening the rear nut. I used a  $\frac{3}{4}$ " aluminum bar because it

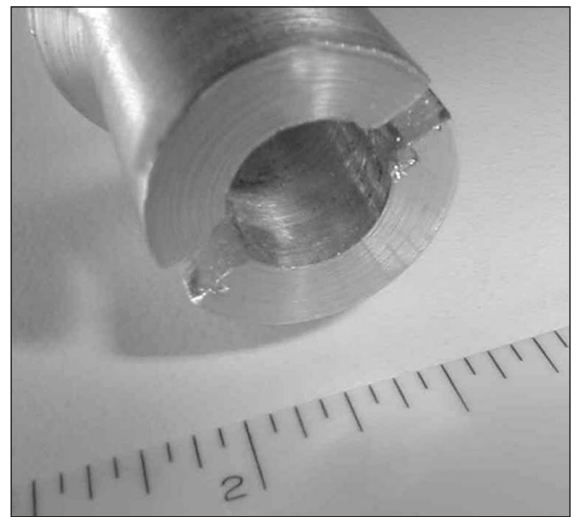


PHOTO 1: BNC alignment tool end view.

