

# VALVE

*the magazine of astounding sound*

**hardcore action - Buddhafied Afterglow**

**Deep Throat - a Lowther front horn**

**C<sup>4</sup>Sing the Decware Zen**

**da basics -  $V=IR$ , it's not just a good idea,  
it's the law!**

**mo' Heavy Metal**





# *B-Glow*

*single ended 300B amp kit*

*another masterpiece from Electronic Tonalties*

*active loaded 5965 driver*

*MagneQuest TFA-204 air gapped output transformer*

*8 watts*

*\$900 the pair, you just supply the 300 Bs*



# VALVE

*the magazine of  
astounding sound*

*Editor and Publisher*

Dan "Dr. Bottlehead" Schmalte

*Chief Administrator*

"Queen Eileen" Schmalte

*Resident Smart Guy and Technical Editor*

Paul "Brainiac" Joppa

*Graphic Design*

Bruce "Badd Dawg" Borley

*Resident Hot Iron and Dr. B's Bodyguard*

John "Smoothplate" Tucker

*Big gun OEM advisor*

Michael "Airgap" LaFevre

*The Guy With Answers*

John "Buddha" Camille

*Contributing Editors*

David "Full Track" Dintenfass

"Crazy Eric" Lenius

*Our mailing address:*

**VALVE**

P.O. Box 2786

Poulsbo, WA 98370

by phone: 360-697-1936

business hours: 9-5 PST, Mon -Fri

fax: 360-697-3348

e-mail - bottlehead@bottlehead.com

website - <http://www.bottlehead.com>

**VALVE** in no way assumes responsibility for anyone harming themselves through exposure to the contents of this magazine. We believe electrons flow from minus to plus, and that they can kill you along the way if you're not careful. Vacuum tube audio equipment operates at potentially lethal voltages. Always treat it with respect.

Many ideas published in this magazine are untried, and involve the use of potentially dangerous parts and tools. In attempting any idea or project published herein, you assume total responsibility for your actions and any harm caused to yourself or others. Please, be careful!

This publication is produced as a service to the audio community and is wholly owned and published by Electronic Tonalities.

The intent of this publication is to offer ideas to inspire and educate audiophiles in an effort to increase their understanding of the audio equipment they use and cherish. Blatant copying of the circuits published in this magazine for use in commercial products shows a complete lack of original thought.



## editor's thing

Yo, bottleheads-

Discussion came up at the last meeting that while the new surge in local VALVE membership has been bringing in lots of folks who are eager to learn the basics of design, there seems to be a general swing towards requests for "cookbook" circuits in VALVE by the worldwide membership.

(definition: if you read VALVE, you're a VALVE member, we are quite democratic)

How can I put this diplomatically-

Ain't gonna happen, no way, no how.

For those of you who have recently discovered the pleasures of tube audio, and are finding a desire to construct your own gear, maybe partly for economy's sake (Amen, bro!), maybe partly for the satisfaction of telling others "I made it myself!", we aren't going to let you off that easy.

See, VALVE was formed by a bunch of guys who didn't just roll tubes, or hook up a new piece of used gear every week. The guys who started VALVE learned early on to dig up the forgotten nuggets of information in arcane texts, apply that knowledge in their own experiments, and share that knowledge - not just the end result, but the *method* behind the madness as well. In fact the most hardcore DIY guys I know are usually more proud of their tube electronics book collection than they are of their projects!

What we intend to present in VALVE is not just a canned circuit full of exact Digi-Key numbers and a preprinted circuit board, but rather a general design and just enough information to make you work a bit to get the project finished.

This may seem a bit overwhelming the first time you work through a project published

here, and that's part of the reason we've started "da' basics" column, to help you through the math and other basic knowledge you will use again and again in designing tube gear. You'll usually find the math to help you through the tough spots, and once you finish a project or two, our hope is really that you'll go off on your own, devise some devilishly clever new circuit, and share it with the readership (complete with color photos, of course). Which brings me to another important point-


We need article submissions like yesterday. We need not only your new circuit designs, but also your photos of finished ET kits and other projects, stories of your experiences learning the craft of tube audio, and your pieces on the theory of various aspects of design. You needn't be intimidated by the fanatical attention to detail of Buddha or the way math rolls off the pen of Brainiac. Some of our most popular articles are those like the original old S.E.X. speaker piece, where we slapped a couple of drivers on a cardboard box! And in fact I can't think of two guys to whom the sharing of knowledge is more important. Believe me, they will appreciate your contributions more than anyone, no matter what your skill level at the time of writing.

So fire up the iron and the pen,  
but- don't let the blue smoke out,

Doc B.
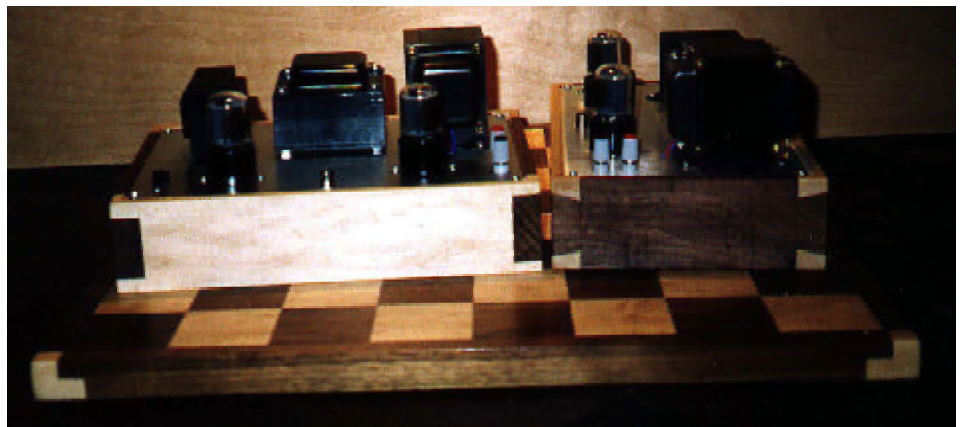
## on the cover

Mike Connly sent us these photos of his S.E.X. amps. Mike not only built the amp kits and made the custom walnut and maple bases for the amps, he also made the chessboard upon which they rest. Mike was the first bottlehead to build a Blues Master, and rumor has it he will be putting the completed amp in a new chassis soon. Another cover girl, maybe?



# NEW EXOTICA FROM FIRST IMPRESSION MUSIC



## FIM CD019 Favorite Chinese Instrumentals

### The Jin Ying Soloists

1 Like Wave Again The Sand (Pipa solo with ensemble) 4:36 2 Singing the Night among Fishing Boats (Jung solo) 4:15 3 Night (Percussion ensemble) 5:54 4 Love Song Of The Grassland (Tung-hsiao with ensemble) 2:34 5 Ducks Quacking (Percussion ensemble) 4:00 6 Love At The Fair (Er-hu solo with ensemble) 5:04 7 The Fishing Song (Ba-woo solo with ensemble) 4:53 8 Happy Reunion (Xylophone solo with ensemble) 2:55 9 Chinese Martial Art (Emsemble) 1:43 10 The Flowing Stream (Er-hu solo with Yang chin) 8:25 11 Spenpadei Folksong (Yang-chin solo with ensemble) 4:32 12 Autumn Moon (Er-hu solo with ensemble) 7:06 13 Moonlight Over The Spring River (ensemble) 9:22 14 Variation On Yang City Tune (Ku-jung solo) 5:36

## FIM CD020 A Vocal Tribute to Ben Webster

### Jacintha, Vocal

Teddy Edwards, tenor sax; Kei Akagi, piano; Darek Oles, bass; Larance Marable, drums

1 Georgia On My Mind (Gorrell-Carmichael/BMI) 5:19 2 The Look Of Love (Baccharach-David/ASCAP) 4:08 3 Danny Boy (Traditional) 7:26 4 Somewhere Over The Rainbow (Harburg-Allen/ASCAP) 9:43 5 Stardust (Parish-Carmichael/ASCAP) 6:40 6 In The Wee Small Hours Of Morning (Hillard-Mann/ASCAP) 4:15 7 Tenderly (Lawrence-Gross/ASCAP) 5:25 8 Our Love Is Here To Stay (George & Ira Gershwin/ASCAP) 3:19 9 How Long Has This Been Going On? (George & Ira Gershwin/ASCAP) 5:28 10 Pennies From Heaven (Burke-Johnston/ASCAP) 3:12



#189 16149 Redmond Way  
Redmond, WA 98052

<http://www.fimpression.com>

Tel: 425-868-5326  
Fax: 425-836-9061

# ***Buddhafied Afterglow***

Hi Dan,

Talked to Ken Dangerfield and he has been busy on the Internet. He told some group about the beefed up design I gave him for a two chassis layout for the Afterglow. (we had this info posted on the old website -B.)

He has been getting numerous questions about the power supply, switching, noise suppression and CMCs. He came up with the idea of putting the mod on your internet site, so I cleaned up the drawings so you might scan them into the gadget. Evidently you are assembling a compendium of A-glow mods - pretty neat.


Included a short theory-of-ops to save you from a bunch of questions. Hope you do not find all of this too presumptuous.

Regards,

John C.

Can you believe this guy? Too presumptuous? Zowie, this article has some incredible gems in it! Study these pages hard, learn from Buddha, and be a better builder for it!


Doc B.

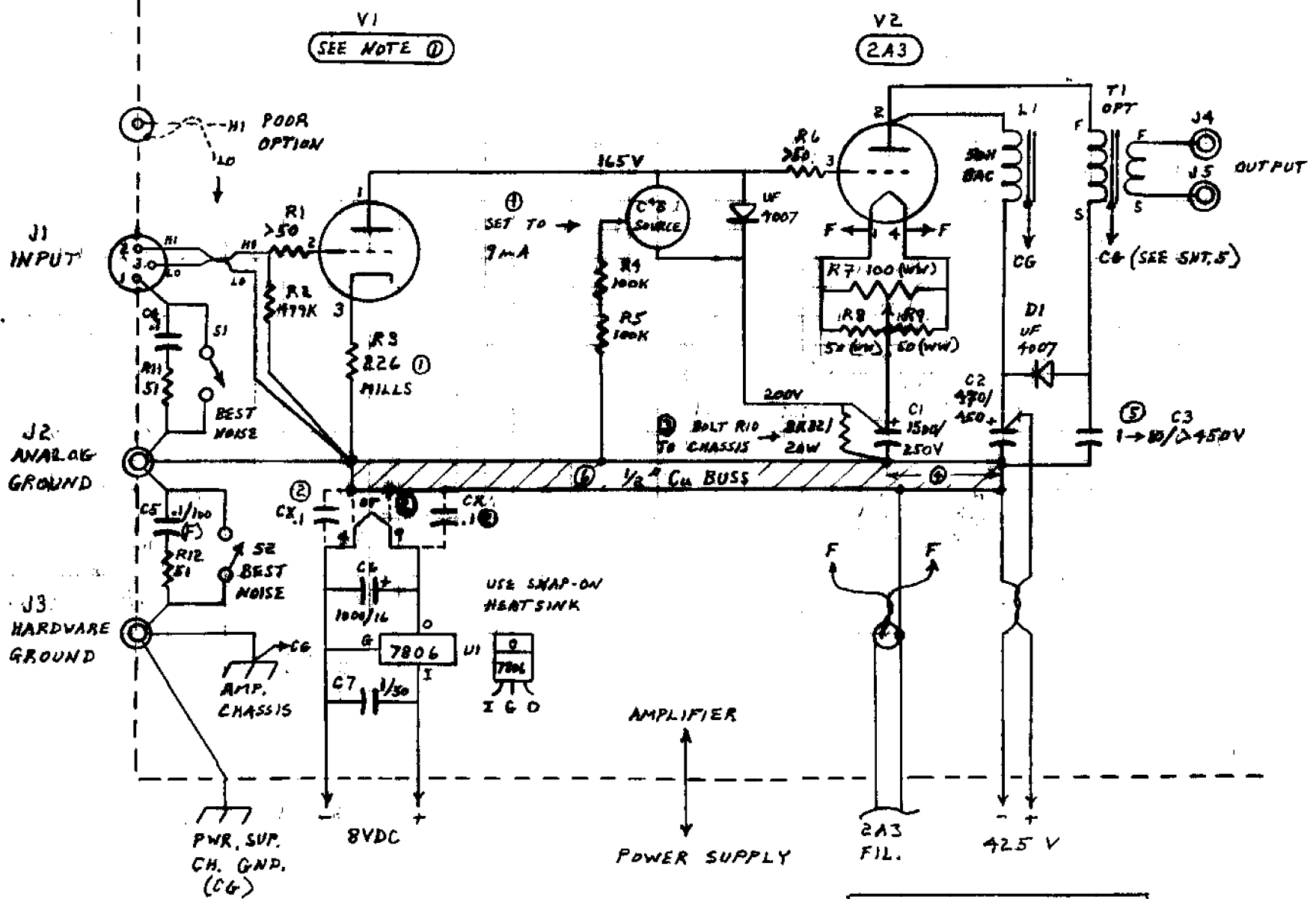


AFTER-GLOW MOD 1

AFTER-GLOW MOD 1 NOTES:

- ① PIN-OUT & CIRCUIT VALUES SHOWN FOR  $\frac{1}{2}$  5965. THE OTHER AMP. SHOULD BE WIRED USING THE OPPOSITE HALF OF THE TUBE, THUS, TUBES CAN BE ROTATED FOR LONGER LIFE. HIGH  $G_m$  / MEDIUM  $\mu$  TUBES SUCH AS THE 6BN4, 12AV7, 5670/2C51 MAYBE SUBSTITUTED BY ADJUSTING  $R_k$  & THE  $C^1S$  CURRENT TO OBTAIN THE PROPER BIAS, THUS PLATE CURRENT FLOW, FOR THE 2A3. SEE PARTS SH. T.
- ② TEST VARIOUS COMBINATIONS OF FIL. BYPASS OR A DIRECT CONNECTIONS TO GROUND FOR BEST HUM & NOISE. INSTALLATION SPECIFIC.
- ③ THE METAL CASE OF THE SPECIFIED RESISTOR MUST BE ADEQUATELY HEAT-SINKED IN ORDER TO DISSIPATE 12 W. IF CHASSIS IS LESS THAN .063 ALUMINUM, FIT ADEQUATE HEAT-SINK TO CHASSIS TOP SIDE.

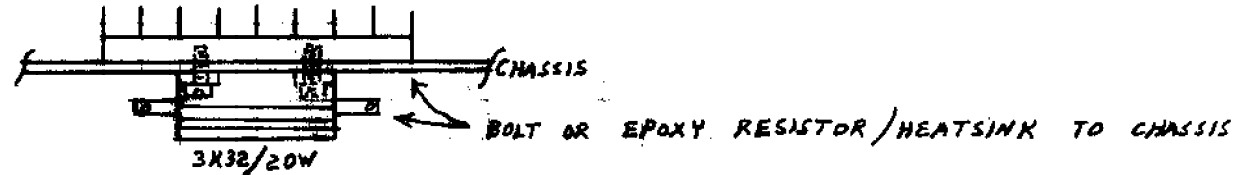

- ④ MOUNT BYPASS CAPS. WITH NEGATIVE LEADS SOLDERED TO BUSS WITHIN 1" OF EACH OTHER.
- ⑤ EXPERIMENT WITH VARIOUS VALUES OF OPT BYPASS CAPS. EACH AMP. / SPKR. COMBINATION WILL HAVE A GENERAL SWEET SPOT AT THE LOW FREQUENCY EXTREME. AS THE CAPACITY IS VARIED,
- ⑥ A FAST, LO-NOISE GROUND BUSS MAYBE FABRICATED ⑦ COPPER SHIELDING TAPE LND OVER PTFE FILM. 3M GLASS CLOTH TAPE MAY BE SUBSTITUTED FOR THE HIGH COST PTFE TAPE. HI-TEMP TAPES MUST BE USED TO ALLOW DIRECT SOLDER TO THE TAPE. DO NOT USE ACETATE, VINYL OR OTHER LO-TEMP FILMS.

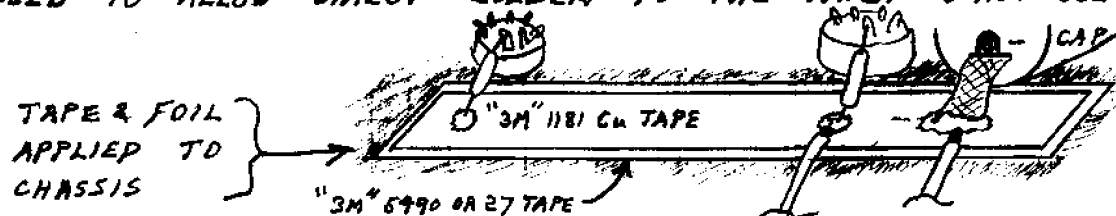

TAPE FROM  
NEWARK  
1-800-463-9275

HOBBY OR FLASHING COPPER MOUNTED ⑧ NYLON HDWR. MAY ALSO BE UTILIZED.

AFTER-GLOW MOD 1 PARTS:

MOST PARTS AVAIL. FROM:

- C1, 1500 mF/250V ELEC. PAN. TSHB (DIGI. P10134)
- C2, 470 mF/450V ELEC. PAN. TSHB (DIGI. P10170)
- C3, 1 TO 10 mF / > 450 VDC FAVORITE DIELECTRIC
- C4, C5 & C6, 0.1/100V FILM
- C6, 1000 mF/16V ELEC.
- C7, 1 mF/50V FILM
- J1, XLR PANEL RECEPTACLE OR ISOLATED BNC/RCA
- J2 → J5, 5WAY BINDING POSTS
- R1, 50Ω OR GREATER GRID STOP-YOUR TWEAK-
- R2, 499K/0.25W FILM
- R3, 226Ω QUIET WIRE WOUND (MILLS)
- R4, R5, 100K 1% METAL FILM / BULK FOIL
- R7, 100Ω ONE TURN TRIMMER, WIRE WOUND (MOUSER 510-U80-100) NOTE: TREAT (☺) PRO-GOLD
- R8, R9, 50Ω/1W WIRE WOUND (DIGI. 43F50/DHMIT) TANNER MAY HAVE EQUIVALENT.


TANNER ELECTRONICS 972-242-8702  
 ALSO  
 DIGI-KEY 800-344-4539  
 Mouser 800-346-6873

- R10, 3K32Ω/20W DALE RH STYLE CHASSIS MOUNT (WW)
- R11, R51Ω/0.25W FILM
- C+S, CURRENT SOURCE KIT (ELECTRONIC TONALITIES)

MISC.


- L1, 50H/20mA MAGNAQUEST BIG-ASS-CHDRE (BAC)
- T1, >2500Ω TO 8Ω OPT, MAGNAQUEST FINSTRIP OR NIKKEL
- U1, 7806 V-REG. TO-220 (☺) SNAP-ON HEATSINK
- S1, S2, SPST TOGGLE
- DIODES, UF4007 (TANNER ELEC)
- PLUS: TUBES, SOCKETS, HDWR, WIRE, 3M TAPES, ETC.

COMMENT (CONT)

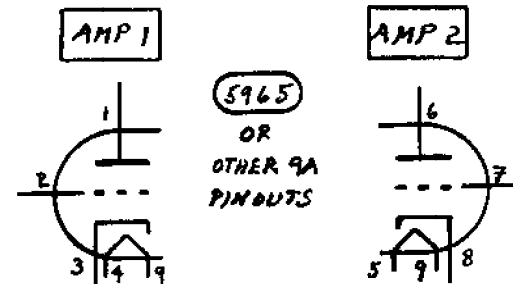

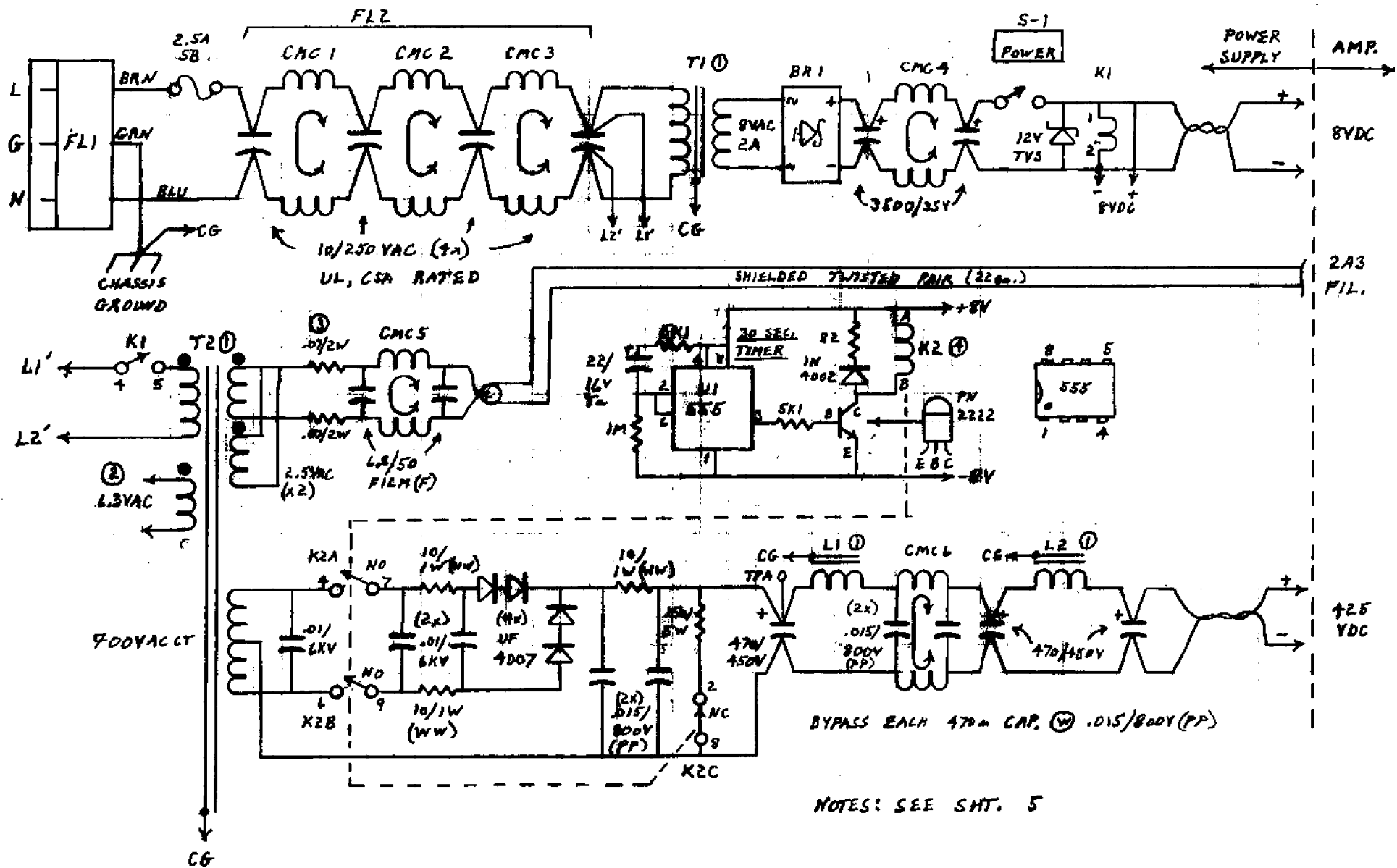TYPICAL DUAL-TRIODE WIRING FOR EXTENDED LIFE. SWITCH TUBES BETWEEN AMPS. AT THE END OF LIFE TO USE THE UNUSED PORTION. GROUND UNUSED CATHODE, GRID & PLATE PINS.






MINIMALIST POWER SUPPLY

SHEET 4


POWER SUPPLY NOTES:

- ① ALL IRON SHOULD BE MOUNTED ON SHOULDER WASHERS SUCH THAT NO CONNECTION EXISTS  $\text{\textcircled{W}}$  CHASSIS. RUN SEPERATE LEADS FROM EACH XFRMR. CHOKE FRAME TO SINGLE POINT CHASSIS GROUND. DO NOT DAISY CHAIN GROUND LEADS.


WARNING: DO NOT OMIT

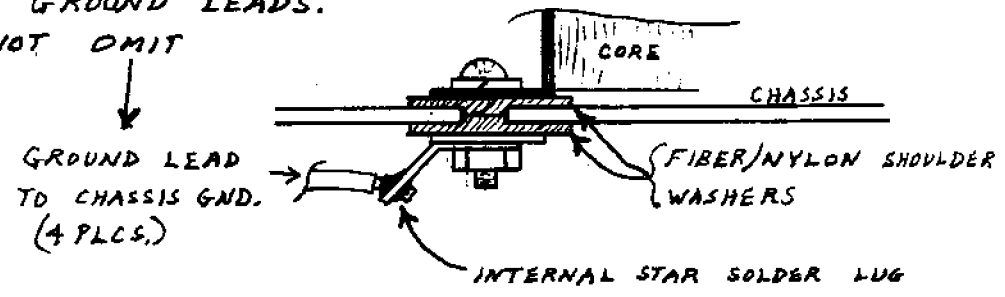

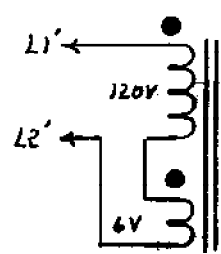- ② THE 6.3VAC WINDING IS USED AS A BUCK-BOOST WINDING TO TAILOR B+ OUTPUT TO THE LOCAL LINE VOLTAGE. B+ MUST STAY BELOW 450 VDC AT TPA (TEST POINT A). PROPER HOOK-UP MUST BE DETERMINED DURING DE-BUG. USE NORMAL CONNECTION (AS DRAWN) IF B+ IS BETWEEN 400 & 430V. USE THE BUCK CONFIGURATION IF B+ IS NEAR OR OVER 450VDC. USE THE BOOST (REVERSE 6.3VAC WINDING LEADS) IF B+ IS BELOW 400 VDC.




BUCK CONFIGURATION

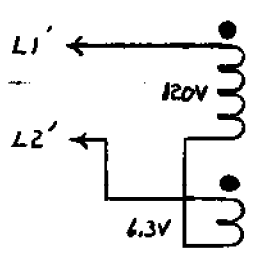

BOOST CONF.

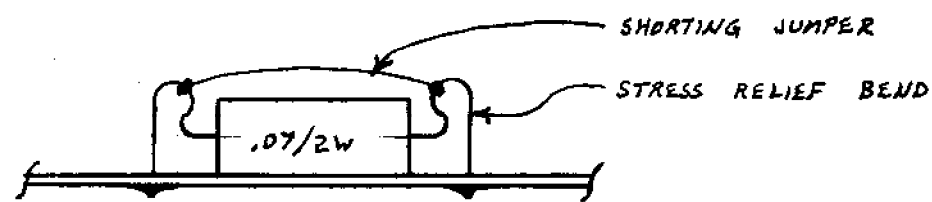- ③ MOUNT 0.07 $\Omega$ /2W (WW) RESISTORS  $\text{\textcircled{W}}$  EXPANSION STRESS RELIEF LEAD CONFIGURATION. SHORT RESISTORS AS NECESSARY TO ACHIEVE 2.25  $\rightarrow$  2.5 VAC @ 2A3 SOCKET. THIS PROCEDURE MUST BE ACCOMPLISHED AFTER STEP ② ABOVE. ADD 0.07 $\Omega$  RESISTORS AS NECESSARY IF FILAMENT VOLTAGE IS OVER 2.5 VAC. DO NOT OVER-VOLT FILS.



- ④ USE ONLY THE SPECIFIED RELAY TO SWITCH THE HV SUPPLY. PAY PARTICULAR ATTENTION TO CONTACT NUMBERS EMBOSSED ON RELAY INSULATOR BLOCK. SUBSTITUTE RELAYS MUST HAVE ADEQUATE INSULATION & LEAKAGE PATHS FOR VOLTAGE INVOLVED. HI-POT SUBS. @ 1000 VAC. FOR 71 HR. CONTACTS TO CONTACTS & TO FRAME.

MINIMALIST POWER SUPPLY PARTS LIST:

FROM: TANNER ELEC. 972-242-8702

- FL1 SPRAGUE IEC FILTER 4A  $\odot$  WIRE LEADS  
 F1 2.5A JAG 5LD-8LD 8 HOLDER  
 (4ea.) 10mF/250VAC ACROSS LINE CAP.  
 CMC1  $\rightarrow$  CMC5 PANASONIC 4700mH/1A COMMON MODE CHOKE  
 T1 .8V/2A SURPLUS XFORM.  
 RR1 SCHOTTKY DIODE BRIDGE (4ea) 3A/60V DIODES  $\mu$ S R306  
 (2ea) 3300/35V ELEC. CAPS.  
 12V/5W TVS TRANSIENT VOLT. SUP.  
 K1 SPDT 10A CONTACT /RV COIL [SCHRAACK (ORANGE)]  
 S1 SPST 10A TOGGLE SW.  
 T2 ORIGINAL A-BLOW PVR. XFORM.  
 (2ea) .07 $\Omega$ /2W (WW) RES  
 (2ea) 6.8/50V FILM CAP.  
 22mF/16V DIPPED TANTALUM CAP.  
 (2ea) 5K1/.25W CARBON FILM (CF)  
 1M/.25W (CF)  
 555 TIMER IC  $\odot$  8 PIN DIP SCKT.  
 82 $\Omega$ /.25W (CF)  
 2 1N4002 DIODE  
 MTS OR PN 2222 NPN XSTR.  
 K2 3PDT/10A - 9V RELAY [DELTRON (BLUE)]  
 (3ea) .01/6KV CAP  
 (3ea) 10/1W (WW) RESISTOR  
 (8ea) .015/800V CAP  
 150  $\rightarrow$  200 $\Omega$ /5W (WW) RES.  
 (3ea) 470/450V ELEC. CAP.  
 L1, L2 5H/150mA/105 $\Omega$  DCR CHOKE (ANTIQUE) SUB  $\odot$  CHOKES HAVING <100 $\Omega$  DCR  
 (4ea) UF4007 ULTRA-FAST DIODES  
 CMC 6 104 mH/200 mA CMC (DIGI PLK1064)

SEVERAL ANNOTATED PARTS FROM:  
 ANTIQUE 602-820-5411  
 DIGI-KEY 800-344-4539  
 MOUSER 800-346-6873

## AFTER-GLOW COMMENTS

THIS "A-GLOW" MODIFICATION WAS DESIGNED TO FIT A CONSTRAINED PHYSICAL LAYOUT USING READILY AVAILABLE PARTS & TO A CERTAIN EXTENT <sup>WAS</sup> LIMITED BY COST.

THE BASIC, TWO-STAGE, DIRECT-COUPLED AMPLIFIER HAS ONLY BEEN TWEAKED TO LOWER HUM/NOISE & TO SPEED IT UP SLIGHTLY.

CONVERTING BOTH CATHODE BIAS NETWORKS TO ALL WIRE WOUND WILL HELP THE NOISE LEVEL. DO NOT WORRY ABOUT INDUCTANCE - HERE IT HELPS. THE U80 STYLE PBT USED AT R7 LOOKS A BIT KLUDGY BUT THEY HOLD A SETTING FOR YEARS & DO NOT MIND DC.

THE DUAL GROUND SYSTEM WAS ADDED TO MAKE THE SYSTEM COMPATIBLE WITH ULTRA-LOW-NOISE PRE-AMPS, ETC.

A DC FILAMENT SUPPLY WAS ADDED FOR HUM REDUCTION.

C1 & C2 ARE INORDINATELY LARGE COMPARED TO OTHER DESIGNS. THE 1500  $\mu$ F @ C1 PUTS MOST OF THE SIGNAL DEVELOPED BY V2 ACROSS THE OPT. C1'S 1.8  $\Omega$  REACTANCE AT 60 Hz. ALSO HELPS IN THE HUM NULL DEPARTMENT. C2 KEEPS MOST OF THE AC SIGNAL DEVELOPED ACROSS L1 ON-CHASSIS & OUT OF THE POWER SUPPLY. A SHUNT REGULATOR WITH A .01  $\Omega$  IMPEDENCE IS NOTICEABLY BETTER WHEN THE POWER SUPPLY CAPABILITY EXISTS.

THE UF4007 DIODE AT D1 DRAINS THE OPT BYPASS CAP UPON SHUT-DOWN. THIS ACTION KEEPS MOST OF THIS DC CURRENT FROM MAGNETIZING THE NICKEL CORE OF T1. A COMPLETE CURE ENVOLES PLACING A SET OF RELAY CONTACTS ACROSS THE PRIMARY THAT ARE ACTUATED DURING START-STOP OPERATIONS.

## AFTER-GLOW POWER SUPPLY COMMENTS

A FAIR AMOUNT OF NOISE & HUM FILTERING WERE ADDED AS SPACE PERMITTED. THE SPEC'D LINE FILTER FL1 (FROM TANNER) STARTS BECOMING EFFECTIVE @ 50 KHZ VS 10 MHZ FOR OTHERS USUALLY SPEC'D. THE DISCRETE FILTER FL2 STARTS ROLLING OFF @ SEVERAL HUNDRED HZ. THIS COMBINATION REDUCES LINE NOISE OVER MUCH OF THE SPECTRUM. FL2 ALSO FORMS A LINEAR TRANSFORMER THAT REDUCES THE NORMAL AC LINE IMPEDENCE OF 100→150  $\Omega$  DOWN TO APPROX. 65  $\Omega$ . THUS, A LITTLE BEEF IS ADDED TO THE LOW-END ALONG WITH A SIGNIFICANT DROP IN BACK GROUND NOISE.

COMMON MODE CHOKES ARE ALSO USED IN THE SIGNAL PATH OF EACH POWER SUPPLY IN ORDER TO REDUCE THIS MOST COMMON FORM OF RFI INTRUSION.

SCHOTTKY DIODES AT BR1 STOP THE HUGE AMOUNTS OF REVERSE-RECOVERY NOISE GENERATED BY  $p_n$  DIODES USUALLY SPECIFIED FOR FILAMENT SUPPLIES.

THE HV RECTIFIERS SPEC'D (UF4007) HAVE A REVERSE RECOVERY CHARACTERISTIC THAT IS MUCH EASIER TO FILTER THAN EVEN HEX-FRED DEVICES. WITH THE RC FILTERING PROVIDED BY THE 10 $\Omega$ /.01 COMBINATIONS, RECOVERY SPIKES ARE USUALLY BELOW 10mV IN AMPLITUDE VS 10'S OF VOLTS FOR MOST  $p_n$ 'S & HEX-FREDS. CMC 6 SHOWS THE REVERSE RECOVERY  $dv/dt$  RATE SO THAT SUBSEQUENT FILTERS ARE MORE EFFECTIVE.

THE 55 TIMER CIRCUIT ALLOWING DELAYED B+ APPLICATION SAVES THE TUBES & PREVENTS HV SOARING. THE UNUSUAL USE OF A SPARE SET OF NC RELAY CONTACTS ALLOW GROW-BARRING THE B+ UPON SHUT DOWN. THIS ACTION REDUCES STRIPPING AS EACH CATHODE COOLS & REDUCES SHOCK HAZARD. THE FULLY DISCHARGED CAP'S ALSO CAUSE B+ TO RISE AT A PREDICTABLE RATE THROUGH OUT THE ENTIRE CIRCUIT. <sup>AT TURN ON.</sup> THE 555 IS ALSO CONFIGURED TO OPEN K2 FOR 30 SEC. EACH TIME THERE IS A POWER INTERRUPTION PREVENTING SHORT-CYCLE SURGES FROM LIGHTNING, ETC.

ALL IRON IS MOUNTED ON INSULATING WASHERS TO REMOVE CIRCULATING CURRENTS FROM THE CHASSIS.

FOR B+

ONLY TWO LC FILTER SECTIONS USED, DUE TO SPACE LIMITATIONS & AVAILABLE B+. ONE OR TWO MORE SECTIONS ARE NEEDED FOR BETTER LOW NOISE OPERATION.



*3 Watts...106dB....*

*Can't get much more efficient than that!*

*Lowther America and Welborne Labs have teamed up to offer the best package deal in Audio.*

*Hi-Fi enthusiast or just plain music lover take a look at this.....*

*A combo package featuring Welborne Labs Moondog 2A3 SE monoblock amplifiers along with Lowther America's Medallion 99 cabinets and Lowther PM2A drivers.*

*And... the best part is..... the price!*

*Full Kit only... \$2949.00*

*Completely Assembled... \$3999.00*

*For more information on this package deal contact either party*



**Welborne Labs**

P.O. Box 260198, Littleton, CO 80126 USA  
tel: 303.470.6585 fax: 303.791.5783  
<http://www.welborne.com>

**Lowther - America**

P.O. Box 4758, Salem, OR 97302 USA  
tel: 503.370.9115 fax: 503.365.7327



*the Deep Throat Horn*



*a front horn for Lowther drivers*

*by Bent Audio*

John Chapman of Bent Audio sent us these wild horns a few months back, and Doc just finally got around to setting them up. The tractrix expansion contour horns are molded from ABS and have a theoretical cut off frequency of 140Hz.

The horn mouth is about 34" in diameter, and the horn is 18" deep, hence the name Deep Throat. The throat opening is 7-1/2", just right for fitting snugly against the frame of a Lowther driver.

The driver mounts to a piece of PVC pipe which comes cut to just the right length to make a nice mounting flange, as seen in the picture to the right. John suggests attaching the flange with 5 minute epoxy putty, which worked nicely. The putty is rolled into a snake of a length approximately equal to the throat circumference and then pressed in the tapered gap between the outside of the horn throat and the PVC flange.

Once the epoxy dried holes were drilled for 3/16" hanger bolts and the drivers were slipped on and secured with brass nuts and washers.

The backs of the drivers were left open for the first audition, and fiberfill was piled over the backs to damp the rear wave. A quick and dirty frequency sweep by ear indicated that the horns went down pretty smoothly to 200hz, where they begin to roll off.

Anyone who has listened to Lowthers knows they have a 'presence peak' which is generally centered around 2-2.5kHz.

I have measured my PM2As as having more of a plateau from 2 kHz clear up to 10 kHz, so I was curious to see if these horns would fill in the midrange and upper bass.


Yup! The peak is still there a bit, but the front loading does wonders for the balance without losing any of the speed and life that the Lowthers are known for. The dynamics are stunning, I have a drum solo that will blow your mind on these guys. I estimate overall sensitivity at something a r o u n d 101dB@1W@1M.

I have been using a Whamo subwoofer temporarily, but we'll develop a woofer that's a better match both in terms of bandwidth and sensitivity in the future. These babies may not be 'plug'n'play', but they are really worth trying if you're a hardcore Lowther tweak. The Deep Throat Horns are \$520 the pair,



plus shipping. Contact John Chapman at Bent Audio, [Ichapman@home.com](mailto:Ichapman@home.com) or 604-533-6684 for more info.

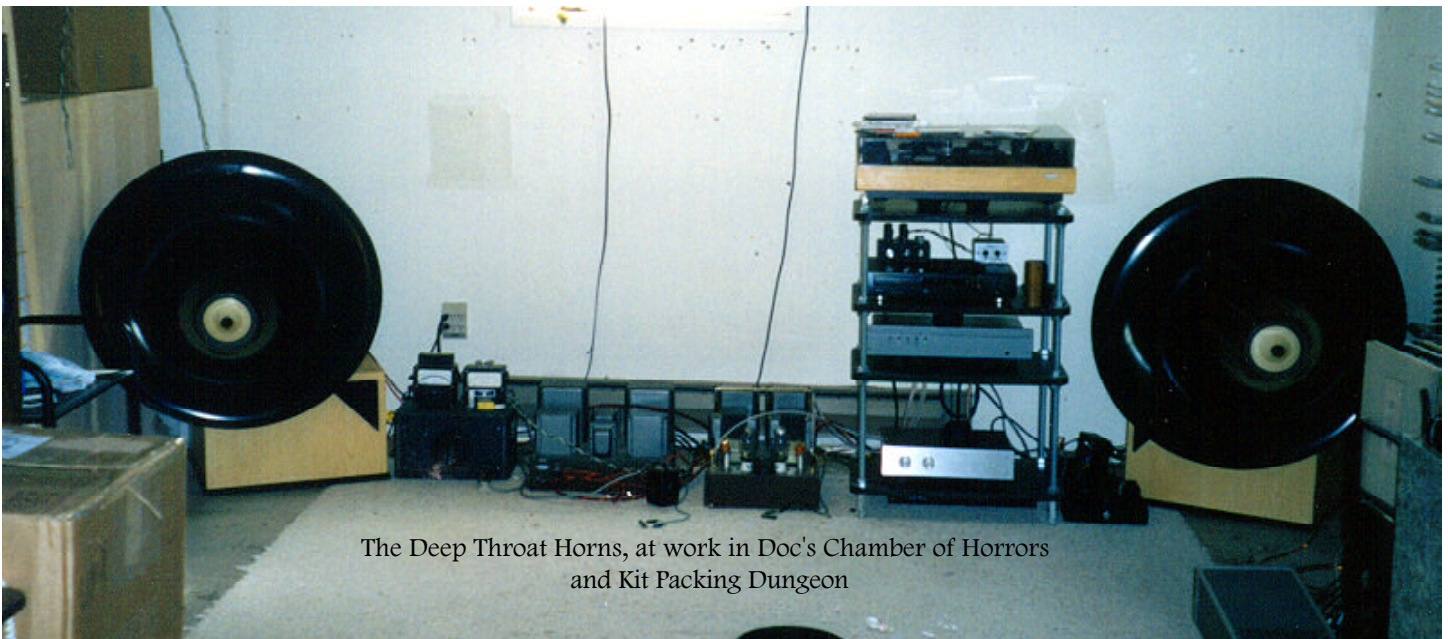A similar horn called the Oris 150 has been developed by Bert Doppenberg. More info about it can be had at <http://home.wxs.nl/~lowther/final.htm>



The Deep Throat Horns, at work in Doc's Chamber of Horrors and Kit Packing Dungeon

# Out with the Old

We are closing out the KR Enterprise VV Valves to make room for the new generation of KR tubes. All sale tubes below have the KR 1 year warranty from date of purchase. Visit our website for KR pictures, specs and curves. <http://www.welbornelabs.com/krhome.htm>

**Please Note: These VV Valves all have 2A filament current requirements. Please check your equipment specification before ordering and make sure they will operate in your amps.**

**No returns on these sale items.**

**VV300B**...the following are all electrically the same tube, just different glass shapes and color. The cylinder tubes are just that...they have a cylindrical shape with a flat top.

VV300B	regular transparent glass	\$200 per pair
VV300BL	regular blue glass	\$200 per pair
VV302BL	regular blue glass	\$200 per pair
VV302BC	blue cylinder	\$200 per pair

**VV32B**...these VV32Bs are all electrically the same tube except for glass color and shape.

VV32B	regular transparent glass	<b>all sold</b>
VV32BL	regular blue glass	\$250 per pair
VV32BC	blue cylinder	<b>all sold</b>

**VV52B**...these VV52Bs are all electrically the same tube except for glass color.

VV52B	regular transparent glass	<b>all sold</b>
VV52BL	blue glass	<b>all sold</b>



**Hurry, quantities are limited.**

**All sales are final.**

**Buy 2 pair... take a 5% discount.**

**Buy 3 pair... take a 10% discount.**

# In with the New

**New From KR Enterprise. All tubes feature a 2 year warranty.**

**KR10 Dual Triode Pre-amp and Driver Tube.**

A 6SN7 on Steroids? **\$395.00/pair**

**KR2A3 Single-Plate Vacuum Tube**

A great new single plate 2A3. 2.5V/2.0A filaments. 2-6 watts of glorious sound. **\$395.00/pair**

**KR PX25 Vacuum Tube**

A replica from the past. 4.0V/2.0A filaments. 8 watts. **\$435.00/pair**

**KR300B Vacuum Tube**

An awesome 300B replacement. 7 to 14 watts, 5.0V/1.2A filaments. **\$435.00/pair**

**KR300BXL5 Vacuum Tube**

8 to 20 watts of power and dynamics. 5.0V/1.2A filaments. **\$575.00 per pair**

 **Welborne Labs**

ph: 303.470.6585 fax: 303.791.5783

<http://www.welbornelabs.com>

e-mail: [wlabs@ix.netcom.com](mailto:wlabs@ix.netcom.com)



**New KR2A3**



you  
asked  
for it


# C4Sing the Decware Zen

By Doc B.

We've had several calls from folks who've been using the Decware SE84B Zen amp, a single ended SV83 amp manufactured by Steve Deckert ([www.decware.com](http://www.decware.com)). A few of the callers have listened to the Zen amp and have asked us for a way to make the Zen sound a bit more dynamic.

I point out here that the folks who have called *liked* the Zen amp, this article is not intended in any way to be a flame job of the stock amp. This mod is offered strictly in the spirit of experimentalism that makes VALVE what it is.

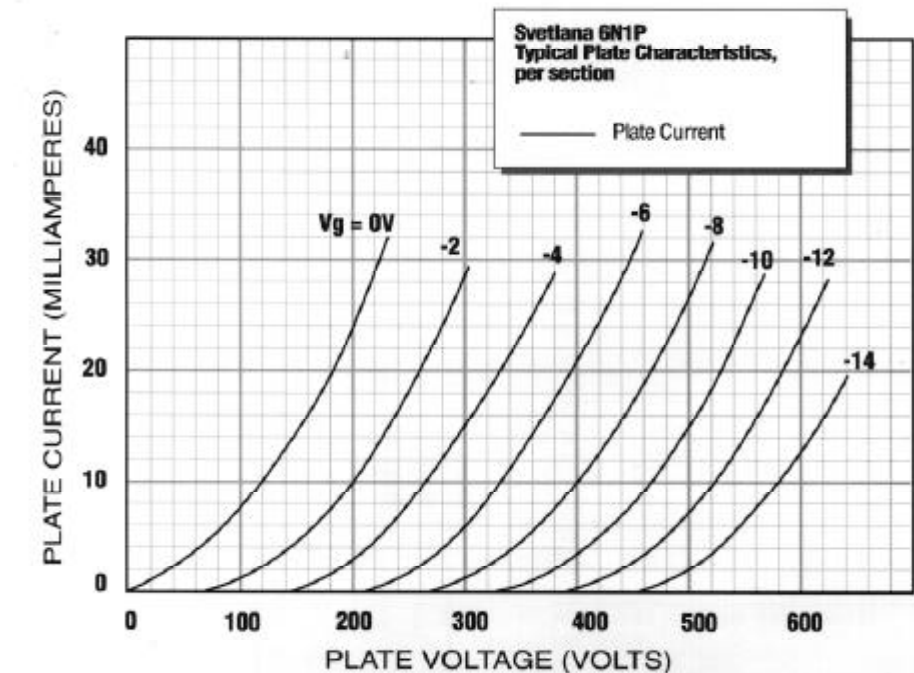The choice of tubes is cool - The driver is Svetlana's 6N1P, sister to the 6922, but with a bigger cathode and vastly reduced microphony. In fact we like the tube so well we are using it in a new prototype parafeed line stage here at Rancho Tonalities. The SV83 output tube is a sister to the 6BQ5, which any triode guy will tell you is the



best sounding pentode made.

The circuit is as simple as possible, the only adjustment being a choice of cathode resistance on the straightforward voltage amp driver stage. The output stage is operated in triode mode with a 1K resistor tying the screen to the plate.

The simplicity of the circuit makes the C4S installation easy. The 6N1P is set up to run at a plate voltage of 156VDC with a cathode bias of 4.3VDC and a cathode resistance of 2.7K, or a plate voltage of about 104VDC, cathode bias of 2.3VDC and a cathode resistance of 964 ohms.

The first operating point gives us a plate current of 1.6 mA, and the second operating point gives us a plate current of 2.4mA.

## Version 1

Looking at the curves published by Svetlana for this tube, these are really kind of low operating points. I'll do a conversion sticking with a low 2.4mA current first, and using the curves I'll shoot for an op point of about 110VDC on the plate and 2VDC of cathode bias.

The SV83 grid is biased only 10V or so, so

the voltage swing requirements for the 6N1P are minimal.

To hit our numbers means replacing the 2.7K and 1.5K resistors with a single 833 ohm (820 is a common value that would be close enough) 1/4W resistor on each cathode.

Our C4S's R1, the current set resistor, will need to be .95V 0.0024A, or 396 ohms 1/4W (390 is close enough).


To set the bias resistors we will need to go back upstream in the circuit and figure out what our voltage should be at the top of the C4S loads and how to make it so.

At point b in the power supply schemo we know we have a pretty stable 260 VDC or just a few volts less available.


We will have a total draw of 6.8mA from our new circuit, 4.8 mA total thru the two plates and 2 mA total thru the bias diodes of the two C4Ss.

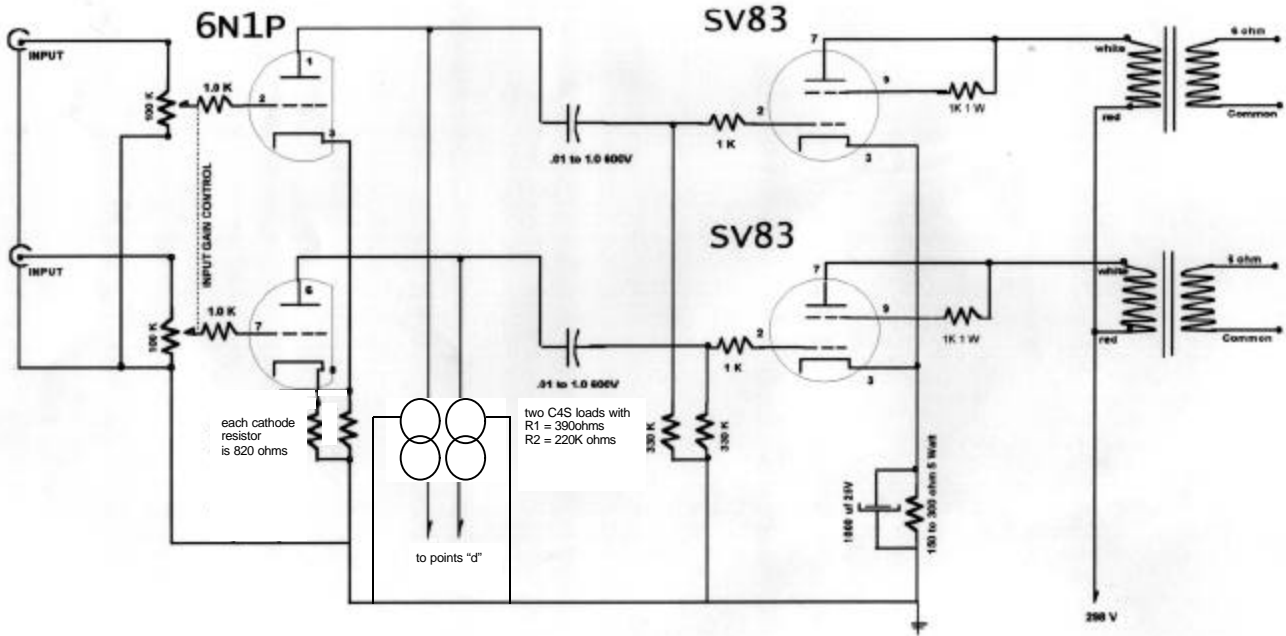The 15K and 10K resistor in parallel between points b and c equal a 6K resistor. The drop across this puppy at 6.8 mA would be 22.8V, so let's say we would have around 256 - 22.8= 233VDC available at point c. The actual value may vary a bit but this is close enough for jazz.






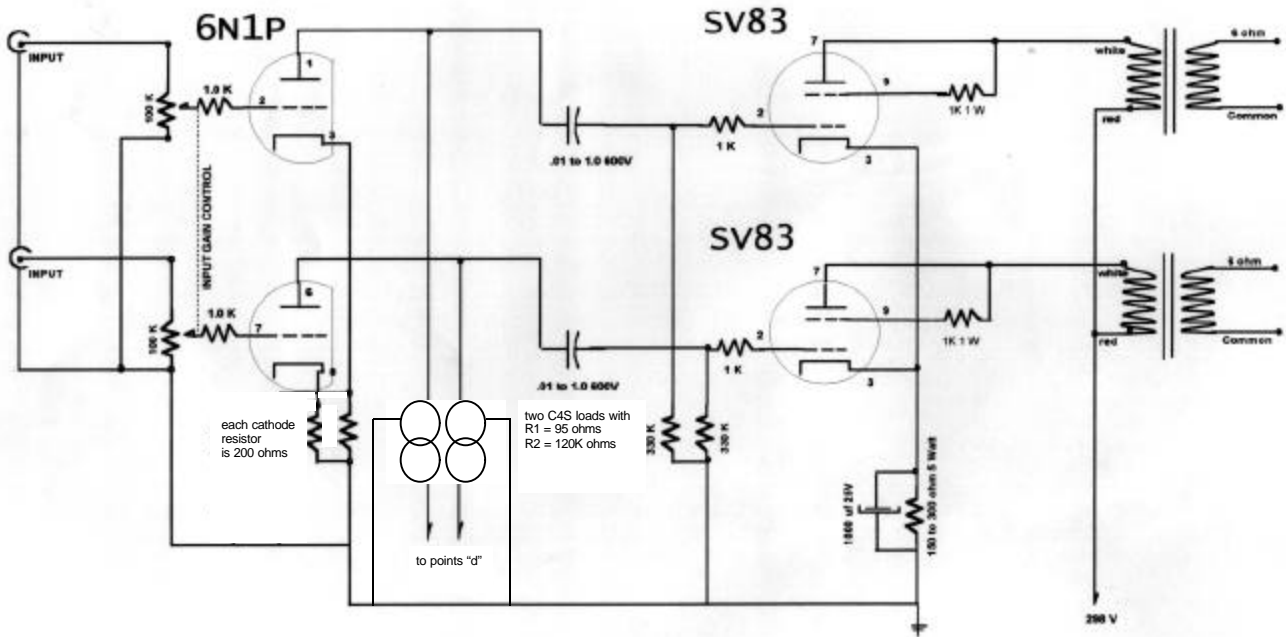**SE84B Zen Amp with C4S active loads**  
version 1



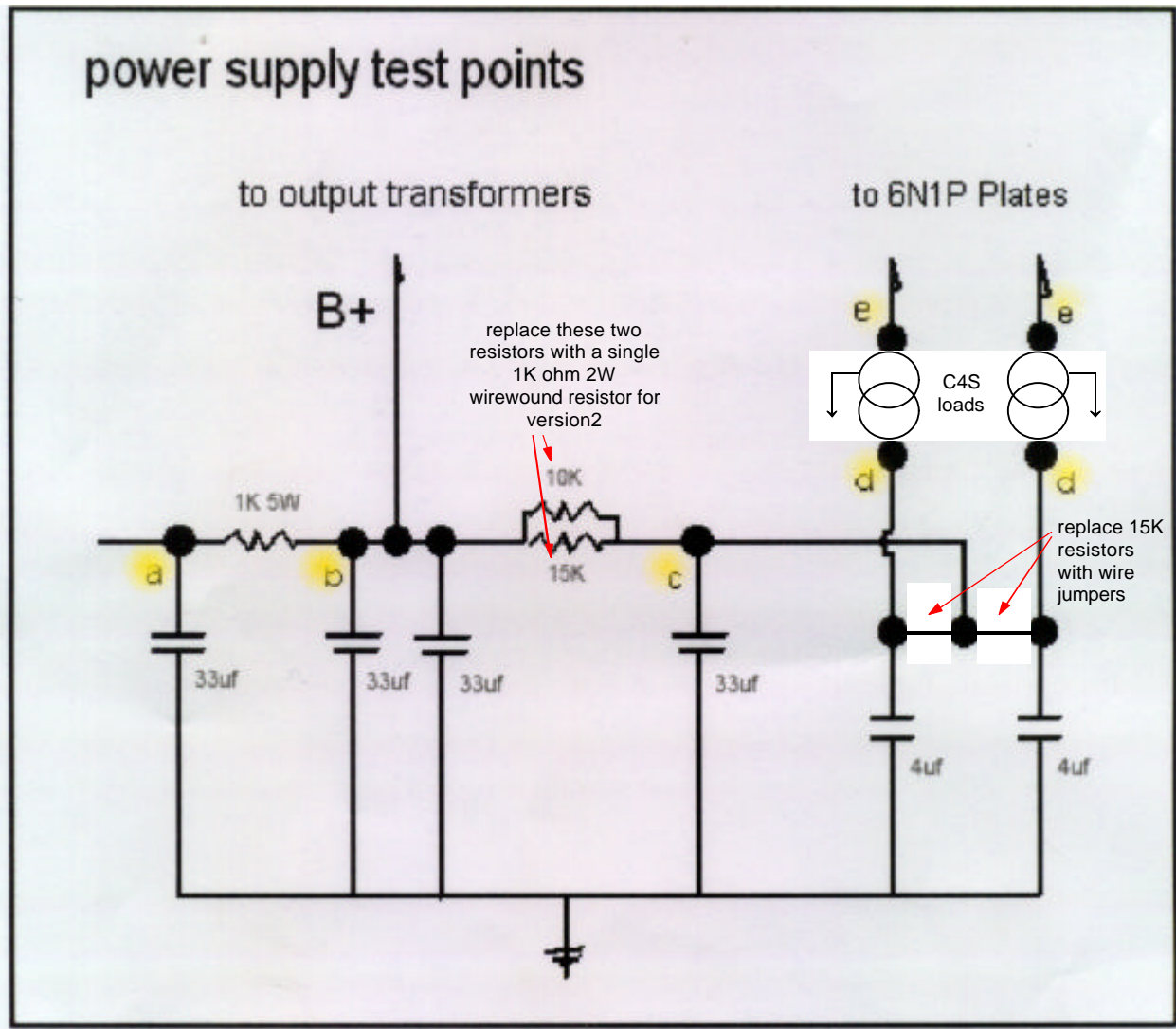**SE84B Zen Amp with C4S active loads**  
version 2



Now we calculate our bias resistors R2 on our C4Ss as  $233V / .001mA = 233K$  ohms. A 220K 1/2watt resistor will do. Substitute wire jumpers for the 15K resistors between points c and d. The C4S loads replace the 47K plate loading resistors between points d and e, obviously...

### Version 2

For a higher current version that will have the 6N1P running at a point we like in other circuits we use, let's shoot for 10 mA at 200V as an operating point for our 6N1P. The SV83s draw a maximum of 66 mA total, so the total draw of two SV83s and the two halves of the 6N1P running with C4Ss will be  $66 + 20 + 4 = 90$  mA, well within the maximum 150 mA current rating of the Hammond 372-FX power trans.

R1, the current set resistor on the C4S board, will need to be  $.95V / .01A = 5$

ohms.

The cathode bias on the 6N1P halves will need to be 2V, so we need a cathode resistor on each triode of  $2V / .01 mA = 200$  ohms.

Let's bump the LED's current draw up to 2 mA. We already figured our current draw by the 6N1P halves and C4Ss to be 24 mA. The voltage drop across that 10K and 15K resistor from point b to point c would now be 144V, way too much!

No sweat, let's just change the 10K and 15K resistors in our previously modified power supply (modified by the jumpers replacing the 15K resistors at points c and d) to a single 1K 2W WW resistor. This would give us 24V of drop, and our voltage at the top of the C4S loads should be about  $260 - 24 = 236$  V. This is just enough plate to source compliance for our C4S load to work, and remember, we only need about

10V of drive for the grid of the SV83.

We can now compute the value for R2. With 236V available at the top of the load and a 2mA current through the LEDs we need a  $236V / .002A = 118K$  resistor rated for 1 watt. 120K is plenty close.

What else can you do?

### Parafeed it, Baybee

Disconnect the secondaries of the existing output transformers, and cap couple a suitable PA matching type transformer, ala ParaS.E.X., to the plates of the SV83. Try a 2-3mfd coupling cap.

The plate resistance of the SV83 may be a bit high with respect to the inductance of the Zen output-trannie-now-plate choke, so you may not get much sub 30 Hz bass, but there's only one way to find out, and it would be a cheap experiment..... B.

# da' basics

Ohm's law -  
the most important formula you'll need

If you can remember this one, you can figure about 80% of the math out in a given circuit design. Ready?

$$V=IR$$

where V= Voltage  
I= Current  
R= Resistance

How about some applications, you say? OK, here s one:

You need to calculate the value of a cathode resistor for a 2A3 self biased at 43 Volts and drawing 60 mA of current.

We use our junior high algebra and rearrange Ohm's law to read

$$V/I=R$$

Substituting 43 Volts for V and .060A (that s the same as 60 mA, get it?) for I we get

$$43V/.06A=R$$

which equals about 717 ohms.

Now a nice feature of Ohm's Law is that we can relate power to it with the following formula

$$P=VI$$

where P = power and the other variables keep the same definitons.

With this information we can calculate what kind of power rating our 2A3 cathode resistor needs. We know V = 43 Volts and I = .06A, so we can find P by substituting

$$P= 43V \times .06A$$

which equals 2.58 Watts.

By the way a good rule of thumb is that you want the power rating of a resistor to be at least twice ( the conservative say four times) the power radiated by the resistor. In this case you would want to use a 5 watt resistor at the very least, and a 10 watt resistor would be safer.

There may be cases where you are working on a design and don't have one or the other of V or I through a given component, but you know the value of the resistor. You can still calculate the power rating.

Since we know that  $V=IR$ , and hence  $I=V/R$  and we can substitute for I in our power formula:

$$P=VI=V \times V/R=V^2/R$$

$$\text{or } P=IR \times I=I^2R$$

Cool, huh.


Estimated voltage at rated current  
2.66 + 2.66v  
6.13 v  
343-0-343 v\*

\* the high voltage winding was estimated on the basis of 60mA RMS through the whole secondary, which is a reasonable approximation for capacitor-input circuits but is not exact. Leakage inductance was not evaluated but may reduce the B+ output voltage slightly.

Equivalent source resistance in the B+ is about 267 ohms, or about 4% of the likely load resistance. With a capacitor-input filter and using silicon diodes, a maximum of 445 volts could be generated at 60mA. Remember however to allow for the drop in the DC resistance of any filter choke used, plus the loss in the rectifier tube if used. With a choke-input filter an output of 305 volts at 90mA could probably be obtained without excess heating, again minus the losses in chokes and rectifiers.

Unusual in smaller power transformers, the regulation is pretty good. You can probably draw more B+ current if the filament windings are not fully utilized, but no more than half the extra volt-amp capability can be used this way without excess heating.

## Brainiac's

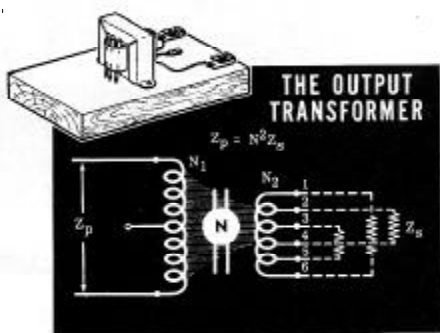

## Heavy Metal

...an occasional review of some nifty chunk of iron (usually cheap!)

by Paul Joppa

Today's Topic:

*the De Young Mfg. S.E.X. kit  
"universal" power transformer*

This is the transformer supplied with the S.E.X. kit for international orders. It differs from the U.S. version in having more primary windings so it can be wired for several power line voltages, it is rated for 50 or 60 Hz operation, and it has less B+ current capability than the Magnequest unit offered for the domestic market. It weighs about 3.5 pounds on my kitchen scale, and the lamination stack is 3 x 2.5 x 1.5 . The laminations are moderate, about 0.01 , and they are interleaved one by one. It is mounted horizontally with an upper metal end bell, and takes mounting holes 2 x 2.5 . All the wires come out on the bottom.

The primary can be wired for 100, 120, or 240 volts and measures 7.1 ohms DC wired for 120 volts. There are four secondaries. The ratings and my measurements are as follows:

Rated voltage	Rated current
2 x 2.5v	2 x 1.25A
6.3vCT	2A
350-0-350v	60mADC

Open circuit voltage	DC resistance
2.90 + 2.90v	0.12 + 0.12 ohms
6.67v	0.17 ohms
366-0-366v	404 ohms CT

**jc morrison smashes  
record for the worlds  
largest S.E.X. speaker...**

This is a photo of one of a pair of speakers constructed by jc morrison and demoed at nyNoise, a very cool show put on in Hoboken, NJ by jc and pal Blackie Pagano, which we attended on March 13. The speaker is a 9' tall open baffle with 18 of the drivers that Doc worked with MCM Electronics on a couple years back (PN 55-1870). The tweeter is a Raven (sounded very nice!). There was also a TAD based subwoofer with this system. The overall sensitivity was quoted as 100dB, and it sounded like it.

You long time bottleheads will note a basic resemblance to the open baffle S.E.X. speaker born from the unstable minds of Doc and Brainiac at the first VALVE Xmas party after several bottles of Champagne. If you want to take a project like this on, we might recommend that you try what is often called the "original S.E.X." drivers instead (PN 55-1290), With their high Q they are quite a bit more open baffle friendly, going lower on an open baffle (about 110 Hz vs. 200Hz for the drivers shown here) and a bit more efficient to boot. See our new Whamo webpages for lots more info.

Thanks to jc and Blackie for great hospitality and a fun show. We hope to twist their arms and get them to come to the next VSAC. Hey jc, will those things ship?



**now that looks dangerous**

All you gotta do to get bottleheads to look at the camera is say "beer".

Here's Smoothplate, John Hoffman, Brad Brooks (he's the one guy who's working), Tom Vetromile, Richard Riley and Brainiac in his disguise, hard at work on the new VALVE listening room. Those joists that Tucker's almost hitting his head on will come out, and if you look close you will see the new ones he put in at 9-1/2 feet. The room will finish out to about 19' x 11'.

We're planning on installing two layers of 1/2" sheetrock, and there's four hospital grade sockets on the front wall and one side wall, in case we audition speakers that like long walls, like Ariels.

Oh yeah, there'll be a small wine bar in the back corner too. Brainiac smiled very wide when I announced this...





Doc,

This is Joe from Australia. Thanks for the Foreplay Kit with the upgrades. I have received the package in December last year. Unfortunately, I was away in Malaysia for a couple months. So, I was able to finish the kit just a few weeks ago. Anyway, I have managed to build another deluxe version of the kit using better parts like the Hovland musicap, Holco, Kiwame resistors.

I have used VSE Allen Wright's voltage regulator together with the power supply of the Foreplay to provide the B+. Heater is also DC regulated as well. I have put the whole package in a Hammond Aluminium box with the valves sticking out proudly (see pic).

I have managed to have a power transformer custom wound for operating in 240V country. I went to Octave Electronics ([www.members.xoom.com/octave/](http://www.members.xoom.com/octave/)) in Malaysia and they did it for me at a reasonable price (works out to be about US\$27 / VA). So if someone from 240V territory



needs the service, I would recommend them.

Anyway, thanks again.

Regards,  
Joe Ling


**Time.  
Quality.  
Price.**

**Wouldn't you like  
to have it all?**

**Mission Statement**


*Our goal is to provide precise and cost effective P.C.B. design and development services for Industry, Engineers and Inventors. To provide these services on schedule and on budget, assuring total Satisfaction!*

*"When a project is handled by an individual, you get the results you want."*



Leo Lester

**Providing Quality P.C.B. Services Since 1983**



**Midland Technologies**

34374 East Frontage Road  
Bozeman, Montana 59715  
1-800-726-8871  
Fax: 406-586-0300  
E-Mail: [midtech@imt.net](mailto:midtech@imt.net)

**Printed Circuit Board Services**

**P.C.B. Design Layout**


- Ω Thru-Hole
- Ω Surface Mount Technology
- Ω Multi-Layer
- Ω Accel EDA Design Software

**Assembly**

- Ω Thru-Hole
- Ω Small Project Specialists
- Ω Kit or Turn-Key

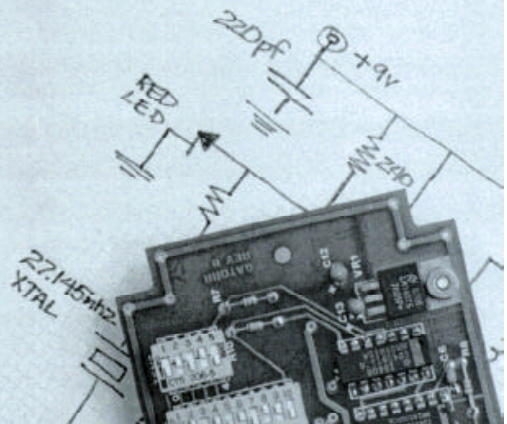**P.C.B. Fabrication**

- Ω In-House Development Prototype
- Ω 1 and 2 Layer
- Ω Plate-Thru Holes







# Entwined

*interconnect cable kits from Electronic Tonalities  
pre-cut twisted pair 20.5 gauge High purity continuous cast long crystal solid copper  
conductors with a high temperature insulative coating, pre-cut polyethylene outer jacket  
and Vampire Wire RCA plugs  
\$49 per 1 meter pair \$10 each additional meter*