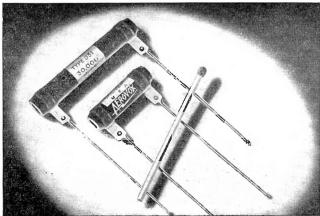


# SPACE-SAVERS




## PYROHM Jr. RESISTORS

NOT much larger than carbon resistors, these vitreous-enamel wire-wound units provide extra wattage rating in tight places. • Quality wire, refractory tubing. Wire ends brazed to lugs. Pigtails soldered to terminal bands. Permanent glazed coating. • In 5, 10, 15 and 20 watt sizes.


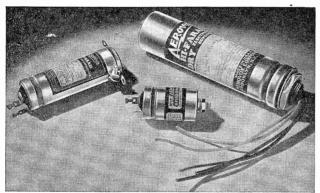
## GENERAL UTILITY ELECTROLYTICS

THESE popular PBS midges have proved that they can take it. Ultra compact in bulk but giants in useful service. • Electrolytic sections. Heavy cardboard case thoroughly impregnated and sealed. Flanges for ready mounting—tear off if not needed. Polarity coded pigtailed. • In 250 and 525 v. ratings. Standard capacities. Single, dual and triple capacities. Unit shown is 8-8 mfd, 525 v. • Prices are so low!




## MOLDED MICA CAPACITORS

DESPITE popular price, these units are intended for severe service such as transmitting circuits. Type shown especially desirable because of insulated mounting holes separate from terminals, permitting of stacking and connecting in any desired combination. Also insulated mounting on any metal support.


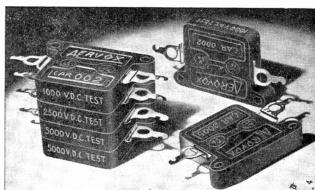
## METAL-CAN ELECTROLYTICS

FOR the most economical condenser service, nothing excels AEROVOX hermetically-sealed metal-can electrolytics. • Carefully selected section in metal can with edge rolled over into soft rubber gasket for perfect sealing. • No seepage, leakage, deterioration during longest service life. • These units are the cheapest in the final cost analysis.



Latest edition contains many new items of interest to you, no matter what your particular need may be. Also timely supplements with new listings.

## SEND FOR CATALOG



**AEROVOX CORPORATION**

70 WASHINGTON STREET, BROOKLYN, N. Y.

Sales Offices in All Principal Cities



H. HOOVER, H. HOOVER

The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenters, Engineers, and other authoritative first hand information on condensers and resistances for radio work.

# AEROVOX

## Research Worker

VOL. 8, NO. 6


JUNE, 1936

60c per year in U.S.A.  
60c per year in Canada
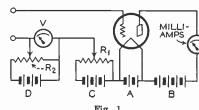
## Peak Voltages

By the Engineering Department, Aerovox Corporation

SOMETIMES it happens that condensers in a certain circuit keep burning out for no apparent reason. A d.c. voltmeter placed across the condenser shows that the potential is well below the normal peak rating. The answer may be that there are alternating voltages, not shown by the meter, which subject the condenser to potentials above the maximum allowable limit. In addition, continually recurring peaks of this nature there may be occasional peaks due to surges in the line or sometimes when switching the apparatus "on" or "off".




A typical example of a condenser subject to such peaks is the filter condenser in a power pack. Blocking condensers in an output stage have an alternating voltage super-imposed on the direct voltage. So instead of being subjected to 200 or 300 volts, the potential across such a condenser may vary between 50 and 500 volts. When a receiver is not operating properly it may be that the power supply will cause abnormally high peak voltages.

The question is now how to test for the condition and how to measure the voltage across a suspected condenser.

There is, of course, the cathode-ray tube and its associated sweep circuit which will enable the user to observe wave shapes and to measure voltages. However, it can be done with rather simple and inexpensive apparatus.

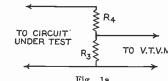A modification of the above circuit, which is better adapted for the measurement of high peak voltages, is shown in Figure 3. Here the unknown voltage is applied to the anode while the grid is tied to the cathode. As before, with the input terminals closed, first adjust the slider S1 for the lowest current which the milliammeter can show. Then adjust slider S2 far enough towards the right to



safeguard the meter, apply the unknown voltage and adjust the slider S2 for the same low current as before. The voltmeter shows the peak voltage. If the peak voltage is too great, the voltage divider of Figure 1a may be again used. The value of R3 and R4 must be very high so as not to draw any appreciable power from the circuit under test.

Another type of peak voltmeter consists of a half-wave rectifier, a large condenser and a very high resistance with a microammeter. The circuit is shown in Figure 4. If the resistance across the condenser is very high the current through it will be very low and the condenser will charge up to the

**AEROVOX PRODUCTS ARE BUILT BETTER**

Printed in U. S. A.

Copyright 1936 by Aerovox Corporation

peak voltage of the circuit under test very nearly. The recommended values in Figure 4 would provide a peak voltmeter with a full scale indication of 1000 volts. The tube can be any of the usual rectifiers though some triodes can be employed by connecting grid and plate together.


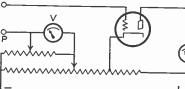


Fig. 2  
cation of 1000 volts. The tube can be any of the usual rectifiers though some triodes can be employed by connecting grid and plate together.
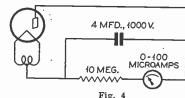
## Methods of Phase Inversion

Phase inversion consists of obtaining the input for a push-pull stage from a single-ended stage by resistance coupled circuits and without the use of a push-pull input-transformer.



The chief reason is the fact that the phase inverter is a relatively simple and inexpensive arrangement which could not be equalled unless a transformer of excellent quality and consequently high price were used. While a phase inverter can be designed as a phase inverter can be made to deliver two signal voltages exactly 180 degrees out of phase and of equal amplitude. Moreover there need not be any frequency distortion and phase shifts can be reduced to a negligible amount.

First let us consider a circuit which has been used in the past but which is now more or less out of date. Figure 5 shows the output stage of an amplifier which is intended to be accomplished by the output tube A. The signal voltage in the plate circuit of a tube is opposite in phase to that in the grid circuit. The grid voltage becomes negative (more less negative) the plate current increases, and the voltage drop across the plate load increases making the plate voltage lower. Thus, so when the grid voltage is positive, the plate current is a resistor, but when the grid voltage is negative as in the case of Figure 5, the voltage drop across the load is not in phase with the current through it and consequently the plate and grid circuits do not have signal voltages in exact opposite phase.

When using any of these instruments it is important to observe the maximum peak voltage obtainable on the d.c. voltage across a condenser might be 400 while the continuous peaks—those recurring each cycle—are 440 volts. Then the moment the set is turned on the peaks may rise to over 500 volts. Sometimes these occasional peaks are so great that when the set has come up to temperature while in some cases they are easily overlooked when the set is turned on after it has cooled. These things have to be taken into consideration. The peak voltage has to be observed when turning on the set, then they have to be measured again while the apparatus is in normal opera-

tion, finally another measurement has to be made of peaks occurring when the set is heated, turned off and on again.

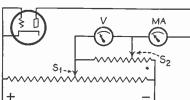


Fig. 3  
It is felt that readers will be amply repaid when making one of the described testing instruments.

The second requirement, that of equal amplitudes can be met by employing a voltage divider with the proper ratio so as to supply to tube B the same voltage as was applied to tube A.

The system of Figure 5 thus suffers from a phase shift which results in some distortion and in the inability to obtain full output.

The next step obviously leads to a circuit with a resistance load which would remove the above objection.

There are several variations of this but they are really all the same. Figure 6 shows the same idea in Europe. It accomplishes the same thing as Figure 5 but the load is resistive therefore the signal voltages in plate and grid circuits are opposite in phase.

There is of course no gain provided by the tube. It delivers a voltage equal to e and in opposite phase but there is no amplification. Some consider that the gain equals 2.

In Figure 7 is shown the American version of the same idea. It is a resistance-coupled stage ahead of it. A double triode is often used but there is no objection to employing two different triodes. The gain of the two tubes must be considered since the gain of one, in other words, the phase inversion tube again has a gain of 2. Otherwise this circuit has the same characteristics and drawbacks as the one in Figure 6.


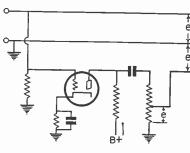


Fig. 6  
In a radio receiver employing a diode detector it is possible to obtain perfect inversion in the detector cir-

cuit. This arrangement is illustrated in Figure 8. The load resistor of the diode circuit is simply divided into two equal parts and the center is grounded. Each of the sections has to

be an experimenter has burned the midnight oil trying to make the circuit of Figure 9 suitable for an input device. There is no original tube. Ae must be less than e if there is going to be something left over; then A is less than unit and Aa must be less than 2. The actual value of A is somewhere around .8 to .9 depending on the mu of the tube and the design of the circuit. The fact that the tube does not deliver any gain is really not important. It can be considered as a replacement for a push-pull transformer. Since there is no reactance in the plate load or in the grid circuit there is no frequency discrimination.

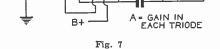

be filtered individually. The circuit delivers two signals which are exactly 180 degrees out of phase and which are equal if the resistors are equal. There are no other electrical characteristics which may upset the balance later. However, if it is necessary to control volume in the same circuit a tandem volume control will be used. It will be very difficult to find two volume controls which will always be equivalent at all positions of the moving arm.

This difficulty is overcome in the circuit of Figure 9. The inversion in this case is not obtained directly in the first audio stage. It depends on the following principle: The signal voltage across a resistor in the plate circuit of a tube is out of phase with the signal voltage across the grid. If the plate load is placed in the cathode circuit, the voltage drop across it will be in phase with the input signal. Then, if it is possible to couple the signal equally between the plate circuit and the cathode circuit, the two sides of the push-pull signal can be obtained. The two signals must be summed. The two signals are equal and they are exactly opposite in phase because both sides will have the same number of condensers.

The fly in the ointment is that such an arrangement requires the input circuit to be insulated from ground because the grid voltage is at zero potential and goes up and down with the signal. This is no objection in the case of the diode detector of a superheterodyne since the secondary can be coupled from the front end. Figure 9 shows how it is connected. The bias can be obtained by means of a small battery or it may be supplied by the voltage drop across a portion of the plate load. This portion must then be bypassed by a high-capacity electrolytic condenser. It does not count as a part of the plate load and it must be equal to the required bias and it is not a part of the cathode load. The volume control in this case can be at the same time the load of the diode tube.

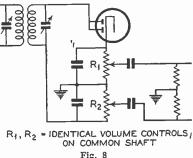


Fig. 8

The circuit of Figure 10 is due to Richter (Electronics for October 1935). The tube is a 76, R1 and R2 are the two equal load resistances. Since the diode is operating properly there will be a voltage drop of 70 volts across the cathode resistor R2. The required bias is 8 volts. The grid circuit need not remain constant since the diode which is 8 volts negative with respect to the cathode. This point is 62 volts positive with respect to ground. The voltage drop must be bypassed across the condenser C1 might be .1 mfd. paper but C2 should be a high capacity electrolytic condenser.


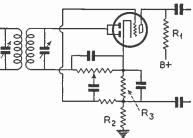


Fig. 9


It was explained before that this arrangement insures the two halves of the signal to be equal and exactly opposite in phase. It is not affected by changes in the plate voltage or by changes in the characteristics of the tube.

The total gain obtainable from a stage like this is less than 2. It is obvious that any voltage, e, applied to the grid circuit appears multiplied in the diode circuit and would have a value of Ae volts. Another signal of Ae volts is developed across the plate load R1. The total gain is then 2A. The next question is, how large is A.

Whatever voltage is developed across the cathode resistor, R2, is again applied to the grid in a direction so as to pull down the original voltage. Ae must be less than e if there is going to be something left over; then A is less than unit and Aa must be less than 2. The actual value of A is somewhere around .8 to .9 depending on the mu of the tube and the design of the circuit. The fact that the tube does not deliver any gain is really not important. It can be considered as a replacement for a push-pull transformer. Since there is no reactance in the plate load or in the grid circuit there is no frequency discrimination.

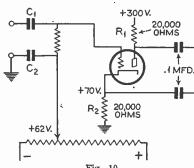

Another way of accomplishing the same result is shown in Figure 11. The equal load resistances are the combination of R1 in the plate circuit and R3 and R4 in the cathode circuit. These have been selected so that their combined effect is equal to R1. R2 is of the proper size to obtain the required bias. R2 is in parallel with R1 as far as the signal is concerned, is very much larger than R4. The equivalent resistance of R3 and R4 in parallel is much smaller than R1. The condenser C2 is again very large so that its impedance is nearly zero for alternating currents. It will be seen that the grid bias is the potential at the junction of R2, R3 and R4 and that it is being kept constant due to the resistance-capacity filter R3-C2. The circuit has the same degeneration effects as the one in Figure 10; the gain is less than 2.

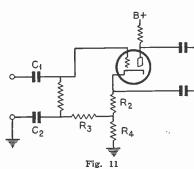

It is recommended to use triodes only for the purpose of inversion since the screen supply of tetrodes or pentodes would offer another problem.