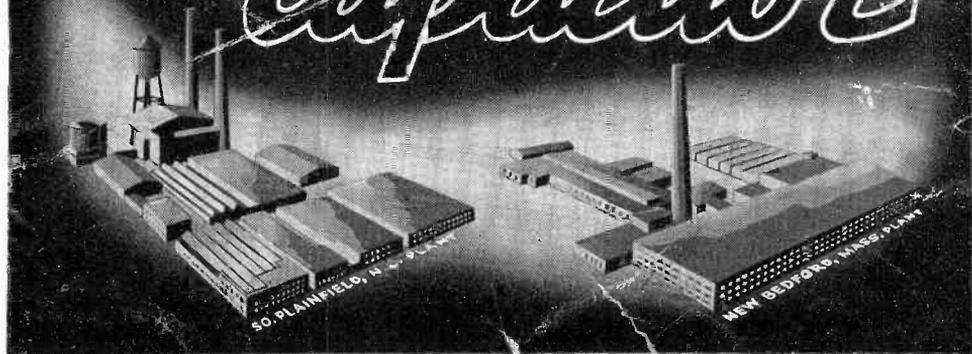


The CORNELL-DUBILIER Capacitor



Vol. 8

DECEMBER, 1943

No. 11

CORNELL-DUBILIER ELECTRIC CORP.
HAMILTON BOULEVARD
SOUTH PLAINFIELD, N. J.

Sec. 562, P. L.&R.
U. S. POSTAGE
PAID
So. Plainfield, N. J.
Permit No. 1

FOR VICTORY



**BUY
UNITED
STATES
WAR
BONDS
AND
STAMPS**

Mr. W. J. Morrice
21 St.
Milwaukee, Wis.

COMPENSATING TONE IN CRYSTAL PICKUPS*


Crystal phono pickups have a wide range of frequency response characteristics that are not always matched to the amplifier with which they are used. Certain compensation in the overall response can improve the performance.

In the accompanying diagrams three simple resistance-capacity compensating networks are shown. In circuit 1 the part values can be adjusted to change the response at both high and low frequencies. The shunt resistance R_1 controls the response at low frequencies and reducing its value will reduce the response. Since the crystal pickup is equivalent to a generator with an internal capacity reactance that increases as frequency increases, the voltage appearing across R_1 will be largest at low frequencies if the resistance is high. Usual values in this position are 250M to 1 meg or more. The capacitor C_1 paralleled by resistor R_2 and the resistor R_3 form a voltage divider for the output. The ratio of R_3 to $R_2 + R_3$ determines the output. The capacity of C_1 will determine the high frequency response. Making C_1 larger will improve the gain at high frequencies. R_2 can be about 100M to 500M, C_1 250 mmfd. to 1000 mmfd., R_3 1 to 5 megs. R_3 could conveniently be a potentiometer for volume control. Connect the arm and lower terminal to input of amplifier.

In circuit 2, increasing R_1 will increase the low frequency response, while increasing R_2 will increase high frequency response. The size of the

capacity C_1 regulates the output as well as the high frequency response if R_2 is low.

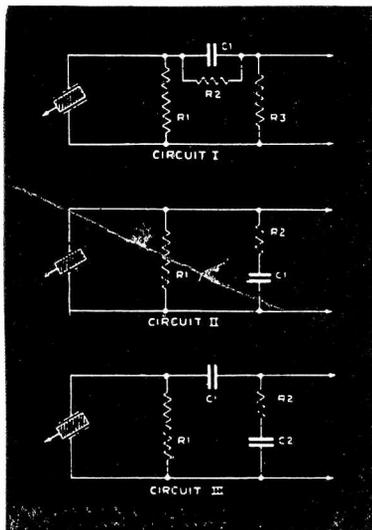In circuit 3 R_1 controls the low frequency response as in the other two circuits. Increasing R_2 increases the



R-C networks described at left.

high frequency response, and increasing C_1 with respect to the sum of $C_1 + C_2$ will increase the output.

Any of the resistors may be made variable or several values of capacitors can be selected with a switch as a form of tone control. A control of the high frequencies is desirable in phono reproduction since it allows effective control of the scratch noise which is objectionable in some records.

* By courtesy "Radio Today."



A Free Market-Place for Buyers, Sellers, and Swappers.

These advertisements are listed FREE of charge to C-D readers so that there is anything you would like to buy or sell; if you wish to obtain a position or if you have a position to offer to C-D readers just send in your ad.

These columns are open only to those who have a legitimate, WANTED, SELL or SWAP proposition to offer. The Cornell-Dubilier Electric Corp. reserves the right to edit advertisements submitted, and to refuse to run any which may be considered unsuitable. We shall endeavor to restrict the ads to legitimate offers but cannot assume any responsibility for the transactions involved.

Please limit your ad to a maximum of 40 words, including name and address. Advertisements will be run as promptly as space limitations permit.

FOR SALE — Parts from KW transmitter. Send for list. Want good SW receiver, state price. Will consider swaps. Nelson K. Stover, 1357 Hill St., York, Pa.

WANTED — Rider's vol. 3, 5, and 9. Also VOM including vacuum tube voltmeter. State make, condition, and lowest price. O. Sandman, 227 S. Pearl St., Havana, Ill.

WANTED — Any late model tube testers, signal generators, VOM meters. Send make, model, and price. Cash waiting. Beacon Radio Distributors, 703 Varick St., Utica, N. Y.

FOR SALE — Hickok RFO5 3" scope, \$173; also dictograph with equipment \$150. Write, do not call. Prices F.O.B. New York. Sterling Electronic Lab., 521 W. 131st St., New York, N. Y.

WANTED — Weston A.C. Voltmeter model 155. Wm. P. Sommers, 909 E. Main St., Knoxville, Ill.

FOR SALE — Radio books and manuals. Write for list. E. L. Reton, R. 1, Adrian, Mich.

WANTED — All of Rider's Manuals in good condition; also vacuum tube voltmeter and other Rider books and Radio Craft magazines. Radio Electric Service, Lemongrove, Calif.

WANTED — Weston analyzer model 772. State price and condition. J. E. McManus, Thornton, Ark.

WANTED — RCA signalyst. State condition and price. Fox Radio Service, 435 S. 5th St., Richmond, Ind.

FOR SALE — Lionel, standard gauge, freight train set in excellent condition, with many accessories. Make offer. W. Bickmeyer, 31 Azalia Ct., Hempstead, N. Y.

FOR SALE — "Dependable" tube checker; also old style tubes. Acme Radio Co., 189 Valley St., N. Tarrytown, N. Y.

WANTED — Morris coil winder with instruction sheet. Must be complete. State price. Acme Radio Co., 189 Valley St., N. Tarrytown, N. Y.

WANTED — All kinds of radio equipment, tools and magazines. Quote what you have to sell and best cash prices. H. B. Howell, Anna, Tex.

FOR SALE — Hanovia Alps sun lamp in perfect condition, \$85; or will swap for Meissner analyst. J. Lipiner, 1032 Hutland Road, Brooklyn 12, N. Y.

FOR SALE — SW receiver and 6 watt amplifier \$35; or will swap for Precision E200 signal generator. J. Lipiner, 1032 Hutland Road, Brooklyn 12, N. Y.

SALE OR TRADE — Guns and sporting equipment; G. E. dynamotor 24/1500 volt; 30 watt amplifier; battery radios; small motors. Want Barometer; hand-book of photography, Henney & Dudley; mech.-engrs. handbook by Marks; Eyemo or Film cameras. Wm. Hansen, R. 3, Niles, Mich.

WANTED — All-wave or communications table type radio set which includes B.C. band. Please give model, complete description and price. Cash. Mosier Radio Service, 313 Mamaroneck Ave., Mamaroneck, N. Y.

FOR SALE OR SWAP — Set of accounting books (6 vols.) \$10, or trade for pocket VOM, ohmmeter, slide rule, meters, or radio equipment. Joseph Miller, 515 Melish Ave., Apt. 20, Cincinnati 29, Ohio.

WANTED — Precision E-200 signal generator, must be in A-1 condition. Will pay cash. Describe condition, serial number, date of purchase and price desired in first letter. J. Lipiner, 1032 Rutland Road, Brooklyn 12, N. Y.

WANTED — RCA Bound volume service manuals 1937, 1939, 1941, 1942. Also need 2 each 50Z7-G and 50Y6-G or GT tubes. Prefer new tubes in cartons. Will pay cash or what do you need? North Side Radio Service, 652 E. 19th St., Indianapolis, Ind.

WANTED — Precision E-200 signal generator from party residing around New York City. State condition and price. George Cannova, 40-13 Union St., Flushing, L. I.

FOR SALE — Volumes 1, 2, 4, 6, and 7 of Gernsbacks official radio service manuals. These 5 manuals contain a total of over 4,000 pages. Herman Yellin, 351 New Lots Ave., Brooklyn 7, N. Y.

WILL BUY 8 mm camera and projector. Must be in good condition. Also want record players and changers, with or without cases. Must be perfect. L. Stein, 114 East 3rd St. Mt. Vernon, N. Y.

WANTED — Pocket multimeter, Precision Supreme, Triplett, or any good make in excellent condition. Have for sale Triplett vibrator tester model 1671 and Philco Dynamic tester model 030, both in good condition. Royce Saxton's Radio Shop, Route 1, Pontiac, Ill.

WANTED — Supreme Analyzer model 585. Riders Manuals 1 to 8, oscillators, and Philco model 17, 16B, and 16X chassis and speaker. Louis A. Goldstone, 1279 Sheridan Ave., Bronx, N. Y.

WANTED — Good home recorder of standard make. Have Confidence tube tester for sale, can be brought to date easily, have all necessary parts. Booth Music Store, Lamar, Colo.

SELL OR SWAP — Westinghouse 5 tube radio, Columbia SGB, Knight 6 tube, all wave, 6 volt battery radio, 1 Utah 10" DC or AC field speaker, 1 Newcomb-Hawley 10" AC or DC field speaker, and 3 auto speakers. Want Superior model 1280 set tester, Radio City model 802 tube and set tester, or Supreme model 599 all purpose instrument or what have you. A. E. Haseman, Beecher, Ill.

WANTED — Meissner high fidelity PA tuner, radio books by John F. Rider, radio operating questions and answers by Nilson and Hornung. State price and condition. Edward E. Materski, 1950 Trowbridge St., Hamtramck 12, Mich.

WANTED — Tubes in any quantity. State price, kind and quantity. Will also purchase portable analyzers and meters. Must be in perfect working order (any make) no homemade jobs. Leading Radio Service, 114 East Third St., Mount Vernon, N. Y.

WANTED — Any quantity of used or new midget radios and table model phono combinations with or without cabinets. Please give make, model, and condition in first letter. Leo Stein, 7 Monroe St., Mount Vernon, N. Y.

FOR SALE — Multimeter and signal generator, chanalyzer, tube tester, and sound projector amplifier. Want Riders manuals. Central Film, Hastings, Mich.

WANTED — Voltohmmist, audolyzer, vedolyzer, 3" scope, and Riders manuals. R. Robleski, Hastings, Mich.

WANTED — Any good 2 or 3 inch oscilloscope. State price and condition. Geo. Miller, 520 W. 124th St., New York City 27, N. Y.

FOR SALE OR TRADE — SX25 like new, Stancor P20 trans. New Imperial tube tester model 200, model 310 tube tester series 3 and 4 Radio City Prod. Clough Brengle signal generator model OCA, still projector model F 200 watt, 4 inch focus. Gerald Hess, Moravia, N. Y.

WANTED — Tube tester in good condition. Swap \$200 RTI radio course or what? W. B. O'Brien, c-o D. Shannon, R. R. 1, Gladstone, Mich.

WANTED — Meissner signal booster (9-1031); Meissner Traffic Master (10-1174); Meissner 3 tube receiver (10-1163) or (10-1193) prefer ac-dc type; Meissner 7 tube long wave (10-1111) or other long wave receiver. L. C. Chapman, Rt. 1, Columbus, Miss.

FOR SALE — Misc. items such as meters, transformers, tubes, kino-lamps, PE cells, etc., also sound picture text books. Send for list of items interested in. J. J. Cermak, 1928 Grove Ave., Berwyn, Ill.

WANTED — Will pay cash for electric phono motor suitable for use with a PA system for portable use. Must be for 110-115 volt 60 cycle AC 78 RPM. State make, model, condition and price. No junk. George Keefe, 4937 Chancellor St., Philadelphia 39, Pa.

SELL OR SWAP — Weston model 301 DC milliammeters, voltmeters, ammeters. Readrite model 430 tube tester, Weston model 506 DC milliammeters 0-100, 0-200. Want Riders manuals vol. 8 to 13; also condenser tester. C. F. McCracken, Hughes Park, Bridgeport, Pa.

FOR SALE — Sound equipment, test equipment, radio parts. Send for list. Fox Sound Equipment Co., 435 South Fifth St., Richmond, Ind.

FOR SALE OR SWAP — 1 pair 110 volt motors with gear boxes and turntable mounts, geared for 33-1/3 RPM. Ideal for non-sync. table. Handle 15" records. Good condition. Make offer or what have you? J. L. Demann, 1346 Woodbine St. Pittsburgh 1, Pa.

SALE OR TRADE — Sprague Telomike, "Radio Service" neon sign, 4" letters, Weston 772 with analyzer cable and adapters. Want good signal generator. Samuel Hornick, 8707 12th St., Detroit, Mich.

FOR SALE — New Philco parts in original cartons; also tubes. C. E. Ranniger, Gowrie, Iowa.

WANTED — Used 3525 and 50L6 tubes, galvanometer, midjet sets any condition, Treasure Finder circuits and parts, 5-9 inch foundation meter, electric drill, long nose pliers, cotton covered magnet wire, meters, etc., or what have you? Ponce de Leon Radio Service, 463 Ponce de Leon Ave., Atlanta, Ga.

WANTED — C-D capacitor analyzer BF-50 or Solar CB model condenser analyzer. A Solar "Quick-Check" model QCA 1-60. Will pay cash. Let me know what you have in good condition. Clyde W. Wimer, R. D. 2, Ellwood City, Pa.

WANTED — Signal generator and Riders manuals 10, 12, and 13. Will pay good price. J. B. Mosley, 1426 North 24th St., Birmingham, Ala.

FOR SALE — 2 PA trumpets, 9-lb. P-M units, 1 steel and 1 aluminum University L H reflex horns, 25" bell, 21" long. Acoustic length 4 1/2 ft., rubber rims, 1 crowsfoot bracket, 1 U bracket, 16 ohm V.C. Used very little. In perfect condition. Extra voice coil and diaphragm assembly. 1 extra crowsfoot bracket. \$95 F.O.B. Half cash, balance C.O.D. M. A. Porter, 1713 Larrabee St., Chicago, Ill.

FOR SALE OR TRADE — Triplett model 1213, 16.2 and Superior model 1240 tube tester in good condition, takes all tubes. Clough Brengle model OC test oscillator 60 k.c. to 30 m.c. in good condition. Riders Manuals 1 to 13 inclusive like new. Want Riders chanalyt, Volt-ohm-Ma similar to Triplett 666 in good condition. Radio Service, Unionville, Mo.

WANTED — Condenser bridge or tester. C-D BN bridge preferred. Could also use a good tube tester. State condition and price. Will pay cash. Abel Gomes, 8 Duke St., Ludlow, Mass.

WILL TRADE — FBXA with two sets of coils no power supply. Want phonograph motor, crystal pickup, 0-1 milliammeter, tools, test equipment, or what have you? R. W. Sederholm, Box B, St. Cloud, Minn.

WANTED — Thordarson transformers of various types and sizes, both receiving and transmitting. Also late model, high quality, test instruments. Please send list stating condition and lowest cash prices. The Radio Man, Box 183, Victory Center Station, N. Hollywood, Calif.

FOR SALE — Weston Therm-Galvanometer model 425 5.2 ohms 1-115 M-A. Also 1 Weston 01 M-A meter. J. B. Mosley, 1426 North 24th St., Birmingham, Ala.

FOR SALE OR EXCHANGE — Philco tube tester, model 050, signal generator, Supreme 561 or Hickok 188x or the equivalent. Frank Grinnell, 26 Queen Street, Milton, Pa.

WANTED — Typewriter portable preferred; 12 or 15 ga. slide action shotgun; welding generator. For sale or trade — new Astatic DN-HZ mike and adjustable floor stand, new 12" Utah PM speaker, new signal transmitting key stamp collection, battery charger, also 2 S127 cameras. Ralph Freyberger, Fleetwood, Pa.

FOR SALE — Cinadagrap SU-18" PM speakers; also W.E. jack strips; no priority needed. A. Sylvane, 231 E. 47th St., New York, N. Y.

(Continued on page 13)

WANTED: Signal Corps Equipment

You may have Radio-Amateur and Photographic equipment that is urgently needed by the Army Signal Corps. The Army will buy the following from private individuals.

Radio: Standard and commercial built short wave transmitters (such as Hallicrafters HT-1, etc.; Temco and Collins Model 32 and 30) and Standard and commercial built short wave receivers (such as Hallicrafter, National, RCA, RME, Hammarlund or Howard); AC and DC Voltmeters, Ammeters, Milliammeters, Radio Frequency Meters and Volt-ohm-milliammeters; Oscilloscopes, 2-3 inch; Audio sig. gen. 30-15,000 cycles; RF sig. gen. 15-215 megacycles; late model Tube Checkers, and other test equipment.

Photographic: 35 MM Motion Picture Cameras (such as Mitchell (all models), Bell & Howell - Standard Professional, Akeley-Professional (all models) and Eyemo (all models) Bell & Howell Mfg.), etc., and 16 MM Motion Picture Cameras (such as Cine-Kodak Special, Magazine Cine-Kodak, Filmo 70.D or Filmo Auto Master); Tripods; Lenses, all types for 35mm and 16mm equipment; Exposure Meters; and Cameras (such as Speed Graphic 4" x 5", and Speed Graphic 2 $\frac{1}{4}$ " x 3 $\frac{1}{4}$ " with or without flash synchronizers) and Leica Model III (F) or 11B (C), or equal; Range Finders; Pack Adaptors and Cut Film Holders.

If you have this type of equipment, you can assist the war effort materially by selling it to the Army. Write to:

EMERGENCY RELIEF SECTION
PHILADELPHIA SIGNAL CORPS PROCUREMENT DISTRICT
5000 WISSAHICKON AVENUE, PHILADELPHIA, PA.

briefly describing the equipment you have and stating the price at which you can offer each item, FOB Philadelphia. Do not ship any material without specific directions from that office.

Price consideration is based upon your net cost less reasonable depreciation for use, age, and condition of equipment. Inasmuch as all equipment is being purchased FOB Philadelphia, cost of packing and shipping can be shown separately so that an allowance for the costs can be made when material is accepted.

DESIGN OF BROAD-BAND AMPLIFIERS*

Simplified method for solving general problems dealing with amplifier response characteristics

There is a great deal of prior art on broad-band amplification. From a theoretical standpoint, practically every phase of this subject has been covered many times over. Most of the standard texts on radio engineering devote space to the analysis of this subject, which an engineer can utilize to solve a particular problem. There is some need, however, for a universal method of attack employing a unified and simplified form of mathematics. It is the purpose of this paper to present what is believed to be a useful method, from the engineering standpoint, for solving a large majority of broad-band problems.

This method is an approximate method. It involves the calculation of resonant circuit response on the basis of pure numbers. For such calculations, the concept of "relative frequency," as introduced by Wheeler,¹ replaces the concept of frequency; and the concept of power-factor is used. "Relative staggering" is shown to be synonymous with coupling, for staggered-stage calculations. Rule-of-thumb formulas are developed for engineering design, based on a family of universal response curves.²

The symbols R , L , c , f , etc., will refer to circuit parameters as is usual in the literature. Other symbols will be used to denote quantities, as follows:

A denotes amplification

p denotes power factor $= 1/Q$

k denotes coupling $=$ coefficient of coupling

s denotes relative staggering (explained in Section III)

B denotes relative bandwidth

G is defined as the "gain-constant" of an amplifying stage

The subscript "zero" refers to center-frequency response (i.e., A_0 is center-frequency amplification)

A "primed" symbol refers to peak response (i.e., B' is relative peak-separation)

The subscript "—" refers to series circuits (i.e., R_{-} is series resistance)

The subscript "||" refers to parallel circuits

d denotes differential frequency $= \pm (f-f_0)/f_0$ (on either side of resonance)

x and y denote relative frequency $= 2d$ (refers to total differential frequency difference on both sides of resonance, i.e.: $+d - (-d)$).

An approximation developed from General Circuit Theory will be employed throughout the text.

$$(1) \quad p = R_{-} \omega_0 = 1/R_{||} \omega_0 = 1/Q$$

The impedance of a series resonant circuit is:

* By Madison Carwin in "Electronic Industries."

$$(2) Z_- = R_- + j\omega L + 1/j\omega C$$

$$(3) \omega = 2\pi f = 2\pi (f_0 - f_0 + f_0) \\ = 2\pi f_0 (d+1) = \omega_0 (1+x/2)$$

(3) expresses ω in terms of relative frequency. Substitute (3) in (2) and simplify, neglecting d wherever it appears in the expression $(1 + d)$.

(This assumes that d is small in comparison to unity. Whenever this approximation is used in numerator or denominator, the fact will be indicated by the symbols $*$ / or $/*$ following the equation.)

$$(5) Z_p = (\omega M)^2 / Z_-$$

$$(6) Z_p = k^2 \omega_0^2 L^2 / (p + jx)$$

(6) is equation (5) simplified by means of (4) and substitution of $M = kL$.

Other equations relating to the equivalent circuit in Fig. 1 are:

$$(7) 1 = E_m e_g = i_1 + i_2$$

$$(8) i_- = e_- / Z_-$$

$$(9) e_- = -j\omega M i_2$$

$$(10) e = i_- / j\omega C$$

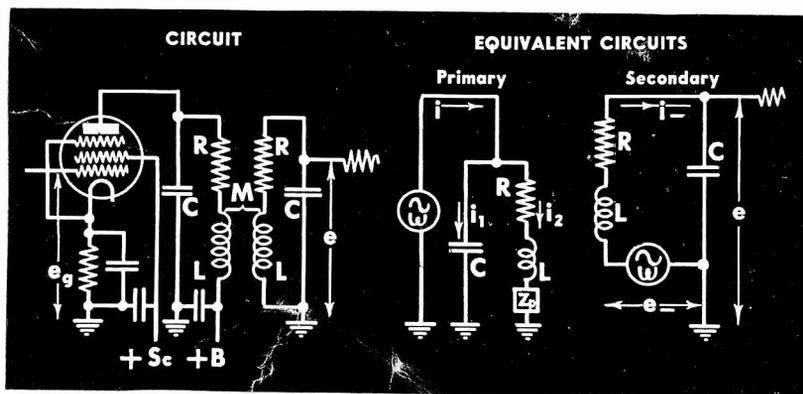


Fig. 1. Universal reference circuit and a simplified equivalent.

$$(4) Z_- = \omega_0 L (R_- C \omega_0 + jx) = \omega_0 L (p + jx) \quad */$$

Fig. 1 shows a typical double-tuned amplifier stage and its equivalent circuit. The impedance reflected in series with the primary of the transformer, from a resonant secondary of impedance Z_- , is:

The equivalent circuit of the primary is a constant current generator feeding two circuit branches in parallel. An impedance Z_p is reflected in series with the inductive branch and it may be proved easily that its value is as given in equation (5). Equation (7) is a statement of the approximate truth that in a pentode, considered as a con-

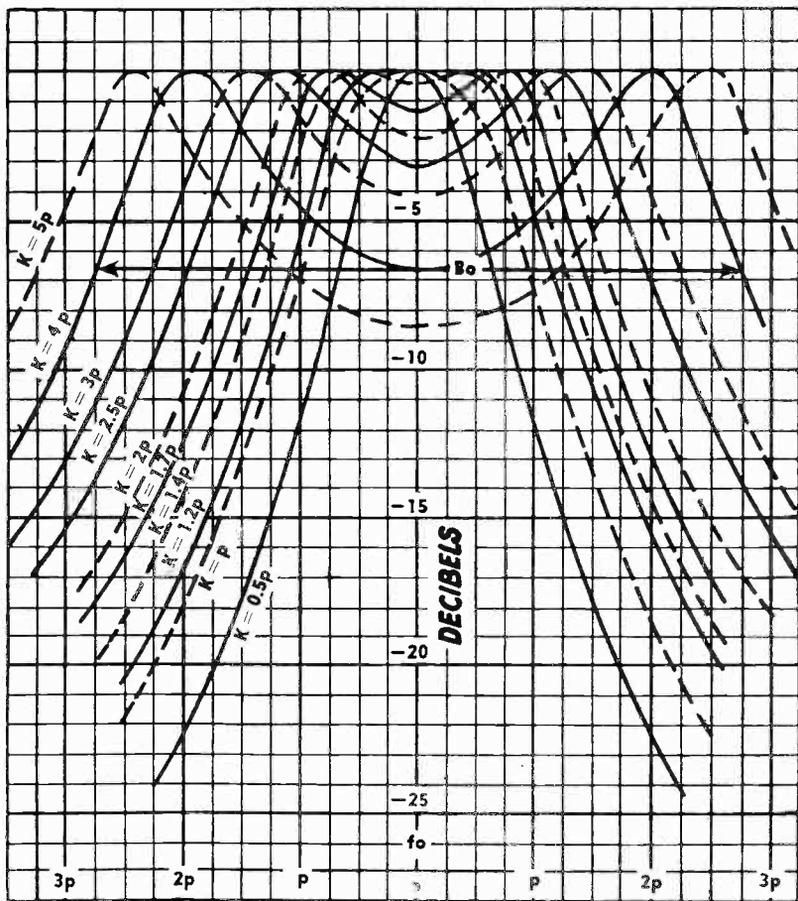


Fig. 2. Here the scale of abscissae is pure number: that is, units of $p=1/Q$. To convert to frequency, multiply by f_0 . For example, if the Q of the coils is 20, and the center-frequency is $f_0=10$ mc, then each division (p) represents π cycles $=0.05 \times 10$ mc $=500$ kc.

stant current generator, the current is independent of the load and is proportional to the grid voltage. The factor of proportionality is the mutual conductance.

The equivalent circuit of the secondary is a constant-voltage generator feeding a series circuit. Equation (9)

states that the generator voltage is in negative quadrature with the current in the inductive branch of the primary circuit and is equal in magnitude to the product of the mutual reactance and this current. Equation (10) states that the secondary grid-voltage is the product of the secondary current and

the terminating capacitive reactance, which is in parallel with this grid.

Equations (2) to (10) are merely mathematical representations of the experimental laws of electric circuits.

The voltage amplification is:

$$(11) \quad A = e/e_g = 1/J\omega c_e g = e/J\omega c_e Z_- \\ = - \frac{J\omega M I_2}{J\omega c_e Z_-} \text{ or } A = - \frac{kI_-}{ce g} \left| \frac{I_2}{Z_-} \right|$$

Simple calculation of i_2 from the laws of parallel circuits, and substitution from equations (3) to (10) show that:

$$(12) \quad i_2 = \frac{g_m e_g (p + jx)}{(p + jx)(jp - x) + jk^2} \quad *, / *$$

$$(13) \quad A = \frac{k g_m}{\omega c \sqrt{(p^2 + k^2 - x^2)^2 + 4p^2 x^2}}$$

obtained by substituting (4) and (12) in (11). It shows a symmetrical function of x . A is here expressed in terms² of the relative frequency x , and the constant parameters p and k . Since x , p and k are pure numbers, the graph of the function A is a family of universal curves. These are plotted in Fig. 2.

There are three forms of equation (13), obtained by algebraic manipulation:

$$(a) \quad A = kG / \sqrt{(p^2 + k^2 - x^2)^2 + 4p^2 x^2} \\ (13) \quad (b) \quad A = kG / \sqrt{(p^2 + k^2 + x^2)^2 - 4k^2 x^2} \\ (c) \quad A = kG / \sqrt{(p^2 - k^2 + x^2)^2 + 4p^2 k^2}$$

$G = g_m / \omega c$ is the gain-constant of the stage, and defines the absolute level of amplification. It would seem at first glance that this level is, then, inversely proportional to the frequency:

this is true only because as f_o is increased (Fig. 2) the relative bandwidth, which depends on x , increases proportionally; unless the scale of x is changed by modifying the power-factor, p . This will be clarified later.

Differentiation of (13) shows that the maximum value of A occurs at (or, can be determined by an examination of equation (13c))

$$(14) \quad p^2 + x^2 = k^2 \text{ or } x = B^1 = \sqrt{k^2 - p^2}$$

which is a well-known equation defining the relative peak-separation.

The gain at the peaks

$$(x = \sqrt{k^2 - p^2}) \text{ is } (15) \quad A^1 = G/2p$$

The gain at the center frequency ($x = 0$) is:

$$(16) \quad A_0 = kG / (p^2 + k^2)$$

The dip-to-peak ratio is:

$$(17) \quad R_0 = A_0 / A^1 = 2pk / (p^2 + k^2)$$

The simultaneous solution of (14) and (17) gives two very useful relations:

$$(18) \quad p^2 = \frac{(B^1)^2}{2} \frac{1 - \sqrt{1 - R_0^2}}{\sqrt{1 - R_0^2}} = \frac{(B^1)^2 D}{2} = \frac{R_0^2 D}{4}$$

$$(19) \quad k^2 = \frac{(B^1)^2}{2} \frac{1 + \sqrt{1 - R_0^2}}{\sqrt{1 - R_0^2}} = \frac{(B^1)^2 D'}{2} = \frac{R_0^2 D'}{4}$$

D and D' will be called the dip-function and the conjugate dip-function, respectively. These are related by the equation:

$$(20) \quad D' = D + 2$$

regardless of the value of R_o . Thus, for over-coupled stages (R_o is im-

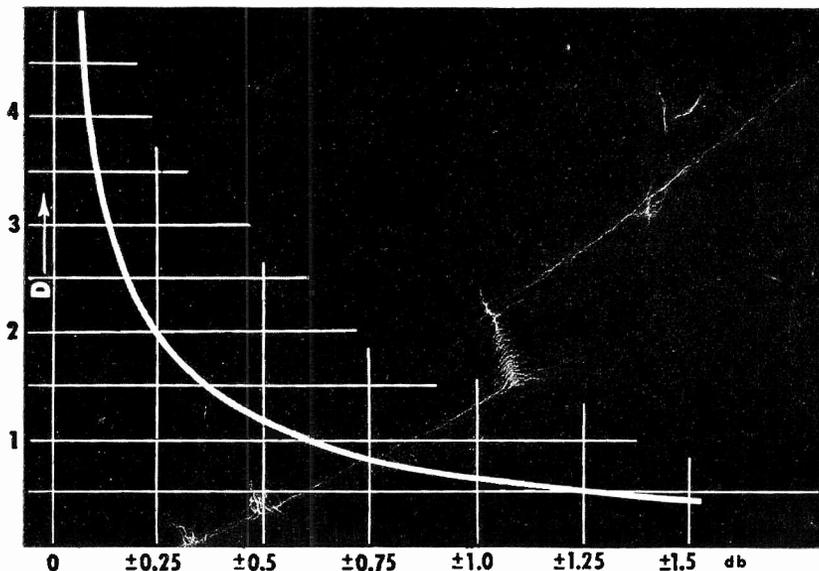


Fig. 3. Values of the Dip Function, D , as a pure number for various departures from flatness, in decibels

imaginary unless k is equal to or greater than p) the following holds:

$$(21) \quad k^2/p^2 = D'/D$$

The graph of D is shown in Fig. 3. In Fig. 3 the scale of abscissae has been plotted in decibels of departure from flatness (\pm db from mean level between peaks and valley) for the convenience of those engineers who prefer to work with db-gain rather than absolute gain.

Thus, in designing an over-coupled stage of amplification, the only necessary data required is the determination of the bandwidth, B_0 , and the desired departure from flatness over this band. k and p may then be calculated from (18) and (19).

The center-frequency amplification is, from (16):

$$(22) \quad A_0 = G\sqrt{D'/B_0(D+1)}$$

from which the amplification is seen to be independent of center-frequency, but is inversely proportional to the bandwidth in cycles (the factors G and B_0 each contain $1/f_0$, which cancels out of numerator and denominator).

Let B_n = relative bandwidth of resonance curve at the gain-level of the dip.

Then the relative bandwidth, B_0 , across the valley is

$$(23) \quad B_0 = \sqrt{2} B'$$

This is shown in Fig. 2, curve K = 4p, and can be proved easily by calculating the value of x which makes A = A_m. This bandwidth is of some significance, as will be discussed later.

The analysis given in this section has been symmetrical, even as regards circuit components. Actually, if it is desired to get the maximum gain from a broad-band amplifier, it is usual to design the coils to resonate with the distributed capacitance on each side. These capacitances are in general slightly different. High-g_m amplifiers, such as the 6AC7, together with circuit components have a realizable minimum plate circuit capacitance of about μμf, and a realizable minimum grid circuit capacitance of about 16 μμf. The actual dissymmetry of the peaks (which did not show up in the mathematical analysis due to neglects indicated by */, /*) can be equalized by detuning the plate and/or grid circuits slightly from resonance at f₀.

It is usual to omit the plate-side damping resistor shown in Fig. 1, and to introduce all the damping in the grid side. This is allowable because of the fact that power factors are additive. As has been shown by Mountjoy,³ the use of a grid damping-resistor only will increase the gain by several db per stage.

The design formulas are obtained in such a case by the methods outlined in this section, using different values of L, c, and R on each side of the transformer. Let p be the resulting power-factor of the grid circuit, and p₁ that of the plate circuit. Then, it can be shown that equation (13) becomes:

$$(13.1) \quad A = kG / \sqrt{(pp_1 + k^2 - x^2)^2 + x^2(p + p_1)^2}$$

$$(13.2) \quad A = kG / \sqrt{(k^2 - x^2)^2 + x^2 p^2}$$

obtained when p₁ is zero, which is double peaked, quite flat, and very selective for k > p. Since the value p₁ = 0 cannot be realized, the equation for a value of p₁ = np will be of more practical use:

$$(13.3) \quad A = kG / \sqrt{(np^2 + k^2 - x^2)^2 + x^2 p^2 (n+1)^2}$$

It is possible to realize a value of n = 0.1. The amplification calculated from equation (13.3) will be found to be about 6 db higher than that from equation (13), for this value of n. That is, a higher gain per stage is realized by using grid damping instead of grid and plate damping of the double-tuned transformer.

The peaks occur at a value of x obtained from differentiation of (13.3):

$$(13.4) \quad x' = 0.7 \sqrt{2k^2 - p^2 [(n+1)^2 - 2n]}$$

A flat response is obtained by making k = p in this case, which gives an overcoupled response having a departure from flatness corresponding approximately to a value of D = 2. The value of optimum coupling is obtained by making (13.4) equal to zero, and solving for k₀:

$$(13.5) \quad k_0 = 0.7 p \sqrt{(n+1)^2 - 2n} \frac{1}{p/2}$$

for small values of n. The relative peak separation and the relative bandwidth are, respectively:

$$(13.6) \quad B' = 0.7 p \quad (\text{for } k = p)$$

$$(13.7) \quad B_0 = \sqrt{2} B' = p$$

Thus, the relation between parameters is $k = p = B_0$ for flat design when using single-sided damping.

It is of interest to the experimental engineer that the formulas for k and p given by equations (18) and (19) depend upon quantities which can be checked with a signal generator and a vacuum-tube voltmeter, i.e., on bandwidth B_0 , and on a function of valley-peak gain as expressed by D .

REFERENCES

1. H. A. Wheeler and J. K. Johnson, "Proceedings of the I.R.E.," June, 1935, page 594.
2. F. E. Terman, "Radio Engineering," page 56, McGraw-Hill, 1937.
3. Garrard Mountjoy, "RCA Review," January, 1940, page 299.

When You Move or Change Your Address

Be sure to notify the Mailing Dept. of "The C-D Capacitor," Cornell-Dubilier Electric Corp., South Plainfield, New Jersey, giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your co-operation.

THE RADIO TRADING POST

(Continued from page 5)

WANTED — For C.A.P. Communications: 4 lowloss local sockets, 2 small single button carbon microphones; 2 small carbon button microphone transformers; 2 200-500 ohm line to grid transformers; 1 500 watt AC light plant, 5 Amphenol 72 ohm coaxial cable. Fox Radio Service, 435 S. 5th St., Richmond, Ind.

WANTED — 9002 radio tubes and sockets. Fox Radio Service, 435 S. 5th St., Richmond, Ind.

WANTED — Superior 1240, Teco T-10 or similar tube tester. Also Superior Model 1230 signal generator. H. R. Ringold, 132 N. Doheny Dr., Beverly Hills, Calif.

WANTED — Expert auto and home radio serviceman. Permanent. Good salary. Also one Riders Chanalyst by RCA. F. W. Mango, 380 N. Winton Rd., Rochester, N. Y.

WANTED — We need 50 of the following tubes: 12SA7, 12SK7, 12SQ7, 50L6, 35Z5. State price and condition. Miller Radio Service, 1017 Westgate Road, Troy, Ohio.

SALE OR SWAP — \$250 Waltham watch. Want indicating instruments, oscilloscope or camera. George B. Stanton, 310 Windsor Pl., Brooklyn 13, N. Y.

WANTED — Electronic voltmeter. Will pay well if allowed 3 day inspection with return option if not satisfied. Might also be interested in Weston 776 Carl Schradieck, 65 Hazard Ave., Providence, R. I.

WANTED — Will pay good price for RCA Chanalyst and Signolyst, Hickok 202 vacuum tube voltmeter; Precision E200 signal generator; Supreme 589 tube tester; and copies of Riders Manual. Felix M. Whitaker, 8.6 Wilkerson Ave., Durham, N. C.

FOR SALE — Collector of standard radio tubes (new). Want late model signal generator. Fred Wollenbarger, 1945 S. Custer Rd., Monroe, Mich.

WANTED — Signal generator, any make; used copy of "Radio Operating Questions and Answers," for commercial radio licenses by Nilson and Hornung. Lt. J. P. Conrad, 5708 N. 11th St., Arlington, Va.

FOR SALE — 22 cal. target pistol with holster, \$40. 1 GE motor, type KH 1/40 1140 RPM, in original carton; 1/6 HP motors used; Esco motor generator converters, 230 v to 110 v ac, single phase, 60 c. Write for details. Nelson K. Stover, 1357 Hill St., York, Pa.

WANTED — Complete set of Riders manuals. Will pay cash. Will buy single manuals if unable to get complete set. Philip V. LaMantia, 1757 Welch Ave., Niagara Falls, N. Y.

WANTED — Will pay cash for Riders manuals, vol 1 to 13 incl. State lowest price and condition. George M. Gum, Maj. T. C., Fort Slocum, N. Y.

WANTED — Signal generator; Precision E200, Clough Brengel, Hickok 188X, or other good type of oscillator. State cash price or will trade Delta jig saw. Need Supreme 562 Audolyzer. Cash waiting. Martin Radio Service, 142 Ralph Ave., Brooklyn, N. Y.

SELL OR SWAP — \$135 Western Electric Hearing Aid complete. Make cash or trade offer. Want HO gauge model train equipment or accessories. Metal working lathe. R. N. Eubank, 1227 Windsor Ave., Richmond 22, Va.

WANTED — Riders manuals 1 to 13 with index. Must be clean and in good condition. Cash. Radio and Electric Service, 2215 N. 14th St., Terre Haute, Ind.

WANTED — Clough-Brengle model OC or 110 signal generator, RCA frequency wobblur (motor driven type), 0-50-0 and 0-200 micro-amp. meters. Have misc. parts, etc., to trade or cash. V. R. Parker, RFD, Lunenburg, Mass.

WANTED — I will pay highest cash price for radio test equipment. Roxy Radio Repair, Mitchell, S. D.

FOR SALE — Special Victrola set consisting of two turntable assemblies, Victrola pickup, amplifying circuit and relays. Assemblies have multiple record attachment and two-hand set desk telephones. G. D. Onderdonk, National Gypsum Company, Buffalo, N. Y.

FOR SALE — New radio tubes, 25 per cent discount. Burt's Radio, P.O.B. 308, Elyria, Ohio.

WANTED — 2 cylinder Onan gasoline engine driven 110 volt, 60 cycle, single phase, 3000 watt alternating current generator. Paul H. Thomsen, 903 Philadelphia Ave., Silver Spring, Md.

WANTED — Shure Unidyne model 55C dynamic microphone. Advise output impedance, condition and price. Paul H. Thomsen, 903 Philadelphia Ave., Silver Spring, Md.

FOR SALE OR SWAP — Riders manuals 2 to 10 incl. \$75; Reardrite model 641 Free Point tester \$12.50; Weber model 40 oscillator electric powered \$20. All in A1 condition. Want C-D model BF-50, Aerovox 95 LC checker, Solar model CE Exameter or what have you. H. L. Mills, 8006 Truxton Ave., Los Angeles 43, Calif.

WANTED — English setter male pup, FDSB registry, and 16 or 20 gauge shotguns. In exchange can offer microphones, amplifiers, or what do you need. Lou Marko, 45 Carlton Place, Passaic, N. J.

WANTED — One RCP multi-tester model 661 electronic voltmeter. Will pay cash. State condition and price in first letter. Wilbur DuVall, Gravette, Ark.

FOR SALE — Foote-Pierson tape recorder, double pen. Brush VP-1 vibration pickup, brand new. Astatic lapel mike model 218, also new. List of other desirable items for the asking. A. F. Toth, 3608 29th St., Long Island City 1, N. Y.

WANTED — Converter from 110 AC to 110 DC Rotor type preferred. Also want Philco 71 chassis with power transformer, all or most of parts mounted. Will consider speaker also, not necessarily in playing condition. McKinley Radio Service, Zebulon, Ga.

WANTED — High quality output transformer with 500 ohm Sec for P-P 6L6's. State price, make, and type. Have audio and power transformers and tubes for sale. C. L. Goebel, 221 W. 233 St., New York 63, N. Y.

FOR SALE — Parts for a powerful PA amplifier including pre-amplifier, special microphone, and heavy RCA speakers, Kenyon transformers, or will assemble to order. Robert E. Leutz, 39 Burnet St., Maplewood, N. J.

FOR SALE — Over 50 good used phonograph records, good selections. Will ship entire lot with albums to first person sending \$5. 6.00x16 new 2-ply, self-vulcanizing endless tire liners \$2.95 each. Will swap for radios, ready to sell. Auto and Appliance Supply, Cor. Main at Newton, Granby, Mo.

WILL TRADE Clough Brengle battery operated oscillator or 32 hammerless break-open H. and R. revolver or 22 bolt action repeating rifle, all in A-1 condition for A.C. operated oscillator. Charles Royer, 391 Liberty St., Allentown, Pa.

WANTED — Supreme de luxe model 189 signal generator. State price and condition. Glen Wolfe, 2127 Milford, Houston, Tex.

FOR SALE — Used radio equipment. Send for list. Fred Craven, 2216 S. 7th St., Philadelphia 48, Pa.

WANTED — Superior tube checker model 1240 or 1280 and Superior signal generator model 1230; also want meter for RCP 415. Must be in A-1 condition. State price in first letter. Tom Selles, 4411 34th Ave. S., Seattle 8 Wash.

FOR SALE — Complete NRI course in practical radio and television. 65 books including reference books, \$10. Ray Williams 4405 Arlington Ave., Ft. Wayne, Ind.

WANTED — Late model Supreme tube checker and analyzer with a 20 meg ohm reading. Will pay cash. Richard Jones, 3043 Phyllis St., Jacksonville, Fla.

WANTED — High grade tube tester such as Precision, RCP, or Supreme. Must be in perfect condition. Will pay cash. Al Werhan, Manlius, N. Y.

WANTED — Will pay cash for 200 or 250 watt converter (D.C. to A.C.) in good condition. L. D. Harmon, Box 97, Gatlinburg, Tenn.

FOR SALE — Several Racon trumpets and units; six volt power pack; genemotor; one set of chanalyst test leads (4). National Sound Equipment Co., 625 Main St., Worcester, Mass.

FOR SALE — Model 148 oscillograph, Dumont 5" with instruction book. Used about 20 hours or will trade for A-1 late chanalyst. Highest offer takes it. Rexall Radio Stores, 205 Pearl St., Utica, N. Y.

WANTED — Cutting head unit for General Industries Recorder, either crystal or magnetic. K. L. Mengle, 1319 "D" St. N.E., Washington, D. C.

WANTED — National Radio Institute correspondence course in radio and the additional lessons in radio communications. Also experimental kits. Cash. Arthur Kruger, 1316 Morgan Ave. N., Minneapolis 11, Minn.

FOR SALE — Radio books and equipment. Write for list. Percy Ott, 507 Juniper St., Quakertown, Pa.

FOR SALE — Triplet 1178 set tester and free point tester in oak case. Good condition except batteries. Best offer takes it. Ovie B. Ball, R. R. 3, Connersville, Ind.

FOR SALE OR TRADE — A single unit dash push button auto radio for a 1939 Chrysler, Dodge, De Soto, or Plymouth car in good condition or will trade. Paul Capito, 637 W. 21st St., Erie, Pa.

WANTED — Midget radios, any condition; also S.W. radios all types. Give best cash price and condition of radio in replying. G. Samkofsky, 110 Wilson St., Brooklyn, N. Y.

WANTED — Any popular make record changer in good condition; also want Jensen type "J" 15" dual loudspeaker. Give complete details and price. E. P. Schoeneck, R. 2, Box 16, Wahpeton, N.D.

WANTED — Superior model 1240 tube tester (used). Will pay cash. Also small used AC-DC set. B. Paine, 1186 Lexington Ave., New York City.

WANTED — Outboard motor. Give full particulars as to condition. Dewey Goshen, 4073 Fireman Ave., Detroit, Mich.

WANTED — Jackson, Precision or Supreme tube checker, signal generator, and condenser checker. Will pay cash. A. L. Fry, Jr., Station KSO, Des Moines 4, Iowa.

WANTED — Riders chanalyst in good condition. Will pay top price. Also want Riders Manuals 8 to 13. John Leone, 28 Verona Pl., Verona, N. J.

WANTED — Model 89 de luxe Supreme tube tester. Will pay cash. State price. Firth Midgley, Fulda, Minn.

WANTED — VOM; gas engine driven A.C.-D.C. generator 300 or 450 watt. Also capacitor analyzer. A. Saulwater, 820 State St., Schenectady 7, N. Y.

WANTED — 1-inch cathode-ray oscilloscope. Condition of 913 is not important. Must be in good condition otherwise. Will pay cash. Leslie Bigelow, 603 E. Market St., Iowa City, Iowa.

WANTED — RCP 661 or 662 electronic multimeter; also supreme 589 or 599 tube tester. Will pay cash. The Radio Man, 1724 Central Ave., Middletown, O.

Keep 'em listening
with
CORNELL-DUBILIER
Capacitors

*"Never
a failure"*

— writes W. B. GILLESPIE, Prop.
Gillespie Radio Service
O'Neill, Nebraska

"I use C-D Condensers and have for several years," continues Mr. Gillespie. "Am still waiting for the first failure!" Hundreds of the nation's leading servicemen have used virtually the same words when writing us. Outstanding performance pays off — in added profits, customer good-will and valued repeat business. You can standardize on Cornell-Dubilier Capacitors with confidence!

WRITE FOR CATALOG



MICA • PAPER • DYANOL • WET AND DRY ELECTROLYTIC CAPACITORS

Cornell Dubilier

ELECTRIC CORPORATION

1089 HAMILTON BLVD. • SO. PLAINFIELD, N. J.

MORE IN USE TODAY THAN ANY OTHER MAKE