



HAM NEWS

TUBES

SPRING, 1963

KCS COMPACTRON AMATEUR BAND RECEIVER

PART II — Construction, Alignment and Operation

By Norman L. Morgan, W7KCS/9

CONSTRUCTION of the KCS Compactron Amateur Band Receiver is outlined in detail in this issue. About 80 to 100 hours are required for assembly and alignment, or about twice the time that assembling a comparable receiver assembled from a commercial kit will take. The mechanical work—drilling the chassis, sub-chassis, dial brackets and assembly, bandswitch and coils, etc.—should be pretty well completed before the wiring is started.

MECHANICAL CONSTRUCTION — The main chassis of the receiver is 8x12x3 inches, of aluminum (*Bud AC-424*, or equivalent). The chassis layout diagram, Fig. 3, shows the mounting dimensions for the components. It is suggested that these be followed closely because of space limitations.

Dimensions shown for the crystal sockets (Y_1 to Y_8) are for *National* type CS-6 ceramic sockets. Other types may require slightly different dimensions. The crystal sockets touch each other to conserve space.

Location of the VFO subchassis is shown in the center of the drawing. The shaft extensions for the various control knobs are shown through the front edge of the chassis. Dashed lines indicate the positions of the shield partitions below the chassis which isolate the various sections of the receiver.

Six $\frac{3}{4}$ -inch long spacers with No. 6-32 threaded holes space the front panel away from the front edge of the chassis. All panel controls are mounted behind the front edge of the chassis, except for the function switch (S_3) and the vernier mechanism for the PRE-SELECT control, which are mounted on the front panel.


THE VFO CHASSIS is a $3\frac{1}{4} \times 2\frac{1}{2} \times 1\frac{1}{2}$ -inch miniature aluminum box (*Bud CU-3001 Minibox*, or equivalent). It is drilled according to the layout diagram, Fig. 4. When drilling the bottom section of

the box, clamp it to the main chassis in the proper location and drill all holes through both parts at the same time to assure good alignment.

The front wall of the bottom cover is cut out as shown in Fig. 4, and a $1\frac{5}{8} \times 3\frac{3}{16}$ -inch cover plate made of $\frac{1}{32}$ -inch thick sheet aluminum is fastened over the opening with self-tapping screws. A $\frac{3}{8}$ -inch diameter hole in the cover is drilled for the lead running to C_{24B} . A completely-enclosed oscillator box is necessary to prevent feedback from the oscillator.

THE CRYSTAL OSCILLATOR coil assembly (L_{13} to L_{20}) is built into the home-made box shown in Fig. 6. This box is made of $\frac{1}{32}$ -inch thick sheet aluminum in two parts, the main body and a small cover. The box is folded after the various holes are drilled. The box is then centered over the large cutout in the chassis above S_{1E} and S_{1F} . Matching holes for machine screws are drilled through the box bottom flanges into the main chassis.

Shield partitions made from $\frac{1}{32}$ -inch thick sheet aluminum are next installed in the chassis in the locations shown in Fig. 6. Flanges $\frac{1}{4}$ -inch wide are bent on the sides and ends to facilitate mounting on the underside of the chassis deck, and to the side walls of the chassis and adjacent shields. All shields are $2\frac{3}{4}$ -inches wide. The straight shield running from front to rear between the worm-gear drive and the 455-kilocycle IF amplifier runs across the 9-pin miniature socket for the mechanical filter. A slot is hacksawed across the portion of the socket in line with pins 3 and 8 down to the metal mounting ring on the socket. The partition is then cut out to fit into the slot. This effectively shields the input and output circuits of the mechanical filter, preventing the IF signal from leaking around the filter.

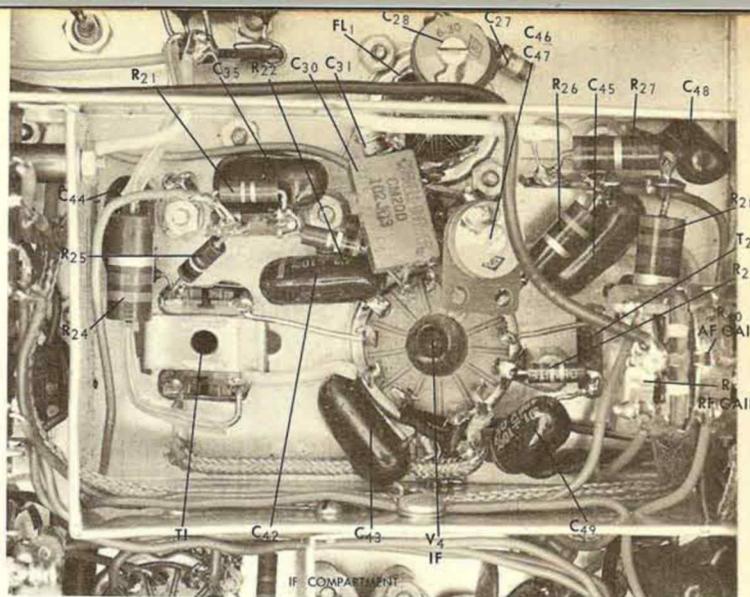

CLOSEUP VIEW OF the 455-kilocycle second IF amplifier (V_4) compartment. The neutralizing capacitor (C_{46}) which assures stable operation is on the 12-pin compactron tube socket. Note the shield partition running across the 9-pin miniature tube socket for FL_1 .

PART I —

Design and electrical circuit details of the KCS Compactron receiver appeared in the November-December, 1962 issue.



W7KCS/9 DEMONSTRATES the performance of his new KCS Compactron receiver to a youthful aspiring novice radio amateur.

The small $2\frac{1}{4} \times 1\frac{3}{16}$ -inch "U" shaped shield which fits onto the bandswitch (S_1) should have a $\frac{1}{4}$ -inch wide slot cut into it so that it will slide over the switch shaft and side rods. This shield encloses S_{1E} and S_{1F} —the crystal oscillator switch sections—and isolates segments S_{1A} and S_{1B} from segments S_{1C} and S_{1D} .

THE CABINET for the receiver is a *Bud* type SB-2140 *Shadow Cabinet* and is $14\frac{1}{4}$ -inches wide, 8 inches high, and 10 inches deep. A home-made cabinet for the receiver—similar in construction to that described for the LWM-3 transceiver in the January-February, 1962 issue of *G-E HAM NEWS*—could be made from solid and perforated sheet


IN THIS ISSUE


Copyright, 1963, by General Electric Company

KCS COMPACTRON AMATEUR BAND RECEIVER.....page 1

MEET YOUR EDITOR.....page 8

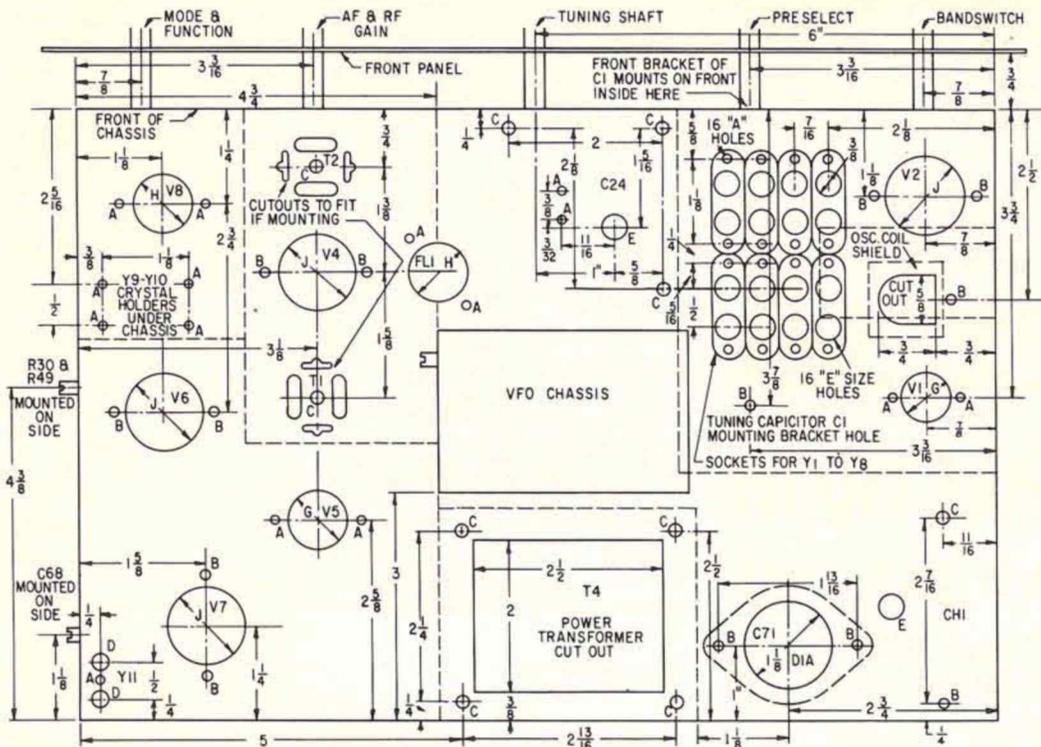ADDRESSES TO OBTAIN INFORMATION ON G-E PRODUCTS.....page 8



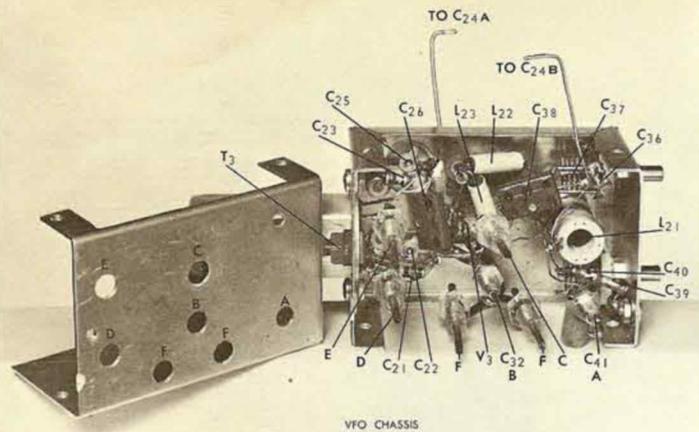

INSIDE VIEW of VFO-second mixer (V₃) subchassis with bottom cover plate (at left) removed. Machine screws on both sides of first IF transformer (T₃) are for grounding lugs on inside of box to which grounded ends of C₂₂ and C₂₅ are connected. Note that opening is cut in one side of bottom cover for cover plate which provides access to inside of VFO box after it is installed on chassis of receiver.

A 1/4-inch diameter hole about 1 inch deep is carefully drilled in the rim of the pulley so that a small spring may be mounted inside to exert a tension on the dial cord.

THE DIAL SCALE is rotated as the band-switch turns by a second dial cord drive. It starts with a 1 1/2-inch diameter pulley on the bandswitch shaft, and runs up to the dial drum, passing around a short brass rod screwed to the front panel to provide the 90-degree change in direction required. Since the bandswitch does not make a complete revolution, only one turn of the dial cord around the lower pulley is needed.

However, the dial drum has two turns of cord around it, with a small holding pin in the center to prevent slippage. A similar pin keeps the cord from slipping on the bandswitch pulley. A small piece of springy material is mounted on the front edge of the chassis and rides against this dial cord to provide a constant tension takeup. A rubber band is wrapped around the dial drum at each end to keep it from slipping out of the support brackets.

An escutcheon plate for the tuning dial is made from 1/4-inch thick sheet plastic material—black was used on this model—cut and drilled as shown in Fig. 12. The slot may be cut out with a saber saw, or hacksaw after drilling holes to start the blade. The bevel is formed, and the corners rounded, with a half-round file to a smooth surface. Sanding the escutcheon with fine sandpaper or emery cloth will give it a satin-smooth appearance.

After openings and holes are cut for the major components—power and

IF transformers, capacitors, switches, etc.—the parts should be fitted into place and any necessary trimming and filing done. When all such work—cutting, drilling and folding—is completed, remove all sharp edges and burrs before the metal pieces are assembled. Use lock washers under the nuts on all machine screws to prevent parts from becoming loose later on.

Starting with the bare chassis, install all tube and crystal sockets, but the shield partitions can be left out temporarily to allow more room to work inside the chassis.

ELECTRICAL CONSTRUCTION—The largest subassembly—and the most critical—to go into the receiver is the band-switch and RF coils, so it should be assembled first. One of the reasons for the outstanding performance of this receiver is the high Q of the RF coils. The coils should be wound with care using close winding techniques and the finished coil covered with a good grade coil dope. When the completed coils (L₁ thru L₁₂) have dried they are mounted one by one on the coil brackets with necessary solder connections completed before the next coil is put into the bracket.

On coils L₁ thru L₆, the end of the A, or antenna coil, together with the end of the B coil, are connected together and soldered to the lower coil solder terminal. The other end of Coil A is connected to the respective switch terminal of S_{1A}. The beginning of coil B is connected to the top of the coil terminal lug and this combination soldered directly to the appropriate switch terminal on S_{1B}.

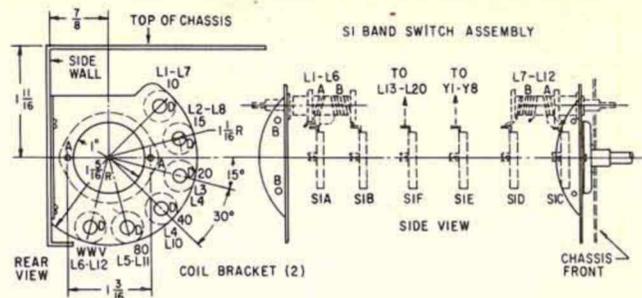


FIG. 8. BANDSWITCH ASSEMBLY, showing the positions of the switch wafers and coils. The brackets on which the RF coils (L₁ to L₆, and L₇ to L₁₂) are mounted are cut as 2 5/8-inch diameter circles from 1/16-inch thick sheet aluminum, then drilled, trimmed and bent as shown.

All of the lower terminal lugs are connected together with a piece of No. 18 solid tinned wire to form a ring which is finally connected to a convenient chassis ground at L₆. Assembly of the coils should start with L₁ and proceed around the bandswitch, since the higher frequency coils have heavier wire and can support the ground wire ring better without the undue stress which would be placed on the smaller wire of the lower frequency coils.

The RF amplifier plate coils (L₇ to L₁₂) are also mounted by starting with L₇ and progressing to L₁₂. These coils are mounted on the bracket so that the top coil terminal rests on their respective switch terminals of S_{1D}. The top of coil A is connected to the respective switch terminal of S_{1C}. Two solid wire rings are required for this coil set, one at the end of coil B, which is grounded at a convenient point, and the other at the end of Coil A, which is connected to C₅ and R₆ for plate voltage. Make sure this latter ring does not touch ground around its periphery since it does carry plate voltage. After the bandswitch assembly has been completely finished and appropriate leads brought out for later connection, it may be set aside to await further completion of the under-chassis wiring.

The oscillator coils and tuning capacitors L₁₃ thru L₂₀ and C₁₂ thru C₁₉ are all mounted inside the oscillator coil shield box. There is not a great deal of room inside the shield; consequently, it is wise to wire in one coil and capacitor combination at a time starting with the WWV coil (L₂₀). The leads from these coils which go to S_{1F} should be labeled, stripped and have sufficient length to easily reach S_{1F} under the chassis after assembly.

The bottom ends of the coils—actually the physical tops—are all connected together and brought out to C₂₀ and R₁₃ which are mounted close to the switch on the underside of the chassis. Resistors and capacitors associated with the 6BZ6 RF amplifier tube (V₁) should be mounted close to the socket, except for R₆, R₁₀, R₁₄, R₁₁ and R₂, which may be mounted on a terminal strip behind the RF tuning capacitor (C₁). Wiring of the first mixer V_{2A} and V_{2B}, together with the crystal oscillator (V_{2C}), should be completed before the bandswitch assembly is installed in the chassis. Input and output leads should be well separated to avoid intercoupling or oscillation in the mixer.

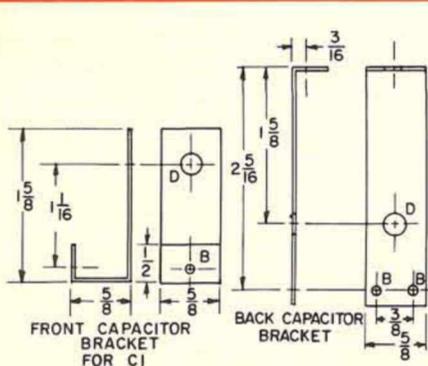


FIG. 9. BRACKETS supporting the dial scale tubing are formed using this diagram as a guide.


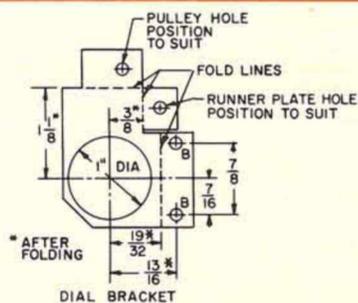
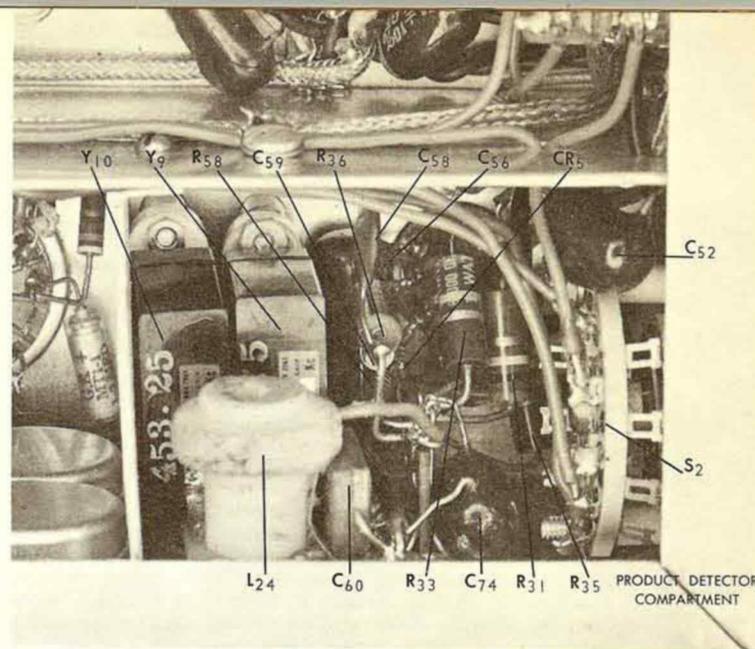


FIG. 10. DIAGRAM showing how the brackets on which C₁ is suspended below the chassis are formed and drilled, using 1/16-inch sheet stock. The dimensions and holes fit the Hammarlund MCD-100-S RF tuning capacitor used on this model.

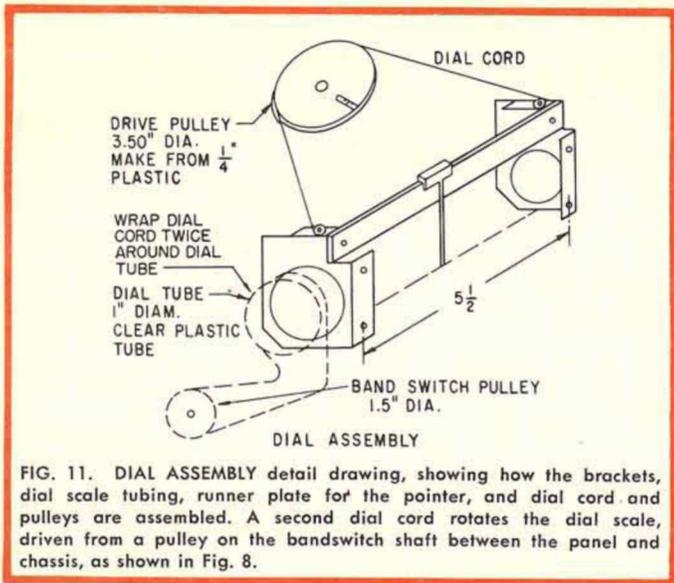

PRODUCT DETECTOR section (V₈) is detailed in this view of the front right-hand corner of the receiver.

After the underchassis wiring of the RF amplifier and mixer stages is completed, check to insure they will operate correctly. The first oscillator coil box (housing L₁₃ to L₂₀) is mounted on top of the chassis, and the various leads run down through the chassis to section S_{1F}.

Next, the bandswitch assembly is mounted in place in the chassis, and the leads to S_{1F} from the oscillator coils are dressed and soldered into place. Leads from the oscillator crystal sockets (Y₁ to Y₈) are brought to S_{1E} and permanently connected, after making sure that they are bundled and lay against the under side of the chassis. Before putting in the RF tuning capacitor (C₁) the small shield around S_{1F} and S_{1E} should be permanently installed, making sure that no leads touch it and are grounded. All the connections are then completed inside the RF amplifier compartment area and the preselector capacitor (C₁) is assembled into its position and soldered in. The shield around the RF and mixer stage may next be installed to protect these components from damage during assembly of other sections.

VFO ASSEMBLY — Next, the components for the VFO and second mixer (V₃) are mounted on the *Minibox* which was previously drilled, and oscillator connections made with No. 14 solid tinned wire. Those connections running via the feedthru bushings to the underside of the chassis should be cut to lengths which will allow the respective feedthru bushings to line up with the holes "A" through "F" indicated on the drawing for the bottom cover of the box in Fig. 4.

The first IF transformer (T₃) is made from a *Miller* 13W1 1500-kilocycle IF input transformer. It is taken apart and the two capacitors across the coils are disconnected. They are at the bottom of the transformer and are formed by the extension of the solder terminal lugs on the bottom. Drilling through the small metal grommet on the bottom releases the capacitor plates and they are removed. The transformer is then reassembled and is ready to be assembled into the VFO chassis. The solder lugs on the IF transformer are glued to the plastic support inside the IF shield and make convenient and rigid

connection to the respective feedthru insulators.

A hand-wound coil was originally used on one of the experimental prototypes of this receiver, however, it was found that it was exceedingly difficult to wind anything by hand approaching the quality of commercial IF coils. Before completing the VFO compartment set the bottom slug of T₃ six turns away from the full clockwise position.

After all wiring is completed, heavy wires for connecting to the stators of C_{24A} and C_{24B} are brought out through the access opening on the front side of the box. The bottom cover is then assembled, slipping the various feedthru bushings through their respective holes. The VFO box is then placed in position on the main chassis with the feedthrus through their holes in the chassis.

The removable side plate on the *Minibox* allows a small screwdriver to be used to advantage in positioning the feedthrus, guiding them through the holes. Nuts are then installed on the feedthru insulators to hold the VFO chassis in place. Lastly the leads running to C_{24A} and C_{24B} are connected. When soldering leads to the feedthru bushings, use needle-nose pliers as a heat sink to prevent the feedthru wires from becoming too hot. These are polystyrene insulators and will melt if undue heat is applied to them. The heater voltage feedthrus provide convenient junction soldering points to continue the heater leads to other tube sockets on the chassis.

Next the shield running across the chassis and through the center of the mechanical filter socket is installed after appropriate lead holes are drilled. C₂₈ is mounted directly on the mechanical filter socket. The IF stage is wired, making all leads as short as possible between tube elements, and making sure that bypass capacitors have short leads to ground. C₄₇ is wired directly between the screen grid of V_{4B} on pin 7 and a ground lug on the mechanical filter socket. Two terminal strips are shown in the IF compartment picture, one in the lower left corner holding the grid capacitors and resistors, and the plate and screen capacitors, and resistors for V_{4B} on the strip in the upper left hand corner.

Note that the input leads to V_{4B} and output leads are shielded. This stage is somewhat critical and it is wise to follow the component placement in the product detector detail view as closely as possible. Before the L shaped shield is placed around the right side of the IF compartment, wire the product detector (V₈) compartment in the upper right hand corner of the chassis. The various dropping resistors to the 6JH8 tube should be soldered in first, followed by the crystal sockets which mount below the chassis on 1/2-inch spacers.

Next the switch S₂ is installed and wired, using leads with sufficient length to run to other points where needed. Lastly, coil L₂₄, with C₆₀ soldered across its leads, is assembled and soldered into the circuit. After completing this stage, the L shaped bracket on the right side of the IF stage, and the small shield behind the product detector, are installed. Finally those leads running through the shields are connected to their appropriate locations.

Various components should be grouped around the 6AL5 AM detector tube (V₅) and the audio amplifier (V_{6A}) together with the gate and diode sections V_{6B} and V_{6C}. A terminal board of thin Textolite or other insulating material is made approximately 4 1/2 inches long by 1 3/4 inches wide with 14 positions. The bottom view of the receiver (page 6, previous issue) shows 17 positions, all of which are not needed. These should be equally spaced with eight on one side and six on the other. This allows easy assembly of various resistors, and bypass and coupling capacitors.

The audio output transformer (T₅) is assembled before the output tube (V_{7A}) and crystal calibrator (V_{7B}) have their components wired in. A small piece of coaxial cable is run from C₇₅ back to the antenna terminal coaxial input. Finally, R₄₉ and R₃₀ are assembled in the right hand side wall of the chassis and connected into the "S" meter circuit.

Holes should be provided near the bottom of the front of the chassis to take various leads to the S meter, and switch S₃. Although R₄₀, the audio gain control can be assembled now, it is better to temporarily ground the end

of R_1 and not assemble the RF gain control (R_5) until after the IF stages are aligned. Unfortunately, even though R_5 is short it has sufficient length to cover the IF output transformer lower tuning hole.

The small components in the power supply — rectifiers, resistors and capacitors — are all mounted on a terminal board made of $\frac{1}{16}$ -inch thick sheet Textolite* or other insulating board, assembled as shown in Fig. 13. The terminal lugs for tie points were made by running short No. 6-32 machine screws through the board with soldering lugs under the heads and nuts.

The power transformer (T_4) as purchased has No. 10-32 machine screws just long enough to fasten the transformer to the chassis. These screws should be removed and replaced with screws which extend about 2 inches beyond the chassis bottom. The power transformer is then mounted in its hole, and the rectifier components board is suspended from the ends of these screws with No. 10-32 machine nuts on either side of the board.

Other miscellaneous small parts and wiring are installed to complete the electrical assembly of the receiver. It is best to finally install the tuning dial mechanism after most of the construction has been completed to avoid damaging it while working on the receiver.

RECEIVER ALIGNMENT — The alignment method used and described by W7KCS/9 is unique in that the receiver is aligned by starting at the antenna terminals and peaking each succeeding stage for maximum performance. This is in contrast to the usual receiver alignment procedure which starts at the last detector stage and proceeds back through the receiver to the antenna input circuit. However, it is a good idea to first check out the audio portion of the receiver by feeding an audio tone (a code-practice oscillator is a good source) into the arm on the audio gain control (R_{40}). All tubes should be plugged in to check the heater circuit.

The test equipment needed for alignment includes a signal generator covering 455 kilocycles and the amateur bands from 3.5 to 30 megacycles and a vacuum-tube voltmeter with an RF probe. A general-coverage communications receiver also comes in handy for making certain tests. Connect the signal generator to the antenna jack (J_1), and a 72-ohm resistor from the center terminal on J_1 to a chassis ground. Set trimmers C_2 and C_6 to the center of their capacitance range.

RF AMPLIFIER — Starting with the 3.5-megacycle band, set C_1 near maximum capacitance. Set the signal generator

at 3.5 megacycles and adjust L_6 and L_{12} for maximum signal, obtaining a VTVM reading with the RF probe on the control grid (pin 11) of V_{2A} . Tune the signal generator and PRE-SELECT knob to 4.0 megacycles. If the slugs in L_6 and L_{12} need adjustment to peak the signal, adjust C_2 and C_6 instead. Recheck the adjustment of L_6 and L_{12} at 3.5 megacycles so that the same meter reading as noted at 4 megacycles is obtained.

Next turn the bandswitch to the 7-megacycle position, turn the PRE-SELECT knob to 7, and with the signal generator on 7.0 megacycles, tune L_5 and L_{11} for maximum signal strength. Do not adjust C_2 and C_6 once they have been adjusted on 4.0 megacycles. Proceed to the higher frequency bands, setting the PRE-SELECT knob, and adjusting the proper RF amplifier grid and plate coils with the signal generator set on 14.0, 21.0 and 28 megacycles, respectively. The tuning of the high "Q" RF coils is quite critical.

THE CRYSTAL first oscillator (V_{2C}) is then checked by adjusting the coil for each crystal, (L_{13} to L_{20}) until the mixer injection voltage — as measured with the VTVM RF probe on pin 9 of V_{2B} — is about 1 volt on all bands. The negative control grid voltage on V_{2C} (pin 11) is about 0.3 volts. This much of the receiver can now be checked by connecting the antenna lead from a general coverage receiver to feedthru bushings D and E through a blocking capacitor (0.01 mfd.). The receiver may then be used as a tunable IF amplifier, tuning from 3495 kilocycles down to 2995 kilocycles, to check the operation of the front end.

The tunable IF transformer (T_3) is next roughly aligned by removing the 6D10 first mixer tube and applying a 2995-kilocycle signal to points D and E through a blocking capacitor. The capacitor tuning knob is rotated $2\frac{1}{2}$ turns from the maximum capacitance position of C_{24} . The top slug of T_3 is adjusted for a maximum reading at this frequency. The RF output voltage is read with the VTVM RF probe on capacitor C_{24A} . Set the RF signal generator at 3495 kilocycles and the tuning dial $22\frac{1}{2}$ turns from maximum capacitance of C_{24} . Then adjust C_{25} for maximum voltage at the stator of C_{24A} .

Capacitor C_{22} should be adjusted to approximately one-half maximum capacitance before these adjustments are made. This adjustment is to get the mixer tuned circuit close until the tunable oscillator circuit is aligned. With voltage applied to the oscillator portion of the 6U8A tube check for oscillation by measuring the bias volt-

tage on pin 9 of V_3 . If oscillation does not occur reverse the connection to L_{21B} . If oscillation still does not occur more turns may have to be added to L_{21B} . If the oscillator frequency is not stable, this is indicative that L_{21B} has too many turns.

The best procedure for roughly aligning the VFO is to check the frequency coverage by listening on another communications receiver. Adjust capacitor C_{37} and C_{40} to approximately their center positions. Rotate the tuning dial to $2\frac{1}{2}$ turns of maximum on C_{24} and adjust L_{21} so that the oscillator frequency is 2540 kilocycles.

Next, rotate the capacitor tuning dial $22\frac{1}{2}$ turns from maximum on C_{24} and adjust C_{37} until the oscillator is tuned to 3040 kilocycles. Turn the tuning dial to $12\frac{1}{2}$ turns from maximum on C_{24} and adjust C_{40} for an oscillator frequency of 2790 kilocycles. Repeating this procedure, readjust L_{21A} , C_{37} and C_{40} until the desired tuning linearity is achieved.

Now with the correct frequency tracking of C_{24B} accomplished, go back and readjust the mixer coil and trimmer capacitors (T_3 and C_{25}). For greater accuracy after this rough alignment is completed the crystal calibrator may be turned on and used as a marker for final VFO and mixer adjustment.

IF ALIGNMENT — With a 455-kilocycle signal from the generator applied to the grid of V_{3A} , and the VTVM RF probe on the control grid (pin 5) of V_{4A} , adjust C_{28} for maximum output reading. This tunes the mechanical filter input; the mechanical filter output tuning is fixed and needs no adjustment.

Using the same setup, as above except with the VTVM connected to pin 11 of V_{4B} , adjust both the primary and secondary of T_1 for maximum RF reading. Connect the VTVM at the output of T_2 and adjust the output IF transformer (T_2) for maximum reading. Make sure that this reading is not from an oscillation within the IF stage. If so, capacitor C_{47} is adjusted until no output RF voltage is read on the output of T_2 with no signal at the antenna input. Recheck the alignment of the IF transformers by connecting the vacuum tube voltmeter at some audio point, such as pin 7 of V_{5B} , with a tone-modulated signal from the generator. Incidentally during IF alignment the AVC line should be disconnected. After the IF stages have been aligned, install R_5 and its associated components.

No problem with the SSB oscillator section of V_8 should be encountered if the circuit and component values specified are used. However in case of no oscillation, C_{60} should be increased in



FIG. 12. DIAL ESCUTCHEON is formed $\frac{1}{4}$ -inch thick plastic with window slot for dial scale. It may be painted in a color which matches the color scheme selected for the receiver.

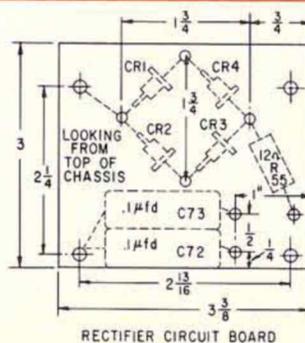


FIG. 13. ASSEMBLY of the rectifier circuit board, looking from top of chassis. Mounting holes in corners should match the mounting bolt locations on the power transformer.

FOOTNOTES

- ¹The Jackson Bros. Precision Planetary-vernier drive is listed for \$1.50 in advertisements of Arrow Electronics, Inc., 65 Cortlandt Street, New York 7, N.Y., in QST, CQ and 73 magazines.
 - ²Electro-Kit is manufactured and sold by Halmar Electronics, 1550 West Mound Street, Columbus 23, Ohio.
- * T.M. of General Electric Company

value by adding small capacitances across it, or by using the next lower value and adding small capacitances to it if the value appears to be high. Should a high mixing noise level be heard from the 6JH8 when the mode switch is in the single sideband position, it is probably due to the bias voltage on the deflector (pin 2) being too high. In this case reduce the value of R_{29} accordingly to reduce the mixing hiss noise.

The S meter should be calibrated with the mode switch (S_2) in the AM position, and set on zero with the zero set potentiometer (R_{49}) with the antenna terminals open. Maximum setting is adjusted with R_{30} while listening to a loud signal and calibrating the S meter according to one's own estimation of the signal strength. On single sideband the S meter will characteristically read higher than on AM; however its purpose is primarily for indication of relative signal strength within the mode of operation rather than an absolute reference. If single sideband operation is mainly contemplated, the zero set and maximum set on the meter may be calibrated with switch S_2 in the LSB or USB positions.

The crystal calibrator is adjusted by means of C_{68} with the mode switch in the calibrate position. After allowing some warm up time zero-beat its 100th harmonic against WWV on the 10-megacycle WWV band of the receiver.

After alignment is complete the receiver is slipped into its housing by sliding the top part of the cabinet over the chassis, since the controls on the sides of the chassis prevent its assembly via the cabinet front.

OPERATION — Operation of the KCS Compactron Receiver is quite simple, requiring only that the function switch be turned on to operate, and after a suitable warm up period, selecting the band of operation by bandswitch S_1 . After the PRE-SELECT knob is set in the approximate position for the particular band in use the tuning dial is tuned to the desired signal frequency. The PRE-SELECT knob is once again

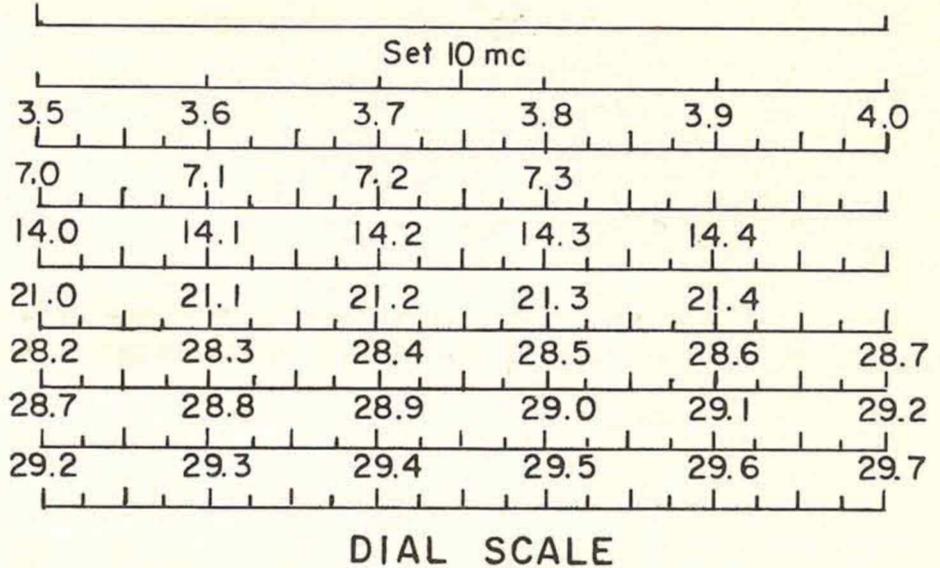


FIG. 14. DIAL SCALE used on the receiver, reproduced in full size here so that it may be clipped out and inserted into the scale tubing shown in Fig. 11.

peaked for maximum signal strength as read on the S meter. The RF gain control may be reduced on 3.5- and 7-megacycles especially if background noise and QRM are bothersome. If single sideband reception is desired the mode switch (S_2) is switched to either the upper or lower sideband and the tuning dial tuned until the signal is copyable at a natural voice pitch.

In the CALIBRATE position of S_3 harmonics of the 100-kilocycle from the crystal calibrator injects into the antenna circuit. These signals are strong on the 3.5- and 7-megacycle bands, and adequate for checking calibration on the higher frequency bands.

The KCS compactron receiver, as in the case of all receivers, represents a compromise between several mutually incompatible criteria. It has proven to be a very versatile, easily used receiver capable of reproducing signals with performance comparable to commercial receivers costing several times as much.

Its characteristics on single sideband are hard to beat. The fast attack, slow release AVC circuit on single sideband is quite effective and proves very useful during rapid break-in operation. It is rather difficult to realize that the receiver is on even on 28-megacycles with the volume control full open and no signal being received.

Using all new parts the cost of this unit should run about \$250 and, of course, may be much less, depending upon whether the coils are wound by the constructor and the parts in his junk box. Changes in various components can be made by using less expensive parts in various stages. However, this type of experimenting was not done on this receiver although a great deal of experimenting and "optimizing" was done with the circuit themselves to insure peak performance.

The receiver weighs approximately 22 pounds and its small size should be attractive to the XYL.


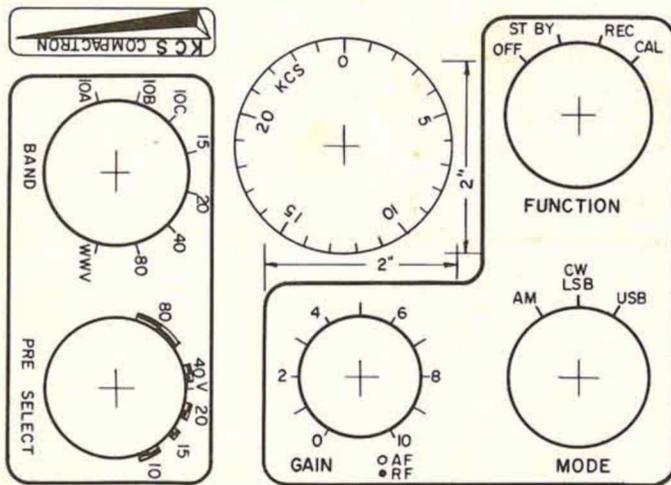


FIG. 16. CONTROL MARKINGS used on the KCS receiver, shown half size. Halmar Electro-Kit name plate process² was used to make up marking plates on the model receiver.

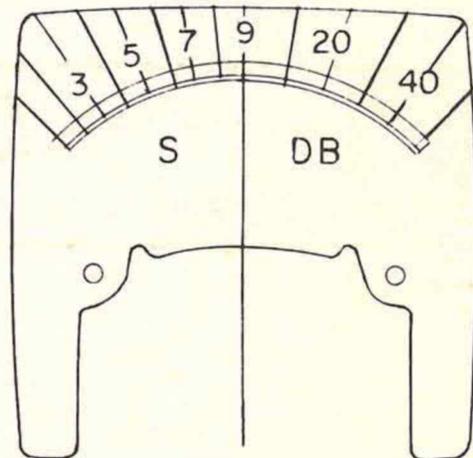

"S" METER SCALE

FIG. 15. "S"-METER SCALE, drawn in full size for G-E type DW-91 1/2-inch square panel meter.



"—this is W4ITC saying 73."

MEET YOUR EDITOR —

During the past several years we have received many requests asking that we publish a picture of the editor, W4ITC, and a description of his own ham shack. So, we finally cornered Ed "at work" during a recent on-the-air session. His station equipment—typical of thousands of amateur stations—includes a Drake 1A receiver, a 20A SSB exciter driving a pair of GL-813's in a linear amplifier, plus assorted home-built VHF equip-

ment. Antennas include a fan dipole for 3.5 megacycles, a rotary dipole for 7 megacycles, a 3-element triband beam, and VHF beams, all up about 50-60 feet.

It seems appropriate to show his station at this time, since W4ITC is transferring to a new assignment with General Electric's Computer Department in Phoenix, Arizona. This is the last issue he is editing, and so we wish him the best in his new location.

—Lighthouse Larry

ADDRESSES FROM WHICH TO OBTAIN INFORMATION ON GENERAL ELECTRIC PRODUCTS

When writing to large companies—such as General Electric—for information on their products, the problem of where to address the request often arises. Many major firms have plants and offices in a number of cities. Vague addresses—the company's name and a city—can result in a delay while the request is forwarded to the proper operation in that company.

With this in mind, and to help you readers send your General Electric inquiries direct to the proper locations, I've prepared a listing to which your inquiries should be addressed. For all addresses, add "General Electric Company" as the first line.

However, when you need publications on electronic components, first check with your local authorized General Electric distributor. He has a number of publications available at nominal cost, such as: Essential Characteristics on receiving, picture and industrial tubes; Industrial Tube catalogs; transistor, tunnel diode and rectifier manuals, etc. Mail requests for these books can be handled only when the full remittance accompanies the request.

Information on certain "war-surplus" electronic equipment which General Electric originally produced is covered quite thoroughly in several books on war surplus conversions which are available from publishers in the electronics field. No additional information is available from G.E.

—Lighthouse Larry

PRODUCT OR SERVICE

Appliances—Major: Ranges, washers and dryers, refrigerators, air conditioners, etc.

Appliances—Small: Toasters, Mixers, irons, vacuum cleaners, hair dryers, electric utensils, etc.

Communication Products: G-E Two-Way radio, carrier current and microwave relay equipment, etc.

Computers: business data processing, data accumulation equipment, computing services.

High-fidelity components and stereo audio systems, etc., and service information.

Lamps: miniature, incandescent, fluorescent, photoflash, etc.

Radios: Home, clock and portables, portable phonographs, etc., and service information.

Rectifiers: Germanium, silicon, Copper oxide, selenium, and silicon controlled rectifiers.

Space Systems and Vehicles.

Television Receivers, and Service information.

Transistors, and Tunnel and signal diodes.

Tubes—Power types: UHF TV transmitting, traveling wave, magnetron, klystron, ignitron, etc.

Tubes—Receiving, thyratron, ceramic and other industrial tubes, replacement capacitors and semiconductors, meters.

ADDRESS ("General Electric Co. &)

Customer Information Section
Major Appliance Division

Appliance Park, Louisville, Ky.

Customer Information Section

Small Appliance Division

1285 Boston Avenue,

Bridgeport 9, Conn.

Advertising & Sales Promotion,

Communication Products Department

Lynchburg, Virginia

Computer Department

Deer Valley Park, P. O. Drawer 270

Phoenix, Arizona

Publications Section

Audio Products Department

2200 No. 22nd St., Decatur, Ill.

Product Information Section

Lamp Division, Nela Park

Noble Road, Cleveland, Ohio

Product Information Section

Radio Receiver Department

1001 Broad St., Utica, N.Y.

Advertising & Sales Promotion

Rectifier Components Department

W. Genesee St., Auburn, N.Y.

Public Information Section

Missile and Space Division

P. O. Box 8555, Philadelphia 1, Pa.

Product Information Section

Television Receiver Department

Electronics Park, Syracuse, N.Y.

A & SP, Semiconductor Products Dept.

Bldg. 7, Electronics Park,

Syracuse, New York.

Technical Information Section

Power Tube Department, Bldg. 267,

Schenectady, N.Y.

Technical Information & Product Service (TIPS),

Receiving Tube Dept.,

P. O. Box 1009, Owensboro, Kentucky



Available **FREE** from
your G-E Tube Distributor

SPRING, 1963

Vol. 18, No. 1