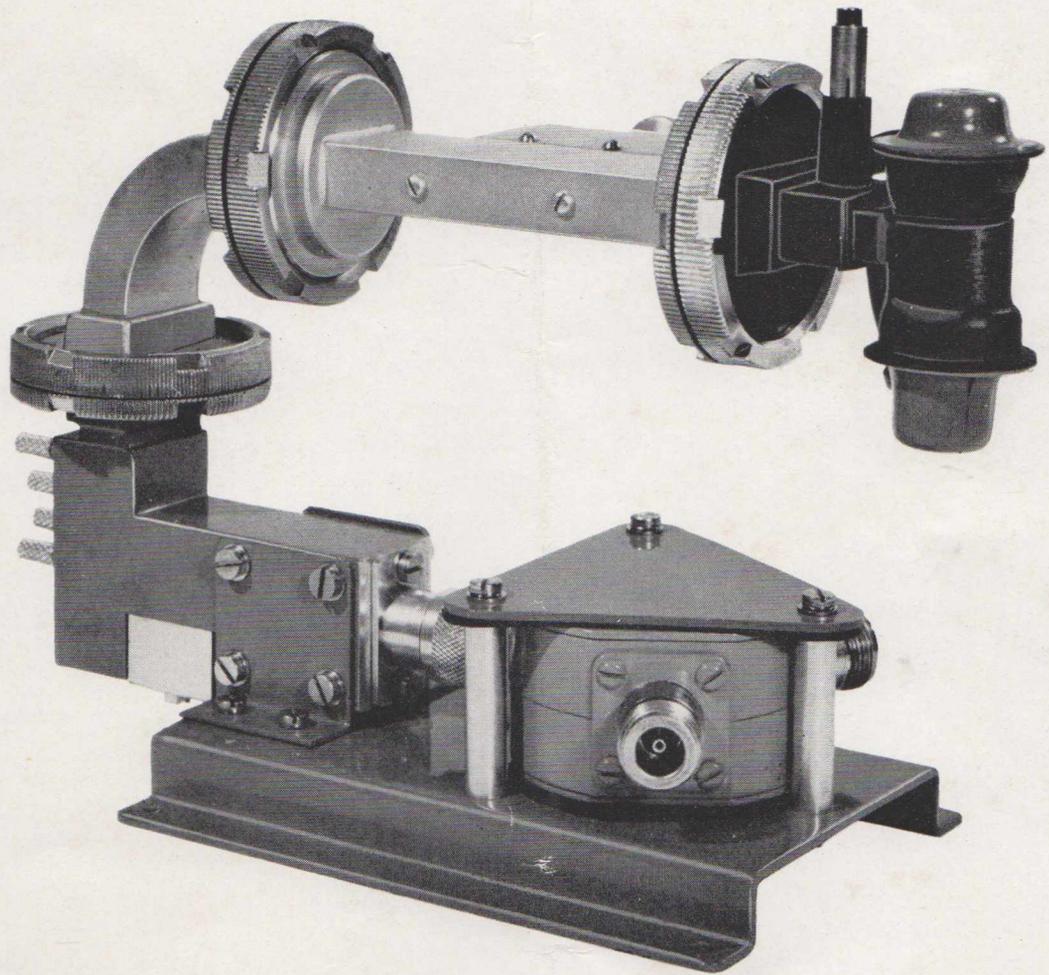


# Mullard Outlook

AUSTRALIAN EDITION



VOL. 6. No. 4  
JULY-AUGUST, 1963



MULLARD-AUSTRALIA PTY. LTD.



VOL. 6 — No. 4.

JULY-AUGUST, 1963


Editorial Office:  
35-43 Clarence Street, Sydney.  
Telephone: 29 2006

Editor:  
**JOERN BORK**

All rights reserved by Mullard-Australia Pty. Ltd., Sydney. Information given in this publication does not imply a licence under any patent. Original articles or illustrations reproduced in whole or in part must be accompanied by full acknowledgement: Mullard Outlook, Australian Edition.

### TABLE OF CONTENTS

|   | Page |
|---|------|
| Editorial .....   | 50   |
| Viewpoint with Mullard .....                            | 51   |
| Transistorised Modulator for Mobile Installations ..... | 52   |
| New 100 Litre per Second Penning Pump .....             | 57   |
| Silicon P-N-P Transistors; BCY38, 39, 40 .....          | 57   |
| Vinkor Manual .....                                     | 57   |
| New 23-inch Picture Tube AW59-91 .....                  | 58   |
| Silicon Rectifiers; OA605, OA610 .....                  | 58   |
| Power Output Transistor; AD139 .....                    | 58   |
| Preferred Semiconductors:                               |      |
| The AF114N Series .....                                 | 59   |
| Mercury Thyatron; ZT1000 .....                          | 59   |
| Voltage Reference Tube ZZ1000 .....                     | 59   |
| Mullard Photoemissive Cells .....                       | 60   |

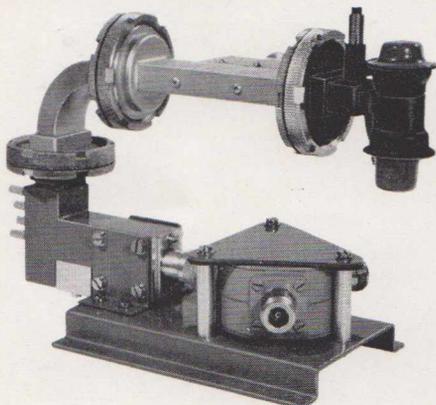

*This S-Band Solid State Parametric Amplifier is for operation over a frequency range of 2.7Gc/s to 3.3Gc/s. It has a bandwidth of 25Mc/s and a noise figure as low as 3dB. Tuning over the 500Mc/s frequency range can be achieved by adjustment of the pump frequency and power level without alteration to the amplifier or the circulator. Pump power is provided by a suitable klystron.*

### MULLARD-AUSTRALIA PTY. LTD.

35-43 CLARENCE STREET, SYDNEY  
Phone: 29 2006

123-129 VICTORIA PDE., COLLINGWOOD, N.5  
VICTORIA

Phone: 41 6644

Associated with  
MULLARD LTD., LONDON

## Some Play It By Ear

My thoughts on this particular editorial commenced as a cross between "East Lynne" and "Eric, or Little by Little" — something of a dilemma, poignant and courageous. When matched with to-day's telly and barely provoking reproachful criticism against the bizarre repertoire of 1963 youthful endeavour, it is directed towards the need for skilled technicians in the art of servicing transistor equipped devices. Trite nonsense to some, but to most the profound and inevitable desire to achieve.

For AM radio service and those who played it by ear, a well used test instrument was a slender screwdriver, preferably with insulated handle, augmented by the other well tried methods of brute force and ignorance, or suck it and see.

The fascinating and expanding world of semiconductors has a romance far removed from Fleming and de Forest. No wonder then our desire as semiconductor principals to assist in the training of technicians and offering our particular experience and skill in the application of semiconductors.

No question of playing it by ear, as also our customers right along the line; those who incorporate semiconductors in equipment for re-sale, retailers selling the end product, design engineers contemplating the use of semiconductors — they all know, with sound engineering abounding, the end product equipped with Mullard semiconductors can only enhance their sales, their profits and their prestige.

M.A.B.

### MULLARD DISTRIBUTORS

#### New South Wales

Martin de Launay Pty. Ltd.  
Cnr. Druitt & Clarence Sts.,  
Sydney. Phone: 29 5834  
Cnr. King & Darby Streets,  
Newcastle. Phone: 2 4741  
144 Keira St., Wollongong.  
Phone: 2 6020  
21 Bayliss Street, Wagga.  
Phone: 4644

#### Victoria

Howard Electrical & Radio  
Company.  
Vere Street, Richmond.  
Phone: 42 4716

#### South Australia

Agents:  
Woollard & Crabbe Limited  
180 Wright Street West,  
Adelaide. Phone: 51 4713

#### Western Australia

Tedco Pty. Ltd.  
7 Fitzgerald Street, Perth.  
Phone: 28 4921

#### Queensland

C. A. Pearce & Co. Pty. Ltd.  
33 Bowen Street, Brisbane.  
Phone: 2 3201  
13 Palmer St., Townsville.  
Phone: 5864

#### Tasmania

Medhursts Wholesale Ltd.  
163 Collins Street, Hobart.  
Phone: 2 2911  
136 Wellington Street,  
Launceston. Phone: 2 2091  
106 Wilson Street, Burnie.  
Phone: 1919

and all leading wholesalers throughout the Commonwealth

# VIEWPOINT WITH MULLARD

## KNOW YOUR TRANSISTORS

### Don't be Scared of Them

It was a toss up whether the analogous drawing would be Little Miss Muffet or one of our typists making an hysterical and noisy effort to avoid a mouse. Miss Muffet won, solely on the score that most transistors look more like a spider than a mouse. But transistor circuit techniques to the capable technician are as frightening as a mouse and a mouse far less than *Antrax robustus*\* and here the confusion must finish.



### The Field

It is estimated that in the comparatively small Australian consumer domestic equipment market approximately 3,600,000 transistors and 2,000,000 semiconductor diodes will be absorbed this calendar year in new AM receivers alone. Add to this the number of present exotic and near exotic semiconductors used in telecommunications, professional and industrial electronic equipment and all the semiconductors already in service in Australia and we have only the beginning of an era.

Relate this to the research development and production of these devices elsewhere, the increasing tempo, the improvements, the tailoring of new types for a specific purpose, and the seeking of new applications for the types designed for other purposes, and this is where we came in!

### Know your Product

Hackneyed these days and hammered into the salesmen at every consumer product sales conference and convention. By some now treated as a joke, with the back benchers chanting steadily and precisely "Next — Saturday — night, or rather Know Your Product, etc., etc." The technician *must* also know the product, why it works, how it works and how to swiftly fix it when it works erratically or stops working and there is going to be an awful lot of transistor equipped devices in service.

### First Steps

As we at Mullard design, develop and make these things we need to know a bit about them, in fact we believe we are quite good at it, having been debunked and deflated on many occasions, and likely

\* *Antrax robustus*: the Sydney Funnel-Web Spider, generally black to red-brown in colour, about 1" in body length. ("Know Your Spiders & Ticks" by B. Hadlington).

to be at any time. The 1963 boys at school make transistor sets and talk transistors long before they talk valves, which seem to be old stuff to them. The old campaigners, long since left the bench, getting bogged down with an avalanche (*sic*) of types and data. Our advice to them is to play with a few basic transistors in basic circuits, altering component values and looking at bottoming and what Zener gave his name to, rather than who he was.

### Next Steps

By this time one is better fitted to do some selected reading, then tackle a composite device, perhaps a piece of useful test gear—or even a complete receiver! The latter, a good exercise after cleaning up the audio, sorting out the A.G.C. and taming the mixer. Back to the reading and perhaps a nibble at fancy control circuits or a closer examination of  $\alpha$ ,  $\beta$  and  $\theta$ , and in no time the new experts are confident the original designer's compromise was inadequate or overdone and components values are changed, to say nothing of this new thing—spread.

### The Touch

Touch and spread must be difficult words to the newcomer in English, particularly the mercenary translation of touch, and perhaps a better choice of word—feel, for the good technician must have a feeling for his work and a feel for transistors, much as the good linguist thinks in the language he is using, a good transistor technician thinks in semiconductors.

### 220 Attend Transistor Lectures

This language theme was emphasised by our General Manager, Mr. M. A. Brown, at the concluding night of a series of successful lectures on transistor receiver servicing recently held by Pye Industries Ltd. in Sydney and being repeated in other States. Mr. Brown complimented Mr. P. M. Threlfall, Pye Managing Director, and Harry Dennis, Pye Technical Liaison Officer, for their enterprise in seeing the need and arranging the lectures, which were presented by Mr. R. L. Webb, Mullard-Australia Senior Applications Engineer. At the final function the top student Ernie Venturato (specialist technician) of Eric Anderson's was presented with a AVO Multi-minor MK4, as also was the runner-up Bob Hedger of Reg. Lindsay Service Co., Wollongong. At the function Mr. Os Mingay said that the manufacturer could teach the technician many things and he commended the 220 technicians who attended the course for their enthusiasm and went on to say "All servicemen must be good salesmen—sell yourself, your service, your company and finally sell your product".

Pye Australasian Sales Manager, Bob Toone, reminded servicemen of their need for good customer relations in supporting the original sale and future sales and said "unless a favourable image is created by word of mouth we are both out of business. Consider this and aim for it. It is not enough just to fix up the problems. You must keep yourself sold to keep your company profitable and create a better image all round."

## MULLARD-AUSTRALIA PERSONALITIES



MR. T. DUNCAN

Tom Duncan, senior sales clerk in the Professional and Industrial Department, joined Mullard some three years ago, bringing with him a background of twelve years' experience in the electronics industry, including several years with the Newcastle branch of our New South Wales distributor, Martin de Launay Pty. Ltd.

He needs no introduction to our customers in the Professional and Industrial fields and Government Departments who, whilst they may not have met him personally, know Tom through contact over the 'phone and at some time or another have been grateful for his assistance with the "hard ones".

Having recently moved into a new home with his wife and two year old daughter, Tom's leisure time is divided between laying out lawns and gardens and setting up a darkroom to further his hobby—photography.



Mr. M. A. Brown congratulates top student Ernie Venturato

### Training Aids and Facilities

From time to time we publish in Outlook a current list of Mullard 16 mm sound films, film strips, education series pamphlets, broadsheets and booklets, and many Outlook readers are subscribers to our advanced professional publications. We

Continued on page 58

# Transistorised Modulator for Mobile Installations

The prototype modulator was based on the public address amplifier described in Chapter 17 (page 175) of the Mullard "Reference Manual of Transistor Circuits" (available from Mullard offices and distributors throughout the Commonwealth at 15/- plus 1/5d postage).

Following construction of the prototype it became obvious that there was a need for modulator designs of even higher power ratings and as a result three basic designs of 15W, 25W and 40W, are presented herein to cater for AM transmitters having a maximum DC input to the final RF amplifier of up to 80W.

When used with a valve transmitter having a transistorised power supply (see Outlook Vol. 4 No. 2) the standby current


drawn on the battery may be reduced to that required to supply the heaters of the RF valves in the transmitter. The availability of quick heating valves such as the QZ06-20, etc. (see Outlook Vol. 6 No. 2) will enable the transmitter standby current to be eliminated and such a transmitter, when used in conjunction with a fully transistorised receiver, will result in an AM installation which is capable of approaching the ultimate in battery economy for a given RF power output.

The power frequency response of the original design has been modified by changing component values in order to achieve a roll-off of some 12dB per octave below 300 c/s and above 3000 c/s. This form of speech processing is highly

desirable since it contributes both to an increase in modulation efficiency and a reduction in transmitted signal bandwidth. Home constructors wishing to change the degree of speech processing may experiment with coupling and emitter bypass capacitors to achieve the desired results.

The microphone used in the prototype amplifier, Zephyr Products Insert type 192 is of the electro-magnetic rocking armature type and has an impedance rating of 2000Ω, thus enabling it to be connected to the input of the first transistor without the need for a matching transformer. The sensitivity of all three modulators is sufficient to achieve full output with this microphone at the appropriate gain control settings.

Fig. 1—Basic Pre-amplifier and Driver Stages and 15W Modulator Output Stage

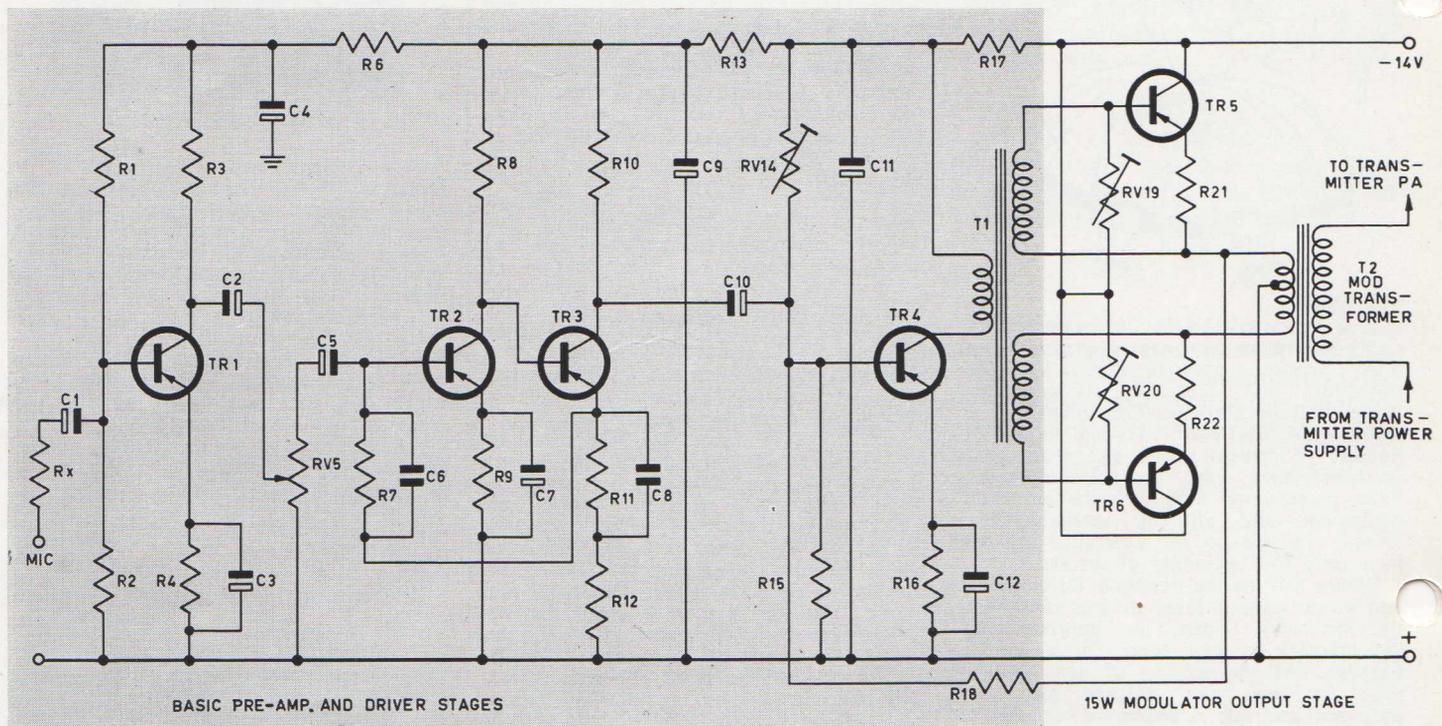

## COMPONENT PARTS LIST FOR PRE-AMPLIFIER AND DRIVER STAGE

### Resistors

| Circuit Reference | Value      | Tolerance (±%)          | Rating (W) |
|-------------------|------------|-------------------------|------------|
| Rx                | (see text) |                         |            |
| R1                | 18 kΩ      | 10                      |            |
| R2                | 10 kΩ      | 10                      |            |
| R3                | 3.9kΩ      | 10                      |            |
| R4                | 3.9kΩ      | 10                      |            |
| RV5               | 10 kΩ      | log pot.                |            |
| R6                | 1 Ω        | 10                      |            |
| R7                | 2.2kΩ      | 10                      |            |
| R8                | 1.8kΩ      | 10                      |            |
| R9                | 1.0kΩ      | 10                      |            |
| R10               | 270 Ω      | 10                      |            |
| R11               | 270 Ω      | 10                      |            |
| R12               | 3.3 Ω      | 10                      |            |
| R13               | 68 Ω       | 10                      |            |
| *RV14             | 1 kΩ       | WW trim pot. (see text) |            |
| R15               | 220 Ω      | 10                      | ½          |
| R16               | 22 Ω       | 10 (see text)           | ½          |
| R17               | 3.9 Ω      | 5                       | 3          |

### Capacitors

| Circuit Reference | Value (μF) | Tolerance (±%) | Description  | Rating (VW) |
|-------------------|------------|----------------|--------------|-------------|
| C1                | 4.0        | 10             | electrolytic | 6           |
| C2                | 10.0       | 10             | "            | 12          |
| C3                | 25.0       | 10             | "            | 6           |
| C4                | 100        | 10             | "            | 12          |
| C5                | 10         | 10             | "            | 12          |
| C6                | 0.03       | 10             | polyester    | 125 Volts   |
| C7                | 50         | 10             | electrolytic | 6           |
| C8                | 100        | 10             | "            | 6           |
| C9                | 100        | 10             | "            | 12          |
| C10               | 4          | 10             | "            | 12          |
| C11               | 1000       | 10             | "            | 12          |
| C12               | 100        | 10             | "            | 12          |

T1. Driver Transformer: Turns Ratio 2:1+1. Secondary wound bifilar. Primary DC resistance, ≤5Ω. Secondary DC resistance 5Ω+5Ω (see Fig. 4). National Transformer type D5437 requires 1.5Ω additional resistance in series with each half secondary for 15W and 25W designs.

**Mullard Transistors**  
 TR1: OC71 or AC125; TR2: OC71 or AC125; TR3: OC74, OC74N or AC128; TR4: OC26.

## COMPONENT PARTS LIST FOR 15W OUTPUT STAGE

### Resistors

| Circuit Reference | Value | Tolerance (±%)          | Rating (W) |
|-------------------|-------|-------------------------|------------|
| R18               | 3.3kΩ | 10                      | ½          |
| *RV19             | 500 Ω | WW trim pot. (see text) |            |
| *RV20             | 500 Ω | WW trim pot. (see text) |            |
| R21               | 0.5 Ω | 5                       | 3          |
| R22               | 0.5 Ω | 5                       | 3          |

### Mullard Transistors

TR5 2-OC26 (matched pair)  
 TR6 Heat sinks 2 Ferris 7000  
 T2 Modulation Transformer A&R MT26 or similar.

\* May be replaced by a fixed resistor after adjustment and measurement.

\* May be replaced by a fixed resistor after adjustment and measurement.

### Basic Pre-amplifier and Driver Stages

The use of a basic pre-amplifier and driver stage (see shaded area of Fig. 1) increases the flexibility of the overall design inasmuch as the output stage may be changed at any time without the need for modification of the basic unit. Whilst it will be obvious that the sensitivity of the modulator will be reduced when changing from a 15W output stage to a 40W output stage, there is still more than sufficient gain available to enable the use of the microphone insert type referred to above. This unit is capable of an output of 10 to 20mV peak-to-peak across 2000Ω, dependent of course on voice level.

Resistor Rx may be adjusted by substitution of lower values where increased sensitivity is required. As a guide, the recommended value for the 25W unit, when using the Zephyr Insert 192, is 6.8k. The 2000Ω resistor provides correct microphone matching, whilst Rx in conjunction with the input impedance of the first stage provides attenuation. This gives a useful range of control with RV5. The method of connection is shown in Fig. 2.

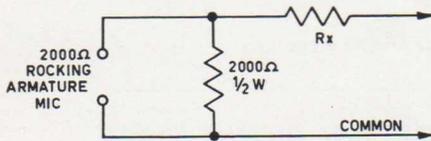


Fig. 2

Should home constructors wish to use a standard carbon microphone, the first transistor stage may be omitted, in which case the method of connection is as shown in Fig. 3.

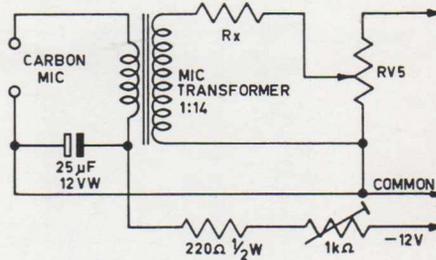


Fig. 3

Using the interstage transformer shown in the Parts List, the quiescent current of the OC26 driver should be set to 175mA by adjustment of RV14 with an applied voltage of 14V. Following adjustment, the resistance of RV14 may be measured and a suitable fixed resistor substituted.

The collector dissipation will be approximately 2W under "no signal" conditions, reducing to a lower value under "drive". Whilst the heat sink requirements of this stage are not stringent, the use of a Ferris type 7000 heat sink will be found most convenient.

The gain of the unit is quite high and normal layout precautions should be employed in constructing the pre-amplifier and driver. It is anticipated that a printed wiring board will become available for mounting the components from the microphone input to the OC26 driver. The interstage transformer and OC26 may be mounted on the chassis using a mica insulating washer for the OC26.

R18 may be adjusted to provide any desired degree of feedback up to a level somewhat below the stability margin, however, the recommended value of 3.3kΩ for the 15W unit will be found quite satisfactory for the 25W and 40W modulators.

### 15W MODULATOR

In this instance, the original design (see circuit page 176 "Reference Manual of Transistor Circuits") may be converted to a modulator by merely replacing the centre-tapped audio output choke by a transformer having the correct turns ratio to reflect a load of 15Ω to the primary (see non-shaded area Fig. 3).

Such a unit is the A&R MT26 which, when terminated at the nominal 4000Ω tap with a modulating impedance of 4760Ω, will provide a correct match.

For example, a transmitter having an applied power to the final stage of 380W at 80mA requires a modulating impedance of

$$\text{Mod } Z = \frac{380}{80 \times 10^{-3}} = 4750\Omega.$$

$$\text{Power input to final} = 380 \times 80 \times 10^{-3} = 30.4\text{W}.$$

This represents an ideal application for the 15W modulator using the A&R MT26 modulation transformer.

The quiescent current for the OC26 output transistors should be set to 30mA for each output transistor by adjustment of RV19 and RV20. Following adjustment, the resistance of the preset pots may be measured and fixed resistors substituted.

With the method of bias stabilisation employed it is important that the resistance of each half of the driver transformer secondary should be adjusted to 5Ω by the insertion of additional resistance R if necessary (see Fig. 4).

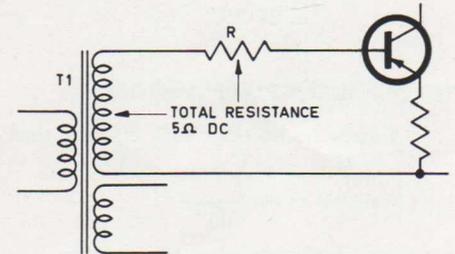


Fig. 4

### 25W MODULATOR

The design procedures for the 25W and 40W modulator designs make certain assumptions and because of this it is desirable for home constructors to carry out a complete set of measurements on the output stage to ensure that the output transistors are operating within the limits set down in the published data.

These simplified design procedures make it possible for home constructors without a great deal of experience with semiconductors, to design output stages for public address amplifiers and modulators. The procedures are based on the information contained in Chapters 9, 13, 14 and 17 of "Mullard Reference Manual of Transistor Circuits" and represent a quite practical approach to the design of Class 'B' output stages.

This unit is an extension of the former 15W Modulator with the substitution of OC29's for the OC26's in the output stage, thus enabling the higher values of peak current to be provided to achieve a power output of 25W (see Fig. 5).

(1) **Load impedance** — To allow for losses in  $R_c$  ( $0.15\Omega$ ) and the modulation transformer a total AC power from the supply of 32W will be assumed. The power supply rail will be 14V.

$$P_{AC} = \frac{(V_{cc})^2}{2R_{cc}}$$

$V_{cc}$  = supply rail voltage.

$R_c$  = load presented to collector circuit of one transistor.

$R_{cc}$  =  $R_c + R_e$ .  $R_e$  is chosen to be  $0.15\Omega$  for adequate stability.

Therefore:—

$$R_{cc} = \frac{(V_{cc})^2}{2P_{AC}} = \frac{14^2}{2 \times 32} = 3.06\Omega.$$

(2) **Knee Voltage** —  $\tan \phi$  for OC29 is a constant having a value of 0.1Ω.

$$\text{Max output voltage} = \frac{V_{cc} \times R_{cc}}{R_{cc} + \tan \phi}$$

where  $\tan \phi$  = slope of transistor knee characteristic expressed as a resistance.

therefore

$$V_{\text{out(pk)}} = \frac{14 \times 3.06}{3.06 + 0.1} = 13.55\text{V}.$$

(3) Output current

$$\begin{aligned} \text{Max output current} &= \frac{V_{cc(pk)}}{R_{ce} + \tan \phi} \\ &= \frac{13.55}{3.06 + 0.1} \\ &= 4.3 \text{ A.} \end{aligned}$$

(4) Max output power

$$\begin{aligned} P_{tot} &= \frac{V_{cc(pk)} \times I_{c(pk)}}{2} \\ &= \frac{13.55 \times 4.3}{2} \\ &= 29.2 \text{ W.} \end{aligned}$$

(5) Useful output power in primary of modulation transformer

$$\begin{aligned} P_{out} &= \frac{P_{tot} \times R_c}{R_{ce}} \\ &= \frac{29.2 \times 2.91}{3.06} \\ &= 27.7 \text{ W.} \end{aligned}$$

(6) Modulating Power Available

Assume transformer 90% efficient, then

$$\begin{aligned} \text{Power available} &= \frac{27.7 \times 90}{100} \\ &= 24.9 \text{ W.} \end{aligned}$$

(7) Load  $R_{(c-o)}$

$$\begin{aligned} R_{(c-o)} &= R_c \times 4 = 2.91 \times 4 \\ &= 11.64 \Omega. \end{aligned}$$

Using the component values shown in the Parts List and recalculating for an 11.64Ω load 12V and 16V supply rails:—

| Supply rail          | 12V   | 16V     |
|----------------------|-------|---------|
| $V_{out(pk)}$        | 11.62 | 15.5 V  |
| $I_{out(pk)}$        | 3.68  | 4.9 A   |
| $P_{tot}$            | 21.4  | 38 W    |
| $P_{out(primary)}$   | 20.4  | 36.2 W  |
| $P_{out(secondary)}$ | 18.36 | 32.58 W |

The above figures show the spread of output power with changes in supply voltage and emphasise the need to provide good power supply regulation.

The resistance of each half of the driver transformer secondary should be made up to 5Ω for bias stabilisation (see Fig. 4).

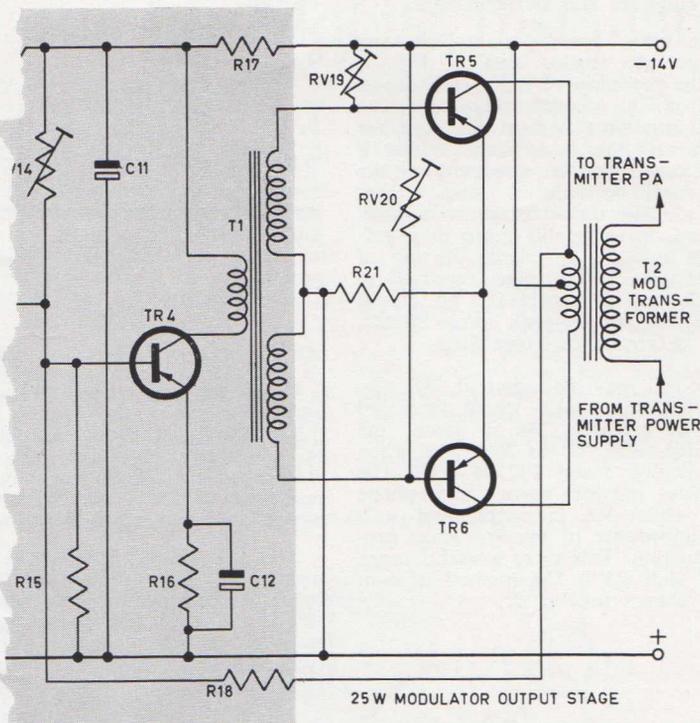


Fig. 5—25W Modulator Output Stage

COMPONENT PARTS LIST FOR 25W OUTPUT STAGE

| Circuit Reference | Value  | Tolerance (±%) | Rating (W)              |
|-------------------|--------|----------------|-------------------------|
| <b>Resistors</b>  |        |                |                         |
| R18               | 3.3 kΩ | 10             | ½                       |
| *RV19             | 1 kΩ   |                | WW trim pot. (see text) |
| *RV20             | 1 kΩ   |                | WW trim pot. (see text) |
| R21               | 0.15 Ω | 5              | 5                       |

Mullard Transistors

TR5  
TR6                    2-OC29 (matched pair)

Heat Sinks 2 Ferris 7000

Modulation Transformer turns ratio to reflect 11.64Ω between collectors OC29's. Primary wound bifilar  $R_p < 0.1 \Omega$  per side.

\* May be replaced by a fixed resistor after adjustment and measurement.

**Heat Sink Requirements**—With a Class 'B' stage maximum dissipation per transistor

$$P_c = \frac{2}{\pi^2} \times \frac{(V_{cc})^2}{2R_{ce}} \approx \frac{1}{5} P_{tot}$$

now since, with the 25W design  $P_{tot} = 29.2 \text{ W}$

$$P_c \text{ (per transistor)} = \frac{29.2 \text{ W} \times 1}{5} = 4.82 \text{ W.}$$

From OC29 data:—

$$P_c = \frac{T_{j(max)} - T_{(amb)}}{\theta_{j-amb}}$$

$\theta_{j-amb}$  (when using a mica washer coated with silicone grease between the transistor and a Ferris 7000 heat sink)

$$\begin{aligned} &= \theta_{case} + \theta_i + \theta_h \\ &= 1.5^\circ \text{C/W} + 0.5^\circ \text{C/W} \\ &\quad + 3.6^\circ \text{C/W} \\ &= 5.6^\circ \text{C/W.} \end{aligned}$$

For continuous operation  $T_{j(max)} = 90^\circ \text{C}$  therefore the maximum permissible ambient temperature

$$\begin{aligned} T_{(amb)} &= T_{j(max)} - \theta_{j-amb} \\ &= 90 - (4.82 \times 5.6) \\ &= 63^\circ \text{C.} \end{aligned}$$

### 40W MODULATOR

Where higher output powers are required, the 40W modulator design is recommended (see Fig. 6) and the following calculations show how a nominal 40W may be obtained from a matched pair of OC29's and a 14V supply rail. As a compromise between the requirements of temperature stabilisation and minimisation of cross-over distortion, the quiescent current will be set to 60mA for the matched output transistors (i.e. 30mA per transistor).

- (1) **Load impedance** — to allow for losses in  $R_e$  and modulation transformer, for an output of 40W, assume an initial value of 60W with a 14V supply rail. Then

$$P_{AC} = \frac{(V_{cc})^2}{2R_{ee}}$$

$V_{cc}$  = supply rail voltage.  
 $R_e$  = load presented to collector circuit for one transistor.  
 $R_{ee}$  =  $R_e + R_e$ .  $R_e$  is chosen to be 0.15Ω for adequate stability.

Now

$$R_{ee} = \frac{(V_{cc})^2}{2P_{AC}} = \frac{14^2}{2 \times 60} = 1.63\Omega$$

- (2) **Knee Voltage** —  $\tan \phi$  for OC29 is a constant having a value of 0.1Ω.

$$\text{Max output voltage} = \frac{V_{cc} \times R_{ee}}{R_{ee} + \tan \phi}$$

Therefore

$$V_{out(pk)} = \frac{14 \times 1.63}{1.63 + 0.1} = 13.2V$$

- (3) **Output current**

$$\text{Max output current} = \frac{V_{cc(pk)}}{R_{ee} + \tan \phi}$$

Therefore

$$I_{out(pk)} = \frac{13.2}{1.63 + 0.1} = 7.63A$$

- (4) **Max output power**

$$P_{tot} = \frac{V_{cc(pk)} \times I_{c(pk)}}{2} = \frac{13.2 \times 7.63}{2} = 50W$$

- (5) **Useful output power in Primary of Modulation Transformer**

$$P_{out} = P_{tot} \times \frac{R_e}{R_{ee}} = 50 \times \frac{1.48}{1.63} = 45W$$

- (6) **Modulating power available** — assume transformer 90% efficient.

Then power available in secondary

$$= \frac{45 \times 90}{100} = 39.5W$$

- (7) **Load  $R_{(e-c)}$**

$$R_{(e-c)} = R_e \times 4 = 1.48 \times 4 = 5.92\Omega$$

Using the component values given above and re-calculating for a 5.92Ω load 12V and 16V supply rails:—

| Supply Rail          | 12V  | 16V    |
|----------------------|------|--------|
| $V_{out(pk)}$        | 11.3 | 15.1 V |
| $I_{out(pk)}$        | 6.53 | 8.73 A |
| $P_{tot}$            | 32   | 66 W   |
| $P_{out(primary)}$   | 29   | 60 W   |
| $P_{out(secondary)}$ | 26.1 | 54 W   |

Whilst the output power may appear at first sight to be unduly dependent on supply voltage, it must be realised that the DC input to the RF section of the transmitter will vary with supply rail voltage changes, irrespective of whether a vibrator, genmotor or DC-DC converter is

employed for the HT supply. This, in some measure, tends to level out the effect of supply rail variations and results in a sound, practical design.

#### Heat Sink requirements

With a Class 'B' stage maximum dissipation per transistor

$$P_c = \frac{2}{\pi^2} \times \frac{(V_{cc})^2}{2R_{ee}} \approx \frac{1}{5} P_{tot}$$

now since with the 40W design  $P_{tot} = 50W$

$$P_c \text{ (per transistor)} = \frac{50 \times 1}{5} = 10W$$

From OC29 data:—

$$P_c = \frac{T_{j(max)} - T_{(amb)}}{\theta_{j-amb}}$$

$\theta_{j-amb}$  (when using a mica washer coated with silicone grease between the transistor and a Ferris 7001 heat sink)

$$= \theta_{case} + \theta_i + \theta_h = 1.5^\circ C/W + 0.5^\circ C/W + 2.1^\circ C/W = 4.1^\circ C/W$$

For intermittent operation  $T_{j(max)} = 100^\circ C$ , therefore the maximum permissible ambient temperature

$$T_{amb} = T_{j(max)} - 10(\theta_{j-amb}) = 100 - (10 \times 4.1) = 59^\circ C$$

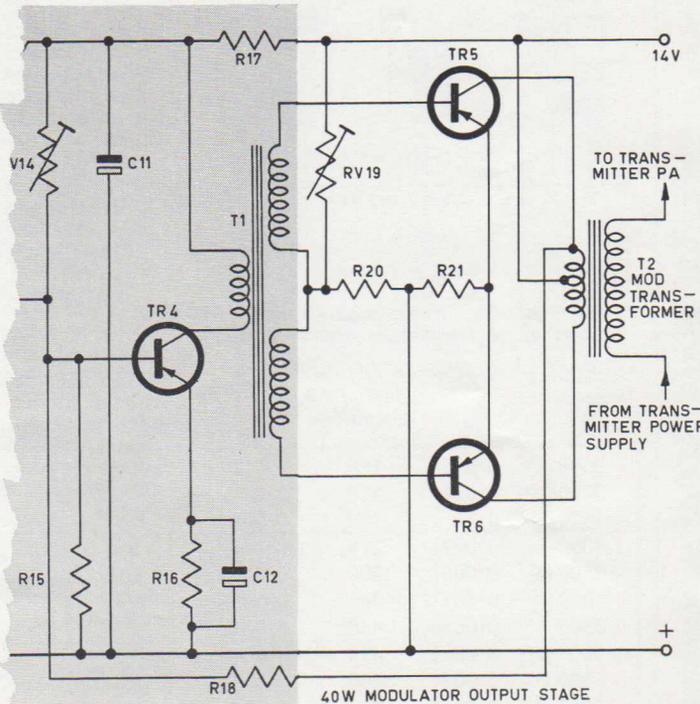


Fig. 6—40W Modulator Output Stage

### COMPONENT PARTS LIST FOR 40W OUTPUT STAGE

#### Resistors

| Circuit Reference | Value | Tolerance (±%) | Rating (W)    |
|-------------------|-------|----------------|---------------|
| R18               | 3.3kΩ | 10             | ½             |
| *RV19             | 500Ω  | WW trim pot.   | 5W (see text) |
| R20               | 3.9Ω  | 5%             | 1             |
| R21               | 0.15Ω | 10             | 7             |

#### Mullard Transistors

TR5 TR6 2-OC29 (matched pair)

#### Heat Sinks

- 1 Ferris 7000
- 2 Ferris 7001

Modulation Transformer turns ratio to reflect 6Ω between collectors of OC29's.

Primary wound bifilar  $R_p < 0.1\Omega$  per side.

\* May be replaced by a fixed resistor after adjustment and measurement.

## 40W Modulator (Continued)

### Drive requirements

- (1) Transistor gain spreads dictate that lowest gain transistors are assumed to be in use and a lower limit OC29 will have a large signal current gain in common emitter of

$$\frac{1}{a} \approx 35$$

Therefore drive current

$$i_b = \frac{i_e}{a} = \frac{7.63}{35} = 218\text{mA.}$$

### (2) Drive voltage required

$$(a) V_{\text{drive}} = (i_e - 2I_q) R_e + V_{\text{be}(i_e)} - V_{\text{be}(I_q)} + i_b R_b$$

Where

$i_e$  = peak emitter current  
 $I_q$  = 30mA per transistor chosen as a compromise between linearity and temperature stability

$V_{\text{be}(i_e)}$  = peak base-emitter voltage for  $i_e$

$R_b$  = 5Ω for a practical transformer.

- (b) From OC29 data and 40W design above:—

$$V_{\text{drive}} \approx 2.8\text{V}$$

### (3) Drive power (RMS)

$$= \frac{1}{2} (i_b \times V_{\text{drive}}) \\ = \frac{0.218 \times 2.8}{2} \\ = 305\text{mW.}$$

### (4) Drive impedance $Z_b$

$$= \frac{V_{\text{drive}}}{i_b} \\ = \frac{2.8}{0.218} \approx 13\Omega$$

therefore

$$Z_{b-b} = 13 \times 4 = 52\Omega.$$

### Driver Stage

To ensure that adequate drive is available under all conditions, the driver should be capable of providing an output power of 750mW.

An OC26 in Class 'A' is capable of achieving this figure and the ready availability of interstage transformers having a turns ratio of 2 : 1 + 1, with the two halves of the secondary wound bifilar suggests the choice of this ratio.

Such a transformer, under maximum drive conditions, will reflect an impedance of 52Ω into the primary winding and an OC26 operating at a quiescent current of 175mA will provide an output power approaching 800mW which is quite sufficient to accommodate circuit losses at the same time providing the desired drive to the final stage, i.e.,

$$P_{\text{out(max)}} = \frac{1}{2} I_q^2 R_L \\ = \frac{(0.175)^2 \times 52}{2} \\ = 796\text{mW.}$$

This stage in turn is adequately driven by an OC74, OC74N or AC128.

## ADDITIONAL NOTES

### High-level Clipping

The circuit of a typical high level clipper is shown in Fig. 7. It is fully automatic in operation and allows extension of the positive peaks of modulation whilst, at the same time, limiting the negative peaks.

Since a form of splatter may result from clipping of the negative modulation peaks, it is essential to follow the clipper with a low pass filter placed between the secondary of the modulation transformer and the RF power amplifier.

Capacitors C2, C3 and C4, in conjunction with choke L form the low pass filter, whilst an additional constant k section is provided by the leakage inductance of the modulation transformer secondary in conjunction with C1 and C3.

The Table gives details of the values of L and C for a wide variety of modulating impedances, however C1 is dependent on the inductance of the modulation transformer secondary and some experimentation may be necessary. As a starting point a value of 0.001μF is a good choice.

A suitable clipping diode may be selected from the range of silicon power diodes now available for power rectification. In practice, the OA210 will be satisfactory in most applications involving HT supplies up to 400V. Above this figure the OA211 is recommended.

The RF plate supply bypass capacitor in the transmitter may be modified to act as C4 by changing it to the correct value.

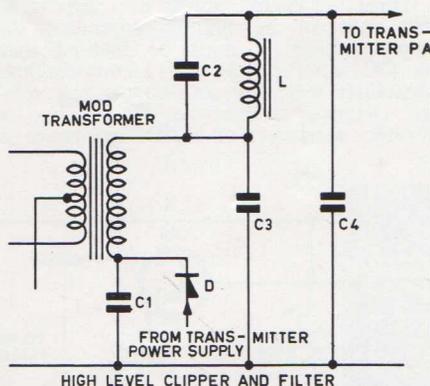


Fig. 7

\*Table showing component values for attenuation of frequencies above 3000 c/s.

| Modulating Impedance (Ω) | C3, C4 (μF) | L1 (mH at PA operating current) | C2 (μF) |
|--------------------------|-------------|---------------------------------|---------|
| 2500                     | 0.015       | 180                             | 0.011   |
| 3000                     | 0.013       | 210                             | 0.01    |
| 3500                     | 0.11        | 250                             | 0.0085  |
| 4000                     | 0.009       | 270                             | 0.007   |
| 4500                     | 0.008       | 300                             | 0.0062  |
| 5000                     | 0.007       | 380                             | 0.0055  |
| 5500                     | 0.0066      | 420                             | 0.0052  |
| 6000                     | 0.0062      | 470                             | 0.0047  |
| 6500                     | 0.006       | 500                             | 0.0043  |
| 7000                     | 0.0055      | 540                             | 0.004   |
| 7500                     | 0.005       | 580                             | 0.0038  |

### Construction and Installation

- When constructing mobile equipment it is essential to ensure that heavy components are securely mounted and this applies equally in the case of transistorised equipment.
- Reliability under high ambient temperatures dictates the use of effective heat sinks. It is preferable to err on the generous side when designing high-power transistor devices.
- Where the modulator is built as an integral part of the transmitter, the transistors should be isolated from the high power RF amplifier as induced RF can cause heating of the transistor junction, apart from difficulties associated with RF feedback. Ensure that the inherent temperature rise is not excessive and provide some means of effective convection cooling or provide a blower to increase air circulation.
- Transistors are less tolerant of load changes than valves. Attempt to achieve as perfect a match as possible between the transmitter modulating impedance and modulator load.
- Fit fuses of correct minimum values, preferably of the English Electric "quick blow" type. Do not use a 20A fuse where a 5A unit is adequate.
- Arrange switching sequences so that a load is always presented to the modulator. For example, make sure that the transmitter final is providing output before power is applied to the modulator. The reverse sequence should apply on switch-off. This may be achieved by an interlocking circuit, operated by sampling the RF output, rectifying and amplifying the sample and using it to close a relay which applies power to the modulator.  
A less sophisticated, but quite practical, method is to fit an RF indicator at the operating position and refrain from speaking into the microphone until an indication of RF output appears.
- For hand-held microphones, the Zephyr Rocking Armature Insert type 192 is excellent, however, where a lighter insert suitable for a boom extension on a headband is required, the M4 hearing-aid insert may be preferred.

The filter capacitors must have a working voltage rating at least 3 times the RF amplifier supply voltage and the choke L should preferably have high voltage insulation between the winding and core or, alternatively, may be insulated from the chassis.

The rated inductance of the choke, which should not approach saturation, should be achieved at the desired DC current level.

\*Reference: CQ Mobile Handbook, First Edition (1963).

B. P. A. Beresford.

# 100 LITRE PER SECOND PENNING PUMP

Latest addition to the wide range of Mullard ultra-high vacuum devices\* is a new 100 litre per second pump type number VPP-100.

This pump, which is continuous in operation, is based on the principle of the Penning gauge, in which electrons are made to oscillate between cold cathodes. A magnetic field perpendicular to the direction of electron movement causes the electrons to traverse spiral paths as they oscillate in the electrostatic field formed by the cathodes and the anode. Ions produced by these electrons are accelerated to the cathodes and liberate more electrons, the combined action being self-supporting.

The pump comprises many Penning electrode units in parallel using common titanium cathodes on each side of a nest of anodes. During operation, the titanium sputters from the cathode, forming fresh surfaces which getter very actively.

The size, shape, pumping speed and bake-out temperature of the VPP-100 make it particularly suitable for use in nuclear physics and space research. For example, the pump could be used to evacuate the particle acceleration cavities of cyclotrons and space simulation chambers.


The pumping action of the VPP-100 will begin at a pressure of  $5 \times 10^{-3}$  torr and continue until a pressure as low as  $10^{-10}$  torr is reached. Over this range the pumping speed for air is approximately 100 litres per second.

Although an anode voltage of 3kV is used to operate the pump, a higher pumping speed may be obtained by increasing this voltage to 5kV. This increase in pump-

ing speed can be usefully applied to counteract outgassing which is often troublesome in vacuum systems at very low pressures. At a pressure of  $10^{-6}$  torr the pump has a life expectancy of approximately 40,000 hours.

Features of the VPP-100 include all-welded stainless steel construction, magnets that may be left in position during bake-out and interchangeable cathodes. Care has been taken to keep the stray magnetic field to a minimum. The pump is connected to a vacuum system by means of a demountable flange joint with a gold-wire seal. The seal has a 4" orifice and can be baked to a temperature of 450°C.

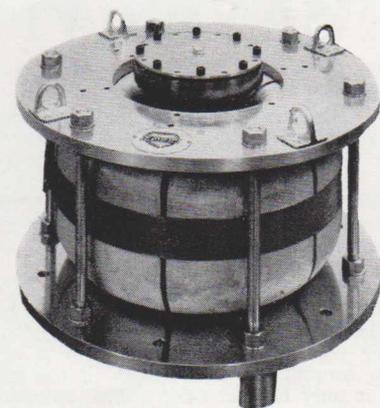\* Operating notes and data on other ion pumps and high vacuum gauges may be found in Volume 3 of the Mullard Technical Handbook.



## ABRIDGED DATA

### CHARACTERISTICS

|   |                                       |
|---|---------------------------------------|
| Pumping range   | $5 \times 10^{-3}$ to $10^{-10}$ torr |
| Pumping speed (air)   | 100 litre/sec                         |
| Fore pressure required to start pumping operation                                   | $5 \times 10^{-3}$ torr               |
| Over the operating range of the pump the pressure, but varies with different gases. | pumping speed is independent of       |

### LIMITING VALUES

|                               |       |
|-------------------------------|-------|
| Maximum operating temperature | 150°C |
| Maximum bake-out temperature  | 450°C |

### POWER REQUIREMENTS

|                   |        |
|-------------------|--------|
| Operating voltage | 3.0 kV |
|-------------------|--------|

### WEIGHT

205 lbs

### OVERALL DIMENSIONS

15" diameter  $\times$  9" height


## Three New High-Voltage Medium-Power Silicon P-N-P Transistors

Three new large-signal transistors, the BCY38, BCY39 and BCY40 complete a compatible range of Mullard silicon p-n-p transistors in TO-5 encapsulation.

With good bottoming characteristics and extremely efficient heat dissipation, these types are intended for use in pulse and audio applications, in oscillator and switching circuits and in servo process control.

With their high peak current ratings and good linearity, they are suitable for push-pull output stages; whilst their high maximum junction temperature of 150°C, coupled with low thermal resistance, provides a high dissipation factor.

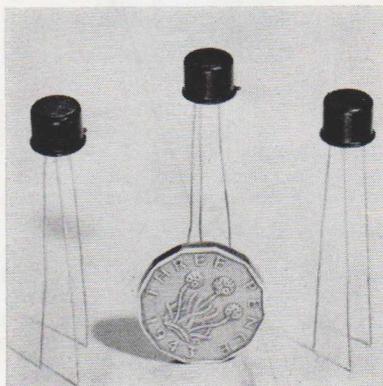The complete range, shown in the Table, consists of eight types falling into two groups according to their voltage ratings, with further subdivisions into low-current and high-current types.



TABLE

| Type Number | $V_{CB}$ max (V) | Current Amplification Factor | $I_C$ at (mA) | $I_{CM}$ max (mA) |
|-------------|------------------|------------------------------|---------------|-------------------|
| BCY33       | -32              | 15 to 35                     | 1.0           | 100               |
| BCY38       |                  | 10 to 30                     | 150           | 500               |
| BCY34       |                  | 25 to 60                     | 1.0           | 100               |
| BCY40       |                  | 16 to 120                    | 150           | 500               |
| BCY30       | -64              | 15 to 35                     | 1.0           | 100               |
| BCY32       |                  | 35 to 80                     | 1.0           | 100               |
| BCY31       |                  | 25 to 60                     | 1.0           | 100               |
| BCY39       |                  | 10 to 50                     | 150           | 500               |

## NEW STOCKS

The Mullard Vinkor Manual, which has been temporarily out of stock, is again available from Mullard Offices and Distributors throughout the Commonwealth, priced at 5/3d plus 8d postage.





# NEW 23-inch PICTURE TUBE SAVES VITAL INCHES

The flatness of the screen of the 23-inch Mullard picture tube AW59-91 offers a wide viewing angle and greater freedom from distortion when viewed obliquely.

The "unipotential" focusing lens in the AW59-91 prevents deflection defocusing and thus ensures excellent spot quality over the whole picture area.

The design of the electrode structure of the AW59-91 is such that a very short gun has been achieved. In addition to this, the sealing pip at the base of the gun is very small, so that the total length of the tube neck is only 110mm (4 $\frac{3}{16}$ ""). This compares with a neck length of 130mm (5 $\frac{1}{4}$ "") for the AW59-90. The overall reduction in the length of the AW59-91 resulting from the short-neck construction has made possible even greater reduction in the depth of television cabinets, leading to the more slender appearance of present-day receivers.

The AW59-91 may be used as a replacement for the following 23-inch television tubes in common use in Australia—AW59-30, AW59-90, AME2351B, AME-2354B, 23MP4J and 23WP4.



## TWO NEW SILICON RECTIFIERS


The range of Mullard silicon power diodes has been supplemented by two new types, the OA605 and the OA610, in SO-17 encapsulation.

These silicon diodes may be used as power rectifiers where an average current of 0.5A, at an ambient temperature of 70°C, is not exceeded.

### ABRIDGED PRELIMINARY DATA

OA605 OA610

|   |     |     |   |
|---|-----|-----|---|
| Max. PIV  | 50  | 100 | V |
| Max. forward current peak (at PIV max.)                         | 5   | 5   | A |
| Av. current (averaged over any 50 msec. period or DC component) | 0.5 | 0.5 | A |

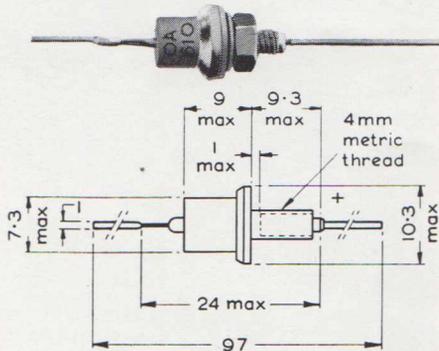

## WATSON OVERSEAS



Mr. H. S. Watson, Chief Engineer Mullard-Australia, and heading our applications engineering team, left Sydney on 19th August for an extended visit overseas.

Outlook, Volume 6, No. 2, page 15, shows and tells something of the Applications Engineering Laboratory and, needless to say, the outcome of Mr. Watson's visit will be to enhance the facilities of this activity and, in turn, the applications service to our customers.

Mr. Watson will be spending most of his time with our Parent Company, Mullard Limited, London, and in addition will be visiting the United States, Canada, Holland, Switzerland, Western Germany and France. He is scheduled to return to Australia mid-December.

maintains a healthy and ever growing technical answer service by correspondence and telephone, both from our Head Office in Sydney and the branches in the other States; visitors are always welcome and invariably depart with a handful of Mullard books and data sheets.

May we be of assistance to you?

## New Medium Power Output Transistor

In addition to the preferred range of transistors for entertainment applications, the AD139 output transistor has been made available for use in audio amplifiers and radio receivers.

The AD139 is a medium power, alloy-junction transistor of the p-n-p type designed for an output power of 2W in Class 'A'. When used in a transformerless single-ended push-pull DC-coupled amplifier, two AD139 transistors are capable of delivering to the loudspeaker voice coil 10W of audio power at very low distortion levels.

### ABRIDGED ADVANCE DATA

#### Absolute Maximum Ratings

|   |     |   |
|---|-----|---|
| $V_{CB}$                                | -32 | V |
| $V_{CE}$                                | -32 | V |
| $V_{EB}$                                | -10 | V |
| $I_C$ (averaged over any 50msec period) | 1   | A |
| $I_{CM}$                                | 2   | A |
| $I_B$ (averaged over any 50msec period) | 0.2 | A |

#### Temperature Ratings

|  |     |      |
|--|-----|------|
| Junction temperature continuous operation  | 90  | °C   |
| Storage temperature                        | 75  | °C   |
| Temperature rise junction to mounting base | ≤ 4 | °C/W |
| Dissipation $P_C$                          | 13  | W    |



#### Characteristics

At  $T_{amb} = 25^\circ C$ .

|                                     |       |    |
|-------------------------------------|-------|----|
| $I_B$ at $I_E = 10mA, V_{CB} = 0V$  | ≤ 0.6 | mA |
| $I_B$ at $I_E = 1A, V_{CB} = 0V$    | ≤ 33  | mA |
| $V_{BE}$ at $I_E = 1A, V_{CB} = 0V$ | ≤ 0.7 | V  |

The case is smaller than the T03 case as used in OC26 and similar transistors, having the same mounting hole spacings as the OC30 transistor (now a maintenance type).

#### Outlines and Dimensions

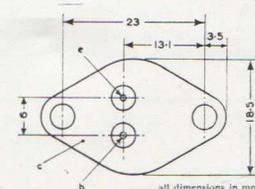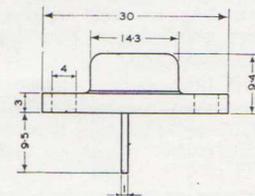

Continued from page 51

remind readers that we are glad to provide lecturers, instructional films and group publications for clubs, institutions, schools, indeed wherever enthusiasts gather for the common purpose of improving their technical knowledge.

The Technical Service Department also

## Mullard Range of Preferred Semiconductors for Entertainment Applications

This issue of Outlook contains an insert sheet which provides abridged data on the Mullard preferred range of semiconductors for use in entertainment applications. Of particular interest is the AF114N series, which supersedes the OC170 series in RF applications. The new range of transistors may be used as direct replacements for the OC170 series listed below.

### Applications

The AF114N—may be used as a replacement for the OC171 as an RF amplifier in VHF receivers. The increased power gain and lower noise figure at 100Mc/s provides superior performance.

The AF115N—may be used as a replacement for the OC171 as a mixer-oscillator in VHF receivers and for short-wave mixer-oscillator circuits at frequencies up to 26Mc/s. Increased conversion gain and lower noise figure are achieved.

The AF116N—may be used as a replacement for the OC170 as an AM mixer-oscillator up to 16Mc/s. The lower output conductance enables improved selectivity to be achieved, together with a reduced noise figure.

The AF117N—may be used as a replacement for the OC169 as an IF amplifier in AM receivers.

The adoption of the TO-44 case for the new transistor types contributes to a reduction in size of equipment when used in conjunction with the new preferred range of transistors for audio applications which are mounted in the TO-1 case.

### Improved Characteristics

1. New small case.
2. Maximum collector voltage rating 32V instead of 20V.
3. Increased gain ( $h_{re}$ ) facilitates the design of AGC controlled stages, such as in car radios and portables.
4. Reduction of  $I_{CBO}$  from 260 $\mu$ A to 50 $\mu$ A at 60°C results in improved AGC performance in car radios operating at high ambient temperatures.
5. Increased emitter-to-base breakdown voltage  $V_{EB}$ . 1V compared with 0.5V for OC170 series.
6. Improved noise figure.

## ALLOY-DIFFUSED GERMANIUM P-N-P TRANSISTORS

### AF114N, AF115N, AF116N, AF117N

#### ABRIDGED PRELIMINARY DATA

#### ABSOLUTE MAXIMUM RATINGS (for all four types)

|  |           |            |    |
|--|-----------|------------|----|
| Collector-to-base voltage                                | $-V_{CB}$ | 32         | V  |
| Collector-to-emitter voltage                             | $-V_{CE}$ | 32         | V  |
| Collector current  | $I_C$     | 10         | mA |
| Emitter current  | $I_E$     | 11         | mA |
| Reverse emitter current                                  | $-I_E$    | 1          | mA |
| Base current   | $I_B$     | 1          | mA |
| Collector dissipation at $T_{amb} \leq 45^\circ\text{C}$ | $P_C$     | 50         | mW |
| Junction temperature                                     |           |            |    |
| Continuous operation                                     | $T_j$     | 75         | °C |
| Intermittent operation (200 hours max.)                  | $T_j$     | 90         | °C |
| Storage temperature                                      | $T_{stg}$ | -55 to +75 | °C |

#### CHARACTERISTICS at $T_{amb} = 25^\circ\text{C}$

|   |                       |       |          |
|---|-----------------------|-------|----------|
| Emitter breakdown voltage at $-I_E = 50\mu\text{A}$ , $-I_C = 0$  | $-V_{EB}$ (all types) | max 1 | V        |
| Frequency at which $h_{re} = 1$ at $-V_{CB} = 6\text{V}$ , $I_E = 1\text{mA}$                                   | $f_1$ (all types)     | 75    | Mc/s     |
| Current amplification factor at $-V_{CE} = 6\text{V}$ , $I_E = 1\text{mA}$ , $f = 1\text{ kc/s}$                | $h_{re}$ (all types)  | 150   |          |
| Intrinsic base impedance at $-V_{CB} = 6\text{V}$ , $I_E = 1\text{mA}$ , $f = 2\text{ Mc/s}$                    | $ Z_{rb} $ (AF114N)   | 20    | $\Omega$ |
|   | $ Z_{rb} $ (AF115N)   | 25    | $\Omega$ |
|   | $ Z_{rb} $ (AF116N)   | 27    | $\Omega$ |
|   | $ Z_{rb} $ (AF117N)   | 35    | $\Omega$ |
| Feedback capacitance at $-V_{CE} = 6\text{V}$ , $I_E = 1\text{mA}$ , $f = 450\text{ kc/s}$                      | $-C_{re}$             | 1.5   | pF       |
| Noise figure at $-V_{CB} = 6\text{V}$ , $I_E = 1\text{mA}$ , $f = 100\text{ Mc/s}$ , $R_s = 60\Omega$           | F (AF114N)            | 8     | dB       |
| $f = 100\text{ Mc/s}$ , $R_s = 60\Omega$  | F (AF115N)            | 9.5   | dB       |
| $f = 10.7\text{ Mc/s}$ , $R_s = 200\Omega$  | F (AF116N)            | 3     | dB       |
| $f = 1\text{ Mc/s}$ , $R_s = 500\Omega$   | F (AF117N)            | 1.5   | dB       |
| Conversion noise figure at $-V_{CB} = 6\text{V}$ , $I_E = 1\text{mA}$ , $f = 1\text{ Mc/s}$ , $R_s = 500\Omega$ | $F_{conv}$ (AF116N)   | 3     | dB       |

#### SMALL SIGNAL Y PARAMETERS

For small signal y parameters and design curves, refer to AF114, AF115, AF116 and AF117 data in Volume 4 of the Mullard Technical Handbook.

## Mercury Vapour Thyatron ZT1000

The mercury-vapour filled thyatron ZT1000 has a negative control characteristic and is rated for a maximum peak inverse voltage of 21kV at an average anode current of 2.5A. At peak inverse voltages below 15kV average anode currents of 3A are permissible and at 2.5kV the average anode current may be up to 5A.

The ZT1000 is intended for use in HT power supplies with DC output voltages up to 21kV. It may also be used as a quick-acting electronic switch or for regulation and stabilisation purposes in HT power supplies.

#### ABRIDGED DATA

|   |                   |     |
|---|-------------------|-----|
| Heater voltage                                  | 5.0               | V   |
| Heater current                                  | 13                | A   |
| Maximum operating frequency                     | 150               | c/s |
| Maximum peak inverse voltage                    | 21                | kV  |
| Maximum average anode current                   | 2.5               | A   |
| Maximum negative grid voltage before conduction | 300               | V   |
| Maximum overall dimensions                      |                   |     |
| length  | 325               | mm  |
| diameter  | 75                | mm  |
| Weight  | 0.75              | kg  |
| Base  | B4D (Super jumbo) |     |

## SUB-MINIATURE VOLTAGE REFERENCE TUBE

The ZZ1000 is a new sub-miniature voltage reference tube intended for use in applications where a small physical size is an essential requirement.

At the recommended cathode current of 3mA the ZZ1000 has a stabilising voltage of 81V and an ignition voltage of 120V. Tests carried out on these tubes have shown that after 2000 hours of continuous operation at a bulb temperature of 45°C and with a cathode current of 3mA, the stabilising voltage did not change by more than 300mV. Life expectancy under these conditions is 30,000 hours.

The ZZ1000 will withstand maximum impact acceleration of 500g and a maximum vibrational acceleration, for extended periods, of 2.5g. Satisfactory operation is possible at altitudes up to 15 miles (24km) over a temperature range of  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$ .

The ZZ1000 measures 300mm by 6.1mm diameter and may be soldered directly into the circuit.



# Mullard Audio Amplifier Manual



## 15 COMPLETE CHAPTERS including:

- Amplifying Systems
- Sources of Distortion in Recorded Sound
- High-quality Amplification
- General Notes on Construction and Assembly
- Twenty-watt Amplifier
- Ten-watt Amplifier
- Three-watt Amplifier
- Two- and Three-valve Pre-amplifiers
- Input-mixing Pre-amplifiers
- Three-watt Tape Amplifier
- Tape Pre-amplifier
- Seven-watt Stereophonic Amplifier
- Three-valve Stereophonic Amplifier
- Stereophonic Pre-amplifier

With the growing demand for high quality sound reproduction, more and more of the circuits in use today require specialised knowledge. This publication fully describes the wide range of high-quality audio amplifier circuits designed by engineers of the Mullard Developmental Laboratories in the United Kingdom.

Four introductory chapters give a full technical explanation of monaural and stereophonic sound reproduction. The rest of the book comprises circuit descriptions, constructional details and performance figures of twelve Mullard circuits. These circuits include well-known Mullard designs, some modifications and improvements to these designs and a number of completely new designs.



MULLARD-AUSTRALIA PTY. LTD. Box 2118 G.P.O. SYDNEY

Please send me ..... copies of "Circuits for Audio Amplifiers" for which I enclose ..... remittance, being 12/6, plus 1/5 postage per copy.

NAME.....

ADDRESS.....


STATE.....

# Mullard

MULLARD-AUSTRALIA PTY. LTD. • 35-43 CLARENCE STREET, SYDNEY, N.S.W., 29 2006.  
123 VICTORIA PARADE, COLLINGWOOD, N.S. VIC., 41 6644.  
Associated with MULLARD LIMITED. LONDON



# Mullard Stereo Sound Systems

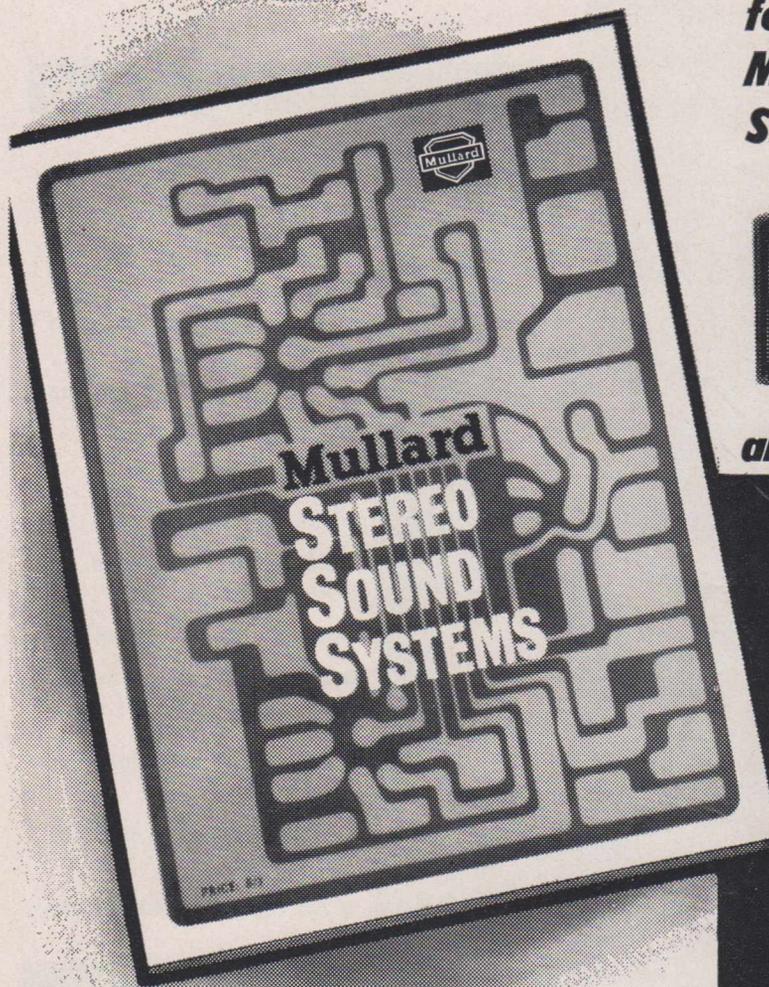

featuring . . .  
**Mullard Wideband Tuner**  
**Stereophonic Pre-amplifier**



also . . .

- **MULLARD STEREO "TEN-TEN"**  
 (with printed circuit boards)  
 Two 6GW8 triode pentodes and one low-noise AF pentode type EF86 in each channel provides a power output of 10 W at a total harmonic distortion of 0.05%. The input sensitivity (for 10 W output) is 260 mV.
- **MULLARD STEREO "THREE-THREE"**  
 (with printed circuit boards)  
 One 6GW8 triode pentode in each channel provides 3 W of audio power with a total harmonic distortion below 4%. The input sensitivity (for 3 W output) is 500 mV.
- **STEREOPHONIC TAPE RECORDER**  
 3 W per channel with synchronised oscillators and with a modulation level indicator.
- **LOUDSPEAKER ENCLOSURES**  
 Choosing and using loudspeakers.  
 Enclosures for large audiences.  
 Quality enclosures.  
 Economy enclosures.

The amplifiers contained in this publication were designed by engineers in the Mullard Applications Laboratory, Sydney. Printed boards are used throughout to facilitate ease of assembly with the minimum of tools. Since "lay-out" problems are non-existent, the amplifiers, the pre-amplifier and the wideband tuner may be successfully constructed by the hobbyist and professional alike, to provide a source of high quality reproduction.

This booklet may be obtained by forwarding the coupon, together with remittance, to the addresses shown.

Mullard-Australia Pty. Ltd., Box 2118, G.P.O., Sydney, N.S.W.  
 Mullard-Australia Pty. Ltd., P.O. Box 97, Collingwood, N.5, Vic.

Please send me \_\_\_\_\_ copies of "Stereo Sound Systems" for which I enclose \_\_\_\_\_ remittance, being 6/3 plus 8d. postage per copy.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 State \_\_\_\_\_



**Mullard-Australia Pty. Ltd.**

35-43 CLARENCE STREET, SYDNEY. - - - - 29 2006  
 123 VICTORIA PARADE, COLLINGWOOD, N.5, VIC., 41 6644  
 Associated with MULLARD LIMITED, LONDON

# MULLARD PREFERRED RANGE OF TRANSISTORS FOR ENTERTAINMENT APPLICATIONS IN AUSTRALIA

The following semiconductor types are included in the Mullard preferred range in Australia and, whilst the information provided is abridged, more comprehensive design information is contained in Volume 4 of the Mullard Technical Handbook.

Other semiconductor types not tabulated are also available upon application to Mullard-Australia Pty. Ltd.

| Type Number                    | Description and Application   | $-V_{CB}$<br>max<br>(V) | $-V_{CE}$<br>max<br>(V) | $-V_{EB}$<br>max<br>(V) | $-I_C$<br>max<br>(mA) | $-I_B$<br>max<br>(mA) | $T_J$<br>max<br>(°C) | $P_{tot}$ max<br>$T_{amb}$ 25°C<br>(mW) | Outlines<br>and<br>Dimensions |
|--------------------------------|---|-------------------------|-------------------------|-------------------------|-----------------------|-----------------------|----------------------|---|-------------------------------|
| <b>AC125</b>                   | General purpose audio pre-amplifier and driver of the p-n-p alloy junction type   | 32                      | 32                      | 10                      | 100                   | 5                     | 90*                  | 500**                                   | TO-1                          |
| <b>AC126</b>                   | High-gain audio pre-amplifier and driver of the p-n-p alloy junction type   | 32                      | 32                      | 10                      | 100                   | 5                     | 90*                  | 500**                                   | TO-1                          |
| <b>AC127</b>                   | n-p-n/p-n-p germanium alloy junction transistors for use in complementary Class 'B' output stages   | +32                     | +32                     | +10                     | +200                  | +10                   | 90*                  | 280**                                   | TO-1                          |
| <b>AC132</b>                   |   | 32                      | 32                      | 10                      | 200                   | 10                    | 90*                  | 500**                                   | TO-1                          |
| <b>AC128</b><br><b>2-AC128</b> | High-gain germanium alloy junction transistor of the p-n-p type designed for use in Class 'B' output stages                                       | 32                      | 32                      | 10                      | 1A                    | 20                    | 90*                  | 550**                                   | TO-1                          |
| <b>AF114N</b>                  | Germanium transistor of the p-n-p alloy diffused type designed for use up to 100Mc/s  | 32                      | 32                      | —                       | 10                    | 1                     | 75                   | 50***                                   | TO-44                         |
| <b>AF115N</b>                  | Germanium transistor of the p-n-p alloy diffused type designed for use up to 100Mc/s as mixer-oscillator and for use as RF amplifier up to 27Mc/s | 32                      | 32                      | —                       | 10                    | 1                     | 75                   | 50***                                   | TO-44                         |
| <b>AF116N</b>                  | Germanium transistor of the p-n-p alloy diffused type designed for use as mixer-oscillator and RF amplifier up to 16Mc/s                          | 32                      | 32                      | —                       | 10                    | 1                     | 75                   | 50***                                   | TO-44                         |
| <b>AF117N</b>                  | Germanium transistor of the p-n-p alloy diffused type designed for use as mixer-oscillator and RF amplifier up to 6Mc/s                           | 32                      | 32                      | —                       | 10                    | 1                     | 75                   | 50***                                   | TO-44                         |
| <b>OC26</b><br><b>2-OC26</b>   | Power junction transistor of the p-n-p alloy type intended for use in output stages of car radio receivers  | 32                      | 32                      | 10                      | 3.5A                  | 500                   | 100*                 | 12.5W**                                 | TO-3                          |
| <b>OC74N</b><br><b>2-OC74N</b> | High-gain germanium alloy junction transistor of the p-n-p type designed for use in Class 'B' output stages                                       | 20                      | 20                      | 6                       | 300                   | —                     | 90*                  | 550**                                   | TO-1                          |

\*\*\*  $T_{amb} = 45^\circ\text{C}$


\*\* with suitable heat sink

\* 200 hours operation

# MULLARD PREFERRED RANGE OF DIODES FOR ENTERTAINMENT APPLICATIONS IN AUSTRALIA

| Type Number      | Description and Application                      | Max PIV (V) | $I_{FM}$ (mA) | $I_{F(AV)}$ (mA) | $I_{F(surge)}$ (A) | $T_{amb}$ max (°C) | Outlines and Dimensions |
|------------------|--|-------------|---------------|------------------|--------------------|--------------------|-------------------------|
| AA119<br>2-AA119 | AM/FM detector diode                             | 45          | 100           | 35               | 0.2                | 60                 | SO-6                    |
| OA90             | Sub-miniature HF detector diode                  | 30          | 45            | 10               | 0.2                | 75                 | SO-6                    |
| OA91             | Sub-miniature high-voltage general purpose diode | 115         | 150           | 50               | 0.5                | 75                 | SO-6                    |
| OA95             | Sub-miniature high-voltage general purpose diode | 115         | 150           | 50               | 0.5                | 75                 | SO-6                    |
| OA210            | Silicon junction power rectifier                 | 400         | 5A            | 500              | —                  | 70                 | SO-17                   |
| OA211            | Silicon junction power rectifier                 | 800         | 4A            | 400              | —                  | 60                 | SO-17                   |
| OA675            | Compensation diode for Class 'B' output stages   | —           | 10            | —                | —                  | 75                 | TO-1                    |

## Semiconductor Outlines and Dimensions

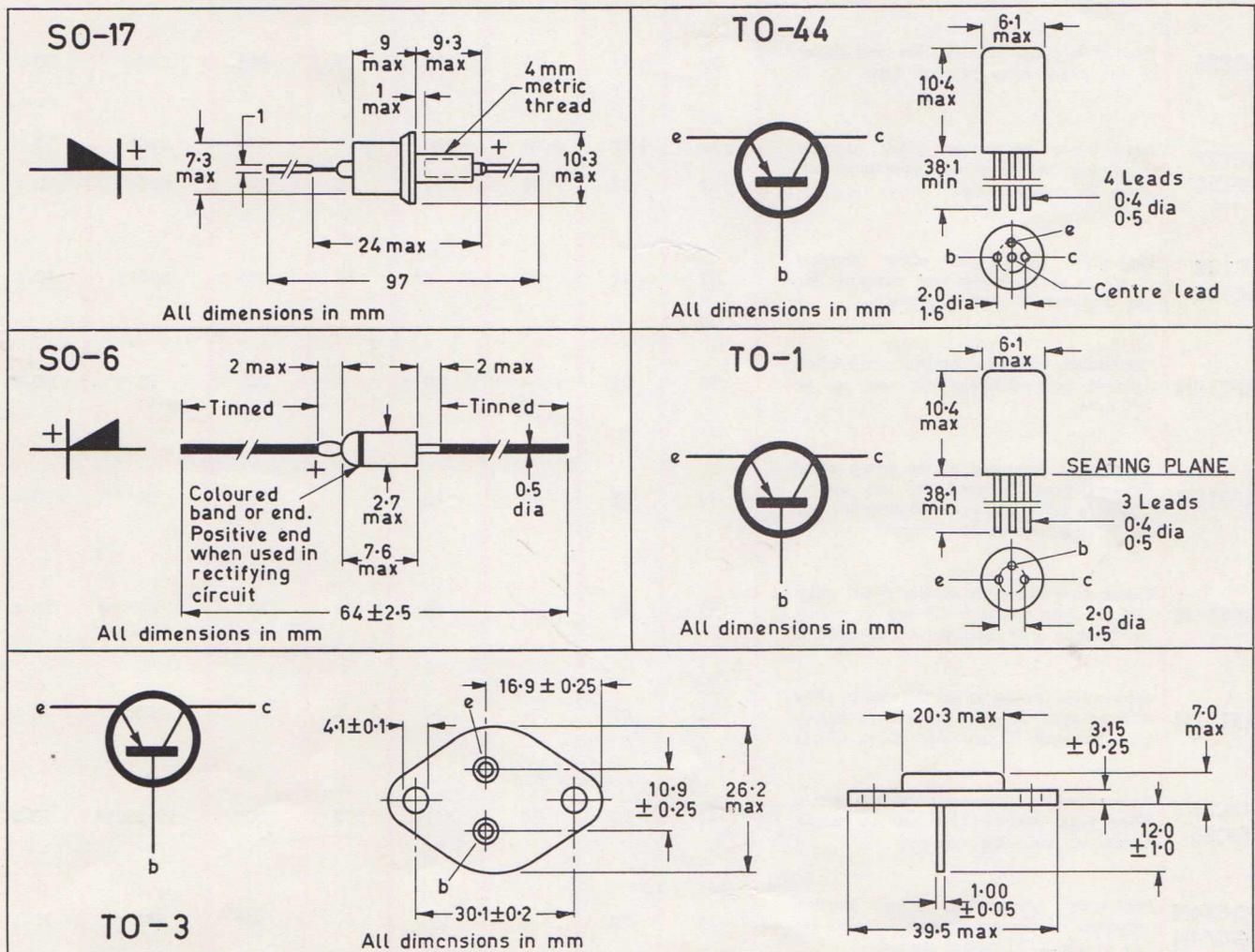

MULLARD-AUSTRALIA PTY. LTD., 35-43 CLARENCE STREET, SYDNEY, 29 2006; 123 VICTORIA PARADE, COLLINGWOOD, N.5, VIC. 41 6644  
 Associated with MULLARD LIMITED, LONDON