



# Service Scope

USEFUL INFORMATION FOR USERS OF TEKTRONIX INSTRUMENTS

NUMBER 44

PRINTED IN U.S.A.

JUNE 1967

## A PRACTICAL APPROACH TO TRANSISTOR AND VACUUM TUBE AMPLIFIERS

BY F. J. BECKETT

TEKTRONIX, INC.


ELECTRONIC INSTRUMENTATION GROUP

DISPLAY DEVICES DEVELOPMENT

PART 3

A DC ANALYSIS OF A TYPICAL

TEKTRONIX HYBRID CIRCUIT

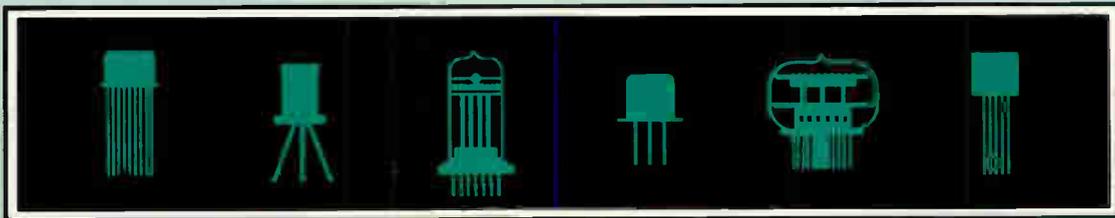

This is the third in a series of three articles offering a new approach to transistor and vacuum-tube amplifiers. This new approach is based on a simple DC analysis that incorporates the concepts of "trans-resistance" and the principles of Thévenin's Theorem.

In this article, conclusions reached in Part 1, "The Transistor Amplifier" (Service Scope #42, February 1967) and Part 2, "The Vacuum Tube Amplifier" (Service Scope #43, April 1967) form the basis for a DC analysis of a typical Tektronix, Inc. hybrid-amplifier circuit.

As a typical example of a Tektronix, Inc. hybrid circuit on which to demonstrate our DC analysis, we have chosen the vertical amplifier of a Type 545B Oscilloscope. This circuit is representative of the hybrid circuit one encounters so often in electronic instrumentation today.

The Type 545B vertical amplifier is a hybrid push-pull amplifier operating in a class A mode. It incorporates a few extra circuits such as trigger pick-off amplifiers necessary to accomplish its function, but, basically it is a hybrid push-pull amplifier.

To begin our analysis of the amplifier, the first thing we must do is select a portion of the amplifier circuit which will give us the information necessary for us to make our first calculation. We are going to analyze the whole circuit so we can choose our point of entry. The input circuit is as good a point as any. Bear in mind that, for our purpose, this is not the only point of entry. Any point on the circuit which will give us useful information would do.

A quiescent DC voltage of +67 volts is the nominal voltage at the output of the plug-in amplifiers used in the Type 545B oscilloscope. This voltage appears at terminals 1 and 3 of J11 in Figure 17, and thus, at the grids of V494A and V494B, a 6DJ8 dual triode. The input cathode follower (V494 A & B) has a bias of about 4 volts; therefore, both cathodes will be at +71 volts. The base voltage of Q514 and Q524 is then fixed at 71 volts. This sets the emitter voltages of Q514 and Q524 at one junction drop more negative (they are both NPN transistors) than the base. Therefore, the voltage at the emitter of Q514 and Q524 is 70.5 volts. T500 is a small toroidal transformer used for high-frequency common-mode rejection. The DC BALANCE Control, R495, sets the quiescent condition. We mean by this that the trace is centered.

We have made certain assumptions about the bias of a vacuum tube and the base-to-emitter voltage drop of a transistor. This is quite justifiable since we know what function the device performs. One helpful hint about transistors is that you can expect a base-to-emitter voltage drop of about 0.5 to 0.6 volts for a silicon transistor and about 0.2 volts for a germanium transistor.

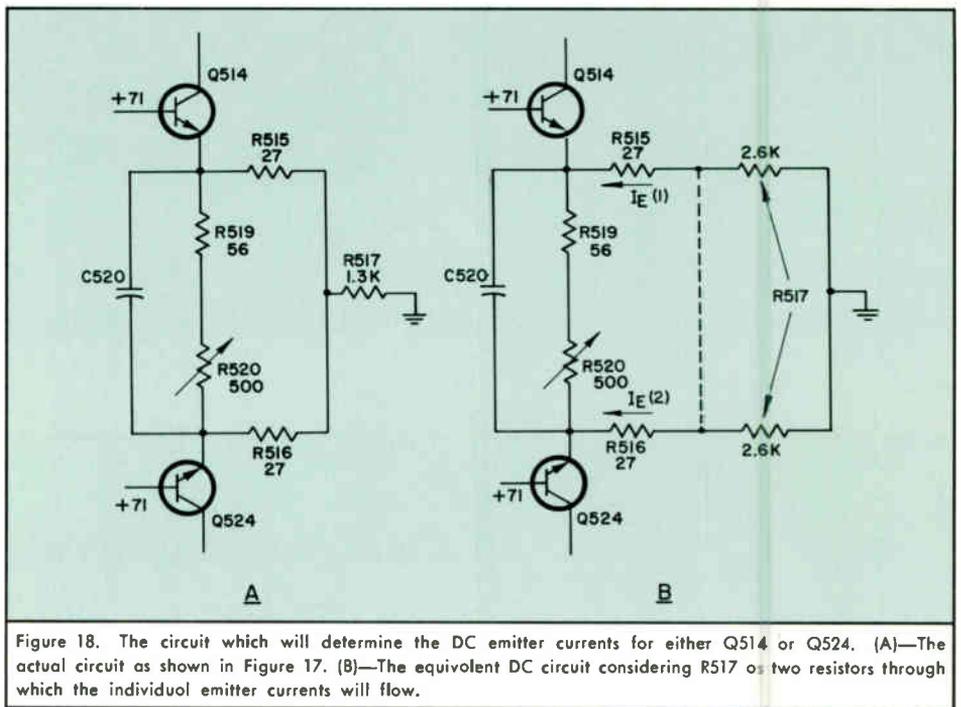


Figure 18. The circuit which will determine the DC emitter currents for either Q514 or Q524. (A)—The actual circuit as shown in Figure 17. (B)—The equivalent DC circuit considering R517 as two resistors through which the individual emitter currents will flow.

We are now able to calculate the emitter current of either Q514 or Q524. The DC-emitter current will flow through R515 or R516 and into R517 to ground. Since the emitter currents of Q514 and Q524 both pass through R517, we may think of R517 being made up of two resistors, each of 2.6 kΩ in value, in which the individual emitter currents will flow, refer to Figure 18: Therefore,

$$I_E (1) \text{ or } (2) = \frac{70.5 \times 10^3}{2.627 \times 10^3} \text{ mA}$$

$$= 27 \text{ mA}$$

We can now calculate the value of  $r_e$ , the dynamic-emitter resistance,

$$r_e = \frac{26}{I_E} = \frac{26}{27}$$

$$= 0.96 \Omega$$

to this we can add our constant,  $R_r$ , of say, 4 Ω. We recall that:

$$R_t = r_e + R_r \quad (9)$$

therefore:

$$R_t = 0.96 + 4 = 4.96 \Omega$$

or approximately 5 Ω. We have now established the value of the emitter current and the value of  $R_t$  for Q514 and Q524.

Our next step is to find the value of  $R_E$ . We must know this value in order to calculate gain. You will recall that  $R_E$  will be that impedance through which the signal current will flow to the AC ground. Let us take another look at the resistive network between the emitters of Q514 and Q524. The signal currents flowing in this circuit will be equal and opposite at two points, refer to Figure 19. These points are virtual AC-ground points; therefore, the impedance seen by the signal current from the emitters of Q514 or Q524 will be the parallel combination of 153 Ω and 27 Ω or approximately 23 Ω to the AC ground points. Hence,  $R_E$  for Q514 or Q524 will be 23 Ω.

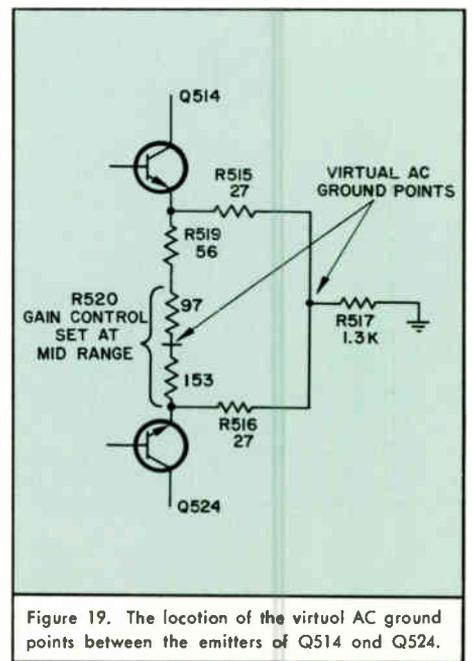


Figure 19. The location of the virtual AC ground points between the emitters of Q514 and Q524.

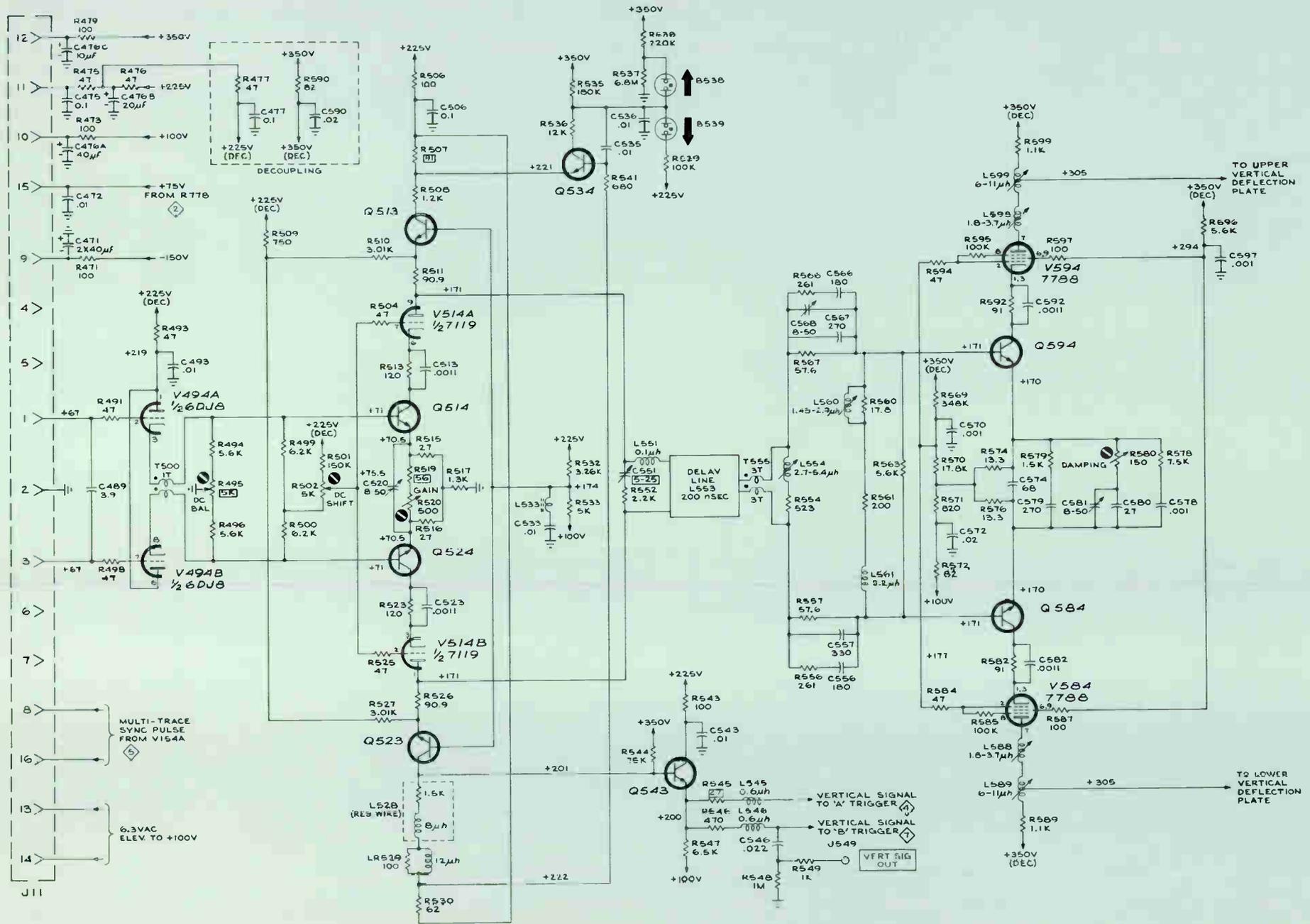


Figure 17.

TYPE 545B OSCILLOSCOPE

VERTICAL AMPLIFIER



When we apply a negative signal to the vertical input of the oscilloscope, the base of Q524 is driven negative and the base of Q514 moves in a positive direction by a similar amount. Therefore, the current through R530 decreases and the current through R507 increases. The voltage at the emitter of Q534 increases and the voltage at the base of Q534 decreases. As a result, the base-to-emitter junction of Q534 becomes reverse biased and Q534 ceases to conduct.

Therefore, the voltage at the junction of R535 and R536 rises towards 350 volts striking neon B539 which indicates trace has shifted down.

R513 and R523 and the DC SHIFT control R502 are thermal-compensation networks. The thermal time constants are long and the visible result appears on the CRT display as a DC shift in trace position after a step function. The DC SHIFT con-

trol is adjusted for the best dynamic thermal compensation, typically about 1% tilt.

We will now analyze the output circuits to the right of the delay line, refer to Figure 17. The first thing we must do is to calculate the voltage at the base of Q594 or Q584. The voltage at the junction of R532 and R533 (174 volts) will set the base voltage of Q513 and Q523. Assuming a junction drop of 0.5 volt the voltage at the emitter of Q513 and Q523 will be 173.5 volts. The current through R511 and R526 is 27 milliamps, hence the voltage drop across these resistors will be

$$\frac{90.9 \times 27}{1000} \approx 2.5 \text{ volts}$$

therefore, the voltage at the plate of V514A and V514B is

$$173.5 - 2.5 = 171 \text{ volts.}$$

This 171 volts is directly coupled to the base of Q594 and Q584 via the delay line. The voltage at the emitter of both Q594 and Q584 is then 170.5 volts. We will now calculate the current flowing into the emitter of Q594 or Q584. Figure 21 shows a step-by-step approach in solving this problem. The simplest approach is to use Thévenin's Theorem to simplify the resistive network R569, R570, R571 and R572. The result is we have a  $V_{oc}$  of +100 volts and a  $Z_{th}$  of 900  $\Omega$  to the junction of R574 and R576. Therefore, looking from the emitter of either Q594 or Q584 we see an impedance of 13.3  $\Omega$  in series with 1800  $\Omega$  to +100 volts.

$$I_E = \frac{(170.5 - 100)10^3}{1.8 \times 10^3} \text{ mA}$$

$$= \frac{70.5}{1.8} = 39 \text{ mA}$$

we now calculate  $r_e$

$$r_e = \frac{26}{I_E} = \frac{26}{39}$$

$$\approx 0.7 \Omega$$

and to this we add our constant  $R_r$  of 4  $\Omega$ ; therefore,

$$R_t = r_e + R_r \quad (9)$$

$$= 0.7 + 4.0$$

$$= 4.7 \Omega's$$

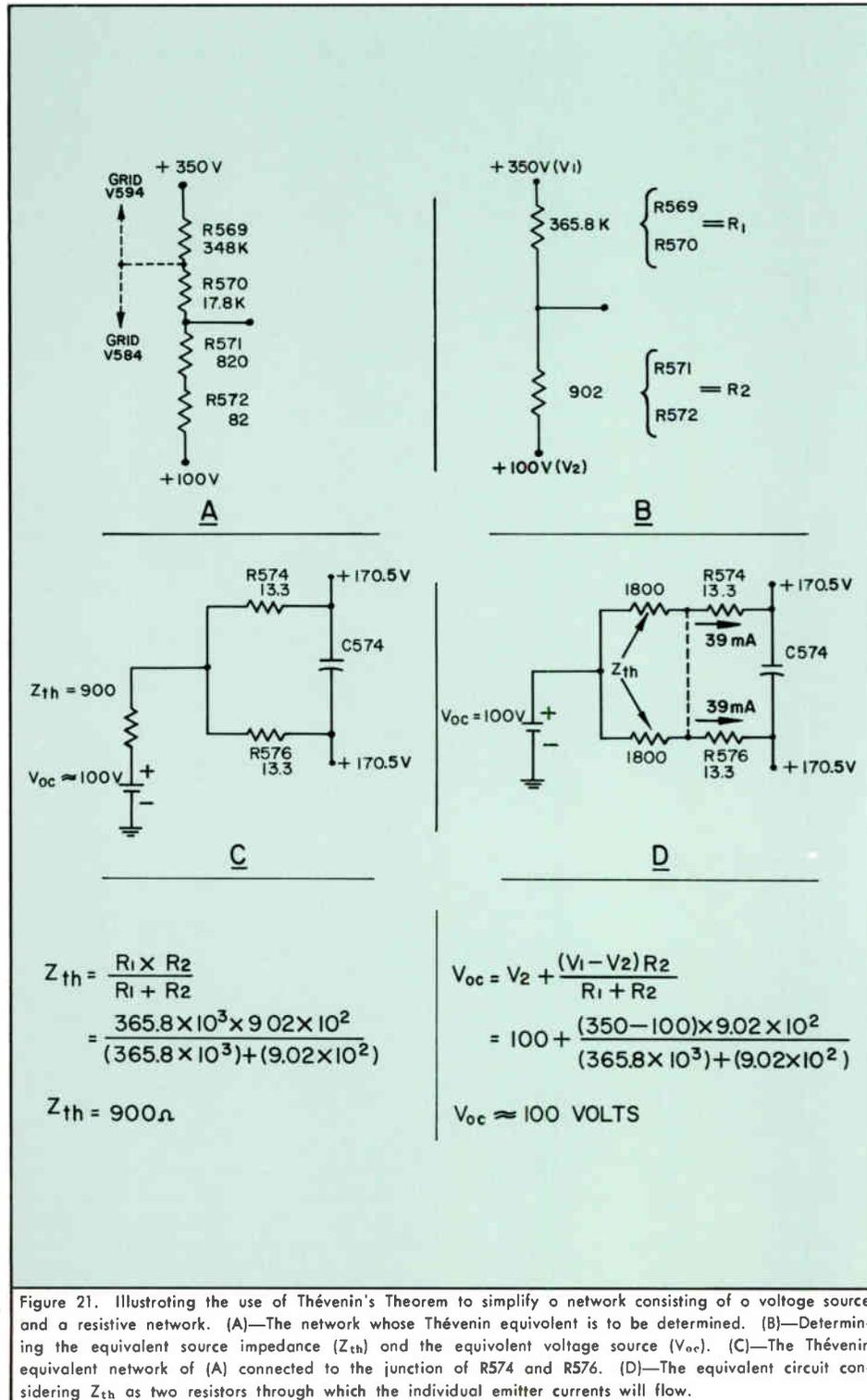


Figure 21. Illustrating the use of Thévenin's Theorem to simplify a network consisting of a voltage source and a resistive network. (A)—The network whose Thévenin equivalent is to be determined. (B)—Determining the equivalent source impedance ( $Z_{th}$ ) and the equivalent voltage source ( $V_{oc}$ ). (C)—The Thévenin equivalent network of (A) connected to the junction of R574 and R576. (D)—The equivalent circuit considering  $Z_{th}$  as two resistors through which the individual emitter currents will flow.

We have only one point in this circuit (a virtual AC ground point) at which the signal currents will be equal and opposite. That point is the junction of R574 and R576 (13.3Ω resistors). This fact sets  $R_E$  at 13.3Ω. The purpose of the RC network to the right of R574, R576 is to compensate the high frequencies.

The input impedance we see looking into the base of Q594 or Q584 is

$$R_{in} = \beta (R_E + R_t) \quad (10)$$

A beta of 75 for this type of transistor is a close figure to use for practical purposes. Therefore,

$$\begin{aligned} R_{in} &= 75 (13.3 + 4.7) \Omega's \\ &= 1350 \Omega \end{aligned}$$

The value of  $R_{in}$  is part of a resistive network which will terminate the delay line in its correct impedance. Therefore, before we leave this section we must check to see if our

value of  $R_{in}$  is within practical limits. Figure 22 shows a progressive breakdown of this network.

This network will induce a loss between the two stages. The signal is reduced in amplitude by a factor of 0.64 because of the voltage divider network consisting of 57.6Ω and the parallel combination of 100Ω, 2800Ω, and the input impedance into Q594 or Q584.

The gain of the output stage is

$$\begin{aligned} A_{(v)} &= \left[ \frac{R_{L(1)} + R_{L(2)}}{R_{E(1)} + R_{E(2)} + R_{t(1)} + R_{t(2)}} \right] \eta \\ &= \left[ \frac{1100 + 1100}{13.3 + 13.3 + 4.7 + 4.7} \right] \eta \\ &= \left[ \frac{2200}{36} \right] \eta \\ &= 61 \eta \end{aligned}$$

You recall that the gain equation of a hybrid cascode amplifier (refer part 2, "The Vacuum Tube Amplifier," Service Scope #43, April 1967) must be multiplied by the plate efficiency factor ( $\eta$ ) if the vacuum tube is not a triode. The plate efficiency factor ( $\eta$ ) normally varies from between 0.7 to 0.9. In this case ( $\eta$ ) is approximately 0.9 - 0.88 to be exact. So finally,

$$\begin{aligned} A_{(v)} &= 61 \times \frac{9}{10} \\ &= 54.9 \end{aligned}$$

The gain of the complete Type 545B vertical amplifier is

$$\begin{aligned} A_{(v)} \text{ (total)} &= 54.9 \times 1.68 \times 0.64 \\ &= 59 \end{aligned}$$

#### Summary

This brings to a close this series of three articles dealing with a practical approach to transistor and vacuum-tube amplifiers. This approach has been offered as a direct method of trouble shooting and understanding circuits. There are limitations as to its application as we have seen. However, these limitations do not impair the practical approach we must apply to our everyday maintenance and trouble shooting problems.

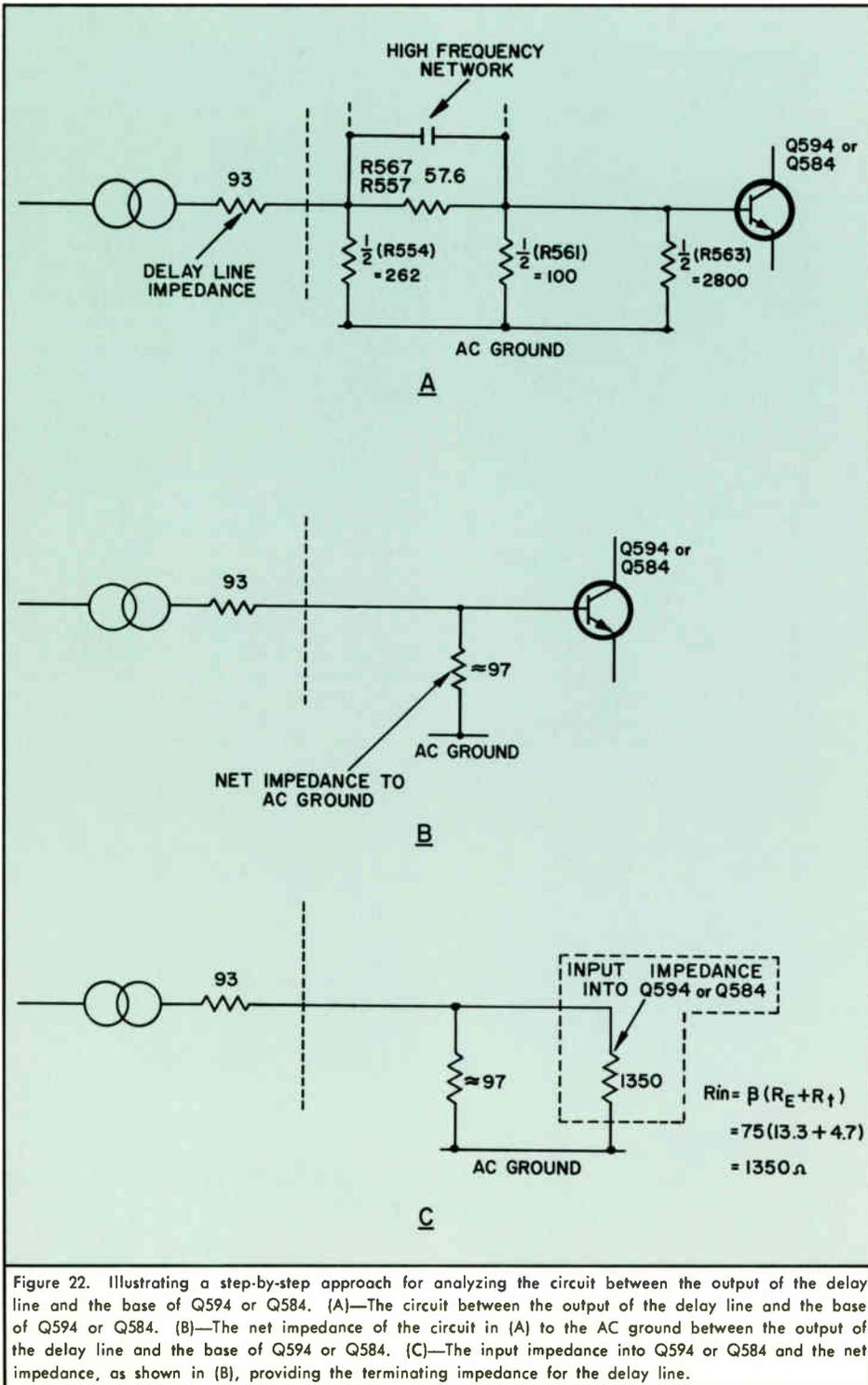


Figure 22. Illustrating a step-by-step approach for analyzing the circuit between the output of the delay line and the base of Q594 or Q584. (A)—The circuit between the output of the delay line and the base of Q594 or Q584. (B)—The net impedance of the circuit in (A) to the AC ground between the output of the delay line and the base of Q594 or Q584. (C)—The input impedance into Q594 or Q584 and the net impedance, as shown in (B), providing the terminating impedance for the delay line.

## USED INSTRUMENTS FOR SALE

1—Type 502A Dual-Beam Oscilloscope, sn 24036. Less than 5 hours actual time. Due to a change in our requirements, we will sell this instrument for \$900.00 or trade for a Type 321A. Contact: Mr. Payne, Payne Engineering Company, Charleston, West Virginia 25314. Telephone: 304-755-4353.

1—Type L Plug-In Unit, sn 21482; 1—Type CA Dual-Trace Plug-In Unit, sn 66599. Contact: Mr. Norm Friedman, Professional Closed-Circuit Television, Inc., 342 Madison Avenue, New York, New York. Telephone: 212-MU 7-4422.

1—Type 545B Oscilloscope, sn 397; 1—Type B Plug-In Unit sn 19773; 1—Type 500/53A Scopemobile®, Model 7. Contact: Electro-Mech Corporation, Attention: Mr. W. R. Sandman, Vice-President, P. O. Box 102, Wrightsville, Georgia 31096. Telephone: 912-864-3366.

1—Type 1S1 Sampling Unit, sn 417; 1—Type 3S76 Dual-Trace Sampling Unit, sn 492; 1—Type 3T77 Sampling Sweep Unit, sn 489. 80% off original cost. Contact: Mr. Greenburg, Information Control Company, 138 Nevada Street, El Segundo, California 90245. Telephone: 322-6931.

1—Type 517 Power Supply, sn 370; 1—Type 112 Differential High-Gain Amplifier, sn 570. Contact: Lenn Chatis, 512 N. Citrus Avenue, Los Angeles, California 90036. Telephone: 213-934-5762.

1—Type 517A Oscilloscope, sn 529. Will sell for cash or trade for a Tektronix portable oscilloscope. Contact: Fred Kortright, Basler Electric Company, Box 269, Route 143, Highland, Illinois. Telephone: 618-654-2341.

1—Type 315D Oscilloscope, sn 1253. Please contact: Mr. Louis Posner, Marine Radio Equipment, Inc., 10 Rogers Street, Gloucester, Massachusetts 01930.

1—Type 551 Dual-Beam Oscilloscope, sn 003247; 1—Type K DC-to-30 MHz Unit, sn 9907; 1—Type CA Dual-Trace Unit, sn 017074. Price for all three instruments: \$1575.00. All are in good condition. Contact: Jack Sveta, Exact Electronics, Inc., 455 Second Street, Hillsboro, Oregon 97123.

1—Type 132 Power Supply; 1—Type O Operational Amplifier. Contact: Dr. Neil Moore, Comparative Cardio Vascular Studies Unit, Philadelphia, Pennsylvania 19104. Telephone: 594-8897.

## USED INSTRUMENTS WANTED

1—Scopemobile® for Type 530/540 Oscilloscopes. Please contact: Mr. Sam Rosen, Vibacall Corporation, 26300 Telegraph, Southfield, Michigan 48075. Telephone: 313-353-2885.

1—Type 321 or Type 321A Portable Oscilloscope. Contact: Mr. R. L. Meisenheimer, LaMar Engineering Company, Burlington County Airport,

Medford, New Jersey. Telephone: 609-267-6710.

1—Type 317, Type 515, Type 515A, or Type 516 Oscilloscope. Contact: Mr. Sam L. Fulwood, 806 N. Rio Vista Boulevard, Ft. Lauderdale, Florida 33301.

1—Type 545B Oscilloscope with 1—Type 1S1 Sampling Plug-In Unit. Contact: Mr. Bob Saul,

Aul Instruments, Inc., 24-13 Bridge Plaza North, Long Island City, New York 11101. Telephone: 212-729-6565.

1—Type 310A, Type 317, or Type 516 Oscilloscope. Please state condition and price. Contact: A. T. Ferguson, 10 Bayberry Drive, Newport News, Virginia 23601. Telephone: 596-7347.

## MISSING INSTRUMENTS

Following are the instruments reported to us in the past 60 days as lost or presumed stolen. With each instrument (or group of instruments) we list their legal owner. Should you have any information on the present whereabouts of any of these instruments, or if you have information that might lead to their eventual recovery, please contact the individual or firm listed as the owner. If you prefer, you may relay your information to your local Tektronix Field Office, Field Engineer or Field Representative, or, The Editor, Service Scope, Tektronix, Inc., P. O. Box 500, Beaverton, Oregon 97005. Telephone: 503-292-2611, Ext. 318.

1—Type 321A Portable Oscilloscope, sn 1040. Missing since September 1966 and believed stolen. Reported by: Mr. N. A. Burtch of University of Alberta, Electrical Engineering Department, Edmonton, Alberta, Canada.

1—Type 561A, sn 015376; 1—Type 3B3 Time-Base Unit, sn 005767; 1—Type 3A1 Dual-Trace Amplifier, sn 010759. These instruments were removed by an unauthorized person (or persons) from the

Federal Aviation Agency's Aircraft #N-11 in Bakersfield, California. They are considered stolen. Mr. Del Kidman is the person to contact if you have information on these instruments. His address: Federal Aviation Agency, Aircraft Maintenance Base, 5885 West Imperial Highway, Los Angeles, California. Telephone: 213-670-7030, ext. 701.

1—Type 545 Oscilloscope, sn 476; 1—Type CA Dual-Trace Plug-In Unit, sn 10538; 1—Type 531A Oscilloscope, sn 22786; 1—Type H Plug-In Unit, sn 10271. These instruments were missed on April 19, 1967 and were apparently removed from the premises on the night of April 18, 1967. These instruments are owned by Unitron, Inc., 1624 North First Street, Garland, Texas. Mr. Jerry Munn is the man to contact there.

1—Type 422 DC-to-15 MHz Oscilloscope, sn 1963. This instrument disappeared from the U.S.S. Baya. It is the property of the U. S. Navy Electronics Laboratory in San Diego, California.

1—Type 321A Portable Oscilloscope, sn 223. Reported as stolen from Gurton Semi-Products,

211 East Avenue, Linden, New Jersey. Telephone: 201-925-5161.

1—Type 453 DC-to-50 MHz Portable Oscilloscope, sn 8812; 1—Type 422-MOD 125B DC-to-15 MHz Oscilloscope, sn 6276; 1—Type 564 Storage Oscilloscope, sn 6489; 1—Type 3A2 Analog/Digital Amplifier Unit, sn 110; 1—Type 3B4 Time-Base Unit, sn 1018; 1—Type 531 Oscilloscope, sn 5957; 1—Type CA Dual-Trace Plug-In Unit, sn 47381. These instruments are missing from the Waltham, Massachusetts area. Contact: Mr. Lee Heaton, Tektronix, Inc., 244 Second Avenue, Waltham, Massachusetts. Telephone: 617-894-4550.

1—Type 321A Portable Oscilloscope, sn 3851. Taken from Magnavox Company, 2131 Bueter Road, Fort Wayne, Indiana. These instruments are believed stolen. Contact: Mr. Jerry Buchan. Telephone: 219-743-9721, ext. 341.

1—Type 515A Oscilloscope, sn 5802. Missing from Picker X-Ray Engineering. Contact: Mr. Gjernes, Manager. Telephone: 604-253-7571.



# *Service Scope*

USEFUL INFORMATION FOR

USERS OF TEKTRONIX INSTRUMENTS

Tektronix, Inc.  
P.O. Box 500  
Beaverton, Oregon, U.S.A. 97005

BULK RATE  
U. S. POSTAGE  
**PAID**  
Beaverton, Oregon  
Permit No. 1

Mr. Ed Harding  
5329 Dupont Ave. S.  
Minneapolis, Minn. 55419

4/66

RETURN REQUESTED