

# 73

# Amateur Radio's Technical Journal

A Wayne Green Publication

**8 New  
And Useful  
Projects!**

**Home-Brew II  
Contest Winner**  
Page 10

**Tearing Into  
Ten-Tec's  
Corsair**  
Page 105

**Coffee-Can  
Cavity Filter**  
Page 74

**OSCAR Gear  
From Junk**  
Page 18

**More  
Simple  
Circuits**  
Page 110



### RTTY Tuning: The New Solution

This simple tuning indicator whipped the competition and took first place in 73's Home-Brew II Contest. . . . . WB2OSZ 10

### Uncover Equipment for OSCAR Phase III

Lurking in flea markets and junk boxes is everything you need to work OSCAR. K6KLY tells what to look for and how to make it work. . . . . K6KLY 18

### Up and Coming: Direct-Broadcast Satellites

Part II looks at the technical problems with communications at 12 GHz, which may be offset by the advantages. . . . . N8RK 26

### The Fun-Vac: A Synthesis of Old and New

This one-tube transmitter combines the circuits of the fifties with the technology of the eighties. It also keeps your coffee warm. . . . . WA0RBR 32

### Adventure in Sarawak

Two DXpeditioners journey to the land of headhunters—and send a signal to the rest of the world. . . . . VK9NL 42

### Put 2 Meters in Your Shirt Pocket

Radio Shack's Pocket Weatheradio makes a dandy 2-meter receiver. A few quick modifications will get it right on target. . . . . K3PJG 46

### The Secret Telemetry of OSCAR 8

Do those numbers from the sky mean anything? You bet. . . . . K5OM 52

### Scandinavia: The 2-Meter Dream Vacation


Licensing, frequencies, and procedures—it's all here. All you need is a plane ticket. . . . . WA6OGW 58

### Twisted Remote Control

This circuit is easy to build and easy to use. The twist is that you probably own the most important part. . . . . WD5JWY 64



Sarawak 9M8—42

 

RTTY Tuning—10

### Take Your IC's Temperature

Like people, solid-state devices get sick if they get too hot. W3KBM provides a way to answer the burning question, "How hot is hot?" . . . . . W3KBM 70

### The Q-Master Cavity Filter

A high-Q filter that uses no copper and no silver-plating—just coffee cans and some ingenious thinking. . . . . KB6AL 74

### Push Your Radar Detector to the Limit

Without this simple modification, you won't know what you are missing—until it's too late. . . . . W5LFM 86

### Personalize the M800 RTTY Program

Now you can design and save your own version of this popular software package. All it takes is a POKE or two. . . . . VE4AFO 94

Never Say Die—6  
Ham Help—95, 97,  
100, 103, 109, 117  
Social Events—96  
Contests—98  
Review—104  
Awards—108  
Circuits—110  
Reader  
Service—114

Satellites—115  
Fun!—116  
Corrections—117  
RTTY Loop—118  
DX—118  
New Products—120  
Letters—122  
Dealer  
Directory—146  
Propagation—146

# IC-740

## Extensive Versatility for the Serious Operator



The ICOM IC-740 offers features found only on the best amateur equipment and performance second to none.

### Dynamic Range.

The IC-740 is built to withstand strong adjacent signals and still maintain sensitivity and distortion-free output of the desired signal in its

passband. With a dynamic range of over **100 dBm** and an intercept point of **+18dBm**, the IC-740 receiver is a true performer. The IC-740 receiver is also **crunch proof**, and unlike many receivers that have good receiver specifications, it does not collapse under the presence of an RF field.

Other outstanding features that are a must for a modern, high-performance amateur receiver are included in the IC-740:

**Passband Tuning**, adding an additional filtering element to the receiver passband plus

giving control of the actual width of the IF stages of the receiver... variable from 2.4 kHz to 700 kHz in SSB, CW or RTTY.

**Variable AGC**, a two speed AGC with an OFF position allows proper selection of AGC speed **regardless** of mode, VOX or CW breakin. The OFF position makes the IC-740 easily adaptable to frequency converters.

A **Noise Blanker** that really works with both wide and narrow pulse widths and a threshold control to give the optimum blanking with minimum of signal distortion.

And...the IC-740 has an optional **Internal**

**Power Supply** giving 160-10 meter transceiver coverage in **one** package.

EX238  
AC POWER  
SUPPLY



These and other fine receiver features plus ICOM's renowned transmitter audio make the IC-740 the **finest amateur transceiver** around today.

**\$50**  
Cash Rebate

\$50.00 for the purchase of an IC-740.

Begins Dec. 15, 1982  
Expires Mar. 31, 1983



## The World System

# KLM/Tri-EX SALE!

**KT-34A**

REGULAR \$389.95

**SALE \$299**

**KT-34XA**

REGULAR \$569.95

**SALE \$459**

**TRI-EX W-51, 51' TOWER**

REGULAR \$999.95

**SALE \$799**

**NEW! 30M BEAM**  
CALL FOR PRICE/INFO.

PRICES ARE FOB CALIF. EXCEPT FOR CERTAIN COMBINATIONS. PLEASE INQUIRE.



## YAESU



**FT-208R**  
2 METER FM.

**FT-708R**  
70CM, FM.

CALL FOR  
SALE PRICES



## KENWOOD

### TS-930S



W/ANTENNA TUNER

PLUS FREE  
BONUS.

SP-930 SPKR.  
MC-60A MIC  
YK-88C-1 FILTER

**\$1799 SAVE \$230**

### TS-430S



CALL FOR PRICES

## MIRAGE



**2 METER AMPLIFIERS**

**B-3016** 30W IN, 160W OUT  
REG. \$239.95 **\$199.95**

**B-1016** 10W IN, 160W OUT  
REG. \$279.95 **\$249.95**

**B-108** 10W IN, 80W OUT.  
REG. \$179.95 **\$159.95**

**B-23** 2W IN, 30W OUT.  
REG. \$89.95 **\$79.95**

# 5-STORE BUYING POWER in action!

IF ITS FOR HAM RADIO  
WE SHOULD HAVE IT IN  
STOCK AT LOW PRICES.

## ETD ALPHA



SPECIAL PRICES ON  
ALL ALPHA EQUIPMENT.



## ICOM

**NEW! AVAILABLE!**

### IC-R70



GENERAL COVERAGE  
RECEIVER

REGULAR \$749

**SALE \$649**

**FREE SHIPMENT** (U.P.S. Brown)  
CONTINENTAL U.S.A.

EXCEPT FOR SOME ALPHA, TRI EX and KLM ITEMS.

**FREE PHONE 800 854-6046**

9:30AM to 5:30PM PACIFIC TIME.

**OVER-THE-COUNTER, 10AM to 5:30PM.**

**MONDAY THROUGH SATURDAY**

CALIFORNIA CUSTOMERS PLEASE PHONE OR VISIT LISTED STORES.

**ANAHEIM, CA 92801**

2620 W. La Palma,  
(714) 761-3033 (213) 860-2040  
Between Disneyland & Knott's Berry Farm

**BURLINGAME, CA 94010**

999 Howard Ave., (415) 342-5757  
5 miles south on 101 from S.F. Airport.

**SERVING HAMS  
BETTER.**

North...south...east...west.

Bob Ferrero, W6RJ  
Jim Rafferty, N6RJ  
other well known hams  
give you courteous,  
personalized  
service.



**OAKLAND, CA 94609**

2811 Telegraph Ave., (415) 451-5757  
Hwy 24 Downtown. Left 27th off-ramp.

AEA • ALLIANCE • ALPHA • AMECO • AMPHENOL • ARRL • ASTRON  
AVANTI • BELDON • BENCHER • BERK TEC • BIRD • B & W  
BUTTERNUT • CALBOOK • CDE • COLLINS • CURTIS • CUSHCRAFT

**SAN DIEGO, CA 92123**

5375 Kearny Villa Road (619) 560-4900  
Hwy 163 & Clairemont Mesa Blvd.

DAIWA • DRAKE • DX EDGE • DX ENGINEERING • EIMAC  
HUSTLER • HY-GAIN • ICOM • J. W. MILLER • KENWOOD • KLM  
LARSEN • LUNAR • METZ • MFJ • MICRO-LOG • MINI-PRODUCTS

**VAN NUYS, CA 91401**

6265 Sepulveda Blvd., (213) 988-2212  
San Diego Fwy at Victory Blvd.

MIRAGE • NYE • PALOMAR • RUBOT • ROHN • SHURE • TELEX  
TEMPO • TEN-TEC • TRISTAO • VOCOM • YAESU and many more!

Prices, specifications, descriptions subject to change without notice. Calif. residents please add sales tax.



## R-X Noise Bridge



- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less.

The price is \$59.95 in the U.S. and Canada. Add \$3.00 shipping/handling. California residents add sales tax.




Send for FREE catalog describing the R-X Noise Bridge and our complete line of SWR Meters, Preamplifiers, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

# Palomar Engineers

Box 455, Escondido, CA 92025  
Phone: (619) 747-3343

## Ducks are getting smaller! and...

 

## better!



Actual Size

Because you and the leading radio manufacturers want the best-performing, the best looking antenna; Centurion has grown to be the Duck leader. We've developed many smaller antennas to make the hand-held radio perform better, and now the newest duck...the Tuf Duck "mini". It's shorter (about 3") yet it's a full 1/4 wave radiator on VHF.

# CENTURION TUF DUCK ANTENNAS

### CENTURION

Phone 402/467-4491  
Telex 48-4377 CENTURION LCN  
P.O. Box 89246 Lincoln, NE 68501 2846

✓ 102

# INFO

## Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request.

## Editorial Offices:

Pine Street  
Peterborough NH 03458  
Phone: 603-924-9471

## Advertising Offices:

Elm Street  
Peterborough NH 03458  
Phone: 603-924-7138

## Circulation Offices:

Elm Street  
Peterborough NH 03458  
Phone: 603-924-9471

## Subscription Rates

In the United States and Possessions:  
One Year (12 issues) \$25.00  
Two Years (24 issues) \$38.00  
Three Years (36 issues) \$53.00

## Elsewhere:

Canada and Mexico—\$27.97/1 year only, U.S. funds. Foreign surface mail—\$44.97/1 year only, U.S. funds drawn on U.S. bank. Foreign air mail—please inquire.

## To subscribe, renew or change an address:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients.

## Subscription problem or question:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73: *Amateur Radio's Technical Journal* (ISSN 0745-080X) is published monthly by 73, Inc., a subsidiary of Wayne Green, Inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Entire contents copyright © 1983, Wayne Green, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition—University Microfilm, Ann Arbor MI 48106. Postmaster: Send address changes to 73, Subscription Services, PO Box 931, Farmingdale NY 11737.


# ANNOUNCING PRIVATE PATCH II

## TONE TO PULSE SIMPLEX INTERCONNECT

AT LAST...Professional quality interconnect at an *affordable* price! Imagine the convenience of having your own private, commercial quality mobile telephone in your car. And without the hassles of shared systems. Put your base FM transceiver to work while on the road. Our *ultra state of the art* digitally processed audio scheme (Patent pending) *totally* eliminates the continuous train of squelch tails which has kept you away from sampling interconnects. Our nonsampling approach has additional benefits: 1. Interface to your transceiver is the MOST SIMPLE EVER. Connects only to microphone and speaker jacks! NO INTERNAL CONNECTIONS OR MODIFICATIONS REQUIRED! 15 minutes typical installation time. 2. Works with ANY FM transceiver. (T/R speed is not critical.) 3. Operates through any repeater or simplex without use of tone equipment. Imagine having TOTAL access to your own home phone from 100 miles away! Our *busy channel ringback inhibit logic* prevents "accidental" interference to a QSO in progress when a phone call is received. This feature will keep you out of hot water with co-channel users! Discover for yourself what high quality simplex interconnect sounds like. Call us, and listen to actual "on the air" tapes of this incomparable interconnect product.
 
### STANDARD FEATURES

- Compatible with either rotary or tone exchanges
- 16 Digit buffer memory — dial as fast as you want
- 3201 tone decoder chip
- High quality glass circuit board
- CW identification



**QUALITY AND ENGINEERING...  
THAT YOU CAN DEPEND ON!!**



- Five digit user programmable sequential access code — 60,000 code combinations
- Sophisticated toll restrict — restricts any quantity of leading digits
- Both accessing and dialing are compatible with speed dialing equipment
- Operates superb through repeaters — no special tone equipment required
- Three/six minute "time out" timer is resettable from mobile four CW ID warnings during last minute
- Ringback (reverse patch) pages you once with CW ID — answer when convenient with your access code
- Busy channel ringback inhibit logic — prevents accidental interference to QSO in progress
- Most easily interfaced autopatch on the market
- Positive control logic
- Fully digital timing — there are *no* timing adjustments! assures quick easy set-up
- Touch tone™ digits and strobe pulse available on DIP socket
- Modular phone jack and cord
- Self contained 115 VAC supply (230 VAC 50/60 cycle export model available)

**PRIVATE PATCH II \$475**

**NOW REDUCED**

**PRIVATE PATCH I \$399**

HAS MOST OPERATIONAL FEATURES  
OF PRIVATE PATCH II — BUT IS FOR  
USE ONLY ON DTMF EXCHANGES

**AND OF COURSE:**

**ONE YEAR WARRANTY  
14 DAY RETURN PRIVILEGE  
UNMATCHED CUSTOMER SERVICE**



SEND OR CALL FOR BROCHURES  
INQUIRE ABOUT COMMERCIAL MODELS  
DEALERSHIPS INVITED


# Connect Systems

Formerly Auto Connect

P.O. BOX 4155  
TORRANCE, CA 90510  
PHONE (213) 540-1053

# W2NSD/1 NEVER SAY DIE

editorial by Wayne Green

 

## THE CONNECTICUT CONTEST, CERTIFICATE, AND CHOWDERHEAD CLUB

There are three items on my agenda which may be of less than great importance to you. One has to do with some wondrous changes wrought by the International Amateur Radio Union, wherein, I was told by several of the assembled at the recent Bangkok hamfest, the ARRL was finally dumped out of the driver's seat. There was an unseemly amount of rejoicing among our supposed friends overseas.

While the League has graciously permitted foreign amateur radio societies to belong to this illustrious organization, HQ always insisted that they have complete control of it. Unrest has

been brewing for quite a few years over this, with a growing number of malcontents fomenting revolution over the high-handed, low-action management by the League.

Oh, there goes that miserably crotchety old Wayne Green, griping about the League again... right? Well, you probably believe in the Tooth Fairy, too, so who am I to suggest you take off your smoked glasses and see what your bumbling voting record at ARRL elections has cost you. But, if you even have a shred of question about how our beloved League is perceived overseas, then for heaven's sake try to find your old rig up there in the attic and get on the air for a day or two... make some DX contacts... and, after you've gone

through all the usual drivel... probably mercifully covered up by QRM... ask 'em what they think. You'll get an earful from a bunch of 'em.

At any rate, there was general rejoicing at Bangkok over the freeing of the slaves as news of the vote to move IARU headquarters from some almost totally unknown town in Connecticut to Geneva was spread. Who knows, perhaps the IARU will now be able to develop some clout!

Item two has to do with the recent director election wherein Mary Lewis eked out a win by less than ten votes... raising hell with the morale of the entrenched chauvinists at HQ. They'd said for years that, dammit, this was a man's hobby and they didn't need any women on the board of directors. One ex-president of the outfit said that hell would freeze over before they'd let a woman get on the board. I wondered about that, so while in Bangkok I made a visit to Hell (a well-known Bangkok restaurant) and found that it had not, in fact, frozen over. Well, so much for ex-presidential predictions. No wonder they dumped him.

Then there was the defeat of poor Don Miller out in Indiana. Don has had a rough time of it. First the HQ gang did all they could to keep him from being elected the first time. Then they trumped up a bunch of baloney and scared him into resigning, threatening to put on the pressure to get him fired from his job. Knowing that HQ had been able to get Mary's job, he panicked. With Dannals and Baldwin out of the driver's seat at HQ, Don apparently thought he might be able to make it back into the di-


rector's chair again. Well, one thing no one at HQ wants to have to live with is a director who starts asking questions and shows any initiative at really directing. They have their short yearly meeting, vote on everything unanimously, and go home. Do not rock the boat, please. Remember that we here at ARRL are all one happy family and that Wayne Green is a kook. Close, but no cigar... actually I'm a cook... love to cook.

So Metzger is your Midwest Director and those who voted for this chap are welcome to him. Some of the other directors like him, others sneer and call him a toadying turkey. That sort of talk is ill-becoming of directors, even if it might be true. I try to look at the bright side... the more all this politics screws up the League, the more interesting things I can write about.

Since most of the older timers at the League have bailed out, the attitude has improved a bit. The old-timers' perception of the membership was as a bunch of nitwits who could easily be led into anything they wanted. Unfortunately, there was more truth in this perception at times than was comfortable. For every thinking ARRL member, there was a counterbalancing group of blind followers, eager to buy whatever the latest party line demanded.

The laughter was uncontrolled at HQ when they came out with incentive licensing. This was their plan to disenfranchise 85% of the hams from the phone bands, returning us to the pre-WWII licensing system of two classes, one with phone bands and the other without. Would you believe that almost 50% of the ARRL members bought the idea... mostly on the basis of the nice name they'd given it. Who could be against *incentive* licensing? Only those who bothered to read the fine print, which turned out to be a minority. And a lot of those opposing it were fighting it because they didn't want to have to go down and retake the test all over again rather than because the whole idea was ridiculous.

 The few firms still left in the amateur radio industry are waiting to see some positive moves by the new management of the League. There's not much left of the industry any more. 95% of the manufacturers are long gone... and 95% of the dealers are gone. We used to



## DL9GI

### QSL OF THE MONTH

This month's winning QSL is from Lutz Hännig DL9GI of Berlin, West Germany. Lutz's unique design depicts a confused-looking Red Baron flying into the center of a multi-colored radio wave. The card cleverly focuses your attention to the center by moving from the black background to the bright yellow and red of the middle. The rapid shift in hue lends depth to the scene, making it appear as if the aviator were flying into the maw of some great creature. Lutz's callsign, emblazoned in white at the bottom, ensures that the viewer knows where this card is from.

If you would like to enter our QSL card contest, put your QSL in an envelope with your choice of a book from 73's Radio Bookshop and send it to 73, Pine Street, Peterborough NH 03458, Attn: QSL of the Month. Entries which do not use an envelope or do not specify a book will not be considered.

# NEW

# Watts to see...



## Big LCD, Big 45 W, Big 21 memories, compact.

### TR-7950/7930

Outstanding features providing maximum ease of operation include a large, easy-to-read (direct sunlight or dark) LCD display, 21 multi-function memories, automatic offset, programmable priority channel, memory and band scans, built-in lithium battery memory back-up, built-in 16-key autopatch encoder, and a choice of a hefty 45 watts output (TR-7950), or 25 watts output (TR-7930).

#### TR-7950/TR-7930 FEATURES:

- **NEW, large, easy-to-read LCD digital display**  
Easy to read in direct sunlight or dark (back-lighted). Displays transmit/receive frequencies, memory channel, repeater offset, (+, S, -), sub-tone number (F-0, 1, 2, 3), tone, scan, and memory scan lock-out. Includes LED S/R/F bar meter, and LED indicators for REVERSE, CENTER TUNING, PRIORITY, and ON AIR.
- **21 NEW, multi-function memory channels**  
Stores frequency, repeater offset, and optional sub-tone channels. Memories 1 through 15 for simplex or  $\pm 600$  kHz offset. Memory pairs 16/17, and 18/19 are paired for non-standard repeater offset. Memories "A" and "B" set upper and lower scan limits, or for simplex or  $\pm 600$  kHz offset. In MEMORY mode, a circle of light appears around the memory selector knob. When the memory selector knob is rotated in either direction to channel 1, an audible "beep" will sound.
- **Choice of 45 or 25 watts output**  
The TR-7950 provides a hefty 45 watts output, while the TR-7930 features a more modest 25 watts. A HI/LOW power switch allows power reduction to approx. 5 watts.

- **Long-life lithium battery memory back-up**  
Built-in lithium battery has an estimated 5 year life.
  - **Automatic offset**  
The microprocessor is pre-programmed for simplex or  $\pm 600$  kHz offset, in accordance with the 2 meter band plan. "OS" key allows manual change in offset.
  - **Programmable priority alert**  
The PRIORITY channel may be programmed in any of the 21 memories. With ALERT switch "ON," a dual "beep" sounds when a signal is present on the PRIORITY channel. An OPER switch allows an easy move to the PRIORITY channel.
  - **Programmable memory scan lock-out**  
"LO" key for programming scan to skip selected memory channels, without erasing the memory.
  - **Programmable band-scan width**  
The lower limit may be programmed into memory "A," and the upper limit into memory "B"
  - **Center stop during band-scan, with indicator**  
Stops in center of channel during band-scan, with center tuning indicator.
  - **Scan resume selectable**  
Scan stops on busy channel. Selectable automatic time resume-scan (approx. 5 sec., adjustable), or carrier operated resume-scan. A scan delay of approx. 1.5 seconds built-in.
  - **Scan control using up/down microphone**  
Momentarily pressing UP or DOWN button on microphone tunes one step in the selected direction, on memory or on 5-kHz step tuning. Holding the button for about 2 seconds starts UP or DOWN automatic scan action. Scan start also possible using "SC" key on keyboard. Scan may be cancelled by momentarily pressing the PTT switch, or by pressing both UP/DOWN buttons simultaneously.
  - **Programmable sub-tone channels**  
Optional TU-79 3 frequency sub-tone unit provides keyboard selectable sub-tone channels, which may be stored in memory.
  - **Built-in 16-key autopatch, with monitor**  
The keyboard functions as a 16-key autopatch encoder during transmit. DTMF tones appear in the speaker output when a key is pressed during transmit.
  - **Front panel keyboard control**  
Used for selecting frequency, offset, programming memories, controlling scan, and autopatch encode. Keyboard lighting is provided.
  - **Extended frequency coverage**  
Covers 142.000-148.995 MHz, in 5-kHz steps.
  - **Repeater reverse switch**  
Locking-type switch, with indicator.
  - **"Beeper" amplified through speaker**
  - **Compact, lightweight design**
  - **Easy-to-install adjustable-angle mobile mounting bracket**
- Optional accessories:**
- TU-79 three frequency tone unit.
  - KPS-12 fixed-station power supply for TR-7950.
  - KPS-7A fixed-station power supply for TR-7930.
  - SP-40 compact mobile speaker.
- More information on the TR-7950 and TR-7930 is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.

# KENWOOD

...pacesetter in amateur radio

Specifications and prices are subject to change without notice or obligation.

# STAFF

**PUBLISHER/EDITOR**

Wayne Green W2NSD/1

**EXECUTIVE VICE PRESIDENT**

Sherry Smythe-Green

**ASSISTANT PUBLISHER/EDITOR**

Jeff DeTray WB8BTB

**MANAGING EDITOR**

John Burnett

**ASST. MANAGING EDITOR**

Susan Philbrick

**EDITORIAL ASSISTANTS**

Nancy Noyd  
Richard Phenix  
Steve Jewett

**TECHNICAL EDITOR**

Avery L. Jenkins WB8JLG

**ASSISTANT TO THE PRESIDENT**

Matthew Smith KA1EI

**ASSOCIATES**

Robert Baker WB2GFE  
John Edwards K1ZU  
Bill Gosney KE7C  
Sanger Green  
Chod Harris VP2ML  
Dr. Marc Leavey WA3AJR  
J. H. Nelson  
Bill Pasternak WA8ITF  
Peter Stark K2OAW

**PRODUCTION MANAGER/ PUBLICATIONS**

Nancy Salmon

**ASST. PRODUCTION MANAGER/PUBLICATIONS**

Michael Murphy

**ADVERTISING GRAPHICS MANAGERS**

Scott W. Philbrick  
Fiona Davies  
Bruce Hedin  
Jane Preston

**PROMOTION COORDINATOR**

Christine Destrempes

**PRODUCTION**

Frances Benton  
Linda Drew  
Denzel Dyer  
Michael Ford  
Phil Geraci  
Donna Hartwell  
Kimberly Nadeau  
Paula Ramsey  
Dianne K. Ritson  
Anne Rocchio  
Mary Seaver  
Deborah Stone  
Theresa Verville  
David Wozmak  
Karen Wozmak

**PHOTOGRAPHY**

Thomas Villeneuve  
Sandra Dukette  
Laurie Jennison  
Irene Vail  
Robert M. Villeneuve

**TYPESETTING**

Sara Bedell  
Marie Barker  
Melody Bedell  
Michelle DesRochers  
Jennifer Fay  
Lynn Haines  
Linda Locke  
Nancy Wilson-Newman  
Debbie Nutting  
Karen Stewart  
Susan Wellier

**GENERAL MANAGER**

Debra Wetherbee

**CONTROLLER**

Roger J. Murphy

**ACCOUNTING MANAGER**

Knud Keller KV4GG/1

**CIRCULATION MANAGER**

Patricia Ferrante  
603-924-9471

**BULK SALES MANAGER**

Ginnie Boudrieau  
1-800-343-0728

**ADVERTISING**

603-924-7138  
Jim Gray W1XU, Mgr.  
Nancy Clampa, Asst. Mgr.  
Ross Kenyon KA1GAV  
Cornelia Taylor

have nearly a thousand ham dealers around the country selling 73 over their counters! Now there's a few score. You know this when you look around for some place to go to see a new rig. A few years ago, ham stores were almost everywhere... today they aren't. There's just one or two left in all of New England, for example.

## THE CODE

Which really brings us to a discussion of the Morse code. Just what you really wanted, eh? Yes, I know the League is dedicated to preserving the code. And, believe me, I have heard all the old saws about the code being the only thing protecting us from the hordes of CBers and keeping the ham bands from being like the CB bands. What a crock of...er...stuff. Frankly, I'm not at all convinced that if we set up booths on the street and gave away ham tickets to

any passerby, we could attract anyone to our hobby.

There is now a rising call for getting older people into amateur radio, our having failed to interest kids any longer. Just what we need. Sure, the hobby is great for oldsters. It would keep them from getting lonely. It would give them something to do in their twilight years...kerchunking repeaters and jamming nets. Why save all that fun for just the Extra-class hams, eh? Of course, we aren't going to provide our country with much in the way of technicians, engineers, and scientists this way...or electronic fodder for our war machine, should we decide to save the world for capitalism again. But we would be able to sell some rigs, thereby enriching the lives of the Japanese manufacturers. I say let's get at it. Let's get into the old folks homes and set up club stations...give licensing classes

...and call in Bash so faltering memories won't even have to learn any theory.


Word from the underground has reached me that the outfit selling the FCC Morse-code exams at Dayton was run by none other than a very well-known California ham. We really have to see that those tapes get better distribution so that old people, who have more trouble than kids with the code, are not discriminated against. Why should we penalize old people just because they can't learn the code?

As a matter of fact, if we are going to go along with the modern morality, we should set up a system whereby anyone who has shown proof that he has seriously tried to learn the code, yet failed, would get a license. In today's world, it is not the answer to the question

*Continued on page 101*

## Well... I Can Dream, Can't I?

by Bandel Linn K4PP

 

**"It's the FCC! They're not just renewing your license—they're also giving you a Caribbean cruise!"**

**TRADE IN  
or  
CASH DISCOUNT**

**Call Toll-Free  
1-800-325-3636  
for the  
BEST DEAL**

**We trade on NEW or USED  
Call for prices on available  
USED equipment**

**HAM RADIO CENTER**

8340-42 Olive Blvd. • P. O. Box 28271 • St. Louis, MO 63132



IN MISSOURI CALL  
**1-314-993-6060**



# RTTY Tuning: The New Solution

*This simple tuning indicator whipped the competition and took first place in 73's Home-Brew II Contest.*

What is your favorite method to tune in a radioteletype (RTTY) signal quickly and accurately on an SSB receiver? A dual ellipse on an oscilloscope? Light-emitting diodes (LEDs) activated by mark and space filters? A signal-strength meter? By ear? Here is a new one that might make you change your mind.

## Background/The Problem

When Teletype® signals are sent through audio channels, they are usually conveyed by switching between two tones with a different timing pattern for each of the characters. During peri-

ods when no characters are being sent, a steady tone, called the "mark" tone, is present. The other tone is called the "space" tone. A device called a "terminal unit" (TU) extracts these two particular tones from any background noise and produces a digital signal suitable for a printer or computer.

If this audio signal is coming across a telephone line or an FM radio link, the frequencies of the tones at the receiving end will be the same as at the origin. However, there can be a problem when using an SSB receiver, because a slight mistuning will change the frequencies

of the tones heard and the terminal unit will not work. Over the years, various methods have been devised to indicate when the proper tones are detected. Here is a new one.

## A New Solution

As shown in Photo A, the circuit displays its output with a row of 20 LEDs. Each one will light up when the strongest audio frequency present is within its particular range. The two with the pointers over them correspond to the mark and space tones. A constant mark signal is tuned properly when the LED under the left marker is lit. When characters are being received, the LEDs under both markers will be lit. If the tones are low in frequency, LEDs to the left of these positions will be lit. Higher frequencies activate LEDs farther to the right. It's as easy as tuning an FM broadcast receiver with a tuning meter!

## Theory of Operation

The simplified block dia-

gram in Fig. 1 illustrates the basic principle involved. Each time the input signal completes a cycle, the current content of the counter is captured in the latch. After a brief delay, the counter is reset and resumes counting for another cycle of the input signal. Meanwhile, a decoder is looking at the output of the latch and selects one of the LEDs based upon it.

For example, let's suppose we had a clock of 200 kHz and an input signal of 2 kHz. During each cycle of the input signal there would be 100 clock pulses, so the counter would contain 100 when the latch grabs the counter's output. If there was an LED corresponding to a count of 100, the decoder would cause it to light up until a different count was obtained from the counter. A higher frequency input would result in a shorter period, a smaller count, and a different LED.

Keeping this simplified model in mind, let's look at the actual circuit (Figs. 2 and

Photo by Mark Hood

 


Photo A. Appearance of the display for a correctly tuned signal.

 


Fig. 1. Simplified block diagram.

 


Fig. 2. Main circuit for tuning indicator.

3) and see how it differs. Starting from the audio input on the left, the first thing you will notice is the 565 phase-locked loop. I initially tried some experiments with bandpass filters and a Schmidt trigger. This worked great with a nice clean waveform from a signal generator, but was pretty useless with a noisy signal from a sideband receiver. The phase-locked loop does a good job of following a signal through the noise and providing a nice clean square wave of the same frequency for later logic circuits. The two diodes before it provide protection against large signals that could damage the IC.

Next we have a couple of one-shots (IC2) to generate timing pulses at the end of each cycle. Four separate steps are involved: (1) Stop the clock so the count isn't changing during latching. (2) Capture the contents of the counter in the latch. (3) Reset the counter. (4) Restart the clock.

When the counter is reset,

it is set to -3 rather than zero as you would probably expect. (See pins 9, 10, 1, and 15 of the counters.) This is to make the mark and space tones fall in the middle of the frequency ranges for the corresponding LEDs.

When the most significant bit of the count (IC5, pin 7) is 0 and the next bit (pin 6) is 1, the count is in the range of 64-127. This is the region where the display is

enabled. If the counter content reaches 128, IC6 is disabled through pin 4 and counting stops. This prevents overflowing and a false display for a very low frequency input.

Under the latch (IC7), you will notice a 7485 magnitude comparator. Each time the latch is clocked, it compares the counts for the current and preceding cycles. When the low-order four

bits are the same, the display is enabled for the next cycle. This blanks the display during changes, resulting in a much cleaner appearance and dimming with only noise present. High-order bits could also be compared with another chip but I doubt it would have much effect because counts for consecutive cycles differing by a multiple of 16 are probably quite rare.

 


Fig. 3. Display portion of tuning indicator.

```

10 REM-- RTTY TUNING INDICATOR DESIGN PROGRAM.
20 REM--
30 REM-- WR20SZ, APRIL 1982
40 REM--
50 REM-- M9 AND S9 ARE DESIRED COUNTS FOR MARK & SPACE LEDS.
60 REM--
70 M9=91
80 S9=84
90 REM--
100 PRINT "WHAT IS MARK (LOWER) FREQUENCY";
110 INPUT M
120 PRINT "WHAT IS SPACE (HIGHER) FREQUENCY";
130 INPUT S
140 IF M>S THEN PRINT "MARK MUST BE LOWER FREQUENCY." \ STOP
150 REM--
160 REM-- CALCULATE COUNTER PRESET VALUE.
170 REM--
180 P=INT((M9*M-S9*S)/(M-S)+.5)
190 IF ABS(P)>63 THEN PRINT "INVALID PRESET COUNT." \ STOP
200 REM--
210 REM-- CALCULATE THE CRYSTAL FREQUENCY.
220 REM--
230 X=((M9-P)*M+(S9-P)*S)*8
240 REM--
250 REM-- PRINT CALCULATED VALUES FOR CIRCUIT AND
260 REM-- PRODUCE CHART OF FREQUENCY RANGES FOR EACH LED.
270 REM--
280 PRINT "WHERE WOULD YOU LIKE THE OUTPUT (TERMINAL IS
DEFAULT)";
290 INPUT O$
300 IF O$="" THEN O$="TT:"
310 OPEN O$ FOR OUTPUT AS FILE #1
320 PRINT #1,"MARK FREQUENCY =";M;"HZ, SPACE FREQUENCY =";S;"HZ"
330 PRINT #1
340 REM--
350 PRINT #1
360 PRINT #1,"COUNTER PRESET = ";P;" (BINARY ";
370 N=128
380 F2=P
390 IF F2<0 THEN F2=F2+256

```

```

400 IF P2<N THEN 440
410 PRINT #1,"1";
420 F2=F2-N
430 GO TO 450
440 PRINT #1,"0";
450 N=N/2
460 IF N>=1 THEN 400
470 PRINT #1,"";
480 PRINT #1,"CRYSTAL FREQUENCY =";X/1.00000E+06;"MHZ"
490 PRINT #1
500 PRINT #1
510 PRINT #1
530 B=127.5 \ GOSUB 620 \ GOSUB 680
540 B=111.5 \ GOSUB 620 \ GOSUB 680
550 FOR B=95.5 TO 79.5 STEP -1
560 GOSUB 620 \ GOSUB 680
570 NEXT B
580 B=71.5 \ GOSUB 620 \ GOSUB 680
590 B=63.5 \ GOSUB 620
600 CLOSE #1
610 STOP
620 REM--
630 REM-- PRINT AUDIO FREQUENCY BOUNDARY.
640 REM--
650 F=INT(X/16/(B-P)+.5)
660 PRINT #1,"---";F
670 RETURN
680 REM--
690 REM-- PRINT "##" REPRESENTING A LED.
700 REM-- APPEND 'M' OR 'S' FOR MARK AND SPACE TONES.
710 REM--
720 C$="###"
730 IF B-.5=M9 THEN C$=C$+" M"
740 IF B-.5=S9 THEN C$=C$+" S"
750 PRINT #1,"C$
760 RETURN

```

Fig. 4. Basic program to compute crystal frequency and counter preset for given mark and space tones.

## Construction and Adjustment

As shown in Photo A, the LED displays and three decoder chips are mounted on a small piece of perfboard which can be installed on the front panel of a terminal unit. The rest of the proto-

type was constructed with wire wrapping for ease of modification during development. You can reduce the cost by using solder-tail sockets with point-to-point wiring or making a PC board.

With no input applied to the circuit, adjust R3 so that

the LED just to the left of the center line is lit.

Power requirements are + and -12 volts at about 25 milliamps and 5 volts at about 350 milliamps.

## Modifications

The crystal frequency and

counter preset value shown in the schematic are for the standard RTTY tones of 2125 and 2295 but can easily be changed for a different pair of tones in the same neighborhood. The Basic program in Fig. 4 computes these values from

## Parts List

### Semiconductors

IC1	NE565		\$ 1.00
IC2	74221		1.25
IC3	7404		.22
IC4	7493		.52
IC5, 6	74191	2 x	.85
IC7	74273		1.25
IC8	7410		.19
IC9	7485		.65
IC10-12	7445	3 x	.69
D1, 2	1N4148 or 1N914 diode	2 x	.20
Z1, 2	1N4735A 6.2-V, 1-Watt zener	2 x	.30
LED1, 2	MV57164 10-segment bar-graph display (Radio Shack part number 276-081)	2 x	3.79

### Resistors (1/4-Watt unless noted)

R1, 2	1k	2 x	.07
R3	5k 15-turn trimmer		1.25
R4, 5	220-Ohm, 1/2-Watt	2 x	.07
R6, 7	4.7k	2 x	.07
R8	330-Ohm		.07
R9	470-Ohm		.07
R10	82-Ohm		.07

### Capacitors

C1, 3	.1-uF, disc ceramic	2 x	.15
C2	.001-uF, disc ceramic		.10
C4	.047-uF, mylar™		.15
C5, 6	33-pF, mica	2 x	.26

C7, 8	20-pF, mica	2 x	.26
—	.01-uF, disc ceramic (to bypass +5 volts to ground)	5 x	.10
<b>Other</b>			
X1	3.195-MHz crystal, FT-243 holder, .01% tolerance, 32-pF load capacity (available from Jan Crystals)		3.00
	solder-tail IC sockets, 14-pin	7 x	.14
	16-pin	4 x	.16
	20-pin		.29
	perfboard		1.59
	total about		\$28.00

## Obtaining Parts

The only unusual components in this device are the 10-segment LED bar-graph displays. As indicated in the parts list, these are available at your local Radio Shack store. If there is not a Radio Shack in your part of the world, use 20 separate LEDs instead.

I happened to use a crystal in an HC6/U holder. If you don't mind the size and appearance of an FT-243 holder (like Novices used in the old days) you can save a couple of bucks by getting a crystal with only .01% tolerance which is still more than adequate.

Everything else is quite ordinary and available from various dealers who advertise in the back of 73. The circuit is not at all critical and minor substitutions should not affect performance.

# Ringo Ranger II

## Simply the best

The best combination of gain, bandwidth and low angle radiation for simplex or repeater operation.

**Quick easy assembly and installation**

**Mount anywhere with compact dimensions and neat appearance**

**Proven performance and durability in all environments**

**Complete FM band coverage**

**One year warranty**

Cushcraft antennas created the FM antenna revolution by making the best performance and value available to every ham. We continue to set the pace with a broad line of antennas for every FM application. Tune across the band and you will find the overwhelming majority of hams using one, two, or more Cushcraft antennas. The reason is very simply that they are the best. Now is the time for you to enjoy the value of a Cushcraft antenna. See your nearby dealer today.

### RINGO RANGER II

ARX-2B	134-164 MHz
ARX-220B	220-225 MHz
ARX-450B	435-450 MHz

### RINGO RANGER


ARX-2	134-164 MHz
-------	-------------

### RINGO

AR-6	50-54 MHz
AR-2	135-175 MHz
AR-10	28-29.7 MHz
AR-220	220-225 MHz
AR-450	440-460 MHz

### MOBILE ANTENNAS

AMS-147	144-148 MHz	Magnetic Mount
ATS-147	144-148 MHz	Trunk Lip Mount
AMS-220	220-225 MHz	Magnetic Mount
ATS-220	220-225 MHz	Trunk Lip Mount

 

### YAGIS

A147-4	145.5-148 MHz	4 Element
A147-11	145.5-148 MHz	11 Element
A147-22	145.5-148 MHz	22 Element
214-FB	145.5-148 MHz	14 Element
A220-7	220-225 MHz	7 Element
A449-6	440-450 MHz	6 Element
A449-11	440-450 MHz	11 Element

### CROSS YAGI

FOR CW/SSB and FM

A147-20T	144-146 MHz	Horizontal
	145.5-148 MHz	Vertical



**cushcraft**  
CORPORATION

**THE ANTENNA COMPANY**  
48 Perimeter Road, P.O. Box 4680  
Manchester, NH 03108

106

# CES INTRODUCES THE NEW 510SA "SMART PATCH"

## The State of the Art Simplex Interconnect

Communications Electronics Specialties introduces the CES 510SA "Smart" Simplex Autopatch, with many important new features never available before:

- Three digit control codes with user programming.
- A sophisticated toll restrict provides positive long distance lock out.
- Time-out and COR activity timers with warning beeps and digital programming.
- Rotary or DTMF dialing.
- Phone line in-use detector prevents interrupting a call in progress, and sends unique CW sequence.
- Phone ring detection logic enables unique CW sequence.
- Digital programming of the sample rate and width, and noise gate sensitivity control, for easy interfacing with most radios.

Simple and direct connections to radio.

Options available:

- Smart CW identifier with unique CW messages for each patch function.
- FCC type accepted phone line coupler.
- Special tone squelch kit to operate patch through repeaters.



The 510SA—the newest advance in interconnect technology, from the innovators at:  
**Communications Electronics Specialties, Inc.**  
 Post Office Box 507 • Winter Park, Florida 32790  
 (305) 645-0474 • Toll-free (for orders only): (800) 327-9956

## NEW ELECTRONIC KITS

<b>ALL IN ONE RTTY DEMODULATOR KIT</b> FEATURES: ON BOARD POWER SUPPLY, AFSK GENERATOR, PROVISIONS FOR LOOP SUPPLY, ACTIVE FILTERS OR OPTIONAL TORROID FILTER, AUTOSTART, ANTISPACER. PCB KIT NO. 23-1776 \$89.95		<b>ONE AMP POWER SUPPLY KITS</b> BELOW 3 KITS 22 EDGE CON 4-1/2X6 TU/LOOP SUPPLY PCB 23-1723 \$57.99 + 6 - 12V & +5 PCB 23-2128 \$35.99 LOOP SUPPLY PCB 23-2028 \$33.99 BELOW 2 KITS NOT ABOVE FORMAT + 6 - 12V & +5 2-1/2 X 5 FOR PLL TU 12 PIN EDGE CONN. PCB 23-1716 \$29.95 + OR -5 TO 24V (SPECIFY POLARITY AND VOLTAGE) PCB 23-0512 2X4-3/8 \$14.95	
<b>RTTY SPEED CONVERTER</b> CONVERTS 80, 75 & 100 WPM BAUDOT CODE TO 100 WPM CODE FOR BAUDOT MACHINES REVERSES SAME FOR SENDING. FEATURES SELCAL, BUFFERING AND INTERFACE FOR BAUDOT PTR. PCB KIT 23-1816 \$89.95		<b>RTTY DEMODULATORS</b> DM-60 ACTIVE OR OPTIONAL TORROID FILTER, AUTOSTART, ANTISPACER, SINGLE SHIFT (UP-DATED ST-6 ON ONE BOARD.) PCB KIT NO. 23-1712 \$59.95 DM-10 PLL TU DESIGN WITH ACTIVE FILTER FRONT END. PCB 23-1719 \$29.95	
<b>BAUDOT/ASCII CONVERTER</b> MICRO BASED RTTY CONVERTER CONVERTS BAUDOT TO ASCII FOR RECEIVE, ASCII TO BAUDOT FOR TRANSMITTING. FEATURES SELCAL, BUFFERING AND INTERFACE FOR 110 BAUD PTR. PCB KIT 23-1815 \$89.95		<b>AFSK GENERATOR FOR RTTY</b> ROCK SOLID CRYSTAL CONTROLLED AFSK GENERATOR, VIRTUALLY DRIFT FREE, TWO POPULAR SIZES -- SPECIFY SIZE. PCB KIT NO. 23-1717 2-1/2X6 \$29.95 PCB KIT NO. 23-1710 4-1/2X6 \$31.95	
<b>AUTO CW/D KIT</b> FEATURES ON BOARD TEN MINUTE TIMER WITH TTL, PLUS/MINUS 12 INTERFACE AND UP TO 32 DOTS, DASHES OR SPACES. PCB KIT NO. 23-1721 4-1/2X6 \$29.95		<b>INTERFACE KIT</b> OPTED RS232C XSTR LOOP TO TTL TTL TO LOOP PCB23-1722 \$13.95	
<b>TU BANDPASS FILTER</b> ACTIVE FILTER AP60 PCB 23-1718 \$ 9.95	<b>LOGIC/GLITCH PROBE</b> FREEZES HIGH SPEED PULSE OR LOGIC LVL PCB 23-1706 \$15.95	<b>RS232 LINE MONITOR</b> MONITORS 9 COMMON RS232 LINES W/LED PCB 23-1707 \$19.95	<b>ONE KC SOURCE KIT</b> PCB 23-1733 \$ 3.95
<b>AUDIO AMPLIFIER KIT</b> PCB 23-1731 \$ 3.98	<b>tone CONTROL RELAY</b> PCB 23-1730 \$ 3.95	<b>PULSE GENERATOR KIT</b> PCB 23-1732 \$ 3.95	

## QUALITY LOW PRICED COMPONENTS

<b>CABINETS</b> 03-5004 4.0 2.5 2.0 \$5.53 03-5008 4.0 5.0 2.0 6.20 03-5010 4.0 6.0 3.0 7.99 03-5016 6.0 2.5 2.0 5.95 03-5020 5.0 7.5 2.5 8.79 03-5024 4.0 3.0 4.0 6.75 03-5028 8.0 3.5 2.5 7.65 03-5032 5.0 6.0 4.0 8.99 03-5036 4.0 3.0 6.0 7.47 03-5040 10.0 5.0 3.5 10.45 03-5044 5.0 5.0 7.5 11.49	<b>UNIVERSAL CIRCUIT BOARDS</b> THREE SIZES AVAILABLE AS SHOWN FOR ONE I.C. 11-1700 \$ .89 FOR 3 ICS NOT SHOWN 11-1702 \$1.39 HORIZ. LAYOUT-UP TO 4-14PIN ICS. \$1.29 11-1703
<b>DRY TRANSFER DATAMARK SETS</b> TV AND HI-FI 21-0058 \$2.50 HAM RADIO & CB 21-0059 \$2.50 EXPERIMENTER 21-0060 \$2.50 TEST & INSTRUL 21-0061 \$2.50 MARK & SWITCH 21-0062 \$2.50 ALPH & NUMBERS 21-0063 \$2.50 1/4 IN ALPHABET 21-0064 \$2.50 1/2 IN ALPHABET 21-0065 \$2.50 TITLES FOR ELECTRONIC EQUIP. 21-9581 - BLACK TITLES \$9.95 METER DIAL KIT 21-0988 \$9.95 DATAMARK SPRAY SEALER GLOSS 21-4177 \$4.25 MATTE 21-4178 \$4.25	DONT MISS OUR 1983 CATALOG WITH OVER 1200 ITEMS SEND \$1.00 (REFUNDABLE ON FIRST ORDER) FOR OUR CATALOG, OR SEND A TWO STAMPS FOR OUR FREE FLYER ALL KITS INCLUDE PARTS FOR PRINTED CIRCUIT BOARD ONLY. PLEASE ADD \$2.00 FOR SHIPPING. ADD \$5.00 ADDITIONAL FOR ORDERS UNDER \$8 CHECKS - MASTER CARD - VISA - COO <b>Daytapro Electronics, Inc.</b> 3029 N WILSHIRE LN., ARLINGTON HTS. ILL. 60004 VISA 312-870-0555

the tone frequencies and prints a chart (Fig. 5) indicating the frequency range for each LED.

Mark frequency = 2125 Hz,  
 Space frequency = 2295 Hz,  
 Counter preset = -3 (binary 1111101), Crystal frequency = 3.19532 MHz

- ## -1530
- ## -1744
- ## -2027
- ## -2048
- ## -2070
- ## -2091
- ## -2113
- ## M -2136
- ## -2159
- ## -2183
- ## -2207
- ## -2231
- ## -2257
- ## -2282
- ## S -2309
- ## -2336
- ## -2363
- ## -2392
- ## -2421
- ## -2681
- ## -3003

## Use and Conclusion

The circuit requires a minimum of 10 millivolts peak-to-peak for good tracking of the input signal. Acceptable results can be obtained by connecting the tuning indicator directly to the receiver's speaker, but a cleaner signal will produce a more pleasant display. If your terminal unit has a bandpass filter, connect this circuit after the filter, but before the limiter. If you don't have a bandpass filter, I suggest that you build one (see 73, September, 1977, page 38) or buy one such as the Flesher PS-170. It's simple, inexpensive, and makes a big difference when trying to copy RTTY under noisy conditions.

For a couple decades, most people agreed that a dual ellipse pattern on a CRT was the best way to see when a RTTY signal was tuned in properly. Try this circuit and you might not be one of them anymore. ■

Fig. 5. Output of program in Fig. 4 for standard tones of 2125 and 2295.

# hy-gain®

## V Series Antennas

### More ERP\* for your Repeater


Hy-Gain V Series antennas focus the omnidirectional pattern evenly at the horizon, without high angle lobes or horizontally polarized content. By concentrating the power at the horizon you get cleaner transmissions over longer distances, improved communications in valleys and reduced picket fencing of the signal between tall structures. A Hy-Gain V antenna is like adding an amplifier and receiver pre amp. And, because antennas which "talk" louder, also "hear" better, a V Series antenna is also ideal for your home QTH.

Extended double zepp V Series antennas consist of two stacked .64 wave vertical sections in phase. Two sets of 1/4 wave radials decouple the antenna from the mast and feed line so all RF goes into the antenna and is not radiated by the coax. The feed line connects through the lower section to the center matching coil. This not only provides weather protection for the connector (SO-239 connectors for V2, V3. Type N connector for V4) but also places the entire antenna at dc ground to reduce lightning hazard and QRN.

V Series antennas are easily assembled in one hour or less. Rugged and maintenance free, they're made of seamless, corrosion resistant 6063-T832 aluminum and all critical hardware is of passivated stainless steel. They'll withstand winds of 100 mph (160 km/h). V models accept mast diameters up to 2" (50 mm) so you can readily mount a V above your HF antenna.

Since a Hy-Gain V Series antenna costs only a fraction of a re-tuned landmobile antenna, you can now realize the *full* potential of your communications with the repeater or your home station, economically.

 For unbiased information ask any of several thousand V2 users or read the product review in QST May '82 or Amateur Radio Profiles Vol. 2, No. 3.



V Series antennas cover the entire band with VSWR below 1.5:1. Broadband characteristics insure optimum repeater performance on both input and output frequencies.

\*Effective Radiated Power

# TELEX hy-gain

TELEX COMMUNICATIONS, INC.

9600 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A.  
Europe: Le Bonaparte - Office 711, Centre Affaires Paris-Nord, 93153 Le Blanc-Mesnil, France

# Super Loaded Or "Basic" Repeater / Link Systems - Spectrum's

**new**

**Get Both!**

VHF/UHF  
LINK/CONTROL  
RCVR.


COMMERCIAL VHF/UHF  
TRANSCEIVERS



**NEW SCR77**

SCR1000/4000 & XCVRS. F.C.C.  
TYPE ACCEPTED FOR COMMERCIAL SERVICES.

Shown in  
Optional Cabinet

 

Spectrum now makes 2 lines of Repeaters—the world famous 'Super Deluxe' SCR1000/4000, and our new Low Cost line of SCR77 Repeaters/Link Transceivers.

The New SCR77 10-30 Wt. Repeaters maintain the quality of design, components and construction which have made Spectrum gear famous throughout the world for years. However, all of the "bells & whistles" which you may not need or want have been eliminated—at a large cost savings to you! The SCR77 is a real "workhorse" machine designed for those who want excellent, superior performance year after year—but no frills! ('PL', 12 Pole IF Filter, Front End Preselector, and a 30 Wt. Transmitter are the only 'built-in' options available; but Autopatch, Remote Control, and other equipment can be connected via the rear panel jacks.)

Of course, if you do want a full featured/Super Deluxe Repeater, with higher power (30-75 Wts.), and a full list of 'built-in' options, then you want our SCR1000 or 4000—'The Lifetime in Repeaters'. Available with: Full Autopatch/Reverse Patch/Land Line Control; Touch Tone Control of various repeater functions; 'PL'; "Emergency Par. ID"; various Tone & Timer Units, etc. Rack mount Link Receivers & Xmitters also available.

Call or write today for data sheets & prices! Sold Factory Direct or through Export Sales Reps only. Get your order in A.S.A.P.!

NOW LOCATED IN OUR NEW LARGER PLANT!  
THANKS FOR YOUR 8+ YEARS OF SUPPORT!




**SPECTRUM**  
Export Orders Welcomed

1055 W. GERMANTOWN PK., DEPT S3

# Spec Comm Repeater Boards & Sub-assemblies

These are Professional "Commercial Grade" Units—Designed for Extreme Environments ( - 30 to + 60° C).  
All equipment assembled & tested. For 2M, 220 MHz & 450 MHz!

## SCR200 & SCR 450 BOARD

 

10M ALSO AVAILABLE

**new**

### SCR200 VHF Receiver Board

- **Totally New Advanced Design!**
- 8 Pole Front End Filtr. + wide dynamic range—reduces overload, spurious Resp. & IMs!
- Sens. 0.3 uV/12dB SINAD typ.
- Sel. -6dB @ ± 6.5 KHz. -130dB @ ± 30KHz. (8 Pole Crystal + 4 Pole Ceramic Filtrs.
- 'S Meter,' Discriminator & Deviation Mtr. Outputs!
- Exc. audio quality! Fast squelch! w/0.0005% Crystal. ("Super Sharp" IF Filtr. also avail.)

### SCR200 Receiver Assembly

- SCR200 mounted in shielded housing
- Completely asmbld & tested, w/F.T. caps, SO239 conn.
- As used in the SCR1000. Ready to drop into your system! *High Recommended!*
- Also available in 19" Rack Mount SCR450 UHF Receiver Bd. or Assy.
- Similar to SCR200, except 420-470MHz



### SCAP Autopatch Board

- Provides all basic autopatch functions
- Secure 3 Digit Access, 1 Aux On-Off function, Audio AGC, Built-in timers, etc. Beautiful Audio!
- O/I Inhibit bd. also available
- Write/call for details and a data sheet

### RPCM Board

- Used w/SCAP board to provide "Reverse Patch" and Land/Line Control of Repeater
- Includes land line answering circuitry

### Lightning Arrester For SCAP

- Gas Discharge Tube shunts phone line surges to ground
- Handles up to 20,000 Amps!
- The Best device available to protect Autopatch equipment from lightning damage. \$14.00 + S/H.

**new**



FL-6

### FL-6 Rcvr. Front-End Preselector

- 6 Hi Q Resonators with Lo-Noise Transistor Amp (2M or 220 MHz).
- Provides tremendous rejection of "out-of-band" signals w/out the usual loss! Can often be used instead of large expensive cavity filters
- Extremely helpful at sites with many nearby VHF transmitters to "filter-out" these "out-of-band" signals

### CTC100 Rptr. COR Timer/Control Bd.

- Complete solid state control for rptr. COR, "Hang" Timer, "Time-Out" Timer, TX Shutdown/Reset, etc.
- Includes Inputs & Outputs for panel controls & lamps

### Repeater Tone & Control Bds.—For SCR1000/4000 & CTC100/ID250 only

#### TRA-1 "Courtesy Tone Beeper" Board

- Puts out a tone beep apx. 1 sec. after RX sig drops—thus allowing time for breakers
- Resets T.O. Timer after "beep"

#### TMR-1 "Kerchunker Killer" or "Time Out Warning Tone" Bd.

- For One of above 2 functions
- "Kerchunker Killer" provides adj. delay (0-10 sec.) for initial rptr. access. Auto-Reset at end of QSO.
- T.O. Warning Tone provides alerting "warble tone" apx. 10 sec. before "time out."

**new**

### PSM-1 Repeater Power Supply Mod Kit

- For SCR-1000 or SCR-4000
- Replaces Darlington Pass Tr.—for improved reliability
- Includes new overvoltage "Crowbar" shutdown circuit
- Complete kit, w/assembled PC board. \$19.50 + \$3.50 shipping/handling

### PRM200 Power Supply Filter Cap/Regulator/Metering Board

- As used in the SCR1000 as main part of 13.8VDC/8A Pwr. Sply.
- Includes 14,000 µF Filter Cap, Reg. IC and Driver Trans., V/I Meter shunts and cal pots.
- Requires Xfmr., Br. Rect., Pass Tr./Heat Sink, (Optional Meter), for complete supply.



10M ALSO AVAILABLE

SCT410 XMTR. ASSY.

### SCT110 VHF Xmtr/Exciter Board

- 10 Wts Output 100% Duty Cycle!
- Infinite VSWR proof.
- True FM for exc. audio quality
- Designed specifically for continuous rptr service. Very low in "white noise"
- Spurious 70 dB. Harmonics 60 dB
- With .0005% xtal.
- BA-10 30 Wt. Amp board & Heat Sink, 3 sec. L.P. Filter & rel. pwr. sensor. BA75 75 Wt. unit also available.

### SCT110 Transmitter Assembly

- SCT110 mounted in shielded housing.
- Same as used on SCR1000.
- Completely asmbld. w/F.T. caps, SO239 conn.
- 10, 30, or 75 Wt. unit.

### SCT 410A UHF Transmitter Bd. or Assy.

- Similar to SCT110. 10 Wts. nom.
- Now Includes "on board" proportional Xtal Osc./Oven circuitry for very high stability!
- BA-40 40W. UHF AMP. BD. & HEAT SINK.

### PCB-1 Xmtr. Power Control Board

- For SCT110 or SCT410 Exciters
- Varies B+ to control Pwr. Out
- Switchable Hi, Low, or Med. Pwr. out, locally or remotely. Adj. levels.

### TTC100 Touchtone

### Control Board



Interface to any Radio or AF system!

- 3 digit ON, 3 digit OFF control of a single repeater function, or (optional) 2 functions (2 digits ON/OFF each).
- Can be used to pull in a relay, trigger logic, etc.
- Typically used for Rptr., ON/OFF, HI/LO Pwr PL ON/OFF, Patch Inhibit/Reset, etc.
- Stable anti-falsing design 5s limit on access
- For add'l function(s), add a "Partial TTC" board

# COMMUNICATIONS CORP.

INQUIRE ABOUT 'SURPLUS' RX & TX BOARDS. REDUCED PRICE! ✓68

Norristown, PA 19401 • (215) 631-1710

Call, or Send for Data Sheets!

# Uncover Equipment for OSCAR Phase III

*Lurking in flea markets and junk boxes is everything you need to work OSCAR.*

*K6KLY tells you what to look for and how to make it work.*

R. Bentson K6KLY  
3432 Lodge Drive  
Belmont CA 94002

**T**his article is for the amateur who wants to get on OSCAR Phase III inexpensively. This can be done by converting a surplus GE UHF transmitter strip to a 435-MHz SSB mixer.

With the upcoming launch of OSCAR Phase III, I was looking for a way to get on the 435-MHz input inexpensively when I found some old GE Progress-line UHF transmitter strips at a ham flea market. I asked a friend who had a GE data file to send me a copy of the schematic, which he did.

After reviewing all the material he sent me, I found

that I had a 450-to-470-MHz transmitter, model 4ET24A2. It could be modified to be a mixer for 435 MHz, but it would be upconverting in frequency with the local oscillator frequency on the high side of the wanted output-signal frequency. Thus, the sideband signal would be inverted and when I wanted to change frequency in an upward direction on 435

MHz, I would have to go down in frequency with the 28-MHz exciter.

This was too confusing to try to handle while tracking a satellite, so I looked further and found in the data my friend sent me a schematic on a unit, model 4ET24A1 or A11, which covered 406 to 420 MHz. This was perfect. When you want 435 out and you are putting 28 MHz into a mixer, you need a 407-MHz local oscillator to make the mixer work correctly. This 4ET24A1 was in the right frequency range. I started looking around at the swap meets and asking my friends who were into old FM equipment to keep an eye out for this model for me. I found out later that GE did not make too many of these A1-type strips as compared with the A2-type strips. I finally found a 4ET24A1 strip at an FM-equipment auction and paid \$20 for it, complete with all the tubes.

After cleaning the dirt off the unit and making sure it had not been modified or robbed for parts, I started the conversion. My first task was to order a crystal from the ICM crystal company in

 


Photo A. Overall view. Notice orientation of the crystal oven.

Oklahoma City. Since we need a 407-MHz local oscillator and the transmitter strip has a multiplier of 36, the crystal frequency needed is 11.3055 MHz. When ordering the crystal, tell ICM that the crystal is for a GE model 4ET24A1. If your strip has a crystal oven or if you can get a GE crystal oven, tell ICM that the crystal will be used in a GE oven.

### Modification

The modification of the transmitter strip is very easy. First, remove the cover over the three large tubes in the caged-in area. This is done by removing one screw next to the MULT-4 test point (see Photo A). Next, pull off the cover, starting with the end over the 2E26. The far end of the cover fits under a notch in the output filter. Then, find C171, the PA grid-tuning capacitor of the last tube, a 6907. Drill a 3/16" hole in the plate that C171 is mounted on, halfway between C171 and the edge of the plate closest to the red test point, PA CATH (see Photo A). Next, using a small pair of wire cutters, cut off the capacitor and wire going to pin 4 of the 6907 tube. Pin 4 is right under C171.

Prepare a three-foot length of RG-58-type coax by stripping off 2 inches of the outside rubber jacket, followed by one and one half inches of the coax braid. Next, remove 1/4 inch of the inner insulation from one end of the coax. Prepare the other end of the coax to accept a PL-259 coax fitting with the adapter ring for the RG-58 coax. Push the center conductor of the coax through the 3/16" hole in the plate and then wrap and solder the center conductor to pin 4 of the 6907 tube under C171. Push the coax braid down around the 3/16" hole and solder the braid to the plate.

Find the cover and, using a reamer or a set of drill bits, enlarge the vent hole in the cover that is closest to being

right over where the 3/16-inch hole is in the plate when the cover is replaced. Enlarge this hole to about 1/4 inch, which is big enough to allow the coax to pass through it. Feed the coax through the hole and replace the cover on the cage.

Solder a PL-259 with the adapter to the end of the coax cable you prepared earlier. Find a 28-MHz rf choke coil such as a Miller RFC28 or Ohmite Z28. Solder this rf choke inside another PL-259 coax fitting. One end of the rf choke goes to the center pin of the PL-259 and the other end goes to the outside rear edge of the PL-259. Using a UHF coax T-fitting, connect the new cable from the mixer unit and the coax fitting with the rf choke inside it to the T-fitting. Later, the coax from the 28-MHz exciter will connect here also.

**Caution:** The rf choke must be connected or damage could result to your exciter. Check the rf choke with a VOM to be sure it is good, after soldering to the PL-259.

Locate the socket the crystal oven plugs into and cut off the ground wires going to pin 5. If there are any other wires going to pin 5, cut them off pin 5 also and solder them to ground points. Next, remove V108, a 12AU7/6680 tube. It will not be used. If any other tubes are missing, replace them per the following list:

V101	6BH6/6661
V102	6U8
V103	6CL6
V104	2E26
V105, 106	6907/6252
V107	12AU7/6680

Install the crystal in the GE oven between pins 4 and 8; then plug the GE oven into the 8-pin socket on the mixer. If an oven is not used, plug the crystal into pins 4 and 6 on the 8-pin socket.

### Power Supply

Power supply connections are as follows:

 


Photo B. The coax from the 28-MHz exciter is soldered to pin 4 of the last 6907 tube right under the variable capacitor, C171.

- Pins 1 and 2 are not used. Audio input for FM.
- Pin 3 to ground. Oscillator-select channel 1 on A11 model.
- Pin 4 is not used. Oscillator-select channel 2 on A11 model.
- Pin 5 to +6 volts dc keyed on transmit, if antenna relay is used.
- Pin 6 to 6 volts ac or dc filament supply (not used if 12-volt filament supply is used).
- Pin 7 to ground (filament-return lead for 6-volt filament). (To 12 volts ac or dc if 12-volt filament supply is used.)
- Pin 8 bias supply, -22 volts dc, adjustable.
- Pin 9 B+ final, 450 volts dc, keyed on transmit.
- Pin 10 B+ multiplier, 300 volts dc, keyed on transmit.
- Pin 11 B+ oscillator, 200 volts dc.

This transmitter strip is normally used with a GE model 4EP4A power supply. This is the same supply that is used on GE Progress-line repeater stations. Since many older 2-meter and 440-MHz repeaters are going to solid-state equipment, some of these power supplies are showing up at auctions and flea markets now. The 4EP4A power supply is selling for about \$30 to \$40 in working condition. See the photos of the complet-

ed mixer mounted on the power supply to help you recognize the power supply at the flea markets.

When using the 4EP4A power supply, the bias-supply section will need to be modified to a voltage-multiplier-type power supply in order to get the required -22-volts-dc bias. See the *ARRL Handbook* under power supplies for circuits. This requires only the addition of two capacitors and two diodes.

Here are the terminal-strip connections on the 4EP4A power supply:

- Terminals 1, 2, and 4: not used. Audio lines.
- Terminal 3: key to ground on transmit PTT line.
- Terminal 5: 250 volts dc "caution."
- Terminal 6: to ground channel A select on model A11.
- Terminal 7: ground.
- Terminal 8: 6.3 ac filament line.
- Terminal 9: one side of 110-V-ac input.
- Terminals 10 and 11: other side of 110-V-ac input.
- Terminal 12: not used. Channel B select on model A11.
- Terminal 13: not used. Transmit light line.
- Terminal 14: not used. Rec mute line.
- Terminals 15 and 16: not used. Spares.

 


Fig. 1. Schematic.

If you have a model A1 unit and want to modify it to be an A11-type unit so you can switch between 432 and 435 MHz at the flip of a switch, send me an SASE for a schematic.

Install a 10-Ohm, 2-Watt resistor in another PL-259. This will replace the PL-259 with the rf choke for the bias setting in the alignment procedure only.

#### Alignment

Replace the PL-259 with the rf choke in it with the PL-259 with the 10-Ohm resistor in it on the T-fitting. Connect a voltmeter (2.5-volt scale) to where the exciter

should connect on the T-fitting. Turn on the power supply and, after a few minutes warm-up, turn on the B+ voltages. Adjust the bias supply until you just start to get a reading on the voltmeter. This indicates that the mixer tube is just starting to draw cathode current. Remove the B+ voltages and replace the PL-259 with the rf choke in it. Do not connect the exciter yet. Turn the variable resistor on the side of the cage to fully counterclockwise.

**Caution:** Do not key the transmitter for more than 30 seconds at a time during the entire alignment procedure.

Connect the negative

lead of the voltmeter to the MULT-1 test point and the positive lead to ground. Key the B+ voltage and you should see a reading of about 1 volt. This shows the oscillator is working. Move the negative lead to the MULT-2 test point and adjust the two transformers between the 6U8 and 6CL6 tubes for maximum voltage on the voltmeter (approximately .75 volts).

Move the negative lead to the MULT-3 test point and adjust the two transformers between the 6CL6 tube and the end of the transmitter voltage (approximately 1.5 volts). Move the negative

lead to the MULT-4 test point on the top of the cage next to the 2E26 tube. Using a nonconductive screwdriver, adjust C126, the 2E26 plate-tuning capacitor, for maximum voltage on the meter (approximately 2 volts).

Move the negative lead to the test point marked PA GRID. This is near where the new coax cable is coming out of the cage and the test point is green in color. Using a nonconductive screwdriver, adjust C129, the plate-tuning capacitor of the first 6907 tube, for maximum voltage by putting the screwdriver through the hole in the cage cover and down about an inch to engage the plate-tuning capacitor. This is a very sensitive adjustment. With the negative lead in the same place, adjust C171, the grid-tuning capacitor of the mixer tube, for maximum voltage on the meter. C171 is the capacitor right next to where the new coax cable comes out of the cage cover. You should repeak C129 again.

Connect a load to the output of the transmitter and connect the exciter to the coax T-fitting. You may want to connect a good UHF wattmeter between the transmitter and the load. I suggest a Bird wattmeter with a 25-Watt 200-500-MHz element. Connect the voltmeter with the negative lead going to ground and the positive lead going to the test point marked RF at the end of the cage area. Remember, do not key the transmitter for more than 30 seconds at a time in CW mode or you could burn out R132, a 6.8k 1/2-W resistor connected to the screen pin of the mixer tube.

Apply about 10 Watts of 28-MHz energy from your exciter and turn the B+ voltages on. Tune C172, the mixer-tube plate-tuning capacitor, for maximum voltage on the meter. Be sure you use a nonconductive screwdriver and place it down through

# RECEIVE WEATHER CHARTS IN YOUR HOME!



## You can DX and receive weather charts from around the world.

Tune in on free, worldwide government weather services. Some transmitting sites even send weather satellite cloud cover pictures!

## You've heard those curious facsimile sounds while tuning through the bands — now capture these signals on paper!

Assemble ALDEN's new radiofacsimile Weather Chart Recorder Kit, hook it up to a stable HF general-coverage receiver, and you're on your way to enjoying a new hobby activity with many practical applications. Amateurs, pilots, and educators can now receive the same graphic printouts of high-quality, detailed weather charts and oceanographic data used by commercial and government personnel.

## Easy to assemble — Backed by the ALDEN name.

For over 40 years, ALDEN has led the way in the design and manufacture of the finest weather facsimile recording systems delivered to customers worldwide. This recorder kit includes pre-assembled and tested circuit boards and mechanical assemblies. All fit together in a durable, attractive case that adds the finishing professional touch.

## Buy in kit form and save \$1,000!

You do the final assembly. You save \$1,000. Complete, easy-to-follow illustrated instructions for assembly, checkout, and operation. And ALDEN backs these kits with a one-year limited warranty on all parts.

## Easy to order.

Only \$995 for the complete ALDEN Weather Chart Recorder Kit. To order, fill out and mail the coupon below. For cash orders enclose a check or money order for \$995. Add \$5 for shipping and handling in the U.S. and Canada (for Massachusetts delivery, add \$49.75 sales tax). To use your MasterCard or Visa by phone, call (617) 366-8851.

## ALDEN ELECTRONICS

Washington Street, Westborough, MA 01581 216

NAME:	_____
CALLSIGN:	_____
ADDRESS:	_____
CITY:	STATE: ZIP:
<input type="checkbox"/> I've enclosed a check or money order for \$995.00 and \$5.00 for shipping and handling, plus applicable sales tax.	
<input type="checkbox"/> Charge to: <input type="checkbox"/> MasterCard  <input type="checkbox"/> Visa 	
ACCOUNT # (ALL DIGITS)	
<input type="text"/>	
EXPIRATION DATE	
<input type="text"/> <input type="text"/> - <input type="text"/> <input type="text"/>	
SIGNATURE REQUIRED IF USING CREDIT CARD _____	


## CONTROL IN BASIC

FOR \$169.95

### No Need For

- Assembly Language
- Development Station
- Expensive Test Gear

... Just a Terminal

 

### THE JARR Z8 BSC CONTROLLER

#### INCLUDES:

- \*Tiny Basic Monitor
- \*Timer/Event Counter
- \*4K User Eprom or Ram
- \*Over 200 Pages of Documentation
- \*RS-232 Serial Line
- \*14 Parallel I/O Lines
- \*Expandability!

#### FOR INTERFACING TO:

- \*Sensors
- \*Displays
- \*Keyboards
- \*SCR's
- \*Triacs
- \*Relays
- \*Switches
- \*A/D & D/A

#### APPLICATIONS:

- \*Heating Control
- \*Home Security
- \*Lighting Control
- \*Speech Synthesis
- \*Programmable Rotor Controller
- \*RTTY / CW Control
- \*Home Automation

With the Jarr Z8 Controller, 1000's of dedicated microprocessor control applications can be realized.

#### Development of a control program is easy!

By utilizing simple BASIC commands, create a program to accomplish your specific task. When your program does what you want, simply download from RAM to EPROM. From, then on, whenever the Z8 controller powers up it will automatically execute your control program.

#### JARR Z8 Controller Peripherals:

- \*Eprom Programmer/Cassette Interface (Model # Z8-ECI)
- \*24 Line Parallel I/O Card (Model # Z8-PIO)
- \*8 Channel Relay Control Card (Model # Z8-RCC)
- \*2 Channel Temperature Sensing Card (Model # Z8-TSC)
- \*Breadboard Interface Card (Model # Z8-BIC)
- \*Speech Synthesizer Card (Model # Z8-SSC)

Call, Write or Circle reader service number for detailed information on the JARR Z8 Control Family.

## JARR CORPORATION

"We Make Control Easy"

9127 Benavides SW  
Albuquerque, N.M. 87105  
(505) 831-0221 ✓209

the hole in the cover of the cage to engage with C172. This is a very sensitive adjustment. Adjust the two controls on the output filter at the end of the cage area, by the antenna relay, for maximum voltage on the voltmeter or maximum output on the wattmeter. Go back and readjust C172 again for maximum output. I suggest that you take the output power right from the filter output connector without going through the antenna relay. You should go back and adjust C171 (PA GRID) again for maximum output.

Turn R135, the variable resistor on the side of the cage, fully clockwise again. Increase the 28-MHz input power up to 20 to 25 Watts and you should get between 8 and 12 Watts out of the mixer at 435 MHz. This completes the alignment procedure.

#### Operation

You may connect the mixer directly to the antenna or run the output of the mixer into an amplifier. I have used this mixer on 432 MHz with a 4CX250B amplifier to win many ARRL VHF contests in the Pacific Division. I have also used its predecessor, the A2 version of the transmitter strip, to make over 500 contacts on OSCAR 7, mode B.

As you can see, this is an inexpensive way to get a 435-MHz SSB signal on the air to input OSCAR Phase III. If you would like to use this same unit on 432 SSB, substitute a crystal with a frequency of 11.2222 MHz and follow the same alignment procedure as before. I hope this article will help many more stations get on OSCAR that would not have because of the high cost of new equipment. ■

## AT LAST!

This service will be available nationally. Lab tested & time proven modifications professionally installed in your amateur Handy-Talkie 2M, 220, 440, MH2 transceiver by Henry Radios warranty technicians (KNOWN AS "A&W PRODUCTIONS")



#### HAVE ALL PL TONES AVAILABLE AT YOUR FINGER TIPS

Outboard the dip switch! Have it neatly inlaid into the back cover of your Handy-Talkie making all 32 PL Tones Selectable at a moment's notice.

**\$25** Got your own PL? Send it to us with your Handy-Talkie unit and we do the professional installation for you.

**\$55** We will install a new PL and inlay the dip switch into the back cover of your Handy-Talkie ready to operate.

Send us your Handy-Talkie unit and a check or money order plus \$3.50 for shipping and handling payable to A&W PRODUCTIONS, INC.

For **TEMPO** units the dip switch is inlaid into the Push-to-Talk bar. The **TEMPO S-15** will have the dip switch inlaid into the back cover.

**\$45** We will install a **NEW BATTERY BEATER** in your **TEMPO S-1, S-2, S-4, S-5** READY to operate. Your New Battery Beater will use the same jack as the charger with no new holes and regulation circuits built into unit. Comes with Cigar Lighter Adapter with internal fuse.

**CONTACT A&W PRODUCTIONS FOR SPECIAL MODIFICATIONS YOU MAY WANT TO HAVE DONE. WE SPECIALIZE IN THE TEMPO HANDY-TALKIES.**

WE ARE AN OFFICIAL "TEMPO" REPAIR STATION  
ALL WORK GUARANTEED FOR 30 DAYS. SEND YOUR HANDY-TALKIE AND A CHECK OR MONEY ORDER TO:

**A&W PRODUCTIONS**  
3305 Pico Blvd., Santa Monica  
California 90405 (213) 828-9310

✓164



# ICOM

# - Check the Big Savings at AES!



**HF Transceivers:**

IC-720A 9-band Xcvr/1.30 MHz Rcvr	Regular SALE	\$1349.00 1099
FL-32 500 Hz CW filter		59.50
FL-34 5.2 KHz AM filter		49.50
MB-5 Mobile mount		19.50

**IC-740 • \$50 REBATE**  
**Low AES Price + \$\$ back from ICOM**  
*Hurry! - offer ends March 31st, 1983*



IC-740 9-band 200w PEP Xcvr	Regular SALE	\$1099.00 949 <sup>95</sup>
EX-238 Internal power supply		159.00 149 <sup>95</sup>
EX-241 Marker unit		20.00
EX-242 FM unit		39.00
EX-243 Electronic keyer unit		50.00
FL-44 455 KHz SSB filter		159.00 129 <sup>95</sup>
FL-45 9 MHz 500 Hz CW filter		59.50
FL-54 9 MHz 270 Hz CW filter		47.50
FL-52 455 KHz 500 Hz CW filter		96.50 89 <sup>95</sup>
FL-53 455 KHz 250 Hz CW filter		96.50 89 <sup>95</sup>
EX-254 Mobile mount		TBA
HM-10 Mobile scan microphone		39.50

IC-730 8-band 200w PEP Xcvr w/mic	Regular SALE	\$829.00 649 <sup>95</sup>
FL-30 SSB filter (passband tuning)		59.50
FL-44 455 KHz SSB filter		159.00 129 <sup>95</sup>
FL-45 500 Hz CW filter		59.50
EX-195 Marker unit		39.00
EX-202 LDA interface; 730/2KL/AH-1		27.50
EX-203 150 Hz CW audio filter		39.00
EX-205 Transverter switching unit		29.00
HM-10 Mobile scan microphone		39.50

**Common accessories - 720/740/730**

PS-15 External 20A power supply	Regular SALE	\$149.00 134 <sup>95</sup>
EX-144 Adaptor; CF-1/PS-15		6.50
CF-1 Cooling fan for PS-15		45.00
PS-20 20A switching ps w/speaker		229.00 199 <sup>95</sup>
CC-1 Adaptor; HF radio to PS-20		10.00
CF-1 Cooling fan for PS-20		45.00
SM-5 8-pin electret desk mic		39.00
SP-3 External speaker		49.50
Speaker/phone patch (specify radio)		139.00 129 <sup>95</sup>
AT-100 100w 8-band automatic ant tuner		349.00 314 <sup>95</sup>
AT-500 500w 9-band automatic ant tuner		449.00 399 <sup>95</sup>
AH-1 5-band mobile ant w/tuner		289.00 259 <sup>95</sup>

**HF Linear Amplifier**

IC-2KL 160-15m/WARC solid state linear	Regular SALE	1795.00 1299
--	--------------	--------------



**VHF/UHF Multi-modes:**

IC-251A 2m FM/SSB/CW Xcvr/AC ps	Regular SALE	\$749.00 599 <sup>95</sup>
IC-551D 80w 6m Xcvr		699.00 599 <sup>95</sup>
PS-20 20A switching ps/spkr		229.00 199 <sup>95</sup>
CF-1 Cooling fan for PS-20		45.00
EX-106 FM adaptor		125.00 112 <sup>95</sup>
IC-451A 430-440 SSB/FM/CW Xcvr/ps		899.00 769 <sup>95</sup>
IC-451A/High440-450 MHz Xcvr/ps		899.00 769 <sup>95</sup>
AG-1 15 db preamp for IC-451A		89.00 79 <sup>95</sup>
IC-290H 25w 2m SSB/FM Xcvr, TTP mic		549.00 489 <sup>95</sup>
IC-560 10w 6m SSB/FM/CW Xcvr		489.00 439 <sup>95</sup>
IC-490A 10w 430-440 SSB/FM/CW Xcvr		649.00 579 <sup>95</sup>

**VHF/UHF FM:**

IC-25A Compact 25w 2m Xcvr/TTP mic	Regular SALE	\$349.00 299 <sup>95</sup>
IC-45A 10w 440 FM, TTP mic		399.00 359 <sup>95</sup>
EX-270 CTCSS encoder for IC-45A		TBA
IC-22U 10w 2m FM non-digital Xcvr		\$299.00 249 <sup>95</sup>
EX-199 Remote frequency selector		35.00

**VHF/UHF Portables:**

IC-202S 2m port. SSB Xcvr, 3w PEP	Regular SALE	\$279.00 249 <sup>95</sup>
IC-505 3/10w 6m port. SSB/CW Xcvr		449.00 399 <sup>95</sup>
BP-10 Internal nicad battery pack		79.50
BC-15 AC charger		12.50
EX-248 FM unit		49.50
LC-10 Leather case		34.95
IC-402 432 port. SSB Xcvr, 3w PEP		389.00 349 <sup>95</sup>

**Amplifiers for portables:**

IC-20L 2m amp, 10w PEP or FM	Regular SALE	98.00 89 <sup>95</sup>
IC-30L 432 amp, 10w PEP/FM		105.00 94 <sup>95</sup>



**Shortwave receiver:**

R-70 100kHz-30MHz digital receiver	Regular SALE	\$749.00 649 <sup>95</sup>
EX-257 FM unit		TBA
EX-261 Transceiver interface; 720A		TBA
FL-44 455 KHz SSB filter		159.00 129 <sup>95</sup>
FL-63 9 MHz 250 Hz CW filter		TBA
SP-3 External speaker		49.50
EX-254 Mobile mount		TBA

## AES STORE HOURS

Mon. thru Fri. 9-5:30; Sat. 9-3

## E-X-P-A-N-D-E-D WATS HOURS

Milwaukee WATS line 1-800-558-0411 answered evenings until 8:00 pm, Monday thru Thursday.

Please use WATS line for Placing Orders. For other information, etc. please use Regular line.



## ICOM Handhelds

The Transceivers. The IC-2A features full coverage of the 2 meter ham band. The IC-3A covers 220 to 224.99 Mhz, and the IC-4A, 440 to 449.995 Mhz. Each comes with BP-3 rechargeable battery, AC wall charger, flex antenna, earphone, wrist strap, and belt clip. Accessories are interchangeable. Slide on, removable battery pack allows quick change and may be charged while removed from transceiver.

**2 meters:**

IC-2A .15/1.5w 2m HT/batt/wall cgr	Regular SALE	\$239.50 214 <sup>95</sup>
IC-2AT .15/1.5w 2m HT/batt/cgr/TTP		269.50 219 <sup>95</sup>

**220 MHz:**

IC-220 HT/batt/wall cgr		269.95 229 <sup>95</sup>
IC-3AT .15/1.5w 220 HT/batt/cgr/TTP		299.95 239 <sup>95</sup>

**440 MHz:**

IC-4A .15/1.5w 440 HT/batt/wall cgr		269.95 229 <sup>95</sup>
IC-4AT .15/1.5w 440 HT/batt/cgr/TTP		299.95 239 <sup>95</sup>

### Hand-held Accessories:

BC-25U Extra 15-hour wall charger	Regular	\$10 <sup>00</sup>
BC-30 1/15-hour drop-in charger for BP-2/3/5		69 <sup>00</sup>
BP-2* 450 ma, 7.2v 1w extended time battery		39 <sup>50</sup>
BP-3 Extra standard 250ma 8.4v 1.5w battery		29 <sup>50</sup>
BP-4 Alkaline battery case		12 <sup>50</sup>
BP-5* 450 ma, 10.8v 2.3w high power battery		49 <sup>50</sup>

\*BC-30 required to charge BP-2 & BP-5

FA-2 Extra 2m flexible antenna		10 <sup>00</sup>
CA-2 Telescoping 1/4-wave 2m antenna		10 <sup>00</sup>
CA-5 3/8-wave telescoping 2m antenna		18 <sup>95</sup>
CA-3 Extra 220 flexible antenna		9 <sup>12</sup>
CA-4 Extra 440 flexible antenna		9 <sup>12</sup>
CP-1 Cigarette lighter receptacle charger for BP-3		9 <sup>50</sup>
DC-1 DC operation module		17 <sup>50</sup>
HM-9 Speaker/microphone		34 <sup>50</sup>
LC-2A Leather case without TTP cutout		34 <sup>95</sup>
LC-2AT Leather case with TTP cutout		34 <sup>95</sup>
ML-1 2m 2.3/10w HT amplifier (Reg. \$89)	SALE	79 <sup>95</sup>

**Marine band:**

IC-M12 12 ch Marine hand-held	SPECIAL	\$199 <sup>95</sup>
-------------------------------	---------	---------------------

### Misc. accessories:

24-PP 24-pin accessory plug	Regular	\$ 4 <sup>00</sup>
BC-10A Memory back-up; 551/720/730/740		8 <sup>50</sup>
BC-20 Nicads & DC-DC charger for portables		57 <sup>50</sup>
BU-1 Memory back-up; 25A/290A/490A		38 <sup>75</sup>
EX-2 Relay box w/marker; 720A/730/701		34 <sup>00</sup>
HM-3 Deluxe mobile microphone (specify radio)		17 <sup>50</sup>
HM-5 Noise canx mobile microphone, 4 pin		34 <sup>50</sup>
HM-7 Amplified mobile microphone, 8 pin		29 <sup>00</sup>
HM-8 Touch-tone mic; 255A/260A, 8 pin		49 <sup>95</sup>
HM-10 Scan mic; 255A/260A/290A/25A		39 <sup>50</sup>
HP-1 Headphones		34 <sup>50</sup>
IC-3PS Power supply for ports. (Reg. \$95)	SALE	89 <sup>95</sup>
SM-2 4-pin electret desk microphone; 551D		39 <sup>00</sup>
SM-5 pin electret desk mic.; 251A/451A		39 <sup>00</sup>
SP-4 Remote speaker for portables		24 <sup>95</sup>

Speaker/phone patch, specify (Reg. \$139)... SALE 129<sup>95</sup>



## Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

# AMATEUR ELECTRONIC SUPPLY Inc.

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

## AES BRANCH STORES

**WICKLIFFE, Ohio 44092**  
 28940 Euclid Avenue  
 Phone (216) 585-7388  
 Ohio WATS 1-800-362-0290

**ORLANDO, Fla. 32803**  
 621 Commonwealth Ave.  
 Phone (305) 894-3238  
 Fla. WATS 1-800-432-9424

**CLEARWATER, Fla. 33575**  
 1898 Drew Street  
 Phone (813) 461-4267  
 No In-State WATS

**LAS VEGAS, Nev. 89106**  
 1072 N. Rancho Drive  
 Phone (702) 647-3114  
 No In-State WATS

## Associate Store

**CHICAGO, Illinois 60630**  
 ERICKSON COMMUNICATIONS  
 5456 N. Milwaukee Avenue  
 Phone (312) 631-5181

Outside Ohio 1-800-321-3594


Outside Florida 1-800-327-1917

No Nationwide WATS

Outside Nevada 1-800-634-6227

Outside Illinois 1-800-621-5802

# Now you can chirp back!

 

Been wondering what those "chirp-chirp" signals were around 14075? They're AMTOR, AMateur Teleprinting Over Radio. European hams have been enjoying the benefits of error free RTTY for sometime. (It's a must for commercial Maritime traffic.) Now, U.S. Amateurs are on the threshold of a new era of RTTY.

Old problems of QRM, QRN, & QSB are gone! If a propagation path exists, AMTOR will get the message thru — with no "hits" — "newspaper" perfect copy!

Two modes are available; AMTOR mode A transmits a three character block specially coded so that the receiving station can re-

cognize an error. The three character block is repeated until the receiving station confirms reception by replying with the proper control code signal. Flawless print is possible with this "hand-shake" style operation.

Mode B, "FEC" or Forward Error Correction, is actually a time diversity mode where text is repeated and inter-mixed in the transmission. The receiving station unscrambles it and prints the clear text. This "broadcast" mode allows more than two stations to communicate. It's more effective than conventional Baudot or ASCII, but not as reliable as AMTOR mode A.

The actual DATA transfer in either AMTOR mode is

nominally equivalent to conventional RTTY at 50 baud, or 66 WPM.

A receive only "Listen" mode is also available for reception of mode A data by a station not directly involved in the "hand-shake" communication.

Start with a new AMTOR ACT-1, ATR-6800, or update your present system.

Microlog is ready with AMTOR! Give us a "chirp" at Microlog Corporation, 18713 Mooney Drive, Gaithersburg, MD 20879. TEL (301) 258-8400. TELEX 908153

**MICROLOG**  
INNOVATORS IN DIGITAL COMMUNICATION

# AMTOR, WHAT IS IT?

**AMTOR, AMateur Teleprinting Over Radio will change the way you communicate. AMTOR is both a code and a method. This radically different RTTY system can provide virtually error-free copy under conditions that you wouldn't even attempt with conventional Baudot or ASCII. It is, in fact, the most well thought-out communication code since Sam Morse pounded brass. Every facet is designed to overcome the real-world problems of fading, noise and interference.**

## THE METHOD:

There are two variations, namely modes A & B (clever names eh?). In describing mode A, imagine the time wasted with lengthy repeats of whole messages just to correct a few errors, or the uncertainty of whether your traffic got through. How many times has one of your long dissertations been lost when the band folds? AMTOR mode A shortens each "message" to only three characters. The sending station (Tx) transmits this "block" of three then goes to receive so that reception can be confirmed by the receiving station (Rx). This is accomplished by the Rx transmitting a short "control signal" back to the Tx. Upon confirmation, Tx sends the next three character block. If not confirmed, the same block is repeated again, and again until it's perfect, or the computer decides it's not possible. As you can guess, this eliminates the necessity to type out repeats such as name, call etc. Signal reports are also redundant because you

can tell by the number of repeats requested how well you're being copied! Even deep fades just slow down the traffic a bit until the signal recovers and copy resumes. All without the usual "garbage" print typical of poor conditions. A special "over" sequence reverses Rx and Tx roles.

## THE AMTOR CODE:

Your next logical question will be "How does the Rx know it got a good block or not?" The answer lies in the code itself. The AMTOR code is neither Baudot nor ASCII. On the contrary, it is a "synchronous" code without start or stop bits. (Makes the computer work a little harder!) There are seven "BITS" per character, and always a constant 3 to 4 ratio of mark / space. This fixed ratio allows the Rx to determine good or bad data. (It is possible for two bits to reverse, 0 to 1, and 1 to 0, but the probability is extremely low!) This "double parity" limits the number of combinations to 35, which is directly compatible with the current Baudot character set.

## Tx/Rx TIMING:

The continuous switching from receive to transmit makes some critical demands on the radio, because each three character block is sent in 210 MSec., (21 bits at 100 baud). The confirming control signal falls in the next 240 MSec., usually after a 10 to 20 MSec. delay for a total time of 450 MSec. (This explains the familiar "chirp-chirp" signal of about 2 per second that you hear.) The radio must fully recover from transmit to receive in less than 10 MSec. Generally, QSK rigs and most of the current crop of radios can handle it. Some might require an AGC tweak etc. A simple method is to use a separate receiver. That's the way a lot of commercial ships do it. Information on individual rigs will be made available as we go.

## PROPAGATION TIMING:

The timing requirement also limits the total distance that can be traversed due to propagation delays out and back. Simply put, "long-path" is out! But direct short path up to one-half the earth's circumference is easily accomplished within the 240 MSec. time frame.

## MODE B, FEC:

So far we've been discussing AMTOR mode A. The second, mode B, or Forward Error Correction mode is useful for bulletins or round tables. The same 7 bit synchronous code is used, but each character is transmitted twice, separated in time and inter-mixed. Hence the term "Time Diversity" is applicable. The transmission is continuous, with no hand-shake just as standard Baudot or ASCII is sent. (FEC sounds more rhythmically flowing than Baudot with its periodic start/stop bits.) The receiving stations recompile the data and display only the clear text. The same 3:4 mark/space ratio determines valid characters.

## COMPUTER TRICKS:

By definition, in mode A, an entire block of 3, 7-bit characters, or 21 synchronous bits must be received, all with the proper 3:4 ratio to be considered valid. In our system, if any characters are valid, we save them and ask for a repeat. Chances are, the missing characters will be recovered in the next block. By accumulating characters, the "thruput" (computer jargon!) is significantly increased under poor operating conditions. Also, if signals do drop out entirely, we repeat for 32 tries before we discontinue.



**MICROLOG**  
INNOVATORS IN DIGITAL COMMUNICATION

# Up and Coming: Direct-Broadcast Satellites

*Part II looks at the technical problems with communications at 12 GHz, which may be offset by the advantages.*

Timothy Daniel N8RK  
7 Peabody Drive  
Oxford OH 45056

**H**ams love a challenge. Why else would they erect 200-foot towers, endure cold mountaintops, or spend hours designing and building the ultimate receiver? The current generation of satellite television was a natural attraction for hams. Dedicated to doing more with less, electronics hobbyists took on the TVRO challenge and ended up creating a new home-entertainment industry.

Will the 1980s version of spacecasting, Direct-Broadcast Satellites (DBS), offer the same kind of opportunity that beckoned TVRO pioneers like W5KHT, W6HD, K4AWB, and N6TX? The first part of this article, in last month's 73, concluded that DBS holds a different kind of promise. The presence of large, technically-advanced companies is likely to discourage garage-style entrepreneurs. But what about the basement tinkerer? For him, DBS could be a challenge par excellence.

This is not a "how to" article. With DBS service planned to begin in the mid

to late 1980s, it would be premature to start manufacturing circuit boards. But if you have already mastered the reception of present-day 4-GHz satellite signals, then consider taking on the challenge of receiving 12-GHz signals from one of the "communications" satellites already in orbit or soon to be launched. Though no hobbyist has publicly announced such an accomplishment, an examination of the technical parameters will show that it is doable.

## Why 12 GHz?

The choice of 12 GHz for DBS is not as baffling as it may first appear. Perhaps the most important reason behind 12 GHz is the need for small, inexpensive receive antennas. Fig. 1 shows that a dish, one meter in diameter, has roughly 30 dB of gain at 4 GHz, making it far too small for catching satellite TV signals on that band. The same dish has about 40 dB of gain at 12 GHz. A dish antenna's gain at a particular frequency is proportional to the reciprocal of the wavelength squared, hence the increase of 10 dB.

A second argument for 12 GHz centers on the ability to use larger bandwidths.

DBS proponents have suggested using signals with bandwidths as wide as 400 MHz. The tenfold increase over 4-GHz signal bandwidths holds some exciting possibilities. We might be treated to high resolution video and have our choice of several different audio channels!

The technical attractions of the 12-GHz Ku-band are accompanied by some substantial drawbacks. While much of the theory that works at 4 GHz holds true at 12 GHz, actual Ku-band components require another magnitude of precision. Consider that a Ku-band signal has a freespace wavelength that is less than one inch long. At these frequencies, hardline gives way to waveguide and suitable microwave transistors, when available, cost in the hundreds rather than the tens of dollars.

## The Satellites

DBS planners have laid the groundwork for a multi-satellite network. Depending on the proposal, there will be either three or four geosynchronous spacecraft, each one beaming to a separate region of the US. The multi-satellite approach offers two advantages over

 


Fig. 1. The gain of a dish antenna depends on the frequency of operation and its efficiency. A one-meter dish has 10 dB more gain at 12 GHz than it has at 4 GHz, provided efficiency remains the same.

the current system of using a single satellite to blanket the country.

First, by concentrating the satellite's signal on a smaller area, the cost and complexity of receivers can be lessened. When the antenna-size limitation, receiver-noise performance, and the substantial path loss (approximately 205 dB) are weighed against the need for snow-free pictures, it becomes clear that the new satellites must have an effective radiated power far greater than the 30- to 35-dBW signals emanating from the 4-GHz satellite-TV birds. Ku-band DBS signals will probably exceed 50 dBW and may even approach 65 dBW. A satellite capable of covering the continental US with that kind of signal would need close to 1000 Watts of output power, severely taxing the weight and power-supply limitations for spacecraft.

How do spacecasting transmitters generate high-powered microwave signals? The answer is, very carefully. Traveling-wave tube amplifiers (TWTAs) are used, often in groups of two or more since the largest single unit can generate no more than a couple of hundred Watts. TWTAs, like amplifiers for ham radio, can fail at the worst time. The world's first direct-broadcast satellite, a Japanese experimental spacecraft, had a shortened life due to TWTA problems. The push is now on to build higher power TWTAs and improve satellite power generation and cooling systems.

A second drawback to the single-satellite approach stems from biannual eclipses where the Earth prevents the sun's rays from reaching a satellite's solar cells. The satellite must cease transmitting or rely on heavy and expensive storage batteries. Rejecting the second alternative, it may be possible to place the sat-

ellite in an orbital location that causes the blackout to occur at an hour when few people expect television service. But, as Harley Radin pointed out in the August, 1982, issue of *Satellite Communications*, such a location would be over the Pacific Ocean and impractical for east coast reception.

With the single-satellite approach presenting problems at every turn, planners have suggested a multi-satellite system where each craft would serve either one-fourth or one-third of the continental US. In arguing for the three-satellite approach, Radin questions the need to match program times with the national time zones, a feature of the four-bird proposal. Instead, he suggests that using only three satellites will reduce the overall cost (satellites are expected to cost in the \$100-million range) and make better use of the frequency spectrum and orbital space.

Should DBS become a money-maker, two additional problems may develop. First, there is a limited number of ways to launch a satellite. Companies that counted on the European Space Agency's Ariane launcher are beginning to have second thoughts, and the best alternative, the US Space Shuttle, is almost completely booked through the mid-1980s.

If a large number of satellites do end up in orbit, it could present problems on the receiving end. Dish antennas are limited to a very narrow beamwidth—about 3 degrees—and may need to be rotated to receive signals from different satellites. If motorized antennas prove too costly, an electronically-steered "flat" array could be introduced.

### Receiver Performance

The plight of satellite-receiver designers is best expressed by the old saying, "He robs Peter to pay Paul."

 


Fig. 2. The NHK Corporation of Japan receiver, described in the January/February, 1982, issue of *High Technology*, uses direct conversion for low cost and a reasonably good noise figure.

The tradeoff is between receiver-noise performance and antenna size. It boils down to getting acceptable performance at a reasonable cost. Acceptable performance is usually equated with a carrier-to-noise ratio (C/N) of at least 10 dB. While 10-dB C/N may not be studio quality, it does ensure reasonably snow- or sparklie-free pictures. DBS backers realize that their signals must compete favorably with conventional broadcasting and cable TV if they are to stand a ghost of a chance.

For an in-depth look at the "rob Peter, pay Paul" dilemma, read Stephen Gibson's "How Big a Dish?" in the November, 1981, 73. The culprit, as Gibson points out, is noise.

In his article, "Direct Satellite TV: The 12-GHz Challenge" (*High Technology*, January/February, 1982), James Fawcette outlined three approaches to building receivers. The first and perhaps most startling method (shown in Fig. 2) is direct conversion, developed by the Japanese broadcasting giant, NHK. Akin to the simplest of ham receivers, the NHK design features a very low manufacturing cost. The signal goes from the antenna to a diode mixer via waveguide. There is no low-noise preamplifier stage. Fawcette cites an NHK claim of a 3.4-dB noise figure and 300-MHz bandwidth!

A more traditional approach to receiver design centers on a low-noise pre-

amplifier circuit operating at 12 GHz. Like the current 4-GHz gear, several gallium arsenide (GaAs) field-effect transistors (FETs) are chosen because of their minimal noise contribution to form a preamplifier before the mixer stage. GaAsFETs are, however, expensive and difficult to use. Designers must pay close attention to the transition from waveguide to printed circuitry and use isolators to insulate the FETs from high swr. These additions can add to the receiver noise level and require a lot of individualized alignment. The result, while expensive, should be better than that which is achieved with the direct-conversion approach.

Hobbyists who want to roll their own 12-GHz low-noise amplifier might want to consider the Mitsubishi MGF-1403. This GaAsFET, offered by at least one 73 advertiser, has a Ku-band noise figure of less than 2 dB. If your pocketbook permits, you might want to try for an even better noise figure.

Manufacturers hope to avoid the cost of discrete GaAsFET front ends by fabricating GaAs integrated circuits. It is conceivable that the entire receiver could be on one chip. But until GaAs technology is refined and yield levels are boosted, receivers probably will employ hybrid circuitry using discrete front ends and integrated circuits for intermediate frequencies and signal processing. Siemens A.G., a European

 


Fig. 3. ANIK C3, a Canadian satellite, may be the first source of North American 12-GHz television broadcasting. Its footprint will favor the northern United States. (Illustration from *Satellite Communications*, July, 1982.)

 


Fig. 4. By using a 4-GHz TVRO dish, front-end module from Plessey Corp. and integrated circuits for the i-f and signal-processing stages, a 12-GHz receiver could be within the reach of many hobbyists. For dyed-in-the-wool do-it-yourselfers, there are suitable GaAs FETs for building a 12-GHz low-noise amplifier, and a Gunn-diode oscillator could be used with a passive mixer for the downconverter stage.

corporation, already has introduced GaAs ICs that would follow the mixer stage in a DBS receiver.

A number of companies have finished prototype receivers and are laying the groundwork for manufacturing them in 100,000 quantity levels. European and Japanese companies like Plessey, Philips, Sony, NHK, and Siemens seem to be in the forefront. The late entry by American firms may be due to the lengthy FCC-approval process and lack of 12-GHz satellites for testing. Just who will dominate the US market remains to be seen. The ability to keep costs to a minimum could be the deciding factor.

### Getting Started

If you have read this far and like a challenge, then

consider getting in on the ground floor. In late 1980 a satellite built by Hughes Aircraft was put in a geosynchronous orbit of 106 degrees west. Operated by Satellite Business Systems (SBS), the spacecraft has ten-Ku-band transponders and is used by large corporations for high-speed data communication.

The all digital-time division multiple-access data format will make it difficult for hobbyists to receive any meaningful data from the SBS signals, but what the satellite does offer is a steady source for testing antennas and receivers. The transmitter footprint is said to be in the 43-dBW range, favoring the east central and western United States. SBS recommends that users have a 5.5- or 7.5-meter dish.

The first North American

satellite to carry 12-GHz video on a regular basis will probably be ANIK C3, which was launched from the Space Shuttle last November. (See Fig. 3.) Built by Hughes Aircraft for Telesat Canada, ANIK C3 has 16 12-GHz transponders that can accommodate data traffic or two FM TV channels each. Telesat Canada plans to lease most of the transponder space to US companies, including several interested in experimenting with direct broadcasting. Although ANIK C3 transmissions aren't as strong as future DBS signals, they should be easier to receive than those from the SBS satellite, especially if you live in the northern US.

Finding suitable 12-GHz hardware will be the biggest problem facing pioneer tinkers. One logical starting point is the dish antennas for 4-GHz TVRO reception. Some manufacturers even claim that their antenna will work just as well at the higher frequency. Whether you build or buy, remember that any dish antenna's performance is severely degraded if flaws in the surface accuracy exceed .1 times the wavelength of operation. For 12-GHz work, this means a tolerance of less than a tenth of an inch!

When choosing an antenna, pay close attention to the feed since it plays a big role in determining an antenna's efficiency. Remember, the feedhorn designed for a 4-GHz satellite system is not what is best for 12-GHz experimentation.

Choosing receiver components could be tough. If you have the necessary experience and test gear, you can roll your own 12-GHz LNA. Otherwise, you'll have to scour the surplus markets or save up enough money for a commercial-grade unit. Engineering evaluation models are starting to become available; Plessey Corp., for

example, offers a complete receiver front-end module.

Hams who have experimented with Gunn-diode-based oscillators may want to try building their own local oscillator and diode mixer. The secret seems to be keeping the local oscillator's frequency stable and reducing unwanted sideband noise. Once you have perfected the preamplifier, local oscillator, and mixer stages, you can rely on proven intermediate-frequency and signal-processing designs. Fig. 4 shows one possible approach at assembling a working 12-GHz terminal.

Does all this sound like too much—an impossible feat? Then think about the not-so-distant past when Bob Coleman K4AWB built a 4-GHz satellite terminal using a few hundred dollars worth of surplus "junk" and a VTVM. For him, satellite TV was an opportunity rather than a roadblock and there was no need to wait for someone else to lead the way.

Who will be the first to master the 12-GHz DBS challenge?

### Author's Note

Since the legality of unauthorized reception of satellite signals has not been decided, readers are urged to use discretion in decoding or disseminating any information they might receive. ■

### References

- Aviation Week & Space Technology*, December 8, 1980.
- 73 Magazine*, "How Big A Dish?," November, 1981.
- High Technology*, "Direct Satellite TV: The 12-GHz Challenge," January/February, 1982.
- Satellite Communications*, "Satellite Notebook 16," July, 1982.
- Satellite Communications*, "Satellite Notebook 17," August, 1982.
- Satellite Communications*, "More Is Not Better: The Case for Three DBS Service Areas," August, 1982.

# SATELLITE EARTH STATIONS BY Boman

## SAMPLE VOLUME DISCOUNT COUPON

Submit this coupon with your order, and/or payment, and receive one EFH-75 POLAR-MATIC FEED for evaluation purposes at the 24 lot price (Limit one per customer) \$99.50

NAME \_\_\_\_\_  
 COMPANY \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
 PHONE \_\_\_\_\_



## "SUPER DISH"

THERMO COMPRESSION MOLDED


By **Prodelin**

OPTIONAL  
CASSAGRAIN  
FEED


The Boman SA-3000 is a THERMOCOMPRES-  
 SION MOLDED Satellite Antenna ... NO  
 MORE GRIEF! FEATURES: 3.0 meter diameter  
 — 8 interlocking fiberglass sections for quick,  
 precise assembly — Unique design allows for  
 superior stress resistance to withstand exte-  
 reme environmental changes ... NO MORE  
 GRIEF!
 
## LNC

Why bother with a  
 separate Down Converter,  
 cables, etc.? Combined  
 Low-Noise Amplifier/  
 Down Converter features:  
 Grounded input coupling  
 protects against static in-  
 terference and lightning  
 damage — Low-loss, high  
 VSWR integrated circuit  
 assembly — One-piece  
 housing and gaskets en-  
 sure a weather tight case.



\*FOB FT. WAYNE, IN.

 

## SR-800 RECEIVER

ORDER WITH:


A - 100° (LNC)

B - 110° (LNC)

C - Down Converter

The Boman SR-800B Satellite Receiver uses advanced technology to provide high quality reception at a very affordable price. Features: 24 Channel capability — 6 audio channels — fine tuning control — AFC — illuminated signal strength meter — attractive design fits any decor.

## The "NEW" Polar-matic Ultra Feed

 


Improve your system quality with the  
 EFH-75 Microwave Feed. It offers  
 precision polarity selection using the  
 attractive control shown here.

INSTALLATION FEATURES: 130 ft. of 3 conductor wire included  
 TERMINALS attached at each end - NO MORE SPLICING - Molded  
 terminal posts on motor cover - Painted part prevents corrosion -  
 ON-OFF switch on control box - Power-on light on control box - All  
 necessary hardware included.

 
# \$99.50

DISTRIBUTOR PRICE

\* PRECISION CONTROL WITH  
 ON OFF SWITCH AND L.E.D.  
 INCLUDES "NO SLIP" CONTACT TAPE



 \* WEATHER PROOF TERMINAL STRIP  
 TO INSURE YEAR AROUND  
 CONNECTION (NO MORE SPLICING)



\* RIGHT ANGLE ADAPTER  
 PERMITS VERTICAL OR  
 RIGHT ANGLE L.N.A. MOUNTING




**BOMAN INDUSTRIES** 157  
**SATELLITE PRODUCTS DIVISION**  
 9300 HALL RD., DOWNEY, CA 90241  
 (213) 869-4041

Toll Free Numbers:

INSIDE CA: (800) 352-2553 OUTSIDE CA: (800) 421-2533

When it comes to

# QSL's...

 

it's the  
**ONLY BOOK!**

US or Foreign Listings

## 1983 callbooks NOW READY!

Here they are! The latest editions of the world-famous Radio Amateur Callbook are available now. The U.S. edition features over 400,000 listings, with over 75,000 changes from last year. The Foreign edition has over 370,000 listings, over 50,000 changes. Each book lists calls and the address information you need to send QSL's. Special features include call changes, census of amateur licenses, world-wide QSL bureaus, prefixes of the world, international postal rates, and much more. Place your order for the new 1983 Radio Amateur Callbooks, available now.

	Each	Shipping	Total
<input type="checkbox"/> US Callbook	\$19.95	\$3.05	\$23.00
<input type="checkbox"/> Foreign Callbook	\$18.95	\$3.05	\$22.00

Order both books at the same time for \$41.95 including shipping.

Order from your dealer or directly from the publisher. All direct orders add shipping charge. Foreign residents add \$4.55 for shipping. Illinois residents add 5% sales tax.



### SPECIAL OFFER!

Amateur Radio  
Emblem Patch  
only \$2.50 postpaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on Jackets and caps.

ORDER TODAY!

61

RADIO AMATEUR  
**callbook** INC.



Dept. B  
.....  
925 Sherwood Drive  
Lake Bluff, IL 60044, USA


# NEW



## TU-170A

This single shift TU-170A is designed for standard RTTY communications and modern high-speed rates to 300 baud ASCII. Comes standard with crystal controlled AFSK, RS-232C and TTL compatible I/O for computers, 2125Hz and 2295Hz filters. Options include LO-tones, CW demodulator, and loop power supply for TTY machines.

**\$189.95** kit  
**\$289.95** wired

 

## TU-300

The TU-300 offers all of the features of the TU-170A and more with the capability of three shifts selectable on the front panel. The TU-300 comes standard with crystal controlled AFSK, 2125Hz, 2295Hz, 2550Hz, and 2975Hz filters. (LO-tones, CW demodulator and Loop supply optional.)


**\$289.95** kit  
**\$399.95** wired



## TU-170

This single shift TU-170 is compact, economical and ideal for HF or VHF applications up to 110 baud ASCII. Single board construction with AFSK and loop supply included. TTL compatible I/O, active filters and AFSK tuned for 2125Hz, 2295Hz.

**\$149.95**  
kit only

 

## DM-170

The DM-170 demodulator is truly state-of-the-art, with active filters used throughout. The DM-170 includes anti-space circuitry, autostart output with adjustable threshold, scope outputs, meter output and loop keyer output. Requires additional  $\pm 12$ VDC power supply.

**\$47.95**  
kit only

Call or write for our 1983 catalog with complete specifications and our full line of products and accessories. Dealer inquiries welcome.




## Flesher Corporation

507 Jackson • P.O. Box 976 • Topeka, Kansas 66601  
913-354-7633 • Telex 437125

23
 
# T.V.I. problems?

Low pass T.V.I. filters from  
Barker & Williamson



427 425      424 423

Model	Power (Watts)	Cut Off Frequency	Frequency of Maximum Attenuation	Minimum Attenuation	Frequency Range	Price
425	1000	34 MHz	52 MHz	70 db	18 - 30 MHz	\$29.50*
424	100	44 MHz	57 MHz	60 db	18 - 30 MHz	\$22.50*
427	1000	55 MHz	63 MHz	70 db	6 meter	\$36.00*
423	100	55 MHz	63 MHz	50 db	6 meter	\$25.00*

All above to match  
50 ohm transmitters  
and antennas.

\*Add \$2 shipping  
and handling

ALL OUR PRODUCTS MADE IN USA



**BARKER & WILLIAMSON**

Quality Communication Products Since 1932

At your Distributors write or call  
10 Canal Street, Bristol PA - 19007

(215) 788-5581 ✓ 11



## 80M IN 24 FT!



Put a broad bandwidth 80M dipole in 24 ft with the SLINKY DIPOLE® antenna. Comparable low SWR, space savings and performance on ALL HF bands, including SWL and WARC. Complete kit: 2 special 4" coils, 50' RG-58/U coax, balun kit, mounting hardware and instructions. Great for apartments, condominiums, motels and vacation use. Easy set up and adjustment.

Ask for **FREE** antenna comparison sheet

**Blacksburg Group**  
Box 242 Suite 500  
Blacksburg, Virginia 24060  
703/951-9030

✓ 118

**49.95 postpaid** (In U.S.A.)  
Money Back Guarantee  
Virginia residents  
add 4% sales tax



# Have Rod... Will Travel

## 3 in one 1/4 Wave Mag Mount Antenna

2 Meters

220 MHz

440 MHz

## Super Rod 3

# \$ 19<sup>99</sup>

Complete set with cable assembly

- Fiber Glass Construction
- No Corosion
- Quick Change Rods
- Fits in any Attache Case
- Triple Chrome Mag Base
- Tuned Antenna Quality

The Tuned Antenna Co. has done it again with the "Super Rod 3" 1/4 wave 2 meter, 220 MHz, 440 MHz magnetic mount antenna system. With a twist of the base thumb screw you can change the 1/4 wave rods from one frequency range to another or adjust the SWR.

Truly a universal portable antenna system for car, hotel room, apartment or house. The "Super Rod 3" is the answer-all for under \$20.00.

THE TUNED ANTENNA CO.

✓ 57

Prices and/or specifications are subject to change without notice or obligation. Terms: C.O.D., check or money order. Please add \$3.00 for first antenna and \$2.00 for each additional antenna to cover shipping and handling. California residents add 6% sales tax.

For dealer location or

To order  
Call **(619) 268-0720**



The Tuned Antenna Co. 9520 Chesapeake Dr., #606, San Diego, CA 92123



to 24 V is much, much safer to work with than 300 V!

### Objectives

My main objective with this rig was to design a tube transmitter that fit in with the entire Fun series of simple, low-cost gear. It would be worthwhile to review the entire series, particularly the article on the Fun-Mitter (73 Magazine, February, 1981; see also "Fun-Equipment Revisited" in the January, 1983, issue). The Fun-Mitter is a 5-Watt, 80- through 15-meter solid-state transmitter. The characteristics of the Fun gear are: small size, simple construction, no adjustments, and all parts available from Radio Shack.

The objectives of the Fun-Vac were, in addition:

- PC board construction with the same size board as other Fun gear (2¼" × 3")
- a cost less than \$25
- easy assembly
- 2 to 5 Watts output

All of these objectives were met. Even a 300-volt power-supply design is included here.

### Circuit

The basis of the transmitter is a 6BQ5, a 9-pin miniature beam-power pentode available from Radio Shack. The 6BQ5 is a rugged device capable of dissipating 10 to 15 Watts under a 50% CW duty cycle.

The 6BQ5 functions as both oscillator and amplifier. The oscillator uses FT243 fundamental crystals in a Pierce configuration. C1 and C2 provide feedback between the control grid and cathode. The oscillator is keyed by breaking the cathode-to-ground connection. L1, R2, C3, and C4 comprise a wave-shaping circuit to eliminate clicks and sluggish starting of the oscillator.

The big power-waster of this circuit (as with all tube circuits) is the filament. A tube works by heating the cathode to jar electrons loose from its specially-coated surface. This is the

function of the filament (or heater) which actually glows orange, warming the cathode. The 6BQ5 requires 6.3 V at .75 Amps applied to the filament. (This is about 4½ Watts, or as much as the total output power of the tube!)

The plate operating voltage (250 to 300 V) is applied through plate choke L2. In order to meet the objective of using Radio Shack parts, L2 was required to be 100 uH. This is somewhat less inductance than the normal value of plate choke, but absolutely no problems were encountered. Rf output is taken from the plate through C7 and applied to the matching network, L3, L4, C8-C10. This network serves two purposes and is different from the norm in tube circuits.

Its first purpose is to match the impedance of the plate (about 2500Ω) to a 50Ω antenna load. This is accomplished by C8, C9, and L3. The second purpose is harmonic filtering, which is accomplished by both sections. The matching network is actually two pi networks combined. One matches 2500Ω to 50Ω and the other is a 50Ω-to-50Ω match.

Although the pi network is a standard method of matching impedances in a plate circuit, this network is different in one aspect: it is fixed-tuned. Normally, a variable-load capacitor would be used at C10 to adjust for an antenna load of between 30Ω and 70Ω. All of today's equipment is fixed-tuned for a 50Ω antenna load, and with antenna transmatches in abundance, the necessity for a variable load control no longer exists. Another norm in tube circuits is to use a variable-tune-control capacitor at C8. By designing for a somewhat lower Q, this capacitor was made fixed. No tuning adjustments are required! The entire transmitter can be built on a small PC board just like today's solid-state rigs, with no

 


Photo A. Front view of the Fun-Vac.

bulky front-panel variable capacitors!

The matching inductors, L3 and L4, are made from Radio Shack 10-uH chokes as has been done with all previous Fun gear. By removing the required amount of turns, the needed inductance is easily obtained. These chokes make for small and easy-to-make inductors—again, something quite unusual in a tube circuit.

The LED, CR1, was included to provide a method of monitoring plate current. The LED is wired in series with the plate voltage and lights brightly when the plate current passes through it. Because of the very low voltage drop across the LED, no power is lost in it. (It also is fun to use a modern solid-state device to monitor current in a tube rig!)

### Power-Supply Circuit

The Fun-Vac operates from two power-supply voltages, 6.3 volts ac and ap-

proximately 300 volts dc. The 6.3-V-ac filament voltage is somewhat critical in value, but the high voltage can vary between 200 and 350 volts. These voltages can be obtained from an existing supply or a supply can easily be built and incorporated into the same box with the Fun-Vac PC board. I chose to include power supply and Fun-Vac in one box, as shown in Photo B. However, the voltages can easily be "stolen" from a tube-transceiver supply or a similar supply by using the appropriate connector on the Fun-Vac chassis.

A simple circuit to obtain the needed voltages is shown in Fig. 2. An attempt was made to design a supply that also met the Fun gear objective of obtaining all parts from Radio Shack. The design shown meets that objective although it represents a rather unorthodox approach. By using two step-down transformers

 


Fig. 2. Fun-Vac power-supply schematic.

 


Fig. 3. Using the Fun-Oscillator and Fun-Amp with the Fun-Vac. The Fun-Amp relay-control voltage is needed due to the methods used with the Fun-Mitter. Mount resistors R1 and R2 very close to S1.

back to back, a secondary ac voltage of 117 volts is obtained. This is possible because of the relationship of the turns ratio of the transformer. (It is an old trick, used in the past to obtain a negative bias voltage for tube rigs.) The 117 volts ac is applied to a full-wave volt-

age doubler which provides 2.8 times the rms voltage ( $2.8 \times 117$ ) to provide about 320 volts dc.

This arrangement is not extremely efficient and the parts shown do not provide a very "stiff" high-voltage supply. This results in less power output than the tube

is actually capable of, but the parts are easy to obtain and the circuit is easy to build. The transformer windings must be connected in phase in order to add voltages. If, after the supply is wired, no ac output occurs at T2 secondary, then reverse the connections at T1 secondary.

Using the Radio Shack parts shown does make the power-supply portion of the Fun-Vac nearly as expensive as the rf circuitry. It may be possible to substitute for the filter capacitors by using the junk box or buying from a local TV repair shop. A value of 50 to 100  $\mu$ F will work fine, and even less capacitance can be used at the expense of less filtering and regulation. Also, the transformers can be replaced by any transformer that can supply the needed voltages.

 


Fig. 4. PC board.

 


Fig. 5. Component layout.

## Construction

Before beginning the actual construction of the Fun-Vac, a review of safety practices with high voltages is necessary. The high voltage used in this circuit can be lethal! When voltage is applied, never touch anything on the PC board or in the box. Always keep one hand away when making any measurements.

Using PC board construction for the Fun-Vac greatly simplifies building the rig and makes it as simple to build as solid-state gear. PC board use also eliminates wiring errors. All of the parts except the jacks, switches, and the plate-current LED are mounted on the board.

The 6BQ5 tube can be soldered directly to the PC board without a tube socket. This makes the loaded board shorter, which is important in mounting. If you purchase a new 6BQ5 from Radio Shack, there should not be a need to replace the tube, rendering the usual practice of using a tube socket unnecessary.

FT243 crystals and sockets can be obtained from a number of sources and are quite inexpensive. Mount the socket on the front panel to facilitate easy changing during operation.

The plate-current LED should be mounted in a hole on the front panel and glued in place. Route the wires to the LED carefully since these wires carry the high voltage. If possible, don't leave bare wire exposed anywhere in the high-voltage circuit.

The sheet-metal work necessary with the Fun-Vac is much simpler than it was in a comparable tube transmitter from fifteen years ago. Before, heavy metal was used, often even steel, and it had to be punched for tube sockets, variable capacitors, and large coils. Using the Radio Shack cabinet makes sheet-metal work easy. The light-gauge alumi-

# IC-740

## Internally Mounted Options



EX242  
FM UNIT

EX241  
MARKER  
UNIT

OPTIONAL  
FILTER  
LOCATIONS

EX243  
ELECTRONIC  
KEYER

**Internal options are provided for the IC-740 to increase its flexibility.**

EX238  
AC POWER  
SUPPLY



FAN (Part of  
EX238 Kit)

**The internal power supply, the EX238,** gives the IC-740 portability and also makes a clean looking shack.

With an installation time of under 30 minutes and clear instructions, the IC-EX238 can be installed easily. The EX238 works from either 110 or 220 VAC 50/60 Hz.

**The EX242 FM unit** allows transmission and reception of FM signals on 10 meters.

**A marker unit, EX241,** gives clear frequency marking signals at 25 or 100 KHz, selectable by top panel switches.

With the installation of the **EX243 electronic keyer and optional filters,** the IC-740 becomes a compact, complete CW station.

### Filtering

Control in Center Position

	Modes Of Use	4dB Bandwidth	40dB Bandwidth
<b>Standard Filtering IF Shift Mode</b>	CW/RTTY/SSB	2.4	4.5
<b>Standard Filtering PBT Mode</b>	CW/RTTY/SSB	2.2	3.6
<b>Optional FL44 with Standard PBT Filter</b>	CW/RTTY/SSB	2.2	3.0

### Optional Filters

Use	Center Frequency	6dB Bandwidth	40dB Bandwidth
<b>FL44</b> SSB/CW/RTTY	455.0KHz	2.4KHz	4.2KHz
<b>FL45</b> CW/RTTY	9.0115MHz	500Hz	1.6KHz
<b>FL54</b> CW/RTTY	9.0115MHz	270Hz	1.1KHz
<b>FL52</b> CW/RTTY	455.0KHz	500Hz	820Hz
<b>FL53</b> CW/RTTY	455.0KHz	250Hz	480Hz



# ICOM

## The World System

 


Photo B. Inside view of the Fun-Vac.

num is easily worked using a hand drill and a knife.

Mounting of the PC board in the cabinet should be done with care. If the Radio Shack cabinet is used, it will be necessary to mount the board at right angles to the case, as shown in Photo B. If desired, the bottom of the board can be covered with electrician's tape to keep fingers from accidentally touching the high voltage.

The wiring used is not particularly critical. The filament wire should be at least 22 gauge. All rf wiring should be with coax, and RG-58 will work fine.

After the power-supply section is completed, do not connect the voltages to the Fun-Vac PC board. This will be done after proper operation of the supply is verified.

#### Vfo and Amplifier Use

The Fun-Vfo (2/82) and Fun-Amp (5/82) can be used with the Fun-Vac easily. Using the Fun-Vfo requires the addition of a step-up transformer to match the output impedance of the Fun-Vfo to the high impedance of the control grid of the Fun-Vac. The vfo signal is applied to the crystal socket. A switch can be used to switch between vfo and crystal. Details of the impedance transformer and

possible switching arrangement are shown in Fig. 3.

The Fun-Amp is easily added to the Fun-Vac. It requires a control signal to control the Fun-Amp relay; this can be brought out of the Fun-Vac through a phono jack. The Fun-Amp will provide around 20 Watts of output power from the Fun-Vac. Details of the Fun-Amp use are given in Fig. 3.

 


Photo C. PC board for the Fun-Vac.

#### Adjustment

The safety factor cannot be overemphasized. During adjustment, with the case open, it is very easy to accidentally touch the high voltage. Whenever the cover is off, always be aware of where the high-potential voltage points are.

The only adjustments of

the Fun-Vac are really not adjustments at all, they are checks to ensure proper operation. If possible, obtain a voltmeter capable of measuring ac and dc voltage of greater than 300 V. At this time the two power-supply voltages should not be hooked up to the Fun-Vac. With the power on, carefully measure the high voltage. The reading should be between +250 volts and +350 volts.

Next, connect the filament-voltage wire to the PC board. Switch the voltmeter to the ac range and measure the filament voltage. It should be around 6.3 V. If it reads more than 7 volts ac, a filament-voltage dropping resistor may need to be added— $R = (V - 6.3) / .75$ . At this time, with 6.3 V ac on the filament, there should be an orange glow from the tube, indicating that the tube filament is working.

Next, with power off, connect the high voltage to the circuit board through the front-panel plate-current LED. Also, hook up a dummy load to the antenna connector and insert a key into J1.

Turn the power switch on and wait at least 30 seconds for the filament to warm up.

#### Fun-Vac Parts List (with Radio Shack numbers)

C1	4.7 pF	272-120
C2	100 pF	272-123
C3	.01 $\mu$ F	272-131
C4	.47 $\mu$ F	272-1071
C5	.005 350 V	272-1051 (Two in series)
C6	.005 350 V	272-1051 (Two in series)
C7	.005 350 V	272-1051 (Two in series)
C8	94 pF 100 V	272-121 (Two 47 pF in parallel)
C9	940 pF	272-125 (Two 470 pF in parallel)
C10	470 pF	272-125
CR1	LED	276-041
J1	Phone jack	274-252
J2	SO-239 ant. jack	278-201
J3	SO-239 ant. jack	278-201
L1	100 uH choke	273-102
L2	100 uH choke	273-102
L3	Remove 7 turns from 273-101A choke	
L4	Remove 17 turns from 273-101A choke	
R1	47k, 1/4 W	271-1342
R2	100, 1/4 W	271-1311
R3	15k, 1 W	271-040 (Two in parallel)
S1	DPDT	275-1546
V1	6BQ5	
Y1	7-MHz FT243 crystal	
Case		270-253

# LARSEN ANTENNAS TRAVEL IN THE FAST LANE.



Race car communications demand the best from an antenna under some of the worst conditions. Split second decisions require reliable signals at exceptionally high speeds.

That's why Larsen Antennas are used on race cars at the Indy 500. Because Larsen Antennas are designed to take high speed with minimal signal distortion. Proving they can travel in the fast lane without putting a drag on their performance.

Larsen's precision tapered stainless steel whip provides maximum flexibility while minimizing radiation pattern distortion, giving you a clear consistent signal. And Larsen's

exclusive Kūlrod® plating, gives your antenna high conductivity to assure that maximum power goes into communicating — not heat.

That full measure of performance goes into our product integrity too. With a no nonsense warranty that won't slow you down.

So, whether you're following the racing circuit or a local rescue effort, you'll find Larsen Antennas will keep you ahead of the situation with dependable performance. Ask your favorite Amateur dealer to demonstrate how you can hear the difference with Larsen Antennas. Write for our free Amateur catalog.



322

IN USA: Larsen Electronics, Inc.  
11611 N.E. 50th Avenue P.O. Box 1799 Vancouver, WA 98668 Phone: 206-573-2722

IN CANADA: Canadian Larsen Electronics, Ltd.  
283 E. 11th Avenue, Unit 101  
Vancouver, B.C. V5T 2C4 Phone 604-872-8517

Kūlrod® is a registered trademark of Larsen Electronics, Inc. in U.S.A. and Canada.

Kūlrod® is a registered trademark of Larsen Electronics, Inc. in U.S.A. and Canada.



**Fun-Vac Power Supply Parts List  
(with Radio Shack numbers)**

C1	Each capacitor should be about 25 $\mu$ F at a	
C2	voltage rating of at least 200 volts. This can be done by wiring four 272-1044 100- $\mu$ F 50-volt caps in series for each.	
CR1	400-V, 1-Amp diode	276-1103
CR2	400-V, 1-Amp diode	276-1103
R1	10 $\Omega$ 1/2 W	271-001
R2	10 $\Omega$ 1/2 W	271-001
S1	SPDT switch	275-324
T1	Transformer, 12.6 V ac, 1.2 Amps	273-1505
T2	Transformer, 12.6 V ac, 1.2 Amps	273-1505
	Fuseholder	270-365
	1/2-Amp fuse	270-1271
	Line cord	278-1255

With a 40-meter crystal installed and the receive/transmit switch set to transmit, close the key. The front-panel plate-current LED should light, indicating the plate current of around 30 to 50 mA. This indicates proper operation. If a wattmeter is connected between the antenna jack and the dummy load, a power output of between 2 and 5

Watts should be observed, with the key closed.

For vfo operation, merely substitute the Fun-Oscillator for the FT243 crystal and proceed as above.

If problems are encountered, a logical analysis should reveal the trouble. If power-supply voltages are correct, then the problem can be isolated to the Fun-Vac PC board. Measure the

voltages at the various points around the board corresponding to the indicated voltages on the schematic. If your voltages vary significantly from those given, then check and re-check for improperly soldered connections, miswiring, or faulty components.

**Operation**

Using the Fun-Vac for contacts is almost as much fun as building it! As with the Fun-Mitter, a 50 $\Omega$  resonant antenna must be used. This usually will provide an swr of 1 to 1, which is a good method of monitoring load conditions. With today's stations, the necessary 50 $\Omega$ -load antenna probably already exists due to the prevalent use of transmatches.

Allow the Fun-Vac to warm up for at least 30 seconds before use. In some ways, the soft warm glow of the tube as you operate is a reassuring feeling—reminis-

cent of days gone by. Incidentally, the heat generated by the soft, warm glow of the tube literally will keep your coffee warm—a side benefit of the Fun-Vac.

To operate, merely select the correct operating frequency, switch S1 to transmit, and begin keying. The receiver is connected to the receive antenna jack on the rear panel of the Fun-Vac. The low power of the Fun-Vac eliminates the necessity of a sidetone or receiver mute control since the actual signal can be listened to on the receiver without overloading.

**Conclusion**

The Fun-Vac provides a means of experimenting with tubes using modern methods. (If other band coverage is desired, refer to the Fun-Mitter articles.) It's amazing how simple those massive old rigs can be. Happy nostalgia! ■

**GET COMPETITIVE...GET DATONG!**  
World's finest accessories for the serious operator

**FL-3 = FL-2 +  
AUTO-NOTCH**

That's right! What you have been asking for is here. Combining the knife-edge selectivity of the FL-2 with the unique auto-notch feature of the FL-1 has produced our most effective multi-mode audio filter ever. Double-notch capability (one manual and one auto) for when that second whistle appears.



**\$284.95**

**ASP —  
RF SPEECH  
PROCESSOR**

Installs in MIC line. RF clipping with speech shaping from 0 to 30 db in 6 db steps. Frequency response 400-3400 Hz  $\pm$  3 db. Total harmonic distortion at 1 KHz, at 30 db clip level — 1/2%. Accepts Hi or Lo impedance MICs.



**\$179.95**

**RFA — BROADBAND  
PREAMPLIFIER**

Strengthens signal reception of any transceiver/receiver between 5 and 200 MHz. 9 db gain + low noise and 3rd order intercept of + 20 dbm. RF switched. Requires 12 dc @ 40 ma.



**\$74.95**

**"G4MH MINIBEAM  
ANTENNA"**

High performance, miniature antenna has 6' turning radius. Built from quality materials for durability in the worst weather. 11' element/5' boom. Weighs 14 lbs. Operating frequencies: 20m, 15m, 10m. Kit — \$139.95.



**\$169.95**

- ALL DATONG PRODUCTS CARRY A 90 DAY WARRANTY
- VISA-MASTERCARD WELCOME



**AR** Technical Products Corp. ✓329

877 S. Adams Road  
P.O. Box 62  
Birmingham, MI 48012  
Phone (313) 644-5698

# MFJ ANTENNA TUNERS 16 MODELS

## MFJ-941C 300 Watt Versa Tuner II

Has SWR/Wattmeter, Antenna Switch, Balun. Matches everything 1.8-30 MHz: dipoles, vees, random wires, verticals, mobile whips, beams, balanced lines, coax lines.



Ham Radio's most popular antenna tuner. Improved, too.

**\$89<sup>95</sup>** (+ \$4)

Fastest selling MFJ tuner . . . because it has the most wanted features at the best price.

Matches everything from 1.8-30MHz: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balanced and coax lines.

Run up to 300 watts RF power output.

SWR and dual range wattmeter (300 & 30 watts full scale, forward/reflected power). Sensitive meter measures SWR to 5 watts.

Flexible antenna switch selects 2 coax lines, direct or through tuner, random wire/balanced line, or tuner bypass for dummy load.

12 position efficient airwound inductor for lower losses, more watts out.

Built-in 4:1 balun for balanced lines. 1000V capacitor spacing.

Works with all solid state or tube rigs.

Easy to use, anywhere. Measures 8x2x6", has

SO-239 connectors, 5-way binding posts, finished in eggshell white with walnut-grained sides.

4 Other 300W Models: MFJ-940B, \$79.95 (+ \$4), like 941C less balun. MFJ-945, \$79.95 (+ \$4), like 941C less antenna switch. MFJ-944, \$79.95 (+ \$4), like 945, less SWR/Wattmeter. MFJ-943, \$69.95 (+ \$4), like 944, less antenna switch. Optional mobile bracket for 941C, 940B, 945, 944, \$3.00.

### MFJ-900 VERSA TUNER



MFJ-900  
**\$49<sup>95</sup>** (+ \$4)

Matches coax, random wires 1.8-30 MHz.

Handles up to 200 watts output; efficient airwound inductor gives more watts out. 5x2x6". Use any transceiver, solid-state or tube.

Operate all bands with one antenna.

#### 2 OTHER 200W MODELS:

MFJ-901, \$59.95 (+ \$4), like 900 but includes 4:1 balun for use with balanced lines.

MFJ-16010, \$39.95 (+ \$4), for random wires only. Great for apartment, motel, camping, operation. Tunes 1.8-30 MHz.

### MFJ-949B VERSA TUNER II



MFJ-949B  
**\$139<sup>95</sup>** (+ \$4)

MFJ's best 300 watt Versa Tuner II.

Matches everything from 1.8-30 MHz, coax, randoms, balanced lines, up to 300W output, solid-state or tubes.

Tunes out SWR on dipoles, vees, long wires, verticals, whips, beams, quads.

Built-in 4:1 balun. 300W, 50-ohm dummy load. SWR meter and 2-range wattmeter (300W & 30W).

6 position antenna switch on front panel, 12 position air-wound inductor, coax connectors, binding posts, black and beige case 10x3x7".

### MFJ-962 VERSA TUNER III



MFJ-962  
**\$229<sup>95</sup>** (+ \$10)

Run up to 1.5 KW PEP, match any feed line from 1.8-30 MHz.

Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected.

6 position antenna switch handles 2 coax lines (direct or through tuner), wire and balanced lines.

4:1 balun. 250 pf 6KV cap. 12 pos. inductor. Ceramic switches. Black cabinet, panel.

ANOTHER 1.5 KW MODEL: MFJ-961, \$189.95 (+ \$10), similar but less SWR/Wattmeter.

MFJ-10, 3 foot coax with connectors, \$4.95.

### MFJ-984 VERSA TUNER IV



MFJ-984  
**\$329<sup>95</sup>** (+ \$10)

Up to 3 KW PEP and it matches any feedline, 1.8-30 MHz, coax, balanced or random.

10 amp RF ammeter assures max. power at min. SWR. SWR/Wattmeter, for ref., 2000/200W.

18 position dual inductor, ceramic switch.

7 pos. ant. switch. 250 pf 6KV cap. 5x14x14".

300 watt dummy load. 4:1 ferrite balun.

3 MORE 3 KW MODELS: MFJ-981, \$239.95 (+ \$10), like 984 less ant. switch, ammeter.

MFJ-982, \$239.95 (+ \$10), like 984 less ammeter, SWR/Wattmeter. MFJ-980, \$209.95 (+ \$10), like 982 less ant. switch.

### MFJ-989 VERSA TUNER V



MFJ-989  
**\$329<sup>95</sup>** (+ \$10)

New smaller size matches new smaller rigs — only 10-3/4Wx4-1/2Hx14-7/8D".

3 KW PEP. 250 pf 6KV caps. Matches coax, balanced lines, random wires 1.8-30 MHz.

Roller inductor, 3-digit turns counter plus spinner knob for precise inductance control to get that SWR down.

Built-in 300 watt, 50 ohm dummy load.

Built-in 4:1 ferrite balun.

Built-in lighted 2% meter reads SWR plus forward/reflected power. 2 ranges (200 & 2000W).

6 position ant. switch. Al. cabinet. Tilt bail

To order or for your nearest dealer

CALL TOLL FREE 800-647-1800

For tech. info., order or repair status, or calls outside continental U.S. and Inside Miss., call 601-323-5869.

• All MFJ products unconditionally guaranteed for one year (except as noted).

• Products ordered from MFJ are returnable within 30 days for full refund (less shipping).

• Add shipping & handling charges in amounts shown in parentheses.

Write for FREE catalog, over 80 products

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

# FLEXI- BILITY



AEA once again breaks new ground in the code communications field with the new model MBA-RC reader/code converter. The MBA-RC decodes Morse, Baudot or ASCII signals off the air and displays them on a large 32 character alphanumeric vacuum fluorescent display. In addition, it will output Morse code for keying your transmitter. It will also generate RTTY (Baudot or ASCII AFSK two tone output. (170 or 850 Hz shifts.) Any of the acceptable input codes can be converted to any of the specified output codes (any speed to any speed). If you have any of the common Baudot RTTY terminals as an example, you can now send and receive Morse and ASCII with your keyboard and printer. You can even generate ASCII or BAUDOT RTTY using your Morse hand key or memory keyer.

Prices and Specifications subject to change without notice or obligation.  
Software ©copyright by AEA.

**BRITT'S TWO-WAY RADIO**  
2508 N. Atlanta Rd.  
Smyrna, GA 30080  
(404) 432-8006  
1-800-241-2027 ↗223

**AEA** Brings you the  
Breakthrough!

## HI ZOOT\* DOWNCONVERTER

\$149.95




API ELECTRONICS  
P.O. Box 4532  
Las Vegas, Nevada 89106  
(702) 386-7029

2300 MHz Amateur Downconverter  
Unequaled in performance at any price.

- 55+ db system gain.
- Special image rejection circuitry gives additional 3 db improvement over other designs.
- Unique temperature compensation circuit gives high stability.
- Highly sensitive for very weak signal reception.
- Tunes 2000 to 2500 MHz.
- 120° low noise amplifier in front end.
- Complete with power supply, cables and mast mount.

\*Hi Zoot = total absolute ultimate performance.

## Put Your Computer "On-The-Air"

 

### The Interface™ Sugg. Price \$189.95

Your personal computer becomes a complete CW/RTTY/ASCII send and receive terminal with The Interface linking it to your transceiver.

If you own an Apple II or Apple II Plus, Atari 400 or 800, TRS-80 Color Computer, or VIC-20, The Interface will put your computer "On-The-Air".

Software for each system features split screen display, buffered keyboard, status display, and message ports. Attach any Centronics compatible printer for hard copy. Software is available, on diskette for the Apple and program boards for the others, at an additional cost.

Apple diskette	Atari board	VIC-20 board	TRS-80C board
\$29.95	\$49.95	\$49.95	\$59.95

See The Interface at your authorized Kantronics dealer, or contact:

## Kantronics

(913) 842-7745 1202 E. 23rd Lawrence, Kansas 66044

# Barry Electronics Corp.

WE SHIP WORLDWIDE

WORLD WIDE AMATEUR RADIO SINCE 1950

305

**Your one source for all Radio Equipment!**

COMMERCIAL RADIOS  
stocked & serviced on  
premises.

**We Will Not Be Undersold Call:  
212-925-7000**

**KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK.**

**Saturday & Sunday 10 to 4 PM**

**Monday-Friday 9 to 6:30 PM**

**Come to Barry's for the best buys in town. For  
Orders Only Please Call: 1-800-221-2683.**



**Anchors A' Weigh for our Sale  
on Washington's Birthday!!**




**ICOM**

**IC-R70, IC-720A, IC-730, IC-740, IC-25A,  
IC-251A, IC-2KL, IC-451A, IC-290H, IC-45A**



 **YAESU**



**FT-ONE, FT-980R FT-102, FT-101ZD, FT-707, FT-230R,  
FT-480R, FT-720RU, FT-290R, FRG-7700, FT-625RD**



  **ROBOT Slow Scan TV 400 & 800**

Color Conversion Kit  
for Robot 400... \$450

**POWER PACKET  
VoCom Power  
Amplifier &  
5/8λHT Gain  
Antennas IN STOCK**



**BIRD  
Wattmeters &  
Elements  
In Stock**

**KANTRONICS  
Mini-Reader, Interface,  
Software & Code Tapes**

**EIMAC  
3-500Z  
572B, 6JS6C  
12BY7A &  
4-400A**



**AEA 144 MHz  
AEA 440 MHz  
ANTENNAS**

**YAESU  
FT-208R  
FT-708R**

**ICOM  
IC2AT  
IC3AT  
IC4AT**

**Land-Mobile HT  
Wilson Mini-Com II  
Yaesu FTC-2203, FT-4703  
Icom IC-M12 (Marine)  
IC-H12**



**DRAKE TR-5, TR-7A, R-7A, L-7, L-15, Earth  
Satellite Receiver ESR-24, THETA 9000E & 500,  
Digital Multimeter Model #8550-\$95.00**

**SMART PATCH**

CES-Simplex Autopatch 510-SA Will Patch FM  
Transceiver To Your Telephone. Great For  
Telephone Calls From Mobile To Base. Simple  
To Use - \$319.95



**SANTEC  
ST-144/UP  
ST-440/UP**



**NEW IMPROVED  
MURCH Model UT2000B**

Dentron Amplifiers, Tuners, Receivers Stocked:  
Clipperton T, Clipperton L, GLA-1000B,  
GLT-1000, Gallon, MLA-2500 2 Meter 1800  
Watts Linear, MLX Mini Transceiver, The  
Scout C.A.P. Transceiver, Horizon One  
Transceiver, Station One CW Radio Station.  
Write for specs, or call.



**MIRAGE B-23, B-1016, B-108,  
B-3016, C-22, C-106, D-24, D-1010**

**Tokyo Hy-Power  
Linears In Stock  
HL-20U HL-82V  
HL-32V HL-160V**

**Communications Specialists  
Encoders In Stock!**

**DIGITAL  
FREQUENCY  
COUNTER**

Trionyx-  
Model TR-1000  
0-600 MHz  
Digimax Model D-510 50 Hz-1GHz



**BENCHER PADDLES &  
Vibroplex Keys In Stock!!**



**New TEN-TEC  
Corsair In Stock**

Tri-Ex Towers  
Hy-Gain Towers & Antennas,  
and Rotors will be shipped  
direct to you FREE of shipping cost.

**New York City's LARGEST STOCKING HAM DEALER  
COMPLETE REPAIR LAB ON PREMISES**

**MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.**

BARRY INTERNATIONAL TELEX 12-7670  
TOP TRADES GIVEN ON YOUR USED EQUIPMENT  
STORE HOURS: Monday-Friday 9 to 6:30 PM  
(\$1.50 parking across the street)  
Saturday & Sunday 10 to 4 PM (Free Parking)

AUTHORIZED DIST. MCKAY DYMEK FOR  
SHORTWAVE ANTENNAS & RECEIVERS.

IRT/LEX-"Spring St. Station"

Subways: BMT-"Prince St. Station"

IND-"F" Train-Bwy. Station"

Bus: Broadway #6 to Spring St.

Clearance on our WW II  
surplus inventory on  
Washington's Birthday.

**"Aqui  
Se Habla  
Español"**

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic,  
Astron, B & K, B & W, Bash, Bencher, Bird, Battenut, CDE, CES, Collins,  
Communications Spec. Connectors, Covercraft, Cubic (Swan),  
Cushcraft, Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Elmac, En-  
comm, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics,  
Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage,  
Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook,  
Robot, Rockwell Collins, Saxton, Shure, Swan, Telex, Tempo, Ten-Tec,  
Tokyo Hi Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and  
Commercial Radlos, Vocom, Vibroplex, Curtis, Tri-Ex, Wacom Duplexers,  
Repeaters, Phelps Dodge, Fanon Intercoms, Scammers, Crystals.

**WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS  
DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED.**

**Amateur Radio & Computer Courses Given On Our Premises, Call**

**Export Orders Shipped Immediately. TELEX 12-7670**


# Adventure in Sarawak

*Two DXpeditioners journey to the land of headhunters—  
and send a signal to the rest of the world.*

*Kirsti Jenkins-Smith VK9NL  
PO Box 90  
Norfolk Island  
Australia 2899*



 *The three 9M8s; left to right, Jim 9M8JS, Paul 9M8PW, and Kirsti 9M8NL.*



*Jim at the rig.*

Sarawak—the land of the Hornbills, in Northwest Borneo: It is a country of rain forests, rivers, and unexplored areas. It is also a country of culture, arts, and handcrafts. Once the domain of headhunters, Sarawak is now the largest of Malaysia's 13 states.

So reads the caption on our QSL card from this operation. The idea of visiting Sarawak during our holidays came to us early in the year. It did not seem to appear on any of the guided-tour brochures which came our way, and as we are not very tourist-minded, this made us look into the possibility of visiting and also doing some operating from there.


There were no problems regarding travel and visas. Modern jet-liners connect with Kuching daily, and for us it was a matter of traveling Norfolk Island—Sydney—Singapore—Kuching. We had contacted Paul 9M8PW beforehand and he was most helpful in arranging accommodations for us in the Anglican Church hostel. Here we were able to rent a small flat and thus be independent.

This is necessary in this sort of venture since not everyone appreciates their houseguests staying up through the night making cups of coffee and shouting into a mike. And hotel accommodations—apart from

being expensive—present a problem in that hotel meal-times do not coincide with the times of the day when band conditions are down to nothing and it is most suitable for the operators to take a meal. In fact, they have a way of serving dinner and breakfast at peak operating times. So the hostel was ideal in many ways. It also was central and close to shops and restaurants.

We had applied for our licenses months before, and on arrival in Kuching were informed that these would be issued for the period of time we were visiting the country. This was good news indeed, as we were well aware of the reluctance to issue guest-licenses in Malaysia.

It now was a matter of proceeding to set up our operating quarters and station. Jim got busy with the multi-band dipole which we eventually were able to hang from under the roof of the building across the yard and make fast in a suitable tree. Paul had a beam he was not using which he lent us. It needed some repairs and handiwork done to it, and Jim got busy with this chore. At the same time, we were making enquiries as to where we might be able to obtain a steel water pipe to mount the beam on. We were met with a strange re-

 

*The battery setup after the lightning strike.*



*Our water-pipe antenna, overlooking Kuching.*

luctance which we did not get to understand until over a week later, but we decided to find pipe for ourselves.

Nowhere did we see such an item, but after making our way through nooks and crannies in the shopping center, we finally found a shop where they said that they could help. So across the street we went; a large storage room was unlocked, and there within were literally hundreds of pipes. We selected a 20-foot piece and asked if it could be brought home to us.

"No, no... (with an apologetic smile)!" Well, by this time we thought we had wasted enough time on the project, and the main thing was that we had the pipe within our reach. So resolutely we picked it up between us and paraded home through the streets to the vast enjoyment of the locals. Once home, there were no more difficulties. The caretaker and one of the gardeners came along, offered to help us put it up, and the job was done in minutes.

Later on, visiting the police museum at Fort Marguerita, we realized why we had experienced some reluctance in "operation water pipe." There on display were several guns and mortars homemade from water pipes which had been

confiscated from terrorists. We hasten to say that Sarawak is a well-ordered and safe state at present, but obviously they have learned from history and are not taking any chances.

We were now in business. We had decided to concentrate on CW contacts as this mode was more needed from East Malaysia. We did not have a thundering success that first day. We had the dipole only up to the first floor and there was a CW contest on that weekend. So, unless people were looking for us, we could not break through on the busy bands. We also found that propagation was not the best to America and Europe, but was excellent to Asian countries and the Pacific. It took a couple of days to get the antennas erected to their full potential, but gradually we worked our way into the rest of the world.

Openings to America and Europe continued to be a bit tricky, but with cooperation from the people calling, we were able to work pileups giving such reports as 529 and even 429. This is not possible unless there is some restraint on behalf on the ones awaiting their turn. The bands usually opened properly for a few hours from midnight on and the path would be open to the USA

and Europe, which created some tremendous pileups. The Europeans are not known for their patience and restraint in these circumstances, so it was plain hard work. It was, on the other hand, a pleasure to work a pileup of JA-boys. Their operating manner is above reproach.

Anyway, we continued in this manner for the first week and were looking forward to the weekend when lots of people who have only weekends available for their hobby would be around. On Saturday afternoon, however, there was a tremendous flash of lightning simultaneous with a deafening crash of thunder. Jim was outside making improvements to the antennas and was holding the 40-meter dipole in his hand at the time. It was lucky that he escaped being sizzled. That the power supply to the rig died instantly is really of minor importance in comparison. However, we were effectively shut down for 24 hours while we tried to repair the power supply.

We were able to buy some of the components we knew had blown, but after struggling until 2:00 am Sunday replacing these and still not making it work, we realized we were going nowhere unless we could gain access to a good ham shop. With one

resident ham in the country, the shops did not stock ham gear. We finally arranged to hire a battery and charger which gave us 25 Watts, and by borrowing Paul's linear, we could bring this up to 100-150 Watts and continue operation.

The second week was mostly a continuation of the first week. The number of QSOs crept upwards, and it was nice to meet old friends in the pileups. We had realized by now that checking into nets we usually checked into from Norfolk Island was virtually impossible due to lack of propagation at those specific times. So, we carried on with the pileups, still concentrating on CW, Jim with his fancy electronic keyer and I with my old faithful straight key. (I want to go down in history as the only DXpeditioner stubbornly sticking to a 1940-model straight key in 1982, hi.)

We had by now been in Sarawak long enough to have spent time sightseeing and getting the feel of the place. Kuching is a fascinating city with all its old-world charm intact. There are the old narrow streets lined with shops absolutely spilling goods of every description out onto the footpaths. There were the handmade souvenirs made from local materials, and there were



The author stayed at the rig when the aerial fogging to kill mosquitoes began.



A typical shop in Kuching.

the friendly people, hard-working and cheerful. We spent many hours in the museum, learning a lot about the culture and history of the country.

And not far out of town was the jungle, practically undisturbed. We also were aware now that the dreaded

dengue fever was around. We swallowed anti-malaria tablets against malaria and kept our fingers crossed against cholera, but as far as dengue was concerned, we just did our best to keep the mosquitos at bay by spraying the rooms and burning mosquito-coils through the

night. We still became covered with bites and just hoped it was not the dengue-carrying kind of mosquito that had feasted on us.

The authorities had an ongoing eradication scheme against this particular beast, and one rule was that if someone contracted dengue, every house in the neighborhood was treated with a sort of spray. So it was that on one fine evening there was a whirring sort of noise outside, and the next thing we knew the flat started filling up with a dense fog. (See photo of the author at the rig at the beginning of the fogging process.)

It got so thick that we could not see at all at a distance of 2-3 meters. We could not breathe, either, so we agreed there was a limit to how devoted one can be, hi, and we would not be much use to our fellow amateurs if we suffocated. There was also the fact that we did not know exactly what the fog contained and just how harmful it might be to humans. So it was a matter of QRT and escape downtown for a meal. (The frogs were particularly noisy that night. We think they were kicking up a row because their favorite food had been done away with!)

All things come to an end,


and so also did our stay in Kuching. We had settled in properly and were most reluctant to leave. We took one last look out the window at the view of tile-covered roofs, charcoal smoke rising amongst them, and one last admiring look at the orchids growing in a hedge along the footpath. Then a quick good-bye and *au revoir* to Paul's family and Paul drove us to the airport.

We really had not wanted to go, but we had received the good news that we had been successful in chartering a vessel, the *Cheyne II*, for our January, 1983, Heard Island DXpedition. So, although we had an unforgettable holiday and made 10,500 QSOs in Sarawak, we knew that loads of work regarding our Heard Island trip would be waiting for us at home and we just had to move on.

Afterthought: It was very hot in Kuching. There never seemed to be any breeze to relieve the heat of the day. And as the bands closed in the middle of the day, this was when we emerged outside for sightseeing and shopping. Strange how that old tune kept coming into my mind all the time: Mad dogs and Englishmen go out in the midday sun... It could just as well read: Mad dogs and ham-band-fans go out... etc.! ■

## PROGRAMMABLE CTCSS ENCODER

**\$26<sup>95</sup>**

 

- All 37 EIA Tones
- Quartz Accurate
- Less than 1 inch square

AVAILABLE FOR IMMEDIATE DELIVERY  
For more information call TOLL-FREE  
(800) 828-6884

NY: (800) 462-7242

CANADA: (416) 884-3180

218



**FERRITRONICS**  
MOBILE DATA SYSTEMS

1319 PINE AVE.  
NIAGARA FALLS NY 14301  
(716) 282-7470 TLX 64-6303

# AZDEN

## PCS-2800 10-METER MICROCOMPUTER FM TRANSCEIVER



- Just 6-3/4" x 2-3/8" x 9-3/4"
- Microcomputer controlled
- Detachable head
- 6 channels of memory with scan
- Full band scan
- 10 watts output - also 1 watt low power
- Dynamic microphone, internal speaker, mobile mounting bracket, and hardware included

SPECIAL  
**\$229<sup>00</sup>**

- 28 - 29.995 MHz, 10 kHz steps with -100 kHz offset

**AMATEUR-WHOLESALE ELECTRONICS**  
8817 S.W. 129th Terrace, Miami, FL 33176 ✓5  
Phone 305-233-3631  
Toll Free 800-327-3102



CREDIT CARD HOLDERS MAY USE OUR  
TOLL FREE ORDERING NUMBER

### TUSA

A WHOLE NEW WORLD OF TV VIEWING WITH TUSA'S NEW MODEL CVU-60, 40 CHANNEL CABLE TV CONVERTER. Receive all the EXTRA CABLE TV "MIDBAND" & SUPERBAND CHANNELS on your UHF DIAL. Eliminates the need for renting or leasing. This stable and reliable system converts extra cable TV channels so they can be received on the UHF tuner of your TV set.

Now available in a MUST FOR VIDEO TAPING FROM CABLE TV! The system allows you to program both pay day TV decoder required and standard cable channels for taping on any VCR - while you are watching a different channel on your TV. Now **\$28.95 ea.** Simple to install and operate on any make of TV with UHF. PLUS POSTAGE

**NOW AVAILABLE  
NEW TUNEABLE DELUXE MODEL CVU-1000 \$34.95..**

### POPULAR IC'S

TOP QUALITY NO SECONDS

TYPE	DESCRIPTION	1-9	10-19
LM-3804	2 watt Audio Power Amp	\$1.49	\$1.12
LM-3884-3	Low Voltage Audio Amp	500WV	
NE-5644	Digital Phase Locked Loop	1.59	1.19
LM-9854	Phase Locked Loop	1.49	1.12
LM-7334	Video Amp	1.69	1.27
MC-1330	Video Detector	2.49	1.87
MC-1349	Video If Amp	2.08	.56
MC-1350	Video If Amp	1.75	.31
MC-1352	Video If Amp AGC	2.69	2.09
MC-1356	Audio If Amp	1.95	.46
MC-1374P	RF Modulator	3.19	2.30
MC-1458	Dual Comp. Op Amp	.86	.66
MC-1498A	Biased Mod-Demodulator	1.79	.34
LM-1900	PLL Stereo Decoder	4.49	3.37
LM-1888	Video Modulator	2.95	2.21
<b>LINEAR VOLTAGE REGULATORS</b>			
LM-7805	5 Volt Positive Volt. Reg.	1.30	1.04
LM-7808	8 Volt Positive Volt. Reg.	1.39	1.04
LM-7812	12 Volt Positive Volt. Reg.	1.39	1.04
LM-7815	15 Volt Positive Volt. Reg.	1.39	1.04
LM-7818	18 Volt Positive Volt. Reg.	1.39	1.04
LM-7824	24 Volt Positive Volt. Reg.	1.39	1.04

### WINEGARD

75 OHM UHF YAGI ANTENNAS

12 db GAIN CHANNELS 44 - 52 **\$8<sup>95</sup> ea.**

9 OR MORE **\$6<sup>95</sup> ea.**

OPTIONAL Winegard UHF Antenna Phasing Bolt Gain **\$39<sup>95</sup> ea.**

### BRAND NEW UHF VARACTOR TUNERS

Sanyo **45 MHz Output \$24.95 ea.**

Mitsumi **45 MHz Output \$24.95 ea.**

Call for Quantity Prices

### POPULAR MICROWAVE PARTS

MRF-801	\$2.75
9-Up	2.19
MRF-911	3.46
9-Up	3.12
MBO-101	.98
CHIP CAPS - .001 mfd	.50
20-Up	.20
2N6603 (formerly MRF 802)	11.96

### Special Purchase

MV-2109  
33pf Tuning Diode  
1-9 **\$.69 ea.**  
10-Up **\$.39 ea.**

5% MICA CAPS 5%  
100pf .42c ea. 500pf .65c ea.  
43pf .36c ea. 1200pf .89c ea.  
110pf .36c ea. 3000pf 1.39c ea.

### CABLE CONNECTOR

F-59 Male connector for RG-59/U cable. Complete with ferrule. Mates with female "F" connectors.

20c ea.  
100 for **\$14.70**

### TUSA MAX-2 LOW LOSS MATCHING TRANSFORMERS

Indoor 75-300 **\$.98**  
10-Up **.79**  
Outdoor 75-300 **1.59**  
10-Up **1.19**

### 5" DELUXE SPEAKER

Handles up to 15 watts, 4 Ohms, 3 oz. Ceramic Magnet

**\$1.89 ea.**  
10 up **\$14.95 ea.**

### WINEGARD DELUXE A-B SWITCH TV-1051

For CATV - MATV - VCR  
75 ohm - 90 db Isolation  
While They Last **\$6.95 ea.**

### PROJECT BOXES

Woodgrain

This box is 1 1/2" W. 4 1/2" H. 6 1/2" D. with a removable aluminum U-shaped chassis 1 1/2" W. 3 1/2" H. 6" D. inside.

**\$12.50 ea.**  
4 or more **\$10.95 ea.**

### AC LINE CORDS

Gray 16 ga. wire  
6 ft. long cable  
Prestripped and tinned ends for easy installation.

1-9 **59c ea.**  
10-99 **49c ea.**  
AC-6G 100-Up **39c ea.**

### POPULAR MISCELLANEOUS PARTS

10K Volume Control with DPDT switch **\$1.49**  
10-Up **1.19**  
1/2w 10K Thumbwheel pots **.39**  
1-12 **.29**  
13-Up **.29**  
Toroids T30-12 **.46**  
20-Up **.25**  
Toroids T32-2 **.38**  
20-Up **.25**

### UHF - VHF - FM SPLITTER

40-90C Mhz  
For RF2TV  
Low Loss 3.5-4 db. Low VSWR  
Waterproof Housing  
10-Up **\$1.89 ea.**

### ORDER NOW TOLL FREE

800-854-4655  
OUTSIDE CALIFORNIA  
714-635-5090  
INSIDE CALIFORNIA

### R.F. ELECTRONICS

1056 N. STATE COLLEGE BLVD., DEPT. G  
ANAHEIM, CALIFORNIA 92806

PERSONAL CHECKS HELD FOR CLEARANCE

MAIL ORDERS WELCOME - INCLUDE POSTAGE - SHIPPED SAME DAY RECEIVED - NO MINIMUM ORDER

Introducing our Latest Model — NOVAX II  
Inquire about our spring sale!

SIMPLEX / DUPLEX  
AUTOPATCH

NOVAX I



NOVAX II



NOW TWO MODELS TO  
SERVE YOU BETTER  
YOUR OWN PRIVATE AUTOPATCH

**NOVAX**  
MOBILE CONNECTION

NOVAX interfaces your standard 2 meter, 220; 450; etc. Base station and telephone, using a high speed scan switching technique so that you can direct dial from your automobile or with your HT from the backyard or poolside — Automatically ... Easy installation transceivers, featuring solid state switching, offer best results ... Available interfaced with an ICOM 22U.

FEATURES	NOVAX I	NOVAX II
• 3 min. Call duration timer	YES	YES
• Up to 45 sec. activity timer	YES	YES
• Single digit Access Control	YES	NO
• DTMF (Touch Tone)* phone connection	YES	YES
• 4 digit Access Control	NO	YES
• Toll Restrict	NO	YES
• LED Digital Display	NO	YES
• Vinyl covered alum. case size	8" x 6" x 2"	10" x 8" x 1 1/2"
• Directly Interfaces with Repeater	NO	YES
• Rotary Dial System (incl. Last digit dial)	NO	YES—"Option"—\$49.95
• Ring Back (reverse autopatch) "Option"	YES—\$39.95; Kit \$29.95	YES—Wired—\$39.95
• Price	Kit \$169.95/wired \$219.95	Wired only \$279.95
N.Y.S. Res. add appro. Sales Tax	SHIPPING ADD \$3.50 in U.S.A.	

To order, send check, money order to:  
MASTER CHARGE AND VISA ACCEPTED

LABENT DEVELOPMENT CORPORATION  
(formerly R.W.D. Inc.)

Box 162 - Tudman Rd.  
Westmoreland, N.Y. 13490  
or Phone 315-829-2785

\* Trademark IIT

## HIGH PERFORMANCE PRESELECTOR-PREAMP

The solution to most interference, intermod, and desense problems in AMATEUR and COMMERCIAL systems.




- 40 to 1000 Mhz - tuned to your frequency
- 5 large helical resonators
- Low noise - High overload resistance
- 8 db gain - ultimate rejection > 80 db
- 10 to 15 volts DC operation
- Size - 1.6 x 2.6 x 4.75" exc. connectors
- FANTASTIC REJECTION!

Typical rejection:

± 600 Khz @ 144 Mhz: -28dB  
± 1.6 Mhz @ 220 Mhz: -40dB  
± 5 Mhz @ 450 Mhz: -50dB

Price - \$69.95 bipolar w/RCA jacks  
Connector options: BNC \$5, UHF \$6, N \$10  
SUPER HOT! GaAs Fet option \$20

## AUTOMATIC IDENTIFIERS

 

ID-1



ID-2

- For transceivers and repeaters - AMATEUR and COMMERCIAL
  - Automatic operation - adjustable speed and amplitude
  - Small size - easy installation - 7 to 15 volts DC
  - 8 selectable, reprogrammable messages - each up to 2 min. long
  - Wired, tested, and programmed with your message(s)
- Model ID-1 - \$39.95 Model ID-2 w/2 to 10 minute timer - \$59.95

We offer a complete line of transmitter and receiver strips and synthesizers for amateur and commercial use.  
Request our free catalog. Allow \$2 for UPS shipping - Mastercard and VISA welcome

**GLB ELECTRONICS**  
1952 Clinton St. Buffalo, NY 14206  
716-824-7936, 9 to 4

✓ 143

# Put 2 Meters in Your Shirt Pocket

*Radio Shack's Pocket Weatheradio makes a dandy 2-meter receiver. A few quick modifications will get it right on target.*

Lester Kolb K3PJG  
PO Box 161  
Lebanon OR 97355

Quality, simplicity, and low price make this shirt-pocket two-meter receiver surpass anything on the market, if indeed such a compact gadget with these features is available.

The heart of the FM monitor is a "Pocket Weatheradio" which is listed in Radio Shack's 1982 catalog for \$12.95 and measures less

than  $4 \times 3 \times 1\frac{1}{4}$  inches. Originally covering the 162.40-162.55-MHz weather-band, the state-of-the-art circuit features of the Weatheradio make it an ideal choice for conversion to two-meter FM. The frequency modification consists of simply adding three 5-pF capacitors across three inductors. This modification alone makes a dandy monitor, but the addition of a simple squelch circuit puts icing on the cake.

## Weatheradio Circuit

The schematic included with the radio shows a simple, well-designed circuit consisting of a zener-regulated, three-transistor front

end followed by a 4.5-MHz ceramic filter and a total of two ICs for i-f amp/FM detector and audio amp. The local oscillator is tuned by a varicap diode, and a 10k pot serves as a tuning control. The rf amp is not variably tuned since the small frequency range does not require it. Selectivity and frequency stability are excellent for a tunable VHF receiver, but don't expect top sensitivity.

## Disassembly

Snap the plastic cover off the Weatheradio case. A cardboard insert over the circuit board is firmly glued to one of the electrolytic caps. Carefully remove this

insert from the cap to have a look at the board. The cardboard insert can be cut off permanently except for the nine-volt-battery area. With a miniature phillips screwdriver, remove the two screws holding the volume and tuning knobs to their shafts. Also remove the two screws from the circuit board and the one anchoring the whip antenna. Remove the whip through the top of the case and take out the circuit board. Unsolder the leads from the speaker itself to avoid errors when reconnecting. Use small clip leads to the speaker while testing.

## Frequency Modification

All that is required to cover two meters is the addition of a 5-pF capacitor (parallel) directly across inductors L1, L2, and L4. The locations of these coils are shown in Fig. 1. No existing parts are removed. After soldering these caps into place on the foil side of the board, reconnect the speaker, slip the board back into the case, and install the knobs and

 


Fig. 1. Weatheradio component layout.

 


Fig. 2. Hybrid squelch circuit.

whip for final testing. Reconnect the battery, set the tuning knob to mid-position, and with a toothpick or pointed nonmetallic tool, spread or compress L4 (local oscillator) until you hear a local repeater signal or desired center frequency from a signal generator. L2 and L1 (rf amp) should be spread or compressed in the same manner for maximum quieting, which can be accomplished only with a weak signal, preferably from a signal generator. Even though coupling between the local oscillator and the rf amp is very light, peaking of L2 for maximum sensitivity will shift the receive frequency slightly, so keep retuning on-to frequency as L2 is being peaked; an increase in noise may be a shift off frequency rather than a decrease in sensitivity. Strong signals can be received even without adjustment of L2 and L1, but peaking (especially L2) is recommended for best sensitivity.

### Hybrid Squelch

Drilling holes or adding controls and switches to an otherwise attractive custom case is both difficult and unsightly. With this in mind, I came up with a novel idea which I call a hybrid squelch; the volume control doubles as a squelch control. The squelch engages at (and remains engaged above) any preset volume level suited to preference by varying the squelch sensitivity setting of R2 (Fig. 2). Once this R2 level is set, it needs no further adjustment. Although the most sensitive volume/squelch setting is just at threshold, a moderately strong signal will open squelch even if set at full volume. The use of the volume control as a squelch control is accomplished by coupling the input of the 741 op amp directly to the center tab of the Weatheradio volume control with a 240-pF capacitor. Thus, the input level to


the noise amp/squelch switch varies with the volume setting.

Fig. 2 shows the complete squelch circuit. The 741 (DIP) op amp serves as a high-gain noise amplifier. Germanium diodes D1 and D2 provide a dc voltage which mutes the Weatheradio audio amp (IC2) at pin 2 when no signal is present. The 240-pF coupling capacitor helps eliminate passage of voice frequencies. However, if you find that, at high-volume settings, heavy modulation activates the sensitive squelch during voice peaks, reduce squelch sensitivity R2 until a compromise position is reached. To save space and eliminate the need for a subminiature pot, I adjusted R2 to the desired level, measured the resistance on each side, and substituted fixed resistors as a divider. An alternative would be to substitute a fixed 10k resistor for the R2 pot (connecting C2 to the junction of R2 and pin 6 of IC3) and to lower the gain of IC3

by reducing R1 to anywhere between 6.8 and 2.2 megohms. For this approach, I found the optimum value to be somewhere between 2.2 and 4.7 megohms. R3 and R4 on pin 3 of the 741 are standard practice, but optional; mine functions perfectly without them.
 
### Construction Notes

Store all tiny screws and the knobs in a cup; they have a tendency to wander off. All parts for these modifications were soldered directly to the foil side of the Weatheradio board, each supported by its own leads or short lengths of thin but rigid wire. Space is limited, requiring 1/4-Watt resistors and other parts of miniature variety. The 741 DIP was mounted against the foil side of the board, leads up, between IC1 and the immediate side edge of the board, with leads trimmed short. Keep parts placement near the board edges, as the speaker magnet area has the least room for clearance.



*Circuit modifications.*

The protective coating on the foil can be scraped away at points needing the solder connections. Watch battery polarities and note that the Weatheradio schematic chassis symbol designates nine volts *positive*. Be sure to connect the positive lead of the squelch circuit to a point *after* the on/off switch so it does not draw current when the radio is turned off. A circuit modification or error on the Weatheradio schematic has pins 2 and 3 of audio amp IC2 reversed. Squelch output (from D2 and C3 of Fig. 2) goes to actual pin 2 of IC2. As each part is added to the board, it is a good idea to seat the board into position in the plastic case to check for parts clearance and to avoid shorting leads to the metal speaker. Care and patience cannot be overemphasized. It is quite easy to make optical reversals while looking at both sides of the board for circuit points of inductors and IC pin numbers. Triple check. Insert a milliam-



# We stock: RADIOS

Azden  
Icom  
KDK  
Kenwood  
Santec  
Ten-Tec  
Yaesu

# ANTENNAS

AEA Isopoles  
Antenna Specialists  
Avanti  
Butternut  
Cushcraft  
Hustler  
Hy-Gain  
KLM  
Larsen  
Mini-Products  
Mosley  
VoCom

# ACCESSORIES

AEA Keys, Code Readers  
Alliance Rotors  
Amertron Amplifiers  
ARRL Publications  
Astron Power Supplies  
B & W  
Bencher Paddles  
Callbooks  
CDE (Telex) Rotors  
Daiwa/MCM/J.W. Miller  
Kantronics  
MFJ  
Benjamin Michael Clocks  
Microlog  
Mirage Amplifiers & Meters  
Saxon Cable  
Telex Headsets  
Tokyo Hy-Power Amplifiers  
VoCom Amplifiers

# ege, inc.

13646 Jefferson Davis Highway  
Woodbridge, Virginia 22191  
Store Hours: M-W-F 12 noon-8 p.m.  
T-Th-S 10 a.m.-4 p.m.  
Information and Virginia Orders:  
(703) 643-1063  
Call for Quotes  
Dealer Inquiries Invited

Your SWL & Marine Communications Dealer

## ORDER TOLL FREE 1-800-336-4799

(Orders Only, Please)

Order Hours: M-F 11 a.m. to 7 p.m.;  
Saturday 10 a.m. to 4 p.m.  
Bonus: 2% Discount  
for Prepaid Mail Orders  
(Cashiers Check or Money Order)

Send stamp for a flyer.  
Terms: Prices do not include  
shipping. VISA and Master Charge  
accepted. 2% discount for prepaid  
orders (cashier's check or money  
order). COD fee \$2.00 per order.  
Prices subject to change without  
notice or obligation. No personal  
checks accepted. Returns  
subject to 10% restocking fee.

# Alaska Microwave Labs

P.O. BOX 2049 PALMER, ALASKA 99645  
(907) 376-3098 DEPT 73

## GaAs FETS

MGF1400 NF 2.00B @ 4GHZ MAG 150B \$14.00  
MGF1412 NF 0.80B @ 4GHZ MAG 180B \$50.00  
MCF1200 NF 1.00B @ 1GHZ, NF 2.20B & MAG 140B @ 4GHZ \$11.00

## VTO

V72T-1 2.7GHZ TO 3.2GHZ MIN POWER OUT 10 MW  
TUNING VOLTAGE 0 TO 20V Vcc +15 vdc at 60 MA \$98.00  
V72T-2 2.8GHZ TO 3.3GHZ REST SAME AS V72T-1 \$98.00  
V82T-1 SAME AS V72T-1 BUT FREQ 3.0GHZ TO 3.5GHZ \$98.00  
V82T-2 SAME AS V72T-1 BUT FREQ 3.6GHZ TO 4.2GHZ \$98.00  
V82T-3 SAME AS V72T-1 BUT FREQ 4.0GHZ TO 4.5GHZ \$98.00  
V92T-1 SAME AS V72T-1 BUT FREQ 4.5GHZ TO 5.0GHZ \$98.00  
V56T-1 .9GHZ TO 1.6GHZ POWER OUT 13 MW TUNING  
VOLTAGE 2 TO 50V Vcc +15 VDC AT 60 MA \$98.00  
V56T-1 SAME AS V56T-1 BUT FREQ 1.5GHZ TO 2.5GHZ \$98.00

## CHIP CAPACITORS

1.2 2.2 2.7 3.3 4.7 6.8 10 18 22 27 47 100 120 180,  
220 270 330 390 470 560 680 820 1K 1.2K 1.8K 3.9K,  
8.2K 10K 100K \$60

## PISTON TRIMMERS

TRIKO 201-01M \$5.50  
3-1.8PF \$2.50  
5-3 PF \$2.50  
1-8 PF \$2.50

## TEFLON CIRCUIT BOARD DBL SIDED 1 OZ

APPROX 3.25" x 5.0" x .010 \$5.50  
APPROX 3.25" x 5.0" x .0312 \$6.50  
APPROX 3.25" x 5.0" x .0625 \$10.50

## MIXERS

3.7GHZ TO 4.2GHZ MIXER, LO 2.6GHZ TO 5.1GHZ,  
IF DC-9GHZ SSB CONVERSION LOSS TYP 5.50B MAX  
6.50B, TO-8 PACKAGE \$55.00  
9GHZ TO 1.36GHZ MIXER, LO 7GHZ TO 1.5GHZ, IF OC-  
26GHZ SSB CONVERSION LOSS TYPE 7.00B, TO-8  
PACKAGE \$15.00

## CHIP RESISTORS

50 OHM 1/2 WATT \$1.50  
3 1% CHIP RESISTORS FOR:  
50 OHM T NETWORK 3 OZ PAO \$6.00

NO WARRANTY ON SEMICONDUCTORS

OPEN AT 8 PM EST CLOSED 8PM PST  
ORDERS ARE POSTAGE PAID  
COD - VISA - MASTERCARD

## NEW TS830S for \$150?

Yes indeed! Just add a Matched Pair of top-quality 2.1KHz BW (bandwidth) Fox Tango Filters. Here are a few quotes from users:

"... Makes a new rig out of my old TS830S!..."  
"... VBT now works the way I dreamed it should..."  
"... Spectacular improvement in SSB selectivity..."  
"... Completely eliminates my need for a CW filter..."  
"... Simple installation - excellent instructions..."

The Fox Tango filters are notably superior to both original 2.7KHz BW units but especially the modest ceramic 2nd IF; our substitutes are 8-pole discrete-crystal construction. The comparative FT vs Kenwood results? VBT OFF — RX BW: 2.0 vs 2.4; Shape Factor: 1.19 vs 1.34; 80dB BW: 2.48 vs 3.41; Ultimate Rejection: 110dB vs 80. VBT SET FOR CW at 300Hz BW — SF 2.9 vs 3.33; Insertion Loss: 1dB vs 10dB.

## AND NOW A NEW TS 930S!

Tests prove that the same filters improve the '930 even more than our '830. Don't buy CW filters— not even ours. You probably won't need them!

INTRODUCTORY PRICE: (Complete Kit)...\$150  
Includes Matched Pair of Fox Tango Filters, all needed cables, parts, detailed instructions. Specify kit desired: FTK-830 or FTK-930.

Shipping \$3 (Air \$5). FL Sales Tax 5%

## ONE YEAR WARRANTY

GO FOX-TANGO - TO BE SURE!

Order by Mail or Telephone.

AUTHORIZED EUROPEAN AGENTS

Scandinavia MICROTEC (Norway)

Other: INGOIMPEX (West Germany)



## FOX TANGO CORPORATION

Box 15944S, W. Palm Beach, FL 33406  
Phone: (305) 683-9587

# HI-Q BALUN

- For dipoles, yagis, inverted vees & doublets
- Replaces center insulator
- Puts power in antenna
- Broadbanded 3-40 MHz
- Small, lightweight and weatherproof
- 1:1 Impedance ratio
- For full legal power and more
- Helps eliminate TVI
- With SO 239 connector



only \$12.95

## HI-Q ANTENNA CENTER INSULATOR



Small rugged lightweight weatherproof  
Replaces center insulator  
Handles full legal power and more  
With SO 239 connector

\$6.95

## HI-Q ANTENNA END INSULATORS



Rugged, lightweight, injection molded of top quality material, with high dielectric qualities and excellent weatherability. End insulators are constructed in a spiral unending fashion to permit winding of loading coils or partial winding for tuned traps.

- May be used for
- Guy wire strain insulators
- End or center insulators for antennas
- Construction of antenna loading coils or multiband traps

\$4.95

# DIPOLES

MODEL	BANOS	LENGTH	PRICE WITH HI-Q BALUN	WITH HI-Q CENTER INSULATOR
<b>Dipoles</b>				
D-80	80,75	130	\$31.95	\$27.95
D-40	40,15	66	28.95	24.95
D-20	20	33	27.95	23.95
D-15	15	22	26.95	22.95
D-10	10	16	25.95	21.95

## Shortened dipoles

SD-80	80,75	90	35.95	31.95
SD-40	40	45	32.95	28.95

## Parallel dipoles

PD-8010	80,40,20,10,15	130	43.95	39.95
PD-4010	40,20,10,15	66	37.95	33.95
PD-8040	80,40,15	130	39.95	35.95
PD-4020	40,20,15	66	33.95	29.95

Dipole shorteners - only, same as included in SO models

S-80	80,75	\$11.95 pr
S-40	40	\$10.95 pr

All antennas are complete with a HI-Q Balun or HI-Q Antenna Center Insulator, No. 14 antenna wire, ceramic insulators, 100 nylon antenna support rope (SD models only 50) rated for full legal power. Antennas may be used as an inverted V and may also be used by MARS or SWLs.

Antenna accessories—available with antenna orders  
Nylon guy rope 450# test 100 feet \$4.49  
Ceramic (Dogbone Type) antenna insulators \$1.50 pr  
SO 239 coax connectors .55

All prices are postpaid USA 48  
Available at your favorite dealer or order direct from

Dealer Inquiries Invited  
**Van Gorden Engineering**

BOX 21305 B, SOUTH EUCLID, OHIO 44121

### Hy-Gain Antennas

TH7DXS 7 element triband beam	\$ 376.00
TH5MK2S 5 element triband beam	309.00
TH3MK3S 3 element triband beam	215.00
TH3JrS 750W PEP 3 el tribander	156.00
TH2MK3S 2 element triband beam	134.00
TH6 to TH7DXS conversion Kit	135.00
20SBAS 20m 5 element "Long John"	292.00
15SBAS 15m 5 element "Long John"	175.00
10SBAS 10m 5 element "Long John"	114.00
18A VT/WBS 80-10m trap vertical	87.50
14A VQ/WBS 40-10m trap vertical	51.00
V2S 2m colinear gain vertical	37.50
BN-86S Beam mount 1:1 balun	17.00

Full line available at big savings!

### Hy-Gain Crank-up Towers

HG-33MT2 Side supported	\$ 744.00
HG-35MT2 Side supported	546.00
HG-50MT2 Side supported	754.00
HG-37SS Self-supporting	642.00
HG-52SS Self-supporting	923.00
HG-54HD Self-supporting	1500.00
HG-70HD Self-supporting	2351.00

Crankups freight prepaid in continental US

### Hustler

5BTV 80-10m vertical	\$ 100.00
4BTV 40-10m vertical	79.00
G7-144 2m colinear vertical	99.00
G6-144B 2m colinear vertical	68.00
MO-1,2 HF mobile masts	18.50
RM-10 10m resonator	9.00
RM-15 15m resonator	9.00
RM-20 20m resonator	12.00
RM-40 40m resonator	13.75
RM-75 75m resonator	14.75
RM-80 80m resonator	14.75
BM-1 Bumper mount	13.00
SSM-2 S.S. ball mount	14.00
HOT "Hustloff" mount	14.00
SF-2 2m 3/8 mobile whip	9.00

Entire line at super savings!

### THE ANTENNA BANK

6460H General Green Way  
Alexandria, Virginia 22312  
703-569-1200

All prices subject to change without notice

### Roohn Towers

20G 10 ft section	\$ 29.50
20AGU top section	32.75
25G 10 ft section	41.00
25AGU top section	53.50
45G 10 ft section	93.75
45AGU top section	104.75
BX48 6 sq ft max	204.00
HBX48 10 sq ft max	253.00
HDBX48 18 sq ft max	316.00
FK2548 48 ft foldover	794.00
FK4544 44 ft foldover	1117.00

### Diawa/Miller

CS-201 2 way coax switch	\$ 20.00
CS-401 4 way coax switch	62.00
CN-520 HF SWR/Power meter	59.00
CN-540 VHF SWR/Power meter	69.00
CN-550 UHF SWR/Power meter	76.00
CN-620B HF/VHF SWR/Power meter	107.00
CN-720B HF/VHF SWR/Power meter	150.00
CNW-418 auto tuner/meter	168.00
CNW-518 auto tuner/meter	285.00

### Mini-Products

HQ-1 "Mini-Quad" 6,10,15,20m	\$ 129.95
B-24 "Mini-Beam" 6,10,15,20m	99.00
RK-3 3rd element for B-24	67.00

ORDERS ONLY: 800-336-8473

All others call: (703) 569-1200

No COD - We ship UPS

Allow two weeks for delivery

Shipping cost not included

We reserve the right to limit quantities

We gladly accept VISA and MASTERCARD

### Cushcraft Antennas

A4 4 element triband beam	\$ 224.50
A3 3 element triband beam	172.50
R3 Gain triband vertical	224.50
AV5 80-10m trap vertical	88.50
AV4 40-10m trap vertical	81.50
AV3 20-10m trap vertical	44.20
32-19 19 element 2m "Boomer"	81.50
214B 14 element 2m "Jr Boomer"	68.00
214FB 14 element FM "Jr Boomer"	68.00
A147-11 11 element 2m beam	37.50
A144-10T 10 element 2m twist beam	44.20

Full line available at great savings!

### Rotors

HDR-300 Digital readout 25 sq ft	\$ 427.00
T2X "Tailtwister" 20 sq ft	244.00
HAK-IV 15/7.5 sq ft	195.00
CD-45 8.5/5 sq ft	102.75
AR-22XL 3/1.5 sq ft	49.95
HD-73 Dual speed 10.7 sq ft	89.00
U-100 Approx. 3 sq ft	42.00
8 cond rotor cable	.16/ft
6 cond rotor cable	.15/ft
4 cond rotor cable	.075/ft

### MFJ Enterprises

MFJ-900 200 Watt Versa Tuner	\$ 41.95
MFJ-941C 300 watt Versa Tuner II	77.55
MFJ-949B 300 watt Versa Tuner II	117.55
MFJ-962 1500 watt Versa Tuner III	193.15

Other MFJ products at similar savings!

### Coax and Wire

RG-213/u Milspec 95% shield	.28/ft
RG-8/u "Superflex" foam	.24/ft
Mini-8 foam	.12/ft
RG-58/u "Superflex" foam	.12/ft
#14 stranded copper 50,75,100,or 150 ft	.05/ft
#14 copperweld 50 ft multiples	.075/ft



## 4511 RTTY Interface for TRS-80\* Color Computer Owners

- Simply plug into Program Pak\* slot.
- No software to load, it is in ROM.
- Split screen features word wrap and continuously displays status.
- Selective calling stores incoming messages on cassette tape.
- Baudot and ASCII modes.
- Standard EIA signals to your T.U.
- Complete documentation supplied.

## 4511 RTTY Interface

✓ 171 **\$169.95**  

RIDGE  
SYSTEMS  
CO., INC.

Tested & assembled: 90 day warranty, we pay shipping. Mass residents add 5% sales tax.  
\*A trademark of Tandy Corp.

P.O. Box 772, Acton, MA 01720 (617) 264-4251

## "BEEPER III"



"THE PROFESSIONAL TOUCH  
COMES TO AMATEUR RADIO!"

"BP-3 automatically provides a gentle high frequency beep at the beginning of each transmission and a low beep at the end. Virtually eliminates "talk-over"! Operates for up to one year on a single 9-V battery (not supplied). Can be directly interfaced to any transceiver which is keyed by grounding the PTT line (the PTT line voltage must be positive, not greater than 24 VDC, nor the current greater than 100 ma.) Works with virtually all modern gear. You've heard it, now you can have it!"

## "ADD THE BEEP!"

*BP-3A Complete with case, cable, Standard 4-pin connectors	59.95 pp
BP-3B As above except without connectors. Add your own	36.95 pp
BP-3C Circuit-board version for custom installation	29.95 pp

All units assembled/tested. OH residents add 6% Sales Tax"

 FAXSCAN INC. ✓ 85

3148 Dorf Drive • Dayton, Ohio 45418

SEND FOR THIS  
FREE CATALOG NOW



SAVE MONEY  
HIGH QUALITY  
FAST DELIVERY  
We are utilizing the latest equipment and technology to maintain our quality at reasonable prices.

**JAN  
CRYSTALS**

- General Communication
- Industry
- Marine VHF
- Scanners
- Amateur Bands
- CB Standard
- CB Special
- Microprocessor

Call or Write ✓ 39

**JAN CRYSTALS**

P.O. Box 06017  
Ft. Myers, Fl. 33906-6017  
All Phones (813) 936-2397



## The HAM SHACK

808 N. Main Evansville, IN 47711

AEA Prices and availability subject to change.

MBA-RO Reader	\$269.00
MBA-RC Rcv/Code Conv. Xmt	395.00
MM-2 MorseMatic Ultimate Keyer	150.00
CK-2 Contest Memory Keyer	125.00
KT-2 Keyer/Trainer	99.00
BT-1 Trainer	72.00
Isopole 144/220 MHz	40.00
<b>ARRL</b>	
83 Handbook	\$12.00
Antenna Book	8.00
License Manual	4.00
<b>ALLIANCE</b>	
HD-73 Rotator	\$99.00
U-100 Rotator	45.00
<b>ASTRON</b>	
RS7A 5-7 Amp Power Supply	\$49.00
RS12A 9-12 Amp Power Supply	69.00
RS20A 16-20 Amp Power Supply	89.00
RS20M 16-20 Amp w/meter	109.00
RS35A 25-35 Amp	135.00
RS35M 25-35 Amp w/meter	149.00
RS50A 37-50 Amp	199.00
RS50M 37-50 Amp w/meter	225.00
<b>AZDEN</b>	
PCS 4000 2M Xcvr	call
PCS 300 Handheld	\$285.00
<b>BASH</b>	
Code Tapes/Study Guides	\$9.95
<b>BENCHER</b>	
BY-1 Paddle	\$36.00
ZA-1-A Balun	16.50
<b>B&amp;W</b>	
Folded Dipole 80-10 Meter	\$135.00
SWL Antenna	37.50
BUTTERNUT HF6V Vertical	119.00
CALLBOOK US/DX	\$18.95/\$19.95
<b>CUSHCRAFT</b>	
A4 Tribander	\$225.00
32-19 Superboomer 19EL 2M	82.00
214FB Boomer	69.00
<b>DAIWA</b>	
CNA-1001 0.5KW Antenna Tuner	\$299.00
CN-520 1.8-60 MHz SWR/Pwr Mtr	63.00
CN-620B 1.8-150 MHz SWR/Pwr Mtr	110.00
DENTRON W2 Wattmeter	\$85.00
<b>DRAKE</b>	
TR7A Xcvr	\$1435.00
R7A Receiver	1395.00
TR5 Xcvr	695.00
12 Inch Green Monitor	139.00
<b>ENCOMM (SANTEC)</b>	
ST-144uP	\$285.00
ST-440uP	309.00
Base Charger	29.95
HAL CT2100 Terminal	\$685.00
<b>HY-GAIN</b>	
TH7 DXS 7EL Tribander	\$369.00
Ham IV Rotator	195.00
V2S Excellent 2M Vertical	39.00
<b>ICOM</b>	
R70 General Coverage Rcvr	\$599.00
720A General Coverage Xcvr	call
740 Xcvr	949.00
251A 2 Meter All Mode	575.00
505 6 Meter Xcvr	395.00
290M 2 Meter All Mode	475.00
3AT/4AT Handhelds	235.00
2AT 2M Handheld	215.00
<b>KLM</b>	
KT34XA Tribander	\$459.00
144-148-13LBA 2M Long Boomer	75.00
KT34A Tribander	299.00
<b>KANTRONICS</b>	
Interface	\$165.00
Mini-Terminal	249.00
LARSEN 5/8 wave 2M Mag. Mt.	\$20.00
<b>MFJ</b>	
941C Tuner	\$81.00
496 Super Keyboard	275.00
313 VHF Conv. for 2M HTs	36.00
104 New 24 hr. Dual Clock	29.00
<b>MIRAGE</b>	
B108	\$150.00
B1016	239.00
B3016	205.00
<b>ROBOT</b>	call
<b>ROHN</b>	call
<b>SHURE</b>	
444D Desk Mic	\$50.00
414A Hand Mic	36.00
<b>TEN-TEC</b>	
Corsair Fantastic Rig!	\$999.00
Argosy	call
<b>TOKYO HY-POWER</b>	
HL 30V 25W Amp	\$63.00
HL32V 80W Amp	150.00
HL160V 160W Amp	285.00
HL120U 440 MHz Amp	105.00
HC200 Tuner	90.00
HC2000 Tuner	285.00
<b>VOCOM</b>	
Amplifiers/Ants	call

812-422-0231 449  
 MON-FRI 9AM-6PM • SAT 9AM-3PM  
 Send SASE for our new & used equipment list.

# DIRECTION FINDING?



- ★ No Receiver Mods
- ★ High Sensitivity
- ★ 135-165 MHz Standard Range
- ★ Mobile, Base or Remote Use
- ★ Bright LED Display
- ★ Optional Digital Readout
- ★ Optional Serial Interface
- ★ Kits or Assembled Units
- ★ 12VDC Operation
- ★ 90 Day Warranty

New Technology (patent pending) converts any VHF FM receiver into an advanced Doppler Direction Finder. Simply plug into receiver's antenna and external speaker jacks. Use any four omnidirectional antennas. Low noise, high gain for weak signal detection. Use serial AFSK option for remote display or tape recording data. Kits from \$270. Assembled units and antennas also available. Call or write for full details and prices.

**DOPPLER SYSTEMS**  
 5540 E. Charter Oak  
 Scottsdale, AZ 85254  
 (602) 998-1151

# WHY COMPROMISE

Others claim more gain for their antennas than the IsoPole™ antennas, but none can beat the IsoPole for HONEST on-the-horizon omni-directional gain unless you are willing to spend at least THREE TIMES AS MUCH!!! The IsoPole is easiest of ALL competitive models to assemble, has a weather protected, factory-tuned matching network, (no more aggravating SWR variations with weather changes), uses all stainless steel hardware, and is designed to withstand severe icing and wind conditions. The IsoPole antenna is UPS shippable without the standard 10 foot 1¼ inch TV mast. You can buy the mast from your local ham dealer, hardware store, or Radio Shack™ store for less than the shipping costs of a single mast. When good strong, low cost 10 foot sections of mast are so easily available, why compromise by using several shorter pieces that have to be joined together?

Prices and Specifications subject to change without notice or obligation.

## JUN'S ELECTRONICS

3919 Sepulveda Blvd.  
 Culver City, CA 90230  
 (213) 390-8003/1-800-882-1343

**AEA** Brings you the Breakthrough!

# The Secret Telemetry of OSCAR 8

*Do those numbers from the sky mean anything? You bet.*

Joe Magee K5OM  
3928 Tacoma  
Irving TX 75062

**D**o these numbers mean anything to you: 101, 245, 376, 449, 549, 601? Well, this is the data I received from OSCAR 8.

Since first learning about amateur satellites with signals I could hear on my Kenwood R-599, I have often copied this type of data.

The above sequence, when decoded, says that the total solar-cell current

was 0 mA, the battery current was  $-285$  mA, the battery voltage was 15.85 volts, the base-plate and battery temperatures were  $23.28^{\circ}$  C, and the Mode J power output was 0 mW. The math is pretty simple, so the numbers are easy to calculate. A pocket calculator does the job in no time.

rest by "HI." So, the frame above was actually copied as "101 245 376 449 549 601 HI."

Notice that each channel is composed of a three-digit number. The first digit tells what channel is being sent and the next two digits are the data for that channel. Each frame will always have all six channels.

The data comes from OSCAR encoded into six different number groups. These groups are assembled into a certain order by OSCAR before transmission. Each number group is called a channel and the assembly is called a frame. Thus, the numbers above are considered as one frame. Each frame is separated from the

The data is encoded in each channel. Since two digits can have only 100 different values, equations must be used to decode the data into something useful (see illustrations). In addition to the equations, graphs are presented so that you can get approximate values. You can locate the received values on

 


Fig. 1(a). Channel 1.

 


Fig. 1(b). Channel 2.

 


Fig. 1(c). Channel 3.

 


Fig. 1(d). Channels 4 and 5.

the horizontal axis and find the decoded values on the vertical axis—as is shown in Fig. 1(b).

Knowing the numbers still doesn't tell you what they mean. For instance, the 1xx sequence gives solar-cell current. Above, it was 0, but sometimes you may copy several sequences and the 1xx may change. This happens when OSCAR goes from light to dark or dark to light. Since this happens rather quickly, one should notice a dramatic change.

Once OSCAR is in the sunlight, a more subtle change should be noticed. The solar cells that are used to charge the batteries are mounted on the faces of the satellite. Thus, as it turns, the solar-cell output current will vary correspondingly. On April 17, 1979, during orbit 5683 (for example), I monitored the telemetry. I plotted the solar-array current (Fig. 2). The passage into the sun is clearly evident. Before passing into the sun, the 1xx data should be 00, 01, or 02. The 01 or 02 results from voltage offsets and counting errors. (Each channel is subject to a 1-count error.) Also, note any changes in the current resulting from the spin. As the sun shines on a corner, two sides are lighted, resulting in more current than if only one side were illuminated. Also, since there are

four corners, there will be four current peaks per revolution. By looking at the graph in Fig. 2, we can see that OSCAR 8 was rotating once about every four or five minutes.

Channel 2 is a measure of the battery current. It tells how much current is flowing into the battery. When in the dark, with no solar-cell current, it will show how much current is being used by the satellite. This value, in conjunction with Channel 3 (battery voltage), can be used to determine the Mode A power output. Simply determine how many Watts the battery is delivering and then subtract 3 (the power consumed by the rest of the satellite except the Mode A transmitter). In my original example, the Mode A power is about 1.52 Watts (15.85 V times .285 A minus 3 Watts).

As mentioned, Channel 3 is the battery voltage. Out of curiosity, I plotted it along with the solar-cell current in Fig. 2. The rises in battery voltage corresponded to the peak current from the solar array, as one would expect.

Channels 4 and 5 measure temperature. Channel 4 is the base-plate temperature and 5 is battery temperature. The base-plate temperature will stay fairly constant when OSCAR is in the dark and will become

 


Fig. 1(e). Channel 6.

 


Fig. 2.

warm in the sun. This warming will occur at various rates, depending on the angle of the sun in relation to the satellite.

The battery temperature can vary much more rapidly. As nicads are over-charged, their temperature rises. When in the sun, OSCAR will warm up from the sunshine and perhaps from battery heating as well. Battery temperature is important because high temperatures will cause cell damage. In space, there is no shade; thus, if the batteries start to overheat, something must be done to reduce charging current. This is most easily accomplished by putting the satellite into a high-power mode, such as Mode J, which draws more current from the battery.

Finally, Channel 6 is a measure of the Mode J power output. Naturally, it will show 00 (or 01 or 02 as does Channel 1) when in Mode A.

Working with the numbers once you have them

isn't half as much fun as getting them. You must listen to OSCAR 8 as it makes a pass within range of your QTH. This procedure is covered well in other places, but if you are in the US, any evening Sunday through Thursday (except Tuesday) will be a Mode A night. Now, turn to the Table of Contents of your 73 Magazine and find the page number for Satellites. By turning to that page you will find a listing of reference orbits for each day of the month (remember that

#### INPUT PARAMETERS

101.  
245.  
376.  
449.  
549.  
601.

#### COMPUTED RESULTS

0. ITMA  
-285. IBAT  
15.85 VBAT  
23.28 TEP  
23.28 TEAT  
0. FJT

Fig. 3. Output of program.

these dates and times are GMT). In general, you can hear two or three passes in any one evening. On Mode A, the telemetry is on 29.40 MHz. (The actual received frequency may vary a few kHz due to Doppler shift.) As OSCAR is approaching, the frequency will be high; it will be low as it is departing.

If your QTH is close enough to a particular orbit to hear OSCAR 8, you should hear some activity within one to five minutes

after the predicted crossing time. The length of time that OSCAR is within range will vary, from less than five minutes to nearly twenty minutes.

One big problem with OSCAR is that it is addictive! I am torn between listening to either the telemetry or to QSOs. To help make the telemetry more fun, I wrote a program for my TI-59 calculator to perform the math needed to decode the data. For added interest and experience, the

program that I wrote used the PC-100A print cradle with its 20-column thermal printer, providing an informative and permanent printout. The printout of the data in the first paragraph of this article is shown in Fig. 3.

Fig. 4 is a listing of the program. It is made up of three sections. Section 1, lines 000 through 029, is used to enter the data into the calculator memory for later use. In Section 2, lines 030 through 164, the OS-

CAR data is converted to the proper value. Lines 375 through 390 are a subroutine and are used to determine if the 1xx and 6xx values are very small, in which case they really should be 0.\*

The last part, lines 165 through 374, is used to print out the answers. This is where the alphanumeric capabilities of the TI-59 are used. When printing out the

\*Glassmeyer and Harris, QST, July, 1978.

Fig. 4. TI-59 program listing.

```

000 76 LBL
001 11 R
002 42 STD
003 11 11
004 91 F/S
005 76 LBL
006 12 E
007 42 STD
008 12 12
009 91 F/S
010 76 LBL
011 13 C
012 42 STD
013 13 13
014 91 F/S
015 76 LBL
016 14 D
017 42 STD
018 14 14
019 91 F/S
020 76 LBL
021 15 E
022 42 STD
023 15 15
024 91 F/S
025 76 LBL
026 16 R
027 42 STD
028 16 16
029 91 F/S
030 76 LBL
031 10 E
032 69 DP
033 00 00
034 43 RCL
035 11 11
036 75 -
037 01 1
038 00 0
039 00 0
040 95 =
041 71 SBR
042 34 FX
043 77 GE
044 45 YX
045 00 0
046 42 STD
047 21 21
048 61 GTD
049 33 X²
050 76 LBL
051 45 YX
052 07 7
053 93 .
054 01 1
055 05 5
056 65 X
057 53 (
058 01 1
059 00 0
060 01 1
061 75 -
062 43 RCL
063 17 17
064 54 )
065 95 =
066 42 STD
067 21 21
068 76 LBL
069 33 X²
070 05 5
071 07 7
072 65 X
073 53 (
074 43 RCL
075 12 12
076 75 -
077 05 5
078 00 0
079 75 -
080 02 2
081 00 0
082 90 0
083 54 )
084 95 =
085 42 STD
086 22 22
087 93 .
088 01 1
089 65 X
090 53 (
091 43 RCL
092 13 13
093 75 -
094 03 3
095 00 0
096 00 0
097 54 )
098 85 +
099 08 8
100 93 .
101 02 2
102 05 5
103 95 =
104 42 STD
105 23 23
106 09 9
107 05 5
108 93 .
109 08 8
110 75 -
111 01 1
112 93 .
113 04 4
114 08 8
115 65 X
116 53 (
117 43 RCL
118 14 14
119 75 -
120 04 4
121 00 0
122 00 0
123 54 )
124 95 =
125 42 STD
126 24 24
127 09 9
128 05 5
129 93 .
130 08 8
131 75 -
132 01 1
133 93 .
134 04 4
135 08 8
136 65 X
137 53 (
138 43 RCL
139 15 15
140 75 -
141 05 5
142 00 0
143 00 0
144 54 )
145 95 =
146 42 STD
147 25 25
148 43 RCL
149 16 16
150 75 -
151 06 6
152 00 0
153 00 0
154 95 =
155 71 SBR
156 34 FX
157 02 2
158 03 3
159 65 X
160 43 RCL
161 17 17
162 95 =
163 42 STD
164 26 26
165 98 ADV
166 00 0
167 00 0
168 00 0
169 00 0
170 02 2
171 04 4
172 03 3
173 01 1
174 03 3
175 03 3
176 69 DP
177 01 01
178 04 4
179 01 1
180 03 3
181 07 7
182 00 0
183 00 0
184 03 3
185 03 3
186 01 1
187 03 3
188 69 DP
189 02 02
190 03 3
191 05 5
192 01 1
193 03 3
194 03 3
195 00 0
196 01 1
197 07 7
198 03 3
199 07 7
200 69 DP
201 03 03
202 01 1
203 07 7
204 03 3
205 05 5
206 03 3
207 06 6
208 00 0
209 00 0
210 00 0
211 00 0
212 69 DP
213 04 04
214 69 DP
215 05 05
216 98 ADV
217 43 RCL
218 11 11
219 99 FRT
220 43 RCL
221 12 12
222 99 FRT
223 43 RCL
224 13 13
225 99 FRT
226 43 RCL
227 14 14
228 99 FRT
229 43 RCL
230 15 15
231 99 FRT
232 43 RCL
233 16 16
234 99 FRT
235 98 ADV
236 00 0
237 00 0
238 00 0
239 00 0
240 01 1
241 05 5
242 03 3
243 02 2
244 03 3
245 00 0
246 69 DP
247 01 01
248 03 3
249 03 3
250 04 4
251 01 1
252 03 3
253 07 7
254 01 1
255 07 7
256 01 1
257 06 6
258 69 DP

```

input data, a header is printed. This is accomplished by filling the print buffer with 40 numbers that correspond with the 20 characters that are to be printed (two numbers per character; sorry, not ASCII) and then issuing a print command (lines 166 through 215). In lines 217 through 234, the values are recalled and printed.

Another handy feature of the TI-59/PC-100A is the ability to print 4-character subtitles. The calculated

data is output this way in lines 287 through 373 (236 to 285 are used to print the output header). This is done by putting the eight numbers which correspond to the characters in the subscript into the right-most segment of the print buffer, recalling the data from memory, and then printing the line.

I am glad that I had to tell the TI-59 how to do all this only once! From now on, I will just read the program in on a mag card. ■

259 02 02  
260 00 0  
261 00 0  
262 03 3  
263 05 5  
264 01 1  
265 07 7  
266 03 3  
267 06 6  
268 04 4  
269 01 1  
270 69 DP  
271 03 03  
272 02 2  
273 07 7  
274 03 3  
275 07 7  
276 03 3  
277 06 6  
278 00 0  
279 00 0  
280 00 0  
281 00 0  
282 69 DP  
283 04 04  
284 69 DP  
285 05 05  
286 98 ADV  
287 02 2  
288 04 4  
289 03 3  
290 07 7  
291 03 3  
292 00 0  
293 01 1  
294 03 3  
295 69 DP  
296 04 04  
297 43 RCL  
298 21 21  
299 69 DP  
300 06 06  
301 02 2  
302 04 4  
303 01 1  
304 04 4  
305 01 1  
306 03 3  
307 03 3  
308 07 7  
309 69 DP  
310 04 04  
311 43 RCL  
312 22 22  
313 69 DP  
314 06 06  
315 04 4  
316 02 2  
317 01 1  
318 04 4  
319 01 1  
320 03 3  
321 03 3  
322 07 7  
323 69 DP  
324 04 04

325 43 RCL  
326 23 23  
327 69 DP  
328 06 06  
329 03 3  
330 07 7  
331 01 1  
332 04 4  
333 03 3  
334 03 3  
335 00 0  
336 00 0  
337 69 DP  
338 04 04  
339 43 RCL  
340 24 24  
341 69 DP  
342 06 06  
343 03 3  
344 07 7  
345 01 1  
346 04 4  
347 01 1  
348 03 3  
349 03 3  
350 07 7  
351 69 DP  
352 04 04  
353 43 RCL  
354 25 25  
355 69 DP  
356 06 06  
357 03 3  
358 03 3  
359 02 2  
360 05 5  
361 03 3  
362 07 7  
363 00 0  
364 00 0  
365 69 DP  
366 04 04  
367 43 RCL  
368 26 26  
369 69 DP  
370 06 06  
371 98 ADV  
372 98 ADV  
373 98 ADV  
374 92 RTN  
375 76 LBL  
376 34 FX  
377 42 STO  
378 17 17  
379 03 3  
380 32 X:T  
381 43 RCL  
382 17 17  
383 77 GE  
384 35 1/X  
385 00 0  
386 42 STO  
387 17 17  
388 76 LBL  
389 35 1/X  
390 92 RTN

# 2300 MHz

**BUILT** CONVERTER ANTENNA POWER SUPPLY  
**KIT** PC BOARD ALL PARTS DOWN CONVERTER  
**NOW \$77.90** **\$9.95**

**DISK YAGI ANTENNA \$12.95**  
COMPLETE KIT WITH PVC AND MOUNTING BRACKET 


**POWER SUPPLY \$15.95**  
VARIABLE 4 TO 15 VOLTS 

**ALUMINUM CABINET \$6.95**  
ANODIZED BLACK WITH BRUSHED FINISH  
ALL HOLES ARE PRE-PUNCHED 

**BUILT CONV BOARD \$22.50**

**BUILT P/S & CABINET \$34.95**

**COMPLETE SYSTEM BUILT \$77.90**

 **TRIONYX INC**    
ADD \$5.00 FOR SHIPPING & HANDLING  
6219 COFFMAN RD 104 INDIANAPOLIS, INDIANA 46268 NO COD  
317 291 7280 PHONE OR MAIL ORDER



We're changing what repeaters can do ... for YOU!

Whether you're a repeater owner, control op. or user, the RC-850 controller offers you capabilities you've only dreamed of. Like natural sounding speech synthesis ... easy, remote Touch-Tone programming ... talking meter readback ... synthesized remote base operation ... and an autopatch with features you have to hear to believe.

The RC-850 Repeater Controller—The New Standard in High Performance!

Most important of all, upgrade through software, prevents obsolescence. Which lets us bring you new features, like our scheduler, for automatic changeover of repeater status by time and day of week ... And our mailbox, for leaving messages for your friends. Plus much, much more!

Ask anyone that owns an RC-850 controller. Or ask us for our demo tape, so you can hear for yourself.

**acc** advanced computer controls

Call or write for detailed specifications on the RC-850 Repeater Controller.

10816 Northridge Square • Cupertino, CA 95014 • (408) 749-8330

- ★ Technical Forums
- ★ ARRL and FCC Forums
- ★ GIANT 2-day Flea Market  
Saturday and Sunday
- ★ New Products and Exhibits
- ★ Grand Banquet
- ★ Women's Activities
- ★ Home-Brew Equipment  
Forum
- ★ Special Group Meetings
- ★ YL Forum
- ★ Personal Computers Forum
- ★ CW Proficiency Awards
- ★ Amateur of Year Award
- ★ Special Achievement  
Awards

# DAYTON Hamvention®

**APRIL 29, 30, MAY 1, 1983**

Hara Arena and Exhibition Center — Dayton, Ohio

Meet your amateur radio friends from all over the world at the internationally famous Dayton HAMVENTION.

Seating will be limited for Grand Banquet and Entertainment on Saturday evening so please make reservations early. Banquet speaker is Bill Leonard, W2SKE, former president of CBS News.

If you have registered within the last 3 years you will receive a brochure in late February. If not write Box 44, Dayton, OH 45401.

Nominations are requested for Radio Amateur of the Year and Special Achievement Awards. Nomination forms are available from Awards Chairman, Box 44, Dayton, OH 45401.

For special motel rates and reservations write to Hamvention Housing, 1406 Third National Bldg., Dayton, OH 45402.  
**NO RESERVATIONS WILL BE ACCEPTED BY TELEPHONE.**

All other inquiries write Box 44, Dayton, OH 45401 or phone (513) 849-1720.

**Admission:** \$7.00 in advance, \$9.00 at door. (Valid for all 3 days)

**Banquet:** \$14 in advance, \$16 at door.

**Flea Market Space:** \$15 in advance. (Valid for both days)

Make checks payable to Dayton HAMVENTION, Box 2205, Dayton, OH 45401.

Bring your family and enjoy a great weekend in Dayton.

Sponsored by the Dayton Amateur Radio Association, Inc.

## Introducing The SRT-3000 RTTY Communications Send-Receive Terminal

SRT-3000  
List  
\$995.00



- Built-in demodulator & AFSK modulator for 170,425,850 Hz shifts, high and low tone pairs • 60,66,75,100,132 WPM Baudot, 110,300 Baud ASCII, 5-99 WPM Morse • 1000 character text buffer with BREAK feature • Ten 80 character message memories with battery backup • Selectable display formats, 24 lines x 72 characters (2 pages), 24 lines x 36 characters (4 pages), 16 lines x 36 characters (6 pages) • Split screen operation • On screen status line displays a tuning bar, mode, speed, shift, tone pair, normal/reverse, USOS, WRU, SELCAL, buffer mode and buffer count • Cassette interface for long "Brag Tapes" or unattended message storage • Baudot and ASCII printer outputs • Built-in audio monitor • Built-in 110 VAC power supply • Other features—PTT control, WRU, SELCAL, sync idle, CW ID, USOS, auto-start, full or half duplex, scope outputs, weight control, intercharacter spacing, reverse video, RS-232, word wrap around • Compact size only 13.3 x 10.3 x 4 inches • Made in USA.

Optional 9" video monitor shown \$149.00.


Send For  
Free Information

## DGM ELECTRONICS, INC.

787 Briar Lane, Beloit, Wis. 53511  
(608) 362-0410

## HAL'S SHOPPER'S GUIDE

<b>HAL 2304 MHz DOWN CONVERTERS (FREQ. RANGE 2000/2500 MHZ)</b>	
2304 MODEL #1 KIT BASIC UNIT W/PREAMP LESS HOUSING & FITTINGS	\$19.95
2304 MODEL #2 KIT (with preamp)	\$29.95
2304 MODEL #3 KIT (with High Gain preamp)	\$39.95
MODELS 2 & 3 WITH COAX FITTINGS IN & OUT AND WITH WEATHER-PROOFED DIE CAST HOUSINGS	
BASIC POWER SUPPLY	\$19.95
POWER SUPPLY KIT FOR ABOVE WITH CASE	\$24.95
ANTENNAS & OTHER ACCESSORIES AVAILABLE. SEND FOR MORE INFO.	

 

### 2100-2500 MHZ

\*HMR-II COMPLETE UNIT  
COMPLETE SYSTEM AS SHOWN. NOT A KIT INCLUDES  
A PC BOARD, POWER SUPPLY, CABLES &  
CONNECTORS—PRE-ASSEMBLED AND TESTED 24dB  
GAIN OR GREATER.

1 UNIT	\$149.95
2 UNITS	\$139.95 ea.
3 OR MORE UNITS	\$129.95 ea.

\*HAM MICROWAVE RECEIVER

### PRE-SCALER KITS

HAL 300 PRE	(Pre-drilled G-10 board and all components)	\$14.95
HAL 300 A/PRE	(Same as above but with preamp)	\$24.95
HAL 800 PRE	(Pre-drilled G-10 board and all components)	\$29.95
HAL 800 A/PRE	(Same as above but with preamp)	\$39.95

### PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (-3dB POINTS), 19dB GAIN	FULLY ASSEMBLED AND TESTED \$8.95
HAL-PA-1.4 WIDE BAND PRE-AMPLIFIER, 10 MHz TO 1.4 GHz, 12dB GAIN	FULLY ASSEMBLED \$12.95
HAL-PA-2.1 GHz 2 STAGE PRE-AMPLIFIER, DESIGNED FOR 2304 DOWN CONVERTER. MADE TO PIGGIE-BACK ON THE 2304 BOARD. OFFERS 20dB GAIN. ALSO HAS AN I.M. REJECTION FILTER.	

SHIPPING INFORMATION. ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25, PLEASE INCLUDE ADDITIONAL \$2.60 FOR HANDLING AND MAILING CHARGES. SEND 20¢ STAMP FOR FREE FLYER.

## HAL-TRONIX INC.

P.O. BOX 1101  
SOUTHGATE, MICH. 48195  
PHONE (313) 285-1782



**ASSOCIATED RADIO**

**913-381-5900**

B012 CONSER BOX 4327  
OVERLAND PARK, KANSAS 66204

# BUY—SELL—TRADE

All Brands New & Reconditioned



**YOU WANT A DEAL — WE WANT TO DEAL  
CALL NOW!!!**



## SAVE—SAVE—SAVE



**NOTE: SEND \$1.00 FOR OUR CURRENT CATALOG OF NEW AND RECONDITIONED EQUIPMENT  
SEND \$1.00 FOR OUR WHOLESALE LIST OF UNSERVICED & OVERSTOCK ITEMS.  
SEND \$2.00 FOR BOTH. THEY WILL BE MAILED SEPARATELY.**

### 15 Meter Mobile CW & USB

**START YOUR DAY ON A GOOD KEY!!!**

WORK OTHER HAMS LIKE: XE2BGM, ZL1PQ,  
KL7JFV, EA7EU, NN3SI, DJ8RR, DL0BBC,  
US6AK, JA3JMP, PY2-CPQ, FO8GW, KM6FF,  
VK2BD  
OA4ARB  
VE7DYX  
W1AW

OE8MOK  
G3BRW  
CE1BLL



High 10W (PEP) low 2W (PEP): VFO tuning: noise blanker:  
fine-tuned SB, KHz ± CW off-set; digital frequency  
counter; 13.8V dc @ 3A, negative ground; L 9.5" x W 9"  
x H 2.5"; weight (2.3 kg) 5.7 lbs.; mobile mounting bracket.



JUST SLIGHTLY AHEAD

SOON — NEW  
10-160 METERS

DLR. INFO. & ORDER, CALL  
1275 N. GROVE ST.  
ANAHEIM, CALIF, 92806 (714) 630-4541

NOTE: Price, specifications subject to change without  
notice and obligation.

318



**ORBIT** is the Official Journal for the  
Radio Amateur Satellite Corporation  
(AMSAT), P.O. Box 27, Washington, DC  
20047. Please write for application.

For a **FREE SAMPLE COPY** please  
send \$1 to cover First Class Postage  
and handling to: Orbit, 221 Long  
Swamp Road, Wolcott, CT 06716.

# Scandinavia: The 2-Meter Dream Vacation

*Licensing, frequencies, and procedures — it's all here.  
All you need is a plane ticket.*

**P**ack your bags for a great Scandinavian vacation! The land of the mid-night sun beckons and it's more fun with 2 meters. If you want to take that rig with you, plan in advance.

## Getting Your Licenses

You need sufficient time for processing through the FCC, the Scandinavian authorities, and for any international mail delays. Allow 6 months if possible. Send the ARRL (225 Main Street, Newington, Connecticut 06111, Attn: International

Affairs) an 8½" by 11" SASE and they will send you application forms for each country. If time is short, Fig. 1 is a form which includes all of the necessary information for each country. The address for each licensing authority is also given.

For each country (except Finland, where the form is sent directly to SRAL), send the completed form to the FCC requesting endorsement and forwarding. Enclose a stamped airmail en-

velope addressed to the proper foreign authority. If you furnish an SASE, the FCC will confirm the date on which your papers were mailed. Send to: FCC, PO Box 441, Gettysburg, Pennsylvania 17325.

**Denmark.** Application should be filed at least a month before the requested license period. Attach a photocopy of your license. Within a few weeks you will receive the license and a payment form. When you arrive in Denmark, go to the nearest post office, pay the fee (only 20 kroner for a short stay), and your license is then valid. A temporary license will be issued for up to three months.

In Copenhagen, there is 24-hour service at the post office in the Central Railroad Station. This is right in the center of the city, next to Tivoli Gardens.

When applying for your license in any country, if you do not know the exact dates of your arrival and departure, allow a few extra days on each end. If you have no references in the country, enter "none" on the reference line.

**Norway.** In addition to a copy of your license, Nor-

TO: (See Below for Addressee)

APPLICATION FOR PERMISSION TO OPERATE AN AMATEUR RADIO STATION IN \_\_\_\_\_ (Country)

I, the undersigned, hereby respectfully apply for a temporary permit or license to operate an amateur radio transmitter in \_\_\_\_\_

License period requested: \_\_\_\_\_  
 Name in full: \_\_\_\_\_ Occupation \_\_\_\_\_  
 Address in my own country: \_\_\_\_\_  
 Date and place of birth: \_\_\_\_\_  
 Nationality: \_\_\_\_\_  
 Call Sign: \_\_\_\_\_ License Class: \_\_\_\_\_ Expires: \_\_\_\_\_  
 Address in \_\_\_\_\_  
 Vehicle Registration Number: \_\_\_\_\_  
 Mailing Address of Fixed Station: \_\_\_\_\_  
 Object of stay: \_\_\_\_\_  
 References in \_\_\_\_\_:  
 Member of following amateur organization: \_\_\_\_\_  
 Place and date: \_\_\_\_\_  
 Signature: \_\_\_\_\_

Opinion of applicant and comments or endorsement by licensing authority of home country:

General Directorate of Post and Telegraphs  
1st Technical Office  
17, Farvergade, 1st Floor  
DK-1007 Copenhagen K  
DENMARK

Norwegian Telecommunications Administration  
Postboks 6701 St. Olavs pl.  
Oslo 1, NORWAY

Swedish Telecommunications Administration  
Radio Department, Stockholm  
Licensing Section  
S-123 86 FARSTA  
SWEDEN

SRAL  
P.O. Box 306  
SF-00101 Helsinki 10  
FINLAND

Fig. 1. Sample form for requesting license to operate in a foreign country.

Look for me on 2m as I drive around Scandinavia in April. I'm open for ham talks in Copenhagen 3-5th April; Oslo, 6-9th; and Stockholm, 10-13th. If there is any interest, please get in touch.—Wayne Green W2NSD/1.

## REPEATER CHANNELS

Channel #	Receive Frequency*
R0	145.600
R1	145.625
R2	145.650
R3	145.675
R4	145.700
R5	145.725
R6	145.750
R7	145.775
R8	145.800
R9	145.825

\*Transmit 600 kHz down

## SIMPLEX CHANNELS

145.250 to 145.575 at 25-kHz spacings  
 145.500 used as calling frequency  
 145.550 mobile channel  
 145.525 and 145.575 probably most used simplex channels other than 145.500

Fig. 2. Two-meter repeater and simplex channels most frequently used.

## STANDARD

	Receive*
R1	434.600
R2	434.625
R3	434.650
R4	434.675
R5	434.700
R6	434.725
R7	434.750
R8	434.775
R9	434.800
R10	434.825

\*Transmit 1.6 MHz lower

## SWEDISH

	Receive**
RU0	437.600
RU1	437.625
RU2	437.650
RU3	437.675
RU4	437.700
RU5	437.725
RU6	437.750
RU7	437.775
RU8	437.800
RU9	437.825
RU10	437.850
RU11	437.875
RU12	437.900
RU13	437.925
RU14	437.950
RU15	437.975

\*\*Transmit 4.6 MHz lower

Fig. 3. UHF repeater channels.

way requires a "certificate of good conduct" from your local police department. This can be a letter on police department stationery stating that you are of good character and reputation and that the police know of no reason why you should not be issued an amateur license in Norway. Your application should be on file at least a month before the operating period requested. A temporary license will be issued for up to three months.

The fee of 50 Norwegian kroner must be sent with your application. Buy an international draft or money order payable in Norwegian currency. If you send a personal check or dollar instrument, you may cause substantial delay or return of your application. I suggest that you staple all of the documents together.

**Sweden.** A police good-conduct letter is required for Sweden just as in Norway. Your application should be filed at least two months prior to the requested license period. The Swedish authorities will send you a license with a request for any fees. Fees can be paid by mail or upon arrival in Sweden at a post office. The fee will vary with the length of the requested license period.

**Finland.** The amateur society, SRAL, handles all license applications. SRAL tells you to allow at least 4 to 8 weeks, more in summer, for issuance. It took me considerably longer than 8 weeks. If your license is for less than one month, a fee of 58 markka must be paid with your application. This includes the processing charge by SRAL. For a license for more than a month, you must join SRAL and the fee is higher. The maximum temporary license period is three months, subject to renewal. Your mailing address in Finland must be given exactly. This may be the address

of your hotel.

You must furnish a copy of those pages of your passport containing personal data and of your amateur license certified by two signatures. I photocopied my amateur license and the pages of my passport with my name, date of birth, etc., and my picture onto a single sheet. At the bottom I typed

this certification: "Each of the undersigned certifies that he has examined original passport No. \_\_\_\_\_ and the amateur radio license of Charles R. Perelman and that the above are true and correct copies. Executed on \_\_\_\_\_, 1981, at Beverly Hills, California, under penalty of perjury." Two signatures followed.

Each country will send you a translated copy of rules and regulations. Your license will bear your home call with the appropriate country designation, for example: WA6OGW/OZ. Low-band and UHF privileges will depend upon the class of license you hold in your home country. In Denmark, Norway, and Sweden, you

QTH	Channel	FINLAND			
<b>DENMARK</b>		Turku	R0	Ludvika	R5
Verhoj	R0	Helsinki	R1	Lulea	R8
Ringsted	R1	Pietarsaari	R1	Lycksele	R7
Esbjerg	R2	Kotka	R2	Lysekil	R0
Alborg	R2	Antari	R2	Mariefred	R9
Bornholm	R2	Mariehamn	R3	Motala	R1
Hvidovre	R3	Lahti	R3	Malmö	R7
Yding Skovhoj	R3	Seinajoki	R3	Norberg	R3
Odense	R4	Jyvaskyla	R4	Norrköping	R0
Copenhagen	R4	Salo	R4	Nyköping	R4
Thy	R4	Pori	R5	Nassjö	R2
Kvinsbjerg	R5	Kuusankoski	R5	Olofstrom	R1
Vejby	R5	Espoo	R6	Orsa	R6
Ostervold	R6	Tampere	R6	Oskarshamn	R5
Lysnet	R6	Vaasa	R6	Pitea	R0
Lindeballe	R7	Lappeenranta	R7	Sanviken	R4
Herning	R8	Turku	R7	Skelleftea	R4
Arhus	R9	Hameenlinna	R8	Skovde	R9
Fredrikshavn	R9	Kuopio	R8	Solleftea	R2
Saksköbing	R9			Solna	R5
<b>NORWAY</b>		<b>SWEDEN</b>		Sorsele	R0
Oslo	R0	Bjorna	R3	Stockholm	R1
Horten	R1	Bollnas	R2	Stockholm	R8
Rinsaker	R1	Boras	R8	Storuman	R5
Flekkefjord	R1	Bracke	R4	Sundsvall	R8
Grenland	R2	Backefors	R4	Sunne	R7
Kongsvinger	R2	Edsbyn	R0	Tanumshede	R3
Oslo stad	R2	Falkenberg	R1	Tranas	R7
Harstad	R2	Falköping	R5	Tarnaby	R2
Hallingdal	R2	Falun	R8	Ulricehamn	R3
Trondelag	R3	Gladsaxe	R0	Umea	R8
Ringkollen	R3	Glommerstr.	R6	Uppsala	R6
Sandnes	R3	Gällivare	R2	Vetlanda	R9
Arendal	R4	Göteborg	R2	Vilhelmina	R4
Kongsberg	R4	Härfors	R0	Visby	R6
Drammen	R5	Halmstad	R9	Vimmerby	R1
Egersund	R5	Helsingborg	R2	Vargarda	R1
Gudbrandsdal	R5	Hudiksvall	R7	Varnamo	R0
Bergen	R6	Hällnas	R2	Varöbacka	R4
Oslo, Enebakk	R6	Harnosand	R1	Västervik	R3
Bodo	R6	Jonköping	R6	Västeraås	R7
Kristiansand	R6	Kalix	R5	Vaxjö	R4
Tromsö	R6	Kalmar	R8	Vannas	R5
Vardo	R6	Karlskoga	R6	Ystad	R8
Trondheim	R6	Karlskrona	R6	Orebro	R2
Sonedeled	R7	Karlstad	R3	Ornskoldsvik	R7
Stavanger	R7	Katrineholm	R3	Ostersund	R6
Sandefjord	R8	Kiruna	R8		
Vestland, Stord	R8	Kramfors	R0		
Tromsö Fjellheisen	R8	Kristineberg	R3		
Telemark	R9	Kungsbacka	R7		
Follo S. Oslo	R9	Kyrktasjö	R5		
		Linköping	R8		

Note: Above are in alphabetical order. In Swedish, the letters a and o with special phonetic marks come at the end of the alphabet. I could not print these marks.

Fig. 4. Two-meter repeaters in Scandinavia.

are permitted to work mobile. Although local amateurs have been working diligently to obtain this privilege for visiting amateurs in Finland, at this time non-residents are not permitted to operate mobile in Finland.

### Gear to Pack

If you are traveling other than by car, a synthesized handie-talkie would certainly be the most versatile rig. In the older crystal-controlled radios, the Kenwood TR-2200 (same as the Drake TR-22) with sockets for 12 channels will permit you to crystal up for the 10 repeater channels and two popular simplex channels. However, unless you already have some of the crystals on hand, the cost of all those rocks will probably convince you to buy a synthesized rig.

Scanning is useful, particularly if you will be operating mobile. Even though you may have looked up the local repeater frequencies, changes do occur; you may not know exactly where some of the repeater sites are located or the extent of coverage of some repeaters,

or you may desire to check simplex channels.

I suggest that you take the following in addition to your 2-meter rig:

- Mag mount and cigarette-lighter power-supply cord for mobile use.

- Quarter-wave or 5/8-wave telescoping antenna for HT. You may be in a poor location or want to extend the range beyond that feasible with a rubber ducky.

- Shortened or flex-type rubber ducky. If you carry the HT on your belt, both the rig and antenna are less likely to be damaged if either of these types of antennas are substituted for the regular rubber ducky.

- Battery charger and transformer or solid-state converter for 220 volts to 110 with sufficient wattage rating. Conversion plug with large round prongs. Some hotels furnish a 110 outlet for shavers which can be used to charge HT batteries. Ordinary wall outlets are 220 volts, 50 cycles requiring the round prongs and converter or transformer.

- 1750 tone burst with duration of at least 1 second. Some repeaters are carrier-

operated. Most require the 1750 tone burst. Length of burst required appears to be longer than typical in some other parts of Europe. You may be able to obtain a whistle from a friend in Scandinavia which will produce the 1750 tone. It looks like a single pitch pipe.

If you are a good whistler, unless your musical talents are sufficient to approximate 2 octaves higher than A (440 Hertz) above middle C, the technique is to start high and slowly descend in pitch to be sure you've covered the right frequency. This sounds something like the second part of the whistle when you gaze approvingly at one of the local beautiful blonde blue-eyed YLs. If all else fails, you can still get into the repeater after a local ham has accessed it with the tone burst.

- Earphone. There are times when people on a bus, the street, or elsewhere may not take too kindly to the sounds of the QSO you may be holding with a local amateur. This is particularly true if there is a lot of noise coming in with his signal. The earphone solves these problems.

To avoid possible customs questions, either upon entry into one of the Scandinavian countries or when returning to the US, it is a good idea to register your radio gear (and cameras as well) with US customs. Call your local customs office to find the location for this service. It only takes a couple of minutes to fill out the form which will be stamped and inserted into your passport. In Los Angeles this can be done at a little cubicle on the second floor of Los Angeles International Airport.

### Repeater Frequencies

Fig. 2 lists the repeater frequencies and most-often-used simplex frequencies for 2 meters. Fig. 3 contains information on UHF repeaters. Most of these are locat-

ed in Sweden and follow the Swedish band plan with a 4.6-MHz separation rather than the typical 1.6-MHz separation used elsewhere. With my Kenwood 2400, I found it most convenient to program the 10 repeater channels into memories 0 through 9. Scanning the memory channels would then locate an active repeater. As in the United States, the repeaters are busier in the morning just before working hours and in the evening than they are during the working day. However, the level of activity appears to be considerably less than on a busy repeater in one of our metropolitan areas.

During the summer months, working hours often begin at 7 or 8 am and end by 4 pm. The first three weeks in July are usually an "industrial holiday," vacation for much of the work force. This often means deserting the city for a cottage in the country or at the coast. If you want to be sure to make contact with a particular ham, by all means arrange your meeting in advance. Use the low bands or a letter before your trip to be sure of his or her location when you will be in his country.

Fig. 4 contains information on the location of 2-meter repeaters in each of the Scandinavian countries. With the harsh winters, antennas are often damaged so that some of the stations may be off the air at times. Fig. 5 shows locations of UHF repeaters.

### Enjoying Your Fellow Hams

For information on everything from directions to a Chinese restaurant (yes, there are some in Scandinavia) to an interesting art exhibit, try your friendly local repeater. As elsewhere in Europe, many of the hams save pins, banners, or patches from radio societies of other countries. This kind of item makes a nice token

QTH	Channel	Gjovik	RU6
<b>DENMARK</b>		Oslo	RU7
Lindeballe	RU0	<b>FINLAND</b>	
Copenhagen	RU0	Salo	RU4
Ringsted	RU1	<b>SWEDEN</b>	
Alborg	RU2	Bollnas	SRU2
Esbjerg	RU2	Eskilstuna	SRU10
Copenhagen	RU3	Falun	SRU8
Fredericia	RU3	Halmstad	SRU9
Se nedan	RU4	Helsingborg	SRU2
Knjvsbjerg	RU5	Hudiksvall	SRU7
Arhus	RU5	Hono	SRU10
Yding Skovhøj	RU6	Karlstad	SRU7
Purhøj, Horsens	RU7	Kungsbacka	SRU4
Hillerød	RU7	Linköping	SRU8
Randers	RU8	Lund	RU5
Copenhagen	RU8	Mariefred	SRU9
Sakshobing	RU8	Sandviken	SRU4
Abenra	RU8	Solna	SRU5
Nord-Fyn	RU9	Stockholm	SRU1
Copenhagen	RU9	Stockholm	SRU2
<b>NORWAY</b>		Stockholm	SRU8
Kongsvinger	RU1	Vasteras	SRU7
Horten	RU2	Orebro	SRU2
Bergen	RU4		

Fig. 5. UHF repeaters in Scandinavia.

## UHF and VHF RECEIVE CONVERTERS

FOR

2 - METER Synthesized Handie - Talkies

THE ORIGINAL -

**HANDI-CON** Series

Each one of these easy to use converters will turn an average 2-meter, fully synthesized H.T. into an extended coverage receiver. Choose either UHF or VHF PUBLIC SERVICE coverage or 220MHz AMATEUR coverage.

A micro-processor controlled H.T. can be a hand-held, programmable scanner, thus avoid the expense and bulk of a second receiver for emergency "traffic" and general pleasure monitoring.




Model No.	HC-V	HC-V220	HC-U2	HC-U2L
Nominal Coverage (MHz)	154-158 (PSB) 159-163 (MB)	221-225	460-464 480-484	470-474 506-510
Type (summary)	Police, fire, other public service. Marine telephone, N.A. weather	Amateur	Police, etc.	Police, etc.
Price	\$39.95	\$54.95	\$59.95	\$59.95

See a dealer near you - or write or call,

\*SIMPLE CONNECTION TO RADIO & ANTENNA.

**\*NEW** for '83

 - LOW LOSS TO A NOMINAL 2METER ANT. IN "OFF" MODE.
- LIGHT WEIGHT.
- ACCIDENTAL TRANSMIT PROTECTED.
- LOW CONVERSION LOSS.
- SINGLE SWITCH CONTROL.
- EFFICIENT DESIGN USES 1 AAA CELL.
- CASE IS BLACK, BRUSH ANODIZE FINISH.
- LOW COST.



**M-SQUARED ENGINEERING, INC.**

1446 LANSING AVE.  
SAN JOSE, CALIFORNIA 95118  
408-266-9214

above prices subject to local sales tax.  
CAL. res. add 6.5%

# MFJ 24 HOUR CLOCKS

Your choice: dual 24 hour LCD display, or 24/12 hour with ID timer, or 12 inch quartz analog.



**\$39.95** DUAL 24 HOUR LCD MFJ-104

Two independent 24 hour LCD displays! Read both GMT and local times at a glance. Six digit main display has seconds readout. Four digit auxiliary. Switch reverses main/aux. Alarm plays 4 selectable melodies. Alarm "ON" indicator. Snooze button. Quartz timing. Synchronizable to WWW. Flip-top cover serves as stand. Night light. Forward/reverse, fast/slow set buttons. Lock function prevents mis-setting. Display main time only, main/auxiliary or main/alarm time. Includes battery. 4x2x1/2 inches.



24/12 HOUR, ID TIMER **\$32.95** MFJ-102

Switchable 24 hour GMT or 12 hour format. ID timer sounds every 9 minutes after reset. Switchable seconds readout. Observed timer. Just start clock from zero and note time of event up to 24 hours. Bright blue 0.6" vacuum fluorescent diglts. Alarm with snooze function. Synchronizable with WWW. Fast/slow set buttons. Lock function prevents mis-setting. Power out, alarm "ON" indicators. 110 VAC, 60 Hz (50 Hz with simple modification). UL approved. Black, brushed aluminum top/front. 6x2x3".



24 HOUR QUARTZ MFJ-105 **\$49.95**

True 24 hour quartz wall clock has huge 12 inch diameter face. Gives excellent visibility across computer /radio room. Fifteen seconds per month accuracy. Single "AA" battery provides over one year operation, immunity from power line failure and eliminates power cord. Sweep second hand. Brown hi-impact case. Glass front. 24 hour military time format.

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). One year unconditional guarantee. Order yours today. Call toll free 800-647-1800. Charge VISA, MC. Or mail check, money order. Add \$4.00 each for shipping and handling.

**CALL TOLL FREE 800-647-1800**

Call 601-323-5869 in Miss., outside continental USA, tech/repair info. Telex 53-4590 MFJ STKV

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

## FILTER CASCADING

The most cost-effective way to improve the selectivity of any receiver - old or new - is to improve its IF filtering. A Fox-Tango Cascading Kit puts a high-quality steep-sided 8-pole filter in series with your present filter(s), both SSB and CW. The result is narrower Bandwidth and better Shape Factor, both of which dramatically reduce adjacent channel QRM - a necessity in today's crowded bands.

### CONSIDER THESE KIT FEATURES

- Easy installation - 30 minute average.
- No drilling, switching, alignment.
- 16 poles of filtering yield:  
Filter Shape Factor as high as 1.19.  
Ultimate Rejection better than 100dB.  
Works wonders on SSB; improves CW.
- Compensates for Filter insertion loss.
- Complete Instructions, clear diagrams.
- No RX audio impairment, TX unaffected.
- Includes Filter and all needed parts.
- Fits all models of Series - any letter.
- All Filters 8-pole - Guaranteed One Year.

### SPECIFY KIT WANTED WHEN ORDERING

YAESU FT101 \$75; FT101ZD \$70; FT107 \$75; FT901/2 \$65; FR101 \$55 (filter only). KENWOOD TS520/R599 \$70; TS820 \$70; TS830/RB20 \$150 (Two Filters). HEATH SB104A \$60.

Shipping \$3 (Air \$5). FL Sales Tax 5%

In addition to the above, FOX-TANGO stocks a wide line of \$55 SSB, CW, and AM 8-pole filters for Yaesu, Kenwood, Drake R4C and 7-line, and Heathkit. Also, special filters made to order. Send specs for quote.



GO FOX-TANGO - TO BE SURE!

Order by Mail or Telephone.

AUTHORIZED EUROPEAN AGENTS

Scandinavia: MICROTEC (Norway)

Other: INGOIMPEX (West Germany)

FOX TANGO CORPORATION

Box 15944S, W. Palm Beach, FL 33406

Phone: (305) 683-9587

323



Organize your shack with a **CLUTTERFREE MODULAR CONSOLE \$223.69**

- Large, 42" H x 57" W x 29"D
- Strong groove-construction
- Mar-resistant wood grain finish
- Options, drawers & face plate
- For ham or home computer
- Visa and Master Charge

**CLUTTERFREE MODULAR CONSOLES**

P.O. Box 5103 Tacoma, WA 98405  
(206) 272-0713

# TERMINALL

## RADIO MODEM



Apple TRS-80 ATARI

### SEND & RECEIVE CW & RTTY

TERMINALL is a hardware and software system which converts your Personal Computer into a state of the art communications terminal.

- TERMINALL is easy to use. Plug into your receiver headphone jack and copy Morse code or radioteletype. Plug into your CW key jack and send Morse code. Attach a Microphone connector and send Baudot or ASCII RTTY using audio tones (AFSK). That's all there is to hooking it up.
- Fantastic Morse reception. No adjustments are necessary to receive Morse code. It's fully automatic! Six stage active filter demodulator and auto adaptive Morse algorithm copes the weak and sloppy ones.
- Separate RTTY and CW demodulators. Built in crystal controlled AFSK CW and PTT keying 60 mil loop interconnect, RS 232 IN and OUT, hand key input and side tone output.
- Built in parallel printer driver software allows hardcopy in all modes.
- Hardware clock maintains accurate time.

- Multiple user defined WRU functions. You select initiate sequence, terminate sequence, what to transmit back and whether to save on tape or disk.
- Word wrapping, word mode editing, diddle, ignore carriage returns, user programmable end of line sequence, adjustable carriage width, transmit delay (fixed, none or auto adaptive), excellent documentation, break mode and much more.
- TERMINALL has capabilities for surpassing dedicated terminal systems. And since it works on a general purpose computer, the majority of your investment (your computer) spread out over many different applications. You get more for your money.
- Complete with software on cassette and diskette, assembled and tested hardware, and extensive instruction manual. Call or write for specifications on TERMINALL for TRS-80 Model I or Model III, Apple or ATARI 400/800 COMPUTERS. \$499.
- 15 day money back trial period. One year parts and labor limited warranty on factory direct orders.

To Order

(209) 667-2888

✓ 44



**MACROTRONICS, Inc.**  
1125 N. Golden State Blvd  
Turlock, CA 95380

\* Apple is a Registered Trademark of Apple Inc.  
TRS-80 is a Registered Trademark of Tandy Corp.  
Atari is a Registered Trademark of Atari Inc.  
Shipping U.P.S. Reg. Del. \$4.00 CA residents add 6% sales tax.

gift. Yaesu and Kenwood rigs are widely used and you make a friend for life by obtaining a needed service manual for a Scandinavian ham. If a radio friend is contemplating a trip to the US, he may appreciate a repeater directory or road maps. An auto club is the best source for maps.

I think the most enjoyable contact in a foreign country is with a ham with whom you've talked on the low bands. When your itinerary is firm, set up a definite rendezvous. You will probably learn more about life in that country in an evening than during the rest of your trip.

Chance contacts resulting in bending elbows together at one of the local pubs can make new friends and be a lot of fun as well. However, alcohol and driving definitely don't mix in Scandinavia. Penalties for driving with even a very small quantity of alcohol in the blood are severe. Therefore, expect

your friend to pass up the beer for a soft drink if he is driving.


In Copenhagen, don't be surprised to have Swedish stations from Malmo, Falkenberg, or some of the other southern towns come back to you through the local repeaters. In Finland, the repeaters in the less populous parts of the country, north of Hameenlinna, Tampere, and Lahti, may not be operational from time to time. You should check this out through low-band QSOs if you are planning to travel in the more northerly areas.

Two meters can be your key to opening up better paths of understanding of the beautiful countries and people of Scandinavia. Plan ahead, make new friends on the low bands, and have the fun of eyeball QSOs far from home. You will learn more, have more fun, and have some unforgettable memories through the power of amateur radio. ■

## 2300 MHz VARIABLE DOWNCONVERTER

### ANTENNA KIT

\$16.95

 

- 32 WASHERS
- 31 SPACERS
- MOUNTING BRACKET
- 6" RG 174 COAX
- 'F' CONNECTOR
- 6 1/2" x 4" P.V.C. PIPE
- 2 DRILLED END CAPS
- 35" ROD
- HARDWARE

### POWER SUPPLY KIT

\$16.95



- POWER TRANSFORMER
- COURSE TUNE POT.
- FINE TUNE POT.
- 3 'F' CONNECTORS
- RESISTORS & CAPS
- LED WITH HOLDER
- TERMINAL STRIP

- P.C. BOARD
- RF CHOKE
- KNOB
- WIRE
- 2 SWITCHES
- 4 DIODES
- LM 317 REG.

WOOD GRAIN CABINET WITH SILK SCREENED front and back \$10.95 Extra  
BUILT POWER SUPPLY.....\$34.95

Complete Down Converter System INCLUDES ANTENNA KIT POWER SUPPLY KIT CONVERTER KIT SPECIAL \$49.95

#### QUANTITY DISCOUNTS Any Price in Adv.

10 pcs.	12% off
25 pcs.	18% off
50 pcs.	25% off
100 pcs.	30% off
1000 pcs.	35% off


No Mixing for Quantity Discount

### PARTS

- Converter P.C. Board Plated through holes for stability.....\$4.95
- Power Supply
- P.C. Board .....2.95
- MRF 901 .....2.00
- NEO2135 .....4.95
- 2835 Diodes ..... .95
- .001 Chip Caps. .... 10/3.95
- Choke Set of 4.....1.95
- LM 317 Regulator 1.25
- 'F' Connectors
- Chassis ..... .50
- Wall Transformer
- 12 VAC 700 MA.....4.95
- 'U' Bolt ..... .95
- BALUN
- 75 to 300 ohm.....1.95
- BALUN for rabbit ears...2.95
- \*RG 59/U COAX WITH CONNECTORS FACTORY MADE
- 100 Ft. .... \$17.50
- 50 Ft. .... 9.50
- 25 Ft. .... 5.75
- 3 Ft. .... 2.50

### CONVERTER KIT

\$16.95

 

P.C. BOARD PRE-DRILLED SOLDER PLATED WITH PLATED THROUGH HOLES FOR A MORE STABLE PICTURE.

- NEW!! 2137 HOT TRANS...
- 3 MRF 901 TRANSISTOR
- 2 HP 2835 Diodes
- 6 .001 Chip Caps.
- 9 Resistors
- 4 Prewound chokes
- 1 Electrolytic Cap.
- 1 Pre Made Probe



\* WIRED P.C. BOARD TESTED, READY TO CONNECT TO CAN WITH PROBE & CABLE CONNECTOR ATTACHED. \$24.95

We will tune converter board for \$12.50  
trouble shoot add .....7.50  
trouble shoot power supply. \$12.50  
plus any parts needed.


We will accept telephone orders for Visa & Mastercard  
No C.O.D. Orders  
TO ORDER CALL 317-291-7262  
800-428-3500  
Complete kit weighs 10 lbs. Please add sufficient postage  
6254 LaPas Trail  
Indianapolis, Indiana 46268

# ELECTRONIC RAINBOW

✓ 146


 
# 2 METER 90 WATT OUTPUT AMPLIFIER WITH 18 DB GAIN PREAMP




Model 90PL  
FOR ONLY

**\$139.95\***  
PLUS SHIPPING

FACTORY DIRECT

- FREQUENCY range 144 - 148 MHz
- OPERATION FM or SSB (completely linear) Class AB1
- RF DRIVE 1 to 30 watts
- KEYING RF activated with high quality relays
- SSB operation built in delay
- POWER REQUIREMENTS typical 10 watts drive, 13 amps at 13.8 VDC
- IDLE current 20 mills
- MOBILE or FIXED operation
- PREAMP 180dB gain minimum
- NOISE FIGURE less than 1.5 DB
- PREAMP KEYING independent — separately RF activated relays
- CONSTRUCTION wrap around aluminum heat sink 2 pieces 360 degrees cooling
- SIZE 7"(w) x 6"(d) x 3"(h) — WEIGHT 3 lbs. 9 ozs.
- IMMEDIATE SHIPMENT

 

### SPECIAL OFFER

Matching Power Supply

**\$99.95\***  
PLUS SHIPPING

15 AMP SUPPLY wt. 13 lbs. size 8"(w) x 5"(h) x 6"(d)  
IMMEDIATE SHIPMENT  
ALL PARTS AND LABOR WARRANTED ONE FULL YEAR

VJ90PL Amplifier \$139.95 plus \$3.00 shipping  
VJ15 POWER Supply \$99.95 plus \$7.00 shipping  
\*Prices USA only

VISA, MASTER CHARGE, M.O. or C.O.D. • PHONE (713) 477-0134

**V-J PRODUCTS, INC.** 505 East Shaw, Pasadena, Texas 77506

SERVING THE ELECTRONICS INDUSTRY SINCE 1965

# Hear Police / Fire Weather

on 2 Meter Handhelds with this MFJ VHF Converter.



Scanning Handhelds become Police/Fire Scanners

MFJ-313

**\$39.95**

New MFJ VHF converter turns your synthesized scanning 2 meter handheld into a hot Police/Fire/Weather band scanner.

144-148 MHz handhelds receive Police/Fire on 154-158 MHz with direct frequency readout. Hear NOAA weather, maritime coastal plus more on 160-164 MHz.

Mounts between handheld and rubber ducky. Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No missed calls.

Highpass input filter and 2.5 GHz transistor gives excellent uniform sensitivity over both bands. Crystal controlled.

Bypass/OFF switch allows transmitting. Won't burn out if you transmit (up to 5 watts) with converter on. Low insertion SWR. Uses AAA battery. 2 1/4 x 1 1/2 x 1 1/2 in. BNC connectors.

Enjoy scanning, memory, digital readout, etc. as provided by your handheld on Police/Fire band.

### 220 MHz Converter for 2 M Handheld



MFJ-314

**\$59.95**

MFJ-314, like MFJ-313 but lets you receive 221-225 MHz on your 2 meter handheld.

### Police/Fire/Weather Band Converter for 2 Meter Mobile Rigs.



MFJ-312

**\$59.95**

MFJ-312, like MFJ-313 but for mobile 2 meter rigs. Transmit up to 40 watts thru converter without damage. SO-239 connectors. Mobile mounting brackets. Rugged. "ON" LED. Use 12 VDC or AAA battery. 3x4x1 in.

Order from MFJ and try it-no obligation. If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus \$4.00 each shipping.

Hear police/fire/weather. Order now. <47

CALL TOLL FREE ... 800-647-1800

Call 601-323-5869 in Miss., outside continental USA. tech/order/repair info Telex 53-4590.

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

## DIGITAL DISPLAY

30 DAY FREE TRIAL



YAESU  
HEATH  
DRAKE  
COLLINS  
KENWOOD

NEW YAESU DIGITAL DISPLAYS CONVERTED FOR THE ABOVE. 3/8" INCH RED LED DIGITS READ DOWN TO 10Hz. REAR PANEL 10Hz DIGIT OFF SWITCH. FROM A COLD START - MAXIMUM 100Hz DRIFT IN 24 HOURS. 1 3/8" HIGH, 4 1/2" WIDE & 6 1/2" DEEP. STEEL CASE IS BLACK. LOWER FRONT PANEL IS BRUSHED ALUMINUM. UNITS FOR MOD. NUMBERS UNDERLINED WORK WITHOUT ANY INSTALLATION BY PLUGGING INTO EXISTING JACKS ON THE RADIOS. MODELS WITH AN \* ASTERISK HAVE A POWER SUPPLY/TRANSFORMER AND OFF SWITCH. ALL POSTAGE PAID. IF YOUR EXTERNAL VFO JACK IS USED FOR A VFO, REC. OR TRANSMITTER; FOR A MALE/FEMALE PLUG/JACK ADD ----- \$5.00

F101 SERIES F17 F1301 IS5205 PLUG INTO REAR JACK FOR VFO SIGNAL AND POWER. NO INSTALLATION. ----- \$110.00

IS520 ISB20 IS600 IS900 R599 IS99 FRG7

F17B F1620B M104 TR7 101MX FR101 FL101-PARTS & INFO \$115.00

\*75S, \*MM & \*32S SERIES \*R-4 & \*1-4 SERIES \*SPR-4

\*F1100 \*F1400-W1 \*F1560-570 \*SB100-102

\*SB100-103 \*HR1680 \*H100-101 --ALL PARTS & INFO. --- \$130.00

YC221 FOR F1721R w/D SER F1221 F1225R IS700A 7 DIG -- \$85.00

SEND U.S. CASHIERS CHECK OR M.O., 30 DAY MONEY BACK. YOU PAY RETURN POSTAGE. WRITE WITH MOD. & SERIAL NO. FOR INFORMATION. WRITE IF YOUR RADIO IS NOT LISTED. WILL MAKE ONE YR WARRANTY.

## 30M KITS & MORE

HANDHELD PORTABLE RADIOS. --TOP QUALITY CONWIDE "QUICK DRAW" BELT HOLSTER. YOUR RADIO SNUG AND SECURE ON YOUR HIP - READY FOR IMMEDIATE WITHDRAWAL AND USE. YOU WILL BE DELIGHTED. SPECIFY MAKE AND MODEL OF HANDHELD. BLACK OR BROWN LEATHER. \$30.00

ALSO AVAILABLE. FINALLY!! A CAR WINDOW LEDGE CLIP ON BRACKET TO HOLD YOUR HANDHELD RADIO. YOU'LL LOVE IT! NO MORE FUMBLING ON THE DASH OR SEAT. SIMPLE AND ADJUSTABLE FOR YOUR CAR. SPECIFY HANDHELD MAKE AND MODEL. \$20.00

102A/AT/E SERVICE MANUALS 8x12 WITH LARGE DIAGRAMS. - \$12.00

NEW 30 METER BAND!! -- GRANDKIT F101 SERIES KITS GIVE 10MHz OPERATION ON THE EXISTING W/W/JY POSITION. ALL INFORMATION AND PARTS REQUIRED. POSTPAID. ----- \$15.00 GRANDKITS FOR MANY OF THE RADIOS WE MAKE DISPLAYS FOR--WRITE.

250 MHz DIVIDE BY TEN PRESCALERS. ASSEMBLED AND TESTED ON A CIRCUIT BOARD. JUST NEED FIVE VOLTS TO OPERATE. \$15.00 FOR A PREAMP ON THE ABOVE ADD ANOTHER FIVE DOLLARS. ALL AD PRICES INCLUDE POSTAGE. -- SEND CASHIERS CHECK OR M.O.

### GRAND SYSTEMS

P.O. BOX 2171 20352 40A AVE.  
BLAINE WASH. ✓ 132  
U.S.A. 98230 (604) 530 4551 CANADA V3A2Y8

## LACOMBE DISTRIBUTORS

Louisiana's  
Only  
Authorized



Large selection  
of Amateur and  
Marine Communications  
Equipment Available

Call for Quotes

**800-336-4799**

Lacombe Distributors  
Davis & Jackson Road ✓ 204  
P.O. Box 293  
Lacombe LA 70445  
(504) 882-5355





1982-1983

**AMATEUR  
RADIO**

**CALL  
DIRECTORY**

THE BARGAIN AT **\$14<sup>95</sup>**  
Plus Shipping



A no frills directory of over 411,000 U.S. Radio Amateurs. 8½x11, easy to read format. Completely updated.

Also available for the first time ever—  
(Alphabetically arranged—Sold separately)  
**Geographical Index**  
by State, City and Street No. and Call  
**Name Index**  
by Name and Call

Ordering Information:

- Directory—\$14.95
- Geographical Index—\$25.00
- Name Index—\$25.00

Add \$3.00 Shipping to all orders.

Dealers/Clubs inquiries welcome

Send your order—enclosing check or money order in U.S. dollars to:

**Buckmaster Publishing**

70-J Florida Hill Road  
Ridgefield, CT 06877 U.S.A. ✓226

## MFJ RF NOISE BRIDGE

Lets you adjust your antenna quickly for maximum performance. Measure resonant frequency, radiation resistance and reactance. Exclusive range extender and expanded capacitance range gives you much extended measuring range.



This MFJ-202 RF Noise Bridge lets you quickly adjust your single or multiband dipole, inverted Vee, beam, vertical, mobile whip or random system for maximum performance.

Tells resonant frequency and whether to shorten or lengthen your antenna for minimum SWR over any portion of a band.

MFJ's exclusive range extender, expanded capacitance range ( $\pm 150$  pf) gives unparalleled impedance measurements, 1 to 100 MHz. Simple to use. Comprehensive computer proven manual.

Works with any receiver or transceiver. SO-239 connectors. 2 x 3 x 4 inches. 9 volt battery.

Other uses: tune transmatch; adjust tuned circuits; measure inductance, RF impedance of amplifiers, baluns, transformers; electrical length, velocity factor, impedance of coax; synthesize RF impedances with transmatch and dummy load. ✓47

- Exclusive range extender
- Expanded capacitance range
- Series Bridge

# \$59<sup>95</sup>

Order from MFJ and try it — no obligation. If not delighted, return it within 30 days for a refund (less shipping). This bridge is unconditionally guaranteed for one year.

To order, simply call us toll free 800-647-1800 and charge it on your VISA or MasterCard or mail us a check or money order for \$59.95 plus \$4.00 for shipping and handling for MFJ-202.

Put this MFJ Noise Bridge to work improving your antenna. Order from MFJ or see dealer.

**CALL TOLL FREE ... 800-647-1800**

Call 601-323-5869 for technical information, order/repair status. Also call 601-323-5869 outside continental USA and in Mississippi.

**MFJ ENTERPRISES, INCORPORATED**  
Box 494, Mississippi State, MS 39762

# REMOTE -O- MIKE

## \$34<sup>95</sup>

### FM Wireless Mike

- Range—up to 300 ft.
- FM Audio
- XTAL Controlled
- Simple Hook-up
- Reliable years of service

Stop: The steering wheel mike cord tangle. Stop: Running back and forth to answer a call on your radio. Stop: The inconvenience of being tied to your radio during long QSO's. The Remote-O-Mike may be connected to any HF, VHF or UHF ham transceiver. Just connect the Remote-O-Mike receiver to the mike input jack and each time you press the PTT button on your cordless mike your ham rig will function as your normal mike. The Remote-O-Mike receiver will provide both the PTT and audio to your ham rig.

Use in and around the house, auto, boat, etcetera. Just like a repeater with a range of up to 300 ft. Each Remote-O-Mike includes a XTAL controlled wireless FM mike and FM receiver. How do you spell mike cord tangle relief (Remote-O-Mike) Order today for your mike cord relief.



FM RECEIVER



WORKS ON ANY RADIO—MOBIL OR BASE



## To Order Call (714) 268-8131—Free Shipping

Discount Ham Radio

9520 Chesapeake Dr., #606 A, San Diego, CA 92123

pulse at the output of U1 is applied to the clock input of U2, causing the output of U2 to toggle to a high state which turns on Q2 and energizes relay K1. The output of U2 will remain high until another pulse is applied to the clock input, at which time it will toggle back to its original low state.

Since the limiting action of most inexpensive FM receivers is not what it should be, C1 (connected across the Q1 collector resistor) is included to prevent possible false triggering caused by noise spikes from the output of the receiver.

No power supply is shown in Fig. 1, since these have been extensively covered elsewhere in the ham literature. As shown, any voltage from 6 to 12 volts will work. The amount of supply voltage you decide to use will depend upon the voltage rating of the relay you purchase, or that of one you may have on hand.

It should be mentioned here that the receiver you use must have some type of external antenna, and an earphone jack. If your receiver has no earphone jack, one must be added, which is simple to do using a three-conductor phone jack.

### Transmitter Circuit

The FM wireless microphone circuit shown in Fig. 2 was originally published in the April, 1969, issue of *Popular Electronics*. The circuit, as shown in that issue, used an RCA KD-2114 linear IC for the active device but discrete transistors were used here since they were more readily available. The circuit is shown here with one modification; the microphone input network has been replaced with a simple tone-generating circuit composed of R1, C1, Q1, and T1. It has an output of about 800 Hz and provides the necessary control signal.

 


Fig. 2. Schematic diagram of the transmitter. See text for L1 dimensions.

### Switching Unit and Transmitter Construction

The switching unit can be built most easily using perf-board construction, and sockets should be used for both U1 and U2, in case replacement becomes necessary. The unit may be enclosed in any type of case you may have on hand.

Perfboard construction also may be used for the transmitter, although I have used the PC board square block method with good success. This means using a hacksaw to cut the foil side of a piece of PC board into squares and mounting the components on the squares. Placement of parts in the transmitter is not too critical, but an orderly in-line layout ought to be used. The connections in the rf portion of the circuit should be kept as short and as direct as possible.

Coil L1 consists of 6 turns of #12 tinned copper wire with an inside diameter of 5/16 inches and spread to 3/4 inches in length. The antenna tap is made one and one-half turns from the cold, C3, side, and tuning capacitor C2 is soldered directly to the top and side of the first and last turns of the coil. Coil L1 should be mounted as firmly to the board as possible to enhance frequency stability. The antenna can be fashioned from a piece of heavy-gauge copper wire, and can be anywhere from 3 to 12 inches in length. A

plastic case similar to those sold by Radio Shack can be used for housing the transmitter.

### Test and Adjustment

First, the transmitter should be tested and adjusted to a clear operating frequency. To do so, turn on your FM receiver and tune for a clear spot on the dial. The afc should be turned off, if possible, to prevent the receiver from tuning automatically to a strong adjacent channel. Once a clear spot is found, apply power to the transmitter and adjust tuning capacitor C2 until an audio tone is heard from the receiver. Now, either continue adjusting C2 or vary the tuning of the receiver until the purest tone possible is obtained.

The switching unit may now be tested for proper operation. Plug P1 into the earphone jack of your FM receiver and apply power to the switching unit. At this point, the volume control of the receiver should be set at some low level. Each time the transmitter is momentarily activated, the relay on the switching unit should energize and stay energized until a second pulse is transmitted, at which time it will return to its normally-closed position. The volume control may have to be increased a small amount to ensure reliable operation at a distance.

If the switching unit does not operate as just de-

scribed, then either a wiring error has been made or one of the active devices is defective.

The range of the transmitter will vary with operating conditions and depends to a certain extent upon the orientation of both the transmitting and receiving antennas. It has been my experience that reliable operation can be had with distances up to 75 feet.

### Summary

The uses that may be found for this simple system are many and are limited only by your imagination. If you happen to own a video tape recorder and like to record movies without the commercials, then this remote-control system can be used to pause the recorder and to cut them out. It could also be used as a commercial killer for the television itself. To use it this way, one of the television's speaker leads is broken and connected to a set of the relay's normally-closed contacts. In fact, you might even connect your ham-band receiver's mute terminals to the relay's other set of contacts, and that way be able to listen to it while the television sound is off.

There are, undoubtedly, many other applications that can be thought of, but whatever you may use it for, always be careful to observe the relay's contact power rating, otherwise an expensive relay may be ruined. ■

# At Last.

A microthin, synthesized, programmable, sub-audible tone encoder that fits inside the ICOM IC-2AT.

Need we say more?

\$29<sup>95</sup>



**COMMUNICATIONS  
SPECIALISTS**

426 West Taft Avenue, Orange, CA 92667  
800/854-0547 California 714/998-3021

## SWD-1 VIDEO CONVERTER

FOR CABLE TV



The SWD-1 Video Converter is utilized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms, 117VAC.

SWD-1 Video Converter Kit ..... \$69.95

## VTR ACCESSORIES

### SIMPLE SIMON VIDEO STABILIZER



Simple Simon Video Stabilizer, Model VS-125, eliminates the vertical roll and jitter from "copy guard" video tapes when playing through large screen projectors or on another VTR. Simple to use, just adjust the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments. Includes 12V power supply.

VS-125 Video Stabilizer, wired ..... Reg. 54.95... **\$39.95**

NEW VCR Quality

### MODULATOR



Not a Game Type Modulator The MPS-1 Kit converts Video/Audio signals to a crystal controlled RF output for TV Channels 3 and 4. The MPS-1 Modulator inputs are designed to match all TV Cameras and VCR's and features a voltage regulated power supply, power switch and LED Indicator. No Tuning Required. Operates on 117VAC.

MPS-1 Kit ..... **\$39.95**

## UHF ANTENNAS AND ACCESSORIES

### MDS-AMATEUR-ETV 32 ELEMENT YAGI ANTENNA



Not A Kit  
● 1.9-2.5 GHz ● 38 1/2" Long  
● 23dB Average Gain ● Commercial Grade  
● Die Cast Waterproof Housing with 4 1/4" x 2 1/2" Area for Electronics  
● Includes P.C. Probe, F-61 Connector and Mounting Hardware

MAE-2 32 Element YAGI Antenna ..... **\$23.95**

### Kato Sons' Down Converter Kit ★1.9 - 2.5GHz★

Designed for Simple Simon by former Japanese CQ Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antenna housing. Requires 1 hour assembly. IC and capacitors pre-soldered.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit ..... **\$34.95**

### Kato Sons' Regulated Variable DC Power Supply

For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.

Model KSPS-1A Assembled Power Supply ..... **\$23.95**


SPECIAL INTRODUCTORY SAVINGS

### ORDER ALL THREE ITEMS

MAE-2, KSDC-KIT and KSPS-1A for Only **\$74.95**

Regular price if ordered separately \$82.95  
— CO-AX CABLES ARE NOT INCLUDED —
 
### ZYZZX VHF-UHF Wideband Antenna Amplifier




Revolutionary New HYBRID IC Broadband Amplifiers  
50 MHz - 900 MHz  
Model ALL-1 12dB Gain  
Model ALL-2 35dB Gain

These units are not available anywhere else in the world. Each unit will serve many purposes and is available in kit or assembled form. Ideal for outdoor or indoor use. I/O impedance is 75 ohms. Amplifiers include separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors to tune or adjust.

ALL-1 Complete kit w/power supply \$24.95 ALL-1 W/inst./Tested w/power supply \$34.95

ALL-2 Complete kit w/power supply 34.95 ALL-2 W/inst./Tested w/power supply 44.95
 
### Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80 ..... **\$19.95**

STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52 ..... **\$19.95**

RC-59/U 75 ohm Low Loss Coax Cable \$129/ft. F-59 Coax Connector, \$ .39 ea.

MT-1 Special UHF 75-300 ohm Matching Transformer \$1.45 ea.

# Switch to Bambi!

Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.

The Bambi Electronic Video Switch is an electronic switching network which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ... not being able to use more than one function at a time.

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Completely Wired and Assembled. Includes comprehensive Instruction/Operation Manual and Decal Set for customizing your Video Switch installation.

**\$129.95**



FREE Bambi Poster with any purchase



Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without referring to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.



Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually shielded for 65dB min. Isolation).



### Bambi's Specifications:

- Input/Output Impedance 75 ohm
- Signal Loss 3dB ±1dB
- Noise 40dB ±1dB
- Input Return Loss 12dB min.
- Isolation 65dB min.
- Power Req. 117VAC 60 Hz 2W
- Dimensions 10" W x 6" D x 3 1/4" H
- Weight 4 1/2 lbs

## 7+11 PWD PARTS KITS

### INTRODUCING OUR 7+11 PWD PARTS KITS



KIT No	PART No	DESCRIPTION	PRICE
1	1VT1-PWD	Variable UHF Tuner	\$24.95
2	2CB1-PWD	Printed Circuit Board, Pre-drilled	18.95
3	3TP11-PWD	PCB Potentiometers 4-20K, 1-.5K, 2-10K, 2-5K, 1-1K, and 1-50k. (11 pieces)	8.95
4	4FR-31-PWD	Resistor Kit, 1/4W, 5% 29-pcs, 1/2 W 2-pcs	4.95
5	5PT1-PWD	Power Transformer, PRI-117VAC, SEC-24VAC at 500ma	8.95
6	6PP2-PWD	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT with switch	5.95
7	7SS17-PWD	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Transistors 2-pcs, Heat Sinks 2-pcs	29.95
8	8CE14-PWD	Electrolytic Capacitor Kit, 14-pieces	8.95
9	9CC20-PWD	Ceramic Disk Capacitor Kit, 50 WV, 20-pcs	7.95
10	10CT5-PWD	Variable Ceramic Trimmer Capacitor, 5-65pfd, 5-pieces	4.95
11	11L5-PWD	Coil Kit, 18mhs 3-pcs, .22uhs 1-piece (pawound inductors) and 2 T37-12 Ferrita Toroid cores with 6 ft. #28 wra	8.00
12	12ICS-PWD	IC Sockets, Tin Inlay, 8 pin 4-pcs, 14 pin 1-pc and 18 pin 2-pcs	2.95
13	13SR-PWD	Enclosure with PM Speaker and Pre-drilled Backpanel for mounting PCB and Ant. Terms	14.85
14	14MISC-PWD	Misc. Parts Kit, Includes Hardware, (8/32, 8/32 Nuts & Bolts), Hookup Wire, Solder, Ant. Terms OPDT Ant. Switch, Fuse, Fuseholder, etc	8.95
15	15MC16-PWD	Mylar Capacitors, 14-pcs and Silver Mica Capacitors 2-pieces	7.95
When Ordering All Items, (1-15), Total Price			159.95

**CUSTOMER NOTICE:** BUY WITH CONFIDENCE... BEWARE OF LOW QUALITY IMITATORS. All of our kits consist of New, 1st Class, RF Quality, Parts Engineered for Optimum Operation, not factory seconds or stock close-outs. We service your completed kits that you've purchased and built. You will never get stuck with a BAG OF PARTS when ordering from Simple Simon.

## SIMPLE SIMON ELECTRONIC KITS, Inc.

3871 S. Valley View, Suite 12, Dept. 7, Las Vegas, NV 89103

In Nevada Call: 702-871-2892

NEEDS OR MORE OF AN ITEM? WRITE FOR QUANTITY DISCOUNTS

Outside Nevada Call: 1-800-782-3716

Available by Mail Order Only  
Send Check\* or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00  
— VISA and Mastercard Acceptable —  
\*Check orders will be held 30 days before shipping.

# HUSTLER HF MOBILES DELIVER FIXED STATION PERFORMANCE

Hustler HF antennas deliver outstanding signal reports — wherever you're mobile!

Design your own HF mobile from a full selection of top-quality; U.S.-made stainless steel ball mounts, quick disconnects, masts, springs, and resonators. You can cover any 6-to-80-meter band. Choose from medium or high power resonators with broadest bandwidth and lowest SWR for optimum performance on any band. Easy band change and garaging with Hustler's fold-over mast, too.



Ask any ham — the best HF mobiles on the road come from: Hustler — still the standard of performance.

**HUSTLER**

3275 North "B" Avenue  
Kissimmee, Florida 32741

An **AMERICAN** Company

# DISPLAY YOUR STUFF

With the AEA MBA-RO Reader Automatic display of transmitted and received Morse and RTTY coded signals has come of age. It is proving to be most worthwhile for improving one's own transmitted "fist" and for allowing SWL's or visitors the opportunity to experience the thrill of Amateur Radio coded transmission.



While no machine can yet match the ability of a skilled CW operator in copying poor fists or signals buried in the noise, the MBA-RO by AEA excels even when compared against units costing much more. The large 32 character display allows much easier reading than shorter displays, especially at higher speeds such as 60 WPM or 100 WPM RTTY. The MBA-RO also features dual filters for RTTY decoding of either 170 Hz or 425 Hz (easily changed to 850 Hz) shift transmissions.

Prices and Specifications subject to change without notice or obligation. Software ©copyright by AEA.



ELECTRONIC

EQUIPMENT BANK

516 Mill Street  
Vienna, VA 22180  
(703) 938-3350 / 1-800-368-3270  
Ten miles west of Washington, D.C.

**AEA** Brings you the  
Breakthrough!

# Forward, March!

<b>ICOM</b>	
R70 .....	\$665.00
IC730 .....	665.00
IC740 .....	969.00
IC290H .....	489.00
<b>KENWOOD</b>	
TS130SE .....	599.00
TS530S .....	599.00
TS930S .....	Call
TS430S .....	Call
R2000 .....	599.95-Call
R1000 .....	499.95-Call
<b>YAESU</b>	
FT707 .....	649.00
FT102 .....	999.00
FT980 .....	Call
FT77 .....	Call
<b>BIRD Stock</b> .....	Call
<b>KANTRONICS</b> Interface .....	169.00
Software in Stock	
<b>DIELECTRIC, CURTIS,</b>	
<b>SHERWOOD</b> .....	10% Off List
<b>SANTEC ST144μP</b> .....	279.00
HT1200 + extra battery + DC .....	250.00
<b>TRI-EX</b>	
W51 .....	(F.O.B. Calif) 799.00
<b>TCG 2.5A/1000 piv Epoxy diode</b> ..	19¢
<b>SPRAGUE 500PF/1000v</b>	
Feedthru .....	1.95
500PF/20KV Doorknob .....	16.00
<b>CDE 1000PF/20KV Cap</b> .....	1.95
<b>DRAKE</b>	
TR7A/RV75 .....	1700.00
TR5 .....	699.00
R7A .....	1400.00
<b>CUSHCRAFT A3</b> .....	179.00
A4 .....	229.00
<b>AEA MBARO</b> .....	269.00
MBARC .....	399.00
MM2 .....	139.00
CK2 .....	119.00
<b>DOW-KEY</b> Coax Relay .....	99.00
<b>Antique Tubes</b> .....	Call
<b>HUSTLER 5BTV</b> .....	115.00
<b>BUTTERNUT HF6V</b> .....	125.00
<b>QSL Holder \$2.00</b> .....	Coax Seal 2.00
<b>COLLINS Crystals</b> .....	ea. 12.00
<b>SIGNAL/ONE</b> Milspec 1030 ..	4995.00
Less your trade-in.	

Any new equipment ordered from us can be tested and approved by our factory trained technicians prior to shipment if you request it. This requires opening the box, but the technicians approval card will be enclosed.

#### MASTERCARD VISA

All prices fob Houston except where indicated. Prices subject to change without notice. All items guaranteed. Some items subject prior sale. Texas residents add tax. Please add sufficient postage. balance collect.

**MADISON**  
Electronics Supply  
1508 McKinney  
Houston, Texas 77010  
713-658-0268 ✓45

# Take Your IC's Temperature

*Like people, solid-state devices get sick if they get too hot. W3KBM provides a way to answer the burning question, "How hot is hot?"*

Allen S. Jofie W3KBM  
1005 Twining Road  
Dresher PA 19025

**B**y now solid-state devices are old hat. We all know that too much heat is one good way to send such a device to semiconductor heaven. Since touching a hot transistor or IC with a finger either makes for one big "ouch" or leaves the question of "How hot is it?" largely unanswered, here is some surplus to the rescue.

Digital Research of Garland, Texas, has advertised "Thermistors... 5000 Ohms at 25 degrees centigrade," four for a buck. Upon arrival they proved to be Fenwal KA35J3 thermistors.

A quick trip to Herbach and Rademan in Philadelphia produced a surplus cabinet and a nice 200-microampere meter with a scale calibrated from 0 to 100. With the addition of very few parts, this collection was turned into a solid-state centigrade thermometer that allows me to answer "How hot is my IC?" very adequately.

The schematic in Fig. 1 shows the simplicity of the electrical hookup. Resistors R1 and R2 of the bridge should be as closely matched in value as possible. They can range from 4700 to 5000 Ohms; the important part of the matter is that they be as alike in value as possible.

Resistor R3 should be as close to the indicated 15k as you can get. The significance of R3 lies in the fact that at zero degrees centigrade the thermistor resistance will be rather close to this value. My four samples checked out this way as indicated by a fairly good digital meter. Thus, at zero degrees, the bridge will be balanced and the meter should read zero. Taking this route eliminates the need for a low-end calibrating element in the circuit. I used a fresh D-cell to drive the bridge; since the current drain is very low, the useful life of the battery should approach its shelf life.


My meter is 200 microamperes full scale, which is about the practical limit of usable sensitivity in the upward direction. That is to say, if you have a more sensitive meter, then use it, but avoid using a less sensitive meter. The reason for this is that even small currents flowing through the thermistor tend to produce "self heat" which changes its ohmic value just as much as heat from a device being measured. If you use a 50-microampere movement, you may have to increase the value of the variable resistor in series with the meter movement. This resistor is used as the sole calibrating element for the thermometer.

The photo shows the finished meter with its probe and also an unmounted thermistor which gives an indication of the size of this circuit element.

Now for some notes on the probe construction. The body of the probe was made from a discarded fiber-tipped type of marker such as a Flair or other brand. The point was pulled off and the residual ink was carefully wiped out of the barrel. I say carefully as there is enough ink left to ruin several sets of clothes, soil your hands, and provide some interesting comments from the family if care is not used in this regard.

The sides of the thermistor are painted with clear nail polish where the leads are attached. The same treatment is given to the first half inch of lead length near the body of the thermistor after a suitable length of cable

Photo by Ira Jofie WA3PTC

 

Completed meter with probe attached.

 


Fig. 1. Schematic diagram of meter.

has been soldered to the extreme ends of the leads.

The cable is then threaded through the empty pen body and the thermistor is checked for a good snug fit in the open end as shown in the photo. If you have to ream out the end a bit to achieve a snug fit, by all means do so. When this has been done, pull the thermistor and cable out an inch or so and work some artificial rubber compound like GE silicone seal into the end of the probe barrel. Pull the thermistor back in, seat it nicely, and put the assembly aside to dry. You may also want to use the silicone seal in the end of the probe from which the cable exits to provide a bit of strain relief. That is all there is to the probe.

When the construction of the probe and associated circuitry is finished, turn on the switch and the meter should be reading somewhere about 20 to 25 de-

grees on the meter face. Turning the calibration control should allow a meter variation of about eight to ten degrees total.

It may pay to make a "big deal" out of the initial calibration so you can see that it works. The big deal is as follows. Obtain a reliable thermometer such as a unit used to check the temperature of photographic solutions. Fill a jar with hot water from the kitchen tap. Check its temperature with your known good thermometer. Add a bit of cold water if necessary to get the water to about 120 to 125 degrees Fahrenheit. After this thermometer reading has stabilized for about one minute, gently place your thermistor probe into the water so that it just dimples the surface of the water. Give the meter a chance to settle to a reading, which may take as much as thirty seconds to ensure that a maximum has been reached. Multiply your

meter reading by 1.8 and add 32 to the result to convert the meter reading to Fahrenheit degrees as shown on your comparison thermometer. If it is high or low, make an adjustment with the calibrating pot so that the two readings coincide.

If you do not want to go through the "big deal" version of calibration, then use one of the best thermal standards around. That standard is you and the normal temperature of your body, which is just about 98.6 degrees Fahrenheit or 37 degrees centigrade. Touch the tip of the probe to your tongue and hold it there until the meter reading stabilizes. Set the calibration control for a reading of 37 degrees on the meter and you are done. This is one instrument where you will never lose the source of calibration.

Do not use this thermistor thermometer to take the temperature of hot liquids.

Use it for its intended purpose of measuring the temperature of ICs and discrete semiconductors. When you do this, I suggest that you take a small bit of thermal compound such as you would use on a power transistor to make sure that it is in good thermal contact with a heat sink. Place this on the semiconductor or IC of interest and then apply the probe tip to it so that you have good thermal contact with the subject at hand. This should give you reliable comparative readings. You can easily see the effect of different sizes and materials of heat sinks in terms of getting rid of heat from the power devices. Please note the use of the phrase "reliable comparative" readings. This simple device will not put the National Bureau of Standards out of work, but it is a nice adjunct to aid any ham working with power semiconductor devices. ■

## THE RTTY ANSWER



THINKING OF RTTY??  
APPLE ... TRS ... HEATH ... DEDICATED SYSTEM? SOFTWARE?  
INTERFACE? PERFORMANCE? PRICE? We know you have questions ...  
check our answers. Call today for information on our terminal units!

VISA OR MASTER CHARGE ACCEPTED  
IMMEDIATE DELIVERY

**IRL**  
T.M.

700 TAYLOR RD.  
COLUMBUS, OHIO 43230  
(614) 864-2464



## WE'RE **ROLIN** ✓418 IN CRYSTALS!

**2 Meter Crystals — \$3.95 each  
(10 or More — \$3.50 each)  
Quick Delivery**

### We Stock Crystals For:

Clegg Drake Icom  
Kenwood Midland Regency  
Standard Wilson Yaesu  
Lafayette Tempo VHF Eng

### Rollin Distributors

P.O. Box 436 Department 7  
Dunellen, N.J. 08812  
201-469-1219

(Custom Crystal Orders Accepted.) Precision Cut Land Mobiles Available

## Take your favorite H.T. out for a drive tonight.

VISA or MASTERCARD for  
same day shipment.

For \$69.95 you get the most efficient,  
dependable, fully guaranteed 35W 2 meter  
amp kit for your handy talkie money can buy.

Now you can save your batteries by operating  
your H.T. on low power and still get out like a  
mobile rig. The model 335A produces 35 watts  
out with an input of 3 watts, and 15 watts out with  
only 1 watt in. Compatible with IC-2AT, TR-2400,  
Yaesu, Wilson & Tempo! Other 2 meter models are avail-  
able with outputs of 25W and 75W, in addition to a 100W  
amplifier kit for 430MHZ. ✓382

**Communication Concepts Inc.** 2648 N. Aragon Ave., Dayton, OH 45420  
(513) 296-1411



## Touch-Tone Decoders


Ask for your **FREE** copy of the  
new Palomar Engineers Tone  
Control Catalog which in-  
cludes:

- P-200** Single Digit Decoder ..... \$77.50
- P-411** 16 Digit Decoder ..... \$195.00
- P-416** 16 Digit Decoder ..... \$385.00
- AR-3** 3 Digit Sequencer ..... \$67.50
- RL-1** Relay Latch ..... \$55.00
- PP-1** 12 Digit Encoder ..... \$55.00
- PP-2** 16 Digit Encoder ..... \$59.00

Order from:
 
## Palomar Engineers

Box 455, Escondido, CA. 92025  
Phone: (619) 747-3343



## SATELLITE TELEVISION SYSTEMS

**WE WILL NOT BE UNDERSOLD!!**

Complete Systems, Antennas,  
Receivers, LNA's & Accessories

CALL US TODAY! ✓320

**812-238-1456**

**hoosier  
electronics**

"Nation's Largest Total Communications Distributor"  
P.O. BOX 3300 • TERRE HAUTE, INDIANA 47803

## ALL NEW H.F. 10/160 METER SOLID STATE P.L.L. TRANSCEIVER



### USB-LSB

4 Memories  
3 Way Auto-Scan  
Includes New Bands  
3-Step Tuning Speed  
IF Tune  $\pm 1$  KHZ  
Built-in Dual VFO

### CW-W CW-N

200 W. PEP (160M-12M)  
100 W. PEP (10M)  
Built-in Power Supply  
AC-120 VAC  
DC-13.8 V -Ground  
External ALC  
13.5 VDC Relay



JUST SLIGHTLY AHEAD

1275 N. GROVE ST.  
ANAHEIM, CA 92806

TO ORDER OR  
DLR INFO. CALL  
(714) 630-4541

✓318

NOTE: Price, Specifications subject to change  
without notice and obligation

**New!**  
**AZDEN® PCS-4000**

*Small - yet so Sophisticated...  
 so Advanced - there is  
 No Comparison!*

**FEATURES SO  
 UNIQUE AND  
 OF SUCH  
 SUPERIOR  
 COMMERCIAL-  
 GRADE  
 QUALITY,  
 THAT...**



**IT CARRIES A  YEAR LIMITED WARRANTY!**

- **8 MHZ COVERAGE, CAP/MARS BUILT IN:** 142 000-149 995 MHz in selectable steps of 5 or 10 kHz. **COMPARE!**
- **TINY SIZE:** Only 2" H x 5.5" W x 6.8" D! **COMPARE!**
- **MICROCOMPUTER CONTROL:** At the forefront of technology!
- **UP TO 8 NON-STANDARD SPLITS:** Ultimate versatility for CAP/MARS. **COMPARE!**
- **16-CHANNEL MEMORY IN TWO 8-CHANNEL BANKS:** Retains frequency and standard offset.
- **DUAL MEMORY SCAN:** Scan memory banks either separately or together. **COMPARE!**
- **TWO RANGES OF PROGRAMMABLE BAND SCANNING:** Limits are quickly reset. Scan the two segments either separately or together. **COMPARE!**
- **FREE AND VACANT SCAN MODES:** Free scanning stops 5 seconds on a busy channel. Vacant scanning stops on unoccupied frequencies.
- **DISCRIMINATOR SCAN CENTERING (AZDEN EXCLUSIVE PATENT):** Always stops on frequency.
- **TWO PRIORITY MEMORIES:** Either may be instantly recalled at any time. **COMPARE!**
- **NICAD MEMORY BACKUP:** Never lose the programmed channels!
- **FREQUENCY REVERSE:** The touch of a single button inverts the transmit and receive frequencies, no matter what the offset.
- **ILLUMINATED KEYBOARD WITH ACQUISITION TONE:** Unparalleled ease of operation.
- **BRIGHT GREEN LED FREQUENCY DISPLAY:** Easily visible, even in direct sunlight.
- **DIGITAL S/R F METER:** Shows incoming signal strength and relative output.
- **BUSY-CHANNEL AND TRANSMIT INDICATORS:** Bright LEDs show when a channel is busy and when you are transmitting.
- **FULL 16-KEY TOUCHTONE™ PAD:** Keyboard functions as autopatch when transmitting.
- **PL TONE:** Optional PL tone unit allows access to PL repeaters. Deviation and tone frequency are fully adjustable.
- **TRUE FM:** Not phase modulation. Unsurpassed intelligibility and fidelity.
- **25 WATTS OUTPUT:** Also 5 watts low power for short-range communication and battery conservation. (Transmitter power is fully adjustable)
- **SUPERIOR RECEIVER:** Sensitivity is 0.2 uV for 20-dB quieting. Audio circuits are designed to rigorous specifications for exceptional performance, second to none. **COMPARE!**
- **REMOTE-CONTROL MICROPHONE:** Memory A-1 call up/down manual scan, and memory address functions may be performed without touching the front panel! **COMPARE!**
- **OTHER FEATURES:** Dynamic microphone, built-in speaker, mobile mounting bracket, remote speaker jack, and all cords, plugs, fuses and hardware are included.
- **ACCESSORIES:** CS-6R 6-amp ac power supply, CS-AS remote speaker, and Communications Special sts SS-32 PL tone module.
- **ONE-YEAR LIMITED WARRANTY!**

EXCLUSIVE DISTRIBUTOR:

**AMATEUR-WHOLESALE ELECTRONICS**

**TOLL FREE... 800-327-3102**

8817 S.W. 129th Terrace, Miami, Florida 33176 Telephone (305) 233-3631 Telex: 80-3356

MANUFACTURER:

 **AZDEN**

**JAPAN PIEZO CO., LTD.**

1-12-17 Kamirenjaku, Mitaka, Tokyo, 181 Japan.

Telex: 781-2822452



# The Q-Master Cavity Filter

*A high-Q filter that uses no copper and no silver-plating—  
just coffee cans and some ingenious thinking.*

A few months ago, some experimental work I was doing with a low-power, home-brew repeater system required a sharp filter to restrict the bandwidth of the signal presented to the antenna terminals of the receiver section, particularly at the transmitter frequency. Since the cost and availability of commercially-produced cavities were prohibitive, I decided to research the problem and see if I could make my own.

Several of the amateur publications, engineering texts, and reference books in my library discussed the subject (see reference list at end of article); some even gave dimensions and bills of materials. Since I live in a somewhat remote part of the Pacific Northwest, availability of many of the

materials specified and machining services required was a problem. I decided that I should tackle the problem with the idea of using only readily-available parts and home-brew construction techniques and see what could be done. This is the story of that effort.

First, it was necessary for me to determine just how a cavity operates and what the critical conditions were. Research showed that the cavity is merely a tuned circuit, consisting of a quarter-wave stub centered in an enclosure. The combination results in a well-shielded, high-Q filter when inserted in series with the transmission line. As with any tuned circuit, the circulating currents are quite


high at resonance, so losses must be kept low to ensure high Q. The losses are generally the result of the resistance of the materials from which the cavity is made. For this reason, most commercial units are made of brass or copper and silver-plated.

Coupling into and out of the cavity can be accomplished by any of several means, but the most common is inductive coupling, whereby small loops are positioned near the inner stub and act as transformer windings in relation to it. The loops are mounted on opposite sides of the stub so that there is minimum direct coupling between them. Thus, the input loop induces the signal into the stub (which is, remember, part of a resonant circuit),


and the stub in turn induces the signal into the output loop. Since the response of the resonant circuit is appreciable only at or near the resonant frequency, appreciable coupling between the input and output loops occurs only in that range, and we have a band-pass filter.

Fig. 1 shows the low-frequency equivalent of the cavity filter, using discrete coils and a capacitor, and may help the reader to understand the operation of the circuit.

 In order to build the device with a reasonable chance of success, it is necessary to identify the critical areas first. Obviously, the length of the center stub is critical. It must be an electrical quarter wave-



 *First coffee can soldered to the top plate. Note the telescoping tuning stub.*



*Overall view of the two-meter coffee filter. One can was left unpainted for effect.*

# More kit quality

A triumph of price and performance — Heath's new HW-5400 Synthesized HF SSB Transceiver kit makes high technology affordable. With more versatile, far-reaching capabilities, it puts the original skill and adventure back into Amateur Radio...



HW-5400 Transceiver

control when used with the Split Memory function. The matching HWA-5400-1 Power Supply/ Speaker & Digital Clock (not shown) provides a double-fused source of 13.8 VDC from 120 or 240 VAC.

Heath breaks the price barrier on sophisticated transceivers, offering the highest value for your hamshack dollar. The slim, new HW-5400 is a marvel of kit-form engineering that performs like a dream on 80-10 meters.

## MORE ADVANCED IDEAS

Solid state and broadbanded, the HW-5400 incorporates more performance-improving features at a lower price than any comparable transceiver. It's fully synthesized for crystal stability and accuracy. Operating in USB, LSB and CW with automatic sideband selection, it has full break-in (QSK) for proficient keyers, two memories per band, power supply activation at the Transceiver, defeatable amplifier relay, reverse and over voltage protection as well as high VSWR forward power cut-back circuitry for the finals.

A custom microprocessor yields flexible, fingertip control over all phases of T/R operation.

## MORE CONVENIENCE

This perfection-packed kit has many benefits. A unique dual-speed tuning system can extract new QSOs or fly through a band in 1 kHz increments with 50 Hz resolution! *Split-Memory Access* lets you review and change the transmit frequency while in receive, without missing a single word or fragment of code. With it, you can beat the QRM every time. Essential vox and sidetone controls are located behind the front panel nameplate. Seven mode and function symbols confirm transceiver status at a glance.

The HW-5400's Frequency Entry Keypad option allows directly-synthesized QSY to any point in the band, and permits fast DX

## MORE ENJOYMENT

Novice or active pro, the HW-5400 is perfect for operators who want a Transceiver that's second to none, plus the pride, knowledge and satisfaction that come from building it yourself with our world famous step-by-step manuals. You may find it to be the first microprocessor-controlled rig with enough potential to match the level of professionalism in every radio amateur!

## MORE DETAILS IN CATALOG

**FREE!** For complete details and specs, get a copy of the latest Heathkit catalog. Remove and mail the coupon today or write: Heath Company, Dept. 011-994, Benton Harbor, MI 49022.

Visit your local Heathkit Electronic Center\* for an exciting hands-on tryout.



## There's more for the Ham at Heath

Also see our state-of-the-art SS-9000 Deluxe HF Synthesized Transceiver (pictured below), which can be controlled by a computer or ASCII terminal.

\*Units of Veritechnology Electronics Corporation in the U.S., a subsidiary of Zenith Radio Corp.

Please send me a FREE Heathkit catalog. 303

Mail to:  
Heath Company, Dept. 011-994  
Benton Harbor, MI 49022


Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

AM-436

 

# Heathkit®

Company

length long and, since this dimension is influenced by conducting materials near it, we must make it adjustable so that we can tune it precisely to the desired frequency.

Also, we must minimize the losses to maintain high Q and the sharpness of the filter. Silver-plating was out—for economic as well as practical reasons. Previous research showed that silver-plating at two-meter frequencies yields only marginal improvement—unless the plating is very heavy, the signal still penetrates beyond it to the base metal. Several articles on homemade cavities reported using brass or copper with apparently satisfactory results.

Another way to reduce the losses when the housing of the device is a relatively high resistance material is to increase the spacing between the stub and the housing, thus reducing the magnitude of the induced currents and hence the losses; however, the impedance of the circuit is also dependent upon these dimensions. The question, then, was how to ensure a proper impedance match into and out of the completed cavity filter. None of the references available covered this point; they only gave dimensions that had been used and worked, but did not back them up with theory so that the effects of variations could be determined.

A little more thought provided the answer, though. If the input and output coupling loops were made identical and mounted so that the relationship of each to the stub was identical to the other, the problem would be solved without even knowing what the stub/cavity combination impedance was. It would be like two identical transformers connected back to back—the load impedance would be transformed to

 


Fig. 1. Equivalent circuit of cavity filter.

whatever the stub/cavity combination required and then back down to the same impedance level in the other coupling loop.

With this encouraging reasoning, construction was begun. A source of brass tubing, of thin wall but quite rigid, was found at the local hobby shop. It comes in varying diameters and 12" (30.48-cm) lengths and is not expensive in the quantities required. I used a 1" (2.54-cm)-diameter length for the upper section of the stub, and a 3/4" (1.91-cm)-diameter length for the lower section, so that they could telescope together, allowing the length of the completed stub to be varied as required.

Since circulating currents in any resonant circuit can be quite high, as mentioned earlier, it appeared essential that the two sections be in very good electrical contact at all times. I used some finger stock from the junk box for this purpose, soldering it to the bottom of the upper tube and another piece to the top of the lower one. In this manner, when the two were telescoped together, we not only had good electrical connection, but also the smaller tube was held centered in the larger. The brass tubing used, however, is sufficiently "springy" that the finger stock is not necessary. You can simply saw a number of narrow slits in the ends of the tubing and form the fingers from the resulting tabs. It is a good idea to deburr the fingers thus formed with steel wool and to form slight "hooks" in them so that the contact is not made by sharp corners that

 


Fig. 2. Details of tuning stub construction.

might bind and hinder adjustment. Fig. 2 shows both the upper and lower stub assemblies in greater detail, including the homemade finger contacts.

Adjustment of the length of the assembled stub is accomplished by means of a threaded rod from the local hardware store. I chose a 1/4"-20 size. It is secured to the bottom of the inner stub section by means of a brass plumbing fitting. I chose one just slightly larger than the inside diameter of the stub tubing; I ground and filed it down to a snug fit and used it as the plug shown in the drawing. It is soldered to the stub and a nut, threaded over the end of the shaft, is soldered to it, thus ensuring that the threaded shaft is fairly well centered in the stub for smooth operation when tuning. Any of several standard brass plumbing fittings, such as adaptors to couple one size of pipe to another, will be satisfactory. Note that the threaded rod is soldered to the plug and the nut so that it may turn in relation to them.

A top plate for the cavity was made from some 1/16" (0.64-cm)-thick copper plate I had on hand. Any material could be used that is a good conductor, but brass, copper, or aluminum would be best. The latter, however, would require different (and probably difficult) methods for making mechanical and electrical connections to it; the copper or brass stock allows soldering them directly to it.

A clearance hole for the threaded rod was drilled in the center of the top plate and a suitably-sized nut soldered over it. The two sections of the stub were assembled and the threaded rod screwed into that nut. The upper tube of the stub assembly was then soldered to the top plate, centered as closely as I could manage.

A note here about soldering these pieces together: Trying to accomplish this task with a torch or large soldering iron proved difficult. Either I couldn't heat the entire assembly enough to get a good solder connection or it was heated so much that previously sol-

 


Fig. 3. Top plate assembly.

The BEST is still  
"made in U.S.A."



# MIRAGE

**American made RF Amplifiers and Watt / SWR Meters of exceptional value and performance.**

• 5 year warranty • prompt U.S. service and assistance

## RF AMPLIFIERS

### 2 METERS-ALL MODE

**B23** 2W in=30W out \$89.95  
(useable in: 100 mW-5W)

**B108** 10W in=80W out \$179.95  
(1W=15W, 2W=30W) RX preamp

**B1016** 10W in=160W out \$279.95  
(1W=35W, 2W=90W) RX preamp

**B3016** 30W in=160W out \$239.95  
(useable in: 15-45W) RX preamp  
(10W.=100W)

### 220 MHz ALL MODE

**C106** 10W in=60W out \$199.95  
(1W=15W, 2W=30W) RX preamp

**C1012** 10W in=120W out \$289.95  
(2W=45W, 5W=90W) RX preamp

**C22** 2W in=20W out \$89.95  
(useable in: 200mW-5W)

### RC-1 AMPLIFIER

**REMOTE CONTROL** \$24.95  
Duplicates all switches, 18' cable

## WATT / SWR METERS

- peak or average reading
  - direct SWR reading
- MP-1** (HF) 1.8-30 MHz  
**MP-2** (VHF) 50-200 MHz  
\$119.95

### 430-450 MHz ALL MODE

**D24** 2W in=40W out \$199.95  
(1W=25W)

**D1010** 10W in=100W out \$319.95  
(1W=25W, 2W=50W)


Available at local dealers throughout the world.

**MIRAGE**  
COMMUNICATIONS/EQUIPMENT, INC.

P.O. Box 1393, Gilroy, CA 95020 (408) 847-1857

dered parts came loose. The solution was to preheat the material in the kitchen oven to some temperature below the softening point of the solder; then a relatively small iron could be used to attach new pieces, without heating the surrounding area sufficiently to loosen previously-made joints.

The coupling loops were formed from 1/16" (0.64-cm) brass tubing from the same hobby shop source. They are formed to be 1 1/4" (3.18 cm) wide overall by 1 1/2" (3.81 cm) high, with extra material on the inner leg to protrude through the top plate, allowing for connection to the outside world. The offset shown in the accompanying drawings was used to provide clearance between the loop and stub adjustment screw as they came through the top plate and is 1/2" (1.27 cm) in size. I used a Teflon™ bushing, as shown in Fig. 3, to insulate the inner end of each loop where it passed through the top plate, but if not available, one could be fashioned from almost any scrap plastic. Be very careful that each loop is identi-

 

Close-up of the tuning stub, coupling loops, and shunt capacitor.

cal to the other and that both are mounted in an identical manner so that the impedance transformation for each is correct, as mentioned earlier.

The two loops were soldered to the top plate, positioned so that their inner side cleared the stub by 1/4" (0.64 cm), as shown in Fig. 3. It will be easier to position them accurately if a hole is drilled in the top plate where the outer leg of the loops should go and then the loops are soldered in these holes.

Next, I was faced with the problem of finding a suitable outer housing for the cavity. The construction articles in the references available included one calling for a 4" (10.16-cm)-diameter copper pipe for this material, 22 1/2" (57.15 cm) long. Such pipe is not readily available in my area and has to be ordered from some distance away. Also, it is available only in much greater lengths than required and is relatively expensive. I decided to find an alternative.

A search of the local hardware stores yielded nothing that would be adequate. Then, one day while doing my grocery shopping, I noticed that some brands of coffee came in one-pound cans that appeared to be about the desired diameter! Eureka! Remember the "beer-can" antennas of some years back? I had found my source of material for the cavity. The only question was if the tinned steel cans would have too much loss to be usable. I decided to try and see.

I wanted new cans that weren't corroded or dented; this meant stocking up on quite a bit of coffee. I decided to try four cans, giving an overall length of 22" (55.88 cm). After storing the fresh coffee in everything I could find in the kitchen, I proceeded to cut both ends out of three of the cans and leave the bottom in the other. They were soldered end-to-end, and then the open end was soldered to the underside of the top plate, centered on the stub.

 


Fig. 4. Cutaway view, assembled cavity filter. The trimmer capacitor used to insert a notch in the response curve is included.

 


Fig. 5. Test setup for tuning and evaluating the cavity filter.

The addition of a small aluminum box to the outside of the top plate and mounting two BNC connectors on its ends allowed connection to be made to the ends of the coupling loops. Adding a second nut to the threaded shaft to allow it to be locked in place after tuning and a knob to the top of the threaded shaft to make it easier to adjust completed the job. I had a cavity filter, but would it work?

Fig. 4 shows a cutaway view of the entire assembly and may be of use to those desiring to build their own cavity filter.

Tuning the filter and evaluating its performance showed promise of being a problem without the availability of a well-equipped laboratory. I had an old VHF signal generator and a frequency counter available; that combination would serve as an adequate source with precise frequency calibration. The signal generator had an output meter so I could keep the input signal constant, and valid measurements could thus be made. But I needed a detector to permit measurement of the output of the filter. If the attenuation of the filter was anywhere near as great as it should be, I would be trying to measure signal levels far below those readable on a VTVM with an rf probe.

Finally, I borrowed a technique used by hidden transmitter hunters—I used a two-meter receiver with an S-meter and a calibrated step attenuator between it and the filter to keep the signal out of the limiting range of the receiver. Fig. 5 shows the test setup. With this arrangement, I was able to make measurements of sufficient accuracy to tune the filter and to gain a reasonable feel for how it worked.

Actual tuning proved unexpectedly easy. Adjust the threaded rod for maximum

# The inside story on TEN-TEC's CORSAIR.

**All solid-state** broadband design.

**All 9 HF bands**—160-10M. All bands ready to go.

**Full output at 100% duty cycle**, all bands, any mode, even RTTY and SSTV. 200 W. input.

**Triple Conversion Receiver** with switchable RF Preamp. for sensitivity of 0.25  $\mu$ V on all bands with dynamic range of 90 dB or better. 3rd order intercept +15 dBm.

**Variable Bandwidth plus Pass-band Tuning.**

Narrow the bandwidth or move the passband anywhere in 2.4 kHz bandwidth. Standard 12 pole filter; optional filter converts to 16 pole performance.

**Dual-range, triple-mode, Offset Tuning** receiver, transmitter, or both— $\pm 1$  kHz or  $\pm 4$  kHz.

**Variable Notch Filter**—adjustable frequency, better than 50 dB depth.

**Speech Processor**—clipper/compressor design with up to 10 dB processing.


**Fast/Slow AGC** to suit conditions.

**Adjustable ALC** for maximum power without distortion.

**WWV Reception** 10 MHz band.

**Headphone Attenuator** to enhance signal-to-noise ratio.

**Variable Threshold Noise Blanker**

 

**5-Function Meter**—monitors collector current, processor level, peak forward power on voice and cw, SWR, and signal strength.

**LED Status Indicators** show when RF amp. is on, Processor on, ALC, and Offset.

**6-Digit Readout**—with LSI true frequency counter, accurate on both sidebands.

**Electret Polarizing Voltage** at Mic. Jack.

**Full or Semi Break-in** for cw.

**CW Signal Spotter**—easier to use, just match tones instead of zerobeat.

**High Articulation Keying**—3.5 msec rise-decay time.

**Complete Interfacing** for accessories—separate rec. ant., QSK linear, separate VFO, keyer, speaker, ant. relay, RTTY, Phone Patch, remote band switching.

**Less than 2% audio distortion**—compression loaded bottom mounted speaker.

**13V dc design**—for easy mobile operation.

**Made in the USA**—fully warranted for 1 year, final transistors for 5 years, pro rata. Backed by reliable American service.

**Full accessory line:** Remote VFO, Power Supplies, Microphones, Keyers, Antennas and Tuners, SSB and CW Filters.

**CORSAIR**—a new level of achievement in amateur radio design, with every feature for effortless, effective operation. Try CORSAIR at your TEN-TEC dealer—you'll discover what easy operating is all about. And what a remarkable value CORSAIR represents.


See your TEN-TEC dealer or write for full information.

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862

output at the frequency desired. Results indicated that the response was similar to that shown in Fig. 6; I had a filter. But it wasn't sharp enough for my needs—I needed (or at least wanted) additional attenuation at the repeater's transmitter frequency, 600 kHz above the receiver's frequency. Something else was needed.

Let's go back to theory for a minute. At resonance, the inductive reactance is exactly equal to the capacitive reactance of the circuit and each cancels out the other; that's the very definition of resonance. At frequencies below resonance, the inductive reactance is smaller than the capacitive reactance; hence, the overall result is a circuit that looks like a capacitor. Above resonance, the reverse is true, and the circuit appears to be an inductor. Since my transmitter frequency was above the receiver (filter) frequency, the filter would look like a small inductor there. If I put a small value of capacitance in parallel with the filter, it should be possible to make it resonate with this apparent inductance, hopefully at the frequency of the (undesired) transmitter output. This would, in effect, form a parallel resonant trap in series with the receiver input, just as the traps in many multiband antennas are formed. The results should be similar.

I used a 2-15-pF air trimmer. By alternately tuning the threaded rod for maximum output at the receiver frequency and the trimmer for minimum output at the transmitter frequency, I was able to achieve results similar to those shown in Fig. 7. The peak of the response fell at the desired receiver input frequency, while the notch in the response curve fell at the transmitter output frequency. The difference between the two measured on the or-

 

Detail showing top plate, coupling loops, and upper portion of tuning stub. Stub in this version was soldered to a threaded fitting which in turn was fastened in a hole in the top plate.

der of 16 to 18 dB and, because of suspected leakage around the cavity, is probably greater. Since some references claimed that the maximum rejection for such a cavity is about 20 dB, I wasn't doing too badly. I couldn't measure the insertion loss accurately, but it appears to be about 1.5 dB, which is entirely satisfactory and near the values quoted for commercially available cavities.

Subsequent investigation revealed that at the higher end of the tuning range, the Q appeared to be substantially higher, as evidenced by a sharper filter response. This is probably due to the fact that the distance between the center stub and the inside of the cavity is larger (in terms of a wave-

length), so losses are reduced; also, the end of the stub is further from the bottom of the cavity, also reducing losses. If I were planning to build another of these filters, I would try the larger 2-pound coffee cans and use five rather than four of them.

It has been many months since I built this filter. Rechecking its tuning and response curve indicates no change, even though I live in a high humidity area and some corrosion was expected; apparently it is tight enough that this will be no problem. I have detected no noticeable shift in its parameters due to temperature excursions, although I have not subjected it to wide extremes.

 


Fig. 6. Shape of the response curve of the cavity filter without shunt trimmer.

 


Fig. 7. Shape of the response curve of the cavity filter with shunt capacitor included.

The proof of the pudding is in the eating, they say, and the proof of this filter is in the system it was intended for. Without the filter, the very poor receiver I had responded to a 10-Watt signal anywhere in the two-meter band when the source was a few feet away from it; with the filter inserted between the antenna and receiver, an 80-Watt signal, at the same distance, has no effect until it is within about 30 kHz of the receiver frequency—the bandwidth of the filter included in the receiver's first i-f.

So what have we learned? It is possible, even easy, to make a cavity for your own use. It isn't expensive. Home tools and building techniques are more than adequate. Readily-available components can be used, and most dimensions are not at all critical. It is not difficult to tune up, and readily-available equipment can be used.

We don't have to pay a fortune for commercial cavity filters or duplexers for low-power use. While it may be advisable to do so for wide-coverage, heavily-used machines, we can quite easily use these for low-power, local-coverage machines. By substituting a small inductor for the trimmer capacitor, the notch can be moved to the low side of the response curve so several cavities can be connected together to form a duplexer; although adjusting the inductor would be more difficult than the trimmer, it can be done. Maybe now we can see more of these low-power, local-coverage machines, reducing the load on the wide-coverage systems. ■

#### References:

- The Radio Amateur's VHF Manual*, 3rd Edition, ARRL.
- VHF-UHF Manual*, 3rd Edition, RSGB.
- Electronics Engineers' Handbook*, 2nd Edition, Fink and Christiansen, McGraw-Hill.

# WORLD TIME WATCHES

the newest and best watches for hams from ACI



- 5 modes plus hourly chime
- dual time shows GMT & local time
- 12/24 hour time
- 5 year lithium battery

ACI's new HAM-II's functions include local time, a second time zone for GMT, count-up and count down stopwatches, alarm, hourly chime, and high brightness backlight. The special tri-function display shows a two-alpha day of the week, digital day-month, and six digit time in the main display. The second time zone display shows mode (T2), four digit local time and six digit GMT (or any other time zone). It's ideal for contests and logkeeping. The HAM-II, like its predecessor the HAM-I, is built rugged to last with a scratch resistant mineral glass crystal. The HAM-II case is polycarbonate, water resistant to 2.4 ATM, and the polyurethane band remains flexible even at very low temperatures.



- 4 modes plus hourly chime
- Independent analog/digital
- 12/24 hour time

ACI's HAM-III breaks the ana-digi price barrier with a rugged and functional, yet handsome watch for hams. It combines independently functioning analog and digital timepieces, both with quartz crystal accuracy. While the analog section is on local time, the digital section can display your choice of month-date-day, six digit time (ideal for GMT) with a 12/24 hour option, alarm time, or six digit chronograph. The HAM-III is built rugged with a scratch resistant crystal, die cast case, stainless steel band, and German time movement. The HAM-III is water resistant to 2.4 atm. It's available with a white face and stainless band, or goldtone face and stainless/goldtone band.

### SPECIAL OFFER

buy a HAM-II and a HAM-III and get a 10% discount off the HAM-III


HAM-II ..... \$22.95 HAM-III ..... \$49.95  
 HAM-III/stainless-gold ..... \$59.95  
 add \$3.00 per order for shipping and handling. CA. residents add 6 1/2% sales tax. VISA, M/C accepted.

To order, call or write:

Advanced Communications Int'l  
 2411 Lincoln Avenue  
 Belmont, CA. 94002  
 (415) 595-3949



448

 

144-148-13LBA




### WHY SETTLE FOR HALF THE BAND?

Enjoy super-gain, low VSWR, and FULL COVERAGE, 144 through 148 MHz, with less weight and windload. Dual-driven elements, balanced feed for a better match and clean pattern.


Bandwidth:	144-148 MHz	Balun:	2KW 4:1
Gain:	15.5 dBd	Boom:	21' .5/1 1/2"
VSWR:	1.2:1 & less	Windload:	1.6 sq ft
Beamwidth:	28°	Weight:	9 lbs

 CIRCULAR POLARIZED For the Phase IIIB satellite and terrestrial DX, ATV, and FM. Minimizes multipath and flutter fading. Rugged symmetrical construction.



420-450-18C

Bandwidth:	420-450 MHz	Windload:	.5 sq ft
Gain:	12 dBdc	Weight:	3.6 lbs
VSWR:	1.5:1 & less		
F/B:	20 dB		
Baluns:	2KW, 4:1 (2)		
Boom:	88" / 1"		

 

420-470-6

Boom:	2' / 1" O.D.	Beamwidth:	60°
Weight:	1.2 lbs	F/B:	20 dB, min

IDEAL for point-to-point and repeater control. Rear-mounted, vertically polarized, compact. Continuous coverage, 420-470 MHz. Direct coax feed suitable for most installations.

Bandwidth:	420-470 MHz
Gain:	8dBd
VSWR:	1.2:1 & less

### SEE YOUR KLM DEALER:

**KLM** Electronics, Inc. P.O. Box 816, Morgan Hill, CA 95037  
 (408) 779-7363



# Food for thought.

Our new Universal Tone Encoder lends its versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequency - just dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers' repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

- All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak
- Instant start-up.
- Off position for no tone output.
- Reverse polarity protection built-in.

## Group A

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 MI

- Frequency accuracy,  $\pm .1$  Hz maximum - 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- Continuous tone

## Group B

TEST-TONES:	TOUCH-TONES:	BURST TONES:			
600	697 1209	1600	1850	2150	2400
1000	770 1336	1650	1900	2200	2450
1500	852 1477	1700	1950	2250	2500
2175	941 1633	1750	2000	2300	2550
2805		1800	2100	2350	

- Frequency accuracy,  $\pm 1$  Hz maximum - 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Model TE-64 \$79.95

 **COMMUNICATIONS SPECIALISTS**

426 West Taft Avenue, Orange, California 92667  
(800) 854-0547/ California: (714) 998-3021



# Great Minds Think Alike.

Hertz . . . Marconi . . . Armstrong . . . they all would have read **73**. Why?

Great pioneers get their ideas from great pioneering articles. Armstrong read detailed accounts of Marconi's Cornwall to St. Johns transmission. Marconi was inspired by an article about the experiments of the late Heinrich Hertz. And Hertz was guided in his experiments by the theories of the English mathematician Maxwell.

Throughout its 22-year history, **73** has been a leader in the field of radio communications, publishing more articles that helped to pioneer new areas of amateur radio than any other ham magazine. Articles on single sideband, solid state, repeaters, narrow band communications, satellites . . . the list goes on and on.

Today, the spirit of the pioneer lives on in each and every issue of **73**.

You need **73**.


You need it to keep up with the latest radio news. You need it to stay abreast of the most recent technological developments. You need it to find out what your future rig will be like, and how you can modify your present rig to get more out of it, and what the word is on the latest gear, contests, DX . . . You need **73** to help you be the best ham you can be.

And who knows? Maybe the pioneering articles in **73** will inspire you to heights you never thought you could achieve . . . right up there with Hertz, Marconi, and Armstrong.

To order simply fill out the coupon below and send it in, or dial toll free

**1-800-258-5473.**

**Be a pioneer.  
Subscribe to 73.**

 

**YES!** I want to be a pioneer. Send me 12 issues of **73** for only \$19.97.

Canada \$22.97 US funds  
Foreign \$39.97 US funds drawn on US bank

Check  MC  VISA  AE  BILL ME

Card # \_\_\_\_\_  
Interbank # \_\_\_\_\_ Exp. Date \_\_\_\_\_  
Signature \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**73: Amateur Radio's Technical Journal** 333R6  
**Subscription Dept., P.O. Box 931, Farmingdale NY 11737**

Your first issue will arrive in 6 to 8 weeks.

# WAYNE GREEN BOOKS

## KILOBAUD KLASROOM

by George Young and Peter Stark

Makes learning electronics fun and easy. First published as a series in *Kilobaud Microcomputing*, the book combines the learning of essential theory with practical, hands-on experience. The course begins with basic electronic projects and culminates in the construction of your own programmable microcomputer. The direct instructional methods of authors Young & Stark make KILBAUD KLASROOM a simple way for you to acquire a solid background in digital electronics.

BK7386 (419 pages).....\$14.95



## THE SELECTRIC INTERFACE by George Young

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. The SELECTRIC™ INTERFACE, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Kilobaud Microcomputing* magazine's popular "Kilobaud Classroom" series, offers a low-cost alternative to buying a daisy wheel printer. The SELECTRIC INTERFACE includes: step-by-step instructions, tips on purchasing a used Selectric, information on various Selectric models, including the 2740, 2980, and Dura 1041, driver software for Z80, 8080, and 6502 chips, tips on interfacing techniques. With The SELECTRIC INTERFACE and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.

BK7388 (125 pages).....\$12.97




## GENERAL LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-and-answer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world.

SG7358 (87 pages).....\$6.95

 


## NOVICE LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

Here is the most up-to-date novice guide available. It is complete with information about learning Morse code, has the latest FCC amateur regulations and the current FCC application forms. This guide is *not* a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price.


SG7357 (98 pages).....\$4.95

 

## THE NEW WEATHER SATELLITE HANDBOOK by Dr. Ralph E. Taggart WB8DQT

Here is the completely updated and revised edition of the best-selling *Weather Satellite Handbook*—containing all the information on the most sophisticated and effective spacecraft now in orbit. Dr. Taggart has written this book to serve both the experienced amateur satellite enthusiast and the newcomer. The book is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Not just ideas, but solid hardware designs and all the instruction necessary to operate the equipment are included. For the thousands of experimenters who are operating stations, the book details all procedures necessary to modify their equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment.

BK7383 (132 pages).....\$8.95

 

## FOR TOLL-FREE ORDERING CALL 1-800-258-5473 WAYNE GREEN BOOKS•PETERBOROUGH NH 03458

Itemize your order on a separate piece of paper and mail to Wayne Green Books, Attn: Sales, Peterborough, NH 03458. Be sure to include check or detailed credit card information. (Visa, MC or AMEX accepted.) No C.O.D. orders accepted. All orders add \$1.50 for the first book, postage and handling; \$1.00 each additional book; \$10.00 per book foreign air mail. Please allow 4-6 weeks after publication for delivery. Questions regarding your order? Please write to Customer Service at the above address.

... at last - everything at your

**fingertips !!!**



**\$184<sup>50</sup>**

Radio Equipment  
NOT Included  
F.O.B. Culver City  
(CA Residents add 6% sales tax)

Bring ORGANIZATION & CONVENIENCE to your HAM Station! Eliminate clutter and provide lots of space for everything you need - Tuners, VFO, CW Keyers, Filters, Telephone, Log Book, Etc...

- ANGLED REAR SHELF
  - ALL PARTS FITTED
  - STURDY CONSTRUCTION
  - WALNUT or PECAN FINISH
- Floor space: 39" w by 30" d.  
Also: 51" w by 30" d - \$199.50  
Dealers Inquiries Invited

**A Finely Crafted Piece of Furniture  
With a REAL Purpose . . .**

Call : (213) 837-4870 or Write for Information

**S-F Amateur Radio Services**

4384 Keystone Ave., Culver City, CA 90230

**QUALITY SPECIALS**

**MONSTER-SIZED MULTI-PAKS \$10.95 each**  
(You are guaranteed brand new merchandise from manufacturers such as: Solimans, I.C.C., Panasonic, Micron, etc.)

PART #	PIECE COUNT	DESCRIPTION
PK001	100	ASSORTED LOW VALUE ELECTROLYTIC CAPACITORS (VARIOUS VALUES LESS THAN 500 MFD)
PK002	40	ASSORTED MEDIUM VALUE ELECTROLYTIC CAPACITORS (VARIOUS VALUES FROM 1000MFD TO 10000MFD)
PK003	2 DOZEN	ASSORTED HIGH VALUE ELECTROLYTIC CAPACITORS (VARIOUS VALUES FROM 1000MFD TO 9000MFD)
PK004	40	ASSORTED LOW VALUE DIPPED TANTALUM CAPACITORS (VARIOUS VALUES FROM 0.1MFD TO 2MFD)
PK005	2 DOZEN	ASSORTED HIGH VALUE DIPPED TANTALUM CAPACITORS (VARIOUS VALUES FROM 1.0MFD TO 60MFD)
PK006	50	LOW PROFILE SOLDER PIN SOCKETS TEN EACH OF 8, 14, 28, AND 40 PIN SOCKETS
PK007	200	LOW VALUE 1/2% RESISTORS (W/ AT LEAST 35 DIFFERENT VALUES LESS THAN 100 OHMS ARE GUARANTEED)
PK008	200	MEDIUM VALUE 1/2% RESISTORS (W/ AT LEAST 35 DIFFERENT VALUES BETWEEN 100 AND 10,000 OHMS ARE GUARANTEED)
PK009	200	HIGH VALUE 1/2% RESISTORS (W/ AT LEAST 30 DIFFERENT VALUES BETWEEN 10K AND 15M OHMS ARE GUARANTEED)
PK010	132	SAME AS PK007 BUT RESISTORS ARE WATT 1/2%
PK011	132	SAME AS PK008 BUT RESISTORS ARE WATT 1/2%
PK012	132	SAME AS PK009 BUT RESISTORS ARE WATT 1/2%

**MONSTER JR. MULTI-PAKS \$2.95 EACH.**

ANY OF THE MULTI-PAKS ABOVE ARE AVAILABLE WITH 1% PIECE COUNT FOR \$2.95 PER PAK. SPECIFY JUNIOR PAK AFTER THE PART NUMBER, THE I.C. SOCKET JR. PAKS AND THE 1/2 WATT RESISTOR JR. PAKS MAY DIFFER SLIGHTLY FROM THE FULL SIZE PAKS DESCRIPTION.

**SOPHISTICATED I.C.'S**

DATA SHEETS AND APPROPRIATE APPLICATION NOTES ARE PROVIDED FREE WITH ALL INTEGRATED CIRCUITS LISTED BELOW

PART # & MANUF.	DESCRIPTION	PRICE (#s)
ROD104 (LSI COMP SYS)	CMOS DIVIDER I.C. HAS TRUTH-TABLE SELECTABLE INPUT TO FIELD DIVIDE BY 10, 100, 1000, OR 10000 OUTPUTS	\$ 1.30
LS7031 (LSI COMP SYS)	D.C. TO 50MHZ SIX DECADE MOS UP COUNTER WITH 8 DECADE LATCH AND MULTIPLE BCD OUTPUTS AND DIGIT STROBES. ACCESS TO L5D LATCHES ALLOW ATTACHMENT OF PRESCALERS FOR COUNTING TO 1000MHZ	\$ 1.75
LS7220 (LSI COMP SYS)	14 PIN CMOS AUTOMOTIVE MARINE ANTI-THEFT DIGITAL LOCK CIRCUIT HAS 5000 4-DIGIT COMBINATIONS WITH 25 MICROAMP STANDBY. SAVE MODE FOR VALET PARKING	\$ 3.00
ZM3050 (FERRANTI)	3-DIGIT DIGITAL MULTIMETER I.C. WITH LCD DRIVE ON CHIP CLOCK AND REFERENCE A COMPLETE DVM CIRCUIT CAN BE MADE WITH 8 PASSIVE EXTERNAL COMPONENTS	\$ 14.25
14ND1010 (FAND CORP.)	3-DIGIT LCD DISPLAY	\$ 12.00

**CAPACITORS**

DIPPED TANTALUMS (#s)		AXIAL ELECTROLYTICS (#s)		RADIAL ELECTROLYTICS (#s)	
1 mfd 35V	30	1 mfd 40V	15	1 mfd 50V	5
22mfd 35V	30	1.5mfd 25V	15	2.2mfd 35V	10
22mfd 50V	30	4.7mfd 16V	15	4.7mfd 16V	10
47mfd 35V	30	10 mfd 63V	17	33 mfd 25V	13
1.0 mfd 35V	30	47 mfd 25V	17	47 mfd 16V	13
1.5 mfd 35V	30	100 mfd 25V	17	220 mfd 25V	10
2.2 mfd 16V	25	220 mfd 10V	27	470 mfd 25V	25
8.2 mfd 35V	25	470 mfd 10V	27	560 mfd 25V	25
10 mfd 35V	1.80	1000 mfd 25V	81	1000 mfd 25V	73
100mfd 16V	80	2200 mfd 10V	80	2200 mfd 10V	70
68mfd 10V	1.80	2200 mfd 35V	177	3300 mfd 10V	85

**GOLDSMITH SCIENTIFIC CORPORATION**

P.O. Box 318 B, COMMACK, NY 11725  
PHONE ORDERS WELCOME—(516) 979-7944  
MINIMUM ORDER \$10.00—U.S. FUNDS ONLY  
NEW YORK STATE RESIDENTS ADD SALES TAX  
POSTAGE—ADD 8% PLUS \$1.50 INSURANCE C.O.D. \$2.00 EXTRA  
MASTER CHARGE AND VISA ACCEPTED  
AVAILABILITY OF CERTAIN ITEMS MAY BE LIMITED

**HOT ROD ANTENNA**

Achieve 1 or 2 db gain over ANY 1/2 wave two meter telescopic antenna. The AEA model HR-1 Hot Rod™ antenna was designed by Dr. D.K. Reynolds (designer of the IsoPole) to deliver maximum performance for any hand-held transceiver with a BNC fitting.

The factory-tuned HR-1 is 20% shorter, lighter and places far less stress on your hand-held connector and case. It will easily handle over 25 watts of power, making it an excellent emergency base or mobile antenna. In the collapsed position, the Hot Rod antenna will perform like a helical quarter wave.

The Hot Rod antennas can be expected to make the same improvement to hand-held communications that the IsoPole brand antennas have made to base station operations. Why pay more when the best costs less?

Prices and Specifications subject to change without notice or obligation.

**ADVANCED ELECTRONIC APPLICATIONS, INC.**

P.O. Box C-2160, Lynnwood, WA 98036  
(206) 775-7373  
Telex: 152571 AEA INTL

**AEA Brings you the Breakthrough!**

**Have You Ever Used Satellites?**  
**Let the Pathfinder Series FROM**



**Make It Easy For You**

**Pathfinder II**

**A Satellite Tracking Package For The Apple II Plus™**



Has a world AND a US map and can print BOTH on your Epson MX™ printer. Tracks in real time w/o a clock. SYSTEM REQUIREMENTS: Apple II Plus. 48K RAM. DOS 3.3.

THESE EASY TO USE AND UNDERSTAND PACKAGES ENABLE YOU TO: (1) Track circular orbit satellites in real time on a world map. (2) Print all data tables on your printer. (3) Rapidly predict accessible orbits, reference orbits and all orbits between your specified dates. (4) Rapidly compute AOS time, LOS time, time in range, maximum elevation, CPA time, and CPA range. (5) Maintain a disk resident data base of satellite reference data.

Pathfinder II is provided on a DOS 3.3 disk and Pathfinder III is on a TRSDOS 1.3 disk. Both have a comprehensive users manual.

**Pathfinder III**

**A Satellite Tracking Package For The TRS 80 Mod III™**



Pathfinder III can track TWO satellites simultaneously!! SYSTEM REQUIREMENTS: TRS 80 MOD III. 48K RAM, TRSDOS 1.3.

All this is included for only **\$34.95**

Please add \$2.00 for shipping and handling (California residents add 6% (\$2.10) sales tax).

Send Check or Money Order To:  
**COMPUTER APPLICATIONS**  
3628 A Court, Oxnard, CA 93033

# Push Your Radar Detector to the Limit

*Without this simple modification, you won't know what you are missing—until it's too late.*

The use of speed-detection radar devices by law-enforcement agencies as a means of enforcing speed-limit laws is becoming very controversial in the

United States. A court in Miami, Florida (Dade County) already throws out radar speeding cases if there is no other data presented. The State of Kentucky has a

court case pending to determine the validity of radar as a speed-law enforcement tool. If the courts later rule that radar cannot be used as a means of enforcing the

speed laws of the country, radar sets will probably not be used by enforcement agencies. The auto radar detector thus would no longer have an operational requirement. What will you do with your radar detector which has accompanied you so faithfully in your auto all these past years?

## Extend Its Usefulness

Until such time that auto radar detectors become "useless," in the sense that they may not be needed to provide an alerting function for you, a simple modification to almost any detector will let you extend your use and interest in a radar detector. Before we go into how the simple modification works, let's review how the speed radar works so we will better understand our radar detection operation.

Law enforcement agencies use the familiar Doppler shift principle (named after Johann Doppler, 1803-1853) to determine the speed of a vehicle. A hand-held radar transmitter emits about 100 milliwatts of continuous microwave energy



*The author's radar detector modified to receive signals from 5 to 15 GHz. Both receiver and audio amplifier operate off 9-volt batteries and are self-contained.*

 


Fig. 1. Pulse radar signal (a) and audio signal (500 pps) when detected at a distance (b).

at 10,525 MHz (X-band) or 24,100 MHz (K-band). The radar signal is concentrated in a narrow beam by a horn-type antenna so that the target vehicle is illuminated with the maximum amount of energy. Because of the movement of the vehicle, the 10,525-MHz signal is Doppler-shifted up in frequency about 940 Hz for an auto traveling at 60 mph. This upward Doppler shift is obtained for the emitter stationary (but vehicle moving) and is arrived at by the expression: Emitter stationary:  $f_{D1} = f_1[(V + V_0)/V]$ , where  $f_{D1}$  is the Doppler shift frequency in Hz,  $f_1$  is the operating frequency (10,525 MHz),  $V$  is the velocity of light, and  $V_0$  is the velocity of the vehicle in same units as  $V$ .

However, the transmitted signal must now be returned (reflected) to the radar receiver. So now the vehicle acts like a transmitter and originates (reflects) a signal (emitter moving) which also is Doppler-shifted up in frequency when it arrives at the radar receiver. The returning signal is shifted up in frequency according to the expression: Emitter moving (vehicle):  $f_{D2} = f_2[V/(V - V_S)]$ , where  $f_{D2}$  is the Doppler shift frequency in Hz,  $f_2$  is the reflected frequency (vehicle) (10,525 MHz +  $f_{D1}$ ),  $V$  is the velocity of light, and  $V_S$  is the velocity of source (vehicle) in the same units as  $V$ .

We thus find that the total Doppler-shifted frequency is equal to  $f_{D1} + f_{D2}$ . For a vehicle traveling at 60 mph toward a radar, the total

Doppler-shifted frequency is equal to 950 Hz + 950 Hz for a total shift of 1900 Hz. We arrive at this frequency after accounting for the original frequency of 10,525 MHz. This is about 31 Hz per mile for a radar operating at a frequency of 10,525 MHz. The total Doppler shift for a K-band radar would be about 2.3 times greater, or 72.5 Hz per mile.

The speed radar receiver must now process the Doppler-shifted frequency into miles per hour and then display and store it for record until the display is reset, awaiting another vehicle. The speed radar has to be triggered on for only a few seconds in order to lock on and obtain a good speed reading on a vehicle, although older units may be left on all the time. The time available to "hear" the radar transmitter, therefore, isn't very long.

### How the Auto Radar Detector Works

**Pulse Radar.** Before the auto radar detector came along, there was only the radar speed detector. But with the advent of the auto-equipped radar detector, the detector became the detectee! (Or the chaser became the chasee.) And so the hunt has continued for about 30 years.

Old speed radar sets used the pulse principle as was used during World War II. Fig. 1 shows a series of radar pulses used to determine range to a target and the audio (500 pulses per second) produced by a diode detec-

 


Fig. 2. Continuous-wave (CW) radar signal (a) produces no audio signal when detected at a distance (b).

 


Fig. 3. Standing waves on a shorted transmission line. In (c) we see that a short is reflected every half wavelength.

tor receiver when listening to the radar. The rapid turning on and off of the radar carrier produces a music-like audio tone when the radar signal is detected and amplified.

**Doppler Radar.** Speed radar sets for the past 20 years or so have employed a continuous-wave transmitter, that is, one not modulated with any type of signal. It depends on the rapid Doppler shift in frequency (up in frequency when approaching and down when receding) to produce a shift in frequency which can be equated to velocity of a target rather than

Fig. 4. Standing waves on an open transmission line. In (c) we see that an open is reflected every half wavelength.

distance to a target as in the pulse-radar case. However, as we see in Fig. 2, the continuous carrier signal does not produce an audible signal when you detect and listen to it. Since there is no modulation on the signal at the transmitting end, we must do something to it at the receiving end so that we can detect its presence. And, of course, we must do this as inexpensively as possible as many consumer units will be bought.

**Chopping the Radar Signal.** You have no doubt driven or walked down a tree-studded roadway when the

 


Fig. 5. Auto radar detector diagram showing chopping diode, detector diode, audio amplifiers, comparison circuit, and alerting buzzer or sounder.

sun is shining brightly. As you move along, bursts of sunshine are seen to stream through the foliage between patches of shadows. We are observing the modulation of the sun's steady rays of light where they are rapidly "turned on and off" by the foliage. In much the same manner, we will interrupt, or chop, the radar signal we receive so that we can process it to turn on an audio-altering device or a visual indicator.

In order to fully appreciate the uniqueness of the technique used to "chop" the radar signal, let's take a look at some fundamentals as they relate to antenna transmission lines.

**The Shorted Transmission Line.** When you take a transmission line such as an open-wire line or coax line as used in your amateur radio or CB mobile installation and short it at the antenna end, you will have zero volts across the end (as shown in Fig. 3). We see a generator sending a signal down the lines with a short at the right-hand end (a). In (b) we see that on a line terminated in a short, the voltage is zero at the end and maximum one-quarter wavelength back from the end. We see, also, that the short is repeat-

ed every half wave at the operating frequency (c). No voltage exists at the short, although the current is maximum. This can be likened to placing a screwdriver (zero Ohms) across an ac outlet of 115 volts. There will be a lot of current flowing till the fuse blows or the circuit breaker trips out, but there won't be any voltage! (Don't try this at home!)

**The Open Transmission Line.** Now let's look at an open terminated transmission line. In Fig. 4, we see a generator driving a signal down the line (a). In (b) we see that there is maximum voltage at the open end of the line and every half wave back toward the generator. In (c) we also see that the open circuit becomes a short circuit just one-fourth wavelength back from the open end.

What we have here is a means of chopping the radar signal as it comes down the waveguide transmission line from the horn antenna used in most radar detectors. What we do is to cause a diode placed across the transmission line to act as an open and a short, alternately, at an audio rate between 1000 and 3000 times per second. When a diode conducts in the forward direc-

tion, it acts like a short circuit (very low resistance) but when it does not conduct, it acts as an open circuit (very high resistance).

**The Radar Diode Detector.** An abbreviated circuit and block diagram of my Snooper (Autotronics, Inc.) radar detector is shown in Fig. 5. The shorting, or chopping, diode is turned on and off by the multivibrator circuit which puts out a square-wave signal at an audio rate of 1000 to 3000 pulses per second. Note that when the shorting diode is conducting (anode positive), it acts as a short in the waveguide. A half wave away, a short is also reflected so that the detector diode is shorted. The detector diode is one-fourth wavelength away from the short in the end of the waveguide so that it always appears as an open, free to detect and rectify any microwave energy coming down the waveguide from the 10-dB gain horn antenna that is chopped up by the shorting diode.

**The Comparison Circuit.** The detected audio from the detector diode is amplified in several IC chips (type 741) and then routed to a comparison or coherent detector where it is compared to an audio signal arriving from

the 1000-Hz multivibrator. A manual sensitivity control is used to set a level at which the audio alarm buzzer or lamp is turned on. The comparison circuit is activated when the signal arriving from the detected audio channel (outside signal) is stronger than the signal from the multivibrator (inside signal). This means a radar signal is being received and the alarm is activated.

**The Case of the False Alarm.** There are a number of signals, however, that can activate the detector, other than a real speed radar signal. We will look at the signals in greater detail further on, but let's examine what happens when you receive a signal. The first thing you do is to look for the speed radar vehicle. Not seeing one, but the audio alarm is still sounding off, you turn the manual sensitivity control down until the sounder stops. However, what you have done is to make your detector less sensitive to outside signals. You are now very likely to get "pinged" by a real speed radar and not know it (till the bubble machine starts!).

**Modify Your Detector to Receive Other Signals.** What we will do at this time is to make a slight modification to your detector—to add an audio output capability. We then run this audio output to a small self-contained packaged audio amplifier so that we can listen to all signals that are detected by your receiver. We will let your ear become trained so that it can tell the difference between a pulse radar from an airplane, an airport radar, a strong TV station, or a real bubble-machine emitter!

Referring to Fig. 5, we see a dotted area which shows the added circuitry to provide the audio output capability. Any battery-operated audio amplifier will do the job, and one readily-available is the speaker/amplifier from Radio Shack No. 277-1008 for under \$12.00. The

# THE AUTEK "QRM ELIMINATOR"



**Model QF-1A  
For SSB & CW  
\$69.00 (+ \$4)**

115 VAC supply built-in. Filter by-passed when off.

Auxiliary Notch rejects 80 to 11,000 Hz! Covers signals other notches can't touch.

Four main filter modes for any QRM situation.

Continuously variable main selectivity (to an incredible 20 Hz!)

Continuously variable main frequency. (250 to 2500 Hz)

AUTEK pioneered the ACTIVE AUDIO FILTER back in 1972. Today, we're still the engineering leader. Our new QF-1A is the latest example. It's INFINITELY VARIABLE. You vary selectivity 100:1 and frequency over the entire usable audio range. This lets you reject whistles with dual notches (to 70 dB), or reject SSB hiss and splatter with a fully adjustable lowpass plus aux. notch. Imagine what the NARROWEST CW FILTER MADE will do to QRM! HP rejects low frequencies. Skirts exceed 80 dB. 1 watt speaker amp.

Built-in 115 VAC supply. 6 1/2 x 5 x 2 1/2. Two-tone grey styling. Even latest rigs include only a fraction of the QF-1A selectivity. Yet it hooks up in minutes to ANY rig—Yaesu, Kenwood, Drake, Swan, Atlas, Tempo, Heath, Collins, Ten-Tec, etc. Just plug it into your phone jack and connect spkr. or phones to the output. Join the thousands of owners who now hear stations they couldn't copy without a QF-1A! It really works!

## WORLDS RECORD KEYS. OVER 4000 DX QSO'S IN 2 DAYS!



**\$100.50 (+ \$4)**

Model MK-1 Keyer

Probably the most popular "professional" contest keyer in use, yet most owners are casual CW operators or novices. After a few minutes, you'll see how memory revolutionizes your CW operation! Just start sending and record your CQ, name, QTH, etc. in seconds. 1024 bits stores about 100 characters (letters, numbers). Playback at any speed. Dot/dash memories, triggered clock, repeat, combine, 5 to 50+ WPM, built-in monitor and 115 VAC supply. Works with any paddle. Sit back and relax while your MK-1 calls CQ and handles standard exchanges!

Optional memory expander (ME-1) expands any MK-1 to 400 characters. ME-1 factory installed \$35. Owner installed, only \$21 (+ \$4). Add more memory now or later!

*Autek Research*

BOX 302 DEPT. S

ODESSA, FLORIDA 33556 • (813) 920-4349

**NO LONG DELAYS. WE SHIP 95% OF  
ORDERS FROM STOCK**

We sell only factory direct. No dealer markup in our price. Order with check, M.O., VISA, MC. Add \$4 postage and handling in 48 states. (\$7 for UPS air). Add \$7 to Canada, HI., Ak. Add \$22 elsewhere (shipped air). Add 5% tax in Fla.

*Radio World*

CENTRAL NEW YORK'S MOST COMPLETE HAM DEALER



Featuring Kenwood, Yaesu, Icom, Drake, Ten-Tec, Swan, Dentron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Grain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Bird, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure, Collins, AEA. *We service everything we sell!*

Write or call for quote. You Won't Be Disappointed.

We are just a few minutes off the NYS Thruway (I-90) Exit 32

OUT OF STATE  
ORDER TOLL FREE  
800-448-9338

ONEIDA COUNTY AIRPORT TERMINAL BUILDING  
ORISKANY, NEW YORK 13424

Warren - K2IXN  
Bob - WA2MSH  
Al - WA2MSI

N Y Res Call (315) 736-0184

## PORTAPEATER™

**\$179.00 assembled  
unit**

**M100 A**

**\$99.00 assembled  
board**

**INSTANT REPEATER  
ANY BAND ANY MODE**

• 4 Channel PROM  
CW I Der

• VOX or COR  
operation

• 250 volt  
switching  
capability

• An Instant  
Repeater

• Works with any  
type radios

• Complete Timer  
Functions

• Built In Test  
Functions


• 20 Page  
Technical Manual



(Fully tested, programmed, assembled) ✓ 302

**W-S ENGINEERING P.O. BOX 58, PINE HILL, N.J. 08021  
(201-852-0269)**

**BUTTERNUT  
ELECTRONICS  
COMPANY**

 

Model 2MVC "Trombone"  
Model HF6V  
Model 2MVC-5 "Super Trombone"

**THE  
WINNERS**

Model HF6V. Completely automatic bandswitching 80 through 10 plus 30 meters. Outperforms all 4- and 5-band "trap" verticals of comparable size. Thousands in use worldwide since December '81! 160 meter option available now. retrofit kits for remaining WARC bands coming soon. Height: 26 ft/7.8 meters; guying not required in most installations.

Model 2MVC "Trombone" — omnidirectional collinear gain vertical for 2 meters having the same gain as "double-1/4" types, but the patented "tombone" phasing section allows the radiator to remain unbroken by insulators for maximum strength in high winds. No coils "plumber's delight" construction and adjustable gamma match for complete D.C. grounding and lowest possible SWR. Height: 9.8 ft/2.98 meters

Model 2MVC-5 "Super-Trombone" — Same advanced features as the basic 2MVC but a full wavelength taller with additional "Trombone" phasing section for additional gain. Height: 15.75 ft/4.8 meters

All BUTTERNUT ANTENNAS use stainless steel hardware and are guaranteed for a full year. For further information on these and other BUTTERNUT products write for our FREE CATALOG!

**BUTTERNUT  
ELECTRONICS**

GARY AIRPORT, BOX 356 E. RTE 2  
SAN MARCOS, TEXAS 78666

 


Fig. 6. Arrangement to probe for detector audio circuit. A hiss shows you have located a suitable point to connect the audio output.

 


Fig. 7. Radar receiver modified to operate off a 9-volt battery for hand-carry operation.

 


Fig. 8. Block diagram of typical X- and K-band radar detectors. Audio output modification covers both bands.

photo shows my Snooper detector modified for ear-phone output and an audio amplifier connected by a short piece of shielded audio cable which has male miniature audio connectors on each end.

In order to locate a circuit connection point in your detector which has sufficient audio voltage to drive the amplifier, use the arrangement shown in Fig. 6. Remove your detector from its housing, and with power applied to both units, probe the circuit board near where the manual sensitivity control is wired. There will be several points in the circuit where you will hear white noise, or hiss. This tells you that you have located an audio tone present of 1000 to 3000 Hz. This is the chopping or switching rate that you are hearing and it tells you that the unit is operating properly. When you shut off the radar detector (but

leave the audio amplifier on), you may hear the tone become very clear as the white noise disappears before the switching tone. This may not occur in all modified units.

I have added a 9-volt transistor battery and switch to the detector/receiver so that the unit is entirely self-contained and can be hand-carried anywhere. It can be used on aircraft, boats, bicycles, and the like. Connect the battery to the same circuit point as the auto cigarette lighter as shown in Fig. 7. A battery will operate the radar receiver for a number of months with several hours use each day.

Connect the audio circuit as shown in Fig. 5 using a capacitor of 0.01 to 100 μF. To help you make the simple modification to your detector, ask a radio amateur or CB repair shop for assistance. You need not alter the appearance of your de-

detector if you run a pair of small size wires outside your unit where the audio pair can connect to the amplifier.

### Radio Signals You Can Receive

Now that you have modified your radar detector, you will be able to receive other radio signals. So that you will now know what signals you are receiving, leave your unit operating at its maximum sensitivity while you ignore those signals, keeping an alert ear open for the pure tone of a speed radar as it grows slowly out of the noise level. Remember, your detector is a fairly inexpensive device which is called upon to do a rather scientific task—receiving weak continuous-wave radar signals. As such, it is also subject to receiving and detecting any radio energy which is able to enter its detection circuits. You will use your ear to reduce the false alarm rate, and at the same time greatly increase your interest in your electronic surroundings. Let's look at some of the radar signals you may receive on your converted radar detector.

**Speed Radar.** Two bands are authorized by the FCC: X-band—10.525 GHz (10.5–10.55 GHz), and K-band—24.15 GHz (24.05–24.15 GHz). Power output—100 milliwatts (times antenna gain).

Stationary hand-held units are usually detected at about a half-mile away. If the transmitting unit is on continuously, you will hear the signal begin weakly as a pure tone of 1000 Hz or so, growing out of the white noise hiss. This hiss will not disturb you as it will be masked by road and car noise. But when that pure tone-signal jumps up at you, you'll know you have a live one! Remember—the signal you hear out of your detector (1000 Hz or so) is the switching frequency of the chopping diode. It has noth-

ing to do with any Doppler frequency shift associated with vehicle velocity. You will hear the signal with both vehicles stationary if the radar is transmitting. The longest distance over which I have detected signals, over several hills and dales, is 8 miles. But you must be line-of-sight to the radar to hear him and hope he "pings" someone else so you will be able to hear him.

My modified Snooper covers only the X-band, so you may be pinged on K-band and not know it unless your unit has both X- and K-bands. There is presently little operation in K-band, but its use is increasing. In Fig. 8 we see the block diagram of typical X- and K-band detectors, with one modification covering both bands since there is a common audio channel.

Many law-enforcement vehicles will drive around with the radar switched on and transmitting all the time. The hand-held unit, aimed like a spot light, is temporarily placed face down on the front passenger seat. However, enough radio energy is scattered out of the vehicle so that you can detect it several blocks away, be it moving or stationary. You will also be able to detect a radar vehicle passing in the opposite lane of a divided highway from several blocks away. When you receive these signals on your receiver, you will know that you have achieved a good sensitivity level as the radar unit does not have its antenna beam aimed out of the car.

**Aircraft Radar.** These radars operate in the range of 9300–9500 MHz and usually are heard during inclement weather when the radar is used to navigate around bad weather. You'll hear a "zip-zip" as the airborne antenna sweeps back and forth. You'll be able to track it for many miles as you aim your

**RTTY - 50**  
Basic Terminal Unit

- 60 mA Loop Keying
- PLL Demod w/2 pole filter
- AFSK Generator

**\$7900**

Call or write for **FREE** catalog with over 65 P.C. Boards & Kits.

**RTTY - 100**  
Expanded Version of the Popular  
RTTY - 50

- AFSK
- 850/170
- TTL & RS232
- 60 mA Loop
- Loop Supply
- Auto Start
- 4 Pole Filters
- AGC (80db)

**\$18900**

**COMMUNICATIONS DESIGN INC.**

1105 Lehr St. — West Memphis, Arkansas 72301  
(501) 735-4568

**ALL BAND TRAP ANTENNAS!**

PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. INPUT FOR NOVICE AND ALL CLASS AMATEURS! IMPROVED DESIGN!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6"- you just switch to band desired for excellent worldwide operation - transmitting and receiving! Low SWR over all bands - Tuners usually NOT NEEDED! Can be used as inverted V's - slopers - in attics, on building tops or narrow lots. The ONLY ANTENNA YOU WILL EVER NEED FOR ALL DESIRED BANDS - WITH ANY TRANSCEIVER - NEW - EXCLUSIVE! NO BALUNS NEEDED!

80-40-20-15-10-6 meter - 2 trap --- 104 ft. with 90 ft. RG58U - connector - Model 998BUC... \$89.95  
40-20-15-10 meter --- 2 trap --- 54 ft. with 90 ft. RG58U - connector - Model 1001BUC... \$88.95  
20-15-10 meter --- 2 trap --- 26ft. with 90 ft. RG58U - connector - Model 1007BUC... \$87.95

SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical - customs etc) or order using VISA - MASTER CARD - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES MAY INCREASE... SAVE - ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM WESTERN ELECTRONICS Dept. A7- 3 Kearney, Nebraska, 68847 ✓80

**GILFER'S**  
"BEST SELLER"  
SHORTWAVE  
BOOKS



New 5th Edition

**CONFIDENTIAL FREQUENCY LIST**  
Identifies 9,000 non-broadcast shortwave stations (utility, coast, military, FAX, etc.) from 4-28 MHz. Includes "Updater" \$10.95 ppd USA, \$13 UPS, US\$16 elsewhere. Updater separately \$2.50.

1983 Edition

**WORLD RADIO TV HANDBOOK**  
"Bible" of the SWL - comprehensive list of all shortwave broadcasters with all details - plus new receiver reviews. \$17.50 ppd USA, \$19 UPS; US\$25 elsewhere.

Totally New 2nd Edition

**GUIDE TO RTTY FREQUENCIES**  
Details on 5,500 radioteletype stations (including Press skeds) plus reverse list by call sign. How to read USSR Cyrillic. \$9.95 ppd USA, \$12 UPS; US\$14 elsewhere.

- SPECIAL OFFERS SAVE**
1. CFL+Updater+RTTY: \$21, UPS.
  2. CFL+Updater+WRTVH: \$27, UPS.
  3. RTTY+WRTVH: \$26, UPS.
  4. ALL 3 BOOKS: \$36, UPS.

NOTE: All SPECIAL OFFER books shipped UPS (Except Canada, AK & HI). First Class Mail add \$1.00, per book. Non-UPS orders shipped USPS Book Mail.

• Receivers • Accessories • Books •  
**GILFER SHORTWAVE**  
Dept.733, Box 239, Park Ridge, NJ 07656  
USA Phone 201/391-7887

**LINEAR**  
2 TO 400 MHZ  
**PLANBOOK**

15 to  
1000 WATT

14 Different Models, 100 pgs  
\$11.95

**A.P. Systems**  
Box 263 sm.  
Newport, RI 02840 (401) 846-5627

**A Breakthrough**  
for Amateur and  
Commercial Repeater Users.

**DIVERSITY RECEPTION**—the ability to add a second receiver to your repeater system—can now be a reality for even the small user. The Pegasus VS-2 will allow your repeater to "listen" to two receivers simultaneously and to noiselessly switch between receivers as often as necessary to adjust for fading and nulls. This is particularly useful for repeaters that wish to provide coverage for hand held users or where receiver desense is a problem. You supply the second receiver & RF link and the VS-2 does the rest. Complete instructions and diagrams included with the VS-2.

**\$179<sup>00</sup>**  
Postpaid

Pegasus Electronics, Inc.  
88 New Dorp Plaza  
Suite 106  
Staten Island, NY 10306  
(212) 667-9137  
Affiliated with Comsec Corp.



✓201

**AZDEN**  
**PCS-4000**

ADVANCED MICROCOMPUTER CONTROL - 16 MEMORIES - 25 WATTS - SUPER COMPACT 142-160 MHZ - ANY SPLITS - ONE-YEAR WARRANTY -

ALSO: PCS-300 HT, PCS-2800 10M FM, accessories, etc.

**KDK**  
**FM-2030**

EASY TO OPERATE - SINGLE-KNOB TUNING - RIT - 10 MEMORIES - 25 WATTS - SCAN BAND OR MEMORIES - TT MIC. WITH UP/DOWN FREQ. CONT. - ANY SPLITS BEEPS AT MEMORY BAND LIMITS FOR EYES-OFF OPERATION

Special discounts - call for quote

**B. G. CARL ELECTRONICS**

11128 Claire Ave. Northridge, CA 91326

Call: 1-213-363-1216 (anytime) Bryan AG6R

detector in azimuth and in elevation to the aircraft. Remember, these are pulse radars with high-power output and you can hear them for about ten miles from your location.

**Ship and Coastal Radar.** These radars operate in the 2900-3100-, 5350-5650-, and 9300-9500-MHz bands. Rotate your detector around slowly as you look for them near the coast as they will have an antenna rotation rate of 5-10 rpm. Large ships will move slowly as you track them while small vessels will move more rapidly and you may soon lose them. While driving along, you'll hear them for 5 to 10 miles before they fade out.

**Weather Radar.** These radars operate around the clock from a number of locations in the country as part of the NOAA weather service, in a band of frequencies from 2900-3100 MHz. These signals are heard on occasion from as far away as 40 miles when the sky is filled with clouds of rain or heavy moisture. The radars have a low antenna-rotation rate as well as a low pulse-recurrence frequency (prf) which sounds like "burt, burt." On occasion, you may find these signals being reflected off large thunder clouds that are 10 to 20 miles away.

**Microwave Communications.** These signals will fool you the most as they sound like a real Doppler (continuous-wave) radar. As you drive around in the city or country, you may pass into their beam and hear the pure tone increase in intensity. You'll look around for a bubble-machine car but not see anything. Then, as you drive further, the signal may disappear as you get closer to, and pass under, the beam from the antenna (probably a 3' to 5' dish) mounted on the side of a building or on a tower.

These signals usually lie in the frequency range of

12.985-13 GHz. Other users might lie in the 7-9-GHz band. These systems usually operate with just a few Watts of power to the antenna but with a high-gain beam. Once you locate the position of such a signal, you can use it to check the proper operation of your receiver each time you drive by. In the event a real Doppler radar were to begin operation in that same area, your trained ear will still be able to discern a difference between the two.

**CB Transmitters and Mobile Radiotelephones.** On occasion, you will hear a brief whistle of a signal as you pass other vehicles on the highway. The signal might last for just a few seconds and you'll think you've been pinged. What you have done is pass very close to a CB or mobile radiotelephone in operation. If you glance quickly at the passing autos, you may observe someone talking into a telephone handset. These transmitters usually operate in the 150-170-MHz or 450-MHz range and you are hearing a harmonic due to the closeness of your receiver to them.

**Television Stations.** Depending upon the TV channels in your location, you may or may not hear false alarms. UHF stations which operate on channels 14-83 (470-890 MHz) at power levels up to 1 million Watts may be received up to 20 miles away, causing you to turn down your manual sensitivity to quiet the alarm. While driving in a strange city, you'll need the discerning power of your ears to tell you what sounds are a TV channel and what sounds are the pure tone of your friendly gendarme radar. These TV signals are so strong that they plainly drive through the X-band antenna and are detected (chopped) and you hear them as real "fake" signals.

**Aircraft Runway Landing Aids.** As you drive by or near

some airports, you may hear all sorts of signals being picked up by your 5-15-GHz receiver. Some of the approach-control radars are at 2800 MHz and you'll hear their prf buzz each time the antenna rotates by your auto as you drive by. You may also hear reflections off buildings by aiming your receiver antenna at the buildings. You may also hear side-lobes from the radar as it sweeps in azimuth.

One very interesting airport radar operates at a frequency of 9080 MHz with prf of 5500 Hz as it sweeps in azimuth and elevation, looking down the runway at approaching aircraft. As you drive by, you will hear its signal. It goes "cheep, cheep" as it scans its pattern across your vehicle. You might hear this one as far as three miles from the end of the runway.

**Other Signals You May Receive.** There are now a number of microwave burglar alarm systems that operate throughout the country at X-band. As a consequence, depending on the sensitivity of your receiver, you may detect them when driving in residential areas, shopping centers, and industrial areas. Again, you will be able to recognize their sound and identify the area of the city where you receive them.

### Other Receiving Considerations

**Inverse Square Law ( $1/R^2$ ).** A radio signal undergoes a loss as it propagates through space; this is called the inverse square law. Double the distance, and the power received is one-fourth strength. For the radar receiver case, the signal suffers a  $1/R^2$  power loss in reaching the target and a  $1/R^2$  loss in the signal returning from the target to the radar receiver. For the radar case, therefore, the total power loss is figured by  $1/R^4$ . However, for the radar detector case, the power loss is

only  $1/R^2$ , not  $1/R^4$ , as it does not have to look at reflected (bounced) radar energy. Thus, the detector can see the detectee twice as far away. All things being equal, you should hear him at twice the distance that he can see you. That provides a beep to the wise.

**X-Band Radars.** There are over 70,000 speed radar sets in operation in the US—about 95% in X-band.

**K-Band Radars.** About 5% of the radars operate in this band, and this number is increasing as equipment-design technology for this band improves.

**Radar Detectors.** It is estimated by manufacturers that there are approximately 2 million radar detectors in use in the US. Their use probably will increase as federal laws are enforced additionally by state authorities.

**The Superheterodyne Radar Detector.** The superheterodyne receiver is the best type of circuit that you can buy. They are just now becoming available in quantity on the radar-detector market and range in price from about \$150 to \$300. The circuit is the same as that employed in most AM, FM, and TV receivers and is very selective in frequency. Because of this feature, the receiver is able to reject almost all the signals that can be found in the outside world of the present-day radar speed detectors.

**Use of the 5-15-GHz Receivers.** The modified receiver you are using covers about 5-15 GHz. You'll hear many different kinds of signals in this frequency band, some of interest, some of no interest, and some a bother. Whatever the reason for you to use it, remember—the FCC under Title 47 of the Communications Act of 1934 states that no radio receiver can be licensed, restricted, or banned. And that includes any government agency or state. Happy listening! ■



# Personalize the M800 RTTY Program

*Now you can design and save your own version  
of this popular software package.  
All it takes is a POKE or two.*

Since the introduction of the low-priced micro-computer for the home market, radio amateurs have quickly taken advantage of the fact to modernize their ham shacks. These individuals very quickly realized that not only was the machine capable of doing housekeeping chores, but also it could be used on the air. The first software for the TRS-80's use on CW and RTTY was the Macrotronics M80 written by Dr. Ron Lodewick N6EE. This program was a fantastic learning experience for all users and the enthusiasm generated was sufficient to convince Ron to create the M800. As the FCC opened the door for the use of ASCII in the USA, shortcomings were found in that portion of the program. It was not long at all before Ron issued FREE a corrected version called the M800 1.1.

Now come the shortcomings of any software that is mass-produced. Being mass-produced, one must organize the program to suit his or her operating circumstances. I do not fault Macrotronics for this be-

cause to maintain a viable operation, one soon has to lose the personal touch. If the software was to be constructed tailor-made for the individual, the cost would be astronomical, as you can well appreciate.

To get started, simply load and run the M800 as usual (make sure you have the hardware turned on). Once you have entered your name and callsign, you can proceed to set the program as you would for operating, such as CW shift, ignore returns, fast diddle, etc. Now that you are satisfied, run through the operating steps until you are sure you have it the way you want. Proceed to program the three message memories and try them out as well just to be sure that they function correctly. Once satisfied, go to the receive mode and enter the name of the station that you work most often. This is an added touch that saves time.

Now that the program is running properly, break the out by resetting (don't forget to use the break key if you have the expansion interface) and POKE the number

of diddles and lines of CQ, RY, and QBF. You can now load TBUGHI and punch a new tape with the P command as follows:

```
P 43FO 6652 4575 M800 <ENTER>
```

This will give you a permanent copy. It would be advisable to make a few backups prior to trying out the tape as TBUG does not verify. I have made several different copies, for normal operating, contesting, DXing, and other operations.

The information that I have to pass on to you is very simple and should make the software a dream to use. The program will come up running in the receive mode with all of your information stored as an integral part of the program. The only other software that you require to accomplish the task is TBUG, but this must be relocated out of the way of the M800. If you have trouble with the relocation, an excellent article is available in *80 Microcomputing*, issue #1, January, 1980, page 118.

Disk users will also benefit as the program can be auto-loaded. Using the Aparat 40 Track Newdos+, it

takes less than five seconds to receive. Also using Newdos SUPERZAP, you can change the CQ, RY, and QBF messages to suit the operation. I have changed the CQ message from

```
CQ CQ CQ CQ CQ CQ CQ  
CQ CQ CQ CQ CQ CQ CQ  
CQ CQ CQ CQ CQ
```

to

```
CQ TEST CQ TEST CQ TEST  
DE VE4AFO CQ TEST CQ  
TEST CQ TEST DE VE4AFO.
```

This is only a simple example of program manipulation; you are limited only by your own imagination.

An added feature is one that should make people very happy: The troublesome keybounce can be overcome using the utility DBNC found in *80 Microcomputing*, issue #1, January, 1980. If you have more than 16K, it is very simple to relocate by changing the ORG statement.

I hope this will help your operating; your comments would be appreciated. Special thanks go to my father, Jim Bowman, and to Bert Anderson VE4AP. Without their help, this article would not have been possible. ■

# HAM HELP

I need an audio frequency counter which will work with a Swan 350. I am blind and need some way of determining the exact frequency I am working.

Norm Fetting K9GIR  
309 E. Yorkshire Dr.  
Stockton CA 95207

I need information on the US Navy's WWII MBM transceiver. I am also looking for technical information and parts for the General Dynamics AM/PRC-70 (XE 2) or a similar model.

Tony Grogan WA4MRR  
5 Rollingwood Dr.  
Taylors SC 29687

I am looking for schematics and technical manuals for the Exam-eter solar capacitor checker, model CF, type 1.60; Graetz 2000 long-wave, medium-wave and broad-

cast radio, nr. 87(267)x53, series 171/7, 586828; US Navy model RBB-1 CRV46147 receiver; Hanlmex model TDP 850 calculator; and Collins ART-13 transmitter.

Roger Moe N7KGG  
Route 1, Box 1140  
Wapato WA 98951

I would like to start an Alcoholics Anonymous net. Any recovering alcoholics or others interested in such a net, please contact me.

Raymond W. Guenther N2CWB  
20-47 33rd St.  
New York NY 11105

I am still looking for a manual for the Globe Scout 680-A. I will pay for all costs.

Dennis Comell WD4HRO  
7835 Captain St.  
Millington TN 38053

Custom Mailing Lists on Labels!

## Amateur Radio Operator NAMES

Custom lists compiled to your specifications —Geographic by ZIP and/or State; by Age or Birthdate; by Licence Issue or Expiration Date—on labels of your choice.

Total List: 411,000 Price: \$25/Thousand

Call 203: 438-3433 for more information

Buckmaster Publishing ✓ 226

70 Florida Hill Rd., Ridgefield, CT 06877

## this publication is available in microform



University Microfilms International

300 North Zeeb Road  
Dept. P.R.  
Ann Arbor, MI 48106  
U.S.A.

18 Bedford Row  
Dept. P.R.  
London, WC1R 4EJ  
England

## The Spider™ Antenna

The modern multi-band mobile antenna —switch to 10, 15, 20 or 40 meters without stopping to change resonators.

### Features of the Spider™ Antenna

- The Spider™ Antenna is less than six feet high and the longest resonator projects out from the mast 24 inches. This gives a slim profile, low height and light weight, offering little wind resistance and eliminating the need for a spring mount.

- Each resonator is tuned to the desired portion of the band by a tuning sleeve which slides over the outside of the resonator.

- SWR is approximately 1:1 at the selected resonant frequency.

- Base impedance approximately 50 ohms, requiring no matching network.

- Ideal for use on vans, campers, motor homes, travel trailers; also in mobile home parks, apartment houses and condominiums.

**The Spider™ Adapter** converts any mono-band antenna with a half-inch mast into a modern four-band antenna.

**The Spider™ Maritimer™** is the ultimate for marine use. Made of non-magnetic stainless steel and nickel-chrome plated bronze, using regular Spider™ resonators and tuning sleeves.

**Accessories** — Bumper, ball, angle and stud mounts. Quick disconnects. RG-58A/U coaxial cable and connectors. Ground radial systems. Copper foil and copper braid ground straps.

For further information, prices write or call

## MULTI-BAND ANTENNAS

7131 OWENSMOUTH AVENUE, SUITE 463C  
CANOGA PARK, CALIF. 91303  
TELEPHONE: (213) 341-5460 ✓173

## Subscription Problem?

73 Magazine does not keep subscription records on the premises; therefore calling us only adds time and doesn't solve the problem.

Please send a description of the problem and your most recent address label to:

73 Magazine  
Subscription Dept.  
PO Box 931  
Farmingdale, NY 11737

Thank you and enjoy your subscription.

## SONY Closeout SAVE \$150



**SONY ICF-2001 Shortwave Receiver**  
Receives AM, SSB & CW modes from 150 to 29,999 KHz & FM 76 to 108 MHz. PLL/Synthesized keyboard tuning, LCD digital readout; Scan, 6 memories; 5-step LED S-meter, SSB/CW clarifier; Slide bass & treble controls; 4" speaker; Sleep timer; Tape jack; Tilt-stand; AM/FM telescopic antenna; Built-in ferrite bar antenna; AM long wire antenna; 12vdc or 120vac. Uses AC adaptor, (3) "D" + (2) "AA" cells or optional car battery cord. Supplied with AC adaptor, AM long wire antenna, carrying strap & shortwave handbook. Batteries not included. 6 7/8" h x 12 1/2" w x 2 1/4" d. 4-lbs.  
**Reg. \$349<sup>95</sup> - Closeout \$199<sup>95</sup>**

Quantity limited. Send Check or Money Order. For prompt shipment, Call TOLL FREE 1-800-558-0411 and use MASTERCARD/VISA or request CASH COD. Allow \$5 for UPS shipping charges in the 48 States.



Use your CREDIT CARD!

## AMATEUR ELECTRONIC SUPPLY®

4828 W. Fond du Lac Avenue  
Milwaukee, Wisconsin 53216  
Phone: (414) 442-4200

Wisconsin WATS: 1-800-242-5195

Nationwide WATS: 1-800-558-0411

AES Branch Stores in: Clearwater, FL • Orlando, FL • Wickliffe, OH • Las Vegas, NV

## ALL BAND TRAP VERTICAL ANTENNAS!

FULL 1/4th WAVE - All Bands! Automatic Selection with proven HI-Q Traps. 3 Models-ALL self supporting Ground or roof mount. HEAVY Double wall seamless Aluminum tower section - HI STRENGTH FIBER-GLASS TUBING OVER -ALL NO WOBBLY, LUMPY TRAPS - NO UNSIGHTLY CLAMPS needed Same size all the way up 1 1/4" - Traps hidden inside. You can use it in a 1 ft. sq. Backyard! Neighbors will never know this is a HI-Power ALL Direction DX Antenna. FOR APARTMENTS, ROW HOUSES, MOBILE HOMES - CONDOS etc. where minimum space and neat appearance is MANDATORY! Instant "Drive In" ground mount (Included). Use with or without radials (Included). (All angle roof mount - Extra) COMPLETELY PRE-TUNED - NO ADJUSTMENTS NEEDED EVER! NO TUNER NEEDED - Over All Bands (except BC) meter - 400 KC) SWR 1:1 to 2:1 at Band edges, Std. SO239 connector - 50 ohm for any length RG58U - RG8U feedline. Matches ALL MAKES TRANSCIEVERS, 2000 Watt PEP. Input power. Shipped - PRE-PAID IN USA. Assembles in 10 min. using only screwdriver. WEATHERPROOF!

No.-AVT80-10 — 5 Band — 25'6" — \$179.95  
No.-AVT40-10 — 4 Band — 18'9" — \$129.95  
No.-AVT20-10 — 3 Band — 11'4" — \$99.95

SEND FULL PRICE FOR PP DEL IN USA (Canada is \$5.00 extra for postage, clerical, Customs etc.) or order using VISA, MASTERCARD or AMERICAN EXPRESS. Give Number and Ex. date. Ph 1-308-236-5333 9AM-6PM weekdays. We ship in 2-3 days. Prices will increase, so order NOW

AND SAVE. All Antennas Guaranteed for 1 year - 10 day money back trial. If returned in new condition. Free Inf.

WESTERN ELECTRONICS ✓80  
Dept. A7-3 Kearney Nebr. 68647

# SOCIAL EVENTS

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received at 73 Magazine by the first of the month, two months prior to the month in which the event takes place. Mail to Editorial Offices, 73 Magazine, Pine Street, Peterborough NH 03458.

## MORRIS PLAINS NJ MAR 4

The Split Rock Amateur Radio Association will hold its sixth annual electronics auction on Friday, March 4, 1983, at VFW Post #3401, State Route 53, Morris Plains NJ. The Morris Plains VFW hall is located a short distance from US 202 and NJ 10 and is easily reached via I-80, I-287, and US 46. Admission is \$1.00. Doors will open at 7:00 pm for unloading and inspecting equipment and the auction will commence at 8:00 pm sharp. Items to be sold must be working equipment and loose parts must be bagged in the largest quantity possible. A commission of 10% will be taken on the first \$50.00 of each sale. Commissions are payable in cash only. Refreshments will be available. Talk-in on 146.385/146.985 (WR2ADB) and 146.52. For more information, please write to SARA, PO Box 3, Whippany NJ 07981.

## OLD BRIDGE NJ MAR 6

The Old Bridge Radio Association will hold its third annual auction on March 6, 1983, at the K of C Hall, Pine Street (just off Route 18), Old Bridge NJ. Doors will open for registration and inspection at 9:00 am and the sale will begin at 10:00 am. Admission is \$2.50. On successful sales, there will be a club commission of 10% on the first \$100 and 5% on the remainder. Food and drink will be available. Talk-in on .72/12, .34/94, and .52. For more information, contact Fred Goldberg WA2BJZ, 29 Clearview Road, East Brunswick NJ 08816, or phone (201)-257-8753.

## SOUTH ST. LOUIS MO MAR 11

The Jefferson Barracks Amateur Radio Club will hold its annual auction and hamfest on March 11, 1983, at the Carondelet Sunday Morning Athletic Club in South St. Louis MO.

## EGG HARBOR CITY NJ MAR 12

The Shore Points Amateur Radio Club will hold Springfest '83 on Saturday, March 12, 1983, from 9:00 am to 3:00 pm, at the Atlantic County 4-H Center, Route 50, Egg Harbor City NJ (near Atlantic City). Admission is \$3.00 at the gate and \$2.50 in advance; XYLs and children will be admitted free. Sellers' space is \$5.00 and sellers must bring their own tables. There will be a large, heated building with commercial power, as well as outside covered tailgating spaces. Refreshments will be available. Talk-in on 146.985 and .52. For more information and reservations, write SPARC, PO Box 142, Absecon NJ 08201.

## LAFAYETTE LA MAR 12-13

The Acadiana Amateur Radio Association will sponsor the ARRL-approved 23rd annual Lafayette Amateur Radio Hamfest on Saturday and Sunday, March 12-13, 1983, at the Carencro High School, Highway 182 North, 2 1/2 miles north of I-10, Lafayette LA.

## FORT WALTON BEACH FL MAR 12-13

The Playground Amateur Radio Club will hold its 13th annual North Florida Swapfest on Saturday, March 12, 1983, from 8:00 am to 4:00 pm, and on Sunday, March 13, 1983, from 8:00 am to 3:00 pm, at the Okaloosa County Fairgrounds, Fort Walton Beach FL.

## MARTINSVILLE IN MAR 13

The Morgan County Amateur Radio Club will sponsor the Martinsville Hamfest on March 13, 1983, beginning at 8:00 am, at the Morgan County 4-H Building and Fairgrounds. Admission is \$3.00 in advance and \$4.00 at the door; children 11 and under will be admitted free. Flea-market space with a table is \$5.00 and flea-market space without a table is \$3.00. Premium tables are \$20.00. Tables will be available on a first-come basis and the best spaces will be assigned first. Vendor setups will start at 5:00 am and parking will be free. Talk-in on 147.667.06. For tickets, table reservations, and information, send an SASE to Aileen Scales KA9MBK, 3142 Market Place, Bloomington IN 47401.

## TRENTON NJ MAR 13

The Delaware Valley Radio Association will hold its 11th annual flea market on Sunday, March 13, 1983, from 8:00 am to 4:00 pm, at the New Jersey National Guard 112th Field Artillery Armory, Eggerts Crossing Road, Lawrence Township. Registration is \$2.50 in advance and \$3.00 at the door. There will be an indoor and outdoor flea-market area and refreshments, including breakfast at 7:00 am. Sellers must bring their own tables. Talk-in on 146.52 and 146.077.67. For further information, send an SASE to DVRA, PO Box 7024, West Trenton NJ 08628.

## WINCHESTER IN MAR 13

The Randolph Amateur Radio Association will hold its 4th hamfest on Sunday, March 13, 1983, from 8:00 am to 5:00 pm, in the National Guard Armory, Winchester IN. Ticket donation is \$3.00 and children under 12 years old will be admitted free. Table space (by reservation only) is \$5.00 with a table and \$2.50 without. There will be a flea market, dealers, programs, food, and drink. Setups will be on Saturday from 6:00 pm to 8:00 pm and on Sunday from 6:00 am to 8:00 am. Talk-in on 147.90/30, 224.90/223.30, and 146.50. For reservations and more information, contact RARA, Box 203, Winchester IN 47394, or phone Jake Life W9VJX at (317)-584-9361.

## ERIE PA MAR 19

The Radio Association of Erie PA will

hold The RAE Eyeball QSO Party on Saturday, March 19, 1983, at the Perry Highway Hall, 8/10 of a mile south of I-90 on the west side of Route 19. Admission is \$2.00 per person. Tables (8-foot) are \$3.00 each and are by reservation only. Food will be available. There will be FCC testing for applicants that mail Form 610 to the Buffalo office by February 22nd. Talk-in on .011/61 and .221/82.

## MARSHALL MI MAR 19

The Southern Michigan ARS and the Calhoun County Repeater Association will hold the 21st annual Michigan Crossroads Hamfest on March 19, 1983, beginning at 8:00 am, at the Marshall High School, Marshall MI. Tickets are \$2.00 at the door and \$1.50 in advance. Table space is \$.50 a foot. Doors will be open at 7:00 am for exhibitors and there will be plenty of carry-in help and free parking. Food service will be available in the cafeteria. For tables or tickets, contact SMARS, PO Box 934, Battle Creek MI 49016, or phone Chuck Williams at (616)-964-3197.

## SAN FRANCISCO CA MAR 19

The ARRL will sponsor the second Amateur Radio Computer Networking Conference on March 19, 1983, in San Francisco CA. The conference will be in cooperation with the 8th West Coast Computer Faire being held March 18-20, 1983. This event will be hosted by the Amateur Radio Research and Development Corporation (AMRAD) and the Pacific Packet Radio Society (PPRS). For more information, contact Paul L. Rinaldo W4RI, 1524 Springvale Avenue, McLean VA 22101, or phone (703)-734-0878.

## UPPER SADDLE RIVER NJ MAR 19

The Chestnut Ridge Radio Club will hold a ham radio flea market on Saturday, March 19, 1983, in the Education Building, Saddle River Reformed Church, East Saddle River Road at Weiss Road, Upper Saddle River NJ. Admission is free. Tables are \$10.00 for the first and \$5.00 for each additional one. Tailgating is \$5.00. Food and soda will be available. For further information, phone Jack Meagher W2EHD at (201)-768-8360 or Roger Soderman KW2U at (201)-666-2430.

## MIDLAND TX MAR 19-20

The Midland Amateur Radio Club will hold its annual St. Patrick's Swapfest on March 19-20, 1983, from 8:00 am to 6:00 pm on Saturday and from 8:00 am to 3:00 pm on Sunday, at the Midland County Exhibit Building, east of Midland on Highway 80 on the north side. Pre-registration is \$5.00 (at the door, \$6.00). Tables are \$4.00 each. Refreshments will be available. Talk-in on .16/76 and .01/61. For further information and reservations, please contact Midland Amateur Radio Club, PO Box 4401, Midland TX 79704.

## JEFFERSON WI MAR 20

The Tri-County Amateur Radio Club will hold its annual hamfest on March 20, 1983, from 8:00 am to 3:00 pm at the Jefferson County Fairgrounds, Jefferson WI. Tickets are \$2.50 in advance and \$3.00 at the door. Tables are \$2.50 in advance and \$3.50 at the door. Parking is free and there will be plenty of food available. Talk-in on 146.52, 146.22/82, and 144.89/145.49. For more information, advance tickets, and tables, send an SASE to Horace Hilker K9LJM, PO Box 204, 261 E. High Street, Milton WI 53563.

## MAUMEE OH MAR 20

The Toledo Mobile Radio Association, Inc., will hold its 28th annual auction and hamfest on Sunday, March 20, 1983, from 8:00 am to 5:00 pm, at the Lucas County Recreation Center, Key Street, Maumee OH. Tickets are \$2.50 in advance and \$3.00 at the door. The auction is free and starts at 10:00 am. Ample free parking will be available all day and overnight. Flea-market tables will be available and displays will be limited to electronics and ham gear only. There will also be commercial exhibits, special programs for the ladies, and refreshments. Talk-in on 146.01/.61, .19/79, .34/94, 147.87/27, .975/375, and 146.52/52. For more information, send an SASE to J. Honisko KB8YD, 1733 Parkway Drive N., Maumee OH 43537.

## MAUMEE OH MAR 20

The annual meeting of the American Signaling Society is scheduled for March 20, 1983. The meeting will begin promptly at 0100 hours UTC. Members and guests will convene in the Main Exhibit Hall of the Lucas County Recreation Center, 2901 Key Street, Maumee OH. In addition to the election of officers, the ever-popular forum on the latest signaling techniques will be offered. A Century Club confab will also be held. For additional information, please send an SASE to The American Signaling Society, 4015 Windermere Road, Columbus OH 43220.

## CIRCLEVILLE OH MAR 20

The Teays Amateur Radio Club will hold its sixth annual King of the Pumpkin Hamfest on Sunday, March 20, 1983, from 8:00 am to 4:00 pm, at the Pickaway County Fairgrounds Coliseum. Tickets are \$2.00 in advance and \$3.00 at the door. Tables (8-foot) are \$4.00 in advance and \$5.00 at the door. Doors will be open for setups on Saturday at 4:00 pm and overnight security will be provided. A large parking area and food will be available. Talk-in on 147.78/18 and .52/52. For additional information, please send an SASE to Dan Grant W8UCF, 22150 Hulse Road, Circleville OH 43113, or phone (614)-474-6305.

## STERLING IL MAR 20

The Sterling/Rock Falls Amateur Radio Society will hold its 23rd annual hamfest on March 20, 1983, beginning at 7:30 am, at the Sterling High School Field House, 1608 4th Avenue, Sterling IL. Tickets are \$2.00 in advance and \$2.50 at the door. Commercial tables and flea-market tables requiring electricity are \$5.00; all others are \$3.00. A concession stand, free parking, and overnight space for self-contained campers will be available. There will be commercial distributors, dealers, and a large flea market. Talk-in on 146.25/85 (W9MEP). For advance tickets, tables, and information, contact Sue Peters, 511 8th Avenue, Sterling IL 61081, or call (815)-625-9262.

## BLACKSBURG VA MAR 21-24

The Virginia Polytechnic Institute and State University will hold a Personal Microcomputer Interfacing and Scientific Instrumentation Automation Workshop on March 21-24, 1983, on the Virginia Tech campus in Blacksburg VA. The workshop, directed by Drs. Paul Field, Chris Titus, Jon Titus, and Mr. David Larsen, is hands-on, with the participant designing and testing concepts with actual hardware.

The charge is \$595.00. For more information, write Dr. Linda Leffel, C.E.C., Virginia Tech, Blacksburg VA 24061, or call (703)961-4848.

#### CANTON OH MAR 26

The Canton Amateur Radio Club will hold an auction on March 26, 1983, beginning at 5:00 pm, at the Nlmsihillen Grange, Easton Street NE, Canton OH. Admission is \$2.00; flea-market table space is \$2.00. Free parking will be available. Talk-in on 147.121.72. For general information, phone Herb Bushong WD8IPE at (216)488-2920.

#### JOHNSTOWN PA MAR 27

The Conemaugh Valley Amateur Radio Club will hold its sixth annual hamfest on Sunday, March 27, 1983, from 8:00 am to 4:00 pm, at the East Taylor Fire Hall, which is located on Route 271, 5 miles south of Route 22 (4 miles north of Johnstown). There will be plenty of food and refreshments available. Talk-in on 146.34/94.

#### GRAYSLAKE IL MAR 27

The Libertyville and Mundelein Amateur Radio Society will hold LAMARS-FEST 1983 on Sunday, March 27, 1983, beginning at 8:00 am, at the Lake County Fairgrounds, Routes 45 and 120, Grayslake IL. Tickets are \$2.00 in advance or \$3.00 at the door. Tables (9-foot) are \$5.00 each. Reservations are encouraged because choice locations will be assigned first. Commercial setups will begin at 6:30 am and other setups will begin at 7:00 am. There will be free parking, and breakfast and lunch will be available. Talk-in on 147.63/03 and 146.94. For tickets, table reservations, or exhibitor information, send a SASE to LAMARS, PO Box 751, Libertyville IL 60048.

#### MADISON OH MAR 27

The Lake County Amateur Radio Association will hold their fifth annual Lake County Hamfest and Computer Fest on Sunday, March 27, 1983, from 8:00 am to 4:00 pm, at Madison High School, Madison OH (40 miles east of Cleveland). Admission is \$2.50 in advance and \$3.50 at the door. Table and display space (all indoors) is \$5.00 for a 6-foot table and \$6.50 for an 8-foot table. There will be plenty of free parking. Doors will open for exhibitors at 5:30 am. Talk-in on 147.81/21. For reservations and more information, send a SASE to Lake County Hamfest Committee, 3777 Lake Shore Boulevard, Eastlake OH 44094, or phone (216)953-9784.

#### BALTIMORE MD MAR 27

The Baltimore Amateur Radio Club, Inc. (BARC), will hold the 1983 Greater Baltimore HamBoree and Computerfest on March 27, 1983, beginning at 8:00 am, at the Maryland State Fairgrounds Exhibition Complex (located east of I-83 exit 17, three miles north of I-695, north of Baltimore), Timonium MD. Admission is \$3.00; children under 12 will be admitted free. Overnight accommodations are available in the immediate area. Amateur-radio, personal-computer, and small-business-computer dealers will be present. There will be an indoor flea market, a large hard-surfaced outdoor tailgate area, food service, free parking, and guest speakers throughout the day. For additional information and table reservations, contact GBH&C, PO Box 95, Timonium MD 21093-0095, or

phone (301)561-1282. For a recorded announcement, dial (301)-HAM-TALK.

#### SOMERSWORTH NH APR 9

The Great Bay Radio Association will hold its 3rd annual hamfest-flea market on Saturday, April 9, 1983, from 9:00 am to 3:00 pm, at the Somersworth Armory, Somersworth NH. The entrance fee is \$1.00 per person. Food, refreshments, and free parking will be available. For advance registrations and further information, write Great Bay Radio Associations, PO Box 911, Dover NH 03820.

#### MADISON WI APR 10

The Madison Area Repeater Association, Inc. (MARA), will hold its eleventh annual Madison Swapfest on Sunday, April 10, 1983, at the Dane County Exposition Center Forum Building, Madison WI. Doors will open at 8:00 am for commercial exhibitors and flea-market sellers, and at 9:00 am for the general public. Admission is \$2.50 per person in advance and \$3.00 at the door. Children twelve and under will be admitted free. Flea-market tables are \$4.00 each in advance and \$5.00 at the door. Features will include commercial exhibitors, a flea market, an all-you-can-eat pancake breakfast, and a barbecue lunch. Plenty of parking space and nearby hotel accommodations are available. Talk-in on 146.161/76 (WR9ABT). For reservations (early ones are advised) or more information, write to MARA, PO Box 3403, Madison WI 53704.

#### FRAMINGHAM MA APR 10

The Framingham Amateur Radio Association, Inc., will hold its 8th annual spring flea market on Sunday, April 10, 1983, at the Framingham Civic League Building, 214 Concord Street (Route 126), downtown Framingham MA. Admission is \$2.00 and doors will be open at 10:00 am. Tables are \$10.00 (pre-registration required) and sellers may set up beginning at 8:30 am. Radio equipment, computer gear, and food will be available. Talk-in on 75/15 and 52. For more information, contact Ron Egalka K1YHM, 3 Driscoll Drive, Framingham MA 01701.

#### SOUTH SIOUX CITY NE APR 15-17

The 39 Hundred Club will hold the 1983 Midwest ARRL Convention on Friday, Saturday, and Sunday, April 15-17, 1983, at the Marina Inn, South Sioux City NE, directly across the river from Sioux City. On Saturday, features will include a QCWA breakfast, a 3900 Club luncheon, an all-day ladies' program, and an evening banquet with entertainment. There will be seminars, displays, commercial exhibits, and a 66-table flea market, all indoors in the same building. Tables (8 ft. x 30 in.) are \$5.00 for the 3 days, \$4.00 for Friday night and Saturday. For table reservations, contact Al Smith W0PEX, 3529 Douglas Street, Sioux City IA 51104. Exhibitors should contact Jim Boise KA0GZY, 22 LaSalle Street, Sioux City IA 51104. Setup time is Friday afternoon, April 15th. Convention fees are \$6.00 for the 3 days; advance banquet reservations are \$10.00 (at the door, \$12.00). For advance banquet tickets and motel reservations, write to Jerry Smith W0DUN, Akron IA 51001. For general information, contact Dick Pinner W0FZO, General Chairman, 2931 Pierce Street, Sioux City IA 51104.

#### DAYTON OH APR 23

The Washington University Amateur Radio Club will hold a reunion dinner on Saturday, April 23, 1983, at the Dayton Hamfest. All past members of the club are invited. For more information, contact Washington University ARF W0QEVE, Box 1128, St. Louis MO 63130.

#### PARAMUS NJ MAY 1

The Bergen ARA will hold a Ham Swap 'n' Sell on May 1, 1983, from 8:00 am to 4:00 pm, at Bergen Community College, 400 Paramus Road, Paramus NJ. Admission for sellers is \$3.00; buyers will be admitted free. There will be thousands of spaces but tailgating only. Sellers must bring their own tables. Talk-in on .79/.19 and .52. For more information, contact Jim Greer KK2U, 444 Berkshire Road, Ridgewood NJ 07450, or phone (201)445-2855.

#### DULUTH MN MAY 7

The Arrowhead Radio Amateur Club will hold its annual swapfest on Saturday, May 7, 1983, from 10:00 am to 3:00 pm, at the Holiday Inn, 207 West Superior Street, downtown Duluth MN. Admission will be \$2.50 in advance or \$3.00 at the door. Tables (4-foot) are \$3.50 in advance or \$4.00 at the door. There will be plenty of food, free parking in the ramp, and an enclosed shopping mall for the XYLs. Talk-in on .34/94. For advanced reservations, room discount rates, or more information, send an SASE to Jerry Frederick N0BNG, 1127 104th Avenue West, Duluth MN 55808.

#### CEDARBURG WI MAY 7

The Ozaukee Radio Club will sponsor its 5th annual swapfest on Saturday, May 7, 1983, from 8:00 am to 1:00 pm, at the Circle B Recreation Center, Highway 60, Cedarburg WI (located 20 miles north of Milwaukee). Admission is \$2.00 in advance and \$3.00 at the door. All 8-foot tables are \$3.00. Sellers will be admitted at 7:00 am for table setups. Food and refreshments will be available. For tickets, tables, maps, or more information, send an SASE to 1983 Ozaukee Radio Club Swapfest, PO Box 13, Port Washington WI 53074.

#### ROCHESTER NY MAY 20-21

The Rochester Hamfest, in conjunction with the ARRL New York State and Atlantic Division Conventions, will be held on May 20-21, 1983, at the Marriott Thruway Hotel and the Monroe County Fairgrounds. Tickets are \$4.00 in advance and

\$5.00 at the gate. Flea-market tickets are \$2.00 per space. The banquet will be held at 6:30 pm on Friday and be followed by the annual Funfest at 8:00 pm. The flea market will open at 6:00 am on Saturday; the commercial exhibits, at 8:30 am. The hamfest will close at 6:00 pm. There will be FCC exams given at the Rochester Hamfest for those who have sent Form 610 to FCC, 1307 Federal Building, 111 W. Huron Street, Buffalo NY 14202, by May 1st. A ladies' program will be available. Talk-in on 146.28/88 and 144.51/145.11. For advance tickets, contact K2MP, 737 Latta Road, Rochester NY 14612. For more information, write Rochester Hamfest, 300 White Spruce Boulevard, Rochester NY 14623.

#### MUNCIE IN MAY 22

The fourth annual MAARC Hamfest will be held on Sunday, May 22, 1983, in the Memorial Building located on the grounds of the Delaware County Fairgrounds. Advance admission tickets are \$2.00 and tables are \$5.00 each. Two new features are computer displays and the first annual Middletown USA QSO Party which will be run during this weekend. The MAARC club station will be in operation from the hamfest site. Electrical hookups and security will be provided during the entire show in a clean and fully enclosed building. For additional information, write Walt Robbins, Jr. WA9ZES, Publicity Chairman, RR 2, Box 340E, Muncie IN 47302.

#### CUMBERLAND ME JUL 30

The Blackstrap Repeater Association will hold the second annual Greater New England Hamfest on Saturday, July 30, 1983, from 8:00 am to 5:00 pm, at Cumberland Fairgrounds, Cumberland ME. Tickets are \$1.00 in advance and \$2.00 at the gate. There will be forums, exhibits, meetings, speakers, dealers, and a giant flea market. Food and free camping will be available. Talk-in on 147.69/09, 146.52, 3.940, and 146.13/73. For more information, call Ed Williams KA1FZD at (207)846-3509.

#### TRUMANSBURG NY AUG 27

The annual Finger Lakes Hamfest will be held on August 27, 1983, from 8:00 am to 5:00 pm, at the Trumansburg Fairgrounds, Rt. 96, 12 miles NW of Ithaca NY. Admission is \$2.00 at the gate. There will be a flea market, commercial exhibitors, a boat anchor auction, refreshments, and a craft show for the ladies. Talk-in on .37/97 and .52. For further details, write Dave W2CFP, 866 Ridge Road, Lansing NY 14882.

## HAM HELP

I have the following equipment available for cost of postage or free pickup; the Heathkit GR-88, which shorts the ac power supply, and the Heathkit GR-98, which drifts slightly.

Steve Clifton WA2TYF  
800 W. End Ave.  
New York NY 10025

I need frequency-determining networks with 2125-Hz and 2295-Hz center frequencies for use with a Northern Radio Company dual-frequency-shift tone converter.

type 152, model 2.

Bob Workman WA4ZNN  
PO Box 942  
Atlantic Beach NC 28512

I would like to find a Knight KG687 sweep generator and the schematics for a Sony MX-12 microphone mixer and the Scott 299-T audio amplifier.

Dave Overton  
1709 W. 30  
Austin TX 78703

# CONTESTS

Robert Baker WB2GFE  
15 Windsor Dr.  
Atco NJ 08004

## QCWA QSO PARTY—PHONE

**Starts: 0001 GMT March 12**  
**Ends: 2000 GMT March 13**

This is the second part of the 26th annual QCWA QSO party. You can work the same station more than once providing it is on another band. Only the bands listed under frequencies will count in this QSO party.

### EXCHANGE:

QSO number, operator's first name, QCWA chapter identification (official number or name), and state or country. Members not affiliated with a chapter should use "AL."

### FREQUENCIES:

Any authorized amateur frequency in the bands that are listed below is permissible. The following suggested frequencies have been selected to minimize interference to others; however, please feel free to wander up or down from these if you so desire: 3900-3930, 7230-7260, 14280-14310, 21350-21380, 28600-28630. These frequencies are selected as a starting place. When pileups occur, don't be afraid to go either side of these frequencies.

### SCORING:

Each contact made with another QCWA member will count as a single point. This year's contest has three multipliers: chapters, states, and countries. For each band, every new chapter is a multiplier of one, every new state (USA) is a multiplier of one, and every new country (ARRL DXCC

list) is a multiplier of two. At the end of the party, add up your total contacts for all bands and multiply it by the sum of all your multipliers for all bands. This will give you your total and final score.

### ENTRIES:

Please keep separate logs for each band. Logs should include the following information: time (GMT), call, QSO numbers, name, chapter number or name, and state or country. It is the responsibility of each contestant to provide a legible log, no carbon copies, and to list all claimed contacts. The total contacts and multipliers for each page should be recorded at the bottom of each page. The total contacts for the party will not be returned. Make sure you have correct postage when you mail your logs. Send logs no later than March 31st to: Spaceport Center #66, Donald McClenon N4IN, 3075 Florida Avenue, Melbourne FL 32901. Separate logs and scores must be submitted for both the CW and phone parties.

## YL ISSB QSO PARTY—CW

**Starts: 0001 GMT March 12**  
**Ends: 2359 GMT March 13**

Two six-hour rest periods are required. Operating categories include: single operator, DX/WK partners, and YL/OM teams. All bands will be used and the same station may be contacted on different bands for contact points but not as country multipliers. VHF and UHF may be used but all contacts must be direct and not through repeaters. Nets are not allowed!

### EXCHANGE:

Name, RST, SSB number, country, W/K state or VE province, and DX/WK partner's call. If no partner, leave blank. If non-member, send "no number."

### FREQUENCIES:

On HF, use the USA General-class band portions. Check 80 and 40 meters on the hour.

### SCORING:

Score 3 points for each member contacted on own continent, 6 points if different continent. Nonmember contacts count one point. Only member station contacts count for multipliers. Multipliers are each state, country, and VE province; also, each team contacted but only once for each team. When DX/WK partners contact each other, it counts as a double multiplier. If your total dc input power is 250 Watts or less during the entire QSO party, then count an additional power multiplier of two. Final score is sum of QSO points times the total multiplier.

### AWARDS:

Special certificates will be awarded to the winners of each category. Regular certificates for country, US state, and Canadian province winners.

### ENTRIES:

Logs must show date/time (GMT); station contacted; RST; mode; band; SSB number; US state, VE province, or country; and period of rest time. Summary sheets show states, Canadian provinces, countries, YL/OM teams, and DX/WK teams and partner contacts. Send logs and summary sheets to: Rick & Minnie Connolly (K0RDJ & KA0ALX), Star Rt. 1, Crocker MO 65452 prior to June 1st. Be sure to indicate who your DX/WK partner is!

## WORKED ALL MORTON CONTEST

**0001 GMT March 12 to**  
**2400 GMT March 13**

Morton stations will be working all bands, phone and CW, about 5 kHz apart up from the bottom edge of the General

portion of each band. Contest exchange consists of RS(T) and state, province, or country. Certificates will be issued to those hams who have QSOs with five or more members of the Morton Amateur Radio Club or residents of Morton, Illinois during the contest period. To receive the award, applicants should send log information listing at least five Morton contacts along with a large SASE to: WD9AEU, 701 Columbus Ave., Morton IL 61550.

## IDAHO QSO PARTY

**Starts: 0000 GMT March 12**  
**Ends: 2359 GMT March 14**

Sponsored by the Kootenai Amateur Radio Society of northern Idaho.

### EXCHANGE:

RS(T) and Idaho county, state, province, or country.

### FREQUENCIES:

SSB—3920, 7260, 14250, 14325, 21325, 21380, 28550.

CW—50 kHz up from the lower band edge.

Novices—25 kHz up from their lower band. No net frequencies, please!

### SCORING:

Idaho stations score 1 point for each QSO and multiply by the number of Idaho counties, states, VE provinces, and countries worked. Others score 1 point per Idaho QSO and multiply by the total number of Idaho counties worked.

### AWARDS:

Awards will be issued to the top scorer in each Idaho county, state, VE province, and country.

### ENTRIES:

Mailing deadline for all entries in the USA is April 16th, May 1st for all DX coun-

# CALENDAR

Mar 5-6	ARRL International DX Contest—Phone
Mar 12-13	YL ISSB QSO Party—CW
Mar 12-13	QCWA QSO Party—SSB
Mar 12-13	Morton Contest
Mar 12-14	Idaho QSO Party
Mar 12-14	Virginia QSO Party
Mar 13	Wisconsin QSO Party
Mar 19-20	Bermuda Amateur Radio Contest
Mar 19-20	Tennessee QSO Party
Mar 19-21	BARTG Spring RTTY Contest
Apr 9-10	CARF Commonwealth Phone Contest
Apr 9-10	ARRL QSO Party—CW
Apr 16	Holiday in Dixie QSO Party
Apr 16-17	ARRL QSO Party—Phone
Jun 11-12	ARRL VHF QSO Party
Jun 25-26	ARRL Field Day
Jul 9-10	IARU Radiosport Championship
Jul 15-17	A5 Magazine SSTV DX Contest
Aug 6-7	ARRL UHF Contest
Aug 19-21	A5 Magazine UHF FSTV DX Contest
Sep 10-11	ARRL VHF QSO Party
Oct 8-9	ARRL QSO Party—CW
Oct 9-10	ARRL QSO Party—Phone
Oct 15-16	ARRL Simulated Emergency Test
Nov 5-6	ARRL Sweepstakes—CW
Nov 19-20	ARRL Sweepstakes—Phone
Dec 3-4	ARRL 160-Meter Contest
Dec 10-11	ARRL 10-Meter Contest



## NEWSLETTER OF THE MONTH

Galena crystals, horn speakers, and 4-pillar tubes are all subjects you would not expect to find in a modern amateur publication—unless it happened to be the *Old Timer's Bulletin*, this month's winner in 73's newsletter contest.

The *Bulletin* is published by the Antique Wireless Association, which is devoted to the research and documentation of the early history of wireless communications.

What differentiates this bulletin from many others is the relatively little space devoted to organizational news; instead, the *Bulletin* contains a variety of construction articles, historical shorts, and sage antique-radio restoration advice.

The December, 1982, issue included construction plans for a 1928-vintage transmitter using two UX-210 tubes and the design parameters for Atwater Kent horn speakers. Another article, "Arthur Wehnelt and His Wonderful Cathode," looked at the contributions of this little known physicist, while contributor Alan Douglas pulled Raytheon's 4-pillar tubes out of the cobwebs.

Special sections include columns for antique-radio collectors, a section on home-brewing parts, and tips on restoring old radios.

The *Bulletin* is spiced with reprints of news articles and cartoons from early in the century, and the artwork throughout meshes with the publication's focus on that era. Reading it, you could almost imagine that you were back in the days of the spark gap.

The *Bulletin* is typeset and printed, with good-quality black and white photographs throughout. Even those who do not remember the days when the tube was king can enjoy reading about the early progress of electronics and probably learn a thing or two in the process.

Congratulations to the Antique Wireless Association for making the good old days alive and interesting.

If your club would like to enter 73's newsletter contest, send a copy to: Editorial Offices, 73, Peterborough NH 03458.

tries and Canada. Send entries to: Vladimir J. Kalina KN7K, South 1555 Signal Point Road, Post Falls ID 83854.

### VIRGINIA QSO PARTY

**Starts: 1800 GMT March 12**  
**Ends: 0200 GMT March 14**

The 1983 QSO party is again sponsored by the Sterling Park Amateur Radio Club of Sterling Park, Virginia. The same station may be worked on each band and each mode. Virginia stations may contact in-state stations for QSO and multiplier credit. Virginia mobile stations may be worked in each new county they operate from for new QSO and multiplier credit regardless of whether or not previously worked on the same band and mode in another county. QRP stations must run 5 Watts or less for their entire operating time.

#### EXCHANGE:

QSO number starting with 001 and QTH consisting of state, province, DX country, or Virginia county. Virginia stations note that the reference for valid counties is *CO's Counties Award Record Book* which lists a total of 95 counties.

#### FREQUENCIES:

Phone—3930, 7230, 14285, 21375, 28575, and anywhere on 160-meter band except in DX windows for US stations.

CW—60 kHz up from the low end of each HF band except anywhere in 10- and 160-meter bands or Novice subbands.

#### SCORING:

Count one point per QSO. Virginia stations multiply total QSOs by the sum of states, Canadian provinces, DX countries, and Virginia counties worked. Others multiply QSOs by the number of Virginia counties worked.

#### AWARDS:

Engraved plaques to the top scoring stations in the following categories: high Virginia single operator (fixed location), sponsored by K3RZR and KA3DTE; high Virginia mobile station donated by Electronic Equipment Bank of Vienna, Virginia; high out-of-state (including DX) station; high QRP station (if 5 or more QRP entries are received) donated by K7HMP.

#### ENTRIES:

Follow ARRL standard contest guidelines for logs. Indicate each new multiplier as worked. Send a summary sheet, with your log and an SASE for a copy of the results, to: Virginia QSO Party, c/o Barry Pybas KW4I, 313 W. Derby Avenue, Sterling Park VA 22170. Mailing deadline is April 15th.

### WISCONSIN QSO PARTY

**1700 TO 2400 GMT March 13**

Use both CW and phone, stations may be worked once per mode on each band. Mobiles may be worked again when changing counties. No repeater QSOs!

#### EXCHANGE:

RS(T) and state, province, or Wisconsin county.

#### FREQUENCIES:

Phone—3990, 7290, 14290.  
CW—3560, 7050, 14060.

#### SCORING:

Phone contacts count 1 QSO point while CW contacts count 2 QSO points. Wisconsin stations multiply QSO points

by total number of states, provinces, and Wisconsin counties. DX countries count for QSO points but not multipliers. Non-Wisconsin stations multiply QSO points by number of Wisconsin counties (72 max). As a bonus, Wisconsin mobiles add 500 bonus points for each county that you operate from outside your home county with a minimum of 15 QSOs per county to qualify.

#### AWARDS:

Awards will be presented to the highest scores in each state and province, as well as to the highest aggregate club score.

#### ENTRIES:

All entries must contain a log consisting of: time in GMT, call, RS(T), state, Wisconsin county, mode, and a score summary. Logs containing more than 100 QSOs must be accompanied by a dupe sheet. Entries must be postmarked by April 15th and sent to: Wisconsin QSO Party, c/o West Allis Radio Amateur Club, PO Box 1072, Milwaukee WI 53201.

### BERMUDA AMATEUR RADIO CONTEST

**Starts: 0001 GMT March 19**  
**Ends: 2400 GMT March 20**

The Bermuda Amateur Radio Contest, in its 25th year, is again sponsored by the Radio Society of Bermuda. The contest is open to all licensed amateurs in Canada, the USA, the United Kingdom, and the Federal Republic of Germany. Of the 48-hour contest period, your total operating time cannot exceed 36 hours with off periods clearly logged. Each off period must not be less than three consecutive hours. All stations must be single operator only and must be operating from their own private residence or property. Use all bands, 80 through 10 meters. No crossband or crossmode contacts are permitted. Additionally, no phone contacts are allowed between W and G or West Germany on 40 meters.

#### EXCHANGE:

All stations will send RS(T) reports and give the following: Canadians add province, UK stations add county, US stations add state, West German stations add DOK number, and Bermuda stations add parish. US and Canadian stations may exchange reports with West German, UK, and Bermuda stations only. UK and West German stations may exchange reports with US, Canadian, and Bermuda stations only.

#### SCORING:

Each completed contact, on each band, counts 5 points. Only one contact per station on each band regardless of mode. For all stations outside Bermuda, the multiplier is the total number of VP9s worked on each band. For Bermuda stations, the multiplier is the total number of states, provinces, counties, and DOK numbers for West Germany worked on each band.

#### AWARDS:

Printed awards to the top scorer in each state, province, county, and DOK area in West Germany. The top scorer in Canada, US, UK, and West Germany shall receive a trophy to be awarded at the Society's annual dinner held in October of each year. Round trip air transportation plus accommodation will be provided to overseas winners to enable them to receive their awards. Top winners for the 1979 through 1982 contests shall be eligible for the area awards only.

# RESULTS

## 1982 WASHINGTON STATE QSO PARTY CERTIFICATE WINNERS

Callsign	QSOs	Multipliers	Total	Callsign	QSOs	Multipliers	Total
<b>Alaska</b>				<b>Oregon</b>			
NL7D	28	16	896	WA7ROS	120	36	9,432
<b>Arizona</b>				<b>Pennsylvania</b>			
W7ZMD	104	32	9,216	WA3JXW	30	16	1,296
W7RIR	63	29	4,785	<b>South Carolina</b>			
<b>Arkansas</b>				KE4VP	3	3	18
WB5RYB	44	20	2,180	<b>South Dakota</b>			
<b>California</b>				WA0BZD	4	4	36
N6QA	64	29	5,568	<b>Tennessee</b>			
W6OUL	45	19	2,242	WD4SIG	17	13	663
<b>Colorado</b>				<b>Texas</b>			
WA4EFE	55	24	3,936	W5PWG	73	27	5,724
<b>Connecticut</b>				N5QQ	37	25	2,775
KA1ICX	28	14	1,176	WA5DTK	44	20	2,300
<b>Florida</b>				<b>Utah</b>			
WA4FNA	49	16	2,352	W7LN	13	9	351
<b>Georgia</b>				K7SQD	13	8	312
N4NX	66	27	4,401	<b>Vermont</b>			
KE4XW	61	21	2,772	WB2NDE + K2QE	61	27	4,428
<b>Idaho</b>				<b>Virginia</b>			
KU7Z	3	3	18	W4KMS	27	16	1,168
<b>Illinois</b>				<b>Wisconsin</b>			
N9AUZ	59	25	4,050	WB9PYE	47	19	2,489
K9HRC	37	20	2,220	<b>Canada</b>			
W9QWM	28	16	1,200	British Columbia			
<b>Indiana</b>				VE7FBS	27	13	702
K19U	94	36	9,000	Manitoba			
KK9G	46	21	2,415	VE4RF	29	18	1,566
WD8QBB	42	23	2,277	Ontario			
<b>Kansas</b>				VE3KK	42	18	2,268
WD0CCW	96	34	6,528	Prince Edward Island			
K0FPC	37	23	2,438	VE1ABU	6	4	72
<b>Kentucky</b>				<b>Brazil</b>			
WA4EBN	50	26	3,900	ZY1NEZ	11	7	154
<b>Louisiana</b>				<b>Japan</b>			
W5WG	101	33	9,174	JA2YKA (JE2SRB, JA9SSY, JR2GMC)	51	25	3,250
<b>Maine</b>				JA1VVK	19	8	440
KA1HB	18	15	810	<b>New Zealand</b>			
<b>Maryland</b>				ZL2RY	29	13	1,131
W3FG	40	18	2,106	<b>Washington</b>			
<b>Massachusetts</b>				Adams county			
W1AQE	26	17	1,326	N7AYF/M	92	37	6,808
KA1CLV	28	12	1,008	KN7L	181	46	24,426
<b>N. Michigan</b>				Benton county			
W8WVU	70	30	6,300	K7FR	250	46	23,000
WB8WKQ	75	30	5,640	Chelan county			
KS8Q	66	26	4,472	K7GAH	63	28	5,292
<b>Minnesota</b>				Clallam county			
WB0LNO	13	10	260	WA7YMC	175	44	18,832
<b>Missouri</b>				Clark county			
WA4PGM	19	13	494	W7GHT/M	25	15	1,125
<b>Nebraska</b>				Columbia county			
W0JLJ	12	7	238	N7AYF/M	93	34	6,324
<b>New Jersey</b>				Cowlitz county			
W2CC	2	2	8	KA7JVW	185	43	15,910
<b>New Mexico</b>				Douglas county			
K5QQ	11	8	184	N7AYF/M	52	27	2,808
<b>New York</b>							
W2WSS	25	15	1,125				
N2DBD	25	12	900				
<b>North Carolina</b>							
W4OMW	39	23	2,668				
<b>Oklahoma</b>							
K5KW	40	20	2,380				

## ENTRIES:

Logs must show all dates and times in GMT. A separate sheet must be used for each band. All contestants to compute their own scores and check for duplicate contacts. Dupe sheets must be submitted with logs to cover each band where more than 200 contacts are logged. For every duplicate contact for which points are claimed, a penalty of three contacts will be deducted by the contest committee. An excess of claimed duplicates may mean disqualification. No penalty will be exacted against duplicates for which no points are claimed. Each page must be clearly numbered and marked with contestant's call, year, and band to which it refers. All contestants must sign a statement that they have complied with the rules and terms of their license. All logs must be received by the Contest Committee, Radio Society of Bermuda, Box 275, Hamilton 5, Bermuda, not later than May 31st. Overseas contestants are recommended to forward their logs via airmail. All decisions of the contest committee are final.

Bermuda parish abbreviations are as follows: SAN—Sandys, PEM—Pembroke, SOU—Southampton, HAM—Hamilton, STG—St. George, DEV—Devonshire, WAR—Warwick, SMI—Smiths, PAG—Paget.

## TENNESSEE QSO PARTY

**2100 GMT March 19 to  
0500 GMT March 20,  
1400 to 2200 GMT March 20**

This is the 13th annual QSO party sponsored by the Tennessee Council of Amateur Radio Clubs. You may work the same station on different bands, modes, or counties. Repeater contacts are not allowed. Mobiles compete against mobiles, portables against portables. Single-transmitter entries only. No county line operations allowed for multiple contacts. Portable stations must set up per field-day rules. No "list" operations are allowed. No CW contacts in phone bands.

## EXCHANGE:

Signal report and state, province, county, or Tennessee county.

## SCORING:

Score one point per phone QSO; 1.5 points per CW QSO. Combine phone and CW scores as one contest. Recognition will be given for phone or CW only scores. Tennessee stations multiply QSO points

by sum of number of different states, Tennessee counties, and VE/VO provinces. All others multiply QSO points by the number of different Tennessee counties worked (95 max). For each portable or mobile station working outside their home Tennessee county, score 500 bonus points for each county outside of home county with a minimum of 10 QSOs.

## FREQUENCIES:

Phone—1860, 3980, 7280, 14280, 21380, 28580.

Novice—3725, 7125, 21125, 28125.

CW—1815 and approximately 50 kHz up from bottom of each band. Note, you must log a minimum operating time of 10 minutes for each change of band or mode.

## AWARDS:

Plaque to highest scoring Tennessee fixed, Tennessee mobile and portable, plus out-of-state fixed. First place certificates to highest scoring station in each state, Canada, DX country, Tennessee Novice/Technician, out-of-state Novice/Technician, Tennessee phone only, and Tennessee CW only. Participation certificates to every station sending in logs with at least 15 contacts.

## ENTRIES:

Logs must show date/time in GMT, station worked, band, mode, exchange, and score. Submit a cross-check sheet similar to ARRL CD77 for each band and mode with 100 or more contacts. Logs must be legible to avoid disqualification. Logs must be postmarked by May 1st and sent to: Oak Ridge ARC, Attn: Contest Coordinator, PO Box 291, Oak Ridge TN 37830. Please include a business-size addressed envelope with your logs.

## BARTG SPRING RTTY CONTEST

**Starts: 0200 GMT March 19  
Ends: 0200 GMT March 21**

The total contest period is 48 hours, but not more than 30 hours of operation is permitted. Time spent listening counts as operating time. The 18 hours of nonoperating time can be taken at any time during the contest, but off periods may not be less than 3 hours at a time. Times on the air must be summarized on the summary sheet.

There are separate categories for single-operator, multi-operator, and short-wave-listener stations. Use all amateur

bands from 80 through 10 meters. Stations may not be contacted more than once on any one band.

## EXCHANGE:

The message exchange consists of: 1) Time in GMT; this must consist of a full four-figure group, and the use of the expression "same" or "same as yours" will not be acceptable. 2) RST and message number; the message must consist of a three-figure group starting with 001 for the first contact made.

## SCORING:

All 2-way RTTY contacts with other stations within one's own country are two points; outside your country are ten points. All stations can claim a bonus of 200 points for each country worked, including their own. Note that any one country may be counted again if worked on a different band, but continents are counted only once. The ARRL country list is used and, in addition, each WIK, VE/VO, and VK call area will be counted as a separate country. Final score is (sum of QSO points times the total number of countries worked) added to (the number of countries times 200 bonus points each times the number of continents).

Note, proof of contact will be required in cases where the station worked does not appear in any other contest log received, or the station worked does not submit a check log.

## AWARDS:

Certificates will be awarded to the leading stations in each of the three classes, the top station in each continent, and the top station in each WIK, VE/VO, and VK area.

If a contestant manages to contact 25 or more different countries on 2-way RTTY during the contest, a claim may be made for the Quarter Century Award (QCA) issued by BARTG and for which a charge of \$3.00 (USA) or 15 IRCs is made. Make your claim at the same time you send in your log. Holders of existing QCA awards should indicate and list any new countries to be added to their existing records. Make your claims at the same time that you send in your log. However, due to the high volume of work, it will not be possible to prepare and dispatch any new awards or update any existing awards until the final results of the contest have been evaluated and published.

Additionally, if any contestant manages to contact stations on 2-way RTTY on each of the six continents and the BARTG contest manager has received either a contest or check log from each of the six stations concerned, a claim may be made for the WAC Award issued by the *American RTTY Journal*. The necessary information will be sent to the *Journal* who will issue the WAC Award free of charge.

## ENTRIES:

Use a separate sheet for each band and indicate all times on the air. Logs should contain: date/time in GMT; call sign of station worked; RST and message number sent; time, RST, and number received; and points claimed. Logs received from short-wave listeners *must* contain the call sign of the station heard and the report sent by that station to the station he is working. Incomplete loggings are not eligible for scoring. The summary sheet should show the full scoring, the times on the air and in the case of multi-operator stations, the names and call signs of all operators involved with the operation of the station. All logs must be received by May 31st in order to qualify. Summary and log sheets

are available from the contest manager at the address shown below. The judges decision will be final and no correspondence can be entered into, in respect of incorrect or late entries, and all logs submitted will remain the property of the British Amateur Radio Teleprinter Group. Send entries to: Ted Double G8CDW, 89 Linden Gardens, Enfield, Middlesex, England EN1 4DX.

## SPRING VHF/UHF QSO PARTY

**Starts: 2100 GMT March 26  
Ends: 0400 GMT March 27**

Sponsored by the Ramapo Mountain Amateur Radio Club, this year's rules for this VHF/UHF contest are similar to last year's rules and current ARRL contest rules. Operating classes are defined as follows: single operator—one person performs all transmitting, receiving, spotting, and logging functions; multi-operator—those obtaining any form of assistance, such as the use of relief operators, loggers, or spotting nets.

## EXCHANGE:

Each 2-way QSO must include an exchange of station call sign and section designator.

## SCORING:

The grid-square and range scoring system has been retained, based on proven results obtained from the 1982 ARRL UHF contest. Each section is a geographical area one degree in longitude by one degree in latitude, identified by a 4- or 5-digit number indicating the next lowest degree of longitude and latitude. For example, RMARC club station WA2SNA, located in Oakland NJ at 74° 15' west and 41° 03' north, would use a section designator of 7441.

Each QSO has a point value based on the distance between stations as determined by the larger of the differences between the section designators' latitude or longitude plus 1, with a maximum of 10 QSO points. For example, WA2SNA in 7441 works W3XX in 7638. The difference between 74 and 76 is 2. The difference between 41 and 38 is 3. The larger difference is three; adding one to it results in 4 QSO points.

The section multiplier is the total number of different sections worked per band. The following band multipliers are used to determine the final score for each band: 50 MHz = × 2, 144 MHz = × 1, 220 MHz = × 8, 432 MHz = × 4, and 1296 MHz = × 16. The score per band is equal to the total of QSO point values per band times the section multiplier times the band multiplier. The total score is the sum of individual band scores.

## ENTRIES:

Prepare a separate log sheet for each band. Heading information must include your station call sign, section designator, and class of entry. Each QSO entry must include the date and time in UTC, call sign, section designator, and QSO point value. Each band summary must include the total of QSO point values and the total of different sections worked.

One entry sheet should be prepared for each band. They should include the band, QSO point total, number of sections, band multiplier, and band score. Also include the total of all band scores, your station call sign, your section designator, ARRL section and division, and mailing address. It must also be signed by the licensee or trustee of the call used.

Until May 1, you may send an SASE to the Ramapo Mountain ARC, PO Box 364, Oakland NJ 07436, to receive logs and entry forms.

# HAM HELP

I am looking for original copies of the TME 11-227 and TME 11-227A directories of WWII German and Japanese radio equipment. I also need Intelligence equipment from pre- and post-WWII such as the SSTR-1 and the SSTR-5.

Tony Grogan WA4MRR/F0NZ  
5 Rollingwood Dr.  
Taylors NC 29687

I want to get in touch with people who are experienced in dealing with power companies and who know what can be considered normal or abnormal power line noise.

Gary Mitchell KH8AC  
PO Box 184  
Comwall Bridge CT 06754

Could someone please help me find a manual for the Telequipment model D-66 oscilloscope? It was made in England. I will gladly pay for the manual or for a good copy of it.

W. G. Driscoll KC4KE  
6060 James Rd.  
Austell GA 30001

I would like to locate the manual and schematics for the Hammarlund HFM-40. I will pay for postage and copying costs. I am also interested in hearing from anyone who has put the HFM-40 on 6-meter FM as a repeater.

David Kelly N4HHE  
4223-D Myrtlewood Dr.  
Huntsville AL 35805

# W2NSD/1 NEVER SAY DIE

editorial by Wayne Green

from page 8

which is sought in schools, but merely that the right system be used in getting an answer.

We know that some people have no problem at all in learning the code. These people normally see no reason why everyone else shouldn't have to learn the code, too. I'm fortunate in that I am able to get my code speed anywhere I want it in a jiffy. A few hours and I'm zipping along. It took me maybe a half hour to learn the code in the first place and just a few hours to get to 13 per. The nervousness of the exam put me off the first few times I went down, but finally... after not having practiced more than an hour total since failing the test, I went down... more to help another chap than to take the test myself. I decided that well, hell, as long as I was there, why not? Passed—no strain.

Others are able to rack up hundreds of hours trying for the big 13 and develop quite an inferiority complex over the situation. They try code tapes, copying over the air, classes, and so on. Nothing works. I'm talking about reasonably intelligent people. The army found that a certain percentage of their recruits were just flat unable to learn the code, so they would try them out for a few days and get rid of the people who were difficult learners.

Now, if a person makes a serious effort to learn the code, but is prevented by a lack of the right brain circuits, I assume that this is the kind of stupid person we want to keep out of our hobby, right? And I assume that no matter what this person has achieved outside of this code failure, he should be prevented from getting a ham ticket and bothering us. I have in mind some absolutely brilliant electronics engineers I've known who tried and tried to get the code and just couldn't... who needs that kind of trash on the bands?

No, the majority is probably right in pushing hard for us to keep our present system of encouraging everyone to cheat as much as possible on the technical exam, using the Bash materials so they don't have to know one damned thing about electricity... and sorting it out with the fabled code test... unless, of course, they buy those California tapes... in which case, they will have in their hands the actual FCC code test. Oh, well, we can't win 'em all, right? Will these tapes be available in Dayton again this year? Bet they will.

More than changes in the exams or in the code tests, perhaps it is time for us to consider putting more of the responsibility for the growth of amateur radio onto our clubs. Right now, most of our clubs attract newcomers, who attend a few meetings and then get bored, dropping out. For the most part, I've been finding our ham clubs in the hands of a few old-timers who like to get together and meet each other. Not much more than that happens. I see youngsters very rarely at club meetings and when I do, I often hear grumbling by the grizzled old men who sit toward the back of the room in a separate group.

Perhaps we are happy with a dying hobby and perhaps these old-timers are absolutely right... we shouldn't make any changes. Why should we go out and try to get 12-year-old kids into hamming? They're a bore on the air and create trouble at club meetings. Besides, all this stuff about needing kids so they can become career engineers and technicians is a waste of time... we can buy all we want from Japan and other Asian countries. Heck, even if we did develop technicians, our companies couldn't afford to compete with Japan and Taiwan... wages are too low over there. And besides, their governments are backing their electronics industries while ours is doing its best to screw ours.

Yes, perhaps the old-timers are right and the situation is completely hopeless and there is no use in even trying to do anything about it.

But, Pollyanna me... always the hopeless idealist... I keep thinking that if we could only get our ham clubs to get into the excitement of recruiting youngsters in the 12-15-year age bracket... infect them with the virulent virus of hamming... run classes as part of our club activities... and then have it so our clubs could give the license exams instead of wasting FCC money on this, we just might get some growth started.

We have such an incredible way to go to even catch up with Japan, much less get ahead of them again in electronics, that even if we were to get ham radio growing at 33% per year, it would take over ten years just to catch up... and a few more years to get ahead again. It may take that long before the government (congress) recognizes that business needs help, instead of regulation and taxing, if it is going to compete on a world basis. I really hate to see the US losing one electronics market after another to Asia... because we have so few technicians, so much difficulty getting growth capital, minimum wages driving up costs, so little emphasis on automation and robotics... and so on.

When I looked into building a new plant for our instant Software division, I found where the bottom line was. Let's say I wanted to set up a plant with \$100,000 worth of equipment to produce a product which I would sell largely worldwide. Now, in the US, before I could invest the \$100,000, I would have to earn \$200,000 and send half of that to the government in taxes. In Ireland, I found that I would have to invest only \$50,000 and the government there would match that, giving me the needed \$100,000. Further, the government would train workers for me at their expense... and wages would be far below ours to boot. Is it any wonder that Apple, Memorex, and many other firms expanded into Ireland instead of adding facilities here? You get four times the bang for the buck there, so businessmen put down their waving flags and were practical.

Getting back to hamming... one of the reasons I have been pushing so hard for all these years to get the legislation through to allow clubs to give the tests is my faith in the clubs as the best approach we have to getting growth of the hobby.

Now that the law has been changed to permit this, I'm anxious for us to get started. I believe that if clubs do the teaching of our newcomers and the testing, we won't need any FCC tests or code. The clubs will know who is serious and who isn't. I'm hoping that this sort of entry into the hobby, where newcomers are taught not only theory, rules, and such, but operating procedures and ham lore as well, will result in much better hams.

In the meantime, I'll be pushing where I can... publishing articles on construction projects... and so on, all trying to keep things moving in the direction that seems most productive for hamming... and our country... In the long run, I'd sure like to have your help and support, but I'm used to being fought and jammed, so I'll do my best with or without help.

## BASHED YET?

Yep, my good friend Dick Bash is at it again. You really have to give him a lot of credit. A lesser person would have become discouraged when the FCC changed the test on his blitz-taught students and flunked almost all of them. Well, Dick had their money, so it was no skin off his... er... nose, right?

So Bash is going out again, giving his one-day intensive memorization of the FCC answer courses, all for the low, low price of \$150 for the Tech/General or Advanced, or \$225 (wow, a bargain!) for both. Dick has a nice guarantee for you, too... if you pass, he keeps the money. If you flunk, he keeps the money. What could be fairer than *that*? Oh, if he runs the class again, you can take it again for free if you can find it. If you don't register ahead of time, it's \$25 more at the door for each course.

Will the FCC be waiting for their nemesis again with a new exam and flunk his trusting flock? Heh, heh, only the Shadow knows.

If the FCC doesn't change the questions, Bash will definitely get you ready to pass the exam. And you don't have to worry one little bit about having to learn a thing about electricity or radio. No knowledge or understanding whatever is necessary to pass this test once you have been grilled in the answers for a full day. But better not wait a day or you may start forgetting some of the test answers.

Bash will be going around to Seattle, Los Angeles, San Jose, Chicago, Boston, and Dallas. Let me see... with about thirty students per class, twelve classes in about a one-month period, ole Dick is going to really rake it in. Who says you can't make big money out of amateur radio? Not counting all of his sales of books and code courses (\$10), it looks as if Dick could pull in \$45,000 in that one big swing. Hey, good work there, Dick!

I don't know if Dick picked up the FCC's actual code exam from the booth near his at Dayton, but if he did, you are really in luck. Why, you would then be able to pass the whole FCC exam without knowing either the code or the theory, rules... or anything! By golly, if we can't get some growth in the hobby this way, what will do it?

## ANOTHER OGRE

Not all of the falling behind of electronics manufacture in our country can be laid at the feet of the ARRL and their incentive licensing disaster of 1963. The resulting loss of engineers and technicians to the country has been devastating, but there have been other factors involved which

have worked to cut American production and put Americans out of work.

One of the more insidious robberies of jobs has been caused by the borrowing of cash by the government to pay the increasingly large government debt. They've done this via short-term, high-interest notes which investors have been buying. According to the most recent figures, the government is now responsible for 29.7% of *all* borrowing. This has doubled in the last decade and has a lot to do with the unemployment situation.

Remember that the more profits companies can make, the more they will expand their operations, creating jobs. And as people make higher salaries they will spend more, again creating jobs. But when the government comes in with super high interest on their borrowing, this takes billions away from the private sector... billions which would otherwise be invested in making more jobs.

The deficit of 1982 is mind-boggling, of course, but one sadder result of this is that the 200 billion will have to be borrowed from investors, further robbing our industries of investment capital and thus preventing them from investing in growth and the badly needed creation of jobs.

This bleeding of investment capital by the government reflects back on us in another insidious way, too. By keeping our industries from getting reasonably-priced money for modernizing plants, they are forced to be ever less competitive with foreign manufacturers. Today, the US has the highest percentage of obsolete plants, the lowest percentage of capital investment, and the lowest growth of productivity of any major country.

This is a difficult situation for those who want to expand welfare and unemployment benefits. In order to get the money to pay people who are not working, we have to borrow it from those who are. And when we use money in that way, the government has to compete against our industries to borrow the money, taking it from them with higher interest rates. Yes, these people spend the money, but make nothing for us to buy in return for it, so the capital thus used up does not end up making more. This unwinds the economy and makes us less productive.

There is no simple answer to everything, but we do at least see a lot of the problems which are sinking our country. The lack of capital for building new and modernizing old businesses is damaging. The lack of trained technicians and engineers puts us at a further disadvantage. If we did have the cash to expand electronics production, we would probably send it to Asia, where we would get more return for the investment because they have more and better technicians there.

If we are able to start getting our kids interested in amateur radio, we could, in a decade, begin to turn the engineer and technician problem around. The cash situation is not going to improve until we make it clear to politicians that we are serious about eliminating deficits. I note that there are a lot of senators and representatives who do not yet have this message... which means that we are not making that clear.

## TOO MUCH SCIENCE?

On my birth certificate, it lists the occupation of my father as "aviator" and my mother as "artist." If you think about that, you'll get some insight into my trains and lapses of thought. There is the mixture of the mechanical and the artistic which resulted in a technical publisher.

This same background has led me to be interested in both the scientific explanations for the world and the occult ques-

tions which science has been unable to answer. Science has done a good job of answering many questions about how the universe works. But it has also failed to successfully tackle a great many observable phenomena. We have come to terms with many of these via religions, which call for belief without scientific proof. Other questions which are not answered either by science or religion tend to be pushed aside with annoyance.

But it is dishonest of a scientist to deny the existence of data just because he is unable to explain it or set up an experiment which repeats it. Science, if it is going to be true to itself, is going to have to admit that there are a lot of things which do not fit into the framework of the universe that they have built up. Scientists are going to have to start seriously trying to understand pesky things such as UFOs, ESP, reincarnation, PK, the spirit body, how memory works and where it is, medium communication with the dead, ghosts, and so on.

The easy path pursued by most scientists has been to unmask a few charlatans and then ignore everything else. Proving that a few of the UFO photos are fake doesn't solve the UFO situation at all.

The more we interest our kids in technical hobbies, the more scientists we'll end up with. You don't develop first-rate scientists by starting people in their 20s any more than you get good ballet dancers from late starters. No, it takes the twist of mind provided by amateur radio or computers (and I think we can all agree that these hobbies definitely do twist the mind) to get a good scientist going.

Dr. Hynek, the outstanding scientist investigating UFO phenomena, got his start as a ham. His credo seems to be much like mine...pointing to a wealth of data and a paucity of provable explanations...and asking if anyone can come up with a theory to explain all of this.

For all of our wonderful progress in science and the high technology gadgets we have derived from it, we still have an enormous number of rather key things which we don't understand and thus have to accept on belief. Once we start getting a handle on some of these mysteries, we will have powerful tools for further progress. Will an understanding of the essence of man lead to time and space travel in some mode barely dreamed of today?

Or will we find out that there really is some benefit to praying to the coffee table to have a nice day?

The questions are there in large numbers. We have to find out more about talking with plants, Kirlian photography, mind photographs, bent spoons, and so on. Can an understanding of human memory lead us to design computer memories in a different way, perhaps ridding ourselves of all size limitations?

Until we understand all of the mysteries of our world, we have plenty of room for science to work...and we need a good supply of new scientists. Hopefully, there will be a few more with the combination of the artistic and the mechanical...the scientific and the metaphysical...so that we will have some scientists able to tackle these things. Just ignoring them and refusing even to think about them is not a scientific answer.

In the past, I have written about such odd phenomena as UFOs, both about my own experiences in this field and those of other readers. I got quite a bit of mail from hams who had had personal UFO experiences. The easiest way to handle things like this is to ignore them. There was a "Nova" program recently which went to rather great lengths to debunk UFOs. And since then, I've read quite a bit about the

films they took for the show which were not shown...or even mentioned...films which give strong evidence that something odd really is going on. For some reason, they wanted to do another whitewash on the subject.

The same situation surrounds many of the anomalies which perplex the more thoughtful and open-minded scientists today. One can still find scientists with good reputations in some field who refuse to accept that there is any such thing as mental communication. Yet most of us have experienced this at one time or another, so we know it exists...and wonder at the objectivity of someone who won't even check the evidence. I will never forget some emotional distress I was under one day many years ago. I was distraught...and at that very moment the phone rang. It was my mother asking what was wrong, calling from 135 miles away. She'd never done that before...and never has since. There was no way on Earth that was a coincidence. She knew nothing of any of the situation or its development.

Ask me sometime about the UFO which a bunch of us here at the magazine saw just down the road one evening...and which suddenly sped away over the horizon in seconds when it started moving. We could see it for at least fifteen miles, a distance it covered in about four seconds—after hovering for several minutes.

There are a lot of things to investigate...if we can develop enough scientists...and they are able to break away from orthodox thinking enough to handle these elusive problems. But until we start getting more kids started in high-tech hobbies, our chances of making progress will be slight. Has your ham club done anything to spread the ham radio bug in your local schools?

#### DOWN WITH DXCC

My recent editorial pointing out the harm which DXCC and the Honor Roll has done to our hobby brought in an interesting letter from a well-known DXer. His response was to attack me, not the ideas which I had discussed.

The problem with DXCC is that it puts a premium on making contacts with operators in rare countries. This, in turn, if you stop even for a moment to think about it (which may be too much to ask DXers), means that operators in rare countries are not permitted to get on the air and rag-chew. Now, let's think about that for a minute. What is the most popular aspect of amateur radio? No, rag-chewing is by a wide margin the most popular amateur radio activity. We see the bulk of our low bands used for this, as well as virtually all of our VHF operation.

What chance does Paul 9M8PW in Sarawak have to rag-chew? He is no sooner on the air than the pileups start, with ops getting ever more insistent that he stop talking and give them a report and a QSL. They don't want to know about the Sarawak River and the twenty-foot-long croc which has been grabbing children up river. They don't want to know about Paul and what he teaches or that the monsoon rains have flooded half of Kuching that morning. They don't really care that his name is Paul or how long he has lived there or what he is doing...they want a QSL card so they can get a certificate. Many callers have no idea of where 9M8 actually is.

It turns out that Kuching is a fascinating place to live. Just a generation away from head-hunting, the people there are friendly and hard working. Once you get away from the capital city, you find that many of the small towns are built on stilts. Not just the houses, but entire villages are on stilts. They call them long

houses—often they contain hundreds of families living together. Each family has a separate set of rooms, but they are together, sort of like a bamboo-made hotel or motel. The ladders down to the ground are made out of single trees, notched to provide the steps. The people zip up and down these narrow stairs just as we do our three-foot-wide staircases.

Having towns on stilts keeps them above the water that runs off on the ground after the monsoon rains, which hit just about every day during half of the year. The temperature is comfortable, even though this is only about a hundred miles from the equator, running about 70° at night and maybe 88° during the hot afternoons. The humidity? Ugh! The rains last a few minutes to maybe an hour at a time, so you can usually outwait them.

Living is easy in a place like this, with hunger unknown. Wild bananas and pineapples are all around, coconuts, and so on. All sorts of fruit and vegetables grow in profusion. You just plant 'em and jump back. And living up off the ground not only keeps you away from the floods after each rainfall, but also keeps you away from most of the small animals and bugs. It's cooler, too. Even in town, many of the houses are built up in the air, with an open parking space for cars on the ground level.

But each remote country of the world has a different story to tell, if you'll listen. However, until we take off the pressure of the awards for getting QSL cards from rare countries, how are we going to share in these things? And how are we going to make hamming fun for ops in these spots?

I enjoy getting on for a few days from some weird place and making thousands of contacts. But remember that I do this for fun. I know that if I were to live in one of these places, I would get pretty tired of the unending pressure for the shortest contact possible, writing down calls month after month so chaps can get QSL cards. The paperwork involved is a drudge.

It's no wonder that every now and then we develop a DXpeditioner who uses this pressure to make money. People on the Honor Roll will eagerly pay \$50 each for a contact with a new spot. Indeed, that was the going price ten years or so ago. I'll bet that a mercenary today could ask for and get \$250 each for a new country. The charge for those not on the Honor Roll would be down to around \$25. If I ever retire from publishing, I just might grab a couple of portable rigs and set out to prove that I can make \$100,000 a year via DXing.

Now, for those readers who have not followed my personal enthusiasms, I'd like to assure you that you will have to look hard to find a more energetic contest. And I think I can keep up with anyone in the world when it comes to making fast contacts from rare spots. I've got that down to a science now, if you'll break quickly with the last letter of your call, please. Hold off for a few seconds and give it to me just once phonetically and I'll get you. If you give it twice, you'll go to the end of the list. I don't just work the loud stations that way—I work right down to the weak mobile stations and other rare DX callers.

Can anything be done about DXCC and the Honor Roll? Of course not, but that isn't going to stop me from beefing about what it has done to amateur radio. Who knows, I may come up with something even more pernicious.

#### ASIAN TOUR

Speaking of Asia, I'm sponsoring a tour

of Asia for this coming May. If you're interested in a first-class trip. This will be a short one, running about two weeks, and will visit Tokyo, Taipei, and Hong Kong. This is aimed more at the computer aficionados, so it will coincide with the micro-computer show in Tokyo, plus smaller get-togethers in the other countries (which are not as deeply into micros as Japan).

The tour will use the best of hotels...strictly first-class...and includes breakfasts and even some of those spectacular dinners. Having just returned from one, I can tell you that they are truly first-rate.

In Tokyo, we'll try for a meeting with the TIARA, the Tokyo International Amateur Radio Association. You'll not want to miss Akhabara, the electronics section of Tokyo, with hundreds of stores selling electronic equipment, ham gear, parts, and so on. You'll find most of the ham rigs running about 50% to 75% of the American price...unless you wait for Hong Kong, where they are generally even lower.

You'll get a kick out of Tokyo. The subways are easy to use. There are McDonald's all over the place in case you get a Big Mac attack...plus all the old home features such as Shakey's, Kentucky Fried, and even Wendy's. For the more adventurous, there are all kinds of Japanese meals, from raw fish right on through. This last trip, we had a complete raw-fish meal, with two courses of raw whale included...courtesy of the chaps at TDK.

If we get some hams on the trip...and you're interested...I'm sure we'll get a good reception from Kenwood as well as TDK...and perhaps Yaesu. We'll be too far away for Icom, unfortunately...wonderful people.

In Taipei, you'll enjoy the city...the people...and some of the incredible things you can see there. We can certainly get together to meet Tim Chen and see the radio club...and BV1A. I don't know if we can swing it to let you sit down at the mike of the station or not...but it's worth a try.

The next stop is Hong Kong, where you won't believe the prices on electronic equipment. There are dozens upon dozens of small shops, all trying to outdo each other. The city is big, with hundreds upon hundreds of high-rise apartments and business buildings. Transportation? Anything and everything...from modern subway to trishaws. I like Phil VS6CT's approach to crossing the ever-jammed streets. He just steps into the traffic without looking at the cars and they always stop for him. It takes some guts to get used to his system, but I can assure you that it works. He's lived there for years and is still alive as testimony.

If you bring along an HT, we can get ham tickets in Hong Kong. No problem...get 'em in minutes. They have a repeater, of course.

The ferry across the bay between Hong Kong and Kowloon costs 8¢ for first class, as I recall. Wonderful sight—and you'll get great pictures.

The tour starts from Los Angeles on May 20th and will be returning two weeks later, June 3rd. This is immediately after NCC in Anaheim, which runs May 16th-19th. I'll be there for NCC and then go on the tour, so if you go, you might not only have someone interesting to talk to, but you will also have someone who really knows the ropes.

If you have the wanderlust as I have, you may want to delay your trip back for a few days and add some other countries to your trip. This can be done remarkably inexpensively. Travel in that part of the world can be surprisingly low-cost. This last trip, I added a bunch of extra stops to

the tour, going to Singapore, Bangkok, Kuching (Sarawak), Brunei, Sabah, and Manila. I traveled a day and then visited two days, taking three days more for each country visited. The hams in each country were first-rate. The hotels were fine (except for Brunei... and now I know of a good one there) and the food superb. I gained five pounds on the trip... despite my jogging just about every morning. You'd laugh to see me running three and four miles in the early morning through the streets of Taipei, stopping now and then to snap a picture.

Other than imitation diamond-encrusted \$15,000 Tiffany watches for \$30, what bargains are there in Taipei? Plenty. You'll be shopping up a storm in the department stores there. You'll also get pretty sharp with chopsticks.

I don't have the exact price of the tour yet, but I'm sure it will run no more than around \$2,500 for the air fare, hotels, many meals, all ground transportation, tips, airport taxes, and so on. Also, when you are in a group like this the usual baggage limits are waived, so you can pick up all the souvenirs you want. Drop me a line if you're interested and I'll send you letters on to Commerce Tours in San Francisco, the firm we work with on trips like this.

#### TAIWAN IN TROUBLE

Taiwan has been growing almost incredibly in exports over the last few years, but they are getting into deep trouble these days... mostly as a result of their success. Most of the products of Taiwan have been labor-intensive, depending for their success on low wages. But now, as their wages have escalated... inevitable with only a little over 1% unemployment... they are becoming uncompetitive with similar goods from other low-wage countries such as the Philippines, where the minimum wage is around \$2 a day and many people still have to live in the streets.

The obvious route is to change from labor-intensive goods to higher-priced things such as electronics... but here they are up against an educational problem of enormous proportions. Japan made this change from inexpensive exported goods to high-priced, high-tech manufacturing years ago and has built up the infrastructure of education needed to support such an industry.

As any DXer is well aware, there is exactly one ham in Taiwan. I had the pleasure of having breakfast with Tim Chen BV1A during my recent visit to Taipei and discussing this with him. Tim had some hope because there is a move underway to bring more people into amateur radio in Taiwan which could eventually result in dozens of stations on the air. In the past, the government has discouraged new amateurs or even shortwave listening,

with the result that there has been no real incentive for kids to get interested in radio. This, in turn, has made it so that there have been very few electronics engineers or technicians in Taiwan.

I've been getting to the Taiwan Consumer Electronic Shows for several years now, seeing their products and talking with the manufacturers. I've also endeared myself to businessmen of Taiwan by pointing out what they already know... that their electronic equipment is all imitative, with no creativity in evidence. Thus their equipment has had to sell almost entirely on price, with new ideas and quality taking a back seat.

Lacking the scientists to develop new products, or the engineers to put in automation and robots, Taiwan has had to depend mostly on copying the equipment from other countries and on their low wages. Now, with their wages rising faster than those of the rest of the world, they are in trouble, and they haven't the supply of engineers and technicians to turn to for help.

Business has been brisk in recent months in rip-offs of the Apple computer. Again, lacking anything significant in technicians, Taiwan manufacturers have had to turn to copying the most successful of the microcomputers, the Apple. There are over a hundred small firms... and some fair-sized ones, too... making Apple imitations. I saw them everywhere at the electronics show in Taiwan and even had a chance to talk with some of the manufacturers personally.

If Taiwan is able to get kids interested in high-tech hobbies such as amateur radio and computers, the country could, in a few years, be able to get away from trying to make a living from the ideas of others and come up with creative ideas of their own, as has Japan. Within the memory of those of us who were around in WWII is the image of Japanese products as being junk. For many years, most Japanese products were cheap imitations of better products, with shoddy workmanship.

Today, as you know, not only has Japan set the world standard for productivity, but also for quality. They've left most other countries far behind in these regards. And in the last few years, we've also seen the emergence of Japanese creativity.

Though I put a good deal of emphasis on the importance of getting kids into high-tech hobbies as a way for a country to develop technicians and engineers, I am among the first to agree that this is by no means the only problem we have in trying to compete with the Japanese. But without being able to match them... or even come close... in engineering talent, no amount of government help of industries, more favorable tax climates for electronics firms, etc., is going to help us

to regain world superiority in technology.

There have been a number of good programs on television lately showing the difference in education between the US and Japan (and even Russia). Our schooling system has disintegrated a good deal since I went to school, with math, sciences, and so forth being almost done away with in many areas. No wonder kids are having a problem even with the Novice ticket, which anyone with a high-school science education should be able to pass. The fact is that few kids are getting a high-school science education. Phooey.

Oh, there are a lot of things we need to overhaul... and I will make few friends by bringing these things up. One only has to read the reports in *Reader's Digest* on the activities of unions to terrorize uncooperative manufacturers to realize that America has no monopoly on human rights. While we are indignant over the Israelis making life extremely miserable for the Palestinians, the torture in Argentina, the executions in Guatemala, and so on... things which are going on all over the world... we have not too different things going on right here which we want to cover up.

The worker who works harder than his fellow workers is harassed until he slows down and stops making everyone else look bad. I saw that one myself back when I worked for a company which made transmitters for the Army. The union there was furious that the test people didn't just pass along anything put together by the production people... and never mind that the transmitter would be needed by the Army in working shape. When I got busy and turned out about double what my fellow workers could manage a day, they started sabotaging the units I'd aligned to prove that I was turning out poor work. No, I've been there, so when I read about this happening all over the country, I tend to believe it.

We geared up and won WWII, getting the cooperation of millions of people. I think we can surmount the current depression if we make a decision to do it and stop our own people from fighting each other. Unions can do worlds of good to help people and production... they can also drive you crazy with featherbedding, slowdowns, restrictive work rules, intra-union fighting, and so on. Unions which insist on using every weapon at their command to maintain their members at higher than the normal wage for their work are robbing the rest of us. This comes to roost when they come up against foreign competition, such as with cars. American cars would drive the Japanese cars right out of the country if the car unions would settle for average wages for their workers and put on the pressures for productivity and quality.

When I have to rent an American-made

car on a trip, I am invariably amazed at the poor performance and quality of the product I am driving as compared with my Japanese cars. That door doesn't fit right because someone on the production line just didn't care... and the inspector was under union pressure not to make the worker look bad... or was out on coffee break when my car went by.

Well, the world is changing. More and more "workers" are going to be replaced by robots who do not forget a few screws and bolts when assembling a car. Robots will make the windows fit exactly right. Robots will not call in sick when a DXpedition is brewing on 20m or when hung over from too much brew the previous night. Workers are going to have to think in terms of education... perhaps with some science in the mix so they will be able to cope with the type of work we have today... and will have in the next twenty years.

The world of 1999 looks to me as if it is going to be a high-tech world, with telecommunications on the order of 10,000 times more than we have today... with people able to communicate with others anywhere in the world in seconds from small hand-held computer-like communicators. We'll have teleconferencing and so on. But these developments are going to call for an incredible number of technicians, engineers, and scientists. Our present school system is totally inadequate to cope with this need.

Taiwan has the same problem, only it is hitting them hard right now. They need thousands of technicians and engineers and they need them today. In all of Taiwan, I found one firm with an innovative computer product. That was the Micro Professor, which looks like a comer. It will run Apple programs, but does not appear to be an Apple rip-off, even in its electronics.

One is struck by the impact of the lack of copyright enforcement in Taiwan. Not only are there many bookstores full of cheap copies of almost all of our best-selling computer books, but one can also go into stores all over Taipei and buy a \$15,000 watch for about \$30. Sure, it's a copy, but a good one. I picked up some local copies of Apple manuals... and saw any number of copies of well-known programs, usually selling for about \$10. Not bad for VisiCalc. Within days of a new program coming out in the US, it is available all over Taipei for a few dollars.

Taiwan will be able to shift to higher-tech products and thus make more income per sale... and be able to pay higher wages... if they have the technical people to cope with the changes in world technology. To me, this means getting their kids into high tech and providing the schools they need to take this interest and develop it.

## HAM HELP

I have a Midland model 13-866 CB radio which I converted to 10 meters, following the modifications outlined in the April, 1981, issue of 73. However, it does not receive on 10 meters, the transmit signal is garbled, and it will not change frequencies. I need information on how to make it work.

Joe Oden WD9HYM  
4129 South Wichita  
Wichita KS 67217

I need the following items: horn speakers, spark gear, high impedance headphones with cords, 201A (or equivalent) tubes, old terminals, bus-bar wire, vernier dials made prior to 1930, 2- to 4-inch bakelite 0-100 dials, and telegraph keys.

Alan Shawsmith VK4SS  
35 Whynot St.  
West End, Brisbane  
Q 4101, Australia

I am looking for construction plans or a schematic for a one-tube QRP rig.

MacArthur Moore  
5230 Heston  
Philadelphia PA 19131

Could someone help me find the schematic for an Elco model 150 signal tracer?

A. B. Wells WA5COM  
PO Box 50  
Tunica LA 70782

I am looking for CB magazines printed prior to 1967.

John W. Heacock K3YCP  
8100 Bass Lake Rd.  
Apartment 110  
New Hope MN 55428

I am trying to find the manual and replacement capacitors for a Hallicrafters Sky Ranger S-39 receiver. I also need an operational or as-is DX-40 transmitter and a manual. I am willing to cover copying and postage costs.

Dave Drinnan VE3MPX  
21 Beaverbrook Lane  
Kanata, Ontario  
Canada K2K 1L4

I am searching for service manuals or schematics for the Jefferson-Travis model 350A-1, vintage unknown. I will pay for postage and copying costs.

Steve Stout WA5CRI/9  
1537 Kinselow Dr.  
Palatine IL 60067

# REVIEW

## THE AEA CODE TRAINER

Everybody has his own way of learning the code, and most people think that the way that they learned it was the best. It was with this possible bias in mind that I approached the AEA BT-1 code trainer, a Morse-code training device that uses no tapes but an IC to produce the tones.

AEA, which specializes in keyers and code readers, should know the code better than many manufacturers, and this knowledge has led to a novel approach for learning the code. The BT-1 is designed for use by people who are completely unfamiliar with Morse code. With the trainer, you move step by step through each character, singly and then in groups.

So far, this is pretty standard fare. However, the machine does not teach the code from simplest to more complex, for example from E to Y. The first character learned is F, and from there the student moves on to K, B, Q, and the last letter learned is I.

In addition, the code trainer does not begin sending each character at a slow speed. Every character is at its 20-wpm length, regardless of the spacing between characters. As they explained in the manual, this is to overcome the proverbial plateau many people encounter at about 10 wpm. By learning the sound at a higher speed at the start, your ear will have to adapt less as you increase the code speed.

AEA also suggests a strict adherence to the sequence of characters which they suggest. After learning to recognize each character, both by itself and in groups of increasing length, the student moves to the next character. As he or she moves down the list of new characters, the characters previously learned are thrown into the

groups at random. However, the character being learned is weighted at 50 percent—that is, one-half of the characters will be the new character.

Once all of them have been learned (the list includes numbers and common CW ciphers), the student can increase the speed by decreasing the spacing between characters and changing the character length as well. Each training selection may also be called up without weighting the new character, making the characters of each group completely random.

The BT-1 has several accessories which enhance its use, such as a full-sized headphone jack instead of a 1/4-inch earphone jack, and a second jack in which a key may be inserted for use as a code practice oscillator. The pitch of the tone is also selectable in discrete steps, adapting the trainer to a variety of ears. Its small size and the included nicad battery pack and charger make it extremely portable, so you can get your daily half-hour of practice in many situations.

A 12-button keypad controls the operations of the BT-1. However, one of the difficulties in using the trainer is learning the commands which control it. All of the commands, except for the stop command (#), are at least 2 keystrokes, and in most cases 4. I found that to use it I had to have the manual close by at all times for quite a while until I learned the proper commands.

Because of the relatively complex controls, the speed at which you are copying is also difficult to determine. One command sets the character speed from 18 to 99 words per minute, and another command sets the delay between groups of characters. The delay range is from 0.1 to 9.9

seconds, with a default value of three seconds. The character speed default, as mentioned above, is 20 words per minute.

For this reason, as well as the somewhat limiting factor of listening to code in purely random groups, I found that the code trainer worked most effectively in conjunction with tapes. For characters with which I have difficulty, such as X and some of the CW ciphers, I drilled myself on the BT-1 to increase my proficiency. But to increase my overall speed, I found that I used tapes. With the known speed for the tapes, it was easier to keep track of my progress, and it alleviated the boredom of listening to and writing random groups.

However, I would recommend the code trainer to Novice classes and individual students. AEA's method, while not the standard procedure, seems to work. The portability of the unit would hopefully lead to more frequent use. And, as we all know, there is no substitute for diligent practice when trying to learn the code.

For additional information, contact *Advanced Electronic Applications*, PO Box C-2160, Lynnwood WA 98036; (206) 775-7373. Reader Service number 486.

Avery L. Jenkins WB8JLG  
73 Staff

## THE AZDEN PCS-4000

The progress of large-scale integration (LSI) has left harms somewhat in its wake, because this technology is highly dependent upon the economy of scale—the more you make, the cheaper they get. The amateur market is often too small to bring the advantages of LSI to bear in new products. However, Azden has brought amateurs back to the state of the art with the introduction of its new PCS-4000 2-meter transceiver.

Azden's use of LSI has enabled it to produce a microcomputer-controlled radio that is little larger than the average in-dash AM radio. The PCS-4000 measures 2 inches high by 5 1/2 inches wide by 6 1/4 inches deep, and much of this miniaturization has been accomplished by replacing mechanical control mechanisms with logical functions performed by the microcomputer.

All of the transceiver's tuning is conducted through the 16-button keyboard, which doubles as a touchtone™ pad. The Azden has an extended range of 142 to 149.995 MHz and frequencies may be selected in 5- or 10-kHz steps or from the two banks of 8 memory locations. The relationship between the memory banks is controlled by a 4-position memory mode switch. This switch allows the operator to choose a frequency from either bank, both banks, or select a receive frequency in one bank and a transmit frequency in the other. By using this switch, non-standard repeater offsets may be programmed into the machine.

Standard offsets and simplex operation are also selected via the keyboard, and the offset may be stored in memory with the chosen frequency. Nine LEDs indicate the memory address and bank currently in use.

Other indicators on the front panel include the green LED frequency display, which indicates the transmit frequency as well as the receive frequency, a digital S-meter, and a channel-busy indicator. Other LEDs show whether the PLL circuit is locked, which offset has been chosen, and whether the frequency is from the memory bank or has been directly keyed in.

Besides the volume, squelch, and memory mode controls, the PCS-4000 sports only 4 mechanical controls. Three switches choose the frequency step, select whether the scanning feature will settle on busy or vacant frequencies, and turn on the optional 1750-Hz tone.

The scanning features may be used in conjunction with the memories, or an entire portion of the band may be scanned to locate

either busy or empty channels. These options are also keyboard-selectable. The scanner will also automatically resume after monitoring a busy channel for about 10 seconds, which gives you enough time to decide whether you want to stay on that frequency or not.

The Azden puts out a husky 25 Watts in the high power mode and 5 Watts in low power. Current consumption runs from 0.6 A in receive to 6.0 A while transmitting, and spurious frequency rejection is better than -60 dB.

The receiver has a sensitivity of 0.2 uV and a selectivity of 6 dB down @ ± 6 kHz and 60 dB down @ ± 15 kHz. The audio output is 2 W into a 2-inch speaker. The receiver is a double heterodyne operating with a first i-f of 16.9 MHz and a second at 455 kHz.

The transceiver is controlled with an MB 8855222M single-chip microcomputer. Circuitry has been sectioned into four boards—the control board, the PLL and transmit circuitry, the receive unit, and a PA board. All of the functions of the PCS-4000 have been packed into 15 ICs, 9 FETs, and 34 transistors.

The flexibility of the microprocessor control system has given the PCS-4000 a variety of special functions which I have found valuable. Besides being able to select a frequency or memory address from the keyboard, a single button will reverse transmit and receive frequencies. I have found this feature useful for quickly finding out whether a station is strong enough to work simplex.

Another very valuable feature not found on many other radios with programmable memories is the nicad backup which Azden built into the transceiver. Although the manual recommends supplying power to the radio directly from the battery, the nicad will preserve the radio's memory when it is removed from the permanent power source. I regularly take my radio inside for safekeeping, so without this feature I would have to reprogram 16 channels every morning. The nicad is automatically recharged whenever the radio is on, and it only supplies enough power to retain the memory; you cannot operate the transceiver from the battery.

The battery comes with the initial charge already completed, unless the unit sat on a dealer's shelf for several months. Azden has included as an accessory the necessary jumper cable and instructions for charging the battery should it be necessary.

There is also one priority channel in each memory bank, in the first memory address. The priority channel in either bank can be instantly accessed, regardless of what bank you are presently operating from. Two buttons on the keyboard are reserved for this function, and the priority channel in the first memory bank may also be called up with the remote control located on the microphone.

The microphone incorporates two other controls as well. The up/down buttons will change the frequency by 5- or 10-kHz steps or will proceed sequentially through the memory if you are operating in the memory mode.

The scanning circuitry has proved to be especially versatile, and with it I have found and immediately been able to access repeaters that I previously did not even know existed. In addition to searching for your choice of busy or vacant channels and scanning the memory or a selected band slice, the scan may be conducted with a repeater offset. For example, if you are scanning the range above 147 MHz, you can instruct the transceiver to automatically add 600 kHz to your transmit frequency.

The 25-W output gives the PCS-4000 a good signal range, and all comments on the transceiver's audio give it a good report card. It picks up little road noise, and the audio lacks the heavy bass component found on some other transceivers.

Although I have had some problems with the transceiver, they have been relatively



AEA's BT-1 code trainer.

minor and can be expected as an operator adapts to a new radio. The microphone button which calls the priority channel is located on the upper tip of the transmit button, and therefore is easily activated when you are pawing for the microphone while keeping one eye on the road. Until I became used to handling the microphone differently, I sometimes would begin a QSO on 146.150 and suddenly find I was talking to the breeze on .52 simplex.

There is also an interesting feature on this radio which could be made more useful. The PCS-4000 will emit a beep whenever a keyboard command is received, enabling the operator to do some extensive radio fiddling while keeping his or her eyes on the road. Unfortunately, the beep is not always loud enough to hear over the road noise.

However, these are minor problems and not integral to the otherwise excellent capabilities exhibited by the PCS-4000. By using the options available on this radio, I have found a versatility in mobile operation previously just imagined and proved to my satisfaction that bells and whistles are not always superfluous, but can become a useful adjunct to my operating. And by bringing state of the art back to hams, Azden has provided an incentive for other manufacturers to try to catch up.

For further information, contact *Amateur-Wholesale Electronics, Inc.*, 8817 SW 129 Terrace, Miami FL 33176; (303) 233-3631. Reader Service number 487.

Avery L. Jenkins WB8JLG  
73 Staff

## TEN-TEC MODEL 560 CORSAIR TRANSCIVER

It was with a great deal of anticipation that I sliced the packing tape on a huge shipping carton whose return address said Sevierville, Tennessee—Ten-Tec's home in the foothills of the Great Smoky Mountains.

For some time, those of us involved with the amateur radio industry had been hearing rumors of a new Ten-Tec transceiver reputed to be even better than, and a replacement for, their respected Omnicon. Very few, if any, of amateur radio's press had yet seen the new rig, and it wasn't until the dealer notices were out and some of the ads in hand that any of us really knew what the rig looked like or what its features were supposed to be. The introduction had been carefully planned to take maximum advantage of the traditional year-end buying season... a strategy sharing popularity with Dayton's famous Hamvention as an ideal time for the debut of new amateur radio equipment.

Like its privateering namesake, the Corsair was clearly intended to capture a share of the amateur radio marketplace from other well-known transceiver manufacturers. The ultimate test of that effort will be the reception by John and Joe Ham, but, for now, it was my privilege to have one of these brand-new, solid-state transceivers for evaluation. The 73 staff had requested that a full complement of crystal filters be provided to take care of RTTY and CW needs as well as SSB operation, so it was with considerable excitement that I finished opening the box. Time to see what was inside.

Two other cartons inside the large one appeared: a small and rather heavy one, and a somewhat larger but lighter one. Opening the small one first, I noticed the foam-in-place packing material completely surrounding the contents, conforming to every contour of the equipment to protect it from transit damage. Pulling this aside, I found the deluxe power supply neatly bagged in a heavy transparent plas-

tic envelope. "What a good-looking unit," I thought as I set it on the operating desk. "Ooh, what a pretty radio," said my wife who had been watching the unveiling. "Is that your new rig?"

Next, I opened the larger carton and again found the same secure foam surrounding another plastic-bagged unit. Here was a piece of gear that looked good even before it was unwrapped, and I thought back to all of the earlier Ten-Tec equipment I had seen come from the box: my first PM-1, then the PM-2, the Argonaut, the Century 21, the Models 540 and 544, and the Omni series. All were innovative and unusual, presenting new ideas and approaches in performance and styling for solving age-old problems. It is no wonder then that I keenly anticipated the setup and operation of the new Model 560, Corsair.

The Corsair is slightly wider than it is deep, and one's first impression is of crisp, contemporary styling and no-nonsense, rugged construction. A band of darkened glass along the top of the front panel is set off from the rest of the panel by a trim stripe cleverly painted to look like brushed chrome or aluminum, which nicely sets off the bronze-black finish... guaranteed to look attractive on my walnut operating desk.

The six-digit LED frequency display and the meter, next to it on the left. (I'll be behind the glass band, called a "blackout" display because when the rig is off, neither the display nor the meter is visible. When lighted, the display is large and easy to see: five digits in red and the sixth in green, showing 100-Hz steps. The meter is also easy to read and presents four selectable functions.

The speaker/power supply matches the decor of the transceiver, and together they make a handsome pair sitting side-by-side on the desk. Black knobs with bright-metal centers peaceably coexist with aluminum toggle switches for the most frequently used controls, while smaller knobs in a flat black finish serve the set-and-forget functions. A tilt bail under the rig allows the front of the rig to be raised to a comfortable viewing angle. The standard four-in microphone connector and the usual earphone jack immediately above it occupy the lower left corner of the panel.

Dominating the center of the front panel is the tuning dial with its fluted knob and vernier skirt. It is divided into 100 increments, each representing one kHz, to facilitate frequency reset and supplement the LED readout. The accompanying photograph reveals more than a detailed description for the moment, so we will leave that until later. First, let's take a look at the more technical aspects of the rig.

### General Description

The Model 560, Corsair is a medium-powered transceiver employing the latest solid-state technology. As received from the factory, it contains all necessary crystals for operation in the 160-, 80-, 40-, 30-, 20-, 17-, 15-, 12-, and 10-meter bands (full coverage of the latter). Although intended primarily as a fixed station, it may be used mobile or portable because it operates from a 12-14-volt-dc source or from a 115-volt-ac source through an optional external power supply. Broadband circuitry eliminates the need for tune-up, and the normal sideband for the band in use is automatically selected when bandswitching. LED indicators are provided so the operator can tell at a glance which particular functions are in use. Nominal input power is 200 Watts, and full output power at a 100% duty cycle (RTTY and SSTV buffs take note) is available on all modes



The Corsair transceiver from Ten-Tec.

and bands. Further, the Corsair is capable of operating into an infinite SWR without damage to its finals.

Frequency coverage on the various bands includes a generous 40-kHz overrun at the top and bottom edges of each band, whose limits are: 1.8-2.3, 3.5-4.0, 7.0-7.5, 10.0-10.5, 14.0-14.5, 18.0-18.5, 21.0-21.5, 24.0-24.5, and 28-30 MHz. The heart of the frequency-determining circuit is a permeability-tuned oscillator operating in the 5.0-5.5-MHz range. Note that phase-locked-loop circuits were purposely not used in order to provide better receiver performance.

Stability of the vfo (PTO) is less than 15-Hz change per degree F over a 40-degree change from 70-110° F after 30 minutes warm-up, and less than 10-Hz change between 105 and 125 volts ac using the Ten-Tec 18-Amp supply. The tuning is vernier and gives approximately 100 kHz per full revolution of the dial skirt and about 18 kHz for one full revolution of the knob. Readout is direct with +/- 100-Hz accuracy in 0.3"-tall numerals. The last numeral is green while the first five are red.

The transceiver contains one LSI, 20 ICs, 94 transistors, 107 diodes, and six LED readouts on 22 PC assemblies with plug-in cables. Its construction is a rigid steel chassis with dark-painted, textured aluminum panels and a snap-up steel tilt bail. Dimensions are 5 1/4" H x 15" W x 14" D (including the massive heat sink). Weight is 14 pounds. The rig requires 12-14 volts dc for operation, at 850 mA in the receive mode and 18.5 A maximum in the transmit mode.

### Receiver

The receiver is a triple-conversion superhet having a sensitivity of 0.25 microvolts for a 10-dB signal-plus-noise-to-noise ratio on all bands and 0.8 microvolts typical with the rf preamplifier switched off. It is interesting to note that the preamplifier circuit attenuates incoming signals by being switched out of the circuit (giving 10 dB of attenuation) and by inserting 10 dB of resistive attenuation in series with the antenna lead and input, for a total of 20 dB of signal attenuation. The dynamic range is better than 90 dB with a third-order intercept point of +15 dBm. Selectivity is obtained through 12-pole crystal filtering in the IF circuits (consisting of 8-pole and 4-pole filters in series) instead of the more usual 8-pole filters, resulting in a nominal SSB bandwidth of 2.4 kHz and a 1.7:1 shape factor between the 6-dB and 60-dB down points on the selectivity curve. Optional 250-Hz, 500-Hz, and 1.8-kHz filters were installed in the

unit sent for test by 73's staff. If desired, an optional 8-pole filter may be substituted for the standard 4-pole filter (giving 16 poles, cascaded) to provide nearly ideal steep-sided skirts on the selectivity curve and an even better shape factor. A notch filter is also provided for attenuating interfering signals by a minimum of 50 dB and is tunable between 200 Hz and 3.5 kHz, which means that you can notch out annoying heterodynes within the audible range and obtain vastly improved reception. This is particularly useful on SSB, but is very successful on CW as well. A CW "spotting" tone of 750 Hz is also provided for zero-beating a received signal. This is done by tone-matching instead of zero-beating; that is, when the "spot" tone matches the received tone, you are exactly zero-beat with the desired signal. Incidentally, this system is much more accurate than the null, or zero-beat, method, because the latter method could introduce an error of at least 200 Hz since the audio response of the circuits cuts off at about 200 Hz.

IF frequencies are 9 MHz and 6.3 MHz, and the PTO covers 5.0-5.5 MHz. Audio output up to 1 Watt with less than 2% distortion (reference to 8 Ohms) can be selected. Spurious responses are all below the equivalent 10-dB S+N/N ratio except at 1.838 MHz (where the equivalent 15-dB S+N/N ratio applies), at 21.300 MHz (where the equivalent 20 dB S+N/N ratio applies), and at 28.980 MHz, where the "birdie" can be eliminated by tuning to the next higher band segment (29.0-29.5 MHz) and tuning 20 kHz below the lower band edge. Although the birdies are detectable, they were not objectionable in our evaluation and could be heard only under quiet band conditions. There is an adjustable noise blanker whose threshold may be varied by rotating a small knob on the front panel. IF rejection is greater than 60 dB.

The S-meter is factory set to provide an S9 indication at a signal input level to the antenna terminal of 50 microvolts. Each transceiver is supplied with its own performance specifications as measured in the laboratory before shipment. In the case of the one tested by 73, S9 was obtained with an input signal of 47 microvolts at the antenna terminals.

The antenna input is low impedance (nominal 50 Ohms), unbalanced to ground. The dynamic range is given as 90 dB nominal, and the 73 test transceiver was measured in the laboratory before shipment (see box). Offset tuning is provided in two ranges: a low range of +/- 500 Hz and a high range of +/- 4

**Corsair #560-00056**  
as tested by 73

**Sensitivity/RX Performance**

	Sens.	Image	I-F Rej.	Bird or RX Spur
160m	-119 dBm	>90 dB	>90 dB	-
80m	-120 dBm	-67 dB	-77 dB	-
40m	-120 dBm	-64 dB	-75 dB	6.999
30m	-120 dBm	-66 dB	-64 dB	-
20m	-121 dBm	-84 dB	-84 dB	14.0
18m	-121 dBm	>80 dB	>90 dB	18.00, 18.165
15m	-121 dBm	-64 dB	>90 dB	21.000, 21.300, 21.320, 21.365
12m	-109 dBm	-53 dB	>80 dB	-
10A	-121 dBm	-51 dB	>80 dB	-
10D	-122 dBm	-52 dB	>80 dB	28.98

Note: Sensitivity reference point is 10 dB Signal-Plus-Noise/Noise

**S-Meter:**

Threshold - 121 dBm

S-9 = 45 µV

IP<sub>3</sub> = +5 dBm (rf amplifier on) and +15 dBm (rf amplifier off)

**TX: Output Harmonics**

	TX: Output	Harmonics
160m	98 W	-50 dBc 3rd order two-tone: -28 dB
80m	97 W	-45 dBc Carrier -55 dB
40m	95 W	-48 dBc -
30m	97 W	-50 dBc -
20m	95 W	-52 dBc Opp. Sideband > -45 dB
18m	95 W	-45 dBc ALC range: to 30 W
15m	93 W	-55 dBc -
12m	93 W	-52 dBc -
10m	93 W	-65 dBc -

*Measured performance of the Ten-Tec Corsair transceiver tested by 73.*

kHz. This feature is particularly useful for netting (low range) or for DXing where the foreign station listens up or down by several kHz.

**Transmitter**

The transmitter dc power input is 200 Watts maximum at 14 volts dc (CW and SSB) and a 100% duty cycle of up to 20 minutes is permitted without exceeding the temperature limitation as measured on the final amplifier heat sink. Operation in excess of this limitation should only be undertaken by force-cooling the heat sink with a small fan (not supplied). Rf power output is 85-100 Watts typical into a resistive load, and each transmitter is measured on all bands prior to shipment (see box). Output impedance is nominally 50 Ohms, unbalanced to ground, through a UHF-type connector. The microphone input, although nominally high impedance, will accept either Hi-Z or Lo-Z microphones with 5-millivolt output. An optional electret microphone may be obtained from Ten-Tec. Polarizing voltage is available on pin 4 of the connector for microphones such as the electret sent with the unit for 73's evaluation.

T/R switching is by VOX or PTT on SSB and Instant or semi-break-in on CW. The CW sidetone is internally generated, and its pitch and volume (which is independent of the receiver's audio control) may be adjusted to suit the operator by means of two thumbwheel controls inside the rig and reachable through a hole in the bottom of the metal cover near the tilt bail. The CW sidetone operates only in the CW mode.

SSB generation is by means of a four-pole crystal-lattice filter at 9 MHz, using the balanced modulator system of carrier suppression which is typically 60 dB (see box). Unwanted sideband suppression exceeds 45 dB with a 1.5-kHz tone input (see box). Spurious output is better than -45 dB relative to full output of the transmitter.

The panel meter is switchable to read several functions: forward (output) power, collector current (Ic), vswr, and speech

processor level. These functions are selected by a front-panel switch near the meter.

CW offset is 750 Hz, automatically provided, and ALC is front-panel adjustable between 30 and 100 Watts output. An LED indicator flashes at the ALC threshold as drive is increased or as modulation peaks reach a preset level.

**Observations on Use of the Operating Controls and Accessory Features**

OFFSET tuning is similar in function to the receiver incremental tuning offered on most modern transceivers, except that this one has a dual range selectable by a toggle switch on the front panel plus the fact that the receiver, the transmitter, or both at once may be varied by this control through switch selection... particularly useful for net operation and for working DX.

Passband tuning adjusts the position of the second i-f crystal filter in relation to the fixed first i-f filter. When the filter selected by the XTAL switch is wide (2.4 or 1.8 kHz), the PBT control becomes essentially a variable bandwidth control whereby counterclockwise rotation reduces the bandwidth on the low side of the selectivity curve, and clockwise rotation reduces the bandwidth of the high side of the selectivity curve. When the XTAL switch selects a narrow filter (500 or 250 Hz), the PBT control is used in the normal passband tuning sense. The Ten-Tec PBT circuit produces the effect of varying the blo, changing the pitch of signals passing through the narrow filter to separate signals that are very close together. For example, on RTTY, the passband tuning can be adjusted to pass only the 2295- and 2125-Hz tones for superior rejection of adjacent signals.

VOX/QSK depends upon the mode of operation selected (SSB or CW) and the position of a front-panel switch. For example, in the SSB mode, if you select the VOX position, normal VOX operation is achieved and VOX gain, VOX delay, and anti-VOX controls are effective to tailor it

to your own preferred style. If you select the FAST position, you have PTT operation with fast recovery. If you select the SLOW position, you also have PTT operation but with slow recovery from the microphone switch. In the CW mode, however, the VOX is inoperative and T/R switching is accomplished by the break-in keying circuits. In this mode, FAST gives you full break-in keying, while SLOW permits semi-break-in keying.

AGC switching is provided so that the hang time, i.e., receiver recovery time, may be selected to suit the operator. In the OFF position, there is no auto gain control, and I-f gain is controlled by the rf gain control.

Noise blanker level is adjustable and sets the blanking threshold. In the fully counterclockwise position, the blanker is off. Clockwise rotation of the control increases blanker sensitivity, permits fine adjustment, and prevents overloading, ensuring the best possible fidelity of the received signal.

The DRIVE control adjusts both the microphone gain and CW level.

The ALC control sets the threshold level at which automatic level control starts. When rotated fully clockwise, the input power is factory-adjusted for 200 Watts on the least efficient band when the ALC LED indicator just starts to blink. Power can be reduced below this level to approximately 30 Watts by rotating the control fully counterclockwise. A change in the ALC control adjustment requires a change in the DRIVE setting.

You can use either high- or low-impedance earphones with the Ten-Tec Corsair, and the equalizing audio circuit is such that the audio amplifier operates at its best signal-to-noise ratio at all times.

WWV is received at 10 MHz. Set the LED frequency readout at 10.000 with the bandswitch and tuning knob. Set the switch for selectivity at position 3 (2.4 kHz) and zero-beat WWV's carrier. If the LED frequency display does not read exactly 10.0000, you may adjust the timebase oscillator internally to read the exact frequency at zero beat.

The rear panel of the Corsair contains some interesting features that will make operation of the rig and accessories more convenient and will permit great versatility. Before looking at the back-panel features, we should have a look at some interesting front-panel provisions that may at first seem a bit confusing.

The RF-POWER dual-function control contains a push-pull switch which turns the rig on and off (in = on; out = off). Rotation of the control varies the gain by changing the bias to the i-f amplifiers. This is the rf-gain control and on-off switch.

As you might expect, the input level to the audio amplifier of the receiver is controlled by the AF-RF AMP knob, but it also has a push-pull switch connected to the control which activates the rf amplifier of the Corsair. The LED lights when the control is pushed in, telling you that the rf amplifier is operative. When the switch is pulled out, a 10-dB attenuator is switched into the circuit and the 10-dB-gain rf amplifier is disconnected entirely. The effect is a 20-dB reduction in signal applied to the rf mixer stage, which results in improved dynamic range and better sensitivity than would be possible if only an attenuator were used. Superior operation in the QSK or VOX modes can be obtained by temporarily setting the rf control fully clockwise, and then adjusting the setting (while receiving a strong station at about S7 or better) to a level slightly higher than desired. Then reduce the level of that signal by means of the rf control to a comfort-

able level. In this way, only one setting of the AF-RF power control need be made, and agc pumping and intercharacter signal blasting when QRM is present may be avoided when operating CW.

**Rear-Panel Features**

The EXT T/R jack is intended to actuate a high-power linear amplifier and is derived from a set of normally-open contacts on the auxiliary relay located on the control board. When operating CW, a thumb potentiometer located on the control board controls the drop-out delay of the relay, but in SSB, the drop-out delay function is switched out of the circuit. Adjustment should be made to suit the individual station requirements only after external equipment is installed and must be controlled by this relay.

Obviously, the key or keyer plug is inserted in the KEY jack. Keys designed for negative-line keying, i.e., grid-block keying, will not work. The key line is positive and is a high-impedance circuit requiring very little current for actuation.

Two AUX 12 VDC jacks are provided, either of which may be used to power external equipment such as an external vfo or keyer. The jacks are connected to the +12-V-dc line after the protective fuse, which is rated at 20 Amperes.

A nine-pin female connector (ACCESSORIES) is available for interfacing an external vfo. When the vfo is not used, an external jumper must be used and the rig is shipped with the jumper in place.

The LINEAR socket consists of a 12-pin female connector which enables front-panel bandswitching of a linear amplifier or antenna relays. Nine band positions correspond to nine switch terminals, while three additional terminals are intended for a common, a ground, and a T terminal.

AUDIO IN-OUT jacks provide connections to the microphone and speaker for attachment of a phone patch or a RTTY unit. AUDIO OUT may also be used for connecting an external speaker without disabling the internal speaker.

A RECEIVE ANTENNA jack is provided for connection of a receiving antenna to the receiver input at all times by placing the small switch nearby in the receive position. In the transceive position, the receiver input is connected to the antenna socket for normal transceiver operation.

VFO IN-OUT jacks make it possible to switch off the transceiver's internal PTO such as when using an external vfo. The Corsair is shipped with an external U-shaped jumper in these jacks, enabling the internal PTO.

The PTT jack is in parallel with the microphone switch for activating the push-to-talk line and is operable in the SSB mode only. This permits an external switch such as a foot switch to be used for transmit/receive control.

The EXT SPKR jack is for an external station speaker and disables the speaker of the Corsair when an external station speaker is plugged in.

**Operating the Corsair Transceiver**

The bottom line, of course, is how the Corsair operates. Is it smooth and easy? Is it convenient? What are the disadvantages and drawbacks, if any? What is the "feel" of the rig, an indeterminate quality that is very subjective and depends upon the operator... but nevertheless important.

When I first spoke with Dan Tomcik at Ten-Tec about this rig, I stressed the importance of CW in my own operating and allowed as how I expected this Ten-Tec rig to excel in that department. Dan quickly corrected my impression... but he didn't

tell me I was wrong. What he said was, "yes, indeed, Ten-Tec has the reputation of building CW rigs that delight the operator with their QSK features and their rock-solid signals. . . . but Ten-Tec rigs also have fine SSB performance which has often been overlooked." He wanted to make sure that I knew the Corsair was a no-holds-barred, fine SSB and CW rig. Consequently, I was on the lookout for something above average in audio quality on both transmitting and receiving.

Now we can return to the setup in my own shack, and I have to tell a little story at this point. In their effort to send the rig to us as quickly as possible, Ten-Tec omitted the instruction manual (which, by the way, is very complete and clear with good diagrams and descriptions). I used this opportunity as an advantage to see if it would be possible to set up the rig and operate it *without* the manual. Now I realize that this is the time-honored, traditional American way to do things. . . . after all else fails, read the instructions. So here I was in exactly that position, but I reasoned that the rig was designed to operate into an infinite SWR without damage to the transistors and the heat sink looked big enough to cool the Hercules kilowatt, so I wasn't too worried. Therefore, I proceeded with care and carefully connected the proper plugs to their mating receptacles. Each was labeled clearly. Ground strap first, antenna connector, speaker, keyer power supply interconnection (yep, switch was off), and finally, I plugged it into the ac outlet in my shack wall. The moment of truth was about to arrive; switch on and what do you know—signals, loud and clear, coming from the neat compression-loaded speaker!

I first checked the band edges on receive and checked the calibration against WWV. . . . perfect. Then I adjusted the controls for CW reception and checked the filters—very nice! Next, I tried the various other controls, including notch filter, off-set tuning, passband tuning, and the various gain controls. Do you detect a bit of delay here, sort of a putting off of the ultimate test? Well, you're right. The manual was missing, and I didn't want to blow the rig by inadvertently doing a no-no. I needn't have worried.

From previous Ten-Tec rigs I knew that the LOCK position of the control is the tune-up position, so I selected LOCK and slowly advanced the DRIVE control with the meter reading FWD, or forward power. The needle obediently came up and my antenna seemed to be taking the load nicely. As received from the factory, the ALC control had been set fully clockwise. Not realizing that this was the normal full-output position, I backed it off to minimum, or maximum counterclockwise position, wondering why I could not obtain full-rated output (and input). By bringing the ALC up slowly, I found the reason that it had been set fully clockwise in the first place. It provides a limited variable adjustment of output power.

From that point on, contacts were quick and simple. Everyone commented on the keying quality and the solid signals, and I particularly enjoyed full QSK, in spite of some QRM close to the frequency. By appropriate adjustment of the rf gain, I was able to minimize its effect, and a tweak of the NOTCH and PBT knobs solved the problem. Many contacts later I decided that the Corsair was some nice rig. I had used it on 160, 80, 40, 30, 20, 15, and 10 meters. . . . all with good signal strength and quality reports.

"But what about SSB," you ask? Wait a minute: I am coming to that! I hadn't requested a microphone with the rig so one wasn't sent. A stupid oversight on my

part, so I scrounged around the shack and workshop for a mike that would work. Ah! Found one. Oh, oh. . . . no four-pin connector anywhere. SSB would have to wait until another day.

For the next three days (and nights), I burned up the bands with this Corsair, getting to know it better and better. I found the more I used it, the better I liked it.

Finally, the manual and microphone arrived, and I was relieved to see that I had done everything right according to the book. In fact, I guess I had been a bit conservative. Now to check it out on SSB.

Evening operation with a vertical antenna on 40-meter SSB is not conducive to your average quiet QSO. The band was alive with foreign broadcasts, but I managed one or two QSOs using the processor to keep average voice power up. Incidentally, if you use the processor according to the manual, you will get very complimentary reports! I got some unsolicited praise for "excellent and natural voice quality," "lots of punch," "nice, narrow signal," "didn't know you were using a processor," and the like.

Next, I ran some DX on 15 meters with essentially the same reports. Much praise and no objections of any kind. Well, why not try it on 20? Isn't that the ultimate test for low power and modest antennas? So, I did. . . . and results were the same. "Your audio is smooth," "Broadcast quality," "unusual for a sideband rig," etc. I got the same kind of reports on 160: "Mellow. . . nice, easy listening."

What more can be said? I like the Corsair and, for once, I felt completely comfortable (well. . . almost) on SSB; for me, that's quite an admission. Naturally, I expected to be happy with CW, and I was. The reports have been uniformly complimentary, and just this evening I worked a Colorado station on 15 meters who told me (in an *unsolicited* report, mind you) that he had looked at the keying waveform on his scope and it was *perfect*!

Here's another thing, too, that may be of importance to you: The Corsair is roomy inside. Things are well laid out and spaced for service. You don't feel crowded, and you have the confidence in your own ability to remove and replace a PC board, for example, if it is ever needed. Here is another Ten-Tec plus: SERVICE. That is intentionally capitalized, too. I had a problem with a Century 21 a few years ago and called Ten-Tec's service department. They helped me troubleshoot the cause over the phone, asked me to mail the board with its defective component back to them, and put a new board in the mail on the day of my call! You can't beat that—anywhere. With Ten-Tec you have a feeling that you would *like* to do your own servicing, and that's a new feeling for most of us with other rigs. Sure, they could have made it smaller, but why should they? This way, it's very neat and open and still of a reasonable size for desk or den. The rig is fully warranted for one year, and the transistor finals are warranted for five years on a *pro rata* basis!

Okay, you've heard the favorable impressions. What about the *bad* things, you ask? Well, there are a couple of things that aren't bad, but could be improved upon. . . . and probably will be. They aren't serious, and might not even bother someone else—you, for example. But for the record, here they are.

There is no frequency memory. That is, there is no extra on-board selectable frequency that can be stored until needed. Frankly, I admit being lazy and have become used to some of the newer rigs with their keypad memory entry and recovery. I also missed the dual on-board vfo's provided by some of the rigs. This is conven-

ient, and although not a requirement, sure is handy. Ten-Tec provides an optional external vfo for connection to the Corsair, and up until a few years ago, that would have been the epitome of luxury. Today, it's okay, but not state-of-the-art. Nevertheless, the DX operator will want his external vfo for split-band operation.

Next, I do a fair amount of shortwave listening and really appreciate general coverage in a receiver. It's true that this is a communications transceiver and is not intended to have all the bells and whistles, but when you have a basic rig this good, you'd like to have it cover some of the SWL bands, too. I also missed having an AM reception position on the mode switch. Frankly, I don't give a hoot for transmitting AM anymore, but I do like to listen to BBC or Deutsche Welle occasionally without having to zero-beat their carriers to recover audio. Nit-picking, sure; I know.

Finally and most bothersome to me was an essential feature that did not meet my expectations: the tuning vernier. It felt rubbery and I think it has a teeny bit of backlash. It left me with the impression that it might creep after being set on a frequency. It turns a tad easier clockwise than it does counterclockwise, so I checked with the boys at Ten-Tec and they tell me this is easily corrected by a dial adjustment. . . . it's purely mechanical and the function of alignment during assembly. Great! I'm happy to hear that this isn't the way all Corsairs behave. Yours will probably be perfect in this respect. The only reason I noticed it is that some of the contemporary rigs have such silky-smooth tuning that one quickly comes to expect it in all rigs. In possible defense of dial friction is the undeniable fact that it isn't as easily knocked off frequency or inadvertently shifted. However, a dial lock is the solution to that problem.

In summary, while the Corsair lacks a few bells and whistles, it sure has *performance aplenty*.

The suggested retail price at \$1169 is ballpark for a rig that has all these good points; the external power supply is available at \$199 for the deluxe model with a front-radiating speaker and \$169 for the utility supply without speaker. If you want more than the nominal 2.4-kHz selectivity, you will have to specify extra crystal filters when ordering your Corsair. These are available for 1.8 kHz (SSB) and 500 and 250 Hz (CW and RTTY). They all fit into the rig and can be selected when needed. This is an improvement over some of the newer rigs where you have to choose only one of the three for use in addition to the standard one supplied. Many hams don't need and wouldn't want the narrow filters anyway, so it's logical to offer them as options.

All in all, I like the Corsair and would probably be happy with it in my shack as an only transceiver. When it comes to sheer operating ability, the Corsair will probably hold its own against anything available today. It's rugged, honest, easy to use, and nice to look at. . . . besides which it sounds great on the air. Its sensitivity, selectivity, dynamic range, and resistance to front-end overload are superior. . . . and it stays put on the frequency of your choice.

Whether or not the Corsair is your cup of tea depends on what you rate as desirable features and what you like in a rig. . . . but after all, that's what makes horse races and amateur radio fascinating.

For more information, contact Ten-Tec, Inc., Sevierville TN 37862.

Jim Gray W1XU  
73 Staff

## DOVETRON'S WIDGET

In this era of expensive, state-of-the-art rigs and microprocessor-controlled transceivers, there is still room for useful gadgets. Dovertron has recognized this largely unsatisfied need with the introduction of a new, simple gadget, appropriately named the Widget.

The Widget is designed to alleviate one problem which has accompanied the increasing miniaturization of 2-meter transceivers—that of low-quality audio reproduction. When so much is compressed into a small space, there is little room left for the speaker, and it is usually placed in a position better suited for the heater fan to hear than the driver. However, with the Widget, you can listen to your 2-meter radio through the in-dash AM radio and benefit from the higher fidelity as well as the larger speaker size and better placement.

The Widget takes the receive audio output of your transceiver and retransmits it at the low end of the broadcast band. You then tune your radio to the appropriate frequency and capture the low-power signal.

Connection of the Widget is simple—you just plug it into the external speaker jack of your mobile rig and unwind the enclosed wire antenna to ensure good pickup. The cable included with the Widget has a sub-miniature plug on one end, which is standard for most mobile radios. The antenna is not always necessary, and it can be unplugged from the back of the device. I found that with my mobile installation, the transceiver and the radio were close enough that I did not need the antenna. No power connection is necessary; the Widget rectifies part of the incoming audio to power the circuit.

The circuit is housed in a small (about 2 by 1 by 1/2 inches) sturdy black box with an LED on one end. The LED signifies that the Widget is receiving a signal and indicates the relative signal level. The box is made of high-temperature plastic designed for year-round exposure in an automobile, and the PC board is made of epoxy-glass FR4. It includes an audio high-pass filter to limit the bass characteristics; the tone may also be controlled by the AM radio.

But why let the uses of the Widget stop with that? The circuitry can be powered by miniscule audio output, so use with a handie-talkie is feasible. If your handie-talkie also doubles as a mobile rig, the Widget will make marginal contacts much easier.

With the antenna fully extended, I found that the Widget has a range of 40 or 50 feet, which gives it some usefulness around the home. You could hook it up to the HF rig and use a cheap portable radio to monitor the frequency, or connect it to the television set for remote listening. By hooking up the Widget to a high-fidelity AM receiver, it could also be used to improve the audio quality of small tape recorders or other portable radios.


Unfortunately, the Widget is crystal-controlled, which gives it good stability but prevents the transmitter frequency from being moved to avoid interference from the commercial broadcast stations. I encountered this problem in the Boston area, where there is a station located near 530 kHz. This is the Widget's transmit frequency. Although the station was not directly on 530 kHz, my radio, like many other car radios, lacked the selectivity to reject the nearby station. Thus, the relatively low signal of the Widget was overrun by the station, making it unusable on that frequency.

However, the second and third harmonics, at 1060 and 1590 kHz, respectively, are also available at a slightly lower power level. In my case, the signal was strong enough to use one of the harmonics.

According to the specifications, the unit has a life expectancy of about 10 years. In addition, the nature of the Widget prevents it from becoming outdated—unlike a transceiver, small gadgets do not have to be state of the art. It comes with a 30-day warranty and may be repaired for a nominal fee within 90 days.

For further information, contact *Dove-tron*, Box 267, South Pasadena CA 91030; (213) 682-3705. Reader Service number 488.

Avery L. Jenkins WB8JLG  
73 Staff

 

### RTTY CALLBOOKS

For anyone interested in RTTY, here are two books which are indispensable—*The World Wide Radioteletype Call Sign List* and *World Wide Radioteletype Stations in Frequency Order*. These books provide a vast amount of RTTY information in a minimum of space, and they have been de-

signed for easy access and cross-referencing.

The RTTY station frequency list has 2,198 listings, a number which is continuously growing, according to the book's publisher Thomas Harrington WB8MV. Harrington collects his information from a variety of sources, including the ITU, the RTTY services themselves, and two dozen listeners he has stationed worldwide.

The book lists stations from 3 to 30 MHz in ascending frequency order. In addition to the frequency and callsign of the station, Harrington has included the station's location, the service it represents (if known), and any other information he has been able to collect. If the baud rate differs from the standard 50 baud, the different rate is noted.

The type of traffic each station handles is also noted. This will range from test slips such as "ry" or "the quick brown fox jumps over the lazy dog" to military traffic and weather bulletins.

Harmonic emissions of identified stations are listed as such, and their fundamental frequencies are also given. Harrington has included unofficial stations, those with callsigns not approved by the ITU, and other apparently underground transmissions. With each of these listings, the date a transmission from the station was last heard is given, as well as any other information obtained.

The language each station is transmitting is also identified, including Serbo-Croatian. Similarly, stations transmitting in the Cyrillic alphabet or third-shift Cyrillic alphabet are also identified.

The back of the book contains a list of press service frequencies by country, service, and frequency. Another appendix lists stations transmitting meteorological data, and a third gives utility stations abbreviations and mnemonics.

The callsign list, although smaller than the frequency list, contains about 4,000 entries. In addition to the callsign, each entry includes the location and service of the station. Appendices offer further information, from a partial reproduction of ITU rules relating to station identification to a list of service and country abbreviations.

Not only does this book cover RTTY stations, but also it includes CW, weather, and satellite stations as well.

The callsign book provides a useful adjunct to the frequency list, in addition to carrying information not contained in the other book. It is especially useful because stations do not always remain on their posted frequencies, and the call letter book provides a rapid means of identifying them.

To facilitate merging these lists with additional information garnered by the user, neither book has been bound. Both lists are held together with staples, so the pages may be easily separated and placed into a loose-leaf binder or other notebook.

The amount of information contained in these books, as well as the amount of information transfer which they represent, is nothing short of fantastic. I did not realize until I began to peruse the lists how much information is accessible to the ham or SWL equipped with RTTY and a general-coverage receiver.

Imagine listening to weather bulletins from Kuwait, or military messages from El Salvadoran forces. Although the transmissions may be encoded or otherwise untranslatable, the material is available for your study.

The press frequencies listed would also appear to be an extremely valuable tool. A vast amount of filtering occurs in the world's newsgathering forces as the day's events are distilled into a half-hour newscast or a few columns of print. By tuning in the press frequencies, you can catch much of the news before it has become victim to the filtering process.

You need not worry about the information becoming very far out of date, either. Harrington updates his material three times a year in supplements to the main list. All of the entries have been positively verified before they can be listed in the books. Harrington's stringent requirements include verification of the station's existence by the station itself, by the ITU, or by three reports of the station from different sources or at different times.

My surprise upon seeing these lists may be likened to the feeling I had when I turned on a ham-band radio for the first time. There's a whole new world out there waiting to be explored, and these books are the key to it.

For further information, contact *Universal Electronics, Inc.*, 1280 Aida Drive, Reynoldsburg OH 43068; (614) 866-4605. Reader Service number 484.

Avery L. Jenkins WB8JLG  
73 Staff

# AWARDS

Bill Gosney KE7C  
Micro-80, Inc.  
2665 North Busby Road  
Oak Harbor WA 98277

### THE ELECTRIC CITY CHAPTER OF 10-X INTERNATIONAL

Electric City is the nickname given to Schenectady, New York, because of the numerous electrical developments generated by the Edison General Electric Company, now the General Electric Company (GE). GE was founded in 1882 by the merger of the Edison General Electric Company and the Thomas Houston Company.

The design of this award certificate is based on three of the most famous people

associated with the Electric City. As you have probably already recognized, Thomas A. Edison is the top picture and Charles P. Steinmetz is the bottom picture. The center picture is of Ernst F. W. Alexanderson, who is responsible for the design of the Fessenden alternator used at Brant Rock, Massachusetts.

To go back a little, Reginald Fessenden (physicist, inventor, and radio pioneer) of the National Electric Signaling Company believed in the possibility of developing smooth and continuous flow of high-frequency vibrations, which, at the time, was impossible with the intermittent spark-gap system then in use. He envisioned the idea of superimposing the human voice on the continuous flow of high-frequency vibrations in much the same manner as

Alexander G. Bell had done on the direct current with the telephone. How to produce the high-frequency-vibration flow was the great problem. Believing that a generator might be built with this capability and being familiar with the high-frequency dynamo built by Elihu Thomson of GE, he contacted GE. In 1903 Steinmetz built a 10,000-Hertz alternator for Fessenden. The output of this alternator was a whopping 1000 Watts.

In 1904 Fessenden ordered an alternator capable of 100,000 Hertz. The order was assigned to a brilliant young engineer at GE—Ernst Alexanderson. The machine was completed and tested at 50,000 Hertz in the summer of 1906 and was delivered to Fessenden at Brant Rock. Its first demonstration deserves to go down in history as one of the great events in scientific annals. The demonstration, performed on Christmas Eve, 1906, is described as follows: Early in the evening, wireless operators on ships within a radius of several hundred miles sprang to attention as they caught the call "CQ CQ" in Morse code. Was it a ship in distress? They listened eagerly and, to their amazement, heard a human voice coming from their equipment—someone was speaking! Then, they heard a woman's voice in song. It was uncanny! Many of the operators called their officers to come and listen. Soon, the wireless rooms were crowded. Next, someone was heard reading a poem, then there was a violin solo. Then, a man made a speech, and they could understand most of the words. Finally, everyone who had heard the broadcast was asked to write to R. A. Fessenden at Brant Rock. This was how the first voice radio broadcast in history was transmitted.

Now you can understand why the Electric City chapter of 10-X International chose for their center picture a man whose picture is probably not recognized, but whose achievements in voice communications made possible the hobby and the way of life we now all enjoy.

To obtain the distinguished Electric City award, stations must accumulate a total of 50 points as well as work a minimum of three 10-X International chapters. Five points are scored for CH plus CM. C equals four points, HC plus L is three points, FS plus DX is two points, and all others are one point.

Forward a list of your contacts and be sure to include the 10-10 number for each station worked. Enclose \$1.00 plus two US first-class stamps; DX stations enclose \$2.00 in US funds.

For further information about this awards program or to submit an award application, address your correspondence to: Ivan Stillwell WA2OIZ, 18 Englehart Drive, Scotia NY 12302

### TWO-LETTER CALL WAS

Representing the Heart of America Radio Club, Inc., out of Kansas City, Missouri, comes this Worked All States award announcement from our good friend, A. Hoogenraad WB0RAF.


To qualify for the Two-Letter Call Worked All States award, the applicant must work one two-letter callsign in each of the fifty US states. Two-letter calls would be, for example, W0RR, AK0A, KB0VL, etc. In short, any call with two or less characters in the suffix qualifies as a good contact.

To apply for this award, prepare a list of contacts in alphabetical order by state, giving the callsign, date worked, band, mode, and state. Have your list of contacts verified by two amateurs or any club secretary. Send a \$2.00 (US funds only) award fee to: Adrianus Hoogenraad, 7204 E 28th Street, Kansas MO 64129.

### WORKED LAEN P AWARD

The Borås Amateur Radio Society of Sweden is proud to announce the Worked All Laen P award. This award is available to licensed amateurs and SWL stations worldwide.

To be valid, all contacts must be made

 

on or after January 1, 1980. Applicants may utilize any band or mode; however, repeater contacts such as those made on 10-meter FM are invalid.

Scandinavian countries must work and confirm 25 different stations in Laen P Sweden. Other Europeans must work 15 different stations, while stations outside the European continent must work a minimum of five different stations in Laen P Sweden.

GCR applies. Forward your verified list of contacts to: Lars Lind SM6NT, Eskesund S-520 11, Vegby, Sweden. Enclose \$2.00 (US) or ten IRCs.

### THE DX LONG CHAT HAM

This award is sponsored by the Long Chat Ham Club in celebration of its sensational start. All the club members prefer a long QSO with DX stations rather than a short contact. The DX-LCHA is issued for confirming contacts with five foreign ham stations for more than fifteen minutes each.

For the award, send your application, GCR, or log, certified by a local radio club or two other amateurs, with four IRCs to: Award Manager Aki Kogure JG1UNE, Charne #303, 5-37-5 Denenchofu, Ohtaku, Tokyo 145, Japan. Be sure your application clearly indicates the beginning and ending time of each contact made.

### ISLE OF EIGHT FLAGS AWARD

Representing the only location in the United States governed under eight flags, Vance LePierre W5IJU writes to share with us the Isle of Eight Flags award. As they appear on the certificate, they include France (1562-1597), Spain (1597-1735, 1748-1763, and 1783-1821), Great Britain (1736-1748 and 1763-1783), the Patriot's Flag of 1812, the Green Cross of Florida (1817), Mexico (1817), the Confederate Flag (1861-1862), and the US Flag (1821).

To qualify, the applicant must work any two stations on Amelea Island Florida on or after January 1, 1975. You may use any band or mode. Submit log data and \$2.00 or eight IRCs to: Vance LePierre, 2618 McGregor Blvd., Fernandina Beach FL 32034.

### JUMBUNNA AWARD

Chris Levingston VK3AOR, from Kilsyth, Australia, writes to tell us about an award dedicated to the Australian Novice.

The award requires the applicant to work and confirm a minimum of 15 VK3 Novice stations. Prepare a list of qualifying contacts in order by their callsign, giving the date, time, band, and mode of communications. Have this list verified by at least two amateurs or a radio club official. The cost of this award is \$3.00 or 12 IRCs. Send your application to: Chris Levingston VK3AOR, 2 Acacia Avenue, Kilsyth, Victoria, Australia 3137.

By the way, VK Novice stations are identified by the suffix N, V, P, or K. The K suffix denotes a combined Novice and limited license holder. These stations are permitted CW on 3.525-3.625 MHz, 21.125-21.200 MHz, and 28.100-28.600 MHz. They are limited to ten Watts dc of power. On SSB, Australian Novices may operate thirty Watts PEP on 3.500-3.625 MHz, 21.150-21.100 MHz, and 28.300-28.600 MHz.

### THE BEST LITTLE DXPEDITION IN TEXAS

Chartered under the laws of amateur radio camaraderie and brotherhood, the Texas Independent Telegraphers Society is proud to announce the Best Little DXpedition in Texas on the weekend of March 12-13, 1983. Members and friends of the society will be operating from LaGrange, Texas, the location of the famous Chicken Ranch.

For those hams who need a peck of Texas history, the Chicken Ranch represents the oldest institution in Texas. It became

a part of Texas folklore when it was exploited by a Houston newscaster who projected it into the living rooms and political backrooms of Texas. It became nationally famous when used as the setting for a Broadway musical and a Hollywood movie.

Now, radio amateurs of the world will have an opportunity to work the home of the Chicken Ranch. Using the callsign, W5VD (very distinctive), the station will operate from 1200Z March 12th until 1800Z March 13th. Depending on the band conditions and the time of day, prime frequencies will be 7.280, 14.280, and 21.380 MHz. CW frequencies will be 7.100, 14.050, and 21.100 MHz with period excursions into the Novice band. Special certificates and QSL cards will be available to those who work the Chicken Ranch special-event station. QSL to W5VD, PO Box 3225,

Bryan TX 77801. Hope to pluck you from the pileup.

### SOUTHWIRE COMPANY

The Southwire Employees Amateur Radio Society (SWEARS), based in Carrollton, Georgia, announces that the second annual SWEARS anniversary special-event station will be activated on March 26, 1983, to honor the 33rd anniversary of the parent company's (Southwire Co.) first production of wire. Specially-designed QSL cards will be awarded.

Plans call for operation on 14.270 ( $\pm 10$  kHz), 21.345 MHz ( $\pm 10$  kHz), and 28.600 ( $\pm 10$  kHz). Novices should check the first 10 kHz of the 15- and 10-meter bands. Operation will likely not be continuous on all bands, so check all frequencies. For further information, contact: Terry Martin WD4AON at (404)-832-5375.



### ELMER OF THE YEAR

Francis C. Leonard W2NPT was chosen as QCWA's Northern New Jersey Chapter's "Elmer of the Year" by a committee which included such prominent local amateurs as George Diehl W2IHA, newly elected director of the Hudson Division of the AARL, Curtis Williams W5DTR12, section communications manager of the Northern New Jersey Section, and Joseph Painter W2BHM, head of the W2 QSL Bureau.

W2NPT, a founder and past president of the Fairlawn, New Jersey, Radio Club, has devoted most of his time for the past 20 years to helping new and would-be hams—old and young, boys and girls—obtain their tickets and get on the air. His basement ham shack continues to be a haven for hatching new ham ops.

## HAM HELP

I need the service manual and schematic for a Hammarlund HQ-145 and a Galaxy V transceiver. I would prefer the original, but a copy is OK.

Henry Galbraith W9RDJ  
1214 S. Alvord Blvd.  
Evansville IN 47714

Issue of 73. Any assistance would be greatly appreciated.

William Eyer, Jr.  
454 Kent Ave.  
Catonsville MD 21228

I would like to purchase a copy of the CQ Surplus Conversion Manual and the manual for a Hammarlund HQ-110A receiver.

Richard McCubbin WD8RQH  
Box 65  
Mulliken MI 48861-0065

I am looking for RTTY software to use in conjunction with my TRS-80 model I and the Micro Modem, which I built from plans which appeared in the September, 1982,

**The Best Little DXpedition  
In Texas**

"The Chicken Ranch"

**March 12-13, 1983**

PLUCKED FROM THE PILEUP, AMATEUR RADIO OPERATOR was caught in the Act of socializing with the folks at the "Chicken Ranch". This award is presented as testimony to one of the quickest encounters in the hundred year history of the brothel, the entire affair lasting on the order of one minute!

CONGRATULATIONS!

One of Texas' oldest institutions, the "Chicken Ranch" at LaGrange achieved national prominence through a media showdown that led to its closing. Broadway and Hollywood came to the rescue of the colorful history of the "boarding house", so the Chicken Ranch continues to entertain folks coast-to-coast.

Your contact with W5VD adds your name to the guest list of the Ranch. We enjoyed having you drop in. Ya'll come again!


A special events station of the Texas Independent Telegraphers Society



# RADIO BOOKSHOP
 
## FOR THE NOVICE

New, updated editions  
of our famous novice  
license study guide and novice study tapes.



73

**Code Tapes**  
any four tapes for  
**\$15.95! \$4.95 each**

● **NOVICE LICENSE STUDY GUIDE**—by Timothy M. Daniel N8RK. Here is the most up to date novice guide available. It is complete with information about learning Morse Code, has the latest FCC amateur regulations and the current FCC application forms. This guide is not a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price. SG7357 \$4.95.\*

● **NOVICE STUDY TAPES**—If you are just getting started in ham radio, you'll find these tapes indispensable! This up-to-the-minute revision of the 73 Study Course is the perfect way to learn everything you need to breeze through the Novice written exam. Theory, FCC regulations, and operating skills are all covered, and you'll be amazed at how fast you learn using these tapes!

Once the test is behind you, these tapes will go right on being useful, because they are packed with the latest information on setting up your own ham station, and getting on the air.

Thousands of people have discovered how easy learning from cassette can be—order now and enter the fascinating world of ham radio! CT7300 Set of 3—\$15.95.\*

Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time—even while you're driving! You get more and more info each time you hear it. You can't progress without solid fundamentals. These three hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to these tapes?

**Special Offer! Both Novice License Study Guide and Novice Study Tapes \$19.95 Order NP7300.**

### "GENESIS"

**5 WPM**—CT7305—This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people—including kids of ten—are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

### "THE STICKLER"

**6+ WPM**—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly—under pressure—faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.

### "BACK BREAKER"

**13+ WPM**—CT7313—Code groups again, at a brisk 14 per so you will be at ease when you sit down in front of the steely-eyed government Inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heaven you had this back-breaking tape.


### "COURAGEOUS"

**20+ WPM**—CT7320—Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape.

### "OUTRAGEOUS"

**25+ WPM**—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered it. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."

## GENERAL LICENSE STUDY GUIDE

 

**GENERAL LICENSE STUDY GUIDE**—By Timothy M. Daniel N8RK This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-and-answer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world. SG7358 \$6.95



Style W



Style Y



Style X

● **QSL CARDS**—73 turns out a fantastic series of QSL cards at about half the cost of having them done elsewhere because they are run as a fill-in between printing books and other items in the 73 Print Shop. 250 Style W—QW0250—for \$8.95\*; 500 Style W—QW0500—for \$13.95\*; 250 Style X—QX0250—for \$8.95\*; 500 Style X—QX0500; 250 Style Y—QY0250—for \$8.95\*; 500 Style Y—QY0500—for \$13.95\*. Allow 6-12 wks. for delivery.

**LIBRARY SHELF BOXES**—These sturdy white corrugated, dirt boxes each hold a full year of 73, Microcomputing or 80 Micro. With your order, request self-sticking labels for any of the following: 73, Microcomputing, 80 Micro, CQ, QST, Ham Radio Personal Computing, Radio Electronics, Interface Age, and Byte. Order 1—BX1000—for \$2.00\*; order 2-7—BX2002—for \$1.50 each\*; order 8 or more—BX1002—for \$1.25 each\*.

## For Your Ham Shack 73 Magazine Binders

● Preserve and protect your collection for a lifetime! Order these handsome red binders with gold lettering. \$7.50 for 1, 3 for \$21.75, 6 for \$42.00. (Postpaid within USA, please add \$2.50 per order outside USA.) Check or money orders only, no phone or C.O.D. orders. 73 Binders, P.O. Box 5120, Philadelphia, PA 19141.

\*NOTE—Above address for Binders only.

**BACK ISSUES**—Complete your collection; many are prime collectables now, classics in the field! A full collection is an invaluable compendium of radio and electronics knowledge!

73300	73 BACK ISSUE—BEFORE JULY 1980	\$ 3.00
73350	73 BACK ISSUE JULY 1980 THRU OCT. 1981	\$ 3.50
73350P	73 BACK ISSUE NOV. 1981 TO PRESENT	\$ 3.50
73005	73 BACK ISSUE—5 YOUR CHOICE	\$10.75
73010	73 BACK ISSUE—10 YOUR CHOICE	\$16.00
73025	73 BACK ISSUE—25 YOUR CHOICE	\$27.00
73125	73 BACK ISSUE—25 OUR CHOICE	\$14.00

Shipping: Please add \$1.00 per magazine. Orders of ten magazines or twenty-five magazines add \$7.50 per order.

\*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

**FOR TOLL FREE ORDERING CALL 1-800-258-5473**

# RADIO BOOKSHOP

## HAND BOOKS FOR NEW! THE HAMSHACK

**AMATEUR RADIO CALL DIRECTORY, 1982-1983 Edition.** Compiled by: Jack A. Speer N1BIC and Ashok K. Anand. Here it is, and at a price you can afford! A directory of over 410,000 radio amateurs in the United States (as licensed by the U.S. Gov't). Completely updated for 1983. Easy to handle 8 1/2 x 11 format. BK1254 \$12.95

**THE TEN METER FM HANDBOOK**—by Bob Hell K9EID. This handbook has been published to help the ten meter enthusiast learn more about the many methods of conversions and tricks that are used to make existing units work better. Join the great "tinkerers" of the world on ten FM and enjoy the fantastic amount of fun in communicating with amateur stations worldwide on ten meter FM. BK1190 \$4.95.\*

**THE COMPLETE SHORTWAVE LISTENER'S HANDBOOK, 2nd EDITION** by Hank Bennett and Harry L. Helms. This comprehensive volume contains loads of new information from all over the world on the latest developments in SWL technology clubs, associations, practices and stations. A thorough guide to stations of the world by general continental area and frequency is included. BK1241 \$9.95

**THE PRACTICAL HANDBOOK OF AMATEUR RADIO FM REPEATERS**—by Bill Pasternak WA6ITF (author of 73 Magazine's monthly column "Looking West") This is the book for the VHF/UHF FMer, compiled from material submitted by over a hundred individuals, clubs, organizations and equipment manufacturers. A "must have" for your ham shack shelf. BK1185 \$12.95.\*



**TOOLS & TECHNIQUES FOR ELECTRONICS**—by A. A. Wicks is an easy-to-understand book written for the beginning kit-builder as well as the experienced hobbyist. It has numerous pictures and descriptions of the safe and correct ways to use basic and specialized tools for electronic projects, as well as specialized metal-working tools and the chemical aids which are used in repair shops. BK7348 \$8.95.\*

**BEHIND THE DIAL**—This book explains, in detail, what's going on on all the frequencies, from shortwave up to microwave. It gives the reader a good idea of what he can find and where to find it, including some of the secret stations such as the C.I.A. and the F.B.I. Everything is covered short of microwave monitoring. Anyone interested in purchasing a shortwave receiver should have a copy of this book, surveillance, station layout consideration, antenna systems, interface, and the electromagnetic spectrum, are included. BK7307 \$4.95

**THE NEW WEATHER SATELLITE HANDBOOK**—by Dr. Ralph E. Taggart WB8DQT. Here is the completely updated and revised edition containing all the information on the most sophisticated and effective spacecraft now in orbit. This book serves both the experienced amateur satellite enthusiast and the newcomer. It is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Solid hardware designs and all the instructions necessary to operate the equipment are included. For experimenters who are operating stations, the book details all procedures necessary to modify equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment. BK7383 \$8.95.\*

\*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

## THE 73 TEST EQUIPMENT LIBRARY

**VOL. II AUDIO FREQUENCY TESTERS**—Jam-packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you... a good book for hi-fi addicts and experimenters, too! LB7360 \$1.95.\*

**VOL. III RADIO FREQUENCY TESTERS**—Radio frequency waves, the common denominator of amateur radio. Such items as SWR, antenna impedance, line impedance, RF output, and field strength; detailed instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads, and much more. LB7361 \$1.95.\*

**VOL. IV IC TEST EQUIPMENT**—Become a troubleshooting wizard! Here are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes for the 73 TEST EQUIPMENT LIBRARY. LB7362 \$1.95.\*

**ALL THREE OF THE ABOVE ONLY \$4.95 ORDER LB7365**

**RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD**—BK1044—Rf burst, function, square wave generators, variable length pulse generators—100 kHz marker, i-f and rf sweep generators, audio osc, a/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. BK1044 \$5.95.\*

## THE 73 TECHNICAL LIBRARY



### INTERFERENCE HANDBOOK

How to locate and cure RFI  
Amateur Radio, CB Radio, Power Line RFI  
TV & Hi-Fi Interference  
The World of Antenna Interference




**THE CHALLENGE OF 160**—The growth of amateur radio today is encouraging the use of 160 meters. All the information necessary to get started on this unique band, the all-important antenna and ground systems are described in detail. Also, how to get on, top-band operating tips, top-band transmitters, propagation, weather receiving equipment, and more are covered in full. The introduction contains interesting photos of Stew Perry's (the King of 160) shack. This reference is useful to new and experienced top-band operators. BK7309 \$4.95

**INTERFERENCE HANDBOOK**—by William R. Nelson, WA6EQG—This timely handbook covers every type of RFI problem and gives you the solutions based on practical experience. Covers interference to TV, radio, hi-fi, telephone, radio amateur, commercial and CB equipment. Power line interference is covered in depth—how to locate it, cure it, work with the public, safety precautions, how to train RFI investigators. Written by an RFI expert with 33 years of experience, this profusely illustrated book is packed with practical easy-to-understand information. BK1230 \$8.95.\*

**OWNER REPAIR OF RADIO EQUIPMENT**—by Frank Glass K6RO. Here's a book that will teach you an approach to troubleshooting without a shack full of test equipment. Written in a narrative, non-mathematical style, it will encourage you to successfully fix your own rig problems 80 to 90% of the time. Even if you don't want to fix, you can learn a lot about how things work and fail. Add to your library and personal expertise. BK7310 \$7.95.\*
 
## FOR THE CONTESTER

**THE CONTEST COOKBOOK**—This book reveals the secrets of that elite group of operators who top the list when the contest results are published. It contains detailed suggestions for the first-time contestee as well as tips for the advanced operator. Domestic, DX, and specialty contests are all discussed, complete with photographs and diagrams showing the equipment and operating aids used by the top scorers. For the serious contestee. BK7308 \$5.95.



NEW

**EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TELEVISION, (but were afraid to ask)**—By Mike Stone WB0QCD. This book is a complete guide to setting up your own amateur radio television station. It contains—A history, what equipment you need, video theory, cameras, recorders, lighting, special effects, sound ATV DXing, mobile FSTV, ATV repeaters, ATV groups, building projects, test equipment, dealer directory, a cumulative index of over 1000 articles on amateur TV and much more. This is the new, 1982 edition. From the publishers of *Amateur Television Magazine*. BK1244 \$9.95

**WORLD PRESS SERVICE FREQUENCIES**—by Thomas Harrington Can't wait to hear the evening news, or are you wondering about the news that you aren't hearing? Receive by Radio Teletype (RTTY) all the world news and financial happenings from the world capitals on a 24 hour a day basis. This book gives you the frequencies and times of broadcast of such news services as AP, UPI, Reuters, TASS, VOA and London Press. Also included is an introduction to RTTY with information on equipment, antennas, abbreviations—everything you need to get started in RTTY. BK1202 \$7.95\*



**SSB... THE MISUNDERSTOOD MODE**—by James B. Wilson. Single Sideband Transmission... thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. BK7351 \$5.50.\*

**PROPAGATION WIZARD'S HANDBOOK**—by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940s, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reliable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. BK7302 \$6.95.\*

FOR TOLL FREE ORDERING CALL 1-800-258-5473

# RADIO BOOKSHOP

## ANTENNA BOOKS

  

**VHF ANTENNA HANDBOOK**—The new *VHF Antenna Handbook* details the theory, design, and construction of hundreds of different VHF and UHF antennas... a practical book written for the average amateur who takes joy in building, not full of complex formulas for the design engineer. Packed with fabulous antenna projects you can build. BK7368 \$5.95.\*

**ALL ABOUT CUBICAL QUAD ANTENNAS (2nd edition)**—The "Classic" on Quad design, theory, construction, and operation. New 2nd edition contains new feed and matching systems and new data. BK1196 \$5.95.\*

**THE RADIO AMATEUR ANTENNA HANDBOOK**—All about wire antennas, beams, tuners, baluns, coax, radials, SWR and towers. Clear and complete information. BK1199 \$6.95

**VHF HANDBOOK FOR RADIO AMATEURS**—Contains information on FM theory, operation and equipment, VHF antenna design and construction, satellite-EME, and the newest solid-state circuit. BK1198 \$6.59\*

**SIMPLE, LOW-COST WIRE ANTENNAS FOR RADIO AMATEURS**—All new data and everything you want to know about low-cost, multi-band antennas, inexpensive beams, "invisible" antennas for hams in "tough" locations. BK1200 \$6.95

**73 DIPOLE AND LONG-WIRE ANTENNAS**—by Edward M. Noll W3FQJ. This is the first collection of virtually every type of wire antenna used by amateurs. Includes dimensions, configurations, and detailed construction data for 73 different antenna types. Appendices describe the construction of noise bridges, line tuners, and data on measuring resonant frequency, velocity factor, and swr. BK1016 \$5.50.\*

**BEAM ANTENNA HANDBOOK (New 5th edition)**—by William I. Orr and Stuart D. Cowan. Yagi beam theory, construction and operation. Information on wire beams, SWR curves and matching systems. A "must" for serious DXers. BK1197 \$5.95.

**HOW TO DEFEND YOURSELF AGAINST RADAR**—by Bruce F. Bogner and James R. Bodnar, a lawyer and radar expert. This book gives you the ammunition to challenge the radar "evidence" that usually leads to a speeding conviction. The major part of the book details the inner workings of radar—you'll become more of an expert than most police officers and judges. The remainder of the book outlines how to defend yourself against a speeding ticket—the observations, measures and testimony you must obtain to defend yourself without the help of a lawyer. The price is a lot less than a fine! BK1201 \$6.95.\*

## MICROCOMPUTER BOOKS

**THE SELECTRIC INTERFACE**—by George Young. You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. **SELECTRIC™ INTERFACE**, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Kilobaud Microcomputing* magazine's popular "Kilobaud Classroom" series, offers a low-cost alternative to buying a daisy wheel printer. **SELECTRIC INTERFACE** includes: step-by-step instructions, tips on purchasing a used Selectric, information on various Selectric models, including the 2740, 2980, and Dura 1041, driver software for Z80, 8080, and 6502 chips, tips on interfacing techniques. With **SELECTRIC INTERFACE** and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included. BK7388 \$12.97

**40 COMPUTER GAMES FROM KILOBAUD MICROCOMPUTING**—Forty games in nine different categories. Games for large and small systems, and a section on calculator games. Many versions of BASIC used and a wide variety of systems represented. A must for the serious computer gamesman. BK7381 \$7.95\*

**KILOBAUD CLASSROOM**—By George Young and Peter Stark. Learning electronics theory without practice isn't easy. And it's no fun to build an electronics project that you can't use. *Kilobaud Classroom* the popular series first published in *Kilobaud Microcomputing*, combines theory with practice. This is a practical course in digital electronics. It starts out with very simple electronics projects, and by the end of the course you'll construct your own working microcomputer! BK7386 \$14.95

**HOBBY COMPUTERS ARE HERE!** If you want to come up to speed on how computers work—hardware and software—this is an excellent book. It starts with fundamentals and explains the circuits and the basics of programming, along with a couple of TVT construction projects, ASCII, Baudot, etc. This book has the highest recommendations as a teaching aid. BK7322 \$2.47.

**TEXTEDIT—A Complete Word Processing System in kit form**—by Irwin Rappaport. **TEXTEDIT** is an inexpensive word processor that you can adapt to suit your needs, from writing form letters to large texts. It is written in modules, so you can load and use only those portions that you need. Included are modules that perform right justification, ASCII upper/lowercase conversion, one-key phrase entering, complete editorial functions, and much more! **TEXTEDIT** is written in TRS-80\* Disk BASIC, and the modules are documented in the author's admirably clear tutorial writing style. Not only does Irwin Rappaport explain how to use **TEXTEDIT**; he also explains programming techniques implemented in the system. **TEXTEDIT** is an inexpensive word processor that helps you learn about BASIC programming. It is written for TRS-80 Models I and III with TRS-DOS 2.2/2.3 and 32K. \*TRS-80 and TRSDOS are trademarks of the Radio Shack Division of Tandy Corporation. BK7387 \$9.97

**SOME OF THE BEST FROM KILOBAUD/MICROCOMPUTING**—A collection of the best articles that have recently appeared in *Kilobaud/MICROCOMPUTING*. Included is material on the TRS-80 and PET systems, CP/M, the 8080/8085/Z80 chips, the ASR-33 terminal. Data base management, word processing, text editors and file structures are covered too. Programming techniques and hardware construction projects for modems, high speed cassette interfaces and TVTs are also included in this large format, 200 plus page edition. BK7311 \$10.95.\*

**THE NEW HOBBY COMPUTERS**—This book takes up from where "HOBBY COMPUTERS ARE HERE!" leaves off, with chapters on Large-Scale Integration, how to choose a microprocessor chip, an introduction to programming, low-cost I/O for a computer, computer arithmetic, checking memory boards... and much, much more! Don't miss this tremendous value! BK7340 Only \$2.47.

\*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

## COOK BOOKS


**TTL COOKBOOK**—by Don Lancaster. Explains what TTL is, how it works, and how to use it. Discusses practical applications, such as a digital counter and display system, events counter, electronic stopwatch, digital voltmeter and a digital tachometer. BK1063 \$9.50.\*

**CMOS COOKBOOK**—by Don Lancaster. Details the application of CMOS, the low power logic family suitable for most applications presently dominated by TTL. Required reading for every serious digital experimenter! BK1011 \$10.50.\*

**TVT COOKBOOK**—by Don Lancaster. Describes the use of a standard television receiver as a microprocessor CRT terminal. Explains and describes character generation, cursor control and interface information in typical, easy-to-understand Lancaster style. BK1064 \$9.95.\*

**IC OP-AMP COOKBOOK**—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, liberally illustrated. 592 pages, 5 1/2 x 8 1/2, softbound. BK1028 \$14.95.\*

## THE WELL EQUIPPED HAM SHACK

 

**WORLD REPEATER ATLAS**—Completely updated, over 230 pages of repeater listings are indexed by location and frequency. More than 50 maps pinpoint 2000 repeater locations throughout the USA. Foreign listings include Europe, the Middle East, South America, and Africa. BK7315 \$2.00

**THE MAGIC OF HAM RADIO**—by Jerrold Swank WB4HXR. Under various call signs, WB4HXR has been heard on the ham bands since 1919. He has watched amateur radio grow from the days of Model A spark coils to an era of microprocessors and satellite communications. Jerry has responded to calls for help from earthquake-stricken Managua and tornado-ravaged Xenia, Antarctica, one of man's loneliest outposts, has been a bit less lonely, thanks to Jerry's tireless phonepatching efforts. Drawing on his own colorful experiences and those of many other hams, Jerry has compiled this work-picture of ham radio during the past six decades. BK7312 \$4.95

**A GUIDE TO HAM RADIO**—by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC license. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. BK7321 \$4.95.\*

**WORLD RADIO TV HANDBOOK 1983, 26TH EDITION**—This book is the bible of international broadcasters, providing the only authoritative source of exact information about broadcasting and TV stations world wide. This 1981 edition is completely revised, giving comprehensive coverage of short, medium and long wave, 560 pages of vital aspects of world listening. BK1184 \$16.50

FOR TOLL FREE ORDERING CALL 1-800-258-5473

# ADVERTISERS

\*Please contact these advertisers directly.  
To receive full information from our advertisers please complete the postage-paid card.

R. S. No.	Page	R. S. No.	Page	R. S. No.	Page	R. S. No.	Page	
2	AEA/Advanced Electronic Applications	48, 85	15	Communications Specialists	67, 82	476	Hamtronics, NY	120
486	AEA/Advanced Electronic Applications	104	222	Computer Applications	85	460	Handi Tek	130
115	A5 ATV Magazine	129	190	Control Products Unlimited	123	303	Heath Co.	75
164	A&W Productions	22	21	Current Development Corp.	45	320	Hoosier Electronics	72
448	Advanced Communications International	81	106	Cushcraft Corp.	13	*	Hustler, Inc.	69
124	Advanced Computer Controls	55	346	Data Service	93	*	ICOM	Cov. II, 35
*	Alaska Microwave Labs	49	*	Dayton Hamvention	56	78	Independent Crystal Supply	129
20	All Electronics	130	312	Daytapro Electronics	14	445	Instant Software	
216	Alden Electronics	21	*	DGM Electronics, Inc.	56	*	Amateur Radio Program	125, 127
*	Amateur Electronic Supply	23, 95	225	Digi Com Engineering, Inc.	48	36	International Crystal	48
5	Amateur-Wholesale Electronics	45, 73	57	Discount Ham Radio	65	*	IRL	71
487	Amateur-Wholesale Electronics	104	425	Doppler Systems	51	39	Jan Crystals	50
169	A. P. Systems	91	479	Dotronix, Inc.	121	209	Jarr Corp.	22
213	API Electronics	40	488	Dovetron	107	*	JK Audio	93
329	AR Technical Products	38	219	E-Tek	129	*	Jun's Electronics	51
*	Associated Radio	57	453	EGE, Inc.	49, 123	*	Kantronics	40
*	Autek Research	89	*	Electronic Equipment Bank	69	*	Kenwood	Cov. IV, 7, 121
*	Auto Connect	5	447	Electronic Hobby Innovations	93	*	KLM Electronics	81, 120
469	BG Carl Electronics	91	146	Electronic Rainbow Industries, Inc.	62	204	Lacomb	63
11	Barker & Williamson, Inc.	31	481	Electronic Specialists, Inc.	121	322	Larsen Antenna	37
305	Barry Electronics Corp.	41	400	Engineering Consulting Service	130	214	A. Lascurain	115
157	Boman Industries	29	22	Fair Radio	129	*	Liberty Electronics	130
223	Britt's Two-Way	40	85	Faxscan, Inc.	50	220	Lunar Electronics	130
226	Buckmaster Publishing	65, 95	218	Ferritronics	44	77	M-Squared Engineering, Inc.	61
*	Butternut Electronics Corp.	89	23	Flesher Corp.	30	44	Macrotronics, Inc.	62
187	Call Letter Hats	116	323	Fox-Tango Corp.	49, 61	45	Madison Electronics	69
102	Centurion International	4	178	Galaxy Electronics	129	134	Martin Engineering	93
89	Clutterfree Modular Consoles	61	*	Gilfer Shortwave	91	47	MFJ Enterprises	39, 61, 63, 65
163	Com-Rad Industries	129	*	GFS Electronic Imports	129	480	MFJ Enterprises	120
382	Communications Concepts, Inc.	72	143	GLB Electronics	45	48	MHz Electronics	132-141
*	Communications Design	91	195	Goldsmith Scientific Corp.	85	51	Microlog	24, 25
462	Communications Electronics Specialties, Inc.	14	132	Grand Systems	63	*	Mirage Communications	77
482	Communications Electronics Specialties, Inc.	122	31	Hal-Tronix	56	318	National Comm. Group Co.	57, 72
			485	Hal Communications	121	412	Nemal Electronics	123
			*	Ham Radio Center	9	483	Non-Linear Systems	120
			*	Ham Radio Outlet	3	137	Nuts & Volts	130
			33	Hamtronics, NY	142, 143	*	Orb/I Magazine	57
						*	P. C. Electronics	93
						*	Palomar Engineers	4, 72
						159	Parsec Communications	129
						201	Pegasus Electronics Ind.	91
						182	Peterson Electronics	130
						61	Radio Amateur Callbook, Inc.	30
						397	Radio World	89
						62	Ramsey Electronics	131, 145
						156	RF Electronics	45
						171	Ridge Systems Co., Inc.	50
						133	Rivendell Associates	115
						418	Rollin Distributors	72
						150	Royal	123
						477	Royal	121
						65	S-F Amateur Radio Services	85
						500	73	
							Books	84, 111-114, 123, 126, 128
							Dealer Ad	128
							Moving	128
							Subscriptions	83, 95
							University Microfilms	95
						*	Simple Simon Electronics Kits	68
						*	Spectronics	144
						68	Spectrum Communications	
								16, 17
						436	Spectrum International, Inc.	116
						173	Splder Antenna	95
						*	Telex Communications	15
						224	Telton	130
						478	Telton	121
						*	Ten-Tec, Inc.	79, 105
						*	The Antenna Bank	50
						118	The Blackburn Group	31
						249	The Ham Shack	51
						405	The Metheny Corp.	129
						57	The Tuned Antenna	31
						104	Trionyx	55
						484	Universal Electronics	108
						*	V-J Products, Inc.	63
						*	Van Gorden Engineering	49
						311	Vanguard Labs	130
						200	Votuc Communications	93
						*	W9INN Antennas	115
						302	W-S Engineering	89
						80	Western Radio Electronics	91, 95
						83	Yaesu Electronics	Cov. III



# BOOKS, ETC.

To order, complete the postage-paid card, or itemize your order including detailed credit card information or check and mail to: 73 Magazine/Mail Order Dept./Peterborough NH 03458.

Catalog#	Item	Price	Catalog#	Item	Price	Catalog#	Item	Price	Catalog#	Item	Price
73300	73 BACK ISSUE—BEFORE JULY 1980	\$ 3.00	BK7309	CHALLENGE OF 160	\$ 4.95	BK7310	OWNER REPAIR OF RADIO EQUIPMENT	\$ 7.95	SG7358	STUDY GUIDE—GENERAL CLASS.	\$ 6.95
73350	73 BACK ISSUE—JULY 1980 THRU OCT 1981	\$ 3.50	BK1011	CMOS COOKBOOK	\$10.50	BK1185	THE PRACTICAL HANDBOOK OF FM REPEATERS	\$12.95	BK1190	THE TEN METER FM HANDBOOK	\$ 4.95
73350P	73 BACK ISSUE—NOV. 1981 TO PRESENT	\$ 3.50	CT7305	CODE TAPE—5 WPM	\$ 4.95	BK7302	PROPAGATION WIZARD'S HANDBOOK	\$ 6.95	LB7360	TEST EQUIP LIB V2—AUDIO TESTERS	\$ 4.95
73005	73 BACK ISSUE—5 YOUR CHOICE	\$10.75	CT7306	CODE TAPE—6+ WPM	\$ 4.95	QW0250	QSL CARDS—STYLE W—250	\$ 8.95	LB7361	TEST EQUIP LIB V3—RADIO EQUIP	\$ 4.95
	Add \$1.00 per magazine for shipping		CT7313	CODE TAPE—13+ WPM	\$ 4.95	QW0500	QSL CARDS—STYLE W—500	\$13.95	LB7362	TEST EQUIP LIB V4—IC TEST EO.	\$ 4.95
73010	73 BACK ISSUE—10 YOUR CHOICE	\$16.00	CT7320	CODE TAPE—20+ WPM	\$ 4.95	QX0250	QSL CARDS—STYLE X—250	\$ 8.95	BK7387	TEXTEDIT—WORD PROCESSING KIT	\$9.97
73025	73 BACK ISSUE—25 YOUR CHOICE	\$27.00	CT7325	CODE TAPE—25+ WPM	\$ 4.95	QX0500	QSL CARDS—STYLE X—500	\$13.95	DS7387	TEXTEDIT—DISK	\$19.97
73125	73 BACK ISSUE—25 OUR CHOICE	\$14.00	CT7394	CODE TAPES (ANY FOUR ABOVE)	\$15.95	QY0250	QSL CARDS—STYLE Y—250	\$ 8.95	BK7348	TOOLS & TECHNIQUES	\$ 4.95
	Add \$7.50 per order for shipping		BK1241	THE COMPLETE SHORTWAVE LISTENER'S HANDBOOK	\$ 9.95	QY0500	QSL CARDS—STYLE Y—500	\$13.95	BK1063	TTL COOKBOOK	\$ 9.50
BK1196	ALL ABOUT CUBICAL QUAD ANTENNAS	\$ 5.95	BK7308	THE QNTST COOKBOOK	\$ 5.95	BK1199	THE RADIO AMATEUR ANTENNA HANDBOOK	\$ 6.95	BK1064	TVT COOKBOOK	\$ 9.95
BK7384	ANNOTATED BASIC, VOL 1	\$10.95	BK7381	40 COMPUTER GAMES	\$ 7.95	BK1044	RF & DIGITAL TEST EQUIPMENT	\$ 5.95	BK7382	UNDERSTANDING & PROGRAMMING MICROCOMPUTERS	\$10.95
BK7385	ANNOTATED BASIC, VOL 2	\$10.95	BK1244	EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TV	\$ 9.95	BK1016	73 DIPOLE & LONG WIRE ANTENNAS	\$ 5.50	BK7368	VHF ANTENNA HANDBOOK	\$ 5.95
BK1197	BEAM ANTENNA HANDBOOK	\$ 5.95	BK7321	A GUIDE TO HAM RADIO	\$ 4.95	BK1000	SHELF BOX—1	\$ 2.00	BK1198	VHF HANDBOOK FOR RADIO AMATEURS	\$ 6.95
BK7307	BEHIND THE DIAL	\$ 4.95	BK7322	HOBBY COMPUTERS ARE HERE	\$ 2.47	BK1001	SHELF BOXES—2-7	\$1.50 each	BK1202	WORLD PRESS SERVICE FREQUENCIES	\$ 7.95
			BK1201	HOW TO DEFEND YOURSELF AGAINST RADAR	\$ 6.95	BK1002	SHELF BOXES—8 AND UP	\$1.25 each	BK7315	WORLD REPEATER ATLAS	\$ 2.00
			BK1028	IC OP AMP COOKBOOK	\$14.95	BK1200	SIMPLE LOW COST WIRE ANTENNAS FOR RADIO AMATEURS	\$ 6.95			
			BK1230	INTERFERENCE HANDBOOK	\$ 8.95	BK7311	SOME OF THE BEST FROM KILOBAUD	\$10.95			
			BK7386	KILOBAUD KLASROOM	\$14.95	BK7351	SSB THE MISUNDERSTOOD MODE	\$ 5.50			
			BK7312	MAGIC OF HAM RADIO	\$ 4.95	SG7357	STUDY GUIDE—NOVICE CLASS.	\$ 4.95			
			BK7340	THE NEW HOBBY COMPUTERS	\$ 2.47						
			BK7383	THE NEW WEATHER SATELLITE HANDBOOK	\$ 8.95						
			CT7300	NOVICE THEORY TAPES	\$15.95						

SHIPPING AND HANDLING CHARGES: \$1.50 for the first book, \$1 for each additional book for US delivery and foreign surface; \$10 per book for foreign airmail.

# SATELLITES

## Amateur Satellite Reference Orbits

Date	OSCAR 8		RS-5		RS-6		RS-7		RS-8		Date
	UTC	EQX	UTC	EQX	UTC	EQX	UTC	EQX	UTC	EQX	
Mar 1	0024	87	0124	140	0049	134	0135	143	0154	145	1
2	0028	88	0119	140	0034	132	0125	142	0151	145	2
3	0033	89	0114	140	0019	130	0115	141	0148	146	3
4	0037	90	0108	140	0003	127	0106	140	0145	147	4
5	0041	91	0103	140	0147	155	0056	139	0142	148	5
6	0046	92	0058	140	0131	153	0046	138	0139	149	6
7	0050	93	0052	141	0116	150	0037	138	0137	149	7
8	0054	95	0047	141	0100	148	0027	137	0134	150	8
9	0059	96	0042	141	0045	146	0017	136	0131	151	9
10	0103	97	0036	141	0030	143	0008	135	0128	152	10
11	0108	98	0031	141	0014	141	0157	164	0125	153	11
12	0112	99	0026	142	0158	168	0148	163	0122	154	12
13	0116	100	0020	142	0142	166	0138	162	0120	154	13
14	0121	101	0015	142	0127	164	0128	161	0117	155	14
15	0125	103	0009	142	0111	161	0119	160	0114	156	15
16	0130	104	0004	142	0056	159	0109	160	0111	157	16
17	0134	105	0158	173	0041	157	0059	159	0108	158	17
18	0138	106	0153	173	0025	154	0050	158	0105	158	18
19	0000	81	0148	173	0010	152	0040	157	0103	159	19
20	0004	82	0142	173	0153	180	0030	156	0100	160	20
21	0008	83	0137	173	0138	177	0021	155	0057	161	21
22	0013	85	0132	173	0122	175	0011	154	0054	162	22
23	0017	86	0126	174	0107	173	0001	153	0051	163	23
24	0022	87	0121	174	0052	170	0151	182	0048	163	24
25	0026	88	0115	174	0036	168	0141	181	0046	164	25
26	0030	89	0110	174	0021	166	0132	181	0043	165	26
27	0035	90	0105	174	0005	163	0122	180	0040	166	27
28	0039	91	0059	175	0149	191	0112	179	0037	167	28
29	0043	93	0054	175	0133	188	0103	178	0034	167	29
30	0048	94	0049	175	0118	186	0053	177	0031	168	30
31	0052	95	0043	175	0103	184	0043	176	0029	169	31
Apr 1	0057	96	0038	175	0047	181	0034	175	0026	170	1
2	0101	97	0033	175	0032	179	0024	174	0023	171	2
3	0105	98	0027	176	0016	177	0014	173	0020	172	3
4	0110	99	0022	176	0001	175	0005	173	0017	172	4
5	0114	100	0017	176	0144	202	0154	202	0014	173	5
6	0119	102	0011	176	0129	200	0145	201	0012	174	6
7	0123	103	0006	176	0113	197	0135	200	0009	175	7
8	0127	104	0001	177	0058	195	0125	199	0006	176	8
9	0132	105	0155	207	0043	193	0116	198	0003	176	9
10	0136	106	0149	207	0027	190	0106	197	0000	177	10
11	0141	107	0144	207	0012	188	0056	196	0157	208	11
12	0002	83	0139	207	0155	216	0047	195	0154	209	12
13	0006	84	0133	208	0140	213	0037	194	0152	210	13
14	0011	85	0128	208	0124	211	0028	194	0149	211	14

## AMATEUR SATELLITE NEWS

### Soviet Telemetry Update

Russia's RS (Radio Sputnik) amateur satellites continue to transmit a steady stream of telemetry data. Since I last discussed RS telemetry in this column (73, Sept., 1982, p. 140), new interpretations of some data items have come to light. Table 1 is a revised list of the 35 RS telemetry items and the equations for decoding the raw numbers into interesting information about the spacecraft.

All RS telemetry is transmitted in Morse code at speeds from 15 to 25 words per minute. When the satellites are in range, virtually any 10-meter receiving installation should be capable of hearing the transmissions. Table 2 gives the telemetry beacon frequencies for all six of the RS satellites. It's easy—give it a try!

Thanks to *Amateur Satellite Report* for the updates.

### The Home Stretch

The second half of April—probably the 21st—is now the scheduled date for the launch of the AMSAT Phase III B amateur satellite. If the launch takes place as planned, it will occur a little less than three years after the ill-fated attempt that sent the Phase III A satellite to the bottom of the Atlantic.—Jeff DeTray WB8BTH, Assistant Publisher, 73.

### Prefix Interpretation

Prefix	Interpretation
K	0.2 x N = output power of transponder in mW
D	N x 0.2 = voltage of main power source
O	20 x (100 - N) = charge current in mA
G	Service parameter; usually = zero (00)
U	Gas pressure of sealed system; equation unknown
S	N = temp. of voltage regulator (Celsius)
W	N = temp. of transmitter cooling fins (Celsius)
IK or SK	Same as K
ID or SD	Telemetry baseline; usually = zero (00)
IO or SO	0.2 x N = output power of beacon in mW
IG or SG	When N = 10 ± 1, a 10-dB attenuator is in line with main receiver front end
IU or SU	0.1 x (N - 10) = relative S-units, main receiver
IS or SS	0.1 x (N - 10) = relative S-units, robot receiver
IW or SW	0.1 x (N - 10) = relative S-units, command receiver
NK or RK	Same as K
ND or RD	50 x N = solar panel current in mA
NO or RO	2.7 x (N - 26) = temp. of 1st solar panel (Celsius)
NG or RG	2.7 x (N - 26) = temp. of 2nd solar panel (Celsius)
NU or RU	2.7 x (N - 26) = temp. of 3rd solar panel (Celsius)
NS or RS	0.8 x (N - 5) = temp. of structure (Celsius)
NW or RW	0.8 x (N - 5) = temp. of hermetically-sealed casing

See List of Advertisers on page 114

**NEW 20MHZ DUAL TRACE NEW**  
**BUILT IN COMPONENT TESTER**

\$555

COMPLETE WITH PROBES

## ONE YEAR WARRANTY

**X-Y Operation, (1:1 Ratio)**

**2x 20MHz, max. 2mV/cm**  
max. 1% Overshoot

**Timebase 40ns — 0.2s/cm**  
Incl. Magnification x8

**Trigger Bandwidth 30MHz**  
Internal at 5mm

(603) 434-5371

*Rivendell Assoc.*

RFD-5
DERRY, N.H. 03038
WARNER HILL

## MULTI-BAND SLOPERS

160, 80, and 40 meters

Outstanding DX performance of slopers is well known. Now you can enjoy 2 or 3 band BIG-SIGNAL reports! Automatic bandswitching · Very low SWR · Coax feed · 2kw power · Compact · Ground or tower feed · Hang from any support 25 ft. high or higher · Easy to install · Very low profile · Complete instructions · Immediate shipment · Check off

3-BAND SLOPER - 160, 80, & 40 Meters - 60 ft. long	\$ 43.00 frt. ppd
2-BAND SLOPER - 80 & 40 Meters - 41 ft. long	\$ 30.00 frt. ppd
3-BAND NO TRAP DIPOLE - 160, 80 & 40M - 113 ft. long	\$ 66.00 frt. ppd
2-BAND NO TRAP DIPOLE - 80, & 40M - 84 ft. long	\$ 49.00 frt. ppd

FOR ADDN'L INFO on these and other unique antennas: send SASE

W9INN ANTENNAS

BOX 393-S MT. PROSPECT, IL 60056

## HOME BREW "THE SOUTHERN CROSS"

ONE OF THE MOST EFFECTIVE, SIMPLE, STRONG AND INEXPENSIVE, TWO ELEMENT MULTI-BAND

## QUADRICUBE ANTENNA

EXTRAORDINARY DX PERFORMANCE IDEAL FOR 20-15 AND 10 METER BANDS. THE TOTALLY PLASTIC MATERIAL STRUCTURE OF TRIANGULAR SHAPE THAT MATCHES PERFECTLY THE ELECTRONIC REQUIREMENTS, LEADS TO STRAIGHTFORWARD DESIGN THAT REDUCES LOSSES, SIMPLIFIES ADJUSTMENTS & STRENGTHENS CONSIDERABLY THE ANTENNA. MATERIALS REQUIRED ARE OBTAINABLE IN ALMOST ANY LOCALITY. COMPLETE DESCRIPTION, DRAWINGS AND ALL NECESSARY INFORMATION TO BUILD IT, IN ENGLISH OR SPANISH, AIR MAILED TO ANY COUNTRY \$20 U.S. CHECK CASHABLE IN U.S.A. TO A. LASCURAIN PINO N° 59 MEX. D. F. 01030 MEXICO 214

AK or UK	Same as K
AD or UD	0.1 x N = voltage of transponder 9-volt line
AO or UO	0.1 x N = voltage of transponder 7.5-volt line
AG or UG	0.1 x N = voltage at first 9-volt stabilizer
AU or UU	0.1 x N = voltage at first 7.5-volt stabilizer
AS or US	0.1 x N = voltage at second 9-volt stabilizer
AW or UW	0.1 x N = voltage at second 7.5-volt stabilizer
MK or WK	Same as K
MD or WD	N = # of OSOs made by robot (occasionally reset to zero by ground controllers)
MO or WO	N x 0.1 = power consumption of heating system in Watts
MG or WG	N x 20 = input power of robot transmitter in mW
MU or WU	N x 20 = input power of service channel in mW
MS or WS	When N = 10 ± 1, a 10-dB attenuator is in line with the robot receiver front end
MW or WW	When N = 10 ± 1, a 10-dB attenuator is in line with the service receiver front end

Table 1. RS telemetry channel prefixes and their meanings. N is the two-digit number sent after the prefix. Where two prefixes are given, the first is used when the service (or command) channel aboard the satellite is not active. The second is used when the service channel is active, indicating the satellite is under command by ground controllers.

Satellite	Frequencies (MHz)	Satellite	Frequencies (MHz)
RS3	29.321, 29.401	RS6	29.411, 29.435
RS4	29.360, 29.403	RS7	29.341, 29.501
RS5	29.331, 29.452	RS8	29.461, 29.502

Table 2. RS beacon frequencies.

# FUN!

John Edwards K12U  
78-56 86th Street  
Glendale NY 11385

## POTPOURRI

Potpourri! As our readers in F, VY, HH, FS, FR, FM, and FG-lands undoubtedly know, the word signifies a medley of various items. And that's what this month's Fun! is, a grab bag of questions on topics spanning the entire spectrum of amateur-radio activity. Think you're an amateur-radio renaissance man? Give this month's puzzlers a try.

### ELEMENT 1—MULTIPLE CHOICE

- From 1978 to 1979, a person claiming to be a lawyer threatened to take away all of our bands and give them to CB. Can you remember this generous chap's name and the organization he purported to represent?
  - Richard Cooper and the Communications Attorney Service
  - Harry Dannals and the American Radio Relay League
  - Jon Ingram and the Citizen's Radio Coalition
  - David Simpson and the Committee for Fair Communication
- Remember that Jack Anderson column a few years back? You know, the one that claimed hams were controlling just about everything in Washington from the FCC to the Pentagon. Well, can you name the US Representative who gave Scoop Anderson his story?
  - Claude Pepper of Florida
  - Tip O'Neill of Massachusetts
  - Elliott Levitas of Georgia
  - Fred Richmond of New York
- Roy Neal K6DUE hosted the films "The World of Amateur Radio" and "Moving Up to Amateur Radio." Can you name the narrator of "Ham's Wide World"?
  - Walter Cronkite K2IBE
  - Arthur Godfrey K4LIB
  - Dick Van Dyke WJ6L
  - Phil Donahue KE9UF

4) Which of the following amateurs is not a Westlink anchorman?

- Jim Davis KU8R
- Alan Kaul W6RCL
- Burt Hicks WB6MQV
- Stan Martin WA2DCS

5) A number of years ago, there was an amateur-radio column written in broken English supposedly by an oriental writer. Name the "author" and the magazine.

- Scratch!, in CQ
- Itchy, in QST
- Ching Chow in Ham Radio Horizons
- Hong Wouff in 73

### ELEMENT 2—TRUE-FALSE

- |   | True | False |
|---|------|-------|
| 1) A ham was involved in the production of the movie "E.T.—The Extra Terrestrial." TM   | ___  | ___   |
| 2) The first ham to operate from orbit was Neil Armstrong aboard Gemini 6.  | ___  | ___   |
| 3) In 1982, the Soviet Union launched two amateur Iskra satellites from the Solyut 7 space station. The word Iskra means "peace."                             | ___  | ___   |
| 4) Ken Sessions K6MVH wrote the very first book dealing with ham repeaters.   | ___  | ___   |
| 5) A famous DXer is known by the name of Dr. DX.  | ___  | ___   |
| 6) At the relatively tender age of 22, James Hendershot WA6VQP was the youngest person ever to serve as the head of a repeater coordination council.          | ___  | ___   |
| 7) Joseph Merdler N6AHU is the current president of the Personal Communications Foundation.   | ___  | ___   |
| 8) A few years back, a novel that included ham radio as an integral part of its plot not only hit the best sellers list, but also was turned into a TV movie. | ___  | ___   |
| 9) King Juan Carlos of Spain is a ham.  | ___  | ___   |
| 10) Queen Elizabeth of England is a ham.  | ___  | ___   |

### ELEMENT 3—SCRAMBLED WORDS

Unscramble these terms and slangs relating to ham radio.

- |           |          |       |
|-----------|----------|-------|
| BUST      | ETADOMLU | RETME |
| NCTOLREEA | EKY      | DNAB  |
| KIME      | CORK     | GLSU  |
| RETHE     |          |       |

## WORK THE U.H.F. BANDS

Add a transverter or converter to your existing 10m, 6m or 2m equipments. Choose from the largest selection of modules available for DX, OSCAR, EME, ATV.

### TRANSVERTERS



- |                |          |
|----------------|----------|
| MMT 50-144     | \$209.95 |
| MMT 144-28     | \$199.95 |
| MMT 432-28 (S) | \$299.95 |
| MMT 439-ATV    | \$349.95 |
| MMT 1296-144   | \$374.95 |
- OTHER MODELS AVAILABLE  
write for details

### POWER AMPLIFIERS

all models include RF VOX & Low Noise RX Pre-Ampl.  
(no pre-amp in MML432-100)

2 Meters:	100W output	MML144-100-LS	1W or 3W in	\$284.95
	100W output	MML144-100-S	10W input	\$264.95
	50W output	MML144-50-S	10W input	\$239.95
	30W output	MML144-30-LS	1W or 3W in	\$124.95
	25W output	MML144-25	3W input	\$114.95

432 MHz:	100W output	MML432-100	10W input	\$444.95
	50W output	MML432-50	10W input	\$239.95
	30W output	MML432-30-L	1W or 3W in	\$ ask

1268-1296 MHz:

Coming soon. Watch for details.


### ANTENNAS (incl. 50 ohm balun)

- |                         |               |         |
|-------------------------|---------------|---------|
| 2 Meter J-Beams:        | 12.3 dBd gain |         |
| 8 over 8 Horizon'l pol  | D8-2M         | \$63.40 |
| 8 by 8 Vertical pol     | D8-2M-vert    | 76.95   |
| 1250-1300 MHz Loop-Yagi | 1296-LY       | \$49.75 |

Send 36¢ stamps for full details of all our VHF/UHF items.

- Pre-selector filters
- Low-pass filters
- Varactor triplers
- Pre-amplifiers

 - Transverters
- Converters
- Antennas
- Crystal Filters



D8/2M



# si

Spectrum International, Inc.  
Post Office Box 1084S  
Concord, Mass. 01742 USA

436



## CALL LETTER

HATS — T SHIRTS ✓ 187

101 & Elm Street, Suite 4 Peterborough, NH 03458

### HATS

Only \$6

HAT COLORS

- Royal Blue Navy Blue
- Red Gold Green

Hats Are One Size Fits All - Nylon Mesh Back



LINE 1 CIRCLE ONE OF THE DESIGNS ABOVE

LINE 2

OR

LINE 3

OR

NOTE\* Hats Maximum 8 Large or 16 Small Letters Per Line

LINE 4

OR



### T SHIRTS

Only \$8

SHIRT SIZES

- Adult: Sm Med Large X-Large
- Child: 2-4 6-8 10-12 14-16

SHIRT COLORS

- Lgt Blue Tan Wht/Blue Trim
- Wht/Red Trim

Attractive and Durable, just the thing for field days, contests, conventions or any other activity. Ideal personalized gifts for special occasions and they carry your own personal message. Imprints are permanent and guaranteed not to fade, peel or shrink. Order 12 or more and we will reproduce your own business or club logo FREE. Remember, every item can have a Different name or message in addition to your logo. Imprints are generated by computer for total flexibility and FAST service.

CALL LETTER HATS 101 & Elm Street Suite 4 Peterborough, NH 03458

Name  Phone

Address

City  State  Zip

Ck  Money Order  Charge Card  #

Signature To Validate Order  Exp. Date

ORDER BLANK  Add \$2 To Total For Shipping Charges

## ELEMENT 4—ALPHABET GUESS

Complete the words below by placing letters of the alphabet on every dash. Use each letter only once. The letter "Z" isn't used.

- A B C D E F G H I J K L  
M N O P Q R S T U V W X Y
- 1) \_ I \_ D E
  - 2) \_ O T \_ \_ T \_ O M E \_ \_ \_
  - 3) \_ O U L E
  - 4) \_ \_ \_ \_ \_ G U I D E
  - 5) Y O \_ E
  - 6) D U P \_ E \_ \_
  - 7) \_ T U \_
  - 8) \_ A R R I E R
  - 9) \_ R E \_ \_ E N C \_ \_
  - 10) \_ A \_ \_

## THE ANSWERS

### Element 1:

- 1—1 He's now believed to be living south of the border.
- 2—3 Still in Congress, but probably has found other ways to fish for votes.
- 3—2 Seems like old times just thinking about that film.
- 4—4 Stan's probably the missing "link."
- 5—5 Think ol' Scratch! ever got paid?

### Element 2:

- 1—True Indirectly, anyway. Henry Feinberg K2SSQ designed the little alien's space communicator.
- 2—False As of yet, no ham has ever operated "spaceship mobile." That may change later this year, though, when Dr. Owen Garriott W5LFL is scheduled to take an HT aboard the shuttle.
- 3—False Spark.
- 4—True Not an easy question.

- 5—True A name given to him by Westlink's Alan Kaul.
- 6—True You read it here first.
- 7—True A much-needed and under-appreciated organization.
- 8—True "The French Atlantic Affair," by Ernest Lehman K6DXK.
- 9—True I've yet to work him, though.
- 10—False Not yet.

### Element 3:

Stub, tolerance, mike, ether, modulate, key, rock, meter, band, slug.

### Element 4:

1—DIODE, 2—POTENTIOMETER, 3—JOULE, 4—WAVEGUIDE, 5—YOKE, 6—DUPLEX, 7—STUB, 8—CARRIER, 9—FREQUENCY, 10—HAM.

## SCORING

### Element 1:

Five points for each correct answer.

### Element 2:

Two and one-half points for each correct answer.

### Element 3:

Two and one-half points for each word unscrambled.

### Element 4:

Two and one-half points for each word completed.

Potpourri literally translates to "rotten pot." How rotten are you?

- 1-20 points—Rancid
- 21-40 points—Green around the gills
- 41-60 points—Slightly sour
- 61-80 points—Fresh as a daisy
- 81-100 points—Prime condition

Special thanks for this month's column go to Bill Pasternak WA6ITF (of 73's "Looking West" fame), who provided many of the trickier questions.

# CORRECTIONS

Builders of the "Keyer on a Shoestring" (73, November, 1982, page 104) should note that the Radio Shack 276-2008 transistor specified for Q1 is no longer available. An appropriate substitute is the Radio Shack 276-2061 or Motorola MPSA42. When using these transistors, the resistor connected to the base of Q1 should be changed from 2.2k to 1k.

Jeff DeTray WB8BTH  
73 Staff

Radio Shack recently introduced a new style of 10-uH choke which affects all of the coils in 73's series of Fun-Gear articles. Those articles were "The Fun-Mitter — A Goof-Proof Rf Project," Feb., 1981; "The Fun-Ceiver," July, 1981; "The Fun-Oscillator," Feb., 1982; "The Fun-Amp," May, 1982; and "Fun-Equipment Revisited," Jan., 1983.

The new Radio Shack choke can be identified by a smaller body, fewer turns (a total of 22), and the part number 273-101A. These new chokes will operate fine, provided the correct number of turns are removed. Table 1 shows the number of turns that must be removed from the full choke.

Mark Oman WA0RBR  
Ft. Collins CO

### Fun-Mitter

	L1	L4
80m	5 (8.4 uH)	14 (2.4 uH)
40m	0 (10 uH)	17 (1.2 uH)
20m	13 (2.8 uH)	18 (.6 uH)
15m	17 (1.2 uH)	19 (.4 uH)

### Fun-Amp

	L2	L3
80m	10 (4.7 uH)	7 (6.2 uH)
40m	13 (2.9 uH)	10 (4.3 uH)
20m	18 (1.0 uH)	17 (1.4 uH)
15m	20 (0.5 uH)	18 (1.0 uH)

### Fun-Ceiver


	L2, L3	L4
80m	5 (8.4 uH)	0 and 7 (16.2 uH)
40m	0 (10.0 uH)	7 (6.2 uH)

### Fun-Oscillator

	L1
80m	0 and 7 (16.2 uH)
40m	7 (6.2 uH)

Table 1. Correct dimensions for Fun-Gear coils.

 "A Tuner for Antenna Fanatics," which appeared in the November, 1982, issue, contained an incorrectly-drawn schematic. The switching system in Fig. 1 on page 42 should be wired as shown here. The only component change necessary is the substi-



Revised Fig. 1, "A Tuner for Antenna Fanatics."

tion of a 6-pole switch for the 5-pole switch suggested in the article. Thanks to Jeff Steinkamp KA5MYF for pointing out the error.

Avery L. Jenkins  
73 Staff

D6 and the 1-uF capacitor. The 100k resistor should go directly to pin 6 of U3.

Avery L. Jenkins WB8JLG  
73 Staff

A diagram error appeared in Fig. 3 (page 33) and Fig. 5 (page 36) of "What? Another Audio Filter Project?" in the November, 1982, issue. Both diagrams show the cathode of diode D7 connected to a 100k resistor and pin 6 of U3. However, the cathode of D7 should be connected to the junction of

The addresses of Ameco Equipment Company and Amidon Associates were accidentally reversed in "Beating the Untraceable Buzz" on page 58 of the January, 1983, issue. Amidon Associates is located at 12033 Otsego St., North Hollywood CA 91607; Ameco's offices are located at 275 Hillside Ave., Williston Park NY 11596.

Avery L. Jenkins WB8JLG  
73 Staff

# HAM HELP

I would like to hear from anyone who has successfully used a hidden antenna.

Michael H. Landwehr KE7T  
PO Box 4502  
Huachuca City AZ 85616

Wanted: the schematic for an Electrodata model AG-1 audio generator.

R. H. Klapheke  
4113 Sunflower Dr.  
Louisville KY 40216

I am looking for a way to modify a Motorola HT battery-pack recharger so that an Icom HT can be inserted in it.

Don Setliff WB8IMA  
4729 Darnell Rd. #17  
Huntington WV 25705

Can anyone supply me with the schematic needed to interface a modulator with a Pet 4032? I also need CW and RTTY programs.

Nazzaro Limongelli  
Milano 1, 09100  
Cagliari, Italy

I am searching for a CRT for a Tektronix 422 oscilloscope, or any information on repairing the old tube.

Robert L. Rowles KC5GT  
701 NW 24th St.  
Guymon OK 73942

I would like to locate someone in the Marion IL area who could help me learn the code. I am working toward my Novice license.

Ron Banfield  
RR 4, Box 174, Lake Estates  
Marion IL 62959

# RTTY LOOP

Marc I. Leavey, M.D. WA3AJR  
4006 Winlee Road  
Randallstown MD 21133

Random ruminations at the end of winter. "What do I need to do to get an article published describing my new LSI circuit that not only multiplies Q, but divides, adds, and subtracts it as well?" Boy, how many times I get that one! First of all, look critically at what you want to write about. Is it interesting to others? Bounce the idea off a few close friends; if they are friends, they won't (shouldn't) pirate your idea. If it's not technical, ask your wife (husband/mother/father/significant other) for an opinion.

If all is still okay, write up an outline for the article. Now, I don't necessarily mean the formal (I-A-1-a, etc.) outline that you learned back in the fifth grade, but rather an informal sketch of the points you want to cover. Try to organize the article with, as radical as it sounds, a beginning, a middle, and an end.

For technical articles, the first segment normally introduces what the device is, perhaps why it is needed, and general specifications. The central part of the article deals with the nuts and bolts (design and construction) phase. At the end, alignment and testing, applications, and potential other uses or pathways may be explored.

Non-technical articles follow the same train of thought, but on a parallel track. Open your idea, develop it, and close, trying to keep some sense of order. Diagrams, drawings, or photographs might occur to you as being appropriate at certain places. Note these now for later development and inclusion.

Now it's time to, as they say, flesh it out; write the words that make the whole world read, or whatever. If you have not written before or are unsure of your ability to set down words that make sense, I have a tip for you. Get a tape recorder and say what you want to write. Describe the gizmo, investigate the concept, or expand the theme

vocally, then listen to it and write down what you said. Alternatively, type it into a word processor (my favorite technique) or write it down in longhand on a yellow pad (my second favorite technique); just get those first ideas down onto paper. You will need it in this rough form so that it can be polished into a finished gem.

Once you get the first draft down, read it. Yes, look for misspelled words and the like, but also *read it* (out loud is a good idea). Does it make sense? Are there areas which could be explained better or places where the explanation is so long-winded that it chokes the meaning to death? Clean it up, revise it (this is where a word processor makes life easy!), and when you are happy, go back to the friend you approached before and see what he or she thinks. Does your opening try to "grab" the reader? Is your last sentence a conclusion or close, or does it just end in space?

Finished? Now type up a good copy. I know we aren't all typists, but there are some standards which should be followed. Your submission copy should be typed, not handwritten, on standard 8.5" by 11" white bond paper. It should be in upper- and lowercase, be double spaced, and have generous margins on all four sides. It should *not* be uppercase-only printer output (this is a human readable article, not a program) on newsprint-weight roll paper or pasted-up sheets from a narrow thermal printer. If you have a dot-matrix printer which produces good quality upper- and lowercase print, check with the publisher before you use it; most editors would still prefer typewriter-style characters for their weary eyes.

Diagrams should be neatly drawn, with black ink on 8.5" by 11" paper. They don't have to be super-artsy; most magazines will have them redrawn by a draftsman if your article is published. Just make sure they are clear and correct. Photographs should be sharp and clear, with 8" by 10" black and whites preferred. Little Instamatic™ or Polaroid™ snaps just won't reproduce

well. Color should not be used unless it is essential to the picture; most magazines cannot or will not print color photos, anyway.

Now that you've worked on this labor of love to a state of perfection, where do you send it? Here are some items to help you make up your mind. For amateur radio articles, the ARRL's journal QST, pays you nothing for your contribution, allowing you to bask in the glory given to those few authors whose work is published each month. On the other hand, 73 pays its authors upon acceptance of the article, with the average being perhaps \$100 or more. I need not go into the number of articles published here every month.

For computer-related articles, the choice is more difficult. With the great number of specialty and general-interest magazines being published, you may well choose to direct your work to a specific audience. Payment practices vary widely, though, from reasonable amounts of cash to extending your subscription for a couple of months to a letter of thanks. To the best of my knowledge, unlike 73, those computer magazines that pay for articles pay on *publication*, not when they accept your article. Therefore, they can, and do, hold your article for many months or years on the promise of payment. Check it out before you submit your masterpiece.

When you have decided where to send your article, wrap it in a sturdy envelope, enclose a cover letter introducing both you and your work, and mail it off first class to the magazine. You should enclose sufficient first class postage for the article's return if it is (sob) rejected; otherwise it might find its way into the editor's circular file. Then sit back and wait a couple of weeks and, who knows, your article might lead the next issue of 73!

Membrane keyboards—feh! I mentioned here a few months back that I purchased an Atari 400 computer for both the kids and some looks into the more "popular" (as opposed to my 6800) side of computers. After poking around a bit, I have reached my First Conclusion of Home Computers: Membranes may be good for a lot of things, but keyboards ain't one of them. I shall elaborate. Many of the "new breed" computers sport flat membrane keyboards rather than

the more traditional typewriter-style keys. These flat panels are kidproof and less expensive to produce; they are also practically impossible to type on. Not much better are the little calculator-style keyboard keys found on another raft of personal computers. Others' widespread frustration with this trend is evidenced by magazine articles and independent manufacturers' production of full-sized keyboards for the Atari 400, Sinclair ZX-81, Pet, and others. But if you add a \$100 keyboard to an Atari 400, do you know what you get? An Atari 400 with an external keyboard. It reminds me of the time in high school when I tried to put expensive speakers on a cheap hi-fi compact. Couldn't understand why it sounded only marginally better. For the ham contemplating using a computer on RTTY or to write with, anything short of a standard (also called full-sized) keyboard is asking for trouble. No, membrane pads are fine for DTMF entry buttons, control switches on microwave ovens, or other occasional use terminals. But as keyboards designed for data entry? Feh!

Around the world with RTTY Loop brings a note here from Steve Pöpler VE3KHU in Ottawa, Ontario. Steve is using a Mite teleprinter for computer output and is in need of a part. Steve, the sources I had for Mite parts dried up several years ago, and I have had no new leads since. If anyone knows of a source, drop me a line and I will let Steve and other Mite owners know about it.

Hans Granberg SM2DHG, a RTTY/computer buff from Sweden, relates his interest in the 6800 and its use on RTTY. I am sending Hans copies of old issues of RTTY Loop which may be of help in his endeavors.

This and many other letters raise another question for you all out there. Would you like to see a compilation of old RTTY Loops in book form? If so, are there any sections you would specifically like to see expanded or condensed? Please drop me a line (a postcard or QSL would be fine) with some sense of what you, the readers of this column, would like. I have been trying to work on such a tome, but I keep getting bogged down in the material. Let me know what you would like to see.

Next month, a tip of the hat to Al Jolson. Don't follow? You'll just have to wait for next month's RTTY Loop!

# DX

Chod Harris VP2ML  
Box 4881  
Santa Rosa CA 95402

## AMATEUR RADIO IN SOUTHERN AFRICA

What's the only country in the world which is completely surrounded by one other country and has no land below 1500 meters high? If you're up on your geographic trivia, you might be able to identify this mystery country as Lesotho, in southern Africa.

Not many people know where Lesotho is; fewer still know much about the tiny "mountain kingdom." Even the official Lesotho tourist brochures seem to be talking about a different place. These brochures are filled with photographs of the country's railroad and hotels; they mention the local TV station, the happy Basotho natives, and the rain-free climate.

What the tourist brochures do not mention is that Lesotho is one of the 20 least developed nations in the world. It is totally surrounded by South Africa, on which it depends for electricity, employment of the Basotho people, money from gambling at the Holiday Inn in Maseru, and food. That highly touted national railroad is less than a mile long, and half the hotels in the brochures don't really exist. It rains so seldom in Lesotho that the country must import almost all of its foodstuffs. In fact, the motto of the tiny kingdom is "Peace, Rain, Prosperity." And just because it has little rain doesn't mean the climate is perfect; Lesotho boasts the highest incidence of lightning in the world, and frequent high winds sweep dust storms across the treeless country. And that prized television broadcast with a power of only 400 mW! Can you imagine how easy it must be to cause television interference?

What the kingdom does have includes

one of the longest reigning monarchs in the world, King Moshoeshoe II. It has majestic mountains, lots of them. The country is all mountains; even the "lowlands" are more than a mile high. And it has foreign aid. As a "non-aligned" nation, Lesotho enjoys frequent donations from other countries, including the US, France, Germany, and England. Lesotho recently received a grant of nearly 40 million dollars to fix up the nation's telephone system. There are only 4,000 phones in all of Lesotho; that's 10,000 dollars per phone!

With the highest incidence of lightning in the world, no trees to hang antennas from, a milliwatt TV station, and frequent high winds, you wouldn't think Lesotho would be an amateur-radio paradise, would you? But Rich Kingston 7P8BX (see photo) consistently receives signal reports 2 S-units louder than he gives out.

About half way along his round-the-world tour, Rich spent a few days in northern California with your DX editor. Rich offered to share his experiences as an amateur in southern Africa with 73 readers.

Rich finds amateur radio in Lesotho very successful. Using only a mobile whip, Rich and fellow Lesotho amateur Ed 7P8CG have worked stations around the world from a four-wheel-drive truck. And Rich

finds no problems with his modest antenna farm of dipoles. "The other day I got on 40 SSB and worked VS6, VK, and a bunch of JAs. They couldn't believe I was barefoot into a dipole," Rich said. Rich claims the good signal reports he receives are due to strange propagation in Lesotho, but I think the 7P8 callsign is worth at least 2 S-units.

While Lesotho is not exactly rare on the amateur bands, there are many DXers still looking for their first 7P8 contact. Perhaps this information will help.

Among the more active Lesotho amateurs are 7P8s BX, CG, CL, CM, and CR. Ed 7P8CG is Vice Consul at the American Embassy in Maseru, the capital of Lesotho. Ed hopes to work DXCC on CW while in Lesotho and also can be caught working mobile. Martin 7P8CM uses a 40-meter dipole on 40 and 15 meters. A new Lesotho amateur, 7P8CR, hails from Italy and often can be heard on phone speaking Italian and Spanish. Rich himself puts his TR-44C and Swan radios on the air from his home station (7P8BX) and mobile (7P8CG). Rich hopes to supplement his existing dipole antennas with some new aerials soon, including a 15-meter beam.

Rich suggests the best time to look for 7P8 stations is early evening, Lesotho time. 1730 UTC is 7:30 pm, local time. Beginning



Rich Kingston 7P8BX, president of the Lesotho Amateur Radio Society (right), discusses schedules with Paul Hansen AE6H, president of the Redwood Empire DX Association.

about 1700 UTC, 10 meters is often open to the States. You can listen for ZS stations or the ZS 10-meter beacon to check propagation to Lesotho. 10 meters tends to fade away completely during the stateside summer. Rich explains, so try lower-frequency bands between June and August. 15 meters often opens to the States about an hour later, around 1800 UTC.

Rich says 2 IRCs or a green stamp will provide return airmail postage for your 7P8 QSL card. Rich's own QSL card (see photo) features a map of the continent, with Lesotho marked, and a colorful one-cent stamp. Lesotho, like many small countries, produces beautiful postage stamps; they add a nice touch to Rich's custom card. Rich has included on his QSL the logos from two International organizations to which he belongs: the Radio Society of Great Britain and Mensa, the high-IQ society.

Rich is also president of the newly formed Lesotho Amateur Radio Society (LARS). LARS recently held its first meeting at the home of the German ambassador to Lesotho, 7P8CI. Of the approximately 18 amateurs in Lesotho, 12 joined LARS. Only about 6 of these amateurs are active on HF, however.

At the first meeting, Rich presented the International Amateur Radio Union (IARU) films on amateur radio. Several Basotho (lifelong residents of the tiny mountain kingdom of Lesotho) attended the first meeting, but none has an amateur radio license to date.

Rich has helped bring some formal structure to amateur radio in Lesotho and has patterned the license examinations after the British model. The theory portion of the amateur examination is taken directly from the British test. The code requirement of 12 wpm is also similar to the British system. Unlike the US test, Lesotho amateurs must copy the 12-wpm code without error! No multiple choice to make it easier!

The Lesotho Amateur Radio Society has exciting plans for encouraging amateur radio activity within the country and with hams in other countries. A club station, 7P8RS, is under construction and looking for donated or loaned gear. LARS plans a Field-Day-type operation, perhaps in connection with the king's birthday. And an award for working 7P8 amateurs is in the works. About the latter, Rich says, "It won't be an easy award. Perhaps work 7P8RS and 7P8 stations on 4 bands. You'll have to try hard to earn this one."

One of the duties of a young national amateur radio society such as LARS is to

set up an incoming QSL bureau for its members. The Lesotho Amateur Radio Society has started such a QSL bureau for local 7P8 amateurs. You can send your cards direct, to individual QSL managers, or to the bureau at Box 949, Maseru, Lesotho, Afrlca.

Any cards for 7P8 amateurs sent to the Lesotho Amateur Radio Society will arrive at LARS's PO box. The secretary or QSL manager of LARS will sort the incoming cards by callsign and hand them to appropriate LARS members at the next club meeting.

The Incoming QSL bureau in the States works in much the same way, but on a much larger scale. Let's follow a card back from Rich 7P8BX to a stateside ham, KK6X.

At a club meeting, the members of LARS bundle up their stateside QSL cards without SASEs and mail them to the USA's official IARU incoming QSL bureau at ARRL headquarters. The cards are then sorted by call areas and mailed to the QSL bureaus in each amateur radio call district. The card we are following is sent to the sixth district QSL bureau in Sun Valley, California.

Here, local volunteer amateurs enter the picture, donating hundreds of hours of time to sort the many thousands of QSLs by the first letter of the suffix. KY6A, K6ANP, KB6AG, and WB6ANT would all go to the "A" letter sorter. At the next radio club meeting, the individual letter sorters pick up their shopping bags full of QSLs. Our card is sent to the "X" sorter in northern California.

Every month, the individual letter sorter gets 10-100 lbs. of QSLs to sort by individual callsign. The "X" sorter gets a break because there are no three letter suffixes beginning with X, as these callsigns are reserved for experimental licenses. With only one- and two-letter suffixes, the "X" sorter gets only a fifth of the cards the sorters of other letters receive.

At the same time as he gets our card, the "X" sorter gets any return envelopes for stations with X as the first letter of their suffix. He puts these into callsign order and adds them to the file of envelopes on hand. After he sorts the incoming QSLs, he puts each amateur's QSLs into the SASE provided by that ham. If there are enough cards in the envelope, our sorter will seal and mail the envelope, and a few days later a happy KK6X will pull his 7P8BX card out of the envelope from the bureau.

There are many potential pitfalls for the QSL card along this extended journey from Lesotho to a mailbox in California, any of



Jay W6GO (left) and Jan K6HHD O'Brien are in charge of the program at the International DX Convention at the Holiday Inn, Valsia, California, April 22-24, 1983.

which can delay delivery. The card might sit around for a while before being shipped to the sixth district bureau. It might just miss a sorting session there and not be sent off to the letter sorter for another month. That letter sorter might be forced to skip a month for various reasons. So the card could easily take six months to get across the country. If you think that's slow, think about how much you are paying for this service.

The cards move through the QSL bureaus entirely by volunteer hands. The sixth district QSL bureau handled more than 600,000 cards last year! That's almost 2,000 a day, 365 days a year! The QSL bureau volunteers contribute thousands of

hours of rather tedious work to make a lot of DXers happy. And you'll never guess their biggest problem: unclaimed QSLs!

Thousands of cards pile up each year for amateurs who do not have an envelope on file at the correct QSL bureau. Sometimes there are thousands for a big contest station; sometimes only one or two for a ham who "doesn't work DX." One Technician who was helping sort cards came across three for himself! One was a call sign error, but two were from South American stations worked on 6 meters, years before.

What can you do to speed the process and get your QSLs back as fast as you can? I suggest three things: 1) get the proper



LESOTHO

# 7P8BX



QSO with		Date	Time	
			Z	
FREQ	A1A	J3E	R	S T
MHz				
Equipment				
Aerial				

73 de Richard D. Kingston,  
P.O. Box 1264,  
MASERU LESOTHO  
AFRICA

Rich Kingston's QSL card features logos, a map of Africa, and a postage stamp for color.

envelopes or money to the bureau, 2) be patient, and 3) be patient.

You will seldom get your QSLs if you don't have an envelope or postage credits on file at your district QSL bureau. Your bureau is based on the number in your call sign, not where you live. WB2CHO/6 keeps postage credits on file at the 2nd district bureau.

Most district bureaus sell postage credits, a route often preferred by both bureau and DXer. You can find out the details of your own bureau's envelope credit system by sending an SASE to the bureau address, listed in the front pages of the *Callbook* or in *QST*. Generally, you send some money and your address, and they'll deduct postage as needed to mail your cards. When you run low, they'll note it on your return envelope.

Many bureaus prefer this method to receiving prepared envelopes, as they can buy standard envelopes in quantity, simplifying storage and reducing costs. Also, postage credits aren't outdated by a postage rate increase, and the QSL bureau finds it easier to keep the addresses and call signs up to date with postage credits.

If you choose the envelope route, be sure to follow the bureau's suggestions for preparation of your return envelope. Get

some 5" x 7½" envelopes and print your call sign *neatly* in the upper left corner. Put a single \$0.20 stamp in the upper right corner and print your name and address neatly in the center of the envelope. Send a few envelopes prepared this way to your correct bureau, and wait.

Don't hold your breath. Cards can take many months or a year just to work their way through the bureau system to you. And this doesn't include the time it took your card to get to the DX amateur or the time it took the DX station to get around to answering your card.

In the case of the Russian stations, through Box 88, Moscow, a delay of several years is commonplace. It is not unusual to find Russian QSLs for contacts made 3-7 years ago in the bureau.

After you work a station who promises to QSL "via the bureau," you might wait six months or a year for the card. While a new DXer eagerly awaits his first bureau shipment, he can reflect on why most Honor Roll DXers are old: It takes years to finally get some cards. Longevity is one of the most important DX skills.

What if you have sent off envelopes or money to the bureau, worked a bunch of DX, waited a very long time, and still have

nothing? Don't be afraid to drop a note to the bureau asking if you have any cards or asking them to mail any cards for you, no matter how few. Be sure to include an SASE for any reply, and be prepared to wait a few months while your envelope works its way through the system. And be nice; these are volunteers handling your cards, remember, and screaming that you have worked hundreds of DX stations and must have cards waiting won't help.

Ask politely if you have any cards waiting, and if so, would the sorter please mail them? On rare occasions, the sorter or bureau has a temporary problem, and your query might point it out. But more likely, the reason you haven't gotten anything back from the bureau is that the bureau has not received any cards for you!

Sorting the cards, putting them into the correct envelope, and mailing them takes even the "X" letter sorter a full day every month. Improper postage on envelopes costs the sorter about \$4.00 of his own money every month. Why does someone contribute so much time and effort to this nearly thankless task? Well, one reason is that the letter sorter gets first peek at the incoming cards and gets to pull his own out. "That's why I volunteered to sort the 'X' cards," our sorter says. "I get mine first!"

But this is not the *only* motivation of these hard-working volunteers. Some amateurs in the Washington DC area sort cards from a different call district. They'll never see one of their own cards first. These amateurs are more motivated by the thrill they help provide. The thrill when the ham eagerly rips open the envelope from the bureau to see what treasures might lie inside.

Receiving an envelope from your QSL bureau is like receiving an invitation to a treasure hunt. For the active DXer, each envelope from the bureau will contain at least one prize, and sometimes a whole handful of new ones arrives at once. Inside that little envelope could be those long-awaited Asiatic Russians, or that South American who swore he would QSL via the bureau. Or it might be returns of one's own QSLs, marked "callsign unknown," or SWL cards from countries most DXers would love to work.

So some volunteers work in the QSL bureaus because they know just how eager you are for your cards and just how happy you are going to be when you open that envelope. So think of the hard-working volunteers at the QSL bureau the next time you wait for your 7P8 QSL "via buro."

## NEW PRODUCTS

### CIRCULAR SATELLITE TECHNOLOGY FROM KLM


The new KLM 143-150-14C circularly-polarized antenna not only provides optimum reception of OSCAR satellite signals, but also can dramatically improve 2-meter terrestrial communication. Linearly polarized signals (any mode, fixed or mobile) are frequently affected by buildings, mountains, and movement and, as a result, circular wavefronts develop. Reception with the 14C reduces flutter fading and multipath distortion and often improves S/N ratios. Benefits of circular polarity on transmit are similar, regardless of the polarization of the receiving antenna.

Since circularity may have a right-hand or left-hand "twist," the 14C antenna kit includes a feedpoint-mounted switcher keyed by +9 to +15 V dc right from the shack. For single feedline convenience, a special

matching harness is included. If desired, the 14C can also function as two separately fed antennas, one vertical and one horizontal. Each set of feedpoints is equipped with a 2-kW balun ready for direct coax feed.

The 143-150-14C is built to provide years of reliable service. All aluminum is 6061-T6 and 6063-T832 alloys. All hardware is stainless steel except the U-bolts. The matching harness and balun coax features weather-imperious Teflon™ insulation and silver-plated conductors.

 With seven elements in each plane, the 14C produces 11-dB-dc gain at better than 1.5:1 vswr. Circularity is maintained within 3 dB. Virtually unbreakable 3/16" rod parasitic elements, anchored through the 1½" boom, help reduce weight to 7½ pounds, windload to 1.2 square feet. For more information, contact *KLM Electronics, Inc., PO Box 816, Morgan Hill CA 95037; (408) 779-7363.*



New KLM 143-150-14C circularly-polarized antenna.


### TEST ADAPTER

The new NLS Touch Test 20 test adapter for axial- and wire-lead electronic components has found a home with test engineers in test labs across the United States. Its popularity has caused Non-Linear Systems, Inc. to add this last test product to its accessory line of digital panel meter and digital test equipment line.

Measuring 1/2" by 2" by 5/8", the adapter has two slots on the side opposite the banana plus terminals, into which the leads of individual components may be inserted for component testing. The adapter eliminates the tedious task of applying prods and/or using test lead clips to make contact with the terminals of small components. Once the component leads are inserted, the testing becomes a hands-free operation, allowing for easier adjustment and control of the testing instrument. This method also eliminates the ambiguity introduced by lead or cable resistance. With banana-plug terminals 3/4" on center, the adapter can be used with any measuring instrument utilizing standard banana-plug receptacles with like separation.

This product is now available nationwide from local electronics distributors handling the NLS digital panel meter and digital equipments line of products.

 For additional information, write *Non-Linear Systems, Inc., PO Box N, Del Mar CA 92014.* Reader Service number 483.



Non-Linear Systems test adapter.

### NEW HAMTRONICS® CATALOG

Hamtronics, Inc., announces publication of their new 1983 catalog crammed full of goodies for the VHF/UHF/OSCAR enthusiast and two-way shops. The 36-page two-color catalog features many new products, including FM repeaters, new VHF and UHF FM receivers, helical resonator preamps and filters, low-noise receiver preamps, and a UHF receiver to listen to the space shuttle. Also included are the popular FM transmitters and power amplifiers, VHF and UHF receiving and transmitting converters, VHF transceivers, and other products Hamtronics has long been noted for.

For your free copy of this attractive new catalog (for overseas mailing, please send \$2.00 or 4 IRCs), call (716) 392-9430 or write to *Hamtronics, Inc., 65F Maul Rd., Hilton NY 14468.* Reader Service number 476.

### THE NEW MFJ-1440 VIDEO CONTROL CENTER

The new MFJ-1440 video control center combines enhancer, stabilizer, fader, switcher, distribution amplifier, and rf modulator to make professional-quality dubs and to give improved viewing quality of videotapes. You can make copies as good as the original, stop copyguard, improve sharpness, separate scenes, select from 4 inputs, and make 4 copies simultaneously. An rf modulator lets you monitor what you are taping or playing back on your TV set.

An Enhance control dramatically improves picture clarity, detail, sharpness, and increases contrast. You can actually see individual strands of hair and blades of grass.

An exclusive Logarithmic mode enhances light areas only for improving dark scenes.

A Noise Cancel control reduces picture noise exaggerated by enhancement.

Enhance before recording to cancel VCR and tape loss. Enhance during viewing to bring out detail and sharpness and to improve viewing of older tapes.

Enhancement can make viewing quality of 6-hour mode recordings comparable to 2-hour mode.

A bypass switch compares the enhanced with the unenhanced picture.

A Stabilizer control removes copyguard and stops picture roll and jitter. Play copy-

guarded tapes on any TV set. Duplicate any prerecorded tapes. Has stabilizer bypass switch.

The new Fader Design separates scenes, dubs out commercials, and cleans up edits and glitches for professional results. It has automatic and manual modes, simultaneous video and audio fade, continuously adjustable fade-out times, and audio dub jack for bypassing audio fade. The picture is in sync during fade.

The Video/Audio switcher adds convenience and eliminates messy cables. Select from 4 sources. (Connect VCRs, video disk, computers, games, video camera, etc.)

The Distribution Amplifier gives 4 video and 4 audio outputs for multiple recordings or monitoring.

The FCC-approved rf modulator converts video and audio signals to channel 3 or 4 for monitoring on your TV set.

The cabinet is eggshell white with walnut grain slides and measures 12 x 2 x 6 inches. The MFJ-1440 operates on 110 V ac or 12 V dc for portable use.

MFJ provides a 30-day money-back trial period. If you are not satisfied, you may return it for a full refund (less shipping). MFJ also provides a one-year unconditional guarantee.

For further information, contact *MFJ Enterprises, Inc.*, 921A Louisville Road, Starkville MS 39759. Reader Service number 480.

## DTMF RECEIVER KITS FROM TELTONE

Teltone announces the addition of two new DTMF receiver kits. These receivers will allow you to turn your telephone into a control device.

The TRK-927 contains the Teltone M-927 DTMF receiver and rotary dial pulse counter, a 3.58-MHz crystal, and a 40-pin DIP socket. The TRK-947 contains the M-947 DTMF receiver, a 3.58 crystal, and a 22-pin DIP socket. These units are packaged to simplify breadboarding by engineers, scientists, and hobbyists alike. Typical applications of these receivers include computer data entry, equipment monitoring and remote control, and central-office-quality DTMF-to-rotary conversion. Both kits are currently available.

For additional information, contact *Teltone Corp.*, PO Box 657, 10801 120th Avenue Northeast, Kirkland WA 98033; (206) 827-9626. Reader Service number 478.


## R-2000 COMMUNICATIONS RECEIVER

Trio-Kenwood has just announced the new R-2000, a highly sophisticated, all-mode communication receiver that covers 150 kHz-30 MHz in 30 bands. Designed to answer the needs of the shortwave listener as well as the radio amateur, this new radio is capable of receiving signals on AM, USB, LSB, CW, and FM. Among the more interesting features to be found on this model are digital vfo's, 10 memories that store frequency, band, and mode data, memory scan, programmable band scan, and dual 24-hour quartz clocks, with a timer that can be programmed to turn the radio on and off on a pre-selected schedule. Additional features include a built-in lithium battery memory backup (estimated 5-year life), fluorescent tube digital display, 3 built-in I-F filters with switch, manual "UP/DOWN" band scan, squelch, S-meter, noise blanker, and rf step attenuator. The R-2000 operates on 100/120/220/240 V ac or may be operated on 13.8 V dc using an optional DCK-1 cable kit.

For additional information, contact your local Kenwood amateur radio dealer or write *Trio-Kenwood Communications*, 1111 West Walnut Street, Compton CA 90220.



The MFJ-1440 video control center.

 

New receiver kit from Teltone.



R-2000 communications receiver from Kenwood.

## CONTACT-80/MARK II SYSTEM FROM ROYAL

Royal has announced the release of the Contact-80/Mark II RTTY and Morse system for the TRS-80. The system consists of an interface unit which will link the computer to the station equipment and the necessary software on either disk or cassette.

The interface will mate with any stand-alone terminal unit for use as a RTTY terminal, and the interface contains its own decoder and keying circuits when used on CW. The program will send and receive RTTY at 60, 66, 75, and 100 wpm, ASCII at 110 baud, and Morse at any speed. The Morse receive mode will automatically syn-

chronize its speed with that of the received code. The user may also change the decoding parameters to compensate for closely-spaced characters and machine-gun dots.

Contact-80 features a tri-split screen which shows received data, stored message numbers and text, and the transmitted message. The screen format may be easily changed for different uses.

The system also has MSO capability, a line printing spooler, automatic frequency monitoring, and a special mode to send and receive Basic programs.

For additional information, contact *Royal*, 407 Conkle Rd., Hampton GA 30228; (404) 946-9314. Reader Service number 477.

## SOFTWARE POLLUTION CONTROL

Electrical pollution drives micro programs bananas! Power-line electrical noise, hash, and spikes often cause erratic computer operation. In addition, severe spikes from lightning or heavy machinery may damage expensive hardware.

Many systems create their own pollution! Disks and printers often create enough electrical interface to disrupt an entire program. Nearby electronic equipment is affected as well.

Electronic Specialists' recently announced Magnum Isolator is designed to control severe electrical pollution. Incorporating heavy-duty spike/surge suppression, the Magnum Isolator features four individually quad-pl filtered ac sockets. Equipment interactions are eliminated and disruptive/damaging power-line pollution is controlled. The Magnum Isolator will control pollution for an 1875-Watt load. Each socket can handle a 1000-Watt load.

The model ISO-17 Magnum Isolator eliminates severe ac power-line pollution for smooth program operation.

For additional information, contact *Electronic Specialists, Inc.*, 171 South Main Street, PO Box 389, Natick MA 01760; (617) 655-1532. Reader Service number 481.

## HAL'S MPT3100 SOFTWARE EXPANSION FOR THE DS3100 ASR VIDEO TERMINAL

Hal Communications Corporation has announced the MPT3100 software expansion of the popular DS3100 ASR video terminal. The MPT3100 expands the features of the mailbox option and adds a separate mode for collection, editing, and relay of multiple message texts.

The MPT3100 package will store any length of message up to 32,000 characters in any format. Each file receives a sequential serial number ID, and a directory of stored files may be accessed. The messages may be edited after they have been stored by using the MPT3100's edit mode, which includes custom identifier codes for user designs.

The relay mode allows repetitive transmission of text, and transmission order is user-set, rather than in the order the text was received. Different texts may also be grouped for retransmission to specific geographic areas or stations.


The mailbox enhancements allow the user to edit while receiving or transmitting or during a mailbox access by an outside station. Added comments have also made the directory search and SDIR listing more useful tools for the mailbox user.

For more information, contact *Hal Communications Corporation*, Box 365, Urbana IL 61801; (217) 367-7373. Reader Service number 485.
 
## DTU-12 AMATEUR DATA DISPLAY FROM DOTRONIX

Dotronix, Inc., manufacturer of CRT displays, offers commercial-grade US-manufactured CRT displays for Morse-code translators, SSTV, ATV, or personal computer applications.

Get a clean, crisp computer-quality data display for your next ham project with a DTU-12 from Dotronix, available in kit, chassis, or chassis/ac power versions, and either P4 (white) or P31 (green) phosphor. The DTU-12 requires only 12 V at 1.5 Amps, standard TTL horizontal and vertical con-



DTU-12 display from Dotronix, Inc.

trol signals, and 2.5-V video drive. Scan rate is 15,750 Hz. Interface is through a 10-pin edge card connector.

These are brand new commercial-grade displays, factory adjusted for proper geometry and supplied with written specifications.

Dotronix, Inc., produces a complete line of compact and economical CRT displays, including 5-, 7-, 9-, 12-, 13-, 15-, and 17-inch sizes, in both chassis and kit configura-

tions. Dotronix displays are used in the computer terminal industry, medical instrumentation, automated phototypesetting, airline flight information, and closed-circuit television applications. The company maintains sales and service operations in Minnesota, Texas, and Illinois.

For additional information, contact Dotronix, Inc., 160 First Street SE, New Brighton MN 55112; (612)-633-1742 or (612)-633-8236. Reader Service number 479.



CES MD22 chip.

### NEW LOW-POWER DTMF MEMORY DIALER CHIP FROM CES

Communications Electronics Specialties, Inc., introduces the MD22 memory dialer chip, the only memory dialer in a single chip.

"We foresee a very broad range of applications for the MD22," CES President Ron Hankins remarks. "Its low power requirements and impressive capabilities lend it to quite a few types of communications systems." Component sales are available on the copyrighted chip, Hankins says.

No external RAM or tone generator is required with the MD22's unique design. This new proprietary chip actually operates off

telephone line power due to its CMOS technology. The MD22 features a ten-year memory backup with a single lithium cell.

Other features of the MD22 include: 10- or 22-number capacity, programmable pause, manual or automatic dialing, automatic redial of the last manually dialed number, and program inhibit input to avoid memory loss.

The MD22 is programmed and operated from a standard twelve-button keypad.

CES is offering qualified users a complete dialer for installation in any standard telephone for product evaluation. For complete information, contact Ron Hankins, CES, Inc., PO Box 507, Winter Park FL 32790; (305)-645-0474. Reader Service number 482.

## LETTERS

### DISTORTED NEWS

We are Americans who have made our home in Latin America for seven years. Lately, we are seeing much distorted news about the Americas coming out of the US and would like to set the record straight for 73 readers.

When we first moved to Costa Rica—bag, baggage, grandmother, teenagers, and pets—we spoke no Spanish and knew little about the country. But, soon, our rural neighbors accepted us and graciously taught us their language, their culture, and how a city-bred family could enjoy ranch life in a foreign land. Truly, our delightful adventures there merit a book, at least!

My husband's love for the sea (Pearl Harbor survivor, retired Navy) prompted a further move, two years ago, to Colombia's Caribbean coast. We found a lovely old coconut plantation on the Pan American Highway near Santa Marta, the oldest (457 years), most fascinating city in all of the Americas.

Imagine, green palms waving in gentle ocean breezes, blue sea and sky, pounding surf and golden sand, and, towering 19,000 feet over all and snow-capped the year 'round, majestic Mount Columbus. We feel we have much... incomparable beauty, fine neighbors, perfect climate, a stable democratic government, and a satisfyingly-low cost of living.

Like Columbus, we have discovered a new frontier with a vast potential and, being

human, are driven to tell others about our dream-come-true. If you are interested in the future of the Americas... and the Birds... write us by international airmail (35¢ a half-ounce) at PO Box 5222, Santa Marta, Colombia. It may take a while, but we promise to answer.

Now, from beautiful Santa Marta, we wish you salud (health), pesetas (wealth), amor (love), and the time to enjoy them all!

Juanita Bird  
Santa Marta, Colombia

### ICOM FOLLOW-UP

You may possibly recall that last June 19th I wrote to 73 to tell of my problem in trying to get some kind of response from Icom regarding a part I needed to repair a pair of Icom headphones that I have. You were kind enough to forward my letter to Icom's customer service manager, Tom Snellings. He, in turn, promised to get the part to me even if it was necessary to go to the factory for it.

As it turned out, this particular part was not available separately and Icom offered to exchange my set of phones for a new one. I naturally accepted their offer, which was more than I expected. If Icom had told me that the part was not available, I would have "jury rigged" something and would have settled for that.

What disturbed me was the complete lack of response. What I suspect happened was that some employee discarded my let-

ters when they found that the item was not available. Of course, this is conjecture on my part, but I have that feeling.

The main purpose of this letter is to thank you and to let you know the way Icom followed up. Once again, thanks very much for your help.

Sam Zolick KB2UH  
Howard Beach NY

### FIST OR PHONE

Before all the stuffed shirts bury amateur radio and drive off all the young talent, how about developing a license that has either code or phone privileges or both? In other words, one can work CW on that portion of the band if one has the necessary license endorsement. You may work someone on the phone portion of the band if you have the phone endorsement. An amateur may work both modes if he or she has passed the tests for both endorsements. This is a simple solution which should satisfy everyone.

I foresee that if the "code establishment" continues to thwart some type of compromise like the one I have mentioned, then you can say "good-bye" to the recruitment of many bright young men and women into amateur radio.

Robert Baker KA1JDD  
S. Yarmouth MA

### THANKS TO BASH

I feel I must take exception to the editorial regarding Dick Bash and *The Final Exam* in your November, 1982, issue.

About four years ago I decided to get my General license after dutifully working my fingers to the bone for two years in the

Novice bands. On advice from our local electronics store, I selected the Ameco Amateur Radio Theory Course and proceeded to study like hell for the next three months while working with the ARRL code tapes to bring my speed up to a solid 13 wpm.

In the Ameco book I took and passed every single test and when I went down to the dear old FCC, I got the surprise of my life. Although I passed the code with ease, the whole damn written test was on UHF; ergo, three months wasted. To hell with it—I quit ham radio!

I packed my TS-820 away and found another hobby (this is a hobby).

Per chance, about two months ago, I wandered into our local electronics store and there on the shelf was Bash—B.S., I figured, but what the hell—I bought it anyway. I dug up the ARRL code tape (why don't you pick on them?) and got my code back up and passed both with ease. I am now working on the Advanced, thanks to Dick Bash.

Since you chose to come down hard on Dick and CQ, I feel it is only fair for me to advise that this is the first and last 73 I will purchase. By the way, you may be interested in knowing that my former call from the 1950s was K6DDC (General class) so I am not exactly unfamiliar with amateur theory.

Scott Smith KH6JKX/HL  
Kaneohe HI

P. S. Print this in your rag sheet if you want to.

Scott, lacking much in the way of letters protesting the Bash approach to licensing... which you endorse... perhaps that is the way to go. But I honestly think it is stupid to even ask anyone to bother with a written test at all under these conditions. There seems to be strong sentiment for letting in any dummy who can copy the code. So, how about it, shall we go this route and

Don't Be Left Out in the Cold with the Russian Woodpecker

# GET A MOSCOW MUFFLER™

Another first from AEA. The Woodpecker Blanker, WB-1 really works. This unit effectively blanks the pulsing interference of the Russian Woodpecker. Two versions are available, the WB-1 for use with communication receivers and WB-1C for use with all popular transceivers.



This extremely useful accessory is designed for direct insertion between your receiver (or transceiver) and the antenna. It is both MORE EFFECTIVE than I.F. type blankers and requires NO MODIFICATIONS to your receiver! The unit operates from a 13 VDC ± 2 VDC power source at less than 575 mA. (AEA AC wall unit AC-1 will operate the blanker.)

The blanker works well on both CW and SSB modes that are being interfered with by a woodpecker. Controls on the front panel include; four push button switches, a synchronize control and a width control. The WB-1 also features a low-noise untuned broadbanded 6 db gain pre-amp which can be selected with or without the blanker enabled. The WB-1C uses the same circuitry but includes a carrier operated relay (COR). This provides protection to the receiver section during transmissions from the attached transceiver.

Prices and Specifications subject to change without notice or obligation.

**ege, inc.** ✓453

13646 Jefferson Davis Highway  
Woodbridge, VA 22191

(703) 643-1063: Information and Virginia calls.

1-800-336-4799: orders only.

**AEA** Brings you the Breakthrough!

## PRESERVE 73 MAGAZINE BINDERS & FILE CASES

Keep your issues of 73 Magazine together, handy and protected in handsome and durable library files or binders. Both styles bound in red leatherette with the magazine logo stamped in gold.

Files: Each file holds 12 issues, spines visible for easy reference. \$5.95 each, 3 for \$17.00, 6 for \$30.00

Binders: Each binder holds 12 issues and opens flat for easy reading. \$7.50 each, 3 for \$21.75, 6 for \$42.00

(Postage paid in USA. Foreign orders include \$2.50 per item)

Please state years: 1977 to 1983

Send check or money order to:

JESSE JONES BOX CORP.

P.O. Box 5120

Philadelphia, PA 19141

Allow 4 to 6 weeks for delivery

## CONTACT-80...



RTTY your TRS-80 with CONTACT 80 MARK II for 1983!

TRS-80, MOD III INTERFACE (included with system) gives keyboard STATION CONTROL and connects with the TTY TU of your choice.

(No other equipment needed for CW operation)

### Cassette & Disk Features:

- BAUDOT, ASCII & MORSE
- CW RX speed AUTOSYNC & unique FIST-FIXER
- TRI-SPLIT screen (user sets HIS way)
- "Unlimited" STORED MSG. sizes
- Automatic DYNAMIC BUFFER ALLOCATION
- Live HARDCOPY plus other Line-printing
- AUTO-ID, TIME/DATED transmissions
- On screen "OSCILLOSCOPE", CLOCK, COUNTERS
- Unique EDITOR, LOCKED-KEYING, NAME-LINE
- AUTO-DIDDLE, K/B ROLLOVER, REPEATING KEYS
- Fast CASSETTE I/O and many other features

### Additional Disk Features:

- Two-way message SELCALL. A "PERSONAL MSO"
- AUTO-MONITOR frequency activity to disk
- SAVE, LOAD, KILL & DIR plus other I/O

### INTRODUCTORY SPECIAL

DISK VERSION \$199.00

CASSETTE VERSION \$179.00

CASSETTE, later upgrade to DISK \$20.00

Guaranteed-include Amateur CALLSIGN-POST PAID

### ROYAL

407 Conkle Road ✓150  
Hampton, GA 30228 Telephone: (404) 946-9314

## NICAD MEMORY ERASE - WHAT??

- Complete automatic operation
- Erases - Charges - Checks
- Rapid charges in 35 min. (typically)
- Automatically repairs shorted cells
- No dangerous heat build up
- Front panel selects up to 3 different packs
- Unlimited battery combinations with program modules (user programmable)
- LED status indicators
- Supplied with universal EZ hook wire leads

Specify Voltage of Battery Pack(s) with order.

**\$79.95 plus \$3.00 Shipping**

(PA Residents add 6% sales tax)

Coming Soon - Multiple pack memory erase charger for municipal commercial applications - write for information or send requirements.



The GMS 401 is a complete automatic NICAD conditioner and rapid charger. Never before has this been offered anywhere at any price and it's so good it's being patented. NICAD memory characteristics must be dealt with otherwise your battery pack is not delivering all it could. The GMS 401 will automatically erase and rapid charge any type NICAD pack from 1 to 10 cells automatically.

CONTROL PRODUCTS UNLIMITED, INC.

P.O. Box 10, Downingtown, PA 19335

215-383-6395 ✓190

## NEMAL ELECTRONICS COAXIAL CABLE SALE

This Month's  
Specials  
Same Day  
Shipping

### POLYETHYLENE DIELECTRIC

RG213 noncontaminating 95% shield mil spec. 36¢/ft.  
RG174/U mil spec. 96% shield. 10¢/ft.  
RG11U 96% shield. 75-ohm mil spec. 25¢/ft.  
RG8U 96% shield, mil spec. \$27.95/100 ft. or 31¢/ft.  
RG6A/U double shield, 75-ohm 25¢/ft.  
RG58A/U stranded mil spec. 12¢/ft.  
RG58 mil spec. 96% shield. 11¢/ft.

### LOW LOSS FOAM DIELECTRIC

RG8X 95% shield (black, white or gray) \$14.95/100 ft.  
17¢/ft.  
RG8U 80% shield. 18¢/ft.  
RG58U 80% shield. 07¢/ft.  
RG58U 95% shield. 10¢/ft.  
RG59U 100% foil shield, TV type \$7/100 ft. 10¢/ft.  
RG8U 97% shield 11 ga. (equiv. Belden 8214) 31¢/ft.

Rotor Cable 8-con. 2-18 ga. 6-22 ga. 19¢/ft.

RG8U-20 ft., PL-259 ea. end. \$4.95  
RG214U dbi silver shield, 50 ohm \$1.35/ft.  
100 ft. RG8U with PL-259 on each end \$19.95  
BELDEN Coax in 100 ft. rolls  
RG58U #9201 \$11.95  
Grounding strap, heavy duty tubular braid  
3/16 in. tinned copper 10¢/ft.  
3/8 in. tinned copper 30¢/ft.

### CONNECTORS MADE IN USA

Amphenol PL-259 79¢  
PL-259 push-on adapter shell 10/\$3.89  
PL-259 & SO-239 10/\$5.89  
Double Male Connector. \$1.79  
PL-258 Double Female Connector. 98¢  
1 ft. patch cord w/RCA type plugs each end 3/\$1.00  
Reducer UG-175 or 176 10/\$1.99  
UG-255 (PL-259 to BNC) \$3.50  
Elbow (M359) \$1.79  
F59A (TV type) 10/\$2.15  
UG 21D/U Amphenol Type N Male for RG8 \$3.00  
BNC UG88C/U, male \$1.25  
3/16 inch Mike Plug for Collins etc. \$1.25  
UG273 BNC to PL-259 \$3.00

### FREE CATALOG

COD add \$1.50—FLA. Res. add 5% Sales Tax

Connectors—shipping 10% add'l, 2.50 minimum ✓412

Cable—shipping \$3.00 1st 100 ft. \$2.00 each add'l 100 ft

1327 NE 119th Street, Dept. RLO, No. Miami, FL 33161 Call (305) 893-3924

just do away with anything but the ability to sign a name and copy code? Or is that signing the name too much to ask? Oh, about your ability to cope with the theory... the 50s?... have you opened a radio recently?—Wayne.

## CW IS FUN

You keep insisting that SSB can get through every bit as well as CW. Well, this summer during a sked with AAQP, conditions deteriorated on 20m SSB, due to QRM and QSB, until I could not copy AAQP anymore. However, when we resorted to CW... Q5 copy! CW has a place.

Yes, RTTY is faster and more efficient. Yes, CW is slow. Yes, ASCII is the way to go. But I don't operate CW because I think CW is efficient or easy to receive or because of the "tradition." I like CW because it's fun. Isn't that why a lot of us got into this?

Bob Reynolds KB9MU  
McHenry IL

P. S. I'm not an old-time CW operator. I'm 29 and I also enjoy SSTV and RTTY.

*Yep, Bob, there are times when CW can get through... and there are times when SSB can't be beat. No emission is best all the time... as yet. I suspect that when we put our minds to it, we will be able to come up with some sort of machine-readable transmissions which will be virtually jam-proof and which will go right on through interference, static, fading, and so on. That's a good challenge. Meanwhile, I agree that CW can be fun and should be accepted because it is fun—not because there are people who want to force it on you.—Wayne.*

## RICH HERITAGE

Come on now, Wayne. Let's be realistic about this second language thing (73, November, 1982). You and I are savvy enough folks to know that the language of the ruling tribe is the language of the common little folks who live outside the castle gates. And the last thing the little guy wants is trouble with the rulers.

The language you and I speak would be a lot closer to Frisian or Dutch, were it not for the victory of some francophone Vikings at Hastings in 1066. And those same francophone Vikings might have ended up speaking a form of Gaelic, had not the Romans overrun Gaul some centuries earlier. (And had not the Gauls been chased into western Europe by the Slavs and Germanic tribes, our language would be closer to Basque—well, maybe.)

The fact remains that languages change, as do politics and economics. America is not so much a melting pot as it is a mulligan stew. By and large, we are the cultural descendants of herds of people, from Athabaskan and Algonquin, through Spaniard and Anglosaxon, to Oriental and African. We are the cultural descendants of any group which has dragged or been dragged up on these shores.

These people—our cultural and linguistic forebears—deserve their rich heritage. Keeping this heritage alive in non-English-language press and media is not some heinous crime against "us." Rather, it would be far more heinous to ban these non-English media forces. The thought of banning such publications and media forces conjures up visions of some multi-media Kristallnacht. It won't hurt us at all to reach out to our fellow man, even if he doesn't speak our language as nicely as we think he should.

But this of course is a two-way street. We

should indeed have a populace which speaks one language. To do that, we need to give the non-English speakers a reason to join the rest of us "anglos."

I can think of no better reason for the rest of us, who presumably speak English, to exorcise our prejudices, whether racial, sexual, religious, political, or linguistic.

Nils R. B. Young WB8JN  
New Carlisle OH

## CB OR HAM?

A letter to you has been in limbo for some time now, but I just came across something which is really disgusting and an absolute insult to amateur radio.

While sitting here working on my antenna tuner and listening to the last few fading signals of 15 meters, I had an idea to drop my R4C down on 11 meters to hear what was going on. Brother, was that a mistake. Man, did I get hot!

On 27.395, at least the frequency was legal. I found a couple of CBers discussing their rigs. Let me see, Woody, in Trenton, has a Tempo transceiver, a ground-mounted vertical, and a set of "moon rakers." Harold has a ham rig that has great ears and a keyer that does great at 25 wpm! Wow, a CBER who can send and copy 25 wpm... a prime candidate for a ham ticket, right? Wrong. Come to find out, these turkeys were amateurs, I think, down on 11 with their ham rigs. Oh, yes, they did ID, naturally with their "callsigns" Mercury 5119 and Mercury 927, I believe. Come to think about it, these guys may have been doing this for a couple of years; I believe I have heard them before.

It is really sickening to hear these guys. Man, are they doing a great job of public relations for all of us amateurs in this area. To them, all we are is glorified CBers. That's the pits!

As you can probably tell, I am a new amateur. My ticket is just 6 months old and my pride has really gone to my head. It really gets my goat when I hear some of the stuff so-called amateurs are putting out on the air. They seemingly have no remorse for their behavior.

Turkeys or not, I am proud of amateur radio and of being an amateur radio operator. I will defend its principles and ideals until I am blue in the face. Just believe me though, this enthusiasm will be turned loose on these two if they keep it up!

On a lighter note, I have worked all states and 41 countries. Not bad for a mobile antenna on a balcony, is it? Thanks for listening.

Jerry Rogers KA8PTL  
Monroe OH

*Jerry, It is unlikely that those chaps were actually amateurs. Zillions of CBers bought ham rigs a few years ago and had them converted for 11 meters. As a matter of fact, a couple of our very large ham dealers made quite a business of making those conversions because CBers paid full price for rigs with no questions asked while hams would do virtually anything to save \$10 on the purchase... so they sold CBers first and we got what was left over. With the fading interest in HF operating, as the frequencies above the 40 CB channels were called, hams have been able to buy ham rigs again. There is still activity on the HF band, but it is a shadow of what we were hearing ten years ago. The FCC has never shown any serious interest in trying to shut down this illegal activity, so it has indeed been going for many years relatively unimpeded. There was a time when hams were screaming that these hordes of CBers were going to invade the ten-meter band, but it never really happened. I didn't think it would and said so at*

*the time, but that was not a popular way to think then. Come to think about it, I always seem to be out of step like that.—Wayne.*

## EDUCATION

Here I go again, penning my second letter. Many of your ideas are echoes of my feelings, and further discussion would be redundant. Some of your ideas go contrary to my feelings, but thank goodness we are all different, and I am sure you get plenty of feedback. One topic which you hit on in your Never Say Die (Never Spend a Dollar?) column that I must respond to is education.

Your September NSD column stated, among other things, that the school system is set up so as to virtually guarantee failure as far as making any real money is concerned. How you reach this conclusion is questionable, but I have a more important query: What can be done to change this?

My wife and I are both teachers (as well as hams). Karen works with learning-disabled children and I have a sixth-grade classroom. What are your thoughts on how to instill that desire of success with students who do not care? Any ideas would be welcomed.

The Whiteside Amateur Radio Club, which I sponsor, recently purchased your code series cassettes and the kids seem to be learning the code better than when I send it on an oscillator.

Thanks for any suggestions a teacher could use, and keep on plunking away at what you feel is right concerning amateur radio, politics, or whatever.

Carl J. Buehler WB9ZAJ  
Belleville IL

*Sure, Carl, whenever I discuss a problem I try to offer a solution to it. In the case of education, I noted that our colleges are geared towards training kids to work in the three proven areas for non-wealth... large corporations, government, and teaching. Once we recognize that the easiest way to make money is to be an entrepreneur, we can see the need for schools which teach kids how to be entrepreneurs. My aim is to set up a pilot-program college which will teach the fundamentals of electronics and computers, and then all of the business courses which are needed if one is going to successfully run one's own business or manage a business. In order to keep the cost down and also to provide the best possible teaching in the shortest time, the college will work hand-in-hand with a group of on-campus businesses with which the kids can get practical professional experience in advertising, sales, accounting, marketing, legal problems, production lines, technical developmental work, and so on. Between practical college courses and actually working at business, the students will be ready to go to work and be of value the day they graduate.—Wayne.*

## DX JUNKIES

I am calling for help as a battered, insulted, and reviled ham who has the misfortune to be "nearby DX" to hundreds of thousands of frantic thoughtless hams. At present, I seem to be the only active ham in the US Virgin Islands on CW.

It's almost impossible to keep a schedule with some old friends with dozens of hams cramming the frequency calling me. For what? The stupid endless waste of time known as 5-band DXCC. These misguided souls are frantic, like a bunch of starving junkies with their fix being my QSL card.

I have been an active ham since 1928

(W2AIS—'28-'51, KH6ARA—'51-'59, and KV4CI—'60 until the present). I am now retired and own my home, 6/10 of an acre, and a big active Labrador retriever. I have barely enough time to keep up with domestic chores let alone reply to a flood of QSL cards.

When we were young, it took a QSL card to convince people that we really talked to the Far East or Iowa. Now, if you can't work DXCC in a few weeks, your antenna is no good.

For the past few weeks, I have endured insults, jamming, and vicious gossip. One morning, I heard a ham chide another working me by asking, "Why do you QSO that bastard? He doesn't QSL." My God! This is supposed to be a hobby, not a dogfight.

Though I had notices published in RSGB's *Radio Communication*, the JA magazine, and CQ telling of my intention to cease QSLing, the cards still pour in. When a ham asks me if I QSL and I tell him I don't, he will send me begging letters and homemade QSLs especially designed for my signature. Add to that dollar bills and countless IRCs. I could make a good side income on the dollar per QSL route, but that is not ham radio. Yesterday, I had to stand in line for a registered letter, and the Christmas lines are long. It was a registered, return letter from a JA ham. I added up the stamps plus the IRCs, and it exceeded \$5! The worst aspect of this whole mess is what I call the "bang-bang thank you ma'am" type which is "ur 599 pse ur QSL ino."

Wayne, you have clout and your editorials are read widely. Though I detest the whole QSL mess, I would cooperate by answering a "yes/no" printout for QSO claims. Why don't these crazed fanatics get together and have a master computer to handle it? God knows they spend multi-thousands of dollars on ham gear. Why not set up a "DX info center," hire help, buy software, and charge the applicants a yearly fee for the service? It could be done now.

If they did, the overloaded post office would be thankful and innocent victims would be relieved of the foul filth being spewed out by a deranged minority of DXaholics.

It is a timely topic for a "good Green tirade" to help these misguided souls regain some perspective as to what ham radio is meant to be—fun, not misery.

H. Miller KV4CI  
St. Thomas, Virgin Islands

*Sorry, OM, there is no escape from DXCC and its SBDXCC extravaganza... plus the (dis)Honor Roll. This is an ARRL-made nightmare which makes life miserable for all hams in relatively rare DX countries. Of course, being within contact range of the entire US all of the time, you get the very worst of it. One of the reasons so many countries are rare is that the DXers drive any new ham off the bands as quickly as they can with demands that no contacts be over a few seconds long... and that the ham in the rare country devote his life to the unending pile of DXers. Even if a ham in one of these countries could work every single DXer just to get it over with, within two days he would be piled up again with chaps just piling on the heaps to prove they can get through. I'm sure we all really love the guy with the multi-kilowatt and big beam who gets a rare one and thanks him for the instant contact a few days ago... 73. OM, there is no answer to your problem that I know of. The ARRL certainly is not going to cancel DXCC just because it ruins the hobby for ops in 250 countries... and even if they did, there would be a replacement award within seconds to keep the pileups shrieking. Say, have you thought of moving to Florida?—Wayne.*



# Be a Shooting Star

## with these out-of-this-world programs from Instant Software.



### COSMIC PATROL

Do unto the Quelons before they do unto you. But you must be accurate—every shot you take uses precious units of your limited energy supply. Fast action, optional sound and great graphics! Arcade. Joystick optional.  
TRS-80<sup>®</sup> Tape Mod I & Mod III Sound Option 16K  
#0223R \$19.95  
TRS-80 Disk Mod I & Mod III Sound Option 16K #0224RD \$24.95

### BALL TURRET GUNNER

Fight back against the Petro Giants that threaten your existence! Maneuver your laser cannon and gun down the elusive gnat ships. . . If you can. Fast action in an interstellar battle. Arcade. Sound. TRS-80 Tape Mod I & Mod III 16K.

#0051R \$14.95



### JET FIGHTER PILOT

Takeoff, intercept the enemy, return to the base or carrier and land safely. This is as close to real combat flying as you can get without pulling G's. A challenge you'll never outgrow, that only the best can master. Simulation. TRS-80 Tape Mod I & Model III 16K.

#0159R \$14.95

### DANGER IN ORBIT

Only nerves of steel and lightning reflexes will enable you to blast the alien ships and destroy the hurtling asteroids. But watch out—those asteroid fragments can destroy your ship! Arcade. Sound. Joystick optional. TRS-80 Tape Mod I & Mod III 16K.  
#0237R \$19.95  
TRS-80 Disk Mod I & Mod III 16K 0247RD \$24.95



### ALIEN ATTACK FORCE

Earth's defenses are dead. You're the last hope for the planet as hundreds of armed invaders begin their final assault. Nine levels of difficulty separate the survivors from the boys. Arcade. Joystick optional. TRS-80 Tape Mod I & Mod III 16K.

#0240R \$14.95

### SPACE SHUTTLE

Experience the ultimate flight as you command the next launch, orbit, re-entry and landing of the U.S. Space Shuttle Columbia. An incredibly accurate simulation. The next best thing to being there! TRS-80 Tape Mod I & Mod III 16K

#0332R \$19.95



## Instant Software The best software under the sun . . . and beyond.

### YES! I WANT TO BE A SHOOTING STAR!

Send me:

___ copies of 0240R @ \$14.95	___ copies of 0223R @ \$19.95
___ copies of 0159R @ \$14.95	___ copies of 0224RD @ \$24.95
___ copies of 0051R @ \$14.95	___ copies of 0332R @ \$19.95
___ copies of 0237R @ \$19.95	___ copies of 0247RD @ \$24.95

VISA

Amer. Ex.

MasterCard

Check/money order

Please add \$2.50 for postage & handling.

## Instant Software



CARD NO. \_\_\_\_\_

INTERBANK # \_\_\_\_\_ EXP. DATE \_\_\_\_\_

SIGNATURE \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_


333B6S

Call toll free: 1-800-258-5473

Rte 101 and Elm St., Peterborough, NH 03458

\*TRS-80 is a trademark of the Radio Shack Division of Tandy Corp.

# THE SELECTRIC™ INTERFACE

 

## Daisy wheel quality without daisy wheel expense.

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. *The Selectric™ Interface*, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Microcomputing* magazine's popular "Kilobaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer.

*The Selectric™ Interface* includes:

- step-by-step instructions
- tips on purchasing a used Selectric™
- information on various Selectric™ models, including the 2740, 2980, and Dura 1041
- driver software for Z80, 8080, and 6502 chips
- tips on interfacing techniques

With *The Selectric Interface* and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.

Credit card orders call TOLL-FREE 1-800-258-5473. Or mail your order with payment plus \$1.50 shipping and handling to: Wayne Green Inc. Attn: Retail Book Sales, Peterborough, NH 03458.

Dealer inquiries invited.

ISBN 0-88006-051-4

128 pages

**\$12.97**

Yes, I want **Selectric Interface** (BK7388). Enclosed is \$12.97 per copy plus \$1.50 for shipping and handling.

MASTER  VISA  AMEX

Card # \_\_\_\_\_ Expires \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State and Zip \_\_\_\_\_

All orders shipped UPS if complete street address is given.

333B6S

## Make A Name For Yourself In Technical Publishing.

**Wayne Green Books** announces a June 1, 1983 deadline for submitting manuscript proposals for the upcoming publication list. Ideas for book-length manuscripts about any microcomputer system or area of electronics will be considered. In addition to payment and royalties, we offer our distribution channels and the marketing support your book deserves.

Send proposals or requests for a copy of our *Writer's Guide* to: Editor, Wayne Green Books, Peterborough, NH 03458. Or call toll-free 1-800-258-5473.



MAKE IT  
EASY  
TO  
SAVE



your copies of  
**73 Magazine**

Your magazine library is your prime reference source—keep it handy and keep it neat with these strong library shelf boxes. They are made of white corrugated cardboard and are dust resistant. Use them to keep *all* your magazines orderly yet available for constant reference.

Self-sticking labels are available for the following:

80 Micro	73 Magazine	Radio Electronics
Microcomputing	QST	Personal Computing
inCider	CQ	Byte
Desktop Computing	Ham Radio	Interface Age

One box (BX1000) is \$2.00, 2-7 boxes (BX1001) are \$1.50 each, and 8 or more boxes (BX1002) are \$1.25 each. Be sure to specify which labels we should send.

Call TOLL-FREE for credit card orders:  
**1-800-258-5473**

Or use the order form in this magazine and mail to:

**73 Magazine**

Attn: Book Sales, Peterborough, NH 03458

SHIPPING AND HANDLING CHARGES \$2.00 per order

# Turn your computer into an advanced operating system . . .

The Best Utilities Available from Instant Software for your TRS-80\*

- Enhance
- Accelerate
- Expand

**SUPER UTILITY PLUS** The most powerful program of its kind! Machine language, stand-alone program with its own I/O routines. No ROM or DOS calls. Works on single AND double density systems. Features ZAP, PURGE, FORMAT, DISK COPY, TAPE COPY, DISK REPAIR, MEMORY, FILE, and CONFIGURE SYSTEM functions. Very sophisticated, menu driven, single RAM resident program! A must for every serious TRS-80 disk installation.


48K RAM Model I & III Disk

**DOSPLUS 3.4** The fastest, smoothest, easiest to use Disk operating system for your TRS-80! Jam-packed with powerful options: BASIC Array Sort, Tape/Disk—Disk/Tape Utility, Controlled Screen Input, Random Access and ASCII modification on Disk/Dump, BASIC Checks for Active "DO", Backup and Format from a "DO" file, and much much more. Energize your operating system with DOSPLUS 3.4!

TRS-80 2 for Model I, 1 for Model III Disk



The best software under the sun.

 

**KEY COMMANDER** Easy editing of programs, and direct entry of graphics into Basic programs are yours with this highly sophisticated yet easy to use utility package. Features On Screen Editing, Graphic Print Statement, Assignable Keys, and Total Flexibility. Automatically relocates into high memory and protects itself in memory. Enhance the power and capabilities of your keyboard!

Model I/Model III 16K and up Tape

**ABE Accelerate** your writing and editing of Basic programs with the Advanced Basic Editor. Dramatically improves your Basic editing and programming capabilities by providing such indispensable features as Formatted Screen, Global Search and Replace, Line Copy Ability, Assignable Keys, Called From Basic. Advance your skills as a programmer with ABE.

Model I 32K TRSDOS 2.3 or NEWDOS 80 v2 Disk in 32K & 48K version.

To place your order for Instant Software's Utility Programs, call toll free 1-800-258-5473

or simply fill in the coupon and mail to:

INSTANT SOFTWARE, Rte. 101 & Elm St. Peterborough, NH 03458

TRS-80 is a trademark of the Radio Shack division of Tandy Corp.

Yes I want to order:

- |  |   |
|--|---|
| <input type="checkbox"/> ABE #5026RD @ \$19.95 ea.               | <input type="checkbox"/> Dos Plus 3.4 Single Density #5023R @ \$149.95 ea.    |
| <input type="checkbox"/> Key Commander #5027R @ \$29.95 ea.      | <input type="checkbox"/> Dos Plus 3.4 Double Density #5024RD @ \$149.95 ea.   |
| <input type="checkbox"/> Super Utility Plus #5022RD @\$74.95 ea. | <input type="checkbox"/> Dos Plus 3.4 Mod III Version #5025RD3 @ \$149.95 ea. |

Shipping & Handling \$2.50

For C.O.D. orders add \$1.50 extra Total of above \_\_\_\_\_

VISA  MC  AE  Check  Money Order

Name \_\_\_\_\_ Card # \_\_\_\_\_

Address \_\_\_\_\_ Interbank # \_\_\_\_\_

City \_\_\_\_\_ Exp. Date \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Signature \_\_\_\_\_



Call toll free 1-800-258-5473

INSTANT SOFTWARE, Rte. 101 & Elm St. Peterborough, NH 03458

333B6U

# MAKE SAVING MONEY A WAY OF LIFE

With **LIVING ON A SHOESTRING**: A Scrounge Manual for the Hobbyist. Almost anything you find can be put to good use if you follow the techniques of a master scrounger. George Ewing shows you how to:

- Find electronic parts
- Scrounge by the rules
- Scrounge a vehicle
- Locate tools and other surplus
- Read up on scrounging
- Scrounge a place to live

Cartoons and case histories of scroungers add a humorous touch. With **LIVING ON A SHOESTRING**, you can't always get something for nothing, but you can certainly get it for less.

\$7.97 Softcover, 7 x 9, 128 pp. approx.,

ISBN 0-88006-059-X

Call TOLL FREE 1-800-258-5473 for credit card orders. Or mail your order with payment or complete credit card information. Include \$1.50 for shipping and handling. Send to:

Wayne Green Inc.  
Attn: Book Sales  
Peterborough, NH 03458

A Wayne Green Publication

Dealer Inquiries Invited



## YES, I want to scrounge!

Send me \_\_\_\_\_ copies of **LIVING ON A SHOESTRING**. Enclosed is \$7.97 (BK7393) per copy plus \$1.50 shipping and handling.

MASTERCARD bank # \_\_\_\_\_  VISA  AMEX  
Card # \_\_\_\_\_ Expires \_\_\_\_\_  
Signature \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State and Zip \_\_\_\_\_ 333B6L

# MOVING?

Let us know 8 weeks in advance so that you won't miss a single issue of 73 Magazine.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

**73 magazine**

Subscription Department  
P.O. Box 931  
Farmingdale NY 11737

- Extend my subscription one additional year for only \$19.97  
 Payment enclosed  Bill me

Canada and Mexico \$22.97, US funds, Foreign Surface \$39.97; US funds, drawn on US banks, Foreign Airmail, please inquire.

*If you have no label handy, print OLD address here.*

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

*print NEW address here:*

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

333R6M

Dealers...  
**BELL**

Selling 73 Magazine will make money for you. Consider the facts:

**Fact #1:** Selling 73 Magazine increases store traffic—our dealers tell us that 73 Magazine is the hottest-selling amateur radio magazine on the newsstands.

**Fact #2:** There is a direct correlation between store traffic and sales—increase the number of people coming through your door and you'll increase sales.

**Fact #3:** Fact #1 + Fact #2 = INCREASED SALES, which means more money for you. And that's a fact.

For information on selling 73 Magazine, call 800-343-0728 and speak with Ginnie Boudrieau, our bulk sales manager. Or write to her at 73 Magazine, 80 Pine St., Peterborough, NH 03458.

**73 MAGAZINE**

80 Pine Street Peterborough, NH 03458

800-343-0728

**TIME-DUAL TONE DECODER \$15**

The LJM2RK decoder kit converts your receiver into a special receiver or control. When a user-selected time-tone combination is received, the output provides a relay control for activating speakers or other devices.

INPUT: Audio from transceiver, scanner, etc.  
OUTPUT: SPST (N.O.) relay.

FEATURES: Single or dual tones adjustable over the T/T range • Adjustable time delay • Relay output • Manual or auto reset • Single tone ON latching with different single tone reset OFF • Operates on 12VDC • Interfacing of multiple boards for multi-digit sequential activation and reset.

APPLICATIONS: Call-up system • Repeater or commercial controls • Etc. limited only to your imagination • Write for information on the LJM2RK for your application.

LJM2RK decoder kit includes all component, relay, and P.C. Board...\$15 plus \$1.50 ship

LJM2RC enclosure kit includes molded case, speaker, input cable.....\$5 plus \$1.50 ship.

THE METHENY CORPORATION  
204 Sunrise Drive, Madison, IN 47250 ✓205

See Product Review Jan. 1983 issue of 73

**NEW!** **DDRR Space Beaters!**  
*The Repeater Beaters*

- With as little as one square foot of ground plane, these unique antennas provide communication from virtually anywhere.
- Low SWR match to a 50 ohm line across the entire band.
- Magnetic mount included.
- **Two antennas in one** when used with the optional CR2X or CR3X range extender.

CR2A\* of CR3A **\$39** plus **\$2** shipping

CR2X or CR3X **\$12** plus **\$2** shipping  
(continental USA)

\*AS REVIEWED IN 73 MAGAZINE OCTOBER 1982

**COM-RAD, INC.**  
1635 WEST RIVER PARKWAY  
GRAND ISLAND, NEW YORK 14072  
(716) 773-1445

Visa and MasterCard accepted ✓163

M/C Visa **\$129.95**

**NEW! HF WATTMETER**

- Digital Resolution (0.1 or 1 Watt)
- Wideband (160 through 10 meters)
- Wide range (ORP to 1999 Watts)
- Detachable (RF Sampler un-plugs)
- Battery Saver turns off minutes after RF disappears
- Price includes—Readout, HF Sampler, battery, VSWR nomogram and complete schematics.
- 90 day warranty ✓219

write or call:  
e-tek P.O. Box 625, Marietta, OH 45750  
1-(614)-374-2280

**"KEEP IN TUNE WITH THE WORLD"**

**\*\*TECHNICAL ASSISTANCE BY F.C.C. LICENSED TECHNICIANS:**

- repairs
- alignments
- modifications
- installation of custom circuits

**\*\*PRODUCTS AVAILABLE:**

- QSK keying
- VOX
- Power supplies—[memory keep alive]

\*All above circuits for solid state equipment manufactured by

12325 Madonna Dr. Lansing, Michigan 48917  
(517) 627-2650 or 627-2879 ✓159

\*\*\*\*\*  
**QUALITY MICROWAVE TV SYSTEMS**  
\*\*\*\*\*

Complete Systems From **'69<sup>95</sup>**

**1.9 to 2.5 GHz Antennas**

**Galaxy Electronics**  
6007 N. 61st Ave.  
Glendale, Az. 85301  
(602) 247-1151

COD's ✓178  
Dealers Wanted

VISA  
MasterCard

\*\*\*\*\*

**RTTY THE EASY WAY**

**AFSK MOD-DEMOM FOR RTTY, ASCII, 45 to 1200 BAUD MODEL MDK-17 KIT**

- \* Interfaces directly to baudot Type Machines.
- \* Provides for all Combinations of TTL or high voltage send-receive systems. \* Only single +12V Supply required. A high Gain Amp/Limiter and active band pass filter precede an XR2211 Demod I.C. \* Good Data recovery is assured, even under difficult conditions \*
- Excellent temperature stability is provided by an XR2206 I.C. in the tone generator. \* Sense invert capability \* LED indication of transmit tones, receiver tuning and valid signal. \* Auto start output available (TTL). \* Supplied with comprehensive documentation.

**MDK-17 Kit \$98 Plus \$10 Airmail, Assembled and Tested \$148**

GFS Electronic Imports.  
15 McKeon Road, Mitcham, 3132, Victoria  
Australia Ph 61 3 873 3939 Telex 38053 GFS

sample issue only \$2.50 PPD

**OUR 16TH YEAR!**

**AMATEUR TELEVISION MAGAZINE** ✓115

"FOR THE SPECIALIZED COMMUNICATION RADIO AMATEUR"

	Surface U.S./Canada	Surface All Mexico	Surface All Foreign	Airmail Central S. America	Airmail All Other Foreign
1/2 year	\$ 10.00	\$ 13.00	\$ 20.00	\$ 23.00	\$ 23.00
1 year	\$ 20.00	\$ 26.00	\$ 40.00	\$ 46.00	\$ 46.00
2 year	\$ 38.00	\$ 50.00	\$ 78.00	\$ 90.00	\$ 90.00
3 year	\$ 56.00	\$ 74.00	\$116.00	\$134.00	\$134.00

ATV-SSTV-FAX-RTTY-Satellites-EME  
Microwave and Computers.

Published 12 times per year by Mike Stone WB0QCD  
P.O. Box H, Lowden, Iowa 52255 0408

**CB TO TEN METER CONVERSION KITS**

**10 METER FM**—Limiter discriminator board with specific instructions to fit over 80 different AM & SSB chassis

**SSB-AM KITS**—Now in stock kits for most CB models—23 or 40 channels

**NEW & USED**—FM—SSB—AM converted C.B.'s in stock

**ANEXTER MARK ANTENNAS**  
—You saw them at Dayton. Now in stock the HW-3 three band heliwhip that covers 10—15—20 meters with no traps

**FREE CATALOG**—Write or call today

**INDEPENDENT CRYSTAL SUPPLY COMPANY**

141 Rt. 6A, Box 183  
Sandwich, Ma. 02563-0183  
(617) 888-4302 ✓78

**COLLINS RECEIVER**


**R-388/COLLINS 51J3 RECEIVER - 0.5-30.5 Mhz AM-CW in 30 bands, 1 Mhz per band. Bandwidth 0.2-6 KHz; 500 KHz IF. 5-step crystal selectivity. "S" meter, and 100 KHz calibration points. Requires 115/230 VAC 60 Hz; 10 1/2"x19"x13". 56 lbs. sh. Used-repairable: \$925- \$265. Checked: \$400- \$330. Manual, partial repro: \$10.**

**RF TUNER**  
From 400 watt transmitter; has Jennings UCSXF-1200 7.5 KV vacuum variable capacitor and 0.5-50 uH variable ribbon inductor. Selectable 50 ohm or whip antenna load and turns counters. 24 VDC required for capacitor and inductor drives; schematic included. 13 1/2"x10 1/4"x5 1/4". 24 lbs. sh. #RF1200/GRC14, used-excellent **\$195.**

Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted.  
Allow for Shipping • Write for Our FREE CATALOG  
Address Dept. 73 • Phone: 419/227-6573

**FAIR RADIO SALES** ✓22  
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

 **Teltone DTMF Receiver kits  
turn phones into control devices**



Teltone's DTMF Receivers let you turn the phone system into a control network. They outperform other receivers in noisy environments and operate over a wide dynamic range.

Two DTMF kits are available. The TRK-947 kit at \$53.00, decodes DTMF. For both Rotary and DTMF, order the TRK-927 for only \$75.00. Both include a 3.58 MHz crystal and a DIP socket.

To order call: (800) 227-3800 ext 1130  
[In CA. (800) 792-0990 ext 1130]



CIRCLE NO. 224

**YAESU FT-207R OWNERS**  
AUTO SCAN MODULE AND BATTERY  
SAVER KIT

**WRITE FOR CLUB DISCOUNTS**

**15 minutes to install; scan restarts when carrier drops off, busy switch controls automatic scan on-off; includes module and instructions.**

**Model AS-1. \$25.00**

**FT-207R BATTERY SAVER KIT  
MODEL BS-1 \$14.95**

- \*No more dead batteries due to memory back-up
- \*30% less power drain when squelched
- \*Simple to install, step-by-step Instructions and parts included
- \*4 mA memory backup reduced to 500  $\mu$ A.
- \*45 mA receiver drain reduced to 30 mA.
- \*Improved audio fidelity and loudness

**ENGINEERING CONSULTING**  
P.O. Box 216  
BREA, CALIFORNIA 92621

**GO MOBILE WITH YOUR H.T.!**

Model I—Icom IC-2AT, Etc.  
Model K-1 for TR-2500  
—slides on bottom of radio

**Guaranteed!**

Model K—TR-2400;  
—powered thru battery plug  
Model N—FT-208R  
Model T—Simple mod for Tempo

**NOW FOR FT-208R & TR-2500**

Model Y—FT-207R,  
—fits into battery compartment

\*A unique battery eliminator\*  
**HANDI-TEK Regulator** allows constant hand-held operation from auto DC or base supply with no nicad drain and **WITHOUT RADIO MODIFICATION!** \$24.95 PPD in USA. CA add \$1.50 Sales Tax.

✓ 460  
**HANDI-TEK**  
P.O. BOX 2205, LA PUENTE, CA 91746

**for  
Tired Receivers**

Lunar's line of RF actuated in-line receiving preamplifiers can spark up that otherwise dead band. Missing those weak ones? Become an elephant with new ears. Models available from 28-220 MHz bands. Simply insert between your transceiver and antenna, apply 12 VDC and enjoy. Standard SO-239 connectors on RF ports - BNC available. Typical performance at 144 MHz: 1.4 dB NF 10 dB gain. Low noise performance from Lunar - simply, the best.

2775 Kurtz Street, Suite 11  
San Diego, Ca 92110  
(619) 299-9740 • Telex 181747

**SYNTHESIZED  
SIGNAL GENERATOR**

MADE IN USA

MODEL SG1000  
\$349.95 plus shipping

- Covers 100 to 185 MHz in 1 kHz steps with thumb-wheel dial • Accuracy 1 part per 10 million at all frequencies • Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate • Spurs and noise at least 60 dB below carrier • RF output adjustable from 5-500 mV at 50 ohms • Operates on 12 Vdc @ 1/2 Amp • Available for immediate delivery • \$349.95 plus shipping
- Add-on Accessories available to extend freq. range, add infinite resolution, voice and sub-audible tones, AM, precision 120 dB calibrated attenuator
- Call for details • Dealers wanted worldwide.

**VANGUARD LABS** ✓311  
198-23 Jamaica Ave., Hollis, NY 11423  
Phone: (212) 488-2720

**FREE! FREE! FREE! FREE! FREE!**

**SEND FOR OUR NEW  
1983  
PARTS CATALOG**

**THOUSANDS OF  
SURPLUS ELECTRONIC  
PARTS, SUPPLIES AND  
DEVICES.**

**ALL ELECTRONICS CORP**  
905 S. Vermont Ave.  
P.O. Box 20406  
Los Angeles, Cal. 90006

**FREE! FREE! FREE! FREE! FREE!**

**WANTED**

HIGHEST PRICES PAID FOR:

**HARRIS RF-301  
&  
ASSOCIATED EQUIPMENT**

CALL COLLECT:  
**LIBERTY ELECTRONICS, INC.**  
**(212) 925-6048**

**THE  
BEST PLACE  
To Look For  
New & Used  
Equipment  
Buy-Sell-Trade  
Our 4th Year**

**NUTS & VOLTS  
MAGAZINE**

PO BOX 1111-G • PLACENTIA, CA 92670  
(714) 632-7721 ✓137

JOIN THOUSANDS OF READERS  
NATIONWIDE, EVERY MONTH

**U.S.A. SUBSCRIPTIONS**  
\$ 7.00 - 1 YR. 3RD CLASS MAIL  
\$12.50 - 1 YR. 1ST CLASS MAIL  
\$25.00 - LIFETIME - 3RD CLASS

With Free Classified Ad

**RELIABLE MICROWAVE TV ANTENNAS**

**2.1 to 2.6 GHz Frequency Range**  
**34db System Gain (or Greater)**

Complete System (as pictured)	\$149.95
Down Converter Probe Style (Assembled and Tested)	\$ 64.95
Power Supply (12V to 16V DC+) (Assembled and Tested)	\$ 59.95

**PETERSON ELECTRONICS**  
4558 Auburn Blvd.  
Sacramento, CA 95841  
(916) 486-9071 ✓182

C.O.D.'s  
**SPECIAL QUANTITY  
PRICING**  
Dealers Wanted

**1 YEAR WARRANTY  
PARTS & LABOR**

MasterCard VISA

We now have available a bunch of goodies too good to bypass. Items are limited so order today

Call your Phone Order in Today. **TERMS:** Satisfaction guaranteed or money refunded. C.O.D. add \$2.50. Minimum order \$6.00. Orders under \$10.00 add \$1.50. Add 6% for postage, insurance, handling. Overseas add 15%. N.Y. residents add 7% tax.

**MINI KITS - YOU HAVE SEEN THESE BEFORE NOW  
HERE ARE OLD FAVORITE AND NEW ONES TOO.  
GREAT FOR THAT AFTERNOON HOBBY.**

## FM MINI MIKE



A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available

FM-3 Kit **\$14.95**  
FM-3 Wired and Tested **19.95**

### Color Organ

See music come alive! 3 different lights flicker with music. One light each for high, mid-range and lows. Each individually adjustable and drives up to 300 W runs on 110 VAC

Complete kit, ML-1 **\$8.95**

### Video Modulator Kit

Converts any TV to video monitor. Super stable, tunable over ch 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market! Complete kit VD-1 **\$7.95**

### Super Sleuth

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker. Complete kit, BN-9 **\$5.95**

### Led Blinky Kit

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts. Complete kit, BL-1 **\$2.95**

### CPO-1

Runs on 3-12 Vdc 1 wall out, 1 KHZ good for CPO Alarm, Audio Oscillator. Complete kit **\$2.95**

## CLOCK KITS

Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!



Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify).  
Clock kit, 12/24 hour, DC-5 **\$24.95**  
Clock with 10 min. ID timer, 12/24 hour, DC-10 **\$29.95**  
Alarm clock, 12 hour only, DC-8 **\$29.95**  
12V DC car clock, DC-7 **\$29.95**

For wired and tested clocks add \$10.00 to kit price  
SPECIFY 12 OR 24 HOUR FORMAT

### FM Wireless Mike Kit

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage.  
FM-1 kit **\$3.95** FM-2 kit **\$4.95**

### Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC. Complete kit, WL-1 **\$6.95**

### Tone Decoder

A complete tone decoder on a single PC board. Features 400-5000 Hz adjustable range via 20 turn pot, voltage regulation 567 IC. Useful for touch-tone burst detection. FSK etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts. Complete kit, TD-1 **\$5.95**

### Universal Timer Kit

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs.  
UT-5 Kit **\$5.95**

### Mad Blaster Kit

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio. Runs on 6-15 VDC. Complete kit, MB-1 **\$4.95**

### Siren Kit

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker. Complete kit, SM-3 **\$2.95**

### 60 Hz Time Base

Runs on 5-15 VDC. Low current (2.5 ma) 1 min/month accuracy TB 7 Kit **\$5.50**  
TB-7 Assy **\$9.95**

## SATELLITE TV KIT



image rejection, fully tunable audio to recover 'hidden' subcarriers, divide by two PLL demodulator for excellent threshold performance, tight tracking AFC to assure drift free reception, and of course, full 24 channel tunable coverage.

Build your satellite TV system around the R2B, close to ten thousand others already have and now it's available in kit form at a new low price. Order yours today.

THE POPULAR SAT-TEC RECEIVER IN KIT FORM!

Featured in a Radio Electronics magazine cover story (May 82), the reliable R2B Sat-Tec TV receiver is now operating in thousands of locations. The R2B is easy to build, pre-etched, plated boards with screened component layout assures accurate component placement and the critical IF section and local oscillator are pre-assembled and aligned! All parts are included for the R2B; attractive case, power supply, descriptive operating manual as well as complete assembly instructions. Features of the receiver include: dual conversion design for best

A complete Satellite TV System requires a dish antenna, LNA (low noise amplifier), Receiver and Modulator **\$359.00**  
R2B Receiver Kit **\$595.00**  
R2B Receiver, Wired and Tested **\$595.00**  
120" K AvanteK LNA **\$495.00**  
RM3 RF Modulator **\$49.95**  
Prices include domestic UPS shipping and insurance.

# PARTS PARADE

## IC SPECIALS

LINEAR	TTL
301 <b>\$1.35</b>	74S00 <b>\$1.40</b>
324 <b>\$1.50</b>	7447 <b>\$1.65</b>
380 <b>\$1.50</b>	7475 <b>\$1.50</b>
555 <b>\$1.45</b>	7490 <b>\$1.50</b>
556 <b>\$1.00</b>	74196 <b>\$1.35</b>
565 <b>\$1.00</b>	
567 <b>\$1.25</b>	
741 <b>\$10.20</b>	
1458 <b>\$1.50</b>	
3900 <b>\$2.50</b>	
3914 <b>\$2.50</b>	
8038 <b>\$2.95</b>	

CMOS	SPECIAL
4011 <b>50</b>	11C90 <b>\$15.00</b>
4013 <b>50</b>	10116 <b>\$1.25</b>
4046 <b>\$1.85</b>	7208 <b>\$17.50</b>
4049 <b>50</b>	7207A <b>\$5.50</b>
4059 <b>\$9.00</b>	7216D <b>\$21.00</b>
4511 <b>\$2.00</b>	7107C <b>\$12.50</b>
4518 <b>\$1.35</b>	5375A/B <b>\$2.95</b>
5639 <b>\$1.75</b>	7001 <b>\$2.95</b>

Resistor Ass'l	Crystals
Assortment of Popular values - 1/4 watt. Cut lead for PC mounting, 5% center, 5% leads, bag of 300 or more <b>\$1.50</b>	3579545 MHZ <b>\$1.50</b>
	10 00000 MHZ <b>\$5.00</b>
	5 248800 MHZ <b>\$5.00</b>

Switches	AC Adapters
Mini toggle SPDT <b>\$1.00</b>	Good for clocks, nicad chargers, all 110 VAC plug one end <b>\$1.00</b>
Red Pushbuttons N/O <b>3/\$1.00</b>	8.5 vdc @ 20 mA <b>\$1.00</b>
	16 vac @ 160mA <b>\$2.50</b>
	12 vac @ 250mA <b>\$3.00</b>

Earphones	Solid State Buzzers
3' leads, 8 ohm, good for small tone speakers, alarm clocks etc. 5 for \$1.00	small buzzer, 450 Hz, 86 dB sound output on 5-12 vdc at 10-30 mA, TTL compatible <b>\$1.50</b>

Slug Tuned Coils	AC Outlet
Small 3/16" Hex Slugs turned coil, 3 turns <b>10 for \$1.00</b>	Panel Mount with Leads <b>4/\$1.00</b>

CAPACITORS	DC-OC Converter
TANTALUM Opped Epoxy	-5 vdc input prod -9 vdc @ 30ma -9 vdc produces -15 vdc @ 35ma <b>\$1.25</b>
ALUMINUM Electrolytic	
1.5 uF 25V 3/\$1.00	
500 uF 20V Avial <b>\$5.00</b>	
1.8 uF 25V 3/\$1.00	
150 uF 16V Avial <b>\$1.00</b>	
22 uF 25V 3/\$1.00	
100 uF 15V Radial <b>\$1.00</b>	
047 16V <b>20/\$1.00</b>	

### Audio Prescaler

Make high resolution audio measurements, great for musical instrument tuning, PL tones, etc. Multiplies audio UP in frequency, selectable x10 or x100, gives 01 HZ resolution with 1 sec gate time! High sensitivity of 25 mv, 1 meg input z and built-in filtering gives great performance. Runs on 9V battery, all CMOS.  
PS-2 kit **\$29.95**  
PS-2 wired **\$39.95**

### 600 MHz PRESCALER



Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity specify -10 or -100.  
Wired, tested, PS-1B **\$59.95**  
Kit, PS-1B **\$44.95**

### 30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 W in for 15 out, 4 W in for all parts out. Max output of 35 W, incredible value, complete with 30, less case and T-R relay.  
PA-1, 30 W pwr amp kit **\$22.95**  
TR-1, RF sensed T-R relay kit **6.95**

### Power Supply Kit

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and .5 at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3 V 1 A and 24 VCT.  
Complete kit, PS-3LT **\$6.95**

### READOUTS

FNO 359 4" C.C. **\$1.00**  
FNO 507/510 5" C.A. **1.00**  
MAN 72-HP/730 33" C.A. **2.00**  
HP 7651 43" C.A. **2.00**

### Sockets

8 Pin **10/\$2.00**  
14 Pin **10/\$2.00**  
16 Pin **10/\$2.00**  
24 Pin **4/\$2.00**  
28 Pin **4/\$2.00**  
40 Pin **3/\$2.00**

### FERRITE BEADS

With info and specs **15/\$1.00**  
6 Hole Balun Beads **5/\$1.00**

### DC-OC Converter

25K 20 Turn Trim Pot **\$1.00**  
1K 20 Turn Trim Pot **\$.50**

### Ceramic IF Filter

Min: **SOLD OUT** kHz  
B.W. **\$1.50 ea.**



Trimmer Caps  
Sprague - 3.40 pf  
Stable Polypropylene  
50 ea.

### TRANSISTORS

2N3904 NPN C-F **15/\$1.00**  
2N3906 PNP C-F **15/\$1.00**  
2N4033 PNP C-F **15/\$1.00**  
2N4410 NPN C-F **15/\$1.00**  
2N4916 FET C-F **4/\$1.00**  
2N5401 PNP C-F **\$1.00**  
2N6028 C-F **4/\$1.00**  
2N3771 NPN Silicon **\$1.50**  
2N5178 UHF NPN **3/\$2.00**  
Power Tab NPN 40W **3/\$1.00**  
Power Tab PNP 40W **3/\$1.00**  
MPE 102 2N5404 **\$.50**  
NPN 3904 Type T-R **50/\$2.50**  
PNP 3906 Type T-R **50/\$2.50**  
2N3055 **\$.80**  
2N2646 UJT **3/\$2.00**

### Diodes

1N1V Zener **20/\$1.00**  
5N914 Type **50/\$1.00**  
1KV 2Amp **8/\$1.00**  
100V 1Amp **15/\$1.00**

### Crystal Microphone

Small 1" diameter 1/2" thick crystal mike cartridge **\$.75**

### Coax Connector

Chassis mount **\$1.00**  
BNC type **\$1.00**

### 9 Volt Battery Clips

Nice quality clips **5 for \$1.00**  
1/2" Rubber Grommets **10 for \$1.00**

### Parts Bag

Ass't of chokes, disc caps, tant resistors, transistors, diodes, MICAs caps etc. 50 pc bag (100 pc) **\$1.00** 100 pc bag (300 pc) **\$2.50**

### Connectors

6 pin type gold contacts for mA-1003 car clock module **.75 ea.**

### Leds

- your choice, please specify  
Mini Red, Jumbo Red, High Intensity Red, Illuminator Red **8/\$1**  
Mini Yellow, Jumbo Yellow, Jumbo Green **6/\$1**

### Varactors

Motorola MV 2209 30 PF Nominal cap 20-80 PF - Tunable range - **50 each or 3/\$1.00**

### Regulators

78M **\$1.25**  
79M **\$1.25**  
723 **\$.50**  
309K **\$1.15**  
7805 **\$1.00**

### Shrink Tubing Nubs

Nice pre-cut pcs of shrink size 1" x 1/4" shrink to 1/4" Great for splices **50/\$1.00**

### Mini TO-92 Heat Sinks

Thermalloy Brand **5 for \$1.00**  
To-220 Heat Sinks **3 for \$1.00**

### Opto Isolators - 4N28 type

Opto Reflectors - Photo diode + LED **\$5.00 ea.**

### Molex Pins

Molex already pre-cut in length of 7. Perfect for 14 pin sockets **20 strips for \$1.00**

### COS Photocells

Resistance varies with light. 250 ohms to over 3 meg **3 for \$1.00**


FACIT 4555 SERIAL PAGE PRINTER

The Facit 4555 alphanumerical serial printer is complete. Equipped with RS232C Interface, printing mechanism, control electronics, drive electronics, power supply and character generator. The adaptation electronics can be modified in four versions: Bit-parallel data transfer, CCITT (EIA, RS232C) for bit-serial data transfer and the current loop (TTY) interface also for bit serial data transfer. The Facit 4555 prints on ordinary paper and is adjustable for different paper widths and formats, 9.5" paper width with 66 lines per page or DIN A4 with 70 lines per page.

SPECIFICATIONS

Print speed	up to 60ch.s.	Char. spacing	2.54mm/1/10" 80ch/line
Printing mode	Incremental.		1.55mm/0.06" 132ch/line
Max. # of ch/line	80 alt. 132.	Char. Code	ECMA-6 7-bit coded char. set
Matrix	7 X 5 dot matrix.	Char. Set	63 Char. various national versions.
Char. Size Height	2.7mm/1/8"	Feed mechanism	Sprocket feed.
Char. Size Width	1.3mm/0.05" 132ch/line		
	2.1mm/0.083" 80ch/line		

 THESE UNITS WERE PULLED OUT OF SERVICE IN GOOD WORKING CONDITION. WE CHECK EACH UNIT ON A RADIO SHACK TRS-80 COLOR COMPUTER.



PRINTER ONLY \$129.99

Printer with linecord, box of paper, inter-connect cable for TRS-80 COLOR COMPUTER. \$149.99

GENEVA CALCULATOR WATCH

This attractive watch has the following modes:  
 Normal Time Setting,  
 Calendar Setting,  
 Daily Alarm Time Setting,  
 Weekly Alarm Time Setting,  
 Chronograph,  
 Calculator.



Featured in Black Plastic \$24.99

or Featured in Stainless Steel \$29.99

SILICON DIODES

MR751	100vdc	6Amps	10/\$5.00	100/\$38.00
MR510	1000vdc	3Amps	10/\$3.75	100/\$24.00
HEP170	1000vdc	2Amps	20/\$2.00	100/\$15.00
IN3209	100vdc	15Amps	\$2.00	10/ \$15.00
BYX21/200	200vdc	25Amps	\$2.00	10/ \$15.00
IN2138A	600vdc	60Amps	\$5.00	10/ \$40.00
DS85-04C	400vdc	80Amps	\$10.00	10/ \$80.00
IN3269	600vdc	160Amps	\$15.00	10/\$120.00
275241	300vdc	250Amps	\$20.00	10/\$175.00
7-5754	300vdc	400Amps	\$30.00	10/\$250.00
RCD-15	15KVDC	20ma.	\$3.00	10/ \$20.00
SMFR20K	20KVDC	20ma.	\$4.00	10/ \$30.00
IN4148	signal		30/\$1.00	100/ \$3.00

FEED THRU SOLDER RF CAPACTORS

470pf +-20%
5/\$1.00 or 100/\$15.00 or 1000/\$100.00
1000pf/.001uf +-10%
4/\$1.00 or 100/\$20.00 or 1000/\$150.00

E PROMS

2708 1024x1	\$2.00 each
2716 2048x8	\$4.00 each
27L32/25L32	\$10.00 each

FAIRCHILD 4116 16K DYNAMIC RAMS 200ns. Part # 16K75

25 For \$25.00 or 100 For \$90.00 or 1000 For \$750.00

HEWLETT PACKARD MICROWAVE DIODES

IN5711	(5082-2800)	Schottky Barrier Diodes	\$1.00 or 10 for \$ 8.50
IN5712	(5082-2810)	" " "	\$1.50 or 10 for \$10.00
IN6263	(HSCH-1001)	" " "	\$ .75 or 10 for \$ 5.00
5082-2835		" " "	\$1.50 or 10 for \$10.00
5082-2805	Quad Matched	" " "	per set \$5.00 or 10 for \$40.00

**Toll Free Number  
 800-528-0180  
 (For orders only)**

**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# "MIXERS"

## WATKINS JOHNSON WJ-M6 Double Balanced Mixer

LO and RF 0.2 to 300MHz	IF DC to 300MHz	\$21.00
Conversion Loss (SSB)	6.5dB Max. 1 to 50MHz	
Noise Figure (SSB)	8.5dB Max. .2 to 300MHz	WITH DATA SHEET
Conversion Compression	same as above	
	8.5dB Max. 50 to 300MHz	
	.3dB Typ.	

## NEC (NIPPON ELECTRIC CO. LTD. NE57835/2SC2150 Microwave Transistor

NF Min F=2GHz	dB 2.4 Typ.	MAG F=2GHz	dB 12 Typ.	\$5.30
F=3GHz	dB 3.4 Typ.	F=3GHz	dB 9 Typ.	
F=4GHz	dB 4.3 Typ.	F=4GHz	dB 6.5 Typ.	

Ft Gain Bandwidth Product at Vce=8v, Ic=10ma. GHz 4 Min. 6 Typ.  
Vcbo 25v Vceo 11v Vebo 3v Ic 50ma. Pt. 250mw

## UNELCO RF Power and Linear Amplifier Capacitors

These are the famous capacitors used by all the RF Power and Linear Amplifier manufacturers, and described in the RF Data Book.

5pf	10pf	18pf	30pf	43pf	100pf	200pf	1 to 10pcs.	\$1.00 ea
5.1pf	12pf	22pf	32pf	51pf	110pf	220pf	11 to 50pcs.	\$ .90 ea
6.8pf	13pf	25pf	33pf	60pf	120pf	470pf	51 up pcs.	\$ .80 ea
7pf	14pf	27pf	34pf	80pf	130pf	500pf		
8.2pf	15pf	27.5pf	40pf	82pf	140pf	1000pf		

## NIPPON ELECTRIC COMPANY TUNNEL DIODES

		MODEL 1S2199	1S2200	\$7.50
Peak Pt. Current ma.	Ip	9min. 10Typ. 11max.	9min. 10Typ. 11max.	
Valley Pt. Current ma.	Iv	1.2Typ. 1.5max.	1.2Typ. 1.5max.	
Peak Pt. Voltage mv.	Vp	95Typ. 120max.	75Typ. 90max.	
Projected Peak Pt. Voltage mv.	Vpp Vf=Ip	480min. 550Typ. 630max.	440min. 520Typ. 600max.	
Series Res. Ohms	rS	2.5Typ. 4max.	2Typ. 3max.	
Terminal Cap. pf.	Ct	1.7Typ. 2max.	5Typ. 8max.	
Valley Pt. Voltage mv.	VV	370Typ.	350Typ.	

## FAIRCHILD / DUMONT Oscilloscope Probes Model 4290B

Input Impedance 10 meg., Input Capacity 6.5 to 12pf., Division Ratio (Volts/Div Factor) 10:1, Cable Length 4Ft., Frequency Range Over 100MHz.

These Probes will work on all Tektronix, Hewlett Packard, and other Oscilloscopes.

PRICE \$45.00

## MOTOROLA RF DATA BOOK

Lists all Motorola RF Transistors / RF Power Amplifiers, Varactor Diodes and much much more.

PRICE \$7.50

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**PRICES SUBJECT TO CHANGE WITHOUT NOTICE**

# RF TRANSISTORS, MICROWAVE DIODES

PART	PRICE	PART	PRICE	PART	PRICE
1S2199	\$ 7.50	2N6083	\$ 13.25	CA2612 (TRW)	\$ 25.00
1S2200	7.50	2N6084	15.00	CA2674 (TRW)	25.00
2N1561	25.00	2N6094 /M9622	11.00	CA2881-1 (TRW)	25.00
2N1562	25.00	2N6095 /M9623	12.00	CA4101 (TRW)	25.00
2N2857	1.55	2N6096 /M9624	15.50	CA4201 (TRW)	25.00
2N2857JAN	2.55	2N6097	17.25	CA4600 (TRW)	25.00
2N2876	11.00	2N6136	21.85	CD1889	20.00
2N2947	18.35	2N6166	40.25	CD2545	20.00
2N2948	15.50	2N6201	50.00	CMD514AB	20.00
2N2949	3.90	2N6459	18.00	D4959	10.00
2N2950	4.60	2N6603	12.00	D4987M	20.00
2N3375	8.00	2N6680	80.00	D5147D	10.00
2N3553	1.57	2SC756A	7.50	D5506	10.00
2N3632	13.80	2SC781	2.80	D5827AM	20.00
2N3818	5.00	2SC1018	1.00	DMD6022	30.00
2N3866	1.30	2SC1042	12.00	DMS-2A-250	40.00
2N3924	3.35	2SC1070	2.50	HEP76	4.95
2N3927	17.75	2SC1239	2.50	HEPS3002	11.30
2N3950	25.00	2SC1251	12.00	HEPS3003	30.00
2N4072	1.80	2SC1306	2.90	HEPS3005	10.00
2N4127	21.00	2SC1307	5.50	HEPS3006	19.90
2N4427	1.30	2SC1760	1.50	HEPS3007	25.00
2N4428	1.85	2SC1970	2.50	HEPS3010	11.34
2N4957	3.45	2SC2166	5.50	HTEF2204 H.P.	112.00
2N4958	2.90	8B1087 (M.A.)	25.00	5082-0112 H.P.	14.20
2N4959	2.30	A50-12	20.00	5082-0253 H.P.	105.00
2N5090	13.90	A283B	5.00	5082-0320 H.P.	58.00
2N5108	4.00	ALD4200N (AVANTEK)	395.00	5082-0386 H.P.	POR
2N5109	1.70	AM123	97.35	5082-0401 H.P.	POR
2N5160	3.45	AM688	100.00	5082-0438 H.P.	POR
2N5177	21.62	BB105B	.52	5082-1028 H.P.	POR
2N5179	1.00	BD4/4JFBD4 (G.E.)	10.00	5082-2711 H.P.	23.15
2N5583	4.00	BFQ85	1.50	5082-3080 H.P.	2.00
2N5589	8.65	BFR90	1.30	5082-3188 H.P.	1.00
2N5590	10.35	BFR91	1.65	5082-6459 H.P.	POR
2N5591	13.80	BFW92	1.50	5082-8323 H.P.	POR
2N5635	10.95	BFX89	1.00	35826E H.P.	POR
2N5637	15.50	BFY90	1.00	35831E H.P.	29.99
2N5641	9.20	BGY54	25.00	35853E H.P.	71.50
2N5642	10.95	BGY55	25.00	35854E H.P.	75.00
2N5643	15.50	BGY74	25.00	HPA0241 H.P.	75.60
2N5645	13.80	BGY75	25.00	HXTR3101 H.P.	7.00
2N5646	20.70	BL161	10.00	HXTR3102 H.P.	8.75
2N5691	18.00	BLX67	11.00	HXTR6101/2N6617 H.P.	55.00
2N5764	27.00	BLY568CF	25.00	HXTR6104 H.P.	68.00
2N5836	5.45	BLY87	13.00	HXTR6105 H.P.	31.00
2N5842	8.00	BLY88	14.00	HXTR6106 H.P.	33.00
2N5849	20.00	BLY89	15.00	QSCH1995 H.P.	POR
2N5913	3.25	BLY90	20.00	JO2000 TRW	10.00
2N5922	10.00	BLY351	10.00	JO2001 TRW	25.00
2N5923	25.00	C4005	20.00	JO4045 TRW	25.00
2N5941	23.00	CA402 (TRW)	25.00	K3A	10.00
2N5942	40.00	CA405 (TRW)	25.00	MA450A	10.00
2N5944	9.20	CA612B (TRW)	25.00	MA41487	POR
2N5945	11.50	CA2100 (TRW)	25.00	MA41765	POR
2N5946	19.00	CA2113 (TRW)	25.00	MA43589	POR
2N6080	9.20	CA2200 (TRW)	25.00	MA43636	POR
2N6081	10.35	CA2213 (TRW)	25.00	MA47044	POR
2N6082	11.50	CA2418 (TRW)	25.00	MA47651	25.50

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**MHz electronics**

# GaAs, TUNNEL DIODES, ETC.

PART	PRICE	PART	PRICE	PART	PRICE
MA47100	\$ 3.05	MRF503	\$ 6.00	PT4186B	\$ POR
MA47202	30.80	MRF504	7.00	PT4209	POR
MA47771	POR	MRF509	5.00	PT4209C	POR
MA47852	POR	MRF511	8.65	PT4566	POR
MA49558	POR	MRF605	20.00	PT4570	POR
MB4021	POR	MRF629	3.47	PT4571	POR
MBD101	1.00	MRF644	23.00	PT4571A	POR
MDO513	POR	MRF816	15.00	PT4577	POR
MHW1171	42.50	MRF823	20.00	PT4590	POR
MHW1182	48.60	MRF901	3.00	PT4612	POR
MHW4171	49.35	MRF8004	2.10	PT4628	POR
MHW4172	51.90	MS261F	POR	PT4640	POR
MHW4342	68.75	MT4150 Fair.	POR	PT4642	POR
MLP102	25.00	MT5126 Fair.	POR	PT5632	POR
MM1500	32.32	MT5481 Fair.	POR	PT5749	POR
MM1550	POR	MT5482 Fair.	POR	PT6612	POR
MM1552	50.00	MT5483 Fair.	POR	PT6626	POR
MM1553	50.00	MT5596 Fair.	POR	PT6709	POR
MM1614	10.00	MT5764 Fair.	POR	PT6720	POR
MM2608	5.00	MT8762 Fair.	POR	PT8510	POR
MM3375A	11.50	MV109	.77	PT8524	POR
MM4429	10.00	MV1401	8.75	PT8609	POR
MM8000	1.15	MV1624	1.42	PT8633	POR
MM8006	2.30	MV1805	15.00	PT8639	POR
MO277L	POR	MV1808	10.00	PT8659	POR
MO283L	POR	MV1817B	10.00	PT8679	POR
MO3757	POR	MV1863B	10.00	PT8708	POR
MP102	POR	MV1864A	10.00	PT8709	POR
MPN3202	10.00	MV1864B	10.00	PT8727	POR
MPN3401	.52	MV1864D	10.00	PT8731	POR
MPN3412	1.00	MV1868D	10.00	PT8742	POR
MPSU31	1.01	MV2101	.90	PT8787	POR
MRA2023-1.5 TRW	42.50	MV2111	.90	PT9790	41.70
MRF212/208	16.10	MV2115	1.55	PT31962	POR
MRF223	13.25	MV2201	.53	PT31963	POR
MRF224	15.50	MV2203	.53	PT31983	POR
MRF237	3.15	MV2209	2.00	PTX6680	POR
MRF238	12.65	MV2215	2.00	RAY-3	24.99
MRF243	25.00	MWA110	7.45	40081	POR
MRF245	34.50	MWA120	7.80	40281	POR
MRF247	34.50	MWA130	8.25	40282	POR
MRF304	43.45	MWA210	7.80	40290	POR
MRF315	23.00	MWA220	8.25	RF110	25.00
MRF420	20.00	MWA230	8.65	SCA3522	POR
MRF421	36.80	MWA310	8.25	SCA3523	POR
MRF422	41.40	MWA320	8.65	SD1065	POR
MRF427	16.10	MWA330	9.50	SS43	POR
MRF428	46.00	NEC57835	5.30	TP1014	POR
MRF450/A	13.80	ON382	5.00	TP1028	POR
MRF453/A	17.25	PPT515-20-3	POR	TRW-3	POR
MRF454/A	19.90	PRT8637	POR	UTO504 Avantek	70.00
MRF455/A	16.00	PSCQ2-160	POR	UTO511 Avantek	75.00
MRF458	19.90	PT3190	POR	V15	4.00
MRF463	25.00	PT3194	POR	V33B	4.00
MRF472	1.00	PT3195	POR	V100B	4.00
MRF475	2.90	PT3537	POR	VAB801EC	25.00
MRF477	11.50	PT4166E	POR	VAB804EC	25.00
MRF502	1.04	PT4176D	POR	VAS21AN20	25.00

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

## MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

COAXIAL RELAY SWITCHES SPDT

Electronic Specialty Co./Raven Electronics FSN 5985-556-9683 \$49.00  
 Part # 25N28 Part # SU-01  
 26Vdc Type N Connector, DC to 1 GHz.



Amphenol  
 Part # 316-10102-8  
 115Vac Type BNC DC to 3 GHz.




FXR  
 Part # 300-11182  
 120Vac Type BNC DC to 4 GHz.  
 FSN 5985-543-1225

FXR  
 Part # 300-11173  
 120Vac Type BNC Same  
 FSN 5985-543-1850

\$29.99

\$39.99

\$39.99

   

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

\$7.99 or 2 For \$13.99 or 10 For \$50.00

\$8.99 or 2 For \$15.99 or 10 For \$60.00



SOLID STATE RELAYS

P&B Model ECT1DB72 5vdc turn on  
 PRICE EACH \$5.00

Digisig, Inc. Model ECS-215 5vdc turn on  
 PRICE EACH \$7.50

Grigsby/Barton Model GB7400 5vdc turn on  
 PRICE EACH \$7.50

120vac contact at 7amps or 20amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

240vac contact 14amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

240vac contact at 15amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

NOTE: \*\*\* Items may be substituted with other brands or equivalent model numbers. \*\*\*

**MHz** electronics


"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

 **PRICES SUBJECT TO CHANGE WITHOUT NOTICE**

RECALL PHONE MEMORY TELEPHONE WITH 24 NUMBER AUTO DIALER

The Recall Phone Telephone employs the latest state of art communications technology. It is a combination telephone and automatic dialer that uses premium-quality, solid-state circuitry to assure high-reliability performance in personal or business applications. \$49.99




ARON ALPHA RAPID BONDING GLUE

Super Glue #CE-486 high strength rapid bonding adhesive. Alpha Cyanoacrylate. Set-Time 20 to 40 sec., 0.7 fl. oz. (20gm.) \$2.00



TOUCH TONE PAD

 This pad contains all the electronics to produce standard touch-tone tones. New with data.



\$9.99 or 10/\$89.99

MITSUMI UHF/VHF VARACTOR TUNER MODEL UVE1A

Perfect for those unscrambler projects. New with data.



\$19.99 or 10/\$149.99

INTEGRATED CIRCUIT.

		1 to 10	11up
MC1372P	Color TV Video Modulator Circuit.	\$ 4.42	\$2.95
MC1358P	IF Amp., Limiter, FM Detector, Audio Driver, Electronic Attenuator.	5.00	4.00
MC1350P	IF Amplifier	1.50	1.25
MC1330A1P	Low Level Video Detector	1.50	1.15
MC1310P	FM Stereo Demodulator	4.29	3.30
MC1496P	Balanced Modulator/Demodulator	1.50	1.25
LM565N	Phase Locked Loop	2.50	2.00
LM380N14	2Watt Audio Power Amplifier	1.56	1.25
LM1889N	TV Video Modulator	5.00	4.00
NE564N	Phase Locked Loop	10.00	8.00
NE561N	Phase Locked Loop	10.00	8.00

FERRANTI ELECTRONICS AM RADIO RECEIVER MODEL ZN414 INTEGRATED CIRCUIT.

Features:

1.2 to 1.6 volt operating range., Less than 0.5ma current consumption. 150KHz to 3MHz Frequency range., Easy to assemble, no alignment necessary. Effective and variable AGC action., Will drive an earphone direct. Excellent audio quality., Typical power gain of 72dB., TO-18 package. With data. \$2.99 or 10 For \$24.99

NI CAD RECHARGEABLE BATTERIES

AA Battery Pack of 6 These are Factory New. \$5.00

SUB C Pack of 10 2.5Amp/Hr. \$10.00

Gates Rechargeable Battery Packs

12vdc at 2.5Amp/Hr. \$11.99  
12vdc at 5Amp/Hr. \$15.99



**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**We will be closed April 27th through May 2nd...**

**See you at the Dayton Hamvention!**

Toll Free Number  
800-528-0180  
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# "SOCKETS AND CHIMNEYS"

## EIMAC TUBE SOCKETS AND CHIMNEYS

		\$POR
SK110	Socket	\$520.00
SK300A	Socket For 4CX5000A,R,J, 4CX10,000D, 4CX15,000A,J	260.00
SK400	Socket For 4-125A,250A,400A,400C,4PR125A,400A,4-500A,5-500A	74.00
SK406	Chimney For 4-250A,400A,400C,4PR400A	36.00
SK416	Chimney For 3-400Z	390.00
SK500	Socket For 4-1000A/4PR1000A/B	51.00
SK600	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	73.00
SK602	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	11.00
SK606	Chimney For 4CX250B,BC,FG,R,4CX350A,F,FJ	60.00
SK607	Socket For 4CX600J,JA	60.00
SK610	Socket For 4CX600J,JA	66.00
SK620	Socket For 4CX600J,JA	10.00
SK626	Chimney For 4CX600J,JA	66.00
SK630	Socket For 4CX600J,JA	34.00
SK636B	Chimney For 4CX600J,JA	36.00
SK640	Socket For 4CX600J,JA	71.00
SK646	Chimney For 4CX600J,JA	225.00
SK700	Socket For 4CX300A,Y,4CX125C,F	225.00
SK711A	Socket For 4CX300A,Y,4CX125C,F	86.00
SK740	Socket For 4CX300A,Y,4CX125C,F	86.00
SK770	Socket For 4CX300A,Y,4CX125C,F	225.00
SK800A	Socket For 4CX1000A,4CX1500B	40.00
SK806	Chimney For 4CX1000A,4CX1500B	225.00
SK810	Socket For 4CX1000A,4CX1500B	300.00
SK900	Socket For 4X500A	57.00
SK906	Chimney For 4X500A	650.00
SK1420	Socket For 5CX3000A	585.00
SK1490	Socket For 4CV8000A	

## JOHNSON TUBE SOCKETS AND CHIMNEYS

124-111/SK606	Chimney For 4CX250B,BC,FG,R, 4CX350A,F,FJ	\$ 10.00
122-0275-001	Socket For 3-500Z, 4-125A, 250A, 400A, 4-500A, 5-500A	(pair) 15.00
124-0113-00	Capacitor Ring	15.00
124-116/SK630A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
124-115-2/SK620A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
	813 Tube Socket	20.00

## CHIP CAPACITORS

.8pf	10pf	100pf*	430pf
1pf	12pf	110pf	470pf
1.1pf	15pf	120pf	510pf
1.4pf	18pf	130pf	560pf
1.5pf	20pf	150pf	620pf
1.8pf	22pf	160pf	680pf
2.2pf	24pf	180pf	820pf
2.7pf	27pf	200pf	1000pf/.001uf*
3.3pf	33pf	220pf*	1800pf/.0018uf
3.6pf	39pf	240pf	2700pf/.0027uf
3.9pf	47pf	270pf	10,000pf/.01uf
4.7pf	51pf	300pf	12,000pf/.012uf
5.6pf	56pf	330pf	15,000pf/.015uf
6.8pf	68pf	360pf	18,000pf/.018uf
8.2pf	82pf	390pf	

PRICES:	1 to 10 - .99¢	101 to 1000 .60¢	* IS A SPECIAL PRICE:	10 for \$7.50
	11 to 50 - .90¢	1001 & UP .35¢		100 for \$65.00
	51 to 100 - .80¢			1000 for \$350.00

WATKINS JOHNSON WJ-V907: Voltage Controlled Microwave Oscillator \$110.00

Frequency range 3.6 to 4.2GHz, Power output, Min. 10dBm typical, 8dBm Guaranteed.  
Spurious output suppression Harmonic (nf<sub>0</sub>), min. 20dB typical, In-Band Non-Harmonic, min. 60dB typical, Residual FM, pk to pk, Max. 5KHz, pushing factor, Max. 8KHz/V, Pulling figure (1.5:1 VSWR), Max. 60MHz, Tuning voltage range +1 to +15volts, Tuning current, Max. -0.1mA, modulation sensitivity range, Max. 120 to 30MHz/V, Input capacitance, Max. 100pf, Oscillator Bias +15 +/-0.05 volts @ 55mA, Max.

## TUBE CAPS (Plate)

HR1, 4	\$11.00
HR2,3, 6 & 7	13.00
HR5, 8	14.00
HR9	17.00
HR10	20.00

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

# MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



# "FILTERS"

## COLLINS Mechanical Filter #526-9724-010 MODEL F455Z32F

455KHZ at 3.2KHz wide. May be other models but equivalent. May be used or new. \$15.99

### ATLAS Crystal Filters

5.595-2.7/8/LSB, 5.595-2.7/LSB	
8 pole 2.7KHz wide Upper sideband. Impedence 800ohms 15pf In/800ohms 0pf out.	19.99
5.595-2.7/8/U, 5.595-2.7/USB	
8 pole 2.7KHz wide Upper sideband. Impedence 800ohms 15pf In/800ohms 0pf out.	19.99
5.595-.500/4, 5.595-.500/4/CW	
4 pole 500 cycles wide CW. Impedence 800ohms 15pf In/800ohms 0pf out.	19.99
9.0USB/CW	
6 pole 2.7KHz wide at 6dB. Impedence 680ohms 7pf In/300ohms 8pf out. CW-1599Hz	19.99

### KOKUSAI ELECTRIC CO, Mechanical Filter #MF-455-ZL/ZU-21H

455KHz at Center Frequency of 453.5KC. Carrier Frequency of 455KHz 2.36KC Bandwidth.	
Upper sideband. (ZU)	19.99
Lower sideband. (ZL)	19.99

### CRYSTAL FILTERS

NIKKO	FX-07800C	7.8MHz	\$10.00
TEW	FEC-103-2	10.6935MHz	10.00
SDK	SCH-113A	11.2735MHz	10.00
TAMA	TF-31H250	CF 3179.3KHz	19.99
TYCO/CD	001019880	10.7MHz 2pole 15KHz bandwidth	5.00
MOTOROLA	4884863B01	11.7MHz 2pole 15KHz bandwidth	5.00
PTI	5350C	12MHz 2pole 15KHz bandwidth	5.00
PTI	5426C	21.4MHz 2pole 15KHz bandwidth	5.00
PTI	1479	10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB	20.00
COMTECH	A10300	45MHz 2pole 15KHz bandwidth	6.00
FRC	ERXF-15700	20.6MHz 36KHz wide	10.00
FILTECH	2131	CF 7.825MHz	10.00

### CERAMIC FILTERS

AXEL	4F449	12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.4KHz	10.00
CLEVITE	TO-01A	455KHz+2KHz bandwidth 4-7% at 3dB	5.00
	TCF4-12D36A	455KHz+1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz	10.00
MURATA	BFB455B	455KHz	2.50
	BFB455L	455KHz	3.50
	CFM455E	455KHz +5.5KHz at 3dB, +8KHz at 6dB, +16KHz at 50dB	6.65
	CFM455D	455KHz +7KHz at 3dB, +10KHz at 6dB, +20KHz at 50dB	6.65
	CFR455E	455KHz +5.5KHz at 3dB, +8KHz at 6dB, +16KHz at 60dB	8.00
	CFU455B	455KHz +2KHz bandwidth +15KHz at 6dB, +30KHz at 40dB	2.90
	CFU455C	455KHz +2KHz bandwidth +12.5KHz at 6dB, +24KHz at 40dB	2.90
	CFU455G	455KHz +1KHz bandwidth +4.5KHz at 6dB, +10KHz at 40dB	2.90
	CFU455H	455KHz +1KHz bandwidth +3KHz at 6dB, +9KHz at 40dB	2.90
	CFU455I	455KHz +1KHz bandwidth +2KHz at 6dB, +6KHz at 40dB	2.90
	CFW455D	455KHz +10KHz at 6dB, +20KHz at 40dB	2.90
	CFW455H	455KHz +3KHz at 6dB, +9KHz at 40dB	2.90
	SFB455D	455KHz	2.50
	SFD455D	455KHz +2KHz, 3dB bandwidth 4.5KHz +1KHz	5.00
	SFE10.7MA	10.7MHz 280KHz +50KHz at 3dB, 650KHz at 20dB	2.50
	SFE10.7MS	10.7MHz 230KHz +50KHz at 3dB, 570KHz at 20dB	2.50
	SFG10.7MA	10.7MHz	10.00
NIPPON	LF-B4/CFU455I	455KHz +1KHz	2.90
	LF-B6/CFU455H	455KHz +1KHz	2.90
	LF-B8	455KHz	2.90
	LF-C18	455KHz	10.00
TOKIN	CF455A/BFU455K	455KHz +2KHz	5.00
MATSUSHIRA	EFC-L455K	455KHz	7.00

### SPECTRA PHYSICS INC, Model 088 HeNe LASER TUBES

POWER OUTPUT 1.6MW.	BEAM DIA. .75MM	BEAM DIR. 2.7MR	8KV STARTING VOLTAGE DC
68K OHM IWATT BALLAST	1000VDC +100VDC	At 3.7MA	\$59.99

### ROTRON MUFFIN FANS Model MARK4/MU2A1

115 VAC	14WATTS	50/60CPS	IMPEDENCE PROTECTED-F	88CFM at 50CPS	\$ 7.99
105CFM at 60CPS	THESE ARE NEW				

# MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

# "CHIPS"

FAIRCHILD VHF AND UHF PRESCALER CHIPS		PRICE
95H90DC	350MC Prescaler divide by 10/11	\$ 8.50
95H91DC	350MC Prescaler divide by 5/6	8.50
11C90DC	650MC Prescaler divide by 10/11	15.50
11C91DC	650MC Prescaler divide by 5/6	15.50
11C06DC	UHF Prescaler 750MC D Type Flip Flop	12.30
11C05DC	1GHz Counter Divide by 4 (Regular price \$75.00)	50.00
11C01FC	High Speed Dual 5/4 Input NO/NOR Gate	15.40
82S90	Presetable High Speed Decade/Binary Counter used with the 11C90/91 or the 95H90/91 Prescaler can divide by 100. (Signetics)	5.00
11C24DC	This chip is the same as a Motorola MC4024/4324 Dual TTL Voltage Control Multivibrator.	3.37
11C44DC	This chip is the same as a Motorola MC4044/4344 Phase Frequency Detector.	3.37

**GENERAL ELECTRIC CO. GUNN DIODE MODEL Y-2167**  
 Freq. Gap (GHZ) 12 to 18, Output (Min.) 100mW, Duty (%) CW, Typ. Bias (Vdc) 8.0, Type. Oper. (MAdc) 550, Max. Thres. (mAdc) 1000, Max. Bias (Vdc) 10.0. **\$39.99**

**VARIAN GALLIUM ARSENIDE GUNN DIODES MODEL VSX-9201S5**  
 Freq. Coverage 8 to 12.4GHz, Output (Min.) 100mW, Bias Voltage (Max.) 14vdc, Bias current (mAdc) Operating 550 Typ. 750 Max., Threshold 850 Typ. 1000 Max. **\$39.99**

**VARI-L Co. Inc. MODEL SS-43 AM MODULATOR**  
 Freq. Range 60 to 150MC, Insertion Loss 13dB Nominal, Signal Port Imp. 50ohms Nominal, Signal Port RF Power + 10dBm Max., Modulation Port BW DC to 1KHZ, Modulation Port Bias 1ma. Nominal. **\$24.99**

AVANTEK CASCADABLE MODULAR AMPLIFIERS			
Frequency Range	Model UTO-504	UTO-511	
Gain	5 to 500 MHz	5 to 500 MHz	
Noise Figure	6dB	15dB	
Power Output	11dB	2.3dB to 3dB	
	+ 17dB	- 2dB to - 3dB	
Gain Flatness	1dB	1dB	
Input Power Vdc	+ 24	+ 15	
mA	100	10	
	PRICE \$70.00	PRICE \$75.00	

## HEWLETT PACKARD

MIXERS MODELS	10514A	10514B
Frequency Range	2MHz to 500MC	2MHz to 500MC
Input/Output Frequency L & R	200KHz to 500MC	200KHz to 500MC
	X DC to 500MC	DC to 500MC
Mixer Conversion Loss (A)	7dB	7dB
(B)	9dB	9dB
Noise Performance (SSB) (A)	7dB	7dB
(B)	9dB	9dB
PRICE	\$49.99	PRICE \$39.99

## FREQUENCY SOURCES, INC MODEL MS-74X MICROWAVE SIGNAL SOURCE

MS-74X: Mechanically Tunable Frequency Range (MHz) 10630 to 11230 (10.63 to 11.23GHz) Minimum Output Power (mW) 10, Overall Multiplier Ratio 108, Internal Crystal Oscillator Frequency Range (MHz) 98.4 to 104.0, Maximum Input Current (mA) 400.

The signal source are designed for applications where high stability and low noise are of prime concern. These sources utilize fundamental transistor oscillators with high Q coaxial cavities, followed by broadband stable step recovery diode multipliers. This design allows single screw mechanical adjustment of frequency over standard communications bands. Broadband sampling circuits are used to phase lock the oscillator to a high stability reference which may be either an internal self-contained crystal oscillator, external primary standard or VHF synthesizer. This unique technique allows for optimization of both FM noise and long term stability. List Price is \$1158.00 (THESE ARE NEW) **Our Price—\$289.**

## HEWLETT PACKARD 1N5712 MICROWAVE DIODE

This diode will replace the MBD101, 1N5711, 5082-2800, 5082-2835 ect. This will work like a champ in all those Down Converter projects **\$1.50 or 10/\$10.00**

## MOTOROLA MHW1172R LOW DISTORTION WIDEBAND AMPLIFIER MODULE.

Frequency Range: 40 to 300 MHz., Power Gain at 50MHz 16.6min to 17.4max., Gain Flatness ±0.1 Typ. ±0.2 Max. dB., DC Supply Voltage - 28vdc. RF Voltage Input + 70dBmV **PRICE \$29.99**

## GENERAL ELECTRIC AA NICADS

Model #41B905HD11-G1  
 Pack of 6 for \$5.00 or 60 Cells, 10 Packs for \$45.00  
 These may be broken down to individual cells.

### ORDERING INSTRUCTIONS

**DEFECTIVE MATERIAL:** All claims for defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed properly or it will void all warranties.

**DELIVERY:** Orders are normally shipped within 48 hours after receipt of customer's order. If a part has to be backordered the customer is notified. Our normal shipping method is via First Class Mail or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point.

**FOREIGN ORDERS:** All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.D. is not available to foreign countries and Letters of Credit are not an acceptable form of payment either. Further information is available on request.

**HOURS:** Monday thru Saturday, 8:30 a.m. to 5:00 p.m.

**INSURANCE:** Please include 25c for each additional \$100.00 over \$100.00, United Parcel only.

**ORDER FORMS:** New order forms are included with each order for your convenience. Additional forms are available on request.

**POSTAGE:** Minimum shipping and handling in the US, Canada, and Mexico is \$2.50 all other countries is \$5.00. On foreign orders include 20% shipping and handling.

**PREPAID ORDERS:** Order must be accompanied by a check.

**PRICES:** Prices are subject to change without notice.

**RESTOCK CHARGE:** If parts are returned to MHZ Electronics due to customer error, customer will be held responsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returns must have approval.

**SALES TAX:** Arizona must add 5% sales tax, unless a signed Arizona resale tax card is currently on file with MHZ Electronics. All orders placed by persons outside of Arizona, but delivered to persons in Arizona are subject to the 5% sales tax.

**SHORTAGE OR DAMAGE:** All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY  
 NO INFORMATION WILL BE GIVEN. 1 800-528-0180.

**TERMS: DOMESTIC:** Prepaid, C.O.D. or Credit Card

**FOREIGN:** Prepaid only, U.S. Funds—money order or cashier's check only.

**C.O.D.:** Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's check. We are sorry but we cannot accept personal checks for C.O.D.'s.

**CONFIRMING ORDERS:** We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, customers will be held responsible for any charges incurred, plus a 15% restock charge on returned parts.

**CREDIT CARDS:** WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.

**DATA SHEETS:** When we have data sheets in stock on devices we do supply them with the order.

**MHz electronics**



(602) 242-3037

(602) 242-8816

2111 W. CAMELBACK ROAD  
 PHOENIX, ARIZONA 85015

Toll Free Number

800-528-0180

(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

# NEW LOW-NOISE PREAMPS RECEIVING CONVERTERS TRANSMIT CONVERTERS

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.



Models LNA( ), P30, and P432 shown

Model	Tunable Freq Range	Noise Figure	Gain	Price
LNA 28	20-40	0.9 dB	20 dB	\$39.95
LNA 50	40-70	0.9 dB	20 dB	\$39.95
LNA 144	120-180	1.0 dB	18 dB	\$39.95
LNA 220	180-250	1.0 dB	17 dB	\$39.95
LNA 432	380-470	1.0 dB	18 dB	\$44.95


## ECONOMY PREAMPS

Our traditional preamps, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freq. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

- P30K, VHF Kit less case \$14.95
- P30C, VHF Kit with case \$20.95
- P30W, VHF Wired/Tested \$29.95
- P432K, UHF Kit less case \$18.95
- P432C, UHF Kit with case \$24.95
- P432W, UHF Wired/Tested \$33.95

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

## HELICAL RESONATOR PREAMPS

 

Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49.95
HRA-220	213-233 MHz	\$49.95
HRA-432	420-450 MHz	\$59.95



Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	Antenna Input Range	Receiver Output
<b>VHF MODELS</b>	28-32	144-148
Kit \$44.95	50-52	28-30
Less Case \$39.95	50-54	144-148
Wired \$59.95	144-146	28-30
	145-147	28-30
	144-144.4	27-27.4
	146-148	28-30
	144-148	50-54
	220-222	28-30
	220-224	144-148
	222-226	144-148
	220-224	50-54
	222-224	28-30

	Antenna Input Range	Receiver Output
<b>UHF MODELS</b>	432-434	28-30
Kit \$54.95	435-437	28-30
Less Case \$49.95	432-436	144-148
Wired \$74.95	432-436	50-54
	439.25	61.25

**SCANNER CONVERTERS** Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only \$79.95.

**SPECIAL FREQUENCY CONVERTERS** made to custom order \$119.95. Call for details.

## SAVE A BUNDLE ON VHF FM TRANSCEIVERS!

FM-5 PC Board Kit - ONLY \$159.95 complete with controls, heatsink, etc. 10 Watts, 5 Channels, for 6M, 2M, or 220



Cabinet Kit, complete with speaker, knobs, connectors, hardware. Only \$59.95

While supply lasts, get \$59.95 cabinet kit free when you buy an FM-5 Transceiver kit. Where else can you get a complete transceiver for only \$159.95?

**REPEAT OF A SELLOUT!**

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 watts output.

	Exciter Input Range	Antenna Output
For VHF, Model XV2	28-30	144-146
Kit \$79.95	28-29	145-146
Wired \$119.95	28-30	50-52
(Specify band)	27-27.4	144-144.4
	28-30	220-222
	50-54	220-224
	144-146	50-52
	50-54	144-148
	144-146	28-30

	Exciter Input Range	Antenna Output
For UHF, Model XV4	28-30	432-434
Kit \$99.95	28-30	435-437
Wired \$149.95	50-54	432-436
	61.25	439.25
	144-148	432-436*


\*Add \$35 for 2M input

**FREE OFFER**


For limited time, buy a transmit converter above with 40-45W PA (\$129.95) and get \$39.95 cabinet FREE.




## LOOK AT THESE ATTRACTIVE CURVES!

 

 R144 & R220 Front Ends. HRA 144/220, & HRF-144/220




R451 Receiver Front End

 

Rcvr I-F Selectivity

 Typical Selectivity Curves of Receivers and Helical Resonators.



HRA-432, HRF-432

- Call or Write for **FREE CATALOG** (Send \$1.00 or 4 IRC's for overseas mailing)
- Order by phone or mail ● Add \$2 S & H per order (Electronic answering service evenings & weekends) Use VISA, MASTERCARD, Check, or UPS COD.

**hamtronics, inc.**

65-W MOUL RD. ● HILTON NY 14468  
Phone: 716-392-9430

Hamtronics® is a registered trademark

**AT LAST —  
A REPEATER  
YOU CAN AFFORD!**

For years, Hamtronics® Modules have been used by individual hams and manufacturers to make repeaters. Now, in the Hamtronics tradition of top quality and superb value, we are proud to offer a complete repeater package.



**JUST LOOK AT THESE PRICES!**

Band	Kit	Wired/Tested
6M, 2M, 220	\$595	\$745
440	\$645	\$795

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

**CALL OR WRITE FOR COMPLETE DETAILS.**


Also available for remote site linking/crossband & 10M.

**FEATURES:**

- SENSITIVITY SECOND TO NONE; TYPICALLY 0.15 uV ON VHF, 0.2 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY-TUNE TRANSMITTER; UP TO 20 WATTS OUT.


**HIGH QUALITY MODULES FOR  
REPEATERS, LINKS, TELEMETRY, ETC.**

**INTRODUCING —  
NEW 1983 RECEIVERS**

 


R144 Shown

- **R144/R220 FM RCVRs** for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity (curves at left). AFC incl., xtal oven avail. Kit only \$119.95
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.2 uV sens. Kit only \$119.95.
- **R76 FM RCVR** for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only \$109.95. Also avail w/4 pole filter, only \$94.95/ kit.
- **R110VHF AM RECEIVER** kit for VHF aircraft band or ham bands. Only \$84.95.
- **R110 UHF AM RECEIVER** for UHF uses, including special 296 MHz model to hear SPACE SHUTTLE. Kit \$94.95.

 


- **HELICAL RESONATOR FILTERS** available separately on pcb w/connectors.
- HRF-144 for 143-150 MHz \$34.95
- HRF-220 for 213-233 MHz \$34.95
- HRF-432 for 420-450 MHz \$44.95

(See selectivity curves at left.)

 


 - **COR KITS** With audio mixer and speaker amplifier. Only \$29.95.
- **CWID KITS** 158 bits, field programmable, clean audio. Only \$59.95.



- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Only \$18.00.

**TRANSMITTERS AND  
ACCESSORIES**

 

- **T51 VHF FM EXCITER** for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts continuous. Kits only \$59.95



- **T451 UHF FM EXCITER** 2 to 3 Watts on 450 ham band or adjacent. Kits only \$69.95.
- **VHF & UHF LINEAR AMPLIFIERS.** Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Kits from \$69.95.

# INTRODUCING SONY'S NEW DIGITAL DIRECT ACCESS RECEIVER!



only **\$199<sup>95</sup>** plus \$5.00 shipping  
**(NOW IN STOCK)**

## Revolutionary Instant Access Digital Shortwave Scanner


- Continuous Scanning of LW, MW, SW, & FM Bands
- Instant Fingertip Tuning—No More Knobs!
- 6 Memories for Any Mode (AM,SSB/CW, & FM)
- Dual PLL Frequency Synthesized—No Drift!

**A WHOLE NEW BREED OF RADIO IS HERE NOW!** No other short wave receiver combines so many advanced features for both operating convenience and high performance as does the new Sony ICF-2001. Once you have operated this exciting new radio, you'll be spoiled forever! Direct access tuning eliminates conventional tuning knobs and dials with a convenient digital keyboard and Liquid Crystal Display (LCD) for accurate frequency readout to within 1 KHz. Instant fingertip tuning, up to 8 memory presets, and continuous scanning features make the ICF-2001 the ultimate in convenience.

Compare the following features against any receiver currently available and you will have to agree that the Sony ICF 2001 is the best value in shortwave receivers today:

**DUAL PLL SYNTHESIZER CIRCUITRY** covers entire 150 KHz to 29.999 MHz band. PLL<sub>1</sub> circuit has 100 KHz step while PLL<sub>2</sub> handles 1 KHz step, both of which are controlled by separate quartz crystal oscillators for precise, no-drift tuning. **DUAL CONVERSION SUPERHETERODYNE** circuitry assures superior AM reception and high image rejection characteristics. The 10.7 MHz IF of the FM band is utilized as the 2nd IF of the AM band. A new type of crystal filter made especially for this purpose realizes clearer reception than commonly used ceramic filters. **ALL FET FRONT END** for high sensitivity and interference rejection. Intermodulation, cross modulation, and spurious interference are effectively rejected. **FET RF AMP** contributes to superior image rejection, high sensitivity, and good signal to noise ratio. Both strong and weak stations are received with minimal distortion.

### EXTENDED SPECTRUM CONTINUOUS TUNING

 

### OPERATIONAL FEATURES

**INSTANT FINGERTIP TUNING** with the calculator-type key board enables the operator to have instant access to any frequency in the LW, MW, SW, and FM bands. And the LCD digital frequency display confirms the exact, drift-free signal being received. **AUTOMATIC SCANNING** of the above bands. Continuous scanning of any desired portion of the band is achieved by setting the "L<sub>1</sub>" and "L<sub>2</sub>" keys to define the range to be scanned. The scanner can stop automatically on strong signals, or it can be done manually. **MANUAL SEARCH** is similar to the manual scan mode and is useful for quick signal searching. The "UP" and "DOWN" keys let the tuner search for you. The "FAST" key increases the search rate for faster signal detection. **MEMORY PRESETS.** Six memory keys hold desired stations for instant one-key tuning in any mode (AM, SSB/CW, and FM), and also, the "L<sub>1</sub>" and "L<sub>2</sub>" keys can give you two more memory slots when not used for scanning. **OTHER FEATURES:** Local, normal, DX sensitivity selector for AM; SSB/CW compensator; 90 min. sleep timer; AM Ant. Adjust.

### SPECIFICATIONS

**CIRCUIT SYSTEM:** Fm Superheterodyne; AM Dual conversion superheterodyne. **SIGNAL CIRCUITRY:** 4 IC's, 11 FET's, 23 Transistors, 16 Diodes. **AUXILIARY CIRCUITRY:** 5 IC's, 1 LSI, 5 LED's, 25 Transistors, 9 Diodes. **FREQUENCY RANGE:** FM 76-108 MHz; AM 150-29,999 KHz. **INTERMEDIATE FREQUENCY:** FM 10.7 MHz; AM 1st 66.35 MHz, 2nd 10.7 MHz. **ANTENNAS:** FM telescopic, ext. ant. terminal; AM telescopic, built-in ferrite bar, ext. ant. terminal. **POWER:** 4.5 VDC/120 VAC **DIMENSIONS:** 12 1/4 (W) X 2 1/4 (H) X 6 3/4 (D). **WEIGHT:** 3 lb. 15 oz. (1.8 kg)



**SPECTRONICS, INC.**  
 1009 GARFIELD ST. OAK PARK, IL. 60304

PHONE  
**(312) 848-6777**



ramsey

# the first name in Counters!



## 9 DIGITS 600 MHz \$129<sup>95</sup>

WIRED

**SPECIFICATIONS:**

Range: 20 Hz to 600 MHz  
 Sensitivity: Less than 10 MV to 150 MHz  
 Less than 50 MV to 500 MHz  
 Resolution: 0.1 Hz (10 MHz range)  
 1.0 Hz (60 MHz range)  
 10.0 Hz (600 MHz range)  
 Display: 9 digits 0.4" LED  
 Time base: Standard-10,000 mHz, 1.0 ppm 20-40°C  
 Optional Micro-power oven-0.1 ppm 20-40°C  
 Power: 8-15 VAC @ 250 ma

**PRICES:**  
 CT-90 wired, 1 year warranty \$129.95  
 CT-90 Kit, 90 day parts warranty 109.95  
 AC-1 AC adapter 3.95  
 BP-1 Nicad pack + AC Adapter/Charger 12.95  
 OV-1 Micro-power Oven time base 49.95  
 External time base input 14.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

## 7 DIGITS 525 MHz \$99<sup>95</sup>

WIRED



**SPECIFICATIONS:**

Range: 20 Hz to 525 MHz  
 Sensitivity: Less than 50 MV to 150 MHz  
 Less than 150 MV to 500 MHz  
 Resolution: 1.0 Hz (5 MHz range)  
 10.0 Hz (50 MHz range)  
 100.0 Hz (500 MHz range)  
 Display: 7 digits 0.4" LED  
 Time base: 1.0 ppm TCXO 20-40°C  
 Power: 12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as: three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

**PRICES:**

CT-70 wired, 1 year warranty \$99.95  
 CT-70 Kit, 90 day parts warranty 84.95  
 AC-1 AC adapter 3.95  
 BP-1 Nicad pack + AC adapter/charger 12.95



## 7 DIGITS 500 MHz \$79<sup>95</sup>

WIRED

**PRICES:**

MINI-100 wired, 1 year warranty \$79.95  
 AC-Z Ac adapter for MINI-100 3.95  
 BP-Z Nicad pack and AC adapter/charger 12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

**SPECIFICATIONS:**

Range: 1 MHz to 500 MHz  
 Sensitivity: Less than 25 MV  
 Resolution: 100 Hz (slow gate)  
 1.0 KHz (fast gate)  
 Display: 7 digits, 0.4" LED  
 Time base: 2.0 ppm 20-40°C  
 Power: 5 VDC @ 200 ma

## 8 DIGITS 600 MHz \$159<sup>95</sup>

WIRED



**SPECIFICATIONS:**

Range: 20 Hz to 600 MHz  
 Sensitivity: Less than 25 mv to 150 MHz  
 Less than 150 mv to 600 MHz  
 Resolution: 1.0 Hz (60 MHz range)  
 10.0 Hz (600 MHz range)  
 Display: 8 digits 0.4" LED  
 Time base: 2.0 ppm 20-40°C  
 Power: 110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

**PRICES:**

CT-50 wired, 1 year warranty \$159.95  
 CT-50 Kit, 90 day parts warranty 119.95  
 RA-1, receiver adapter kit 14.95  
 RA-1 wired and pre-programmed (send copy of receiver schematic) 29.95



## DIGITAL MULTIMETER \$99<sup>95</sup>

WIRED

**PRICES:**

DM-700 wired 1 year warranty \$99.95  
 DM 700 Kit, 90 day parts warranty 79.95  
 AC-1, AC adaptor 3.95  
 BP-3, Nicad pack + AC adapter/charger 19.95  
 MP-1, Probe kit 2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually fool-proof! The DM-700 looks great, a handsome, jet black, rugged ARS case with convenient retractable tilt bail makes it an ideal addition to any shop.

**SPECIFICATIONS:**

DC/AC volts: 100uV to 1 KV, 5 ranges  
 DC/AC current: 0.1uA to 2.0 Amps, 5 ranges  
 Resistance: 0.1 ohms to 20 Megohms, 6 ranges  
 Input Impedance: 10 Megohms, DC/AC volts  
 Accuracy: 0.1% basic DC volts  
 Power: 4°C cells

### AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

### ACCESSORIES

Telescopic whip antenna - BNC plug ..... \$ 7.95  
 High impedance probe, light loading ..... 15.95  
 Low pass probe, for audio measurements ..... 15.95  
 Direct probe, general purpose usage ..... 12.95  
 Tilt bail, for CT 70, 90, MINI-100 ..... 3.95  
 Color burst calibration unit, calibrates counter against color TV signal ..... 14.95

### COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
  - BNC Connectors
  - Great for sniffing RF with pick-up loop
- \$34.95 Kit \$44.95 Wired

ramsey electronic's, inc.



2575 Baird Rd. Penfield, NY 14526

PHONE ORDERS  
 CALL 716-586-3950

**TERMS**

Satisfaction guaranteed - examine for 10 days, if not pleased return in original form for refund. Add 5% for shipping insurance to a maximum of \$10. Overseas add 15%. COD add \$2. Orders under \$10 add \$1.50. NY residents add 7% tax.

# DEALER DIRECTORY

## Culver City CA

Jun's Electronics, 3919 Sepulveda Blvd., Culver City CA 90230, 390-9003. Trades 463-1886 San Diego, 827-5732 (Reno NV).

## Fontana CA

Complete lines ICOM, DenTron, Ten-Tec, Mirage, Cubic, Lunar, over 4000 electronic products for hobbyist, technician, experimenter. Also CB radio, landmobile. Fontana Electronics, 9626 Sierra Ave., Fontana CA 92335, 822-7710.

## New Castle DE

Factory Authorized Dealer! Yaesu, ICOM, Ten-Tec, KDK, Azden, AEA, Kantronics, Santee. Full Line of Accessories. No Sales Tax in Delaware. One mile off I-95. Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 328-7726.

## San Jose CA

Bay area's newest Amateur Radio store. New & used Amateur Radin sales & service. We feature Kenwood, ICOM, Azden, Yaesu, Ten-Tec, Santee & many more. Shaver Radio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.

## Smyrna GA

For your Kenwood, Yaesu, ICOM, Drake and other amateur needs, come to see us. Britt's Two-Way Radio, 2506 N. Atlanta Rd., Smyrna GA 30080, 432-8006.

## Preston ID

Ross WB7BYZ has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham needs. Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.

## Bloomington IL

ROHN TOWERS—Large stock plus all UNARCO ROHN items available for fast drop shipments. Wholesale prices to all users. Also wholesale distributor for Antenna Specialists, Regency, and Wilson. Hill Radio 2503 G.E. Road Box 1405, Bloomington, IL 61701 663-2141

## Terre Haute IN

Your ham headquarters located in the heart of the midwest. Hoosier Electronics, Inc., #9 Meadors Center, P.O. Box 3300, Terre Haute IN 478003, 238-1456.

## Littleton MA

The Reliable Ham Store Serving N.E. Full line of ICOM & Kenwood, Yaesu HTs, Drake, Daiwa, B&W accessories, Curtis & Trac keys, Larsen, Hustler, Telex/Hy-Gain products, Mirage amps., Astron P.S., Alpha Delta protectors, ARRL & Kantronics instruction aids, Whistler radar detectors. Full line of coax fittings. TEL-COM Electronic Communications 675 Great Rd. (Rt. 119), Littleton MA 01460, 617-486-3400/3040.

## Ann Arbor MI

See us for products like Ten-Tec, R. L. Drake, DenTron and many more. Open Monday through Saturday, 0830 to 1730. WB8VGR, WB8UXO, WVD8OKN and W8RP behind the counter. Purchase Radio Supply, 327 E. Hoover Ave., Ann Arbor MI 48104, 666-8696.

## Hudson NH

New England's Distributor and Authorized Service Center for all Major Amateur Lines. Tufts Radio Electronics, Inc., 61 Lowell Road, Hudson NH 03051, 883-5005.

## Somerset NJ

New Jersey's only factory-authorized ICOM and Yaesu distributor. Large inventory of new and used specials. Most major brands in stock. Complete service and facilities. Radios Unlimited, 1760 Easton Avenue, P.O. Box 347, Somerset NJ 08873, 469-4599.

## Buffalo NY WESTERN NEW YORK

Niagara Frontier's only full stocking Amateur dealer. Also Shortwave, CB, Scanners, Marine, Commercial. Operating displays featuring Kenwood and others. Towers, Antennas, Sales and Service. DX Communications, 3214 Transit Road, West Seneca NY, 668-8873.

## Amsterdam NY UPSTATE NEW YORK

Kenwood, ICOM, Drake, plus many other lines. Amateur Dealer for over 35 years. Adirondack Radio Supply, Inc., 185 West Main Street, Amsterdam NY 12010, 842-8350.

## Syracuse-Rome-Utica NY

Featuring: Kenwood; Yaesu, ICOM, Drake, Ten-Tec, Swan, DenTron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy-Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products. You won't be disappointed with equipment/service. Radio World, Oneida County Airport-Terminal Building, Oriskany NY 13424, 736-0184.

## Columbus OH

The highest and best Ham Store in the midwest featuring quality Kenwood products with working displays. We sell only the best. Authorized Kenwood Service, Universal Amateur Radio Inc., 1280 Aida Dr., Reynoldsburg (Columbus) OH 43068, 866-4267.

## Scranton PA

ICOM, Bird, Cushcraft, Beckman, Fluke, Larsen, Hustler, Antenna Specialists, Astron, Avanti, Belden, W2AU/W2VS, CIDE, AEA, Vibroplex, Ham-Key, CES, Arapahoe, Sony, Fanon/Courier, B&W, Ameco, Shure, LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.

## San Antonio TX

Amateur, Commercial 2-way. Selling Antenna Specialists, Avanti, Azden, Bird, Hy-Gain, Standard, Vibroplex, Midland, Henry, Cushcraft, Dielectric, Hustler, ICOM, MFJ, Nye, Shure, Cubic, Tempo, Ten-Tec and others. Appliance & Equipment Co., Inc. 2317 Vance Jackson Road, San Antonio TX 78213, 734-7793.

## DEALERS

Your company name and message can contain up to 25 words for as little as \$150 yearly (prepaid), or \$15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the May '83 issue must be in our hands by March 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

# PROPAGATION

J. H. Nelson  
4 Plymouth Dr.  
Whiting NJ 08759

## EASTERN UNITED STATES TO:

GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14A	7A	7	7	7	7	7	14	14A	21	21A	21A
ARGENTINA	21	14	14	14	7A	7	14	21A	21A	21A	21A	21A
AUSTRALIA	21A	14A	14	14	7B	7B	7B	14B	14	14	21A	21A
CANAL ZONE	21	14	14	7	7	7	14	21A	21A	21A	21A	21
ENGLAND	7	7	7	7	7	7A	14A	21A	21A	21	14A	14
HAWAII	21A	21	14	7	7	7	7	14B	14	21A	21A	21A
INDIA	14B	14	7B	7B	7B	7B	14	21	21	14	14	14
JAPAN	21	14	7B	7B	7B	7B	7	7	7B	7B	14	21A
MEXICO	21	14	7	7	7	7	7	14A	21A	21A	21A	21A
PHILIPPINES	21	14	7B	7B	7B	7B	7B	14B	14	14	14	21
PUERTO RICO	14	7	7	7	7	7	14	21	21A	21A	21A	21
SOUTH AFRICA	14	14	7	7	7B	14	21	21A	21A	21A	21A	21
U. S. S. R.	7B	7	7	7	7B	7B	14	21A	21A	14	14B	7B
WEST COAST	21A	14A	7	7	7	7	7	14	21A	21A	21A	21A

## CENTRAL UNITED STATES TO:

ALASKA	21	14	7A	7	7	7	7	14	14A	21A	21A	21A
ARGENTINA	21A	14	14	14	7A	7	14	21A	21A	21A	21A	21A
AUSTRALIA	21A	21	14	14	7B	7B	7B	14B	14	14	21A	21A
CANAL ZONE	21A	14	14	7	7	7	14	21A	21A	21A	21A	21A
ENGLAND	7	7	7	7	7	7	14	21	21A	21	14A	14
HAWAII	21A	21A	14	7	7	7	7	14	21A	21A	21A	21A
INDIA	14	14	7B	7B	7B	7B	14	14A	14	14	14	14
JAPAN	21A	21	14	7B	7B	7B	7	7	7B	7B	14	21A
MEXICO	14A	14	7	7	7	7	7	14	21	21	21A	21A
PHILIPPINES	21A	14A	14	7B	7B	7B	7B	14	14	14	21A	21A
PUERTO RICO	21	14	14	7	7	7	14	21A	21A	21A	21A	21A
SOUTH AFRICA	21	14	7	7	7B	7B	14	21A	21A	21A	21A	21
U. S. S. R.	7B	7	7	7	7B	7B	7B	14A	21A	14	14B	7B

## WESTERN UNITED STATES TO:

ALASKA	21	14	7A	7	7	7	7	7	7A	14	21A	21A
ARGENTINA	21A	21	14	14	7A	7	7B	21	21A	21A	21A	21A
AUSTRALIA	21A	21A	21	14	14	14B	7B	7B	14	14	21A	21A
CANAL ZONE	21A	14A	14	7	7	7	7A	21	21A	21A	21A	21A
ENGLAND	7B	7	7	7	7	7B	7B	14	21A	21	14	14
HAWAII	21A	21A	21	14	14	7A	7	7	14	21A	21A	21A
INDIA	14	14	14	14B	7B	7B	7B	14	14	14	14	14
JAPAN	21A	21A	14A	14	7B	7B	7	7	7	7B	14	21A
MEXICO	21A	14A	7A	7	7	7	7	14	21A	21A	21A	21A
PHILIPPINES	21A	21A	14A	14	7B	7B	7B	14	14	14	21A	21A
PUERTO RICO	21A	14A	14	7	7	7	7	21	21A	21A	21A	21A
SOUTH AFRICA	21	14	7	7	7B	7B	7B	14	21A	21A	21A	21
U. S. S. R.	7B	7B	7	7	7B	7B	7B	14	14	14B	7B	7B
EAST COAST	21A	14A	7	7	7	7	7	14	21A	21A	21A	21A

A = Next higher frequency band may also be useful.

B = Difficult circuit this period.

First letter = night waves. Second = day waves.

G = Good, F = Fair, P = Poor. \* = Chance of solar flares.

# = Chance of aurora.

NOTE THAT NIGHT WAVE LETTER NOW COMES FIRST.

MARCH						
SUN	MON	TUE	WED	THU	FRI	SAT
		1 G/G	2 G/G	3 F/G	4 F/F	5 F/G
6 F/G	7 G/G	8 G/G*	9 F/F	10 F/G	11 G/G	12 G/G
13 F/F	14 G/G	15 G/G	16 F/F*	17 P/F*	18 P/F*	19 P/F
20 F/G	21 F/G	22 F/F	23 F/G	24 F/G	25 F/G	26 F/F*
27 F/F	28 G/G	29 G/G	30 G/G	31 F/G		

# DEALER DIRECTORY



# INTRODUCING . . . THE FT-980 CAT SYSTEM !!!



Join the computer revolution in Amateur Radio with the Computer Aided Transceiver  
. . . the new FT-980 from Yaesu Electronics!

- 8-Bit microprocessor for greater operating flexibility.
- High-voltage, all solid state transmitter PA for excellent linearity.
- Keyboard entry of frequencies into any of twelve independent VFO/memory registers.
- Amateur band transmit plus general coverage receive capability.
- Full CW break-in with quiet solid state switching.
- CW Spot switch on front panel.
- Digital frequency display with resolution to 10 Hz. Digital readerboard-type coarse frequency sub-display.
- Keyboard entry of sub-bands for Novice, General, or Advanced Class operators. Separate sub-bands may be programmed on each memory.
- Up/Down scanning plus instant  $\pm 5$  kHz/step QSY from front panel.
- SSB/CW/AM/FSK/FM operation built in. CW and AM Wide/Narrow selection using optional filters.
- Wide dynamic range and noise floor maintenance provided by husky front end design and IF filter gain balancing.
- 10 Hz synthesizer steps. Quick frequency change via keyboard or scanning controls.
- IF Notch filter at 455 kHz for interference rejection.
- Audio Peak Filter for narrow band CW signal enhancement.
- RX Audio Tone Control for signal laundering in AF line.
- Variable IF Bandwidth and IF Shift using cascaded filters.
- Memory storage of both frequency and operating mode.
- Pushbutton Memory Check feature for verification of memory frequencies without actually changing operating frequency in use.
- Pushbutton Offset Check feature for verification of memory-to-VFO frequency difference.
- Variable Pulse Width Noise Blanker.
- IF Monitor with front panel volume control.
- RF Speech Processor.
- Dual metering of Vcc, Ic, ALC, Compression, Discriminator Center, Relative PO, and SWR (Calibrated).
- Selectable AGC: Slow/Fast/Off.
- Separate RX-only antenna jack.
- Three FSK shifts built in.
- Optional Electronic Keyer Module
- Optimization of audio passband for mode in use, for preservation of noise figure with changing bandwidth.
- Computer interface optional module available mid-1983, for remote transceiver control from personal computer terminal.

For a detailed brochure covering the FT-980 CAT System, call or write your Authorized Yaesu Dealer.

Price And Specifications Subject To  
Change Without Notice Or Obligation

**YAESU**  
*The radio.*



0183

✓83

YAESU ELECTRONICS CORPORATION, 6851 Walthall Way, Paramount, CA 90723 ● (213) 633-4007  
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45146 ● (513) 874-3100

# NEW

# "DX-traordinary."



Superior dynamic range, auto. antenna tuner, QSK, dual NB, 2 VFO's, general coverage receiver.

## TS-930S

The TS-930S is a superlative, high performance, all-solid state, HF transceiver keyed to the exacting requirements of the DX and contest operator. It covers all Amateur bands from 160 through 10 meters, and incorporates a 150 kHz to 30 MHz general coverage receiver having an excellent dynamic range.

Among its other important features are, SSB slope tuning, CW VBT, IF notch filter, CW pitch control, dual digital VFO's, CW full break-in, automatic antenna tuner, and a higher voltage operated solid state final amplifier. It is available with or without the AT-930 automatic antenna tuner built-in.

### TS-930S FEATURES:

- **160-10 Meters, with 150 kHz-30 MHz general coverage receiver.** Covers all Amateur frequencies from 160-10 meters, including new WARC bands, on SSB, CW, FSK, and AM. Features 150 kHz-30 MHz general coverage receiver. Separate Amateur band access keys allow speedy band selection. UP/DOWN bandswitch in 1-MHz steps. A new, innovative, quadruple "UP" conversion, digital PLL synthesized circuit provides superior frequency accuracy and stability, plus greatly enhanced selectivity.
- **Excellent receiver dynamic range.** Receiver two-tone dynamic range, 100 dB typical (20 meters, 50-kHz spacing, 500 Hz CW bandwidth, at sensitivity of 0.25  $\mu$ v, S/N 10 dB), provides the ultimate in rejection of IM distortion.
- **All solid state, 28 volt operated final amplifier.** The final amplifier operates on 28 VDC for lowest IM distortion. Power input rated at 250 W on SSB, CW, and FSK, and at 80 W on AM. Final amplifier protection circuits with cooling fan, SWR/Power meter built-in.
- **CW full break-in.** CW full break-in circuit uses CMOS logic IC plus reed relay for smooth, quiet operation. Switchable to semi-break-in.

- **Automatic antenna tuner, built-in.** Covers Amateur bands 80-10 meters, including the new WARC bands. Tuning range automatically pre-selected with band selection to minimize tuning time. "AUTO-THRU" switch on front panel.
- **Dual digital VFO's.** 10-Hz step dual digital VFO's include band information. Each VFO tunes continuously from band to band. A large, heavy, flywheel type knob is used for improved tuning ease. T.F. Set switch allows fast transmit frequency setting for split-frequency operations. A=B switch for equalizing one VFO frequency to the other. VFO "Lock" switch provided. RIT control for  $\pm 9.9$  kHz.
- **Eight memory channels.** Stores both frequency and band information. VFO-MEMO switch allows use of each memory as an independent VFO, (the original memory frequency can be recalled at will), or as a fixed frequency. Internal Battery memory back-up, estimated 1 year life. (Batteries not Kenwood supplied).
- **Dual mode noise blanker ("pulse" or "woodpecker").** NB-1, with threshold control, for pulse-type noise. NB-2 for longer duration "woodpecker" type noise.
- **SSB IF slope tuning.** Allows independent adjustment of the low and/or high frequency slope of the IF passband, for best interference rejection. HIGH/LOW cut control rotation not affected by selecting USB or LSB modes.
- **CW VBT and pitch controls.** CW Variable Bandwidth Tuning control tunes out interfering signals. CW pitch control shifts IF passband and simultaneously changes the pitch of the beat frequency. A "Narrow/Wide" filter selector switch is provided.
- **IF notch filter.** 100 kHz IF notch circuit gives deep, sharp, notch, better than -40 dB.
- **Audio filter built-in.** Tuneable, peak-type audio filter for CW.
- **AC power supply built-in.** 120, 220, or 240 VAC, switch selected (operates on AC only).

- **Fluorescent tube digital display.** Six digit readout to 100 Hz (10 Hz modifiable), plus digitalized sub-scale with 20-kHz steps. Separate two digit indication of RIT frequency shift. In CW mode, display indicates the actual carrier frequency of received as well as transmitted signals.
- **RF speech processor.** RF clipper type processor provides higher average "talk-power," improved intelligibility.
- **One year limited warranty on parts and labor.**
- **Other features:**
  - SSB monitor circuit, 3 step RF attenuator, VOX, and 100-kHz marker.
- **Optional accessories:**
  - AT-930 automatic antenna tuner.
  - SP-930 external speaker with selectable audio filters.
  - YG-455C-1 (500 Hz) or YG-455CN-1 (250 Hz) plug-in CW filters for 455-kHz IF.
  - YK-88C-1 (500 Hz) CW plug-in filter for 8.83-MHz IF.
  - YK-88A-1 (6 kHz) AM plug-in filter for 8.83-MHz IF.
  - SO-1 commercial stability TCXO (temperature compensated crystal oscillator). Requires modifications.
  - MC-60A deluxe desk microphone with UP/DOWN switch, pre-amplifier, 8-pin plug.
  - TL-922A linear amplifier (not for CW QSK).
  - SM-220 station monitor (not for pan-adaptor).
  - HS-6, HS-5, HS-4, headphones.

More information on the TS-930S is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.

# KENWOOD

...pacesetter in amateur radio



Specifications and prices are subject to change without notice or obligation.