

75 cents


*hr*<sub>m</sub>

focus  
on  
communications  
technology . . .

# ham radio

magazine

JUNE 1972

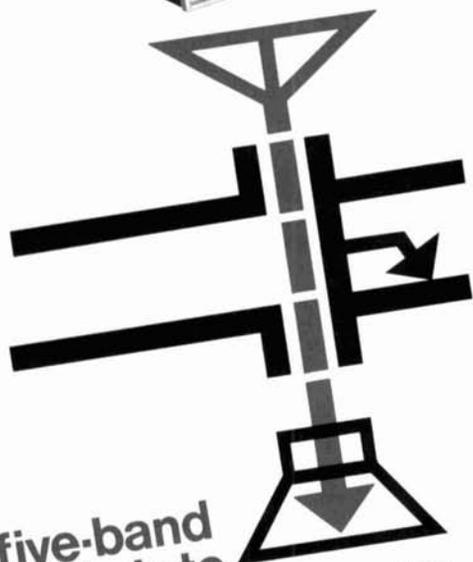


five-band  
solid-state  
COMMUNICATIONS  
RECEIVER

## *this month*

- fm repeater control 22
- noise figure measurements 36
- sstv sync generator 50
- microwave experimenting 53
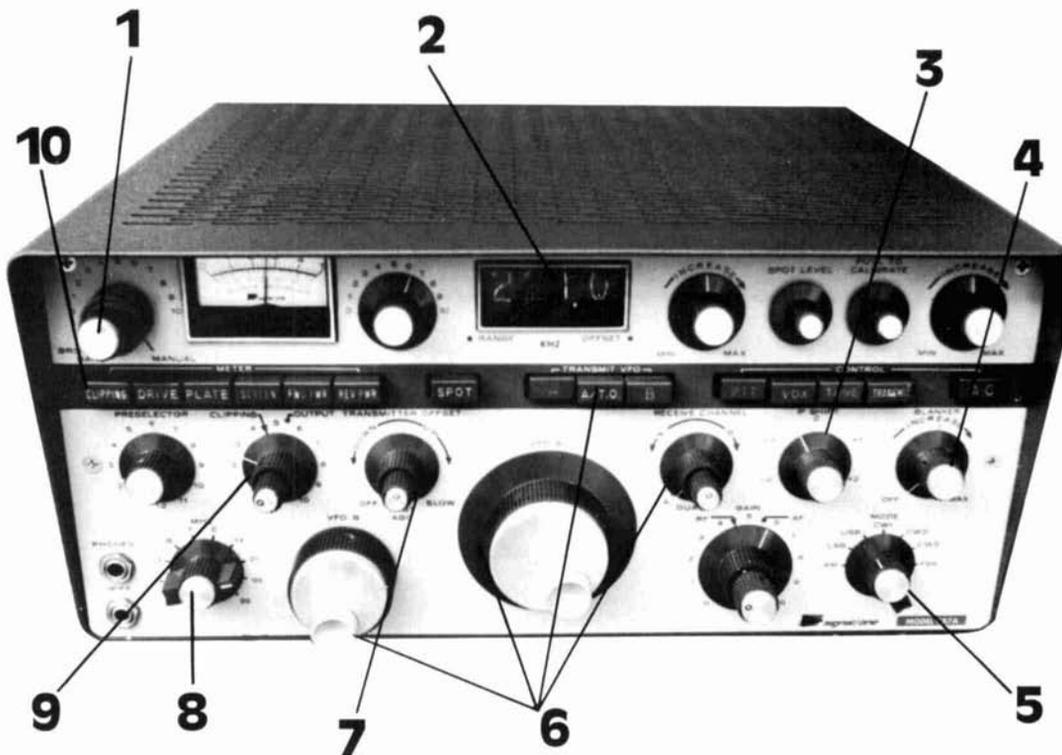
# Somebody once said there's no price for perfection.



## Now there is: \$2,195.

Perfection. It's another name for signal/one's CX7A. When signal/one engineers set out to design the CX7, they started with a clean slate.

They sat down and brainstormed. They tried to come up with every conceivable feature the serious amateur would want in a rig.

Once they had the features figured out, they started engineering innovative circuitry . . . right from the chassis up. And they didn't compromise, either in circuitry or in the components they chose for the rig.

Oh, sure, there were problems. You always

run into that when you're making electronic history. But we've been ironing out those problems. And we've come up with a rig that should answer every amateur's prayer . . . the CX7A.

In fact, the CX7A makes all other amateur gear seem obsolete. It's like having a room full of sophisticated gear in one single desk-top unit.

See the CX7A at your signal/one dealer. Or write us today for a detailed brochure. You'll be perfectly delighted when you see what dedication to perfection has come up with. Even at \$2,195.

### Features:

1. Instant band change without tuneup.
2. Instantaneous digital frequency readout.
3. IF shift control.
4. Built-in pre-IF noise blanker.
5. All popular modes of operation.
6. Transceiver-plus-receiver operation.
7. Hang AGC levels out wide swings in signal strength.
8. All ham bands from 160 through 10 meters.
9. RF envelope clipping provides matchless talk power.
10. Metering of all critical functions.

 **signal/one**

a subsidiary of  
**Computer Measurements, Inc.**  
1645 West 135th Street  
Gardena, California 90249  
Phone: (213) 532-9754

# Why won't Don Wallace listen to anyone else?


W6AM doesn't have to, since he began using our professional quality VHF-FM 2 meter transceiver with exclusive *Astropoint*. The precise and powerful *Astropoint* system actually blocks out all interference. So when one of the nation's number one hams is having a 2-way conversation he won't have unwanted interference.

*Astropoint* is featured on all standard transceivers including the rugged, 12 channel SR-C826M.

It's not only a compact mobile but even fully portable with the addition of a battery pack. And there's a lot more that appeals to Don about the SR-C826M

than just *Astropoint*. All silicon semi-conductors with solid state circuitry. Ten watts of R.F. output power combined with low power consumption. MOSFET R.F. Amplifiers and mixers. And the list of features goes on.

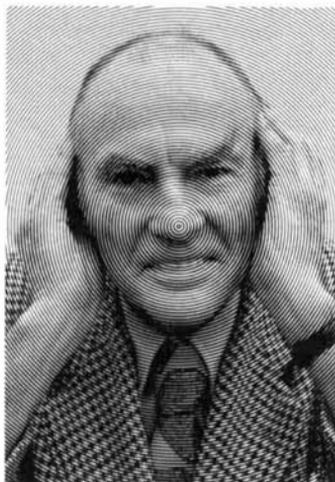Which is why Don Wallace hasn't been listening to anyone else lately. Not that he's choosy about who he listens to. Just whose equipment he listens on.



For complete specifications and the name of your nearest dealer, write:



**STANDARD  
COMMUNICATIONS  
CORP.**

639 North Marine Ave.,  
Wilmington, Calif. 90744  
(213) 775-6284



# Only an MC-4 can "top" a Drake TR-4



the optimum  
Sideband  
Transceiver

(Sometimes even  
the MC-4 ends up  
on the bottom . . .)



Adding an MC-4 Mobile Console, with its excellent wattmeter and built-in speaker, is the only way to improve a Drake TR-4.

## BUILT-IN TR-4 FEATURES

- Full Frequency Coverage on all amateur bands 10 through 80 meters. No additional crystals required.
- 300 Watts PEP input on SSB.
- Shifted-Carrier CW 260 watts input
- Upper and Lower Sideband all bands.
- Controlled-Carrier Screen Modulator for AM
- VOX or PTT
- Output Impedance Adjustable with pi-net.
- Two Special 9 MHz Crystal Filters for sideband selection.
- 1 kHz Dial Accuracy.
- 100 kHz Crystal Calibrator
- Price \$599.95 Amateur Net

## ACCESSORIES

MC-4 Mobile Console (shown in photos above) . . . . .	\$ 69.00
MMK-3 Mobile Mounting Kit . . .	\$ 6.95
AC-4 115/230 VAC 50/60 Hz Power Supply . . . . .	\$ 99.95
DC-4 12 VDC Solid State Power Supply . . . . .	\$125.00
34PNB Noise Blanker . . . . .	\$100.00

**TR-4 SPECIFICATIONS:** • **Frequency Coverage:** Full coverage on all amateur bands 10 thru 80 meters, in seven 600 kHz ranges: 3.5 to 4.1 MHz, 7.0 to 7.6 MHz, 13.9 to 14.5 MHz, 21 to 21.6 MHz, 28 to 28.6 MHz, 28.5 to 29.1 MHz, 29.1 to 29.7 MHz. • **Solid State VFO:** Has linear permeability tuning. Tunes 4.9 to 5.5 MHz for all ranges. • **Dial Calibration:** 10 kHz divisions on main tuning dial and 1 kHz divisions on the tuning knob skirt. • **Frequency Stability:** High stability solid state VFO tunes same range on all bands. Drift is less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change. • **Modes of Operation:** SSB Upper and Lower Sideband, CW and AM. • **Misc:** 20 tubes including voltage regulator; two transistors; 8 diodes; 100 kHz crystal calibrator built in; Dimensions: 5½" high, 10¼" wide, 14¾" deep. Weight: 16 lbs. . . . **TRANSMITTER:** • **Single Sideband:** 300 watts P.E.P. input power, VOX or PTT. Two special 9 MHz crystal filters provide upper or lower sideband selection on any band, without the necessity of shifting oscillators. • **CW:** Power input 260 watts. Carrier is shifted approximately 1000 cycles into one sideband, and mixer and driver are keyed. Grid block keying is free from chirps and clicks. Automatic transmit/receive switching when key is operated. CW sidetone oscillator for monitoring. • **AM:** Controlled carrier AM screen modulator is built-in. 260 watts P.E.P. input. Low carrier power increases 6 times to 50 watts output at maximum modulation. This system is compatible with SSB linears, VOX or PTT. Diode detector used for receiving on this mode. Product Detector can be used by switching manually . . . **RECEIVER:** • **Sensitivity:** Less than ½ microvolt for 10 dB S/N • **I. F. Selectivity:** 2.1 kHz at 6 dB, 3.6 kHz at 60 dB. • **Antenna Input:** Nominal 50 ohms. • **Audio Response:** 400 to 2500 cycles at 6 dB. • **Audio Output Power:** 2 watts. • **Impedance:** 4 ohms.

**MC-4 SPECIFICATIONS:** • **Frequency Coverage:** 1.8-54 MHz • **Line Impedance:** 50 Ohm resistive • **Accuracy:** ± (5% of reading +3 watts) • **Power Capability:** 300 watts forward or reflected • **Controls:** Front panel 2-position switch selects forward or reflected power • **Speaker:** 3" x 5" oval, 2.98 ounce ceramic mag.

**R. L. DRAKE COMPANY**  
540 Richard St. Miamisburg, Ohio 45342



**DRAKE**

Phone: (513) 866-2421

Telex: 288-017

June, 1972  
volume 5, number 6

**staff**

James R. Fisk, W1DTY  
editor

Douglas S. Stivison, WA1KWJ  
assistant editor

Nicholas D. Skeer, K1PSR  
vhf editor  
J. Jay O'Brien, W6GDO  
fm editor

Alfred Wilson, W6NIF  
James A. Harvey, WA6IAK  
associate editors

Curt J. Witt  
art director

Wayne T. Pierce, K3SUK  
cover

T. H. Tenney, Jr. W1N1LB  
publisher

Hilda M. Wetherbee  
advertising manager

**offices**

Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**ham radio** magazine is  
published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048

Subscription rates, world wide  
one year, \$6.00, three years, \$12.00  
Second class postage  
paid at Greenville, N. H. 03048  
and at additional mailing offices

Foreign subscription agents  
United Kingdom  
Radio Society of Great Britain  
35 Doughty Street, London WC1, England

All European countries  
Eskil Persson, SM5CJP, Frotunagrand 1  
19400 Upplands Vasby, Sweden

African continent  
Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1972 by  
Communications Technology, Inc  
Title registered at U. S. Patent Office  
Printed by Wellesley Press, Inc  
Wellesley, Massachusetts 02181, USA

**ham radio** is available to the blind  
and physically handicapped on magnetic tape  
from Science for the Blind  
221 Rock Hill Road, Bala Cynwyd  
Pennsylvania 19440  
Microfilm copies of current  
and back issues are available  
from University Microfilms  
Ann Arbor, Michigan 48103


Postmaster: Please send form 3579 to  
**ham radio** magazine, Greenville  
New Hampshire 03048



**ham**  
**radio**  
magazine
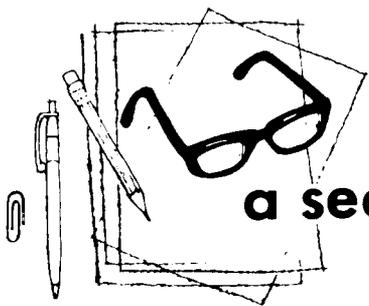
# contents

- 6 five-band communications receiver**  
M. A. Chapman, K6SDX
- 22 sequential switching for touch-tone  
repeater control**  
Richmond B. Shreve, W8GRG
- 30 RTTY ribbon re-inkers**  
Irvin M. Hoff, W6FFC
- 36 accurate vhf noise-figure  
measurements**  
Louis N. Anciaux, WB6NMT
- 42 digital multivibrators**  
Edward M. Noll, W3FQJ
- 50 sync generator for sstv**  
David R. Patterson, WA2EWO
- 53 getting started in microwaves**  
William T. Roubal
- 58 tape recorder operating aid**  
James R. Huffman, WA7SCB
- 4 a second look**                      **62 ham notebook**  
**94 advertisers index**                **64 new products**  
**42 circuits and techniques**      **94 reader service**  
**83 flea market**



## a second look

by jim  
fisk

Recently, I overheard a contact on 40 meters between two long-time amateurs who felt that amateur radio today just isn't as exciting, inviting and mysterious to today's youth as it had been to them forty years ago. They felt that in today's era of technological miracles, our hobby has less uniqueness and fewer opportunities to offer than it had in years past. Similar feelings have underlined many amateur discussions recently.

A. Prose Walker, W4BW, in speaking at amateur gatherings around the nation, has mentioned that amateur radio up to this day has been exciting and has seen tremendous technical progress and growth. But Mr. Walker maintains that the past has only been a prologue to what is to come.

Along with many others, we at *ham radio* note that the day of the amateur-built receiver may have passed in favor of the vastly superior and less expensive commercial version. However, look to the applications to which this commercial gear can be used for experimentation and growth.

Some oldtimers say that even the thrill of working DX is gone now — anybody with money and a big antenna can work all the DX he wants. Yet today we see the phenomenal growth of QRP as hundreds of old-timers and experienced kilowatt-wielders leave their high-power equipment to marshal three or four watts and chase DX across oceans or across state lines.

Modern solid-state technology and manufacturing techniques have provided

us with equipment which has fostered the amateur spirit — perfecting the art of getting the message through in spite of the limitations of equipment or power. Rather than making more "appliance operators," new low-power commercial equipment has presented new challenges and opportunities for fun and better training to help amateurs serve in the public interest.

A recurring theme of Mr. Walker's has been the undreamed of opportunities presented to today's amateurs by satellite communication. Rather than bemoaning the passing of the simple homebrew a-m transmitter, look toward the possibilities of intercontinental communication *when you want it* rather than at the whim of the ionosphere. The amateur's traditional communication expertise, inquisitiveness, patience, resourcefulness and determination must again come to the fore in this present and indescribably exciting field of amateur satellite communication.

Most importantly, though, our present level of sophisticated communications equipment gives us all the ability, and the real *responsibility*, to truly communicate with our fellow amateurs — either through the local fm repeater or on the other side of the world. And if that still isn't exciting, if it isn't challenging, if it isn't rewarding, if it isn't as new and vital as *today*, then maybe we should start the funeral dirge for amateur radio. However, I agree with Mr. Walker — the past is only a prologue to the future.

Jim Fisk, W1DTY  
editor

The most powerful signals under the sun!



# Got a space problem? Hy-Gain Has The Answer

Even if you're limited to just a few square feet of real estate, you've got room for a Hy-Gain multi-band vertical antenna. Unquestionably the ultimate in strength and performance... occupies minimum ground space. Whatever your requirements... you can't do better than Hy-Gain.

## The incomparable Hy-Gain Hy-Tower 18 Ht. For 80 thru 10 meters.

The finest multi-band omnidirectional vertical antenna on the market today. Entirely self-supporting and virtually indestructible. Takes maximum legal power with ease. Automatic band switching. All hardware iridite treated. *Outstanding performance!* Wt. 96.7 lbs. Ht. 50'  
**No. 182** **\$179.95**

## NEW! Hy-Gain 18 AVT/WB For 80 thru 10 meters.

Superb wide-band omnidirectional performance combined with extra heavy duty construction... for the red-hot action you want. So strong it mounts without guy wires. Automatic switching with three Hy-Q traps. Top loading coil. True 1/4 wave resonance on all bands. *A great buy!* Wt. 16.2 lbs. Ht. 25'  
**No. 386** **\$59.95**

## Versatile Hy-Gain 18 V For 80 thru 10 meters.

Low cost, high efficiency vertical antenna. Easily tuned to any 80 thru 10 meter band by adjusting feed point on the base inductor. Easily mounted, highly portable. *Installs almost anywhere!* Wt. 5 lbs. Ht. 18'  
**No. 193** **\$21.95**

## Hy-Gain 14 AVQ/WB For 40 thru 10 meters

Successor to the famous 14 AVQ... totally improved. Entirely self-supporting, automatic band switching, omnidirectional vertical antenna. Three separate Hy-Q traps with large diameter coils for very high Q. True 1/4 wave resonance on all bands. *Peak performance!* Wt. 9.2 lbs. Ht. 18'  
**No. 385** **\$39.95**

## Hy-Gain 12 AVQ For 10, 15 and 20 meters

Low cost, plus performance. Completely self-supporting vertical with Hy-Q traps. Low radiation angle for top performance. *Great antenna for your money!* Wt. 7.2 lbs. Ht. 13'6"  
**No. 384** **\$26.95**

## HY-GAIN ELECTRONICS CORPORATION

P.O. Box 5407-WF / Lincoln, Nebraska 68501





## five-band solid-state communications receiver

The A80-10 receiver —  
a straightforward  
reproducible design  
for 80- through 10-meter  
CW, ssb and a-m reception

This receiver, which I call the A80-10, has been designed for simplicity of construction, and uses standard solid-state circuits in a dual-conversion system. You can see from the photographs that an attempt was made to minimize the number of operating controls without compromising performance. So often, the extra knob (or switch) for some special feature is difficult to apply correctly, and many of them cause operator confusion.

The A80-10 receiver provides excellent amateur-band performance in any of the standard operating modes. The across-band sensitivity is less than  $1 \mu\text{V}$  for 10 dB S+N/N ratio. The passband is controlled by a Collins 2.1-kHz mechanical filter, with added skirt improvement provided by an i-f transformer serving double duty as an impedance-matching network.

Frequency drift is negligible. Either of two methods is available to the builder to minimize drift problems — NPO capacitor compensation or the installation of a British *Tempatrimmer*,\* an adjustable

\*The Oxley 6.5-pF *Tempatrimmer* is available from British Radio Electronics Limited, 1742 Wisconsin Avenue, N. W., Washington, D. C. 20007. The unit is priced at \$13.25; add \$.50 for postage and handling.

M. A. Chapman, K6SDX, 1262 Orkney Lane, Cardiff, California 92007

temperature-compensating device. Both methods satisfy today's stringent stability requirements.

The CW passband is effectively much less than that provided by the mechanical filter. An added op-amp audio filter allows peaking of any audio tone, thereby filtering out unwanted adjacent signals. A few minutes spent learning to operate the upper and lower bfo control with the CW audio filter should allow you to obtain passband selectivity that is adequate in the most dense operating conditions.

The A80-10 receiver has two poor functional features which should be pointed out. First, there are internal birdies at 7.0 and 21.0 MHz. The 7.0-MHz birdie is quite strong and can result in the loss of the bottom 2-kHz of the 40-meter band. Both birdies are second-overtone harmonics from the band-switching oscillator in the converter. The 21.0-MHz spurious is relatively small by comparison, but can be easily recognized. Second, the printed-circuit board, panel, etc., were not designed for a particular commercial cabinet.\* All peculiar parts, panels, etc., were developed for this design: *on the plus side*, the size of the PC board and grouping of operating controls lends itself to a variety of cabinets at the builder's option.

Receiver performance will be directly proportional to the builder's patience and efforts. Poor wiring and assembly practice will result in disastrous failure. As in any design, compromise and options exist.

table 1. Coil-winding data for the A80-10 receiver.

L1,L2	4 $\mu$ H. 25 turns no. 32 on Miller 4500-2 coil form. Link is 4½ turns no. 32 on cold end. Resonates to 14.2 MHz
L3	40 turns no. 32 on Miller 4500-3 coil form. Link is 10 turns no. 32 on cold end. Resonates to 3.9 MHz
L4	1.2 $\mu$ H. 10 turns no. 32 on Miller 4500-3 coil form
L5,L6	3.4 $\mu$ H. 20 turns no. 32 on Miller 4500-3 coil form
L7	1.2 $\mu$ H. 20 turns no. 32 on Miller 4500-3 coil form
L8	11 turns no. 32 on Miller 4500-2 coil form. Resonates to 24.5 MHz
L9	15 turns no. 32 on Miller 4500-2 coil form. Resonates to 17.5 MHz
L10,L11, L12	11 $\mu$ H. 40 turns no. 32 on Miller 4500-2 coil form. Link is 10 turns no. 32 on cold end
L13	15 $\mu$ H. 50 turns no. 32 on Miller 4500-2 coil form

Miller 4500 coil form is a slug-tuned ceramic form, 0.260" diameter. The -2 powdered iron slug (color coded red) is designed for the frequency range from 1 to 20 MHz. The -3 slug (color coded green) is designed for use between 20 and 50 MHz. Miller coil forms are available from the J. W. Miller Company, 5917 South Main Street, Los Angeles 90003.


The builder with a well-stocked parts reservoir will find a major portion of his receiver completed. The guy starting from scratch is up against it. Although there are a nearly infinite number of parts substitutions that can be made, only the gross types will be discussed.

## basic design

An overall schematic/block diagram is shown in fig. 1†. Briefly, the receiver uses the 3.5- to 4.0-MHz band as the first conversion frequency, mixing with a high-frequency oscillator for a second conversion to 455 kHz. A 2.1-kHz Collins

\*A complete set of drawings for the cabinet illustrated in the photographs is available from the author. Please include a large self-addressed, stamped, envelope.

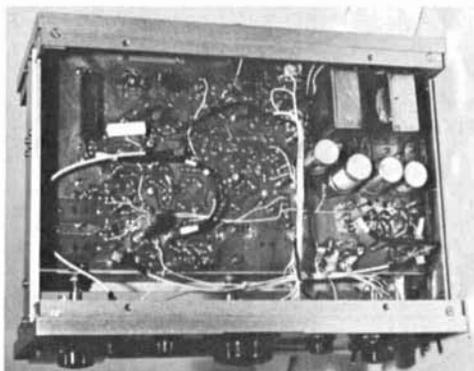†The power supply circuits, mixer circuit and 100-kHz marker oscillator are essentially the same as those published in the ARRL "Radio Amateur's Handbook," 1970 edition.



Rear view of the pc board.

filter shapes the passband. The 455-kHz i-f signal is then amplified and beat against an upper or lower sideband oscillator in a product detector. Detected audio is amplified by a single IC to the 1-watt level, suitable for low-power speakers. Higher frequency bands are

on a common PC board. Fig. 10 illustrates the functional arrangement for each section of the receiver. You can use your own judgement as to where to start. I found myself moving back and forth from section to section as components became available.

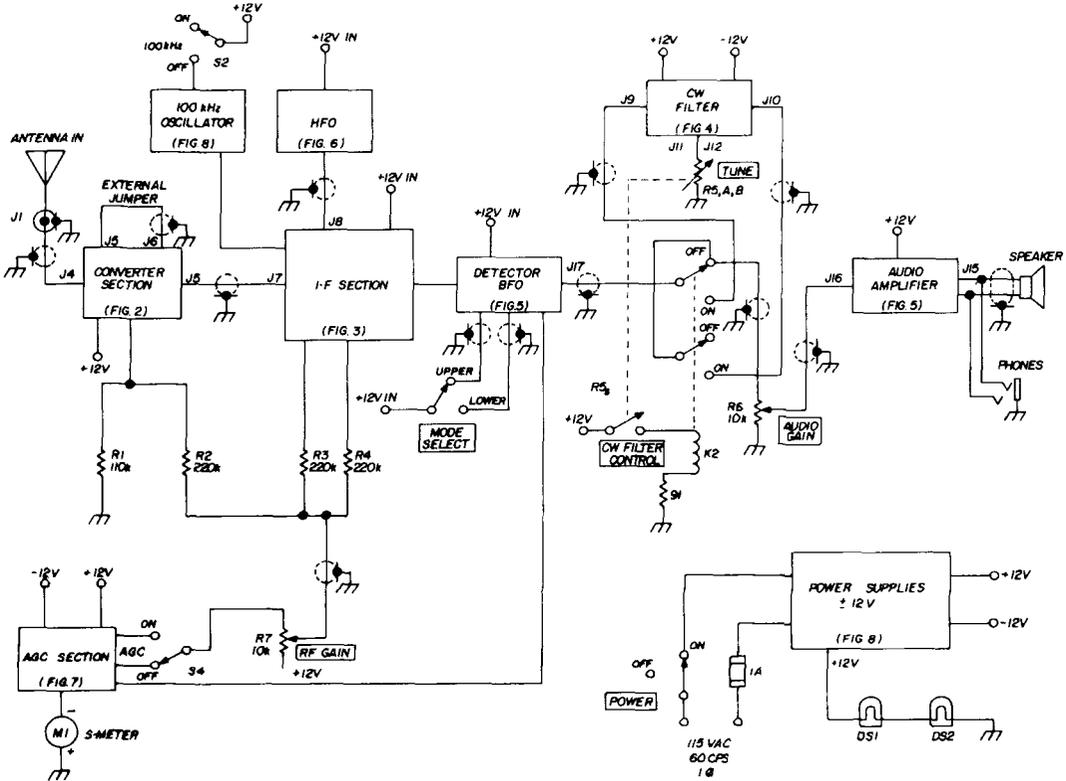


fig. 1. Block diagram of the all-band A80-10 high-performance communications receiver.

tuned with the simple two-stage crystal-converter method. Specific bands are selected from the front panel.

For CW operation, as previously mentioned, a tunable audio filter controls the detected signal. The same knob which is used for tone selection has a built-in switch which activates a relay circuit for in-out control.

### construction

As you can see from the photographs, all of the active components are mounted

The serious builder will be able to make an inventory of the items he needs and immediately recognize those items having long procurement times. I would suggest ordering the i-f transformers, filter capacitors and rotary switches immediately, even before the printed-circuit board is available.

The bfo crystal frequencies are determined by the 20-dB points of the Collins mechanical filter. It is important to obtain the filter before ordering the crystals. The bfo and 100-kHz marker

crystals are soldered directly to the PC board. Either ceramic or piston-type trimming capacitors may be used in the bfo and 100-kHz circuits.

If you like to do your own thing, the PC board layout in fig. 10 has enough information for taping and etching your

### construction sequence

The following sequence is a suggested procedure for building the A80-10 receiver:

1. Install all of the printed-circuit components, rf chokes and smaller filter components to the board.


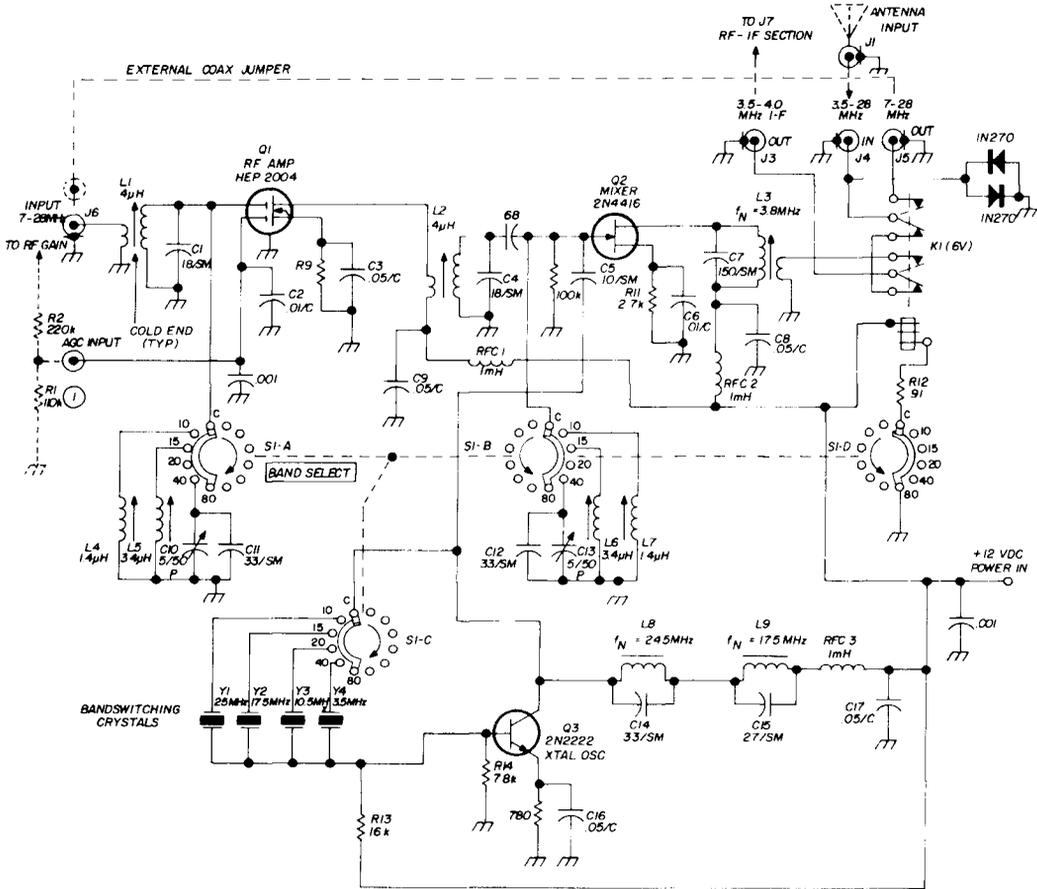


fig. 2. High-frequency converter covers the 40, 20, 15 and 10 meter bands. Complete coil-winding data is given in table 1.

own board, with whatever mechanical arrangements and component substitutions seem appropriate. However, fig. 13 is a half-scale layout of the PC board used in my receiver. A double-sided board is used, with the same circuit pattern on both sides for stiff ground plane and continuity.

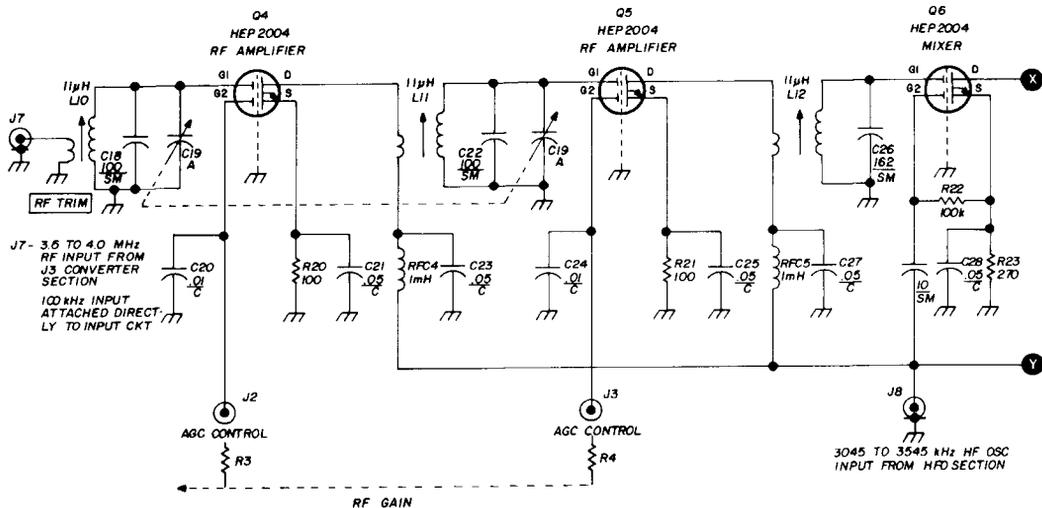2. Add the dc power straps and agc lines.
3. Install the ICs, transistors and fets (with the exception of the dual-gate mosfets).
4. Add the inductors; each of these coils has been wound several times so the turns ratios are accurate and considerable lati-



tude exists. Figs. 10 and 15 show the proper orientation of the inductor terminals.

5. Install the trimming capacitors.
6. Add the shields to the rf stage; 0.005 to 0.010-inch copper is suggested. If significantly thicker material is used, soldering to the PC board may be a problem (see fig. 14).
7. Add the shield to the converter stage.

8. Install the subpanel, rf peaking capacitor, bandswitch and the two relays.

9. Complete that portion of the wiring which interfaces with the subpanel components and the board.

10. Assemble the power-supply regulator panels and install them on the PC board along with the power transformers, rectifiers and filter capacitors. Add jumper wires to the regulator panels, but do not hookup the dc buses at this time.

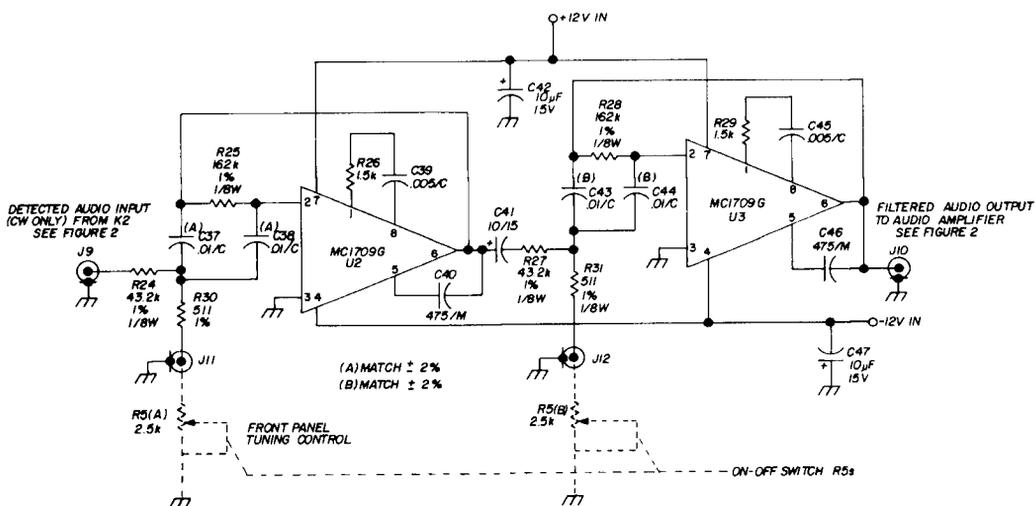


fig. 4. Audio filter provides excellent selectivity for CW communications.

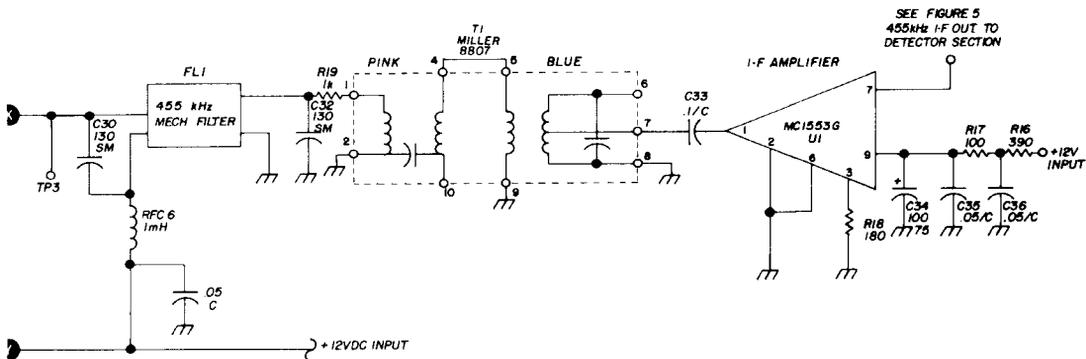


fig. 3. Circuit of the 3.5- to 4.0-MHz rf amplifier and 455-kHz i-f. The Collins mechanical filter provides desired selectivity.

11. Install the assembled printed-circuit board and subpanel into the cabinet. Fig. 10 shows the brackets and supports which adapt the sub-assembly to the cabinet.
12. Add the front panel components and interwiring except for the S-meter wiring.

### construction hints

The rf tuning capacitors and band-switch are all mounted on the same center-line. Use the switch mounting feet as a common point for mounting the PC board; the bushings are mounted on the subpanel as indicated in the cross-section

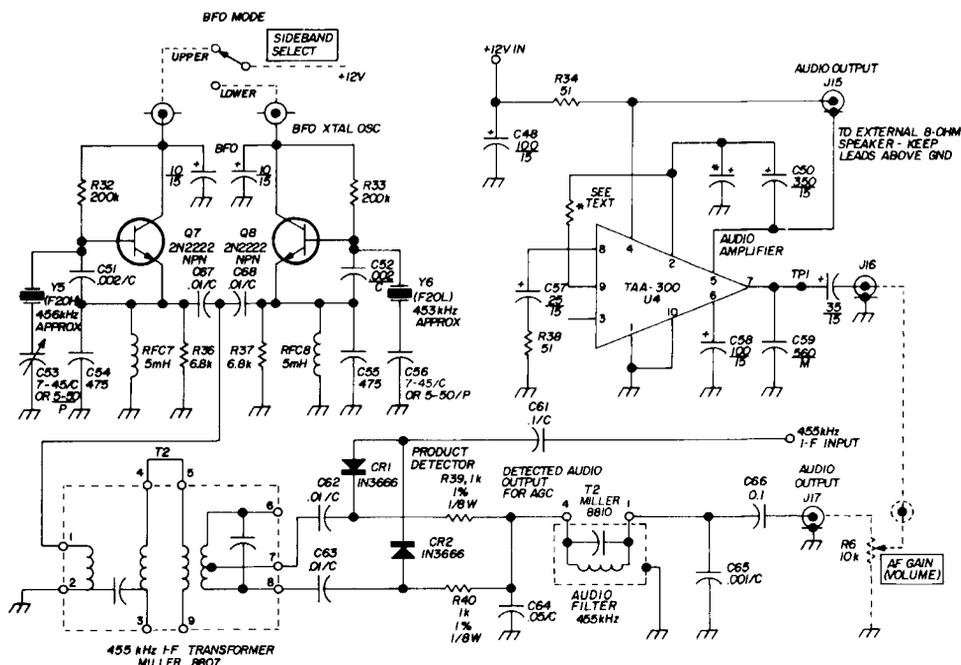


fig. 5. Bfo, product detector and audio amplifier circuits.

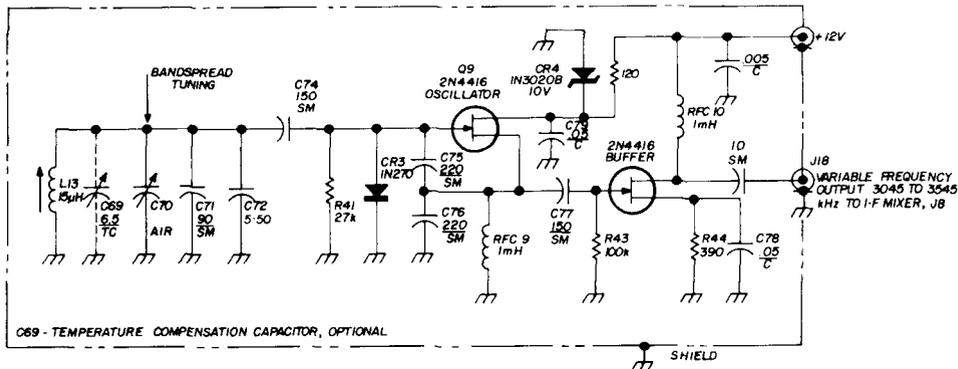


fig. 6. High-frequency oscillator circuit has excellent stability and low drift characteristics.

views in figs. 11 and 12. I found that the *feel* of the Centralab PA-2021 rotary switch was poor; there are ball-detent switches similar to the PA-2021 which you may want to use. Both Oak Manufacturing and Centralab have good miniature ball-detent units.

To make maximum room available for adding the jumper wires between the converter components and the band-switch, remove all the excess contacts. This will minimize coupling problems as well. Referring to fig. 10, the shields between stages in the i-f and converter sections are just high enough to clear the

ends of the inductors; a small bead of solder is run along the bottom of the shield as shown in fig. 14.

To provide for maximum slug adjustment in the inductors, the coils should be wound as shown in fig. 15. Complete winding data is given in table 1.

In my receiver I used no. 20 solid,

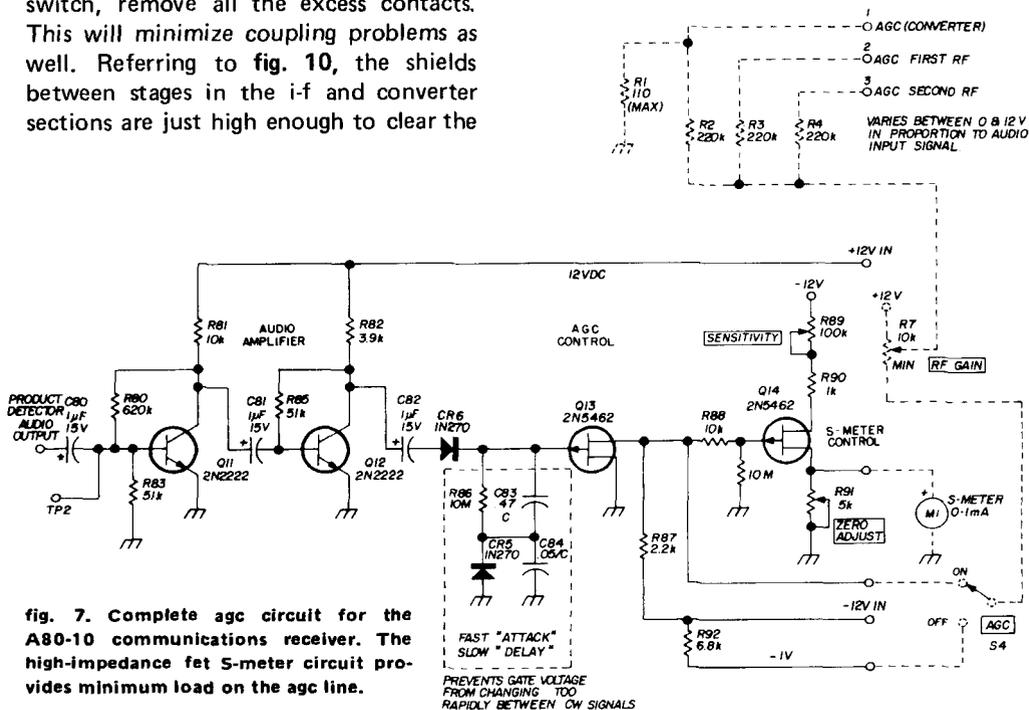


fig. 7. Complete agc circuit for the A80-10 communications receiver. The high-impedance fet S-meter circuit provides minimum load on the agc line.

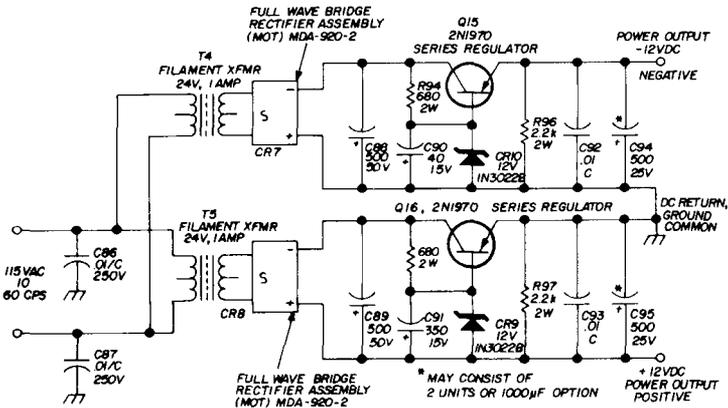


fig. 8. Regulated power supply for the receiver provides plus and minus 12 Vdc.

tinned wire for the jumpers from the tuning inductors to the printed-circuit board, bandswitch and resonating capacitors. For all other wiring I used no. 24; miniature coaxial cable was used for shielded leads.

If you look at fig. 10 you will see that there is an offset between the integrated-circuit terminal centerline and the printed-circuit pads. The ICs should be installed as shown in fig. 16. The IC lead offset provides stress relief for the leads as well as allowing larger pad sizes to simplify etching the board. Note that the ICs are all installed from the back side of the board.

I tried HP2800 hot-carrier diodes in the detector, agc rectifier and agc attack circuits without significant improvement. These diodes provide low forward voltage drop and high leakage; however, the use of 1N270, 1N191, 1N914, 1N100 or 1N3600 diodes in these circuits provides almost equivalent performance. Don't be hesitant about using any good germanium device in the detector and agc attack circuits. Almost any good silicon rectifier will work well in the high-frequency oscillator circuit.

## semiconductors

Transistor types used in the A80-10 receiver were standardized wherever possible. For example, all small-signal bipolar stages are handled by the 2N2222, an npn

high-speed switching transistor. However, any general-purpose npn transistor may be used so long as it has comparable current gain ( $h_{FE} = 50$  minimum) and adequate voltage ratings.

In the agc circuit, transistor Q11 is operated class A, but saturates with strong signals. Transistor Q12 operates almost entirely in class B to accentuate positive pulses and provide a wider gate voltage swing on Q13. Some adjustments in bias values may be necessary if substitute transistors are used in these stages.

The 2N5462 p-channel depletion-mode fet used in several stages is a


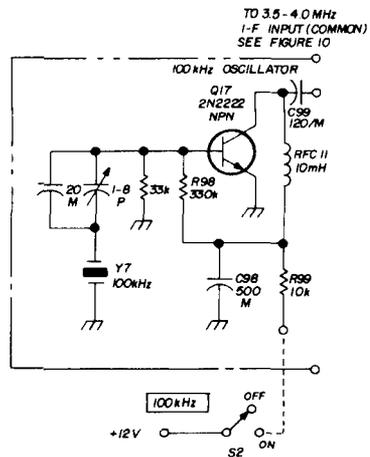


fig. 9. Circuit for the 100-kHz marker oscillator.

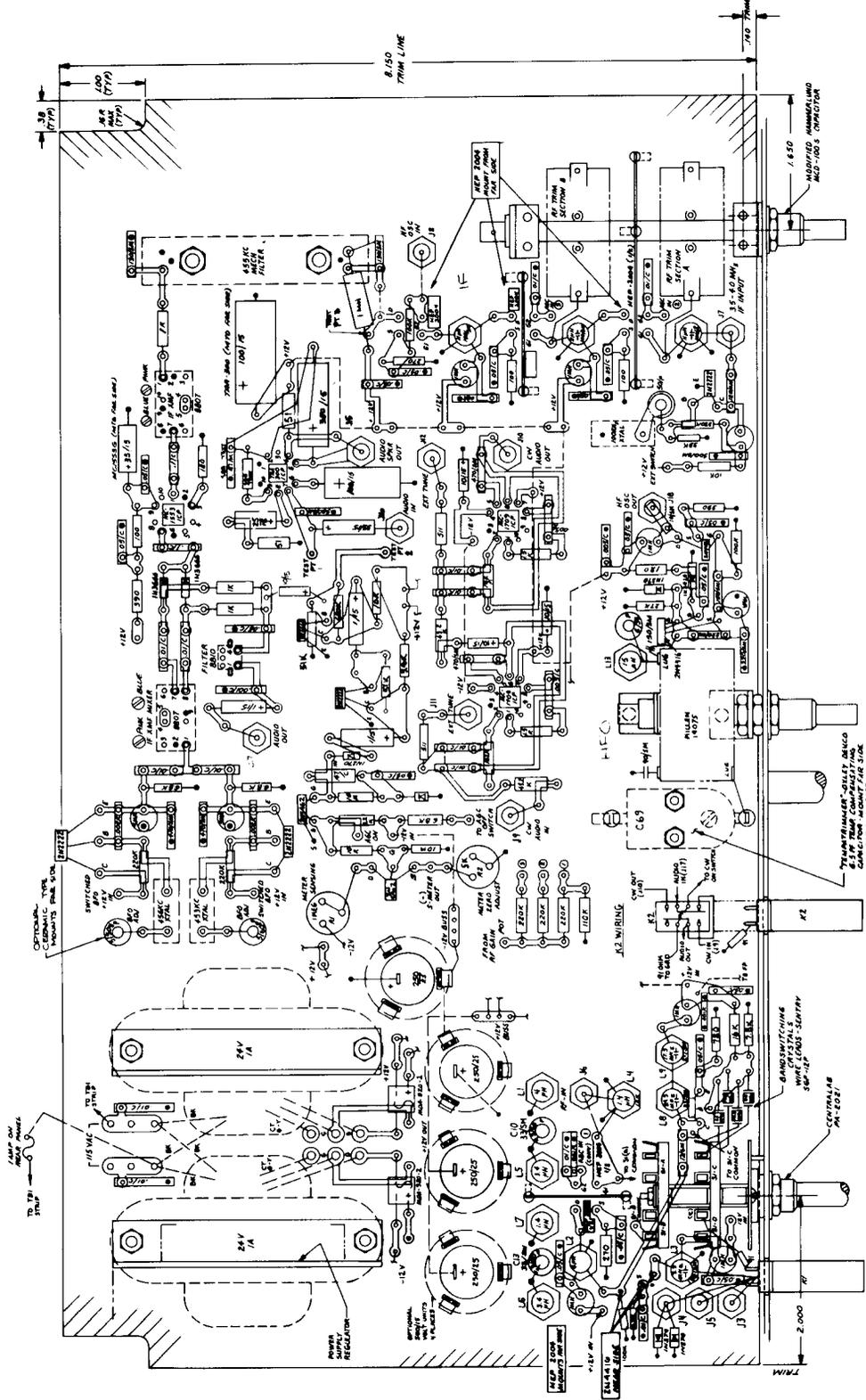


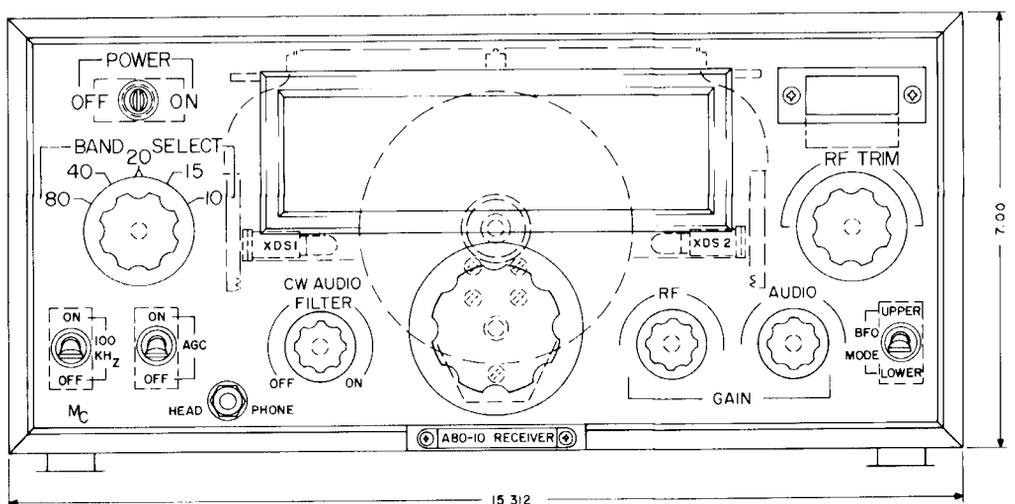
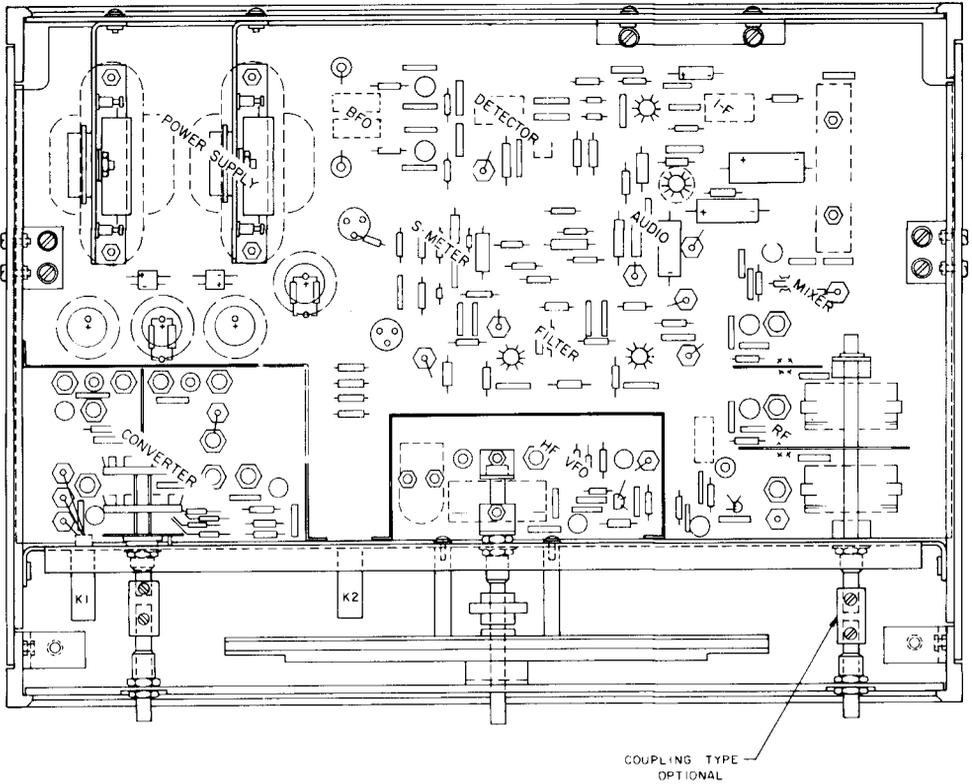


fig. 10. The complete parts layout for the A80-10 is shown on the facing page, the printed-circuit layout is shown in fig. 13 and the construction and panel layout of the receiver is shown above.

general-purpose type. The 2N5463 or 2N4360 are acceptable substitutes. Since large variations in gate voltage vs drain current between different devices will cause the maximum agc voltage swing to vary considerably, it's a good idea to have several transistors to select from. Adjust

diodes are installed across the antenna input circuits for over-voltage protection.<sup>1, 2</sup>

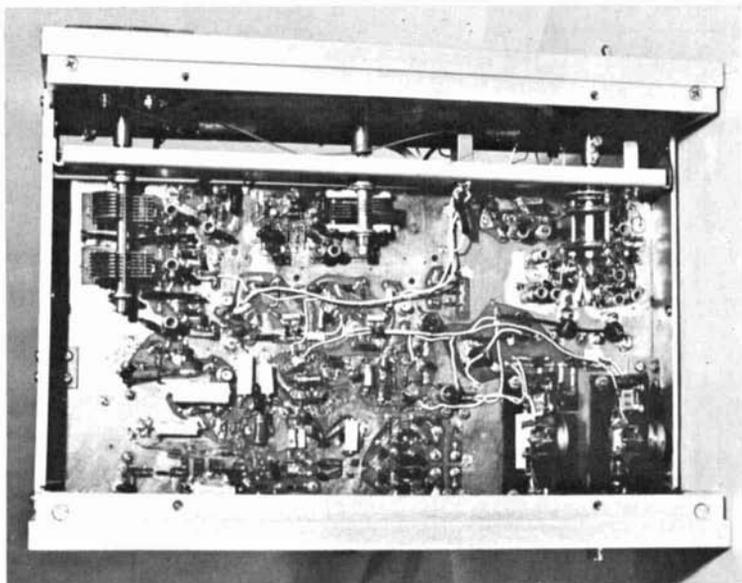A Motorola MC-1553G wideband linear amplifier IC was selected for use in the A80-10. The MC-1552G may be used with somewhat reduced gain and sensi-



Top view of pc board with converter and hfo covers removed. The i-f is along the left, the hfo is in the middle.

the 2.2k agc drain resistor slightly (between 1.5k and 3k) to maximize the agc voltage swing.

The 2N4416 n-channel fet used in the rf amplifier and mixer stages provides exceptionally good noise figure. Alternate types, which work well in these circuits, are the 2N3823, 2N5459, MPF-102, MPF-105 and MPF-108. However, the 2N3823 is the best choice for low mixer noise and maximum vfo output voltage.

The HEP-2004 dual-gate mosfet is used in the vhf amplifier and mixer circuits. The MFE-3006, MFE-3007, MFE-3008, MPF-120, MPF-121 and MPF-122 are superior substitutes since wider gain variations can be expected from the HEP-2004. However, there is sufficient i-f gain to offset this, and the cost of the HEP-2004 is much less than the recommended substitutes. Protective

activity. I experimented with some similar ICs manufactured by RCA, but they all required an additional buffer stage to obtain equivalent results. The cost of the MC-1553G is relatively high, but well worth the investment because of the circuit simplicity it provides.

Although I used the Motorola MC1709C operational amplifier in the audio filter, a variety of suppliers makes this same device, including Fairchild (W5B77092IX), Philco (PA70931), Raytheon (RM4709) and Texas Instruments (SN52709L). In a recent issue of *ham radio*, WA1JSM discussed some additional design features of this device, as well as applications.<sup>3</sup>

The Amperex TAA-300 audio amplifier IC used in the audio power amplifier stage provides 1-watt into an 8-ohm load. This device requires a heat sink. You may

want to obtain a copy of the Amperex data sheet on this device since there are considerable variations in external capacitors and feedback resistors for various operating requirements.<sup>4</sup>

In some installations, to prevent instability, you may have to connect a capacitor (47 pF minimum) from pin 2 of the TAA-300 to ground. The printed circuit board indicates this component location. However, motorboating may result if this capacitor is installed prior to test and found not to be required. Some devices may require an additional capacitor (100 to 500  $\mu$ F) from pin 4 to ground to prevent low-frequency oscillation.

### test and alignment

Before applying any power, double check all your wiring connections, checking for continuity and short circuits. Check all transistors, capacitors and ICs for correct orientation. Without the power-supply regulator section connected to the circuit, you should obtain the following resistance readings from the plus and minus 12-volt lines to ground:

- +12V bus approximately 50 ohms
- 12V bus approximately 400 ohms

These measurements are made with the dual-gate-mosfet transistors installed in the board.

Apply ac power to the unloaded power supplies. The output voltage should be between 11.2 and 12.2 volts. Variations in zener-diode tolerances cause wide variation in output voltages. If the power supply voltages are within tolerance, connect the  $\pm$ 12-volt outputs from the regulator circuit to the corresponding bus points on the printed-circuit board.

Apply a 5- to 15-mV, 1000-Hz audio signal to TP-1. If the speaker is disconnected, install a 10-ohm resistor across the two output leads; connect a scope across the resistor — the audio signal will be displayed on the scope if everything is working properly. Of course, if the speaker is connected, you will hear the 1000-Hz tone.

Disconnect the speaker and install a 10-ohm resistor in its place. To properly

test the agc circuit all of the rf stages must be tested and aligned. For preliminary agc alignment, however, apply a 25- to 50-mV audio signal to the base of Q11; varying this input voltage should cause a corresponding variation in negative voltage at the drain of Q13. If all is going well, a zero audio level applied to the base of Q11 should result in a corresponding Q13 drain voltage of -1 V; increasing the audio signal level to 25 or 50 mV should cause the Q13 drain voltage to change proportionately to -6 or -9 volts.

If the Q13 drain voltage swing is not as large as indicated, then something is wrong. Since Q11 is operating in class A, the collector voltage should be about 6 V, and the output signal should be nice and clean except when overdriven — then the output should start saturating a little. If Q12 is operating correctly the collector voltage should be about 1 or 2 volts with no signal, and 6 to 10 volts with a high input and some saturation may be apparent; i. e., the output could consist of square waves at about 6 to 10 volts positive.

The gate voltage on Q13 should be slightly less than the collector voltage of Q12, and vary in direct proportion. With this much gate voltage swing the drain current should cause the previously indicated voltage variations across the 2.2k resistor. I had to play a little with this circuit since there are so many variables between different fets that under some circumstances Q12 can operate in class A. Just a few volts on the gate of Q13 will provide a significantly large agc voltage. The circuit in **fig. 7** gives a little larger gate voltage swing under touchy CW conditions where the large agc voltage will save your eardrums.

Another agc circuit which works well if the beta of the transistors is high is shown in **fig. 17**. Note that the value of the coupling capacitors between stages is unimportant so long as you use a minimum value of 0.1  $\mu$ F. If higher values are used as suggested in **fig. 7**, there is an improvement in low-frequency response. Diode CR6 can be any device exhibiting

low forward voltage drop and moderate to high leakage such as the 1N914 or 1N191. Other circuits you might want to try are shown in Bill Orr's "Radio Handbook."<sup>5</sup>

### s-meter

The 1970 ARRL "Radio Amateur's Handbook" suggests a typical S-meter

Adjustment of the S-meter circuit is quite simple since the sensitivity can be set for any preferred rf reference level. The meter responds to the decay agc feature so it does not hang up on a-m signals.

### high-frequency oscillator

If this circuit is properly wired, and

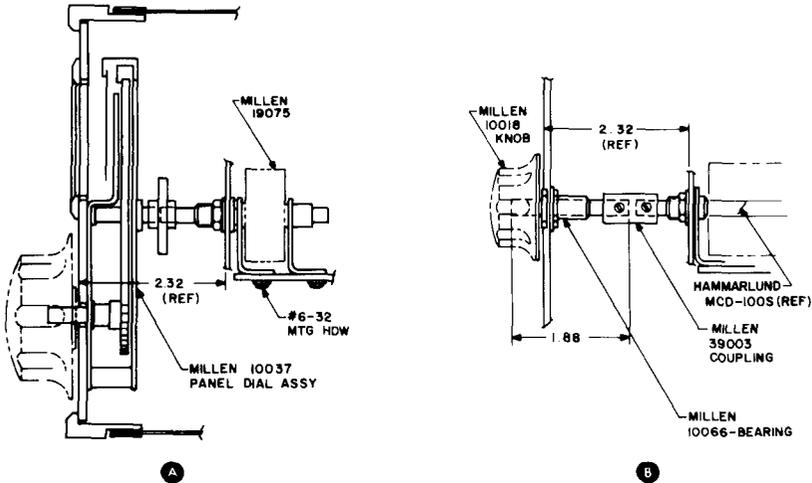


fig. 12. Construction details of the main tuning dial (A) and the rf trimming capacitor (B).

circuit for receivers which use negative agc lines. However, the input impedance of the circuit is so low it severely loads the agc line. The fet S-meter circuit I used in the A80-10 (see fig. 7) is similar to the ARRL circuit, but does not load the agc line.

the coil is properly wound, there is absolutely no way that it will not work (see fig. 6). To align the oscillator, first set the bandspread capacitor to the center position. Grid dip the coil to the same approximate frequency (3.25 MHz) and apply power. Signal output should be from 1 to 3 volts peak, depending on the transistor used in the circuit.

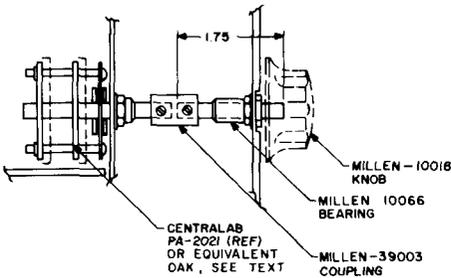


fig. 11. Construction details of the band-selection switch.

The oscillator may be built without the *tempatrimmer* if you wish. If the *tempatrimmer* is not used, the 100-pF silver-mica capacitor should be an NPO type to compensate for temperature drift. The voltage of the zener diode is unimportant - 8, 9 or 10 volts is satisfactory. If you use an 8- or 9-volt zener, slightly increase the series resistance.

The L/C ratios used in the oscillator will allow you to adjust the oscillator from 350 to 500 kHz on five bands. This

means that if you are particularly interested in a certain segment of the bands, by properly selecting the converter crystals and adjusting the L/C combination, bandspread of a particular band segment can be adjusted to suit your interest.

Let's assume that you are interested in a straightforward 500-kHz bandspread as

results will provide temperature drift levels less than 25 Hz hour.

Probably the easiest i-f section to build and align is the one shown in fig. 3. The coils are easily wound with an error latitude of one or two turns. The coil/capacitor assembly is shown quite clearly in fig. 10. Put the trimmer capacitor (C19) in the half-mesh position, grid dip

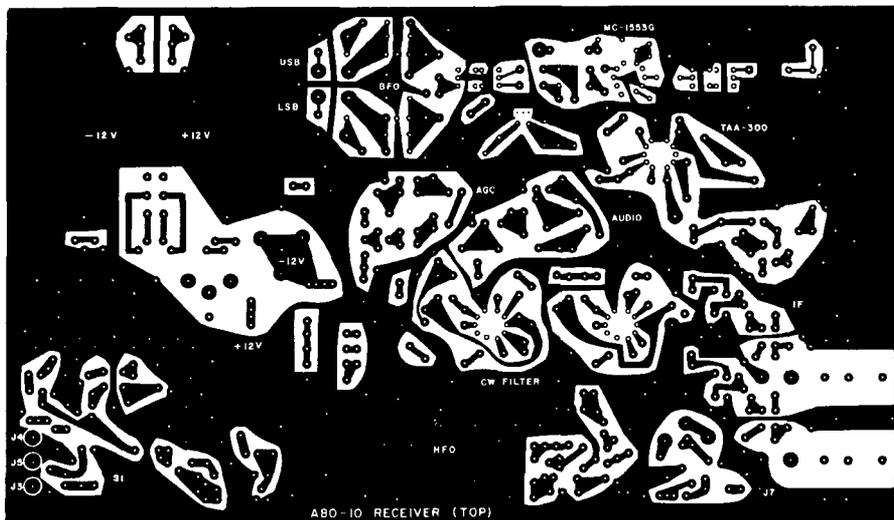


fig. 13. Printed-circuit board layout for the A80-10 communications receiver. Full-size templates are available for 25c from ham radio. Printed-circuit boards with critical component holes drilled are available from Spectrum Research Laboratory.\*

illustrated. Not too much trial and error is required to obtain low end frequency output at 3045 kHz with maximum capacitance and minimum slug; then tune to the other end of the scale, setting the inductor slug to a frequency slightly lower, and then backing off the capacitor. Returning to the low end and trimming both inductance and capacitance should get the oscillator into the required tuning range (3045 to 3545 kHz) within 4 or 5 tries.

Let the receiver operate for 72 hours, retrim the tuning components, and then coil-dope the L13 slug and capacitors into position. Adjustment and installation of the *tempatrimmer* is best accomplished using the manufacturer's instructions; the

the inductor slugs to 3750 kHz in each of the rf and mixer stages. Recheck circuit wiring and make sure that agc voltage is available at the mosfet gates.

Apply a 5-mV signal to the output of the 455-kHz mechanical filter or at TP3. If the i-f amplifier is operating correctly, an oscilloscope will display an audio signal at the audio input capacitor or across the 10-ohm load resistor. If you have finished the agc and S-meter sections, then visible S-meter movement

\*Printed-circuit boards are available from Spectrum Research Laboratory, Inc., P. O. Box 5824, Tucson, Arizona 85703. The double-sided plated, completely drilled board is \$27.50, including handling and postage.

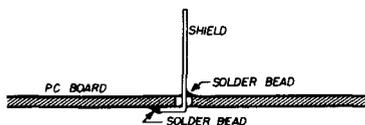


fig. 14. Installation of shields on the printed-circuit board.

should occur and agc control should be apparent by putting the agc switch in the *on* position and varying the 5-mV 455-kHz input signal from 1 to 15 mV while monitoring the mosfet gate voltages.

Install the dual-gate mosfet in the rf and mixer stages. Connect the hf oscillator to the mixer. Apply a 30- $\mu$ V 3750-kHz signal to the input connector of the i-f and attach the oscilloscope to the output of the i-f amplifier IC. Tune the hf oscillator to a point where an i-f output is apparent. Adjust both slugs of the i-f transformer for maximum output signal. Adjust coils L12, L11 and L10, in that order, for maximum output signal. Now go back and readjust all trimmer components for 3750 kHz, and zero adjust the band-spread and capacitor trimmer. At this point, the receiver may be used for 80-meter reception.

To verify receiver operation, apply a 1- $\mu$ V signal to the input with an oscilloscope monitor at the audio output. Tuning across the 1- $\mu$ V signal and peaking the trimming controls should produce an obvious audio signal. With a 30- $\mu$ V signal applied, 100% modulated with 1000 or 400 Hz, the upper and lower sideband trimming capacitors in the bfo circuit can be adjusted to provide audio reception at the appropriate level. Individually tune the bfo capacitors for maximum audio

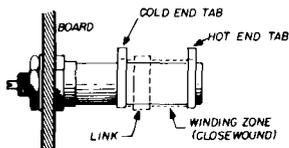


fig. 15. Inductor assembly. Complete coil winding data is given in table 1.

output. The output levels can be matched by adjusting R32 and R33.

## cw filter

Properly wired and with good op-amps, the CW filter circuit should function immediately. Review the wiring of relay K2; turning the CW control clockwise should activate the relay, switching the audio through the operational amplifier circuits rather than directly to the audio amplifier. The potentiometer provides tunable audio; for CW operation a particular beat-note may be accentuated over another adjacent signal, much like a Q-multiplier. CW operators will find that by carefully using either the upper or lower bfo positions and the CW audio filter, passband characteristics will be equivalent to a 500-Hz filter. If you don't

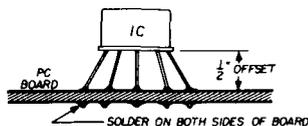


fig. 16. ICs are slightly offset as shown here to provide stress relief.

want to use 1% precision resistors, matched carbon composition types with values close to those indicated in fig. 4 are quite suitable for this circuit.

## oscillators

Any npn transistor with current gain greater than 50 should work without difficulty in the bfo and 100-kHz oscillators. In the 100-kHz oscillator, substitution of an inductance value other than 10 mH will cause odd collector loading and erroneous oscillator frequencies. Adjustments in the collector-to-base resistor  $R_A$  will correct for variations in device gain and crystal impedance (see fig. 18).

## converter section

To align the converter, the following procedure is suggested. First, verify the operation of transistor Q3, the crystal oscillator, moving the switch from the 40-

through 10-meter positions. Oscillator operation should be apparent by monitoring the common terminal of S1-C for the signal; the voltage level may vary between crystals. Some difficulty may be experienced in obtaining stable oscillation on the correct frequency in each of the oscillator positions. Variations in impedance between crystals will cause the base bias voltage to shift and cause erroneous output. Some adjustment of R13 and R14 is required, depending upon the device you use. In the circuit in fig. 2, the gain of the transistor was approximately 85. VE3GFN suggests a slightly different circuit;<sup>5</sup> however, I was not able to duplicate his circuit and obtain a stable output signal in all four crystal positions.

Minimum output voltage in the 10-meter position is approximately 1 volt.

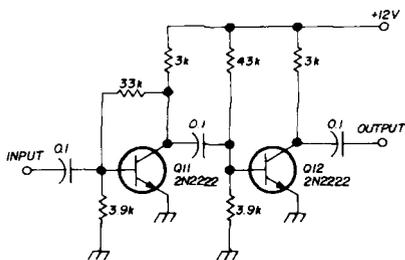


fig. 17. Alternate agc circuit.

Inductors L8 and L9 should be peaked for maximum signal output level at the appropriate crystal frequency. Grid dip L1 and L2 for 14.2 MHz, and L3 at 3.8 MHz. Put the band selection switch in the 20-meter position and apply a 100- $\mu$ V 14.250-MHz signal to the antenna input. With a scope monitoring either the i-f amplifier output or the audio output, tune the hf oscillator for apparent signal reception. Adjust L3 for maximum signal output. Apply a 10- $\mu$ V signal to the antenna input and adjust L1, L2 and L3 for maximum output level.

Put the band selection switch in the 40-meter position and apply a 100- $\mu$ V 7.250-MHz signal to the antenna input. Adjust only C10 and C13 for maximum output signal.

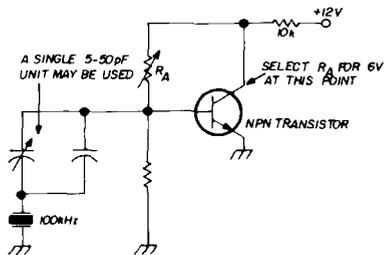


fig. 18. When initially adjusting the bfo or 100-kHz oscillators using other than the recommended transistors, it may be necessary to select the base-to-collector resistor  $R_A$  to compensate for variations in transistor gain and crystal impedance. Adjust  $R_A$  for 6 volts at the collector of the transistor.

The 10- and 15-meter bands are aligned in the same way, peaking the appropriate inductors for maximum signal. Final trimming of all inductors should be made again after installing shielding or covers around the converter section.

Some sensitivity and gain losses can be expected on 10 meters if you substitute different devices. Substitution of HEP 2004 transistors and adjustments in the value of R1 may be necessary. The more stable MFE-3006, MFE-3007 or MFE-3008 might prove useful.

And last, but not least, adjust transformer T2 for minimum 455-kHz speaker hiss.

#### references

1. Donald W. Nelson, WB2EGZ, "Deluxe Mosfet Converters," *ham radio*, February, 1971, page 41.
2. "Small Signal RF Design with Dual-Gate Mosfets," Motorola Semiconductor Data Book, 5th edition, October, 1970, page 11-46.
3. N. J. Nicosia, WA1JSM, "A Tunable Audio Filter for CW," *ham radio*, August, 1970, page 34.
4. "The Amperex TAA-300 Monolithic Integrated Circuits Used as a Complete Audio Amplifier," Amperex Application Report S-138.
5. William I. Orr, "Radio Handbook," 18th edition, Editors and Engineers, 1970, pages 634-645.
6. Paul Hrivnak, VE3ELP, "Integrated-Circuit Communications Receiver for 80 Meters," *ham radio*, July, 1971, page 6.

ham radio

# integrated-circuit sequential switching for Touch-Tone repeater control

Modular construction  
combined with  
three-digit  
sequential decoding  
gives this  
all-IC unit  
flexibility  
with immunity from  
accidental keying

R. B. Shreve, WBGRG, 2842 Winthrop Road, Cleveland, Ohio 44120

**Touch-Tone signals**, which combine one frequency below 1 kHz with one above to represent each of ten digits, can be decoded with filters and relays or with integrated circuits. The Bell System 247B KTU uses LC filters, transistors and relays; a solid state IC decoder is described in the July, 1971 *QST*.<sup>1</sup> Either will provide a discrete digital impulse for each Touch-Tone signal received.

Using one of these impulses to control a switched circuit is easy — so ten tones should make it possible to perform ten functions. And they would, if no one else ever transmitted the same tones on the frequency you selected for a control frequency. To make a system that will act only on signals addressed to it and disregard all others, circuits are needed that will recognize multiple digits in a prescribed sequence. This article describes such a system.

## design requirements

What should a Touch-Tone control unit for a repeater provide? At the Lake Erie Amateur Radio Club repeater, WB8CQR, the objectives were:

1. Accept Touch-Tone signals as reproduced at the output of a standard fm receiver.
2. Retransmit signals not addressed to the repeater control, but otherwise disregard them, so that others can use Touch-Tone on the same frequency

without interfering with the repeater controls.

3. Recognize signals directed at the control unit, interpret them and act on them without retransmitting them.

4. Disregard erroneous, irrelevant or incomplete codes, resetting to its stand-by state automatically.

The control unit is designed for a repeater with the transmitter and the primary receiver about a half mile apart, connected by a single telephone pair. There are two receivers on the primary input frequency, one at the main receiver site and one remote, both tone guarded. A second receiver at the main site, on a secondary frequency and unguarded, is used principally by base stations.

Wire control of the transmitter from a number of remote points is provided in accordance with the station license. The Touch-Tone control unit, located at the main receiver site, supplements the wire control but does not replace it. The Touch-Tone unit performs the following functions:

1. Disables the keying circuit to the transmitter, without affecting the receivers.

2. Switches the output to an alternate frequency.

3. Switches a guarded receiver from tone guarded to open.

4. Disables each receiver separately. The disabling circuits are interlocked so that it is impossible to disable all inputs at the same time.

Since each of the listed functions must be reversible, a total of twelve codes is required. Although two-digit codes would suffice, and allow plenty of room for expansion, it was felt that three-digit codes would give enough greater security against false or accidental keying to justify the additional equipment.

To get greatest flexibility during development and maximum adaptability to future change, all integrated circuits are grouped in modules, on etched circuit boards. The boards are plug approximately four inches square and plug into sockets


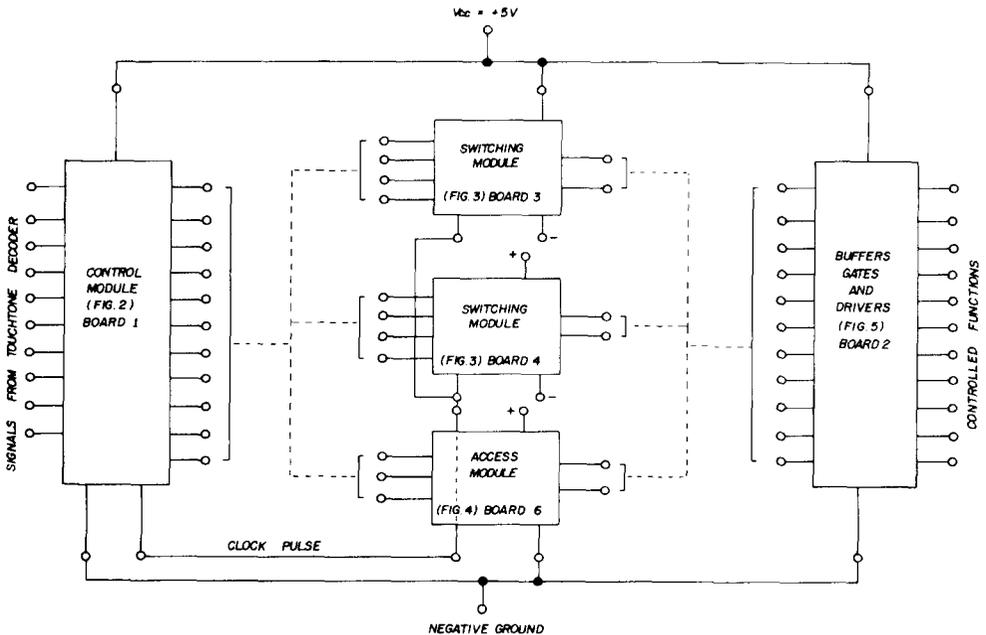


fig. 1. Overall block diagram showing relationship between all modules.

The unit occupies one half of a 19-inch rack. On the left is the power supply; the tops of the logic boards are visible to its right behind the panel on which indicator lights show the status of the six functions controlled. Space is provided for two additional lights if another switching module board is added later. The box in the foreground is the local control unit, with ten digital keys in the Touch-Tone pattern, a button to key the transmitter and a light showing when the gate is open to permit access to the unit.

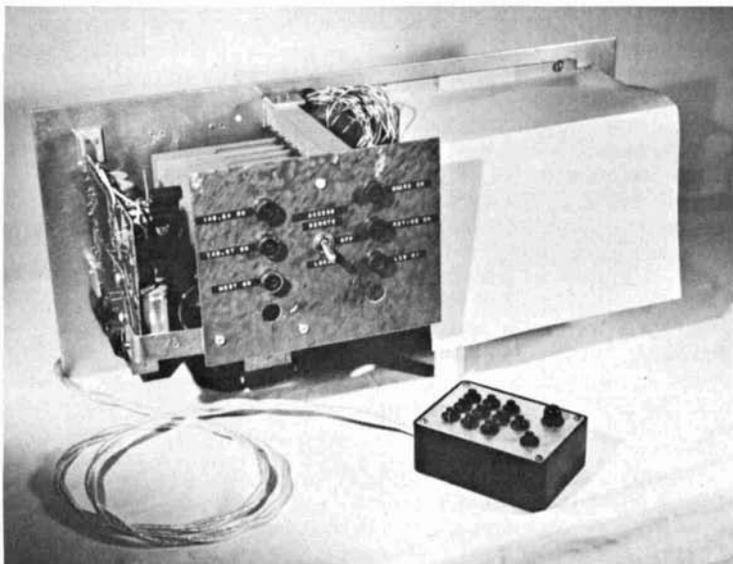

that provide 22 possible connections to each side of the board. There are four types of modules, as shown in **fig. 1**. They are:

**Control module** (board 1, **fig. 2**). Processes incoming Touch-Tone signals and generates a clock pulse to drive the J-K flip-flops on the other circuit boards.

**Buffers, gates and drivers** (board 2, **fig. 5**). Provides additional logic elements to expand and combine outputs of other circuits.

**Switching modules** (boards 3, 4 and 5, **fig. 3**). Identical switching modules, two on each board; each module performs one on-and-off function.

**Access module** (board 6, **fig. 4**). A special switching module and timer that controls access to the switching modules.

Audio input to the decoder is taken from a circuit that also carries the transmitter audio input, so that tones heard by the decoder are also retransmitted if the transmitter is keyed. The decoder is one that grounds one of ten output terminals for the duration of each tone combination representing a digit. If the Blakeslee

solid-state decoder is used, output inverters should be used, or the NOR gates in the output circuits should be replaced with POSITIVE OR gates, so that each Touch-Tone digit is represented by a "low" decoder output.<sup>1</sup>

### control module

The control module circuitry is shown in **fig. 2**. Decoder outputs are connected to terminals 2, 4, 6, 9, 11, 13, 15, 17, 18 and 20. For each input an inverted output is provided at the adjoining terminal. These outputs are the digital impulses used to drive the sequential switching circuits. Eight of the digits are also connected to the inputs of an SN7409 quadruple AND gate used to expand the input capability of one half of an SN7413. The other two digits are connected directly to the SN7413 inputs — which digits to which inputs is immaterial; the arrangement shown was the simplest circuit-board layout.

The Texas Instruments SN7413 is a dual quad-input NAND gate with Schmitt-trigger action, characterized by hysteresis of about 0.8 volts between the levels of the turn-on and turn-off input signals. This makes it possible to operate one half of the gate as a multivibrator by

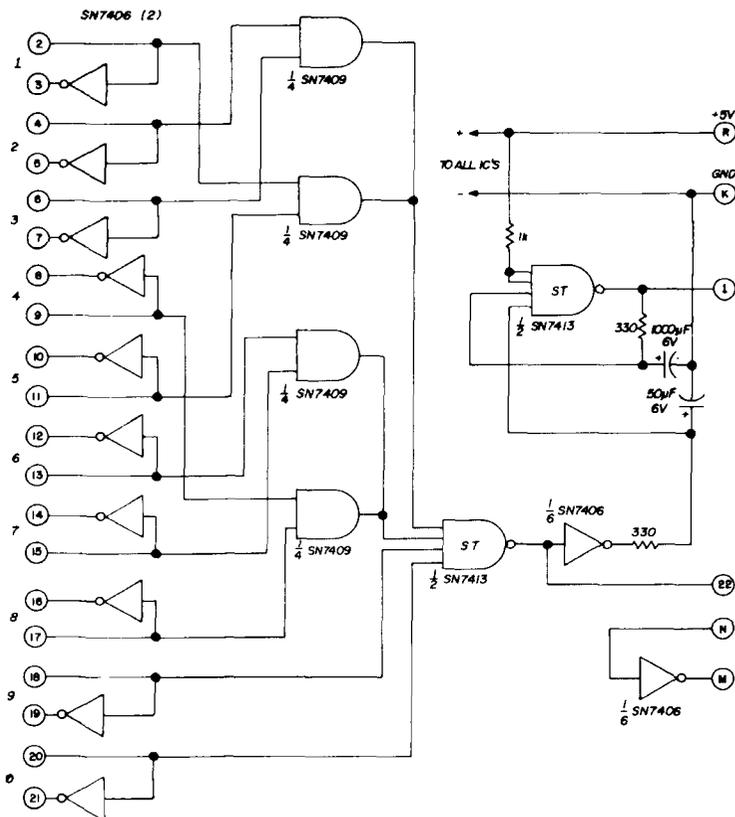


fig. 2. Diagram of the control module (referred to as circuit board number 1). Numbers in circles identify terminals on one side of board, letters those on other side.

feeding its output back to one of its inputs. The 330-ohm resistor and 1000- $\mu$ F capacitor give a cycle time of about 0.63 seconds — 32 cycles in approximately 20 seconds. This is the clock pulse for the switching and timing circuits.


Its rate can be changed if desired by using a different value of capacitance. The 330-ohm resistor should not be changed as it will affect the operation of other parts of the circuit. Two unused inputs of the multivibrator are stabilized at high level by connection to V+ through a 1000-ohm resistor, as recommended by the manufacturer.

The fourth multivibrator input is connected to an inverter driven by the output of the other half of the SN7413, used here as a simple NAND gate. As long as this input to the multivibrator is in a high state, the multivibrator will oscillate

under control of its own feedback circuit. When any Touch-Tone digit is received, however, it will cause a low input and high output at the NAND gate. The resulting low input to the multivibrator overrides the feedback circuitry, stopping the clock with its output in a high state until the tone signal ends. The 50- $\mu$ F capacitor and its companion 330-ohm resistor introduce just enough delay into

Note: The control module and the buffer/driver printed circuit boards are two-sided which might make them impractical for home etching. The author can offer commercial-quality glass-epoxy boards for \$10 for a set of three — the control module, the buffer/driver and one switching board of two modules. Additional switching module boards are \$3 each. Boards are undrilled, but the price includes postage. Add \$1 per board for drilling. The author can also supply the Texas Instruments ICs for those unable to get them locally. Write to R. B. Shreve, W8GRG, 2842 Winthrop Road, Shaker Heights, Ohio 44120.



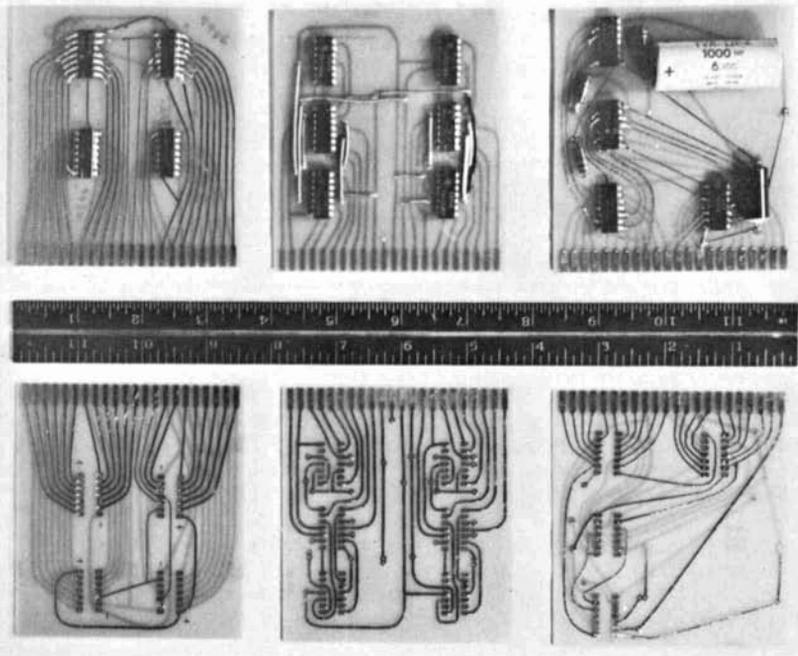

Front and back views of the three circuit boards. On the left, the buffer/driver board; in the center a typical board with two switching modules; on the right the control module.

guish between sequences such as 743 and 734.

If on first thought a 0.63-second clock cycle seems too short an interval in which to send successive Touch-Tone digits, it should be remembered that the clock stops as long as a tone is held. Clock "low" time is also lengthened when a tone is received, as the 1000- $\mu$ F timing capacitor is fully charged instead of being limited by the Schmitt-trigger hysteresis voltage.

The switching action has been described in simple form, with the switching-module clock input directly connected to the control board. In actual service, multiple switching modules require additional logic elements between the clock and the flip-flops. The SN7413 has a fanout capability of ten, and each switching module board has eight clock inputs, so SN7417 drivers are used to expand the clock output. One SN7417 will drive twelve flip-flops, so two are needed for each three switching-module circuit boards.

Additional control of the clock impulse is used to accomplish the objective, mentioned earlier, of having the repeater retransmit Touch-Tone signals intended for call-up or control of other stations without acting on them, and suppress transmission of signals used in its own control. A two-digit access code serves to identify the signals addressed to the repeater.

### access module

The access module, board 6, is shown in **fig. 4**, which also shows related logic circuits on the other boards. The access module has two parts—a two-digit sequential switch similar to the three-digit switching modules, and a six-stage binary counter. The AND gate connection for access digit one is unnecessary, but the board was made by modifying a switching module board, and it was easier to connect the input to the gate than directly to the flip-flop.

In the access module, the control-module clock output drives the switching

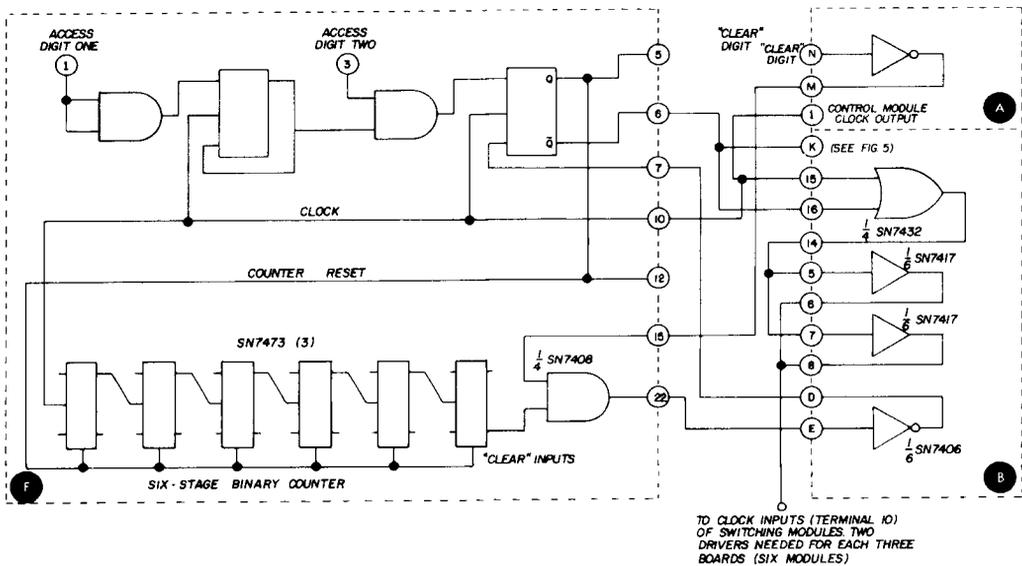


fig. 4. Diagram of the access module (circuit board 6) and related logic circuits on the other boards. The access module is labeled F, the control module is A and the output and driver logic on board 2 is B.

unit programmed to recognize the access code, and the first stage of the binary counter. It is also connected to one input of a SN7432 POSITIVE OR gate. The other input of this gate is driven by the Q output of the switching unit. As long as this output is high, the gate output is high regardless of the state of the control-module clock.

The gate actuates two SN7417 drivers, which in turn provide the clock impulses for all the switching modules on the other boards. Until the access switching module is set by receipt of the appropriate two-digit code, no clock pulses reach the switching modules on the other boards, so no Touch-Tone signals affect them. In addition, although the control clock is connected directly to the first stage of the binary counter, the counter clear inputs are connected to the Q output of the access switch, so it can not count as long as this switch output is low.

When the access switching module is set by the correct two-digit code, its Q output goes high and  $\bar{Q}$  goes low. The SN7432 gate output now cycles with the control clock, activating the switching modules on boards 3, 4 and 5. The high Q output also releases the clear inputs of

the binary counter, which starts counting the clock cycles.

As long as the access switch is set, the other switching modules will respond to the codes for which they are programmed. When the desired actions are completed, transmission of a single *clear* digit, generating a low at terminal 15 on board 6 resets the access switch, deactivating the other switching modules. If the unit is wired in this way, to clear with a single digit, that digit can not be used as part of an instruction code. If the *clear* input is not wired, or if the operator fails to transmit the *clear* signal, the binary counter will reset the access switch automatically after 32 clock cycles.

### output logic

Design of the output logic circuits will depend on the functions to be performed and the nature of the equipment being controlled. Board 2 can be assembled with a variety of buffers, gates and drivers. Mine has a SN7406 inverter-driver, SN7417 non-inverting driver, SN7403 quad NAND gate and SN7432 quad POSITIVE OR gate. Use of some of this logic in the control unit has already been described. A good example of what

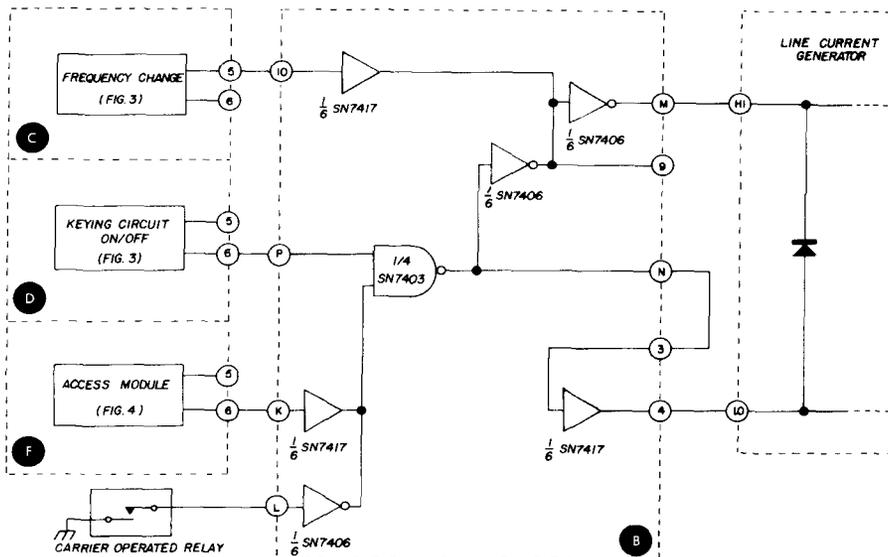


fig. 5. The keying control logic on circuit board 2 is labeled B, C and D are switching modules and F is the access module.

can be done by combining several outputs with appropriate logic is the keying control logic circuit shown in fig. 5.

As mentioned earlier, the receiver and transmitter are about a half mile apart, connected by a single telephone pair which carries both audio and dc keying current. The latter is supplied by a line current generator which will put either a low or high dc current on the line, depending on how it is keyed. The difference in current level may be used to select one of two transmitter frequencies. High line current flows when the generator *hi* input is grounded; low current flows if *lo* is grounded and *hi* is ungrounded. No current flows when both inputs are ungrounded.

For the *hi* input to be grounded, the input to the SN7406 inverter to which it is connected must be high. A low output from the *frequency change* switching module will prevent the *hi* input being keyed, while a high level output from it will permit the other part of the logic circuit to control.

Output of the SN7403 NAND gate is low when both its inputs are high. When low, it keys the *lo* generator input, and also keys the *hi* input if not inhibited by

the *frequency change* switch. Low output of the *keying circuit on/off* switch prevents the transmitter being keyed. Likewise, a low  $\bar{Q}$  output from the *access* switch, present when the switch is set to give signals access to the switching modules, prevents their retransmission.

If none of the logic is set to disable the keyer circuit, the carrier operated relay (COR) controls keying of the transmitter.

### conclusion

Other control functions — silencing a single input, or switching the tone guard on or off, use very simple logic and will not be described in detail. It is hoped that what has been described will give you a picture of the unit's versatility.

Power requirements of the complete unit of six circuit boards, excluding the Touch-Tone decoder, total about 600 mA at 5V. Each additional pair of switching modules adds approximately 100 mA to the load.

### reference

1. Douglas A. Blakeslee, W1KLK, "A Second Look at Linear Integrated Circuits," *QST*, July, 1971, page 29.

ham radio

# RTTY ribbon re-inkers

A quick conversion  
of a \$2  
surplus unit  
gives  
almost endless  
perfect page copy

Irvin M. Hoff, W6FFC, 12130 Foothill Lane, Los Altos Hills, California 94022

Any typing machine takes some kind of ribbon at periodic intervals in order to present a good appearance. Teleprinters for RTTY are no exception. Depending upon the amount they are used, a typical ribbon might last from a few weeks in a busy station to a few months in one less active. Cotton ribbons are normally used, as they are relatively inexpensive and can be tossed out when the page copy becomes too light to read easily. While nylon ribbons are much stronger, fray less readily and present a somewhat better appearance, they are also higher priced.

A few years ago I was given a ribbon re-inker. I managed to whack this unit up and mount it on my 28ASR, although it required drilling a hole in the case-hardened steel used on the model


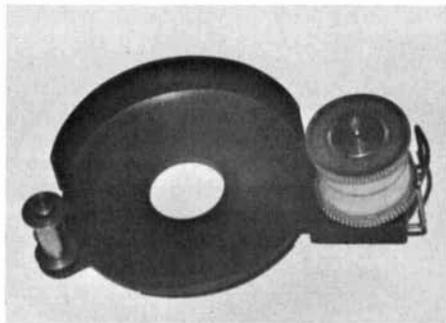


fig. 1. View of the basic reinker as used on the model 15 or 19. For the 28, this is inverted, the reservoir plugged into the other side and the unit modified as in fig. 2.

28 — no easy feat. A nylon ribbon came with the unit, and even though the teleprinter at W6FFC is running 7 to 10 hours per day, the same ribbon is still in use after some three years! Whenever it gets a bit light, I merely put a little additional ink in the reservoir, and the copy looks excellent again for a week or so more.

Normally, I do not write articles about hard-to-find surplus items. However, recently I was able to get a fairly large supply of these items and thus felt such an article might be of general interest. The kits were originally made for model 15 machines in the military services. The basic re-inker unit is shown in **fig. 1** and has a detachable reservoir around which the ribbon is placed prior to its being wound on the spool. The top of this reservoir unscrews and ink is poured in, it then seeps out two small holes onto felt pads that surround the reservoir, and the ink then is distributed on the ribbon as it contacts the pads. One reservoir-full will take approximately one full ribbon traverse to distribute; once on the ribbon it then evens itself from layer to layer in a few hours or several traverses. The usual tendency is to overink, but after several years, I can usually get the results I want.

As it comes in **fig. 1**, the unit adapts immediately to the model 15 or 19 merely by removing one nut and exchanging this unit for the one already on these teleprinters. The re-inker also can be

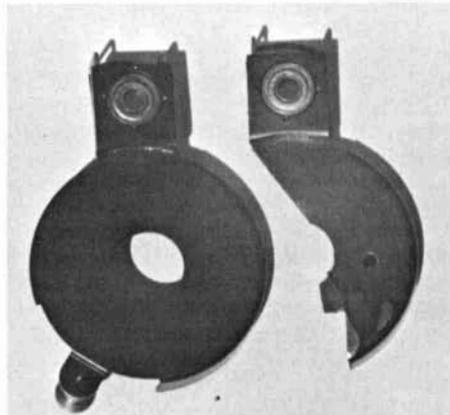


**fig. 2** The reinker base: before and after.

modified quickly so it will go on a model 28 teleprinter.

**Fig. 3** is a full-size template for cutting and drilling the re-inker. Cut out or copy the template, turn the re-inker so the flanged lip and post are down and place the template on the re-inker base with the legs of the template around the reservoir plate.

Mark lines B and C on the re-inker base and, using tin snips, a hack saw or a sabre saw, cut out at A (non-critical), B and C. The cut at C is critical and should be done carefully. Discard the shaded portions entirely.

Mark the hole, but do not drill it yet. Take the bolt out of the ribbon holder, and while holding the re-inker in position, swing it slightly until you can see your mark in the hole—check to make sure

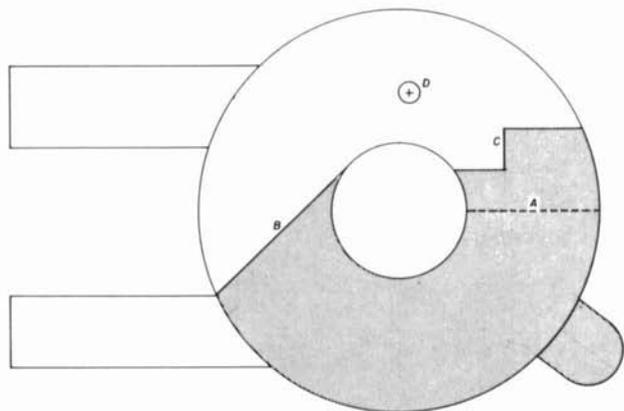

**fig. 3.** Template for modifying the basic unit to fit the model 28 or 35.

your hole is centered or remark it correctly. Drill the hole with a 7/64-inch drill, replace one short 1/4-inch 4-40 bolt on the model 28 with a 3/8-inch 4-40 and fasten the re-inker in place with a nut. Beside changing the 4-40 bolt, there is no modification to the model 28 itself.

An exact-size template is furnished with each re-inker sent out by the author if a self-addressed stamped envelope is furnished for the purpose.

Possibly I got ahead of the story, so I will try to give a better explanation. On the model 28, the left-hand ribbon holder has a spindle on front for the ribbon to pass over, just to the right of this is a vertical gate through which the ribbon passes — when the ribbon comes to the end, a rivet in the ribbon catches in this gate, carrying it to the right, activating the reversing mechanism. If you remove the ribbon spool, you will note this reversing lever is pivoted at the rear and held in position with the 1/4-inch 4-40 bolt previously mentioned. A collar prevents the lever from binding as the bolt is tightened. This is the bolt that is exchanged for a longer one, and it is to this bolt that the re-inker attaches. Fig. 4 shows how this appears when finished — it is not necessary to even remove the ribbon holder from the teleprinter. Fig. 5 shows how this appears from the bottom — and also shows how the ribbon goes through the gate, past the spindle and around the reservoir prior to being

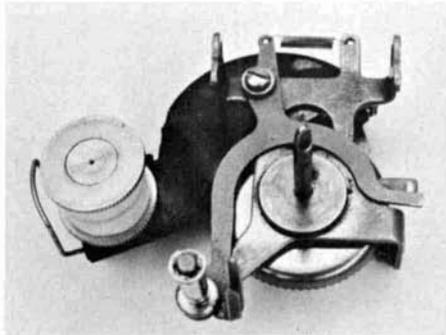


fig. 4. The ribbon holder has been removed to show how the modified re-inker is attached for the 28 or 35.

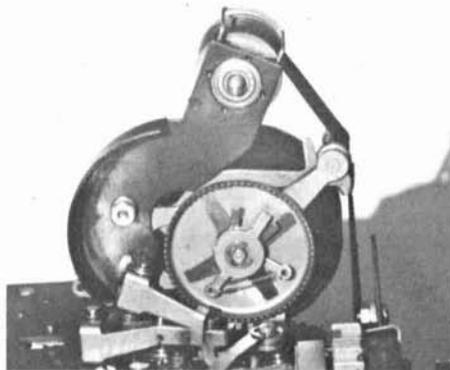


fig. 5. The underside of the ribbon holder with the re-inker held in place.

wound on the spool. Fig. 6 illustrates the end result.

After getting the unit mounted, make sure the reservoir is at the same height as the ribbon spool itself — or of the spindle, and that it is vertical with respect to the spindle. Otherwise the ribbon might want to "overlay" onto itself a little as it goes past, indicating the reservoir is not centered properly. You can bend this up or down somewhat with a pair of needle-nosed pliers if needed, or with your fingers.

### ribbon holder removal

Although not necessary, some of you may prefer to remove the ribbon holder entirely — it only takes a moment and does make the installation of the re-inker simpler, as well as offering a good means of determining if the reservoir is centered the best. There are two C-clamps and one spring to unhook, and the unit pulls right off the post around which it oscillates up and down. Fig. 7 shows the first retaining ring to be removed on the bottomside of the unit, the lever is then pulled free. Normally this lever causes the ribbon spool to oscillate up and down, allowing you to read the page copy when the typing unit is not striking a letter.

Fig. 8 shows the retaining ring at the top of the ribbon holder and fig. 9 shows the one spring on the right side of the



fig. 6. The complete reinker in use on a model 28 teleprinter.

ribbon unit as observed from the front. When reassembling the ribbon holder, refer to fig. 7 again and make certain the two levers shown on the left of the photo are interhooked as shown, which is simple enough to do while you are sliding the unit back into place.

#### other re-inkers

Other re-inker ideas have been tried and one is offered commercially. This latter system involves removing the ribbon from the machine, taking off the top plate of a special ribbon spool that comes with the kit, dropping ink at strategic places around the wound-up ribbon, and leaving it overnight for the ink to distribute itself uniformly. Then the special top is replaced and the ribbon and spool are placed back on the machine. This system never appealed to me.

Another system that was developed by Rex Peters, W4ZAG, merely was to take an empty ribbon spool and drill large holes in it at various places so that dropping some ink into the holes would allow the ribbon to disperse this ink over a period of time. Rex used this system for several years, but now uses the reservoir method described in this article. Other systems have been tried, but they seem to have little merit compared to the reservoir method.

#### ink

Various firms sell ink that is satisfactory. I use metal tubes of ink obtained from the National Cash Register Company — they resemble medium-sized toothpaste tubes. Ink used for ribbons is considerably thicker than ink used for fountain pens, so it is not as runny, although it is still in liquid form, and not really a paste. NCR ink comes in several colors; I use their black K-575. One tube is enough for at least a year's supply unless your station is quite active. Ink is available through any NCR distributor; look in the Yellow Pages in your phone book. The price has been 75c a tube.

When printed copy gets a little light, just remove the top of the reservoir and insert some ink — do not fill it too full or it will ooze out the hole in the top of the reservoir when it is replaced. You can put ink in regardless of the direction the ribbon is going, or whether it is at one end or in the middle. However, it will work the very best if you wait until the ribbon is all wound up on the right-hand spool and just starting to come back to the left. This puts ink on as it winds up, rather than as it unwinds. You can force the ribbon to go either direction you wish if you manually hold that reversing gate to one side for a few characters.

The usual tendency is to wait too long

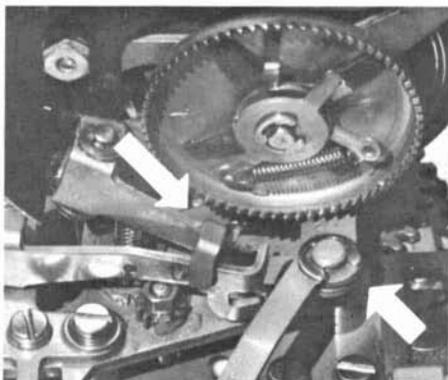


fig. 7. The bottom side showing the retaining ring (right) that is removed to take off the ribbon holder and (left) the manner in which the ratchet levers are unhooked.

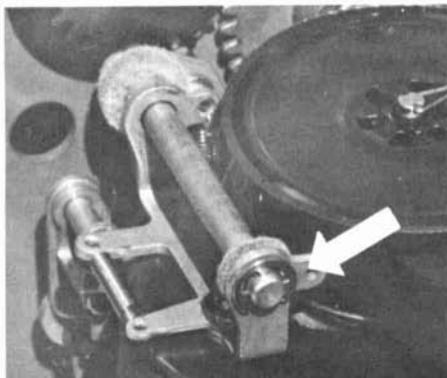


fig. 8. The retaining ring at the rear of the left spool is also removed to take off the ribbon holder.

and then over-ink. Do not put more than one reservoir full at a time on the ribbon. It may appear for awhile that nothing is happening and that it really needed lots of ink — you will want to put more on, but don't. Give it at least 24 hours or a few traverses of the ribbon (best of all, both!), and it will act like a new ribbon again. If you load several reservoirs full concurrently, you will soon find it is too black and certain characters will fill up and smudge, making terrible looking page copy for a few hours. This has been one reason a few people have not cared for re-inkers, but if you use some of these hints, you will not have the usual problems.

### the re-inker kit

These kits contain the base plate, two reservoirs (one for a spare), a nylon ribbon, a large number of spare felts (after three years, I'm still using the original ribbon and original set of felts), a tool (plastic) for slipping the new felts onto the reservoir cylinder, a nice plastic box (excellent for storing radio parts), a small wire tool for cleaning out the seep holes in the cylinder (I've never needed to do this) and finally a plastic bottle of ink. This ink is pretty old, and too thick — I recommend you throw it out first thing. It will clog the seep holes and generally be unsatisfactory unless thinned — too much bother to mess with.

With this system, you can keep copy looking as though you had a new ribbon on, all the time, and still not get your fingers dirty. Even if you had unlimited access to free ribbons for merely carting them home, you would soon prefer using the same nylon ribbon with a re-inker.

The re-inker has been so nice I tried for some time (mentally) to see if I could figure out some method by which I could re-ink the nylon IBM cartridges on my Selectric typewriter (about \$2.50 each). I gave up, although Dave, W7RSJ, says he has figured out a way to do it! Many typewriter ribbons could be re-inked on your teleprinter and then replaced on the typewriter, too!

### availability

The author has a number of these available for \$2, postage paid anywhere in the U. S. A. Please do not order from outside the U. S. A., as we have no facilities for going through customs, nor

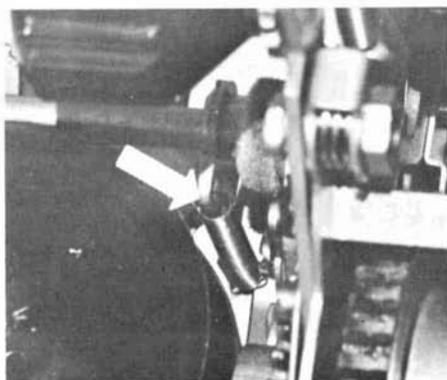


fig. 9. The third and final thing to remove the ribbon holder is to unhook this spring at the right of the ribbon holder.

an export license. Include an sase for an extra template for model 28s or to return your money in case we run out of the limited supply available. Send to:

Irvin M. Hoff W6FFC  
12130 Foothill Lane  
Los Altos Hills, Calif. 94022  
Attn: Re-inker

ham radio

# AMATEUR ELECTRONIC SUPPLY

is the Best Place to purchase your new  
**DRAKE** gear for the following reasons

- Performance
- Versatility
- Resale Value



TR-22



ML-2F



R-4B



2C



TR-4

ML-2F "Marker Luxury" 2m FM	\$329.95
TR-22 Portable 2m FM Transceiver	199.95
AA-22 Rec/Xmtr Amplifier - 12vdc	149.95
MMK-22 Mobile Mount	6.95
Extra crystals for ML-2F, TR-22 - each	5.00
DRS-1 Digitally Synthesized Receiver	2195.00
2C Receiver	255.00
2AC Calibrator for 2C	18.75
2CS Speaker for 2C	22.00
2CQ Speaker/Q-multiplier for 2C	39.95
2NB Noise Blanking for 2C	26.95
R-4B Receiver	475.00
MS-4 Speaker for TR-4/6, R-4B	22.00
TR-4 Transceiver 80-10 Meters	599.95
34PNB Noise Blanking (plug-in)	100.00
RV-4 Remote VFO for TR-4	110.00
FF-1 Crystal Control adaptor	46.95
TR-6 Transceiver - with noise blanker	650.00
RV-6 Remote VFO for TR-6	110.00
AM Plug-in Filter for TR-6	35.00
CW Plug-in Filter for TR-6	35.00
LSB Plug-in Filter for TR-6	35.00
AC-4 AC supply for TR-4/6, T-4XB	99.95
DC-4 12vdc Supply for TR-4/6	125.00
MMK-3 Mobile Mounting kit for TR-4/6	6.95
MC-4 Mobile Console for TR-3/4/6	69.00
2NT CW Transmitter	164.00
T-4XB SSB Transmitter	495.00
L-4B Linear Amplifier	825.00
MN-4 Antenna Match Network	99.00
MN-2000 Antenna Match Network	195.00
W-4 RF Wattmeter (2-30 Mc)	61.95
WV-4 RF Wattmeter (20-200 Mc)	73.50
C-4 Station Control Console	299.95
TC-6 6m Transmitting Converter	250.00
TC-2 2m Transmitting Converter	300.00
SC-2 Receiving Converter for 2m	76.00
SC-6 Receiving Converter for 6m	71.00
CPS-1 Power Supply for SC-2, SC-6	19.75
SCC-1 VHF Crystal Calibrator	26.95
CC-1 Converter Console	26.95
TV-300HP High-Pass Filter	4.95
TV-1000LP Low-Pass Filter	18.75
LN-4 Line Filter 120v 5 amp	8.00
729SRD Microphone with plug	17.00
SPR-4 Programmable Receiver	495.00
5NB Noise Blanking	65.00
DC-PC DC Power Cord	5.00
TA-4 Transceiver Adaptor	15.00
SCC-4 Crystal Calibrator	20.00
RY-4 Teletype Adaptor	10.00
CRYSTAL KITS FOR SPR-4	
Aeronautical Overseas - 7 crystals	32.00
Amateur Bands - 6 crystals	27.00
Citizens Band - one crystal	5.00
Marine Bands - 11 crystals	49.00
MARS - 5 crystals	22.00
Teletype Commercial - 4 crystals	18.00
Time & Freq. Std., WVW - 5 crystals	22.00
Tropical Broadcast - 3 crystals	13.50

- TOP TRADES for your good clean equipment
- STAY-ON-THE-AIR PLAN - Enables you to keep your trade-ins until your new gear arrives - Lose no operating time!
- PERSONAL SERVICE from fellow hams who understand your problems.
- SAME DAY SERVICE on most Orders and Inquiries from our Centrally Located Modern Facilities
- Top Notch Service Department
- LARGE COMPLETE STOCK means Fast Deliveries. United Parcel Service available to most parts of the country. - UPS Blue label (AIR) to the West Coast.
- LOW LOW 1% Monthly Service Charge (ONLY 12% per annum) on GECC Revolving Charge Plan. Only 10% Down Plus LOW Monthly Payments - For Example: \$10 a month finances up to \$300, \$20 up to \$610. Write for complete information and credit application.

If you purchase any of the new Merchandise listed below at the Regular Price and Without a Trade-In, you may take the "Bonus" Credit indicated below toward the purchase of other merchandise (such as power supplies, antennas, towers, microphones, crystals, linears, accessories, etc.).

2NT Transmitter	\$10 Bonus	TR-4 Transceiver	\$50 Bonus
2C Receiver	\$20 Bonus	TR-6 Transceiver	\$60 Bonus
SPR-4 Receiver	\$40 Bonus	L-4B Linear	\$80 Bonus
R-4B Receiver	\$40 Bonus	ML-2 2M FM Xcvr	\$30 Bonus
T-4XB Transmitter	\$40 Bonus	TR-22 2M FM Xcvr	\$10 Bonus

- SIX EZ-WAYS TO PURCHASE
1. CASH
  2. C.O.D. (20% DEPOSIT)
  3. MASTER CHARGE
  4. BANK AMERICARD
  5. AMERICAN EXPRESS
  6. GECC REVOLVING CHARGE



Order Today  
Direct from this Ad



Ray Grenier, K9KHW  
Mgr. Mail Order Sales

To: **AMATEUR ELECTRONIC SUPPLY**  
4828 W. Fond du Lac Ave, Milwaukee, Wis. 53216

I am interested in the following new equipment: \_\_\_\_\_

I have the following to trade: (what's your deal?) \_\_\_\_\_

Ship me: \_\_\_\_\_

I Enclose \$ \_\_\_\_\_; I will pay balance (if any):

COD (20% Deposit)  GECC Revolving Charge Plan

Master Charge\*  BankAmericard  American Express

Account Number: \_\_\_\_\_

Expiration DATE \_\_\_\_\_ \*Master Charge Interbank number \_\_\_\_\_ (4 digits)

Name: \_\_\_\_\_

Address: \_\_\_\_\_

City & State: \_\_\_\_\_

Send used gear list  Send Drake literature

**AMATEUR ELECTRONIC SUPPLY**  
4828 West Fond du Lac Ave. Milwaukee, Wis. 53216  
Phone (414) 442-4200

HOURS: Mon & Fri 9-9; Tues, Wed & Thurs 9-5:30; Sat 9-3  
CLEVELAND Area Hams may wish to visit our Branch store located at: 17929 Euclid Ave., Cleveland, Ohio, Ph. 486-7330. Pete Smith, Mgr.  
ALL Mail Orders and Inquiries should be sent to our Milwaukee store.

More Details? CHECK-OFF Page 94

# accurate noise-figure measurements for vhf

For the serious  
vhf experimenter  
a simple circuit  
and procedure  
for measuring  
vhf noise figures  
with accuracy

Building a low-noise preamplifier utilizing the solid-state devices available today, you can obtain very impressive receiver sensitivities at vhf.<sup>1</sup> For weak-signal work, such as meteor scatter, long-haul tropo and moonbounce, lowest noise performance obtainable is paramount. To ensure this, an accurate measure of the receiver's nf (noise figure) must be obtained. Adjusting for lowest noise performance using a noise source or a weak-signal source is unsatisfactory at best, and actual performance is unknown. The nf is still unknown.

Ready access to an automatic laboratory nf meter is generally not possible for many, so a suitable means of obtaining nf measurements must be found. Several nf meters utilizing the characteristics of a temperature-limited diode have been published previously.<sup>2, 3</sup> The Sylvania type 5722 is a diode specially constructed for use as a temperature-limited noise source. This tube, selling for approximately \$8.40, exhibits predictable noise output response, which is readily determined by measuring the current passing through the diode.

## noise factor

Using this diode, the *noise factor* of the receiver may be obtained when the noise output of the diode exactly

Louis N. Anciaux, W6NMT, Box 1000, Dixon, California 95620

matches the noise output of the receiver. When this condition is satisfied, the *noise factor* is simply

$$20 IR \quad (1)$$

where  $I$  is the current thru the diode,  $R$  is the load resistance and the number 20 is a constant.<sup>4</sup> For the usual 50-ohm system, this reduces to  $1000I$ ; or the *noise factor* is equal to the magnitude of the current in mA passing through the diode. To obtain *noise figure* (nf), merely take ten times the logarithm of the *noise factor*.

### design notes


To make accurate nf measurements, you must know the load resistance and current through the meter with a fair degree of certainty. Previous models have failed to consider the load resistance as an rf network, using only a 50-ohm resistor and excessive lead lengths. Above 100 MHz especially, the small reactances associated with lead lengths of the order of 0.5 inch are sufficient to cause an error approaching 1 dB when measuring receivers with under 3-dB nf. Current through the diode must be known with precision, 5% error being an excessive amount.

The nf meter described here gives excellent performance and repeatable results through the 432-MHz band. Comparison with industrial meters of high accuracy have shown excellent agreement. Error is under 0.1 dB for the bands 220 MHz and below, and at 432 MHz, the meter consistently reads within 0.5 dB of the industrial meter. At 432 MHz, W6FZJ consistently measured preamps at 0.3-dB higher with the meter described here than with a commercial meter.
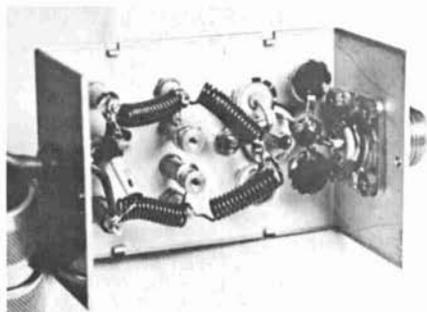
### precautions

Be careful with the rf head construction and with the meter circuitry. A large scale meter is a must, as the current must be measurable to less than 0.1 mA. Since most nf measurements of greatest interest are under 5 dB, a 4-inch or larger scale meter with full-scale deflection of 5 mA is an excellent choice. You can use a

shunt to obtain readings up to 25 mA, as desired. If you use a meter with less than a 5-mA movement and a shunt resistor, it must be calibrated against a known standard. Particularly under 3 mA, readings *must be accurate* to less than 0.1 mA. Note that the current path is directly



Interior view of the rf head. Readily visible are the various components and their placement within the minibox. The three 150-ohm resistors must be placed to ensure shortest possible leads. Low-loss ceramic socket for the 5722 keeps losses low at higher vhf ranges.

through the meter and should the rf head develop a short, it means an instant demise for the meter. You may add some sort of meter protection if you want.


### construction

To begin building the rf head, place the tube socket near one end of the minibox, so that R9, the 50-ohm quarter-watt resistor, will just fit between the anode pin and the center pin of the connector which is mounted on the end of the minibox. Either three 150- or four 200-ohm quarter-watt resistors may be used for the load, R10. Carefully select these resistors to obtain a near match between them, as well as a final paralleled value as close to 50 ohms as possible. By placing them symmetrically around the UG-58A/U connector, their leads, soldered directly to the connector body and to the center pin, are no longer than 1/32 inch. This will ensure a load resist-

ance which exhibits a very few ohms reactance at 432 MHz.

The single 50-ohm quarter-watt resistor from the anode pin to the connector center pin acts as a swamp to minimize swr effects from the receiver

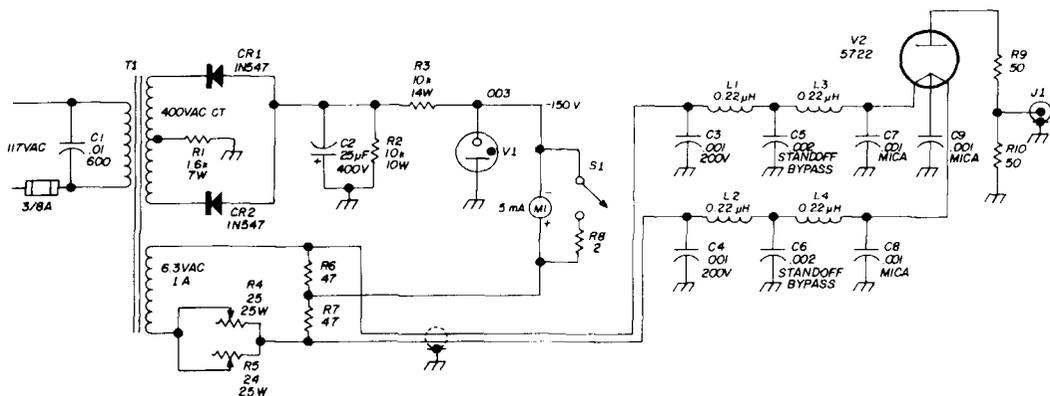non-critical, as long as the voltage does not vary radically and is free from excessive ripple. A 100- to 200-volt supply is satisfactory, and will be beyond the diode's space-charge potential sufficiently to ensure repeatable results.<sup>5</sup> The VR



- J1 UG-58A/U chassis jack
- L1,L2 approx. 0.3  $\mu$ H, 16 turns no. 20 wire,  $\frac{1}{4}$ -20 bolt used as mandrel. L1 and L2 may be up to 10  $\mu$ H.
- L3,L4

- R10 three 150-ohm  $\frac{1}{4}$ W or four 200-ohm  $\frac{1}{4}$ W resistors selected to yield 50 ohms when paralleled

fig. 1. Complete schematic of the noise figure meter including the power supply and the rf head. They are shown here connected with shielded cable. Consult the text for modification to the inductors for different frequency ranges.

input circuitry which can cause erratic readings. The uhf button-mica bypass capacitors at each of the three cathode leads should be located to keep lead lengths as short as possible, and of equal length. The rfc's farthest from the 5722 socket may be made larger, up to 10  $\mu$ H, to allow use well below 100 MHz. The model shown here is used mainly for 220-MHz preamps; thus both rfc's were chosen as 0.3  $\mu$ H.

### power supply

The best way to control filament voltage is with a small Variac in the primary of a separate 6.3 V transformer. A second method, as shown, uses two power rheostats in parallel. One allows the filament voltage to be increased to the point of diode conduction (approximately 1 mA) and the other acts as a fine-tuning control to set the current to the appropriate level. The dc supply is


tube is not necessary, as only the current through the diode affects the noise produced, and small voltage variations will not hurt.

### operation

To use the meter for determining *nf*, you must be able to accurately measure a 3 dB change in noise output of the receiver. When the noise output of the 5722 diode equals that being produced by the receiver, the *nf* of the receiver may be determined from the diode's characteristics. A vtvm, or a vom on low-ac range, may be used to measure the receiver's audio output. In this case, the receiver must use a product detector and the agc must be disabled. In receivers using square-law detectors (diode types), you must use the 3-dB pad insertion method. Some receivers have very responsive S-meters which may be used as indicators when using the 3-dB pad.

The 3-dB pad insertion method is the most accurate, and therefore, the preferred method of obtaining nf measurements. Connect a speaker to the receiver output and set the volume to some reference level. Attach the nf meter rf

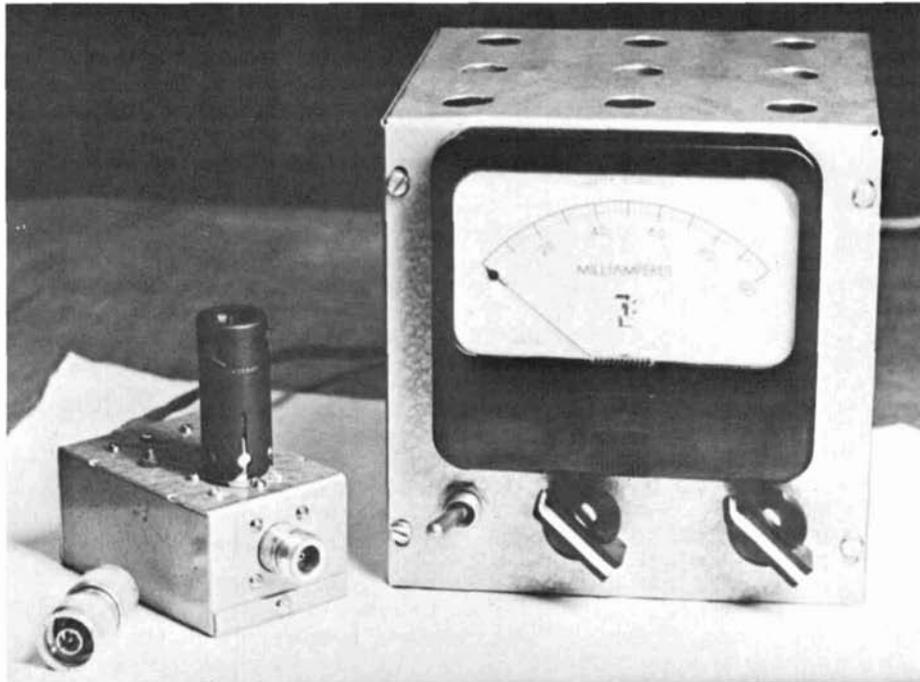change the reference level to another value, and repeat the same procedure to obtain diode current. If all diode-current readings are the same and are repeatable, then it is generally safe to assume the readings are valid. However, if the read-



The noise figure meter and rf head. The 4½-inch scale meter allows direct reading to 0.1 mA with interpolation to 0.025 mA readily possible. The interconnecting cable allows the rf head to be used separated from the nf meter, facilitating measurements. The UG-57B/U adaptor connects two UG-58A/U chassis jacks together directly, keeping losses to a minimum.

head directly to the converter or preamp input. Insert a 3-dB pad into the i-f line between the converter and receiver, noting a decrease in output from the receiver. As you turn on the 5722's filaments slowly, and as the diode current increases, the noise output of the receiver will also increase. When the output of the receiver is the same as the reference level prior to insertion of the pad, read the diode current and turn the filaments off.

Removing the pad should return the indicator to its original reference level. If it does, then repeat the procedure to obtain another diode-current reading. If the diode current is the same, then

ings vary from trial to trial, then precautions are necessary.

### problems

If you obtained erratic diode-current readings, there are several possible causes. First, if the audio output is being read on a vtm and a 3-dB change is sought, inserting a 3-dB pad in the i-f line should also indicate a 3-dB change on the vtm. If it does not, then either the agc is not disabled or you are overloading the mixers or detectors. Second, if the swr between the converter and receiver is not 1:1, then using two additional pads should cure this problem. Inserting the

3-dB pad between these two pads will allow you to make repeatable measurements. The two additional pads act as swamps to stabilize the circuitry. Third, if the converter or preamp-input circuit is grossly mis-adjusted, (not 50 ohms) erratic readings will also occur. Fourth, if the converter or preamp is not properly neutralized, very erratic readings result.

If a preamp, previously measured into another converter at a low noise figure, shows considerably higher nf, it may be due to very high nf in the second stage (converter input). This is seen from the relationship:

$$F_T = F_1 + \frac{F_2}{G_1} \quad (2)$$

where  $F_1$  and  $F_2$  are *noise factors* of the first and second stages,  $F_T$  is system *noise factor*, and  $G_1$  is the *gain factor* of the first stage.<sup>4</sup> In this case, the second stage nf must be reduced to an acceptable level, either by redesigning or by adding another rf stage.

For example, consider a 2-dB nf preamp with 10-dB gain and a converter with a 15-dB nf. Converting dB to *factors*, 2 dB = 3.01, 15 dB = 17.61, 10 dB = 10; and plugging into the equation yields a *noise factor* of 4.77 and a system nf of 3.0 dB. This shows the importance of having the second stage nf reasonably low in order to enjoy fully a good preamp's performance. In the case of a 5-dB second stage, system nf would be 2.34 dB. Increasing the gain of the preamp to 15 dB would further reduce the system nf to 2.2 dB.

## procedure

As an example in making a nf measurement, connect the rf head of the nf meter to your preamp input. The converter output is fed into a 6-dB pad, through a piece of coax to another 6-dB pad and into the i-f receiver. The S meter on the receiver reads S-3. Inserting the 3-dB pad in the i-f line after the first 6-dB pad, shows a drop to nearly S-2. The diode filament current is slowly increased until the noise produced by the diode just equals the S-3 reference level. The diode

current is read as 2.3 mA. The diode filaments are turned off and the 3-dB pad removed from the i-f line. The S-meter should again read S-3.

Repeat the above procedure and obtain another diode current. Assuming it is again 2.3 mA, remove one of the 6-dB pads and insert a 10-dB pad in its place, obtaining a new reference level. The diode current obtained now should be the same if all is well, otherwise, problems exist. Make at least two tests to obtain diode current.

To convert this reading of 2.3 mA to nf, simply take ten times the logarithm of 2.3. That is,  $\log 2.3 = 0.362$ , thus  $nf = 3.62$  dB. The accuracy of the current meter becomes apparent at this point. If the accuracy is only  $\pm 0.1$  mA, then the current may be 2.2 mA or 2.4 mA. The nf corresponding to these currents are 3.4 dB and 3.8 dB. The nf of the receiving system is  $3.6 \pm 0.2$  dB. When making readings around 1.5 mA,  $\pm 0.1$  mA error corresponds to nf of 1.46 dB at the low- and 2.04 dB at the high-error point. This 0.5 dB or so difference in nf at this level represents more like 1 or 2 dB in receiving sensitivity, and for moonbounce work, those dB really count.

I would like to express my appreciation to W6FZJ for originally bringing to me the idea of the distributed impedance load in the rf head, and to W7CNK for many enlightening discussions during which we both came to understand many of the reasons for doing things the way we have and for his helpful criticism in reading the drafts of this article.

## references

1. L. N. Anciaux, "220 MHz EME Notes," *Bay Area 220 MHz News*, (WA6GYD publication).
2. "The Radio Amateur's Handbook," 45th edition, ARRL, 1968, pages 544-546.
3. H. L. Gibson, G8CGA, "A Switched Noise Source and Noise Factor Comparator," *Radio Communication*, March, 1971, page 174.
4. F. E. Terman, "Electronic and Radio Engineering," McGraw-Hill, New York, 1955, pages 440-442.
5. R. W. Landee *et al*, "Electronic Designer's Handbook," McGraw-Hill, New York, 1957, pages 7-24.


ham radio


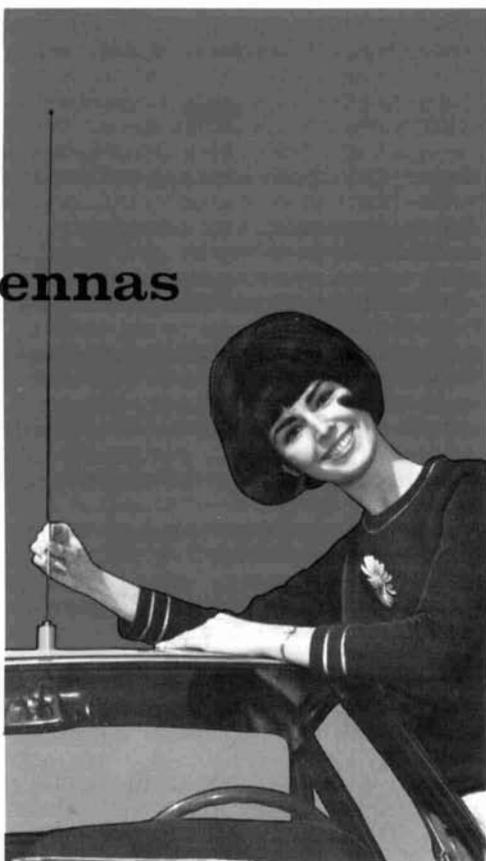
## Larsen Antennas

the mobile antenna  
that lets you  
hear the  
difference!

**new...** *A leader in  
the commercial V.H.F.  
Communications Field. . .  
Now available for Amateurs.*



When you double your power you expect a more solid QSO . . . more ability to cut through and to hear and be heard. With Larsen Antennas you get 3db gain or better. Mobile to mobile (no repeater) that's a 6db system gain . . . equivalent to quadrupling your power. In no other way can you get so much for your money.

### High Band Gain Antenna (144 MHz)

- 3db + gain on transmit over 1/4 wave whip
- V.S.W.R. less than 1.3 to 1
- Handles full 100 w. continuous
- Covers entire band. Just cut whip to desired frequency.

### UHF Gain Antenna (420-450 MHz)

- Collinear design for greatest efficiency
- Full 5db gain over 1/4 wave whip
- V.S.W.R. less than 1.3 to 1
- Lowest silhouette . . . least wind drag

Every Larsen Antenna is fully guaranteed. They are built to the highest commercial standards and to take the roughest usage. All whips are stainless steel, silver plated for greatest radiation efficiency. Models available to fit every type of mount with no special adaptors required.

### ORDER YOURS TODAY

Amateur Net . . . \$24.50 postpaid  
to fit your mount. Specify  
make or type you will use.


Antenna also available complete  
with mount and co-ax. Write  
for fact sheet.

*Full fact sheet available on request*

**Larsen**  
**Electronics, INC.**

11611 N.E. 50th Ave. Vancouver, Wash. 98665

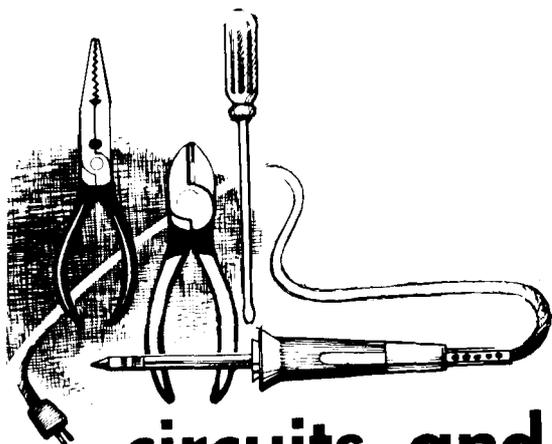For fastest service send orders to:  
P.O. Box 1686 — Vancouver, WA 98663




# circuits and techniques

ed noll, W3FQJ
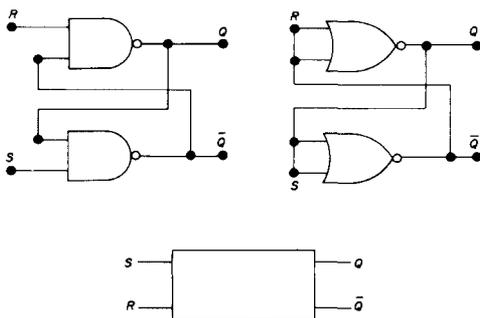
## digital multivibrators

**Old-fashioned circuits** acquire new names. One of the most common electronic circuits is the bistable multivibrator which, for more than three decades, has been standard in television and radar circuits. It is often called a toggle or flip-flop multivibrator. In the clipped computer language it is called an FF. There are a variety of multivibrator types to be found packaged in digital integrated circuits. Although some refinements have been made by the computer industry, the multivibrator circuitry is rather funda-



mental as compared to some of the earlier versions used in radar and television equipment. You old timers will remember the phanastron!

Two vacuum tubes or two transistors fed back upon themselves can be made to flip-flop. A very basic multivibrator can be formed by feeding back two NAND or NOR gates upon themselves as shown in **fig. 1**. In computer vernacular the inputs are called *set* and *reset* or simply S and R, while the outputs are designated Q and  $\bar{Q}$ . These correspond to the trigger inputs and the MV outputs of the past. The block symbology and the truth tables are also shown in **fig. 1**.

The Q and  $\bar{Q}$  can be given logic 0 and logic 1 designations. The *set* or logic 1 state of such a flip-flop corresponds to a Q output of 1 and a  $\bar{Q}$  output of 0. The converse of the above (Q of 0 and  $\bar{Q}$  of 1) is spoken of as the *reset*, cleared or zero-state position. Customarily you say that the circuit has been *set to 1* or *reset to 0* representing the two states of the flip-flop. These designations are shown on the truth table.

When there are simultaneous logic 1 inputs the next state becomes indeterminate and in truth chart language it is said to be not allowed, forbidden or indeterminate. In general, simultaneous logic 0 inputs represent a no-change condition and values are related to the previously set or reset position.

An additional input can be added to a multivibrator which permits toggling or flip-flop operation. This input applies so-called *clock* information to both inputs simultaneously, **fig. 2A**. As per the fundamental triggered-multivibrator, the output frequencies are one-half the clock

**fig. 1. The basic flip-flop multivibrator and its truth chart.**


S	R	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	----- forbidden	
0	0	----- no change	

input frequency. This is the basic binary multivibrator, or 2-to-1 divider, or 2-to-1 counter. The logic of the output is controlled by the set and reset inputs of the clocked R-S multivibrator.

A popular multivibrator circuit in-


change over the output logic.

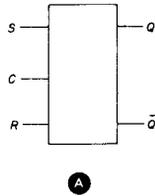A popular digital multivibrator is the universal flip-flop such as the 7472N shown in **fig. 3**. This combination permits you to set up a variety of multivibrator functions because it has both input pairs,



S	R	Q	Q̄	
1	1	---	---	forbidden
0	1	0	1	
1	0	1	0	
0	0	---	---	no change

**fig. 2. Clocked R-S and J-K flip-flops.**

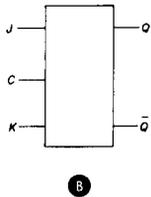



J	K	C	Q	Q̄	
0	1	1	1	0	
1	0	1	0	1	
1	1	1	---	---	complement
0	0	0	---	---	no change
					all other combinations — no change

cluded in digital ICs is the J-K flip-flop, **fig. 2B**. This arrangement permits ease in setting the flip-flop to a desired condition. In addition to the usual set and reset positions as shown in the truth chart, it is possible to supply logic 1 level to the J and K inputs simultaneously. If the clock pulse is also of logic 1 level there will be a switchover of the output logic voltages. However, if both the J and K inputs are logic 0 the clock pulse is not able to

R-S and J-K. The use of the J, K and C inputs permit J-K FF operation. Since the R and S inputs are overriding, the multivibrator can also be operated in the R-S manner. For simple operation as a 2-to-1 divider, you need only apply signal to the clock C input.

### experiments

You can learn much by experimenting with several of the low-cost digital ICs.

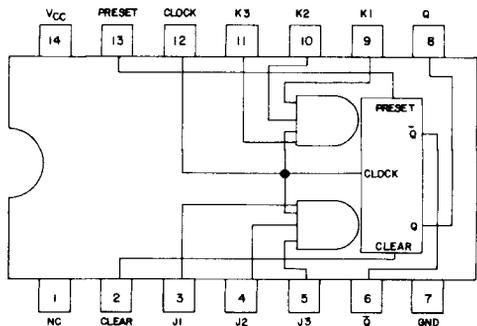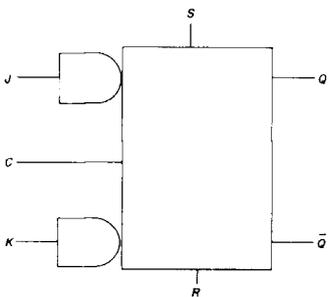

**fig. 3. Universal flip-flop (A) and the actual pin connections of the 7472N (B).**

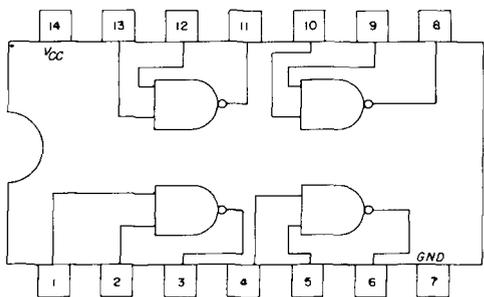


fig. 4. Connection diagram for the 7400 quadruple 2-input NAND gate.

Later these can be combined into a calibrator, counter or some other unit that can be useful in your station.

A small perforated board, 4½ x 5½ inches, supported on four stick-on protector pads can serve as a versatile test board. Several 14-pin in-line sockets can be attached to the board. All socket terminals, or as many as are needed, can be wired to soldering lugs that are screwed to the board. This arrangement gives you versatility and better experimental wear-and-tear with frequent re-wiring when various types of digital ICs are to be used.

### experiment 1 NAND gate

A readily available and low-cost digital IC NAND gate is the SN7400N (7400 series) which consists of four individual NAND gates with dual inputs, fig. 4. Supply voltage is connected to pin 14 for this TTL device, while common (ground), is connected to pin 7.

Connect the circuit of fig. 5. Use just one of the gates in the device. The circuit connections are simple; the dual inputs

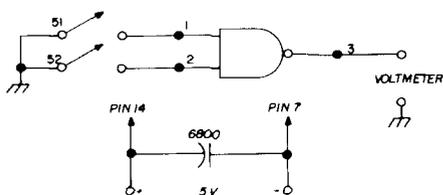


fig. 5. One-quarter of an SN7400N NAND gate connected to show dc operation.

are pins 1 and 2 and the output, pin 3. Connect a voltmeter across the output. Two spst switches permit you to establish the logic 0 and logic 1 inputs. This device has two states as in any binary logic system. The logic 1 state or *high* is represented by a voltage greater than plus 2 volts (positive logic) while the logic 0 state or *low* is represented by a voltage of 0.8 volts positive or less.

When the gates are open, the emitter voltage in the basic TTL circuit of fig. 6 is more than 2 volts positive, and the emitter junction is being reverse biased. Open both switches and measure the dc voltage at pins 1 and 2 to confirm this statement.

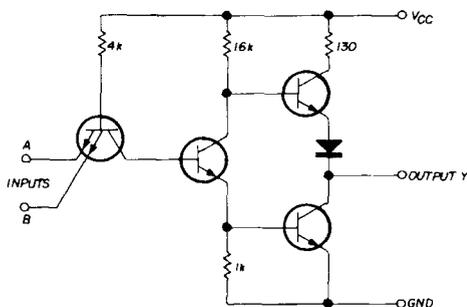


fig. 6. Basic circuit for a single gate in a 7400 digital IC.

The collector junction is forward biased and the collector current present in the base-emitter circuits of the output transistor results in a saturation current and 0 output voltage as indicated by the voltmeter. In this connection then, logic 1 voltage is present at pins 1 and 2 while logic 0 voltage appears at the output.


Now close switch S1. What happens to the voltmeter reading? Measure the voltages at pins 1 and 2. Note in particular that the voltage at pin 1 represents logic 0. Logic 1 voltage remains at pin 2 and the output voltage is also logic 1. When switch S1 is closed the input emitter junction is forward biased and the collector current now changes direction and cuts off the output transistor. Its col-

lector voltage rises to near the supply voltage and produces logic 1 output.

Repeat this step with switch S2 closed and S1 open. Repeat again with both switches S1 and S2 closed. Set down the truth table of a NAND circuit as given previously in the April column.

## experiment 2 flip-flop

Rewire the experiment board to the circuit of **fig. 7**. Two of the NAND gates of the device are now wired together. The output at pin 3 is connected to pin 4 while output 6 is fed back to pin 2. This

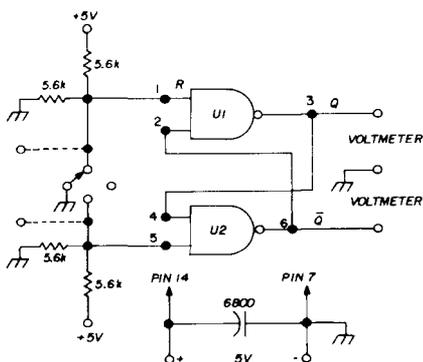

**fig. 7.** NAND gates in flip-flop. U1 and U2 are each  $\frac{1}{4}$  of an SN7400N. Dashed lines show connections for an audio input.

feedback path is normal for a flip-flop multivibrator.

Connect the voltmeter between output 3 and common. Connect ground to input 1 with the switch. Is output 3 logic 1 or logic 0? Connect the voltmeter to output 6. Is it logic 1 or logic 0?

Restore the voltmeter to output 3. Set the switch to its unused center position. What happens to output 3 and output 6?

Connect the voltmeter to output 3. Use the switch to ground input 5. What happened as the switch closed? Check the outputs at 3 and 6. Note how the output is toggled as the switch is changed from input 1 to input 5 and vice versa. Complete the truth chart of **fig. 8**.

1 R	5 S	3 Q	6 $\bar{Q}$

**fig. 8.** NAND gate flip-flop truth chart to be filled in from actual experimental readings taken with the circuit of **fig. 7**.


## experiment 3 ac flip-flop

Change the input of the flip-flop, **fig. 7**, in accordance with the dashed lines. Set the switch to its unused center position. Apply a 1000-Hz sine wave to the input. Connect the oscilloscope between output 3 and common.

Slowly increase the amplitude of the audio signal. When the audio level is adequate the sine wave will toggle the flip-flop. Note the quality of the output square wave. It has steep leading and trailing edges. Flip-flops are often used to sharpen the edges of slower rising and distorted waveforms.

Increase the level of the audio input wave. Observe how constant in voltage the output remains once the input wave is sufficient in magnitude to cause toggling. Try audio input frequencies of 100, 10,000 and 100,000 Hz. The quality of the output waveform remains good and the amplitude constant.

Reset to 1000 Hz. Display four square

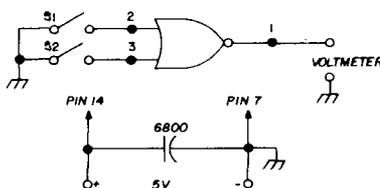

**fig. 9.** A 7402 NOR gate set up for dc operation.

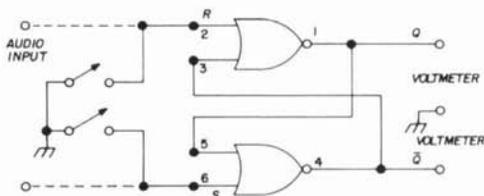



fig. 10. NOR gates arranged into a flip-flop.

waves on the oscilloscope screen. Transfer the oscilloscope to input 1 and note that output frequency and input frequency are the same.

## experiment 4
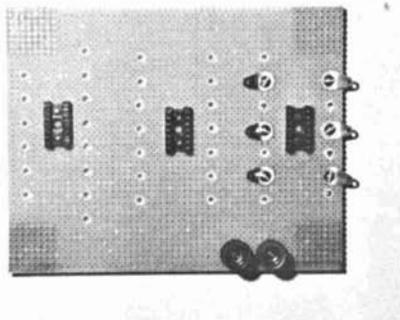
### NOR gate

Remove the 7400 positive NAND gate and prepare to use a 7402 NOR gate IC. Connect the circuit of fig. 9. Positive voltage is applied to pin 14 and ground to pin 7 as for the 7400. In this case, however, pins 2 and 3 are the inputs while pin 1 is the output. Switching arrangement is the same as that of the NAND circuit shown in fig. 5. Open is again logic 1; the switch closed to common corresponds to logic 0. Connect the voltmeter to the output and set down the voltage readings with both switches open, both switches closed, S1 open and S2 closed and, finally, S2 open and S1 closed. Prepare your own truth chart and compare with the NOR logic truth table of April's column.



W3FQJ's breadboard for IC experiments uses IC sockets and solderless binding posts for quick circuit changes while still protecting the delicate IC wire leads.

Open both switches and apply a 1000-Hz tone to the input. Connect the oscilloscope across the output. Remember, to activate the NOR gate both inputs must be driven to the logic 0 state. Therefore, when driven from a single audio source, the two inputs must be paralleled.

Slowly increase the audio level. After passing a certain point you will obtain NOR gate output. Again, a good square wave is obtained. Check the output on 100, 10,000 and 100,000 Hz.

2 R	6 S	1 Q	2 $\bar{Q}$

fig. 11. NOR gate flip-flop truth chart to be filled in from actual experimental readings taken with the circuit of fig. 10.

## experiment 5

### NOR gate flip-flop

Connect the flip-flop circuit of fig. 10. To observe the operation of the NOR gate flip-flop you will need two spst switches. Use the voltmeter to measure the voltage at outputs 1 and 4. Record these outputs for switches S1 and S2 closed, S1 and S2 open, S1 open and S2 closed, and, finally, S2 open and S1 closed. Note that for both S1 and S2 closed, logic 0, the output is indeterminate and is a function of whether S1 or S2 was closed previously. Complete the truth chart of fig. 11.

## experiment 6

### master crystal oscillator

A simple dual-input NOR gate, fig. 12, can be connected externally into a feed-

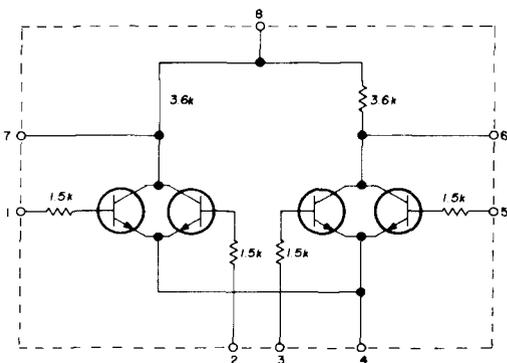


fig. 12. HEP580 MRTL dual-input NOR gate.

back circuit to perform as either a free-running multivibrator or a crystal-controlled square-wave generator. In the latter case, a crystal is inserted in the feedback path between output 6 and paralleled inputs 1 and 2. The second feedback path is provided by a capacitor inserted between output 7 and inputs 3 and 5.

The HEP 580 IC has an 8-pin base. Mount an 8-pin round socket on the breadboard. Assemble the circuit shown in fig. 13. Only four external parts are required: two resistors, a capacitor and the crystal socket. This is one of the simplest 100-kHz crystal calibrators you can make.

The square wave output can be observed at pins 7 and 6. The harmonic content of the IC output is high and clear

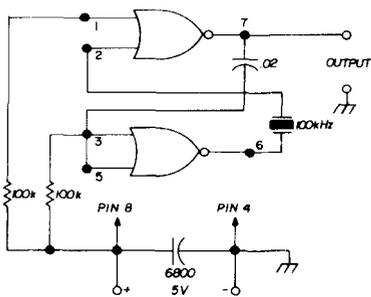


fig. 13. 100-kHz crystal oscillator using the HEP580.

calibration points can be found on frequencies as high as 52 MHz.

## experiment 7

### 2-to-1 flip-flop counter

The addition of a low-cost J-K flip-flop multivibrator to the output of the 100-kHz generator provides you with a 50-kHz output as well. A TTL SN7472 will do, fig. 14. It can be inserted into the same in-line socket used previously in experimenting with the NAND and NOR gates. Supply voltage and common are again attached to pins 14 and 7 respectively. The output of the 100-kHz generator, pin 12, is applied to the clock input, pin 12. It is possible to obtain 50-kHz output at either the Q or  $\bar{Q}$ , pins 8 and 6

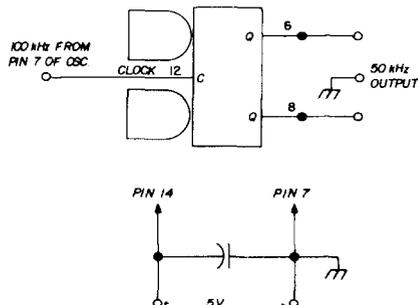


fig. 14. An SN7472 J-K flip-flop used as a 2-to-1 divider.

respectively, of the counter.

Observe the input signal at pin 12 with the oscilloscope. Display four cycles of the square wave. Now transfer the oscilloscope to the Q output, pin 8, and note that the frequency has been halved. A 2-to-1 count has been made.

Calibration points can be heard readily up into the six-meter band. In using a calibrator, the oscillator alone (divider switched off) can be used to locate 100-kHz points. Output of the divider can then be used to locate the 50-kHz intermediate points.

Next month additional counter stages will be added to the calibrator.

ham radio

# Semiconduct

• MOTOROLA • RCA • FAIRCHILD



Actual Size

## DIGITAL READOUT

At a price everyone can afford **\$3.20**

- Operates from 5 VDC
- Same as TTL and DTL
- Will last 250,000 hours.

The MiNiTRON readout is a miniature direct viewed incandescent filament (7-Segment) display in a 16-pin DIP with a hermetically sealed front lens. Size, and appearance are very similar to LED readouts. The big difference is in the price. Any color filter can be used.

## SPECIAL OFFER

- Digital readout
- BCD to 7 — Segment Decoder/driver
- 7490 Decade Counter
- 7475 Latch

Only **\$8.20**

## PLESSEY SL403D

**3.5 W AUDIO AMP IC**  
**HI-FI QUALITY**

**\$3.95**

with 12 pages of construction data

## NATIONAL DEVICES

LM370 AGC/Squelch amp .....	\$4.85
LM373 AM/FM/SSB IF strip/Det .....	\$4.85
LM309K 5V 1A regulator. If you are using TTL you need this one. ....	\$3.00

## POPULAR IC's

MC1550	Motorola RF amp .....	\$1.80
CA3020	RCA 1/2 W audio .....	\$3.07
CA3020A	RCA 1 audio .....	\$3.92
CA3028A	RCA RF amp .....	\$1.77
CA3001	RCA .....	\$6.66
MC1306P	Motorola 1/2 W audio .....	\$1.10
MC1350P	High gain RF amp/IF amp .....	\$1.15
MC1357P	FM IF amp Quadrature det .....	\$2.25
MC1496	Hard to find Bal. Mod. ....	\$3.25
MFC9020	Motorola 2-Watt audio .....	\$2.50
MFC4010	Multi-purpose wide-band amp .....	\$1.25
MFC8040	Low noise preamp .....	\$1.50
MC1303P	Dual Stereo preamp .....	\$2.75
MC1304P	FM multiplexer stereo demod .....	\$4.95

## FETS

MPF102	JFET .....	\$0.60
MPF105/2N5459	JFET .....	.96
MPF107/2N5486	JFET VHF/UHF .....	\$1.26
MPF121	Low-cost dual gate VHF RF .....	.85
MFE3007	Dual-gate .....	\$1.98
40673	.....	\$1.75
3N140	Dual-gate .....	\$1.95
3N141	Dual-gate .....	\$1.86

## PLESSEY INTEGRATED CIRCUITS GREAT FOR SSB RCVRS AND XMTRS

SL610	low noise 150 MHz RF good AGC .....	\$5.65
SL612	low distortion IF good AGC .....	\$5.65
SL621	AGC generator for SSB rcvrs .....	\$8.30
SL620	AGC gen. SL630 Audio .....	\$8.30
SL630	multipurpose audio amp .....	\$5.35
SL640	top performing balanced mixer .....	\$10.88
SL641	low-noise rcvr mixer .....	\$10.88

## SIGNETICS PHASE LOCKED LOOP

NE561B	Phase Lock Loop .....	\$9.50
NE562B	Phase Lock Loop .....	\$9.50
NE566V	Function Generator .....	\$9.50
NE567V	Tone Decoder .....	\$9.50
N5111A	FM/IF Demodulator .....	\$2.65

## PREMIUM QUALITY TEXAS INSTRUMENTS TTL IC's

7447	7-seg. decoder/driver for the digital readout. ....	\$2.25
7400	gates .....	.30
74H00	high speed gate .....	.96
7401	same as 7400 except open collector .....	.30
7402	Quad 2-input NOR gate .....	.30
7404	Hex inverter .....	.30
7405	Hex inverter .....	.30
7410	Triple 3-input NAND .....	.30
7420	Dual 4-input NAND .....	.30
7441	NIXIE driver .....	\$1.95
7490	decade counter .....	\$1.40
7475	quad latch .....	\$1.40
7495	shift Reg. ....	\$2.00
7493	divide by 16 .....	\$1.90
74121	monostable .....	\$1.80
7473	dual flip-flop .....	.85
851/951	DTL monostable multivibrator .....	\$1.00

## MOTOROLA DIGITAL

MC724	Quad 2-input RTL Gate .....	\$1.00
MC788P	Dual Buffer RTL .....	\$1.00
MC789P	Hex Inverter RTL .....	\$1.00
MC790P	Dual J-K Flip-flop .....	\$2.00
MC799P	Dual Buffer RTL .....	\$1.00
MC780/880	RTL decade counter .....	\$3.00
MC1013P	85 MHz Flip-flop MECL .....	\$3.25

# r Supermart

NATIONAL • HEP • PLESSEY •

MC1027P	120 MHz Flip-flop MECL	\$4.50
MC1023	MECL Clock driver	\$2.50
MC4024	Dual VCO	\$3.00
MC4044	Freq. Phase Det	\$3.00

## TRANSISTORS & DIODES

MPS6571		.60
MPS A12	NPN Darlington gain 20K	.90
2N706	packet of 4	\$1.00
2N2218	packet of 2	\$1.00
1N4001	packet of 6	\$1.00
1N4002	packet of 6	\$1.00
1N4004	packet of 6	\$1.00

## NEW FAIRCHILD ECL HIGH SPEED DIGITAL IC's

9528 Dual "D" FF toggles beyond 160MHz \$4.65  
 9582 Multi-function gate & amplifier \$3.15  
 95H90 300 MHz decade counter \$16.00  
 A 95H90 & 9582 makes an excellent prescaler to extend low frequency counters to VHF — or use two 9528s for a 160 MHz prescaler.

## MORE RCA IC's

CA3088E	AM rcvr subsystem	\$2.50
CA3089E	FM IF system with circuits for IF amp., Det., AF preamp., AFC, Squelch, & tuning meter	\$3.90
CA3018	Transistor array	\$1.55
CA3011	FM IF amp	\$1.65
CA3053	Cascode amp	.90

## MORE MOTOROLA IC's

709	Op amp dual in-line	.70
741	Op amp dual in-line	.80
MC1437P	Op amp dual in-line	\$2.35
MC1460G	Voltage reg. TO-5	\$3.85
723	Voltage reg. dual in-line	\$1.25
MC1466L	Voltage reg. dual in-line	\$8.00
MC1463R	Voltage reg. power pkg.	\$4.60
MFC6040	Electronic attenuator	\$1.30
MFC6030	Voltage reg	\$1.40
MFC4000	¼ watt audio	\$1.00
MC1454G	1-watt audio TO-5 (same as MC1554G)	\$4.00

## ALSO TEXAS INSTRUMENTS OP AMPS

709	Op amp TO-5	.80
741	Op amp TO-5	.95
747	Dual 741 in TO-5	\$1.25

## MOTOROLA TUNING DIODES

Silicon voltage variable capacitance diodes in TO-92 plastic case like plastic transistors. Both standard Motorola and HEP numbers are listed devices are same. Capacitance value is typical at -4Vdc. Tuning ratio is approx. 3:1.

MV2101/R2500	6.8 pF	\$1.10
MV2103/R2501	10 pF	\$1.10
MV2105/R2502	15 pF	\$1.10
MV2109/R2503	33 pF	\$1.10
MV2112/R2504	56 pF	\$1.10
MV2115/R2505	100 pF	\$1.10

## FAIRCHILD RTL DIGITAL IC's

UL900	Buffer	.80
UL914	Dual 2-input Gate	.80
UL923	JK flip-flop	\$1.50

## MOTOROLA ALL-IN-ONE COUNTER

MC4050P	Decade counter-Latch-7 Seg. decoder in one dual in-line	\$10.60
---------	---	---------

## CORES AND BEADS

T200-2		\$2.00
KW	Balun kit only	\$3.50
T68-2	3 cores	\$1.00
T50-2	3 cores	\$1.00
T50-6	3 cores	\$1.00
T50-10	3 cores	\$1.00
T44-10	3 cores	\$1.00

## BEAD SPECIAL

Ferrite Beads	1 doz.	\$1.00
---------------	--------	--------

NOTE THERE ARE MORE THAN 500K DIFFERENT TRANSISTOR, DIODE AND INTEGRATED CIRCUIT DEVICE TYPES AVAILABLE FROM THE VARIOUS MANUFACTURERS. WE CAN SUPPLY MOST OF THEM ON ORDER — SPECIALS WHICH ARE NOT IN STOCK ONLY TAKE A COUPLE OF WEEKS. SO IF YOU NEED MOTOROLA, RCA, FAIRCHILD, NATIONAL DEVICES SEND IN YOUR ORDER. ANY EXCESS YOU REMIT WILL BE REFUNDED IN CHECK OR CASH. NO CREDIT COUPONS.


NOTE: WE DO NOT SELL SURPLUS OR REJECT DEVICES. ALL ARE PREMIUM QUALITY AND FULLY GUARANTEED.

Please add 35¢ for shipping
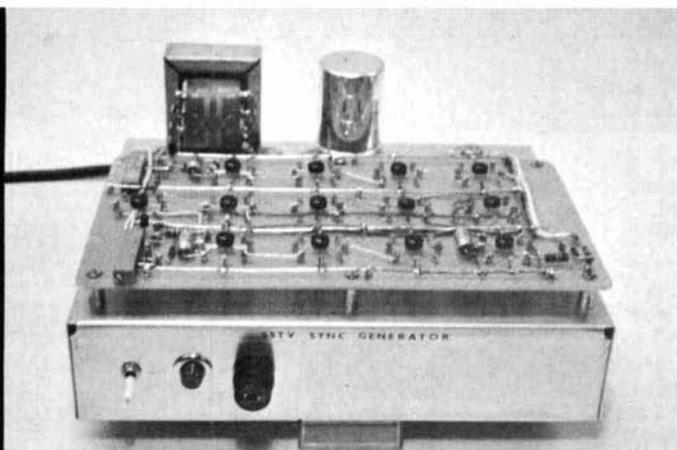
## CIRCUIT SPECIALISTS CO.

Box 3047, Scottsdale, AZ 85257

FACTORY AUTHORIZED  
HEP-CIRCUIT-STIK  
DISTRIBUTOR



## sync generator

for  
sstv

RTL flip-flops  
and gates  
in a circuit  
designed to provide  
stable horizontal  
and vertical  
sync pulses for  
slow-scan television

David R. Patterson, WA2EWO, 524 Gropp Avenue, Trenton, New Jersey

The availability of low-cost resistor-transistor logic (RTL) ICs suggests the possibility of constructing a stable sync generator for slow-scan television application.

Present sstv standards use a 15-Hz line-scanning rate and an 8-second frame rate. This combination gives the 120-line raster suggested under present standards. Normally these scanning rates are referenced to the 60-Hz power line frequency to provide stability and reduce 60-Hz hum in the sstv picture.

### counting circuit

The counting-type sync generator shown here was built using two popular IC twins — the RTL 914 dual 2-input positive-logic NOR gate and the RTL 923 J-K flip-flop.\* The J-K flip-flop is a very convenient device for use in counting circuits. One input pulse changes the output state, while a second pulse is

\*Don't overlook the HEP line of ICs for this and similar projects. The HEP series are selected "universal" substitutes chosen from Motorola's extensive family of devices for "Hobbyists, Experimenters, and Professionals" — hence "HEP". For example the 914 gate (Motorola MC714G) is available as HEP584. It will perform as indicated in this application. **editor.**



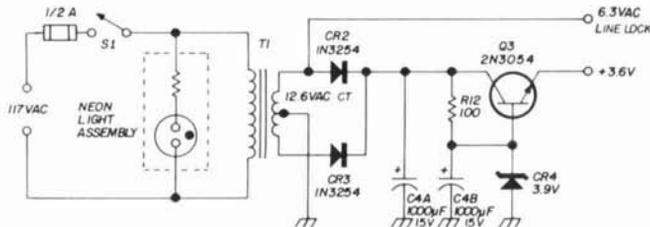


fig. 3. Suggested power supply. Regulation is provided by the zener in the base of Q3.

## counting sequence

The block diagram of fig. 1 shows three basic counting sequences in the sync generator. The reference frequency, 60 Hz, is divided or counted by 4. As explained previously, this process will require two flip-flops; i. e.,  $2^2 = 4$ . This circuit provides one output pulse for four input pulses, or an output frequency of 15 Hz. The next counter is a basic "divide by 16" counter that has been modified by gates to count by 15. Two gates (one IC package) are parallel-connected to sense the output of each J-K flip-flop and reset on the 15th input pulse. Thus the output is 1 Hz. The final counting sequence is provided by a "divide by 8" counter. Since  $2^3 = 8$ , three flip-flops and no gates are required. For every 8 pulses one output pulse results, or one output pulse every 8 seconds. This provides the stv frame rate described above.

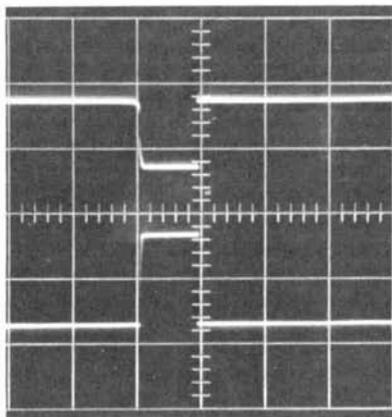


fig. 4. Oscillograph of the 15 Hz scanning pulse.

To provide the desired output-pulse width, two gates (one IC package) may be connected as a monostable multivibrator. The multivibrator output pulse can be adjusted to the desired pulse width by changing the RC time constant and bias voltage, or both, applied to the gate. Two units supply the proper output-pulse width of 5 ms for the 15-Hz scanning rate and 30 ms for the 8-second vertical or frame rate. A third multivibrator supplies a fast-fall-time pulse, derived from the power-line frequency, to trigger the first counter. The complete sync generator is shown in fig. 2.

## power supply

Both output-pulse polarities are indicated on the schematic. Individual preferences will determine the actual polarity used. A simple emitter follower, zener-referenced power supply is shown in fig. 3.

## adjustments

Only two adjustments are required. The output-pulse width is adjusted by R4 to provide the 5-ms output pulse at a 15 Hz rate, and R8 is adjusted to provide a 30-ms pulse every 8 seconds. Fig. 4 shows the plus and minus output of the 15-Hz, 5-ms line-scanning pulse. Positive output is 1 volt, and negative output is 3.6 volts.

The circuit described has proved to be an economical way to obtain stable synchronizing pulses for sstv use. The breadboard-type construction allows easy access to any point in the counting circuits if pulses other than those for sstv are desired.

ham radio

# getting started in microwaves

Buy new,  
build your own,  
or scrounge surplus;  
here is how  
to start experimenting  
with microwaves

William T. Roubal, 2725 Montlake Boulevard East, Seattle, Washington 98102

Many potential microwave enthusiasts have probably been frightened away simply because of the high price of new equipment. Such fears need not prevail, however, since many quality waveguide components, tubes and auxiliary pieces are available from dealers in surplus, often for as little as 1% of the new-market cost. Additionally, if you are mechanically inclined and can do metal work, you can fabricate some really beautiful pieces of your own equipment. Homemade components may not be devices calibrated to the nth degree, but they will be quite functional and will illustrate basic principles.

This article, therefore, is to show that you don't need unlimited resources to do some very interesting things with microwaves. Accordingly, nothing in the way of theory will be presented here. There are numerous applications for microwaves, both in communication and scientific research. The beginner as well as the advanced reader will find the public and college libraries the best source of information on both theory and applications.

## getting started

Pick up an inexpensive, low-power

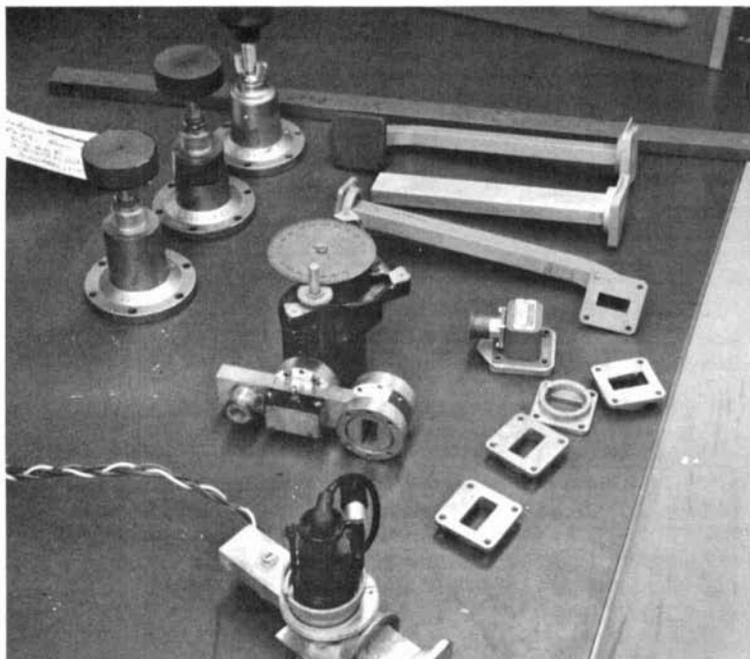


fig. 1. X-band waveguide components. From bottom to top are surplus 723 A/B klystron and holder, surplus resonant cavity, straight and bent sections of waveguides, UG-39/U waveguide flanges for do-it-yourself construction projects and waveguide-to-coax adaptor (next to flanges). The peculiar looking objects at the upper left are waveguide supports and were made by turning down the bakelite knobs salvaged from broken pressure regulators. The total value of the components if purchased outright would exceed \$1,000. From surplus, all were obtained for less than \$50.

klystron tube, hook it up to an appropriate power supply, and you're generating microwaves — no need to worry about interelectrode capacitance limiting

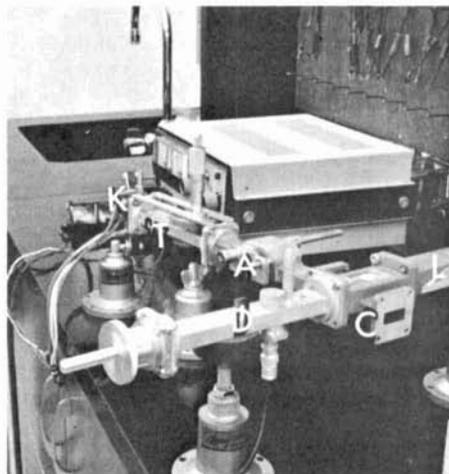


fig. 2. Experimental X-band microwave string.

your frequency, adjusting external tank circuits or watching lead dress, for all of these, and more, go out the window when you use a klystron. Add a few more inexpensive surplus items (or use homemade devices) and you're off and running. You can gradually expand your projects as your knowledge and technique develop.

Waveguides and related "plumbing" found most commonly are for X-band (9 GHz) applications (fig. 1). Fortunately some of the least expensive klystrons are also X-band generators. Accordingly, I shall limit my discussion to X-band components and methodology.

Fig. 2 shows a microwave string consisting of a Varian 998044 klystron (K), cooled by a small squirrel-cage fan (always force cool even the smallest klystron), homemade slide screw tuner (SST), surplus attenuator (A), surplus directional coupler (C), surplus absorptive

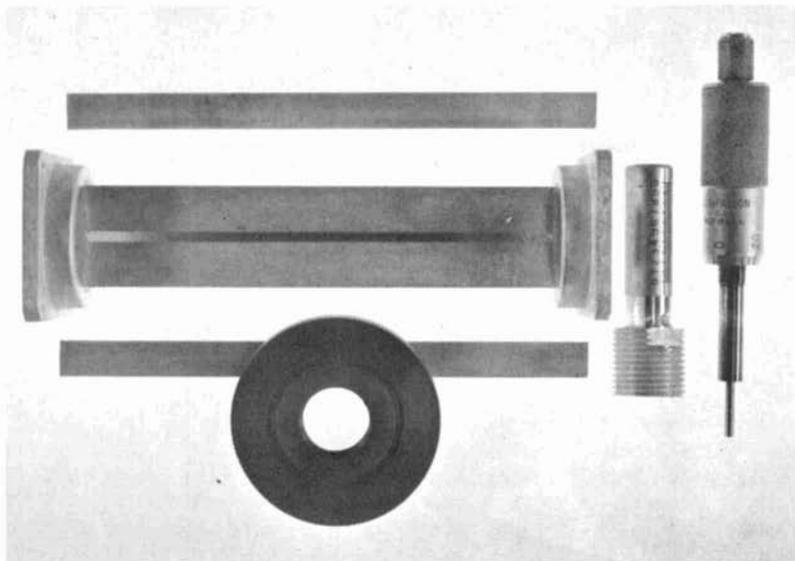


fig. 4. The homemade slide screw tuner. The tuning mechanism is a Sears micrometer body. In this version the threaded cylinder which holds the micrometer is  $\frac{3}{4}$ -inch OD instead of the specified 1 inch. The 1-inch piece is better electrically as it presents a larger surface area upon which to slide. It is included in fig. 5.

load (L) and a homemade tunable crystal detector (D). What you connect beyond the directional coupler will depend on what you want to study or illustrate. The assembly of fig. 2 is used for studying

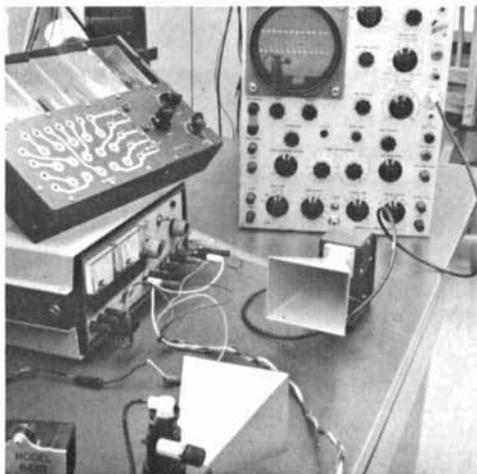


fig. 3. Microwave transmitter and receiver. The Berkeley Physics Lab by Heath-kit — transmitter and receiver (right foreground) and experimental patch board (sitting on power supply) — can be purchased prefabricated and complete, or ordered a part at a time, obtaining only what you need.

dielectric properties of materials which are inserted into a short section of empty waveguide and attached to the open port of the coupler. A simpler setup might consist of a klystron and horn radiator (transmitting antenna), and, at some distance away, a receiver (another horn coupled directly to a crystal detector). Such an arrangement can be used for demonstrating microwave propagation polarization and reflection. Fig. 3 shows one such setup using Heath equipment. Here a square wave is being used to modulate the klystron (achieved simply by coupling a square wave source to the repeller voltage source using a  $0.01 \mu\text{F}$  coupling capacitor.)

### equipment assembly

Since the exposed metal envelope of the reflex klystron tube forms the anode, the tube is normally operated with the anode grounded and with the cathode and repeller operated below ground potential. For either the Varian klystron shown in fig. 2 (\$300, new) or the more common 723A/B (or 2K25) shown in fig. 1 (about \$30, new), you will need a



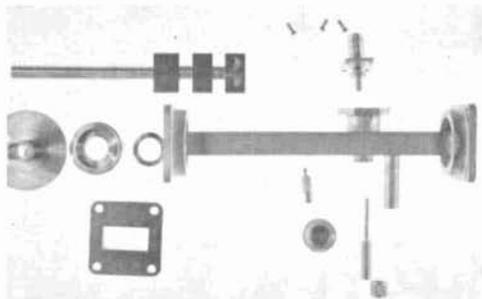


fig. 7. Construction details of the tunable crystal detector. The movable short and the tuning screw are adjusted for maximum crystal output. The drawing of fig. 6 differs in a few dimensions from the unit shown here. The text includes a few construction suggestions and hints on plating the parts. The real perfectionist can plate all the parts with gold.

slotted lines and certain couplers are very carefully mated together during assembly and are best left intact) and remove the tarnish using any of the ordinary liquid dip tableware tarnish removers.

Many used components will be made entirely of copper, bronze or brass without plating; more often than not, tarnish, corrosion and old paint are to be expected. Heavy tarnish, pitting and old paint can be removed from exterior surfaces with fine grit, wet-dry sandpaper and water. Generally, the internal surfaces will show less imperfections than the outside. Unless absolutely necessary, do not apply sandpaper or files to internal surfaces because close tolerances should not be altered. After the piece has been cleaned up, etch the piece briefly in mild acetic acid (or very dilute nitric acid). Rinse and dry the part, and plate the entire part with electroless tin.\* The tin plate will improve electrical conductivity and will add new life to the metal. Tin-plated metal to be soldered can be heated in a direct flame; the plating will prevent oxidation and discoloration. For the ultimate in conductivity and corrosion resistance, brass parts can be gold plated with Shipley's electroless gold.

ham radio

• LEADERS IN COMPACT ANTENNAS •  
**MAXIMUM EFFICIENCY/MINIMUM SIZE**  
 FOR APARTMENTS • SUBURBAN HOMES  
 Marine and Portable Operation  
 Packaged for APO and FPO Shipping




ALL MODELS COMPLETELY WEATHERPROOFED

**NEW**

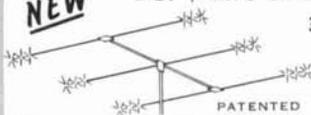**B-24 + RK-3 COMBINATION**

**3 ELEMENTS**  
**10-15-20**  
**METERS**




PATENTED

Bands	10-15-20 Meters
Power Rating	1400 Watts P. E. P.
Total Boom Length	11'
Turning Radius	7'-10"
Total Weight	23 lbs.
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

**B-24 + RK-3 Combination Net \$94.95**  
**RK-3 Reflector Kit (only) Net \$36.95**

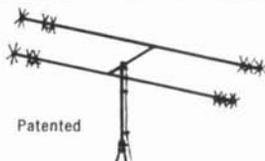The features of the popular B-24 plus the new RK-3 reflector kit make a unique 3 element combination. Choose the combination or add the RK-3 to your present B-24 and enjoy the improved gain and front to back.



Patented

Bands	6-10-15-20 Meters
Power Rating	1400 Watts P.E.P.
El. Length	11'
Turn. Radius	7'
Total Weight	13 lbs.
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

**6-10-15-20**  
**METERS**

The time proven B-24 4-Band antenna combines maximum efficiency and compact design to provide an excellent antenna where space is a factor. New and loading for maximum radiation efficiency. No center loading.

**Model B-24**  
**Net \$62.95**

**MULTIBAND COAXIAL ANTENNA**  
 for 6 - 10 - 15 - 20 METERS

Needs no ground plane radials. Full electrical 1/2 wave on each band. Excellent quality construction. Mount with inexpensive TV hardware. Patented.

Power Rating	1400 Watts P.E.P.
Total Weight	6 lbs.
Height	11'
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

**Model C4 Net \$36.95**




See our entire line at your nearby distributor or write the factory for further information and literature.

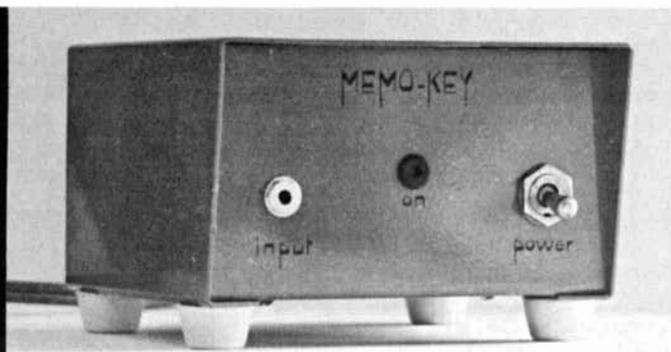**Mini-Products, Inc.**

Call 814 - 454-2171

1001 W. 18th Street • Erie, Pennsylvania 16502




## memo-key

An inexpensive  
tape recorder  
and this  
electronic switch  
will increase your  
enjoyment of CW  
and RTTY

This article may revolutionize your thinking about using code wheels for CW operation and paper tapes for RTTY. The memo-key can enhance your operating pleasure in many ways. Applications of the design are numerous and are limited only by your imagination.
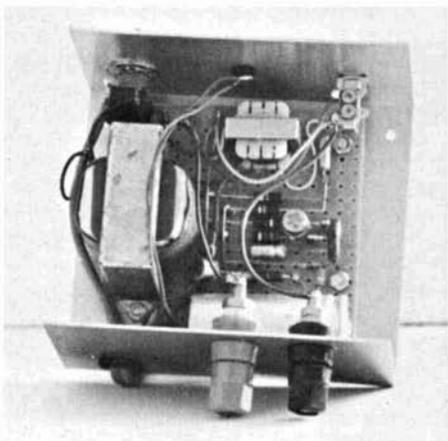
### how it works

The memo-key is shown in **fig. 1**. The circuit detects the presence of tones of various lengths that have been pre-recorded on tape. These tones, which may be the recorded output of a code oscillator, side-tone from a receiver or keyer, or even a whistle, are converted to



Suggested parts layout.

James R. Huffman, WA7SCB, Box 307, Mountain View, Wyoming 82939

on-off switching impulses in the output stage. The device will switch a maximum of 100 mA at 40 volts, which is sufficient to actuate a CW keying relay or drive a grid-block-keyed transmitter directly. Other applications are described later.


The memo-key may be operated from batteries or a power supply, as shown in **fig. 1**. Current drain is low, because the high-current output switch is not connected across the power supply. When driving a relay, a diode should be placed across the relay coil to suppress high-voltage spikes. The value of capacitor C4 may have to be changed slightly when switching currents other than 100 mA. The discharge time constant of the circuit is set for switching 100 mA; any load less than 100 mA slows the switching action considerably. In fact, when switching a low-current RTTY load, you may wish to eliminate C4 entirely, although sensitivity will decrease.

Two modifications may be necessary if you wish to use the memo-key with a tape deck. A level control should be connected across the deck output, then to the memo-key input. Also, no transformer will be needed at the input (T1 in **fig. 1**).

### construction

Building the memo-key is no problem. A suggested layout is shown in the photo; however, layout isn't critical, nor is packaging. You may wish to use the utility box shown; rack-mount the unit, or even install it in the same enclosure with an RTTY converter. If you'd like to build a code oscillator, try one of the small 2-transistor units available from *Burstein-Applebee* or *Allied Radio Shack*. These units are small, operate from 6 Vdc, and are inexpensive.

As for the tape recorder, a good rule-of-thumb is: your existing tape recorder will probably be satisfactory for the applications shown. If you must purchase a tape recorder for this project, bear in mind the convenience of filling cassettes. Some of the catalog outlets

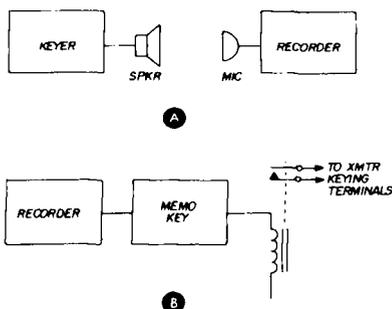


**fig. 1.** Memo-key schematic. Circuit is a simple electronic switch that will handle loads to 40 volts at 100 mA. Observe polarities when using suggested power supply or batteries.

send flyers showing cassette recorders for less than \$20.00. Any of these recorders is satisfactory for use with the memo-key applications shown in this article.

### some applications

Applying the memo-key to your particular needs is easy. For example, memo-key may be used as a code-wheel replac-

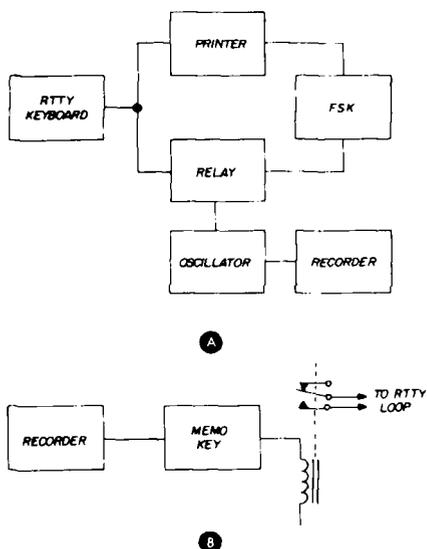

**fig. 2.** Using the memo-key for CW. Circuit keys the transmitter according to prerecorded input on magnetic tape. Reprogramming is easy, unlike paper tapes or "code wheels."


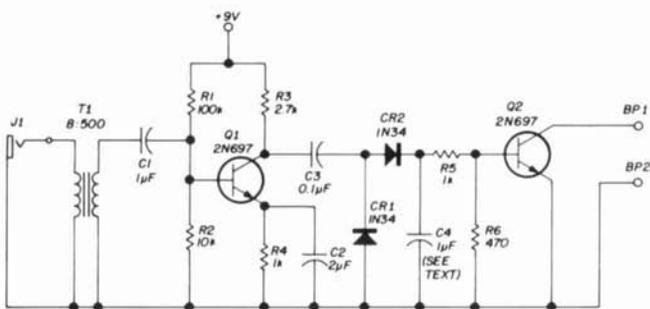


fig. 3. Memo-key for RTTY. Recorded input is stored on tape (mark = tone; space = no tone). Recorder output drives memo-key, which actuates a relay to drive the RTTY keyboard. To keep loop closed, the bias oscillator can feed a mark signal except in "play" mode.

ement to call CQ in contests. It may be used to close and open your end of a contact. In RTTY, you may use the memo-key to send "fox" tests, standard CQ's, elaborate ID's, or anything that can

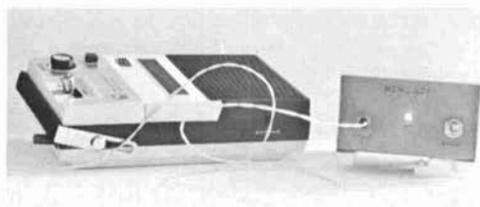station is also possible—all information is remembered and stored as in a complex digital computer. You could push a "play" button on the tape recorder, and instantly the room lights would come on, then the transmitter and receiver tube filaments — all by feeding a shift register with the memo-key output.



Complete memo-key with cassette recorder. System is compact and offers easy storage of data for the active operator.

be put on paper tape. Other applications are also possible. Voiced "dits" and "dahs" can be converted to code-oscillator output for code-practice sessions.

Control of transmitters, receivers, or other equipment in the home or amateur

### concluding remarks

The advantages of using a system like memo-key are numerous: for one, programming is easily changed. The old code wheel is fine for calling CQ, but it doesn't lend itself to reprogramming. With memo-key, you can record yourself calling a station; then at the beginning and end of each transmission merely energize the recorder, and memo-key takes care of the identification.

Another advantage of memo-key is that tape storage is easily accomplished—a boon to the active RTTY and contest operator. A small cassette properly labeled would reduce storage space considerably. Since those paper tapes represent a lot of work it's to your advantage to use magnetic-tape storage, because magnetic tape is nearly impossible to rip, tear, or otherwise mutilate if the tape is neatly tucked inside a cassette case.

Wherever you put it; however you package it; however you use it—the memo-key will serve you well.

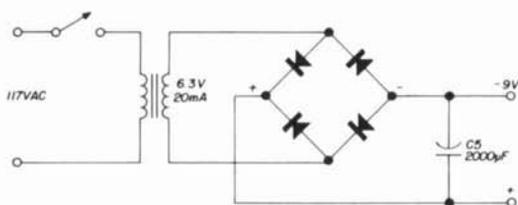


fig. 4. Suggested power supply circuit.

ham radio


# Savoy

## High Accuracy Crystals

For over 30 years



TYPE 900 A

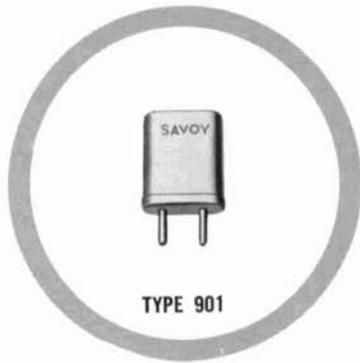

TYPE 901

*Crystals shown are actual size.*

Either type, for transmitter or receiver.

**\$3.75**

Postpaid in U.S.A.

Specify crystal type, equipment make and model,  
desired frequency, transmit or receive.

For amateur two meter FM use in Regency, Varitronics, Standard  
Drake, Tempo, Swan, Galaxy, Trio, Sonar, Clegg, Linear SBE.


GE, Motorola, RCA, oven use \$4.95. Gladding \$7.95



**Savoy Electronics, Inc.**

P.O. Box 7127 - Fort Lauderdale, Florida - 33304

Tel: 305-566-8416 or 305-947-1191

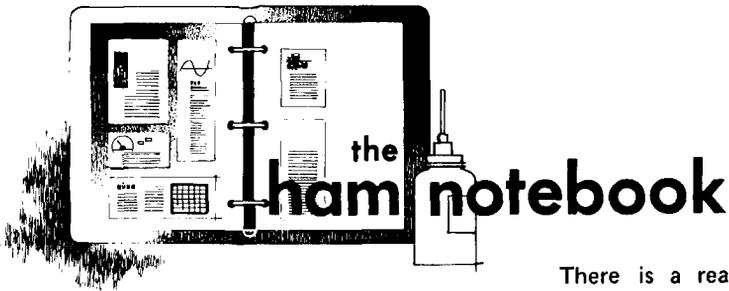

## horizontal or vertical?

Antennas are considered to be reciprocal devices, transmitting and receiving equally well. Common amateur practice is to use the same antenna for both functions. Under some conditions, though, better results can be obtained with separate antennas.

On 1.8 and 3.5 MHz, and to a lesser extent on 7 MHz, high-gain directional antennas are impractical for most hams. The average amateur low-frequency antenna is fairly omnidirectional. Therefore, the antenna can generally provide no improvement in the signal-to-noise ratio, when the principal noise source is atmospheric.

Long-distance communication requires low-angle radiation. A study of theoretical antenna patterns shows that a horizontal dipole has the best low-angle radiation characteristics when it is one-half wavelength above ground. Since this is 140 feet at 3.5 MHz, most amateur 3.5-MHz horizontal antennas radiate at predominantly high angles — fine for short skip, but not very good for the really long-haul stuff.

The radiation from a vertical antenna is mostly low-angle at any height less than  $5/8$  wavelength. Many hams, hoping to improve their low-frequency DX performance, have installed vertical antennas and radial ground systems. They have generally been disappointed; they did not hear any more DX than they did on their old horizontal antennas, nor was the DX they did hear any louder. Sometimes the vertical seemed to be worse.

There is a reason for this. On the low-frequency bands the chief limiting factor is noise. At any time, atmospheric and man-made noise have a local field strength with which the signal must compete to produce a usable signal-to-noise ratio at the output of the receiver. If the signal field strength does not have a favorable relationship to the noise field strength, there is nothing to be done. The improvement has to be made at the transmitting end — either by the distant station raising power, or by increasing the efficiency of *his* antenna. It might almost be said that the configuration of the *receiving* antenna on the low-frequency bands is unimportant. As long as the receiving antenna is long enough to produce a fairly loud noise output from the receiver, it might as well be a short, random-length piece of wire!

The transmitting antenna may actually be worse for receiving. This is likely to be true if the antenna is vertical. Vertical antennas are much more sensitive to man-made noise, which is predominantly vertically polarized. Even after point sources of man-made noise are eliminated, almost every amateur lives in an environment with a background of man-made noise that is difficult to distinguish from true static. The situation is worst on the low-frequency bands.

I have been reading about the sensitivity of vertical antennas to man-made noise for years, but it was not until I had both vertical and horizontal 7-MHz antennas available at the flick of a switch that I realized how great the difference was. Switching from horizontal to vertical usually resulted in a noise increase of about 10 dB!

Transmitting, it was a different story.

For example, from my location ZS1A is pretty good DX on 7 MHz. I was able to work him with relative ease using my roof-mounted trap vertical. Using my horizontal dipole, I was usually able to hear him with a better signal-to-noise ratio. But I was *never* able to work him using the horizontal for transmitting.

Later experiments working the Orient and the Pacific confirmed this. The horizontal was better for receiving, but the vertical was from one to three S-points better on transmit. The difference, of course, was the greater man-made noise pickup of the vertical. I did not have a vertical antenna for 3.5 or 1.8 MHz, but I am sure the results would have been comparable.

From my own experience and a study of antenna and noise theory, I believe the following principles can be established:

1. For extreme long-distance transmission on low-frequency bands, verticals should be better than horizontals and probably are.

2. Comparisons of the effectiveness of low-frequency verticals with horizontals on the basis of receiving tests are not always valid. Field-strength measurements should be made.

3. For low-frequency DX reception, the antenna is of little importance, but a vertical may be worse than a horizontal because of man-made noise.

Undoubtedly the best scheme is to have both vertical and horizontal antennas available, with switching to make it possible for either to be used for receiving or transmitting independently of the other.

Of course, these findings only apply when it is not possible to erect an antenna having worthwhile gain and directivity — the usual situation on the low-frequency bands.

Harry R. Hyder, W7IV

## Swan 350 CW monitor

This simple circuit provides a built-in CW monitor for the Swan 350. It can be

built compactly, installed quickly and has plenty of output.

The parts were mounted on a small printed-circuit board with the resistors installed vertically. I used a solder lug as a mounting foot, secured by one of the crystal filter mounting nuts. This location permits relatively short leads to the required locations.

The resistor, R6, provides isolation of the circuit to prevent loading of the 6GK6 grid circuit and to attenuate the oscillator output to a comfortable level. A value between 1 and 2 megohms should

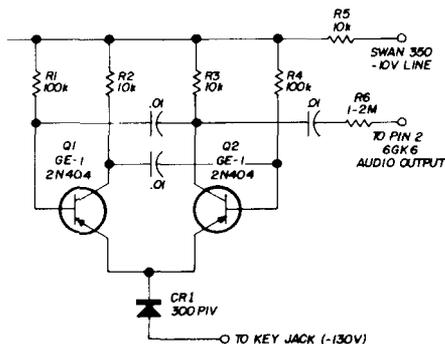


fig. 1. Simple CW monitor for the Swan 350.

do. With the components shown, the frequency is approximately 800 Hz. This frequency may be changed by altering any of the constants shown. The simplest way would be substituting various transistors. Just about all transistors will oscillate, and combining a germanium audio type and a pnp silicon rf type can provide some interesting notes!

With the transceiver in the receive mode and the audio and rf gain controls down, the oscillator can be used for practicing the code or adjusting a keyer. I use a pair of stereo headphones with the sections connected in parallel, and the note has more than enough volume. If you use a speaker, decreasing R6 to 1 megohm or 0.5 megohm should blast your eardrums. Changing the volume control during transmit will vary the output but will not change the pitch of the note.

Paul K. Pagel, K1KXA

# new products

## hf receivers



Radio Shack has introduced two new all solid-state 11-band receivers, the AX-190 for amateur band coverage and the SX-190 for general communications and shortwave listening.

Both receivers are dual conversion with a crystal-controlled first oscillator and tunable second oscillator. Sensitivity is given as 0.5  $\mu$ V on ssb and CW, and 1.0  $\mu$ V on a-m for 10 dB S+N/N.

A built-in Q-multiplier provides better than 60-dB image rejection and 50-dB spurious rejection. Built-in 25- and 100-kHz crystal calibrators assure visual dial accuracy of within 200 Hz. The dial reads direct to 1 kHz. Frequency stability is said to be better than 500 Hz per hour.

Other features include ceramic filters for sharp selectivity, dual time-constant agc, anl, crystal-controlled bfo, illuminated S-meter and a line/tape output and headphone jack. Each receiver has dual-

regulated power supplies for operation on 120 Vac and 12 Vdc.

The AX-190 is crystal-controlled on 3.5-4, 7-7.5, 14-14.5, 15-15.5, 21-21.5, 27-27.5, 28-28.5, 28.5-29, 29-29.5 and 29.5-30 MHz, with a blank channel for special monitoring between 3.5 and 10 MHz. It has a vfo output and simplified interconnections for easy transmitter hook-up.

The SX-190 is supplied with crystals for reception on 3.5-4, 5.7-6.2, 7-7.5, 9.5-10, 11.5-12, 14-14.5, 15-15.5, 17.5-18 and 27-27.5 MHz, with blank channels for special monitoring on 3.5-10 MHz and 10-30 MHz.

The AX-190 and SX-190 receivers are priced at \$249.95 each, with metal cabinet, 7 x 15 x 10-inches. A matching speaker is available for \$19.95. The receivers are available at any of the local Allied Radio Shack stores. More information is available by using *check-off* on page 94.

## regulated power supplies

The benefits of regulated power supplies are explained by Irving Gottlieb, W6HDM, in his new book "Regulated Power Supplies" published by Howard W. Sams. The first chapter lists the reasons why regulated power supplies are used. These include such benefits as increased efficiency, precision, greater dynamic range, feedback stabilization, higher signal-to-noise ratio and wider frequency response.

The second chapter discusses the static characteristics of regulated power sup-

plies such as dc regulation, temperature effects, stability, long-time and short-time deviations and drift. Other chapters cover dissipation control and the uses of integrated circuits and monolithic modules. Representative examples of commercial power supplies are also explained. 160 pages; \$5.95, softbound, from Comtec Books, Greenville, New Hampshire 03048.

## fm transceiver with tone encoder



SAROC featured the introduction of Ross and White's new two-meter fm transceiver with built-in tone-burst encoder. The new RW-Bnd transceiver offers twelve-channel operation (four crystals supplied), three power levels of 0.1, 1 and 10 watts, all solid-state design, and the three-tone encoder. The tones are factory set for the three most common tone-burst frequencies, but they are easily changed in the field.

The unit sells for \$359.95 with the built-in encoder. The same rig, but without the encoder, sells for \$319.95. This model has provision for the installation of the encoder at any time in the future. Both units come with a microphone and mobile mounting bracket.

For complete specifications on this new rig, write to Ross and White Company, 50 West Dundee Rd., Wheeling, Illinois, 60090 and request the information sheet on the RW-Bnd. You can get the same information by using *check-off* on page 94.

## DIODES

PIV	STUD. MOUNT			
	TOP-HAT 1.5 AMP	EPOXY 1.5 AMP	EPOXY 3 AMP	6 AMP
50	.04	.06	.12	.15
100	.06	.08	.16	.20
200	.08	.10	.20	.25
400	.12	.14	.28	.50
600	.14	.16	.32	.58
800		.20	.40	.65
1000		.24	.48	.75

## RESISTORS

The Following Resistors Are All American Made 1/2 Watt Carbons With Full Leads, Completely Standard. Some 5% Some 10% Some 20%

6.8	1300	24K	1 Meg.
22	1500	33K	1.5 Meg.
27	1800	51K	1.8 Meg.
39	2200	68K	2.2 Meg.
47	2400	75K	2.7 Meg.
82	2700	100K	4.7 Meg.
100	3300	120K	5.6 Meg.
270	4700	180K	9.1 Meg.
330	5600	220K	10 Meg.
390	6800	330K	
470	8200	390K	
620	10K	470K	PRICE: 33/\$1.00 ppd.
750	18K	680K	Values may be mixed.
1000	22K	910K	



Black, Aluminum, Anodized, Heat Sink. Size Approximately 4 3/4" x 1 3/8" h. x 1 1/2" w. Predrilled For TO-3 Transistors. Delco Part #7277151. Factory New. 75¢ Each 3 for \$2.00 ppd.

Rectangular 0 to 1 Mil. Meter. Panel Size Approximately 1 3/8" x 3/4" x 1 1/4" Deep. Basic Movement 0-1 ma. Easily Adjusted For 0 Center With Instructions supplied. Ideal meter For RTTY Use, Etc. American Made. Price: \$1.00 Each ppd.



American Made P.C. Board Type Miniature Trim Pots. Size Approx. 1/2" Diameter. Factory New. Following Values Available: 200 ohm, 500 ohm, 700 ohm, 1500 ohm, 5000 ohm. Price: 25¢ Each, 5 For \$1.00 ppd.

High quality, American Made Transformer. 115 Volt Primary. Secondary 17-0-17 Volt @ 150 ma. Tap At 6.3 Volt For Pilot Light. Ideal For Transistor Pre-Amps, VFO's, etc. Fully Shielded. \$1.50 Each ppd.



Power Transformer. 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3". Price: \$2.50 Each ppd.

6.3 Volt 1 Amp Transformer. Fully Shielded. \$1.60 Each ppd.

ITT 1N4007 28¢ Each ppd.

ERIE 1N270 5 For \$1.00 ppd.

GI 1N914 16 For \$1.00 ppd.

RCA - 2N3055 \$1.50 Each or 3 For \$4.00 ppd.

SEND STAMP FOR BARGAIN LIST  
Pa. Residents add 6% State sales tax  
ALL ITEMS PPD. USA


**m. weinschenker**  
K 3DPJ BOX 353 · IRWIN, PA. 15642

The most powerful signals under the sun!



**Hy-gain**

550A

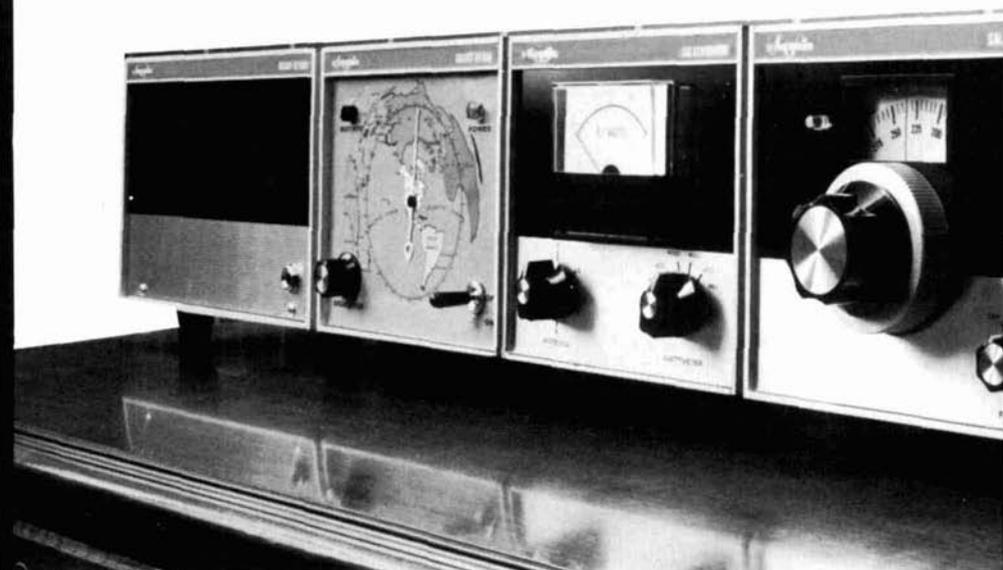

The Hy-Gain 550A is more than precision, professional-quality HAM equipment...it's a complete communications system. Each separate piece is an integral part of a matched system, precision designed and engineered toward one goal...ultimate efficiency.

#### **GT-550A Transceiver**

Top power, runs 550 watts PEP input / Unmatched dependability, flexibility either fixed station or mobile / Low cost / Upper and lower SB selectable without frequency jump / Frequency calibration and read-out accurate to 1 kc using interpolation / Fast attack—slow release AVC for no-pop signal control / Automatic ALC prevents over-driving and adjacent channel splatter / Constant output through high end of 10 meters / Hybrid construction for low-temperature operation and reliability / Standard of the industry in frequency stability / Outstanding receiver sensitivity and selectivity.

**Order No. 855**

**Ham Net \$495.00**

#### **RV-550A Remote VFO**

Solid-state construction / Complete with plug-in cables / Function switch controls Receive-Transceive-Transmit frequency independently.

**Order No. 856**

**Ham Net \$95.00**

#### **RF-550A R.F. Console**

Contains precision wattmeter with top accuracy in range of 3.5/30.0 MHz / Switch select forward or reflected power—calibrated scales are 400 and 4,000 watts full scale / 6-position switch selects 5 antennas or a dummy load.

**Order No. 857**

**Ham Net \$75.00**

#### **SC-550A Speaker Console**

Matching speaker with headphone jack for the transceiver, complete with cable / AC-400 power supply mounts inside console.

**Order No. 858**

**Ham Net \$29.95**

# The Sound System



## NEW! RB-550A Rotator and Control

All new control head and famous Hy-Gain model 400 Rotor Brake Rotator / Now in one complete package, one low price / Solid-state logic circuit furnishes electrical information for rotation and control of tower mounted rotator / 10 times the rotating and braking power of any other rotator.

Order No. 859 Ham Net \$199.95

Phone Patch PR-550 Order No. 812	Ham Net \$ 49.00
Crystal Controlled Adaptor XO-550 Order No. 811	Ham Net \$ 49.00
AC Supply AC-400 Order No. 801	Ham Net \$ 99.95
Mobile Supply G-1000DC Order No. 802	Ham Net \$129.95
CW Filter F-3 Order No. 808	Ham Net \$ 37.50
Calibrator CAL-250 Order No. 806	Ham Net \$ 25.00
VOX Accessory VOX-35C Order No. 807	Ham Net \$ 29.95
Mobile Dashboard Mounting Bracket—GTM Order No. 809	Ham Net \$ 8.95
Floorboard Adaptor—ZSM (Not Shown) Order No. 810	Ham Net \$ 6.00


Get the complete Sound System...550 from Hy-Gain

## HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WF Lincoln, Nebraska 68505

**HALLETT**  
**ELIMINOISE**

Ignition Noise Suppression Kit

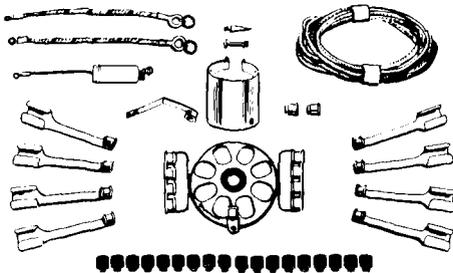


MODEL 80 - UNIVERSAL KIT FITS ALL 8 CYL. AMERICAN CARS

LIMITED

**SPECIAL \$24.95**

\$55.00 VALUE

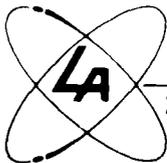

*Electronix Sales*

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4456 or (213) 534-4402

**ADD A LINEAR\* TO MY 2M FM RIG? WHY NOT?**

**YOU DID IT ON 80-40-20-15-& 10!**

**And you did it for a good reason!**

You wanted to put out a signal that others could hear — without noise, fade, fatigue, or interference.

A **DYCOMM BOOSTER\*** can do for you what it has for over 3,000 amateurs:

- Provide up to 50 times increase in power.
- Reduce the cost over a higher power rig.
- Is fully transistorized — no tubes to ever replace.
- Provide mobile rig with more variety — car-car, car-base plus more repeaters you can work through.
- Is fully guaranteed to perform with an outstanding warranty program.

**A model for virtually EVERY 2M rig!**

Model Line Up:


10-0	10 W input	100 W output	<b>\$195.00</b>
D	10 W input	40 W output	<b>99.95</b>
ES	1 W input	40 W output	<b>99.95</b>

**Write for a brochure or call your nearest amateur dealer — you hear!**

\*A common term for add-on amplifiers.

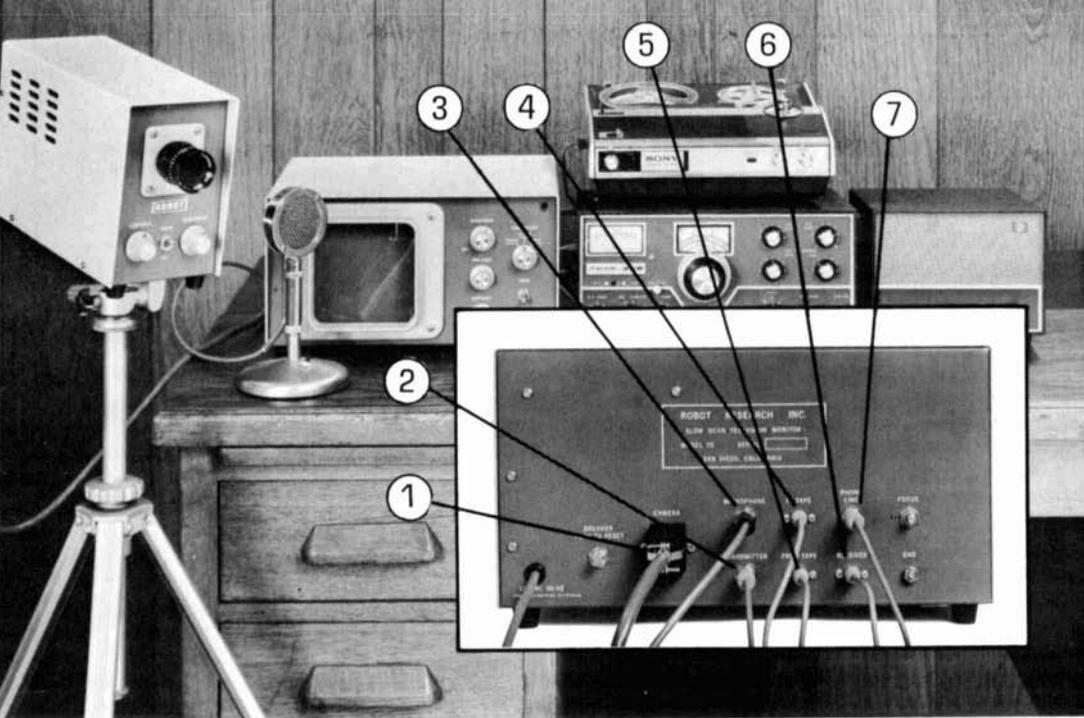**DYNAMIC COMMUNICATIONS, INC.**

948 AVENUE E, P. O. BOX 10116  
 RIVIERA BEACH, FLORIDA 33404  
 305-844-1323



## Convert your ham station to a complete SSTV station in 7 easy steps:

**Just add a Robot monitor and camera and follow these simple instructions:**

All popular ham radio sets may be used with the Robot SSTV equipment and absolutely no modification is required. Pictured above is a complete SSTV station. The inset photo shows the back of the Robot monitor, with all connecting cables. To convert your existing amateur station to an SSTV station:

Connect the cable supplied with the Robot Model 80 camera to the socket ① on the back of the Model 70 monitor. Power is then supplied to the camera from the monitor and the video image from your camera is displayed on the monitor.

Next, connect the transmitter connecting cable ② to the microphone jack on your transmitter or transceiver. Your microphone cable now connects to the microphone jack provided on the back of the Robot Monitor ③.

Phono jack ④ connects the signal from your camera or radio receiver to your tape recorder so that it may be recorded for later viewing or transmitting.

Phono jack ⑤ also connects to your tape recorder so SSTV signals previously recorded on audio tape may be displayed on the Robot monitor for viewing, or transmitted, whenever you wish.

SSTV signals coming from any radio receiver or transceiver are relayed to the Robot monitor for viewing and recording by means of

cable ⑥ which is connected to the receiver by means of a "Y" connector in the speaker lead.

SSTV signals are connected to the phone line ⑦ to provide two-way SSTV exchange with other Robot SSTV sets connected to the phone line.

After these connections are made, the station is operated by switches on the monitor front panel.

That's all there is to it. As you can see, absolutely no modifications of your existing equipment are required. All necessary cables are included with your Robot monitor and camera.

*For a demonstration of Robot SSTV equipment, contact your Robot dealer. Write us for complete information on Robot SSTV equipment, and the name of your nearest dealer.*

**ROBOT**

**ROBOT RESEARCH, INC.** 7591 CONVOY COURT, SAN DIEGO, CA 92111 (714) 279-9430

# MINI-MITTER II SSB!

**Portable Transceiver Kit  
Handheld! QRP!**



ALL TRANSISTOR SSB TRANSCEIVER KIT DESIGNED EXPRESSLY FOR THE HAM

- \* BIG TRANSCEIVER SOPHISTICATION \* ALL SOLID STATE \* EASY TO ASSEMBLE \* SIMPLE TO OPERATE \* POWERED BY 8 NI-CAD BATTERIES
- \* RUGGED ALL METAL CASE \* 3 3/8" W X 1 3/4" D X 10" H \* WEIGHS LESS THAN 1 LBS \* PRINTED CIRCUIT BOARD \* QUALITY COMPONENTS

SSB GEAR THAT GOES WITH YOU! Introducing the new, delightfully wild MINI-MITTER II KIT designed especially for the Ham. Get it together in a few enjoyable hours of creative fun. Carefully engineered using the latest techniques this fully transistorized-solid state transceiver features commercial grade components, diode switching, a Collins Mechanical Filter along with the easy to follow instructions for assembly. The transceiver is powered by 8 Ni-Cad Batteries easily accessible through a hinged door at the rear of the case for recharging. The printed circuit board chassis and the complement of Field Effect Transistors along with Integrated Circuits ensures the highest performance, yet simplifies the circuitry for easy assembly. The tune-up procedure requires no special test equipment since all of the tuned circuits are pre-tuned at the factory and need only minor adjustment. For final setting and performance checks a receiver is recommended.

RECEIVER: Crystal controlled on 40 meters, supplied with 7215 or 7255 (specify). Crystal Tuning Range: Approx. .01% of frequency. Audio Power Output: .2 watts nominal. Sensitivity: Less than 1 uv for 10 db S/N. Selectivity: 2.1 KHz at 6 db. TRANSMITTER: 4 watts P.E.P. Carrier Suppression: -40 db or better. Modulation Freq. Range: 350 to 2450 Hz. Antenna Impedance: 50 ohms resistive. GET WITH THE QRP FUN!!! ORDER TODAY!!!

- MINI-MITTER II KIT \$149.95  7215  7255.
- ACCESSORY ANTENNA \$ 7.95
- F.O.B. Mtn. View, Calif. 94040 Ca. tax 5%
- Batteries not included.
- Enclosed \$.....  BankAmericard.
- Acc't #.....  Master Charge.
- NAME.....
- ADDRESS.....
- CITY..... STATE.....

**AMERICAN STATES ELECTRONICS**

1074 WENTWORTH STREET MOUNTAIN VIEW CALIFORNIA 94040

**AT LAST --  
A SPEECH COMPRESSOR THAT  
REALLY WORKS!**




RPC-3M MODULE  
(ONLY \$22.50)

- LOW DISTORTION CIRCUIT
- FULLY WIRED & TESTED NOT A KIT
- WORKS WITH PHONE PATCH
- INTERNAL UNITS & MODULES WORK MOBILE
- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES (Illinois residents add 5% Sales Tax)

Write for specifications and information sheets (free)

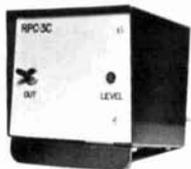Demonstration Tape (cassette) available (\$2.00 deposit)



RPC-3C CABINET MODEL  
(\$34.95)



RPC-3,3U INTERNAL UNIT  
(\$24.95)

**Rp Electronics**

BOX 1201H  
CHAMPAIGN, ILL.  
61820



Radio Amateurs  
Reference Library  
of Maps and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables . . . . . postpaid **\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. . . . . postpaid **\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries . . . postpaid **\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 3/4" x 12" . . . . . postpaid **\$2.00**

Complete reference library of maps — set of 4 as listed above . . . . . postpaid **\$3.50**

See your favorite dealer or order direct.

**WRITE FOR  
FREE  
BROCHURE!**

RADIO AMATEUR

**callbook INC.**



Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# for the EXPERIMENTER!

## INTERNATIONAL EX CRYSTAL & EX KITS

OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



### 1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50



### 2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50




### 3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....\$3.75


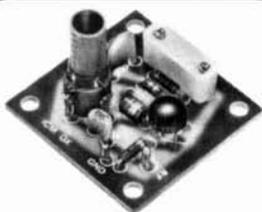
### 4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur .....\$3.75



### 5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....\$2.95



### 6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is  $\pm .02\%$  when operated in International OX circuit or its equivalent. (Specify frequency) .....\$3.95

## for the COMMERCIAL user...

### INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

**CRYSTAL TYPES:** (GP) for "General Purpose" applications  
(CS) for "Commercial Standard"  
(HA) for "High Accuracy" close temperature tolerance requirements.



## write for CATALOG



CRYSTAL MFG. CO., INC.  
10 N. LOE • OKLA. CITY, OKLA. 73102

# IRON POWDER TOROIDAL CORES

CORE SIZE	-41 Mix Green 'HR'	-3 Mix Gray 'HP'	-2 Mix Red 'E'	-6 Mix Yellow 'SF'	-10 Mix Black 'W'	-12 Mix Grn-Wh 'IRN-8'	Outer Diameter (inches)	Inner Diameter (inches)	Height (inches)
	20 kc - 100 kc $\mu=75$	50 kc - 1 mc $\mu=30$	500 kc - 30 mc $\mu=10$	10 mc - 90 mc $\mu=8$	30 mc - 150 mc $\mu=7$	60 mc - 200 mc $\mu=5$			
T-200	\$2.50	\$2.75	\$3.00	\$3.50			2.000	1.250	.550
T-130	1.50	1.75	2.00	2.50			1.300	.780	.437
T-106	.95	1.00	1.00	1.50			1.060	.560	.437
T-94	.70	.75	.75	.95			.942	.560	.312
T-80	.55	.60	.60	.80	.90		.795	.495	.250
T-68	.45	.50	.50	.65	.75		.690	.370	.190
T-50	.40	.45	.45	.50	.60	.65	.500	.303	.190
T-37	.30	.40	.40	.45	.45	.55	.370	.205	.128
T-25	.25	.30	.30	.35	.40	.45	.255	.120	.096
T-12	.25	.25	.25	.25	.25	.35	.125	.062	.050

**Sustained Availability**

**Postage 50 Cents**

**AMIDON**  
*Associates*

12033 OTSEGO STREET  
NORTH HOLLYWOOD, CALIF. 91607

FERRITE BEADS: .125" x .125",  $\mu = 900$ . With Spec Sheet & Application Notes Pkg of 12, \$2.00

KILOWATT TOROID BALUN KIT: Still only \$5.00

EXPERIMENTER'S 2 CORE TOROID KIT—This famous kit contains cores, wire, and charts so that you can make your own high Q modern inductors for hundreds of practical applications.:

\$1.50

## New 3 Digit Counter



The model fm-36 3-digit frequency meter has the same features that has made the 2 digit model so popular with Hams — low price, small size (smaller than a QSL card), 35 Mhz top frequency, simple connection to your transmitter, +0 -0.1 KHz readout — PLUS the added convenience of a third digit to provide a 6 digit capability. Kit or Assembled.

Example: 28,649,800 Hz reads 28.6 MHz or 49.8 KHz. (Add the 10 Hz module to read 9.80.)

FM-36 KIT \$134.50

NEW . . . . .

300 MHz PRESCALER only \$45.00  
with fm-36 order

**Micro-Z Co.**

Box 2426 Rolling Hills, Calif. 90274

## ALL SOLID-STATE SSB TRANSCEIVER



- Complete single-band SSB transceiver 4 to 5 watts PEP output 15, 20, 40 or 75 meters.
- VFO tuning 3750 to 4000 on 75, full coverage on 40, 20 and 15 meter amateur bands.
- Suitable for dry battery operation.
- Light weight, small size, makes excellent portable — boat, aircraft, field or mobile.
- Contains 15 transistors, 1 mosfet, 2 Darling-ton amps, 1 I.C. and 17 diodes. Four-pole filter.
- Available accessories, AC power supply, MIC, headsets, lightweight dipole and 40 watt PEP linear amplifier.
- Xtal controlled emergency and net transceiver available. Write for full information on transceivers and accessories.

**JUSTIN INC.**

2663 LEE STREET  
SOUTH EL MONTE, CALIF. 91733

## hobbyist LEDs


Priced for the amateur experimenter, premium-quality light-emitting diodes are now available through the national network of Sprague distributors. Each distributor will have a working display of many LEDs and a specially-selected inventory of LEDs and related gallium arsenide semiconductors including visible light sources, infra-red sources, indicator lamps, alpha-numeric readouts, photo-sensors and opto-isolators made by Monsanto.

Although intended primarily for the experimenter, the new line of LEDs are exact replacements for thousands of devices in standard equipment and for many conventional miniature lamps.

Sprague suggests numerous experimenter projects using the new devices stressing the low-current demands and exceptional long-life of the LEDs. Panel indicators, light communications and digital readouts are a few of the more conventional suggestions.

More information is available from Sprague Products Company, North Adams, Massachusetts 01247, or by using *check-off* on page 94.

## jewelry

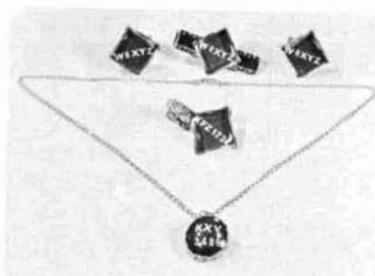

Hobby Jewelry offers a variety of earrings, tie clips, locket and cufflinks custom made with any call sign, initial or photograph. A variety of sizes and a choice of gold or silver finish is offered, with both finishes guaranteed for a year. More information and prices are available from Hobby Jewelry, 13407 Shoup Avenue, Hawthorne, California 90250 or by using *check-off* on page 94.

When you want  
an authoritative,  
up to date,  
complete,  
reference  
It's the **QTH**  
and  
**CALLBOOK**  
you know it

The U.S. and DX Editions lists licensed radio amateurs throughout the world plus many other valuable features including maps, charts & tables all designed to make your operating more efficient and more fun.

### PLUS

New this year!

A special subscription service of one basic CALLBOOK plus three service editions, one issued every three months to keep you completely up-to-date for less than half of the cost of purchasing four complete CALLBOOKS as before. You save money — you stay better informed.

Over 285,000 QTH's  
in the U.S. edition  
Complete for 1972 U.S.  
CALLBOOK subscription  
just **\$14.95**

U.S. CALLBOOK for 1972  
(less service editions)  
**\$8.95**



Over 180,000 QTH's  
in the DX edition  
Complete for 1972 DX  
CALLBOOK subscription  
just **\$11.45**

DX CALLBOOK for 1972  
(less service editions)  
**\$6.95**

See your  
favorite dealer  
or Send today to

(Mail orders add 25¢ per CALLBOOK  
for postage and handling)

WRITE FOR  
FREE  
BROCHURE



RADIO AMATEUR  
**callbook** INC.  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044


the  
Incomparable

**CX7A** by  **signal/one**

**Features:**

- **RELIABILITY IS NOW** standard equipment. Every CX7A "burnt-in" and cycled more than 48 hours.
- **QUALITY-PLUS.** Every component is instrument grade, American-made, and individually tested.
- **ALL MODES** 10 thru 160 meters in full 1 MHz bands with overlaps.
- **BROAD-BAND TUNING.** Instant band changes without tuning.
- **TRUE BREAK-IN CW** with T/R switching.
- **IF SHIFT** — deluxe QRM slicer.
- **PRE-IF NOISE-BLANKER** that really works.
- **RF ENVELOPE CLIPPING** — sounds like a Kw.
- **TWO VFO'S.** Transceiver Plus receiver.
- **BUILT-IN:** Spotter, FSK shift, transmit offset, wattmeter, SWR meter, electronic CW Keyer.

*It's Perfection  
for \$2195*

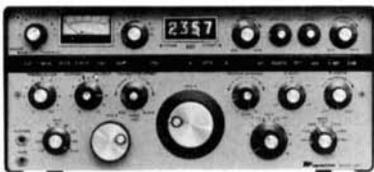

If you want to move up to the **BEST**, give **DON PAYNE, K4ID**, a call for personalized service, a brochure, and a **KING-SIZE** trade-in on any gear you have — one piece — or the whole station.

**PAYNE RADIO**

Box 525

Springfield, Tenn. 37172

Days  
(615) 384-5573

Nites - Sundays  
(615) 384-5643

**Specifications:**

**SENSITIVITY:** Better than 10db signal-plus-noise-to-noise ratio for .25 microvolts at 28MHZ.

**SELECTIVITY:** 2.4 KHz @ -6db 1.8:1 (6:60db) shape factor. (16 pole crystal lattice filters) optional: CW-400 and 250 HZ. FSK-1200 HZ.

**CARRIER** and unwanted sideband suppression: Minimum 60db.


**IMAGE** and **IF REJECTION:** more than 60db.

**POWER LEVEL:** 300 to 500 watts p.e.p. plus, continuous duty cycle.

**POWER AMPLIFIER:** 8072 final completely broadband driver and final. 150 watt continuous dissipation rating.

**STRUCTURAL GLASS  
GEM-QUAD\***

FOR 10, 15 AND 20 METERS

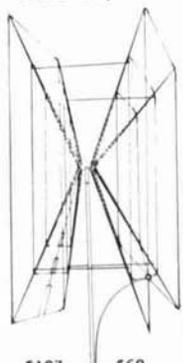

A two element fibre glass quad antenna designed for better signal discrimination & directivity on 10, 15 & 20 meters!

**NEW**

- Stronger Arms (closer wound).
- Strong alloy RF wire.
- Improved quality nylon straps.
- UV resistant.
- Low wind resistance (2.4 sq. ft.)

Send for literature

**STRUCTURAL  
GLASS LIMITED**

20 Burnett Ave., Winnipeg 16, Manitoba

\$107    \$60  
Two Element    Extra Element  
Quad  
Includes U.S. Customs  
Import Duty or Canadian  
Federal Sales Tax  
Shipped Collect  
Please include check or  
money order with your order.  
WORLD-WIDE DEALER  
INQUIRIES INVITED  
except U.S., Canada & Mexico

\*patented

**CRYSTAL BARGAINS**

Depend on . . .

We supply crystals from 16 KHz to 100 MHz in many types of holders. Over 6 million crystals in stock. We manufacture crystals for almost all model SCANNERS, MONITORS, 2-WAY RADIO, REPEATERS, ETC. Inquire about special quantity prices. Order direct with check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.

**JAN  
CRYSTALS**

DIVISION OF BOB  
WHAN & SON  
ELECTRONICS, INC.

2400 Crystal Dr.  
Fort Myers  
Florida 33901  
(813) 936-2397

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

**SPECIALS! CRYSTALS FOR:**

Frequency Standards	
100 KHz (HC13/U)	\$4.50
1000 KHz (HC6/U)	4.50
Almost All CB Sets, Trans. or Rec. (CB Synthesizer Crystal on request)	2.50
Any Amateur Band in FT-243 (Except 80 meters)	1.50
80 Meter Range in FT-243	4 for 5.00
Color TV 3579.545 KHz (wire leads)	2.50
	1.60
	4 for 5.00

# LOOK


The CRICKET is here — and it has the jump on all the others in its field!

This low cost keyer has more features for your dollar than all others in its price range. Even some in a higher price range! Go ahead — look around — compare the rest! Then buy the BEST — Data Engineering's new CRICKET I.

- Jam-proof spacing
- Self-completing dots and dashes
- Sidetone osc. and speaker
- Built-in key
- Relay keys 300 V at 1 amp
- Keyed time base. Instant start
- 3.5 to 50 w.p.m.
- "Full-control" weight ratio
- Speed, volume and tone controls
- Transmitter tune switch
- Auto/semi-auto. switch
- AC powered. Can also operate from 12V battery.

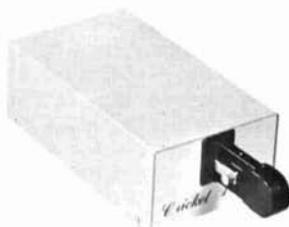**\$49.95**

Why don't you get the jump on all the others — too?



## AT LAST —

### A FREQUENCY STANDARD DESIGNED SPECIFICALLY FOR THE FM'ER!

Now, for the first time, you can be exact with your channel spacing and deviation.

This deluxe marker allows you to check your receive and transmit spacing for channels in the 10, 6, 2, and 1 3/4 meter FM bands. Markers are at 5, 10, 15, 20, 30, 40, 60 and 120 KHz. Precision 12 MHz crystal. Osc. and output buffered. No unwanted markers. Rich harmonics beyond 220 MHz.

**\$44.50** (Less batteries)



### MEMORY-MATIC 500 KEYSER

Today's newest and most advanced keyer. 500 bit/40 character Read-Write memory. Stores any message instantly. Near-Full and overload alarms. Includes all Space-Matic 21 features.

**\$198.50**



### FREQUENCY MARKER STANDARD

Markers at 5, 10, 25, 50, 100, 200 and 400 kHz. 400 kHz crystal. No unwanted markers. Latest low power ICs. Buffered osc. and output.

**\$32.95** (Less Batteries)



### SPACE-MATIC 21 KEYSER

Instant self-starting, self-completing dots, dashes, and associated dot, dash, character and word spacing. Adjustable weighting. 3.5-85 wpm. Built-in sidetone and speaker. Iambic. Dot and dash memories. Suitable for use with all standard keys.

**\$89.50**



### ELECTRONIC FEATHER TOUCH KEY

The solid-state design detects the mere touch of your finger and eliminates such problems as contact bounce, proper adjustments and dirty contacts. Operates with all keyers. Weighted.

**\$22.95, \$25.95** (with SPDT Switch Option)



5-year guarantees • PPD USA • Send for brochures



**DATA ENGINEERING INC.**

Box 1245 • Springfield, Va. 22151



## communication/navigation electronics MAGAZINE

This monthly technical magazine fills a "communication gap" within the electronic communication and navigation equipment industry. Its function is to provide comprehensive and authentic information not available in any other single publication. The types of feature articles include the following:

### SYSTEM DESIGN

The planning of radio communication and electronic navigation systems, as well as CCTV and electronic security systems.

### EQUIPMENT DESIGN

State-of-the-art design techniques—analysis of newly developed equipment.

### TECHNOLOGY

Reports on technical developments—looking into the future—measurement techniques.

### FCC REPORTS

Comprehensive reports on FCC petitions, proposed rulemaking and newly adopted rules changes—long before they are published in FCC Rules and Regulations.

### SERVICING

The latest techniques for maintaining equipment—troubleshooting—analysis and use of test equipment.

### INSTALLATION

Solutions to unique installation problems—local and national codes—interference and interface problems.

### APPLICATIONS

Utilization of system components—scope of equipment applications—interface requirements.

### CASE HISTORIES

Economic and operational aspects of unique systems—examples of how problems were solved.

Subscription rate \$12 per year, \$20 for two years. When Check or Money Order accompanies subscription request, special rate is \$10 for one year or \$16 for two years. Advertising rate card sent on request.

**COMMUNICATION AND NAVIGATION, INC.**  
250 PARK AVE., NEW YORK, NY 10017



**CAMP ALBERT BUTLER INVITES  
HAM RADIO ENTHUSIASTS OF ALL AGES  
TO TRY FOR YOUR  
GENERAL CLASS TICKET**

*This Summer! Our 13th Season*

**STUDY INSTRUCTION  
LEADING TO GENERAL ADVANCE  
and AMATEUR EXTRA LICENSE**

This co-ed Amateur Radio Camp, Y.M.C.A. owned and operated, can accommodate 60 campers. There is no age limit. We have had campers from 7 through 74 years of age. It is very helpful if you can copy 5wpm or have a Novice or Technician ticket but it is not necessary. Time is divided between radio classes in code and theory and usual camp activities, such as swimming, archery, riflery, hiking, etc. Golf privileges are included at the beautiful New River Country Club course.

Entire staff consists of licensed hams who are instructors in electrical engineering in some of our finest colleges and universities. Camp opens July 29th and closes August 12th. Tuition of \$200.00 includes all camp expenses: room, meals, notebooks, textbooks, and insurance. Send for our brochure.

**C. L. Peters, K4DNJ**  
General Secretary  
Gilvin Roth Y.M.C.A., Elkin, N. C. 28621

Please send me the Booklet and Application Blank for the Camp Albert Butler Radio Session.

NAME .....  
CALL .....  
ADDRESS .....  
CITY ..... STATE ..... ZIP .....

## FREQUENCY STANDARD



**Only  
\$32.50**  
(less batteries)  
POSTPAID USA

- Precision crystal
- Fully guaranteed
- Markers at 100, 50, 25, 10 or 5 kHz selected by front panel switch.
- Zero adjust sets to WWV. Exclusive circuit suppresses unwanted markers.
- Compact rugged design. Attractive, completely self contained.
- Send for free brochure.

**PALOMAR  
ENGINEERS**  
BOX 455, ESCONDIDO, CA 92025



## Is YOUR amateur station a serviced station?

When signal/one engineers set out to design the most advanced ham rig ever, they knew they were getting into trouble. Because they wanted to build a rig that incorporated every feature the serious amateur would want. They knew

that would take a lot of circuitry and a lot of innovation. With that comes bugs. And they had their share of them. We're not ashamed to tell you some of the earlier models literally went up in smoke. But . . . live and learn. We went back in and got the bugs out. What we've ended up with is the world's most sophisticated rig. And it works! Fantastically so. Ah . . . you're thinking that anything so complicated is someday going to need service. And we know that, too. That's why we maintain a factory-only service center. With fast turn-around time. And the job's always done right, with original factory replacement parts. You pay \$2,195 for the CX7A. It's worth it, as you'll discover when you see it at your signal/one dealer's. It serves every purpose an amateur could dream of. Including reliability. And service you can count on.

### FEATURES

1. Instant band change without tuneup.
2. Instantaneous digital frequency readout.
3. IF shift control.
4. Built-in pre-IF noise blander.
5. All popular modes of operation.
6. Transceiver-plus-receiver operation.
7. Hang AGC levels out wide swings in signal strength.
8. All ham bands from 160 through 10 meters.
9. RF envelope clipping provides matchless talk power.
10. Metering of all critical functions.

Write for information on the new Alpha PA-77A using the new Eimac 8877. Available soon at a tentative price of \$1,775.

Remember we will stock the Robot Model 70 Monitor at \$495 and the Robot Model 80 Camera at \$465 and the 25mm. f 1.9 lens at \$30.

A50-3, 6 meter 3 element beam	\$18.50
A26-9, 6&2 meter beam	\$29.95
A144-7, 2 meter 7 element beam	\$13.95
A144-11, 2 meter 11 element beam	\$17.95
A220-11, 1 1/4 meter 11 element beam	\$15.95
AR-2, 3/8 wave 2 meter vertical	\$12.50
DI-2, Diplomat 3/8 wave vertical	\$11.20
BBLT-144, 3/8 wave 2 meter mobile	\$34.70
2 meter magnetic mount antenna	\$9.95
TH-2 tribander, 2 element	\$99.95
TH3mk3 tribander, 3 element	\$144.95
18AVT/WB 5 band vertical	\$53.95
14AVQ/WB 4 band vertical	\$39.95
14RMQ roof mount for 14AVQ/WB	\$19.95
HAM "M" rotator	\$99.95
TR-44 rotator	\$63.95
AR-33 rotator	\$79.95
AR-20 rotator	\$29.95
8 wire cable for Ham "M"/TR-44	10¢/ft.
4 wire cable, 100 ft. coil	5¢/ft.
LAC-1 lightning arrester	\$3.95
LA-1 deluxe lightning arrester	\$24.95
HY-GAIN SP3T antenna switch	\$9.95
MOSLEY coax wall feed thru	\$1.15
RG-8A/U superflex foam	20¢/ft.
TIMES wire FM-8 foam	24¢/ft.
RG-59/U	7¢/ft.
RG-58/U	7¢/ft.
#12 enamelled wire, 100 ft.	5¢/ft.
4" open wire spreaders	20¢
DOW-KEY #72-220101 SP3T weatherproof antenna relay, 12 VDC. Shorts unused antenna terminals. Type "N" connectors	\$33.35

EGG insulators	25¢
HY-GAIN BN-86 balun	\$14.95
JOHNSON kilowatt matchbox	\$154.95
JOHNSON 250 watt matchbox	\$94.95
AN/SRA-15, 6-18 MHz multicoupler	\$99.95
DRAKE W-4 wattmeter	\$61.95
DRAKE 2NT demo	\$135.00
DRAKE TR-22, new	\$199.95
DRAKE ML-2, new	\$299.95
DRAKE SW4-A, demo	\$250.00
DRAKE 2-C, demo	\$195.00
DRAKE DC-3, good	\$65.00
SWAN 250C with 117XC	\$325.00
HEATH HW-101 transceiver	\$250.00
(NOTE: Mobile & base supplies avail.)	
HT-44 with PS-150-120	\$250.00
PEARCE-SIMPSON Gladding 25, new	\$249.95
DYCOMM 10-0 FM 100 watt amp	\$195.00
ROBOT slo scan TC camera, #80	\$465.00
ROBOT slo scan TV monitor, #70	\$495.00
ROBOT Macro lens, f 1.4	\$60.00
DX Engineering RF speech clipper	\$79.50
(NOTE: Specify 32S or KWM2 model)	
SB-144 2 meter FM transceiver	\$239.95
IC-21 24 channel FM transceiver	\$389.95
MILLEN 90672 antenna bridge	\$59.25

Come in and look around! Our hours are 9:00 till 5:30 weekdays and 10:00 till 2:00 on Saturday. We stock very large quantities of tubes. Write for a quote or else call us at (212) 925-7000. We are distributors for Eimac, Amperex, Cetron, Westinghouse, etc.

**BARRY** 512 Broadway NY, NY 10012  
212-WA-5-7000 **ELECTRONICS**

# ELECTRONIC SURPLUS BARGAINS



## KLEINSCHMIDT TELETYPWRITERS

Model TT-100. Capable of sending 60-100 WPM., 115 v, 60 cyc. Self contained pwr. supply. Shipping wt. 70 lbs. ....\$59.50 ea.  
 Model TT-483 - Same as above.  
 UNUSED .....\$150.00 ea.



## REPERFORATOR-TRANSMITTER


Model TT-179/FG Mfg by Kleinschmidt  
 Tape printing & punching, also transmitter-distributor. 115 volts, 60 cyc, shpg. wt. 90 lbs. Used, excellent cond., (gov't. cost \$2,000). ....\$59.50
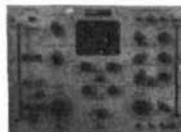
## TELETYPWRITER TABLES

Heavy duty construction, shpg. wt. 20 lbs. for page printer, 22" x 18" x 27" ht. ....\$15.95



2-METER-VHF  
 BC-640 X-MITTER  
 50 watt - CW and AM.  
 Freq. range 100-156  
 MC crystal controlled  
 Pwr. reqmt. 100/125 60  
 cyc. Crated wt. 600  
 lbs. 6' x 22" wide.  
 \$49.50



AN/USM-50 OSCILLOSCOPE \$79.00

A wide-range, high gain, portable test unit for observation of pulses, short-period electrical disturbances, sine waves. Band width 3 cyc-15 mc. 105/125 VAC. 50-1000 cyc.

## AUDIO OSCILLATOR

TS-382-C - 20CPS to 200KC  
 Var. 0-10volts - power 110v, 60cyc  
 17" x 10" x 11"  
 Shp. Wt. 45 lbs.  
 Used, good condition - \$65.00



**ANDY ELECTRONICS**

(DIV. OF ANDY INTERNATIONAL, INC.)

6427 Springer Houston, Texas 77017  
 713-645-7057 Richard Hall — W5ZJG

F.O.B. Houston, Tex. — Payment with order

# GATEWAY ELECTRONICS

8123 PAGE AVENUE  
 ST. LOUIS, MISSOURI 63130  
 314-427-6116

455 KC MECHANICAL FILTER IF ASSEMBLY — IF Chassis from R-390A receiver. Contains 4 mechanical filters, BFO, etc. Complete with tubes and schematic. Ship. wt. 7 lbs. \$65.00

PUSH TO TALK TELEPHONE HANDSET — 6 wire coil cord-mike, earphone, and switch separately wired — modern G type handset — new. Ship. wt. 2 lbs. \$12.50

MUFFIN FANS — 115 VAC. Ship. Wt. 1 lb. \$7.50

THUMBWHEEL SWITCHES — Min. size 0.312x 1.3x1.3. 10 pos. decimal — \$2.00, 10 pos. BCD & compliment — \$2.75 — end plates \$.50 pr. Standard Size — 0.5x2.125x1.78 — 10 pos. decimal — \$2.75, 10 pos. BCD & compliment \$3.75 — end plates 1.00 pr. Ship. wt. ¼ lb.

Minimum order \$5.00. Stop in and see us when you're in St. Louis.

## NEW CT-1 From

Will allow you to Dynamically test all types of capacitors.



The Model CT-1 features a built-in electronic power supply providing BOTH AC and DC Test Voltages in a special circuit with highly sensitive NEON type leakage indicator.

Only \$16.95 postpaid

Capacitor Range: .00025 — 1000 mfd.  
 Sensitivity: Over 200 MEGOHMS

30 DAY MONEY-BACK GUARANTEE  
**LEE ELECTRONIC LABS, INC.**



88 Evans St., Watertown, MA 02172

Dealer Inquiries Invited.

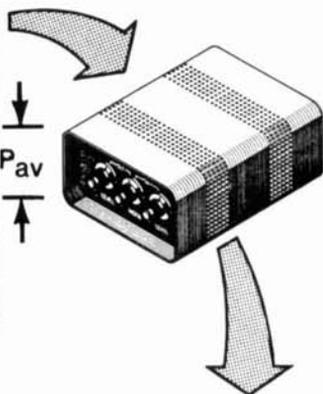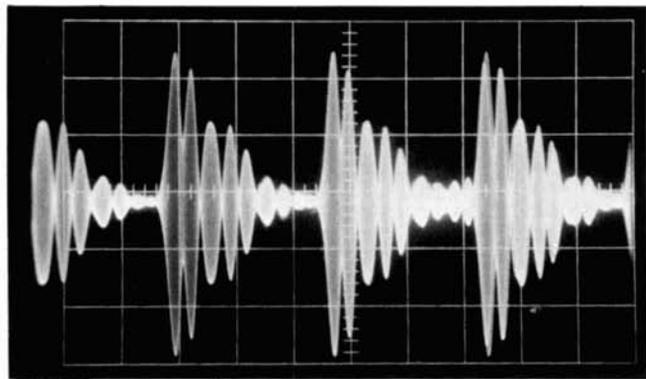
# MAGNUM SIX

RF SPEECH PROCESSOR FOR

COLLINS 'S' LINE & HEATH 'SB'/'HW'\* SERIES



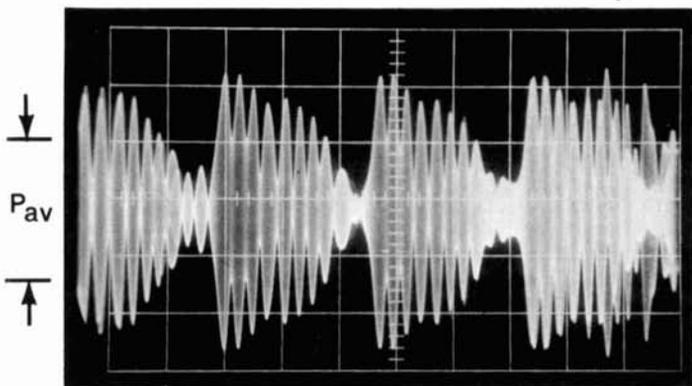↑  
KWM-2 SB100  
32S - 1 SB101  
32S - 3 SB102  
SB400  
SB401  
\*HW100  
\*HW101



INTRODUCTORY  
OFFER

🌀 \$129.95 🌀

Postpaid U.S.  
(Add 5% in Washington)

- TRUE RF SPEECH CLIPPING
- $\geq 6$ db AVERAGE POWER GAIN
- DUPLICATE O.E.M. CRYSTAL (HEATH) OR MECHANICAL (COLLINS) FILTER
- HIGHEST QUALITY SOLID STATE COMPONENTS
- REGULATED FAIL-SAFE POWER SUPPLY

Send for FREE Brochure  
Communication Technology Group  
(A Division of Bitcil Systems Inc.)  
31218 Pacific Highway South  
Federal Way, Washington 98002



# THE VANGUARD FREQUENCY SYNTHESIZER

**YOU'LL NEVER  
HAVE TO BUY  
CRYSTALS  
AGAIN**



**MODEL: ST-140**

**SIZE: 1 1/2" HIGH x 3 5/8" WIDE  
x 8" LONG**

**PRICE:**

**\$119.95 ppd.**

**NOTE: NY State residents add sales tax.**

- 1000 channels from one crystal (yes, that's one thousand) selectable every 10 KHz. from 140.00 to 149.99 MHz.
- Better than .0005% (5 parts per million) from -10° to +60°C down to -30°C with accessory heater available later.
- Thumbwheel switches with digital readout for fast selection.
- Uses a super precision crystal reference source operating at 5 MHz. for easy checking with WWV. RF output is obtained from a VCO tightly locked to the reference source in a digital phase-locked loop circuit.
- Present model is available with output in the 6, 12 or 18 MHz. band (corresponding to 144 MHz). for direct substitution of transmitting crystals. Built-in computer selects the appropriate frequency when you set the readout to the transmitter output you want.
- Changes frequency almost as fast as you can switch. Settling time is in milliseconds

even when switching from one band limit to the other. No hunting or false locks as with some other synthesizers.

- Operates from 10 to 15 VDC. Includes 3 precision IC voltage regulators (one for each major circuit function) to prevent interaction and to take care of those wide voltage swings in mobile installations. Can also be used on 110 volts AC with a small 12 volt 1/2 amp power supply.
- 50 ohm output for remote operation.

**COMING SOON:** A frequency synthesizer for 45 MHz. receive crystals, a combination transmit and receive synthesizer, a synthesizer with direct output in the 144 and 220 MHz. band, and a whole series of synthesizers to cover from sub-audio to microwave frequencies.

**IMPORTANT:** When ordering be sure to state if you want the 6, 12 or 18 MHz. output.

**VANGUARD LABS • 196-23 Jamaica Ave. • Hollis, N. Y. 11423**



## 2 METER FM GLADDING 25™

- Full 25 watts output
- Six channel capability  
Crystals supplied for 146.34/.94 and 146.94/.94
- Complete with mounting cradle and push to talk handset

### Special Package Deal

INCLUDING AC POWER SUPPLY

**Only \$275 - June Only**

**BOB'S DISCOUNT ELECTRONICS**

720 N. HUDSON, OKLAHOMA CITY, OK 73102  
405-232-1384

### KOJO AUDIO FILTERS FOR SSB AND CW

The KOJO audio filters can greatly improve reception on all receivers, even the most sophisticated receivers. Large amounts of high-frequency hiss, background noise and sideband buckshot can be removed.

The SSB filter is of a low pass configuration, designed with a sharp cutoff to provide a rejection of better than 30 decibels at all ham band frequencies above approximately 3500 Hz. The filter is specifically designed to be placed in a low-impedance line for earphones or speaker.

The CW filter has a spot frequency of 780 Hz and a passband of 1100 Hz with a reference level, 40 decibels below the signal level at the design frequency. The peak of the passband is 100 Hz wide at the -3 decibel reference points. The CW filter is specifically designed for low-impedance input and high-impedance output. High-impedance crystal earphones are recommended. However, with low impedance earphones a small auxiliary amplifier or impedance matching transformer may be used.

KOJO filters are made up of top grade coils and components and are available in easy to assemble kit form with simplified instructions, or in a deluxe model. The deluxe model is completely built up and ready for use and is enclosed in a Gray cabinet® with convenient IN-OUT switch.

Try a KOJO and see what you can hear now and could not clearly hear before.  
\*Slight cabinet layout changes subject to take place without notice.

**CW Filter Kit \$ 8.95     Deluxe CW Filter \$16.95**  
**SSB Filter Kit \$12.95     Deluxe SSB Filter \$21.95**

All filters shipped postpaid. Arizona residents add 4% sales tax.

**THE J. LYNCH CO.**  
P. O. Box 7774, Phoenix, Arizona 85011



## Plug yourself into a bargain

You don't plug the Yaesu FTdx 570 into a power supply, you plug it into the wall. The 570 is ready-to-go, with 560 watts of PEP SSB and 500 watts of CW power built-in.

In a rig selling for \$549.95.

And power isn't the only reason why the FTdx is the world's best transceiver value. For a nickel less than \$550 you get a whole lot more. Like a built-in noise blanker. VOX. Calibrators. A built-in speaker and cooling fan. WWV channel. And 80 to 10 meter coverage on transmit and receive.


You get a rock-stable VFO, and a receiver so sensitive it hears things

clearly other rigs don't hear at all. Plus a lot of other features detailed in our brochure. Features that would cost you a fortune if you could find them all in any other rig.

For a little more than the \$549.95 price tag, you can order the 570 with a CW filter.

Send us the coupon and we'll send you a brochure on the FTdx 570.

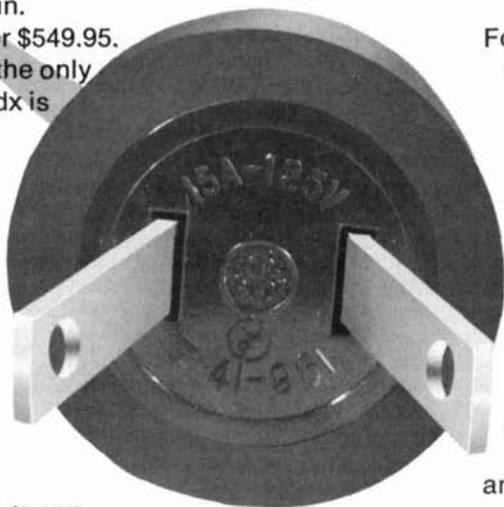Include a check for \$549.95 and we'll send you the real thing. Do that, and you'll be plugged in to amateur radio operation at its finest.



### SPECTRONICS WEST

Dept. Q, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

### SPECTRONICS EAST

Dept. Q, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send detailed information on all Yaesu products.

Enclosed find \$ \_\_\_\_\_

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All prices F.O.B. Signal Hill, Ca.

Master Charge and BankAmericard accepted. "H1"

CW or RTTY, whichever way you go,  
**HAL HAS TOP QUALITY  
 YOU CAN AFFORD!**



**TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU.** Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).\*



**TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER.** Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.\*

**OTHER HAL PRODUCTS INCLUDE:**

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00\*
- ID-1 (completely assembled in 1½" rack cabinet) . . . \$115.00\*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00\*
- W3FFG SSTV Converter Kit . . . \$ 55.00\*
- Mainline ST-5 TU Kit . . . \$ 50.00\*
- Mainline AK-1 AFSK Kit . . . \$ 27.50\*
- HAL RT-1 TU/AFSK Kit . . . \$ 51.50\*



**TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.**

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00; in kit form, \$175.00.\*



**NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT.** Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. Complete, \$495.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.\*

**TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD.** Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. Optional automatic ID available. RKB-1 assembled, only \$275.00; in kit form, only \$175.00.\*




HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products available.

\*Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

**HAL COMMUNICATIONS CORP.,** Box 365 H, Urbana, Illinois 618

# flea market

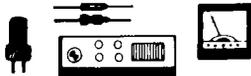

■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be type-written or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**WANTED:** Ham Radio magazines — March, April, November 1970, March 1971. WN8LZP, 8255 Memphis Ave. #2, Brooklyn, Ohio 44144.

**MECHANICAL FILTERS:** 455Khz. 2.1 Khz \$18.95 300Hz \$22.95. J. A. Fredricks, 314 South 13th Avenue, Yakima, Washington 98202.

**AMATEUR SALES & SERVICE.** Discount prices and service after the sale. Such leading names as Clegg, Kenwood, Pearce Simpson, Regency, SBE, Signal/One, and Tempo One. Write or call today. Amateur Sales and Service, 111 Rand Mill Road, Garner, North Carolina 27529. Tel. 1-919-772-6044.

**SWAPFEST,** June 25, Egyptian Radio Club, Granite City, Ill., 1 mile Southwest intersection 3 — Interstate 270. Food available. 146.76 talk-in. W9YIY, William F. Guennevic, 318 Hickory, Troy, IL 62294.

**SPECTRUM ANALYZER,** TS-1379A, newest Navy type, transistorized, 2-30mhz, bandwidth 150hz-30khz, 5 inch CRT, \$400. Two tone AF oscillator, SG-376, \$175. TS-1379A and SG-396, \$475. SG-24/TRM-3, AM-FM signal Generator, 15-400mhz, \$240. Bird 673 wattmeter, to 2.5 kw in three ranges, \$140. AN/URQ-9 primary frequency standard, .1, 1, and 5mhz output, Stability, one part in ten to the ninth power per day, \$250. All in excellent condition. Much more, flyer available. James Walter, 2697 Nickel St., San Pablo, Ca. 94806.

**ASK HARRY FIRST.** Good trades accepted. S.A.S.E. Name literature wanted. Harry's Amateur Radio Supply, 3528 Gaskin Rd. (Belgium) Baldwinville, NY 13027. 10AM-9PM. Closed Sunday. 315-635-7452.

**TONE ENCODERS AND DECODERS** — New line of solid state encoders and decoders compatible with any sub-audible continuous tone system. Small in size, usable from 67-250 Hz, \$8.95 to \$14.95. Send for literature. Communications Specialists, Box 153, Brea, Calif. 92621.

**READOUT TUBES** — 7 Segment, 5 Volt Incandescent \$3.00. Polarizing filters. SASE complete list. Display Electronics, Box 1044, Littleton, Colo. 80120.

**FIGHT TVI** with the RSO Low Pass Filter — p115 March 73 — write for brochure — Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada.

**CLEANING OUT SHACK,** miscellaneous components and 6C21 triodes. Send for list. Clyde Peters, WA7OTN, 185 East 550 No., Bountiful, Utah 84010.

**SAVE MONEY** on parts and transmitting-receiving tubes. Foreign-Domestic. Send 25¢ for giant catalog. Refunded first order. United Radio Company, 56-HR Ferry Street, Newark, N.J. 07105.

**AUDIO FILTERS:** Knock down that background noise. KOJO SSB, AM and CW filters do the job. Write for free brochure and see how serious DX boys hear them. KOJO, Box 7774, 741 E. Highland Ave., Phoenix, Arizona 85011.

**FOR SALE:** Delco car radios, 12 volts, transistor. Speaker, knobs included. New \$14.50 postpaid. W5RSN, 1826 Cypress, Irving, Texas 75061.

**WANTED:** tubes, transistors, equipment what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

**COPY MORSE CODE** automatically, (Ham Radio November 1971) detailed construction plans \$14.95. VMG Electronics, 2138 West Sunnyside, Phoenix, Arizona 85029.

**ALUMINUM MAST SECTIONS:** 9 1/2" x 3" o.d., 20 lbs. ea. Extremely strong and rigid. Use as mast, boom, lamp/fence-post. \$5.75 ea. Model 14 reperf, \$15. Aircraft emergency horn (loud!), \$32. 28LPR (typing reperf), unused, in original sealed carton, \$75. Unused, unboxed: 4CX250K, \$19; 4CX300A, \$19; RCA 4500 vidicon (SSTV), \$480 catalog, \$65; 3BG1P, \$22. B&W 850A, \$35. IBM Standard electric typewriter, \$135. K3MNJ, 8361 Langdon St., Phila., Pa. 19152.

**EARLY VACATION?** Then tear up that ticket to Tahiti. There'll be more fun at the ARRL Hudson Division Convention, October 21-22, Hilton Motor Inn, Tarrytown, N. Y. Exhibits, Lectures, 2-Meter FM, RTTY, Contests, Gabfests, New York Sight-seeing, Fun! No charge for a suntan. Info: Dave Popkin, WA2CCF, 303 Tenafly Road, Englewood, N. J. 07631.

**2W. AUDIO AMPLIFIER I.C.** short-proof ideal for monitors, intercomms, headphone applications, etc. Module \$4.75, I.C. \$2.85. Low noise dual preamp I.C. \$3.55. 5V/1A regulator I.C. \$2.95. Digital Clock/Counter power supply \$12.95. Phone Patch module \$21.95. Hundreds of I.C.'s and modules in Giant Catalog and Applications Guide. 25¢. Movevox Enterprises, Dept. 11S, P. O. Box 40073, Indianapolis, Indiana 46260.

**YAESU Ftdx 560** with speaker and CW filter \$400. Electrovoice 619 microphone \$20. Heathkit SB-610 monitor scope \$45. Heathkit HD-10 keyer \$30. Hustler 4BTV vertical \$25. All perfect. Doug Henry, WA7OHD/6, 292 N. Main St., Orange, Ca. 92668.

**SWAN 270 AC/DC** with mike. Excellent condition \$300. Ray Conway, W6WNA, 1012 No. 6th St, Burbank, Calif. 91504.

**"DON AND BOB" GUARANTEED BUYS.** Motorola HEP170 epoxy diode 2.5A/1000PIV 39¢; Ham-M 99.00; TR44 59.95; AR22R 31.95; MOT MC1709CG OP amp 50¢; Mosley CL33 114.00; CL36 134.00; TA33 105.00; CAP: Sangamo DCM600MFD/450V 4.95; SBE144 2MFM 199.95; Gladding 25, AC 255.00; Hy-Gain TH6DXX 139.00; Hy-Qud 99.00; 400 rotor 148.00; Airdux 2408T coil 5.00; Collins 75A4(clean) 345.00; #14 antenna wire 1.95/C write quote note Drake, Robot, Rohn. Tempo Kenwood dealer. Prices collect. Mastercharge, BAC. Warranty guaranteed. Madison Electronics, 1508 McKinney, Houston, Texas 77002. (713) 224-2668.

**TELL YOUR FRIENDS** about Ham Radio Magazine.

**LOWEST PRICES ON BRAND NEW FULLY TESTED & GUARANTEED IC'S**  
**BEST SERVICE: 10% DISCOUNT ON ALL ITEMS NOT SHIPPED IN 24 HOURS**  
**MOST CONVENIENT: ORDER DESK 1-800-325-2595 (TOLL FREE)**

PLEASE NOTE: To qualify for prices in the last three columns, you must order in EXACT Multiples of 10 per item for all IC items on your order.

Catalog Number	ANY QUANTITY PER ITEM(MIN)			MULTIPLES OF 10 PER ITEM(MIN)			Catalog Number	ANY QUANTITY PER ITEM(MIN)			MULTIPLES OF 10 PER ITEM(MIN)		
	1-99	100-999	1000-10000	999	9990	up		1-99	100-999	1000-10000	999	9990	up
7400	.26	.25	.23	.22	.21	.20	74122	-.70	.67	.63	.60	.56	.53
7401	.26	.25	.23	.22	.21	.20	74123	1.21	1.06	1.00	.94	.89	.83
7402	.26	.25	.23	.22	.21	.20	74141	1.63	1.55	1.46	1.38	1.29	1.20
7403	.26	.25	.23	.22	.21	.20	74145	1.41	1.33	1.26	1.18	1.11	1.04
7404	.28	.27	.25	.24	.22	.21	74150	1.63	1.55	1.46	1.38	1.29	1.20
7405	.28	.27	.25	.24	.22	.21	74151	1.20	1.13	1.07	1.01	.95	.88
7406	.52	.50	.47	.44	.42	.39	74153	1.63	1.55	1.46	1.38	1.29	1.20
7407	.52	.50	.47	.44	.42	.39	74154	2.43	2.30	2.16	2.03	1.89	1.08
7408	.32	.30	.29	.27	.26	.24	74155	1.46	1.39	1.31	1.23	1.16	1.08
7409	.32	.30	.29	.27	.26	.24	74156	1.46	1.39	1.31	1.23	1.16	1.08
7410	.26	.25	.23	.22	.21	.20	74157	1.56	1.48	1.39	1.31	1.23	1.15
7411	.28	.27	.25	.24	.22	.21	74158	1.56	1.48	1.39	1.31	1.23	1.15
7413	.58	.55	.52	.49	.46	.42	74160	1.89	1.79	1.68	1.58	1.47	1.37
7416	.52	.50	.47	.44	.42	.39	74161	1.89	1.79	1.68	1.58	1.47	1.37
7417	.52	.50	.47	.44	.42	.39	74162	1.89	1.79	1.68	1.58	1.47	1.37
7420	.26	.25	.23	.22	.21	.20	74263	1.89	1.79	1.68	1.58	1.47	1.37
7421	.26	.25	.23	.22	.21	.20	74180	1.20	1.13	1.07	1.01	.95	.88
7426	.34	.32	.31	.29	.27	.26	74181	5.20	4.90	4.59	4.26	3.98	3.47
7430	.26	.25	.23	.22	.21	.20	74182	1.20	1.13	1.07	1.01	.95	.88
7437	.56	.53	.50	.48	.45	.42	74192	1.98	1.87	1.76	1.65	1.54	1.43
7438	.56	.53	.50	.48	.45	.42	74193	1.98	1.87	1.76	1.65	1.54	1.43
7441	1.73	1.64	1.55	1.46	1.37	1.27	74198	2.81	2.65	2.50	2.34	2.18	2.03
7442	1.27	1.21	1.14	1.07	1.01	.94							
7443	1.27	1.21	1.14	1.07	1.01	.94							
7444	1.27	1.21	1.14	1.07	1.01	.94	HE501	2.99	2.82	2.66	2.49	2.32	2.16
7445	1.71	1.62	1.53	1.44	1.35	1.26	HE531	3.81	3.58	3.36	3.14	2.91	2.69
7446	1.24	1.17	1.11	1.04	.98	.91	HE533	3.81	3.58	3.36	3.14	2.91	2.69
7447	1.15	1.10	1.04	.98	.92	.85	HE535	7.31	6.88	6.45	6.02	5.59	5.16
7448	1.44	1.37	1.29	1.22	1.14	1.06	HE540	2.16	2.04	1.92	1.80	1.68	1.56
7450	.26	.25	.23	.22	.21	.20	HE550	1.24	1.17	1.11	1.04	.98	.91
7451	.26	.25	.23	.22	.21	.20	HE560	3.57	3.36	3.15	2.94	2.73	2.52
7453	.26	.25	.23	.22	.21	.20	HE561	3.57	3.36	3.15	2.94	2.73	2.52
7454	.26	.25	.23	.22	.21	.20	HE562	3.57	3.36	3.15	2.94	2.73	2.52
7460	.26	.25	.23	.22	.21	.20	HE565	3.57	3.36	3.15	2.94	2.73	2.52
7470	.42	.40	.38	.36	.34	.32	HE566	3.57	3.36	3.15	2.94	2.73	2.52
7472	.88	.86	.84	.82	.80	.78	HE567	3.57	3.36	3.15	2.94	2.73	2.52
7473	.50	.48	.45	.43	.40	.38	HE511	.90	.86	.81	.77	.72	.68
7474	.50	.48	.45	.43	.40	.38	HE556	1.87	1.77	1.66	1.56	1.46	1.35
7475	.80	.76	.72	.68	.64	.60	HE558	.80	.76	.72	.68	.64	.60
7476	.56	.53	.50	.48	.45	.42	HE595	3.40	3.20	3.00	2.80	2.60	2.40
7480	.76	.72	.68	.65	.61	.57	HE596	1.87	1.77	1.66	1.56	1.46	1.35
7483	1.63	1.55	1.46	1.38	1.29	1.20	709	.42	.40	.38	.36	.34	.32
7486	.58	.55	.52	.49	.46	.44	711	.44	.42	.40	.37	.35	.33
7489	4.25	4.00	3.75	3.50	3.25	3.00							
7490	.80	.76	.72	.68	.64	.60	723	1.00	.95	.90	.85	.80	.75
7491	1.43	1.35	1.28	1.20	1.13	1.05	741	.44	.42	.40	.37	.35	.33
7492	.80	.76	.72	.68	.64	.60	748	.48	.46	.43	.41	.38	.36
7493	.80	.76	.72	.68	.64	.60							
7494	1.18	1.12	1.05	.99	.93	.87	1H770	.15	.14	.13	.12	.11	.10
7495	1.18	1.12	1.05	.99	.93	.87	1H751A	.10	.08	.06	.04	.02	.01
74100	1.52	1.44	1.36	1.28	1.20	1.12	1H914	.10	.09	.08	.07	.06	.05
74107	.52	.49	.47	.44	.42	.39	1H4002	.15	.14	.13	.12	.11	.10
74121	.56	.53	.50	.48	.45	.42	1H4154	.15	.14	.13	.12	.11	.10
							2N3860	.25	.23	.21	.19	.17	.15

All IC's are supplied in 8-, 14-, 16-, or 24-pin DIP (Dual-in-line) plastic package, except for HE536, HE537, HE540, and HE540 which come in TO-5 package. We give FREE data sheets upon request, so ask for those data sheets that you NEED, even for those listed IC's you are not buying. On orders over \$25.00 we'll send you a new 270-page COMPLETE TTL IC data book FREE. Or, you may obtain a new 240-page LINEAR data book instead. Orders over \$50.00 will receive both books. Orders over \$100.00 will receive a complete LIBRARY of DIGITAL & LINEAR data & application books totaling 1000s pages FREE. (EXCLUDE HOSTS) Data books are shipped separate from your order. Please allow two weeks for delivery.

**UNIVERSAL DECADE COUNTING UNITS**

1. Easy to read single plane LED or Filament-type Readout with wide angle viewing.
2. BCD Outputs available
3. Readout Lamp Test
4. Selectable Ripple Blanking
5. Selectable Decimal Point
6. Counter Reset
7. Plug-in Module
8. Molex Sockets for all IC's & Readout
9. Tin-Plated G-10, 2-oz Copper, Glass Epoxy Board
10. Your choice of 1 to 6 decades on one P.C. board.
11. Grouping up to 2 or more readouts on the same card, for custom designed appearance.
12. 5-Volt TTL compatible single supply.
13. First in a series of universal plug-in modules to be introduced soon! for frequency counting, time measurements, event counting, DMM, magnitude comparison, etc.
14. Well documented application note with step-by-step assembly and hook-up instructions.

Price (Per Decade):

Basic Unit consisting of 7490, 7447, Filament-type 7-segment Readout...\$8.00

Options:  
 For LED Readouts instead of Filament-type add \$2.00  
 For 7475 latch add...\$1.25  
 For 74176 instead of 7490 add.....\$0.50  
 For 74192 instead of 7490 add.....\$1.00  
 For 74196 instead of 7490 add.....\$0.75  
 For Fully assembled and tested unit add.....\$2.50

**LED 7-SEGMENT DISPLAY \$4.95 Each**

50-99 \$4.75  
 100-999 \$4.50  
 1000-up \$4.25

Large 7-segment LED readout similar to the popular MAN-1 but with improved brightness. Has left-hand decimal point. Fits in a DIP socket. Expected life: Over 100 Yrs. Regularly \$12.95 in single lots. These are BRAND NEW with full data sheet and 4-page MULTIPLEXING Application Note. Needs a 7447 for driver and ONE CURRENT-LIMITING RESISTOR PER SEGMENT. We can supply you with one or ten thousand FROM STOCK. Also available, 11 OVERFLOW digit at the same prices. Mixing of Regular & Overflow digit allowed.

Package of 9, 470, & W limiting R's.....10C

Incandescent Type of 7-segment display. With right-hand decimal point. Rated 8mA per segment at TTL supply of 5V. Design life of 50,000 hours. Needs a 7447 as a driver. In DIP Package. Each \$3.25

MOLEX IC SOCKET PINS: Use these economical pins instead of soldering your IC's to PC boards. Sold in continuous strips in multiples of 100 pins only.  
 100 for \$1.00; 200 for \$1.80; 300 for \$2.60  
 400 for \$3.40; 500 for \$4.20; 600 for \$5.00  
 700 for \$5.80; 800 for \$6.60; 900 for \$7.40  
 1000 for \$8.20. Each additional 1000 \$7.50

ALLEN-BRADLEY MIL-GRADE (5-BAND) RESISTORS. Any of the 84 STANDARD 10% values from 2.70 to 22MΩ. 1/4 or 1/2 WATT. EACH.....5C

CERAMIC DISC CAPACITORS. Type 5CA-1000MVDC. 5, 7.5, 10, 12, 15, 20, 22, 25, 27, 30, 33, 39, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220, 250, 270, 300, 330, 360, 390, 470, 500, 560, 680, 820, 1000, 1200, 1500, 1800, 2000, 2200, 2500, 2700, 3000, 3300, 3900, 4700, 5000μF. EACH.....10C  
 0.01μF. EACH.....11C 0.02μF. EACH.....12C

LOW VOLTAGE DISCS, Type UK.  
 0.1 μF, 3V.....25C 2.2 μF, 3V.....30C  
 1.0 μF, 10V.....12C 0.2 μF, 10V.....20C  
 0.47μF, 3V.....25C 0.01μF, 16V.....10C

ELECTROLYTIC CAPACITORS: All values are available in both, axial or upright (PC board) mount. PLEASE INDICATE YOUR CHOICE.  
 100 μF, 15V.....15C 100 μF, 25V.....25C  
 50 μF, 25V.....30C 1000 μF, 35V.....50C

VOLTAGE REGULATORS. Internally-set, overload and short-circuit proof regulators need no external components to set. With data sheet and application notes. TO-3 Package.  
 LM-315, 5V, 600mA.....\$2.85  
 LM-316, 12V, 500mA.....\$3.85  
 LM-337, 15V, 450mA.....\$4.05  
 LM-347 PC-Board Type HEAT SINK.....\$1.20

STANCOUR P-8180, 25.2 VCT, 1-Amp Transformer. Ideal for use with LM-series. EACH.....\$3.00

**SOLID STATE SYSTEMS, INC.**  
 P.O. BOX 773  
 COLUMBIA, MO. 65201  
 PHONE 314-443-3673  
 TWX 910-760-1453

TERMS: RATED FIRMS NET 30 DAYS. Others CHECK or MONEY ORDER with order. Add 35¢ to orders under \$5.00 for postage & handling. For UPS add 45¢ and for AIR MAIL add \$5¢ to your order. We pay the balance. If you are served by UPS in your area, we strongly recommend this service with its built-in \$100 insurance. COD orders are FOB Columbia with 85¢ COD fee additional. Canadian residents please add 50¢ for INSURANCE.

MISSOURI RESIDENTS: Please add 4% Sales Tax. WRITE OR CIRCLE READER SERVICE CARD FOR OUR CATALOG OF PARTS & SERVICES. IT'S FREE.

**NEED:** Data, Manuals, Schematics for: Weston Selective Analyser Model 665; Knight T-150A Trans; Electronics Design VOM Model 125AT. Evans, 803 Rosselle, Jacksonville, Florida 32204.

**100 WATT RF AMPLIFIER.** Model AKT-7 RF amplifier will run 100 watts input to an Ampere 5894. In like new condition, still in original military packing. Tunes 200 to 400 MHz as is, can be easily converted to 2 meter FM amplifier or used now as 220 MHz FM Amplifier. Recent issue (1962), only \$20.00 shipped prepaid. Enclose SASE for copy of schematic and 4 page list of other goodies. Richard Solomon, 19 Pierce Rd., Watertown, Mass. 02172.

**DISCOUNTS!** Standard, Sonar, Clegg, Robyn, Mosley, Cush Craft, Others. Also Marine Gear. Write stating needs. Arena Communications, Dept. H, 1169 N. Military Hwy., Norfolk, Va. 23502.

**COLLINS:** Service - Sales - Trades. The house that treats you like a V.I.P. WIGEY, 321 Eastfield Dr., Fairfield, Conn. 06430. 203-374-8117.

**IRISH GUESTHOUSE** holiday exchanged for your unwanted VHF, mobile, sideband gear. Plenty of leisure activities, sightseeing and fishing opportunities locally and throughout southern areas. Contact Des Walsh, E15CD, Ballyllynch Carrick-on-Suir, Ireland.

**FOR SALE:** Complete SSB Station HW-100, Amp, TA-33 ant. All accessories. SASE WABZND, Larry Woerdehoff, Rt. 1, Box 774, Buchanan, MI 49107.

**WARREN, OHIO ARA'S** Family Hamfest. Aug. 20. Giant fleamart, swimming, picnicking, all free. Displays, mobile checkin. Camping available. Yankee Lake, Rt. 7 near I-80. Details: QSL W8VTD.

**TOROIDS,** Iron powder "E", 80-10 meters. O.D. .500, Eight for \$1.00, O.D. .940, 4 for \$1.00, O.D. 2.310, \$1.50 each or 3/\$4.00. Have several other sizes. Include \$50 postage. Fred Barken, WA2BLE, 274 East Mt. Pleasant Ave., Livingston, NJ 07039.

**SURPLUS MILITARY RADIOS,** Electronics, Radar Parts, tons of material for the ham, free catalogue available. Sabre Industries, 1370 Sargent Avenue, Winnipeg 21, Manitoba, Canada.

**QSL'S — BROWNIE W3CJI —** 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

**FREE INFORMATION.** Get FCC license new, easy way. Academy of Communications Technology. HR-3, Box 389, Roswell, New Mexico 88201.

**SELL:** HEATH SB303, mint cond. Only 7 months old. Factory aligned \$300. 1 pay shipping. Frank C. Vesco, 112 5th Ave., Latrobe, Pa. 15650.

**QSL'S.** Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

**DIGITONE TONE CONTROL DEVICES**—New improved product line of reliable, reasonably priced, compact, solid-state, plug-in modules. Decoders, logic processors, auto-patch control, 12-button "pads", other associated devices. 12 or 24-VDC operation. Application Notes/Catalog. Write Digitone, Box 73, Bellbrook, Ohio 45305.

**VHF NOISE BLANKER** — See Westcom ad in Dec. '70 and Mar. '71 Ham Radio.

**TV & RADIO TUBES** 36¢. FREE CATALOG. Cornell, 4219 N. University, San Diego, California 92105.

**NEW ELECTRONIC PARTS.** Buy-Sell. Free Flyer. Large catalog \$1.00 deposit. Bigelow Electronics, Dept. HR, Bluffton, Ohio 45817.

**WANTED:** BC-946 or R-24/ARC-5 Receivers and parts. R. J. Ellis, 3613 Chalmers Ave., Huntsville, Alabama 35810.

**NU SIGMA ALPHA** International Amateur Radio Fraternity. Memberships available. Handsome Certificate, I.D. card, Newsletter, contests, nets, and more. Send for our free illustrated brochure. Box 310, Dept. R, Boston, Mass. 02101.

# INCREASE YOUR TALK POWER!

PROVEN ON-THE-AIR PERFORMANCE



MODEL ACA-1

\$49.95 KIT

ASSEMBLED

\$69.95

**MODEL ACA-1 AUDIO COMPRESSOR** features 45 DB compression range ■ Flat 20-20,000 Hz response ■ Extremely low distortion ■ Front panel compression meter and in/out switch ■ Accepts both high and low-impedance mikes ■ Easily installed in mike line ■ 110-volt a.c. or 12-volt d.c. operation ■ Only 5" W x 2 1/4" H x 4 1/2" D.

MODEL ACP-1

\$24.95 KIT

ASSEMBLED

\$34.95



**MODEL ACP-1 COMPRESSOR-PREAMP** has 30 DB compression range ■ Flat 20-20,000 Hz response and low distortion ■ Designed for high-impedance mikes ■ Easily installed in mike line ■ 9-volt battery operation ■ Only 4" W x 2 1/2" H x 3 1/2" D.

## IDEAL FOR TAPE RECORDERS!

Try one of these compressors as an automatic recording-level control. Used by recording studios, schools, and radio-tv stations. Great for p.a. systems, too!

3-CHANNEL WWV RECEIVER

(5, 10, and 15 MHz)

\$74.95 KIT

ASSEMBLED

\$99.95



0.25 microvolt sensitivity ■ Crystal controlled ■ 110-volt a.c. or 12-volt d.c. operation ■ Compact size only 4 1/2" W x 2 1/2" H x 5 1/2" D.

Send check or money order, plus \$1.50 for shipping anywhere in U.S.A. California residents add 5% sales tax.

DEALER INQUIRIES INVITED




CARINGELLA ELECTRONICS, INC.

P.O. Box 327 □ Upland, California 91786

Phone 714-985-1540

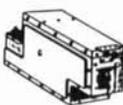**ARC-5 VHF RECEIVER, TRANSMITTER, MODULATOR 100-156 Mhz**

R-28 RECEIVER with tubes and crystal,  
Excellent Used..... **\$19.50**  
T-23 TRANSMITTER with tubes and crystals.  
Brand New in Original Carton... **\$23.50**  
MD-7 MODULATOR with tubes,  
Excellent Used ..... **\$10.50**  
Set of Plugs for MD-7..... \$ 8.50



**AN/ART-13 TRANSMITTER**

Makes fine Ham transmitter for 80, 40, 20 and 10 meters. Power output 100 watts on AM, CW, MCW. 10 preset channels. Complete with all tubes, crystal.  
Exc.Used...\$49.50 **LIKE NEW. \$59.50**  
Accessories Available: Prices Upon Request



**2" DC VOLTMETER**

Mounts in 2-1/8" hole. Flange diameter 2-5/8"  
Two scales: 0-15 and 0-600. Calibrated for use on steel panel. Standard brand. **SPECIAL NEW, boxed..... Each \$1.75 2 for \$3.00**



**BRAND NEW BC-645 TRANSCEIVER**

**EASILY CONVERTED FOR 420 MC. OPERATION**



**FOR FIXED OR MOBILE USE** BRAND NEW, complete with 15 tubes, less dynamotor and accessories, in original factory carton **\$16.95** **DEPENDABLE TWO WAY COMMUNICATION MORE THAN 15 MILES!**

FREQUENCY RANGE: About 435 to 500 Mc.  
TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7  
RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7  
RECEIVER I.F.: 40 Mc.  
SIZE: 10 1/2" x 13 1/2" x 4 1/2". Shpg Wt 25 lbs.

Superb quality components and circuitry, ideal for the technician experimenter. Many fabulous experiments, for example: you can construct a Yagi antenna for the 420 Mc band that will produce a gain of 10 db and yet fit on your operating desk!

**ACCESSORIES FOR BC-645**

- MOUNTING for BC-645 Transceiver.....\$1.50
- PE-10IC DYNAMOTOR, 12-24 Volts, (easily converted to 6 volts)..... 7.95
- MOUNTING for PE-10IC Dynamotor..... 1.00
- UHF ANTENNA ASSEMBLIES(set of 2), per set... 2.95
- COMPLETE SET OF 11 CONNECTORS..... 5.95
- CONTROL BOX BC-646..... 2.95
- MOUNTING for BC-646 Control Box..... 1.00

**SPECIAL "PACKAGE" OFFER:**

SPECIAL PACKAGE OFFER:  
BC-645 Transceiver, Dynamotor and all accessories above, COMPLETE, BRAND NEW, While Stocks Last....

**\$26.95**

**TC-34A CODE KEYS**, self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM Built-in speaker. Brand new with tech manual, takeup reel and AC line cord... **\$24.50**  
Code practice tapes for above P.U.R.



**BC-1206 C RECEIVER** Aircraft Beacon Receiver 200 to 400 Kc. Operates from 24V DC 1.5A. Continuous tuning, vol control, on-off switch and phone jack. Very sensitive. Compact. Complete with tubes, NEW..... **\$12.50**



**DUAL AMPLIFIER** has two input circuits each feeding a single 6SN7GT twin triode amplifier. Complete with 115V 60 cy. power supply using 6X5GT rectifier. NEW..... **\$5.95**



**BC-603 FM RECEIVER** Converted for 35-50 Mhz. 10 preset pushbutton channels or manual tuning. Complete with 10 tubes, checked out, like new **\$39.50**  
AC Power Supply, New.....\$14.95  
DM-34 12V Power Supply, New..... \$ 4.45  
DM-36 24V Power Supply, Exc.Used... \$ 2.25  
Technical Manual..... \$ 2.50  
Set of 10 tubes for BC-603 Receiver... \$ 5.95



**BC-604 FM TRANSMITTER** 20 to 27.9 Mc. Output approx 30 watts. 10 crystal controlled channels. Complete with tubes. NEW..... **\$12.50**



ARC-111A Modern Q-5 Receiver 190 - 550 KHz ..... **\$10.95**  
ARC-R22 540 - 1600 KHz Receiver with tuning graph ..... **\$15.95**  
R-4/ARR-2 Receiver 234-258 KHz, 11 tubes, NEW ..... **\$8.95**

BC-605 INTERPHONE AMPLIFIER, NEW \$3.45 EXC. USED.... **\$1.95**  
TELEPHONE HANDSET, W.E. type..... **LIKE NEW \$2.95**  
SCR-522 TRANSMITTER-RECEIVER, with 18 tubes, **LIKE NEW \$32.50**

**HANDMIKE**

Rugged, heavy-duty carbon hand mike with press-to-talk switch. Equipped with 4-ft cord & phone plug. **SPECIAL NEW, boxed..... Each \$1.88 2 for \$3.25**



**LM FREQUENCY METER**

Fine general purpose Navy unit 125 to 20,000 Hz. Operates on 12 or 24 VDC. Complete with tubes, crystal, calibration book. Checked out, Excellent Used .... **\$59.50**  
As above, less book ..... **\$22.50**



**CATHODE RAY TUBES - STANDARD MAKE**  
All New in Original Carton

- 3FP7\*.. .98 ea. | 3JP7\*.. 1.75 ea. | 7BP7 .. 3.25
  - 3CP1\*.. .98 ea. | 3AP1\*.. 1.95 ea. | 5MP1 .. 2.75
  - 5CP7A .. 4.25
- \* Sold in Lots of 3 only

**EE-8 SIGNAL CORPS FIELD PHONES**

Checked out, perfect working order. Complete with batteries.

Excellent Used ..... **\$16.95**



**APN-1 FM TRANSCEIVER** 400-450 Mc. Freq. modulated by moving coil transducer. Easily converted for radio control or 70 cms. Complete with 14 tubes, dyn. BRAND NEW..... **\$9.95**



BB-208/AMT BATTERY PACK contains three BB52 36V miniature lead acid type storage batteries and one BB51 6V battery..... **\$1.49**  
PE-219 BATTERY CHARGER charges one or two 6V batteries at 7 amps from 6/12 or 24V source. NEW..... **\$5.95**  
FL-30 Filter with PL-55 plug and JK-26 Jack, Exc.Used... **\$1.59**

**WILLARD 2-VOLT STORAGE BATTERY** Rated at 20 Amp.-Hours. Model 20-2. Rechargeable. Compact nonspill construction. Lightweight polystyrene container, 3x4x5 1/2". Shipped dry, uses standard electrolyte. Shipping Weight 3 lbs. NEW, each..... **\$2.79**



TERMS: F.O.B. NYC. 25% deposit with order, balance COD or remittance, in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change

**G&G RADIO ELECTRONICS COMPANY**

45-47 Warren St. (2nd Fl.) New York, N.Y. 10007 Ph. 212-267-4605

**A5 MAGAZINE:** The all new ATV publication covering all modes of ham TV. Subscription \$2.50 per year. Bi-monthly. P. O. Box 6512-B, Phila., Penna. 19138.

**MORSAVERTER READS HAND-SENT MORSE CODE** off the air and converts it to RTTY code. Connects to station receiver and Teletype. No speed adjustments required 5-40 WPM. Supplies CR, LF, LTRS, FIGS automatically. All on one 8x10 inch circuit board. Kits from \$185, wired and tested \$560. Write for information, Petit Logic Systems, 908 Washington, Wenatchee, Wash. 98801.

**WANTED:** Collins Mechanical Filter F250Z-5 and/or any other mechanical filter for the Lower Sideband with carrier freq. of 250Khz and 2.85Khz bandpass. Also, any mechanical filter for the Upper Sideband with carrier freq. of 300Khz. Philip Kellogg, P. O. Box 209, Beverly Hills, CA 94713.

**32S-3, 516F-2,** clean, mint, functioning perfectly. \$500. Call or write Tom Sessions, Jr., P. O. Box 278, Lexington, SC 29072. 803-359-4131 9AM-6PM EDT.

**IRCC PICNIC/HAMFEST!** Try it! You'll like it! July 9, Fairgrounds, Lafayette. Advance \$1.50, Gate \$2.00. Order: SASE to W9YIP, 477 Robinson, West Lafayette, Indiana 47906.

**VHF-UHF SSB STATION:** 100wts SSB on 432, 220, 144, 50 giving up everything; Drake line, equipment, antennas, much test gear, parts, tubes. S.A.S.E., WA1LNJ, D. Schier, 6 Tremont St., Cos Cob, Conn. 06807.

**YAESU FTdx 400 \$349, FL2000 \$199,** mint cond. New tubes. 213-472-2413. Box 1975, Beverly Hills, CA 90213

**WANTED** — Noise blanker for HQ-170. R. Brearley, 805 Wake, Arvida, P. Q.

**WE BUY ELECTRON TUBES,** diodes, transistors, integrated circuits, semiconductors. ASTRAL ELECTRONICS, 150 Miller Street, Elizabeth, N. J. 07207. (201) 354-2420.

**THE NINTH ANNUAL PENN-CENTRAL HAMFEST** will be held by the Milton and Williamsport clubs on Sunday, June 4th starting at 12:00 Noon at the Union Township Volunteer Fire Grounds on Route 15 in Winfield. Bring your own lunch or use the snack bar. Indoor and outdoor facilities. Auction, contest and swapping. Gate registration is \$2.50 — XYL and children free — Free parking. Talk in frequencies 3940, 50.4, 146-940 2 Meter FM. More information from Paul Mitch, W3LNX, RD #2, Milton, Pa. 17847. — Phone 717-742-8648.

**SWAP MANUFACTURERS DIRECTORIES,** Thomas Register 7 volumes, each 1,600 pages; McRaes 4 volumes; Conaver-Nast. Need Hammarlund Converters SP 10 or H10. Kennedy, 731 Greenwch St., New York 10014.

**TECH MANUALS** for Govt. surplus gear only \$6.50 each: R-388/URR, R-390/URR, R390A/URR, R-220/URR, R-274/FRR, URM-25D, TS-403/U, TS-418/U, URT-7, TS-479B/URR, OS-8C/U. Hundreds of others available. W3IHD, 4905 Roanne Dr., Washington, DC 20021.

**2 METER FM gear** for sale: Motorola L43 base on 146.58 \$135. Motorola T43 trunk mtg 2 freq tuned and xtals \$125. GE M36W trunk mtg 4 freq on 2M \$175. FDFM-2 10w on 2M transistorized 6 channels 12vdc w/AC power supply \$150. W7YHS 319 N. 26th St., Billingt, MT 59101.

**IT IS WITH PLEASURE** I can announce that WA5MPQ (Hernando, Miss.) and myself (W5BW) have started up the "PURPLE MARTIN NET" and would be happy to have bird lovers to check in at 4 PM CST every Sunday afternoon on 7.251 1/2 mhz. WA5MPQ is the Net Control and I will be the Alternate.

**MOVING, MUST SELL** Standard CUA64 free standing crankup TOWER with winched hinged base, custom powered crankup winch, rotor shelf \$400. Cliff-Dweller 40-75 \$60. SBE 34 \$80. Call 312-835-1045, Jack Weiss, WA9TBZ, 341 W. Elm Ct. Glencoe, Illinois 60022.

## USED TEST EQUIPMENT

All checked and operating unless otherwise noted, FOB Monroe. Money back (less shipping) if not satisfied.

GR736A-Wave analyzer 10Hz-16kHz .....	\$249
GR1100AP - Freq. Standard, includes 1101A osc., 1102A multivib., 1103A Synchronometer and PS complete .....	350
HP100D-Freq. stand. w/scope-Acc. 1ppm .....	165
HP150A - 10mHz Scope w/152B .....	295
HP160B(USM105)-14mHz dual trace scope .....	495
HP175A - 50mHz scope w/dual trace, delayed sweep plug-ins .....	795
HP185B-DC-1gHz samp. scope w/186B .....	625
HP525A-10-100mHz plug-in for above .....	65
HP540-B-Trans. Osc. for counter-to 12gHz .....	385
HP2590B-Precision Trans. osc-synchronizer 1165 Kintel 301-DC standard-null voltmeter .....	220
Meas. 80 - Standard Sig. Gen. 2-400mHz .....	225
NE 14-20C-Freq.counter (sim. HP524C) .....	209
NE 14-21C-10-100mHz plug-in for above .....	65
NE 14-22C-100-220mHz plug-in for above .....	80
Nems Clark 1671-FM rcvr, 175-260mHz .....	210
NLS M-24-Digital Volt-ratio-ohmmeter .....	585
NLS V-35 - Digital Voltmeter complete .....	385
Polarad R-microwave rcvr (plug-ins avail) .....	285
Polarad TSA-spectrum analyzer 10mHz-44gHz (plug-ins available) .....	325
Polarad SAB4W-spectrum analyzer, band switching 10mHz-41gHz .....	1260
Rollin 30-Stand.sig.gen.40-400mHz-hi-pwr. ....	585
Stoddart NM52A-RFI mtr, .375-1gHz, w/acc. ....	985
Tek B - 30mMz Hi-gain plug-in .....	40
Tek RM15-DC-15mHz GP scope .....	325
ME26D/U-(HP410B) VTVM-to 700mHz .....	85
TS-403A-Sig. Gen. (HP616) 1.8-4gHz .....	385
USM-16-Stand. Sig. Gen.10-440mHz AM-CW-FM-Pulse-Sweep, Phase-locked osc. ....	675

(Send SASE for complete list)

**GRAY Electronics**  
P. O. Box 941 Monroe, MI 48161  
Specializing in used test equipment

ONE COMPLETE SOURCE  
SPECIALIZING

**DALE**  
ELECTRONICS

**2 METER  
FM RIGS**

**TOP BRANDS**

AVAILABLE FOR  
**IMMEDIATE SHIPMENT**

- SONAR RADIO
- STANDARD COMMUNICATIONS
- DYCOMM
- GAM ANTENNAS
- HYGAN
- DRAKE
- CUSH CRAFT
- ANTENNA SPECIALTIES
- INTERNATIONAL CRYSTAL
- GALAXY
- BOMAR
- CRYSTEX
- LARSEN ANTENNAS
- SHURE COMM MIKES

**We stock crystals  
and parts for all sets we sell**

— Write for free literature —

**DALE ELECTRONICS CORP.**

244 West 14th St., New York, N.Y. 10011  
Free Parking 212-255-3660



# CRYSTAL FILTERS

By KVG of WEST GERMANY



High performance 9 and 10.7 MHz crystal filters for SSB, FM, AM and CW application. Symmetrical input and output. Small size (1 27/64" x 1 3/64" x 3/4") perfectly suited for miniaturized solid-state equipment.

Filter Type	XF-9A	XF-9B	XF-9C	XF-9D	XF-9E	XF-9M
Application	SSB-Transmit.	SSB	AM	AM	FM	CW
Number of Filter Crystals	5	8	8	8	8	4
Bandwidth (6dB down)	2.5 kHz	2.4 kHz	3.75 kHz	5.0 kHz	12.0 kHz	0.5 kHz
Passband Ripple	< 1 dB	< 2 dB	< 2 dB	< 2 dB	< 2 dB	< 1 dB
Insertion Loss	< 3 dB	< 3.5 dB	< 3.5 dB	< 3.5 dB	< 3 dB	< 5 dB
Input-Output	Z <sub>1</sub> 500 Ω	500 Ω	500 Ω	500 Ω	1200 Ω	500 Ω
Termination	C <sub>1</sub> 30 pF	30 pF	30 pF	30 pF	30 pF	30 pF
Shape Factor	(6:50 dB) 1.7	(6:60 dB) 1.8	(6:60 dB) 1.8	(6:60 dB) 1.8	(6:60 dB) 1.8	(6:40 dB) 2.5
		(6:80 dB) 2.2	(6:80 dB) 2.2	(6:80 dB) 2.2	(6:80 dB) 2.2	(6:60 dB) 4.4
Stop Band Attenuation	> 45 dB	> 100 dB	> 100 dB	> 100 dB	> 90 dB	> 90 dB
Price	\$23.12	\$32.85	\$35.40	\$35.40	\$35.40	\$24.49

HC-25/U crystals: 8998.5 kHz (USB), 8999.0 kHz (BFO), 9000.0 kHz (carrier) 9001.5 kHz (LSB). \$2.75 each.

10.7 MHz filters with bandwidth: 14 kHz, 16 kHz (for 5 kHz freq. dev. FM) \$30.25 each.  
 9 MHz crystal discriminators for max. freq. dev. of 1.5, 3 and 8 kHz. \$17.95 each.  
 10.7 MHz crystal discriminators for max. freq. dev. of 10 and 20 kHz. \$15.95 each.



**SPECTRUM INTERNATIONAL**  
 BOX 1084 CONCORD  
 MASSACHUSETTS 01742

## CQ de W2KUW

5% BONUS PAID FOR  
 EIMAC AND VARIAN TUBES

### ESPECIALLY:

4-65A, 4-125A, 4X150A, 4-250A,  
 4CX250B-K or R, 4-400A, 445A,  
 4-1000, 4CX1000, 4CX5000, X13,  
 etc.

### EQUIPMENT:

R390A, GRC 106-108, PRC 9, 10,  
 25, 74, 77, URC9, VRC 12, 618T  
 T/R, 490T load coils.

ALL COLLINS GEAR

**The TED DAMES Co.**

308 HICKORY ST., ARLINGTON, N. J. 07032  
 Phone: 201 998-4246

### BROADBAND AMPLIFIERS at a price you can afford

The BBA-1 series offers high gain over the HF to UHF region with low noise figures. BBA-1PA, a remotely powered unit for mounting near the antenna, covers 30 to 400 MHz with a 20±1dB gain dropping to 17 dB at 500 MHz. Maximum NF is 3.5dB. BBA-1PB has the same specs as the BBA-1PA but is locally powered. BBA-1P covers 3 to 500 MHz. with gain between 15 and 30dB. Maximum NF is 3.0dB. For less critical use order BBA-1 with same coverage as the BBA-1P, but reduced UHF gain and higher NF.



BBA-1PA - \$50.00; Adapter Kit, KT-1 - \$5.00  
 BBA-1PB, BBA-1P - \$45.00; BBA-1 - \$30.00

Please include \$1.00 for shipping.

**RADIATION DEVICES CO.**  
 P. O. Box 8450, Baltimore, Md. 21234

## FM Schematic Digest

A COLLECTION OF  
 MOTOROLA SCHEMATICS  
 Alignment, Crystal, and Technical Notes  
 covering 1947-1960

136 pages 11 1/2" x 17" ppd \$6.50

**S. Wolf**

P. O. Box 535

Lexington, Massachusetts 02173

**STOLEN, COLLINS 62S-1** Transverter #10728 from Michigan State Univ. Amateur Radio Club. Please call 517-355-2221 or your nearest State Police Headquarters.

**1972 EXPERIMENTAL AIRCRAFT ASSOCIATION CONVENTION**, Wittman Field, Oshkosh, Wis. July 30 thru August 6, 1972. All Flying Amateur Radio Operators are invited to attend. Will be monitoring 146.94 mh before, and all during the convention, as well as the Wis. SSB net. For a little something extra your QSL card dropped in a container at the Ham Headquarters may be a lucky one, and win you a piece of amateur gear as donated by Amateur Electronic Supply Co., 4828 W. Fond du Lac Ave., Milwaukee, Wis. If you are not a member of the EAA and would like to join, membership applications will be available at the Ham Headquarters, or you may request one by filing formal traffic addressed to W9KKK, Omro, Wis. via the Wis. SSB net or write to Elmer C. Erickson, W9KKK, 455 Birch St., Omro, Wis. 54963.

**COLLINS Mechanical Filters**, 455 kHz, 2.4 kHz bandwidth, \$11.00 Postpaid, V. Mozarowski, VE3AIA, 1 Belgrave Drive, Islington, Ontario, Canada.

**JULY 9, LAFAYETTE, INDIANA FAIRGROUNDS.** Annual Indiana Radio Club Council Picnic and Hamfest. The fairgrounds is located at 1100 Teal Road, (Indiana Route #25), in the city of Lafayette, Ind. Easy access to Lafayette by Interstate 65. Hams flying in should use Halsmer Airport. There will be free shuttle service to and from Halsmer. This is a family affair. Fleamarket for the hams and fun and games for the rest of the family. Trailer parking. Advance tickets at \$1.50 each by mail from W9YIP, 477 Robinson, West Lafayette, Ind. Orders should be mailed by July 4. Enclose payment and SASE or pick up advance tickets at hamfest. Tickets at the gate will be \$2.00. Usual talk in frequencies.

**MUSIC CITY HAMFEST**, Nashville, TN presented by the Nashville ARC June 18 (Father's Day) at Lock Two Park, Lock Two Rd. off Pennington Bend Road, two miles North of Opryland USA. Flea market, refreshments and more. Drawing at 1:30 PM. Talk in, call K4CPO on 75m and FM 146.94. For more information write Music City Hamfest, P. O. Box 8085, Nashville, TN 37207.

**RECEIVER**, National HRO-500 w/matching speaker. Two years old; guaranteed perfect condition. \$900 firm. Real professional equipment. (805) 942-3531. James Hathorn, 44862 Lorimer, Lancaster, Calif. 93534.

**CLEGG ZEUS**, manual, some spare tubes, excellent condition \$200. firm. Duncan Smith, WA1UII, 6 Lawson Drive, Easthampton, Mass. 01027. 1-413-527-1761.

**WANTED** 115 volt A.C. Power Inverter. 200 watts or more. R. J. Brubaker, 3932 Charlotte, Kansas City, Mo. 64110.

**4-1000A** new pair \$130. One like new \$30. 4X500A like new with chimney \$40. 6907 new pair \$20. 5253 S. Luna, Chicago, Illinois 60638.

**MODEL ROCKETEERS** will hold an on the air convention July 15, 1972 on the Freq.: 3992 KC ± 5KC and 14300 KC ± 5KC. Net control: WA1NIC. Net call up will be: CQ Model Rocketeers. Be there.


**THE KANSAS NEBRASKA RADIO CLUB** will hold their annual Hamfest on August 6 at the Moose Club at Concordia, Kansas. Registration will start at 9:00 AM. All amateurs welcome.

**ON THE 23rd AND 24th SEPTEMBER, 1972** the North West Amateur Radio Conference is being held at this University. We would like to extend a warm welcome to any American Amateurs, who will be in Britain at that time, to attend the conference. University of Lancaster Amateur Radio Society, Bailrigg, Lancaster, England.

**YOUR AD belongs here too.** Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.
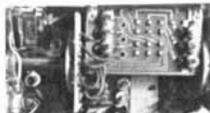
## NEW — 6T-HR-2

ADD MORE TRANSMIT FREQUENCIES TO YOUR HR-2



Will let you add six more transmitter frequencies to your HR-2 or HR-2A, also may be used on Transcan.

6T-HR-2 Kit	\$ 9.50
6T-HR-2 Wired	\$13.50
Shipping	\$ .60
Complete with all mounting hardware.	

Large stock of crystals for HR-2's and TMR scanners.	
HR-2 Xmit. xtals	\$5.75
HR-2 Receive xtals	\$3.99
TMR Receive xtals	\$3.99
Shipping	\$ .60

Entire Regency amateur line in stock. We ship pre-paid in Continental U.S.A.

**HT-200 users** add 2 more transmit frequencies to your H23 dcn or den: **H23 2 frequency kit: \$29.95.**

Includes all hardware, wiring, switch and knob. The above wired is \$39.95.

Can be used only with standard squelch HT200.

### TFME 2 METER PRE-AMPS



**New!**

Improved HF-144U pre-amp. Silver plated epoxy glass circuit board. Filter kit and B+ kit. All mount on new circuit board which is slightly smaller than original. This new board replaces all former except Motrac. Comes with mounting hardware and feet. Designed to work with the new solid state transceivers and older tube equipment. Kit-\$11.50 wired-\$16.50. Ship.-60¢



**TOPEKA FM ENGINEERING**  
1313 East 18th Terrace  
Topeka, Kansas 66607



## SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA, Model XT-1A, Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for hams, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.  
DIAL 402-987-3771

Many other kits, parts and plans available including shorter kits, focus, defl. coils, vidicon tubes, const. plans, etc.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731

## TOROIDS — TELETYPE

Lowest Prices Anywhere!



44 or 88 mhz TOROIDS

\$10 FOR 40

ALL PPD. U.S.


MODEL 15-19  
60 W P.M. GEAR SET  
(79112-1913)

\$3.50

FRESH RIBBONS  
FIT ALL MODELS 14-15  
19 20 32 33

\$3.50 BOX OF 12

MANY OTHER BARGAINS—SEND FOR CATALOG

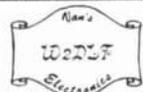

Van's W2DLT Electronics

302H Passaic Avenue  
Stirling, N. J. 07980  
CALL 201-647-3639

## GROTH-Type

### COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

#### PRICES

	POST PAID
TC 2	\$7.00
TC 3	\$7.50
Spinner (S)	\$1.00

Add \$0.75 for Air or UPS

Case: 2x4"; shaft ¼"x3"  
 Model TC2: Skirt 2½"; Knob 1½"  
 Model TC3: Skirt 3"; Knob 2½"

### R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143



## 220 MHz

Join the action on 220MHz with the JANEL deluxe receiving converters and preamps. Extremely sensitive with freedom from spurious responses.

220CA Converter, 28-32 MHz i-f. \$69.95 ppd  
 220PA Preamp, 2.5 dB NF, \$19.95 ppd

Write for full details. Other models available for 50, 144, and 432 MHz.

P. O. BOX 112  
 SUCCASUNNA, N. J.  
 07876  
 (201) 584-6521

### JANEL LABORATORIES

COMPUTER BOARDS, CORE MEMORIES, I.C.'s and EXPERIMENTER'S ELECTRONIC COMPONENTS AT TRUE BARGAIN PRICES. 16 BIT CORE MEMORY WITH DRIVERS & SENSE CIRCUITRY ALL ON PLUG-IN CARDS - \$135.00

7400 Series TTL I.C.'s 25c ea. - \$19.50 HUND. I.E.D.'s 55c - 4 LAYER TRIGGER DIODES 8/\$1.00 WIDE VARIETY OF TOGGLE & MAGNETIC SWITCHES, I.C. RELAYS, I.C. BOARDS, POWER SUPPLY REGULATORS, ELECTRONIC HARDWARE, WIRE & CABLE P.C. SOCKETS, S.C.R.'s, KEYBOARDS, COPPER CLAD P.C. MATERIAL & DOZENS OF OTHER EXPERIMENTER ITEMS.

ALL POSTPAID  
 SEND 10c FOR CURRENT CATALOG.  
 TRI-TEK, INC.  
 P.O. BOX 14206, PHOENIX, ARIZ. 85031

## AT LAST!!

An Inexpensive Connector for RG-17/U Coax

- Less than .1db loss at 500MHz
- Teflon insulation • Solderless
- Connects directly to standard SO239

\$9.95 each PPD or Write for full information

### WAYNE SMITH PRODUCTS

P. O. Box 46521, Bedford, Ohio 44146

NEW SSB MINIATURE CRYSTAL FILTERS — Made U.S.A.  
 Write us about your crystal filter needs  
 Model WF-4 Model WF-8



No. Crystals	4	8
Center Freq.	9.0 MHz	9.0 MHz
Band Width at 6db	2.5 kHz	2.5 kHz
60db/6db Shape	2.0 (45/6)	1.8 max
Ultimate Rejection	45 db	100 db min.
In/Out Termination	120 Ω	140 Ω
PRICE	\$18.95	\$26.95

WHEATLANDS ELECTRONICS  
 P. O. BOX 343  
 ARKANSAS CITY  
 KANSAS 67005

Matching Crystals USB (8998.5 kHz) or LSB (9001.5 kHz) \$2.75 each



ARC R-19 (R-508) Receiver 118-148 MHz tunable. 9 tube Superheterodyne AM Receiver. If 15 MHz checked out with schematic, \$14.95. Blower 115 VAC 60 CPS 1PH. 20 CFM 3400 RPM, \$4.95. Teletype Tape 3/8 canary, 10 rolls \$1.25. New catalogue now available 10¢

FRANK ELECTRONICS

407 Ritter Road, Harrisburg, Pa. 17109

### SPACE ELECTRONICS division of MILITARY ELECTRONICS CORP. WANTS TO BUY

All types of military electronic equipment and parts. Call collect for cash offer.

76 Brookside Drive, Upper Saddle River  
 New Jersey 07458 • (201) 327-7640

## ULTRA-BAL 2000

- Advanced design
- No radiation from coax, more power to antenna
- Less noise on receive
- Full 2kW - 3 to 30 Mcs., 1:1 or 1:4 ratios
- Encapsulated ultra weather-proof
- Mt. type 2KV Teflon insulation over silver plated wire for ultra low loss



Specify ratio desired \$ 8.95 ppd.

### K.E. Electronics

Box 1279, Tustin Calif. 92680

### NEW GLADDING 25

FM TRANSCEIVER, 25 WATTS OUTPUT, 6 channels complete with xtals for 146.34/146.76 and 146.94/146.94, low power position, completely separate xmit-rec xtal switching, built in 12V DC supply (Amateur net \$249.95) OUR LOW INTRODUCTORY PRICE \$208.50. With matching AC supply (reg. \$299.95) \$254.00. Write for literature. Ham-M's \$99.00.

### AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129 Terrace, Miami, FL 33156 305-233-3631

## F.C.C. EXAM MANUAL


The Original Test-Answers exam manual that prepares you at home for FCC First and Second class licenses. Includes Updated multiple choice tests and key Schematic diagrams. PLUS - "Self-Study Ability Test." - ONLY: \$9.95 Postpaid



COMMAND PRODUCTIONS P.O. BOX 26348-K  
 RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126
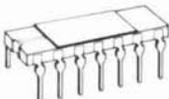
## IC PRICES SLASHED

FACTORY FIRSTS  
 SIGNETICS • NATIONAL  
 RAYTHEON



— SATISFACTION GUARANTEED —

DIGITAL TTL	7474N	50¢
7400N 27¢	7440N	27¢
7401N 27¢	7441AN	\$1.33
7402N 27¢	7442N	\$1.25
7403N 27¢	7447N	\$1.52
7404N 29¢	7451N	27¢
7410N 27¢	7454N	27¢
7420N 27¢	7472N	50¢
7430N 27¢	7473N	60¢
	7474N	50¢
	7475N	\$1.15
	7476N	62¢
	7490N	\$1.18
	7492N	\$1.18
	7493N	\$1.18
	7495N	\$1.39
	74107N	65¢
	74121N	75¢

### LINEAR INTEGRATED CIRCUITS

DIP or TO-5 709 50¢ 10/\$4.50, 741 62¢ 10/\$5.75  
 723C TO-5 \$1.17 NE565A PLL DIP \$6.00

### GENERAL PURPOSE TRANSISTORS

2N5134 Si NPN or 2N5138 Si PNP 15¢ 8/\$1.00

1 AMP SILICON SUBMINIATURE RECTIFIERS  
 1N 4001 50 PIV, 1N4002 100 PIV, 1N4004 400 PIV  
 1N4005 600 PIV 10/\$1.00, 100/\$7.50

Free catalog - Large quantity discounts - Orders less than \$10. add 25¢ - others postpaid.

### PRICE PACESETTER FOR QUALITY IC'S

DIGI-KEY, Box 126A, Thief River Falls, MN 56701

## TRANSKEY (TM)



**\$34.95**

Postpaid

Electronic Keyer and Monitor

- Transistorized; relay output.
- Key built-in; wired, ready to operate.
- Continuously variable speeds 5-50 WPM.
- Penlight cells or 6V external source.
- Key contacts adjustable.
- Push switch on back, automatic or semi-automatic operation.
- Dot-space ratio adjustable.
- Variable tone control on monitor.
- Keyer 3 1/2 x 5 1/2 x 1 3/4. Weight 2 lbs.
- Unconditional one year guarantee.

**W6PHA — GLOBAL IMPORT CO.**

BOX 246, EL TORO, CALIF. 92630

10 day return privilege for cash refund

"Dealers wanted"

This is the Beautiful KW202 Receiver that you keep hearing about!



**KW**  
ELECTRONICS  
LIMITED

160-10M; SSB/CW/AM; Q-Multiplier; Xtal Calibrator

**KW Electronics** ALL for ONLY  
\$395

10 Peru St., Plattsburgh, NY 12901

In Canada: 222 Newkirk Road,

Richmond Hill, Ontario

Matching  
Speaker

\$28.50



**250 MHz! 6 DIGITS!**

FREQ. RANGE: 10 hz to 250 mhz. LEVEL: 1 mw to 50 watts. ACCURACY: .0005%. Write for specs.

MODEL 6-VHF-A \$350 fob

**PAGEL ELECTRONICS**

6742-C TAMPA AVENUE  
REBEDA, CALIF. 91335

## AMERICAN CRYSTAL CO.

1623 Central Ave., Kansas City KS 66102, 913-342-5493

Mfg. Crystals for most communication Equip.

Small Orders Accepted

For use in:	Crystal prices @	.002%
TWO WAY	FUNDAMENTALS	
SCANNERS	2 to 14.9Mhz	\$5.25
MONITORS	15 to 19.9Mhz	6.10
TRANSMITTERS	THIRD MODE	
C.B. SYNTHESIZERS	10 to 44.9Mhz	5.35
REPEATERS	45 to 55.9Mhz	6.10
SCANNERS (oper. 152.50 to 163.50 Mhz .002%)		\$5.00
ELEMENT CRYSTALS .0005%		
(channel freq. changed in customer's element)		15.00
C.B. (Class D Single channel)		2.75
AMATEUR NOVICE, (HC6/U, ±1 kc, 32 mmF, Fund. 3.5-8.9 Mhz)		3.00
Extras: Oven use \$1.50, Subminiature 25¢, .093 pins 10¢		
Postage 1-2 crystals 2 oz. each additional 1-2 crystals 1 oz.		
Write for quantity discount		



## signal/one CX7-A



ALPHA SEVENTY

NEW ALPHA 70 — NOW BY CMI • NEW 8877 FINAL • THE LINEAR FOR THE CX7-A. YOU WILL NEVER KNOW HOW LITTLE IT COSTS TO OWN THE INCOMPARABLE PRESTIGE CX7-A OR ALPHA 70 UNTIL YOU WRITE OR PHONE US THE TRADE IN DEAL YOU WANT • WE USUALLY SAY YES! NO ONE ANYWHERE BEATS OUR DEAL!

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129 Terrace • Miami, FL 33156

Days (305) 233-3631

Nights-Weekends (305) 666-1374



EK-404 DELUXE KEYS \$124.95

ALL THE FEATURES YOU'VE ASKED FOR


115Vac AND +12Vdc

READ JAN 1972 CQ AND MAR.

1972 QST FOR REVIEW OF SIMILAR EK-402 PROGRAMMABLE KEYS

KEYER

WRITE FOR BROCHURES

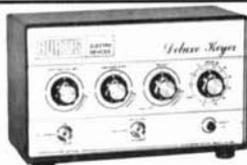

ECKMAN ELECTRO DEVICES BOX 6090 • MOUNTAIN VIEW, CALIFORNIA, 94040 • TEL. (415) 964-3730

## VARACTORS and VVC'S

for Amateur Radio Service in Voltage Controlled Oscillators, AFC, remote tuning, variable filters . . . try the NEW WAY TO TUNE.

write for data sheets

**EASTRON CORP.**

25 Locust St., Haverhill, MA 01831



## HAM RADIO CENTER

Announces!



**NOW:** Call your order in, and we'll pick up the tab for the phone call. (Minimum order \$25.00)  
**HOW:** Place station to station call. When phone bill is received, forward copy along with our invoice covering order phoned in, we'll send refund check. DO NOT CALL COLLECT.

**PLUS:** We will ship your order for NEW equipment PREPAID if destination is in our UPS surface shipping area. (Limit-108" width & girth combined and 50 lbs. max. wt.)

COMPLETE STOCKS ALL NATIONAL BRANDS  
WE BUY-SELL-TRADE USED EQUIPMENT

Write for List

**HAM RADIO CENTER, INC.**

8342 Olive Bl., St. Louis, Mo. 63132

Phone (314) 993-6060

**BRAND NEW FREQ-SHIFT TTY MONITOR**

NAVY OCT-3: FM Receiver type, freq. range 1 to 26 MHz in 4 bands, cont. tuning. Crystal calib. Reads up to 1500 Hz deviation on built-in VTVM. Cost \$1100.00 each! In original box, with instruct. book & cord, fob Mariposa, Cal. Shpg. wt. 110 lbs. 49.50.

**HIGH-SENSITIVITY WIDE-BAND RECEIVER**

COMMUNICATIONS • BUG DETECTION

• SPECTRUM STUDIES

38-1000 MHZ AN/ALR-5: Consists of brand new tuner/converter CV-253/ALR in original factory pack and an exc. used, checked OK & grtd main receiver R-444 modified for 120 v. 50/60 hz. The tuner covers the range in 4 bands: each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.4 mhz, 0.9 at 133 mhz, 5 at 538 mhz, 4 1/2 at 778 mhz, 7 at 1 ghz. The receiver is actually a 30 mhz IF ampl. with all that follows, including a diode meter for relative signal strengths: an atten. calibrated in 6 db steps to -74 db, followed by an AVC position; Pan., Video & AF outputs; switch select pass of  $\pm 200$  kHz or  $\pm 2$  mhz; and SELECT AM or FM! With Handbook & pwr. input plug, all only 375.00

We have SP-600-JX, R390, WRR-2 Receivers. Ask!

**REG. PWR. SPLY FOR COMMAND. LM. ETC.**

PP-106/U: Metered. Knob-adjustable 90-270 v up to 80 ma dc; also select an AC of 6.3 v 5A, or 12.6 v 2 1/2 A or 28 v 2 1/2 A. With mating output plug & all tech. cata. Shpg. wt. 50 lbs. 19.50

**BARGAINS WHICH THE ABOVE WILL POWER:**

LM-(1/2) Freq. Meter: 125-20 MHz, .01%, CW or AM, with serial-matched calib. book, tech. data, mating plug. Shipping wt. 16 lbs. 57.50  
 TS-323 Freq. Meter: 20-480 MHz, .001% 169.50  
 R22A/ARC5 Command Q-5er 190-550 kHz, exc. cond. 16.95  
 A.R.C. R22 Command rcvr 540-1600 KHz, exc. cond. 17.95  
 A.R.C. R15(MIL R-509)Command. 108-135 MHz, new 27.50

NEMS-CLARKE #1670 FM Rcvr 55-260 MHz like new 475.00  
 WWV Rcvr/Comparator 2 1/2 - 20 MHz 195.00  
 Empire Devices NF-114 RFI meter is a red-hot receiver from 150 KHz to 80 MHz 295.00

Attention Buyers, Engineers, Advanced Technicians: We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have.

**R. E. GOODHEART CO. INC.**

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

**FREE ALARM CATALOG**

64 PAGES FILLED WITH 350 BURGLAR AND FIRE ALARM PRODUCTS FOR INSTALLERS AND ELECTRONIC TECHNICIANS. INCLUDES RADAR, INFRARED, CONTROLS, HARD-TO-FIND PARTS, AND 6 PAGES OF APPLICATION NOTES.

 mountain west alarm  
 4215 n. 16th st., phoenix, az. 85016

**2 METER PREAMP**

More Gain, Less Noise For The Money!

20 DB GAIN  
 NOISE FIGURE 2.5  
 12 VDC OPERATION

Small Size: 1 1/4 x 2 1/4 x 1/2 - Only \$12.50  
 Kit \$9.50

Option for 150-250 VDC Operation - \$1.00



DATA ENGINEERING INC.  
 Box 1245 Springfield, Va. 22151

Central New York Specialty Headquarters

**FM by STANDARD COMMUNICATIONS**

High Power by EHRHORN

Quality-Selected Used Ham Gear

Write for listing, updated twice monthly

**CFP ENTERPRISES**

10 Graham Road West  
 Ithaca, New York 14850  
 607-257-1575

QSOs

EN

ESPAÑOL

Special

Any Course on 5" reel

\$9

(check)

Spanish

German

Japanese

QSOs

AUF

DEUTSCH

Courses in Spanish, German, and Japanese designed for amateurs. Enables hams to exchange greeting and signal reports and to chat with foreign hams. Each course has many typical QSO's, technical terms, and slang. Narrated by native speakers.

**Spanish course:** 75 minutes Spanish dialogue with English-Spanish manual taped on 7" reel 3 3/4 IPS for \$11.95, on C-90 Cassette \$10.95. For **German course** running 90 mins, add \$2 to above prices. **Japanese course** 30 mins. same prices as Spanish course. Dual language manuals alone \$2.50. Mailed 3rd class in U.S. PPD. Send checks to:

Foreign Language QSOs, Box 53, Acton, Mass. 01720

**NEW 2M PREAMPLIFIER**

12 vdc powered

27 db gain (approximately)

noise figure 2.5

will bring most receivers

to .1  $\mu$ v sensitivity

without appreciable noise.

Metal case. ONLY \$17.95 ppd.

**CRAWFORD ELECTRONICS**

302 West Main, Genoa, IL 60135

**WE PAY HIGHEST**

PRICES FOR ELECTRON  
 TUBES AND SEMICONDUCTORS

**H & L ASSOCIATES**

ELIZABETHPORT INDUSTRIAL PARK

ELIZABETH, NEW JERSEY 07206

(201) 351-4200

# Just Printed!

Application Rules FOR  
TTL INTEGRATED CIRCUITS  
INCLUDING **Operating**  
Instructions FOR ALL  
POPULAR MODELS

send 50¢  
for your copy  
FREE WITH ANY ORDER  
OVER \$5.00



Digital Clock  
Semi-kit

MINITRON 7-SEGMENT  
READOUT \$3.70

15 IC'S & 4 MINITRONS (ONLY)  
120 VAC 5.35 00

SEND 25¢ FOR CATALOG

**Arizona Semiconductor**

PO BOX 112  
GOODYEAR, ARIZONA  
85338

## WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

... COMPLETE YOUR HAM SHACK with

OUR NEW HOME WEATHER INSTRUMENT:

• READ WIND SPEEDS ON TWO SCALES; CALIBRATION to 106 mph

• HANDSOME HARDWOOD CASE

• 2 YEAR WRITTEN GUARANTEE

• ELECTRONICS EMPLOYS INTEGRATED CIRCUITS

• 5% DISCOUNT TO ALL HAMS ACTIVE IN WEATHER NETS

• Includes Display Unit and Rotor mechanism (both shown), 60 ft. lead in, mounting hardware, battery, instruction manual



\$ 69.95 COMPLETE  
POSTAGE PAID  
(dealer inquiries invited)

**CU associates, BOX 333, GOODYEAR, AZ 85338**

### NEW SB-144

FM TRANSCEIVER, 12 channels complete with xtals for 146.16/146.76, 146.34/146.94, and 146.94/146.94, dynamic mic., "S" and output meter, ceramic filter, back lighted dial, FET front end, double conversion, tiltable mobile bracket, 12V DC built in (amateur net \$239.95) OUR LOW INTRODUCTORY PRICE \$203.50 + with AC supply (reg. \$259.90) \$223.45 + Write for literature.

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129 Terrace, Miami, FL 33156 305-233-3631

5 VOLT, 1 AMP POWER SUPPLY  
on a plug-in PC card  
PERFECT FOR DIGITAL IC'S

INPUT	115 VAC 60 HZ
OUTPUT	5V 1 AMP DC
LOAD REGULATION	100 mv (NL to FL)
LINE REGULATION	50 mv (105-125VAC)
SHORT CIRCUIT PROTECTED	1 sc = 750 ma, typ.
SIZE	3.6" x 3.2" x 1.7"
MATING CONNECTOR	22 pin on .156 ctrs.

PRICE: \$14.90 ppd. U.S.A.  
Mass. residents add 3% sales tax

**ELCOM Industries, Inc.**

CIVILIAN TERMINAL, HANCOM FIELD  
BEDFORD, MASS. 01730  
617-274-6090

**TYMETER**

"Time At A Glance"  
DIGITAL CLOCKS



# 24 HOUR CLOCK

## CALL-IDENT 10-MINUTE STATION CALL REMINDER

# 124

# 23<sup>50</sup>

Made in U.S.A.



10-minute repeating timer buzzes warning to sign in your call letters. Walnut or ebony plastic case. 4" H, 7 3/4" W, 4" D. 110V, 60 cy. One Year Guarantee. Made in U.S.A.

At Your Dealer, or DIRECT FROM

**PENNWOOD NUMECHRON CO.**

TYMETER ELECTRONICS

7249 FRANKSTOWN AVE.

PITTSBURGH, PA. 15208

AMPEREX  
READOUT  
TUBE

170 volt neon  
Brand new  
\$3.00 ea.  
10/\$25.00




7 SEGMENT  
LO-VOLTAGE

GE #Y4075, 25V,  
readout, 1.6 inch  
hi. Wire leads.  
Brand new, \$3.00  
each or 10/\$25.



Giant Alpha-Numeric Neon Readout.

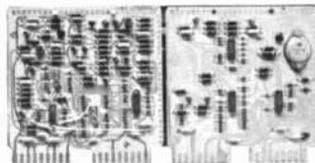Complete alphabet plus all digits; 15 segments, 2 1/2" high. \$3.00 each, 10 for \$25.00. Sockets available at 50¢ each. Sockets available only for tube purchasers.



IC computer boards. Along with all the other goodies you will find each board will have marked IC's on them. 3 boards \$1.00, 20/\$5.00

3 WATT LASER DIODE TA-2628	\$5.00
PANADAPTER BC 1031 Used	\$45
Unused w/spares	\$75
56K MEMORY CORE STACK	\$100
LASER DISCHARGE CAP	
40 uf 3 KV 180 JOULES	\$10
COMPUTER GRADE CAPS 1000 uf 450V	
\$1.50 ea. 10/\$12	
MAN-3 LED READOUT \$3.50 ea. 10/\$35	

Please add postage for above items.  
Send 25¢ for Surplus Catalog . . .

**JOHN MESHNA JR. ELECTRONICS**  
P.O. Box 62 E. Lynn, Mass. 01904

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

## INDEX

- American States
- Amidon
- Andy
- Allied-Radio Shack
- Amateur-Wholesale
- American Crystal
- Arizona
- Barry
- Bauman
- Bob's
- CFP
- CNE
- Camp Butler
- Caringella
- Circuit Specialists
- Command
- Comtec
- Crawford
- CTG-Bitcil
- CU
- Curtis
- Dale
- Dames
- Data
- Digi-Key
- Drake
- Dycomm
- Eastron
- Eimac
- Elcom
- Foreign Language
- Frank
- Gateway
- Global
- Gray
- H & L
- HAL
- Ham Radio Center
- Henry
- Hobby
- Hy-Gain
- International Crystal
- Jan
- Janel
- Justin
- KE
- KW
- L.A.
- Larsen
- Lee
- Lynch
- Meshna
- Micro-Z
- Mini-Products
- Mountain West
- Pagel
- Palomar
- Pennwood
- RP
- Radiation
- Callbook
- Robot
- Ross & White
- Savoy
- Signal/One
- Solid State
- Space-Military
- Spectronics
- Spectrum
- Sprague
- Standard
- Structural Glass
- Topeka
- Tri-Tek
- Van's
- Vanguard
- Wayne Smith
- Weinschenker
- Wheatlands
- Wolf
- World QSL

June 1972

Please use before July 31, 1972

Tear off and mail to  
**HAM RADIO MAGAZINE** — "check-off"  
 Greenville, N. H. 03048

NAME.....  
 CALL.....  
 STREET.....  
 CITY.....  
 STATE..... ZIP.....

# Advertisers iNdex

American States Electronics	70
Amidon Associates	72
Andy Electronics	78
ATV Research	89
Amateur Electronic Supply	35
Amateur-Wholesale Electronics	90, 91, 93
American Crystal Co.	93
Arizona Semi-Conductor	93
Barry	77
Bauman	90
Bob's Discount Electronics	80
CFP Enterprises	92
CNE Magazine	76
Camp Albert Butler	76
Caringella Electronics	85
Circuit Specialists	48, 49
Command Productions	90
Crawford Electronics	92
CTG-Bitcil Systems, Inc.	79
CU Associates	93
Curtis Electro Devices	91
Dale Electronics Corp.	87
Dames Co., The Ted	88
Data Engineering, Inc.	75, 92
Digi-Key	90
Drake Co., R. L.	2
Dynamic Communications, Inc.	68
Eastron Corp.	91
Eimac, Div. of Varian Assoc.	Cover IV
Elcom Industries, Inc.	93
Foreign Language QSO's	92
Frank Electronics	90
G & G Radio Supply Co.	86
Gateway Electronics	78
Global Import Co.	91
Goodheart Co., Inc., R. E.	92
Gray Electronics	87
H & L Associates	92
HAL Communications Corp.	82
Ham Radio Center, Inc.	91
Henry Radio Stores	Cover III
Hy-Gain Electronics Corp.	5, 67, 73, 96
International Crystal Mfg. Co., Inc.	71
Jan Crystals	74
Janel Labs	90
Justin Inc.	72
KE Electronics	90
KW Electronics	91
L.A. Electronix Sales	68, 95
Larsen Electronics, Inc.	41
Lee Electronics	78
Lynch Co., J.	80
Meshna, John, Jr.	93
Micro-Z Co.	72
Mini-Products, Inc.	57
Mountain West Alarm	92
Pagel Electronics	91
Palomar Engineers	76
Payne Radio	74
Pennwood Numechron Co.	93
RP Electronics	70
Radiation Devices Co.	88
Radio Amateur Callbook	66, 70
Robot Research	69
Savoy Electronics	61
Signal/One Corporation	Cover II
Solid State Systems, Inc.	84
Space-Military Electronics	90
Spectronics, Inc.	81
Spectrum International	88
Standard Communications Corp.	1
Structural Glass Limited	74
Topeka FM Engineering	89
Tri-Tek, Inc.	90
Van's W2DLT	89
Vanguard Labs	80
Wayne Smith Products	90
Weinschenker, M.	65
Wheatlands Electronics	90
Wolf, S.	88
World QSL Bureau	93

# BONUS THE BEST ANTENNA PACKAGES YET!

*OPTIMUM PERFORMANCE  
GUARANTEED SAVINGS*



ALL NEW, engineered for optimum performance with TRI-EX's Certified\* Antenna Towers & HY-GAIN's TOP Performance Antennas. The utmost in craftsmanship and construction for your satisfaction. . . .

Local Bank Financing - 15% Down or Trade-In Down - Good Reconditioned Equipment. Nearly all makes and models. Our reconditioned equipment carries a 30 day warranty and may be traded back within 90 days for full credit toward the purchase of NEW equipment. Inquiries invited.

\* Certified Welders & Approved by L.A. City

W51 SHOWN

LAE MW35 "STANDARD" Package  
(Free Standing Crank-Up Tower  
9.5 Sq. Ft. - 50 MPH) (35 FT.)  
CDR AR-22R Rotator\*  
100 ft. RG-58/U Coax & Control Cable  
Substitute 50 ft. free standing, add \$100  
*Complete with one of the following antennas:*

HY-GAIN TH2MK3	\$275
HY-GAIN TH3JR	\$275
HY-GAIN DB10-15A	\$285
HY-GAIN HY QUAD	\$285
HY-GAIN TH3MK3	\$295
*TR-44 rotor w/cable add:	\$ 35
HAM-M rotor w/cable add:	\$ 65

LAE W51 "DELUXE" Package (51 Ft.)  
(Free Standing, 9 Sq. Ft. - 50 MPH)  
CDR TR-44 rotor\*  
100 ft. RG58/U Coax & Control Cable  
Substitute 67 ft. free standing, add \$400  
*Complete with one of the following antennas:*

HY-GAIN DB 10-15A	\$590
HY-GAIN HY QUAD	\$599
HY-GAIN 204BA	\$625
HY-GAIN TH3MK3	\$625
HY-GAIN TH6DXX	\$645


Free stdg. base incld. NO/CHARGE  
\*HAM-M rotor w/RG8/U add: \$ 45  
LAE LM354 "SUPER" Package (54Ft.)  
(16 Sq. Ft. - 60 MPH)

CDR HAM-M Rotor  
100 ft. RG8/U Coax & Control Cable  
Substitute 70 ft. free standing, add \$650  
*Complete with one of the following antennas:*

HY-GAIN TH3MK3	\$750
HY-GAIN 204BA	\$765
HY-GAIN TH6DXX	\$785

Freight PREPAID to your door in the Continental USA west of the Rockies. For shipment east of the Rockies, add \$15.00. Substitutions may be made.... write for prices.

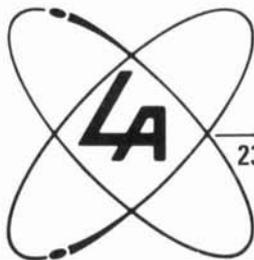"WEST COAST'S FASTEST GROWING AMATEUR RADIO DISTRIBUTOR"  
"WE SELL ONLY THE BEST"



## Electronic Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4456 or (213) 534-4402

HOME of LA AMATEUR RADIO SALES

*the most powerful antennas under the sun!*



## **The Best Vertical There IS!** *80 through 10 meters*

# **Hy-gain 18AVT/WB**

### **New, from the inventors of wideband verticals.**

Pack some punch! All the omnidirectional performance of Hy-Gain's famous 14AVQ/WB...plus 80 meter capability! Unrivalled performance, rugged extra heavy duty construction, and the price you want...all in one powerful package!

- Automatic switching on all five bands through the use of three beefed-up Hy-Q traps...featuring extra large diameter coils for exceptional L/C ratio and extremely high Q.
- Recessed coax connector furnished.
- Top loading coil and four element static hat.
- Constructed of extra heavy wall high tensile aluminum.
- Hot performance all the way across the band with just one setting (10 through 40).
- Hy-Q traps effectively isolate antenna sections for full 1/4 wave resonance on all bands.
- No dissimilar metals to cause noise.
- SWR 2:1 or less at band edges.
- Maximum legal power with low frequency drift.
- Exceedingly low radiation angle makes DX and long haul contacts a cinch...whether roof or ground mounted.
- Very low RF absorption from insulating materials.

The 18AVT/WB is constructed of extra heavy duty, taper swaged, seamless aircraft aluminum with full circumference, corrosion resistant compression clamps at all tubing joints. This antenna is so rigid, so rugged...that its full 25' height may be mounted using only a 12" double grip mast bracket...no guy wires, no extra support...the 18AVT/WB just stands up and dishes it out!

**Order No. 386**

**\$59.95**



Get the strength, the performance and the price you want...from the man who sells the complete line of quality Hy-Gain equipment.

## **HY-GAIN ELECTRONICS CORPORATION**

Box 5407-WF Lincoln, Nebraska 68505

# TEMPO...a quality name...a growing family


## TEMPO "ONE"
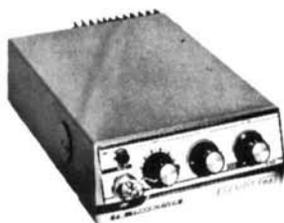
### SSB TRANSCEIVER

.....represents the culminating achievement of many years of experience in the amateur radio field. Modern design, superb performance, high styling, sturdy construction, outstanding reliability, exceptional value.



Tempo "ONE" Transceiver \$319.00  
AC/ONE Power Supply (117/230 Volt 50/60 cycle) \$ 99.00  
DC/1-A Power supply (12 volts DC) \$110.00



## TEMPO/fma

the top of the Tempo VHF line. This transceiver offers all of the famous Tempo quality and performance at 25 watts of power output. The unit also features a low power position for 10 watts output to conserve battery power. Here is a true value in VHF FM; Tempo presents high power operation for only \$349.00.

## TEMPO DKT ELECTRONIC KEYS

The Tempo DKT keyer is the latest in electronic keyer design. Using integrated circuit techniques it provides the unique features of dot memory and single dot injection which, with a specially designed twin lever key assembly, affords effortless sending and perfect character formation regardless of speed.

Price: \$89.00.



## TEMPO FMP

Truly mobile, the Tempo fmp-3 watt portable gives amateurs 3 watts, or a battery saving 1/2 watt, FM talk power anyplace at anytime. With a leather carrying case included, this little transceiver will operate in the field, in a car, or at home with an accessory AC power supply. The battery pack is of course included. Price: \$225.00.

## TEMPO LW 1500 DUMMY LOAD WATTMETER

The Tempo LW1500 load-wattmeter offers typical Tempo price-performance value. Designed for amateur or commercial use, the LW1500 is completely portable. An internal "D" cell battery powers the overheating warning light so no AC connections are necessary. The built-in handle and light weight make the load convenient for desk, bench, auto or field testing.

Price: \$119.00.



### Other Tempo products:

FMV 450 - 10 watt UHF transceiver  
FMV - 10 watt 2 meter transceiver  
RBF-1 Wattmeter & SWR Bridge  
VHF & UHF Solid State Amplifiers

# Henry Radio



11240 W. Olympic Blvd., Los Angeles,  
Calif. 90064  
931 N. Euclid, Anaheim, Calif. 92801  
Butler, Missouri 64730

213/477-6701  
714/772-9200  
816/679-3127
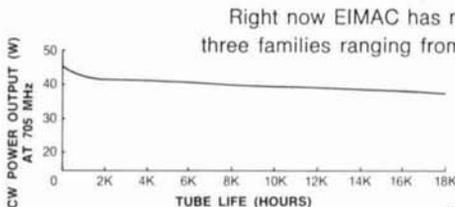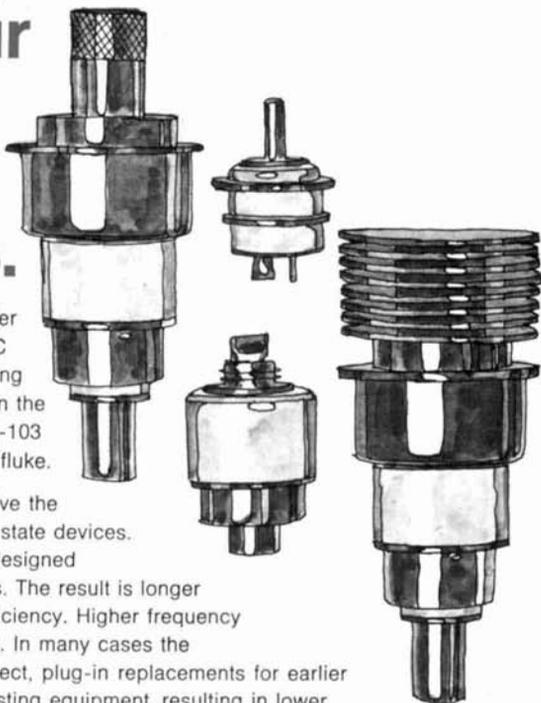
# Plug more life into your system with EIMAC planar triodes.

To make a long story short, after 18,000 hours of life test EIMAC improved 7211's were still delivering over 35 watts CW at 705 MHz in the r-f cavities for the Army's GRC-103 Radio Set. And that's no fluke.

Several design improvements give the 7211 life comparable to solid state devices. These improvements have been designed into all EIMAC planar triodes. The result is longer life. Higher power and efficiency. Higher frequency operation. And better linearity. In many cases the improved tubes are direct, plug-in replacements for earlier models in existing equipment, resulting in lower cost per operating hour to the user.



Right now EIMAC has more than 70 planar triode types in three families ranging from the 2C39A types through the latest miniature planar triodes. In CW, EIMAC frequency capability goes up to 5 GHz and powers to 450 watts. For pulse applications, EIMAC has models capable of delivering up to 1 kilowatt peak at 6 GHz.

When it comes to planar triodes for retrofit or new equipment, only EIMAC has full capability. For a copy of our planar triodes applications manual, get in touch with EIMAC, 1678 Pioneer Road, Salt Lake City, Utah 84104. Or your local Varian/EIMAC Electron Tube and Device Group Sales Office.

