

75 cents

*hr*

focus  
on  
communications  
technology . . .

# *ham* **radio**

*magazine*

JULY 1973



## *this month*

- carrier-operated relay 16
- vhf receiver 22
- two-meter frequency synthesizer 34
- antenna matching 58
- sweepstakes winners 68

# Savoy

## BASSETT

High efficiency mobile and portable antennas for all amateur bands, CAP, MARS, CB, SECURITY, PUBLIC SERVICE, MARINE, AND GOVERNMENT USE.

- 2-6-10-15-20-40-75
- Identical size, cost, and appearance
- FULLY ADJUSTABLE TO FREQUENCY IN FIELD
- Low weight, low drag, high strength fiberglass
- Polished chrome brass standard 3/8-24 thread
- High gain collinear on 2 meters

MODEL DGA-2M  
\$29.50 postpaid  
in U.S.A.



\$3.75

Postpaid in U.S.A.

TYPE 900 A

TYPE 901



## HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Vari-tronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all other equipments.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.




### BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075 . . . . .	\$59.50
MODEL DGA-204075 . . . . .	\$79.50
MODEL DGA-2040 . . . . .	\$59.50
MODEL DGA-152040 . . . . .	\$79.50

## BASSETT VACUUM BALUN

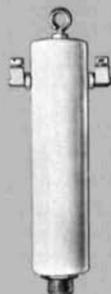

The famous sealed helium filled Balun employed with the DGA Series Antenna Systems. Solderless center insulator easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95  
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA


# Savoy Electronics, Inc.

P.O. Box 7127 - Fort Lauderdale, Florida - 33301

Tel: 305-566-8416 or 305-947-1191


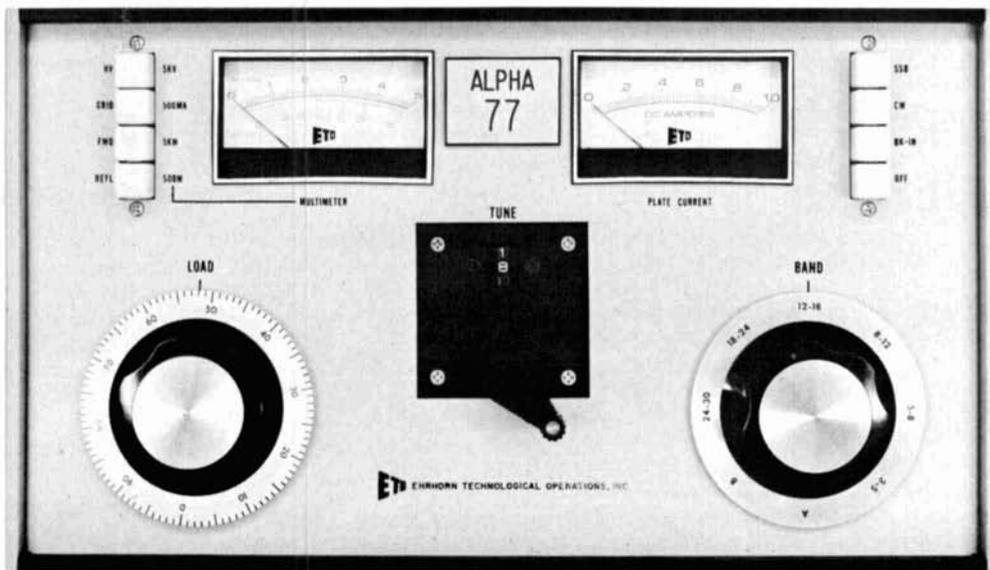
# “OPERATING ON-THE-AIR WITH THE ALPHA 77 IS A PURE PLEASURE”



*“IF THE AMATEUR WANTS TO GO FIRST CLASS  
IN EVERY SENSE OF THE WORD,  
THE ALPHA 77 IS ONE WAY TO DO IT.”*

(QST — March 1973)

The superb ALPHA 77 legal-limit amplifier is truly in a class by itself . . . a sleek desk-top powerhouse that delivers *a whole rack full* of performance. The '77 is engineered and built to operate *continuously* at maximum legal power in *any mode* including FSK or SSTV — and to stay cool and quiet in the process.

Now the ALPHA 77 is the *only linear* to provide full *standard* coverage of 10 through 160 meters — a feature not available elsewhere even as an option.

You really have to *see and use* the ALPHA 77 to fully appreciate its unmatched quality and ruggedness. If *you* enjoy owning and using *the very finest*, you owe it to yourself to *at least investigate the ALPHA 77* by phoning or writing for detailed literature. Available direct from ETO and from selected dealers coast-to-coast. ALPHA 77 domestic net price, \$1995.



EHRHORN TECHNOLOGICAL OPERATIONS, INC.  
BROOKSVILLE, FLORIDA 33512  
(904) 596-3711

**for over 20 years we've  
been designing VHF-FM  
antennas for some  
pretty tough customers.**

**we know  
you're just as tough.**

A product in the amateur market gets a reputation very quickly. It measures up to what you expect in engineering, performance and quality — or else. That's why A/S amateur antennas are built to the identical design and construction standards as their commercial counterparts. Standards that have made them specified for more police and public safety vehicle installations than all other brands combined.

**HM-177  
2 Meters**

Features new high conductivity copper and nickel coated 17-7 PH stainless steel whip. Shunt fed coil encased in waterproof PVC jacket. All fittings chrome plated brass. Easy snap-in mounting. 3 dB gain.\*

**NEW! HM-223  
1 1/4 Meters  
(220 MHz)**

High performance 3/4 wavelength design for the new 220 MHz activity! Directly fed with low loss coil in new low-profile design. Spring and whip easily removable leaving only 1 3/16" high base for car wash clearance. 3 dB gain.\*

**HM-175  
3/4 Meters**

Collinear design with truly hot performance! Base fittings have silver plated contacts. Can handle 100 watts. Whip and phasing coil assembly is a one piece molded design to resist vibration and moisture. 5 dB gain.\*

**HM-4  
2 Meters**

Tough, virtually indestructible antenna for hand-helds. Completely insulated. Base fitting matches Motorola HT, E. F. Johnson, and Standard portables.

**HM-5**

Same as above but for Drake and other packet portables with SO-239 fittings.

**NEW ASCOM® TOWERS**

High strength, low maintenance aluminum towers for HF and VHF antenna installations. There is a complete line of ASCOM self-supporting towers — in heights from 30 to 90 feet — at attractive prices!

\*Measured over a 1/4 wavelength whip

WRITE FOR FREE AMATEUR ANTENNA  
and/or TOWER CATALOGS



**the antenna  
specialists co.**

Division of ORION INDUSTRIES, INC., 12435 Euclid Ave., Cleveland, Ohio 44106  
Export: 2200 Shames Dr., Westbury, L.I., New York 11590 Canada: A. C. Simmonds & Son

July, 1973  
volume 6, number 7



**ham**  
**radio**  
magazine

**staff**

James R. Fisk, W1DTY  
editor

Patricia A. Hawes, WN1QJN  
editorial assistant

Nicholas D. Skeer, K1PSR  
vhf editor  
J. Jay O'Brien, W6GDO  
fm editor

Alfred Wilson, W6NIF  
James A. Harvey, WA6IAK  
associate editors

Wayne T. Pierce, K3SUK  
cover

T.H. Tenney, Jr. W1NLB  
publisher

Hilda M. Wetherbee  
assistant publisher  
advertising manager

**offices**

Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**ham radio** magazine is  
published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048

Subscription rates, world wide  
one year, \$7.00, three years, \$14.00  
Second class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices

Foreign subscription agents  
United Kingdom  
Radio Society of Great Britain  
35 Doughty Street, London WC1, England

All European countries  
Eskil Persson, SM5CJP, Frotunagrand 1  
19400 Upplands Vasby, Sweden

African continent  
Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1973 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office  
Printed by Wellesley Press, Inc  
Framingham, Massachusetts 01701, USA

**ham radio** is available to the blind  
and physically handicapped on magnetic tape  
from Science for the Blind  
221 Rock Hill Road, Bala Cynwyd  
Pennsylvania 19440  
Microfilm copies of current  
and back issues are available  
from University Microfilms  
Ann Arbor, Michigan 48103

Postmaster: Please send form 3579 to  
**ham radio** magazine, Greenville  
New Hampshire 03048

# contents

**6 slow-scan tv test generator**  
A. A. Kelley, K4EEU

**16 carrier-operated relay**  
J. Jay O'Brien, W6GDO

**22 superregenerative receiver for vhf**  
Courtney Hall, WA5SNZ

**26 standing-wave ratios**  
Earl W. Whyman, W2HB

**34 frequency synthesizer  
for two-meter fm**  
William H. Craig, WB4FPK


**52 transistor curve tracer**  
Daniel G. Wright, WA9LCX

**58 antenna-matching systems**  
Robert E. Baird, W7CSD

**64 comparing rf amplifier efficiency**  
Carl C. Drumeller, W5JJ

**68 1973 sweepstakes winners**  
T. H. Tenney, Jr., W1NLB

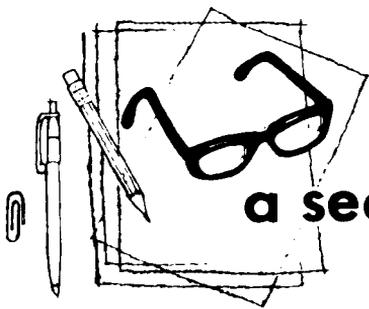**4 a second look**                    **70 ham notebook**  
**110 advertisers index**           **74 new products**  
**99 flea market**                    **110 reader service**



## a second look

by jim  
fisk

**Amateur radio operators**, especially those on two-meter fm, are using more and more dry batteries than ever before. Zinc-carbon batteries rate very high on the list because they are relatively inexpensive and easy to find, although some amateurs use the more expensive but higher powered alkaline-manganese cell, and a few swear by rechargeable nicads. A new dry battery, which will be on the market in the near future, just might revolutionize the whole field of portable dc power.

The new battery, the lithium organic cell, has been receiving enthusiastic reviews from the military, which depends on man-carried batteries for much of its power. The reason for the enthusiasm is that lithium apparently produces a battery with greater energy density than that of any other existing type. Lithium batteries are lighter, have greater power output, can operate over wide temperature ranges and have a remarkably long shelf life -- up to 20 years.

Several companies are currently manufacturing lithium cells, including Mallory, Eagle-Picher and Power Conversion, Inc. Both Mallory and Power Conversion use lithium with a sulfur dioxide electrolyte; experimental Eagle-Picher lithium batteries are based on lithium and a carbon flourine compound in conjunction with an organic electrolyte.

Mallory also has a solid-state lithium battery that uses a metal lithium anode and a metal salt as the cathode. The electrolyte is an electronically insulating solid. Because of the reactive nature of these materials when exposed to the atmosphere, this battery must be hermetically sealed. However, the absence of any

liquid in the battery completely eliminates any corrosion or gassing. In fact, these cells have been stored for long periods at more than 200° F with no detectable loss in energy capacity.

One of the big advantages of the new lithium batteries is their very high energy density. Prior to this, the most energetic batteries have been the silver-zinc units used on the manned Apollo program -- they provided approximately 110 watt-hours per pound per cell. Some of the new lithium batteries can generate 200 watt-hours per pound per cell, a nearly 85% increase. When compared to carbon/zinc and other commonly used batteries, the energy density of the lithium cell is even more impressive. What this means, basically, is that if you presently use 5 pounds of batteries to power your communications gear, lithium batteries would cut the weight in half, approximately.

As far as power output is concerned, the energy from one lithium D-cell at a discharge rate of 1 ampere is equivalent to four mercury-zinc cells, five alkaline-manganese or 30 carbon-zinc cells! The introductory cost for these new lithium batteries is expected to be quite high, about \$9.00 each for D-cells, but that price can be expected to come down as usage and production increase. However, when you consider that one lithium D-cell can provide the same power as 30 carbon-zinc units, the price isn't nearly as astronomical as it first appears. Now, if somebody can figure out a way to recharge them. . .

Jim Fisk, W1DTY  
editor

# From Olson Electronics... AN EXTRAORDINARY PURCHASE OPPORTUNITY

## Olson

MAIL ORDER ONLY

# 189<sup>95</sup>

Plus \$3 Shipping



## 25-WATT SOLID-STATE SECOND GENERATION 2-METER 12-CHANNEL FM TRANSCEIVER

**• Manufactured Prior to Revaluation of the Dollar—Manufacturer's Cost Today Would Be Greater Than Our Selling Price!**

The Unimetrics ULTRACOM-25 is a 144-148 MHz FM transceiver with provision for 12 crystal-control transmit channels and 12 crystal-control receive channels. It features rugged, commercial-quality construction throughout. The dual-gate FET front end results in a sensitivity of better than 0.5 uV for 20 dB quieting. It includes controls for volume, power and squelch, illuminated channel selector, RF power output signal-strength meter, hand-held dynamic mike and mounting bracket. The transceiver is factory equipped for operation on the following frequencies— .94/.94 Simplex, .34/.76 Duplex, .76/.76 Simplex and .34/.94 Duplex. It also has an integral 12VDC power supply—if you purchase it with our antenna below, you'll be ready for immediate mobile

operation. An AC power supply, additional crystals, and touch-tone pad for auto patch are also available. For further information or phone orders, contact Walt Corrigan WB8PCP, Olson Electronics (216) 535-1800.

**Hustler 2-Meter Mobile Antenna.** 5/8 wavelength, stainless steel, 3.4 dB gain. With trunk lip mobile mount.

**Regulated AC Power Supply.** 4 amps, 12 volts. Operate the Ultracom-25 from 117 VAC house current.

**Crystal Certificates.** Fill out and mail to manufacturer with desired transmit or receive frequency indicated. Each certificate good for a single crystal.

**Touch-Tone Encoder.** Ties Ultracom-25 into repeaters with TT auto patch facilities.

**FREE!** 1974 Olson Catalog  
Reg. \$2 W910P DX Calculator  
GIVEN AWAY with first 250  
catalog requests!



**Olson electronics THE VALUE LEADER SINCE 1931**  
260 So. Forge Street, Dept. HH Akron, Ohio 44327



Please send me the following:

- Ultracom-25. DX-067 **192<sup>95</sup>**
- AC Power Supply. BA-234 **29<sup>95</sup>**
- Mobile Antenna. AA-762 **17<sup>95</sup>**
- Phone Patch. DX-076 **44<sup>50</sup>**
- Crystal Certificate. DX-041 **4<sup>95</sup>**

Check or money order for \$\_\_\_\_\_ enclosed. (Total amount plus applicable sales taxes).

- Send me my FREE 1974 Olson Catalog. (DX calculator with 1st 250 requests!)

Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_

Charge Card No. \_\_\_\_\_ Zip

Charge my purchase to  BankAmericard  Interbank N.o.

Master Charge\*

Good Thru Date: \_\_\_\_\_

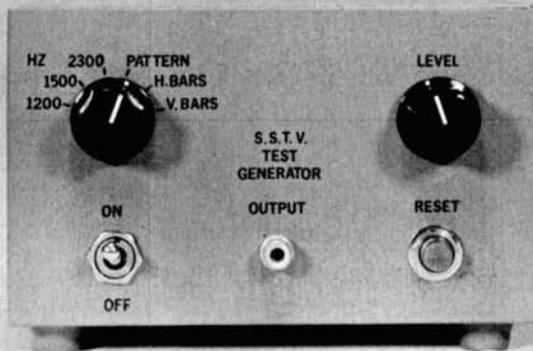

## slow-scan tv test generator

Complete construction  
details for a  
slow-scan tv  
pattern generator  
for troubleshooting  
sstv equipment

Bert Kelley, K4EEU, 2307 South Clark Avenue, Tampa, Florida 33609

Anyone who builds his own slow-scan television equipment soon learns why so many other operators go the commercial equipment route. It's not so much the circuit complexity or parts procurement problems as it is the difficulty of getting the circuits properly adjusted. Almost all the circuits in the sstv monitor have to be operating correctly before you can see any results on the picture tube, so the monitor itself is useless as a test unit.

Some authors have suggested that a tape recorder and a length of audio tape be used as a test signal during adjustments. However, unless this tape is obtained from a sstv manufacturer, the quality is questionable. The sync and video pulses may be off frequency because it is almost impossible to accurately tune in a sstv signal without a monitor. To add to the difficulty, video quality will vary from station to station, and there is usually interference from nearby stations. Any good transmissions will be short so the tape will have to be rewound again and again during use.

What is needed is a sstv test generator which can deliver a continuous high quality test signal and require no atten-

tion. The unit described here can be used to align and test bandpass filters, video discriminators, video amplifiers and sync separators, as well as to check horizontal and vertical sweep linearity and size.

### features

If test equipment is to be useful, it should be accurate. The sync and video frequencies in this sstv test generator are inherently accurate because they are derived from sources that do not vary. Digital logic does the rest. The division ratios are set by selection of IC types and the pin-to-pin strapping. There are no multivibrators that have to be locked in with a pot adjustment.

nominal 1200 Hz. This means that the sstv circuits may be adjusted with confidence in your signal source.

### test signals

A checkerboard test pattern was chosen as the primary test signal because the deep transitions between peak white and picture black will critically test any sync separator circuits. The 60-Hz square wave "video" is an easily recognized pattern that can be traced through the video circuits of the sstv monitor with any scope.

Since the transitions are sharp and clean, the reproduced picture should have sharp, clean edges and this gives an

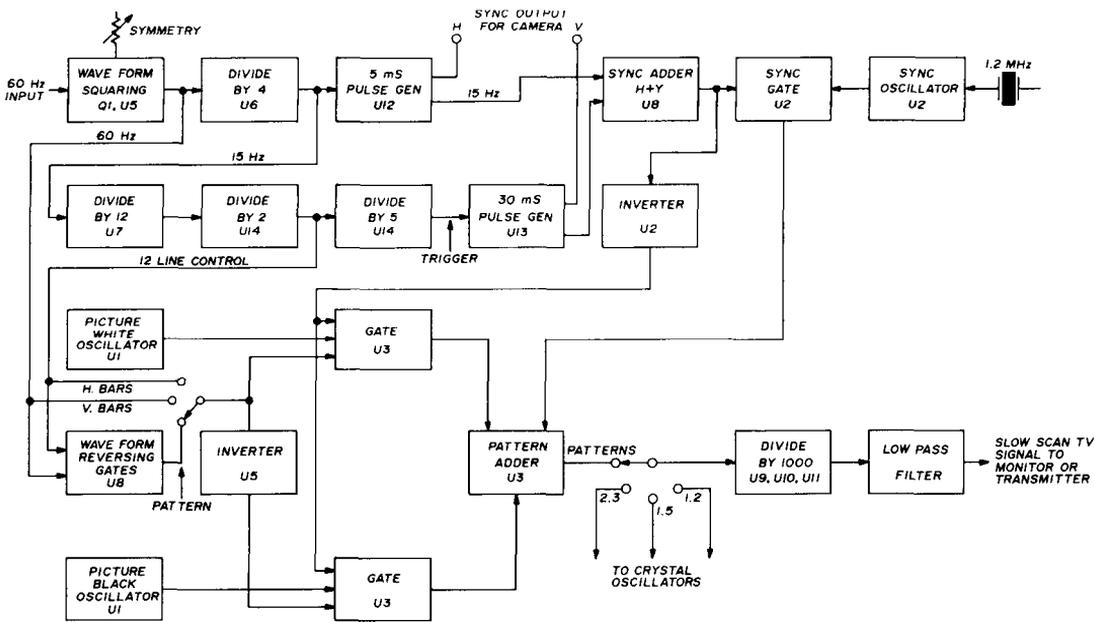


fig. 1. Block diagram of the slow-scan tv test-pattern generator.

The three basic frequencies are derived from crystal oscillators and divided down to the sstv range with digital logic. Digital division removes switching transients and increases the accuracy of the audio tones. The 1.2-MHz crystal may be as much as 1 kHz off frequency, but the sstv sync frequency will still be within 1 Hz of the

excellent indication of picture resolution (see checkerboard photo).

The horizontal and vertical bars are a good indication of sweep linearity although the checkerboard pattern could also be used for this purpose. Since the horizontal and vertical signals are already available in the circuitry, it was only a

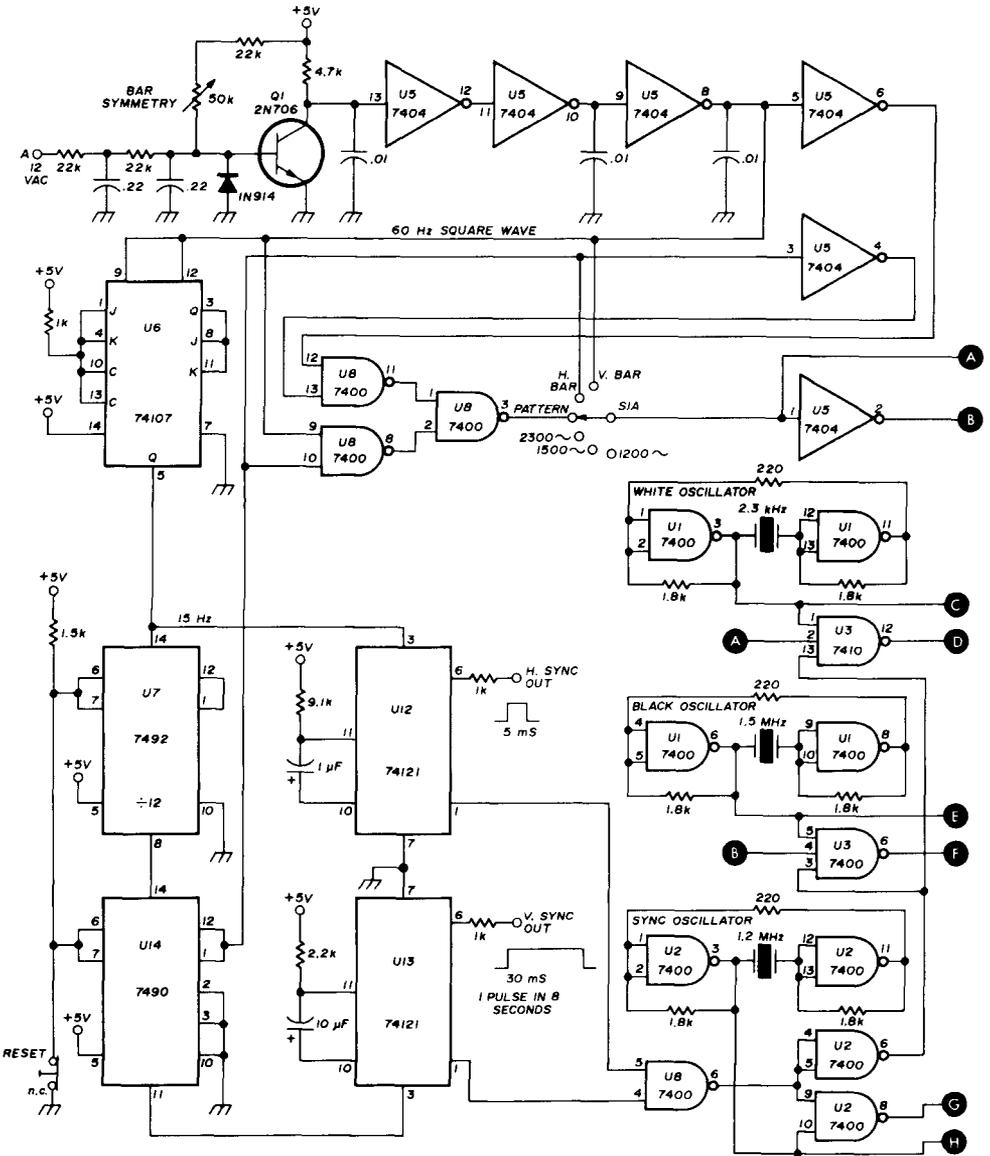


fig. 2. Circuit for the sstv test generator makes extensive use of integrated circuits. Complete unit is housed in a small 3-1/2x6x10-inch Minibox.

matter of adding a selector switch to provide three video patterns as well as the three basic slow-scan audio tones of 1200, 1500 and 2300 Hz. These tones can be used to tune discriminator coils or the all important sync-separator circuit.

### how it works

Refer to the block diagram in fig. 1

and the logic diagram in fig. 2. The 60-Hz signal that drives the test generator is obtained from one side of a 24-volt center-tapped power transformer, filtered, and connected to a transistor, Q1, which turns on for each positive going half-cycle of the waveform. The bias on Q1 is adjusted by a 50k trimmer to make the output symmetrical. The signal is

further squared by three sections of a SN7404 integrated circuit, U5.

The square-wave output from U5 is applied to a JK flip-flop, U6, which divides by four. This is the slow-scan horizontal scanning frequency. However, the pulses are too long so they are used to trigger a 5-millisecond pulse generator, U12. Each pulse generator IC has two outputs. One output is normally low and one is normally high. The positive-going pulse at the Q output is connected to the rear panel jacks for external use.


Two cascaded IC counters, U7 and U14, count the 120 horizontal lines and trigger the 30-millisecond vertical monostable oscillator, U13. Horizontal and vertical sync pulses are then combined in

The lowpass audio filter\* does a good job cleaning up the square wave output from U11. The measured harmonic distortion is only 2.4% at 1200 Hz, 0.53% at 1500 Hz and 0.1% at 2300 Hz.
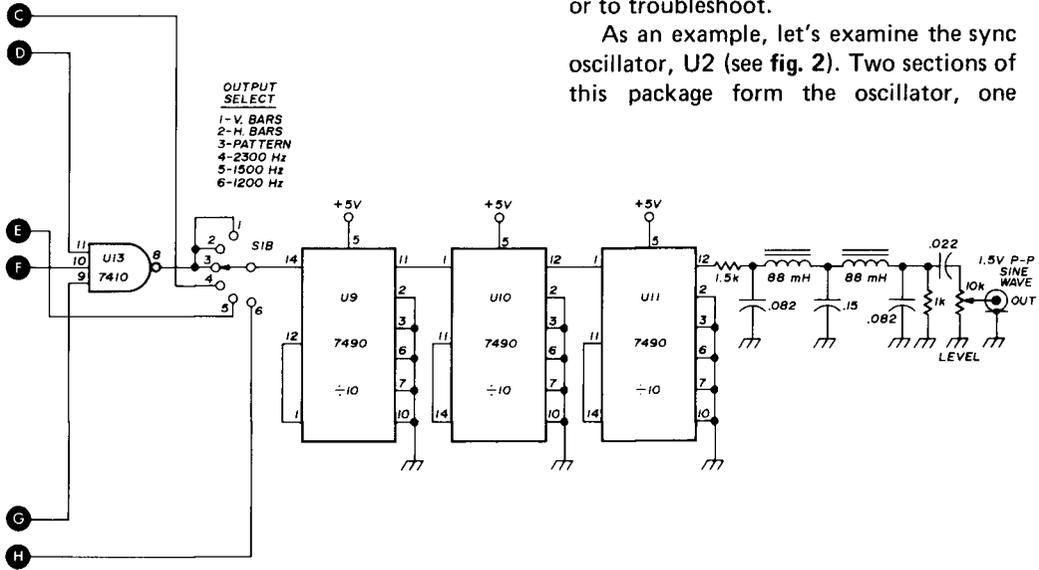
### the digital logic

The TTL logic used in this circuit is fairly fast — much faster than needed. This can be a problem if the filtering is omitted at the base of Q1 or the input to U5 — the unit would become sensitive to power line spikes and result in erratic operation. This logic, however, provides at least two advantages. First, the signal frequencies used in this generator are mostly dc or 60 Hz so any small oscilloscope may be used. Also, most of the circuits are ordinary simple TTL NAND gates, so they are not hard to understand or to troubleshoot.

As an example, let's examine the sync oscillator, U2 (see fig. 2). Two sections of this package form the oscillator, one




the sync adder, U8. The sync signal is connected to signal gates so that sync always has precedence.


The three key frequencies in the generator are provided by continuously operating crystal oscillators that generate rf square waves. These three oscillators are gated so that only one signal may be on at a time. The output is a sequentially switched rf waveform divided down to the audio range by U9, U10 and U11.

section is used as a gate, and one as an inverter. A NAND gate has to have all inputs positive to get a low, or zero, volt output. If pins 4 and 5 of U2 are connected together the gate is converted to an inverter. If, on one section of the

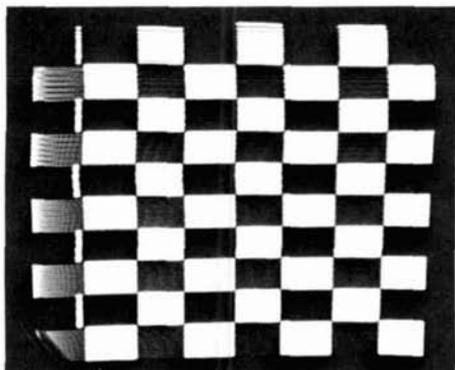\*The 88-mH toroids used in the low-pass filter may be obtained from M. Weinschenker, Box 353, Irwin, Pennsylvania 15642, five for \$2.00, postpaid.



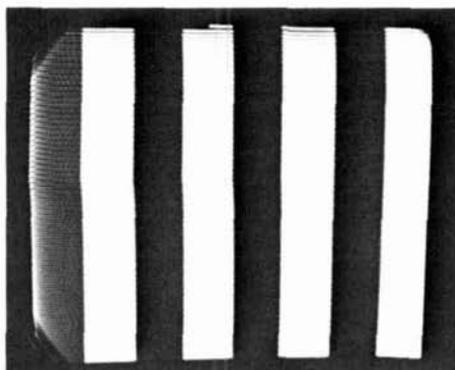Checkerboard test pattern displayed on the K4EEU sstv monitor. The gray bars on left are due to second harmonics of the sync frequency, removed by the test-generator filter, but restored by the limiter in the monitor. This second harmonic, at 2400 Hz, is close to 2300 Hz, sstv picture white.



Vertical-bar test pattern displayed on the sstv monitor. Gray bar on the left side of the monitor tube is caused by the second harmonic of the sync frequency.



Sstv horizontal-bar test pattern, displayed on K4EEU's monitor.

IC, the output is connected back to the input with a resistor, an inverse feedback connection is made which linearizes the gate to a degree and prevents crystal lockup or starting problems.

The output at pin 3, U2, is a 3.5-volt p-p rf square wave, or, more accurately, it is a pulsating dc voltage which rises in a positive direction from the zero baseline up to 3.5 volts and falls again to zero at an rf rate. If this square wave is applied to pin 10, U2, it will pass through, inverted, to pin 8 provided the gate is enabled by making pin 9 positive. Normally, however, pin 9 of U2 is at zero volts and the gate is inhibited. Therefore, the output at pin 8 is high and stays high regardless of what signal is applied to the input, pin 10. To turn off any input to a NAND gate, any of the other inputs can be made low.

The sync-pulse monostable outputs at pin 1 of U12 and U13 are normally high; both are connected to the sync adder gate, U8. With both inputs high, the output at pin 6 of U8 is low. If either input to this gate goes low, as during a horizontal or vertical sync pulse, pin 6 goes high for the duration of that pulse. This enables pin 9, U2, and the sync rf passes through the gate.

When any gate is cut off, the output is high, so several such gates may be connected to a mixer such as U3 without inversion. When U2, pin 9, is high, turning on the sync, U2, pin 6, is low, or inverted, which inhibits the other two gates and prevents picture frequencies from passing during the sync interval. Pin 2, U5, is connected to pin 4, U3, so that either the black or white picture gates may be enabled, but not both at the same time.

The waveform reversing gate, U8, reverses the phase of the 60-Hz square wave every twelve picture lines. The output appears alternately at pin 8 or pin 11 of U8, but not both at the same time.

## construction

Most of the components are mounted on a 5½ x 8-inch circuit board with the

rest of the parts mounted on the ends of a small 3½ x 6 x 10-inch Minibox. A LM309K voltage-regulator IC is directly bolted to the rear of the Minibox, which is used as a heat sink.

Complete information on board layout is given in fig. 6. The circuit trails are

the input of the LM309K voltage regulator is properly connected before turning on the supply. Verify the 5-volt output before wiring in any of the TTL devices (it is possible to have 18 volts unregulated where there should be only 5 volts). The regulator needs no adjust-

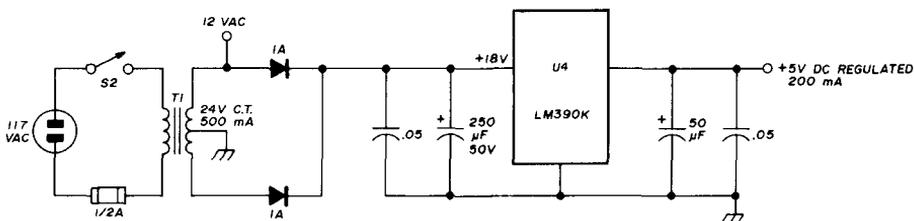


fig. 3. Power supply for the sstv generator. LM309K voltage-regulator IC uses one end of the Minibox enclosure for a heat sink.

drawn on the copper with a RMP-700 Kepro resist pen, or one similar. A parts list and epoxy, plated circuit board is available from the author for \$10.00 postpaid in the United States.\*

Inexpensive crystals are available from JAN crystals from stock in the FT-243 holder, but I prefer the HC-6/U crystal holder since it takes less space on a printed-circuit board. The tolerance of the crystal is not critical; if you wish, however, 0.005% tolerance custom ground crystals can be obtained.


Since this is a fairly complex construction project, I always build in sections and debug if necessary, starting at the power supply, fig. 3. Make sure

\*A kit of parts is available from Truman Boerkoel, K8JUG, Stotts-Friedman Company, 108 N. Jefferson Street, Dayton, Ohio 45402.

fig. 4. Output waveforms of the slow-scan television test generator.

ments and has built-in current limiting so that, if the 5-volt line is shorted, the current is held to about 1 ampere, protecting the power supply.

The sync generator section can now be built and checked out with an oscilloscope. There should be a square wave at the collector of the transistor Q1 at the input to U6, pins 9 and 12. The pulse width at pin 6, U12, should be 5 milliseconds. This can be measured with suf-

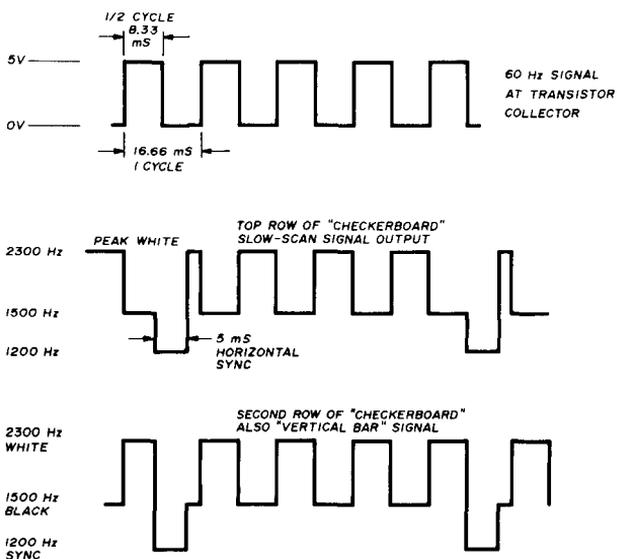


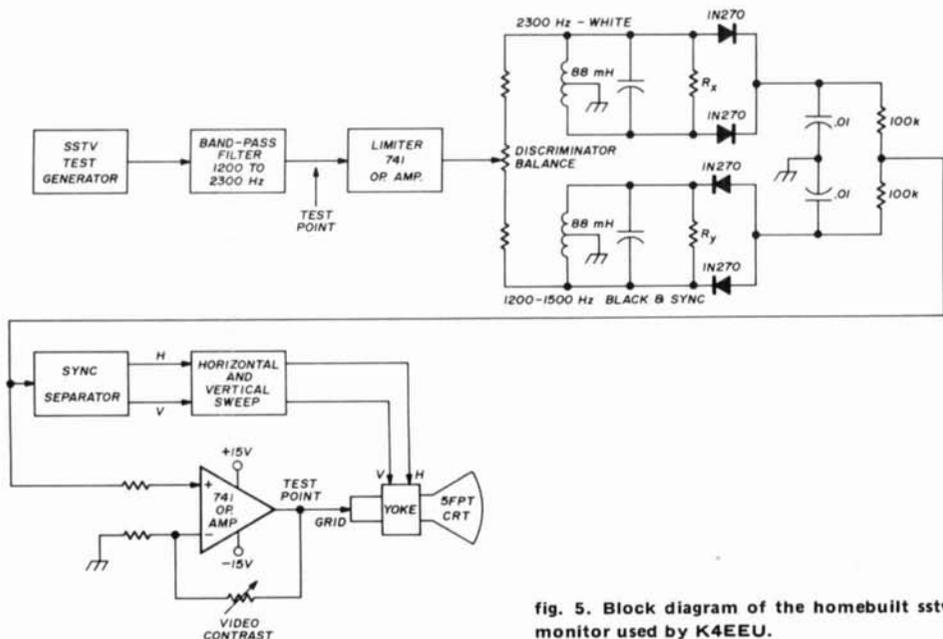


fig. 5. Block diagram of the homebuilt sstv monitor used by K4EEU.

ficient accuracy by referencing the scope to one cycle of the 60-Hz signal which has a time interval of 16.66 milliseconds. The sync pulse width should be about one-third the length of one 60-Hz cycle (see fig. 4).

The vertical sync pulse is a little more difficult to measure because it occurs

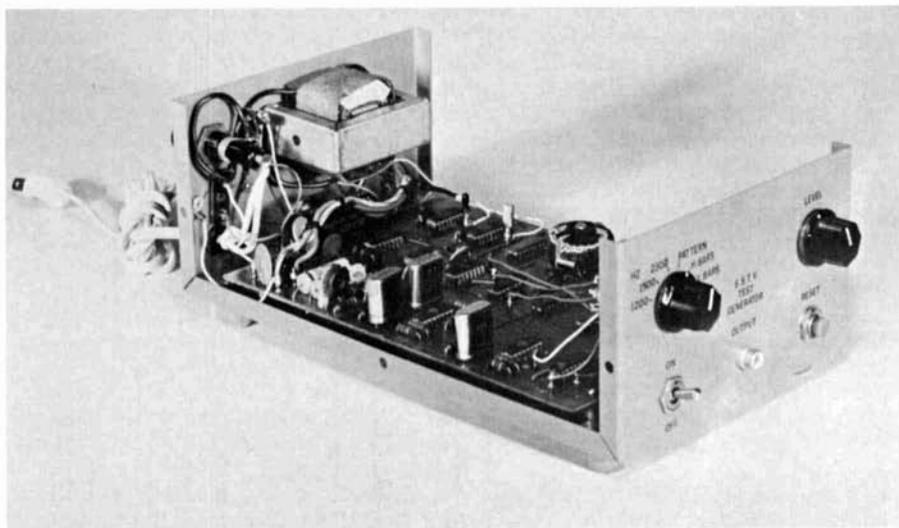once every eight seconds. This may be speeded up, either by repeatedly operating the *reset* button or by temporarily rerouting the lead that runs from pin 3, U13, to U14 so that it is connected directly to pin 5, U6. The pulse from U13 will then be at a 15-Hz rate and much easier to measure on a scope.



Construction of the slow-scan tv test generator.

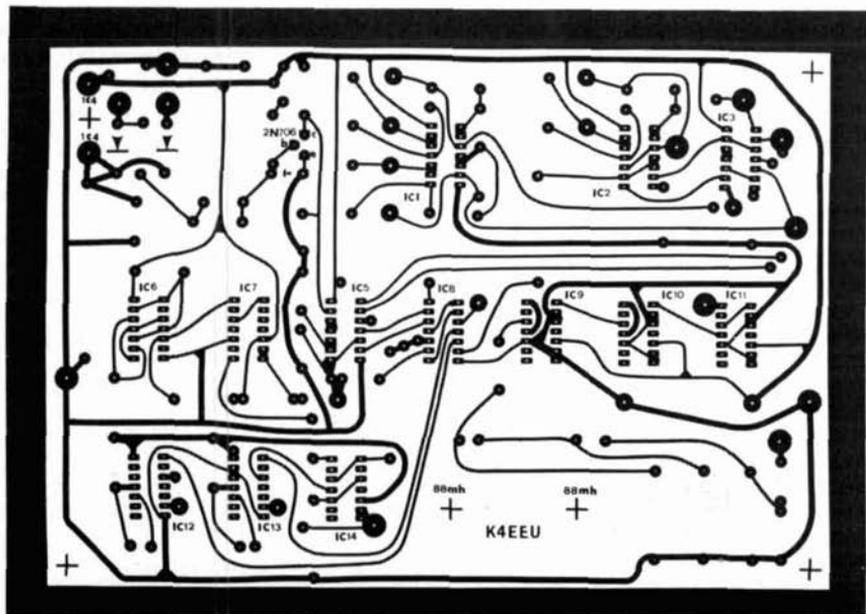


fig. 6. Layout for the printed-circuit board for the sstv test generator. A circuit board and parts list is available from the author.

The pulse width should not be less than 30 milliseconds. Two 60-Hz waves are about 33-milliseconds long and this is close enough for practical purposes. The pulse widths should be sufficiently close without any circuit changes. However, if they are not, the pulse width can be adjusted by changing the value of the resistor connected to pin 11 of the appropriate 74121 IC.


The pattern generator can be checked out by wiring in the waveform reversing gate, U8, and checking the waveform at pin 3. Externally sync your scope and see if the polarity of the waveform is reversing about once a second.

If you cannot observe the crystal oscillators on a scope, the signal can be detected on a broadcast receiver. Of course, if you have an output at the filter, it's a good indication that the crystal oscillators are operating all right.

The foregoing is not intended to emphasize the complications but to be of assistance if troubleshooting becomes necessary. Usually ICs can be wired into a circuit as so many building blocks, and, if wired correctly, everything works.
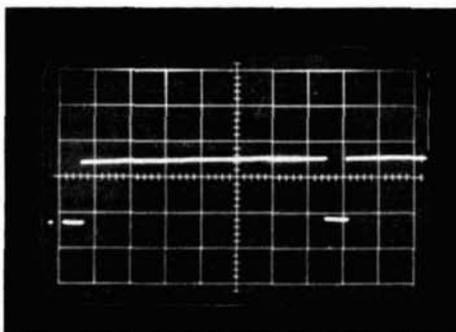
## operation

The sstv test generator can be used with an oscilloscope to check the slow-scan signal at the different points in the monitor. If you want to see if the input bandpass filter is operating correctly, put the test generator switch on pattern or bars and look at the output of the filter with a scope. The amplitude should be the same for the three frequencies. Similarly, the demodulated composite video signal can be seen at the discriminator




Clipped and restored horizontal sync pulse taken from the sync separator of the K4EEU sstv monitor.

output and traced up to the picture tube grid.

The sync separator circuit in the monitor should show a clean sync pulse with no interference between the sync and the black video pulses. This circuit can be

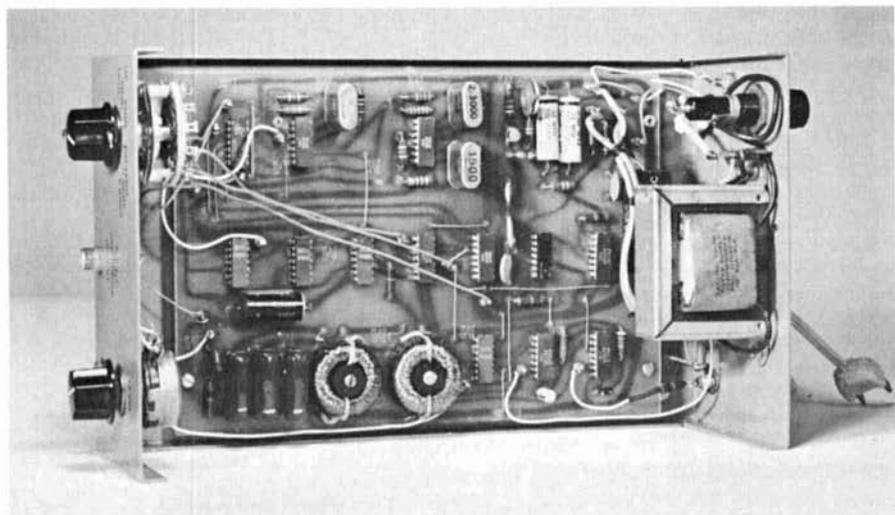then the exact value of the damping resistors selected by viewing the demodulated pattern on a scope. The correct resistor will result in minimum ringing and best square wave response, and can be found in less time than it takes to



Complete sstv test generator is built on 5-1/2x8-inch printed-circuit board and installed in a 3-1/2x6x10-inch Minibox. LM309K voltage-regulator IC is mounted on the rear of the Minibox.


optimized by setting the selector to 1200 Hz and tuning.

The sstv monitor may use a discriminator circuit similar to that used in a RTTY demodulator (fig. 5). The discriminator coils can be individually set on frequency with the test generator and

tell about it by using variable pot (about 50k). The sync pulse waveform is relatively unimportant here but it should be separated from picture black. The sync circuit will clean up the sync pulse.

The reset button was installed on the test generator so that a vertical pulse could be obtained immediately at any time when working with a sync circuit in a monitor. Otherwise, the pulses are separated with an 8-second time interval. If this button is omitted, pins 6 and 7 of U7 and U14 must be grounded or the dividers will not operate.

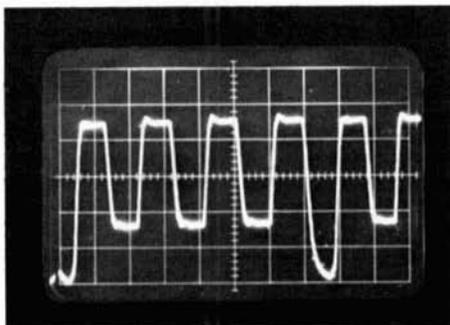Once you build this sstv test set, you will wonder how you ever got along without it. At my station it revived a faltering monitor project. With only a few hours work a trouble in the monitor sync separator was cleared and I started receiving good pictures.



Demodulated test-generator signal at the output of the monitor discriminator.

ham radio

# If you like 2 METER . . .

## YOU'LL LOVE OUR



**10 OR 1 WATT POWER OUT/SWITCH SELECTABLE /  
FULL 12 CHANNEL TRANSMIT AND RECEIVE CAPABILITY**

All the advantages of 2 Meter FM . . . away from the crowds. With the HR-220, Regency pioneers the way to put you out on the most exciting ham band ever. The HR-220 is equipped with all the quality features you demand—compact design, big signal power at low current drain, HI/LO power switch, crystal clear reception, superb sensitivity *and* low price.

**\$239<sup>00</sup>**

AMATEUR NET

includes plug-in ceramic mike, dash mounting bracket and factory installed transmit and receive crystals for 223.50 MHz.

  
the first name in solid state

**THE FM LEADER IN 2 METER AND 6 METER . . . AND NOW 220 MHz**

# operational-amplifier relay for motorola receivers

Complete  
construction details  
for the SOOPAR —  
a Signal-Operated  
Operational Relay

The SOOPAR, A Signal-Operated Operational Amplifier Relay, is the answer to your carrier-operated relay troubles. This circuit uses an inexpensive integrated circuit, an inexpensive, easy-to-obtain relay and a few parts to provide you with a reliable unit that can be adjusted to fit your needs for receiver control of an external device. The external device could be a light to indicate the receiver is receiving a signal, a Transmitter in a repeater system, or control functions such as a garage door opener, etc.

## squelch circuit

The Motorola compensated squelch circuit, diagrammed in **fig. 1**, operates to silence the speaker when no signal is present. The SOOPAR derives its input signal from this squelch circuit.

The squelch circuit operation is as follows: Signal and noise from the antenna, mixers and the i-f amplifier stages are fed into the limiter stages which are driven into saturation, thus limiting the limiter output to a constant voltage. This output voltage, at the last i-f, is the same whether it is signal or noise or any proportion of both.

The action of driving the last limiter stage into saturation generates limiter grid current and, thus, a negative voltage at the limiter grid. This grid voltage is picked off, filtered and used as bias by the later squelch stages. The i-f output of the limiter is connected to the discriminator stage where it is converted to audio. The voice-audio components are amplified by the audio amplifiers and drive the speaker when the first audio stage is unsquelched.

Audio components produced by the discriminator that are above the voice-range (noise) are filtered out from the voice-range components and amplified by the noise amplifier. The noise amplifier gain may be adjusted by a variable resistor in the cathode circuit; this variable resistor is the squelch control.

The output of the noise amplifier is rectified by the noise rectifier. The positive-going dc output of the noise rectifier

J. Jay O'Brien, W6GDO, 6606 Fifth Street, Rio Linda, California 95673

is proportional to the noise output of the noise amplifier. That is, more noise into the rectifier produces a more positive dc voltage out of the rectifier.

The dc output of the noise rectifier is connected in series with the negative bias obtained from the limiter stage and is

sation built into the biasing arrangement. When the drive to the limiter stage is reduced as a result of tube aging or low supply voltage, the negative bias derived from the limiter is reduced proportionately. The noise component of the discriminator output is also reduced with tube

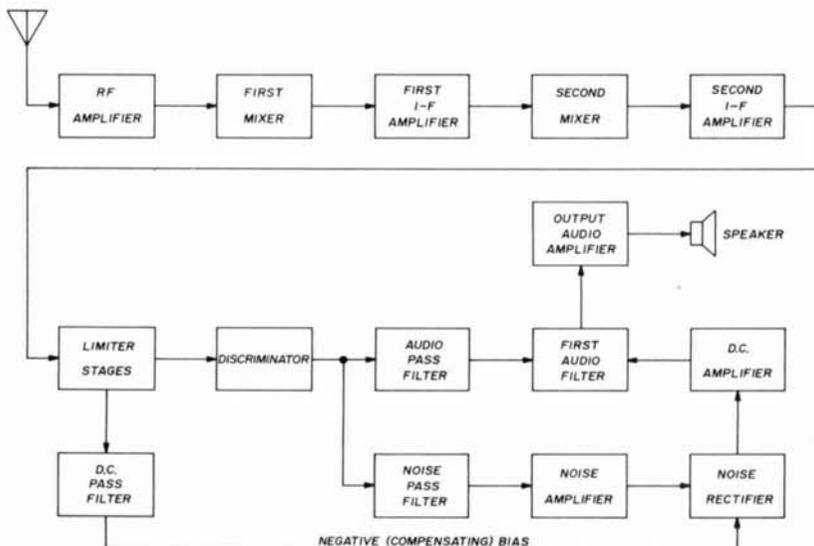


fig. 1. Block diagram of a typical Motorola receiver using a Motorola compensated squelch circuit.


applied to the dc amplifier grid. The dc amplifier turns the first audio amplifier stage on and off. Typically, the dc amplifier keeps the first audio amplifier turned off (squelched) whenever its dc input from the noise rectifier is zero volts or more positive.

The dc amplifier turns the audio amplifier on when the dc voltage applied to it from the noise rectifier becomes more negative than zero volts. This condition occurs when the noise voltage is removed from the noise amplifier and rectifier. This "quieting" occurs when a carrier is received by the receiver.

This circuit has a measure of compen-

aging or reduced supply voltage, resulting in a lower positive going noise rectifier output. Since these two voltages are of opposite polarity and are connected in series, the result is a negligible change in

photos by Mike Keller, WA6RWR

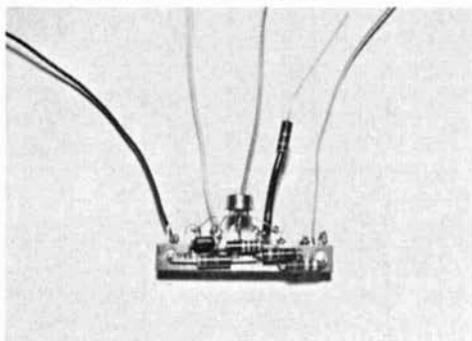

The SOOPAR, ready to be installed and connected to an external relay.

**Editor's note:** This is more than an article on a signal-operated op-amp relay — it also presents a comprehensive review of squelch operation in Motorola tube-type fm receivers.

the voltage fed to the dc amplifier from the noise rectifier. Thus, supply voltage changes and tube aging tend to be automatically compensated for by this circuit.

When the squelch control is set for reception of a slightly noisy but useable signal, the voltage presented to the dc amplifier when no signal is being received is approximately +5 volts.

### tube-type carrier-operated relays

Tube-type carrier-operated relay (COR) circuits, when used, are connected to sample the voltage presented to the dc amplifier. A representative circuit is shown in fig. 2.

The signal voltage applied to the grid of the dc amplifier is sampled through R1 and connected to the grid of the first half of the COR tube which goes into conduction whenever the sampled voltage is more positive than the 1.8-volt cathode bias developed by R2 and R3. When the first half of the tube conducts, the voltage at its plate approaches zero. This is connected to the grid of the second half of the tube, which, under this condition, draws little current. The voltage drop across relay K1 is 27 volts or less, and K1 is released.

When the receiver is un-squelched, the voltage presented to the dc amplifier and sampled by the COR goes negative. This causes the current drawn thru R4 by the first half of the COR tube to reduce. As this current reduces, the voltage drop

across R4 reduces, making the voltage on the grid of the second half of the COR more positive. When this voltage rises to about 50 volts, the neon tube fires, preventing the voltage from reaching a higher potential that could damage the tube.

When the voltage at the second grid goes more positive, the second half of the COR draws more current through K1. When the current is sufficient to produce a 35-volt drop across K1, it closes, actuating the external device.

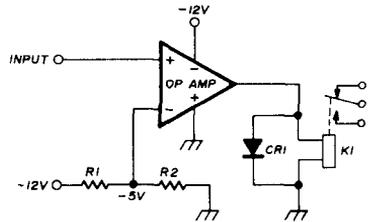


fig. 3. Circuit for using an operational amplifier IC to operate a relay.

### cor disadvantages

Users of conventional tube type CORs will agree that the COR is the real trouble spot in a repeater receiver. Part of this is due to the fact that the voltage across the relay does not go from zero to "all on" when a signal is received. Rather, the relay operate and release voltages play an important part in COR operation. As the COR tube ages, the voltage presented to the relay changes, thus effectively changing the COR sensitivity. A circuit that would only produce two relay voltage conditions, full on and full off, would eliminate most of these relay problems.

Another problem is the inconsistent loading effect that the COR has on the receiver squelch circuit. When the squelch voltage is more positive than the voltage on the cathode of the first half of the COR tube, the grid and cathode act like a diode and conduct current, placing a 1-megohm load on the squelch circuit and reducing its adjustment range. Below this voltage, the current is negligible unless the COR tube becomes gassy; when this happens, the effect is unpredictable.

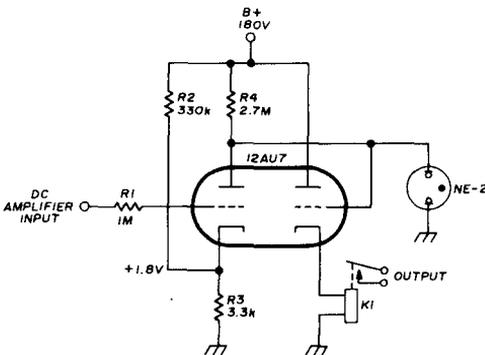


fig. 2. Motorola carrier-operated relay circuit. Relay K1 is an 8000-ohm relay which picks up at 39 volts and drops out at 27 volts.

It is difficult to adjust this type of tube COR to open and close in the correct relationship to the audio squelch. The proper relationship is one where the audio squelch opens just before the COR closes as a received signal is slowly increased in level, and where the COR opens just before or at the same time as the audio squelch closes when the signal is decreased. This is almost impossible to maintain with a tube-type COR, even if an additional control is added to independently adjust COR sensitivity.

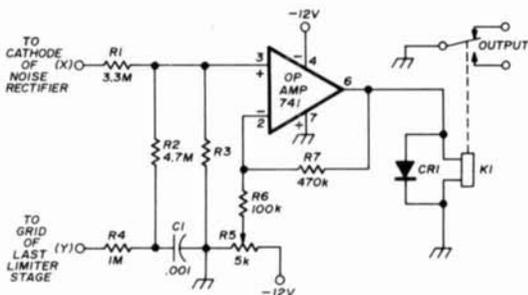


fig. 4. Schematic for the SOOPAR, signal-operated operational relay. Relay K1 is a Sigma 65FP1A. Diode CR1 is silicon. See table 1 for value of R3.

## op-amps

Operational amplifiers are miracle devices that seem to perform magic. In the case of the SOOPAR, an op-amp is used as a dc amplifier with almost infinite gain. In this case the op-amp looks at two input voltages; one constant (adjustable) and one variable with signal level. When the variable input is equal or more positive in voltage than the constant, the output from the op amp is in the "off" condition.

When the variable input is slightly negative as compared to the constant, the output of the op amp changes to the "on" condition. A 10-volt change (from 2 to 12 volts) at the output is produced by an input voltage change of a hundredth of a volt or so. The op amp in the SOOPAR is capable of directly operating a relay; of course, this voltage change can be adapted to solid-state circuits that do not use any relays.

## op-amp relay


A simple circuit using an op-amp to sense an input voltage and operate a relay is shown in fig. 3. A negative 12-volt supply is connected to the op-amp and to a voltage divider, R1 and R2. The inverting input of the op-amp is connected to the junction of R1 and R2, whose values are chosen to present a bias potential of -5 volts. The non-inverting input of the op-amp is the input terminal of the op-amp relay.

If the input voltage is between zero and -5 volts, the relay is released. When the voltage is raised above -5 volts, the relay is operated. To prevent damage to the op-amp the input voltage should not exceed the supply voltages. The current drawn by relay K1 must not exceed the rating of the op-amp. Diode CR1 prevents damage to the op-amp from reverse voltage spikes generated by K1 when it is released.

## soopar

The signal-operated op-amp relay or SOOPAR is an adaption of the op-amp relay circuit and is shown in fig. 4. Resistor R5 takes the place of R1 and R2 in fig. 3 and is set, nominally, to about -5 volts. R1 is connected to the squelch circuit of the receiver, and R4 picks off the limiter voltage. C1 and R4 act as a filter to remove the i-f signal voltage present at the grid of the last limiter.

Resistors R1, R2, R3 and R4 make up

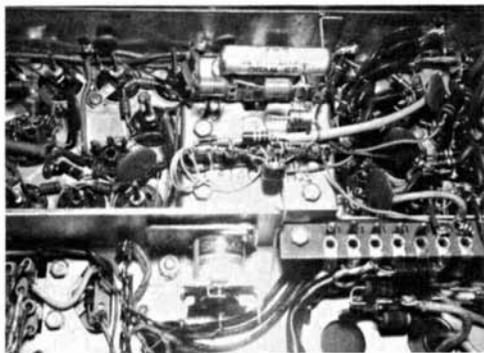


A SOOPAR and power supply mounted on the Permakay filter of a Motorola Sensicon G receiver. The relay is shown mounted on the power-supply chassis.

a complex voltage divider; their values are chosen to present a potential of about -5 volts to the non-inverting input of the op-amp. The values are also chosen to limit the maximum voltage presented to the op-amp to less than the +12-volt op-amp supply voltage.
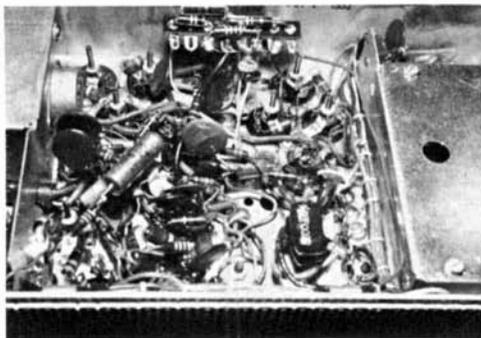
## hysteresis

The advantage of the SOOPAR to turn on and off with a very small input voltage change is a disadvantage when very weak



A SOOPAR mounted on the side of the chassis of a Motorola Sensicon A receiver.

signals are received. The relay will chatter, going on and off rapidly. The tube-type COR avoids this due to the inherent magnetic "hysteresis" in the relay; that is, once the relay is operated, you can reduce the voltage across the relay somewhat and it will remain energized.

The relay's pick-up and drop-out voltages are a major factor in the proper operation of a tube-type COR. Resistors R6 and R7 are added to the SOOPAR to introduce electrical hysteresis. The bias presented to the inverting input of the op-amp is raised when voltage is applied to K1 by the op-amp. The amount of this change in potential is determined by the values of R6 and R7.

The net effect of the hysteresis is to cause the relay to release at a SOOPAR input voltage lower than the input voltage required to operate the relay. For example, if the relay drops out at -3 volts (at the non-inverting, or + op-amp input),

and picks up at -4 volts, it will release again at -4 volts if there is no hysteresis. By adding hysteresis, it drops out at -3.5 volts.

Incidentally, if you don't want it, this action is called "slop" or "backlash;" it is called "hysteresis" if you do want it. If more hysteresis is desired in the SOOPAR, raise the value of R6 - try 220k or 330k. For less hysteresis try 47k; if no hysteresis is desired, disconnect R7 and short out R6.

## receiver connection

Typical connections to Motorola receivers are shown in table 1. Resistors R1 and R4 should be connected directly to the tube socket pins shown, and C1 should be connected directly to R4 and ground. The lead length from R1, R2 and R3 to the op-amp should be kept at a minimum to reduce stray rf pickup. The op-amp itself should be mounted inside the receiver; relay K1 may be mounted externally.

If you adapt the SOOPAR to a different receiver, connect R1, R2, R3, R4 and C1 before connecting the op-amp. Measure the voltage at the junction of R1, R2 and R3 with a vtvm or high-impedance fet volt-meter. It should be between -3 and -6 volts with the receiver set for nominal squelch sensitivity, and should not exceed -12 volts with a saturating signal applied to the receiver input. If necessary, adjust R3 (and perhaps R2) to satisfy these conditions, then

table 1. Connection points for installing the signal-operated operational relay into Motorola fm receivers.

typical Motorola receiver	lead X	lead Y	R3 value
Sensicon A high-band PA 8433/8476	V309 pin 1	V312 pin 5	2.2M
Sensicon G high-band TA 140	V110 pin 1	V113 pin 7	not used
T44 type uhf rcvr TA 141	V14B pin 8	V12B pin 2	2.2M

connect the remainder of the SOOPAR circuit.

### adjustment

The threshold adjustment is R5. First adjust the receiver squelch control to quiet the receiver, then adjust R5 to the point where K1 just releases. This adjustment should suffice for most applications, but R5 may be trimmed as necessary to track the SOOPAR operation with the audio squelch.

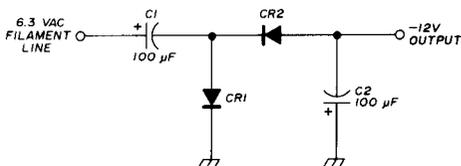


fig. 5. Power supply for the op-amp relay. Diodes CR1 and CR2 are silicon units.

### construction

As long as the input leads are kept short, the layout of the SOOPAR is not critical. Small 8-lug terminal strips have been used by some builders. Spare terminals on existing terminal strips within receivers have been used by others. The recommended relay, a Sigma 65FP1-12DC, is a 90-mW, 12-volt dc relay with a 1600-ohm coil. These are available from Allied Radio and others for less than \$3.00 each.

A simple voltage-doubler power supply for the SOOPAR is shown in fig. 5. Any small power diodes may be used for CR1 and CR2, and any value of capacitance of 100 µF or more will suffice for C1 and C2. This power supply may be built on a small multi-lug terminal strip similar to the SOOPAR.

### conclusion

Several SOOPARs are presently in use in Northern California repeater receivers, including the vhf input receivers of the Mt. Vaca Radio Club's repeaters. This circuit has proven itself reliable under temperature extremes and continuous usage.

ham radio

## CRYSTAL FILTERS and DISCRIMINATORS

by K.V.G.

1 27/64" x 1 3/64" x 3/4"

### 9.0 MHz DISCRIMINATORS

XD9-01	± 5 kHz	RTTY	\$21.10
XD9-02	± 10 kHz	NBFM	\$21.95
XD9-03	± 12 kHz	NBFM	\$21.10

### 9 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$3.35
XF901	8998.5 kHz	USB	\$3.35
XF902	9001.5 kHz	LSB	\$3.35
XF903	8999.0 kHz	BFO	\$3.35
F-05	Hc25/u	Socket	.50

### 9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$27.95
XF9-B	2.4 kHz	SSB RX	\$39.75
XF9-C	3.75 kHz	AM	\$42.85
XF9-D	5.0 kHz	AM	\$42.85
XF9-E	12.0 kHz	NBFM	\$42.85
XF9-M	0.5 kHz	CW	\$29.95

## VARACTOR

### VHF TRIPLERS UHF

#### MMv 432 \$69.95

INPUT: 140-153 MHz  
20 watts max.

OUTPUT: 420-459 MHz  
12 watts min.

Size: 4 1/2" x 2 1/2" x 1 1/4" + Connectors

#### MMv 1296 \$79.95

INPUT: 420-459 MHz  
12 watts max.

OUTPUT: 1260-1377 MHz  
6 watts min.

Size: 4 1/2" x 2 1/2" x 1 1/4" + Connectors

**si**

SPECTRUM  
INTERNATIONAL  
BOX 1084 CONCORD  
MASSACHUSETTS 01742



## low-voltage superregenerative receiver for vhf

This superregenerative receiver tunes from 100 to 170 MHz and operates from a single flashlight battery

Courtney Hall, WA5SNZ, 7716 La Verdura Drive, Dallas, Texas 75240

This receiver was built as an experiment to investigate the quality of reception that could be expected from various modulation modes using a superregenerative detector, and to experiment with the diode tank loading technique discussed in previous articles.<sup>1,2</sup> Another design goal was to operate the receiver from a single flashlight battery and to achieve long battery life at low cost. The frequency range of approximately 100 to 170 MHz covers wide-band fm in the fm broadcast band, a-m in the aircraft band and narrow-band fm in the public service band.

Since superregenerative detector theory is covered in the above referenced articles and elsewhere, I will not go into that here.

### circuitry

As shown in fig. 1, the receiver consists of a superregenerative detector followed by a three-stage audio amplifier which drives a pair of 2000-ohm headphones. Regeneration is controlled by varying the base bias on the detector transistor. A two-section RC filter between the detector and audio amplifier

attenuates the detector's quench frequency, and each stage of the audio amplifier is "rolled off" with a 180-pF feedback capacitor to prevent response at the quench frequency.

The TIS97 transistors used in the audio amplifier have dc current gains of around 500; if lower beta transistors are substituted, the 150k base-bias resistors

is housed in an LMB 555N aluminum cabinet, which is a five-inch cube. A piece of copper-clad board is held on the inside of the front panel by the tuning capacitor's mounting bushing. This provides a ground plane to which all of the detector's ground connections are soldered.

All detector wiring should be as short and direct as possible. In my receiver

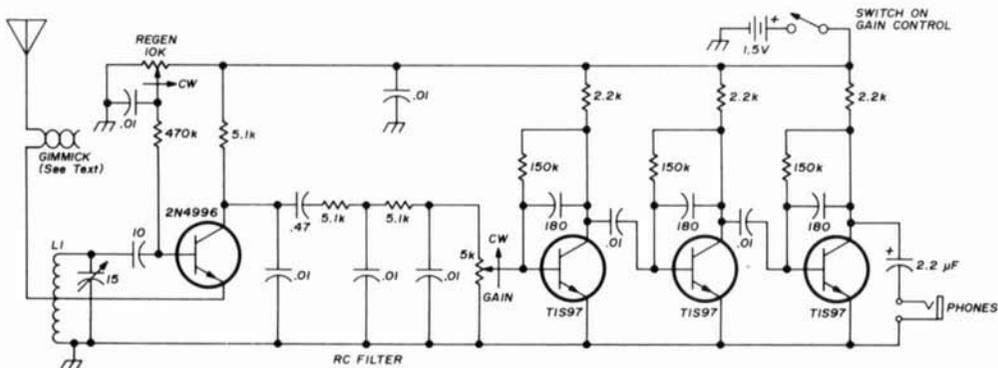


fig. 1. Schematic of the low-voltage superregenerative receiver that tunes from 100 to 170 MHz. Coil L1 is 3 turns Mini-ductor stock, 1/2" diameter, 8 turns per inch.

may need to be decreased to set the dc collector voltage at about 0.8 volt. Since current drain is about one milliampere, an AA penlight cell could be used instead of the D cell I used.


The tuning capacitor is a Hammarlund HF-15-X having about 15-pF maximum capacitance; the coil is three turns of Miniductor stock, 0.5 inch diameter, 8 turns-per-inch. The emitter and antenna are connected to the center of the coil. I found that if the antenna was coupled too tightly to the tank circuit, the detector would not operate properly at the high end of its frequency range.

I used a gimmick capacitor made from two pieces of number-22 hookup wire twisted together for a length of 1.25 inches and inserted between the antenna terminal and the coil. This seemed to provide a good compromise between sensitivity and stable operation when using a three-foot wire antenna.
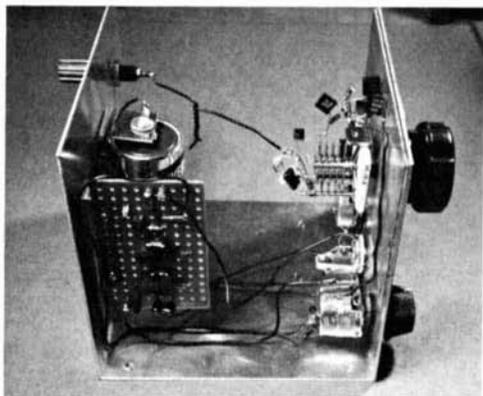
## construction

The entire receiver, including battery,

most of the detector components are just soldered together and supported by their leads. The audio amplifier is assembled on a piece of perf-board mounted on the rear panel with the battery holder and antenna terminal.



Construction of the vhf superregenerative receiver. Receiver components are mounted with short, direct leads around tuning capacitor on front panel. Audio power module is mounted on perf board in rear of enclosure.

## operation


For best results, the regeneration control should be advanced to a point just above the spot where the rushing sound begins; this adjustment is not critical, but may need to be varied somewhat with tuning. The receiver should be tuned slightly to one side of an fm station's frequency to achieve slope detection.

Using a three-foot wire antenna, local fm broadcast stations and aircraft came in loud and clear; the aircraft signals are a-m while the fm broadcast signals are wide-band fm. Narrowband fm signals in the public-service band were difficult to

and produce plenty of room volume. Although I have used only 2N697s and 2N5449s, the circuit should work well with almost any medium power silicon npn devices.

Allied Radio part numbers are shown for the transformers, but any of the less expensive imported transformers having the same impedance levels should be ok. No volume control is included because I

fig. 2. Simple audio power amplifier may be used with any small receiver which is capable of driving a pair of 2000-ohm headphones.

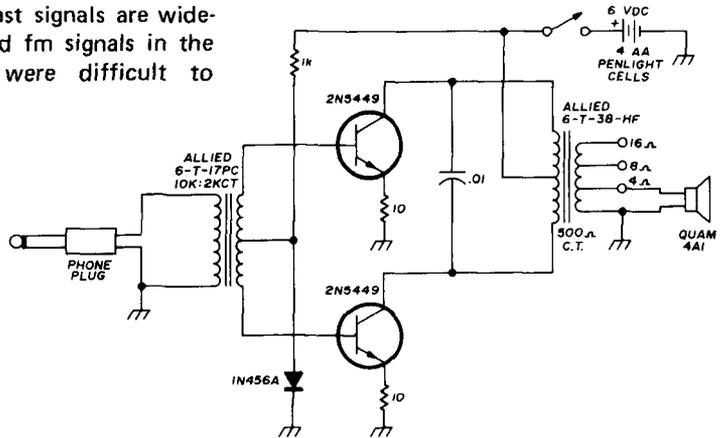

copy; although their carriers can completely quiet the receiver's noise, their low deviation doesn't provide much audio output from the detector.

I experimented with germanium diodes connected across part or all of the tank coil as described in the referenced articles, but I was unable to detect any improvement in performance.

## audio power amplifier

Most of my audio circuits are designed to drive 2000-ohm headphones; these phones are easy to drive, and the rest of the household doesn't want to listen to all that shortwave racket, anyway. At times, however, it's desirable to have speaker capability so I built a simple power amplifier which plugs into the phone jack (fig. 2). It is mounted with a 4-inch speaker and batteries in a 6x6x4-inch LMB 664 aluminum box.

Any circuit which will drive a pair of 2000-ohm headphones will drive this unit

usually have one on the equipment designed to drive the phones. Battery drain is 10 mA or less, depending on output level, and four AA penlight cells connected in series will last a long time.

## conclusion


Superregenerative receivers can be designed to operate from a 1.5 volt dc supply; they are suitable for a-m and wideband fm reception, but their performance with narrowband fm is poor. Operation of these detectors from a very low voltage source can decrease their radiated power and lessen the possibility of interference to other nearby receivers.

## references

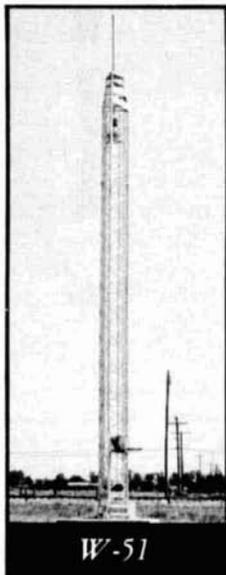
1. C.L. Ring, "Optimizing the Superregenerative Detector," *ham radio*, July, 1972, page 32.
2. A. Iwakami, "Improved Superregenerative Receiver," *ham radio*, December, 1970, page 48.

ham radio


**NOW.**  
*Top-of-the-Line*  
**Tri-Ex Towers**  
*for HAM operators*  
*at basic prices!*




**W-51**

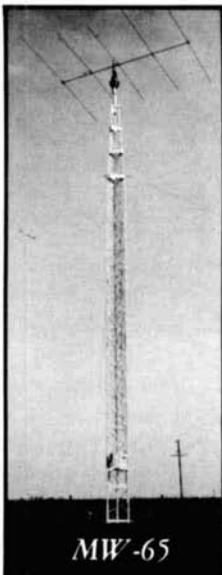


**MW-65**

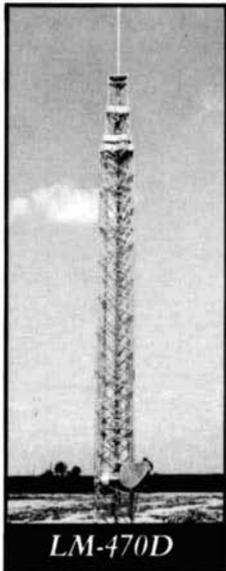

**LM-470D**

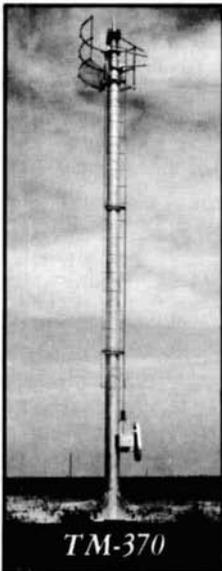

**TM-370**

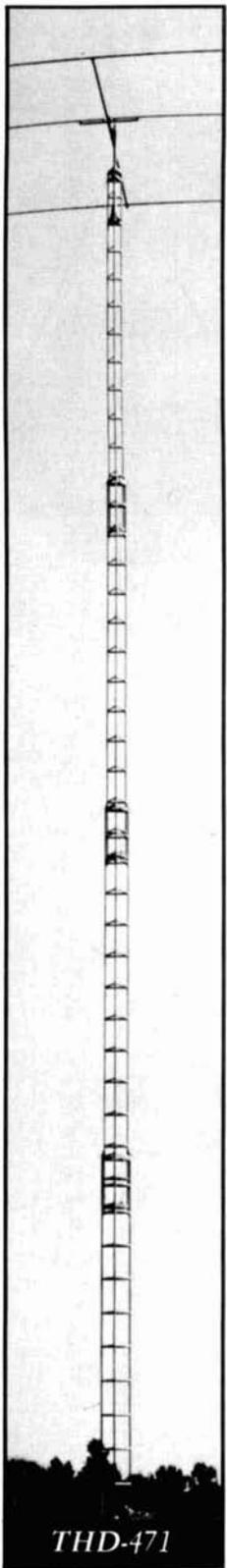

**THD-471**

Now you can afford the best! Free-standing or guyed, Tri-Ex Towers stress quality. All towers are hot dipped galvanized after fabrication for longer life. Each series is specifically engineered to HAM operator requirements.

**W Series**

An aerodynamic tower designed to hold 9 square feet in a 50 mph wind. Six models at different heights.

**MW Series**

Self-supporting when attached at first section — will hold normal Tri-Band beam. Six models.

**LM Series**

A 'W' brace motorized tower. Holds large antenna loads up to 70 feet high. Super buy.

**TM Series**

Features tubular construction for really big antenna loads. Up to 100 feet. Free-standing, with motors to raise and lower.

**THD Series**

Very popular. Low Cost. Holds Tri-Band antennas. Eight models — all support 7 square feet of antenna at full height in 70 mph winds. Guyed.

Start with Top-of-the-Line Tri-Ex Towers. At basic prices. Write today, for your best buy.



**TOWER CORPORATION**

7182 Rasmussen Ave.  
 Visalia, Calif. 93277

# importance of standing-wave ratios

This discussion  
of standing-wave ratios  
should clear up  
many of the  
misunderstandings  
that persist among  
many radio amateurs

Twenty five years ago the Micromatch, the first of many vswr bridges designed for use by the radio amateur, was introduced in the pages of *QST*.<sup>1</sup> Prior to that time the radio amateur had not given much attention to vswr and his understanding on the subject was accordingly limited. The fact that vswr measurement might provide a means of effectively evaluating and monitoring the performance of an antenna system was an exciting prospect, and amateurs began to realize that the vswr bridge was a significant development.

Thus, vswr became the subject of many technical articles in the amateur journals, with each writer addressing himself to a discussion of the various phenomenon associated with the presence of standing waves. A considerable bibliography on the subject of vswr has been accumulated, but, nevertheless, a brief period of listening on the amateur bands will reveal that a great deal of misunderstanding continues to exist. For example, it is still a widespread belief that radiated power will increase with decreasing vswr; that reflected power represents lost power; and that the reflected power is somehow dissipated within the transmitting system. One of the invalid theories postulates the reflected power returning to the output stage of the transmitter where it causes overheating of the output tube.

The following discussion is aimed at enabling the reader to obtain a better understanding of the effects of standing waves, and to do so in terms of transmission line theory with which the radio amateur is already well acquainted. In particular, the role of the reflected wave, which has become such an enigma as a result of so many conflicting opinions, will be explained in a way that I believe to be unique.

Part of the discussion will be in the form of a description of experiments performed upon a transmission system which has been mismatched to cause a vswr of 2:1 to exist. In addition, the effects of system vswr upon the output network of the transmitter will be discussed with the aid of numerical examples, and it will be shown that the criteria

Earl W. Whyman, W2HB, 375 Mount Vernon Road, Snyder, New York 14226

of proper operation is simply the ability to tune the transmitter for normal rated plate current.

Knowledge of basic transmission line theory, such as found in the *ARRL Handbook*, is all that is necessary to understand this material. However, a brief review of this theory, with particular

stalled in the transmission line, dividing it into three identical line-sections, each one-quarter wavelength ( $90^\circ$ ) long. The total length is, therefore,  $3/4$ -wavelength ( $270^\circ$ ).

The transmission line may be readily opened at the junction points for measurements, and for other purposes to be

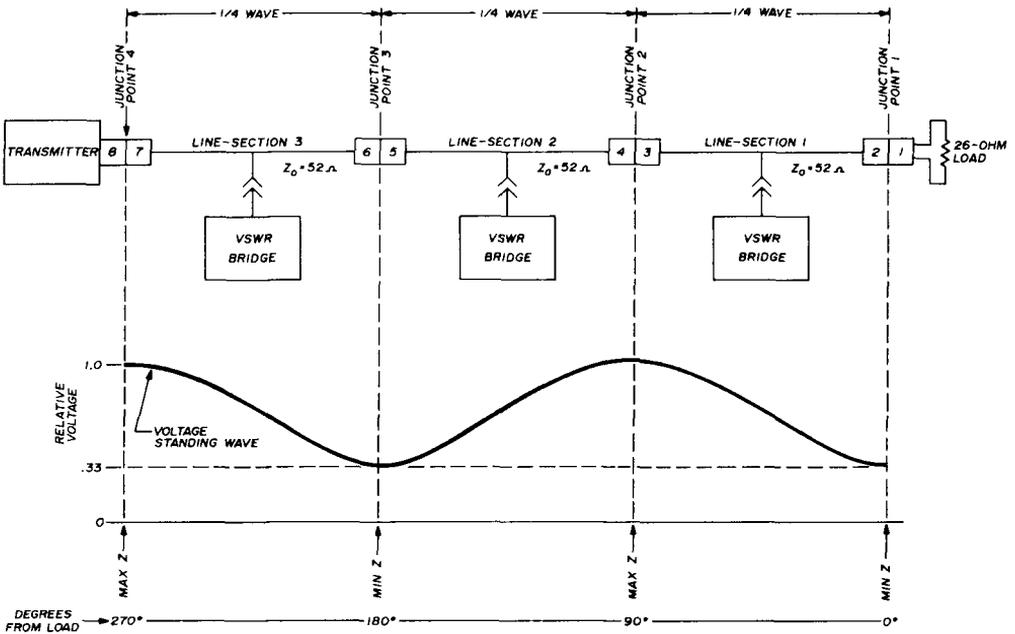


fig. 1. Antenna system discussed in text includes a  $3/4$ -wavelength transmission line with a vswr of 2:1. For diagram of transmitter matching network, see fig. 4.

emphasis on the aspects most pertinent to this discussion, is included with this article in the form of an appendix. It is suggested that you first review this appendix if only to identify the theoretical aspects which I wish to emphasize.

### the experimental system

The most common form of amateur antenna installation in use today uses coaxial cable for the transmission line. Therefore, it is appropriate to base this discussion on the coaxial system shown in fig. 1 where provisions have been made to facilitate the performance of some experimental tests. Connectors have been in-

detailed later in this article. Each line-section, each junction-point and each connector have been assigned a number for reference in the text. In addition, means for monitoring the vswr on each line-section has been provided.

Although a means for opening the transmission line at the resistive impedance points is essential for the experiments to be performed, it is not necessary to control total line length or to select a specific load impedance. The values selected for the system of fig. 1 are simply convenient and lead to less complication in the analytical discussion.

Fig. 1 also shows the position of the

standing wave and the location of the points of maximum and minimum impedance. From transmission line theory we know that the maximum and minimum impedance points are the only points on the transmission line where the impedance is a pure resistance. Later it will be shown that the points of pure resistance are of particular significance in understanding the action of reflected waves.

The system of **fig. 1** has other conditions to be specially noted and kept in mind: First, each line-section is made of RG-8A/U coaxial cable which has a characteristic impedance ( $Z_o$ ) of 52 ohms; second, a vswr of 2:1 exists on each line-section as a result of the 26-ohm resistive load at connector no. 1. Finally, each line-section may be considered separately as a quarter-wave impedance transformer where the impedance at its input connector (connectors 3, 5 and 7) may be readily found by dividing the square of line impedance,  $Z_o$  ( $52^2 = 2704$ ), by the impedance at its output connector (connectors 2, 4 and 6). Thus, the impedance at connector 3 is  $2704/26 = 104$  ohms. Since connector 3 and connector 4 are joined together, the impedance at connector 5 is  $2704/104 = 26$  ohms. In a like manner, the impedance at connector 7 is found to be 104 ohms; this is the impedance seen by the transmitter.

## experiments and observations

Referring again to **fig. 1**, let's conduct our first experiment by inserting a short section of transmission line between connector 3 and connector 4 so that the system appears as shown in **fig. 2**. A section of transmission line with a characteristic impedance of 104 ohms is chosen for this purpose so that it will be perfectly terminated (matched) by the 104-ohm resistive load which we know exists at connector 3.

We also know that when a transmission line is operated in this manner there will be no standing wave on it, and the input impedance will be equal to the characteristic impedance,  $Z_o$ , regardless

of the length of the line. Therefore, at connector 2A the impedance is 104 ohms, and the load impedance on line-section 2 remains unchanged. Indeed, if you made detailed comparisons of vswr and impedance between the system of **fig. 1** and the system of **fig. 2**, you would be unable to detect any differences — in spite of the fact that the latter system includes the 104-ohm line-section on which there is no reflected wave. The only change is some additional phase delay which is not important to this system.

An interesting and extremely important point has been demonstrated by this experiment. Since no standing wave is present on the 104-ohm line-section, the reflected wave on line-section 1 has ceased to exist at the junction of connectors 3 and 1A. More significant, however, is the fact that the reflected wave has ceased to exist at a point on the transmission line where the impedance is a pure resistance. And, if you were to repeat the above experiment for all other points where the impedance is a pure resistance, the results would be the same.

Thus, in the system of **fig. 1** there are three points on the line where the reflected waves cease to exist. However, the impedance at junction-point 2 (104 ohms) is a mismatch for line-section 2, and the impedance at junction-point 3 (26 ohms) is a mismatch for line-section 3. Thus, each of the three line-sections is mismatched by the load impedance at its respective output connector, and the magnitude of the mismatch is such as to cause a vswr of 2:1 on each line-section. Reflected waves are therefore developed independently on each line-section and it is apparent that the reflected wave due to a mismatched antenna load does not travel back toward the transmitter without interruption.

Although it may be somewhat redundant to discuss further the change that was made to convert the system of **fig. 1** into the system of **fig. 2**, some readers may appreciate further clarification of the role of the inserted line-section. Suppose that we experiment further with the

system of fig. 2 by shortening the 104-ohm line-section in successive steps, each time cutting the remaining line-section in half. Theoretically, the line-section would never be reduced to zero length. However, from a practical standpoint you can see that, as a limit, its length would approach zero, thereby making the systems of fig. 1 and fig. 2 identical. Furthermore, if the system is examined

applied years ago in the design of the "Q-Match Antenna."<sup>2,3</sup> In this system the 75-ohm impedance of a center-fed half-wave dipole is matched to 600-ohm open-wire transmission line by using a quarter-wave section of transmission line with a  $Z_0$  of 212 ohms. The 212-ohm line operates with a vswr of 2.8:1, and the 600-ohm line with a vswr of 1:1. Thus, as demonstrated in the foregoing, the re-

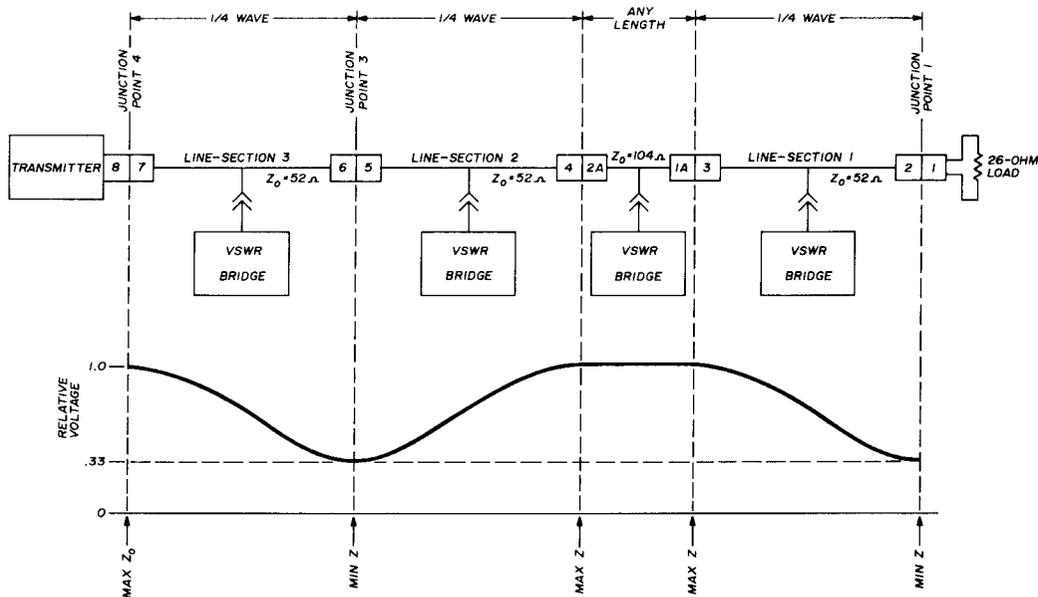


fig. 2. Since the impedance at junction point 2 in fig. 1 is 104 ohms, a section of 104-ohm transmission line, any length, may be inserted at that point with no effect upon the performance of the rest of the transmission line.

after each shortening operation, you would find the operational characteristics (such as vswr and impedance at each junction-point) unchanged. Therefore, it must be concluded that the system is independent of the length of the 104-ohm line-section, including zero length.

The 104-ohm line-section in this case has served as an analytical tool to enable the behavior of the reflected wave to be observed, and to further prove that this behavior remains unchanged after the line-section is removed from the system.

The principle applied in the foregoing experiments is the basis of many impedance-matching systems and was

flected wave on the 212-ohm line ceases to exist at the junction of the two lines because the impedance exhibited at that point is a pure resistance of 600 ohms.

### effects on the transmitter

Most present day transmitter designs use a pi-network to couple the antenna system to the output stage. In general the pi networks are designed for a nominal load impedance of 50 ohms at a maximum vswr of 2:1. This means that the transmitter can be loaded to its rated power input as long as the load impedance is maintained within specific limits. By specifying a maximum allowable vswr

the manufacturer is indirectly specifying the impedance limits of the transmitter and the amateur is provided with a parameter he is able to measure.

The easiest way to determine the impedance values which this specification permits is to make a plot on a Smith chart. Simply scribe a circle, with a radius equivalent to a  $v_{swr}$  of 2:1, about the center of the chart. This circle is the locus of all possible values of impedance on a system with a  $v_{swr}$  of 2:1. A Smith chart with a  $v_{swr} = 2:1$  plot, based upon a  $Z_0$  of 52 ohms, is shown in fig. 3; points 1 and 2 on the circle locate the only resistive impedances (26 ohms and 104 ohms, respectively) and point 3 locates the complex impedance of  $41.6 + j31.2$  ohms for later use in this discussion.

When designing a pi network the value of inductance,  $L$ , is determined such that the inductive reactance

$$X_L = \frac{QR_1 + \left(\frac{R_1 R_2}{X_{C2}}\right)}{Q^2 + 1}$$

This expression contains two terms which may be separately equated, one to  $X_{L1}$  and the other to  $X_{L2}$ , the sum of which is equal to  $X_L$ . The significance of  $X_{L1}$  and  $X_{L2}$  lies in the fact that any pi network can be shown to be exactly equivalent to two L-networks connected back-to-back as shown in fig. 4A. It is no coincidence therefore that  $X_{L1}$  and  $X_{L2}$  are the respective values of inductive reactance required for L-network 1 and L-network 2. The junction point of the two L-networks must be an impedance match. In fact, if you were to analyze any specific pi-network design you would find that at the junction point the impedance is always a pure resistance with a value lower than either the input or output impedances. For convenience, this point will be referred to as the intermediate impedance of the pi network. Referring again to fig. 4A, capacitors C1 and C2 are the conventional tuning and loading controls, respectively, and  $L$  is an inductance value that is fixed for each band. Specific values of reactance for each of these

elements is required when a particular pi-network design is desired.

As an example, a pi-network designed to match a single 6146 AB1 linear amplifier to a nominal 52-ohm resistive load is shown in fig. 4B. This network is designed to provide a 3000-ohm resistive load for the 6146 and to operate at a  $Q$  of 15. In this case the intermediate impedance is 13.27 ohms. When a load

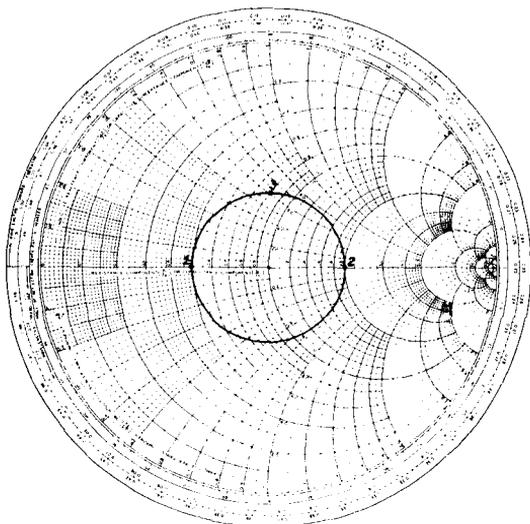


fig. 3. Smith chart plot of  $v_{swr}$  of 2:1. Only two pure resistances are possible: point 1 and 2 at 26 and 104 ohms, respectively. Point 3 locates the complex impedance,  $41.6 + j31.2$  ohms, discussed in the text. (Since this is a normalized Smith chart, all values on the chart must be multiplied by the characteristic impedance of the system, 52 ohms in this case.)

impedance other than 52 ohms resistive is used with this network, C1 and C2 are simply adjusted until normal rated plate current is obtained. When this is done the plate load will always be 3000 ohms resistive — however, the intermediate impedance and the operating  $Q$  of the network will change. Fig. 4C shows the values of  $X_{C1}$  and  $X_{C2}$  readjusted to match a load of 104 ohms resistive; the intermediate impedance is now 11.95 ohms and the operating  $Q$  has increased slightly to about 15.8.

When the load at the transmitter's

terminals is complex, i.e., some combination of resistance and reactance, the reactance will affect the tuning of the output network in the transmitter.

Every value of complex impedance can be shown to be simultaneously equivalent to either a resistance in series with a reactance, or a resistance in parallel with a reactance. Thus, there is a choice of using either a series or parallel reactance

can be determined for a match to this value of resistive load. This value of  $X_{C2}$  is then combined with the required compensating reactance to obtain the final circuit value of  $X_{C2}$ .

The result of applying the above procedure to a pi-network designed for use with the 6146 linear amplifier is shown in fig. 5. Fig. 5A illustrates that when an 86-ohm capacitive reactance,  $X_{CL}$ , is

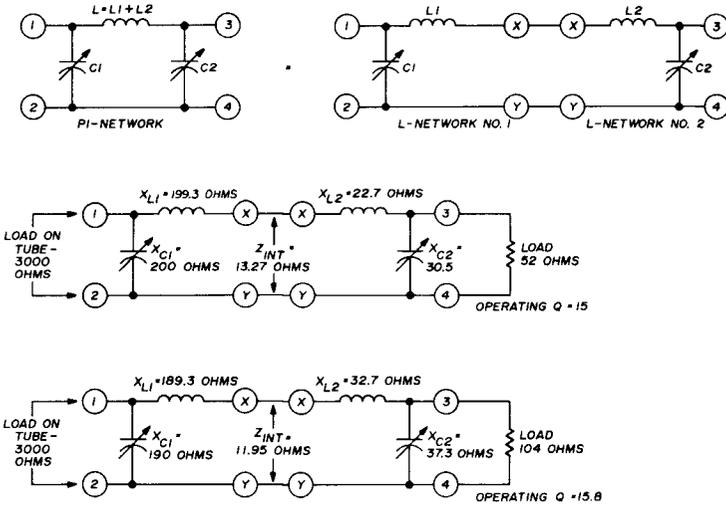


fig. 4. The inductor in the basic pi network consists of two theoretical parts, L1 and L2 (A). When operating into the design load of 52 ohms the operating Q is 15 and the intermediate impedance is 13.27 ohms (B). With a 104-ohm load (vswr = 2:1) the operating Q is 15.8 and the intermediate impedance is 11.95 ohms (C).

to tune out, or compensate for, the load reactance. However, the value of the compensating reactance, and the value of the resulting resistive load, are different in each case.

Thus, point 3 on the Smith chart, fig. 3, is a complex impedance consisting of a 41.6-ohm resistance in series with a 31.2-ohm inductive reactance; its parallel equivalent is a resistance of 65 ohms and an inductive reactance of 86 ohms. The parallel form is of special interest because C2 in the pi network is ideally situated to provide the required compensating reactance in addition to performing its normal function. Since the compensating reactance converts the load impedance into a pure resistance, values of  $X_{C1}$  and  $X_{C2}$

shunted across the parallel equivalent of the above complex load the result is a pure resistance of 65 ohms. Fig. 5B shows the network of fig. 4B tuned for a load of 65 ohms resistive. Fig. 5C shows the final network values when  $X_{C2}$  is adjusted to include the compensating reactance. Note that the network's internal impedance is 12.6 ohms and its operating Q is 15.6. Thus, the capacitance of C2 had to be increased to supply the compensating reactance. If the load had contained a capacitive reactance, the capacitance of C2 would have to be decreased to achieve compensation.

In practice, the dual role of C2 is obscured by the ease with which the circuit can be adjusted. As long as normal

rated plate current can be obtained the compensation takes place without the operator being aware of it. If it is found that the transmitter cannot be tuned for normal plate current, the vswr is probably in excess of that specified for the transmitter and the output network is unable to provide the required amount of compensation. The solution is either to revise the antenna system or to use some type of antenna tuner.

Figs. 4B, 4C and 5C demonstrate that a pi network designed for a nominal load of 52 ohms resistive can be used with an antenna system on which the vswr is 2:1. In each case the network is tunable to provide a pure resistance load of 3000 ohms for

power tube and the intermediate impedance is always a pure resistance.

Whenever a pure resistance exists in a circuit, at that point power can flow in only one direction. Therefore, power must flow from the generator (or transmitter) toward, and into, the point of pure resistance. This is so because resistance is strictly passive. That is, it cannot reflect, and all of the power that flows into it must be absorbed. A resistive point

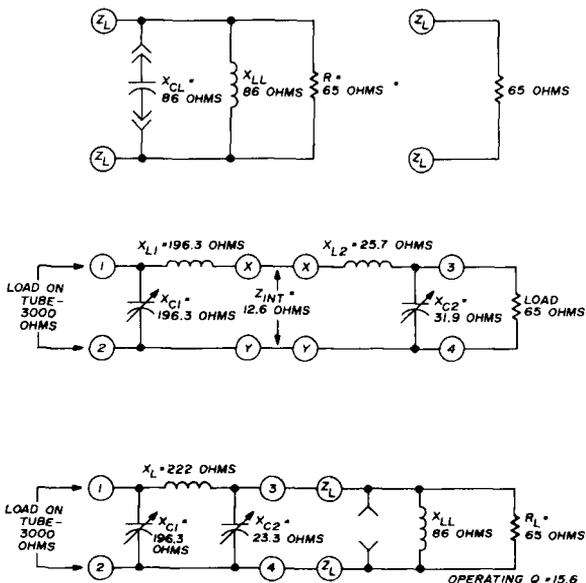


fig. 5. A capacitive reactance may be shunted across an inductive load to tune out the inductance, leaving a resistance of 65 ohms (A). The pi network of fig. 4 may be adjusted to match a resistive 65-ohm load (B). Final pi network reactance values, when C2 has been adjusted to include the compensating capacitive reactance, are shown in (C).

the plate circuit of the tube, the internal impedance of the pi network is a pure resistance, and the deviation from the desired operating Q is minimal.

### summary

Throughout this article the points of resistive impedance have been given special emphasis. When the experiments performed on the transmission line were discussed, the points of resistive impedance were significant because it was shown that reflected waves cease at these points. When the operation of the pi network was discussed it was shown that, for moderate values of system vswr, the network can always be tuned to produce the proper value of resistive load for the

in a circuit is no different than any other resistor in this respect. Therefore, you should not expect it to act any differently when it occurs in a transmission line system.

Thus, you can see that there is no way for power to return to the transmitter, and except for minor transmission line losses, the transmitter's power has no place to go except into the antenna, regardless of the presence of standing waves.

### appendix

Standing waves on a transmission line are the result of a reflected voltage wave combining with (or interfering with) the forward voltage wave. Since the two

waves are traveling in opposite directions at a constant velocity, the resulting rms voltage at any point on the transmission line will be constant and will depend upon the relative phase and amplitude of the two waves.

Locations of peak voltage will occur where the forward and reverse wave voltages are in exact phase and add together; in the same manner, voltage nulls will occur where the forward wave voltage and the reverse wave voltage are in exact opposite phase and the resulting amplitude is the difference between the two voltages. Peaks and nulls will be alternately spaced at one-quarter wave intervals (90 electrical degrees) along the transmission line with their number dependent upon the electrical length of the line.

The vswr is obviously the ratio of the voltage at peak to the voltage at a null and may be stated algebraically as

$$vswr = \frac{E_f + E_r}{E_f - E_r} \quad (1)$$

where  $E_f$  is the voltage amplitude of the forward wave and  $E_r$  is the voltage amplitude of the reflected wave. Eq. 1 can be rearranged, and if at the same time  $E_f$  is assigned a value of unity, a new expression is obtained

$$E_r = \frac{vswr - 1}{vswr + 1} \quad (2)$$

The amplitude of the reflected wave voltage can now be expressed as a fraction of the forward wave voltage for any value of vswr. For example, if the vswr is 2:1, the reflected wave will be 1/3 the amplitude of the forward wave.

Transmission-line theory is frequently discussed in what is termed "the lossless case." The assumption is made that there is no loss in the dielectric material of the transmission line and no losses in the electrical conductors. Nevertheless, in the practical case losses do exist in both the dielectric and the conductors. However, if the system being considered is limited in length to a few wavelengths, and if the operating frequency is not above the high-frequency range, there is little error

involved in assuming the losses to be zero and the discussion becomes much more manageable.

If the transmission-line losses are assumed to be zero, the product of line voltage and line current must be the same for any point on the line. It follows that to satisfy this condition of constant power, a standing wave of current must exist such that the current nulls coincide with the voltage peaks, and the current peaks coincide with the voltage nulls. Since impedance is the ratio of voltage to current,  $Z = E/I$ , it should be noted that high line impedance occurs at voltage peaks, and low line impedance occurs at voltage nulls. With a little further manipulation of the foregoing analysis the ratio of maximum impedance,  $Z_{max}$ , to minimum impedance,  $Z_{min}$ , may be expressed as a function of vswr

$$\frac{Z_{max}}{Z_{min}} = vswr^2 \quad (3)$$

This ratio is 4 when the vswr is 2:1.

One quarter-wavelength (90°) sections of transmission line have the unique property of operating as impedance transformers when terminated in any impedance other than  $Z_o$ . Thus, the input impedance ( $Z_{in}$ ) for any value of output impedance ( $Z_{out}$ ) is readily found from

$$Z_{in} = \frac{Z_o^2}{Z_{out}} \quad (4)$$

It is obvious that when  $Z_{out}$  is equal to  $Z_o$  the input impedance will be equal to  $Z_o$  and no impedance transformation will take place. It is also apparent that the input impedance will be a pure resistance only when the output impedance is a pure resistance.

#### references

1. Jones and Sontheimer, "The Micromatch," *QST*, April, 1947.
2. Marshall, "Antenna Matching with Line Segments," *QST*, September, 1948.
3. Geiser, "Resistive Impedance Matching with Quarter-Wave Lines," *QST*, February, 1964.

ham radio

# frequency synthesizer for two-meter fm

Although this  
all-channel two-meter  
frequency synthesizer  
was designed for the  
GE Progress Line,  
it may be used  
with other equipment

**One of the first things** a newcomer to fm learns is that he never seems to have enough room in the rig for all the crystals he wants, or needs, especially when using obsolete commercial equipment. While he could go out and buy a commercial amateur transceiver, with multi-channel capabilities, there is a considerable price differential between these and surplus

commercial equipment, not to mention that commercial equipment usually has a far better intermodulation figure than most of the amateur rigs currently available. This can be a very valuable asset in areas served by several repeaters that are not very far apart in frequency.

Obviously, to invest in a large number of crystals would be a financial hardship to the ham with a limited pocketbook, and hardly anyone would be interested in purchasing 100-plus crystals just to be able to cover all the available channel combinations, simplex and duplex. My aim in designing this unit was to have a low-cost unit with limited capability. This unit will only synthesize frequencies that are spaced at 30-kHz intervals starting at 146.01 MHz, which allows full coverage of the entire portion of the two-meter band which is available for repeater operation.

Naturally, this presents certain limitations, as in some areas there are still repeaters which are not on "standard" frequencies. But they are (fortunately) few and far between. In a situation like this, the synthesizer could be used to drive one channel of a two-frequency rig, and the special crystals could be installed in the other channel.

Synthesizers have been covered in quite great detail in recent months in various publications, so I refer you to the articles mentioned in the reference list at the conclusion of this article.

Bill Craig, WB4FPK, Post Office Box 947, Grayson, Kentucky 41143

While I designed this unit for use with the GE Progress Line equipment, it can be modified to operate with other commercial equipment such as Motorola, RCA, etc. I would be glad to assist anyone interested in adapting the unit to other equipment if they will send me full details of what they want to do, as well as the multiplication factors of the receiver and transmitter and the receiver first i-f frequency, etc., along with a stamped, self-addressed envelope.

To permit rapid channel switching, channel selection is accomplished by means of a 24-position, 10-deck rotary switch, in conjunction with small diode matrices, which are used to convert the binary-coded decimal (BCD) numbers required by the programmable dividers into their decimal values. While this involves considerable wiring at the switch, it also makes operation much simpler, as changing channels only requires a twist of the wrist, as would be compared to some similar circuits which would require setting 6 to 8 thumb-wheel switches. Again, some versatility is sacrificed, but there is a way out of this which I will discuss later.

The 10-deck switch is in reality, two 5-deck switches on a common shaft. A second *band* switch, a 6 pdt rotary switch, selects either one or the other bank of five decks, depending upon whether the frequency desired is above or below 147.00 MHz. In this manner, 24 possible combinations are available in either bank, each covering a full MHz. A dual set of channel markings is provided on the front panel, one set for Band A, the other for Band B. You could simply eliminate all frequencies above 147.00 MHz, and use a 5-deck switch (which would also eliminate the other band-switch) as you would have to retune the transmitter at least in order to operate over the frequency spread that the synthesizer is capable of. The receiver will operate reasonably well over a wider range than the manufacturer specifies, however. A

base-station operator might wish to retain the full coverage so he can take advantage of possible DX openings.


Whenever possible, I used low-cost general-purpose replacement type transistors to eliminate any problem of procuring replacements (these items can be obtained in most any radio/tv supply house in the country). All ICs used were of the lowest cost types available at this time, and can be obtained from most of the specialty houses dealing in these items at very nominal cost.

### circuit description

The programmable dividers are made from SN74192N decade up/down counters, wired in a modulo n configuration. These divider ICs have a parallel load capability, which allows you to enter a certain count, and then count down to zero, whereupon, an output will be generated and the number will again be re-entered into the dividers.

The number is entered in BCD form, as was mentioned previously, which is derived from diode matrices. Note that only the units and 10s of the numbers to be entered require the matrices, as the 100s only change at infrequent points during the coverage of the 2-MHz segment. The 1000s never change and are coded directly at the PC board. The coding of the 100s occurs at two decks of the channel switch.

For those readers not acquainted with BCD numbers, each of the dividers is provided with a parallel input lettered A, B, C and D which correspond to the BCD numbers 1, 2, 4 and 8, respectively. If we were to connect the A input to a 1 voltage (more than approximately +2.0 V), the divider would preset to the count of 1; if we wanted to encode the number 7, we would connect the A, B and C inputs to 1, etc. All other inputs are connected to zero (less than 0.8 V) or grounded. Of course, we would also have to apply the proper signal to the load control lead from this package before we could enter

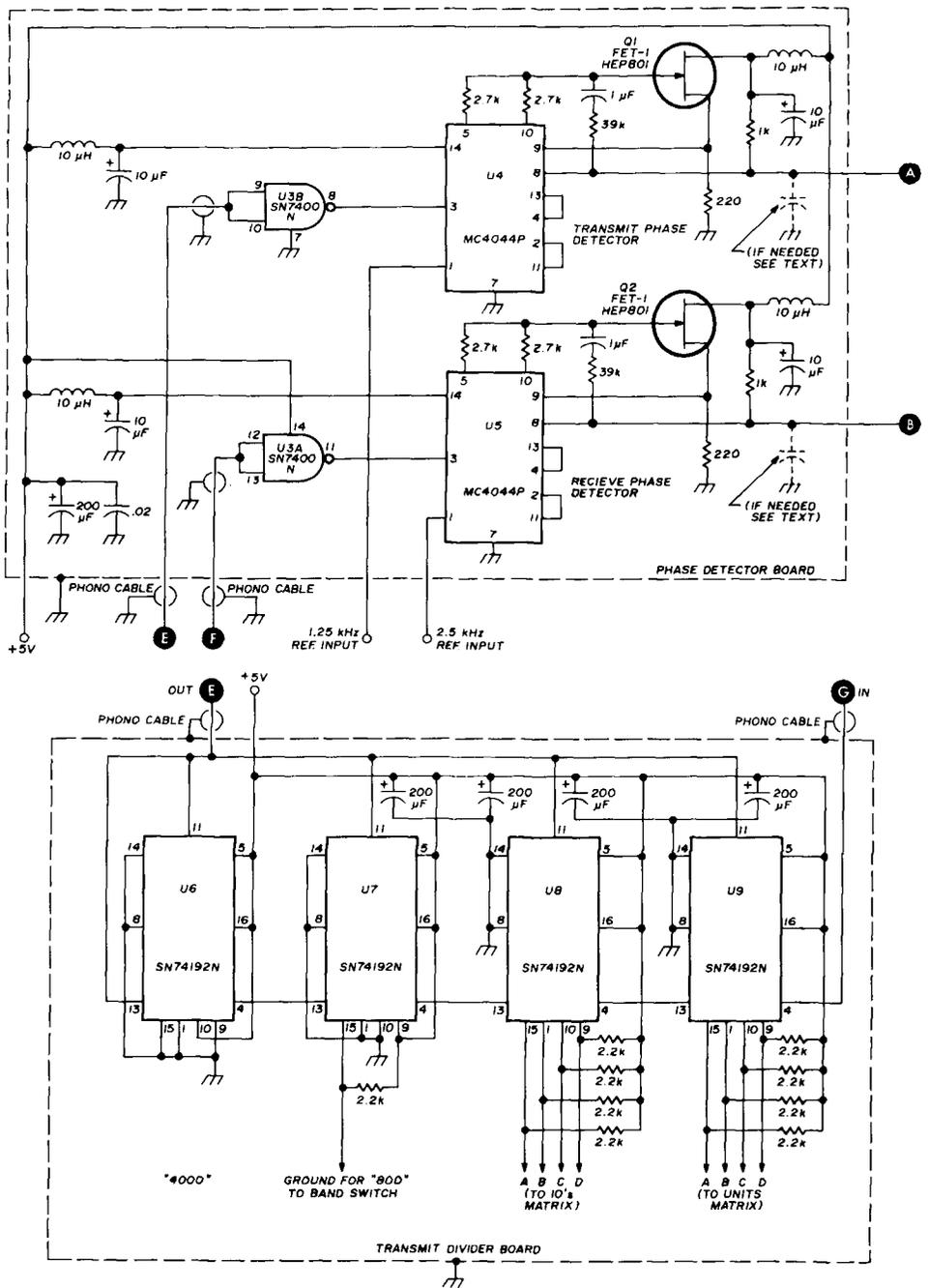

- |         |   |                                |  |
|---------|---|--------------------------------|--|
| C1      | 10 pF, N750   | L3,L4                          | turns as required on Millen 69041 slug-tuned form (see text) |
| C2      | 20 pF, N750   | C <sub>A</sub> ,C <sub>B</sub> | temperature-compensating capacitors (see text)               |
| CR1,CR2 | 22-pF varicap (TRW PC-116)                                | C <sub>T</sub>                 | 0.8 to 11 pF piston capacitor (JFD NVC9G)                    |
| L1      | 24 turns no. 24 enamelled on Millen 69041 slug-tuned form | X1                             | 5-MHz crystal (International Crystal HA-1)                   |
| L2      | 10 turns no. 24 enamelled on Millen 69041 slug-tuned form |                                |  |

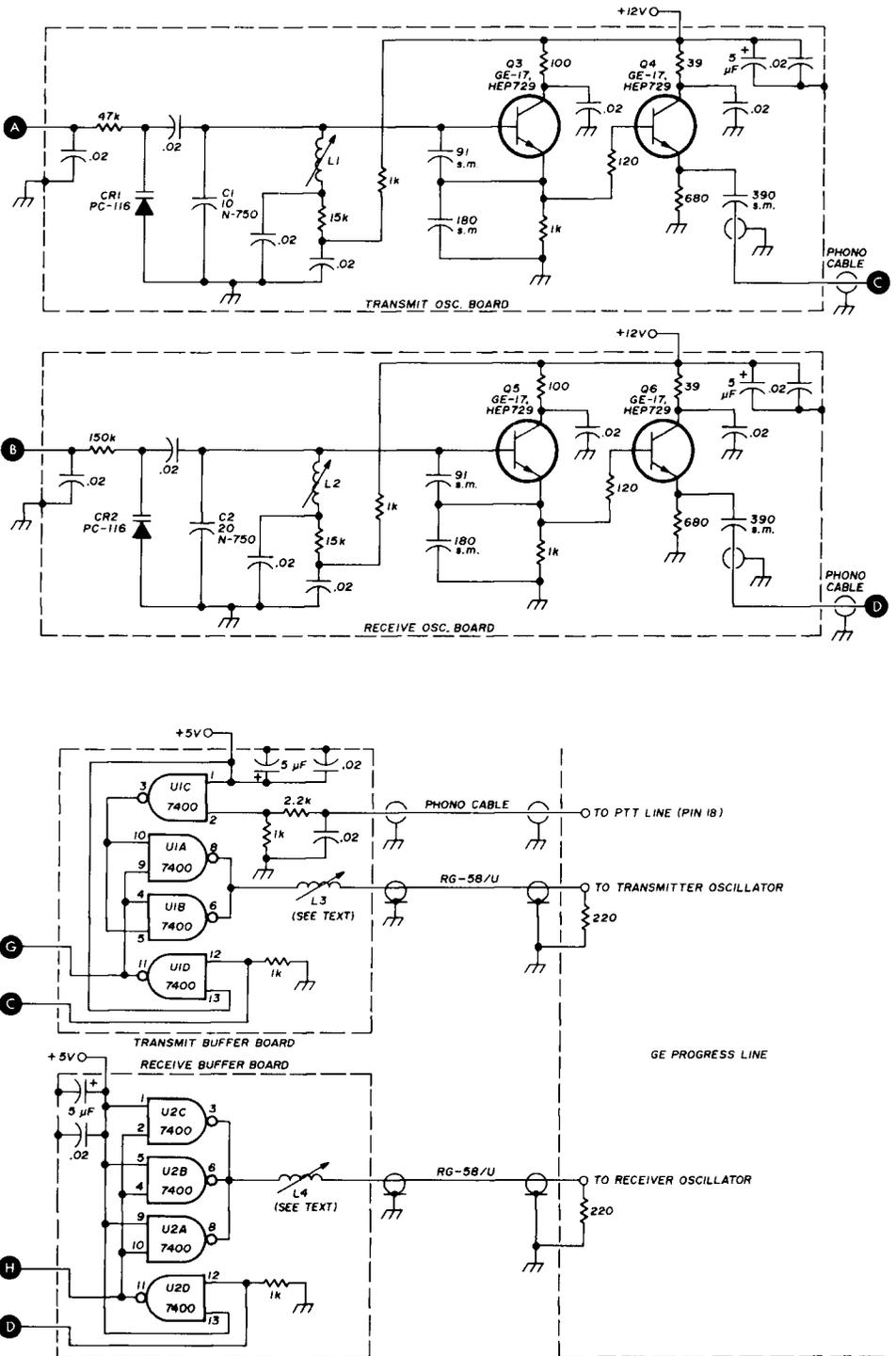



fig. 1. Circuit diagram for the two-meter transmit and receive synthesizer. This unit covers the entire two-meter fm band in 30-kHz steps, starting at 146.01 MHz. The 10-μH rf chokes are J.W. Miller type 9340-20. L1-4 are James Millen type 69041. L1 is 24 turns no. 24 enameled wire. L2 is 10 turns no. 24 enameled wire (scramble wound). Schematic for receiver divider board is on the next page.

the numbers. The load lead requires a zero to enter the data.

Each package has two clock inputs and two outputs marked count up, count down, carry and borrow. In this particular application we are only going to count down. The rules for using this IC require that the unused clock input be connected to 1 voltage. The carry output is not connected to anything in this particular application.

when an output occurs at its borrow, toggling the second divider in the chain one time. The first divider continues to count down 9,8,7, etc., until zero is reached again, and the second divider is again toggled. As you will note, the divider is working as a decade divider after it counts down the initial 6 of our number 4866.

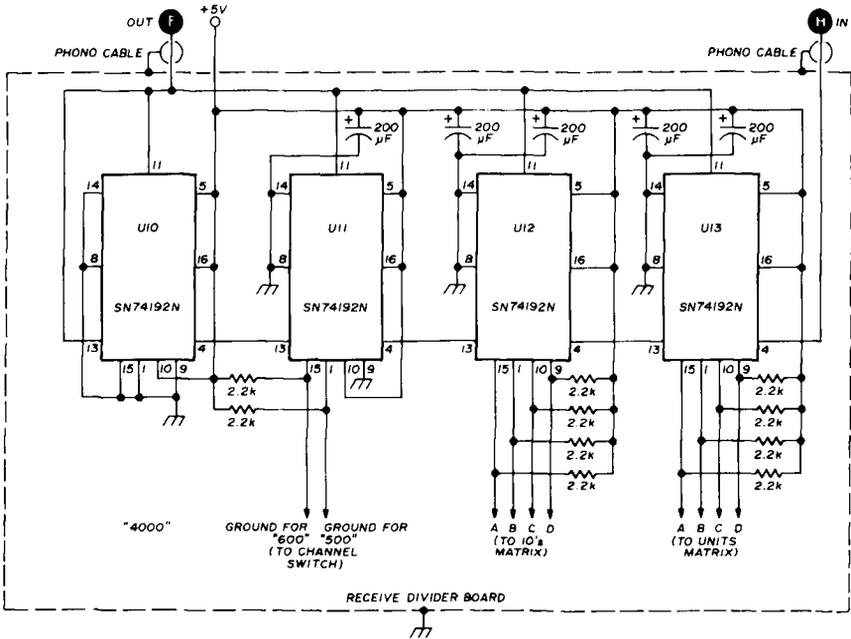This process continues until the second divider has counted down from



Schematic for the receiver divider board. Circuit points F and H are connected to the circuit in fig. 1, shown on the preceding pages.

Note that all the load inputs are connected to the *borrow* of the last (most significant number) divider. It happens that whenever an output occurs from the *borrow* the output changes from 1 to zero. It becomes apparent then that every time an output occurs from the divider chain the same signal is applied to all the parallel load leads re-entering the number into the dividers.

Suppose we take a short-cut and say we already have the number 4866 entered in our dividers. Now we apply clock pulses to the first count down input and the divider counts down, "6,5,4,3,2,1,0,"

the initial 60 it was coded with, indicating we have counted the 66 part of our original number, where the second divider also now acts as a decade divider in conjunction with the first divider to divide by 100 which will toggle the third divider in exactly the same fashion until the total number 4866 is reached, whereupon an output will occur at the borrow of the last divider in the chain. This causes the number to be re-entered into all the dividers again though the action of the output signal also being applied to the load leads of each package.

However, one little problem slips in

here, but it's quite simple to solve. Note that the dividers don't toggle on the negative transition of the clock pulse or the borrow pulse, but on the positive transition, meaning that the total count is short-changed by almost a full clock pulse. Note that as soon as the borrow occurs (not at the end of the borrow as is occurring between the sections of the dividers) the new number is re-entered into the dividers again. As soon as this number is reentered, the output obviously cannot any longer be zero because the number 4 has just been entered. So instead of getting an output pulse that is equal in length to one cycle of the input frequency (about 166 nanoseconds at 6 MHz) the output pulse is shortened to something on the order of 5-10 nanoseconds — the switching time of the TTL logic, and counting starts immediately instead of at the end of 166 nanoseconds as would be the case if you were using the more expensive modulo n dividers such as are manufactured by Motorola.

The solution to this problem is quite simple. We merely say that, instead of counting by 4866, we actually counted by 4867. The net result is that the frequency error is quite minute if we simply deduct one number from the division ratios that we calculate (the tables accompanying this article take this into account), and we end up with modulo-n counters at about one-half the price of devices intended specifically for this purpose.

Note that all the inputs that will require programming are connected to 1 via resistors. Those inputs that never change are connected to either zero or 1 directly at the PC board, as is appropriate in each instance. By shorting the inputs that go to 1 to ground (via resistors) through paths developed within the diode matrices or the bandswitch and channel switch, you can program the dividers for any count, within certain limits. The count can be programmed for considerably further range than is listed in the tables, however, if desired.

Since the basic crystal frequency of the GE Progress Line transmitter is in the 6-MHz range, and is multiplied by 24 to the output frequency, you can determine the required division ratio for the divider by dividing the desired output frequency by 24, and then by the reference frequency (1250 Hz in the case of the transmitter) remembering to subtract one count from the answer as explained above. After working out a few of these it becomes apparent that the reference frequency is related to the channel spacing ( $1.25 \text{ kHz} \times 24 = 30 \text{ kHz}$ ).

The same procedure is used to determine the division ratio required for the receiver divider, bearing in mind that the multiplication factor is only 12 in this case and subtracting the first i-f frequency from the desired receive frequency before dividing by 12. This figure is then divided by the reference frequency which in the case of the receiver is now 2.5 kHz ( $2.5 \text{ kHz} \times 12 = 30 \text{ kHz}$ ). Don't forget to deduct the one count from the final answer here, also.

The output of each programmable divider is buffered through a TTL gate to eliminate any possible transients that may appear in the output signal which are below the threshold level of the gate but which might affect the action of the phase detector. Large value capacitors are provided liberally on the PC boards to help reduce transient amplitude which could alter the total count.

### phase detectors

Phase detector circuits are provided for each of the programmable dividers, and their associated vcos. External components must be added to provide an active low-pass filter circuit which is tailored to the reference frequency, the maximum number of divider steps (loop sensitivity), the maximum lockup time desired, and the maximum permissible overshoot. To go into the math for the design of these filters would be beyond the scope of this article and the interested reader is referred to Motorola Application Note AN-535. The use of a fet transistor

rather than a bipolar type in the low-pass filter circuit makes the filtering easier to accomplish as the time constants of the associated R-C components are not affected as badly by the relatively high gate impedance of the fet.

Notice that the circuit provides for rf decoupling in the supply leads to both the active filters and phase detectors. This is required to prevent the steep wave front of the reference and output signals from the dividers from pulse modulating the resulting dc control voltage which is being obtained from the phase detector circuit and which would also modulate the vcos in turn.

### voltage controlled oscillators

The vcos are conventional Colpitts design, with a single transistor buffer stage. Frequency variation is accomplished by applying the voltage derived from the phase detectors to a varicap diode wired into the tank circuit. Isolation of the rf is adequately provided by a series resistor to this diode, which also serves the purpose of limiting the swing of the oscillator, as the diode will be somewhat self-biased by some rectified rf from the oscillator tank circuit. This requires that the applied control voltage be raised above this value before any appreciable change in capacitance can occur.

The chosen L/C ratios for the two oscillators cover the required frequency spread by about a ratio of 2:1, ensuring that adequate margin will exist in the event that the oscillator changes frequency due to changes in temperature, but when corrected by the output from the phase detector, will still be within the range of that circuit. Some frequency stability is imparted by the parallel padding capacitors in each tank circuit. However, this could probably be improved somewhat if the builder has available N-1500 type capacitors instead of the specified N-750 types. The oscillators operate from 12 volts, and are ac coupled to the following logic buffer stages. The two oscillators are identical in construction, with the exception of the

table 1. Division ratios for standard repeater pairs and simplex pairs. (Channel 22 of group A, and channels 20, 21, 22, 23 and 24 of group B are spares.)

switch pos	xmit freq (MHz)	receive freq (MHz)	xmit xtal frequency (kHz)	xmit divisor	rcv xtal frequency (kHz)	receive divisor
<b>group A</b>						
1	146.01	146.61	6083.75	4866	11492.5	4596
2	146.04	146.64	6085.00	4867	11495.0	4597
3	146.07	146.67	6086.24	4868	11497.5	4598
4	146.10	146.70	6087.50	4869	11500.0	4599
5	146.13	146.73	6088.75	4870	11502.5	4600
6	146.16	146.76	6090.00	4871	11505.0	4601
7	146.19	146.79	6091.25	4872	11507.5	4602
8	146.22	146.82	6092.50	4873	11510.0	4603
9	146.25	146.85	6093.75	4874	11512.5	4604
10	146.28	146.88	6095.00	4875	11515.0	4605
11	146.31	146.91	6096.25	4876	11517.5	4606
12	146.34	146.94	6097.50	4877	11520.0	4607
13	146.37	146.97	6098.75	4878	11522.5	4608
14	146.40	146.40	6100.00	4879	11475.0	4589
15	146.43	146.43	6101.25	4880	11477.5	4590
16	146.46	146.46	6102.50	4881	11480.0	4591
17	146.49	146.49	6103.75	4882	11482.5	4592
18	146.52	146.52	6105.00	4883	11485.0	4593
19	146.55	146.55	6106.25	4884	11487.5	4594
20	146.58	146.58	6107.50	4885	11490.0	4595
21	146.70	146.70	6112.50	4889	11500.0	4599
22	-	-	-	-	-	-
23	146.94	146.94	6122.50	4897	11520.0	4607
24	147.00	147.60	6125.00	4899	11575.0	4629
<b>group B</b>						
1	147.03	147.63	6126.25	4900	11577.5	4630
2	147.06	147.66	6127.50	4901	11580.0	4631
3	147.09	147.69	6128.75	4902	11582.5	4632
4	147.12	147.72	6130.00	4903	11585.0	4633
5	147.15	147.75	6131.25	4904	11587.5	4634
6	147.18	147.78	6132.50	4905	11590.0	4635
7	147.21	147.81	6133.75	4906	11592.5	4636
8	147.24	147.84	6135.00	4907	11595.0	4637
9	147.27	147.87	6136.25	4908	11597.5	4638
10	147.30	147.90	6137.50	4909	11600.0	4639
11	147.33	147.93	6138.75	4910	11602.5	4640
12	147.36	147.96	6140.00	4911	11605.0	4641
13	147.39	147.99	6141.25	4912	11607.5	4642
14	147.42	147.42	6142.50	4913	11560.0	4623
15	147.45	147.45	6143.75	4914	11562.5	4624
16	147.48	147.48	6145.00	4915	11565.0	4625
17	147.51	147.51	6146.25	4916	11567.5	4626
18	147.54	147.54	6147.50	4917	11570.0	4627
19	147.57	147.57	6148.75	4918	11572.5	4628

changed circuit values of the tank components and the series resistor to the varicap diode.

## logic buffer stages

A quad two-input gate is used to provide direct coupling to the GE unit and the logic divider stage. One section is used as a buffer between the vco and the dividers, and also drives the inputs of two gates wired in parallel that are used as the output buffers to drive the GE unit. Note that by ac coupling the output of the oscillator stage in the synthesizer to this

parallel, and the transmitter buffer only two, as I wanted to use one gate section as an inverter. Note that the unused inputs to the gates in the transmitter buffer are not returned to +5 volts as they are in the receiver buffer, but are connected to the output of this inverter stage. The input of this inverter is connected to the line running between the transmitter push-to-talk relay and the microphone switch contacts. When the push-to-talk button is released, approximately +12 volts\* appears on this line, driving the output of this gate to zero,

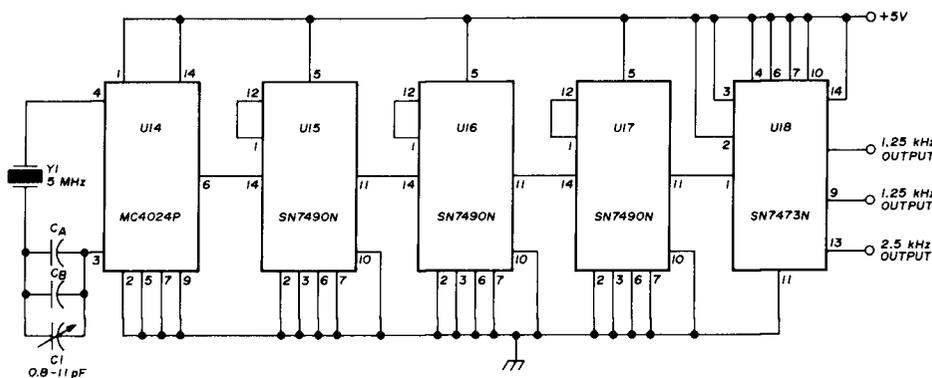


fig. 2. Crystal oscillator reference generator board.

gate, the gate can only respond to that portion of the sine wave output of the oscillator that is 0.8 volt above the zero axis of the ac signal. Consequently, the rise and fall times of the output of the gate are more than adequately fast enough to drive the divider stages without the need of a Schmitt trigger or other pulse-forming device (approximately 40 nanoseconds rise/fall time as measured on a Tektronix 513D scope).

The output from the paralleled gates is fed to the GE unit through a length of coaxial cable. The length is not especially critical, as I tried lengths up to 15 feet and still obtained adequate drive for the multiplier stages, even though the end of this line was terminated in a 220-ohm resistor.

The two buffer stages are essentially alike in their function, although the receiver buffer has three gates tied in

which disables the two buffer gates. During transmitter operation this same point is at ground and consequently the output of the inverter is at 1, which enables the buffer gates. Since it only controls the buffers and doesn't interrupt the path between the output of the vco and the dividers, no frequency searching occurs when going from transmit to receive. This suppresses the output of the transmitter oscillator signal to a level below the internal noise level of the receiver strip so as not to interfere with weak-signal reception.

This was ascertained with a narrow-

\*Some GE Progress Line equipment uses the -22 volt bias supply to operate the relays. In this case connect the center pin to the cathode of the 6AQ5 audio output tube in the receiver instead of connecting it to pin 18 of the Jones connector.

band receiver strip that was carefully checked for sensitivity and found to be somewhat better than the original specifications for this strip. However, the addition of a preamplifier would probably change the entire picture, and it would probably become necessary to supply transmit excitation through a coaxial relay keyed along with the transmitter relays. Good shielding will help in this instance more than any other technique.

match to the logic and also act as a rudimentary low-pass filter.

### construction details

The printed-circuit boards are stacked to provide as compact a package as possible. With the arrangement shown, all the ICs can be replaced without the necessity of dismantling anything. It is most important that the two oscillators and their two buffers be mounted in as fr

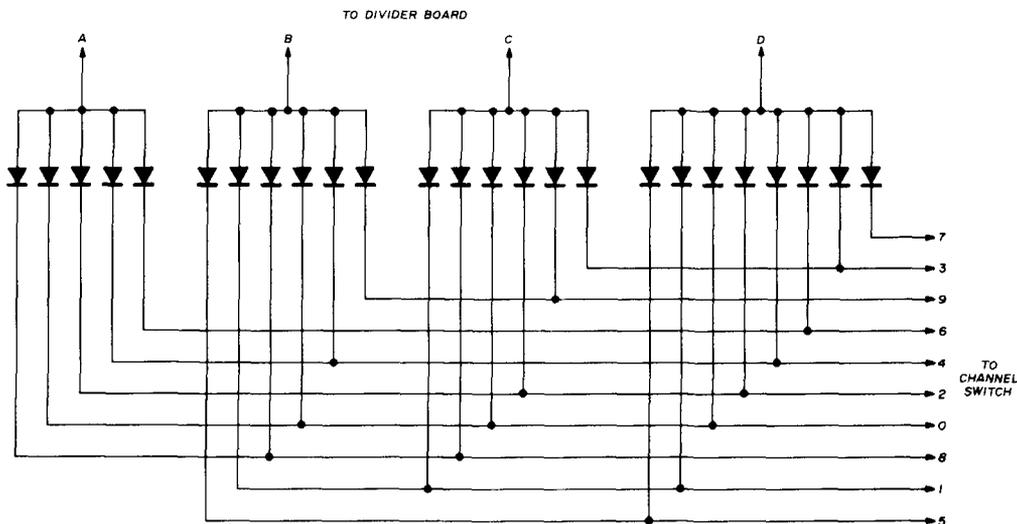


fig. 3. One-half of each diode matrix. All diodes are germanium types with a forward current rating of 10 mA, PIV = 10 volts (minimum).

Of course, this presents no problems when operating duplex as the synthesized transmit frequency is considerably removed from the receiver frequency. If only this type of operation is contemplated the additional circuitry can be deleted. I originally tried tank circuits at each end of the feed line in an attempt to improve the waveform and consequently, reduce the harmonic content. However, the additional complexity of the circuit was considerable as additional drive requirements would have to be provided to make up for losses in all these additional inductors. I feel that the simplicity of this circuit far outweighs any disadvantage it may incur. The small inductors wired in series between the end of the coax and the buffers provide a better impedance

tight a package as you can possibly make! Any coupling between the two oscillators will result in spurious outputs due to the fact that the mixing of the two signals will produce sidebands at intervals of 312.5 and 412.5 kHz when operating on repeater pairs spaced at 600 kHz. These spurious outputs will be treated by the transmitter as modulation components due to their equal spacing from the synthesized frequency, and will be multiplied, and appear in the output at the same spacing!

Bear in mind that an fm transmitter, although it multiplies the carrier and the sideband frequencies an identical amount, also causes the modulation index to increase with each multiplication. Consequently, the spurious outputs still

appear at the output. However, these that are apparent are the offspring of the original pairs since multiplication causes additional side frequencies to appear which will be spaced at the same intervals from the carrier as the original pairs were.

The compartment for the two oscillators was made from sheet copper bent into a channel shape to form the sides, and has an internal divider also made of sheet copper, and top and bottom made of PC board. Input power leads, vco control leads, etc., are bypassed immediately inside the compartment. Each oscillator has its own separate power leads. This is also most important to prevent mixing of the two rf signals. The buffer stages are treated in the same manner. However, in this case I constructed the shielded compartments entirely from copper clad PC board, soldering the sides and bottom entirely, and then lining the openings with Eimac finger stock. A rectangular shaped piece was then formed from a strip of ¼-inch wide copper strap, which was made a tight press fit into the opening.

The edges of these pieces were then soldered to lids made from PC board to complete the installation. The circuit boards that are installed inside these compartments are soldered to the sides of the compartment using small no. 6 solder lugs bent at right angles to reinforce the solder joint. Leads are then run from the boards to the appropriate terminal connections on the wall of the enclosure.

This type of construction is most necessary at these points to prevent rf from the output of the transmitter from being re-amplified which would cause hum, excessively wide bandwidth of the transmitter output, audio distortion, etc. The series inductors that I mentioned earlier in the discussion of the buffer stages also help to some extent to decouple the rf path that would otherwise exist on the center conductor of the coax. BNC connectors were used extensively here, which also helps in this regard.

Good quality phono connectors such

as the Switchcraft 3502 plugs and 3501FP jacks are a good choice for the reference leads going from the buffer compartments to the programmable dividers. These plugs are completely shielded, and the jacks only require a single ¼-inch hole for mounting.

Notice that the 24-position channel switch is mounted directly to the two matrice boards (front two boards) that contain the four diode matrices. This provides for very short leads here (not really a necessity here as only dc paths are located here) which makes for a neater layout. The front board contains the two matrices for encoding the units of the receive and transmit dividers, the board immediately to the rear of this contains the two matrices for encoding the receive and transmit 10s of the dividers, and the board next to the rear of that position is the transmit divider board. To the rear of that board is the receive divider board, the phase-detector board, then the compartments housing the two oscillators, and lastly, the compartments housing the buffers.

The diodes used in the matrices are germanium types to permit remote location of the channel switch if desired, as this would allow for almost 0.5 V drop across the interconnecting wiring. This type of diode is recommended in all cases to provide margin for error, and to allow future additions to the equipment. This would permit the synthesizer to be trunk mounted in a mobile installation with just the channel switch mounted at the dash in a Minibox.

Not included in my rig are the time-base and power supply boards, which were not used with this particular unit as the reference and supply voltages were obtained from a frequency standard that was already in the shack. However, I have included the necessary information for building these boards. The crystal oscillator board and its dividers can be mounted to the left of the stack of boards so the trimmer capacitor would be accessible from the front panel through a small opening. The power supply board can be

mounted on the righthand side or wherever is most convenient to the constructor.

The oscillator board uses the Motorola dual-vco package (only one-half used) as the crystal oscillator circuit. This makes construction quite simple as the only external components required are the crystal, trimmer capacitor and a temperature compensating capacitor. A high quality crystal is recommended here, as the output frequency stability of the

determination of the fixed temperature compensating capacitor is left to the builder. As a start, set the trimmer to approximately half capacity and install a 10-pF N-750 capacitor on the pads provided (CA). Tune in WWV (at the highest frequency possible) and attempt to zero beat the oscillator to WWV's signal by adjusting the trimmer. It may be necessary to add or subtract some capacitance from CA in order to get the oscillator in

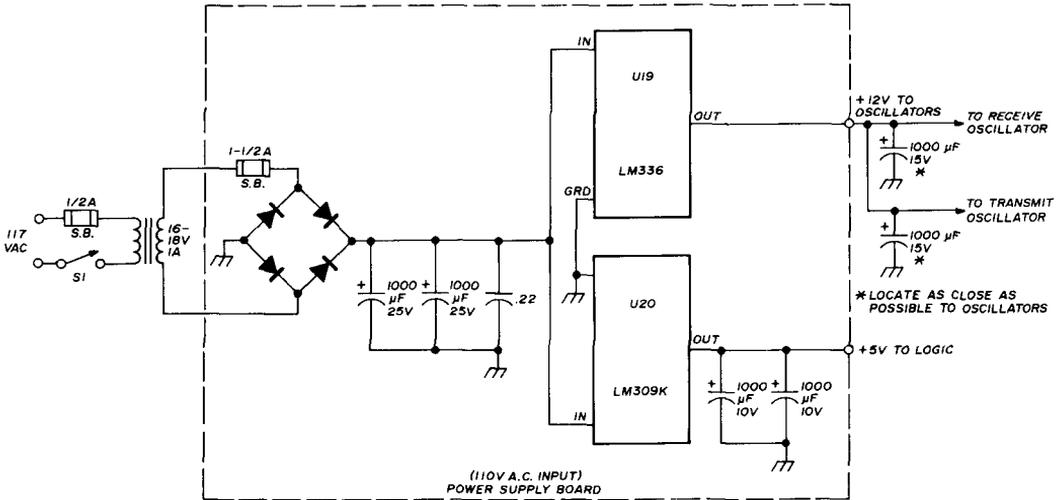


fig. 4. Ac power supply for the frequency synthesizer. Transformer T1 is a control or doorbell transformer with 16 to 18 volts output across the secondary.

synthesizer can never be any better than the stability of the reference frequency. The International type HA-1 crystal is recommended for this purpose. It should be ordered for room temperature, 12-pF parallel load for this circuit (HC6 type holder).

For mobile use an oven and suitable oven-type crystal would be required, especially in northern climates. The oscillator is then followed by three decade dividers, whose output is divided by two by the first section of a dual J-K flip-flop, yielding the 2.5-kHz reference output. This is then again divided by two by the other half of the flip-flop producing the 1.25-kHz reference output.

Due to variations in crystal and component tolerances and characteristics, the

proper range of the trimmer. Once in zero beat, hang a 100-watt lamp a foot or so above the board and allow the board to be warmed by this for about an hour.

Unless you are extremely lucky, the oscillator should no longer be in zero beat with WWV. Carefully noting which way you have to turn it, adjust the trimmer to bring the oscillator back into zero beat again. If you had to turn it clockwise (more capacitance) then the oscillator is over-compensated. Remove the capacitor from CA and install one of half that value (still type N-750) and in addition, install another capacitor of the same value at CB (type NPO) and repeat the test. If, after the initial test, you instead had to turn the capacitor counter-clockwise (less capacitance) the oscillator was not sufficient-

ly compensated. In this case install a N-1500 type capacitor as a replacement for the original N-750 type and again repeat the test. (The circuit board should be permitted to cool between tests so as not to give meaningless indications.) By using various ratios of capacitance at CA and CB (the former being either N-750 or N-1500, the latter NPO) any intermediate value of compensation can be obtained.

## power supply

The power supply is quite simple, using two self-contained, protected ICs to provide the regulated outputs. The power transformer can be a doorbell transformer or control transformer with 16-18 volts output at 1 amp. This output is rectified by a bridge circuit and applied to the two regulators. A fuse is provided in the secondary (as well as the primary) in the unlikely event of a short in one of the rectifiers or ICs. The 5-volt regulator is a National Semiconductor LM-309K (in a TO-3 case). The 12-volt regulator can be either the National LM-336 (in TO-5 case) or the Fairchild  $\mu$ A7812 (TO-220 case). For mobile use, the 12-volt regulator is deleted, the 12-volt battery is applied directly to the 5-volt regulator input, and also to a simple shunt zener diode regulator operating at 10-volts. (This will require readjustment of the oscillators with the lower supply voltage, however.) The output from the zener regulator is additionally filtered through four 88-mH toroids wired in series.

If PC board layouts shown\* are used, the construction of the boards is just a matter of mounting parts. It is strongly recommended that you use IC sockets on all the boards (as well as transistor sockets in the two oscillator boards) to make changing of defective ICs and transistors simple, as some of the PC board wiring is quite minute and could easily be damaged by repeated soldering and un-

soldering of components. Also, in the oscillator compartments, the sockets would eliminate the need of unsoldering the small printed-circuit boards from the enclosure if a transistor becomes defective. After all the boards are mounted, solder a heavy braid from each board to the next with as short a lead as possible.

All cables that are indicated as shielded on the schematic diagram should be RG-58/U coax unless otherwise indicated. Both ends of the cable shield must be grounded to the nearest ground point and the inner conductor should be as little exposed as possible. Note that all power and control leads leaving or entering the vco and buffer shielded compartments must be bypassed immediately within the compartment with 0.02- $\mu$ F disc capacitors with the shortest possible leads, soldered directly to the copper surface of the compartment. (The small electrolytic capacitors indicated are also mounted in a similar fashion.) The power and control leads were made through miniature pin jacks to make it easy to disconnect a sub-assembly for repair or testing. Feed-through capacitors could also be used in lieu of these but would require that the leads be unsoldered to disconnect it from the rest of the wiring.

## synthesizer adjustment

After completing construction, connect the logic circuits to the output of the 5-volt supply with a milliammeter inserted in series (0-1 amp range). Note the current, which should be between 450-550 mA for the logic circuits, exclusive of the crystal oscillator and divider board. If it is more or less than this range you have either a defective IC or filter capacitor or something that isn't connected. If this checks ok, connect the oscillators to the 12-volt supply with a series milliammeter (0-100 mA scale) and note the current here, which should be 30-40 mA (both oscillators). If all checks well to this point, connect a voltmeter (20,000 ohm/volt or vtm) from the vco control line to the receiver oscillator (and to ground) and turn the channel switch to

\*Full-size templates of the original prototype printed-circuit boards are available from the author along with additional schematics and parts placement diagrams for \$1.00 postpaid.

the highest receive frequency (refer to the chart, as the highest receive frequency is not necessarily the highest switch position) and adjust the slug in the receive oscillator coil form (L2) for a reading of 3.8-4.0 V (use the 0-10 volt scale). Then turn the channel switch to the lowest receive frequency and note the meter reading, which should be between 2.5-3.0 volts. If outside these limits, the L/C ratio

exterior wall of the compartment and the threaded shank should be used to make the adjustments.

### troubleshooting

If the voltage stays at or near zero or +4.8 volts, some problem exists in the loop circuits. This can be caused by any number of interrelated problems such as no reference input to the phase detector,

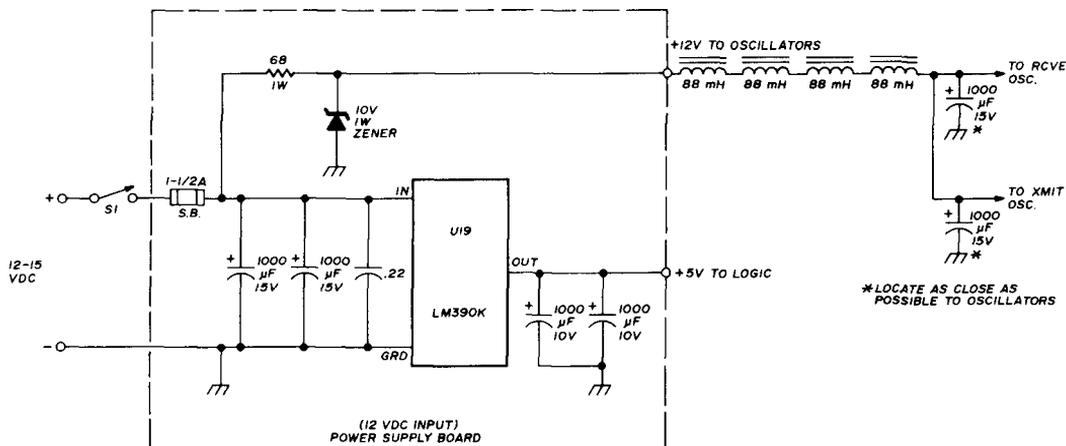


fig. 5. Alternate dc power supply for 12 to 15 Vdc input.

of the oscillator tank circuit must be adjusted, since this indicates that the oscillator control sensitivity is not correct.

If the voltage is too high, add more parallel padder capacitance to the tank circuit and reduce total inductance. Repeat the adjustment procedure until the voltage falls within these limits. If the voltage is too low, remove some of the parallel padder capacitance and increase the inductance.

Repeat this procedure for the transmit oscillator (L1), checking at the transmit vco control lead. This is probably locking the barn door after the horse has strayed, but I hope you read all the instructions before starting on this project. The oscillator compartments should be provided with access holes for adjustment of the coil slugs. Do not remove the compartment covers to make this adjustment. The coil forms should not be mounted to the

no input to or output from the programmable dividers, improper operation of oscillators or buffers, or oscillator frequency so far removed from the desired frequency that the loop cannot make the necessary corrections. Obviously, some troubleshooting will be required here and a good oscilloscope will be quite useful.

Check to see if the oscillators are actually operating near the desired frequencies by listening for their outputs on a general-coverage receiver. The oscillators should, with the vco control lead disconnected, be operating about 200 kHz below the lowest frequency in the list. Generally speaking, a reading of +4.8 volts on the vco control lead indicates that there is no input from the programmable dividers to the phase detector (or no input to the dividers from the buffer stage, etc.) or the oscillator is tuned too low in frequency.

A reading of zero (or nearly zero)

indicates that there is no input to the phase detector from the reference frequency source, or that the oscillator is tuned too high in frequency. A general-coverage receiver is handy at this point to determine if there is any output from the oscillators at all or any output from the buffer stages.

Once you have determined that the oscillators are working and the loops are

synthesizer is working correctly, the next step is to make the necessary connections to the GE unit. Begin by installing a phono jack on the front panel as near to the receiver oscillator crystal socket as possible. Attach one of the ends of a short piece (6 to 8 inches) of RG-58/U coax to this jack, and install a suitable plug on the other end that will mate with the crystal socket. (A suitable plug can be

table 2. Channel switch connections for programming per table 2. Column heading AT indicates group A, transmit; BT: group B, transmit; AR: group A, receive; BR: group B, receive.

switch pos	Deck 10	Deck 9	Deck 8	Deck 7	Deck 6	Deck 5	Deck 4	Deck 3	Deck 2	Deck 1
	units AT	units BT	units AR	units BR	10s AT	10s BT	10s AR	10s BR	100s AR	100s BR
1	6	0	6	0	6	0	9	3	5	6
2	7	1	7	1	6	0	9	3	5	6
3	8	2	8	2	6	0	9	3	5	6
4	9	3	9	3	6	0	9	3	5	6
5	0	4	0	4	7	0	0	3	6	6
6	1	5	1	5	7	0	0	3	6	6
7	2	6	2	6	7	0	0	3	6	6
8	3	7	3	7	7	0	0	3	6	6
9	4	8	4	8	7	0	0	3	6	6
10	5	9	5	9	7	0	0	3	6	6
11	6	0	6	0	7	1	0	4	6	6
12	7	1	7	1	7	1	0	4	6	6
13	8	2	8	2	7	1	0	4	6	6
14	9	3	9	3	7	1	8	2	5	6
15	0	4	0	4	8	1	9	2	5	6
16	1	5	1	5	8	1	9	2	5	6
17	2	6	2	6	8	1	9	2	5	6
18	3	7	3	7	8	1	9	2	5	6
19	4	8	4	8	8	1	9	2	5	6
20	5	spare	5	spare	8	spare	9	spare	5	spare
21	9	spare	9	spare	8	spare	9	spare	5	spare
22	spare	spare	spare	spare	spare	spare	spare	spare	spare	spare
23	7	spare	7	spare	9	spare	0	spare	6	spare
24	9	spare	9	spare	9	spare	2	spare	6	spare

locking, tune in the output frequencies on a general-coverage receiver and, with the bfo turned on, note whether the tone is stable and reasonably pure. (Don't overload the frontend of the receiver as this will give erroneous results. Keep the rf gain control turned as low as possible while making this test.)

### interconnections

Once you have determined that the

made from a defunct FT-241 crystal holder. Some radio/tv supply houses carry a twin-lead plug that also has the correct dimensions.) Solder a 220-ohm resistor across the plug, too.

The grounded side of the plug should go in the crystal pin hole that is nearest the right-hand edge of the receiver chassis (when looking from the front). Install a known, good crystal and measure the multiplier voltage at the jack provided on

the chassis with a 20,000 ohm/volt meter set on the 0-2.5 V scale. Note this reading. Remove the crystal and connect the plug from the synthesizer instead, and again note the reading. It should be nearly the same or higher.

Adjust the series inductor in the buffer compartment (L4) to obtain the highest possible reading and tune the synthesizer to a channel that is in use. Observe if the audio output from the receiver is distortion free and if there is anything more than just the slightest trace of the 2.5-kHz reference frequency apparent. (If everything is working correctly you should only be able to hear, and then just barely, the reference frequency with receiver gain wide open when listening to a strong unmodulated carrier.)

If an objectionable level of reference frequency is apparent it is probably due to insufficient shielding of the oscillator in the synthesizer, or of the buffer stages, or insufficient bypassing of the supply and control leads. It is possible, but not very likely, that the components used in the phase detector are incorrect in value. However, there is quite a bit of leeway here, and the values would have to be drastically different from those specified to cause this. In some instances, adjustment of the series inductor in the buffer compartment will reduce the amplitude of the reference-frequency trace and should be tried first. However, after the final adjustment you should still have adequate meter indication at the multiplier test jack.

Assuming that the receiver is now working correctly, install a BNC connector on the front panel of the GE unit as far to the left as possible from the jack installed for the receiver. This should be a bulkhead-type connector so that the cable shielding is uninterrupted. Attach an 18-inch length of RG-58/U cable to this connector and install a phono plug on the other end. Route this cable down the left-hand edge of the receiver chassis, around the rear of the receiver to the left-hand corner of the transmitter chassis. There is just enough room in the

left rear corner of the transmitter chassis to mount a phono jack. From the center pin of this jack, run a short stiff wire to the grid of the A oscillator tube (single-channel versions) or a short length of miniature coax to the grid of the B oscillator tube (two-frequency versions). Wire a 220-ohm resistor across the existing 100k grid resistor. For best results it is strongly recommended that you convert the oscillator tube to an amplifier by bypassing the screen and cathode of the tube with .02- $\mu$ F disc capacitors.

If you only have a single-channel rig it is suggested that you convert it to a two-frequency version for this application. You don't need any special parts such as trimmers or temperature compensating capacitors if it's only going to be used as an amplifier, and this will leave the A channel available for crystal operation if so desired. In the two-frequency version, the screen lead of the B oscillator should be disconnected from the screen lead of the A channel oscillator tube socket, and then connected through a 47k resistor to the B+ point. This will prevent the added bypassing at the screen and cathode of the B oscillator from bypassing the A oscillator as well. Refer to the appropriate GE manual for your rig for the proper connections for making a two-frequency rig from your unit. It's a simple job.

### tuneup

The transmitter can now be connected to a dummy load, placed in the tune position, and, with a multimeter connected to the first multiplier test jack, note the voltage which is obtained from a known, good crystal. (If you have a single frequency model, make this measurement before converting the oscillator to an amplifier and note the reading for future reference.) Connect the synthesizer, preferably at or near the same frequency as the crystal was, and compare the readings. These should be as nearly alike as possible, and may be changed by adjusting the series inductor in the buffer compartment (L3).

If the voltage is too high, you probably have too much series inductance; too low, not sufficient inductance. About 8 to 10 turns of no. 24 enameled wire is correct for a three-foot length of cable

table 3. Division ratios for all frequencies between 147.99 and 146.01 MHz.

frequency (MHz)	transmit divisor	receive divisor	frequency (MHz)	transmit divisor	receive divisor
146.01	4866	4576	147.00	4899	4609
146.04	4867	4577	147.03	4900	4610
146.07	4868	4578	147.06	4901	4611
146.10	4869	4579	147.09	4902	4612
146.13	4870	4580	147.12	4903	4613
146.16	4871	4581	147.15	4904	4614
146.19	4872	4582	147.18	4905	4615
146.22	4873	4583	147.21	4906	4616
146.25	4874	4584	147.24	4907	4617
146.28	4875	4585	147.27	4908	4618
146.31	4876	4586	147.30	4909	4619
146.34	4877	4587	147.33	4910	4620
146.37	4878	4588	147.36	4911	4621
146.40	4879	4589	147.39	4912	4622
146.43	4880	4590	147.42	4913	4623
146.46	4881	4591	147.45	4914	4624
146.49	4882	4592	147.48	4915	4625
146.52	4883	4593	147.51	4916	4626
146.55	4884	4594	147.54	4917	4627
146.58	4885	4595	147.57	4918	4628
146.61	4886	4596	147.60	4919	4629
146.64	4887	4597	147.63	4920	4630
146.67	4888	4598	147.66	4921	4631
146.70	4889	4599	147.69	4922	4632
146.73	4890	4600	147.72	4923	4633
146.76	4891	4601	147.75	4924	4634
146.79	4892	4602	147.78	4925	4635
146.82	4893	4603	147.81	4926	4636
146.85	4894	4604	147.84	4927	4637
146.88	4895	4605	147.87	4928	4638
146.91	4896	4606	147.90	4929	4639
146.94	4897	4607	147.93	4930	4640
146.97	4898	4608	147.96	4931	4641
147.00	4899	4609	147.99	4932	4642

between the synthesizer and the front panel of the GE unit. This is approximately correct for the receiver coil, too, by the way. With a 15-foot length of cable, about 18 turns is correct. As a rough starting point, the inductive reactance of the coil should be approxi-

mately equal to the capacitive reactance of the cable. The voltage at the multiplier test point must remain nearly the same as with a crystal as otherwise the modulation index will change.

Next, listen to the transmitter on a good fm receiver and carefully adjust the series coil, until you null out any hum that is apparent on the carrier. Hum in this case is usually caused by rf feedback, and careful adjustment will usually eliminate the path through the coax. If the hum persists, and the adjustment of the inductor doesn't seem to change it, then possibly rf is getting back into the buffer or oscillator stages by another path. All the shielding should be carefully checked to eliminate any other entry points for rf. If this eliminates the hum switch to high power and listen again. Note if there is any audio distortion or echo apparent; this is also an indication of rf feedback.

If everything is fine up to this point, listen carefully to the unmodulated carrier with an fm receiver for noise (this noise, if present, will probably sound like weak static). If this condition is noted, try adding a 5- $\mu$ F capacitor from the transmit vco control line to ground, and increase this value up to 20- $\mu$ F to eliminate this condition. This problem is caused by variation in tolerances in the components used in the low-pass filter in the phase detector. Don't add this capacitor unless it's really needed, as it will slow down the loop lock-up time.

At this point the only remaining thing to do is to install a phono jack on the front panel of the GE unit near the Jones connector going to the control head. From the center pin of this jack run a lead to pin no. 18 of the Jones connector. Install a shielded cable from the jack to the control connection to the inverter stage in the transmitter buffer compartment. This circuit will suppress the output from the transmit buffer during receiving periods.

The oscillator board (crystal oscillator) should now be zero beat against WWV. If a frequency counter is available the output of the synthesizer should be meas-

ured and the crystal trimmer adjusted accordingly. It's not a bad idea to check all the output frequencies (including the receiver) to make sure that you actually wired the band and channel switches correctly as well as to make certain that the synthesizer is locking on all frequencies.

## other frequencies

As I mentioned earlier there is a way to externally program the unit for unusual channel combinations if desired: for example, you might want a .34 simplex combination for some testing purpose. This is quite simple to do if you leave the last position of the rotary channel switch in the second group (B) of frequencies blank and mark this *external* on the front panel. You then bring out all the decimal leads from the matrices, the hundreds leads from the receiver divider board, and the hundred lead from the transmit divider board. The Units and 10s leads are wired to thumb-wheel switches (the decimal encoding types, not the BCD type) with the hundreds leads from the receiver divider board going to a spdt toggle switch. The common leads from all these switches are returned to the position 24 segments of the B group decks on the channel switch.

The hundreds lead from the transmit divider can be obtained from the unused connection on the bandswitch, run to one side of a spst toggle switch the other side of which is connected to ground.

The proper division ratios are then read from a frequency chart and entered into the switches to obtain these special frequencies. You must remember to leave the transmit hundreds switch in the 900 position, however, whenever using the regular channel selector switch in the B group. (When using the A group this precaution is not necessary as the external switch will be disconnected by the bandswitch and the lead is normally grounded by the bandswitch.) A chart of the division ratios that would have to be set on the thumbwheels and toggle switches is included for frequencies from 146.01 to 147.99 MHz (see table 3).

## acknowledgement

I would like to express my thanks to Don Rees, W4VQA, and Chuck de Santis, WB8FQY, who were most helpful in providing suggestions and assistance in the initial testing of the synthesizer, as well as to all the patient people who use the Huntington *machine* who had to live through the birth pains and countless hours of discussion and testing that went on. Their patience and comments are greatly appreciated.

## references

1. A. D. Helfrick, K2BLA, "High-Frequency Frequency Synthesizer," *ham radio*, October, 1972, page 16.
2. R. S. Stein, W6NBI, "Frequency Synthesizer for the Drake R-4 Receiver," *ham radio*, August, 1972, page 6.
3. D. H. Stevens, W1UYK, "A 4000-Channel Two-Meter Synthesizer," *QST*, September, 1972, page 17.
4. J. DeLaune, "MTTL and MECL Avionics Digital Frequency Synthesizer," Motorola Applications Note AN-532.
5. G. Nash, "Phased-Locked Loop Design Fundamentals," Motorola Applications Note AN-535, Motorola Semiconductor Products Inc.

ham radio



"Mother, I'm positive he's having an affair with another woman. I just heard him say Juliet. . .Sugar. . .Hotel. . .Whiskey. . . Two. . .Love."

*the most powerful antennas under the sun!*



## **The Best Vertical There IS!** *80 through 10 meters*

# **Hy-gain 18AVT/WB**

### **New, from the inventors of wideband verticals.**

Pack some punch! All the omnidirectional performance of Hy-Gain's famous 14AVQ/WB...plus 80 meter capability! Unrivalled performance, rugged extra heavy duty construction, and the price you want...all in one powerful package!

- Automatic switching on all five bands through the use of three beefed-up Hy-Q traps...featuring extra large diameter coils for exceptional L/C ratio and extremely high Q.
- Recessed coax connector furnished.
- Top loading coil and four element static hat.
- Constructed of extra heavy wall high tensile aluminum.
- Hot performance all the way across the band with just one setting (10 through 40).
- Hy-Q traps effectively isolate antenna sections for full 1/4 wave resonance on all bands.
- No dissimilar metals to cause noise.
- SWR 2:1 or less at band edges.
- Maximum legal power with low frequency drift.
- Exceedingly low radiation angle makes DX and long haul contacts a cinch...whether roof or ground mounted.
- Very low RF absorption from insulating materials.

The 18AVT/WB is constructed of extra heavy duty, taper swaged, seamless aircraft aluminum with full circumference, corrosion resistant compression clamps at all tubing joints. This antenna is so rigid, so rugged...that its full 25' height may be mounted using only a 12" double grip mast bracket...no guy wires, no extra support...the 18AVT/WB just stands up and dishes it out!

**Order No. 386**


**\$69.95**



Get the strength, the performance and the price you want...from the man who sells the complete line of quality Hy-Gain equipment.

## **HY-GAIN ELECTRONICS CORPORATION**

Box 5407 - WG Lincoln, Nebraska 68505

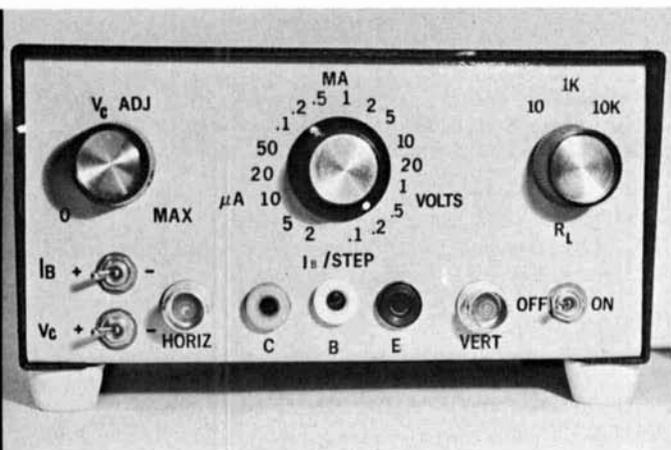

Photos by WAØLOG

## transistor curve tracer

This semiconductor  
curve tracer  
can be used  
with npn and  
pnp transistors,  
junction fets  
and mosfets,  
as well as diodes

Nothing is more frustrating than trying to design a circuit without the family of characteristic curves for the device you're going to use. In many instances the curves are not readily available or the device is unmarked. The simple-to-build, low-cost (less than \$30) curve tracer shown in the photograph is the answer to this problem. It will display a family of collector characteristic curves for npn, pnp, jfets (P and N channel) and mosfets. It can also be used to display the volt/current characteristics of two-terminal semiconductors.

### circuit

To produce the family of curves it is necessary to vary the base voltage in discrete steps while sweeping the collector voltage from zero to maximum at each step. As shown in **fig. 1**, the collector voltage is a 120-Hz rectified sine wave from a bridge rectifier, CR10-CR13. The maximum collector voltage is varied by R36 and the proper polarity is selected by S5.

The base voltage steps are synchronized to the 120-Hz collector voltage by Q1, Q2 and Q3. Transistor Q1 is an input amplifier that squares up the rectified sine wave. Q2 and Q3 form a one-shot

Dan Wright, WA9LCX, 286 East 4575 South, Ogden, Utah 84403

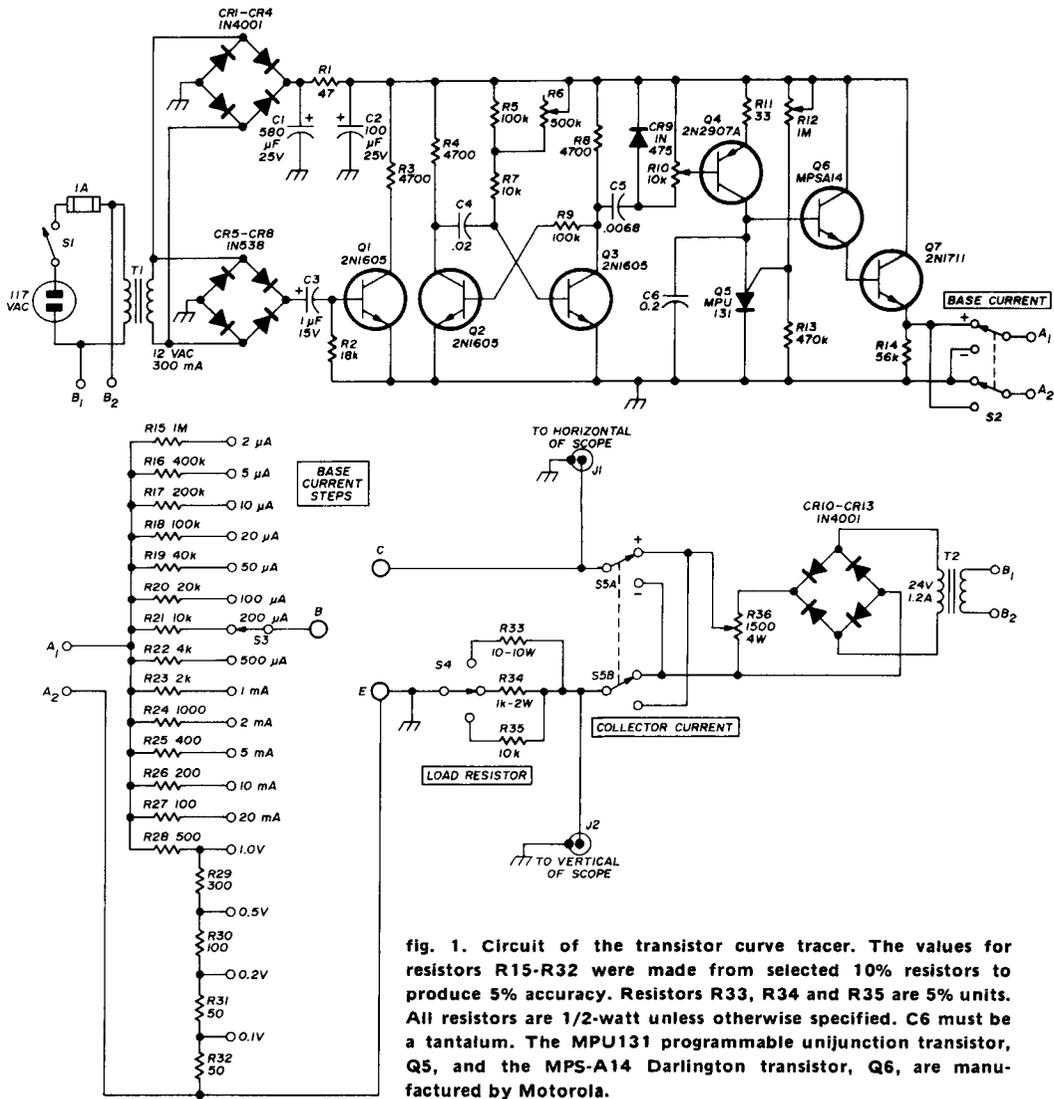


fig. 1. Circuit of the transistor curve tracer. The values for resistors R15-R32 were made from selected 10% resistors to produce 5% accuracy. Resistors R33, R34 and R35 are 5% units. All resistors are 1/2-watt unless otherwise specified. C6 must be a tantalum. The MPU131 programmable unijunction transistor, Q5, and the MPS-A14 Darlington transistor, Q6, are manufactured by Motorola.

multivibrator. The output pulse from the multivibrator is differentiated by R10 and C5. This pulse is synchronized with the beginning of the collector sweep by adjusting R6. Each time the step generator transistor Q4 is turned on by the synchronizing pulse, C6 receives equal current pulses, producing equal voltage steps.

The voltage between each step is controlled by R10. The programmable unijunction transistor, Q5, resets the stair-

step generator back to zero. When the anode voltage goes higher than the gate voltage, the unijunction transistor fires and the generator is reset. The gate voltage is adjusted by R12. The staircase voltage waveform is coupled to the selectable bias resistors (R15 - R32) for the test transistor by Q6 and Q7. The base bias is selected by S3 and the proper bias polarity is selected by S2.

The collector voltage is measured directly and applied to the horizontal

input of the oscilloscope. The collector current is determined by measuring the voltage across one of the load resistors (R33, R34 or R35) and applying it to the vertical input of the scope.

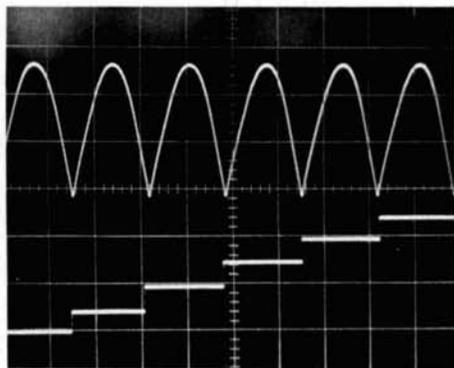


fig. 2. This dual-trace oscilloscope display shows the relationship between the base and collector voltage waveforms.

selecting and combining 10% resistors to obtain the necessary 5% tolerance.

Alignment is fairly simple. First, preset R12 to minimum resistance. Monitor the step voltage output at the emitter of Q7

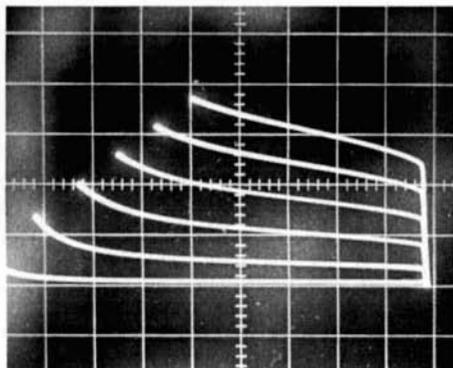


fig. 3. Curves for a 2N404 pnp transistor. Horizontal sensitivity is 2V/cm and vertical sensitivity is 2mA/cm. Base current is 5  $\mu$ A per step.

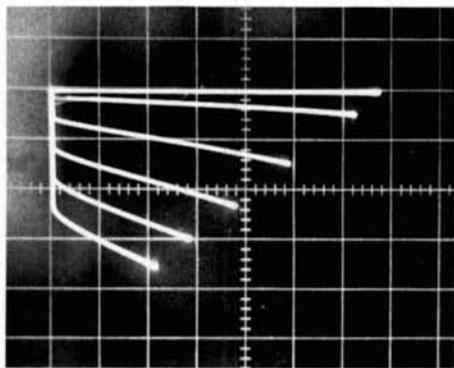


fig. 4. Curves for a 2N3055 npn power transistor. Horizontal sensitivity is 10V/cm and vertical sensitivity is 100mA/cm. Base current is 0.5 mA per step. The curves for all npn transistors will be inverted unless your oscilloscope has the capability to reverse signal polarity.

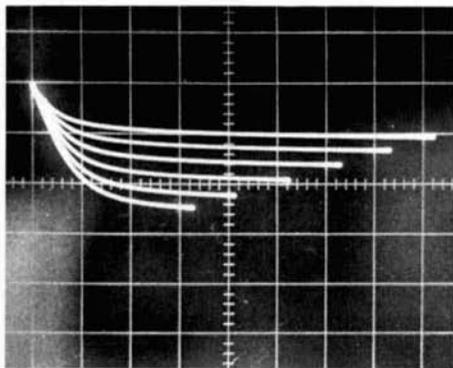


fig. 5. Characteristic curves for 2N4416 n-channel fet. Horizontal sensitivity is 2V/cm and vertical sensitivity is 5mA/cm. Gate voltage is +0.2 volts per step. Switch S2 can be used to provide characteristic fet curves with negative values of gate voltage.

## construction and alignment

The curve tracer can be built on a perforated board or a printed circuit board, depending on the builder. Parts layout is not critical although it seems logical to keep all lead lengths short to minimize any stray signal pick-up. The base resistors (R15 - R32) are made by

with a scope and adjust R10 to produce the first step at approximately 2.2 volts. Adjust R12 to produce six steps before Q5 resets the generator. Adjust R6 so the base steps are synchronized with the collector waveform as shown in fig. 2. If a dual-trace scope is not available, this alignment can be made by adjusting R6 for the least amount of clutter on the

scope when a transistor is being tested on the curve tracer.

## parts substitution

Before starting a project such as this,

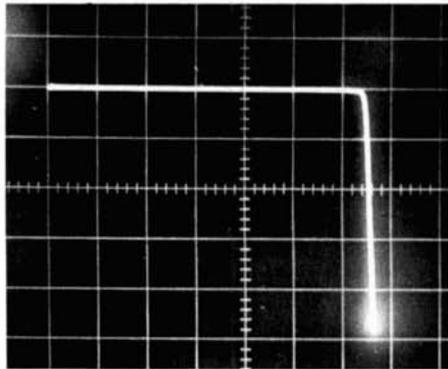


fig. 6. The curve tracer can also be used to display the voltage-current characteristics of a two-terminal semiconductor, such as a diode. This is the characteristic curve of a 1N429 zener diode. Vertical sensitivity is 2mA/cm and horizontal sensitivity is 1V/cm.

you always wonder if your junkbox parts can be substituted. This circuit seems to be very forgiving. Almost any npn transistor can be used for Q1, Q2 and Q3 (I used 2N1605s because that is what was in my junkbox). Almost any pnp transistor can be used for Q4. If you replace Q7, be sure to replace it with one of equal power dissipation and collector current.

I do not recommend any substitutions for Q5 or Q6. They seem to work better than any of the other devices I tried, and they only cost 80 cents each from the surplus houses. The diodes can be substituted as needed so long as the replacements have similar PIV and forward current characteristics.

## operation

Operation of the curve tracer is straightforward. First, select the proper base current and collector voltage for the device being tested. Select a load resistor, 1000 ohms for most small-signal devices, 10 ohms for power devices or 10k when you want to limit current for breakdown tests. Adjust your scope for a horizontal

sensitivity of 2 volts/cm (this setting is convenient for most cases). The vertical sensitivity can be computed from the formula

$$I_c/cm = \frac{\text{sensitivity/cm}}{R_L}$$

Now, connect the transistor to the curve tracer. For fets the C terminal is connected to the drain, the B terminal is connected to the gate and the E terminal is connected to the source. Fig. 3 through fig. 6 show actual scope displays for various devices that were tested on this curve tracer.


## conclusion

The completion of this project is only the beginning. If you consult a good textbook on transistors the meaning of these curves becomes much more explicit. If you do much work with semiconductors the information gained from these curves will save you countless hours of trial and error. I wish to thank my wife for her encouragement throughout this project.

ham radio



"Get that thing out of here!"

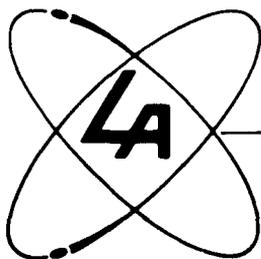

*Electronix Sales*

## JULY SPECIALS

### TRI-EX-HYGAIN ANTENNA TOWER PACKAGE

W-51 Free-Standing Tower w/base, HYGAIN TH6DXX antenna, Ham-m rotor ..... **\$599.00**

### TRI-EX-HYGAIN TRI-EX MW-35 SELF SUPPORTING

Complete w/HYGAIN TH3MK3 antenna, and TR44 rotor\* ..... **\$319.95**  
\*Add \$50.00 for Ham-m, Add \$90.00 for HyGain Rotor Brake

### TRI-EX-HYGAIN "SUPER" TOWER PACKAGE

LM354 Tower w/base, HYGAIN TH6DXX, and Ham-m rotor..... **\$849.00**


**FREIGHT PREPAID in Continental USA**

48 hour shipment with cashier's check or money order.  
Add 4% to Master Charge, BankAmericard or American Express Card Orders.

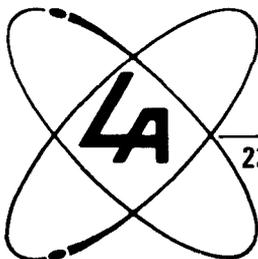**WRITE FOR OTHER ANTENNA/TOWER PKG DEALS!!**

Closed Sundays and Mondays

"WEST COAST'S FASTEST GROWING AMATEUR RADIO DISTRIBUTOR"  
"WE SELL ONLY THE BEST"




*Electronix Sales*



23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4402

HOME of LA AMATEUR RADIO SALES

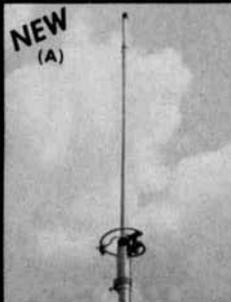

NEW  
(C)

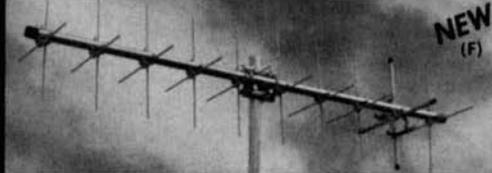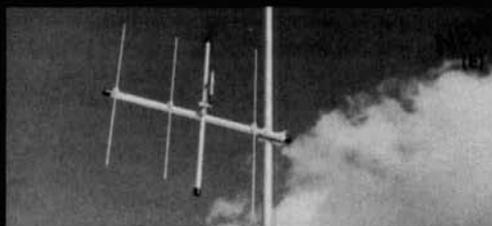

# Cush Craft

## 2 METER FM ANTENNAS

**NEW** FROM THE WORLD'S LEADING MANUFACTURER OF VHF/UHF COMMUNICATION ANTENNAS

(A) **FM GAIN RINGO:** The most popular — high performance, half-wave FM antennas. Give peak gain, and efficiency, instant assembly and installation.

AR-2	100 watts	135-175 MHz	\$12.50
AR-25	500 watts	135-175 MHz	17.50
AR-220	100 watts	220-225 MHz	12.50
AR-450	100 watts	420-470 MHz	12.50
AR-6	100 watts	50-54 MHz	18.50

(B) **4 POLE:** A four dipole gain array with mounting booms and coax harness 52 ohm feed, 360° or 180° pattern.

AFM-4D	1000 watts	146-148 MHz	\$42.50
AFM-24D	1000 watts	220-225 MHz	40.50
AFM-44D	1000 watts	435-450 MHz	38.50

(C) **FM MOBILE: IMPROVED** Fiberglass  $\frac{1}{2}$  wave mobile antenna with new molded base and quick grip trunk mount. Superior strength, power handling and performance.

AM-147	146-175 MHz mobile	\$26.95
--------	--------------------	---------

(D) **POWER PACK:** A 22 element, high performance, vertically polarized FM array, complete with all hardware, mounting boom, harness and 2 antennas.

A147-22	1000 watts	146-148 MHz	\$49.50
---------	------------	-------------	---------

(E) **4-6-11 ELEMENT YAGIS:** The standard of comparison in VHF/UHF communications, now cut for 2 meter FM and vertical polarization. 4 & 6 Element models can be tower side mounted.

A147-4	1000 watts	146-148 MHz	\$ 9.95
A147-11	1000 watts	146-148 MHz	17.95
A220-11	1000 watts	220-225 MHz	15.95
A449-6	1000 watts	440-450 MHz	10.95
A449-11	1000 watts	440-450 MHz	13.95

(F) **FM TWIST:** A Cush Craft exclusive — it's two antennas in one. Horizontal elements cut at 144.5 MHz, vertical elements cut at 147 MHz, two feed lines.

A147-20T	1000 watts	145 & 147 MHz	\$39.50
----------	------------	---------------	---------

Freight Prepaid in Continental U.S.A.

Write for King Sized Savings on other Antenna/Tower Package Deals.



## Electronics Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4402

HOME of LA AMATEUR RADIO SALES

# designing impedance-matching systems

A graphical method  
of designing  
impedance-matching networks  
for your  
favorite antenna

There's a line from Porgy and Bess, "the things that you're liable to read in the Bible — they ain't necessarily so." It's also a fact that the things you read in a good antenna theory book ain't necessarily so when it comes to your particular antenna.

What is the impedance of a vertical antenna? Well, you can look up the impedance on carefully constructed charts with electrical height in one direction and ohms in the other and get some ball-park estimates for both resistance and reactance. But what is the impedance of *your* vertical? What is its electrical height and is it the same for a 3-inch pipe as it is for a piece of wire? Down at the bottom of the page containing the graph

you may find a footnote that says, "over a perfect ground." (Sometimes this footnote appears 3 pages removed from the chart.) Now, do you have a perfect saltwater ground or do you have a piece of wire ten-feet long or do you have the body of a motor vehicle?

There are just too many variables to come up with an answer either by eye balling or by taking physical measurements. To really know, you need to take some electrical measurements. And, to get any kind of precision, you need a good rf bridge. A \$1000 rf bridge is not available to everybody but I had the use of one for a short time and came up with some rather surprising results.

## mobile-mounted vertical

This article will involve itself with a couple of outstanding examples, but to start with, I was motivated by the results I obtained from a vehicle-mounted vertical. I don't care much about mobiling but I do like to ham from a camp location once I get there. If there are trees around, a good dipole is hard to beat. I get mine up by shooting a fish sinker, attached to a spinning outfit, with a slingshot. These surgical rubber tubing slingshots (available in any sports store) will shoot a one-ounce sinker over a fifty-foot-high limb quite easily. Then you reel the fish line back with a nylon cord attached, and raise your antenna.

But in some places, like the seashore, trees are not handy. So, I wanted a good vertical whip, a full quarter-wavelength high on 20, 15 and 10 meters. This was made from telescoping aluminum tubing.

Bob Baird, W7CSD, 3740 Summers Lane, Klamath Falls, Oregon 97601

The time-honored method of grid dipping to achieve resonance was followed to get the required length on the three bands.

I have a Ford van station wagon which has quite an expanse of roof for a ground plane. I looked in the good book for an approximate resistance for a quarter-wave ground plane and came up with the magic number of 36 ohms. "Aha, two hunks of 72-ohm coax in parallel should yield 36 ohms." Well, maybe it does, but my swr was higher than a cat's back and adjusting the telescoping whip to some point off resonance didn't help at all.

Finally, I took off one of the pieces of coax and things were just as bad as before (this was on 20 meters). In desperation I got a piece of 50-ohm coax and everything was hunky-dory. Then, I went to 15 meters — with 50-ohm line the swr was way too high. I changed back to 72-ohm coax and got on board. I had the same experience on 10 meters.

### impedance measurement

Well, I finally got everything working all right, but I wondered just what was really going on, anyway. So, I borrowed an rf bridge and made some measurements. The General Radio 1606A rf bridge has two dials that read out resistance and reactance. At resonance the so-called j-factor or reactive component should read zero. With the vertical adjusted to the proper height in the middle of the 20-meter phone band I obtained a readout of  $52 \pm j0$ . On 15 meters the reading was  $70 \pm j0$ , and on 10 meters,  $75 \pm j0$ . All of these measurements were for one-quarter wavelength height. The differences in R seems to be attributable to the mounting (one corner of the van) and the extent of the ground plane (vehicle body). They would, of course, differ for every installation and every vehicle. However, I suspect that a lot of installations would work best with a 50-ohm line on one band and a 72-ohm line on another.

Measurements were actually made at the end of an electrically measured half wavelength of line in each case, in order to remove the equipment from proximity to the vehicle.

### vertical antenna

In the W7CSD part of the world, crops are irrigated, and a 40-foot length of aluminum irrigation pipe is pretty easy to come by. (\$14.30 for 3-inch tubing.) I set a one-quart soft-drink bottle in concrete and mounted a 40-foot section of irrigation pipe on top of it guyed with polyurethane rope (the kind used for water skiing). I thought this would work pretty



Author W7CSD with his three-band 40-foot irrigation-pipe vertical.

well on 20 meters and also 40 and 75. The big problem was building matching networks for each band.

First of all, I needed to make some impedance measurements to see what I had. The first thing that I determined was that long radials will work fine on 20 meters, but short radials will not work well on 75. So, I used three 75-foot radials (actually, not really radial, but following convenient fence lines). More



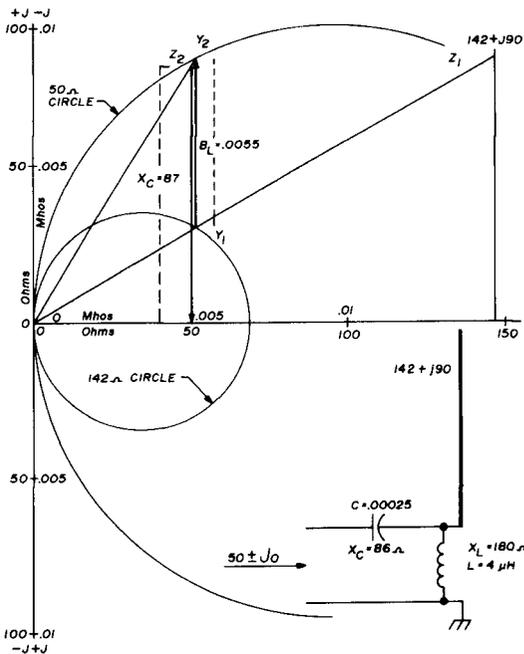


fig. 2. Another graphical solution for an impedance-matching network for a 40-foot irrigation pipe vertical for use on 7.25 MHz. Compare this network with the one shown in fig. 1.

2. Draw the 142-ohm circle, diameter =  $1/142 = 0.00705$ , radius =  $0.00352$ .
3. Point  $Z_1 = 142 + j90 = 142$  to right and  $90^\circ$  up.
4. Draw line from Point  $Z_1$  to origin.
5. Transfer  $Z_1$  to  $Y_1$  along this line to the 142-ohm circle.
6. Draw vertical line from point  $Y_1$  down to  $Y_2$  on the 50-ohm circle. The distance  $Y_1$  to  $Y_2$  is the susceptance of  $Y_C = +jB = 0.01175$  mhos or  $X_C = 85$  ohms.  $C = 0.000256 \mu\text{F}$  at 7.25 MHz (use a  $0.00025$  mica).
7. Draw line from  $Y_2$  through origin.
8. From the origin go out 50 ohms on the horizontal and draw a vertical line to the intersection of the line drawn in step 7. (In this case it just happens to coincide with line drawn in step 6.) This vertical distance (actually from  $Z_3$  to the horizontal) is  $X_L = 87$  ohms;  $L = 1.9$  microhenries.

Now, in case you are suspicious of all this hocus-pocus, let's take the result and work it out to see if it is true. Looking into the network, we are supposed to see  $50 \pm j0$  ohms. Going out to the far end, we have the antenna,  $142 + j90$  ohms in parallel with the capacitor,  $0 - j85$  ohms. Using the formula for parallel impedances,

$$Z_{\text{combination}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = \frac{(-j85)(142 + j90)}{-j85 + 142 + j90}$$

Changing to the polar form,

$$Z = \frac{(85 / -90^\circ)(168 / 32.4^\circ)}{142 / 2^\circ}$$

$$= 101 / -59.6^\circ = 51 - j87 \text{ ohms}$$

Combining the series inductance,  $X_L = 87$  ohms, we obtain  $51 - j87 + j87 = 51 \pm j0$  ohms. Accuracy is as good as the graphical method. Greater accuracy can be obtained from a larger graph.

The above solution is the one you want for two reasons. First of all, the network should look like a low-pass filter which will discriminate against harmonics. Also, you can eyeball the 75-meter situation and see that all you need is a series inductance,  $X_L = j167$  ohms — the 54 ohms R is close enough. Likewise, the same kind of network is desirable for 20 meters so that the same coil, tapped at the proper places, can be used for all three bands. However, there is another solution which, for another problem, might be more desirable.

## example 2

Steps 1 through 5 same as in example 1.

6. Draw vertical line from point  $Y_1$  up to  $Y_2$  to the 50-ohm circle. This vertical distance (in the up direction =  $-jB$ , is the susceptance  $Y_L = -jB = 0.0055$  mhos or  $K_L = 180$  ohms;  $L = 4$  microhenries (see fig. 2).



1.0:1 on the first trial. The swr on 20 meters was up near 1.5:1 and minimum was with the little 11-pF variable wide open. Removal of the variable capacitor and moving the inductor tap one-half turn yielded an swr of 1.0:1. Apparently, the capacitance of the coil to the aluminum box housing the network was very close to the required 11-pF. The final circuit of the network is shown in fig. 4.

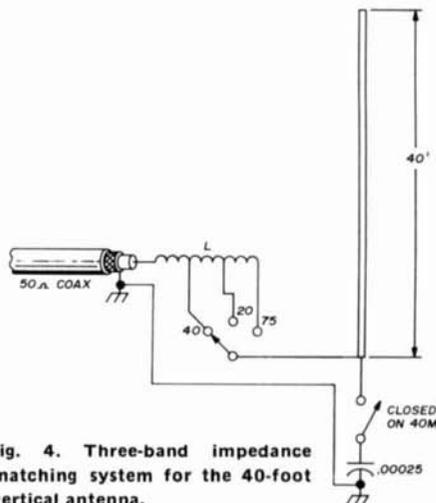


fig. 4. Three-band impedance matching system for the 40-foot vertical antenna.

## summary

I have received excellent reports on all bands. I have no comparison on 75 and 40. On 20 the vertical cannot compete with a cubical quad, but this is not surprising. However, on DX contacts it is only down about 1 S-unit.

The big problem is how to measure the impedance of the antenna without a \$1000 bridge. I think I may have some answers for this which I will verify when antenna weather comes again. There are several possibilities that are close enough that little trial and error would be necessary to get everything tuned up.

## reference

1. George Frese, "Graphical Solutions to RF Networks," *Broadcast Engineering*, January, 1964, page 12.

ham radio

**Proved in  
Commercial 2-way  
Now Available  
To Amateurs!**

## Larsen Mobile Gain Antenna 144-148 MHz



The result of over 25 years of two-way radio experience. Gives you . . .

- 3 db + gain over 1/4 wave whip
- 6 db + gain for complete system communications
- V.S.W.R. less than 1.3 to 1
- Low, low silhouette for better appearance

The fastest growing antenna in the commercial 2-way field is now available to Amateurs. It's the antenna that lets you HEAR THE DIFFERENCE. Easily and quickly adjusted to any frequency. Hi-impact epoxy base construction for rugged long life. Silver plated whip radiates better. Handles full 100 watts continuous. Models to fit any standard mount. Available as antenna only or complete with all hardware and coax.

Get the full facts on this amazing antenna that brings signals up out of the noise . . . provides better fringe area talk power. Write today for fact sheet and prices.

---

*Sold with a full money back guarantee.  
You hear better or it costs nothing!*

---

also available . . .

### 5 db Gain Antenna for 420-440 MHz and 440-460 MHz

Phased Collinear with same rugged construction as Larsen 2 meter antennas and 5 db gain over reference 1/4 wave whip. Models to fit all mounts. Comes with instructions. Write today for full fact sheet and price.



**Larsen Antennas**

11611 N.E. 50th Ave. ■ Vancouver, WA. 98665  
Phone 206/695-5383

# how to compare the efficiency of linear power amplifiers

Accurately comparing  
the efficiency  
of two linear amplifiers  
is not difficult,  
but it requires  
some care

While listening on an amateur band, I overheard one amateur telling another his results in comparing the efficiency of two commercially-built rf power amplifiers. Each of these amplifiers used vacuum tubes, and was designed for amplifying the output of ssb exciters. The comparison was based solely upon the ratio of dc power input to rf power output while speaking the same words into the exciter's microphone at approximately the same amplitude.

Carl Drumeller, W5JJ, 5824 N.W. 58 Street, Warr Acres, Oklahoma 73122

This seems to be a commonly-used and more or less universally accepted means of evaluating the efficiency and effectiveness of rf power amplifiers used as linear amplifiers. But is it a valid comparison?

In the particular instance in question, one rf power amplifier showed an efficiency of 67%, the other 40%. The high apparent efficiency of one is an immediate *flag* for suspecting the validity of the test. That figure, 67%, borders upon the theoretical maximum that a vacuum-tube amplifying stage can produce in linear service. It supposes that every parameter is at its perfect peak of optimum adjustment, that associated circuits are without loss, that nirvana has been achieved. The other figure, 40%, is a much more believable one!

## the comparison

What, then, constitutes a valid means of comparing the efficiency of two linear amplifiers? The clue lies in that term, *linear*. Vacuum-tube amplifiers can be designed and constructed to be amazingly efficient as converters of dc power input into rf power output. By running dc grid bias very, very high (many times the cutoff point) and running the rf grid excitation high enough to saturate the tube, an efficiency of around 90% can be achieved.

But, would you want it? You probably wouldn't, for that rf output would contain as much power in harmonics as in the

fundamental. This is not precisely what you would desire if you wanted to keep on good terms with the FCC. Nor is it what you would want for amplifying any form of amplitude-modulated signal, and, of course, ssb is one form of amplitude modulation.

Leaving such an extreme, really a class-C stage, and looking toward class B or AB, the classes usually associated with linear amplification, you do not find a high degree of efficiency. The true efficiency, the conversion of dc input power into rf output power of the desired

(really neither difficult to build nor expensive to buy) and a simple spectrum analyzer, such as the Heathkit SB-620. The two-tone audio-frequency signal generating device needs to embody a low duty cycle pulser, something that will let the signal through for a third or less of the time. This permits running the amplifier under test at full load for moderate periods of time without cooking the tubes.

Of course, for any power output test you have to have a dummy load/rf wattmeter. And for the dc input measure-

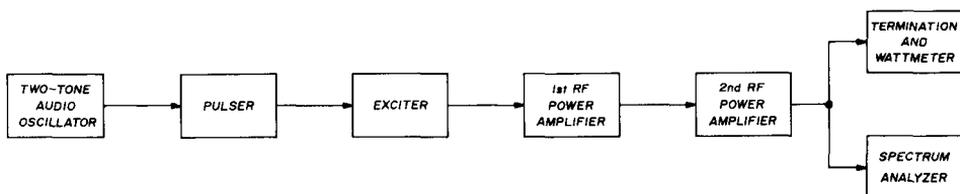


fig. 1. Equipment arrangement for comparing the efficiency of two rf power amplifiers. The amplifiers are switched in and out of the line with their own built-in bypass relays.

frequency, is not significantly less than that achieved with a class-C stage. What you do find, however, is the possibility of approaching truly linear amplification, amplification in which the output waveform is a true reproduction (in every manner except amplitude) of the input waveform. And this is what you desire when you build, buy, or tune up an amplifying stage connected to the output of a ssb exciter. A serendipitous side effect of such a stage is a satisfying reduction in the generation of harmonics.

### how to do it

This suggests some guidelines for comparative tests. You would like to set some limits on just how much of a departure from linearity you will tolerate in the interest of efficiency. Manufacturers do this sort of thing; they come up with a figure like, say, -35 dB for third-order intermodulation products.

Like most trustworthy and informative measurements, such a measurement requires rather expensive tools. In this case, the tools are a two-tone oscillator

ments you have to have the needed voltage and current meters.

As most linear amplifiers are built with integral dpdt bypass relays, a convenient way of making a comparison test is to arrange the two linear amplifiers in series, following the exciter. The control actuating the in-circuit or out-of-circuit status of the bypass relay can then be used to instantly select the particular amplifier to be observed. Fig. 1 shows a block diagram of the necessary arrangement.

### linearity

Since it's highly probable that any amplifier approaching true linearity will have low harmonic output, it is not necessary to use a wideband spectrum analyzer to check the relative (or the absolute) power contained in harmonics. Only a narrow-band analyzer is needed. The odd-order, or intermodulation, distortion products shown in fig. 2 can be observed only with an analyzer that has fairly good resolution. However, such resolution is not absolutely necessary; an ideal of relative magnitude of, say,  $2f_2 - f_1$

# L. I. Electronic Supermart

(Off the wall self service)

New P.C. Boards — G10, 1 oz. - 1 side copper-fiber glass

6" x 6", 80¢ ea. — 6 x 12, \$1.50 ea. - 12 x 12, \$2.85 ea.

New P.C. Boards — G10, 1 oz. - 2 side copper-fiber glass

6" x 6", \$1.10 ea. - 6 x 12, \$2.00 ea. - 12 x 12, \$3.75 ea.

New P.C. Boards — G10, Fiber glass punch:

F Pattern 4.5 x 6.5, .062 holes, 5 per 1" \$1.30

P Pattern 4.5 x 6.5, .042 holes, 10 per 1" \$1.35

G Pattern, 4.5 x 6.5, .062 holes, \$1.30

Pkg. 10 Bircher P.C. Board, metal 2" slides \$1.00

Package of 50 flea clips for above punched Boards, .062 75¢

30 ¼ or ½ W resistors, packaged 5 per value your choice of values \$1.00

25-1W resistors, packaged 5 per value, your choice of values \$1.00

15-2W resistors, packaged 5 per value, your choice of values \$1.00

5 ¼ or ½ W, 1% resistors, packaged 5 per value, your choice of values .50

5 ceramic disk caps, .001-01, packaged 5 per value, your choice of values .50

5 mica dip caps, 1 pf-150 pf, packaged 5 per value, your choice of values .50

5 mica dip caps, 180 pf-820 pf, packaged 5 per value, your choice of values .75

5 mica dip caps, 910 pf-1500 pf, packaged 5 per value, your choice of values \$1.00

Wire Kit #22 solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit # 22 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 Solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

10' — Ten cond. ribbon wire, color coded, #22 or #24, stranded \$1.50

C & K #7101 mini switch, SPDT on-on \$1.05

C & K #7103 mini switch, SPDT on-off-on \$1.20

C & K #7201 mini switch, DPDT on-on \$1.35

C & K #7203 mini switch, DPDT on-off-on \$1.55

Alco 105D MST momentary on-off-momentary on \$1.25

Central Lab DPDT push momentary. SPEC. 4/ \$1.00

Connectors, PL259, \$.45; PL258, \$.70; 175U or 176U, \$.20 ea.; UG 88 cu., \$.50; UG 201 a/u (N to BNC adapter), \$.75; RCA to UHF, \$.90.

Encapsulated chokes 1uh to 5 Mh, choice 3/ \$1.00

Vaco type mini bridge rectifiers, approx. ¾" sq. size: 2 amp. - 50 v., \$1.25; 4 amp. - 50 v., \$1.25; 6 amp. - 50 v., \$1.25; 2 amp. - 100 v., \$1.25; 4 amp. - 100 v., \$1.25; 6 amp. - 100 v., \$1.25; 2 amp. - 200 v., \$1.50; 4 amp. - 200 v., \$1.50; 6 amp. - 200 v., \$1.50; 2 amp. - 400 v., \$1.50; 4 amp. - 400 v., \$1.50; 6 amp. - 400 v., \$1.50

Triacs — thermo tab package — 1 amp. - 400 v., \$.80 ea.; 3 amp. - 400 v., \$1.40 ea.; 4 amp. - 200 v., \$1.20 ea.; 6 amp. - 200 v., \$1.40 ea.; 6 amp. - 400 v., \$1.60 ea.; 6 amp. - 500 v., \$1.80 ea.; 8 amp. - 200 v., \$1.60 ea.; 8 amp. - 500 v., \$1.80 ea.

To-5 case, 1 amp. - 200 v., \$.70 ea.; 1 amp. - 400 v., \$1.00 ea.

SCR 200 v. - 8 amp. thermo tab \$ .80 ea.

SEND SELF ADDRESSED ENVELOPE FOR FREE MAILER. INCLUDES MANY HUNDREDS OF ITEMS NOT LISTED ABOVE.

Send check or money order - include 60¢ to cover parcel post and handling. UPS shipping available. Minimum order \$4.50.

FREE BONUS WITH EACH \$10.00 ORDER

50' SPOOL 600 V. #22 PVC WIRE

## KRP

### ELECTRONIC SUPERMART, INC.

219 WEST SUNRISE HIGHWAY  
FREEPORT, L. I., N. Y. 11520  
516-623-3346-9

as compared with either  $f_1$  or  $f_2$  (which probably will be seen as a single blip) can be quite definitive. By making a note of this relationship and then shifting over to the other amplifier, you can form an accurate idea of their relative linearity.

Having established an idea of relative linearity, the next step is to optimize the linearity of each amplifier by careful adjustment of tuning, loading and rf

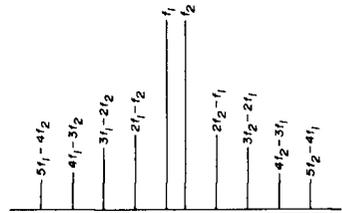


fig. 2. Spectrum of odd-order distortion products in an rf amplifier with input frequencies  $f_1$  and  $f_2$ .

excitation. Then, make both amplifiers exhibit equal linearity by decreasing the rf excitation to the amplifier having the greater distortion. Measure its dc power input and rf power output. Go to the other amplifier, remembering to restore the rf excitation to its optimum value, and measure its input and output. Then and only then are you in a position to talk about the relative efficiency of two different rf power amplifiers.

### references

1. Lawrence F. Gray and Richard Graham, "Radio Transmitters," McGraw-Hill Book Co., New York, 1961.
2. Ralph S. Carson, "Principles of Applied Electronics," McGraw-Hill Book Co., New York, 1961.
3. E.W. Pappenfus, Warren B. Brune, and E.O. Schoenike, "Single Sideband Principles and Circuits," McGraw-Hill Book Co., New York, 1964.
4. B. Whitfield Griffith, Jr., "Radio-Electronic Transmission Fundamentals," McGraw-Hill Book Co., New York, 1962.
5. Morris Engelson, "Spectrum Analyzer Circuits," Tektronix, Inc., 1969.
6. Dan Welch, "Spectrum Analyzer Measurements," Tektronix, Inc., 1969.

ham radio

**WHY SETTLE FOR HALF A RIG?**  
 Get ALL the  
 versatility, capability  
 and quality you REALLY want...  
 at a surprisingly low price!



**Clegg**  
**FM 27B**

The only 2-meter rig  
 with any combination of  
 Transmit or Receive Frequency  
 from 146 to 148 MHz.

After buying any other transceiver, plus an amplifier with 25 watts or more and a handful of crystals, you've spent more than the cost of the Clegg FM 27B. And you still don't have the **only** rig that's totally integrated with all the coverage built-in. Why settle for half a rig? Get it all—get a Clegg FM 27B!

Amateur Net \$479.95



**Clegg** DIVISION

3050 Hempland Road  
 Lancaster, Pennsylvania 17601  
 (717) 299-3671 Telex: 84-8438

CLEGG—the PROFESSIONAL amateur line!

The Clegg FM 27B ACTUALLY COSTS YOU  
 LESS in the long run!  
 Check these specifications:

**GENERAL**

**POWER REQUIREMENTS:** 12 to 14 VDC  
 Current Consumption at 13.5 VDC:  
 Receive: 400 Ma squelched,  
 1.2 amps un-squelched.  
 Transmit: 6 amps max.

**DIMENSIONS:** 7 $\frac{3}{8}$ " x 3 $\frac{1}{2}$ " x 9 $\frac{1}{4}$ "  
 deep; 4 lbs. net weight.

**RECEIVER**

**TUNING RANGE:** 146.00 to 148.00 MHz,  
 continuously tuneable with reset  
 capability of approx. 1 KHz to any  
 frequency in range.

**SENSITIVITY:** .35  $\mu$ V max. for 20 db  
 quieting; .1  $\mu$ V for reliable squelch action.

**SELECTIVITY:** 11 KHz at 3 db; Less than  
 30 KHz at 70 db. Adjacent (30 KHz  
 spaced) channel rejection more than 70 db.

**AUDIO OUTPUT:** 2.0 watts (min.) at less  
 than 10% THD into internal or external  
 ohm speaker.

**TRANSMITTER**

**TUNING RANGE:** Same as RECEIVER.  
**POWER OUTPUT:** 25 watts Min. into 50  
 ohm load. P/A transistor protected  
 for infinite VSWR.

**MODULATION:** Internally adjustable up to  
 10 KHz deviation and up to 12 bd  
 peak clipping.



## ham radio sweepstakes winners

WA9YII wins grand prize,  
puts new Drake TR-4C  
hf transceiver and  
L-4B linear on the air;  
WB4KIT is lucky winner  
of Robot sstv camera  
and monitor


*It was more work than ever, opening ten's of thousands of your letters and trying to keep our records straight. However, the 1973 Ham Radio Sweepstakes is now history, and our local post office can take a breather and so can we.*

This year's contest seems to have created more interest than ever before, not only through the mail, but also at many of the Hamfests we have visited this year such as SAROC, the Tropical Ham-boree, the Dayton Hamvention and a number of others.

Our Grand-prize winner was Randy E. Thompson, WA9YII. He won a brand new R.L. Drake TR-4C Transceiver and AC power Supply plus a Drake L-4-B Linear Amplifier. Randy tells us that although he is now a Technician he is going for his Advanced license in the very near future. He is in the graduating class at the Vocational-Technical Institute of Southern Illinois University and has accepted a position with the National Accelerator Laboratory near Batavia, Illinois.

The new TR-4C offers everything that made it's predecessor, the TR-4, so popu-

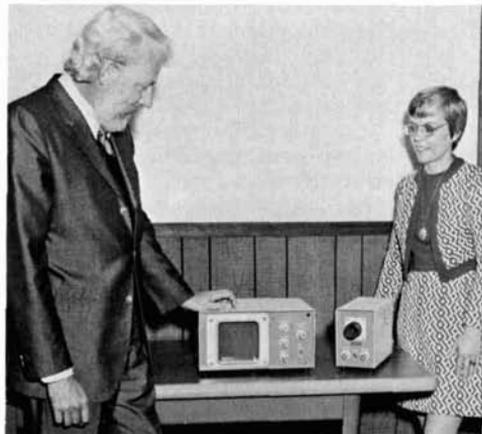Jim Fisk and Pat Hawes of the Ham Radio editorial staff look over the Robot SSTV Camera and Monitor won by WB4KIT.



Skip Tenney, W1NLB, Publisher, Ham Radio Magazine

lar, plus a number of new features including 1-kHz dial calibration. This versatile transceiver provides ssb, CW and a-m operation on all amateur bands from 80 to 15 meters plus 28.5 to 29.1 MHz. Accessory crystals are available to cover the complete 10 meter band.

Of course, the L-4-B is one of the best known 2-kW amplifiers in the business. Rugged and dependable, it features a trouble-free, conservative design. Randy should be set for many years of service from this fine equipment. The L-4-B uses a pair of Eimac 3-500Zs in a class-B grounded-grid circuit featuring a broadband-tuned input, negative rf feedback and transmitting agc for higher audio level without clipping.

The second prize, a Robot Slow-Scan Television Camera and Monitor, created much interest from many of our entrants. This is the same package that has added a whole new dimension, that of sight, to amateur radio for so many operators all over the World. The lucky winner of the Robot Model 70 SSTV Monitor and Model 80 SSTV Camera was John S. Harvey, WB4KIT. We'll all be "looking" for him on the air very soon.

Both the Robot Camera and the Robot Monitor feature an all solid-state design except for the picture and camera

**Skip Tenney, W1NLB, publisher of Ham Radio, picks the Grand Prize winner in the 1973 Ham radio Sweepstakes. Looking on are assistant publisher Hilda Wetherbee, editorial assistant Pat Hawes, WN1QJN, and editor Jim Fisk, W1DTY.**



**Skip Tenney calls WA9YII to let him know he has won the Grand Prize — a new Drake TR-4C transceiver and L-4B linear. Randy, obviously very pleased, said, "This is the first time I've ever won anything!"**

tubes. Particular design attention has been given to making these units easily adaptable to virtually any ssb station. A couple of patch cables, one to the microphone jack and one to the audio output, is all that is necessary to connect the equipment to your rig, and put it on the air.

Versatility plus was the third prize. Each of our three third-prize winners received a Drake TR-22 Two-Meter FM Transceiver. This is that wonderful little unit that is equally at home over your shoulder, in your car or at home. It can operate on its own battery pack or on 12 Vdc or 115 Vac. John R. Low, K3YHR, Vinton A. Buffenager, W6PSC, and Robert K. Jackson, WBØISI will be coming through on their local repeaters in the near future, and we're sure that they'll be saying good things about their nifty new rigs.

We're sorry that everyone couldn't win this year, but there are some exciting, new prizes that we're lining up for 1974. We hope that you'll plan on winning one of them and we will try our best to help you out.

ham radio

# the ham notebook

## arc suppression networks

Unless special precautions are taken, operation of a relay or switch in close proximity to sensitive electronic circuits is a potential source of trouble. This trouble generally results from arcs caused by opening of the relay contacts, causing transients that can easily interfere with the proper operation of sensitive circuits.

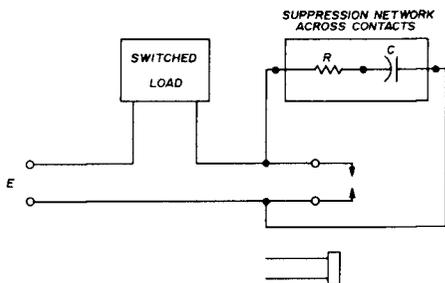


fig. 1. Simple arc-suppression network eliminates transients which can cause problems in sensitive circuits. Values of R and C may be determined with nomograph in fig. 2.

The effects of these arcs can be minimized by the installation of an arc suppression network directly across the relay contacts to absorb the energy which would otherwise be dissipated in the arc itself.

The network itself is simply a resistor and capacitor in series. The capacitor just "absorbs" the arc by charging when the contacts open (see fig. 1). The resistor limits the current generated by the discharging capacitor upon contact closure.

Were it not for the resistor, severe contact pitting could result from large momentary discharge currents.

The optimum values of R and C can be chosen by the equation

$$R = \frac{E}{10 (3.16 \sqrt{C})^{1 + 50/E}}$$

where R is the resistance in ohms, C the capacitance in microfarads and E the open-circuit potential in volts. Obviously, this equation is rather unwieldy, and selection of values from it could prove to be quite a chore! For convenience, this equation has been solved graphically in fig. 2. By using this nomograph any number of R-C combinations can be chosen with ease.

Suppose, for example, that a suppress-

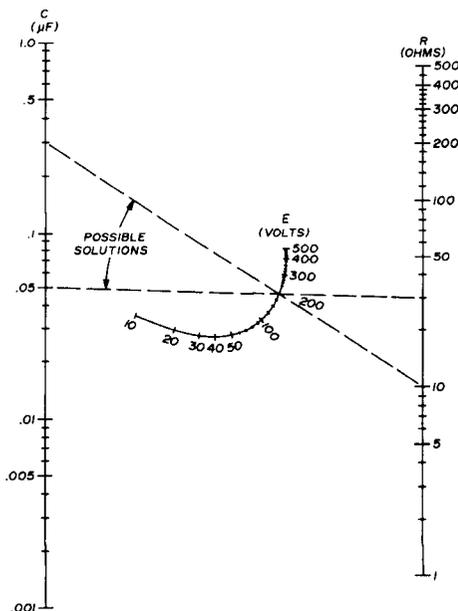


fig. 2. Nomograph for finding R and C values for the arc-suppression network shown in fig. 1.

sion network must be selected for a switched potential of 200 volts and that a 0.05- $\mu$ F capacitor is readily available. Drawing a line from 0.05 on the C scale through 200 on the E scale yields a value of 30 ohms on the R scale. The network, therefore, will be the series combination of 30 ohms and 0.05  $\mu$ F. An infinite number of other combinations of R and C are possible, and the final choice of components will probably depend upon what you have on hand. Another suitable choice here would be 0.3  $\mu$ F and 10 ohms. This can be verified from fig. 2.

Since the nomograph is so easy to use, several combinations of R and C should be tried to find the one which is physically smallest and can be constructed with only two standard values. The result will be a network which will go a long way in eliminating headaches caused by contact arcing.

James McAlister, WA5EKA

## pilot-lamp life

For some time, I have been experiencing relatively short life for the 120-volt pilot lights I use. Investigation showed that the green light had short life, but the high-voltage indicator (red bulb) seemed to last indefinitely. The reason? The red indicator came on by steps — that is, half-power, then full power.

An ohmmeter check showed that the hot resistance of the S6 bulb was 2400 ohms, while the cold resistance was only 200 ohms. This meant that the small bulb had to sustain a temporary power surge of 72 watts. I recalled that BC stations, where dependability is of great importance, have, for years, used a dropping resistance in series with most indicator lamps. The resulting setup at W2OLU calls for a dropping resistor of approximately 450 ohms. This is not at all critical — any value from 400 to 500 ohms will do. The resultant *hot* current is about 42 mA and the maximum surge is reduced to a small fraction of its former value.

Neil Johnson, W2OLU

## pogo stick for reflex klystrons

Stabilizing klystrons is an important part of the microwave station. There are several ways of accomplishing this, but the following, I feel, is more advantageous than others. The primary problem is connecting the output of the afc network which is operating at low voltage levels to the high voltage levels of the klystron.

The output from the receiver discriminator is around zero. It is therefore logical to make the afc compatible. Type 741 op amps connected as an integrator, impedance matcher and inverter perform this function at minimum cost and parts.

Now the problem comes to light. How do we get this to the reflector of the klystron and do it inexpensively with semi-conductors? After all, excluding the klystron, the entire station consists of semiconductors. Let's not spoil it.

ICU1 is not necessary to the operation of this circuit (see fig. 3). However, with the afc disconnected, the voltage at point C is not controllable. The fact that the input to U1 is a voltage node and the loop is operating around zero means we can open the loop at point X and not appreciably change the output frequency of the klystron. The slight change that does occur is due to the input offset current of the 741 IC.

Let's disconnect R7 at point X and look at the operation of this circuit. The output of U1 is zero with R7 open or grounded. If point A is zero, and the base of Q1 is at -12 V, we must have approximately 1 mA through R1. If the emitter current of Q1 is 1 mA then the collector current is 1 mA; 1 mA through R2 gives us 75 volts across R2.

Note the voltage divider R3 and R4 which makes the base of Q2 -150 V. Therefore, the emitter must be the same, plus one diode drop, which is insignificant. With the emitter of Q2 at -150 V, 75 V across R2 and 12 V across R1, we are left with approximately 63 V across Q1.

The reason for Q2 is now evident. It is not necessary except that if only Q1 was used it would have to be a high-voltage device which implies high cost. As the circuit stands, Q1 and Q2 can be 100 volt devices and still maintain a good safety margin.

We established earlier that the current through R1 was 1 mA. Q1 and Q2 are in series with R1, thus the current in the

R9 reduces, making point C more negative. With a negative voltage at point X, A goes positive. More current results in the string causing point C to become less negative (positive direction).

By changing R7, the gain of U1 changes, thus changing the loop transfer function (ratio of point-X voltage change to point-C voltage change). The value of R7 will thus be determined primarily by

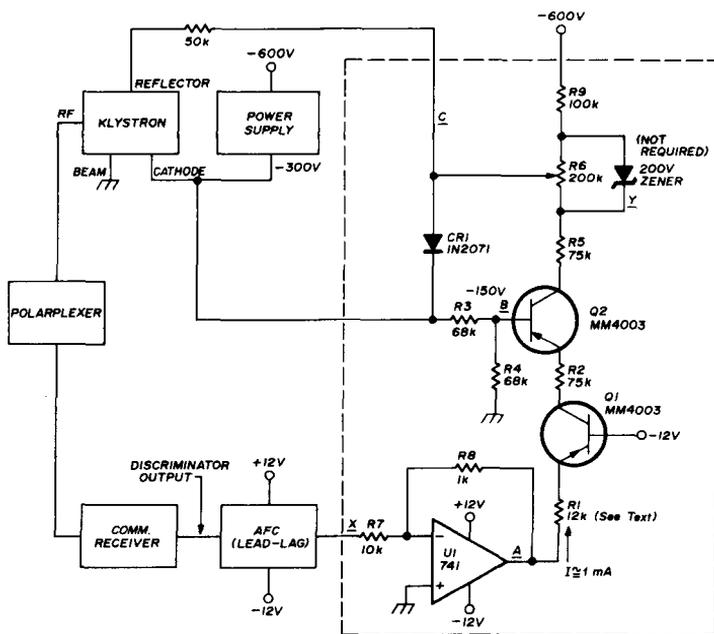


fig. 3. Solid-state voltage-tracking circuit for reflex klystrons.

series string is 1 mA. This results in Q2 and R5 having the same voltage drops as Q1 and R2 respectively. The voltage at point Y is now 300 volts. This leaves 300 volts across R6 and R9. R6 is a ten-turn Helipot for adjusting the voltage on the klystron repeller so it is operating in its proper mode (160 volt mode is used at this station).

Understanding that Q1, Q2 and the resistors constitute a series circuit is important. With this in mind let's put a positive voltage at point X. Point A goes negative (U1 inverts). With point A less than zero the current in R1 reduces, thus reducing the current in the series string. With a reduced current the voltage across

the transfer function of the particular afc circuit used. (In my station U1 is operated with a gain of -10.)

Resistor R1 is chosen so the voltage at point-Y is approximately -350 V (slightly more than 1 mA). This is to insure a good voltage swing at point C without causing point C to go above -300 volts. CR1 is for protection of the klystron. The repeller should never go positive with respect to the cathode.

This circuit is in use at two stations operating at 3335 and 3365 MHz with great results. The klystron is able to track over its entire electrical tuning range. Total cost was less than \$5.

Francis E. Adams, W6BPK

# RIGHT ON!

## Heathkit "Maxi Rig" with Digital Display



New Heathkit Digital Frequency Display...counts the 3 frequencies produced in receiver, computes and displays operational frequency within 100 Hz accuracy. Six bright digits let you read frequencies 80 through 10 meters from up to 30 ft. away. Reads kHz to 5 places, plus tenths of a kHz. No band-switching necessary. Operates with Heathkit SB-100/101/102 Transceivers; HW-100/101 Transceivers; and SB-300/301/303 Receivers. With transceivers, it displays both transmitted and received frequencies.

Kit SB-650, 10 lbs. ....179.95\*

Heathkit SB-102 — the "big one"...with better than 0.35 $\mu$ V sensitivity for 10 dB S+N/N; solid-state LMO with 1 kHz calibration; less than 100 Hz drift per hr. after 10 min. warmup; dial resettable to 200 Hz and bandspread equal to 10 ft. per MHz; switch selection of built-in 2.1 kHz SSB filter or optional 400 Hz filter, plus upper and lower sideband; built-in 100 kHz crystal calibrator; 180 watts PEP SSB input, 170 watts CW; built-in sidetone and VOX; 5-position metering facilities.

Kit SB-102, 24 lbs. ....385.00\*

Heathkit SB-220 2 kW Linear...with 2 Eimac 3-500Zs in grounded grid circuit delivering up to 2000 W PEP SSB or a full 1 kW on both CW & RTTY, requiring only 100 W of drive; broad-band pre-tuned pi input; solid-state 120/240 VAC power supply; circuit breaker; zener diode regulating operating bias; ALC; metered grid current, high voltage and relative power; big quiet fan.

Kit SB-220, 69 lbs. ....369.95\*

Visit your nearest Heathkit Electronic Center...or send for FREE catalog

**HEATHKIT ELECTRONIC CENTERS — ARIZ.:** Phoenix; **CALIF.:** Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; **COLO.:** Denver; **CONN.:** Hartford (Avon); **FLA.:** Miami (Hialeah); **GA.:** Atlanta; **ILL.:** Chicago, Downers Grove; **IND.:** Indianapolis; **KANSAS:** Kansas City (Mission); **MD.:** Baltimore, Rockville; **MASS.:** Boston (Wellesley); **MICH.:** Detroit; **MINN.:** Minneapolis (Hopkins); **MO.:** St. Louis; **N.J.:** Fair Lawn; **N.Y.:** Buffalo (Amherst), New York City, Jericho; **L.I.:** Rochester; **OHIO:** Cincinnati (Woodlawn), Cleveland; **PA.:** Philadelphia, Pittsburgh; **R.I.:** Providence (Warwick); **TEXAS:** Dallas, Houston; **WASH.:** Seattle; **WIS.:** Milwaukee.



World's largest selection of electronic kits

**HEATH COMPANY, Dept. 122-7**  
Benton Harbor, Michigan 49022

Please send FREE Heathkit Catalog.  
Enclosed is \$ \_\_\_\_\_, plus shipping.

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*Mail order prices; F.O.B. factory. AM-285

# new products

## electronic frequency counter



Regency Electronics has moved in to a new area of electronic equipment with production of a six-digit electronic frequency counter. The all American made unit, the EC-175 Electronic Counter, is priced at \$449.00

The unit's low price, combined with high stability, ease of operation and portability make the Regency Counter very desirable. The EC-175 is designed to enable the operator to measure crystal frequencies without mathematical computation. The counter reads out frequencies ranging from 5 Hz to 175 MHz. A five-position range switch with gate times of 1 ms, 10 ms, 100 ms, 1 second and 10 seconds allows direct measurement of any in-range frequencies to within 0.1 Hz.

The six-digit LED display features automatic blanking, automatic decimal point positioning and leading zero sup-

pression. There is an overrange LED indicator for readings over 6 digits and separate LED indicator for count rate.

EC-175's proportional oven-controlled time base gives a short-term stability of 2 parts in  $10^8$  per day for FCC certification work. Long term stability is one part in  $10^6$  per 6 months. Temperature stability is 3 parts in  $10^9$  per degree Centigrade from zero to 50°C.

The Regency frequency counter has a built-in 100-kHz harmonic generator for direct calibration to WWV. A 10,7-MHz crystal oscillator for afc locking and i-f alignment work is also a built-in feature. A built-in mosfet preamp gives sensitivity of 100 mV at 100 MHz.

The Regency EC-175 Electronic Counter is now available from Regency distributors throughout the country. For more information, write to Regency Electronics, Inc., 7900 Pendleton Pike, Indianapolis, Indiana 46226 or use *check-off* on page 110.

## keyer memory



A large capacity programmable-reprogrammable CW message memory, designed as a plug-in accessory for the EK-420 keyer, has been announced by Curtis Electro Devices. Aimed to satisfy the most demanding contest or traffic handler, the standard KM-420 offers a solid-state memory capacity of 1,024-bits — equivalent to 100 Morse characters. A second, optional, 1,024-bit plug-in memory doubles this capacity. For maximum flexibility, the memory organization is switch selected to yield four different program arrangements.

Programs are selected and started by

pushbuttons; terminated by a message pause or by manual break-in. A "reset" button instantly stops and resets the memory, a "hold" function allows manual insertion into a sequence. A 1 to 20 second repeat feature allows send and wait operation.

Memory programming is accomplished simply by sending the desired sequence in the "record" mode. Messages may be written as often as desired and stored indefinitely. Automatic and manual sending are indistinguishable. The KM-420 is priced at \$299.95. The optional extra memory is \$34.95. A remote control head for the Brown Brothers CTL Key is also \$34.95.

For additional information, contact Curtis Electro Devices, Inc., Box 4090, Mountain View, California 94040, or use *check-off* on page 110.

## vintage radio

This new pictorial album of old radio equipment, edited by Morgan E. McMahon, should hold particular interest to amateurs and antique radio buffs who would like to know more about radio during the early part of the century. The book is full of interesting photographs and text describing much of the early apparatus used by such wireless pioneers as Marconi, DeForest and Sir Oliver Lodge. There's a complete section on early receivers including models manufactured by Grebe, Remler, Atwater-Kent and RCA; early vacuum tubes, coherers, crystal sets, headphones, horn speakers, test equipment and many special components. The list of 3000 radio models by manufacturer and year should be a particular aid to collectors who are having trouble dating a particular radio in their collection.

Soft-bound, 263 pages, hundreds of photographs and drawings, \$4.95. Also available with hard cover for \$6.95. Order from Vintage Radio, Box 2045, Palos Verdes Peninsula, California 90274. For more information, use *check-off* on page 110.

## NEW


Transformer — American Made — Fully shielded. 115 V Primary. Sec — 24-0-24 @ 1 amp with tap at 6.3 volt for pilot light.  
Price — A low \$2.90 each ppd.

### DISC CERAMIC CAPACITORS ALL FULL LEADS AMERICAN MADE

.01 Mfd @ 1000 Volts  
.001 Mfd @ 1000 Volts  
.005 Mfd @ 1000 Volts  
.01 Mfd @ 500 Volts  
.001 Mfd @ 500 Volts  
.015 Mfd @ 500 Volts

YOUR CHOICE 20 for \$1.00 ppd.

### MOLDED 1 1/2 AMP BRIDGE RECTIFIER

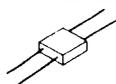

1200 Volts PIV Per Leg. Ideal For P.C. Board Use. Size Approximately 1/2" Square x 3/16" Thick.  
\$1.00 each 3 for \$2.50 ppd.



### 3 AMP BRIDGE RECTIFIER


400 Volts PIV Per Leg. Manufactured by Semtech.  
\$1.00 Each or 3 for \$2.50 ppd.




Black, Aluminum Anodized, Heat Sink. Size Approximately 4 3/4" x 1 3/8" h. x 1 1/2" w. Predrilled For TO-3 Transistors. Delco Part #7277151. Factory New. 75¢ Each, 3 for \$2.00 ppd.
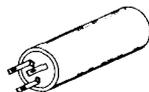
### DUAL SECTION ELECTROLYTIC CAPACITOR.

100 mfd x 100 mfd Both at 380 Volts. Common Ground. Ideal for Transceiver power supplies.  
\$1.00 ea. ppd.



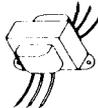High quality, American Made Transformer. 115 Volt Primary. Secondary 17-0-17 Volt @ 150 ma. Tap at 6.3 Volt For Pilot Light. Ideal For Transistor Pre-Amps, VFO's, etc. Fully Shielded.  
\$1.50 Each ppd.



Power Transformer. 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3".  
Price: \$2.50 Each ppd.

6.3 Volt 1 Amp Transformer. Fully Shielded  
\$1.60 Each ppd.

Toroids-Unpotted-Centertapped. Your choice — 88 mhy or 44 mhy  
5 for \$2.00 ppd. or 15 for \$5.00 ppd.

Transformer — American Made fully shielded. 115 Volt Primary  
Secondary #1 18-0-18 Volts @ 4 Amps  
Secondary #2 5 Volts @ 2 Amps  
A very useful unit for LV Power supply use.  
Price — A low \$4.75 ppd.

### PRINTED CIRCUIT BOARD MATERIAL

Factory Direct. All board 2 oz. Copper 1/16" Glass Epoxy

3" x 3" 45¢ ea. ppd.  
3" x 6" 85¢ ea. ppd.  
6" x 9" \$2.75 ea. ppd.  
12" x 12" \$6.00 ea. ppd.

Pa. Residents add 6% State sales tax  
ALL ITEMS PPD. USA



**m. weinschenker**  
K 3DPJ BOX 353 · IRWIN, PA. 15642

# know this sign



To most people this is a symbol from Greek mythology. But to hundreds of thousands of active amateurs, Pegasus is the symbol of the Radio Amateur CALLBOOK the single most useful operating reference for active amateur stations. The U.S. Edition lists over 285,000 Calls, Names and Addresses in the 50 States and U.S. possessions while nearly 200,000 amateur stations in the rest of the World are listed in the DX edition.

Both editions contain much other invaluable data such as World Maps, Great Circle Maps, QSL Managers around the World, ARRL Countries list and Amateur Prefixes around the World, Time information, Postal Information and much, much more. You can't contest efficiently, you can't DX efficiently, you can't even operate efficiently without an up to date CALLBOOK.

To make the CALLBOOK even more valuable, three supplements are issued each year which bring your copy completely up to date every three months. These are available at a modest extra cost. Full details in every CALLBOOK.

Get your copies of the big new 1973 CALLBOOKS today.

**US CALLBOOK**  
(less service editions)  
Just \$8.95

**DX CALLBOOK**  
(less service editions)  
Just \$6.95

**US CALLBOOK**  
(with service editions)  
\$14.95

**DX CALLBOOK**  
(with service editions)  
\$11.45

Mail orders add 50¢ per CALLBOOK postage and handling.

See your favorite dealer or send today to:

WRITE FOR FREE BROCHURE  RADIO AMATEUR **callbook** INC.  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044


## MECL data book

Motorola's new *MECL Data Book* is a fact book and a design guide wrapped in one cover. Basic performance specifications are provided for each IC device in the MECL II, MECL III and MECL 10,000 logic families. In 410 pages, complete dc, ac and performance data are given for each MECL product announced up to press-time. Convenient abbreviated guides offer a quick selector for MECL logic blocks.

In the 36-page general information section is contained a synoptic discussion of topics of value to the designer planning a MECL system: product performance data, design rules, system considerations, etc. In addition, dimensioned drawings of MECL IC packages are shown. References to the extensive MECL software support available are included by way of Motorola Application note abstracts, as well as references to a sampling of MECL articles in the trade press.

Motorola's *MECL Data Book* may be purchased for \$2.00 per copy. Copies may be obtained by sending check or money order payable to Motorola, Inc. at Post Office Box 20924, Phoenix, Arizona 85036.

## rf load resistor

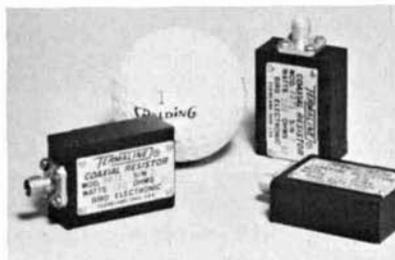

A nearly hundred-to-one breakthrough in size reduction for a coaxial rf load resistor has been accomplished by Bird Electronic Corporation. The New *Termline Miniload*® Model 8071 100-watt load weighs just 1¼ ounces and requires less than 3/4 cubic inch of space. Designed for reflection-free termination of 50-ohm coaxial systems, these dry miniature

high-power loads may be directly mounted to equipment cabinets or panels which serve as its heat sink.

*Miniloads* can be built into avionics transceivers, laboratory power oscillators or any rf signal source where space is at a premium and the environment is unfavorable. In this unique design, the terminating element is solidly tied to the component body, resulting in the lightest, tiniest package available. Model 8071 miniature construction also permits excellent performance over the entire frequency range of dc - 2000 MHz (vswr is below 1.1 from dc - 1000 MHz, and below 1.2 to 2000 MHz) with a female SMA connector.

The Model 8071 100-watt *Termaline Miniload*® is priced at \$125. For more information, write to Bird Electronic Corporation, 30303 Aurora Road, Cleveland (Solon), Ohio 44139, or use *check-off* on page 110.

## computer dictionary and handbook

Computers are quickly becoming common-place in today's technological society. In fact, computer language has expanded an astounding 250% in the past ten years. The second edition of the popular Howard Sams *Computer Dictionary and Handbook* is designed especially to keep abreast with the constantly changing computerized world.

It's new and updated and compiled from an information base of over 22,000 separate definitions and concept explanations. Each entry in the first edition has been checked and rechecked. Whenever necessary, the definition has been revised to reflect the present state of the art — or to give added meanings to the term. Also the hundreds of new terms — not in use when the first edition was produced — have been clearly defined and added.

Over 450 pages are devoted to defining computer-related terms. Principles and procedures of computer systems, computer systems personnel, operations re-

# G & G CATALOG

## MILITARY ELECTRONICS

**24 PAGES, crammed with Gov't Surplus Electronic Gear — the Biggest Bargain Buys in America!**

**SEND FOR YOUR COPY**



**LORAN APN-4**  
FINE QUALITY NAVIGATIONAL EQUIPMENT  
4-Channel long range dual units, will determine exact geographic position of your boat or plane. Indicator and receiver complete with all tubes and crystal. **INDICATOR ID-5950**  
68/APN-4, and Receiver R-9B/APN-4, complete with tubes. Exc. Used

**LORAN R-65/APN-9 RECEIVER & INDICATOR**  
4-Channel single unit system, used in ships and aircraft. Determines position by radio signals from known stations. Accurate to within 1% of distance. Complete with tubes and crystal. **IN LIKE NEW CONDITION.**  
As above, less tubes **\$14.50** **\$5950**  
All accessories for Loran Equipment in stock. 12 or 24 V Inverter Power Supplies available for APN-4 and APN-9 Receivers above. Prices upon request.



**BC-645 TRANSCEIVER**  
15 TUBES. — 435 to 500 Mc. Easily adapted for 2 way voice or code on Ham, Mobile, Television Experimental and Citizens' Bands. With tubes, less power supply in factory carton. Brand new  
**SPECIAL PACKAGE OFFER:** BC-645 Transceiver, Dynamotor and all accessories, including mounting, UHF Antenna Assemblies, control box, complete set of connectors, plugs. **BRAND NEW**

**\$1695**

**\$2695**

**AN/APR-4Y FM & AM RECEIVER "FB" FOR SATELLITE TRACKING!**  
High precision lab instrument, for monitoring and measuring frequency and relative signal strength, 38 to 4000 Mc. in 5 tuning ranges. For 110 x 60 cycle AC. Built-in power supply. Original circuit diagram included. Checked out, perfect.  
**LIKE NEW** **\$7950**  
All Tuning Units Available for Above. Prices upon request.

**APN-1 TRANSMITTER-RECEIVER FM 400-450 Mc. Easily converted for Radio Control or 70 cms. Complete with 14 tubes, dynamotor and wobbulator.**

Exc. Used **\$695** Brand New **\$995**

**TERMS:** F.O.B. NYC. 25% deposit with order, balance COD or remittance in full. **MINIMUM ORDER \$5.00.** Subject to prior sale and price change

**G & G RADIO ELECTRONICS COMPANY**  
45-47 Warren St. Dept. HJ New York, NY 10007 Ph. 212-267-4605

DIGITAL:THEORY,DESIGN,  
CONSTRUCTION

# LOGIC NEWSLETTER ©

SAMPLE COPY \$ 1.00  
LOGIC NEWSLETTER  
POB 252  
WALDWICK,N.J. 07463

# YAESU

Racom has the following Yaesu models  
in stock for immediate delivery.

**FT-101, FTDX-570 & 401,  
External VFO's, Speaker-Patches  
Frequency Counters.**

Also 2 Meter FM Mobile Transceivers  
FT-2FB and FT-2 Auto

Write to Woody, W7RC

**Racom Electronics, Inc.**  
15051 S.E. 128 ST., RENTON, WA. 98055  
Telephone 206-AL5-6656

# KW107

## SUPERMatch *is beautiful!*

- \* E-Z Match Tuner
- \* SWR Meter
- \* Power Meter
- \* Dummy Load
- \* Antenna Switch
- \* 350 watts PEP

**\$134.95**

Ppd in USA & Canada  
Money back Guarantee

Clean up the unsightly  
tangle of wires around  
the shack and your wife  
will think it's beautiful



Send for FREE Literature



**KW Electronics**

55 Bridge St., Plattsburg, NY 12901  
In Canada: 214 Dolomite Dr.,  
Downsview, Ont. M3J 2P8

## FREQUENCY STANDARD



**Only**

**\$32.50**

(less batteries)  
POSTPAID USA

- Precision crystal
- Fully guaranteed
- Markers at 100, 50, 25, 10 or 5 kHz selected by front panel switch.
- Zero adjust sets to WWV. Exclusive circuit suppresses unwanted markers.
- Compact rugged design. Attractive, completely self contained.
- Send for free brochure.

**PALOMAR  
ENGINEERS**

BOX 455, ESCONDIDO, CA 92025

search, number systems, mathematical definitions, and computer languages are just a few of the subjects covered in the 13 appendices. The book concludes with a sound report on the progress, impact, and future of computers.

New additions include: a description of the structure of the computer industry, an evaluation of the latest types of main memory hierarchies, a discussion of the intricacies of the various operating systems and a classification of new information storage devices by function. These and others enhance the reference value of this already popular book.

It's authoritative and unabridged — a must professional resource for libraries, schools, and literally anyone in the computer industry. Written by Charles J. and Charles P. Sippl, 784 pages, hardbound, \$16.95 (\$22.25 in Canada). Available from Comtec Books, Greenville, New Hampshire 03048.

## portable uhf/vhf a-m radio



A new three-band portable radio that includes uhf has been introduced by Radio Shack at a price the company says is well below any other radio with uhf capability presently on the market.

The Realistic® Patrolman®-3 tunes a-m, 450-470 MHz uhf and 144-174 MHz vhf for police, fire, public utilities, business radio, weather broadcasts, two-meter amateur radio and other two-way radio services. The uhf band is currently used by many major metropolitan areas for

police, fire and municipal services. Separate tuning controls are provided for a-m and for uhf/vhf, and each band has a window-type rotary dial for accurate frequency selection. An adjustable squelch control reduces background noise while monitoring.

The Realistic Patrolman-3 is priced at \$49.95 and includes four penlight cells and an earphone, and high-impact case with carrying handle. An optional ac adapter is available for \$4.95.

Realistic products are available at more than 1600 Radio Shack and Allied Radio stores in all 50 states and Canada. For more information, use *check-off* on page 110.

## scientific and technical catalog

Do you work in a scientific or technical career field? Are you an electronics enthusiast or do-it-yourselfer? Then Howard W. Sams & Co., Inc. has a new book catalog published especially for you.

It has 80 information-packed pages featuring over 400 popular hardbound and paperback books. Electronics, electricity, amateur radio, audio & hi-fi, mathematics, plus Audel do-it-yourself books on appliances, mechanical power, sheet metal, etc., are just a few of the dozens of topics covered.

The titles, which range from *ABC's of Electronics* and *Tape Recording for the Hobbyist* to *Modern Dictionary of Electronics* and *Upholstering*, are available through electronic parts distributors and book-stores or directly from the publisher. They're authored by experts and professionals, written in easy-to-understand language, and made completely clear with show-how photographs and drawings.

Copies of the catalog are available free of charge from Robert W. Soel, Advertising Coordinator, Howard W. Sams & Co., Inc., 4300 W. 62nd Street, Indianapolis, Indiana 46268, or use *check-off* on page 110.

**NES**

**NURMI ELECTRONIC SUPPLY**  
1727 Donna Road - West Palm Beach, Florida 33401  
PHONE - (305) 886-8553

**HEP 170** - 2½ Amp, 1,000 Volt diodes. Factory packs of 10. Free HEP Cross Reference with HEP 170 order. 10/\$3.00 - 100/\$25.00

**COMPUTER GRADE ELECTROLYTIC CAPS**


Screw		Terminals - 	
1,400mf	100V \$1.25	18,000mf	10V \$1.10
2,000mf	50V 1.10	18,000mf	25V 1.25
3,000mf	35V 1.00	29,000mf	10V 1.25
3,400mf	25V 1.00	34,000mf	50V 2.00
4,800mf	25V 1.25	39,000mf	10V 1.35
6,000mf	10V .95	90,000mf	20V 2.00
17,000mf	25V 1.25	240,000mf	10V 3.00

**RG - 174/U** - Mini 50 ohm coax. Mfg. - ITT \$2.00/100 Ft.

**TO - 5 SIZE TRIM POTS** - Spectrol No. 82-3-8 or equivalent. Available values: 100, 250, 500, 1,000, 2,000, 5,000 ohms. Mix or match price only: 10/\$5.00 - 25/\$10.00 - 100/\$30.00

**600 OHM CT: 600 OHM CT TRANSFORMER** -

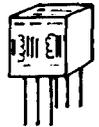Miniature ½" cube. ±1 db 300 Hz-25KHz, ±3 db 100Hz-75KHz, 300 mw. Good for phone patches and lots of other audio uses, fits inside any telephone. Broadcast Engineers love this one. 5/\$4.95 - 10/\$9.00



**BELDEN TEST LEAD WIRE** - 20KV breakdown, 5KV Working, 18 ga., super flexible. Available in Red, Black, Gray, Blue, White, Yellow & Green. Designed for meter leads, test leads, clip leads, etc. Cut to your length. Minimum of 10 feet per color. Factory Fresh! Belden No. 8899. 6¢/Foot - 100 Ft./\$5.00

**RCA 40673 DUAL GATE MOS FET** - Only - 5/\$6.00

**MAGNET WIRE - SUPER SPECIAL** -

Sold by the spool. 16ga-32ga average spool 7 lbs. 33ga-47ga average spool 2 lbs. ONLY:  
16-32 ga. spool . . . . . \$5.00  
33-47 ga. spool . . . . . \$1.50

- TAKE 20% OFF \$20 MAGNET WIRE ORDER -

**26 GAUGE TWISTED PAIR TEFLON WIRE** -

Tinned, solid, great hook-up and speaker wire. 1,100 foot factory sealed spools. Only \$4.75

WE ARE FACTORY AUTHORIZED DISTRIBUTORS FOR MOTOROLA, BELDEN, KEYSTONE, PHILMORE, AIRCO SPEER, etc.

WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

# ECHO II



ALL  
SOLID  
STATE

STOCK  
FREQS:  
16/76  
22/82  
28/88  
34/94

**2 METER  
AMATEUR REPEATER — ONLY \$600.00**

PROVEN STATE OF THE ART DESIGN  
INSTALLATIONS WORKING GREAT IN U.S., EUROPE AND ASIA  
STOCK FREQS DELIVERED IMMEDIATELY, OTHERS 3-4 WEEKS  
WRITE FOR FREE DATA SHEET — FULL MANUAL \$5.00

## DYCOMM

948 AVENUE E P.O. BOX 10116  
RIVIERA BEACH, FLA. 33404

## SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!!

FROM **RP**



### MFA-22 DUAL VERSION

Also Available MFA-2 SINGLE VERSION

- Transmit and Receive Operation: All units have both Simplex and Repeater Modes
- Accurate Frequency Control: .0005% accuracy
- Stable Low Drift Outputs: 20 Hz per degree C typical
- Full 2 Meter Band Coverage: 144.00 to 147.99 MHz. in 10KC steps
- Fast Acting Circuit: 0.15 second typical settling time
- Low Impedance (50 ohm) Outputs: Allow long cable runs for mobiles
- Low Spurious Output Level: similar to crystal output

SEND FOR  
FREE DETAILS

**RP Electronics**

Prices MFA-2 \$210.00 BOX 1201H  
MFA-22 \$275.00 CHAMPAIGN, ILL.  
Shipping \$3.00 extra 61820

## NEW - 440 MHz PREAMPS

**\$54.95**

POSTPAID  
432PA-1



Two stage preamps use KMC Bipolar and Mosfet Transistors. 20db gain, 20 MHz bandwidth. These are high quality preamps suitable for the most demanding applications. AC models have die cast case, others have metal enclosure.

432PA	3.5db NF	12VDC	\$29.95
432PA-1	3.5db NF	117VAC	\$54.95
432PC	1.5 to 2.0db NF	12VDC	\$69.95
432PC-1	1.5 to 2.0db NF	117VAC	\$94.95

Write for our new catalog.

**JANEL**  
LABORATORIES P. O. BOX 112  
SUCCASUNNA, N. J. 07876  
201-584-6521

## WE'VE MOVED!

Your  
**VHF-FM Headquarters**  
for South Florida

Now in new larger quarters to keep up  
with your growing needs.

## EMPORIUM SOUNDS OF POMPANO

1304 E. Atlantic Blvd.  
Pompano Beach, Florida 33060  
305-782-3464

Drake gear keeps getting better and better...

NOW, OUR FINEST...  
THE NEW  
**Drake C-Line**

**NEW FEATURES:**

- 1 kHz Dual Concentric Dial Readout
- Receiver and transmitter lock together in transceive operation
- No side controls
- Iridited cadmium-plated chassis
- Compatible with all previous Drake lines



**R-4C Receiver**

The receiver hams have dreamed of...

**NEW R-4C FEATURES:**

- 8-pole crystal filter combined with passband tuning, SSB filter supplied
- Provision for 15 additional accessory 500 kHz ranges
- Transistorized audio
- Optional high-performance noise blander
- AVC with 3 selectable time constants
- Optional 8 pole filters available for CW, AM, RTTY
- \$499.95



**T-4XC Transmitter**

The one worthy of the R-4C

**NEW T-4XC FEATURES:**

- Plug-in relay
- More flexible VOC operation; Including separate delay controls for phone and CW
- Crystal control from front panel for amateur, Mars, commercial uses
- Provision for AFSK RTTY operation
- \$529.95

See for yourself — at your dealer's.

**R. L. DRAKE COMPANY**



**DRAKE**®

540 Richard Street, Miamisburg, Ohio 45342 • Phone (513) 866-2421 • Telex 288-017

## 400% MORE AVERAGE SSB POWER OUTPUT

USE A **MAGNUM SIX**  
THE QUALITY R F SPEECH PROCESSOR



Collins Heath ..... \$139.95  
Drake T4X/T4XB ..... \$154.95  
Drake TR4 ..... \$159.95  
Yaesu FT101 ..... \$139.95  
Kenwood TS99, TS-511. \$139.95  
Add 5% Tax in Washington

- 4 TIMES THE SSB POWER ON ALL BANDS
- ADDED PUNCH FOR PILE-UPS
- EXCELLENT VOICE QUALITY
- SPLATTER FREE, NARROW BAND OUTPUT SIGNAL
- SOLID STATE DESIGN
- PUT YOUR TRANSMITTER TO WORK FOR THE FIRST TIME IN ITS LIFE. POWER UP WITH A MAGNUM SIX FOR MORE ADDED POWER PER \$ THAN ANY OTHER METHOD!

Send for FREE Brochure  
Communication Technology Group  
31218 Pacific Highway South  
Federal Way, Washington 98002



A Division of Elliott Systems Inc.

## CW/RTTY/ REPEATER IDENTIFIER



Uses 256 bit read-only-memory programmed for your call or message. NE555 timers for clock, tone generator and 5 minute timer. Apply 5 volts and COR and it outputs tone and PTT. Board \$8, Kit \$30, Tested \$35

OTHER BOARDS AVAILABLE:  
Two Tone Decoder: \$25 Tested 16 Button Decoder:  
\$95 Phase Locked Loop RTTY Converter: \$30 RY  
Generator: \$17 2 Meter Preamp: \$13 8 Channel  
Scanner: \$25 WRITE FOR FREE FLYER

.....  
.....  
.....  
.....  
**SIGNAL SYSTEMS**  
2650 DURANGO DRIVE  
COLORADO SPRINGS, CO. 80910  
(303) 475-0380

## LOW PRICES ON POPULAR COMPONENTS

### IF FILTERS

- Monolithic crystal filters at 10.7 and 16.9 MHz
- Ceramic filters at 455 kHz

### SEMICONDUCTORS

- VHF power transistors by CTC-Varian
- J and MOS FETS
- Linear ICs — AM/FM IF, Audio PA
- Bipolar — RF and AF popular types

### INDUCTORS

- Molded chokes
- Coil forms — with adjustable cores

### CAPACITORS

- Popular variable types

### QUALITY COMPONENTS

- No seconds or surplus
- Name brands — fully guaranteed
- Spec sheets on request

### GREAT PRICES

- Price breaks at low quantities
- Prices below large mail-order houses

## WRITE FOR CATALOG 173

# AMTECH

P. O. BOX 624, MARION, IOWA 52302  
(319) 377-7927 or (319) 377-2638

K2DEL  
KNIGHT RAIDERS VHF CLUB INC.  
SEVENTH ANNUAL HAMFEST  
PASSAIC-CLIFTON YM-YWHA DAY CAMP  
West Paterson, N. J.

SATURDAY, AUGUST 11, 1973  
10:00 A.M. TIL DUSK

Gigantic Flea Market, Equipment Displays, Contests, Door Prizes, Swimming, Boating and Play Area.

Talk-in station on 50.2, 145.71 and 146.94 FM • Tables and Cooking area • Come early — Stay late!

ADULTS — \$1.00 IN ADVANCE

\$1.50 AT THE DOOR

CHILDREN UNDER 12 — FREE

**NOW**


EXCLUSIVE 66 FOOT

**MDR & AIN**

75 THRU 10 METER DIPOLE

NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS

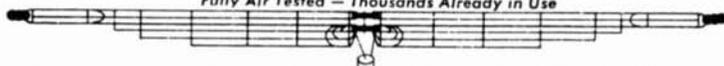Fully Air Tested — Thousands Already in Use



**IS  
BACK**

#16 40% Copper Weld wire annealed so it handles like soft Copper wire—Rated for better than full legal power AM/CW or SSB-Coaxial or Balanced 50 to 75 ohm feed line—VSWR under 1.5 to 1 at most heights—Stainless Steel hardware—Drop Proof Insulators—Terrific Performance—No coils or traps to break down or change under weather conditions—Completely Assembled ready to put up—Guaranteed 1 year—ONE DESIGN DOES IT ALL; 75-10HD—ONLY \$12.00 A BAND!

Model 75-10HD	..... \$60.00	..... 66 Ft. ....	75 Thru 10 Meters	Model 75-40HD	..... \$40.00	..... 66 Ft. ....	75 Thru 40 Meters
Model 75-20HD	..... \$50.00	..... 66 Ft. ....	75 Thru 20 Meters	Model 40-20HD	..... \$33.00	..... 35 Ft. ....	40 Thru 20 Meters
			Model 80-40HD	..... \$42.00	..... 69 Ft. ....	80-40-15 Meter (CW)	

ORDER DIRECT OR WRITE FOR  
FULL INFORMATION

**MDR & AIN**

300H Shawnee  
Leavenworth, Kansas 66048

OR THRU YOUR FAVORITE  
DISTRIBUTOR

CW or RTTY, whichever way you go,  
**HAL HAS TOP QUALITY  
 YOU CAN AFFORD!**



**TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU.** Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).\*

**OTHER HAL PRODUCTS INCLUDE:**

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00\*
- ID-1 (completely assembled in 1½" rack cabinet) . . . \$115.00\*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00\*
- W3FFG SSTV Converter Kit . . . \$ 55.00\*
- Mainline ST-5 TU Kit . . . \$ 50.00\*
- Mainline AK-1 AFSK Kit . . . \$ 27.50\*



**TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER.** Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.\*



**TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.**

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.\*



**NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT.** Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.\*

**TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD.** Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.\*

HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products available.

\*Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

**HAL COMMUNICATIONS CORP.,** Box 365 H, Urbana, Illinois 61801

## ON LINE SWR & POWER METERS



PRICE — \$29.95

FREQUENCY RANGE: 3 - 150 MHz  
 IMPEDANCE: 50 ohms  
 POWER: 0 - 1 Kw



PRICE — \$49.95

FREQUENCY RANGE: 3.5 - 150 MHz  
 IMPEDANCE: 50 or 75 ohms  
 POWER: 0 - 2 Kw

For further information and catalogs write, cable or call:

### CARVILL INTERNATIONAL CORP.

P. O. Box 4039, Foster City, Ca., U.S.A. 94404  
 Cable "CARVILL" • Phone (415) 341-9959 • Telex 349334

## ... SPECIAL SALE ... QVS NI-CAD TESTER



This dual meter unit gives positive proof of Ni-Cad battery quality. Cell meter has expanded scale (1.15-1.33v by .01v) Battery meter is three range — tests up to 20 cells. All units checked — guaranteed satisfaction or money back. w/instructions FOB Monroe —

**\$30**

### — OTHER TEST EQUIPMENT —

Also in stock, wide range of used test equipment, military and commercial. Signal generators, oscilloscopes, voltmeters, frequency standards, counters and more. HP, Tektronix, Fluke, Measurements, Polarad, etc. All equipment shipped same guarantee as QVS Ni-Cad Tester above — money back (less shipping cost) if not satisfied. Send self-addressed, stamped envelope for current list.

### GRAY Electronics

P. O. Box 941, Monroe, MI 48161

Specializing in used test equipment

### KITS



Encoder \$8.95  
 Wired \$13.95

Sub-Audible Tone Decoder \$9.95  
 Wired \$14.95



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass epoxy PCB's & Silicon xstrs throughout
- Any reeds, except special dual coil types may be used: Motorola, G.E., RCA, S.D.L., Bramco, etc.
- All are powered by 12 vdc
- Use on any tone frequency 67 Hz to 250 Hz
- Small size 1.5 x 4 x .75"
- All parts included except reed and reed socket

### COMMUNICATIONS SPECIALISTS

P. O. Box 153, Brea, CA 92621

## F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study — "1973 Tests-Answers" for FCC First and Second class Radio-telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams. — plus "Self-Study Ability Test." \$9.95 Postpaid.



COMMAND PRODUCTIONS P.O. BOX 26348-K  
 RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

## 46 Element Multibeam For 432 MHz Band

The ultimate UHF antenna for long distance communication. #70/MBM 46



Gain: 20 dB over Dipole  
 Length: 104"; Width: 18"  
 Weight: 6 Lbs.  
 Hor. Beamwidth (—3 dB: 24°)

Broadband — works over entire 420-450 MHz. Band.

70/MBM 46 \$52.50 FOB Distributor



## FM Schematic Digest

A COLLECTION OF  
 MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes  
 covering 1947-1960

136 pages 11½" x 17" ppd \$6.50

S. Wolf

P. O. Box 535

Lexington, Massachusetts 02173



## VHF COMMUNICATIONS

EAST  
 915 N. MAIN ST.  
 JAMESTOWN, N. Y. 14701


CENTRAL  
 53 ST. ANDREW  
 RAPID CITY, S. D. 57701

WEST  
 6725 EAST SHERIDAN ST.  
 SCOTTSDALE, AZ. 85257

WESTERN CANADA  
 1170 BASSETT CRES. NW.  
 MEDICINE HAT, ALB., CANADA

# GRAB HOLD OF . . . 22 channels of pure pleasure

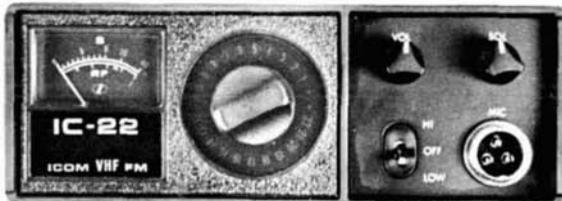**\$289 gets you 22 channels of pure pleasure with . . .**



- TEN crystals . . . (now that *alone* is going to save you about \$40.00) . . . easy to hold noise canceling dynamic mike . . . a quick disconnect mobile mount . . . battery saving HI (10 watts)/Lo (1 watt) power option.
- Your IC-22 will have a receiver that just *won't quit* with a super hot mosfet front end, 5 helical resonators (you can forget about inter-mod), and a large speaker that will punch out plenty of audio for the car.
- You'll also be on frequency with trimmer caps on both trans. and rcv. on all 22 channels. . . with a discriminator output jack in the back to let you get on and stay on freq.
- PLUS the '22' is one good lookin' compact rig that you will be proud to put in your car—(the XYL won't mind it either)—with soft green back lighting on the front panel and a light to silently let you know you are getting out . . . and a second light to let you know there is an incoming signal (even though you may have the volume down).
- There is much, much more to tell you about the IC-22, but suffice it to say, the IC-22, with all of its unique features and performance record at \$289.00, has got to be one of the best all-around values available on two meters today!

SEE THE WHOLE ICOM FAMILY . . . AND GRAB HOLD OF YOUR IC-22 AT ANY OF THE AUTHORIZED ICOM DEALERS LISTED BELOW:

## ALABAMA

Wolfe Electronics  
Box 358  
Foley, Alabama 36535

## ARKANSAS

Gavin Electronics  
516 Ridgeway  
Little Rock, Ark. 72205

## ARIZONA

Eil Dee Enterprises  
1342 AE Indian School Rd.  
Phoenix, Ariz. 85014  
(602) 942-9715

## CALIFORNIA

ICOM FM Sales  
6234 A. Fountain Blvd.  
Hollywood, Calif. 92028  
(213) 462-1502

## Sequoia Stereo

773 - 8th Street  
Arcadia, Calif. 95521

Henry Radio Company  
11240 W. Olympia  
Los Angeles, Calif. 90064  
(213) 477-6701

Sichel Equipment Co.  
245 E. Harris Ave.  
S. San Francisco, Calif. 94080  
(415) 871-7500

## FLORIDA

Goldsteins  
Box 3561  
Pensacola, Fla. 32506

## ILLINOIS

Erickson Communications  
4653 N. Ravenswood  
Chicago, Ill. 60640  
(312) 334-3200

## MARYLAND

COM Electronics  
900 Crain Hwy. S.W.  
Glenn Burnie, Md. 21061  
(301) 761-3666

## NEW MEXICO

Robert Foster  
Box 198 - Escabosa Star Rt.  
Tijeras, N.M. 87059  
(506) 281-3975

## NEW YORK

R. E. Nebel Laboratories  
31 Whitehall Blvd.  
Garden City, N.Y. 11530

Barry Electronics  
512 Broadway  
New York, N.Y. 10012  
(212) 925-7000

## OHIO

H & C Electronics  
6271 Hammell Ave.  
Cincinnati, Ohio 45237

## OKLAHOMA

Blacks Radio Company  
413 N.E. 38th Terrace  
Oklahoma City, Okla. 73106

Roland Radio Company  
5923 E. 31st Street  
Tulsa, Okla 74114  
(918) 836-6833

## OREGON

Portland Radio Supply  
Portland, Oregon

## SOUTH CAROLINA

Electronic Systems Inc.  
1518 Gregg Street  
Columbia, S.C. 29201

## TEXAS

Bellaire Electronic Supply  
5204 Bellaire Blvd.  
Bellaire, Texas 77401  
(713) 667-4294

Electronic Center Inc.  
2929 N. Haskell  
Dallas, Texas 75204  
(214) 526-2023

K. A. Sales, Inc.  
1312 Stocum  
Dallas, Texas 75207  
(214) 747-2662

Trimble Electronics  
2810 Alexandria  
Tyler, Texas 75701

## UTAH

Utah FM Sales  
1365 E. 5360 So.  
Salt Lake City, Utah 84117

## WASHINGTON

ABC Communications  
17541 - 15th N.E.  
Seattle, Wash. 98155  
(206) 364-6410

ABC Communications  
2002 Madison Ave.  
Everett, Wash. 98200  
(206) 353-6616

N.H.E. Communications  
15112 S.E. 44th  
Bellevue, Wash. 98006  
(206) 747-8421

Progress Electronics  
852 Commerce Street  
Longview, Wash. 98632  
(206) 636-5100

Distributed by:



**ICOM**

## ICOM WEST

1251 - 170th St. N.E.  
Bellevue, Wash. 98008  
(206) 641-0554

ADIRONDACK  
RADIO SUPPLY

185 West Main Street  
Amsterdam, N.Y. 12010

## ICOM EAST

Div ACS, Inc.  
Box 331  
Richardson, Tex. 75080  
(214) 235-0479

DEALERS!

GET WITH THE SATISFIERS!  
WRITE TODAY FOR DETAILS!!!

SSB CONVERTER CV-591A: Get upper or lower sidebands from any recvr. OK gald. w/book \$137.50  
 SP-600(\*) RECEIVER 0-54.54 MHz continuous, overhauled, aligned, grtd, w/book \$250.00

### BRAND NEW FREQ-SHIFT TTY MONITOR

NAVY OCT 3: FM Receiver type, freq. range 1 to 26 MHz in 4 bands, cont. tuning. Crystal calib. Reads up to 1500 Hz deviation on built-in VTVM. Cost \$1100.00 each! In original box, with instruct. book & cord. fob Mariposa, Cal. Min. signal needed: 15 mv. Shpg wt 110 lbs. \$49.50

### HIGH-SENSITIVITY WIDE-BAND RECEIVER

COMMUNICATIONS • BUG DETECTION  
 SPECTRUM STUDIES

38-1000 MHz AN/ALR-5; Consists of brand new tuner/converter CV-253/ALR in original factory pack and an exc. used, checked OK & grtd main receiver R-444 modified for 120 v. 50/60 hz. The tuner covers the range in 4 bands; each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.4 MHz, 0.9 at 133 MHz, 5 at 538 MHz, 4½ at 778 MHz, 7 at 1 ghz. The receiver is actually a 30 MHz IF ampl. with all that follows, including a diode meter for relative signal strengths; an atten. calibrated in 6 dB steps to -74 dB, followed by an AVC position; Pan., Video & AF outputs; switch select pass of ±200kHz or ±2 MHz; and SELECT AM or FM! With Handbook & pwr. input plug, all only \$375.00

30 MHz PANADAPTER OK grtd \$137.50

NEMS-Clarke #1670 FM Rcvr 55-260 MHz like new \$275.00

#### Attention!

Buyers, Engineers, advanced Technicians:

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

### R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

## CRYSTAL BARGAINS

Depend on . . .

We supply crystals from 16kHz to 100MHz. Over 6 million crystals in stock.



DIVISION OF BOB WHAN & SON ELECTRONICS, INC.

2400 Crystal Dr.  
 Fort Myers  
 Florida 33901  
 (813) 936-2397

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

### SPECIAL

Crystals for most amateur 2-Meter F.M. Transceivers:

**\$3.75 Each**

Inquire about quantity prices. Order direct. Send check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.

### SPECIALS! CRYSTALS FOR:

Frequency Standards	
100 KHz (HC13/U)	\$4.50
1000 KHz (HC8/U)	4.50
Almost All CB Sets, Trans. or Rec.	2.50
(CB Synthesizer Crystal on request)	
Any Amateur Band in FT-243 (Except 80 meters)	1.50
	4 for 5.00
80 Meter Range in FT-243	2.50
Color TV 3579.545 KHz (wire leads)	1.60
	4 for 5.00

## signal/one CX7A



### Special Purchase Sale \$1895\*

Last chance to buy latest series CX7A.

90 day warranty by dealer.

complete parts inventory available

\*5% discount for no-trade in sale  
 Phone/write Don Payne, K4ID  
 for a King-Size trade on your gear

## PAYNE RADIO

BOX 525

SPRINGFIELD, TENN. 37172

Days  
 (615) 384-5573

Nites  
 (615) 384-5643



## TRI-TEK, INC.

P.O. BOX 14206, DEPT HR  
 PHOENIX, ARIZONA 85063

0 thru 9, plus some letters. Left decimal point. 1/4 X 3/8 character size. 20mA per segment. Common anode format. Similar to MAN-1. Fits in 14 pin DIP socket. Stock # LRO-1090 . . . . . \$3.95



Plus, minus, 1 digit overflow. Same size. Stock # LRO-1001 . . . . . \$3.95

G.E. 2139D miniature 3 volt lamps. 10¢ each, 25/\$2.00

#### DIPPED MICA CAPACITORS

CAPACITY	CASE
43pf	CMO4
68pf	CMO4
110pf	CMO4
180pf	CMO4
2/15¢, 10/50¢, 100/\$4	

2000pf	CMO6
3900pf	CMO6
2/25¢, 10/80¢, 25/\$1.50	

#### TANTALUM CAPACITORS


0.47ufd @ 6V	12/\$1.00
4.7 ufd @ 6V	10/\$1.00
6.8 ufd @ 6V	8/\$1.00
Glass sealed, axial leads	



Coaxial visible red, 3/16 dia.  
 Catalog # LED1316 . . . . .2/\$1  
 Micro-miniature coaxial red.  
 Catalog # LED1218 . . . . .3/\$1



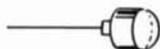5 VOLT COMPUTER  
 GRADE CAPACITOR  
 Just right for IC circuits  
 5400ufd, 5V, 2/\$1.00



NEW AND SURPLUS ELECTRONIC COMPONENTS FOR THE PRO AND SERIOUS AMATEUR. AN ORDER OR 8¢ STAMP PUTS YOU ON OUR MAILING LIST. MINIMUM ORDER \$3.00 U.S., \$15.00 FOREIGN. ALL ORDERS POSTPAID. PLEASE ADD INSURANCE

# FREE:

Apply for your personal SWAN Credit Card simply by completing and mailing this form to **SWAN ELECTRONICS**, 305 Airport Road, Oceanside, CA 92054.



## SWAN REVOLVING CREDIT SERVICE APPLICATION H (PLEASE PRINT)

Name: \_\_\_\_\_  
(First Name) (Middle Name) (Last Name)

Mailing Address: \_\_\_\_\_  
(Street) (City)

How long at this address: \_\_\_\_\_ Phone: \_\_\_\_\_  
(State) (Zip Code) (Area Code) (Number)

Former Address \_\_\_\_\_  
(if less than two years at present address:)

How Long: \_\_\_\_\_

Occupation: \_\_\_\_\_ Birthdate: \_\_\_\_\_

Social Security #: \_\_\_\_\_ Amateur Radio Call: \_\_\_\_\_

Employer: \_\_\_\_\_ How Long: \_\_\_\_\_

Company Address: \_\_\_\_\_  
(Street) (City) (State) (Zip Code)

Former Employer: \_\_\_\_\_ How Long: \_\_\_\_\_

Name of Your Bank: \_\_\_\_\_

Address: \_\_\_\_\_  
(Street) (City & State)

Savings \_\_\_\_\_ Checking \_\_\_\_\_ Loan \_\_\_\_\_ Home Loan Account No.: \_\_\_\_\_

Bank Loans, Finance, etc.:

Current Credit Cards: \_\_\_\_\_  
(Name of Firm) (Address) (City & State) (Account #)

\_\_\_\_\_  
(Name) (Account No.) (Name) (Account No.)

\_\_\_\_\_  
(Name) (Account No.) (Name) (Account No.)

Relative or Personal Reference:

\_\_\_\_\_  
(Name) (Address) (City) (State)

The above information is true and correct. I/We will make no charge purchase until reading the Swan Credit Service Agreement and Disclosure to be provided.

Your Signature: \_\_\_\_\_ Date: \_\_\_\_\_

Signature of Spouse: \_\_\_\_\_ Date: \_\_\_\_\_

# A COMPLETELY PORTABLE FREQUENCY COUNTER WITH . . .

- \* 10 HZ to 65 MHz range
- \* Full six digit readout (L.E.D.)
- \* Sensitive front end (LESS THAN 10 MV.)
- \* Only \$199

## FEATURES

- High capacity rechargeable Ni Cd batteries
- Crystal controlled time base (can be field calibrated)
- Convenient 3-position range select switch allows:
  1. Readout always in MHz.
  2. Eight digit resolution by range selection
  3. Direct reading pre-scaler operation to 999.999 MHz.
- "Battery save" switch for spot checks
- Less than 5 watts power consumption (5 volts @ 0.9 AMPS)
- Dimension 6" x 3.5" x 2.3"
- TTL input for use with pre scaler
- Can be operated on internal or external power, with trickle charge and full charge positions
- Sample control lets operator determine how often the readout is updated. Can "hold" present count without being updated



Mail orders directly to:  
Great American Miniatures,  
Inc.  
P. O. Box 10990  
Midwest City, Okla. 73110

Model C-65 Freq. counter \$199.00  
Battery charger 8.00  
Battery charger & eliminator 18.00

# ENJOY CW! USE A MATRIC KEYSER & PADDLE

- SELF COMPLETING • BATTERY OPERATED
- RELAY OUTPUT



MODEL 10  
CIRCUIT BOARD KIT (LESS CASE) \$12.95  
KIT (LESS BATT).....\$21.90  
WIRED (LESS BATT).....\$26.50  
SIDETONE KIT \$4.95 • WIRED \$6.95

# PADDLE MODEL 11

- ★ ADJUSTABLE TRAVEL
- ★ NON-SKID WEIGHTED BASE
- ★ FULLY ASSEMBLED



ONLY  
\$9.95

SEE YOUR DEALER  
OR ORDER DIRECT. PRICES F.O.B. FRANKLIN, PA.



RD 1, PONE LANE  
BOX 185A  
FRANKLIN, PA. 16323

PHONE: AREA CODE (814) 432-3647

## DIGIPET-60

See Nov. '72 CQ & Apr. '73 QST reviews

Digipet-60  
Frequency  
Counter  
1 KHz-60 MHz  
(130-160 MHz with  
optional converter)  
Reg. \$299



A frequency counter with a range of 1 kHz to 60 MHz (or 130-160 MHz when used with our Digipet-160 converter). With a resolution of 1 kHz or 1 Hz (at 1 ms or 1 s gate times). It can be operated on either ac or dc, with complete overload protection. Plus a stability aging rate of 1 part in 10<sup>6</sup>/week. And the whole unit is a mere 7" deep by 2 1/2" high! Superb precision quality at LESS THAN KIT PRICES. Call or write for literature and trade in or our LOW INTRODUCTORY PRICE, 1 year warranty.

Also MIDA PRECISION AUTORANGING DIGITAL VOLTMETERS (reg. \$319) LESS THAN KIT PRICES. Compare before you buy! 1 YEAR WARRANTY.

NO ONE ANYWHERE BEATS OUR DEAL!



AMATEUR-WHOLESALE ELECTRONICS  
8817 S.W. 129 Terrace • Miami, FL 33156  
Days (305) 233-3631  
Nights-Weekends (305) 666-1347




## Andy Electronics Co., Inc.

Department "B" 6431 Springer Houston, Texas 77017  
All prices FOB Houston, Texas


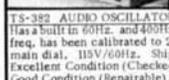
### AN/USM-50-05-02 PRECISION OSCILLOSCOPE

AC scope with a frequency response of 3MHz, 20MHz, and a risetime of .022us. Sensitivity is 24-255mv./inch over the entire frequency range. This unit has a built in 1,000Hz. calibrator and superimposed marker dots at intervals of .2, 1, 5, 20, 100, 500, and 2,000us, for determining frequency. The CRT is 3". Also has a illuminated scale, 115V/60Hz, 50p. Wt. 14.65 lbs. Excellent Condition (Checked).....\$79.95  
Good Condition (Reparable).....\$65.95



TS-392 AUDIO OSCILLATOR. Tunes from 20KHz. - 20KHz. Has a built in 60Hz. and 400Hz. calibrator meter. The output freq. has been calibrated to 2% of the freq. indicated on the main dial. 115V/60Hz. Ship Wt. 85 lbs. Excellent Condition (Checked).....\$79.95  
Good Condition (Reparable).....\$65.95



### AN/URM-79 FR-4 PRECISION FREQUENCY METER

Covers the frequency range of 100KHz. - 25MHz. In seven bands. Accuracy is .001% over the entire range. Frequency measurements and calibration checking are made by means of a blinker light and earphones. This Frequency meter has a 3" CRT for visual interpolation of the frequency being measured. Units are complete with interpolation book and operation manual, 115V/60Hz. Ship Wt. 120 lbs. Excellent Condition (Checked).....\$79.95

# NES

NURMI ELECTRONIC SUPPLY

1727 Donna Road · West Palm Beach, Florida 33401 · Phone — (305) 686-8553

## DELUXE Equipment Enclosure

Great for Linears, SSTV Monitors, Station Controls, etc.

AIR INTAKE

EXHAUST  
Rotron Whisper  
Fan & Grill on  
Back Panel.

### FEATURES:

- Rubber Feet
- Cream/Lt. Green Textured Finish
- Heavy Steel Construction
- ½" Felt Lining for Quiet
- Holds Over 80 Lbs. of Equipment
- Heavy Duty Piano Hinges
- Cabinet & Base Bolt to Pedestal
- Cabinet Can Be Used Alone
- All Wires Including Line Cord Can Be Routed thru Pedestal & Out Grommeted Hole in Base.
- Front Panel 9"x19"

### FEATURES:

- Rocker ON/OFF Switch
- Internal Power Outlet
- Rotron Whisper Exhaust Fan
- Hinged Top Cover
- Hinged Front Panel
- Belden Line Cord Installed
- Welded Construction
- ¼ Turn Knobs on Front Panel

GROMMET HOLE  
in Rear of Base

### LIMITED SUPPLY

THIS OFFER CANNOT BE  
REPEATED — LESS THAN  
100 LEFT!!!!

ALL THIS  
ONLY

# \$39<sup>00</sup>

*A Real Beauty!*

**DIMENSIONS:** CABINET: 21"W x 16"D x 11"H  
BASE: 18"W x 14"D x 2"H  
PEDESTAL: 6"W x 6"D x 36"  
OVERALL HEIGHT: 49"


**SHIPMENT:** Shipped in Two Heavy Triwall Cardboard Cartons.  
Shipped VIA Motor Freight. Freight Charges will be Collected upon  
Delivery. Florida Residents, Please Enclose 4% State Sales Tax.

# NEW RX-144C RECEIVER KIT

*For Repeaters or Those  
Who Need The Best*

**\$69.95**

WITH 10.7 CRYSTAL FILTER

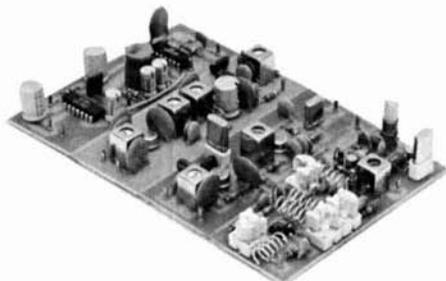

- Low cross modulation front end
- 10.7 MHz crystal filter
- Sensitive noise squelch
- COR output for control
- 2 watts audio output
- Less than .2  $\mu$ V sensitivity
- Measures 4 x 6 x 1 inches

## ALSO AVAILABLE

TX-144 Transmitter Kit \$29.95 — RX-144 Receiver Kit \$59.95 — PA-144 Amplifier Kit \$29.95

Add \$1.00 shipping per kit ordered. New York Residents add sales tax.

We are now in our new location, please note the new address.



# VHF ENGINEERING

— DIV. OF BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, N.Y. 13902 607-723-9574



## MODEL "A" Frequency Counter

10 Hz to 80 MHz ( $\pm 1$  Hz) Direct Count  
Guaranteed (1 Hz to over 100 MHz typical)

Read Out: 5 digit LED + Over Range

Sensitivity: 100 millivolts

Either 120 VAC or 12 VDC power required

Small Size: 2.34" x 5.68" x 8.18"

Price: \$250.00 FOB Vista, Ca.

## MODEL "AS" Frequency Counter

EXACTLY AS ABOVE PLUS AN INTERNAL  
SCALER ( $\pm 10$  Hz) 70 MHz to over 250 MHz  
DIRECT COUNT

ONE BNC CONNECTOR FOR BOTH RANGES

INTRODUCTORY PRICE UNTIL 1 SEPT. 1973:

\$325.00 FOB Vista, Ca.

(CA residents add sales tax)



**ELECTRONICS**

P.O. BOX 1672  
VISTA, CA. 92083  
714-726-1313

## TECO ELECTRONICS

ALL ITEMS CHECKED AND OPERATING, SHIPPED FOB  
GARLAND, TEXAS. 10 DAY MONEY BACK GUARANTEE  
IF NOT SATISFIED (RETURNED PRE-PAID)

MIDA 60 COUNTER AS IN CQ AND QST MAG. 60 MHz SOLID STATE 50 MV SENSITIVITY .....	\$299.00
URM-25D SIGNAL GENERATOR, 10 kHz-52MHz WITH CALIBRATED OUTPUT, BUILT-IN XTAL CALIBRATOR, AM MOD. SMALL SIZE .....	\$125.00
PRM-10 GRID DIP METER 2 MHz-400 MHz .....	\$60.00
HP-524B COUNTER DC-10MHz NEON READOUT .....	\$95.00
HP-524C COUNTER DC-10MHz NIXIE READOUT .....	\$275.00
HP-524D COUNTER DC-10MHz NEON READOUT .....	\$195.00
HP-525A OR B PLUG-IN 10MHz TO 220 MHz .....	\$50.00
HP-540A TRANSFER OSCILLATOR FOR 525 COUNTERS EXTENDS RANGE 10MHz TO 5GHz .....	\$50.00
HP-540B SAME AS ABOVE BUT TO 12.4 GHz .....	\$125.00
HP-233A AUDIO GENERATOR 50Hz-500kHz .....	\$65.00
HP-400HR AC VTVM TO 4 MHz 1MV-300V .....	\$65.00
HP-430C/477B POWER METER AND MOUNT .....	\$85.00
CMC 707D XSISTOR 7 DIGIT 50 MHz COUNTER .....	\$395.00
LAMBDA 12V/11A PS 0.02% REG. NEW UNITS .....	\$65.00
TEK 535 SCOPE DC-11 DELAYED SWEEP .....	\$295.00
FLUKE 801 DC DVM TO 500 VOLTS 0.05% ACC .....	\$45.00
FLUKE 803 SAME AS ABOVE BUT AC-DC .....	\$85.00
GERTSCH FM-7 & DM-3 FREQUENCY METER .....	\$795.00
POLARAD TSA/STU-1 SPECT. ANAL. 10MHz-1GHz .....	\$225.00
SORENSEN 500BB PS 0-500V/300MA 0.5% REG .....	\$45.00
L&N K3 UNIVERSAL POT. NEW CONDITION .....	\$275.00
TELETYPE CORP LS200 DISTORTION TEST SET .....	\$50.00
ELECTRONICS TUBE CORP DUAL BEAM SCOPE .....	\$175.00
HP-650AR AUDIO GENERATOR 10Hz-10MHz .....	\$75.00
HP-330BR DISTORTION ANALYZER .....	\$225.00


OVER 15,000 ITEMS IN STOCK, PRICED TO SELL  
WRITE TODAY WITH YOUR REQUIREMENTS OR CALL

## TECO ELECTRONICS

P.O. BOX 1050-B, GARLAND, TEXAS 75040, 214-276-4931  
STORE HOURS 11 AM TO 7 PM CLOSED SUN. & MON.

The most popular three  
band beam in the world!

# ### *hy-gain* TH3Mk3

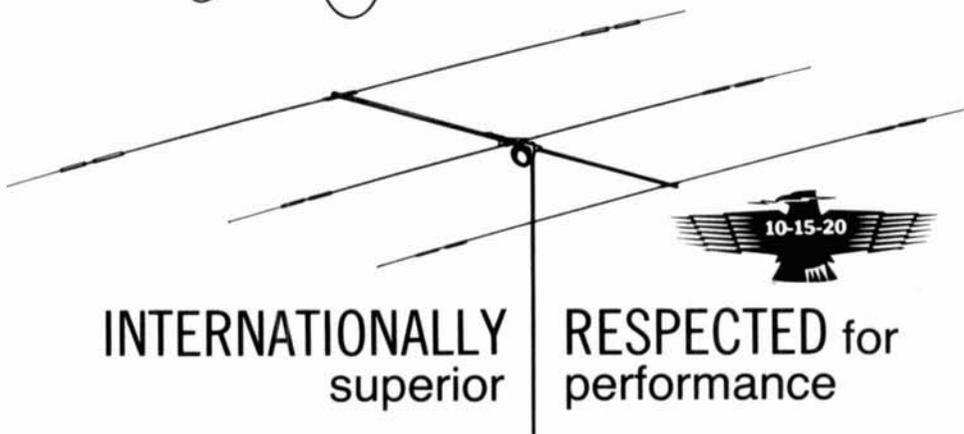

INTERNATIONALLY  
superior

RESPECTED for  
performance



Superior construction and performance make the difference in Hy-Gain's popular 3-element Thunderbird.

- Thunderbird's "Hy-Q" traps provide separate traps for each band. "Hy-Q" traps are electronically tuned at the factory to perform better at any frequency in the band—either phone or CW. And you can tune the antenna, using charts supplied in the manual, to substantially outperform any other antennas made.
- Thunderbird's superior construction includes a new, cast aluminum, tilt-head universal boom-to-mast bracket that accommodates masts from 1¼" to 2½". Allows easy tilting for installation, maintenance and tuning and provides mast feed-thru for beam stacking.  
Taper swaged, slotted tubing on all elements allows easy adjustment and re-adjustment. Taper swaged to permit larger diameter tubing where it counts! And less wind loading. Full circumference compression clamps are mechanically and electrically superior to self-tapping metal screws.
- Thunderbird's exclusive Beta Match achieves balanced input, optimum matching on all 3 bands and provides DC ground to eliminate precipitation static.
- Up to 8 db gain
- 25 db front to back ratio
- Power capability 1Kw AM, 2Kw PEP
- SWR less than 2:1
- Extra heavy gauge, machine formed, element to boom brackets with plastic sleeves used only for insulation. Bracket design allows full mechanical support.

**Model 388 \$144.95**

**Other tri-band beams to choose from:**

- 6-element Super Thunderbird TH6DXX
- 3-element Thunderbird Jr. TH3JR
- 2-element Thunderbird TH2Mk3

**Model 389 \$179.95**

**Model 221 \$ 99.95**

**Model 390 \$ 99.95**

AVAILABLE FROM AMATEUR DEALERS THROUGHOUT THE WORLD

## HY-GAIN ELECTRONICS CORPORATION

8601 Northeast Highway 6 Dept. WG Lincoln, Nebraska 68507  
402/434-9151 Telex 48-6424

## URC-11 WALKY TALKY

243 MC 2 way radio, hand held, measures 3 x 4 inches. Used for survival in downed aircraft. May be converted for other frequencies.

URC-11 \$15 each or 3 for \$40.00



## 7 SEGMENT LED



Hobby craft due to being factory rejects. Most have a segment or decimal inoperative. Still a great "buy" for the experimenter. What an unusual tie clip you can make with pocket battery . . . demo displays, etc. In many applications you don't need full 7 segments. \$1.00 each or \$10 the dozen. 0.333 inches high character.

As above only this one is the giant display 13/16 inches hgt. of character. First time offered and as far as we know, offered no where else. This one is quite an attention getter. Also available in this giant display numeral "one" with "plus" and "minus" sign. Again, these are rejects. Giant display \$1.50 each 12 for \$15.00

## GIANT 7 SEGMENT

As above only this one is the giant display 13/16 inches hgt. of character. First time offered and as far as we know, offered no where else. This one is quite an attention getter. Also available in this giant display numeral "one" with "plus" and "minus" sign. Again, these are rejects. Giant display \$1.50 each 12 for \$15.00

JOHN MESHNA JR. ELECTRONICS

## GIANT LED 83¢

Price break at last on these giant LED with 1,000,000 hours of life. Measure full 1/4 by 1/4 inch. First time offered.

RED \$1.00  
GREEN \$1.25

SUPER BRIGHT collimated RED with parabolic reflector, measures 3/16 diameter. A real hi-intensity red visible over 100 ft.


SUPER RED \$1.25

All above LED's 12 for the price of 10



## CORE STACK

Late model memory stacks, unused

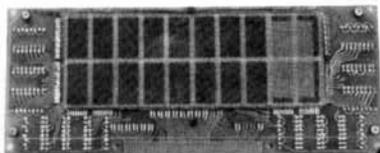

1Kx9 .....	\$ 35.00
2Kx9 .....	\$ 50.00
8K 4 bit Y-plane .....	\$ 40.00
16K 4 bit Y-plane .....	\$ 60.00
147K stack .....	\$100.00

Postage Extra on all Items

P. O. Box 62 E. Lynn, Mass. 01904

## "INTRODUCTORY PRICES"

ST-5 BOARDS ONLY .....	\$ 5.25
ST-5 KIT OF ELECTRONIC PARTS .....	\$ 47.50
ST-5A BOARDS ONLY .....	\$ 5.25
ST-5A KIT OF ELECTRONIC PARTS .....	\$ 54.00
ST-6 BOARDS ONLY (These are the 8 original with W6FFC) .....	\$ 18.00
ST-6 KIT OF ELECTRONIC PARTS .....	\$128.50
MOD. KIT FOR UPDATING THE ST-5 TO THE ST5A .....	\$ 9.00
PEMCO MODEL 50A FREQUENCY COUNTER SEMI-KIT .....	\$125.00

This is a fully assembled and tested board, you add only your own power supply and cabinet, etc. Write for details.

You must supply the cabinet, A.C. cord, meter, switches, etc. on all kits except where noted otherwise. (All prices are postage paid (we pay shipping)).

We will do most any printed circuit board for individuals or prototypes. If required we will also do the layout of the boards. All our boards are G-10 glass-epoxy solder plated and come drilled only. At present time we can do only single sided. All component parts used in our kits are new manufacturers stock. We Do Not Use Any Used or Surplus Parts. All inquiries are answered promptly.

**PEMCO** ELECTRONICS  
MANUFACTURING  
422 18th St., N.E., Salem, Ore. 97301, (503) 585-1641

## WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

**SPACE ELECTRONICS** division of  
**MILITARY ELECTRONICS CORP.**

76 Brookside Drive, Upper Saddle River  
New Jersey 07458 • (201) 327-7640

## ACTIVE AUDIO FILTERS

IC's FOR SUPER  
HIGH PERFORMANCE

### CW FILTER (CWF-2)

Get razor sharp selectivity; No impedance matching! BW (selectable) 80 Hz, 110 Hz, 180 Hz; Center frequency F=750 Hz; Skirts 60 dB down at 1/2 F and 2F; 4 op amps; 2" x 3" PC board; \$14.95 wired, tested, guaranteed; \$12.95 kit.



CWF-2: \$12.95 KIT

### CW MINI FILTER (CWF-3)

1 1/2" x 2" PC board; Center frequency F=750 Hz; 30 dB down at 1/2 F and 2F; BW 110 Hz, 180 Hz; 2 op amps; \$8.95 wired, tested, guaranteed; \$7.95 kit.

### LOW PASS FILTER (LPF-1)

Resistors set cutoff 500 Hz to 20 kHz; Factory set to 2.5 kHz; Roll-off 48 dB per octave; Input imp 1 M; Gain=1; 5 op amps; 2" x 3" PC board; \$16.95 wired, tested, guar.; \$14.95 kit. Please include 55¢ postage on all orders.

**MFJ ENTERPRISES** Send for FREE Spec Sheet  
PO 494-A, Miss. State, MS 39762

# SAROC SAROC SAROC SAROC

9th annual fun convention

Best of Las Vegas — Best of Amateur Radio

January 3-6, 1974

SAROC Box 73 Boulder City, Nev. 89005

# LIKE FM OR CW ?



*Then you'll love  
Data Engineering's  
new catalog*

**Write for your free copy today!**

## TOUCH TONE PADS

More features than any other pad including built-in monitor speaker and latest Phase-Lock loop circuitry.

TTP-1 Standard pad for portable transceiver mounting.

TTP-2 Standard pad in attractive case for home or mobile use.

TTP-3 Mini-pad in attractive case for home or mobile use.

TTP-4 Mini-pad for portable transceiver mounting.

TTP-1, 2, 3 & 4, Sh. wt. 1 lb. .... \$44.50

TTP-1K, 2K, 3K & 4K, Sh. wt. 1 lb. .... \$34.50

## AUTO-PATCH CONSOLE

This mobile or home console includes all the features you need for complete auto-patch operation. A Touch-Tone Pad; an automatic dialer for sending one access code plus five Touch-Tone phone numbers; a single/dual tone burst encoder adjusted to your choice of frequency above 500 Hz, a continuous sub-audible tone encoder, and a built-in monitor. Complete PTT operation with one second transmitter hold. Sh. wt. 2 lbs.

APC-4K Comp. Kit \$84.50 APC-4 Assembled \$98.50

## 2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain at 2.5 N.F. to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit  
\$12.50 wired

Please include sufficient postage for shipping.



# DATA ENGINEERING INC.



Ravenswood Industrial Park, Springfield, Va. 22151

5554 Port Royal Road • 703-321-7171



<b>NATIONAL MOS</b> DYNAMIC shift registers MM502 dual 50 bit 1.25 MM506 dual 100 bit 1.50 MM506 dual 100 bit 1.50 MM513 1024 bit 2.00 MM5017 dual 512 DIP 2.00 MM5016 512 bit 1.50 STATIC shift registers MM504 dual 16 bit 1.50 MM505 dual 32 bit 1.75 MM550 dual differential analog switch 2.50		<b>CT5005</b> CALCULATOR ON A CHIP This chip has a full four function memory. Memory is controlled by four keys, W (adds entry to memory), M (subtract entry from memory), CM (clear memory—without clearing rest of registers), BK (read memory or use as entry).  -12 DIGIT DISPLAY AND CALC. -FIXED DECIMAL AT 0,1,2,3, 4, OR 5 -LEADING ZERO SUPPRESSION -SEVEN SEGMENT MULTIPLEXED OUTPUT -TRUE CREDIT SIGN DISPLAY -SINGLE 28 PIN CHIP Chip and data—\$14.95 Data only—1.00 (refundable)		<b>7400 TTL</b> DIP 7400-----\$ .35 7401----- .35 7402----- .35 7403----- .35 7404----- .35 7405----- .35 7408----- .40 7410----- .35 7411----- .35 7420----- .35 7430----- .35 7440----- .35 7441----- 1.30 7442----- 1.00 7446----- 1.50 7448----- 1.25 7450----- .35 7451----- .35 7453----- .35 7454----- .35 7460----- .35 7472----- .40 7473----- .55 7474----- .40 7476----- .55 7480----- 3.50 7483----- 1.15 7486----- .65 7489----- 3.00 7492----- .90 7493----- .90 7495----- 1.15 74107----- .55 74154----- 2.50 74181----- 3.50 74193----- 2.00 74195----- 1.00	
<b>3 CHIP</b> CALCULATOR SET This calculator set has eight digit floating point with left hand entry. It will add, subtract, multiply, and divide. Overflow and negative signals are provided. - Chips and data—\$6.95 - Data only—1.00 (refundable)		MC1013 ECL 85mc ff 1.00 MC1023 ECL driver 2.00 MC1039 ECL-TTL interface 2.00 8850,9601—one shot multivibrator 1.00 B269 Sigmatic is same as 8200 National 4 bit comparator 1.60 MC853 dual JK DTL .30 LU321 dual JK "utlogic".60 SP629 RS/T Sigmatic .40 SP659 dual 4 input buf. .25		<b>LINEARS</b> LM100-----\$ .80 LM309H----- 1.00 LM309C----- 2.50 NE555E----- .75 741(MEM) DIP----- 1.50 747(MINI)----- 4.45 709----- .30 710----- .40 711----- .40 723----- 1.00	
<b>MV-50</b> red emitting IG-40ma @ 2V .39 <b>MV5020</b> red LED .45 <b>MV-108</b> Visible red 5-70ma @ 2V .45		<b>SCHOTTKY</b> TTL \$3.00 EACH B2530 8 input multiplexer B2533 2 input 4 bit multiplexer B2541 quad EX/OR element B2542 4 bit comparator B2562 9 bit parity gen./checker B2567 2 input 4 bit multiplexer DM8880 (Sperry 0D700 202) 7 segment high voltage nixie driver—\$1.75		<b>LED FL 100</b> special !!!! .39 each 3.50 for ten 29.95 for 100	
<b>MANSA</b> Each \$3.00 ten or more—2.50		<b>CMOS</b> CD4001-----\$ .75 CD4002----- .75 CD4011----- .75 CD4012----- .75 CD4023----- .75		<b>MANSA</b> P.O. Box 3 California 95608 (916) 966-2111	

## HAM RADIO CENTER

### Announces!






**NOW:** Call your order in, and we'll pick up the tab for the phone call. (Minimum order \$25.00)

**HOW:** Place station to station call. When phone bill is received, forward copy along with our invoice covering order phoned in, we'll send refund check. **DO NOT CALL COLLECT.**

**COMPLETE STOCKS ALL NATIONAL BRANDS**  
**WE BUY-SELL-TRADE USED EQUIPMENT**

*Write to Bill Du Bord, W4KF*  
*for Trade-in Quote & Used List*

**HAM RADIO CENTER, INC.**  
 8342 Olive Bl., Dept. H., St. Louis, Mo. 63132  
 Phone (314) 993-6060

**NEW MINIATURE CRYSTAL FILTERS — Made U.S.A.**

Write us about your crystal filter needs  
 Model WF-4 Model WF-8

No. Crystals	4	8
Center Freq.	9.0 MHz	9.0 MHz
Band Width at 6db	2.5kHz	2.5 kHz
60db/6db Shape	2.0 (45/6)	1.8 max.
Ultimate Rejection	45 db	100 db min.
In/Out Termination	120 Ω	140 Ω
PRICE	\$18.95	\$26.95

Matching Crystals USB (8998.5 kHz) or LSB (9001.5 kHz) \$2.75 each  
 Include .75 for postage and handling.

Portable Radio Phone Model FLP-2/CBFL, 31.5 MHz, AM. Made by Morrow Radio. Easy to convert. Approx. 1w input pwr/squelch. Mic. included. A1 CONDITION \$14.95  
 Headset-Microphone H-63/U 600Ω earphones 100 ohm mike suspended on headband. NEW \$4.95  
 Chest Set AN/GSA6 adapts above to GRC-VRC equipment NEW \$2.95  
 Potter & Brumfield industrial control relay New KU-4129-2 SPDT, SPST 115 VAC 60 cps 50¢  
 Teletype Ribbons — 35¢ ea., 12 for \$3.50  
 Sales Sheet now available. Send SASE for copy.  
**FRANK ELECTRONICS, 407 Ritter Rd., Harrisburg, PA 17109**

## FREE Catalog

OF THE WORLD'S FINEST  
 GOVERNMENT SURPLUS  
 ELECTRONIC EQUIPMENT  
**And BETTER Than Ever!**

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**Mail Coupon for Your FREE Copy, Dept. HR**

**FAIR RADIO SALES**  
 1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outstanding QSL Bureau) for \$12.95 a year.



Greenville, New Hampshire 03048



Your assurance of Performance and Quality

YAESU

# FTdx401

Transceiver



## More For Your Money

### FTdx401

Built-in AC Power Supply  
 Built-in WWV 10 MHz Band  
 Built-in Noise Blanker  
 25 and 100 KHz Calibrators  
 VOX  
 Clarifier  
 Break-in CW with Sidetone  
 600Hz CW Filter  
 1 KHz Readout  
 Selectable SSB  
 6 Month Warranty by Dealer  
 Cooling Fan

### \$599.00

No charge  
 No charge

**Total only \$599.00**

Amateur Price Net  
Price Subject To Change

**Tomorrow's Transceiver Today:** 20 tubes plus 50 silicon semiconductors, passive crystal filter (6 pole), velvet smooth tuning, superb noise blanker, standard electrical parts. This is truly the best buy in the amateur field today. See your local dealer for brochure & demonstration.

Factory Service is available even after your warranty has expired for the cost of labor and parts.

### YAESU DEALERS:

HENRY RADIO STORES / 213-477-6701  
 Los Angeles, Anaheim, Ca., Butler, Mo.  
 HAM RADIO OUTLET / 213-272-0861  
 Burlingame, Ca.  
 RACOM ELECTRONICS / 206-255-6656  
 Renton, Wash.  
 WILSON ELECTRONICS / 702-457-3596  
 Pittman, Nev.

ED JUGE ELECTRONICS / 817-926-5221  
 Fort Worth, Tex.  
 AMATEUR ELECTRONICS SUPPLY / 414-442-4200  
 Milwaukee, Wis., Cleveland, Ohio, Orlando, Fla.  
 FRECK RADIO & SUPPLY / 704-254-9551  
 Asheville, N. Carolina  
 HARRISON RADIO / 516-293-7990  
 Farmingdale, L. I., Valley Stream, L. I., New York City, N. Y.



### YAESU MUSEN USA INC.

7625 E. Rosecrans Avenue, Unit #29  
 Paramount, California 90723

Phone 213-633-4007

# BARRY HAS ANTENNAS

Cush-Craft Trick Stick, universal dipole, 10-2 meters. 1.5 dB gain at 146 MHz ..... \$ 8.95  
 English deluxe balun, low power ..... \$ 9.95  
 W2AU 10/15/20 Quad, bamboo ..... \$ 49.00  
 Joy Stick (English) with original tuner \$ 29.00  
 RINGO AR-2 3.75 dB gain ..... \$ 12.50  
 BBLT-144 Trunk Lip, 3.75 dB gain ..... \$ 34.95  
 Newtronics CGT-144 mobile 5.2 dB gain \$ 37.75  
 Quick Disconnect by Newtronics for CGT, etc. \$ 9.95  
 CG-1 Gutter Clip by Newtronics ..... \$ 1.25  
 2M MAGNETIC MOUNT w/RG58 & PL259 with 10 ft. RG 58 ready to go ..... \$ 9.95  
 14AVQ/WB VERTICAL ..... \$ 47.95  
 18AVT/WB VERTICAL ..... \$ 69.95  
 HY GAIN 2 METER, 15 element beam \$ 35.00

NEW ULTRA BALUN 1:1 ..... \$ 9.95  
 C.D. HAM "M" ROTATORS, new, complete \$99.95  
 HAM "M" CABLE ..... @ 13¢/ft.  
 C.D. TR-44 ROTATORS, new, complete \$63.95  
 CABLE FOR TR-44 ..... 6¢/ft.  
 RG-8A/U 100 ft. rolls. VHF connector PL-259 one end Type "N" (UG-21E/U) other end \$ 12.50  
 RG8A/U — 65 feet with PL-259 connectors on each end ..... \$9.50  
 B & W Vacationer apartment house antenna, 2, 6, 10, 15 & 20 meters. Hang out your window. Take along on your vacation ..... \$ 24.95  
 Authorized factory dealers for Antenna Specialists, CushCraft, Gam, Heights Towers, Hy Gain, Mor-Gain Antenna, Mosley, Newtronics, Tri-Ex, Rohn, E-Z Way, Times Wire

**TOWER PROBLEMS?** Let Barry get factory engineering answers from TRI-EX on your new installation.

**NEW! VENUS SSTV MONITOR.** Advanced features. Late Summer availability.

## BIRD

4350 80-10M 2KW Ham Mate ..... \$ 79.00  
 43 Wattmeter ..... \$100.00  
 BIRD 43 SLUGS, spec. freq./power, HF VHF, \$35.00 ea. VHF, \$32.00 ea.

## SWR BRIDGE COUPLER, DC-800 MHz

(no indicator) full amateur power  
 \$90.00 Value  
**\$10.95**

## MISC.

Gonset 900A 2 meter Sidewinder with 901A AC power supply. 144-148 MHz SSB, AM & CW. 20w. PEP. 6w. AM ..... mint, \$250.00  
 Gonset 903A 2 meter amplifier, 5 watts in, 500 watts out all modes ..... \$375.00  
 HQ-180 with clock. Mint condition, professionally calibrated. Needs new RF gain control \$275.00  
 Milen magnetic shields for 3" C.R. scope tubes with brackets. .... Brand new \$ 6.95  
 TP-9 Similar to EE-8 field telephone with built-in amplifier. Up to 50 mi. Less easily obtained batteries ..... Brand New \$ 75.00  
 Power Supply for BC-221, slips into battery compartment ..... \$29.50  
**ALUMINUM DIE CAST BOXES** in many different sizes. Dossy boxes. Details in New Green Sheet No. 23.  
 2 METER VHF DUMMY LOAD/WATTMETER Good up to 15 watts — w/SO-239 CONNECTOR ..... \$19.95



Jackson G80 brass 50:1 anti-backlash dial drive 1/4" to 1/4". \$12.00 value ..... \$5.50

## INVERTER/CONVERTER:

MODEL 612 provides 12 VDC neg. ground power in automobiles with either 6 v. neg. ground or 12 v. pos. ground. 10 amp surge, 3 amp continuous ..... new, \$22.95  
 INVERTER, 12 volt DC input, 115 volt AC out, Model 12-115 solid state power supply, 200 watts continuous ..... new, \$ 59.95

## BARKER & WILLIAMSON

Dummy Load - Wattmeters - 52Ω  
 333 DC - 300 MHz, 1000 watts int. .... \$139.95  
 334A DC - 230 MHz, 1500 watt ..... \$169.95  
 374 DC - 300 MHz, 250 watt int. .... \$ 79.95  
 850A, 852 Inductors ..... \$ 59.95  
 851 Inductor ..... \$ 29.95  
 425 Low Pass Filter, 10-80 meters ..... \$ 24.95  
 210 Audio Osc., ideal for lab & broadcast ..... \$329.95  
 410 Distortion Meter, ideal for lab & broadcast ..... \$369.95  
 AM-141 Amplifier, 2000 watts RF output, continuous 2-18 MHz, complete with coils and 833-A's. Built-in 115 VAC Supply, unused ..... \$950.00

## E. F. JOHNSON

Matchbox complete with directional coupler and indicator, 10-80 meters.  
 2KW PEP, 1 KW AM — new, \$154.50  
 275 watts — new, \$ 94.95  
 151-1-4 Variable Capacitor, 250 pF, medium Xmitting type ..... \$2.95 ea.

Tube Headquarters. Diversified Stock.  
 Heavy inventory of Eimac tubes, chimneys, sockets, etc.

**572B** ..... \$ 17.50  
 Barry Now Stocks Bogen, Electrovoice & University. Call or Write.

Separate export department to expedite overseas orders.

**CASH PAID . . . FAST!** For your unused TUBES, Semiconductors, RECEIVERS, VAC, VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LN1. We Buy!

We ship all over the World.

Send for Green Sheet Supplement 23.

Send 10¢ plus 40¢ postage & handling (refund 1st order).



**GE INDUSTRIAL SILICON RECTIFIER**  
 1400 PIV

250 amp., GE #41A281049-11. Quantities in stock. \$90.00 value, brand new ..... \$22.50

**BARRY** 512 Broadway NY, NY 10012  
 DEPT. H-7  
**212-WA-5-7000** **ELECTRONICS**

See Page 112 for more from Barry

# for the EXPERIMENTER!

**INTERNATIONAL EX CRYSTAL & EX KITS**  
 OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER




## 1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....**\$3.50**


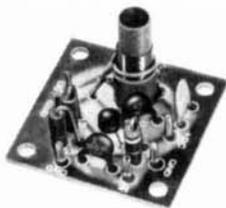
## 2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....**\$3.50**



## 3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....**\$3.75**




## 4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL. Experimenter or Amateur .....**\$3.75**


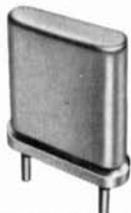
## 5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....**\$2.95**



## 6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is  $\pm .02\%$  when operated in International OX circuit or its equivalent. (Specify frequency) .....**\$3.95**

# for the COMMERCIAL user...

**INTERNATIONAL  
PRECISION RADIO CRYSTALS**

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

**CRYSTAL TYPES:** (GP) for "General Purpose" applications  
 (CS) for "Commercial Standard"  
 (HA) for "High Accuracy" close temperature tolerance requirements.



**write for  
CATALOG**



**CRYSTAL MFG. CO., INC.**  
 10 NO. LEE • OKLA. CITY, OKLA. 73102

CUSH-CRAFT 2M ANTENNAS!

IN STOCK... SHIPPING PREPARED

1R-2 - FM RINGO - 3.75 DB Gain! 135-175 MHz - 100W Omnidirectional	\$12.50
1FV-10 - 4 POLE - Up to 9 DB Gain! All Hardware 360° 6 DB, 180° 9 DB	\$12.50
1M-17 - FM MOBILE - 3 DB Gain! Fiberglass - Roof or Trunk	\$26.95
1V17-11 - 11 ELEMENT YAGIS - 13.2 DB Gain! Can be Vertically Polarized	\$17.95
1V17-22 - POWER PACKS - 16 DB Gain! Two A147-11's and Complete Stacking Kit	\$19.50
A147-4 - 4 ELEMENT YAGIS - 9 DB Gain! 1KW Mast or Tower Side Mount	\$ 9.95
DL-120 - 20 ELEMENT DX-ARRAYS - 14.2 DB Gain! Combine the Best Yagi and Colinear Features. Can be Stacked Up To 80 Elements - Dynamite for DX-ing and Moonbounce	\$29.50

ASK FOR COMPLETE CUSH-CRAFT CATALOG... AMATEUR, COMMERCIAL, CB

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7400	.34	.32	.30	.28
7401	.34	.32	.30	.28
7402	.34	.32	.30	.28
7403	.34	.32	.30	.28
7404	.36	.34	.32	.30
7405	.36	.34	.32	.30
7406	.56	.53	.50	.47
7407	.56	.53	.50	.47
7408	.38	.36	.34	.32
7409	.38	.36	.34	.32

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7410	.34	.32	.30	.28
7411	.34	.32	.30	.28
7412	.60	.57	.54	.51
7416	.54	.51	.48	.45
7417	.54	.51	.48	.45
7418	.38	.36	.34	.32
7420	.34	.32	.30	.28
7421	.34	.32	.30	.28
7423	.84	.80	.76	.72
7425	.54	.51	.48	.45

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7426	.40	.37	.34	.31
7430	.34	.32	.30	.28
7432	.56	.53	.50	.47
7438	.56	.53	.50	.47
7440	.34	.32	.30	.28
7444	1.73	1.64	1.55	1.46
7442	1.34	1.27	1.20	1.13
7443	1.34	1.27	1.20	1.13
7444	1.34	1.27	1.20	1.13
7445	1.71	1.62	1.53	1.44

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7415	2.00	1.90	1.80	1.70
74180	1.30	1.23	1.16	1.09
74181	5.20	4.90	4.60	4.30
74182	1.26	1.19	1.12	1.05
74192	2.10	2.00	1.90	1.80
74193	2.10	2.00	1.90	1.80
74198	3.10	2.95	2.80	2.65
74199	3.10	2.95	2.80	2.65

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7416	1.34	1.27	1.20	1.13
7417	1.34	1.27	1.20	1.13
7418	1.40	1.37	1.29	1.22
7419	1.34	1.27	1.20	1.13
7451	.34	.32	.30	.28
7453	.34	.32	.30	.28
7454	.34	.32	.30	.28
7455	.34	.32	.30	.28
7460	.34	.32	.30	.28
7470	.16	.13	.10	.07

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
74820	.88	.84	.79	.75
74821	.88	.84	.79	.75
74822	.88	.84	.79	.75
74823	.88	.84	.79	.75
74824	.88	.84	.79	.75
74851	.88	.84	.79	.75
74860	.88	.84	.79	.75
74861	.88	.84	.79	.75
74862	.88	.84	.79	.75
74863	.88	.84	.79	.75
74873	1.82	1.73	1.63	1.54
74874	1.82	1.73	1.63	1.54

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
7490	.85	.80	.75	.70
7491	1.48	1.41	1.34	1.27
7492	.85	.80	.75	.70
7493	.85	.80	.75	.70
7494	1.32	1.26	1.20	1.14
7495	1.32	1.26	1.20	1.14
7496	1.32	1.26	1.20	1.14
74100	1.80	1.70	1.60	1.50
74104	.70	.67	.64	.61
74105	.70	.67	.64	.61

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
74107	1.82	1.73	1.63	1.54
748112	1.82	1.73	1.63	1.54
748114	1.82	1.73	1.63	1.54
748110	1.00	.95	.90	.85

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
74107	.54	.51	.48	.45
74121	.60	.57	.54	.51
74122	.74	.71	.68	.65
74123	1.30	1.20	1.10	1.00
74141	1.75	1.66	1.57	1.48
74145	1.50	1.43	1.36	1.29
74150	2.00	1.85	1.70	1.55
74151	1.30	1.24	1.18	1.12
74153	1.70	1.60	1.50	1.40
74154	2.75	2.55	2.35	2.05

Catalog Number	Qty		100-990	100-990
	Per Item (Mtx)	Per Item (Mtx)		
74155	1.56	1.49	1.42	1.35
74156	1.46	1.39	1.31	1.23
74157	1.56	1.48	1.39	1.31
74158	1.56	1.48	1.39	1.31
74160	2.20	2.10	2.00	1.90
74161	2.20	2.10	2.00	1.90
74162	2.20	2.10	2.00	1.90
74163	2.20	2.10	2.00	1.90
74164	2.20	2.10	2.00	1.90
74166	2.20	2.10	2.00	1.90

All IC's are supplied in 8-, 14-, or 24-pin DIP (Dual-in-line) plastic or ceramic package except for NE536, NE540, and SE540 which are supplied in TO-3 package. Voltage Regulators LM335, LM336 and LM337 are supplied in TO-3 (Diamond) package.

We give FREE data sheets upon request, so ask for those data sheets that you NEED, even for those listed IC's that you are not buying.

LED 7-SEGMENT DISPLAY:

Solid State Systems has now expanded it's line of LED Displays and also reduced their cost. The following are now available from us at these prices.

	1-49	50-99	100-499	500-999	1,000 up
SSS-1	4.50	4.25	3.75	3.40	3.00
SSS-1C	4.75	4.50	4.00	3.65	3.25
SSS-2	4.50	4.25	3.75	3.40	3.00
SSS-3	7.75	7.50	7.00	6.75	6.50
SSS-4	7.75	7.50	7.00	6.75	6.50
SSS-7	3.50	3.25	3.00	2.75	2.50
SSS-9	3.50	3.25	3.00	2.75	2.50
Minitrans *	3.00	2.75	2.50	2.25	1.90

The SSS-7 and SSS-9 are the common .33 in character height 7-segment and overflow display respectively, with decimal point on the left and wide angle viewing. The SSS-1 and SSS-2 have the same physical dimensions as the SSS-7 and SSS-9 with increased Bie and slightly lower current requirement. The SSS-1C is the same as the SSS-1 except it has a colon instead of a decimal point, making it ideal for use in a digital clock. The SSS-3 and SSS-4 are the new .77 in character height 7-segment and overflow display respectively, with decimal point on the right and readability up to 40 feet. \*Also included above is a new reduced price on our Incandescent 7-segment Display.

Package of 8, 1/4 watt current limiting resistors ..... \$0.30.

**MOLEX IC SOCKET PINS:** Use these economical pins instead of soldering your IC's to PC boards. Sold in continuous strips in multiples of 100 pins only.

100 for \$1.00	200 for \$1.80	300 for \$2.60	400 for \$3.40
500 for \$4.20	600 for \$5.00	700 for \$5.80	800 for \$6.60
900 for \$7.40	1000 for \$8.20	each additional 1,000 \$7.50	

Dual-in-line SOCKETS. Brand new with gold plated pins.

	1-49	50-99	100-499	500-999	1,000 up
14 Pin /Solder	.50	.45	.40	.35	.25
16 Pin /Solder	.55	.50	.45	.40	.30
16 Pin /Wire Wrap	.55	.50	.45	.40	.30
16 Pin /Closed-Entry	.60	.55	.50	.45	.35
16 Pin /Cap	.05	.05	.04	.04	.03

STANCOR TRANSFORMERS: Ideal for use with LM series.

P-8180, 25.2VCT, 1 amp	\$2.75
P-6134, 6.3VCT, 1.2 amp	\$3.00

HEAT SINKS: Wakefield series 680 circuit board coolers. 1 1/2" high with a dissipation up to 20 watts. Designed for use with TO-3 package.

	1-49	50-99	100-499	500-999	1,000 up
Type 680-1.25A	1.20	1.10	1.00	.90	.80

ALLEN-BRADLEY MIL-GRADE (5-band) RESISTORS. Any of the 84 STANDARD 10% values from 2.7Ω to 22MΩ 1/4 or 1/2 WATT. EACH ..... \$0.05

CERAMIC DISC CAPACITORS. Type 56A-1000WVDC:

5, 7.5, 10, 12, 15, 20, 25, 27, 30, 33, 39, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220, 250, 270, 300, 330, 360, 390, 470, 500, 560, 680, 750, 820, 1000, 1200, 1500, 1800, 2000, 2200, 2500, 2700, 3000, 3300, 3900, 4700, 5000μF.

EACH .10μF. EACH ..... \$1.00  
0.01μF. EACH ..... \$1.12

LOW VOLTAGE DISCS, Type UK.

1.0μF, 3V	\$.25	0.47μF, 3V	\$.25	0.2μF, 10V	\$.20
0.2μF, 10V	\$.12	2.2μF, 3V	\$.30	0.01μF, 16V	\$.10

ELECTROLYTIC CAPACITORS: All values are available in both, axial or upright (PC Board) mount. Please indicate your choice.

10μF, 15V	\$.10	30μF, 35V	\$.20	5μF, 50V	\$.10
30μF, 15V	\$.10	50μF, 35V	\$.20	10μF, 50V	\$.15
50μF, 15V	\$.10	100μF, 35V	\$.20	20μF, 50V	\$.20
100μF, 15V	\$.10	500μF, 35V	\$.40	50μF, 50V	\$.20
220μF, 15V	\$.15	1000μF, 35V	\$.50	100μF, 50V	\$.30
500μF, 15V	\$.20	1μF, 50V	\$.10	200μF, 50V	\$.40
1000μF, 15V	\$.30	2μF, 50V	\$.10	500μF, 50V	\$.55
20μF, 25V	\$.15	3μF, 50V	\$.10		


TERMS: Rated firms NET 30 days. Otherwise check or money order with order. BankAmericard and Mastercard are welcome. All invoicing is now done by computer therefore, the following standard charges will automatically be added to your order.

If your merchandise total is between:

			SPECIAL CHARGES	
\$ 0.00 - \$ 4.99	add \$1.00	COI	\$1.00	additional
\$ 5.00 - \$24.99	add \$0.75	Air Mail	\$0.50	additional
\$ 25.00 - \$49.99	add \$0.50	Postal Insurance	\$0.25	additional
\$ 50.00 - \$99.99	add \$0.25	Special Delivery	\$0.75	additional
\$100.00 and up	add \$0.00			

With this new system all shipments will be F.O.B. destination, via First Class or UPS (your choice). These charges include shipping, handling and insurance.

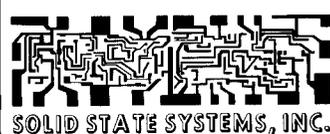MISSOURI RESIDENTS: Please add 4% sales tax.



P. O. BOX 773 • COLUMBIA, MISSOURI 65201

TWX 910-760-1453 • PHONE 314 - 443-3673

BankAmericard  
Master Charge  
ORDER DESK  
1-800-325-2981  
1-800-325-2959

# flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**FOR SALE** Drake R4A, T4X, AC4, and MS4. Factory re-conditioned three months ago. Asking \$525. 601-896-4062. Alvin Schmidt, 147 Brentwood Blvd., Gulfport, Miss. 39501.

**WILL CONSIDER TRADE** of your Drake 2-C for my Drake ML-2. For details write K9DHD, 1006 Wilson, Wheaton, IL 60187.

**METERS, Parts, etc.** List. Barlowe, 55 Wilson, Bethpage, N. Y. 11714.

**VIKING THUNDERBOLT LINEAR**, 10-80 meters. 2000 w. P.E.P. mint, \$200.00 F.O.B. Not modified, with manual, two extra 4-400 A's. WA0KOE, Chet Dill, 1037 Manatt St., Lincoln, Nebr. 68521.

**MODERNIZE FOR PEANUTS!** Frame & Display QSL's with 20 pocket plastic holders. Two for \$1.00, seven for \$3.00. Prepaid, guaranteed. Universally used and approved. Order now. TEPABCO, Box 198H, Gallatin, Tennessee 37066.

**PRINTED CIRCUIT DRILL BITS.** Trumbull, 833 Balra Drive, El Cerrito, California 94530.

**THE CHESAPEAKE BAY BRIDGE-TUNNEL AWARD** is awarded to stations which are operated within the continental United States who work 25 Virginia stations, 5 of which must be located in Virginia Beach. Foreign stations must work 10 Virginia stations, 3 of which must be in Virginia Beach. Amateurs must submit log data, including the dates, times (GMT), stations worked, bands, modes. All contacts must be dated after April 15, 1964. The club reserves the right to request the cards be sent in for examination whenever uncertainty exists. Please send 16¢ in U. S. stamps or two IRC's to cover the cost of postage. The Virginia Beach Amateur Radio Club, 1040 Lockwood Court, Virginia Beach, Virginia 23462 U.S.A.

**WE BUY ELECTRON TUBES**, diodes, transistors, integrated circuits, Semiconductors. Astral Electronics, 150 Miller Street, Elizabeth, New Jersey 07207, (201) 354-2420.

**NEW JERSEY QSO PARTY** from 1900 GMT, Aug. 18 to 0600 GMT Aug. 19 and from 1200 GMT on Aug. 19. Phone and CW are the same contest. A station may be contacted once on each band — phone and CW are considered separate bands. N.J. stations may work other N.J. stations. N.J. stations are to identify by signing "DE NJ" on CW and "New Jersey calling" on phone. Suggested frequencies: 1810, 3535, 3735, 3905, 7035, 7135, 7265, 14035, 14280, 21100, 21355, 28100, 28600, 50-50.5, 144-146. Suggest phone activity on even hours. Exchange consists of QSO numberr, RST, ARRL Section or country. N.J. stations send their county. Other stations multiply number of contacts with N.J. stations by the number of N.J. counties worked. N.J. stations: W-K-VE-VO QSOs count 1 point; DX stations 3 points. Multiply total points by number of ARRL sections (including NNJ and SNJ. KP4, KH6, KL7, KZ5 count both as DX contacts and as section multipliers. Logs must show GMT, date, band, and emission, and be received by Sept. 15, 1973. The first contact for each multiplier must be indicated and numbered. A check list of contacts and multipliers should be attached. Multi-operator entries should be noted and calls of operators listed. Logs and comments should be sent to Englewood Amateur Radio Association, Inc., 303 Tenafly Road, Englewood, N. J. 07631. A #10 SASE should be included for results. Stations planning participation in N. J. are requested to advise the EARA by Aug. 4th so that we may plan for coverage from all counties.

**REPAIR TV TUNERS** — High earnings, complete course details, 12 repair tricks, many plans, two lessons, all for \$1. Refundable. Frank Bocek, Box 3236 (Enterprise Branch), Redding, Ca. 96001.

**QSL'S** — **BROWNIE W3CJI** — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

**USED MYLAR TAPES** — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

**MONTREAL AREA HAMFEST.** Aug. 5. Flea Market, bingo, games, talk-in on all area RPTR's & 146.94 Simplex. For more info, MARC Hamfest, 535 Lansdowne, Westmount, Que.

**REWARD, info., recovery.** Stolen: Yaesu FT-101 s/n 82G12279/CW, 1.8 MHz, Regency HR-2 s/n 03-02030, W4GF, 7216 Valleycrest Blvd., Annandale, Va. 22003, (703) 560-5229.

**27TH ANNUAL VHF Picnic and Hamfest** on Sunday, July 29, 1973, at Turkey Run State Park near Marshall, Indiana. Registration \$1.50 or 4 for \$5.00. There will be prizes, huge flea market, XYL Bingo, and plenty of good fellowship. Talk in on .94/.94 and 52.525 MHz.

**BECKMAN MDL**, 1453 recorder v.g. \$90.00; Beckman 1453 with 4005 scanner v.g., \$120.00; HP/Sanborn twinviso with gears, manual and most attachments in cabinet, \$130.00; WE R067/FSA-14 oscillograph, g-v.g., \$24.00; Cleary printers 16 column, 15 lines per second. One good, \$115.00, one better, \$130.00; Librascope Mdl 200B XY plotter, \$105.00; Amperex NRZ amplifiers for GS 80 as new, \$20.00. Douglas Craton, 5625 Balfrey Dr., W. Palm Beach, Fla. 33406.

**CANADA'S MOST UNUSUAL** Surplus and Parts Catalog. Jam packed with bargains and unusual items. Send \$1. ETCO-HR, Box 741, Montreal, Canada.

**VERY in-ter-est-ing!** Next 6 big issues \$1. "The Ham Trader," Sycamore IL 60178

**SOUTH DAKOTA HAM PICNIC**, August 4, 1973 at Wylie Park, Aberdeen, from 10:00 to ??? Prizes, flea market, activities for XYL and Jr. ops. Limited camping available. For information or tickets contact: WOOGS, 1017 7th Ave. S.W., Aberdeen, S. D. 57401. Talk in on 3955 kHz and 146.94 MHz.

**WORLD QSL** — See ad page 105.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4

**WANTED:** Lafayette HA46, Bob, K6GEV, 11 Wool, San Francisco 94110.

**PLASTIC ENGRAVED CALL PLATES**, w/pin \$1.25. WA2UUY, 15 Vincent St., Parlin, N. J. 08859.



**YAESU FT-101**  
now with 160 meters

SEE **WILSON**  
for your Yaesu products

FTDX 401 Transceiver  
FL2100 Linear Amplifier  
FL2000B Linear Amplifier


Interested in trading Tempo One's  
and other Yaesu equipment.

## WILSON ELECTRONICS

BOX 794 HENDERSON, NEVADA, 89105  
702-451-5791



SHORAN  
AN/APN-84

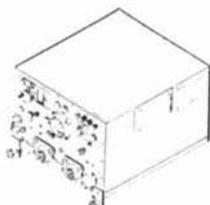

HIRAN  
AN/CPN-2A

## WANTED HIGHEST PRICES EVER

Needed immediately. Hundreds of dollars paid. Want complete units or parts in any condition. AN/APN-84 consists of IP-186/APN-84 Receiver-Indicator and T-342/APN-84 Transmitter. AN/CPN-2A consists of IP-68/CPN/2A Receiver-Indicator, T-230 A Transmitter and 0-18 Oscillator. **Wire collect immediately for top prices.**

Also wanted: RADIO SETS: RT-581/URC-9; AN/GRC-106; AN/ARC-51 AX; AN/ARC-102; AN/ARC-94; AN/ARC-131; AN/ARC-133; RECEIVERS: R-1388/ARN-82; R-1391/ARN-83; TACAN: AN/ARN-52; Plotting Tables: PT-434/ASA-13; AN/ARM-22; MD-83A/ARN; SG-2A/GRM; SG-1A/ARN. We also purchase all Collins Modules and Plug in Units as well as Indicator and Controls. What have you got in Military equipment?

## SPACE ELECTRONICS

Div. of Military Electronics, 76 Brookside Drive,  
Upper Saddle River, N. J. 07458; (201) 327-7640  
TELEX 134-599

WE PAY **HIGHEST**  
PRICES FOR ELECTRON  
TUBES AND SEMICONDUCTORS

## H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK  
ELIZABETH, NEW JERSEY 07206  
(201) 351-4200

## LEARN RADIO CODE



**\$9.95**

Album contains three 12" LP's 2 1/2 hr. Instruction

## THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in **LESS THAN HALF THE TIME!** Available on magnetic tape \$9.95 - Cassette, \$10.95

## EPSILON RECORDS

508 East Washington St., Arcola, Illinois 61910

● QRM QRM QRM QRM QRM QRM QRM QRM ●

### WHY FIGHT QRM?

Win the battle against CW QRM with the new DE-101 using advanced integrated circuit design. Connect it between your receiver and high impedance earphones for a guaranteed superior CW reception. Operate your receiver the same way as before except now you discriminate against QRM. No adjustments, the DE-101 is factory tuned and complete with built in ac supply. One year warranty. 4" x 2 1/2" x 6" \$29.95 plus \$2.00 shipping. Ala. residents add 5% sales tax.

### DYNAMIC ELECTRONICS INC.

BOX 1131 DECATUR, AL. 35601

● QRM QRM QRM QRM QRM QRM QRM QRM ●

**SIGNAL ONE OWNERS**, expert and prompt service by ex-Signal/One engineer. Write or call for details. Larry Pace, K2IXP/7, 1071 W. Roller Coaster, Tucson, AZ. 85704 (602-888-5234).

**THE MT. AIRY VHF RADIO CLUB** (Pack Rats) will hold the 18th annual family day and picnic, Sunday, August 12 (rain date August 19) at the Fort Washington State Park, Flourtown. The event features games, entertainment, and free soda. Talk-in stations will be on 50.2 MHz AM, 52.525 MHz FM, and 146.52 MHz FM.

**16TH ANNUAL PICNIC AND HAMFEST**, on Sunday August 5th at the Frankfort Picnic Grove, 1 mile north of U. S. 30 on U. S. 45, Frankfort, Ill. Food and Drinks, Swap and Shop. Advance registration \$1.50. Admission at gate \$2.00. For further information and advance tickets contact Val Hellwig, K9ZWW, 3420 South 60th Court, Cicero, Ill. 60650.

**FOR YOUR FUTURE ROBYN RADIOS** send your order to, Two Way Radio Sales, 1501 Monroe Street, Bogalusa, La. 70427 or 202 Farrell Street, Picayune, Miss. 39466.

**W9OG**, will be on the air daily during the Evansville Freedom Festival, June 29 through July 4, 1973. This year will mark the fourth annual Freedom Festival, a six day celebration, ending with the nation's largest aerial fireworks display. All amateurs are invited to attend in person or call CQ Freedom Festival during the festival. An appropriate QSL card will be sent to all stations worked.

**DISCOUNT SPECIALS!** Clegg FM-27A @ \$378! Standard SR-C146 @ \$219.50, SR-C826M @ \$258! Genave, Miida, Mosley, Tri-Ex, Gladding, Sonar, Shakespear, many others. Also Marine and C.B. Arena Communications, Dept. C., 1169 N. Military Highway, Norfolk, Virginia 23502.

**TO CELEBRATE** the 350th Anniversary of the first settlement in the State of New Hampshire, the special events station WP1ORT will operate during the period 1-19 August 1973. Modes of operation will be cw, ssb and SSTV. Probable phone frequencies are 14.230 (SSTV), 14.300, 7.250 and 3.925 MHz. QSL with s.a.s.e. or s.a.e. and IRC to P. O. Box 1973, Portsmouth, New Hampshire 03801.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 543-H West 184th, Gardena, California 90248.

**BECKMAN R1** Fitgo amplifier 1000 Mohm input impd. Transistorized, rack mount, \$125.00; Servo Corp. 880CS sweeper. Sweeps up or down. Adjustable sweep width, rate and markers, \$250.00; Hermach Englehart transfer standard mdl. A, \$170.00; Elin precision power oscillator, rm, \$65.00; Sylvania H35F black light, approx. 4-6 watt, \$3.00 ea.; 5/10.00 ppd.; 2N575 180 w. Honeywell, good for high power inverter, \$3.00; 100v 125A rectifier, \$2.50, 100v 160A, \$3.50, 200v 160A, \$5.00, 200v 260A, \$8.00; 70/752 vdt 12" ASCII RS232, vg., \$900.00; 70/752 vdt with 3 special features and tty coupler, \$170.00. Douglas Craton, 5625 Balfrey Dr., W. Palm Beach, Fla. 33406.

**TOROIDS**, iron "E" powder 80-10 meters. .500" — 8/1.00, .680" — 5/1.00, .940" — 4/1.00, 1.437" — 75¢ each or 3/\$2.00, 2.310" — \$1.50 or 3/\$4.00. Please include 50¢ postage, slightly more on large orders. Fred Barken, WA2BLE, 274 E. Mt. Pleasant Ave., Livingston, N. J. 07039.

**COLLINS F500, Y500, A6910** 455 kHz mechanical filters, 6 kHz wide \$20.00 ppd. John K7DOT, 1462 Harrop, Ogden, Utah 84404.

**GREATER INDIANAPOLIS HAMFEST**, August 12, 1973. Gas Co. Recreational Area, 2 miles East of Emerson Ave. on Thompson Rd. P. O. Box 19449, Indianapolis, Ind. 46219.

**CAPE COD'S** fabulous Hyannis! N. E. ARRL Convention, September 29 & 30. Flea market, seminars, FM, SSTV, AMSAT, YL trips, 2 pools, golf, beaches, sailing. Early bird registration \$3. W1KCO, 572 Berkley Street, Taunton, MA. 02780.

**YOUR KWM2 CAN WORK BETTER** — You can do it, too. Write W0BNF, Box 105, Kearney, Nebr. 68847.

## SPACE SAVER TOWERS & MASTS

CZ series towers, cranks up, installs without guy wires. New lacing design creates greater strength. Mini and Magna rotating masts . . . high strength galvanized tubing, self supporting crank-up.

For complete details and prices please check your local dealer or write  
Certified Welders L.A. City License #634

**TRISTAO TOWER CO.**  
P. O. Box 115, Hanford, California 93230

## SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model ST-1A Series D, \$116.50 pp. Solid State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for home, experiments, education, industry, etc.

PHONE OR WRITE FOR CATALOG.  
DIAL 402-967-3771

Many other kits, parts and plans available including starter kits, focus bellows, coils, vidicon tubes, camera plans, etc.

1301 BROADWAY, N.W. **ATV Research** - DAKOTA CITY, NEBR. 68731

**AM/FM P.C.B.** Unused rejects, some with broken connections, broken resistors, etc. AS IS. With AM/FM loop stick; 2 gang, AM/FM tuning capacitor; 8 transformers, miniature, RF, IF, etc.; (IF's 455 KC & 10.7 MC); transistors, diodes, resistors, capacitors; etc. On brown, bakelite board, 3 3/4" x 3" x 1 1/2" high, with all parts. 1 lb. 10/\$7.00; 5/\$3.75; ea. 79¢

**CO-AX CONNECTORS.** ALL BRAND NEW, individually polyfilm bagged; except \* which are unused, bulk, some discoloration.

### N TYPE

**UG-21/U**, cable male for RG8 or RG9/U. \* 10/\$3.50; 3/\$1.10; each 39¢

**UG536/U**, cable male, for RG58/U or RG55/U. 4/\$3.00; each 79¢

**UG-27/U**, rt. angle adapter, 1 3/4" each side; \* 10/\$4.00; 5/\$2.25; each 50¢

**UG-27A/U**, as above but 1 1/2" each side; 10/\$7.50; 5/\$4.00; each 85¢

**UG-997A/U**, rt. angle chassis receptacle. 10/\$7.50; 4/\$4.00; each 85¢

**UG-201A/U**, adapter; fits N type chassis receptacle, takes BNC type cable male; 10/\$9.25; 5/\$4.75; each \$1.00

### BNC TYPE

**UG909A/U**, bulkhead receptacle, for RG55 & RG58/U. 4/\$2.50; each 69¢

**9113T-5**, chassis receptacle. Heavy gold plated. 10/\$9.25; 5/\$4.75; each \$1.00

**RF-01172-75**, cable male for RG-179/U, RG187/U or RG-188/U, 75 ohm. 4/\$2.50; each 69¢

**95712A-100-594**, cable male for RG-176/U; 50 ohm. 4/\$2.50; each 69¢

**CH-239**, male chassis plug, UHF type. Fits SO-239, so transmitter accessories can plug direct to transmitter, eliminating double males, or cable with 2 PL-259. BULK, clean, bright. Reduced to clear 10/\$4.75; 5/\$2.40; each 50¢

New flyer ready. Included free with each order.

All others — SELF ADDRESSED STAMPED ENVELOPE REQUIRED.

All prices are NET, FOB store. PLEASE include sufficient for postage & insurance. Any excess returned with order. For Illinois deliveries, please add 5% for "sales tax".

**BC ELECTRONICS — c/o BEN COHN**

Store at 5696 N. Ridge Ave., Chicago, Ill. 60666.

Hours - Wed. 11:00 a.m. to 2:30 p.m.; Sat. 10:00 a.m. to 2:30 p.m. Other times by appointment.

**MAILING ADDRESS**


1249 W. Rosedale Ave., Chicago, Illinois 60660

Phones — 312-334-4463 & 784-4426
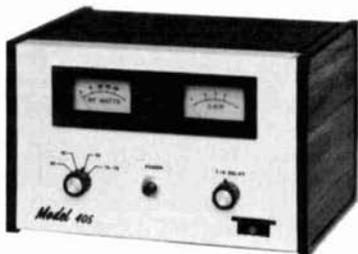
# Summertime is Ten-Tec time...

Wherever you go, take Ham Radio with you. A TEN-TEC solid-state transceiver will keep you in touch with old and new friends.

Enjoy the out-of-doors, operate on vacation, mobile or portable, with a rig you will use year around.



## ACCESSORIES

- Model 210**  
115/230V AC to 12V DC, for  
Argonaut only .....Price \$24.95
- Model 250**  
115/230V AC to 12V DC, for  
Argonaut and "405" Linear....Price \$49.00
- Model 215**  
Ceramic microphone for  
Argonaut .....Price \$17.00
- Model KR5**  
Keyer .....Price \$34.95
- Model 206**  
Calibrator. 100 kHz .....Price \$23.95

## Argonaut

- 80-40-20-15-10 meters SSB/CW.  
5 Watts input .....Price \$288.00

## Model 405 Linear

- Solid-state, 100 watts input.  
12V DC. ....Price \$149.00

## PM3A

- 40-20 meters. VFO CW. 5  
Watts input .....Price \$89.95

## PM2B

- 80-40-20 meters. VFO CW. 3  
Watts input .....Price \$65.95

WRITE FOR DETAILS

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862

**MOTRACS:** Late solid state models, Hi-Band, low-split, with all accessories and manuals. A-1 condition. Best reasonable offer. Paul Cuda, WA7QEX, 13502 SE Harold St., Portland, Ore. 97236. Tel. 503-760-2846.

**WANT OLD RADIO SHOW TRANSCRIPTION** discs. Any size or speed. Send details to, Larry Kiner, W7FIZ, 7554 132nd Ave. N.E., Kirkland, Wa. 98033.

**TR-22:** 50 watt dycomm, gain ant., extra xtals. May separate. \$315.00 or trade. Dave Leonard, WA7VKC, 4296 SW Sunset Dr., Lake Oswego, Ore. 97034. Tel. 503-636-2379.

**WARREN HAMFEST,** Largest family style Hamfest in East. Sunday, August 19th, at famous Yankee Lake Park. Giant Fleamarket, swimming, picnicing — All free. QSL W8VTD, Box 809, Warren, Ohio 44482.

**"DON AND BOB" NEW GUARANTEED BUYS.** Triex MW50 tower 250.75; MW65 331.50; W51 (FOB Calif.) 386.00; Ham-M 99.00; TR44 59.95; AR22R 31.95; Hygain TH6DX 139.00; 204BA 129.00; TH3MK3 114.00; Mosley CL36 149.00; CL33 124.00; TA33 114.00; MCQ3B 91.00; S402 143.00; MP33 90.00; Belden 8214 RG8/U foam coax 17¢/ft; 8448 8-wire rotor cable 10¢/ft; Mallory 2.5A/1000 PIV epoxy diode 29¢; write specific needs new panel meters, many stock; quote discontinued tubes; quote Clegg FM27B; Hallicrafters FPM300A; Standard; Regency; Eimac; Midland 2MFM; Collins and CDE replacement parts stock; hardbound technical magazines, many types from Petro library 3.00/yr, write needs. 9-pin ceramic 6LQ6 socket 50¢; 6V/12V/24V/1.5A transformer 2.49; 135V/500MA-6.3V/3A 2.95; All items guaranteed, shipping charges collect. Madison Electronics, 1508 McKinney, Houston, Texas 77002 (713) 224-2668.

**CLEANING OUT SHACK,** Eico 753 transceiver with AC supply, \$100.00; Motorola 41 TRU, 2 meter FM transceiver with accessories, \$50.00; Viking Adventurer novice transmitter, \$25.00; Lafayette communications receiver HA-225, \$40.00. Barry Fluxe, WB8LSV, 32 Willow Spring, Wheeling, W. Va. 26003.

**WANTED** — Hammarlund SP-600JX21 receivers — Need 20 or more. P. O. Box 4039, Foster City, California 94404.

**FINDLAY ANNUAL HAMFEST,** Riverside Park, Findlay, Ohio, Sunday, Sept. 9. Advance donation tickets \$1.00 from C. Foltz, W8UN, W. Hobart, Findlay OH 45840.

**TELETYPEWRITERS** — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

**MOBILE OPS** — Completely shielded ignition system kits available for most U.S. cars 1965-72. Alternator, generator and regulator filters, feed-thru capacitors, copper braid in stock. Write Summit Enterprises, 36 Winchip Road, Summit, N. J. 07901.

**PC BOARDS,** CW time identifier \$12.50, RTTY speed converter \$5.00, TT decoder \$6.50, 200 MHz decade scaler \$1.95. All boards sent ppd. & drilled. Many others available. Charles R. Sempirek/W8WDC, Rt. 3, Box 1, Bellaire, Ohio 43906.

**"P.C.'S"** I can supply boards for any construction article that includes the full size artwork. Many in stock. Write: D. L. McClaren, W8URX, 19721 Maplewood Avenue, Cleveland, Ohio 44135.

**ACTIVE HAMS** — Monthly mailer of reconditioned and new equipment specials. Sell - Buy - Trade. Write: Associated Radio, 8012 Conser, Overland Park, Kansas 66204.

**THE NORTH ALABAMA HAMFEST** will be held in Decatur, Alabama, August 19, 1973. For information write: North Alabama Hamfest Assn. Inc., Box 9, Decatur, Alabama 35601.

**FREQUENCY SYNTHESIZER REPLACES VFO** and delivers clean output from 1 to 30 MHz continuous coverage with calibration accuracy, resolution, and stability to one hertz: \$490. Video adapter converts your oscilloscope into flexible 1024-letter readouts: \$400. Reduced price on MT-5 Morse-RTTY translator gives you complete kit for \$390. TMC-1 Baudot loop to ASCII converter, \$120. Baudot to Morse complete kit \$290. Write for full information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277.

See the TEN-TEC line of solid state transceivers at any of these stocking distributors:

- ALABAMA**  
James W. Clary Co.  
Birmingham
- ALASKA**  
Yukon Radio Supply  
Anchorage  
Fairbanks
- CALIFORNIA**  
M-Tron  
Oakland  
Communications Headquarters  
San Diego  
Quement Electronics  
San Jose  
L.A. Electronic Sales  
Torrance
- COLORADO**  
CW Electronics  
Denver
- CONNECTICUT**  
Hstry Electronics  
Hartford
- FLORIDA**  
Amateur-Wholesale Electronics  
Miami  
Amateur Electronic Supply  
Orlando  
The Ham Shack  
Sarasota
- GEORGIA**  
Johnson Electric Sales  
Griffin
- ILLINOIS**  
Spectrosonics, Inc.  
Chicago  
Trigger Electronics  
River Forest
- INDIANA**  
Graham Electronics  
Indianapolis  
Radio Distributing Co.  
South Bend
- IOWA**  
Hobby Industry  
Council Bluffs
- KANSAS**  
Electronics, Inc.  
Salina
- MICHIGAN**  
Purchase Radio Supply  
Ann Arbor  
RSE Electronics  
Clawson  
Electronic Distributors, Inc.  
Muskegon  
Niles Radio Supply  
Niles
- MINNESOTA**  
Electronic Center  
Minneapolis
- MISSOURI**  
Ham Radio Center, Inc.  
St. Louis
- NEW HAMPSHIRE**  
Evans Radio, Inc.  
Concord
- NEW JERSEY**  
Atkinson & Smith, Inc.  
Eatontown
- NEW MEXICO**  
Lektronix Supply  
Farmington
- NEW YORK**  
Adironack Radio Supply  
Amsterdam  
Arrow Electronics  
Bayside  
Harrison Radio Corp.  
Farmingdale  
Grand Central Radio  
New York  
Barry Electronics Corp.  
New York
- NORTH CAROLINA**  
Freck Radio & Supply Co.  
Asheville  
Vickers Electronics  
Durham
- OHIO**  
Amateur Electronic Supply  
Cleveland  
Universal Service  
Columbus  
ARC Electronics  
Columbus
- OREGON**  
Portland Radio Supply Co.  
Portland
- PENNSYLVANIA**  
Electronic Exchange  
North Wales  
Tydings Company  
Pittsburgh  
"Ham" Buerger, Inc.  
Willow Grove
- SOUTH DAKOTA**  
Burghardt Amateur Center  
Watertown
- TENNESSEE**  
Russ Hellen's "CB Center"  
Memphis
- TEXAS**  
Ed Juge Electronics, Inc.  
Dallas  
Ed Juge Electronics, Inc.  
Fort Worth
- VIRGINIA**  
Arcade Electronics  
Annadale
- WASHINGTON**  
Amateur Radio Supply Co.  
Seattle
- WISCONSIN**  
Amateur Radio Supply  
Milwaukee
- CANADA**  
Ray Hunter & Associate  
Toronto, Ontario  
C. M. Peterson Co. Ltd.  
London, Ontario  
Payette Radio Ltd.  
Montreal, Quebec
- EXPORT**  
E. D. Magnus Co.  
Chicago, Ill.

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862

### 'HAM' UHF 400 MC HIGH POWER TRANSISTORS

3 for \$10. **\$3.95**

By RCA or equal 2N3632, NPN, 23 watts, 3 amps, TO-60 case, with stud mtg. VCEV max 65.



3 for \$10.

### LED 7-SEGMENT READOUTS MAN-4 EQUAL 3.95

0-9 plus letters, Snaps in 14-pin DIP socket. 3/4" x 1/4" x 3/4", 5V 10ma, with decimal point. Like MAN-1

Socket for above, 50c

## Lowest Prices Largest Selection TTL IC's

Brand New "DIP" Packages Order by type number! Spec sheets on request "ONLY"

Type	Price	Type	Price	Type	Price	Type	Price
SN7400	\$0.30	SN7438	.60	SN7481	1.50	SN74145	1.40
SN7401	.30	SN7440	.30	SN7482	.95	SN74151	1.25
SN7402	.30	SN7441	1.40	SN7483	1.50	SN74152	1.60
SN7403	.30	SN7442	1.25	SN7485	1.41	SN74153	2.10
SN7404	.35	SN7443	1.35	SN7486	.55	SN74155	1.55
SN7405	.32	SN7444	1.35	SN7489	3.75	SN74156	1.55
SN7406	.55	SN7445	1.35	SN7490	1.30	SN74157	1.55
SN7407	.85	SN7446	1.65	SN7491	1.50	SN74158	1.55
SN7408	.35	SN7447	1.65	SN7492	1.10	SN74160	1.95
SN7409	.35	SN7448	1.50	SN7493	1.10	SN74161	1.95
SN7410	.30	SN7450	.35	SN7494	1.10	SN74162	1.95
SN7411	.35	SN7451	.35	SN7495	1.10	SN74163	1.95
SN7412	.30	SN7452	.35	SN7496	1.10	SN74164	3.30
SN7415	.55	SN7453	.35	SN7497	1.10	SN74165	3.50
SN7416	.55	SN7454	.35	SN7498	1.10	SN74180	2.20
SN7417	.55	SN7455	.35	SN7499	1.10	SN74181	4.50
SN7420	.30	SN7460	.35	SN7499	1.10	SN74182	2.20
SN7421	.35	SN7464	.35	SN7499	1.10	SN74184	2.50
SN7422	.35	SN7468	.35	SN7499	1.10	SN74185	1.95
SN7426	.37	SN7470	.50	SN7499	1.10	SN74192	1.95
SN7430	.30	SN7472	.50	SN7499	1.10	SN74193	1.95
SN7432	.30	SN7473	.65	SN7499	1.10	SN74194	1.95
SN7437	.60	SN7476	.75	SN7499	1.10	SN74195	1.95
		SN7478	.95	SN7499	1.10	SN74199	2.65
		SN7480	.75	SN7499	1.10	SN74200	9.99

Factory Marked!

### TTL LOGIC TRANSFORMERS

115/1/60 to 5 volts @ 120 ma. Strap mtg. Stancor

1 for \$1 each

**\$1.98** 3 for \$4.50

1 AMP STRAP MOUNTED FILAMENT TRANSFORMERS

115/1/60 in to 12VCT  
115/1/60 in to 24VCT

### SILICON TUBES

5U4	\$1.49
5R4	3.95
866	7.95

### INTEGRATED CIRCUIT SOCKETS

Buy Any 3 - Take 10% Discount!

14-Pin, dual in line	\$4.45
16-Pin, dual in line	.50
TO-5, 8 or 10 pins	.29

### NATIONAL 'OP' AMPS

BUY ANY 3 - TAKE 10%

Type	Description	Sale
LM-300	Super 723 V. reg.	\$1.49
LM-301	Hi-performance amp	.49
LM-302	Voltage follower	1.49
LM-303	Weg. V. reg.	1.49
LM-305	Pos. V. reg.	.95
LM-307	Super 741	.59
LM-308	Super gain op amp	1.50
LM-309H	SV 200 mil V. reg.	1.50
LM-309K	SV 1-amp V. reg.*	2.25
LM-311	Comparator	1.50
LM-320	Minus 5V 1-amp V.R.*	2.95
LM-320	Minus 12V 1-amp V.R.*	2.95
LM-320	Minus 15V 1-amp V.R.*	2.95
LM-350	Dual peripheral driver	.59
LM-370	AGC squelch op amp	1.49
LM-371	R-F, I-F, op amp	.69
LM-373	AM, FM, SSB, I-F strip	3.75
LM-380	2-watt audio amplifier	1.95

\*TO-3 case, — others TO-5

### LINEAR Op Amps


FACTORY MARKED

531	Hi slow rate op-amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.50
533	Micro power 709 (TO-5)	2.50
536	FET input op amp (TO-5)	3.95
537	Precision 741 (TO-5)	2.50
540	709 pwr driver amp (TO-5)	2.04
545	Precision 723 voltage reg. (DIP)	1.17
555	Timer 2 uSeconds to 1-yr (A)	1.00
556	5 Times faster than 741C	2.80
558	Dual 741 (mini DIP)	3.25
560	Phase lock loops (DIP)	3.25
561	Phase lock loops (DIP)	3.25
562	Phase lock loops (DIP)	3.25
565	Phase lock loops (A)	3.25
566	Function generator (A)	3.25
567	Tone generator (A)	3.10
595	4-bit quad multiplier	.44
702C	Hi-gain, DC amp (TO-5)	1.00
703C	RF-I-F, amp, 14 db (TO-5)	.44
709C	Operational amp (A)	.49
710C	Op amp (mini DIP)	.44
711C	Dual diff. comp (A)	.44
712C	Dual diff. comp (A)	.44
723C	Voltage regulator (A)	.95
741C	Frequency compensator 709 (A)	.49
741C	Freq. comp 709 (Mini DIP)	1.25
747C	Dual 741C (A)	.44
748C	Freq. adj. 741C (A)	.44
748C	Freq. adj. 741C (mini DIP)	.49
709-709	Dual 709C (DIP)	1.00
739-739	Dual stereo preamp	1.00
741-741	Dual 741C (A)	1.00
7545	Dual peripheral driver (DIP)	.69

(A) TO-5 or DIP dual in line pak

### 3 "FANS ON A RACK"

Only \$12.00 2 for \$20

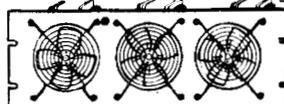

Tri "prop" fans on a silver-gray relay rack panel (19"). Excellent for your "rig", darkroom or any type of electronic work. Even ideal for hobby projects. 200 CFM per 4" fan. Each fan has 5" close mesh guard on each side of fan. Easily reversible. 3000 rpm motor, has hp of 1/80. Operates on 115/160 cycles. Wt. 7 lbs. By Howard Industries.

### HIGH POWER TRANSISTOR WITH HEAT SINK

Removed from new equipment! Includes popular 2N174 'doorknob' transistor TO-36, germanium, PNP, 150 watts, V<sub>CE0</sub> 80V, 15 amps, 40 hfe. For ignition, high power transmitters, etc. Mounted on heat sink 5 x 2 1/2 x 1 1/4".

**\$1.98** 3 for \$4.50



### LITRONIX FDL-7 LED 7-SEGMENT READOUT

Pin-for-pin substitute for famous MAN-1. Electrically the same. Snaps into 14-pin DIP socket. Requires same drivers, i.e., SN7446 or SN7447. Requires 5V @ 20 mils per segment. 0.30 size character with left decimal. Size: 7/16 x 3/16".

**\$2.95** 3 for \$7.98


Buy 3 - Take 10%



### Potter & Brumfield KAP RELAYS

Excellent for "HAM" use as antenna switching, latching, transmit, receive, etc., and 100's of commercial or industrial uses. Includes plastic dust-cover with diagram and hookup info, 11-pin plug-in base, 1/2" x 1/2" moveable gold flashed silver, stationary overlay, with silver cadmium oxide moveables. All contacts 10 amp 3PDT. Coil data, 115VAC 2250 ohms, 17.5 ma. 12 VDC 21 mils 168 ohms. Size: 2 1/4" x 1 5/16". Wt. 4 ozs. Center pin missing. Comar Mfg. type equal too. **\$115 VAC** **\$12 VDC**

**\$2.98** 3 for \$7.98

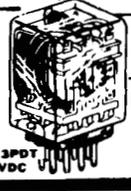

### HOT MOS FETS

2-MOS FETS, N channel 10k umos 3N128, TO-18, RCA	\$1
2-MOS FETS, DUAL GATE, N chan., 3N187-1, TO-18, \$1	
2-MOS FETS, DUAL GATE, N chan., 3N140-1, TO-18, \$1	

### NATIONAL EQUALS ON 'DIGITAL CLOCK on a CHIP'

\*Money Back Guarantee! Any "Chip" \*With Spec Sheet! **\$12.88**

Mfrs	Description	Sale
5311	28-pin, ceramic, any readout, 6-digits: A-B-D	\$12.88
5312	24-pin, ceramic, any readout, 4-digits: C-D	\$12.88
5313	28-pin, ceramic, any readout, 6-digits: A-C	\$12.88
5314	24-pin, plastic, LED and incandescent readouts, 6-digits: A-B	\$12.88

Code: A—Hold Count. C—1 PPS Output. B—Output Strobe. D—BCD



### LED MITY DIGITS "DCM'S"

**9.99** Digital Counting Modules

INCLUDES P.C. EDGE CONNECTOR — FREE!

Will outperform any other DCM on the market today, not gaseous, not incandescent, but a device that will READ almost for life. MAN-4, Monsanto equal.

Kit includes: 3 x 2" printed ckt board, with fingers tool. Side-mounting socket, MAN-4 resistors, 7448, 7475, 7490, booklet.

Terms: add postage. Phone Orders: Wakefield, Mass. (617) 245-3829. Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

Rated: net 30

15¢ CATALOG on Fiber Optics, IC's, Semi's, Parts

## POLY PAKS

P.O. BOX 642H, LYNNFIELD, MASS. 01940

**WANTED:** tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 252, Canal Station, New York, N. Y. 10013.

**BAY STATE SG-132A**, 15 Mc - 400 Mc sweep gen. Ex. cond., manual included, \$750. B. F. Williams Co., P. O. Box 7057, Norfolk, Va. 23509.

**FT-101 YAESU SSB, AM, CW** transceiver. Like new. 260 watts PEP with built in 110/220 volt AC and 12 volt DC power supply. Complete with power cables, microphone, and manual. CW filter and fan. \$555.00. Schedler, W3GQS, 14322 Heathersfield, Houston, Texas 77024.

**KLEINSCHMIDT TELETYPES**, all types. Inquire for prices. All kinds surplus equipment. Send 25¢ for catalog. Andy Electronics, Inc., 6431 Springer, Houston, Texas 77017.

**GLOBAL RESEARCH & Supplies**. Ham equipment & supplies. Dycmm, Galaxy, Tempo, Kenwood, Inoue, B & W, SBE, Hy-Gain, Cush-Craft, Larson. 312/279-4658, P. O. Box 271, Lombard, Ill. 60148.

**GONSET Communicator III** 2 meters \$100, Gonset 3063 2 meter power amplifier \$75, package \$150; Motorola P-33BAC with Ni-Cads 94/94 34/94 \$125; Heath HX-20 \$110, HR-20 \$75, HP-20 \$25, HP-10 \$35, Hustler 80-10 mobile antennas, mast mount \$35, package \$245; you pay shipping — WSPNY, 2506-A 35th St., Los Alamos, New Mexico 87544.

**HAMFESTERS** 39th Hamfest and Picnic, Sunday, August 12, 1973, Santa Fe Park, 91st and Wolf Road, Willow Springs, Illinois. Southwest of Chicago. Exhibits for OM's and XYL's, Famous Swappers Row. Information contact John Raiger, K9DRS, 8919 Golfview, Orland Park, Illinois 60462. Tickets write Joseph Poradyka, WA9IWU, 5701 So. California Ave., Chicago, Ill. 60629.

**VICTOREEN SURVEY METER** for sale, Model 440 — RF/C New, \$90 or best offer. Bayard Rowan, W2GKF, 55 Runnymede Road, Berkeley Heights, N. J. 07922.

**AMERICAN PRODUCTS WANTED** for sales in the Far East. W6PHA, Global America Corp., Box 246, El Toro, Calif. 92630.

**RESISTORS:** Carbon composition brand new. All standard values stocked. 1/2W 10% 40/\$1.00; 1/4W 10% 30/\$1.00 — 10 resistors per value, please. Minimum order \$5.00. 15W RMS 1C Audio Amplifier — Panasonic. Frequency response 20Hz-100 kHz. 1/2% distortion. Price \$6.95 Postpaid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520.

**THE TIPPECANOE ARA** and the Indiana Radio Club Council is again sponsoring the Annual Indiana Club Council Picnic and Hamfest on August 19 at the Tippecanoe County Fairgrounds, located at 1100 Teal Road (Indiana Route #25), Lafayette, Indiana. This is a family hamfest. Flea market, games, trailer parking, awards, and more! Tickets from any IRC club by mail, or at the gate. Tickets by mail from WB9FOT, 2233 Delaware Drive, West Lafayette, Indiana 47906. All tickets \$2, but if purchased by August 1, owner is eligible for pre-registration prize of a Motorola HT X20.

**FOR SALE** — Must sell brand new CX7A Signal/One, \$1600.00. Contact Lewis Grigsby Jr., Farmers State Bank, Pittsfield, Ill. 62363. 217-285-2194.

**HOOSIER ELECTRONICS** — Your ham headquarters in the heart of the Midwest where only the finest amateur equipment is sold. Individual, personal service by experienced and active hams. Factory-authorized dealers for Regency, Genave, Drake, Standard, Clegg, Ten-Tec, Kenwood, Tempo, Midland, Galaxy, Hy-Gain, Cush-Craft, Mosley, Ham-M, Hustler, plus many more. Orders for in-stock merchandise shipped same day. Write or call today for our quote and try personal, friendly Hoosier service. Hoosier Electronics, R. R. 25, Box 403, Terre Haute, Indiana 47802. (812) 894-2397.

**QSLs.** Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

**YOUR AD belongs here too.** Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

**KM-420 CW MESSAGE MEMORY** Write for brochures \$299.95  
**EX-420 CW DELUXE KEYER** Write for QRP 10R AW \$199.95

**GURMS ELECTRO DEVICES** TEL: (415) 964-3136 FAX: (415) 964-3136  
 INC., BOX 4080, MOUNTAIN VIEW, CA. 94040

**1973**

**WORLD QSL BUREAU**  
**THE ONLY QSL BUREAU** to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.  
**5200 Panama Ave., Richmond, CA USA 94804**

**SUMMER IN VERMONT**  
 is a beautiful thing.  
 Come see for yourself while you attend  
**1973 INTERNATIONAL FIELD DAY**  
 Charlotte, Vermont  
**SUNDAY, AUGUST 19, 1973**  
 Details from Bob Hall, W1DQO  
 General Greene Rd., Shelburne, Vt. 05482  
 802-985-2235

**This will turn your repeater on.**

**Automatic Station Identifier \$65**

The CWD-50 provides precisely timed automatic CW ID. The heart of the unit is a factory programmed IC; no more cumbersome diode matrices. The CWD-50 comes ready to install with preset parameters (user may adjust): code speed — 20 wpm, ID interval — 3 min, audio frequency — 1020 Hz, initial delay — 750 msec. The CWD-50 will bring up the repeater for final ID after last use. This is the smallest, most versatile, lowest price CW identifier on the market! To order yours, give call sign and whether you desire 'de'. Enclose \$65 and we pay postage, or remit \$10 and pay balance COD. Fully guaranteed for one year. We also have CWD's for other applications. Write us for more information. For a phone demonstration or to reserve a CWD call Barbara: (303)-794-7234.

**CSC CONTROL SIGNAL COMPANY**  
 5964 W. Columbia Pl., Denver, Colorado 80227

# WE'LL PUT YOU 20 FEET ABOVE THE ROOF


## No Matter How High Your Home May Be

There's a Heights tower to fit every need and every budget. Crank ups, foldovers, TV stand-alones -- we've got 'em all....and they're all aluminum. You can make sure your antenna is mounted at the maximum legal limit the right way, the Heights way. And remember, Heights towers are all aluminum, Heliarc welded for light weight. They're extremely rugged, and very easy to erect.

Write for 12 page brochure giving dozens of combinations of height, weight and wind load. We think you'll be setting your operating conditions to new heights.
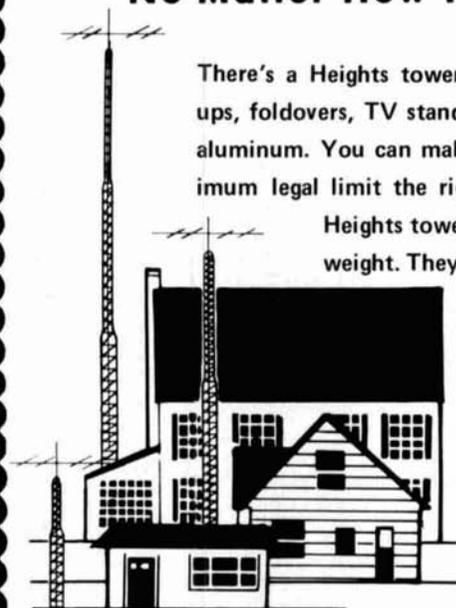
### HEIGHTS MFG. COMPANY

Almont Heights Industrial Park "AT"  
Almont, Michigan 48003



## GATEWAY ELECTRONICS

8123 PAGE AVENUE  
ST. LOUIS, MISSOURI 63130  
314-427-6116

- L. E. D. 7 SEGMENT READOUT — MAN 1 TYPE — NEW \$2.75  
L. E. D. SINGLE SEGMENT — STANDARD SIZE — RED — NEW 35¢ 3/\$1.00  
5 MHz CRYSTAL — Miniature size w/wire leads — \$2.50  
10 MHz CRYSTAL — Standard HC-6/U in 24 volt oven \$2.50  
HEP 411 MOTOROLA DATA LIBRARY SET — contains data on transistors and diodes — both house numbers and registered — 8 lb. \$6.50  
THUMBWHEEL SWITCHES  
— 0.5 x 2.125 x 1.78 — 10 position decimal \$3.00  
— 10 position BCD & Complement \$4.00  
— End Plates (per pair) \$1.45  
MINIATURE SIZE  
— 0.312 x 1.3 x 1.3 — 10 position decimal \$2.50  
— 10 position BCD & Complement \$3.75  
— End Plates (per pair) \$1.00

**\$5 Minimum Order.**

Visit us when in St. Louis.

Please include sufficient postage.



Radio Amateurs  
Reference Library  
of Maps and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables — postpaid \$1.25

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D. C., Miami, Seattle, San Francisco & Los Angeles. — postpaid \$1.25

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries. — postpaid \$1.25

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. size 8 3/4" x 12" — postpaid \$2.50

**Complete reference library of maps** — set of 4 as listed above — postpaid \$3.75

See your favorite dealer or order direct.

WRITE FOR  
FREE  
BROCHURE!

RADIO AMATEUR

callbook INC.



Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

The most powerful signals under the sun!



# Hy-gain

## Redesigned

# HAMCAT


## Out-hustles them all!

The famous HAMCAT...now redesigned for greater performance...*equals* or *exceeds* the performance of any other Amateur Mobile antenna. *We guarantee it!* And you need buy only one mast...whether you mount it on fender, deck or bumper. There's just one set of coils and tip rods...and they all stand up to maximum legal power. That's performance, that's value...*THAT'S HY-GAIN!*

Original Hy-Q "quick changer" coils wound on tough fiberglass coil forms for greater heat resistance, less RF absorption / Fiberglass shielded coils can't burn up, impervious to weather / Shake-proof, rattle-proof, positive lock hinge now even stronger...eliminates radio noise / All stainless steel tip rods won't bend or break / Full 5' mast gives you 10% more radiating area than the competition / Rugged swivel-lock stainless steel base for quick band changes, easy garaging.
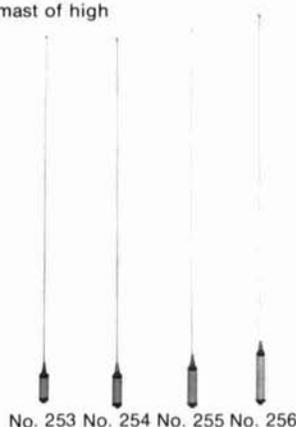
### Get the Hamcat...from Hy-Gain

- Order No. 257 All new design 5' long heavy duty mast of high strength heavy wall tubing **\$16.95**
- Order No. 252 75 meter mobile coil **\$19.95**
- Order No. 256 40 meter mobile coil **\$17.95**
- Order No. 255 20 meter mobile coil **\$15.95**
- Order No. 254 15 meter mobile coil **\$12.95**
- Order No. 253 10 meter mobile coil **\$10.95**
- Order No. 499 Flush body mount **\$ 6.50**



## HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WG, Lincoln, Nebraska 68505

No. 499

### March 1968 (first issue)

**FEATURING:** 5-band SSB exciter, IC-regulated power supply, Remotely-tuned 10-meter beam, Transistor curve tracer, Double-balanced mixers.

### May 1969

**FEATURING:** Potpourri of integrated-circuit applications, FM repeater receiver performance, RTTY converter, IC noise blander, The ionospheric e-layer.

### June 1969

**FEATURING:** Solid-state single-band SSB transceiver, External-anode tetrodes, FM communications receiver, RTTY tuning unit, Top-loaded vertical.

### August 1969

**FEATURING:** Homebrew Parabolic Reflector, Solid-state Q-5er, Frequency calibrator with mos IC's, New multiband quad antenna, Troubleshooting with a scope.

### September 1969

**FEATURING:** FM techniques and practices, IC power supplies, 1296-MHz varactor tripler, Tunable bandpass filters, Amateur microwave standards.

### October 1969

**FEATURING:** Hot Carrier Diodes, Low-cost linear IC's, Diversity antennas, solid-state 432-MHz exciter, Tropospheric-duct communications.

### November 1969

**FEATURING:** Op Amps . . . theory, selection & application, WWV receiver, Multiband antenna, Electronic key, Six-meter collinear.

### June 1970

**FEATURING:** Communications experiments with light emitting diodes, FM modulation standards, Designing phase-shift networks, Transistor frequency multipliers, RTTY frequency-shift meter.



### July 1970

**FEATURING:** Inductively tuned high frequency tank circuit, Solid-state receiver, Digital frequency counter, Two-meter kilowatt, SCR-regulated power supplies, High-frequency hybrids and couplers.

### August 1970

**FEATURING:** High-performance filter/preamplifier for vhf-uhf receivers, 100 MHz digital frequency scaler, Tunable audio cw filter, Stable solid-state vfo, Cubical-quad antenna design.

### October 1970

**FEATURING:** An swr meter for accurate rf power measurements, Direct-conversion receiver, IC voltage regulators, 432MHz converter, Introduction to thyristors.

### December 1970

**FEATURING:** SSB generator, RF interference, Antenna bridge, QRP transmitter, AFSK oscillator.

### April 1971

**FEATURING:** Inductors, VHF and UHF coil-winding data, Using ferrite and powdered cores, FM control head, Power fets, Five-band linear amplifier.

### June 1971

**FEATURING:** A practical approach to 432-MHz SSB, FM carrier-operated relay, Audio

agc systems, Practical IC's, Low-noise 1296-MHz preamp.

### September 1971

**FEATURING:** Practical Photo-fabrication of Printed-circuit boards, Injection lasers, FM sequential encoder, Multimode i-f system, RTTY afc, IC phase-locked loops.

### March 1972

**FEATURING:** Remotely switched broadband HF linear, 2300 MHz converter, FM i-f filter, reciprocating detector, digital integrated circuits.

### April 1972

**FEATURING:** 2 meter FM transmitter, SSB two-tone tester, direct conversion receiver, audio-actuated squelch, tuning toroidal inductors.

### June 1972

**FEATURING:** 5 Band solid-state communications receiver, FM repeater control, SSTV synch generator, microwave experimenting.

### August 1972

**FEATURING:** Frequency synthesizer for Drake R-4, 2304 MHz preamp, audio filters, RTTY Monitor scope, mobile touch-tone.

### September 1972

**FEATURING:** HF power amplifier pi-network design, HF log periodics, RTTY distortion, frequency scaler, repeater timers.

### October 1972

**FEATURING:** 4 channel spectrum analyzer, HF frequency synthesizer, all-band dipole, 160 meter vertical, multi-function IC's.

### December 1972

**FEATURING:** Satellite communications, UHF swr bridge, RTTY monitor, receiver, FM channel elements, helical mobile antenna.

There's no place like a good collection of HAM RADIO back issues to find answers you're looking for. Go over the list above and find the ones you need.



Just 75 each ppd. worldwide.

Enclosed is.....for the issues I have checked.

Name..... Call.....

Address.....

City.....

State..... Zip.....


- March 1968 (first issue)
- May 1969       April 1971
- June 1969       June 1971
- August 1969     September 1971
- September 1969  March 1972
- October 1969     April 1972
- November 1969  June 1972
- June 1970       August 1972
- July 1970       September 1972
- August 1970     October 1972
- October 1970     December 1972
- December 1970

for the most advanced antennas under the sun!



# HY-GAIN 204BA MONOBANDER

...a  
tiger  
on  
20 meters

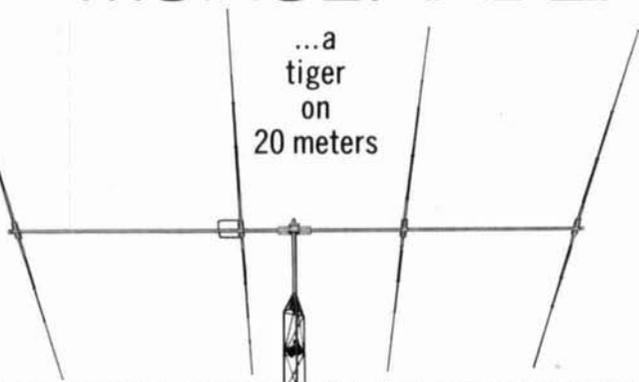

The best antenna of its type on the market. Four wide spaced elements (the longest 36'6") on a 26' boom along with Hy-Gain's exclusive Beta Match produce a high performance DX beam for phone or CW across the entire 20 meter band.

- 10 db forward gain
- 28 db F/B ratio
- Less than 1.05:1 SWR at resonance
- Feeds with 52 ohm coax
- Maximum power input 1 kw AM; 4 kw PEP
- Wind load 99.8 lbs. at 80 MPH
- Surface area 3.9 sq. ft.

The 204BA Monobander is ruggedly built to insure mechanical as well as electrical reliability, yet light enough to mount on a lightweight tower. (Recommended rotator: Hy-Gain's new Roto-Brake 400.) Construction features include taper swaged slotted tubing with full circumference clamps; tiltable cast aluminum boom-to-mast clamp; heavy gauge machine formed element-to-boom brackets; boom 2" OD; mast diameters from 1½" to 2½"; wind survival up to 100 MPH. Shipping weight 51 pounds.

See the best distributor under the sun...the one who handles the Hy-Gain 204BA Monobander.

- Model 204BA** (4-element, 20 meters).....\$149.95
- Model 203BA** (3-element, 20 meters).....\$139.95
- Model 153BA** (3-element, 15 meters).....\$ 69.95
- Model 103BA** (3-element, 10 meters).....\$ 54.95



## FERRITE BALUN MODEL BN-86

Improves transfer of energy to the antenna; eliminates stray RF; improves pattern and F/B ratio. **\$14.95**

## HY-GAIN ELECTRONICS CORPORATION

BOX 5407 - WG / LINCOLN, NEBRASKA 68505

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

## INDEX

- |                             |                     |
|-----------------------------|---------------------|
| —Amateur-Wholesale          | —KRP                |
| —Amtech                     | —KW                 |
| —Andy                       | —Knight Raiders     |
| —Antenna King               | —L. A. Electronix   |
| —Antenna Specialists        | —Larsen             |
| —BC                         | —Logic              |
| —Babylon                    | —MFJ                |
| —Barry                      | —Matric             |
| —Bird                       | —Meshna             |
| —Bitcil                     | —Mor-Gain           |
| —Carvill                    | —Motorola           |
| —Clegg                      | —Nurmi              |
| —Command                    | —Olson              |
| —Communications Specialists | —Palomar            |
| —Comtec                     | —Pemco              |
| —Control Signal             | —Poly Paks          |
| —Curtis                     | —RP                 |
| —Data                       | —Racom              |
| —Drake                      | —Callbook           |
| —Dycomm                     | —Radio Shack        |
| —Dynamic Electronics        | —Regency            |
| —Ehrhorn                    | —Sams               |
| —Eimac                      | —Saroc              |
| —E. S. P.                   | —Savoy              |
| —Epsilon                    | —Signal Systems     |
| —Fair                       | —Solid State        |
| —Frank                      | —Space-Military     |
| —Gateway                    | —Spectrum           |
| —Gray                       | —Swan               |
| —Great American             | —Teco               |
| —H & L                      | —Ten-Tec            |
| —HAL                        | —Tri-Ex             |
| —Ham Radio                  | —Tri-Tek            |
| —Ham Radio Center           | —Tristao            |
| —Heath                      | —VHF Communications |
| —Heights                    | —VHF Engineering    |
| —Henry                      | —Vintage            |
| —Hy-Gain                    | —Weinschenker       |
| —Icom                       | —Wheatlands         |
| —International Crystal      | —Wilson             |
| —International Field Day    | —Wolf               |
| —Jan                        | —World QSL          |
| —Janel                      | —Y & C              |
|                             | —Yaesu              |

Limit 15 inquiries per request.

July 1973

Please use before August 31, 1973

Tear off and mail to  
HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME.....  
CALL.....  
STREET.....  
CITY.....  
STATE..... ZIP.....

# Advertisers iNdex

ATV Research .....	101
Amateur-Wholesale Electronics .....	88
Amtech .....	82
Andy Electronics, Inc. ....	88
Antenna King .....	56, 57
Antenna Specialists Co. ....	2
BC Electronics .....	101
Babylon Electronics .....	94
Barry .....	96, 112
CTG Bitcil .....	82
Carvill International Corp. ....	87
Clegg Division of ISC .....	64
Command Productions .....	84
Communications Specialists .....	84
Comtec .....	94
Control Signal Corp. ....	105
Curtis .....	105
Data Engineering, Inc. ....	93
Drake, Co. R. L. ....	81
Dycomm .....	80
Dynamic Electronics, Inc. ....	100
Ehrhorn Technological Operations, Inc. ....	1
Eimac, Div. of Varian Assoc. ....	Cover IV
Emporium Sounds of Pompano .....	80
Epsilon Records .....	100
Fair Radio Sales .....	94
Frank Electronics .....	94
G & G Radio Supply Co. ....	77
Gateway .....	106
Goodheart Co., Inc. R. E. ....	86
Gray Electronics .....	84
Great American Miniatures .....	88
H & L Associates .....	100
HAL Communications Corp. ....	83
Ham Radio .....	108
Ham Radio Center, Inc. ....	94
Heath Company .....	73
Heights Manufacturing Co. ....	106
Henry Radio Stores .....	Cover III
Hy-Gain Electronics Corp. ....	51, 91, 107, 109
Icom .....	85
International Crystal Mfg. Co. Inc. ....	97
International Field Day .....	105
Jan Crystals .....	86
Janel Labs .....	80
KRP Electronic Supermart, Inc. ....	66
KW Electronics .....	78
Knight Raiders Hamfest .....	82
L. A. Electronix Sales .....	111
Larsen Electronics, Inc. ....	63
Logic Newsletter .....	77
MFJ Enterprises .....	92
Matric .....	88
Meshna, John, Jr. ....	92
Mor-Gain, Inc. ....	82
Nurmi Electronic Supply .....	79, 89
Olson Electronics .....	5
Palomar Engineers .....	78
Payne Radio .....	86
Pemco, Inc. ....	92
Poly Paks .....	104
RP Electronics .....	80
Racom Electronics, Inc. ....	77
Radio Amateur Callbook .....	76, 106
Regency Electronics, Inc. ....	15
Saroc .....	92
Savoy Electronics .....	Cover II
Signal Systems .....	82
Solid State Systems, Inc. ....	98
Space-Military Electronics .....	92, 100
Spectrum International .....	21
Swan Electronics .....	87
Teco Electronics .....	90
Ten-Tec, Inc. ....	102, 103
Tri-Ex Tower Corp. ....	25
Tri-Tek, Inc. ....	86
Tristao Tower Co. ....	101
VHF Communications .....	84
VHF Engineering, Division of Brownian Electronics Corp. ....	90
Weinschenker, M. ....	75
Wheatlands Electronics .....	94
Wilson Electronics .....	100
Wolf, S. ....	84
World QSL Bureau .....	105
Y & C Electronics .....	90
Yaesu Musen USA Inc. ....	95



# "2" Rigs in one!

No longer is it necessary to choose between AM and FM on two meters. Now you can have both in one compact unit. Join the gang on the new FM repeaters yet still be able to "rag chew" with old friends either AM or FM anywhere in the two meter band.

**ALL SOLID STATE - NO TUBES**

MADE IN AMERICA



## Compare These Features

### TRANSMITTER:

- Built-in VFO (Frequency converted for stability)
- AM and FM both crystal and VFO
- Four transmit crystal positions (8 MHz)
- 12 watt input AM and FM
- High level transmitter modulation on AM
- Bandpass coupled transmitter requiring only final tune and load
- Three internal transmit crystal sockets with trimmers for netting
- One transmitter crystal socket on the front panel
- Deviation limiting
- 146.94 MHz crystal included

### RECEIVER:

- Double conversion
- Crystal controlled first conversion
- MOS FET receiver front-end
- Integrated circuit limiter and discriminator for FM
- Envelope detector and series gate noise clipper for AM
- Built-in squelch for both AM and FM


### GENERAL:

- Separate transmitter and receiver tuning
- Built-in 115VAC power supply
- Direct 12VDC operation for mobile or portable operation
- Optional portable rechargeable snap-on battery pack available
- "S" Meter also used for transmitter tune up
- Military style glass epoxy circuit boards
- Anodized lettering and front panel
- Baked epoxy finish on the cabinet
- 47 transistors, 22 diodes, 1 integrated circuit
- Dimensions: 10 1/4" W x 6 1/4" H x 7 1/2" D

All this for just **\$489.95**

*plus*

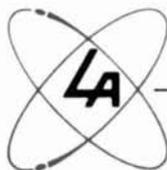**FREE SHIPPING IN U.S.A.  
5 FREE CRYSTALS (\$29.50 VALUE)**



## Electronix Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4456 or (213) 534-4402

CLOSED SUNDAY & MONDAY

See LA for your SWAN needs



# the tempo line

## ...a reputation built on quality and value

IN LESS THAN THREE YEARS THE TEMPO LINE HAS ESTABLISHED A SOLID REPUTATION FOR FIRST RATE PERFORMANCE AT A REASONABLE PRICE. WHETHER YOUR INTERESTS LIE IN HIGH FREQUENCY SSB OR VHF/UHF FM, TEMPO DESERVES YOUR SERIOUS CONSIDERATION. YOU WILL NEVER BE SORRY.



### THE TEMPO ONE SSB TRANSCEIVER

Look at the specifications... look at the price tag... ask any of the thousands of Tempo ONE owners about its reliability... and the reason for its unparalleled popularity will be obvious. The Tempo ONE is now the proven ONE.

**FREQUENCY RANGE:** All amateur bands 80 through 10 meters, in five 500 kHz. ranges: 3.5-4 mhz., 7-7.5 mhz., 14-14.5 mhz., 21-21.5 mhz., 28.5-29 mhz. (Crystals optionally available for ranges 28-28.5, 29-29.5, 29.5-30 mhz.)

**SOLID STATE VFO:** Very stable Colpitts circuit with transistor buffer provides linear tuning over the range 5-5.5 mhz. A passband filter at output is tuned to pass the 5-5.5 mhz. range.

**RECEIVER OFFSET TUNING (CLARIFIER):** Provides  $\pm 5$  kHz. variation of receiver tuning when switched ON.

**DIAL CALIBRATION:** Vernier scale marked with one kilohertz divisions. Main tuning dial calibrated 0-500 with 50 kHz. points.

**FREQUENCY STABILITY:** Less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change.

**MODES OF OPERATION:** SSB upper and lower sideband, CW and AM.

**INPUT POWER:** 300 watts PEP, 240 watts CW

**ANTENNA IMPEDANCE:** 50-75 ohms

**CARRIER SUPPRESSION:** -40 dB or better

**SIDE BAND SUPPRESSION:** -50 dB at 1000 CPS

**THIRD ORDER INTERMODULATION PRODUCTS:** -30 dB (PEP)

**AF BANDWIDTH:** 300-2700 cps

**RECEIVER SENSITIVITY:**  $\frac{1}{2}$   $\mu$ v input S/N 10 dB

**AGC:** Fast attack slow decay for SSB and CW.

**SELECTIVITY:** 2.3 kHz. (-6 dB), 4 kHz. (-60 dB)

**IMAGE REJECTION:** More than 50 dB.

**AUDIO OUTPUT:** 1 watt at 10% distortion.

**AUDIO OUTPUT IMPEDANCE:** 8 ohms and 600 ohms

**POWER SUPPLY:** Separate AC or DC required. See AC

"ONE" and DC1-A.

**TUBES AND SEMICONDUCTORS:** 16 tubes, 15 diodes, 7

transistors

TEMPO "ONE" TRANSCEIVER \$349.00

AC/ONE POWER SUPPLY 117/230 volt 50/60 cycle \$ 99.00

DC/1-A POWER SUPPLY 12 volts DC \$110.00


VF-ONE EXTERNAL VFO \$ 99.00



### THE TEMPO 2001 LINEAR AMPLIFIER

Small but powerful, reliable but inexpensive, this amplifier is another top value from Henry Radio. Using two 8874 grounded grid triodes from Eimac, the Tempo 2001 offers a full 2 KW PEP input for SSB operation in an unbelievably compact package (total volume is .8 cu. ft.). The 2001 has a built-in solid state power supply, a built-in antenna relay, and built-in quality to match much more expensive amplifiers. This equipment is totally compatible with the Tempo One as well as most other amateur transceivers. Completely wired and ready for operation, the 2001 includes an internal blower, a relative RF power indicator, and full amateur band coverage from 80-10 meters. PRICE: \$545.00

### THE TEMPO 6N2

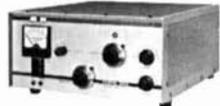

For 6 and 2 meter amateur operation. 2000 watts PEP input on SSB or 1000 watts input on FM or CW. Completely wired in one small package with an internal solid-state power supply, built-in blower, and RF relative power indicator. \$595.00

Prices subject to change without notice.

### THE TEMPO RBF-1



Dual meters continuously monitor output power and SWR during transmission. Offers two power scales of 0-200 and 0-2000 watts plus operation from 1.9 to 150 MHz. Tempo offers this combination in-line SWR bridge and wattmeter at a surprisingly low \$33.50

The Tempo line is available at select dealers throughout the U.S.

Henry Radio stores can now supply the complete line of Yaesu equipment.

# Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701


931 N. Euclid, Anaheim, Calif. 92801 714/772-9200

Butler, Missouri 64730 816/679-3127

"World's Largest Distributor of Amateur Radio Equipment"
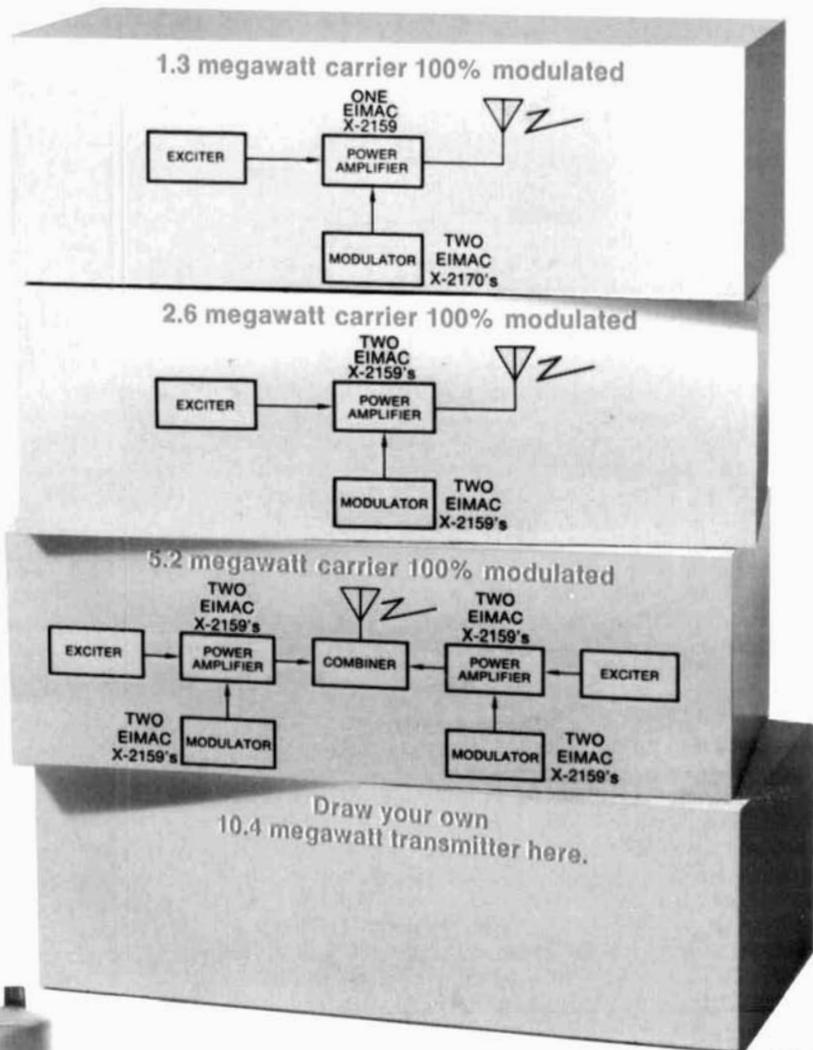
# 10,400,000 Watts!

EIMAC super-power tetrodes provide transmitter "building blocks" up to 10.4 megawatts, 100% modulated.



For information on the X-2159 and X-2170 super-power tetrodes, contact the EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070. Or any of the more than 30 Varian /EIMAC Tube and Device Group Sales Offices throughout the world.



X-2159



X-2170

