

\$2.00

ham radio

magazine

hr 

AUGUST 1980

- tone alert monitor 24
- IC function generator 30
- digital logic probe 38
- AFSK generator 56
- 5CX1500A notes 61



Henry

...STILL THE TOP FAMILY IN LINEAR AMPLIFIERS



IT'S A FACT...HENRY RADIO STILL PRODUCES THE BROADEST LINE OF SUPERIOR QUALITY AMPLIFIERS IN THE WORLD. WHETHER FOR AMATEUR RADIO, COMMERCIAL OR MILITARY USE, WE OFFER A CHOICE OF FIELD PROVEN STATE-OF-THE-ART UNITS TO FIT THE REQUIREMENTS AND BUDGETS OF THE MOST DISCRIMINATING USER.

The 1KD-5 ...the newest member of the famous Henry Radio family of fine amplifiers. And we're still convinced that it's the world's finest linear in its class. The 1KD-5 was designed for the amateur who wants the quality and dependability of the 2KD-5 and 2K-4, who may prefer the smaller size, lighter weight and lower price and who will settle for a little less power. But make no mistake, the 1KD-5 is no slouch. Its 1200 watt PEP input (700 watt PEP nominal output) along with its superb operating characteristics will still punch out clean powerful signals...signals you'll be proud of. Compare its specifications, its features and its fine components and we're sure you will agree that the 1KD-5 is a superb value at only \$695.

The 2KD-5 We have been suggesting that you look inside any amplifier before you buy it. We hope that you will. If you "lift the lid" on a 2KD-5 you will see only the highest quality, heavy duty components and careful workmanship...attributes that promise a long life of continuous operation in any mode at full legal power. The 2KD-5 is a 2000 watt PEP input (1200 watt PEP nominal output) RF linear amplifier, covering the 80, 40, 20, and 15 meter amateur bands. It operates with two Eimac 3-500Z glass envelope triodes and a PI-L plate circuit with a rotary silver plated tank coil. Price \$945.

And don't forget the rest of the Henry family of amateur amplifiers...the Tempo 2002 high power VHF amplifier and the broad line of top quality solid state amplifiers. Henry Radio also offers the 3K-A and 4K-Ultra superb high power H.F. amplifiers and a broad line of commercial FCC type accepted amplifiers for two way FM communications covering the range to 500 MHz.

In a class by itself
2K-4A
If you want to move up to the very best, this is it. The 2K-4A offers engineering, construction and features second to none. Loads along at full legal power for as long as you wish. \$1195.



NEW TOLL FREE ORDER NUMBER: (800) 421-6631
For all states except California.
Calif. residents please call collect on our regular numbers.

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Prices subject to change without notice.

Henry Radio

fact: ARMCHAIR COPY begins here!

The NEW Model 444D For: High/Low Impedance SSB/FM

The Model 444D incorporates all the tried-and-proven features that made Shure's Model 444 the recognized "standard" fixed-station microphone among serious amateurs. The 444D retains the Shure-designed, super-rugged CONTROLLED MAGNETIC® microphone element that lets you come across with "armchair copy"! Its unmatched performance characteristics include a tailored response for maximum voice intelligibility, PLUS...

DUAL IMPEDANCE—(150 ohms) Low & High. Impedance selector switch located on bottom of base.

FREE NAMEPLATE IMPRINTED WITH YOUR CALL LETTERS—Personalized nameplate with your station call letters.

ALL-NEW WIRING GUIDE—Provides user instructions for wiring the microphone to major manufacturers' ham equipment.


IMPROVED CONTROL BAR—Shure Million-Cycle push-to-talk (PTT) improved fingertip action actuates microphone and an external relay or control circuit.

VOX/NORMAL SWITCH—Defeats PTT switch, for VOX equipment requiring continuously "on" microphone. Located conveniently on bottom of base.

PROFESSIONAL BLACK FINISH—Sturdy, high impact ARMO-DUR® base and microphone case is metalized for RF shielding. It is comfortable to the touch in any temperature or humidity, and will not rust or deteriorate.

CONVENIENT INSTALLATION
—The coiled cable leads and push-to-talk switch are arranged to permit immediate hookup to transmitters with either isolated or grounded switching.

FREE! Personalized call letter nameplate

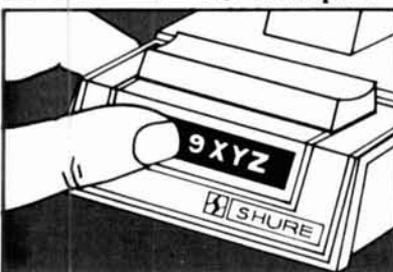

Intelligibility &
Reliability

®  **SHURE** ®

Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204
In Canada: A. C. Simmonds & Sons Limited

Outside the U.S. or Canada, write to Shure Brothers Inc., Attn: Dept J6 for information on your local distributor.
Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

NEW MFJ Multi-Sensor SWR/Peak Wattmeters

MFJ-825 lets you monitor SWR, Peak/Average power, for HF, VHF, QRP rigs. Plug in up to 3 sensors of your choice. Connect and operate up to 3 rigs simultaneously. Switch selects rig to monitor.



Multi-Sensor SWR/Peak Wattmeter
monitors HF, VHF, QRP rigs.

\$119⁹⁵

This NEW MFJ-825 Deluxe Power Sentry is MFJ's exclusive Multi-Sensor SWR/Peak Wattmeter.

With one unit you can monitor SWR, peak, average power for HF, VHF, or QRP rigs.

Secret is plug-in sensors. Plug in up to 3 sensors of your choice (HF, VHF, or QRP, see below). Connect and operate up to 3 rigs simultaneously. Front panel switch selects rig to monitor.

Comes with one sensor of your choice. Use sensors remote or mount in cabinet.

Read forward and reflected power on separate meters. 2 ranges. 2% meter movements.

Read SWR from 1:1 to 6:1. Has SWR sensitivity control, lighted meters, battery check.

Black, etched front panel, rugged metal cabinet. 6-3/4 x 5-3/8 x 5-3/4 in. 9V battery or 110 VAC with optional AC adapter, \$7.95.

MFJ-820 POWER SENTRY, \$69.95. Same as MFJ-825 but less peak function, only one meter,

plug in one sensor at a time.

Comes with one sensor of your choice (see specs below). Use remote or mount in cabinet.

Monitor forward/reflected average power, 2 ranges. SWR 1:1 to 6:1. 2% meter movement.

Has range/mode, reflected/forward power switches, SWR sensitivity control.

Lighted meter (req. 12 V). Black, etched panel, metal cabinet. 3-7/8 x 5-3/8 x 4-1/2 in.

PLUG-IN SENSORS: \$29.95 ea.

Plug up to three in MFJ-825, one in MFJ-820.

MFJ-830 HF SENSOR. 1.8 to 30 MHz. 200/2000 watts, forward, 20/200 watts reflected, full scale. 5 watt SWR sensitivity. Accuracy, $\pm 5\%$.

MFJ-831 VHF SENSOR. 50 to 175 MHz. 20 and 200 watts full scale forward and reflected power. 5 watt SWR sensitivity. Accu., $\pm 7.5\%$.



MFJ-832 QRP HF SENSOR. 1.8 to 30 MHz. 2 and 20 watts full scale forward and reflected power. 500 MW SWR sensitivity. Accu., $\pm 7.5\%$.

MFJ-833 HI-PWR VHF SENSOR. Same as MFJ-831 but 200/2000 W fwd. 20/200 W ref.

Alum. cabinet. SO-239. 2-1/2 x 2-5/8 x 2-1/4 in. Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping).

One year unconditional guarantee.

Order yours today. Call toll free 800-647-1800. Charge VISA, MC. Or mail check, money order. Add \$4.00 each for shipping and handling.

CALL TOLL FREE ... 800-647-1800

Call 601-323-5869 for technical information, order/repair status. Also call 601-323-5869 outside continental USA and in Mississippi.

MFJ ENTERPRISES, INC.
BOX 494, MISSISSIPPI STATE, MS 39762

MFJ Tunable SSB/CW Filter

Instantly zero in SSB/CW signals with tunable peak, notch, lowpass filter.



\$59⁹⁵

Peak, notch or lowpass signals, zero in with freq. control, adjust bandwidth for minimum QRM. Double tuned for extra steep skirts.

Linear freq. control tunes 300 to 3000 Hz. Output is constant as bandwidth is varied flat to 40 Hz. Tight notch to 70 db. 5x2x6 in.

Hear off frequency calls with simulated stereo. Plugs in phone jack. 2 watts out. 110VAC or 9-18 VDC. One year unconditional guarantee.

Try it. If not delighted, return within 30 days for refund (less shipping).

Order your MFJ-751 today. Call toll free 800-647-1800. Charge VISA, MC. Or mail check, money order for \$59.95 plus \$3.00 shipping.

CALL TOLL FREE ... 800-647-1800

For technical information, order/repair status, in Miss., outside continental USA, call 601-323-5869.

MFJ ENTERPRISES, INC.
BOX 494, MISSISSIPPI STATE, MS 39762

NEW MFJ VERSALOAD

MFJ KW DUMMY LOAD

Lets you tune up fast into 50 ohm resistive load. Extend life of finals. Reduce QRM. Includes transformer oil. 1 KW CW, 2 KW PEP for 10 minutes. Low VSWR to 400 MHZ.



Includes high quality transformer oil.
Low VSWR to 400 MHZ.
1 KW CW, 2 KW PEP.

\$29⁹⁵

New MFJ-250 VERSALOAD kilowatt dummy load lets you tune up fast. Extends life of transmitter finals. Reduces on-the-air QRM.

Run 1 KW CW or 2 KW PEP for 10 minutes, 1/2 KW CW or 1 KW PEP for 20 minutes. Continuous duty with 200 watts CW or 400 watts PEP. Complete with derating curve.

Quality 50 ohm non-inductive resistor. Oil cooled. Includes high quality, industrial grade transformer oil (contains NO PCB).

Low VSWR to 400 MHZ: Under 1.2:1, 0-30 MHZ. 1.5:1, 30-300 MHZ. 2:1, 300-400 MHZ.

Ideal for testing HF and VHF transmitters.

SO-239 coax connector. Vented for safety. Removable vent cap. Has carrying handle. 7-1/2 inches high, 6-5/8 inches diameter.

Order from MFJ and try it — no obligation. If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for \$29.95 plus \$4.00 shipping for MFJ-250.

Don't wait, tune up fast and save those finals and reduce on-the-air QRM, order today.

CALL TOLL FREE ... 800-647-1800

Call 601-323-5869 for technical information, order/repair status. Also call 601-323-5869 outside continental USA and in Mississippi.

MFJ ENTERPRISES, INC.
BOX 494, MISSISSIPPI STATE, MS 39762

ham radio

magazine

AUGUST 1980

volume 13, number 8

T. H. Tenney, Jr., W1NLB
publisher and
acting editor

editorial staff

Martin Hanft, WB1CHQ
administrative editor
Robert Schneider, N6MR
assistant editor
Alfred Wilson, W6NIF
technical editor
Thomas F. McMullen, Jr., W1SL
Joseph J. Schroeder, W9JUV
Leonard H. Anderson
associate editors
W. E. Scarborough, Jr., KA1DXG
graphic production manager
Catherine M. Umphress
production assistant
Wayne Pierce, K3SUK
cover

publishing staff

J. Craig Clark, Jr., N1ACH
assistant publisher
advertising manager
Susan Shorrock
circulation manager

ham radio magazine
is published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048
Telephone: 603-878-1441

subscription rates

United States, one year, \$15.00
two years, \$26.00, three years, \$35.00
Canada and other countries (via Surface Mail)
one year, \$18.00, two years, \$32.00
three years, \$44.00
Europe, Japan, Africa (via Air
Forwarding Service) one year, \$25.00
All subscription orders payable in
United States funds, please

foreign subscription agents

Foreign subscription agents are
listed on page 87

Microfilm copies
are available from
University Microfilms, International
Ann Arbor, Michigan 48106
Order publication number 3076

Cassette tapes of selected articles
from ham radio are available to the
blind and physically handicapped
from Recorded Periodicals
919 Walnut Street, 8th Floor
Philadelphia, Pennsylvania 19107

Copyright 1980 by
Communications Technology, Inc
Title registered at U.S. Patent Office


Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices
ISSN 0148-5989

Postmaster send Form 3579 to ham radio
Greenville, New Hampshire 03048



contents

- 12 theory and application
of light-emitting diodes**
Ken Powell, WB6AFT
- 20 measuring signal strength**
Carleton F. Maylott, W2YE
- 24 tone alert monitor**
Harry F. Wetzel, W4KRT
- 30 integrated circuit
function generator**
Frank C. Getz, N3FG
- 34 simplified semiconductor
curve tracing**
Fred Brown, W6HPH
- 38 digital logic probe**
Raymond S. Isenson, N6UE
- 45 challenge for
microwave-antenna designers**
D. Howard Phillips, W6FOO
- 50 cascade intercept point calculations
for communications receivers**
Brian P. Gross, WA7TDB
- 54 diode frequency divider**
Henry S. Keen, W5TRS
- 56 accurate and practical
AFSK generator**
Garry A. Boldenow, K0SFU
- 61 notes on the Eimac
5CX1500A power pentode**
Arthur Reis, K9XI
- 64 160-meter base-loaded
vertical antenna**
Ed Marriner, W6XM
- 66 digital capacitance meter**
Marion D. Kitchens, K4GOK
- 94 advertisers index**
- 87 flea market**
- 92 ham mart**
- 74 ham notebook
6 letters**
- 80 new products**
- 4 observations and
comments**
- 8 presstop**
- 94 reader service**

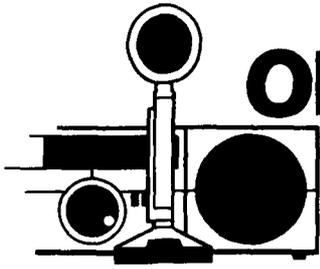

Observations & Comments

Living things change and *ham radio* is no exception. Since the passing of Editor-In-Chief Jim Fisk, I have been asked to take over his editorial page, at least during this difficult transition period. His is not an easy act to follow. Jim was close to the pulse of Amateur Radio, its problems, and the direction in which it's going. Jim did a superb job, and certainly all active Amateurs benefited by Jim's "second look."

My job is to try to carry on the precedent set by Jim in illuminating issues that affect Amateur operating, technology advances, and the future. I'm not as close to the immediate issues of Amateur Radio as Jim was, but that's going to change. I'll have to educate myself so that I can carry on *ham radio's* editorial page in the established tradition. I ask the support of readers in bearing with me.

I'd like to introduce in *observations and comments* some contributions by Amateurs who have something constructive to say. This material will reflect *your* ideas, problems, and what to do about them. If your contribution is positive, it could end up as a guest editorial. Here are some ideas:

Much has been published on FCC proposed rule making affecting Amateurs. If such PRM would have an impact on your sphere of interest, we'd like to hear about it. Give us the pros and cons from your point of view. If your contribution is in the best interest of Amateur Radio, we'll print it in *observations and comments*.

Do you have a club? We'd like to know about the problems you may have encountered in running a ham club so that others may benefit. What about a club paper? How do you run yours?

Say you're a contest operator. What can be done about the selfish attitudes of those who interrupt contest operation?

You've run across a new adaptation of current IC technology. Let's hear about it. Can it be adapted to Amateur Radio?

You don't like the restrictions on satellite communications. Why not? Do you have a better solution?

What about slow-scan TV and interference by SSB operation? The upper end of the 20-meter band is a good example. Is time-sharing the answer?

These are just a few ideas that come to mind. Others are welcome from our readers and will certainly be considered.


The object of this column is to present ideas and comments from our readers that will provide a positive thrust forward for other Amateurs. Reader contributions will be supplemented by editorial comment on current issues and their relationship to Amateur Radio. The idea behind this column is to present an image of what our readers think. Let's hear from you.

Alf Wilson, W6NIF
technical editor



*Simply...
the Best*

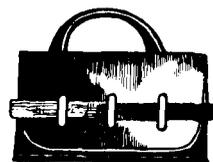ICOM AMERICA, INCORPORATED
2112 116th Avenue N.E., Bellevue WA 98004, (206) 454-8155
3331 Towerwood Dr., Suite 307, Dallas, TX 75234, (214) 620-2780



comments speech processors

Dear HR:

I read with interest the letter by Walter Schreuer of Maximilian Associates and the reply by Wes Stewart concerning his split-band speech processor. Since I have done some comparative on-the-air testing of the two designs, I think that my findings will be of interest.

For my tests, I used three different speech processors: a Vomax, a N7WS split-band, and a quasi-logarithmic audio clipper. All three units were connected to a switching system that allowed instantaneous switching of the various units between the transmitter and microphone. The units were adjusted to provide the transmitter with an equal amount of drive measured by observing the metered ALC level.

Various tests were run with some of the local fellows on 10 meters as well as with DX stations on several bands. At the beginning of the contact, I explained the test I was about to run and asked the operator to note his preference, which unit he thought sounded the best, as well as which provided the most signal "punch." First, a transmission was made with no audio processing to be used by the receiving station as a reference. The three speech processing units were designated **A**, **B**, and **C**, and the stations were not told which was which until the test sequence was completed.

A test run was made by using unit **A**, then unit **B**, then unit **C**; in between testing the units I switched back to a "No Processing" mode for comparison. By keeping a record of these tests, I found that approximately 90 per cent of the stations preferred the N7WS design split-band processor. Operators who preferred the N7WS design said that although there was as much — or slightly more — than average power output with the

Vomax, the N7WS design sounded "crisper." Monitoring my signal with a separate receiver, it sounded to me as though the Vomax suffered from a highly restricted audio bandwidth, with the most notable point being the lack of low frequencies.

I've heard others on the air using the Vomax, and it seems that, while some operators sound excellent, others suffer from the same problem I observed during my tests. This leads me to conclude that the microphone audio response and/or timbre of the operator's voice will determine the audio quality when using the Vomax. (I should point out that only one Vomax unit was available for these tests; I would have liked to have been able to obtain another unit to see if it had the same characteristics.) The quasi-logarithmic processor, while contributing punch to the signal, did not fare well during these tests when compared with the other units because of its high percentage of distortion.

I make no claim that these tests were scientific or definitive; they were conducted only to satisfy my personal curiosity.

Gale A. Steward, K3ND
Quakertown, Pennsylvania

speed of light

Dear HR:

I would like to comment on the paper published in January, 1980 issue by Harold Tolles, W7ITB, regarding the speed of light. The measurement of the speed of light is a difficult task to accomplish, at best, to the precision quoted today. It should be noted that the speed of light has been given to at least six places since before 1930, i.e., 2.99796×10^8 meters per second (m/s). This value has, so to speak, converged to 2.997924580×10^8 m/s as recommended by the Committee on Data

surplus tubes

Dear HR:

The comments by KB5EY and W6SAI in the December issue were very interesting. I, too, have a collection of 813 tubes and presently use one on 75 meters. I am building a near-kW transmitter which will use two in a class-C final.

But let me say something about those surplus, commercial and military, tantalum plate triodes, like the 100-TH and the 250-TH. They were advertised by Eimac many years ago as "gas-free." They can be bought (without warranty) for one or two dollars each at club auctions and flea markets. This is definitely not a "wad" of money. Interestingly, forty years after manufacture these tubes are still "gas-free." If not abused, and such abuse is readily discerned visually, they will perform as per specifications. I am now using a pair of Heintz and Kaufman HK-24 tubes that were made in 1939 in a class-C final on ten meter FM! No TVI, either.

My present collection includes such gems as the 35-T, 100-TH, 250-TH, and 450-TH — with spares. With these tubes 70 per cent (or more) efficient single-band class-C finals are planned. What old timer can deny the romance of ham radio that comes from a room softly illuminated with the glow from those tungsten filaments, and the nearly-white hot plates of a pair of (quite) fully loaded tantalum plate triodes?

Byron H. Kretzman, W2JTP
Huntington, New York

for Science and Technology, and the International Council of Scientific Unions (CODATA-ICSU) in 1973. The principal improvement in the knowledge of the speed of light has been the reduction in the measurement uncertainty from 4000 m/s in 1929, to 1000 m/s in 1951, to 100 m/s in 1963, to 1.2 m/s in 1973. Surely four parts per billion is adequate for ham radio work!

It should be noted that these speeds are in vacuum. When light propagates through any material (e.g., air), its speed is reduced by a factor of one over the material's index of refraction. The index of refraction of air, for example, is dependent on the temperature, pressure, and frequency of the EM radiation on a "point-by-point" basis (for most rf work, electron density distribution in the atmosphere plays a significant role), from which one can (reasonably) infer that the speed of an EM wave varies over the path of propagation. Finally, I suggest that we and Mr. Tolles not despair about c and simply use 3×10^8 m/s, which is good to 0.07 per cent; this value is adequate for all Amateur Radio requirements.

R. Barry Johnson, W4MLM
Rancho La Costa, California

receiver dynamic range

Dear HR:

WB6CTW is to be complimented for his fine article on measuring receiver dynamic range in the November, 1979, *ham radio*. His technique makes it possible for the average Amateur to make meaningful measurements with homebrew equipment. WD6FMG, N6ST, and I have been using Hewlett-Packard signal generators to perform similar measurements. Based on our experiences, I would like to offer several comments on this subject.

1. The measurement of dynamic range for either third-order intermodulation (undesired mixing of two in-

terfering signals) or gain compression (overload by one interfering signal) is not particularly sensitive to the exact difference in the frequencies of the signals. Any difference between 20 and 100 kHz can be used. If the signals are too close together, i-f skirt rejection or local oscillator noise sidebands confuse the measurements; if they are too far apart, the rf preselector attenuates one or both of the signals.

2. Various receivers will show somewhat different results if tested on different bands. Just the same, if all of the receivers in **Table 1** of the article were tested on 40 instead of 20 meters, the ranking would probably be similar. Therefore, the cost of the crystals for the two oscillators could be saved by using some Novice band crystals from the junk box.

3. When performing the two-tone test, misleading measurements may be obtained with some receivers if the AGC is allowed to reduce the rf gain. The intermodulation signals should be kept weak enough that the S-meter barely moves. In some receivers, the stage that generates the intermodulation is a mixer or second amplifier stage that follows a stage with AGC. As the level of the two interfering signals is increased to the point that the intermodulation product appears out of the noise, passes through the i-f filter, and reaches the detector, the AGC will reduce the rf gain. Less signal reaches the intermod generating stage, and less intermod is produced than would be the case if the AGC were disabled. AGC, of course, also decreases receiver sensitivity.

The dynamic range of a receiver is the difference between the weakest signals it can detect, and the largest signals it can handle simultaneously. Unfortunately, different values for dynamic range will be measured depending on the definition of a "weak" signal. Some of the companies that publish dynamic range performance

seem to use creative specsmanship. In one case, the measured value of dynamic range is much better if the sensitivity and intermodulation are compared for a weak signal of S-6 than for a weak signal of S-1. Can you guess which value is the published value?

4. The article suggests that gain compression can be tested with only one signal. This procedure will often give false and inflated results. It is much better to tune the receiver to a weak signal; then adjust the amplitude of a second signal on a different frequency until reception of the first signal is impaired.

For example, a while ago we checked the performance of a popular synthesized 2-meter handheld transceiver. This rig was claimed to have 80 dB rejection 30 kHz away. The signal level for full quieting was measured. Next the receiver was tuned 30 kHz away. Then the amplitude of the signal generator was increased by approximately 80 dB, at which point the receiver was again fully quieted. From this test, one might suppose that the dynamic range was 80 dB.

The receiver was next tested using two signal generators. The first one was tuned to the receiver frequency, frequency modulated with a 1 kHz tone, and adjusted in amplitude until full quieting was achieved. The second signal generator was tuned 30 kHz away and increased in amplitude until the 1 kHz modulation of the first signal became noisy. The difference in the two signal strengths was only 56 dB . . . a lot less than the 80 dB measured the first way!

5. Based on testing one of each model, the TS-520S is much improved over the TS-520 and even slightly better than the TS-820. Owners or prospective owners of the TS-520S should perform their own measurements before they panic.

Paul A. Zander, AA6PZ
Los Altos, California

A LAW PROHIBITING "INTERFERENCE by Radio Transmitter" has been enacted by the Township of Winslow, New Jersey, in the aftermath of TVI/RFI problems experienced by a local Amateur, WB2SZK. Just over a year ago a neighbor complained of TVI plus interference to his stereo, electronic organ, and intercom. Stubs cured the TVI problem, but filters were only partially effective on the other equipment. WB2SZK, after urging the neighbor to seek manufacturer's help with the remaining problems, was summoned to court in November for violation of a township nuisance ordinance and ordered to stay off the air for 30 days pending FCC inspection. When he refused, he was fined \$250 and costs.

The FCC's Inspection in early December gave WB2SZK a clean bill of health, and the complainants were so advised. On December 19 the township then adopted a new ordinance, Chapter 50-10.2, that makes it unlawful to transmit any radio signal that "...causes or creates electrical, visual or audible interference..." or "...annoys, disturbs or endangers the comfort, repose, health, peace, safety or general well being of others within the township." Any interference with "...receiving sets, musical instruments, phonographs or other machine..." is included under the ordinance's omnibus coverage.

WB2SZK Was Again Summoned for hearing, this time under the new ordinance, in February. On his request the FCC submitted a 1977 Public Notice citing federal pre-emption of the control of radio transmissions to township officials, but to no avail. His attorney was able to obtain an interim injunction from the New Jersey Superior Court halting prosecution under the new ordinance, but at a May 2 hearing the Superior Court judge upheld the township ordinance on the grounds that there is no specific federal pre-emption of control of radio communications—it's only implied.

Since This Decision Contradicts previous decisions on the pre-emption question, it sets a dangerous precedent and must be challenged. Over \$1000 (including \$500 from the Mt. Airy Pack Rats) has already been spent, and the necessary appeal in Federal Court will cost much more. Contribution checks made out to Harry B. Stein, W3CL, with the notation "Randy Bynum Defense Fund" can go to 2087 Parkdale, Glenside, Pennsylvania 19038.

A NEW COMMUNICATIONS ACT REWRITE bill, S-2827, has been introduced in the Senate by the Senate Communications Subcommittee. Combining the better and less controversial ideas of the previous rewrite proposals (S-611 and S-622), the new bill includes the 10-year license term, authorizes the FCC to require TVI rejection standards for TV receivers, and—most important—gives the FCC authority to delegate license examination authority to nonemployees.

The Full Text Of S-2827 appears in the June 13 issue of the Congressional Record. Because of the very pro-Amateur-Radio aspects of this revised bill, Amateurs are again urged to write their Senators and Representatives as well as the Subcommittee Chairman, Sen. Ernest F. Hollings (D., South Carolina), and minority leader, Sen. Barry Goldwater. A complete list of the Senate Committee members who are directly concerned with S-2827 appears in the May, 1980, QST editorial. Some Washington observers believe that, with public support, S-2827 has a good chance of being passed by Congress this year.

SSTV AND FACSIMILE WOULD BE permitted on all Amateur voice frequencies above 3775 kHz, under a Notice of Proposed Rule Making adopted by the Commission June 3. Personal Radio Docket 80-252 proposes dropping the present subband restrictions on SSTV, meaning that Generals as well as Advanced and Extra class licensees would be able to use that mode on 80 through 15 meters. Facsimile would be permitted on the same frequencies thus opened to SSTV. 160 was not included in the NPRM at this time, as that band is still shared with Loran, Amateur Radio being a secondary user through 1981. Under the proposed rules change, bandwidth for either mode would be limited to SSB bandwidths below 50 MHz, and to AM bandwidths above.

Comment Due Date is September 22, with Reply Comments due October 22.

FCC'S NEW EXAMS SCORED AN "A" with the first group of applicants who took them recently. According to instructors from several parts of the country, their students rated the new FCC efforts well written, unambiguous, and closely related to the new FCC study guides. They also liked the practical emphasis on operating procedures in the Technician/General-class exams with more technical subjects covered in the higher class tests. Congratulations to Jay Jackson, AF40, and the other FCC staff members who are responsible for the new exams.

HAM RADIO'S NEW TECHNICAL Editor is Alf Wilson, W6NIF. Alf is no stranger to ham radio, having been Jim Fisk's technical right-hand man since the magazine's early days. He will be working on ham radio through the summer to help ensure its continued technical accuracy while the search for a permanent editor continues. Prior to his retirement several years ago, Alf was a Technical Publications Specialist for General Dynamics in San Diego.

Move over imports, here's the new TEN-TEC

DELTA

the notable change in hf transceivers



All new, all nine hf bands and only \$849!

DELTA — the symbol of change—the name of a great new TEN-TEC transceiver. A transceiver for changing times, with new features, performance, styling, size and value. **TOTAL SOLID-STATE.** New, by the world's most experienced manufacturer of hf solid-state amateur radio equipment.

ALL 9 HF BANDS. First new transceiver since WARC. 160-10 Meters including the three new hf bands (10, 18 & 24.5 MHz). Ready to go except for plug-in crystals for 18 and 24.5 MHz segments (available when bands open for use).

SUPER RECEIVER. New, low noise double-conversion design, with 0.3 μ V sensitivity for 10 dB S+N/N.

HIGH DYNAMIC RANGE. 85 dB minimum to reduce overload possibility. Built-in, switchable, 20 dB attenuator for extreme situations.

SUPER SELECTIVITY. 8-pole monolithic SSB filter with 2.4 kHz bandwidth, 2.5 shape factor at 6/60 dB points. And optional 200 Hz and 500 Hz 6-pole crystal ladder filters. Eight pole and 6-pole filters cascade for 14 poles of near ultimate skirt selectivity. Plus 4 stages of active audio filtering. To sharpen that i-f response curve to just 150 Hz bandwidth. 4-position selectivity switch.

BUILT-IN NOTCH FILTER. Standard equipment. Variable, 200 Hz to 3.5 kHz, with notch depth down to -50 dB. Wipes out interfering carriers or CW.

OFFSET TUNING. Moves receiver frequency up to ± 1 kHz to tune receiver separately from transmitter.

"HANG" AGC. For smoother, clearer, receiver operation.

OPTIONAL NOISE BLANKER. For that noisy location, mobile or fixed.

WWV RECEPTION. Ready at 10 MHz.

"S"/SWR METER. To read received signal

strength and transmitted standing wave ratio. Electronically switched.

SEPARATE RECEIVER ANTENNA JACK. For use with separate receiving antenna, linear amplifier with full break-in (QSK) or transverters.

FRONT PANEL HEADPHONE AND MICROPHONE JACKS. Convenient.

DIGITAL READOUT. Six 0.3" red LEDs.

BROADBAND DESIGN. For easy operation. Instant band change—no tuneup of receiver or final amplifier. From the pioneer, TEN-TEC.

SUPER TRANSMITTER. Solid-state all the way. Stable, reliable, easy to use.

200 WATTS INPUT. On all bands including 10 meters (with 50 ohm load). High SWR does not automatically limit you to a few watts output. Proven, conservatively rated final amplifier with solid-state devices warranted fully for the first year, and pro-rata for five more years.

100% DUTY CYCLE. All modes, with confidence. 20 minutes max. key-down time. Brought to you by the leader in solid-state finals, TEN-TEC.

QSK — INSTANT BREAK-IN. Full and fast, to make CW a real conversation.

BUILT-IN VOX AND PTT. Smooth, set-and-forget VOX action plus PTT control. VOX is separate from keying circuits.

ADJUSTABLE THRESHOLD ALC & DRIVE. From low level to full output with ALC control. Maximum power without distortion. LED indicator.

ADJUSTABLE SIDETONE. Both volume and pitch, for pleasant monitoring of CW.

SUPER STABILITY. Permeability tuned VFO with less than 15 Hz change per F^o change over 40° range after 30 min. warmup—and

less than 10 Hz change for 20 Volt AC line change with TEN-TEC power supply.

VERNIER TUNING. 18 kHz per revolution, typical.

SUPER AUDIO. A TEN-TEC trademark. Low IM and HD distortion (less than 2%). Built-in speaker.

SUPER STYLING. The '80s look with neat, functional layout. "Panelized" grouping of controls nicely human engineered for logical use. New, smaller size that goes anywhere, fixed or mobile (4 3/4" h x 11 3/8" w x 15" d).

Warm, dark front panel. Easy-to-read contrasting nomenclature. Black "clam-shell" aluminum case. Tilt bail.

MODULAR/MASS-TERMINATION CONSTRUCTION. Individual circuit boards with plug-in harnesses for easy removal if necessary. Boards are available.

FULL ACCESSORY LINE. All the options: Model 282 200 Hz CW filter \$50; Model 285 500 Hz CW Filter \$45; Model 280 Power Supply \$139; Model 645 Dual Paddle Keyer \$85; Model 670 Single Paddle Keyer \$34.50; Model 247 Antenna Tuner \$69; Model 234/214 Speech Processor & Condenser Microphone \$163; Model 215 PC Ceramic Microphone \$34.50; Model 283 Remote VFO; Model 287 Mobile Mount, and Model 289 Noise Blanker available soon.

Experience The Notable Change In HF Transceivers, Experience DELTA. See your TEN-TEC dealer or write for full details.

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862
EXPORT-105 LINCOLN AVE. CHICAGO, ILL. 60644




114.8	2000	118.8	2100
110.9	841	123.0	2150
107.2	852	127.3	2200
103.5	1950	131.8	2250
100.0	770	136.5	2300
97.4	1900	141.3	2350
94.8	1850	146.2	2400
91.5	1900	151.4	1900
88.5	887	156.7	2450
85.4	1750	162.2	2500
82.5	1700	167.6	2550
79.7	1840	173.8	1238
77.0	1600	179.9	2171
74.4	1500	186.2	1477
71.9	1600	192.8	1633
67.0	800	203.5	2806
OFF			

Communications Specialists TE-64

Food for thought.

Our new Universal Tone Encoder lends it's versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequency-just dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

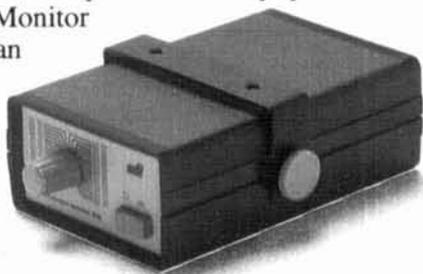

- All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak.
- Instant start-up.
- Off position for no tone output.
- Reverse polarity protection built-in.

Group A

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 M1

- Frequency accuracy, $\pm .1$ Hz maximum - 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- Continuous tone

Group B

TEST-TONES:	TOUCH-TONES:	BURST TONES:			
600	697 1209	1600	1850	2150	2400
1000	770 1336	1650	1900	2200	2450
1500	852 1477	1700	1950	2250	2500
2175	941 1633	1750	2000	2300	2550
2805		1800	2100	2350	

- Frequency accuracy, ± 1 Hz maximum - 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Wired and tested: \$79.95

 **COMMUNICATIONS SPECIALISTS**

426 West Taft Avenue, Orange, California 92667
(800) 854-0547/ California: (714) 998-3021



light-emitting diodes: theory and application

A digest of LEDs —
how they work
and how they're used
in many of
today's electronic circuits.
Also included is
a simple logic probe
for testing digital circuits

Learning the theory of the electronic devices we use can be greatly enhanced by putting the theory to work with a weekend construction project. This is just what we have in this article: some basics, a few applications, and a very easy construction project. A few hours invested should yield a good understanding of light-emitting diodes (LEDs) and a unique logic probe that fits well with today's technology.

Initially these LED devices were too expensive for the Amateur or experimenter, but their wide acceptance and availability now make them a workable addition to our hobby. As Amateurs continue their transition from vacuum tubes, through transistors and into integrated circuits, the LED will become more valuable as an indicator, display, or active component.

For practical applications we can think of the LED indicator, or the individual segments of a LED display, as being the same as any other diode; much like the power diodes used as rectifiers, or the small-signal diodes used as detectors. As with any diode, we must operate within the parameters of the device as specified by the manufacturer. Under these conditions the LED will function well.

To illustrate the relationship between a silicon diode and a LED, I've shown both devices under similar conditions in **fig. 1**. Both are forward biased, and the current through each is limited by the series resistor, R1. The voltage drop across the silicon diode, or its threshold voltage, is approximately 0.6 volt. If the value of R1 is changed, the current through the diode will vary, but the voltage across the diode will remain fairly constant. In effect, the diode will act as a voltage regulator. The diode could be used as a shunt regulator in the same manner as a voltage-regulator tube found in many receivers and VFOs of the past. In semiconductor circuits, one or more of these diodes are often used as regulators and clamps, making good use of this threshold action.

The same conditions exist for the LED except that the threshold voltage is higher, usually about 1.6 volts for the red LEDs. As with the silicon diode, varying the series resistor will vary the current through the LED and thus its intensity, but the voltage drop across the LED will remain fairly constant at 1.6 volts.

From **fig. 1** it can be seen that all we must do to activate a LED is apply forward bias and limit the current to a safe value, as specified by the device manufacturer. As shown in **fig. 1**, a simple application of Ohm's law is all that's needed to use the LED as an indicator. An understanding of the basic principles of the diode will enable you to get started in the applications of LEDs.


Fig. 2 illustrates the parameters of a typical red LED. As shown, 100 per cent of the rated intensity is achieved with 1.6 volts at 0.020 ampere. These parameters were used to calculate the series-resistor value in **fig. 1**. The threshold voltage for colors other than red vary from this norm. Typical values are, for amber devices, approximately 2.0 volts. For green units threshold approaches 4.0 volt level.

These numbers are adequate approximations for general use and will provide a starting point for unknown surplus units. The amber and green LEDs generally require more current than the red LEDs to achieve equal intensity. However, our eyes are very understanding in this area, and the current through the diode can vary over a formidable range without a profound effect on the indicator's appearance.


By Ken Powell, WB6AFT, 6949 Lenwood Way,
San Jose, California 95120

applications

We tend to think of LEDs as low-voltage devices primarily associated with transistors or integrated circuits. However, with suitable current-limiting resistors, these devices will function equally well in higher-voltage circuits. The type 4403, for example, has an isolation voltage rating between the leads and case of 300 volts. This rating allows the device to serve as an indicator in moderately high voltage circuits.

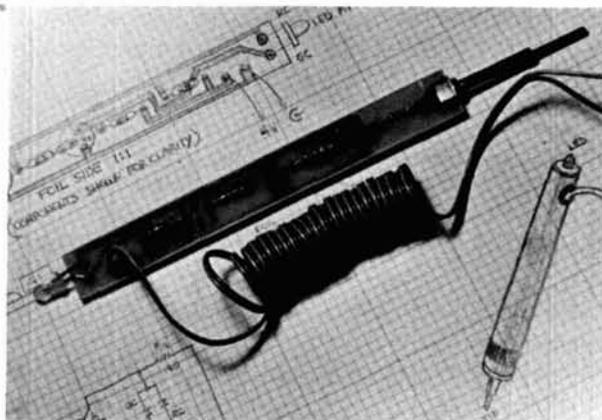

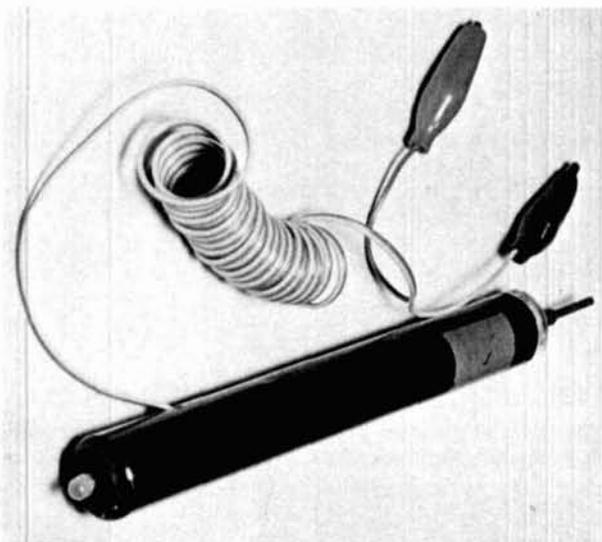Complete logic-probe board ready for assembly.



A logic probe for testing digital circuits. A few parts and as many pleasant hours at the workbench produced this useful and handsome piece of test gear.

Voltage monitor. Fig. 3 illustrates this principle by the use of a LED to monitor the power-supply voltage in a tube-type receiver. The calculations required to determine the value of the series resistor is shown;

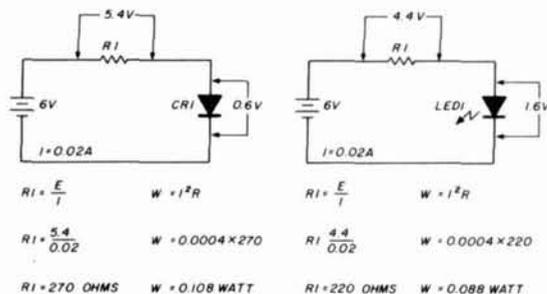


fig. 1. Silicon diode and LED under similar operating conditions: each is forward biased, and current through each device is controlled by series resistor R1. Threshold voltage across the silicon diode is about 0.6 volt, whereas that across the LED is somewhat higher, usually about 1.6 volts (for red LEDs). Simple application of Ohm's law determines device operating parameters.

note that this application is no different than the basic circuit discussed in fig. 1. From this application it can be seen that we're not limited to low-voltage or solid-state circuitry in the use of LED devices. With higher voltage applications, the series-resistor value becomes greater along with increased power requirements; but the physical size is still within reason, and the looks are more in keeping with today's technology.

The majority of LED applications encountered are in dc circuits, but these devices aren't limited to dc and make excellent indicators for ac if some precautions are taken in their application. One of the parameters not yet discussed is the reverse-voltage specification. The reverse breakdown voltage of LEDs is

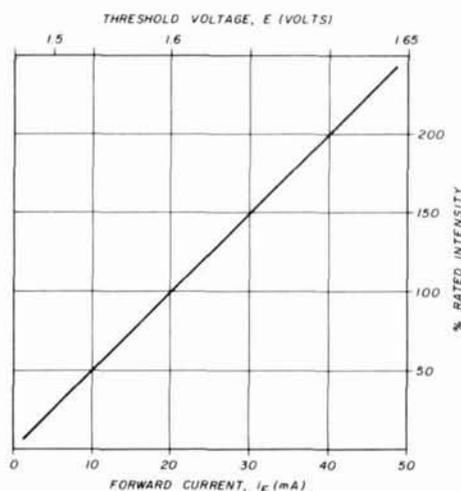


fig. 2. Intensity of a typical red LED as a function of threshold voltage and forward current. One-hundred per cent of rated intensity occurs with 1.6 volts at 20 mA. These data were used to calculate the series resistor, R1, in fig. 1.

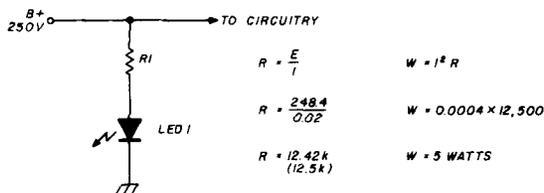


fig. 3. A voltage monitor that can be used, for example, in a power supply of moderate voltage. Calculations for series-resistor values are shown.

$$R = \frac{E}{I} \quad W = I^2 R$$

$$R = \frac{248.4}{0.02} \quad W = 0.0004 \times 12,500$$

$$R = 12.42k \quad W = 5 \text{ WATTS}$$

generally low, so particular attention must be paid to this specification. The reverse breakdown voltage for the type 4403 is typically 3 volts, meaning that the reverse bias voltage must be kept below this level.

Filament-circuit monitor. In fig. 4 an LED is used to monitor a filament circuit, and a diode is placed inversely in parallel with the LED to limit the reverse voltage applied to the LED to approximately 0.6 volt, or the threshold of the silicon diode. This diode will protect the LED during negative excursions of the filament voltage. As in the previous circuits, the limiting-resistor value is calculated with Ohm's law as shown in fig. 4A, but the power must be calculated as in fig. 4B, since the current flow will be greater on the negative half cycles when shunt diode CR1 is conducting. That is because of the difference in LED threshold voltage and that of the silicon diode. In this case, the difference in power is minimal but should be taken into account, particularly with higher source voltages and higher threshold LED devices, such as amber and green units. The reverse-voltage parameter is an important factor and must be kept in mind when thinking about LED applications.

Color transistions. Another type LED, the MV-5491, is illustrated in fig. 5. This unit is actually

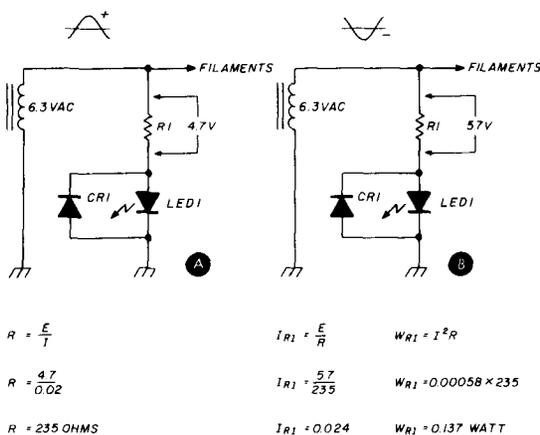


fig. 4. Using an LED to monitor a filament circuit. The limiting-resistor value is calculated as in (A), but the power dissipation must be calculated as shown in (B).

two LED junctions in a single package placed inversely in parallel. One of the parallel diodes is red; the other is green. As with the LEDs discussed earlier, the threshold voltages of the two diodes are different, so a bit more thought is required in their application.

With the MV-5491, the color can be changed by reversing the voltage applied to the diode pair; and with the application of an ac voltage, an alternating color that approximates yellow can be obtained. This device can achieve four states: red, green, amber, and off.

In fig. 5A the red diode is conducting and the limiting resistor, calculated for a specification of 1.65 volts at 0.20 ampere, controls the current through

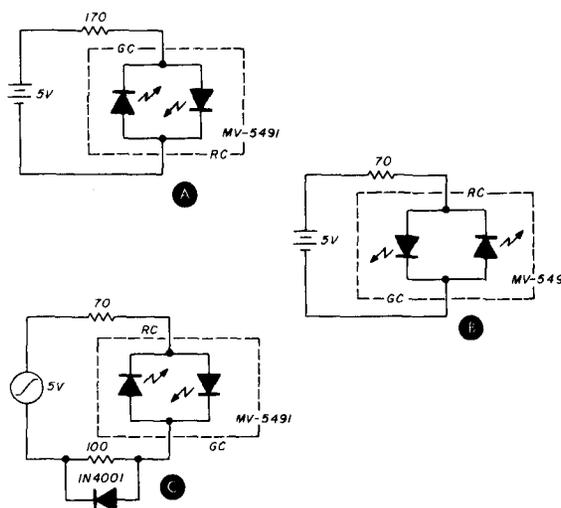


fig. 5. Example of a dual-diode LED, type MV-5491. This device is actually two LED junctions in single package placed inversely in parallel. Sketches (A), (B), and (C) show, respectively, how the LED colors are generated. (A) shows the diode pair in a red configuration; (B) shows green. With the application of an ac voltage and the use of a compensating diode, as seen in sketch (C), an amber color can be generated.

the diode. In fig. 5B, the green diode is in conduction, and the limiting resistor has been chosen to provide 3.0 volts at 0.020 ampere. Because of the difference in the specifications of the red and green diodes, external components must be used to provide compensation. Fig. 5C illustrates this compensation in the form of a silicon diode that will shunt the 100-ohm resistor when the green LED is conducting. Reversing the polarity of the input voltage will reverse bias the silicon diode, placing an effective 170-ohm resistance in series with the red LED. In this manner the correct voltage and current can be furnished to the dissimilar LED junction.

LED drivers. So far in the discussion all the LED applications have been of the static type. To make these units dynamic, or to turn them on and off with signals, a switching device must be added in series with the LED to control the current flow. In **fig. 6** a transistor switches the LED on and off with a signal or logic level to be monitored. In **fig. 6A** the voltage across each element of the circuit is shown with the transistor in conduction and the LED indicator lighted. The calculation for the current-limiting resistor is the same as in previous illustrations except for the added voltage drop of the transistor, usually on the order of 0.2 volt. As in previous illustrations, 1.6 volts appears across the LED and 3.2 volts across the limiting resistor. In **fig. 6B** the circuit is shown with the transistor cut off and the LED indicator extinguished. In **fig. 6C** a similar circuit is depicted for use with a negative power supply.

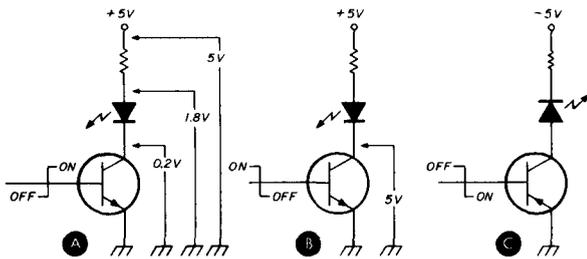


fig. 6. Dynamic application of LEDs. A transistor controls current flow; that is, a switching device is used. (A) shows the transistor conducting (LED illuminated); (B) shows the transistor cut off (LED extinguished). In (C) a circuit is shown for use with a negative power supply. In these applications the device is called an "LED driver."

Integrated circuits lend themselves well to driving LED devices, and six LEDs can be controlled from a single IC package. The SN7406 and SN7407 are well suited for this application. The 7406 is a hex-inverter with each of its output circuits rated at 0.040 ampere and 30 volts. As shown in **fig. 7**, the 7406 will cause the LED to conduct when conditioned with a high, or positive, input. The 7407 is the same basic package but is a noninverting circuit, so a high input will yield a non-conducting, or high output, extinguishing the LED.

In applications requiring more than one LED indicator, the 7406 and 7407 form a very compact and cost-effective circuit. They are useful for adding monitors to keyboards and for data bus applications. The calculations for the current-limiting resistors in this application are identical to those discussed earlier. Just about any open-collector TTL IC will work well as an indicator driver; and for practical applications, the LED current can be limited to 0.010 ampere to

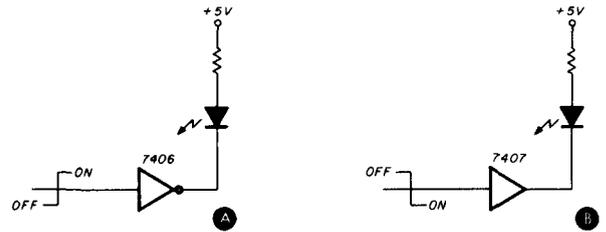


fig. 7. In this example of LED drivers using ICs, as many as six LEDs can be controlled from a single IC package. (A) and (B) show, respectively, drivers with inverting and noninverting inputs.

reduce current use. This will yield adequate light output in virtually all situations.

Driving a dual LED, such as the MV-5491, is a bit more complex. But the result of the LED changing color with changes in the signal is more dramatic and can be accomplished with ICs. **Fig. 8** shows a driver circuit for dual LEDs using one mini-dip, type SN75452, and one section of a SN7404 inverter.

The calculations for resistor values are the same as those in previous illustrations, but the power requirements are a bit more. With the driver input low, the input to IC1A is high and its output is low. In this state 4.8 volts will be dissipated across the 220-ohm resistor, placing the green cathode (GC) at 0.2 volt. IC1B, with its low input, will have a high or nonconducting output. This action will allow the green diode to be forward biased, and 1.8 volts will be dissipated across the 100-ohm resistor. When the circuit input goes high, IC1A and IC1B outputs will change state, and 4.8 volts will be dissipated across the 100-ohm resistor. The red diode will go into conduction, and 3.15 volts will be dissipated across the 220-ohm resistor. Rapid transitions of the input signal will alternate the red and green LEDs and form a somewhat amber indication.

The dual-LED indicator makes a very nice display. The ability to display a number of states with a single

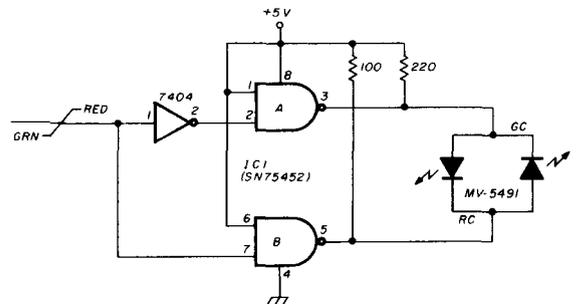


fig. 8. A dual LED driver using the type SN75452 IC. Calculations for the resistor values are the same, but the power requirements are a bit higher.

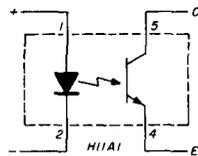


fig. 9. Application of the LED as an optical coupler. In this case the LED has been packaged with its light output focused onto a photo transistor. In this configuration the device can provide a signal path while providing electrical isolation of more than 2500 volts.

indicator is very useful, particularly in digital applications such as circuit monitoring. The IC driver circuitry could be replaced with discrete transistors if desired, and no doubt many applications for this unique device will be implemented by Amateurs and experimenters. As with many other devices, these units were expensive when first developed but are readily available at low cost today. The MV-5491 is packaged in the standard T-1 $\frac{3}{4}$ package and uses the same mounting hardware as most LEDs.

the optical coupler

All of the LEDs previously discussed have been indicator types, so now is a good time to take a break and look at another LED device known as the optical coupler. The coupler uses the LED for a much different purpose — that of isolation. This device can provide a signal path while furnishing electrical isolation in excess of 2500 volts. Again it is the basic LED with virtually the same parameters as those of the LED indicator. However, in the coupler configuration the LED has been packaged with its light output focused on the sensitive surface of a photo transistor (fig. 9). In this manner, the current flow through the LED will provide base bias for the transistor through an optical path within the package, providing signal coupling while maintaining physical isolation.

While I've not seen these devices used extensively in Amateur gear, I have used them in keyer circuits to

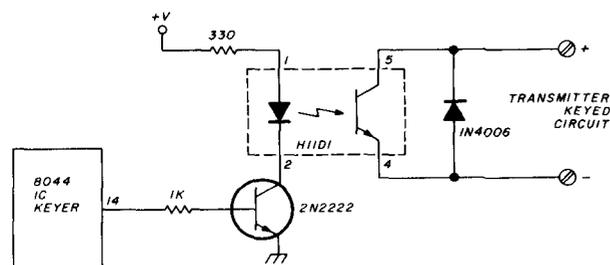


fig. 10. Use of the LED optical coupler in an Amateur keyer. Device isolates the IC keyer from the transmitter, removing grid-block keying voltage, which is sometimes rather high, from the keyer paddles.

isolate the keyer from the transmitter. They are a very effective device in this application and remove the grid-block keying voltage, which is sometimes at a fairly high potential, from the paddles. This application is depicted in fig. 10. The optical coupler, or opto-isolator as it is also called, is used extensively in medical and data-processing equipment. I think that, as Amateurs become more aware of the unique properties of this device, many new and worthwhile applications will ensue.

The coupler in fig. 10, type H11D1, is packaged in a six-pin mini-dip, so it lends itself well to today's construction techniques. Keep this device in mind for both safety and noise reduction applications.

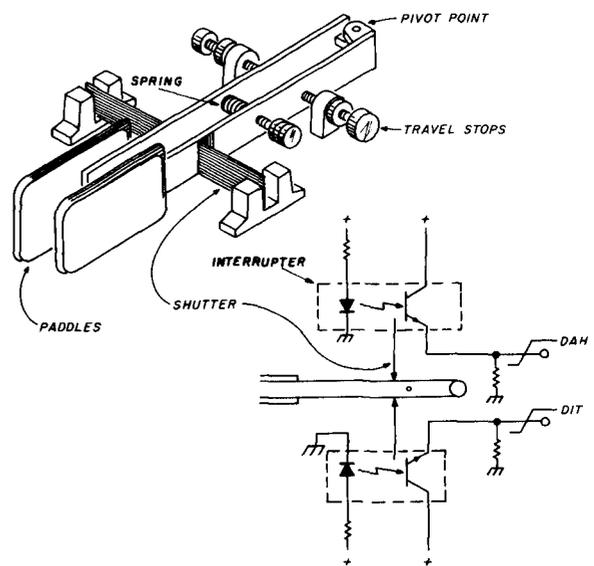


fig. 11. A contactless keyer, or "optical paddle," using an LED optical interrupter. The optical interrupter is similar to the optical coupler, except that the light path from the diode to the photo transistor can be interrupted with a shutter or other mechanical device.

optical interrupter

Another interesting device in the LED family is the optical interrupter. Its construction is similar to that of the optical coupler, except that the light from the diode to the photo transistor is accessible, meaning that the light path can be broken or interrupted with a shutter blade or other mechanical device. When this action occurs, the output transistor will be cut off, which allows an easy mechanical interface to electronic circuitry. I've not seen this device used to any great extent in Amateur applications, but I think a contactless keyer would be a good item to begin with. I've shown one in fig. 11 and hope to build a device such as this in the near future. The ease with which it will interface digital logic makes it a natural.

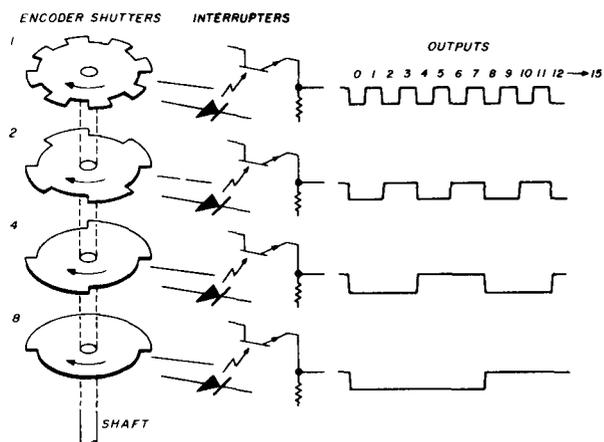


fig. 12. Example of a shaft encoder using the optical interrupter. No electrical contacts in the encoder mean increased reliability and low maintenance. BCD outputs are shown for each encoder shutter. A neat way to encode your antenna rotator for digital readout!

shaft encoder

Another application comes to mind and seems quite reasonable, since the once-plentiful selsyns are rather difficult to find these days. This application is a position indicator or shaft encoder. Using digital techniques, you could easily get sixteen discrete positions with only four optical interrupters. Adding another interrupter would double the resolution; this could be carried out to any degree desired.

By arranging the shutters and interrupters in a for-

mat such as shown in fig. 12, you would obtain a four-wire BCD output. This could be carried out to an eight-digit arrangement and applied to the input of a micro processor if you really wanted sophistication and had an extra eight-bit port on your micro. This would yield 256 discrete outputs or positions.

Put a device like this under your antenna rotator or weather vane and you would have a real winner! The same scheme could be used for 180-degree capacitors and multi-turn inductors for remote tuning. This low current, contactless device could form the basis for some interesting, reliable equipment.

LED displays

The seven-segment display is probably the most widely used LED display available today. This popularity has made the price right for the Amateur. The display can be thought of as seven individual LEDs placed in a single easy-to-use package and arranged to provide a numeric output. Each individual element or segment has parameters that are similar to those of the diodes discussed earlier. These devices are available in a common-anode configuration, which is generally used for applications involving a positive power supply and the common-cathode configuration usually associated with negative supply designs. Fig. 13 illustrates both types and the physical relationship of the individual diodes as viewed from the front or display side.

This illustration shows how the characters are formed by forward biasing the individual diodes, or segments, in a prescribed manner. The character

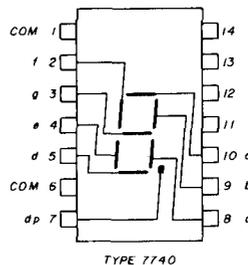
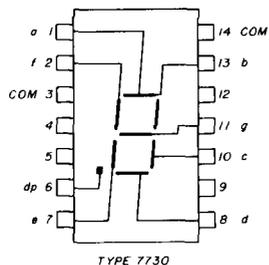
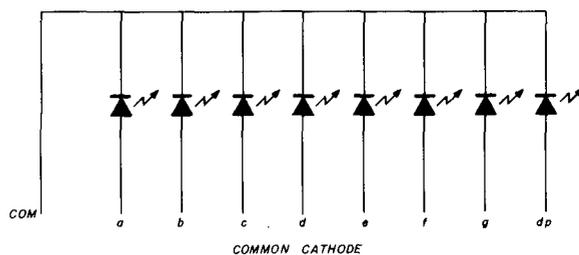
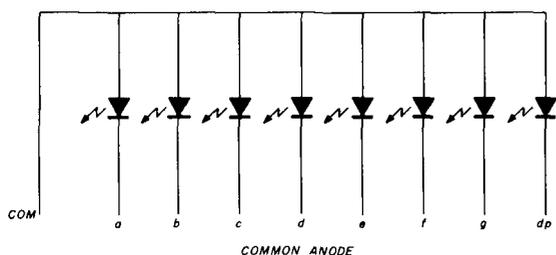


fig. 13. Examples of seven-segment LEDs designed for positive power supplies (common anode) and negative supplies (common cathode). The characters are formed by forward biasing the individual diodes, or segments, in a prescribed manner. These displays have decimal points (DP). Units are available with left-hand, right-hand, both, or no decimal point. Colors are red, green, and yellow (amber).

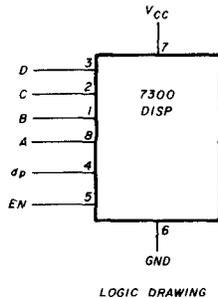
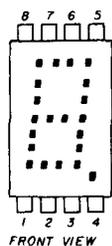
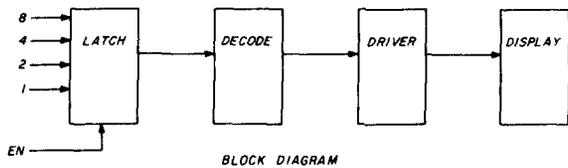



fig. 14. Integrated displays have an IC built into the package. The IC provides decoding, storage, and a display driver. Cost, however, is five to ten times that of the seven-segment type on the surplus market. Device is a dot matrix type and accepts a four-wire BCD input. Others are available with bar-type LEDs such as used in the seven-segment displays.

"0" would be formed by forward biasing the elements labeled "a" through "f." The displays used for this illustration have decimal points (dp), and units are available with left-hand, right-hand, both, and no decimal point. As with the other LEDs discussed, seven-segment displays are available in red, green, and yellow; as with the indicator units, voltage and current parameters vary accordingly.

A number of physical sizes and package configurations are available, and the price is often less than a dollar per digit on the surplus market. The units used in the illustrations are configured in a 14-pin DIP package and furnish a character height of 0.3 inch (7.6 mm). This seems to be an adequate size for most projects, and bezels are readily available to give your project a finished look.

the integrated display

The integrated display unit is a display much like the seven-segment LED, with the addition of an IC built into the display package. The IC provides decoding, storage, and display driver — all within the display package, and requires no more space than the seven-segment display. All these functions being performed by the display unit make it much simpler to use and reduces component count considerably. As can be expected, there's a hitch: the cost of the display is five to ten times that of the seven-segment type on the surplus market. This sounds very high indeed, but in figuring the total expense of the compo-

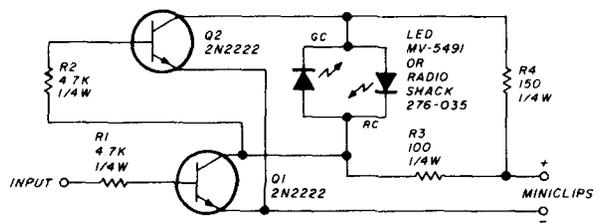

PC BOARDS, PARTS, AND KITS ARE AVAILABLE FROM:
J. OSWALD 1436 GERHARDT AVE.; SAN JOSE, CA 95125
COMPLETE KIT \$15.50 PPD. (AT TIME OF PUBLICATION)

fig. 15. Schematic diagram of a logic probe that can be built in a few hours with readily available components. Logic probe output indicator yields three discrete states according to input signal or level. Power is borrowed from the circuit under test.

nents required to do the functions of the integrated display, it's often cost effective, particularly when space is at a premium.

The integrated display illustrated in fig. 14 is a dot matrix type and accepts a four-wire BCD input. Other integrated displays are available with bar-type LEDs such as used in the seven-segment display. Various types of logic configurations are available such as counters, latches, and hexadecimal decoders. These devices interface TTL logic very well and can make the design and construction of counters and similar devices relatively easy.

logic probe

The logic probe is a good application of the theory discussed earlier and makes an ideal instrument for digital testing. It can be constructed in a few hours using readily available components. The output indicator of the logic probe yields three discrete states according to the input signal or level. The probe borrows power from the circuit under test and is designed to function with the popular TTL logic families.

The circuit of the logic probe is shown in fig. 15 and is a variation of the dual LED circuit in fig. 8. When power is applied to the probe through the power leads, and the tip or input is touched to a low level or ground, Q1 is cut off. This condition will cause Q2 to conduct since the base is positive with respect to the emitter. With Q1 cut off and Q2 conducting, the green diode of the dual LED will be forward biased, yielding a green output from the LED. Touching the probe tip to a high level will cause Q1 and Q2 to complement, and the red diode will be forward biased, yielding a red output from the LED. An

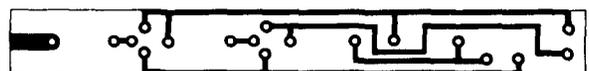


fig. 16. Full-size foil pattern for the logic probe.

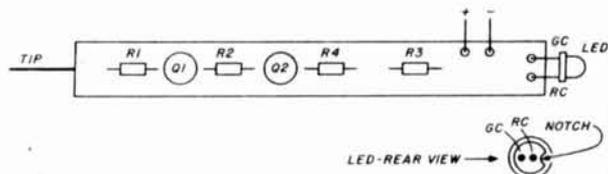


fig. 17. Logic-probe component layout.

alternating signal will cause alternating conduction of the red and green diodes and will yield an indication approximating amber. In this manner both static and dynamic signals can be traced with the logic probe.

Printed circuit construction is used for the logic probe, and a full-size foil pattern is shown in fig. 16. After etching and drilling the PC board, the components are mounted as shown in the component-side view, fig. 17. Fig. 18 is a sketch of the probe assembly. I used the components from an Eico demodulator probe for construction, but any plastic or plexiglass tubing with approximately 1/2-inch (13-mm) ID will suffice. The end caps can be cemented in place after the PC board is slipped into the tubing, and your logic probe should be ready to go to work.

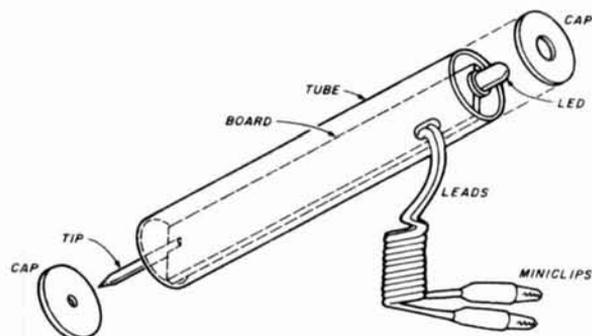


fig. 18. The logic probe. Any plastic tubing about 1/2 inch (13 mm) ID will suffice for the probe container.

summary

I've enjoyed building and using the logic probe and certainly found LED devices to be interesting and a very useful addition to equipment designs. As stated earlier, they are no more complex than any other diode and can be a lot more fun to use. The digital revolution is rapidly gaining acceptance in the world of Amateur Radio, and the logic probe and associated LED theory will help you to accept and enjoy the benefits we will all gain from this new technology.

bibliography

- Jacobson, Loren, WA8ELA, "LED Tuning Indicator for RTTY," *ham radio*, March, 1980, pages 50-53.
 Powell, K.E., WB6AFT, "Novel LED Circuits," *ham radio*, April, 1977, pages 60-63.


ham radio



Vacationitis? Hand-Held Transceivers Are Prescribed For Holiday Hamming

KITTY INVITES YOU to come in and see **BARRY'S** complete line of hand-held transceivers.

YAESU

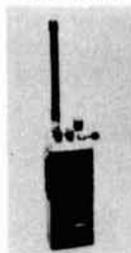

FT-207R

ICOM



IC-2A

TEMPO




S-1, 2, 5

NICE FOR TRAVELLING . . .



FT-707

OR AT HOME . . .

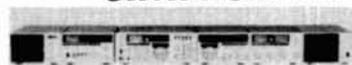

FT-107

Our lines include:

- | | | |
|----------------|------------|-----------------|
| AEA | DRAKE | MURCH |
| ALLIANCE | ETO | ROBOT |
| ANTENNA | EIMAC | ROHN |
| SPECIALISTS | E-Z WAY | SHURE |
| ASTRON | HUSTLER | STANDARD |
| B & W | HY-GAIN | SWAN |
| BIRD | ICOM | TEMPO |
| COLLINS | KDK | TRI-EX |
| COMMUNICATIONS | KLM | YAESU |
| SPECIALISTS | KANTRONICS | VHF ENGINEERING |
| CUSHCRAFT | MFJ | AND MORE... |
| DSI | MIRAGE | |
| DENTRON | MOSLEY | |

BUSINESSMEN: Ask about BARRY'S line of business-band equipment. We've got it!

Amateur Radio License Classes:

Wednesday & Thursday: 7-9 pm

Saturday 10 am-Noon

The Export Experts Invite Overseas orders

¡ AQUI SE
HABLA
ESPAÑOL !

— We Ship Worldwide

BARRY ELECTRONICS

512 BROADWAY, NEW YORK, N.Y. 10012

TELEPHONE (212) 925-7000

measuring signal-strength

Receiver S-meter readings
are no guarantee
of true signal strength —
here's how
to quantify
this controversial subject

Amateur radio transmitters require many measurements, most of which are obtainable from one or more internal or external meters. Some meters have two or more scales, which are selected by switches. Readings may include grid current, plate current, high voltage, relative power, SWR, forward power, reflected power, and ALC level. Other readings may be taken with rf ammeters, rf voltmeters, frequency meters, and impedance bridges. Also, field-strength indicators may be used to adjust the dimensions of fixed or mobile antennas. These indicators are basically short-range portable receivers with loop or whip antennas and meters with arbitrary uniform scales. They are often called field-strength meters despite their inability to receive and measure distant radio signals.

Amateur radio receivers, unlike transmitters, have only one meter and no meter switch. Transceivers also have only one meter, but a switch provides two

or more transmitter readings and a receiver S-meter reading. An S-meter gives relative values of signal strength on a uniform 0 to 9 scale, followed by a dB scale. It reflects the last i-f stage level of all signals by responding to the average agc voltage, and is not related to af gain. Readings are based on maximum rf gain and peaked tuning of an antenna or preselector circuit.

S-meter problems

In general, S-meter readings depend on three variables: signal field intensity, antenna characteristics, and receiver gain. Unfortunately, readings bear no fixed relationship to antenna voltage, as receiver gain varies with various makes, models, units, frequency bands, and parts of bands. Also, there is no accepted standard of input voltage for S9 readings, so various manufacturers have chosen signal-generator outputs of 25, 50, or 100 microvolts for calibration at a specified frequency. Hammarlund *Superpro* receivers for military use were made to read S9 with 50 microvolts input at 3.5 MHz, and modern receivers are not very different.

A typical receiver has a one-milliamper meter in a bridge network containing a potentiometer, which balances no-signal plate or cathode current during zero adjustment. *Superpro* receivers had a 200-microampere meter with an adjustable 1000-ohm shunt for sensitivity adjustment, and also had an AVC amplifier preceding the AVC rectifier. Modern receivers usually avoid these features. Zero and sensitivity adjustments often vary with time.

Although S-meter scales are uniform, S-units are

By Carleton F. Maylott, W2YE, 279 Cadman Drive, Williamsville, New York 14221.

not. One manufacturer states that a change of one S-number on the meter indicates a change in signal strength of approximately two to one (6 dB). Another manufacturer states that each S-unit indicates a 3-dB increase in signal strength. Both statements are thus questionable. An instruction book for a Collins receiver defined neither S9 input nor S-meter steps, but a calibration showed 50 microvolts and steps of about 1.4, or 2 to 1 in voltage ratio, or 3-6 dB, on the 80-meter band.

Since S-meter readings can be either optimistic or pessimistic, and give only qualitative information at best, it follows that quantitative readings would be more desirable. Field intensity, often called field strength, is the only true measure of signal strength. Broadcast-station operators often use field-intensity measuring equipment because they must submit field intensity data to the Federal Communications Commission. This data shows the extent of service areas and interference areas for other stations using the same frequencies.

field-intensity meters

Despite the vagaries of S-meters, Amateurs have avoided using field-intensity meters because of their cost and complexity, and also because Amateurs have no service area and interference area limits. Unlike broadcasters, Amateurs can enhance their service areas by changing frequency, power, and time of operation. Likewise, Amateurs can avoid interference by changing the same variables.

A field-intensity meter is basically a combination of a local oscillator or signal generator of known output, an attenuator, a portable receiver containing an output meter, and a loop or whip antenna of known effective height or length. Another antenna can be used if it is calibrated by comparison with the loop antenna. It follows that, with certain additional equipment, an ordinary receiver can serve as the major component of a field-intensity measuring set.¹

High accuracy is unnecessary in field-intensity measurements of distant radio stations. Propagation conditions, such as fading, vary considerably with time. A receiving station may intercept ground waves, sky waves, or a variable combination of both, which results in multipath interference. Sky-wave fields can be measured with a horizontal antenna, regardless of whether horizontal or vertical polarization is used at the transmitter, since practically equal amounts of both types of polarization are present in the incident ionospheric field.

Radio waves are travelling electric and magnetic fields that are perpendicular to each other and to the direction of propagation. Both fields convey equal power at a distance from their source, so either field

may be considered as a measure of total radiation. It is customary to measure the electric field component, which may be horizontally or vertically polarized, according to the direction of that field. Measurements of field intensity are usually expressed in units of rms microvolts or millivolts per meter at some point, which are really potential gradients.

When a radio wave strikes an antenna, it induces a voltage equal to the product of the field intensity and the effective height or length of the antenna. Thus, if the antenna voltage and effective height or length are known, the field intensity is given by the quotient of their values. Algebraically, since

$$V = EH \text{ or } EL, E = V/H \text{ or } V/L \quad (1)$$

Therefore, the measurement of field intensity depends primarily on the measurement of a small, variable antenna voltage. This is usually done by substituting a measurable and attenuated local signal in place of the real signal and noting the attenuation for equal output from a receiver. Another, less used, method compares the voltage induced into the antenna by the desired signal field with that from a standard local field. In general, an incoming signal is measured by comparing it with a known calibration signal.²

Any kind of signal can be measured with the aid of a receiver. An S-meter will serve as a comparison output meter, as it responds to a-m or fm carrier levels of single-tone SSB modulation and shows about one-half maximum output for CW signals. Audio gain and output are of interest during tune up and zero beating the real and artificial signals for frequency match, but are otherwise irrelevant.

If the real and artificial signals are equal and the antenna characteristics are known, it should be easy to determine field intensity. In principle, a calibrated signal generator is a substitute for the antenna and its output is adjusted to give the same output-meter reading as the real signal. But it is hard to design an attenuator that is accurate at high radio frequencies. This problem was avoided over fifty years ago by putting an attenuator before the i-f amplifier in a special set, which included a local oscillator and calibrating means. The theory and operation of such a set was covered in an IRE paper and will not be discussed.³

effective height

The effective height of the receiving antenna must be known to complete a field-intensity measurement. A loop antenna is a standard of comparison because its effective height can be calculated. The relation is as follows.⁴

$$H = 2\pi AN/\lambda = 2.0944 \times 10^{-5} fAN \text{ meters} \quad (2)$$

SUMMER FEATURES



11CO5 1 GHz, pre. Special \$59.95
ATF 417 pre-amp. net Special \$19.95
MRF 901 UHF transistor, 1 GHz Special \$3.95

COMPLETE KITS: CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM. **COMPLETE KIT \$129**

HAL-300A 7-DIGIT COUNTER (SIMILAR TO 600A) WITH FREQUENCY RANGE OF 0-300 MHz. **COMPLETE KIT \$109**

HAL-50A 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT. ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HAL-TRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM. **COMPLETE KIT \$109**

FREE: HAL-79 CLOCK KIT PLUS AN INLINE RF PROBE WITH PURCHASE OF ANY FREQUENCY COUNTER.

PRE-SCALER KITS

HAL 300 PRE (Pre-drilled G-10 board and all components) **\$14.95**
HAL 300 A/PRE (Same as above but with preamp) **\$24.95**
HAL 600 PRE (Pre-drilled G-10 board and all components) **\$29.95**
HAL 600 A/PRE (Same as above but with preamp) **\$39.95**

HAL-1 GHz PRESCALER, VHF & UHF INPUT & OUTPUT, DIVIDES BY 1000. OPERATES ON A SINGLE 5 VOLT SUPPLY. **PREBUILT & TESTED \$79.95**

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES. HAS 12 LINES OUT. ONLY **\$39.95**

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT UTILIZING THE NEW ICM 7206 CHIP. PROVIDES BOTH VISUAL AND AUDIO INDICATIONS! COMES WITH ITS OWN TWO-TONE ANODIZED ALUMINUM CABINET. MEASURES ONLY 2-3/4" x 3-3/4". COMPLETE WITH TOUCH-TONE PAD, BOARD, CRYSTAL, CHIP AND ALL NECESSARY COMPONENTS TO FINISH THE KIT. **PRICED AT \$29.95**

FOR THOSE WHO WISH TO MOUNT THE ENCODER IN A HAND-HELD UNIT, THE PC BOARD MEASURES ONLY 9/16" x 1-3/4". THIS PARTIAL KIT WITH PC BOARD, CRYSTAL, CHIP AND COMPONENTS. **PRICED AT \$14.95**

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK. **\$16.95**

ACCUKEYER — MEMORY OPTION KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY. **\$16.95**

PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (-3dB POINTS), 19 dB GAIN. **FULLY ASSEMBLED AND TESTED \$8.95**

CLOCK KIT — HAL 79 FOUR-DIGIT SPECIAL — \$7.95. OPERATES ON 12-VOLT AC (NOT SUPPLIED). PROVISIONS FOR DC AND ALARM OPERATION

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND COMM. CATH. READOUTS, 13 TRANS., 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA. **PRICED AT \$12.95**

CLOCK CASE AVAILABLE AND WILL FIT ANY ONE OF THE ABOVE CLOCKS. REGULAR PRICE \$6.50 BUT ONLY **\$4.50 WHEN BOUGHT WITH CLOCK.**

SIX-DIGIT ALARM CLOCK KIT FOR HOME, CAMPER, RV, OR FIELD-DAY USE. OPERATES ON 12-VOLT AC OR DC, AND HAS ITS OWN 60-Hz TIME BASE ON THE BOARD. COMPLETE WITH ALL ELECTRONIC COMPONENTS AND TWO-PIECE, PRE-DRILLED PC BOARDS. BOARD SIZE 4" x 3". COMPLETE WITH SPEAKER AND SWITCHES. IF OPERATED ON DC, THERE IS NOTHING MORE TO BUY. **PRICED AT \$16.95**

*TWELVE-VOLT AC LINE CORD FOR THOSE WHO WISH TO OPERATE THE CLOCK FROM 110-VOLT AC. **\$2.50**

SHIPPING INFORMATION — ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$15.00 PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.

NOW AN ALUMA TOWER DISTRIBUTOR



"HAL"
 HAROLD C. NOWLAND
 WBZ XH

HAL-TRONIX

P. O. BOX 1101
 SOUTHGATE, MICH. 48195
 PHONE (313) 285-1782



where A is the loop antenna area in square meters
 N is the number of turns of that area
 λ is the wavelength in meters
 f is the frequency in kHz

The effective height of a grounded quarter-wave vertical antenna is not the true height, H , but $2H/\pi$ or $0.6366 H$. It is the height of an imaginary conductor, which carries a uniform current equal to that at the base of a real conductor and radiates the same field along the horizontal. The effective height of a much shorter vertical antenna is about one-half of the true height.⁵

The true length of a horizontal half-wave dipole antenna is $143/f$ meters, where f is in MHz. This is 95 per cent of a half wave in space, but the effective length is only 62 per cent of that value, or 65.26 per cent of the true length, or $94.3/f$ meters. If a horizontal dipole is used to measure field intensity, the horizontal component of the field is quite independent of ground characteristics, which differ with location.

The effective lengths of horizontal dipole antennas designed for the 20, 40, and 80 meter phone bands are about 6, 12 and 24 meters respectively. Thus, 50-microvolt S9 signals would produce field intensity readings of approximately 8, 4, and 2 microvolts per meter. Other calibrations and S-readings could be used, with the assumption that S-units are 6 dB apart or 2 to 1 in voltage ratio. This shows that, with the aid of a calibrated signal generator, an ordinary receiver can serve as a substitute for a field intensity meter if accuracy is unimportant.

Broadcast stations use commercial field-intensity measuring equipment and take readings at various distances in various directions, called radials. Field intensity is plotted against distance along each radial on log-log coordinate paper and a smooth curve shows the distance to any value of interest. Distances so obtained from all radials are plotted on polar coordinate paper or map to show the contours of various field intensities, hence service areas. Field intensities of two interfering stations may be plotted against distance in opposite directions on ordinary graph paper to show regions between them where interference may occur.

references

1. Edward M. Noll, *First Class Radiotelephone License Handbook*, third edition, page 270, Sams and Bobbs-Merrill, New York, 1970.
2. *Standards on Radio Wave Propagation — Measuring Methods*, Institute of Radio Engineers, New York, 1942.
3. H.T. Friis and E. Bruce, "A Radio Field-strength Measuring System for Frequencies up to Forty Megacycles," *Proceedings of IRE*, Vol. XIV, August, 1926, page 507.
4. Henry Jasik, editor, *Antenna Engineering Handbook*, McGraw-Hill, New York, 1961, pages 6-1 and 6-2.
5. F.E. Terman, *Radio Engineers' Handbook*, McGraw-Hill, New York, 1943, pages 813, 841, and 991.

ham radio

Low Noise GaAs FET – D432

0.5 dB NF / 18 dB GAIN

AT

432 MHz.

This GaAs FET won the West Coast V.H.F. Convention (May 1980.) It has been used in low noise applications from 144 MHz to 4200 MHz, and offers outstanding performance for the low price of \$25.00 each.



DEXCEL, Inc.

2285C Martin Avenue, Santa Clara, California 95050
Phone: (408) 727-0692

ORDER FORM

Send me _____ pieces of D-432 FET at \$25.00 each

Name _____

Address _____

Telephone _____

Please send me application note #H100 VHF/UHF circuit techniques at \$3.50 each (Free with FET order)

Enclosed is my check or money order for \$ _____

(California residents add \$1.50 sales tax for each FET. Allow 2 weeks delivery.)

tone alert monitor

Design and construction of a tone call system for Radio Amateurs interested in emergency communications

Recently it has been emphasized many times that the need for Amateur Radio communications in disaster situations is very real and necessary. Many groups of Amateurs and clubs have spent money for equipment and much time in drills and practices to make themselves ready for emergency communications.

One problem that continually bothers Amateur operators who are striving to maintain their proficiency is the need to monitor one or more radio communications links. Such monitoring is necessary so that a central agent can quickly "call up" operators who can provide communications for disaster services. Many Amateur operators would be more willing to monitor for the call up if it were not for the task of listening to a party line such as a 2-meter repeater, national calling frequency on 2 meters, or other busy radio frequencies.

alert monitor

This problem of requiring an individual to monitor for an alert, either real or during practice, has inspired the design of an Alert Monitor that will alert each station without the operator having to listen to the party line chatter associated with most frequencies. The Alert Monitor is also handy for those using a receiver in a busy household or in an automobile, where a busy repeater sometimes can be annoying. The monitor can be used with almost any receiver capable of passing normal audio-frequency informa-

tion. It is not recommended for SSB transceivers that can't hold tight frequency stability.

This Alert Monitor also can alert groups of stations simultaneously (Group Call), or it can alert one station at a time. The Alert Monitor operates with standard *Touch-Tone** audio. It uses two digits for normal operation and a long, single digit for the Group-Call feature.

circuit description

Fig. 1 shows the schematic. The audio is applied to the Alert Monitor through the audio-input jack and a 2.2k resistor. Audio amplitude is limited by two 1N914 back-to-back connected diodes. A 5k pot adjusts the audio input level, which is coupled to the tone decoder ICs by 4.7- μ F capacitors. U-1/U-2 decode the high and low tones for the first *Touch-Tone* digit, and U-3/U-4 decode the tones for the second digit. The resistor and capacitor at the output of each decoder IC provide a delay between the time that the decoder IC senses a tone and the time that the NOR gate will respond. This prevents falsing on other audio that may be present in the decoder.

When the first digit has been received, a logic high is applied to U7A pin 1 for 2.5 seconds through timer IC U6. A logic high must be applied to U7A pin 2 during this 2.5 second period for the Alert Monitor to operate. Therefore, the second digit must be received within 2.5 seconds of the first for a valid call. This sequence ultimately sets U10B and causes Q1 to conduct. This, in turn, causes relay K1 to transfer the audio to the audio-output jack. In this condition, the audio signal is connected to the speaker, and the receiver can be monitored for the "Alert Call."

For continuous receiver audio monitoring, the monitor switch can be connected to the monitor positions and the communications receiver can then be used normally without the Alert Monitor defeating the receiver audio.

The Group Call feature works by the sending station (encoder) transmitting the second digit of the

*Touch-Tone is a registered trademark of the American Telephone and Telegraph Company.

By H.F. Wetzel, W4KRT, Route 2, Box 167-C,
Berryville, Virginia 22611




Control box of the prototype Alert Monitor.

two digits for 6 seconds or longer. In this mode, U-1/ U-2 don't respond. The signal path now appears in the form of a pulse at U8A pin 6 and will, after 6 seconds, produce a logic high at U10A pin 3. If, in fact, the second tone is still being received, it will cause a logic high to be applied to U10A pin 2. This action will enable the Group Call Detector to produce a logic high, which will emanate from U10A pin 5. This high is applied to U5D pin 12. U5D is a NOR gate; and from this point on, the operation is the same as when two digits were received.

Whenever U10B is set, either by receiving the correct two tones or the Group Call tone for 6 seconds minimum, three reactions take place:

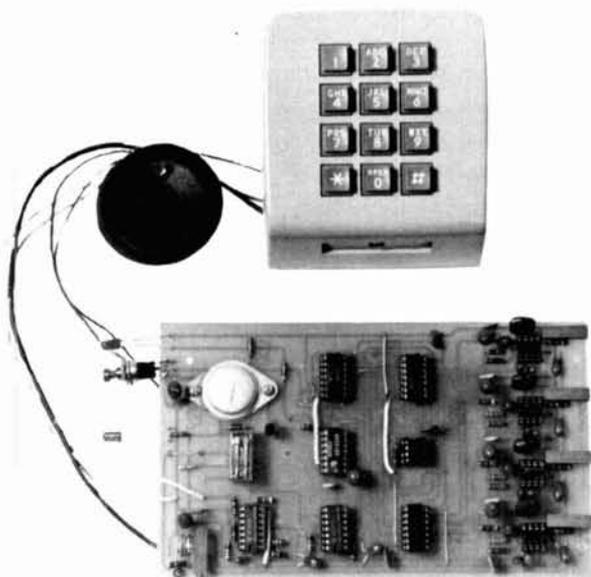1. The audio is applied to an external speaker as described earlier.
2. A call indicator is illuminated. This is an LED mounted on the front panel.




Alert Monitor built on PC board, shown here ready for alignment and testing.

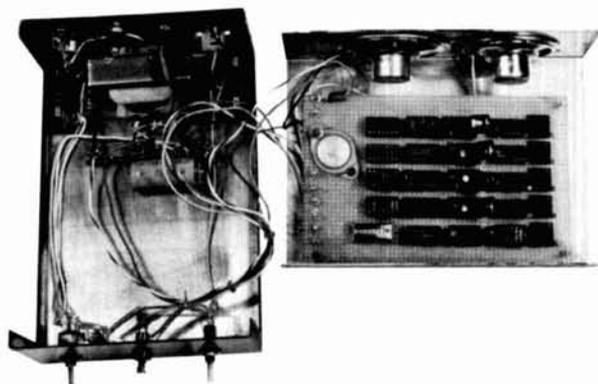3. The Alert Monitor oscillator is triggered for 4 seconds, producing a two-tone "twee-dell" audible signal from the Alert Monitor.

The reason for the visual call indicator is in case a call has been received while the operator is out of hearing range. Upon returning, if the call indicator is illuminated, the operator knows that an alert tone has been received, even though the receiver may be squelched or silent at that particular time.

To put the Alert monitor back into the alert mode, press the RESET push-button to reset U10A and B and to extinguish the call indicator LED. It will also disable the audio path through K1 contacts. This action will again silence the receiver speaker until the next proper alert tone is detected.



Complete prototype Alert Monitor showing perf-board construction, power supply, speakers, and minibox enclosure.

power requirements

Power requirement for this unit is from 8-20 Vdc at approximately 150 mA. This makes the unit adaptable for mobile operation, and the low current drain should not present any problems so far as leaving the receiver and the Alert Monitor on while away from the automobile. The prototype was built to include a dc power supply which also houses the Alert Monitor speaker as well as a speaker for receiver audio. A power supply is shown in fig. 2.

construction

The original Alert Monitor was constructed on a fiberglass perf board using wire-wrap sockets. All discrete components except variable potentiometers, the relay, and the capacitors associated with U12, were mounted on 14-pin header plugs. Fig. 3 shows the wiring of the discrete components to the ICs.

No special construction practices were observed, except that all V_{CC} connections for the ICs were carried back to the power source at U12 pin 2. Each IC

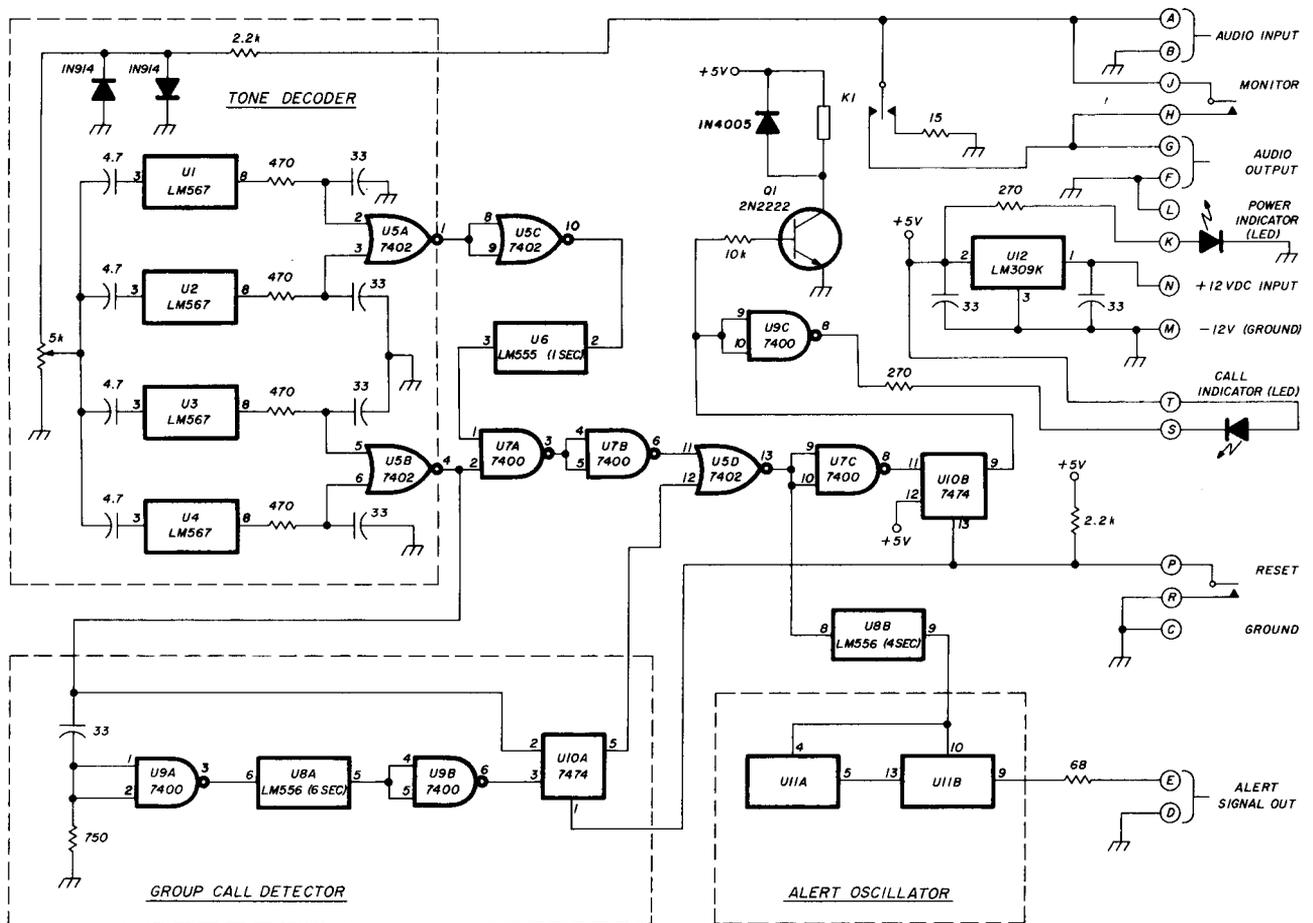


fig. 1. Alert Monitor schematic. Circuit operates with standard *Touch-Tone* audio. Two digits are used for normal operation and a long, single digit for Group Call. Original circuit was constructed on a fiberglass perf board using wire-wrap sockets, but a PC board is now available (see text).

also had its power ground returned to the central ground input point at the case of U12 to reduce transients on "daisy-chained" power leads, which could cause unstable operation.

Bypass capacitors across the plus and minus power connections of the ICs may be added if necessary. No heatsink was provided for the LM309K (U12). At the low-current level required for the unit, it was found to be unnecessary. The 5.0k trim-pots used for frequency adjustment and input-level adjustment are all multi-turn potentiometers. These are necessary, especially for the frequency-adjusting pots, for the vernier action needed to "tune" the LM567s to their correct frequency.

Should you not wish to use the wire-wrap method of construction, a PC board is available.* The board is single-sided and requires very few jumpers. I prefer this method of single-sided PC board because it's


*Order boards from MJW Boards, Route 2, Box 167-C, Berryville, Virginia 22611.

much easier to use or copy. All component parts used for both prototypes (perf board or PC board) were purchased from Jameco Electronics.[†] Of course, parts from other suppliers are acceptable, but this attempt at standardization should help the builder. The only part I did not get from Jameco was the relay. It was purchased from Radio Shack, and the part number for this item is 275-215.

alignment

Several methods for alignment of the tone decoder section are available. The fixed-value resistor connected to pin 5 of each LM567 in series with the 5.0k variable resistor and the 0.1-µF capacitor connected to pin 6 are the frequency-control elements for each single-tone detector (LM567). A good-grade Mylar capacitor should be used in this circuit to prevent frequency drift with temperature or internal leakage. If an oscilloscope is available, it can be connected to

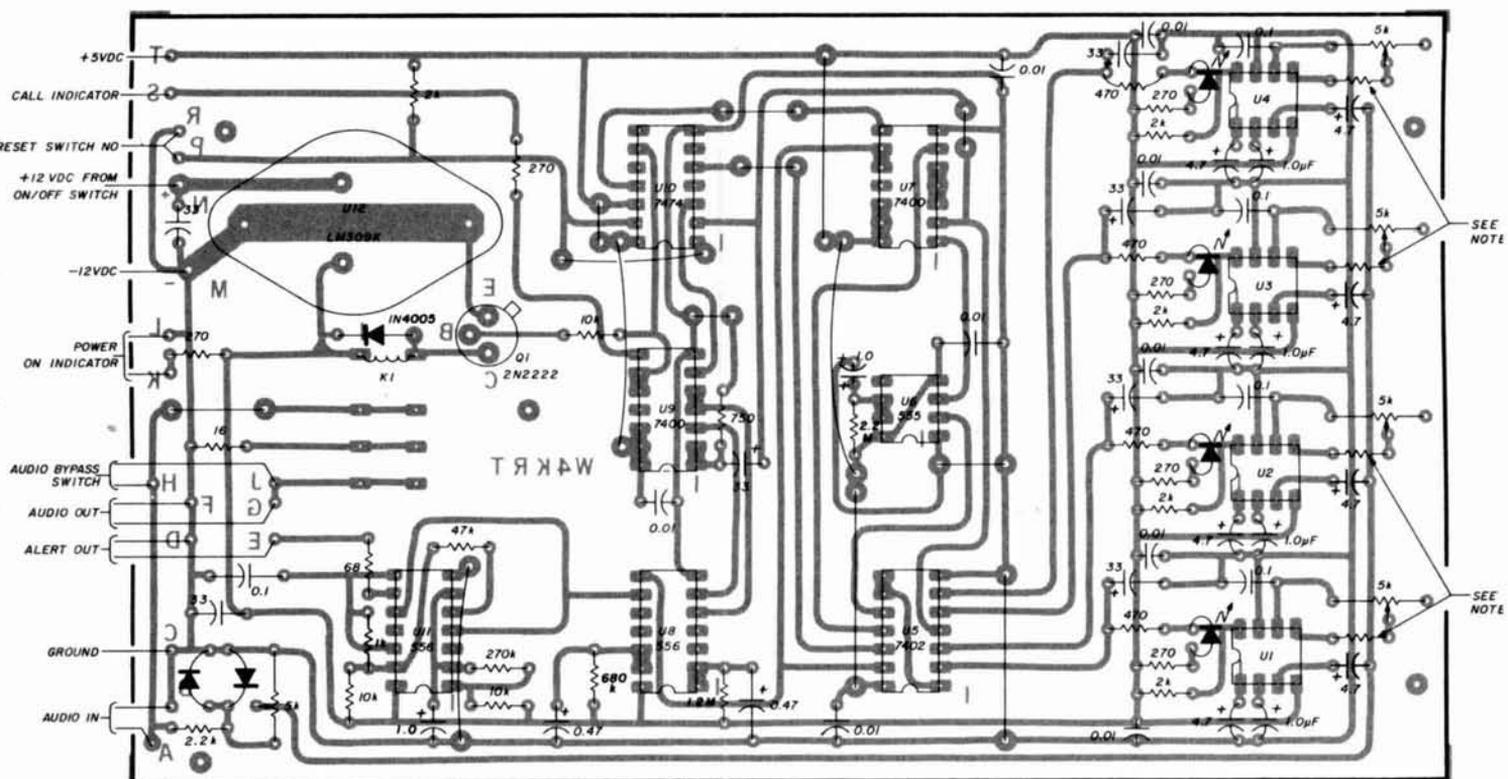[†]Jameco Electronics, 1021 Howard Avenue, San Carlos, California 94070.



NOTE: FREQUENCY DETERMINING RESISTOR—SEE TEXT

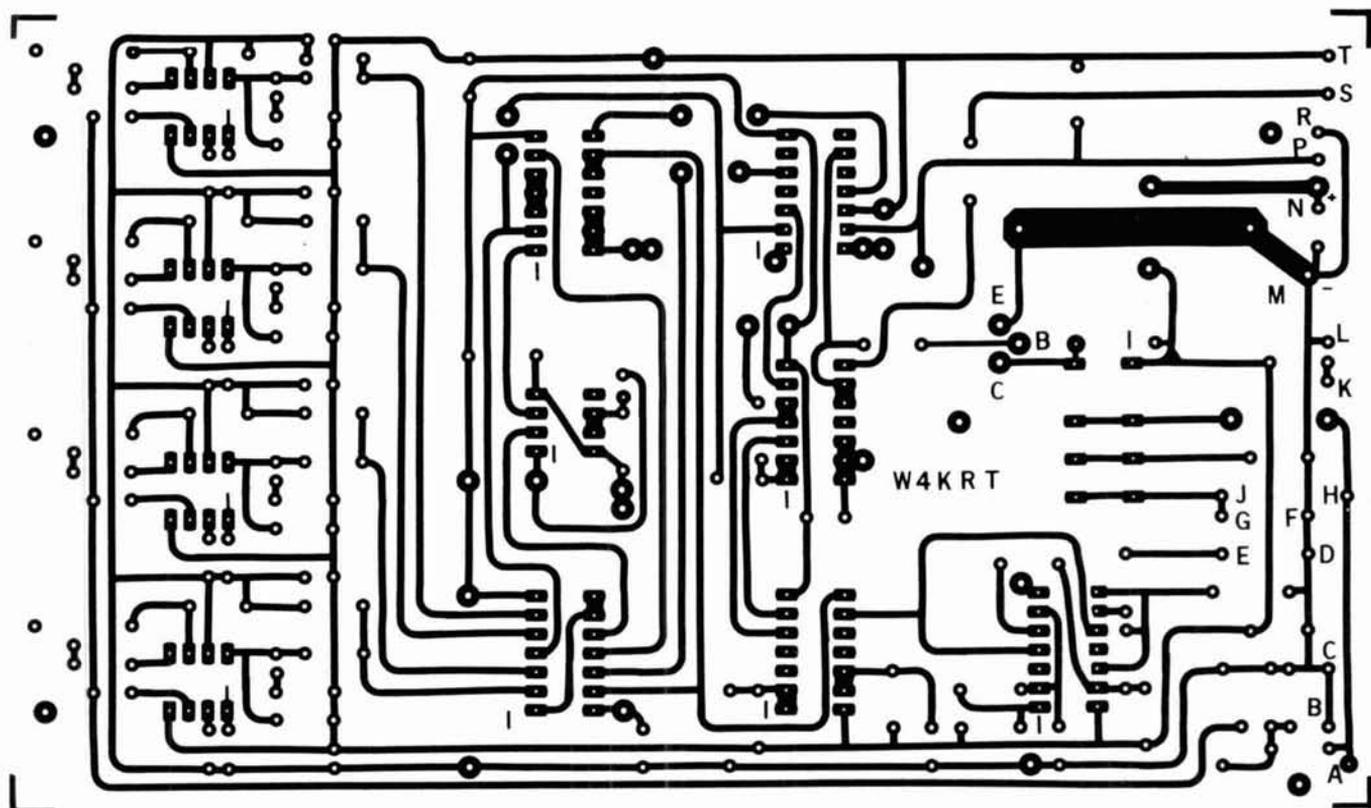


fig. 4. Above, component placement on PC board. Below, Alert Monitor PC board, foil side.

table 1. Relationship between frequencies produced by the various Touch-Tones.

digit	high tone (kHz)	low tone (kHz)
1	1209	697
2	1336	697
3	1477	697
4	1209	770
5	1336	770
6	1477	770
7	1209	852
8	1336	852
9	1477	852
*	1209	941
0	1336	941
#	1477	941

manufacturer. See table 1 for the frequencies produced by various touch tones.

acknowledgments

I'd like to thank all of my Amateur friends who gave suggestions and encouragement for this project. In particular, I'd like to thank KA4GCF, Bob, for his help with the manuscript; WB4HID, Harry, for his help with construction tips; Don Bungard for his help with the PC board; and KA4HOP, Janie, my XYL, for her many hours of assistance in testing the Alert Monitor and for her typing work.

bibliography

Berlin, Howard M., "Homebrew Touch-Tone Encoder," *ham radio*, August, 1977, pages 41-43.

Connors, John F., "Three-Digit Touch-Tone Decoder for Selective Calling," *ham radio*, December, 1974, pages 37-41.

De Laune, Jon, W7FBB, "Digital Touch-Tone Encoder for VHF FM," *ham radio*, April, 1975, page 28.

Hejhall, Roy C., K7QWR, "Solid-State Mobile Touch-Tone Circuit," *ham radio*, March, 1973, pages 50-53.

Heptig, Robert, K0PHF, "Multifunction Touch-Tone Decoder," *ham radio*, October, 1973, pages 14-17.

Hood, Joseph M., "Converting Slim-Line Touch-Tone Handset," *ham radio*, June 1975, pages 23-25.

McDavid, Larry, W6FUB, "Universal Tone Encoder for VHF FM," *ham radio*, July, 1975, pages 16-21.

Lowenstein, Al, K7YAM, "Handheld Touch-Tone," *ham radio*, September, 1975, pages 44-46.

Shreve, Pat, W8GRG, "Subaudible Tone Encoders and Decoders," *ham radio*, July, 1978, pages 26-33.

Stahley, David M., "Tone Encoder and Secondary Frequency Oscillator," *ham radio, the ham notebook*, June, 1969, pages 66-67.

Digital Linear MOS Data Book, Signetics, Menlo Park, California 94025

ham radio



The newest rig in Kenwood colors. Providing 15 memories, offset recall, scan, touch-tone®, 25 watts output and a priority feature. The touch-tone® pad is built-in for easy frequency selection or autopatch use, and the memories not only recall frequency, but the offset as well! Available soon. Call for quote.



For both mobile or base operations (with an external supply), here's the answer to your VHF dreams. Dual VFO's, RIT, five memories and scan, FM, SSB, and CW, plus 100Hz resolution on the dial, make operating the TR-9000 both simple and exciting. OSCAR anyone? The retail price of \$499.00 is great enough, but call for quote!



Not the first, but the best. Quality, with 1.5 watts output, full digital synthesis with visible LCD frequency display. The reputation that this rig is gaining is testimony enough to say here's the HT you've been dreaming about. \$395.00 retail price, but call for quote!

MADISON


Electronics Supply, Inc.

1508 McKinney • Houston, Texas 77002 • (713) 658-0268

integrated circuit function generator

A function generator
based on the
Exar XR-2206
which features
multiple waveforms
over the range
10 to 100 kHz

If you are a builder, experimenter, or just like to maintain your own equipment, I am sure you appreciate the value of a good signal source. Ideally, the perfect signal source should be able to provide whatever frequency, amplitude, waveform, and impedance level required for the job at hand. But, unfortunately, like most things in life, we must compromise a little. The classical signal source was either an audio generator or an rf generator. At best, it produced a sine wave and, in the case of the audio generator, perhaps a squarewave. In recent years, a third entry has appeared on the scene. It is called a function generator and is distinguished primarily by its ability to produce a variety of waveforms (functions) through the audio and sometimes low rf frequency ranges. Its repertoire usually includes the sine, square, triangle, and perhaps saw-tooth or pulse output waveforms. The spectral purity of a particular waveform is usually not quite as good as that from a comparably priced generator that is designed to produce only one waveform, but is usually more than adequate for general purpose use.

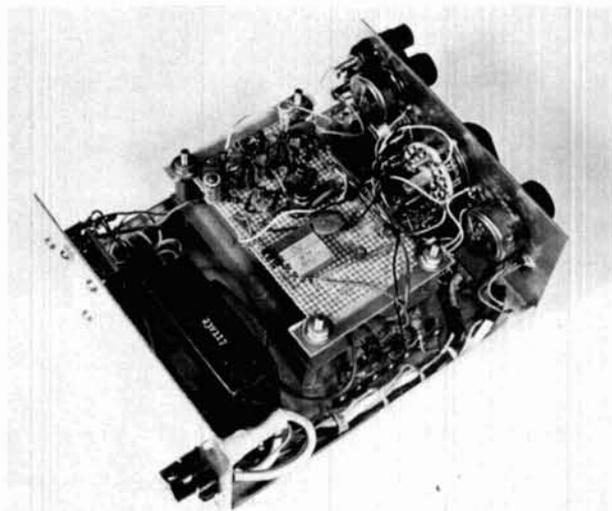

Internal view of the function generator showing perf-board.

Until recently, high cost has relegated the function generator to the laboratory, but now several new integrated circuits have made it possible for the Amateur to construct his own for a very modest investment. The function generator described in this article uses the XR-2206 integrated circuit manufactured by Exar. This IC can supply a sine wave, triangular wave, square wave, and a 50 per cent duty cycle positive pulse and has the options of a-m and FSK modulation. The frequency can be varied from about 1 Hz to above 100 kHz and the output waveform, although not lab quality, is suitable for most Amateur applications. The manufacturer states that the sinusoidal distortion is less than three per cent over the

By Frank C. Getz, N3FG, 685 Farnum Road,
Media, Pennsylvania 19063

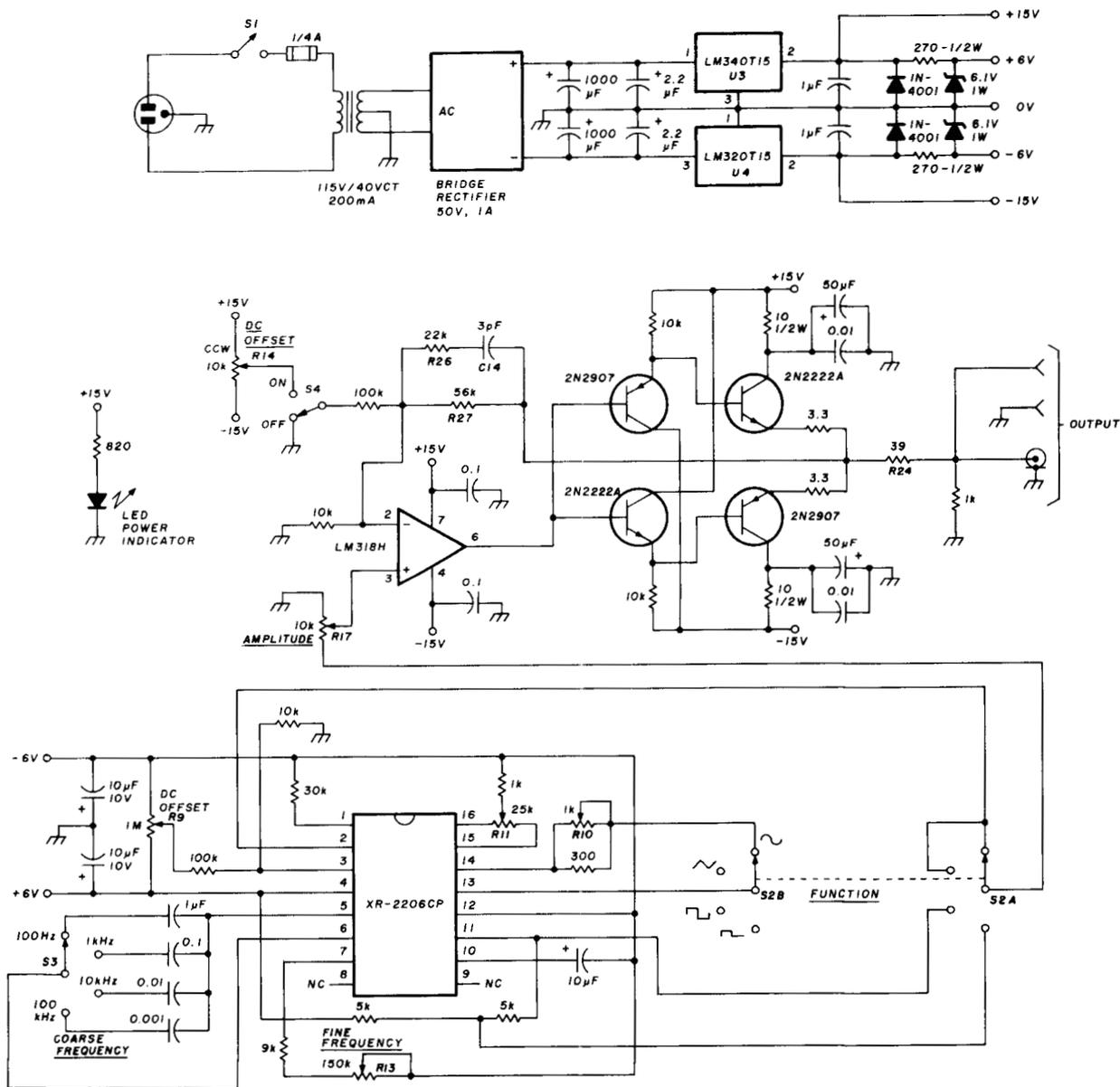


fig. 1. Complete schematic diagram of the function generator based on the Exar XR-2206 integrated circuit.

entire frequency range; this isn't bad considering the versatility and circuit simplicity.

I added a suitable power supply and power amplifier to the basic XR-2206 and came up with a very handy addition to my home workshop. The power amplifier increases the amplitude range, lowers the output impedance, and provides a means of introducing an adjustable dc offset level to the basic waveforms.

circuit description

The oscillator circuit is lifted almost entirely from Exar's application data on the XR-2206. I elected not to incorporate the a-m and FSK inputs, although they

would be simple to include. R13 controls the frequency and is panel mounted. R9, R10, and R11 are all trimpots mounted on the circuit board. R10 adjusts sine wave distortion. R11 controls sine wave symmetry, and R9 is adjusted to eliminate any residual dc component in the sine and triangular waveforms. With the components shown in the schematic (see fig. 1), the frequency can be varied from about 10 Hz at the low end to slightly over 100 kHz at the high end in four overlapping ranges, each with a 100-to-1 ratio. S3 selects the frequency range and S2 selects the waveform. R17 is the amplitude control; it is panel mounted and controls the signal level fed to the LM318 operational amplifier which in turn drives

the power amplifier stage. R26, R27, and C14 provide negative feedback around the entire amplifier section, as well as frequency compensation. R14 and S4 provide an adjustable dc component for the output waveform. R24 brings the output impedance up to the vicinity of 50 ohms. The power supply uses two three-terminal regulators and although the positive and negative voltages do not track, it has proven quite satisfactory.

construction

I built my generator in a small aluminum box with most of the circuit, with the exception of some of the larger power supply components, mounted on perf-board. U3 and U4 use the cabinet as a heatsink and the two output transistors are equipped with small push-on heatsinks.

adjustment

Initial adjustment consists of setting R9, R10, and R11 to their optimum settings. Switch S4 to the off position and select the sine wave. Be sure that the amplitude control (R17) is set so that the output waveform is not clipped when viewed on an oscilloscope. Alternately, adjust R10 and R11 for the least sine wave distortion and best symmetry. Adjust R9 to eliminate any dc component and repeat the process until no further improvement can be seen. A distortion analyzer would be helpful for these steps if one is available, but the "eyeball" technique gives fairly good results. Make these adjustments at a frequency of about 10 kHz.

operation

Operation is fairly straightforward with the exception that the square wave will have a slight dc component with S4 in the off position. This is easily eliminated by switching on S4 and adjusting R14 to eliminate the offset. The waveforms deteriorate slightly around 100 kHz, but are still useful.

For the modest investment in time and material, this little generator has proven to be a very handy addition to my shop. I'm sure that some readers may have suggestions for improvements and modifications, and I would be most interested in hearing from them.

I would like to thank Mr. Ralph Flagel for his help with the photographs.

references

1. XR-2206 Data Sheet, Exar Integrated Systems, Inc., 750 Palomar Avenue, Sunnyvale, California 94086.
2. William Orr, W6SA1, *Radio Handbook*, 20th edition, page 31.35, Editors and Engineers, Indianapolis, 1975.

ham radio

STOP RF SPILLOVER!

You may be losing up to half the available output from your vertical gain antenna because of RF spillover. The amazing AEA Isopole with unique decoupling design, virtually eliminates RF spillover and can help you multiply your power in all directions on the horizon relative to an ideal half-wave dipole, or end-fed non-decoupled "gain" antennas.

Get the Facts.

We'll send you a design for an RF spillover tester and a copy of our booklet: *Facts about Proper VHF Vertical Antenna Design* simply for contacting Advanced Electronic Applications, Inc., P.O. Box 2160, Lynnwood, WA 98036. Call 206/775-7373.

AEA Brings you the Breakthrough!



Gift a ham.

Anytime is a great time to give HORIZONS!

Share the fun and excitement of Ham Radio HORIZONS with a special friend — that would-be ham, beginner or old-timer. HORIZONS is definitely a thoughtful, inexpensive, and unique gift . . . actually it's 12 gifts all year long. Just for the fun of it, **GIFT A HAM today!** 1 year (12 issues), \$12.00



ORDER TOLL FREE 800-258-5353
or send gift instructions and payment to:

Ham Radio HORIZONS
Greenville, NH 03048

Even WEAK SIGNALS print clearly with a HAL Demodulator.

ST-6000 Demodulator \$659.00



ST-5000 Demodulator \$239.00



Pulling in weak or distorted signals with a HAL Demodulator is no problem. Even if the band is crowded.

With high-gain, wide-bandwidth limiters and extremely linear active detector circuits, both the ST-6000 and ST-5000 Demodulators convert RTTY tones into strong, readable signals that display bright and clear.

Tones necessary for transmitting RTTY are conveniently generated and receive filters and transmit tones are accurately set and matched to assure on-the-money transceive operation.

Both the ST-6000 & ST-5000 offer these features:

- Internal Loop Supply
- Internal AFSK Generator with CW ID Tone
- Internal Tuning Indicator
- Autostart Motor Control
- Line/Local Loop Control
- TTY Machine Compatibility
- RS-232 type DATA Interface
- "High" or "Low" Tones
- 120/240, 50/60 Hz Power
- Normal/Reverse Switch
- 170 and 850 Shift
- Active Discriminator
- Metal Cabinets for RF Shielding.

Special Features of the ST-6000:

- Mark-Hold
- Antispace
- Automatic Threshold Control (ATC)
- Decision Threshold Hysteresis (DTH)
- Keyboard Operated Switch (KOS)
- MIL-188 and CMOS Data Interface
- Oscilloscope Tuning Indicator
- Crystal Controlled AFSK Tones
- Active Input Bandpass Filter
- Pre-Limiter AGC
- Three Shifts (170 - 425 - 850)

Write or give us a call. We'll be glad to send you our new RTTY catalog.



HAL COMMUNICATIONS CORP.

Box 365
Urbana, Illinois 61801
217-367-7373

For our European customers, contact: Richter & Co. D3000
Hannover 1 • I.E.C. Interelco, 6816 Bissone/Lugano • Radio
Shack Ltd., London NW6 3AY • Erik Torpdahl Telecom, DK 3660
Stenlose Denmark


semiconductor curve tracing simplified

When used with
a good scope,
this versatile circuit
provides a
wealth of information
about any
unknown semiconductor

Most experimenters have accumulated a vast assortment of semiconductors, many unmarked, undecipherable, or otherwise of unknown characteristics. An ohmmeter can provide some information about them, such as which transistors are PNP and which are NPN; it can also distinguish silicon from germanium, and establish diode polarity. But to really gain detailed information requires a curve tracer and scope. A curve tracer will reveal nearly all low-frequency transistor parameters such as current gain, breakdown voltages, and input-output impedances. It will also identify, at a glance, zeners, tunnel diodes, and other specialized semiconductors, and give much valuable information about their operating characteristics.

A laboratory-type curve tracer usually injects a staircase waveform of current into the base of the unknown transistor, then displays a complete family of collector current waveforms on the screen.¹ This is an ideal arrangement, but not exactly simple. The curve tracer described here displays only one curve at a time; to look at an entire family requires the turning of a knob. I consider this a small price to pay for simplicity. It also has the advantage of providing a

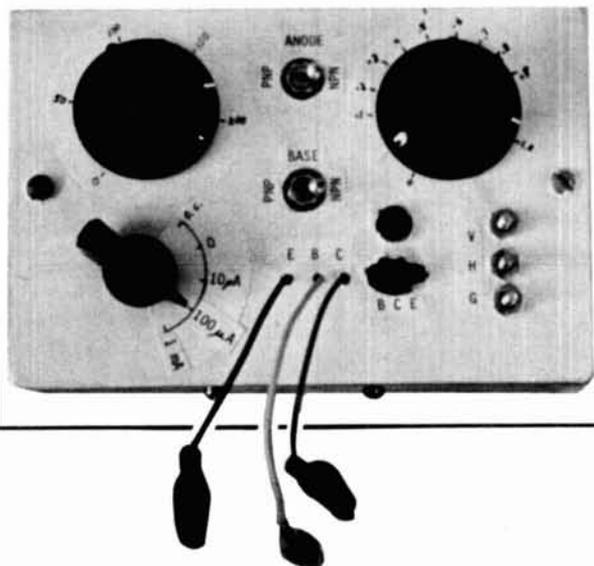The complete curve tracer unit. Upper lefthand knob controls peak collector (or anode) voltage swing. The knob on the right is the base current adjustment potentiometer, R2.



By Fred Brown, W6HPH, 1169 Los Corderos,
Lake San Marcos, California 92069

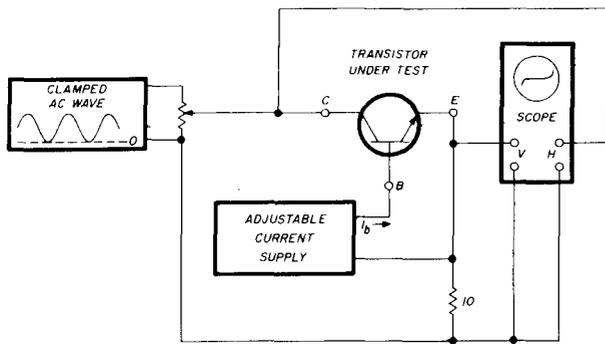


fig. 1. Simplified diagram of the curve tracer.

continuously adjustable base current, which permits the display of *any* collector curve, rather than only discrete values. It's sometimes nice to be able to see "between" those discrete curves.

theory

Fig. 1 is a simplified diagram of the curve tracer. The clamped ac supply swings the collector voltage from zero to a peak value determined by the potentiometer setting. This voltage is also applied to the scope horizontal input. Vertical deflection is provided by sampling current through the 10-ohm resistor in series with the emitter. The result is a trace of collector current vs collector voltage. The small voltage drop across the 10-ohm resistor does not significantly affect collector-to-emitter voltage; the error is only 1/10 volt for 10 mA of collector current. The 10-ohm value permits current readings to 100 microamperes per cm when the vertical gain is turned up to 1 mV per cm.

If greater sensitivity is desired, a 100-ohm resistor could be used, at the expense of a tenfold increase in error. The error in V_{CE} can be avoided by using a scope with completely independent horizontal and vertical inputs or by tolerating a downward deflection for increasing current. But since most scopes have one terminal common to both inputs (ground), and give a positive deflection upwards, the circuit was designed for this type of scope.

The clamped ac voltage for the collector is created by the simple circuit of fig. 2A. This voltage is positive throughout the cycle (fig. 2B) except for the

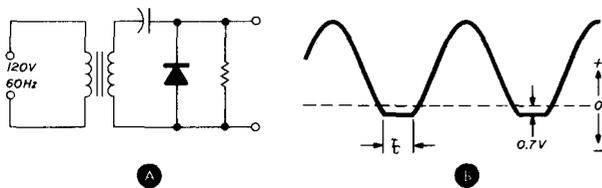


fig. 2. The simple circuit shown at A will produce the clamped ac waveform shown at B.

brief interval, T_c , when the diode is conducting. During this interval, the waveform swings slightly negative by an amount equal to the diode barrier potential, about 0.7 volt.

If the transformer and diode were perfect, the charge time, T_c , for the capacitor would be zero, and the output would be a pure sine wave. But since they are not, the waveform dwells at approximately -0.7 volt for the time it takes to charge the capacitor. In my unit a very small transformer was used, which resulted in a T_c of about 3 milliseconds; with a larger transformer it would be less. The dwell time results in a bright spot at the beginning of the trace — not really a disadvantage since it makes the origin easy to


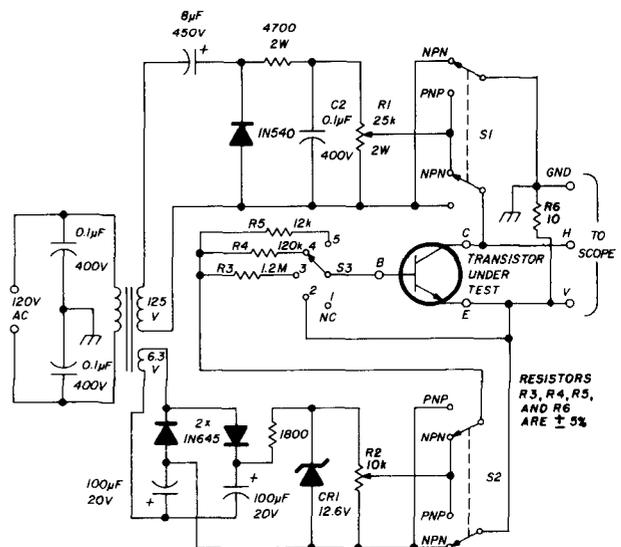


fig. 3. Schematic of the tracer. The power transformer can be a Stancor P8181 or an Allied PS8415.


identify. The spot can be made brighter by omitting C2 in fig. 3.

the circuit


The complete circuit is seen in fig. 3. A small "one-tube" power transformer of the type used on early uhf TV converters, boosters, and other one-tube devices is used for the two power supplies. The "plate" winding is used for the clamped ac supply, and the 6.3 Vac "filament" winding is used for the constant-current base supply. The latter uses a full-wave voltage doubler and is regulated to a constant 12.6 volts by zener diode CR1. A voltage of 12.6 rather than 12.0 volts is used because of the 0.6-volt base-to-emitter voltage drop in a silicon transistor. Since this drop is about 0.2 volt for germanium transistors, base currents will be about 4 per cent higher than indicated when measuring germaniums.

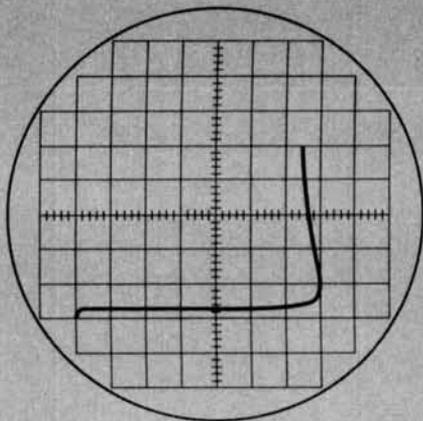

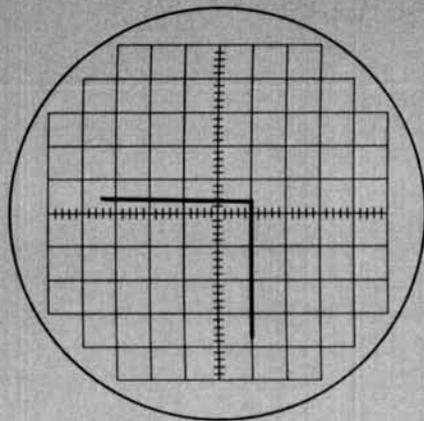
Collector characteristic curve of a 2N498 with base current of $9 \mu\text{A}$. Scales are 20 V/cm horizontally and 1 mA/cm vertically. Notice the negative resistance effect in the avalanche breakdown part of the curve at about 120 collector volts.



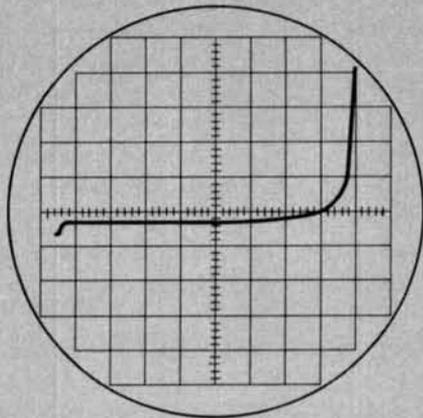Sharp breakdown characteristic of a 1N1527 zener diode at approximately 20 volts. Scales are 5 v/cm horizontally and 1 mA/cm vertically.



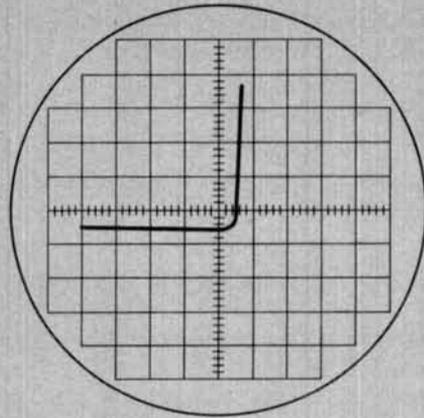Collector characteristic curve of a 2N2369A with $8 \mu\text{A}$ of base current. Scales are 2 V/cm horizontally and 1 mA/cm vertically.



Reverse characteristic of a 1N914 showing avalanche breakdown at -90 volts. Scales are 20 V/cm horizontally and 1 mA/cm vertically.

Switch S3 provides three ranges for the base current adjustment pot, R2. The maximum currents, 10 μA , 100 μA , and 1 mA, are determined by resistors R3, R4, and R5. These resistance values ideally should be close tolerance, 5 per cent or better, to ensure the precise values of maximum base currents indicated on S3. The scale of R2 is calibrated 0-1.0 in divisions of 1/10 to indicate the fraction of base current shown on S3. For instance, if S3 is set to 10 μA , and R2 is at 0.4, base current would be 4 μA .

Switches S1 and S2 are polarity-reversing switches to accommodate either PNP or NPN transistors. You might wonder why these two switches are not combined into one 4-pole switch. The use of two separate switches makes possible the testing of depletion-mode fet's with no further increase in complexi-

ty. For instance, an N-channel fet is tested by placing S1 in the NPN position and S2 in the PNP position. The fet source, gate, and drain are connected to the curve tracer emitter, base, and collector terminals, respectively. The result is a positive drain supply and a negative gate voltage; the latter adjustable by R2. Negative gate voltage can be measured with a VTVM connected between gate and source, or base to ground terminals on the tracer.

For the $I_b = 0$ position of S3, the base is grounded. Switch S3 also provides a fifth position in which the base is left floating, which is handy for checking BV_{CEO} and I_{CEO} .

construction

This unit was built into a 2 x 4 x 6 inch (51 x

102 x 152 mm) chassis without much crowding of components; parts placement isn't critical.

A variety of transistor sockets can be wired in parallel to accommodate the various transistor basing arrangements in common use. It's also recommended that alligator clips on short leads be included for those diodes and transistors that will not fit into conventional sockets. These three leads should preferably be of different colors and clearly labeled E, B, and C.

Wirewound pots are recommended for R1 and R2. Both these controls have hand-drawn scales. The scale of R1 indicates collector (or anode) voltage in peak volts; the range is zero to roughly 200 volts peak.

operation

For best results the tracer should be used with a laboratory-type scope that has accurately calibrated vertical and horizontal deflection. I use a Hewlett-Packard 130B, which works beautifully in this application.

Nearly all work is done with vertical gain set at 10 mV per cm; the scope then reads 1 mA per cm vertically. Horizontal sensitivity, however, ranges all the way from 0.1 volt per cm to at times as much as 50 volts per cm.

Since the curve tracer operates at 60 Hz, it will tell you nothing about the frequency limitations of your transistors. To determine high frequency performance, an rf transistor tester is recommended.²

The current-limiting resistors in series with the base make transistor damage unlikely. However, damage is possible if R1 is run too high. When testing an unknown device, it's wise to start with R1 set near minimum and keep an eye on the scope screen as the control is gradually advanced.

At times you'll notice that part of the characteristic curve drifts upwards. This is usually due to heating of the device under test. It doesn't normally occur unless the amount of heat generated is a significant fraction of the maximum device dissipation. It's particularly apparent with germanium transistors because of their considerable temperature sensitivity.

You'll also notice the characteristic curve occasionally takes the form of a very elongated loop rather than a single trace. This is because of what is called "temperature hysteresis" and is caused by cyclical heating of the transistor junction during collector voltage peaks.³

references

1. D. Wright, "Transistor Curve Tracer," *ham radio*, July, 1973, page 52. Also *short circuits*, *ham radio*, April, 1974, page 63.
2. F. Brown, "An rf Transistor Tester," *CQ*, April, 1975, page 35.
3. John Mulvey, *Semiconductor Device Measurements*, Tektronix, Inc.

ham radio

State
of the art



by

K.V.G.

CRYSTAL FILTERS and DISCRIMINATORS

9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$50.60
XF9-B	2.4 kHz	SSB RX/TX	\$68.60
XF9-C	3.75 kHz	AM	\$73.70
XF9-D	5.0 kHz	AM	\$73.70
XF9-E	12.0 kHz	NBFM	\$73.70
XF9-M	0.5 kHz	CW (4 pole)	\$51.55
XF9-NB	0.5 kHz	CW (8 pole)	\$91.35

Export

Inquiries

Invited

9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$5.95
XF901	8998.5 kHz	USB	\$5.95
XF902	9001.5 kHz	LSB	\$5.95
XF903	8999.0 kHz	BFO	\$5.95
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

Shipping

\$1.75

per filter

VARACTOR TRIPLERS

The low cost, easy way to operate on the 432 MHz and 1296 MHz bands. For OSCAR 7, mode B, drive the MMv432 family varactor tripler with your 2 meter transmitter. The wide-band varactor triplers cover the full 2M/432 band without retuning. NO power supply required for varactor triplers; efficiency approximately 50%. Three models available at 432, two at 1296.

Model	Max Drive	
MMv432	30 W	\$85.30
MMv432M	50 W	\$89.95
MMv432H	70 W	\$136.95
MMv1296	20 W	\$104.95
MMv1296H	35 W	\$136.45
MMv1265 ATV		\$104.95
MMv1265H ATV		\$136.45



RECEIVE CONVERTERS



MODELS FOR ALL BANDS 50 MHz THRU 1296 MHz. LOW NOISE OPTIONS AT 432 MHz.

STANDARD I.F. 10M.
POWER 12V D.C.

I.F. OPTIONS 6M & 2M AVAILABLE.
Shipping \$2.50

MMc144	N. F. 2.8 dB typ.	\$54.95
MMc432	N. F. 3.8 dB typ.	\$69.95
MMc 439/ATV	Ch2 or Ch3 IF	\$69.95
MMc1296	N. F. 8.5 dB typ.	\$89.95
MMc 1280/ATV		\$99.95

ANTENNAS (FOB CONCORD, VIA UPS)

144-148 MHz J-SLOTS

8 OVER 8 HORIZONTAL POL.	+ 12.3 dBd	D8/2M	\$55.95
8 BY 8 VERTICAL POL.		D8/2M-VERT.	\$65.60
8 + 8 TWIST		8XY/2M	\$57.75



420-450 MHz
MULTIBEAMS

For local, DX, OSCAR,
and ATV use.

48 EL.	GAIN + 15.7 dBd 70/MBM48	\$69.95
88 EL.	GAIN + 18.5 dBd 70/MBM88	\$99.95

UHF LOOP YAGIS

26 LOOPS	GAIN + 20 dBi	
1250-1340 MHz	1296-LY	\$49.75
1650-1750 MHz	1691-LY	\$54.75

Send 30¢ (2 stamps) for full details of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters
Varactor Triplers
Decade Pre-Scalers
Antennas

Amplifiers
Crystal Filters
Frequency Filters
Oscillator Crystals

SSB Transverters
FM Transverters
VHF Converters
UHF Converters



si

Spectrum
International, Inc.
Post Office Box 1084
Concord, Mass. 01742, USA

digital logic probe

A discussion
and several designs
for TTL and CMOS
logic probes,
featuring short pulse
type memories

When electronic equipment consisted primarily of analog circuitry, most maintenance and troubleshooting could be handled with a simple volt-ohmmeter and some common sense. The VOM was the one instrument that could always be found on the bench of any ham or electronic experimenter. In addition to being generally useful, the VOM had much going for it. It was relatively small and easily handled. It was generally affordable even by Radio Amateurs of very modest means. Although it wasn't a precision instrument, if one knew how to use it, very good results could be obtained. By and large, it is still a most useful tool, but it's one whose relative importance has considerably diminished.

Complementing the VOM today, as the general purpose test instrument of digital circuitry, is the logic probe. Like the VOM, the logic probe is easy to handle, convenient, inexpensive, and, when used intelligently, capable of furnishing the needed troubleshooting information.

There isn't much to a logic probe. It is simply a device that will indicate the "state" of an accessible point in a digital circuit. Using some sort of quick response display, like an LED for example, the probe will indicate whether the voltage at the test point is high, low, or, perhaps, alternating. Does every ham and electronic experimenter need one now? Well, that's pretty much for the individual to decide, a decision to be based on what other equipment is around the shack and whether he does his own maintenance or pays someone else to do it.

There is no getting around the fact that each new piece of electronic gear hitting the market contains more digital circuitry than did its predecessor. Not too long ago the digital circuitry in the typical ham shack might have been limited to that in the electronic keyer or, if there was a new and expensive oscilloscope, in the trigger circuit of the horizontal sweep. Today, digital circuitry is the heart of the fully synthesized, VFO, of frequency counters, modern capacitance meters, fashionable readouts and displays, to name a few places, and it's becoming ever more commonplace.

For troubleshooting these digital circuits, it is pretty tough to find better instrumentation than the simple logic probe. Coupling that observation with the fact that a generally adequate logic probe can be quickly and easily assembled at a cost of anywhere between a few quarters and a few dollars, depending upon the status of your "junk" box, it's hard to justify not having one around the shop bench or shack. Just how elegant or sophisticated a probe is needed for any given shack is easily determined and, using one or more of the following circuit ideas, built.

If all of the digital circuitry currently in your shack operates on +5 Vdc and you have no particular interest in detecting very short pulses (10 μ s or less) occurring at very low frequencies, then the very simplest of TTL (transistor transistor logic) probes should suffice. If your equipment is all in the 5-volt category, but there is a reasonable chance that you'll be looking for fleeting pulses, troubleshooting the triggered sweep of a modern oscilloscope is a prime example, then the logic probe should be slightly more elegant. The probe will still be based on a TTL integrated circuit, but some technique for capturing those elusive pulses need be added.

Some of the newest frequency synthesizers and frequency counters are built around LSI, or large-scale integrated circuits. Many of these are made up of mosfet rather than bipolar transistors. They may be operating on any voltage between about +4 and

By Raymond S. Isenson, N6UE, 4168 Glenview Drive, Santa Maria, California 93454

circuit of **fig. 1**. MAN 3A or MAN 3M LED readouts, or their equivalents, are available for as little as \$1.00 (or less) on the surplus market. One of these devices coupled to the output of the SN7404 hex inverter, as shown in **fig. 1**, makes for a most ingenious little display. A high at the probe tip causes the hex inverter to drive the numeric display so that a 1 appears. A low at the probe tip results in a 0 being displayed. If there is a pulsating signal at the test point you will see a P.

I did not originate this circuit; it is merely one of several that were available as inexpensive kits over the past several years. The output transistors of the hex inverter source the current to drive the LED segments. As this circuit uses no current-limiting transistors between the 7404 and the display, a short in the latter will likely destroy the inverter. That's the primary weakness of an otherwise very clever circuit.

The MAN 3A was used because it was available. A common-anode display could be used with, of course, appropriate interchange of connections. The significant point is that the output transistor is capable of sinking up to 30 mA, so that you can use either a common-cathode or common-anode display. This is not true, as will be discussed later, if the TTL device is replaced with an MOS device. Referring again to the probe shown in **fig. 1**, the two leads are connected to the V_{CC} and ground of the circuit under test, and the probe is held against the test point. **Fig. 3** shows the printed circuit board layout as seen from the foil side. The overall size of the board is tailored to fit snugly into the pill bottle so it may be necessary to make some slight changes to the printed-circuit board layout to fit any given plastic bottle.

pulse memory

When the instrumentation target is a very fleeting positive going pulse, such as in the previously suggested example of the trigger circuit of a modern oscilloscope, or if you are trying to ferret out some suspect random noise pulses in that new desk top computer, the logic probe must see and retain the high long enough to produce a visible signal on the


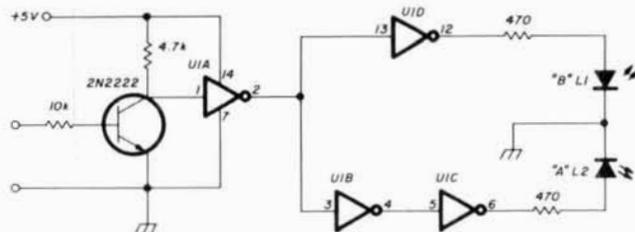


fig. 2. Schematic of the basic logic probe which used single LEDs to indicate either a high or low logic level. A cyclic signal will cause the LEDs to flash or both appear to be on due to the repetition rate.

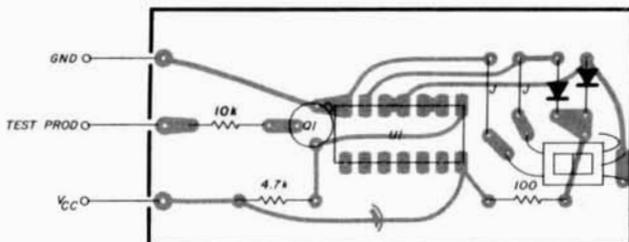

NOTE: J-DENOTE JUMPER

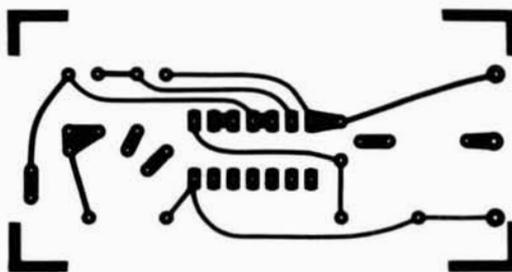


fig. 3. Etching pattern and parts placement diagram for the simple TTL logic probe.

LED display. An acceptable way of accomplishing this pulse "stretching" is through recourse to a one-shot multivibrator as a memory circuit. A very short incoming pulse, too short to be seen directly on the LED, is fed by the input amplifier of the probe to the input of the one shot, triggering it on. The output of the multivibrator is placed in parallel with one of the normal outputs of the hex inverter. The pulse duration at the output of the multivibrator is tailored by the time constants of the circuit so as to ensure a visible signal. Where the logic probe is to be used only on a +5 Vdc supply, and if there is an SN74121 in the junk box, a possible probe circuit is shown in **fig. 4**. The length of the output pulse duration needed to yield an acceptable display can be determined experimentally by varying R1, C1, or both.

versatile logic probe

An alternative short term memory uses the ubiquitous 555 timer. The connections for the 555 as a pulse stretcher is shown with a CMOS rather than a TTL hex inverter. Nevertheless, it can be used with the latter in exactly the same way. This, the most flexible and elegant logic probe, is presented in **fig. 5**. It can be used with any logic circuitry operating between approximately 4 and 15 Vdc. This means the logic probe can be used for RTL, DTL, TTL, or CMOS; in fact, for about any existing digital circuitry except for I²L. On the lower side, the voltage limitation is the efficiency of the LED display. With prime LEDs, it might be possible to work down to about 3 volts. On the high side, the limitation is the upper

limit on V_{DD} for the 4049 CMOS hex inverting buffer used as the logic chip and display driver. If a Fairchild F4049 is used, V_{DD} could safely go as high as 18 Vdc without damaging the probe. At any rate, it is most unlikely that the user will be confronted by voltages exceeding the range of 4.5 to about 13.8 volts so any 4049 will be acceptable and almost any surplus common-anode, seven-segment readout will work satisfactorily.

Being aware that the 74C04 and CD4069 CMOS hex inverters are pin compatible with the TTL 7404, one might well ask why go to the trouble of redesigning the circuit. Why not just replace the 7404 of the previously described logic probe with its CMOS counterpart and let the circuit go at that? There are two reasons why this cannot be done. The first has to do with the nature of the output mosfet of the CMOS chip, the second with the current limitation of the LED display.

In discussing the logic probe built around an SN7404 TTL hex inverter, note was made that the output transistors could each source about 15 mA or sink 30 mA. This permits the designer to select either a common-anode or common-cathode seven-segment LED display with the full confidence that there will be adequate current for safe direct drive of the LEDs. The 74C04 or 4069, on the other hand, are specified as being able to sink or source considerably less than 1 mA for +5 Vdc V_{DD} operation and 1.5 to 2 mA for 15-volt operation. The chip might be used with a common-cathode display, but the light intensity would be low. Used with a common-anode display, the CMOS output stage would quickly fail if it were forced to sink enough current for the LED to be acceptably visible, a function of the voltage applied to the common anode of the display and the size of the current-limiting resistors.

The problem is circumvented by turning to the CMOS 4049, a hex inverting buffer. These CMOS buffers provide both the necessary logic for the probe and a high current output capable of safely driving the LED load. It is not, however, as flexible as the TTL 7404. The CMOS buffer will typically sink about 5 mA with a V_{DD} of 5 volts and about 20 mA for a 15V V_{DD} . Under the same operating voltages, it will source only 1 to 3 mA. Thus, the TTL design option of using either a common-anode or a common-cathode configured display is closed; only a common-anode device can be used. How this is done is shown in the circuit in fig. 5.

The other major concern when designing the logic probe for this very wide range of operating voltages is the current limitations of the LEDs themselves. The generally useful current range of most LEDs is about 2 or 3 to 1. That is, starting with no current through

the LED, current is gradually increased until first, the light output is barely adequate to be seen in a lighted room and then second until the LED fails. The current at failure will be about 2 to 3 times that at "visible." By the way, this isn't offered as a "scientific truth," but rather as an observation based on experience and generally supported by pertinent specification sheets. Q2 and ZD1 in fig. 5 provide a voltage regulator whose output is applied to the common anode of the display. As the applied voltage at the V_{DD} lead of the probe is varied between +5 and +15 volts, the voltage at the output of the regulator varies between 4.4 and 6.2 Vdc. In the path between the output of the regulator and ground there is the 1N914, across which there will be about a 0.6-volt drop, the LED itself, which will account for a drop of 1.7 volts, and the current-limiting resistor which must make up the rest of the drop. The variation in voltage across the resistor, for the 4.4 to 6.2-volt swing, will thus be 2.1 to 3.9 volts, considerably less than 2:1 range. The LED current will be limited to the same range, one that is quite safe.

Three 1N914 diodes are shown between the 4049 and the LED readout in fig. 5. These diodes perform several functions so, unlike the diodes in fig. 1, cannot be replaced by slightly larger current-limiting resistors. This probe is designed to be used with operating voltages as high as 15 volts. Under this condition, and when the output of the buffer is in the high state, the output will approach 15 volts. Meanwhile, because of the voltage regulator, the anodes of the LEDs are close to 5 volts. The 1N914s protect the LEDs from what otherwise would be about a 10-volt reverse voltage, some 4 to 7 volts more than the maximum permitted according to the manufacturer's specifications. A second function of the diodes, or at least two of them, is to isolate the output mosfets of

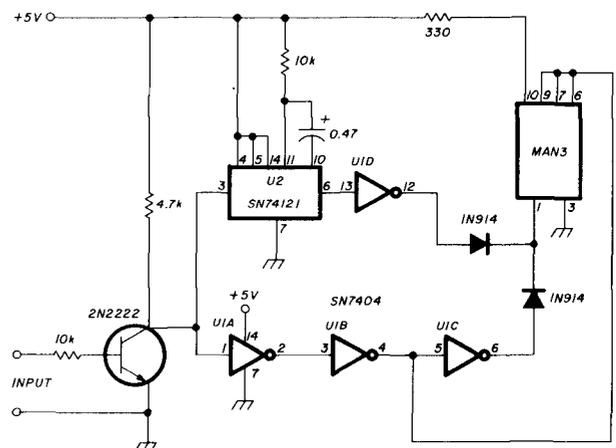


fig. 4. Diagram of the TTL probe with a short pulse memory. The monostable is used to capture any short-duration pulses for display on the LED display.

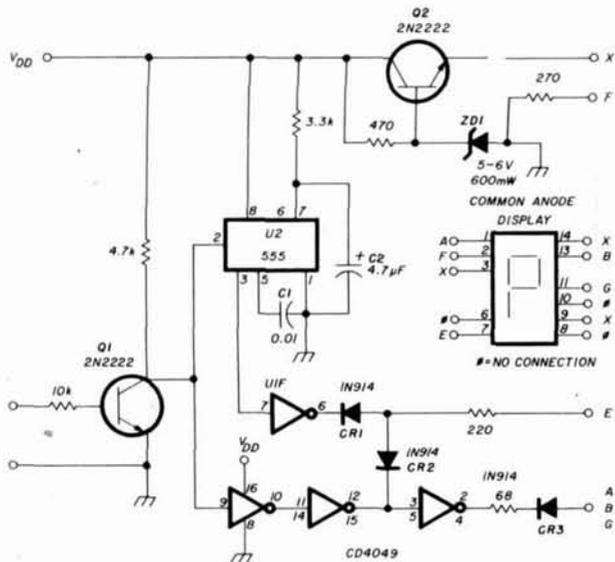


fig. 5. Schematic of the CMOS type logic probe with a short pulse memory. A 555 timer is used as the memory element; a common-anode display must be used in this version.

the inverter buffers from each other. Either of two inverters may go low to turn on segment E of the LED while the other is high. The diode isolation permits this to occur without risk to the 4049.

Unused inputs of CMOS ICs are never allowed to float. They are tied high, low, or to a used input. In the design of the circuit of fig. 5 the inverters were simply paralleled as necessary so that no inputs were allowed to float.


Just as the pulse stretcher for the TTL-based logic probe design could have been a 74121, this CMOS-based design could as well be a CD4047A monostable/astable multivibrator. The 555 timer was used because it's smaller and was available; it is also less expensive. There's nothing unusual about the employment of the 555; the one-shot configuration is right out of the book for a negative going trigger input and a one-shot stretched output. The output pulse length is given as $1.1 RC$ where the RC applies to the resistor between V_{DD} and pins 6 and 7 and the capacitor between this point and ground. The component values shown on the schematic were found, experimentally, to give a pulse that was just long enough to barely flash the Litronix readout. For test purposes, 0.25-microsecond pulses were generated at a pulse frequency of one pulse per second. Readout visibility was very acceptable. The test circuit is described briefly at the end of this article.

Obviously, the readability of the output for a stretched pulse can be enhanced simply by increasing the RC time constant in the 555 timer circuit. In designing the probe, however, the duration of the stretched pulse was deliberately kept to the useful

minimum; the probe readout differentiates between short pulses or noise pulses at low frequency recurrence rates and low frequency "clocking" phenomenon.

With a low-frequency, alternating state signal at the probe point (10 Hz or less), the readout will alternate between 1 and 0. At a higher frequency and in particular where the duty cycle is between 20 and 80 per cent, the eye of the observer is fooled into seeing a steady P. For very short positive-going pulses at low-frequency rates, the display is a brief P followed by an extended 0. At higher frequencies, the display takes the form of a fairly bright 0 with a dim staff to form the P.

None of the described logic probes will indicate the presence of a brief negative-going pulse. This is a design limitation accepted because I have never found need for that capability and because providing for it does cause some additional circuit complication. If the added capability is required, it can be achieved by modifying the CMOS logic probe as follows. Replace the 555 timer with a 556 dual timer. Isolate the two paralleled hex inverters. Connect the input of one of these inverters to the collector of Q1 and its output to the input of the added timer. Connect the output of the added timer to the input of the other freed inverter and its subsequent output to the cathode of an additional 1N914. The anode of the 1N914 connects to the anode of the existing 1N914 in the circuit coupled to the three LED segments that

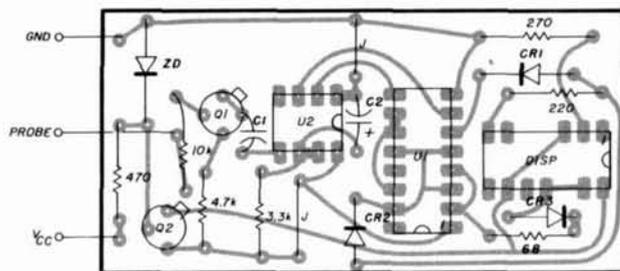

NOTE: J-DENOTES JUMPER

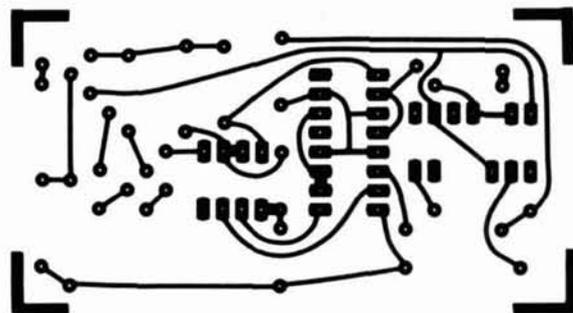


fig. 6. Printed circuit board layout and the parts placement diagram for the CMOS logic probe.

make up the switched element of the σ . In the presence of an occasional negative-going pulse, the display should be a 1 changing to a P when each pulse appears. The passive components associated with each half of the 556 should be the same as those shown for the probe in fig. 5.

Having decided upon the circuit to be implemented, the next step is to collect the pill bottle to be used as the case. This is an important step because the size and shape of the pill bottle will determine the size and layout of the circuit. Fig. 6 shows the circuit board layout of the CMOS logic probe described in detail above. It will be useful if your pill bottle will take a $1\frac{1}{4} \times 2\frac{1}{2}$ -inch (3.0 x 6.0-cm) board.

Printed circuit board techniques were used for both probes shown in this article only because it was convenient to do so. Wire wrap techniques or even point-to-point wiring on sockets mounted in perf board would be just as good. The logic probe is fundamentally a low-frequency device. It would be difficult to find a poor construction technique as long as the workmanship is good!

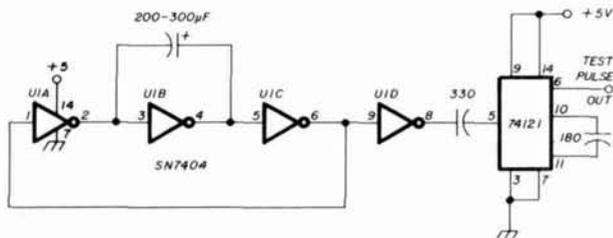


fig. 7. Pulse generator to test the short pulse memory capability of the logic probes.

Test of the completed circuit for all but the pulse stretching feature is easily accomplished. Connect the V_{DD} and V_{SS} or V_{CC} and ground wires, depending upon your choice of CMOS or TTL, to an appropriate power source. If everything is working properly the readout will display a σ . Touch the probe to the positive voltage terminal of the power supply and the σ should change to 7. The circuit shown in fig. 7 will test the pulse capture feature if one has been included. Pulse length of the output pulse of the 74121 is approximately $1400 \cdot C_1$ seconds. If C_1 is 180 pF, the pulse at the test point would be $1400 \cdot 180 \cdot 10^{-12}$ second or approximately 0.25 microsecond.

The logic probe is a very practical instrument to have around the shop or shack. If you don't have one and can squeeze out an evening, try one of the circuits presented here. It won't be long before you begin to wonder how you ever managed to get along without it!

ham radio

Aye! Larsen's clan of Kūlrod® Antennas deliver top performance and value!



Performance and value are built into every Larsen Antenna because of craftsmanship that accepts no compromise.

Making mobile antennas, mounts and accessories is Larsen's *only* business. All of the company's research, engineering and production efforts are directed to making the best antennas money can buy. The end result is the exclusive Kūlrod by Larsen. A Kūlrod antenna delivers maximum radiation efficiency instead of losing power to heat.

Larsen's antenna clan includes low band, high band, quarter wave, VHF, UHF, mobile, fixed base and Kūlduckies for hand-helds. And Larsen offers every type of permanent and temporary vehicle mount — including a magnetic model that's a real grabber.

So whatever band you operate on, if your antenna is a Larsen you'll HEAR the difference!



Larsen Antennas

P.O. Box 1686
Vancouver, WA 98668
Phone: (206) 573-2722

In Canada, write to:
Canadian Larsen Electronics, Ltd.
283 E. 11th Ave., Unit 101
Vancouver, B.C. V5T 2C4
Phone: (604) 872-8517

® Kūlrod is a Registered Trademark of Larsen Electronics, Inc.
® Kūlduckie is a Trademark of Larsen Electronics, Inc.

TALK IN

146.16/76

146.52

N.W. INTERSECTION
OF ILL. RT. 45 & 120
GRAYSLAKE ILL.

10TH

RADIO EXPO

SEPT. 6TH AND 7TH

FIRST WEEKEND AFTER LABOR DAY

WA9ORC/R

SPONSORED BY THE CHICAGO FM CLUB,

**LARGEST EVER
SOMETHING FOR ALL!**

HUGE MANUFACTURER DISPLAY BLDG.

FLEA MARKET/INDOORS AND OUTDOORS

SPACE FOR ALL/BRING TABLE AND CHAIRS

SEMINARS and TECHNICAL TALKS

LADIES PROGRAMS and PRIZES

**THOUSANDS OF DOLLARS
WORTH OF DOOR PRIZES!**

FREE PARKING AND OVERNIGHT CAMPING

TICKETS GOOD FOR BOTH DAYS

\$3.00 AT GATE—\$2.00 ADVANCED

ADVANCED TICKETS SEND #10 S.A.S.E. AND \$2.00 FOR EACH TO

BOX 1532

EVANSTON, ILL. 60204 (312) 278-3976



challenge for microwave-antenna designers

New ideas are needed
for low-cost, efficient
microwave antennas
for satellite
TV reception

Attention antenna-design enthusiasts: Will you be the person who develops a novel idea for low-cost antennas for satellite TV reception? There's a real challenge waiting to be met, and this challenge is a prime opportunity for Amateur Radio operators to make a significant contribution to an important new and growing segment of space-communications technology. Conventional parabolic-reflector antennas are too costly — new ideas are needed to reduce the cost of antennas with 40-50 dB gain at 4 GHz.

TV receive-only terminals

There is a TV technological revolution underway, and the advanced hobbyists who are a part of that revolution have been searching for a gallium arsenide fet low-noise amplifier or a low-cost 12-foot (3.7-meter) parabolic reflector antenna for a home TV receiver terminal. Many hobbyists have succeeded in obtaining enough gain and a decent signal from a backyard antenna aimed at one of a dozen — soon to be more — satellites transmitting from above the equator.¹

These installations are called TV receive-only terminals, or home TVROs. Home TVROs are already the province of skilled and dedicated experimenters. The number of private terminals in operation is difficult to determine since very few are licensed, but some estimates are as high as 1000.²

Video programming on domestic satellites currently offers a great deal in the way of quality entertainment and information, and it will get even better in the future. Satellite distribution of these TV programs to private and shared receiver terminals allows anyone in this country to participate in a new and entertaining form of communications. Technical sessions at WESCON by J.C. Bacon,¹ J. Kinik,² H.P. Shuch,³ and H.T. Howard⁴ form the basis for much of the information in this article.

FCC deregulation

Much is happening in Washington to help give people these new opportunities.¹ Bills in both the Senate and House to rewrite the 1934 Communications Act have been introduced, deregulation trends are underway at the FCC, and the Executive Branch has initiated several actions to expedite these efforts.

The Justice Department has responded to the FCC in favor of deregulation of receive-only earth stations stating that the language of the 1934 Communications Act, which created the FCC, authorized regulation of transmitting devices — not receive only.¹

The Federal Communications Commission decided on October 18, 1979, to drop its licensing requirements for satellite receiving stations.⁵ The action eliminates the requirement that persons constructing a receiving antenna have it coordinated to eliminate interference. It also ends a requirement that they

By **D. H. Phillips, W6FOO**, 1345 Arizona Avenue, Milpitas, California 95035

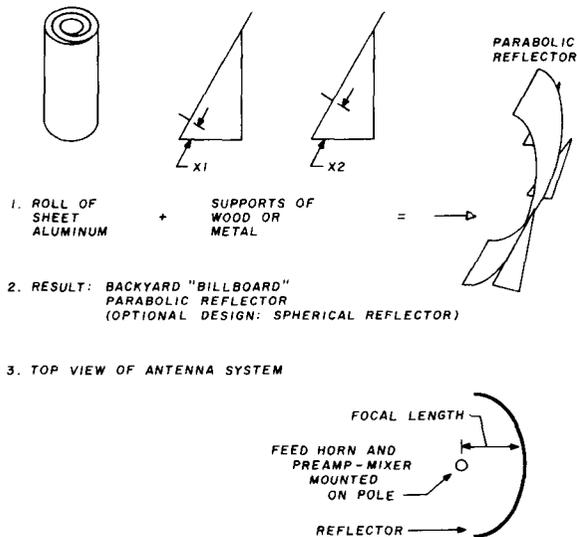


fig. 1. Billboard parabolic reflector construction for low-cost TVRO antenna.

obtain a construction permit and ultimately a license to operate the receiving station.

Those who want licenses, to obtain government protection from interference with the signals they receive, will still be able to apply, the commission said. But it also said the licensing will be entirely optional. The FCC said it took the action to eliminate the costs of the licensing process for builders of receiving stations and to end delays involved in obtaining a license.

FCC Chairman Charles D. Ferris noted that, while operators of unlicensed stations will not be protected from interference, this can normally be eliminated by relocating the station slightly, which is usually less costly than obtaining a license.⁵ Operators of receiving stations will still have to obtain permission from the operators of the sending satellites to receive their transmissions.⁵

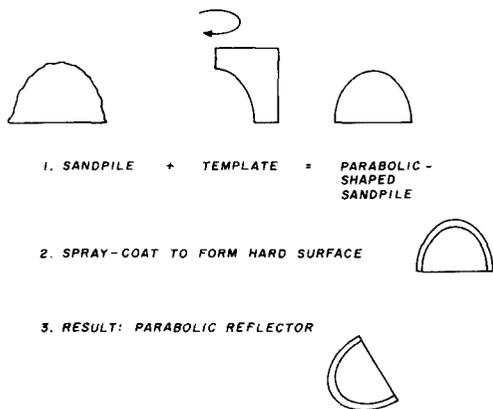


fig. 2. Sandpile parabolic reflector construction for low-cost TVRO antenna.

low-cost novel designs are needed

In January, 1977, the FCC ruling allowing the use of 4.5-meter diameter antennas for TV receive-only earth terminals created a strong need for low-cost antennas in the 4.5 to 6 meter size range for the first time.²

Two suppliers, Scientific Atlanta and Anixter-Mark, have invested in tooling to stamp out panels to the correct curvature on a mass production basis.² Another supplier, United States Tower Company, has combined a fiberglass reflector with an aluminum

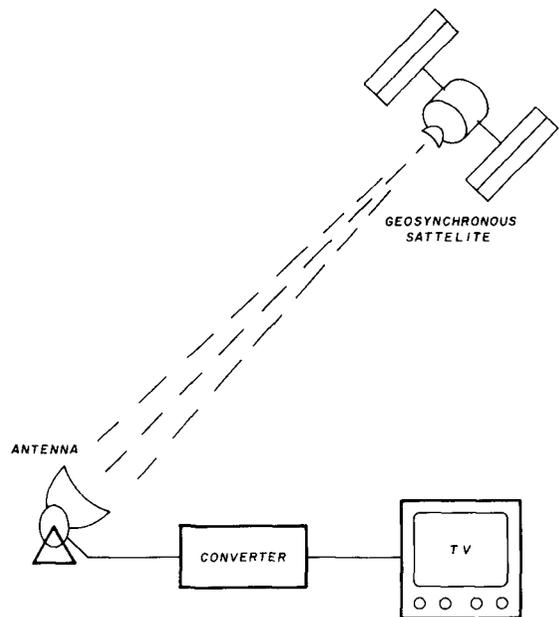


fig. 3. Typical TV receive-only (TVRO) terminal for receiving signals from geosynchronous communications satellites. Problem: Design a low-cost antenna of good structural integrity and adequate rf performance.

backup structure to realize a more cost-effective design. The nominal current price levels for the lowest-cost designs offered by the commercial suppliers are \$1500 for 3-meter diameter, \$4000 for 4-meter diameter, and \$6000 for 5-meter diameter antennas.² These antenna costs must be reduced, through novel antenna designs, so that the total cost of a complete TVRO terminal can be kept low enough to be afforded by nearly everyone.

satellite TV signals

The technological revolution which makes possible the distribution of television programming via satellite is based on receiving DOMSAT (Domestic Communications Satellite) signals.³ The downlink band used by most North American DOMSATS is 500 MHz

wide, and for a given antenna polarization there will be present up to twelve video carriers spaced 40 MHz apart. These signals are of extremely low amplitude, and this complicates the design of TVRO antennas.

It has been shown that, for the illumination contours typical of most North American DOMSATs,³ an optimum private-terminal antenna will exhibit on the order of +41 dBi gain.* Given the signal power (EIRP) and path loss numbers listed in **table 1**, the signal level available to the low-noise amplifier will be on the order of -90 dBm.

technical requirements

The dominant requirement for private TVRO antennas is low cost, while of course retaining reasonable structural integrity and adequate rf performance. These three considerations establish the baseline for a set of requirements, but the process of arriving at a set of such requirements is one which is more practical than scientific — thereby creating a challenging opportunity for ham radio operators and experimenters who can make a significant contribution to an important new and growing segment of space-communications technology.

A low-cost design must not require high-cost fabrication methods, tooling, or labor. It should also have a minimum weight and volume to keep costs down, and it should be designed with ease of installation in mind to avoid expensive hoisting equipment. Total installation time should be kept to a minimum. An additional requirement is that the design should be amenable to kit construction techniques. These goals, if met, can be combined with gallium arsenide

table 1. Typical DOMSAT signal characteristics (from reference 3).

video carrier	
channels	24
adjacent channel spacing	40 MHz
orthogonal channel spacing	20 MHz
frequency band	3.7-4.2 MHz
peak deviation	10.25 MHz
maximum video frequency	4.2 MHz
pre-emphasis curve	CCIR 405-1
audio subcarrier	
frequency	6.8 MHz
peak deviation	75 kHz
maximum audio frequency	15 kHz
pre-emphasis time constant	75 μ Sec
composite	
EIRP	+ 65 dBm
path loss	- 196 dB
99% power bandwidth	36 MHz
received spectral density	- 206 dBm/Hz

*Gain referred to an isotropic source. Editor.

table 2. Technical performance goals for 3.7-4.2 MHz TVRO antenna.

	required minimum	desired
antenna gain	40 dBi	45 dBi
rf efficiency	45%	55%
wind survival	75 mph	75-100 mph

integrated circuit technology⁶ to develop a superior TVRO terminal.

new design ideas?

The optimum low-cost TVRO antenna has yet to be designed and developed. This is an active area of research, and some new ideas are beginning to emerge. One idea, shown in **fig. 1**, requires only low-cost materials and requires no expensive metal shaping. A second idea is illustrated in **fig. 2**. This clever design is based on an idea by John, K6EJF, who suggested using spray-on material of the type often used for coating swimming pools. The template can be made of plywood and a guide-pin or rod can be driven into the sandpile for attachment to the template.

New microwave antenna designs and discoveries are bursting forth at a rapid rate. An example of this is the discovery that the snow sled saucers sold as kids' toys exhibit 22 dB of gain at S band!⁴ A similar antenna was constructed from a child's 25-inch (64-cm) snow sled saucer and a feed horn was made from a one-pound coffee can. The saucer is not a true parabola but is close enough to give 15+ dB of gain at 2 GHz.⁷

Will you be the person who develops a new idea for low-cost antennas for satellite TV reception? I'd like to hear from you if you have a clever idea for the construction of a new low-cost antenna. Your information may be useful during the preparation of a subsequent article on the subject of TVRO terminals. Write to Dr. D.H. Phillips, 1345 Arizona Avenue, Milpitas, California 95035.

references

1. J.C. Bacon, "Those Great Repeaters in the Sky," WESCON Session 25, September, 1979.
2. J. Kinik, "Antennas and Feeds for Domestic Satellite TV Reception," WESCON Session 25, September, 1979.
3. H.P. Shuch, "A Low-Cost Modular Receiver for DOMSAT Video," WESCON Session 25, September, 1979.
4. H.T. Howard, "The Inexpensive, Private TVRO Terminal — A simple design with a Complex Impact," WESCON Session 25, September, 1979.
5. "A Ruling on Satellite Receiving Stations," San Francisco Chronicle, October 19, 1979.
6. D.H. Phillips, "GaAs Integrated Circuits for Military/Space Applications," *Military Electronics/Counter-measures*, Vol. V, No. 3, March, 1979.
7. J. Barber and J. Kieberg, "You Can Watch Those Secret TV Channels," 73, August, 1979, pages 32-43.

ham radio

Top-Notch.



VBT, notch, IF shift, wide dynamic range

TS-830S

Now most Amateurs can afford a high-performance SSB/CW transceiver with every conceivable operating feature built in for 160 through 10 meters (including the three new bands). The TS-830S combines a high dynamic range with variable bandwidth tuning (VBT), IF shift, and an IF notch filter, as well as very sharp filters in the 455-kHz second IF. Its optional VFO-230 remote digital VFO provides five memories.

TS-830S FEATURES:

- **160-10 meters, including three new bands**
Covers all Amateur bands from 1.8 to 29.7 MHz (LSB, USB, and CW), including the new 10, 18, and 24-MHz bands. Receives WWV on 10 MHz.
- **Wide receiver dynamic range**
Junction FETs (with optimum IMD characteristics and low noise figure) in the balanced mixer, a MOSFET RF amplifier operating at low level for improved dynamic range (high amplification level not needed because of low noise in mixer), dual resonator for each band, and advanced overall receiver design result in excellent dynamic range.

- **Variable bandwidth tuning (VBT)**
Continuously varies the IF filter passband width to reduce interference. VBT and IF shift can be controlled independently for optimum interference rejection in any condition.
- **IF notch filter**
Tunable high-Q active circuit in 455-kHz second IF, for sharp, deep notch characteristics.
- **IF shift**
Shifts IF passband toward higher or lower frequencies (away from interfering signals) while tuned receiver frequency remains unchanged.
- **Various IF filter options**
Either a 500-Hz (YK-88C) or 270-Hz (YK-88CN) CW filter may be installed in the 8.83-MHz first IF, and a very sharp 500-Hz (YG-455C) or 250-Hz (YG-455CN) CW filter is available for the 455-kHz second IF.
- **Built-in digital display**
Six-digit large fluorescent tube display, backed up by an analog dial. Reads actual receive and transmit frequency on all modes and all bands. Display Hold (DH) switch.
- **Adjustable noise-blanker level**
Built-in noise blanker eliminates pulse-type (such as ignition) noise. Front-panel threshold level control.

- **6146B final with RF NFB**
Two 6146B's in the final amplifier provide 220 W PEP (SSB)/180 W DC (CW) input on all bands. RF negative feedback provides optimum IMD characteristics for high-quality transmission.
 - **More flexibility with optional digital VFO**
VFO-230 operates in 20-Hz steps and includes five memories. Also allows split-frequency operation. Built-in digital display. Covers about 100 kHz above and below each 500-kHz band.
 - **Built-in RF speech processor**
For added audio punch and increased talk power in DX pileups.
 - **RIT/XIT**
Receiver incremental tuning (RIT) shifts only the receiver frequency, to tune in stations slightly off frequency. Transmitter incremental tuning (XIT) shifts only the transmitter frequency.
 - **SSB monitor circuit**
Monitors IF stage while transmitting, to determine audio quality and effect of speech processor. Ask your Authorized Kenwood Dealer about the many operating features offered by the TS-830S... at a very reasonable price!
- NOTE:** Price, specifications subject to change without notice and obligation.

MATCHING ACCESSORIES FOR FIXED-STATION OPERATION:

- SP-230 external speaker with selectable audio filters
- VFO-230 external digital VFO with 20-Hz steps, five memories, digital display
- AT-230 antenna tuner/SWR and power meter
- MC-50 desk microphone
- YG-455C (500-Hz) and YG-455CN (250-Hz) CW filters for 455-kHz IF
- YK-88C (500-Hz) and YK-88CN (270-Hz) CW filters for 8.83-MHz IF
- HC-10 digital world clock
- HS-5 and HS-4 headphones
- MC-30S and MC-35S noise-cancelling hand microphones

Other accessories not shown:

- TL-922A linear amplifier
- SM-220 Station Monitor
- PC-1 phone patch



New 2-meter direction.



A compact transceiver with FM/SSB/CW plus... TR-9000

Kenwood's done it again! Now, it's the exciting TR-9000 2-meter all-mode transceiver...complete with a host of new features. Combining the convenience of FM with long-distance SSB and CW in a very compact, very affordable package, the TR-9000 is the answer for any serious Amateur Operator! Versatile? You bet! Because of its compactness, the TR-9000 is ideal for mobile installation. Add on its fixed-station accessories and it becomes the obvious choice for your ham shack!

TR-9000 FEATURES:

- FM, USB, LSB, and CW... all popular modes
- Compact size... only 6 11/16 inches wide X 2 21/32 inches high X 9 7/32 inches deep
- Digital dual VFOs... with selectable tuning steps of 100 Hz, 5 kHz, and 10 kHz, convenient for each mode of operation
- Digital frequency display... five, four or three digits, depending on selected tuning step

- Extended frequency coverage... 143.9000 - 148.9999 MHz
- Five memories:
 - M1 - M4... for simplex or ± 600 kHz repeater offset
 - M5... for nonstandard offset (memorizes transmit and receive frequency independently)
- Scan of entire band... automatic busy stop and free scan
- SSB/CW search... sweeps over selectable 9.9-kHz bandwidth segments, for easy monitoring
- UP/DOWN microphone (standard)... "beep" sounds with each frequency step
- Noise blanker... eliminates pulse-type noise on SSB and CW
- Low-noise, dual-gate MOSFET and two-stage monolithic crystal filter for improved receiver front-end characteristics
- RIT (receiver incremental tuning) for SSB and CW... effective even on memory channels
- RF gain control
- CW sidetone
- Automatic selection of AGC time constant with MODE switch (slow for SSB and fast for CW)
- Improved power module for reliable and stable linear RF output
- Selectable power outputs... 10 W (HI)/1 W (LOW)
- Mobile mounting bracket... easy to mount, with quick-release levers
- LED indicators... ON AIR, BUSY, and VFO
- Accessory terminals on rear panel... KEY, BACKUP DC, STBY, EXT SP, DC, TONE INPUT, and ANT

See your Authorized Kenwood Dealer now for details on the TR-9000... the new direction in 2-meter all-mode transceivers!

NOTE: Price, specifications subject to change without notice and obligation.

MATCHING ACCESSORIES FOR FIXED-STATION OPERATION:

- PS-20 power supply
- SP-120 external speaker
- BO-9 System Base... with power switch, SEND/RECEIVE switch for CW operation, backup power supply for memory retention (BC-1 backup power adaptor may also be used for this application), and headphone jack



calculating the cascade intercept point of communications receivers

New equations
for calculating
a receiver's
cascade intercept point
are a powerful
design tool

On today's heavily used Amateur bands which have many extremely strong signals, receivers with high dynamic range are required. Many articles have treated the considerations and problems of designing a high dynamic range receiver from the circuitry point of view, but a systematic approach to receiver design seems to be lacking.

receiver system design

The best way to approach a receiver design problem is with a block diagram. By identifying the various functional blocks in a receiver, the critical parameters for dynamic range (input intercept point, noise figure, and bandwidth) can be predicted for the overall receiver.

Dynamic range may be defined as

$$DR = \frac{2}{3} (IP_{i3} - MDS) \quad (1)$$

where DR = spurious-free dynamic range, dB
 IP_{i3} = third-order input intercept point, dBm
 MDS = minimum detectable signal (noise floor), dBm

For a system at room temperature the minimum detectable signal is

$$MDS = -174 \text{ dBm} + NF_t + 10 \log BW_n \quad (2)$$

where NF_t = overall system noise figure, dB
 BW_n = system noise bandwidth, Hz


Note that the system noise bandwidth is usually well approximated by the 3-dB bandwidth of the narrowest filter in the system. The total (or cascade) noise figure of a system is

$$F_t = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_2 G_1} + \dots \quad (3)$$

$$NF = 10 \log F_t \quad (4)$$

The minimum discernible signal can be calculated from the last three equations, but some method is needed to predict the system's input intercept.

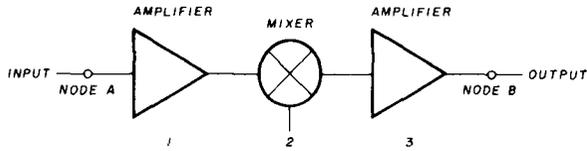By Brian P. Gross, WA7TDB, 2900 East Aurora Avenue, No. 146, Boulder, Colorado 80303



Gain	+ 10 dB	- 7 dB	+ 20 dB
IP _{o3}	+ 20 dBm	+ 20 dBm	+ 50 dBm

fig. 1. Simple converter used to illustrate cascade IMD equations. Note that although only two nodes are specified, there are two other nodes (on either side of the mixer) that could be used for intercept point calculations.

cascade intercept point

To obtain the intercept point for a system, the intercept points of the various functional blocks will be combined in such a way as to predict the input or output intercept of a system.

There are two ways of approaching the cascade intercept point equations. The first is to assume the intermodulation products are coherent; when the products are coherent their voltages will add in phase. The second approach is to assume the intermodulation products are non-coherent; in this case their voltages will combine as a sum of squares.

The assumption of coherence will always result in the lower predicted intercept point and for most Amateur applications is the preferred approach. There are situations, however, where the assumption of non-coherence is reasonable; the most obvious situation is a microwave system where phase shifts between system elements may place the products out of phase.

coherent summation

The equation for coherent summation* is

$$IP_t = \frac{20}{n-1} \log \left(10^{\frac{-(n-1)IP_1}{20}} + 10^{\frac{-(n-1)IP_2}{20}} + \dots \right) - 1 \quad (5)$$

where n is the order of the intermod (2 for second order, 3 for third order, etc.), and

IP_m is the reflected intercept (of the appropriate order) of the m th element

All the intercepts of the various system elements must be reflected to a single node. The example in fig. 1 will help clarify this.

First a table must be drawn up (table 1) that contains the reflected intercept points. Note that input intercept plus gain equals output intercept ($IP_i + G = IP_o$).

Substituting the information in table 1 into eq. 5, the input intercept (node A) turns out to be $IP_{it} = +9.14 \text{ dBm}$. The output intercept (node B) is $IP_{ot} = +32.14 \text{ dBm}$.

table 1. Table of reflected intercept points for the system of fig. 1. This listing not only gives the intercept information, but also pinpoints the weakest elements in a system, in this case element 1.

element	reflected intercept point	
	node A	node B
1	+ 10 dBm	+ 33 dBm
2	+ 17 dBm	+ 40 dBm
3	+ 27 dBm	+ 50 dBm

non-coherent summation

For the case of non-coherent summation the cascade intercept point equation is

$$IP_t = \frac{10}{n-1} \log \left(10^{\frac{-(n-1)IP_1}{10}} + 10^{\frac{-(n-1)IP_2}{10}} + \dots \right) - 1 \quad (6)$$

If non-coherent summation was assumed for the system of fig. 1, the input intercept becomes

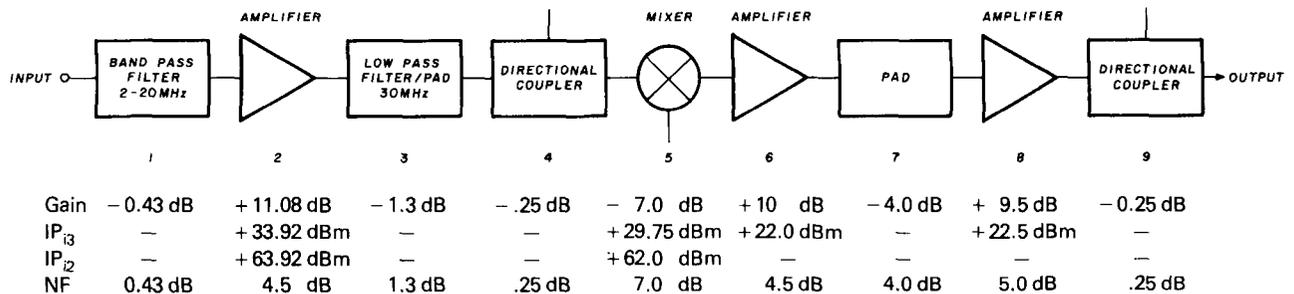


fig. 2. Block diagram of a receiving converter built by the author with performance data for each of the elements in the system. When a dash is used in place of data, it indicates no contribution from that particular system element.

ANTENNA COMPONENTS

Antenna wire, stranded #14 copperweld.....	\$.08 ft.
75, 100, 130, 150, 300, or 1,000 ft. rolls	
Antenna Wire, stranded #15 copperweld.....	.06 ft.
75, 100, 130, 150, 200, or 300 ft. rolls	
Antenna wire, stranded #16 copperweld.....	.05 ft.
75, 100, 130, 150, 200, or 300 ft. rolls	
Van Gorden HI-Q Baluns, 1:1 or 4:1.....	10.95 ea.
Unadilla/Reyco, W2AU Baluns, 1:1 or 4:1.....	14.95 ea.
Van Gorden HI-Q center insulators.....	5.95 ea.
Ceramic "Dogbone" end insulators, pair.....	.98
Van Gorden plastic end insulators, pair.....	4.95
Nylon guy rope, 450 lb. test, 100' roll.....	3.49
Unadilla/Reyco W2VS Traps, KW-10 thru KW-40.....	21.95 pr.
Belden 8214 RG-8U type foam coax.....	30 ft.
50, 60, 75, 100, and 125 ft. rolls	
Belden 8219 RG-58 A/U foam coax.....	12 ft.
50, 60, 75, 100, 125, 200, 300 and 1,000 ft. rolls	
Berk-Tex 6211 RG-8X foam coax, Ultraflexible.....	16 ft.
50, 60, 75, 100, 125, 200, 300, and 500 ft. rolls	
Amphenol 83-1SP PL-259 connectors.....	.75 ea.
Amphenol UG-175/U adapters (RG-58).....	.25 ea.
Amphenol UG-176/U adapters (RG-8X, RG-59).....	.25 ea.
Amphenol PL-258, straight adapter.....	1.07

ALSO IN STOCK

Larsen Mobile Antennas • Hustler Mobile Antennas • Palomar Engineers • Centurion International Rubber Duck Antennas

WRITE FOR A FREE COPY OF OUR CATALOG

MASTER CHARGE

VISA

All items F.O.B. Lincoln, \$1.00 minimum shipping. Prices subject to change without notice. Nebraska residents please add 3% tax.

g & c Communications
730 Cottonwood Lincoln, Nebraska 68510

$IP_{it} = +9.91 \text{ dBm}$ and the output intercept becomes $IP_{ot} = +32.91 \text{ dBm}$. In this simple example the results from eq. 5 and eq. 6 are nearly identical. In general, however, as the system becomes more complicated, the difference between the two will be much larger.

receiving converter

The block diagram of fig. 2 represents a receiving converter I built. It provides a convenient example system for comparing the predicted and measured parameters. Using the data in fig. 2, a table of reflected intercept points can be drawn up (table 2); by using the formula for coherent summation (eq. 5) the resultant input intercept can be calculated, and from eq. 4, the system noise figure can be calculated.

table 2. Calculated intercept point for the receiving circuit shown in fig. 2. Measured intercept point is shown in parentheses for comparison and shows good agreement.

element	reflected intercept point	
	IP_{i2}	IP_{i3}
2	+64.35 dBm	+34.35 Bm
5	+52.90 dBm	+20.65 dBm
6	—	+19.90 dBm
8	—	+13.90 dBm
IP_{it}	+50.84 dBm (+54.0 dBm)	+12.22 dBm (+13.0 dBm)

Using eq. 4 the predicted system noise figure is 7.1 dB; dynamic range can now be predicted. If a 500-Hz filter were placed after the system shown in fig. 2, then the $MDS = -139.91 \text{ dBm}$ and the dynamic range would be 101.42 dB.

Two-tone and noise figure tests were run on the system of fig. 2 which resulted in measured $IP_{i2} = +54.0 \text{ dBm}$, $IP_{i3} = +13.0 \text{ dBm}$, and $NF_t = 6.9 \text{ dB}$. These tests show excellent agreement with the predicted data.

conclusion


The cascade intercept point equations, when used in combination with the cascade noise figure equation, provide a powerful tool for rf system design. Derivations of eq. 5 and eq. 6 will be sent to interested readers upon receipt of a self-addressed, stamped envelope. With these equations a receiver designer can predict a system's characteristics without investing in any hardware.

acknowledgments

My thanks to Rich Phillips of ARGOSystems (formerly of ESL, Inc.) for initially pointing out the utility of these equations. My thanks also to Wes Hayward, W7ZOI, for kindling my interest in receiver design.

ham radio

New!

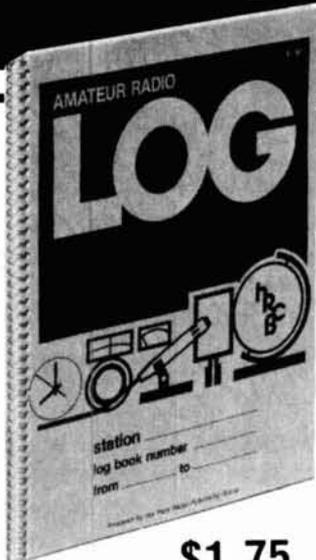

Twice as much for less.

□ **HR-LB** Here's the log book every one is talking about. This new offering from HRB is far superior to any other log available today! With over 2,000 entries, you have twice as much space for less cost in comparison to its nearest competitor. There are 80 big (8½ × 11) pages, 30 entries per page for an "easy-count" during contests, a frequency spectrum chart, callsign prefixes and much more. This is unquestionably the best log book value anywhere. 80 pages. ©1978. Spiralbound.

\$1.75

Send check, money order or credit card information plus \$1.00 shipping to:

Ham Radio's Bookstore
Greenville, NH 03048

ATTENTION IC-2A OWNERS:

IC-2A TONE DECKS ARE HERE!

CUSTOM DESIGNED TO FIT WITH NO TROUBLE!

IT'S HERE NOW!

The question used to be, "When is Icom coming out with a hand-held?"...Now that it's become one of the hottest two meter rigs around, the big question now is, "When will a sub-audible tone option be available for my IC-2A?" The answer is: Spectronics has it now!




FULLY TUNABLE!

We are proud to be first in offering you a fully tunable miniature sub-audible tone deck specifically designed to fit the Icom IC-2A hand-held transceiver. If you own one of the other synthesized hand helds, you'll be delighted to know that you can put it in your unit as well.



QUALITY TO LAST!

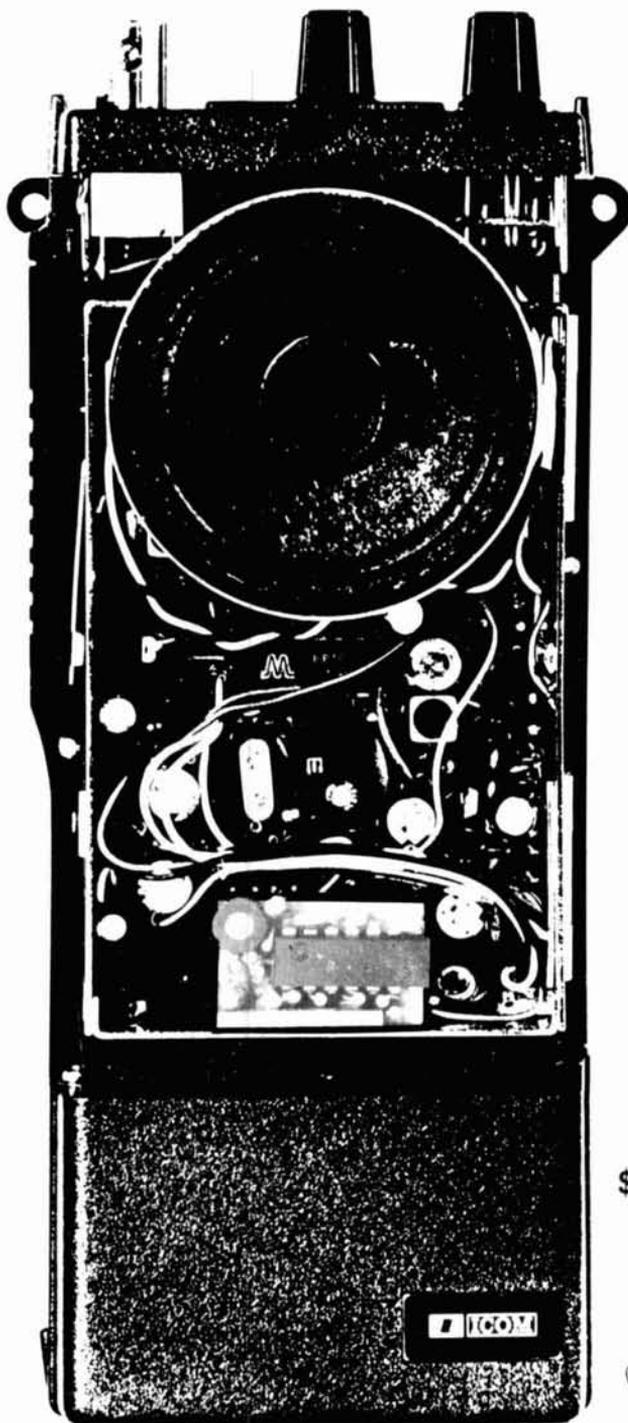This unit is manufactured by Transcom, Inc., to their exacting standards, and is guaranteed to be stable to within ± 1 Hz, after proper tuning. All units are pre-set to your specified tone, and require no further adjustment for frequency.



ANOTHER SPECTRONICS FIRST!



TOP VIEW



SIDE VIEW

- Fits plain or TT.
- Fully tunable! No tone elements to buy - ever!
- Also fits other synthesized hand-helds as well.
- Easy to install; no cutting, chopping, or remote parts!
- Accurate to ± 1 Hz.

\$ **29**⁹⁵
Plus \$2.00
S & H



PHONE: (312) 848-6777



SPECTRONICS, INC. — 1009 GARFIELD ST.
OAK PARK, ILL.-60304

diode frequency divider

Using diodes as
voltage-variable capacitors
to produce
a sine wave
at one-half
the input frequency

The use of diodes as frequency multipliers, and particularly as doublers, has been well known for a good many years. Such applications are covered quite well in a recent ARRL publication¹ and provide many ideas to the Amateur builder and experimenter. However, one application for diodes that I don't recall finding in an Amateur publication is their use in a frequency divider, with what is practically the same circuit!

Consider fig. 1A, which is a standard full-wave rectifier. It is familiar to just about every ham as is the output waveform, fig. 1B. The fundamental frequency has been cancelled by the full-wave circuit, and a quite respectable frequency doubler is the result.

frequency-divider circuit

Now let's change the circuit slightly to that of fig. 2. We will feed a signal of frequency f through a blocking capacitor to the diodes, reversing the direction taken when the circuit was a rectifier. There is another difference, as well, as the clamping action of the diodes builds up a bias voltage across the blocking capacitor, and the diodes are operating in their nonconducting range. Furthermore, the center-tapped transformer has become a center-tapped tank circuit by the addition of a capacitor that tunes the circuit to $f/2$, one-half the input frequency.

Operating in their nonconducting range, the diodes present only their junction capacitance to the circuit and are now regarded as capacitors. Even though both diodes may be of the same type and rating, their junction capacitances will not be identical, so a voltage will build up on one end of the tank circuit. The voltage on the other end will be of opposite polarity, increasing the reverse voltage on that diode, further increasing any differences in the capacitances. When the next input pulse appears, the polarity of the voltages on the tank circuit will have reversed due to the flywheel effect of the tuned tank. Thus, successive input pulses will affect alternate ends of the tank, resulting in a signal of half the input frequency. Input power transfer will probably

By Henry S. Keen, W5TRS, Fox, Arkansas
72051

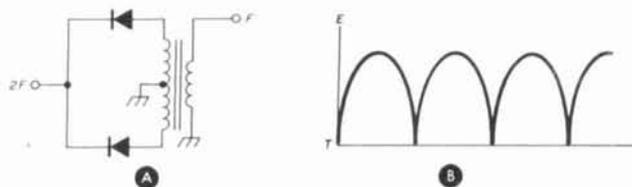


fig. 1. Standard full-wave rectifier (A) and the typical output waveform it produces (B).

be improved if some form of input matching network is used.

The power limitations of this circuit are a function of the diode characteristics, such as junction capacitance, leakage, and peak inverse voltage. Of course, power varactors are available at several bucks a throw, which would probably be more predictable in their operation; but silicon diodes out of your junk box may be pressed into service for a tryout.

suggested applications

A frequency divider such as this should offer a quick means of giving 160 meters a whirl, using the 80-meter rig, and without the necessity of building a separate new transmitter! My first use of the circuit involved a pair of top-hat diodes to reduce a 910-kHz

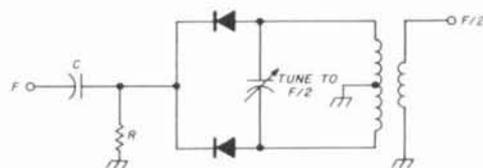


fig. 2. The diode frequency divider. A signal, f , is applied through a blocking capacitor, which reverses the signal direction. The center-tapped transformer is now a center-tapped tank circuit with the addition of a variable capacitor. Circuit delivers a good sine wave with good efficiency.

oscillator signal to 455 kHz in experiments with DSB reception. Unless the diodes are badly mismatched, it works right off. The value of resistor R of fig. 2 should be quite high, as we are interested only in biasing the diodes into the non-conductive region. With a good pair of diodes, resistances up to 100 k would seem a reasonable figure.

This circuit delivers a good sine-wave signal with good efficiency, as there is little in the circuit to dissipate input power when the diodes function as voltage-variable capacitors.

reference

1. Hayward and DeMaw, *Solid State Design for the Radio Amateur*, Chapter 3, ARRL, Newington, Connecticut.

ham radio

Factory Direct Only!

THE WORLDS FIRST

1800 CHANNEL FULLY SYNTHESIZED
COMPACT VHF FM MONITOR

AR-22
FACTORY DIRECT
PRICE \$125.00

This price in U.S. only

- FULL BAND COVERAGE
141.000-149.995 MHZ
5 KHZ Steps by digital switches.
- SLIM SIZE AND LIGHT-WEIGHT.
5¼"(H) x 2½"(W) x 1"(D)
7.1 oz with NiCd Battery Pack



- COMMERCIAL BAND TYPE (151-159 MHZ) IS ALSO AVAILABLE.
- CREDIT CARDS/MONEY ORDER OR ANY COMMERCIAL GUARANTEED CHECK...U.P.S. COD

ACE COMMUNICATIONS, INC.

2832-D Walnut Avenue, Tustin, California 92680

Phone (714)544-8281

FAST SCAN ATV

WHY GET ON FAST SCAN ATV?


- You can send broadcast quality video of home movies, video tapes, computer games, etc, at a cost that is less than sloscan.
- Really improves public service communications for parades, RACES, CAP searches, weather watch, etc.
- DX is about the same as 2 meter simplex — 15 to 100 miles.

ALL IN ONE BOX



TC-1 Transmitter/Converter
Plug in camera, ant., mic, and TV and you are on the air. Contains AC supply, T/R sw, 4 Modules below \$ 399 ppd

PUT YOUR OWN SYSTEM TOGETHER

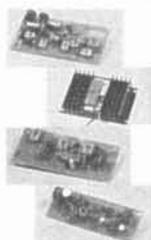

TXA5 ATV Exciter contains video modulator and xtal on 434 or 439.25 mHz. All modules wired and tested \$ 84 ppd

PA5 10 Watt Linear matches exciter for good color and sound. This and all modules run on 13.8 vdc. \$ 79 ppd

TVC-1B Downconverter tunes 420 to 450 mHz. Outputs TV ch 2 or 3. Contains low noise MRF901 preamp. . . \$ 49.50 ppd

PACKAGE SPECIAL all four modules \$ 225 ppd

FMA5 Audio Subcarrier adds standard TV sound to the picture \$ 25 ppd

SEND FOR OUR CATALOG, WE HAVE IT ALL

Modules for the builder, complete units for the operator, antennas, color cameras, repeaters, preamps, linears, video ider and clock, video monitors, computer interface, and more. 19 years in ATV.

Credit card orders call (213) 447-4565. Check, Money Order or Credit Card by mail.



P.C. ELECTRONICS

Maryann
WB6YSS

2522 PAXSON
ARCADIA, CA 91006

Tom
W6ORG



an accurate and practical AFSK generator

Putting the Exar XR-2206C IC to work in a circuit for RTTY enthusiasts

It's no secret that Amateur RTTY is enjoying a huge rate of growth and energy. Much of this interest can be directly traced to the newer video display type of TTY terminal and its quiet fascination. This same upsurge has caused many old-time RTTYers to dust off the mechanical machine and join in. Regardless of the type of terminal used, electronic or mechanical, the operator must provide the tone demodulation and FSK generator between his terminal and the radio gear. Most high-frequency stations use an AFSK audio input to an SSB transmitter, thus creating a need for a good AFSK generator. A great many circuits have been developed to fulfill this need, both simple and complex.

To fulfill my need for an AFSK generator, I looked over what had been designed and found either the 555 IC type oscillator or the crystal-controlled system. The former is not known for best stability with time and/or temperature, and the latter sometimes deserves a Nobel prize for complexity and would not fit the space requirements in my new converter.

Some time ago a data sheet came across my desk on a function generator in one IC package, made by Exar.* If that data sheet was to be believed, my answer was in the XR-2206C. After thoroughly testing the final circuit (fig. 1), I believe this AFSK generator is the most accurate and simply practical circuit possible considering stability, space requirements, and cost.

the XR-2206C IC

The device is a function generator designed for instrumentation and communications use. It will

operate from a single supply range of 10-26 volts, or a split supply of ± 5 to ± 13 volts. Its stability is excellent; drift rate is 20 ppm/ $^{\circ}$ C. It produces very-low-distortion sine, square, triangular, ramp, or pulse waveforms. And it's ready made for FSK operation with a built-in switch to select between two timing resistors for two-frequency output. In this FSK operation, the output is phase-continuous during frequency transitions, so distortion never results during switching (a common source of trouble for many of the simpler circuits).

AFSK generator

Fig. 1 shows the simplicity of the AFSK generator. It has six trimpots (four for setting frequency and two for IC controls). Supply voltage indicated is ± 12 volts. This was the supply in use for my converter, and it was borrowed to operate the AFSK generator as well.

Sinewave output from the XR-2206C is selected by connecting the 200-ohm resistor between pins 13 and 14. (If this resistor is removed, the output becomes triangular.) Pin 1 is used to set overall gain in this circuit by trimpot R5. The dc offset of an internal amplifier is set by trimpot R6 at pin 3. The 1- μ F tantalum capacitor bypasses an internal reference voltage at pin 10. The value isn't critical, but a tantalum type is definitely needed here.

stability considerations

The IC data sheet indicated that, for optimum temperature stability, the timing resistors should be as close as possible to 10k. The timing-capacitor value is then adjusted to yield the desired output frequency.

Working through Exar's formulas, a capacitor value of just less than 0.05 μ F is required, so I connected two 0.022- μ F caps in parallel; the result turned out to be just right.

*R-Ohm Corporation, Exar Integrated Systems, P.O. Box 4455, Irvine, California 92664.

By Garry A. Boldenow, K0SFU, Route 2, Box 153, Peabody, Kansas 66866

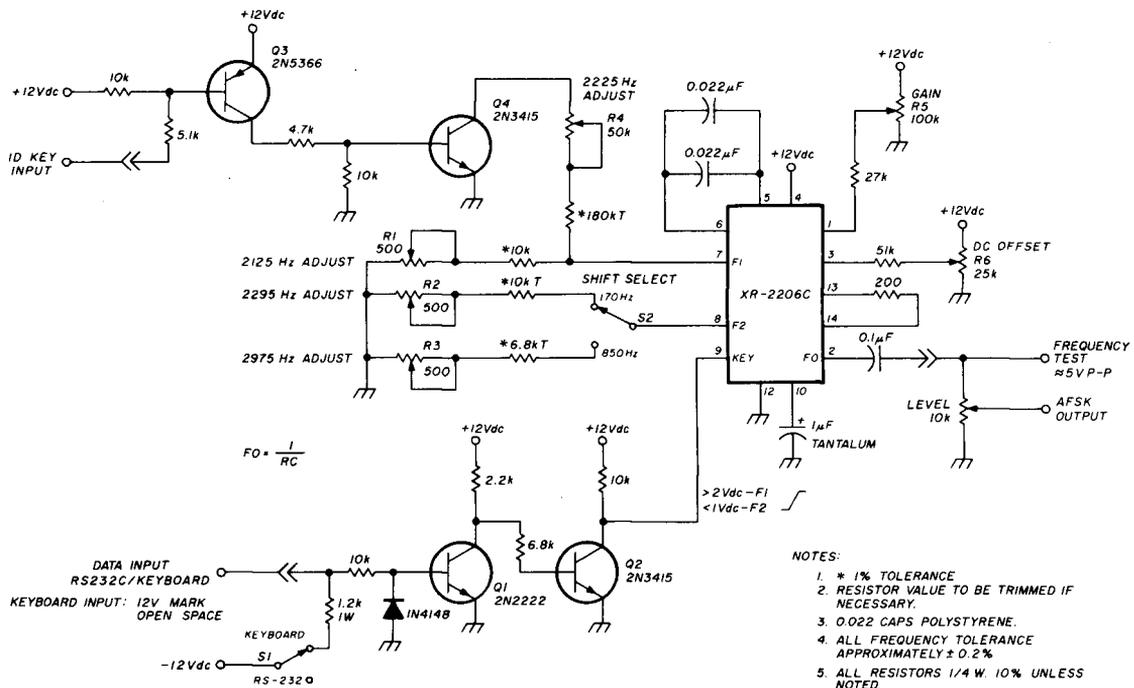


fig. 1. Schematic diagram of the AFSK generator. Circuit is built around the XR-2206C, which is a function-generator IC designed for instrumentation and communications use. This device has excellent frequency stability and low-distortion output. The circuit features optional CW IDENT circuit. Values of timing capacitors are critical; they must be polystyrene for maximum stability.

The timing-capacitor combination is connected to pins 5 and 6. These caps *must* be polystyrene for best stability. Do not use disc or Mylar caps in this application.

The timing-resistor networks connect to pins 7 and 8, with pin 7 being the F₁ frequency and pin 8 the F₂ frequency. We'll designate F₁ as mark (2125 Hz) and F₂ as space (2295 or 2975 Hz). Two resistors are selected by S2 for either 170-Hz or 850-Hz shifts. Obviously, if only 170 Hz shift is needed, delete the unnecessary components.

CW IDENT

I desired a CW IDENT feature, so I added Q3 and Q4. When the ID key input is pulled to ground or nearly so, R4 and 180-k resistor are in parallel with the 2125-Hz timing resistors, which shifts the output frequency upward 100 Hz for identification. Again, if this feature isn't needed, simply delete this little circuit.

Frequencies F₁ and F₂ (mark and space) are switched by the input at pin 9. If the level at pin 9 is greater than about 2 volts, F₁ is selected; if the level is less than about 1 volt, F₂ is selected.

input level translator

Q1 and Q2 act as an input level translator and

switch for either RS-232C or mechanical keyboard inputs. This feature allows the generator to be used by the computer world as well as by traditional equipment. S1 is opened for RS-232C input signals, which will switch between +10 and -10 volts. A keyboard should be wired as shown to +12 volts (or the A+ level being used), and S1 is closed. This action applies -12 volts through the 1.2 k resistor to the keyboard, which applies 24 volts at 20 mA across the keyboard contacts. A high level at the DATA INPUT will cause F₁ to be selected; a low level (or ground) will cause F₂ to be output.

construction

Construction of the AFSK generator can be by any method convenient to the builder. Layout is anything but critical. Leave room to trim the fixed timing resistors from pins 7 and 8 if necessary.

tune up

Tuning the generator will require a frequency counter and oscilloscope. Frequency setting could be done by applying the output through a known accurate tone demodulator and tuning for maximum output levels, but a counter sets frequency precisely. A scope will be needed to adjust for minimum distortion and best waveform.



Spring into summer with these sizzling titles.



ELECTRONIC COMMUNICATION (4th Edition)

by Robert L. Shrader

This popular volume presents, as simply as possible, the practical basic theory of radio and electronics. In wide use as a college and technical school text, **Electronic Communication** is based on the latest sample questions from FCC Commercial Operator License Exams and Amateur Exams, rearranged into a more effective teaching and learning order. The author also provides checkup quizzes every few pages to greatly reinforce learning. Its bold face type and multiple diagrams make it a pleasure to read. With careful, independent home study, this book will enable you to pass any FCC Amateur, Commercial Radiotelephone or Telegraph license exam including the radar and broadcast endorsements. 783 pages. ©1980.

□ MH-57138

Hardbound \$19.50

80 METER DXING

by John Devoldere, ON4UN

Going for 5 Band DXCC or just looking for a new DX challenge? This is positively the last word on working 80 meter DX. The author combines his many years of 80 meter operating experience with that of others to produce chapters on propagation, antenna systems, station equipment and international operating practices peculiar to 80 — all in a handy scrapbook format. What are the best times to be on? What's the best antenna? You'll find answers to these and many more 80 meter questions. 80 pages. ©1978.

□ HR-80M

Softbound \$4.50

AMATEUR SINGLE SIDEBAND

Originally by The Collins Radio Company

Ham Radio in cooperation with The Collins Radio Group has reprinted what many consider "the bible on Amateur single sideband". This softbound edition features an introduction to SSB, nature of SSB signals, excitors, RF linear amplifiers, SSB receivers, tests and measurements, and what comprises an Amateur SSB station. Absolutely THE finest publication available on SSB. 143 pages. ©1977.

□ HR-SSB

Softbound \$4.95

PRACTICAL ANTENNAS

From the folks at SCELBI, **PRACTICAL ANTENNAS** is not quite like any of the other ham antenna books. Written by a knowledgeable DX'er, this new book is chock-full of helpful hints and suggestions on the how-to's of putting up a super antenna system. Chapters include information on design and construction of practical Yagis, quads and wire type antennas. Inside you'll also find a complete bibliography of antenna articles from the popular amateur publications. Charts and tables are designed to eliminate all those tricky calculations. And, SCELBI has included a list of computer generated beam headings from major population centers to all the countries of the world. A new format, large easy-to-read text and durable vinyl cover make **PRACTICAL ANTENNAS** a "must" for every amateur library. ©1979.

□ SC-PA

\$9.95

Begin tuning by opening S1 and setting all trim-pots to mid range.

1. Open the ID KEY input, if used. Apply a positive-level (+10 or +12 volts) to the DATA INPUT point, then apply voltage power to the circuit. There should be some kind of waveform at pin 2 or at the output side of the 0.1- μ F coupling capacitor.

2. Initially, adjust R5 and R6 for best waveform. With a 12-volt supply, the output level will be around 5 volts p-p.

3. Next, adjust R1 throughout its range to determine if 2125 Hz can be set with the values as shown. If not, center R1 and trim the 10k fixed series resistor for about 2125 Hz; then readjust R1. If the 10k resistor value must be shifted by more than 5 per cent, trim the timing capacitors with other values. Try to keep the 2125-Hz resistors as close to 10k as possible. Once the mark frequency has been set, do not readjust R1 for any other frequency.

4. If the CW IDENT circuit has been added, ground the ID KEY input. Adjust R4 for 2225 Hz, trimming the 180k fixed resistor as required.

5. Next, either ground the DATA INPUT point or apply a negative voltage level.

6. Set S2 to the 170-Hz shift side and adjust R2 for 2295 Hz.

7. Trim the 10k fixed resistor with a 150k resistor to begin with, and trim from there.

8. Repeat the procedure with S2 in the 850-Hz position, adjusting R3 and trimming the 6.8k resistor as needed.

9. After all four frequencies have been initially adjusted, let the generator run for an hour or so, then carefully reset each frequency. A drift of only ± 2 Hz can be expected over a long-term period and over a wide temperature swing.

10. Carefully look at the output waveform and adjust R5 and R6 for the most perfect and smooth sine waveform possible. Set gain trimpot R5 for just less than maximum perfect waveform level.

closing remarks

Considering the space this generator consumes inside a typical RTTY converter cabinet, and the fact that its stability is better than 0.2 per cent over a wide temperature and time range (if 1 per cent resistor and 2.5 per cent polystyrene capacitors are used), this circuit offers much in terms of simplicity and accuracy.

ham radio

HAM RADIO'S BOOKSTORE
GREENVILLE, NH 03048

ham
radio's
bookstore

QUALITY THAT SPEAKS FOR ITSELF!

Hustler fixed station two meter gain antennas.


Hustler is the choice of those who know quality. Because we're known for precision engineering and electronic expertise.

Only the finest materials are used to make a Hustler amateur antenna. And each model is the result of years of design excellence.

From easy and precise assembly to outstanding long-range transmitting and receiving, Hustler quality speaks for itself. See your dealer and find out why!

HUSTLER INC.

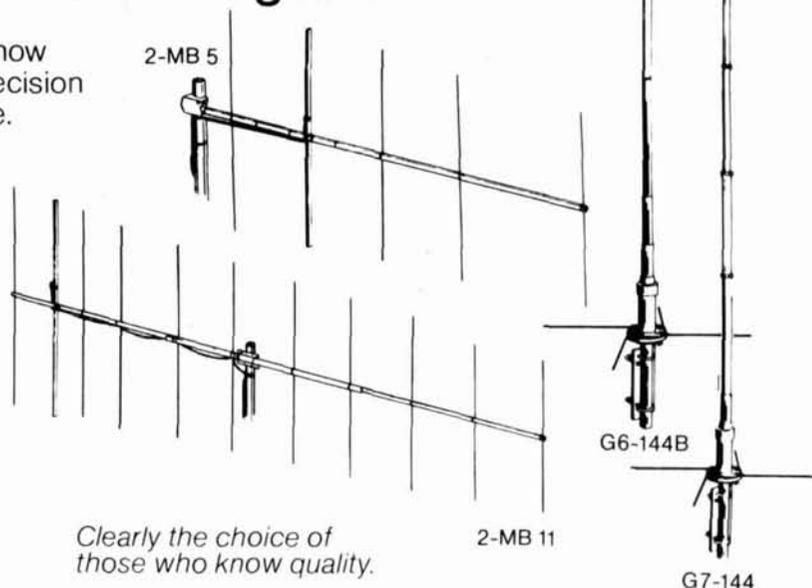3275 North B. Ave., Kissimmee, Florida 32741



Clearly the choice of those who know quality.

NEWCOMER OR OLD PRO . . . ALPHA POWER IS YOUR KEY TO A BIG SIGNAL

ALPHA/VOMAX can boost the "talk power" of any rig up to ten times or more. The new SBP-4 split band speech processor uses the only system more effective than rf clipping — AND distortion is extremely low so your voice sounds natural. Under tough conditions VOMAX can help as much as most linears. Combine VOMAX with a good linear and WOW! It's simple to install and operate with any rig.



ALPHA 374A is a heavy-duty "rock crusher" . . . a full kilowatt (2+KW PEP), No Time Limit, all band, NO TUNE UP desk top linear amplifier. It's a no-compromise ALPHA with a TWO YEAR FACTORY WARRANTY.

Other superb ALPHA s include the "Ultimate LINEAR" ALPHA 77Dx and the new ALPHA 78, which combines NO-TUNE-UP maximum legal power, No Time Limit, and high speed (vacuum relay) CW break-in. Call or write your dealer or ETO direct for illustrated literature on all ALPHA products.

ETO EHRHORN TECHNOLOGICAL OPERATIONS, INC.
P.O. BOX 708, CANON CITY, CO 81212
(303) 275-1613

NEW FROM GLB

A complete line of **QUALITY 50** thru 450 MHz **TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. 4 pole crystal filter is standard. Use with our **CHANNELIZER** or your crystals. Priced from \$69.95. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from \$29.95.

SYNTHESIZER KITS from 50 to 450 MHz. Prices start at \$119.95.

Now available in **KIT FORM** — GLB Model 200 **MINI-SIZER**.

Fits any HT. Only 3.5 mA current drain. Kit price \$159.95 **Wired and tested. \$239.95**

Send for **FREE 16 page catalog**.

We welcome **Mastercharge** or **VISA**

GLB ELECTRONICS
1952 Clinton St., Buffalo, N. Y. 14206

S-LINE OWNERS ENHANCE YOUR INVESTMENT

with

TUBESTERS™

Plug-in, solid state tube replacements

- S-line performance—solid state!
- Heat dissipation reduced 60%
- Goodbye hard-to-find tubes
- Unlimited equipment life

TUBESTERS cost less than two tubes, and are guaranteed for so long as you own your S-line.

SKYTEC

Box 535
Talmage, CA 95481

Write or phone for
specs and prices.
(707) 462-6882

FACSIMILE

**COPY SATELLITE PHOTOS,
WEATHER MAPS, PRESS!**

The Faxes Are Clear — on our full size (18-1/2" wide) recorders. Free Fax Guide.

TELETYPE

RTTY MACHINES, PARTS, SUPPLIES

ATLANTIC SURPLUS SALES (212) 372-0349
3730 NAUTILUS AVE. BROOKLYN, N.Y. 11224

DIPOLE ANTENNA CONNECTOR



HYE-QUE (HQ-1) dipole connector has coax 50-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feeding. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealer or \$5.95 postpaid. Companion insulators \$1.25/pr.

BUDWIG MFG. Co. PO Box 829, Ramona, CA 92065
Ca. Res. add 6% Sales Tax

notes on the EIMAC 5CX1500A power pentode

Some operating tips on the use of this tube in ham gear

Ask any experienced ham to list the tubes most likely to be used in a linear amplifier in the Amateur service, and chances are that the 5CX1500A won't be mentioned.

And, small wonder. In this day of zero bias, high-mu triodes, the 5CX1500A doesn't really seem to be the ideal tube for ham use. It's expensive (about \$500); its socket is expensive and, in this day of single-power-supply-tubes the 5CX1500 requires *three* power supplies plus filament voltage.

the case for the 5CX1500A

So, why even consider it here? For two reasons. First, at least one manufacturer of high-power linear amplifiers, Tempo, uses this tube in their Model 4K. The typical 4K owner may not know enough about his final for his own peace of mind. Second, this tube is rather common in the broadcast service, and some of these tubes, with reduced emission, have become available at reasonable prices at swapfests and such.* It is for these reasons that this article is presented.

background

The 5CX1500A was designed by EIMAC about a dozen years ago at the request of an American manufacturer of fm transmitters for the 88-108 MHz broadcast band. The need was for a final amplifier or driver tube that would operate in the 2-3 kW power range, Class B or C service, with good stability and ruggedness, a reasonable life expectancy (about 8000 hours in continuous commercial service [CCS])

*Another source of these and other high-power tubes is your local fm broadcast or TV station. The tubes are replaced after a specified number of operating hours and in many cases have a lot of life in them, especially when used in the Amateur service. Contact your local station and talk to the engineer in charge. **Editor.**

and high efficiency. The original 5CX1500 was the result.

There are some problems, of course. The '1500A is a beam-power pentode, and because of its parameters, which were dictated by the specifications listed above, the tube is very difficult to construct. As a result, EIMAC is still the only manufacturer of the tube in the world. Couple this with the fact that every major manufacturer of broadcast fm transmitters in this country uses the 5CX1500A in all their transmitters designed for this power level, and you can guess the rest. The tube is not always readily available. As of this writing, however, that situation has not existed for some months.

early tube problems

Several years ago the assembly line for the 5CX1500A was moved from EIMAC's main plant in California to a new facility in Salt Lake City, Utah. Shortly thereafter, problems arose. Tube life in the field began to drop, particularly in rf driver service, but later in all fm broadcast service. Tubes began to lose emission to the point where they had to be replaced after about 3000-4000 hours. EIMAC and the broadcast equipment manufacturers began to re-search the problems, and two differing causes began to emerge. There was one common denominator: the filament was being "poisoned" by gas.*

First it was discovered that the tube, especially when used in rf driver service (CCS), was being loaded much too lightly. This action resulted in high rf circulating currents in the tube, particularly across the aluminum oxide insulating ring between the suppressor ring and the anode. As a result undue heating occurred, which caused minute cracking of the ring. These cracks are not visible to the naked eye, except through the use of the special dye applied to the ring.

Second, investigators found that, on tubes made between mid-1975 and early 1979, the metal alloy used in the construction of the screen grid emitted

*An interesting sidelight on the problem of contamination of thoriated tungsten filaments by gas is discussed in reference 1. **Editor.**

By Arthur Reis, K9XI, 8510 Sunset, Wonder Lake, Illinois 60097

excessive levels of carbon-monoxide gas, which is lethal to your typical 5CX1500A cathode. EIMAC corrected that problem early in 1979, and tubes manufactured after that date show no ill effects from that quarter.

operating tips

Now, in practical terms, what does this all mean to present and potential users of the 5CX1500A? Here are some tips on its operation that might help.

1. Load the tube as heavily as possible, consistent with the ability of your power supply to deliver the extra current. If your plate impedance is over 6000 ohms, it's too high! Reduce this impedance as much as possible by decreasing plate voltage and increasing current to reduce circulating rf currents in the tube.

2. If your tube is beginning to go "soft," determine if the problem is loss of cathode emission. To do this, record your present current drain on all tube elements that show current, and compare them to your observations when the tube was "fresh." If *all* currents are down, then the problem is low cathode emission caused by poisoning (contamination). These currents must be determined with drive power applied. Dc values alone will tell you nothing, since at radio frequencies the peak current drawn by the cathode may be 2-3 amperes. It's the inability of the cathode to deliver *that* amount of current that causes the tube to be considered "soft," no matter what the dc values may be.

3. Do *not* try to increase the cathode voltage above 5.1 volts to increase emission. For every 1/4 volt the filament is increased over its specified value, expect your tube life to drop in half (i.e., 5-1/4 volts, 4000 hours on an original 8000-hour tube; 5-1/2 volts, 2000 hours, etc.). Remember, this is a "carburized" thoriated tungsten filament. At the present state of the art, if the filament opens up, it can't be rebuilt.

4. If the tube is too "soft" to live with but seems to be OK otherwise (no short circuits), it can be rebuilt for about half the cost of a new tube. If indeed the cathode has been contaminated as determined in 2. above, you can ship it to Econco Broadcast Service, 1302 Commerce Avenue, Woodland, California, 95695. Unlike the process used in rebuilding other tube types, rebuilding the 5CX1500A doesn't usually require replacement of its grids. Instead, as EIMAC informs me, a process called "recarburization" is used. The tube seal is broken and a gas with a high carbon content, such as methane, is admitted. The gas-loaded tube is then fired in an oven, or its filament run at 120 percent voltage for a few seconds, during which time a new carbon coating is deposited

onto the cathode. The tube time is then re-evacuated and resealed. Generally, if the tube has no other problems, the renewability rate is in the 80-90 percent range. If your tube loses here, you pay nothing more than shipping charges one way. By the way, this rebuilding process can be done more than once, thereby increasing the life of the tube in your rig.

5. If your 5CX1500A develops a short circuit, it will generally be from cathode to control grid. That's a pretty safe statement, considering the fact that the control grid is located a mere four *mils* from the cathode (the grid wire mesh is one mil thicker than that!). As the tube ages, the cathode can get brittle, and a strand from the filament may break away and fall across the grid.

Don't dismiss the idea of burning out the short in this case. I've heard of this happening several times, and a car battery is ideal for the purpose. If the short does not disappear, you'll have to admit that, with a little polishing and a walnut base, the tube makes a nice looking award for "Ham of the Year" at your local radio club. (This is particularly true of tubes manufactured before 1980, which are silver plated. EIMAC has changed the outer plating of the tube to nickel for cost reasons. There is no noticeable electrical effect on the tube.)

summary

The 5CX1500A tube may not be the best of all possible worlds for linear amplification in the Amateur service. However, for those who want a stable, very conservative amplifier for up to, say, 225 MHz, or for those who already are using this tube in such an amplifier, I hope this article has shed some new light on a tube that few Amateurs seem to know much about. The interested reader is referred, for further information, to "The Care and Feeding of Power Grid Tubes," by EIMAC. Data sheets for the 5CX1500A are also available from EIMAC.*

acknowledgments

My thanks to Ken Atkinson at EIMAC/Salt Lake City, Ed Numerych at EIMAC/Chicago, Dave Gilden, formerly of CECO, Ray Shurtz at ECONCO, and Bill Hoyt, Lou Pifer, and Bob Gorjance at Harris Corporation, for their help in providing information for this article.

reference

1. Alf Wilson, W6NIF, "Rejuvenating Transmitting Tubes with Thoriated-Tungsten Filaments," *ham radio*, August, 1978, page 80.

*EIMAC division of Varian, 301 Industrial Way, San Carlos, California 94070.

ham radio

Low Cost...High Performance

DIGITAL MULTIMETER



\$99.95 WIRED

Low cost, high performance, that's the DM-700. Unlike some of the hobby grade DMMs available, the DM-700 offers professional quality performance and appearance at a hobbyist price. It features 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch high LED display, with automatic decimal placement, automatic polarity, and overrange indication. You can depend upon the DM-700, state-of-the-art components such as a precision laser trimmed resistor array, semiconductor band gap reference, and reliable LSI circuitry insure lab quality performance for years to come. Basic DC volts and ohms accuracy is 0.1%, and you can measure voltage all the way from 100 μ V to 1000 volts, current from 0.1 μ A to 2.0 amps and resistance from 0.1 ohms to 20 megohms. Overload protection is inherent in the design of the DM-700, 1250 volts, AC or DC on all ranges, making it virtually goof proof. Power is supplied by four 'C' size cells, making the DM-700 portable, and, as options, a nicad battery pack and AC adapter are available. The DM-700 features a handsome, jet black, rugged ABS case with convenient retractable tilt bail. All factory wired units are covered by a one year limited warranty and kits have a 90 day parts warranty.

Order a DM-700, examine it for 10 days, and if you're not satisfied in every way, return it in original form for a prompt refund.

Specifications

DC and AC volts:	100 μ V to 1000 Volts, 5 ranges
DC and AC current:	0.1 μ A to 2.0 Amps, 5 ranges
Resistance:	0.1 Ω to 20 megohms, 6 ranges
Input protection:	1250 volts AC/DC all ranges fuse protected for overcurrent
Input impedance:	10 megohms, DC/AC volts
Display:	3 1/2 digits, 0.5 inch LED
Accuracy:	0.1% basic DC volts
Power:	4 'C' cells, optional nicad pack, or AC adapter
Size:	6"W x 3"H x 6"D
Weight:	2 lbs with batteries

Prices

DM-700 wired + tested	\$99.95
DM-700 kit form	79.95
AC adapter/charger	4.95
Nicad pack with AC adapter/charger	19.95
Probe kit	3.95

TERMS: Satisfaction guaranteed or money refunded, COD, add \$1.50. Minimum order \$6.00. Orders under \$10.00, add \$3.75. Add 5% for postage, insurance, handling. Overseas, add 15%. NY residents, add 7% tax.



600 mHz COUNTER



\$99.95 WIRED

The CT-70 breaks the price barrier on lab quality frequency counters. No longer do you have to settle for a kit, half-kit or poor performance, the CT-70 is completely wired and tested, features professional quality construction and specifications, plus is covered by a one year warranty. Power for the CT-70 is provided by four 'AA' size batteries or 12 volts, AC or DC, available as options are a nicad battery pack, and AC adapter. Three selectable frequency ranges, each with its own pre-amp, enable you to make accurate measurements from less than 10 Hz to greater than 600 mHz. All switches are conveniently located on the front panel for ease of operation, and a single input jack eliminates the need to change cables as different ranges are selected. Accurate readings are insured by the use of a large 0.4 inch seven digit LED display, a 1.0 ppm TCXO time base and a handy LED gate light indicator.

The CT-70 is the answer to all your measurement needs, in the field, in the lab, or in the ham shack. Order yours today, examine it for 10 days, if you're not completely satisfied, return the unit for a prompt and courteous refund.

Specifications

Frequency range:	10 Hz to over 600 mHz
Sensitivity:	less than 25 mv to 150 mHz less than 150 mv to 600 mHz
Stability:	1.0 ppm, 20-40°C, 0.05 ppm/°C TCXO crystal time base
Display:	7 digits, LED, 0.4 inch height
Input protection:	50 VAC to 60 mHz, 10 VAC to 600 mHz
Input impedance:	1 megohm, 6 and 60 mHz ranges 50 ohms, 600 mHz range
Power:	4 'AA' cells, 12 V AC/DC
Gate:	0.1 sec and 1.0 sec LED gate light
Decimal point:	Automatic, all ranges
Size:	5"W x 1 1/2"H x 5 1/2"D
Weight:	1 lb with batteries

Prices

CT-70 wired + tested	\$99.95
CT-70 kit form	75.95
AC adapter	4.95
Nicad pack with AC adapter/charger	9.95
Telescopic whip antenna, BNC plug	7.95
Tilt bail assembly	3.95

ramsay electronics

BOX 4072, ROCHESTER, N. Y. 14610

PHONE ORDERS CALL

(716) 586-3950 (716) 381-7265

base-loaded vertical antenna for 160 meters

No room for a
160-meter beam?
Try this
vertical antenna
which can be
easily made from
readily available materials

Much has been written and discussed on the best antenna for 160 meters. The most popular solution seems to be to tie the ends of an 80-meter antenna together and feed the system on 160 meters with an antenna matching network. Some Amateurs string up an inverted L antenna. Both work fine for local contacts, but if you really want to work across the country, the vertical antenna is best.

the case for a vertical antenna

Several 160-meter enthusiasts use phased vertical antennas. Their signals are outstanding all year around compared with signals from other antennas. For those who don't have room for a beam, the top-loaded vertical is the next best. The loading coil should be wound with no. 10 AWG (2.6 mm) wire. It requires a long coil and an extended tube for adjustments. I tried such an antenna, but the assembly swayed back and forth like a pendulum, and the nylon guys would not remain tight enough to hold it. After the coil broke off, I experimented with a base-loaded vertical.

base-loaded vertical

I was surprised that my signals seemed to be equally good, but not before some testing of the wire size used on the base coil. My vertical uses a 32-foot (9.8-meter) length of aluminum irrigation tubing, which is 2 inches (50 mm) in diameter. (It cost \$20.00.) The tube was set on a beer bottle for an insulator and guyed with nylon rope. This assembly was backed up by burying a 6-foot (1.8-meter) length of 4 × 4 lumber into the ground and using insulators and wood blocks to secure the tube to it (**fig. 1**).

To resonate the tube to 160 meters, a series capacitor and coil were first tried. However, I was told it would be better to just use the coil. First tried was a wire coil, but later a coil made from 3/16-inch (5-mm) diameter copper tubing was substituted, and the signal increased by 1 dB.

coil construction

The inductance was wound with 3/16-inch (5-mm) diameter copper tubing which cost \$9.75 for a 50-foot (15.25-meter) coil. I used a 4-inch (102-mm) diameter pipe as a mandrel and wound a coil of forty turns.

Next three pieces of plastic were cut 1 inch (25.4 mm) wide and 1/4 inch (6.5 mm) thick for the length of the coil. Holes were drilled in these strips with a drill just over 3/16 inch (5 mm), so that the copper would slide through it easily. The first hole was 1/4 inch (6.5 mm) from the end.

The holes were cut with a drill sharpened like a sheet metal drill so that it did not shatter as it came through the plastic. A small hole could have been drilled, then a large drill put through half way on each side. That takes patience. Once the pieces are snaked onto the coil and spaced, they are treated with coil dope. The coil was rugged enough to be mounted on insulators and put into a wooden dog house at the base of the antenna.

By Ed Marriner, W6XM, 528 Colima Street, La Jolla, California 92037

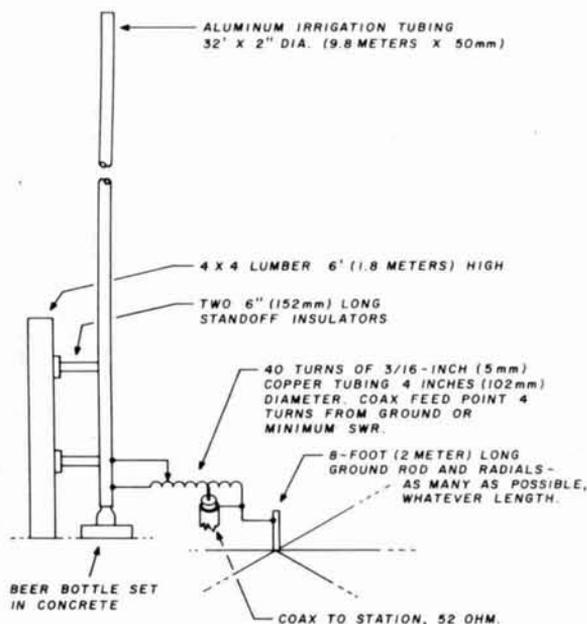


fig. 1. Construction details of a base-loaded vertical antenna for 160 meters. Antenna performs as well as a top-loaded affair and is much more stable and easier to construct. Use as many radials as possible in the ground system.

tune up

Antenna tuning was accomplished by leaving the feeder off and grid dipping the coil with it all in place. The coil was then tapped for resonance at 1820 kHz. Wide copper straps can be formed around the 3/16-inch (5-mm) copper and soldered once the proper place is found. The next step is to vary the tap for the 50-ohm feeder from the bottom of the coil for minimum SWR. Mine came out at the fourth turn up from the bottom. (This will depend on your ground system.) I used an 8-foot (2-meter) rod driven into the ground at the antenna base and four or five radials of various lengths pushed into the grass. None are over 30 feet (9 meters) long, but make them as long as you can and use as many as possible. The more the better on 160 meters.*

performance

We have a daytime 160-meter net here in California, and records are kept of signal strengths up and down the coast. At 11 AM Sunday mornings Santa Barbara checks in with signal reports. I can say this antenna receives and sends equally as well as my old top-loaded affair. I've worked the East Coast with it and am pleased to report that it is more stable and easier to construct. All in all, it seems like the best answer to many 160-meter antenna problems — if you can't have a phased array.

*Or on any frequency. Editor.

ham radio

QUALITY CRYSTALS

In Welded Holders

Quick delivery...

Emergency 48 hour service


Visa or MasterCharge orders welcome!
Call or write Cal Crystal NOW!



CAL CRYSTAL

California Crystal Lab., Inc.
1142 North Gilbert Street
Anaheim, California 92801
(714) 991-1580

WANTED FOR CASH

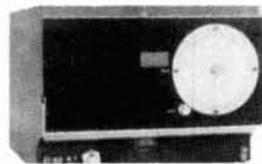


490-T Ant. Tuning Unit
(Also known as CU1658
and CU1669)



618-T Transceiver
(Also known as MRC95,
ARC94, ARC102, or VC102)

4CX150
4CX250
4CX300A
4CX350A

4CX1000
4CX1500
4CX3000
4CX5000

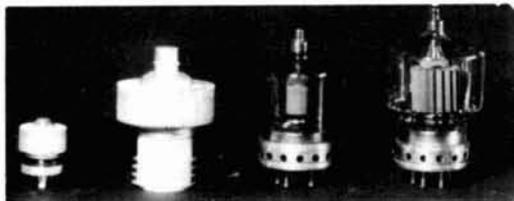

4CX10,000 4-65 4-250 4-1000
5CX1500 4-125A 4-400 304TL

Other tubes and Klystrons also wanted.

Highest price paid for these units. Parts purchased. Phone Ted, W2KUW collect. We will trade for new amateur gear. GRC106, ARC105, ARC112, ARC114, ARC115, ARC116, and some aircraft units also required.

DCO, INC.

10 Schuyler Avenue
Call Toll Free
800-526-1270

No. Arlington, N. J. 07032
(201) 998-4246
Evenings (201) 998-6475

digital capacitance meter

Easy to build
digital capacitance meter
for the home shop
features ranges from
1000 pF to 100 μ F

Amateurs who build or service electronic equipment sooner or later encounter the situation where replacing a capacitor with a "larger" one produces the wrong results: power supply ripple worsens or the time constant of a timing circuit decreases when it should increase. Highpass or lowpass audio might have their actual 3-dB rolloff points at 200 Hz instead of the intended 300-Hz point. Such differences often occur because the actual value of the capacitor used is different from its marked value. The best performance of narrow bandpass filters and notch filters is obtained when matched capacitors of exactly the same value are used. There are many good "100-for-a-dollar" capacitor buys available, but they often included unmarked or house-numbered units. Those 25-cent, 68- μ F capacitors I bought at a hamfest were actually 6.8 μ F — the reason, no doubt, they were only 25 cents!

Capacitors are among the most common components used in electronics. Most users assume that the value marked on the capacitor is its actual value; specifications simply guarantee a minimum value. Most electrolytics, for example, are specified to be within +80 to -20 per cent of their indicated value. There are a few that are within ± 10 per cent of their marked value; some small capacitors are available with 1 per cent and 5 per cent tolerances. The true value of a capacitor is not important in some cases, such as audio bypass applications, while in other applications the capacitance must be accurately known to produce the desired results.



The digital-capacitor meter presented in this article was built to preclude the type of problems described above. It measures capacitors from 0.001 μ F to 999 μ F in six ranges, with accuracy of about 1 per cent. The three-digit display has the decimal point correctly positioned as the ranges are switched. The circuit uses low-cost components which are readily available. It requires no difficult adjustments for reliable operation and is easy to duplicate with the printed circuit board layout shown. The meter requires about 100 mA from a 5-volt regulated source, so it lends itself to battery operation if desired. The circuit includes a flashing overflow indicator.

circuit description

The circuit is based upon a digital counter that counts a reference oscillator. The input to the counter is gated by the C_x monostable which has its period determined by the capacitor to be measured.

By Marion D. Kitchens, K4GOK, 7100 Mercury Avenue, Haymarket, Virginia 22069

Construction of the short lead adapter.

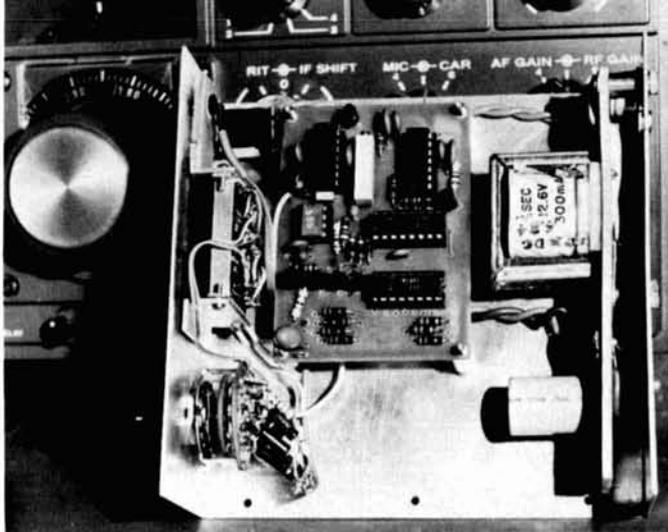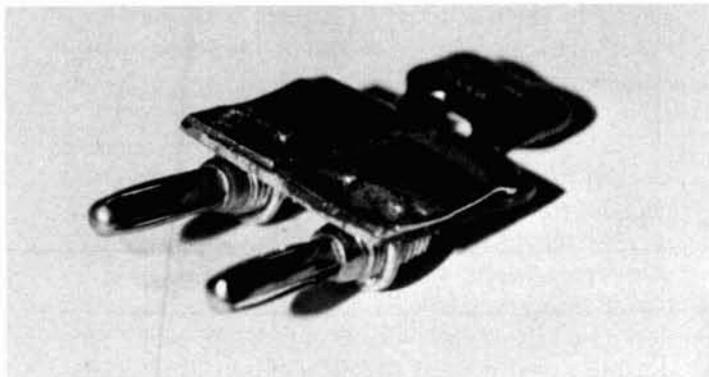


An interior view showing arrangement of the display, circuit board, power supply, and range switch. This was a prototype circuit board which has its overflow circuit mounted below the main board.

Digi Cap



Two different meters showing suggested range switch labeling for right-hand decimal displays per the text (on top) and left-hand decimal displays. The unit with the small display (top) was used to develop the circuit. The bottom unit was built by WA4RVN to verify the circuit reproducibility and performance consistency.

Closeup view of the point-to-point wired power supply. The 7805 voltage regulator is snugged beneath the 1000- μ F filter. Yes, the capacitor was measured before use. Would you believe 998 μ F?

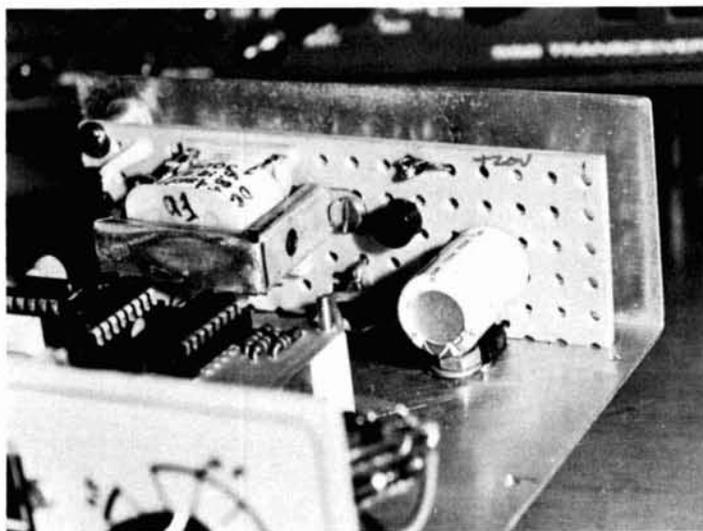

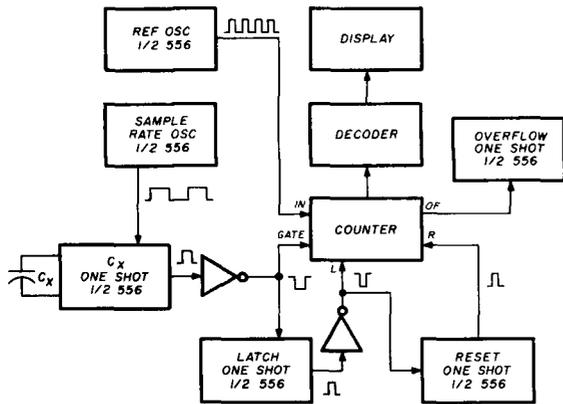


fig. 1. Functional block diagram of the digital capacitance meter. The meter is based upon the 14553 counter. The other ICs provide the necessary gating for the oscillators and display functions.

The functional block diagram is shown in fig. 1. About twice a second, the sample rate oscillator triggers the C_x monostable circuit. This monostable output is inverted and applied to the counter control gate. The duration of this control gate input is directly dependent upon the value of the capacitor being measured. If the reference oscillator input to the 14533 IC counter is at the proper frequency, the resulting display will indicate the value of the capacitor. One half of a 556 dual timer serves as the sample rate oscillator, while another 556 dual timer is used as the C_x monostable and reference oscillator.

The 14553 counter chip contains all the circuitry to count and multiplex three digits. It has built-in latch and reset functions and an input control gate. The counter chip's BCD output is applied to a single seven-segment decoder which drives the multiplexed LED displays. The required latch and reset functions are provided by another 556 dual timer with each of its sections operating in the monostable mode. The latch signal is applied to the 14553 at the end of the input gate enable period to store and display the accumulated count. Immediately thereafter the reset signal is applied. The 14553 holds the outputs for the displays, even though the internal counters have been reset, until the latch signal is again low. The latch signal goes low only after the capacitor value has been measured again. This produces a constant or steady display that does not flicker or count up to the final value.

The circuit timing diagram is shown in fig. 2. The overflow signal from the 14553 is applied to one half of a 556 dual timer to provide an overflow indication. The timer is run as a monostable to produce a flashing LED overflow indicator. Fig. 1 shows wave forms at significant locations and indicates the direction of information flow in the circuit. The complete schematic diagram is shown in fig. 3.

Construction is uncomplicated when using the printed circuit board. Fig. 4 shows the location of components on the board, while fig. 5 shows the circuit board foil pattern. Careful examination of fig. 4 will reveal the location of the numbered and lettered points to be wired to the display and the range switch. These points are shown on the schematic for easy reference. Switch wiring is shown in fig. 6. Points X, Y, and Z are not used.

The circuit uses a common-anode multiplexed display. The seven 82-ohm resistors near the 7446 decoder are the recommended value for displays that require around 10 mA per segment. The suggested value for displays rated at 5 mA per segment is 150 ohms. These values can be varied to achieve the desired display brightness. One unit was built without the seven current limiting resistors (to achieve the maximum brightness) and has worked without any LED burnout problems.

None of the circuit component values are critical, but best performance can be obtained with a good quality capacitor, preferably plastic, for the reference oscillator. This particular capacitor is the 0.001- μ F capacitor located near the 100k pot and connected to pins 2 and 6 of U2. Q1 is used to boost the current-handling capability of the C_x monostable (U2) and should have low capacitance and a power rating of $\frac{1}{2}$ to 1 watt. A 2N3906 will work with good results. Transistors Q1, Q4, Q5, and Q6 are PNP transistors, while Q2, Q3, and Q7 are NPN transistors; 2N3906s and 2N3904s can be used, respectively. Q4, Q5, and Q6 should be installed so that their emitters go to the 5-volt land, bases go to the 1 kilohm resistors, and their collectors to the anodes of the display. The overflow LED is connected with its anode to point F on the circuit board and the cathode to ground.

A well-regulated, 5-volt power supply capable of 100 to 150 mA is required. Fig. 7 shows a schematic for a suitable supply. Point-to-point wiring on a insulated board is an easy way to build the supply.

Care should be taken to keep the wiring between Q1, the range switch, and the C_x input jacks as short as possible and away from the 60-Hz ac line.

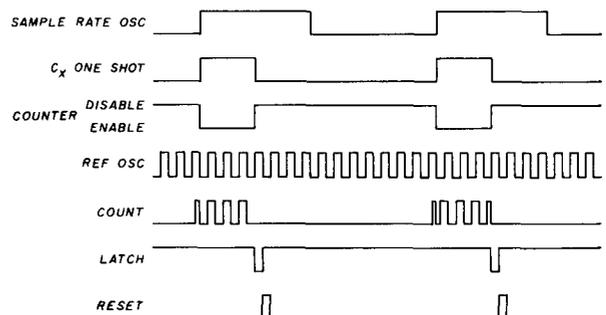


fig. 2. Timing diagram of signals in the capacitance meter.

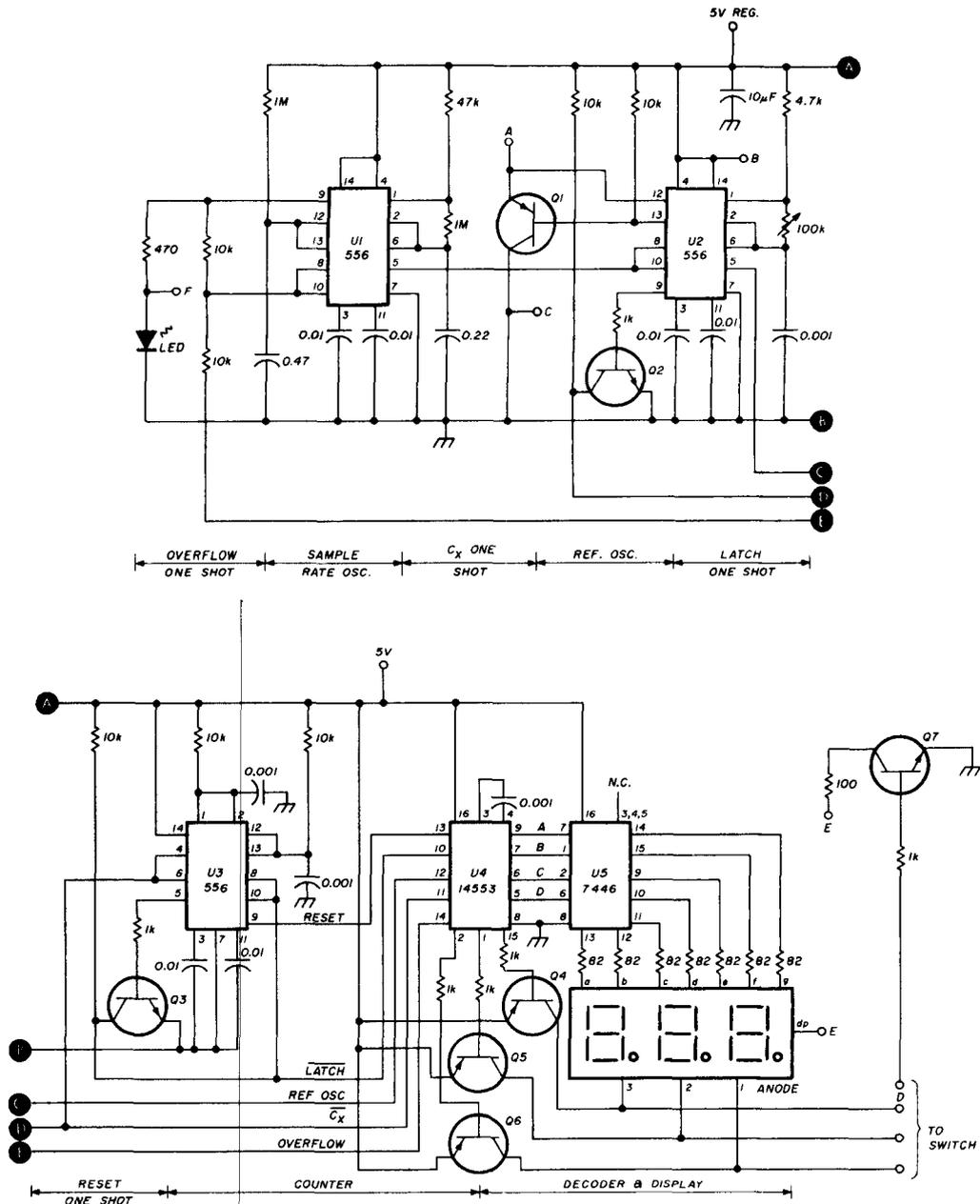


fig. 3. Complete schematic diagram of the digital capacitance meter. Suggested types for the transistors are given in the text. The current requirement of the meter is approximately 100 mA, small enough that a battery supply can be used for field use.

checkout and calibration

The circuit board should be completed and all wiring connected to the display, overflow indicator, and range switch before starting checkout. Make sure that the power supply is delivering 5 volts and is properly connected to the circuit board. At power turn on, the display should light and the overflow indicator should flash once. The display should show 000 or 001 with no connection at the C_x input. With a short across the C_x input, the display should show a number, say 433, and the overflow indicator will flash

continuously. This number should not change when the range switch is moved to other positions. The display should show a number of 000 to 002 with the range switch in position 1 (see fig. 6) and no connection at the C_x input. An unsteady count ranging from 000 to about 060 indicates that the meter is picking up stray 60 Hz. If this happens, try redressing or re-routing the wiring between the circuit board, range switch, and C_x input jacks. K4ZKU found that reversing the ac line cord at the wall outlet would help with such a situation. A simple test of U5, the display, and

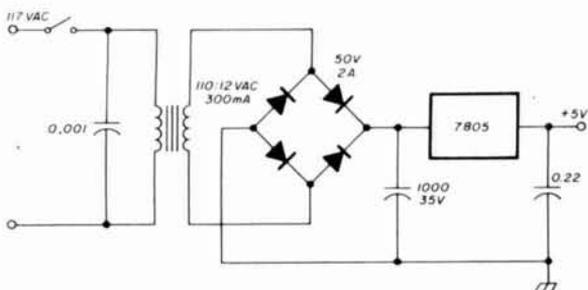


fig. 7. Schematic diagram of a small power supply suitable for home station use of the capacitance meter.

to build and it has been a time- (and agony-) saver around the ham shack. I hope that others who enjoy building and experimenting will find it to be the same. I will offer film negatives (or positives) so that builders can make their own circuit boards. Correspondence regarding the meter will be answered if an SASE is included.

table 1. Switch positions for various measurement ranges showing display and associated capacitance value. In switch position 1, a display of 1.50 indicates a capacitance of 0.015 μ F (1500 pF), a reading of 2.20 indicates a capacitance of 0.002 μ F (2200 pF), etc.

switch position	display	capacitance	range
1	1.00	0.001	1000 pF (1 nF)
2	10.00	0.010	10k pF (10 nF)
3	100.00	0.100	100k pF (100 nF)
4	1.00	1.000	1 μ F
5	10.00	10.000	10 μ F
6	100.00	100.000	100 μ F

acknowledgments

Several hams have been of great assistance in developing the digital capacitor meter, in particular WA4RVN, K4ZKU, and W4PVA. K4ZKU provided valuable information on driving the display to full brightness, and W4PVA helped with the information on the 14553 counter chip without which the project could not have been undertaken. WA4RVN built his meter according to this article to verify the construction and checkout notes.

ham radio



FOX-TANGO CORP.

Box 15944H, West Palm Beach, FL 33406

Visa/MC welcomed. Money back if not satisfied.

8-POLE FILTER BANDWIDTHS IN STOCK

CRYSTAL FILTER	CW (Hz)						SSB-AM (kHz)				
	125	250	400	500	600	800	1.8	2.1	2.4	6.0	8.0
YAESU	\$55 EACH										
*FT-101/F/FR-101	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
*FT-301/FT-7B/620	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
*FT-901/101ZD/107	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
FT-401/560/570	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
FT-200/TEMPO 1	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
KENWOOD	\$55 EACH										
*TS-520/R-599	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
*TS-820/R-820	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
HEATH	\$55 EACH										
ALL HF	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
DRAKE	FOR PRICES SEE NOTES										
R-4C	GUF-1 Broad 1st IF Superior Shape Factor/Ult Rej \$65										✓
	GUF-2 Narrow 1st IF										✓
	2nd IF										✓
	GUD Product Detector										✓
	+ pcb w sw relays										\$90
	Plug in type										\$65
	pcb w relay double balanced type										\$30
COLLINS:	SPECIAL \$125 EACH										
75S-3B/C	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
	EQUALS OR EXCELS \$400 COLLINS UNIT										

*DIODE SWITCHING BOARDS available to permit 1, 2 or more filters than those for which manufacturer provides room. SPECIFY make and model.

Single-filter type: \$12 Airmail postpaid

Dual-filter type: \$21 Airmail postpaid

Florida residents add 4% (sales tax) (FOREIGN ADD \$3 per filter)




BROCHURE ON REQUEST
Dealer Inquiries Welcomed



New Improved Adhesive Mount for the 2 Meter Avanti Mobile Antenna.

Mounts on glass — no holes!

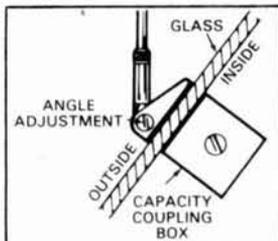- Receives and transmits through glass.
- Superior performance equivalent to 5/8 wave.
- Superior radiation full Omni-Directional.



It's easy to install — No holes to drill, no magnet to scratch the paint, no clamps. Uses an especially developed silicone adhesive that secures antenna to window. The capacity coupling box is simply attached with a special adhesive tape to inside of window. Worried about crimping or corroding coaxial cables? It's all inside and out of sight.

Models also available for 220 MHz and 450 MHz.

See Avanti's other new mobile and base antennas. Write for new catalog today. Send 50¢ for handling and postage.

avanti® antennas

Avanti Research and Development, Inc.
340 Stewart Ave., Addison, IL 60101 (312) 628-9350
In Canada: Lenbrook Ind., Scarborough, Ontario MIH IH5

"Summer Book Sale"

WORLD TIME CALCULATOR **NEW!**

Here's a very handy operating aid for your ham shack. To use it, you locate your local time, move the dial to your local time zone and voila — you know the time anywhere around the world. Besides determining time, you get a full explanation of many confusing terms such as: mean solar time, ephemeris time, atomic time, and more. Indispensable aid for both the contester and DX'er. ©1980.

VG-TC

\$2.95



SAVE TIME & MONEY!

Shop By Mail

RADIO FREQUENCY INTERFERENCE by ARRL

Finally! A new book that helps you understand RFI. Here's a convenient, practical source that details everything from good neighbor relations to simple technical cures for RFI. Six complete chapters take you from RFI definition to good workable solutions. The final section is an FCC reprint that presents a step-by-step procedure to identify, localize, and resolve specific radio-TV interference problems. 64 pages. ©1978.

AR-FI

Softbound \$3.00

OWNER REPAIR OF RADIO EQUIPMENT by Frank Glass K6RQ

"The successful repair of any device results in restoring its operation at least to the level it had just before it quit." With this basic concept in mind, author Frank Glass gives you step by step instructions on how to repair all kinds of electronic equipment. Fourteen chapters cover every aspect of repair procedure from component use and failure and how to read schematic diagrams to a most important subject, safety. This book is a must for the amateur new to servicing his own equipment. 85 pages. ©1979.

RQ-OR

Softbound \$7.95

1980 34th EDITION WORLD RADIO & TV HANDBOOK

The world's only complete reference guide to international radio and television. This 1980 edition has complete information on each station including address, frequency and scheduling. Much additional information such as solar activity and World Time Table is included. Unquestionably the leading book of this type. 554 pages. ©1980.

WR-TV

Softbound \$14.95

THE ARRL ANTENNA ANTHOLOGY by the ARRL staff

This brand new book pulls together a wide selection of antenna articles from QST. Written for Amateurs of all levels and interests. Included are phased arrays, verticals, Yagi's . . . even the VHF Quagi! Detailed instructions and full illustrations make this a really useful book for any Amateur. 152 pages. ©1979.

AR-AA

Softbound \$4.00

FM and REPEATERS for THE RADIO AMATEUR by the ARRL staff

This completely new and updated edition gives you the latest in FM technology and design theory. Highlights include microprocessor control circuitry, and a Phase Lock Loop 2 meter transceiver. This mobile operator's favorite now has more to offer. If you're into FM and repeaters or just want to learn more, we have the book you're looking for. 176 pages. ©1978.

AR-FM

Softbound \$5.00

ARRL CODE KIT

A good practice kit for upgrading your Novice or Technician license. Two 60 minute cassettes with 30 minutes each at speeds of 5, 7-1/2, 10 and 13 wpm. Also you'll receive an instruction booklet containing hints and suggestions on methods for mastering code.

AR-CK

\$8.00

RADIOS THAT WORK FOR FREE by K. F. Edwards

It's not often that you can get something for nothing in this world, but this book will tell you how to come as close to it as possible. "Radios that Work for Free" tells you how to build several circuits, each of which will provide you with music, news and entertainment while using only the intercepted power of the station itself. The parts used are inexpensive, or if you are a good scrounger and salvage expert, you'll find most of the parts for free, just as the signals are. Descriptions are amazingly complete. You are led through some of the mystery areas of radio such as antennas, grounds, coils, capacitors, earphones, schematic diagrams, and how to plan, layout, and wire your projects. More than just a trip into nostalgia, the book is a lesson in basic radio principles and techniques — and you can dance to the results. 137 pages. ©1977.

HO-RWF

Spiralbound \$5.00

PRACTICAL ANTENNAS

From the folks at SCELBI, **PRACTICAL ANTENNAS** is not quite like any of the other ham antenna books. Written by a knowledgeable DX'er, this new book is chock-full of helpful hints and suggestions on the how-to's of putting up a super antenna system. Chapters include information on design and construction of practical Yagis, quads and wire type antennas. Inside you'll also find a complete bibliography of antenna articles from the popular amateur publications. Charts and tables are designed to eliminate all those tricky calculations. And, SCELBI has included a list of computer generated beam headings from major population centers to all the countries of the world. A new format, large easy-to-read text and durable vinyl cover make **PRACTICAL ANTENNAS** a "must" for every amateur library. ©1979.

SC-PA

\$9.95

GUIDE TO RTTY FREQUENCIES by Oliver P. Ferrell

Radioteletype to many hams and SWL's is an exotic, complicated form of electronic communication. The author is a well known expert in this interesting field and brings to you a wealth of knowledge and practical experience. First he covers the basics of RTTY identification codes and equipment. Once you've mastered the basics, he gives you a complete rundown on how to receive and understand what you'll be seeing. And — there are over 60 pages of worldwide station listings. For your convenience, listings are made by frequency with station location and service. ©1980, 96 pages.

GL-RF

Softbound \$8.95

Order \$30.00 or more and take a 5% discount. Order will be shipped postpaid.



ANTENNA BOOKS by Bill Orr, W6SAI

THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart Cowan, W2LX

If you are pondering what new antennas to put up, we recommend you read this very popular book. It contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. But, you'll also get information not usually found in antenna books. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and some new information on the increasingly popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. We don't expect you'll agree with everything Orr and Cowan have to say, but we are convinced that **The Radio Amateur Antenna Handbook** will make a valuable and often consulted addition to any Ham's library. 190 pages. ©1978.

RP-AH **Softbound \$6.95**

ALL ABOUT CUBICAL QUAD ANTENNAS

The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. In Bill Orr's latest edition of this well known book, you'll find quad designs for everything from the single element to the multi-element monster quad, plus a new, higher gain expanded quad (X-Q) design. There's a wealth of supplementary data on construction, feeding, tuning, and mounting quad antennas. It's the most comprehensive single edition on the cubical quad available. 112 pages. ©1977.

RP-CQ **Softbound \$4.75**

SIMPLE LOW-COST WIRE ANTENNAS

Learn how to build simple, economical wire antennas. Even if you don't know a feedline from a feed-through, W6SAI will get you on the air with an effective low-cost wire antenna. And, apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. For the old-timer as well as the beginner, it's a clearly written, well diagrammed, and even humorous antenna book. 192 pages. ©1972.

RP-WA **Softbound \$6.95**

BEAM ANTENNA HANDBOOK

Here's recommended reading for anyone thinking about putting up a yagi beam this year. It answers a lot of commonly asked questions like: What is the best element spacing? Can different yagi antennas be stacked without losing performance? Do monoband beams outperform tribanders? Lots of construction projects, diagrams, and photos make reading a pleasurable and informative experience. 198 pages. ©1977.

RP-BA **Softbound \$5.95**

**THE WORKS. ALL FOUR BOOKS
\$22.60 VALUE — JUST \$18.95**

RP-OL **FOUR BOOKS \$18.95**

GOING SAILING WITH AMATEUR RADIO

Are you into sailing? Then you need **Going Sailing** — an extremely helpful book, especially for the boating and yachting enthusiast who wants to incorporate Amateur Radio in his ship's gear. Whether it is just for fun or safety measures, bringing Amateur Radio aboard makes a lot of sense. Next time you're headed for sea, take Amateur Radio and a copy of this great new book for long-range radio communications. 64 pages. ©1978.

HR-GS **Softbound \$3.95**

SHORTWAVE PROPAGATION HANDBOOK

Edited by George Jacobs, W3ASK, and Theodore J. Cohen, N4XX

For many hams, both new and old, radio wave propagation is still a mystery. Realizing this, the authors went about the task of preparing a simplified text that could be understood by hams, swl's and engineers alike. Stress has been given to simplified explanations and charts. The authors also detail a simplified method of do-it-yourself propagation forecasting. To assist your forecasting efforts, the book contains a complete listing of the 12 month smoothed sunspot numbers since 1749. Join those who know how to predict when the bands will open to specific areas of the world. ©1979.

CQ-PH **\$7.50**

ARRL Q & A SERIES

Each book is full of sample questions that cover just about every aspect of the FCC Amateur exam series. These handy study guides are a must for the soon-to-be or ready-to-upgrade Amateur. Convenient pocket size lets you take your study guide with you everywhere. Softbound.

AR-QA Novice ©1979 **\$2.00**
 AR-TG Technician, General ©1979 **\$2.50**
 AR-AE Advanced, Extra ©1979 **\$3.00**

RSGB AMATEUR RADIO OPERATING MANUAL

Edited by R. J. Eckersley

Compiled by the RSGB, this exciting new book covers just about every facet of Amateur Radio. Starting with a precise description of the Amateur Service worldwide, the **Amateur Radio Operating Manual** leads the Amateur through the steps to setting up a station correctly, how to operate properly, DX, contests, satellites, RTTY and Slow Scan Television. You also get 5 big appendixes jam-packed with more information; callsigns in use, maps, DXCC country list, time zones and international callsign assignments. 190 pages. ©1979.

RS-OM **Softbound \$9.95**

GENERAL CLASS AMATEUR LICENSE STUDY GUIDE

by Phil Anderson, WØXI

This book was written in simple laymen's language with uncomplicated explanations and examples used to present electronic radio concepts and ideas. Throughout each chapter, questions and answers are used to strengthen your understanding of the terms and concepts presented. This book also covers several methods that can be used to improve code reception skills. The final chapter is a sample FCC exam which the author feels he would ask if he were to give the FCC exam. 160 pages. ©1979.

21617 **Softbound \$6.50**

KANTRONICS THEORY CASSETTE

Here's a new, easy way to study theory for your Novice, General, Advanced or Extra class exam. Designed for folks on the run. All you have to do is drop in the cassette at home, work, or in the car and listen to an interview-style tape covering Novice, General, Advanced or Extra class theory. A great way to reinforce other study methods.

KT-NT Novice Class Theory Cassette **One tape \$4.95**
 KT-GT General Class Theory Cassette **Two tapes \$8.95**
 KT-AT Advanced Class Theory Cassette **One tape \$4.95**
 KT-ET Extra Class Theory Cassette **One tape \$4.95**

**IN A HURRY?
ORDER
TOLL FREE
1-800-258-5353**

Mail payment and order form to:

Greenville, NH 03048

Ham Radio's Bookstore

the ham notebook

a fresh look at linear tuning

Most Amateurs expect the benefits of a linear-spaced tuning dial when they purchase new equipment. The expression "linear tuning" refers to the ability to rotate the tuning dial or knob, knowing that a certain number of kilohertz will be traversed with each turn of the knob, say 25 or 50 kilohertz. Amateurs expect to find this feature in professionally designed equipment, but rarely is it found in home-built Amateur gear. Why does this situation exist, and what can the Amateur who prefers to build his own do about it? Let's take a look at how commercial manufacturers handle the problem.

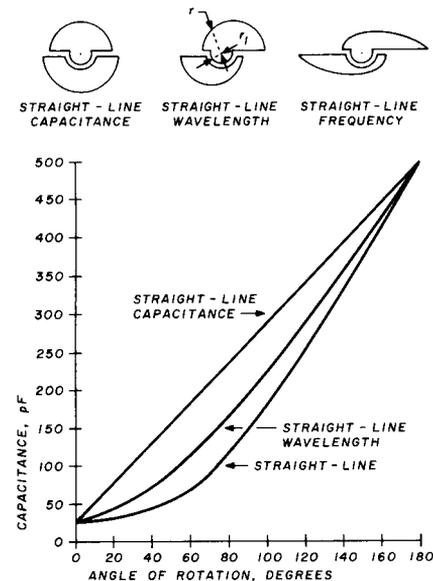


fig. 1. Characteristics of SLC, SLW, and SLF variable capacitors showing capacitance as a function of angle of rotation in typical cases, together with approximate plate shapes. (From *Radio Engineers' Handbook* by F.E. Terman, McGraw-Hill, Inc., 1943.)

Frequency change requires that we square the product of inductance, L , and capacitance, C , to effect a 2:1 frequency change. For example, the product of LC is approximately 520 for 40 meters. The product of LC amounts to about 2080 at 3.5 MHz. Since it would be mechanically unwieldy to alter both inductance and capacitance, the accepted method is to vary either the capacitance or inductance in a typical circuit. (The foregoing remarks apply to high-frequency circuitry in this discussion.)

Most manufacturers handle this situation by limiting the excursion of their oscillator circuit to, say, 500 kHz and by using a VFO coil with windings spaced nonlinearly. A tuning slug moves into the coil form and causes an inductance change. Collins refers to this method as "permeability tuning." It's a good system; unfortunately it's not suitable for easy duplication by the home builder. Another method would be to use capacitor plates with special shaping. This also poses a problem for the home builder.

variable-capacitor plate shapes

Fortunately there's a way of "making it" without having a large machine shop at your disposal. The solution to the problem came to me while watching my wife making some designs on a quilt with a mix-and-match pattern.

A look at most transmitting capacitors shows that they use half-round plates in the rotor section, whereas most capacitors for broadcast reception use different shapes. The first shape is called straight-line capacitance (SLC), while the second is

called midline, or straight-line frequency (SLF). See fig. 1. In short, a variable capacitor with the proper arrangement of SLC and SLF plates

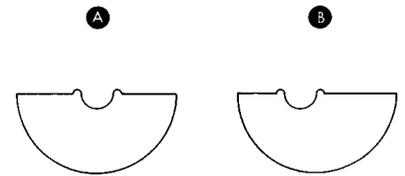


fig. 2. Comparison of rotor plates in the popular "Command" transmitter. A shows approximate shape of an SLC plate; B an SLF plate.

should satisfy the need for truly linear tuning.*

modifying transmitting variable capacitors

Some variable capacitors, which use aluminum plates spaced with washers or metal spacers, can be modified easily in the rotor section to accomplish this objective. In my case, I removed half-round plates from the middle capacitor in a Command transmitter and re-installed them on the rotor shaft of the master oscillator tuning capacitor, which had been altered by lifting out several of the SLF rotor plates.

With the correct amount of fixed L and C , linear tuning will result. If you're willing to settle for a limited frequency excursion, exceptionally high accuracy can be achieved. The

*Still another shape for variable-capacitor plates is called straight-line wavelength (SLW) in which the plates are shaped so that, when used to tune an inductance to resonance, the wavelength at resonance is a linear function of the angle of rotation. Practical capacitors use intermediate characteristics or a combination of these basic types (see fig. 2). Editor.

calibration chart (table 1) shows this to the last hertz. Note that this is not a one-of-a-kind experiment. Equally satisfying results have been accomplished in a half-dozen instances. There's no reason why this technique can't be applied to other ranges, such as the popular 5.0-5.5 MHz range used in many VFOs.

My original intentions were satisfied, as shown by a 3.5-3.6-MHz curve. However, high-accuracy linear readout continued throughout at least a 200-kHz span between 3.45-3.65 MHz. All of the above was achieved without trimming or bending of the master-oscillator variable capacitor plates; thus it's fair to say that similar results could be obtained by any careful experimenter or builder.

Neil Johnson, W2OLU

solid-state amplifier switching

Forget about carrier-operated relay (COR) circuits and other mechanical antenna and power switching arrangements by going solid-state. This diode-switching circuit provides maintenance-free, reliable switching

without fuss or bother. Best of all, it's simple.

Simply use two quarter-wave-length sections of RG-174/U coax and appropriate diodes (fig. 1). The 1N4148 diodes are adequate for moderate power levels commonly used on 2-meter f-m.

David D. Holtz, WB2HTH

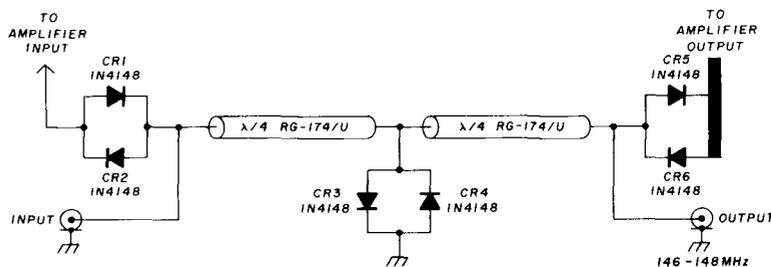


fig. 1. Solid-state switch for 2-meter f-m. Circuit was adapted from an article appearing in the April, 1973, issue of *ham radio*.

de-icing the quad

Probably more quad antennas have come to grief because of ice than from all other reasons combined. At least that seems to have been my experience. It seems that something may be lacking in our planning. A simple means of de-icing the quad should be a real boon to those who usually have a couple such examples of nature's contempt for us each winter.

The quad driven element is usually fed at bottom center through coaxial line. If, for the driven element, we use a wire having a higher resistance at dc than at rf, such as galvanized electric fence wire or smaller size copper-weld, 60-Hz power, fed through the coaxial line should provide enough heat to prevent the formation of ice, or if it has already formed, to melt it. After all, ice usually forms at temperatures quite close to freezing, and this idea wouldn't require a temperature increase of more than a few degrees to thwart Jack Frost.

The average quad has at least two elements, and it wouldn't do to leave the parasitic elements out in the cold. By going to the top of the quad, opposite the feed point, one finds a volt-

age node. A capacitor of suitable power-handling capability may be inserted here without affecting array performance. A value of 0.01 or 0.02 μF should be enough capacitance. The same thing can be done with the reflector (and the director if you have more than two elements). A pair of wires that connect all the elements in series for dc, running parallel to the boom, should permit you to apply

enough current through the coaxial line to keep the ice away. An ordinary filament transformer should supply enough power for most applications.

The diamond configuration might be preferable for this application, as more support would be provided for the capacitors and connecting wires; the square configuration makes a clearer illustration (fig. 1).

Henry S. Keen, W5TRS

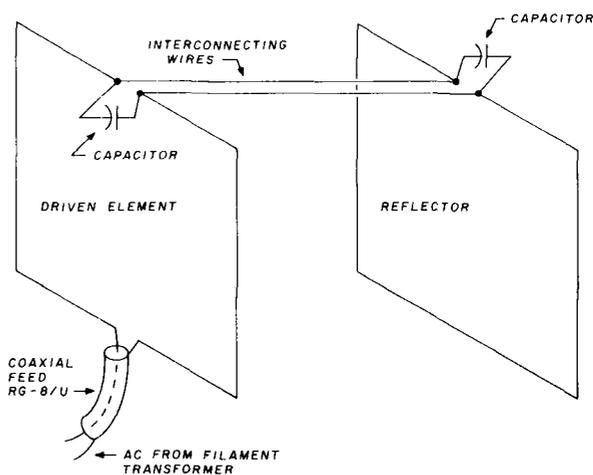


fig. 1. Power applied to a quad from an ordinary filament transformer will generate enough heat to prevent ice formation, or if already formed, to melt it. The capacitors are inserted at the voltage nodes of the elements, and don't affect array performance.

MHz electronics

1900 MHz to 2500 MHz DOWN CONVERTER

This receiver is tunable over a range of 1900 to 2500 mc and is intended for amateur radio use. The local oscillator is voltage controlled (i.e.) making the i-f range approximately 54 to 88 mc (Channels 2 to 7).

PC BOARD WITH CHIP CAPACITORS 13	\$44.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY	\$79.99
PC BOARD ASSEMBLED AND TESTED	\$120.00
POWER SUPPLY KIT	\$44.99
POWER SUPPLY ASSEMBLED AND TESTED	\$69.99
YAGI ANTENNA 4' LONG APPROX. 20 TO 23 dB GAIN	\$59.99
YAGI ANTENNA 4' WITH TYPE (N, BNC, SMA Connector)	\$64.99
2300 MHz DOWN CONVERTER	
Includes converter mounted in antenna, power supply, antenna, 75' and 3' RG59 cable with connectors, 75 to 300 ohm adapter, Plus 90 DAY WARRANTY	
OPTION #1 MRF902 in front end. (7 dB noise figure)	\$299.99
OPTION #2 2N6603 in front end. (5 dB noise figure)	\$349.99
OPTION #2 2N6603 in front end. (5 dB noise figure)	\$400.00
2300 MHz DOWN CONVERTER ONLY	
10 dB Noise Figure 23 dB gain in box with N conn. Input F conn. Output	\$149.99
7 dB Noise Figure 23 dB gain in box with N conn. Input F conn. Output	\$169.99
5 dB Noise Figure 23 dB gain in box with SMA conn. Input F conn. Output	\$189.99
DATA IS INCLUDED WITH KITS OR MAY BE PURCHASED SEPARATELY	\$15.00

Shipping and Handling Cost:

Receiver Kits add \$1.50, Power Supply add \$2.00, Antenna add \$5.00, Option 1/2 add \$3.00, For complete system add \$7.50.

Replacement Parts:

MRF901	\$5.00	MBD101	\$2.00
MRF902	\$10.00	.001 chip caps	\$2.00
2N6603	\$12.00	PC Board only	\$25.00 with data

3.7 to 4.2 Gc SATELLITE DOWN CONVERTER

70 MHz i-f (40 MHz @ 1 dB)	10 dB min. IMAGE REJECTION	
15 dB max. Noise Figure	25 dB Gain	
ASSEMBLED AND TESTED WITH SMA CONNECTOR FOR INPUT AND F CONNECTOR FOR OUTPUT		\$499.99

I-F AMPLIFIER FOR ABOVE 70 MHz

45 dB Gain — 30 MHz @ 3 dB — ASSEMBLED AND TESTED F CONNECTOR	\$129.99
---	-----------------

DEMOD FOR ABOVE 70 MHz

COMPOSITE VIDEO OUTPUT (NO RF) — ASSEMBLED AND TESTED	\$159.99
---	-----------------

TERMS:

WE REGRET WE NO LONGER ACCEPT BANK CARDS.

PLEASE SEND POSTAL MONEY ORDER, CERTIFIED CHECK, CASHIER'S CHECK OR MONEY ORDER. PRICES SUBJECT TO CHANGE WITHOUT NOTICE. WE CHARGE 15% FOR RESTOCKING ON ANY ORDER.

ALL CHECKS AND MONEY ORDERS IN US FUNDS ONLY.

ALL ORDERS SENT FIRST CLASS OR UPS.

ALL PARTS PRIME AND GUARANTEED.

WE WILL ACCEPT COD ORDERS FOR \$25.00 OR OVER, ADD \$1.50 FOR COD CHARGE.

PLEASE INCLUDE \$1.50 MINIMUM FOR SHIPPING OR CALL FOR CHARGES.

WE ALSO ARE LOOKING FOR NEW AND USED TUBES, TEST EQUIPMENT, COMPONENTS ETC.

WE ALSO SWAP OR TRADE.

FOR CATALOG SEE JANUARY, 1980, 73 Magazine, 10 Pages.

(602) 242-3037

(602) 242-8916

**2111 W. Camelback
Phoenix, Arizona 85015**

FAIRCHILD VHF AND UHF PRESCALER CHIPS

95H90DC	350 MHz Prescaler Divide by 10/11	\$9.50
95H91DC	350 MHz Prescaler Divide by 5/6	9.50
11C90DC	650 MHz Prescaler Divide by 10/11	16.50
11C91DC	650 MHz Prescaler Divide by 5/6	16.50
11C83DC	1 GHz Divide by 248/256 Prescaler	29.90
11C70DC	600 MHz Flip/Flop with reset	12.30
11C58DC	ECL VCM	4.53
11C44DC/MC4044	Phase Frequency Detector	3.82
11C24DC/MC4024	Dual TTL VCM	3.82
11C06DC	UHF Prescaler 750 MHz D Type Flip/Flop	12.30
11C05DC	1 GHz Counter Divide by 4	74.35
11C01FC	High Speed Dual 5-4 input NO/NOR Gate	15.40

WISPER FANS

This fan is super quiet, efficient cooling where low acoustical disturbance is a must. Size 4.68" x 4.68" x 1.50", Impedance protected, 50/60 Hz. 120 Vac. \$9.99

TRW BROADBAND AMPLIFIER MODEL CA615B

Frequency response 40 MHz to 300 MHz
Gain: 300 MHz 16 dB Min., 17.5 dB Max.
50 MHz 0 to -1 dB from 300 MHz
Voltage: 24 volts dc at 220 ma max. \$19.99

CARBIDE — CIRCUIT BOARD DRILL BITS FOR PC BOARDS

Size: 35, 42, 47, 49, 51, 52	\$2.15
Size: 53, 54, 55, 56, 57, 58, 59, 61, 63, 64, 65	1.85
Size: 66	1.90
Size: 1.25 mm, 1.45 mm	2.00
Size: 3.20 mm	3.58

CRYSTAL FILTERS: TYCO 001-19880 same as 2194F

10.7 MHz Narrow Band Crystal Filter
3 dB bandwidth 15 kHz min. 20 dB bandwidth 60 kHz min. 40 dB bandwidth 150 kHz min.
Ultimate 50 dB: Insertion loss 1.0 dB max. Ripple 1.0 dB max. Ct. 0 +/- 5 pf 3600 ohms. \$5.95

MURATA CERAMIC FILTERS

Models: SFD-455D 455 kHz	\$3.00
SFB-455D 455 kHz	2.00
CFM-455E 455 kHz	7.95
SFE-10.7 10.7 MHz	5.95

TEST EQUIPMENT — HEWLETT PACKARD — TEKTRONIX — ETC.

Hewlett Packard:

491C	TWT Amplifier 2 to 4 Gc 1 watt 30 dB gain	\$1150.00
608D	10 to 420 mc .1 uV to .5 V into 50 ohms Signal Generator	500.00
612A	450 to 1230 mc .1 uV to .5 V into 50 ohms Signal Generator	750.00
616B	1.8 to 4.2 Gc Signal Generator	400.00
618B	3.8 to 7.2 Gc Signal Generator	400.00
620A	7 to 11 Gc Signal Generator	400.00
623B	Microwave Test Set	900.00
624C	Microwave Test Set	950.00
3200B	10 to 500 mc vhf Oscillator	450.00
8691A	1 to 2 Gc Plug In For 8690A Sweeper	800.00
8692A	2 to 4 Gc Plug In For 8690A Sweeper	800.00
8693A	4 to 8 Gc Plug In For 8690A Sweeper	800.00
8742A	Reflection Test Unit 2 to 12.4 Gc	1800.00

Alltech:

473	225 to 400 mc AM/FM Signal Generator	750.00
-----	--------------------------------------	--------

Singer:

MF5/VR-4	Universal Spectrum Analyzer with 1 kHz to 27.5 mc Plug In	1200.00
----------	---	---------

Keltek:

XR630-100	TWT Amplifier 8 to 12.4 Gc 100 watts 40 dB gain	9200.00
-----------	---	---------

Polarad:

2038/2436/1102A	Calibrated Display with an SSB Analysis Module and a 10 to 40 mc Single Tone Synthesizer	1500.00
-----------------	--	---------

RF TRANSISTORS

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2N1561	\$15.00	2N5590	\$8.15	MM1550	\$10.00
2N1562	15.00	2N5591	11.85	MM1552	50.00
2N1692	15.00	2N5637	22.15	MM1553	56.50
2N1693	15.00	2N5641	6.00	MM1601	5.50
2N2632	45.00	2N5642	10.05	MM1602/2N5842	7.50
2N2857JAN	2.52	2N5643	15.82	MM1607	8.65
2N2876	12.35	2N6545	12.38	MM1661	15.00
2N2880	25.00	2N5764	27.00	MM1669	17.50
2N2927	7.00	2N5842	8.78	MM1943	3.00
2N2947	18.35	2N5849	21.29	MM2605	3.00
2N2948	15.50	2N5862	51.91	MM2608	5.00
2N2949	3.90	2N5913	3.25	MM8006	2.23
2N2950	5.00	2N5922	10.00	MMCM918	20.00
2N3287	4.30	2N5942	46.00	MMT72	1.17
2N3294	1.15	2N5944	8.92	MMT74	1.17
2N3301	1.04	2N5945	12.38	MMT857	2.63
2N3302	1.05	2N5946	14.69	MRF304	43.45
2N3304	1.48	2N6080	7.74	MRF420	20.00
2N3307	12.60	2N6081	10.05	MRF450	11.85
2N3309	3.90	2N6082	11.30	MRF450A	11.85
2N3375	9.32	2N6083	13.23	MRF454	21.83
2N3553	1.57	2N6084	14.66	MRF458	20.68
2N3755	7.20	2N6094	7.15	MRF475	5.00
2N3818	6.00	2N6095	11.77	MRF476	5.00
2N3866	1.09	2N6096	20.77	MRF502	1.08
2N3866JAN	2.80	2N6097	29.54	MRF504	6.95
2N3866JANTX	4.49	2N6136	20.15	MRF509	4.90
2N3924	3.34	2N6166	38.60	MRF511	8.15
2N3927	12.10	2N6265	75.00	MRF901	3.00
2N3950	26.86	2N6266	100.00	MRF5177	21.62
2N4072	1.80	2N6439	45.77	MRF8004	1.60
2N4135	2.00	2N6459/PT9795	18.00	PT4186B	3.00
2N4261	14.60	2N6603	12.00	PT4571A	1.50
2N4427	1.20	2N6604	12.00	PT4612	5.00
2N4429	7.50	A50-12	25.00	PT4628	5.00
2N4430	20.00	BFR90	5.00	PT4640	5.00
2N4957	3.62	BLY568C	25.00	PT8659	10.72
2N4958	2.92	BLY568CF	25.00	PT9784	24.30
2N4959	2.23	CD3495	15.00	PT9790	41.70
2N4976	19.00	HEP76/S3014	4.95	SD1043	5.00
2N5090	12.31	HEPS3002	11.30	SD1116	3.00
2N5108	4.03	HEPS3003	29.88	SD1118	5.00
2N5109	1.66	HEPS3005	9.95	SD1119	3.00
2N5160	3.49	HEPS3006	19.90	TA7993	75.00
2N5179	1.05	HEPS3007	24.95	TA7994	100.00
2N5184	2.00	HEPS3010	11.34	TRWMRA2023-1.5	42.50
2N5216	47.50	HEPS5026	2.56	40281	10.90
2N5583	4.55	HP35831E/	40282	40282	11.90
2N5589	6.82	HXTR5104	50.00	40290	2.48
		MM1500	32.20		

CHIP CAPACITORS

1pf	27pf	220pf	1200pf
1.5pf	33pf	240pf	1500pf
2.2pf	39pf	270pf	1800pf
2.7pf	47pf	300pf	2200pf
3.3pf	56pf	330pf	2700pf
3.9pf	68pf	360pf	3300pf
4.7pf	82pf	390pf	3900pf
5.6pf	100pf	430pf	4700pf
6.8pf	110pf	470pf	5600pf
8.2pf	120pf	510pf	6800pf
10pf	130pf	560pf	8200pf
12pf	150pf	620pf	.010mf
15pf	160pf	680pf	.012mf
18pf	180pf	820pf	.015mf
22pf	200pf	1000pf	.018mf

We can supply any value chip capacitors you may need.

PRICES

1 to 10	\$1.99
11 - 50	1.49
51 - 100	1.00
101 - 1,000	.75
1,001 up	.50

ATLAS CRYSTAL FILTERS FOR ATLAS HAM GEAR

- 5.52-2.7/8
- 5.595-2.7/8/U
- 5.595-.500/4/CW
- 5.595-2.7LSB
- 5.595-2.7USB
- 5.645-2.7/8
- 9.0USB/CW

YOUR CHOICE \$24.95




MRF454

\$21.83

NPN SILICON RF POWER TRANSISTORS

... designed for power amplifier applications in industrial, commercial and amateur radio equipment to 30 MHz.

- Specified 12.5 Volt, 30 MHz Characteristics -
Output Power = 80 Watts
Minimum Gain = 12 dB
Efficiency = 50%

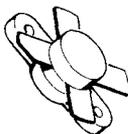

MRF458

\$20.68

NPN SILICON RF POWER TRANSISTOR


... designed for power amplifier applications in industrial, commercial and amateur radio equipment to 30 MHz.

- Specified 12.5 Volt, 30 MHz Characteristics -
Output Power = 80 Watts
Minimum Gain = 12 dB
Efficiency = 50%
- Capable of Withstanding 30:1 Load VSWR @ Rated P_{out} and V_{CC}

NPN SILICON RF POWER TRANSISTOR

... designed primarily for use in large-signal output amplifier stages. Intended for use in Citizen-Band communications equipment operating at 27 MHz. High breakdown voltages allow a high percentage of up-modulation in AM circuits.

- Specified 12.5 V, 27 MHz Characteristics -
Power Output = 4.0 Watts
Power Gain = 10 dB Minimum
Efficiency = 65% Typical

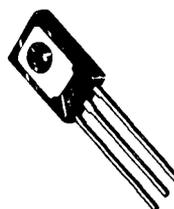

MRF472

\$2.50

MRF475

NPN SILICON RF POWER TRANSISTOR

... designed primarily for use in single sideband linear amplifier output applications in citizens band and other communications equipment operating to 30 MHz.

- Characterized for Single Sideband and Large-Signal Amplifier Applications Utilizing Low-Level Modulation.
- Specified 13.6 V, 30 MHz Characteristics -
Output Power = 12 W (PEP)
Minimum Efficiency = 40% (SSB)
Output Power = 4.0 W (CW)
Minimum Efficiency = 50% (CW)
Minimum Power Gain = 10 dB (PEP & CW)
- Common Collector Characterization



\$5.00

MHW710 - 2

\$46.45

440 to 470MC

UHF POWER AMPLIFIER MODULE

... designed for 12.5 volt UHF power amplifier applications in industrial and commercial FM equipment operating from 400 to 512 MHz.

- Specified 12.5 Volt, UHF Characteristics -
Output Power = 13 Watts
Minimum Gain = 19.4 dB
Harmonics = 40 dB
- 50 Ω Input/Output Impedance
- Guaranteed Stability and Ruggedness
- Gain Control Pin for Manual or Automatic Output Level Control
- Thin Film Hybrid Construction Gives Consistent Performance and Reliability



Tektronix Test Equipment

B	Wideband High Gain Plug In	\$ 51.00
CA	Dual Trace Plug In	150.00
K	Fast Rise DC Plug In	63.00
N	Sampling Plug In	200.00
R	Transistor Risettime Plug In	116.00
W	High Gain Differential Comparator Plug In	283.00
TU-2	Test Load Plug In for 530/540/550 Main Frames	50.00
IA2	Wideband Dual Trace Plug In	216.00
151	Sampling Unit With 350PS Risettime DC to 1GHZ	730.00
2A61	AC Differential Plug In	133.00
353	Dual Trace Sampling DC to 1GHZ Plug In	250.00
3576	Dual Trace Sampling DC to 875MHZ Plug In	250.00
3777A	Sampling Sweep Plug In	250.00
3L10	Spectrum Analyzer 1 to 36MHZ Plug In	1000.00
50	Amplifier Plug In	50.00
51	Sweep Plug In	50.00
53B	Wideband High Gain Plug In	25.00
53/54B	Wideband High Gain Plug In	45.00
53/54C	Dual Trace Plug In	112.50
53/54D	High Gain DC Differential Plug In	38.00
53/54G	Wideband DC Differential Plug In	68.00
53/54L	Fast Rise High Gain Plug In	75.00
84	Test Plug In For 580/581 Main Frames	48.00
107	Square Wave Generator .4 to 1MHZ	63.00
RM122	Preamplifier 2Hz to 40KHZ	25.00
123	AC Coupled Preamplifier	148.00
127	Power Supply For 2 Plug In's	50.00
131	Current Probe Amplifier	363.00
184	Time Mark Generator	150.00
8240	Program Control Unit	84.00
280	Trigger Countdown Unit	2000.00
455	Portable Dual Trace 50MHZ Scope	2500.00
465	Portable Dual Trace 100MHZ Scope	250.00
503	DC to 450KHZ Scope Rack Mount	263.00
535A	DC to 15MHZ Scope Rack Mount	300.00
543	DC to 3MHZ Scope Rack Mount	150.00
561	DC to 10MHZ Scope Rack Mount	200.00
561A	DC to 10MHZ Scope Rack Mount	200.00

Scopes with Plug-ins

567	Digital Readout Scope with a 6RIA Digital Unit and a 3S3 Dual Trace DC to 1GHZ Sampling Plug In and a 3T77A Sweep Plug In.	750.00
561A	DC to 10MHZ Scope with a 3S76 Dual Trace DC to 875MHZ Sampling Plug In and a 3T77A Sweep Plug In. Rack Mount	600.00
565	DC to 10MHZ Dual Beam Scope with a 2A63 Diff. and a 2A61 Diff. Plug In's	900.00
581	DC to 80MHZ Scope with a 82 Dual Trace High Gain Plug In	650.00
661	Sampling Scope with a 5T3 Timing Plug In and a 4S2 Dual Trace DC to 3.5GHZ Sampling Plug In.	575.00

Tubes

2E26	\$ 5.00	4CX350FJ	\$116.00	6146W	12.00
3-5002	102.00	4CX1000A	300.00	6159	10.60
3-10002	268.00	4CX1500B	350.00	6161	75.00
3B28/866A	5.00	4C215000A	750.00	6293	18.50
3X2500A3	150.00	4E27	50.00	6360	6.95
4-65A	45.00	4X150A	41.00	6907	40.00
4-125A	58.50	4X150D	52.00	6939	14.75
4-250A	68.50	4X150G	74.00	7360	12.00
4-400A	71.00	5726/1160L	39.00	7984	10.40
4-1000A	184.00	6LF6	5.00	8072	49.00
5-500A	145.00	6LQ6	5.00	8106	2.00
4CX250B	65.00	811A	12.95	8156	7.85
4CX250F/G	55.00	813	29.00	8226	127.70
4CX250K	113.00	5894/A	42.00	8295/PL172	324.00
4CX250R	92.00	6146	5.00	8458	25.75
4CX300A	147.00	6146A	6.00	8560A/AS	50.00
4CX350A	107.00	6146B/8298A	7.00	8908	9.00
				8950	9.00

MICROWAVE COMPONENTS

COMPUTER I.C. SPECIALS

ARRA

2416	Variable Attenuator	\$ 50.00
3614-60	Variable Attenuator 0 to 60dB	75.00
KU520A	Variable Attenuator 18 to 26.5 GHz	100.00
4684-20C	Variable Attenuator 0 to 180dB	100.00
6684-20F	Variable Attenuator 0 to 180dB	100.00

General Microwave

Directional Coupler 2 to 4GHz 20dB Type N	75.00
---	-------

Hewlett Packard

H487B	100 ohms Neg. Thermistor Mount (NEW)	150.00
H487B	100 ohms Neg. Thermistor Mount (USED)	100.00
477B	200 ohms Neg. Thermistor Mount (USED)	100.00
X487A	100 ohms Neg. Thermistor Mount (USED)	100.00
X487B	100 ohms Neg. Thermistor Mount (USED)	125.00

J468A	100 ohms Neg. Thermistor Mount (USED)	150.00
478A	200 ohms Neg. Thermistor Mount (USED)	150.00
8478A	200 ohms Balanced Neg. Thermistor Mount (USED)	175.00
J382	5.85 to 8.2 GHz Variable Attenuator 0 to 50dB	250.00
X382A	8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	250.00

X885A	8.2 to 12.4 GHz Phase Shifter +/- 360°	250.00
394A	1 to 2 GHz Variable Attenuator 6 to 120dB	250.00
NK292A	Waveguide Adapter	65.00
K422A	18 to 26.5 GHz Crystal Detector	250.00
K375A	18 to 26.5 GHz Variable Attenuator	300.00
8436A	Bandpass Filter 8 to 12.4 GHz	75.00

B439A	2 GHz Notch Filter	75.00
8471A	RF Detector	50.00
342A	VHF Noise Source	100.00
X347A	8.2 to 12.4 GHz Noise Source	250.00
H532A	7.05 to 10 GHz Frequency Meter	300.00
G532A	3.95 to 5.85 GHz Frequency Meter	300.00
J532A	5.85 to 8.2 GHz Frequency Meter	300.00

809A	Carriage with a 444A Slotted Line Untuned Detector Probe and 809B Coaxial Slotted Section 2.6 to 18 GHz	175.00
809B	Carriage with a 442B Broadband Probe 2.6 to 12.4 GHz and a X810B Slotted Section	200.00
809B	Carriage with a X810B Slotted Section and a PRD 250A Detector Mount 2.4 to 12.4 GHz	200.00

Merrimac

AU-25A/	801115 Variable Attenuator	100.00
AU-26A/	801162 Variable Attenuator	100.00

Microlab/FXR

Y410A	Frequency Meter 12400 - 18000 MC	250.00
N414A	Frequency Meter 3950 - 11000 MC	350.00
X638S	Horn 8.2 - 12.4 GHz	60.00
601-818	X to N Adapter 8.2 - 12.4 GHz	35.00
Y610D	Coupler	75.00

Narda

3095/	22909 Directional Coupler 7 to 12.4 GHz 10dB Type N	250.00
4013C-10/	22540A Directional Coupler 2 to 4 GHz 10dB Type SMA	90.00
4014-10/	22538 Directional Coupler 3.85 to 8 GHz 10dB Type SMA	90.00
4014C-6/	22876 Directional Coupler 3.85 to 8 GHz 6dB Type SMA	90.00
4015C-10/	22539 Directional Coupler 7.4 to 12 GHz 10dB Type SMA	95.00
4015C-30/	23105 Directional Coupler 7 to 12.4 GHz 30dB Type SMA	95.00
3044-20	Directional Coupler 4 to 8 GHz 20dB Type N	125.00
3040-20	Directional Coupler 240 to 500 MC 20dB Type N	125.00
3041-20	Directional Coupler 500 to 1000 MC 20dB Type N	125.00
3043-20/	22006 Directional Coupler 1.7 to 4 GHz 20dB Type N	125.00
3003-10/	22011 Directional Coupler 2 to 4 GHz 10dB Type N	75.00
3003-30/	22012 Directional Coupler 2 to 4 GHz 30dB Type N	75.00
3042-20	Directional Coupler 950 to 2 GHz 20dB Type N	125.00
3043-30/	22007 Directional Coupler 1.7 to 3.5 GHz 30dB Type N	125.00
22574	Directional Coupler 2 to 4 GHz 10dB Type N	125.00
3033	Coaxial Hybrid 2 to 4 GHz 3dB Type N	125.00
3032	Coaxial Hybrid 950 to 2 GHz 3 dB Type N	125.00
784/	22380 Variable Attenuator 1 to 90dB 2 to 2.5 GHz Type SMA	550.00
22377	Waveguide to Type N Adapter	35.00
720-6	Fixed Attenuator 8.2 to 14.4 GHz 6 dB	50.00
3503	Waveguide	25.00

PRD

U101	12.4 to 18 GHz Variable Attenuator 0 to 60dB	300.00
X101	8.2 to 12.4 GHz Variable Attenuator 0 to 60dB	200.00
C101	Variable Attenuator 0 to 60dB	200.00
205A/367	Slotted Line with Type N Adapter	100.00
195B	8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	100.00
185B51	7.05 to 10 GHz Variable Attenuator 0 to 40dB	100.00
196C	8.2 to 12.4 GHz Variable Attenuator 0 to 45dB	100.00
170B	3.95 to 5.85 GHz Variable Attenuator 0 to 45dB	100.00
588A	Frequency Meter 5.3 to 6.7 GHz	100.00
140A,C,D,E	Fixed Attenuators	25.00
109J,I	Fixed Attenuators	25.00
WEINSCHEL ENG.	2692 Variable Attenuator +30 to 60dB	100.00

MEMORY

2708	1K x 8 EPROM	\$ 7.99
2716/2516	2K x 8 EPROM 5VOLT Single Supply	20.00
2114/9114	1K x 4 Static RAM 450ns	6.99
2114L2	1K x 4 Static RAM 250ns	8.99
2114L3	1K x 4 Static RAM 350ns	7.99
4027	4K x 1 Dynamic RAM	3.99
4060/2107	4K x 1 Dynamic RAM	3.99
4050/9050	4K x 1 Dynamic RAM	3.99
2111A-2/8111	256 x 4 Static RAM	3.99
2112A-2	256 x 4 Static RAM	3.99
2115AL-2	1K x 1 Static RAM 55ns	4.99
6104-3/4104	4K x 1 Static RAM 320ns	14.99
7141-2	4K x 1 Static RAM 200ns	14.99
MCM6641L20	4K x 2 Static RAM 200ns	14.99
9131	1K x 1 Static RAM 300ns	10.99

C.P.U.'S ECT.

MC6800L	Microprocessor	13.80
MCM6810AP	128 x 8 Static RAM 450ns	3.99
MCM68A10P	128 x 8 Static RAM 360ns	4.99
MCM68B10P	128 x 8 Static RAM 250ns	5.99
MC6820P	PIA	8.99
MC6820L	PIA	9.99
MC6821P	PIA	8.99
MC68B21P	PIA	9.99
MCM6830L7	Mikbug	14.99
MC6840P	PTM	8.99
MC6845P	CRT Controller	29.50
MC6845L	CRT Controller	33.00
MC6850L	ACIA	10.99
MC6850P	ACIA	4.99
MC6852P	SSDA	5.99
MC6852L	SSDA	11.99
MC6854P	ADLC	22.00
MC6860CJCS	0-600 BPS Modem	29.00
MC6862L	2400 BPS Modem	14.99
MK3850N-3	F8 Microprocessor	9.99
MK3852P	F8 Memory Interface	16.99
MK3852N	F8 Memory Interface	9.99
MK3854N	F8 Direct Memory Access	9.99
8008-1	Microprocessor	4.99
8080A	Microprocessor	8.99
Z80CPU	Microprocessor	14.99
6520	PIA	7.99
6530	Support For 6500 series	15.99
2650	Microprocessor	10.99
TMS1000NL	Four Bit Microprocessor	9.99
TMS4024NC	9 x 64 Digital Storage Buffer (FIFO)	9.99
TMS6011NC	UART	9.99
MC14411	Bit Rate Generator	11.99
AY5-4007D	Four Digit Counter/Display Drivers	8.99
AY5-9200	Repertory Dialler	9.99
AY5-9100	Push Button Telephone Diallers	7.99
AY5-2376	Keyboard Encoder	19.99
AY3-8500	TV Game Chip	5.99
TR1402A	UART	9.99
PR1472B	UART	9.99
PT1482B	UART	9.99
8257	DMA Controller	9.99
8251	Communication Interface	9.99
8228	System Controller & Bus Driver	5.00
8212	8 Bit Input/Output Port	5.00
MC14410CP	2 of 8 Tone Encoder	9.99
MC14412	Low Speed Modem	14.99
MC1440B	Binary to Phone Pulse Converter	12.99
MC14409	Binary to Phone Pulse Converter	12.99
MC1488L	RS232 Driver	1.00
MC1489L	RS232 Receiver	1.00
MC1405L	A/D Converter Subsystem	9.00
MC1406L	6 Bit D/A Converter	7.50
MC1408/6/7/8	8 Bit D/A Converter	4.50
MC1330P	Low Level Video Detector	1.50
MC1349/50	Video IF Amplifier	1.17
MC1733L	LM733 OP Amplifier	2.40
LM565	Phase Lock Loop	2.50

MHz electronics

(602) 242-2037

(602) 242-8916


2111 W. Camelback
Phoenix, Arizona 85015



smaller thumbwheel switch

A new line of *subminiature*, digital thumbwheel switches is now available from Unimax Switch Corporation, a subsidiary of the Unimax Group, Inc. Designated as "Series S2D," a single, rear-mounted switch (with up to sixteen positions) will require a panel cutout only 0.748 inch (19 mm) high by 0.670 inch (17 mm) wide! This size reduction for this type of switch will greatly simplify the job of laying out crowded control panels of modern electronic equipment.

In addition to their small size, the new switches offer all the "traditional" benefits found in Unimax standard digital thumbwheel switches. These include the unique degree of freedom in mounting — any Series S2D switch can be mounted either from the front or the rear of the panel simply by using different sets of end plates (in both instances, end plates fit either the left or right side, which translates into smaller inventories and simplified assembly).

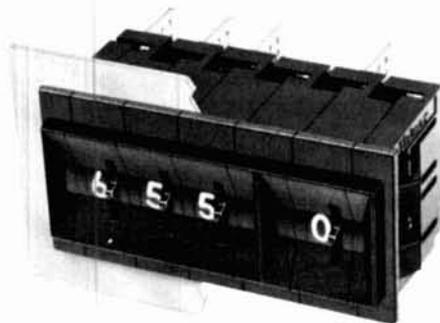

Like standard Unimax digital thumbwheel switches, the new Series S2D units offer Unimax's "No-Hardware" feature — meaning that a wide vari-

ety of switching assemblies can be made by simply snapping together standard switch bodies, dividers, blank bodies, and end plates. Other Series S2D features include a high degree of reliability due to the fact that each switch consists of only five components, and has a life of 1,000,000 operations.

The new Series offers as standard the nine most widely used output codes; other codes can be supplied on request. Standard output codes include Single-Pole Decimal, 10-Position; 10-Position BCD, Complement only; 10-Position BCD only; 10-Position BCD with Complements; Single-Pole, 16-Position, Binary; and Single Pole, Repeating. For more information contact Unimax Switch Corporation, Ives Road, Wallingford, Connecticut 06492.

CompuClock

CompuClock from Comtronics, Inc., is a free-standing, non-interruptible digital clock, delivering time and date on software command. Time is also visually displayed, and the date appears with the push of a button.



Time and date are delivered on software command to an RS232C computer port as a serial string of 21 ASCII characters. For example:

```
03:17:16 PM [SP], 01-31-80 [CR]
[LF]
```

where [SP], [CR] and [LF] refer to the ASCII codes for space, carriage return and line feed. This output can be supplied to any format desired.

CompuClock has a backup power supply and maintains the time and date precisely in the event of power failure. The visual display goes out to save the battery, but time can be

maintained for up to two weeks until power is restored.

For more information write Comtronics, Inc., 105 N.W. 43rd Street, Boca Raton, Florida 33431, or phone Chuck Staples at (305) 392-8700.

Keithley hand-held DMM

Keithley Instruments announces its first hand-held digital multimeter (DMM). The 3 1/2 digit Model 130, with a large LCD display is intended to be a technician's tool. Priced at only \$99, it is a basic instrument, designed to meet the needs of the field service technician. It is easy to use, straightforward, and rugged.



Keithley has gained considerable market share with the complete line of bench digital multimeters that it has brought out in the past two years. The addition of the Model 130 rounds out that line.

A survey conducted by Keithley found that most service technicians prefer rotary switches and liquid-crystal displays (LCD). They also want a hand-held model that is convenient in a bench situation, so the display is the same size, 0.6 inch, as the displays on Keithley's bench instruments.

In addition, the simplicity of construction makes the Model 130 the most rugged hand-held DMM on the market. For more information write Keithley Instruments, Inc., 28775 Aurora Road, Cleveland, Ohio 44139.

mini-mount antennas

A complete line of eight low-priced miniature antennas, featuring the new Mini-Mag Mount and Mini-Mount, are now available from Antenna Incorporated.


Designed to fill the need for low-cost business communications antennas, six of the miniature antennas cover the 5-dB-gain uhf band and two cover the 1/4-wavelength 136-512 MHz band. The 136-512 MHz Model 42013 1/4-wave Mini-Mag magnet-mount antenna is priced at \$21.25. The mount has a 2-inch diameter magnet and stands 1-1/4 inches high with the whip adapter; overall length with 136-MHz antenna whip is 20 inches. The electrically equivalent Model 42008 Mini-Mount is priced at \$11.81. The Mini-Mount is adaptable for installation in either a 3/4-inch or 3/8-inch hole (although the installer must have access to the

underside of the roof in order to use the 3/8 inch mount). It also stands 1-1/4 inches with whip adapter and 20 inches with 136 MHz antenna whip.

The 3/8-1/4 inch Mini-Mount is also available on 450 MHz skirt antennas at a price of \$30.00 in these frequency ranges: 406-420 MHz (Model 43128); 420-435 MHz (Model 43228); 435-450 MHz (Model 43328); 450-470 MHz (Model 43428); 470-490 MHz (Model 43528); 490-512 MHz (Model 43628).

The 3/8-3/4 inch Mini-Mounts come with 17 feet of RG-58/U coaxial cable and PL-259 in-line connectors, as does the 42013 Mini Magnet Mount.

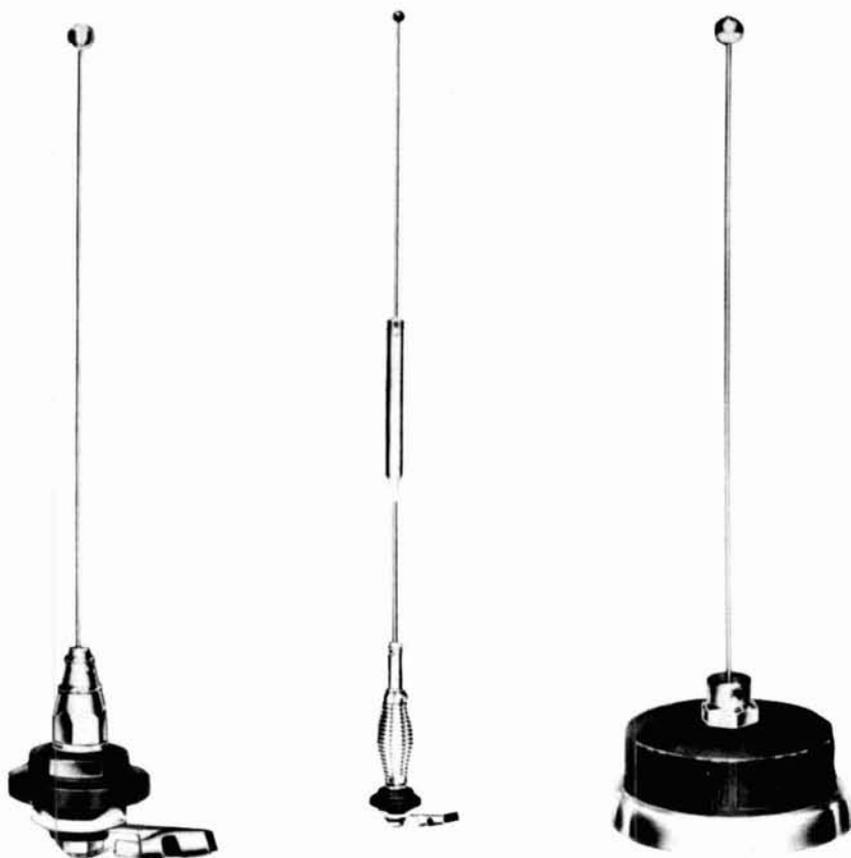For more information on the new miniature line, and other Antenna Incorporated antennas, write Randall J. Friedberg, Antenna Incorporated, 26301 Richmond Road, Cleveland, Ohio 44146, or phone (216) 464-7075.



When it comes to AMATEUR RADIO QSL's...



it's the
ONLY BOOK!
US or DX Listings

1980 callbooks

Here they are! The latest editions. World-famous Radio Amateur Callbooks, the most respected and complete listing of radio amateurs. Lists calls, license classes, address information. Loaded with special features such as call changes, prefixes of the world, standard time charts, world-wide QSL bureaus and more. The new 1980 Radio Amateur Callbooks are available now. The U.S. Edition features over 400,000 listings, over 120,000 changes from last year. The Foreign Edition, over 315,000 listings, over 90,000 call changes. Place your order now.

	Each	Shipping	Total
<input type="checkbox"/> US Callbook	\$16.95	\$1.75	\$18.70
<input type="checkbox"/> Foreign Callbook	\$15.95	\$1.75	\$17.70

Order both books at the same time for \$34.65, includes shipping.

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.75 for shipping. Illinois residents add 5% Sales Tax.



SPECIAL LIMITED OFFER!
**Amateur Radio
Emblem Patch**
only \$2.50 postpaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on jackets and caps. Sorry, no call letters.

ORDER TODAY!

RADIO AMATEUR
callbook INC.
Dept. FB 2
925 Sherwood Drive
Lake Bluff, IL 60044

Kantronics Announces Gold Label Series Tapes

Choosing and Using the Best Antenna

Find out how a better antenna adds power and versatility to your station. C-60 \$6.95

Ins and Outs of Running Your Own Ham Station

Learn the tricks of operating a station that make ham radio more fun. Set of 2 C-60 Tapes \$11.95

Sounds of Shortwave

Hear examples and explanations of many strange signals you've heard, plus a discussion of antennas and receivers. C-60 \$6.95

Understanding the Mysterious Ionosphere

Learn more about the ionized layers and improve your contacts. C-60 \$6.95

General Class Q and A Tape

Review theory and regulations covered on the General- or Technician-Class exam. C-60 \$6.95

The New Extra-Class Study Cassette

The basics to understand before taking the new Extra-Class exam. C-60 \$6.95

Please add \$1.00 shipping for one tape and \$2.00 shipping for 2 or more tapes.

Kantronics
(913) 842-7745
1202 E. 23rd Street
Lawrence, Kansas 66044



Heath IC timers self-instruction program

Heath Continuing Education, a division of Heath Company, Benton Harbor, Michigan, announces a new self-instruction program which covers integrated-circuit timers. The new program, Model EE-103, includes an introduction to the common types of IC timers, how each works, what they do, and where they are used.

Among the types of IC timers covered are the popular 555 and 556 series general-purpose timers; the 322 and 3905 wide-range, precision, monostable timers, and programmable timer/counters — including the 2240 binary programmable timer/counter; the 2250 BCD programmable timer/counter; and the 8260 seconds/minutes/hours BCD programmable timer/counter.

generators, phase-locked loops, universal appliance timers, as precise clock sources, and many others.

All of the electronic components required to perform the experiments are included with the program. The Heathkit ET-3300 Laboratory Breadboard is a recommended option.

The EE-103 IC Timers course is one of four Electronic Technology Series self-instructional programs. They are designed to provide detailed knowledge for engineers, technicians, and other technical people. Other programs in the series include Operational Amplifiers (EE-101, \$39.95), Active Filters (EE-102, \$29.95), and Phase-Locked Loops (EE-104, \$49.95).

For more information on the EE-103 IC Timers Self-Instruction Program — priced at \$39.95 mail-order FOB Benton Harbor, Michigan — send for a free catalog containing more than four hundred other useful electronic kits. Write Heath Company, Dept. 350-230, Benton Harbor, Michigan 49022, or pick up a copy at the nearest Heathkit Electronic Center (units of Veritechnology Products Corporation).

Heath Company is a subsidiary of Zenith Radio Corporation.

hand-held digital multimeter

The new Fluke Model 8024A, "The Investigator," 3½-digit digital multimeter detects logic states, finds loose connections, shorts, hot spots, and peaks (and holds them). Convenient visual and audio indications have also been added.

The 8024A provides all of the ranges, functions, and features of its highly successful predecessor, the Fluke 8020A, plus the ability to detect logic state changes from +0.8 volts ("0") to +2.5 volts ("1") at pulse rates (TTL) up to 20 kHz. An audio indication and arrows on the LCD display indicate "up" and "down", "1" or "0".

A peak and hold feature allows the



The program's self-teaching text, with the assistance of review quiz questions and lab experiments, completely covers how each timer works and how each is used — in logic functions, output drive circuits, time-delay relay circuits, wide-range pulse

GROTH-Type
COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole
- Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft ¼"x3"

TC2 \$10.00
TC3 \$11.00
Spinner Handle
Add \$1.50

Prices include UPS or Parcel Post

Model TC2: Skirt 2-1/8";
Knob 1-5/8"
Model TC3: Skirt 3";
Knob 2-3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

FREE BOOK FLYER

Whether you're interested in Amateur Radio, Electronics, Radio Astronomy, Old-Time Radio, VHF, SSB or just novels that involve Amateur Radio — you'll find a large selection of these books and more! Vast inventory of over 200 titles. Send your name and address to:

HAM RADIO'S BOOKSTORE
Greenville, NH 03048


We'll send you our most current book flyer and add your name to our bookstore list.

Antenna Baluns

user to concentrate on taking a reading when working on a sensitive or hazardous circuit then view the reading on the LCD display. This feature is provided for ac/dc volts and ac/dc current and provides a short term memory, also useful in capturing the peak value of a transient signal such as motor starting currents. It also provides the capability of detecting intermittent open circuits in connections or cables, sounding an audible signal as well as providing the visual display.

The 8024A will also read directly in Celsius degrees the output of any type "K" thermocouple, over a range of -20 C to 1265 C. This feature will be important to anyone servicing process control and air conditioning systems, detecting heat rise in electrical motors, and system or circuit components. Whenever it becomes necessary to measure temperature in operating systems or hardware, the 8024A provides an early and economical solution to these types of problems.

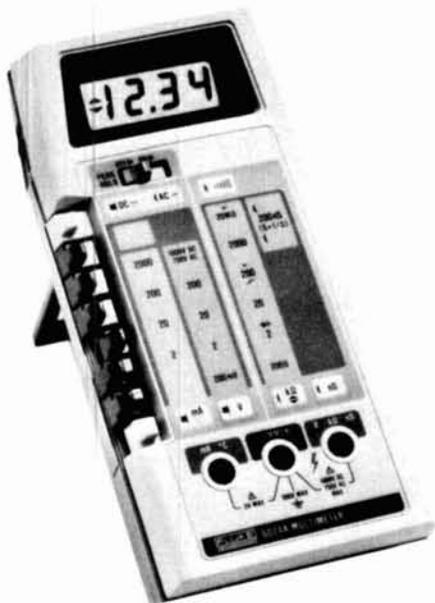For additional information, write Frank Partin, at John Fluke Mfg. Co., P.O. Box 43210, Mountlake Terrace, Washington 98043, or phone (206) 774-2322.




All Palomar Engineers products are made in U.S.A. Since 1965, manufacturers of Amateur Radio equipment only.



1 Kw CW, 3 Kw PEP input.
For dipoles, inverted Vees,
beams, quads.
Dependable. Takes
temporary overloads in
stride.

Specify 1:1 or 4:1 ratio.

Model 1K \$32.50

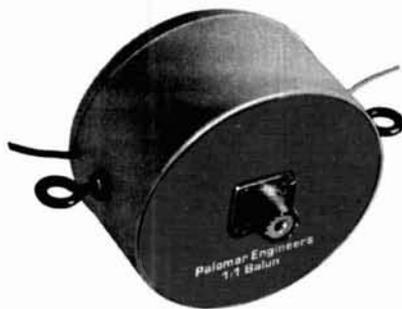

2 Kw CW, 6 Kw PEP input.
Far more rugged than any
other balun made for
amateur use.

Specify 1:1 or 4:1 ratio.

Model 2K \$42.50



2 Kw CW, 6 Kw PEP input.
Our heavy duty balun with
mounting bracket for 2''
mast or boom.

Specify 1:1 or 4:1 ratio.

Beam Balun \$47.50

Only Palomar Baluns Have All These Features

- RF toroidal core for highest efficiency.
- Teflon insulated wire.
- Stainless steel hardware. Won't rust.
- Epoxy filled case. Waterproof.
- Wideband 1.7 to 30 MHz.
- White case to reflect the sun.
- Lightning protection built in.

Free brochure sent on request

How many lightweight baluns have you burned out already? Install the balun that will stay up there working year after year.

To order, add \$3 shipping/handling. California residents add sales tax.



Palomar Engineers

Box 455, Escondido, CA. 92025 • Phone: [714] 747-3343



Bind 'em and Find 'em

Keep those valuable issues of both Ham Radio and HORIZONS like new. Prevent smears, tears and dog ears. Bind 'em together and enjoy for years to come. You'll be happy you did!

★ ★ ★

HAM RADIO BINDERS

Beautiful buckram binders complete with date labels. Available in our new large size to accommodate HAM RADIO'S hefty issues.

HR-BDL Each Just \$6.95, 3 for \$17.95

HAM RADIO MAGAZINE FILES

Your collection of HAM RADIO Magazines is a valuable resource. Here's a brand new, inexpensive way to store them. These sturdy cardboard magazine files keep them clean, neat and up front where you can use them for quick and easy reference.

HR-HRMF \$1.95 each, 3/\$4.95

HAM RADIO HORIZONS BINDERS

Handsome washable binders complete with date labels.

HR-HRDL

Each Just \$6.95, 3 for \$17.95

HORIZONS MAGAZINE FILES

Your collection of Ham Radio HORIZONS is a valuable resource. Here's a brand new, inexpensive way to store them. These sturdy cardboard magazine files keep them clean, neat and up front where you can use them for quick and easy reference.

HR-HRHF

\$1.95 each, 3/\$4.95

ORDER TODAY

Ham Radio's Bookstore

GREENVILLE, NEW HAMPSHIRE 03048

OR CALL TOLL FREE 1 (800) 258-5353

BINDERS

HR-BDL \$6.95 ea.

HR-HRDL 3/\$17.95

HR-HRMF \$1.95 ea.

HR-HRHF 3/\$4.95

CASH

CHARGE

MC

VISA

Exp. _____ Card Number _____

Name _____

Address _____

City _____ State _____ Zip _____

IRON POWDER and FERRITE PRODUCTS

AMIDON Associates

Fast, Reliable Service Since 1963

Small Orders Welcome

Free 'Tech-Data' Flyer


Toroidal Cores, Shielding Beads, Shielded Coil Forms
Ferrite Rods, Pot Cores, Baluns, Etc.

12033 OTSEGO STREET, NORTH HOLLYWOOD, CALIFORNIA 91607

Isotron Antennas

THE ULTIMATE space savers...
for 80 and 40 meters.

Designed and proved by W0BEJA

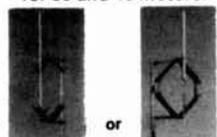

Hear on 7245 kHz at 3 & 5 PM MDT

80 Meters

Length Weight Bandwidth Feed Price

40 Meters

4 1/2 ft.
8 lbs.
110 kHz*
500 coax
\$54.95

31 in.
4 lbs.
250 kHz*
500 coax
\$44.95

*Limits for 2:1 SWR; center frequency adjustable

Isotron antennas need no radials or matching devices. Feed with 500 coax. For indoor or outdoor mounting. Excellent for all amateur uses.



BILAL COMPANY

(303) 687-3219



STAR ROUTE

FLORISSANT, CO. 80816

HAM SCAN II

The only full-band scanner with one channel of memory for the following rigs: KENWOOD 7625, 7600, 7400A; KDK 2015R, 2016A; CLEGG FM-28; MIDLAND 13-510; HEATHKIT HW-2036; Others coming soon.

- Adds one channel of memory to any above rig
 - Selectable scan range — up to 4 MHz (— by position of radio's MHz switch)
 - Scan rate 200 kHz/sec. in 10 kHz steps (— 3-second pause on all active channels)
 - Mike-mounted switch provides 3 functions: start/stop, remote frequency incrementing, and transmit interlock while actively scanning.
 - Scanner mounts inside radio — no external box
 - Assembled, tested, and guaranteed — specify type of radio
- Ask about our TM-1 timer module, our TC-2 sub-audible tone encoder, and our Ham Scan I for the Yaesu FT227R

Technical Clinic

P.O. BOX 636

STERLING HTS. MI 48078

Phone Orders Call: (313) 286-4836



Larsen improved magnetic mount

Larsen Electronics, Inc., of Vancouver, Washington, has improved their Magnetic Mount design to give it even stronger holding power and reduce even further the chance of scratching the vehicle finish.

Larsen's super-strength magnetic assembly has been engineered to closer tolerances for more holding power per square inch. Every magnetic mount leaves the Larsen factory fully "charged" to maximum flux density.

In addition, the Larsen Magnetic Mount has a new boot of resilient Nordel that will not crack or harden, even with long-term exposure to weather and sunlight. This rubber-like boot also minimizes the possibility of scratching the finish of the vehicle to which it is attached.



Amateur Radio

Just getting started? This book is ideal for you. It will help you get your first license. Or if you already have your ticket, the book will serve as your handy station manual. Written by Bill Lowry, W1VV, it includes a brief description of major activities, equipment and procedures to help the new ham decide where to begin, what equipment to buy initially, and how to make contacts with other hams after the station is assembled. Most importantly, this book tells the beginner how to study for the test, and presents the facts that must be learned in order to pass the written part of the exam. It includes complete FCC rules and official study guide for all license classes. Also included is a colorful call-area wall map.

Just \$6.95

• *Amateur Radio Poster.* Add this beautiful poster to your amateur radio station. Rich-in-color lithograph is produced from artwork shown on Amateur Radio book. Suitable for framing.

Just \$3.50



LOOKING FOR A SPECIAL BOOK?



Practical Antennas for the Radio Amateur

Brand new antenna book in a new easy-to-read format with big diagrams. You've never seen an antenna book quite like this! Written by well-known author, Robert Myers, W1XT, it tells you how to choose, use and build your antenna system. Here's what you get: How to build practical beams, quads and wire antennas . . . Compute generated beam headings to every known country in the world . . . Charts and tables to eliminate tricky calculations . . . Practical ideas for the newcomer . . . OSCAR antennas . . . Complete bibliography of magazine articles on antennas . . . Antenna safety . . . Trick antennas for portable work . . . Tips on how to keep your antenna up. Durable vinyl cover. *Only \$9.95*

Ham Radio's Bookstore

Greenville, NH 03048

Amateur Radio Poster Practical Antennas

Name _____


Street _____

City _____ State _____ Zip _____

Please enclose proper amount for books plus \$1.00 shipping or credit card information.

Order NOW!!

flea market

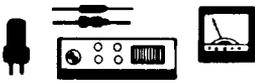

RATES Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N.H. 03048.

OMNI A/B SERIES with 217, 218, 248, 243, 6 months old, \$899. SB-221 new, \$500., SB-634 \$125., or will trade any of above for Collins gear KWM-2, S-line, 30-L1, accessories, etc. John, N1JM, (315) 699-3268.

MOBILE HF ANTENNA 3.2-30 MHz inclusive, 750 watts PEP, center loaded, tuned from the base, eliminating coil changing or removing from mount. Less than 1.5 to 1 VSWR thru entire coverage. \$129.95 ea. plus shipping. Contact your local dealer, if none in your area order direct. Antecq, Inc., Route One, Hansen, Idaho 83334. (208) 423-4100. Master Chg., and VISA accepted. Dealer and factory rep. Inquiries invited.

WANTED: Eimac SK-710 socket for 4CX300. R. Guerin, 24 High Range Rd., Londonderry, NH 03053. (603) 432-7305.

VERY In-ter-est-Ing! Next 3 Issues \$1. "The Ham Trader", Wheaton, IL 60187.

NEW, Exciting Amateur Operators' Picture Yearbook, sponsored by the First United Pentecostal Church, Inc. Send call sign, address, photo, and \$20 to Lee Kent, WD0FFZ, P. O. Box 236, Malden, MO 63863. You will receive one copy of the book for each \$20. Tell everyone.

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
F. Baati
Hauptplatz 5
A-2700 Wiener Neustadt
Austria

Ham Radio Holland
MRL Electronica
Postbus 88
NL-2204 Delt
Holland

Ham Radio Belgium
Sterehouse
Brusselsesteenweg 416
B-8218 Gent
Belgium

Ham Radio Italy
G. Vulpetti
P.O. Box 37
I-22083 Cantu
Italy

Ham Radio Canada
Box 400, Goderich
Ontario, Canada N7A 4C7

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7860 Loerrach
West Germany

Ham Radio Europe
Box 444
S-194 04 Upplands Vasby
Sweden

Ham Radio UK
P.O. Box 83, Harrow
Middlesex HA3 6HS
England

Ham Radio France
SM Electronic
20 bis, Ave des Clarions
F-96000 Auxerre
France

Holland Radio
143 Greenway
Greenaside, Johannesburg
Republic of South Africa

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7860 Loerrach
West Germany

BUY, SELL, TRADE new and used amateur radio and computer equipment. Monthly publication. Lifetime subscription \$5.00. Send to Nuts & Volts, Box 111-F, Placentia, California 92670.

FOR SALE: SATELLITE TV 3.7-4.2 GHz down converter 70 MHz I-F PCB with parts provision for on board local oscillator, \$75.00. Birkhill 4 GHz LNA PCB bipolar or gasfet, \$15. Both for \$25.00 — SASE to Norman Gillaspie, 2225 Sharon Rd., 224 Menlo Park, CA 94025.

WANTED: Radio Frequency Amplifier AM 494/GR. Any condition, with or without tubes — Top Dollar. K8MKJ, 6128 Lodi Lane, Salline, MI 48176.

SPECIAL SALE: Alliance HD-73 Heavy Duty Rotor \$99.99 plus \$3.00 shipping Continental USA. MC and Visa accepted. Scanner World, USA., 10-H New Scotland Ave., Albany, NY 12208. 518-436-9606.

RECONDITIONED TEST EQUIPMENT for sale. Catalog \$5.00. Walter, 2697 Nickel, San Pablo, CA 94806.

10-40 MHz SYNTHESIZER provides continuous coverage 1-31 MHz in 100 Hertz steps with your 9-MHz I-F. PCB, kit, or wired. SASE for data sheet. Petitt Logic Systems, P.O. Box 51, Oak Harbor, WA 98277.

WANTED: Early Hallicrafter receivers, transmitter, accessories, parts, manuals for my collection. Special interest in silver colored panel receivers and ones with "airplane" dials. Also need "ultra Skyrider" SX-10, "Skyrider Commercial" SX-12 and others. Chuck Dachis, WDEOG, 4500 Russell, Austin, TX 78745.

RADIO BROADCAST TECHNICIANS: Voice of America has opportunities in Washington, D.C. for qualified Radio Broadcast Technicians. These positions require a comprehensive background in the recording, maintenance, studio and field areas. Salary range: \$10.59-\$14.87 per hour depending on qualifications. U.S. citizenship required. Submit standard Federal application form, SF-171, to International Communication Agency, MGT/PDE (1-78) Washington, D.C. 20547. An Equal Opportunity Employer.

WANTED: EICO #720 or #723 xmt, Hallicrafters HT40 xmt and HA5 vfo. J. Titus, Box 242, Blacksburg, VA 24060 (703) 952-2684.

CB TO 10 METER PROFESSIONALS: Your rig or buy ours — AM/SSB/CW. Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412; (616) 924-4561.

MOTOROLA ALL SOLID-STATE MOTRAN RADIOS. Model X43LSN-2170, four frequency, transmit 150 MC (30W), receive 450 MC. Will operate in Ham Bands. No modification required. Large stock available. \$150.00 each. Omni Communications. Call (312) 852-0738.

QSL'S: No stock designs! Your art or ours; photos, originals, 50¢ for samples & details (refundable). Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412.

HAM RADIO REPAIR, alignment. Prompt, expert, reasonable. "Grid" Gridley, W4GJO, Route 2, Box 138B, Rising Fawn, GA 30738.

TRANSMITTER TECHNICIANS: Voice of America has opportunities for qualified technicians at VOA stations near Delano, California, and Greenville, North Carolina. Duties include operations/maintenance of high power shortwave transmitters and related facilities on shift basis. Minimum qualifications: 3-years chief broadcast engineer 5 to 50 KW, or 3-years supervisor of operations/maintenance high power military transmitting plant, or equivalent. U.S. citizenship required. Starting salary \$18,760. Submit standard Federal application form, SF-171, to International Communication Agency, MGT/PDE (1-78) Washington, D.C. 20547. An Equal Opportunity Employer.

MICROWAVE TV downconverters, preamps, parabolic dish antennas, remote tuning. Covers 2000 MHz band. Write for information. LAB-TRONICS, Box 171, Rogers, MN 55374.

NEED HELP for your Novice or General ticket? Recorded audio-visual theory instruction. No electronic background required. Free information. Amateur License, P.O. Box 8015, Norfolk, VA 23508.

RTTY: Solid state automatic CQer. Board with PROM programmed your call \$21.50 ppd. Wired/tested \$29.50 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

ATLAS OWNERS DD8-C and 350XL Digital Dial/Frequency Counters. \$175.00 + Shipping (Calif. add tax). Mical Devices, Box 343, Vista, CA 92083.

ANTIQUE (PRE-1950) TELEVISION SETS WANTED. Will pay top dollar for unusual or pre-WWII sets, Arnold Chase, 9 Rushleigh Road, West Hartford, Connecticut 06117 (203) 521-5280.

VARIABLE POWER SUPPLY KITS
12-28 VDC ADJ @ 250 MA
5-12 VDC ADJ @ 500 MA
PARTS INCLUDED ARE:
*TRANSFORMER *PC BOARD
*POT & RESIS. *HEAT SINK
*1000UF@35VDC *DIODES
*REG. 7805-7812 *HARDWARE
*OSC. SUP. CAP. *INSTRUCTION

12-28VDC PS-0074 \$7.95
5-12VDC PS-0073 \$7.95

Miniature Toggle Switches

1 EA. 10 EA.
SPDT \$1.00 \$8.95
DPDT \$1.50 \$12.95

DIODES

PIV AMP	COST
100 5	\$1.00
100 12	3/\$1.00
100 40	\$1.35
400 450	\$18.50

2200UF 16VDC 25¢

LED JUMBOS RED

1V FOR \$1.00
100 FOR \$7.95

SOUND ALERT
6-28 VDC
3-14 MA
\$4.95

SEND FOR NEW CATALOG

FANS 100 CFM
115VAC 60HZ
4.5" X 1.5"
USED \$6.95
GUARANTEED
NEW \$12.95

MPF-131
N-CHANNEL DUAL GATE
MOS-FET GOOD FOR 60
& 200MHZ. DATA SHEET
HOUSE MARKED. **50¢**

Touch-Tone Housing.
BLACK only...\$3.50

50 ohm COAX
RG 174U 25 FT.
\$1.75

.1OHM 5WATT RESISTORS
5 FOR \$1.00

BRIDGES
25 AMP.
50 PIV
\$1.75 EA. 3 FOR \$5.00

POWER SUPPLY MODULE
RATED AT 12V @ 2.5A. CAN
BE MODIFIED BY CHANGING
THE ZENER.
PARTS: 4-3A DIODES, 1-2.5A
FUSE, 1-2200MF @ 35V CAP.,
1-12V ZENER, 1-PASS TRANS.
WITH HEAT SINK. \$4.95

COAX RELAY
12 VDC SPDT
500 MHZ @ 100 WATTS
SBS-450 BLOS SUBST 20A
CONTACT. \$9.95

HIGH VOLTAGE SUPPLY
15KVDC @ 30 WATTS
INPUT 115VAC 60HZ
\$9.95

ANTENNAS

ANS PTBS BNC STRAIGHT
ANS PTUS UHF STRAIGHT

ANS PTB90 BNC 90° ELBOW
ANS PTU90 UHF 90° ELBOW

ANS PTBAJ BNC ADJ ELBOW
ANS PTUAJ UHF ADJ ELBOW

\$7.95

ALL ANTENNAS ARE FOR TWO METERS

'N'-F/PANEL UG58 \$2.25
'N'-M/CABLE UG21B \$2.95
'N'-F/UHF-M UG83 \$4.95
'N'-M/UHF-M UG146 \$4.95

UHF 90° F/M M359 \$2.50
UHF 112° F/M M358 \$2.95
BNC 90° F/M UG306 \$3.75
BNC 112° F/M UG274 \$4.00

UHF-M/UHF-M DM-1 \$2.50
UHF-F/UHF-F PL258 \$1.50
BNC-M/BNC-M UG491 \$3.85
BNC-F/BNC-F UG914 \$2.25

BNC-F/CABLE UG1094 \$1.00
BNC-M/CABLE UG88 \$1.35
BNC-T/UHF-M UG273 \$3.00
BNC-M/UHF-F UG255 \$3.50

UHF-F/PANEL SO-259 \$7.65
UHF-M/CABLE M-259 \$7.65
BNC ADAPTER R289 \$9.17
UHF 178 \$2.95

M P J **Marlin P. Jones & Assoc.**
P.O. Box 12685-E
Lake Park, FL 33403
(305) 848-8236

MC, VISA, CORD ACCEPTED
*ADD \$1. ORDERS UNDER \$10. *FLA. RES. 4% SALES TAX
PLEASE ADD SUFFICIENT POSTAGE

Alaska Microwave Labs

4335 E. 5TH STREET
ANCHORAGE, ALASKA 99504
(907) 338-0340

TRANSISTORS

MRF901 FT4.5GHZ	\$ 3.25
BFR90 FT5.0GHZ	\$ 3.00
NEC 02137 FT4.5GHZ	\$ 3.25

HOT CARRIER DIODES

MBD101 UHF—MICROWAVE	\$ 1.50
ND4131 4GHZ NF—5.75 DB	\$ 13.25
1.4GHZ NF—6.5 DB	\$ 2.00

CHIP CAPACITORS

10 () 47 () 1000 () P1	\$.60
---------------------------	--------

RF-IF I.C. AMP

MWA-110 RF-IF AMPLIFIER I.C. 1 TO 400 MC 14 DB GAIN TYP 3 TERMINAL IN, OUT, & GROUND	\$ 7.95
---	---------

DUAL GATE MOSFET

RCA 40673	\$ 1.50
-----------	---------

COAX CONNECTORS

BNC CHASSIS MOUNT SQUARE FLANGE	\$ 1.87
BNC PLUG FOR RG-58	\$ 1.87
SMA CHASSIS MOUNT SQUARE FLANGE	\$ 5.90
SMA PLUG FOR RG-58	\$ 6.57
SMA PLUG FOR RG-174	\$ 6.57
TYPE N CHASSIS MOUNT SQUARE FLANGE	\$ 3.20
TYPE N PLUG FOR RG-9/RG-8	\$ 3.69

FEED-THRU CAPACITORS

500 PF	\$.50
--------	--------

TEFLON CIRCUIT BOARD

APPROX 3.5" x 5.0" x .010	\$ 5.50
APPROX 3.5" x 5.0" x .0312	\$ 6.50

CHIP RESISTORS

50 OHM 1/2 WATT	\$ 1.50
-----------------	---------

CHIP TRIMMERS

Triko 201—10M 5—3P() 1—8P()	\$ 2.50
-------------------------------	---------

**OPEN AT 8PM EST
CLOSED AT 8PM PST**

IF YOU DO NOT SEE

WHAT YOU WANT ASK

ORDERS ARE POSTAGE PAID

COD—VISA—MASTERCARD



\$109.95
P. PD.
USA

10 Watts In - 75 Watts Out

2 Meter FM or SSB Amplifier

Complete Kit Model 875-K

See article in Sept. 79 QST pgs. 11-16

COMMUNICATION CONCEPTS, INC.

2648 North Aragon Ave.

MASTER CHARGE Dayton, Ohio 45420 VISA
Phone: (513) 296-1411

UHF Kits Also Available Send For FREE Data Sheet

SYNTHESIZED SIGNAL GENERATOR



• Covers 100 to 179.999 MHz in 1 kHz steps with thumb-wheel dial • Accuracy .00001% at all frequencies • Internal frequency modulation from 0 to over 100 kHz at a 1 kHz rate • Spurs and noise at least 60dB below carrier • RF output adjustable from 50 to 500mv across 50 ohms • Operates on 12vdc @ 1/2 amp • Price \$299.95 plus shipping.

In stock for immediate shipping. Overnight delivery available at extra cost. Phone: (212) 468-2720.

VANGUARD LABS

196-23 Jamacia Ave. Hollis, NY 11423

MANUALS for most ham gear 1937/1970. Send 25¢ for "Manual Catalog." H.I., Inc., Box H864, Council Bluffs, Iowa 51502.

SOLAR CELLS .4v, 4" diameter, 2 amps. \$8.75, 10 for \$85.00 plus shipping. Kenneth Foster, 1742 Dowd, St. Louis, MO 63136. (314) 522-6667.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 98362.

TEST EQUIPMENT: Tektronix 1L20 spectrum analyzer, 1 to 4200 MHz \$1,000.00. AIL precision test receiver \$300.00 (used for extremely accurate noise figure measurements). AIL automatic noise meter \$200.00. Hewlett-Packard noise source, 1 to 500 MHz \$80.00. K3AP, Parkhurst Drive, Salisbury, MD 21801. (301) 742-7333.

BUY-SELL-TRADE. Send \$1.00 for catalog. Give name address and call letters. Complete stock of major brands new and reconditioned amateur radio equipment. Call for best deals. We buy Collins, Drake, Swan, etc. Associated Radio, 8012 Conser, Overland Park, KS 66204. (913) 381-5900.

WANTED: A GR 1606A/B rf impedance bridge or HP 250A/B RX meter. Please describe condition and price. W0VDJ, 250 Ogden St., Denver, Colorado 80218.

CW/SSB FILTERS: IC audio install in any radio, sharp CW, stagger tuned SSB — \$15, \$32. SASE info: W8CBB, 80 W. Mennonite, Aurora, OH 44202.

FREE HAM/COMPUTER NEWSLETTER: Send self-addressed stamped envelope for your copy. W5YI; P.O. Box #10101; Dallas, Texas 75207.

TO SELL: Mirage B1016 2-meter linear amplifier with pre-amp, like new — \$195. York AM-FM stereo 8-track, good condition, \$75. Radio Shack variable DC supply, good condition, \$15. ADC equalizer, new condition, \$55. Yaesu CPU-2500R 2 meter mobile, like new — \$300. Optex photostat machine, \$100. Mitchell Rakoff, 6433 98th St., Rego Park, NY 11374. Phone: (212) 830-0097.

ICOM INTERNATIONAL USER'S CLUB. Details SASE NBRT, Pohorence, 9600 Kickapoo Pass, Streetsboro, Ohio 44240.

THE MOR-GAIN HD DIPOLES are most advanced, highest performance multi-band HF dipole antennas available. Patented design provides length one-half of conventional dipoles. 50 ohm feed on all bands, no tuner or balun required. Can be installed as inverted VEE. Thousands in use world wide. 22 models available including two models engineered for optimum performance for the novice bands. The Mor-Gain HD dipoles N/T series are the only commercial antennas specifically designed to meet the operational requirements of the novice license. Our 1-year warranty is backed by nearly 20 years of HD dipole production experience. Write or call today for our 5-page brochure. (913) 682-3142. Mor-Gain, P.O. Box 329H, Leavenworth, KS 66048.

WANTED: Hallicrafters SX88 Band Selector Drive Belt (Made like timing belt) K9EY, P.O. Box 1225, Bloomington, Indiana 47402.

DX, YOU BET! THE DX BULLETIN — Best weekly DX info in the world. For FREE sample copy, send business-size SASE to: The DX Bulletin, 306 Vernon Avenue, Vernon, Connecticut 06066.

WANTED: Microwave Dish 6 feet or larger. Willis, W9FGJ, 402 E. Cole St., DuQuoin, IL 62832. (618) 542-2274.

STOP LOOKING for a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. Now more than ever where you buy is as important as what you buy. We are factory-authorized dealers for Kenwood, Drake, Yaesu, Collins, Wilson, Ten-Tec, ICOM, DenTron, MFJ, Tempo, Regency, Hy-Gain, Mosley, Alpha, CushCraft, Swan and many more. Write or call us today for our low quote and try our personal and friendly Hoosier Service. HOOSIER ELECTRONICS, P.O. Box 2001, Terre Haute, Indiana 47802. (812) 238-1456.

SATELLITE TV RECEPTION: 36-page "How-To" book. Complete reprint of Bob Cooper's 7-article series from *Radio Electronics* magazine. \$6 postpaid, U.S. and Canada. All others add \$3 postage. N.Y.S. residents add 48¢ sales tax. Satellite TV Reception, Box C, Radio Electronics, 45 E. 17th Street, New York, N.Y. 10003.

MACROTRONICS M800-M80 RTTY SYSTEM for TSR80 microcomputer. Hardware and software tapes for CW, RTTY, and ASCII. Manual and bulletins. \$130.00. Write: A. W. Hubbard, 5705 Junonia-S.P.V., Ft. Myers, FL 33908.

HW-2036A WITH MICODER II and QST digital readout. \$205.00. WD4GRI, 1907 Lodgepole, N. Augusta, SC 29841. (803) 279-6513.

NEGATIVES MADE FOR PC BOARDS from magazine articles (up to 5" by 7"). Send page and \$6.00 or write: Graham Johnson Studio, 2 Spruce Terrace, Portland, CT 06480.

Coming Events

NEW YORK: HAM-O-RAMA '80 on September 12th and 13th at the Erie County Fairgrounds in Hamburg. Exhibits, tech programs, prizes, flea market. Plenty of free parking, free RV hookups. Advance tickets \$3 — contact Ron Brodowski, KC2P, 260 Hilltop Drive, Elma, NY 14059. (716) 652-6754.

RADIO EXPO '80' Lake County fair grounds, Rt. 45 & 120. Sept. 6 & 7 — advanced tickets \$2.00, \$3.00 at gate. Write: Radio Expo Tickets, P.O. Box 1532, Evanston, IL 60204. Exhibitor information call (312) BST-EXPO.

ILLINOIS: Fox River Radio League Hamfest, Sunday, August 24th, Kane County Fairgrounds, St. Charles. Free outside flea market - inside display area. Table discounts available. Contact Gary Senesac, KA9ADP, 926 Britta Lane, Batavia, IL 60510. Tickets: \$1.50 advance; \$2 at gate. Contact Jerry Frieders, W9ZGP, 1501 Molitor Rd., Aurora, IL 60505. Talk-in on 146.94.

OHIO: The Way International of New Knoxville Ohio annual Rock Of Ages festival on August 10-16. Christian Music Festival on 3.930, 7.230, 14.330, and 146.52 MHz. Commemorative "ROA 1980" QSL's will be sent to those stations worked.

NEW JERSEY: The Englewood Amateur Radio Association's 21st annual QSO party from 2000 UTC Saturday, August 16 to 0700 UTC Sunday, August 17 and from 1300 UTC Sunday, August 17 to 0200 UTC Monday, August 18. Phone and CW are considered same contest. A station may be contacted once on each band — phone and CW are considered separate bands. New Jersey stations may work other New Jersey stations. General call is "CQ New Jersey" or "CQ NJ". Suggested frequencies are: 1810, 3535, 3900, 7035, 7135, 7235, 14035, 14280, 21100, 21355, 28100, 28610, 50-50.5 and 144-146. Suggest phone activity on even hours; 15 meters on odd hours (1500 to 2100 UTC); 160 meters at 0500 UTC. Exchange consists of QSO number, RST and QTH (ARRL section or country). Logs, showing UTC date and time, band, and emission, must be received no later than September 13, 1980, at: Englewood ARA, Inc., PO Box 528, Englewood, NJ 07631 with #10 SASE enclosed.

NEW JERSEY: Sussex County Amateur Radio Club's second annual hamfest at Sussex County Farm and Horse Show grounds on Plains Rd. off Rte. 206 in Augusta, NJ. Indoor and outdoor flea market. Outdoor sellers at door: \$5 or \$4 preregistered. Indoor sellers: \$6 at door or \$5 preregistered. \$1 door prize ticket. Free admission. For info and preregistration: Sussex Co. A.R.C., P.O. Box 11, Newton, NJ 07860 or Ed Woznicki, AC2A, (201) 852-3268. Talk-in on 147.90/30 and 146.52 simplex.

RHODE ISLAND: East Bay Amateur Wireless Association's QSO Party. Two periods: August 16 1700-0500 August 17, and August 17 0100-1000 August 18. Stations work other R.I. stations and the rest of the world. Same band may be worked once per band and mode. Frequencies: CW: 1810, 3550, 3710, 7050, 7110, 14050, 21050, 21110, 28050, 28110. Phone: 3900, 7260, 14300, 21360, 28600, 50.110, 144.2. Use of FM simplex is encouraged. (NO REPEATERS). Logging: must show: date, time (GMT), call, exchange, band and mode. Deadline: SASE and logs by September 15.

OHIO: Warren A.R.S. Hamfest, August 17, 1980 at the Trumbull Branch, Kent State University. Huge flea market, tech forums, DX programs, dealer displays, XYL activities. QSL W.A.R.A., P.O. Box 809, Warren, Ohio 44482.

FINDLAY HAMFEST: The 38th Annual Findlay Hamfest greets you on Sept. 7th with a fine new indoor/outdoor location, The Hancock Recreational Center, just east of I-75 exit 161, on the north edge of Findlay, 40 miles south of Toledo. Main Prizes: a TS-120s W/supply, two TR-2400's, and an AT-120 matcher. Tickets \$2.00 advance and \$2.50 at the door. Reserve your tables early: \$2.50 per 1/2. Open Saturday 17:00 till 22:00 for forums and set-up, Sunday at 05:00. Join the over 8000 people attending Findlay Hamfest this year and spend your bucks on the best! For tickets, info, and reservations send S.A.S.E. to P.O. Box 587, Findlay, Ohio 45840.

TEXAS: Golden Spread Hamfest and convention on the evening of August 1 and all day August 2 and 3 at the Student Activities Center of West Texas State University, Canyon, Texas. Commercial displays, Swapfest, ARES program, Station operation demonstration, guided tours, bingo, Navy and Army MARS meetings, ARRL forum, Tech sessions and many door prizes. Pre-registration is \$5.00. At the door: \$6.00. Sponsored by the Panhandle Amateur Radio Club of Amarillo, Texas. Talk-in on 146.07.67, 147.99/39, and 146.52.

Announcing the Heathkit VF-7401 2-meter FM Digital Scanning Transceiver



Optional Micoder II Microphone/Auto Patch Encoder lets you phone through repeaters with auto patch input. Draws power from the 7401, so no mike battery is necessary.

The Squelch Control also functions as the receiver's sensitivity control to stop scanning only upon reception of "full-quieting" signals, skipping the weak ones.

The 100 kHz Selector button controls the VF-7401's tuning in 100 kHz increments. **The 7401's 1 MHz Selector button** lets you choose any 1 MHz segment of the 2-meter band.

The 10 kHz Selector advances in 10 kHz steps. In Scan, as it recycles from "9" to "0," it also causes the 100 kHz readout to advance by one digit. Depress once to resume scan function.

LED indicates 5 kHz position.

The 0 kHz/5 kHz Switch gives you an effective choice of 800/2-meter channels in 5 kHz steps.

Dim/Bright Switch for bright illumination of frequency read-out and meter for daytime, and lower intensity for safe mobile operation at night.

The Manual/Scan Switch lets you choose your frequency manually, or have the VF-7401 find an active channel for you.

Lock/Latch Switch. In Scan Latch mode, a channel latch-up signal inhibits scan circuits when signal is detected, and the 7401 stays on that frequency. If it detects a 4-8 second break in received signal, scanning resumes. In the Scan-Lock mode, once the receiver scans to a signal, it remains on that channel until reset.

More features that make the VF-7401 the 2-meter rig that belongs in your shack and vehicle

No more searching through repeater guides while mobiling in unfamiliar territory - your new Heathkit VF-7401 will find the active channels for you. It will even alert you to band openings. You're going to enjoy building your VF-7401... and you're going to love using it. The VF-7401, the ultimate 2-meter rig... from the more than 200 Hams at Heath.

- Adjustable, 15-watt (nominal), solid-state, narrow-band FM Transceiver. Fully synthesized digital circuitry provides full-band coverage without need for added crystals.

- All-new, state-of-the-art circuits provide the exciting, exclusive features of 1 MHz bandwidth scanning, and Scan Lock/Latch capability on 2-meters.
- A receiver hotter than Heath's HW-2036A features dual-gate MOSFET front-end to minimize overload and adjacent-channel interference.
- "Power-up" on a pre-programmed frequency of your own choice, such as your favorite repeater.
- Convenient detachable mike using 4-pin connector.
- Power to the Micoder II Microphone (if used) eliminates need for a battery.
- Sturdy SO-239 rear-panel antenna jack.
- Chassis-mounted power and external speaker plugs.
- Improved synthesizer, eliminating need for panel mounted sync lock light.
- Tuning for Power Amplifier and output power level adjustment is accessible without removing case.
- Capability of mobile or base operation (with Model VFA-7401-1 AC Power Supply - 13.8 V at 4A nominal, transmit).



SEND FOR FREE CATALOG

The new VF-7401 is featured in the latest Heathkit Catalog. For a free copy write: Heath Company, Dept. 122-684, Benton Harbor, MI 49022. Or visit the nearest Heathkit Electronic Center in the U.S. or Canada where Heathkit products are displayed, sold and serviced. See the white pages of your phone book for location. In the U.S., Heathkit Electronic Centers are units of Veritechnology Electronics Corporation.

This device has not been approved by the Federal Communications Commission. This device is not, and may not be, offered for sale or lease, or sold or leased until the approval of the FCC has been obtained.



Heathkit®

THERE'S MORE FOR THE HAM AT HEATH!

MINIATURE AUTOMATIC MORSE CODE RADIO STATION IDENTIFIER MODEL - 97813



REDUCED 40%, NOW \$59.95

COMPLIES WITH NEW FCC RULES, PARTS 89, 91, 93, 95
MULTI-MODE OPERATION: MANUAL, SEMI-AUTO AND AUTO.

MANUAL MODE — A pushbutton switch triggers the identifier which keys the transmitter for the duration of the ID cycle.

SEMI-AUTO MODE — The PTT line activates the ID'er if the repeat interval time has elapsed and keeps the transmitter keyed throughout the duration of the ID cycle.

AUTO MODE — The identifier will key the transmitter and ID every time the repeat interval time has elapsed.

CONNECTS DIRECTLY TO MICROPHONE AND PTT INPUTS OF MOST TRANSMITTERS. MINIATURE SIZE MAKES IT FEASIBLE TO MOUNT INSIDE THE TRANSMITTER.

PROGRAMMABLE CODE SPEED, TONE, AND REPEAT TIME.

ADJUSTABLE CODE AUDIO LEVEL.

PREPROGRAMMED MEMORY ELEMENTS — 254 OR (510 BIT) (OPTIONAL)

SIZE — 1 X 4 INCHES

INCLUDES SWITCHES, WIRING AND INSTRUCTION MANUAL.

MODEL 97813 — NOW ONLY \$59.95 assembled & tested

MODEL 11765 — Beacon CW ID'er with programmable code speed • great for 1750 meter band • 254 bit memory; 510 bit optional • 1.3 x 2.0 PCB • LIST PRICE \$24.95/kit; \$34.95/assembly

All orders must be prepaid or C.O.D. allow four weeks delivery. CA. res. add sales tax. Additional preprogrammed memory elements available. Include \$3.00 shpg/hdng on all orders. One year warranty.

Securatron Co.

P.O. Box 32145 • San Jose, Ca. 95152
 Phone (408) 294-8383

Digitrex Electronics

PA-19 Wideband Preamplifier

- 2 to 200 MHz Bandwidth (3dB Fomts)
- 19 dB Gain
- 50 Ohms Input & Output Impedance
- Tiny PC Board Size (7/8" x 1-5/8")
- Absolutely No Tuning Required
- Extremely Stable
- Draws only 20mA @ 12VDC
- Great Way to Increase Sensitivity of Receivers, Counters, etc

only \$8.95
 + .50 Shipping/Handling

- Fully Assembled and Tested
- Instructions Provided, Full Warranty

Portable 600 MHz Frequency Counter

- 1-600 MHz Range
- 1 KHz or 100 Hz Resolution
- Assembled and Tested
- Full Lifetime Warranty
- Size 5" L x 2" W x 1 1/2" H
- BNC Whip Antenna Opt. \$8.95

\$69.95 (less ant.)

C.O.D. Orders Welcome
Digitrex Electronics
 4412 Fernie, Royal Oak
 Michigan 48073 313 651 9247

• 75 mV Sensitivity

NOT A SUBSCRIBER?

DO IT TODAY!

Use the handy card between pages 92 & 93.

PENNSYLVANIA: Butler County Amateur Radio Association's hamfest on Sept. 7 in the Butler Farm Show Grounds at Roe Airport. Free parking, \$1.00 donation admission. Overnight camping welcome. Handicap parking available. Food and refreshments. Many prizes including Kenwood TS-520 SE Transceiver, specials and others. For more info: Dan Metrick, WA3GDS, 130 Rieger Rd., Butler, PA 16001. (412) 283-1719.

MAINE: The Sandy River Amateur Radio Club will hold a Hamfest/Flea Market on Saturday and Sunday, August 16th and 17th, 1980, at the Farmington Fair Grounds, Farmington, Maine. Admission will be \$1.00. No charge for tailgating. Commercial dealers welcome. Door prizes both days and a raffle on Sunday at 1:00 P.M. Free camping available from Friday starting at 5:00 P.M. until Sunday afternoon. Refreshments and snacks during the days and a lobster or chicken dinner late Saturday afternoon. Talk in on 146.37/97 and 146.52. For information and map, send S.A.S.E. to Charles Stenger W1HTG, Box 111, East Dixfield, Maine 04227.

VIRGINIA STATE ARRL CONVENTION: The Fifth Annual Tidewater Hamfest and ARRL Virginia State Convention will be in the great new Virginia Beach, Virginia Arts and Conference Center, October 4 and 5, 1980. ARRL, Traffic, DX Forums, XYL free bingo and lounge. Admission \$3.50. Advance admission ticket drawing for Kenwood FM transceiver. Flea market spaces \$3.00 day. Ticket and information - TRC, P.O. Box 7101, Portsmouth, Virginia 23707 SASE.

NEW JERSEY: The Ramapo Mountain Amateur Radio Club will hold its annual flea market on Saturday, August 16, 1980, at the American Legion Hall, Oak Street, Oakland, New Jersey. Indoor tables are \$5.00 and tailgating is \$3.00. No admission fee for buyers. Refreshments will be available on premises. Talk in on 147.49/146.49 WR2AHD or 146.52 simplex. Call Bud Hauser WA2JJO at 201-797-8471 or 791-0589 for advance reservations and information.

THE ANNUAL LAPORTE COUNTY HAMFEST will be held rain or shine, Sunday, Aug. 24, 1980, at the County Fairgrounds on Highway 2, west of LaPorte, Indiana (50 miles S.E. of Chicago). Paved flea market area outdoors. Indoor tables \$1.00 each. Overnight trailer hookups available on site for early birds. Advance tickets \$2.00 with SASE to P.O. Box 30, LaPorte, IN 46350.

OHIO: The 44th annual Cincinnati Hamfest will be September 21. Location: Stricker's Grove on State Rte. 128 in Ross, Ohio. Exhibits and booths, prizes, flea market, entertainment and a sensational and thrilling air show by The Hawks. Admission and registration: \$4.00 in advance. For information, contact W8ALW, W8BSTX, or K8CKI.

INDIANA: 10th annual Lafayette Hamfest will be Sunday, August 17 at the Tippecanoe County Fairgrounds in Lafayette, 18th St. at Teal Rd. Flea Market set-ups can be made anytime after 1800 hours Saturday. Pre-registration and grand prizes will be ICOM IC-2A Synthesized 2M Hand-held with Tone Pads and Chargers. Also B&W AC-DC portable TV and others. Refreshments available. Cost: \$2.50 each by mail in advance to qualify for pre-registration prize or at the gate. Mail orders: Send SASE with check or money order to K9KRE, J. B. Van Sickle, R. R. #1, Box 63, West Point, IN 47992. Talk-ins on 146.73 repeater and 146.94 simplex. Call in station is W9REG.

NEW YORK: Seaway Valley Hamfest at Louisville, N.Y. in the Louisville Municipal Arena on September 7. Turn south off Rt. 37 near Rt. 131 and Louisville School. Host Club: Massena Amateur Radio Club. Registration and Flea Market: 9:00 A.M. Activities: Flea Market, door prizes, raffles, auction, ladies program, children's activities and others. Registration and door prizes: \$2.50 Adv. sales: \$2.00. Children under 12 free. Ticket Manager: Lois Ierlan, WA2RXQ, 725 Proctor Ave., Ogdensburg, NY 13669.

WEST VIRGINIA: Cedar Lakes Hamfest on August 10 at the Cedar Lakes FFA-FHA Conference Center, Ripley, WV. Flea Market, Forums, Demonstrations, Prize Drawings, Ladies and Children Activities. Cafeteria on grounds. 9 A.M. to 4 P.M. Talk-in on 146.52/52 and 146.07/67. Advanced tickets \$2.00 — 3 for \$5.00. \$2.50 at the door. Bob Morris, WA8CTO, 308 Edgewood Circle, Ripley, WV 25271.

WASHINGTON: Radio Club of Tacoma's 14th annual "Hamfair" will be on August 23rd and 24th at Pacific Lutheran University, Tacoma, Wash. Door prizes, flea market, banquet, exhibits, and much more. Contact Joe Winter, 819 N. Mullen, Tacoma, WA 98406. Talk-in on 88/28.

NEW JERSEY: Gloucester Co. A.R.C.'s second annual hamfest on August 24 from 8 to 3 at the Gloucester County College, Tanyard Rd., Sewell. Tailgaters set up at 7:00. Indoor and outdoor spaces available. Food and prizes. Tickets \$2.00 in advance, \$2.50 at the door. Dealers and tailgaters \$5.00. Talk-in on .52 and .78/18. For info and tickets, contact Bob Grimmer, KN2QWO, 229 William Ave., Barrington, NJ 08007.

INDIANA: Crooked Lake's 22nd annual hamfest and F.M. picnic. Door prizes, large electronic flea market, overnight camping (small fee), bar-b-q, and big exhibition hall. Tickets: \$2.00 by donation. Talk-in on 147.81/21 and 146.52. August 3. Presented by the Steuben County Radio Amateurs.

DELAWARE: Fifth annual New Delmarva Hamfest on August 17th at Gloryland Park, Bear, Del. Admission: \$2.00 in advance, \$2.50 at the gate. Tailgating, \$2.50. Tables under pavilion, \$4.00. Prizes, food, etc. Talk-in on .52 and .13/73. For more info, send SASE to Stephen Momot, K3HBP, 14 Balsam Rd., Wilmington, DE 19804.

ALABAMA: North Alabama Hamfest on August 17 at the Von Braun Civic Center in Huntsville, Al. Free admission. Prizes, exhibits, forums, flea market, ladies activities, and tours of the Alabama Space and Rocket Center. Hamfest supper on Saturday night. Camping sites with hookups available on a first-come, first-serve basis. Flea market tables available for \$3.00. Talk in on 3.965 and .34/94. Write: NAHA, P.O. Box 423, Huntsville, AL 35804.

KENTUCKY: Bluegrass Amateur Radio Club's annual Central Kentucky Hamfest on August 10 at the Fasig-Tipton Sales Paddock, Newtown Pike, Lexington, Ky. Grand prizes, hourly door prizes, manufacturer's exhibits, indoor/outdoor flea market, forums and guest speakers. More info: SASE Edward B. Bono, WA4ONE, 2077 Dogwood Dr., Lexington, KY 40504.

FLORIDA: Jacksonville hamfest and ARRL Florida State Convention on August 2nd and 3rd at the Orange Park Kennel Club. Intersection of I-295 and U.S. Highway 17. Interesting programs and forums, with exhibits and displays. Special hotel rates available. Advanced registration: \$3.00, \$3.50 at door. Jacksonville Hamfest, 1249 Cape Charles Ave., Atlantic Beach, FL 32233. Swap tables: \$5.00. Order from Andy Burton, WA4TUB, 5101 Younis Rd., Jacksonville, FL 32218.

ILLINOIS: Rockford Amateur Radio Association's hamfest and A.R.R.L. Convention on August 31 at the Grand Exhibition Hall, Winnebago County Fairgrounds, Pecatonica, IL. Speakers, seminars, presentations, contests, commercial dealers, and more. More info: James L. Ambrosio, Hamfest Chairman, Rockford Amateur Radio Assoc., 3712 Huffman Blvd., Rockford, IL 61103.

CALIFORNIA: The Antelope Valley A.R.C.'s DXpedition to Alpine County on August 16 and 17. All bands, modes and county hunter nets used. Operated under K6OX. All QSO via K6GXO, sase necessary. Plans may change due to weather or availability of gas. More info: K6OX, Box 1221, Lancaster, CA 93534.

OHIO: DX-Pedition to the Center of the World will be operated by the Warren Amateur Radio Club, from 1300 GMT August 2, to 2000 GMT August 3. Freqs. are 28.265, 21.360, 14.285, 7.235, 3.900 MHz SSB. Also 21.125 for CW fans. QSL for a beautiful certificate with a large SASE to W8VTD, Box 809, Warren, OH 44482.

ILLINOIS: Hamfester's Radio Club's 46th annual hamfest on August 10 at Santa Fe Park, 91st and Wolf Rd., Willow Springs, Ill. More info: Les Taylor, WB9ZPP, Hamfest Chairman, 8960 W. 105th St., Palos Hills, IL 60465.

VERMONT: Burlington Amateur Radio Club's International Hamfest on August 9th and 10th at the Old Lantern Campgrounds 14 miles south of Burlington. Flea Market, Commercial exhibitors, traditional Can-am tug-of-war and door prizes. Admission: \$4.00. For more information, contact Hap Preston, W1VSA, Box 312, Burlington, VT 05402. Talk-in on .34/94, W1KOO/RPT.

CONNECTICUT: Super Scarafest "80" at the North Haven Ramada Inn at Exit #12 of I-91 in North Haven, CT. Held on August 16 & 17. Exhibits, giant flea market, and on Sunday, an all day auction. Prizes all day both days. Grand prizes will include a solid state low band transceiver, synthesized two meter handie-talkie, microcomputer, 600 MHz frequency counter, and over 60 others. Call Jeff Wayne, W1YLV at (203) 281-6038 between 9 A.M. and 9 P.M., E.S.T. for more details.

ILLINOIS: Illiana Repeater System, Inc. Amateur Radio Club's 11th annual hamfest will be August 30 and 31 at the Georgetown, Illinois fairgrounds. Advanced donations are \$1.50 for adults and \$2.00 at the gate. Children 14 and under are free. Flea markets, commercial exhibitors, RTTY setups, antique wireless Assn. display, homebrew builders contest, USAF MARS station and other interests. Meals and refreshments served. Overnight camping available. For more info or advanced tickets send SASE to Illiana Repeater System, Inc., P.O. Box G, Catlin, IL 61817.

OHIO: Union County Amateur Radio Club's Hamfest 80 on August 23 and 24 at the Fairgrounds in Marysville, Ohio. Talk-in on .52 or use club repeater 147.99/39. Door prizes, huge swap area, and plenty of good food. For more info: U.C.A.R.S., 13613 US 36, Marysville, OH 43040.

FALL TUNE UP TIME

Check-Tune your rig for maximum power use B & W
Dummyload-Wattmeter



Model 334A

Freq. Range: DC-300 MHz
VSWR: Less than 1.3:1
Power Range: Up to 1000 watts

Model 374

Freq. Range: DC-300 MHz
VSWR: Less than 1.3:1
Power Range: Up to 1500 watts



Model 333 Medium Power Model

Freq. Range: DC-300 MHz
VSWR: Less than 1.3:1
Power Range: Up to 250 watts



Barker & Williamson, Inc.
10 Canal Street,
Bristol, Pa. 19007

YAESU FT-207R OWNERS AUTOMATIC SCAN MODULE



15 minutes to install; scan restarts when carrier drops off; busy switch controls automatic scan on-off; includes module and instructions.

Model AS-1
\$25.00

ENGINEERING CONSULTING
P. O. BOX 94355
RICHMOND, B. C. V6Y2A8, CANADA

NEW ELECTRONIC PARTS

Brand name, first line components. Stocked in depth. 24 hour delivery. Low prices and money back guarantee on all products we carry.
STAMP BRINGS CATALOG

Daytapro Electronics, Inc.
3029 N. WILSHIRE LN. ARLINGTON HTS., ILL. 60004
PHONE 312-870-0555

I PAY CASH

for your military surplus electronics
If you have or know of availability:
TT-98 TT-76 Teletypewriter
phone me collect
Dave — (213) 760-1000

ASTRON POWER SUPPLIES

• HEAVY DUTY • HIGH QUALITY • RUGGED • RELIABLE •

SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output.
- CROWBAR OVER VOLTAGE PROTECTION on Models RS-7A, RS-12A, RS-20A, RS-35A, RS-20M & RS-35M
- MAINTAIN REGULATION & LOW RIPPLE at low line input Voltage.
- HEAVY DUTY HEAT SINK • CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD
- ONE YEAR WARRANTY • MADE IN U.S.A.
- VOLT & AMP METER ON MODELS RS-20M & RS-35M

PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105 - 125 VAC
- OUTPUT VOLTAGE: 13.8 VDC ± 0.05 volts
(Internally Adjustable: 11-15 VDC)
- RIPPLE: Less than 5mv peak to peak (full load & low line)
- REGULATION: ± 0.5 volts no load to full load & low line to high line

Other popular POWER SUPPLIES also available: (Same features and specifications as above)

Model	Continuous Duty (amps)	ICS* (amps)	Size (in.) H X W X D	Shipping Wt. (lbs.)	Price
RS-35M	25	35	5 X 11 X 11	29	\$167.95
RS-35A	25	35	5 X 11 X 11	29	\$149.95
RS-20A	16	20	5 X 9 X 10½	20	\$99.95
RS-12A	9	12	4½ X 8 X 9	13	\$74.95
RS-7A	5	7	3¾ X 6½ X 9	8	\$54.95
RS-4A	3	4	3¾ X 6½ X 9	5	\$39.95


*ICS — Intermittent Communication Service (50% Duty Cycle)
If not available at your local dealer, please contact us directly.



ASTRON 20 AMP REGULATED POWER SUPPLY Model RS-20M

16 Amps continuous
20 Amps ICS*
5" (H) x 9" (W) x 10.5" (D)
Shipping Weight 20 lbs.

Price \$117.95

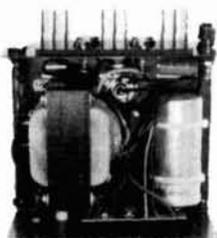

Inside View — RS-12A

ASTRON
CORPORATION

1971 South Ritchey Street
Santa Ana, CA 92705
(714) 835-0682



Ham Radio's guide to help you find your local

Arizona

POWER COMMUNICATIONS CORPORATION

6012 N. 27TH AVE.
PHOENIX, AZ 85017
602-242-6030 or 242-8990
Arizona's #1 "Ham" Store. Yaesu, Kenwood, Icom and more.

California

C & A ELECTRONIC ENTERPRISES

2210 S. WILMINGTON AVE.
SUITE 105
CARSON, CA 90745
213-834-5868
Not The Biggest, But The Best — Since 1962.

JUN'S ELECTRONICS

11656 W. PICO BLVD.
LOS ANGELES, CA 90064
213-477-1824 Trades
714-463-1886 San Diego
The Home of the One Year Warranty — Parts at Cost — Full Service.

QUEMENT ELECTRONICS

1000 SO. BASCOM AVENUE
SAN JOSE, CA 95128
408-998-5900
Serving the world's Radio Amateurs since 1933.

SHAVER RADIO, INC.

1378 S. BASCOM AVENUE
SAN JOSE, CA 95128
408-998-1103
Atlas, Kenwood, Yaesu, KDK, Icom, Tempo, Wilson, Ten-Tec, VHF Engineering.

Connecticut

HATRY ELECTRONICS

500 LEDYARD ST. (SOUTH)
HARTFORD, CT 06114
203-527-1881
Connecticut's Oldest Ham Radio Dealer.

THOMAS COMMUNICATIONS

95 KITTS LANE
NEWINGTON, CT 06111
203-667-0811
Authorized dealer for Kenwood, Yaesu, Drake, Icom, etc. - CALL US!

Delaware

DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD
NEW CASTLE, DE 19720
302-328-7728
ICOM, Ten-Tec, Swan, DenTron, Tempo, Yaesu, Azden, and more.
One mile off I-95, no sales tax.

Florida

AGL ELECTRONICS, INC.

1898 DREW STREET
CLEARWATER, FL 33515
813-461-HAMS
West Coast's only full service Amateur Radio Store.

AMATEUR RADIO CENTER, INC.

2805 N.E. 2ND AVENUE
MIAMI, FL 33137
305-573-8383
The place for great dependable names in Ham Radio.

RAY'S AMATEUR RADIO

1590 US HIGHWAY 19 SO.
CLEARWATER, FL 33516
813-535-1416
Atlas, B&W, Bird, Cushcraft, DenTron, Drake, Hustler, Hy-Gain, Icom, K.D.K., Kenwood, MFJ, Rohn, Swan, Ten-Tec, Wilson.

Illinois

AUREUS ELECTRONICS, INC.

1415 N. EAGLE STREET
NAPERVILLE, IL 60540
312-420-8629
"Amateur Excellence"

ERICKSON COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE.
CHICAGO, IL 60630
Chicago - 312-631-5181
Outside Illinois - 800-621-5802
Hours: 9:30-5:30 Mon, Tu, Wed & Fri.; 9:30-9:00 Thurs; 9:00-3:00 Sat.

Kansas

ASSOCIATED RADIO

8012 CONSER, P. O. BOX 4327
OVERLAND PARK, KS 66204
913-381-5900
America's No. 1 Real Amateur Radio Store. Trade - Sell - Buy.

Maryland

THE COMM CENTER, INC.

LAUREL PLAZA, RT. 198
LAUREL, MD 20810
800-638-4486
Kenwood, Drake, Icom, Ten-Tec, Tempo, DenTron, Swan & Apple Computers.

Massachusetts

TEL-COM, INC.

675 GREAT ROAD, RT. 119
LITTLETON, MA 01460
617-486-3040
The Ham Store of New England You Can Rely On.

TUFTS RADIO ELECTRONICS

206 MYSTIC AVENUE
MEDFORD, MA 02155
617-391-3200
New England's friendliest ham store.

Minnesota

PAL ELECTRONICS INC.

3452 FREMONT AVE. NO.
MINNEAPOLIS, MN 55412
612-521-4662
Midwest's Fastest Growing Ham Store, Where Service Counts.

New Hampshire

EVANS RADIO, INC.

BOX 893, RT. 3A BOW JUNCTION
CONCORD, NH 03301
603-224-9961
Icom, DenTron & Yaesu dealer. We service what we sell.

Dealers: *YOU SHOULD BE HERE TOO!*
Contact Ham Radio now for complete details.

Amateur Radio Dealer

New Jersey

RADIOS UNLIMITED
P. O. BOX 347
1760 EASTON AVENUE
SOMERSET, NJ 08873
201-469-4599
New Jersey's Fastest Growing
Amateur Radio Center.

ROUTE ELECTRONICS 46
225 ROUTE 46 WEST
TOTOWA, NJ 07512
201-256-8555
Drake, Swan, DenTron, Hy-Gain,
Cushcraft, Hustler, Larsen, Etc.

WITTIE ELECTRONICS
384 LAKEVIEW AVENUE
CLIFTON, NJ 07011
(201) 546-3000
Same location for 63 years.
Full-line authorized Drake dealer.
We stock most popular brands of
Antennas and Towers.

New Mexico

**PECOS VALLEY
AMATEUR RADIO SUPPLY**
115 W. WALNUT ST.
ROSWELL, NM 88201
505-623-7388
Your DX, Contest, and Antenna
Headquarters featuring A.E.A.,
Hy-Gain, Azden, Butternut, and
Most Major Brands.

New York

GRAND CENTRAL RADIO
124 EAST 44 STREET
NEW YORK, NY 10017
212-599-2630
Drake, Kenwood, Yaesu, Atlas,
Ten-Tec, Midland, DenTron,
Hy-Gain, Mosley in stock.

HAM-BONE RADIO
3206 ERIE BLVD. EAST
SYRACUSE, NY 13214
315-446-2266
We deal, we trade, all major brands!
2-way service shop on premises!

HARRISON RADIO CORP.
20 SMITH STREET
FARMINGDALE, NY 11735
516-293-7990
"Ham Headquarters USA"
since 1925.
Call toll free 800-645-9187.

RADIO WORLD
ONEIDA COUNTY AIRPORT
TERMINAL BLDG.
ORISKANY, NY 13424
Toll Free 800-448-7914
NY { 315-337-2622
Res. { 315-337-0203
New & Used Ham Equipment.
See Warren K2IXN or Bob WA2MSH.

Ohio

UNIVERSAL AMATEUR RADIO, INC.
1280 AIDA DRIVE
COLUMBUS (REYNOLDSBURG)
OH 43068
614-866-4267
Complete Amateur Radio Sales and
Service. All major brands - spacious
store near I-270.

Pennsylvania

**HAMTRONICS, DIV. OF
TREVOSE ELECTRONICS**
4033 BROWNSVILLE ROAD
TREVOSE, PA 19047
215-357-1400
Same Location for 30 Years.

LaRUE ELECTRONICS
1112 GRANDVIEW STREET
SCRANTON, PENNSYLVANIA 18509
717-343-2124
ICOM, Bird, Cushcraft, CDE,
Ham-Keys, VHF Engineering,
Antenna Specialists.

SPECIALTY COMMUNICATIONS
2523 PEACH STREET
ERIE, PA 16502
814-455-7674
Service, Parts, & Experience
For Your Atlas Radio.

TELL YOUR FRIENDS
about

**ham
radio**

1 year
subscription **\$15.00**
US ONLY

HAM RADIO MAGAZINE
GREENVILLE, NH 03048

DEALERS WANTED

TOWERS

by ALUMA

HIGHEST QUALITY

ALUMINUM
& STEEL

60 Ft. Aluminum.
Crank-Up
Model T-60-H

40' Steel
Crank-Up
Model SHD-40

- ★ TELESCOPING (CRANK UP)
 - ★ GUYED (STACK-UP)
 - ★ TILT-OVER MODELS
- Easy to install. Low Prices.
Crank-ups to 100 ft.

EXCELLENT FOR
HAM COMMUNICATIONS

SPECIAL
Four Section 50 Ft.
Van Mounted Crank-Up
Aluma Tower

Over 36 types aluminum
and steel towers made—
specials designed and
made—write for details



ALUMA TOWER CO.

Box 2806HR
VERO BEACH, FLA 32960
PHONE (305) 567-3423
TELEX 80-3405

The Best Got Better



MODEL 4381 RF POWER ANALYST

This new generation
RF Wattmeter with nine-mode
system versatility reads...

IN STOCK QUICK DELIVERY

AUTHORIZED **Webster** DISTRIBUTOR

Webster
associates

115 BELLARMINE
ROCHESTER, MI 48063

CALL TOLL FREE
800-521-2333
IN MICHIGAN 313 - 375-0420

Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio 234

Ace Comm. ___ 850	Henry ___ 062
AEA ___ 677	Hustler ___ 171
Alaska Microwave ___ 826	Icom *
Aluma ___ 589	Int. Crystal ___ 066
Amidon ___ 005	Jameco ___ 333
Antenna Inc. ___ 686	Jones ___ 626
Astron ___ 734	Kantronics *
Atlantic Surplus *	Keithley ___ 837
Avanti ___ 775	Kenwood *
Barker ___ 015	Larsen ___ 078
Barry *	MFJ ___ 082
Bauman ___ 017	MHz Elec. ___ 415
Bilal ___ 817	Madison ___ 431
Budwig ___ 233	Microcraft ___ 774
Cal Crystal ___ 709	P.C. Elec. ___ 766
Comm. Concepts ___ 797	Palomar Eng. *
Comm. Spec. ___ 330	Callbook ___ 100
Comtronics Inc. ___ 852	Radio Expo *
DCO ___ 324	Radio World *
Dave *	Ramsey ___ 442
Daytapro ___ 455	Securitron ___ 461
Dexcel ___ 851	Shure ___ 771
Digitrex ___ 823	Skytec ___ 704
E. T. O. *	Spec. Int. ___ 108
Elec. Research Virginia *	Tech. Clinic ___ 845
Eng. Consulting *	Telrex *
Fox-Tango ___ 657	Ten-Tec *
Fluke ___ 049	Unimax Switch ___ 841
G & C Comm. ___ 754	Vanguard ___ 716
GLB ___ 552	Varian ___ 043
Hal ___ 057	Webster Assoc. ___ 423
Hal-Tronix ___ 254	Western Elec. *
H. R. Bookstore ___ 150	Yaesu ___ 127
Horizons *	Zitnan *
H. R. Magazine *	
Heath ___ 060	

*Please contact this advertiser directly.

Limit 15 inquiries per request.

August, 1980

Please use before September 30, 1980

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME

CALL

STREET

CITY

STATE..... ZIP.....

AU-GUSTO

ALPHA 76, 374, 78 in Stock Call
Cushcraft "boomer" 69.95
OMNI-J2 Meter Antenna 39.95
Bird 43 and slugs, UPS paid in USA stock
Microwave Modules, Less 10% off list
stock
Telrex TB5EM, in stock 425.00
Telrex TB6EM 540.00
Complete Line Monobanders. stock
New Telrex TB5ES, 2KW
Pep version. 315.00
Robot 800 Keyboard 699.00
Bencher Paddles, Standard 39.95
Bencher Paddles, Chrome 49.95
Vibroplex Paddles and bugs. stock
Lunar 6M-2M-220 In-line Preamps stock
Janel QSA-5 41.95
HAM-X Taitwister Rotor 239.00
HAM-4 Rotor 169.00
Cetron or GE 572B 32.00/ea
GE, AMPEREX, Raytheon 6146B 9.95
Motorola HEP170 0.29
Mallory 2.5A/1000 PIV Epoxy diode 0.19
Sprague 100MFD/450VDC Cap. 2.00
Aerovox 1000PF/500V Feedthru Cap 1.95
Adel Nibbling Tool. 8.45
Technical books: Ameco, ARRL, Sams,
TAB, Rider, Radio Pub., Callbook,
Cowan, WRTVH, etc. Call
New Belden 9405 (2#16) (6#18) 8 wire
Rotor cable, heavy duty for
long runs. 0.38/ft
8448 8 wire Rotor Cable 0.24/ft
9888 Double Shield RG8 Foam 0.56/ft
8214 RG8 Foam 0.32/ft
8237 RG8 Regular. 0.28/ft
8267 RG213 0.36/ft
9251 RG8 A/U 0.42/ft
Belden #8000 14GA
Stranded Antenna wire 0.10/ft.
Amphenol Silverplate PL259 (831SP)
1.00
Berktex RG8X 52 OHM, KW 0.19/ft.

Need a schematic?
We've got 'em — \$2.00

ICOM IC 2A HANDHELD
W/TTP, battery pack, Rubber Duck
and charger \$229.00

Looking for antique parts?
Write specific need to W5GJ.

THIS MONTH'S SPECIALS:

New IC720, AC — Call
New ICOM, IC251A — 2M \$599.00
IC551D — 6M-100W \$599.00
IC551 \$399.00

Kenwood TS-180S/DFC — SSB
Call for quote
Bearcat 250, 220 299.00
Bearcat 300 399.00

MASTER CHARGE • VISA

All prices fob Houston except where indicated. Prices subject to change without notice, all items guaranteed. Some items subject prior sale. Texas residents add 6% tax. Please add postage estimate. \$1.00 minimum.

MADISON
Electronics Supply, Inc.
1508 McKinney • Houston, Texas 77002
713/658-0268

Advertisers iNdex

Ace Communications Inc.	55
Advanced Electronics Applications	32
Alaska Microwave Labs	88
Aluma Tower Company	93
Amidon Associates	84
Astron Corporation	91
Atlantic Surplus Sales	60
Avanti Research & Development	71
Barker & Williamson, Inc.	91
Barry Electronics	19
Bauman, R. H. Sales Company	82
Bilal Company	84
Budwig Mfg. Company	60
Cal Crystal Lab, Inc.	65
Communication Concepts, Inc.	88
Communications Specialists	10, 11
DCO, Inc.	65
Dave	91
Daytapro Electronics	91
Dexcel	23
Digitrex Electronics	90
Ehrhorn Technological Operations	60
Electronic Research Corp. of Virginia	96
Engineering Consulting Services	91
Fox-Tango Corp.	71
G & C Communications	52
GLB Electronics	60
Hal Communications Corp.	33
Hal-Tronix	22
Ham Radio's Bookstore 52, 58, 71, 72, 73, 82, 84, 86, 88, 90, 95, 96	
Ham Radio Horizons	32
Ham Radio Magazine	88
Heath Company	89
Henry Radio Stores	Cover II
Hustler, Inc.	60
Icom America, Inc.	5
International Crystal Mfg. Co.	95
Jameco Electronics	59
Jones, Marlin P. & Associates	87
Kantronics	82
Trio-Kenwood Communications, Inc.	48, 49
Larsen Antennas	43
MFJ Enterprises	2
MHz Electronics	76, 77, 78, 79
Madison Electronics Supply	29, 94
Microcraft Corporation	85, 96
P.C. Electronics	55
Palomar Engineers	83
Radio Amateur Callbook	81
Radio Expo	44
Radio World	85
Ramsey Electronics	63
Securitron	90
Shure Brothers Inc.	1
Skytec	60
Spectronics	53
Spectrum International	37
Technical Clinic	84
Telrex Laboratories	85
Ten-Tec	9
Vanguard Labs	88
Varian, Eimac Division	Cover IV
Webster Associates	93
Western Electronics	96
Yaesu Electronics Corp.	Cover III

1980 HANDBOOK

STEP INTO THE 80'S WITH
THE LATEST HANDBOOK
FROM THE EDITORS
AT ARRL

NEW LOW
PRICE!!
WAS \$10,
NOW JUST
\$7⁹⁵



Full of exciting new features for the 80's, NOW is the time to order your copy of the **1980 ARRL "RADIO AMATEUR'S HANDBOOK."** Internationally recognized and universally consulted, every Amateur should have the latest edition. The new **HANDBOOK** covers virtually all of the state-of-the-art developments in electronics theory and design. Novices will find it to be an indispensable study guide, while the more advanced Amateur will enjoy building the many new projects.

- Order AR-HB80
Softbound **\$7.95**
- Order AR-BB80
Hardbound **\$15.75**

**HAM RADIO'S
BOOKSTORE**

GREENVILLE, N. H. 03048

(800) 258-5353

1980
1980
CALLBOOKS
See page 96 for super value
on 1980 Callbooks.
1980

More Details? CHECK — OFF Page 94

INTERNATIONAL RF-1200

1296 LOW NOISE PREAMPLIFIER



FOR AMATEUR OR COMMERCIAL APPLICATIONS

1100-1300 MHz • Satellite • Microwave

The RF-1200 is a single stage bipolar low-noise amplifier followed by a 2-stage output filter. Ion-implanted microwave transistors and microstripline construction. Die-cast case.



SPECIFICATIONS

Gain 15 db
Noise Figure 2 db
Bandwidth 1 db 50 MHz
Tuning Range 1100-1300 MHz
Power Supply 13.5 vdc 20 MA
Connectors SMA
Third Order Intercept +24 dbm

PRICE **\$160**



INTERNATIONAL CRYSTAL MANUFACTURING CO., INC.
10 N. Lee, Oklahoma City, Oklahoma 73102, 405-236-3741

ERC Promises Up To The Minute State-Of-The-Art Design and Performance

Four Simultaneous Filters in One for Unparalleled QRM Free Reception (SSB & CW)
★ Plus a Special Patented CW Processor ★

The brand new SL-56 Audio Active Filter supercedes our SL-55 in both concept and performance. Consolidation of many components has allowed us to make 13 operational amplifiers (compared to 6 in the SL-55) into a filter guaranteed to out perform any other at a cost only slightly higher than the SL-55. The features of the SL-56 are so advanced from its predecessor that calling it the SL-55A is not justified. Unlike other filters that simply offer a choice of one or two filter types at a time (notch, bandpass, etc.) SL56 provides what is really needed - the simultaneous action of a 6 pole 200 Hz fixed highpass filter and a 6 pole 1600 Hz fixed lowpass filter with a 60 dB notch which is tunable over the 200-1600 Hz range. This 3 filter combination is unbeatable for the ultimate in QRM free SSB reception. Adjacent channel QRM is eliminated on the high and low sides at the same time and does not introduce any hollowness to the desired signal. On CW the SL-56 is a dream. The lowpass, highpass and notch filters are engaged along with the tunable bandpass filter (400-1600 Hz) providing the needed action of 4 simultaneous filter types. The bandpass may be made as narrow as 14 Hz (3dB). Additionally, a special patented circuit follows the filter sections which allows only the peaked signal to "gate itself" through to the speaker or headphones (8-2000 OHMS). Receiver noise, ring and other signals are rejected. This is not a regenerator, but a modern new concept in CW reception. The SL-56 connects in series with the receiver speaker output and drives any speaker or headphones with one watt of audio power. Requires 115 VAC. Easily converted to 12 VDC operation. Coal black cabinet and wrinkle gray panel.



SL-56
Audio Active Filter
(3.5 x 5.5 x 7.5 Inches)

Warranted One Full Year Fully RFI Proof Fully Wired and Tested Available Now
\$79.00 Postpaid in the USA and Canada
Virginia Residents Add 4% Sales Tax.
Attention SL-55 Owners: The Circuit Board of the SL-56 is Completely Compatible with the SL-55 Chassis. Our Retrofit Kit is Available at \$40.00 Postpaid.

Electronic Research Corp. of Virginia

P. O. Box 2394 • Virginia Beach, Virginia 23452 • Telephone: (804) 463-2669

AFFORDABLE CW KEYBOARD



Transmits perfect Morse Code • Built-in 16 character buffer • Internal speaker and sidetone • Reed relay output eliminates keying problems • All solid state circuits and sockets for reliability • Speed range 5-35 WPM.


MORSE-A-KEYER KIT, model MAK-K, Complete kit of parts & manual \$159.95
MORSE-A-KEYER, model MAK-F, Factory wired & tested \$205.95
MORSE-A-KEYER ESSENTIAL PARTS KIT, model EPK-K. \$ 69.95
(Essential parts kit for home-brewers consists of pc board, board parts and manual. You supply ASCII keyboard, cabinet, power supply & miscellaneous parts.)

Send check or money order. Use your VISA or MasterCard. Add \$5.00 shipping and handling for Continental U.S. Wisconsin residents add 4% Wisconsin State Sales Tax.

Microcraft

Corporation Telephone: (414) 241-8144
Post Office Box 513HR, Thiensville, Wisconsin 53092

ALL BAND TRAP ANTENNAS!

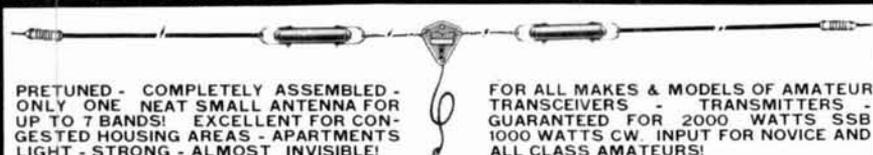

PRE-TUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW INPUT FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6"- you just switch to band desired for excellent worldwide operation - transmitting and receiving! Low SWR over all bands including 80/75-Tuners usually NOT NEEDED! Can be used as inverted V's - slopers - in attics, on building tops or narrow lots - on 160 meters too! (Instructions incl.) The ONLY ANTENNA YOU WILL EVER NEED FOR ALL BANDS - WITH ANY TRANSCEIVER - NEW - EXCLUSIVE!

80-40-20-15-10-6 Meter --- 104 ft. long - with 90 ft. of RG58U - connector - Model 998BU. . . \$69.95
SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical-customs etc.) or order using VISA - MASTER CHARGE - CARD - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES WILL INCREASE . . . SAVE - ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM
WESTERN ELECTRONICS Dept. AR-B Kearney, Nebraska, 68847

1980

US Radio Amateur Callbook

To keep track of all the changes in callsigns, you ought to have a copy of the 1980 Callbook on your operating table. It's been a best seller for years because of features like these:

- **Bold face calls, names, and addresses of every licensed ham in the US** • ARRL countries list • QSL managers list • International Postal info • Standard time charts • and more.

Keep up to date. You can't afford to be without the very latest Callbook.

CB-US Softbound \$16.95

The Foreign Callbook

DXing is a real joy, but it's even better when you get back QSL cards from the countries you've worked. The most important tool in getting those cards is to have a copy of the 1980 Foreign Callbook on your operating table. Stations are listed by country, call, name and address in bold, easy-to-read type. CB-F Softbound \$15.95
Please include \$1.75 additional shipping for each Callbook ordered.


HAM RADIO'S BOOKSTORE

GREENVILLE, N. H. 03048

(800) 258-5353

1980
1980
HANDBOOK
See page 95 for super value
on 1980 ARRL Handbook.
1980

DOUBLE YOUR PLEASURE

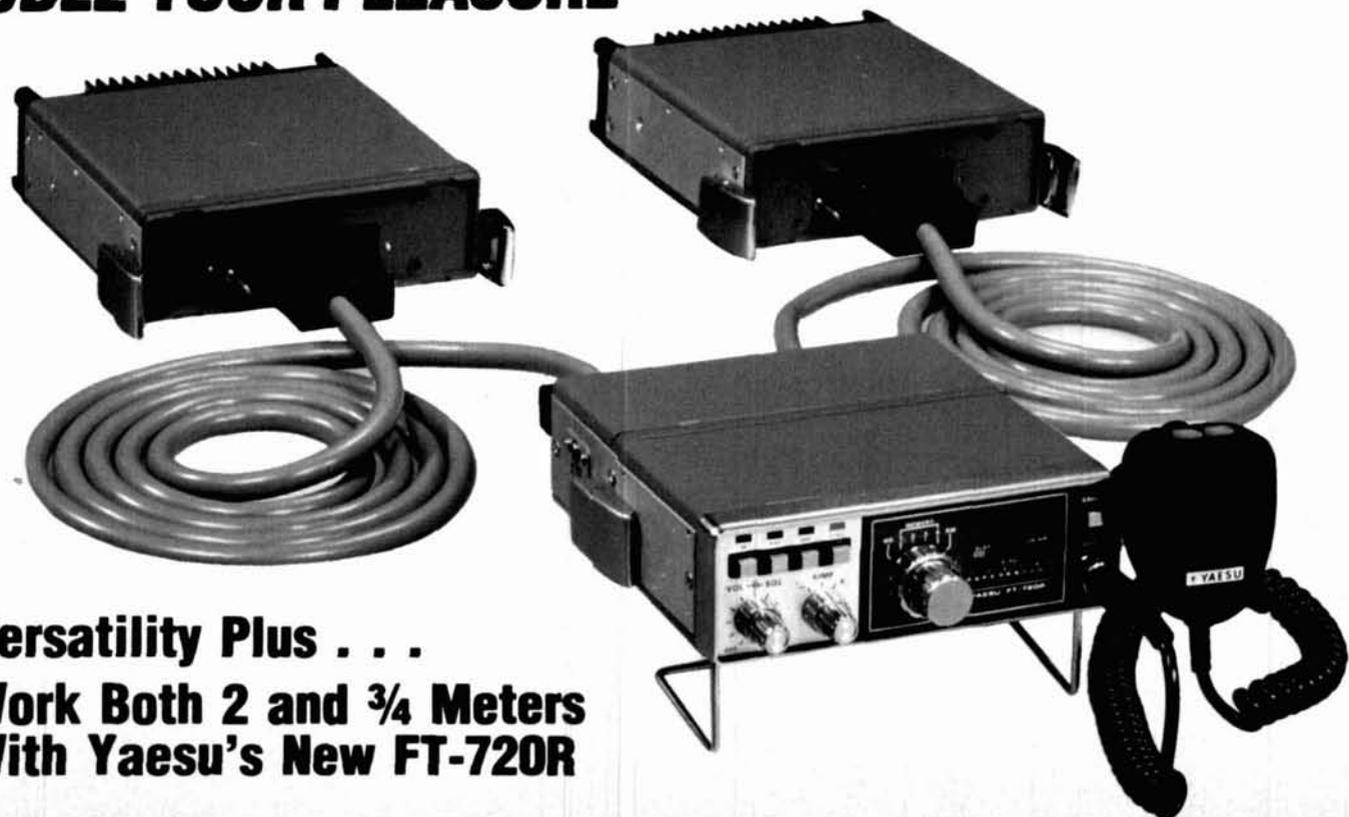

Versatility Plus . . . Work Both 2 and $\frac{3}{4}$ Meters With Yaesu's New FT-720R

The FT-720R series is a compact VHF/UHF mobile transceiver that harnesses the incredible power of the microprocessor to bring you top-operating flexibility. Start with the FT-720R Control Head, then add either the 10 watt FT-720RU 440 MHz or 25 watt FT-720RVH 2 meter RF Deck. You can clamp the Control and RF Deck together or use an optional remote cable to hide the RF Deck. The best news is still to come! By using the optional S-72 Switching Box and two remote cables, you can use a single Control Head for operation with both the 440 MHz and 2 meter decks, giving you a high-performance two band FM station for your car or home. Compare the features below, then ask your dealer for a demonstration of the fabulous FT-720R series. . . another winner from the performance leader . . . Yaesu.

- Four simplex/repeater memory channels, plus receive-only memory channel.
- Scanning controls on microphone with search for busy or clear channel.
- Optional 32 tone CTCSS module for accessing private repeaters.
- Colorful, easy-to-read LED power output/S meter.
- Built-in 1800 Hz tone generator.
- Priority channel with search-back feature.
- Pause feature that holds, then restarts scan, on busy or clear channels.
- Digital display of last four digits of operating frequency.
- Single Control Head may be used for operation on both 440 MHz and 2 meters via optional switching box and remote cables.
- Extremely compact size, light weight.

FT-720RVH	Specifications	FT-720RU
144.00-147.99 MHz	Frequency Coverage	440.00-449.975 MHz
10 kHz	Synthesizer Steps	25 kHz
25 watts	Power Output	10 watts
.32 uV for 20 dB quieting	Sensitivity	0.5 uV for 20 dB quieting
±6 kHz (-6dB)	Selectivity	±12 kHz (-6dB)
±12 kHz (-60 dB)		±24 kHz (-60 dB)

YAESU
The radio.



480

Price And Specifications Subject To
Change Without Notice Or Obligation

YAESU ELECTRONICS CORP., 6851 Waltham Way, Paramount, CA 90723 ● (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

Eighteen Continental superpower transmitters use EIMAC megawatt tetrodes for long life and reliability.

On the air now.

Continental Electronic's new superpower broadcast transmitters are on the air at four overseas sites providing extended coverage and 24 hour operation.

These rugged transmitters provide a fully modulated carrier output of one or two megawatts. Each transmitter bay employs one EIMAC X-2159/8974 tetrode as a carrier tube and a second X-2159/8974 as a peak tube. An EIMAC 4CW25,000A serves as a driver and three 4CW25,000As are used in a cathode follower class-A modulator stage.

Fourteen transmitters are now in service and four more will follow shortly. This speaks well for Continental's transmitters design and for their choice of long life EIMAC power tubes.



Contact EIMAC today for tomorrow's transmitter.

Follow Continental Electronics selection of EIMAC power tubes for your next transmitter design. From VLF to VHF, make EIMAC your choice. For full information write Varian, EIMAC Division, 301 Industrial Way, San Carlos, CA 94070. Telephone (415) 592-1221. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.



X-2159/8974



4CW25,000A