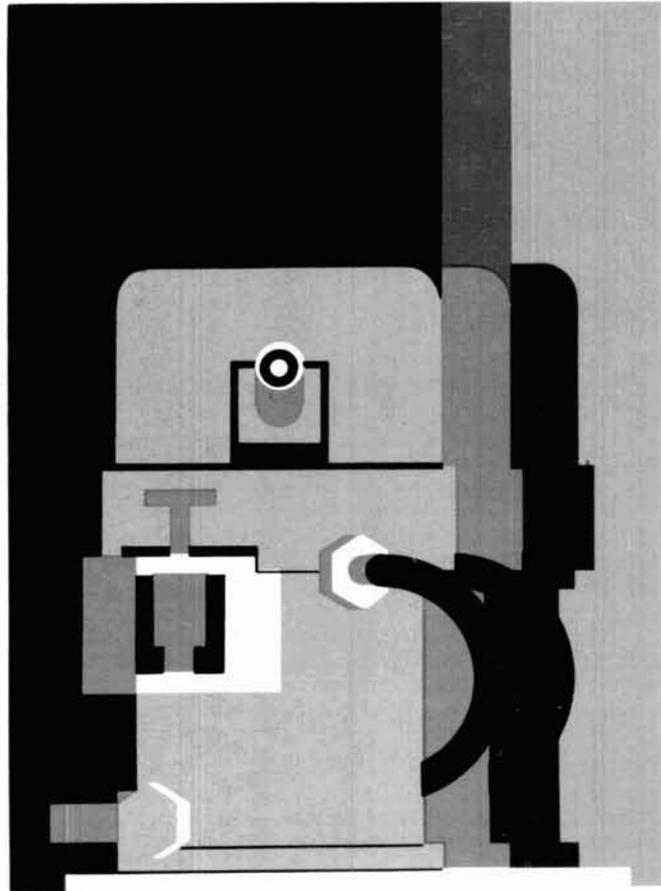


# ham radio

magazine

incorporating  
**HAM RADIO**  
**HORIZONS**

- Collins owners' report ..... 22
- digital frequency display ..... 28
- tracking satellites..... 46
- adding fm to your receiver ... 74



**converting  
surplus  
AN/UPX-6  
cavities**

**hr**

for

communications  
technology



# 2K Classic

A new edition of the world's most famous linear amplifier

The 2K Classic represents the culmination of fifteen years experience in developing, manufacturing and improving the 2K series. It remains as always a "workhorse", engineered and built to loaf along at full legal power for days or weeks without rest. A look inside shows why! No expense has been spared to make the 2K a truly "Classic" Amateur amplifier. Heavy duty, top quality components along with its rugged construction assures you of trouble free operation. The 2K Classic offers engineering and features second to none. It will put your signal on the air with greater strength and clarity than you ever dreamed possible. The 2K Classic operates on all amateur bands, 80 through 15 meters (export models include 10 meters).

- Features:**
- Two rugged Eimac 3-500 grounded grid triodes
  - Pi-L plate circuit with silver plated tank coil
  - Resonant cathode pi input circuit
  - Maximum legal input on all modes
  - Price: \$1195.00

*The 1KD-5* ...Another fine member of the famous Henry Radio family of superior amplifiers. And we're still convinced that it's the world's finest linear in its class. The 1KD-5 was designed for the amateur who wants the quality and dependability of the 2KD-5 and 2K-4, who may prefer the smaller size, lighter weight and lower price and who will settle for a little less power. But make no mistake, the 1KD-5 is no slouch. Its 1200 watt PEP input (700 watt PEP nominal output) along with its superb operating characteristics will still punch out clean powerful signals...signals you'll be proud of. Compare its specifications, its features and its fine components and we're sure you will agree that the 1KD-5 is a superb value at only \$695.

*The 2KD-5* We have been suggesting that you look inside any amplifier before you buy it. We hope that you will. If you "lift the lid" on a 2KD-5 you will see only the highest quality, heavy duty components and careful workmanship...attributes that promise a long life of continuous operation in any mode at full legal power. The 2KD-5 is a 2000 watt PEP input (1200 watt PEP nominal output) RF linear amplifier, covering the 80, 40, 20, and 15 meter amateur bands. It operates with two Eimac 3-500Z glass envelope triodes and a PI-L plate circuit with a rotary silver plated tank coil. Price \$945.

And don't forget the rest of the Henry family of amateur amplifiers...the Tempo 2002 high power VHF amplifier and the broad line of top quality solid state amplifiers. Henry Radio also offers the 3K-A and 4K-Ultra superb high power H.F. amplifiers and a broad line of commercial FCC type accepted amplifiers for two way FM communications covering the range to 500 MHz.

\*\*\*\*\*  
*Announcing!*  
 A brand new "super" linear...the 3K Classic! Designed for the most critical Amateur Radio operator...the individual who wants and appreciates owning the finest. Available in spring 1981.  
 F.C.C. approval pending  
 \*\*\*\*\*



Please note, as of Dec. 1, 1980 we will occupy our new world headquarters building with a new Los Angeles address and phone number

2050 S. Bundy Dr., Los Angeles, CA 90025  
 931 N. Euclid, Anaheim, CA 92801  
 Butler, Missouri 64730

(213) 820-1234  
 (714) 772-9200  
 (816) 679-3127

TOLL FREE ORDER NUMBER: (800) 421-6631  
 For all states except California  
 Calif. residents please call collect on our regular numbers

**Henry Radio**  
 Prices subject to change without notice

**Switch it...  
tune it...  
load it...  
measure it...  
send it...with  
Heathkit®  
amateur  
gear**



Low SWR and maximum radiation are yours with the SA-2040 2 kW Antenna Tuner.



Measure power and SWR with the HM-2141 Dual Meter VHF Wattmeter you build yourself.

No matter what you are doing to your signal, Heath has the amateur gear to help you do it better....and to save you money, too. Heath is your one-stop headquarters for accessories, antennas and complete, build-it-yourself rigs. And they're all backed by the more than 200 hams at Heath.

The new Heathkit Catalog describes one of the most complete selections of ham gear anywhere. You'll also find the latest in home computers, fine stereo components, color TV's, precision test instruments and innovative electronics for your home...all in easy-to-build, money-saving kits.

It's one catalog you don't want to be without. Write for your free copy today or pick one up at your nearest Heathkit Electronic Center.

The easy-to-build Cantenna™ Dummy Load reduces QRM during tune-up.



Send smooth, easy-to-read CW with the Heathkit HD-1410 Electronic Code Keyer.



**SEND FOR FREE CATALOG**

Write to Heath Company, Dept. 122-754, Benton Harbor, MI 49022. In Canada, write Heath Co., 1480 Dundas Highway East, Mississauga, Ontario L4X 2R7.

**VISIT YOUR HEATHKIT STORE**


In the U.S. and Canada, visit your nearby Heathkit Electronic Center where Heathkit Products are displayed, sold and serviced. See the white pages of your phone book. In the U.S., Heathkit Electronic Centers are units of Veritechnology Electronics Corporation.



Switching antennas is easy with the low-priced SA-1480 Remote Coax Switch.

**Heathkit®**

# It couldn't be anything but...

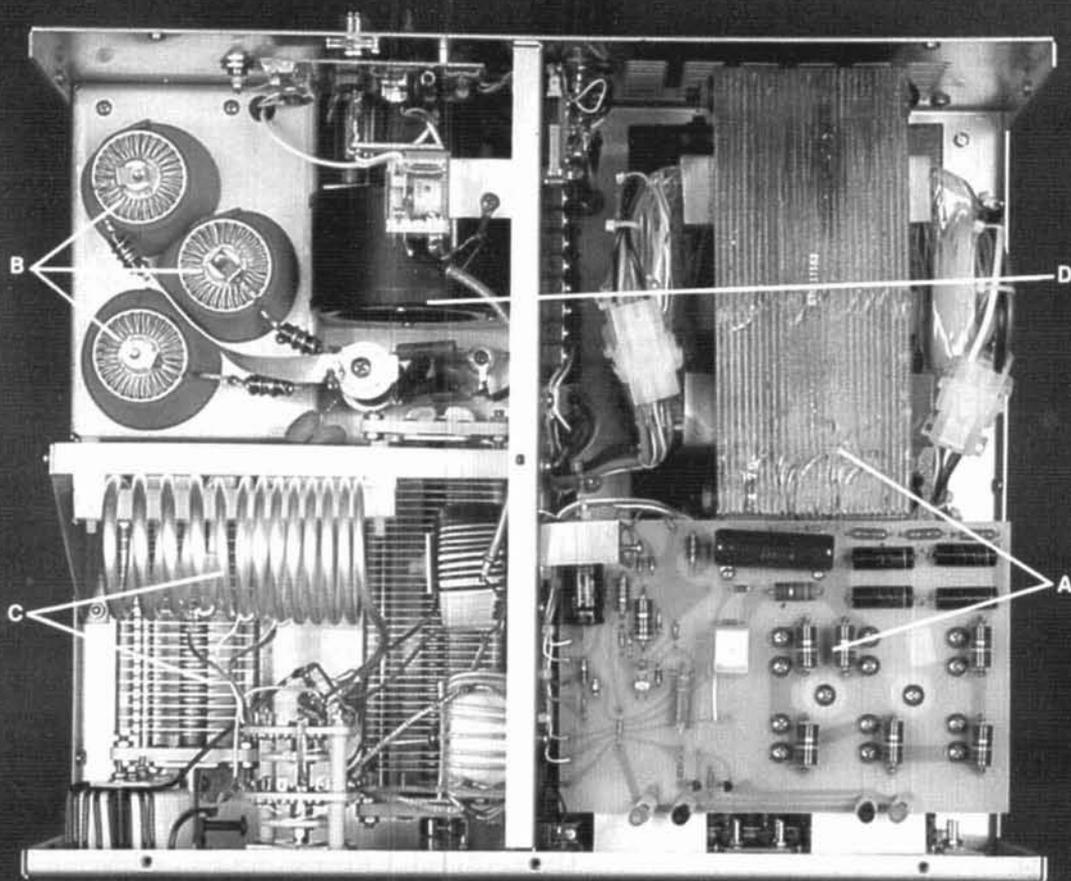

WHAT OTHER  
MAXIMUM LEGAL POWER  
AMPLIFIER GIVES YOU...

(A) A FULL KW CCS POWER SUPPLY WITH A 45 POUND, 1.5 KVA TRANSFORMER that plugs in for easy handling...

(B) TOUGH EIMAC CERAMIC TRIODES, THOROUGHLY COOLED by ETO's exclusive full-cabinet ducted air system...

(C) HEAVY SILVER PLATED TUBING COIL IN A FULL PI-L NETWORK that extends to 160 meters and provides 10-15 dB better harmonic suppression than the pi networks commonly used...

(D) CENTRIFUGAL BLOWER FLOATING ON A FOAM RUBBER "SANDWICH" that absorbs noise and vibration, permitting whisper quiet operation...

AND WHO ELSE BUT ETO rates linears for "a full kilowatt key-down forever?"



(ALPHA 76 PA SHOWN)

# Alpha!

NOBODY BUT ETO, so far as we know, provides amplifier warranty coverage beyond a scant 90 days. We'd be embarrassed to offer you a 90 day warranty! That's scarcely long enough to become really familiar with your new linear.

EVERY NEW ALPHA CARRIES A TWO YEAR (limited) FACTORY WARRANTY-just one factor that makes ALPHA such a sensible investment. Most ALPHA's command resale prices close to what they sold for new five or even ten years earlier!

To prevent a sad case of linear buyer's remorse later on, your best move now is to investigate ALPHA carefully before you buy any amplifier. Call or write your dealer or ETO today. Just ask for our full color brochure; it contains inside and outside photographs and detailed specifications for all the famous ALPHA amplifiers.

Ehrhorn Technological Operations, Inc.  
Box 708, Canon City, CO 81212  
(303) 275-1613

# ETO

# ham radio

magazine

incorporating

## HAM RADIO HORIZONS

**MARCH 1981**

volume 14, number 3

**T. H. Tenney, Jr., W1NLB**  
publisher and  
editor in chief

**Alfred Wilson, W6NIF**  
editor

**editorial staff**

Martin Hanft, WB1CHQ  
production editor

Joseph J. Schroeder, W9JUV  
Leonard H. Anderson  
associate editors

W.E. Scarborough, Jr., KA1DXQ  
graphic production manager

Irene Hollingsworth  
editorial assistant

Wayne Pierce, K3SUK  
cover

**publishing staff**

J. Craig Clark, Jr., N1ACH  
assistant publisher and  
advertising manager

Susan Shorrock  
circulation manager

ham radio magazine  
is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**subscription rates**

United States: one year, \$15.00  
two years, \$26.00; three years, \$35.00

Canada and other countries (via Surface Mail)  
one year, \$18.00; two years, \$32.00  
three years, \$44.00

Europe, Japan, Africa (via Air  
Forwarding Service) one year, \$28.00

All subscription orders payable in  
United States funds, please

**foreign subscription agents**

Foreign subscription agents are  
listed on page 89

Microfilm copies  
are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3076

Cassette tapes of selected articles  
from ham radio are available to the  
blind and physically handicapped  
from Recorded Periodicals  
919 Walnut Street, 8th Floor  
Philadelphia, Pennsylvania 19107

Copyright 1981 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office

Second-class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices  
ISSN 0148-5989

Postmaster send Form 3579 to ham radio  
Greenville, New Hampshire 03048



## contents

**12 converting surplus AN/UPX-6 cavities**  
Robert S. Stein, W6NBI

**18 DXer's Diary**  
Bob Locher, W9KNI

**22 Collins Owners' Reports:**  
**KWM-2 and KWM-2A**  
Martin Hanft, WB1CHQ

**28 digital frequency display for**  
**single-conversion transceivers**  
Everett L. Beall, K6YHK

**34 ham radio techniques**  
Bill Orr, W6SAI

**38 genesis of a synthesizer**  
Ken Grant, VE3FIT

**44 CW anyone?**  
Harry W. Lewis, W7JWJ

**46 tracking satellites in elliptical orbits**  
Paul C. Bunnell, WA6VJR

**52 protection for your solid-state devices**  
Henry H. Cross, W100P

**64 transmission-line circuit design:**  
**part 4**  
H.M. Meyer, Jr., W6GGV

**74 add fm to your receiver**  
John LaMartina, K3NXU

**110 advertisers index**

**78 DX forecaster**

**89 flea market**

**102 ham mart**

**84 ham notes**

**7 letters**

**106 new products**

**4 observation and**  
**opinion**


**8 presstop**

**60 questions and**  
**answers**

**110 reader service**

**109 short circuits**

**74 weekender**

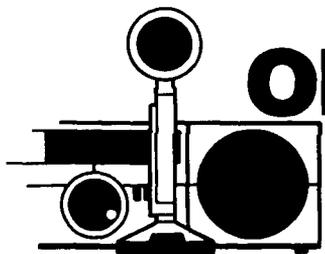

# Observation & Opinion

The January, 1981, issue of *ham radio*, which incorporated Ham Radio *Horizons*, resulted in a flood of mail. Responses were mixed, as expected. Readers who had never seen an issue of *ham radio* were surprised and pleased with the new magazine. Old-guard *ham radio* readers appreciated the new mix of articles. We also received complaints from *Horizons* readers, who expected all of their favorite features in the combined magazine.

A major change in a magazine format, such as was begun in the January, 1981, issue cannot be accomplished overnight. When the decision was made to discontinue Ham Radio *Horizons*, the January, 1981, issue of *ham radio* was almost "locked up" and ready to be sent to the printer. This state of affairs resulted in an intense scramble to include at least *some* of the Ham Radio *Horizons* articles. Production schedules are demanding and unforgiving in the magazine-publishing business, so it was impossible to include all the *Horizons* features in the January issue. Under the circumstances, we did the best we could.

We don't intend to abandon our faithful *Horizons* readers, nor do we intend to compromise the technical integrity of the magazine. If *Horizons* readers will bear with us for a few months, they will find more and more articles and features that made the *Horizons* magazine so popular. *Ham radio* has enjoyed a reputation for technical excellence for many years. We plan to continue this tradition.

Suggestions for article subjects were many and varied. These and the constructive criticism we received are gratefully appreciated. All were carefully considered, and future issues, now in the planning stage, will include as many different subjects as space will allow.

We received requests ranging from "more antenna theory" to "more on operating practices, station accessories, DX, and elementary theory." The demand for the continuation of "Ham Radio Techniques," "DXer's Diary," "Equipment Owners' Survey," and "Q and A" came through loud and clear. We got the message. You will see these features as well as some great stories that we've been keeping on the back burner. For the advanced Amateur, we have some interesting construction articles — in short, something for everyone. You asked for it; you'll get it.

## caution

I'd like to direct your attention to a letter in this month's "Comments" column taking us to task for a potential safety hazard in the modular amplifier article that appeared in the January issue on page 12. It's a point very well taken, and I'd recommend that anyone planning to build this circuit take a close look at my reply to the letter.

That's it for now. See you next month.


**Alf Wilson, W6NIF**  
Editor

# ICOM MOBILE! ICOM MOBILE!

TAKE ANOTHER LOOK AT THE POPULAR MOBILE TWINS . . .  
IC-260A AND IC-255A.

**ICOM IC-260A.** Enjoy VHF mobile at its best. Sideband, FM or CW, the ICOM IC-260A does it all. The ICOM IC-260A contains all the features a mobile operator would want in a compact 2 meter mobile package with FM, SSB, CW operation. Features customers ask for most including:

- ★ Squelch on SSB. The 260A will automatically and silently scan the SSB portion of the band seeking out the SSB activity on 2.
- ★ 3 memories built in.
- ★ Memory scan.
- ★ Programmable band scan.
- ★ 600kc repeater offset built in.
- ★ Variable repeater split — with the 2 built in in VFOs, it's possible to work the odd splits.
- ★ Multimode operation — USB, LSB, CW, and FM. Great for getting into OSCAR, plus enjoying SSB rag chewing as well as repeater operation.

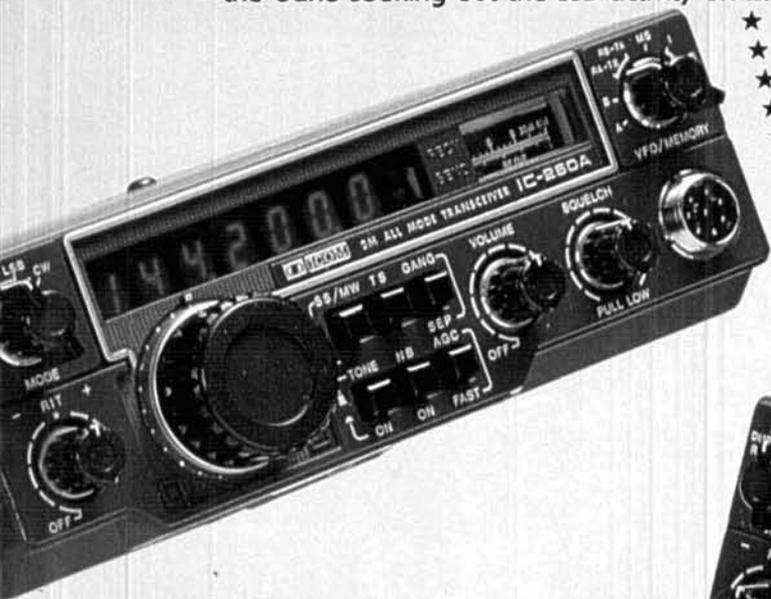

**ICOM IC-255A.** Features that have made the field proven and tested IC-255A the most popular 2 meter FM rig on the air today.

- ★ 25 W / 1 W battery saving output.
- ★ Scanning (memory and programmable limit band scan), now with automatic scan resume.
- ★ Programmable splits — Flexibility for new repeater offsets.
- ★ Dual speed tuning — 15 KHz Steps, 5 KHz Steps with TS Switch depressed.
- ★ 5 memory channels — For easy access to your favorite repeaters.
- ★ Dual VFO's built in, lockable, mobile mount, dynamic mic standard, RIT fine tuning.
- ★ Simple, easy to use single knob tuning system for mobile operation.



HF/VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT



# ICOM

2112 116th NE, Bellevue, WA 98004  
3331 Towerwood Drive, Dallas, TX 75234

## Two Meter Boomers

Whether you have the space for the 3.2  $\lambda$  32-19 or the compact 2.2  $\lambda$  models, two meter Boomers are your best choice. They offer the maximum gain available for their boom length (See NBS no. 688). They feature trigon reflectors for additional front-to-back ratio and clearer patterns. All stainless steel hardware and heavy gauge heat treated aluminum are used throughout. Whatever your choice of two meter amateur activity, the Boomer will fill your needs. For FM use the 228FB or 214FB. For CW/SSB on the low end use 32-19 or 214B, in EME, DX or just reliable QSOs Boomer will perform for you.

## Six Meter Boomer

The new six meter Boomer offers more boom and more gain from its new element spacing. The six meter Boomer has Cushcraft's typical attention to detail, including T match feed with balun, and extra heavy duty mechanical construction. The key to this Boomer's super performance and relatively lightweight is special element spacing and boom length.

## Specifications

Model No.	32-19	214B	214FB	228FB	617-6B
Frequency range (MHz)	144-146	144-146	144.5-148	144.5-148	50.0-51
Forward gain (dBd)	16.2	15.2	15.2	18.2	14
Front to back ratio (dB)	24	24	24	24	30
E-plane B/width (deg)	2x14	2x17	2x17	2x17	2x19
H-plane B/width (deg)	2x17	2x18	2x18	2x9	NA
Side lobe attenuation (dB)	>60	>60	>60	>60	>60
SWR less than (typ)	1.2:1	1.2:1	1.2:1	1.2:1	1.2:1
Impedance (ohm)	50	50	50	50	50
Recommended stacking distance					
E-plane (ft)	14	10	10	10	NA
E-plane (m)	4.27	3.05	3.05	3.05	NA
H-plane (ft)	12	10	10	10	22.5
H-plane (m)	3.66	3.05	3.05	3.05	6.86
Weight (lbs)	12	8	8	22	26
(kg)	5.44	3.63	3.63	9.98	11.79
Length (ft)	22	15	15	15	34
(m)	6.71	4.57	4.57	4.57	10.36
Longest element (in)	40%	40%	39%	39%	113%
(cm)	102.5	102	100.3	100.3	289
Turning radius (ft)	11	7.5	7.5	9.5	17.7
(m)	3.35	2.29	2.29	2.90	5.39
Windload (sq ft)	3.5	1.7	1.7	4.0	4.8
(sq m)	33	16	16	37	45

## Stacking Kits

For stacking two Boomers, use the following coax harness and power divider kits

32-19 = 32-SK 214B = 22-SK 617-6B = 617-SK


When stacking four Boomers, use the following complete stacking kits. They include H frame, harness, hardware and complete instructions.

32-19 = 324-QK 214B = 224-QK

## Specifications, Stacked Boomers



Antenna	2x214-B	2x32-19	2x617-6B	4x214-B	4x32-19
Forward gain (dBd)	17.8	18.8	16.6	20.2	21.2
Front to back ratio (dB)	24	24	30	24	24
E/H plane beamwidth (deg)					
E-plane	34*	28*	35*	17*	12*
H-plane	19*	17*	20*	19*	15*
Stacking dist. Vert. (ft)	10	12	34	10	12
(m)	3.05	3.66	10.36	3.05	3.66
Horiz. (ft)	—	—	—	10	14
(m)	—	—	—	3.05	4.27
Wt approx (lb)	18*	26*	62*	69	97
(kg)	8.16	11.79	28.12	31.30	44.00
Turn radius (ft)	9	11	18	9	13'4"
(m)	2.74	3.35	5.49	2.74	4.06
Wind Area (F <sub>1</sub> <sup>2</sup> )	3.4*	7.0*	9.6*	8.3	15.2
(sq m)	32	65	89	77	1.41

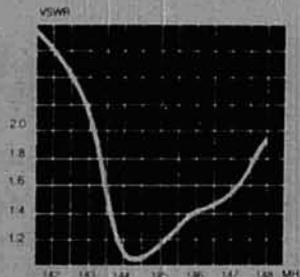(2) 1 + 2.6dB (4) 1 + 2.6 + 2.4 \*Support mast not included  
The nominal dimensions and weights listed are for complete arrays. The antennas and stacking kits must be ordered separately.




# Boomer


6 and 2 meter High Performance Yagis

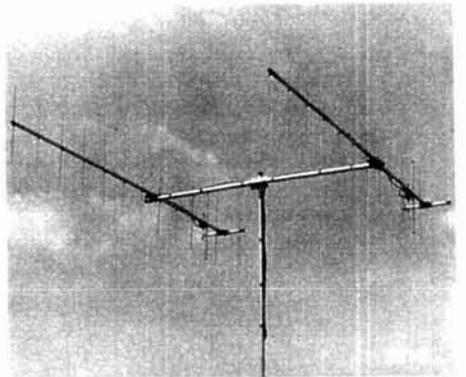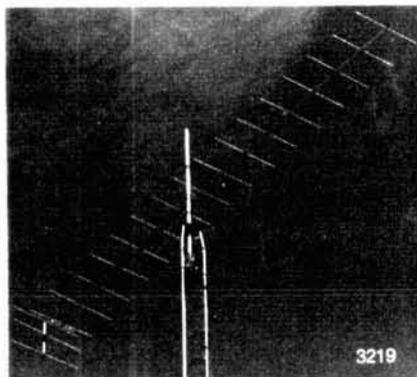

214FB

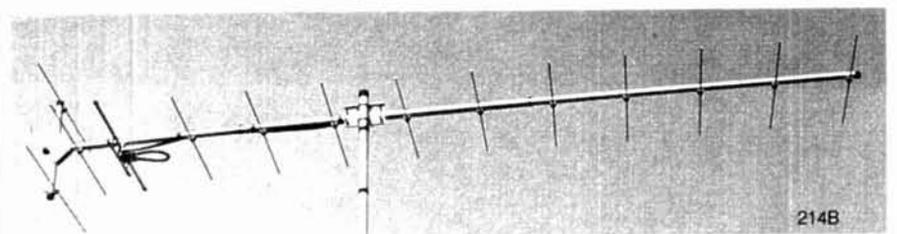

214B

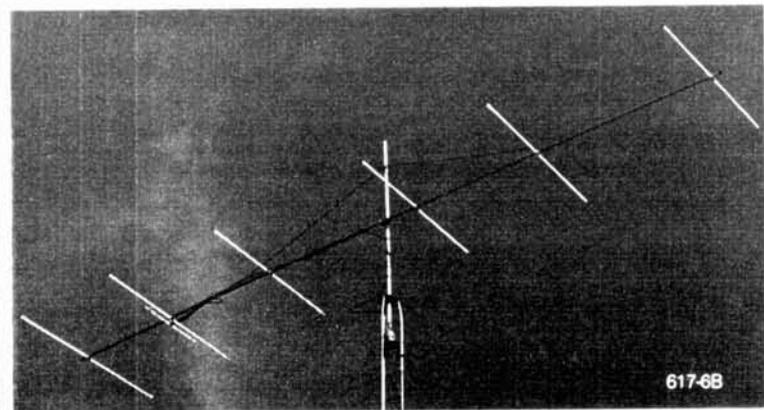

617-6B



The Antenna Company

48 Perimeter Road, P.O. Box 4680  
Manchester, NH 03108

Tell 'em you saw it in HAM RADIO!




## comments

### safety hazard

Dear HR:

The otherwise excellent design of the modular linear amplifier by K8RA in the January, 1981, issue contains a potential safety hazard. In fig. 3, the amplifier control circuit, the two transformers are shown with one side of their primary windings connected to ground. If these primaries ever become disconnected from ground or were not properly soldered to the chassis, the entire chassis would be floating at 110 volts ac above ground. I sure wouldn't want to be touching the chassis if that ever happened.

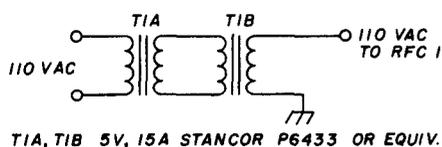Dave Karpiej, K1THP  
Plainville, Connecticut



T1A, T1B 5V, 15A STANCOR P6433 OR EQUIV.

Neither would I. An easy and inexpensive solution is to use two small filament transformers connected back-to-back as shown in the drawing. This circuit thus isolates the two transformers in the amplifier control circuit and provides a much-needed safety feature. Editor.

Dear HR:

The circuit in the September, 1980, issue of *ham radio* referred to by Mr. Nelson is used in several thousand commercial radio telephone trans-

ceivers in New Zealand, and the notes I made on it were as a result of my bench work following modifications to put it on 144 MHz. The shorting of the crystal was only during a test setup. (Surely Mr. Nelson does not think I employ a little green man to short out the crystal each time I switch it on!) It is still flying too, after a year's operation.

True, there were other circuits in his article which probably would have been suitable, but this was the circuit built into the equipment so it had to be got going on its new frequency. It was satisfactory outside the Amateur band in its commercial use.

B.E. Graham Goodger, ZL2RP  
Napier, New Zealand

Dear HR:

Author Mead, K4DE, did an excellent job of making a complex subject clear with his article, "How to Determine True North for Antenna Orientation." The only problem is that two years from now we will all have forgotten where that issue of *ham radio* is, along with its graph for the equation of time. There is another way to determine the time of meridian passage of the sun (local apparent noon), a way which does not require knowledge of the equation of time. It goes like this:

Look in your local newspaper and record the times of sunrise and sunset. Convert the sunset time to 24-hour time by adding 12 hours to it. Subtract the time of sunrise from the time of sunset. Add half the difference to the time of sunrise. You now have the time of meridian passage of the sun for the location for which the times of sunset and sunrise were computed. You will now have to determine what that location is (a call to the local U.S. Weather Service Office is probably your best bet) and make a correction for longitude difference between that location and your QTH, as explained in Mr. Mead's article.

Since the times of sunrise and sunset as published in newspapers are accurate only to the nearest minute,

this method may not be quite as accurate as the method explained by author Mead. However, even though the sun's azimuth is changing more rapidly at meridian passage than at any other time of the day, 30 seconds' error in time will result in only a fraction of a degree of error in the resulting orientation. As an example, at latitude 35 degrees the azimuth change in 4 minutes at meridian passage is 1.7 degrees when the sun's declination is 0 degrees; it's 1.1 degrees when the sun's declination is 23 degrees south and 4.4 degrees when the sun's declination is 23 degrees north. Happy hunting to all you seekers after true north!

Thurman Smithey, N6QX  
Chula Vista, California

Dear HR:

In response to W6DLQ, I would like to say the following: there are a variety of ways of determining true north. W6DLQ has correctly pointed out one of the better-known methods. My article was intended to be both educational and practical, and, in particular, to introduce some little-known concepts that can be used in Amateur Radio practice.

The use of Polaris is limited to those regions of the globe where the star is visible. This rules out the entire Southern Hemisphere, as I'm sure Jim realizes. Azimuth by meridian transit of the sun, on the other hand, does not have this limitation. Further, because Polaris is a circumpolar star (sidereal hour angle 329°, declination 89° N), accurate work requires a theodolite for taking azimuths at each elongation (not simply at dawn and dusk), afterwards splitting the difference. Alternatively, a time sight (at either upper or lower culmination) may be precomputed using the local hour angle of Aries and the Greenwich hour angle of Polaris. Tables for this method, along with latitude corrections, are included in the nautical almanac.

Donald C. Mead, K4DE  
Greensboro, North Carolina

# presstop

CABLE TV SYSTEMS, now expanding rapidly into many major urban areas, are posing a potential threat to Amateur Radio operations. Since they are supposed to be closed (non-radiating) systems, many utilize the VHF spectrum from 50 to above 225 MHz for their multi-channel content, providing subscribers with continuous tuning converters to permit them to tune in cable channels outside the standard 12-channel VHF TV band. This puts some cable-carried signals into the Amateur (as well as aircraft and public safety) bands, and when systems leak (an all-too-common occurrence due to corrosion, loose connectors, or cable damage) interference results. Cases of cable-system interference on Amateur repeater inputs have been documented.

Amateur Interference To Cable Reception is the other side of the coin. Cable subscribers who've paid to watch cable material being transmitted within an Amateur band aren't likely to be very sympathetic when poorly shielded converters pick up Amateur signals. The cable interference issue has come to a head in Richland, Washington, where Amateurs (and others) have thus far successfully opposed Teleprompter's efforts to open its transmissions across the VHF spectrum. Forty to fifty Amateurs were at the Richland City Council meeting January 19 to testify along with unhappy cable subscribers and an airline pilot about radiation and poor system performance. They convinced the council to vote against the expansion, and Teleprompter is required to improve its performance and report back March 3.

ARRL Has Been Watching the development of potential problems from cable TV, and would like to hear from any Amateur who has had difficulties with interference to or from cable TV systems. Because cable TV is a regulated utility, cable systems operators are required to take care of problems with their systems.

ARRL'S DXCC ETHICS RULE, Rule 12, has been strengthened considerably in a move directed primarily at DX stations who have allegedly been demanding payment before providing confirmation of a contact. The rules change comes as two additions to Rule 12, the first addition stating, "Credit for contacts with individuals who have displayed continued poor operating ethics may be disallowed by action of the ARRL Awards Committee," and the second including "confirmation procedures" as "operating ethics."

Impetus For The New Rule tightening had come from the ARRL's DX Advisory Committee, which in turn had been under ongoing pressure from many DXers over the practices of "buying" QSLs. The issue had come to a head following a well-known Israeli Amateur's insistence that only QSLs accompanied by a dollar bill would be acknowledged for his recent operations from various rare Pacific locations. The specifics of the change have been worked out and approved unanimously by the League's Awards Committee, and circulated to the DXAC.

The Expanded Rule 12 will actually become effective with its publication in QST, possibly as early as March. There are no plans to enforce it retroactively.

AN AMATEUR HAS BEEN PUT OFF THE AIR in yet another court action that could have far-reaching implications for the Amateur Radio community. In early December, K2AHL of Springfield, New Jersey, was ordered by Judge Kentz of the New Jersey Superior Court in Elizabeth to cease operating his station, as a result of a suit filed in 1977 by neighbors over TVI and stereo interference.

The Problem Had Surfaced a year earlier, when, without previous warning, he received a letter from the neighbor's lawyer stating that he'd be sued if he didn't stay off the air. Since the suit began, technical experts for both sides have agreed that a proper antenna plus filters would solve the TVI, and a properly designed stereo system would eliminate the problem in that area. Although K2AHL offered them a new stereo, they refused to make any changes. The judge apparently agreed they shouldn't have to, and even told K2AHL's lawyer he would have the FCC suspend K2AHL's license!

The Suit Has Cost K2AHL and his family \$7,000 thus far, and an appeal is estimated at another \$10,000. Nonetheless, he's willing to continue the fight if there are indications the Amateur community is behind him.

K6EOA WAS SENTENCED TO THREE YEARS felony probation and fined \$500 for his threats against FCC engineers who were investigating jamming charges against him in 1979. The sentence was handed down in January by the Superior Court In and For the County of Los Angeles, and his probation will hinge on the condition that he does not use any of his Amateur equipment during the probation period and that he does not threaten, call, or harass either FCC officials or certain specified area Amateurs during his three years on probation.

He Will Also Be Required to obtain psychiatric treatment from a qualified M.D. at least once a week, and must obey all instructions from his probation officer and all other laws during his probation. Failure to comply with any of these conditions could put him into prison for the balance of the three years. The judge said the provision that he not use his Amateur equipment was an appropriate one in this case, since Munson had used his Amateur station in committing his crime.



# MFJ Super Keyboard

*For \$279.95 you get: CW, Baudot, ASCII, buffer, programmable and automatic messages. Morse code practice, full featured keyer, human engineering.*

Sending CW has always been a task, especially when you get a little tired. Electronic keyers help, but it's still too much work.

Now MFJ has a Super Keyboard that makes sending perfect CW effortless. It also sends Baudot RTTY and ASCII.

"Big deal" you say. "What's so special about that. There are lots of keyboards." Yes, but this one is different.

## HUMAN ENGINEERED

A lot of thought has gone into human engineering the MFJ-494 Super Keyboard.

For example, you press only a one or two key sequence to execute any command.

All controls and keys are positioned logically and labeled clearly for instant recognition.

Pots are used for speed, volume, tone, and weight because they are more human oriented than keystroke sequences and they remember your settings.

A meter gives continuous readout of buffer memory and speed. Two characters before full, the meter lights up red and the sidetone changes pitch.

## PROGRAMMABLE, AUTOMATIC MESSAGES

Four automatic messages and two programmable message memories (A and B) are provided. Messages A and B can be a total of 30 characters. B starts where A ends.

When recalled, each message takes only one character of the buffer. They may be chained and/or repeated via the buffer.

"Well," you say, "that sure is not much memory." But it's more than it seems because of the built-in automatic messages.

For example, type your call into message A. Then by pressing the CQ button you send CQ CQ DE (message A). Press twice to send twice, etc.

The other automatic messages work the same way: CQ TEST DE (message A), DE (message A), ORZ (message A).

Special keys for KN, SK, BT, AS, AA, and AR.

## TEXT BUFFER

The 50 character text buffer sends smooth perfect code even if you "hunt and peck."

Since each automatic or programmable message takes only one buffer character, this gives a far larger effective buffer.

You can preload a message into the buffer. Then when you are ready to transmit press the control key.

You can hold the buffer by pressing the shift key and space bar.

With the buffer in hold, you can send a comment with an external paddle as a keyer. To resume sending buffer, press the control key.

Simply backspace to delete errors.

## RTTY: BAUDOT, ASCII

5 level Baudot is transmitted at 60 WPM. RTTY and CW ID are provided via message A.

Carriage return, line feed, and "LTRS" are sent automatically on the first space after 63 characters on a line. After 70 characters the function is initiated without a space. This gives unbroken words at the receiving end and frees you from sending the carriage return.

All up and down shift is done automatically. A downshift occurs on every space to quickly clear any garbles in reception.

The buffer, programmable and automatic messages, backspace delete and PTT control (keys your rig) are included.

The ASCII mode includes all the features of baudot. Transmission speed is 110 baud. Both upper and lower case are generated.

## MORSE CODE PRACTICE

There are two Morse code practice modes. Mode 1: random length groups of random characters. Mode 2: pseudo random 5 character groups in 8 separate repeatable list. With answer list.

Insert space between characters and groups to form high speed characters at slower speed for easy character recognition.

Select alphabetic only or alphanumeric plus punctuation. Pause function lets you stop and then resume.

## IT'S A KEYSER, TOO

Plug in a paddle to use it as a deluxe full feature keyer with automatic and programmable memories, iambic operation, dot-dash memories, and all the features of the CW mode.

## MORE FEATURES

Tune switch with LED keys transmitter for tuning. Tune key provides continuous dots to save finals. Built-in sidetone and speaker.

PTT (push-to-talk) output keys transmitter for Baudot and ASCII modes.

Reliable solid state keying for CW: grid block, cathode, solid state transmitters (-300 V, 10 ma. Max, +300 V, 100 ma. Max). TTL and open collector outputs for RTTY and ASCII.

Fully shielded. RF proof. All aluminum cabinet. Black bottom, eggshell white top. 12"D x 7"W x 1 1/4"H (front) x 3 1/2"H (back).

9-12 VDC or 110 VAC with optional adapter.

## OPTIONS

**MFJ-53 AFSK PLUG-IN MODULE.** 170 and 850 Hz shift. Output plugs into mic or phone patch jack for FSK with SSB rigs and AFSK with FM or AM rigs. \$39.95 (+ \$3).

**MFJ-54 LOOP KEYING PLUG-IN MODULE.** 300 V, 60 ma. loop keying circuit drives your RTTY printer. Opto-isolated. TTL input for your computer to drive your printer. \$29.95 (+ \$3).

**BENCHER IAMBIC PADDLE.** \$42.95 (+ \$4).

**110 VAC ADAPTER.** \$7.95 (+ \$3).

## A PERSONAL TEST

Give the MFJ-494 Super Keyboard a personal test right in your own ham shack.

Order one from MFJ and try it — no obligation. See how easy it is to operate and how much more enjoyable CW and RTTY can be. If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

To order, call toll free 800-647-1800. Charge VISA, MC or mail check or money order for **\$279.95** for MFJ-494 Super Keyboard, **\$39.95** for MFJ-53 AFSK module, **\$29.95** for the MFJ-54 loop keying module, **\$42.95** for Bencher Paddle, and **\$7.95** for the 110 VAC adapter. Include \$5.00 shipping and handling per order or as indicated in parentheses if items are ordered separately.

Why not really enjoy CW and RTTY? Order your MFJ Super Keyboard at no obligation today.

**TO ORDER OR FOR YOUR NEAREST DEALER  
CALL TOLL FREE . . . . 800-647-1800**

Call 601-323-5869 for technical information, order/repair status. Also call 601-323-5869 outside continental USA and in Mississippi.

Write for FREE catalog, over 60 products

**MFJ ENTERPRISES,  
INCORPORATED**

Box 494, Mississippi State, MS 39762

# HAMVENTION<sup>®</sup> '81 DAYTON

- ★ Technical Forums
- ★ ARRL and FCC Forums
- ★ GIANT 3-Day Flea Market
- ★ New Products and Exhibits
- ★ Grand Banquet
- ★ Women's Activities
- ★ Special Group Meetings
- ★ Microprocessor Forum
- ★ YL Forum
- ★ Hundreds of Prizes
- ★ Amateur of Year Award
- ★ Special Achievement Awards

**April 24, 25, 26, 1981**

**Hara Arena and Exhibition Center – Dayton, Ohio**

Meet your amateur radio friends from all over the world at the internationally famous Dayton HAMVENTION.

Seating will be limited for Grand Banquet and Entertainment on Saturday evening so please make reservations early.

If you have registered within the last 3 years you will receive a brochure in late February. If not write Box 44, Dayton, OH 45401.

Nominations are requested for Radio Amateur of the Year and Special Achievement Awards. Nomination forms are available from Awards Chairman, Box 44, Dayton, OH 45401.

For special motel rates and reservations write to Hamvention Housing, 1980 Winters Tower, Dayton, OH 45423. **NO RESERVATIONS WILL BE ACCEPTED BY TELEPHONE.**

All other inquiries write Box 44, Dayton, OH 45401 or phone (513) 296-1165 — 5-10 P.M. EST.



---

#### Rates for ALL 3 Days:

Admission: \$6 in advance, \$7 at door.

Banquet: \$12 in advance, \$14 at door.

Flea Market Space: \$12 in advance, \$14 at gate.

---


Make checks payable to Dayton HAMVENTION, Box 33, Dayton, OH 45405.

Bring your family and enjoy a great weekend in Dayton.

Sponsored by the Dayton Amateur Radio Association, Inc.
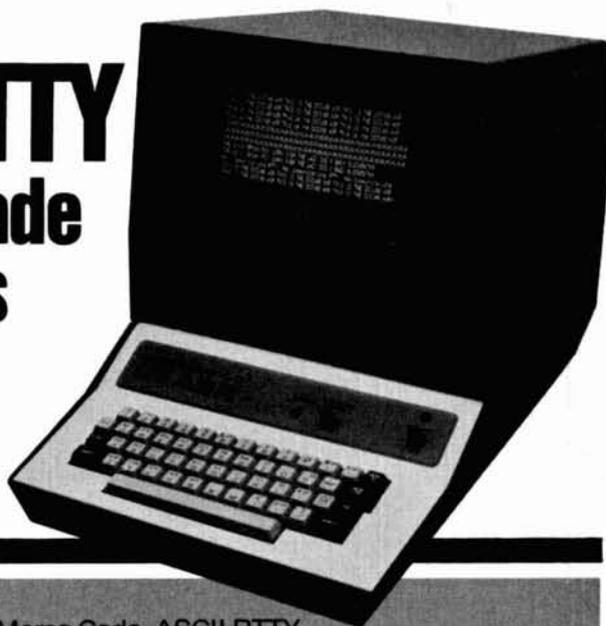
# UNSURPASSED RTTY

No other RTTY terminal made gives you ALL the features of our new DS3100 ASR:



- TX/RX operation with 3 codes: Baudot RTTY, Morse Code, ASCII RTTY
- Storage buffers for 150 lines of RX storage and 50 lines of TX storage
- The HAL "original" split screen shows both RX and TX buffers or whole screen for RX
- Ten programmable "Here Is" messages can be chained from one to next
- The EAROM allows power-off storage of 2 "Here Is" messages and terminal operating conditions
- Programmable WRU answer-back and selective-call features
- Separate CW identification key for RTTY operations
- Automatic TX/RX control with KOS plus 4 keyboard controlled accessory switches
- Internal real time clock keeps 24 hour time plus date
- Newly developed CW receive circuitry and programs give superior CW reception
- New green, P31 phosphor display screen gives clear, eye-easing viewing
- On-screen status indicators give continuous display of terminal operating conditions
- Word-Wrap-Around prevents splitting of words at end of display line
- Continuous, line, and word modes offer flexibility in editing transmit text
- Attractive streamlined metal cabinet gives effective RFI shielding from transmitters

*Here Are More DS3100 ASR Specifications that Give You State-of-the-Art RTTY Operation:*

QBF and RY test messages ■ Loop and RS 232 RTTY I/O ■ Plus or minus CW key output ■ 25 pin EIA modem connector ■ Half or full duplex ■ Upper-lower case ASCII ■ All ASCII control codes ■ Optional line printer for all codes ■ Selectable ASCII parity ■ 110 to 9600 baud ASCII ■ 45 to 100 baud Baudot ■ 1 to 175 WPM Morse receive and transmit ■ UnShift on space for Baudot ■ SYNC idle for RTTY and Morse ■ Break key for RTTY ■ Tune key for Morse ■ Automatic CR-LF ■ 120/240 v, 50/60 Hz power ■ Custom labeled key tops show control operation ■ Copy receive text into transmit buffer ■ TX flags allow segmenting of TX buffer ■ One year warranty

**PRICE: \$1995.00**



**HAL COMMUNICATIONS CORP.**  
Box 365  
Urbana, Illinois 61801  
217-367-7373

For our European Customers Contact:  
Richter & Co., D3000 Hannover 1  
I.E.C. Interelco, 6816 Bissone/Lugano

*Write or give us a call.  
We'll be glad to send you our  
new RTTY catalog.*

# converting surplus AN/UPX-6 cavities

A little scrounging,  
a little work,  
and you're on 1296 MHz  
with 40 watts output

In this day of microprocessor control, frequency synthesis and miniaturization, the thought of using surplus military equipment is almost an anachronism. Nevertheless, Amateur Radio can be served by tried and true methods — experiment! For example, if you've ever considered running more than a few watts output on 1296 MHz and have looked at the price of transistors capable of producing that power, you seek an alternative. One possibility is to obtain and convert the three-cavity assembly (described in this article) from the AN/UPX-6 transmitter. With 100 milliwatts of drive and a 600-volt power supply, you can obtain about 40 watts output on 1296 MHz.

According to *MIL-HDBK-162B*, "Radar Recognition Set AN/UPX-6 is part of the target identification equipment for a radar set in an IFF\* system."

So much for background, and on to the important data. The main component of the AN/UPX-6 is *Radio Receiver-Transmitter RT-264( )/UPX-6*<sup>†</sup>. The three-cavity assembly to be converted is part of that unit.

Each cavity houses a 2C39A, with the three cavities gang-tuned to cover a frequency range of 1080-1130 MHz. I've never seen the complete RT-264 ( )/UPX-6, but the cavity assemblies frequently show up at flea markets. (If any of this equipment is available from surplus dealers, I'm sure that it will be advertised shortly after this article is published.) At any rate, you can identify the complete receiver-transmitter from its nameplate or the cavity assembly alone from the pictorial presentation of **fig. 1**. There may be considerably more hardware attached to the cavities than shown, but only that part of the assembly shown in **fig. 1** is used. Even if the interstage coaxial cables have been cut, don't despair — they can be restored with a minimum of effort provided that the end ferrules are still attached to the cavities.

<sup>†</sup>The use of open parentheses in military nomenclature indicates that the basic number or a letter-suffixed version applies; for example, RT-264/UPX-6, RT-264A/UPX-6, etc.

By Robert S. Stein, W6NBI, 1849 Middleton Avenue, Los Altos, California 94022

\*IFF: Military jargon for "Identification of Friend or Foe." Editor.

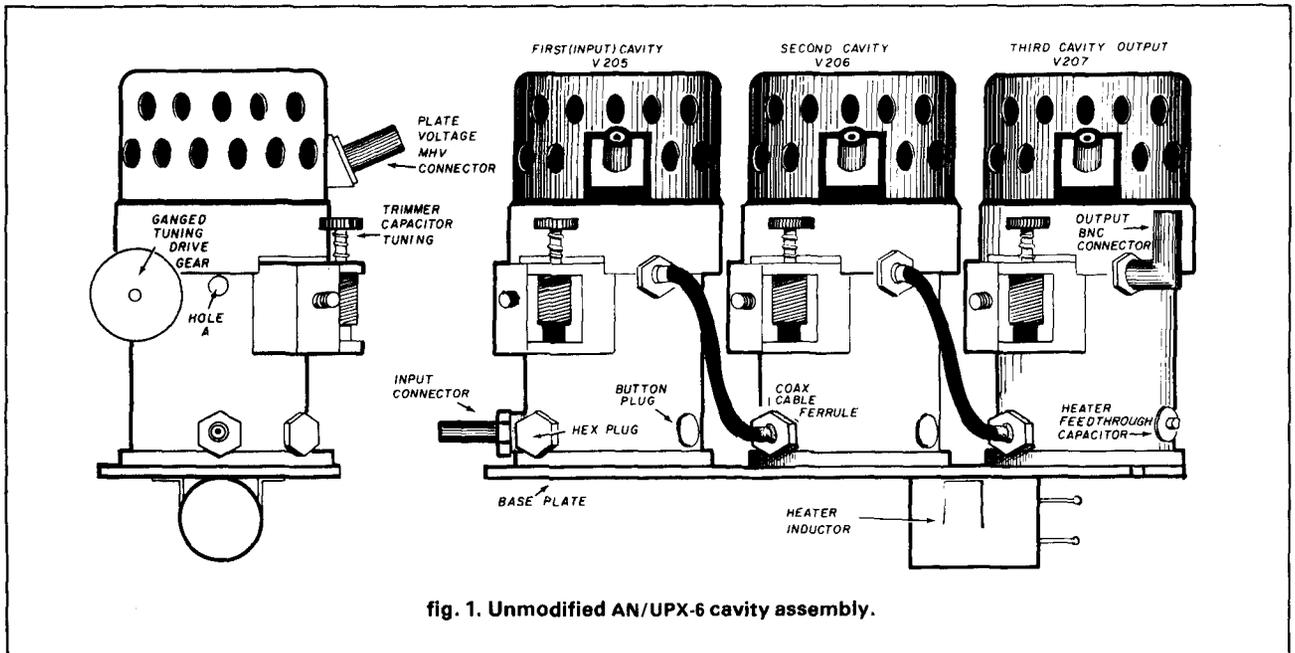


fig. 1. Unmodified AN/UPX-6 cavity assembly.

## modifying the cavities

The mechanical modifications that must be made to raise the cavities' resonant frequency are relatively simple and require only standard hand tools. If you follow my instructions exactly as written, you should be able to complete the basic conversion in a couple of hours:

1. Remove all extraneous parts and material so that only the basic cavity assembly shown in fig. 1 remains. Then refer to fig. 1, as necessary, when performing the following steps.
2. Remove the heater inductor and all wiring between the bases of the cavities and inside the base of the third cavity. Also remove the 10-ohm resistor and solder lug in the base of the third cavity.
3. Remove the perforated cover from each cavity. Remove the three screws, nuts, and washers that secure the spring-loaded tube retainer to the inside of each cover. Save the perforated covers; everything else may be discarded.
4. Carefully withdraw the tubes from the cavities (if you were lucky enough to find tubes in place) and clean out the accumulated dust, cobwebs, and spiders.
5. Remove the square access plate on the side of each cavity opposite the view shown in fig. 1. This permits access to the rotors of the ganged tuning capacitors. Save the access plates and the attaching hardware.
6. Loosen the setscrews that secure all the capacitor rotors, bushings, couplings, and spacers to the tuning shaft.
7. Remove the tuning shafts from the first and third cavities by pulling on the end of the shaft with pliers. Don't worry about using whatever force is necessary — the shaft and all the parts that will fall off are discarded.
8. Loosen the hex nut, at the bottom of the second cavity, which secures the coax cable between the first and second cavities. Unsolder the center of the cable from the input coupling capacitor in the base of the second cavity and pull the coax out of the cavity.
9. Remove the first cavity from the baseplate.
10. Perform step 7 on the second cavity.
11. Loosen the hex nut at the input connection of the first cavity. Unsolder the wire from the center of the input coupling capacitor so that the input connection assembly can be removed and discarded.
12. Remove the hex plug from the base of the first cavity and save the plug.
13. Use a hacksaw to cut off the threaded portion of the input connection boss at the bottom of the first cavity. Then file down the remaining part of the boss so that it is flush with the flange at the base of the cavity.
14. Replace the hex plug that was removed in step 12.
15. Enlarge the input connection hole in the first cavity by drilling it out with a 3/8-inch (9.5-mm) drill.

Then ream or file the hole so that it will accept the threaded end of a UG-1094/U BNC connector. *Be careful not to damage the input coupling capacitor inside the base of the cavity!* Clean out all filings, especially on the faces of the input coupling capacitor.

**16.** Insert the UG-1094/U connector into the input connection hole to determine how much of its center contact must be trimmed so that it just touches the center contact of the input coupling capacitor. Cut and/or file the connector contact accordingly. *NOTE:* Be sure to use a UG-1094/U, not a UG-1094A/U; the latter is too long.

**17.** Install the UG-1094/U connector in the input connection hole, and solder its center contact to the center of the input coupling capacitor.

**18.** On the *input* sides of the first and second cavities only, locate a point directly below hole **A** which is 1/2 inch (12.7 mm) below the bottom of the top flange, or 7/32 inch (5.6 mm) below the bottom of hole **A**. At each of these points, drill and tap a 10-32 (M5) hole.


**19.** On the first cavity only, locate a point directly above the button-type heater feedthrough capacitor (not visible in **fig. 1**), which is 27/32 inch (21.4 mm) below the bottom of the top flange. At this point, drill and tap another 10-32 (M5) hole.

**20.** Use an ohmmeter to determine that there are *no shorts to ground* a) from the center contacts of the input coupling capacitors, b) from the heater feedthrough capacitors, and c) from the plate-voltage connectors of all three cavities.

**21.** In each of the three tapped holes, insert a 10-32 x 5/8 inch (M5 x 16 mm) brass screw so that it butts against the grid line inside the cavity. The screw must seat firmly to ensure a good rf short circuit between the grid line and the cavity wall. Be careful *not to overtighten* the screw and strip the threads in the thin cavity wall.

**22.** Reinstall the first cavity onto the baseplate, then resolder the center conductor of the coax to the input coupling capacitor in the base of the second cavity. Tighten the hex nut.

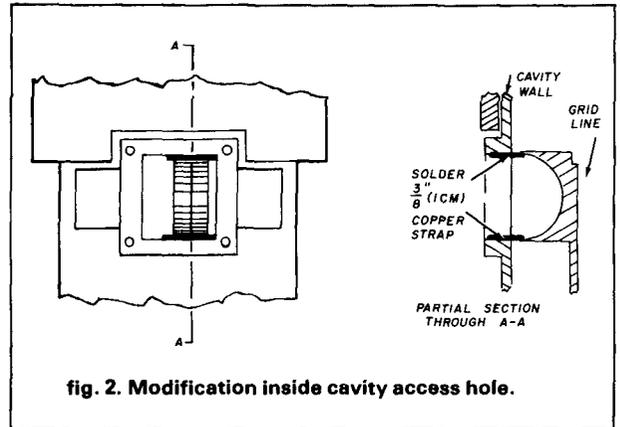**23.** **Fig. 2** is a view looking into the access hole from which the cover was removed in **step 5**. Use a heavy soldering iron to tin the tips of the crescent-shaped bosses on the grid line inside each cavity and to tin the top and bottom horizontal surfaces of the access hole flange. Solder a short length of 3/8-inch (1-cm) wide copper strap between the crescent tips and the flange of the access hole as shown.



**24.** Replace the access hole cover plate on each cavity.

**25.** If the inter-cavity coax cables are intact on your cavity assembly, you have completed the mechanical changes and can proceed directly to **step 46**. However, if you have to replace one or both of the cables, continue with **step 26**.

**26.** If not already done, cut the cable close to the end ferrules.

**27.** Remove and save the hex nut and washer used at the end of each cable.

**28.** At the ends of the old cable, unsolder the center conductor from the output coupling loop (physically, a grounded plate parallel to the cavity wall) and from the input coupling capacitor. Remove the remainder of the coax. Save the ends of the coax to recover the end ferrules.

**29.** Clean out the old solder from the holes in the output coupling loop and the center of the input coupling capacitor.


**30.** Extract the center conductor from the ferrules on the ends of the old coax, and trim off as much of the old coax as possible. Then, using a number 17 drill, enlarge the hole in each ferrule to 0.173 inch (4.4 mm).

**31.** Clean out the solder holes in the ferrules. Make sure that the inside bore of the ferrule is smooth.

**32.** Trim a length of RG-142 B/U coaxial cable to 6-1/2 inches (16.5 cm). (The instructions which follow, covering the assembly of the ferrule to the coax, apply to one end.)

**33.** Strip back the outer jacket 1-1/2 inches (3.8 cm). Take care not to nick the braid.

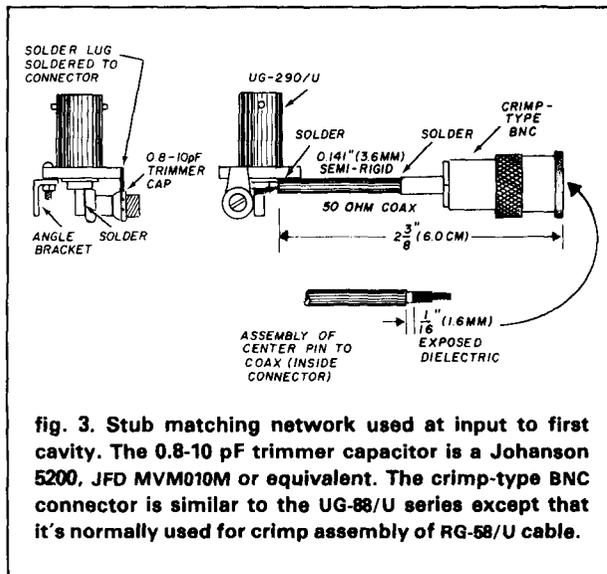**34.** Push the braid back slightly, being careful not to unravel the braid. Cut 1/8 inch (3.2 mm) of dielectric and center conductor off the end.



35. Reform the braid so that it tapers over the cut end, which will make it easier to assemble the ferrule to the cable.

36. Slide the modified ferrule over the end of the coax so that the corrugated end butts against the jacket.

37. Solder the braid to the ferrule through the solder holes in the ferrule. Be sure that the solder is sweated around the entire periphery of the cable.

38. Trim the braid that extends through so that it's flush with the end of the ferrule.

39. Trim the dielectric so that only 1/8-inch (3.2 mm) extends beyond the end of the ferrule. Do not cut off the center conductor.

40. Place one washer and hex nut, removed in step 27, over the end of the coax so that the washer is against the ferrule and the threaded end of the hex nut is against the washer.

41. Place a second washer and hex nut onto the cable so that they are a mirror image of the set already in place.

42. Repeat steps 33 through 39 for the other end.

43. Insert one end of the cable into the top of the applicable cavity so that the bared center conductor passes through the hole in the output coupling loop. Determine how much of the center conductor must be cut off so that it will extend through the coupling loop about 1/32 inch (1 mm). Remove the cable and cut off the excess center conductor.

44. Reinsert the cable center conductor into the hole in the plate coupling loop and tighten the hex nut.

Solder the center conductor to the coupling loop.

45. Insert the other end of the cable into the bottom of the succeeding cavity so that the center conductor passes through the hole in the center of the input coupling capacitor. Tighten the hex nut, solder the center conductor to the capacitor, and trim the excess center conductor.

46. Install a 2C39A tube in each cavity. Replace the perforated covers removed in step 3. Do not substitute a 7289 or 3CX100A5 tube for the 2C39A. Although they are similar, neither will work properly in the modified cavities.

### input matching

The VSWR at the input of the first cavity will be between 40 and 50 (that's right!) after it's been modified. Therefore, to obtain a reasonable power transfer, especially from a solid-state driver, some form of input matching must be provided. A simple matching network, which should bring the VSWR down to better than 2:1, is shown in fig. 3. The configuration is that of a stub matching network in which a discrete variable capacitor is used instead of a shunt capacitive stub, thereby permitting the network to be tuned to compensate for variations in the input impedance of the cavity.

The matching network should be constructed exactly as shown in fig. 3. Use a crimp-type BNC connector, similar to a conventional UG-88/U, designed for RG-58/U cable; the crimping sleeve is not used. Before cutting the semi-rigid coax to length, solder the connector pin to one end, trimmed as shown. Insert the semi-rigid cable into the connector body to position the pin properly. Solder the coax to the connector cap.

Trim the outer conductor to the 2-3/8-inch (6.0-cm) length shown, allowing about 1/2 inch (13 mm) of additional bare center conductor for connection to the center contact of the UG-290/U receptacle. Solder the outer conductor of the coax to the body of the receptacle to minimize the length of the unshielded center conductor to be soldered to the receptacle contact. Trim the excess center conductor after soldering it to the connector.

Solder the trimmer capacitor on the UG-290/U as shown in fig. 3. The small angle bracket is not required electrically; it is used only to secure the connector to the chassis or mounting surface upon which the cavity assembly will ultimately be mounted.

### input VSWR

The input VSWR can be checked at this point, before applying any power to the cavities, if a signal generator, slotted line, and SWR indicator are avail-

able. Otherwise, an alternative check can be performed under operating conditions.

Using the slotted-line technique, you should be able to reduce the input VSWR to 2:1 or less by adjusting the trimmer capacitor on the matching stub. If the measured minimum VSWR is greater than 2:1, add a 5.5-18 pF trimmer across the 2C39A input circuit inside the base of the first cavity. One side of the trimmer should be soldered to the solder lug in the center of the cathode structure (one of the heater rf chokes is connected to this lug). Add a solder lug and nut to one of the studs that support the ends of the cathode structure. Solder the other side of the trimmer to this lug. Adjustment of this capacitor, in conjunction with the matching-stub trimmer, will then result in better than a 2:1 VSWR.

### power supplies

I'll not attempt to detail the heater and plate power supplies, since the choice of plate voltage and bias voltage usually depends on what each person has available and his preference as to control. Instead, I'll present some ideas, along with tube limitations, which may be helpful. I assume that all operation will be CW or SSB.

First let's consider the plate-voltage supply, since bias and control may depend on this voltage. My preference is to use as high a voltage as possible, but not over 1000 volts, on the output stage, and to use about 350 volts on the first two stages. This provides for maximum power output, yet allows the first two tubes to operate with zero bias so that only two heater supplies are required. (More about this under the discussion of heater requirements.)

If the plate voltage is limited to 350 volts, a 2C39A will draw 50 to 60 milliamperes static plate current when zero biased. The plate dissipation limits for the tube are 12 watts with convection cooling and 100 watts with forced-air cooling. Therefore, a small blower or fan is recommended, especially if 500 volts or more are used on the last stage. Placing the blower at the end of the cavity assembly, facing the third cavity, will afford maximum cooling for that stage while also dissipating heat from the first two cavities.

Plate voltage is applied to each cavity through the MHV connectors shown in fig. 1. The required mating MHV connector is an Amphenol 29100 for RG-58/U cable, or an Amphenol 28000 for RG-59/U. The latter is recommended, since the RG-59/U has a higher breakdown voltage rating than RG-58/U. If you can't obtain the mating MHV connectors, or if the receptacles on the cavities are damaged, the cavity receptacles can be replaced with more conventional UG-290/U BNC connectors. In that case, use UG-260/U cable connectors so that RG-59/U can be used.

**Biasing.** Because the 2C39As are used as grounded-grid amplifiers, with the grids at dc ground, a positive dc bias must be applied to the common heater-cathode connection when bias is required. This means that each tube must have its own heater supply unless the tubes are zero biased or operated at sufficiently low plate voltages so that a common bias source will keep the plate currents of two or three tubes reasonably close to a bogey value.

As the cavities exist (after the preceding modifications have been made), the heater-cathode leads of the first and second stages are returned to ground through rf chokes, while the rf choke in the other heater lead in each cavity is brought to a feedthrough capacitor in the cavity wall. In the output cavity, both heater rf chokes connect to feedthrough capacitors.

If the plate voltage for the first two stages is limited to about 350 volts, the heater and bias circuits shown in fig. 4A may be used. The values of R1 and R2 must be such that the heater voltage, measured at the heater ends of the rf chokes, is 5.5 volts. CR<sub>k</sub> provides cathode bias and is made of several silicon rectifiers (1N4001 or similar), so that the quiescent

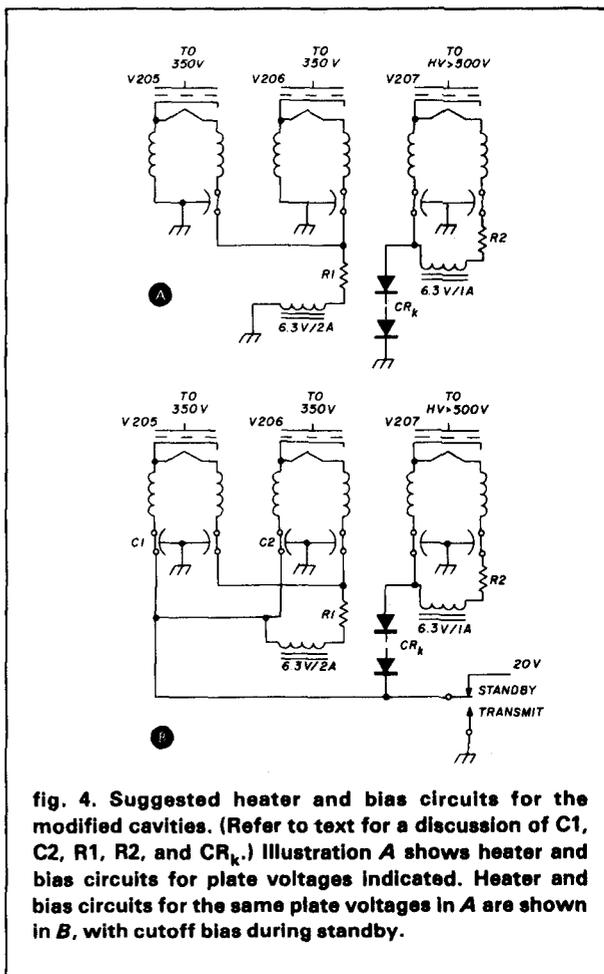


fig. 4. Suggested heater and bias circuits for the modified cavities. (Refer to text for a discussion of C1, C2, R1, R2, and CR<sub>k</sub>.) Illustration A shows heater and bias circuits for plate voltages indicated. Heater and bias circuits for the same plate voltages in A are shown in B, with cutoff bias during standby.

plate current of V207 is between 40 and 60 milliamperes; the number of diodes in series will depend on the plate voltage and the tube characteristics. With a plate supply of 600-700 volts, four diodes should provide the proper bias.

If higher plate voltages are used on the first two stages, or if either is not to be operated under zero-bias conditions, a separate heater transformer will be needed for each tube. The tubes may then be individually biased, in the manner shown for V207.

**Recommended circuit.** One of my phobias is to have transmitting tubes draw plate current during standby. Consequently, I use the biasing circuit shown in **fig. 4B**. Cutoff bias of about +20 volts is applied to the cathodes of all three tubes through the normally closed contacts of a relay. When the relay is energized for transmit, V205 and V206 cathodes and the low end of CR<sub>k</sub> are grounded, allowing plate current to flow. This requires lifting the heater-cathode returns of V205 and V206 from ground as follows:

Cut the ground ends of the rf chokes in the bases of the first and second cavities. Remove the button plug at the bottom of each cavity (see **fig. 1**) and replace it with a button-type feedthrough capacitor, designated C1 and C2 in **fig. 4B** (similar to those used for the ungrounded heater connections). The capacitance value isn't critical; anything between 100 and 1500 pF will do. Connect the ungrounded end of the rf choke to the new feedthrough capacitor.

## operation

After the power supply smoke test has been made and the tube plate currents checked, connect the input matching network to the input connector on the first cavity, then connect your exciter to the matching network. If the matching network capacitor has not previously been adjusted for minimum VSWR, set it near minimum capacitance.

The trimmer capacitors on the cavities (see **fig. 1**) tune the cavities to resonance, the old ganged tuning capacitors having been removed. With rf drive applied, the cavity trimmers are tuned for maximum output, as is the matching network capacitor. If the additional trimmer capacitor has been added to the input of the first stage to minimize the input VSWR, it may also be adjusted for maximum output. Its effect will be slight, however, if it has been set for best VSWR.

## wrap-up

That's all there is to getting the modified cavities on the air. The output-stage plate current will be about 200 milliamperes at full output. However, don't allow the tube to draw that much current for any extended length of time. Maximum plate current

for a 2C39A is 125 milliamperes. Plate efficiency will be about 30 per cent, which is consistent with the tube specifications.

A drive level of 100 milliwatts should be more than enough to obtain full output at any final-stage plate voltage up to 1000 volts.

If you don't have an rf power meter, you can calculate the output power from the dc input power, assuming a plate efficiency of 30 per cent. (We can ignore the feedthrough power from the second stage, since we're assuming the efficiency to arrive at only a rough estimate of the output.)

If you don't obtain output power corresponding to about 26 dB of power gain in the cavity assembly, one or more of the tubes may be weak. However, if the input VSWR hasn't been checked, it's possible that the mismatch loss between exciter and first stage is the culprit. Add a trimmer capacitor across the first-stage input, as described earlier, then adjust this capacitor, along with the trimmer on the input matching network, for maximum output. This should solve the problem.

## postscripts

At drive levels under 1 milliwatt, the over-all gain of the three cavities is 28-34 dB, depending on plate voltages. However, at the higher drive levels needed to produce power outputs of more than 20 watts, full gain can't be realized. It's likely that the over-all gain might be increased at these higher outputs, thereby reducing the drive levels required, by replacing the interstage connecting cables with matching networks.

Although I've not tried this, preferring to stay with the simpler brute-force approach, my rationale is based on the VSWR that the first stage presents after modification. There's no reason not to believe that severe mismatches may occur between first and second and second and third stages.


It's interesting to conjecture on the results that might be obtained by matching. If we assume a gain of 11 dB per stage and an output of 40 watts, only 20 milliwatts of drive should be required.

It should also be apparent that one, two, or three cavities can be used, depending on available drive power. I've run tests using only two cavities and obtained approximately 16 watts output with a drive level of 100 milliwatts — a power gain of 22 dB — indicating that the limiting occurs in the final stage when three cavities are used.

I'd be interested in hearing from anyone who attempts to improve the interstage matching. I'll also answer all inquiries accompanied by a self-addressed, stamped envelope.

**ham radio**

# DXer's diary

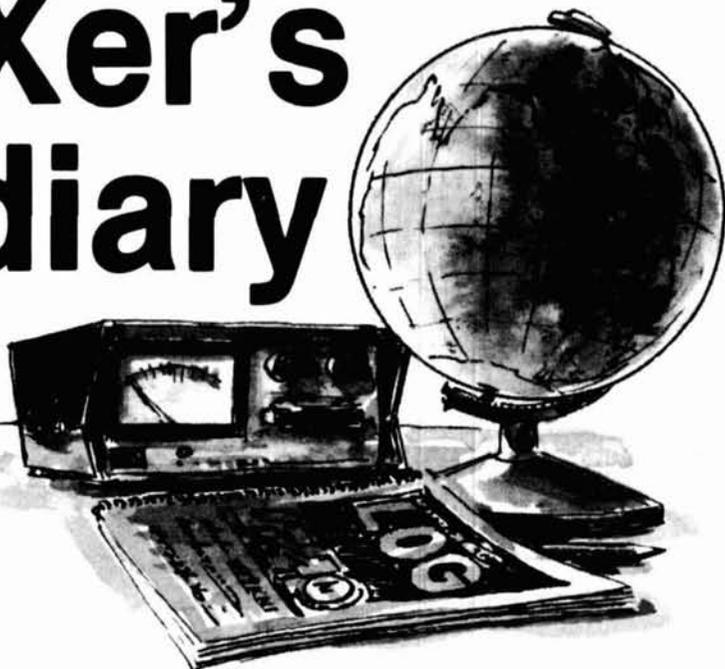

Author Locher was a popular contributor to *Ham Radio Horizons*. Because many *Horizons* readers are now receiving *ham radio*, we are presenting this episode of W9KNI's ongoing battle of the big guns in the DX world. Want to see more articles by W9KNI? Let us know how you like it.

Editor.

By Bob Locher, W9KNI

**It's Saturday at 1300Z;** 7 AM in Chicago, a late winter's morning. Considering the hour, I feel pretty good. An early retirement last night and a good sleep, and now I'm ready for DX.

The warm glow of the dial lamps, the smell of the fresh coffee, the warmth of my heavy bathrobe pulled tightly around me, the headphones nestled over my ears — I'm at peace with the world and ready to go.

There are a couple of stations I'd like to tie into this morning. That A51RT is high on my list; three times now I've heard him, with nothing to show for it. Not that he's being pursued all that widely; he's been listed in the DX bulletins only once, and that was for an evening path. Every time I've heard him was on a morning path. Of course, as soon as I QSO him, I'll report it to the DX bulletins, but with the luck I've been having with that one, the last thing I need is more competition.

But the A51 isn't the only DX station I'm after. The bands were full of

talk and reports last night that ace DXpeditioner KP2A had managed to pull off both a ticket and a pass for Cocos-Keeling, VK9Y, and would be operational any moment now.

Cocos-Keeling has always been a tough one; not an easy shot for propagation to start with, and a location remote from anywhere. Add to that Australia's military making it a high-security area a couple of years ago, and you have the makings of a rare country, a very rare country.

Every one knows the difference between a rare country and a very rare country: A rare country is one that you have and your buddy doesn't. A very rare country is one that your buddy has and you don't. I don't have Cocos Keeling.

Let's see how the band sounds. Hmm. A number of signals; that's certainly a good sign. Let's see where they are from. Haul the antenna around — let's start straight west. Watching for both the A51 and the Cocos-Keeling station poses certain difficulties — beam headings. The

A51 has been coming through on long path, almost dead south, over the Antarctic. The Cocos-Keeling bearing, on the other hand, is more northwest, over Japan. The signal from the A51 is weak enough that I can copy it only when the antenna's on him; no way can I copy him on the side or back of my antenna. Perhaps I should leave my antenna on the long path for the A51?

On the other hand, I can develop a very good case for leaving the antenna on that VK9Y bearing. With any DXpedition, or for that matter, any new country, it is always desirable and advantageous to grab a QSO ASAP — As Soon As Possible!

I'll never forget my lesson of Serrana Bank some years ago. A DXpedition came on one evening from there, and seemingly half the world was in one pileup. I decided to wait a day, so that getting a QSO would be easier. Guess what? An approaching hurricane forced them off the island at dawn, and they never went back. I had to wait years for a Serrana Bank QSO from another DXpedition.

On top of that lesson, the path to Cocos-Keeling is a long one, and this time of year propagation can be a bit tenuous. We certainly will get openings, but the peak part of any opening won't be over half an hour, and perhaps less. Catching the peak is vital on a DXpedition like Cocos-Keeling; the competition can be so fierce from all over the world that in a really huge pileup you need all the help you can get from propagation.

Even so, the easiest way is to catch him calling CQ, and nail him before the ravaging hordes get onto him.

KP2A is fairly predictable. He's a superb operator, cool under fire, which, God knows, he's going to need to be, and he controls pileups very well from DXpedition QTHs. From past observation, I know that he likes to work 5 to 10 kHz up from his own frequency. Also, he has a knack of getting a good signal out; he seems to know how to set up

decent temporary antennas, I guess.

Okay, enough wool gathering. Let's see here, it's 1314Z. Okay, I haven't yet heard the A51 before 1340Z, so I could start watching for him at 1330Z. That would give me fifteen more minutes to hunt for the VK9Y. Then, I think, if there's no action, I'll swing the antenna every five minutes to watch for both the A51 and the VK9Y. If I come across either of them, I'll devote all my attention to that one. So, let's go! I move the antenna into the northwest, the path for Cocos-Keeling, and start hunting.

KP2A seems to like to transmit around 020. I'll center my tuning around there. Let's see what we have here. Lots of W signals, some pretty loud. Phooey. Guess the skip is a bit short today. It figures. If that VK9 shows, sure do hope that the traffic cops don't show up. There's a VK4.

Yes, VK4RF. Good signals. That's not the exact path for Cocos-Keeling, but there's hope.

There go four or five fellows chasing someone. Maybe it's my boy? No — there — one of the Ws gives the call of the fellow he's calling. It's P29ET; Papua/New Guinea. That's a nice catch, but I don't need it. But let's wait a bit and see what kind of signal the P29 has. There he is. Fine, a good S-7 and no flutter. Ohhkayy — if Cocos is going to show up soon, I should be in tall clover, propagation-wise. That P29 isn't as far down the path as the VK9Y is, but it's pretty much the same path, and that's the tougher part of it. It's a pretty safe bet that we'll have at least adequate propagation to Cocos-Keeling.

Let's flip on 2 meters to see if anyone has any late information or hot tips.

"Hellooooo out there. W9KNI here. Any late information on the VK9Y?"

"Yeah. W9KNI from K9QVB. Hello, Bob. I was just going to call you. He showed up a few minutes ago on 20 sideband. He's on four-

teen-one-nine-two, listening up. Said he's going to CW on oh-twenty at fourteen hundred zulu. He's not real strong. Over."

"Okay, great, John, and thanks for the hot stuff. Who's he working?"

"He's mostly on W4s. He's getting a few threes, and W9ZRZ with that super stacked system got him too. But I think the W4s have a long-path opening to him, and they're working it to death. The guy's a pretty good op, for sure."

"Roger, he's that. What path are you copying him on?"

"Definitely short path. I can't hear a whisper on long path. But he's pretty weak. I think he's starting to get stronger, though."

"Okay, fine, John. Appreciate the info. You need him too, I think?"



"Yeah, sure do, Bob. I thought I worked that VK9YK a couple of years ago, but I got my card back with a 'Not In Log,' so I guess I didn't make it. Yeah, I need this one. But I'm not even calling him right now; he's four and four here, and the W4s are all giving him five-eights and five-nines. Hope we get a better shot on CW."

"Okay, I'm going to run and get a cup of coffee, John. I'll be back in five minutes or less. Good hunting. K9QVB from W9KNI."

"Okay, Bob. I'll squawk if anything changes. W9KNI from K9QVB."

I run up the stairs and turn on the water for my coffee. The juices are

starting to flow — a shot at a new one — with a good operator, too. And, on a Saturday. Incredible! It's been a bit dry of late for new ones in the log. Oh, I heard a few — the A6X, the A51, the VK9 on Norfolk. But I'm not chasing SWL awards; I'm looking for QSLs that say, "RST 599" on them, or whatever report. And lately, I'm not getting any of them into the log book. Maybe today's my day.

In minutes I'm back at the rig. Let's see here... I adjust the headset a bit to seat it comfortably, and move the gleaming Bencher paddle to where it is most comfortably placed. KP2A is a pretty sharp operator — I ease the keyer speed up a bit, and dry fire a few letters to get my timing down. My fingers respond almost instantly to the higher speed

— I feel like a sports car driver just before the start of the race: headphones are my driving helmet, my paddle the gear shift, the receiver dial my steering wheel. I fire up the linear, get it all tuned on an empty frequency just above 14030, and I'm set.

"W9KNI from K9QVB. Okay, Bob, he just said that he's going to take a two-minute break, and then be on fourteen-oh-twenty. You ready?"

"Yeah. K9QVB from W9KNI. Great, John, thanks. Yeah, I'm as ready as I'll ever be. Hope we get him."

I reach for my cup of coffee — and leave it — I've got butterflies enough.

I am the knight in armor at the end of the lists, awaiting the trumpet call. I am the Spitfire pilot revving up the engine at the end of the runway, just before takeoff to certain battle. I listen to all the carriers tuning up as I set my receiver on 14,025 — they are all out there, waiting. It's me against the wolfpack.

"Hey Bob?"

"Yeah, John, go ahead."

"Hey, don't forget, it's only a hobby."

That breaks the tension, and my wild flights of fancy. I laugh.

"Naw, you got it all wrong, John. It's not a matter of life and death. It's more important than that."

"Haw, Haw. Okay, he should be on any second now. W9KNI from K9QVB."

"Roger, K9QVB from W9KNI. Hey John, what call is he signing?"

"Oh. Yeah, he's VK9YR — Yankee Radio."

"Thanks."

Ohhkay! Let's go. Lemme see here. KP2A likes to set up a little lower than the usual 025; he'll probably transmit on 14,021 or 022, and listen up around 030.

Huh, what's that? There, on 020, maybe 559, 569, "5NN W4QM, K."

4QM — yeah, he's one of the South Florida aces. I give the receiver a quick turn up a few kHz. "5NN TU VK9YR DE W4QM E E." Yup, there he is, as I pick up the VK9 again.

"R 73 QRZ NA NA UP5 DE VK9YR K."

I blindly set my VFO on 025, and stroke the paddle.

"DE W9KNI K."

"4QQN 5NN K." Hmm. Another four. I check my transmit frequency. There's QQN. Okay, I'm half a kHz low. Move it up. There, a hair above QQN. The VK9 clears. Call. Keep it short, this fellow's good. Okay, N4OW got him. He's in Florida too. He clears. Call now. Huh? He's back to N4WW this time. Florida again. There's K9QVB calling too. Okay, I don't need to alert him on 2. The



VK9 clears; call now! There. He's back to W4FLA — and Florida again. Let's cool it for a moment and consider all this.

I've been calling at about the right frequency every time, almost, but it sure looks like the W4s are milking the long path for all it's worth. But it's getting later in the morning, and that path can't hold up very much longer. Also, our peak time should be coming fairly soon; with any luck we Midwesterners should get a good shot within the next half hour. The fellows that are going to get stung are the boys on the upper East Coast. Their short path peak is being overridden by the Florida long path shot, and by the time that path is gone, so will the East Coast short path. Oh well, they leave us for dead on the short path into the "middle east," so I guess it will all come out in the wash.

But, while the fours still have it in such convincing fashion, I'd be smart to quit transmitting and study his techniques. That way, when he does start working W9s, I'll be ready for him. Okay, he's back to W4MLP. Find MLP. There he is; note the frequency — yes, 026.3, plus or minus.

He clears. Now — KB4CH has him. Okay, 026.6. He clears. Listen to that pileup! Back to the VK9. Yes, he's got KT4X. There's the KT4, 026.9. All right! The VK9 is working up through the pile. Fast, too. One call seems to get him. None of your 1X3s for this boy. Great!

4BW — 027.1. W9QN — huh? No, he's in Florida too, 027.3. Thought for a moment we nines had broken the stranglehold. Oh well, our turn will come.

Hey, this boy IS good. I notice with admiration how he's picking up only the stations that give him an X1 call — in other words only sign their own call, and only once. That's the mark of a very good DXpedition operator. There are two ways to do that, and both are tough. One is copy several signals simultaneously and choose the one that meets the X1 rule. The other is to copy the call a QSO ahead and pick it up one QSO later. But either is tough to do. However, a skilled operator can get a QSO rate that is 50 per cent higher than he can without that selection. And at the rate the VK9's going he might be good for a 150-QSO-per-hour rate. That's really great for us: it

means our chance of a QSO in a brief opening is greatly enhanced.

Okay, KG4TH — where's he? Oh, yes, 027.6. Now it's N4BKU; yup, 028.0. KB4AJ 028.3. Okay, he's moving up 300 to 350 hertz every QSO, apparently always moving after each. Now, is he going to keep moving up, or will he stop and start tuning down, or will he suddenly move down and start tuning up?

W4TO — where's he? He ought to be about 028.6. But no. Back to the VK9's frequency. He clears. Maybe he's moved. There, he's got N4AR. Wait a minute! That isn't Florida, that's Bill in Kentucky. Maybe the path has shifted. Quick, go ahead and look for him. He's probably a back-scatter signal.

Yes! There he is, 024.2. All right! Let's try 024.5. Call; just one. The

paddle dances under my fingers, "DE W9KNI."

"WB8EUN 5NN K." Darn! Okay, there's EUN, right on the same frequency I was. He clears. "DE W9KNI K."

"W9BW DE VK9YR 5NN K." Where's BW? There, above me about 200 hertz. Up 300 for me above BW.

"DE W9KNI K."

"K9QVB 5NN K." Good for QVB. There he is, just about zero with me. Okay, up 200 again.

"DE W9KNI K."

"W0SR 5NN K." Yup, the fours have lost the path. Hope I get one. There's 0SR on backscatter. He's about 200 above me. Okay, my steps up seem to be a little too small now; he seems to be jumping about 400 at a time. Move the VFO.

"DE W9KNI K."

"K9RF 5NN DE VK9YR K." Well, the nines seem to have a lock on him. It would be nice if I could be one of them. Up another 400 hertz.

"DE W9KNI K."

"K9DX 5NN K." Where's DX? He's nowhere near my frequency. Quick, look down. Yes! 023 and a hair. The VK9 shifted back down. Quick, about 300 above DX. Call!

"DE W9KNI K."

"W9KNI 5NN DE VK9YR."

"VK9YR 5NN TNX DE W9KNI."

"R T U E E."

Wow! Just like that. The actual QSO took under ten seconds. But he's all mine. I'm in the log. I notice that I'm breathing fast. Ah, it feels good to inscribe the rest of the details into the log.

I turn 2 meters back up; I must have turned it down earlier in the fray, but I don't remember.

"Twenty-eight. Twenty-eight."

"DWQ's got him. Way to go Ed!"

"Twenty-eight point five, eight point five." I recognize K9DX's voice.

"It's W0VX." There's K9RF giving the call signs.

"Twenty nine oh. Watch it, he's going to move back down."

"K5LM."

"He moved. Oh twenty three two. Call up a little."

"K9AJ, good work, Mike."

"Twenty three five."

Ah, the 2-meter net is having one of its finest hours spotting frequencies for the rest of the club. It was a free-for-all at first, but as soon as a few members made it through, they started coaching the rest. But I'm glad I figured it by myself. Not that I'm against help, but it is nice the other way.

"W9OA — way to go, George."

The basement lights blink; my signal to lift up my headset a moment.

"Bob, breakfast's ready." A wave of sausage aroma follows my wife's voice. They don't need me here on 2 meters — and I'm hungry!

**ham radio**



# Collins Owners' Reports:

## KWM-2 KWM-2A

A survey of owners' opinions on these two popular transceivers

The April, 1980, issues of *ham radio* and *Ham Radio Horizons* carried questionnaires directed at the owners of Collins equipment: 32S-line transmitters, 75S-line receivers, and the KWM-2 and KWM-2A transceiver. In this issue, we will present our readers' opinions on the KWM-2/2A transceiver. Next month, we'll give you a rundown on what our readers had to say about their S-line gear.

### the good features

By far and away the single most commonly mentioned feature of the Collins KWM-2/2A transceiver is its great reliability. More than any other character-

istic, reliability seems to be the hallmark of these radios. In a way, that's not too surprising: many of these rigs (27,000 have been built since 1958) have seen continual use for more than 20 years. Virtually every owner of a KWM-2 or KWM-2A included praise for its reliability among his comments.

Running just behind reliability on the list of best features were stability and audio quality. Take a look at the table of Best Features and you'll get a feel for just how many owners of these Collins radios were happy about the superior stability and audio of their transceivers. Also well represented among the Best Features were wide frequency coverage (making it possible to operate the new frequencies opened to Amateurs as a result of the 1979 WARC), ease of operation, solid construction, and dial accuracy. Below are some representative comments by our respondents to the question, What is the rig's best feature?

"The KWM-2A has excellent stability, accurate readout, and good audio quality both transmit and receive. It has large knobs that are easy to use, and

By Martin Hanft, WB1CHQ, Production Editor, *ham radio* magazine

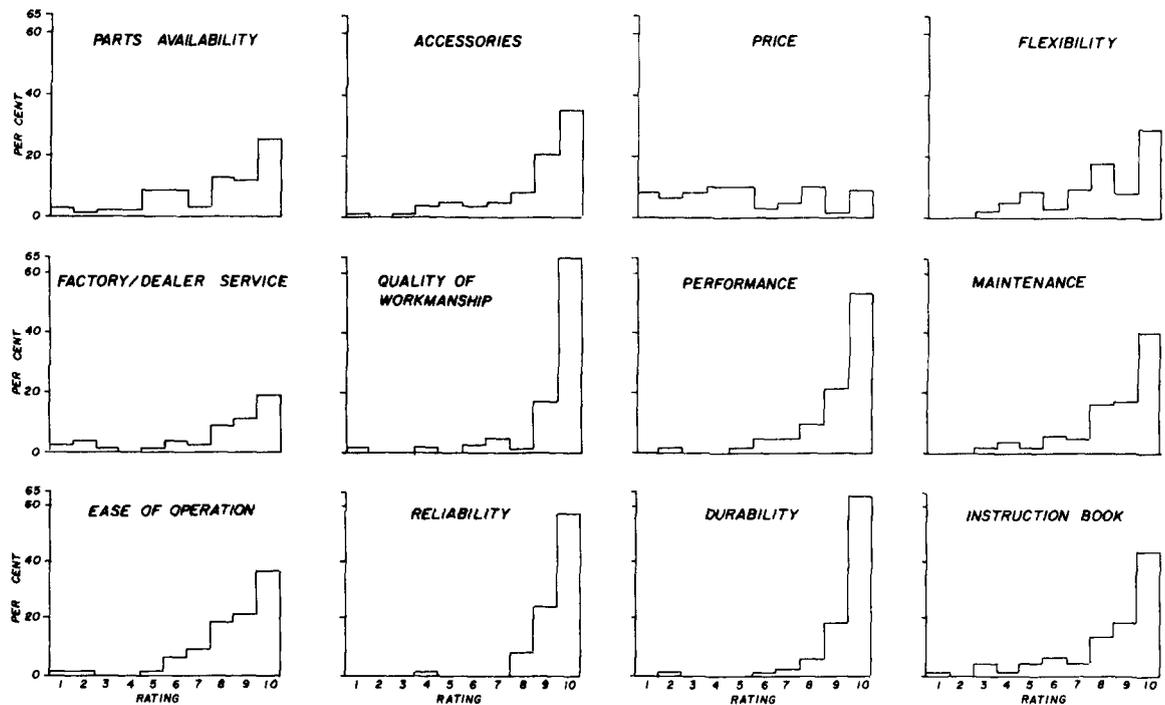


fig. 1. How the KWM-2/2A was rated, from 1 (poor) to 10 (perfect).

it's built like a battleship. Long life expectancy and very neat looking design of front panel." — WØRJ

"Wide frequency coverage, good reliability, easy to operate, good human engineering, good frequency readout and stability, no TVI problems." — W3PE

table 1. Best features	
	percent
reliability	37
stability	25
superior audio quality	18
wide frequency coverage	14
dial accuracy	13
solid construction	13
easy to operate	11
good frequency readout	11
good selectivity	6
front panel design	4
easy to service	4
frequency accuracy	3
service manual	3
resale value	3
no TVI	1
VFO	1

"The VFO. It is low-drift and calibrated accurately enough to be precisely resettable." — KH6S

"Absolutely superb audio quality. Addition of a speech processor increases average audio, but disturbs pureness of the audio signal as originally designed by Collins. Collins Field Service Engineering department very helpful, considerate, and prompt." — WD4CWF

"Dial accuracy and dependability. Stability. Every bit as accurate as the digital (readout), and certainly the dial is easier to turn with the thumb hole." — WA6UJL

"Reliability, ease of operation, and solid construction." — VE3RO

"High resale value. The radio has good audio and is easy to maintain. There's a very good instruction and service book that comes with the equipment." — K5NG

"The design of the receiver circuits. The permeability tuned rf circuits plus the careful design of the whole receive chain are, to me, the hallmarks of this rig. There is a combination of sensitivity and rejection of unwanted signals that is as good as anything manufactured today. There is still nothing that will outperform this KWM-2." — K5RSG

"Superb audio quality combined with sharp selec-

tivity inherent in the mechanical filter. Truly accurate frequency readout without having to resort to digital displays. Beautiful appearance."

"It's a well-engineered tube-type rig, which leads to unusually good frequency stability, matchless audio, tolerance for SWR, and relatively easy owner servicing." — WØRHW

"Faults with the Collins are few and far between." — WAØPSG

"Dependability." — K9LKA

"Durability: This rig is over 20 years old and has needed only minor servicing." — WD5CKA

"This rig with its external VFO, crystal pack, and speech processor is exactly what I need for Navy MARS activities. It will hit all the oddball frequencies and give me all of the output I need without a linear." — W9NZF

"I like the 1-kHz readout on the dial. It has the best sounding audio of any rig I have used, and it is super reliable. A real easy rig to operate." — K9BQL

"Selectivity, sensitivity, and calibration. I would buy another, if I could convince my XYL!" — WB2VXY

"Frequency coverage. Plug in a crystal and operate anywhere." — WA1PEL

"Reliability. I inadvertently left it on FULL TUNE (key down) position for almost two hours with no bad effects. In fact, I am still using the same finals." — WB4KCO

"Easy to tune and operate. It will cover any 200-kHz band between 3 and 30 MHz. Very good receiver front end. Excellent frequency stability, and rear skirt allows easy interface to other station equipment, such as RTTY." — WA9VYB

"I can always count on this rig to do what it is capable of without fail, without eccentricity or deviation — and do it rather well." — K5OCS

"Excellent engineering, very stable, good filter, and repairable. All parts can be worked on and replaced easily. It is only unfortunate that tube technology is phasing out so fast." — VE7AFJ

"Ability to withstand abuse. I have driven all over the U.S.A., including the desert Southwest, gotten dust and sand in it mobiling, accidentally overloaded it, mistreated it in almost any way you can think of short of dropping it out the window. It never has failed to operate." — WØRKU

"Solid investment — especially with today's stock market." — KA6ACD

"Longevity! This rig (serial #42) was purchased by my dad in 1959. It gave him 20 years' service until his becoming a silent key last year. The KWM-2, now in my possession, has since motivated me into earning my Novice ticket and I'm now struggling toward my General. I plan another 20 years' service from the rig." — KA6IYH

"The use of good components makes this the best unit I have ever owned since my first license in 1937. I'd say it's the best rig ever made for Amateur use." — K4FXP

"Maintaining this rig myself sure beats waiting for new solid state modules to arrive — or for factory servicing." — KH6BZF

## the other side of the coin

Some of the very qualities that make the Collins KWM-2/2A so attractive to so many Amateurs are cited by other Amateurs as the radios' faults. The fact that the KWM-2/2A is solid and dependable also means that it's big and heavy in comparison with more modern, solid-state rigs. The fact that it uses tube circuits, which the Amateur can service himself, often without the help of professional service technicians, also means that those tubes will have to be replaced and the radio may put out a lot of heat. Because the radio was designed over 20 years ago, primarily for SSB use, it is less than ideal for CW: there is no CW filter position, and there is no R.I.T. And, hand in hand with its good resale value and the fact that the Collins name is widely respected, this transceiver is not inexpensive.

The worst feature most commonly cited in the KWM-2/2A was the relays. In earlier models, these relays were open (unsealed) and not of the plug-in variety. Dirty contacts were referred to by many of the respondents to this questionnaire. Several of the owners of the KWM-2/2A who wrote to us had replaced the original relays with plug-ins; in later models, Collins began using sealed relays, which

table 2. Worst features

	percent
relays	27
no CW filter position	16
bad CW rig because of frequency offset	11
heat	11
no R.I.T.	9
200 kHz per segment	8
high cost	7
faulty switches	5
RCA phono plug for antenna	5
no noise blanker	4
no internal supply	3
problems with bandpass switch	3
weight and size	2
microphone	1
delay in getting parts	1
broad signal	1

considerably cut down on the number of these problems. In most instances, a simple cleaning of the relay contacts and regular use are all that's necessary to get the rig working properly again. Another common complaint was that the KWM-2/2A is not a good radio for working CW, because of the frequency offset.

See **table 2** for the percentages. Below are some sample replies to the question, What is the rig's worst feature?

"Does not have a noise blanker built in. It should have a cooling fan for the 6146s (I added one on mine). Transceiver is a bit slow on recovery from transmit to receive. Also, the transceiver has no R.I.T." — WØRJ

"No supplied noise blanker. No CW filter position." — W3PE

"Only 200 kHz tuning capability per switch position (crystal)." — W4FDJ

"No good on CW because of 1.5 kHz shift in transmitted signal." — W3US

"The bandpass. There are no selectable options for the bandpass besides the 2.1-kHz installed. This situation becomes a problem when it is desired to copy 850-Hz shift RTTY signals. The high tone is then eliminated. Other than this, the narrow and steep sided bandpass characteristics are superb." — KH6S

"Requirement for external power supply and very long production lead time for parts." — WD4CWF

"Band switch was corroded and had to be cleaned. Even when it came back from Rockwell-Collins, the switch was corroded and had to be cleaned. Not easy if you have it on a rack." — WA6UZL

"It's no good on CW, and it needs a noise blanker. Only 200 kHz per segment, and it's hardly portable." — K6RK

"Initial high cost and factory cost for repairs." — K5NG

"I don't like being able to tune only 200 kHz at a time. And they use a phono plug connector for the antenna." — WA7ZPQ

"Not solid state. I hope the tubes for this rig do not become obsolete. The open relays in the VOX circuit collect dust. No notch filter or noise eliminator." — W5TTF

"The worst feature is the heat given off by the tubes — and the tubes' having to be replaced." — WB4PVT

"Difficult to troubleshoot and repair, and factory work is very expensive." — WB6ZYE

"There is no designed-in way to get narrower selectivity for CW reception, although Collins did point out that the transceiver was intended only for occasional, not serious, CW." — WØRHW

"Noisy VOX relays." — WB1FYV

"Band switch problems." — WB4NTM

"Weight and size. In the summer, it requires a small fan for cooling during extended periods of use: that is, over 30 minutes." — W2HBC

"RCA phono plug for antenna connection (should be BNC-type)." — K2QDE

"The fact that in this period the relays were not plug-in."

"Power consumption on battery source and lack of CW filter." — N7AA

"Poor CW break-in capability. Not too fast on recovery." — WB2VXY

"Not easily adaptable for mobile use." — WA1PEL

"If judged during its heyday, I can think of none. Now, of course, it lacks some of the little conveniences of the newer rigs: R.I.T., digital readout, power requirements, etc." — K5OCS

"VOX controls mounted inside chassis. Key jack is behind the rig and also covered by the power supply. And this radio is very expensive, even used." — KA6ACD

## problems

The most common problem encountered with this rig was having to replace tubes. Take a look at **table 3** and you'll see that tube failures were by far and away the biggest problem. Several owners reported problems with shorted capacitors; and once more, relay problems show up as a main source of trouble for KWM-2/2A owners.

Nevertheless, the fact remains that most of the KWM-2/2A owners who responded to this survey were happy with their rigs and considered the problems to be minor. Many reported no problems. Here are some of their replies to the question, Have you had any problems?

"PTT relay contacts dirty." — WB6AWU

"Changed telephone-type relays to plug-in type." — K7GEX

"C187 shorted and the unit blew fuses. It required removing the band switch housing and band switch

**table 3. Problems**

	percent
tubes	42
relays	23
shorted capacitor	11
long wait for parts	
also high cost	6
band switch	5
VFO dial	4
VOX circuit	4
alignment	2
difficult to change	
components	2
AGC	1

shaft to replace. I occasionally have to replace tubes." — AH6U

"Just worn tubes." — HI3HEG

"I have a KWM-2 which has been almost fully modified to the "A" version. Occasionally (about once a year) the old wired-in relays give me trouble. I remove the M2 from its case, clean the relays, and it's good for another year. I do have the plug-in relay kit and plan to install it the next time the old relays give me trouble." — W3US

"Tubes and alignment." — WA6UZL

"VOX circuit erratic — had to change many components." — K6RK

"In over 20 years of use, I've replaced a few weak and shorted tubes. Original 6146s lasted nine years. Haven't had to change them since. Replaced one capacitor and one resistor!" — K5NC

"Tubes and heat." — K2OB

"Minor problems easily corrected by replacing a soft tube or tightening a loose screw. The equipment is so well made and logically constructed that it almost repairs itself." — KB9IY

"Mica capacitor in the i-f failed. Loose screw in the power supply shorted B +."

"The usual tube replacements." — K9LKA

"An intermittent receiver problem that has been hard to locate." — WD5CKA

"Had to replace the power transformer after ten years."

"Severe audio feedback when mic button released; corrected by cleaning all relay contacts with emery cloth — a very difficult job because my rig does not have plug-in relays." — WA1PEL

"VFO dial slippage." — WA2CBA

## accessories

**Table 4** shows the accessories purchased for the KWM-2/2A. A noise blanker was the most frequent-

table 4. Accessories	
	percent
noise blanker	13
speech processor	10
amplifier	10
external VFO	8
rejection tuning	8
mike	5
crystal pack	5
Q multiplier	4
digital display	4
dummy load	3
wattmeter	3
antenna tuner	1
transverter	1
SWR bridge	1

ly mentioned item, followed by speech processors and amplifiers. It certainly does seem as though finding the wanted accessories is not much of a problem: 98.7 percent of the respondents who had purchased accessories had been able to find all the accessories they'd wanted. And 97.8 percent were satisfied with the accessories they purchased.

## related findings

The beam antenna is by far the most popular antenna with KWM-2/2A owners, accounting for 55 percent of the tally. Next came wire antennas, with 34 percent, followed by all others, 11 percent. As for license class, there were a large percentage of Advanced-class hams represented, 57 percent, followed by 39 percent for Extras. Technicians, Generals, and Novices made up the remaining 4 percent. More than half of the hams who responded did their own servicing, and the majority of those who shipped the rig out for factory service were satisfied with the service they received. A few complained about a minimum parts order of \$50 and delays in service or delivery.

The following twelve categories were scored from 1 to 10 (with 1 being poorest, 4 to 6 average, and 10 perfect): Ease of Operation, Reliability, Durability, Instruction Book, Factory/Dealer Service, Quality of Workmanship, Performance, Maintenance, Parts Availability, Accessories (ease of connection), Price, and Flexibility. The scores are reported in **fig. 1**.

## would you buy one again?

This is the big question, and for the KWM-2 and KWM-2A the answer was that 73 percent said yes versus 27 percent who said no. That's a very good showing for a radio that was designed and built before the days of integrated circuits and modern "conveniences." Yet the KWM-2/2A continues to hold its own — and remains very popular. Of those who answered that they would not buy this rig again, the most common reason was the price, followed by the lack of modern, solid-state construction or "extras" found only on newer rigs. Not a single respondent faulted the Collins KWM-2/2A for lack of quality or workmanship. These transceivers were built to be solid and dependable — and they still are today.

Next month, *ham radio* will present the results of its survey of owners of the 32S-line transmitter and 75S-line receiver. Watch for it. And don't forget to return the questionnaire on the ICOM 701, Drake TR7, and Kenwood 520 series that appeared on page 22 of the February issue. If you own, or have owned, one of these rigs, now is your chance to tell the world what you think of it.

**ham radio**

# MORE KEYSER FEATURES FOR LESS COST


AEA Invites You to Compare the AEA Keyer Features  
to Other Popular Keyers on the Market.

MM-1



MorseMatic™

KT-1

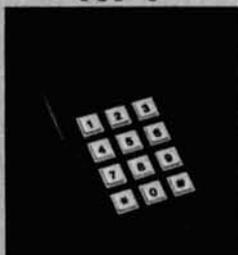

Keyer Trainer

MT-1



Morse Trainer

CK-1



Contest Keyer

MK-1



Morse Keyer

IMPORTANT KEYSER AND/OR TRAINER FEATURES	AEA	AEA	AEA	AEA	AEA	COMPETITOR			
	MM-1	KT-1	MT-1	CK-1	MK-1	A	B	C	D
Speed Range (WPM)	2-99	1-99	1-99	1-99	2-99	8-50	5-50+	?	8-50
Memory Capacity (Total Characters)	500			500		400	100/400	400	
Message Partitioning	Soft			Soft		Hard	Hard	Hard	
Automatic Contest Serial Number	Yes			Yes		No	No	No	
Selectable Dot and Dash Memory	Yes	Yes		Yes	Yes	No	No	No	No
Independent Dot & Dash (Full) Weighting	Yes	Yes	Yes	Yes	Yes	No	No	No	No
Calibrated Speed, 1 WPM Resolution	Yes	Yes	Yes	Yes	Yes	No	No	Yes	No
Calibrated Beacon Mode	Yes			No		No	No	No	
Repeat Message Mode	Yes			No		Yes	Yes	Yes	
Front Panel Variable Monitor Frequency	Yes	Yes	Yes	Yes	Yes	Yes	No	Yes	Yes
Message Resume After Paddle Interrupt	Yes			Yes		No	No	Yes	
Semi-Automatic (Bug) Mode	Yes	Yes		Yes	Yes	No	No	No	No
Real-Time Memory Loading Mode	Yes			Yes		Yes	Yes	No	
Automatic Word Space Memory Load	Yes			Yes		No	No	Yes	
Instant Start From Memory	Yes			Yes		No	No	Yes	
Message Editing	Yes			Yes		No	No	No	
Automatic Stepped Variable Speed	No	No	No	Yes	No	No	No	No	No
2 Presettable Speeds, Instant Recall	No	No	No	Yes	No	No	No	No	No
Automatic Trainer Speed Increase	Yes	Yes	Yes						No
Five Letter or Random Word Length	Yes	Yes	Yes						No
Test Mode With Answers	Yes	Yes	Yes						No
Random Practice Mode	Yes	Yes	Yes						Yes
Standard Letters, Numbers, Punctuation	Yes	Yes	Yes						Yes
All Morse Characters	Yes	Yes	Yes						No
Advertised Price	\$199.95	\$129.95	\$99.95	\$129.95	\$79.95	\$139.95	\$99.50/ \$139.50	\$229.00	\$129.95

## OPTIONS:

MT-1P (portable version of MT-1) with batteries, charger, earphone	\$ 139.95
ME-1 2000 character plug-in memory expansion for MM-1	\$ 59.95
AC-1 600 Ma. 12 Volt wall adaptor for MM-1 with ME-1	\$ 14.95
AC-2 350 Ma. 12 Volt wall adaptor for all AEA keyer and trainer products except MM-1 w/ ME-1	\$ 9.95
DC-1 Cigarette lighter cord for all AEA keyers and trainers except MT-1P	\$ 5.95
MT-1K Factory conversion of MT-1 to KT-1	\$ 40.00

All our keyers (except the MT-1) will operate with any popular single lever or lambic squeeze paddle and will key any type of modern amateur transmitter with no external circuitry required. AEA keyers are as easy to operate as a four function calculator. The internal AEA computers are all pre-programmed for the features shown above. Each AEA product is fully RF protected and receives a complete elevated temperature burn-in and test before it is shipped from the factory.

Ask a friend how he likes his AEA keyer compared to anything else he has ever tried, then JUDGE FOR YOURSELF. See the AEA keyer and trainer family at your favorite dealer.

Advanced Electronic Applications, Inc., P.O. Box 2160,  
Lynnwood, WA 98036. Call 206/775-7373

**AEA** Brings you the  
Breakthrough!

PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT  
NOTICE OR OBLIGATION.

# digital frequency display for single-conversion transceivers

Update your rig  
for numerical  
frequency readout

Digital frequency displays are becoming commonplace in new transceiver designs. Older but still useful rigs lack this refinement. A digital display may be added easily to single-conversion transceivers such as those made by Swan and Atlas. The display described here will enhance operation of these rigs.

Frequency counters are in wide use, and it is quite easy to measure a CW transmitter's frequency. Single sideband is difficult, since a steady tone is required and you must find the carrier by adding or subtracting the tone frequency. Received-signal frequency measurement requires connection to the local oscillator plus mathematical operation on adding or subtracting the intermediate frequency.

## common display methods

Nearly all transceivers use a single master oscillator or VFO for tuning both receive and transmit frequencies. A display can use this variable oscillator output, compensating for the i-f and any other fixed oscillators.

Digital display compensation can be made by heterodyning the VFO pickoff before counting, multiple gating and counting the VFO and fixed transceiver oscillator outputs, or presetting the display counter before a count. The last is the easiest to implement and is easily accomplished with single-conversion transceivers such as the Swan 350, 500C or the Atlas 180, 210, or 215X.

Any of the three methods require some form of bandswitching. Both the Atlas and Swan units add the i-f and VFO on 10, 15, and 20 meters and subtract the i-f and VFO on lower bands. The preset-counter method takes a bit of study.

## preset and complement

Counter ICs such as the 74176 and 74196 can load a specific number into the counter before counting is done. This is *presetting* a state and is the same as addition: final count is the *sum* of the preset value and number of regular count pulses. An equivalent subtraction is possible by borrowing a computer technique called complementing.

When added to a number, a complement will yield a sum value equal to a difference. The highest carry is ignored. Since a count is desired in decimal, subtraction requires the tens complement. The minuend value remains the same; the subtrahend value is replaced by its complement, addition is done, and the resultant value (ignoring the last carry) is the same as the difference.

If you're confused, assume a subtraction that re-

By Everett L. Beall, K6YHK, 715 East Cook Street, Santa Maria, California 93454



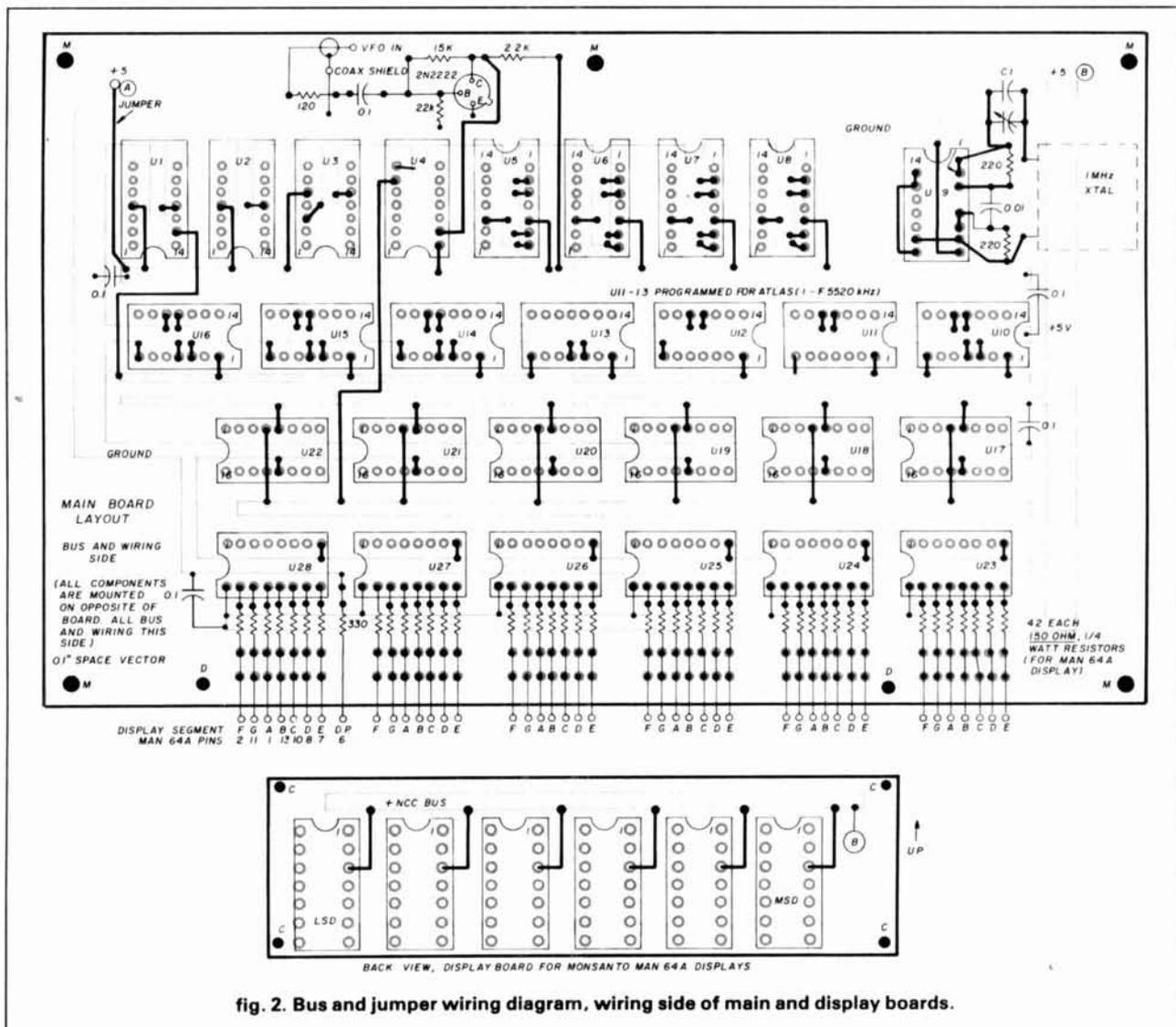



fig. 2. Bus and jumper wiring diagram, wiring side of main and display boards.

stituted. The 74176 consumes less current, and the 35 MHz maximum count frequency is well above any expected frequency.

Counter preset data pin connections are:

decimal preset	11	3	10	4
9	1	0	0	1
8	1	0	0	0
7	0	1	1	1
6	0	1	1	0
5	0	1	0	1
4	0	1	0	0
3	0	0	1	1
2	0	0	1	0
1	0	0	0	1
0	0	0	0	0

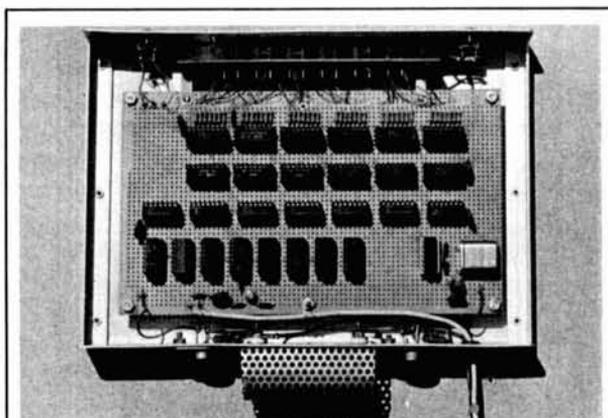A 0 indicates ground, or less than 0.4 volt. A 1 indicates any voltage between 2.4 volts and the 5-volt



Cover removed to show parts placement on perf board. Perforated metal cover on rear is used for protection from the heat of the series-dropping resistor.



which is 9-1/2 inches (24 cm) wide and 6-3/4 inches (17.1 cm) deep, fits nicely on top of an Atlas cabinet. Shown in fig. 4, this homemade enclosure uses aluminum sheet plus angle stock for strength and joining the cover.

Metal spacers and No. 4 screws hold the main board to the bottom section. Since I used 1/2-inch (12.7-mm) spacers, the wire-wrap posts had to be trimmed after wiring to prevent shorts. Height may be increased to eliminate trimming or to include a power supply.

Power regulators and the dropping resistor are

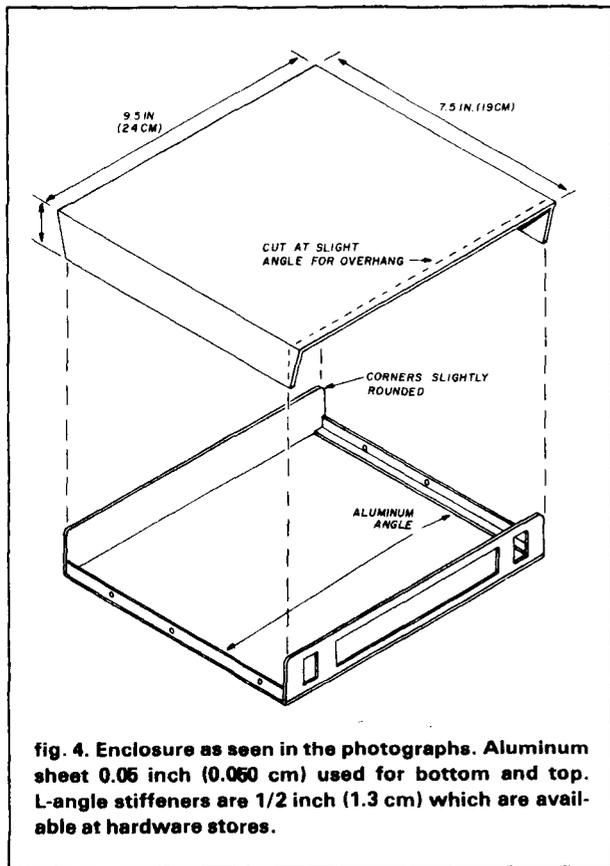


fig. 4. Enclosure as seen in the photographs. Aluminum sheet 0.05 inch (0.050 cm) used for bottom and top. L-angle stiffeners are 1/2 inch (1.3 cm) which are available at hardware stores.

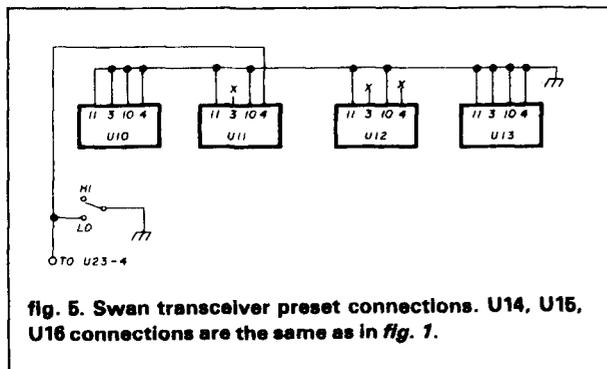


fig. 5. Swan transceiver preset connections. U14, U15, U16 connections are the same as in fig. 1.

mounted on the back surface. The resistor cover prevents possible burns. Wiring from the Atlas is made directly into the display.

### modification for the Swan transceiver

Preset connections must be changed for the Swan's 5500 kHz i-f, and this information is given in fig. 5. Pins 4, 10, 2, and 11 of U14 through U16 remain grounded. External oscillator connection and power-supply arrangements are shown in fig. 6.

The ac-input supply may be used with any transceiver and installed within a larger display cabinet. Only one series regulator is required with the ac supply; LED display power is taken unregulated from the transformer center tap.

A Swan display could use the power supply from either fig. 3 or fig. 6; choice depends on primary power at installation.

### preset options

The tens complement method is limited to single-conversion and certain VFO ranges. Some situations may use the *nines complement* for the MSD preset. The *nines complement* is equal to the *tens complement* minus one. One situation is indicating 12 MHz with a 15-MHz VFO.

The *tens complement* method would display 22000.0 or 2000.0\* with MSD blanked. The added

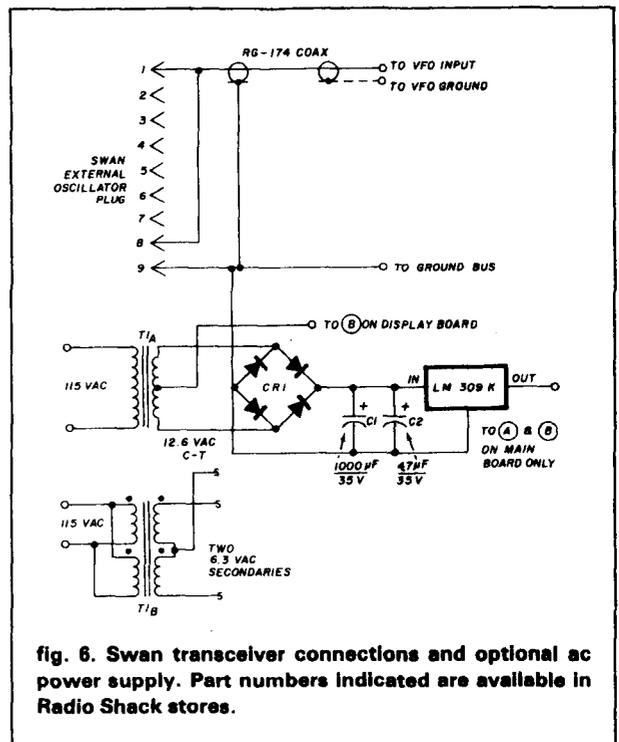


fig. 6. Swan transceiver connections and optional ac power supply. Part numbers indicated are available in Radio Shack stores.

complement would be 07000.0 and obviously wrong. Changing the MSD to nines complement, or 97000.0, would correct this:

load mixed complement	97000.0
add VFO frequency	15000.0
display sum	12000.00 (MSD carry ignored)

Modifications of the preset can be included to correct slight frequency errors in a VFO. Grounding all

presets allows direct frequency measurement subject to the accuracy of the time-base crystal oscillator.

### summary

In this day of synthesizers, built-in digital displays, and other refinements, it's still possible to update good equipment. This isn't a beginner's project, but it can be built by an experienced homebrewer. Options are possible. An added incentive is low cost.

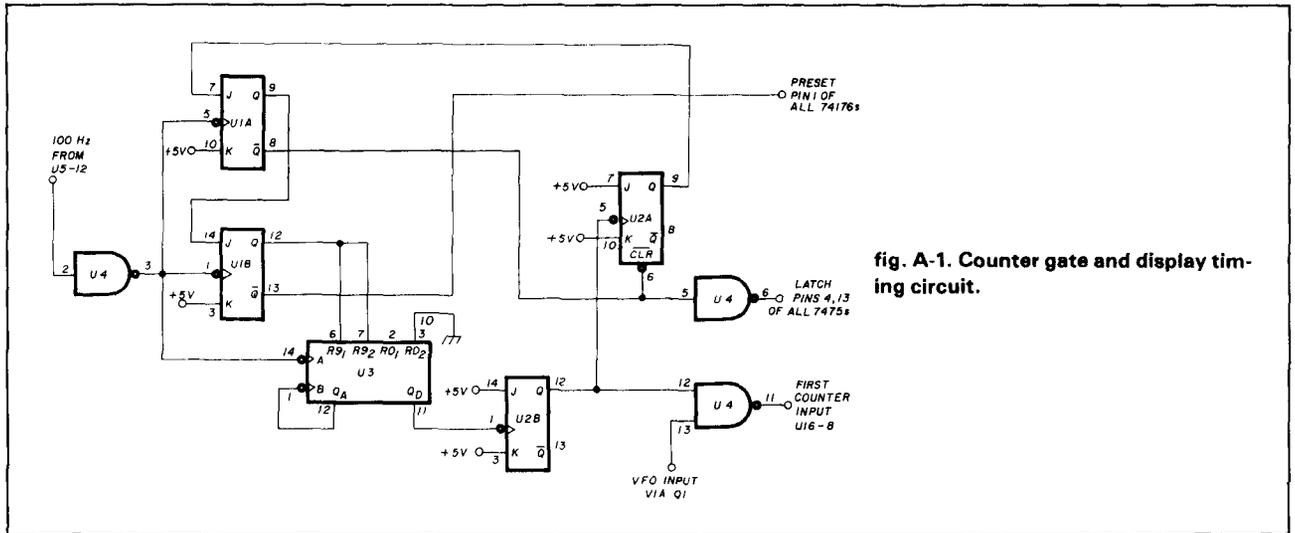


fig. A-1. Counter gate and display timing circuit.

### appendix

This material is included for clarification of the only complex part of the digital display — the count and display control. This circuit has been breadboarded as well as analyzed. It works up to 1 MHz input without trouble.

The digital display operation depends heavily on proper operation of U1 through U4 (fig. A-1). Operation of this circuit is detailed as an aid to trouble-shooting and to illustrate variations in digital circuit designs. This section controls the counting gate, latch, and preset sequencing automatically.

The timing diagram begins with decade counter U3 in a decimal 9 state. U2-12 is low, inhibiting the U4 VFO count gate and holding the counter chain and display idle. The first negative edge from U4-3 will toggle U3 from 9 to zero. U3-11 will go low and toggle U2-12 high; counting begins.

After ten negative edges of U4-3, or 100 milliseconds, U3-11 will go low again. U2-12 will toggle low, inhibiting the VFO gate and toggling U2-9 high. Both U1-9 and U1-12 have remained low due to the low J input at U1-7 from U2-9; both sections of flip-flop U1 are connected as a shift register.

The next negative edge from U4-3 will toggle the first stage of U3 high and toggle U1-9 high, U1-8 low. U1-12 is ready to toggle on the next clock pulse from U3-4, but more significantly, U2-9 is cleared low by the low state of U1-8 into the direct-clear input, U2-6. The LATCH bus goes high through the inverter connection of U4-5,6 and all of the 7475 latches store the full counter state.

The following negative edge from U4-3 will toggle U1-12 high and force U3 into a decimal 9 state through the R9 control pins. The 7490 used for U3 will be held in the decimal 9 state until pins 6 and 7 go low. The first stage of U3 will toggle low and remain for 15 to 20 ns until forced high; flip-flop delays account for the negative spike.

If U1-12 is high, then U1-13 will be low and counter PRESET is

enabled. Counters assume the preset connections, but the latches hold the previous count due to U4-6 dropping to a low state. U1-9 is now low and sets up U1-14 J input for the next clock edge.

The last clock will toggle U1-12 low and remove the forced 9 state of U3. U3 does not toggle, since the forced condition will have been still present at the clock edge arrival time. U3 remains in a 9 state, and all flip-flop Q outputs are low. The counter and display are idle.

The cycle will start again on the next clock edge. Display update occurs every 140 milliseconds, about seven per second.

Take care not to confuse pins 8 or 9; 12 or 13 of both flip-flop packages. An improper connection will cause a short cycle and false display; possibly no display at all.

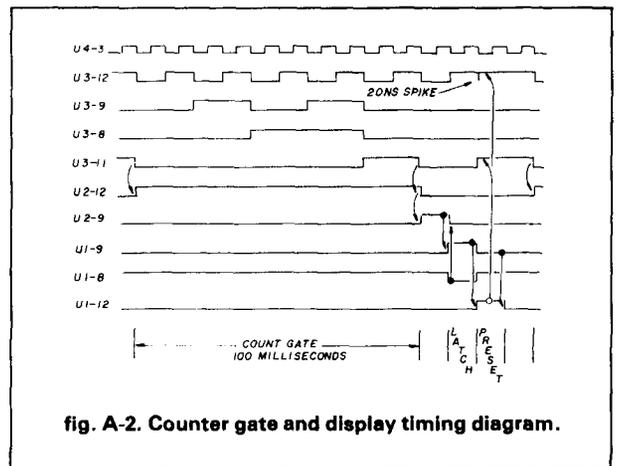


fig. A-2. Counter gate and display timing diagram.

# ham radio TECHNIQUES

Bill Over  
W6SAI

## more about moonbounce

My last column was an introduction to "moonbounce" (earth-moon-earth) communications — the past history of it and the way Radio Amateurs use this exciting means of communicating. One important point I stressed is that EME is totally unlike the more common modes of communications in that the parameters required for moonbounce work are well known and the beginning moonbounce enthusiast can make the larger, more well-equipped stations work for him, thus taking a portion of the communications burden off his back!



The Amateur bands between 6 meters and 1296 MHz have been used for moonbounce work. The most popular bands for this up-and-coming mode are 144 MHz and 432 MHz. There seems to be more activity on the 2-meter band, and the station requirements for this band are well established. This column limits discussion to 144 MHz moonbounce operation.

A representative EME path is shown in fig. 1. If two operators can see the moon at the same time, the path is available for contact. For general operation, EME operators aim for a "window in the sky" called the *universal window*, an area in the sky in

the path of the moon through which most operators can see the moon. Most moonbounce activity occurs when the moon traverses the window.

The round-trip antenna gain required under ideal conditions on 144 MHz is very close to 41 dB. This means that a moonbounce operator having an antenna with a power gain of 21 dB over a dipole should be able to hear his own moon echos and should hear other moonbounce stations having 21 dB of antenna gain, or more.

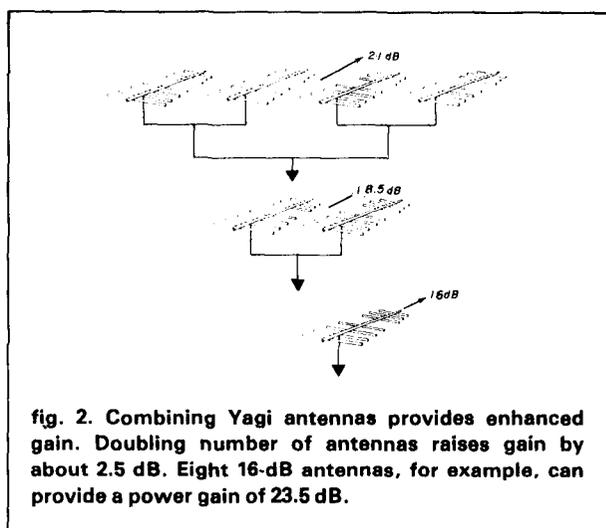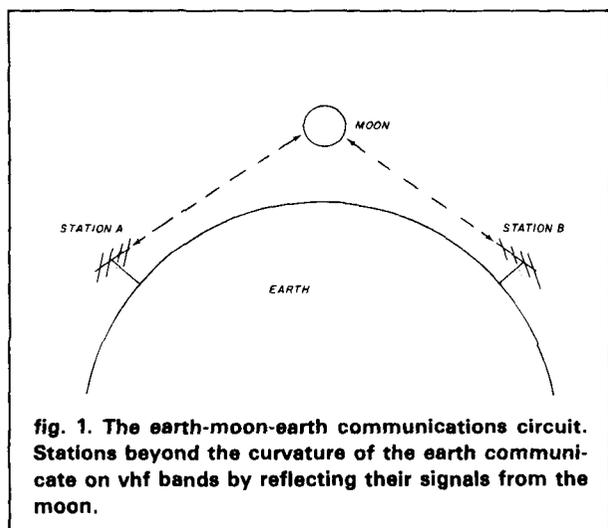Since the round-trip gain is supposedly constant, stations having an antenna gain less than 21 dB can't hear their own echos but can hear other



stations having more than 21 dB of antenna gain. A station having an 18-dB gain antenna, for instance, should be able to hear and work moonbounce stations having an antenna gain of 24 dB. Exceptions to this rule make moonbounce very exciting.

Several commercially available 2-meter Yagi beams have a claimed signal gain of over 16 dB. Taking this as par, then, how does the beginning moonbouncer build up a practical EME array? Well, the 16-dB antenna can hear other moonbouncers having an antenna gain of 24 dB. Enough moonbouncers have arrays of this size to make a 16-dB antenna marginally acceptable for a moonbounce contact. The biggest moonbounce arrays that I know of in everyday use run about 26 dB over a dipole. Once in a while hams in research establishments obtain permission to put a "big dish" (parabolic) antenna on the air for moonbounce work. And that provides a moon-reflected signal that will knock your ear off!

## how to achieve moonbounce antenna capability

How big must the moonbounce array be to provide practical EME work? A 16-dB antenna will permit contact with a few stations. If two 16-dB antennas are combined properly to form a larger array, the overall gain will be increased by about 2.5 dB. If four arrays are combined, the gain will go up another 2.5 dB. Two arrays, then, provide 18.5 dB and four provide 21 dB. Suitable antenna combinations are shown in **fig. 2**.

Many moonbouncers settle for four arrays as this configuration is not too bulky and the feed system is not complicated. Some of the ardent DXers use as many as 24 antennas in a four-by-six arrangement — yet many enthusiasts use only one or two arrays.

Some of the factors to be considered when building a moonbounce array are as follows.

**Distance to the moon.** The dis-

tance to the moon varies because the moon's orbit is an ellipse. At *perigee* (the closest point) the moon is about 221,400 miles (354,240 km) from the earth and at *apogee* (the farthest point) the moon is 252,700 miles (404,320 km) away. The path difference is about equal to 2 dB, so it pays big dividends to use the moon when it is closest to the earth.

**Sky noise.** This phenomenon refers to background noise that may limit reception. There are a lot of radio noise sources in space. The sun, for example, is a prolific radio-noise generator. Certain stars are radio-noise sources, too. A noisy star in line with the moon can override weak moonbounce signals. Wise moonbounce operators operate when the moon is in a quiet portion of the sky to reduce competition from unwanted noise.

**Faraday rotation.** A puzzlement to early EME experimenters was the mysterious loss of signal caused by polarization rotation of the signal as it passed through the earth's atmosphere. Many simple moonbounce antennas are fixed as far as polarization goes, and the operators must patiently wait until polarization aligns itself with their antennas before contact can be established.

In addition, atmospheric effects can blur the signal (*scintillation*) and the rough surface of the moon causes *libration fading*. All of this means that sometimes moonbounce communication is almost impossible, and at other times signal strength is so great it cannot be explained.

But to plan a moonbounce station, a certain set of normal conditions must be taken, and the overall situation is not as gloomy as it might sound. To begin with, a single 16-dBd Yagi antenna will suffice if the beginner wishes to listen for some of the more well-equipped EME stations. Two 16-dBd Yagis will provide improved capability and allow two-way communication with the better moonbounce stations. Four Yagis will provide good EME capability. And from this point, the moon's the limit!

## moonbounce station equipment

Before leaving the discussion of the antenna it should be pointed out that *feedline loss* plays an important part in EME work, and it should be held to as low a value as possible. The length of the line should be short and the antenna mounted near the equipment. Contrary to what is required for ionospheric-reflected DX work, height is not important for EME work as long as the antenna can clearly "see" the moon. Many moonbouncers place their antenna right outside the operating room. In some cases a good grade of RG-213/U or RG-8B/U cable is used, or else the larger, more expensive RG-17/U cable. The better-equipped stations use air-dielectric coaxial line for minimum loss.


Some deluxe moonbounce stations locate the receiver preamplifier and transmitter power amplifier directly at the antenna to eliminate feedline loss. I don't recommend the beginner attempt this, but it illustrates the attention to detail that makes a successful moonbounce station.

Progressing down the feedline, the *antenna relay* is a critical item. The relay must provide adequate isolation of the receiver during periods of transmission. The very sensitive devices used in EME preamplifiers cannot stand seepage of rf from the transmitter around the relay contacts. Many moonbouncers use two separate antenna relays, one to switch the feedline and the second to ground the input terminals of the receiver preamplifier for protection.

Next item to consider is the station receiver. A good, *low-noise preamplifier* is required. The *receiver* may consist of an hf receiver with a 2-meter converter in front of it. The receiver should be equipped with a *narrow-band filter* such as used for CW reception. This will provide the best signal-to-noise ratio and enhance the operator's ability to hear weak signals. A passband of about 500 Hz is a good compromise.

Finally, the transmitter must be considered. While moonbounce contacts have been made on rare occasions by stations using as little as 200 watts output, a practical moonbounce station calls for 1 kW input, with about 700 watts going into the antenna system. Maximum power, of course, provides the greatest margin for success.

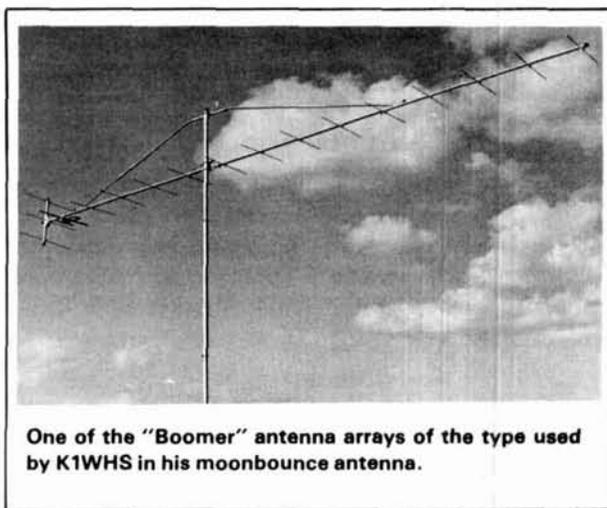In addition to the transmitting and receiving equipment, the practical EME station requires an accurate clock. A tape recorder is very handy for recording received signals. And



One of the "Boomer" antenna arrays of the type used by K1WHS in his moonbounce antenna.

*Sams & Co.* and available at many Amateur Radio distributors and from Ham Radio's Bookstore, Greenville, NH 03048 (\$4.95 plus \$1.00 shipping).

### a day in the life of a moonbouncer — K1WHS

(This is the story of Dave Olean, K1WHS, an active moonbouncer. Dave uses an array of twenty-four large Yagis to provide a power gain of over 26 dBi on 2 meters. This is an actual account of Moonbounce DX using this super-big antenna).

finally, if the moonbounce antenna is steerable, the operator requires alignment information to aid in finding and tracking the moon.

With a tracking antenna and lunar orbital information, the moonbounce operator is able to plan his operation into the future and arrange schedules with other enthusiasts. The *Nautical Almanac* provides lunar information in terms of the *Greenwich Hour Angle* (GHA) and, unless the operator lives in Greenwich, England, he requires a second publication which converts this information into usable data. And, finally, the longitude and latitude of the station must be known.

A helpful handbook which discusses all of this information in detail is *VHF Radio Propagation*, by J.D. Stewart, WA4MVI (book number 21575) published by *Howard W.*

The alarm clock sounds like Big Ben. I awake with a start in the blackness and fumble around to silence the noisemaker. Ah, yes. Tonight is the Universal Window. Saturday morning, 2 A.M. on the east coast. A lot of Europeans will be on 2 meters looking for moonbounce contacts.

Up and at 'em. Wringing the sleep from my eyes, I head toward the shack. I flip on the lamp, view my schedule list and check the clock. The big antenna array of twenty-four Yagis rotates around to intercept the moon at the touch of the controls. The equipment has been running and warm all night in anticipation of this moment.

With a yawn I slip on the ear-phones, key the 2-meter transmitter, and adjust the drive level for 100 watts output. The SWR on the transmission looks good. All seems to be

in order. I send a few dots and switch to receive. Yes! I am greeted by a nice moon-reflected echo of my signals that have just made the 450,000 mile (720,000 km) round trip.

The moon is at perigee, or the closest point to the earth. I know this can make a big difference when a small, marginal moonbounce antenna is being used on one end of the EME circuit. Path loss can increase by 2 dB between perigee and apogee, and this can spell success or failure with a marginal antenna.

All right. I scan the 2-meter band between 144.000 and 144.015 MHz and hear a few signals. They are coming back at me from the moon. WA1JXN/7 is calling CQ on 144.007 MHz. Lance is about two and one-half S units above the background noise and very steady. Good copy. That's a good sign!

Some days the lunar-reflected signals are very "watery" and subject to severe, rapid fading. Such conditions tend to frustrate avid moonbouncers. Stations with small antennas may have a hard time making any contacts at all during a period of disturbed conditions. Not so this evening. Tonight the band sounds perfect! Even the galactic background noise is cooperating. Very little excess noise means signals will be strong and clear.

By this time my first schedule with DL8GP in Germany is about to begin. I tune the receiver to 144.030 MHz and zero-beat my transmitter frequency as close as possible. Wow! I'm hearing his signal!

"K1WHS DE DL8GP...K1WHS DE DL8GP..." He's there. Over and over I hear the two calls, clearly. After two minutes he signs over to listen for me. I transmit calls back for a minute and a half, then in the last 30 seconds I send the letter O several times, to signify that full call sets have been received. That's moonbounce shorthand many stations use.

I stand by and DL8GP answers with more moonbounce shorthand: "R-O-R-O" meaning OK, call sets received. Another moonbounce DX

schedule logged. His signals have been quite steady the whole time. I let him go to work other moonbounce stations looking for a European contact.

The moon at this point is about one hour away from setting in central Europe. I touch up the antenna rotors to peak the array on the moon. A beamwidth of less than 6 degrees means a lot of antenna tweaking to stay on the moon. I generally update my headings every six or eight minutes.

What else is going on? I think 144.004 is clear for a CQ. I am "looking" toward the east and, by convention, should transmit during the even two-minute periods of the hour. As I reach for the key, VE7BQH and WBØQMN both come on calling CQ, about a kilohertz apart. Both signals are of unbelievable strength, considering they are coming at me from the moon. It is hard for a moonbouncer to comprehend the signal levels as received on such a large antenna array. Both Tom and Lionel are S6 on peaks, the receiver meter bouncing with a little libration fading. I quickly drop the idea of sending a CQ and decide to call WBØQMN. To my surprise he doesn't come back! This occurrence, I say to myself, is a perfect example of the K1WHS moonbounce theorem: Namely, that if a signal is loud enough to roll your socks up and down on 2-meter moonbounce, the operator will not even detect your signal! Sort of a vhf version of Murphy's Law.

Back to the idea of a CQ. I move up the band a few kHz and send a short call. Wow! A pileup calling me! This is difficult, as all signals are zero-beat and all about the same strength! Sort of like 20 meters, I say to myself. Through the din I can make out...I4 (Italy) and W...DU. The other calls are lost. After two minutes, I've just been able to pull out one complete call...here it is: HB9QQ (Switzerland)!

I'm really surprised, as the Swiss station is a new one I've never heard before. I've tried schedules with him

off and on since 1976 with no luck, and now here he is, big as life! The big, 24-Yagi array does the job, and I pick him out of a moonbounce pile-up on a CQ. Times do change on vhf! Pierre is running about 339. A good signal. He gives me 539 and we sign off.

Time for another CQ? No, sked-time with G4IDR in England is coming up. This will be a tough one as he's only running a single long Yagi and 400 watts. He can only aim at his horizon since his Yagi is used mainly for tropospheric and meteor scatter work. But now his setting moon is in line with his antenna and the prearranged sked time is upon us.

Watching the sweep second hand on my clock, I begin my calling sequence and pause between characters to listen to my own echo. It is very strong. Now, I listen for Dave, G4IDR. Nothing. I wait for two minutes and start calling again. Half-way through my calling period I detect a signal during the keying sequence. It is very, very weak and sounds like background flutter.

The signal builds up slightly. I hold my breath and close my eyes...an old trick which seems to concentrate hearing comprehension. Parts of a call come through "...1WH...4...DR."

In my next calling sequence I start sending the letter M in the last 30 seconds. This told Dave I was getting parts of his call. Now, I again listen and Dave's moonbounce signal picks up a bit to allow a few sets of calls to sneak through, then a slow, gradual slide into the background noise begins. Faraday rotation has struck again!

From experience I know it will be at least ten or fifteen minutes before I hear him again. I send a batch of Os to G4IDR, telling him I have received the call sets. Moonset in Europe for G4IDR is 0812, and at 0800 I start to hear him again after a 40-minute lapse. Excitement builds as I strain to hear him. I figuratively crawl down the earphone cord. He is building up, now...at 0804 he is much stronger, in

fact, now moving the S meter! The whole 2-minute sequence is nearly Q5 copy.

I acknowledge his transmission with enthusiasm, stopping at 0810 as I know he's lost my signals.

Suddenly, the telephone rings and I jump involuntarily. None other than Dave, G4IDR, is on the line from England! He's so excited he can hardly talk. He was running 400 watts output into a single, 19 element Boomer Yagi. But the surprise was that he had removed the front six feet of the boom and the associated elements so that he could turn the antenna in his small yard. He had a 3-dB loss in his feedline, moreover, giving him only 200 watts into a "lobotomized" Yagi beam! I exchanged excited words with him, set up a new sked, then turned back to the receiver for more listening.

The moon has set in Europe, so I switch my calling period from even 2 minutes to the odd ones and call CQ. There's WBØQMN coming back, weak but readable. I answer Tom and give him a 339 report. No reply. Where did he go? Another call. No reply.

As I start to call again, the phone rings for the second time. It is Tom, WBØQMN.

"Do you know what you just heard?", he asks. "I was running my 10-watt exciter into my moonbounce array! Ten watts! I nearly fell out of my chair when you came back. I decided you must be working someone else and that my ears tricked me. So I didn't reply. Then when you called again..."

"Surely the QRP DX report of the century," I replied. "No way to top that one."

The moonbounce DX session was over by now. The moon "window" was closed. I flipped off all the control switches and headed up the stairs for a quick wink of sleep before I had to go to work. Not a bad "DX window" for 2-meter moonbounce work. Too bad I didn't get the Italian station. Maybe next time...

**ham radio**

# genesis of a synthesizer

## Design and construction of a low-cost 2-meter synthesizer

Several years ago, after purchasing an inexpensive 2-meter rig for the car, I realized that crystals for this new toy were rather expensive. If I loaded up all 23 channels I would have more invested in quartz than in the rig! Clearly, a synthesizer was needed, and so the search for ideas began.

A search of the literature revealed that most designs used TTL, consumed lots of power, used two (or three) crystals in a mixing scheme, and could be improved upon with a dash of newer technology.

Next, some design objectives were laid down. These were the following:

1. Coverage of the entire 2-meter band in 5-kHz increments
2. Adequate output drive at 12 MHz (transmit) and 45 MHz (receive)
3. Switch-selectable offsets of +600 kHz, -600 kHz, or simplex operation
4. Low power consumption (less than 250 mA)
5. Good temperature stability, small physical size, and low cost (less than \$100)

Happily, these objectives have been met, and the result is what follows.

### system design

Referring to fig. 1, the system block diagram, we see that the reference frequency for the phase detector is derived from a very stable 6.82666-MHz crystal oscillator. This signal is divided by 4096 to provide the 1.666-kHz reference frequency. The phase detec-

tor output is smoothed to dc by the loop filter and controls the VCO frequency. This frequency is divided by 2 before being applied to a divide-by-N counter. N is determined by the settings of the thumbwheel switches and the choice of offset.

The divide-by-N counter output supplies the second input to the phase detector, closing the feedback loop. The receive and transmit outputs are the VCO frequency and the VCO frequency divided by four respectively. This scheme was the simplest I could devise consistent with my needs. Now, let's fill in the blocks.

### how it plays

Refer to the schematic, fig. 2. It was suggested to me that, for best frequency stability, the reference oscillator should be in the 5-10 MHz range. For this reason, the crystal is a 6.82666-MHz unit, cut for 30-pF load capacitance. U1, a CD4060B containing the oscillator circuit and an on-chip divide-by-4096 counter, provides the 1.666-kHz reference. (Note the heavy temperature compensation.) Also, the load capacitance can be adjusted slightly to offset the crystal frequency for +5 kHz channel spacing. Zener regulation provides excellent stability over an 11-15 volt supply range.

The desire for low-power consumption made the MC14046 (or RCA CD4046) a logical choice for the phase detector. The loop filter was adapted from the design of DJ2LR<sup>1</sup> and was designed to provide a worst-case settling time of about 50 ms. The output of the loop filter controls the frequency of an MC1648 VCO, tuned by an MV104 varactor. A 2N2369, Q1, converts the VCO output (an ECL square wave) into a TTL-compatible signal to drive the output buffer and divide-by-four circuits.

This signal is divided by two by U14, an SN74S74

By Ken Grant, VE3FIT, 46 Merryfield Drive, Scarborough, Ontario, Canada M1P 1J9


flip-flop. The flip-flop output is then level-translated to clock U15, an MC12013 dual-modulus prescaler. U3-U8, and U15, form the divide-by-N counter. Note that, since the MC12013 output is at  $\approx 2.5$  MHz, subsequent stages can be relatively low-speed CMOS devices. The divide-by-N arrangement divides the VCO signal down to 1.666 kHz for the phase detector. It's based on the scheme used by K4VB and WA4GJT.<sup>2</sup>

The divide-by-N counter is programmed in two ways: first, according to whether you're in transmit or receive mode (Q4 and associated circuit); second, by U9-U12 in conjunction with the thumbwheel switches and the transmit offset selection toggle switch, S2. U9-U12 form a two-decade BCD adder/subtractor capable of adding 0.6 MHz (600 kHz), or zero MHz, or subtracting 0.6 MHz from the thumbwheel switch settings.

Finally the 12- and 45-MHz signals are gated and buffered by U16 to provide low-impedance output drive. (Gating the output signals on or off helps to reduce overall current consumption.) A LM340T-5 provides regulated +5 volts for all the non-CMOS logic.
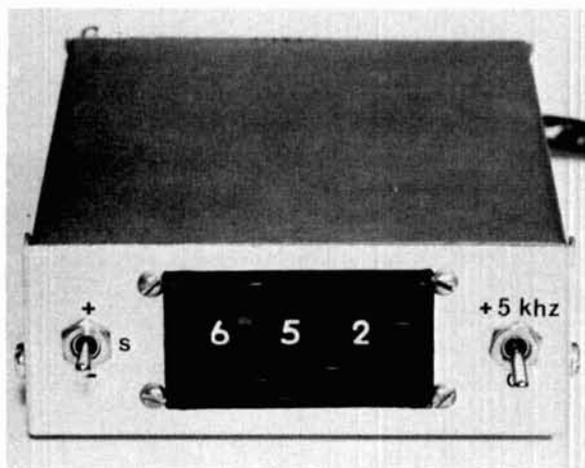
### construction

As you can see from the photos, the unit is very compact. All the CMOS circuits are mounted on a piece of Veroboard measuring 3.25 by 3.25 inches (8.3 by 8.3 cm) and are supported by four 0.25-inch (6.5-mm) standoffs. The remaining circuitry is on a double-sided PC board measuring 2-7/8 by 2-7/8 inches (73 by 73 mm). A resist pen was used to make the circuit trails.



Completed synthesizer. Unit is a compact 4 by 5 by 1.5 inches (10 by 13 by 3.8 cm).

The circuit paths are etched on the top of the PC board, and the bottom is left unetched for a ground and to shield the more sensitive circuit from any CMOS switching garbage.

Be sure to remove a small area of copper (using a small drill bit or deburring tool) from the area around the holes where any ungrounded components protrude. In addition, I fashioned a piece of thin copper into a VCO shield. Be sure that it's grounded! The general circuit board layouts are shown in fig. 3.

Feedthrough caps (500 pF) filter any rf from the PTT and +12-volt lines, while the transmit and receive outputs are taken from a pair of phono sock-

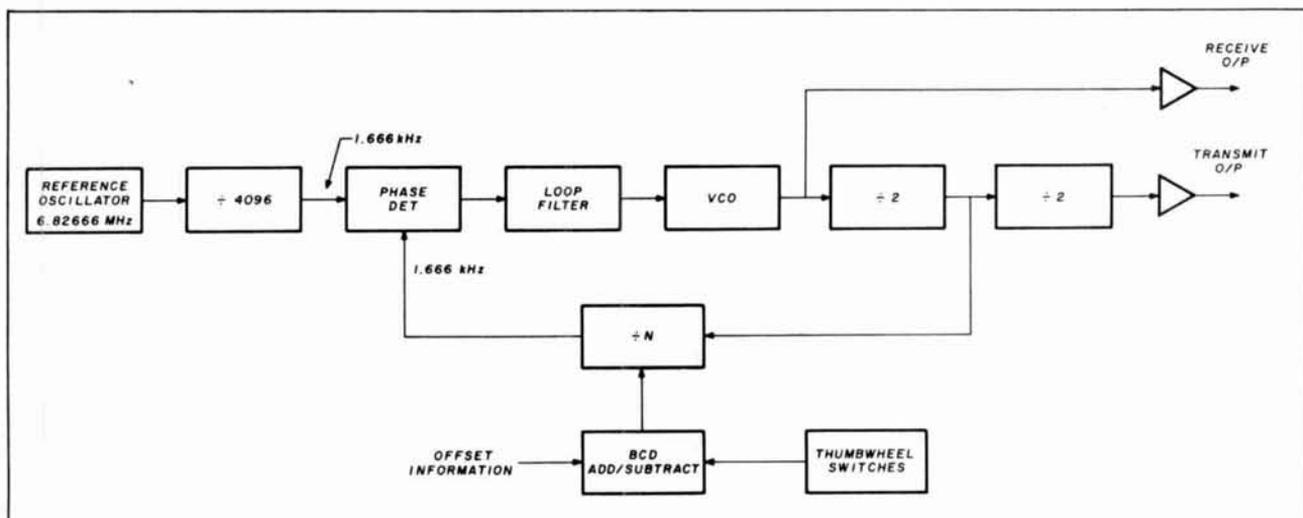


fig. 1. Synthesizer block diagram. "N" is determined by thumbwheel switch settings and the choice of frequency offset. The entire 2-meter band is covered in 5-kHz increments.


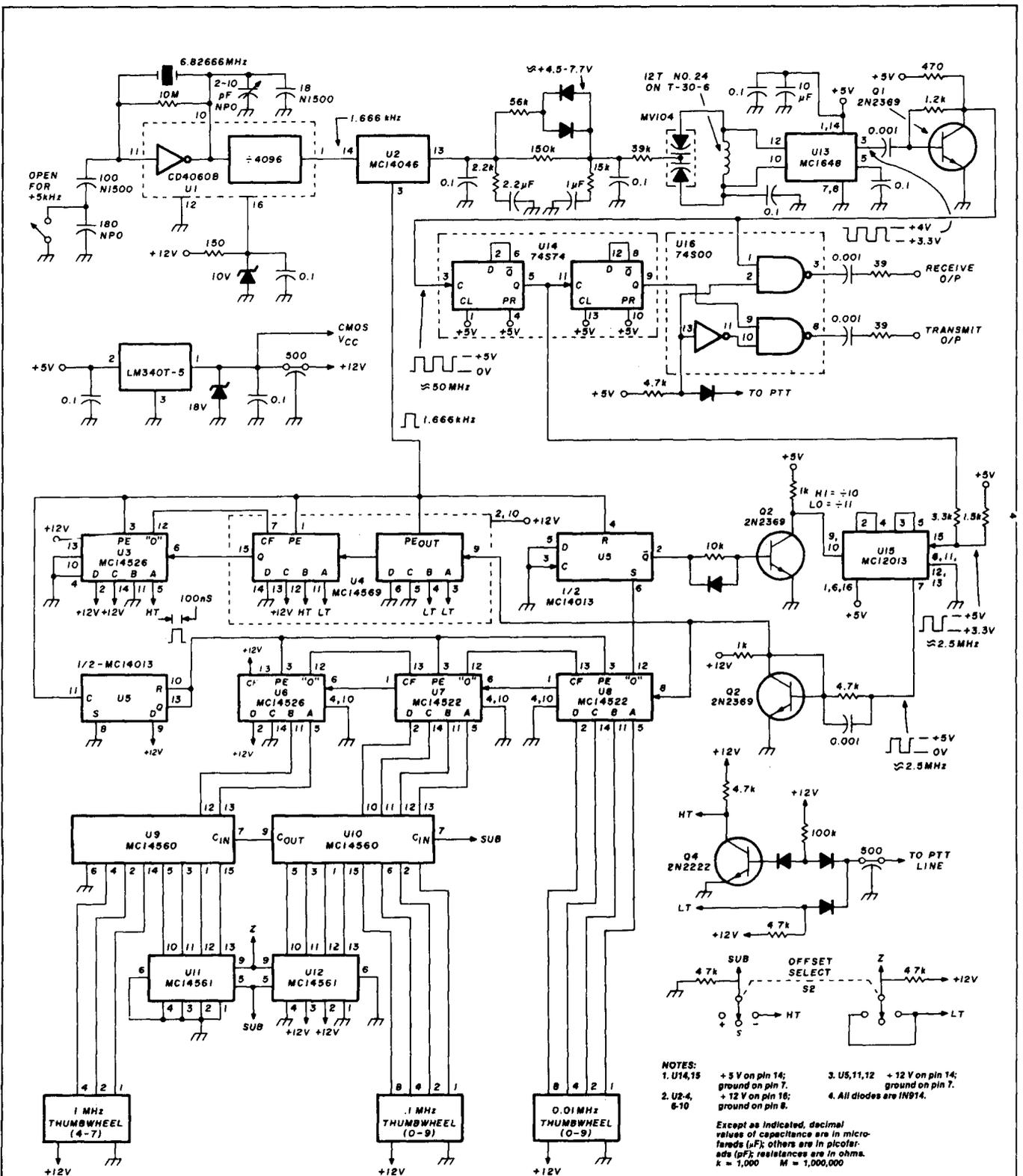


fig. 2. Schematic diagram of the 2-meter synthesizer. Reference oscillator operates in the range 5-10 MHz for best stability. Crystal is cut for 30-pF load capacitance.


FRONT

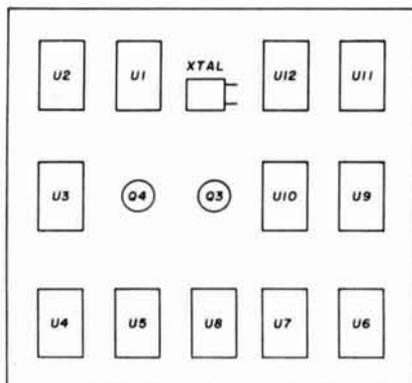

(NOT TO SCALE)

BOTTOM (PERF) BOARD


A

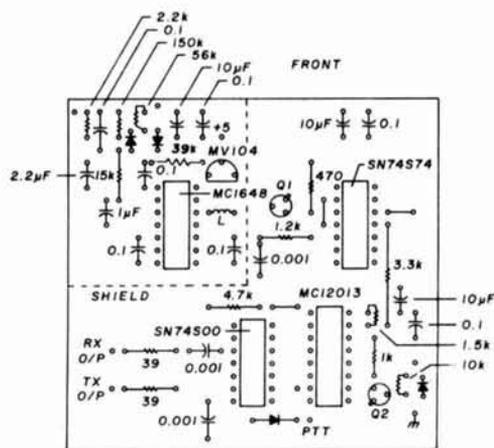

COMPONENT PLACEMENT (PC BOARD)

B


FRONT

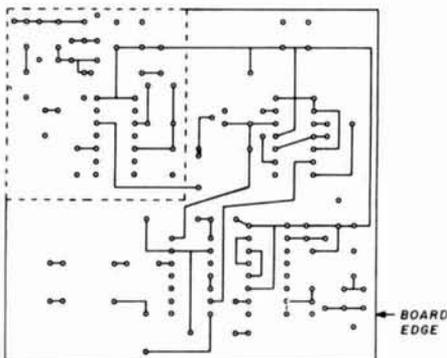

DRILLING AND ETCHING GUIDE  
(PC BOARD)

C

fig. 3. Circuit-board layout. All CMOS devices are mounted on a piece of Veroboard (A). (The American equivalent is Vectorboard No. 3682-4.) Interconnections on this board are made using No. 30 (0.25-mm) insulated wire on the underside. The PC board, (B) and (C), is double-sided copperclad. The bottom is left unetched to serve as a ground plane and shield. Circuit trails, made with a resist pen, are on top.

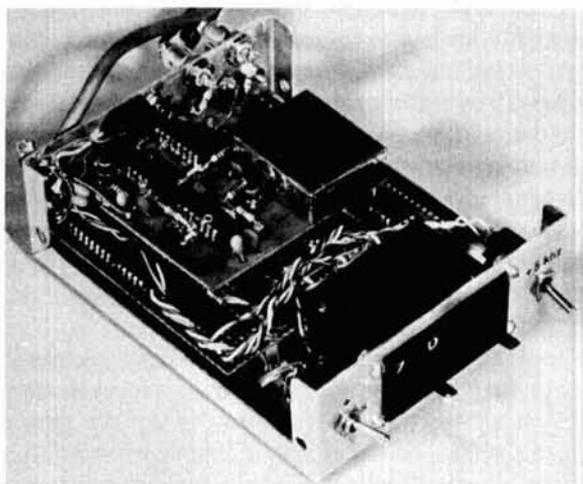

Inside the 2-meter synthesizer. All CMOS circuits are mounted on a piece of Veroboard and are supported by four standoffs. Remaining circuitry is on a double-sided PC board.

ets. The 5-volt regulator is bolted to the rear of the case for good heat dissipation.

### checkout and alignment

After all of your wiring is done, I suggest checking all the interconnections with an ohmmeter. This doesn't really take too long and often saves a lot of time later on.

Once you're satisfied that all is in order, set the thumbwheels and toggle switches for 144-MHz simplex. Ground the PTT line and apply power. If all is well, you should be drawing about 200 mA and there should be a 12-MHz waveform at the transmit output. Lifting the PTT line from ground should cause a 44.433-MHz signal to appear at the receive output.

If all isn't well, start a check with your oscilloscope probe, starting at the reference oscillator and working your way around the loop. Finally, use a frequency counter to adjust the crystal oscillator right onto frequency. Check for proper operation of the transmit offsets (remember that the thumbwheel switches show the received frequency). Opening the +5 kHz toggle switch should shift both receive and transmit outputs by the equivalent of 5 kHz at 144 MHz.


### installation

Only five connections are required between the synthesizer and your rig. These are: +12V, ground, PTT line, and receive and transmit inputs. The latter two should be coaxial cable. Try to terminate both coax lines with somewhere between 50 and 100 ohms. K9LHA provides excellent interfacing suggestions in his article.<sup>3</sup>

A common occurrence in outboard synthesizer installations is one of vhf rf coming back into the synthesizer through the two interconnecting coax lines. My setup was such a case, and the results were very evident — nobody could understand a thing I said for all of the squealing and hum! The cure was to install a pair of in-line lowpass filters, thus stopping the vhf rf before it can get inside the synthesizer. Circuit details are given in **fig. 4**.

## results

After the rf feedback problem was licked, I enlisted the help of several local Amateurs in evaluating the synthesizer. All reported that the signal was spot-on frequency. The audio on transmit is as good using the synthesizer as when using crystal control. Received signals are also of similar quality. Measured frequency drift was  $\pm 50$  Hz at the 12-MHz output between the ambient temperatures provided by a deep freeze and a mildly hot oven. Best of all, the project came in within the budgeted price, thanks partially to some keen scrounging.

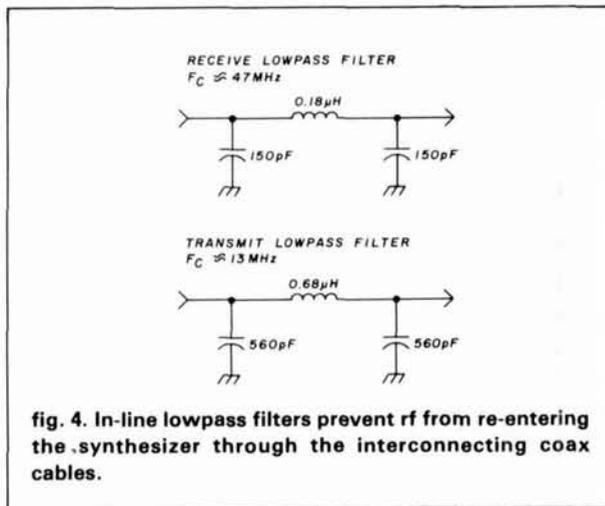

**fig. 4.** In-line lowpass filters prevent rf from re-entering the synthesizer through the interconnecting coax cables.

## acknowledgments

I'd like to thank the authors mentioned previously for the ideas suggested in their articles. Also thanks to my friend Mike Blake, VE3HFP, for his comments and suggestions (and for having the patience to put up with me).

## references

1. Ulrich Rohde, DJ2LR, "Modern Design of Frequency Synthesizers," *ham radio*, July, 1976.
2. B. Fanning, K4VB, and G. Grantland, WA4GJT, "800-Channel 2-Meter Synthesizer," *ham radio*, January, 1979.
3. Tom Cornell, K9LHA, "C-MOS 2-Meter Synthesizer," *ham radio*, December, 1979.

ham radio



## Kitty says We Will Not Be Under- sold On Hand-Held Radios!



The outstanding Yaesu FT-707, FT-902 DM, FT-107 M or the FT-101ZD

FT 720 RVH, 25 watts, 2 meter transceiver. FT 720 RU, UHF transceiver. FT 480, 2 meter, all mode, 30 watts.

### MARCH FEATURES COLLINS KWM 380

and accessories for all major lines  
 ASTRO 103 • BIRD WATTMETERS  
 MIRAGE 2M amplifiers • MURCH UT 2000B

It's Barry's for the Drake TR/DR-7 and R-7  
 CW Ops — we've got NYE keys, Vibroplex  
 and Bencher paddles  
 ICOM 720 All-Band HF

### AND THERE'S MUCH MORE!

Bearcat Scanners, HyGain Antennas 2 m  
 beams & mobile, 18AVT/WB and Rotators

### BARRY'S HAS HAND-HELDS NEW Yaesu FT-404 R (UHF)

Yaesu FT-207R Icom IC-2AT  
 Santec HT-1200

### BARRY'S HAS TUBES - 3-500Z, 572B, 6146's and more

BARRY now carries the ALPHA 76CA  
 with three 8874 tubes, 2,000W PEP  
 and hypersil® transformer

Daiwa/Miller tuners, wattmeters and coax  
 switches • Complete selection of radio books

#### Our lines include:

AEA	CUSHCRAFT	KLM	TEMPO
ALLIANCE	DENTRON	KANTRONICS	TRI-EX
ASTRON	DRAKE	MFJ	VHF ENGINEERING
AVANTI	ETO	MIRAGE	WACOM
B & W	EIMAC	MURCH	YAESU
BIRD	ENCOMM	ROBOT	AND MORE...
COLLINS	HUSTLER	SHURE	
COMMUNICATIONS	HY-GAIN	STANDARD	
SPECIALISTS	ICOM	SWAN/CUBIC	

**BUSINESSMEN:** Ask about BARRY'S line  
 of business-band equipment. We've got it!

#### Amateur Radio License Classes:

Wednesday & Thursday: 7-9 pm Saturday 10 am-Noon

¡ AQUÍ SE  
 HABLA  
 ESPAÑOL !

The Export Experts Invite Overseas orders  
 — We Ship Worldwide



**BARRY ELECTRONICS**  
 512 BROADWAY, NEW YORK, N.Y. 10012  
 TELEPHONE (212) 925-7000  
 TELEX 12-7670

# New Automatic Antenna Tuner Auto-Track Model AT 2500



Options Available at Extra Cost



Shown with Rack Mount



Shown with Front Panel Handles

## Check these state-of-the-art specifications

- Power Capability: 2500 W PEP.
- Frequency Range: Continuous 3.0 to 30 MHz (Including WARC Bands).
- Impedance Matching: 10 ohms to 300 ohms to 50 ohms resistive.
- Direct Reading SWR Meter: 1:1 to infinity.
- Direct Reading Power Meter: Two meter scales from 0 W to 250 W and 0 W to 2500 W; front panel switch selects FWD or Reflected Power (*Illuminated panel meters*).
- Power meter displays RMS with continuous carrier and automatically displays PEAK when driven with SSB signal.
- Average "Automatic" tune-up time: 15 seconds or less.
- Tune-up time not affected by power level; can be as low as 1 W (5-10 W preferred).
- A unique "Linear Disable" circuit automatically switches companion linear amplifier to standby within milliseconds whenever SWR exceeds the threshold preset on front panel, thus protecting the linear from excessive SWR.
- Toroidal bridge coupler provided in separate enclosure, permitting it to be installed directly at the output of the transmitter for meaningful SWR measurements.
- Power requirements are 115/230 VAC 50-60 Hz, 10 W operating / 5 W standby; or 13.5 VDC, 1 A operating / .5 A standby.
- Antenna tuner packaged in cabinet 17"W x 5 1/4"H x 14"D (Front panel handles or rack mount optional).

Specifications subject to change without notice.

**See us in Dayton in April and  
enter drawing for free AT 2500.**

Write for literature.



**J. W. Miller Division  
BELL INDUSTRIES**

19070 REYES AVE. ■ P.O. BOX 5825  
COMPTON, CALIFORNIA 90224

# CW anyone?

## A challenge to break the world's code-speed record

**Have you been telling your wife and kids what a hot-shot code operator you were back in the big war? Your wife was probably impressed, and your kids were spellbound each time you related your war stories. Or perhaps you wax nostalgic over your wireless days in that rusty old oil tanker? Wasn't that the vessel whose officers recruited high-speed operators from Joe's waterfront bar? Didn't you copy code eight hours a day at 50 words a minute from that coastal station? A most remarkable achievement — particularly since that Navy station never transmitted faster than 18 words per minute!**

Perhaps you're a newcomer, just beginning to learn the code. If you have the ability to tune out these old timers, you should do very well indeed. They may tell you about the old-time wireless operator (or did he work for Western Union?) who waited on customers, made change, drank coffee, smoked a pipe, read the paper, and copied Morse code all at the same time. (For some strange reason the narrators can never remember the name of this operator of yesteryear.) The longer these old operators are away from Morse code, the faster they used to copy it.

### a challenge

If you fit into any of the categories mentioned, or

are new to Amateur Radio, then now is the moment of truth: now is the time to put your fist where your mouth is. I propose a threefold challenge:

1. The first is a *sanctioned code contest* to determine a national CW champion.
2. Next is a challenge to manufacturers of CW-oriented equipment to provide a suitable gift certificate to make the effort worthwhile.
3. Finally, I propose that *ham radio* magazine sponsor and perpetuate this contest on an annual basis, with a special award to anyone *officially exceeding the current world's record*. Quite a challenge. Are you game?

### code-speed record

What about this record? According to the *Guinness Book of World Records*, "The highest recorded speed at which anyone has received Morse code is 75.2 words per minute, — over 17 symbols per second. This was achieved by Ted R. McElroy (W1JYN) in a tournament at Asheville, North Carolina, on July 2, 1939."

On that same day, Ted set another record. He copied the American Morse Code at a speed of 77 words per minute. Following the contest, Ted wrote a letter to his old instructor, Walt Candler, in which he complained that the transmitting apparatus would not go any faster, and that there wasn't any competi-

**By Harry W. Lewis, W7JWJ, 10352 Sandpoint Way, N.E., Seattle, Washington 98125**

tion. Ted wrote, "You can't have a contest unless there is competition."

When Ted first learned the code, he used a buzzer set and an ancient typewriter. Consequently, it took him nearly nine months to reach the modest speed of 50 words per minute. So what is the problem now? Why hasn't this record been broken? We're surrounded by electronic keyboards, buffered typewriters, and memory devices that Ted McElroy never dreamed of. Isn't it time to break this record? Perhaps this challenge will initiate a serious attempt to do so.

## the competition

I know a number of operators who can copy Morse in excess of 75 words per minute. Just listen to Bill Eitel, W6UF, and the members of the Five-Star Net as they roar along at this speed. They can do it! Have you heard K7BW and his super speed contacts with N6AO? Watch Evelyn Headings, W7LLD, make a believer out of you as she copies at nearly 60 words per minute with a *pencil*. That's right — with a pencil. Can she break the world's record? Sure she can.

Jerry Ferrell, WB7VKI, has a certificate for 69.4 words per minute. Can he break the record? Well, he can as soon as he upgrades to General class and gets off the Novice bands. After that his code should begin to improve. However, he may be the first Novice to exceed 75 words per minute. There are many operators that can, and will, break this 42-year-old record. Why not this year?

## getting started

If you're a beginner you might ask how to proceed. First, you should learn to type at 75 words per minute without error. Many operators copy in their heads and lose the ability to transcribe and produce "hard copy" of what they receive. In a sanctioned contest this is a must.

What about the code? That's the easy part. However, a word of advice. The first half hour of your initial exposure to code will determine your learning curve. You must develop correct practice habits. Here are some tips. Stay away from those who reside in self-pity as they struggle to attain 5 words per minute but never practice. Don't listen to the "experts" who passed 13 words per minute for just one minute, one time, down at the FCC office. You can do it! Just a little correct practice every day and you can be a winner. Enter that next club code contest and you're on your way.

## contest rules

How about those club code contests? Have you ever listened to what is called code? The guy running the contest can't make a tape that runs over 20

words per minute, so he doubles the tape speed. Hey, don't do that, fella! It sounds like pure garbage. Give the guy who copies a chance!

What about official rules? For a world record to be valid, the contest must be held under rules similar to those in effect at the time Ted McElroy participated. According to those original rules, hard copy was submitted by each contestant. In the event of a tie, the text was checked for capitalization of each sentence and each proper noun. Text was selected, just before the contest, from old newspapers. Dates and common punctuation were permissible. Copy was machine-generated and transmitted. Dot-to-dash ratio was a one-to-three ratio with standard seven-element spacing between words. Contestants were allowed to bring their own typewriters and earphones. Three judges evaluated the contestants.

## word count

What about word count? Our grandfathers counted four letters for each word. Many Amateurs now count five letters for each word. If the bit rate per letter in the alphabet is computed, it will be found that the average bit rate is just in excess of 11.3846 bits per letter. This amounts to 56.923 average bits per word, plus word space. For years the military used the word CODEX, which contains 56 bits of information, plus word space.

In 1922, a count was made of newspaper print, and it was found that the average five-letter word contained only 50 bits of information. The word PARIS contains 50 bits of information and is the timing word now used by the FCC. This later rate, plus word space, should be the standard count.

Addition of numbers and punctuation will change the average transmitted rate. That's right. Transmitted Morse will not be at a constant speed. Speed must be averaged. For this reason, the only acceptable count must be the total bits of information transmitted in a prescribed time frame. Determining the total number of bits transmitted and average speed per minute is a simple program for any computer.

Ever listen to the experts that stand around a hamfest code contest and comment, "That's not 30 words per minute. I can copy that in my head." They are probably the same people who are afraid to try the Extra class code examination. Perhaps all of their copy is in their head. Now is the time for them to put their ears where their mouth is.

Perhaps soon there will be sanctioned state, regional, and national code contests. Then it will be your chance! Practice a little every day beginning today, then participate in the next contest. I intend to participate. I intend to beat the world's record. How about you? Hope to see you there!

**ham radio**

# tracking satellites in elliptical orbits

## Computer program and sample problem for tracking OSCAR

The launch failure of the first AMSAT-OSCAR Phase III satellite was unfortunate but is only a temporary setback. The delay before the next launch will give many Amateurs a chance to get better prepared. This article contains information to enable an Amateur, with the aid of a computer or calculator, to track, in azimuth and elevation, a satellite in an elliptical orbit.

The altitude and velocity of a satellite in a circular orbit are nearly constant. However, both altitude and velocity are always changing during an elliptical orbit. Communication range is greatest at the apogee: the point of maximum altitude. This condition corresponds to the point of minimum velocity with respect to an observer on earth. A low velocity means low Doppler shift; it also means that the satellite will re-

main in view for a longer time and will not demand rapid antenna tracking.

The spot on the earth surface directly beneath the satellite is called the subsatellite point. A plot of the path of this point is the ground track and must include the effects of earth rotation. If the altitude and subsatellite point are known at a given time, the azimuth and elevation can be found using the same equations as for circular orbits.

Ground station latitude,  $\delta_g$ , and longitude,  $\lambda_g$ , will be considered positive if the latitude is in the northern hemisphere and the longitude is west of the prime meridian. South latitude and east longitude must be entered as negative numbers.

### sample program

A program for the HP-41C programmable calculator and printer was written to test the equations and to learn more about elliptic orbits. **Table 1** shows the variable storage locations. Let's work through an example. Our ground station is located in Los Angeles with  $\delta_g = 34^\circ$  and  $\lambda_g = 118^\circ$ . The orbital parameters are:

By Paul C. Bunnell, WA6VJR, 1053 Nordhal Road, San Marcos, California 92069

R02= 0.685

R03= 328

R10= 15

R11= 9

R12= 21.05

R14= 0.5592

R15= 0.8290

R16= 0.8387

R17= 118

R18= 210

R19= 3963.2

R20= 100

R21= 0.1768

table 1. Storage locations of problem variables.

R00 =  $\lambda$

R01 =  $R_e/R_s$

R02 =  $e$

R03 =  $P_s$

R04 =  $\cos \delta_s$

R05 =  $\Gamma$  or  $\cos \theta$

R06 =  $E$  or  $\sin \lambda_{ref}$

R07 =  $\delta_s$  or  $e \cos E - 1$

R08 =  $\Delta t$

R09 =  $\lambda_s$  or  $\sin \theta$

R10 = TIME INCR.

R11 =  $\lambda_{ref}$

R12 =  $T_{ref}$

R13 =  $\sin \delta_s$

R14 =  $\sin \delta_{\theta}$

R15 =  $\cos \delta_{\theta}$

R16 =  $\sin i$

R17 =  $\lambda_{\theta}$

R18 = 0

R19 =  $R_e$

R20 = ORBIT

R21 =  $\mu$

table 2. Problem initial conditions.

GROUND TRACK

TIME	LAT	LONG	RNG	30	45	60	75	90	105	120	135	150	165	180	195	210	225	240	255	270	285	300	315	
-30	21.4	104.2	5.6																					
-15	23.1	106.6	5.6																					
0	24.8	109.0	5.6																					
15	26.5	111.3	5.6																					
30	28.2	113.6	5.6																					
-315	-55.0	159.6	3.1	45	29.0	115.9	5.6																	
-300	-51.0	104.6	4.0	60	31.5	118.0	5.6																	
-285	-38.5	86.2	4.5	75	33.3	120.1	5.6																	
-270	-28.0	79.7	4.3	90	35.0	122.0	5.6																	
-255	-21.4	77.3	5.0	105	36.8	123.7	5.6																	
-240	-15.5	76.7	5.2	120	38.6	125.3	5.6																	
-225	-10.7	77.1	5.3	135	40.5	126.6	5.5																	
-210	-6.7	78.2	5.3	150	42.5	127.6	5.5																	
-195	-3.1	79.6	5.4	165	44.5	128.2	5.5																	
-180	0.0	81.3	5.4	180	46.6	128.2	5.4																	
-165	2.8	83.3	5.5	195	48.8	127.5	5.4																	
-150	5.4	85.4	5.5	210	51.0	125.7	5.3																	
-135	7.7	87.5	5.5	225	53.3	122.4	5.3																	
-120	10.0	89.8	5.6	240	55.3	116.9	5.2																	
-105	12.1	92.1	5.6	255	56.8	108.1	5.0																	
-90	14.1	94.5	5.6	270	56.7	95.0	4.8																	
-75	16.0	96.9	5.6	285	52.9	77.1	4.5																	
-60	17.8	99.4	5.6	300	41.4	56.6	4.0																	
-45	19.6	101.8	5.6	315	14.6	35.2	3.1																	

table 3. Printout of sample problem showing tracking parameters. Range is in thousands of statute miles.

reference orbit No.	100
time reference at apogee ( $T_{ref}$ )	21.0500 (HH.MMSS)
longitude reference at apogee ( $\lambda_{ref}$ )	9°
inclination ( $i$ )	57°
argument of perigee ( $\Omega$ )	210°
eccentricity ( $e$ )	0.685
period of 1/2 orbit ( $P_s$ )	328 minutes

The radius of the earth,  $R_e$ , is 3963.2 statute miles, the normalized gravitational constant,  $\mu'$ , is 0.176842228. We will choose time increments of 15 minutes. These initial conditions are stored as shown in table 2. If ground track information is desired, the program is started at label E. The calculator halts and prompts you for the number of the orbit you wish to investigate. Let's look at orbit 105. Enter that number and press the R/S key to resume program execution. In a few minutes table 3 is printed. The apogee is at time 0, negative times occur before apogee, and the RNG (maximum range) column is in 1000s of statute miles. Also note that negative latitudes are in the southern hemisphere. To print the range with dimensions of kilometers or nautical miles, it's only necessary to enter  $R_e$  in those units.

The ground track can be plotted on a northern hemisphere polar map or just a piece of polar graph paper. I found it useful to use a transparent overlay, pivoted at the north pole. The ground track is marked on the overlay in grease pencil and may be rotated to any desired position. Maximum range information may be used to determine if the satellite is within range of any two ground stations.

Another part of the program calculates satellite azimuth and elevation. Only lines in which the satellite is above the horizon are printed. Start the program at label **ST** and again enter orbit 105. **Table 4** is the result, showing how azimuth and elevation change with time. The asterisk locates the time of apogee. It's not necessary to re-enter any of the orbital constants to plot other orbits. But, keep in mind that elliptic orbits suffer perturbations with time, and the latest orbital parameters available should be used.

The program requires one memory module and uses the 82143A peripheral printer. Data storage registers should be sized to 022. If a card reader is available, the program fits on two magnetic cards.

We're approaching a new era in Amateur satellite communications. New techniques and skills will be developed in the next few years as we gain experience. I hope this article will contribute to those efforts.

## bibliography

- Davidoff, "AMSAT-OSCAR Phase III on the Horizon," *QST*, May, 1980, pages 46-50.  
 Davidoff, "Using Satellites in the Classroom; a Guide for Science Educators," Cantonsville Community College, Cantonsville, Maryland, 1978.  
 Bate, Mueller, and White, *Fundamentals of Astrophysics*, Dover Publications, New York, New York 1971.

## appendix

The derivation of the equations is covered in the references, but there are several points of interest. **Fig. A1** is a view perpendicular to the plane of an elliptic orbit. The earth is at one focus,  $F$ , and the satellite at position  $S$ . Also shown are the apogee,  $A$ ; perigee,  $P$ ; one-half major axis,  $a$ ; and one-half minor axis,  $b$ .

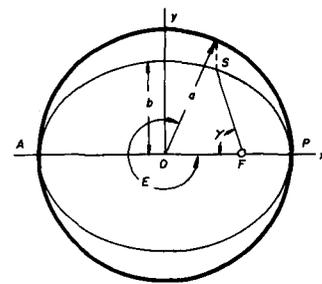


fig. 1. Geometry of the tracking problem for elliptical orbits.

### ORBIT 105

TIME	AZIMUTH	ELEVATION			
23:30	139	5	4:15	146	82
23:45	135	12	4:30	156	85
0:00	132	18	4:45	180	87
0:15	129	23	5:00	247	88
0:30	128	28	5:15	288	86
0:45	127	32	5:30	302	84
1:00	126	36	5:45	310	81
1:15	126	41	6:00	316	79
1:30	126	45	6:15	321	76
1:45	126	48	6:30	326	74
2:00	127	52	6:45	331	72
2:15	127	56	7:00	337	69
2:30	128	59	7:15	344	67
2:45	129	63	7:30	352	65
3:00	131	66	7:45	2	61
3:15	133	69	8:00	13	57
3:30	135	73	8:15	28	50
3:45*	137	76	8:30	44	36
4:00	141	79	8:45	62	11

table 4. Tracking dynamics showing satellite azimuth and elevation as functions of time.

A circle has been constructed with center,  $O$ , bisecting  $AP$ , and with radius  $a$ . Angle  $E$  is identified as the elliptic anomaly, and  $\Gamma$  is the true anomaly. Both  $E$  and  $\Gamma$  are related to the mean anomaly,  $M$  (see eqs. **A1** and **A3**).

The problem to be solved (sometimes called the Kepler problem) is to find  $E$ , given  $\Delta t$  (the time of flight from  $S$  to  $A$ ). With  $E$  known  $\Gamma$  can be found from eq. **A3**, and the satellite position with respect to the earth is then established.

We start the solution by approximating the value for  $E$ , calculating  $M'$ , and generating an error term,  $\xi$ .  $E'$  is formed and checked in eq. **A2** to see if the error term has been reduced to zero. If not, return to eq. **A1**, substituting  $E'$  for  $E$ , and repeat the process. Only four or five iterations are necessary for an accuracy of 1 part in one million.

$\lambda_0$  is commonly called the longitude of the ascending node. It is derived from the argument of perigee,  $\Omega$ . The location of the subsatellite point is given by latitude  $\delta_s$ , and the longitude,  $\lambda_s$ .  $R_s$  is the instantaneous satellite distance from the center of the earth. The maximum range is an arc on the surface of the earth from the subsatellite point to a location where the satellite elevation drops to zero.

01♦LBL "ST"	6° 360	136 ST- 06	206 RTN
02 XEQ 04	70 MOD	137 X=0?	207♦LBL 04
03 STO 00	71 XEQ 08	138 GT0 00	208 FIX 0
04 CF 12	72 "F "	139 RCL 06	209 SF 12
05 "TIME A	73 RCL 05	140 R-D	210 CF 29
ZIMUTH"	74 RCL 01	141 COS	211 "ORBIT
06 "F ELEV	75 -	142 RCL 02	212 PROMPT
ATION"	76 RCL 09	143 /	213 ARCL X
07 AVIEW	77 /	144 RCL 07	214 AVIEW
08♦LBL 05	78 ATAN	145 /	215 ADV
09 XEQ 01	79 XEQ 06	146 ACOS	216 ENTER↑
10 FIX 2	80 GT0 05	147 RCL 08	217 X<> 20
11 60	81♦LBL E	148 SIGN	218 -
12 /	82 XEQ 04	149 *	219 RCL 03
13 RCL 12	83 STO 00	150 STO 05	220 *
14 HR	84 "GROUND	151 RCL 18	221 2
15 +	TRACK"	152 +	222 /
16 RND	85 AVIEW	153 XEQ 07	223 ENTER↑
17 FIX 0	86 CF 12	154 RCL 00	224 X<> 11
18 24	87 ADV	155 -	225 +
19 MOD	88 "TIME	156 RCL 08	226 360
20 INT	LAT"	157 3.989	227 MOD
21 10	89 "F LON	158 /	228 X<> 11
22 X>Y?	G RNG"	159 +	229 15
23 "F "	90 AVIEW	160 RCL 11	230 /
24 ARCL Y	91♦LBL 03	161 +	231 RCL 12
25 "F:"	92 XEQ 01	162 360	232 HR
26 LASTX	93 FIX 0	163 MOD	233 +
27 FRC	94 XEQ 02	164 STO 09	234 24
28 60	95 FIX 1	165 1	235 MOD
29 *	96 RCL 07	166 RCL 02	236 HMS
30 X<Y?	97 XEQ 08	167 RCL 05	237 STO 12
31 "F0"	98 RCL 09	168 COS	238 RCL 03
32 ARCL X	99 XEQ 08	169 *	239 RCL 10
33 RCL 08	100 RCL 01	170 -	240 MOD
34 X=0?	101 ACOS	171 RCL 03	241 RCL 03
35 "F*"	102 D-R	172 PI	242 -
36 X=0?	103 RCL 19	173 /	243 STO 08
37 "F "	104 *	174 2	244 RCL 18
38 RCL 13	105 .1	175 ENTER↑	245♦LBL 07
39 RCL 17	106 %	176 3	246 1
40 RCL 09	107 XEQ 06	177 /	247 P-R
41 -	108 GT0 03	178 Y↑X	248 X<>Y
42 SIN	109♦LBL 01	179 /	249 CHS
43 STO 06	110 FIX 6	180 RCL 21	250 RCL 16
44 X<> L	111 1	181 /	251 *
45 COS	112 RCL 08	182 1	252 STO 13
46 RCL 15	113 RCL 03	183 RCL 02	253 ASIN
47 *	114 /	184 X↑2	254 STO 07
48 RCL 04	115 -	185 -	255 COS
49 *	116 PI	186 /	256 STO 04
50 RCL 14	117 *	187 STO 01	257 /
51 RCL 13	118 STO 06	188 CLA	258 ACOS
52 *	119 ENTER↑	189 RCL 08	259 RCL 07
53 +	120♦LBL 00	190 RTN	260 SIGN
54 STO 05	121 CLX	191♦LBL 08	261 *
55 RCL 14	122 RCL 06	192 "F "	262 RTN
56 *	123 R-D	193♦LBL 02	263♦LBL 06
57 -	124 RCL 02	194 RND	264 XEQ 02
58 RCL 15	125 P-R	195 ENTER↑	265 RCL 2
59 /	126 1	196 ABS	266 X>0?
60 RCL 05	127 -	197 X=Y?	267 AVIEW
61 ACOS	128 STO 07	198 "F "	268 RCL 08
62 SIN	129 CLX	199 100	269 RCL 10
63 STO 09	130 RCL 06	200 X>Y?	270 +
64 /	131 -	201 "F "	271 STO 08
65 ACOS	132 +	202 SORT	272 RCL 03
66 RCL 06	133 RND	203 X>Y?	273 X<Y?
67 SIGN	134 RCL 07	204 "F "	274 STOP
68 *	135 /	205 ARCL 2	275 .END.

Program listing for the Hewlett-Packard HP-41C programmable calculator.



**fact:**  
**armchair copy**  
**begins here**

- ask:**
- |        |        |          |
|--------|--------|----------|
| KA2CLF | WB5VOB | WD8MQJ   |
| W21SB  | W71JH  | KB9NR    |
| W31TG  | W7KHD  | W9BB     |
| K4CX4  | N8AQW  | WB9VCI   |
| K4HCD  | K8ZYK  | N9MP     |
| N4CVV  | K8ZZO  | N9BHT    |
| K5RDP  | KB8GD  | WØJO     |
| W5UKS  | WB8SHV | 4X4AN/W9 |

If you've been "reading the mail" on recent transmissions from the hams listed above, you've heard the kind of solid copy that rates a Q5. One reason is that they've recently switched to Shure's new 444D SSB/FM Base Station Microphone. We've been getting glowing reports on the 444D's switch-selectable dual impedance feature which makes for compatibility and changeability from rig to rig; improved million-cycle PTT control bar (with vox/normal switch and continuous-on capability); and its comprehensive all-new wiring guide. The cable leads are arranged to permit immediate hook-up to transmitters with either isolated or grounded switching. Ask the hams who own one! FREE! Amateur Radio Microphone Selector Folder, ask for AL645.

**444D SSB/FM**  
**Base Station Microphone**



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204  
 In Canada: A. C. Simmonds & Sons Limited  
 Manufacturers of high fidelity components,  
 microphones, sound systems and related circuitry.

**additional definitions:**

- $P_s$  = period of  $\frac{1}{2}$  orbit
- $e$  = eccentricity
- $i$  = inclination
- $\Omega$  = argument of perigee
- $\lambda_{ref}$  = longitude reference at apogee
- $R_e$  = radius of earth
- $R_s$  = distance from earth center to satellite
- $\mu'$  = normalized gravitational constant
- $\delta_g$  = ground station latitude
- $\lambda_g$  = ground station longitude

$$\text{Let } M = \pi \left( 1 - \frac{\Delta t}{P_s} \right) \text{ in radians}$$

$$\text{Guess } E = M$$

$$M' = e \sin \left( \frac{360E}{2\pi} \right) - E \quad \leftarrow \quad \text{(A1)}$$

$$\xi = \frac{M' - M}{e \cos E - 1} \quad \text{LOOP}$$

$$E' = E - \xi$$

If  $E' \neq E$  ————— (A2)

$$\Gamma = \text{SIGN}(\Delta t) \cos^{-1} \left( \frac{\cos E - e}{e \cos E - 1} \right) \quad \text{(A3)}$$

$$\delta_o = \sin^{-1}(-\sin \Omega \sin i)$$

$$\lambda_o = \text{SIGN}(\delta_o) \cos^{-1} \left( \frac{\cos \Omega}{\cos \delta_o} \right)$$

$$\delta_s = \sin^{-1}(-\sin(\Omega + \Gamma) \sin i)$$

$$\lambda_s = \text{SIGN}(\delta_s) \cos^{-1} \left( \frac{\cos(\Omega + \Gamma)}{\cos \delta_s} \right) + \frac{\Delta t}{3.989}$$

$$- \lambda_o + \lambda_{ref}$$

$$\frac{R_s}{R_e} = \frac{\mu' (1 - e^2) (P_s / \pi)^{2/3}}{1 - e \cos \Gamma}$$

$$\text{maximum range} = \frac{R_e}{1000} \frac{2\pi}{360} \left[ \cos^{-1} \left( \frac{R_e}{R_s} \right) \right]$$

$$\theta = \cos^{-1}[\sin \delta_s \sin \delta_g + \cos \delta_s \cos \delta_g \cos(\lambda_s - \lambda_g)]$$

$$\text{azimuth} = \cos^{-1} \left( \frac{\sin \delta_s - \cos \theta \sin \delta_g}{\cos \delta_g \sin \theta} \right)$$

if  $\sin(\lambda_s - \lambda_g) < 0$ , azimuth = 360 - azimuth

$$\text{elevation} = \tan^{-1} \left( \frac{\cos \theta - R_e / R_s}{\sin \theta} \right)$$

Note:  $\text{SIGN}(x) = -1$  if  $x$  is negative  
 $+1$  if  $x$  is positive or zero


**ham radio**

# Quality VHF/UHF Kits at Affordable Prices~
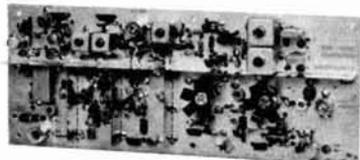
## These Low Cost SSB TRANSMITTING CONVERTERS

Let you use inexpensive recycled 10M or 2M SSB excitors on UHF & VHF!

- Linear Converters for SSB, CW, FM, etc.
- A fraction of the price of other units; no need to spend \$300 - \$400!
- Use with any exciter; works with input levels as low as 1 mW.
- Use low power tap on exciter or simple resistor attenuator pad (instructions included).
- Link osc with RX converter for transceive.



### XV4 UHF KIT — ONLY \$99.95

28-30 MHz in, 435-437 MHz out; 1W p.e.p. on ssb, up to 1½W on CW or FM. Has second oscillator for other ranges. Atten. supplied for 1 to 500 mW input, use external attenuator for higher levels.

Extra crystal for 432-434 MHz range ..... \$5.95  
XV4 Wired and tested ..... \$149.95

### XV2 VHF KIT - ONLY \$69.95

2W p.e.p. output with as little as 1mW input. Use simple external attenuator. Many freq. ranges available.

MODEL	INPUT (MHz)	OUTPUT (MHz)
XV2-1	28-30	50-52
XV2-2	28-30	220-222
XV2-4	28-30	144-146
XV2-5	28-29 (27-27.4 CB)	145-146 (144-144.4)
XV2-7	144-146	50-52

XV2 Wired and tested ..... \$109.95

### XV28 2M ADAPTER KIT - \$24.95

Converts any 2M exciter to provide the 10M signal required to drive above 220 or 435 MHz units.



### NEW! COMPLETE TRANSMITTING CONVERTER AND PA IN ATTRACTIVE CABINET

Far less than the cost of many 10W units!

Now, the popular Hamtronics® Transmitting Converters and heavy duty Linear Power Amplifiers are available as complete units in attractive, shielded cabinets with BNC receptacles for exciter and antenna connections. Perfect setup for versatile terrestrial and OSCAR operations! Just right for phase 3! You save \$30 when you buy complete unit with cabinet under cost of individual items. Run 40-45 Watts on VHF or 30-40 Watts on UHF with one integrated unit! Call for more details.

MODEL	KIT	WIRED and TESTED
XV2/LPA2-45/Cabt (6, 2, or 220)	\$199.95	\$349.95
XV4/LPA4-30/Cabt (for UHF)	\$229.95	\$399.95

## Easy to Build FET RECEIVING CONVERTERS

Let you receive OSCAR and other exciting VHF and UHF signals on your present HF or 2M receiver



- NEW LOW-NOISE DESIGN
- ATTRACTIVE WOODGRAIN CASE
- Less than 2dB noise figure, 20dB gain

MODEL	RF RANGE	OUTPUT RANGE
CA28	28-32 MHz	144-148 MHz
CA50	50-52	28-30
CA50-2	50-54	144-148
CA144	144-146	28-30
CA145	145-147-or-144-144.4	28-30
CA146	146-148	27-27.4 (CB)
CA220	220-222	28-30
CA220-2	220-224	144-148
CA110	Any 2MHz of Aircraft Band	26-28 or 28-30
CA432-2	432-434	28-30
CA432-5	435-437	28-30
CA432-4	432-436	144-148

Easily modified for other rf and if ranges.

STYLE	VHF	UHF
Kit less case	\$34.95	\$49.95
Kit with case	\$39.95	\$54.95
Wired/Tested in case	\$54.95	\$64.95

## Professional Quality VHF/UHF FM/CW EXCITERS

- Double tuned circuits for spurious suppression
- Easy to align with built-in test aids



T51-30	10 Meter, 2W Kit.....	\$44.95
T51-50	6 Meter, 2W Kit.....	\$44.95
T51-150	2 Meter, 2W Kit.....	\$44.95
T51-220	220 MHz, 2W Kit.....	\$44.95
T450	450 MHz, 3/4W Kit.....	\$44.95
T451	450 MHz, 3 W Kit.....	\$59.95
A14T	5 Chan Adapter (T51&T451)	\$9.95

## See our Complete Line of VHF & UHF Linear PA's

- Use as linear or class C PA
  - For use with SSB Xmtg Converters, FM Exciters, etc.
- |         |                        |          |
|---------|------------------------|----------|
| LPA2-15 | 6M, 2M, 220; 15 to 20W | \$59.95  |
| LPA2-30 | 6M, 2m; 25 to 30W      | \$89.95  |
| LPA2-40 | 220 MHz; 30 to 40W     | \$119.95 |
| LPA2-45 | 6M, 2M; 40 to 45W      | \$119.95 |
| LPA4-10 | 430MHz; 10 to 14W      | \$79.95  |
| LPA4-30 | 430MHz; 30-40W         | \$119.95 |
- See catalog for complete specifications

## IT'S EASY TO ORDER!

- Write or phone 716-392-9430
- Electronic answering service evenings & weekends
- Use Credit Card. UPS COD. Check. Money Order
- Add \$2.00 shipping & handling per order


Call or Write to get  
**FREE CATALOG**  
With Complete Details

(Send 4 IRC's for overseas mailing)

HAMTRONICS® IS A REGISTERED TRADEMARK
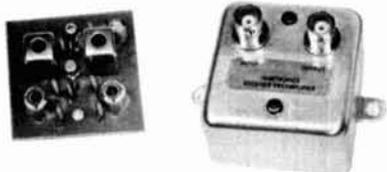
## FAMOUS HAMTRONICS PREAMPS

Let you hear the weak ones too!  
Great for OSCAR, SSB, FM, ATV. Over 14,000 in use throughout the world on all types of receivers.



- NEW LOW-NOISE DESIGN
- Less than 2 dB noise figure, 20 dB gain
- Case only 2 inches square
- Specify operating frequency when ordering

MODEL P-30 VHF PREAMP, available in many versions to cover bands 28-300 MHz.


MODEL P432 UHF PREAMP, available in versions to cover bands 300-650 MHz.

STYLE	VHF	UHF
Kit less case	\$12.95	\$18.95
Kit with case	\$18.95	\$26.95
Wired/Tested in Case	\$27.95	\$32.95
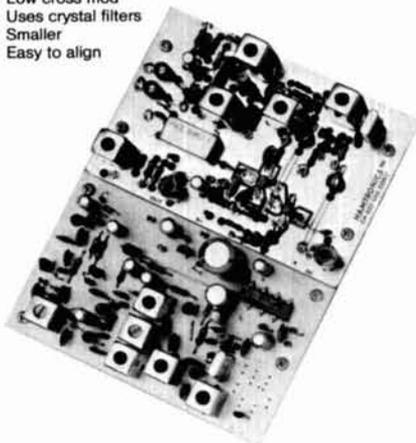
## NEW VHF/UHF FM RCVR'S

Offer Unprecedented Range of Selectivity Options

- New generation
- More sensitive
- More selective
- Low cross mod
- Uses crystal filters
- Smaller
- Easy to align



R75A\* VHF Kit for monitor or weather satellite service. Uses wide L-C filter. -60dB at ± 30 kHz..... \$69.95

R75B\* VHF Kit for normal nbm service. Equivalent to most transceivers. -60dB at ± 17 kHz, -80dB at ± 25 kHz... \$74.95

R75C\* VHF Kit for repeater service or high rf density area. -60dB at ± 14kHz, -80dB at ± 22kHz, -100dB at ± 30kHz.... \$84.95

R75D\* VHF Kit for split channel operation or repeater in high density area. Uses 8-pole crystal filter. -60dB at ± 9kHz, -100dB at ± 15 kHz. The ultimate receiver!... \$99.95

\* Specify band: 10M, 6M, 2M, or 220 MHz. May also be used for adjacent commercial bands. Use 2M version for 137 MHz WX satellites.

R450( ) UHF FM Receiver Kits, similar to R75, but for UHF band. New low-noise front end. Add \$10 to above prices. (Add selectivity letter to model number as on R75.)

A14 5 Channel Adapter for Receivers..... \$9.95

## NEW R110 VHF AM RCVR

AM monitor receiver kit similar to R75A, but AM. Available for 10-11M, 6M, 2M, 220 MHz, and 110-130 MHz aircraft band \$74.95. (Also available in UHF version.)

**hamtronics, inc.**

65M MOUL RD · HILTON, NY 14468

# protection for your solid-state devices

## Fail-safe regulator for bench supply reduces mortality rate

Many Amateur experimenters have learned from experience that active solid-state devices are not as forgiving as vacuum tubes. A 6L6 for example can absorb considerable abuse and keep right on working; long ago we discovered we could avoid a catastrophic failure by quickly switching off the power supply when the plate began to glow.

Unfortunately, solid-state devices don't provide us with that opportunity. High-performance devices such as vhf or microwave transistors react quickly and violently when overloaded; the time required for a GASFET to destroy itself is considerably less than a microsecond. In view of the relatively high cost (and consequent scarcity) of these devices, it seems appropriate to attack the problem at the source — the power source.

Accidents can and do happen. Consider a typical 0-30 volt bench power supply adjusted to 10 volts output, connected to a transistor circuit for test. If the supply includes a large capacitor across its output terminals, it is a potential transistor killer. In the event we should inadvertently increase the output voltage (perhaps by bumping the knob), even though the power supply's current limiting mechanism

should react properly to the ensuing overcurrent condition, the energy already stored in the output capacitor can create a transient that may destroy the transistor.

### built-in protection

If a circuit employing a bipolar transistor is to be tested at known, fixed voltage and current, protection can be built in. The single-stage transistor amplifier shown in **fig. 1** is a typical example. An amplifier of this kind is essentially damage proof.

### general-purpose regulator

A general-purpose bench power supply regulator is illustrated in **fig. 2**. This regulator is particularly useful when testing power amplifiers. It includes provisions for setting the maximum available voltage and current levels to desired safe values. In the circuit shown, the 12-volt zener at the output is used as backup for the MOSFET shunt regulator. If the regulator should fail, the zener would limit the output to 12 volts.

R1 sets the maximum available load power, which in this case is 1.011 watts:

$$P_o(max) = \frac{(E_{in})^2}{4RI}$$

where  $E_{in} = 18.7$  (manufacturer's tolerance)  
 $RI = 91.5$  percent (tolerance)

$$P_o(max) = \frac{(18.7)^2}{4(86.45)} = 1.011 \text{ watts}$$

Note that this maximum power condition provides 98.9 milliamperes and 9.0 volts. Any increase in load

By Henry H. Cross, W1OOP, 111 Birds Hill Avenue, Needham, Massachusetts 02192



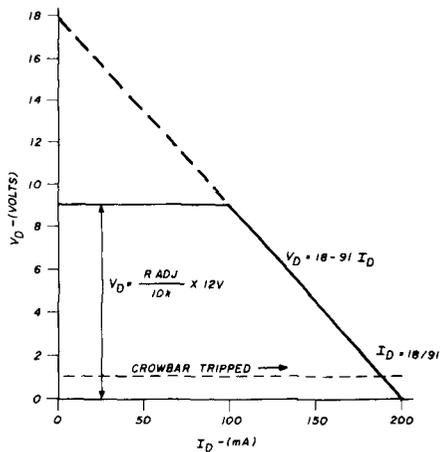


fig. 3. Performance of the general-purpose bench power-supply regulator. Maximum power condition is 98.9 milliamperes at 9 volts.

creases with clockwise rotation. With some additional effort, you may be able to adjust the control-circuit parameter values so that the output voltage and current match the dial readings.

### low-voltage regulators

Lower power GASFETS generally require 5-50 milliamperes at approximately 3 volts. It would be desirable to use a 4-volt zener at the output in this case as backup for the shunt regulator; however, since zeners in this voltage range don't exhibit the sharp knees of higher voltage types, the regulator is in need of some other kind of protective device.

Fig. 4 illustrates a crowbar circuit that can solve this problem. The circuit consists of a shunt SCR that fires when the regulator output voltage exceeds a preset value. The drop across the forward-conducting SCR is about 0.8 volt, not small enough to turn the supply completely off, but low enough to provide a good measure of protection.

An LM339 comparator functions as an open-loop op amp. R6 is adjusted so that the output will go low if the regulator output exceeds 3.1 volts. When this happens, the trigger voltage goes high, firing the SCR. Note that the anode sustaining current is about

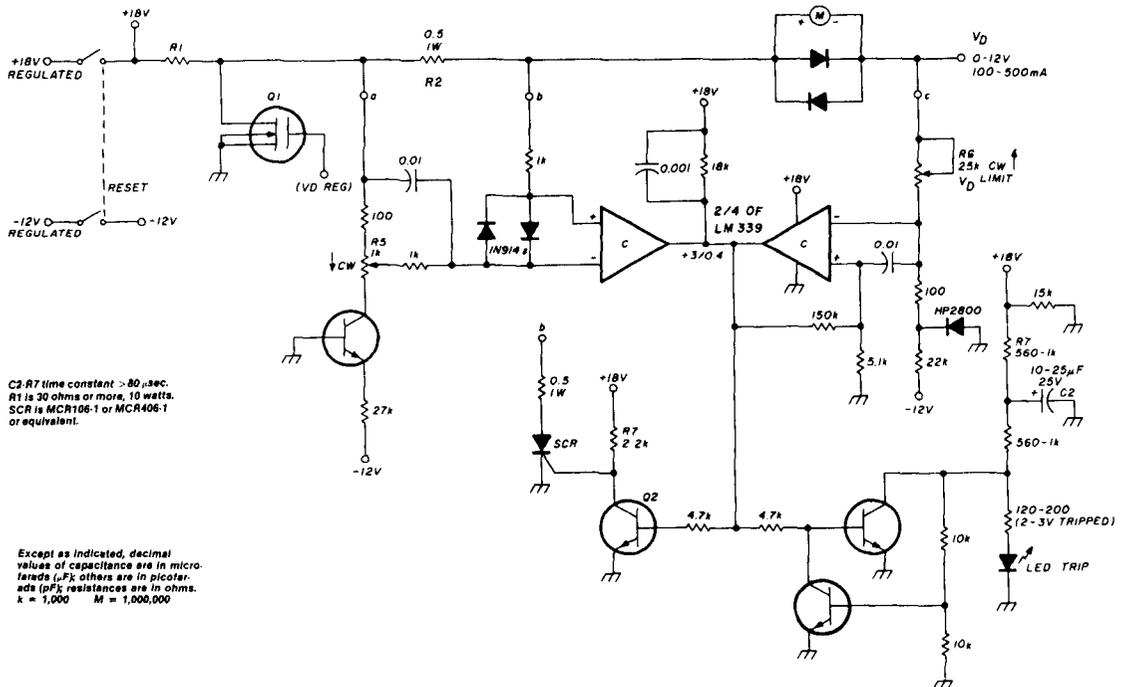


fig. 4. Crowbar circuit for low-voltage regulators.



## DRAKE 7-Line Family



A pacesetter since 1943, Drake led in 1963 with 9 MHz i-f transceiving, and now with 48 MHz i-f "Up Conversion" . . . Drake brings you tomorrow's state of the art today.



# R7

## Synthesized General Coverage Receiver

Model 1240

Full general coverage reception, 0-30 MHz, with no gaps or range crystals required.

Continuous tuning all the way from vlf thru hf. Superb state-of-the-art performance on a-m, ssb, RTTY, and cw—and it transceives with Drake TR7.

- **100% solid state broadband design**, fully synthesized with a permeability tuned oscillator (PTO) for smooth, continuous tuning.
- **Covers the complete range 0 to 30 MHz** with no gaps in frequency coverage. Both digital and analog frequency readout.
- **Special front-end circuitry** employing the high level double balanced mixer and 48 MHz "up-converted" 1st i-f for superior general coverage, image rejection and strong signal handling performance.
- **Complete front-end bandpass filters** are included that operate from hf thru vlf. External vlf preselectors are not required.
- **10 dB pushbutton-controlled broadband preamp** can be activated on all ranges above 1.5 MHz. Low noise design.
- **Various optional selectivity filters** for cw, RTTY and a-m are switch-selected from the front panel. Ssb filter standard.
- **Special new low distortion "synchro-phase" a-m detector** provides superior international shortwave broadcast reception. This new technique permits 3 kHz a-m sideband response with the use of a 4 kHz filter for better interference rejection.
- **Tunable i-f notch filter** effectively reduces heterodyne interference from nearby stations.
- **The famous Drake full electronic passband tuning system** is employed, permitting the passband position to be adjusted for any selectivity filter. This is a great aid in interference rejection.
- **Three agc time constants** plus "Off" are switch-selected from the front panel.
- **Complete transceive/separate functions** when used with the Drake TR7 transceiver are included, along with separate R7 R.I.T. control.
- **Special multi-function antenna selector/50 ohm splitter** is switch-selected from the front panel, and provides simultaneous dual receive with the TR7. This makes possible the reception of two different frequencies at the same time. Main and alternate antennas and vhf/uhf converters may also be selected with this switching network.
- **The digital readout** of the R7 may be used as a 150 MHz counter, and is switched from the front panel. Access thru rear panel connector.
- **The built-in power supply** operates from 100, 120, 200, 240 V-ac, 50/60 Hz, or nominal 13.8 V-dc.
- **The R7 includes a built-in speaker**, or an external Drake MS7 speaker may be used.
- **Built-in 25 kHz calibrator** for calibration of analog dial.
- **Low level audio output** for tape recorder.
- **Up to eight crystal controlled fixed channels** can be selected. (With Drake Aux7 installed.)
- **Optional Drake NB7A Noise Blanker** available. Provides true impulse type noise blanking performance.

*Specifications, availability and prices subject to change without notice or obligation.*

### R. L. DRAKE COMPANY



540 Richard St., Miamisburg, Ohio 45342, USA  
Phone: (513) 866-2421 • Telex: 288-017

# Reach Out!

just like adding a 10-watt amp to your 2-meter hand-held...

- True  $\frac{5}{8}$  wave gain antenna
- Dramatically boosts reception as well as transmit range
- Individually tuned matching network
- Base spring/tuned coil protects radio as well as antenna from accidents
- Extends to 47", telescopes to only 8"
- BNC connector fits most current hand-held and portable radios
- Better than 1.5:1 VSWR across the entire 144-148 MHz band
- Only \$24.95 from your dealer or postpaid from VoCom  
(Illinois residents please include 6% sales tax)


Ask about our 25, 50 and 100 watt amplifiers for hand-helds

**VoCom**  
PRODUCTS CORPORATION


65 E. Palatine Rd., Suite 111  
Prospect Heights, IL 60070  
(312) 459-3680

Dealer Inquiries Invited

## WANTED FOR CASH

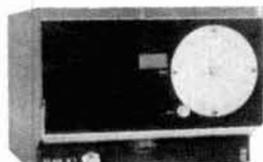

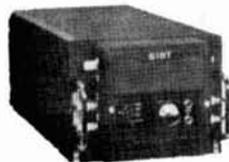490-T Ant. Tuning Unit  
(Also known as CU1658 and CU1669)



618-T Transceiver  
(Also known as MRC95, ARC94, ARC102, or VC102)

4CX150  
4CX250  
4CX300A  
4CX350A

4CX1000  
4CX1500  
4CX3000  
4CX5000



4CX10,000    4-65    4-250    4-1000  
5CX1500    4-125A    4-400    304TL

Other tubes and Klystrons also wanted.

Highest price paid for these units. Parts purchased. Phone **Ted, W2KUW** collect. We will trade for new amateur gear. GRC106, ARC105, ARC112, ARC114, ARC115, ARC116, and some aircraft units also required.

**DCO, INC.**

10 Schuyler Avenue  
Call Toll Free  
**800-526-1270**

No. Arlington, N. J. 07032  
(201) 998-4246  
Evenings (201) 998-6475

5 milliamperes, and it might be less than what the FET is drawing; so we have to keep triggering it. Normally the current through R6 is pulled to ground through the associated forward conducting transistor Q2.

Another comparator compares the voltage across current-sensing resistor R2 against a bucking voltage. When the preset current limit is exceeded, the SCR triggers. R5 is the current-limit control.

Both comparators are operated from a single power supply, with the GND terminals grounded. Under this condition, operation may become erratic if any of the op amp inputs go below ground by more than 0.5 volt. To avoid a possible problem here, the HP2800 diode and 510-ohm resistor should be included as shown.

The current meters are located across terminals b-c, after the crowbar (for obvious reasons). If the crowbar circuit should fire, the output voltage will drop to some value less than 1 volt, and the current will fall to a low value. To reset the regulator, turn off both power supplies, wait one second or longer, and turn them back on again. Note that the order in which the supplies are turned on or off is unimportant because, if the negative voltage is lacking, the positive voltage will not come on.

If a double-pole, single-throw toggle switch were connected between the regulated input voltages and the regulator, it would function as a RESET control. This is indicated at the left in **fig. 4**. The reset switches are normally closed.

The circuits of **figs. 2** and **4** also include LEDs, which indicate that each power supply is ON. Another LED indicates that the overcurrent circuit has tripped. When not otherwise indicated, the transistors are 2N3904 or 2N2222s. The comparators are LM339, 393, 2901, or 2903s.

### summary

Power supplies used for experimental purposes should be equipped with fail-safe regulators, including:

1. Reverse voltage protection
2. Overvoltage protection
3. Thermal runaway protection
4. Limited available power

Regulators should be equipped with limit controls on output voltage and current. (Limit controls should not be confused with adjustments.) Shunt-type regulators can be power limited and stable without requiring a large energy-storing, transistor-killing capacitor across the output terminals. Simple electronic biasing circuits are generally best.

ham radio

# NRI will train you at home to be an electronics professional in the wide world of communications.

Learn to service, repair, and install everything from microwave antennas to two-way radios... from radar sets to TV transmitters.

No other home-study course gives you such complete, professional training in so many fields of communication. No other gives you the actual bench training with kits and demonstration units specially designed for learning. Only NRI gives you the thorough preparation and training you need to achieve professional competence in the wide world of communications.

## Learn at Home in Your Spare Time

Learn at your own pace, right in your own home. There's no need to quit your job or tie up your evenings with night classes. No time or gas wasted traveling to school... NRI brings it all to you. You learn with NRI-pioneered "bite-size" lessons and proven, practical "power-on" training.

## Build Your Own 2-Meter, Digitally Synthesized VHF Transceiver

NRI training is "hands-on" training. You get honest bench experience as you build and test this



Mobile Radio



Microwave Relay



TV Broadcasting



CB Radio



AM & FM Broadcasting

industrial-quality two-way radio and power supply. You reinforce theory lessons as you induce and correct faults, study individual circuits and learn how they interface with others. Or, at your option, you can train with a fully-assembled forty-channel mobile CB and base-station power supply converter.

You also build and keep for use in your work a transistorized volt-ohm meter and digital CMOS frequency counter. NRI even gives you special lessons to get your Amateur License so you can go on the air with your VHF transceiver.

## FCC License or Full Refund

In all, you get 48 lessons, 9 special reference texts, and 10 training kits... the training you need to become a professional. And NRI includes training for the required FCC radiotelephone license examination. You pass or *your tuition will be refunded in full*. This money-back agreement is valid for six months after the completion of your course.

## Free Catalog, No Salesman Will Call

NRI's free, 100-page full-color catalog shows all the equipment you get, describes each lesson and kit in detail, tells more about the many specialized fields we train you for. It includes all facts on other interesting areas like TV and audio servicing or digital computer electronics. Mail the coupon and see how we can make you a pro. If coupon has been removed, write: NRI Schools, 3939 Wisconsin Ave., Washington, D.C. 20016.

## R-X Noise Bridge



- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less. Send for our free brochure.

The price is \$55.00 in the U.S. and Canada. Add \$3.00 shipping/handling. California residents add sales tax.



Fully guaranteed by the originator of the R-X Noise Bridge. ORDER YOURS NOW!

# Palomar Engineers

Box 455, Escondido, CA. 92025  
Phone: [714] 747-3343



**NRI Schools**  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Avenue  
Washington, D.C. 20016

Please check for one  
free catalog only.  
**NO SALESMAN WILL CALL**

- |  |  |
|--|--|
| <input type="checkbox"/> TV/Audio/Video Systems Servicing  | <input type="checkbox"/> Digital Electronics • Electronic Technology • Basic Electronics       |
| <input type="checkbox"/> Complete Communications Electronics with CB • FCC Licenses • Aircraft, Mobile, Marine Electronics | <input type="checkbox"/> Small Engine Repair   |
| <input type="checkbox"/> CB Specialists Course   | <input type="checkbox"/> Electrical Appliance Servicing  |
| <input type="checkbox"/> Computer Electronics Including Microcomputers   | <input type="checkbox"/> Automotive Mechanics  |
|  | <input type="checkbox"/> Auto Air Conditioning   |
|  | <input type="checkbox"/> Air Conditioning, Refrigeration, & Heating Including Solar Technology |

All career courses approved under GI Bill.  Check for details.

Name \_\_\_\_\_ (Please Print) \_\_\_\_\_ Age \_\_\_\_\_

Street \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Accredited by the Accrediting Commission of the National Home Study Council

20-031

**Only  
TEN-TEC  
Offers A  
Money Back  
Guarantee.**



**See your nearest  
participating dealer  
for details  
on this new  
no-risk  
trial offer.**

# TEN-TEC PARTICIPATING DEALERS

## Alabama

Alabama Treasure Hunter  
Huntsville

## California

Ham Radio Outlet  
Anaheim

Ham Radio Outlet  
Burlingame

Ham Radio Outlet  
Oakland

Ham Radio Outlet  
San Diego

Ham Radio Outlet  
Van Nuys

## Colorado

CW Electronics  
Denver

## Connecticut

Hatry Electronics  
Hartford

## Delaware

Delaware Amateur Supply  
New Castle

Amateur & Advance  
Communications  
Wilmington

## Florida

Mike's Electronics  
Fort Lauderdale

Hialeah Communications  
Hialeah

Amateur Electronic Supply  
Orlando

## Idaho

Custom Electronics  
Boise

Ross Distributing Co.  
Preston

## Illinois

Organs & Electronics  
Lockport

## Indiana

Lakeland Electronic Supply  
Angola

The Ham Shack  
Evansville

Electronic Communications  
Industries  
South Bend

## Iowa

Hi Inc.  
Council Bluffs

## Massachusetts

Tufts Radio Electronics  
Medford

## Michigan

Omar Electronics  
Durand

Radio Parts, Inc.  
Grand Rapids

## Missouri

Henry Radio  
Butler

Ham Radio Center, Inc.  
St. Louis

Mid-Com Electronics  
St. Louis

## Nebraska

Omaha Amateur Center  
Omaha

## Nevada

Amateur Electronic Supply  
Las Vegas

## New Jersey

Radios Unlimited  
Somerset

## New Mexico

Pecos Valley  
Amateur Radio  
Roswell

## New York

Grand Central Radio  
New York

Ham Radio World  
Oriskany

## North Carolina

Bino Communications  
Greensboro

## Ohio

Ken-Mar Industries  
North Canton

Universal Amateur Radio  
Reynoldsburg

Amateur Electronic Supply  
Wickliffe

## Oklahoma

Radio Incorporated  
Tulsa

## Oregon

Eugene Radio Supply  
Eugene

## Pennsylvania

Supelco Inc.  
Belleville

South Hills Electronics  
Pittsburgh

Carr Electronics  
Telford

Ham Buerger Inc.  
Willow Grove

## South Carolina

GIZMO Communications  
Rock Hill

## South Dakota

Burgharat Amateur Center  
Watertown

## Tennessee

ARSON  
Madison

Germantown Amateur  
Supply

Memphis  
J-Tron  
Springfield

## Texas

Texas Tower  
Plane

## Virginia

Tuned Circuit  
Harrisonburg

Radio Communications Co.  
Roanoke

## Washington

Amateur Radio Supply  
Seattle

C-COM  
Seattle

## Wisconsin

Amateur Electronic Supply  
Milwaukee

State  
of the art



by

K.V.G.

## XF-9B

### Reduce QRM with improved IF selectivity

The XF-9B crystal filter is the heart of good, modern receiver (and transmitter) designs. It is used between the mixer stage and the IC IF amplifier stage to suppress adjacent channel interference by over 100 dBs.



The XF-9B can also be used to upgrade older receiver designs which use vacuum tube or discrete transistor IF amplifier stages. **PRICE \$68.60** plus shipping.

#### Specification XF-9B

Center Frequency	9.0 MHz	Shape Factor	6:60 dB	1.8
Bandwidth	2.4 KHz		6:80 dB	2.2
Passband Ripple	-2.0 dB	Ultimate Attenuation		100 dB
Insertion Loss	-3.5 dB	Terminations:		500 ohms
				30 pF

Export Inquiries Invited

### 1296 MHz EQUIPMENT

Announcing the new 1296 MHz units  
by Microwave Modules.



Low Noise RECEIVE Converter MM1296-144  
Low Noise RECEIVE Preamplifier MM1296  
Low Power LINEAR TRANSMITTER MM1296-144  
Plus all our regular 1296 MHz items: antennas, filters, triplers.

## TRANSVERTERS FOR ATV OSCARS 7, 8 & PHASE 3

Transverters by Microwave Modules and other manufacturers can convert your existing Low Band rig to operate on the VHF & UHF bands. Models also available for 2M to 70cm and for ATV operators from Ch2/Ch3 to 70cms. Each transverter contains both a Tx up-converter and a Rx down-converter. Write for details of the largest selection available.

Prices start at \$199.95 plus \$3.50 shipping.

#### SPECIFICATIONS:

Output Power	10 W
Receiver N.F.	3 dB typ.
Receiver Gain	30 dB typ.
Prime Power	12V DC



Attention owners of the original MM432-28 models: Update your transverter to operate OSCAR 8 & PHASE 3 by adding the 434 to 436 MHz range. Mod kit including full instructions \$26.50 plus \$1.50 shipping, etc.

## ANTENNAS (FOB CONCORD, VIA UPS)

### 144-148 MHz J-SLOTS

8 OVER 8 HORIZONTAL POL. + 12.3 dBd	DB/2M	\$55.95
8 BY 8 VERTICAL POL.	DB/2M-VERT.	\$65.60
8 + 8 TWIST	8XY/2M	\$57.75



### 420-450 MHz MULTIBEAMS

For local, DX, OSCAR,  
and ATV use.

48 EL.	GAIN + 15.7 dBd 70/MBM48	\$69.95
88 EL.	GAIN + 18.5 dBd 70/MBM88	\$95.95

### UHF LOOP YAGIS

28 LOOPS	GAIN + 20 dBi	50-ohm, Type N Connector
1250-1340 MHz	1296-LY	8 ft. boom \$59.70
1650-1750 MHz	1691-LY	6 ft. boom \$64.70

Send 30¢ (2 stamps) for full details of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters	Amplifiers	SSB Transverters
Varactor Triplers	Crystal Filters	FM Transverters
Decade Pre-Scalers	Frequency Filters	VHF Converters
Antennas	Oscillator Crystals	UHF Converters

si

Spectrum  
International, Inc.  
Post Office Box 1084  
Concord, Mass. 01742, USA

# Questions and Answers

*Entries must be by letter or post card only. No telephone requests will be accepted. All entries will be acknowledged when received. Those judged to be most informative to the most Amateurs will be published. Questions must relate to Amateur Radio.*

*Readers are invited to send a card with the question they feel is most useful that appears in each issue. Each month's winner will receive a prize. We will give a prize for the most popular question of the year. In the case of two or more questions on the same subject, the one arriving the earliest will be used.*

## **congratulations to...**

WD5GMF, for his question about decibels (dB) in the September, 1980, issue of *Ham Radio Horizons*. Several readers commented on the usefulness of that question and the answer given. The subject of dB has mystified thousands of Amateurs and still shows up in discussions of electronics theory and in an exam question now and then. Thanks to WD5GMF for asking the question and thanks to those of you who took the time to comment.

## **narrow-band voice modulation**

*Please explain the narrow-band voice modulation system now being used by some Amateurs. Paul Drunen, KA4CMZ.*

This modulation system is being tried in both Amateur and commercial radio circles, with the expectation that it will allow more signals per band, or permit closer spacing of channelized communications such as vhf business, police, and aircraft. The principle of operation is to carefully shape the audio from the microphone by slicing it into essential segments, then processing those segments before they reach the modulator.

There are several natural gaps in speech; some of these gaps are

essential and some are not. One non-essential gap occurs between approximately 600 and 1,000 Hz. Speech sounds below 600 Hz are essential and preserved. Sounds above approximately 1,500 Hz up to 2,500 or 3,000, are essential and are likewise preserved. There are small gaps in this high range, and they, too, are essential for the understanding of speech, thus are preserved along with the sounds.

The sounds below 600 Hz are transmitted as is, but those in the upper band of 1,500-2,500 Hz are inverted and shifted lower in frequency, then combined with the low (250-600 Hz) audio, and fed to the modulator. This process not only closes the non-essential gap just above 600 Hz, but also reduces the total width of the audio signal to something like 250-1,600 Hz (there is an optional system that provides up to 2,100-Hz width if desired).

Additionally, the audio signal is processed for more nearly constant amplitude in the transmitter (compressed), and then expanded in the receiver, in a process called companding.

The modified audio must be fed through a special circuit in the receiver to eliminate the processing, which restores the proper gap and turns the audio "right-side-up."

At this time, the system uses sever-

al specialized ICs in the transmitter and receiver. It is undergoing many tests and evaluations of effectiveness for Amateur and commercial use.

## **recommended reading**

Harris, R.W., and Gorski, J.C., "A New Era Voice Communications," *QST*, December, 1977. Harris, R.W., and Cleveland, J.F., "A Baseband Communications System," *QST*, November, 1978 (part 1), and December, 1978 (part 2). Also, *The Radio Amateur's Handbook*, 57th edition, 1980, ARRL, Newington, Connecticut 06111, Chapter 14.

## **USB, LSB, or DSB?**


*Would you please explain the difference between USB, LSB, and Double Sideband. Stephen Serio.*

Fig. 1 will help you understand these three modes of voice communication, and how they got that way. At **A**, you see an ordinary amplitude-modulated carrier, abbreviated a-m. It is a natural outcome of the process of modulating an rf signal with a voice signal. It is made up of a carrier and two sidebands, one above and one below the carrier.

If the modulation takes place in a *balanced modulator*, the carrier is balanced out (nulled), and the result is two sidebands with no carrier, **B**.
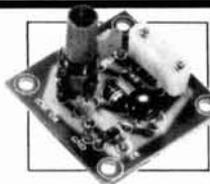
# FOR THE EXPERIMENTER

CRYSTALS & KITS/OSCILLATORS • RF MIXERS • RF AMPLIFIER • POWER AMPLIFIER



## OX OSCILLATOR

Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101.

*Specify when ordering.*


\$6.31 ea.

## MX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 170 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106.

*Specify when ordering.*

\$7.02 ea.

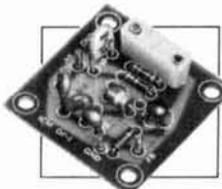

## OF-1 OSCILLATOR

Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 031108, 18 to 60 MHz, OF-1 H Cat. No. 035109.

*Specify when ordering.*



\$5.42 ea.

## PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated 3 to 30 MHz, Cat. No. 035104.

*Specify when ordering.*

\$7.34 ea.

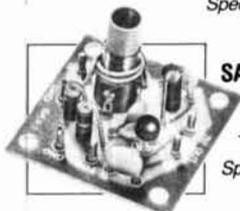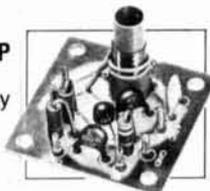

## SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive the MX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 035112. 20 to 170 MHz, Hi Kit, Cat. No. 035103.

*Specify when ordering.*


\$7.02 ea.

## BAX-1 BROADBAND AMP

General purpose amplifier which may be used as a tuned or untuned unit in RF and audio applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat. No. 035107.

*Specify when ordering.*

\$7.34 ea.

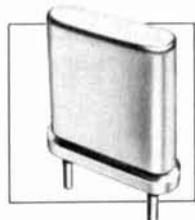

## .02% Calibration Tolerance EXPERIMENTER CRYSTALS (HC 6/U Holder)

Cat. No.	Specifications	
031080 *3 to 20 MHz	— For use in OX OSC Lo	\$6.88 ea.
031081 *20 to 60 MHz	— For use in OX OSC Hi	\$6.88 ea.
031300 *3 to 20 MHz	— For use in OF-1L OSC	\$6.88 ea.
031310 *20 to 60 MHz	— For use in OF-1H OSC	\$6.88 ea.

*\*Specify when ordering*

Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request.



INTERNATIONAL CRYSTAL MFG. CO., INC.  
10 North Lee / Oklahoma City, Okla. 73102

## Loop Antenna



Here is an exciting new device to improve your reception on 160, 80, the broadcast band, and on VLF.

It is well known that loops pick up far less noise than most other antennas. And they can null out interference. Now Palomar Engineers brings you these features and more in a compact, carefully engineered, attractive desktop package.

Unlike ordinary direction-finder loops, it tilts to match the incoming wave front. The result: Deep nulls up to 70 db. You have to listen to believe it!

Does the Loran on 160 give you a headache? The loop practically eliminates it. Broadcast station 2nd harmonic ruining your DX? Turn and tilt the loop and it's gone. Does your friend in the next block with his kilowatt block those weak ones? Use the loop and hear him fade out.

Loop nulls are very sharp on local and ground wave signals but usually are broad or nonexistent on distant skywave signals. This allows local interference to be eliminated while DX stations can still be heard from all directions.

The loops are Litz-wire wound on RF ferrite rods. They plug into the Loop Amplifier which boosts the loop signal 20 db and isolates and preserves the high Q of the loop. The tuning control peaks the loop and gives extra preselection to your receiver.

Plug-in loops are available for these bands:

- 10-40 KHz (Omega)
- 40-150 KHz (WWVB, Loran)
- 150-550 KHz (VLF)
- 540-1600 KHz (Broadcast)
- 1600-5000 KHz (160 & 80 meters)
- 5-15 MHz (HF-1)

Send for free descriptive brochure.



Loop Amplifier \$77.50; Plug-in Loop Antennas \$59.95 each (specify frequency band). To order add \$3 packing/shipping. California residents add sales tax.

# Palomar Engineers

Box 455, Escondido, CA. 92025  
Phone: [714] 747-3343



# Standing waves are a breeze!

Measuring VSWR is as simple as falling off a surfboard. Forward power up to 50 kW and reflected power down to 100 mW — and even below — are read directly from our 1000-A Directional RF Meter. A convenient chart converts them to VSWR.



Hams, 2-way and commercial broadcasters depend on THE MAINE SOURCE for 2-year-warranted RF products—quality meters, couplers and loads.

Call us, toll-free, for the name of your local distributor. Our world-wide network is ready to serve you . . . with a smile.

New England integrity and craftsmanship  
... as traditional as Maine lobster.



RAYMOND, MAINE 04071 / 207-855-4555 / 800-341-9678 / TWX 710-229-6890

# NEW!

from Barker & Williamson, Inc.

## Model 422-2 Two Meter TVI, Harmonic Filter.

A quality filter in a small package.

Power capability to 175 watts FM-AM—350 watts PEP

Size:  
3" L x 1 3/8" x 1 3/8"

SO239 Connectors

Impedance 50/75 ohms



See your Dealer or Write:

Barker & Williamson, Inc.  
10 Canal Street  
Bristol, Pa. 19007



## RADIO WAREHOUSE

No Frills, Just Low Prices



TR-7800  
\$364<sup>95</sup>

IC 255A  
W/HM-8  
\$339<sup>95</sup>

FT-480R  
\$469<sup>95</sup>

IC-260  
\$439<sup>95</sup>

IC-2AT  
\$254<sup>95</sup>

TR-9000  
\$449<sup>95</sup>

TR-2400  
\$354<sup>95</sup>

WE ALSO CARRY TEN-TEC,  
DAIWA AND MFJ

CALL OR WRITE FOR QUOTE.

P.O. BOX 2728  
DALLAS, TX 75221  
Telephone: (817) 496-9000

### COMM AUDIO PROCESSOR

SELECT - 13 POLE VOICE-FILTER OR 9 POLE 100 Hz BW FILTER  
WITH SELECTABLE FLAT SKIRTS • ADJUSTABLE TONE-TAG AND  
ANTI-PHASIC WHITE NOISE - ALL IN SYNTHESIZED BINAURAL

See HR Jan, '80 • COMPLETE SYSTEM, KITS, BOARDS - BROCHURES

Hildreth Engineering

P.O. Box 60003 Sunnyvale, CA 94088

### DIPOLE ANTENNA CONNECTOR



HYE-QUE (HQ-1) dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or \$5.95 postpaid. Companion insulators \$1.25/pr.

BUDWIG MFG. Co. PO Box 829, Ramona, CA 92065  
Ca. Res. add 6% Sales Tax

**NOT  
A  
SUBSCRIBER?  
DO IT  
TODAY!**

Use the handy card between  
pages 22 & 23

The next step is to filter out the unwanted sideband by a mechanical or crystal filter that passes only the sideband you want, C. To obtain the other sideband, you could use another filter to pass that one and reject the unwanted one. However, that's too expensive.

A simpler, and less-expensive way, is to change the frequency of the crystal that supplied the carrier for the modulator in the first place. Thus you simply shift the unwanted sideband to the other side of the filter's window, as shown at D.

To properly receive SSB, you only have to duplicate the frequency of

the carrier oscillator, and place it on the correct side of the sideband you want to hear, which will duplicate the original a-m signal minus one sideband.

## final protection

*I've used an SWR meter with various antenna tuners, and have managed to load up many types of antennas, such as random lengths of wire, zipcord, window screens, and fences. Results have often been surprisingly good. Can I be confident that a load somewhere near 50 ohms is presented to my transmitter, when it works okay, and the SWR reads below 2:1? I don't want to damage the final stage on my Argonaut. John F. Leahy, WB6CKN.*

The only time you can be reasonably sure that your transmitter is working into 50 ohms is when the reading on your SWR meter is 1:1. At any reading higher than this, the impedance at the transmitter is something else. The reading might be 1.5:1, 1.8:1, or 2:1 at the SWR meter, but what is it at the end of the piece of coax that connects to the transmitter? The apparent SWR changes with the length of the coax, and can be something entirely different a few feet down the line from the meter. Try setting up your tuner for a 2:1 reading on 10 meters. Don't touch any tuning controls, and add a 5-foot (1.5-meter) piece of coax between the tuner and the SWR meter. It will probably read something other than 2:1.

As to how your transmitter likes this sort of treatment, if it puts out reasonable power without overheating, there's no problem. Ten-Tec says that the output transistors are rugged enough to withstand an open or short circuit (but, of course, long-term operation with a very high SWR is not recommended), thus an SWR of 2:1 doesn't present any real danger.

## velocity factor

*What is velocity factor? I've seen it*

*in various antenna articles but haven't yet found a good definition. Richard Anderson.*

Velocity factor is a property of transmission lines that must be taken into account when calculating the physical length of a tuned line or a matching transformer made from the line. The velocity of a radio wave traveling down the line is less than in free space. It varies from about 0.65 for polyethylene-dielectric coaxial cables to 0.975 for open-wire (air dielectric) transmission lines.

## efficiency

*I've read about antenna tuners and Transmatches in several publications, but nothing is mentioned about their efficiency. I've noticed that most gear is listed at 50-70 per cent efficiency, so can I assume that with 100 watts dc input into a Transmatch that I'll get 50 to 75 watts output? S. Capasso, KA1ETB.*

First of all, you don't run dc input to a Transmatch or antenna tuner. Dc input numbers refer only to amplifiers or the final stage of a transmitter. A good linear amplifier, as used for SSB, would work at 40 to 60 per cent efficiency, and a class-C amplifier (for CW or fm) can sometimes get up to 70 per cent.

However, the efficiency of a passive device such as an antenna tuner is determined by the losses of the wire in its coils and the material in the toroid (if any). A good antenna tuner with air-wound coils will have very little loss — 5 per cent or less. Using a toroidal balun transformer can introduce more losses, depending on the material used and the frequency of operation, anywhere from 10 to 40 per cent. Sometimes you have to accept these losses to use an unconventional antenna, or to use one antenna on more than one band. It's better if you can design your antenna for an input impedance of 50 ohms, and do without the antenna tuner, if at all possible.

ham radio

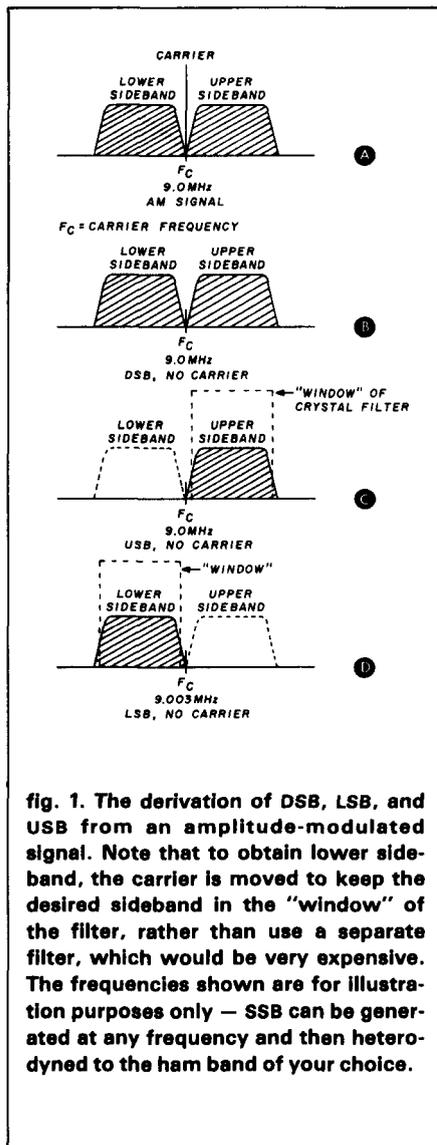


fig. 1. The derivation of DSB, LSB, and USB from an amplitude-modulated signal. Note that to obtain lower sideband, the carrier is moved to keep the desired sideband in the "window" of the filter, rather than use a separate filter, which would be very expensive. The frequencies shown are for illustration purposes only — SSB can be generated at any frequency and then heterodyned to the ham band of your choice.

# transmission-line circuit design


## Using distributed resonant circuits for VHF/UHF transmission lines

This is part 4 of a 5-part article dealing with the design of resonant transmission lines. In part 1, which appeared in *ham radio* for November, 1980, I presented the governing expressions for calculating the parameters for twelve transmission-line configurations. Programs were given using the HP-97 printer capability.

Parts 2 and 3 discussed the geometry and presented the calculator programs for solving the equations for eight of the twelve line configurations: coaxial lines; parallel plates; parallel wires in air; single wire over a plane (*ham radio*, January, 1981); circular wire between planes; parallel wires over a plane; circular wire in an open trough; parallel wires between planes/rectangular box (*ham radio*, February, 1981).

In this part of the article, the last four of the twelve line configurations are examined: circular wire in a square shield; stripline over a plane; stripline centered between parallel planes; and the helical resonator. Part 5 will provide a summary of what has been discussed and show a design example for a 2-meter amplifier.

### circular wire in a square shield

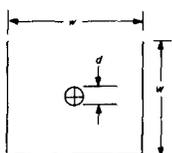

This is not a usual configuration encountered or designed, because the square cavity configuration imposes complexities due to its geometry. However, it is often chosen in the design of production filters and duplexers because dip-braze techniques can be readily used, mitigating other difficulties. The formulation yielding  $Z_0$  (reference 5) is:

$$Z_0 = \frac{59.96}{\sqrt{\epsilon_r}} \ln \left( 1.0787 \frac{w}{d} \right) \quad (41)$$

where  $Z_0$  = transmission-line impedance (ohms)

$\epsilon_r$  = dielectric constant

$w$  = width of each side

$d$  = diameter of center conductor

Fig. 18 shows  $Z_0$  versus  $w/d$  for common values. Table 35 is the HP-67/97 program for calculating the unknown from the known variables. Table 36 identifies the storage registers used. Table 37 shows how the program is controlled.

table 35. HP-67/97 program for calculating  $Z_0$  and  $w/d$  for a wire in a square shield:

step	HP-97 key	HP-97 code	step	HP-97 key	HP-97 code
001	*LBLA	21 11	036	STO5	35 05
002	STO0	35 00	037	5	05
003	$\sqrt{X}$	54	038	9	09
004	STO1	35 01	039	.	- 62
005	RTN	24	040	9	09
006	*LBLB	21 12	041	6	06
007	STO2	35 02	042	+	- 24
008	R1	- 31	043	RCL1	36 01
009	STO3	35 03	044	X=0?	16-43
010	RCL2	36 02	045	GSB8	23 08
011	+	- 24	046	x	- 35
012	STO4	35 04	047	e <sup>x</sup>	33
013	*LBL1	21 01	048	1	01
014	1	01	049	.	- 62
015	.	- 62	050	0	00
016	0	00	051	7	07
017	7	07	052	8	08
018	8	08	053	7	07
019	7	07	054	+	- 24
020	x	- 35	055	STO4	35 04
021	LN	32	056	R/S	51
022	5	05	057	*LBLD	21 14
023	9	09	058	STO4	35 04
024	.	- 62	059	GTO1	22 01
025	9	09	060	*LBL9	21 09
026	6	06	061	1	01
027	x	- 35	062	STO1	35 01
028	STO6	35 06	063	RCL6	36 06
029	RCL1	36 01	064	RCL1	36 01
030	X=0?	16-43	065	RTN	24
031	GSB9	23 09	066	*LBL8	21 08
032	+	- 24	067	1	01
033	STO5	35 05	068	STO1	35 01
034	R/S	51	069	RTN	24
035	*LBLC	21 13	070	R/S	51

By H.M. Meyer, Jr., W6GGV, 29330 Whitley Collins Drive, Rancho Palos Verdes, California 90274


**table 36. Register contents for HP-67/97 program for calculating  $Z_0$  and  $w/d$  for a wire in a square shield.**

STO 0	$\epsilon_r$
STO 1	$\sqrt{\epsilon_r}$
STO 2	$d$
STO 3	$w$
STO 4	$w/d$
STO 5	$Z_0$
STO 6	INTERIM


**table 37. HP-67/97 program control for calculating  $Z_0$  and  $w/d$  for a wire in a square shield:**

calculates	$\sqrt{\epsilon_r}$	
enter	$\epsilon_r$	press A
calculates	$Z_0$	
enter	$w$	press ENTER
enter	$d$	press B
calculates	$w/d$	
enter	$Z_0$	press C
calculates	$Z_0$	
enter	$w/d$	press D

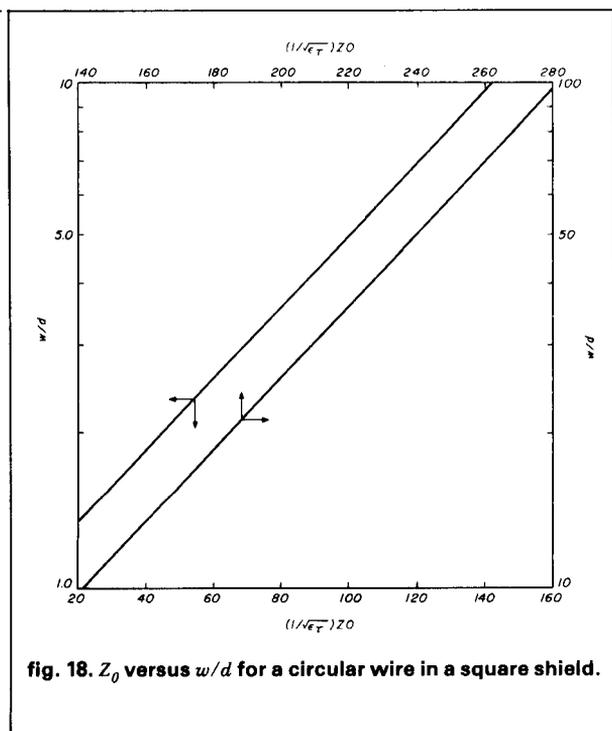Note: If no value for  $\epsilon_r$  is entered, program assumes  $\epsilon_r = 1 = \text{air}$ .



### stripline over a plane

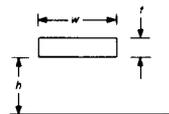

This is perhaps one of the more useful transmission line configurations presently in use. Its applications are primarily stimulated by solid-state technology and the subsequent extensive use of microwave integrated circuits. One original formula-

tion by S.B. Cohn (reference 6) was subsequently followed by M.V. Schneider (reference 7). The most accurate formulation known is by H.A. Wheeler (reference 3), and that is used here.

**Table 38** identifies the method for calculating strip width,  $w$ , with  $h$ ,  $t$ ,  $Z_0$ , and  $\epsilon_r$  known. The formulations from reference 3 are:

$$\frac{w'}{h} = 8 \sqrt{\left[ e \exp\left(\frac{Z_0}{42.4} \sqrt{\epsilon_r + 1}\right) - 1 \right] \left[ \frac{7 + 4/\epsilon_r}{11} + \frac{1 + 1/\epsilon_r}{0.81} \right]} \left[ e \exp\left(\frac{Z_0}{42.4} \sqrt{\epsilon_r + 1}\right) - 1 \right] \quad (42)$$

$$\frac{\Delta w}{t} = \frac{1}{\pi} \ln \frac{4e}{\sqrt{\left(\frac{t}{h}\right)^2 + \left(\frac{1/\pi}{w'/t - 0.26}\right)^2}} \quad (43)$$

$$\Delta w' = \frac{1 + 1/\epsilon_r}{2} \Delta w \quad (44)$$

$$w = w' - \Delta w' \quad (45)$$

For the calculation of line  $Z_0$  the method in **table 39** is used. The formulations from reference 3 are:

$$\frac{\Delta w}{t} = \frac{1}{\pi} \ln \frac{4e}{\sqrt{\left(\frac{t}{h}\right)^2 + \left(\frac{1/\pi}{w/t + 1.10}\right)^2}} \quad (46)$$

$$\Delta w' = \frac{1 + 1/\epsilon_r}{2} \Delta w \quad (47)$$

$$w' = w + \Delta w' \quad (48)$$

$$Z_0 = \frac{42.4}{\sqrt{\epsilon_r + 1}} \ln \left\{ 1 + \left(\frac{4h}{w'}\right) \left[ \left(\frac{14 + 8/\epsilon_r}{11}\right) \left(\frac{4h}{w'}\right) + \sqrt{\left(\frac{14 + 8\epsilon_r}{11}\right)^2 \left(\frac{4h}{w'}\right)^2 + \left(\frac{1 + 1/\epsilon_r \pi}{2}\right)^2} \right] \right\} \quad (49)$$

**table 38. Method of calculating strip width:**

1. Specify  $h$ ,  $t$ ,  $Z_0$ , and  $\epsilon_r$  (from **fig. 1K**).
2. Determine  $w/h$  (from **eq. 42** — yields  $w'$ ).
3. Determine  $\Delta w$  (from **eq. 43**).
4. Determine  $\Delta w'$  (from **eq. 44**).
5. Determine  $w$  (from **eq. 45**).

**table 39. Method of calculating line  $Z_0$ :**

1. Specify  $h$ ,  $t$ ,  $\epsilon_r$ , and  $w$ .
2. Determine  $\Delta w$  (from **eq. 46**).
3. Determine  $\Delta w'$  (from **eq. 47**).
4. Determine  $w'$  (from **eq. 48**).
5. Determine  $Z_0$  (from **eq. 49**).

\*The expression in parentheses following *exp* indicates the power to which  $e$  is raised.

table 40. HP-67/97 program for calculating  $w$  and  $Z_0$  for a stripline over a plane:

step	HP-97 key	HP-97 code									
001	*LBLA	21 11	056	STO9	35 09	111	*LBL2	21 02	166	1	01
002	STO0	35 00	057	RCL1	36 01	112	RCL4	36 04	167	4	04
003	RTN	24	058	1/X	52	113	RCL3	36 03	168	+	-55
004	*LBLB	21 12	059	1	01	114	÷	-24	169	1	01
005	STO1	35 01	060	+	-55	115	1	01	170	1	01
006	RTN	24	061	.	-62	116	.	-62	171	+	-24
007	*LBLC	21 13	062	8	08	117	1	01	172	X <sup>2</sup>	53
008	STO2	35 02	063	1	01	118	+	-55	173	RCL8	36 08
009	RTN	24	064	÷	-24	119	Pi	16-24	174	4	04
010	*LBLD	21 14	065	RCL8	36 08	120	x	-35	175	x	-35
011	STO3	35 03	066	+	-55	121	1/X	52	176	X <sup>2</sup>	53
012	RTN	24	067	√X	54	122	X <sup>2</sup>	53	177	x	-35
013	*LBL E	21 15	068	RCL7	36 07	123	STO7	35 07	178	RCL7	36 07
014	STO4	35 04	069	÷	-24	124	RCL3	36 03	179	+	-55
015	RTN	24	070	8	09	125	RCL2	36 02	180	√X	54
016	*LBL a	21 16 11	071	x	-35	126	÷	-24	181	STO7	35 07
017	STO I	35 46	072	STO6	35 06	127	X <sup>2</sup>	53	182	8	08
018	GSB;	23 45	073	RCL2	36 02	128	RCL7	36 07	183	RCL1	36 01
019	*LBL9	21 09	074	x	-35	129	+	-55	184	÷	-24
020	RCL1	36 01	075	STOC	35 13	130	√X	54	185	1	01
021	1/X	52	076	RCL3	36 03	131	1/X	52	186	4	04
022	1	01	077	÷	-24	132	1	01	187	+	-55
023	+	-55	078	.	-62	133	e <sup>x</sup>	33	188	1	01
024	2	02	079	2	02	134	x	-35	189	1	01
025	÷	-24	080	6	06	135	4	04	190	÷	-24
026	RCL5	36 05	081	-	-45	136	x	-35	191	RCL8	36 08
027	x	-35	082	Pi	16-24	137	LN	32	192	4	04
028	STO A	35 11	083	x	-35	138	Pi	16-24	193	x	-35
029	RTN	24	084	1/X	52	139	1/X	52	194	x	-35
030	*LBL1	21 01	085	X <sup>2</sup>	53	140	x	-35	195	RCL7	36 07
031	RCL1	36 01	086	RCL3	36 03	141	STOB	35 12	196	+	-55
032	1	01	087	RCL2	36 02	142	RCL3	36 03	197	RCL8	36 08
033	+	-55	088	+	-24	143	x	-35	198	4	04
034	√X	54	089	X <sup>2</sup>	53	144	STO5	35 05	199	x	-35
035	RCL0	36 00	090	+	-55	145	GSB9	23 09	200	x	-35
036	x	-35	091	√X	54	146	RCL4	36 04	201	1	01
037	4	04	092	1/X	52	147	+	-55	202	+	-55
038	2	02	093	4	04	148	STOC	35 13	203	LN	32
039	.	-62	094	x	-35	149	RCL1	36 01	204	STO7	35 07
040	4	04	095	1	01	150	1/X	52	205	RCL1	36 01
041	÷	-24	096	e <sup>x</sup>	33	151	1	01	206	1	01
042	e <sup>x</sup>	33	097	x	-35	152	+	-55	207	+	-55
043	1	01	098	LN	32	153	2	02	208	√X	54
044	-	-45	099	Pi	16-24	154	+	-24	209	1/X	52
045	STO7	35 07	100	÷	-24	155	Pi	16-24	210	4	04
046	4	04	101	STO9	35 09	156	X <sup>2</sup>	53	211	2	02
047	RCL1	36 01	102	RCL3	36 03	157	x	-35	212	.	-62
048	+	-24	103	x	-35	158	STO7	35 07	213	4	04
049	7	07	104	STO5	35 05	159	RCL2	36 02	214	x	-35
050	+	-55	105	GSB9	23 09	160	RCLC	36 13	215	RCL7	36 07
051	1	01	106	CHS	-22	161	+	-24	216	x	-35
052	1	01	107	RCLC	36 13	162	STO8	35 08	217	STO0	35 00
053	÷	-24	108	+	-55	163	8	08	218	R / b s	51
054	RCL7	36 07	109	STO4	35 04	164	RCL1	36 01			
055	x	-35	110	R/S	51	165	÷	-24			

**Table 40** is the HP-67/97 program used to calculate  $Z_0$  and  $w$ . **Table 41** identifies the storage registers used, and **table 42** describes how the program is controlled.

A sample problem might readily explain how the program is used. Enter line  $Z_0$ , 50 ohms; dielectric constant,  $\epsilon_r$ , 2.5; height,  $h$ , 1.0 mm; and thickness,  $t$ , 0.1 mm. Calculate the stripline width as indicated in **table 42**,  $w = 2.7038$  mm. Using this value for  $w$ , calculate  $Z_0$  from the same parameters,  $Z_0 = 49.9974$

**table 41. Register contents for HP-67/97 program for calculating  $w$  and  $Z_0$  for a stripline over a plane:**

STO 0	$Z_0$	STO 7	INTERIM
STO 1	$k$	STO 8	INTERIM
STO 2	$h$	STO 9	$\Delta w/h$
STO 3	$t$	STO A	$\Delta w'$
STO 4	$w$	STO B	$\Delta w/t$
STO 5	$\Delta w$	STO C	$w'$
STO 6	$w'/h$	STO D	$h/w'$


**table 42. HP-67/97 program control for calculating  $w$  and  $Z_0$  for a stripline over a plane:**

enter $Z_0$	press A
enter $\epsilon_r$	press B
enter $h$	press C
enter $t$	press D
enter $w$	press E

Enter any four of the above; select one of the following parameters:

1 -  $w$   
2 -  $Z_0$

and press fa.

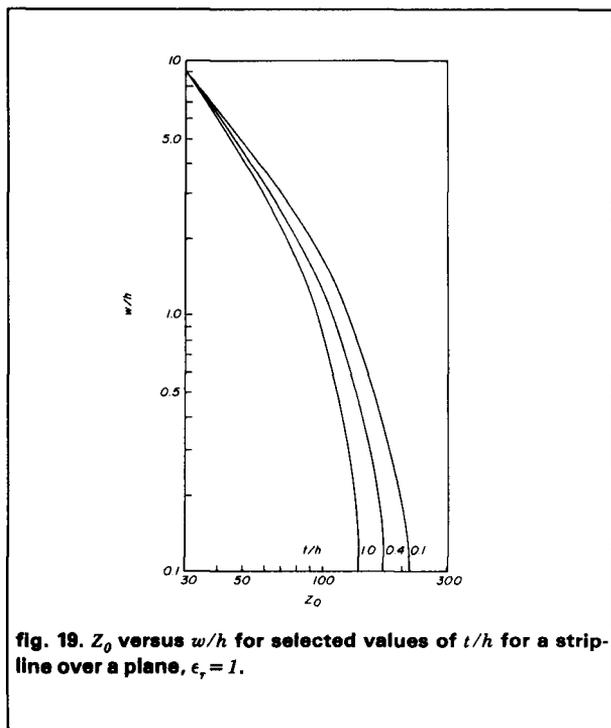

**fig. 19.  $Z_0$  versus  $w/h$  for selected values of  $t/h$  for a stripline over a plane,  $\epsilon_r = 1$ .**


ohms, which is in good agreement with the originally specified 50 ohms.\*

**table 43. Values of  $Z_0$  for  $w/h$  versus  $t/h$  for various values of  $\epsilon_r$  for a stripline over a plane:**

w/h	t/h			
	0.1	0.2	0.4	1.0
$\epsilon_r = 1.0$				
0.1	212.83	190.9	166.47	135.65
0.4	161.66	151.47	138.21	118.19
0.8	137.49	123.38	115.17	101.71
1.0	124.98	113.56	106.73	95.26
4	56.92	54.75	53.31	50.60
8	34.3	33.56	33.04	32.04
10	28.79	28.27	27.90	27.19
$\epsilon_r = 4$				
0.1	137.60	126.19	112.69	94.68
0.4	100.17	95.59	89.26	79.01
0.8	78.11	75.59	71.94	65.57
1.0	70.88	68.84	65.87	60.58
4	31.21	30.85	30.29	29.22
8	18.36	18.24	18.05	17.68
10	15.23	15.20	15.07	14.81
$\epsilon_r = 4.6$				
0.1	130.145	119.501	106.856	89.932
0.4	94.533	90.279	84.411	74.853
0.8	73.616	71.281	67.907	61.996
1.0	66.766	64.887	62.140	57.240
4	29.288	28.955	28.445	27.460
8	17.195	17.084	16.912	16.571
10	14.306	14.230	14.111	13.875
$\epsilon_r = 8$				
0.1	102.94	94.87	85.17	72.05
0.4	74.28	71.12	66.73	59.50
0.8	57.62	55.90	53.40	48.98
1.0	52.18	50.80	48.77	45.12
4	22.64	22.40	22.03	21.31
8	13.21	13.13	13.01	12.76
10	10.97	10.92	10.83	10.66
$\epsilon_r = 12$				
0.1	85.76	79.16	71.21	60.39
0.4	61.69	59.14	55.58	49.68
0.8	47.76	46.38	44.36	40.78
1.0	43.22	42.12	40.48	37.53
4	18.65	18.46	18.16	17.59
8	10.86	10.79	10.69	10.50
10	9.01	8.96	8.90	8.76
$\epsilon_r = 16$				
0.1	75.04	69.33	62.42	53.01
0.4	53.89	51.69	48.62	43.52
0.8	41.69	40.50	38.76	35.67
1.0	37.71	36.76	35.35	32.81
4	16.23	16.06	15.81	15.32
8	9.43	9.38	9.29	9.13
10	7.82	7.79	7.73	7.61

\*Reference 3 sample problem is the same as that presented here, but the result for  $w$  is given as 2.75 mm. Since the reverse procedure here produces a  $Z_0$  of 49.9974 ohms, which is in good agreement with the initial value of 50 ohms specified, perhaps a typographical error accounts for this discrepancy.

The HP-67/97 program was written in this manner to provide a built-in self-check. No graphs are provided for this configuration except for  $\epsilon_r = 1$  in fig. 19. This is because their number is too numerous to present all of the variables. Table 43, for which the value of  $Z_0$  is given for useful values of  $w/h$  versus  $t/h$ , also provides for values of  $\epsilon_r$  of 1, 4, 8, 12, and 16. From these data additional graphs can be prepared covering specific ranges of interest.

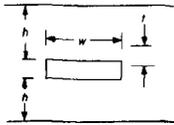

### stripline centered between parallel planes

Previously, the impedance of a stripline centered between parallel planes could be determined only from the work published in reference 6 and a subsequent distillation in reference 4. However, H.A. Wheeler, in 1978 (reference 2), provided an empirically derived formulation permitting direct synthesis with excellent accuracy. This is done in much the same way as for a stripline over a plane previously discussed.

$$\frac{\Delta w}{t} = \frac{1}{\pi} \ln \frac{e}{\sqrt{\left(\frac{1}{\frac{4h}{t} + 1}\right)^2 + \left(\frac{1}{4\pi \frac{w'}{t} - 0.26}\right)^m}} \quad (50)$$

$$\frac{w'}{h} = \frac{16}{\pi} \frac{\sqrt{(e^{4\pi r} - 1) + 1.568}}{(e^{4\pi r} - 1)} \quad (51)$$

$$w = w' - w \quad (52)$$

where  $r = \frac{\sqrt{\epsilon_r} Z_0}{377} \quad (53)$

$$m = \frac{6}{3 + \frac{t}{h}} \quad (54)$$

table 44. Method of calculating stripline width:

1. Specify  $h, t, Z_0,$  and  $\epsilon_r.$
2. Determine  $\frac{\Delta w}{t}$  (from eq. 50).
3. Determine  $\frac{w'}{h}$  (from eq. 51).
4. Determine  $w$  (from eq. 52).

table 45. Method of calculating stripline  $Z_0$ :

1. Determine  $\frac{\Delta w}{t}$  (from eq. 55).
2. Determine  $w'$  (from eq. 56).
3. Determine  $Z_0$  (from eq. 57).

When it is desired to calculate  $Z_0$  with  $h, t, w,$  and  $\epsilon_r$  known, the method is described in table 45. The formulation used to calculate  $Z_0$  is:

$$\frac{\Delta w}{t} = \frac{\ln e}{\pi} \frac{1}{\sqrt{\left(\frac{1}{\frac{4h}{t} + 1}\right)^2 + \left(\frac{1}{4\pi \frac{w'}{t} + 1.1}\right)^m}} \quad (55)$$

$$w' = w + \Delta w \quad (56)$$

$$Z_0 = \frac{30}{\sqrt{\epsilon_r}} \ln \left[ 1 + \frac{1}{2} \left( \frac{16h}{\pi w'} \right) \left[ \left( \frac{16h}{\pi w'} \right) + \sqrt{\left( \frac{16h}{\pi w'} \right)^2 + 6.27} \right] \right] \quad (57)$$

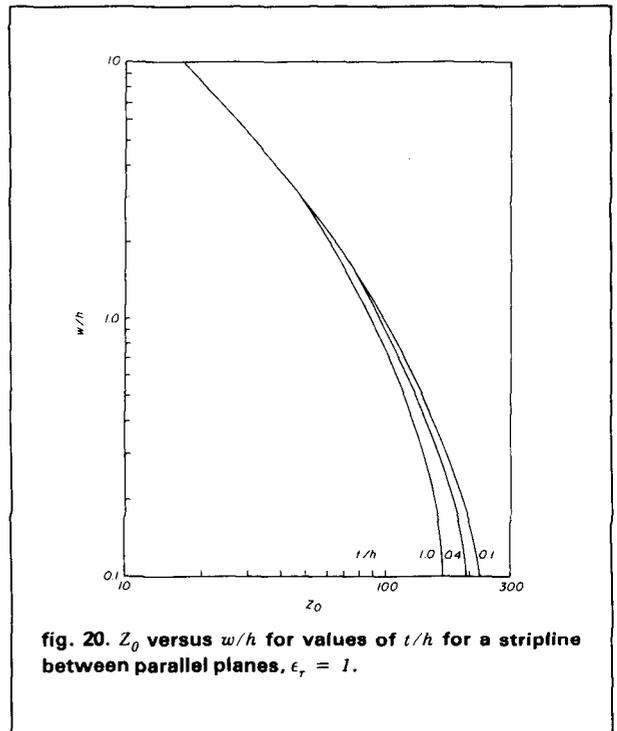


fig. 20.  $Z_0$  versus  $w/h$  for values of  $t/h$  for a stripline between parallel planes,  $\epsilon_r = 1.$

where  $m$  is defined in eq. 54.

Table 46 is an HP-67/97 program for calculating  $Z_0$  and  $w.$  Table 47 identifies the storage registers used, and table 48 describes how the program is controlled.

A sample problem was run using  $Z_0 = 50, \epsilon_r = 1, h = 1,$  and  $t = 0.0625.$  The  $w$  yielded was 2.7687. The reverse was run using the  $w$  just calculated. The resulting  $Z_0$  was 51.31, which is within the limits described in reference 2.

Fig. 20 displays  $w/h$  versus various values of  $t/h$  and the resulting  $Z_0$  for  $\epsilon_r = 1;$  that is, air. Table 49 provides the same data for various values of  $\epsilon_r,$  which are not plotted.

table 46. HP-67/97 program for calculating  $w$  and  $Z_0$  for a stripline between ground planes:

step	HP-97 key	HP-97 code									
001	*LBLA	21 11	052	+	- 24	103	R/S	51	154	STO9	35 09
002	STO0	35 00	053	1	01	104	*LBL9	21 09	155	1	01
003	RTN	24	054	6	06	105	RCL5	36 05	156	6	06
004	*LBLB	21 12	055	x	- 35	106	3	03	157	Pi	16-24
005	DSP4	- 63 04	056	Pi	16-24	107	+	- 55	158	+	- 24
006	$\sqrt{X}$	54	057	+	- 24	108	1/X	52	159	RCL3	36 03
007	STO1	35 01	058	STO8	35 08	109	6	06	160	x	- 35
008	RTN	24	059	RCL3	36 03	110	x	- 35	161	RCL9	36 09
009	*LBL8	21 08	060	x	- 35	111	STO6	35 06	162	+	- 24
010	RCL0	36 00	061	STO9	35 09	112	RTN	24	163	X <sup>2</sup>	53
011	x	- 35	062	RCL4	36 04	113	*LBL2	21 02	164	6	06
012	3	03	063	+	- 24	114	RCL8	36 13	165	.	- 62
013	7	07	064	.	- 62	115	RCL4	36 04	166	2	02
014	7	07	065	2	02	116	+	- 24	167	7	07
015	+	- 24	066	6	06	117	1	01	168	+	- 55
016	STO2	35 02	067	-	- 45	118	.	- 62	169	$\sqrt{X}$	54
017	RTN	24	068	Pi	16-24	119	1	01	170	STOA	35 11
018	*LBLC	21 13	069	4	04	120	-	- 55	171	RCL3	36 03
019	STO3	35 03	070	x	- 35	121	Pi	16-24	172	RCL9	36 09
020	RTN	24	071	x	- 35	122	4	04	173	+	- 24
021	*LBLD	21 14	072	1/X	52	123	x	- 35	174	STOE	35 15
022	STO4	35 04	073	RCL6	36 06	124	1/X	52	175	1	01
023	RCL3	36 03	074	Y <sup>x</sup>	31	125	GSB9	23 09	176	6	06
024	+	- 24	075	STOA	35 11	126	RCL6	36 06	177	Pi	16-24
025	STO5	35 05	076	RCL3	36 03	127	Y <sup>x</sup>	31	178	+	- 24
026	GSB9	23 09	077	4	04	128	STOA	35 11	179	x	- 35
027	R/S	51	078	x	- 35	129	RCL3	36 03	180	RCLA	36 11
028	*LBLa	21 16 11	079	RCL4	36 04	130	4	04	181	+	- 55
029	STOI	35 46	080	+	- 24	131	x	- 35	182	STOA	35 11
030	GSB1	23 45	081	1	01	132	RCL4	36 04	183	RCLE	36 15
031	*LBL E	21 15	082	+	- 55	133	+	- 24	184	1	01
032	STOC	35 13	083	1/X	52	134	1	01	185	6	06
033	RTN	24	084	X <sup>2</sup>	53	135	+	- 55	186	Pi	16-24
034	*LBL1	21 01	085	RCLA	36 11	136	1/X	52	187	+	- 24
035	GSB8	23 08	086	+	- 55	137	X <sup>2</sup>	53	188	x	- 35
036	Pi	16-24	087	$\sqrt{X}$	54	138	RCLA	36 11	189	2	02
037	4	04	088	1/X	52	139	+	- 55	190	+	- 24
038	x	- 35	089	1	01	140	$\sqrt{X}$	54	191	RCLA	36 11
039	x	- 35	090	e <sup>x</sup>	33	141	1/X	52	192	x	- 35
040	e <sup>x</sup>	33	091	x	- 35	142	1	01	193	1	01
041	1	01	092	LN	32	143	e <sup>x</sup>	33	194	+	- 55
042	-	- 45	093	Pi	16-24	144	x	- 35	195	LN	32
043	STO7	35 07	094	+	- 24	145	LN	32	196	3	03
044	1	01	095	STOB	35 12	146	Pi	16-24	197	0	00
045	.	- 62	096	RCL4	36 04	147	+	- 24	198	x	- 35
046	5	05	097	x	- 35	148	STOB	35 12	199	RCL1	36 01
047	6	06	098	STOC	35 13	149	RCL4	36 04	200	+	- 24
048	8	08	099	CHS	- 22	150	x	- 35	201	STO0	35 00
049	+	- 55	100	RCL9	36 09	151	STOD	35 14	202	R/S	51
050	$\sqrt{X}$	54	101	+	- 55	152	RCLC	36 13			
051	RCL7	36 07	102	STOD	35 14	153	+	- 55			

**table 47. Register contents for HP-67/97 program for calculating  $w$  and  $Z_0$  for stripline between ground planes:**

STO 0	$Z_0$	STO 8	$w'/h$
STO 1	$\sqrt{\epsilon_r}$	STO 9	$w'$
STO 2	$r$	STO A	INTERIM CALC
STO 3	$h$	STO B	$\Delta w/t$
STO 4	$t$	STO C	$w$
STO 5	$t/h$	STO D	$\Delta w$
STO 6	$m$	STO E	$h/w'$
STO 7	$e^{4\pi r}$		

**table 48. HP-67/97 program control for calculating  $w$  and  $Z_0$  for a stripline between ground planes:**


enter $Z_0$	press A
enter $\epsilon_r$	press B
enter $h$	press C
enter $t$	press D
enter $w$	press E

Enter any four of the above; select one of the following parameters,

$w$  press 1

$Z_0$  press 2

and press fa.

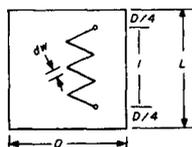

### helical resonator

Helical resonators are a form of transmission line extensively used in vhf/uhf applications. The major advantage is high unloaded  $Q$  in a very small physical space, thus permitting the realization of compact filters in this frequency spectrum.

Using the reasonably accurate, simple formulation presented in references 4 and 8, an HP-67/97 program was written permitting the design to be realized. Reference 9 provides a detailed design procedure and analysis.

The helical resonator configuration is shown in fig. 21. The method for calculating the desired dimensions is given in table 50. The detailed program steps are shown in table 51 with the storage-register contents identified in table 52. Program control is shown in table 53.

A sample problem was run. The line  $Z_0$  was specified at 70 ohms at 144 MHz, and all the resonator parameters were determined:  $D = 0.97$  inch,  $d = 0.53$

<b>table 52. Register contents for HP-67/97 program for calculating helical-resonator parameters.</b>	STO 1	$Z_0$
	STO 2	$F$
	STO 3	$D$
	STO 4	$d$
	STO 5	$L$
	STO 6	$n$
	STO 7	$Q_{\mu}$ circular
	STO 8	$Q_{\mu}$ square
	STO 9	PITCH

inch,  $L = 1.46$  inches,  $n = 13.57$  turns,  $Q_{\mu}$  circular = 583, and  $Q_{\mu}$  square = 700. Where square and circular, refer to the outside cavity configuration.

**table 49. Values of  $Z_0$  for  $w/h$  versus  $t/h$  for various values of  $\epsilon_r$  for a stripline between parallel planes:**

w/h	t/h			
	0.1	0.2	0.4	1.0
$\epsilon_r = 1.0$				
0.1	229.34	221.95	206.47	166.70
0.4	151.45	149.38	144.46	127.64
0.8	112.06	111.05	108.57	99.43
1.0	99.79	99.00	97.06	89.77
4	38.33	38.21	37.93	36.78
8	21.14	21.12	21.02	20.66
10	17.29	17.26	17.21	16.97
$\epsilon_r = 4$				
0.1	114.67	110.97	103.24	83.35
0.4	75.72	74.69	72.23	63.82
0.8	56.03	55.53	54.29	49.72
1.0	49.89	49.50	48.53	44.88
4	19.16	19.11	18.96	18.39
8	10.57	10.55	10.51	10.33
10	8.64	8.63	8.60	8.48
$\epsilon_r = 8$				
0.1	81.08	78.47	73.00	58.94
0.4	53.54	52.82	51.10	45.13
0.8	39.62	39.26	38.39	35.15
1.0	35.28	35.00	34.32	31.74
4	13.55	13.51	13.41	13.00
8	7.47	7.46	7.43	7.31
10	6.11	6.10	6.08	6.00
$\epsilon_r = 12$				
0.01	94.71	85.72	73.46	53.84
0.04	79.58	75.25	67.52	51.71
0.1	66.21	64.07	59.60	48.12
0.4	43.72	43.12	41.70	36.85
0.8	32.35	32.06	31.34	28.70
1.0	28.81	28.58	28.02	25.91
4	11.07	11.03	10.95	10.62
8	6.10	6.09	6.07	5.97

**table 50. Method of calculating helical-resonator parameters:**

1. Specify $Z_0$ (ohms) and frequency (MHz).
2. Calculate $D$ , $d$ , $L$ , $n$ , $Q_{\mu}$ circular, $Q_{\mu}$ square, and coil pitch from the equations below.
$D = \frac{9800}{F Z_0}$
$d = 0.55D$
$L = 1.5D$
$n = \frac{1900}{F D}$
$Q_{\mu}$ circular = $50\sqrt{F D}$
$Q_{\mu}$ square = $1.2 Q_{\mu}$
coil pitch = $\frac{D^2 F}{2300} = \frac{L \cdot D / 2}{n}$

table 51. HP-67/97 program for calculating helical resonator parameters:

step	HP-97 key	HP-97 code	step	HP-97 key	HP-97 code
001	*LBLA	21 11	041	x	- 35
002	STO1	35 01	042	1/X	52
003	RTN	24	043	1	01
004	*LBLB	21 12	044	9	09
005	STO2	35 02	045	0	00
006	RTN	24	046	0	00
007	*LBLa	21 16 11	047	x	- 35
008	STO1	35 46	048	STO6	35 06
009	GSB1	23 45	049	R/S	51
010	*LBL1	21 01	050	*LBL5	21 05
011	RCL1	36 01	051	RCL2	36 02
012	RCL2	36 02	052	$\sqrt{X}$	54
013	x	- 35	053	RCL3	36 03
014	1/X	52	054	x	- 35
015	9	09	055	5	05
016	8	08	056	0	00
017	0	00	057	x	- 35
018	0	00	058	STO7	35 07
019	x	- 35	059	R/S	51
020	STO3	35 03	060	*LBL6	21 06
021	R/S	51	061	RCL7	36 07
022	*LBL2	21 02	062	1	01
023	RCL3	36 03	063	.	- 62
024	.	- 62	064	2	02
025	5	05	065	x	- 35
026	5	05	066	STO8	35 08
027	x	- 35	067	R/S	51
028	STO4	35 04	068	*LBL7	21 07
029	R/S	51	069	RCL3	36 03
030	*LBL3	21 03	070	X <sup>2</sup>	53
031	RCL3	36 03	071	RCL2	36 02
032	1	01	072	x	- 35
033	.	- 62	073	2	02
034	5	05	074	3	03
035	x	- 35	075	0	00
036	STO5	35 05	076	0	00
037	R/S	51	077	+	- 24
038	*LBL4	21 04	078	STO9	35 09
039	RCL2	36 02	079	R/S	51
040	RCL3	36 03			

## acknowledgments

Comments by S. Harrison, WB6PKA, Dr. R.M. Searing, and T.C. McDermott, III, N5EG, are gratefully acknowledged. The most valuable contributions were provided by B.L. Reardon, to whom the author is singularly indebted.


## references

- H.A. Wheeler, "Transmission Line Properties of a Stripline Between Parallel Planes," *IEEE Professional Group on Microwave Theory and Techniques*, Volume MIT 26 No. 11, November, 1978, pages 866-876.
- H.A. Wheeler, "Transmission Line Properties of a Strip on a Dielectric Sheet on a Plane," *IEEE Transactions on Microwave Theory and Techniques*, Volume MIT 25, August, 1977, pages 631-647.

table 53. HP-67/97 program control for calculating helical resonator parameters:

enter $Z_0$	press A
enter $F_{MHz}$	press B
Enter both of the above; select one of the following parameters:	
$D$	press 1
$d$	press 2
$L$	press 3
$n$	press 4
$Q_{\mu}$ circular	press 5
$Q_{\mu}$ square	press 6
Pitch	press 7

and press fa.

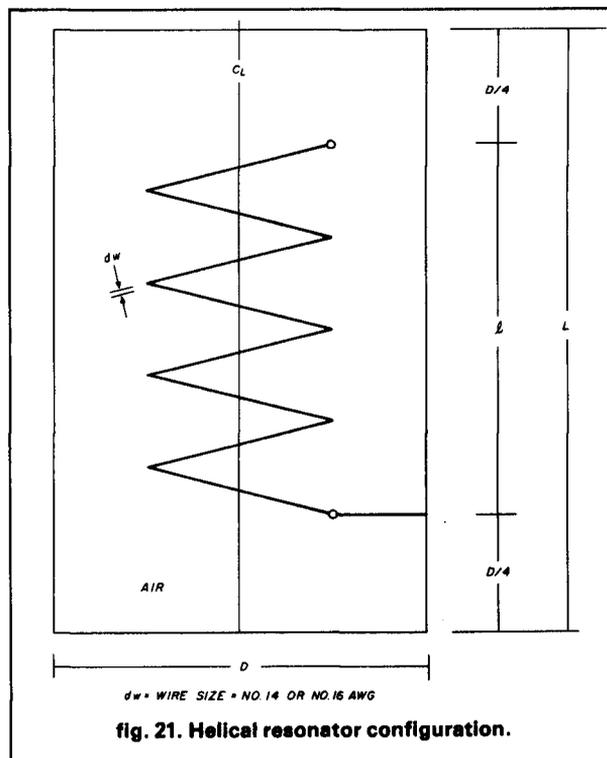

- Reference Data for Radio Engineers, ITT Corporation, 5th Edition, 1968 (included in subsequent editions).
- S.B. Cohn, *Microwave Journal*, November, 1969, page 22.
- S.B. Cohn, "Problems in Strip Transmission Lines," *IRE Professional Group on Microwave Theory and Techniques*, Volume MIT 3, March, 1955, pages 119-126.
- M.V. Schnieder, "Microstrip Lines for Microwave Integrated Circuits," *Bell System Technical Journal*, Volume 48, May, 1969, pages 1421-1444.
- D.S. Evans, et. al., *UHF Handbook*, Radio Society of Great Britain, 3rd Edition, London, England, 1976, pages 3-7.
- Anatol I. Zverev, *Handbook of Filter Synthesis*, John Wiley and Sons, 1967.

## bibliography

- Bahl, Dr. K.J., "Use Exact Methods for Microstrip Design," *Microwaves*, December, 1978, pages 61-62.
- Fisk, J.R., W1HR, "Microstrip Transmission Lines," *ham radio*, January, 1978, page 28.
- Gardioli, F.E., "HP-65 Program computes Microstrip Impedance," *Microwaves*, December, 1977, pages 186-187.
- "Letters to the Editor," *Microwave Systems News*, December, 1978, pages 13-14.
- Murdock, B.K., *Handbook of Electronics Design and Analysis Procedures Using Programmable Calculators*, Van Nostrand Reinhold, 1979.

ham radio



# UNADILLA

FULL POWER - QUALITY

HAM ANTENNA ACCESSORIES  
at your dealer

the Big Signal  
W2AU  
Balun



LONDON:  
VICTORIA:  
CONCEPCION:  
BUENOS AIRES:  
COL. ANAHUAC:  
HELSINKI:  
AUSTRIA  
FRANCE  
GERMANY

AMCOMM 01 804 1166  
Scalar 725 9677  
Telecom Trans Chile 25471  
Multi-Radio 773-1266  
Radiac 2-50-32-40  
Erikoismediat (90) 611258  
Renox Telex: 76021  
SFL (90) 5339 40  
Williges (0421) 504021

HAMS - call for our  
free catalog PC-80

DEALERS - join over 400  
dealers world-wide. Call  
us today for no-risk deal.

HAMFEST MANAGERS -  
UNADILLA cooperates!  
Call us.

US - TOLL-FREE 1-800-448-1666  
NY/Hawaii/Alaska/Canada -  
COLLECT 1-315-437-3953  
TWX - 710-541-0493

Ask for Bonnie, or Emily.

For over 20 years, the choice  
of Hams, Armed Forces and  
Commercial Communications - world-wide.

the Old reliable  
W2VS Traps



"HELICAN-10"

10-Meter  
Indoor  
Helix  
Antenna

- Lo-Pass Filter 2000W
- Quad Parts
- Baluns / Traps
- Insulators
- Wire & Cable
- Connectors
- Antenna Kits

UNADILLA / REYCO Division Microwave Filter Co., Inc., E. Syracuse, NY 13057

## HUSTLER ANTENNAS

5BTV	5-Band trap vertical 10-80 m., reg. \$139.95	125.95
4BTV	4-Band trap vertical 10-40 m., reg. \$109.95	98.96
BM-1	Bumper mount, reg. \$18.95	17.06
MO-1	Mast, fold-over, deck mounting, reg. \$22.95	20.66
MO-2	Mast, fold-over, bumper mount, reg. \$22.95	20.66
RM-75	Resonator, 75 meters, 400 watt, reg. \$18.95	17.06
RM-40	Resonator, 40 meters, 400 watt, reg. \$16.95	15.26
RM-40S	Super resonator, 40 meters, KW, reg. \$24.95	22.46
RM-20	Resonator, 20 meters, 400 watt, reg. \$14.95	13.46
RM-20S	Super resonator, 20 meters, KW, reg. \$21.95	19.76
RM-15	Resonator, 15 meters, 400 watt, reg. \$10.95	9.86
RM-10	Resonator, 10 meters, 400 watt, reg. \$10.95	9.86
CG-144	Mobile 2 meter colinear, w/o mount, reg. \$28.95	26.06
CGT-144	2 meter colinear w/trunk mount, reg. \$45.95	41.36

## PALOMAR ENGINEERS

	Price	Shpg.
R-X	Noise bridge ..... \$ 55.00	\$2.00
VLF	Converter ..... 59.95	2.00
IK	Toriod balun, 3 KW SSB, 1:1 or 4:1 ..... 32.50	2.00
2K	Toriod balun, 6 KW SSB, 1:1 or 4:1 ..... 42.50	2.00
IC	Keyer, battery operated ..... 117.50	3.00
Loop Antenna, plug-in units, 160/80, BCB, VLF.	47.50	2.00
Loop Amplifier	67.50	2.00
Tuner — 10-60 meters, built-in noise bridge	299.95	6.50
CW Filter, 8 pole IC	39.95	2.00

### ALSO IN STOCK

Antenna Components • Larsen Antennas  
Centurion International Rubber Duck Antennas

WRITE FOR A FREE COPY OF OUR CATALOG

MASTER CHARGE VISA

All items F.O.B. Lincoln, \$1.00 minimum shipping. Prices subject to change without notice. Nebraska residents please add 3% tax.

**g & c Communications**

730 Cottonwood

Lincoln, Nebraska 68510

## ANTENNA BOOKS by Bill Orr, W6SAI

### ALL ABOUT CUBICAL QUAD ANTENNAS

The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. In Bill Orr's latest edition of this well known book, you'll find quad designs for everything from the single element to the multi-element monster quad, plus a new, higher gain expanded quad (X-Q) design. There's a wealth of supplementary data on construction, feeding, tuning, and mounting quad antennas. It's the most comprehensive single edition on the cubical quad available. 112 pages. ©1977.

RP-CQ

Softbound \$4.75

### THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart Cowan, W2LX

If you are pondering what new antennas to put up, we recommend you read this very popular book. It contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. But, you'll also get information not usually found in antenna books. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and some new information on the increasingly popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. We don't expect you'll agree with everything Orr and Cowan have to say, but we are convinced that **The Radio Amateur Antenna Handbook** will make a valuable and often consulted addition to any Ham's library. 190 pages. ©1978.

RP-AH

Softbound \$6.95

### BEAM ANTENNA HANDBOOK

Here's recommended reading for anyone thinking about putting up a yagi beam this year. It answers a lot of commonly asked questions like: What is the best element spacing? Can different yagi antennas be stacked without losing performance? Do monoband beams outperform tribanders? Lots of construction projects, diagrams, and photos make reading a pleasurable and informative experience. 198 pages. ©1977.

RP-BA

Softbound \$5.95

Please add \$1.00 to cover shipping and handling.

**HAM RADIO'S BOOKSTORE**  
GREENVILLE, N. H. 03048

ramsey

# the first name in Counters!



## 9 DIGITS 600 MHz \$129<sup>95</sup> WIRED

**PRICES:**

CT-90 wired, 1 year warranty	\$129.95
CT-90 Kit, 90 day parts warranty	109.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC Adapter/Charger	12.95
OV-1, Micro-power Oven time base	49.95
External time base input	14.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10MHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

**SPECIFICATIONS:**

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 10 MV to 150 MHz Less than 50 MV to 500 MHz
Resolution:	0.1 Hz (10 MHz range) 1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	9 digits 0.4" LED
Time base:	Standard-10.000 mHz, 1.0 ppm 20-40°C. Optional Micro-power oven-0.1 ppm 20-40°C
Power:	8-15 VAC @ 250 ma

## 7 DIGITS 525 MHz \$99<sup>95</sup> WIRED



**SPECIFICATIONS:**

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz Less than 150 MV to 500 MHz
Resolution:	1.0 Hz (5 MHz range) 10.0 Hz (50 MHz range) 100.0 Hz (500 MHz range)
Display:	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power:	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as; three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

**PRICES:**

CT-70 wired, 1 year warranty	\$99.95
CT-70 Kit, 90 day parts warranty	84.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC adapter/charger	12.95

## 7 DIGITS 500 MHz \$79<sup>95</sup> WIRED



**PRICES:**

MINI-100 wired, 1 year warranty	\$79.95
MINI-100 Kit, 90 day part warranty	59.95
AC-Z Ac adapter for MINI-100	3.95
BP-Z Nicad pack and AC adapter/charger	12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

**SPECIFICATIONS:**

Range:	1 MHz to 500 MHz
Sensitivity:	Less than 25 MV
Resolution:	100 Hz (slow gate) 1.0 KHz (fast gate)
Display:	7 digits, 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	5 VDC @ 200 ma

## 8 DIGITS 600 MHz \$159<sup>95</sup> WIRED



**NEW READ RECEIVER FREQUENCY**

**SPECIFICATIONS:**

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 25 mv to 150 MHz Less than 150 mv to 600 MHz
Resolution:	1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	8 digits 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

**PRICES:**

CT-50 wired, 1 year warranty	\$159.95
CT-50 Kit, 90 day parts warranty	119.95
RA-1, receiver adapter kit	14.95
RA-1 wired and pre-programmed (send copy of receiver schematic)	29.95



## DIGITAL MULTIMETER \$99<sup>95</sup> WIRED

**PRICES:**

DM-700 wired, 1 year warranty	\$99.95
DM-700 Kit, 90 day parts warranty	79.95
AC-1, AC adaptor	3.95
BP-3, Nicad pack + AC adapter/charger	19.95
MP-1, Probe kit	2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

**SPECIFICATIONS:**

DC/AC volts:	100uV to 1 KV, 5 ranges
DC/AC current:	0.1uA to 2.0 Amps, 5 ranges
Resistance:	0.1 ohms to 20 Megohms, 6 ranges
Input impedance:	10 Megohms, DC/AC volts
Accuracy:	10.1% basic DC volts
Power:	4 °C cells

### AUDIO SCALER

For high resolution audio measurements, multiplies U in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

### ACCESSORIES

Telescopic whip antenna - BNC plug.....	\$ 7.95
High impedance probe, light loading.....	15.95
Low pass probe, for audio measurements.....	15.95
Direct probe, general purpose usage.....	12.95
Tilt bail, for CT 70, 90, MINI-100.....	3.95
Color burst calibration unit, calibrates counter against color TV signal.....	14.95

### COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
- BNC Connectors
- Great for sniffing RF with pick-up loop

\$34.95 Kit \$44.95 Wired


ramsey electronics INC.  
2575 BAIRD RD., PENFIELD, NY 14526

PHONE ORDERS  
CALL 716-586-3950

TERMS

Satisfaction guaranteed - examine for 10 days, if not pleased, return in original form for refund. Add 5% for shipping - insurance to a maximum of \$10. Overseas add 15% COD, add \$2. Orders under \$10, add \$1.50. NY residents add 7% tax.

# the weekender

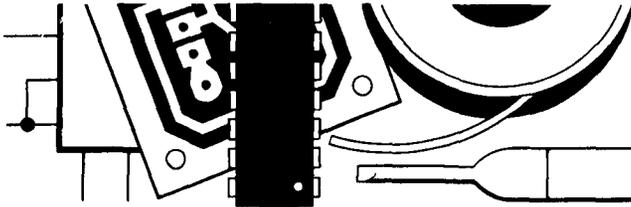

## add fm to your receiver

The fm mode of operation has been around for a long while, but not until the two-meter rage had it been used extensively for Amateur communications. Fm has become commonplace on vhf and uhf frequencies, but now its use is becoming more and more popular in the 29.500 through 29.700 MHz range (10-meter fm). It has always been the forgotten mode on your lowband transceiver. If you wanted to pioneer this spectrum, a piece of commercial-band equipment was your only alternative. But wait. What have we here? Comtronics FM-80, Azden 2800, and now fm on the 901-DM. *There must be someone up there!*

Commercially built ham transceivers as well as many converted CB radios have generated new life to an almost forgotten part of the ten-meter band. Don't scoff at the mention of converted CBs, as these are among some of the top performers when properly converted.


Described here is a conversion that can be made to any receiver using a 455-kHz i-f to add true fm to its current capabilities. The circuit can be built on a piece of vector board approximately two inches (50 mm) square, allowing it to fit nicely in even the smallest transceiver.

By John LaMartina, K3NXU, 105 Skyview Drive, Shrewsbury, Pennsylvania 17361

The chip selected is an MC 1358. Although designed for TV sound service, it works excellently at 455 kHz for nbfm applications. This chip functions as an i-f amplifier, limiter, fm detector and audio driver.
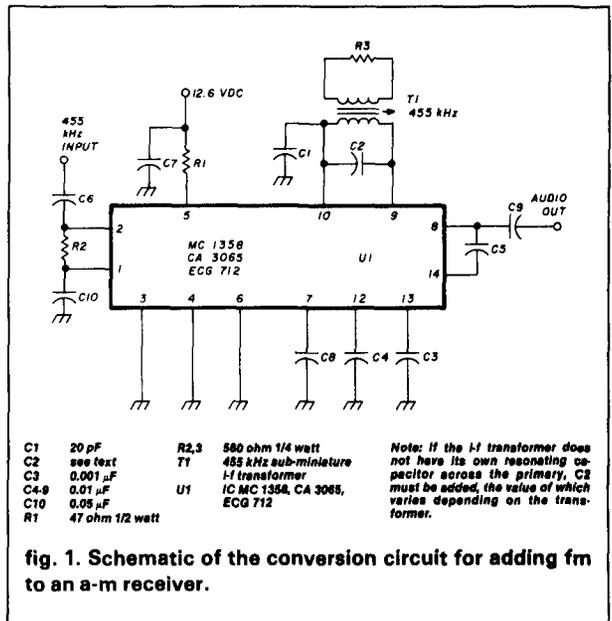
### basic operation

The 455-kHz i-f input to the IC is acquired from the last 455-kHz i-f amplifier. The fm signal is detected and set to the i-f by transformer T1. The audio is fed



to an audio driver with more than enough gain to properly drive your existing audio amplifier.

### construction

The use of a low-profile IC socket doesn't affect

# HAL'S SHOPPER'S GUIDE

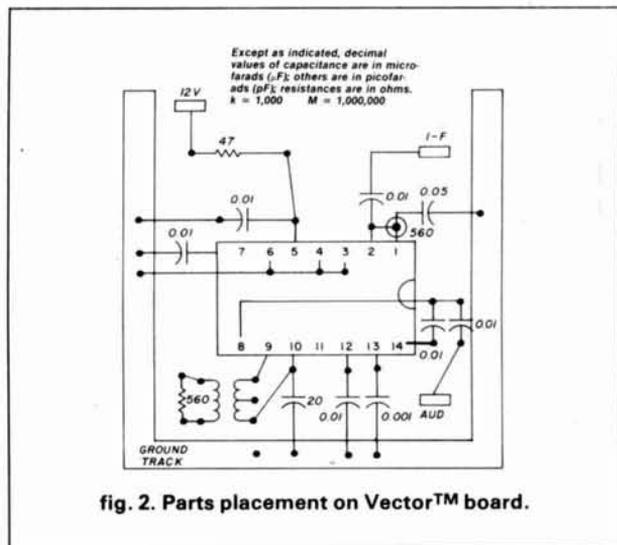


fig. 2. Parts placement on Vector™ board.

the performance of the i-f stage. Personally, I prefer to use them whenever possible (cheap insurance). In addition, try to keep all leads as short as possible. Capacitor C2 may not be required if the transformer selected is already at resonance.

## installation

The existing detector stages of the receiver are left intact so as to not disable the S-meter and squelch function.

1. Connect the 455-kHz i-f input to the base of the last i-f amplifier transistor.
2. The audio output pad of the fm board connects to the top of the volume control pot. The existing lead to this point must be removed or switched off so as to not receive fm and the existing receiver mode simultaneously.
3. Connect 12 Vdc and ground from the receiver to the conversion board.

## adjustment

The only adjustment necessary will be that of transformer T1. This should be set for maximum audio response upon the reception of a signal, either on the air or from an fm signal/tone generator. If too much drive is being delivered from the audio driver stage, insert a 100k resistor between C5 and the top of the volume control.

## closing comments

I have installed several of these fm conversions and have had complete success with each.

Predrilled PC boards with complete wiring diagram are available from the author for \$5.00 each.

ham radio



## SEE YOU AT ORLANDO NATIONAL

**11C05 1 GHz, pre.** Special \$59.95  
**ATF 417 pre-amp. net** Special \$19.95  
**MRF 901 UHF transistor, 1 GHz** Special \$3.95

**COMPLETE KITS:** CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY ± .001%. UTILIZES 10-MHz CRYSTAL 5 PPM. **COMPLETE KIT \$129**

**HAL-300A** 7-DIGIT COUNTER (SIMILAR TO 600A) WITH FREQUENCY RANGE OF 0-300 MHz. **COMPLETE KIT \$109**

**HAL-50A** 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT. ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH AN INTERNALLY MOUNTED HALTRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY ± .001%. UTILIZES 10-MHz CRYSTAL 5 PPM. **COMPLETE KIT \$109**

**FREE:** HAL-79 CLOCK KIT PLUS AN INLINE RF PROBE WITH PURCHASE OF ANY FREQUENCY COUNTER.

### PRE-SCALER KITS

**HAL 300 PRE** . . . . . (Pre-drilled G-10 board and all components) . . . . . \$14.95  
**HAL 300 A/PRE** . . . . . (Same as above but with preamp) . . . . . \$24.95  
**HAL 600 PRE** . . . . . (Pre-drilled G-10 board and all components) . . . . . \$29.95  
**HAL 600 A/PRE** . . . . . (Same as above but with preamp) . . . . . \$39.95

**NEW!** **HAL-1 GHz PRESCALER,** VHF & UHF INPUT & OUTPUT, DIVIDES BY 1000. OPERATES ON A SINGLE 5 VOLT SUPPLY. **PREBUILT & TESTED \$79.95**

### TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES. HAS 12 LINES OUT. ONLY \$39.95

**DELUXE 12-BUTTON TOUCHTONE ENCODER KIT** UTILIZING THE NEW ICM 7206 CHIP. PROVIDES BOTH VISUAL AND AUDIO INDICATIONS! COMES WITH ITS OWN TWO-TONE ANODIZED ALUMINUM CABINET. MEASURES ONLY 2-3/4" x 3-3/4". COMPLETE WITH TOUCH-TONE PAD, BOARD, CRYSTAL, CHIP AND ALL NECESSARY COMPONENTS TO FINISH THE KIT. **PRICED AT \$29.95**

FOR THOSE WHO WISH TO MOUNT THE ENCODER IN A HAND-HELD UNIT, THE PC BOARD MEASURES ONLY 9/16" x 1-3/4". THIS PARTIAL KIT WITH PC BOARD, CRYSTAL, CHIP AND COMPONENTS. **PRICED AT \$14.95**

**ACCUKEYER (KIT)** THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK. **\$16.95**

**ACCUKEYER — MEMORY OPTION KIT** PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY. **\$16.95**

### PRE-AMPLIFIER

**HAL-PA-19 WIDE BAND PRE-AMPLIFIER,** 2-200 MHz BANDWIDTH (-3dB POINTS), 19 dB GAIN. **FULLY ASSEMBLED AND TESTED \$8.95**

**NEW!** **CLOCK KIT — HAL 79 FOUR-DIGIT SPECIAL — \$7.95.** OPERATES ON 12-VOLT AC (NOT SUPPLIED). PROVISIONS FOR DC AND ALARM OPERATION

### 6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND COMM. CATH. READOUTS, 13 TRANS., 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA. **PRICED AT \$12.95**

**CLOCK CASE** AVAILABLE AND WILL FIT ANY ONE OF THE ABOVE CLOCKS. REGULAR PRICE . . . \$6.50 BUT ONLY \$4.50 WHEN BOUGHT WITH CLOCK.

**SIX-DIGIT ALARM CLOCK KIT** FOR HOME, CAMPER, RV, OR FIELD-DAY USE. OPERATES ON 12-VOLT AC OR DC, AND HAS ITS OWN 60-Hz TIME BASE ON THE BOARD. COMPLETE WITH ALL ELECTRONIC COMPONENTS AND TWO-PIECE, PRE-DRILLED PC BOARDS. BOARD SIZE 4" x 3". COMPLETE WITH SPEAKER AND SWITCHES. IF OPERATED ON DC, THERE IS NOTHING MORE TO BUY. **PRICED AT \$16.95**

\*TWELVE-VOLT AC LINE CORD FOR THOSE WHO WISH TO OPERATE THE CLOCK FROM 110-VOLT AC. **\$2.50**

**SHIPPING INFORMATION —** ORDERS OVER \$20.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$20.00 PLEASE INCLUDE ADDITIONAL \$1.50 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.

DISTRIBUTOR FOR

Aluma Tower • AP Products

(We have the new Hobby-Blox System)



"HAL"  
 HAROLD C. NOWLAND  
 WB2XH

**HAL-TRONIX**

P. O. BOX 1101  
 SOUTHGATE, MICH. 48195  
 PHONE (313) 285-1782

# Get on 220 MHz all modes with your present 2 meter rig!

220 is the new frontier in VHF! There is plenty of FM activity now in most areas of the country and SSB and weak signal work is growing rapidly. It's a fact; working on 220 is one of the most rewarding activities since most work is still in the pioneering stages.

You can get on 220 at minimal expense now by adding Lunar's new 220/TV Transverter to your present 2 meter station. It costs about half the price of most all-mode radios yet enables you to work any mode (CW, SSB, FM, SSTV, RTTY) on 220 as you do on 2 meters, using your present 2 meter transceiver.

#### Installation is easy!


Just connect the Lunar 220/TV to a 220 antenna, your 2 meter transceiver, and a 13.5 power supply; select your mode and GO!

The new Lunar 220/TV is Linearized for maximum utilization of all authorized modes. In addition, it has automatic T-R functions, either RF sensed or hard keyed. In the repeat mode the 1 MHz offset adds to the 600 KHz in your 2 meter radio to give you the 1.6 MHz required on 220 MHz.

#### BASIC SPECIFICATIONS

Rx N.F.: 2.5 dB nom.  
Rx Conversion Gain: 25 dB nom.

## with Lunar's new 220/TV transverter

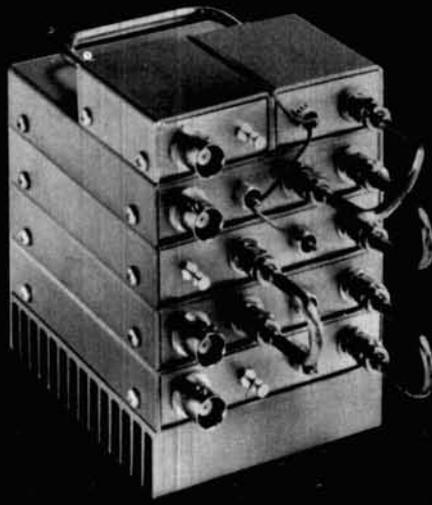

RF Pwr Out: 10 W nom. (CW & PEP)  
Power: 13.6 VDC @ 4 A nom.  
2 meter drive: 10 W nom.  
(Other drive levels available on special order.)

Examples of frequency conversion in the following modes:

#### SIMPLEX I (Nat'l Call Freq.)

Function	2 Meters	220 MHz
Rx Freq.	146.5	223.5
Tx Freq.	146.5	223.5

#### SIMPLEX II (Nat'l SSB Call Freq.)

Rx Freq.	144.1	220.1
Tx Freq.	144.1	220.1

#### REPEATER MODE (2 Meter— 600 KHz Offset Required)

Rx Freq.	147.94	224.94
Tx Freq.	147.34	223.34

See your Lunar dealer or contact Lunar for complete details.



2785 Kurtz Street, Suite 10  
San Diego, CA 92110  
Telephone: (714) 299-9740 Telex: 181747  
Louis N. Anclaux, WB6NMT



Radio equipment  
not included

Also Available . . .  
Floor Space: 51" Wide by 30" Deep  
\$192.50

4384 KEYSTONE AVENUE • CULVER CITY, CALIF. 90230 — PHONE (213) 837-4870

## ... at last ... your shack organized!

A beautiful piece of furniture — your XYL will love it!

### \$16450 S-F RADIO DESK Deluxe - Ready to Assemble

Designed with angled rear shelf for your viewing comfort and ease of operation.

FINISHES: Walnut or Teak Stain.

Floor Space: 39" Wide by 30" Deep

Additional Information on Request.

Checks, Money Orders, BankAmericard  
and Master Charge Accepted.

F.O.B. Culver City. (In Calif. Add 6% Sales Tax.)

— DEALER INQUIRIES INVITED —

**S-f Amateur Radio Services**



## The Best Got Better



MODEL 4381 RF POWER ANALYST

This new generation  
RF Wattmeter with nine-mode  
system versatility reads...

IN STOCK QUICK DELIVERY

AUTHORIZED **Webster** DISTRIBUTOR

**Webster**  
associates


115 BELLARMINE  
ROCHESTER, MI 48063

CALL TOLL FREE  
**800-521-2333**  
IN MICHIGAN 313 - 375-0420

## Isotron Antennas

THE ULTIMATE space savers...  
for 80 and 40 meters.

Designed  
and  
proved by  
W0BEJA

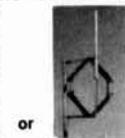

Hear on  
7245 kHz  
at  
3 & 5 PM  
MDT

80 Meters

Length  
Weight  
Bandwidth  
Feed  
Price

40 Meters

4 1/2 ft.  
8 lbs.  
110 kHz\*  
50Ω coax  
\$59.95

31 inches  
4 lbs.  
250 kHz\*  
50Ω coax  
\$49.95

\*Limits for 2:1 SWR; center frequency adjustable

Isotron antennas need no radials or matching devices. Feed with 50Ω coax. For indoor or outdoor mounting. Excellent for all amateur uses.

**BILAL COMPANY**  
(303) 687-3219  
STAR ROUTE FLORISSANT, CO. 80816

## 2m AMPLIFIER

SALE  
See us in DAYTON  
**\$54.95**  
(p. pd USA)



- 35w 2m FM AMPLIFIER KIT • MODEL 335-K
- 3 IN - 35 OUT • 2 IN - 30 OUT • 1 IN - 15 OUT
- COR • CLASS C • 4.5 A AT 13.6VDC
- BNC CONNECTORS

ASK ABOUT OUR OTHER VHF & UHF MODELS

### COMMUNICATION CONCEPTS INC.

2648 NORTH ARAGON AVE.  
DAYTON, OHIO 45420  
(513) 296-1411

# INTRODUCING SONY'S NEW DIGITAL DIRECT ACCESS RECEIVER!



only **\$299<sup>95</sup>** plus \$5.00 shipping

## Revolutionary Direct Access Digital Shortwave Scanner



- Continuous Scanning of LW, MW, SW, & FM Bands
- Instant Fingertip Tuning—No More Knobs!
- 6 Memories for Any Mode (AM,SSB/CW, & FM)
- Dual PLL Frequency Synthesized—No Drift!

**A WHOLE NEW BREED OF RADIO IS HERE NOW!** No other short wave receiver combines so many advanced features for both operating convenience and high performance as does the new Sony ICF-2001. Once you have operated this exciting new radio, you'll be spoiled forever! Direct access tuning eliminates conventional tuning knobs and dials with a convenient digital keyboard and Liquid Crystal Display (LCD) for accurate frequency readout to within 1 KHz. Instant fingertip tuning, up to 8 memory presets, and continuous scanning features make the ICF-2001 the ultimate in convenience.

Compare the following features against any receiver currently available and you will have to agree that the Sony ICF 2001 is the best value in shortwave receivers today:

**DUAL PLL SYNTHESIZER CIRCUITRY** covers entire 150 KHz to 29.999 MHz band. PLL<sub>1</sub> circuit has 100 KHz step while PLL<sub>2</sub> handles 1 KHz step, both of which are controlled by separate quartz crystal oscillators for precise, no-drift tuning. **DUAL CONVERSION SUPERHETERODYNE** circuitry assures superior AM reception and high image rejection characteristics. The 10.7 MHz IF of the FM band is utilized as the 2nd IF of the AM band. A new type of crystal filter made especially for this purpose realizes clearer reception than commonly used ceramic filters. **ALL FET FRONT END** for high sensitivity and interference rejection. Intermodulation, cross modulation, and spurious interference are effectively rejected. **FET RF AMP** contributes to superior image rejection, high sensitivity, and good signal to noise ratio. Both strong and weak stations are received with minimal distortion.

### EXTENDED SPECTRUM CONTINUOUS TUNING

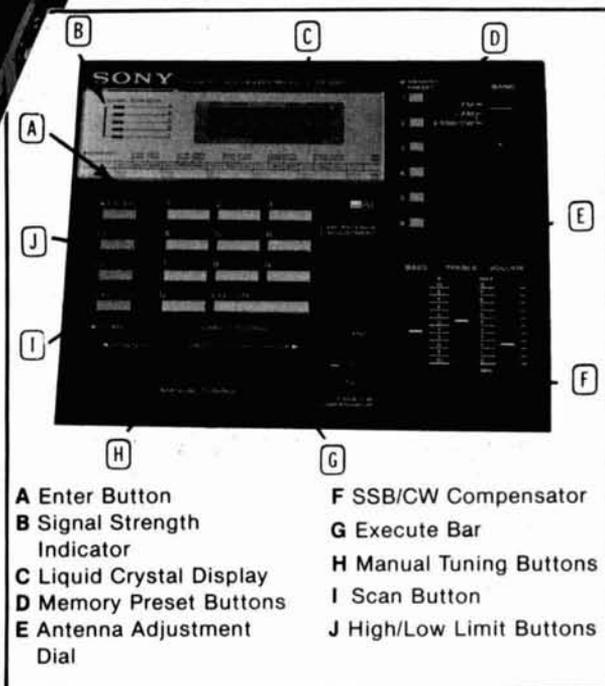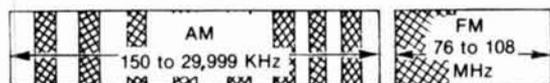

### OPERATIONAL FEATURES

**INSTANT FINGERTIP TUNING** with the calculator-type key board enables the operator to have instant access to any frequency in the LW, MW, SW, and FM bands. And the LCD digital frequency display confirms the exact, drift-free signal being received. **AUTOMATIC SCANNING** of the above bands. Continuous scanning of any desired portion of the band is achieved by setting the "L<sub>1</sub>" and "L<sub>2</sub>" keys to define the range to be scanned. The scanner can stop automatically on strong signals, or it can be done manually. **MANUAL SEARCH** is similar to the manual scan mode and is useful for quick signal searching. The "UP" and "DOWN" keys let the tuner search for you. The "FAST" key increases the search rate for faster signal detection. **MEMORY PRESETS.** Six memory keys hold desired stations for instant one-key tuning in any mode (AM, SSB/CW, and FM), and also, the "L<sub>1</sub>" and "L<sub>2</sub>" keys can give you two more memory slots when not used for scanning. **OTHER FEATURES:** Local, normal, DX sensitivity selector for AM; SSB/CW compensator; 90 min. sleep timer; AM Ant. Adjust.

### SPECIFICATIONS


**CIRCUIT SYSTEM:** Fm Superheterodyne; AM Dual conversion superheterodyne. **SIGNAL CIRCUITRY:** 4 IC's, 11 FET's, 23 Transistors, 16 Diodes. **AUXILIARY CIRCUITRY:** 5 IC's, 1 LSI, 5 LED's, 25 Transistors, 9 Diodes. **FREQUENCY RANGE:** FM 76-108 MHz; AM 150-29,999 KHz. **INTERMEDIATE FREQUENCY:** FM 10.7 MHz; AM 1st 66.35 MHz., 2nd 10.7 MHz. **ANTENNAS:** FM telescopic, ext. ant. terminal; AM telescopic, built-in ferrite bar, ext. ant. terminal. **POWER:** 4.5 VDC/120 VAC **DIMENSIONS:** 12 1/4 (W) X 2 1/4 (H) X 6 3/4 (D). **WEIGHT:** 3 lb. 15 oz. (1.8 kg)



**SPECTRONICS, INC.**  
1009 GARFIELD ST. OAK PARK, IL. 60304

PHONE  
**(312) 848-6777**



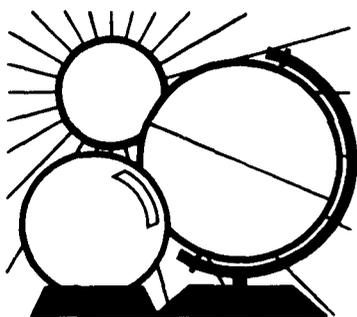

# DX FORECASTER

Garth Stonehocker, KØRYW

## weather affects DX, right?

Besides keeping us indoors or outside? Yes! March and April are months in which weather is usually a series of spring storms bringing rain to much of our country. These storms are usually fronts of warm and cold air, which produce the year's first major thunderstorms. Thunderstorms mean noise (static) that affects the signal-to-noise ratio of our receivers, decreasing readability.

Thunderstorm static propagated from far off is the main overall noise level of our lower-frequency hf bands. The average noise from the thunderstorms all over the world going on at once makes this noise level. However, as a particular storm front comes near, a significant increase in the noise level can be heard. The first notice of this noise increase is at a one-hop distance away (about 600-1200 miles or 960-1920 km) when the storm front is about a day or so to the west of your location. Next, the

noise will usually decrease as the storm moves closer; that is, until it is within a ground-wave distance of 50-60 miles or 80-96 km (near line of sight). Thunderstorm static is then worse, mainly individual crashes, and it becomes part of the local noise. As the storm moves away a similar decrease, then an increase, is heard in a day or so again as the front moves on. You can check this out for your location by coordinating the TV weather program with your operating/listening experience. The effect is more noticeable on the lower frequency bands.

In looking for the rare DX, you may want to make the best use of your time by tracking the storms to give you the best chance at quiet noise conditions. Remember, too, the DX station's operating times and frequencies. An article in the November, 1980, issue of *CQ* lists the foreign national holidays (consider when the DX is home from work), and a *QST*

article (January, 1975) points out the best DX frequencies in each band.

Toward the end of March (associated with the equinox, which is on March 20 at 1703 UT), the geomagnetic field is easily disturbed. The equatorial plane of the sun lines up through space with the earth's equator, giving particles a more direct path to the earth's polar regions. Disturbances are prevalent under this condition. DX can be from unusual locations because of the ionosphere's erratic movements. East-west paths are generally poorer; otherwise during undisturbed times, over-the-pole DX paths are better during the equinox season.

## band-by-band summary

*Six meters* will provide some excellent openings to South Africa from the eastern U.S. and from the western and central U.S. to Australia and New Zealand around local noon-time. The openings are more probable during high solar flux values.

*Ten, fifteen, and twenty meters* will be full of signals from morning into early evening almost every day and to most areas of the world. The openings will be shorter on the higher bands and concentrated more near noon for the path of interest. High solar flux values and geomagnetic disturbance will favor these bands for transequatorial contacts. Noise effects are not too noticeable.

*Forty, eighty, and one-sixty meters* are the night Dxe's bands. The bands are open beginning just before sunset and lasting until just as the sun comes up on the path of interest. Except for daytime short-skip signal strengths, high solar flux values don't affect these bands much. Geomagnetic disturbances, which will be more evident near the equinox, cause much signal attenuation and fading on polar paths. The effects of these disturbances are less on these bands, although noise will be spasmodic and very noticeable on these lower-frequency bands.

ham radio

### WESTERN USA

GMT	PST	WESTERN USA							
		N	NE	E	SE	S	SW	W	NW
0000	4:00	10	20	10	15	10	10	10*	10
0100	5:00	10	20	10	15*	10	10	10	10
0200	6:00	10	20	15	10	10	10	10	15
0300	7:00	10	20	15	10	10	10	10	15
0400	8:00	10	40	20	15	15*	10	10	15
0500	9:00	—	—	20*	15	15	10	10	20
0600	10:00	—	20	20	15	15	10	10	20
0700	11:00	—	—	20	15	15	15	10	20
0800	12:00	20	—	20	20	20	15	15*	20
0900	1:00	20	—	20	20	20	15	15	—
1000	2:00	20	—	—	20	20	15	15	—
1100	3:00	20	—	—	20	20	15	20	—
1200	4:00	20	40*	—	15	20	20	20	20
1300	5:00	20	20	—	15	—	20	20	20
1400	6:00	20	20	15	10	20	20	20	20
1500	7:00	20	20	15	10	20	20*	15	20
1600	8:00	20*	15	15	10	—	15	15	20
1700	9:00	15	15	15*	10	—	15	—	20
1800	10:00	15	10	10	10	15	10	—	20
1900	11:00	15	10	10	10	15	10	—	20
2000	12:00	—	10	10	10	10	10	10	20
2100	1:00	—	20	10	10	10	10	10*	15*
2200	2:00	10	20	10	10	10	10	10	10
2300	3:00	10	20	10	15	10	10	10*	10
MARCH		ASIA FAR EAST	EUROPE	S. AFRICA	S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN

### MID USA

GMT	MST	MID USA								CST
		N	NE	E	SE	S	SW	W	NW	
0000	5:00	10	20	10	10	10	10	10	10	6:00
0100	6:00	10	20	15	10	10	10	10	10	7:00
0200	7:00	10	40	15	10	15	10	10	10	8:00
0300	8:00	15	40	15	15	15	10	10	15*	9:00
0400	9:00	15	40	20	15	15	10	10	15	10:00
0500	10:00	15	40*	20	15	15	15	15	15	11:00
0600	11:00	—	—	20*	15	15	15	15	20	12:00
0700	12:00	—	—	20	20*	20	15	15	20	1:00
0800	1:00	20	—	20	15	20	15	15	20	2:00
0900	2:00	20	—	20	20	20	15	20	20	3:00
1000	3:00	—	20	—	20	20	20	20	20	4:00
1100	4:00	—	20	—	20	20	20	20	20	5:00
1200	5:00	—	20	—	15	20	20	20	—	6:00
1300	6:00	20	15	15	15	—	20	20	20	7:00
1400	7:00	20	15	10	10	—	15	20	20	8:00
1500	8:00	15	10	10	10	—	15	15	20	9:00
1600	9:00	15	10	10	10	15	15	15	20	10:00
1700	10:00	15	10	10	10	15	15*	—	—	11:00
1800	11:00	15	10	10	10	15	10	—	—	12:00
1900	12:00	15	10	10	10	10	10	—	—	1:00
2000	1:00	15	15	10	10	10	10	10	15	2:00
2100	2:00	—	15	10	10	10	10	10*	15	3:00
2200	3:00	—	20	10	10	10	10	10	10	4:00
2300	4:00	15	20	10	10	10	10	10*	10	5:00
		ASIA FAR EAST	EUROPE	S. AFRICA	S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN	

### EASTERN USA

GMT	EST	EASTERN USA								
		N	NE	E	SE	S	SW	W	NW	
0000	7:00	10	20	10	10	10	10	10	10	
0100	8:00	10	20	15	15	15	10	10	10	
0200	9:00	15	20	15*	15	15	10	10	10	
0300	10:00	15	20	20*	15	15	10	15	10	
0400	11:00	20*	40	20	15	15	15	15	10	
0500	12:00	20	40	20	15	20	15	15	15	
0600	1:00	20	40	15	15	20	20*	20	20*	
0700	2:00	—	40	20	20	20	20*	20	20	
0800	3:00	—	40	20	20	20	20*	20	20	
0900	4:00	—	20	—	20	20	20	20	20	
1000	5:00	20	20	—	20	20	20	20	40*	
1100	6:00	20	15	15	15	20	20	20	40*	
1200	7:00	20	15	10	10	20	20	20	40*	
1300	8:00	—	10	10	10	—	—	15	20	
1400	9:00	15	10	10*	10	—	20*	15	20	
1500	10:00	15	10	10*	10	—	15	15	20	
1600	11:00	15	10	10	10	—	15	20	20	
1700	12:00	—	10	10	10	15	10	—	20	
1800	1:00	—	15	10	10	10	10	20	20	
1900	2:00	—	15	10	10	10	10	10	15	
2000	3:00	—	15	10	10	10	10	10	15	
2100	4:00	—	15	10	10	10	10	10	15	
2200	5:00	15	20	10	10	10	10	10	20	
2300	6:00	15	20	15	10	10	10	10	20	
		ASIA FAR EAST	EUROPE	S. AFRICA	CARIBBEAN S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN	

**ASSOCIATED RADIO****913-381-5900**8012 CONSER BOX 4327  
OVERLAND PARK, KANSAS 66204

# BUY—SELL—TRADE

## All Brands New & Reconditioned



We Want to DEAL—Call Us—We'll Do It Your Way.  
**WE'RE #1**



NOTE: SEND \$1.00 FOR OUR CURRENT CATALOG OF NEW AND RECONDITIONED EQUIPMENT.

★ ALSO WE PERIODICALLY PUBLISH A LIST OF UNSERVICED EQUIPMENT AT GREAT SAVINGS.  
A BONANZA FOR THE EXPERIENCED OPERATOR.

TO OBTAIN THE NEXT UNSERVICED BARGAIN LIST SEND A SELF ADDRESSED STAMPED ENVELOPE.

**NOW** An  
**8044 with  
Speedmeter\***



from **CURTIS**

★ EK-480: C-MOS Deluxe Keyer .....	\$134.95
★ EK-480M: Above plus speedmeter .....	149.95
★ I-480: InstructoMate .....	124.95
★ M-480: MemoryMate .....	124.95
★ IM-480: Instructo-MemoryMate .....	179.95
★ KB-480: Morse KeyboardMate .....	199.95
★ KB-4900: Morse-RTTY keyboard .....	379.95
Above prices FOB factory	
8044: Keyer-On-A-Chip (ARRL Hdbk 77-81) .....	14.95
8044-3: IC, PCB, Socket, Manual .....	24.95
8044-4: Semi-Kit .....	54.95
*8044M (incl. speedmeter funct.) add \$5.00	
8045: Morse Keyboard-On-A-Chip IC .....	59.95
8045-1: IC, PCB, FIFO, Sockets, Manual .....	89.95
8045-2: Semi-Kit .....	159.95
8046: Instructokeyer-On-A-Chip IC .....	49.95
8046-1: Semi-Kit .....	79.95
8047: Message Memory-On-A-Chip IC .....	39.95
8047-1: IC, PCB, RAM, Sockets, Manual .....	69.95

(add \$1.75 on kits for postage and handling)

Curtis Electro Devices, Inc.

(415) 494-7223

Box 4090, Mountain View, CA 94040



### YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect  
from the **DX ENGINEERING**  
RF Speech Processor

- 6 db INCREASE IN AVERAGE POWER
- MAINTAINS VOICE QUALITY
- IMPROVES INTELLIGIBILITY
- NO CABLES OR BENCH SPACE REQUIRED
- EXCELLENT FOR PHONE PATCH
- NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED



This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.

#### Models Now Available

Collins 32S, KWM-2 ..... \$ 98.50 ea.  
Drake TR-3, TR-4, TR-6, TR-4C,  
T-4, T-4X, T-4XB, T-4XC \$128.50 ea.  
Postpaid — Calif. Residents  
add 6% Tax

Watch for other models later!

#### DX Engineering

1050 East Walnut, Pasadena, Calif. 91106

## SHORTWAVE EXCITEMENT!

*Tired of watching dull TV programs?  
Bored by long, empty evenings?*

### LISTEN TO THE WORLD!

News, commentaries, music, folklore from foreign lands! Informative, entertaining, cultural! Clean Family FUN! Be better informed than your friends by hearing all sides on international issues *directly!*"THE NORTH AMERICAN SHORT-WAVE LISTENER'S HANDBOOK", 1981 issue, is just what you need to **ACHIEVE MAXIMUM PLEASURE FROM YOUR EQUIPMENT**

—Shortwave basics (Propagation, Broadcasting Conditions, Frequency &amp; Wave Length, Frequency Assignments, International Time, Target Areas, Reception Tips &amp; Reports, more) explained in simple terms for beginners

—Official schedules of programs beamed to North America, in English &amp; other languages from 70 countries, showing languages used, times and frequencies

\$4.00 ppd. Give one to your best friend: Two for \$7.50. Order now from:

LUFEL INTERNATIONAL,  
Box 232-HR Rego Park, NY 11374

# SEMICONDUCTORS SURPLUS

2822 North 32nd Street, #1 • Phoenix, Arizona 85008 • Phone 602-956-9423

<u>ORY</u>	<u>Description</u>	<u>Price</u>
8	1K x 8 Eprom	\$ 5.00
6/2516	2K x 8 5V single supply	9.99
4/9114	1K x 4 Static	5.00
7	4K x 1 Dynamic Ram	2.99
7/4116	16K x 1 Dynamic Ram	5.00
2-6	32K Eprom	39.95
<u>.U.'s, Etc.</u>		
800P	Microprocessor	9.99
8B21P	PIA	6.99
845P	CRT Controller	25.00
850P	ACIA	4.99
852P	SSDA	5.00
8-1	Microprocessor	5.00
0A	Microprocessor	5.00
A	Microprocessor	10.99
A	Microprocessor	8.99
A	PIO	9.99
	S10/0	22.50
	S10/1	22.50
2	8 Bit input/output part	3.99
1	Communication Interface	6.99
602/AY5-1013	UART	6.99
1000NL	Four Bit Microprocessor	4.99
482B	PSAT	5.99
7	DMA Controller	8.99
1	64 x 4 FIFO	3.00
316/F3817	Clock with alarm	5.99
1		60.00
8	8 Bit Microcomputer with programmable/erasable EPROM	60.00
408L/6	6 Bit D/A	3.25
2502		9.99
2601		9.99

CRYSTAL FILTERS  
 001-19880 Same as 2194F  
 7 MHz narrow band  
 3 dB bandwidth 15KHz min.  
 40 dB bandwidth 60 KHz min.  
 60 dB bandwidth 150 KHz min.  
 approximate 50 dB insertion loss 1 dB max.  
 ripple 1 dB max. Ct. 0+/-5 pf 3600 Ohms  
 \$3.99 each

454 Same as MRF458 12.5 VDC, 3-30 MHz  
 .95 each 80 Watts output, 12 dB gain

MRF472  
 12.5 VDC, 27 MHz  
 4 Watts output, 10 dB gain  
 \$1.69 each

CARBIDE Circuit Board Drill Bits  
 for PCB Boards  
 5 mix for \$5.00

MURATA CERAMIC FILTERS  
 SFD 455D 455 KHz \$2.00  
 SFB 455D 455 KHz 1.60  
 CFM 455E 455 KHz 5.50  
 SFE 10.7 MA 10.7 MHz 2.99

ATLAS CRYSTAL FILTERS FOR ATLAS  
 HAM GEAR  
 5.52 - 2.7/8  
 5.595 - 2.7/8/U  
 5.645 - 2.7/8  
 5.595 - .500/4/CW YOUR CHOICE  
 5.595 - 2.7 USB \$12.99 each  
 5.595 - 2.7/8/L  
 5.595 - 2.7 LSB  
 9.0 - USB/CW

J310 N-CHANNEL J - FET 450 MHz  
 Good for VHF/UHF Amplifier,  
 Oscillator and Mixers. 3/\$1.00

AMPHENOL COAX RELAY  
 26 VDC Coil SPDT #360-11892-13  
 100 watts Good up to 18 Ghz  
 \$19.99 each

78M05 Same as 7805 but only 1/2 Amp @  
 5 VDC 49¢ each or 10/\$3.00

NEW TRANSFORMERS  
 F-18X 6.3 VCT @ 6Amps \$6.99 each  
 F-46X 24V @ 1Amp 5.99  
 F41X 25.2VCT @ 2Amps 6.99  
 P-8380 10VCT @ 3Amps 7.99  
 P-8604 20VCT @ 1Amp 4.99  
 P-8130 12.6VCT @ 2Amps 4.99  
 K-32B 28VCT @ 100 MA 4.99  
 E30554 Dual 17V @ 1Amp ea. 6.99

EIMAC FINGER STOCK #Y-302  
 36 in. long x 1/2 in. \$4.99 each

NO ORDERS UNDER \$10

# SEMICONDUCTORS SURPLUS

2822 North 32nd Street, #1 • Phoenix, Arizona 85008 • Phone 602-956-9423

MRF203	\$P.O.R.	BFW92A	\$ 1.00
MRF216	19.47	BFW92	.79
MRF221	8.73	MMCM918	14.30
MRF226	10.20	MMCM2222	15.65
MRF227	2.13	MMCM2369	15.00
MRF238	10.00	MMCM2484	15.25
MRF240	14.62	MMCM3960A	24.30
MRF245	28.87	MWA110	6.92
MRF247	28.87	MWA120	7.38
MRF262	6.25	MWA130	8.08
MRF314	12.20	MWA210	7.46
MRF406	11.33	MWA220	8.08
MRF412	20.65	MWA230	8.62
MRF421	27.45	MWA310	8.08
MRF422A	38.25	MWA320	8.62
MRF422	38.25	<u>MWA330</u>	<u>9.23</u>
MRF428	38.25		
MRF428A	38.25	TUBES	
MRF426	8.87	6KD6	\$ 5.00
MRF426A	8.87	6LQ6/6JE6	6.00
MRF449	10.61	6MJ6/6LQ6/6JE6C	6.00
MRF449A	10.61	6LF6/6MH6	5.00
MRF450	11.00	12BY7A	4.00
MRF450A	11.77	2E26	4.69
MRF452	15.00	4X150A	29.99
MRF453	13.72	4CX250B	45.00
MRF454	21.83	4CX250R	69.00
MRF454A	21.83	4CX300A	109.99
MRF455	14.08	4CX350A/8321	100.00
MRF455A	14.08	4CX350F/J/8904	100.00
MRF472	2.50	4CX1500B/8660	300.00
MRF474	3.00	811A	20.00
MRF475	2.90	6360	4.69
MRF476	2.25	6939	7.99
MRF477	10.00	6146	5.00
MRF485	3.00	6146A	5.69
MRF492	20.40	6146B/8298	7.95
MRF502	.93	6146W	12.00
MRF604	2.00	6550A	8.00
MRF629	3.00	8908	9.00
MRF648	26.87	8950	9.00
MRF901	3.99	4-400A	71.00
MRF902	9.41	4-400C	80.00
MRF904	3.00	572B/T160L	44.00
MRF911	4.29	7289	9.95
MRF5176	11.73	3-1000Z	229.00
MRF8004	1.39	<u>3-500Z</u>	<u>129.99</u>
BFR90	1.00		
BFR91	1.25	TO-3 TRANSISTOR SOCKETS	
BFR96	1.50	Phenolic type 6/\$1.00	

UHF/VHF RF POWER TRANSISTORS  
 CD2867/2N6439  
 60 Watts output  
 Reg. Price \$45.77  
SALE PRICE \$19.99

1900 MHz to 2500 MHz DOWNCONVERTERS  
 Intended for amateur radio use.  
 Tunable from channel 2 thru 6.  
 34 dB gain 2.5 to 3 dB noise.  
 Warranty for 6 months  
 Model HMR 11  
 Complete Receiver and Power Supply  
 \$225.00 (does not include coax)  
 4 foot Yagi antenna only  
 \$39.99

Downconverter Kit - PCB and parts  
 \$69.95  
 Power Supply Kit - Box, PCB and parts  
 \$49.99  
 Downconverter assembled  
 \$79.99  
 Power Supply assembled  
 \$59.99  
 Complete Kit form with Yagi antenna  
 \$109.99  
 REPLACEMENT PARTS  
 MRF901 \$ 3.99  
 MBD101 1.29  
 .001 Chip Caps 1.00  
 Power Supply PCB 4.99  
Downconverter PCB 19.99

NEW BOGNER DOWNCONVERTER  
 Industrial version.  
 1 year guarantee. \$225.00

86 PIN MOTOROLA BUS EDGE CONNECTORS  
 Gold plated contacts  
 Dual 43/86 pin .156 spacing  
 Solder tail for PCB \$3.00 each

CONTINUOUS TONE BUZZERS  
 12VDC \$2.00 each

110VAC MUFFIN FANS  
 New \$11.95 Used \$5.95

PL259 TERMINATION 52 Ohm 5 Watts  
 \$1.50 each

NO ORDERS UNDER \$10

# SEMICONDUCTORS SURPLUS

2822 North 32nd Street, #1 • Phoenix, Arizona 85008 • Phone 602-956-9423

#857JAN	\$ 2.50	2N6097	\$28.00
#949	3.60	2N6166	38.00
#947	15.00	2N6368	22.99
#950	4.60	2N6439	40.00
#375	8.00	A210/MRF517	2.00
#553	1.57	BLY38	5.00
#818	5.00	40280/2N4427	1.10
#866	1.00	40281/2N3920	7.00
#866JAN	2.50	<u>40282/2N3927</u>	<u>10.48</u>
#866JANTX	4.00		
#925	10.00	NE555V TIMERS	
#948	2.00	<u>39¢ each or 10/\$3.00</u>	
#950	25.00		
#959	3.00	NEW DUAL COLON LED	
#960JANTX	10.00	69¢ each or	
#072	1.60	<u>10/\$5.00</u>	
#427	1.10		
#429	7.00	HEP170 1000 PIV	
#877	1.00	2.5 Amps 25¢ each or	
#959	2.00	<u>100/\$15.00</u>	
#976	15.00		
#070	8.00	HIGH VOLTAGE CAPS	
#071	15.00	420 MFD @ 400 VDC OR	
#108	4.00	600 MFD @ 400 VDC	
#109	1.50	<u>\$6.99 each</u>	
#179	1.00		
#583	4.00	NEW ROTRON BISCUIT FANS	
#589	6.00	Model BT2A1 115 VAC	
#590	8.00	<u>\$12.99 each</u>	
#591	11.00		
#635	5.44	TORIN TA700 FANS NEW	
#636	11.60	Model A30340	
#637	20.00	230 VAC @ .78 Amps	
#641	5.00	Will also work on 115 VAC	
#643	14.00	<u>\$29.99 each</u>	
#645	10.00		
#842	8.00	DOOR KNOB CAPS	
#849	20.00		
#942	40.00	470 pf @ 15 KV	\$3.99 each
#946	14.00	Dual 500 pf @ 15 KV	5.99 each
#862	50.00	680 pf @ 6 KV	3.99 each
#080	7.00	800 pf @ 15 KV	3.99 each
#081	10.00	1000 pf @ 20 KV	5.00 each
#082	11.00	<u>2700 pf @ 40 KV</u>	<u>5.99 each</u>
#083	13.00		
#084	14.00	NEW & USED BCD SWITCHES	
#095	11.00	3 switch with end plates	
#096	20.00	\$8.99 New \$6.95 Used	

## ORDERING INSTRUCTIONS

Check, money order, or credit cards welcome. (Master Charge and VISA only) No personal checks or certified personal checks for foreign countrys accepted. Money order or cashiers check in U.S. funds only. Letters of credit are not acceptable.

Minimum shipping by UPS is \$2.35 with insurance. Please allow extra shipping charges for heavy or long items.

All parts returned due to customer error will be subject to a 15% restock charge.

If we are out of an item ordered, we will try to replace it with an equal or better part unless you specify not to, or we will back order the item, or refund your money.

PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE. Prices superseade all previously published. Some items offered are limited to small quantities and are subject to prior sale.

We now have a toll free number but we ask that it be used for charge orders only. If you have any questions please use our other number. We are open from 8:00 a.m. - 5:00 p.m. Monday thru Saturday.

Our toll free number **for orders only** is 800-528-3611.

### JUMBO LED's

Red	8/\$1.00
Clear	6/\$1.00
Yellow	6/\$1.00
Green	6/\$1.00
Amber	6/\$1.00

### MEDIUM LED's

Red	6/\$1.00
Green	6/\$1.00

NEW GE OPTO COUPLERS 4N26  
69¢ each or 10/\$5.00

MICRO-MINI WATCH CRYSTALS  
32.768 Hz \$3.00 each

NEW 2" ROUND SPEAKERS  
100 Ohm coil 99¢ each

PLASTIC TO-3 SOCKETS 4/\$1.00

NO ORDERS UNDER \$10



## inexpensive five-eighth wave ground plane


A year or so ago, my wife won a bicycle flag as a door prize at a meeting. I do own a bicycle but I have no need for such a flag. The other day, I took this work of art out from behind the bedroom door and transformed it into a 2-meter antenna. I measured off approximately 4 feet (1.2 meters) of wire, brought it down the "flag pole" and wound a ten-turn coil at the bottom. I had a coaxial chassis connector (with a missing center conductor) which I drilled to fit the plastic pole. I then soldered on four 20-inch (50-cm) radials made of No. 12 (2.1-

mm) wire. I wrapped the pole with tape, just under the radials, to hold them at the proper level. I soldered the shield of some RG-58/U cable to the radials, and the center conductor to the bottom of the coil.

I fired up the 2-meter rig, and connected an SWR meter into the line; it showed about 2.5:1. I took off a turn of wire; this dropped the SWR to 2:1. I then started cutting the vertical wire an inch at a time, and cut once too often. By pushing all of the coil turns tight together, I came up with 1.1:1 — close enough.

The photograph shows the bicycle-flag antenna in place on the house.

**Bob Baird, W7CSD**

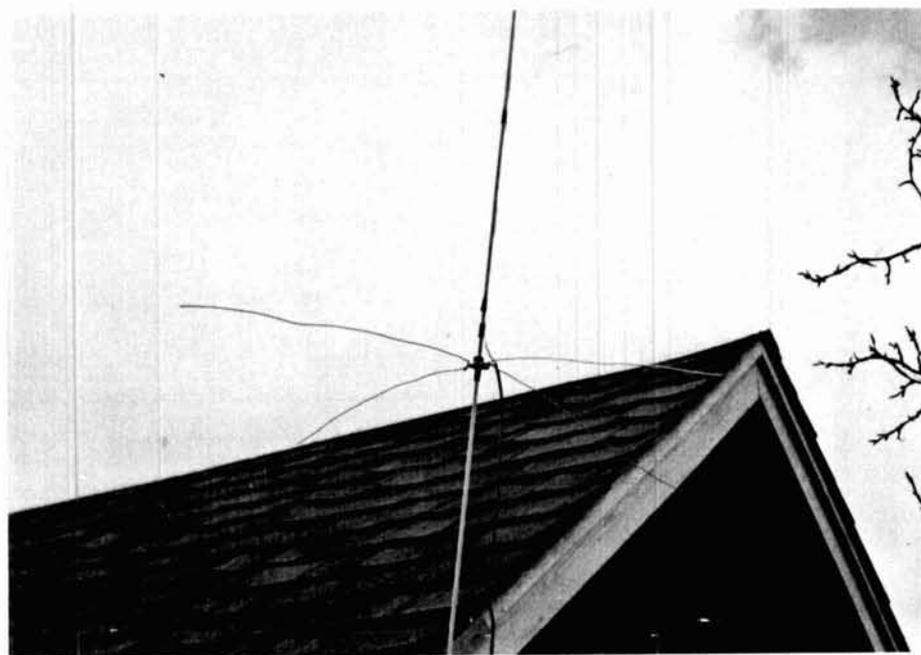

## the best way to get an antenna into a tree

For many years the Los Alamos Amateur Radio Club has set up Field Day in the nearby Jemez Mountains, which are well supplied with tall Douglas fir and spruce trees. Each year we struggled with the problem of getting the antennas up into the trees. We've tried everything: climbing, throwing a weighted line, using a bow and arrow. Finally, about three years ago, K5QIN developed an ingenious but inexpensive device, which was the ultimate solution.

A slingshot was wedged to a spin-casting reel. The *Wrist Rocket* brand slingshot uses surgical rubber tubing as the elastic; it's surprisingly powerful. Fastened to the handle of the slingshot is the spin-casting reel. A one-ounce sinker is tied to the fish line. For ease of finding the sinker, I tied on a piece of bright red tape.

To use, merely unlock the reel, stand near the base of the tree, and fire upward at about a 60-degree angle. The weight easily clears 60-80 foot (18-24 meter) trees, and almost invariably falls all the way to the ground. Remove the sinker from the end of the line (cut it — fish line is cheap) and tie on a light nylon twine, such as 50-120 pound (23-54 kg) test. Then reel back the fish line steadily, until the twine returns to the ground. You can then connect whatever stronger line is needed to raise the antenna.

The advantages of this system are these:

1. It's inexpensive. I bought a spin-cast reel on sale for less than \$3, spent \$5 on the slingshot, and got 2000 feet (610 meters) of 6-pound-test (2.7-kg) monofilament for about

\$1.25. One ounce (28.4g) sinkers cost about 12 cents.

2. If the line becomes tangled, just break it, abandon it, and try again. This is not the case with a bow and arrow, as archers are reluctant to lose expensive arrows.

3. The small weight rarely tangles in the trees.

We have built several of these and find them among the handiest devices ever invented.

Alan Hack, WA5VLX

## antenna bridge calculations

Here is a composite version, using the TRS80, Level 2, of Anderson's fine series of programs, first listed in the May, 1978, issue of *ham radio*. Readers should refer to that article for the formulas used and other background material.

Lines 10, 17, 20, and 300, as written, should duplicate the results given in **programs 1** and **2** using the same input data, and can be edited as required.

Paul Manacek, K6GK

```

5 Print, "Smith Chart Rotation"      ↗ = "UP ARROW"
6 Print; Print
8 Input "Enter next freq. in mhz";F
10 Z0=50
12 Input "Enter noise bridge 'RP' Reading";R
15 Input "Enter noise bridge 'C' reading in picos";C
17 V=.66
20 L=60
35 R1=.006388
45 X= -1.59155/(F*C)
50 A=(R*X/2)/(R/2+X/2)
60 B=(X*R/2)/(R/2+X/2)
65 Input "Enter value of series extender (0 if not used)";SE
75 Print
80 A1=A-SE
85 Print "The line input Z (RG,XG)="A1,B
90 A2=SQR((A1+Z0)/2+(B/2))
95 B2=SQR((A1-Z0)/2+(B/2))
100 Print "the swr is", (A2+B2)/(A2-B2)
110 K=R1*(L/V)
120 XK= Tan (K*F)
130 RG=A1
140 XG=B
150 RO=Z0
160 A=(XG-RO*XK
170 B=(RO+XG*XK)
180 D=RG*XK
190 N= -D
200 X=((RG*B)+(A*N))/(B*B+N*N)
210 Y=((B*A)-(R*N))/(B*B+N*N)
220 Z=X*RO
230 J=RO*Y
240 Print
250 Print "Antenna Z (No-Loss Line) is";Z,J
260 A2=SQR((Z+RO)/2+(J/2))
270 B2=SQR((Z-RO)/2+(J/2))
280 Print "The SWR is", (A2+B2)/A2-B2)
290 Print
300 DB=.8
310 N=8.686
320 E=2.718282
330 A=DB/N
340 B=K*F
350 D=E/(4*A)=1+2*E/(2*A)*Cos(2*B)
360 RA=((E/(4*A)-1))/B
370 B1=2*E/(2*A)*Sin(2*B)
380 A2=D
390 P=A2*A2
400 M=(A2+B1)/(A2*A2)
410 Print
420 Print "Complex Attenuation Factors (RA,XA)=";RA,M
430 Print
440 Print "Next rotation is for Lossy Lines": Print
450 Input "Enter RG from top of screen";RS
460 Input "Enter XG";XG
470 Input "Enter RA";RA
480 Input "Enter XA";XA
490 A4=(RS-RA*RO)
500 B4=(RO-RS*RA+XG*XA)
510 D4=RA*XG
520 G4=RS*XA
530 H4=C4
540 I4=D4+G4
550 L4=RO*XA
560 M4=O4
570 N4=XG-I4
580 O4=A4+M4
590 P4=N4
600 Q4=B4-H4
610 T4=I4
620 V4=((O4*Q4)+(P4*T4))/(Q4*Q4+T4*T4)
630 W4=((Q4*P4)-(O4*T4))/(Q4*Q4+T4*T4)
640 Y4=(V4*RO)
650 Z4=RO*W4
660 Print;Print
670 Print "Antenna Z, (lossy line) is",Y4,Z4
680 Print
690 A3=SQR((Y4+RO)/2+(Z4/2))
700 B3=SQR((Y4-RO)/2+(Z4/2))
710 Print "The Swr, with losses, is", (A3+B3)/(A3-B3)
720 Print;Print
730 Run 8

```

# Homebrew Headquarters

## — COMPONENTS —

- Amphenol connectors
- B & W coils, switches, antennas
- Hammond and LMB enclosures
- Jackson dials and drives
- J.W. Miller parts
- Knobs and shaft couplers
- Millen components
- Multronics roller inductors
- Padders and trimmer capacitors
- Resistors, capacitors, inductors
- Semiconductors
- Toroids, cores, beads, baluns
- Variable capacitors:
  - Cardwell — E.F. Johnson
  - Hammarlund — Millen
- Wire and cable

## — KITS —

Microcomputer-based Contest Keyer (hr 1/81) partial; CMOS 2-Meter Synthesizer (hr 12/79) partial; 40-Meter QRP Transceiver (hr 4/80) partial or complete; Split-band Speech Processor (hr 9/79); IARU Rx and Tx (QST 4/78 & 12/78); W1JR Broadband Balun (hr 4/79); R-X Noise Bridge (hr 2/77); Memory Accu-Keyer (hr 4/79) boards only.

Catalog 25 cents

# RADIOKIT

Box 411H, Greenville, NH 03048  
(603) 878-1033

# the Ultimate IAMBIC PADDLE

WRITE FOR LITERATURE

## BENCHER, INC.

333 W. Lake Street, Dept. A  
Chicago, Illinois 60606 • (312) 263-1808

Standard \$ 42.95  
Chrome \$ 52.95  
Gold plated \$150.00

- Full range of adjustment in tension and contact spacing.
- Self-adjusting nylon and steel needle bearings.
- Gold plated solid silver contact points.
- Polished lucite paddles.
- Precision-machined, chrome plated brass frames.
- Standard model has black, textured finish base; deluxe model is chrome plated.
- Heavy steel base; non-skid feet.

At selected dealers or add \$2.00 handling. Quotation for overseas postage on request.

## Microcraft's New RTTY READER



Decodes RTTY signals directly from your receiver's loudspeaker. \* Ideal for SWLs, novices & seasoned amateurs. \* Completely solid state and self-contained. Compact size fits almost anywhere. No CRT or demodulator required. . . . Nothing extra to buy! \* Built-in active mark & space filters with tuning LEDs for 170, 425 & 850 Hz FSK. \* Copies 60, 67, 75, & 100 WPM Baudot & 100 WPM ASCII. \* NOW you can tune in RTTY signals from amateurs, news sources & weather bulletins. The RTTY READER converts RTTY

signals into alphanumeric symbols on an eight-character moving LED readout. Write for details or order factory direct.

RTTY READER KIT, model RRRK . . . . . \$189.95  
RTTY READER wired and tested, model RRF . . . . . \$269.95  
Send check or money order. Use your VISA or MasterCard. Add \$5.00 shipping and handling for continental U.S. Wisconsin residents add 4% Wisconsin State Sales Tax.

*Microcraft*

Corporation Telephone: (414) 241-8144  
Post Office Box 513HR, Thiensville, Wisconsin 53092

## MICROWAVE TELEVISION

The RP series of complete 2350 MHz downconverter packages for amateur television connect to any standard television set and provide all you need for microwave television viewing.

The standard RP package contains a microstrip converter mounted in a widely used cavity-type microwave antenna. The antenna includes a 36" disc-rod assembly that increases the overall system conversion gain to 38 dB. An attractive set-top power supply with a tuning control that covers three tv channels is included along with all antenna mounting hardware and instructions.

With this package, you are ready for amateur television. Just aim the antenna, connect one 75Ω coaxial line from the antenna to the power supply and a second coaxial line from the power supply to your tv, and you are on the air.

For installations greater than 15 miles, the RP+ package, which uses a higher gain RF stage in the converter, is recommended. Beyond 25 miles, or for installations where a separate antenna is available, the RPC package is available. In this package, the converter is mounted in a separate weather-proof case and is provided with a 50Ω input impedance N connector.

All models use a downconverter built using microstrip construction for long reliable operation. The downconverter contains a low noise preamplifier, a balanced mixer, a trimmed local oscillator, and a broadband output amplifier matched to 75 ohms.

Prices including UPS shipment are as follows:

Model RP receiver package . . . . . \$175  
Model RP+ receiver package . . . . . \$200  
Model RPC receiver package . . . . . \$200

To order your receiver package now, send check or money order to:

K. & S. Enterprises  
P.O. Box 741, Mansfield, MA 02048

## RED HOT SPECIALS

AZDEN PCS-3000, 2 meters . . . . .	315.00
ICOM 260A, All Mode, 2m . . . . .	425.00
KANTRONICS CODE READER . . . . .	360.00
BEARCAT 300 SCANNER . . . . .	357.00
BEARCAT 220 or 250 SCANNER . . . . .	269.00
ICOM IC 255A, 2 meters . . . . .	310.00
SWAN ASTRO 150, New Style . . . . .	750.00
ICOM IC251A, 2m All Mode . . . . .	615.00
JANEL QSA 5, 2m Pre Amp . . . . .	36.50
ICOM IC2A HANDHELD w/ Nicad . . . . .	215.00
with Touch Tone Pad . . . . .	239.00
ICOM 551, 6 meters . . . . .	408.00
ALL MFJ PRODUCTS . . . . .	12% off List

Write for our Large Specials and Used Equipment Lists

## BEN FRANKLIN ELECTRONICS

115½ N. Main Hillsboro, KS 67063  
316-947-2269

## GRID DIP METER

AN/PRM-10 Test Oscillator, a grid dip meter designed to determine resonant frequencies of tuned circuits or the frequency of RF signals. Uses seven plug-in coils in ranges 2-5, 5-10, 10-22, 22-45, 45-100, 100-250, and 250-400 Mhz; 1 KHz internal modulation. Results indicated on meter or can be heard when used with headphones.



Set includes tuning head, coils, 115 VAC power supply, case, and schematic. Head 7x3¼x2¾" on 6' cord, 20 lbs. sh. Used, checked: \$125.00

Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted.  
Allow for Shipping • Send for NEW FREE CATALOG!  
Address Dept. HR • Phone: 419/227-6573

FAIR RADIO SALES  
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802



**CALL TOLL FREE  
1-800-426-7741**



**The Northwest's Largest Ham Store**  
WASHINGTON RESIDENTS CALL 1-800-562-6818  
ALASKA RESIDENTS CALL COLLECT 1-206-784-7337

**AEA  
MORSEMATIC**



- Dual Microcomputers provide many features.
- Approximately 500 character memory with unique "soft-partitioning."
- Morse trainer mode with programmable speed-up.
- Beacon mode for VHF DX scheduling.
- Automatic serial number sequencing.
- For too many features to describe; use it and you will believe it!

**AEA ISOPOLE  
VHF ANTENNAS**

Finally — a properly decoupled antenna with superior performance at a reasonable cost. Raise more repeaters or increase your simplex distance!

- 144 or 220 MHz bands.
- Achieve maximum attainable gain for a twin 5/8 wavelength antenna.
- Patterns independent of mounting or feedline length.
- Greater than 9 MHz band width.
- Completely weather protected matching network and RF connections.
- Easiest to assemble. Mounts on standard TV master (NOT SUPPLIED).



**D800/D802  
DIGITAL MULTIMETERS**



Measures AC and DC voltage and current, resistance and diode test. Conductance also included in D802. Basic DC accuracy 0.5% D800, 0.1% D802. Complete with test leads, battery and manual.

**Only  
\$125 (D800)  
\$179 (D802)**


**C-COMM**  
6115-15th AVE. N.W.  
SEATTLE, WA. 98107  
(206) 784-7337

**Dealers For:** AEA, ALLIANCE, ALPHA, AVANTI, BENCHER, B&W, CDE, CUSHCRAFT, DAIWA, DENTRON, DRAKE, FLUKE, HUSTLER, HYGAIN, ICOM, INLINE, KLM, LARSEN, LUNAR, MFJ, NPC, NYE, ROHN, SHURE, TEMPO, TELEX, TEN-TEC, VIBROPLEX, YAESU, AND MORE.

Mon. thru Sat. 9:00 a.m. to 5:30 p.m.

Prices and specifications subject to change without notice or obligation

trans com inc.

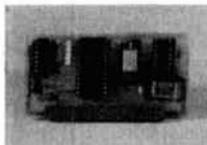

**1021 Touch  
Tone Decoder**

The 1021 Touch Tone decoder is ideal for repeater control. Design your own or use with our 102 DTMF Controller.

**Features:**

- ★ Decodes All 16 Digits
- ★ Binary and Strobe outputs as well as 16 discreet outputs
- ★ 5VDC or 7-20VDC operation
- ★ Current consumption of 4 mA@5VDC
- ★ Measure 3.5"x1.9"x.4"
- ★ Dialing speed to 20 PPS

**PRICED AT \$154.95**

**401 Sub-Audible Tone Encoder  
For the ICOM IC2A/AT**



**The model 401 features:**


- ★ Fits IC2A/AT and most other hand held radios
- ★ Compatible with PL, CG, and most other CTCSS systems
- ★ Fully tuneable from 76.0 Hz to 251 Hz
- ★ Operating voltage is 7-15VDC@4mA
- ★ Adjustable tone level. 0-2 VPP
- ★ Small size 1.0"x.6"x.3"

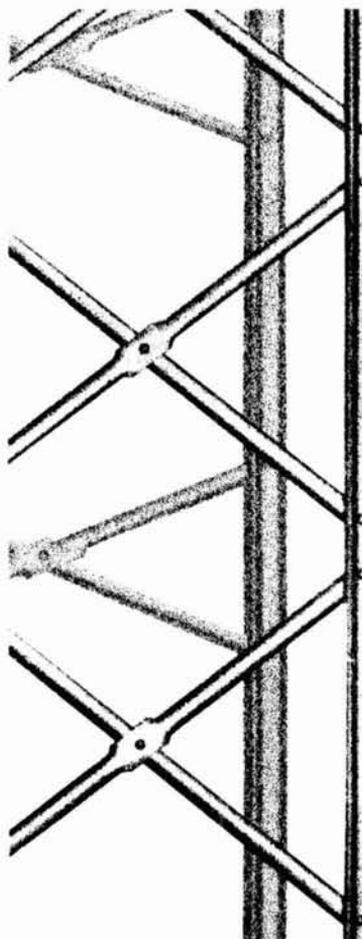**PRICED AT \$29.95**

Send check or money order. Use VISA or Master Charge. IL residents add 5 1/4 % state tax plus \$2.00 S&H. To order or for more information contact:



1104A Ridge Ave., Lombard, IL 60148  
(312) 932-1491



**Rohn  
'BX' TOWERS**

- For Home TV, Ham Radio and CB.
- Up to 18 sq. ft. antenna capacity.
- Available to 64' in 8' sections.
- All riveted construction — no welds.
- Beaded channel leg for added strength.
- All steel — galvanized for added life.
- Can be used with Concrete Base Stubs, Cylinder Base or Hinged Concrete Base.

**UNR-Rohn**

Division of UNR Industries, Inc.  
6718 West Plank Road, P.O. Box 2000  
Peoria, Illinois 61656  
U.S.A.

# MIDCOM



**NOW IN STOCK...  
FULL LINE OF AEA KEYERS  
SUPER EFFICIENT ISOPOLE ANTENNAS**



**LINES:**

AEA	ALPHA	CUSHCRAFT	DENTRON	KLM	MOR GAIN	PALOMAR ENG.	UNIVERSAL
AVANTI	BEARCAT	COLLINS	HY GAIN	KENWOOD	MIRAGE	REGENCY	UNARCO-ROHN
ASTRON	BIRD	CDE	HUSTLER	MICROLOG	MFJ	SWAN	VIBROPLEX
ALLIANCE	BENCHER	DRAKE	ICOM	MINI-PRODUCTS	NYE	TEN TEC	KANTRONICS

**CALL TOLL FREE 1-800-325-3609** IN MISSOURI 314-961-9990  
MID-COM ELECTRONICS • 8516 MANCHESTER ROAD • BRENTWOOD, MO 63144




## IMPROVE YOUR LISTENING. !



100,000 accurate frequencies, agencies and locations  
**\$14.95 Plus \$3.00 U.P.S.**

### SCANNER BEAM

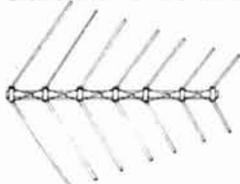

**NEW MONITOR ANTENNA**  
Up to 8dB gain, 108-512 MHz  
**\$39.95 Plus \$4.00 U.P.S.**

Send for **FREE**  
Catalog of accessories  
and publications

Shipping within  
48 hours

Payment must  
accompany order



Identify those strange sounds  
Professional listening tips  
60 minute cassette  
**\$5.95 Plus \$1.00 shipping**

**order desk**  
**TOLL FREE 1-800-438-8155**


• **DEALER INQUIRY INVITED** •

"...SEARCHING FOR THE SOUNDS OF TOMORROW."

**GROVE ENTERPRISES INC**

Dept. Y  
BRASSTOWN, NORTH CAROLINA 28902

# New!

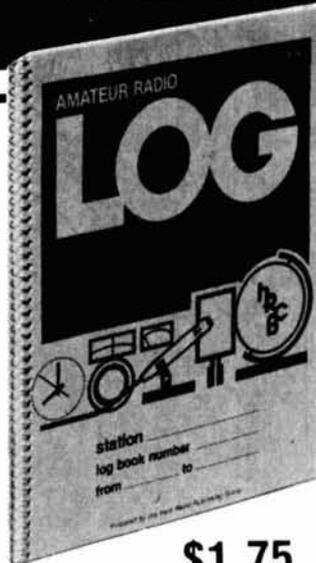


**Twice as  
much for less.**

**HR-LB** Here's the log book everyone is talking about. This new offering from HRB is far superior to any other log available today! With over 2,000 entries, you have twice as much space for less cost in comparison to its nearest competitor. There are 80 big (8½ x 11) pages, 30 entries per page for an "easy-count" during contests, a frequency spectrum chart, call sign prefixes and much more. This is unquestionably the best log book value anywhere. 80 pages. ©1978. Spiralbound.

**\$1.75**

Send check, money order or credit card information plus \$1.00 shipping to:  
**Ham Radio's Bookstore**  
Greenville, NH 03048

# flea market

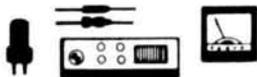

**RATES** Noncommercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. Ham Radio cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**CW/SSB FILTERS:** IC audio install in any radio, sharp CW, stagger tuned SSB — \$15, \$32. SASE info: W8CBR, 80 W. Mennonite, Aurora, OH 44202.

**QSLs & RUBBER STAMPS** — Top Quality! Card Samples and Stamp Info — 50¢ — Ebbert Graphics 5R, Box 70, Westerville, Ohio 43081.

**MOTOROLA RADIOS WANTED:** I need micors, motracs, mocom 70's, H.T.'s, and bases . . . anything Motorola newer than 12 years. I pay all shipping. Len Rusnak, WA3TJO 301-441-1221.

**CRYSTALS FM 2 METERS STILL AVAILABLE!** Crystals for equipment on our parts list, \$4.50 each. For equipment list, send self addressed stamped envelope. SAVOY ELECTRONICS, P.O. Box 5727, Ft. Lauderdale, FL 33310 — Tel. (305) 563-1333.

**WANTED:** Motorola micor base stations. 406-420 MHz. AK7B, 4 Ajax Pl., Berkeley, CA 94708.

**TUBE TESTER,** dynamic plate conductance, Jackson Elec. Inst. model 648S, new with latest roll chart, \$75.00 or best offer. F.O.B. Fort Pierce, FL, F. Pierce, 403 Susan Dr., W4OZS.

**HELP!** A Baptist church affiliated youth summer camp needs Ham help. 2 Meter and HF radios are urgently needed to provide emergency communications from an Appalachian mountain site to the nearest phone, which is five miles away. Donated equipment is tax deductible. Contact Richard Bailey, Amity, PA 15311. (412) 225-1265.

**WANTED:** Collins 455 kHz mechanical filters, F455 variety. Give me bandwidth, condition and price. W9JTO, Paul Sexauer, 515 Lee Road, West Chicago, IL 60185.

**MANUALS** for most ham gear 1937/1970. Send 25¢ for "Manual Catalog." H.I., Inc., Box H864, Council Bluffs, Iowa 51502.

**SATELLITE TELEVISION:** Information on building or buying your earth station. Six pages of what's needed, where to get it, costs, etc. \$4.00 to Satellite Television, RD #3, Oxford, NY 13830.

**ATLAS DD6-C and 350XL Digital Dial/Frequency Counters.** \$175.00 plus \$3.00 UPS. AFC! Stop VFO drift. See June 79 HR. \$65.00 plus \$3.00 UPS. Mical Devices, P. O. Box 343, Vista, CA 92083.

**WANTED:** Help in completing the largest collection of Hallicrafter equipment in the world. Urgently needed are receivers with aluminum colored panels, back lighted plastic dials with "airplane" hands, early transmitters, unusual accessories, etc. Chuck Dachis, WD5EOG, "The Hallicrafter Collector," 4500 Russell Drive, Austin, Texas 78745.

**WANTED:** Cushman Communications Service Monitors, working or non-working units. Also need plug-in modules, manuals, parts, etc., will pay cash or take over payments. Also need RF voltmeters; WB8JX, Fred L. Slaughter, 5844 Grisell Road, Oregon, OH 43618. Phone (419) 698-8597.

**WANTED:** L5B and CW xtal filters for a TR6. Jim Gysan, W1VYB, (617) 922-3850.

**ELECTRONIC BARGAINS, CLOSEOUTS, SURPLUS!** Parts, equipment, stereo, industrial, educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog. ETCO-012, Box 762, Plattsburgh, NY 12901. SURPLUS WANTED.

**ANTIQUE RADIO EQUIPMENT:** Hallicrafters "Sky-Buddy" receiver in fair condition and Hallicrafters speaker model R-42 in excellent condition (designed for use with SX-42). Best offer, contact Bob Schrader, W0PVL, 1521 N. Webster, Liberal, KS 67901.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 98362.

**YAESU FT-277R** transceiver (mint) \$200.00, Galaxy Comm IC transceiver w/P.S. unit for R390A rrv. David Johanson, 423 N. 3rd St., Fort Dodge, IA 50501 (515) 955-7185.

**ETCH IT YOURSELF PRINTED CIRCUIT KIT,** Photo-Positive Method — No darkroom required. All the supplies for making your own boards, direct from magazine article in less than 2 hours. Only \$24.95, S.A.S.E. for details: Excel Circuits Co., 4412 Fernlee, Royal Oak, MI 48073.

**ANNOUNCING A New Ham Radio Recognition and Reference Volume.** "WHO'S WHO IN AMATEUR RADIO". Details SASE, Users International Radio Clubs, 606 Brack Rd., Ft. Pierce, FL 33450.

**HAM RADIO REPAIR** — Professional lab, personal service. "Grid" Gridley, W4GJO. April thru October: Rt. 2, Box 138B, Rising Fawn, Georgia 30738. (404) 657-7841. November thru March: 212 Martin Drive, Brooksville, Florida 33512. (904) 799-2769.

**FOR SALE:** One Hallicrafter HT-40 Transmitter. Write W9HVZ in Lancaster, WI 53813.

**YAESU FRG-7** \$200., Icom 230 \$150., Midland 13-509 \$150., Wilson Handytalky 1402 \$75. WA6JYU (415) 897-3987.

**LINEAR AMPLIFIER PLAN BOOK II,** 13 plans, 1.6 to 400 MHz, 15 to 1000 watts, 92 pages, \$11.95, CB modification kits, crystals, de-scrammers, other titles, electronic flea market and more in our catalog, \$1.00 refundable. A.P. Systems, P.O. Box 263HR, Newport, RI. 02840.

**WILSON WE-800** synthesized 2 meter xcvr, wall charger, flex antenna, Larsen NMO-150 quarter wave antenna and quick release bracket for \$240.00, post paid. Ed Roth, WA5YXX, 207 Forest Hill Dr., Warner Robins, GA 31093.

**BUY-SELL-TRADE** Send \$1.00 for catalog. Give name address and call letters. Complete stock of major brands new and reconditioned amateur radio equipment. Call for best deals. We buy Collins, Drake, Swan, etc. Associated Radio, 8012 Conser, Overland Park, KS 66204. (913) 381-5900.

DIGITRAN MINI KEYBOARD PHONE FORMAT 2-3/4" x 2" 1/4" THICK SWS-0234 \$5.95		SEND FOR FREE CATALOG				
12 VDC CDAX RELAY SPDT 450 MHZ+ 100 WATTS 2 MALE RCA PLUG TO SO-239 RL-0042 \$6.95	BLACK TOUCH-TONE HOUSING, TT-0191 \$3.95					
TWO METER ANTENNAS: BNC ADJ. ELDDW AN-0067 \$7.95 BNC STRAIGHT AN-0065 \$7.95 BNC DUCKIE AN-0269 \$8.95						
UHF-M/CABLE PL-250 \$ 7.75 UHF-F/PANEL SO-239 \$ 6.65 UHF-F/UHF-F PL-25B \$1.50 UHF-M/UHF-M DM-1 \$2.50	BNC-M/CABLE UG-88 \$1.00 BNC-F/PANEL UG1094 \$1.35 BNC-F/BNC-F UG-914 \$2.25 BNC-M/BNC-M UG-491 \$2.85	UHF 90° F/M M-359 \$2.50 UHF-T'2F/M M-358 \$2.95 BNC 90° F/M UG-306 \$3.75 BNC-T'2F/M UG-274 \$4.00				
BNC-M/UHF-F UG-255 \$3.75 BNC-F/UHF-M UG-273 \$3.00 N' F/UHF-F UG-83 \$4.95 N' M/UHF-F UG-146 \$4.95	N' M/CABLE UG-21 \$2.95 N' F/PANEL UG-58 \$2.25 N' F/N' F UG-29 \$3.00 N' M/N' M UG-57 \$4.95	N' 90° F/M UG-27 \$4.50 N' T'2M/F UG-107 \$9.50 N' M/BNC-F UG-201 \$3.65 N' F/BNC-M UG-349 \$4.95				
<table border="1"> <tr> <td>M</td> <td>P</td> </tr> <tr> <td>J</td> <td>A</td> </tr> </table> <b>Marlin P. Jones &amp; Assoc.</b> <b>P.O. Box 12685 E</b> <b>Lake Park, Fl. 33403</b> <b>(305) 848-8236</b> MC, VISA, COD-ADD. \$1. IF UNDER \$10. FL. RES. 4% ADD SUFFICIENT POSTAGE			M	P	J	A
M	P					
J	A					

## Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria F. Bassi Hauptplatz 5 A-2700 Wiener Neustadt Austria	Ham Radio Holland MRL Electronics Postbus 86 NL-2204 Delft Holland
Ham Radio Belgium Stereohouse Brusselsesteenweg 416 B-9218 Gent Belgium	Ham Radio Italy G. Vulpetti P.O. Box 37 I-22063 Cantu Italy
Ham Radio Canada Box 400, Goderich Ontario, Canada N7A 4C7	Ham Radio Switzerland Karin Ueber Postfach 2454 D-7850 Loerrach West Germany
Ham Radio Europe Box 444 S-194 04 Uplands Vasby Sweden	Ham Radio UK P.O. Box 63, Harrow Middlesex HA3 6HS England
Ham Radio France SM Electronic 20 bis, Ave des Clarions F-69000 Auxerre France	Holland Radio 143 Greenway Greenside, Johannesburg Republic of South Africa
Ham Radio Germany Karin Ueber Postfach 2454 D-7850 Loerrach West Germany	

# Now An 8044 with Speedmeter\*

## from CURTIS

* EK-480: C-MOS Deluxe Keyer	\$134.95
* EK-480M: Above plus speedmeter	149.95
* I-480: InstructoMate	124.95
* M-480: MemoryMate	124.95
* IM-480: Instructo-MemoryMate	179.95
* KB-480: Morse KeyboardMate	199.95
* KB-4900: Morse-RTTY keyboard	379.95
Above prices FOB factory	
8044: Keyer-On-A-Chip (ARRL HG2 77-81)	14.95
8044-3: IC, PCB, Socket, Manual	24.95
8044-4: Semi-Kit	54.95
*8044M (incl. speedmeter funct.) add \$5.00	
8045: Morse Keyboard-On-A-Chip IC	59.95
8045-1: IC, PCB, FIFO, Sockets, Manual	89.95
8045-2: Semi-Kit	159.95
8046: Instructokeyer-On-A-Chip IC	49.95
8046-1: Semi-Kit	79.95
8047: Message Memory-On-A-Chip IC	39.95
8047-1: IC, PCB, RAM, Sockets, Manual	69.95
(add \$1.75 on kits for postage and handling)	

Curtis Electro Devices, Inc.  
 (415) 494-7223  
 Box 4090, Mountain View, CA 94040

## When it comes to AMATEUR RADIO QSL's...



it's the  
**ONLY BOOK!**  
US or DX Listings

1981  
**callbooks**  
NOW READY!

Here they are! The latest editions. World-famous Radio Amateur Callbooks, the most respected and complete listing of radio amateurs. Lists calls, license classes, address information. Loaded with special features such as call changes, prefixes of the world, standard time charts, worldwide QSL bureaus, and more. The U.S. Edition features over 400,000 listings, with over 100,000 changes from last year. The Foreign Edition has over 300,000 listings, over 90,000 changes. Place your order for the new 1981 Radio Amateur Callbooks, available now.

	Each	Shipping	Total
<input type="checkbox"/> US Callbook	\$17.95	\$2.55	\$20.50
<input type="checkbox"/> Foreign Callbook	\$16.95	\$2.55	\$19.50

Order both books at the same time for \$37.45 including shipping.

Order from your dealer or directly from the publisher. All direct orders add \$2.55 for shipping. Illinois residents add 5% sales tax.



**SPECIAL LIMITED OFFER!**  
Amateur Radio  
Emblem Patch  
only \$2.50 postpaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on jackets and caps. Sorry, no call letters.

**ORDER TODAY!**

**RADIO AMATEUR**  
**callbook** INC.  
Dept. .... F  
925 Sherwood Drive  
Lake Bluff, IL 60044, USA

**ICOM, KENWOOD OWNERS** — Separate, Very Informative Newsletters. Details SASE U.I.R.C. 606 Brack Road, Fort Pierce, FL 33450.

**MIRROR-IN-THE-LID**, and other pre-1946 television set wanted. Paying 500+ for any complete RCA "TRK" series, or General Electric "HM" series set. Also looking for 12AP4, MW-31-3 picture tubes, parts, literature on pre-war television. Arnold Chase, WA1RYZ, 9 Rushleigh Road, West Hartford, Conn. 06117 (203) 521-5280.

**AMATEUR REPAIR:** Professional service, reasonable rates, ALL brands. USA KDK repair center. Amateur Radio Repair Center, 1020 Brookstown Ave., Suite 5, Winston-Salem, NC 27101 (919) 725-7500.

**YAESU YO-100** monitor scope with manual and original carton, \$145. Comdel RF speech processor, connects between mike and rig, \$85. John Skubick, K8JS, 791-106 Ave., Naples, FL 33940.

**ATLAS 350XL**, DD6 Readout, VFO 350, PS350, Mobile mount. System in excellent condition. \$859. AE5E, Bill, (713) 898-1743.

**500 QSL's**, \$10. Catalogue, 743 Harvard, St. Louis, MO 63130.

**VERY in-ter-est-ing!** Next 6 issues \$2. Ham Trader "Yellow Sheets", POB356, Wheaton, IL 60187.

**DX, YOU BET! THE DX BULLETIN** — Best weekly DX info in the world. For FREE sample copy, send business-size SASE to: The DX Bulletin, 306 Vernon Avenue, Vernon, Connecticut 06066.

**STOP LOOKING** for a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. Now more than ever where you buy is as important as what you buy. We are factory-authorized dealers for Kenwood, Drake, Yaesu, Collins, Wilson, Ten-Tec, ICOM, DenTron, MFJ, Tempo, Regency, Hy-Gain, Mosley, Alpha, CushCraft, Swan and many more. Write or call us today for our low quote and try our personal and friendly Hoosier Service. HOOSIER ELECTRONICS, P.O. Box 2001, Terre Haute, Indiana 47802. (812) 238-1456.

**UPGRADE SUCCESSFULLY!** Pass FCC Exams! TRS-80 owners, I'll show you how! KE7C, H-2665 Busby Road, Oak Harbor, WA 98277. SASE please.

**CB TO 10 METER PROFESSIONALS:** Your rig or buy ours — AM/SSB/CW. Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412; (616) 924-4561.

**TRANSMITTER TECHNICIANS** — Voice of America has overseas positions available at supervisory and operating levels for experienced transmitter technicians. Duties include operation and maintenance of high power VOA transmitters and related facilities. Applicants must have 3 to 5 years "hands-on" experience in technical operation of broadcast, TV or military fixed-station transmitters. Must be available on a worldwide basis to serve in VOA's radio relay station system. U.S. citizenship required. Starting salary commensurate with qualifications, plus housing and overseas allowances. Full federal fringe benefits apply. Qualified candidates should send standard Federal application form SF-171 to International Communication Agency, MGT/PDE, 1776 Pennsylvania Ave., Washington, D.C. 20547. An Equal Opportunity Employer.

**QSL'S:** No stock designs! Your art or ours; photos, originals, 50¢ for samples & details (refundable). Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412.

**NEED HELP** for your Novice or General ticket? Recorded audio-visual theory instruction. No electronic background required. Free information. Amateur License, P.O. Box 6015, Norfolk, VA 23508.

**QSL'S WITH CLASS!** Unbeatable quality, reasonable price. Samples: 50¢ refundable. QSLs Unlimited, 1472 S.W. 13th St., Boca Raton, FL 33432.

**CB TO 10-METER CONVERSIONS.** SSB/AM/CW. Let a specialist convert your rig, or buy one complete. Write Conversion Engineering, Box 183, Sandwich, Massachusetts 02563.

**MAKE HAM RADIO FUN!** Supplement your learning programs with a motivational hypnosis cassette. Tape #3, Learning the Code; Tape #4, Breaking the Speed Barrier; Tape #7, Electronics Theory. Free catalog. For tapes send \$10.95 to John Wolf Hypnosis Center, P.O. Box 497, Hayden, Idaho 83835.

**"CADILLAC" of QSL'S** — FAST 100 - \$9.95 — Our Design. Send \$1.00 for Samples-Refundable. MAC'S SHACK, P.O. Box 43175, Seven Points, Texas 75143.

**HAMS FOR CHRIST** — Reach other Hams with a Gospel Tract sure to please. Clyde Stanfield, WA6HEG, 1570 N. Albright, Upland, CA 91786.

# NEW FROM GLB

A complete line of **QUALITY 50 thru 450 MHz TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. **4 pole crystal filter is standard.** Use with our **CHANNELIZER** or your crystals. Priced from **\$69.95**. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from **\$29.95**.

**SYNTHESIZER KITS** from 50 to 450 MHz. Prices start at **\$119.95**.

Now available in **KIT FORM** — **GLB Model 200 MINI-SIZER**.

Fits any HT. Only **3.5 mA** current drain. Kit price **\$159.95** Wired and tested. **\$239.95**

Send for **FREE 16 page catalog**. We welcome Mastercharge or VISA

**GLB ELECTRONICS**  
1952 Clinton St., Buffalo, N. Y. 14206

## GO MOBILE WITH YOUR H.T.!



**Handi-Tek Regulator** ALLOWS CONTINUOUS HAND-HELD OPERATION FROM AUTO DC OR BASE SUPPLY WITH NO NI-CAD DRAIN. MODEL K - TR2400 MODEL Y - FT-207R, MK II, MK IV MODEL T - SIMPLE MOD FOR TEMPO S-1, S-2, S-5. GUARANTEED. \$19.95 PPD IN USA. CAL ADD \$1.20 ORDER DIRECT OR SEND FOR SPECS...

HANDI-TEK  
P.O. BOX 2205, LA PUENTE, CA 91746

## SPECIAL! PCS-3000

# AZDEN

only \$315.<sup>00</sup>  
Includes T.T. Pad

You'll have more fun and excitement on 2 meter FM with the AZDEN PCS 3000 because of its popular, state-of-the-art convenience features such as micro-computer controlled full band scan and memory functions, CMOS PL digital synthesized, detachable control head, excellent receiver sensitivity, 25 watts out and much more.

Free U. P. S. — 90 day factory warranty



**N.P.S. Inc. WA3IFQ**

1138 Boxwood Rd. • Jenkintown, PA 19046  
1-215-884-6010

**Get your  
TEN-TEC  
'money-back  
guarantee'  
transceiver  
from AES**  
CALL TOLL FREE  
**1-800-558-0411**  
In WI (outside Milwaukee metro)  
**1-800-242-5195**

**AMATEUR  
ELECTRONIC  
SUPPLY®** inc.  
4828 W. Fond du Lac Avenue  
Milwaukee, WI 53216 (414) 442-4200  
— AES BRANCH STORES —  
Wickliffe, OH 44092; 28940 Euclid Ave.  
(216) 585-7388; OH Wats 1-800-362-0290  
Orlando, FL 32803; 621 Commonwealth Ave.  
(305) 894-3238; FL Wats 1-800-432-9424  
Las Vegas, NV 89106; 1072 N. Rancho Dr.  
(702) 647-3114; Outside NV 1-800-634-6227

## IRS

(Interstate Repeater Society)

presents

## AUCTIONFEST '81

**MARCH 21**

- Bring your money —
- Bring your used gear —

## AUCTION

Used Equipment Room

Manufacturers' & Dealers' Displays

Evening Banquet

at the

**HILTON AT MERRIMACK**  
Merrimack, NH  
(1/4 mi. from the Merrimack Tollgate)  
Everett Turnpike

For Details Write:  
**AUCTIONFEST '81**  
Box 94  
Nashua, NH 03060

**DISTINCTIVE QSL's** — Largest selection, lowest prices, top quality photo and completely customized cards. Make your QSL's truly unique at the same cost as a standard card, and get a better return rate! Free samples, catalogue. Stamps appreciated. Stu Goodman, K2RPZ Print, P.O. Box 412, Rocky Point, NY 11778 (516) 744-6260.

**FREE SAMPLE** Ham Radio Insider Newsletter! Send large S.A.S.E., W5Y1, Box #10101-H, Dallas, Texas 75207.

**MAGAZINE SAMPLES!** For a free list of over 135 magazines offering a sample copy, send a stamped, addressed envelope to: Publisher's Exchange, P.O. Box 1368, Dept. 26A, Plainfield, NJ 07061.

## Coming Events ACTIVITIES

**"Just What the Doctor Ordered!"**

**CALIFORNIA:** The 6th West Coast Computer Faire on April 3-5 in San Francisco. Program includes 50 to 120 speakers, over 400 exhibits, and between 20,000 and 24,000 are expected. More info: Jim Warren (415) 851-7075.

**MARYLAND:** Greater Baltimore Hamfest and Computerfest on March 29 at the Maryland State Fairgrounds, Timonium, Maryland. Gates open at 8:00. Admission is \$3.00. Speakers, demonstrations, indoor flea market, outdoor tailgating, large indoor show area for dealers/commercial displays plus prizes, free parking and much more. Exit 16-A of I-83, two miles north of I-695 near Baltimore. Talk-in on 146.07/67 and 146.34/94. More information and table reservations: G.B.H. & C., 2136 Pine Valley Dr., Timonium, Maryland 21093 or (301) 321-1404.

**MISSOURI:** Missouri State ARRL Convention/Northwest Missouri Hamfest on April 11-12. Old airport, Kansas City, Missouri. Over 500,000 feet of commercial, flea market, forums, free parking. Information: P.H.D., P.O. Box 11, Liberty, Missouri 64068.

**NEBRASKA:** The Hamfest 5 on March 21 at the Marina Inn in So. Sioux City. Doors open at 9:00. Exhibits, Flea Market, contests, programs, dinner banquet and more. More info: Dick Pitner, W0FZO or Glen Holder, K0TFT. Advanced registration: Jerry Smith, W0DUN, Box 14, Akron, Iowa 51001.

**NEW HAMPSHIRE:** Auctionfest '81 on March 21 sponsored by the Interstate Repeater Society, P.O. Box 94, Nashua, NH 03106. Location: Hilton in Merrimack. Doors open at 9:00 AM. Vendor exhibits and more. \$5.00 and \$75.00 for Flea Market rooms. Auction begins at 11:00 AM. For accommodations, reservations, more information: write WB1FRE.

**NEW JERSEY:** Chestnut Ridge Radio Club's Ham Radio and Computer Flea Market on April 4 from 9:00 to 3:00 at the Educational Building, Saddle River Reform Church, East Saddle River at Weiss Road in Upper Saddle River, New Jersey. No admission fee. Tables are \$10.00 and tailgating is \$5.00. Contact Jack Meagher, W2EHD, (201) 768-8360 or Neil Abitabile, WA2EZN (201) 767-3575.

**NEW JERSEY:** Annual Flemington, N.J. Hamfest Saturday, March 21 from 8:30 to 3:00 at the Hunterdon Central High School Field House. 20,000 square feet of heated indoor area. Gigantic flea market, 200 tables, major manufacturers, informative seminars. Bring the XYL, kids and friends. Flemington is a tourist area. Talk in 146.52, 147.375, 147.015, 224.12. Admission \$3.00 donation. For reservations or info call 201-788-4080 or write Cherryville Repeater Assn. c/o W2FCW, Box 76, Farview Ave., Annandale, N.J. 08801.

**NEW JERSEY:** The Old Bridge Radio Association's first annual auction of ham radio, electronic, and computer gear on March 1 at the Cheesequake Firehouse, Routes 35 and 9, in Old Bridge. Exhibition begins at 11 AM, sale at noon. Refreshments available. More info, call Fred at (210) 257-8753.

**NORTH CAROLINA:** The 1981 Charlotte Hamfest on March 21 and 22 at the Charlotte Civic Center. The Hamfest and the North Carolina State ARRL Convention will bring more than 8,000 hams and their wives for this electronic feast. For more info: Rick Richardson, KA4EHU, 4609 Montclair Ave., Charlotte, NC 28211.

**OHIO:** The third annual Lake County Amateur Radio Association Lake County Hamfest on March 29 at Madison High School, Madison. Admission: \$2.50 in advance and \$3.00 at the door. Free parking, all displays are indoors, plus much more. Talk-in on 147.81/21. Information and reservations: SASE Lake County Hamfest Committee, 5555 Anaconda Rd., Mentor, Ohio 44060. (216) 953-9784.

## TEST EQUIPMENT RECONDITIONED AND LAB CALIBRATED

HP608C SIGNAL GENERATOR 10 THRU 480 MHZ AM/CW OR PULSE MODULATION, CALIBRATED ATTENUATOR, EXCELLENT LAB GENERATOR \$375.00  
HP612 UHF SIGNAL GENERATOR 450 THRU 1230 MHZ AM/PULSE MODULATION, CALIBRATED OUTPUT ..... 475.00  
TS-497B/URR MILITARY SIGNAL GENERATOR 2 THRU 400 MHZ, CALIBRATED ATTENUATOR 225.00  
AN/URM-25 MILITARY SIGNAL GENERATOR 10 KHZ THRU 50 MHZ, AM/CW, MODULATION 400 & 1 KHZ, CALIBRATED OUTPUT, PRECISION 50 OHM STOP ATTENUATOR, PERFECT FOR AMATEUR OR LAB WORK ..... 285.00  
SG-13/U VOR/ILS MILITARY SIGNAL GENERATOR 108-135.9 MHZ AND 329.3 TO 335 MHZ, OUTPUT SIGNALS INCLUDE VOR, LOC, GLIDESLOPE AND 1000 CPS. SAME AS COLLINS 479T-2 OPERATES FROM 28 VDC PORTABLE OR BENCH POWER SOURCE, IDEAL FOR AIRCRAFT RADIO REPAIR ..... 265.00  
SG-3/U FM MILITARY HIGH BAND SIGNAL GENERATOR, 50 MHZ THRU 400 MHZ, METERED RF OUTPUT 0-1 V AND FM METERED DEVIATION 0-150 KHZ, CALIBRATED OUTPUT, PERFECT FOR AMATEUR, COMMERCIAL AND LAB WORK ..... 345.00  
SG-12/U FM MILITARY LOW BAND SIGNAL GENERATOR 20 MHZ THRU 100 MHZ, METERED RF OUTPUT 0-5 V, METERED DEVIATION 0-100 KHZ PERFECT FOR LOW BAND RADIO FM SERVICING 185.00  
TEKTRONIX 1L20 SPECTRUM ANALYZER PLUG-IN 10 MHZ THRU 4.2 GHZ A "MUST HAVE" ITEM FOR ANY RADIO LAB USING 500 SERIES TEKTRONIX OSCILLOSCOPES ..... 750.00  
TEKTRONIX 3A72 DUAL TRACE DC-650 KHZ PLUG-IN FOR 560 SERIES OSCILLOSCOPES ..... 125.00  
TEKTRONIX 1M1 TEST PLUG-IN ..... 85.00  
TEKTRONIX 1A1 DUAL TRACE DC-50 MHZ PLUG-IN ..... 95.00  
TEKTRONIX 1A5 DIFFERENTIAL PLUG-IN DC-50 MHZ ..... 85.00  
TEKTRONIX PLUG-INS TYPE A, B, H, K, L, R, EACH ..... 65.00  
FAIRCHILD TYPE 74-13A DELAYING SWEEP PLUG-IN, FOR 777 OSCILLOSCOPES ..... 125.00  
GR 1556 IMPACT-NOISE ANALYZER, MEASURES ACCOUSTICAL AND ELECTRICAL NOISE PEAKS 5 HZ TO 20 KHZ ..... 125.00  
KINTEL 202B DC MICROVOLTMETER ..... 45.00  
TS-230E RADAR TEST SET, MEASURES POWER & FREQUENCY, RANGE 8500 TO 9700 MHZ ..... 45.00  
TS-148/UPM-33 RADAR SPECTRUM ANALYZER, RANGE 8470-9630 MHZ SWEEP 10-30 HZ ..... 49.00  
TV-7/U MILITARY TUBE TESTER ..... 45.00  
TS-403/URM-61 SIGNAL GENERATOR RANGE 1800 THRU 4000 MHZ, FM, CW, PULSE, SQUARE WAVE MILITARY VERSION OF HP 616A, PERFECT FOR SATELLITE WORK ..... 300.00  
FOB OTTO, N.C., 30 DAY MONEY BACK GUARANTEE, SEND CHECK, VISA OR MASTER CHARGE, PHONE BILL SLEP 704-524-7519.

**SLEP ELECTRONICS**  **CO.**

P.O. BOX 100, HWY. 441, DEPT. HR  
OTTO, NORTH CAROLINA 28763

## SYNTHESIZED SIGNAL GENERATOR

**MADE IN  
USA**  **MODEL  
SG 100C  
\$329.95  
plus shipping**

- Covers 100 to 179,999 MHz in 1 kHz steps with thumb-wheel dial • Accuracy .00001% at all frequencies • Internal frequency modulation from 0 to over 100 kHz at a 1 kHz rate • Spurs and noise at least 60dB below carrier • RF output adjustable from 5-500mV across 50 ohms • Operates on 12vdc @ 1/2 amp • Price \$329.95 plus shipping.

In stock for immediate shipping. Overnight delivery available at extra cost. Phone: (212) 468-2720.

**VANGUARD LABS**  
196-23 Jamaica Ave. Hollis, NY 11423

# BENCHER 1:1 BALUN

- Lets your antenna radiate—not your coax
- Helps fight TVI—no ferrite core to saturate or reradiate
- Rated 5 KW peak—accepts substantial mismatch at legal limit
- DC grounded—helps protect against lightning
- Amphenol® connector; Rubber ring to stop water leakage

**New** Rugged custom Cyclac® case, UV resistant formulation

**New** Heavy threaded brass contact posts



Available at selected dealers, add \$2.00 postage and handling in U.S.A.

WRITE FOR LITERATURE

<b>Model ZA-1A</b>	3.5-30 mHz	<b>\$15.95</b>
<b>Model ZA-2A</b>	optimized 14-30 mHz includes hardware for 2' boom	<b>\$17.95</b>

BENCHER, INC.

333 W. LAKE ST., CHICAGO, IL 60606 • (312) 263-1808

**PENNSYLVANIA:** Penn Wireless Association, Inc. will hold its Tradefest '81 on March 29 at the National Guard Armory, Southhampton Rd. and Roosevelt Blvd., (Rte. #1) 1/2 mile south of the Pennsylvania Turnpike exit #28. General admission is \$3.00. Prizes, refreshments, displays and surprises. Talk-in on 146.115/715 and .52. Contact Thomas Gallagher, WB3DJF, P.O. Box 734, Langhorne, Pennsylvania 19047.

**TEXAS:** Midland Amateur Radio Club's annual swapfest on March 14 from 1:00 to 7:00 and March 15 starting at 8:00. Doorprizes and more. Pre-registration is \$4.50 or \$5.00 at the door. Talk-in on 146.16/146.76.

**WISCONSIN:** The Madison Area Repeater Association's ninth annual Madison Swapfest on April 5 at the Dane County Exposition Center Forum Building in Madison. Exhibits, flea market, door prizes and more. \$2.50 in advance and \$3.00 at the door. Talk-in on 146.16/76. Reservations and information: M.A.R.A., P.O. Box 3403, Madison, Wisconsin 53704.

**SWEDEN:** The International Radio Amateur Meeting in Goteborg on April 4 and 5. All interested hams are invited. Includes shows, exhibitions, lectures, special displays plus more. The Swedish Maritime Mobile Radio Club and the Scandinavian Amateur Radio Teletype Group are having their annual meetings. Exhibitors and hams outside of Sweden are also welcome.

## OPERATING EVENTS

**MARCH 21st - 22nd:** Tennessee QSO Party from 2100Z (the 21st) to 0500Z (the 22nd) and from 1400Z to 2200Z on the 22nd. Tennessee stations give signal report and county. Out of state, give signal report and state, province or country. Same station on different bands allowed. CW frequencies: Approximately 50 from bottom of each band. Phone: 3980, 7280, 14280, 21380, 28680. Novices within their own bands. Deadline for logs: May 1, 1981. Send business sized SASE with log. More info: SASE Dave Goggio, W4OGG, 1419 Favell Dr., Memphis, Tennessee 38116.

**MARCH 21st - 23rd:** B.A.R.T.G. Spring RTTY Contest 1981. From 0200 GMT Saturday until 0200 GMT Monday. Total contest is 48 hours, but no more than 30 hours of operation is permitted. 18 hours of non-operating time may be taken at any time, but no less than 3 hours at a time. Must be summarized. Bands: 3.5, 7.0, 14.0, 21.0 and 28.0 MHz. Amateur bands. More info or logs (deadline: May 31st) SASE to Ted Double, G8CDW, 89, Linden Gardens, Enfield, Middlesex ENGLAND, EN1 4DX.

**MARCH 28th AND 29th:** YL ISSB QSO Party 1981. CW from 0001 GMT on the 28th to 2359 GMT on the 29th. Two 6 hour rest periods required. Phone from 0001 GMT on April 18th to 2359 GMT on the 19th. Two 6 hour rest periods required. YL/OM and DX/WK teams allowed. CW frequencies: 3665, 7070, 14070, 21070; Phone: 3925, 7290, 14332, 21373, 28673. Listen for DX on 3765 and 7090. More info: SASE to Lyle F. Shaw, KC4LF, 6329 Fairway Blvd., Apollo Beach, Florida 33570.

**MARCH 28th AND 29th:** Spring VHF QSO Party sponsored by the Ramapo Mountain ARC from 1800Z Saturday until 0400Z on Sunday. Exchange signal report and ARRL section. FM operation not permitted below 450 MHz. Use ARRL VHF QSO Party or similar forms or SASE to R.M.A.R.C. for entry forms and/or more information. Deadline: April 27th. Ramapo Mountain ARC, P.O. Box 364, Oakland, NJ 07436.

**CENTURY 21 ARC** — Low power — QRP'ers — CW nets — Contests — Awards — SASE KA4EBW.

**ATTENTION FIREFIGHTERS!** A firefighter net is being formed and will be operating on 10 meters. Times are 1500Z, 2100Z and 0100Z. The frequency is 28.7 MHz. More information: SASE and four first class stamps to Claude L. Fant, Jr., KA8HB, 328 Harrison Ave., Hamilton, Ohio 45023. You will be sent a list of firefighters in the net and other information.

**AWARD INFORMATION:** The "10-K" and "20-K" award, formerly issued by the CHC, is available from WA6CPP, 13779 North Wells Lane, Lodi, California 95240. Work 10 (or 20) stations in the outlying territories and possessions with the miscellaneous K calls (KG4, KC6, KP6, etc.). Send log data and #10 SASE to WA6CPP. Send 3 units postage for return in mailing tube. DX stations send 2 IRC, CPP will supply the envelope. Limited supply.

**OCTOBER 23, 1980 - OCTOBER 23, 1981:** The New Bern Amateur Radio Club is sponsoring "The Swiss Bear Award." This award is given for working three different amateur stations in the New Bern area within the above time period. Extracts from logs for QSO's, along with a SASE or two IRC's (for DX stations) should be sent to: New Bern Amateur Radio Club, Inc., P.O. Box 2483, New Bern, NC 28560. Certificate depicting "The Swiss Bear" will be awarded stating that the station has met the requirements for this award.

## ALL BAND TRAP ANTENNAS!



PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS - LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. INPUT FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1" X 6" - you just switch to band desired for excellent worldwide operation - transmitting and receiving! Low SWR over all bands - Tuners usually NOT NEEDED! Can be used as inverted V's - slopers - in attics, on building tops or narrow lots. THE ONLY ANTENNA YOU WILL EVER NEED FOR ALL DESIRED BANDS - WITH ANY TRANSCEIVER - NEW - EXCLUSIVE! NO BALUNS NEEDED!

80-40-20-15-10-6 meter - 2 trap --- 104 ft. with 90 ft. RG58U - connector - Model 998BUA ... \$69.95  
40-20-15-10 meter --- 2 trap --- 54 ft. with 90 ft. RG58U - connector - Model 1001BUA ... \$68.95  
20-15-10 meter --- 2 trap --- 26ft. with 90 ft. RG58U - connector - Model 1007BUA ... \$67.95

SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical-costs etc) or order using VISA - MASTER CHARGE - CARD - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES WILL INCREASE. SAVE - ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM WESTERN ELECTRONICS Dept. AR-3 Kearney, Nebraska, 68847

## Iron Powder and Ferrite TOROIDAL CORES

Shielding Beads, Shielded Coil Forms  
Ferrite Rods, Pot Cores, Baluns, Etc.

Small Orders Welcome  
Free 'Tech-Data' Flyer

**AMIDON** Associates Since 1963


12033 Otsego Street, North Hollywood, Calif. 91607  
(213) 762-2418

In Germany: Elektronikladen, Wilhelm - Melies Str 88, 4930 Detmold 18, West Germany  
In Japan: Toyomura Electronics Company, Ltd., 7-9, 2-Chome Sota-Kanda, Chiyoda-Ku, Tokyo, Japan



# ASTRO 103 ÷ MADISON > 9 BAND DXCC

## RAVE REVIEWS

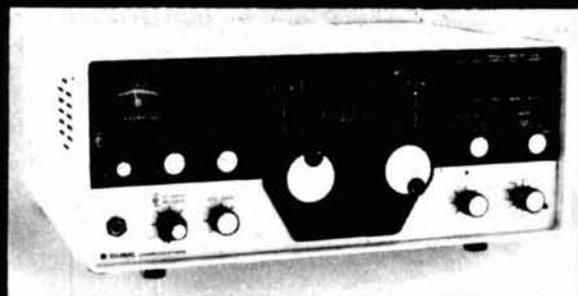

### NEW ASTRO 103 WITH NEW WARC BANDS

#### SPECIFICATIONS

##### Notch Filter:

Provides 30dB typical notch attenuation from .4 to 3.0 kHz

##### Selectivity: (normal)

16 pole crystal filtering 2.7 kHz at -6dB; 3.78 kHz at -100dB. Shape factor 1.4:1

##### RF Output Power:

100 watts all bands all modes—limited by ALC to 100 watts PEP or CW

##### Sensitivity:

.35Mv for 10dB

##### Third Order Intercept

Better than .15dBm

##### Image Rejection:

Better than 70dB

##### Modes:

USB LSB CW

CWV RTTY

Being only two blocks from WIAW is a horrifying experience for an amateur, since simultaneous 1-KW operation takes place almost around the clock on 80 through 10 meters, to say nothing of operation on 160, 6 and 2 meters! Very few receivers can withstand the rf onslaught, and tend to crumble when WIAW is operating. Some have survived when front-end attenuation switched in, but none could handle the WIAW. The 102 BXA not only survives without an attenuator, but can function normally when my beam is headed toward WIAW! Your rig is probably the cause of my finally changing to U.S. made equipment.

Doug DeMaw, W1FB  
Technical Department Manager  
ARRL

This transceiver is the only one I have tested recently that has met all its published specifications or even went beyond. I am specifically impressed with the behavior of the PLL and the AGC. To the best of my knowledge, in this respect, you are better than all current production instruments including the Collins KWM380, which I had tested.

ULRICH L. ROHDE

- NOW HEAR THIS -  
THE ASTRO 102 AND 103 ARE  
NOW HERE AT

# MADISON Electronics Supply

1508 McKinney • Houston, Texas 77002 • (713) 658-0268

## MINIATURE AUTOMATIC C.W. STATION IDENTIFIER



### MODEL 97813, ONLY \$74.95 •

- COMPLIES WITH NEW FCC RULES, PARTS 89, 91, 93, 95
- MULTI-MODE OPERATION:** MANUAL, SEMI-AUTO AND AUTO.
- MANUAL MODE** — A pushbutton switch triggers the identifier which keys the transmitter for the duration of the ID cycle.
- SEMI-AUTO MODE** — The PTT line activates the ID'er if the repeat interval time has elapsed and keeps the transmitter keyed throughout the duration of the ID cycle.
- AUTO MODE** — The identifier will key the transmitter and ID every time the repeat interval time has elapsed.
- CONNECTS DIRECTLY TO MICROPHONE AND PTT INPUTS OF MOST TRANSMITTERS. MINIATURE SIZE MAKES IT FEASIBLE TO MOUNT INSIDE THE TRANSMITTER.**
- PROGRAMMABLE CODE SPEED, TONE, AND REPEAT TIME.**
- ADJUSTABLE CODE AUDIO LEVEL.**
- PREPROGRAMMED MEMORY ELEMENTS** — 254 OR (510 BIT) (OPTIONAL)
- SIZE** — 1 X 4 INCHES
- INCLUDES SWITCHES, WIRING AND INSTRUCTION MANUAL.**
- ONE YEAR WARRANTY • MADE IN U.S.A.**
- Include \$3 shpg/hdlg., \$5 foreign.  
CA. res. add sales tax. allow four weeks delivery.

## Securitron

P.O. Box 32145 • San Jose, Ca. 95132  
Phone (408) 294-8383

# STEP UP TO TELREX

## Professionally Engineered Antenna Systems

### Single transmission line "TRI-BAND" ARRAY

#### MONARCH TB5EM/4KWP

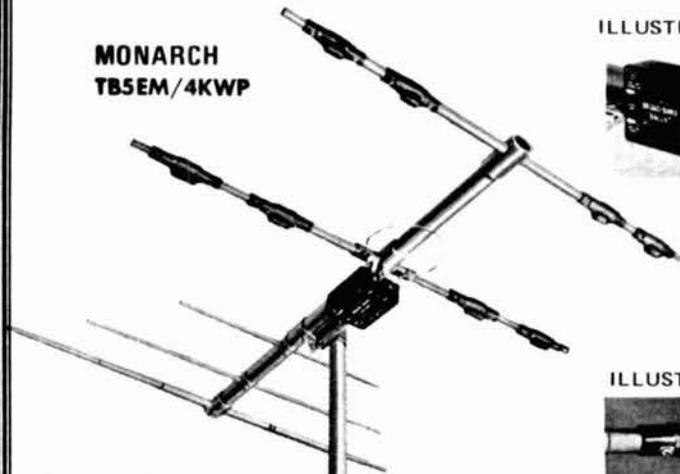


ILLUSTRATION BALUN



ILLUSTRATION TRAP



By the only test that means anything . . . on the air comparison . . . this array continues to outperform all competition . . . and has for two decades. Here's why . . . Telrex uses a unique trap design employing 20 HiQ 7500V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-band performance.

For technical data and prices on complete Telrex line, write for Catalog PL 7

COMMUNICATION  
SYSTEMS  
SINCE 1921 **telrex** Laboratories  
ASBURY PARK, NEW JERSEY 07712 U.S.A.

# Hatry Electronics

500 Ledyard St. (South) Hartford, Ct. 06114

203-527-1881

## TEN-TEC DELTA 580



160-10 Meter including three new hf bands (10, 18 & 24.5 MHz). Low noise double conversion design. 200 watts input on all bands. 100% duty cycle. Offset tuning. Full break-in. Built-in VOX and PTT.

**\$869.00**

Call for quote

## TEN-TEC ARGONAUT (515)



80-10 Meters. Full break-in. 5 watts input. Built-in T.V.I. filter. Restyled cabinet, easy to read controls. The premier ORP rig.

**\$469.00**

Call for quote

## The JR. MONITOR



The JR. MONITOR™ has it all wrapped up in one neat package. All metal cabinet 5 1/4" w x 2 3/4" h x 6" d. Think of the unlimited possibilities you'll have for experimenting with dozens of antennas! Covers 1.8-30 MHz.

**\$79.50**

Call for quote

## The MT-3000A



DenTron's MT-3000A™ does more than tune coax, random wire, and balanced feed antennas. There is a built-in antenna selector switch for selecting five different antennas, plus lets you tune your station off air through a 250 watt dummy load. Dual in-line forward and reflected watt meters provide continuous monitoring of both power output and antenna tuning. Switchable between 200 and 2000 watts. Continuous tuning from 160 through 10 meters with power handling capability in excess of 3 kW PEP.

**\$399.50**

Call for quote

## The BIG DUMMY



A full 1 kW dummy load, the Big Dummy™ offers a flat SWR, full frequency coverage from 1.8-300 MHz, and high grade industrial cooling oil furnished with the unit. The DenTron Big Dummy is built to last... it comes fully assembled and warranted.

**\$39.50**

Call for quote

## AT 1K



A full 1000 watt CW and 1200 watt SSB power handling capability (DC input to amplifier). Matches virtually any feed line. SWR/Relative forward power meter is included for tune-ups without a watt meter. Continuous tuning from 1.8 to 30 MHz.

**\$149.50**

Call for quote



**July 25 thru August 7, 1981**

*Our 22nd year*

Have trouble finding time to study for Upgrading? Do it on your vacation at the **OAK HILL ACADEMY RADIO SESSION** in the

**Blue Ridge Mountains of Virginia**

Two weeks of intensive Code and Theory Study starting at your level.

- Novice to General
- General or Technician to Advanced
- Advanced to Amateur Extra

Expert Instructors — Friendly Surroundings — Excellent Accommodations. Ham Lab set up for all to use.

**"A Vacation with a Purpose"**

C. L. PETERS, K4DNJ, Director  
Oak Hill Academy Amateur Radio Session  
Mouth of Wilson, Virginia 24363

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_



SHIPPING F.O.B. HARTFORD



# DEALERS WANTED TOWERS

by ALUMA  
HIGHEST QUALITY  
ALUMINUM  
& STEEL

60 Ft. Aluminum.  
Crank-Up  
Model T-60-H

40' Steel  
Crank-Up  
Model SHD-40

- ★ TELESCOPING (CRANK UP)
  - ★ GUYED (STACK-UP)
  - ★ TILT-OVER MODELS
- Easy to install. Low Prices.  
Crank-ups to 100 ft.

**EXCELLENT FOR  
HAM COMMUNICATIONS**

**SPECIAL  
Four Section 50 Ft.  
Van Mounted Crank-Up  
Aluma Tower**


Over 36 types aluminum  
and steel towers made—  
specials designed and  
made—write for details



**ALUMA TOWER CO.**  
Box 2806HR  
VERO BEACH, FLA. 32960  
PHONE (305) 567-3423  
TELEX 80-3405
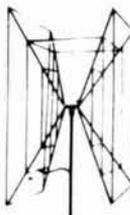
## GEM-QUAD FIBRE-GLASS ANTENNA FOR 10, 15, and 20 METERS

Two Elements \$182.00  
Extra Elements \$130.00  
Price is F.O.B. Transcona  
**INCLUDES U.S. Customs  
Duty**



**KIT COMPLETE WITH**  
\*SPIDER  
\*ARMS  
\*WIRE  
\*BALUN KIT  
\*BOOM WHERE  
NEEDED

WINNER OF MANITOBA  
DESIGN INSTITUTE  
AWARD OF EXCELLENCE

Buy two elements now — a third and fourth may be added later with little effort.

Enjoy up to 8 db forward gain on DX, with a 25 db back to front ratio and excellent side discrimination.

Get maximum structural strength with low weight, using our "Tridetic" arms. Please inquire directly to:

**GEM QUAD PRODUCTS LTD.**

Box 53

Transcona Manitoba  
Canada R2C 2Z5  
Tel. (204) 866-3338

## 2300 MHz DOWN CONVERTER

UNIVERSAL COMMUNICATIONS

DEBORAH and STEVE (WB5KGL)

KNOWN AS THE STOP SIGN BOARD. THIS 2300 MHz DOWN CONVERTER KIT WORKS. THE IMPROVED BOARD EVEN MAKES IT BETTER THAN BEFORE. SO WHY PAY TWICE AS MUCH?

Kit supplied with an 8-page brochure, PC board, Diodes, Chip Caps, Transistors, and all parts to complete a working board...

**\$38.50**

POWER  
SUPPLIES AVAIL.

Money Order or Check. Mail or phone  
**UNIVERSAL COMMUNICATIONS**  
P.O. BOX 6302, ARLINGTON, TEX. 76011  
**817-265-0391**

**39<sup>95</sup>**  
ADD \$2.50 FOR POSTAGE

**30 CHANNEL  
CABLE TV  
CONVERTER**

ORDER No. 185AE047

**ENCO** ROUTE 9N,  
PLATTSBURGH, N.Y. 12901  
Tel. (518) 561-8700

**FREE!**  
UNUSUAL 96 PAGE  
ELECTRONIC PARTS  
& IDEAS CATALOG!

**NEW CATALOG OF  
HARD-TO-FIND  
PRECISION TOOLS**

**FREE**

Lists more than 2000 items: pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Send for your free copy today!

**JENSEN TOOLS INC.**  
1230 S. PRIEST DR. - TEMPE, AZ 85281

# HIGH STABILITY CRYSTALS FOR FREQUENCY OR TIME

## USE THE BEST BUY JAN CRYSTALS

- CB
  - CB standard
  - 2 meter
  - Scanners
  - Amateur Bands
  - General Communication
  - Industry
  - Marine VHF
  - Micro processor crystals
- Send 10¢ for our latest catalog.  
Write or phone for more details.

Jan Crystals  
P.O. Box 06017  
Ft. Myers, Florida 33906  
all phones (813) 936-2397

easy to charge



## HOT DX INFO!!!

### World's Best Known WEEKLY DX BULLETIN

- Calls • Frequencies
- Propagation •

QSL Info for those Rare  
and Exotic countries

SEND Business size SASE  
for sample copy TO:

## THE DX BULLETIN

306 Vernon Ave.,  
Vernon, CT 06066

## GaAs FETs!

We are the U.S. distributor for  
**MITSUBISHI**

MGF FETs,

the affordable GaAs Fets with the best  
price/performance ratio available;  
VHF through 12GHz.

1400 - \$28.30    1400A - \$39.15  
1402 - \$50.00    1412 - \$75.00    1403 - \$135.00

Shipped from stock.  
Quantity discounts available.

ALSO: 10GHz GUNN Diodes,  
low-loss PC laminates,  
assembled preamps

From the source:

APPLIED INVENTION  
RD2 Rte. 21  
HILLSDALE, N.Y. 12529  
(518) 325-3911

ege, inc. TOLL 1-800-336-4799  
FREE ORDERS ONLY

## MARCH SALE

BONUS 2% discount for prepaid orders  
(cashier's check or money order).

NEW ITEMS ..... CALL

### MIRAGE AMPLIFIERS BUTTERNUT VERTICAL

#### HY-GAIN ANTENNAS - Limited Quantities

TH6DXX Triband Beam .....	\$244.95
TH3MK3 3-Element Beam .....	179.95
TH5DX 5-Element Beam .....	204.95
TH3JR 3-Element Triband .....	138.95
18AVT/WB 10-80 Vertical .....	82.95
14AVQ/WB 10-40 Vertical .....	50.77

#### CUSHCRAFT ANTENNAS

A4 New Triband Beam 10-15-20m .....	207.95
A3 New Triband Beam 10-15-20m .....	168.10
AV3 New 10-15-20m Vertical .....	39.40
AV5 New 10-80m Vertical .....	85.95
ARX-2B New Ringo Ranger .....	33.95
A32-19 2m "Boomer" DX Beam .....	71.65
220B 220 MHz "Boomer" .....	67.95
214B Jr. Boomer 144-146 MHz .....	57.30
214FB Jr. Boomer 144.5-148 MHz .....	57.30
A147-11 11-Element 2m .....	32.25
MINIQUAD HQ-1 .....	134.95
ALLIANCE HD73 Rotor .....	96.10
CDE HAM IV ROTOR/CD4511 .....	165.95/94.95

#### MFJ PRODUCTS COMPLETE LINE IN STOCK

989 New 3KW Tuner .....	244.95
984 Deluxe 3 KW Tuner switch/mtr .....	252.95
981 3 KW Tuner with SWR/watt meter .....	169.85
962 1.5 KW Tuner mtr/switch .....	161.55
949B 300 watt deluxe tuner .....	122.00
941C 300 watt tuner switch/mtr .....	78.42
940 300 watt tuner switch/mtr .....	69.70
484 Grandmaster memory keyer 12 msg .....	121.72
482 4 msg Memory keyer .....	87.96
422 Pacesetter Keyer w/Bencher BY1 .....	87.15
422X Pacesetter Keyer only .....	60.98
410 Professor Morse keyer .....	113.95
408 Deluxe Keyer with speed mtr .....	69.69
406 Deluxe keyer .....	58.95
752B Dual tunable filter .....	78.42
624 Deluxe phone patch .....	60.97
102 24 hour clock .....	30.95
525 RF Speech Processor .....	101.95
260/262 Dry Dummy Loads .....	23.50/43.55
250 2KW PEP Dummy Load .....	28.25
820 SWR/Watt Meter + one sensor .....	58.95
825 Dual SWR/watt meter + one sensor .....	101.95
CABLE R8B/U Foam 95% Shield .....	24c/ft.
8 wire Rotor 2 # 18, 6 # 22 .....	16c/ft.

#### BENCHER PADDLES Black/Chrome .....

35.90/43.75

#### ASTRON POWER SUPPLIES (13.8 VDC)

R54A 3 amps continuous, 4 amp ICS .....	35.20
R57A 5 amps continuous, 7 amp ICS .....	48.60
R512A 9 amps continuous, 12 amp ICS .....	66.35
RS20A 16 amps continuous, 20 amp ICS .....	87.20
RS20M same as RS20A + meters .....	105.50
RS35A 25 amps continuous, 35 amp ICS .....	133.95
RS35M same as RS30A + meters .....	150.20

#### TELEX HEADSETS-HEADPHONES

C610 Headphone .....	8.47
C1210 Headphone .....	22.95
C1320 Headphone .....	32.95
PROCOM 200 Headset/dual Imp. MIC .....	77.50
PROCOM 300 Lt/wt Headset/dual Imp. MIC .....	69.95
B & W 370-15 Allband dipole .....	123.45

#### KENWOOD TRANSCEIVERS CALL

VHF - TR2400, TR7800, TR9000  
HF - TS520SE, TS130S, TS830S

#### KLM ANTENNAS/AMPLIFIERS

PA 2 25B 2m 2 in; 25 out Amp .....	79.95
MA35BL 143-149 MHz 3.5 watt Amp. PreAmp .....	110.95
PA 15-40 BL 2m 15 in; 40 out Amp .....	110.46
PA 10-170 BL 2m 5-15 in; 170 out Amp .....	249.95
PA 10-90 BL 2m 5-15 in; 90 out Amp .....	159.95
PA 15-40CL 420-450 MHz 40 watt Amp .....	159.95
K134A 4 Element Triband Beam .....	320.75
KT 34XA 6 Element Triband Beam .....	469.50
144-148-13LB 2m 13 element with balun .....	77.95
144-148-16C 2m 16 element with oscar .....	93.55
219-226-14 219-226 MHz 14 element beam .....	57.15
420-450-18C 420-450 MHz 18 element oscar .....	58.70
HUSTLER 5BT 10-80m Vertical .....	97.62
4BTV 10-40m Vertical .....	76.70
HF Mobile Resonators .....	Standard Super
10 and 15 meter .....	8.50 14.25
20 meters .....	11.25 17.00
40 meters .....	13.50 18.95
75 meters .....	14.95 30.25
Avanti AH151.3G 2m on glass ant .....	28.95

Send stamp for a flyer. Terms: Prices do not include shipping. VISA and Master Charge accepted 2% discount for prepaid orders (cashier's check or money order). COD fee \$2.00 per order. Prices subject to change without notice.



2410 Drexel Street  
Woodbridge, Va. 22192



Information: (703) 643-1063 ORDERS: 1-800-336-4799

## HI-Q BALUN

- For dipoles, yagis, inverted vees & doublets
- Replaces center insulator
- Puts power in antenna
- Broadbanded 3-40 MHz
- Small, lightweight and weatherproof
- 1:1 Impedance ratio
- For full legal power and more
- Helps eliminate TVI
- With SO 239 connector



\$10.95

## HI-Q ANTENNA CENTER INSULATOR



Small rugged lightweight weatherproof  
Replaces center insulator  
Handles full legal power and more

\$5.95 With SO 239 connector

## HI-Q ANTENNA END INSULATORS



Rugged lightweight injection molded of top quality material with high dielectric qualities and excellent weather ability. End insulators are constructed in a special interlocking fashion to permit twisting of loading coils or parallel wiring for tuner traps.

- May be used for Guy wire strain insulators
- End or center insulators for antennas
- Construction of antenna loading coils or multiband traps

\$4.95

## DIPOLES

MODEL	BANDS	LENGTH	PRICE WITH HI-Q BALUN	WITH HI-Q CENTER INSULATOR
<b>Dipoles</b>				
D-80	80-175	1.80	\$28.95	\$24.95
D-40	40-35	.60	29.95	21.95
D-20	20	.30	24.95	20.95
D-15	15	.22	23.95	19.95
D-10	10	.16	22.95	18.95
<b>Shortened dipoles</b>				
SJ3 80	80-175	.95	31.95	27.95
SJ3 40	40	.45	28.95	24.95
<b>Parallel dipoles</b>				
PD-8010	80-40/20/10	1.50	36.95	35.95
PD-4010	40-20/10	.75	33.95	29.95
PD-8040	80-40/15	1.80	35.95	31.95
PD-4020	40-20/15	.60	29.95	25.95

Dipole shorteners - only, same as included in SO models  
S-80 80-175 \$11.95 \$11.95  
S-40 40 \$11.95 \$11.95

All antennas are complete with HI-Q Balun or HI-Q Antenna Center Insulator. No 14 antenna wire or center insulators. 1100 type antenna support rings (SO models only) not listed for full legal power. Antennas may be used as inverted V and may also be used by MARS or SWL.

Antenna accessories - available with antenna orders  
Nylon tape repair kit \$10.95 \$10.95  
Cable ties (10 pack) 1/2" x 1/2" x 1/2" \$1.95 \$1.95  
SO 239 cable crimpers \$2.95 \$2.95

All prices are postage USA-48  
A portion of your funds should be used to support the

Van Gorden Engineering  
BOX 21202, S. EUCLID, OHIO 44121

Dealer Inquiries Invited

## NEW 1981 EDITION

## AMATEUR Radio

## EQUIPMENT DIRECTORY

The most complete directory of Amateur Radio Equipment ever published-over 1500 products - over 100 manufacturers/distributors. Includes prices, specifications and pictures of transceivers, transmitters, receivers, antennas, towers, tuners, power supplies, microphones, meters, keys, test gear, SSVT, RTTY, VFO's, and more! No ham library is complete without a current edition of this Directory. BONUS - Included with each edition is a free newsletter containing the latest prices and product information. Order your copy today! All payments must be in U.S. currency drawn on a U.S. Bank. Prices for the 1981 Edition are as follows (includes postage & handling): U.S. & Canada \$9.95 U.S. & Canada - First Class \$7.95 Foreign (Air) \$10.00 Also, a complete set of 78, 79, 80 & 81 Directories is available for \$15.00 (U.S. & Canada), \$21.00 (Foreign - Air).

KENGROE CORP. DEPT. H  
9 JAMES AVE., KENDALL PK., N.J. 08824

# MHz electronics

## 1900 MHz to 2500 MHz DOWN CONVERTER

This receiver is tunable over a range of 1900 to 2500 mc and is intended for amateur radio use. The local oscillator is voltage controlled (i.e.) making the i-f range approximately 54 to 88 mc (Channels 2 to 7).

PC BOARD WITH DATA .....	\$19.99
PC BOARD WITH CHIP CAPACITORS 13 .....	\$44.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY .....	\$69.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY PLUS 2N6603 .....	\$89.99
PC BOARD ASSEMBLED AND TESTED .....	\$99.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY, POWER SUPPLY AND ANTENNA .....	\$159.99
POWER SUPPLY ASSEMBLED AND TESTED .....	\$49.99
YAGI ANTENNA 4' LONG APPROX. 20 TO 23 dB GAIN .....	\$59.99
YAGI ANTENNA 4' WITH TYPE (N, BNC, SMA Connector) .....	\$64.99
2300 MHz DOWN CONVERTER Includes converter mounted in antenna, power supply, plus 90 DAY WARRANTY .....	\$259.99
OPTION #1 MRF902 in front end. (7 dB noise figure) .....	\$299.99
OPTION #2 2N6603 in front end. (5 dB noise figure) .....	\$359.99
2300 MHz DOWN CONVERTER ONLY	
10 dB Noise Figure 23 dB gain in box with N conn. Input F conn. Output .....	\$149.99
7 dB Noise Figure 23 dB gain in box with N conn. Input F conn. Output .....	\$169.99
5 dB Noise Figure 23 dB gain in box with SMA conn. Input F conn. Output .....	\$189.99
DATA IS INCLUDED WITH KITS OR MAY BE PURCHASED SEPARATELY .....	\$15.00

### Shipping and Handling Cost:

Receiver Kits add \$1.50, Power Supply add \$2.00, Antenna add \$5.00, Option 1/2 add \$3.00, For complete system add \$7.50.

## ★ INTRODUCING THE HOWARD/COLEMAN TVRO CIRCUIT BOARDS ★ (Satellite Receiver Boards)

<b>DUAL CONVERSION BOARD</b> .....	\$25.00
This board provides conversion from the 3.7-4.2 band first to 900 MHz where gain and bandpass filtering are provided and, second, to 70 MHz. The board contains both local oscillators, one fixed and the other variable, and the second mixer. Construction is greatly simplified by the use of Hybrid IC amplifiers for the gain stages. Bare boards cost \$25 and it is estimated that parts for construction will cost \$270. (Note: The two Avantek VTO's account for \$225 of this cost.)	
<b>47 pF CHIP CAPACITORS</b> .....	\$6.00
For use with dual conversion board. Consists of 6 — 47 pF.	
<b>70 MHz IF BOARD</b> .....	\$25.00
This circuit provides about 43 dB gain with 50 ohm input and output impedance. It is designed to drive the HOWARD/COLEMAN TVRO Demodulator. The on-board band pass filter can be tuned for bandwidths between 20 and 35 MHz with a passband ripple of less than 1/2 dB. Hybrid ICs are used for the gain stages. Bare boards cost \$25. It is estimated that parts for construction will cost less than \$40.	
<b>.01 pF CHIP CAPACITORS</b> .....	\$7.00
For use with 70 MHz IF Board. Consists of 7 — .01 pF.	
<b>DEMODULATOR BOARD</b> .....	\$40.00
This circuit takes the 70 MHz center frequency satellite TV signals in the 10 to 200 millivolt range, detects them using a phase locked loop, de-emphasizes and filters the result and amplifies the result to produce standard NTSC video. Other outputs include the audio subcarrier, a DC voltage proportional to the strength of the 70 MHz signal, and AFC voltage centered at about 2 volts DC. The bare boards cost \$40 and total parts cost less than \$30.	
<b>SINGLE AUDIO</b> .....	\$15.00
This circuit recovers the audio signals from the 6.8 MHz frequency. The Miller 9051 coils are tuned to pass the 6.8 MHz subcarrier and the Miller 9052 coil tunes for recovery of the audio.	
<b>DUAL AUDIO</b> .....	\$25.00
Duplicate of the single audio but also covers the 6.2 range.	
<b>DC CONTROL</b> .....	\$15.00
This circuit controls the VTO's, AFC and the S Meter.	

### TERMS:

**WE REGRET WE NO LONGER ACCEPT BANK CARDS.**

PLEASE SEND POSTAL MONEY ORDER, CERTIFIED CHECK, CASHIER'S CHECK OR MONEY ORDER.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. WE CHARGE 15% FOR RESTOCKING ON ANY ORDER.

ALL CHECKS AND MONEY ORDERS IN US FUNDS ONLY.

ALL ORDERS SENT FIRST CLASS OR UPS.

ALL PARTS PRIME AND GUARANTEED.

WE WILL ACCEPT COD ORDERS FOR \$25.00 OR OVER, ADD \$2.50 FOR COD CHARGE.

PLEASE INCLUDE \$2.50 MINIMUM FOR SHIPPING OR CALL FOR CHARGES.

WE ALSO ARE LOOKING FOR NEW AND USED TUBES,

TEST EQUIPMENT, COMPONENTS, ETC.

WE ALSO SWAP OR TRADE.

(602) 242-8916

2111 W. Camelback  
Phoenix, Arizona 85015

**NEW — TOLL-FREE NO. 800-528-0180 — please, orders only!**

# MHz electronics

## RF TRANSISTORS

### FAIRCHILD VHF AND UHF PRESCALER CHIPS

95H90DC	350 MHz Prescaler Divide by 10/11	\$9.50
95H91DC	350 MHz Prescaler Divide by 5/6	9.50
11C90DC	650 MHz Prescaler Divide by 10/11	16.50
11C91DC	650 MHz Prescaler Divide by 5/6	16.50
11C83DC	1 GHz Divide by 248/256 Prescaler	29.90
11C70DC	600 MHz Flip/Flop with reset	12.30
11C58DC	ECL VCM	4.53
11C44DC/MC4044	Phase Frequency Detector	3.82
11C24DC/MC4024	Dual TTL VCM	3.82
11C06DC	UHF Prescaler 750 MHz D Type Flip/Flop	12.30
11C05DC	1 GHz Counter Divide by 4	50.00
11C01FC	High Speed Dual 5-4 input NO/NOR Gate	15.40

### TRW BROADBAND AMPLIFIER MODEL CA615B

Frequency response	40 MHz to 300 MHz	
Gain:	300 MHz 16 dB Min., 17.5 dB Max.	
	50 MHz 0 to -1 dB from 300 MHz	
Voltage:	24 volts dc at 220 ma max.	\$19.99

### CARBIDE — CIRCUIT BOARD DRILL BITS FOR PC BOARDS

Size: 35, 42, 47, 49, 51, 52	\$2.15
Size: 53, 54, 55, 56, 57, 58, 59, 61, 63, 64, 65	1.85
Size: 66	1.90
Size: 1.25 mm, 1.45 mm	2.00
Size: 3.20 mm	3.58

### CRYSTAL FILTERS: TYCO 001-19880 same as 2194F

10.7 MHz Narrow Band Crystal Filter	
3 dB bandwidth 15 kHz min. 20 dB bandwidth 60 kHz min. 40 dB bandwidth 150 kHz min.	
Ultimate 50 dB: Insertion loss 1.0 dB max. Ripple 1.0 dB max. Ct. 0 +/- 5 pf 3600 ohms.	\$5.95

### MURATA CERAMIC FILTERS

Models:	SFD-455D 455 kHz	\$3.00
	SFB-455D 455 kHz	2.00
	CFM-455E 455 kHz	7.95
	SFE-10.7 10.7 MHz	5.95

### TEST EQUIPMENT — HEWLETT PACKARD — TEKTRONIX — ETC.

<b>Hewlett Packard:</b>		
491C	TWT Amplifier 2 to 4 Gc 1 watt 30 dB gain	\$1150.00
608C	10 to 480 mc .1 uV to .5 V into 50 ohms Signal Generator	500.00
608D	10 to 420 mc .1 uV to .5 V into 50 ohms Signal Generator	500.00
612A	450 to 1230 mc .1 uV to .5 V into 50 ohms Signal Generator	750.00
614A	900 to 2100 mc Signal Generator	500.00
616A	1.8 to 4.2 Gc Signal Generator	400.00
616B	1.8 to 4.2 Gc Signal Generator	500.00
618A	3.8 to 7.2 Gc Signal Generator	400.00
618B	3.8 to 7.2 Gc Signal Generator	500.00
620A	7 to 11 Gc Signal Generator	400.00
623B	Microwave Test Set	900.00
626A	10 to 15 Gc Signal Generator	2500.00
695A	12.4 to 18 Gc Sweep Generator	900.00
<b>Alltech:</b>		
473	225 to 400 mc AM/FM Signal Generator	750.00
<b>Singer:</b>		
MF5/VR-4	Universal Spectrum Analyzer with 1 kHz to 27.5 mc Plug In	1200.00
<b>Keltek:</b>		
XR630-100	TWT Amplifier 8 to 12.4 Gc 100 watts 40 dB gain	9200.00
<b>Polarad:</b>		
2038/2438/1102A	Calibrated Display with an SSB Analysis Module and a 10 to 40 mc Single Tone Synthesizer	1500.00

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2N1561	\$15.00	2N5590	\$8.15	MM1550	\$10.00
2N1562	15.00	2N5591	11.85	MM1552	50.00
2N1692	15.00	2N5637	22.15	MM1553	56.50
2N1693	15.00	2N5641	6.00	MM1601	5.50
2N2632	45.00	2N5642	10.05	MM1602/2N5842	7.50
2N2857JAN	2.52	2N5643	15.82	MM1607	8.65
2N2876	12.35	2N6545	12.38	MM1661	15.00
2N2880	25.00	2N5764	27.00	MM1669	17.50
2N2927	7.00	2N5842	8.78	MM1943	3.00
2N2947	18.35	2N5849	21.29	MM2605	3.00
2N2948	15.50	2N5862	51.91	MM2608	5.00
2N2949	3.90	2N5913	3.25	MM8006	2.23
2N2950	5.00	2N5922	10.00	MMCM918	20.00
2N3287	4.30	2N5942	46.00	MMT72	1.17
2N3294	1.15	2N5944	8.92	MMT74	1.17
2N3301	1.04	2N5945	12.38	MMT2857	2.63
2N3302	1.05	2N5946	14.69	MRF245	33.30
2N3304	1.48	2N6080	7.74	MRF247	33.30
2N3307	12.60	2N6081	10.05	MRF304	43.45
2N3309	3.90	2N6082	11.30	MRF420	20.00
2N3375	9.32	2N6083	13.23	MRF450	11.85
2N3553	1.57	2N6084	14.66	MRF450A	11.85
2N3755	7.20	2N6094	7.15	MRF454	21.83
2N3818	6.00	2N6095	11.77	MRF458	20.68
2N3866	1.09	2N6096	20.77	MRF502	1.08
2N3866JAN	2.80	2N6097	29.54	MRF504	6.95
2N3866JANTX	4.49	2N6136	20.15	MRF509	4.90
2N3924	3.34	2N6166	38.60	MRF511	8.15
2N3927	12.10	2N6439	45.77	MRF901	5.00
2N3950	26.86	2N6459/PT9795	18.00	MRF5177	21.62
2N4072	1.80	2N6603	12.00	MRF8004	1.60
2N4135	2.00	2N6604	12.00	PT4186B	3.00
2N4261	14.60	A50-12	25.00	PT4571A	1.50
2N4427	1.20	BFR90	5.00	PT4612	5.00
2N4957	3.62	BLY568C	25.00	PT4628	5.00
2N4958	2.92	BLY568CF	25.00	PT4640	5.00
2N4959	2.23	CD3495	15.00	PT8659	10.72
2N4976	19.00	HEP76/S3014	4.95	PT9784	24.30
2N5090	12.31	HEPS3002	11.30	PT9790	41.70
2N5108	4.03	HEPS3003	29.88	SD1043	5.00
2N5109	1.66	HEPS3005	9.95	SD1116	3.00
2N5160	3.49	HEPS3006	19.90	SD1118	5.00
2N5179	1.05	HEPS3007	24.95	SD1119	3.00
2N5184	2.00	HEPS3010	11.34	TRWMRA2023-1.5	42.50
2N5216	47.50	HEPS5026	2.56	40281	10.90
2N5583	4.55	HP35831E/		40282	11.90
2N5589	6.82	HXTR5104	50.00	40290	2.48
		MM1500	32.20		

### CHIP CAPACITORS

	1pf	27pf	220pf	1200pf
	1.5pf	33pf	240pf	1500pf
	2.2pf	39pf	270pf	1800pf
	2.7pf	47pf	300pf	2200pf
	3.3pf	56pf	330pf	2700pf
	3.9pf	68pf	360pf	3300pf
	4.7pf	82pf	390pf	3900pf
	5.6pf	100pf	430pf	4700pf
	6.8pf	110pf	470pf	5600pf
	8.2pf	120pf	510pf	6800pf
	10pf	130pf	560pf	8200pf
	12pf	150pf	620pf	.010mf
	15pf	160pf	680pf	.012mf
	18pf	180pf	820pf	.015mf
	22pf	200pf	1000pf	.018mf

### PRICES

1 to 10	\$1.49
11 - 50	1.29
51 - 100	.89
101 - 1,000	.69
1,001 up	.49

### ATLAS CRYSTAL FILTERS FOR ATLAS HAM GEAR

5.52-2.7/8
5.595-2.7/8/U
5.595-500/4/CW
5.595-2.7LSB
5.595-2.7USB
5.645-2.7/8
9.0USB/CW

YOUR CHOICE \$24.95

**NEW — TOLL-FREE NO. 800-528-0180 — please, orders only!**

# MHz electronics

**MOTOROLA Semiconductor** The RF Line


**MRF454**

\$21.83

**NPN SILICON RF POWER TRANSISTORS**

... designed for power amplifier applications in industrial, commercial and amateur radio equipment to 30 MHz.

- Specified 12.5 Volt, 30 MHz Characteristics –  
Output Power = 80 Watts  
Minimum Gain = 12 dB  
Efficiency = 50%

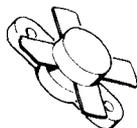

**MRF458**

\$20.68

**NPN SILICON RF POWER TRANSISTOR**

... designed for power amplifier applications in industrial, commercial and amateur radio equipment to 30 MHz.

- Specified 12.5 Volt, 30 MHz Characteristics –  
Output Power = 80 Watts  
Minimum Gain = 12 dB  
Efficiency = 50%
- Capable of Withstanding 30:1 Load VSWR @ Rated P<sub>out</sub> and V<sub>CC</sub>


**NPN SILICON RF POWER TRANSISTOR**

... designed primarily for use in large-signal output amplifier stages. Intended for use in Citizen-Band communications equipment operating at 27 MHz. High breakdown voltages allow a high percentage of up-modulation in AM circuits.

**MRF472**

\$2.50

- Specified 12.5 V, 27 MHz Characteristics –  
Power Output = 4.0 Watts  
Power Gain = 10 dB Minimum  
Efficiency = 65% Typical

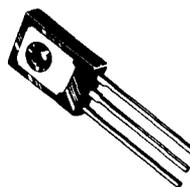

**MRF475**

**NPN SILICON RF POWER TRANSISTOR**

... designed primarily for use in single sideband linear amplifier output applications in citizens band and other communications equipment operating to 30 MHz.

- Characterized for Single Sideband and Large-Signal Amplifier Applications Utilizing Low-Level Modulation.
- Specified 13.6 V, 30 MHz Characteristics –  
Output Power = 12 W (PEP)  
Minimum Efficiency = 40% (SSB)  
Output Power = 4.0 W (CW)  
Minimum Efficiency = 50% (CW)  
Minimum Power Gain = 10 dB (PEP & CW)
- Common Collector Characterization



\$5.00

**MHW710 - 2**

\$46.45

440 to 470MC

**UHF POWER AMPLIFIER MODULE**

... designed for 12.5 volt UHF power amplifier applications in industrial and commercial FM equipment operating from 400 to 512 MHz.

- Specified 12.5 Volt, UHF Characteristics –  
Output Power = 13 Watts  
Minimum Gain = 19.4 dB  
Harmonics = 40 dB
- 50 Ω Input/Output Impedance
- Guaranteed Stability and Ruggedness
- Gain Control Pin for Manual or Automatic Output Level Control
- Thin Film Hybrid Construction Gives Consistent Performance and Reliability



## Tektronix Test Equipment

B	Wideband High Gain Plug In	\$ 51.00
CA	Dual Trace Plug In	120.00
K	Fast Rise DC Plug In	63.00
N	Sampling Plug In	200.00
R	Transistor Rise/Time Plug In	116.00
W	High Gain Differential Comparator Plug In	283.00
FU-2	Test Load Plug In for 530/540/550 Main Frames	50.00
1A2	Wideband Dual Trace Plug In	216.00
1S1	Sampling Unit With 350P Rise/Time DC to 1GHZ	730.00
2A61	AC Differential Plug In	133.00
3S3	Dual Trace Sampling DC to 1GHZ Plug In	250.00
3S76	Dual Trace Sampling DC to 875MHz Plug In	250.00
3177A	Sampling Sweep Plug In	250.00
3L10	Spectrum Analyzer   to 35MHz Plug In	1000.00
50	Amplifier Plug In	50.00
51	Sweep Plug In	50.00
53B	Wideband High Gain Plug In	25.00
53/54B	Wideband High Gain Plug In	45.00
53/54C	Dual Trace Plug In	112.50
53/54D	High Gain DC Differential Plug In	38.00
53/54G	Wideband DC Differential Plug In	68.00
53/54L	Fast Rise High Gain Plug In	68.00
84	Test Plug In For 580/581 Main Frames	75.00
107	Square Wave Generator .4 to 1MHz	46.00
RM122	Preamplifier 2Hz to 40kHz	63.00
123	AC Coupled Preamplifier	25.00
131	Current Probe Amplifier	50.00
184	Time Mark Generator	363.00
R240	Program Control Unit	150.00
280	Trigger Countdown Unit	84.00
455	Portable Dual Trace 50MHz Scope	2000.00
465	Portable Dual Trace 100MHz Scope	2500.00
503	DC to 450KHz Scope Rack Mount	250.00
535A	DC to 15MHz Scope Rack Mount	263.00
543	DC to 33MHz Scope	300.00
561	DC to 10MHz Scope Rack Mount	150.00
561A	DC to 10MHz Scope Rack Mount	200.00

## Scopes with Plug-ins

561A	DC to 10MHz Scope with a 3576 Dual Trace DC to 875MHz Sampling Plug In and a 3177A Sweep Plug In. Rack Mount	600.00
565	DC to 10MHz Dual Beam Scope with a 2A63 Diff. and a 2A61 Diff. Plug In's	900.00
581	DC to 80MHz Scope with a 82 Dual Trace High Gain Plug In	650.00

## Tubes

2E26	\$ 5.00	4CX350FJ	\$116.00	6146W	12.00
3-500Z	102.00	4CX1000A	300.00	6159	10.60
3-1090Z	268.00	4CX1500B	350.00	6161	75.00
3B2B/466A	5.00	4CX1500A	750.00	6293	18.50
3X250A3	150.00	4E27	50.00	6360	6.95
4-65A	45.00	4X150A	41.00	6907	40.00
4-125A	58.50	4X150D	52.00	6939	14.75
4-250A	68.50	4X150G	74.00	7360	12.00
4-400A	71.00	572B/1160L	39.00	7984	10.40
4-1000A	184.00	6LF6	5.00	8072	49.00
5-500A	145.00	6L06	5.00	8106	2.00
4CX250B	85.00	811A	12.95	8156	7.85
4CX250F/G	55.00	813	29.00	8226	127.70
4CX250R	113.00	5894/A	42.00	8295/PL172	328.00
4CX300A	92.00	6146	5.00	8458	25.75
4CX300A	147.00	6146A	6.00	8560A/AS	50.00
4CX350A	107.00	6146B/8298A	7.00	8908	9.00
				8950	9.00

**NEW — TOLL-FREE NO. 800-528-0180 — please, orders only!**

# MHz electronics

## MICROWAVE COMPONENTS

### ARRA

2416	Variable Attenuator	\$ 50.00
3614-60	Variable Attenuator 0 to 60dB	75.00
KU520A	Variable Attenuator 18 to 26.5 GHz	100.00
4684-20C	Variable Attenuator 0 to 180dB	100.00
6684-20F	Variable Attenuator 0 to 180dB	100.00

### General Microwave

Directional Coupler 2 to 4GHz 20dB Type N	75.00
---	-------

### Hewlett Packard

H487B	100 ohms Neg. Thermistor Mount (NEW)	150.00
H487B	100 ohms Neg. Thermistor Mount (USED)	100.00
477B	200 ohms Neg. Thermistor Mount (USED)	100.00
X487A	100 ohms Neg. Thermistor Mount (USED)	100.00
X487B	100 ohms Neg. Thermistor Mount (USED)	125.00

J468A	100 ohms Neg. Thermistor Mount (USED)	150.00
478A	200 ohms Neg. Thermistor Mount (USED)	150.00
J382	5.85 to 8.2 GHz Variable Attenuator 0 to 50dB	250.00
X382A	8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	250.00

394A	1 to 2 GHz Variable Attenuator 6 to 120dB	250.00
NK292A	Waveguide Adapter	65.00
K422A	18 to 26.5 GHz Crystal Detector	250.00
8436A	Bandpass Filter 8 to 12.4 GHz	75.00

8439A	2 GHz Notch Filter	75.00
8471A	RF Detector	50.00
H532A	7.05 to 10 GHz Frequency Meter	300.00
G532A	3.95 to 5.85 GHz Frequency Meter	300.00
J532A	5.85 to 8.2 GHz Frequency Meter	300.00

809A	Carriage with a 444A Slotted Line Untuned Detector Probe and 809B Coaxial Slotted Section 2.6 to 18 GHz	175.00
------	---	--------

### Merrimac

AU-25A/	801115 Variable Attenuator	100.00
AU-26A/	801162 Variable Attenuator	100.00

### Microlab/FXR

X6385	Horn 8.2 - 12.4 GHz	60.00
601-B18	X to N Adapter 8.2 - 12.4 GHz	35.00
Y6100	Coupler	75.00

### Narda

4013C-10/	22540A Directional Coupler 2 to 4 GHz 10dB Type SMA	90.00
4014-10/	22538 Directional Coupler 3.85 to 8 GHz 10dB Type SMA	90.00
4014C-6/	22876 Directional Coupler 3.85 to 8 GHz 6dB Type SMA	90.00
4015C-10/	22539 Directional Coupler 7.4 to 12 GHz 10dB Type SMA	95.00
4015C-30/	23105 Directional Coupler 7 to 12.4 GHz 30dB Type SMA	95.00
3044-20	Directional Coupler 4 to 8 GHz 20dB Type N	125.00
3040-20	Directional Coupler 240 to 500 MC 20dB Type N	125.00
3043-20/	22006 Directional Coupler 1.7 to 4 GHz 20dB Type N	125.00
3003-10/	22011 Directional Coupler 2 to 4 GHz 10dB Type N	75.00
3003-30/	22012 Directional Coupler 2 to 4 GHz 30dB Type N	75.00
3043-30/	22007 Directional Coupler 1.7 to 3.5 GHz 30dB Type N	125.00
22574	Directional Coupler 2 to 4 GHz 10dB Type N	125.00
3033	Coaxial Hybrid 2 to 4 GHz 3dB Type N	125.00
3032	Coaxial Hybrid 950 to 2 GHz 3 dB Type N	125.00
784/	22380 Variable Attenuator 1 to 90dB 2 to 2.5 GHz Type SMA	550.00
22377	Waveguide to Type N Adapter	35.00
720-6	Fixed Attenuator 8.2 to 14.4 GHz 6 dB	50.00
3503	Waveguide	25.00

### PRD

U101	12.4 to 18 GHz Variable Attenuator 0 to 60dB	300.00
X101	8.2 to 12.4 GHz Variable Attenuator 0 to 60dB	200.00
C101	Variable Attenuator 0 to 60dB	200.00
205A/367	Slotted Line with Type N Adapter	100.00
195B	8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	100.00
185BS1	7.05 to 10 GHz Variable Attenuator 0 to 40dB	100.00
196C	8.2 to 12.4 GHz Variable Attenuator 0 to 45dB	100.00
170B	3.95 to 5.85 GHz Variable Attenuator 0 to 45dB	100.00
588A	Frequency Meter 5.3 to 6.7 GHz	100.00
140A,C,D,E	Fixed Attenuators	25.00
109J,I	Fixed Attenuators	25.00
WEINSCHEL ENG.	2692 Variable Attenuator +30 to 60dB	100.00

### COMPUTER I.C. SPECIALS

MEMORY	DESCRIPTION	PRICE
2708	1K x 8 EPROM	\$ 7.99
2716/2516	2K x 8 EPROM 5Volt Single Supply	20.00
2114/9114	1K x 4 Static RAM 450ns	6.99
2114L2	1K x 4 Static RAM 250ns	8.99
2114L3	1K x 4 Static RAM 350ns	7.99
4027	4K x 1 Dynamic RAM	3.99
4060/2107	4K x 1 Dynamic RAM	3.99
4050/9050	4K x 1 Dynamic RAM	3.99
2111A-2/8111	256 x 4 Static RAM	3.99
2112A-2	256 x 4 Static RAM	3.99
2115AL-2	1K x 1 Static RAM 55ns	4.99
6104-3/4104	4K x 1 Static RAM 320ns	14.99
7141-2	4K x 1 Static RAM 200ns	14.99
MCM6641L20	4K x 2 Static RAM 200ns	14.99
9131	1K x 1 Static RAM 300ns	10.99

### C.P.U.'S ECT.

MC6800L	Microprocessor	13.80
MCM6810AP	128 x 8 Static RAM 450ns	3.99
MCM68A10P	128 x 8 Static RAM 360ns	4.99
MCM68B10P	128 x 8 Static RAM 250ns	5.99
MC6820P	PIA	8.99
MC6820L	PIA	9.99
MC6821P	PIA	8.99
MC68B21P	PIA	9.99
MCM6830L7	Mikbug	14.99
MC6840P	PTM	8.99
MC6845P	CRT Controller	29.50
MC6845L	CRT Controller	33.00
MC6850L	ACIA	10.99
MC6852P	SSDA	5.99
MC6852L	SSDA	11.99
MC6854P	ADLC	22.00
MC6860CJCS	0-600 BPS Modem	29.00
MC6862L	2400 BPS Modem	14.99
MK3850N-3	F8 Microprocessor	9.99
MK3852P	F8 Memory Interface	16.99
MK3852N	F8 Memory Interface	9.99
MK3854N	F8 Direct Memory Access	9.99
8008-1	Microprocessor	4.99
8080A	Microprocessor	8.99
Z80CPU	Microprocessor	14.99
6520	PIA	7.99
6530	Support For 6500 series	15.99
2650	Microprocessor	10.99
TMS1000NL	Four Bit Microprocessor	9.99
TMS4024NC	9 x 64 Digital Storage Buffer (FIFO)	9.99
TMS6011NC	UART	9.99
MC14411	Bit Rate Generator	11.99
AY5-4007D	Four Digit Counter/Display Drivers	8.99
AY5-9200	Repertory Dialler	9.99
AY5-9100	Push Button Telephone Diallers	7.99
AY5-2376	Keyboard Encoder	19.99
AY3-8500	TV Game Chip	5.99
TR1402A	UART	9.99
PR1472B	UART	9.99
PT1482B	UART	9.99
8257	DMA Controller	9.99
8251	Communication Interface	9.99
8228	System Controller & Bus Driver	5.00
8212	8 Bit Input/Output Port	5.00
MC14410CP	2 of 8 Tone Encoder	9.99
MC14412	Low Speed Modem	14.99
MC14408	Binary to Phone Pulse Converter	12.99
MC14409	Binary to Phone Pulse Converter	12.99
MC1488L	RS232 Driver	1.00
MC1489L	RS232 Receiver	1.00
MC1405L	A/D Converter Subsystem	9.00
MC1406L	6 Bit D/A Converter	7.50
MC1408/6/7/8	8 Bit D/A Converter	4.50
MC1330P	Low Level Video Detector	1.50
MC1349/50	Video IF Amplifier	1.17
MC1733L	LM733 OP Amplifier	2.40
LM565	Phase Lock Loop	2.50

**NEW — TOLL-FREE NO. 800-528-0180 — please, orders only!**

# DIRECTION FINDERS

If you're serious about direction finding, you want the best, most dependable and proven equipment for a fast find, whether it's for a downed aircraft or a repeater jammer.

If your needs are in the 100-300 MHz range, think of L-Tronics for ground, air, or marine DF. We also have equipment that gives dual capability, such as search & rescue/amateur radio, 146/220 amateur, and air/marine SAR.

Our units will DF on AM, FM, pulsed signals and random noise. The meter reads left-right in the DF mode for fast, accurate bearings, and left to right signal strength in the REceive mode (120 dB total range with the sensitivity control). Its 3 dB antenna gain and .06 uV typical DF sensitivity allow the crystal-controlled unit to hear and positively track a weak signal at very long ranges. It has no 180° ambiguity.

Over 3,000 of our units are in the field being used to save lives, catch jammers, find instrument packages, track vehicles. Prices start at under \$250 for factory-built equipment backed by warranty, money-back guarantee, and factory service and assistance. Write today for a free brochure and price list.

L-TRONICS (Attention Ham Dept.)  
5546 Cathedral Oaks Rd.  
Santa Barbara, CA 93111



**The HAM SHACK**

808 N. Main  
Evansville, IN 47710

## TEN-TEC

546 Omni C	\$1090.00
580 Delta	770.00
570 Century 21	340.00
515 Argonaut	415.00
280 Power Supply	155.00
255 Power Supply/Spkr.	175.00
243 Vfo — Omni	169.00
283 Vfo — Delta	169.00
444 Hercules Amp.	1340.00

## SKIPJACK®

The Keyboard  
they're all talking about  
P.C. Kit \$52.80  
Full Kit 345.00

MFJ Keyboard 256 buffer	\$295.00
KANTRONICS Mini-reader	279.00
AZDEN PCS-3000	320.00
VISTA 8a Power Supply	60.00
MIRAGE B108	150.00
CUBIC Astro 103	1175.00
SANTEC HT 1200	325.00

Write or call Dan, N9APA

**812-422-0231**

MON-FRI 9AM-6PM • SAT 9AM-4PM

## Rx for a Bad Day

Is it one of those dull gloomy days when even the birds are walking, and it's not a fit day to go out and put up that new sloper or inverted vee antenna you wanted to try? DX isn't coming through yet because the MUF isn't right, some jerk squirrel keeps kerchunking the repeater or plays tunes on the Touchtone® so that two meters isn't fun. Maybe the wind played havoc with your beam last night and now it looks like a limp pretzel or some modern art object, or maybe your rig blew up in the middle of a QSO or just before that sked with a rare station in some far off land.

Any fool knows all these things aren't going to happen to you at once. But if it is 'one of those days' maybe you can just forget the whole mess and brighten your and someone else's day a little by taking some time to think of a fellow ham you admire and respect to nominate for Dayton's "Amateur of the Year Award" for 1981. No, it's not too early to think about it. It does take a little time and effort to nominate some one for "Amateur of the Year."

What is the stature of this individual that we seek for recognition each year at Dayton?

First, he or she will be a well-respected person in the community; a leader, not only in amateur radio activity, but in civic activity as well. He will probably be licensed for at least 10 years or more for it is long term overall excellence in amateur radio that we are looking for.

His contribution to amateur radio may be in any of the hobby related areas. Possibly his greatest contribution is in the engineering field of our hobby, or his expertise may be in antenna design, some new type of modulation or an improvement to existing design, etc. Maybe he has contributed greatly to improvement of amateur regulations or possibly his contribution is the legal field of

our hobby, a very important one these days. Get the idea? In short, an outstanding individual and amateur.

In 1974, another award was established, the "Special Achievement Award." This award is just what it would seem to be — an award for one-time special event or specialized activity by an amateur or group of amateurs. This activity may be in the engineering field — QRP — DXpeditions — net activity, — emergency work or any one-time outstanding activity related to the amateur radio hobby.

Nominees for both of these awards may be from anywhere in the world, not just the U.S.A.

So! Don't just sit back and say, "Gee!, somebody ought to nominate that guy for "Amateur of the Year." Don't wait for George to do it. Give us all the details you can gather, especially activities that are directly attributable to him or her.

All nominations are carefully reviewed and are saved from one year to the next for future consideration and to allow some nominees to develop to their full potential. All nominations are considered for both awards, and the awards will be presented at the 1981 HAM-VENTION Banquet.

So, have you nominated some one in the past? You may want to renominate him with

update on recent activities or just send in update information on his latest accomplishments.

Do it now! Besides you may win a set of free tickets to the "HAMVENTION" for your nominee and yourself.

For more information or nomination blanks (not mandatory) write to the address below:

HAMVENTION	or	Bob Roettele, W8UNV
P.O. Box 44		Awards Chairman
Dayton, Ohio 45401		1299 Hanes Road
Attention: Awards Committee		Xenia, Ohio 45385



### 7400

SN7400N	.25	SN7472N	.29	SN74157N	.79
SN7401N	.20	SN7473N	.35	SN74157N	.89
SN7402N	.25	SN7474N	.35	SN74160N	.89
SN7403N	.25	SN7475N	.35	SN74161N	.89
SN7404N	.25	SN7476N	.35	SN74163N	.89
SN7405N	.25	SN7477N	.35	SN74164N	.89
SN7406N	.25	SN7478N	5.00	SN74165N	.89
SN7407N	.25	SN7479N	5.00	SN74166N	1.25
SN7408N	.25	SN7480N	5.00	SN74167N	2.79
SN7409N	.25	SN7481N	.35	SN74168N	.89
SN7410N	.25	SN7482N	.35	SN74169N	.89
SN7411N	.25	SN7483N	.69	SN74170N	1.95
SN7412N	.25	SN7484N	.69	SN74171N	4.95
SN7413N	.25	SN7485N	.69	SN74172N	4.95
SN7414N	.25	SN7486N	.69	SN74173N	1.99
SN7415N	.25	SN7487N	1.35	SN74174N	.99
SN7416N	.40	SN7488N	.49	SN74175N	.89
SN7417N	.49	SN7489N	.49	SN74176N	.79
SN7418N	.29	SN7490N	.59	SN74177N	.79
SN7419N	.29	SN7491N	.59	SN74178N	.79
SN7420N	.29	SN7492N	.45	SN74179N	.49
SN7421N	.29	SN7493N	.45	SN74180N	2.29
SN7422N	.45	SN7494N	.69	SN74181N	1.49
SN7423N	.29	SN7495N	.69	SN74182N	.79
SN7424N	.29	SN7496N	.69	SN74183N	2.49
SN7425N	.29	SN7497N	3.00	SN74184N	.49
SN7426N	.29	SN7498N	1.49	SN74185N	1.25
SN7427N	.29	SN7499N	.35	SN74186N	1.25
SN7428N	.39	SN74107N	.39	SN74187N	2.49
SN7429N	.39	SN74108N	.39	SN74188N	1.25
SN7430N	.25	SN74109N	.39	SN74189N	1.25
SN7431N	.25	SN74110N	.39	SN74190N	1.25
SN7432N	.25	SN74111N	.39	SN74191N	1.25
SN7433N	.25	SN74112N	.39	SN74192N	.89
SN7434N	.25	SN74113N	.39	SN74193N	.89
SN7435N	.25	SN74114N	.39	SN74194N	.89
SN7436N	.25	SN74115N	.39	SN74195N	.89
SN7437N	.25	SN74116N	.39	SN74196N	.89
SN7438N	.25	SN74117N	.39	SN74197N	.89
SN7439N	.25	SN74118N	.39	SN74198N	.89
SN7440N	.25	SN74119N	.39	SN74199N	.89
SN7441N	.25	SN74120N	.39	SN74200N	.89
SN7442N	.25	SN74121N	.39	SN74201N	.89
SN7443N	.25	SN74122N	.39	SN74202N	.89
SN7444N	1.10	SN74123N	3.25	SN74203N	.89
SN7445N	.89	SN74124N	3.49	SN74204N	.89
SN7446N	.79	SN74125N	3.49	SN74205N	.89
SN7447N	.69	SN74126N	3.49	SN74206N	.89
SN7448N	.79	SN74127N	3.49	SN74207N	.89
SN7449N	.20	SN74128N	1.99	SN74208N	.89
SN7450N	.20	SN74129N	1.25	SN74209N	.89
SN7451N	.20	SN74130N	1.25	SN74210N	.89
SN7452N	.20	SN74131N	1.25	SN74211N	.89
SN7453N	.20	SN74132N	1.25	SN74212N	.89
SN7454N	.20	SN74133N	1.25	SN74213N	.89
SN7455N	.20	SN74134N	1.25	SN74214N	.89
SN7456N	.20	SN74135N	1.25	SN74215N	.89
SN7457N	.20	SN74136N	1.25	SN74216N	.89
SN7458N	.20	SN74137N	1.25	SN74217N	.89
SN7459N	.20	SN74138N	1.25	SN74218N	.89
SN7460N	.20	SN74139N	1.25	SN74219N	.89
SN7461N	.20	SN74140N	1.25	SN74220N	.89
SN7462N	.20	SN74141N	1.25	SN74221N	.89
SN7463N	.20	SN74142N	1.25	SN74222N	.89
SN7464N	.20	SN74143N	1.25	SN74223N	.89
SN7465N	.20	SN74144N	1.25	SN74224N	.89
SN7466N	.20	SN74145N	1.25	SN74225N	.89
SN7467N	.20	SN74146N	1.25	SN74226N	.89
SN7468N	.20	SN74147N	1.25	SN74227N	.89
SN7469N	.20	SN74148N	1.25	SN74228N	.89
SN7470N	.20	SN74149N	1.25	SN74229N	.89
SN7471N	.20	SN74150N	1.25	SN74230N	.89

### 74LS

74LS00	.29	74LS192	1.15
74LS01	.29	74LS193	1.15
74LS02	.29	74LS194	1.15
74LS03	.29	74LS195	1.15
74LS04	.29	74LS196	1.15
74LS05	.29	74LS197	1.15
74LS06	.29	74LS198	1.15
74LS07	.29	74LS199	1.15
74LS08	.29	74LS200	1.15
74LS09	.29	74LS201	1.15
74LS10	.29	74LS202	1.15
74LS11	.29	74LS203	1.15
74LS12	.29	74LS204	1.15
74LS90	.29	74LS282	1.15

### 74S

74S00	.50	74S244	3.25
74S01	.50	74S245	1.45
74S02	.50	74S246	1.45
74S03	.50	74S247	1.45
74S04	.50	74S248	1.45
74S05	.50	74S249	1.45
74S06	.50	74S250	1.45
74S07	.50	74S251	1.45
74S08	.50	74S252	1.45
74S09	.50	74S253	1.45
74S10	.50	74S254	1.45
74S11	.50	74S255	1.45
74S12	.50	74S256	1.45
74S13	.50	74S257	1.45
74S14	.50	74S258	1.45
74S15	.50	74S259	1.45
74S16	.50	74S260	1.45
74S17	.50	74S261	1.45
74S18	.50	74S262	1.45
74S19	.50	74S263	1.45
74S20	.50	74S264	1.45
74S21	.50	74S265	1.45
74S22	.50	74S266	1.45
74S23	.50	74S267	1.45
74S24	.50	74S268	1.45
74S25	.50	74S269	1.45
74S26	.50	74S270	1.45
74S27	.50	74S271	1.45
74S28	.50	74S272	1.45
74S29	.50	74S273	1.45
74S30	.50	74S274	1.45
74S31	.50	74S275	1.45
74S32	.50	74S276	1.45
74S33	.50	74S277	1.45
74S34	.50	74S278	1.45
74S35	.50	74S279	1.45
74S36	.50	74S280	1.45
74S37	.50	74S281	1.45
74S38	.50	74S282	1.45
74S39	.50	74S283	1.45
74S40	.50	74S284	1.45
74S41	.50	74S285	1.45
74S42	.50	74S286	1.45
74S43	.50	74S287	1.45
74S44	.50	74S288	1.45
74S45	.50	74S289	1.45
74S46	.50	74S290	1.45
74S47	.50	74S291	1.45
74S48	.50	74S292	1.45
74S49	.50	74S293	1.45
74S50	.50	74S294	1.45

### CA-LINEAR

CA3013H	2.15	CA3089N	3.75
CA3023H	3.25	CA3096N	3.75
CA3031H	1.30	CA3130H	1.39
CA3046N	1.35	CA3140H	1.39
CA3059N	3.25	CA3150H	1.25
CA3060N	3.25	CA3161N	1.25
CA3069H	1.35	CA3169N	1.25

### CD-CMOS

CD4000	.39	CD4082	.39
CD4001	.39	CD4093	.39
CD4002	.39	CD4098	.39
CD4003	.39	CD4099	.39
CD4004	.39	CD4100	.39
CD4005	.39	CD4101	.39
CD4006	.39	CD4102	.39
CD4007	.39	CD4103	.39
CD4008	.39	CD4104	.39
CD4009	.39	CD4105	.39
CD4010	.39	CD4106	.39
CD4011	.39	CD4107	.39
CD4012	.39	CD4108	.39
CD4013	.39	CD4109	.39
CD4014	.39	CD4110	.39
CD4015	.39	CD4111	.39
CD4016	.39	CD4112	.39
CD4017	.39	CD4113	.39
CD4018	.39	CD4114	.39
CD4019	.39	CD4115	.39
CD4020	.39	CD4116	.39
CD4021	.39	CD4117	.39
CD4022	.39	CD4118	.39
CD4023	.39	CD4119	.39
CD4024	.39	CD4120	.39
CD4025	.39	CD4121	.39
CD4026	.39	CD4122	.39
CD4027	.39	CD4123	.39
CD4028	.39	CD4124	.39
CD4029	.39	CD4125	.39
CD4030	.39	CD4126	.39
CD4031	.39	CD4127	.39
CD4032	.39	CD4128	.39
CD4033	.39	CD4129	.39
CD4034	.39	CD4130	.39
CD4035	.39	CD4131	.39
CD4036			



*Ham Radio's guide to help you find your local*

## Arizona

### POWER COMMUNICATIONS CORPORATION

1640 W. CAMELBACK ROAD  
PHOENIX, AZ 85015  
602-242-6030 or 242-8990  
Arizona's #1 "Ham" Store. Kenwood, Yaesu, Icom and more.

## California

### C & A ELECTRONIC ENTERPRISES

2210 S. WILMINGTON AVE.  
SUITE 105  
CARSON, CA 90745  
213-834-5868  
Not The Biggest, But The Best —  
Since 1962.

### JUN'S ELECTRONICS

3919 SEPULVEDA BLVD.  
CULVER CITY, CA 90230  
213-390-8003 Trades  
714-463-1886 San Diego  
The Home of the One Year Warranty  
— Parts at Cost — Full Service.

### QUEMENT ELECTRONICS

1000 SO. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-5900  
Serving the world's Radio Amateurs  
since 1933.

### SHAVER RADIO, INC.

1378 S. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-1103  
Azden, Icom, Kenwood, Tempo,  
Ten-Tec, Yaesu and many more.

## Connecticut

### HATRY ELECTRONICS

500 LEDYARD ST. (SOUTH)  
HARTFORD, CT 06114  
203-527-1881  
Connecticut's Oldest Ham Radio  
Dealer

## Delaware

### DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD  
NEW CASTLE, DE 19720  
302-328-7728  
Icom, Ten-Tec, Swan, DenTron,  
Tempo, Yaesu, Azden, and more.  
One mile off I-95, no sales tax.

## Florida

### AGL ELECTRONICS, INC.

1898 DREW STREET  
CLEARWATER, FL 33515  
813-461-HAMS  
West Coast's only full service  
Amateur Radio Store.

### AMATEUR RADIO CENTER, INC.

2805 N.E. 2ND AVENUE  
MIAMI, FL 33137  
305-573-8383  
The place for great dependable  
names in Ham Radio.

### RAY'S AMATEUR RADIO

1590 US HIGHWAY 19 SO.  
CLEARWATER, FL 33516  
813-535-1416  
Atlas, B&W, Bird, Cushcraft,  
DenTron, Drake, Hustler, Hy-Gain,  
Icom, K.D.K., Kenwood, MFJ, Rohn,  
Swan, Ten-Tec, Wilson.

## Illinois

### AUREUS ELECTRONICS, INC.

1415 N. EAGLE STREET  
NAPERVILLE, IL 60540  
312-420-8629  
"Amateur Excellence"

### ERICKSON COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE.  
CHICAGO, IL 60630  
Chicago — 312-631-5181  
Outside Illinois — 800-621-5802  
Hours: 9:30-5:30 Mon, Tu, Wed & Fri.;  
9:30-9:00 Thurs; 9:00-3:00 Sat.

## Indiana

### THE HAM SHACK

808 NORTH MAIN STREET  
EVANSVILLE, IN 47710  
812-422-0231  
Discount prices on Ten-Tec, Cubic,  
Hy-Gain, MFJ, Azden, Kantronics,  
Santec and others.

## Kansas

### ASSOCIATED RADIO

8012 CONSER, P. O. BOX 4327  
OVERLAND PARK, KS 66204  
913-381-5900  
America's No. 1 Real Amateur Radio  
Store. Trade — Sell — Buy.

## Maryland

### THE COMM CENTER, INC.

LAUREL PLAZA, RT. 198  
LAUREL, MD 20810  
800-638-4486  
Kenwood, Drake, Icom, Ten-Tec,  
Tempo, DenTron, Swan & Apple  
Computers.

## Massachusetts

### TEL-COM, INC.

675 GREAT ROAD, RT. 119  
LITTLETON, MA 01460  
617-486-3040  
The Ham Store of New England You  
Can Rely On.

### TUFTS RADIO ELECTRONICS

206 MYSTIC AVENUE  
MEDFORD, MA 02155  
617-391-3200  
New England's friendliest ham store.

## Minnesota

### PAL ELECTRONICS INC.

3452 FREMONT AVE. NO.  
MINNEAPOLIS, MN 55412  
612-521-4662  
Midwest's Fastest Growing Ham  
Store, Where Service Counts.

## New Hampshire

### EVANS RADIO, INC.

BOX 893, RT. 3A BOW JUNCTION  
CONCORD, NH 03301  
603-224-9961  
Icom, DenTron & Yaesu dealer. We  
service what we sell.

**Dealers:** *YOU SHOULD BE HERE TOO!*  
*Contact Ham Radio now for complete details.*

## Amateur Radio Dealer

### New Jersey

#### RADIOS UNLIMITED

P. O. BOX 347  
1760 EASTON AVENUE  
SOMERSET, NJ 08873  
201-469-4599  
New Jersey's Fastest Growing  
Amateur Radio Center.

#### ROUTE ELECTRONICS 46

225 ROUTE 46 WEST  
TOTOWA, NJ 07512  
201-256-8555  
Drake, Cubic, DenTron, Hy-Gain,  
Cushcraft, Hustler, Larsen, MFJ,  
Butternut, Fluke & Beckman  
Instruments, etc.

#### WITTIE ELECTRONICS

384 LAKEVIEW AVENUE  
CLIFTON, NJ 07011  
201-546-3000  
Same location for 63 years. Full-line  
authorized Drake dealer. We stock  
most popular brands of Antennas and  
Towers.

### New Mexico

#### PECOS VALLEY AMATEUR RADIO SUPPLY

112 W. FIRST STREET  
ROSWELL, NM 88201  
505-623-7388  
Now stocking Ten-Tec, Lunar, Icom,  
Morsematic, Bencher, Tempo,  
Hy-Gain, Avanti and more at low,  
low prices. Call for quote.

### New York

#### BARRY ELECTRONICS

512 BROADWAY  
NEW YORK, NY 10012  
212-925-7000  
New York City's Largest Full Service  
Ham and Commercial Radio Store.

#### GRAND CENTRAL RADIO

124 EAST 44 STREET  
NEW YORK, NY 10017  
212-599-2630  
Drake, Kenwood, Yaesu, Atlas,  
Ten-Tec, Midland, DenTron, Hy-Gain,  
Mosley in stock.

#### HARRISON RADIO CORP.

20 SMITH STREET  
FARMINGDALE, NY 11735  
516-293-7990  
"Ham Headquarters USA" since  
1925. Call toll free 800-645-9187.

#### RADIO WORLD

ONEIDA COUNTY AIRPORT  
TERMINAL BLDG.  
ORISKANY, NY 13424  
TOLL FREE 1 (800) 448-9338  
NY Res. 1 (315) 337-0203  
Authorized Dealer — ALL major  
Amateur Brands.  
We service *everything* we sell!  
Warren K2IXN or Bob WA2MSH.

### Ohio

#### UNIVERSAL AMATEUR RADIO, INC.

1280 AIDA DRIVE  
COLUMBUS (REYNOLDSBURG), OH  
43068  
614-866-4267  
Complete Amateur Radio Sales and  
Service. All major brands — spacious  
store near I-270.

### Pennsylvania

#### HAMTRONICS, DIV. OF TREVOSE ELECTRONICS

4033 BROWNSVILLE ROAD  
TREVOSE, PA 19047  
215-357-1400  
Same Location for 30 Years.

#### LaRUE ELECTRONICS

1112 GRANDVIEW STREET  
SCRANTON, PENNSYLVANIA 18509  
717-343-2124  
Icom, Bird, Cushcraft, CDE, Ham-  
Keys, VHF Engineering, Antenna  
Specialists.

#### SPECIALTY COMMUNICATIONS

2523 PEACH STREET  
ERIE, PA 16502  
814-455-7674  
Service, Parts, & Experience For Your  
Atlas Radio.

### Virginia

#### ELECTRONIC EQUIPMENT BANK

516 MILL STREET, N.E.  
VIENNA, VA 22180  
703-938-3350  
Metropolitan D.C.'s One Stop  
Amateur Store. Largest Warehousing  
of Surplus Electronics.

# CALL TOLL FREE

## For the best deal on

- AEA • Alliance • Ameco • Apple • ASP
- Avanti • Belden • Bencher • Bird • CDE
- CES • Communications Specialists
- Collins • Cushcraft • Daiwa • DenTron
- Drake • Hustler • Hy-Gain • Icom • IRL • KLM
- Kenwood • Larsen • Macrotronics • MFJ
- Midland • Mini-Products • Mirage • Mosley
- NPC • Newtronics • Nye • Panasonic
- Palomar Engineers • Regency • Robot
- Shure • Standard • Swan • Tempo
- Ten-Tec • Transcom • Yaesu

## MARCH SPECIALS

ETO Model 76A 2 kW  
linear ..... \$1339

TenTec Delta 580 trans-  
ceiver ..... \$759

NEW YAESU FT-480R all-  
mode 2-meters .... \$469

KENWOOD TS-830S  
transceiver .... In stock!

TEMPO S-1, only .... \$239  
with touchtone .... \$269

APPLE Disk Based  
System: Apple II or II  
Plus with 48k RAM in-  
stalled, Disk II with con-  
troller, RF Modulator;  
New DOS 3.3..... \$1945

Apple prices include prepaid shipping  
within continental United States

Erickson is accepting late model  
amateur radio equipment for service:  
full time technician on duty

## CALL TOLL FREE

(outside Illinois only)

## (800) 621-5802

HOURS: 9:30-5:30 Mon., Tues., Wed. & Fri.  
9:30-9:00 Thursday  
9:00-3:00 Saturday



## ERICKSON COMMUNICATIONS

Chicago, IL 60630  
5456 North Milwaukee Ave.  
(312) 631-5181 [within Illinois]


# 90 WATT AMPLIFIER: \$89.95!



**SPECIAL PACKAGE DEAL**

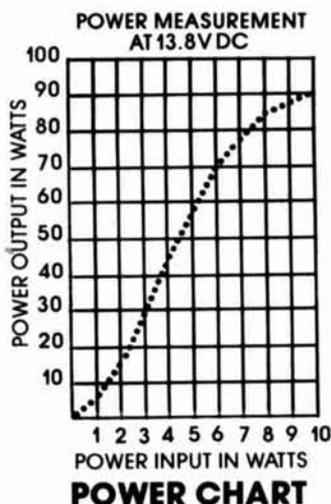**FACTORY DIRECT ONLY**

That's right — 90 watts of linear power for 2 meters class AB1 for FM & SSB for only \$89.95. Also offering a 15 dB gain in-line preamp with integrated T/R relay. A \$29.95 value, for only \$20.00 when purchased with the VJ90L Amplifier.



**\*ORDER TODAY TOLL FREE  
(800) 231-9649**

PRICING OFFER EXPIRES APRIL 1, 1981



VJ90L

Each VJ Product component is hand wired and individually tuned for maximum reliability and performance. VJ Products are guaranteed to be free of defects in parts or workmanship for 1 year from the date of purchase. POWER TRANSISTORS ARE EXCLUDED, BUT WARRANTED FOR 90 DAYS. Visa accepted. Immediate shipment guaranteed by VJ Products, Inc.

Please ship:  VJ90L @ \$89.95 + \$2.00 shipping  
 VJ90L & Preamp @ \$109.95 + \$3.50 shipping

Name \_\_\_\_\_ Call \_\_\_\_\_  
 Street \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
 Send Check, M/O, or Visa # \_\_\_\_\_ Exp. Date \_\_\_\_\_

SERVING THE ELECTRONICS INDUSTRY SINCE 1965 V-J Products, Inc. 505 E. Shaw Street, Pasadena, Texas 77506 (713) 477-0134

**FACSIMILE**  
 COPY SATELLITE PHOTOS,  
 WEATHER MAPS, PRESS!  
 The Faxes Are Clear — on our full size (18-1/2" wide) recorders. Free Fax Guide.

**TELETYPE**  
**RTTY MACHINES, PARTS, SUPPLIES**  
 ATLANTIC SURPLUS SALES (212) 372-0349  
 3730 NAUTILUS AVE. BROOKLYN, N.Y. 11224

**VHF COMMUNICATIONS**  
 is a quarterly radio amateur magazine specializing in VHF, UHF, and microwaves. An introductory annual subscription is \$15.00. USA representative:  
**SELECTO Inc.**  
 372 D Bel Marin Keys Blvd., Novato, CA 94947  
 Phone: (415) 883-2478 Telex: 171-046

**!!!!!!**

(Radio not included)  
**BEAT YOUR BATTERIES!**  
 OPERATE your SYNTHESIZED HT from any 13-30v D.C. source— Auto, Truck, Light Aircraft (12 or 28v system), Home Power Supply!  
 STEWART's New BATTERY-BEATER provides the proper REGULATED voltage for your rig and plenty of current for CONTINUOUS FULL POWER TRANSMIT! All day travel, all evening Simplex Net with NO QRT TO RE-CHARGE!  
 • NOT a battery charger but a FULL POWER SOURCE with Fused Circuit to protect your rig!  
 • RUGGED ALUMINUM CASE (except ICOM unit is built into IC-BP4 case for slide on/slide off power supply change!)  
 • YOUR NiCads REMAIN IN PLACE (except ICOM). Simply unplug for INSTANT PORTABILITY!  
 • DESIGNED by an engineer from NASA's Jet Propulsion Laboratory with components rated 50% beyond requirements!  
 • PRE-WIRED JACK (except ICOM) and detailed installation instructions supplied!  
 • 5 FT. power cord. VELCRO pads supplied to mount anywhere! 1 FULL YEAR WARRANTY!  
 • PRICE: All models— \$25.00 Post Paid, Ca. Res. add \$1.50 Tax. C.O.D.'s— You pay Postage and C.O.D. fees.  
 • NOW AVAILABLE for TEMPO S-1, S-2, S-5, KENWOOD TR-2400 (Retains Memory!), and ICOM IC-2A/T!  
 • PHONE: 1-213-357-7875 Collect for C.O.D.  
 STEWART QUADS P.O. Box 2335 IRVINGDALE, CA. 91706

**"LOOK"**  
 THIS BIG  IS THE  
 SYMBOL OF  
**METROLINA'S FASTEST  
 GROWING HAM DEALER**

**800-845-6183**  
**G.I.S.M.O.**  
 2305 CHERRY ROAD  
 ROCK HILL, S.C. 29730

Service Department  
 Call 803-366-7158

## Alaska Microwave Labs

4335 E. 5TH STREET  
ANCHORAGE, ALASKA 99504  
(907) 338-0340



# NEW! GaAs FETS

MGF 1400 NF 2.0DB  
AT 4GHZ MAG 15DB  
\$28.50

MGF 1412 NF .8DB  
AT 4GHZ MAG 18DB  
\$75.00



### TRANSISTORS

MRF901 FT4 5GHZ	\$3.00
BFR90 FT5 0GHZ	\$3.00
NEC 02137 FT4 5GHZ	\$3.25

### HOT CARRIER DIODES

MBD101 UHF—MICROWAVE	\$1.50
ND4131 4GHZ NF—5.75 DB	\$19.00
4GHZ NF—6.5 DB	\$2.00

### CHIP CAPACITORS

1.2, 2.2, 3.3, 4.7, 6.8, 10, 18, 22, 27,  
47, 100, 120, 180, 220, 270, 330,  
390, 470, 560, 680, 820, 1000,  
1200, 1800, 3900, 8200 \$ .60

### RF-IF I.C.

MWA-110  
RF-IF AMPLIFIER I.C.  
1 TO 400 MC 14 DB GAIN TYP  
3 TERMINAL IN. OUT. & GROUND \$ 7.95

### DUAL GATE MOSFET

RCA 40673 \$ 1.50

### COAX CONNECTORS

SMA CHASSIS MOUNT SQUARE FLANGE	\$ 5.90
SMA PLUG FOR RG-58	\$ 6.57
SMA PLUG FOR RG-174	\$ 6.57
TYPE N CHASSIS MOUNT SQUARE FLANGE	\$ 3.20
TYPE N PLUG FOR RG-9/RG-8	\$ 3.69

### FEED-THRU CAPACITORS

500 PF \$ .50

### TEFLON CIRCUIT BOARD

APPROX 3.5" x 5.0" x .010	\$ 5.50
APPROX 3.5" x 5.0" x .0312	\$ 6.50

### CHIP RESISTORS

50 OHM 1/2 WATT \$ 1.50

### PISTON TRIMMERS

Triko 201-01M 5-3PF( ) 1-8PF( ) \$ 2.50



**OPEN AT 8PM EST  
CLOSED AT 8PM PST**

**IF YOU DO NOT SEE  
WHAT YOU WANT ASK**

**ORDERS ARE POSTAGE PAID  
COD—VISA—MASTERCHARGE**

# Aye!

## Larsen's clan of Kūlrod® Antennas deliver top performance and value!



Performance and value are built into every Larsen Antenna because of craftsmanship that accepts no compromise.

Making mobile antennas, mounts and accessories is Larsen's *only* business. All of the company's research, engineering and production efforts are directed to making the best antennas money can buy. The end result is the exclusive Kūlrod by Larsen. A Kūlrod antenna delivers maximum radiation efficiency instead of losing power to heat.

Larsen's antenna clan includes low band, high band, quarter wave, VHF, UHF, mobile, fixed base and Kūlduckies for hand-helds. And Larsen offers every type of permanent and temporary vehicle mount — including a magnetic model that's a real grabber.

So whatever band you operate on, if your antenna is a Larsen you'll HEAR the difference!



## Larsen Antennas

P.O. Box 1686  
Vancouver, WA 98668  
Phone: (206) 573-2722

*In Canada, write to:*  
Canadian Larsen Electronics, Ltd.  
283 E. 11th Ave., Unit 101  
Vancouver, B.C. V5T 2C4  
Phone: (604) 872-8517

®Kūlrod is a Registered Trademark of Larsen Electronics, Inc.  
™Kūlduckie is a Trademark of Larsen Electronics, Inc.



## mini-speaker

Firestik's Speak-Easy mini-speaker is an acoustically tuned, wide-range air compression speaker that's small in size ( $2\frac{1}{4} \times 2$  inches) yet offers 300 to 10,000 Hz of audio response for crisp and clean sound. The Speak-Easy speaker is molded in an indoor/outdoor shockproof case and is easily mounted anywhere on cars, trucks, motorcycles, vans, airplanes, or RVs. In addition, it is exceptionally weathertight and resistant to corrosion. Mechanical features include a pulse dissipating disk, grill filter, a half-inch voice coil and a  $1\frac{3}{4}$ -inch magnet. Every Speak-Easy speaker comes complete with a  $6\frac{1}{2}$ -inch coaxial cord with a 3.5 mm plug, fully adjustable mounting bracket, and hardware for quick and easy installation. For more information on this new product, write to Firestik Antenna Company, 2614 East Adams, Phoenix, Arizona 85034.

## BASIC coding form

The Pocket-BASIC Coding Form by ARCsoft Publishers simplifies writing programs for the TRS-80 pocket computer. It's available in 50-sheet or 100-sheet pads and makes clear the relationship of overlapping memory locations such as A, A\$, A(01), and A\$(01).

Pocket-BASIC Coding Form displays the computer's fixed memories side-by-side with a large area for listing their contents. It also gives plenty of space for the programmer to label and list his flexible memories. The face of the form has space for program title, programmer's name, date, and page number plus ample room for special notes and comments.


The reverse of the  $8\frac{1}{2} \times 11$  inch form is precision-ruled for thirty horizontal program lines, each divided by eighty vertical columns. Program lines are numbered in standard 10-300 line numbers in the margin for spotting at a glance. Vertical columns, left to right across the 11-inch width of the sheet, are numbered 1-80 for easy identification of available spaces in a standard TRS-80 pocket computer input memory. A program using all available steps and memories can be listed on the form's thirty lines by packing for maximum efficiency. Using shorter line contents, a very elaborate program can be listed on two sheets from a pad. The form can be used with any computer in the BASIC language.

Pads are available from ARCsoft Publishers, P.O. Box 132E, Woodboro, Maryland 21798. Pads of fifty sheets sell for \$2.95 plus \$1.00 postage; pads of one hundred sheets sell for \$3.95 plus \$1.00 postage.
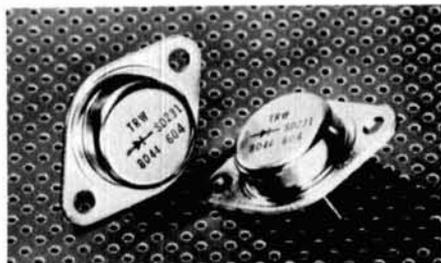
## dual Schottkys

Two dual-power Schottky diodes that require no snubber networks have been introduced by TRW Power Semiconductors. The SD-231 and SD-232 diodes are dual diode versions of TRW's recently introduced SD-31 and SD-32 Schottky diodes. All four devices are high-voltage 30-amp diodes with a junction temperature rating of  $175^{\circ}\text{C}$ , which TRW says is higher than any comparable Schottky device.

The SD-231 is rated at  $60 V_{\text{RMM}}$ , the SD-232 at  $50 V_{\text{RMM}}$ . Both are housed in a TO-204MA package (formerly TO-3), and both are designed for rectification and commutation in



high-current 5-volt logic supplies in military or industrial use. The two new diodes achieve avalanche protection with a shunt P-N diode, which is formed in addition to the Schottky barrier. This P-N diode breaks down at a lower voltage than the Schottky diode. But because the current is more evenly distributed along the P-N junction, large amounts of reverse energy can be tolerated. It is this ability to withstand high reverse energy, along with the devices' high voltage rating, that permit the SD-231/SD-232 dual diodes to be operated without the snubber networks previously required to protect Schottkys from avalanching.

In 100s, the SD-231 diode costs \$8.81 and the SD-232 diode costs \$7.95. Delivery is six to eight weeks. For further information, including data sheets, contact John Power, TRW Power Semiconductors, 14520 Aviation Boulevard, Lawndale, California 90260.

## micro-miniature sub-audible tone encoder

Trans Com, Inc., introduces the new micro-miniature 401 sub-audible tone encoder. Measuring only  $1.0 \times 0.6 \times 0.3$  inch, the encoder can be installed in radios where other similar types of encoders cannot. The 401 has an operating range of 7 to 20 volts with a current consumption of only 4 mA. It is fully tunable from 67 Hz to 251 Hz and has an excellent temperature stability over a broad temperature range. Its features include compatibility with PL, CG and other CTCSS tone systems; small size; operating voltage 7-16 Vdc reverse polarity protected; operating current 4 mA, 12 Vdc; adjustable tone level 0 to 2 VPP; and low tone distortion, less than 1 percent THD. The tone stability is  $\pm 0.2$  percent Hz from  $-20^{\circ}\text{C}$  to  $+70^{\circ}\text{C}$ , and there is a two-year warranty. Contact Trans Com, Inc., 1104A Ridge Avenue, Lombard, Illinois 60148.

## 1981 Radio Shack catalog

Radio Shack's new 176-page 1981 catalog is now available, free on request, from more than 6,000 participating stores and dealers nationwide. The catalog has 120 full-color pages and features the latest in everything electronic from computers and stereo components to toys and electronic games, parts, and accessories for home entertainment hobbyists and experimenters.

Among the products being offered for the first time are the TRS-80 Pocket Computer; the TRS-80 Color Computer; the TRS-80 Model III Desk-Top Computer; six new stereo receivers, two with digital quartz tuning; and five stereo cassette tape decks featuring Dolby noise-reduction circuits.

The new catalog includes the TRS-80 line of microcomputers, Realistic stereo components, CB equipment, radios, tape recorders, thirteen new electronic calculators, six digital clocks, seventeen electronic games, Archer antennas, Micronta test instruments, and ArcherKit and Science Fair hobby kits.


For further information contact Tandy Corporation/Radio Shack, 1800 One Tandy Center, Fort Worth, Texas 76102.

## medium power Darlington's by Motorola

Motorola has announced a new series of complementary TO-92 Darlington transistors, designed specifically for preamplifier applications requiring a high dc current gain and an input impedance of several megohms. The low-cost, plastic-packaged transistors are available with breakdown voltage ratings of 40, 50, and 60 volts, a dc current gain of 10,000, and excellent current-gain linearity from 1 mA to 100 mA. Contact Motorola Semiconductor Products, Inc., P.O. Box 20912, Phoenix, Arizona 85036.
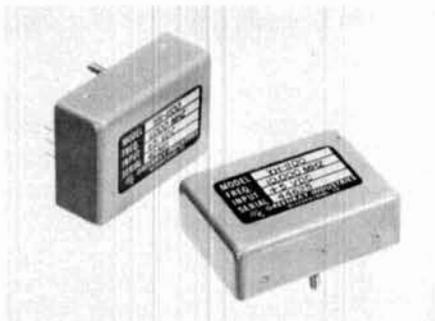
## miniature frequency standard

The model YH-1100 miniature frequency standard provides specified output frequency in the range of 1 MHz - 60 MHz. Although measuring only 4.5 cubic inches (73.7 cc), the unit can provide a frequency stability of  $\pm 5 \times 10^{-8}$  per day. With an output that will drive up to 10 TTL loads, and operating from a single 5 Vdc input, it is ideal for digital applications where size and stability are critical.



The price is \$175.00 for 100-unit quantities, with some common frequencies from stock.

For further information, write Greenray Industries, Inc., 840 West Church Road, Mechanicsburg, Pennsylvania 17055.

## H.H. Smith catalog

Herman H. Smith, Inc., of Brooklyn, New York, is making available its newly published Catalog 810 for design engineers and purchasing agents. The recently produced, 100-page, full-line catalog features a number of new products, including the recently developed "safety engineered" test lead package, which permits the user to assemble complete test lead systems from standard shelf items to retrofit with existing and new equipment. These include prods, meter inputs, input adapters, and cables with connectors. Other new items offered in Smith's Catalog 810 are an extended group of printed circuit board supports, flat wire cable clamps, and many new spacer types, including 3/16-inch O.D., 1/4-inch

## Code reading makes ham radio more fun!



## Field Day 2

A code reader can add to the fun of ham radio by allowing you to copy many signals that are too complex or too fast to decode by ear.

You can get in on such things as news-wire service transmissions, weather information and financial reports that are sent by radioteletype (RTTY), ASCII computer language or Morse code.

Some code readers only copy one or two types of signals, but the **Kantronics Field Day 2™** allows you to copy RTTY at 60, 67, 75 and 100 WPM Baud, ASCII at 110 and 300 (if sent as it is typed) WPM Baud and Morse at 3 to 80 WPM.

The **Field Day 2** even has an editing program to improve sloppy Morse. You get more of the message and fewer illegal character signs than with other code readers. With a **Field Day 2** you also get a 24-hour clock, code speed display and TTL compatible demodulator output.

The **Field Day 2** is a complete unit in one package with a large, easy-to-read, 10-character display and is backed with a full-year limited warranty.

Code reading makes ham radio more fun, and now you can get started with one compact, versatile unit, at \$449.95, suggested price, the **Field Day 2**.

**Call or visit** your Authorized Kantronics Dealer for a demonstration!

 **Kantronics**


(913) 842-7745  
1202 E. 23rd Street  
Lawrence, Kansas 66044

# WHY PAY
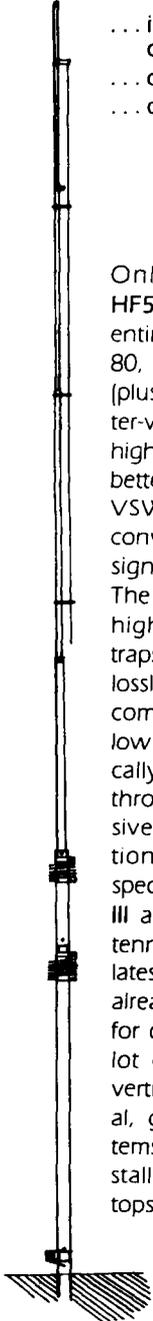
## FULL PRICE FOR AN 80-10 METER VERTICAL

... if you can use only 1/3  
of it on 107  
... or only 1/2 of it on 207  
... or only 3/4 of it on 407

Only Butternut's new HF5V-III lets you use the entire 26-foot radiator on 80, 40, 20 and 10 meters (plus a full unloaded quarter-wavelength on 15) for higher radiation resistance, better efficiency and greater VSWR bandwidth than conventional multi-trap designs of comparable size. The HF5V-III uses only two high-Q L-C circuits (not traps!) and one practically lossless linear decoupler for completely automatic and low VSWR resonance (typically below 1.5:1) on 80 through 10 meters, inclusive. For further information, including complete specifications on the HF5V-III and other Butternut antenna products, ask for our latest free catalog. If you've already "gone vertical," ask for one anyway. There's a lot of information about vertical antennas in general, ground and radial systems, plus helpful tips on installing verticals on rooftops, on mobile homes, etc.



**BUTTERNUT  
ELECTRONICS  
CO.**

P.O. Box #1411  
San Marcos, Texas 78666  
Phone: (512) 396-4111

O.D. and 3/8-inch O.D. in aluminum, brass, and nylon, as well as in male/female configurations.

Herman H. Smith, Inc., produces more than 20,000 electronics components and hardware at its main plant and maintains conveniently located regional warehouses which supply major industrial electronic distributors and OEM users in the U.S. and Canada. Contact H.H. Smith, Inc., 812 Snediker Avenue, Brooklyn, New York 11207.

## soldering iron stand

Wahl Clipper Corporation, manufacturers of the complete line of ISO-TIP brand soldering irons, has introduced a new "double-duty" soldering iron stand. The new stand is a combination soldering iron stand and caddy. When closed, the stand contains the soldering iron shaft and tip within the closed metal compartment, thus allowing an iron that has not yet completely cooled down to be placed in a tool box or caddy without damage to adjacent components. The compact, durable, yet lightweight soldering iron stand/caddy also protects the shaft and tip from possible damage in transit.

In the "open" position, the stand functions as a standard soldering iron stand, holding the iron within easy reach between uses. The stand also features a tip wiping sponge and well. For further information, contact Clipper Corporation, Sterling, Illinois 61081.

## COAX-SEAL for protecting connectors

Keep the name COAX-SEAL in mind the next time you need a means to keep moisture and corrosion out of your coax fittings. It's not too often a new product line crosses our desk that has caused as much excitement as this one. One wonders why COAX-SEAL hasn't appeared sooner. It has been used commercially for eight years and is just now finding its way into the Amateur market.

COAX-SEAL is a pliable, plastic material that can be wound over coax fit-

tings of any size or shape then hand-molded to give a long-lasting, flexible waterproof and dustproof seal. This new material stays flexible at temperatures from -25 to 350 F (-32 to 176.8 C).

COAX-SEAL maintains its sealing qualities regardless of movement of the coax. It also adheres to polyvinyl or vinyl outer coax jackets. The material allows quick decoupling of a coax fitting and also re-sealing of the fitting using the same material. Application is by hand — simply roll off approximately 6 inches (15 cm) of COAX-SEAL, remove backing paper, wrap starting at outer covering and work toward fitting, allowing a one-half overlap as you go. After the wrap is completed, gently knead to form a smooth surface and to force out any air.

COAX-SEAL comes in rolls, 60 inches (152 cm) long, 1/8 inch (3 mm) thick and 1/2 inch (13 mm) wide on backing paper. For more information, contact Universal Electronics, Inc., 1280 Aida Drive, Reynoldsburg, Ohio 43068.

## dummy load

The new Ten-Tec Model 209 air-cooled rf dummy load is an excellent accessory for the ham shack or test bench. It allows transmitter operation for testing or alignment without disturbance to other Amateurs on the air.

Model 209 is rated at 300 watts for 30 seconds with derating curve for extended use. VSWR is 1.1:1 maximum from 0-30 MHz, 1.5:1 maximum for 30-150 MHz. The dummy load is housed in a perforated aluminum enclosure, dark painted for excellent heat dissipation. SO-239 connector is built-in for convenient installation. Price is \$26.00. Contact Ten-Tec, Highway 411, East Sevierville, Tennessee 37862.

## 1021 DTMF receiver

The 1021 DTMF receiver is designed to detect and decode the six-

teen standard tones used for Touch Tone dialing. By incorporating the latest in technology it is possible to have a high-quality DTMF receiver measuring only  $3.5 \times 1.9 \times 0.4$  inch. The 1021 features low current consumption, typically 4 mA at 5 Vdc. The 1021 DTMF receiver consists of dual bandpass filters, dial tone rejector filter and limiters, a DTMF decoder with latched binary outputs, and a four to sixteen line converter. The input signal can vary from a level -30 dBm to 0 dBm with a digit detection time as short as 20 milliseconds. The four-bit binary and strobe outputs are provided through a five-pin header on the card; power and the sixteen discrete lines are available through a 25-pin connector with 0.1-inch spacing. When a digit is decoded, the strobe and digit line goes high for the duration of the tones detected. The binary outputs are normally set for 20 milliseconds, but can be lengthened. Both the filter and decoding circuits are crystal controlled for long term stability and accuracy. Contact Trans Com, Inc., 1104A Ridge Avenue, Lombard, Illinois 60148.

### nick-free wire stripper

O.K. Machine and Tool introduces a new, all-purpose, manual wire stripper, the ST-300. It has a convenient adjustable stop for consistency in wire strip lengths. This easy-to-use tool strips 14 to 22 AWG solid and stranded wire cleanly and quickly. It strips Kynar, vinyl, polyethylene, rubber, neoprene, and irradiated vinyls — almost all insulation materials in use today. With one light squeeze of the handles, cutting blades cut through and remove up to  $\frac{3}{4}$  inch of insulation. Heavy duty and reliable, the tool is ideal for appliance, automotive, electrical fixture, instrumentation and household wiring. The ST-300 won't damage or nick wire. Available from stock for \$9.95 from your local electronics distributor or directly from O.K. Machine and Tool Corporation, 3455 Conner Street, Bronx, New York 10475.

## short circuit

### optional sidetone

Those who are confused as to how to incorporate the optional sidetone into the CW keyboard program for the Apple II computer (October, 1980, *ham radio*) may find the following of interest. It is a program change for the addition of optional sidetone.

1. Enter monitor with CALL -151 or press RESET. (\* cursor).
2. Type 30A: AD 30 C0 88 D0 F5 AD 58 C0 60.
3. Press RETURN.
4. Re-enter BASIC (CTRL C).
5. In both lines 5 and 6, change the number 774 to 772.
6. Delete Line 620 (DEL 620).

To delete the sidetone, merely re-run the program. **Steps 1-4**, however, must be repeated each time the sidetone option is to be used unless the poke statements in lines 18 to 23 are changed, starting at :POKE 778,173, in line 18.

Although left as an exercise, here's a hint for converting hexadecimal numbers to decimal: For a three-digit hex number, multiply the first digit by 16<sup>2</sup>. Add (second digit  $\times$  16) plus third digit.

For a two-digit number, multiply the first by 16, add the second. Example: Convert \$3A7 to decimal. On the Apple keyboard, type: PRINT 3\*16/\ 2 + 10\*16 + 7. (= 935).


Modifications in **steps 5 and 6** are a permanent part of program, with or without sidetone.

contributed by  
Bill Skeen, W6WR

### updating the HW-2036

Those who would like a copy of the reverse side of the printed circuit boards in **fig. 9** (page 55) of WA4BZP's article in the November, 1980, issue of *ham radio* may obtain one by sending a stamped, self-addressed envelope to *ham radio*, Greenville, NH 03048.
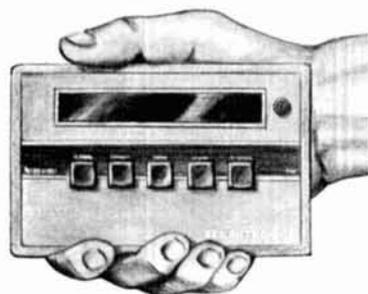
## Copy RTTY, ASCII and Morse from the palm of your hand.



**Have you waited** to get into code reading until you found out what this latest fad was about? You can stop waiting, because it's no longer a fad.

**Amateurs everywhere** are tossing the gigantic clanking monsters of yesteryear that once performed the job of reading radioteletype. They are trading them in for state-of-the-art code-reading devices that are incredibly small, noiseless if desired and infinitely more versatile than their antique predecessors.

**Kantronics, the leader** in code-reading development, has just introduced the latest and most-advanced breakthrough in the copying of Morse code, radioteletype and ASCII computer language.

The **Kantronics Mini-Reader** reads all three types of code, displays code speed, keeps a 24-hour clock, acts as a radioteletype demodulator and reads all of its decoded information out on a traveling display of 10 easy-to-read characters. It is so compact that it fits in a hand-held, calculator-size enclosure.

At \$314.95, the **Mini-Reader** outperforms anything within another \$400 of its price range.

**Call or visit** your Authorized Kantronics Dealer now to find out what the latest in technology has done to code-reading.

**Kantronics**

(913) 842-7745  
1202 E. 23rd Street  
Lawrence, Kansas 66044

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

AEA _____ 677	Jensen _____ 293
AP Products _____ 896	Jones _____ 626
ARCsoft _____ 905	K & S _____ 903
Ace Comm. _____ 850	Kantronics * _____
Alaska Microwave _____ 826	Kenmore _____ 538
Alliance _____ 700	Kenwood * _____
Aluma _____ 589	L-Tronics * _____
Amateur Elect. _____ 659	Larsen _____ 078
Amidon _____ 005	Lunar _____ 577
Applied Inv. _____ 862	Lufel _____ 904
Associated Radio _____ 892	MFJ _____ 082
Atlantic Surplus * _____	MHz Elec. _____ 415
Barker _____ 015	Madison _____ 431
Barry * _____	Microcraft _____ 774
Bencher _____ 629	Microwave Filter _____ 637
Ben Franklin _____ 864	Mid-Com _____ 479
Bilal _____ 817	J. W. Miller _____ 745
Budwig _____ 233	Motorola _____
Butternut * _____	Semiconductor _____ 599
C. Comm _____ 688	N.P.S. _____ 866
Clipper Corp. _____ 508	NRI Schools * _____
Comm. Concepts _____ 797	OK Machine _____
Comm. Spec. _____ 330	Oak Hill Academy A.R.S. * _____
Curtis Electro _____ 034	P.C. Elec. _____ 766
Cushcraft * _____	Palomar Eng. _____
DCO _____ 324	Payne _____ 867
DX Bulletin * _____	Callbook _____ 100
DX Eng. _____ 222	Radio Kit _____ 801
Dayton Ham. * _____	Radio Shack _____
Debcro _____ 900	Radio World * _____
Dielectric _____ 899	Radio Warehouse * _____
Drake * _____	Ramsey _____ 442
EGE _____ 901	S-F A.R.S. _____ 640
ETCO _____ 856	Securitron _____ 461
E. T. O. * _____	Selecto _____ 895
Encomm _____ 888	Semiconductors _____
Erickson Comm. * _____	Surplus _____ 512
Fair Radio _____ 048	Shure _____ 771
Firestik Ant. _____ 906	Slep _____ 535
G & C Comm. _____ 754	H.H. Smith _____ 908
G.I.S.M.O. _____ 691	Spectronics * _____
GLB _____ 552	Spec. Int. _____ 108
Gem Quad _____ 295	Stewart Quads _____ 890
Greenray Ind. _____ 907	TRW _____ 473
Grove _____ 848	Telrex _____
Hal Comm. _____ 057	Ten-Tec * _____
Hal-Tronix _____ 254	Trans Com _____ 891
H. R. B. _____ 150	Trans Comm. _____ 562
H. R. Magazine * _____	UNR-Rohn _____ 410
Ham Shack _____ 879	Universal Comm. _____ 895
Hamtronics, N.Y. _____ 246	Universal Elect. _____ 653
Handi-Tek _____ 893	V-J Products _____ 855
Hatry _____ 889	V. J. Gordon _____ 737
Heath _____ 060	Vanguard Labs _____ 716
Henry _____ 062	Vocom _____ 857
Hildreth _____ 283	Webster _____
Icom * _____	Assoc. _____ 423
Int'l Crystal _____ 066	Western Elec. * _____
Jameco _____ 333	Yaesu _____ 127
Jan _____ 067	

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

**March, 1981**

Please use before April 30, 1981

Tear off and mail to  
HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....

## DON & MIKE'S ST. PAT'S "NO BLARNEY" SPECIALS

Cubic - Swan 103 .....	\$1195.00
Astro 150A. ....	779.00
Mirage B23 1 watt-30 watt amp .....	89.95
DSI 5600A w/Ant/Ac. ....	185.00
Robot 800 .....	749.00
Cushcraft A3 Tribander ...	169.00
AEA Morsematic .....	169.00
Bird 43, Slugs .....	Call
CDE Ham-4 Rotor .....	199.00
Ham-X .....	269.00
BT-1 HF/VHF Rotator. ....	79.95
FDK Palm 2 Handie with BP/AC .....	149.00
Cetron, GE 572B. ....	38.00
Kenwood Service Manuals Stock .....	10.00 ea.
Telrex TB5EM .....	425.00
Telrex Monobanders .....	Call
Santec HT-1200 Synthesized .....	339.00

**Order Your  
KWM380 Now!  
Old Pricing & Free Goods!**

### Rockwell Accessories in Stock

Adel Nibbling Tool .....	8.95
Janel QSA5 .....	41.95
Rohn Tower .....	20% off dealer
25G, 45G Sections	
Belden 9405 Heavy Duty Rotor Cable 2#16, 6#18 ...	38¢/ft
Belden 8214 RG-8 Foam ...	32¢/ft
Belden 9258 RG-8 Mini-coax.	19¢/ft
Alliance HD73 Rotor .....	109.95
Amphenol Silverplate PL259 .....	1.00
ICOM 255A 2M Synthesized	339.00
w/touch-tone mike (limited qty.)	
ICOM 260A 2M SSB/FM/CW	449.00

**Lat Specials:**  
Kenwood TS-520SE, TS-130S . Call  
ICOM IC2AT/TTP/NICAD .. 249.00  
Bearcat 220—\$299.00 300—399.00  
Lunar 2M4-40P .....

Call for TS830S, TS130S  
plus accessories

### MASTER CHARGE • VISA

All prices fob Houston except where indicated. Prices subject to change without notice, all items guaranteed. Some items subject prior sale. Send letterhead for Dealer price list. Texas residents add 6% tax. Please add postage estimate \$1.00 minimum.

# MADISON

Electronics Supply, Inc.

1508 McKinney  
Houston, Texas 77010  
713/658-0268

# Advertisers iNdex

AEA, Advanced Electronics Applications .....	27
AP Products Incorporated .....	116
Ace Communications, Inc. ....	111
Alaska Microwave Labs .....	105
Alliance Mfg. ....	111
Aluma Tower Company .....	94, 116
Amateur Electronic Supply .....	91
Amidon Associates. ....	92
Applied Invention .....	95
Associated Radio .....	80
Atlantic Surplus Sales .....	104
Barker & Williamson, Inc. ....	62
Barry Electronics .....	42
Bencher, Inc. ....	86, 92
Ben Franklin Electronics .....	86
Bilal Company .....	76
Budwig Mfg. Company .....	62
Butternut Electronics .....	108
C. Comm. ....	87
Communication Concepts .....	76
Communications Specialists .....	112, 113
Curtis Electro Devices .....	80, 89
Cushcraft .....	6
DCO, Inc. ....	56
DX Bulletin .....	95
DX Engineering .....	80
Dayton Hamvention .....	10, 100
Debcro .....	116
Dielectric .....	62
Drake, R. L., Co. ....	55
EGE .....	95
ETCO .....	94
Ehrhorn Technological Operations .....	2
Encomm, Inc. ....	115
Erickson Communications .....	103
Fair Radio Sales .....	86
G & C Communications .....	72
G.I.S.M.O. ....	104
GLB Electronics .....	90
Gem Quad .....	94
Grove Enterprises .....	88
Hal Communications Corp. ....	11
Hal-Tronix .....	75
Ham Radio's Bookstore .....	62, 72, 88
Ham Radio Magazine .....	116
The Ham Shack .....	100
Hamtronics, N.Y. ....	51
Handi-Tek .....	90
Hatry Electronics .....	94
Heath Company .....	1
Henry Radio Stores .....	Cover II
Hildreth Engineers .....	62
Icom America, Inc. ....	5
International Crystal .....	61
Jameco Electronics .....	100
Jan Crystals .....	95
Jensen Tools .....	94
Jones, Marlin P. & Associates .....	89
K & S Enterprises .....	86
Kantronics .....	107, 109
Kenmore Corp. ....	95
Trio-Kenwood Communications, Inc. ....	Cover IV
L-Tronics .....	100
Larsen Electronics .....	105
Lunar Electronics .....	76
Lufel. ....	80
MFJ Enterprises .....	9
MHz Electronics .....	96, 97, 98, 99
Madison Electronics Supply .....	93, 110
Microcraft Corporation .....	86
Microwave Filter, Inc. ....	72
Midcom Electronics Inc. ....	88
J. W. Miller Division, Bell Industries .....	43
N.P.S. Inc. ....	90
NRI Schools .....	57
Oak Hill Academy Amateur Radio Session .....	94
P.C. Electronics .....	111
Palomar Engineers .....	57, 61
Payne Radio .....	114
Radio Amateur Callbook .....	90
Radio Kit .....	86
Radio World .....	62, 116
Radio Warehouse .....	62
Ramsey Electronics, Inc. ....	73
S-F Amateur Radio Services .....	76
Securitron .....	93
Selecto, Inc. ....	104
Semiconductors Surplus .....	81, 82, 83
Shure Brothers .....	50
Slep Electronics .....	91
Spectronics .....	77
Spectrum International .....	59
Stewart Quads .....	104
Telrex Laboratories .....	93
Ten-Tec, Inc. ....	58, 59
Trans Comm. ....	87
UNR-Rohn .....	87
Universal Communications .....	94
V-J Products .....	104
Van Gorden Engineering .....	95
Vanguard Labs .....	91
Vocom .....	56
Webster Associates .....	76
Western Electronics .....	92
Yaesu Electronics Corp. ....	Cover III

## FAST SCAN ATV

### WHY GET ON FAST SCAN ATV?


- You can send broadcast quality video of home movies, video tapes, computer games, etc. at a cost that is less than sloscan.
- Really improves public service communications for parades, RACES, CAP searches, weather watch, etc.
- DX is about the same as 2 meter simplex — 15 to 100 miles.

### ALL IN ONE BOX



**TC-1 Transmitter/Converter** . . . .  
Plug in camera, ant., mic, and TV and you are on the air. Contains AC supply, T/R sw, 4 Modules below . . . . . \$ 399 ppd

### PUT YOUR OWN SYSTEM TOGETHER

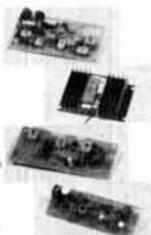

**TXA5 ATV Exciter** contains video modulator and xtal on 434 or 439.25 MHz. All modules wired and tested . . . . . \$ 89 ppd

**PA5 10 Watt Linear** matches exciter for good color and sound. This and all modules run on 13.8 vdc. . . . . \$ 79 ppd

**TVC-2 Downconverter** tunes 420 to 450 MHz. Outputs TV ch 2 or 3. Contains low noise MRF901 preamp. . . . . \$ 55 ppd

**PACKAGE SPECIAL** all four modules \$ 239 ppd

**FMA5 Audio Subcarrier** adds standard TV sound to the picture . . . . . \$ 29 ppd

### SEND SELF-ADDRESSED STAMPED ENVELOPE FOR OUR LATEST CATALOG INCLUDING:

Info on how to best get on ATV, modules for the builder, complete units, b&w and color cameras, antennas, monitors, etc. and more. 20 years experience in ATV.

Credit card orders call (213) 447-4565. Check, Money Order or Credit Card by mail.



Maryann  
WB6YSS

### P.C. ELECTRONICS

2522 PAXSON  
ARCADIA, CA 91006

Tom  
W6ORG



Factory  
Direct Only!

## THE WORLD'S FIRST 1800 CHANNEL FULLY SYNTHESIZED COMPACT VHF FM MONITOR

**AR-22**  
FACTORY DIRECT  
PRICE \$125.00

This price in U.S. only

- FULL BAND COVERAGE  
141,000-149,995 MHz  
5 KHZ Steps by digital switches.
- SLIM SIZE AND LIGHT-WEIGHT.  
5¼"(H) x 2½" (W) x 1"(D)  
7.1 oz with NiCd Battery Pack



- COMMERCIAL BAND TYPE (151-159 MHz) IS ALSO AVAILABLE.
- CREDIT CARDS/MONEY ORDER OR ANY COMMERCIAL GUARANTEED CHECK...U.P.S. COD

ACE COMMUNICATIONS, INC.

2832-D Walnut Avenue, Tustin, California 92680

Phone (714)544-8281

# The HD-73 Rotator by Alliance

## A precision instrument built to last.

The HD-73 combines Dual-Speed rotation and a single 5-position switch with the clear visibility of a backlit D'Arsonval meter. So you get precise control for fast and fine tuning.

And the advanced technology of HD-73 is backed by quality construction. Heavy duty aluminum casings and hardened steel drive gears. Lifetime factory lubrication that

withstands -20°F. to 120°F. temperatures.

The superior design of the HD-73 mast support bracket, with optional no-slip positive drive, assures perfect in-tower centering with no special tools.

Automatic braking minimizes inertia stress.

Easy to install, a pleasure to use.

The HD-73 is on your wavelength. Write for performance details today.



### I want to tune in on HD-73.

- Send complete details
- Give me the name of my nearest dealer.


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



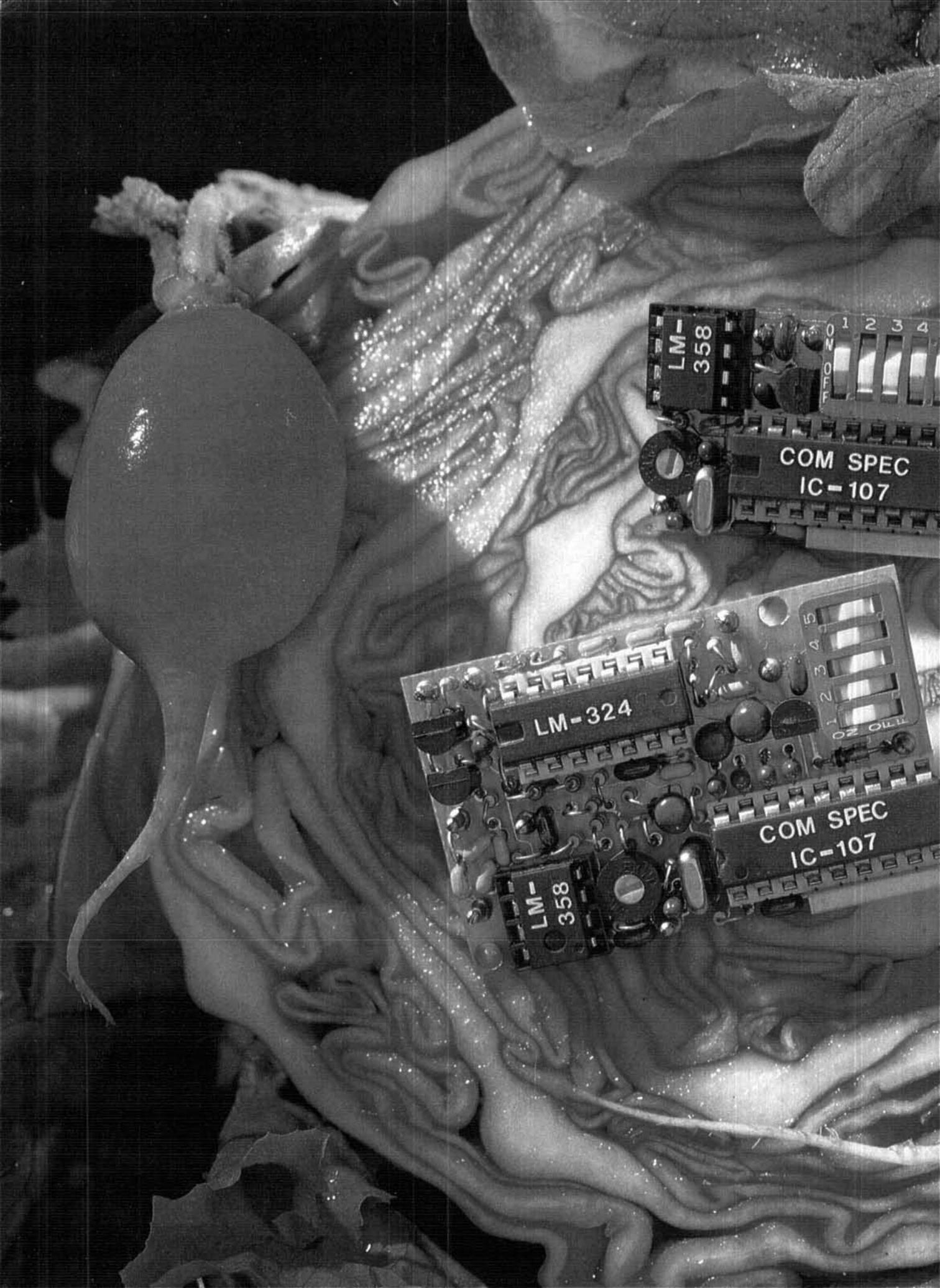The Alliance Manufacturing Company, Inc.,  
Alliance, Ohio 44601




LM-358  
COM SPEC  
IC-107

LM-324  
COM SPEC  
IC-107
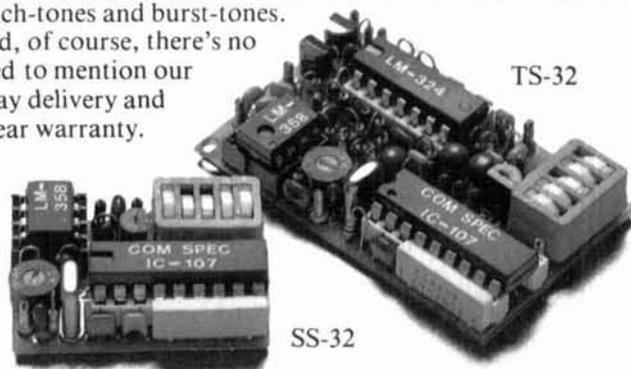
# A fresh idea!

Our new crop of tone equipment is the freshest thing growing in the encoder/decoder field today. All tones are instantly programmable by setting a dip switch; no counter is required. Frequency accuracy is an astonishing  $\pm .1$  Hz over all temperature extremes. Multiple tone frequency operation is a snap since the dip switch may be removed. Our SS-32 encode only model is programmed for all 32 CTCSS tones or all test tones, touch-tones and burst-tones.

And, of course, there's no need to mention our 1 day delivery and 1 year warranty.



## TS-32 Encoder-Decoder

- Size: 1.25" x 2.0" x .40"
- High-pass tone filter included that may be muted
- Meets all new RS-220-A specifications
- Available in all 32 EIA standard CTCSS tones

## SS-32 Encoder

- Size: .9" x 1.3" x .40"
- Available with either Group A or Group B tones

## Frequencies Available:

Group A			
67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 M1

- Frequency accuracy,  $\pm .1$  Hz maximum - 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- Continuous tone

Group B						
TEST-TONES:	TOUCH-TONES:	BURST-TONES:				
600	697 1209	1600	1850	2150	2400	
1000	770 1336	1650	1900	2200	2450	
1500	852 1477	1700	1950	2250	2500	
2175	941 1633	1750	2000	2300	2550	
2805		1800	2100	2350		

- Frequency accuracy,  $\pm 1$  Hz maximum - 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor


Wired and tested: TS-32 \$59.95, SS-32 \$29.95

 **COMMUNICATIONS SPECIALISTS**

426 West Taft Avenue, Orange, California 92667  
(800) 854-0547 / California: (714) 998-3021



# If You Want The Finest

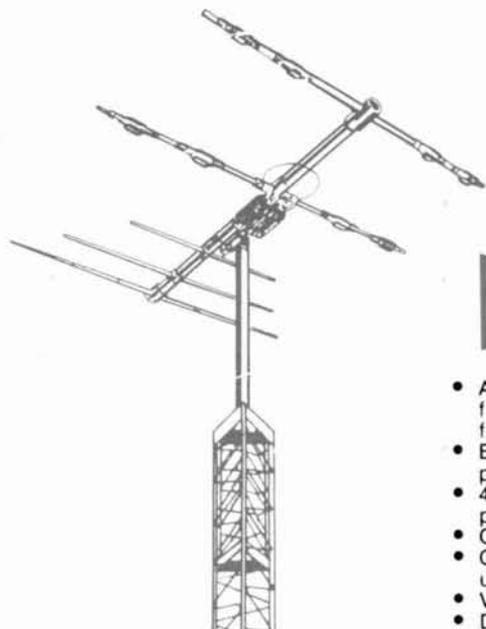

## ETD ALPHA 77DX Amplifier

- Alpha 77DX: The ultimate amplifier for those who demand the finest.
- Eimac 8877 Tube — 1500 watts of plate dissipation.
- 4.4 KVA Hypersil<sup>®</sup>, removable, plug-in Transformer.
- Oil-filled, 25 mfd Filter Capacitor.
- QSK CW: Full break-in, (2) vacuum relays.
- Vacuum Tuning Capacitor.
- Ducted air cooling, large, quiet blower, computer grade.
- Warranty (limited) 24 months, tube by Eimac.
- Other ALPHA's: 78, 76CA, 76PA, 76A, 374A, 77SX (Export Only).



## telrex

LABORATORIES  
"MONARCH" 10, 15, 20  
Meter "Tri-Band"  
Model TB5EM/4KWP



## signal/one CX-11-A Integrated Station

- POWER OUTPUT: 150 watts CW/SSB output all bands (2) MRF 422 Finals.
- OPTIONAL POWER OUTPUT: 200 to 225 Watts CW/SSB output
- SYNTHESIZED FREQUENCY COVERAGE: All amateur bands 1.8-30 MHz in full 1 MHz bands, plus 4 additional 1 MHz bands for future expansion.
- TWO PTO'S: Dual receiving, transceive on either, or split operation.
- QSK CW; Full break-in, vacuum relays. 300 Hz CW Filter built-in.
- SELECTIVITY: Two 8 pole plus one 4 pole filter deliver 20 pole 1.4:1 shape factor (6dB/60dB), plus post detection 1.5, 1.0, .4 and .1 kHz bandwidth.
- BUILT-IN A/C supply, 115/230V, 50/400 Hz, Hypersil<sup>®</sup> transformer. IF shift, noise blanker, RF clipping, CW keyer, notch/peak filter.
- SERVICING: Self service easiest of any transceiver by using gold-plated sockets for transistor and IC replacement.
- RELIABILITY: Less than 1% failure. 99% of problems resolved in field.
- QUALITY: All military and computer grade. 100% American made.
- PRICE \$5900, mfg. by Signal/one Corp., Phoenix, AZ 85021.

Phone Don Payne, K4ID, for Special Prices, Brochure, and OPERATING EXPERIENCE on the CX-11A and Alphas.

## PAYNE RADIO

Personal Phone — (615) 384-2224  
P. O. Box 100, Springfield, Tenn. 37172

# The Warranty and Beyond

or How You Get the Back-Up That Doesn't Back Down In 91 Days.



## ENCOMM, INC. LIMITED WARRANTY

Encomm, Inc. warrants this product against defects in material and workmanship for a period of 90 days from the date of purchase by the original purchaser. Encomm, Inc. will at its option repair or replace any and all defective parts, assemblies or entire units as it deems proper, free of charge for both the parts and the labor necessary to correct any defects in material or workmanship for the 90 day period.

The purchaser is responsible for the transportation costs of returning the equipment to and from Encomm, Inc. or its designated repair center for purposes of obtaining the warranty service described in this form.

### EXTENDED SERVICE PERIOD

FOR A PERIOD OF TWO (2) YEARS FROM DATE OF PURCHASE THE ORIGINAL PURCHASER MAY OBTAIN EXTENDED SERVICE ON ALL THE SEMICONDUCTOR COMPONENTS USED IN THIS UNIT NOT INCLUDING FINAL TRANSISTORS. FAILURES CAUSED BY IMPROPER INSTALLATION, STATIC DISCHARGE, ABUSE, OR UNAUTHORIZED ALIGNMENT ARE NOT INCLUDED. MAXIMUM CHARGE FOR THIS SERVICE WILL BE ONE HOUR AT THE THEN CURRENT ENCOMM, INC. SHOP RATE.

The above warranty does not include incidental or consequential damages and Encomm, Inc. disclaims any liability for any such damages. All implied warranties, if any, are limited in duration to the above-stated 90 day warranty period. Some states do not allow the exclusion of limitation on incidental or consequential damages or on how long an implied warranty lasts, so the above limitations may not apply to you.

The completion and return of the enclosed registration form is a condition precedent to the warranty coverage and the above undertaking to repair. This warranty gives you specific legal rights and you may also have other rights which may vary from state to state.

Encomm, Inc.  
2000 Avenue G  
Suite 800  
Plano, TX 75074

Please send me more information about the Santelec HT-1200 and a list of Authorized Santelec Dealers.

NAME

CALL

ADDRESS

CITY

STATE ZIP

YOU MAY SEND A DUPLICATE OF THIS FORM.

The Santelec HT-1200 is approved under FCC Part 15 and exceeds FCC regulations limiting spurious emissions.

# Radio World

CENTRAL NEW YORK'S MOST COMPLETE HAM DEALER




Featuring Kenwood, Yaesu, Icom, Drake, Ten-Tec, Swan, Dentron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Bird, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure. We service everything we sell!

Write or call for quote. **You Won't Be Disappointed.**  
We are just a few minutes off the NYS Thruway (I-90) Exit 32

OUT OF STATE CALL TOLL FREE **800-448-9338**  
ONEIDA COUNTY AIRPORT TERMINAL BUILDING  
ORISKANY, NEW YORK 13424  
N.Y. Res. Call (315) 337-0203  
Warren - K21XN  
Bob - WA2MSH
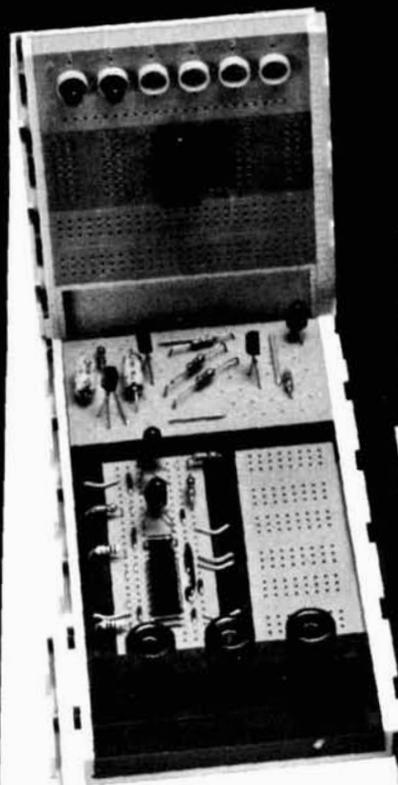
## HOBBY-BLOX™

The modular, circuit building system for electronic hobbyists.



**Be careful. Your hobby is about to become an obsession.**

The 14 modular units in the solderless, Hobby-Blox™ system are color-coded and cross-indexed. Projects go faster, easier.

For the beginner, there are two starter packs. One for integrated circuits, one for discrete components. Each has its own 10 project booklet.

Once you get into Hobby-Blox, look out. You're going to get hooked.

For a free catalog and the name of your nearest Hobby-Blox dealer, call Toll Free **800 321-9668**. In Ohio call collect **(216) 354-2101**.

Patents Pending  
©AP PRODUCTS INCORPORATED 1980



AP PRODUCTS INCORPORATED  
9450 Pinenneedle Drive  
P.O. Box 503  
Mentor, Ohio 44060  
(216) 354-2101  
TWX: 810-425-2250

In Europe, contact A.P. PRODUCTS GmbH  
Baumlesweg 21 • D-7031 Weil 1 • W. Germany

**Free Project-of-the-Month to Hobby-Blox purchasers!**

## DE DEBCO ELECTRONICS

### RAPID MOBILE CHARGER




The DEB-TED Rapid Mobile Charger is a constant voltage charger that will charge your batteries off a 12 Volt source in 4-6 hours. You may use the charger at all times, this includes transmit and receive periods. It is equipped with a cigarette lighter plug on the input side and the appropriate charging plug on the output side. Models available now for the Kenwood TR2400, Yaesu 207R, Tempo S1, S2, S5, the Wilson Mark II and IV, and the Santec HT-1200. Other models available also please call or write for info ..... \$34.95

**COMING SOON  
THE NEW AC VERSION**
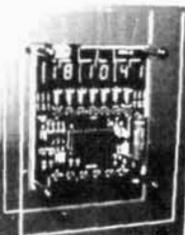
### "SEE THE WORKS" CLOCK

OUR EASIEST CLOCK TO ASSEMBLE!

6 Digits 12 or 24 Hour Format Clock rests between two pieces of clear plexiglas A GREAT CONVERSATION PIECE! Kit is complete including top quality PC board, all components, pre-cut and drilled plexiglas and all hardware ..... \$29.95  
Wired and Tested ..... \$39.95



### VEHICLE INTRUSION ALARM

An easy to assemble and install kit that offers options not normally found in other alarm systems. Hidden switch mounts under the dash. Kit has provisions for sensors and remote control switch. Programmable time delays for exit, entry and alarm periods. Basic hook-up utilizes dome light circuit activating when doors are opened. The alarm will drive a siren or pulse horn at a 1HZ rate. Not prone to false alarm do to reliable CMOS circuitry. No external switch required! Complete kit with easy to follow instructions and diagrams ..... \$12.95  
Wired and Tested ..... \$19.95

P.O. BOX 9169  
CINCINNATI, OHIO 45209


Phone: (513) 531-4499

- Add 5% Shipping for U.S. & Canada
- All foreign orders add 10%
- COD orders add \$1.25
- Master Charge and Visa Welcome
- Orders under \$20.00 add \$1.00 handling
- Ohio residents add 4 1/2% Tax

Dealer Inquiries Invited

CALL OR WRITE FOR CATALOG

# DOUBLE YOUR PLEASURE

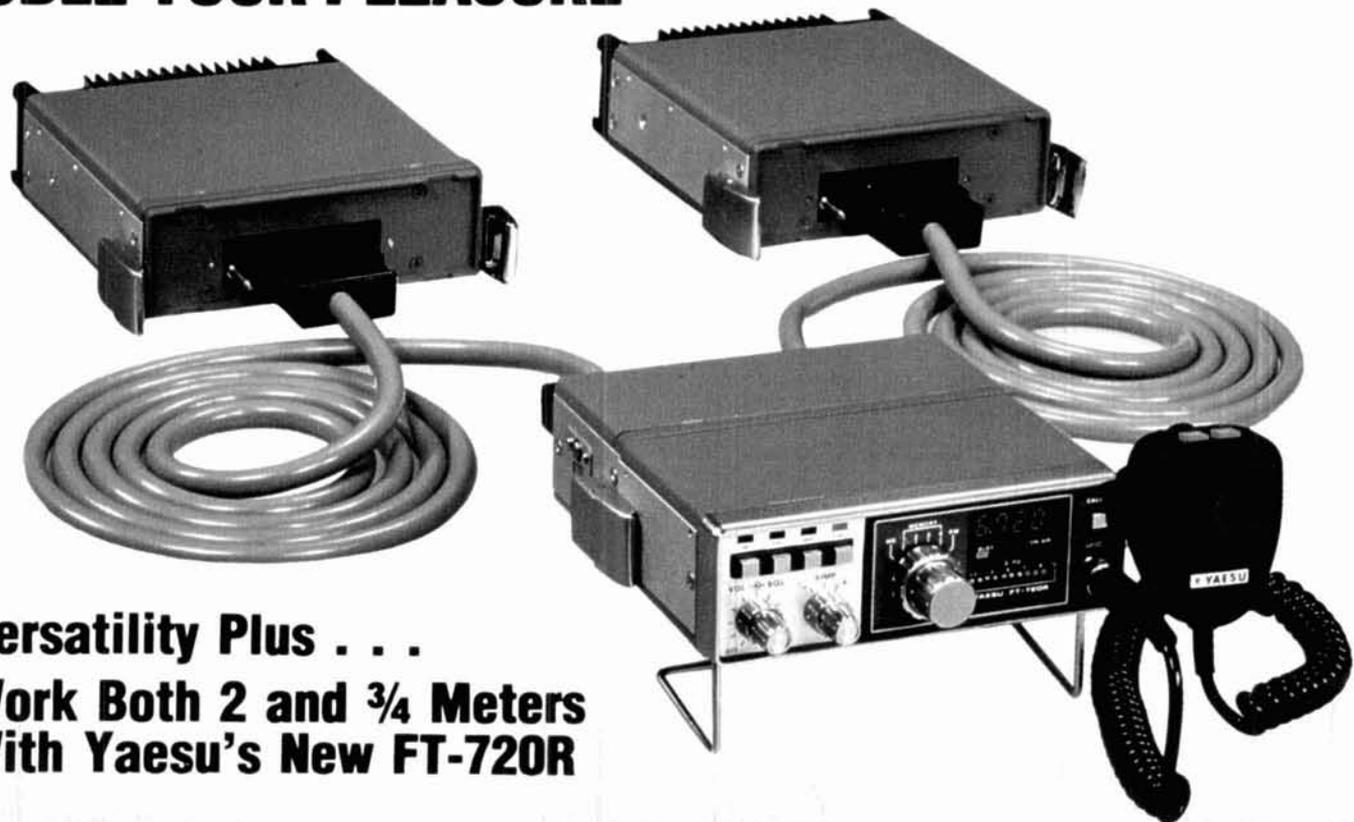

## Versatility Plus . . . Work Both 2 and 3/4 Meters With Yaesu's New FT-720R

The FT-720R series is a compact VHF/UHF mobile transceiver that harnesses the incredible power of the microprocessor to bring you top-operating flexibility. Start with the FT-720R Control Head, then add either the 10 watt FT-720RU 440 MHz or 25 watt FT-720RVH 2 meter RF Deck. You can clamp the Control and RF Deck together or use an optional remote cable to hide the RF Deck.

And for Top Performance while portable . . . Choose the new FT-404R 70cm Hand-held.



**FT-404R**  
Channel, 3 Watt  
JHF Hand-held



**FTT-1**  
16 Key  
DTMF Encoder



**FTS-32ED**  
CTCSS Encode/Decode  
32 Tone Selection



**LCC-4**  
Shorty Case



**LCC-2/LCC-3**  
Heavy Duty Case



**FTS-32E**  
CTCSS Encode Only  
32 Tone Selection

281

### Also available:

**NC-3A** Quick Charger  
**YM-24A** Speaker/Mic  
**PA-2** Mobile Adapter  
**MMB-10** Mobile Bracket

**YAESU**  
*The radio.*



**YAESU ELECTRONICS CORP., 6851 Waltham Way, Paramount, CA 90723 • (213) 633-4007**  
**YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246**

# Small wonder.

Processor, N/W switch, IF shift, DFC option



## TS-130S/V

An incredibly compact, full-featured, all solid-state HF SSB/CW transceiver for both mobile and fixed operation. It covers 3.5 to 29.7 MHz (including the three new Amateur bands!) and is loaded with optimum operating features such as digital display, IF shift, speech processor, narrow/wide filter selection (on both SSB and CW), and optional DFC-230 digital frequency

controller. The TS-130S runs high power and the TS-130V is a low-power version for QRP applications.

Ask your Authorized Kenwood Dealer about the compact, full-featured, all solid-state TS-130 Series.

**NOTE:** Price, specifications subject to change without notice and obligation.

 **KENWOOD**  
...pacesetter in amateur radio

**TRIO-KENWOOD COMMUNICATIONS INC.**  
1111 WEST WALNUT / COMPTON, CA 90220



### Optional DFC-230 Digital Frequency Controller

Allows frequency control in 20-Hz steps with UP/DOWN microphone (supplied with DFC-230). Includes four memories (handy for split-frequency operation) and digital display. Covers 100 kHz above and below each 500-kHz band. Very compact.