

# ham radio

magazine

- Morse time synthesis
- remote control hf operation
- microprocessor repeater controller
- a 6-meter amplifier

an  
inexpensive  
video  
monitor



**hr** 

focus  
on  
communications  
technology

# ICOM IC-25A/H

## More Features and Power Per Square Inch!

**NOW WITH  
EXTRA  
POWER!**

IN THE NEW  
25H MODEL



The smallest 2 meter FM mobile on the market is now even easier to read and use with a green LED readout and a compact touchtone®/scanning microphone and gives you the option of 25 or 45 watts.



**New Green LED.** Easier to read in bright sunlight, and not glaring at night, the IC-25A(H)'s new readout provides good visibility under all conditions.

**5 Memories.** Instant access to most used frequencies. VFO A information is transferred to the selected memory by pushing the write button.

**Priority Channel.** Any memory channel may be monitored for activity on a sample basis, every 5 seconds, without disruption of a QSO conducted on a VFO frequency.

**New HM14 Microphone.** Smaller and lighter... the HM14 microphone provides a 16 button touchtone® pad as well as up and down scan buttons adding easy frequency control of the radio and additional tones for repeater control.

**NOR/REV Capability.** Use of this button in the duplex mode allows one touch monitoring of the repeater input frequency. If simplex operation is possible you will know instantly.

**Scanning.** Pushing the S/S button initiates the scan circuitry. With the mode switch in a memory position the unit will scan all 5 memories plus the 2 VFO frequencies. With the mode switch in a VFO position, the unit will scan the entire band or the portion of the band defined by memories 1 and 2. Full band scan or program band scan is selected from the front panel and internally switched scanning choices of adjustable delay period after a carrier is received then resume scan, or resume on carrier drop, are standard.

**ENLARGED HEATSINK  
FOR 45 WATTS**




**The New 45 Watt IC-25H.** Only slightly longer than its companion IC-25A, the IC-25H packs a powerful 45 watt punch. This 45 watts of power eliminates the need for an external power amplifier in fringe areas and gives a savings of space and wiring.

The IC-25H has all of the standard features of the IC-25A that have made it the most popular 2 meter mobile ever, plus the new green LED readout, new HM14 microphone and extra power. These new features make the IC-25H the best 2 meter mobile value on the market.

 **ICOM**  
The World System


**THE LOOK  
SAYS  
QUALITY ...**

**THE PRICE  
SAYS  
BUY!**

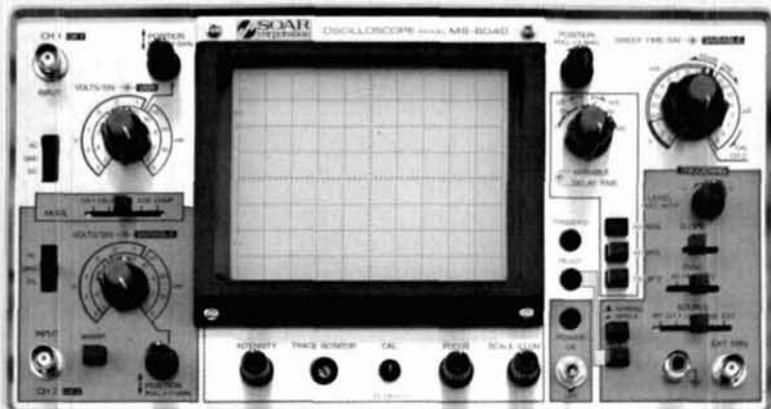

**Model MS-6040 40 MHz DUAL TRACE**

**\$850.00**

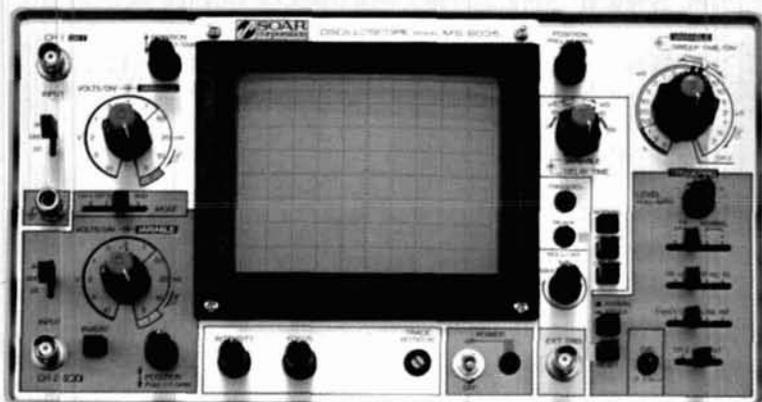

**Model MS-6035 35 MHz DUAL TRACE**

**\$799.00**

#### **PERFORMANCE:**

The MS-6040 vertical bandwidth is 40 MHz (typically  $\geq 50$  MHz and triggers to  $\sim 80$  MHz) with 1 mV sensitivity thru 10 MHz, 5 mV thru 40 MHz both channels, 20 sweep speeds from 0.5 sec. to 0.2  $\mu$ s plus X5 mag.; 15 kV beam acceleration which assures clear bright wave-forms even at low rates and/or fast sweep speeds.

The MS-6035 vertical bandwidth is 35 MHz with 1 mV sensitivity thru 5 MHz, 5 mV thru 35 MHz both channels; 21 sweep speeds from 0.5 sec. to 0.1  $\mu$ s plus X5 mag.; built-in HF and LF filters; trigger hold off as well as alternate trigger capability . . . and SOAR CORP. oscilloscopes typically exceed all our published specifications.

#### **FEATURES:**

Both scopes have 6" PDA rectangular CRT's with internal graticle and external trace rotator; auto trigger level for reference; trigger delay; single sweep; TV (video) sync separators; Z axis intensity modulation input; fully shielded switching regulator power supplies; glass epoxy PCB's laid out for super ease of calibration and maintenance; and they come complete with two 10:1 hook-on probes.

#### **QUALITY:**

**EVERY** SOAR CORP. oscilloscope is fully performance tested **TWICE**, once at the factory and once again prior to shipment from our warehouse. **YOUR DOUBLE GUARANTEE OF SATISFACTION.**

#### **BACK-UP:**

SOAR CORP. is a company with over 20 years of design and manufacturing experience in making and selling Oscilloscopes, Spectrum Analyzers, DMM's, Power Supplies, Frequency Counters, Digital Thermometers, Pulse Generators, AC Clamp Testers, VOM's, Electrical Energy Monitors, and Automatic P.C. Board Test Systems.

**ALL SOAR CORP. PRODUCTS ARE COVERED BY OUR "NO NON-SENSE" ONE YEAR PARTS AND LABOR WARRANTY — JUST IN CASE.**

#### **NORTH AMERICAN SOAR CORP.**

1126 CORNELL AVENUE  
CHERRY HILL, N.J. 08002  
(609) 488-1060

**FOR A "NO OBLIGATION TO BUY" DEMONSTRATION WRITE OR  
PHONE LYSBETH AT N.A. SOAR CORP.**

Soar products are available through selected  
DISTRIBUTORS in the U.S.A., Canada, and Mexico.  
**ORDER YOURS NOW.**

**NORTH  
AMERICAN**



# TR-2500

size, smaller price!

The TR-2500 is a compact 2 meter FM handheld transceiver with every conceivable operating feature.

#### TR-2500 FEATURES:

- Weighs 540 g. (1.2 lbs). 66 (2-5/8) W x 168 (6-5/8) H x 40 (1-5/8) D, mm (inches).
- LCD digital frequency readout.
- Ten memories includes "MO" for non-standard split repeaters.
- Lithium battery memory back-up, built-in, (est. 5 year life).
- Memory scan.
- Programmable automatic band scan, and upper/lower scan limits; 5-kHz steps or larger.
- Repeater reverse operation.
- 2.5 W or 300 mW RF output. (HI/LOW power switch).
- Built-in tunable (with variable resistor) sub-tone encoder.
- Built-in 16-key autopatch encoder.
- Slide-lock battery pack.
- Keyboard frequency selection.
- Covers 143.900 to 148.995 MHz.



#### CONVENIENT TOP CONTROLS



- Optional MS-1 mobile or ST-2 AC charger/supply for operation while charging.
- Battery status indicator.
- Complete with flexible antenna, 400 mAh Ni-Cd battery, and AC charger.

#### Optional accessories:

- ST-2 Base station power supply/charger (approx. 1 hr.)
- MS-1 13.8 VDC mobile stand/charger/power supply.
- VB-2530 2-M 25 W RF power amps., (TR-2500 only).
- TU-1 Programmable CTCSS encoder (TR-2500 only).
- TU-35B Programmable CTCSS encoder (mounts inside TR-3500 only).
- PB-25H Heavy-duty 490 mAh Ni-Cd battery pack.
- DC-25 13.8 VDC adapter.
- BT-1 Battery case for AA manganese/alkaline cells.
- SMC-25 Speaker microphone.
- LH-2 Deluxe leather case.



NEW

# TR-3500

## 70 CM FM Handheld

- Covers 440-449.995 MHz in 5-kHz steps.
- Hi-1.5 W, Low-300 mW.
- TX OFFSET switch,  $\pm 5$  kHz to  $\pm 9.995$  MHz programmable.
- Auto/manual squelch control.
- Tone switch for opt. TU-35B
- Other outstanding features similar to TR-2500.

- BH-2A Belt hook.
- RA-3 2 m 3/8  $\lambda$  telescoping antenna (for TR-2500).
- WS-1 Wrist strap.
- EP-1 Earphone.

# TR-7950/7930

Big LCD, Big 45 W, Big 21 memories, Compact.

Outstanding features providing maximum ease of operation include a large, easy-to-read LCD display, 21 multi-function memories, a choice of 45 watts (TR-7950) or 25 watts (TR-7930), and the use of microprocessor technology throughout.

#### TR-7950/TR-7930 FEATURES:

- New, large, easy-to-read LCD digital display. Easy to read in direct sunlight or dark (back-lighted). Displays TX/RX frequencies, memory channel, repeater offset, sub-tone number, scan, and memory scan lock-out.
- 21 new multi-function memory channels. Stores frequency,

repeater offset, and optional sub-tone channels. Memory pairs for non-standard splits. "A" and "B" set band scan limits. Lighted memory selector knob. Audible "beep" indicates channel 1 position.

- Lithium battery memory back-up. (Est. 5 yr. life.)
- 45 watts or 25 watts output. HI/LOW power switch for reduction to 5 watts.
- Automatic offset. Pre-programmed for simplex or  $\pm 600$  kHz offset, in accordance with the 2 meter band plan. "OS" key for manual change in offset.

- Programmable priority alert. May be programmed in any memory.
- Programmable memory scan lock-out. Skips selected memory channels during scan.
- Programmable band scan width.
- Center stop circuit for band scan, with indicator.
- Scan resume selectable. Selectable automatic time resume-scan, or carrier operated resume-scan.
- Scan start/stop from up/down microphone.

- Programmable three sub-tone channels with optional TU-79 unit (encoder).
- Built-in 16-key autopatch encoder with monitor (Audible tones).
- Front panel keyboard control.
- Covers 142.000-148.995 MHz in 5-kHz steps.
- Repeater reverse switch. (Locking)
- "Beeper" amplified through speaker.
- Compact lightweight design.

#### Optional accessories:

- TU-79 three frequency tone unit
- KPS-12 fixed-station power supply for TR-7950.
- KPS-7A fixed-station power supply for TR-7930.
- SP-40 compact mobile speaker



# KENWOOD

TRIO-KENWOOD COMMUNICATIONS  
1111 West Walnut, Compton, California 90220

NEW

# SAVE \$10.50\* with home delivery

**SAVE \$10.50\*** with home delivery

\* (One year newsstand cost \$30.00)

Payment enclosed

Bill me later

Here's my address label, enter my subscription.

1 Year . . . . . 12 issues . . . . . \$19.50

2 Years . . . . . 24 issues . . . . . \$32.50

3 Years . . . . . 36 issues . . . . . \$42.50

U. S. prices only

Name \_\_\_\_\_ Zip \_\_\_\_\_

Address \_\_\_\_\_ State \_\_\_\_\_

City \_\_\_\_\_

Check here if this is your renewal (attach label)

## Subscribe to **ham radio** magazine

Please allow 4-6 weeks for delivery of first issues.

**Foreign rates:** Europe, Japan and Africa, \$28.00 for one year by air forwarding service. All other countries \$21.50 for one year by surface mail.

Please  
enter my  
subscription




**BUSINESS REPLY CARD**  
First Class    Permit No. 1    Greenville, NH

Postage Will Be Paid By Addressee

**ham  
radio**  
Greenville, NH 03048

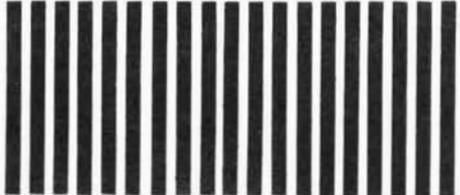NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES



# ham radio

magazine

APRIL 1983

volume 16, number 4

**T. H. Tenney, Jr., W1NLB**  
publisher

**Rich Rosen, K2RR**  
editor-in-chief  
and associate publisher

**Martin Hanft, KA1ZM**  
editor

**editorial staff**

Alfred Wilson, W6NIF  
Joseph J. Schroeder, W9JUV  
Leonard H. Anderson  
associate editors

Susan Shorrock  
editorial production

**publishing staff**

J. Craig Clark, Jr., N1ACH  
assistant publisher

Rally Dennis, KA1JWF  
director of advertising sales

Dorothy Sargent, KA1ZK  
advertising production

Susan Shorrock  
circulation manager

Therese Bourgault  
circulation

ham radio magazine  
is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048-0498  
Telephone: 603-878-1441

**subscription rates**

United States: one year, \$19.50  
two years, \$32.50, three years, \$42.50

Canada and other countries (via Surface Mail)  
one year, \$21.50; two years, \$40.00  
three years, \$57.00

Europe, Japan, Africa (via Air  
Forwarding Service) one year, \$28.00

All subscription orders payable in  
United States funds, please

**foreign subscription agents**

Foreign subscription agents are  
listed on page 111

Microfilm copies  
are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3075

Cassette tapes of selected articles  
from ham radio are available to the  
blind and physically handicapped  
from Recorded Periodicals  
919 Walnut Street, 8th Floor  
Philadelphia, Pennsylvania 19107

Copyright 1983 by  
Communications Technology, Inc  
Title registered at U. S. Patent Office

Second-class postage  
paid at Greenville, N. H. 03048-0498  
and at additional mailing offices  
ISSN 0148-5989

Postmaster send Form 3579 to ham radio  
Greenville, New Hampshire 03048-0498



## contents

**12 inexpensive video monitor**

Carl Gregory, K8CG

**16 Morse time synthesis**

Lawrence G. Souder, N3SE

**27 a state-of-the-art  
Touchtone® decoder**

Mark Forbes, KC9C

**32 remote control hf operation**

Dick Sander, K5QY

**52 ham radio techniques**

Bill Orr, W6SAI

**56 a microprocessor  
repeater controller**

Bill Warner, KB5F

**72 6-meter amplifier**

Fred J. Merry, W2GN

**129 advertisers index**

**8 comments**

**94 DX forecaster**

**111 flea market**

**106 ham mart**

**88 ham notes**

**98 new products**

**10 presstop**

**129 reader service**

**6 reflections**

**46 technical forum**

# REFLECTIONS

**On January 20, 1983**, the FCC proposed the most important Amateur rules change in many years — the proposal to delegate the responsibility for Amateur license examinations to the Amateur community. Unfortunately, the emotion-laden issue of a no-code license has all but obscured this other crucial Notice of Proposed Rule Making.

In consideration of the ARRL's Petition for Rule Making on exam administration, the FCC has proposed a three-man team headed by an Extra Class licensee to administer individual exams. Examiners would have to be certified by one of several recognized supervisory organizations called Volunteer Examiner Coordinators. They would have to be over 18 years old and could not work for a manufacturer or distributor of Amateur equipment or a publisher of training materials. Questions would be chosen from a list made up by the Commission from submissions by individual Amateurs and groups of Amateurs.

There are a lot of hard questions that must be asked about this proposed system. Three-man examining teams (for all licenses except Novice) are fine for major urban areas like Los Angeles, Chicago, or Washington, D.C., but what happens to the would-be upgrader in remote parts of the country? Should there be a mechanism provided to deal with such cases, for example an examining team led by an Amateur but including non-Amateur examiners, such as elected public officials, when three licensed Amateurs aren't available? Should a formal procedure for giving exams at hamfests or in classrooms be included in the new rules?

What should the qualifications for a Volunteer-Examiner-Coordinator (VEC) be? There has been definite interest in this program shown by some non-Amateur groups. How should the long-term integrity of the VECs be ensured?

It seems that the FCC would prefer to have more than one VEC overseeing the exam-administration effort. How could anyone be sure that the different organizations all hew to the same standards? How would the overseeing groups finance their administration costs? The ARRL is already well aware of what this program is going to cost it, and it questions whether it's fair to the League's members to have them pick up the bill. Should there be a fee charged for giving Amateur exams? Who should set the fee, and to whom — the examiners, their overseeing group, or both — should it go?

Should the FCC include the Novice exam in this new overall program, instead of establishing the less demanding Novice exam program they proposed in an NPRM late last year? The ARRL wants Novices included, yet the Commission has indicated its approach would be simpler, faster, and cheaper. The Commission received very few comments on its Novice exam NPRM; does that mean Amateurs want the Novice exam a part of the larger program, or was the FCC's proposed Novice exam program simply overlooked in the concern generated by the no-code license proposal?

There are other considerations as well. It takes time to establish workable procedures (look how long the FCC had). Might not inordinate delays occur at every step of the process, resulting in longer delays in getting licensed? Right now it's a hot topic, but what about one or two years downstream? Might not interest wane among the exam administrators — with newcomers to the hobby being the losers? Most of all, we should be concerned about the possibility that the ham ticket might be devaluated by an unequitable, non-uniform examination procedure. How simple it seems now, to go down to the nearest FCC office and take the exam. Might not a small licensing fee underwrite the cost of FCC-administered exams?

Write the FCC with your opinions. Comments on the exam administration proposal, FCC PR Docket 83-27, are due at the Commission by April 8th. Address them to the Secretary, Federal Communications Commission, Washington, D.C. 20554. You'll need to send an original neatly typed with wide margins, plus five copies (eleven is better, since each Commissioner will receive one). Your name and the Docket number should appear on each page.

What we, as individual Amateurs and through our clubs and organizations, tell the Commissioners may do more to influence the future of Amateur Radio in the United States than anything else we will ever do!

**ham radio**

# RECEIVE WEATHER CHARTS IN YOUR HOME!



## You can DX and receive weather charts from around the world.

Tune in on free, worldwide government weather services. Some transmitting sites even send weather satellite cloud cover pictures!

## You've heard those curious facsimile sounds while tuning through the bands — now capture these signals on paper!

Assemble ALDEN's new radiofacsimile Weather Chart Recorder Kit, hook it up to a stable HF general-coverage receiver, and you're on your way to enjoying a new hobby activity with many practical applications. Amateurs, pilots, and educators can now receive the same graphic printouts of high-quality, detailed weather charts and oceanographic data used by commercial and government personnel.

## Easy to assemble — Backed by the ALDEN name.

For over 40 years, ALDEN has led the way in the design and manufacture of the finest weather facsimile recording systems delivered to customers worldwide. This recorder kit includes pre-assembled and tested circuit boards and mechanical assemblies. All fit together in a durable, attractive case that adds the finishing professional touch.

## Buy in kit form and save \$1,000!

You do the final assembly. You save \$1,000. Complete, easy-to-follow illustrated instructions for assembly, checkout, and operation. And ALDEN backs these kits with a one-year limited warranty on all parts.

## Easy to order.

Only \$995 for the complete ALDEN Weather Chart Recorder Kit. To order, fill out and mail the coupon below. For cash orders enclose a check or money order for \$995. Add \$5 for shipping and handling in the U.S. and Canada (for Massachusetts delivery, add \$49.75 sales tax). To use your MasterCard or Visa by phone, call (617) 366-8851.

## ALDEN ELECTRONICS

Washington Street, Westborough, MA 01581

NAME: \_\_\_\_\_

CALLSIGN: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

CITY: \_\_\_\_\_ STATE: \_\_\_\_\_ ZIP: \_\_\_\_\_

I've enclosed a check or money order for \$995.00 and \$5.00 for shipping and handling, plus applicable sales tax.

Charge to:  MasterCard   Visa 

ACCOUNT # (ALL DIGITS)

\_\_\_\_\_

EXPIRATION DATE

\_\_\_\_ - \_\_\_\_

SIGNATURE REQUIRED IF USING CREDIT CARD \_\_\_\_\_



## filters for Amateur use

Dear HR:

In his letter to the *ham radio* editor (February, 1983, page 8), Ed Marriener, W6XM, mentioned a problem the Radio Amateur too frequently ignores — the need to comply with the FCC requirement that transmitter harmonics be down by 40 dB or more from the fundamental. Ed further explained that to accomplish this on all bands a lowpass filter for each band is necessary. The customarily used 30-MHz lowpass filter, widely advertised by J.W. Miller, Drake, and B&W, is effective, he said only for the Amateur 10-meter band.

A "best solution" offered by Ed was for the Amateur to install lowpass filters designed to cut off just above the upper end of the band being used; however, the recommended designs were from the June, 1957, issue of *GE Ham News* — designs that are more than twenty-five years old!

During the past twenty-five years, the Radio Amateur has witnessed many changes, the most obvious being the transition from vacuum tube to solid state, and more recently the introduction of the personal computer to ham operation. Less obvious was the transition from filter design using the image-parameter-design procedure invented by Otto Zobel to the modern filter (network-synthesis) design procedure. The modern design filter has a simpler configuration

and a more precise performance than the older image-parameter type. Modern lowpass designs (Chebyshev and elliptic) have been developed in which standard-value capacitors are used, thus making them simple for the Amateur to build. These designs have been widely published in the Amateur Radio handbooks, in trade handbooks, and in the Amateur and trade periodicals. I think Ed will agree that these designs are a better solution to the Amateur lowpass filtering requirements than are the old designs.

Ed also mentioned the problem of obtaining suitable high-voltage, low-loss capacitors for use in constructing lowpass filters for Amateur high-power applications. I, too, have experienced this problem, and I have continually been searching for a better high-voltage capacitor than the Centralab ceramic TVL type that Ed mentioned. I think I have finally found a suitable alternative to the TVL capacitor, but the manufacturer of the high-voltage capacitor, KD Components Inc. (3016 S. Orange Ave., Santa Ana, California 92707), sells only in quantities greater than ten and has a minimum billing of \$50. Also, the maximum capacitance available in the 2-3 kV range is 100 pF, so several capacitors will have to be paralleled to get the larger capacities required by the filters for the lower Amateur bands. The approximate cost of the 2-kV, 100-pF, 10 percent capacitor in

quantities of 10-99 is \$4. In quantities above 500, the price drops to \$1.44! Consequently, this capacitor type, although excellent for the application, appears to be financially practical only for a high-volume manufacturer of lowpass filters.

A filter designed from the data in reference 4 (*QST*, December, 1979) was constructed and operated at a 1-kW power level without a failure, but this is feasible only when the VSWR can be carefully controlled, otherwise the voltage rating of the capacitors may be exceeded and the filter damaged if the VSWR becomes excessive. For power levels below 500 watts, the polystyrene and mica capacitors seem suitable. So, contrary to Ed's concluding statement, there does seem to be hope, and I suggest that those not having a filter for each band should review the references included with this letter, and then construct any filters that may be required.

## references

1. *Radio Handbook*, 22nd edition, edited by W.I. Orr, W6SAI, pages 3.35-3.37, copyright 1981 by H.W. Sams & Co., Inc., Indianapolis, Indiana.
2. *The Radio Amateur's Handbook* (1983), 60th edition, edited by George Woodward, W1RN, page 6-41, fig. 65, copyright 1982 by ARRL, Newington, Connecticut.
3. *The Electronic Databook*, edited by R. Graf, to be published in 1983 by TAB Books, Blue Ridge Summit, Pennsylvania.
4. Ed Wetherhold, W3NQN, "Low-pass filters for amateur radio transmitters," *QST*, December, 1979.
5. Ed Wetherhold, W3NQN, "Elliptic lowpass filters for transistor amplifiers," *ham radio*, January, 1981.
6. Ed Wetherhold, W3NQN, "Filter Design," *Comments*, *ham radio*, October, 1981, page 6.
7. Ed Wetherhold, W3NQN, "7-element 50-ohm Chebyshev filters using standard-value capacitors," *rf design*, Vol. 3, No. 2, February, 1980, pages 26-38.
8. Ed Wetherhold, W3NQN, "Low-pass filters (with inductive input and output)," *rf design*, Vol. 4, Nos. 4 and 5, July/August and September/October, 1981.
9. Ed Wetherhold, W3NQN, "Design 7-element lowpass filters using standard-value capacitors," *EDN*, Vol. 26, No. 1, January 7, 1981, pages 187-190.
10. Ed Wetherhold, W3NQN, "Low-pass Chebyshev filters use standard-value capacitors," *Electronics Engineers' notebook*, June 19, 1980.

**Ed Wetherhold, W3NQN**  
Annapolis, Maryland

# MFJ CW/SSB/Notch Filters

MFJ-722 ALL MODE audio filter for CW/SSB has tunable 70 dB notch, no ring 80 Hz CW bandwidth, steep SSB skirts (18 poles total), 2 watts for speaker plus more.



*All mode versatility:  
razor sharp CW and steep-skirted  
SSB filtering with tunable notch  
eliminates QRM.*

**\$69<sup>95</sup>**

**New super-selective filter.** The new MFJ-722 "Optimizer" offers razor sharp, no ring CW filtering with switch-selectable bandwidths (80, 110, 150, 180 Hz centered on 750 Hz), steep-skirted SSB filtering, and a 300-3000 Hz tunable 70 dB notch filter with adjustable bandwidth.

**The 8-pole (4 stage) active IC filter** gives CW performance no tunable filter can match (80 Hz bandwidth gives -60 dB response one octave from center and up to 15 dB noise reduction). The 8 pole SSB audio bandwidth is optimized for reduced sideband splatter and less QRM (375 Hz highpass cutoff plus selectable lowpass cutoffs at 2.5, 2.0 and 1.5 KHz, 36 dB/octave rolloff). Measures 5x2x6".

**New Model MFJ - 723, (\$49.95),** is similar to the 722 but is for CW. Has a 60 dB notch tunable from 300 to 1200 Hz. Measures 4x2x6".

**Other models:** MFJ - 721, \$59.95. Like 722, less notch. MFJ - 720, \$39.95. Like 723, less notch.

**Versatile, all models** plug into the phone jack, provide 2 watts for speaker or can be used with headphones. All require 9-18 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

**Order from MFJ and try it-no obligation.** If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

**Order today.** Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus \$4.00 each shipping and handling. **Enjoy improved readability, order now.**

**CALL TOLL FREE ... 800-647-1800**

Call 601-323-5869 in Miss., outside continental USA or for technical info., order/repair status.

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

# MFJ DUMMY LOADS

**Tune up fast into 50 ohm resistive load. Extend life of finals.**



*Includes high quality transformer oil.*

**\$34<sup>95</sup>**

**New MFJ-250 VERSALOAD** Kilowatt Dummy Load lets you tune up fast. Extends life of transmitter finals. Reduces on-the-air QRM.

**Run 1 KW CW or 2 KW PEP** for 10 minutes, 1/2 KW CW or 1 KW PEP for 20 minutes. Continuous duty with 200 watts CW or 400 watts PEP. Complete with derating curve.

**Quality 50 ohm non-inductive resistor.** Oil cooled. Includes high quality, industrial grade transformer oil (contains no PCB).

**Low VSWR to 400 MHz:** Under 1.2:1, 0-30 MHz. 1.5:1, 30-300 MHz. 2:1, 300-400 MHz. **Ideal for testing HF and VHF transmitters.** SO-239 coax connector. Vented for safety. Removable vent cap. Has carrying handle. 7-1/2 in. high, 6-5/8 in. diameter.

**MFJ "Dry" 300 W and 1 KW Dummy Loads.**

**\$64<sup>95</sup>** MFJ-262 **\$26<sup>95</sup>** MFJ-260

**Air cooled, non-inductive 50 ohm resistor** in perforated metal housing with SO-239 connectors. Full load for 30 seconds, derating curves to 5 minutes. **MFJ-260 (300 W).** SWR: 1.1:1 to 30 MHz, 1.5:1 for 30-160 MHz. 2 1/2 x 2 1/2 x 7 in. **MFJ-262 (1 KW).** SWR 1.5:1 for 30 MHz. 3x3x13 inches.

**MFJ HF SWR/Wattmeter**

**\$29<sup>95</sup>** MFJ-816

**New MFJ-816 low cost HF SWR/Wattmeter** for 1.8 to 30 MHz range. **Toroidal current pickup** gives uniform sensitivity over entire HF frequency. **Read SWR,** forward and reflected power in 2 ranges (30 and 300 watts) on two color scale. SO-239 coax connectors. 4-1/2x2-3/8x2-7/8 in.

**Order from MFJ and try it.** If not delighted, return it within 30 days for refund (less shipping).

**One year unconditional guarantee.** **Order today. Call TOLL FREE 800-647-1800.** Charge VISA, MC. Or mail check, money order. **Write for free catalog.**

**CALL TOLL FREE ... 800-647-1800**  
601-323-5869 in MS, outside continental USA.

**MFJ ENTERPRISES, INCORPORATED**  
Box 494, Mississippi State, MS 39762

# MFJ/Bencher Keyer Combo

**Deluxe MFJ Keyer fits on Bencher Paddle. Curtis 8044 IC. Iambic. Adjustable weight, tone, volume, speed. Semi and automatic modes. Solid state keying. RF proof.**



**MFJ-422 Combo \$99<sup>95</sup>**

**The best of all CW worlds - a deluxe MFJ Keyer** in a compact configuration that fits right on the Bencher iambic paddle! You can buy the combination or just the keyer for your Bencher.

**New MFJ Keyer—small in size, big in features.** Curtis 8044 IC, adjustable weight and tone, front panel volume and speed controls (8-50 wpm). Built-in dot-dash memories. Speaker, sidetone, and push button selection of semi-automatic/tune or automatic modes.

**Ultra-reliable solid state keying:** grid-block, cathode and solid state transmitters (-300 V, 10 mA max., +300 V, 100 mA max.). Fully shielded. Uses 9 V battery or 110 VAC with optional adapter, MFJ 1312, \$9.95.

**Beautiful functional engineering.** The keyer mounts on the paddle base to form a small (4 1/8 x 2 5/8 x 5 1/2") attractive combination that is a pleasure to look at and use.



**MFJ-422X Keyer only \$69<sup>95</sup>**

**The Bencher Paddle is a best seller.** Fully adjustable gold-plated silver contacts, lucite paddles, chrome plated brass, heavy steel base with non-skid feet.

**Order from MFJ and try it - no obligation.** If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

**Order today.** Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus \$4.00 each shipping and handling. **Enjoy CW. See dealer or call MFJ now.**

**CALL TOLL FREE ... 800-647-1800**

Call 601-323-5869 in Miss., outside continental USA or for technical info., order/repair status.

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

LEGAL PROBLEMS WITH BOTH ANTENNAS AND RFI are continuing for a number of Amateurs in various communities, and should be of concern to Amateurs throughout the country. Ceritos, California, long a leader in antenna height restrictions, has resisted a suit brought by several Amateurs attempting to overturn a moratorium on new antennas. That city is in the process of drafting a new, more restrictive ordinance, but the judge ruled the suit was "premature," since the terms of the new ordinance haven't yet been decided. An appeal is being considered, and the ARRL Executive Committee has voted in favor of entertaining a request for the League to match local financial support. Other tower cases in Oklahoma City (N5SW), Farmington, Michigan (WD8BCM), and Burbank, Illinois, are still pending, but N0BCX's challenge of a Brighton, Minnesota, ordinance has been upheld and his 65-footer is still up.

WB2BZK's Appeal To The New Jersey Supreme Court of Winslow township's prohibition of RFI has been turned down. Efforts are continuing to get the township to review and perhaps rescind its ordinance, in view of the federal assumption of such regulation contained in Public Law 97-259 (the "Goldwater Bill").

TWO VITALLY IMPORTANT AMATEUR RULES CHANGES PROPOSED BY THE FCC are up for comments during April. The proposal to establish a volunteer examining procedure for all Amateur licenses, PR Docket 83-27, has a comment closing date of April 8, which leaves little time to consider its implications (see this month's Reflections, page 6). The no-code license proposal, PR Docket 83-28, is open for comments until April 29.

The ARRL's Adamant Position Against No-Code May Be Softening, according to some indications. It appears that the League membership may not be as solidly against a no-code license as was previously reported. With the strong pro no-code position apparent among the Commissioners, the ARRL now feels it may be prudent to support a form of no-code that the Amateur community can live with, rather than oppose it outright and have no say in its final form. The League Executive Committee has agreed informally to prepare a position paper outlining various no-code alternatives for the directors before their April board meeting, at which time the final League position will be determined and comments prepared.

Amateur Exam Administration At This Year's Dayton Hamvention had been sought by the Hamvention Committee, and initial FCC reaction had been positive. However, it now appears that, though exams will be given at the Hamvention, they will be administered under the supervision of the FCC. Barring unforeseen problems, the earliest a complete volunteer program could be put together and set in motion would be late next fall, leaving too many variables to be settled in time for even a dry run at this year's Hamvention.

RICH ROSEN, K2RR, HAS BEEN APPOINTED EDITOR-IN-CHIEF OF HAM RADIO effective February 5. Rich joined Ham Radio last fall, as Senior Technical Editor.

ARRL's New Technical Department Manager Is Paul Rinaldo, W4RI, who's replacing Doug DeMaw, W1FB, upon Doug's retirement in May. Paul currently edits QEX, the ARRL experimenters' newsletter, and is the president of AMRAD.

TEN SCHOLARSHIPS FOR GENERAL CLASS (OR HIGHER) AMATEURS planning to attend (or already attending) college or technical school are available through the Foundation for Amateur Radio. Full details and an application form can be obtained from Hugh Turnbull, W3ABC, 6903 Rhode Island Ave., College Park, MD 20740. May 31 is closing date for requests.

THE PHONE BAND EXPANSION IS STILL IN PROCESS within the Commission, with expectations that it will be finished and released by late spring. Just which bands will (and which won't) be changed isn't yet clear, though it seems very likely that 20 and 10 will both see some expansion of their phone subbands.


Deregulation Of The CB Service Is Also In The Mill, with the new rules (or non-rules) to be announced at about the same time as Amateur phone band expansion.

Extension Of Amateur License Terms To 10 Years from the present five is likely to surface soon. Though the FCC now has the authority to make the change, it will probably be introduced through a Notice of Proposed Rule Making to assess Amateur reaction.

PROFANE AND INDECENT LANGUAGE IS NO LONGER GROUNDS FOR REVOKING an Amateur's license, according to the FCC's Review Board. The license of N6BHU had been revoked last fall by an FCC Administrative Law Judge for such violations, but on January 26 that decision was overturned and his license reinstated. With a suburban Washington, D.C., broadcast station now airing uncensored "party" records, it appears the Commission concern with the content of transmissions may be a thing of the past. However, the ARRL is seeking a review of the subject with the FCC staff in hopes of restoring some standards for Amateurs.

THE SOLAR FLUX SLUMPED TO ITS LOWEST LEVEL SINCE JANUARY, 1978, at mid February, to give a hint of things to come as this sunspot cycle deepens. Solar activity remained low through CW DX Contest weekend, with 10 meters of little value and 15 spotty.

Deteriorating HF Band Conditions Highlight The Value of Beacons, particularly the new 14.100 MHz worldwide system sponsored by the Northern California DX Foundation. In addition, the many beacons in the 28.2-28.3 MHz portion of 10 meters and those operating between 50.0 and 50.1 MHz on 6 will continue to signal openings to users of those bands. See Technical Forum, page 46, for information on a beacon on 28.208 MHz.

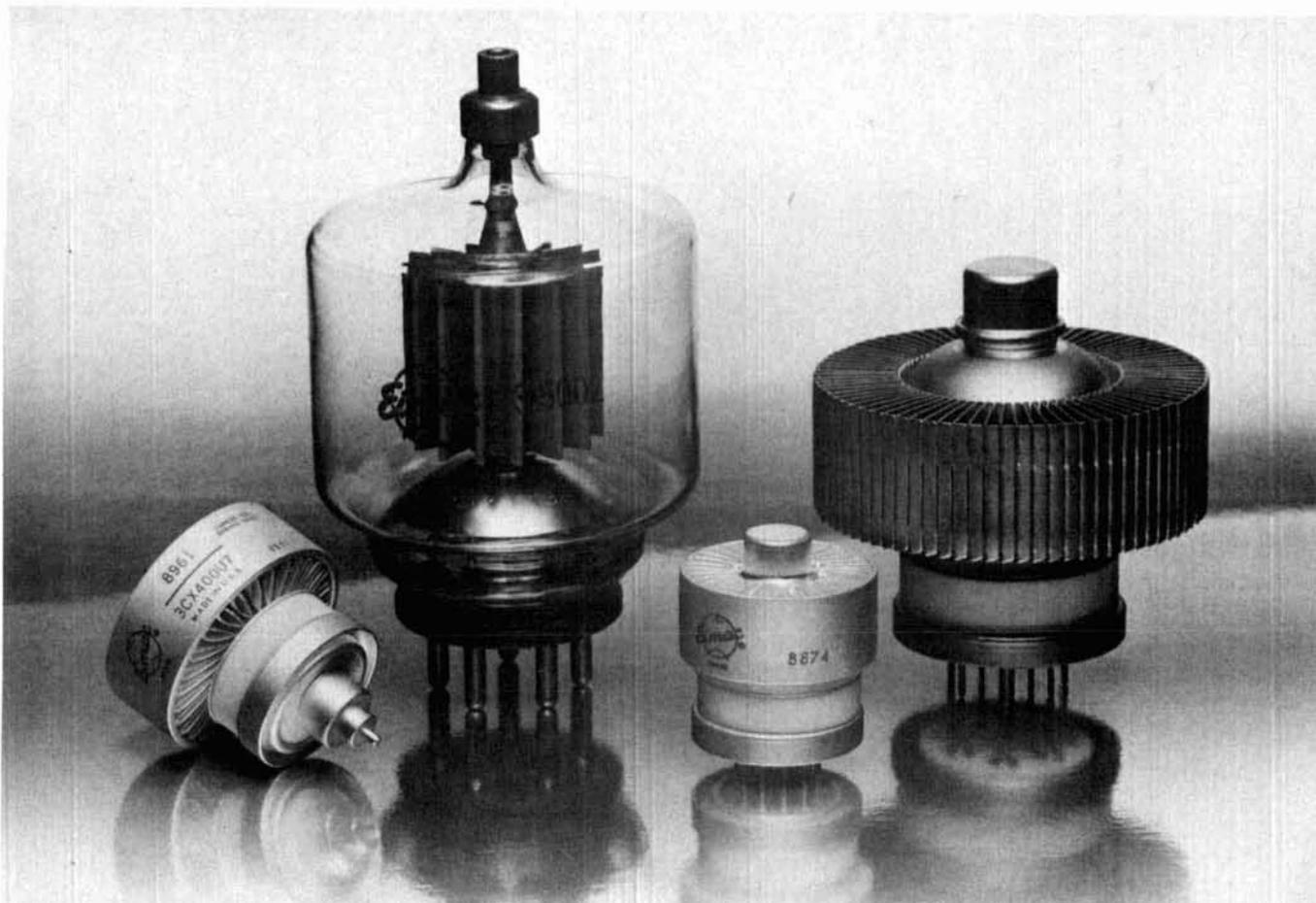

## HF, VHF, UHF, Across the spectrum. VARIAN EIMAC.

Ham operators know that EIMAC started in power tube development with the 150T in 1934. While the 150T is now a collector's item, EIMAC, a division of Varian, still holds leadership in power tube design with its 4CX250B, 8874, 3-500Z, 8877 and 3CX400U7; modern examples of EIMAC's continuing, innovative solutions to tough communication requirements.

EIMAC's proven power tubes are used in amateur service for heavy-duty, reliable performance in traffic; RTTY; SSTV; DX operation; VHF/UHF work; moonbounce, and exploration of the outer limits of communication techniques across the spectrum.

High quality and long life make EIMAC tubes the favorite choice of operator and equipment builder, amateur and professional alike.

For communication and research worldwide, choose EIMAC. For information on VARIAN EIMAC power tubes, call or write today. Or contact the nearest Varian Electron Device Group sales office.

VARIAN EIMAC  
301 Industrial Way  
San Carlos, California 94070  
415-592-1221

VARIAN EIMAC  
1678 S. Pioneer Road  
Salt Lake City, Utah 84104  
801-972-5000

VARIAN AG  
Grienbachstrasse 17  
Postfach  
CH-6300 Zug, Switzerland  
Tel: (042) 31 66 55  
Telex: 845-78789



# inexpensive video monitor

Bypassing rf and i-f sections  
to resurrect old TVs  
for modern use

The current interest in home computers, slow-scan and fast-scan TV, RTTY, and automatic CW keyboards — not to mention home video movies and games — creates a need for an inexpensive display device for the ham shack. Many commercial video products are designed to work with a standard TV, typically using channels 2, 3, or 4 with a video modulator. There are some drawbacks to this procedure, though; for one thing, the family TV is not likely to be located in the ham shack. And, more importantly, the performance of a TV set is less than optimum if high resolution is needed.


I first considered the problems of TV sets when I acquired a TRS-80 Model I microcomputer a few years ago. I figured I could save some money by converting an old black and white TV set for use as a monitor. Typical computer-grade monitors sell for \$100 or more, but a flea-market TV can be found for next to nothing. And TV sets have a 15 to 20 inch screen, unlike the typical 12-inch monitor. Sounds like a bargain, but there's a hitch.

The problem is bandwidth, (or resolution, depending on your point of view). Commercial CRTs use an 80-character display, and many home computers settle for 48, 32, or even 24 characters per line. The res-

olution of TV is typically much less. The TRS-80 uses a sixty-four character display, which is why Radio Shack sells a dedicated monitor. Those sixty-four characters occupy roughly 80 percent of the horizontal scan line. Each character is five dots (pixels) wide, and there is a one-pixel space between letters. So, we have  $6 \times 64 = 384$  pixels per line. In a conventional (U.S.) TV scanning system, one line is scanned in 63.5 microseconds. Only 80 percent of this time is available for the letters, so the pixels are scanned at a rate of  $(384 \text{ pixels/line}) / (0.8 \times 63.5 \text{ microseconds}) = 7.6$  million pixels/second, or 130 nanoseconds/pixel! The situation is even worse for an eighty-character line. (The longer lines are desirable for RTTY — where seventy-two character machines are common — and word-processing.) Furthermore, in order that the pixels reach full brightness when on, and return to the black video baseline when off, the rise and fall times must be much less than the 130-nanosecond duration of a pixel. Otherwise they will run together in the bars on the letters T, E, B, and so on, and fade out in the vertical part of letters I, L, etc., as noted by W9CGI.<sup>1</sup> We require a bandwidth at least twice the pixel rate, or 15 to 20 MHz!

Broadcast TV uses a 6-MHz channel width. The i-f strip is designed to have sharp cutoff, to minimize adjacent channel interference. The video carrier is already 1.25 MHz above the lower band edge in the

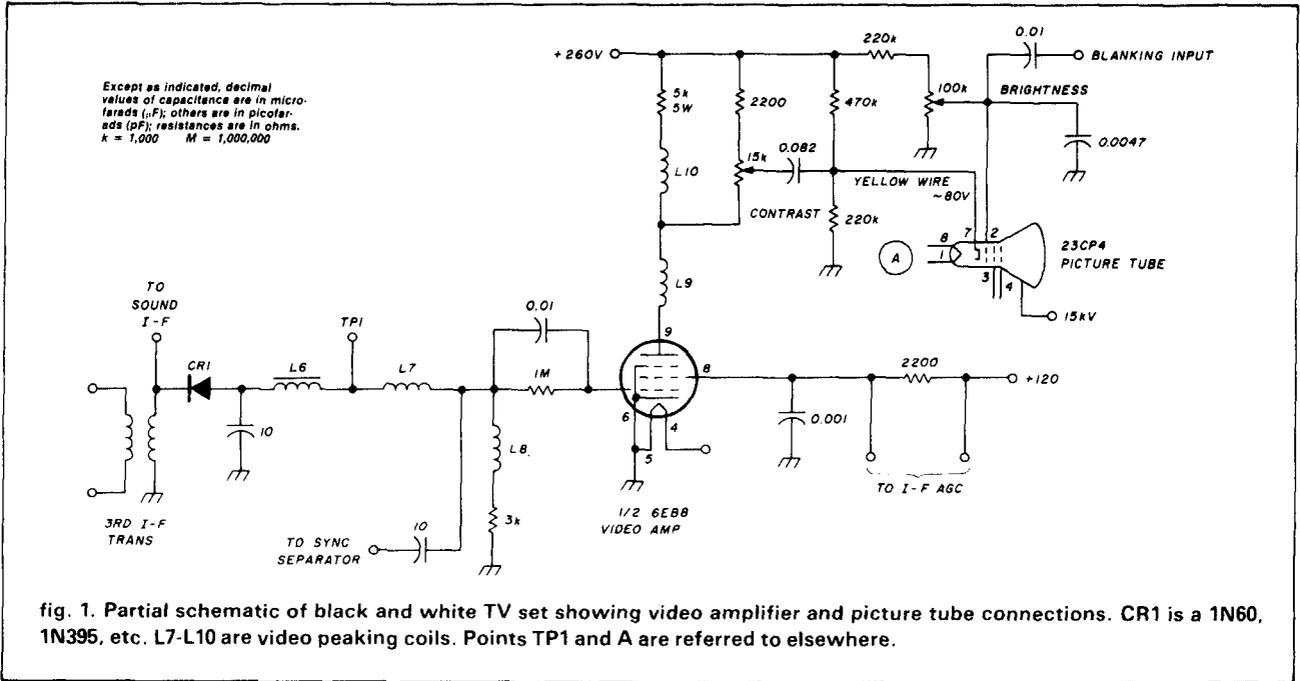By Carl Gregory, K8CG, 203 Trappers Place,  
Charleston, West Virginia 25314




vestigial sideband system. The maximum available video bandwidth is a bit more than 4 MHz, if we use the video-modulated rf carrier approach. It should have been no surprise to me when my TRS-80 display was illegible unless I used the expanded (thirty-two character per line) display. The problem was compounded by snow (low signal to noise ratio) from the aging rf section.

How to remedy this? Several approaches are possible:

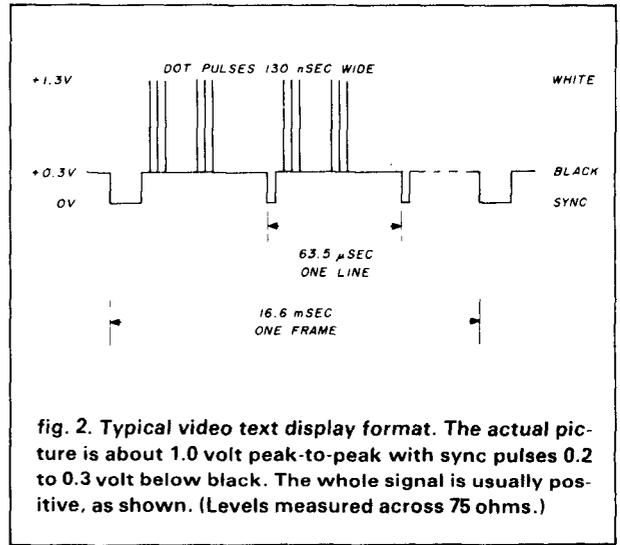1. Slow down the scan rate. This method has two drawbacks in that it causes annoying flicker in the display, and requires major modifications to the TV and the video display-generating circuitry.
2. Pre-process the video signal, emphasizing high frequencies. This approach was used by W9CGI. But you can compensate for only so much high frequency roll-off. The match between compensation and i-f roll-off must be exact.
3. Bypass the problem by skipping the rf and i-f sections of the TV set. This is my approach; it is the simplest, the most effective, and potentially the cheapest, since you can use a TV with a defunct tuner.

Let's consider the modification of a typical tube-type TV set for use as a wideband video display. Fig 1 shows the pertinent parts of the video amplifier stage. (The circuit is from my Setchell-Carlson set<sup>3</sup>). Note that the cathode of the picture tube is driven. Fig. 2 shows the typical video signal level available from the computer, demodulator, or other source. Our problem is to match the two devices.



### simplest approach

The first method uses the existing video amplifier and bypasses the rf and i-f stages. In my set, the detector output (TP-1) was brought out to a test point on top of the chassis. I determined that, since the typical detector level is a couple of volts peak-to-peak, the new video source could just be hooked in parallel here.

Fig. 3 shows the circuit. The signal comes from the computer, VCR, or other source, via the coax. Some 50 or 75-ohm cable is all right as long as it's not more than a few feet long. I used RG-174, which is a nice size — not too stiff. A blocking capacitor is

needed since the 2200-ohm grid leak would otherwise be shorted by the 75-ohm video source. This capacitor must pass frequencies as low as the vertical sync pulses at 60 Hz. For 50- or 75-ohm systems this means  $X_c = 50 \text{ ohms}$  (maximum), so  $C = 1/(2 \times \pi \times 60 \times 50) = 53 \text{ microfarads}$  (minimum). Note the polarity of the capacitor: the grid is negative. *Be cautioned: This circuit will not work on a transformerless TV with a hot chassis unless an ac isolation transformer is installed, because there is no place to safely install the shield side of the video cable!*

I installed this circuit (cost was less than \$3.00 for cable, connectors, and capacitor) in my TV set, and was using my new computer in a day or so. I used it that way for about a year before I had time to try to improve the performance. There was still considerable blurring of pixels, the brightness and contrast needed continuous adjustment as the set warmed up, and the contrast was a bit low.

## second approach

A note in *Byte* magazine suggested the solution.<sup>2</sup> A new video amplifier improves the high-frequency response, and provides the needed gain to get the desired contrast. Unfortunately, the circuit in the magazine had some drawbacks, and I finally came up with my own. The circuit in **fig. 4** has the following properties: no separate power supply needed; adequate gain; sufficient bandwidth to give well-formed characters at 80 per line; linear enough to use for a video-tape or ATV monitor; uses the existing brightness control circuit; no exotic devices required. (Any modern PNP and NPN transistor should work fine.)

## circuit description

The video cable is terminated in a resistive pad,

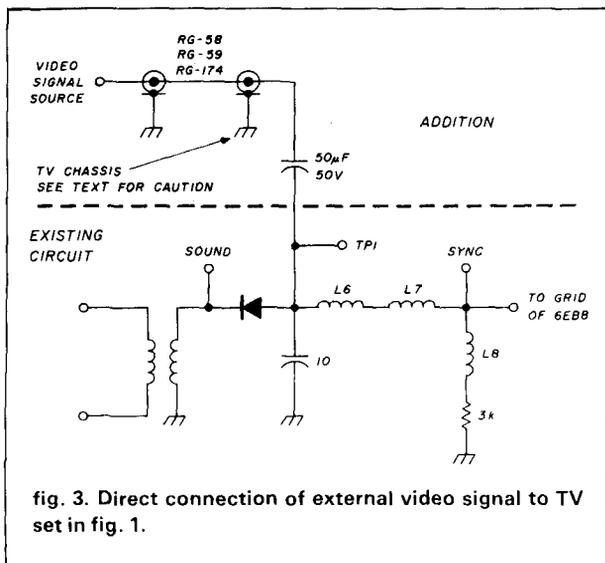


fig. 3. Direct connection of external video signal to TV set in fig. 1.

R1-R3, which also serves as part of the bias circuit for Q1. C1 passes the signal to the video amplifier (for the benefit of the sync circuitry only). Q1 operates as a linear common-emitter amplifier. The gain is about 5 at low frequencies. The emitter bypass (C2) boosts the gain above 5 MHz and compensates for the transistor's reduced beta. It is important to operate all the transistors in the linear region. Saturation of any transistor (clipping) will load the base with charge, requiring time to discharge, resulting in slow switching or reduced bandwidth.

Q2 acts as an inverter and level shifter. The gain is about 0.7. The level shifting is necessary since dc coupling is used to get wide bandwidth, and the gain need not be high since we have one more stage to go. Q3 is another common-emitter amplifier, with a gain of 3 at the collector. The signal has now been inverted three times, so it is inverted overall. The white peaks of the video input are negative peaks at the output (cathode) which drive off many more electrons and make a white spot on the screen.

The cathode of the picture tube is a low current point, so we can use a relatively small capacitor to couple the signal to it (C3). We also need dc here, but the value (+80 volts) is a bit high for the transistors, so I derived it from the existing bias circuit via a filter (R11-12 and C4). The filter removes the video information from the old amplifier, but passes the dc cathode current.

The overall gain is about -15, so a 1-volt peak-to-peak input yields about 15-volts peak-to-peak output. This means the power supply must provide considerably more than 20 volts. By trial and error, dropping resistors (R13-14) were found which gave an acceptable picture without overheating the transistors. (It is difficult to calculate the value, since the current drain of the amplifier varies with  $V_{cc}$  and the nature of the video signal.) C5 filters the resulting 40 volts or so and keeps it relatively constant during each frame. This unregulated supply is the least satisfactory aspect of the circuit, but the heat from the dropping resistors is hardly noticed in a tube-type set.

## construction

This amplifier can be built in a breadboard format, since parts placement is not critical. I used a simple printed circuit board (cover the foil with masking tape and remove some with a knife, leaving large islands where the components are to be attached). The board was installed in the back of the set below the base of the picture tube. I just cut the yellow cathode lead in the middle (point A in **fig. 1**) and attached the two ends to the board. This is probably the only semi-critical item — it wouldn't do to go to all that trouble to get a sharp video signal and then

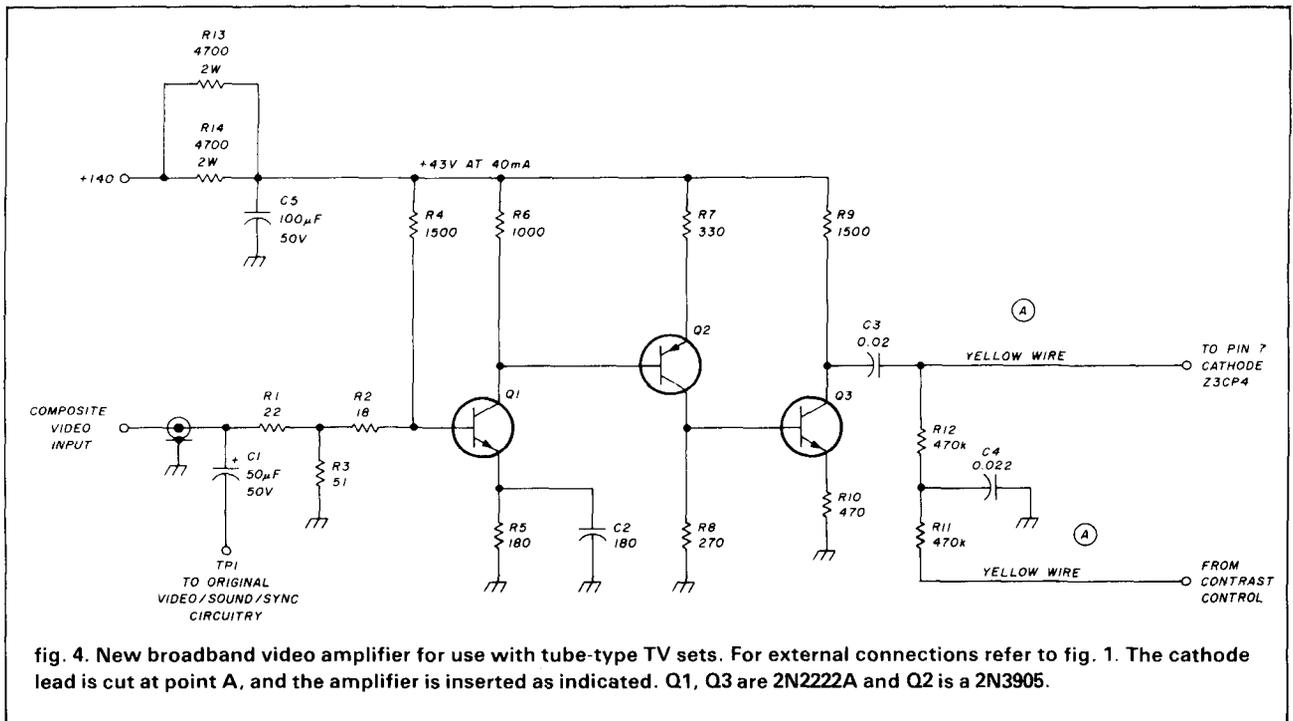


fig. 4. New broadband video amplifier for use with tube-type TV sets. For external connections refer to fig. 1. The cathode lead is cut at point A, and the amplifier is inserted as indicated. Q1, Q3 are 2N2222A and Q2 is a 2N3905.

run it through a long inductive lead. But 6 to 8 inches doesn't seem to hurt. *Caution: This circuit will not work on a transformerless TV with a hot chassis unless an ac isolation transformer is installed, because there is no place to safely install the shield side of the video cable!*

### adjustment

There are no adjustments in the new video amplifier. However, we can improve performance a bit by adjusting the TV set. So far, only the video characteristics associated with the horizontal sweep have been discussed. Another problem with TV is that the scan is not necessarily linear. That is, the picture may be bunched up at one side or the top or bottom of the screen, and spread out elsewhere. This would be intolerable in a color set, but is common in old black and white sets. There should be a pair of pots for adjusting top and bottom vertical linearity, and there are two tabs mounted on the yoke which can be rotated independently to position the picture properly. It should be possible to find a combination in which the part of the picture you want to use the most is conveniently displayed.

Finally, you may find that the focus is not uniform over the screen. The focus control and those positioning tabs may interact, and it should be possible to get a reasonably crisp picture over the most important parts of the screen. (For use as a computer or RTTY display, the right side is less important than the left, for instance.)

I have been using the circuit in fig. 4 with the TRS-80, and more recently with a homebrew S-100 system using an eighty-column display, for about a year now. It sure is nice to not have a lot of short, left-over lines on RTTY — you can see most of the last transmission all at once with the eighty-column display. The large screen is easy on the eyes, although the contrast is a bit low if the room is sunlit. And word-processing is handy, too; this article was written on the big screen. A test with a Panasonic portable VCR and camera showed an excellent picture of the shack. (Everything perfect except the color!)

An old TV set can be given a new lease on life as a modern video monitor for the shack at relatively low cost. The effort required will depend on the bandwidth needed for your application. I hope the principles presented here will save you a good deal of time and frustration as you attack that tube. This project is worthwhile for any experimenter on the more modern modes, such as RTTY, slow or fast-scan TV, or computer communications.

### references

1. D.J. Brown, W9CGI, "CRT Character Enhancer," *ham radio*, August, 1982, page 66.
2. Timothy Loof, "Use Your Television Set as a Video Monitor," *Byte*, February, 1979, page 46.
3. Schematics for older TV sets can be obtained from your local TV-repair parts supplier. Ask for Howard W. Sams "Photofact" sheets by model number.

# Morse time synthesis

This software routine  
lets your micro  
speak the time  
in Morse code

Talking microcomputers are becoming common as more companies develop hardware modules for voice synthesis. Most are reasonably priced, starting from \$100. If you want vocal feedback from your computer and need only a vocabulary limited to the decimal integers, you might consider a software alternative: voice synthesized telegraphy.

The program described here synthesizes a 24-hour clock which provides an audible read-out in Morse code characters. The clock produces Morse characters for the time in hours and minutes on demand, and automatically on the hour. It is especially useful to the blind or seeing-impaired. Even to those unfamiliar with Morse code, the numerals are easy to learn.

This program was conceived on a single-board computer based on the 1802 microprocessor, running at a frequency of 1.7897725 MHz. The program

depends upon only a few hardware features: 256 bytes of RAM, a speaker amplifier on the Q line, and a push-button switch on the EF4 external flag line. All the routines in the program are straightforward, and they can be easily translated into machine code for other microprocessors.

## the program

The main program begins by initializing registers to point to subroutines, locations for binary time, BCD time, and a table of Morse code patterns. The program then enters the time loop (fig. 1). This loop iterates until sixty seconds elapse, at which time binary minutes are incremented. During each iteration, the program checks to see whether the time has been requested by testing external flag EF4, and it checks to see whether sixty minutes have elapsed. In either case program control passes to register R3 for the out subroutine. The time loop also checks for twenty-four hours, at which point the clock is reset to 00:00.

The out routine (fig. 2) is the main subroutine, and produces the Morse code characters. It first clears the old BCD time. Then, after getting binary hours, the program jumps via R4 to the BCD subroutine. On return, the program gets binary minutes and again

By Lawrence G. Souder, N3SE, 4539 Manayunk Avenue, Philadelphia, Pennsylvania 19128

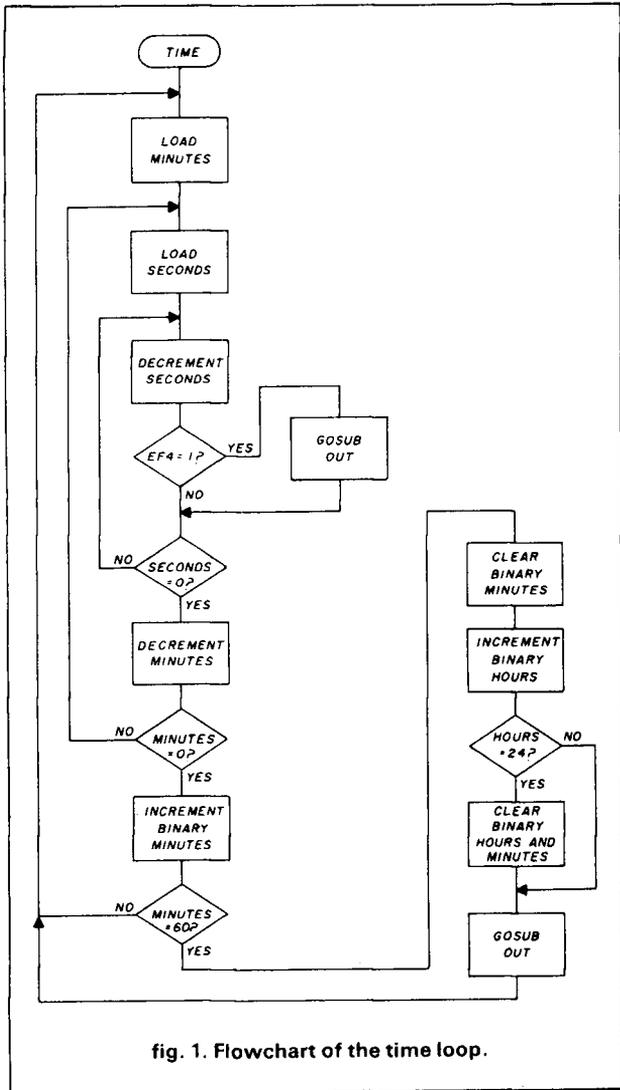


fig. 1. Flowchart of the time loop.

jumps to the BCD subroutine (fig. 3). Now that the program has the time in BCD, control passes to R5 for the Code routine, which converts the BCD digits into Morse characters. On return, program control reverts to R0 to resume the time loop.

BCD is a fairly conventional binary-to-BCD subroutine which converts by successively subtracting ten from the binary value. Every time it subtracts ten, it increments the BCD ten's value and retains the difference as the new binary value. If the subtraction yields a negative difference, the previous binary value is stored as the BCD one's value.

For each BCD digit the code subroutine (fig. 4) finds the bit pattern which corresponds to the appropriate Morse code digit. It then takes this bit pattern and ring-shifts it right, into DF (the 1802's carry flag) five times. After each shift, the code subroutine tests

DF. If DF is 0, a dot is fetched; if DF is 1, it returns a dash. For instance, for the numeral 2 (..- - -) the bit pattern fetched from the table will be XXX11100. (The higher-order three bits are not used.) The code routine will also generate a space between Morse digits.

The routine which produces the tones is called

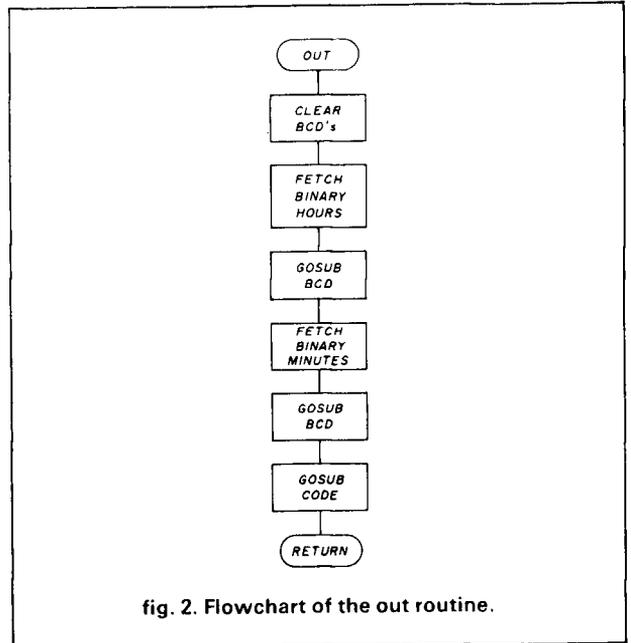


fig. 2. Flowchart of the out routine.

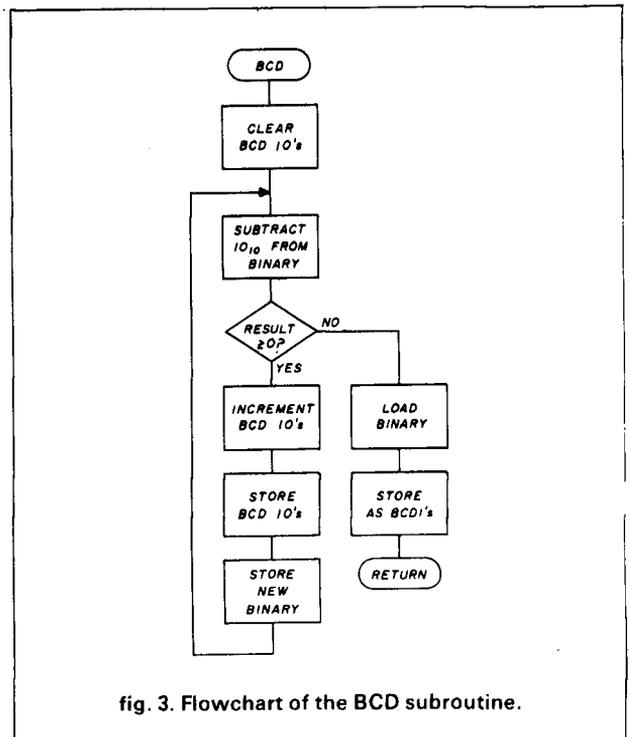


fig. 3. Flowchart of the BCD subroutine.

Program listing.

Register	Use
0	Main program counter
1	Not used
2	Not used
3	Pointer to OUT (0055)
4	Pointer to BCD (0076)
5	Pointer to CODE (0088)
6	Pointer to bit pattern for Morse digits.
7	Pointer to DOT/DASH (00B6)
8	Scratch pad
9	Pointer to Binary Hours (00D0)
A	Pointer to Binary Minutes (00D1)
B	Pointer to BCD Time (starting with 10's hours at 00D2)
C	Counter for Minutes
D	Counter for Seconds
E	Morse character counter (low order)/Temporary code storage (high order)
F	Pointer to top of table of bit patterns for Morse digits (starting at 00D6)

Address	Code	Label	Mnemonic	Operand	Comment
0000	F800	INIT	LDI	00	Set high order of registers
0002	B3		PHI	R3	to 00.
0003	B4		PHI	R4	—
0004	B5		PHI	R5	—
0005	B6		PHI	R6	—
0006	B7		PHI	R7	—
0007	B9		PHI	R9	—
0008	BA		PHI	RA	—
0009	BB		PHI	RB	—
000A	BF		PHI	RF	—
000B	F855		LDI	55	R3 points to OUT (0055).
000D	A3		PLO	R3	—
000E	F876		LDI	76	R4 points to BCD (0076).
0010	A4		PLO	R4	—
0011	F888		LDI	88	R5 points to CODE (0088)
0013	A5		PLO	R5	—
0014	F8B6		LDI	B6	R7 points to DOT/DASH (00B6).
0016	A7		PLO	R7	—
0017	F8D0		LDI	D0	R9 points to Binary Hours (00D0).
0019	A9		PLO	R9	—
001A	F8D1		LDI	D1	RA points to Binary Minutes (00D1).
001C	AA		PLO	RA	—
001D	F8D2		LDI	D2	RB points to BCD Time (00D2).
001F	AB		PLO	RB	—
0020	F8D6		LDI	D6	RF points to Table of Morse
0022	AF		PLO	RF	digits.
0023	F83C	TIME	LDI	3C	Load minute count . . .
0025	AC		PLO	RC	in RC.0.
0026	F86D	SEC	LDI	6D	Load second count . . .
0028	BD		PHI	RD	in RD.1.
0029	2D	DECSEC	DEC	RD	Decrement second count.
002A	3F32		BN4	GETSEC	Anyone want the time?
002C	372C		B4		
002E	F855		LDI	55	If yes, set OUT sub pointer
0030	A3		PLO	R3	R3 to 0055 and . . .
0031	D3		SEP	R3	gosub OUT.
0032	9D	GETSEC	GHI	RD	Get second count.
0033	3A29		BNZ	DECSEC	If ≠ 0, go to DECSEC again.
0035	2C	DECMIN	DEC	RC	Decrement minute count.
0036	8C		GLO	RC	Get minute count.
0037	3A26		BNZ	SEC	If ≠ 0, go to SEC again.
0039	0A		LDN	RA	Get binary minutes.
003A	FC01		ADI	01	Increment binary minutes.
003C	5A		STR	RA	Store new binary minutes.
003D	FF3C		SMI	3C	Have 60 minutes elapsed yet?

Address	Code	Label	Mnemonic	Operand	Comment
003F	3A23		BNZ	TIME	If not, get another minute.
0041	F800		LDI	00	If yes, clear binary minutes
0043	5A		STR	RA	and . . .
0044	09		LDN	R9	increment binary hours.
0045	FC01		ADI	01	—
0047	59		STR	R9	—
0048	FF18		SMI	18	Have 24 hours elapsed yet?
004A	3A4F		BNZ	GONG	If not, output hourly gong.
004C	C4		NOP		—
004D	59		STR	R9	If yes, reset time to 00:00
004E	5A		STR	RA	—
004F	F855	GONG	LDI	55	Set OUT sub pointer R3
0051	A3		PLO	R3	to 0055 and . . .
0052	D3		SEP	R3	gosub OUT.
0053	3023		BR	TIME	Back to TIME.
0055	F800	OUT	LDI	00	Clear BCD 10's Hours.
0057	5B		STR	RB	—
0058	1B		INC	RB	Clear BCD 1's Hours.
0059	5B		STR	RB	—
005A	1B		INC	RB	Clear BCD 10's Minutes.
005B	5B		STR	RB	—
005C	1B		INC	RB	Clear BCD 1's Minutes.
005D	5B		STR	RB	—
005E	F8D2		LDI	D2	Restore BCD Time Pointer RB
0060	AB		PLO	RB	to 00D2.
0061	F876		LDI	76	Restore BCD sub pointer R4
0063	A4		PLO	R4	to 0076.
0064	09		LDN	R9	Get Binary Hours and . . .
0065	D4		SEP	R4	gosub BCD.
0066	F876		LDI	76	Restore BCD sub pointer R4
0068	A4		PLO	R4	to 0076.
0069	0A		LDN	RA	Get Binary Minutes and . . .
006A	D4		SEP	R4	gosub BCD.
006B	F8D2		LDI	D2	Restore BCD Time pointer RB
006D	AB		PLO	RB	to 00D2.
006E	F888		LDI	88	Restore CODE sub pointer R5
0070	A5		PLO	R5	to 0088.
0071	D5		SEP	R5	Gosub CODE.
0072	F8D2		LDI	D2	Restore BCD Time pointer RB
0074	AB		PLO	RB	to 00D2.
0075	D0		SEP	R0	Return to TIME.
0076	A8	BCD	PLO	R8	Put Binary in scratch pad R8.0
0077	FF0A	SUB10	SMI	0A	Subtract 10 <sub>10</sub> from binary.
0079	3B83		BNF	BCD1'S	Use Binary as BCD 1's if result
007B	A8		PLO	R8	≤ 0. Otherwise store result . . .
007C	0B		LDN	RB	and increment BCD 10's.
007D	FC01		ADI	01	—
007F	5B		STR	RB	—
0080	88		GLO	R8	Get new Binary and try to
0081	3077		BR	SUB10	subtract 10 again.
0083	1B	BCD1'S	INC	RB	Since Binary is less than
0084	88		GLO	R8	10 store it as BCD 1's
0085	5B		STR	RB	—
0086	1B		INC	RB	—
0087	D3		SEP	R3	Return to OUT.
0088	F830	CODE	LDI	30	Delay between Morse digits.
008A	B8		PHI	R8	—
008B	28	DECDEL	DEC	R8	Decrement delay value.
008C	98		GHI	R8	—
008D	3A8B		BNZ	DECDEL	Time up yet?
008F	8B		GLO	RB	Check to see if the last

Address	Code	Label	Mnemonic	Operand	Comment
0090	FFD6		SMI	D6	Morse digit has been output.
0092	C6		LSNZ		If it has, return to OUT.
0093	D3		SEP	R3	—
0094	C4		NOP		—
0095	OB		LDN	R8	Get BCD value.
0096	1B		INC	R8	—
0097	FCD6		ADI	D6	Add offset.
0099	A6		PLO	R6	Put result in R6 as Code pointer.
009A	F805		LDI	05	Put Morse character count in RE.0.
009C	AE		PLO	RE	—
009D	06		LDN	R6	Get Morse pattern via R6.
009E	BE		PHI	RE	Store it temporarily in RE.1.
009F	8E	CHR	GLO	RE	Have five Morse characters
00A0	3288		BZ	CODE	been output yet?
00A2	9E		GHI	RE	If not, get code pattern
00A3	2E		DEC	RE	out of temporary storage in
00A4	76		SHRC		RE.1 and shift character bit
00A5	BE		PHI	RE	into DF.
00A6	33AD		BDF	DASH	If bit = 1 load a dash.
00A8	F819	DOT	LDI	19	Otherwise load a dot.
00AA	A8		PLO	R8	
00AB	3BB0		BNF	EXIT	
00AD	F86B	DASH	LDI	6B	
00AF	A8		PLO	R8	
00B0	F8B6	EXIT	LDI	B6	Restore DOT/DASH sub pointer R7
00B2	A7		PLO	R7	to 00B6 and . . .
00B3	D7		SEP	R7	Gosub DOT/DASH.
00B4	309F		BR	CHR	Back for another character.
00B6	F835	DT/DSH	LDI	35	Load pitch value of tone.
00B8	7B		SEQ		"ON"
00B9	FF01	DECPT1	SMI	01	Decrement pitch value.
00BB	3AB9		BNZ	DECPT1	If "ON" time is not up, dec again.
00BD	F835		LDI	35	If it is, load pitch value again.
00BF	7A		REQ		"OFF"
00C0	FF01	DECPT2	SMI	01	Decrement pitch value.
00C2	3AC0		BNZ	DECPT2	If "OFF" time is not up, dec again.
00C4	28		DEC	R8	
00C5	88		GLO	R8	Has the character been sent yet?
00C6	3AB6		BNZ	DT/DSH	If not, go back for more.
00C8	F80A	SPACE	LDI	0A	Load value for space between
00CA	B8		PHI	R8	characters in R8.1.
00CB	28	DECSF	DEC	R8	Decrement space value.
00CC	98		GHI	R8	Is the space up yet?
00CD	3ACB		BNZ	DECSF	If not, decrement it again.
00CF	D5		SEP	R5	Return to CODE.
00D0	—	BINHRS			Binary Hours stored here.
00D1	—	BINMIN			Binary Minutes stored here.
00D2	—	10'sHR			BCD 10's Hours stored here.
00D3	—	1'sHR			BCD 1's Hours stored here.
00D4	—	10'sMN			BCD 10's Minutes stored here.
00D5	—	1'sMN			BCD 1's Minutes stored here.
00D6	1F	DIGIT TABLE			"0"
00D7	1E				"1"
00D8	1C				"2"
00D9	18				"3"
00DA	10				"4"
00DB	00				"5"
00DC	01				"6"
00DD	03				"7"
00DE	07				"8"
00DF	0F				"9"

**The BEST is still  
"made in U.S.A."**



# MIRAGE

**American made RF Amplifiers and Watt/SWR Meters  
of exceptional value and performance.**

• 5 year warranty • prompt U.S. service and assistance

## RF AMPLIFIERS

### 2 METERS-ALL MODE

**B23** 2W in=30W out \$89.95  
(useable in: 100 mW-5W)

**B108** 10W in=80W out \$179.95  
(1W=15W, 2W=30W) RX preamp

**B1016** 10W in=160W out \$279.95  
(1W=35W, 2W=90W) RX preamp

**B3016** 30W in=160W out \$239.95  
(useable in: 15-45W) RX preamp  
(10W.=100W)

### 220 MHz ALL MODE

**C106** 10W in=60W out \$199.95  
(1W=15W, 2W=30W) RX preamp

**C1012** 10W in=120W out \$289.95  
(2W=45W, 5W=90W) RX preamp

**C22** 2W in=20W out \$89.95  
(useable in: 200mW-5W)

### RC-1 AMPLIFIER

**REMOTE CONTROL** \$24.95  
Duplicates all switches, 18' cable

## WATT/SWR METERS

- peak or average reading
- direct SWR reading

**MP-1** (HF) 1.8-30 MHz

**MP-2** (VHF) 50-200 MHz

\$119.95

### 430-450 MHz ALL MODE

**D24** 2W in=40W out \$199.95  
(1W=25W)

**D1010** 10W in=100W out  
(1W=25W, 2W=50W) \$319.95

Available at local dealers throughout the world.

**MIRAGE**  
COMMUNICATIONS EQUIPMENT, INC.

P.O. Box 1393, Gilroy, CA 95020 (408) 847-1857

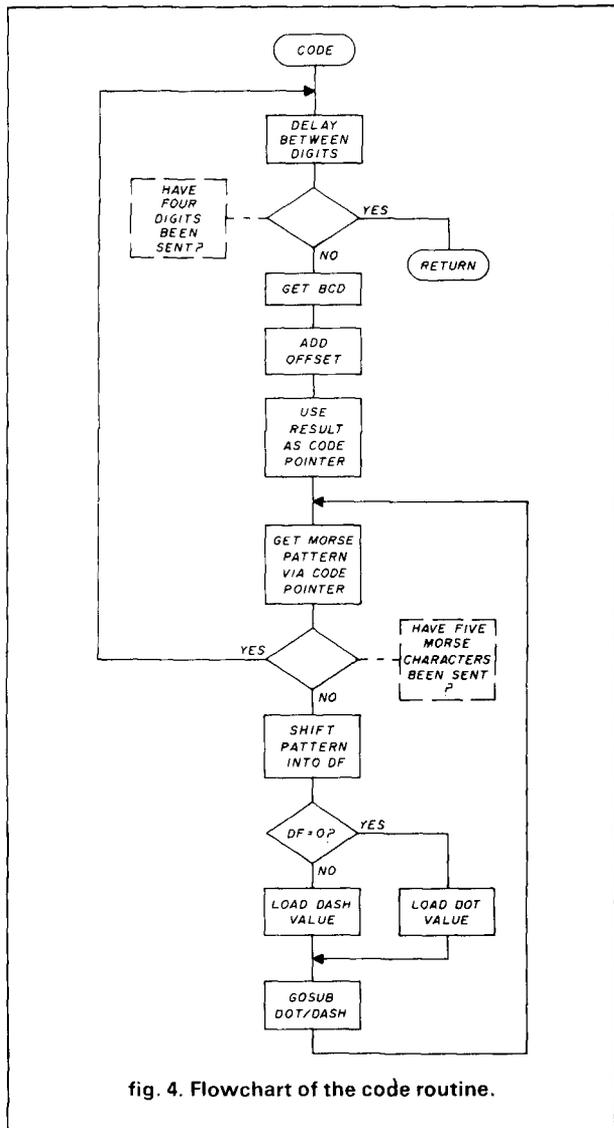


fig. 4. Flowchart of the code routine.

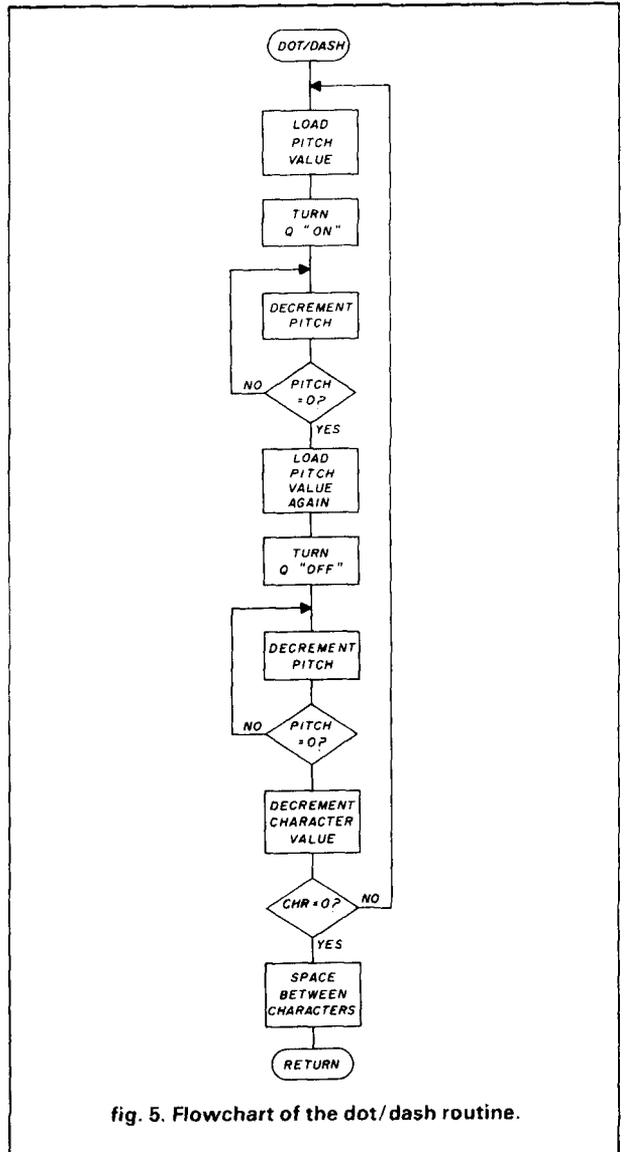


fig. 5. Flowchart of the dot/dash routine.

dot/dash (fig. 5). After the code routine fetches a dot or dash, this subroutine generates a tone of proper duration. (A dash is about three times longer than a dot.) The dot/dash routine also generates a space after each character. This space is a period of silence about as long as a dot.

### operation and fine-tuning

Before running the program, set the clock by entering the time. To do this, convert the hours and minutes values to hexadecimal. Then enter the hours at location 00D0 and the minutes at location 00D1. Now execute the program from location 0000. The program will give the time whenever the EF4 flag is activated, and automatically on the hour.

Although the program should keep accurate time, you may have to adjust its speed if your microprocessor's clock frequency is different. Do this by varying the value at location 0027. Also, you can tune the pitch of the tone by changing the values at locations

00B7 and 00BE. You can alter the speed of the Morse characters by changing the values for dot, dash, and space at locations 00A9, 00AE, and 00C9. Finally, if you prefer a twelve-hour format, change the value at location 0049 to 0C.

### summary

The basic feature of this program is the routine which converts BCD digits into Morse code characters, and in this case, the BCD digits represent time. However, the same routine with some modification could be used where the BCD digits represent something else, like temperature, pressure, voltage, or resistance. You would need more elaborate hardware in these cases, since they involve A/D conversion, but any measuring device could be made to talk with this method.

ham radio

# DUAL DRIVE TRIBANDERS


- 20, 15 and 10 meters • Wideband. Low SWR. No tuner needed
- Exclusive phased dual drive gives higher gain • Exclusive coaxial capacitors have lower losses, higher Q • Transmitter power is radiated not lost in the traps • Full power low loss balun. Gives improved beam pattern

TET Antenna Systems presents three full size trap multiband beams to meet every amateur need. 5 element, 4 element, and 3 element models all with the exclusive TET dual phased drive. This famous drive system originated with HB9CV and was perfected by JA3MP. When you buy TET dual drive you know you have the best. It has more gain - just like adding another parasitic element. And wide bandwidth so you can use your solid-state transceiver on both phone and CW without a tuner.

Only the highest quality materials are used throughout. All aluminum tubing is 6061-T6 alloy. Stainless steel fasteners are provided for all electrical connections. Tubing is cut and predrilled to precision tolerances for easy one afternoon assembly. Light weight and low wind area designs permit use of simpler support structures.

All models feature full 3 Kw PEP power handling, VSWR typical 1.5 or less across all of 20, 15 and, on 10 meters, from 28.0 to 29.2 MHz. Drive impedance is 50 ohms and maximum element length 27'. They accommodate masts from 1 1/2" to 2" diameter, withstand winds to 100 mph and are furnished complete with a low loss balun that easily withstands full rated power. For gain and front-to-back ratio specifications write or call the factory.

	HB35T	HB43SP	HB33SP
Boom Length:	24' 7"	19' 8"	13' 2"
Turn Radius:	18' 10"	16' 9"	15'
Wind Area Ft <sup>2</sup> :	7.9	6.6	4.7
Wind load lbs. @ 80 mph:	160	132	102
Boom Dia.:	2"	2"	1-5/8"
Weight, lbs.:	50	38	27
Price:	\$349.95	\$239.95	\$199.95
	+ shipping	+ shipping	+ shipping

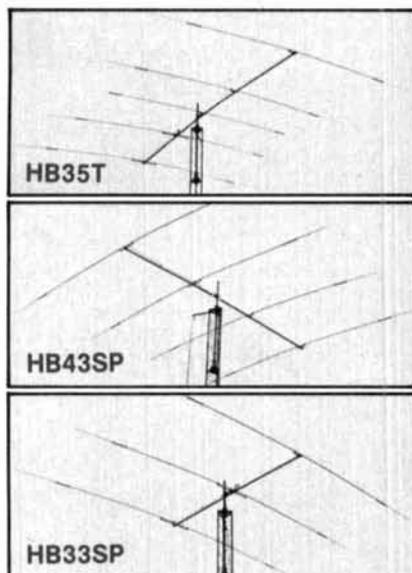

Send for free catalog describing these dual drive beams, our VHF Swiss quads, roof-mount towers, elevation rotators and more.

BY MAIL:




2775 Kurtz St., Suite 11  
San Diego, CA 92110-3171

BY PHONE: 619-299-9740

## TET ANTENNA SYSTEMS

178
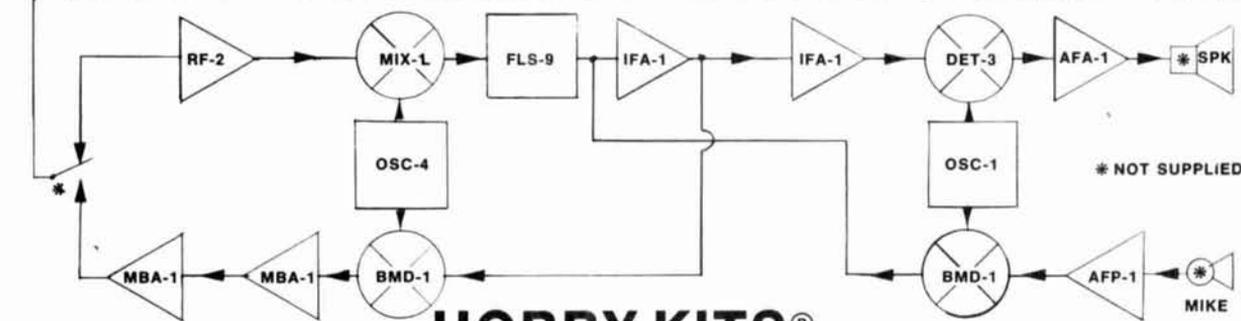
## BUILD THIS SSB TRANSCEIVER FROM OUR MODULES



## HOBBY KITS®

EXPERIMENT — LEARN ELECTRONICS; BUILD AND DESIGN YOUR OWN AM, FM, CW, OR SSB RECEIVERS, TRANSMITTERS AND ETC. WITH OUR MINI-LINEAR CIRCUIT KITS

All kits Come Complete With Etched and Drilled Circuit Boards and All Parts Needed To Function As Described

AFA-1 AUDIO AMP, LM-380 1-2 Watts 4-16 OHM Output	\$4.95	MBA-1 FREQ. MULT, Tuned Output Buffer-Mult-Amplifier To 250 MHZ	\$5.95
AFP-1 AUDIO PREAMP, Dual Audio Preamp — For Mike Etc.	\$3.95	OSC-1 CRYSTAL OSC, 100 KHZ — 20 MHZ Not Tuned	\$3.95
BMD-1 BAL. MIX, LM 1496 Mixer — S.B. Modulator Tuned Output	\$9.95	OSC-2 CRYSTAL OSC, Ov. 18-200 MHZ Tuned Output	\$4.95
DET-1 AM DET, Am Envelope Detector With AGC Output	\$3.95	OSC-3 VARIABLE FREQ OSC Varactor Tuned 455KHZ	\$5.95
DET-2 FM DET, LM 3065 FM Detector (455 KHZ or 4-11 MHZ)	\$7.95	OSC-4 VARIABLE FRFY OSC Varactor Tuned 4-11 MHZ	\$5.95
DET-3 SSB DET, LM 1496 SSB Detector (Needs OSC-1 or OSC-4)	\$9.95	PSV-1 POWER SUPPLY LM 723 With Pass Transistor, 3 amps max	\$7.95
IFA-1 IF AMP, CA 3028 30 DB Gain, Optional AGC (455 KHZ or 9-11 MHZ)	\$6.95	PLL-2 TONE DETECTOR LM567 PLL Tone Detector	\$5.95
FLS-9 SSB FILTER 9 MHZ/2 1 KHZ BW with USB XAL for OSC-1	\$49.95	RF/MIX-1 RF-AMP/MIXER CA 3028 — Tuned RF AMP/Mixer 1-100 MHZ	\$7.95
IFA-2 IF AMP, CA 3028 30 DB Gain 1-100 MHZ Optional AGC	\$6.95	RF/MIX-2 RF-AMP/MIXER 3N204 Tuned RF AM/Mixer 1 — 250 MHZ	\$7.95

MANY OTHER MODULES AVAILABLE

SEND \$2.00 FOR FULL CATALOG  
WITH CIRCUIT DIAGRAMS AND  
TYPICAL RECEIVER AND  
TRANSMITTER HOOK-UPS

ADD \$2.00 SHIPPING & HANDLING  
**MORNING DISTRIBUTING CO.**  
P.O. BOX 717, HIALEAH, FLA. 33011

COMPLETE SET OF MODULES TO BUILD A  
1-WATT SSB/CW MONO-BAND TRANSCEIVER  
LESS CASE, CONTROLS, PWR SUPPLY  
(12 VDC), SPK AND MIKE  
\$149.95 (Specify Band)

155

# SPECIAL PURCHASE!

## Hurry, limited quantity!

SAVE \$49!

### YAESU FT-208R handheld FM transceiver


Tremendous savings on this full feature handheld from Yaesu. The FT-208R is simply loaded with features such as split frequency coverage (144-146 MHz or 144-148 MHz) for non-standard repeaters, built-in autopatch and LCD frequency display. Fully synthesized design allows frequencies to be directly punched in from the keyboard. And up to 10 of your favorite frequencies may be memorized and then scanned. Up/down scanning is also provided in 5 kHz/10 kHz or 12.5/25 kHz steps as well as scanning between two frequencies. RF power output: 2.5 watts and 300 milliwatts. Supplied with NiCad battery pack and flexible rubber antenna. Requires 10.8V DC for external power. Don't let this one get away! Order today as supplies are limited!

**269.95** List Price 319.00 Item No. YAEFT208R  
Add 1.94 shipping & handling

### KENWOOD TR-8400 UHF FM mobile transceiver

Fully synthesized operation makes operation on 440 MHz as easy as 2 meters with the TR-8400! It covers 440-450 MHz in 25 kHz steps and features a bright, LED frequency display, twin VFO's and five memories with memory scan. A multicolored bar meter indicates received signal level and relative RF output. And the supplied microphone features an up/down control for manually scanning the entire band in 25 kHz steps, so you can safely change frequencies while you drive! The TR-8400 is very compact, measuring only 5.9" x 2.1" x 7.7" and comes with a quick release mounting bracket. RF power output: 10 watts and 1 watt. Requires 13.8V DC for operation. Special purchase. Limited quantities!

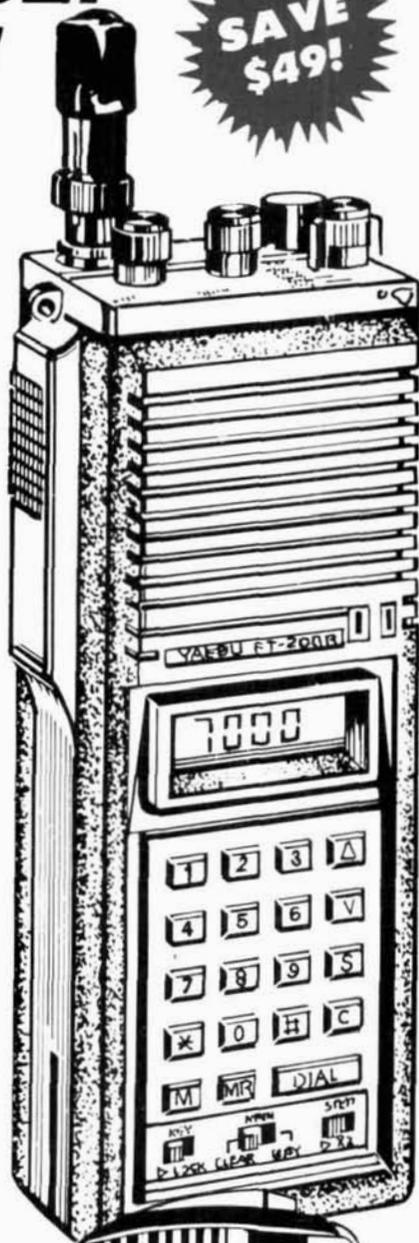**349.00** List Price 499.95 Item No. KENTR8400  
Add 2.14 shipping & handling



# YAESU

SAVE \$150!



# Long's Electronics



# Complete home satellite TV system only \$1595!

## 10 FOOT PARABOLIC

List Price \$2495  
Item No. MISSY97  
Shipped Freight Collect

### What the system will do:

Enables you to receive up to 60 channels of satellite TV programs delivered directly to your home receiver. Movies, sporting events, news, religious programs, other TV stations and much more.

### What the system includes:

1. A 10 foot parabolic antenna constructed of reflective metal bonded with fiberglass. Weather resistant and virtually maintenance-free. Comes in four sections for ease of shipment and assembly.
2. Polar mount complete with azimuth and elevation adjustments for precise satellite-to-satellite tracking. Patented linkage allows antenna to travel from horizon to horizon.
3. LNA mount with rotor and control console for remote polarity adjustment. Tubing for mount legs not included.
4. KLM Sky Eye V satellite receiver with downconverter. Downconverter mounts outdoors, near the LNA and linked to receiver by remote cable. Receiver features the latest single conversion electronics and SAW filter for superb video. Also has large signal strength meter, video invert and variable audio subcarrier tuning (5.5-7.5 MHz). Optional RF modulator available.
5. Drake 120° low noise amplifier. Takes the weak signals gathered by the parabolic antenna and boosts them to a level usable by the downconverter. Uses GaAs FET transistors for maximum performance. Powered via coax feed line. Complete weatherproof.
6. Scalar feed horn. Delivers 0.5 dB more gain than conventional rectangular types. Virtually eliminates system noise.

**Note:** Interconnecting cables between components not included. Your VCR's RF modulator can be used with this system, otherwise an RF modulator will be required. Approximate cost, \$59.



## Read all about Satellite TV!

9.95

Add 1.36 shipping & handling  
Item No. BOOTAB1409

**At last! A complete guide to satellite TV!**  
"Build a Personal Earth Station for Worldwide Satellite TV Reception"

A complete guide to gaining access to the large amount of TV programming available from satellite transmissions. You can choose to build your own system or purchase one ready-to-operate, and both ways are thoroughly covered in this book. It begins with a review of basic television fundamentals and satellite transmission and reception. Building your own system is covered and the complicated task of installing the antenna and aiming it to pick up the signals you want is simplified. There's even a complete list of available satellite programming.




Call Toll Free **1-800-633-3410**

IN ALABAMA CALL 1-800-292-8668 9 AM TIL 5:30 PM CST, MONDAY THRU FRIDAY  
More Details? CHECK-OFF Page 129

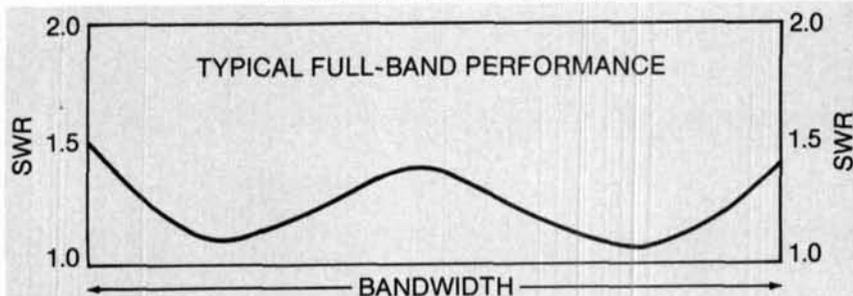
# WORK THE FULL-BAND<sup>®</sup>

free of narrow band antenna limitations  
WITHOUT ANTENNA TUNERS



MHz	MODEL NUMBER	MHz
1.77	FB-160	2.02
3.5	FB-75/80	4.0
6.7	FB-40	7.6
13.2	FB-20	15.1
19.8	FB-15	22.6
26.9	FB-10/11	30.7
48.5	FB-6	55.5

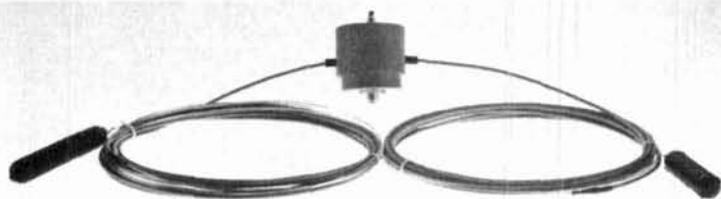FULL-BAND<sup>®</sup> MONOBAND DIPOLES  
EXTREME BANDWIDTH WITHOUT COMPROMISE



All Full-Band Antennas look alike, except for length. Pictured is the model FB-40 which, when extended, measures 66'3" from tip to tip (including end insulators).

- Patent Applied for Design Self-Compensates for Frequency Change.
  - No Resistors, Capacitors or Power Robbing Networks.
  - Linear Response Assures Maximum Efficiency from Microvolts to Full Legal Power—and Minimum Interference with Other Services.
  - Ideal Antennas for Use with Automatic Power Shutdown Rigs.
  - Tested and Approved By: Ham Radio Magazine, CQ Magazine, QST Magazine (ARRL)
  - Install as Flat-Top, Inverted "V", Sloper, Phased Array, etc.
  - Shipped Complete, Ready to Connect to Your 50Ω or 72 Ω Coaxial Feedline.
  - UPS or Postal Shipping Paid in Continental United States
- Use MC, Visa, Check or Money order.

### FACTORY DIRECT PRICES

Model No.	Length	Shipping Wt.	Price
FB-160	248'9"	11 lbs.	\$179.95
FB-75/80	126'7"	6 lbs.	134.95
FB-40	66'3"	5 lbs.	109.95
FB-20	32'	4 lbs.	71.95
FB-15	24'6"	3 lbs.	66.95
FB-10/11	16'6"	3 lbs.	61.95
FB-6	9'	3 lbs.	57.95

Prices include shipping in continental U.S.—Canada, HI and AK add \$5.00 shipping and handling. CA residents add sales tax. Write or phone for specifications and prices for antennas for other frequency bands.

**SAC** SNYDER ANTENNA CORPORATION  
250 East 17th Street • Costa Mesa, CA 92627



Telephone orders—24 hours a day, seven days a week: (714) 760-8882



# YAESU

## FT-ONE



- Three selectivity positions for CW (two for FSK) using optional filters
- 73 mHz first IF
- 0.3 uV sensitivity
- full break in
- Curtis 8044 keyer available as option
- front panel keyboard
- ten VFO's
- one year factory warranty

**Madison Price - \$2300.00**  
with RAM, FM, 4 Filters

# MADISON

## Electronics Supply

TOLL FREE - ORDERS ONLY

**1-800-231-3057**

**(713) 658-0268**

1508 McKinney  
Houston, Texas 77010

✓ 153

1982-1983

## AMATEUR RADIO

# CALL DIRECTORY

THE BARGAIN AT **\$14.95** Plus Shipping

A no frills directory of over 411,000 U.S. Radio Amateurs. 8½ x 11, easy to read format. Completely updated.

Also available for the first time ever—

(Alphabetically arranged. Sold separately.)

**Geographical Index**

by State, City and Street No. and Call

**Name Index**

by Name and Call

Ordering Information:

- Directory—\$14.95
- Geographical Index—\$25.00
- Name Index—\$25.00

Add \$3.00 Shipping to all orders.

Dealers/Clubs inquiries welcome

Send your order—enclosing check or money order in U.S. dollars to:

**Buckmaster Publishing**  
70-B Florida Hill Road  
Ridgely, CT 06877 U.S.A.

✓ 204

# a state-of-the-art Touchtone<sup>®</sup> decoder

Using Silicon Systems  
Inc.'s  
single-chip solution

Silicon Systems Inc.'s DTMF (dual-tone, multiple frequency) decoder IC is revolutionizing the way Amateurs use TouchTones<sup>®</sup>. With this device, it's possible to build a decoder with as few as three ICs, and the resulting circuit (see photo) is small, requires little power, and is very reliable.

## a brief history

It wasn't too long ago that every DTMF decoder used and built by Amateurs was made with the NE567 phase-locked loop-tone decoder. At the time, that was the only way to decode dual-tone audio into a useful digital signal; it required tedious adjustment of a potentiometer for every frequency and that adjustment would rarely remain stable when temperature varied.

About five years ago, Mostek released a product that eliminated all the adjustments and made DTMF decoding relatively simple, but rather costly. In the Mostek system, the incoming audio signal is split into the two components of DTMF (i.e., the high-frequency group and the low-frequency group). These

two components are then limited and squared before being applied to the Mostek DTMF decoder. Although the cost of the splitting filters is high, this remains a superior system to multiple 567s, as the dynamic range is tremendously improved and no adjustments are necessary.

The next logical step in DTMF decoders was to put the filters, limiters, and squarers on the same chip as the decoder. This was accomplished by Silicon Systems Incorporated (SSI) with their SSI201, a single-chip solution that requires only two small bypass capacitors and a 3.58 MHz color-burst crystal.


## operation of the decoder

The major problem was to incorporate rather large capacitors and resistors needed for the filters onto the silicon chip. The largest size capacitor that can be integrated onto a chip is about 100 pF, and even this size requires a large area. Large resistors are not realizable for the same reason. However, a small capacitor can be made to perform, electrically, like a large resistor.

Fig. 1 illustrates the principle of a switched capacitor to realize a large resistor. At time zero, the capacitor is connected to voltage  $V_1$  and the capacitor charges toward the value  $Q = CV_1$ . At some later time,  $t_c$ , the capacitor is switched to voltage  $V_2$  and the value of the charge is  $Q = CV_2$ . The equations in the figure show the mathematics used to manipulate the values; the last equation is the most interesting:  $R = 1/Cf_c$ , in other words, a large resistor can be made (electrically) by just using a small capacitor and switching it between voltages at a very fast rate!

This led to the development of the switched-capacitor filtering used in the SSI201 DTMF decoder. (MOS transistors are used as the switches.)

The block diagram of the entire decoder is shown in fig. 2. As in the multiple-chip Mostek system, the audio is first split into upper and lower bands. These signals are further filtered to determine the two tones present. Next, the output-decoder circuitry converts this information to digital form, and produces BCD (binary-coded decimal), or optional 2-of-8 outputs. A 3.579545 MHz color-burst crystal is used for the frequency references as well as for the switched-capacitor filter networks.

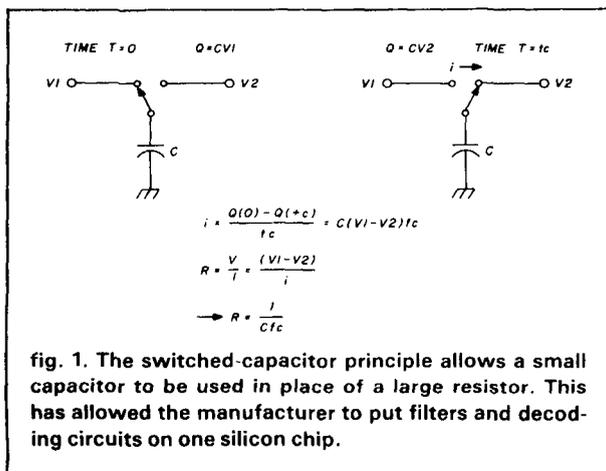

By Mark Forbes, KC9C, 1000 Shenandoah Drive, Lafayette, Indiana 47905

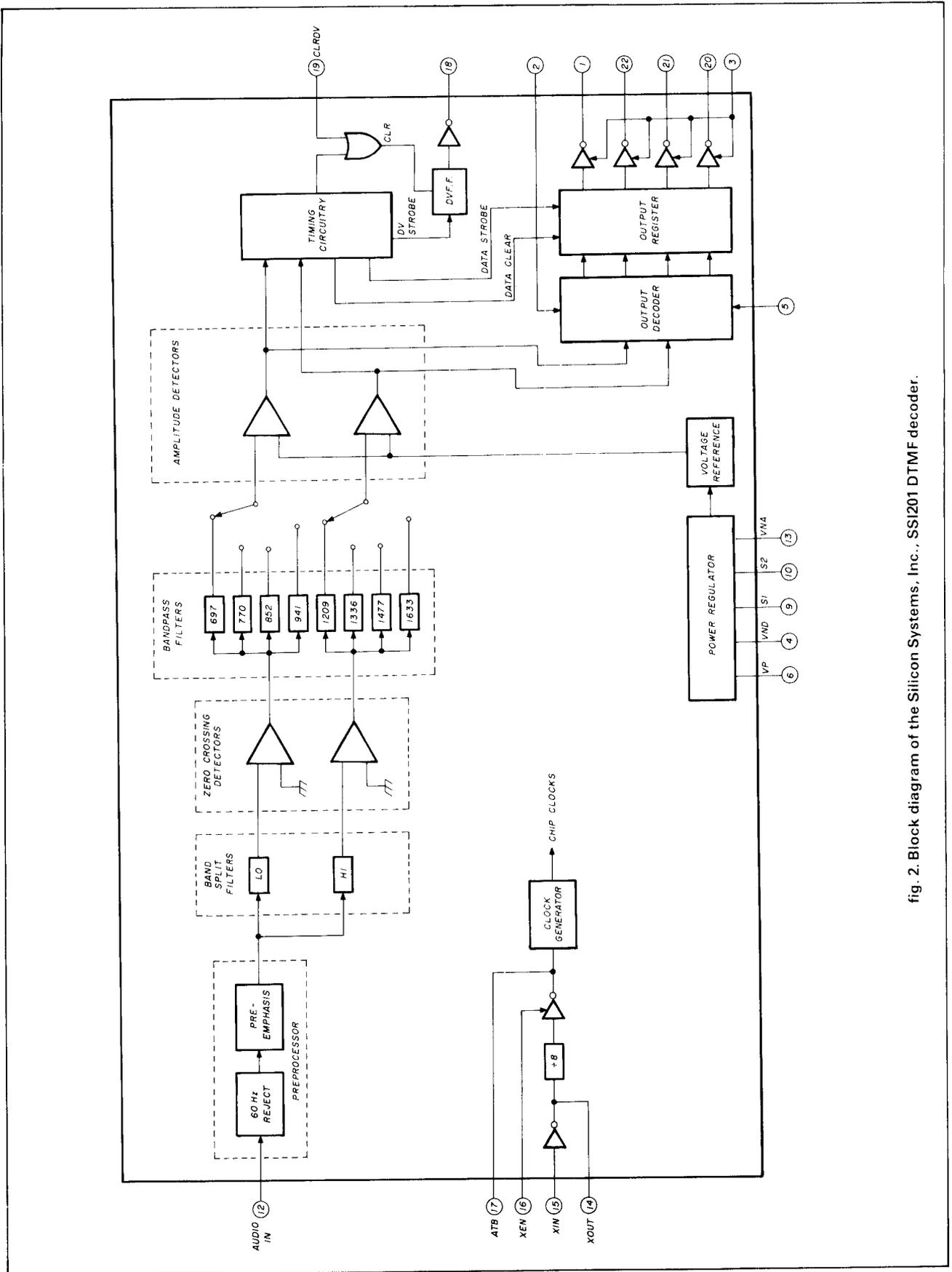


fig. 2. Block diagram of the Silicon Systems, Inc., SS1201 DTMF decoder.

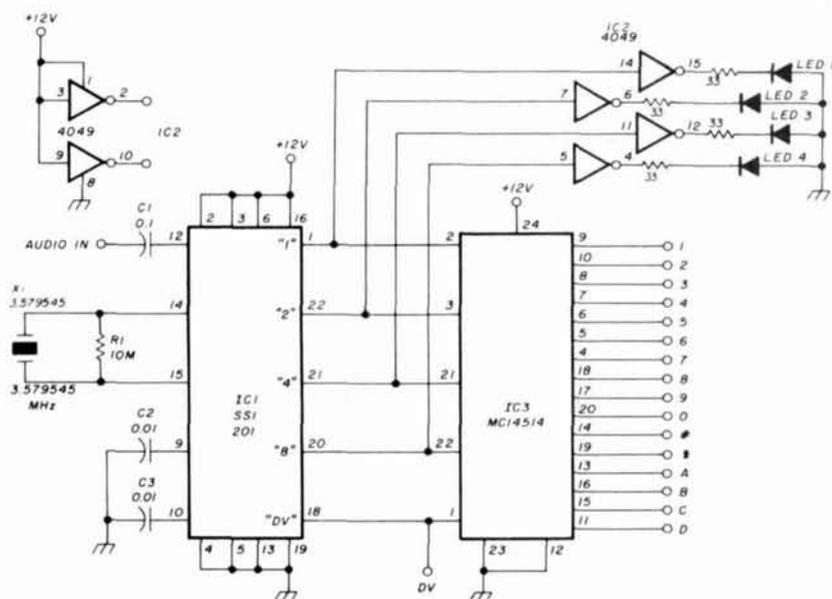


fig. 3. Schematic diagram of the author's completed decoder circuit. The CMOS signals are all 12-volt levels, so a converter is needed if the decoder must drive TTL.


## the complete circuit

To make the SS1201 easier to interface to remote-control and repeater circuits, I have added two IC and four LEDs in this DTMF decoder design. The schematic diagram is shown in **fig. 3**. Audio input is coupled to the SS1201 through a  $0.1 \mu\text{F}$  disk capacitor. The BCD output of the decoder is further decoded into individual "tone-pad" digits by an MC14514B 4-to-16 line demultiplexer.

One useful signal available from the decoder is the DV (data valid) signal. This signal goes high when the output data is in a predefined window of time, and is useful in determining when to sample the outputs of the MC14514 (although these outputs are latched, so the last data remains on the outputs until new data is presented).

As a convenience, LEDs that show the binary value of the decoded output, are included (note: the values for \*, 0, and # are 11, 10, and 12, respectively). A CMOS 4049 inverting buffer is used to drive the LEDs and remove the load from the SS1201.

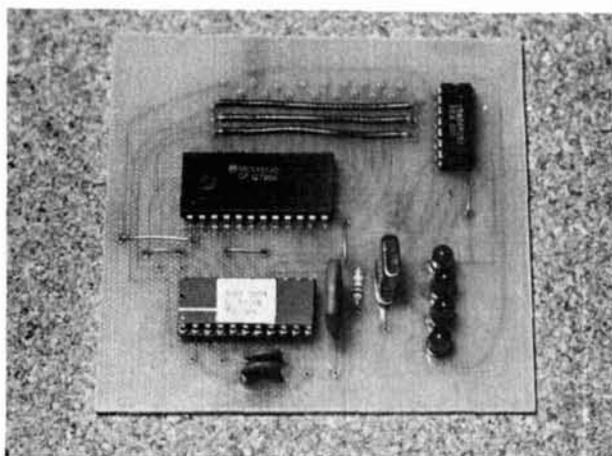All the ICs in the project are powered from 12 Vdc. A note of caution here — the SS1201 requires 12 volts and *not* 13.8 volts as found on many power supplies. A small IC voltage regulator will provide the proper 12 volts if you don't have such a power supply (an LM340-12 is one such regulator). If the outputs are to be interfaced to 5-volt logic such as TTL, a



The DTMF decoder circuit.

voltage converter circuit such as that shown in **fig. 4** can be employed.

Construction of the circuit is very simple, using the printed circuit artwork provided in **fig. 5**. All that is necessary is to solder the ICs and apply 12 volts. Sockets are recommended to keep the heat of soldering off the ICs and to facilitate replacement should any of the components fail.

## applications

The applications of a DTMF decoder seem almost limitless, especially when no adjustments are neces-

sary. The most obvious application is in repeater control. This circuit is highly reliable and not subject to degradation by temperature or variation of signal levels. These features, coupled with the compact size of this circuit, make it perfect for use in repeaters.

A reliable circuit like this one also opens the door to an underexplored facet of Amateur radio: remote control. Remote control of more than just repeaters is allowed by the FCC. In fact, almost anything can be remotely controlled via Amateur radio. Types of applications include remote HF stations, models, or even your house lights.

Another good use of the DTMF decoder is in autopatch circuits. Most autopatches couple the DTMF tones directly to the telephone line from the receiver.

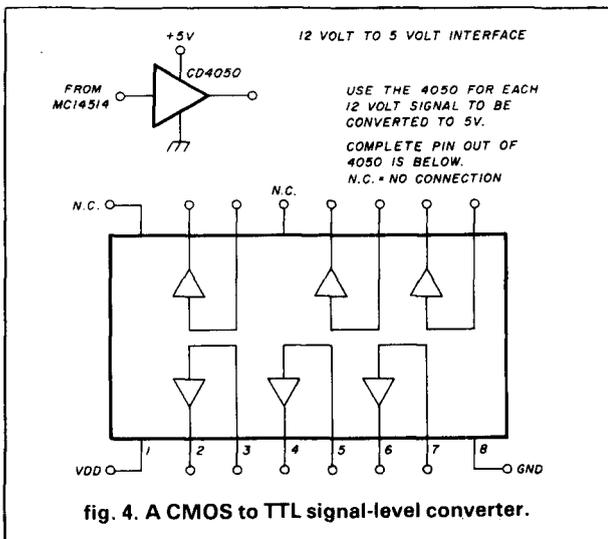


fig. 4. A CMOS to TTL signal-level converter.

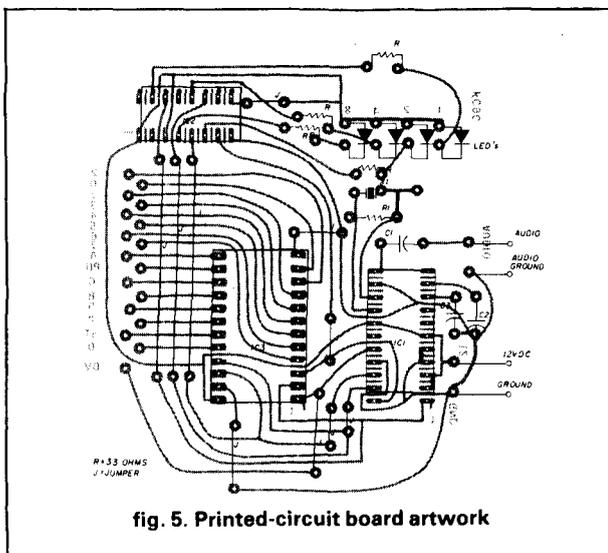


fig. 5. Printed-circuit board artwork

table 1. Parts and Prices List.

part	description	source	price
IC 1	SSI201 DTMF decoder	SAI Marketing*	60.00
IC 2	4049 inverter	Digikey	0.47
IC 3	MC14514 (4514B)	Digikey	1.99
LED 1-4	Light Emitting Diodes	Radio Shack	4 for 1.58
C 1	0.1 uF disk capacitor	Radio Shack	2 for 0.49
C 2,3	0.01 uF disk capacitor	Radio Shack	2 for 0.39
R 1	10 Megohm resistor	Radio Shack	2 for 0.19
X 1	3.579545 MHz crystal	Radio Shack	1.99
PCB	printed circuit board	Author	8.50
Total Cost			67.10
Total w/PCB			75.60

Note: Complete parts kits are available from the author for \$75.60 plus \$1.00 shipping. Or, the ICs and/or PCB may be purchased individually at the listed price plus \$1.00 shipping.

\*The address of SAI Marketing is: SAI Marketing, Attn. Jim Taylor, 5610 Crawfordsville Road, Indianapolis, Indiana 46224.

This results in two things: the user needing to adjust his TouchTone pad to tight telephone company specifications, and frequently misdialled numbers. By decoding the signal first, then re-encoding with a DTMF generator chip, the telephone line will always have a perfect and precise tone for dialing. And, with the wide dynamic range of the SSI201, adjustment of the user's tone pad is almost never necessary. An additional problem can also be solved: in areas where DTMF dialing is not yet available, a pulse dialer chip in conjunction with the SSI201 can provide autopatch functions.

## conclusion

The parts list in table 1 gives the price and availability of each of the parts at the time of writing. Additionally, I have complete parts kits available for the prices shown, so there should be no trouble in finding all the necessary parts.

The SSI201 is, in my opinion, the best DTMF decoder introduced to date. The Amateur press seems to be behind in the DTMF decoder field. In fact, one book on repeaters published in 1980 still showed 567 circuits for decoding DTMF. The switched capacitor has revolutionized the DTMF scene, and will soon find its way into other areas.

## references

Jacobs, G.M., et. al., "Touch-tone decoder chip mates analog filters with digital logic," *Electronics Magazine*, February 15, 1979, McGraw-Hill, Inc.

Silicon Systems Incorporated, "Monolithic Dual-Tone Multi-frequency Receiver Application Note," May 1980.

ham radio

**FILAMENT TRANSFORMERS**

PRI V.	SEC V.	SIZE	WT	PRICE
117	5 @ 9.75 A	29 KV Ins. 6x5x8	10	\$29.95
115	6.6 @ 25 A	4x5x6	15	\$19.95
115	6.6 @ 18 A	4x5x6	12	\$13.95
115	6.6 @ 10 A	3x4x6	8	\$ 9.95
230	6.3 @ 30 A	4x4x6	10	\$15.95

**PLATE TRANSFORMERS**

120	1510 @ 382 Ma	4½x4½x8	15	\$39.00
208 3	phase with taps to allow sec. to be varied from 5900 to 7700 VDC @ 600 Ma out of rect.	11½x11½x13	100	\$175.00
115	#1-600 CT @ 450 Ma #2-580 CT @ 220 Ma	5x4½x8	12	\$19.95
208/ 230/ 240	5700 @ 1.2 A	9½x9½x13	75	\$175.00
215/ 230/ 245	4,000/4,450 @ 26 KVA	38x16x24	845	\$575.00
115	690 @ 450 Ma (Production quantities in stock)	4x5x6	12	\$ 9.95
115/ 230	803 @ 735 Ma. Hypersil core. (Use two of these for a cool KW)	6x5x6½	17	\$59.00

**POWER TRANSFORMERS**

115	#1-1,000 CT @ 220 Ma #2-5.1 @ 2 A #3-5.1 @ 4 A	4x5x6	15	\$ 9.95
115	#1-840 CT @ 230 Ma #2-620 CT @ 25 Ma #3-5 @ 2 A #4-6.3 @ 5.5 A #5-6.3 @ 5 A #6-6.3 @ 5 A	5x6x7	10	\$19.95
115	#1-45 @ 50 Ma #2-68 @ 3 A #3-34 CT @ 25 A #4-20 CT @ 2 A	7x6x6	43	\$24.50
115	#1-105 @ 75 Ma #2-475 @ 200 Ma #3-6.5 @ 9 A #4-6.3 @ 3.3 A #5-6.3 @ 2A	4x5x3	7	\$ 9.95

**FILTER CHOKES**

25 H @ 770 Ma, DC resistance 70 ohms, 13 KV insulation	8x10x9	50	\$69.00
4.5 H @ 950 Ma, 25 KV ins.	10½x12x15	150	\$125.00
2 H @ 130 Ma, DC resistance 155 ohms, 2,000 V ins. (Production quantities in stock)	1x1½x3	1	\$2.95
5 H @ 500 Ma, 700 V ins.	4x5x6	15	\$22.00
4 H @ 350 Ma, Collins	3x3x4	4	\$3.95
1 to 1.5 H @ 1.2 A swinging choke, 18 KV insulation.	13x17x17	248	\$125.00
2 H @ 1.6 A, 15 KV insulation (Production quantities in stock)	6x7x10	45	\$49.00

ATTENTION INDUSTRIAL PLANTS, UNIVERSITIES AND RESEARCH LABS: We are specialists in custom design and fabrication of power oscillators for induction heating, crystal growing, etc. Contact us with your requirements.

**J.S. BETTS COMPANY**

P. O. BOX 426 - Phone: (404) 964-3764  
FAIRBURN, GEORGIA 30213

✓ 114

**CAPACITORS**

MFD	VV	SIZE	WT	PRICE
4	25,000	7x14x26	165	\$175.00
45	1500	4x5x7	5	\$ 29.00
10	2000	4x4x4	3	\$ 19.95
10	660 AC (2000 DC)	2x3x4	1	\$ 6.95
45	330 AC (1000 DC)	2x3½x7	2	\$ 5.95
4	4000	4x4x11	6	\$ 29.95
2	10,000 Aerovox	13¼x4x17½	40	\$ 29.00
.026	32,000 GE	16x7x20	40	\$ 49.00
.01	1200 V mica			\$1.95
.01	2500 V mica			\$2.95
50 pf	15 KV or 40 pf 15 KV ceramic, Centralab type 857			\$2.95

**VARIABLE VACUUM CAPACITORS**

Jennings UCSL-1000, 3 KV, 3" diam, extends 7" behind panel	\$139.00
Jennings UCSXF-1000, 10 KV, 5" diam, 9" long	\$375.00
Jennings UCSXF-1200, 10 KV, 5" diam, 9" long	\$375.00



Energy Labs 7-200 pf, 7.5 KV. ¼ inch shaft, 3" diam., extends 5½" behind panel. Equivalent to Jennings CHV1. (Production quantities in stock)

\$159.00

**MISCELLANEOUS**


KNOBBS, 1¼" diam, for ¼" shaft, with spinner handle	\$2.00
KNOBBS, 2¼" diam, for ¼" shaft, with spinner handle	\$4.00
Squirrel-cage blower, 115 V, 50/60 Hz, 3150 RPM, with 4 MFD capacitor. Eastern Air Devices. 10" diam x 5"	\$39.95
Adjust-a-volt variable trans. 120 V input, 0-140 V out @ 5.5 A	\$29.95
Daven fixed attenuator, 6db, with type N connectors, 50 ohms in and out. 1x1x3¼	\$5.95
Isolation transformer, 120 V to 120 V @ 2500 W. 7x12x8, 125 lbs.	\$89.00
Autotransformer, 115/120/125 V to 230 V @ 3,000 W. 8x8x11, 86 lbs	\$49.00
C-111 telephone repeat coil, 600/600 ohms	\$25.00

ITT 7C23 (5680) rated 2.5 KW plate dissipation up to 30 Mhz. Ideal for linear amplifiers or industrial power oscillators. Fil. 13 volts @36 A. Production quantities in stock.  
New JAN surplus \$149.00  
Fil. transformer \$110.00


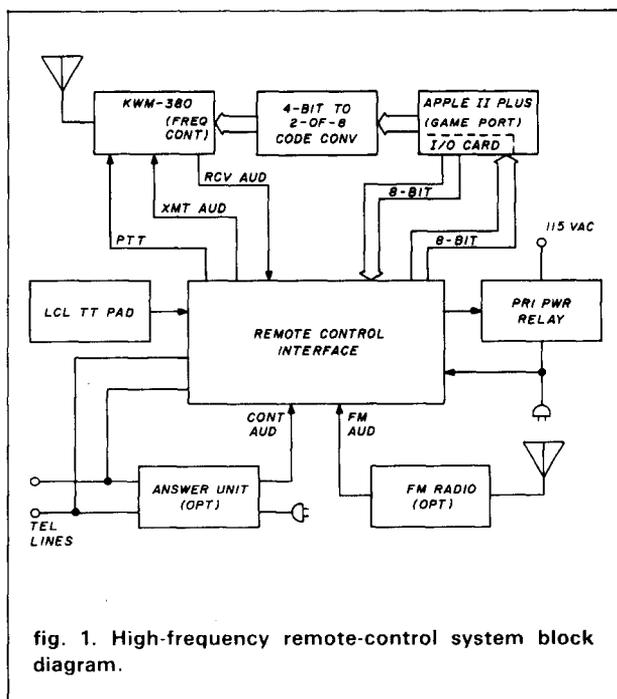
# remote control hf operation

An Apple II and Collins KWM-380  
talk to each other  
via the telephone



You can have remote high-frequency radio operation from a TouchTone™ telephone. In this article I explain this design, including the interface used to control the radio and computer; the interface plugs into the radio and computer without modification to either. A remote operator can thereby use a telephone to turn on and off primary power; use a private access code; tune the radio to any discrete frequency or scan up and down; transmit; and have optional fm radio capability. The interface has a safety shutdown feature in case the power or telephone is interrupted.

The remote system is illustrated by the block diagram in fig. 1. The center of the system is the interface control, which includes a phone patch, a dual tone multi-frequency (DTMF) decoder, audio amplifiers, and control logic. I use a Rockwell-Collins KWM-380 transceiver with the control interface option, and an Apple II Plus microcomputer with an eight-bit input/output card. A regular phone-answering unit detects the telephone ring. A ring-detection circuit could be incorporated into the interface control, but I prefer having a tape recorder tied to the system for logging. A twelve-button TouchTone™ keypad provides local control. A primary power relay, that includes transient protection, turns on the KWM-380 and the Apple. The phone-answering unit and interface control remain on at all times. An interface device that connects between the Apple's game port and the KWM-380's frequency-control interface connector provides frequency control. An optional fm audio-decoder is also included to provide additional system control and operation from a VHF/UHF fm radio.

By Dick Sander, K5QY, 110 Starlite Drive, Plano, Texas 75074

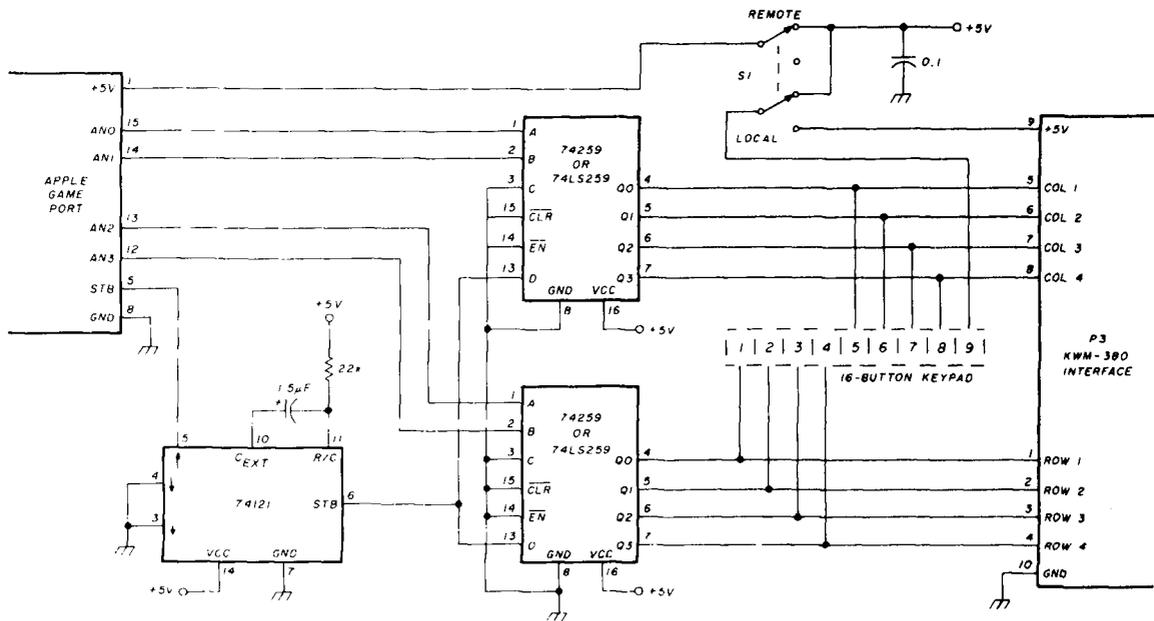


fig. 2. Apple II to KWM-380 interface schematic. It converts a four-bit binary code to a 2-of-8 code with a strobe to load the data into the radio.

The frequency-control circuitry is in a case that contains the KWM-380's sixteen-button keypad. The case also contains a switch that selects +5 volt power from either the radio or the Apple. There are two reasons for interfacing the frequency control separately: the first is that this portion can be a separate project; and the second is that fewer parts are required to build an interface compared to an I/O card to insert into one of the Apple's card slots. The purpose of the interface device is to convert the four binary-outputs and strobe available from the Apple's game port to an eight-bit two-of-eight code required by the KWM-380 (see fig. 2 for the schematic diagram of the frequency interface). The output of each 74259 decoder is tied directly with the sixteen-button keypad to allow frequency input to the radio while the Apple is running. The negative strobe of the Apple triggers a 74121 one-shot and clocks the data into the radio. If only frequency control from the Apple II is going to be used, lines 2000 through 2650 of the program listing form a routine for operating only frequency control for the KWM-380; delete lines 2030 through 2070 and replace them with a **GET F** statement from the keyboard.

The remote control interface is the heart of the system; fig. 3 is its functional block diagram and fig. 4 is its schematic. The phone-answering unit has an earplug that I use to connect the telephone audio to the interface control. After the unit hooks onto the telephone line and sends its outgoing message, it

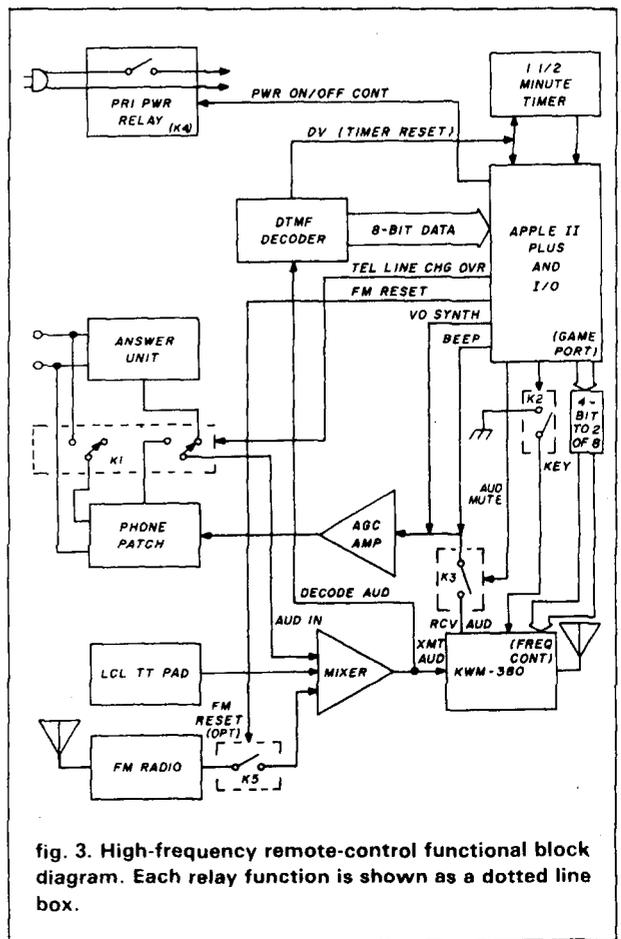


fig. 3. High-frequency remote-control functional block diagram. Each relay function is shown as a dotted line box.

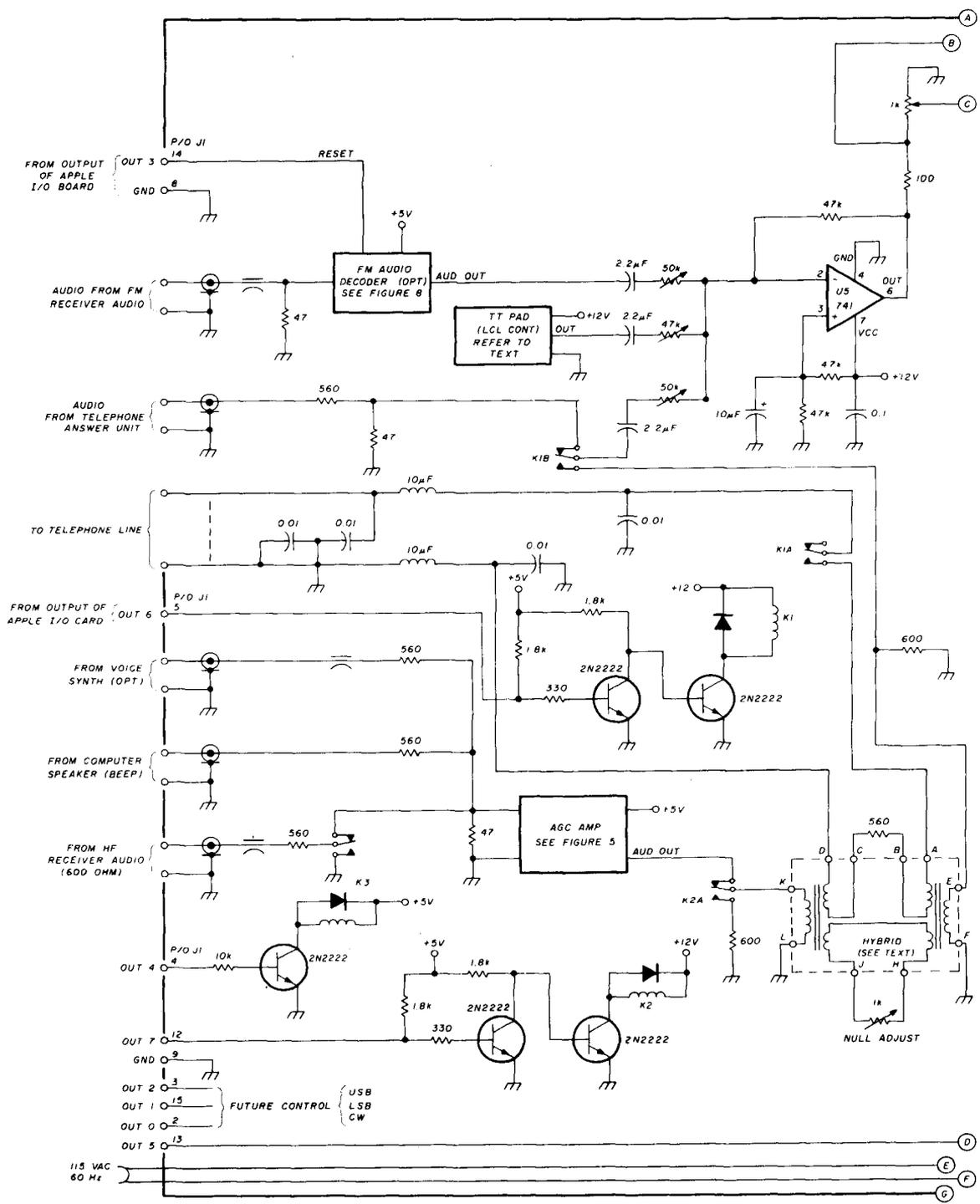


fig. 4. The interface-control schematic diagram. Note that the AGC amplifier and optional fm audio decoder schematic are shown separately.



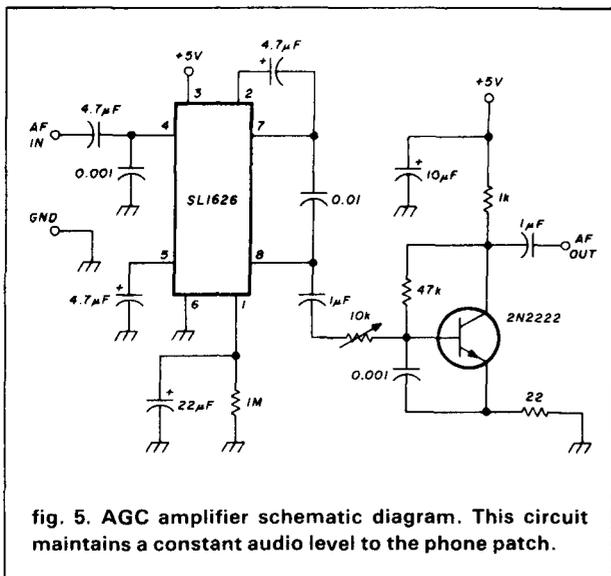


fig. 5. AGC amplifier schematic diagram. This circuit maintains a constant audio level to the phone patch.

allows twenty seconds for an incoming message. During this time you must access the system. The incoming audio is tied through the normally closed contacts of relay K1B directly to U5, a 741 operational-amplifier. U2 is an SSI 201 DTMF CMOS receiver that decodes the incoming audio tones, and U3, a CMOS-to-TTL buffer that passes the data to the eight-bit TTL input of the Apple's I/O card. If the proper access code is present, the output of the Apple pulls in relay K1 and connects the telephone line to the phone patch. The answering unit will drop off by now.

The phone patch contains a transformer-type hybrid with a balancing network. The hybrid transformers that I used were surplus, and no part number is available; the builder must decide upon his own transformers. I'm using a 1-kilohm pot for null adjustment. Some situations may require some series capacitance to null out the telephone line inductance; the system will not work without proper balance. The DTMF decoder requires at least a 12-dB signal-to-noise ratio, which is why a null is important. An AGC amplifier is needed to maintain a constant level to the hybrid. If you were to measure the output of your receiver, you would find the audio level varies by as much as 20 dB. Fig. 5 is the schematic diagram of the AGC amplifier I'm using. It uses an SL1626 voice-operated gain adjusting device (VOGAD) that drives a simple 2N2222 transistor amplifier. The output is extremely constant and maintains proper audio level. Because the VOGAD operates at low levels, resistive dividers are used to reduce the input to the proper levels. The AGC amplifier controls only outgoing audio, which includes the hf received, the beeps, and possibly a voice synthesizer. Throughout the program, beeps from the Apple's speaker tell the

operator where he is during operation. For connecting audio to the system, I couple to the Apple using a 0.47-µF capacitor wrapped between the audio high side of the speaker connector and the interface. For audio low, I connect the grounds together. In the Apple, the speaker is dc-coupled to +5 volts, so be careful when connecting to the Apple's speaker connector (refer to the Apple II reference manual). Incoming audio (tones and voice) from the phone line via the hybrid, the local TT keypad, and optional fm control go to U5, the audio mixer. The output of U5 goes to the DTMF decoder and to the KWM-380 transmit audio.

The control-logic portion of the interface control consists mainly of a timer, a latch, and four control relays. Timer U4, a 555, stays on for one and one-half minutes. It is reset from the data valid (DV) output of U2. If there isn't any key activity before timeout, relays K1 (phone line) and K2 (transmit/receive) drop off. Latch U1, a 4001 quad NOR gate, enables relay K4 (primary power) and turns on the radio and Apple. A shut-off command from data-out 5 causes relay K4 to drop out when U4 times out, and the radio and the Apple will turn off. Relay K3 mutes the high-frequency-received audio when a command from data-out 4 appears. Muting is used when you wish to hear only the beep or voice synthesizer (if used). Relay K2 is the transmit key relay; it sends a ground to the KWM-380's keyline and maintains a 600-ohm load across the input side of the hybrid during transmit. Table 1 gives a detailed description of each data line and its address (I/O card in slot 4) from BASIC.

Fig. 6 is the schematic for the primary power-relay. It contains varistor transient suppressors and

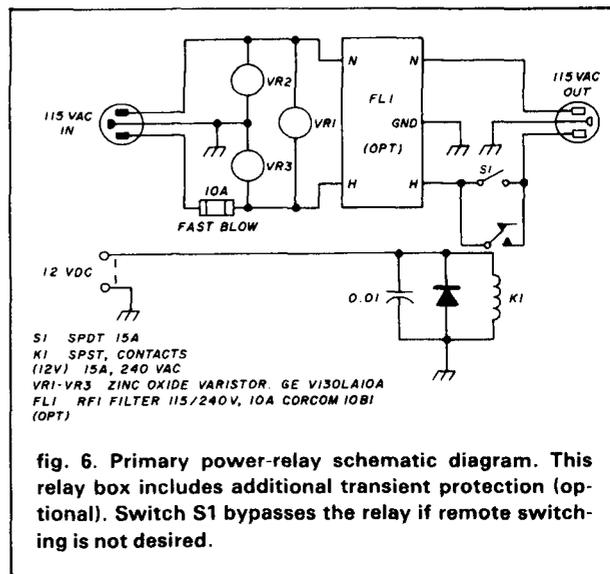


fig. 6. Primary power-relay schematic diagram. This relay box includes additional transient protection (optional). Switch S1 bypasses the relay if remote switching is not desired.

table 1. This table lists the I/O data lines used to interface the KWM-380 and Apple II and gives a description and address from BASIC of each.

data line	description	computer address (slot 4) from BASIC
input: D0-D7	Parallel eight-bit binary input, MSB is data valid (DV)	PEEK (50176)
output: out 7	Pulls in transmit/receive relay K2	POKE 49359,1 on POKE 49351,0 off
out 6	Pulls in telephone relay K1	POKE 49358,1 on POKE 49350,0 off
out 5	Sets input bit to latch U1C and U1D to turn off primary power relay K4	POKE 49347,0 on POKE 49355,1 off
out 4	Pulls in high-frequency receiver mute relay K3	POKE 49356,1 on POKE 49348,0 off
out 3	Resets the fm decoder	POKE 49349,0
out 2-out 0	Future control to be used to change the KWM-380 mode, between USB, LSB, and CW	
game port: AN0		POKE 49241,0 on POKE 49240,0 off
AN1	Parallel four-bit binary code to the two-of-eight code converter to drive the KWM-380	POKE 49243,0 on POKE 49242,0 off
AN2		POKE 49245,0 on POKE 49244,0 off
AN3		POKE 49247,0 on POKE 49246,0 off
STROBE	Clocks data into the KWM-380	PEEK (-16320)

an EMI filter. These aren't necessary, but I had them in my junk box, so I used them. Power is switched on when K4 supplies +12 volts to relay K1, located in the primary power-relay box. When the system is on and I'm away from home, I feel secure knowing there is some protection. Not shown is a 115-Vac antenna change-over relay that grounds the input to the receiver when power is off; when power is on, the antenna is ungrounded. The power supply uses 7812 and 7805 voltage regulators. The entire interface control operates from +12 volts and +5 volts. Fig. 7 is the diagram of the interconnection between the interface control and the Apple's eight-bit I/O card. An optional goodie is the fm audio-decoder, whose schematic is shown in fig. 8. It allows direct access to the computer through the DTMF decoder via fm radio. This is used in case you want to operate remotely from VHF or UHF. The tone decoders are 567s and can be adjusted to detect any dual tone; I'm using tones from my keypad. It is activated by holding the proper key for eight seconds; both the telephone and fm radio operate the system, or the fm radio can operate alone. A command from data-out 3 resets the decoder (turns the fm audio off).

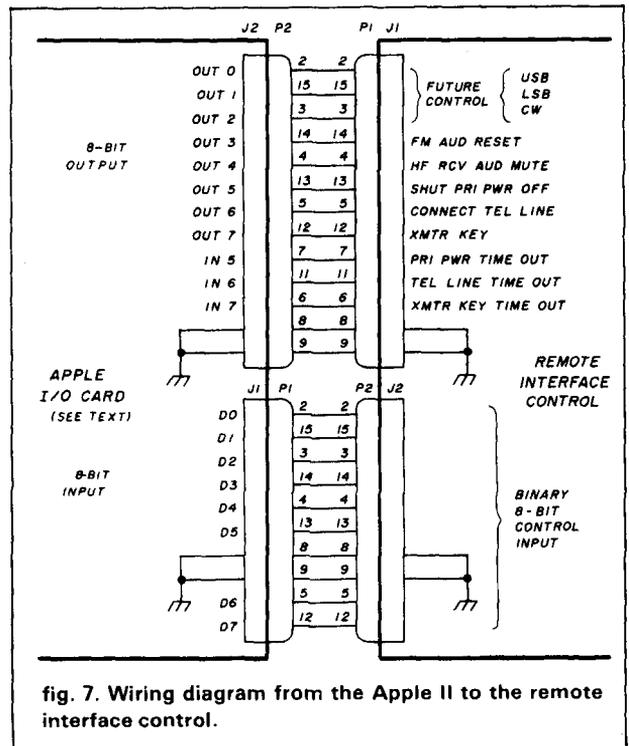


fig. 7. Wiring diagram from the Apple II to the remote interface control.

## system operation

For testing, replace the telephone line with a 900-ohm resistor to provide balance to the hybrid. **Fig. 9** is the BASIC program. The program as listed will not autoboot; after the program is typed in and saved, insert a new disk and type: **INIT HELLO**. Apple DOS will create an autoboot disk. If the radio and Apple are off, push the digit 6 on the local TT keypad for five seconds. This allows U1A to charge the 10- $\mu$ F delay capacitor to set latch U1C and U1D and enable relay K4. System power will now be on. Line 70 is the three-digit access code; this can be changed at will. I use 789 in this program.

Enter the access code and the program menu, which give prompts to each of the functional subroutines that will appear. This portion of the program is lines 400 through 540. There are six



This picture shows all the components that compose the high-frequency remote-control system. See fig. 1 for the block diagram.



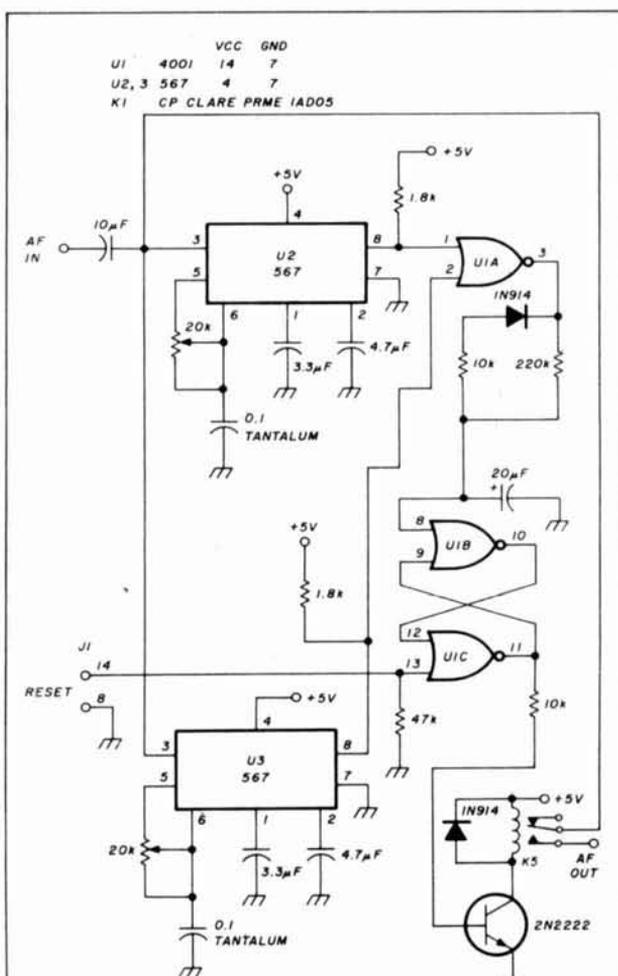


fig. 8. Optional fm audio-decoder schematic diagram. Any pair of tones can be selected. The tones must be held on for about eight seconds before relay K1 pulls in. This permits the system to be operated by an fm radio or telephone link.

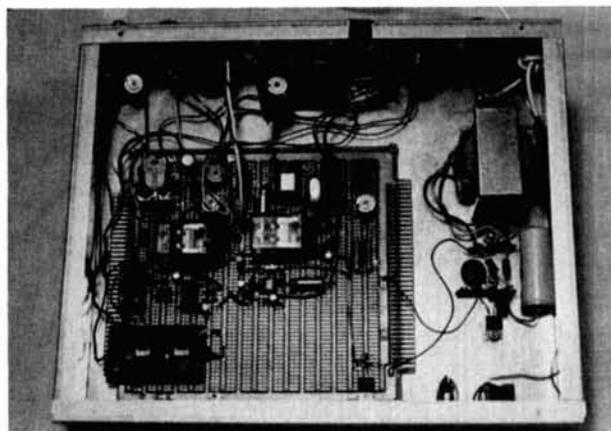

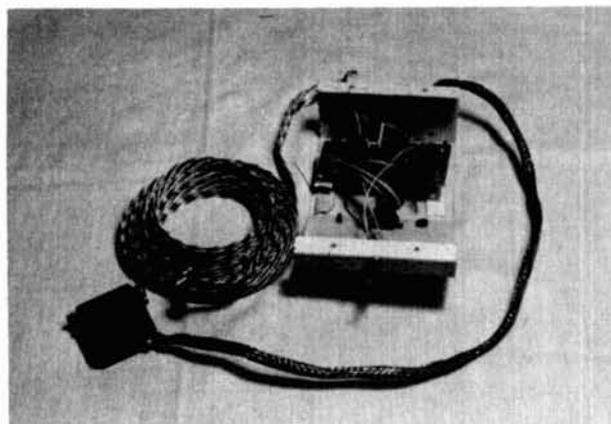This picture shows the remote control interface. This unit contains a phone patch, a DTMF decoder, level amplifiers, control logic and relays. See fig. 4 for its schematic. Note that space is available on the circuit board to fully remote the KWM-380.



This picture shows the frequency interface. It connects between the KWM-380 control interface connector and the Apple game port. See fig. 2 for its schematic.

subroutines, each of which can jump to its particular function when called. Lines 7000 through 7050 show how the Apple gets incoming data that is not from the keyboard.

For the Mute subroutine, enter 1; one beep sounds. This allows the # key to silence the KWM-380 or \* key to return the audio. The subroutine will automatically return to the menu.

For the Frequency Enter subroutine, enter 2; two beeps sound. This subroutine allows the operator to enter any frequency. A \* is used for the decimal place and # loads the KWM-380 and returns to the menu. An example for entering 14.225 MHz is 14\*225#.

For the Scan subroutine, enter 3; three beeps sound. Entering 1 makes the radio scan up. Entering 2 stops the radio from scanning. Entering 3 starts the radio scanning down. Entering \* bumps the radio up 1 kHz; # bumps it up 100 Hz. Entering # bumps the radio down 1 kHz; 9 bumps it down 100 Hz. To return back to the menu, enter 0.

For the Control Option subroutine, enter 4; four beeps sound. The Control Option subroutine allows # to reset the fm radio or \* to shut off the primary power after you exit the program. This subroutine automatically returns to the menu.

fig. 9. BASIC program listing.

```

10 HOME : VTAB 12
20 PRINT " <<<<<  REMOTE CONTROL  >>>>>"
30 HTAB 10: PRINT "WRITTEN BY DICK SANDER"
35 POKE 49358,1
40 FOR D = 1 TO 50: NEXT D
45 CALL - 198
50 POKE 49350,0
52 HOME
54 REM UNKEY:POKE 49357,1
56 POKE 49356,1: POKE 49347,0
60 PRINT "INPUT ACCESS CODE (3 DIGITS)"
70 AX = 7:AY = 8:AZ = 9
75 PRINT : PRINT "ACCESS CODE IS:" : PRINT : PRINT
80 PRINT AX,AY,AZ
90 GOSUB 7000
100 IF B < AX OR B > AX THEN GOTO 90
110 GOSUB 7000
120 IF B < AY OR B > AY THEN GOTO 90
130 GOSUB 7000
140 IF B < AZ OR B > AZ THEN GOTO 90
150 POKE 49358,1
160 POKE 49357,1
170 REM MUTE:POKE 49356,1
180 REM PWR ON:POKE 49347,0
400 REM MENU
410 HOME
420 VTAB 3: HTAB 18: PRINT "MENU": PRINT
430 PRINT : HTAB 10

```

```

440 PRINT "1. ENABLE RECEIVER"
450 PRINT : HTAB 10
460 PRINT "2. ENTER FREQUENCY"
470 PRINT : HTAB 10
480 PRINT "3. SCAN FREQUENCY"
490 PRINT : HTAB 10
500 PRINT "4. CONTROL OPTIONS"
510 PRINT : HTAB 10
520 PRINT "5. TRANSMIT"
530 PRINT : HTAB 10
540 PRINT "6. EXIT"
690 A = PEEK (50176)
700 IF A < 128 THEN 690
710 A = A - 128
720 IF A = 10 THEN A = 0
730 IF PEEK (50176) > 127 THEN 730
740 IF A < 1 OR A > 6 THEN CALL - 198: GOTO 690
750 IF A = 1 THEN GOTO 1000
760 IF A = 2 THEN GOTO 2000
770 IF A = 3 THEN GOTO 3000
780 IF A = 4 THEN GOTO 4000
790 IF A = 5 THEN GOTO 5000
800 IF A = 6 THEN GOTO 6000
1000 REM ENABLE RCVR
1010 CALL - 198
1020 HOME : PRINT "0 ENABLES RCVR - # DISABLES RCVR "
1030 GOSUB 7000
1040 IF B = 11 THEN POKE 49356,1: CALL - 198: GOTO 410
1050 IF B = 12 THEN POKE 49348,0: GOTO 410
1060 IF B > 12 THEN GOTO 1000
1070 IF B < 11 THEN GOTO 1000
2000 REM INPUT FREQUENCY
2010 CALL - 198: CALL - 198
2020 HOME : PRINT "ENTER FREQUENCY"
2025 SF# = ""
2030 F = PEEK (50176)
2040 IF F < 128 THEN 2030
2050 F = F - 128
2060 IF F = 10 THEN F = 0
2070 IF PEEK (50176) > 127 THEN 2070
2080 IF F = 0 THEN GOSUB 2250:SF# = SF# + "0"
2090 IF F = 1 THEN GOSUB 2280:SF# = SF# + "1"
2100 IF F = 2 THEN GOSUB 2310:SF# = SF# + "2"
2110 IF F = 3 THEN GOSUB 2340:SF# = SF# + "3"
2120 IF F = 4 THEN GOSUB 2370:SF# = SF# + "4"
2130 IF F = 5 THEN GOSUB 2400:SF# = SF# + "5"
2140 IF F = 6 THEN GOSUB 2430:SF# = SF# + "6"
2150 IF F = 7 THEN GOSUB 2460:SF# = SF# + "7"
2160 IF F = 8 THEN GOSUB 2490:SF# = SF# + "8"
2170 IF F = 9 THEN GOSUB 2520:SF# = SF# + "9"
2180 IF F = 11 THEN GOSUB 2580:SF# = SF# + "."
2190 IF F = 12 THEN GOTO 2220
2200 PRINT F
2210 GOTO 2030
2220 GOSUB 2550
2230 GOTO 400

```

```

2240 GOTO 2030
2250 POKE 49241,0: POKE 49242,0: POKE 49245,0: POKE 49247,0
2260 BOSUB 2610
2270 RETURN
2280 POKE 49240,0: POKE 49242,0: POKE 49244,0: POKE 49246,0
2290 BOSUB 2610
2300 RETURN
2310 POKE 49241,0: POKE 49242,0: POKE 49244,0: POKE 49246,0
2320 BOSUB 2610
2330 RETURN
2340 POKE 49240,0: POKE 49243,0: POKE 49244,0: POKE 49246,0
2350 BOSUB 2610
2360 RETURN
2370 POKE 49240,0: POKE 49242,0: POKE 49245,0: POKE 49246,0
2380 BOSUB 2610
2390 RETURN
2400 POKE 49241,0: POKE 49242,0: POKE 49245,0: POKE 49246,0
2410 BOSUB 2610
2420 RETURN
2430 POKE 49240,0: POKE 49243,0: POKE 49245,0: POKE 49246,0
2440 BOSUB 2610
2450 RETURN
2460 POKE 49240,0: POKE 49242,0: POKE 49244,0: POKE 49247,0
2470 BOSUB 2610
2480 RETURN
2490 POKE 49241,0: POKE 49242,0: POKE 49244,0: POKE 49247,0
2500 BOSUB 2610
2510 RETURN
2520 POKE 49240,0: POKE 49243,0: POKE 49244,0: POKE 49247,0
2530 BOSUB 2610
2540 RETURN
2550 POKE 49240,0: POKE 49243,0: POKE 49245,0: POKE 49247,0
2560 BOSUB 2610
2570 RETURN
2580 POKE 49240,0: POKE 49242,0: POKE 49245,0: POKE 49247,0
2590 BOSUB 2610
2600 RETURN
2610 REM STROBE ROUTINE
2620 ZZ = PEEK ( - 16320)
2650 RETURN
3000 REM SCAN FREQ
3125 CALL - 198: CALL - 198: CALL - 198
3130 HOME : PRINT "STARTING FREQUENCY? "
3135 PRINT : PRINT
3140 HOME : VTAB 24: HTAB 20: PRINT SF#
3145 VTAB 5: HTAB 10
3150 PRINT "PUSH 1 TO INCREASE FREQUENCY"
3155 VTAB 7: HTAB 10
3160 PRINT "PUSH 2 TO STOP SCANNING"
3165 VTAB 9: HTAB 10
3170 PRINT "PUSH 3 TO DECREASE FREQUENCY"
3175 PRINT : PRINT
3180 T = PEEK (50176)
3185 IF T < 128 THEN 3180
3190 T = T - 128
3195 IF T = 10 THEN T = 0

```

```

3200 IF T = 1 THEN GOTO 3225
3205 IF T = 2 THEN GOTO 3180
3210 IF T = 3 THEN GOTO 3285
3211 IF T = 7 THEN GOTO 3750
3212 IF T = 9 THEN GOTO 3750
3213 IF T = 11 THEN GOTO 3750
3214 IF T = 12 THEN GOTO 3750
3215 IF T = 0 THEN CALL - 198: GOTO 410
3220 IF T > 3 THEN CALL - 198: GOTO 3180
3225 REM SCAN UP
3230 X = VAL (SF#)
3235 Y = X + 100
3240 FOR U = X TO Y STEP .00030
3245 REM CHECK FOR NEW KEY
3250 IF PEEK (50176) < 128 THEN 3260
3255 IF PEEK (50176) - 128 = 2 THEN HOME : CALL - 198: GOTO 3140
3260 VTAB 20: HTAB 10
3265 PRINT U:J = U: BOSUB 3695
3270 SF# = STR# (U)
3275 NEXT U
3280 GOTO 3140
3285 REM SCAN DOWN
3290 X = VAL (SF#)
3295 Y = X - 100
3300 FOR DN = X TO Y STEP - .00030
3305 REM CHECK FOR STOP KEY
3310 IF PEEK (50176) < 128 THEN GOTO 3320
3315 IF PEEK (50176) - 128 = 2 THEN HOME : CALL - 198: GOTO 3140
3320 VTAB 20: HTAB 10
3325 PRINT DN:J = DN: BOSUB 3695
3330 SF# = STR# (DN)
3335 NEXT DN
3340 GOTO 3140
3345 FOR I = 1 TO 9
3350 IF I = 1 THEN IF LEFT# (C#,1) = "." THEN B# = "0": BOSUB 3375
3355 B# = MID# (C#,I,1): BOSUB 3375
3360 IF B# = "E" THEN 3370
3365 NEXT I
3370 RETURN
3375 K = VAL (B#) + 1
3380 IF K < > 1 THEN 3395
3385 IF B# = "0" THEN 3395
3390 GOTO 3405
3395 ON K BOSUB 3440,3455,3470,3485,3500,3515,3530,3545,3560,3575
3400 RETURN
3405 IF B# = "A" THEN BOSUB 3590
3410 IF B# = "B" THEN BOSUB 3605
3415 IF B# = "C" THEN BOSUB 3620
3420 IF B# = "D" THEN BOSUB 3635
3425 IF B# = "E" THEN BOSUB 3650
3430 IF B# = "." THEN BOSUB 3665
3435 RETURN
3440 POKE 49241,0: POKE 49242,0: POKE 49245,0: POKE 49247,0
3445 BOSUB 3680
3450 RETURN
3455 POKE 49240,0: POKE 49242,0: POKE 49244,0: POKE 49246,0

```

## SWD-1 VIDEO CONVERTER

FOR CABLE TV



The SWD-1 Video Converter is utilized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms. 117VAC.

SWD-1 Video Converter Kit ..... \$69.95

## VTR ACCESSORIES

### SIMPLE SIMON VIDEO STABILIZER



Simple Simon Video Stabilizer, Model VS-125, eliminates the vertical roll and jitter from "copy guard" video tapes when playing through large screen projectors or on another VTR. Simple to use, just adjust the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments. Includes 12V power supply.

VS-125 Video Stabilizer, wired ..... \$39.95

NEW VCR Quality

### MODULATOR

Not a Game Type Modulator




The MPS-1 Kit converts Video/Audio signals to a crystal controlled RF output for TV Channels 3 and 4. The MPS-1 Modulator inputs are designed to match all TV Cameras and VCR's and features a voltage regulated power supply, power switch and LED indicator. No Tuning Required. Operates on 117VAC.

MPS-1 Kit ..... \$39.95

## UHF ANTENNAS and ACCESSORIES

### MDS-AMATEUR-ETV 32 ELEMENT

#### YAGI ANTENNA

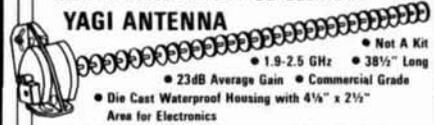

MAE-2 32 Element YAGI Antenna ..... \$23.95

### Kato Sona's Down Converter Kit ★ 1.9 - 2.56GHz ★

Designed for Simple Simon by former Japanese CQ Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antenna housing. Requires 1 hour assembly. IC and capacitors pre-tolerated.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit ..... \$34.95

### Kato Sona's Regulated Variable DC Power Supply

For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.

Model KSPS-1A Assembled Power Supply ..... \$23.95

SPECIAL INTRODUCTORY SAVINGS

ORDER ALL THREE ITEMS  
MAE-2, KSDC-KIT and KSPS-1A for Only **\$74.95**  
Regular prices if ordered separately \$82.85  
— CO-AX CABLES ARE NOT INCLUDED —

### ZYZZX VHF-UHF Wideband Antenna Amplifier




#### Revolutionary New HYBRID IC Broadband Amplifiers

50 MHz - 900 MHz Model ALL-1 12dB Gain  
Model ALL-2 35dB Gain

These units are not available anywhere else in the world. Each unit will serve many purposes and is available in Kit or Assembled form. Ideal for outdoor or indoor use. I/O impedance is 75 ohms. Amplifiers include separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors to tune or adjust.

ALL-1 Complete kit w/power supply \$24.95 ALL-1 Wrod/TESTED w/power supply \$34.95  
ALL-2 Complete kit w/power supply 34.95 ALL-2 Wrod/TESTED w/power supply 44.95
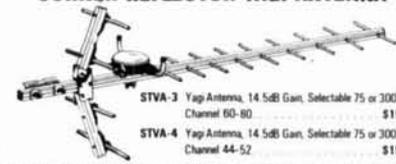
### Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80 ..... \$19.95  
STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52 ..... \$19.95  
RG-58/U 75 ohm Low Loss Coax Cable \$1.22/ft. F-59 Coax Connector \$ .39 ea.  
MT-1 Special UHF 75-300 ohm Matching Transformer ..... \$1.45 ea.

# Switch to Bambi!

## Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.

The Bambi Electronic Video Switch is an electronic switching network which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ... not being able to use more than one function at a time.

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Completely Wired and Assembled. Includes comprehensive Instruction/Operation Manual and Decal Set for customizing your Video Switch installation.

\$129.95




FREE Bambi Poster with any purchase



Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without referring to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.



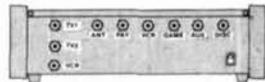Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually shielded for 65dB min. isolation).



Bambi's Specifications:

- Input/Output Impedance 75 ohm
- Signal Loss 3dB ±1dB
- Noise 4dB ±1dB
- Input Return Loss 12dB min.
- Isolation 65dB min.
- Power Req. 117VAC 60 Hz. 2W
- Dimensions 10 1/2" W x 6" D x 3 1/2" H
- Weight 4 1/2 lbs

## 7+11 PWD PARTS KITS

### INTRODUCING OUR 7+11 PWD PARTS KITS



KIT No	PART No	DESCRIPTION	PRICE
1	1VT1-PWD	Varactor UHF Tuner	\$24.95
2	2CB1-PWD	Printed Circuit Board, Pre-drilled	18.95
3	3TP11-PWD	PCB Potentiometers 4-20K, 1-5K, 2-10K, 2-5K, 1-1K, and 1-50K (11 pieces)	8.95
4	4FR-31-PWD	Resistor Kit, 1/4W, 5% 29-pcs, 1/2 W 2-pcs	4.95
5	5PT1-PWD	Power Transformer, PRI-117VAC, SEC-24VAC at 500ma	9.95
6	6PP2-PWD	Panel Mount Potentiometers and Knobs, 1-KBT and 1-5KAT with switch	5.95
7	7SS17-PWD	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Transistors 2-pcs, Heat Sinks 2-pcs	29.95
8	8CE14-PWD	Electrolytic Capacitor Kit, 14-pieces	6.95
9	9CC20-PWD	Ceramic Disk Capacitor Kit, 50 WV, 20-pcs	7.95
10	10CTS-PWD	Variable Ceramic Trimmer Capacitor, 5-65pfd, 5-pieces	4.95
11	11LS-PWD	Coil Kit, 18mhz 3-pcs, 22µh 1-piece (prewound inductors) and 2 T37-12 Ferrite Toroid cores with 6 ft. #26 wire	6.00
12	12ICS-PWD	IC Sockets, Tin inlay, 8 pin 4-pcs, 14 pin 1-pc and 16 pin 2-pcs	2.95
13	13SR-PWD	Enclosure with PM Speaker and Pre-drilled Backpanel for Mounting PCB and Ant. Terms	14.95
14	14MISC-PWD	Misc. Parts Kit, Includes Hardware, (6/32, 8/32 Nuts & Bolts), Hookup Wire, Solder, Ant. Terms DPDT Ant. Switch, Fuse, Fuseholder, etc	8.95
15	15MC16-PWD	Mylar Capacitors, 14-pcs and Silver Mica Capacitors 2-pieces	7.95
When Ordering All Items, (1-15), Total Price			159.95

**CUSTOMER NOTICE:** BUY WITH CONFIDENCE ... BEWARE OF LOW QUALITY IMITATORS. All of our kits consist of New, 1st Class, RF Quality, Parts Engineered for Optimum Operation, not factory seconds or stock close-outs. We service your completed kits that you've purchased and built. You will never get stuck with a BAG OF PARTS when ordering from Simple Simon.

## SIMPLE SIMON ELECTRONIC KITS, Inc.

3871 S. Valley View, Suite 12, Dept. H, Las Vegas, NV 89103

NEED 6 OR MORE OF AN ITEM? WRITE FOR QUANTITY DISCOUNTS

In Nevada Call: 702-871-2892

1-800-782-3716

Outside Nevada Call:

Available by Mail Order Only  
Send Check or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00 — VISA and Mastercard Acceptable — \*Check orders will be held 30 days before shipping.

```

3460 GOSUB 3680
3465 RETURN
3470 POKE 49241,0: POKE 49242,0: POKE 49244,0: POKE 49246,0
3475 GOSUB 3680
3480 RETURN
3485 POKE 49240,0: POKE 49243,0: POKE 49244,0: POKE 49246,0
3490 GOSUB 3680
3495 RETURN
3500 POKE 49240,0: POKE 49242,0: POKE 49245,0: POKE 49246,0
3505 GOSUB 3680
3510 RETURN
3515 POKE 49241,0: POKE 49242,0: POKE 49245,0: POKE 49246,0
3520 GOSUB 3680
3525 RETURN
3530 POKE 49240,0: POKE 49243,0: POKE 49245,0: POKE 49246,0
3535 GOSUB 3680
3540 RETURN
3545 POKE 49240,0: POKE 49242,0: POKE 49244,0: POKE 49247,0
3550 GOSUB 3680
3555 RETURN
3560 POKE 49241,0: POKE 49242,0: POKE 49244,0: POKE 49247,0
3565 GOSUB 3680
3570 RETURN
3575 POKE 49240,0: POKE 49243,0: POKE 49244,0: POKE 49247,0
3580 GOSUB 3680
3585 RETURN
3590 POKE 49241,0: POKE 49243,0: POKE 49244,0: POKE 49246,0
3595 GOSUB 3680
3600 RETURN
3605 POKE 49241,0: POKE 49243,0: POKE 49245,0: POKE 49246,0
3610 GOSUB 3680
3615 RETURN
3620 POKE 49241,0: POKE 49243,0: POKE 49244,0: POKE 49247,0
3625 GOSUB 3680
3630 RETURN
3635 POKE 49241,0: POKE 49243,0: POKE 49245,0: POKE 49247,0
3640 GOSUB 3680
3645 RETURN
3650 POKE 49240,0: POKE 49243,0: POKE 49245,0: POKE 49247,0
3655 GOSUB 3680
3660 RETURN
3665 POKE 49240,0: POKE 49242,0: POKE 49245,0: POKE 49247,0
3670 GOSUB 3680
3675 RETURN
3680 REM STROBE ROUTINE
3685 ZZ = PEEK (- 16320)
3690 RETURN
3695 C% = STR% (J) + "000000000"
3700 IF J < 1 THEN X = 6: GOTO 3715
3705 IF J < 10 THEN X = 7: GOTO 3715
3710 X = 8
3715 C% = LEFT% (C%,X) + "E"
3720 GOSUB 3345
3725 RETURN
3730 REM BUMP FREQ UP OR DOWN
3735 ST = VAL (SF%)
3760 IF T = 11 THEN DL = .001
3765 IF T = 12 THEN DL = -.001
3770 IF T = 7 THEN DL = .0001
3780 J = ST + DL
3785 SF% = STR% (J)
3790 GOSUB 3695
3795 GOTO 3140
4000 REM CONTROL OPTIONS
4010 CALL - 198: CALL - 198: CALL - 198: CALL - 198
4020 HOME
4025 PRINT "CONTROL OPTIONS:"; PRINT; PRINT
4027 PRINT " ENTER # TO MUTE FM RADIO"
4028 PRINT " ENTER # TO SHUT OFF POWER"
4030 GOSUB 7000
4105 IF B = 11 THEN GOTO 4110
4107 IF B = 12 THEN GOTO 4140
4109 IF B < 11 THEN GOTO 400
4110 POKE 49349,0
4120 FOR D = 1 TO 10: NEXT D
4130 POKE 49357,1
4135 CALL - 198: GOTO 400
4140 POKE 49355,1
4170 CALL - 198: GOTO 400
5000 REM ENABLE XMTR
5010 CALL - 198: CALL - 191
5020 HOME; PRINT "# KEYS XMTR - # UNKEYS XMTR"
5030 GOSUB 7000
5040 IF B < 11 THEN POKE 49351,0: CALL - 198: GOTO 410
5050 IF B = 11 THEN GOSUB 5090
5060 IF B = 12 THEN GOSUB 5120
5070 IF B > 12 THEN GOTO 410
5080 IF B = 11 THEN 5020
5085 IF B = 12 THEN 5020
5090 HOME
5100 POKE 49359,1
5110 RETURN
5120 HOME
5130 POKE 49351,0
5140 RETURN
6000 REM EXIT
6010 REM DISCONNECT RCVR & PHONE
6020 POKE 49350,0
6030 REM UNKEY XMTR
6040 POKE 49351,0
6050 REM 10 MHZ MWV
6060 GOSUB 2280
6070 GOSUB 2250
6080 GOSUB 2580
6090 GOSUB 2550
6100 GOTO 75
7000 B = PEEK (50176)
7010 IF B < 128 THEN 7000
7020 B = B - 128
7030 IF B = 10 THEN B = 0
7040 IF PEEK (50176) > 127 THEN 7040
7050 RETURN

```

**ANTENNA SPECIALISTS • AVANTI • AARL PUBS • AMECO • BASH • BEARCAT • BENCHER • B & W • BIRD • CALBOOK • COMMUNICATIONS SPECIALISTS • CUSHCRAFT • DRAKE • HAM KEY • HUSTLER • HY-GAIN • ICOM • KANTRONICS • LANSSEN • MFJ • MORGAIN • PANASONIC • RANNEY • SHURE • SONY • TELEX • TEN TEC • TRAC • TRANSCOM • VAN GORDON • VOCOM**

**POPULAR VALUES FROM SPECTRONICS!**

**DEMO SPECIAL!**  
**SAVE \$\$\$—QUANTITIES LIMITED!**  
**SONY**  
**ICF 6800W 31-BAND**  
**PORTABLE WORLD RECEIVER**  
 "The Best Under \$1,000.00...WRTV Handbook

**SUPER DEMO PRICE!**  
**\$469<sup>95</sup>**  
 Plus \$8.00 Shipping  
 (Cont'l USA)

List ~~\$699.95~~ — Regularly ~~\$549.95~~

**"DEMO" SPECIAL!**  
**SAVE \$80.00 MORE!**  
 We have a limited number of factory demo ICF-6800W's, that are being offered at a saving of \$80.00 over the price of new models. These units were used by SONY sales people at Trade Shows, and are still in mint condition. The full 1 year SONY warranty is also in force. This is a super deal, and is not available from any other dealer in the U.S.A.

**ORDER NOW! LIMITED QUANTITY**

**"easy-talk'r" VOX**  
**PORTABLE TRANSCEIVER**  
  
**\$49<sup>95</sup>** plus \$3.00 shipping

- Up to 1/2 mile FM Transmitting
- "Hands free" VOX operation
- Light weight—less than 9 Oz.

**BEARCAT BC-100 HAND-HELD PROGRAMMABLE SCANNER**  
  
 Reg. ~~\$349<sup>95</sup>~~  
**SALE \$299<sup>95</sup>** plus \$3.00 shipping

- 8 Band, 16 Channel
- Auto Scan • Channel LockOut • "Now Take it With You Anywhere!"

Valuable aid for Amateur use in antenna installation, tuning/pruning, field day, etc., plus hundreds of applications in home business, sports and recreation. Uses 9 volt battery (not supplied).

**KEN-TEC® 24-HOUR DIGITAL MILITARY TIME ALARM CLOCK**  
  
**\$19<sup>95</sup>** PLUS \$1.50 UPS


- .7" Red LED Numerals
- 24-Hr. Memory Alarm
- 1-Year Warranty
- Drowse Control
- Dark Brown Walnut Grain
- 2 1/4" H x 6 1/4" W x 3 1/4" D

**SUB-AUDIBLE TONE HEADQUARTERS**  
 ENCODERS plus \$2.00 shipping  
**\$29<sup>95</sup>** (Cont'l USA only)

We stock Communications Specialists SS 32 and SS 32M encoders for most any mobile or hand-held applications including the very popular Icom Handhelds.

**AMECO PREAMPS**  
  
 plus \$3.00 shipping (Cont'l USA only)

Model PLF 2	\$52.95
Model PLF 2E (240V)	\$57.95
Model PT 2	\$79.95
Model PT 2E (240V)	\$84.95

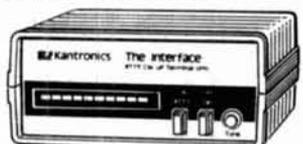**Put Your Computer "On-The-Air"**  
**The Interface™**  
  
 List **\$169<sup>95</sup>**  
~~\$189.95~~ Plus \$3.00 Shipping

Your personal computer becomes a complete CW/RTTY/ASCII send and receive terminal with **The Interface** linking it to your transceiver.

If you own an Apple II or Apple II Plus, Atari 400 or 800, TRS-80 Color Computer, or VIC-20, **The Interface** will put your computer "On-The-Air".

Software for each system features split screen display, buffered keyboard, status display, and message ports. Attach any Centronics compatible printer for hard copy. Software is available, on diskette for the Apple and program boards for the others, at additional cost.

Apple diskette	Atari board	VIC-20 board	TRS-80C board
\$29.95	\$49.95	\$49.95	\$59.95

**VOCOM FAVORITES**  
**5/8 WAVE TELESCOPING ANTENNA \$19<sup>95</sup>** Plus \$2.00 Shipping Cont'l USA

**VoCom POWER POCKET**  
  
 plus \$8.00 shipping (Cont'l USA)  
**\$199<sup>95</sup>**

Accepts any version of the IC-2A, applies its output to a wideband rf amplifier, and delivers 25 watts to your mobile antenna. Mobile talk-out power!

**2C-025 AMP \$76<sup>50</sup>** Plus \$3.00 Shipping

- 2 W In • 25 W Out

**SAVE \$\$\$**  
**SPECIAL PURCHASE**  
  
 List ~~\$349.95~~ Reg. ~~\$289.95~~  
 Now Only **\$259<sup>95</sup>**  
 ADD \$5.00 SHIPPING (CONT'L U.S.)

**SONY ICF-2001 INSTANT-ACCESS DIGITAL SHORTWAVE SCANNER**

- AM, CW, SSB
- 150 KHZ-30 MHz + FM BROADCAST
- PLL SYNTHESIZED WITH SCANNING AND MEMORY • AC ADAPTOR • 1 YEAR FACTORY LIMITED WARRANTY

**LIMITED QUANTITIES**

**ICR-4800 SONY 6-BAND POCKET WORLD RECEIVER**  
  
**\$89<sup>95</sup>** plus \$3.00 shipping (Cont'l USA)

- 6-band pocket world receiver—SW 1-5, plus MW
- Extremely compact and lightweight—palm sized!
- SW band spread dial easy tuning • Tuning indicator

**B & W PORTABLE APARTMENT ANTENNA**  
  
**\$43<sup>75</sup>** plus \$2.00 shipping

Quick, easy mounting. Tunes 2, 6, 10, 15, 20 and 40 meter Amateur bands, plus 5W BC bands in some ranges. 360 watts SSB/CW 2 1/2" whip extends to 37" 14" mount includes 5 base-loading coils. Weighs less than 2 lbs.

**ALEXANDER BP 4-W 500 MAH NICAD**  
  
**\$24<sup>95</sup>** plus \$2.00 shipping

Fits Wilson Mark II and Mark IV plus Yaesu FT-207, 500 MAH, 11.7 V. Nickel Cadmium.

**AVANTI THRU-GLASS ANTENNA**  
  
**\$32<sup>95</sup>** plus \$3.00 shipping

The Avanti On-Glass is the first two-way communications antenna that mounts on glass and transmits and receives through the glass. Extremely low VSWR is achieved by adjusting special tuning slug on matching network inside the vehicle. Can be easily removed for car washes without special tools.

**ICOM HEADQUARTERS**  
  
**ICOM IC25A** • **ICOM IC2A, IC2AT**

- Compact
- Quality Construction
- Versatile
- Affordable
- Wide Range of Accessories Available

**NEW! IC3AT (220 MHz) IC4AT (440 MHz)**

**CALL FOR PRICE & AVAILABILITY**

**TO ORDER:** CALL OR WRITE. MASTER CARD, VISA, MONEY ORDERS, PERSONAL CHECKS TAKE 3 WEEKS TO CLEAR, ACCEPTED. INTERNATIONAL ORDERS WELCOME, PLEASE REQUEST PRO FORMA INVOICE. ILLINOIS RESIDENTS ADD 6% SALES TAX.

**HOURS:** MON. THRU WED. 9:30-6:00, THURS-FRI. 9:30-8:00, SAT. 9:30-3:00

**STOP BY AND VISIT WHEN IN THE CHICAGOLAND AREA!!**

**SPECTRONICS, INC.**  
 1009 GARFIELD ST. OAK PARK, IL. 60304  
 PHONE **(312) 848-6777**

# Two great ways to get Q5 copy

## Ask:

G4HUW KB5DN WA4FNP WD5DMP  
 KJ2E K61MV WD4BKY WD8QHD  
 K4XG K8MKH WD4CCI WB9NOV  
 KA4CFF KB0TM WD4CCZ WD9DYR  
 KA5DXY W4YPL W5GAI

### 444D SSB/FM

#### Base-Station Microphone

Shure's most widely used base-station microphone is a ham favorite because it really helps you get through... with switch-selectable dual impedance low and high for compatibility with any rig! VOX/NORMAL switch and continuous-on capability make the 444D easy to use even under tough conditions. If you're after more Q5's, you should check it out.



### 526T Series II SUPER PUNCH® Microphone


Truly a microphone and a half! Variable output that lets you adjust the level to match the system. The perfect match for virtually any transceiver made, regardless of impedance. Turns mobile-NBFM unit into an indoor base station! Super for SSB operation, too. These and many other features make the 526T Series II a must-try unit.

FREE! Amateur Radio Microphone Selector Folder. Write for AL645.
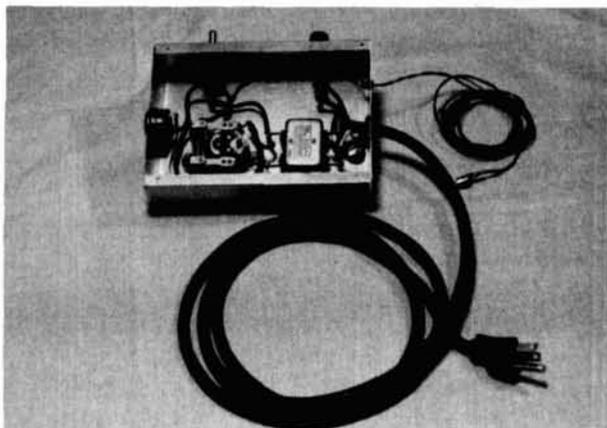
# SHURE®

THE SOUND OF THE PROFESSIONALS®...WORLDWIDE

Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204



This picture shows the primary power relay. Note the transient protection varistors and rfi filter. Relay K4, located inside the remote interface, controls power relay K1. See fig. 6 for its schematic.

For the Transmit subroutine, enter **5**; five beeps sound. Entering **\*** keys the transmitter; **#** unkeys the transmitter. Any digit will return to the menu.

For the Exit subroutine, enter **6**; the interface control will disconnect the telephone line, tune the radio to WWV, and wait for another call; and turn off power if the control option sets power to off.

There are several smaller projects within this project. I have just touched on each, but I feel there is enough information here to reconstruct my system. The program listing does not contain any voice synthesizer coding; my system does, and it also contains the proper card. I use the voice talker to echo back the frequency after I've entered it, or when I stop scanning.

The system described in this article works reliably without a voice synthesizer. The KWM-380's remote interface allows frequency control only; so for now, I only operate 10/15/20 meters USB with the antenna connected to my tri-band beam. Fortunately, the engineers at Collins left the door open for full remote-control.

I'd like to mention what the future holds for this system. I will add mode selection for the KWM-380, to switch USB, LSB, or CW, along with the proper filter and passband tuning. Also, as an addition to this system or as a stand-alone project for the Apple, I will have an interface to my rotator for beam-heading control.

I really enjoy operating during my breaks at work; so far I've worked about twenty countries remotely. I've found one DX-pedition by using the scan mode.

I would also like to thank Tom McDermott, N5EG, for his technical assistance in this project.

ham radio

# RCA is a Leader in Communications Command and Control Systems

RCA Engineers Explore the Leading  
Edge of Technology in:

- Frequency agile HF antenna couplers
- Very fast VLSI frequency synthesizers
- HF-VHF-UHF spread spectrum  
Communications radio design

If you share our commitment to HF long  
range communications and want to  
contribute to circuit and system designs  
of the future, contact:

Dr. U. L. Rohde (DJ2LR)  
RCA Corporation  
Government Communications Systems  
Mail Stop 13-4  
Camden, NJ 08102

**RCA**



# hy-gain

## ANTENNA ROTATORS

### for your peace of mind.

Determine the total wind-load area of your antenna(s), plus any antenna additions or upgrading you expect to do. Now, select the matching rotator model from the capacity chart below. If in doubt, choose the model with the next higher capacity. You'll not only buy a rotator, you'll buy peace of mind.

ANTENNA WIND-LOAD CAPACITY		
ROTATOR MODEL	MOUNTED INSIDE TOWER	WITH STANDARD LOWER MAST ADAPTER
AR22XL or AR40	3.0 sq. ft. (.28 sq. m)	1.5 sq. ft. (.14 sq. m)
CD45 II	8.5 sq. ft. (.79 sq. m)	5.0 sq. ft. (.46 sq. m)
HAM IV	15.0 sq. ft. (1.4 sq. m)	N/A
T <sup>2</sup> X	20.0 sq. ft. (1.9 sq. m)	N/A
HDR300	25.0 sq. ft. (2.3 sq. m)	N/A

For HF antennas with booms over 26' (8 m) use HDR300 or our industrial R3501.



Full details at better Amateur dealers or write:

**TELEX hy-gain**

TELEX COMMUNICATIONS, INC.

1900 Albany Ave. So., Minneapolis, MN 55420 U.S.A.  
Europe: Le Bonaparte - Office 711, Centre Affaires Paris-Haut, 92150 La Plaine-Montfermeil, France

## technical forum

Welcome to the *ham radio* Technical Forum. The purpose of this feature is to help you, the reader, find answers to your questions, and to give you a chance to answer the questions of your fellow Radio Amateurs. Do you have a question? Send it in!

### diesel generator repair

Our organization has a government-surplus 10-kW diesel generator in need of repair. The battery recharging circuitry has been completely destroyed. The unit bears the following markings and information.

#### Unit markings:

Fermont Engine Generator plant  
Division Dynamics Corp. of  
America  
Bridgeport, Conn.  
Model # J-141-1 Contract # J-141  
Serial # J-141-0018  
10 kW 12.5 KVA  
PF .80 120/208 V 35 A  
60 cy. 3 phase 1800 RPM  
Temp. rise 70°

#### Generator markings:

General Electric #  
LC7470B16 Type 6J  
Model # 5SJ4254P22Y12 Figure 2  
generator  
Dia/cen. 2261 Frame 254Y

#### Damaged unit markings:

Fermont # 6064-0001

Please contact us if you have a unit like this. We are in great need of any schematics, manuals, or other information on this unit, and will gladly make arrangements to obtain copies of this information.

The Division of Disaster and Emergency Service is a volunteer search-and-rescue group. We would greatly appreciate any assistance that can be supplied by the readers of *ham radio*.

**Wayne Richardson**  
Lebanon Junction Area Coord.  
Bullitt Co. Div. Disaster &  
Emergency Services  
Main Street  
Lebanon Junction, KY 40150

### another 10-meter beacon

I am writing to inform you that I have designed and built a beacon controller and transmitter and that it is currently in (what I hope will be) permanent operation on 28.208 MHz. The beacon runs twenty-four hours a

day, seven days a week, with an input power of 75 watts CW. QSL information is transmitted along with the beacon transmission.

I hope that *ham radio* readers will find this a propagation aid; and the presence of this signal should indicate when the band is open into New England. The antenna is a ground plane at a height of 20 feet (6.1 meters) with 16 one-wavelength long radials.

(I am presently looking for donations of old Novice transmitters which might make a suitable replacement for my current transmitter, should the need arise. Keeping a transmitter on the air continuously can be quite taxing to transmitters designed for Amateur use. I would particularly like to find a Drake 2NT or a DX-60A.)

**Leonard J. Umina, WA1IOB**  
607 Sudbury Street  
Marlboro, MA 01752

*I am considering transistorizing my old Drake TR-3 transceiver. I do not wish to build or buy the plug-in units that operate from the 250-volt supply in the TR-3. I propose to rectify and filter the 12.6-volt ac originally used for the heaters.*

*The TR-3's i-f stages use 12BA6 tubes, with plate resistance of 1 megohm and transconductance of 4400 micromhos. I haven't found any single transistor which will match these characteristics, along with high input impedance. Of course I would like to use a single transistor, but I am willing to use two per stage if necessary. Can you help? — Farrell A. Buckley, AK7N*

One solution to your question is to use the Solid State Tubes sold by Sartori Associates, P.O. Box 2085, Richardson, Texas 75080. They offer a replacement for the 12BA6. Other solutions are no doubt possible. Perhaps one of our readers can offer a suggestion?

**ham radio**

# hy-gain®

## HF BROADBAND VERTICALS WORK THE WORLD

Hy-Gain broadband vertical antennas load the new auto-tune solid state rigs, require minimal space and provide low angle radiation without the expense or the problems of support structures.

**18AVT/WBS (80-10 meters)** The most successful vertical antenna of all and for good reasons. Broadband performance covers the 40, 20, 15 and 10 meter bands in their entirety. Automatic 5 band switching is accomplished by mechanically superior, highly efficient factory tuned Hy-Q traps with large coils for consistent performance at 2:1 or lower VSWR on 40-10 meter band edges; bandwidth on 80 meters is approximately 40 kHz with VSWR below 2:1. A factory tuned matching network for 50 ohms impedance is dc grounded for lightning protection and reduced precipitation static. The mechanical integrity of this antenna is so stable that performance does not change with the weather. The 18AVT withstands winds to 80 mph (128 km/h) without guying. All stainless steel hardware is included.

**14AVQ/WBS (40-10 meters)** Offers very similar construction and the same excellent broadband performance as 18AVT over the entire 40, 20, 15 and 10 meter bands; automatic band switching with mechanically superior large-coil Hy-Q traps and very low angle radiation pattern. The smaller, low visibility size also makes the 14AVQ very suitable for roof mounting. The optional 14RMQ roof mounting kit includes base plate, mast and radial/guy wires. All antenna hardware is stainless steel.

**18 HTS (80-10 meters, 160 meters with optional loading coil)** The superb reliability of the 18 HTS is manifest in installations now over 20 years old. And, with the improvements we made over the years, the 18HTS is now better than ever. Automatic band selection is achieved through a unique stub decoupling system which effectively isolates various sections of the antenna so that an electrical  $\frac{1}{4}$  wavelength (or odd multiple  $\frac{1}{4}$  wavelength) exists on all bands. For example, outstanding broadband performance on 20, 15 and 10 meters is achieved with an extended  $\frac{1}{4}$  wave collinear. On 80 meters bandwidth is approximately 250 kHz at 2:1 VSWR. With the optional base loading coil exceptional performance is also provided at 160 meters. The galvanized tower requires no guying and withstands winds to 100 mph (160 km/h). A special hinged base allows complete assembly at ground level and permits easy raising and lowering. Includes stainless steel hardware. WARC kits to be available.

Other Hy-Gain vertical multiband antennas are available though not shown here. The 12AVQS (20, 15, 10 meter) is similar to 18AVT above but with VSWR of 1.5:1 or less on all bands. The 18VS (80-10 meter) comes with a base loading coil and may be installed on a short mast driven into the ground. All include stainless steel hardware.

### PHASE FOR GAIN

Any two identical Hy-Gain verticals can be phased for excellent gain and directivity. A great system for beam performance on 40, 80 and 160 meters or for 10, 15 and 20 meters where space is limited. Send for our free technical report "Phased Verticals".


Hy-Gain Verticals that work the world  
at better Amateur Dealers.

# TELEX® hy-gain®

TELEX COMMUNICATIONS, INC.

9500 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A.  
Europe: Le Bonaparte—Office 711, Centre Affaires Paris-Nord, 93153 Le Blanc-Mesnil, France.

HF Vertical Antenna SWR Curves

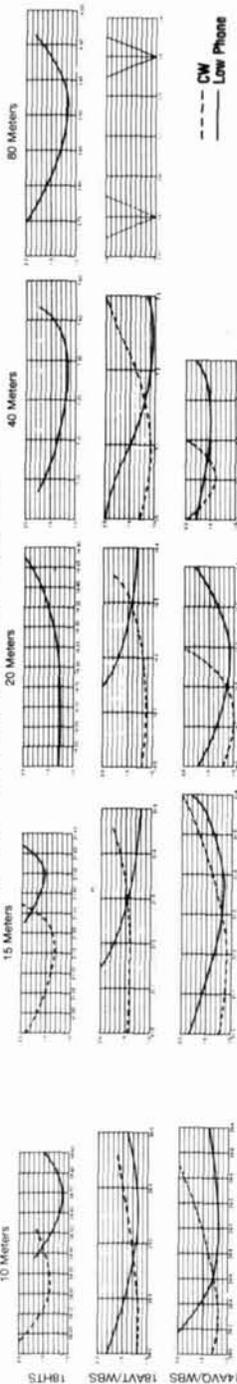

18 HTS 50' (15.2 m)

18 AVT/WBS 25' (7.6 m)

14AVQ/WBS 18' (5.5 m)

# More kit quality

A triumph of price and performance — Heath's new HW-5400 Synthesized HF SSB Transceiver kit makes high technology affordable. With more versatile, far-reaching capabilities, it puts the original skill and adventure back into Amateur Radio...



HW-5400 Transceiver

Heath breaks the price barrier on sophisticated transceivers, offering the highest value for your hamshack dollar. The slim, new HW-5400 is a marvel of kit-form engineering that performs like a dream on 80-10 meters.

## MORE ADVANCED IDEAS

Solid state and broadbanded, the HW-5400 incorporates more performance-improving features at a lower price than any comparable transceiver. It's fully synthesized for crystal stability and accuracy. Operating in USB, LSB and CW with automatic sideband selection, it has full break-in (QSK) for proficient keyers, two memories per band, power supply activation at the Transceiver, defeatable amplifier relay, reverse and over voltage protection as well as high VSWR forward power cut-back circuitry for the finals.

A custom microprocessor yields flexible, fingertip control over all phases of T/R operation.

## MORE CONVENIENCE

This perfection-packed kit has many benefits. A unique dual-speed tuning system can extract new QSOs or fly through a band in 1 kHz increments with 50 Hz resolution! *Split-Memory Access* lets you review and change the transmit frequency while in receive, without missing a single word or fragment of code. With it, you can beat the QRM every time. Essential vox and sidetone controls are located behind the front panel nameplate. Seven mode and function symbols confirm transceiver status at a glance.

The HW-5400's Frequency Entry Keypad option allows directly-synthesized QSY to any point in the band, and permits fast DX

control when used with the Split Memory function. The matching HWA-5400-1 Power Supply/Speaker & Digital Clock (not shown) provides a double-fused source of 13.8 VDC from 120 or 240 VAC.

## MORE ENJOYMENT

Novice or active pro, the HW-5400 is perfect for operators who want a Transceiver that's second to none, plus the pride, knowledge and satisfaction that come from building it yourself with our world famous step-by-step manuals. You may find it to be the first microprocessor-controlled rig with enough potential to match the level of professionalism in every radio amateur!

## MORE DETAILS IN CATALOG

**FREE!** For complete details and specs, get a copy of the latest Heathkit catalog. Remove and mail the coupon today or write: Heath Company, Dept. 122-994, Benton Harbor, MI 49022. Visit your local Heathkit Electronic Center\* for an exciting hands-on tryout.



## There's more for the Ham at Heath

Also see our state-of-the-art SS-9000 Deluxe HF Synthesized Transceiver (pictured below), which can be controlled by a computer or ASCII terminal.

\*Units of Veritechnology Electronics Corporation in the U.S., a subsidiary of Zenith Radio Corp.

Please send me a FREE Heathkit catalog.

Mail to:  
Heath Company, Dept. 122-014  
Benton Harbor, MI 49022

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

AM-436



**Heathkit**  
Heath  
Company

# MAIL THIS CARD TODAY for your **FREE** Heathkit® Catalogs

The new full-color Computer Catalog describes our complete line—including the new, 16-bit/8-bit Z-100 computer! The latest Heathkit Catalog has over 400 easy-to-build kit products for home, car and hobby uses.



307-019

## COMPUTER CATALOG

Hardware and software



122-019

## HEATHKIT CATALOG

Over 400 electronic kits

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Ham Radio




PC-145

**FREE**  
Heathkit  
Catalogs

Post Office  
will not  
deliver mail  
without stamp

**Heath Company**  
Benton Harbor, MI 49022

# quality says it all...

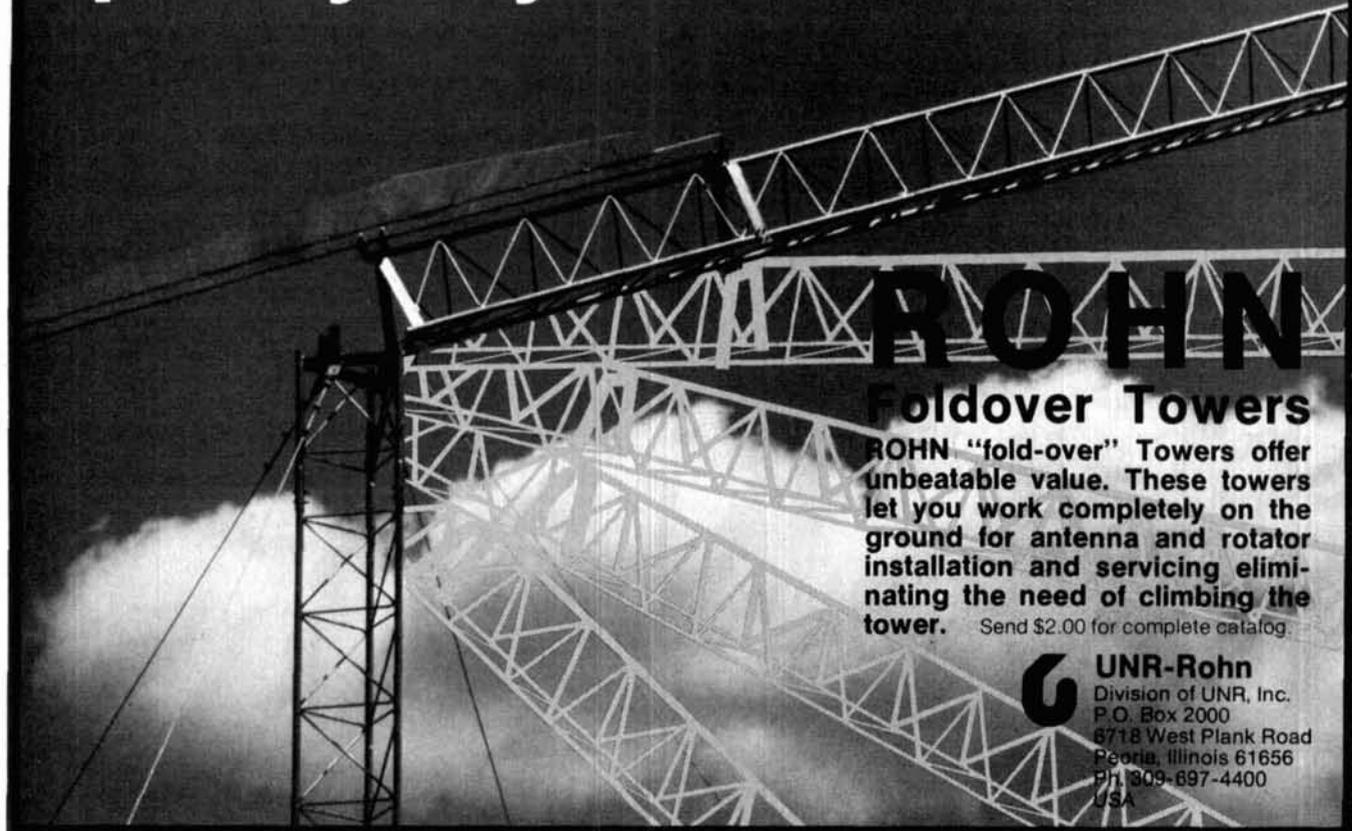

## ROHN Foldover Towers

ROHN "fold-over" Towers offer unbeatable value. These towers let you work completely on the ground for antenna and rotator installation and servicing eliminating the need of climbing the tower. Send \$2.00 for complete catalog.

**UNR-Rohn**  
Division of UNR, Inc.  
P.O. Box 2000  
6718 West Plank Road  
Peoria, Illinois 61656  
Ph. 309-697-4400  
USA

182

# TERMINALL

## RADIO MODEM



APPLE TRS-80 ATARI

### SEND & RECEIVE CW & RTTY

TERMINALL is a hardware and software system which converts your Personal Computer into a state of the art communications terminal.

- TERMINALL is easy to use. Plug into your receiver headphone jack and copy Morse code or radioteletype. Plug into your CW key jack and send Morse code. Attach a Microphone connector and send Baudot or ASCII RTTY using audio tones (AFSK). That's all there is to hooking it up.
- Fantastic Morse reception. No adjustments are necessary to receive Morse code. It's fully automatic! Six stage active filter demodulator and auto adaptive Morse algorithm copies the weak and sloppy ones.
- Separate RTTY and CW demodulators. Built in crystal controlled AFSK, CW and PTT keying, 60 mil loop interconnect, RS 232 IN and OUT, hand key input and side tone output.
- Built in parallel printer driver software allows hardcopy in all modes.
- Hardware clock maintains accurate time.
- Multiple user defined WRU functions. You select initiate sequence, terminate sequence, what to transmit back and whether to save on tape or disk.
- Word wrapping, word mode editing, diddle, ignore carriage returns, user programmable end of line sequence, adjustable carriage width, transmit delay (fixed, none or auto adaptive), excellent documentation, break mode and much more.
- TERMINALL has capabilities for surpassing dedicated terminal systems. And since it works on a general purpose computer, the majority of your investment (your computers) spread out over many different applications. You get more for your money.
- Complete with software on cassette and diskette, assembled and tested hardware, and extensive instruction manual. Call or write for specifications on TERMINALL for TRS-80 Model I or Model III, Apple or ATARI 400/800 COMPUTERS. \$499.
- 15 day money back trial period. One year parts and labor limited warranty on factory direct orders.

To Order  
(209) 667-2888



**MACROTRONICS, inc.**  
1125 N. Golden State Blvd.  
Turlock, CA 95380

\* Apple is a Registered Trademark of Apple Inc.  
TRS-80 is a Registered Trademark of Tandy Corp.  
Atari is a Registered Trademark of Atari Inc.  
Shipping U.P.S. Reg. Del. \$4.00 CA residents add 6% sales tax.

152

More Details? CHECK — OFF Page 129

SEE YOU AT

DAYTON!

**FAST**

Booth #71



**SCAN**

**\$399**

Have you tried it yet?

### ATV TRANSMITTER/CONVERTER



TVC-1

- \* 10 Watts Output
- \* Standard Frequencies Available
- \* Broadcast Standard Sound
- \* High-resolution & color video
- \* Regulated AC Supply Built In
- \* Tuneable Downconverter & Preamp

Connect to the antenna terminals of any TV set, add a good 450 MHz antenna, a camera and there you are... Show the shack, home movies, computer games, video tapes, etc.

### ATV DOWNCONVERTER

For those who want to see the ATV action before they commit to a complete station, the TVC-4 is for you. Great for public service setups, demos, and getting a buddy interested. Just add an antenna and a TV set tuned to CH. 2, 3, or 4 and plug in to 117 volts a.c. **\$89.00**



TVC-4

**TVC-4L extra low-noise version... \$105 delivered in USA**

HOMEBREWERS: ASK FOR OUR BASIC FOUR-MODULE PACKAGE

CALL OR WRITE FOR OUR COMPLETE LIST OF SPECIFICATIONS, station set-up diagrams, and optional accessories which include antennas, modulators, detectors, test generators, cameras, etc. WE ARE A FULL-LINE SUPPLIER OF ALL YOUR ATV NEEDS.

TERMS: VISA or MASTER CARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Allow three weeks after order for delivery.

**P.C. ELECTRONICS**  
Tom W8ORG Maryann WB6YSS

(213) 447-4565  
2522 Paxson Lane,  
Arcadia, California 91006

April 1983 **EM** 51

# ham radio TECHNIQUES

Bill Over  
W6SAI

More and more Amateurs are faced with the problem of getting on the air from a location where a full-size antenna cannot be erected. What's the answer? Stay on 2 meters and work the local repeater? If only the high-frequency antenna could be magically reduced in size!

Mini-antennas have been used on the high-frequency bands for a long time, the most compact type being the loaded whips for mobile service. While these ultra-short antennas do work, their efficiency is very low (of the order of one or two percent) and their bandwidth is very restricted. As the antenna shrinks in size, compared to the length of the radio wave, efficiency drops and bandwidth decreases. However, it is possible to strike a compromise and achieve good efficiency in an antenna that is smaller than the classic half-wave dipole.

## the loaded antenna

Serious investigation of the coil-loaded short antenna started about 1933 when the General Electric Company developed experimental radios for the new mobile police communications system working on the "ultra-

high" frequency of about 35 MHz. A summary of the results appeared in the September, 1934, issue of *QST*. The investigation was continued in

1940 by the National Park Service. The N.P.S. wanted 2-4 MHz mobile operation for the mountainous regions of the National parks, many of which exhibit VHF blind spots.<sup>2</sup>

The conclusions of both these investigations point up that a very short, loaded antenna could be made to work well provided it was properly designed. One of the main requirements of proper design was that a high-Q loading coil be used, and that it be placed near the center of the antenna section.

It was there that the matter rested until Jerry Hall, K1PLP, published a classic article in the September, 1974, issue of *QST*, giving a procedure for determining the inductance of a loading coil no matter where it was placed in an antenna.<sup>3</sup> Jerry's example used a dipole instead of a mobile whip. This interesting mathematical exercise was converted into a computer program by Dick Sander, K5-QY, and published in the December, 1981, issue of *CQ*.<sup>4</sup> The short, loaded antenna had finally arrived.

## loaded dipole program for the TRS-80

Dick's program was designed to be

```

100 REM PROGRAM FROM CQ MAG DEC 1981 BY DICK SANDER, K5QY
200 REM PUT ON TRS-80 AND EXPANDED BY W6SAI FOR W6SAI
400 GOSUB 500
500 PRINT " ** LOADED DIPOLE DESIGN PROGRAM **"
510 PRINT
520 PRINT "THIS PROGRAM REDUCES ANTENNA TO 1/2 ACTUAL SIZE AND"
530 PRINT "INVERTS THE COIL IN THE CENTER OF EACH SIDE"
600 PRINT
700 INPUT "HOW MANY FREDS ARE YOU GOING TO INPUT (10 MAX)";Z
710 FOR I=1 TO Z
720 PRINT "FREQ #";I; INPUT F(I)
730 NEXT
740 FOR I=1 TO Z
750 F=F(I)
900 A=234/F
1100 B=56.3/F
1300 X=((234/F)-B)
1400 Y=(A/2)-B
1450 IF D=0 THEN 2100
1500 INPUT "DO YOU WANT TO USE THE WIRE TABLE (Y OR N)";Y$
1600 IF Y$="Y" THEN GOSUB 3000
1700 IF Y$="N" THEN GOSUB 4300
1800 IF Y$="N" THEN 2100
1900 IF Y$="N" THEN 2100
2000 GOTO 1500
2100 S1=1.46/(60*Z*.1415*2*F*2)
2200 S2=1/X*(LOG(24*X/D)-1)
2300 S3=(1-F*B/234)*2-1
2400 S4=1/Y*(LOG(24*Y/D)-1)
2500 S5=(Y+F/234)*2-1
2600 S6=S1*(S2+S3-S4+S5)
2620 IF I=1 THEN 2700
2650 GOTO 2700
2700 LPRINT: FREQ, "TOTAL", "CENTER", "COIL", "WIRE"
2710 LPRINT: MHZ, "LENGTH", "TO", "IND", "DIAM."
2720 LPRINT: FEET, "COIL", "UNY", "INCHES"
2730 LPRINT
2740 LPRINT F, A, B, S6, D
2900 NEXT I
2910 END
3000 PRINT
3100 INPUT "WIRE GAUGE (#10 TO #22)";ID
3200 IF D=18 THEN D=.101*RETURN
3300 IF D=12 THEN D=.081*RETURN
3400 IF D=14 THEN D=.064*RETURN
3500 IF D=16 THEN D=.058*RETURN
3600 IF D=18 THEN D=.048*RETURN
3700 IF D=20 THEN D=.032*RETURN
3800 IF D=22 THEN D=.025*RETURN
3900 PRINT
4000 PRINT "WIRE GAUGES MUST BE AN EVEN"
4100 PRINT "NUMBER IN THE RANGE 10-22"
4200 PRINT;PRINT; GOTO 3000
4300 PRINT
4400 INPUT "WHAT IS THE ELEMENT DIAMETER IN INCHES";D
4500 RETURN

```

fig. 1. Loaded dipole program for the TRS-80.

used with an Apple II computer, but my good friend Dick Rasor, W6EDE, easily converted it for use with the TRS-80 (fig. 1). A little work with the program showed up some interesting aspects of the loaded dipole which previously had been obscured by the difficulty of the mathematics. These difficulties were now reduced to punching a few computer keys!

An illustration of the loaded dipole is given in fig. 2. For simplicity, the loading coils are located midway down the arms of the dipole: early ex-

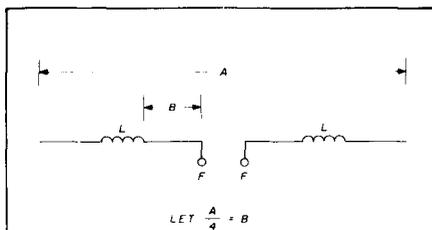


fig. 2. Loaded dipole with loading coils placed one-half the distance from the feedpoint (F-F) to the end. Distance A is one-quarter wavelength.

periments indicated this was the best place to put a loading coil if the assembly was to avoid becoming mechanically too complex.

A computer run of the antenna design shows why coil placement is critical. Fig. 3 plots coil placement against coil inductance. One limit on where the coil can be placed is seen at point 1, the feedpoint of the antenna. A feedpoint-loaded dipole places the coil at the point of maximum current, where the stored magnetic energy is high. A minimum value of inductance is required to establish resonance there, but — unfortunately — the portion of the antenna that does the most radiating is the portion with the maximum current. Winding it up into a coil reduces the radiation resistance, reduces bandwidth drastically, and leads to high antenna losses, principally because the coil will have relatively high loss no matter how well it is built.

Farther out along the antenna, the stored magnetic energy decreases and the inductance required in any

coil placed there increases. At the same time, more of the high-current center section of the antenna is permitted to radiate. Antenna efficiency rises and the radiation resistance increases. Good!

But observe what happens when the coil passes the center point of the dipole leg (point 2). Now instead of increasing somewhat linearly with distance, the coil inductance increases rapidly. When the coil is placed near the end of the antenna (0.3) the required inductance value is more than seven times the value required for center (base) loading, and more than three times the value required when the coil is placed near the midpoint of the element.

It is tempting to place the loading coil near the tip of the antenna element; then, the whole element section has a high value of current in it, and this is thought best for antenna efficiency. But imagine a 925- $\mu$ H inductor at 3.5 MHz. It would be four inches in diameter and have nearly two-hundred turns on it. The length would be over a foot, depending upon wire size. Placing such a coil at a high potential point in an antenna would result in fireworks: corona and brush discharge would occur with but a few watts of power applied. (And the coil would probably burn up after dust and dirt collected on it. In fact, all that would be required to do the job would be fog or rain.)

Fig. 4 shows the inductance of coils needed to make a half-size dipole for the various high-frequency bands. Although the antenna is not thereby reduced to its theoretically smallest size, this will show how an antenna can be cut fifty percent in size and still do a good job.

The computer printout that derived fig. 4 was based on an antenna using No. 16 wire for the coils and flattop. If a larger size wire is used, the tip sections of the antenna should be shortened a few inches (this is not critical).

With this data, a short dipole for 3.8 MHz works out to be about 61 feet 6 inches (18.94 m) long. The

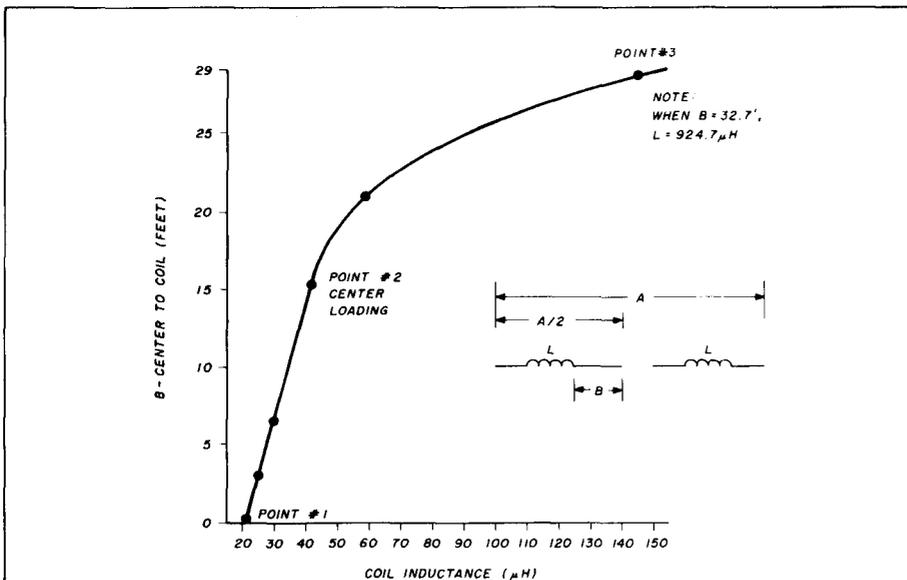


fig. 3. Inductance increases as the coil moves outward from the center of the loaded element. The increase in inductance is linear until coil reaches the center point of the element, and then it increases rapidly approaching the tip. If the coil is placed at the tip, inductance would theoretically have to be infinite. Coil loss increases with inductance, and point 2 on curve represents a practical compromise. Point 1 is for base loading.

loading coils are each 40.1  $\mu\text{H}$ , and they are placed 15 feet 4½ inches (4.69 m) from the center of the insulator.

How do you wind a 40.1- $\mu\text{H}$  coil? There's a computer program for that, no doubt, but I don't have one at hand. However, the simple formula shown in fig. 5 will do the job.

### feeding the loaded dipole antenna

With a portion of the antenna wound up into a loading coil ( $L_1$ ), the radiation resistance of the antenna drops drastically. For this design, the feedpoint resistance (composed of the radiation resistance plus the loss resistance of the coils) is about 22 ohms. This figure varies with height of the antenna above ground. Taking this value as *par*, the inductor-match system (hairpin match) developed by Gootch, Gardner, and Roberts will do the job.<sup>5</sup> For this antenna design, an inductor of about 44-ohms reactance ( $L_2$ ) is placed across the antenna feedpoint. At 3.8 MHz, this corresponds to a coil of 1.86  $\mu\text{H}$ . The reactance of the coil is derived from the graph in fig. 6.

Since the inductor-match is a simple L-network, the capacitive portion of the circuit is achieved by slightly shortening the antenna. Four inches off each end is about right, and the completed antenna is shown in fig. 7.

### complete TRS-80 program for all bands

Using this information as a starting point, some smart computer programmer can develop a complete TRS-80 program which includes the design of the inductor-match coil. And, in addition, the program might be further expanded to include large-diameter elements. This will permit vertical antennas composed of aluminum tubing to be quickly designed for the lower frequency bands. I'll be happy to hear from anyone who completes this task.

### no-code ham license?

A lot of flak is flying around about the so-called no-code license proposed by the FCC. The arguments against a no-code license seem to fall into two categories:

1. I had to pass a code test, so why shouldn't the next guy?
2. A no-code license will open the door to CB operators, who will ruin the ham bands.

I won't comment on the first argument, or the accompanying argument over tradition; others can fight that battle. But I would like to discuss the second argument that a no-code license would open the door to CB operators, who will ruin the ham bands.

$X_L = 2\pi fL$   
 WHEN  $f = \text{MHz}$  AND  
 $L = \mu\text{H}$ , THEN  
 $L = \frac{X_L}{6.281}$

$$L (\mu\text{H}) = \frac{a^2 n^2}{9a + 10b}$$

$n = \text{NUMBER OF TURNS}$

fig. 5. Formula for calculation of small close-wound coils for a given value of reactance, when  $f$  in MHz is known.

Perhaps this is true. But perhaps the CBers don't want to work in a VHF ham band! How about that!

It is very instructive to tune across the hf spectrum with an "all-wave" receiver. Anyone who does will note that there's a tremendous amount of illegal sideband activity between 26.2 MHz and 27.99 MHz. I believe there are more unlicensed stations in this portion of the spectrum than there are licensed stations in all the ham bands, at any one given time. This portion of the spectrum is jammed with thousands of signals.

These pirate operators are called "CBers." Perhaps this is an inaccurate epithet. I doubt if the majority of them have a CB license, and I prefer the term *pirate*. That does not imply CB operation. Be that as it may, the point I am bringing out is that these pirates operate wherever they wish, using modified ham gear. If they want to work on 144 MHz, or 220 MHz, they will do so — regardless of whether or not a no-code license exists.

When the sunspot count drops and the MUF falls, the 11-meter region will be barren of long-distance contacts. What will the tens of thousands of pirate operators do then? Go to the new no-code ham license? I doubt it.

Already many pirate operators in Europe are using the 6.6 to 6.8 MHz portion of the spectrum for SSB operation. The pirates tend to avoid the ham bands. They operate in the large

frequency	total length feet	center to coil feet	coil inductance $\mu\text{H}$	wire diameter inches
1.82	128.57100	32.14290	91.88680	0.058
3.51	66.66670	16.66670	43.87170	0.058
3.80	61.57900	15.39470	40.10240	0.058
7.15	32.72730	8.18182	19.53040	0.058
10.11	23.14540	5.78635	13.12140	0.058
14.17	16.51380	4.12844	8.88137	0.058
18.11	12.92100	3.23026	6.67597	0.058
21.20	11.03770	2.75943	5.55306	0.058
24.95	9.37876	2.34469	4.58680	0.058
28.60	8.18182	2.04545	3.90515	0.058

fig. 4. Computer-derived table of the inductance values of coils needed to make a half-size dipole.

ELECTRICAL  $\lambda/2$

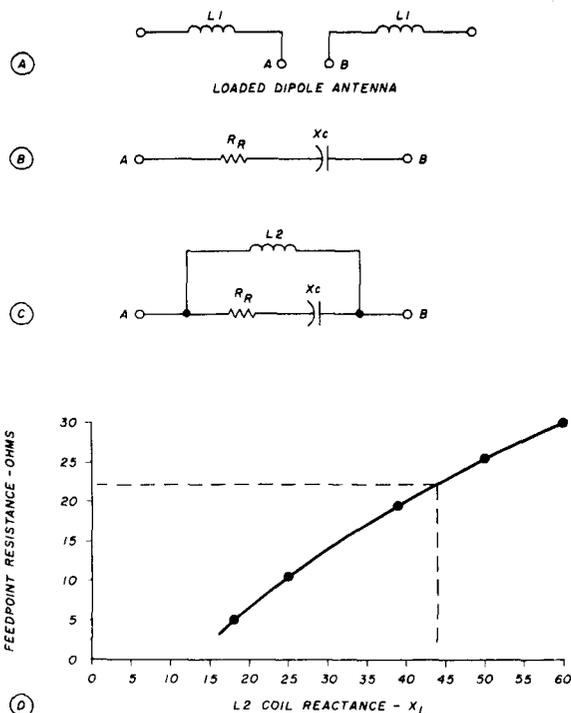


fig. 6. The coil-loaded dipole forms a portion of a network whose input impedance over a small frequency range is close to 50 ohms. The loaded dipole, A, has a low value of radiation resistance and loss resistance, which appears at feedpoint A-B. This low impedance can be made part of an equivalent parallel resonant circuit in which the total feedpoint resistance appears in series with the reactive branch of the circuit. B: The input impedance of such a circuit varies nearly inversely with the radiation resistance of the dipole, thus the low value of feedpoint impedance can be transformed to a larger value to match the line impedance. C: The dipole appears as a capacitive reactance by shortening the element past its resonant length. The inductor L2 consists of a small coil placed across the terminals of the dipole. The reactance of the matching coil is a function of the feedpoint resistance of the antenna. D: The dashed line is the example given in the text. Apply reactance value to formula given in fig. 5.

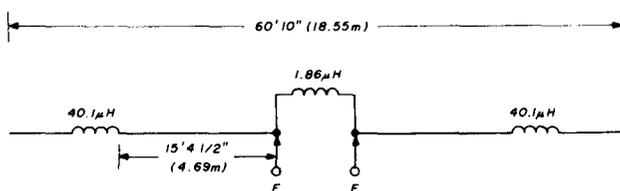


fig. 7. Compact, coil-loaded dipole for 3.80 MHz. Tip length is adjusted for minimum SWR at design frequency. Coil is wound with No. 16 (M1.3) wire per data in fig. 5.

spaces in the commercial and point-to-point regions, where few if any signals exist.

I say that the fear that pirates might invade ham radio via the no-code license is unfounded. They will come in only if they want to, regardless of the license structure, and my prediction is that there are more attractive places in the radio spectrum for them to occupy than a ham band. So I don't see the foundations of ham radio crumbling because a no-code license is introduced.

As time goes on the number of pirate stations will increase, because the various communications authorities throughout the world seem powerless to stop them. A few pirates will inevitably invade the ham bands from time to time, but this will have nothing to do with the Amateur Radio licensing structure. The problem has been swept under the rug up to now, yet it increasingly involves all the radio services. Pirate radio includes illegal broadcasting on medium and shortwave and VHF. In Europe, pirate broadcasting clogs the fm band and the quieter broadcast band channels. There are pirate television stations in operation in Europe, and Central America is full of illegal broadcasting. So far, radio hams are lucky; little of this trash has fallen in their bands. The pirates prefer to go where they can operate under less scrutiny than in a busy ham band.

So don't worry about a VHF no-code license. The pirate operators have more alluring possibilities open to them than competing with hams in a short-range, line-of-sight service.

### references

1. Dome, "Increased Radiating Efficiency for Short Antennas," *QST*, September, 1934, pages 9-13.
2. Hilgedick and Morgan, "Raising the Efficiency of Short Vertical Radiators," *QST*, December, 1940, pages 30-33.
3. Hall, "Off-Center Loaded Dipole Antennas," *QST*, September, 1974, pages 28-34.
4. Sander, "A Computer Designed Loaded Dipole Antenna," *CQ*, December, 1981, page 44.
5. Gootch, Gardner, and Roberts, "The Hairpin Match," *QST*, April, 1962, pages 11-14.

ham radio

# a microprocessor repeater controller

A versatile controller  
for two repeaters

Our radio club recently relocated its 2-meter repeater to a site with a much higher antenna. The repeater committee decided to make major improvements in the control system to accommodate this move. We had a 220-MHz repeater also under construction, and would need a controller for that system as well.

The original controller was a small, wire-wrapped board using 556 timers, some counters, and a ROM for the CW identification. Remote control was by phone line and was not sophisticated. Past experience with this system indicated that adding any simple function would be a major task. Microprocessor enthusiasts in the club had the solution: build *one* microprocessor-based controller for both bands!

The final design may be expanded upon easily. In addition to the hardware description, I would like to

By **Bill Warner, KB5F**, 5418 Vineridge Place,  
Garland, Texas 75042

share some of our thoughts and decisions that went into creating the final design.

### the design approach

Deciding to use a microprocessor as a controller was easy. In the long run it would be cheaper, and it's easier to add features by reprogramming than to add separate pieces of specialized hardware. Some new circuitry would be needed as features were added, but such circuitry would be simple interfaces.

Reliability would be good, thanks to the high reliability of digital circuits and the lower parts count per function (compared with standard small and medium-scale integrated circuits). Two decisions had to be made: which microprocessor to use, and what features to include in the new controller.

### selecting a microprocessor

The microprocessor we finally decided on would have to be easy to program in assembly language, have a simple input/output (I/O) structure, and be supported by good development software. The microprocessor instruction set should be able to handle reentrant programming, allowing one program module to share multiple data sets.

The Intel 8080, Zilog Z80, Motorola 6800, and Texas Instruments 9900 microprocessors were all candidates for our application. The 8080 or Z80 at first appeared to be the best choice. A friend had built an 8080 controller six years ago for the WR8ANW repeater in Columbus, Ohio. The program listing used for that controller was available and could have been converted for our needs. Several club members had 8080 systems that they used for software and hardware development. A major drawback of the 8080 was its I/O structure and the difficulty of writing clean, reentrant code for it.

The Z80 has few of the shortcomings of the 8080. It can set and test single bits in operands, has an indexed addressing mode, and allows I/O port addresses to reside in one of its internal registers. Reentrant programming is easier with it. Unfortunately, none of the club members had Z80 support software at that time.

The 6800 was not really in the running. None of the club members were familiar with it; we would be starting from scratch. This doesn't mean the 6800 won't work for this application. The WR8ANW repeater group, mentioned earlier, has completed a 6800-based controller.

The TMS9980 was our final choice. It is easy to write reentrant code for the 9900 family since any register may be an index. Interrupts are easily handled. Since all general purpose registers are in memory, the only registers saved on interrupt are the pro-

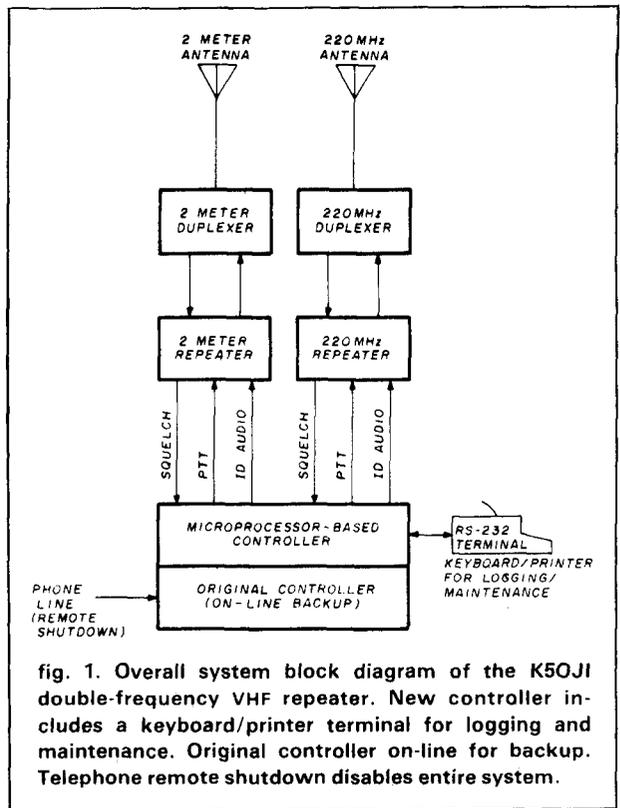


fig. 1. Overall system block diagram of the K5QJ1 double-frequency VHF repeater. New controller includes a keyboard/printer terminal for logging and maintenance. Original controller on-line for backup. Telephone remote shutdown disables entire system.


table 1. CRU address decodes in TMS9901 PSI. Addresses are in hexadecimal.

CRU hardware address	R12 contents	device
00	00	—
20	40	—
40	80	9902(A)
60	C0	9902(B)
80	100	9901
A0	140	—
C0	180	—
E0	1C0	—

gram counter, status register, and workspace pointer. These three restore automatically after interrupt servicing, reducing the programming load. And, support software which became available to the club on a larger 990 minicomputer proved to be a valuable tool when it came time to assemble and edit the controller programs.
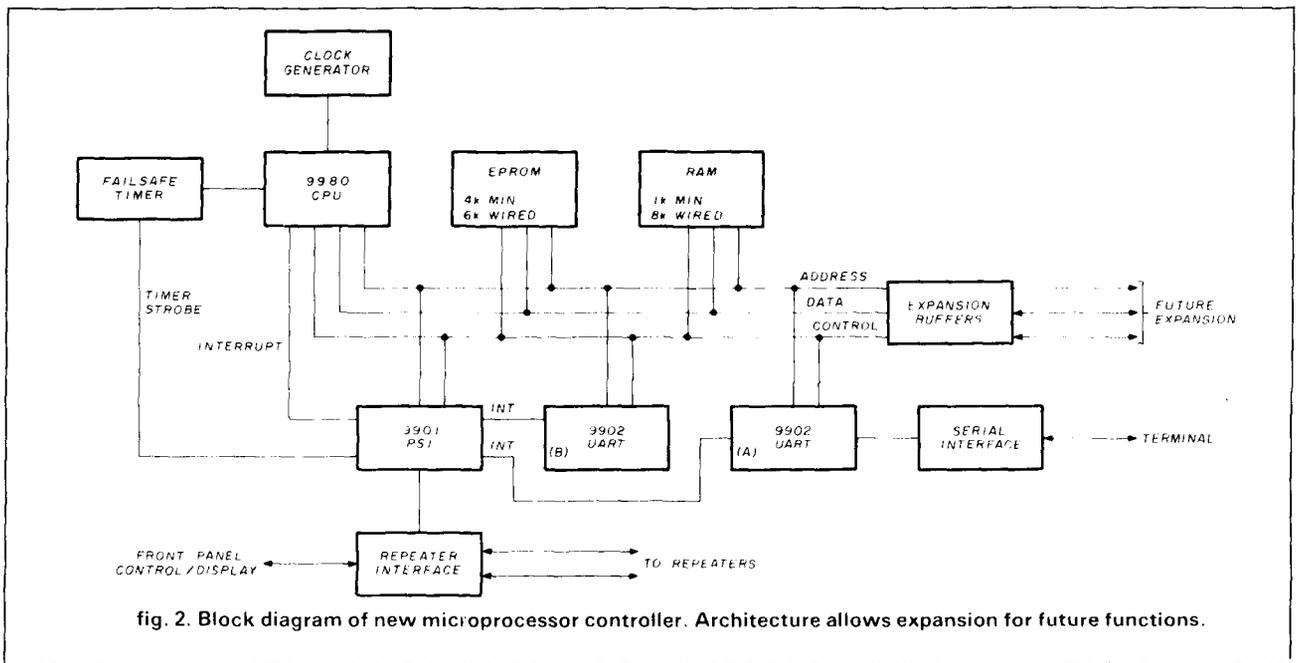
### a choice of features

A list of the minimum functions required for our application was drawn up. These included CW identification, a variable time-out timer, a beep to indicate time-out, timer reset, and a status-logging rou-



tine to print hourly status reports on a terminal. The time of day was added to the CW ID since there would be a counter keeping track of time in the program.

Keeping the original controller, modified to operate as a backup, would retain telephone line shut-down with the ability to disable the repeaters regardless of which controller was operational.

Fig. 1 is the repeater system block diagram. It was constructed so that adding new features would cause only a few hours of downtime. New programming may be installed while the backup controller handles the repeater. Some of the new features include a tone decoder, a modem for RTTY I/O and control, and even a voice synthesis module.

We had defined the general system; features were chosen and the microprocessor would use TMS9900 family components. This left only the hardware details to design.

### build or buy?

Texas Instruments makes several single-board microcomputers. The TM990/100 and TM990/180 boards have a small prototyping area where additional interface circuitry can be built. Each has plenty of on-board EPROM and RAM for program operation.

The final program would be burned in the EPROM, but I wanted to put the program in RAM first to do the final debugging and possible patching. The temporary RAM test-space would be free after program verification. The free RAM could then be used for other functions, perhaps as a message storage area for RTTY users. The only way to get enough check-

out RAM with the TM990 boards is to add at least one additional board.

Designing and wire-wrapping a single board with enough memory and I/O components to meet the basic criteria seemed the best way to proceed. It would include enough circuitry to bring address, data, and control lines off the board for later additions. Later features could be added using separate boards.

Fig. 2 is the single-board controller block diagram. Memory and I/O addressing are similar enough to the TM990 board series to allow using the TIBUG™ monitor ROM for program check-out, and also allow the final debugged control program ROMs to be installed and run on the TM990 board.

### solidifying the design

Figs. 3, 4, and 5 are the schematics for the controller board. Signal mnemonics connect the three main schematic groups. Two edge connectors, P1 and P2, connect the controller to the rest of the system. Details begin with fig. 3. The controller chassis is seen in photo 1.

The Central Processor Unit (CPU) is a TMS9980 with an 8-bit data bus and addressing to 16K (16,384) bytes, more than sufficient for this application. CPU clock frequency is 10 MHz, from the crystal-controlled inverter oscillator in U8. External device clocking is available at U20-22, marked 03.

The CPU resets by interacting with peripheral interfaces, shown in fig. 5. Power-on reset for these in-

\*TIBUG is the Texas Instruments debugging utility.

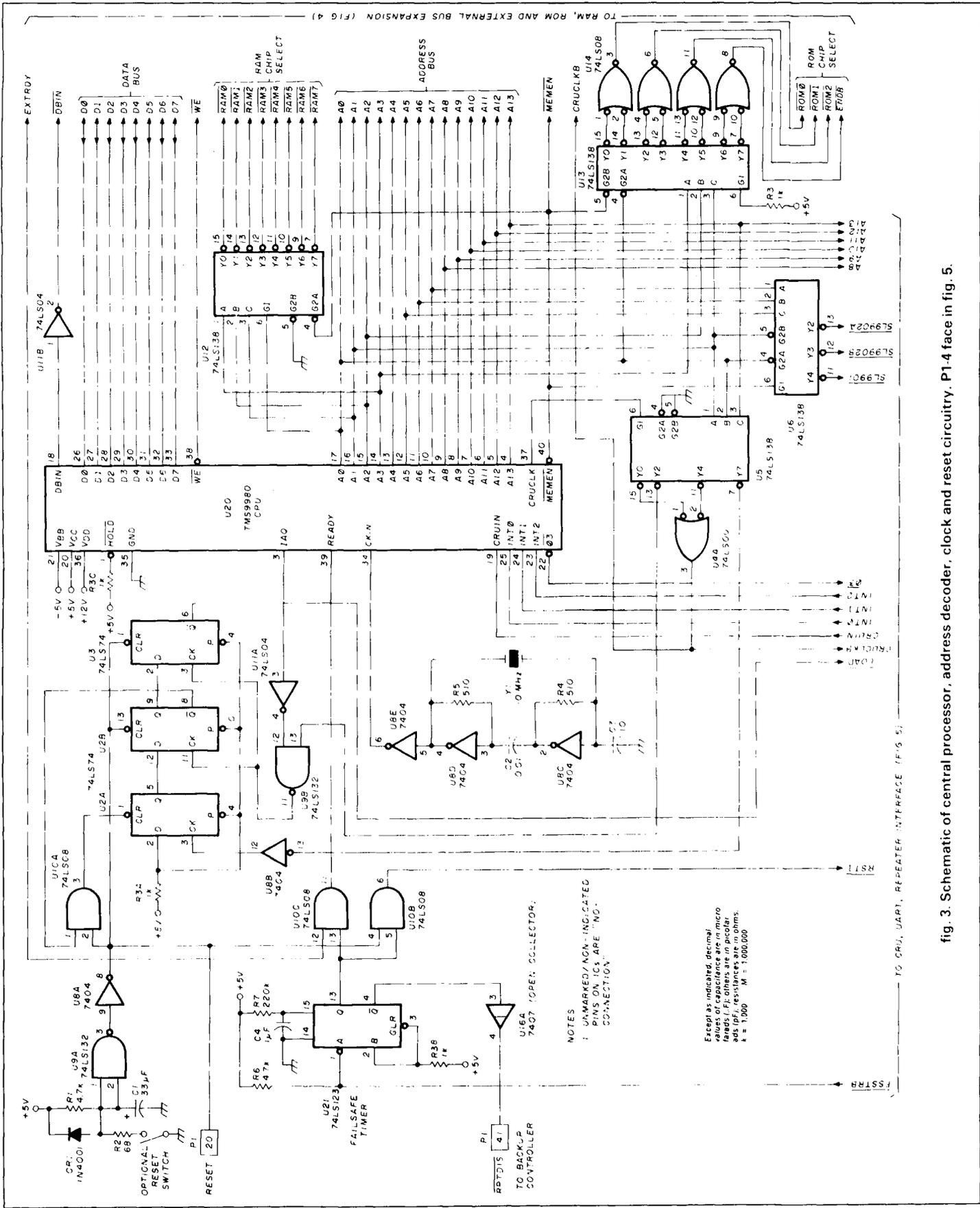


fig. 3. Schematic of central processor, address decoder, clock and reset circuitry. P1-4 face in fig. 5.

NOTES  
 : UNMARKED/ NON-INDICATED  
 PINS ON ICs ARE "NO"  
 CONNECTION"

Except as indicated, decimal  
 values of capacitance are in micro  
 farads (μF), others are in picofarads  
 (pF), resistances are in ohms,  
 k = 1,000 M = 1,000,000

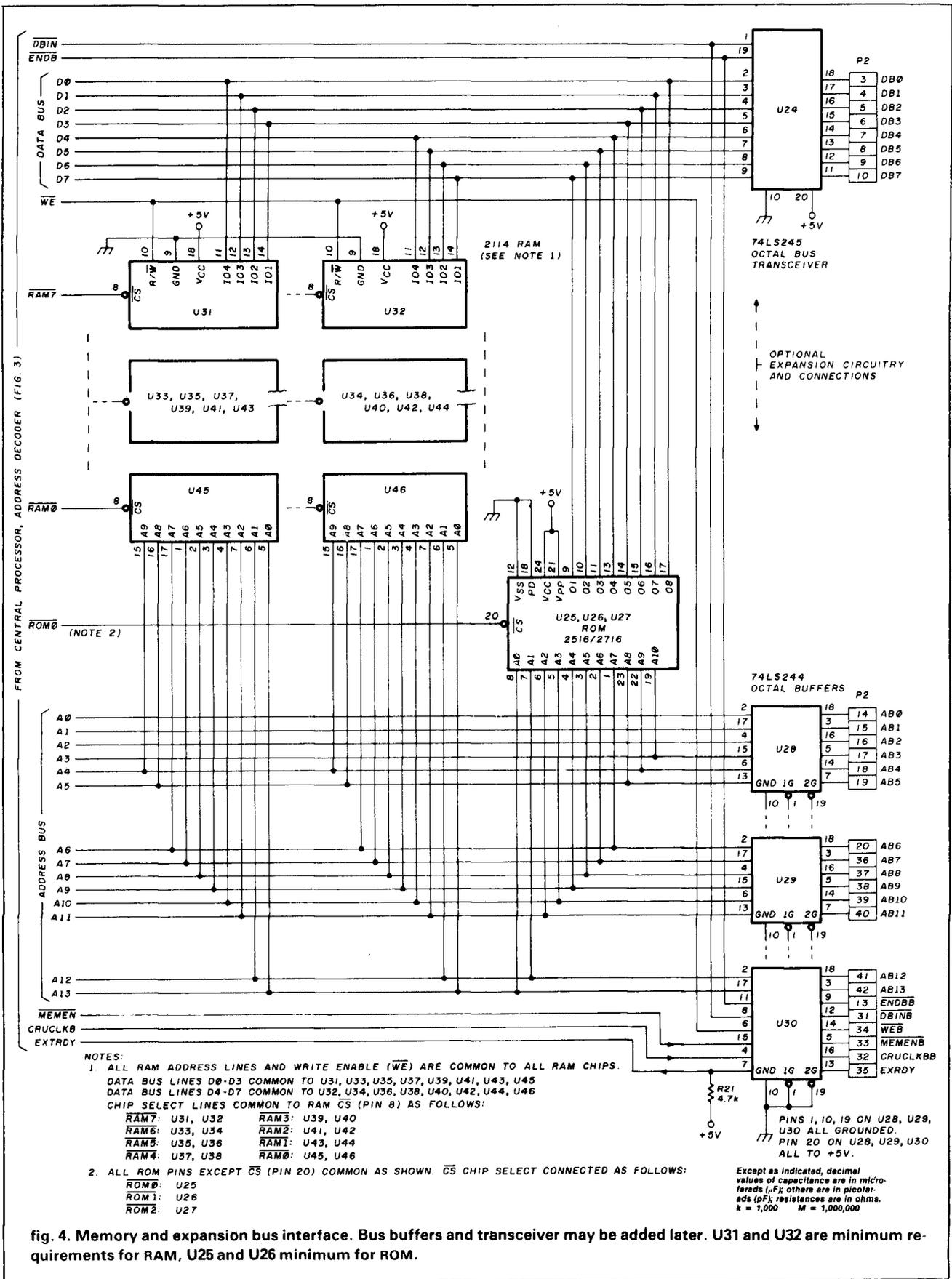


fig. 4. Memory and expansion bus interface. Bus buffers and transceiver may be added later. U31 and U32 are minimum requirements for RAM, U25 and U26 minimum for ROM.

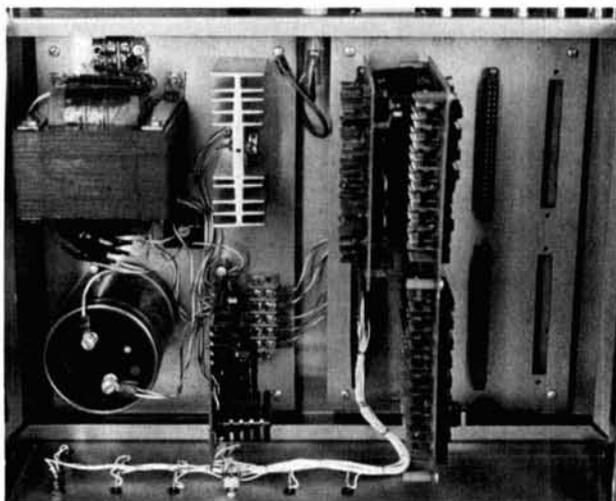


photo 1. Top view of controller chassis with power supply. New controller is long board in second slot. Stand-offs protect wire-wrap pins on IC sockets. First slot contains old controller, smaller board toward chassis rear. Small board in first slot toward front panel contains LED resistors and wire connections to front panel. Empty slots are for future expansion. Edge-connector socket pairs wired in parallel with P1/S1 toward front.

terfaces is provided by Schmitt-input gate U9A, R1, C1 through U8A and U10B to the  $\overline{RSTI}$  line. A normally open reset switch may be added for testing.  $\overline{RESET}$  at P1-20 to reset future external circuits.

The failsafe timer one-shot at U21 is re-triggered by the program through  $\overline{FSSTRB}$  every 16.7 milliseconds. As long as the controller is operational,  $\overline{RPTDIS}$  at P1-41 remains low and disables the backup controller. Controller failure will make  $\overline{RPTDIS}$  high and enable the backup; a TTL pull-up resistor is located in the backup controller.

Flip-flops U2 and U3 generate proper  $\overline{LOAD}$  timing for the interface chips with the help of decoder U5 and gate U9B. The ready signal input to the CPU (U20-39) must be high for normal operation with memory; the low state causes a CPU wait mode, to allow for access with slow memory. AND gate U10C keeps the ready signal high via the failsafe one-shot and expansion signal EXTRDY.

RAM is organized in 1K banks, chip-pairs selected by U12. ROM is in 2K banks, selected by U13 and U14.  $\overline{ENDB}$  is a fourth 2K bank select for expansion. U6 selects the interface chips and is wired for selecting one of three 32-bit CRU I/O bit groups. Addressing is detailed in the last section.

## memory and bus expansion

Fig. 4 is a simplified memory schematic. Static RAM uses 2114 devices having a 1K by 4-bit structure. Address lines A4 to A13 and write enable WE are common to all RAM chips, but data bus lines

must be split as indicated. RAM chip select lines  $\overline{RAM0}$  to  $\overline{RAM7}$  must be common only to a pair of 2114s.

All ROM pins except chip selects  $\overline{ROM0}$  to  $\overline{ROM2}$  are common. Either a 2516 or 2716 EPROM may be used for ROM, but there is a slight programming difference between the two. Both RAM and ROM may use 450 nanosecond access time devices.

A minimum system must have U25, U26, U31, and U32 installed. All memory sockets are wired for ease of check-out. The board in photo 2 shows 4K RAM installed for program verification. The memory map is seen in fig. 4A.

Bus transceiver U24 and bus buffers U28 to U30 are needed only if expansion is considered. R21 must remain to hold EXTRDY high if U30 is removed.

## talking to the rest of the system

The TMS9901 Programmable Systems Interface (PSI) is the key device in fig. 5. It provides interrupt masking, priority encoding, I/O ports, and an interval timer in one package. It also handles interrupts from the TMS9902 Universal Asynchronous Receiver/Transmitter (UART) at U17 and U18.

The 9901 communicates with the CPU through the CPU's communications register unit (CRU), an internal serial interface within the 9980. (The CRU operation is covered briefly later in this article, but the reader is referred to the reference for detail.)

The open-collector buffers to the repeaters and

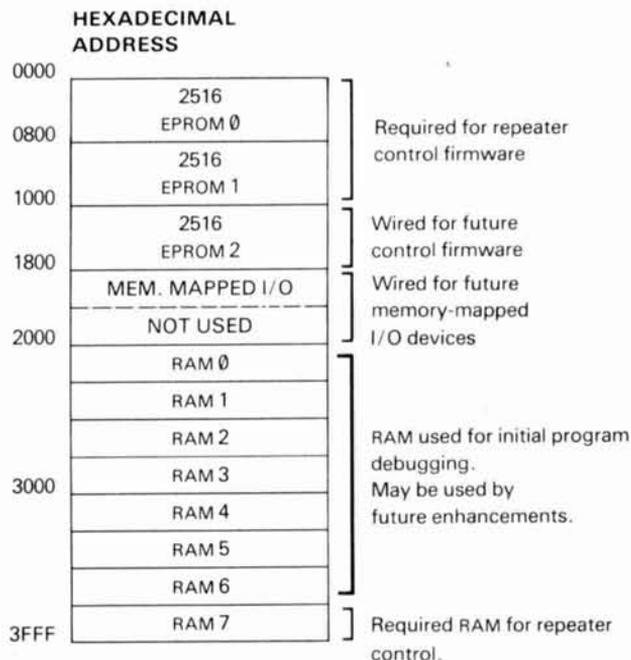



fig. 4A. Memory map of controller. Monitor ROM located in \$0000 to \$07FF address. Minimum RAM in address location \$3D00 to \$3FFF (\$ = hexadecimal).




front panel controls are identical circuit groups to each repeater. Mnemonics for the signals have an A suffix for the 2-meter repeater, a B suffix for the 220-MHz repeater. Direct repeater controls are PTT (push to talk), IDOSC (ID tone or 'oscillator'), and SQOP (squellch open). Other signal lines in each group refer to the front panel controls and indicators shown in **fig. 6A** and in **photo 3**.

PTT is low to transmit. Pull-up for the open-collector buffers (U16E and U15D) is provided within the repeater chassis. The CW identification tone is provided by programming the first-level interrupt period of 512 microseconds for a square-wave frequency just under 1 kHz. RC filtering at the IDOSC output produces a triangular waveform with an amplitude of about 5 volts peak-peak.

Remote shutdown is common to both controllers, but the direct telephone interface is within the old controller. Two rings on the landline will cause SHUTDOWN to go low, disabling the main controller. SHUTDOWN is TTL-compatible but requires R18 to hold U19-20 high when the backup controller is removed.

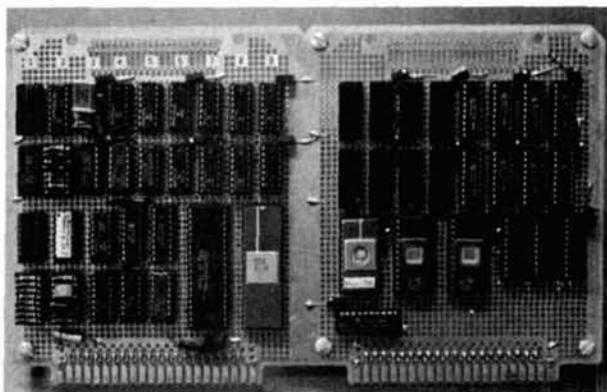

**photo 2.** Photo of controller board made just before final circuit freeze. All ICs are socketed on prototype board. Except for supply bypass capacitors, all discrete components mounted on DIP plugs. Number labels were construction references.

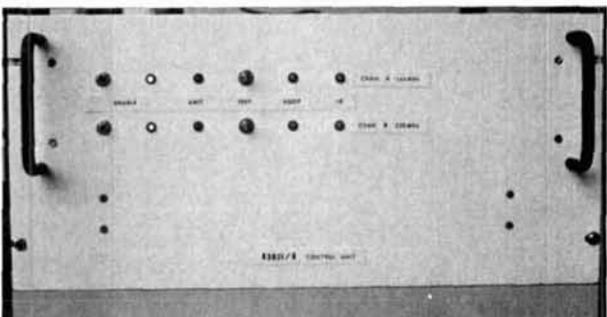

**photo 3.** Front view of front panel controls and indicators.

The RS-232 terminal connections (completed in **fig. 6C**) use high-voltage buffers in U22 and U23 for an ASR-733 terminal. Other devices can be used to interface the UART at U18. The terminal is connected directly to the new controller, and not used in the backup.

The power demand of the single-board controller is 3 A at +5 Vdc, 2 mA at -5 Vdc, 0.2 A at +12 Vdc, and 0.1 A at -12 Vdc. The +5 Vdc supply demand is dependent on the amount and type of memory. A well-regulated supply should be used, but the current should be calculated for your own configuration.

## manual control and indication

The front panel controls are not an absolute requirement, but do provide local control for testing and a quick indication of operation.\* The 2-meter control and indication is shown in **fig. 6A**; the 220 MHz arrangement is identical except for interconnecting pins.

The condition of the ENABLE switch is periodically read by the program. Switch status, shutdown signal, and a flag in memory will determine if the particular transmitter should be turned on when requested. The ENABLE status is displayed by the program as a check of all conditions.

The XMIT display lights up whenever a repeater is transmitting. The TEST switch controls two methods of transmit: manual — without microprocessor control — if the switch is held to the left, or simulation of squellch-open with processor control if it is held to the right. The SQOP display indicates the latter simulation, or normal squellch-open condition, of the repeater.

The ID LED is driven from the same source as the audio tone. Since this signal is a fifty-percent duty cycle, the current limiting resistor is smaller, creating a more uniform brightness.

Four keyboard commands are recognized. An operator can type U on the terminal to update the time, T to print current program time, M to modify the clock, and S to print the current system status. Other entries are ignored. The time correction is the number of seconds to be added to the internal clock each day; there is no provision for tweaking the system clock frequency.

## construction

The controller was wire-wrapped on a prototype board, as shown in **fig. 7** and **photo 2**. Bypass capacitors for the +5 V supply line were soldered directly on the board, one for every three ICs and one

\*User-friendly controls and terminal commands benefit the non-computer-ist in your repeater committee.

# NEW LOW-NOISE PREAMPS RECEIVING CONVERTERS TRANSMIT CONVERTERS

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.



Models LNA( ), P30, and P432 shown

Model	Tunable Freq Range	Noise Figure	Gain	Price
LNA 28	20-40	0.9 dB	20 dB	\$39.95
LNA 50	40-70	0.9 dB	20 dB	\$39.95
LNA 144	120-180	1.0 dB	18 dB	\$39.95
LNA 220	180-250	1.0 dB	17 dB	\$39.95
LNA 432	380-470	1.0 dB	18 dB	\$44.95

## ECONOMY PREAMPS

Our traditional preamps, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freq. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

- P30K, VHF Kit less case \$14.95
- P30C, VHF Kit with case \$20.95
- P30W, VHF Wired/Tested \$29.95
- P432K, UHF Kit less case \$18.95
- P432C, UHF Kit with case \$24.95
- P432W, UHF Wired/Tested \$33.95

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

## HELICAL RESONATOR PREAMPS



Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49.95
HRA-220	213-233 MHz	\$49.95
HRA-432	420-450 MHz	\$59.95



Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	Antenna Input Range	Receiver Output
<b>VHF MODELS</b>	28-32	144-148
	50-52	28-30
Kit \$44.95	50-54	144-148
Less Case \$39.95	144-146	28-30
Wired \$59.95	145-147	28-30
	144-144.4	27-27.4
	146-148	28-30
	144-148	50-54
	220-222	28-30
	220-224	144-148
	222-226	144-148
	220-224	50-54
	222-224	28-30

	Antenna Input Range	Receiver Output
<b>UHF MODELS</b>	432-434	28-30
	435-437	28-30
Kit \$54.95	432-436	144-148
Less Case \$49.95	432-436	50-54
Wired \$74.95	439.25	61.25

**SCANNER CONVERTERS** Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only \$79.95.

**SPECIAL FREQUENCY CONVERTERS** made to custom order \$119.95. Call for details.

## SAVE A BUNDLE ON VHF FM TRANSCEIVERS!

FM-5 PC Board Kit - **ONLY \$159.95** complete with controls, heatsink, etc. 10 Watts, 5 Channels, for 6M, 2M, or 220



Cabinet Kit, complete with speaker, knobs, connectors, hardware. Only \$59.95

**REPEAT OF A SELLOUT!**

While supply lasts, get \$59.95 cabinet kit free when you buy an FM-5 Transceiver Kit. Where else can you get a complete transceiver for only \$159.95?

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 watts output.

	Exciter Input Range	Antenna Output
For VHF,	28-30	144-146
Model XV2	28-29	145-146
Kit \$79.95	28-30	50-52
Wired \$119.95	27-27.4	144-144.4
(Specify band)	28-30	220-222
	50-54	220-224
	144-146	50-52
	50-54	144-148
	144-146	28-30
For UHF,	28-30	432-434
Model XV4	28-30	435-437
Kit \$99.95	50-54	432-436
Wired \$149.95	61.25	439.25
	144-148	432-436*


\*Add \$35 for 2M input

**FREE OFFER**


For limited time, buy a transmit converter above with 40-45W PA (\$129.95) and get \$39.95 cabinet FREE.



## LOOK AT THESE ATTRACTIVE CURVES!

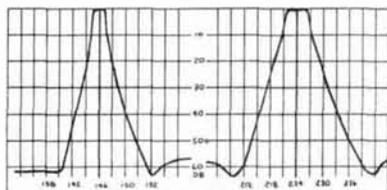

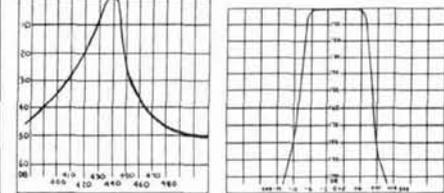
R144 & R220 Front Ends, HRA 144/220, & HRF-144/220



R451 Receiver Front End

Rcvr I-F Selectivity

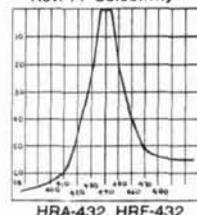Typical Selectivity Curves of Receivers and Helical Resonators.



HRA-432, HRF-432

- Call or Write for **FREE CATALOG** (Send \$1.00 or 4 IRC's for overseas mailing)
- Order by phone or mail • Add \$2 S & H per order (Electronic answering service evenings & weekends) Use VISA, MASTERCARD, Check, or UPS COD.

**hamtronics, inc.**

65-Y MOUL RD. • HILTON NY 14468  
Phone: 716-392-9430

Hamtronics® is a registered trademark

**AT LAST —  
A REPEATER  
YOU CAN AFFORD!**

For years, Hamtronics® Modules have been used by individual hams and manufacturers to make repeaters. Now, in the Hamtronics tradition of top quality and superb value, we are proud to offer a complete repeater package.



**JUST LOOK AT THESE PRICES!**

Band	Kit	Wired/Tested
6M, 2M, 220	\$595	\$745
440	\$645	\$795

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

**CALL OR WRITE FOR COMPLETE DETAILS.**


Also available for remote site linking/crossband & 10M.

**FEATURES:**

- SENSITIVITY SECOND TO NONE; TYPICALLY 0.15 uV ON VHF, 0.2 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY-TUNE TRANSMITTER; UP TO 20 WATTS OUT.

**HIGH QUALITY MODULES FOR  
REPEATERS, LINKS, TELEMETRY, ETC.**

**INTRODUCING —  
NEW 1983 RECEIVERS**

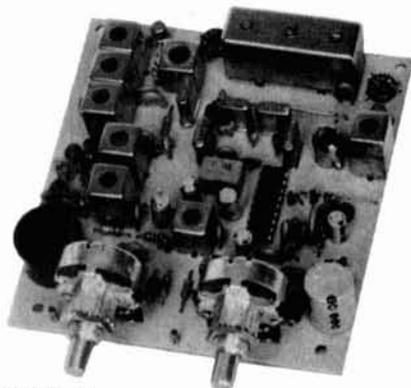

R144 Shown


- **R144/R220 FM RCVRS** for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity (curves at left). AFC incl., xtal oven avail. Kit only \$119.95
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.2 uV sens. Kit only \$119.95.
- **R76 FM RCVR** for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only \$109.95. Also avail w/4 pole filter, only \$94.95/ kit.
- **R110 VHF AM RECEIVER** kit for VHF aircraft band or ham bands. Only \$84.95.
- **R110 UHF AM RECEIVER** for UHF uses, including special 296 MHz model to hear SPACE SHUTTLE. Kit \$94.95.




- **HELICAL RESONATOR FILTERS** available separately on pcb w/connectors.

HRF-144 for 143-150 MHz \$34.95  
HRF-220 for 213-233 MHz \$34.95  
HRF-432 for 420-450 MHz \$44.95

(See selectivity curves at left.)

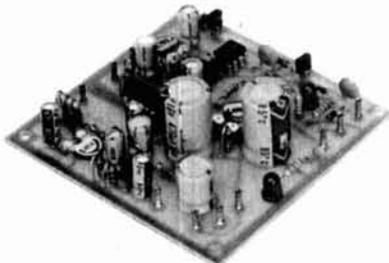


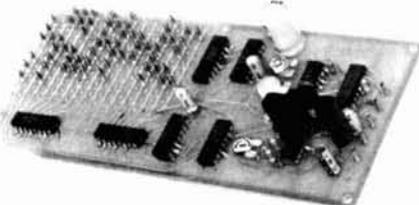- **COR KITS** With audio mixer and speaker amplifier. Only \$29.95.
- **CWID KITS** 158 bits, field programmable, clean audio. Only \$59.95.



- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Only \$18.00.

**TRANSMITTERS AND  
ACCESSORIES**

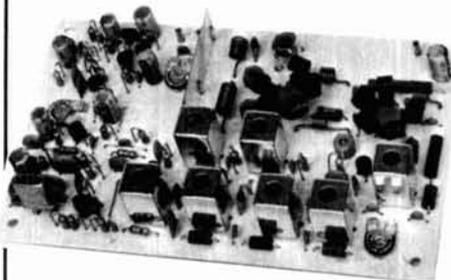

- **T51 VHF FM EXCITER** for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts continuous. Kits only \$59.95



- **T451 UHF FM EXCITER** 2 to 3 Watts on 450 ham band or adjacent. Kits only \$69.95.
- **VHF & UHF LINEAR AMPLIFIERS.** Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Kits from \$69.95.

**hamtronics®**

for every two memory chips. All other discrete components mount on DIP plugs.

A 12 × 17 × 2 inch (30 × 43 × 5 cm) Bud chassis is bracket-mounted to the rack panel. Two 7 × 11 inch (18 × 28 cm) aluminum plates hold the power supply and four pairs of card edge connectors. All interface connectors, the line fuse, and switch are mounted on the rear face of the chassis.

### programming and checkout

The program was coded in short routines, most containing less than fifty lines. The code is heavily commented to facilitate debugging and to provide good documentation. Documentation is essential if you want anyone, even the programmer, to understand the program at a later date.

The program was initially programmed into the EPROM and installed on the board. A short routine was executed to move the program from ROM into RAM. Execution from RAM was under control of the monitor, allowing correction and patching. The monitor used was TIBUG™.

The EPROMs are re-programmed after checkout so

the program can execute from a ROM address area rather than RAM.

Hardware and system checkout procedure used the front panel TEST switch to simulate the receiver squelch-open signal until most of the program bugs were found. Later, the PTTA line was jumpered to SQOPB and PTTB was jumpered to SQOPA; with both channels enabled, the controller would alternately transmit on 2 meters and 220 MHz. We ran the controller only in this mode for several days in the presence of the club's HF and repeater equipment to verify that the controller was rf compatible. No interference was observed. A typical printout is seen in fig. 8.

### history

Total construction time for this project was approximately four months. Most of the board wiring and program design was completed during a two-week vacation. The most time-consuming task was packaging the controller.

The controller was installed in the K5OJI repeater in January, 1981. Up to the time of this writing,

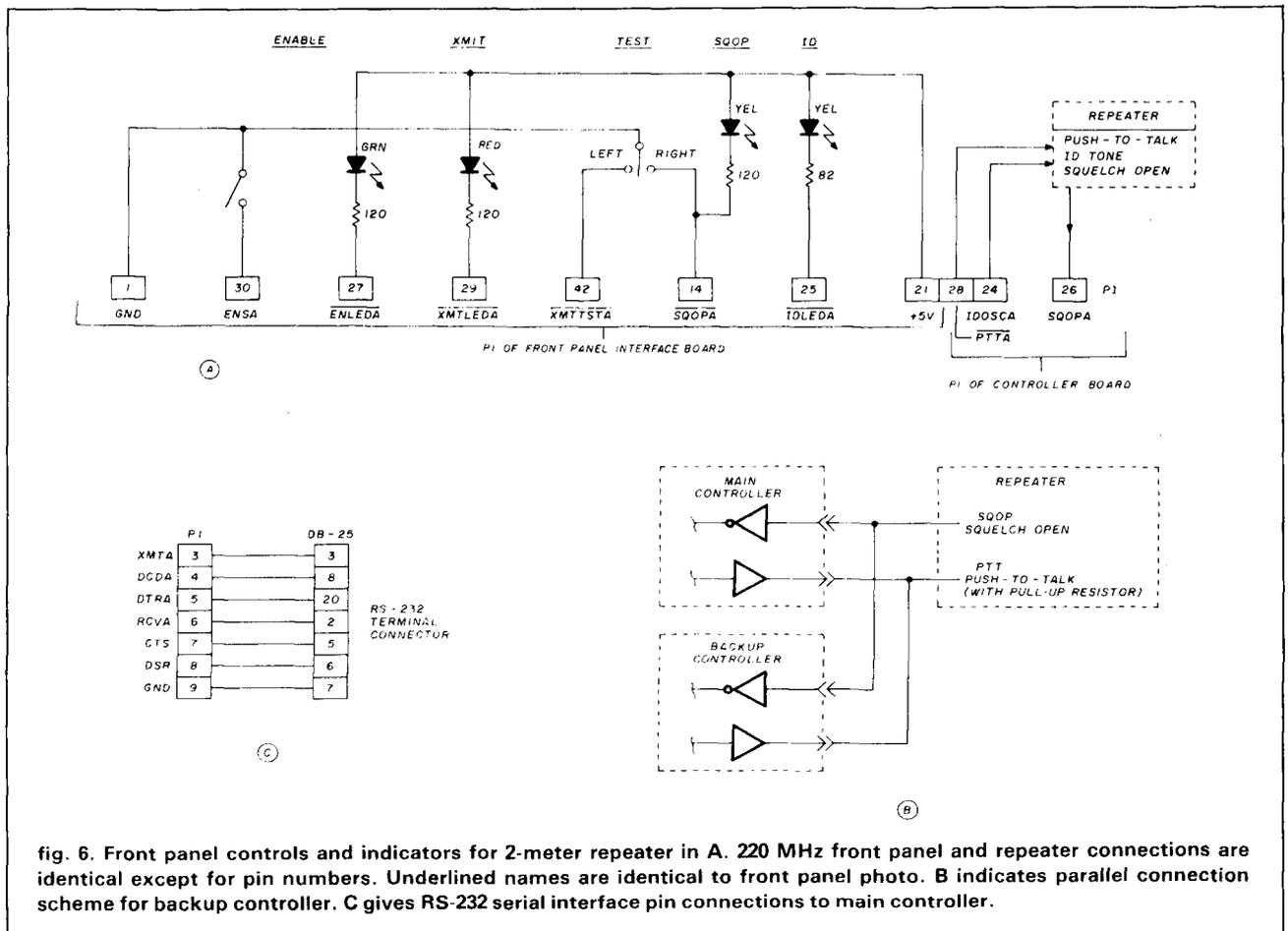


fig. 6. Front panel controls and indicators for 2-meter repeater in A. 220 MHz front panel and repeater connections are identical except for pin numbers. Underlined names are identical to front panel photo. B indicates parallel connection scheme for backup controller. C gives RS-232 serial interface pin connections to main controller.

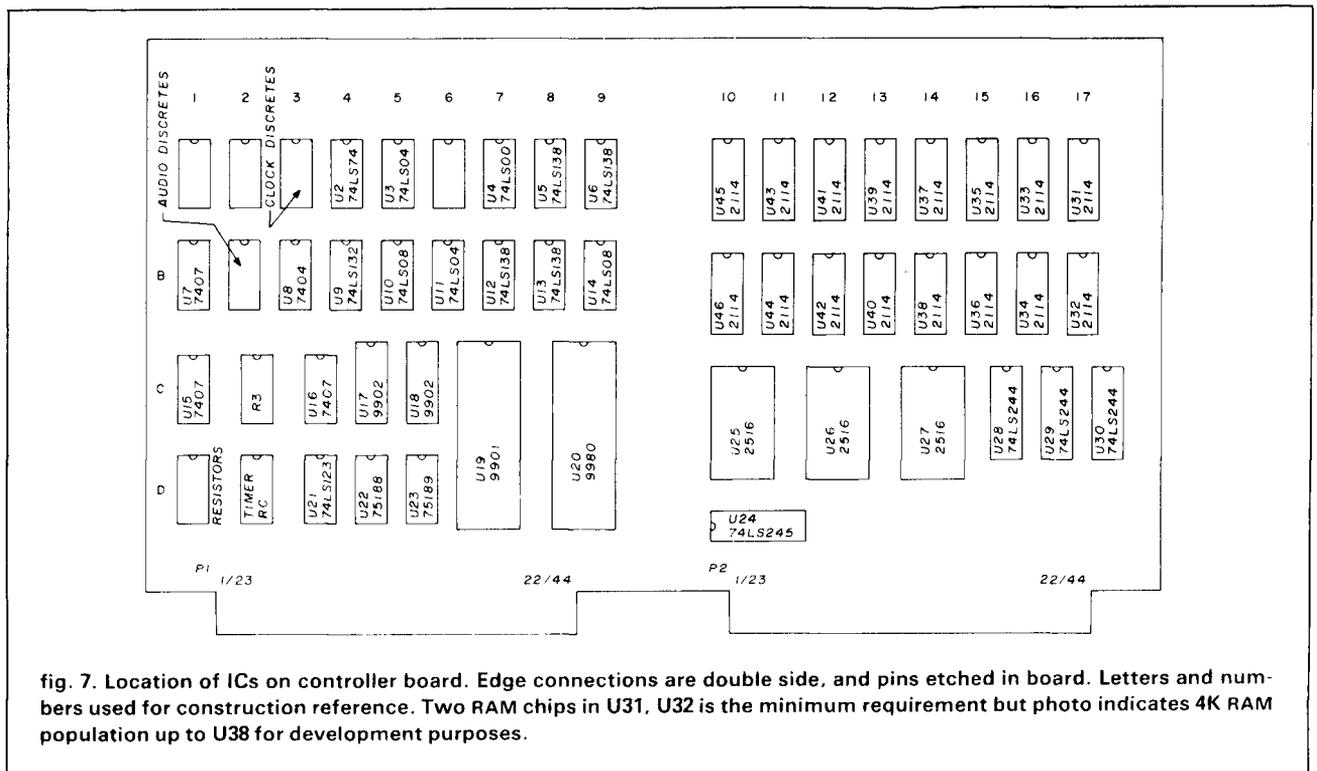


fig. 7. Location of ICs on controller board. Edge connections are double side, and pins etched in board. Letters and numbers used for construction reference. Two RAM chips in U31, U32 is the minimum requirement but photo indicates 4K RAM population up to U38 for development purposes.

about two years, we had only one failure due to bad memory chips. Since the backup controller picked up when the main unit failed, the repeater was never off the air. The bad chips were quickly located and replaced.

The controller is reliable, expandable, and relatively simple. It can be made on a prototype board or it may be an adaptation of commercially available microprocessor boards. Hardware and software is designed so other features may be added easily.

Based on observation of microprocessor loading, the controller should be able to control three repeaters simultaneously. The Level 1 interrupt is the heaviest CPU load and provides the ID tone; a separate hardware oscillator will relieve much of the first-level interrupt handling.

This project would not have been possible without the help of WB8CEB for most of the program editing and N5JS and AJ5L who maintained the rf portions of the repeaters.

A listing of the control program is available on an 8-inch CPM™ compatible disk available from the author for \$15.00. This disk contains the program listing and an object file for programming EPROMs. The disk is single-sided, single-density and the program uses 26 sectors at 128 bytes per sector.

### for the computer technician

Computer technology is a specialized area. Some

```

ENTER CURRENT TIME HHMM: 2040
K50J1 RPT TIME IS 2041
TIME=2100 XMT=1400 000=00 TMO=01 ID=10 KCT=07
TIME=2200 XMT=0112 000=00 TMO=00 ID=07 KCT=00
TIME=2300 XMT=0044 000=01 TMO=00 ID=03 KCT=01
TIME=0000 XMT=0000 000=00 TMO=00 ID=00 KCT=01
TIME=0100 XMT=0031 000=01 TMO=00 ID=02 KCT=00
TIME=0200 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=0300 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=0400 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=0500 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=0600 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=0700 XMT=1600 000=04 TMO=00 ID=09 KCT=03
TIME=0800 XMT=0277 000=02 TMO=00 ID=14 KCT=03
TIME=0900 XMT=0837 000=05 TMO=00 ID=09 KCT=00
TIME=1000 XMT=0000 000=00 TMO=00 ID=00 KCT=00
TIME=1100 XMT=0000 000=00 TMO=00 ID=00 KCT=00

```

fig. 8. Typical printout of part of one day's operation.

explanations and technical arguments follow which will serve the needs of the computer specialist who undertakes this project. ham radio cannot take sides in programming techniques, but a strong relationship between hardware and software is integral to the successful design of this system, and the computer technician should be aware of this before beginning the project. Editor.

Reentrant programming is sometimes confused with recursive programming; we offer the following abbreviated definition from Granino Korn's *Microcomputers for Scientists and Engineers*:

"A special case occurs where a subroutine is inter-

table 2. TMS9901 PSI bit assignments.

select bit	CRU read data	CRU write data
0	Control bit (1)	Control bit
1	INT1-/CLK1 (2)	MASK1/CLK1 (3)
2	INT2-/CLK2	MASK2/CLK2
3	INT3-/CLK3	MASK3/CLK3
4	INT4-/CLK4	MASK4/CLK4
5	INT5-/CLK5	MASK5/CLK5
6	INT6-/CLK6	MASK6/CLK6
7	INT7-/CLK7	MASK7/CLK7
8	INT8-/CLK8	MASK8/CLK8
9	INT9-/CLK9	MASK9/CLK9
10	INT10-/CLK10	MASK10/CLK10
11	INT11-/CLK11	MASK11/CLK11
12	INT12-/CLK12	MASK12/CLK12
13	INT13-/CLK13	MASK13/CLK13
14	INT14-/CLK14	MASK14/CLK14
15	INT15-/INTREQ	MASK15/RST2- (4)
16	--	Fail-safe strobe
17	--	LEVEL 1 INTERRUPT INDICATOR
18	--	LEVEL 2 INTERRUPT INDICATOR
19	--	LEVEL 3 INTERRUPT INDICATOR
20	--	LEVEL 4 INTERRUPT INDICATOR
21	Remote shutdown	--
22	ID Ch A	ID Ch A
23	--	ENABLE Ind Ch A
24	SQ OP Ch A	--
25	--	XMIT Ch A
26	ENABLE SW Ch B	--
27	ID Ch B	ID Ch B
28	--	ENABLE Ind Ch B
29	SQ OP Ch B	--
30	--	XMIT Ch B
31	ENABLE SW Ch B	--

- (1) 0 = interrupt mode, 1 = clock mode  
 (2) Data present on INT pin (or clock value) will be read regardless of mask value.  
 (3) In interrupt mode writing a 1 into mask will enable interrupt; a 0 will disable the interrupt.  
 (4) Writing a zero to bit 15 while in the clock mode executes a software reset of the I/O pins.

rupted and the interrupt calls the *same* subroutine. A program may fail on return from interrupt. Subroutines designed to work properly on interrupt and restoration from interrupt are called 'reentrant.' A good way to obtain reentrant subroutines is to provide temporary storage of addresses and register contents in 'stack' storage. Real-time computation with many interrupt-driven segments make reentrant programming desirable."

When many repeaters need be controlled, the only additional software necessary should be new parameter tables and calls to the routines handling data in these tables. Not only should the data manipulation instructions be reentrant, but so should I/O instructions; controlled devices will not always have the same I/O addresses.

The I/O structure of the 8080 does not lend itself to reentrant programming. I/O routines must be pro-

grammed once for each channel, and you must decide which piece of code to execute, or the code must be written to be self-modifying: the program modifies the instruction set about to be executed before entering the set. The instruction must reside in RAM to be self-modifying. The I/O of the 8080 must transfer eight bits at once, which requires extra logical instructions. This means that the bits which control the repeater must be set, reset, and tested, or only one function can be assigned to each I/O port.

While you need subroutines to load and test an 8080 memory location, a single 9900 instruction performs the same function. The 9900 I/O structure lends itself to reentrant programming. The 9900, through its CRU, may transfer from one to sixteen bits with a single instruction. This makes it suitable for multiple-control applications.

The address bus I/O address is generated by add-

ing the CRU bit address in the instruction to the contents of the CRU base register, one of the user-accessible registers. By setting base register contents differently for each channel, the same I/O instructions can be used to control the same function on different channels.

Since all general purpose registers are in memory, only the CPU program counter, status register, and workspace pointer need be saved during an interrupt. These are saved and restored automatically. The programmer does not have to keep track of which registers to save or restore.

The TMS9980 CPU is part of the 9900 family and uses the same instruction set. This class of processor differs from earlier designs and readers should refer to the reference material for exact details. The following will help you understand the CRU and how it is used in the K50J1 repeater.

### understanding the CRU

The communications-register-unit uses a dedicated bit-addressable interface for I/O between the CPU and 9901, 9902 devices. The CRU interface in the system is the address bus and three signal lines: CRUCLK, CRUIN, and CRUOUT (multiplexed with address line A13 on the 9980). The 9901 and 9902s are enabled via U6 by address lines A0, A1, A5, A6, and A7 while address lines A8 through A12 select the single bit to be input or output. The CRU transfers data one bit at a time, serially, on the CRUIN and CRUOUT lines.

For output, the address lines are set to point to the desired output bit and that bit of data is put on the CRUOUT (A13) line. CRUCLK then clocks the data into the selected device. For input, the address lines are set to point at the desired input, then clocked into the CRU through the CRUIN line. There is no external signal to indicate when an input is read.

**Table 1** lists the hardware and software addresses for the CRU. The 9901 occupies thirty-two bits of CRU input/output space and assignments are given in **table 2**. **Table 3** is a complete parts list for the controller.

**Table 2** needs further explanation: bit 0 controls the mode of bits 1 to 15. If bit 0 is logic 0, the 9901 is in interrupt mode. Writing to bits 1 to 15 sets an internal mask for passing or ignoring an interrupt level.

The 9901 is in clock mode (internal interval timer) if bit 0 is logic 1. Writing to bits 1 to 14 loads a value into the timer's count decremter. As the timer counts down to zero, an interrupt is issued and the timer resets to decrement value. Reading bits 1 to 14 will read the current value of the decremter. Reading bit 15 inputs the status of the interrupt request while writing to bit 15 initiates a reset of input/output pins.

**table 3. Controller parts list.**

quantity	type	
1	TMS9980	U20
1	TMS9901	U19
2	TMS9902	U17, U18
2 min., 16 max.	2114	U31 to U46
2 min., 3 max.	2516	U25 to U27
1	74LS00	U4
1	74LS04	U11
1	7404	U8
3	7407	U7, U15, U16
2	74LS08	U10, U14
2	74LS74	U2, U3
1	74LS123	U21
1	74LS132	U9
4	74LS138	U5, U6, U12, U13
3	74LS244	U28, U29, U30
1	74LS245	U24
1	75188	U22
1	75189	U23
<b>resistors</b>		
(all resistors are 1/4 W, 10% unless otherwise specified)		
1	220 K	R7
1	68 ohm	R2
2	82 ohm	front panel
6	120 ohm	front panel
2	510 ohm (5%)	R4, R5
2	2.2 K	R19, R20
6	4.7 K	R1, R6, R8, R13, R18, R21
6	15 K	R9, R10, R12, R14, R15, R17
2	1 K	R11, R16
1 DIP array	1 K	R3 (Beckman 899-1-1.0 K)
1	220 K	R7
<b>capacitors</b>		
(all capacitors are disk, 25 V min unless other specified)		
24	0.01 $\mu$ F	C2, C7, C8, C9, C11 to C30
2	0.1 $\mu$ F	C5, C6
1	1.0 $\mu$ F	C4
1	10 pF mica	C3
1	33 $\mu$ F	C1 (electrolytic, 10 V min.)
1	47 $\mu$ F	C10 (electrolytic, 10 V min.)
1	CY-18 crystal, 10 MHz	Y1
1	1N4001	CR1
2	LED, green	front panel
2	LED, red	front panel
4	LED, yellow	front panel
2	switch, SPDT, momentary-off-momentary	front panel
2	switch, SPST	front panel

Bits 16 to 31 are for I/O, the majority directly interfacing with the repeaters. Writing a 0 and then a 1 to bit 16 will re-trigger failsafe one-shot U21. Re-triggering must occur at a 60 Hz rate.

Bits 17 to 20 are monitor output which indicates the level of interrupt processing. Entering an interrupt routine sets the appropriate bit for that interrupt level. Completing an interrupt resets the bit. Oscilloscope monitoring verifies the interrupt and indicates CPU loading for each interrupt time. The first three

interrupt levels are used here with the fourth level reserved for future use.

Bit 21 is an input for remote shutdown via telephone line through the old controller. The old controller will shut down through its own interface circuitry and a low state of SHUTDOWN will disable the new controller.

Bits 22 to 26 are I/O control for the 2-meter repeater ("A" suffix mnemonics) while bits 27 to 31 are identical in function for the 220 MHz repeater ("B" suffix).

Interrupt level 3 is internal to the 9901. Interrupt levels 4 and 5 are hardwired to the interrupt outputs on both 9902s. The 9901 will prioritize interrupts, outputting an interrupt code of 0 for highest priority and 15 for lowest priority. The 9980 CPU interprets levels 3, 4, and 5 as interrupt levels 1, 2, and 3, respectively.

Each 9902 UART is assigned thirty-two bits of CRU and each may cause an interrupt from four separate events. Repeater control uses only the interval timer interrupt. The second 9902 (U18) is used solely for the timer, but could be used for a second serial interface.

## software

Author Warner claims that packaging the controller was the most time-consuming task and that software design was second. Judging from the 51 pages of program listing available, we might reverse that statement. The final excerpt contains some details on the program package.

The software design was to include as many features as possible and to break the program into small, easy-to-follow modules. These modules can be called by the appropriate interrupt processor module, depending on the desired frequency of execution. It would not be difficult to add modules for new features.

Modules communicate with each other (on the same and different interrupt levels) via semaphores, flags set in specific memory locations. Seven extended-operation (XOP) instructions are included for I/O with a keyboard/printer. The hardware will support a total of 16 XOPs, so users may add their own XOP routines.

Hardware reset causes an entry into the initialization section of the program. This initializes certain memory locations, I/O interfaces (including all interval timers), and the interrupt mask register in the 9901. Once accomplished, the program enables interrupts and begins execution of the program's polling loop.

The following program names are those included in the program. The interrupt level routines handle all the repeater control functions. Three levels of inter-

rupts are used. Level 1 is highest and occurs when the 9901 interval timer decrements to zero. Program segment C04 generates the CW ID tone on a Level 1 interrupt. This will generate a 1 kHz tone for each repeater.

Interrupt handlers are similar. First the appropriate CRU output bit is set to indicate initiation of processing at the particular interrupt. Register 1, used as an index register, is loaded with the address of the parameter table for one repeater. The proper routines for that repeater are then called to operate on the parameters. When processing for one repeater is complete, Register 1 is re-loaded with the address of the parameter table for the other repeater, and the same routines are called again. When all processing for the interrupt level is complete, interrupt hardware is enabled for the next interval timer decrement-through-zero. The CRU bit, indicating process in operation, is reset and control returns to the interrupted routine.

Level 2 interrupt is caused by the interval timer in the 9902 at U17. This timer is set to decrement through zero every 4.7 milliseconds. The routine labelled C01 is executed on a Level 2 interrupt and forms the ID tone length and beep.

Main repeater timing occurs at Level 3, generated every 16.7 milliseconds. Some system functions, such as time of day and checking for remote shutdown, are executed only once per interrupt. All other repeater routines must be executed once for each channel. Routines R00, R07, and R09 are called only once while repeater routines R01 through R05, R08 are called twice.

When no interrupts are being serviced, the polling loop at I03 is operating. This loop checks for keyboard inputs and checks flags that indicate printout of an hourly repeater status. Once each hour the interrupt level routines move the hourly status for each repeater to a print buffer, clear the next hour's status, and set a print request flag. The polling loop checks this flag and, if set, lists the status from the print buffer on the terminal. If both repeaters are enabled, 2-meter status is printed first.

Each status line printout includes the hour, the number of seconds of total transmission, the number of QSO periods, timeouts and IDs issued. For status purposes, a QSO is defined as a period of exchanges separated by no more than thirty seconds. The last printout column is the number of receptions too short to bring up the repeater.

## reference

1. *9900 Family Systems Design*, publication LCC4400, Texas Instruments, Incorporated.

ham radio

Mention this magazine and get a free gift

# Albia Electronics

Backed by Albia's famous warranty.

## DESIGN MATE™ 2B LOW COST, HAND HELD FUNCTION GENERATOR

### SPECIFICATIONS

- Frequency Range:** 10 Hz to 100 KHz in four ranges; 50 increment 10/1 calibrated dial calibrated within  $\pm 5\%$  of setting @ 10 Hz, 1 KHz and 100 KHz, 10 KHz.
- Waveforms:** Sine Wave: 2% THD over Frequency Range (Typical 1%); Triangle Wave: linearity better than 1% over frequency range; Square Wave: rise and fall times 200 nsec (Typical 100 nsec).
- Outputs:** Sine/Triangle — switch selectable; amplitude 0.1V to 10V peak to peak; impedance 600 Ohms; Square Wave — amplitude 0.1V to 10V peak to peak; impedance 600 Ohms.
- Power Req.:** 105 - 125 VAC, 50/60 Hz, 2.5 Watts
- Size:** 6.25" X 3.75" X 2"

MODEL NO. DM-2B  
STOCK NO. 15-0102

**\$99.99**

INCLUDES ALBIA'S FULL SATISFACTION WARRANTY



## LOW COST FREQUENCY METER MODULE DM-11 "5Hz to 100MHz"

Measure frequencies from 5Hz to 100MHz on your digital Voltmeter with a resolution of 3 1/2 digits — easy to use — perfect for field service — lab testing — home hobbyist! Connect the DM-11 to your DVM, set the DVM to the 2VDC range, connect a signal to the DM-11 via a BNC cable (not included) and measure the frequency of any source. Hi Lo Range LEDs ensure fast accurate readings.



### SPECIFICATIONS

- Frequency Range 5Hz to 100MHz
  - Input Impedance 1 MegOhm
  - Input Sensitivity: 100Hz 80MV  
100Hz 60MHz 30MV  
60MHz 70MV
  - Size 6.25" X 3.75" X 2"
  - External 9V DC power supply included
  - BNC input cable accessory Model PSA-2
- Stock No: 110027 add \$14.99

MODEL NO. DM-11  
STOCK NO. 15-0011

**\$69.00**

## LOW COST DM-8 CAPACITANCE METER MODULE

Connect this high quality low cost Capacitance Meter Module, DM-8 to your digital Volt Meter and turn it into a Digital Capacitance Meter — the Low Cost Way!



### SPECIFICATIONS

- 2V output
- Accuracy better than 5%
- Push to read range (button) from 1 pF to 20,000 F
- Zero Calibration control
- In one easy to use, self-contained package.
- Battery powered, with "push to read" battery saver circuit (9V batteries not included).
- Size - 6.25" X 3.75" X 2"
- Includes Model 336 Test Clips

MODEL NO. DM-8  
STOCK NO. 15-0008

**\$79.99**

Includes Albia's Satisfaction Warranty

PRICES & SPECIFICATIONS SUBJECT TO CHANGE • SPECIAL ENDS MAY 30th



FOR FASTER SERVICE USE YOUR CREDIT CARD.

## Albia Electronics

44 KENDALL STREET  
NEW HAVEN, CT. 06512

MOST ORDERS SHIPPED NEXT DAY.



**CALL TOLL FREE 1-800-243-6953**

9 AM  
5 PM  
EST


# 6-meter amplifier

A companion unit  
to the 2-meter  
and 1 ¼-meter amplifiers

This six-meter amplifier is a companion unit to the 2-meter and 1-1/4-meter amplifiers previously described in *ham radio* articles.<sup>1</sup> All three amplifiers are built using the same chassis configuration originally described by K2RIW for a stripline kilowatt for 432 MHz.<sup>2</sup> The 50-MHz version uses a conventional pi-network output with inductive tuning, and a coil simulated half-wave line for its input section. Both the tetrode (fig. 1) and the triode (fig. 2) versions will be discussed. Like its predecessors, the 50-MHz amplifier uses parallel combinations of any of the 4CX250 type tetrodes, the 8930 tetrodes, or the 8874 triodes. Metering and power supply connections are identical to the 2-meter and 1-1/4-meter amplifiers. Using a standard design for VHF/UHF amplifiers, a single power supply can be switched from one amplifier to another. Remote operation with a separate metering unit at the operating position or built into the power supply is another adaptation, useful particularly at 432 MHz.

These four 12 × 6 × 8 inch (30.5 × 15.2 × 20.3 cm) power amplifiers for the four popular VHF/UHF

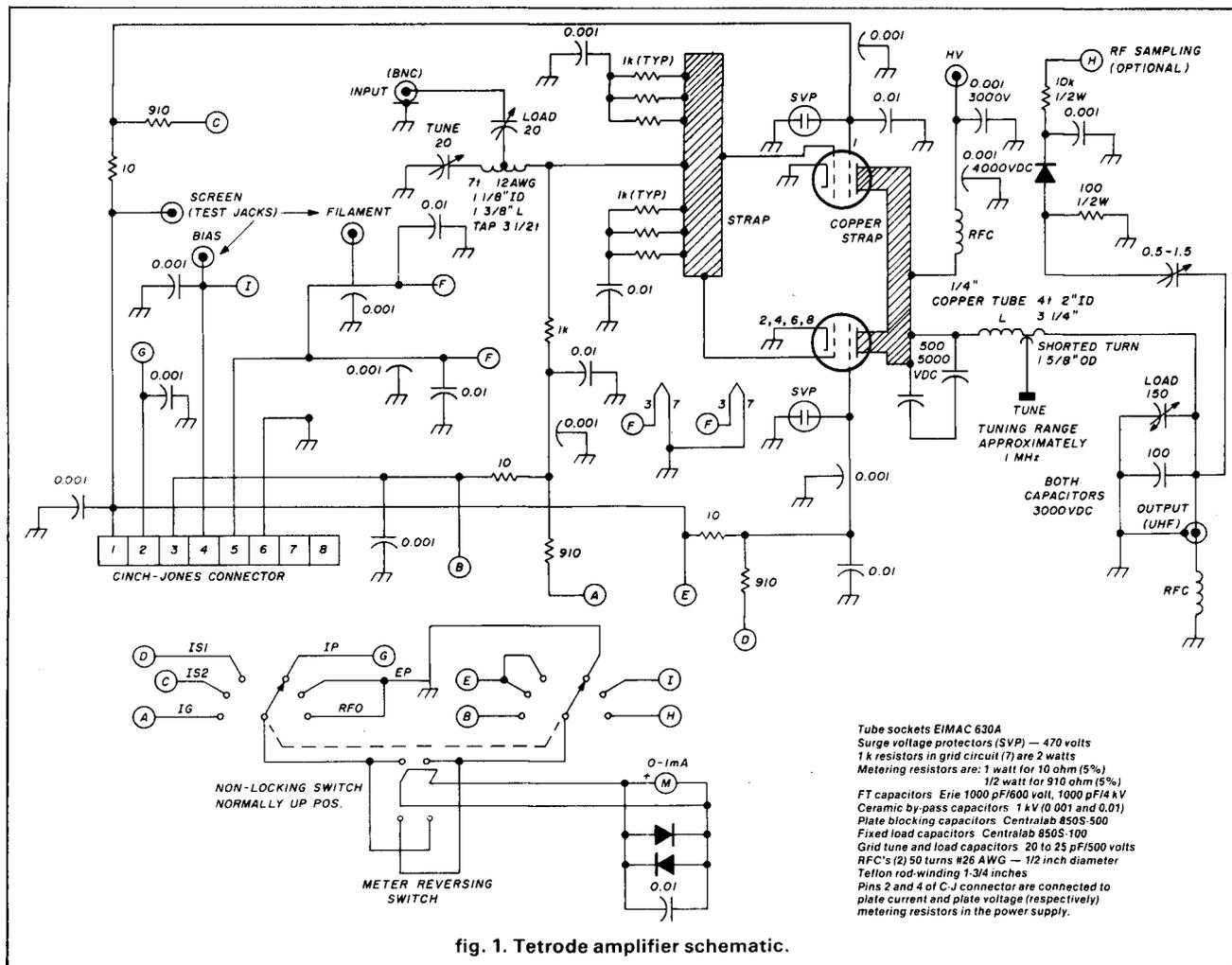By Fred J. Merry, W2GN, 35 Highland Drive —  
P.O. Box 546, East Greenbush, New York 12061



- Tube sockets EIMAC 630A
- Surge voltage protectors (SVP) — 470 volts
- 1 k resistors in grid circuit (7) are 2 watts
- Metering resistors are: 1 watt for 10 ohm (5%)
- 1/2 watt for 910 ohm (5%)
- FT capacitors: Erie 1000 pF/600 volt, 1000 pF/4 kV
- Ceramic by-pass capacitors: 1 kV (0.001 and 0.01)
- Plate blocking capacitors: Centralab 850S-500
- Fixed load capacitors: Centralab 850S-100
- Grid tune and load capacitors: 20 to 25 pF/500 volts
- RF C's (2) 50 turns #26 AWG — 1/2 inch diameter
- Teflon rod-winding 1-3/4 inches
- Plugs 2 and 4 of C-1 connector are connected to plate current and plate voltage (respectively) metering resistors in the power supply.

Amateur bands have been successfully duplicated hundreds of times. They are rugged and offer a proven performance developed by thousands of hours of testing and use over the past eight years. They provide flexible and reliable high-power operation.

By initially drilling and punching a set of chassis boxes for all four models (432, 220, 144, and 50 MHz), an amplifier can be converted from one band to another. This might be achieved by using a quick-change mechanical procedure for the four separate frequency-sensitive circuit elements.

### construction details

The essential dimensions for chassis drilling and punching are contained in the articles listed in reference 1. This article covers only construction details peculiar to the 50-MHz amplifier.


Referring to the schematic of the 50-MHz tetrode amplifier (fig. 1), notice that the two grids are connected by a copper strap between the sockets. The

two anodes are paralleled by a brass or copper plate assembly which uses fingerstock for connection to the anodes, providing a mounting for the plate blocking capacitors and a connection point for the high-voltage RFC. The dc circuitry is similar to that found in the previously described amplifiers.

In the triode amplifier (fig. 2), the rf section is exactly the same as that shown in fig. 1 except that rf chokes are used in the filament leads and in the cathode bias lead. The cathode bias and metering circuitry is conventional for a grounded grid amplifier. Two meters are used with the grid current meter on a non-locking switch to read plate voltage.
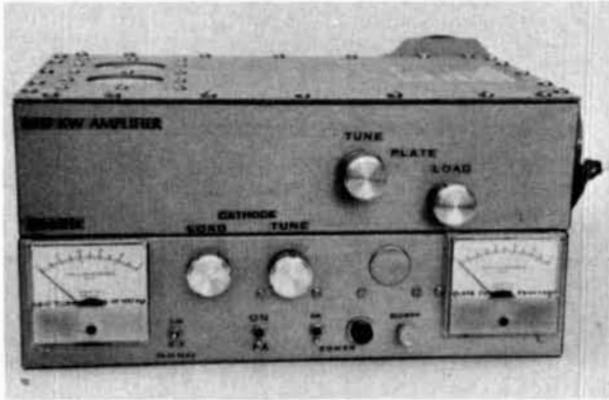
### control and safeguard options


The optional circuitry shown in fig. 2 provides examples of control and safeguard features which can be added to these amplifiers. The blower option provides 120 Vac on pins 2 and 4 of the cable connector. This permits powering the blower from a receptacle on the amplifier chassis, rather than running a lead




Tetrode amplifier — front view.


back to the power supply. An air switch is mounted in the blower air stream and connected via the blower connector to two power switches (one locking and one non-locking) and to pin 7 of the amplifier connector. Pin 7 is the power relay operate lead in the power supply.<sup>1</sup>

To turn the amplifier on, the locking-type power switch is switched to the on position and the non-locking (push-button type-momentary) switch is pressed to operate the power relay. The power relay energizes the power supply and provides 120 Vac on pins 2 and 4 to start the blower. With the blower up to speed, the air switch keeps the power relay actuated. Once the push button is released, the power supply relay is under the control of the air switch.

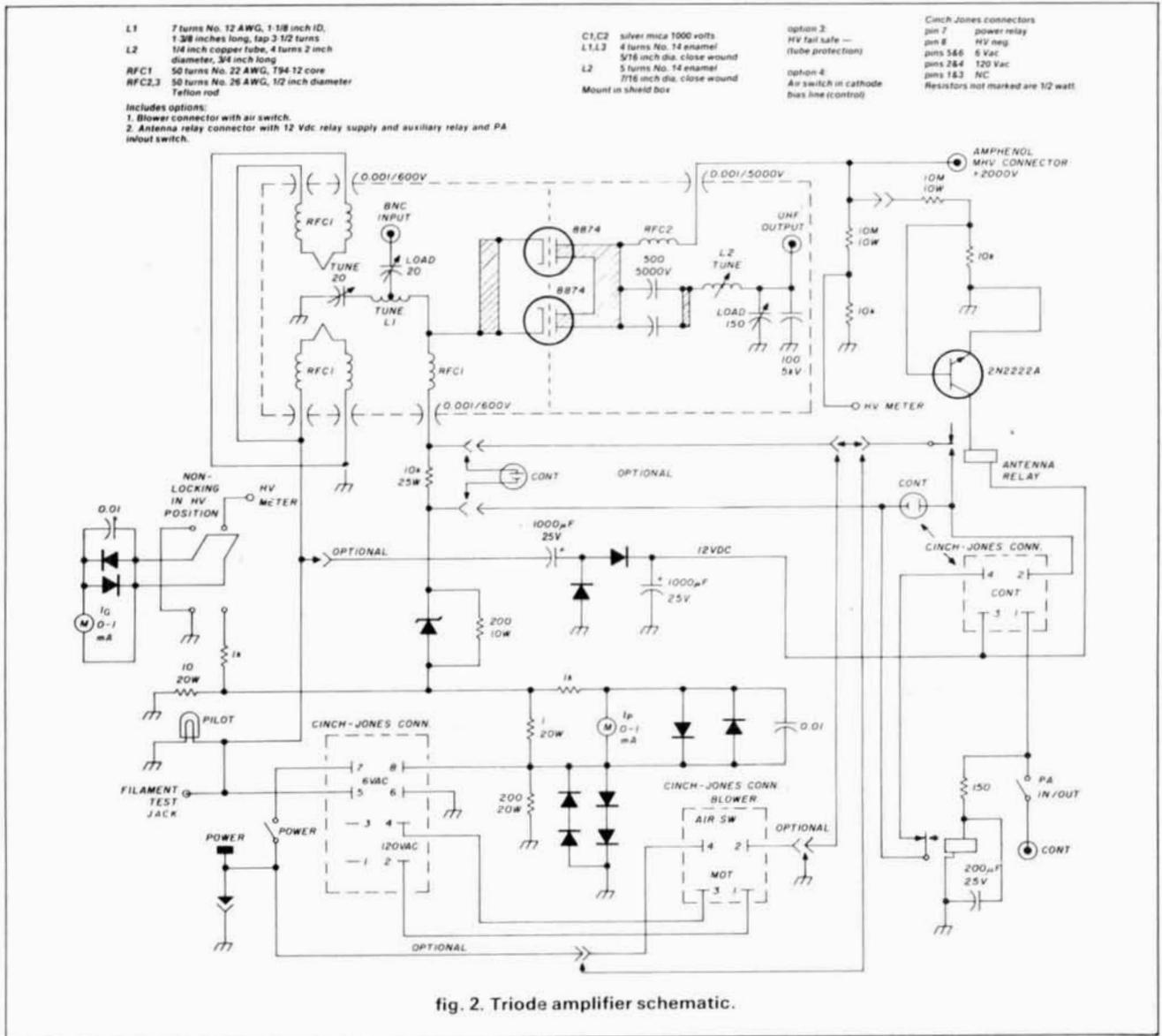

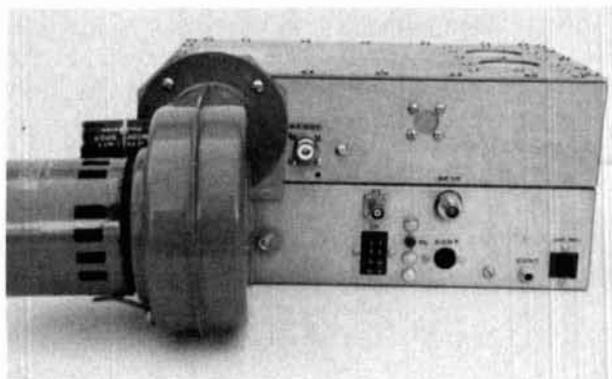

Tetrode amplifier — rear view.

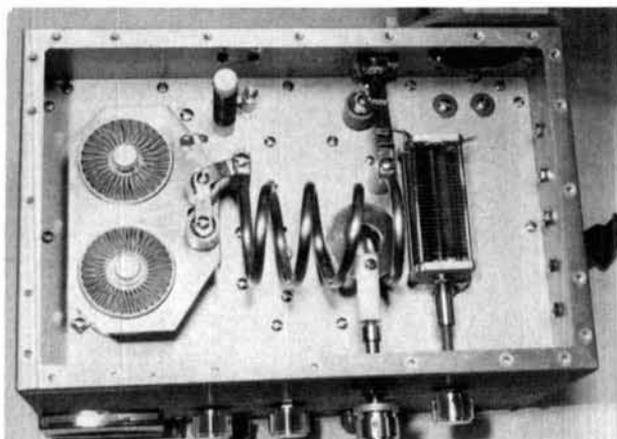

Tetrode amplifier — upper chassis.

Should the blower fail or not come up to speed, the power supply will automatically shut down, an important safeguard considering the two hundred dollar price tag on 8874s.

If excitation is applied with no plate voltage on the tubes, damage to the grid structure may result. The high-voltage fail-safe option provides a safeguard by using a transistor and a relay to open the bias control circuit if high voltage is not present. A 12-volt power supply for this feature is provided by a voltage doubling circuit from the filament line.

The remaining option, shown in **fig. 2**, is used to operate a DPDT coaxial relay which can be mounted (with a coaxial adapter) on the output connector of the amplifier. The coil of the relay and a set of auxiliary make-contacts are connected to the amplifier chassis via a four-contact connector. The 12-volt supply, auxiliary control relay circuitry, a power amplifier (PA) in/out switch, and a control jack com-

plete this feature. Note that a ground on transmit to the amplifier control jack will apply operating bias to the amplifier only if the antenna relay is operated and the auxiliary relay (in this optional circuit) is released. In receive, 12 volts is applied through the winding of the antenna relay to the auxiliary relay winding. The auxiliary relay operates, but the antenna relay, which requires more current than the auxiliary relay, does not operate with the PA switched to the in position. A ground on transmit from the exciter causes the antenna relay to operate immediately and the auxiliary relay to release after a slight delay. This prevents the amplifier from being "hot switched" and provides additional protection for the rf amplifier in the receiver. A layer or two of cellophane tape on the pole piece of the antenna relay is usually required to guarantee release. More sophisticated antenna relay-control circuitry is desirable, however, for EME amplifier applications.

Construction and mounting arrangements for the various options are covered in the construction infor-


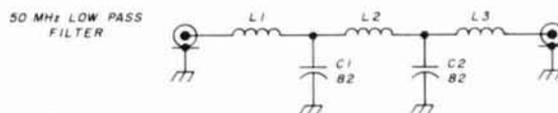



fig. 3A. 50 MHz low-pass filter.<sup>3</sup>

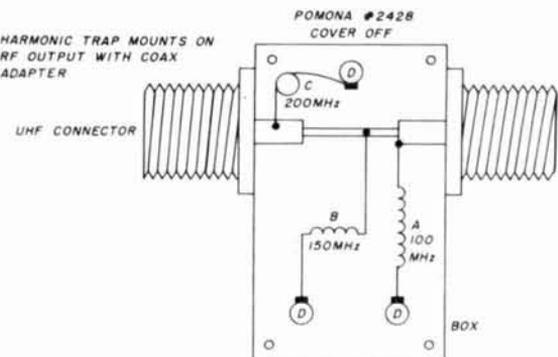

- A 20 turns No. 22 AWG, 3/4 inch long  
1/4 inch Teflon rod
- B 8 1/2 turns No. 20 AWG, 1/2 inch long
- C 6 turns No. 20 AWG, 1/2 inch long
- D Piston trimmer capacitors 10 pF

50 MHz amplifier  
upper chassis — rear  
RF output drilling  
L-P filter

fig. 3B. Trap filter.

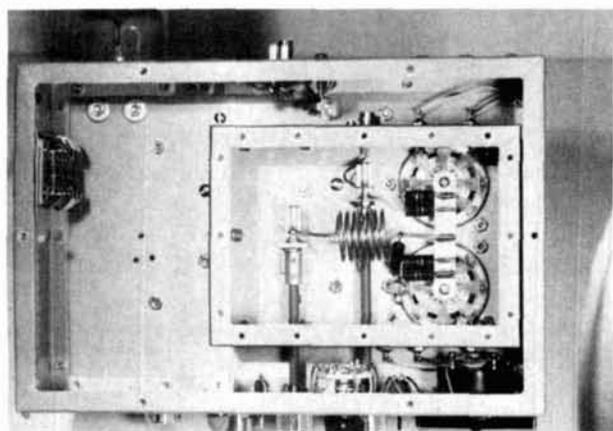

Tetrode amplifier — lower chassis.

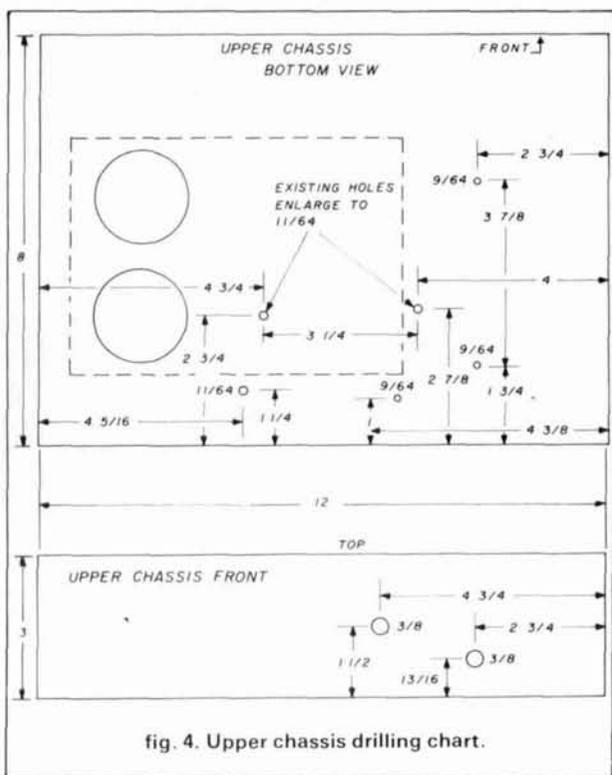


fig. 4. Upper chassis drilling chart.

of harmonic attenuation which no longer meets modern RFI design requirements. A suitable LP filter design for this 50-MHz amplifier is shown in the 1981 *ARRL Handbook*, pages 7-11 (fig. 3A). Harmonic trap circuit construction is shown in fig. 3B.

Information on the triode and tetrode amplifier power supplies has already been provided in the 220-MHz amplifier article.<sup>1</sup>

### construction — tetrode amplifier

If you do *not* intend to use the chassis for the 50-MHz amplifier on any of the other VHF/UHF bands, *omit* the following in its construction: five holes (11/64 inch or 4.4 mm) in the right side of the upper chassis used for mounting the 2-meter plate line, four holes (7/64 inch or 3 mm) and one hole (5/8 inch or 15.9 mm), on the rear of the upper chassis for mounting the rf output connector; two holes (7/64 inch or 3 mm), one hole (3/8-inch or 9.5 mm) for the plate load control in the top plate, and the hole in the front of the lower chassis for the plate tune control. The remaining holes not used for 50 MHz can be drilled and disregarded or filled with 6-32 (M3.5) hardware.


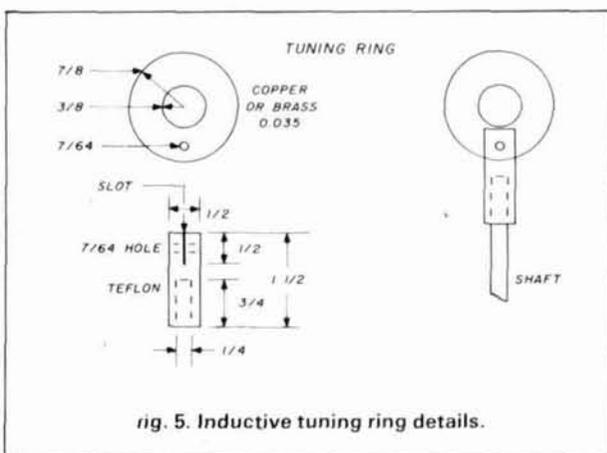


fig. 5. Inductive tuning ring details.

mation for the triode amplifier. Which options are chosen, and whether they are mounted inside or outside the amplifier, is determined by the intended application and the builder's inclination. These options are also applicable to the 50-MHz *tetrode* amplifier version as well as to the other models of these amplifiers, already described.

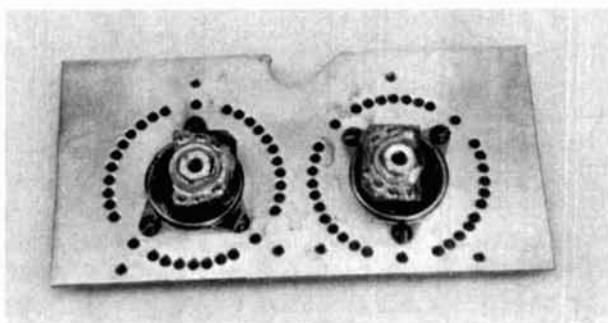A lowpass filter or harmonic trap circuit is needed in the rf output to attenuate harmonics in the amplifier output. These amplifiers, even when operated in the linear mode, may have harmonic components no more than 40 dB down from the fundamental, a level



Triode amplifier socket plate assembly — bottom view.

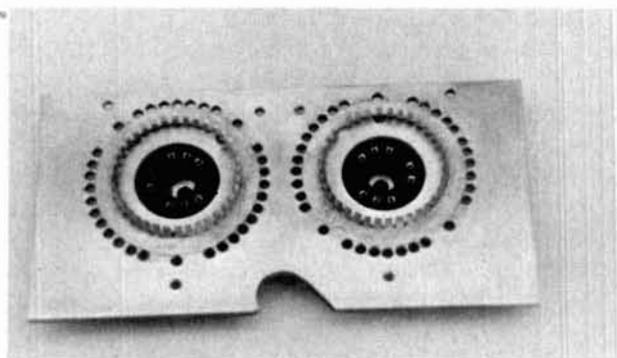
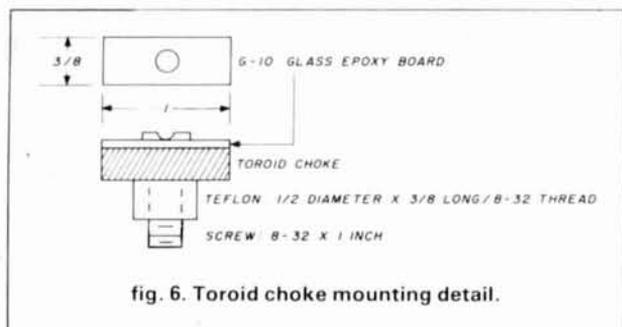





Fig. 4 shows the upper chassis drilling required for mounting the plate coil, variable load capacitor, rf choke, fixed load capacitor, and tune and load controls. Fig. 7 shows the drilling and punching for the rf output connector. This completes the chassis preparation.



Details of the inductive tuning ring are shown in fig. 5. Fig. 8 gives the dimensions for the plate line. Fig. 9 provides information on the plate rf choke.

The plate coil is wound with 1/4-inch (6.3-mm) copper tubing, four turns, 2 inches (50 mm) ID, 3-1/4 inches (8.3 cm) long. The ends of this coil are flattened, bent and drilled 11/64 inch (4.4 mm), to mount the coil on 1-1/2-inch (3.8-cm) Teflon pillars midway between the top and bottom of the upper chassis. When construction is completed, the spacing between the turns of the plate coil is adjusted to provide the required tuning range. The tuning range with the inductive ring is in excess of 1 MHz. An accurate grid dip meter is useful for preliminary adjustment of turns spacing for the desired frequency range. The final adjustment of coil size to the desired range is made during the final rf testing.

The assembly and wiring may be done in the same sequence used for the 144- and 220-MHz amplifier, by first assembling and wiring the lower chassis and

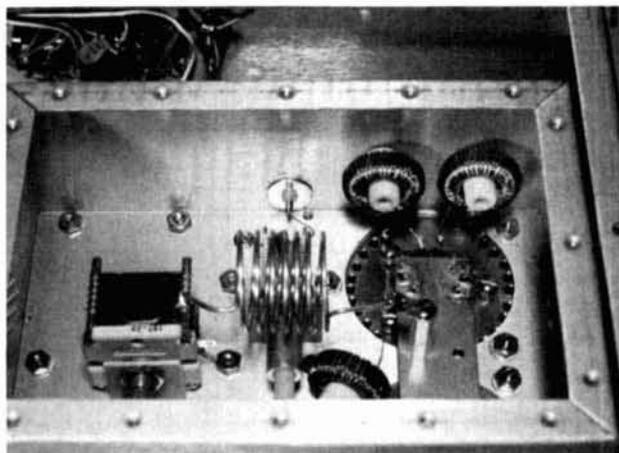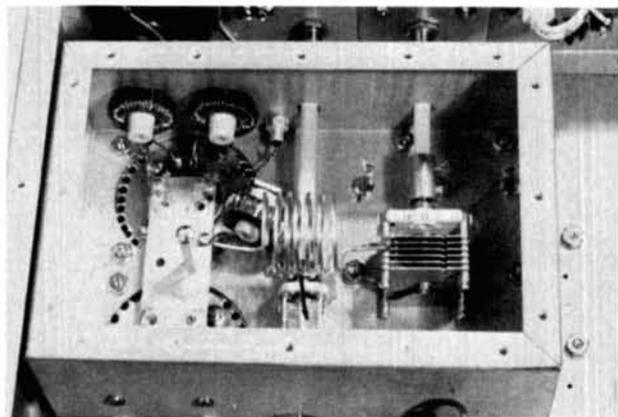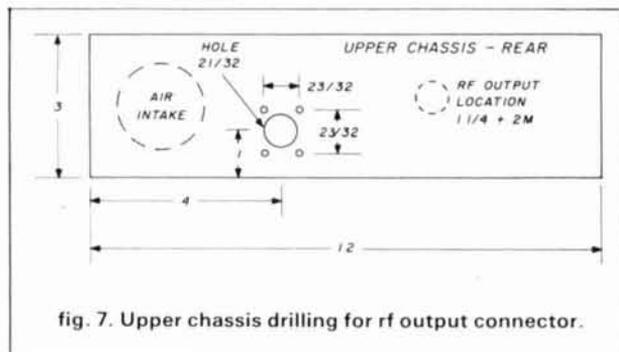then assembling the upper chassis and grid box. Mount the sockets and install the plate line parts. Finally, join the upper and lower chassis, make filament and grid bias connections, and install the grid box parts to complete the assembly.



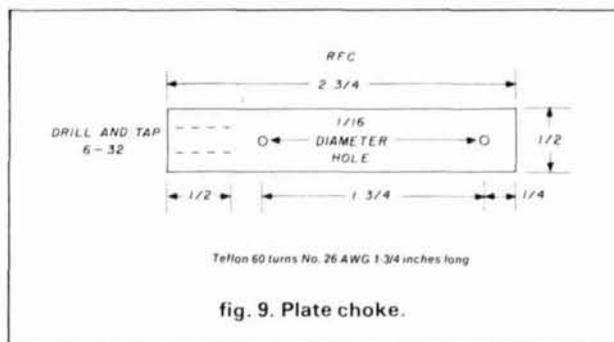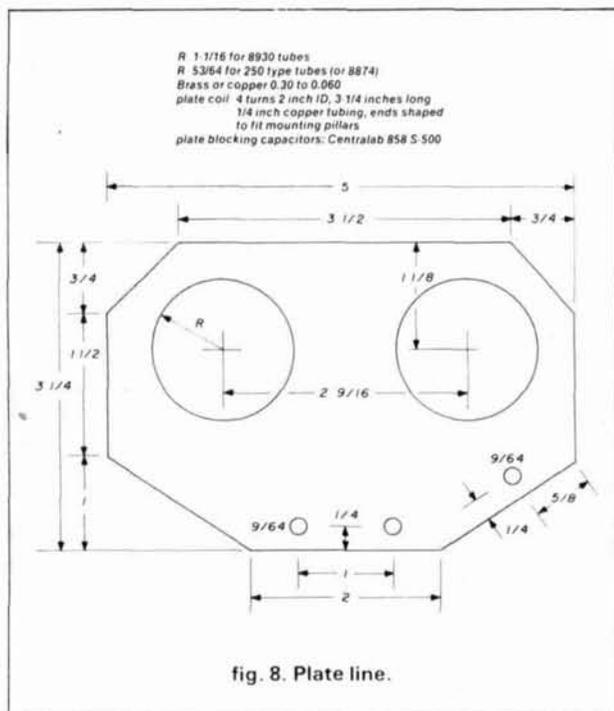


## construction — triode amplifier

Follow the directions for the tetrode amplifier construction for chassis drilling and punching, for the plate line and plate coil. The cathode tuned circuit for the triode amplifier is the same as that described for the grid circuit of the tetrode version. The holes in the grid box for the filament feed-through capacitors are relocated toward the bottom of the box to accommodate the toroid chokes (fig. 6). An additional meter hole is punched in the lower chassis front on the right side.


The tube sockets are mounted on a brass plate, as described for the 220-MHz triode amplifier. This assembly (fig. 10) lets you solder the grid collet (EIMAC part #882931) in position. Vent holes are provided around the base of the tube; it's a good idea to have this assembly silver plated. The assembly is bolted in place in the same position as the two 630A

sockets used for the tetrode amplifier. A brass strip (fig. 11) may be used to connect the cathode pins of the two sockets together. This strap is soldered in place after the socket plate has been mounted. Its position is such that the cathode socket pins protrude through the holes about 1/8 inch (3 mm).

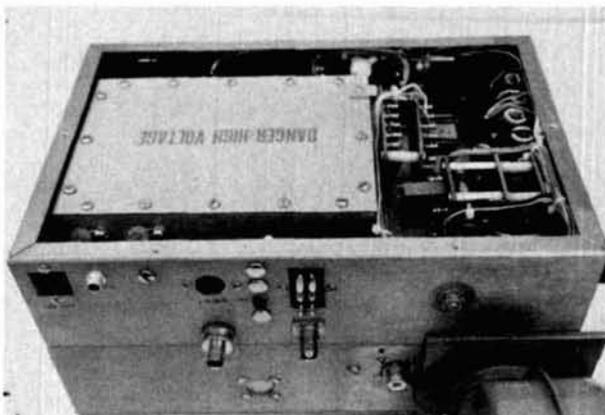Alternatively, a small brass plate mounting a brass bushing (tapped 10-32) may be soldered to the cathode pins of each socket. This method of construction is more involved, but avoids soldering the grid strap in place after the socket plate is mounted. The grid strap is fastened by the 10-32 screws on each mounting plate.



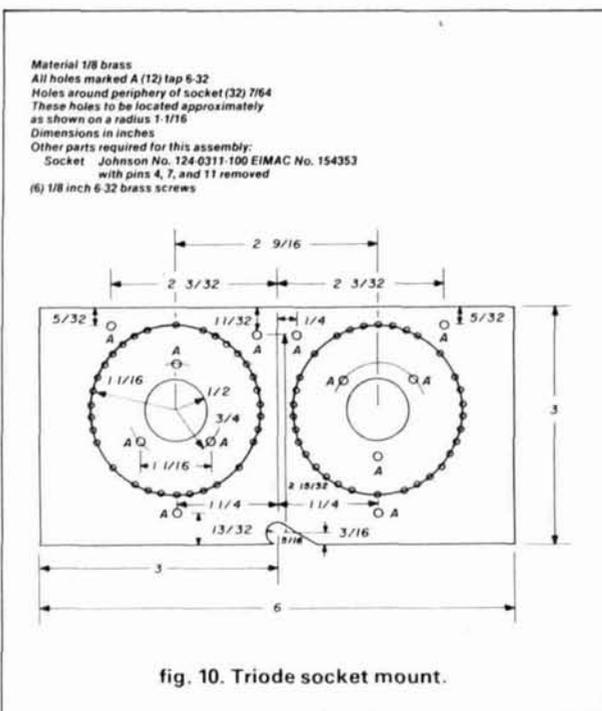Triode amplifier bottom view to illustrate mounting of optional circuit features on terminal boards in lower chassis.



# Barry Electronics Corp.

WE SHIP WORLDWIDE

WORLD WIDE AMATEUR RADIO SINCE 1950

Your one source for all Radio Equipment!

COMMERCIAL RADIOS  
stocked & serviced on  
premises.

We Will Not Be Undersold Call:  
**212-925-7000**

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK.  
**Saturday & Sunday 10 to 5 PM**

Monday-Friday 9 to 6:30 PM  
Come to Barry's for the best buys in town. For  
Orders Only Please Call: 1-800-221-2683.



"Don't let April Showers keep you away from the Best Buys in Amateur Radio".



FT-ONE, FT-980R FT-102, FT-101ZD, FT-707, FT-230R, FT-77,  
FT-726 FT-480R, FT-720RU, FT-290R, FRG-7700, FT-625RD

**ICOM**



IC-R70, IC-720A, IC-730, IC-740, IC-25A, IC-35A  
IC-251A, IC-2KL, IC-451A, IC-290H, IC-45A




DRAKE TR-5, TR-7A, R-7A, L-7, L-15, Earth  
Satellite Receiver ESR-24, THETA 9000E & 500,  
Digital Multimeter Model #8550-\$95.00



**ROCKWELL/COLLINS  
KWM-380**

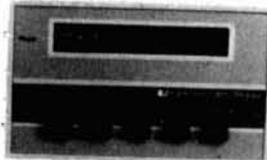**POWER PACKET  
VoCom Power  
Amplifier &  
5/8λ HT Gain  
Antennas IN STOCK**



**KANTRONICS  
Mini-Reader, Interface,  
Software & Code Tapes**



**MBO-Reader**



MIRAGE B-23, B-1016, B-108,  
B-3016, C-22, C-106, D-24, D-1010



**SMART PATCH**

CES-Simplex Autopatch 510-SA Will Patch FM  
Transceiver To Your Telephone. Great For  
Telephone Calls From Mobile To Base. Simple  
To Use - \$319.95.



**SANTEC  
ST-144/UP  
ST-440/UP**

**NEW IMPROVED  
MURCH Model  
UT2000B**

**MFJ  
Model 941C, Model 982**

**DENTRON AMPLIFIERS  
GLA-1000C  
Clipperton-L-QRO**



**EIMAC  
3-500Z  
572B, 6JS6C  
12BY7A &  
4-400A**

**BIRD  
Wattmeters &  
Elements  
In Stock**



**Telrex 10, 15, 20 Meter "Tri-Band"  
Model #TB5EM/4KWP & TB4EC**

**Communications Specialists  
Encoders In Stock!**

Smallest Wireless  
Telephone Available  
600 ft. range w/encoder \$135.00

**BENCHER PADDLES &  
Vibroplex Keys In Stock!!**

**DIGITAL  
FREQUENCY  
COUNTER**

Trionyx-  
Model TR-1000  
0-600 MHz  
Digimax Model D-510 50 Hz-1GHz



**New TEN-TEC  
Corsair In Stock**

Tri-Ex Towers  
Hy-Gain Towers & Antennas,  
and Rotors will be shipped  
direct to you FREE of shipping cost.

**New York City's LARGEST STOCKING HAM DEALER  
COMPLETE REPAIR LAB ON PREMISES**

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

BARRY INTERNATIONAL TELEX 12-7670  
TOP TRADES GIVEN ON YOUR USED EQUIPMENT  
STORE HOURS: Monday-Friday 9 to 6:30 PM  
(\$1.50 parking across the street)  
Saturday & Sunday 10 to 4 PM (Free Parking)  
AUTHORIZED DIST. MCKAY DYMCK FOR  
SHORTWAVE ANTENNAS & RECEIVERS.

IRT/LEX-"Spring St. Station"

Subways: BMT-"Prince St. Station"

IND-"F" Train-Bwy. Station"

Bus: Broadway #6 to Spring St.

Clearance on our WW II  
surplus inventory on  
Washington's Birthday.

**"Aqui  
Se Habla  
Español"**

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic, Astron, B & K, B & W, Bash, Bencher, Bird, Butternut, CDE, CES, Collins, Communications Spec. Connectors, Covercraft, Cubic (Swan), Cushcraft, Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encomm, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics, Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage, Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook, Robot, Rockwell Collins, Saxton, Shure, Swan, Telex, Tempo, Ten-Tec, Tokyo Hi Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and Commercial Radios, Vocom, Vibroplex, Curtis, Tri-Ex, Wacom Duplexers, Repeaters, Phelps Dodge, Fanon Intercoms, Scanners, Crystals.

**WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS  
DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED**

**Amateur Radio & Computer Courses Given On Our Premises, Call**

**Export Orders Shipped Immediately. TELEX 12-7670**


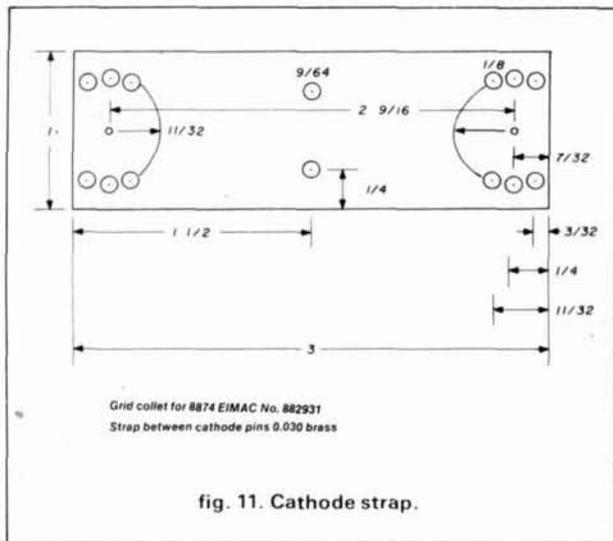


fig. 11. Cathode strap.

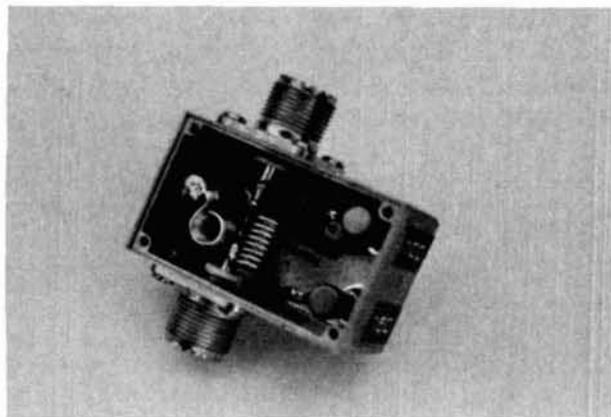

Output harmonic trap assembly. Three series traps — 100 MHz, 150 MHz, and 200 MHz. Piston capacitor adjustment screws (3) protrude out the bottom of the box.

Metering and other circuitry is mounted in the lower chassis, as shown in the photos. The vitreous-type resistors are mounted to the chassis wall. Other resistors and parts are mounted on terminal boards secured to the chassis with mounting spacers.

The options shown on the triode amplifier schematic (fig. 2) are mounted as follows:

The antenna relay connector is located on the right side of the lower chassis (rear). The small relay associated with this option is located in any convenient spot in the lower chassis. The various resistors, capacitors, and other parts for the antenna relay control circuit, the 12-Vdc supply, and the high voltage fail-safe circuitry are on terminal strips which are located in the lower chassis.

The blower connector is located on the left (side) rear of the lower chassis.

The PA in/out switch, the power switch, and the non-locking switch to start the blower are located on the front of the lower chassis.

In assembling and wiring the triode amplifier, follow the same pattern described for the tetrode amplifier — lower chassis parts mounting and wiring first — upper chassis and cathode box, tube socket assembly, plate circuit parts, joining upper and lower chassis, cathode parts, and the final wiring steps.

### automatic load control

An ALC circuit (fig. 12) has been added as an option to the triode amplifier. The parts within the grid box are mounted close to the rf input connector. A bias winding is required on the high-voltage transformer, or a separate small transformer is required to provide the +56 volts threshold control voltage. The bias voltage parts can be mounted in the power supply chassis on a terminal board.

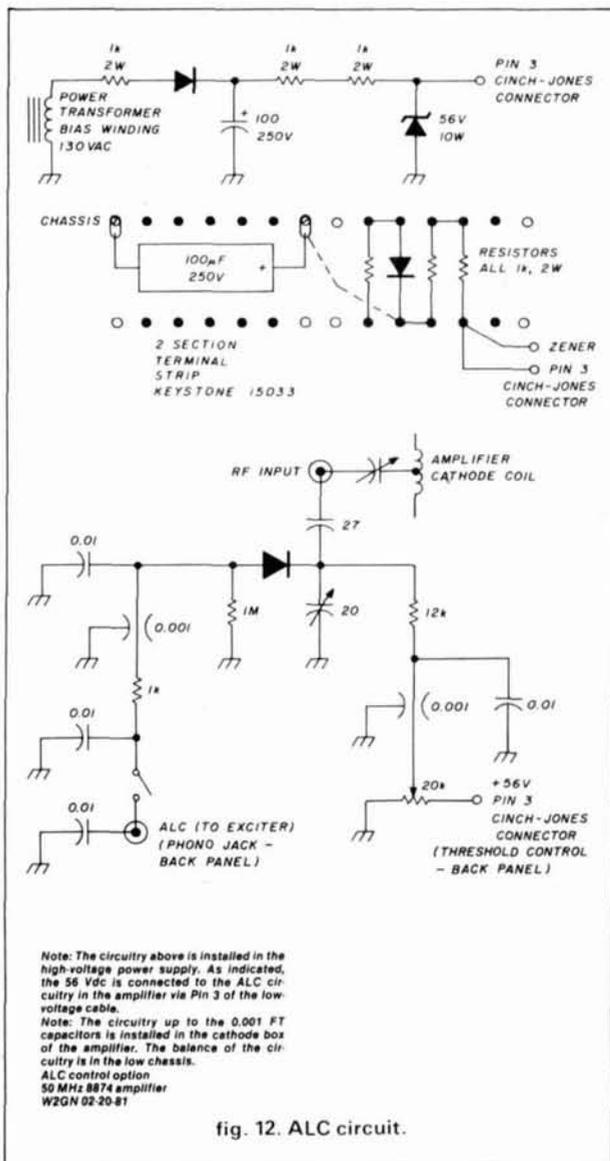


fig. 12. ALC circuit.

# Alaska Microwave Labs

P.O. BOX 2049 PALMER, ALASKA 99645  
(907) 376-3098 DEPT HR

## GaAs FETS

MGF 1400 NF 2.0DB @ 4GHZ MAG 15DB	\$14.00
MGF 1412 NF 0.8DB @ 4GHZ MAG 18DB	\$50.00
MCF 1200 NF 1.0DB @ 1GHZ NF 2.2DB & MAG 14DB @ 4GHZ	\$11.00

## VTO

V721-1 2.7GHZ TO 3.2GHZ MIN POWER OUT 10 MW TUNING VOLTAGE 0 TO 20V Vcc +15 vdc at 60 MA	\$98.00
V721-2 2.8GHZ TO 3.3GHZ REST SAME AS V721-1	\$98.00
V821-1 SAME AS V721-1 BUT FREQ 3.0GHZ TO 3.5GHZ	\$98.00
V821-2 SAME AS V721-1 BUT FREQ 3.6GHZ TO 4.2GHZ	\$98.00
V821-3 SAME AS V721-1 BUT FREQ 4.0GHZ TO 4.5GHZ	\$98.00
V821-4 SAME AS V721-1 BUT FREQ 4.5GHZ TO 5.0GHZ	\$98.00
V561-1 9GHZ TO 1.6GHZ POWER OUT 13 MW TUNING VOLTAGE 2 TO 50V Vcc +15 VDC AT 60 MA	\$98.00
V661-1 SAME AS V561-1 BUT FREQ 1.5GHZ TO 2.5GHZ	\$98.00

## CHIP CAPACITORS

1.2 2.2 2.7 3.3 4.7 6.8 10 18 22 27 47 100 120 180 220 270 330 390 470 560 680 820 1K 1.2K 1.8K 3.9K 8.2K 10K 100K	\$6.00
--------------------------------------------------------------------------------------------------------------------	--------

## PISTON TRIMMERS

BRKO 201.01M	
3-1 BPF	\$2.50
5-3 PF	\$2.50
1-8 PF	\$2.50

## TEFLON CIRCUIT BOARD DBL SIDED 1 OZ

APPROX 3.25" x 5.0" x .010	\$5.50
APPROX 3.25" x 5.0" x .0312	\$6.50
APPROX 3.25" x 5.0" x .0625	\$10.50

## MIXERS

3.7GHZ TO 4.2GHZ MIXER LO 2.8GHZ TO 5.1GHZ IF DC 9GHZ SSB CONVERSION LOSS TYP 5.5DB MAX 6.5DB TO 8 PACKAGE	\$59.00
9GHZ TO 1.3GHZ MIXER LO 7GHZ TO 1.5GHZ IF DC 2GHZ SSB CONVERSION LOSS TYPE 7.0DB 10-8 PACKAGE	\$15.00

## CHIP RESISTORS

50 OHM 1/4 WATT	\$1.50
3 1% CHIP RESISTORS FOR	
50 OHM T NETWORK 3 DB PAD	\$6.00

NO WARRANTY ON SEMICONDUCTORS

102

OPEN AT 8 PM EST CLOSED 8PM PST  
ORDERS ARE POSTAGE PAID  
COD - VISA - MASTERCARD

## NEW TS830S for \$150?

Yes indeed! Just add a Matched Pair of top-quality 2.1 kHz BW (bandwidth) Fox Tango Filters. Here are a few quotes from users:

- "... Makes a new rig out of my old TS830S! ..."
- "... VBT now works the way I dreamed it should ..."
- "... Spectacular improvement in SSB selectivity ..."
- "... Completely eliminates my need for a CW filter ..."
- "... Simple installation — excellent instructions ..."

The Fox Tango filters are notably superior to both original 2.7 kHz BW units but especially the modest ceramic 2nd IF; our substitutes are 8-pole discrete-crystal construction. The comparative FT vs Kenwood results? VBT OFF — RX BW: 2.0 vs 2.4; Shape Factor: 1.19 vs 1.34; 80 dB BW: 2.48 vs 3.41; Ultimate Rejection: 110 dB vs 80; VBT SET FOR CW at 300 kHz BW — SF 2.9 vs 3.33; Insertion Loss: 1 dB vs 10 dB.

AND NOW A NEW TS930S! Tests prove that the same filters improve the '930 even more than the '830. Don't buy CW filters — not even ours. You probably won't need them!

### INTRODUCTORY PRICE: (Complete Kit) ... \$150

Includes Matched Pair of Fox Tango Filters, all needed cables, parts, detailed instructions  
Specify kit desired: FTK-830 or FTK-930  
Shipping \$3 (Air \$5). FL Sales Tax 5%



### ONE YEAR WARRANTY GO FOX-TANGO — TO BE SURE!

Order by Mail or Telephone.  
AUTHORIZED EUROPEAN AGENTS  
Scandinavia: MICROTEC (Norway)  
Other: INGOIMPEX (W. Germany)


### FOX TANGO CORPORATION

Box 15944H, W. Palm Beach, FL 33406  
Phone: (305) 683-9587

131


More Details? CHECK — OFF Page 129

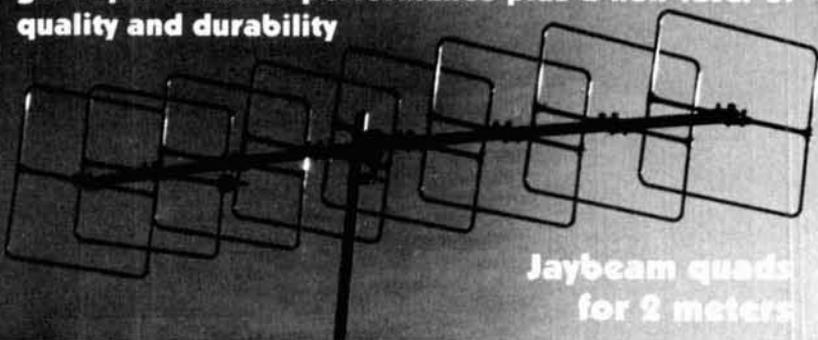get super 2 meter performance plus a new level of quality and durability



Jaybeam quads for 2 meters

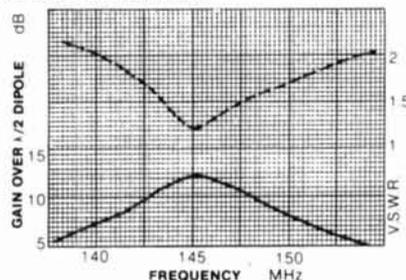Jaybeam 4, 6 and 8 element quads achieve a level of quality, durability and performance not previously available in amateur antennas.



ON DISPLAY AT DAYTON HAMVENTION

Q6/2M

KEY  
..... V.S.W.R.  
—— Gain over 1/2 Dipole

## SPECIFICATIONS

	Q4	Q6	Q8
FREQUENCY (MHz)	144-148	144-148	144-148
GAIN dbd	9.4	10.9	11.9
FRONT TO BACK RATIO	20dB	22dB	25dB
3dB BEAMWIDTH	E48° H50°	E40° H42°	E37° H38°
BOOM LENGTH	4.92'	8.2'	11.6'
LONGEST ELEMENT	24.4"	24.4"	24.4"
TURNING RADIUS (APPROX)	2.6'	4.2'	5.87'
DESIGN IMPEDANCE	50 Ohms	50 Ohms	50 Ohms
POWER RATING (PEAK)	1 kw P.E.P.	1 kw P.E.P.	1 kw P.E.P.
WINDLOADING AT 80MPH	30.8 lbs/ft	45.1 lbs/ft	61.6 lbs/ft
WEIGHT	5.94 lbs	7.7 lbs	10.3 lbs

Contact your ham radio dealer or one of the dealers listed below for Jaybeam Antennas. For further information, contact:

G.I.S.M.O. COMM. INC.  
1-800-845-6183  
Rock Hill, SC

COMMUNICATIONS CENTER  
1-800-928-4097  
Lincoln, NE

ALI'S ELECTRONICS  
(305) 997-5324  
Boca Raton, FL

JASCO INTERNATIONAL INC.  
P.O. Box 29184  
Lincoln, Nebraska 68529

## 1296 & PHASE III MAKI UTV 1200 - \$399<sup>95</sup> 2M or 6M I.F. / 5 WATTS

- 4 TRANSVERTER MODELS
- TX/RX CONVERTERS
- PRE-AMPS, AMPS, FILTERS

LG. SASE FOR CATALOG  
SEE US AT DAYTON 83

## SPECTRUM WEST

5717 NE 56th, SEATTLE, WA  
206-523-6167 98105

## GROTH-Type

COUNTS & DISPLAYS  
YOUR TURNS



- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

TC2 \$12.50

TC3 \$13.50

Spinner Handle Add \$1.50

Prices include UPS or Parcel Post in US

Model TC2: Skirt 2-1/8"; Knob 1-5/8"

Model TC3: Skirt 3"; Knob 2-3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

113

176

State  
of the art



by

K.V.G.

### 9 MHz CRYSTAL FILTERS

MODEL	Application	Bandwidth	Poles	Price
XF-9A	SSB	2.4 kHz	5	\$50.60
XF-9B	SSB	2.4 kHz	8	88.60
XF-9B-01	LSB	2.4 kHz	8	91.35
XF-9B-02	USB	2.4 kHz	8	91.35
XF-9B-10	SSB	2.4 kHz	10	119.65
XF-9C	AM	3.75 kHz	8	73.70
XF-9D	AM	5.0 kHz	8	73.70
XF-9E	FM	12.0 kHz	8	73.70
XF-9M	CW	500 Hz	4	51.55
XF-9NB	CW	500 Hz	8	91.35
XF-9P	CW	250 Hz	8	124.95
XF910	IF noise	15 kHz	2	16.35

### 10.7 MHz CRYSTAL FILTERS

MODEL	Application	Bandwidth	Poles	Price
XF107-A	NBFM	12 kHz	8	\$64.10
XF107-B	NBFM	15 kHz	8	64.10
XF107-C	WBFM	30 kHz	8	64.10
XF107-D	WBFM	36 kHz	8	64.10
XF107-E	Pix/Data	40 kHz	8	64.10
XM107-SO4	FM	14 kHz	4	28.70

Export Inquiries Invited.

Shipping \$3.50

### MICROWAVE MODULES VHF & UHF EQUIPMENTS

Use your existing HF or 2M rig on other VHF or UHF bands.

### LOW NOISE RECEIVE CONVERTERS

1691 MHz	MMk1691-137	\$224.95
1296 MHz	MMk1296-144	119.95
432/435	MMc435-28(S)	74.95
439-ATV	MMc439-Ch x	84.95
220 MHz	MMc220-28	69.95
144 MHz	MMc144-28	54.95

Options: Low NF (2.0 dB max., 1.25 dB max.), other bands & IF's available

### LINEAR TRANSVERTERS

1296 MHz	1.3 W output, 2M in	MMt1296-144	\$374.95
432/435	10 W output, 10M in	MMt435-28(S)	299.95
144 MHz	10 W output, 10M in	MMt144-28	199.95

Other bands & IFs available.

### LINEAR POWER AMPLIFIERS

1296 MHz	10 W output	MML1296-10-L	\$ ask
432/435	100 W output	MML432-100	444.95
	50 W output	MML432-50-S	239.95
	30 W output	MML432-30-LS	209.95
144 MHz	100 W output	MML144-100-S	264.95
	50 W output	MML144-50-S	239.95
	30 W output	MML144-30-LS	124.95
	25 W output	MML144-25	114.95

All models include VOX T/R switching.

"L" models 1 or 3W drive, others 10W drive.

Shipping: FOB Concord, Mass.

### ANTENNAS



#### 420-450 MHz MULTIBEAMS

48 Element	70/MBM48	15.7 dBd	\$79.95
88 Element	70/MBM88	18.5 dBd	111.35

#### 144-148 MHz J-SLOTS

8 over 8 Hor. pol	D8/2M	12.3 dBd	\$63.40
8 by 8 Vert. pol	D8/2M-vert	12.3 dBd	76.95
8 + 8 Twist	8XY/2M	9.5 dBd	ask

#### UHF LOOP YAGIS

1250-1350 MHz 29 loops	1296-LY 20 dB	\$44.95
1650-1750 MHz 29 loops	1691-LY 20 dB	55.95

Order Loop-Yagi connector extra:

Type N \$14.95, SMA \$5.95

Send 40¢ (2 stamps) for full details of all your VHF & UHF equipment and KVG crystal product requirements.



si


(617) 263-2145

SPECTRUM

INTERNATIONAL, INC.

Post Office Box 1084

Concord, MA 01742, U.S.A.

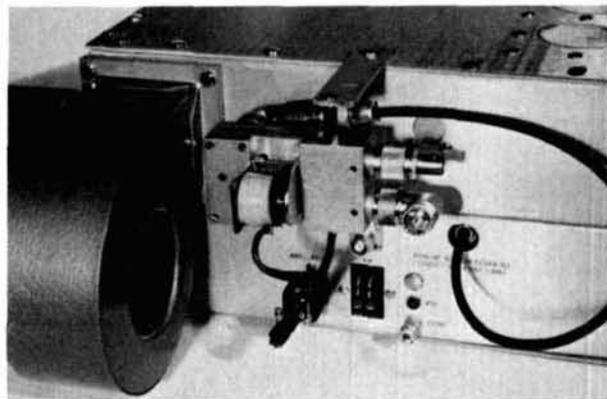

Mounting of double-pole coaxial relay on output connector.

table 1. Typical operation tetrode amplifier.

drive power	grid current	screen current	plate current	plate voltage	power output
0	0	0	0.100	2150	0
2.5	0	0	0.260	2010	177
5.0	0	-0.003	0.430	2000	470
10.0	0.002	0.027	0.600	2000	800

filament volts = 6.07 grid volts = 64 screen volts = 315

table 2. Typical operation triode amplifier.

drive power	grid current	plate current	plate voltage	power output
0	0	0.040	2300	0
2.5	0.002	0.210	2100	140
5.0	0.004	0.300	2050	285
10.0	0.025	0.380	2050	540

filament volts = 6.12

Note: The triode amplifier may be driven to an output level of 1 kW (SSB).

### operation

The 50-MHz amplifiers tune and load in a conventional manner. Make initial adjustments with low drive power. Final adjustment of the grid (or cathode) tuning is made for lowest SWR toward the drive source. Final adjustment of the plate tuning must be done at full power output in order that the load control may be set at its optimum position.

Tables 1 and 2 show typical operation of the tetrode and triode amplifiers.

### references

1. Fred Merry, W2GN, "Stripline Kilowatt For Two Meters," *ham radio*, October, 1977. Also, "Stripline Kilowatt for 220 MHz," *ham radio*, April, 1982.
2. Richard T. Knadle, Jr., K2RIW, "A Stripline Kilowatt for 432 MHz," *QST*, April, 1972, page 48; May, 1972, page 59.
3. *ARRL Handbook*, 1981, pp 7-11.

ham radio

In 2 Meters Today...

# ICOM Leads the Way!



## ICOM IC-251A

ICOM has always been the amateur communications equipment industry's leader in 2 meter solid state digital technology. ICOM continues its established leadership with the all new IC-251A 2 meter multi-mode base transceiver. ICOM's advanced engineering incorporated a multi-memory system, 2 programmable scanning systems, 2 internal VFO's, and built in repeater offsets.

The New ICOM 251A is the most advanced, flexible 2 meter system on the market, incorporating features customers ask for most:

- Memory scan — automatically stop on memory frequency

- 3 memories built in (quick access to your favorite frequencies)
- Programmable band scan — scan the whole band, or any portion of it you desire (adjustable scanning speed). Automatically resumes scanning after 16 seconds if desired.
- Squelch on SSB! The 251A will automatically and silently scan the SSB portion of the band seeking out the SSB activity on 2.
- Multi-mode operation — USB, LSB, CW, FM. Great for getting into Oscar, plus enjoying SSB rag chewing as well as repeater operation (including the new subband).

- 600kc Repeater offset built in. Easy repeater operation on the FM portion of the band.
- Variable repeater split — with the 2 built in VFO's, it's possible to work the odd splits plus accommodate future repeater band plan changes.

The RF amplifier and first mixer circuits using MOS FET's, and other circuits provide excellent Cross Modulation and Intermodulation characteristics. The IC-251A has excellent sensitivity demanded especially for mobile operation, high stability, and with Crystal Filters having the high shape factors, exceptional selectivity.

**\$50**  
**Cash Rebate**

\$50.00 for the purchase  
of an IC-251A.

Begins Mar. 1, 1983  
Expires May 30, 1983


VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT



# ICOM

2112 116th NE, Bellevue, WA 98004  
3331 Towerwood Drive, Dallas, TX 75234
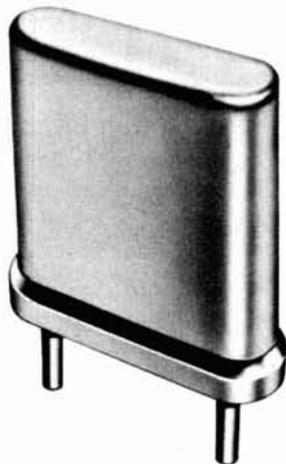
# International Crystals & Kits **FOR THE EXPERIMENTER**



**\$7<sup>80</sup>**  
ea.

.02% Calibration Tolerance

## EXPERIMENTER CRYSTALS


(HC 6/U Holder)

Cat. No.	Specifications
031300	3 to 20 MHz — For use in OF-1L OSC Specify when ordering.
031310	20 to 60 MHz — For use in OF-1H OSC Specify when ordering.

**\$8<sup>00</sup>**  
ea.
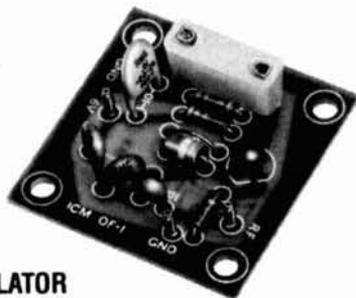
## OF-1 OSCILLATOR

The OF-1 oscillator is a resistor/capacitor circuit providing oscillation over a range of frequencies by inserting the desired crystal, 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 HI, Cat. No. 035109. Specify when ordering.



<b>MX-1 Transistor RF Mixer</b> 3 to 20 MHz, Cat. No. 035105 20 to 170 MHz, Cat. No. 035106	.....	<b>\$8.00 ea.</b>
<b>SAX-1 Transistor RF Amp.</b> 3 to 20 MHz, Cat. No. 035102 20 to 170 MHz, Cat. No. 035103	.....	<b>\$8.00 ea.</b>
<b>BAX-1 Broadband Amp</b> 20 Hz to 150 MHz, Cat. No. 035107	.....	<b>\$8.00 ea.</b>

WRITE FOR BROCHURE



International Crystal Mfg. Co., Inc.

10 North Lee, P.O. Box 26330  
Oklahoma City, OK 73126

CONDITIONS OF SALE: Sold on a cash basis. Shipping and postage inside U.S. will be prepaid by International.  
ORDERING INSTRUCTIONS: Order by catalog number. Enclose check or money order with your order.  
FOREIGN ORDERS: Prices quoted for U.S. orders only. Orders for shipment to other countries will be quoted on request. Prices subject to change. Minimum foreign order \$25.00.

✓ 141

**\$39.95**  
Assembled

**Communications Design, Inc.**  
1504 E. Thompson St. - West Memphis, AR 72301  
501-735-4568

## MORSE ONE KEYSER

Iambic Operation for Squeeze Keys  
Self Completing Dots & Dashes  
Adjustable Volume & Side Tone  
All CMOS Design  
Relay Keying — Fast Acting Reed Keys Any Rig  
Sturdy Black Anodized Aluminum Cabinet  
Self Contained Power Supply (9 v Battery)



Call Or Write For Free Catalog Of Other CDI Products

✓ 122

## SYNTHESIZED SIGNAL GENERATOR

MADE IN USA



MODEL SG1000  
\$349.95  
plus shipping

- Covers 100 to 185 MHz in 1 kHz steps with thumb-wheel dial • Accuracy 1 part per 10 million at all frequencies • Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate • Spurs and noise at least 60 dB below carrier • RF output adjustable from 5-500 mV at 50 ohms • Operates on 12 Vdc @ 1/2 Amp • Available for immediate delivery • \$349.95 plus shipping
- Add-on Accessories available to extend freq. range, add infinite resolution, voice and sub-audible tones, AM, precision 120 dB calibrated attenuator
- Call for details • Dealers wanted worldwide.

**VANGUARD LABS**  
196-23 Jamaica Ave., Hollis, NY 11423  
Phone: (212) 468-2720

✓ 183

**SAY  
YOU SAW  
IT IN  
ham radio!**

Custom Mailing Lists on Labels!

## Amateur Radio Operator NAMES

Custom lists compiled to your specifications  
— Geographic by ZIP and/or State; by Age or Birthdate; by Licence Issue or Expiration Date—on labels of your choice.

Total List: 411,000 Price: \$25/Thousand

Call 203: 438-3433 for more information

**Buckmaster Publishing**

70 Florida Hill Rd., Ridgefield, CT 06877

✓ 116

## ALL BAND TRAP ANTENNAS!



PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR ALL BANDS! EXCELLENT FOR CONDO'S - APARTMENTS - LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS! GUARANTEED FOR 2000 WATTS SSB INPUT FOR NOVICE AND ALL CLASS AMATEURS! IMPROVED DESIGN!

COMPLETE with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6" - you just switch to band desired for excellent worldwide operation - transmitting and receiving! Low SWR over all bands - Tuners usually NOT NEEDED! Can be used as inverted V's - skopers - in attic, on building tops or narrow lots. THE ONLY ANTENNA YOU WILL EVER NEED FOR ALL BANDS - WITH ANY TRANSCEIVER - NEW - NO BALUNS NEEDED!

80-40-20-15-10, -- 2 trap - 104 ft. - Model 998BUC - \$89.95  
40-20-15-10, -- 2 trap - 54 ft. - Model 100BUC - \$88.95  
20-15-10 meter - 2 trap - 26 ft. - Model 1007BUC - \$87.95

SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical - customs etc.) or order using VISA - MASTER CARD - AMER. EXPRESS, Give number and ex. date. Ph 1-308-230-5333 SAM - 6PM, week days. We ship in 2-3 days. ALL PRICES MAY INCREASE ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM

WESTERN ELECTRONICS

Dept. AH-4

Kearney, Nebraska, 68847

✓ 186

Tell 'em you saw it in HAM RADIO!

# The New Plus in Mobile Radio

Universal Communications is offering to you **Wilson's Citi-Com Plus**, the most versatile mobile radio ever designed. This 10 channel VHF synthesized radio is complete with scanning.

It's everything you'll ever need in a 10 channel VHF transceiver. For pricing and more information write or call Universal Communications.



**1691 WEATHER FAX DOWNCONVERTER NOW AVAILABLE PLEASE CALL OR WRITE FOR DETAILS**

**KIT 1 \$49.95**  
**SAVE \$10.00**

DOWNCONVERTER ..... \$19.95  
VARIABLE POWER SUPPLY ..... \$19.95  
CIGAR ANTENNA ..... \$19.95

SUPERVERTER I assembled only . . \$109.95  
crystal not included

**KIT 2 \$79.95**  
**SAVE \$7.00**

DOWNCONVERTER ..... \$19.95  
VARIABLE POWER SUPPLY ..... \$19.95  
KD 44 DISH ANTENNA ..... \$47.95

SELECTIVE PREAMPLIFIER . . \$26.95  
DRIFT MODIFICATION ..... \$1.25

**ASSMBLD SPECIAL \$79.95**  
**SAVE \$10.00**

ASSEMBLED DOWNCONVERTER ..... \$39.95  
ASSEMBLED VARIABLE POWER SUPPLY ..... \$29.95  
CIGAR ANTENNA ..... \$19.95

HIGH GAIN TRANSISTOR ..... \$6.95  
KD44 DISH ANTENNA ..... \$47.95



For Information, Ordering or a Product Brochure contact  
**UNIVERSAL COMMUNICATIONS**

A DIVISION OF INNOVATIVE LABS, INC.

P.O. Box 339 • ARLINGTON, TEXAS 78010-0339 • (817) 860-1641 Metro (817) 265-6638

181

**Tri-Ex TOWER CORPORATION**  
**TRI-EX TOWER — THE TOWER OF YOUR FUTURE**

Tri-Ex is the tower of your future. If you want quality and experience Tri-Ex is the name you want. People from all over the world recognize Tri-Ex, and that is why Tri-Ex is located on every continent of the globe. Tri-Ex towers are manufactured in the United States and licensed for manufacture in Europe.

Tri-Ex puts the same quality in each and every tower. Ask those who own them. Features include high strength low wind resistant W bracing formed guides, galvanizing inside and out, high strength aircraft cabling, hand and motor driven winch systems, bearing rollers, and electronic welding in precision jigs.

Tri-Ex manufactures a complete line of towers, crank-up towers from 25 feet to 150 feet, and stacked towers from 10 feet up.

For additional information write to:  
**TRI-EX TOWER CORPORATION**  
P.O. Box 5009  
Visalia, CA 93278  
(209) 651-2171

Ask for a copy of our dealer list.

180

More Details? CHECK — OFF Page 129

**NEW FROM LUNAR**

**HIGH PERFORMANCE COMMERCIAL QUALITY UHF/VHF CONVERTER KITS**

Professionally engineered using the high performance DBM, these kits are designed with the active VHFer in mind. All parts, components and circuit board are of the highest quality. Gold plated case ensures circuit integrity. Each kit includes easy-to-read, fully illustrated instructions. VHF units use crystal control. UHF converters are tunable. Crystal control UHF models available soon. In the unlikely event of construction problems, complete factory back-up assistance is available from trained technicians.

**Typical Specs:**

Input freq	144 MHz
Image rejection	-65 dB
LD specs	+7, 10 dBm output
Conversion gain	15 dB
Noise fig (tuned min. N.F.)	1.75 dB
Noise fig (tuned max. gain)	2.4 dB
Harmonics	-50 dBc

MODEL	INPUT FREQ	OUTPUT FREQ	PRICE
RCK 6/10	50	28	\$39.95
6/2	50	144	39.95
2/10	144	28	39.95
2/6	144	50	39.95
1.3/10	220	28	39.95
1.3/6	220	50	39.95
1.3/2	220	144	39.95
ATV	439	60	34.95
ATV P	439	60	39.95

Crystals for VHF models available \$14.95 ea.  
Other frequency conversions available. Specify requirements.

**LUNAR electronics**

2775 Kurtz St., Suite 11,  
San Diego, CA 92110

149

April 1983 **h** 85



# Food for thought.

Our new Universal Tone Encoder lends its versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequency—just dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers' repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

- All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak
- Instant start-up.
- Off position for no tone output.
- Reverse polarity protection built-in.

## Group A

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 M1

- Frequency accuracy,  $\pm .1$  Hz maximum - 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- Continuous tone

## Group B

TEST-TONES:	TOUCH-TONES:	BURST-TONES:
600	697 1209	1600 1850 2150 2400
1000	770 1336	1650 1900 2200 2450
1500	852 1477	1700 1950 2250 2500
2175	941 1633	1750 2000 2300 2550
2805		1800 2100 2350

- Frequency accuracy,  $\pm 1$  Hz maximum - 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Model TE-64 \$79.95

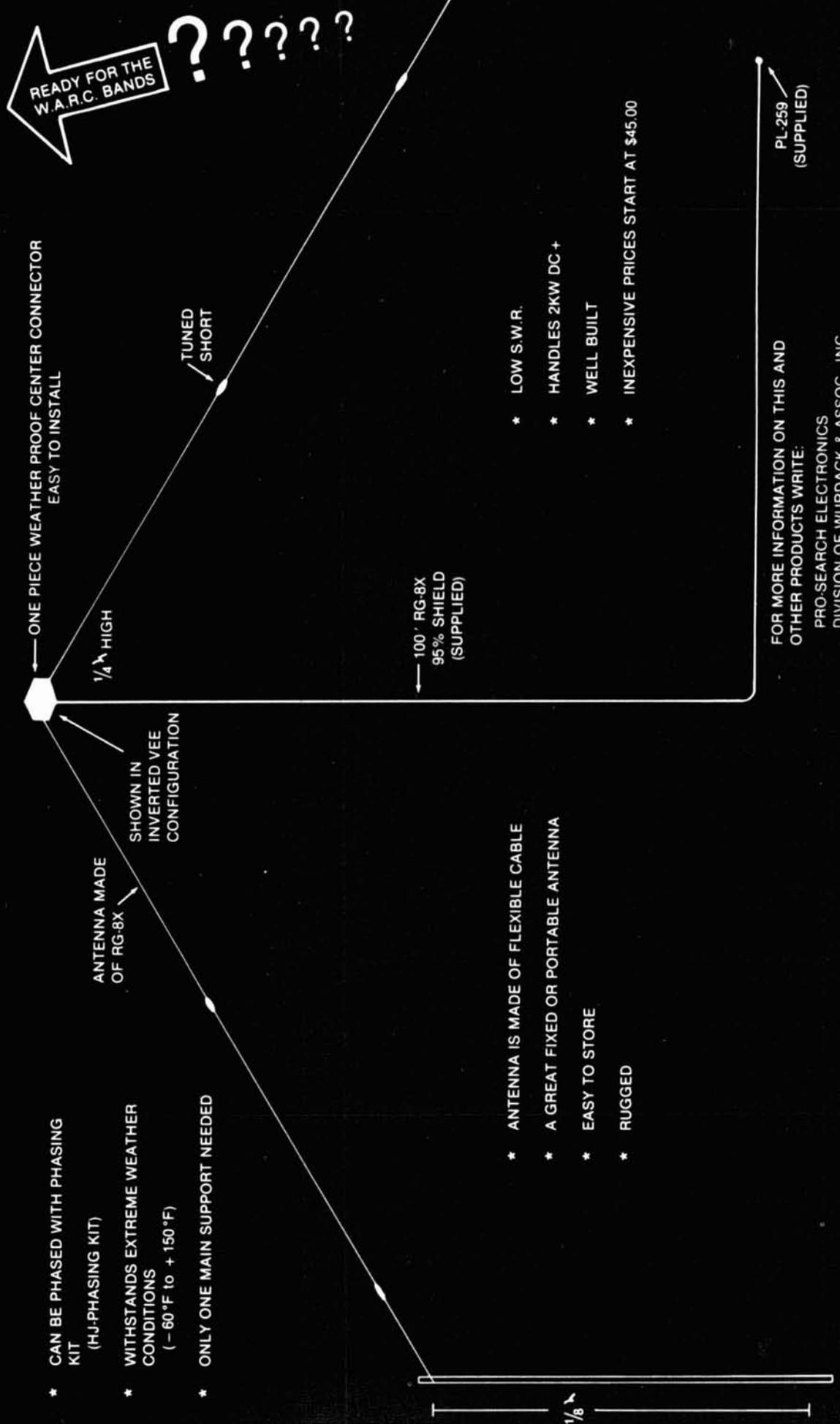
**COMMUNICATIONS SPECIALISTS**

426 West Taft Avenue, Orange, California 92667  
(800) 854-0547/ California: (714) 998-3021





**COAXIAL DIPOLE HJ-SERIES - FOR THE SHORTWAVE LISTENER AND HAM OPERATOR**  
 (MADE FOR ANY FREQUENCY BETWEEN 1.7 MHZ AND 148.0 MHZ)



- \* CAN BE PHASED WITH PHASING KIT (HJ-PHASING KIT)
- \* WITHSTANDS EXTREME WEATHER CONDITIONS (-60°F to +150°F)
- \* ONLY ONE MAIN SUPPORT NEEDED

- \* ANTENNA IS MADE OF FLEXIBLE CABLE
- \* A GREAT FIXED OR PORTABLE ANTENNA
- \* EASY TO STORE
- \* RUGGED

- \* LOW S.W.R.
- \* HANDLES 2KW DC +
- \* WELL BUILT
- \* INEXPENSIVE PRICES START AT \$45.00

FOR MORE INFORMATION ON THIS AND OTHER PRODUCTS WRITE:

PRO-SEARCH ELECTRONICS  
 DIVISION OF WURDACK & ASSOC., INC.  
 10411 CLAYTON RD. SUITE 305  
 ST. LOUIS, MO. 63131, USA  
 314-994-7872

PL-259  
 (SUPPLIED)



## FSK tone generator using an integrated tone dialer

Have you ever thought about redesigning or building an FSK (frequency shift keying) tone generator? If so, you are not alone. How many FSK

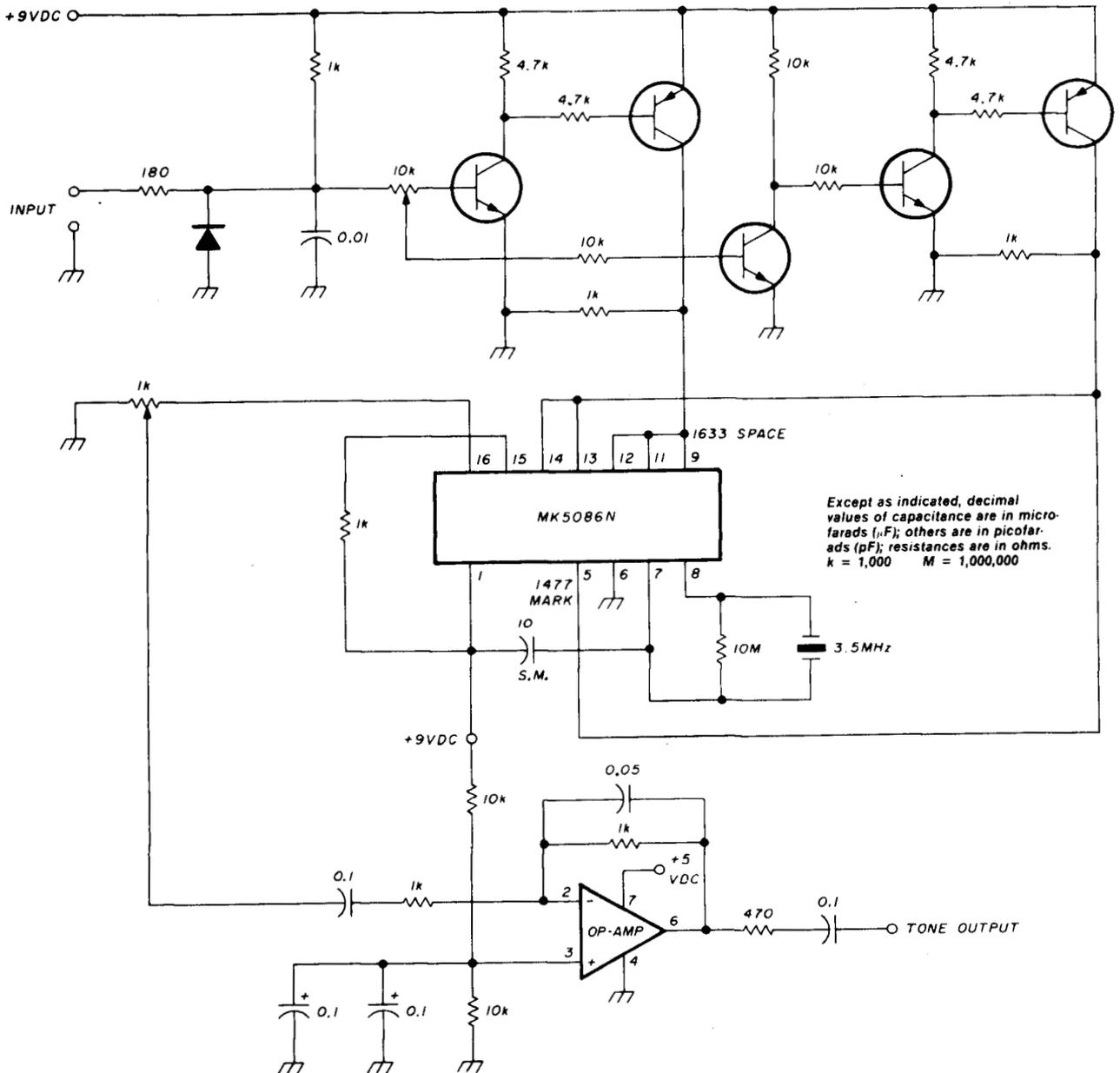


fig. 1. Schematic for the FSK tone generator.

generators have you seen that use an integrated circuit? To my knowledge there aren't very many.

Here is an easy way to build a circuit using a TouchTone™ chip which generates the frequencies needed for FSK. This circuit is connected between the teleprinter and transmitter. There are four main areas in constructing this circuit: the integrated tone dialer chip, switching circuit, filter, and amplifier. See fig. 1.

### frequencies

Both frequencies are generated by a Mostek MK 5086N IC chip. Pin 9 is used for space at 1.633 kHz, and pin 5 as mark at 1.47 kHz. A 3.579545 MHz television color-burst crystal is the frequency-determining element for the chip. To simulate keyboard operation, tie pins 14 and 13 to pin 5 and pins 12 and 11 to pin 9. This makes the Mostek think it is being switched by a keyboard.

Transistors in a switching circuit determine if a space or a mark is sent.

### filter and amplifier

An op amp provides a small amount of needed gain. A lowpass filter is used to reduce the harmonic content generated by the Mostek IC chip. This filter can be made by placing a capacitor across pins 2 and 6 of the op amp.

This circuit was constructed by Charles Aron, Ney Vew, and David Nagel at Northern Montana College in Havre, Montana. Special thanks are also given to Lee Barrett; without his time and advice this project would not have been possible.

**David Nagel**  
Havre, Montana

## capacitive-reactance meter multiplier

Recently I saw a large commercial type 0-150 Vac voltmeter in mint condition — just what I needed for my station control panel to monitor line voltage. However, the external series resistance was missing. Well, the owner sold it to me for \$2.50, as he admitted it didn't have too much value as it was. I discovered it would need an external 15-watt series resistance of about 1500 ohms. I decided to use a capacitor of the same reactance instead of using a resistance; reactances do not dissipate power and I would save energy.

The calculation for finding the required reactance is:

$$C = 1,000,000 / (6.28)(f)(XC)$$

where  $f$  is the line frequency, in this case 60 Hz,  $XC$  is the desired reactance in ohms equal to 1500 ohms, and  $C$  is the required capacity in  $\mu F$ :

$$C = 1,000,000 / (6.28)(60)(1500) = 1.77 \mu F$$

The theory and application worked fine. I used a good accurate ac voltmeter as my calibration standard. By paralleling a few small non-electrolytic fixed condensers from my junk box, it was easy to make my meter read the same. The real advantage of using condensers is that the power drain on the line is practically negligible. Naturally, the calibration is good only for the 60 Hz line voltage you are monitoring.

**William Visser, K4KI**

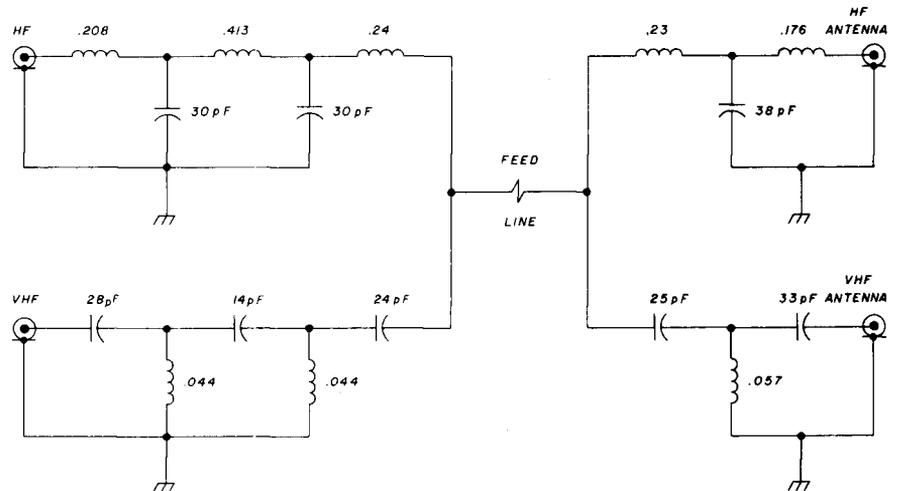


fig. 2. The capacitor changes to the N6RY diplexer mods.

## diplexer mods

You can diplex high frequency to go above 28 MHz (refer to N6RY's article on page 71 in the December, 1980, issue of *ham radio*). By building up the VHF part of the two boxes and changing a couple of the capacitors in the high frequency side of the

boxes, you can operate 10 and 2 or 10 and 220, or 6 and 2 or 6 and 220 meters at the same time. You can also add 6 or 10 meters to your 2 or 220 repeater by adding a box and an antenna on top and a box and a repeater or remote base on the bottom. All additions use the same feed line. The capacitor changes are shown in fig. 2.

If you have a 6-meter rig and want to go mobile, but can't find a spot to mount another antenna, try a 5/8 wave 2-meter antenna and check the SWR. If it is low on 6, just add the box between the 6 and 2-meter rigs and connect it to the same antenna.

**Robert McWhorter, K5PFE**

## simple diode tester

I recently had to check the peak inverse voltage of some surplus diode units. Searching for a suitable device, I decided to use a high-resistance transformer acquired at a flea market sale. This particular unit had a high resistance secondary (over 600 ohms) which precluded its use for service in a power supply unit supplying more than minimal power. This was hooked up as shown (fig. 3), in a simple full-wave doubler circuit, and provides over 1,000 volts dc from a secondary rated 400 volts ac.

There are two methods for checking diodes for PIV. One method is to increase the test voltage until there is 10  $\mu$ A of reverse current (for a 1-ampere diode) and then to rate the diode at a safe peak inverse voltage of 20 percent lower. The method I prefer is to calibrate for a PIV of that value attained when 5  $\mu$ A of reverse current flows. Either way gives a satisfactory rating for diode breakdown voltage, see fig. 4.

Any multimeter with a basic sensitivity of at least 5,000 ohms per volt can provide the needed test current, since the basic limiting resistance is present in the meter's multiplier resistance. A convenient method of checking voltage at the same setting is to simply short out — with an insulated screwdriver — the terminals across the diode being tested. The high-resistance secondary precluded the need for any limiting resistors in the circuit, and the low-capacity filter capacitors cause the output voltage to drop sharply under load, tremendously reducing the hazard of testing with high voltage sources.

Neil Johnson, W2OLU

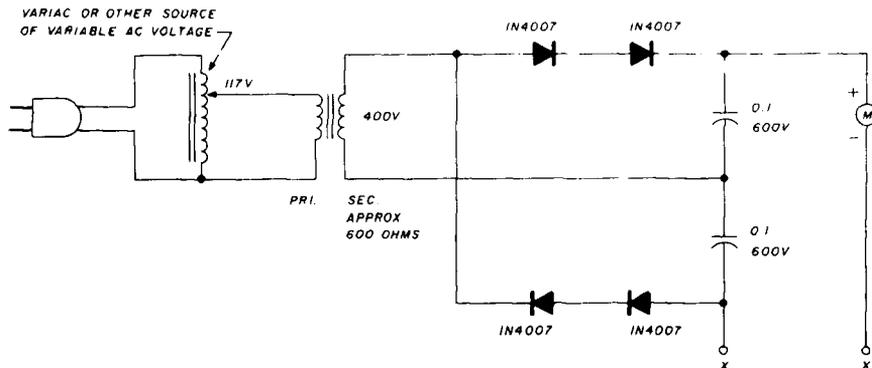


fig. 3. Simple tester for checking silicon diodes. To test diode, insert in circuit at x, and then raise input voltage from zero. Meter M is any sensitive voltmeter on 1,000 volt scale, having sensitivity of 5,000 ohms per volt or more. Alternate method is to utilize a 0-200 microammeter and 5 megohms of resistance.

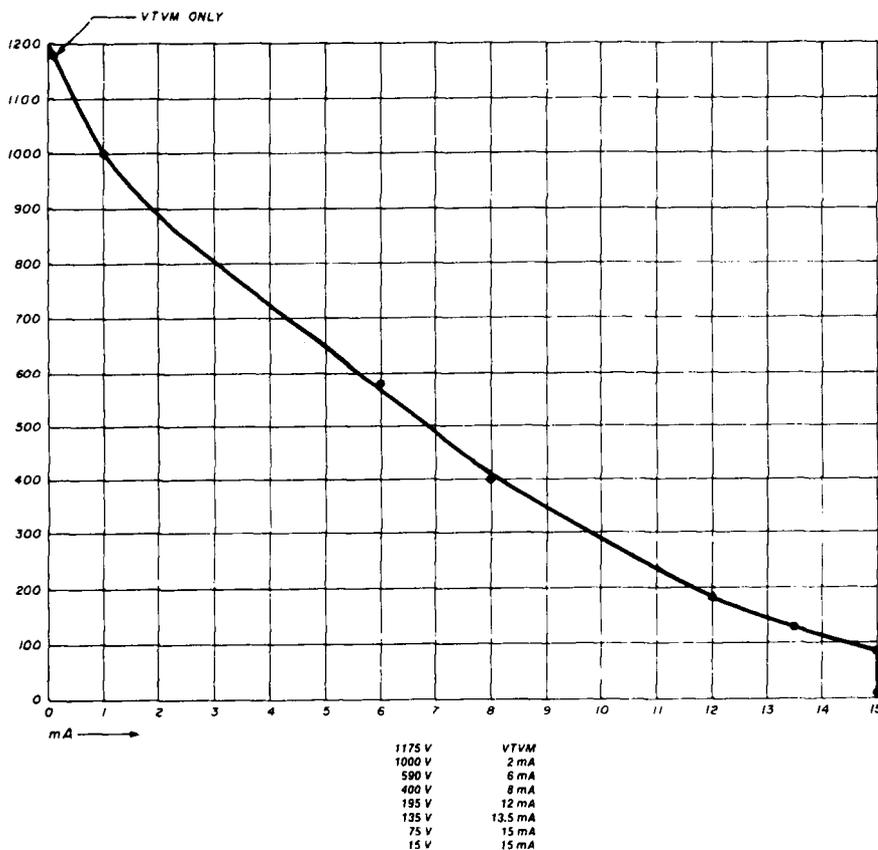


fig. 4. Sample rating chart. Safety is enhanced by limiting current by high impedance supply.

## improved logic probe

I was considering buying or building a logic probe to complement my dual channel scope when troubleshooting my homemade microcomputer. The August, 1980, issue of *ham radio* finally convinced me to build my own version.

The following specs were essential: indication of high-low-open conditions; capture-stretching short-positive or negative pulses; operation at TTL (5V) and at CMOS (5-15V) levels; high and low should be indicated at the specified levels for each logic family and every voltage, that is, 0.8 and 2.5V for TTL and  $1/3 V_{CC}$  and  $2/3 V_{CC}$  for CMOS.

I took two ideas from N6UE's article<sup>1</sup> in the August issue on page 38: using the 555 timer and voltage regu-

lation for the display LEDs? I met the requirements of the first, third, and last specs by using National Semiconductors' 339 quad, single supply comparator.<sup>3</sup> I obtained the required reference levels from a voltage dividing network and a switch, which modifies the resistor values to suit TTL-CMOS levels. See fig. 5.

Comparators a and b serve as a window detector, both being high inside the forbidden voltage region, while going low at a high or low input. A low from comparators a and b is used to drive the high (red), and the low (green) LEDs. The negative transitions are differentiated and ORed by the remaining two comparators, and applied to the 555 for stretching. The timer drives the pulse (orange) LED. An LM309 TO-5 voltage regulator

provides protection for the LEDs against voltage rise.

I wired the prototype on a piece of Veroboard. As I lack a PC board production capability at home, I decided to stay with the prototype.

Tests indicate that the probe operates as required up to about 250 kHz square wave input. The minimum captured pulse width is about 4  $\mu$ s. These results are close enough to the specified delay through the comparators to indicate that speed-pulse width limitations could be reduced by using faster comparators.

### references

1. R.S. Isenson, N6UE, "Digital Logic Probe," *ham radio*, August, 1980, page 38.
2. Signetics NE555V data sheet.
3. National Semiconductors LM339A data sheet.

J. Rozenhal

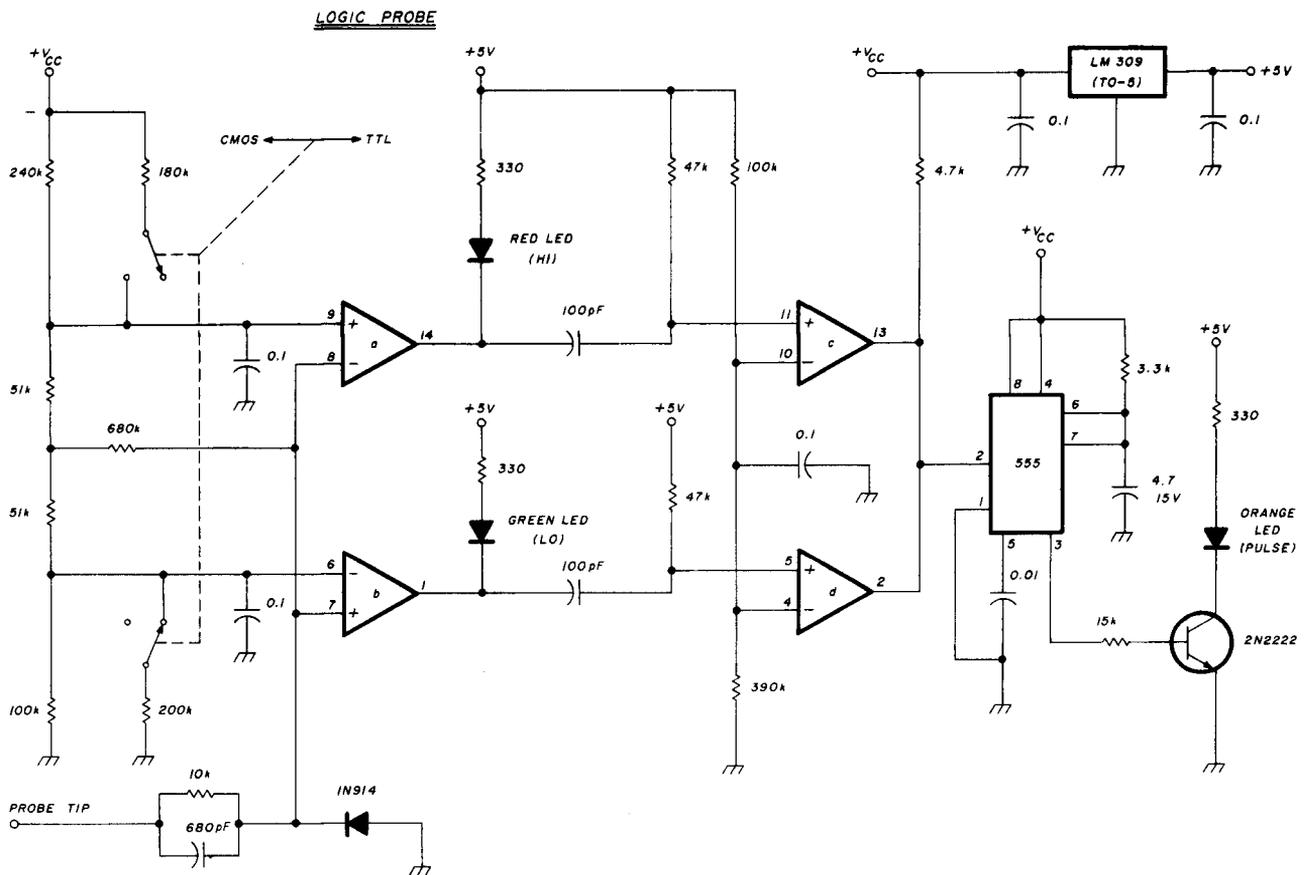


fig. 5. The improved logic probe.

# SEMICONDUCTORS SURPLUS

A DIVISION OF Electronic Emporium, Inc.

2822 North 32nd Street Unit 1  
CALL (602) 956-9423

Phoenix, Arizona 85008  
VISA or M/C ONLY 800-528-3611



**PHILIPS OSCILLOSCOPE**  
Model PM3232 SOLID STATE  
Triggered Dual Beam  
BANDWIDTH: 0-10 MHZ  
SENSITIVITY: 2mV to 50mV/cm  
0.1V to 10V/cm  
SWEEP RANGE: 0.2us to 50us  
0.1ms to 50ms  
0.1sec to 0.5 sec.  
10 selections for sweep  
A-B Beam selector switches  
8cm x 10cm CRT Display  
PORTABLE MODEL \$499.99 each  
LAB MODEL \$309.99 each

Keying Relay #M-7470182  
type 78CCA101 28vdc coil  
SPDT Struthers-Durn Inc.  
\$29.99

Amphenol #300-10099  
Coax relay 26vdc coil  
SPDT type (N) Connectors  
\$49.99

Transco #1460-20  
type SA-303U SPDT  
28vdc coil type (N)  
Connectors \$69.99

Amphenol #327-10582-3  
26vdc coil SP3T type  
BNC Connectors \$39.99

Magnecraft #W120X-14  
SPDT 100 ohm coil 12vdc  
\$29.99

Transco #16500NAU 12-15  
28vdc coil SP3T  
type (N) connectors \$59.99

Amphenol #323-11506-3  
26vdc coil SP4T  
BNC connectors \$59.99

RF Products #DK300-11732  
Amphenol #300-11732  
26vdc coil SPDT \$39.99

Quantatron #SA-70P10-1  
22 to 30vdc coil SPDT \$39.99

FXR #300-11540  
Amphenol #300-11540  
26vdc coil  
BNC Connectors \$39.99

Amphenol #360-11891-48  
26vdc coil SPDT  
BNC Connectors \$49.99

Vacuum Relay  
Jennings #RCSA5101A24  
10KV 25kw @ 30MHz relay  
coil 19 to 29vdc \$139.99

High Voltage Power Supply  
Solid State Model LU-15A  
mfd. by Venus Scientific Inc.  
output + 15kvdc @ 300ua  
@ 16vdc input @ 800ma  
Focus voltage: + 725v @ 1ma  
size 5" long x 3" deep x 1 1/4"  
high \$19.95

Lambda Power Supply  
Model LXD-3-152R  
Dual regulated power supply  
input 105 to 132vac  
output 12 to 15vdc @ 400ma  
\$39.99

Pencil type Soldering Iron  
30watts 110vac  
Model 50B100 \$4.29

Computer Grade Capacitors  
2400mfd @ 200vdc \$2.00  
30000mfd @ 60vdc \$1.00  
22000mfd @ 25vdc \$1.00  
2100mfd @ 200vdc \$2.00  
26000mfd @ 30vdc \$1.00  
900mfd @ 150vdc \$2.00  
1800mfd @ 450vdc \$9.99  
6200mfd @ 150vdc \$3.00  
10000mfd @ 75vdc \$1.00

Spectra-Strip  
twisted pair wire  
24 awg 300V style 1061  
Ins. .009" 80°C 1000ft for \$28.00

Columbia  
22 awg 4 pair shielded  
cable, grey jacket  
style 2464 part #91902  
1000ft for \$100.00

Motorola 3amp 1000piv  
Rectifiers 10 for \$1.20  
or 100 for \$8.00 1000ft for \$65.00

Regulators IC  
78H05 5V @ 5amps \$3.00  
78H12 12V @ 5amps \$4.00  
78M05 5V @ 1/2 amp .39  
79M05 5V @ 1/2 amp .49  
7808 8V @ 1amp .59

AA Nickel Cad Battery Pk.  
(pack of 2) New \$2.00 ea.  
1.2V per cell 500 mah @ cell

Optic Fiber cable  
10ft for \$5.00 or 100ft for \$30.00

IC sockets solder type  
8-pin .07 22-pin .16  
14-pin .10 24-pin .17  
16-pin .11 28-pin .19  
18-pin .13 40-pin .27  
20-pin .14

IC sockets w/wrap  
14-pin .30 40-pin .90  
16-pin .35

Dip switches  
4 position .60 10 position \$1.60  
7 position .80

12VDC lamps, 60ma  
1/8" round x 1/2" long  
w/12" leads .29 ea.  
or 10 for \$2.00

Electrolytic Caps.  
Mallory #TCG1220U075N3C3P  
1200uf 75VDC \$1.39 ea.  
or 4 for \$4.00

Mallory #TCG3720040N3L3P  
3700uf 40VDC \$1.00 ea.  
or 10 for \$8.00

Nichion #50ULB150-T  
150uf 50VDC .39 ea.  
or 4 for \$1.00

Mallory #TCG102U040J2C3P  
1000uf 40VDC .89 ea.  
or 3 for \$2.00

Ayer Eng. #85CX442U006GLY  
4400uf 6VDC .69 ea.  
or 2 for \$1.00

MEM 631 Dual Gate Diode  
protected FET vds = 25V  
Id = 30ma mhos = 800(min).50ea.

Temp. controlled Heating  
Plate 4" x 9" element size  
hot plate size 5 1/2" x 10"  
120vac @ 120 watts \$1.99

Triad F23U 115vac input  
10vct @ 7amps output \$8.99

SCR 25 amps 600 Volts  
stud mount \$1.50

Gould Nickel Cadmium Batteries  
pack of 2 part #405408  
2.4V @ 600mah (new) \$3.29

G.E. Rechargeable Nickel  
Battery pack 6 cells  
a total of 14.4vdc @ 1ah  
#41B001LD5G1 (used) \$7.99

1N4148/1N914 Switching Diodes  
30 for \$1.00 or 120 for \$3.00

NE/CA55V Timer IC's  
.39 ea. or 10 for \$3.00

Dual Color Led's  
.40 ea. or 10 for \$3.29

Trim pots Thumbwheel type  
.30 ea. or 10 for \$2.50  
sold not mixed

100 ohm	20K ohm
150 ohm	25K ohm
200 ohm	200K ohm
250 ohm	250K ohm
500 ohm	500K ohm
1K ohm	750K ohm
1.5K ohm	2meg ohm
2K ohm	2.2meg ohm
2.5K ohm	3meg ohm
5K ohm	5meg ohm
10K ohm	

5 pin din jack & plug set  
1 male & 1 female \$1.00/set  
or 10 sets for \$6.50

TO-3 Transistor sockets  
phenolic type .29 ea.  
or 6 for \$1.00

Cable ties #T-18R 100 per bag  
mil. spec. #MS-33685-4  
4" long made by Tylor Corp.  
\$2.00/bag of 100 or 10 bags/  
1000 for \$15.00

Triad F74U Transformer input 117vac  
output 28vct @ 2amps &  
output 28vct @ 2amps \$19.99

Sciott Corp. #67069940 input 117vac  
output 26.8vct @ 800ma  
26.8vct @ 800ma  
21.9vct @ 1.1amp \$9.99

Triad F23U input 115vac  
output 10vct @ 7amps \$12.99

NATA #30468359 input 117vac  
output 25.2vct @ 2.8amps \$6.99

Electro Vectro #E30554 input 117vac  
output 17v @ 1.5amps  
output 17v @ 1.5amps \$6.99

Keystone #PL-25-10 input 117vac  
output 25vct @ 20va  
output 10vct @ 4va \$5.99

Stancor #P8657 input 117vac  
output 12v @ 2amps \$5.99

Stancor #P-8720 input 230vac  
output 24vct @ 85ma \$2.99

Plug in the wall #Plt-86 input 120vac  
output 6vac @ 10ma \$2.99

Plug in the wall #2-2286 input 120vac  
output 5.8vdc @ 125ma \$2.99

Plug in the wall #C-160 input 117vac  
output 3.6vdc @ 60ma \$2.99

Southern #EX-1163-T input 110vac or  
220vac output 17vct @ 1amp \$3.99

Whistle Activated Switch  
\$2.50 ea. or 3 for \$6.00

IR 3E05 3amp 50piv Rectifier  
10 for \$1.00 or 100 for \$6.00

4MHZ Crystals HC18/U \$1.00  
8MHZ Crystals HC18/U \$1.00  
100KHZ Crystals HC33/U \$3.99

9Volt Battery Clips 10 for .99

40673 FET N-channel MOS FET  
.79 ea. or 10 for \$5.00

MC6860L 0-600 bps Digital  
Modem \$4.99

95H90DC Hi-speed Divide  
10/11 Prescaler \$6.00

Touch Tone Pad  
This pad contains all electronics  
to produce standard touch-tone  
tones. It has an AMI S2559 digital  
tone. Generator has power Cmos IC.  
Uses TV crystal, standard (3.58MHz)  
to derive all frequencies thus  
providing very high mute drivers on  
chip. Interfaces directly to a  
standard telephone push-button or  
calculator type X-4 keyboard. The  
total harmonic distortion is below  
industry specification on chip  
generation of a reference voltage  
to assure amplitude stability of  
the dual tones over the operating  
voltage & temperature range. Dual  
tone as well as single tone capability.  
\$6.99

Gates Rechargeable Lead Acid Batteries  
pack of 6 2Volt 2.5AH D-Cells  
(used) \$7.99

When Calling  
KAT/KS (REV'N)

Presenting the Revolutionary  
**MONGOOSE 2000**



\$279.95

200 CHANNEL 10 METER  
ALL MODE TRANSCEIVER

**Specifications**

**General**  
Frequency composition: PLL synthesizer  
Frequency range: 28 000 MHz to 30 000 MHz  
Channels: 200  
Frequency space: 10 kHz  
Emission: AM/FM/USB/LSB/CW  
Power source: 13.8 V DC

**Receiver**  
Sensitivity: AM — 1 micro-V @ 10 dB S/N  
FM — 1 micro V @ 20 dB S/N  
SSB/CW — 0.5 micro-V @ 20 dB S/N  
Selectivity: 60 dB  
Audio Output: 2 W @ 8 Ohm  
Fine Tune range: ± 800 Hz  
Course Tune range: ± 5 kHz  
Squelch range: 0.5 to 300 micro-V  
Intermediate freq: AM/FM — 10.695 MHz/455 kHz  
SSB/CW — 10.695 MHz

**Transmitter**  
RF power output: High Mid Low  
SSB/CW 12 W 8 W 2 W  
AM 7.5 W 4 W 1 W  
FM 10 W 7 W 2 W

SSB generation: Double-balanced modulator with crystal lattice filter  
Coarse Tune range: +5 kHz

Make Check or Money Order payable to:

**COIN INT'L., INC.**


2305 N. W. 107th Avenue, Miami Free Trade Zone  
Miami, FL 33172 • (305) 593-9300

VISA & MASTER CARD ACCEPTED.

Florida Residents please add 5% sales tax.  
Allow 6-8 weeks for delivery. ✓ 121

**ATTENTION  
RADIO HOBBYISTS!**

**FREE ELECTRICITY  
FROM SUNLIGHT!**

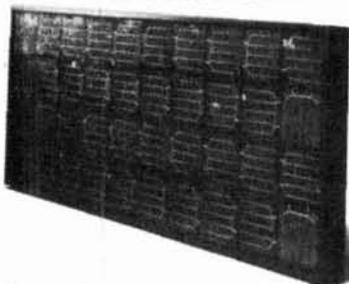

Solar electricity is here, and it can power everything from a portable radio to a complete Amateur station.

Solarex, the nation's pioneer in practical photovoltaics, has a SOLAR WONDERBOOK catalog filled with p-v panels, mini-panels, batteries, ancillary equipment, 12-volt tools, scientific education items, books, and much more.

Here's everything you need to add an exciting new dimension to your do-it-yourself projects.

To get your WONDERBOOK, send \$5 (refunded on your first \$15+ order) to:

**ENERGY SCIENCES**  
Dept. 533, 832 Rockville Pike  
Rockville, MD 20852 ✓ 127

# The Interface

Software Available for Six Computers

The versatility of the personal computer gives you a whole new world with the Kantronics Interface™ and Hamsoft™ or Hamtext™. The Interface™ connects to any of six popular computers with Hamsoft™ or Hamtext™ giving you the ability to send and receive CW/RTTY/ASCII. An active filter and ten segment LED bargraph make tuning fast and easy. All programs, except Apple, are on program boards that plug directly into the computer.

Hamtext™, our new program, is available for the VIC-20 and Commodore 64, with all the features of Hamsoft™ plus the ability to save received information to disc or tape, variable buffer sizes, VIC printer compatibility, and much more. Our combination of hardware and software gives you the system you want, with computer versatility, at a reasonable price.

**Hamsoft™ Features**

Split Screen Display  
1026 Character Type Ahead Buffer  
10 Message Ports-255 Characters each  
Status Display  
CW-ID from Keyboard  
Centronics Type Printer Compatibility  
CW send/receive 5-99 WPM  
RTTY send/receive 60, 67, 75, 100 WPM  
ASCII send/receive 110, 300 Baud

**Hamsoft™ Prices**

Apple Diskette \$29.00  
Atari Board \$49.95  
VIC-20 Board \$49.95  
TRS-80C Board \$59.95  
TI-99 Board \$99.95

**Hamtext™ Prices**

VIC-20 Board \$99.95  
Commodore 64 Board \$99.95



Suggested Retail \$169.95

For more information contact your local Kantronics Dealer or:  
Kantronics 1202 E. 23rd Street Lawrence, KS 66044

**TIDBITS**

**MORSE CODE, BREAKING  
THE BARRIER**

by Phil Anderson, WØXI

Learning the Morse Code does not have to be the painful experience many folks make it out to be. This little booklet is chockfull of helpful and highly recommended hints and tips on how to learn the Morse Code. Uses the high/low method to eliminate the dreaded 10 wpm plateau. ©1982, 1st edition.

PA-MC Softbound \$1.50 each

Please add \$1.00 for shipping and handling.


**HAM RADIO'S BOOKSTORE**  
Greenville, NH 03048

FREE! FREE! FREE! FREE! FREE!

FREE! FREE! FREE! FREE! FREE!

SEND FOR OUR NEW  
1983 PARTS CATALOG  
THOUSANDS OF SURPLUS  
ELECTRONIC PARTS, SUPPLIES  
AND DEVICES.

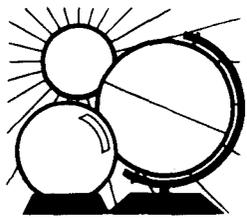**ALL ELECTRONICS CORP**  
905 S. Vermont Ave.  
P.O. Box 20406  
Los Angeles, Cal. 90006 ✓ 105



Garth Stonehocker, KØRYW

## DX FORECASTER

### spring DX

The powerful DX months (around the equinox) are here for us to try again. Over the years March and April have provided excellent 6-meter openings on transequatorial (TE) paths. Using 6-meter openings as a criterion for the higher-frequency-band DX, last year didn't have as many openings as 1981, but the opening on March 4 was acclaimed the best in years in *Westlink Report*. The March 4 opening was a period of high solar flux and geomagnetic disturbance, which probably influenced the TE (one-long-hop) propagation. April was also roaring with TE openings from the southern U.S. to South Africa, South America, New Zealand, and Australia. The other openings in April were not so pronounced, as the solar flux was lower. However, four large disturbances (April 2, 11, 25, and 29) and two smaller disturbances (April 17 and 21) increased the ionization near the geomagnetic equator for high maximum-usable frequencies for TE.

This year's 6-meter openings may be fewer in number since we are already near the half-way point on the down-side of cycle 21. The sunspot number should be about 75 (123 flux units). The second maximum 1981-82-83) period of geomagnetic-ionospheric disturbance in cycle 21 is expected to be the dominating factor for openings this year. These disturbed periods during April are expected around the 5th, 15th, and 23rd. The latter is the longer recurrent type (see February, 1982 DX Forecaster).

### last minute forecast

The higher segment of the h-f bands (6-30 meters) will probably be

best during the middle of the month. Watch for the high radio flux and disturbance numbers from WWV at 18 minutes after the hour. On the lower bands (30-160 meters)\*, night DX will be best during the first and last weeks of the month, particularly in-between the springtime frontal thunderstorms when QRN should be low. Your favorite TV weather forecaster will show these fronts moving across your QTH.

The perigee of the moon's orbit (for moon-bounce DX) is on the 21st at 2100 hours; the moon will be at full phase on the 27th at 0631 hours. There will be a short meteor shower, the Lyrid, on April 20-22. The rate is five per hour, hardly a real help for meteor-scatter DX. But a bigger shower, the Aquarid, starts before the end of the month, peaks on May 5, and ends by mid-May. Its rate is 10 to 30 per hour.

### band-by-band forecast

*Six meters* may provide occasional band openings with a peak during the late afternoon hours. Transequatorial north/south paths will be the best. Your guide to good conditions are strong openings on 10 meters with high values of solar flux and A and K geomagnetic indices.

*Ten and fifteen meters* will be open to many areas of the world from morning until early evening hours most days. Times of geomagnetic disturbances will limit the number of signals heard, but listen carefully — they can be from very unusual places. Fifteen meters should stay open later in the day than 10 meters. Operate 10 first and move down to 15. More hours of daylight means earlier band openings and longer periods of operation.

*Twenty meters* will be the main daytime DX bands, as it is almost always open to some part of the world. It opens to the east as the sun rises and extends into the late evening hours to the west. Geomagnetic disturbances do not affect this band as much as the higher ones, but look for unusual transequatorial DX propagation once in a while. One-hop transequatorial DX of 5,000 to 7,000 miles (8,000 to 11,200 km) may be possible in the late evening hours during some of these unusual conditions.

*Thirty meters* is a day and night band. The day portion should be like 20 meters except the signal strengths may decrease during midday on some days. Days of decreasing strength should be those with high solar flux values. This band will also work well into the night, often through the night. Nights this doesn't hold true will most likely follow a day with a very high solar flux value. The problem time is usually the hour or so before dawn. The workable distance may be expected to be greater than 80 DX at night and less than 20 during the day.

*Forty and eighty meters* will exhibit short skip conditions during daylight hours and lengthen after dark. The bands will open to the east just before your sunset, swing more to the south toward Latin America about midnight, and end up in Pacific areas during the hour or so before dawn. On some nights these bands will be as good as during the winter DX season. The coastal regions usually have the edge for working rare DX on these bands.

*One-sixty meters* will probably bring many nights that will remind you of last summer's noise. However, many good nights are left for working DX before this summer's noise comes to stay. Propagation on 160 meters will approximate a shortened 80-meter condition.

### ham radio

\*Editor's note: 30 meters because of its unique place in the h-f spectrum and characteristics is discussed in both sections (higher/lower segments) of the h-f band forecast.

### WESTERN USA

GMT	PST	N	NE	E	SE	S	SW	W	NW
0000	4:00	15	20	15	10	15	10	10	10
0100	5:00	15	20	20	10	15	10	10	10
0200	6:00	15*	20	20	10	15	10	10	15
0300	7:00	15	20	20	15	15	10	10	15
0400	8:00	15	20	20	15	15	10	10	15
0500	9:00	20	20	30	15	20	10	15	15
0600	10:00	—	40	30	20	20	15	15	20
0700	11:00	—	40	20	20	20	15	15	20
0800	12:00	—	—	20	20	20	15	15	20
0900	1:00	—	—	—	20	20	15	20	20
1000	2:00	—	—	—	—	20	20	20	20
1100	3:00	—	—	—	—	30	20	20	—
1200	4:00	—	—	—	—	—	20	20	—
1300	5:00	—	—	—	—	—	—	—	—
1400	6:00	—	—	—	—	—	—	—	—
1500	7:00	—	—	—	—	—	—	—	—
1600	8:00	—	—	20	15	15*	—	—	—
1700	9:00	20	20	10	15	—	15	15	—
1800	10:00	15*	20*	10	10	—	15	15	—
1900	11:00	15	20*	10	10	20	15	15	—
2000	12:00	15	20*	15	10	15	10	15	15
2100	1:00	15	20*	15	10	15	10	10	15
2200	2:00	15	20*	15	10	15	10	10	10
2300	3:00	15	20	15	10	15	10	10	10

### MID USA

GMT	MST	N	NE	E	SE	S	SW	W	NW
0000	5:00	15	20	15	10	15	10	10	10
0100	6:00	15	20	15	10	15	10	10	10
0200	7:00	15	20	15	10	15	10	10	15
0300	8:00	15	20	20	15	20*	10	15	15
0400	9:00	20	20	30	15	20*	15	15	15
0500	10:00	—	20	30	15	20	15	15	20
0600	11:00	—	20	30	20	20	15	20	20
0700	12:00	—	20	20	20	20	20	20	20
0800	1:00	—	20	20	20	20	20	20	20
0900	2:00	—	20	20	20	20	20	20	20
1000	3:00	—	—	—	—	20	20	—	—
1100	4:00	—	—	—	—	—	—	—	—
1200	5:00	—	—	—	—	—	—	—	—
1300	6:00	20	—	—	15	—	—	—	—
1400	7:00	20	20	20	15	—	—	—	—
1500	8:00	20	20	15	15*	—	—	—	—
1600	9:00	20	15	15	10	—	—	—	—
1700	10:00	20	15	10	10	—	15	15	—
1800	11:00	20	15	10	10	—	15	15	—
1900	12:00	—	15	10	10	—	15	15	—
2000	1:00	—	15	10	10	15	10	15	15
2100	2:00	—	15	15	10	15	10	10	15
2200	3:00	—	15	15	10	15*	10	10	15
2300	4:00	—	15	15	10	15	10	10	10

### EASTERN USA

GMT	EST	N	NE	E	SE	S	SW	W	NW
0000	7:00	15	20	15	10	20	10	10	10
0100	8:00	15	20	15	10	20	10	10	10
0200	9:00	15	20	20	15	20	10	15	15
0300	10:00	15	40	20	15	20	15	15	15
0400	11:00	20	40	30	15	20	15	15	20*
0500	12:00	20	40	30	15	20	15	20	20
0600	1:00	20	20	15	15	20	20	20	20
0700	2:00	—	20	15	20	20	20	20	20
0800	3:00	—	20	20	20	20	20	20	20
0900	4:00	—	—	—	20	20	20	—	—
1000	5:00	—	—	—	20	—	—	—	—
1100	6:00	—	—	—	15	—	—	—	—
1200	7:00	—	—	—	—	—	—	—	—
1300	8:00	—	15	—	—	—	—	—	—
1400	9:00	20	20*	15	—	—	—	—	—
1500	10:00	20	15	15	10	—	—	—	—
1600	11:00	15	15	10	10	—	—	15	—
1700	12:00	20	15	10	10	—	20	15	—
1800	1:00	—	15	10	10	15	20	15	—
1900	2:00	—	15	10	10	15	15	15	—
2000	3:00	—	15	10	10	15	10	10	20*
2100	4:00	—	15	10	10	15	10	10	15
2200	5:00	20	20	15	10	15	10	10	15
2300	6:00	20	20	15	10	15	10	10	10

\*Look at next higher band for possible openings.

# NCG WORLD BAND COMMUNICATIONS



**15M**

Tested and Proven 15 Meter Mobile Transceiver USB and CW

Power-High 10 watts, Low 2 watts  
VFO Tuning, Noise Blanker  
Fine Tune  $\pm 1$  kHz

Digital Frequency Counter  
13.8 VCD @ 3A Neg. Ground  
9.5" L x 9" W x 2.5" H  
All this PLUS the freedom of DXing

Regular Price: \$305.00

**SPECIAL PRICE: NOW \$279.00**

FREE 15 Meter Anixter Mark Antenna with factory direct purchase from this ad

Order Direct — or from your local dealer

Just  
Slightly  
Ahead



**160/10M**

ALL NEW, with the features you have been waiting for  
HF 160-10 meters SOLID STATE Transceiver 200 watt PEP

All 9 HF Bands ready to go  
AC/DC Power supply built in  
3-Step Tuning 1 kHz/100Hz/25Hz  
4 memories, Auto Scan

Automatic Up/Down Tuning Advanced Systems  
Dual VFO, Solid State-Adjustment Free, IF Tuning, IF Offset

Noise Blanker, Mic. Compressor  
VOX, CW Side tone, AC 120V DC 13.8 RTTY-Fax operation  
USB-LSB CW (Narrow CW filter optional).

Regular Price: \$1075.00

**SPECIAL PRICE: NOW \$949.50**

N.C.G. CO.



1275 North Grove Street  
Anaheim, CA 92806  
(714) 630-4541

Prices and specifications subject to change without notice or obligation  
Calif. Res. add Sales Tax

Mail Order COD  
Visa Master Charge  
Cable: NAT COLGLZ

✓ 156

## SPEAKER QUALITY IS THE PRIMARY KEY TO YOUR STEREO SYSTEM'S SOUND

And speakers are easy to make—and very difficult to design. *Speaker Builder*, a new quarterly from the publishers of *Audio Amateur*, has all the design answers you novice-to-experts need to dramatically improve the quality of sound you're getting from your stereo system. The drivers are relatively cheap and the sources for them are all listed in *Speaker Builder's* pages. As an experienced ham, you probably know your way around your audio system already. Here's an easy way to make what you have sound a whole lot better at minimum cost.

*Speaker Builder* can save up to two thirds of the cost of the speakers—which translates to almost one third of your outlay for your stereo system. Over 110,000 Americans will build their own enclosures this year—and you can too! Your dream speaker is probably well within reach if you build it yourself. There's a lot of help around already and now, *Speaker Builder* brings it all together in an assortment of articles that are comprehensive and a mix of both simple and advanced projects to help you choose and build the best type for your listening room.

- ★ Bass Reflex
- ★ Electrostatics
- ★ Infinite Baffle
- ★ Specials: Ribbon, Air motion transformers
- ★ Basic data on passive and electronic crossovers.
- ★ Horns
- ★ Transmission Lines

There will be reports on building the many kit speakers and enclosures now available, and a roundup of suppliers for drivers, parts, and kits. Articles range from the ultimate (650 lbs. each) to tiny plastic pipe extension speakers. From time delayed multi-satellites to horn loaded subwoofers, as well as modifications of many stock designs.

SPEAKER BUILDER, P.O. Box 494H, Peterborough NH 03458-0494 USA <sup>H13</sup>

- Enter my subscription to *SPEAKER BUILDER* for one year at the special rate of \$10.00.  
 Make that a two year subscription at \$18.00.  
 Check enclosed  Charge to my  MasterCard  Visa  charge card.

# \_\_\_\_\_  
 Expire: \_\_\_/\_\_\_/\_\_\_ Phone Orders (603)924-6526

Name: \_\_\_\_\_  
 Street & No. \_\_\_\_\_

Town \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

I understand that the unexpired portion of my subscription will be refunded after my first issue if the magazine is unsatisfactory for any reason. Make checks and money orders payable to Speaker Builder. Rates above are for USA only. Outside USA add \$2.00 per year for postage. Non U.S. checks must be drawn in U.S. currency only.

✓ 174

Gordon West's  
**RADIO SCHOOL**

# STEREO CODE TAPES?

Don't laugh!

It's about time.....code tapes that are fun to listen to, anywhere! Improve your code skills, in days, with these new Stereo Code Cassettes. Whether you are learning the code, or preparing to upgrade for a higher ticket, we have a **RADIO SCHOOL** course for you.

In the car, practice with both channels turned on. You will hear the code, and voice answers, over your stereo system.

At home or work, practice with a pencil by turning off the voice channel and writing down the text.

Practice your sending by turning down the code channel and keying the letters after the voice command.

On regular monaural tape players, both channels play in equal volume.

Gordon West, WB6NOA, has trained thousands of students in his college classes with this method. These stereo tapes are now available nationally by popular demand.

Let's face it, most code tapes are tedious and dull. These are fun! They contain typical FCC type texts, and adhere exactly to FCC recommended code speed ratios and tone. When you take the ultimate code test from the new volunteer examiners, there will be no surprises.

By the way, **RADIO SCHOOL** produces volunteer examiner code test tapes too!

- |                                                                                                                                                       |                                                                                                                                                                           |
|-------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <input type="checkbox"/> <b>Learning Code in Stereo</b><br>4 @ 1½ hour stereo cassettes for learning the code to 6 WPM.                               | <input type="checkbox"/> <b>XTRA Class Code Course</b><br>4 @ 1½ hour stereo cassettes for 13-20 WPM speed increase plus practical FCC type tests.                        |
| <input type="checkbox"/> <b>General Class Code Course</b><br>4 @ 1½ hour stereo tapes for 6-13 WPM code speed increase plus practical FCC type tests. | <input type="checkbox"/> <b>Volunteer Examiner's Code Course</b><br>4 @ 1½ hour stereo tapes for volunteer examiners to test 5WPM, 10 WPM, 13WPM, and 20WPM speed skills. |

Each course is \$39.95 from local dealers or from **RADIO SCHOOL**.

Write for the **RADIO SCHOOL** Catalog of Code & Theory Courses. Dealer, club and instructor quantity inquiries invited. Write: **RADIO SCHOOL, INC.** 2414 College Drive, Costa Mesa, CA 92626, (714) 549-5000

✓ 167



## REVIEW:

### Daiwa CN520 SWR and power meter

About the only time we had a chance to use a dual needle SWR meter was when we used the TMC transmitter at W1AW. That was, until MCM (distributors for selected Daiwa products), sent us their CN520 SWR and power meter.

The Daiwa meter comes in four different models: the CN150 for 1.8-60 MHz 20/200 watts, the CN520 for 1.8-60 MHz 200/2 kW, the CN530 for 50-150 MHz 20/200 watts, and the CN540 for 140-250 MHz 20/200 watts. Each of these units measures just 2.83 x 2.83 x 3.62 inches (72 x 72 x 96 mm) and weighs less than a pound. Rf connectors on each are SO-239 and accuracy is listed at ± 10 percent.

Installing the SWR bridge is a matter of connecting it in-line between your transmitter and load. Setting the meter to the correct power position ensures that you will get an accurate SWR reading. Two needles are used to measure SWR: the left needle measures forward power, the right needle measures reflected power. The point at which the two needles cross is the SWR reading. SWR is clearly marked on the meter face by a series of red lines. This is quite handy and allows the operator to know instantly how well his line is matched between transmitter and antenna.

The meter case has two brackets on the side for possible use as a mobile or remote mount.

This is a nice meter. When compared to a lab-type meter, its accuracy is quite good, well within the rated specifications. We find the CN520 to be a breeze to use and a very valuable addition to our ham shack. In fact, after using the dual reading meter it is very hard to use any other kind of unit.

Price is \$69.95 retail. For more information, contact your local dealer or MCM direct at 858 E. Congress Park Drive, Centerville, Ohio 45449. Reader Service Number 301.

N1ACH


## slow-scan TV system

Commsoft has developed PhotoCaster™, a slow-scan television system for the Apple II computer. PhotoCaster provides an easy way for hams who own Apple computers to get started on SSTV with a full-featured black and white and color system. PhotoCaster includes a circuit board to interface an Apple to a TV camera and a receiver/transmitter, plus a two-disk software package.

PhotoCaster can also add titles and graphics, create video special effects, enhance images, retrieve and store pictures on disk, and print high resolution pictures with an MX-80 printer.

Black and white pictures are processed with a resolution of 128 by 128 pixels and sixteen levels of gray. In the color mode, eight colors are available with sixteen saturation levels. Color pictures are taken with an unmodified black and white TV camera using a three-frame RGB sequence. Standard RGB transmission formats are available in addition to a unique Apple-to-Apple single-frame color mode which takes eight instead of the usual twenty-four (or more) seconds to transmit a color picture.

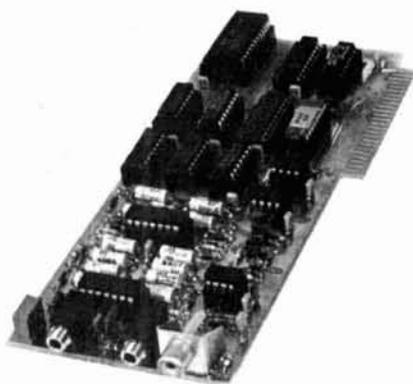PhotoCaster requires an Apple II or Apple II Plus computer with 48K RAM and one disk drive. The price of the PhotoCaster is \$499.95 for the basic system, including an assembled and tested circuit board and software. A com-



plete system, consisting of a Panasonic WV1400 camera, board and software, is available for \$749.95.

For more information, contact Commsoft, Inc., 665 Maybell Avenue, Palo Alto, California 94306. Reader Service Number 302.

## radio teletype and CW

With the Super-Ratt radio teletype and CW program for the Apple II, you can have your own Radio Bulletin Board System (RBBS) station on-line quickly and easily.

The program will operate in ASCII as well as Baudot at any speed from 40 to 300 baud. CW speeds range from 5 to 100 WPM, with an automatic speed adjust on receive.

The program may be run in either manual or RBBS modes. Extensive use of disk files permits storage of canned material for manual operation. In the RBBS mode, the system automatically saves nearly one hundred user messages to the disk. There are thirty-five different, simple English word commands on the RBBS.

Almost any modern terminal unit or converter can be used with Super-Ratt, as well as devices such as the RADCOM card by AF6W. The program is not protected against copying. The BASIC portion may be listed and modified to suit your tastes. (The registered owner's call is installed in the machine code by the factory.)

A free one-year subscription to the user newsletter, *The Ratt's Nest*, is included in the purchase price of \$54.95. For more information, contact Universal Software Systems, Inc., 9 Shields Lane, Ridgefield, Connecticut 06877. Reader Service Number 303.

## helical resonator amplifiers

Hamtronics, Inc., has developed a new line of low-noise receiver preamps with helical resonator filters built in. The HRA-144, HRA-220, and HRA-432 units cover the three major VHF and UHF ham bands. The combination of a low-noise amplifier and the sharp selectivity of a three or four section helical resonator increases receiver sensitivity and reduces cross-band interference. The unit has a low 0.6 to 0.95 dB noise figure and 50 to 60 dB rejection of any signals out of the ham band.

The amplifier circuit uses some of the new microwave transistors developed for satellite TV service. Nominal gain is 26 dB on 2 meters, 22 dB on 220 MHz, and 16 dB on 420-450 MHz. A three-section helical resonator is used in the output circuit of the VHF units, a four-section resonator is used in the UHF unit. The VHF unit is only 1 1/2 x 3 inches, and the UHF unit is only 2 1/2 x 3 inches.

The HRA-144 or HRA-220 costs \$49.95, and the HRA-432 is \$54.95.

For further information contact Hamtronics, Inc., 65 Moul Road, Hilton, New York 14468-9535. Reader Service Number 304.

## Ameco multimeters

Ameco Equipment Company announces preliminary specifications of its new line of Ameco multimeters. Multimeter Model M-300 (available immediately) features highly sensitive 20K ohms/Vdc and 10K ohms/Vac; gold-

plated switching contacts; overload protection by diodes and fuse; and carrying handle that can be used as adjustable stand.

Ranges for dc voltage: 0-0.25, 1, 2.5, 10, 25, 100, 250, 1000 V; ac voltage: 0-10, 25, 100, 250, 1000 V; dc current: 0-50, 500  $\mu$ A, 5, 50, 500 mA; resistance: 0-6K ohms, 60K ohms, 600K ohms, 6M ohms. Volume level: -22 dB to +22 dB to +62 dB in five ranges. Size and weight: 5.5 inches high  $\times$  4.3 inches wide  $\times$  1.6 inches deep.

Model M-300 is a high quality, highly sensitive, laboratory-type instrument. Its large, easy-to-read scale and excellent damping are usually found only in expensive meters. Parallax errors are eliminated by a mirror arc. This meter comes complete with battery, spare fuse, test leads, and instruction manual. Model M-300, completely wired and tested, \$28.95.

Ameco LCD digital multimeter, Model D-200, features high-contrast, large 1/2 inch, 3-1/2 digit LCD display; automatic polarity;



automatic zero adjustment; over-range indication on all ranges; low-battery indication; full overload protection; 10-megohm input impedance; rugged anti-slip case with stand.

Ranges for dc voltage: 0-200 mV, 2V, 20V, 200V, and 1,000V; ac voltage: 0-200V, and 750V; dc current: 0-200  $\mu$ A, 2 mA, 20 mA, 200 mA, and 10 A; resistance: 0-200 ohms, 2K ohms, 20K ohms, 200K ohms, 2000K ohms, and 20M ohms. Size and weight: 7 inches high  $\times$  2.7 inches wide  $\times$  1.6 inches deep.

The latest IC and display technology insure reliability, accuracy, and stability. Dual slope integration provides fast, accurate, noise-free measurements. The same two jacks are used for all functions and ranges (except 10A dc). Model D-200 comes complete with battery, spare fuse, test probes, instruction manual, and an optional carrying case. Model D-200, completely wired and tested, \$69.95; optional carrying case, \$3.75.

For further information, contact Ameco Equipment Company, 275 Hillside Avenue, Williston Park, Long Island, New York 11596. Reader Service Number 305.

### RT-1100 receive terminal

DGM Electronics has just introduced the RT-1100 Receive Terminal for Baudot, ASCII, and Morse. The RT-1100 converts the audio from your receiver, decodes it, and displays the words on a video monitor or TV set (using rf modulator). The RT-1100 incorporates an active filter demodulator with scope tuning outputs. It will copy 170, 425, 850 Hz shift RTTY signals at speeds of 60, 66, 75, and 100 WPM on Baudot and 110 baud on ASCII. The unit will copy 6-60 wpm Morse signals using automatic or manual speed tracking.

The RT-1100 has a parallel ASCII printer output for hard copy. The video output provides sixteen lines of thirty-two characters per line with two pages. The second page is stored in memory and can be recalled by using the page 1-2 switch on the front panel. The unit has a built-in 110 Vac power supply and is housed in an attractive 3  $\times$  10  $\times$  10-inch case with brushed, anodized front and rear panels. The cover is a grey wrinkle finish. The unit comes with a one-year warranty on parts and labor.

For more information, contact DGM Electronics, Inc., 787 Briar Lane, Beloit, Wisconsin 53511. Reader Service Number 306.

### encoder with ultra thin keyboard

Midian Electronics, Inc., has introduced the TTE-1 TouchTone™ encoder with ultra-thin keyboard. The unit features the thinnest available keyboard/DTMF encoder assembly with automatic PTT and side tone. The keyboard mounts virtually flush on a flat surface. DTMF encoder on the back of the keyboard fits into a 1  $\times$  1-1/2 inch hole for flush mounting. It produces digitally synthesized tones for accuracy and stability with adjustable audio output level and generates twelve standard Bell System TouchTones. Options include keyboard only, without encoder, and LED indicating when automatic PTT is activated.

For more information, contact Midian Electronics, Inc., 5907 East Pima Street, Tucson, Arizona 85712. Reader Service Number 307.

### interchangeable antennas

Antenna Incorporated has recently introduced a complete line of interchangeable antennas for use on hand held transceivers and scanners. The Portaswader antennas let the user replace only the radiator section of the antenna while continually reusing the mounting-adaptor fitting for the transceiver. The radiators are all internal threaded (No. 10-32) to accept the male thread of the interchangeable mounting adapter. The outer portion of the

# !NEW!

FROM  
**KENWOOD**



**TS430S**  
New Gen. Cov.  
Solid State Transceiver



**R2000**  
New Gen. Cov.  
Rcvr. W/memories



**TS930S**

THE  
COMM  
CENTER 20810  
INC.

Laurel Plaza  
Route 198  
Laurel, Md.  
MD.: 301-792-0600  
OPEN MON. THROUGH SAT.

**CALL TOLL FREE**  
**1-800-638-4486**

# PB RADIO

1950 E. Park Row Arlington, Texas 76010

★ SPECIALIZING IN: ★  
MDS Receivers & UHF Decoders

MDS COMPLETE COMMERCIAL UNIT.....\$169.95  
MDS SLOTTED ARRAY ANTENNA KIT.....\$25.00  
MDS DOWN CONVERTER KIT.....\$28.50  
MDS COMPLETE POWER SUPPLY.....\$35.00  
\*SPECIAL NE64535 TRANSISTORS.....\$6.50

UHF DECODERS: FV 3 INSTRUCTIONS.....\$5.00  
FV 3 BOARD \$30.00 FV 3 IC CHIP KIT \$50.00  
ZENITH 9-151-03 TUNER.....\$79.95  
BOX \$19.95 DELUXE BOX \$24.95  
POWER SUPPLY KIT.....\$24.95  
EDGE CONNECTORS.....\$2.95

SATELLITE T.V. SYSTEMS: PRODELIN DISHES, DEXCEL  
RECEIVERS, LNA'S & CHAPARRAL POLOROTORS. SEND \$1.00  
FOR MORE INFORMATION.

INFORMATION CALL 817-460-7071  
ORDERS ONLY CALL 800-433-5169



161



socket is etched with the frequency range for that particular radiator. Ten mounts are available to be used with the five different radiator styles.

The short 8-inch whips for 25-54 MHz incorporate a wire-wound base-loading coil and helical-style radiator in six different frequency steps. Tuning has been eliminated and fragile temperature-sensitive ferrite cores have also been eliminated. A distinct feature is the antenna length which is less than 8-inches long, measured from mount to tip. In the 118-174 MHz frequencies, Portasuaders are available in standard tuned helical units, extra-fat helical units and 1/4-wavelength stainless steel whips incorporating a spring section. The advantage of the fat Portasuader is its shorter length (about 2 inches shorter than helical). A secondary benefit in using the fat antenna is its lower Q, broadening the resonance curve and thus achieving a better match over the frequency range.

Also available is a 1/4-wavelength 0.046 inch diameter 17-7PH stainless steel whip incorporating a novel spring construction above the base fitting. This spring allows the whip assembly to bend when the user sits down with his radio attached to his belt. The 1/4-wavelength Portasuader was designed to replace the telescopic antennas, which bend or break or simply do not telescope properly. As a further advantage, the 1/4-wavelength Portasuader antennas exhibit a practical 10 dB gain over the helical or fat helical antennas.

The frequency range is covered in seven frequency steps, thus again removing the need for field tuning. UHF stubby helical whips and 1/4-wavelength speedometer cable antennas are available as radiators in five frequency ranges between 406-512 MHz. An 800 MHz 1/4-wavelength speedometer cable antenna is currently available.

These Portasuaders are constructed from heavy copper-plated spring steel that is screwed onto the base fitting and then soldered to ensure electrical contact. Both helical and speedometer styles are insulated by coating in a multi-stage process. The special process guarantees a solid section of material with minimum voids and high finish gloss. The coating is designed to remain flexible, retain its resilience at -40 degrees F and not to soften at 200 degrees F.

For further information, contact Randy Friedberg, Vice President, Antenna Incorporated, 26301 Richmond Road, Cleveland, Ohio 44146. Reader Service Number 308.

## Your Ham Tube Headquarters!

TOLL 800-221-0860 FREE TUBES

3-400Z	\$85.00	6883B	\$6.75
3-500Z	\$85.00	7360	\$9.15
4-400A	\$80.00	7735A	\$29.50
4CX250B	\$50.00	8122	\$98.00
572B	\$39.50	8156	\$10.95
811A	\$12.00	8844	\$29.50
813	\$35.00	8873	\$175.00
6146B	\$6.50	8874	\$180.00
6360	\$4.25	8877	\$450.00
		8908	\$10.50

E.F. JOHNSON Sockets for 4CX250B & 4-400A \$9.95

SEMICONDUCTORS		RF CONNECTORS	
MRF 245/SD1416	\$30.00	PL 259	10\$4.95
MRF 454	\$18.95	PL 258	10\$8.95
MRF 455	\$12.50	UG 175/176	10\$1.60
		UG 255/U	\$2.50 ea.
MRF 644/SD1088	\$19.95	UG 273/U	\$2.25 ea.
2N3055	\$ .95	M 358	\$2.50 ea.
2N6084	\$12.50	M 359	\$1.75 ea.
		Type "N" twist-on (RGBU)	\$4.75

TOP BRAND Popular Receiving Tube Types  
FACTORY BOXED 75/80% OFF LIST  
FREE LIST Available  
Includes full line of RF Power Transistors.  
Minimum Order \$25.  
Allow \$3.00 Minimum for UPS Charges  
Write or phone for free catalog.  
TUBES—BOUGHT, SOLD AND TRADED

**CeCo**  
Since 1922

Premium Prices  
Paid  
For EIMAC Tubes

COMMUNICATIONS, Inc.  
2115 Avenue X  
Brooklyn, NY 11235  
Phone (212) 646-6300

119

100 April 1983

If you need

# QUARTZ CRYSTALS

—one or hundreds—

## YOU NEED JAN

- high stability
- prompt service
- cost savings

- General Communication
- Industry
- Marine VHF
- Scanners
- Amateur Bands
- CB Standard
- CB Special
- Microprocessor

Call or Write  
**JAN CRYSTALS**

P.O. Box 06017  
Ft. Myers, FL 33906-6017  
All Phones (813) 936-2397

**JAN**  
CRYSTALS

VISA

MasterCard

143

## high resolution SSTV converter

High resolution slow scan television (SSTV) is available with the Videoscanner 1000 by Microcraft Corporation. The unit is completely compatible with Amateur-standard SSTV and first-generation equipment. Videoscanner can convey high-resolution eight-second, 128-line SSTV pictures to first generation scan converters using current standards. In two separate high resolution modes, the TV picture uses the full 256 TV lines and 256 picture elements (pixels) per line, resulting in pictures that rival commercial TV quality. The pixels are quantized to 64 levels of gray, four times better than first generation units. No contouring (false edges) is introduced to detract from the picture.


Some features of Videoscanner are: Split-mode, a special mode that enables viewing four regular 8.5-second SSTV pictures at one



time on the TV monitor as they are received; Stop motion, a single frame of video may be grabbed into memory from a TV camera manually or automatically, thus stopping motion; Cursor, a cursor dot appears on the screen to indicate the current line being transmitted; Gray scale, Call Sign, mode selector activates a gray scale and optional call sign which are superimposed on the picture in memory; Station switching, all necessary switching between transmitter, microphone, and tape recorder is included in Videoscanner.

Microcraft is presently working on a computer input/output port and a color conversion of the Videoscanner 1000.

# PERFORMANCE VERSATILITY CONVENIENCE

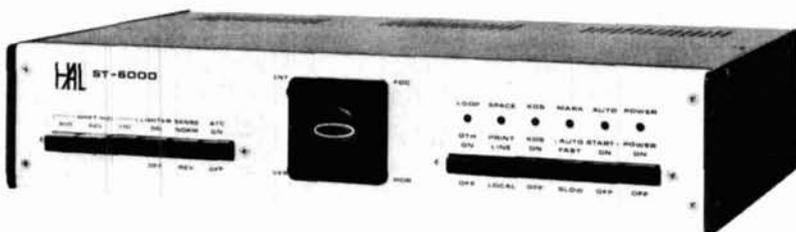

The HAL ST6000 has them all:

- performance to copy the weak and distorted signal
- versatility to match a variety of I/O interfaces
- convenience for simple but accurate operator use

All this at half the price of comparable-performance units.

### PERFORMANCE:

- Optimized active input, discriminator, and low-pass filters.
- Crystal tone keyers match discriminator filters.
- Hard-limiting FM or AM types of operation.

### VERSATILITY:

- Interface current loop circuits; built-in loop supply.
- RS-232C and MIL-188 data I/O connections.
- CMOS pre- and post-autostart data I/O data connections.
- Available for low, high, marine-compatible, and special tones.

### CONVENIENCE:

- Hard-limiting operation for simple but effective operation.
- Tuning oscilloscope for precise receiver tuning.
- ATC, DTH, KOS, autostart, and antispace features.
- Operate 120/220 VAC, 50/60 Hz; table or rack mount.
- Solid state design with proven field-tested dependability.

Write or call for more information on the HAL ST6000.



**HAL COMMUNICATIONS CORP.**

BOX 365  
URBANA, ILLINOIS 61801 217-367-7373

135

## DIRECTION FINDING?

- ★ Doppler Direction Finding
- ★ No Receiver Mods
- ★ Mobile or Fixed
- ★ Kits or Assembled Units
- ★ 135-165 MHz Standard Range



- ★ Circular LED Display
- ★ Optional Digital Display
- ★ Optional Serial Interface
- ★ 12 VDC Operation
- ★ 90 Day Warranty

**New Technology** (patent pending) converts any VHF FM receiver into an advanced Doppler Direction Finder. Simply plug into receiver's antenna and external speaker jacks. Use any four omnidirectional antennas. Low noise, high sensitivity for weak signal detection. Kits from \$270. Assembled units and antennas also available. Call or write for full details and prices.

**DOPPLER SYSTEMS,** 5540 E. Charter Oak, (602) 998-1151  
Scottsdale, AZ 85254

125

## How come you're not on 30 meters? There's no excuse with KLM's New 30M-2 and 30M-3 Antennas!

Two new antennas from KLM using their low loss linearly loaded elements. Small physical size with full size performance. Exclusive "Maxi-Match" for direct 50Ω coaxial feed.

30M-2 (2 element Yagi)		30M-3 (3 element Yagi)	
Gain	4.5 dBd	Gain	7 dBd
F/B	12 dB	F/B	20 dB
SWR	less than 1.5-1 across band	SWR	less than 1.5-1 across band
Boom Length	12'	Boom Length	24'
Max. Elem. Length	34'	Max. Elem. Length	34'
Wind Load	4 sq. ft.	Wind Load	7 sq. ft.

Available now. Stop by your local dealer for more information.  
Maximize your performance today with a 10 MHz KLM Beam Antenna!

**KLM** PO Box 816 • Morgan Hill, CA 95037 • (408) 779-7363



The Videocan 1000 is available as a complete kit for \$595.00 or wired and tested for \$795.00 plus \$6.00 for shipping.

For more information, contact Microcraft Corporation, P.O. Box 513, Thiensville, Wisconsin 53092. Reader Service Number 309.

### improved 225-400 MHz scanner converter

The CVR-1B Scanverter includes a built-in preamplifier for increased sensitivity. It allows complete coverage of the 225-400 MHz military/federal government aircraft band when used with a standard aircraft band scanner. "Bandstacking" allows the entire 175-MHz-wide UHF aircraft band to be compressed into the 118-136 MHz range tunable on any scanner capable of standard aircraft reception. No tuning or adjustments are necessary with the fully automatic converter.

Reception for hundreds of miles is possible when an outside antenna is used. Additional features include high sensitivity, low noise microstripline circuit; all-metal cabinet for superior shielding; double-balanced mixer to reduce images; nine-pole filter to suppress out-of-band interference; crystal oscillator to provide high stability; and Zener diode voltage regulation to limit drift. The scanner is powered by convenient 12 Vdc.



The Scanverter, CVR-1B, costs \$89.00 plus \$2.00 for shipping. Contact Grove Enterprises, 140 Dog Branch Road, Brasstown, North Carolina 28902. Reader Service Number 310.

146

### FREE! CABLE LOSS CHART IN WINTER CATALOG NEMAL ELECTRONICS COAXIAL CABLE SALE POLYETHYLENE DIELECTRIC

RG213 noncontaminating 96% shield mil spec	36'/ft
RG214/U double silver shield 50 ohm	\$1.48/ft
RG142/U double silver shield 50 ohm Teflon	95'/ft
RG11U 96% shield 75 ohm mil spec	25'/ft
★ RG-8/U 96% shield Mil Spec	(\$27.95/100) or 31'/ft
RG62A/U 96% shield mil spec 93 ohm	12'/ft
RG-55B/U double shield (RG-58 size) 50 ohm	50'/ft
★ RG58U mil spec 96% shield	(\$9.95/100) or 11'/ft

#### LOW LOSS FOAM DIELECTRIC

RG-8X (Mini 8) 95% shield	(\$14.95/100) or 17'/ft
★ RG8U 80% shield	(\$15.95/100) or 19'/ft
RG-8/U 97% shield 11 gauge (equiv. Bellden 8214)	31'/ft
RG58U 80% shield	07'/ft
RG58U 95% shield	10'/ft
RG59/U 100% foil shield TV type	(\$7.00/100) or 10'/ft
HEAVY DUTY rotor cable 2-16 ga 6-18 ga	36'/ft
Rotor cable 2-18 ga 6-22 ga	19'/ft

#### CONNECTORS MADE IN USA

Amphenol PL 259	79¢
PL-259 push-on adapter shell	10/\$3.89
PL-259 and/or SO-239	10/\$5.89
Double Male Connector	\$1.79
PL-258 Double Female Connector	98¢
1 ft. patch cord w/RCA type plugs each end	3/\$1.00
Reducer UG-175 or 176	10/\$1.99
UG-255 (PL-259 to BNC)	\$3.50
Elbow (M359) UHF Elbow	\$1.79
F59A (TV type)	10/\$1.99
UG 21 D/U Type N Male for RG8, Amphenol	\$3.00
UG-88C/U BNC Male for RG-58, Amphenol	\$1.25
UG 273 BNC-PL259 Amphenol	\$3.00
3/16 inch Mike Plug for Collins etc. (cutoff)	\$1.25

Call or write for Free Catalog

#### shipping

Cable — \$3.00 1st 100 ft., \$2.50 each add'l 100 ft.  
Connectors — add 10%, \$3.00 minimum.  
Orders under \$20 add \$2 additional plus shipping.  
COD add \$1.50. Florida Residents add 5%.

### NEMAL ELECTRONICS

Dept. H, 1327 N.E. 119 St., N. Miami, FL 33161  
Telephone: (305) 893-3924

158



PAT # 4,259,705

#### WARNING!

Electric Power  
Pollution,  
Spikes,  
Interference  
& Lightning  
HAZARDOUS to  
HIGH TECH EQUIPMENT!!



MicroComputers, VTR, Hi-Fi, Lasers, Spectrometers are often damaged or disrupted due to Power Pollution.

High Tech components may interact!

Our patented ISOLATORS eliminate equipment interaction, curb damaging Power Line Spikes, Tame Lightning bursts & clean up interference.

Isolated 3-prong sockets; integral Spike/Lightning Suppressor. 125 V, 15 A, 1875 W Total, 1 KW per socket.

ISO-1 ISOLATOR. 3 Isolated Sockets; Quality Spike Suppression; Basic Protection ..... \$76.95

ISO-3 SUPER-ISOLATOR. 3 DUAL Isolated Sockets; Suppressor; Commercial Protection ..... \$115.95

ISO-17MAGNUM ISOLATOR. 4 QUAD Isolated Skts; Suppressor; Laboratory Grade Protection ... \$200.95

Master-Charge, Visa, American Express

TOLL FREE ORDER DESK 1-800-225-4876  
(except AK, HI, MA, PR & Canada)

**SATISFACTION GUARANTEED!**

**Electronic Specialists, Inc.**

171 South Main Street, Natick, MA 01760

Technical & Non-800: 1-617-655-1532

126

## the Z-Dubber

The Sinclair ZX81/Timex 1000 is a popular personal computer. One drawback is the difficulty experienced in loading cassette programs. Bytesize Computer Products has introduced the Z-Dubber, an interface between the Sinclair computer and its cassette recorder, which helps even the most difficult cassette program to load easily. Additionally, the Z-

Dubber allows you to connect two cassette recorders together to create perfect back-up copies of your Sinclair programs. The Z-Dubber operates on two AAA cells, and is packaged in an attractive black case. It is available for \$29.95 plus 3 percent for shipping.

For more information, contact Bytesize Computer Products, P.O. Box 21123, Seattle, Washington 98111. Reader Service Number 311.



## Amateur data display, DTU-12

Get a clean, crisp computer-quality data display for your next ham project with a DTU-12 from Dotronix, Inc., available in kit, chassis, or chassis/ac power versions, either P4 (white) or P31 (green) phosphor. It requires only 12 volts at 1.5 amperes, and standard TTL horizontal and vertical control signals with 2.5 volts video drive. The scan rate is 15,750 Hz. Interface is made through ten-pin edge-card connector.

The kit costs \$85.00 (CRT/circuit only); chassis \$95.00; ac supply \$35.00 (for chassis version).

For additional information, contact Dotronix, Inc., 160 First Street S.E., New Brighton, Minnesota 55112. Reader Service Number 312.

## programmable CTCSS encoder

A miniature encoder has been introduced by Ferritronics, Inc., featuring quartz-accurate

stability and all thirty-seven EIA tones. Two variations are available: the FT303A, which is programmed by cutting wire loops; and the FT303B, which uses a dipswitch for programming. The encoder measures 0.9 x 1 x 0.4 inch and draws less than 7 mA. Mounting holes and color-coded lead set make installation simple.



For further information, contact Tom Whitney at Ferritronics, Inc., 222 Newkirk Road, Richmond Hill, Ontario L4C 3G7, Canada. Reader Service Number 313.

## two-meter mobile transceiver

The TR-7950 and TR-7930 are identical in features except for rf output: 45 watts for the TR-7950, and 25 watts for the TR-7930. Their

# Appliance & Equipment Company Inc.

## ATTENTION RADIO DEALERS

Send for our free catalog on commercial, industrial, marine, Amateur and CB products

(512) 734-7793  
733-0334

2317 Vance Jackson  
San Antonio, TX 78213

✓ 110

## Amateur Radio Today

Mini-Magazine offering timely material on a professional basis for all active Radio Amateurs. A.R.T. is six full-size pages, produced bi-weekly on high quality stock using magazine production techniques. Money back guarantee for your \$26/yr. subscription or a quarterly trial (six issues) for \$5. Check what we've covered recently:

✓ 10.1 MHz opens for Amateurs ✓ How low should your transmitted wave angle be? ✓ CQWW phone and cw contests ✓ Sweepstakes ✓ Cordless telephones ✓ FCC ideas on 1500 watts output ✓ Manufacturer responses to 10.1 MHz equip. mods. ✓ Six-meter openings ✓ How to calculate your system noise figure ✓ Worldwide network of 20-meter beacons ✓ 900 MHz ssb ✓ 160-meter DXing ✓ Big antennas at K2GL ✓ Antenna heading calculations ✓ Review of Yaesu FT-102, ICOM-740, and others ✓ How Packet Radio works ✓ Meteor scatter ✓ The Satellite Program ✓ Interview with Madison Electronics ✓ and much, much more!

Amateur Radio Today ✓ 107  
Post Office Box 6243H, Wolcott, CT 06716

## NEW NEW NEW COMPUTER SAVER

Do you have 8 or more interface cards you use occasionally but hate to keep tearing into your computer to get at them and risk damaging them?

Then **Switch-A-Slot** is for you!

**Switch-A-Slot** lets you select up to 4 cards for each port. Select the card to run with the turn of a switch. NO new programming tricks to learn.

### Switch-A-Slot

**SAVES** wear and tear on cards and computer power (only the card that's on draws power)

**PROTECTS** cards from being damaged by static electricity and scratches

Switch-A-Slot works with most cards:  
disk drives printers  
modems clock cards, etc.

Models available for

Apple II Apple IIe Franklin

**INTRODUCTORY PRICE \$155**  
(includes shipping)

Please send orders with payment to:

**BIT "O" BYTE**

PO Box 60972, Sunnyvale, CA 94088

✓ 115

# WARNING

## SAVE YOUR LIFE OR AN INJURY

Base plates, flat roof mounts, hinged bases, hinged sections, etc., are not intended to support the weight of a single man. Accidents have occurred because individuals assume situations are safe when they are not.


Installation and dismantling of towers is dangerous and temporary guys of sufficient strength and size should be used at all times when individuals are climbing towers during all types of installations or dismantlings. Temporary guys should be used on the first 10' or tower during erection or dismantling. Dismantling can even be more dangerous since the condition of the tower, guys, anchors, and/or roof in many cases is unknown.

The dismantling of some towers should be done with the use of a crane in order to minimize the possibility of member, guy wire, anchor, or base failures. **Used towers in many cases are not as inexpensive as you may think if you are injured or killed.**

Get professional, experienced help and read your Rohn catalog or other tower manufacturers' catalogs before erecting or dismantling any tower. A consultation with your local, professional tower erector would be very inexpensive insurance.

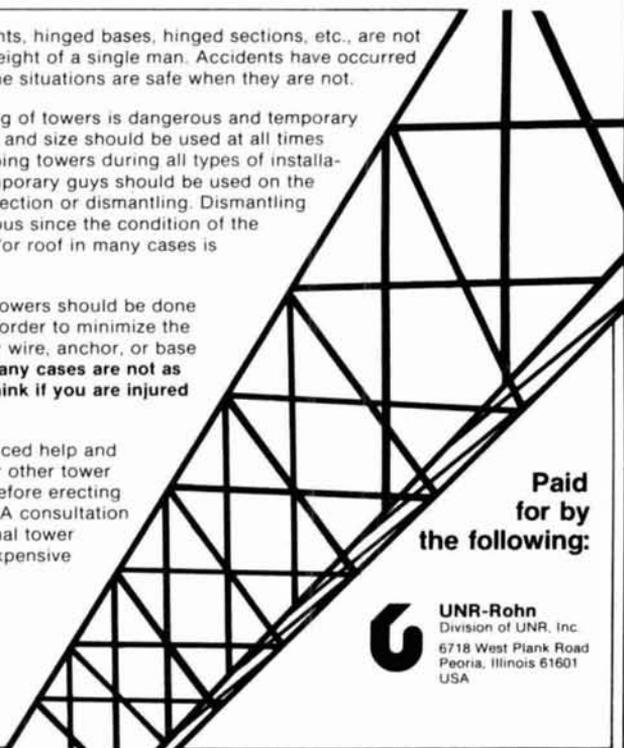**Paid for by the following:**

**UNR-Rohn**  
Division of UNR, Inc.  
6718 West Plank Road  
Peoria, Illinois 61601  
USA



### RE Porta-Tenna 5/8

**TELESCOPIC VHF & UHF 5/8 WAVE FOR HTs**

**High Quality Maximum Performance**

Gain (ref. 1/4 wave helical) ..... 6dB min.  
Bandwidth VHF (1.5:1 VSWR) ... 3.5MHz min.  
Bandwidth UHF (1.5:1 VSWR) ... 10MHz min.  
Maximum power ..... 5 watts  
Connector type ..... BNC

#### LENGTH W/BNC CONNECTOR

Band	Extended	Collapsed
3.4M	44 1/2" (1124mm)	8 1/2" (207mm)
1 1/2M	32 1/8" (815mm)	7 1/4" (197mm)
3.4M	17 3/16" (435mm)	6 5/16" (160mm)

Model No.	Band	Freq. MHz
191-214	2M	144-148
191-814	1 1/2M	220-225
191-914	3/4M	440-450

Models also available for  
148-174 and 450-512 MHz

PRICE - \$19.95 ppd. to 48 states via UPS  
For air delivery add \$1.50  
Florida residents add \$1.00 sales tax  
Payment by M.O. or cashiers ck. only

Dealer Inquiries Invited

**RF PRODUCTS**

P.O. Box 33, Rockledge, FL 32955  
(305) 631-0775



### R-4C+SHERWOOD CRYSTAL FILTERS

**STILL THE FINEST COMBINATION**  
600 HZ LOW-LOSS 1st-IF CW FILTER. Improve early-stage selectivity. Eliminate high pitched leakage around 2nd-IF filters. Improve ultimate rejection to 140 dB. Eliminate strong signals overloading 2nd mixer, causing intermod and desensitization. CF-600/6: \$80.00. New PC board relay switch kit: \$45.00.

1st-IF SSB FILTERS. 140 dB ult. rej. CF-2K/8: \$150.00 pair.  
5kHz 1st-IF FILTER. Reduces hi-pitched QRM. CF-5K/8: \$80.00  
16-POLE R-4C SSB! Plug-in filter. Best skirt selectivity. 1800 Hz, 6 dB; 2400 Hz, 60 dB. CF-2K/16 (Also 1.6K/16): \$135.00.  
250, 500 and 1000 Hz 8-POLE 2nd-IF PLUG-IN FILTERS. CF-250/8, CF-500/8 and CF-1.0K/8: \$80.00.

PC Board mod. and switching kits. Special AM filters/detector. Filters also for R-4 (B), R-7, TR-7, TR-4, Signal/One, Atlas. Add \$3 shipping per order; \$6 overseas air.  
Europeans: Ingompeck, Postfach 24 49, D-8070, Ingolstadt, W. Germany.

**Sherwood Engineering Inc.**

1268 South Ogden St.  
Denver, Colo. 80210  
(303) 722-2257



169

### FACSIMILE

**COPY SATELLITE PHOTOS, WEATHER MAPS, PRESS!**

The Faxes Are Clear — on our full size (18-1/2" wide) recorders. Free Fax Guide.

### TELETYPE

**RTTY MACHINES, PARTS, SUPPLIES**

ATLANTIC SURPLUS SALES (212) 372-0349  
3730 NAUTILUS AVE BROOKLYN N.Y. 11274

THE BEST PLACE TO BUY, SELL or TRADE NEW and USED EQUIPMENT  
**NUTS & VOLTS MAGAZINE**  
BOX 1111-H • PLACENTIA, CA 92670  
(714) 632-7721

Join Thousands of Readers Nationwide Every Month

ONE YEAR U.S. SUBSCRIPTIONS

\$7.00 - 3rd Class • \$12.50 - 1st Class

525.00 - Lifetime - 3rd Class

### NUTS & VOLTS

HAM GEAR  
COMPUTERS  
SOFTWARE  
SCANNERS • OPTICS  
TEST EQUIPMENT  
MICROWAVE  
SATELLITE  
AUDIO VISUAL  
NEW PRODUCTS  
COMPONENTS • KITS  
ANTIQUE ELECT.  
PUBLICATIONS  
PLANS • SERVICES



notable features include 21 multi-function memories, automatic offset, programmable priority channel, memory and band scan, long-life lithium battery memory back-up, built-in 16-key autopatch.

The TR-7950 has a factory-suggested retail price of \$399.95; the suggested retail price for the TR-7930 is \$359.95.



Additional information may be obtained by contacting Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220. Reader Service Number 314.

### 3 1/2 -digit true rms DDM

John Fluke Mfg. Co., Inc., announces the addition of a 3 1/2-digit true rms meter to its 8020B-series of handheld DMMS, called the 8026B. It's an eight-function handheld model featuring true rms ac capabilities while retaining all of the functions of the 8020B.

For further information, contact Frank Parin, John Fluke Mfg. Co., P.O. Box C9090, Everett, Washington 98206. Reader Service Number 315.



160

## Computer Program Books for Beginners

Everything you need to know to get started programming your own computer. These handy books of programs, each jam-packed with easy-to-understand info for beginners, are crammed with hundreds of tips, tricks, secrets, hints, shortcuts, techniques, plus hundreds of tested ready-to-run programs. For the TRS-80 Color Computer. For the TRS-80 Pocket Computer and Sharp PC-1211, PC-1500 pocket computers.

### Color Computer

**101 Color Computer Programming Tips & Tricks**, learn-by-doing instructions, hints, secrets, shortcuts, techniques, insights, for TRS-80 Color Computer, 128 pages **\$7.95**

**55 Color Computer Programs for Home, School & Office**, practical ready-to-run software with colorful graphics for TRS-80 Color Computer, 128 pages **\$9.95**

**55 MORE Color Computer Programs for Home, School & Office**, sourcebook of useful type-in-and-run software with exciting graphics, for TRS-80 Color Computer, 112 pages **\$9.95**

### Pocket Computer

**Pocket Computer Programming Made Easy**, new fast 'n easy way to learn BASIC, make your computer work for you, for TRS-80, Sharp, Casio pocket computers, 128 pages **\$8.95**

**101 Pocket Computer Programming Tips & Tricks**, secrets, hints, shortcuts, techniques from a master programmer, 128 pages **\$7.95**

**50 Programs in BASIC for Home, School & Office**, sourcebook of tested ready-to type-in-and-run software for TRS-80 and Sharp pocket computers, 96 pages **\$9.95**

**50 MORE Programs in BASIC for Home, School & Office**, ideal source for lots more useful software for TRS-80 and Sharp pocket computers, 96 pages **\$9.95**

QTY.	Title	Price	Total

Allow 2-4 weeks for delivery.

SHIPPING **\$2.00**

TOTAL

#### FROM:

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Check or Money Order Enclosed

VISA  MasterCard

Acct. # \_\_\_\_\_

Expires \_\_\_\_\_ MC Bank # \_\_\_\_\_

**SEND TO: HAM RADIO'S BOOKSTORE  
GREENVILLE, NH 03048**

✓ 188

NEW

The only **INTELLIGENT**  
TOUCH-TONE\* CONTROL BOARD



• Repeaters  
• Remote receiver sites  
• Remote bases  
• Home control  
• Security

THE  
**ITC-32**

for only ...  
**\$389**

Microcomputer based power and flexibility with state-of-the-art Mitel tone decoding.

- 28 remotely commandable outputs
- 4 remotely sensed inputs
- Control and monitor over the air or over the telephone\*\*
- Morse code or tone encoded response messages
- Alarm generation
- PLUS Repeater COR/ID/Timer function!

acc

advanced computer controls


Call or write for detailed specs on the ITC-32 Intelligent Touch-Tone Control Board.

10816 Northridge Square, Cupertino, CA 95014

(408) 749-8330

\* Touch-Tone is a registered trademark of AT&T  
\*\* Optional Telephone Interface Board available  
Price and specifications subject to change without notice or obligation.

✓ 101

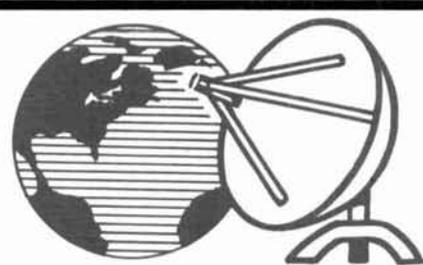

## SATELLITE TELEVISION SYSTEMS

WE WILL NOT BE UNDERSOLD!!

Complete Systems, Antennas, Receivers, LNA's & Accessories

CALL US TODAY!

812-238-1456

# hoosier electronics

"Nation's Largest Total Communications Distributor"  
P.O. BOX 3300 • TERRE HAUTE, INDIANA 47803

✓ 138



Ham Radio's guide to help you find your local dealer

### California

**C & A ELECTRONIC ENTERPRISES**  
22010 S. WILMINGTON AVE.  
SUITE 105  
CARSON, CA 90745  
213-834-5868  
Not The Biggest, But The Best —  
Since 1962.

**FONTANA ELECTRONICS**  
8628 SIERRA AVENUE  
FONTANA, CA 92335  
714-822-7710  
714-822-7725  
The Largest Electronics Dealer in San  
Bernardino County.

**JUN'S ELECTRONICS**  
3919 SEPULVEDA BLVD.  
CULVER CITY, CA 90230  
213-390-8003 Trades  
714-463-1886 San Diego  
800-882-1343  
— Parts at Cost — Full Service.  
Habla Espanol

**SHAVER RADIO, INC.**  
1378 S. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-1103  
Azden, Icom, Kenwood, Tempo,  
Ten-Tec, Yaesu and many more.

### Connecticut

**HATRY ELECTRONICS**  
500 LEDYARD ST. (SOUTH)  
HARTFORD, CT 06114  
203-527-1881  
Call today. Friendly one-stop shop-  
ping at prices you can afford.

### Delaware

**DELAWARE AMATEUR SUPPLY**  
71 MEADOW ROAD  
NEW CASTLE, DE 19720  
302-328-7728  
800-441-7008  
Icom, Ten-Tec, DenTron, Yaesu,  
Azden, Santec, KDK, and more.  
One mile off I-95, no sales tax.

### Florida

**AMATEUR ELECTRONIC SUPPLY**  
1898 DREW STREET  
CLEARWATER, FL 33515  
813-461-HAMS  
Clearwater Branch  
West Coast's only full service  
Amateur Radio Store.

**AMATEUR ELECTRONIC SUPPLY**  
621 COMMONWEALTH AVE.  
ORLANDO, FL 32803  
305-894-3238  
Fla. Wats: 1 (800) 432-9424  
Outside Fla: 1 (800) 327-1917

**AMATEUR RADIO CENTER, INC.**  
2805 N.E. 2ND AVENUE  
MIAMI, FL 33137  
305-573-8383  
The place for great dependable  
names in Ham Radio.

**RAY'S AMATEUR RADIO**  
1590 US HIGHWAY 19 SO.  
CLEARWATER, FL 33516  
813-535-1416  
Your complete Amateur Radio and  
Computer Store.

### Illinois

**ERICKSON COMMUNICATIONS, INC.**  
5456 N. MILWAUKEE AVE.  
CHICAGO, IL 60630  
Chicago — 312-631-5181  
Outside Illinois — 800-621-5802  
Hours: 9:30-5:30 Mon, Tu, Wed & Fri;  
9:30-8:00 Thurs; 9:00-3:00 Sat.

### Indiana

**THE HAM SHACK**  
808 NORTH MAIN STREET  
EVANSVILLE, IN 47710  
812-422-0231  
Discount prices on Ten-Tec, Cubic,  
Hy-Gain, MFJ, Azden, Kantronics,  
Santec and others.

### Kansas

**ASSOCIATED RADIO**  
8012 CONSER, P. O. BOX 4327  
OVERLAND PARK, KS 66204  
913-381-5900  
America's No. 1 Real Amateur Radio  
Store. Trade — Sell — Buy.

### Maryland

**THE COMM CENTER, INC.**  
LAUREL PLAZA, RT. 198  
LAUREL, MD 20810  
800-638-4486  
Kenwood, Drake, Icom, Ten-Tec,  
Tempo, DenTron, Swan & Apple  
Computers.

### Massachusetts

**TEL-COM, INC.**  
675 GREAT ROAD, RTE. 119  
LITTLETON, MA 01460  
617-486-3040  
617-486-3400 (this is new)  
The Ham Store of New England  
You Can Rely On.

### Minnesota

**MIDWEST AMATEUR RADIO SUPPLY**  
3452 FREMONT AVE. NO.  
MINNEAPOLIS, MN 55412  
612-521-4662  
It's service after the sale that counts.

### Nevada

**AMATEUR ELECTRONIC SUPPLY**  
1072 N. RANCHO DRIVE  
LAS VEGAS, NV 89106  
702-647-3114  
Dale Porray "Squeak," AD7K  
Outside Nev: 1 (800) 634-6227

**JUN'S ELECTRONICS**  
460 E. PLUMB LANE — 107  
RENO, NV 89502  
702-827-5732  
Outside Nev: 1 (800) 648-3962  
Icom — Yaesu Dealer

### New Hampshire

**TUFTS ELECTRONICS**  
61 LOWELL ROAD  
HUDSON, NH 03051  
603-883-5005  
New England's friendliest ham store.

### New Jersey

**RADIOS UNLIMITED**  
P. O. BOX 347  
1760 EASTON AVENUE  
SOMERSET, NJ 08873  
201-469-4599  
800-526-0903  
New Jersey's only factory authorized  
Yaesu and Icom distributor. New and  
used equipment. Full service shop.

**ROUTE ELECTRONICS 46**  
225 ROUTE 46 WEST  
TOTOWA, NJ 07512  
201-256-8555

**ROUTE ELECTRONICS 17**  
777 ROUTE 17 SOUTH  
PARAMUS, NJ 07625  
201-444-8717  
Drake, Cubic, DenTron, Hy-Gain,  
Cushcraft, Hustler, Larsen, MFJ,  
Butternut, Fluke & Beckman  
Instruments, etc.

**Dealers:** YOU SHOULD BE HERE TOO!  
Contact Ham Radio now for complete details.

## Amateur Radio Dealer

### New York

**BARRY ELECTRONICS**  
512 BROADWAY  
NEW YORK, NY 10012  
212-925-7000  
New York City's Largest Full Service  
Ham and Commercial Radio Store.

#### GRAND CENTRAL RADIO

124 EAST 44 STREET  
NEW YORK, NY 10017  
212-599-2630  
Drake, Kenwood, Yaesu,  
Ten-Tec, DenTron, Hy-Gain,  
Mosley in stock.

#### HARRISON RADIO CORP.

20 SMITH STREET  
FARMINGDALE, NY 11735  
516-293-7990  
"Ham Headquarters USA" since  
1925. Call toll free 800-645-9187.

#### RADIO WORLD

ONEIDA COUNTY AIRPORT  
TERMINAL BLDG.  
ORISKANY, NY 13424  
TOLL FREE 1 (800) 448-9338  
NY Res. 1 (315) 337-0203  
Authorized Dealer — ALL major  
Amateur Brands.  
We service *everything* we sell!  
Warren K2IXN or Bob WA2MSH.

### Ohio

**AMATEUR ELECTRONIC SUPPLY**  
28940 EUCLID AVE.  
WICKLIFFE, OH (CLEVELAND AREA)  
44092  
216-585-7388  
Ohio Wats: 1 (800) 362-0290  
Outside Ohio: 1 (800) 321-3594

**UNIVERSAL AMATEUR RADIO, INC.**  
1280 AIDA DRIVE  
REYNOLDSBURG (COLUMBUS), OH  
43068

614-866-4267  
Featuring Kenwood and all other  
Ham gear. Authorized sales and ser-  
vice. Shortwave headquarters. Near  
I-270 and airport.

### Oklahoma

**DERRICK ELECTRONICS, INC.**  
714 W. KENOSHA — P.O. BOX A  
BROKEN ARROW, OK 74012  
Your *Discount* Ham equipment dealer  
in Broken Arrow, Oklahoma  
1-800-331-3688 or  
1-918-251-9923

### Pennsylvania

**HAMTRONICS,**  
DIV. OF TREVOSSE ELECTRONICS  
4033 BROWNSVILLE ROAD  
TREVOSSE, PA 19047  
215-357-1400  
Same Location for 30 Years.

#### LaRUE ELECTRONICS

1112 GRANDVIEW STREET  
SCRANTON, PENNSYLVANIA 18509  
717-343-2124  
Icom, Bird, Cushcraft, Beckman,  
Fluke, Larsen, Hustler, Astron,  
Antenna Specialists, W2AU/W2VS,  
AEA, B&W, CDE, Sony, Vibroplex.

#### THE VHF SHOP

BOX 349 RD 4  
MOUNTAINTOP, PA 18707  
717-868-6565  
Lunar, Microwave Modules, ARCOS,  
Astron, KLM, Tama, Tonna-F9FT,  
UHF Units/Parabolic, Santec, Tokyo  
Hy-Power, Dentron, Mirage,  
Amphenol, Belden

### Texas

**MADISON ELECTRONICS SUPPLY**  
1508 MCKINNEY  
HOUSTON, TX 77010  
713-658-0268  
Christmas?? Now?? See ad index  
page.

### Virginia

**ELECTRONIC EQUIPMENT BANK**  
516 MILL STREET, N.E.  
VIENNA, VA 22180  
703-938-3350  
Metropolitan D.C.'s One Stop  
Amateur Store. Largest Warehousing  
of Surplus Electronics.

### Wisconsin

**AMATEUR ELECTRONIC SUPPLY**  
4828 W. FOND DU LAC AVE.  
MILWAUKEE, WI 53216  
414-442-4200  
Wisc. Wats: 1 (800) 242-5195  
Outside Wisc: 1 (800) 558-0411

### QUALITY MICROWAVE TV SYSTEMS

#### 2.1 to 2.6 GHz Antennas 34 db Gain (or Greater)

Complete System as pictured \$99.95  
Down Converter Probe  
(Mounted, Assembled & Tested) \$34.95  
Power Supply (12V to 16V)  
Assembled & Tested \$24.95  
Data Information (Plans) \$9.95



**Phillips-Tech  
Electronics**  
P.O. Box 33205  
Phoenix, AZ 85067  
(602) 274-2885

C.O.D.'s  
Special Quantity  
Pricing



2 YEAR WARRANTY  
PARTS & LABOR

163

### INCREDIBLE CODE!!

Learn the International Morse Code  
by the patented  
"WORD METHOD"

**NO** BOOKS  
CARDS  
VISUAL AIDS  
GIMMICKS

Just listen and learn! The "WORD METHOD"  
is based on the latest scientific and psycho-  
logical techniques. You can zoom past 13  
WPM in less than HALF THE USUAL TIME!!

The kit contains two cassette tapes, over TWO  
HOURS of unique instruction by internationally  
famed educator Russ Farnsworth. Complete  
satisfaction guaranteed.

Available at local Electronic Dealers, or send  
check or money order for \$14.95 plus \$1.50  
for postage and handling to:

#### EPSILON RECORDS

5002 W. McFadden - #73  
Santa Ana, Ca. 92704

129

### NEW

#### BASIC PROGRAM MANUAL FOR AMATEURS

Programs Design: Antennas, Op-amps, Smith-  
charts, R.F. Coils, Pads, Filters, Striplines,  
Microwave and more.

All For \$9.95 (INCLUDES SHIPPING  
AND HANDLING)

#### ATTENTION YAESU FT-207R OWNERS AUTOMATIC

##### SCAN MODULE

15 minutes to install; scan re-  
starts when carrier drops off;  
busy switch controls auto-  
matic scan on-off; includes  
module and instructions.

Model AS-1 \$25.00



##### NEW BATTERY SAVER KIT

Model BS-1 \$14.95

- No more dead batteries due to memory backup
- 30% less power drain when squelched
- Simple to install, step-by-step instructions and parts included
- 4 mA memory backup reduced to 500  $\mu$ A
- 45 mA receiver drain reduced to 30 mA
- Improved audio fidelity and loudness

128

#### ENGINEERING CONSULTING


P.O. BOX 216 DEPT. H  
BREA, CALIFORNIA 92621

# Nampa Satellite SYSTEMS

IDAHO'S LARGEST DEALER

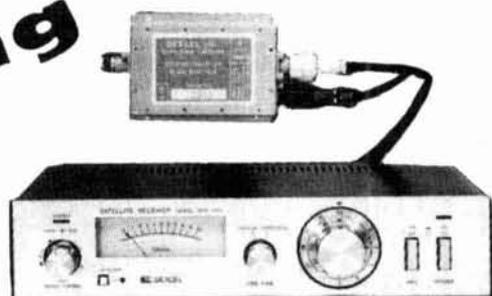
## DEXCEL Receiving Package \$2350<sup>00</sup>

DXR 1100 Stereo Receiver, LNC and remote control 10' Prodelin fiberglass dish with Polarmount • Polatron II Electronic Polarizer and Cables With Motor Drive \$2550<sup>00</sup>


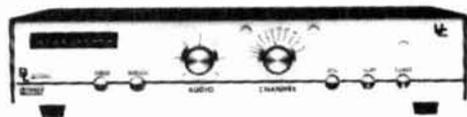
## Universal Communications Package \$1999<sup>00</sup>

Universal Communications DL-2000 • 10' Prodelin fiberglass dish with Polarmount • Polatron II Electronic Polarizer, Dexcel 100° LNA and 100' Cables With Motor Drive \$2199<sup>00</sup>



### THE VHF PROPAGATION HANDBOOK by Jim Stewart, WA4MVI

Theory and practical application in VHF. Chapters on Scatter - Tropo - EME. Available through THE LUNAR LETTER MAGAZINE.  
\$3.95 + \$1.50 postage.

### THE LUNAR LETTER Magazine

Up to the minute news of VHF/UHF Propagation. EME - Tropo - Scatter.

1 year . . . \$12.00

312 12th Ave. So. • Nampa, ID 83651



### DRAKE ESR 24



### Package

Includes ESR-24 - 100° Dexcel LNA - 10' Prodelin Dish. Polarmount, Polatron II Polarizer, and all Cables. \$2250<sup>00</sup> With Motor Drive \$2450

### Motor Drives from . . . \$300<sup>00</sup>

"All systems are complete,  
nothing else to buy".

Electronics shipped UPS prepaid - Dish and Polarmount freight collect.

"HAMS SERVING HAMS"

24 Hour Phone Line for orders 7 days a week

# (208) 466-6727

312 12th Ave. So. • Nampa, ID 83651

# ANTENNAS FOR HF, VHF, UHF

## Two Meter

**"The Big John"\*** 13 Element Quad 22' Boom 16.5dBd gain F/B 30 dB Mast Size Up to 2" Bandwidth 144-145 MHz \$129.95

**"The Little John"\*\*\*** 11 Element Quad 18' Boom 15.5 dBd gain F/B 30db Mast Size 2" Bandwidth 144-145 MHz \$109.95


**"PTG Special"\*\*\*** 9 Element Quad 13' Boom 14.8 DBd F/B 30 dB Bandwidth 144-146 MHz \$89.95

Featuring The Wondermatch Driven Element


## Six Meter

**"6-PTG-4"** 4 Element Yagi 13' Boom 12 dBd Mast Size 2" Longest Element 115" 50-51 MHz \$89.95

You've Heard About Us On The Air, So Call Collect Between 8AM-10PM Or Write For Details

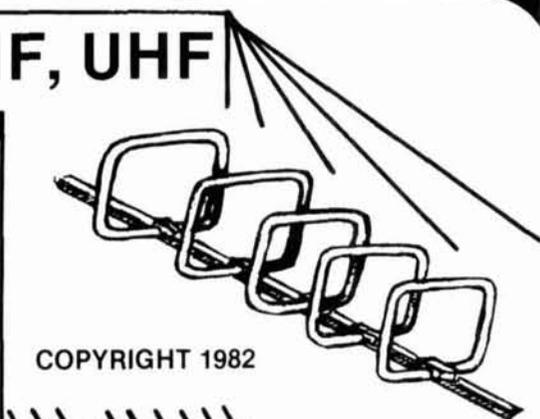

COPYRIGHT 1982

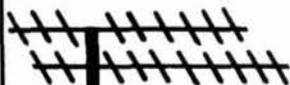

(713) 464-7720 Dick-WB5JWL  
Gordy-KD5NQ

**JWL ELECTRONICS**  
9138 Western Drive  
Houston, TX 77080

\*Measured at JWL Laboratories

\*\*First Place Winner at Baton Rouge Gain Measuring Contest (7/31/82).

\*\*\*Second Place Winner at Baton Rouge Gain Measuring Contest (7/31/82).

142

## ORR BOOKS

### BEAM ANTENNA HANDBOOK

by Bill Orr, W6SAI

Recommended reading. Commonly asked questions like: What is the best element spacing? Can different yagi antennas be stacked without losing performance? Do monoband beams outperform tribanders? Lots of construction projects, diagrams, and photos. 198 pages. ©1977. 1st edition.

□ RP-BA Softbound \$5.95

### SIMPLE LOW-COST WIRE ANTENNAS

by Bill Orr, W6SAI

Learn how to build simple, economical wire antennas. Apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. Well diagramed. 192 pages. ©1972.

□ RP-WA Softbound \$6.95

### THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart Cowan, W2LX

Contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and new information on the popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. **The Radio Amateur Antenna Handbook** will make a valuable and often consulted reference. 190 pages. ©1978.

□ RP-AH Softbound \$6.95

### ALL ABOUT CUBICAL QUAD ANTENNAS

by Bill Orr, W6SAI

The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. You'll find quad designs for everything from the single element to the multi-element monster quad, plus a new, higher gain expanded quad (X-Q) design. There's a wealth of supplementary data on construction, feeding, tuning, and mounting quad antennas. 112 pages. ©1977.

□ RP-CQ Softbound \$5.95

Please add \$1.00 to cover shipping and handling.

**HAM RADIO'S BOOKSTORE**  
GREENVILLE, NH 03048

## PROGRAMMABLE CTCSS ENCODER



\$26<sup>95</sup>

- All 37 EIA Tones
- Quartz Accurate
- Less than 1 inch square

AVAILABLE FOR IMMEDIATE DELIVERY  
For more information call TOLL-FREE

(800) 828-6884

NY: (800) 462-7242

CANADA: (416) 884-3180



**FERRITRONICS**  
MOBILE DATA SYSTEMS

1319 PINE AVE.  
NIAGARA FALLS NY 14301  
(716) 282-7470 TLX 64-6303

130

SEE YOU AT  
DAYTON!  
Booth #71



## BITTEN BY THE ATV BUG?

Let P.C. put you on the air  
and SAVE!

**Complete System price**  
**\$249.00 SAVE \$13.00**

**TXA5-4 Exciter/Modulator** ..... \$89.00 ppd.  
Wired and tested module designed to drive PA5 10 watt linear amplifier. The 100 MHz crystal design keeps harmonics out of two meters for talk back. Video modulator is a full 8 MHz for computer graphics and color. Requires 13.8 VDC reg @ 70 ma. 80 mw output power. Tuned with crystal on 439.25 - 434 or 426.25 MHz. Dual frequency model available ..... \$115.00 ppd.

**PA5 10 Watt ATV Power Amplifier** ..... \$89.00 ppd.  
The PA5 will put out 10 watts RMS power on sync tips when driven with 80 mw by the TXA5 exciter. 50 ohms in and out plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 VDC reg @ 3 amps.

**FMA5 Audio Subcarrier Generator** ..... \$29.00 ppd.  
Puts audio on your camera video just as broadcast does at 4.5 MHz. Puts out 1 V p-p to drive TXA5. Requires low Z mike. 150 to 600  $\Omega$  and 12 to 18 VDC @ 25 ma. Works with any transmitter with 5 MHz video bandwidth.

**TVC-2 ATV Downconverter** ..... \$55.00  
Stripline MRF 901 preamp and double balanced mixer digs out the weak ones and resists intermod and overload. Connects between UHF antenna and TV set. Output channels 2 or 3. Varicap tuner 470 to 450 MHz. Requires 12 to 18 VDC @ 20 ma.  
**Supersensitive TVC 2L with NE64535 preamp**  
(.9 db N.F.) ..... \$69.00 ppd.

Call or write for our complete catalog of specifications, station setup diagrams, and optional accessories which include: antennas, modulators, test generators, cameras and much, much more. See Ch. 14 1983 ARRL Handbook.

TERMS: VISA or MASTERCARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Allow three weeks after order for delivery.  
(213) 447-4565 Charge card orders only

**P.C. ELECTRONICS** 2522 Paxson Lane,  
Tom W6ORG Maryann WB6YSS Arcadia, California 91006

## new HYBRID PHONE PATCH



### NEW DESIGN

### Model P101

- VU meter for line level and null readings
- Separate receiver, transmitter, & null controls
- Either PTT or Vox operation
- Pi-filters to eliminate RF feedback
- Simple phone line hook up
- Attractive blue panel, woodgrain cabinet
- Dimensions 8" wide x 5 3/4" deep x 2 1/4" high

**PRICE \$95.00** Plus \$2.50 Shipping  
and Handling

ALL OUR PRODUCTS MADE IN USA



**BARKER & WILLIAMSON**  
Quality Communication Products Since 1932

At your Distributors, write or call  
10 Canal Street, Bristol, Pa. 19007  
**(215) 788-5581**



112

- ★ Technical Forums
- ★ ARRL and FCC Forums
- ★ GIANT 2-day Flea Market  
Saturday and Sunday
- ★ New Products and Exhibits
- ★ Grand Banquet
- ★ Women's Activities
- ★ Home-Brew Equipment  
Forum
- ★ Special Group Meetings
- ★ YL Forum
- ★ Personal Computers Forum
- ★ CW Proficiency Awards
- ★ Amateur of Year Award
- ★ Special Achievement  
Awards

DAYTON

# Hamvention®

APRIL 29, 30, MAY 1, 1983

Hara Arena and Exhibition Center — Dayton, Ohio

Meet your amateur radio friends from all over the world at the internationally famous Dayton HAMVENTION.

Seating will be limited for Grand Banquet and Entertainment on Saturday evening so please make reservations early. Banquet speaker is Bill Leonard, W2SKE, former president of CBS News.

If you have registered within the last 3 years you will receive a brochure in late February. If not write Box 44, Dayton, OH 45401.

Nominations are requested for Radio Amateur of the Year and Special Achievement Awards. Nomination forms are available from Awards Chairman, Box 44, Dayton, OH 45401.

For special motel rates and reservations write to Hamvention Housing, 1406 Third National Bldg., Dayton, OH 45402.  
**NO RESERVATIONS WILL BE ACCEPTED BY TELEPHONE.**

All other inquiries write Box 44, Dayton, OH 45401 or phone (513) 849-1720.

Admission: \$7.00 in advance, \$9.00 at door. (Valid for all 3 days)

Banquet: \$14 in advance, \$16 at door.

Flea Market Space: \$15 in advance. (Valid for both days)

Make checks payable to Dayton HAMVENTION, Box 2205, Dayton, OH 45401.

Bring your family and enjoy a great weekend in Dayton.

Sponsored by the Dayton Amateur Radio Association, Inc.

# flea market



**RATES** Noncommercial ads 10¢ per word; commercial ads 60¢ per word **both payable in advance.** No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

## QSL CARDS

**QSLs & RUBBER STAMPS** — Top Quality! Card Samples and Stamp Info — 50¢ — Ebbert Graphics 5R, Box 70, Westerville, Ohio 43081.

**TRAVEL-PAK QSL KIT** — Converts post cards, photos to QSLs. Stamp brings circular. Samco, Box 203-c, Wynantskill, New York 12198.

**QSL SAMPLES:** 25¢. Samcards, 48 Monte Carlo Drive, Pittsburgh, PA 15239.

**DISTINCTIVE QSL's** — Largest selection, lowest prices, top quality photo and completely customized cards. Make your QSL's truly unique at the same cost as a standard card, and get a better return rate! Free samples, catalogue. Stamps appreciated. Stu K2RPZ Print, P.O. Box 412, Rocky Point, NY 11778 (516) 744-6260.

**QSL ECONOMY:** 1000 for \$13. SASE for samples. W4TG, Box F, Gray, GA 31032.

**QSL'S: NO STOCK DESIGNS!** Your art or ours; photos, originals, 50¢ for samples & details (refundable). Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412.

**QSL CARDS:** 500/\$12.50 ppd. Free catalog. Bowman Printing, 743 Harvard, St. Louis, MO 63130.

## Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria  
F. Baettl  
Hauptplatz 5  
A-2700 Wiener Neustadt  
Austria

Ham Radio Belgium  
Stereohouse  
Brusselsesteenweg 416  
B-9218 Gent  
Belgium

Ham Radio Canada  
Box 400, Goderich  
Ontario, Canada N7A 4C7

Ham Radio Europe  
Box 444  
S-194 04 Upplands Vastby  
Sweden

Ham Radio France  
SM Electronic  
20 bis, Ave des Clarions  
F-89000 Auxerre  
France

Ham Radio Germany  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Holland  
Postbus 413  
NL-7800 Ar Emmen  
Holland

Ham Radio Italy  
Via Pordenone 17  
I-20132 Milano  
Italy

Ham Radio Switzerland  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio UK  
P.O. Box 63, Harrow  
Middlesex HA3 6HS  
England

Holland Radio  
143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

**SELL:** Icom 701 w/PS \$550.00; Icom 211 \$250.00; Bearcat scanner 250 \$150.00. All mint condition. Prices firm. KB4XU, (803) 766-2831.

**CHASSIS** and cabinet kits. SASE K3IWK.

**YAESU FT-ONE** General coverage transceiver with every option including FM, Curtis keyer and scanning microphone. List \$3700. Tax sale \$2250. Yaesu FL2100Z, 80-10 meter linear \$350. Dentron MT2000A 3KW Ant/Tuner \$200. N6ABE (415) 881-5429 any time.

**KT5B** Multi-Band Antenna 160-80m (WARC) \$59.95, instruction manual \$3.00, 2 KW + center connector \$8.50. Kilo-Tec, PO Box 1001, Oak View, Cal. 93022. Tel (805) 646-9645.

**FOR SALE:** Atlas 210X. Best offer gets it. Works good. Jerry Bayless, 316 S. Delmar, Decatur, IL (217) 428-8218.

**VIDEOSCAN 1000** Slow Scan TV — High resolution (Amateur, phone line, surveillance, teleconferencing). Code\*Star — decode Morse, RTTY, ASCII. Large LEDs or connect computer/printer. Morse-A-Keyer — CW keyboard. Tri-voltage power supply. Kits/assembled. Free brochures. Microcraft Corporation, Box 513-HR, Thiensville, WI 53092. (414) 241-8144.

**ELECTRON TUBES:** Receiving, transmitting, microwave — all types available. Large stock. Next day delivery most cases. Daily Electronics, 14126 Willow Lane, Westminster, CA 92683. (714) 894-1368.

**BUY SELL TRADE** — Next 6 issues \$2.00. WA4OSR's Rigs & Stuff, Box 973-H, Mobile, AL 36601.

**COLLINS 75S3-B** w/500 Hz CW filter, 32S3 Xmtr, 516-F2 power supply. Good condition, round emblem. N3CCW, Larry Caracciolo, 1515 Lakeview Drive, Germansville, PA 18053.

**PRE-1946 TELEVISION SETS** wanted for substantial cash. Finder's fee paid for leads. Also interested in spinning disc, mirror in-the-lid, early color sets, 9AP4 picture tubes. Arnold Chase, 9 Rushleigh Road, West Hartford, Conn. 06117 (203) 521-5280.

**WANTED:** Old bugs for my key collection. Need Vibroplex, Martin, Bunnell, McElroy, Electro, etc. Also need Spark keys, military, homebrew, and keys of historical significance. K5RS, Neal McEwen, 1128 Midway, Richardson, TX 75081.

**WANTED:** Highest prices paid for Harris RF 301 and associated equipment. Call collect (212) 925-6048.

**BUMPER STICKER** — "My favorite radio station is (your call sign here)." Display anywhere! \$3.00. Arpress, 380(H) Wilbanks, Rome, GA 30161.

**RTTY AND ASCII** for Atari. Plans and a drilled PC board to build your own modem. ASCII and RTTY programs on disk all for \$25. Robert Holsti, K7ZJ/DKH2, Box 4426, AAFB Br. Yigo Guam 96912 (USA).

**WANTED:** Polaroid schematics or copying privileges LPU-1, LKU-1, LDU-1, LTU-1,2,3. Maintenance manuals, if available. 9108 New Delaware Rd., Mt. Vernon, Ohio 43050. W8PEN (614) 392-0841.

**TUBES, TUBES** wanted for cash or trade. 304TL, 4CX1000A, 4PR60C, WE300, 7F7, 7N7, 53, 6L6M. Any high power or special purpose tubes of Eimac/Varian. DCO, 10 Schuyler Avenue, No. Arlington, NJ 07032. (800) 526-1270.

**WANTED:** National HRO-50, HRO-60, w/kg. condx. W8PEN, 9108 New Delaware Rd., Mt. Vernon, Ohio 43050. (614) 392-0841.

**SATELLITE TELEVISION INFORMATION.** Build or buy your own earth station. \$4.00 to Satellite Television, RD #3, Oxford, NY 13830. Parabolic antenna construction book also available. Send SASE for details.

**WILL SELL** to highest reasonable offer. Weston Model 537 AC and DC Radio test set. With original book and test leads. Have QST from January 1968 through December 1972. Otto Cordray, 801 N. Temple St., Caldwell, Texas 77836.

**MARCONI WIRELESS TELEGRAPH CO.** Stock Certificates. Authentic 1914 certificates, from the pioneering days of radio, are rare antiques and valuable investments. Suitable for framing. Only \$38.95 including historical pamphlet. Satisfaction Guaranteed. Free information: Tarlen, Box 7554-M, N. Kansas City, MO 64116.

**MOBILE IGNITION SHIELDING.** Estes Engineering, 930 Marine Dr., Port Angeles, WA 98362.

**RTTY-EXCLUSIVELY** for the Amateur Teleprinter. One year \$7.00. Beginners RTTY Handbook \$8.00 includes journal index. PO Box RY, Cardiff, CA 92007.

**MX330** Motorola factory touch tone pad with mother board and daughter board, all interconnecting wiring. Nothing to cut or glue. Complete \$100.00. N6GFE, 980 Wildcat Canyon Road, Berkeley, CA 94708. (415) 843-5253.

## Ducks are getting smaller! and...



## better!



Actual Size

Because you and the leading radio manufacturers want the best-performing, the best looking antenna; Centurion has grown to be the Duck leader. We've developed many smaller antennas to make the hand-held radio perform better, and now the newest duck... the Tuf Duck "mini". It's shorter (about 3") yet it's a full 1/4 wave radiator on VHF.

## CENTURION TUF DUCK ANTENNAS

**CENTURION**  
Phone 402/467-4491  
Telex 48-4377 CENTURION LCN  
P.O. Box 82846 Lincoln, NE 68501 2846

\*\*\*\*\*  
**QUALITY MICROWAVE TV SYSTEMS**  
 \*\*\*\*\*  
**Complete Systems From \$69<sup>95</sup>**  
**1.9 to 2.5 GHz Antennas**  
**Galaxy Electronics**  
**6007 N. 61st Ave.**  
**Glendale, Az. 85301**  
**(602) 247-1151**  
**COD's Dealers Wanted**  
  
  
 \*\*\*\*\*  
 ✓ 132



**MANUALS** for most ham gear made 1937/1970. Send \$1.00 for 18 page "Manual List", postpaid. HI-MANUALS, Box R802, Council Bluffs, Iowa 51502.

**SATELLITE TELEVISION** — Howard/Coleman boards to build your own receiver. For more information write: Robert Coleman, Rt. 3, Box 58-AHR, Travelers Rest, SC 29690.

**WANTED:** Schematics-Rider, Sams or other early publications. Scaramella, P.O. Box 1, Woonsocket, RI 02895-0001.

**WANTED:** Early Hallicrafter "Skyriders" and "Super Skyriders" with silver panels, also "Skyrider Commercial", early transmitters such as HT-1, HT-2, HT-8, and other Hallicrafter gear, parts, accessories, manuals. Chuck Dachis, WD5EOG, The Hallicrafter Collector, 4500 Russell Drive, Austin, Texas 78745.

**RUBBER STAMPS:** 3 lines \$3.25 PPD. Send check or MO to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

**WANTED:** New or used MS and coaxial connectors, synchros, tubes, components, military surplus equipment. Bill Williams, PO #7057, Norfolk, VA 23509.

**VERY in-ter-est-ing!** Next 5 issues \$2. Ham Trader "Yellow Sheets", POB356, Wheaton, IL 60189.

**CB TO 10 METER PROFESSIONALS:** Your rig or buy ours — AM/FM/SSB/CW. Certified Communications, 4138 So. Ferris, Fremont, Michigan 49412; (616) 924-4561.

**CB TO TEN METER CONVERSION KITS**

KITS for AM—SSB—FM 40 Channel PLL chassis conversions  
**DETAILED INSTRUCTIONS** for easy installation with minimum time and equipment  
**BAND COVERAGE** flexibility provides up to 1 MHz coverage for most PLL chassis.  
**PRICES** Low cost prices range from \$8.00 to \$50.00

All kits are in stock including several different FM kits.  
**FREE CATALOG** Write or call today.

**INDEPENDENT CRYSTAL SUPPLY COMPANY**  
 P.O. Box 183  
 Sandwich, Ma. 02563-0183  
 (617) 888-4302 ✓ 140

**FCC LOWERS REQUIREMENTS — GET YOUR RADIO TELEPHONE LICENSE**

FCC changes make obtaining a High-level Radio Telephone License much easier now. Eliminate unnecessary study with our short-cuts and easy to follow study material. Obtaining the General Radio Telephone License can be a snap! Sample exams, also section covering Radar Endorsement.

A small investment for a high-paying career in electronics.

**\$19.95 ppd.**  
 Satisfaction Guaranteed

**SPI-RO DISTRIBUTING**  
 P.O. Box 1538  
 Hendersonville, N. C. 28793

✓ 177

**HAMS FOR CHRIST** — Reach other Hams with a Gospel Tract sure to please. Clyde Stanfield, WA6HEG, 1570 N. Albright, Upland, CA 91786.

**"WEST COAST 160 METER BULLETIN"** devoted to, for and by top band operators. Edited and published 6 times a year by N7CKD. Subscriptions \$7.00 U.S. and U.S. Possessions. Canada and Mexico \$7.00 U.S. Overseas rate \$8.50 U.S. dollars. To 4248 "A" St. S.E., Box 609, Auburn, WA 98002.

**WANTED:** Diagram for TPL VHF-FM 120W, 2 meter Amp. — 1002-S. It uses TRW-PT8780 which I have been unable to find. Any help would be appreciated. WA0QFO.

**WANTED:** Micor and Mstr II Base Stations 406-420 and 450-470 MHz. Also 2 and 6 GHz solid state microwave equipment. AK7B, 4 Ajax Place, Berkeley, CA 94708.

**FOR SALE:** Ten-Tec Argonaut 515, mint, \$280.00; Kenwood TR-7800, exc., \$235.00; Icom R-70 receiver, mint, \$630.00; R-392, exc., extras, \$145.00; add. UPS. Ham mags: SASE for list, details. WA7ZYQ. (208) 245-2070.

**PLANS, CIRCUIT BOARDS, AND KIT PARTS** (author approved) for Leach's construction projects. Power amps, preamps, pre-preamps and loudspeakers. Send SASE for information. Custom Components, Box 33193, Decatur, GA 30033.

**DXPREDICTOR:** Computes MUF, FOT, LUF between any two QTHs. Documented; Easy to Use; Nice Graphical/Tabular output. Adapted from Algorithms currently used by USG agencies. Available for: Apple II + IIe (48kmin) plus DOS 3.3 or cassette); PET/CBM (16kmin, 8050 disk or cassette); VIC20 (16k RAM Card, cassette); CBM 64 (cassette only). Program + Documentation; \$40.00 all except VIC20 (\$30.00). Documentation only: \$5.00 (refundable upon purchase of software). Checks to K.J. Flynn, PO Box 903, Mountain View, CA 94042. (CA residents add 6.5% tax).

**SLEP SPECIALS,** HP608F late model signal generator, 10 MHz thru 455 MHz, 19" panel with blue/gray cabinet, excellent for precision laboratory work \$375.00, URM-25 signal generator 10 kHz thru 50 MHz \$285.00, URM-26 signal generator 4 MHz thru 405 MHz \$245.00, USM-140 oscilloscope DC-25 MHz, dual trace, triggered sweep \$295.00, GRM-46 test set for ARC-27, ARC-55, \$40.00, Tektronix 3S76 dual trace plug-in \$75.00, Tektronix 1L30 spectrum analyzer plug-in 925 MHz thru 10.5 GHz \$495.00, military SG-66/ARM-5 aircraft VOR signal generator equivalent to ARC H-14, perfect for aircraft radio repair \$295.00. Add shipping. We accept M/C, Visa or check. Phone 704-524-7519, Slep Electronics Company, Highway 441, Otto, N. C. 28763.

**Coming Events ACTIVITIES "Places to go..."**

**CALIFORNIA:** The 34th annual International DX Convention, a joint effort of the Northern California and Southern California DX Clubs, Friday, Saturday and Sunday, April 22, 23 and 24, at the Visalia Holiday Inn Hotel, Visalia. DXpedition reports, technical presentations, awards, contests, dining and hospitality rooms, slides, movies

**THE CHAMP**



**BIRD MODEL 4304**

**NO ELEMENTS 25-1000 MHZ RF SAMPLING PORT**

AUTHORIZED BIRD DISTRIBUTOR

**Webster**

**WEBSTER COMMUNICATIONS INC.**  
 115 BELLARMINE  
 ROCHESTER, MI 48063  
 313-375-0420

**CALL TOLL FREE**  
**800-521-2333**  
**800-482-3610**

✓ 185



**July 30 thru August 12, 1983**

*Our 24th year*

Learn why the answers are what they are. Upgrade with electronics professionals.

**OAK HILL ACADEMY RADIO SESSION**  
 in the  
**Blue Ridge Mountains of Virginia**  
 Theory and code together.

- Novice to General
- General or Technician to Advanced
- Advanced to Amateur Extra

Expert Instructors — Friendly Surroundings — Excellent Accommodations.  
 Ham Lab set up for all to use.

**"A Vacation with a Purpose"**

C. L. PETERS, K4DNJ, Director  
 Oak Hill Academy Amateur Radio Session  
 Box 43  
 Mouth of Wilson, VA 24363

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

**A GREAT GIFT IDEA**

**PERSONALIZED  
AMATEUR RADIO  
WINDOW DECALS**

AMATEUR RADIO  
UR CALL

**Beautiful — Durable**

These personalized decals will adhere to the inside of windows —

cars home  
shack boat  
office anywhere

**\$5.50 - 1 \$9.50 - 2 \$12.50 - 3**  
Mich. Res. add 4% Sales Tax

Send check or money order with Ham Call, name and address to:

**DEL CRAFT CO.**  
PO Box 148, Westland, MI 48185  
Clubs and organizations please write or call  
313-425-0009  
for special pricing

✓ 124

**VOICE OF AMERICA**

HAS OPPORTUNITIES IN WASH. D.C. FOR  
QUALIFIED RADIO BROADCAST TECHNICIANS

These positions require technical experience in professional radio, or the audio portion of television broadcasting.

Applicants must qualify in **two** of the following areas:

- Studio Control
- Tape Recording
- Field Operations
- Broadcast Equipment Maintenance

Starting salary: \$11.93 per hour

U.S. Citizenship Required

Submit Standard Federal Application Form SF-171 or resume to:

VOICE OF AMERICA  
Rm. 1341, 330 Independence Ave., S.W.  
Washington, D.C. 20547  
Attention: RBT-83-1

Equal Opportunity Employer

**ATV**

sample issue only \$2.50 PPD

FSTV — NBTV — MSTV — STTV  
FAX — 432 SSB/EME — SATELLITES  
MICROWAVE — COMPUTERS  
PACKET — DIGITAL TECHNIQUES  
12 ISSUES PER YEAR

**AMATEUR TELEVISION  
MAGAZINE™**

"OUR 16TH YEAR — SINCE 1967"

	Surface U.S./Canada	Surface All Mexico	Airmail All Foreign	Airmail Central S. America	Airmail All Other Foreign
1/2 year	\$ 10.00	\$ 13.00	\$ 20.00	\$ 23.00	\$ 23.00
1 year	\$ 20.00	\$ 26.00	\$ 40.00	\$ 46.00	\$ 46.00
2 year	\$ 38.00	\$ 50.00	\$ 78.00	\$ 90.00	\$ 90.00
3 year	\$ 56.00	\$ 74.00	\$ 116.00	\$ 134.00	\$ 134.00

"FOR THE SPECIALIZED COMMUNICATION RADIO AMATEUR"

QCD Publications  
c/o Mike Stone WBOGCD  
P.O. Box H  
Lowden, Iowa 52255-0408

Master Charge

✓ 111

and videotapes, open forums. Many overseas visitors expected. Manufacturers and distributors showing the latest in radio gear. For further information: Northern California DX Club, PO Box 608, Menlo Park, CA 94025.

**COLORADO:** The Grand Mesa Repeater Society's fourth annual Western Slope Swapfest, Saturday, April 2, 10 AM to 4 PM, Plumbers and Steamfitters Union Hall, 2384 Highway 6 and 50, Grand Junction. Free admission. Swap tables \$5.00 each. Auction and refreshments. Talk in on 146.22/82. For information SASE to Bill Brown, K0UK, 582 So. Maple St., Fruita, CO 81521 or call (303) 858-9661.

**GEORGIA:** Kennehoochee Hamfest, Sunday, April 17, 8 AM to 4 PM, Civic Center, Marietta, GA.

**ILLINOIS:** The 17th annual Rock River ARC Hamfest, Sunday, April 10, Lee County 4-H Center, one mile east of jct. 52 and 30, south of Dixon. Doors open 6:30 for dealers; 7:30 general public. 6 ft. tables available \$5.00. Advance ticket donation \$2, at gate \$2.50. Food. Camping available at nominal charge. Talk in on 37/97 repeater. For information and advance tickets: Ed Webb, WD9CJB, 618 Orchard St., Dixon, IL 61021. (815) 284-3811.

**LOUISIANA:** The Baton Rouge Amateur Radio Club's annual Hamfest, Saturday, May 7 and Sunday, May 8, Catholic High School, 855 Hearthstone Drive, Baton Rouge. Swap tables, dealers, tech forums and activities for non-hams and children. Talk in on 19/79 and 52 simplex. For further information: BRARC, PO Box 4004, Baton Rouge, LA 70821.

**MASSACHUSETTS:** The Framingham Amateur Radio Association's 8th annual Spring Flea Market, Sunday, April 10; the largest indoor Ham Flea Market in New England, Framingham Civic League Building, 214 Concord St. (Route 126) in downtown Framingham. Doors open at 10 AM, sellers setup starting at 8:30. Admission \$2. Tables \$10 (pre-registration required). Talk in on 75/15 and 52 direct. Radio equipment, computer gear, bargains galore. For information, tables: Ron Egalka, K1YHM, 3 Driscoll Drive, Framingham, MA 01701.

**MASSACHUSETTS:** The Wellesley Amateur Radio Society's annual auction, Saturday, April 16, First Congregational Church of Wellesley Hills, 207 Washington Street, Wellesley Hills, intersection of Routes 9 and 16. Doors open 9 AM; auction starts 10 AM. (15% commission, \$1.00 minimum, \$30.00 maximum). Talk in on 04:64; 63:03; and 52. Contact: Kevin P. Kelly, WA1YHV, 7 Lawnwood Place, Charlestown, MA 02129.

**MICHIGAN:** S.E.M.A.R.A., The Southeastern Michigan Amateur Radio Association's 25th annual Hamfest Swap and Shop, April 10, 8 AM to 3 PM, Grosse Pointe North High School, Vernier Road between Mack and Lake-shore. Admission \$1.00 advance; \$2.00 at door. Good food, free parking. Talk in on 147.75/15. For information: SEMARA Swap, PO Box 646, St. Clair Shores, MI 48083 or phone Ray Ninness, WD8KXN (313) 777-0119.

**MINNESOTA:** The Arrowhead Radio Amateur Club's annual swapfest, Saturday, May 7, 10 AM to 3 PM, Holiday Inn, 207 West Superior St., downtown Duluth. Admission \$2.50 advance, \$3.00 door. Reserved 4 ft. tables \$3.50 advance, \$4.00 at door. Food, free parking, enclosed shopping mall. Talk in on 34/94. For information, reservations SASE to Jerry Frederick, N0BNG, 1127 - 104th Avenue West, Duluth, MN 55808.

**NEBRASKA:** The 1983 Midwest ARRL Convention, April 15, 16 and 17, Marina Inn, South Sioux City. Seminars, displays, exhibits and large flea market all indoors. Fine entertainment during Saturday night banquet. QCWA breakfast, 3900 Club luncheon and an outstanding ladies' program Saturday. Convention costs \$6.00 for 3 days. Saturday night banquet \$10.00 advance; \$12.00 at door. To reserve flea market table contact Al Smith, W0PEX, 3529 Douglas St., Sioux City, IA 51104. Exhibitors contact Jim Boise, KA0GZY, 22 LaSalle St., Sioux City, IA 51104. For general information contact Dick Pinner, W0FZO, General Chairman, 2931 Pierce St., Sioux City, IA 51104. For advance banquet tickets and motel reservations contact Jerry Smith, W0DUN, Akron, IA 51001.

**NEW ENGLAND:** The Hosstraders will hold their tenth annual Tailgate Swapfest, Saturday, May 7, sunrise to sunset, at Deerfield, NH, Fairgrounds. Admission \$1.00, including tailgaters and commercial. Friday night camping for self-contained rigs at nominal fee. None admitted before 4 PM Friday. Profits benefit Boston Burns Unit of Shriners' Hospital. Last year's donation \$262.75. Questions or map to northeast's biggest ham flea market? SASE to Norm, WA1IVB, RFD Box 57, West Baldwin, ME 04091 or Joe, K1RQG, Star Route, Box 56, Bucksport, ME 04416 or Bob, W1GWU, North Walton Road, Seabrook, NH.

**NEW JERSEY:** The 8th Trenton Computer Festival, Saturday and Sunday, April 16 and 17, 10 AM to 5 PM, Trenton State College, Trenton. Exhibits, electronics flea market, technical sessions, free short courses on Sunday. Admission \$5. (\$3 students). For further information: TCF-83, Trenton State College, Hillwood Lakes CN550, Trenton, NJ 08625. (609) 771-2487.

**BUTTERNUT  
ELECTRONICS  
COMPANY**

**THE WINNERS**

Model HF6V: Completely automatic bandswitching 80 through 10 plus 30 meters. Outperforms all 4- and 5-band "trap" verticals of comparable size. Thousands in use worldwide since December 8'11 160 meter option available now. retrofit kits for remaining WARC bands coming soon. Height: 26 ft/7.8 meters, guying not required in most installations.

Model 2MVC "Trombone": omnidirectional collinear gain vertical for 2 meters having the same gain as "double-YA" types, but the patented "trombone" phasing section allows the radiator to remain unbroken by insulators for maximum strength in high winds. No coils "plumber's delight" construction and adjustable gamma match for complete D.C. grounding and lowest possible SWR. Height: 9.8 ft/2.98 meters.

Model 2MVC-5 "Super-Trombone": Same advanced features as the basic 2MVC but a full wavelength taller with additional "Trombone" phasing section for additional gain. Height: 15.75 ft/4.8 meters.

All BUTTERNUT ANTENNAS use stainless steel hardware and are guaranteed for a full year. For further information on these and other BUTTERNUT products, write for our FREE CATALOG!

**BUTTERNUT  
ELECTRONICS**  
GARY AIRPORT, BOX 356 E RTE 2  
SAN MARCOS, TEXAS 78666

### Check These Prices On Factory Prime Parts

\* AUTHORIZED MAIL ORDER DISTRIBUTORS  
\* MOTOROLA MRO DISTRIBUTOR

\* DON'T SEE IT?? GIVE US A CALL!!

<b>POPULAR MICROWAVE DEVICES</b>			
MRF 901	\$2.15	MRF 911	\$2.15
2N6603		NEC 02135	
replaces MRF 902) \$9.75 high gain/low noise			
MFD 101	\$ .45		\$3.50

<b>LINEAR IC'S</b>			
MC 1330A1P	\$1.75	MC 1350P	\$1.20
MC 1349P	\$1.40	MC 1358P	\$1.70
MC-1374P	\$2.40	MC 1496P	\$1.00
NE 565	\$1.30	MC 1458CP1	\$.70
NE 564	\$3.95	MC 4558CP1	\$.85

<b>LOW PROFILE SOLDER TYPE IC SOCKETS</b>		
8 pin to 40 pin		1C per pin (20 pin = 20¢)

<b>MISCELLANEOUS</b>	
POLARIZED LINE CORD - 5 FT	\$ .42
75 - 300 OHM MATCHING TRANSFORMER	\$.50



**KCS Electronics Corp.**

P.O. Box 33205

Phoenix, Arizona 85067

(602) 274-2885

Special Quantity Pricing. Min. Credit Card Order \$15.00. No Min. on COD or Prepaid. Prepaid Orders Add \$2.50 Ship., Ins., Handling

145

## 30M KITS & MORE

ALL WARC BANDS PLUS MOST OF THE GENERAL COVERAGE BANDS WITH YOUR FT101 SERIES, 15520 SERIES & 55 LINE!!! UNBELIEVABLE YOU SAY --- WELL, WRITE FOR INFORMATION & PRICES ON OUR NEW LINE OF GENERAL COVERAGE SYNTHESIZERS. YOU'LL BE SURPRISED!! NEW 30 METER BAND!!! --- GRANDKIT FT101 SERIES KITS GIVE 10-MHz OPERATION ON THE EXISTING WVV/JJ POSITION. ALL INFORMATION, WIRE AND PARTS REQUIRED. POSTPAID. \$15.00 GRANDKITS FOR MANY OF THE RADIOS WE MAKE DISPLAYS FOR: WRITE.

## HANDIE OWNERS !!

HANDHELD PORTABLE RADIOS --- TOP QUALITY COMIDE "QUICKDRAM" BELT HOLSTER, YOUR RADIO SNUG AND SECURE ON YOUR HIP READY FOR IMMEDIATE WITHDRAWAL AND USE. YOU WILL BE DELIGHTED!! SPECIFY MAKE & MODEL RADIO, BLACK/BROWN LEATHER. --- \$30.00 ALSO AVAILABLE --- FINALLY!!! A CAR DOOR OR DASH BRACKET!!!! HOLDS YOUR HANDHELD RADIO. YOU'LL LOVE IT. NO MORE FUMBLING ON THE DASH OR SEAT. NO TOOLS. SPECIFY MODEL. --- \$20.00 SUPERCHARGER REVITALIZES YOUR DEAD HANDHELD IMMEDIATELY!!! PLUG IT IN AND FINISH THAT QSO. FULL CHARGE IN SIX HOURS. WON'T OVERCHARGE. SIMILAR TO QST ARTICLE OF DECEMBER LAST. COMES WITH AFC AND DFC POWER CORDS. READY TO GO. --- \$70.00 300 MHz DIVIDE BY TEN PRESCALERS, ASSEMBLED AND TESTED ON A CIRCUIT BOARD. JUST NEED FIVE VOLTS TO OPERATE. ADD TEN DOLLARS FOR A PREAMP. WRITE FOR MORE INFO. --- \$25.00 IC24/A1/E SERVICE MANUALS 8x12 WITH LARGER DIAGRAMS. \$12.00

ALL ITEMS POSTPAID. CANADIANS ADD 20% AND ORDER FROM B.C.T! 30 DAY MONEY BACK ON DISPLAYS, SYNTHESIZERS, CHARGERS AND PRESCALERS. YOU PAY RETURN POSTAGE. CASHIERS CHECK OR M.O.

## GRAND SYSTEMS

P.O. BOX 3377 BLAINE WASH. 98230  
P.O. BOX 3254 LANGLEY BC CAN. V3A4R6  
(604) 530 4551

134

## RELIABLE MICROWAVE TV ANTENNAS

2.1 to 2.6 GHz Frequency Range  
34db System Gain (or Greater)

Complete System (as pictured)	\$119.95
Down Converter Probe Style (Assembled and Tested)	\$49.95
Power Supply (12V to 16V DC+) (Assembled and Tested)	\$39.95



## PETERSON ELECTRONICS

4558 Auburn Blvd.  
Sacramento, CA 95841  
(916) 486-9071

C.O.D.'s  
SPECIAL QUANTITY PRICING  
Dealers Wanted



1 YEAR WARRANTY PARTS & LABOR

162

**NEW JERSEY:** Annual Flemington Hamfest, Saturday, April 9 from 8 AM to 4 PM at the Hunterdon Central High School Field House. 20,000 square feet of heated indoor area. Gigantic flea market, 200 tables, major manufacturers and more. Bring the family and your friends. Flemington is located between NYC and Philadelphia at the intersection of routes 202 and 31 just 10 miles south of I-78, and is a tourist area. Talk-in 146.52, 147.375, 147.015, 224.12 and 224.54 MHz. Admission \$3.00 donation. For reservations or information call (201) 788-4080 or write: Cherryville Repeater Association c/o W2FCW, Box 76, Fairview, Dr., Annandale, NJ 08801.

**NEW YORK:** The Suffolk County Radio Club's indoor Flea Market, Sunday, May 1, 8 AM to 3 PM, Republic Lodge No. 1987, 585 Broadhollow Road, Melville, Long Island. Admission \$2.00 (spouses and children under 12 free). Sellers tables \$7.00, includes one admission. Free parking. Refreshments. Talk in on 144.61/145.21 and 146.52. For information: Richard Tygar, AC2P. (516) 643-5956 evenings.

**NEW YORK:** The 24th annual Southern Tier Amateur Radio Club's Hamfest, Saturday, May 7, the Treadway Inn, Oswego. Flea market opens at 8 AM. Vendor displays and sales; tech and non-tech talks; refreshments. Advance tickets only for a dinner at 6:30 PM. Talk in on 22/82, 16/76 or 146.52 simplex. For further info SASE to KF2X, C. England, RD #1, Box 144, Vestal, NY 13850.

**NORTH CAROLINA:** The Raleigh Amateur Radio Society's 11th annual Hamfest, Sunday, April 17, Crabtree Valley Mall, U.S. 70 West, starts 8 AM. Admission \$4.00 includes tailgating. Tables available for rent. Covered Flea Market. CW and homebrew contests, special interests meetings. Talk in on 04/64, 28/88. For information: RARS Hamfest, PO Box 17124, Raleigh, NC 27619.

**OHIO:** The 14th annual B\*A\*S\*H Friday night of Dayton Hamvention, April 29, Convention Center, Main and Fifth Streets. Adjacent parking. Free admission. Refreshments and entertainment. Two exciting top awards and more. For further information contact the Miami Valley FM Association, PO Box 263, Dayton, Ohio 45401.

**OHIO:** The Athens County ARA annual Hamfest, Sunday, May 15, Athens City Recreation Center, U.S. 33 and 50. 8 AM to 4 PM. Setup 7 AM. Outdoor paved flea market space \$2.00. Some indoor space available \$3.00. Food, free parking, restaurants and recreation area within walking distance. Athens Mall next door. Tickets \$1 advance, \$2 at gate. Talk in 146.34/94. Tickets and info: ACARA, PO Box 72, Athens, Ohio 45701. Or call Joe, WB8DOD (614) 797-4874.

**PENNSYLVANIA:** The first annual Southern Alleghenies Hamfest, April 10, 8 AM to 5 PM, Bedford County Fairgrounds, intersection of Routes 30 and 220. Sponsored by the Bedford ARC; Altoona (Horseshoe) ARC; Cumberland, MD, ARC; Somerset ARC and the Blue Knob Repeater Association, this Hamfest features computer demonstrations, displays, ARRL booth, refreshments and more, all in a large heated building. Talk in on the Bedford repeater 145.49 and 146.52 simplex. Admission \$3.00. Includes tables \$5.00. For information: Tom Gutschall, W3BZN (814) 942-7334 or on the 147.75/15 Blue Knob Repeater.

**ROCHESTER HAMFEST:** Atlantic Division/New York State Convention, Saturday, May 21, Monroe County Fairgrounds. Hotel headquarters, Rochester Marriott Thruway. More info? Write or call Rochester Hamfest, 300 White Spruce Blvd., Rochester, NY 14623 (716) 424-7184.

**SOUTH CAROLINA:** The Blue Ridge Amateur Radio Society's Hamfest, Saturday, April 30 and Sunday, May 1, at the American Legion Fairgrounds, White Horse Road, Greenville. Admission \$3.00. Talk in on 146.01/61 and 223.46/224.06. For information: Phil Mullins, WD4KTG, Hamfest Chairman, PO Box 99, Simpsonville, SC 29681. For advance sales: Mrs. Sue Chism, Rt. 6, 203 Lanewood Dr., Greenville, SC 29607.

**TEXAS:** TARS, The Tideland Amateur Radio Society's Springfest 1983 at the fairgrounds in League City, Saturday, April 16. Auction, displays, demonstrations, good food and fellowship. Free admission. Refreshments available from 7 AM. Activities start 9 AM to 4 PM. For information: T.A.R.S., PO Box 73, Texas City, TX 77590.

**WASHINGTON:** The Central Washington State Hamfest sponsored by the Yakima Amateur Radio Club, W7AQ, Saturday, May 14, 9 AM to 5 PM, lunch available, and Sunday, May 15, 8 AM to 2 PM, breakfast and lunch, the Hobby Building, Central Washington State Fairgrounds, Yakima. Combination ticket \$4.00 advance; \$5.00 door. Additional tickets 2/\$5.00. Regional dealer displays and FREE swap and shop with plenty of tables. Talk in on 146.01/61. For tickets and information: Dan Houghton, PO Box 9211, Yakima, WA 98909.

**WISCONSIN:** The Madison Area Repeater Association's 11th annual Swapfest, Sunday, April 10, Dane County Exposition Center Forum Building, Madison. Doors open 8 AM for commercial exhibitors and flea market sellers; 9 AM for general public. Admission \$2.50 advance and \$3.00 door. Children twelve and under free. Flea market tables \$4.00 each advance and \$5.00 door. Reserve early.

Exhibitors and flea market sellers will have equipment and components for hams, computer hobbyists and experimenters. An all-you-can-eat pancake breakfast and a Bar-Bar-Q lunch will be available. Talk in on WR9ABT, 146.16/76. For information and reservations write M.A.R.A., PO Box 3403, Madison, WI 53704.

**WISCONSIN:** The 3F ARC Swapfest, May 7, 8 AM to 3 PM, Neenah Labor Temple, 4 ft. tables \$1.50 advance; \$2.00 at door. Talk in on 144.61/145.21. For advance registration: Mark Michel, W90P, 339 Naymut St., Menasha, WI 54952.

**WISCONSIN:** The Ozaukee Radio Club's 5th annual Swapfest, Saturday, May 7, 8 AM to 1 PM, Circle B Recreation Center, Highway 60, Cedarburg, 20 miles north of Milwaukee. Admission \$2.00 advance, \$3.00 door. 8 ft. tables \$3.00 each. Food and refreshments. Sellers admitted at 7 AM for setups. For tickets, tables, maps or information SASE to Ozaukee Radio Club Swapfest, PO Box 13, Port Washington, WI 53074.

## OPERATING EVENTS

"Things to do..."

**APRIL 6, 7 AND 13, 14:** DX-YL to North American YL Contest. CW: Wednesday, April 6, 1800 UTC to Thursday, April 7, 1800 UTC. Phone: Wednesday, April 13, 1800 UTC to Thursday, April 14, 1800 UTC. All licensed women operators throughout the world are invited to participate. DX YL call "CO North American YL"; N.A. YL call "CO DX YL". All bands may be used. No cross band operation. Net contacts, repeater contacts and contacts with OMs do not count. Stations may be worked/counted once on each band and mode. Exchange: Station worked, QSO number, RS(T), state or country. Entries in log must show time, band, date and xmitter power. Phone and CW scored as separate contests. Submit separate logs for each contest. DX-YLs incl. Hawaii and Alaska, may contact all N.A. continent which includes 48 cont. states and Canadian Provinces. Contestants on N.A. continent may contact DX stations to include Hawaii and Alaska. A station may be counted once on each band for credit and one point is earned for each station worked once on each band. Multiply number of QSO's by number of different states and provinces or countries worked. A multiplier is counted once in contest, NOT on each band. Contestants running 150 watts or less on CW and 300 watts PEP or less on SSB, may multiply results by (E) by 1.25 (low power multiplier). Logs must be signed by operator and postmarked by April 28, 1983 and received NLT May 23, 1983. Send logs to YLRL Vice President.

**APRIL 17 AND 18:** The Central Massachusetts Amateur Radio Association will commemorate Patriot's Day, honoring the Minutemen and other patriots who fought during the American Revolution. Club station W1BIM will operate Sunday, 1700 UTC to 2200 UTC; and Monday, 1500 UTC to 2200 UTC from the Worcester, Mass. Science Center, approx. 20 kHz up from the General phone band edge, 40-10 meters. For a special certificate send QSL card and business SASE to: Alan Freeman, KA1XL, 83 Newton Avenue North, Worcester, MA 01602.

**APRIL 22-24:** A special events station, K0TIK, will operate from the Nebraska State Arbor Lodge, former home of Arbor Day founder, J. Sterling Morton, in Nebraska City, NE, Tree City U.S.A. during the annual Arbor Day celebration. This station plus other club member stations will operate in the general portion of phone and CW bands, 80-10 meters, 2400 UTC Friday to 0600 UTC Sunday. All Amateurs contacting this or any other club member station will be eligible to receive an Arbor Day commemorative certificate. Send one dollar and business SASE to N.C. A.R.C., Box 8, Nebraska City, NE 68410.

**APRIL 23 AND 24:** TSRAC Scavenger Hunt Contest, 0000Z, April 23 to 2359Z, April 24, sponsored by the Triple States Radio Amateur Club. Two trophies to be awarded; one to General Class and above licensee with highest score and one to Novice or Technician Class operator with highest score. Second and third place certificates awarded also. Modes: CW and phone. Exchange: QSOs or "CQ TSHT TEST", 20 kHz ± above bottom of any General or Novice band. Open to all Amateurs. Submit entries to contest chairman: David M. Kinney, KC8YR, RD #1, Mingo Jct., OH 43938 by May 25.

**APRIL 23 AND 24:** The Independent Amateur Radio Group of Delaware will operate from atop the U.S. Geological Survey marker at the point where Pennsylvania, Maryland and Delaware meet, Mason and Dixon's Stone Number one, from 1500Z to 2300Z each day. Rain date April 30 and May 1. 10 through 40 meters in lower ends of General segments. 2M activity announced on local repeaters. ARRL assures QSL cards will count for any or all three states. Each operator will use own call with a "/3/3/" identifier. Special QSL card for SASE to operator worked.

**APRIL 23 AND 24:** QRP Amateur Radio Club International Spring QSO Party, Saturday, 1200 UTC to Sunday, 2400 UTC. Exchange: Members give RS(T), state/prov-

# QUALITY SPECIALS

## MONSTER-SIZED MULTI-PAKS \$10.95 each

(The big guaranteed brand new components from manufacturers such as, Delco, I.C.C., Panasonic, Rishakon, etc.)

PART #	PIECE COUNT	DESCRIPTION
PK001	100	ASSORTED LOW VALUE ELECTROLYTIC CAPACITORS
PK002	40	VARIOUS VALUES LESS THAN 500 MFD.
PK003	2 DOZEN	ASSORTED MEDIUM VALUE ELECTROLYTIC CAPACITORS
PK004	40	VARIOUS VALUES FROM 10 MFD TO 1000 MFD.
PK005	2 DOZEN	ASSORTED HIGH VALUE ELECTROLYTIC CAPACITORS
PK006	30	VARIOUS VALUES FROM 10 MFD TO 20 MFD.
PK007	200	LOW PROFILE SOLDER PIN I.C. SOCKETS, 18 EACH OF 8, 14, 18, 28, and 40 PIN SOCKETS.
PK008	200	LOW PROFILE 5% RESISTORS (1/4W) AT LEAST 35 DIFFERENT VALUES LESS THAN 100 OHMS ARE GUARANTEED.
PK009	200	MEDIUM VALUE 5% RESISTORS (1/4W) AT LEAST 100 DIFFERENT VALUES BETWEEN 100 AND 10,000 OHMS ARE GUARANTEED.
PK010	200	HIGH VALUE 5% RESISTORS (1/4W) AT LEAST 50 DIFFERENT VALUES BETWEEN 10K AND 100 M OHMS ARE GUARANTEED.
PK011	132	SAME AS PK007 BUT RESISTORS ARE 1/2 WATT - 5%.
PK012	132	SAME AS PK009 BUT RESISTORS ARE 1/2 WATT - 5%.

## MONSTER JR. MULTI-PAKS \$2.95 EACH.

ANY OF THE MULTI-PAKS ABOVE ARE AVAILABLE WITH THE PRICE POINT FOR \$2.95 PER PAK. SPECIFY JUNIOR PAK AFTER THE PART NUMBER. THE I.C. SOCKET JR. PAKS AND THE 1/2 WATT RESISTOR JR. PAKS MAY OFFER SLIGHTLY FROM THE FULL SIZE PAK'S DESCRIPTION.

## SOPHISTICATED I.C.'S

DATA SHEETS AND APPROPRIATE APPLICATION NOTES ARE PROVIDED FREE WITH ALL INTEGRATED CIRCUITS LISTED BELOW

PART # & MANUF.	DESCRIPTION	PRICE (EA.)
80104 (LSI COMP SYS.)	CMOS DIVIDER I.C. HAS 10/10 TABLE SELECTABLE INPUT TO YIELD DIVIDE BY 10, 100, 1000, or 10000 OUTPUTS.	\$3.50
LEN01 (LSI COMP SYS.)	D.C. TO 5 MHz SIX DECADE MOD UP/COUNTER WITH 8 DECADE LATCH AND MULTIPLE LED BCD OUTPUTS AND OUTPUT TRIGGER ACCESS TO LOGIC LATCHES. ALLOWS ATTACHMENT OF PRECALCULATED COUNTING TO 1000 MHz TO 500 MHz.	\$13.75
LE222 (LSI COMP SYS.)	14 PIN EPROM AUTOMOTIVE MARINE ANTI-THEFT DIGITAL LOCK CIRCUIT HAS 5 240 x 8 DIGIT COMBINATIONS WITH 25 MICROAMP STANDBY "SAVE" MODE FOR "YAKET" PARKING.	\$3.50
2N486 (PERMANTS)	2 1/2 DIGIT DIGITAL MULTIMETER I.C. WITH LCD DRIVE ON CHIP CLOCK AND REFERENCE. COMPLETE DVM CIRCUIT CAN BE MADE WITH PASSIVE EXTERNAL COMPONENTS.	\$14.25
FE02010 (AND COMP.)	3 1/2 DIGIT LCD DISPLAY	\$12.00

## CAPACITORS

DIPPED TANTALUMS		AXIAL ELECTROLYTIC		RADIAL ELECTROLYTICS	
(EA.)	(EA.)	(EA.)	(EA.)	(EA.)	(EA.)
4 mfd 25V	\$ .30	1 mfd 45V	\$ .15	1 mfd 50V	\$ .08
22 mfd 25V	\$ .50	1.5 mfd 50V	\$ .20	2.2 mfd 50V	\$ .20
33 mfd 25V	\$ .50	4.7 mfd 50V	\$ .15	4.7 mfd 25V	\$ .10
47 mfd 25V	\$ .50	10 mfd 50V	\$ .15	10 mfd 25V	\$ .10
1.0 mfd 50V	\$ .30	47 mfd 25V	\$ .20	47 mfd 15V	\$ .13
1.5 mfd 50V	\$ .30	100 mfd 10V	\$ .17	220 mfd 25V	\$ .28
2.2 mfd 50V	\$ .25	1000 mfd 25V	\$ .27	1000 mfd 25V	\$ .35
5.0 mfd 25V	\$ .77	470 mfd 25V	\$ .57	1000 mfd 25V	\$ .72
10 mfd 25V	\$ .86	1000 mfd 25V	\$ .57	1000 mfd 25V	\$ .72
10 mfd 10V	\$ .80	2200 mfd 10V	\$ .70	2200 mfd 10V	\$ .70
22 mfd 10V	\$ .80	2200 mfd 10V	\$ .70	2200 mfd 10V	\$ .70

## GOLDSMITH SCIENTIFIC CORPORATION

P.O. BOX 318 COMMACK, NY 11725  
PHONE ORDERS WELCOME - (516) 779-7944  
MINIMUM ORDER \$20.00 - U.S. FUNDS ONLY  
NEW YORK STATE RESIDENTS ADD SALES TAX  
POSTAGE - ADD 5% PLUS \$1.50 INSURANCE. C.O.D. \$2.00 EXTRA  
MASTER CHARGE AND VISA ACCEPTED  
AVAILABILITY OF CERTAIN ITEMS MAY BE LIMITED

133

## MOBILE TOWERS by ALUMA

FOR MOBILE VAN, TRUCK OR TRAILERS. USE FOR COMMUNICATION OR CHECK YOUR SIGNALS.

HIGHEST QUALITY ALUMINUM & STEEL

- TELESCOPING Crank-Ups to 100 ft.
  - TILT-OVER MODELS
- Easy to install. Low Prices.

EXCELLENT FOR HAM COMMUNICATIONS



Mobile Trailer Type



Mobile Truck Type

Mobile Van Type

Over 36 types aluminum and steel towers made-specials designed and made-write for details

ALUMA TOWER COMPANY  
BOX 2806HR  
VERO BEACH, FLA. 32960  
(305) 567-3423 TELEX 80-3405

106

ince/country and QRP ARCI membership number. Non-members give RS(T), state/province/country and power output. QSO points (total all bands) times total number of states/provinces/countries (may be worked on more than one band) times power multiplier times bonus multiplier (if any) equals claimed score. Send large SASE or IRCs to contest chairman for scoring summary sheet in advance of contest. Send full log data plus separate worksheet showing details and time off air. No logs returned. For results and scores send large SASE with one ounce of U.S. postage or IRCs. Logs must be received by May 21, 1983. QRP ARCI Contest Chairman, William Dickerson, WA2JOC, 230 Mill St., Danville, PA 17821.

**APRIL 23 AND 24:** The Missouri Valley Amateur Radio Club's fourth annual Pony Express Day, 1000 CST to 1900 CST (Saturday) and 0900 CST to 1200 CST (Sunday). This event commemorates the original running of the Pony Express from St. Joseph, Missouri to Sacramento, Calif. Operating frequencies: 10 kHz from bottom of the general phone bands on 15, 20, 40 and 75 meters. On 10 meters - 28.575 CW; 10 meters - 28.150, 15 meters - 21.150, 40 meters - 7.125. Anyone contacting Club station W0NH is eligible for a special Pony Express certificate. Just send two first-class postage stamps and a QSL card to: Missouri Valley Amateur Radio Club, 401 N. 12th Street, St. Joseph, MO 64501.

**APRIL 29-MAY 1:** The first International VHF/UHF Conference to be held as part of the Dayton Hamvention. Activities span all three days and include tech talks and forums; noise figure and antenna gain measuring contests, a hospitality suite get-together with refreshments. All this along with the rest of the Hamvention features. For further information and to advise of participation in contests contact: Jim Stitt, WA8ONQ, 311 N. Marshall Road, Middletown, OH 45042, (513) 475-4444 business or (513) 863-0820 home.

**MAY 7:** Harry's Haydays. The Southside Amateur Radio Club will operate KA0HXU to commemorate President Harry Truman's 99th birthday. The station will operate at or near the old Truman farm home in Grandview, MO from 1500Z to 2400Z on 21.355, 14.290 and 7.230. Commemorative QSL's will be sent via the bureau unless otherwise requested. For information: Southside ARC, PO Box 412, Grandview, MO 64030.

**WORKSHOP:** Personal Computer Interfacing and Scientific Instrument Automation, \$395.00. Charlotte, NC, June 2-4; Reston, VA, June 16-18; Charleston, SC, July 14-16; Williamsburg, VA, Aug. 11-13; and Greensboro, NC, Sept. 8-10. These are hands-on workshops with each participant wiring and testing interfaces. For more information, call or write Dr. Linda Lefel, C.E.C., Virginia Tech, Blacksburg, Virginia 24061. (703) 961-4848.

## CADELL COIL CORP.

POULTNEY, VT. 05764 802-287-4055

WE LIKE TO WIND COILS - TRY US

COILS FOR HOMEBILT

Sardine Sender 80 Meter QRP Rig	\$8.50
QST Oct '79 p 15	
QRP Transceiver 25 Watt Max	7.00
ARRL Handbook p 350	
Tuna Tin 2 WAS 40 Meter Transmitter	5.25
QST May '76 p 21	
Mini Miser's Dream Receiver	13.25
QST Sep '76 p 21	
20 Meter Direct Conversion Receiver	7.00
QST Apr '78 p 12	
Amplifier for HW-8 QRP Transceiver	13.30
QST Apr '79 p 18	
Harmonic Filter (for above) per band	4.50
Low Frequency Transmitter	9.00
59 Sep '79 p 23	

Prices include postage.

### BALUNS

Get POWER into your antenna. See ARRL Handbook p. 585 or 19.9 or 6-20.	\$12.00
1KW-4:1 impedance	14.50
2KW-4:1	14.50
1KW-6:1, 9:1, or 1:1 (pick one)	13.50
2KW-6:1, 9:1, or 1:1 (pick one)	16.00
100W-4:1, 6:1, 9:1, or 1:1 (pick one)	8.00

Many other interesting coil kits in our NEW LIST SC. You must send a stamped envelope to receive our coil kit list. ✓ 118

## DIPOLE ANTENNA CONNECTOR



NYE QUE (HQ-1) dipole connector has coax SO-238 socket molded into glass filled plastic body to accept coax PL-259 plug on leadline. Drop cap screws coat fittings dry. Instructions included. Guaranteed. At your dealers or \$5.95 postpaid. Companion insulators \$1.25pr.

BUDWIG MFG. Co. PO Box 829, Ramona, CA 92065

Ca. Res. add 6% Sales Tax

117

## AMP-LETTER

All new publication, new owner K8KXX  
The AMP-LETTER is devoted to the design, building, and modification of amplifiers.  
The AMP-LETTER will help you lower your building cost, provide sources for parts and information, keep you abreast of latest techniques and solid state design.  
Subscription cost \$18.00/yr. 12 issues. Sample issue \$2.00 VISA/Master Charge.

THE AMP-LETTER  
73 Maple Drive, Hudson, OH 44226 216-653-8157 ✓ 109

When it comes to

# QSL's...



it's the ONLY BOOK!  
US or Foreign Listings

## 1983 callbooks

Here they are! The latest editions of the world-famous Radio Amateur Callbook are available now. The U.S. edition features over 400,000 listings, with over 75,000 changes from last year. The Foreign edition has over 370,000 listings, over 50,000 changes. Each book lists calls and the address information you need to send QSL's. Special features include call changes, census of amateur licenses, world-wide QSL bureaus, prefixes of the world, international postal rates, and much more. Place your order for the new 1983 Radio Amateur Callbooks, available now.

	Each	Shipping	Total
<input type="checkbox"/> US Callbook	\$19.95	\$3.05	\$23.00
<input type="checkbox"/> Foreign Callbook	\$18.95	\$3.05	\$22.00

Order both books at the same time for \$41.95 including shipping.

Order from your dealer or directly from the publisher. All direct orders add shipping charge. Foreign residents add \$4.55 for shipping. Illinois residents add 5% sales tax.



### SPECIAL OFFER!

Amateur Radio Emblem Patch only \$2.50 postpaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on Jackets and caps.

ORDER TODAY!

## RADIO AMATEUR callbook INC.

Dept. F  
925 Sherwood Drive  
Lake Bluff, IL 60044, USA



166

April 1983 115

FACIT 4555 SERIAL PAGE PRINTER

The Facit 4555 alphanumerical serial printer is complete. Equipped with RS232C Interface, printing mechanism, control electronics, drive electronics, power supply and character generator. The adaptation electronics can be modified in four versions: Bit-parallel data transfer, CCITT (EIA, RS232C) for bit-serial data transfer and the current loop (TTY) interface also for bit serial data transfer. The Facit 4555 prints on ordinary paper and is adjustable for different paper widths and formats, 9.5" paper width with 66 lines per page or DIN A4 with 70 lines per page.

SPECIFICATIONS

Print speed	up to 60ch.s.	Char. spacing	2.54mm/1/10" 80ch/line
Printing mode	Incremental.		1.55mm/0.06" 132ch/line
Max. # of ch/line	80 alt. 132.	Char. Code	ECMA-6 7-bit coded char. set
Matrix	7 X 5 dot matrix.	Char. Set	63 Char. various national versions.
Char. Size Height	2.7mm/1/8"	Feed mechanism	Sprocket feed.
Char. Size Width	1.3mm/0.05" 132ch/line		
	2.1mm/0.083" 80ch/line		

THESE UNITS WERE PULLED OUT OF SERVICE IN GOOD WORKING CONDITION. WE CHECK EACH UNIT ON A RADIO SHACK TRS-80 COLOR COMPUTER.




PRINTER ONLY \$129.99

Printer with linecord, box of paper, inter-connect cable for TRS-80 COLOR COMPUTER. \$149.99

GENEVA CALCULATOR WATCH

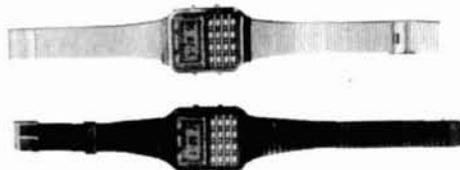This attractive watch has the following modes:  
Normal Time Setting,  
Calendar Setting,  
Daily Alarm Time Setting,  
Weekly Alarm Time Setting,  
Chronograph,  
Calculator.



Featured in Black Plastic \$24.99 or Featured in Stainless Steel \$29.99

SILICON DIODES

MR751	100vdc	6Amps	10/\$5.00	100/\$38.00
MR510	1000vdc	3Amps	10/\$3.75	100/\$24.00
HEP170	1000vdc	2Amps	20/\$2.00	100/\$15.00
IN3209	100vdc	15Amps	\$2.00	10/ \$15.00
BYX21/200	200vdc	25Amps	\$2.00	10/ \$15.00
IN2138A	600vdc	60Amps	\$5.00	10/ \$40.00
DS85-04C	400vdc	80Amps	\$10.00	10/ \$80.00
IN3269	600vdc	160Amps	\$15.00	10/\$120.00
275Z41	300vdc	250Amps	\$20.00	10/\$175.00
7-5754	300vdc	400Amps	\$30.00	10/\$250.00
RCD-15	15KVDC	20ma.	\$3.00	10/ \$20.00
SMFR20K	20KVDC	20ma.	\$4.00	10/ \$30.00
IN4148	signal		30/\$1.00	100/ \$3.00

FEED THRU SOLDER RF CAPACITORS

470pf +-20%
5/\$1.00 or 100/\$15.00 or 1000/\$100.00
1000pf/.001uf +-10%
4/\$1.00 or 100/\$20.00 or 1000/\$150.00

E PROMS

2708 1024x1	\$2.00 each
2716 2048x8	\$4.00 each
27L32/25L32	\$10.00 each

FAIRCHILD 4116 16K DYNAMIC RAMS 200ns. Part # 16K75

25 For \$25.00 or 100 For \$90.00 or 1000 For \$750.00

HEWLETT PACKARD MICROWAVE DIODES

IN5711	(5082-2800)	Schottky Barrier Diodes	\$1.00 or 10 for \$ 8.50
IN5712	(5082-2810)	" " "	\$1.50 or 10 for \$10.00
IN6263	(HSCH-1001)	" " "	\$.75 or 10 for \$ 5.00
5082-2835		" " "	\$1.50 or 10 for \$10.00
5082-2805	Quad Matched	" " "	per set \$5.00 or 10 for \$40.00

**Toll Free Number  
800-528-0180  
(For orders only)**

**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# "MIXERS"

## WATKINS JOHNSON WJ-M6 Double Balanced Mixer

LO and RF 0.2 to 300MHz	IF DC to 300MHz	\$21.00
Conversion Loss (SSB)	6.5dB Max. 1 to 50MHz	
Noise Figure (SSB)	8.5dB Max. .2 to 300MHz	WITH DATA SHEET
	same as above	
Conversion Compression	8.5dB Max. 50 to 300MHz	
	.3dB Typ.	

## NEC (NIPPON ELECTRIC CO. LTD. NE57835/2SC2150 Microwave Transistor

NF Min F=2GHz	dB 2.4 Typ.	MAG F=2GHz	dB 12 Typ.	\$5.30
F=3GHz	dB 3.4 Typ.	F=3GHz	dB 9 Typ.	
F=4GHz	dB 4.3 Typ.	F=4GHz	dB 6.5 Typ.	

Ft Gain Bandwidth Product at Vce=8v, Ic=10ma. GHz 4 Min. 6 Typ.  
 Vcbo 25v Vceo 11v Vebo 3v Ic 50ma. Pt. 250mw

## UNELCO RF Power and Linear Amplifier Capacitors

These are the famous capacitors used by all the RF Power and Linear Amplifier manufacturers, and described in the RF Data Book.

5pf	10pf	18pf	30pf	43pf	100pf	200pf	1 to 10pcs.	\$1.00	ea
5.1pf	12pf	22pf	32pf	51pf	110pf	220pf	11 to 50pcs.	\$ .90	ea
6.8pf	13pf	25pf	33pf	60pf	120pf	470pf	51 up	pcs.	\$ .80
7pf	14pf	27pf	34pf	80pf	130pf	500pf			
8.2pf	15pf	27.5pf	40pf	82pf	140pf	1000pf			

## NIPPON ELECTRIC COMPANY TUNNEL DIODES

		MODEL 1S2199	1S2200	\$7.50
Peak Pt. Current ma.	Ip	9min. 10Typ. 11max.	9min. 10Typ. 11max.	
Valley Pt. Current ma.	Iv	1.2Typ. 1.5max.	1.2Typ. 1.5max.	
Peak Pt. Voltage mv.	Vp	95Typ. 120max.	75Typ. 90max.	
Projected Peak Pt. Voltage mv.	Vpp Vf=Ip	480min. 550Typ. 630max.	440min. 520Typ. 600max.	
Series Res. Ohms	rS	2.5Typ. 4max.	2Typ. 3max.	
Terminal Cap. pf.	Ct	1.7Typ. 2max.	5Typ. 8max.	
Valley Pt. Voltage mv.	VV	370Typ.	350Typ.	

## FAIRCHILD / DUMONT Oscilloscope Probes Model 4290B

Input Impedance 10 meg., Input Capacity 6.5 to 12pf., Division Ratio (Volts/Div Factor) 10:1, Cable Length 4Ft., Frequency Range Over 100MHz.

These Probes will work on all Tektronix, Hewlett Packard, and other Oscilloscopes.

PRICE \$45.00

## MOTOROLA RF DATA BOOK

Lists all Motorola RF Transistors / RF Power Amplifiers, Varactor Diodes and much much more.

PRICE \$7.50

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**PRICES SUBJECT TO CHANGE WITHOUT NOTICE**

# RF TRANSISTORS, MICROWAVE DIODES

PART	PRICE	PART	PRICE	PART	PRICE
1S2199	\$ 7.50	2N6083	\$ 13.25	CA2612 (TRW)	\$ 25.00
1S2200	7.50	2N6084	15.00	CA2674 (TRW)	25.00
2N1561	25.00	2N6094 /M9622	11.00	CA2881-1 (TRW)	25.00
2N1562	25.00	2N6095 /M9623	12.00	CA4101 (TRW)	25.00
2N2857	1.55	2N6096 /M9624	15.50	CA4201 (TRW)	25.00
2N2857JAN	2.55	2N6097	17.25	CA4600 (TRW)	25.00
2N2876	11.00	2N6136	21.85	CD1889	20.00
2N2947	18.35	2N6166	40.25	CD2545	20.00
2N2948	15.50	2N6201	50.00	CMD514AB	20.00
2N2949	3.90	2N6459	18.00	D4959	10.00
2N2950	4.60	2N6603	12.00	D4987M	20.00
2N3375	8.00	2N6680	80.00	D5147D	10.00
2N3553	1.57	2SC756A	7.50	D5506	10.00
2N3632	13.80	2SC781	2.80	D5827AM	20.00
2N3818	5.00	2SC1018	1.00	DMD6022	30.00
2N3866	1.30	2SC1042	12.00	DMS-2A-250	40.00
2N3924	3.35	2SC1070	2.50	HEP76	4.95
2N3927	17.75	2SC1239	2.50	HEPS3002	11.30
2N3950	25.00	2SC1251	12.00	HEPS3003	30.00
2N4072	1.80	2SC1306	2.90	HEPS3005	10.00
2N4127	21.00	2SC1307	5.50	HEPS3006	19.90
2N4427	1.30	2SC1760	1.50	HEPS3007	25.00
2N4428	1.85	2SC1970	2.50	HEPS3010	11.34
2N4957	3.45	2SC2166	5.50	HTEF2204 H.P.	112.00
2N4958	2.90	8B1087 (M.A.)	25.00	5082-0112 H.P.	14.20
2N4959	2.30	A50-12	20.00	5082-0253 H.P.	105.00
2N5090	13.90	A283B	5.00	5082-0320 H.P.	58.00
2N5108	4.00	ALD4200N (AVANTEK)	395.00	5082-0386 H.P.	POR
2N5109	1.70	AM123	97.35	5082-0401 H.P.	POR
2N5160	3.45	AM688	100.00	5082-0438 H.P.	POR
2N5177	21.62	BB105B	.52	5082-1028 H.P.	POR
2N5179	1.00	BD4/4JFBD4 (G.E.)	10.00	5082-2711 H.P.	23.15
2N5583	4.00	BFQ85	1.50	5082-3080 H.P.	2.00
2N5589	8.65	BFR90	1.30	5082-3188 H.P.	1.00
2N5590	10.35	BFR91	1.65	5082-6459 H.P.	POR
2N5591	13.80	BFW92	1.50	5082-8323 H.P.	POR
2N5635	10.95	BFX89	1.00	35826E H.P.	POR
2N5637	15.50	BFY90	1.00	35831E H.P.	29.99
2N5641	9.20	BGY54	25.00	35853E H.P.	71.50
2N5642	10.95	BGY55	25.00	35854E H.P.	75.00
2N5643	15.50	BGY74	25.00	HPA0241 H.P.	75.60
2N5645	13.80	BGY75	25.00	HXTR3101 H.P.	7.00
2N5646	20.70	BL161	10.00	HXTR3102 H.P.	8.75
2N5691	18.00	BLX67	11.00	HXTR6101/2N6617 H.P.	55.00
2N5764	27.00	BLY568CF	25.00	HXTR6104 H.P.	68.00
2N5836	5.45	BLY87	13.00	HXTR6105 H.P.	31.00
2N5842	8.00	BLY88	14.00	HXTR6106 H.P.	33.00
2N5849	20.00	BLY89	15.00	QSCH1995 H.P.	POR
2N5913	3.25	BLY90	20.00	JO2000 TRW	10.00
2N5922	10.00	BLY351	10.00	JO2001 TRW	25.00
2N5923	25.00	C4005	20.00	JO4045 TRW	25.00
2N5941	23.00	CA402 (TRW)	25.00	K3A	10.00
2N5942	40.00	CA405 (TRW)	25.00	MA450A	10.00
2N5944	9.20	CA612B (TRW)	25.00	MA41487	POR
2N5945	11.50	CA2100 (TRW)	25.00	MA41765	POR
2N5946	19.00	CA2113 (TRW)	25.00	MA43589	POR
2N6080	9.20	CA2200 (TRW)	25.00	MA43636	POR
2N6081	10.35	CA2213 (TRW)	25.00	MA47044	POR
2N6082	11.50	CA2418 (TRW)	25.00	MA47651	25.50

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**MHz electronics**

# GaAs, TUNNEL DIODES, ETC.

PART	PRICE	PART	PRICE	PART	PRICE
MA47100	\$ 3.05	MRF503	\$ 6.00	PT4186B	\$ POR
MA47202	30.80	MRF504	7.00	PT4209	POR
MA47771	POR	MRF509	5.00	PT4209C	POR
MA47852	POR	MRF511	8.65	PT4566	POR
MA49558	POR	MRF605	20.00	PT4570	POR
MB4021	POR	MRF629	3.47	PT4571	POR
MBD101	1.00	MRF644	23.00	PT4571A	POR
MDO513	POR	MRF816	15.00	PT4577	POR
MHW1171	42.50	MRF823	20.00	PT4590	POR
MHW1182	48.60	MRF901	3.00	PT4612	POR
MHW4171	49.35	MRF8004	2.10	PT4628	POR
MHW4172	51.90	MS261F	POR	PT4640	POR
MHW4342	68.75	MT4150 Fair.	POR	PT4642	POR
MLP102	25.00	MT5126 Fair.	POR	PT5632	POR
MM1500	32.32	MT5481 Fair.	POR	PT5749	POR
MM1550	POR	MT5482 Fair.	POR	PT6612	POR
MM1552	50.00	MT5483 Fair.	POR	PT6626	POR
MM1553	50.00	MT5596 Fair.	POR	PT6709	POR
MM1614	10.00	MT5764 Fair.	POR	PT6720	POR
MM2608	5.00	MT8762 Fair.	POR	PT8510	POR
MM3375A	11.50	MV109	.77	PT8524	POR
MM4429	10.00	MV1401	8.75	PT8609	POR
MM8000	1.15	MV1624	1.42	PT8633	POR
MM8006	2.30	MV1805	15.00	PT8639	POR
MO277L	POR	MV1808	10.00	PT8659	POR
MO283L	POR	MV1817B	10.00	PT8679	POR
MO3757	POR	MV1863B	10.00	PT8708	POR
MP102	POR	MV1864A	10.00	PT8709	POR
MPN3202	10.00	MV1864B	10.00	PT8727	POR
MPN3401	.52	MV1864D	10.00	PT8731	POR
MPN3412	1.00	MV1868D	10.00	PT8742	POR
MPSU31	1.01	MV2101	.90	PT8787	POR
MRA2023-1.5 TRW	42.50	MV2111	.90	PT9790	41.70
MRF212/208	16.10	MV2115	1.55	PT31962	POR
MRF223	13.25	MV2201	.53	PT31963	POR
MRF224	15.50	MV2203	.53	PT31983	POR
MRF237	3.15	MV2209	2.00	PTX6680	POR
MRF238	12.65	MV2215	2.00	RAY-3	24.99
MRF243	25.00	MWA110	7.45	40081	POR
MRF245	34.50	MWA120	7.80	40281	POR
MRF247	34.50	MWA130	8.25	40282	POR
MRF304	43.45	MWA210	7.80	40290	POR
MRF315	23.00	MWA220	8.25	RF110	25.00
MRF420	20.00	MWA230	8.65	SCA3522	POR
MRF421	36.80	MWA310	8.25	SCA3523	POR
MRF422	41.40	MWA320	8.65	SD1065	POR
MRF427	16.10	MWA330	9.50	SS43	POR
MRF428	46.00	NEC57835	5.30	TP1014	POR
MRF450/A	13.80	ON382	5.00	TP1028	POR
MRF453/A	17.25	PPT515-20-3	POR	TRW-3	POR
MRF454/A	19.90	PRT8637	POR	UTO504 Avantek	70.00
MRF455/A	16.00	PSCQ2-160	POR	UTO511 Avantek	75.00
MRF458	19.90	PT3190	POR	V15	4.00
MRF463	25.00	PT3194	POR	V33B	4.00
MRF472	1.00	PT3195	POR	V100B	4.00
MRF475	2.90	PT3537	POR	VAB801EC	25.00
MRF477	11.50	PT4166E	POR	VAB804EC	25.00
MRF502	1.04	PT4176D	POR	VAS21AN20	25.00

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

## MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE


COAXIAL RELAY SWITCHES SPDT

Electronic Specialty Co./Raven Electronics FSN 5985-556-9683 \$49.00  
 Part # 25N28 Part # SU-01  
 26Vdc Type N Connector, DC to 1 GHz.



Amphenol  
 Part # 316-10102-8  
 115Vac Type BNC DC to 3 GHz.

\$29.99

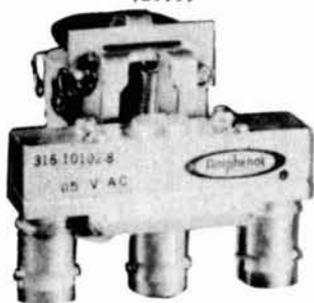


BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

\$7.99 or 2 For \$13.99 or 10 For \$50.00




FXR  
 Part # 300-11182  
 120Vac Type BNC DC to 4 GHz.  
 FSN 5985-543-1225

\$39.99

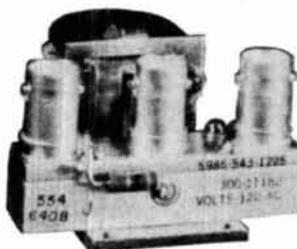

FXR  
 Part # 300-11173  
 120Vac Type BNC Same  
 FSN 5985-543-1850

\$39.99

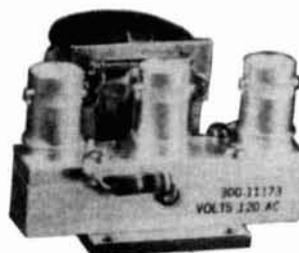

\$8.99 or 2 For \$15.99 or 10 For \$60.00



SOLID STATE RELAYS

P&B Model ECT1DB72 5vdc turn on  
 PRICE EACH \$5.00

Digisig, Inc. Model ECS-215 5vdc turn on  
 PRICE EACH \$7.50

Grigsby/Barton Model GB7400 5vdc turn on  
 PRICE EACH \$7.50

120vac contact at 7amps or 20amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

240vac contact 14amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

240vac contact at 15amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

NOTE: \*\*\* Items may be substituted with other brands or equivalent model numbers. \*\*\*

**MHz** electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

**PRICES SUBJECT TO CHANGE WITHOUT NOTICE**

RECALL PHONE MEMORY TELEPHONE WITH 24 NUMBER AUTO DIALER

The Recall Phone Telephone employs the latest state of art communications technology. It is a combination telephone and automatic dialer that uses premium-quality, solid-state circuitry to assure high-reliability performance in personal or business applications. \$49.99




ARON ALPHA RAPID BONDING GLUE

Super Glue #CE-486 high strength rapid bonding adhesive. Alpha Cyanoacrylate. Set-Time 20 to 40 sec., 0.7fl.oz. (20gm.) \$2.00



TOUCH TONE PAD

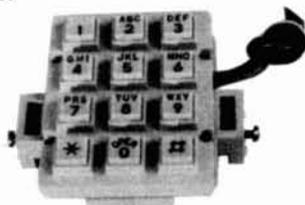This pad contains all the electronics to produce standard touch-tone tones. New with data.



\$9.99 or 10/\$89.99

MITSUMI UHF/VHF VARACTOR TUNER MODEL UVE1A

Perfect for those unscrambler projects. New with data.



\$19.99 or 10/\$149.99

INTEGRATED CIRCUIT

		1 to 10	11up
MC1372P	Color TV Video Modulator Circuit.	\$ 4.42	\$2.95
MC1358P	IF Amp., Limiter, FM Detector, Audio Driver, Electronic Attenuator.	5.00	4.00
MC1350P	IF Amplifier	1.50	1.25
MC1330A1P	Low Level Video Detector	1.50	1.15
MC1310P	FM Stereo Demodulator	4.29	3.30
MC1496P	Balanced Modulator/Demodulator	1.50	1.25
LM565N	Phase Locked Loop	2.50	2.00
LM380N14	2Watt Audio Power Amplifier	1.56	1.25
LM1889N	TV Video Modulator	5.00	4.00
NE564N	Phase Locked Loop	10.00	8.00
NE561N	Phase Locked Loop	10.00	8.00

FERRANTI ELECTRONICS AM RADIO RECEIVER MODEL ZN414 INTEGRATED CIRCUIT.

Features:

1.2 to 1.6 volt operating range., Less than 0.5ma current consumption. 150KHz to 3MHz Frequency range., Easy to assemble, no alignment necessary. Effective and variable AGC action., Will drive an earphone direct. Excellent audio quality., Typical power gain of 72dB., TO-18 package. With data. \$2.99 or 10 For \$24.99

NI CAD RECHARGEABLE BATTERIES

AA Battery Pack of 6 These are Factory New. \$5.00

SUB C Pack of 10 2.5Amp/Hr. \$10.00

Gates Rechargeable Battery Packs

12vdc at 2.5Amp/Hr. \$11.99

12vdc at 5Amp/Hr. \$15.99



**MHz electronics**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**We will be closed April 27th through May 2nd...**

**See you at the Dayton Hamvention!**

Toll Free Number  
800-528-0180  
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# "SOCKETS AND CHIMNEYS"

## EIMAC TUBE SOCKETS AND CHIMNEYS

SK110	Socket	SPOR
SK300A	Socket For 4CX5000A,R,J, 4CX10,000D, 4CX15,000A,J	\$520.00
SK400	Socket For 4-125A,250A,400A,400C,4PR125A,400A,4-500A,5-500A	260.00
SK406	Chimney For 4-250A,400A,400C,4PR400A	74.00
SK416	Chimney For 3-400Z	36.00
SK500	Socket For 4-1000A/4PR1000A/B	390.00
SK600	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	51.00
SK602	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	73.00
SK606	Chimney For 4CX250B,BC,FG,R,4CX350A,F,FJ	11.00
SK607	Socket For 4CX600J,JA	60.00
SK610	Socket For 4CX600J,JA	60.00
SK620	Socket For 4CX600J,JA	66.00
SK626	Chimney For 4CX600J,JA	10.00
SK630	Socket For 4CX600J,JA	66.00
SK636B	Chimney For 4CX600J,JA	34.00
SK640	Socket For 4CX600J,JA	36.00
SK646	Chimney For 4CX600J,JA	71.00
SK700	Socket For 4CX300A,Y,4CX125C,F	225.00
SK711A	Socket For 4CX300A,Y,4CX125C,F	225.00
SK740	Socket For 4CX300A,Y,4CX125C,F	86.00
SK770	Socket For 4CX300A,Y,4CX125C,F	86.00
SK800A	Socket For 4CX1000A,4CX1500B	225.00
SK806	Chimney For 4CX1000A,4CX1500B	40.00
SK810	Socket For 4CX1000A,4CX1500B	225.00
SK900	Socket For 4X500A	300.00
SK906	Chimney For 4X500A	57.00
SK1420	Socket For 5CX3000A	650.00
SK1490	Socket For 4CV8000A	585.00

## JOHNSON TUBE SOCKETS AND CHIMNEYS

124-111/SK606	Chimney For 4CX250B,BC,FG,R, 4CX350A,F,FJ	\$ 10.00
122-0275-001	Socket For 3-500Z, 4-125A, 250A, 400A, 4-500A, 5-500A	(pair)15.00
124-0113-00	Capacitor Ring	15.00
124-116/SK630A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
124-115-2/SK620A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
	813 Tube Socket	20.00

## CHIP CAPACITORS

.8pf	10pf	100pf*	430pf
1pf	12pf	110pf	470pf
1.1pf	15pf	120pf	510pf
1.4pf	18pf	130pf	560pf
1.5pf	20pf	150pf	620pf
1.8pf	22pf	160pf	680pf
2.2pf	24pf	180pf	820pf
2.7pf	27pf	200pf	1000pf/.001uf*
3.3pf	33pf	220pf*	1800pf/.0018uf
3.6pf	39pf	240pf	2700pf/.0027uf
3.9pf	47pf	270pf	10,000pf/.01uf
4.7pf	51pf	300pf	12,000pf/.012uf
5.6pf	56pf	330pf	15,000pf/.015uf
6.8pf	68pf	360pf	18,000pf/.018uf
8.2pf	82pf	390pf	

PRICES: 1 to 10 - .99¢    101 to 1000 .60¢    \* IS A SPECIAL PRICE: 10 for \$7.50  
 11 to 50 - .90¢    1001 & UP .35¢    100 for \$65.00  
 51 to 100 - .80¢    1000 for \$350.00

## TUBE CAPS (Plate)

HR1, 4	\$11.00
HR2, 3, 6 & 7	13.00
HR5, 8	14.00
HR9	17.00
HR10	20.00

## WATKINS JOHNSON WJ-V907: Voltage Controlled Microwave Oscillator \$110.00

Frequency range 3.6 to 4.2GHz, Power output, Min. 10dBm typical, 8dBm Guaranteed.  
 Spurious output suppression Harmonic (nf<sub>0</sub>), min. 20dB typical, In-Band Non-Harmonic, min. 60dB typical, Residual FM, pk to pk, Max. 5KHz, pushing factor, Max. 8KHz/V, Pulling figure (1.5:1 VSWR), Max. 60MHz, Tuning voltage range +1 to +15volts, Tuning current, Max. -0.1mA, modulation sensitivity range, Max. 120 to 30MHz/V, Input capacitance, Max. 100pf, Oscillator Bias +15 +0.05 volts @ 55mA, Max.

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

# MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



# "FILTERS"

## COLLINS Mechanical Filter #526-9724-010 MODEL F455Z32F

455KHZ at 3.2KHz wide. May be other models but equivalent. May be used or new. \$15.99

### ATLAS Crystal Filters

5.595-2.7/8/LSB, 5.595-2.7/LSB	
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out.	19.99
5.595-2.7/8/U, 5.595-2.7/USB	
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out.	19.99
5.595-.500/4, 5.595-.500/4/CW	
4 pole 500 cycles wide CW. Impedance 800ohms 15pf In/800ohms 0pf out.	19.99
9.0USB/CW	
6 pole 2.7KHz wide at 6dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-1599Hz	19.99

### KOKUSAI ELECTRIC CO. Mechanical Filter #MF-455-ZL/ZU-21H

455KHz at Center Frequency of 453.5KC. Carrier Frequency of 455KHz 2.36KC Bandwidth.	
Upper sideband. (ZU)	19.99
Lower sideband. (ZL)	19.99

\*\*\*\*\*

### CRYSTAL FILTERS

NIKKO	FX-07800C	7.8MHz	\$10.00
TEW	FEC-103-2	10.6935MHz	10.00
SDK	SCH-113A	11.2735MHz	10.00
TAMA	TF-31H250	CF 3179.3KHz	19.99
TYCO/CD	001019880	10.7MHz 2pole 15KHz bandwidth	5.00
MOTOROLA	4884863B01	11.7MHz 2pole 15KHz bandwidth	5.00
PTI	5350C	12MHz 2pole 15KHz bandwidth	5.00
PTI	5426C	21.4MHz 2pole 15KHz bandwidth	5.00
PTI	1479	10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB	20.00
COMTECH	AI0300	45MHz 2pole 15KHz bandwidth	6.00
FRC	ERXF-15700	20.6MHz 36KHz wide	10.00
FILTECH	2131	CF 7.825MHz	10.00

\*\*\*\*\*

### CERAMIC FILTERS

AXEL	4F449	12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.4KHz	10.00
CLEVITE	TO-01A	455KHz+2KHz bandwidth 4-7% at 3dB	5.00
	TCF4-12D36A	455KHz+1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz	10.00
MURATA	BFB455B	455KHz	2.50
	BFB455L	455KHz	3.50
	CFM455E	455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 50dB	6.65
	CFM455D	455KHz +-7KHz at 3dB, +-10KHz at 6dB, +-20KHz at 50dB	6.65
	CFR455E	455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 60dB	8.00
	CFU455B	455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at 40dB	2.90
	CFU455C	455KHz +-2KHz bandwidth +-12.5KHz at 6dB, +-24KHz at 40dB	2.90
	CFU455G	455KHz +-1KHz bandwidth +-4.5KHz at 6dB, +-10KHz at 40dB	2.90
	CFU455H	455KHz +-1KHz bandwidth +-3KHz at 6dB, +-9KHz at 40dB	2.90
	CFU455I	455KHz +-1KHz bandwidth +-2KHz at 6dB, +-6KHz at 40dB	2.90
	CFW455D	455KHz +-10KHz at 6dB, +-20KHz at 40dB	2.90
	CFW455H	455KHz +-3KHz at 6dB, +-9KHz at 40dB	2.90
	SFB455D	455KHz	2.50
	SFD455D	455KHz +-2KHz, 3dB bandwidth 4.5KHz +-1KHz	5.00
	SFE10.7MA	10.7MHz 280KHz +-50KHz at 3dB, 650KHz at 20dB	2.50
	SFE10.7MS	10.7MHz 230KHz +-50KHz at 3dB, 570KHz at 20dB	2.50
	SFG10.7MA	10.7MHz	10.00
NIPPON	LF-B4/CFU455I	455KHz +-1KHz	2.90
	LF-B6/CFU455H	455KHz +-1KHz	2.90
	LF-B8	455KHz	2.90
	LF-C18	455KHz	10.00
TOKIN	CF455A/BFU455K	455KHz +-2KHz	5.00
MATSUSHIRA	EFC-L455K	455KHz	7.00

\*\*\*\*\*

### SPECTRA PHYSICS INC. Model 088 HeNe LASER TUBES

POWER OUTPUT 1.6MW.	BEAM DIA. .75MM	BEAM DIR. 2.7MR	8KV STARTING VOLTAGE DC
68K OHM 1WATT BALLAST	1000VDC +-100VDC	At 3.7MA	\$59.99

### ROTRON MUFFIN FANS Model MARK4/MU2A1

115 VAC	14WATTS	50/60CPS	IMPEDENCE PROTECTED-F	88CFM at 50CPS	\$ 7.99
105CFM at 60CPS	THESE ARE NEW				

# MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

# "CHIPS"

## FAIRCHILD VHF AND UHF PRESCALER CHIPS

Part Number	Description	PRICE
95H90DC	350MC Prescaler divide by 10/11	\$ 8.50
95H91DC	350MC Prescaler divide by 5/6	8.50
11C90DC	650MC Prescaler divide by 10/11	15.50
11C91DC	650MC Prescaler divide by 5/6	15.50
11C06DC	UHF Prescaler 750MC D Type Flip Flop	12.30
11C05DC	1GHz Counter Divide by 4	
	(Regular price \$75.00)	50.00
11C01FC	High Speed Dual 5/4 Input NO/NOR Gate	15.40
82S90	Presetable High Speed Decade/Binary Counter used with the 11C90/91 or the 95H90/91 Prescaler can divide by 100 (Signetics)	5.00
11C24DC	This chip is the same as a Motorola MC4024/4324 Dual TTL Voltage Control Multivibrator.	3.37
11C44DC	This chip is the same as a Motorola MC4044/4344 Phase Frequency Detector.	3.37

## GENERAL ELECTRIC CO. GUNN DIODE MODEL Y-2167

Freq. Gap (GHz) 12 to 18, Output (Min.) 100mW, Duty (%) CW, Typ. Bias (Vdc) 8.0, Type. Oper. (MAdc) 550, Max. Thres. (mAdc) 1000, Max. Bias (Vdc) 10.0. **\$39.99**

## VARIAN GALLIUM ARSENIDE GUNN DIODES MODEL VSX-9201S5

Freq. Coverage 8 to 12.4GHz, Output (Min.) 100mW, Bias Voltage (Max.) 14vdc, Bias current (mAdc) Operating 550 Typ. 750 Max., Threshold 850 Typ. 1000 Max. **\$39.99**

## VARI-L Co. Inc. MODEL SS-43 AM MODULATOR

Freq. Range 60 to 150MC, Insertion Loss 13dB Nominal, Signal Port Imp. 50ohms Nominal, Signal Port RF Power + 10dBm Max., Modulation Port BW DC to 1KHZ, Modulation Port Bias 1ma. Nominal **\$24.99**

## AVANTEK CASCADABLE MODULAR AMPLIFIERS

	Model UTO-504	UTO-511
Frequency Range	5 to 500 MHz	5 to 500 MHz
Gain	6dB	15dB
Noise Figure	11dB	2.3dB to 3dB
Power Output	+ 17dB	- 2dB to - 3dB
Gain Flatness	1dB	1dB
Input Power Vdc	+ 24	+ 15
mA	100	10
PRICE	\$70.00	PRICE \$75.00

## HEWLETT PACKARD

MIXERS MODELS	10514A	10514B
Frequency Range	2MHz to 500MC	2MHz to 500MC
Input/Output Frequency L & R	200KHz to 500MC	200KHz to 500MC
X	DC to 500MC	DC to 500MC
Mixer Conversion Loss (A)	7dB	7dB
(B)	9dB	9dB
Noise Performance (SSB) (A)	7dB	7dB
(B)	9dB	9dB
PRICE	\$49.99	PRICE \$39.99

## FREQUENCY SOURCES, INC MODEL MS-74X

### MICROWAVE SIGNAL SOURCE

MS-74X: Mechanically Tunable Frequency Range (MHz) 10630 to 11230 (10.63 to 11.23GHz) Minimum Output Power (mW) 10, Overall Multiplier Ratio 108, Internal Crystal Oscillator Frequency Range (MHz) 98.4 to 104.0, Maximum Input Current (mA) 400.

The signal source are designed for applications where high stability and low noise are of prime concern. These sources utilize fundamental transistor oscillators with high Q coaxial cavities, followed by broadband stable step recovery diode multipliers. This design allows single screw mechanical adjustment of frequency over standard communications bands. Broadband sampling circuits are used to phase lock the oscillator to a high stability reference which may be either an internal self-contained crystal oscillator, external primary standard or VHF synthesizer. This unique technique allows for optimization of both FM noise and long term stability. List Price is \$1158.00 (THESE ARE NEW) **Our Price—\$289.**

## HEWLETT PACKARD 1N5712 MICROWAVE DIODE

This diode will replace the MBD101, 1N5711, 5082-2800, 5082-2835 etc. This will work like a champ in all those Down Converter projects **\$1.50 or 10/\$10.00**

## MOTOROLA MHW1172R LOW DISTORTION

### WIDEBAND AMPLIFIER MODULE.

Frequency Range. 40 to 300 MHz., Power Gain at 50MHz 16.6min. to 17.4max., Gain Flatness ± 0.1 Typ. ± 0.2 Max. dB., DC Supply Voltage - 28vdc, RF Voltage Input + 70dBmV **PRICE \$29.99**

## GENERAL ELECTRIC AA NICADS

Model #41B905HD11-G1  
Pack of 6 for \$5.00 or 60 Cells, 10 Packs for \$45.00  
These may be broken down to individual cells.

### ORDERING INSTRUCTIONS

**DEFECTIVE MATERIAL:** All claims for defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed properly or it will void all warranties.

**DELIVERY:** Orders are normally shipped within 48 hours after receipt of customer's order. If a part has to be backordered the customer is notified. Our normal shipping method is via First Class Mail or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point.

**FOREIGN ORDERS:** All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.D. is not available to foreign countries and Letters of Credit are not an acceptable form of payment either. Further information is available on request.

**HOURS:** Monday thru Saturday 9:30 a.m. to 5:00 p.m.

**INSURANCE:** Please include 25¢ for each additional \$100.00 over \$100.00. United Parcel only.

**ORDER FORMS:** New order forms are included with each order for your convenience. Additional forms are available on request.

**POSTAGE:** Minimum shipping and handling in the US, Canada, and Mexico is \$2.50 all other countries is \$5.00. On foreign orders include 20% shipping and handling.

**PREPAID ORDERS:** Order must be accompanied by a check.

**PRICES:** Prices are subject to change without notice.

**RESTOCK CHARGE:** If parts are returned to MHz Electronics due to customer error, customer will be held responsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returns must have approval.

**SALES TAX:** Arizona must add 5% sales tax, unless a signed Arizona resale tax card is currently on file with MHz Electronics. All orders placed by persons outside of Arizona, but delivered to persons in Arizona are subject to the 5% sales tax.

**SHORTAGE OR DAMAGE:** All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY  
NO INFORMATION WILL BE GIVEN 1-800-528-0180

**TERMS: DOMESTIC:** Prepaid, C.O.D. or Credit Card

**FOREIGN:** Prepaid only, U.S. Funds—money order or cashier's check only.

**C.O.D.:** Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's check. We are sorry but we cannot accept personal checks for C.O.D.

**CONFIRMING ORDERS:** We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, customers will be held responsible for any charges incurred, plus a 15% restock charge on returned parts.

**CREDIT CARDS: WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.**

**DATA SHEETS:** When we have data sheets in stock on devices we do supply them with the order.




(602) 242-3037  
(602) 242-8916  
2111 W. CAMELBACK ROAD  
PHOENIX, ARIZONA 85015

Toll Free Number  
800-528-0180  
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

**NEW**

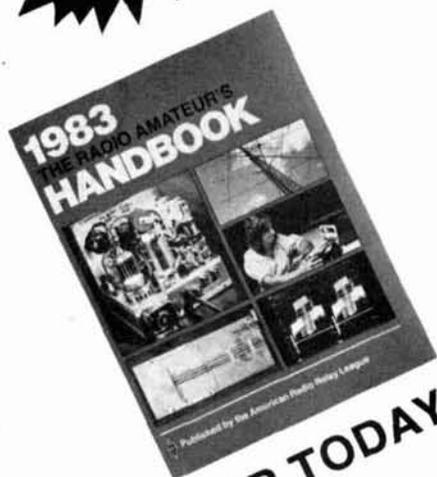

**ORDER TODAY**

# 1983 HANDBOOK

Another super edition of the standard manual of rf communication! Each year, *The Handbook* is revised to reflect changes in the state-of-the-art and this 60th edition is no exception. Expanded emphasis is given to the use of amateur satellites including RS and Phase III information. You will find computer and calculator programs for satellite tracking. There is also a new TVI troubleshooting flow chart and more coverage of amateur television. New construction projects include power supplies, 160-meter kW amplifier, deluxe voice/cw audio filter, single-band superhets, UHF signal source and dip meter plus a universal logic translator for digital communications. In 640 pages and 23 chapters, *The Handbook* presents everything from electrical laws and circuits to sophisticated communications techniques including packet radio and spread spectrum. Order your copy today! Paper edition: \$12 in the U.S., \$13 in Canada, and \$14.50 elsewhere. Cloth edition: \$17.75 in the U.S. and \$20 elsewhere. Payment must be in U.S. funds.



**GET YOUR COPY  
TODAY!**

# ANTENNA BOOK

**14th  
EDITION**

Here is the most comprehensive and up-to-date antenna book available. It's chock-full of theory and practical information and includes proven designs for: Yagis, quads, wires, verticals or the more specialized designs: Beverage, curtain arrays and fish-bone antennas. It also has a chapter that covers UHF and VHF antenna design. You'll find antennas for any kind of real estate from the apartment dweller to the true antenna farm. *The Antenna Book* covers in complete, easy-to-understand language, antenna and transmission line theory and includes the most complete explanation available of the SMITH CHART®. Finally there is a thorough discussion of the phenomena of radio wave propagation. 328 pages 14th edition. Softbound Price \$8.00 in the US. Elsewhere \$8.50 (US FUNDS). Available from your local dealer or direct from ARRL.

Please include \$1.00 per title for shipping and handling.

**THE AMERICAN RADIO RELAY LEAGUE, INC.**

**225 MAIN STREET  
NEWINGTON, CT 06111**



# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

A. C. C. 101	Butternut * 311	Grand Systems 134	Macrotronics 152	Sherwood Eng 169
Alaska Microwave 102	Bytesize Computer 311	Grove 310	Madison Elec 153	Shure Brothers 170
Alba 103	Caddell Coil 118	Hal Comm 135	Microcraft 309	Simple Simon 172
Alden Elec 104	Ceco 119	H. R. B. 188	Midan 307	Sinclair * 173
All Elec 105	Centurion 120	Hamtronics 136	Mirage 154	Snyder 173
Aluma Tower 106	Com Inter 121	N. Y. 136	Morning Dist 155	Speaker Builder 174
Amu. Radio Today 107	Comm Design 122	Health 137	NCG 156	Spectronics * 175
Ameco Equip 305	Comm. Spec 123	Hoosier 138	Nampa Satellite 157	Spectrum Int 175
ARRL 108	Commsoft 302	Icorn 139	Nensal 158	Spectrum West 176
Amp Supply 109	DGM 306	Ind. Crystal 140	N. American Soar 159	Spi Ro 177
Antenna Inc 308	Dayton * 124	Inter Crystal 141	Nuts & Volts 160	Telex * 178
Appliance & Equipment 110	Delcraft 124	JWL 142	Oak Hill Academy A. R. S. * 161	TET 178
Atlantic Surplus * 111	Doppler 125	Jan Crystals 143	P. B. Radio 161	The Comm Center 179
ATV Magazine 111	Dotronix 312	Jasco Inter 144	P. C. * 162	Tri Ex 180
Barker & Williamson 112	Elec. Spec 126	KCS Elec 145	Palomar Eng. * 162	Universal Comm 181
Barry * 113	Energy Sciences 127	KLM 146	Peterson Elec 162	Univ. Software 303
Bauman Sales 114	Eng. Consulting 128	Kantronics 147	Phillips Tech 163	UNR Rohn 182
Betts 114	Epsilon 129	Kenwood * 314	Pro Search 164	Vanguard Labs 183
Bit O Byte 115	Fertronics 130, 313	Lunar 148	RCA * 165	Varian 184
Buckmaster 116, 204	Fluke 315	MCM 301	RF Products 165	Voice of America * 185
Budwig 117	Fox Tango 131	MFJ 150	Callbook 166	Webster 185
	Galaxy 132	MHZ Elec 151	Radio School 167	Western Elec 186
	Goldsmith Scientific 133		Semi Surplus 168	Yaesu 187

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

NAME \_\_\_\_\_ CALL \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Please use before May 31, 1983

April, 1983

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

AFFIX POSTAGE  
OR  
POST OFFICE  
WILL NOT  
DELIVER

**ham**  
**radio**  
*magazine*

READER SERVICE CENTER  
P.O. BOX 358  
ARLINGTON, MA 02174

ATTN: Reader Service Dept.

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

A. C. C. .... 101	Jan Crystals .... 143
Alaska Microwave .... 102	Jasco Inter. .... 144
Albia .... 103	KCS Elec. .... 145
Alden Elec. .... 104	KLM .... 146
All Elec. .... 105	Kantronics .... 147
Aluma Tower .... 106	Kenwood *, .... 314
Ama. Radio Today .... 107	Long's .... 148
Ameco Equip. .... 305	Lunar .... 149
ARRL .... 108	MCM .... 301
Amp Supply .... 109	MFJ .... 150
Antenna Inc. .... 308	MHZ Elec. .... 151
Appliance & Equipment .... 110	Macrotechnics .... 152
Atlantic Surplus * .... 111	Madison Elec. .... 153
ATV Magazine .... 111	Microcraft .... 309
Barker & Williamson .... 112	Midian .... 307
Barry * .... 113	Mirage .... 154
Baumans Sales .... 113	Morning Dist. .... 155
Betts .... 114	NCG .... 156
Bit O Byte .... 115	Nampa Satellite .... 157
Buckmaster .... 116, 204	Nemal .... 158
Budwig .... 117	N. American Soar .... 159
Butternut * .... 118	Nuts & Volts .... 160
Bytesize Computer .... 111	Oak Hill Academy A. R. S. * .... 161
Caddell Coil .... 118	P. C. .... 110, 51
Ceco .... 119	Palomar Eng. * .... 129
Centurion .... 120	Peterson Elec. .... 162
Coin Inter. .... 121	Phillips-Tech .... 163
Comm. Design .... 122	Pro-Search .... 164
Comm. Spec. .... 123	RCA * .... 110, 51
Commsort .... 302	RF Products .... 165
DGM .... 306	Callbook .... 166
Dayton * .... 124	Radio School .... 167
Delcraft .... 124	Semi. Surplus .... 168
Doppler .... 125	Sherwood Eng. .... 169
Dotronix .... 312	Shure Brothers .... 170
Elec. Spec. .... 126	Simple Simon .... 172
Energy Sciences .... 127	Sinclair * .... 110, 51
Eng. Consulting .... 128	Snyder .... 173
Epsilon .... 129	Speaker Builder .... 174
Ferritronics .... 130, 313	Spectronics * .... 110, 51
Fluke .... 315	Spectrum Int. .... 175
Fox-Tango .... 131	Spectrum West .... 176
Galaxy .... 132	Spi-Ro .... 177
Goldsmith Scientific .... 133	Telex * .... 110, 51
Grand Systems .... 134	TET .... 178
Grove .... 310	The Comm Center .... 179
Hal Comm. .... 135	Tri-Ex .... 180
H. R. B. .... 188	Universal Comm. .... 181
Hamtronics, N. Y. .... 136, 304	Univ. Software .... 303
Heath .... 137	UNR-Rohn .... 182
Hoosier .... 138	Vanguard Labs .... 183
Icom .... 139, 205	Varian .... 184
Ind. Crystal .... 140	Voice of America * .... 113
Inter. Crystal .... 141	Webster .... 185
JWL .... 142	Western Elec. .... 186
	Yaesu .... 187

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

April 1983

Please use before May 31, 1983

Tear off and mail to  
HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048-0498

NAME .....

CALL .....

STREET .....

CITY .....

STATE ..... ZIP .....

## R-X Noise Bridge



- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less.

The price is \$59.95 in the U.S. and Canada. Add \$3.00 shipping/handling. California residents add sales tax.



Send for FREE catalog describing the R-X Noise Bridge and our complete line of SWR Meters, Preamplifiers, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

# Palomar Engineers

Box 455, Escondido, CA 92025  
Phone: (619) 747-3343


## Advertisers Index

Advanced Computer Controls	105
Alaska Microwave Labs	81
Albia Electronics	71
Alden Electronics	7
All Electronics Corp.	93
Aluma Tower Co.	115
Amateur Radio Today	103
American Radio Relay League	126
Amp Supply	115
Appliance & Equipment Company, Inc.	103
Atlantic Surplus Sales	104
ATV Magazine	113
Barker & Williamson, Inc.	110
Barry Electronics	79
Bauman, R.H. Sales Co.	81
J.S. Betts Company	31
Bit O Byte	103
Buckmaster Publishing	26, 84
Budwig Manufacturing Company	115
Butternut Electronics	113
Caddell Coil Corp.	115
Ceco	100
Centurion International	111
Coin International	93
Communications Design, Inc.	84
Communications Specialists	86
Dayton Hamvention	110
Delcraft	113
Doppler Systems	101
Electronic Specialists, Inc.	102
Energy Sciences	93
Engineering Consulting	107
Epsilon Records	107
Ferritronics Limited	109
Fox-Tango Corp.	81
Galaxy Electronics	112
Goldsmith Scientific Corporation	115
Grand Systems	114
Hal Communications Corp.	101
Ham Radio's Bookstore	93, 105, 109
Hamtronics, N.Y.	64, 65
Heath Company	48
Hoosier Electronics	105
Icom America, Inc.	Cover II, 83
Independent Crystal Supply Company	112
International Crystal	84
JWL Electronics	109
Jan Crystals	100
Jasco International	81
KCS Electronics	114
KLM Electronics, Inc.	102
Kantronics, Inc.	93
Trio-Kenwood Communications	2, Cover IV
Long's Electronics	24, 25
Lunar Electronics	85
MFJ Enterprises	9
MHZ Electronics	116-125
Macrotechnics	51
Madison Electronics	26
Mirage Communications Equipment, Inc.	21
Morning Distributing Co.	23
NCG	96
Nampa Satellite Receiver Systems	108
Nemal Electronics	102
North American Soar	1
Nuts & Volts Magazine	104
Oak Hill Academy Amateur Radio Session	112
P.B. Radio	100
P.C. Electronics	110, 51
Palomar Engineers	129
Peterson Electronics	114
Phillips-Tech Electronics	107
Pro-Search	87
RCA Government Communications Systems	45
RF Products	104
Radio Amateur Callbook, Inc.	115
Radio School	97
Semiconductors Surplus	92
Sherwood Engineering	104
Shure Brothers	44
Simple Simon Electronic Kits, Inc.	41
Sinclair Research Ltd.	130
Snyder Antennas	26
Speaker Builder	96
Spectronics	43
Spectrum International, Inc.	82
Spectrum West	81
Spi-Ro Distributing	112
Telex Communications	46, 47
TET Antennas	23
The Comm Center	99
Tri-Ex Tower Corp.	85
Universal Communications	85
UNR-Rohn	51, 104
Vanguard Labs	84
Varian, Eimac Division	11
Voice of America	113
Webster Communications, Inc.	112
Western Electronics	84
Yaesu Electronics Corp.	Cover III

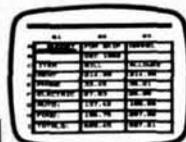
# For ZX81 or TS1000 software savings, rip off this ad.



**THE STAMP COLLECTOR (#31)** Inventory and store up to 600 SCOTT numbers in a single session showing quantity on hand, by major classification, and provide full want list support.



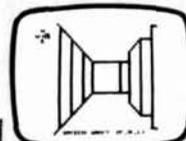**VU-CALC (#11)** This program constructs, generates, and calculates large tables for financial analysis, budget sheets, and projections. An immensely powerful analysis chart.



**SUPERMAZE (#34)** Navigate your way through a three-dimensional maze, with trapdoors, gold bars, marker stones, and compass. Ten separate mazes. Three-dimensional graphics.



**PERSONAL FINANCE PLANNER (#28)** Perform calculations, finance a house, a car, keep savings accounts, repay loans and calculate an amortization schedule which can be generated for any of the financial programs.



**SUPER MATH (#14)** Drill yourself on addition, subtraction, multiplication, and division with five levels of difficulty. Each problem graphically depicted.



**THE HOME IMPROVEMENT PLANNER (#29)** Store up to 20 room measurements (length, width, height), compute total area in each (wall, floor), estimate costs of painting, wall papering and carpets and draw house blueprints.



**STATES AND CAPITOLS (#32)** Test yourself on the fifty states and their capitols. Three options of review are available. (1) States, you provide capitols. (2) Capitols, provide states. (3) A mix of states and capitols.



**THE FLIGHT SIMULATOR (#6)** Take control of highly maneuverable light aircraft. With full controls, instrumentation and navigational aids to avoid hazards in landing.




**CHESS AND CHESS CLOCK (#7)** Six levels. All the legal moves including casting and enpassant. Keeps a separate record of plays made for easy reference. Play another opponent or match wits with the computer.




**BACKGAMMON AND DICE (#8)** A perfect blend of chance and skill. Uses machine code to choose its moves. Full game including graphics board, rolling dice, and double cube. Play the computer or another opponent.



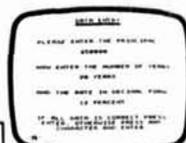**THE CUBE GAME (#9)** The cube can be displayed in three views: (1) Solid; (2) Two-Dimensional (unfolded); and (3) See-thru cube (3-D). You start with the cube solved, set it up any way you like, or pick up from a previous session.



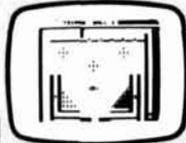**REAL ESTATE INVESTMENT ANALYSIS (#30)** Two different investment strategies. The first selection allows the user to choose between renting or buying. The second selection consists of a detailed analysis of the rental investment property.



**PINBALL (#35)** Plays like real pinball complete with flippers, bumpers, "nudge," bonus points and more. Uses fast, efficient machine code to choose its moves.




**STOCK MARKET GAME (#27)** Bull or bear? This realistic simulation lets you analyze information, buy and sell stocks, take out and pay off loans... and win, if you can accumulate \$50,000 in "The Market."



**FORTRESS OF ZORLAC (#36)** A super fast game in which you are the commander of a fleet of spaceships. Your mission is to rid the galaxy of the dreaded alien, ZORLAC.



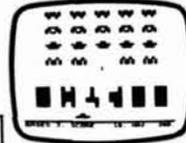**ATOR THE ABC GATOR (#33)** Designed to teach recognition and sequence of the alphabet. Combines computer instruction, music and video games.



**SPACE RAIDERS, BOMBER (#5)** Timex/Sinclair version of the popular arcade games full of bombs and rockets and collisions with skyscrapers.



**FROGGER (#37)** Plays like the arcade game. Hop the frog over traffic, snakes, crocodiles, and treacherous diving turtles before time runs out.

Sinclair, the company that invented the world's most affordable computer, has invented a way for you to order the most affordable software—right from your home!

You've never had this wide a selection before. You can play games that challenge you, instead of bore you. You can learn new household applications and business programs that reduce work dramatically.

Only Sinclair offers this special software savings. Only ZX81 or Timex TS1000 owners are eligible.

**The more you buy, the more you save. A serious Sinclair software offer.**

The first cassette you buy, you buy at normal cost: \$15.00. But every cassette thereafter, you get at a savings.

The list below explains how much you save, based on how much you buy. It couldn't be easier.

You were smart to buy the ZX81 or the TS1000. You'll be even smarter to take us on this software offer. All cassettes listed at left work on both the ZX81 and the TS1000. All cassettes are 16K, which means you need the 16K Memory Module. (If you want more information on this component, please write Sinclair at the address listed below.)

But don't delay. This is a limited time software offer while supplies last.

**How to order today!**

Just call our toll-free number and use your MasterCard or VISA. Or send this ad with a check or money order. It's as easy as that.

Call toll-free: 800-543-3000. Ask for operator 509. In Canada call 513-729-4300, operator 509. Have your MasterCard or VISA ready when calling. Phones open 24 hours a day, 7 days a week. These numbers are for orders only.

If you simply want information, please don't call, write Sinclair Research, Ltd., 2 Sinclair Plaza, Nashua, NH 03061.

(Sorry, no refunds on software. Defective cassettes will be replaced.)

**Call toll free**

**800-543-3000**

(operator 509)

Ad. code: B4HR Mail to: Sinclair Research, Ltd.  
One Sinclair Plaza, Nashua, NH 03061

Check the boxes of all cassettes you want at left.  Check or money order enclosed.

Fill in the space beside total for your total payment

- 1 cassette: \$15.00
- 2 cassettes: \$25.00 (save \$5.00)
- 3 cassettes: \$35.00 (save \$10.00)
- 4 cassettes: \$45.00 (save \$15.00)
- 5 cassettes: \$50.00 (save \$25.00)
- 6 cassettes or more: \$10.00 each \$

Plus Shipping/Handling \$5.00

Total:

U.S. Dollars

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

**sinclair**

\*Sinclair technology is the heart of both the ZOR and the Timex/Sinclair 1000.

# FT-77 The Rig for All Seasons!

Answering the call for an HF rig that goes everywhere, sounds great, and is cost-effective, Yaesu proudly introduces the FT-77 Compact HF Transceiver System.



## Computerized Design and Manufacture

The FT-77 design engineers utilized the latest computerized circuit board layout methods, resulting in a compact, reliable transceiver with maximum utilization of available space. Automated insertion techniques are used in assembly, providing improved reliability and quality control over earlier designs.

## Operating Versatility

The FT-77 is equipped for operation on all amateur bands between 3.5 and 29.7 MHz, including the three new WARC bands. Fully operational on SSB and CW, the FT-77 includes a dual width noise blanker (designed to minimize the "Woodpecker" or ignition noise), full SWR metering, R.I.T., and optional CW filter with wide/narrow selection. The optional FM-77 permits operation on the FM mode, with front panel squelch sensitivity control.

## Expandable Station Concept

Ideal for mobile operation because of its compact size and light weight, the FT-77 forms the nucleus of a versatile base station. Available as options for the FT-77 are the FP-700 AC Power Supply, FV-700DM Synthesized External VFO and Memory System, FTV-707 VHF/UHF Transverter, and FC-700 Antenna Coupler, providing top performance at an extraordinarily low price.

## Best of All, It's a Yaesu!

With most experience in transceiver design and manufacture, the Yaesu trademark is your guarantee of quality and durability. We've got all-new technology and an all-new warranty policy to back it up.

See the FT-77 and the all new line of Yaesu HF, VHF, and UHF transceivers, receivers and accessories at your Yaesu Dealer today! *It's time you tried a Yaesu!*

Price And Specifications Subject To  
Change Without Notice Or Obligation

✓ 187

**YAESU**  
*The radio.*



0283

YAESU ELECTRONICS CORPORATION, 6851 Walthall Way, Paramount, CA 90723 ● (213) 633-4007  
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45146 ● (513) 874-3100

# NEW

# Digital DX-terity...



**General coverage, Superior dynamic range, 2 VFO's, 8 memories, Scan, Notch... COMPACT!**

## TS-430S

The TS-430S combines the ultimate in compact styling with advanced circuit design and performance. An all solid-state SSB, CW, and AM transceiver, with FM optional, covering the 160-10 meter Amateur bands, it also incorporates a 150 kHz-30 MHz general coverage receiver having a superior dynamic range, dual digital VFO's, 8 memories, memory scan, programmable band scan, IF shift, notch filter, all-mode squelch, and built-in speech processor.

### TS-430S FEATURES:

- **160-10 meter operation, with general coverage receiver**  
With 160-10 meter Amateur band coverage, including WARC 30, 17, and 12 meter bands, it also features a 150 kHz-30 MHz general coverage receiver. Innovative UP-conversion digital PLL circuit, for superior frequency stability and accuracy. UP/DOWN band switches for Amateur bands or 1-MHz steps across entire 150 kHz-30 MHz range. Two digital VFO's continuously tuneable from band to band. Band information output on rear panel.
- **USB, LSB, CW, AM, with optional FM**  
Operates on USB, LSB, CW, and AM, with optional FM, internally installed. AGC time constant automatically selected by mode.
- **Compact, lightweight design**  
Measures only 10-5/8 (270) W x 3-3/4 (96) H x 10-7/8 (275) D, inches (mm), weighs only 14.3 lbs. (6.5 kg.).
- **Superior receiver dynamic range**  
Use of 2SK125 junction-type FET's in the Dyna-Mix high sensitivity, balanced, direct mixer circuit provides superior dynamic range.
- **10-Hz step dual digital VFO's**  
10-Hz step dual digital VFO's operate independently, include band and mode information. Different band and mode cross-operation possible. Dial torque adjustable. STEP switch for tuning in 10-Hz or 100-Hz steps. A=B switch quickly shifts "B" VFO

to the same frequency and mode as "A" VFO, or vice-versa. VFO LOCK switch provided. RIT control tunes VFO or memory. UP/DOWN manual scan possible using optional microphone.

- **Eight memories store frequency, mode, and band data**  
Memories store frequency, mode, and band data. Eighth memory stores receive and transmit frequencies independently. M.CH switch for operation of memory as independent VFO, or fixed frequency.
- **Lithium battery memory back-up**  
Estimated five-year life.
- **Memory scan**  
Scans memories in which data is stored.
- **Programmable automatic band scan**  
Scans programmed band width. Scan speed adjustable. HOLD switch interrupts band or memory scan.
- **IF shift circuit for minimum QRM.**  
IF passband may be moved to place interfering signals outside the passband, for best interference rejection.
- **Tuneable notch filter built-in**  
Deep, sharp, tuneable, audio notch filter.
- **Narrow-wide filter selection**  
NAR-WIDE switch for IF filter selection on SSB, CW, or AM, when optional filters are installed. (2.4 kHz IF filter built-in.)
- **Speech processor built-in**  
Improves intelligibility, increases average "talk-power".
- **Indicating tube digital display**  
Indicates frequency to 100 Hz (10 Hz modifiable).

- **All solid-state technology**  
Input rated 250 W PEP on SSB, 200 W DC on CW, 120 W on FM (optional), 60 W on AM. Built-in cooling fan, multi-circuit final protection. Operates on 12 VDC, or 120 VAC, or 220/240 VAC with optional PS-430 AC power supply.

- **All-mode squelch circuit, built-in**
- **Noise blanker, built-in**
- **RF attenuator (20 dB)**
- **Vox circuit, plus semi break-in with side-tone**

### Optional accessories:

- PS-430 compact AC power supply.
- PS-30 or KPS-21 AC power supplies.
- SP-430 external speaker.
- MB-430 mobile mounting bracket.
- AT-130 compact antenna tuner, 80-10 m incl. WARC.
- AT-230 base antenna tuner, 160-10 m incl. WARC.
- FM-430 FM unit.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filters.
- YK-88SN (1.8 kHz) narrow SSB filter.
- YK-88A (6 kHz) AM filter.
- MC-42S UP/DOWN hand microphone.
- MC-60A deluxe desk microphone, UP/DOWN switch.

More information on the TS-430S is available from all authorized dealers of Trio-Kenwood Communications, 1111 Walnut Street, Compton, California 90224

# KENWOOD

...pacesetter in amateur radio



Specifications and prices are subject to change without notice or obligation