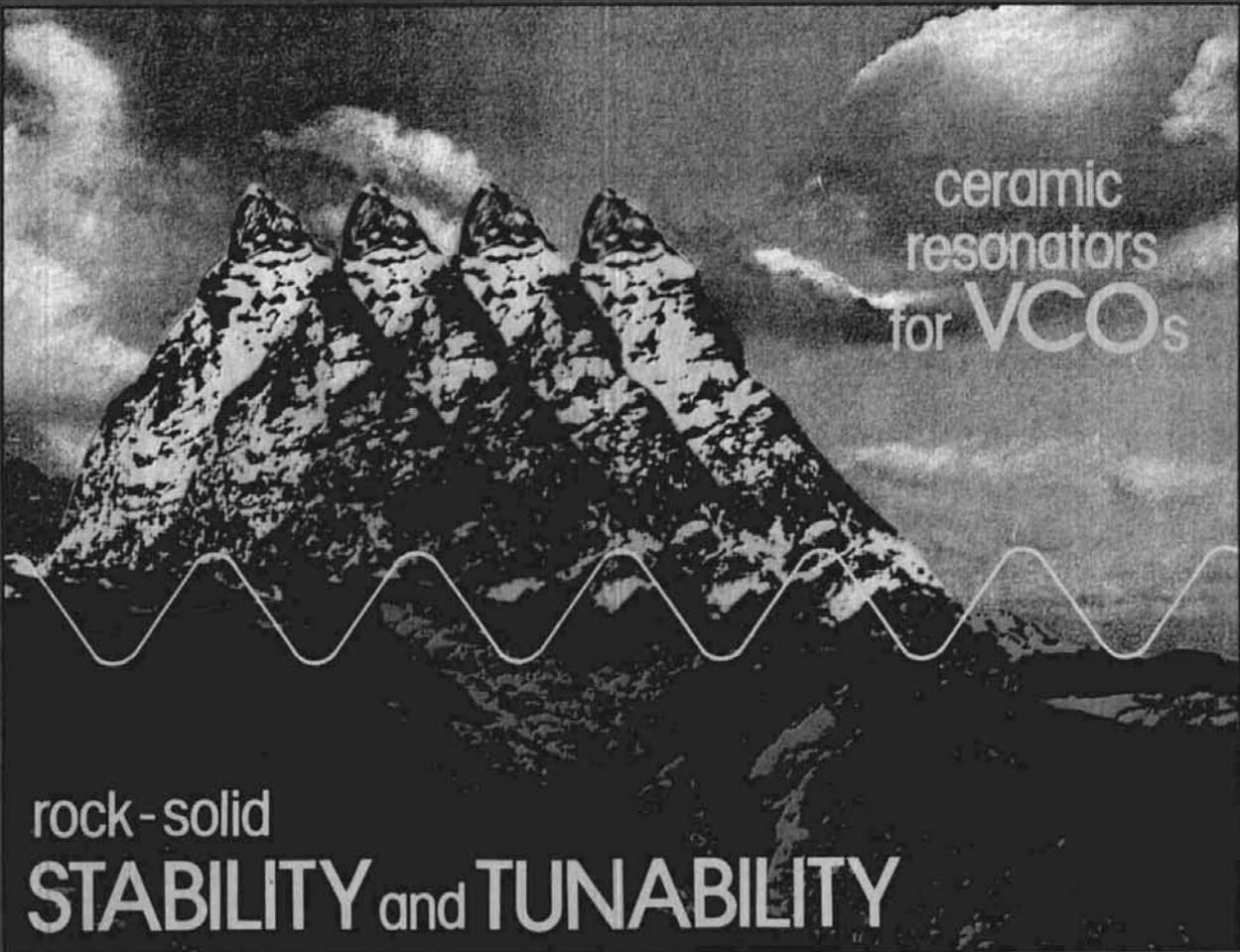


ham radio

magazine



ceramic
resonators
for VCOs

rock-solid

STABILITY and **TUNABILITY**


hrc
focus
on
communications
technology

in this issue: high-stability receiver BFO • compact IF sweep generator • graphical selection of mixer frequencies • speed up your code • designing Yagis with the C-64 • inexpensive elevation indicator • automatic temperature control • wind your own transformers — inexpensively • plus W6SAI, W1JR, KØRYW, and the Guerri report

NEW!

ICOM HF Transceiver

IC-735

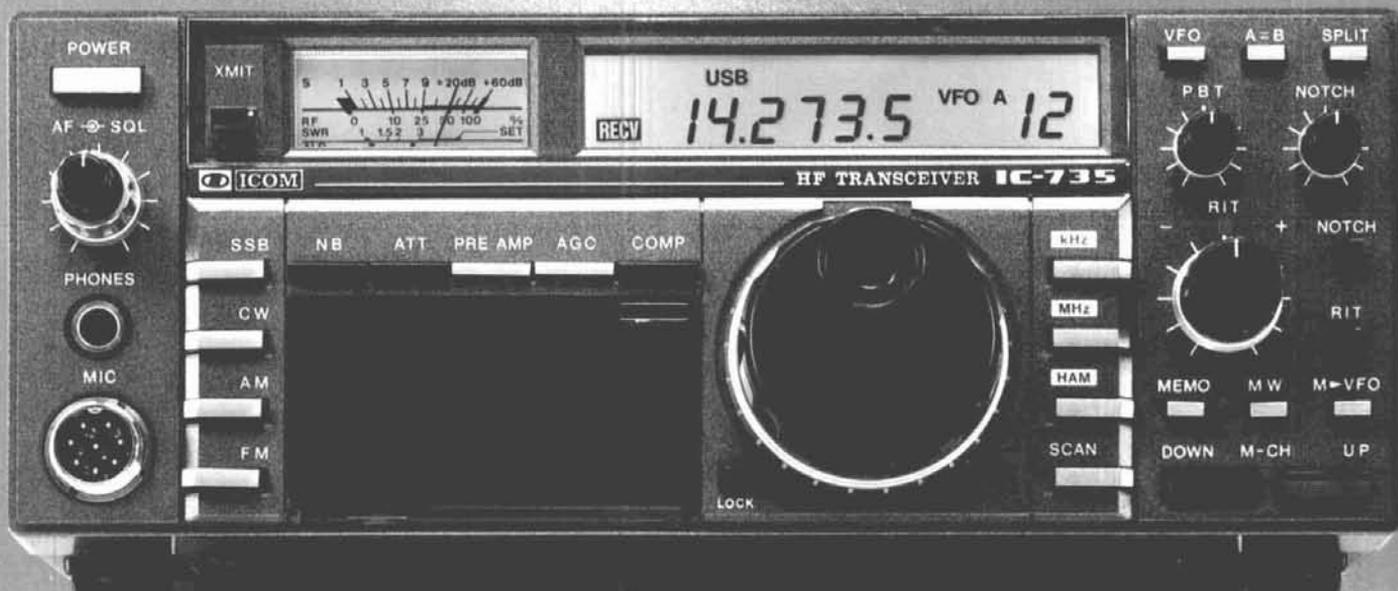

Ultra Compact

The new ICOM IC-735 is what you've been asking for...the most compact and advanced full-featured HF transceiver with general coverage receiver on the market. Measuring only 3.7 inches high by 9.5 inches wide by 9 inches deep, the IC-735 is well suited for mobile, marine or base station operation.

More Standard Features

Dollar-for-dollar the IC-735 includes more standard features...FM built-in, an HM-12 scanning mic, FM, CW, LSB, USB, AM transmit and receive, 12 tunable memories and lithium memory backup, program scan, memory scan, switchable AGC, automatic SSB selection by band, RF speech processor, 12V operation, continuously adjustable output power up to 100 watts, 100% duty cycle and a deep tunable notch.

Superior Performance

It's a high performer on all the ham bands, and as a general coverage receiver, the IC-735 is exceptional. The IC-735 has a built-in receiver attenuator, preamp and noise blanker to enhance receiver performance. PLUS it has a 105dB dynamic range and a new low-noise phase locked loop for extremely quiet rock-solid reception.

Simplified Front Panel

The large LCD readout and conveniently located controls enable easy operation, even in the mobile environment. Controls which require rare adjustments are placed behind a hatch cover on the front panel of the radio. VOX controls, mic gain and other seldom used controls are kept out of sight, but are immediately accessible.



Options. A new line of accessories is available, including the AT-150 electronic, automatic antenna tuner and the switching PS-55 power supply. The IC-735 is also compatible with most of ICOM's existing line of HF accessories.

See the IC-735 at your authorized ICOM dealer. For superior performance and innovative features at the right price look at the ultra compact IC-735.

101



First in Communications

What To Look For In A Phone Patch

The best way to decide what patch is right for you is to first decide what a patch should do. A patch should:

- Give complete control to the mobile, allowing full break in operation.
- Not interfere with the normal operation of your base station. It should not require you to connect and disconnect cables (or flip switches!) every time you wish to use your radio as a normal base station.
- Not depend on volume or squelch settings of your radio. It should work the same regardless of what you do with these controls.
- You should be able to hear your base station speaker with the patch installed. Remember, you have a base station because there are mobiles. ONE OF THEM MIGHT NEED HELP.
- The patch should have standard features at no extra cost. These should include programmable toll restrict (dip switches), tone or rotary dialing, programmable patch and activity timers, and front panel indicators of channel and patch status.

ONLY SMART PATCH HAS ALL OF THE ABOVE.

Now Mobile Operators Can Enjoy An Affordable Personal Phone Patch. . .


- Without an expensive repeater.
- Using any FM transceiver as a base station.
- The secret is a SIMPLEX autopatch, The SMART PATCH.

SMART PATCH Is Easy To Install

To install SMART PATCH, connect the multicolored computer style ribbon cable to mic audio, receiver discriminator, PTT, and power. A modular phone cord is provided for connection to your phone system. Sound simple? . . . IT IS!

With SMART PATCH You are in CONTROL

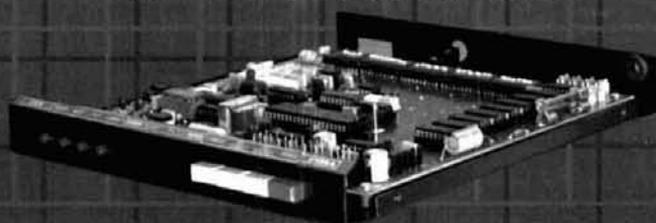With CES 510SA Simplex Autopatch, there's no waiting for VOX circuits to drop. Simply key your transmitter to take control.



SMART PATCH is all you need to turn your base station into a personal autopatch. SMART PATCH uses the only operating system that gives the mobile complete control. Full break-in capability allows the mobile user to actually interrupt the telephone party. SMART PATCH does not interfere with the normal use of your base station. SMART PATCH works well with any FM transceiver and provides switch selectable tone or rotary dialing, toll restrict, programmable control codes, CW ID and much more.

To Take CONTROL with Smart Patch - Call 800-327-9956 Ext. 101 today.


How To Use SMART PATCH

Placing a call is simple. Send your access code from your mobile (example: *73). This brings up the Patch and you will hear dial tone transmitted from your base station. Since SMART PATCH is checking about once per second to see if you want to dial, all you have to do is key your transmitter, then dial the phone number. You will now hear the phone ring and someone answer. Since the enhanced control system of SMART PATCH is constantly checking to see if you wish to talk, you need to simply key your transmitter and then talk. That's right, you simply key your transmitter to interrupt the phone line. The base station automatically stops transmitting after you key your mic. SMART PATCH does not require any special tone equipment to control your base station. It samples very high frequency noise present at your receiver's discriminator to determine if a mobile is present. No words or syllables are ever lost.

SMART PATCH Is All You Need To Automatically Patch Your Base Station To Your Phone Line.

Use SMART PATCH for:

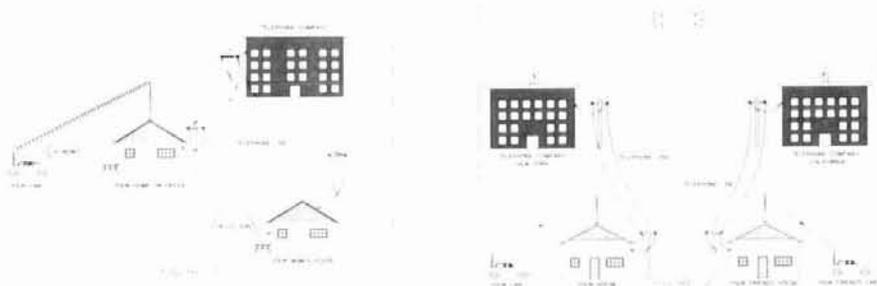- Mobile (or remote base) to phone line via Simplex base. (see fig. 1.)
- Mobile to Mobile via interconnected base stations for extended range. (see fig. 2.)
- Telephone line to mobile (or remote base).
- SMART PATCH uses SIMPLEX BASE STATION EQUIPMENT. Use your ordinary base station. SMART PATCH does this without interfering with the normal use of your radio.



Communications Electronics Specialties, Inc.
P.O. Box 2930, Winter Park, Florida 32790
Telephone: (305) 645-0474 Or call toll-free (800)327-9956

WARRANTY?

YES, 180 days of warranty protection. You simply can't go wrong. An FCC type accepted coupler is available for SMART PATCH.

KENWOOD

...pacesetter in Amateur radio

“Digital DX-terity!”



TS-430S

Digital DX-terity—that outstanding attribute built into every Kenwood TS-430S lets you QSY from band to band, frequency to frequency and mode to mode with the speed and ease that will help you earn that dominant DX position from the shack or from the mobile!



- Covers all Amateur bands 160 through 10 meters, as well as the new 30, 17, and 12 meter WARC bands. High dynamic range, general coverage receiver tunes from 150 kHz to 30 MHz. Easily modified for HF MARS operation.
- Superb interference reduction. Eliminate QRM with the IF shift and tuneable notch filter. A noise blanker suppresses ignition noise. Squelch, RF attenuator, and RIT are also provided. Optional IF filters may be added for optimum interference reduction.

- **Reliable, all solid state design.** Solid state design permits input power of 250 watts PEP on SSB, 200 watts DC on CW, 120 watts on FM (optional), or 60 watts on AM. Final amplifier protection circuits and a cooling fan are built-in.
- **Memory channels.** Eight memory channels store frequency, mode and band data. Channel 8 may be programmed for split-frequency operation. A front panel switch allows each memory channel to operate as an independent VFO or as a fixed frequency. A lithium battery backs up stored information.
- **Programmable, multi-function scan.**
- **Speech processor built-in.**
- **Dual digital VFOs.**
- **VOX circuit, plus semi break-in with sidetone.**

Optional accessories:

- PS-430 compact AC power supply
- SP-430 external speaker
- MB-430 mobile mounting bracket
- AT-130 compact antenna tuner covers 80-10 meters, incl. WARC bands
- AT-250 automatic antenna tuner covers 160-10 meters, incl. WARC bands
- AT-230 base station antenna tuner
- FM-430 FM unit
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filters
- YK-88SN (1.8 kHz) narrow SSB filter
- YK-88A (6 kHz) AM filter
- MC-42S UP/DOWN hand mic.
- MC-60A deluxe desk mic., with UP/DOWN switch
- SW-2000 SWR/power meter
- SW-100A SWR/power/volt meter
- PC-1A phone patch
- HS-4, HS-5, HS-6, HS-7 headphones



KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

ham radio

magazine

JUNE 1985

volume 18, number 6

T. H. Tenney, Jr., W1NLB
publisher

Rich Rosen, K2RR
editor-in-chief
and associate publisher

Dorothy Rosa, KA1LBO
assistant editor

Joseph J. Schroeder, W9JUV
Alfred Wilson, W6NIF
associate editors
Susan Shorrock
editorial production

editorial review board

Peter Bertini, K1ZJH
Forrest Gehrke, K2BT
Michael Gruchalla, P. E.
Bob Lewis, W2EBS
Mason Logan, K4MT
Ed Wetherhold, W3NQN

publishing staff

J. Craig Clark, Jr., N1ACH
assistant publisher

Rally Dennis, KA1JWF
director of advertising sales

Dorothy Sargent, KA1ZK
advertising production manager

Susan Shorrock
circulation manager

Therese Bourgault
circulation

cover:
Anne Fleming

ham radio magazine is published monthly by
Communications Technology, Inc.
Greenville, New Hampshire 03048-0498
Telephone: 603-878-1441

subscription rates

United States:

one year, \$19.95; two years, \$32.95; three years, \$44.95

Canada and other countries (via surface mail):

one year, \$22.95; two years, \$41.00; three years, \$58.00

Europe, Japan, Africa (via Air Forwarding Service): one year, \$28.00

All subscription orders payable in U.S. funds, via international
postal money order or check drawn on U.S. bank

international subscription agents: page 118

Microfilm copies are available from
University Microfilms, International
Ann Arbor, Michigan 48106
Order publication number 3076

Cassette tapes of selected articles from *ham radio*
are available to the blind and physically handicapped
from Recorded Periodicals,
919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1985 by Communications Technology, Inc.
Title registered at U.S. Patent Office

Second-class postage paid
at Greenville, New Hampshire 03048-0498
and at additional mailing offices
ISSN 0148-5989

Send change of address to *ham radio*
Greenville, New Hampshire 03048-0498



contents

**18 voltage controlled oscillator
uses ceramic resonators**

Al Helfrick, K2BLA

**28 a high-stability BFO
for receiver applications**

Peter Bertini, K1ZJH

35 a compact IF sweep generator

Hans Evers, PA0CX/DJ0SA

**41 graphical selection
of mixer frequencies**

G. Timothy Anderson, W2HVN

45 Morse code computer tutor

Lawrence G. Souder, N3SE

51 ham radio techniques

Bill Orr, W6SAI

**59 designing Yagis
with the Commodore 64**

Alan Hoffmaster, WA3EKL

**67 the weekender:
an inexpensive elevation indicator**

George Chaney, W5JTL

75 automatic temperature control

Douglas Rowlett, WB5IRI

83 VHF/UHF world

Joe Reisert, W1JR

**96 wind your own transformers —
inexpensively**

C.F. Hooper, W4GDW

125 the Guerri report

Ernie Guerri, W6MGI

**126 advertisers index
and reader service**

12 comments

102 DX forecaster

118 flea market

112 ham mart

117 ham notes

120 new products

9 presstop

4 reflections

117 short circuits

REFLECTIONS

our own miniseries

Anyone who watches TV has seen, I'm sure, at least one miniseries — be it *The Thorn Birds*, *Wallenberg*, or *SPACE*. Well, *ham radio* is pleased to bring you another. . . but with this one, happily, you won't have to wait until the next evening to see the continuation. We call it "sources for everyone."

Sources are popular items for Radio Amateurs. In fact, I defy you to show me a transmitter or transceiver that doesn't have at least one. In this issue we examine three different kinds of sources, each useful in its own way and each simple enough to be built by the "average" ham (whoever he may be).

Our first source — described in Al Helfrick's article, beginning on page 18 — answers the paradoxical question, What is rock-stable, yet varies in frequency? It's a voltage-controlled oscillator that uses a ceramic resonator for the frequency determining element. To say it's as stable as a crystal oscillator would be an exaggeration, but it does offer a significant improvement in stability over a conventional LC type device. Throw in the additional advantages of low microphonics, high Q , low cost in a small package, and you begin to get an idea of why both the author and I are interested in this device. Though it can be varied in frequency, its variation is limited by the series and parallel resonant frequencies of the resonator, which is about 7 percent. (Not bad considering the insignificant frequency pulling capability of a crystal oscillator.)

If we do need that high stability, Peter Bertini shows us how we can achieve it by using two crystal oscillators in a Colpitts configuration. The author, in designing BFO circuits, found an alternative to using expensive BFO crystals while still retaining the versatility of a variable BFO. In this application (a receiver BFO), very little frequency shift is needed, and it's nicely achieved by varying the voltage on the varactor elements. The difference frequency of the two crystals becomes the exact center of the variable frequency range needed. Tie that concept in with normal good oscillator design practices and we're left with a useful circuit that's inexpensive and quite stable.


The conclusion of this miniseries came out of a need for a simple and practical sweep generator that can be swept across a broad frequency range, yet still exhibit good linearity and constant output. From the Netherlands comes an article by Hans Evers, who discovered an old circuit — described perhaps for the first time — in a 1949 issue of *Wireless World*. The circuit, known as the Butler oscillator, is varied in frequency through control of an out-of-phase RF current that excites a (secondary) coil coupled to the main inductive element, thereby producing an effective turns cancellation. This current, in turn, is controlled through the unbalancing of a differential amplifier. All in all, an interesting technique.

If you like this miniseries, let us know we'll be glad to bring you others. What subjects would you like us to cover?

Rich Rosen, K2RR
Editor-in-Chief

NEW FROM MFJ

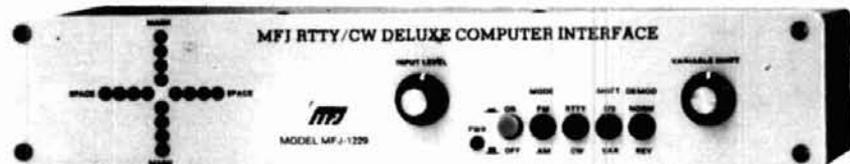MFJ'S MOST ADVANCED RTTY/ASCII/AMTOR/CW COMPUTER INTERFACE HAS FM, AM MODES, LED TUNING ARRAY, RS-232 INTERFACE, VARIABLE SHIFT TUNING, 170/850 Hz TRANSMIT, MARK-SPACE DETECTION.



MFJ RTTY/ASCII/CW software on tape, cables for C-64/VIC-20.

MFJ-1229
\$ **179.95**

Engineering, performance, value and features sets MFJ's most advanced RTTY/ASCII/

AMTOR/CW computer interface apart from others. **FM (limiting) mode** gives easy, trouble-free operation. Best for general use, off-shift copy, drifting signals, and moderate signal and QRM levels.

AM (non-limiting) mode gives superior performance under weak signal conditions or when there are strong nearby stations.

Crosshair mark-space LED tuning array simulates scope ellipse for easy, accurate tuning even under poor signal-to-noise conditions. Mark and space outputs for true scope tuning.

Transmits on both 170 Hz and 850 Hz shift.

Built-in RS-232 interface, no extra cost.

Variable shift tuning lets you copy any shift between 100 and 1000 Hz and any speed (5-100 WPM RTTY/CW and up to 300 baud ASCII). Push button for 170 Hz shift.

Sharp multi-pole mark and space filters give true mark-space detection. Ganged pots give space passband tuning with constant bandwidth. Factory adjusted trim pots for optimum filter performance.

Multi-pole active filters are used for pre-limiter, mark, space and post detection filtering. Has automatic threshold correction. This advanced design gives good copy under QRM, weak signals and selective fading.

Has front panel sensitivity control.

Normal/Reverse switch eliminates retuning while checking for inverted RTTY. Speaker jack +250 VDC loop output.

Exar 2206 sine wave generator gives phase continuous AFSK tones. Standard 2125 Hz mark and 2295/2975 Hz space. Microphone lines: AFSK out, AFSK ground, PTT out and PTT ground.

FSK keying for transceivers with FSK input. **Has sharp 800 Hz CW filter**, plus and minus CW keying and external CW key jack.

Kantronics software compatible socket.

Exclusive TTL/RS-232 general purpose socket allows interfacing to nearly any personal computer with most appropriate software. Available TTL/RS-232 lines: RTTY demod out, CW demod out (TTL only), CW-ID in, RTTY in, PTT in, key in. All signal lines are buffered and can be inverted using an internal DIP switch.

Metal cabinet. Brushed aluminum front. 12 1/2 x 2 1/2 x 6 inches. 18 VDC or 110 VAC with optional AC adapter, MFJ-1312, \$9.95.

Plugs between rig and C-64, VIC-20, Apple, TRS-80C, Atari, TI-99 and other personal computers. Use MFJ, Kantronics, AEA and other RTTY/ASCII/AMTOR/CW software.

MFJ MULTI-FUNCTION TUNING INDICATOR MFJ-1221 \$79.95



Greatly improve your RTTY copying capabilities. Add a crosshair LED Tuning Indicator that makes tuning quick, easy with pin-point accuracy. Add mark and space outputs for scope tuning. Add LEDs that indicate 170, 425, 850 Hz shifts. Great for copying RTTY outside ham bands. Add sharp mark and space filters to improve copy under crowded/weak conditions. 170, 425, 850 Hz shifts. Add Normal/Reverse switch to check for inverted RTTY without retuning. Add output level control to adjust signal into your terminal unit. Add a limiter to even out signal variation for smoother copy. Unit plugs between your tuner and receiver. Mark is 2125 Hz, space is 2295, 2550 or 2975 Hz. Measures 10x2x6 in. and uses floating 18 VDC or 110 VAC with AC adapter, MFJ-1312, \$9.95.

24/12 HOUR CLOCK/ID TIMER MFJ-106 \$19.95

Switch to 24 hour UTC or 12 hour format! Battery backup. ID timer alerts every 9 minutes after reset. Red .6 in. LEDs. Synchronizable to WWW. Alarm, Snooze function. PM, alarm on indicators. Gray/Black cabinet. 110 VAC, 60 Hz.



MFJ ELECTRONIC KEYS MFJ-407 \$69.95



MFJ-407 Deluxe Electronic Keyer sends iambic, automatic, semi-auto or manual. Use squeeze, single lever or straight key. Plus/minus keying. 8 to 50 WPM. Speed, weight, tone, volume controls. On/Off, Tune, Semi-auto switches. Speaker. RF proof. 7x2x6 inches. Uses 9 V battery, 6-9 VDC or 110 VAC with AC adapter, MFJ-1305, \$9.95.

MICROPHONE EQUALIZER MFJ-550 \$49.95



Greatly improves transmitted SSB speech for maximum talk power. Evens out speech peaks and valleys due to voice, microphone and room characteristics that make speech hard to understand. Produces cleaner, more intelligible speech on receiving end. Improves mobile operation by reducing bassy peaks due to acoustic resonances. Plugs between mic and rig. 4 pin mic jack, shielded output cable. High, mid, low controls provide ±12 db boost or cut at 490, 1170, 2800 Hz. Mic gain, on/off/bypass switch. "On" LED. 7x2x6 inches. 9 V battery, 12 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.

MFJ ANTENNA BRIDGE MFJ-204 \$79.95

Trim your antenna for optimum performance quickly and easily. Read antenna resistance up to 500 ohms. Covers all ham bands below 30 MHz. Measure resonant frequency of antenna. Easy to use, connect antenna, set frequency, adjust bridge for meter null and read antenna resistance. Has frequency counter jack. Use as signal generator. Portable, self-contained. 4x2x2 in. 9 V battery or 110 VAC with adapter, MFJ-1312, \$9.95.



MFJ PORTABLE ANTENNA MFJ-1621 \$79.95

MFJ's Portable Antenna lets you operate 40, 30, 20, 15, 10 meters from apartments, motels, camp sites, vacation spots, nearly any electrically clear location where space for a full size antenna is a problem.

A telescoping whip (extends to 54 in.) is mounted on self-standing 5 1/2 x 6 1/4 x 2 1/4 inch Phenolic case. Built-in antenna tuner. Field strength meter. 50 feet RG-58 coax. Complete multi-band portable antenna system that you can use nearly anywhere. Up to 300 watts PEP.



MFJ 24 HOUR LCD CLOCKS

\$19.95 MFJ-108 **\$9.95 MFJ-107**



Huge 5/8 inch bold black LCD numerals make these two 24 Hour clocks a must for your shack. Choose from a dual clock that features separate UTC and local time display or a single clock that displays 24 Hour time. **Mounted in a brushed aluminum frame**, these clocks feature huge 5/8 inch LCD numerals and a sloped face for across the room viewing. Easy set month, day, hour, minute and second function. Clocks can be operated in an alternating time-date display mode. MFJ-108, 4 1/2 x 1 x 2 inches; MFJ-107, 2 1/4 x 1 x 2 inches. Battery included.

MFJ

MFJ ENTERPRISES, INC.
Box 494, Mississippi State, MS 39762

TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE
800-647-1800. Call 601-323-5869 in Miss. and outside continental USA.
Telex 53-4590 MFJ STKV



ICOM HF Transceiver

IC-751



Reach Out To Your Friends With The IC-751

Here's what other hams have to say about the "dream rig."

"To put it concisely, the IC-751 easily meets all of its advertised claims with regard to technical specifications."

"The filters used on the IC-751 are about the sharpest one can imagine."

"It performed flawlessly over the entire period. Particularly if the IC-751 is used with an internal power supply, it has to be regarded as the most compact, full-featured transceiver available for either fixed station or portable operation."

John J. Schultz W4FA
CQ Magazine
September 1984

"...we seriously doubt anyone finding a unit superior to ICOM's new 751 HF 'dream rig.'"

Dave Ingram K4TWJ
Computer Trader Magazine
September 1984

"The general-coverage receiver is excellent."

Mark Wilson AA2Z
QST Magazine
January 1985

"The Notch measured 55dB, and is the best ICOM Notch yet."

"The stability of the 751 deserves mention. We measured 10Hz drift in the first hour."

Robert Pohorence NBRT
International Radio, Inc.
September 1983

Now with a ONE YEAR Warranty!



First in Communications

IC-02AT

ICOM 2-Meter Handhelds

If you want a 2-meter handheld with exceptional features, quality built to last and a wide variety of interchangeable accessories, take a look at the ICOM IC-02AT and IC-2AT handhelds.

Frequency Coverage. The IC-02AT covers 140.000 through 151.550MHz and the IC-2AT, 141.500 through 149.994MHz...both include frequencies for MARS operation.

IC-02AT Features. ICOM's top-of-the-line IC-02AT handheld has the following outstanding features:

- DTMF direct keyboard entry
- LCD readout
- 3 watts standard, 5 watts optional (with IC-BP7 battery pack)
- 10 memories which store duplex offset and PL tone (odd offset can be stored in last 4 memories)
- Frequency dial lock
- Three scanning systems: priority, memory and programmable band scan (selectable increments of 5, 10, 15, 20 or 25KHz)

IC-2AT Features. The IC-2AT is ICOM's most popular handheld on the market. The IC-2AT features a DTMF pad, 1.5 watts output and thumbwheel frequency selec-

tion. The IC-2A is also available and has the same features as the IC-2AT except DTMF.



Accessories. A variety of slide-on battery packs are available for the IC-02AT and IC-2AT, including the new long-life 800mAh IC-BP8 which can be used with both handhelds.

Other accessories include the HS-10 boom headset, HS-10SB PTT switchbox, HS-10SA VOX unit (for IC-02AT) and an assortment of battery pack chargers.

The IC-02AT and IC-2AT come standard with an IC-BP3 NiCd battery pack, flexible antenna, AC wall charger, belt clip, wrist strap and ear plug. See the IC-02AT and IC-2AT 2-meter handhelds at your local ICOM dealer.

Often imitated,
never duplicated.



ICOM

First in Communications



When the FCC changed the rules, EIMAC was prepared for continuing HAM operations.

The FCC changed the allowable output power for linear amplifiers in amateur radio service. Hams can now run at 1500 watts PEP into an antenna. EIMAC was right there to meet requirements with its 3CX1200A7 tube.

Low-cost replacement for small spaces.

RF cabinets of many linear amplifiers currently use the EIMAC 3-500-Z tubes. The new 3CX1200A7 for design takes size into consideration and, by design, is recommended as a single, low-cost replacement for a pair of EIMAC 3-500-Z tubes for new amplifier designs.

General Specifications

The EIMAC 3CX1200A7 is a high- μ , compact, forced air cooled triode for zero-bias class AB2 amplifiers.

- 2.9" dia. x 6.0" long
- Plate dissipation: 1200 watts
- Glass chimney SK-436 available
- Standard EIMAC SK-410 socket available

More information is available on the new EIMAC 3CX1200A7 tube from Varian EIMAC, or any Electron Device Group worldwide sales organization.

Varian EIMAC
1678 S. Pioneer Road
Salt Lake City, Utah 84104
Telephone: 801 • 972-5000

Varian AG
Steinhauserstrasse
CH-6300 Zug, Switzerland
Telephone: 042 • 23 25 75



presstop de W9JUV

AMATEUR RADIO WILL FLY WITH THE SPACE SHUTTLE IN JULY after all, NASA has announced. However, astronaut Tony England, WØORE, will be limited to 2-meter operation only, as the installation of additional Amateur antennas for other bands in the shuttle's payload bay turned out to be too costly as well as a logistically difficult task.

Slow-Scan TV Is The Big Addition On This Shuttle Flight; it's even quite likely that SSTV transmission time will exceed that for voice, with scenes from inside the spacecraft to be sent during orbits when WØORE is busy with other tasks and can't be on the air for voice contacts. Both FM voice and SSTV will be via 2-meter hand-held radios, using the same window-mount antenna used by W5LFL in his pioneering operation.

Little If Any "General" 2-Way Operation Is Planned for this flight. Instead, WØORE's contact emphasis will be with school and club groups, to provide the maximum Amateur involvement. The ARRL will act as liaison to schedule such contacts; contact them in Newington for details. Pre-flight publicity and media contact during the flight will also be handled by the ARRL, but primarily through the League's Washington office.

NASA Expects WØORE To Be On For Between 10 And 20 Passes, and is currently working out his scheduling. A principal limitation will be access to the shuttle's overhead window, which won't be available at all for Amateur antenna use until the middle of the fourth day of the flight. At presstime launch was still scheduled for mid-July.

THE 24-MHZ BAND WILL BECOME AVAILABLE AND 30 METERS "OFFICIAL" JUNE 22, the FCC decided April 25. The new 24890-24990 kHz slot is for General and higher, with phone above 24930; power will be 1500 W PEP. 30 meters remains CW/RTTY only, General and above limited to 200 W PEP. No action was taken on 420 MHz changes or the new 902 MHz band.

International Broadcast Stations May Use 7.1-7.3 MHz In Region 3 (Pacific) areas it administers, the FCC decided April 4. In its Report and Order on Mass Media Docket 84-706 the Commission did specify, however, that broadcast stations operating under the new ruling must beam transmissions away from Region 2. The effective date was May 16.

Expanded 40-Meter Phone Privileges For Caribbean Area Amateurs are proposed in a new FCC Notice of Proposed Rulemaking. In PR Docket 85-104 Amateurs in U.S.-licensed areas of the Caribbean would have their phone band extended down to 7075 kHz; in its proposal the FCC is looking for Amateur input on how the additional frequencies should be utilized.

Comments On PR Docket 85-104 Are Due At The FCC June 17; Reply Comments July 17.

VOLUNTEER EXAMINER COORDINATOR PERFORMANCE MAY SOON be the subject of critical FCC review, now that the program has been on line for a year. Criteria to be used in the review will probably include activity, pass rates, adherence to the rules, integrity, and quality of the paperwork provided to Gettysburg. Some VECs are not expected to fare very well.

A Visit To Gettysburg For VEC Representatives is also being considered, probably for sometime in August. Such a visit would provide the VECs and FCC licensing people an excellent opportunity to discuss each other's problems and review procedures.

DeVry Is Actively Seeking VEs Throughout The U.S., following its accreditation as a national VEC. Interested VEs should call Jim Georgius, W9JUG, at DeVry between 12 noon and 7 PM Chicago time, at (312) 929-8500, ext. 251.

"AUTOMATIC REMOTE CONTROL" FOR AMATEUR OPERATIONS ABOVE 29.7 MHZ has been proposed by the FCC in PR Docket 85-105. Expanding on an ARRL petition that had sought automatic control for Amateurs using digital communications, the Commission is actually looking for Amateur input as to just how far the concept of automatic control should be extended.

Comments On PR Docket 85-105 Are Due at the FCC June 25, and Reply Comments July 25.

THE COMMENT PERIOD ON FCC'S "NATIONAL FREQUENCY COORDINATOR" proposal is being extended at the request of the ARRL. The new dates had not yet been set at presstime.

AMATEUR RADIO'S SPACE PROGRAM WILL BE THE SUBJECT of the Teleconferencing Radio Net (TRN) June 14. Top AMSAT satellite specialists such as W3IWI, W6SP, WA2LQQ, W3XO, K8OCL, and others will participate in the comprehensive program, which will almost surely include the latest news on WØORE's forthcoming Space Shuttle operation.


Over 200 Repeaters Across North America Now Provide TRN programs to their users; any repeater group wishing to join the TRN should write Timothy Lowenstein, WAØIVW, TRN Net Manager, c/o Midway ARC, Box 1231, Kearney, Nebraska 68847-1231.

DAYTON HAMVENTION'S "AMATEUR OF THE YEAR" IS W8ACE/4, John Willig, who's being recognized both for his role as "father" of the Hamvention back in 1951, and for his continuing efforts in maintaining the "Dayton Net" that meets three times weekly to keep former Daytonians in touch with each other. The Hamvention's Special Achievement Award went to Judy Frye, KG8P, for her leadership role setting up DARA's VEC program; the Technical Excellence Award was presented to Rich Whiting, WØTN, for having developed the Teleconferencing Radio Net. Congratulations to all for well-deserved honors!

TOUCH TONE® CONTROL

NEVER BEFORE HAS SO MUCH CONTROL...
COST SO LITTLE!!

MODEL CS-16 \$164 Amateur net | MODEL CS-1688 \$189 Amateur net

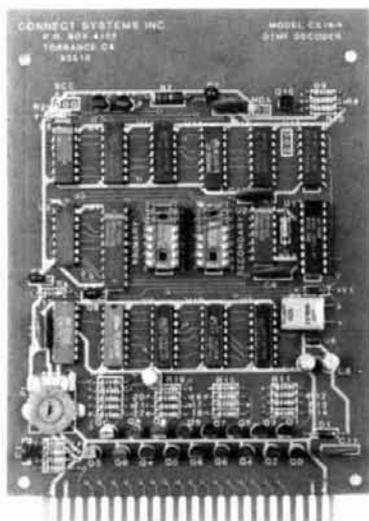


Two independent user programmable three digit passwords permit hierarchy control.

The secondary (user) password can only access 8 of the 16 latched (ON/OFF) functions.

However full 16 function control is available to control operators using the primary password. Additionally secondary password access can be enabled/disabled with a special primary password command.

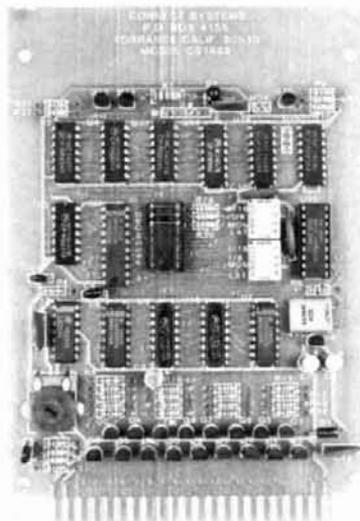Our CS-16 puts repeater control ops... IN CONTROL.



Our new CS-1688 is the most powerful touch tone controller in the industry! DIP switch programmability allows you to choose any of these ten mode/function combinations...

OUTPUT FUNCTIONS

| D 1 2 3 4 5 6 7 | | | | | | | 8 9 0 * # A B C | | | | |
|-----------------|---------------|-----|---------------|--|--|--|-----------------|-----|---------------|--|--|
| D-7 GROUP | | | | | | | B-C GROUP | | | | |
| 1. | 8 LATCHED | and | 8 MOMENTARY | | | | 8 LATCHED | and | 1 OF 8 SELECT | | |
| 2. | 8 LATCHED | and | 1 OF 8 SELECT | | | | 8 LATCHED | and | 8 LATCHED | | |
| 3. | 8 MOMENTARY | and | 8 LATCHED | | | | 8 MOMENTARY | and | 1 OF 8 SELECT | | |
| 4. | 8 MOMENTARY | and | 1 OF 8 SELECT | | | | 8 MOMENTARY | and | 8 MOMENTARY | | |
| 5. | 1 OF 8 SELECT | and | 8 MOMENTARY | | | | 1 OF 8 SELECT | and | 1 OF 8 SELECT | | |
| 6. | 1 OF 8 SELECT | and | 1 OF 8 SELECT | | | | 1 OF 8 SELECT | and | 8 LATCHED | | |
| 7. | 1 OF 8 SELECT | and | 8 LATCHED | | | | | | | | |
| 8. | | | | | | | 16 LATCHED | | | | |
| 9. | | | | | | | 16 MOMENTARY | | | | |
| 10. | | | | | | | 1 OF 16 SELECT | | | | |

COMMON FEATURES

- Open collector (can drive relays directly) and logic outputs for each of the 16 functions
- Operates from 10-25 volts DC. Reverse polarity protected
- SSI-202 central office quality XTAL controlled tone decoder
- 4 1/2" x 6 1/2" glass board with 44 pin gold plated edge connector
- Adjustable pre-amp accommodates 10MV-2 volt input
- Comes complete with manual and mating connector
- Retransmission of control tones can be eliminated by use of either

Add \$3.00 P&H California residents add sales tax

Call or write for information on these signaling products also:

Model CS-10 DIP relay board... packages 10 DIP relays.

Model CS-100... A 19" rack mount that houses a control card and two CS-10's. All inputs and outputs available on convenient barrier strips.

TYPICAL REPEATER CONTROL APPLICATIONS

HI/LO POWER — PL/COR — TIGHT/LOOSE SQUELCH — OPEN/CLOSED SQUELCH — REPEATER ON/OFF — AUTOPATCH ON/OFF — TOLL RESTRICT ON/OFF — RINGBACK ON/OFF — LONG/SHORT HANGTIME — ANTENNA 1/ANTENNA 2 — REMOTE BASE ON/OFF — F/I/F — AUX LINK ON/OFF — TONE MUTING ON/OFF — SPARE TRANSMITTER IN/OUT — ETC. ETC.

SELECTOR MODE APPLICATIONS

1 OF N FREQUENCIES — 1 OF N PHONE LINES — 1 OF N ANTENNAS — 1 OF N REPEATERS ETC.

CONNECT SYSTEMS INCORPORATED

23731 Madison St.
Torrance, CA 90505
Phone (213) 373-6803



* AT&T

MISSOURI RADIO CENTER

ANTENNA SALE

| | |
|----------------------|---------|
| HYGAIN TOWERS | |
| HG37SS | 745.00 |
| HG52SS | 1095.00 |
| HG54HD | 1675.00 |
| HG70HD | 2675.00 |

| | |
|------------------|--------|
| CUSHCRAFT | |
| A3 | 205.00 |
| A4 | 275.00 |
| 40-CD2 | 275.00 |
| AV5 | 96.00 |
| 32-19 | 89.00 |
| 214FB | 75.00 |
| ARX2B | 35.00 |
| A144-11 | 46.00 |
| A144-20T | 69.00 |
| 424B | 75.00 |
| AOP | 137.00 |

| | |
|-----------------|--------|
| KLM | |
| KT34A | 329.00 |
| KT34XA | 475.00 |
| 432-20LBX | 64.00 |
| 432-30LBX | 90.00 |
| 435-18C | 109.00 |
| 435-40C | 149.00 |
| 2M-13LBA | 77.00 |
| 2M-14C | 85.00 |
| 2M-16LBX | 89.00 |
| 2M-22C | 115.00 |

| | |
|---------------|--------|
| HYGAIN | |
| TH3JR | 185.00 |
| TH5 | 385.00 |
| TH7 | 439.00 |
| EX 14 | 289.00 |
| 14AVQ | 69.00 |
| 18AVQ | 99.00 |
| V2 | 42.00 |
| V3 | 40.00 |
| V4 | 49.00 |
| BN86 | 19.95 |

| | |
|--------------------|--------|
| HUSTLER | |
| 25% OFF ALL MOBILE | |
| 6BTV | 125.00 |

| | |
|-------------|-------|
| AEA | |
| 144SR | 42.00 |

| | |
|------------------|--------|
| BUTTERNUT | |
| HF6V | 110.00 |
| HF2V | 110.00 |

| | |
|------------------|-------|
| LARSEN | |
| LM 5/8 MAG | 36.95 |

| | |
|-----------------|--------|
| ROTATORS | |
| CD45 | 135.00 |
| HAM IV | 219.00 |
| T2X | 259.00 |

| | |
|-----------------|-------|
| AVANTI 2M | 29.95 |
| HI-Q BAL | 9.95 |

| | |
|---------------|--------|
| KENPRO | |
| KR400 | 119.00 |
| KR500 | 149.00 |
| KR600 | 199.00 |


✓ 108

2900 N.W. VIVION ROAD
KANSAS CITY, MISSOURI 64150
816-741-8118

CALL TOLL FREE
1-800-821-7323

MASTERCARD, VISA & C.O.D.'s WELCOME


Complete Satellite Systems

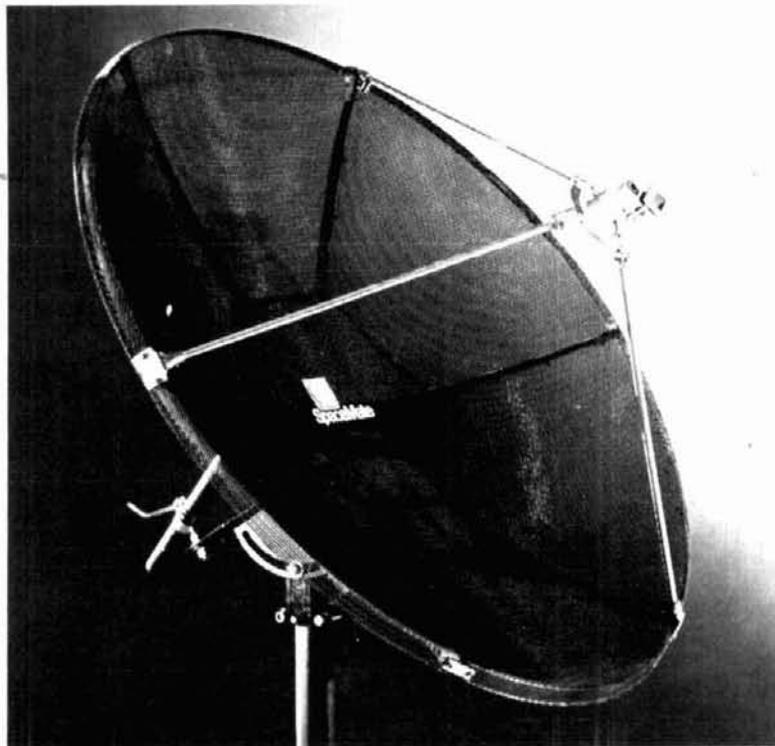

Install
your own
satellite dish
and receiver and
Save up to 50%

Introducing the
SpaceMate 6 foot
perforated aluminum dish
with a lifetime warranty.

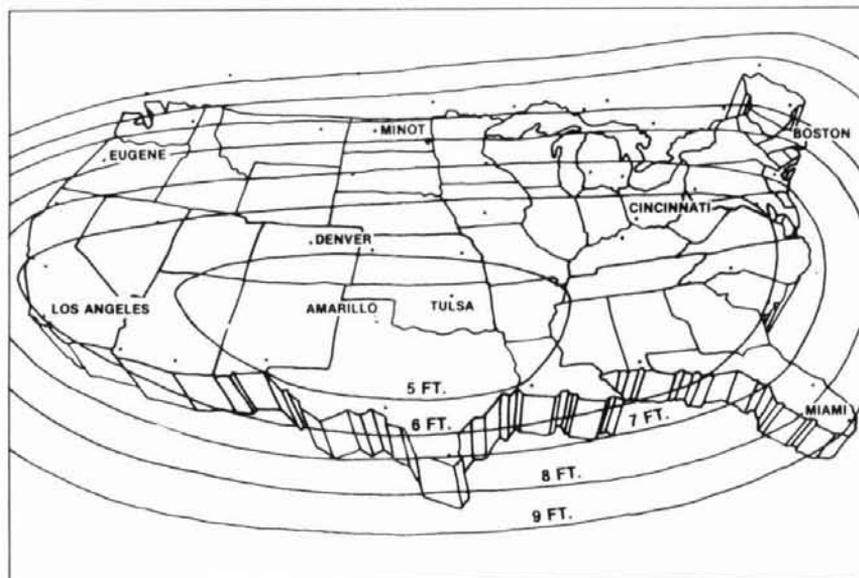Complete systems starting
as low as \$877.00



SATELLITE AT COST

(419) 522-2318

378 Plainview

Mansfield, Ohio 44907



comments

How can Amateur Radio be improved? Here's what some readers suggested in response to questions raised by K2RR and N1ACH in "Reflections" (February and March, 1985). **KA1LBO**

I'd like to see us stop all the concern for increasing *numbers* of hams and instead, try to improve the quality of operators we already have.

Vern A. Weiss, WA9VLK
Kankakee, Illinois

. . . I would like to see the spirit of Amateur Radio as it was in the 1930's restored: *service*, experimentation, operating skill, courtesy, and good fellowship.

I. L. McNally, K6WX
Sun City, California

. . . There seems to be an age of curiosity — maybe between 10 and 15 — when a youngster is thirsty to drink up the experience of the adult world. At that age the young person is curious about the entire world. We, the adults, can "turn that kid on" to electronics, computers, cameras, art, or music — or they can turn on to drugs. It's up to us. . . . My point is that we must make a solid effort to get into the elementary schools, into the summer camps, into the neighborhood community centers, to "turn on" the kids of America to the fun of our hobby. This will, in turn, capture the talents of our youth and reignite the spirit that put a man on the moon!

Marvin Feldman, WG4Q
Annandale, Virginia

In days past, there was a "romance of the airwaves" — the excitement of doing what ordinary people could not do — *and you could do it*, if you knew enough and worked hard enough.

We need to find a new romance, a new excitement.

John Telford, W3TJ
Swampscott, Massachusetts

Here's what I think is important right now — more important than technical development, if we have to choose: *we must learn how to lobby*. We hams must learn individual and group lobbying techniques. Lobbying is power, and groups have more power than individuals.

[We have to] get our emergency nets working and then let the public know what we're doing for them. When the public needs communications for various activities, we should *overwhelm* them with support, and then publicize our contribution.

Ken Uthus, KT7E
Nine-mile Falls, Washington

The way I entered ham radio was via SWL activities. I was in junior high school and could not afford anything but a receiver. I still listen to SW on a day-to-day basis and enjoy it. Perhaps emphasizing such activities will stimulate interest. . . .

Thomas M. Hart, AD1B
Dedham, Massachusetts

. . . What Amateur Radio needs is a new frontier. . . . Why not put the total emphasis on space [communications]? Maybe radio telescope operation. Let's restore the adventure of Amateur Radio to attract the new breed of high-tech communicators.

Fred N. Ackerman, W3JHN
Silver Spring, Maryland

I've been a ham for 54 years. . . . Ten years ago I got the SSTV bug and the biggest thrill from ham radio, ever. *What happened to SSTV articles in most of the magazines?*

Francis M. Duffy, AB3J
Johnstown, Pennsylvania

My main operating interest is CW. I perceive considerable anti-CW pressure these days . . . more publicity and development for very narrow band synchronous CW would help . . . also *improvement in the political climate* for this mode. . . .

To my mind, hand-sent Morse is more basic than BASIC.

Bruce Boyd, W3QA
Ellicott City, Maryland

Let's stop recruiting non-technical people into our fraternity. . . . Let's try to appeal to an average level of technical expertise — on upward.

Mike Kitsko, K6VGO
Cerritos, California

A link is needed between HF, DX, 2 meters, CB, SSTV, etc. A geostationary satellite could do just that.

Greg Waits, WB6EPE
Anaheim, California

The number of licensed Amateur Radio operators may be declining statistically but I feel sure that there are many others out there just as enthusiastically involved as we are here. The new VEC program will reverse the [negative] trend. . . . Amateur Radio clubs all over the country can and will take advantage of the VEC program to promote and assist with the licensing of new Amateur Radio enthusiasts.

Let's not be too concerned with declining numbers. It's only temporary. We, the members of the World Amateur Radio Fraternity, will see to that.

Bob Ruedisueli, W4OWA
Vienna, Virginia

. . . You may want to consider that the new 10-year license (term) will skew the figures.

John D. Gallivan III, N4DGS
Fairfax, Virginia

. . . What's wrong with Amateur Radio? Not a damn thing . . . it's just *different*.

Michael Vuksich, W0VEV
Duluth, Minnesota

KENWOOD

...pacesetter in Amateur radio

Dependable Duo!

TS-830S HF transceiver.

The "Pacesetter" has become a legend in DX and contest circles.

- Covers all 10 Amateur bands (50 kHz extended coverage).
- Wide receiver dynamic range, Junction FETs in the balanced mixer, MOSFET RF amplifier at low level, and dual resonator for each band.
- Variable bandwidth tuning (VBT). Varies IF filter passband width.
- Notch filter high-Q active circuit in 455-kHz second IF.
- Noise-blanker threshold level control.
- IF shift (passband tuning).
- 6146B final with RF negative feedback. Runs 220 W PEP (SSB)/180 W DC (CW) input on all bands.
- Built-in RF speech processor.
- SSB monitor circuit.

- Built-in digital display, (fluorescent tube), with analog dial.
- Narrow/wide filter selection on CW.
- RIT and XIT (transmitter incremental tuning).

- Optional accessories:
- VFO-230 external digital VFO with five memories, digital display.
 - VFO-240 external analog VFO.
 - AT-230 antenna tuner/SWR/power meter.

- SP-230 external speaker.
- YG-455C (500 Hz) or YG-455CN (250 Hz) CW filter for 455 kHz IF.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filter for 8.83 MHz IF.
- KB-1 deluxe heavyweight knob.



TS-530SP HF transceiver.

This "Cents-ational" HF transceiver is recognized worldwide for superior and dependable performance.

- 160-10 meters, LSB, USB, CW, all Amateur frequencies, including new 10, 18, and 24 MHz bands. Receives WWV on 10 MHz.

- Built-in digital display (six digits, fluorescent tubes), with analog dial.
- Narrow/wide filter selector switch for CW and/or SSB.
- Built-in speech processor, for increased talk power.
- IF shift tunes out interfering signals.
- Wide receiver dynamic range, with greater immunity to overload.
- Two 6146B's in final, allows 220 W PEP/180 W DC input on all bands.
- Advanced single-conversion PLL, for better stability, improved spurious characteristics.

- Adjustable noise-blanker, with front panel threshold control.
- RIT/XIT front panel control allows independent fine-tuning of receive or transmit frequencies.

Optional accessories:

- SP-230 external speaker with selectable audio filters.
- VFO-240 remote analog VFO.
- VFO-230 remote digital VFO.
- AT-230 antenna tuner/SWR/power meter.
- MC-50 desk microphone.
- KB-1 deluxe VFO knob.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filter.
- YK-88SN (1.8 kHz) narrow SSB filter.

More information on the TS-830S and TS-530SP is available from authorized Kenwood dealers.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220



Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

HAM RADIO OUTLET

YOUR VERY BEST SOURCE

FOR ANY AND ALL AMATEUR RADIO ITEMS

- 6 STORE BUYING POWER ASSURES TOP VALUE
- BIG, COMPLETE STOCKS. GET WHAT YOU WANT WHEN YOU WANT IT.
- MORE SAVINGS BY FREE DELIVERY MOST ITEMS

KENWOOD

TS-930S



PAY NEW REDUCED PRICE OF

~~\$1599~~ **\$1449**

RECEIVE FREE

AT-930 and MC-60A
ANT. TUNER MICROPHONE
Reg. \$199.95 Reg. \$79.95

PLUS FREE UPS

ICOM



IC-37A

YOUR BEST 220MHz
EQUIPMENT BUY!

REGULAR \$449

SALE! \$299.95

SPECIAL BUY...
LIMITED QUANTITIES



FT-209RH



FT-757GX



FT-2700RH

NEW!

2M/70CM

TRANSCEIVER

CALL FOR GREAT PRICES

KENWOOD

TW-4000A



PAY REGULAR
PRICE OF \$599.95

RECEIVE FREE

ALL THE FOLLOWING

- 1) VS-1 VOICE SYNTHESIZER
\$39.95 VALUE
- 2) TU4-C SUB-AUDIBLE \$39.95 VALUE
- 3) MA-4000 DUO-BAND MOBILE ANT
\$44.95 VALUE

PLUS FREE UPS

ICOM



R-71A

SUPERIOR GRADE
GENERAL COVERAGE
RECEIVER

Regular \$799

SALE! \$629.95



MIRAGE

AMPLIFIER
SALE

| MODEL | BAND | PRE AMP | INPUT | OUTPUT | DC PWR | SALE PRICE |
|--------|------|---------|-------|--------|--------|------------|
| A1015 | 6M | Yes | 10W | 150W | 20A | \$249 |
| B23S | 2M | No | 2W | 30W | 5A | \$79 |
| B215 | 2M | Yes | 2W | 150W | 22A | \$259 |
| B108 | 2M | Yes | 10W | 80W | 10A | \$159 |
| B1016 | 2M | Yes | 10W | 160W | 20A | \$249 |
| B3016 | 2M | Yes | 30W | 160W | 17A | \$199 |
| C22A | 220 | Yes | 2W | 20W | 5A | \$89 |
| C106 | 220 | Yes | 10W | 60W | 10A | \$179 |
| C1012 | 220 | Yes | 10W | 120W | 20A | \$259 |
| D24 | 440 | No | 2W | 40W | 8A | \$179 |
| D1010N | 440 | No | 10W | 100W | 20A | \$289 |

RC-1 Remote Control for MIRAGE Amplifiers, \$24
MP1 and MP2 Peak Reading Wattmeters, each \$99
Limited quantity at this price.



SALE!

W-51 SALE \$899
LM-354 SALE \$1599

IMMEDIATE DELIVERY

BIRD



MODEL
43

THE LONG
TIME STANDARD
FOR ACCURACY

SLUGS



MOST ITEMS IN STOCK

US TOWER CORPORATION

Formerly Tristao Tower Co.

MA-40 40' tubular
Regular \$745

SALE! \$549

MA-550 55' tubular
Will handle 10 sq. ft. antennas
at 50 MPH winds.

Regular \$1245

SALE! \$899

IN STOCK FOR
IMMEDIATE DELIVERY

CALL FOR INFORMATION
ON ALL OTHER MODELS



Eimac TUBE SALE!

IN STOCK...
NO WAIT



3-500Z

\$99.95

8877

\$589.95

FREE SHIPMENT

UPS SURFACE (Continental U.S.) (MOST ITEMS)

Prices, specifications, descriptions subject to change without notice. Calif. and Arizona residents please add sales tax.

Store addresses/Phone numbers
are given on opposite page.

6 STORE BUYING POWER

 **ICOM** R-71A



**SUPERIOR GRADE
GENERAL
COVERAGE
RECEIVER**

REGULAR \$799
SALE! \$629.95
PLUS FREE UPS

 **ICOM**



IC-37A

220 MHz's BEST BUY!
REGULAR \$449
SALE! \$299.95
PLUS FREE UPS

 **ICOM** IC-735

**A BRAND NEW HF TRANSCEIVER
WITH ALL THE
FEATURES
THAT MAKE IT
A TRULY
OUTSTANDING
BUY!**



CALL FOR PRICE AND INFORMATION

 **ICOM** IC-751



**TODAY'S MOST ADVANCED
TRANSCEIVER**

REGULAR \$1399
SALE! CALL FOR SPECIAL PRICE

 **ICOM** **HAND-HELDS**

AT GREAT LOW SUMMER PRICES

IC-02AT
IC-04AT



IC-2AT
IC-4AT



IC-3AT



CALL
NOW!

LATEST  **ICOM** EDITION

**IC-3200A DUAL BANDER
COVERS BOTH 2 METERS and 70CM**



NEW!
CALL FOR PRICE
AND INFORMATION

**PERSONALIZED
SERVICE**



BOB FERRERO, W6RJ
President

JIM RAFFERTY, N6RJ
VP, So. Calif. Div., Anaheim

Managers:

GEORGE, WB6DSV, Burlingame

DON, N6IPE, Oakland

BOB, K7RDH, Phoenix

GLENN, K6NA, San Diego

AL, K6YRA, Van Nuys

and other active amateurs to serve you.

FREE SHIPMENT

UPS SURFACE (Continental U.S.) (MOST ITEMS)

TOLL-FREE PHONE
INCLUDING ALASKA AND HAWAII

800-854-6046

CALIF. AND ARIZONA CUSTOMERS CALL OR VISIT NEAREST STORE

PHONE HOURS: 9:30 AM to 5:30 PM PACIFIC TIME.

STORE HOURS: 10 AM to 5:30 PM Mon. through Sat.

**HAM
RADIO
OUTLET™**

ANAHEIM, CA 92801

2620 W. La Palma,
(714) 761-3033, (213) 860-2040,
Between Disneyland & Knotts Berry Farm

BURLINGAME, CA 94010

999 Howard Ave.
(415) 342-5757,
5 miles south on 101 from San Francisco Airport.

OAKLAND, CA 94609

2811 Telegraph Ave.,
(415) 451-5757,
Highway 24 Downtown. Left 27th off-ramp.

PHOENIX, AZ 85015

1702 W. Camelback Road,
(602) 242-3515,
East of Highway 17.

SAN DIEGO, CA 92123

5375 Kearny Villa Road,
(619) 560-4900,
Highway 163 and Clairemont Mesa Boulevard.

VAN NUYS, CA 91401

6265 Sepulveda Blvd.
(818) 988-2212
San Diego Freeway at Victory Boulevard



PACKET RADIO COMES OF AGE

ANNOUNCING THE FIRST FULLY INTEGRATED

PACKET RADIO TERMINAL

THE PACKETERM IPT

Packet radio is a new mode of Amateur communication which is growing more popular every day. It provides armchair, error-free copy for local, national, and world-wide communication. It is also useable with the new generation of amateur satellites.

Networks are growing across the country and in the DX regions through the use of store-and-forward "digipeater" capability built into packet controllers. Enjoy QSOs, called "connects", with other Amateurs across the street or across the country; send messages; swap computer files; access information of general interest; and much more....

WHY PACKET ??

- * simultaneous use of a single frequency by multiple stations...without interference. Enjoy rag-chewing or round-tables.
- * access to computer bulletin boards to read messages, and leave them!
- * high speed operation...1200 baud
- * error free transmission of long messages or computer files.
- * experiment with the newest and fastest growing mode in Amateur Radio.
- * send messages through SATELLITE to virtually anywhere in the world.
- * enjoy a whole new world of contest operation, or ...



Packeterm IPT with optional printer
(sorry, radio not included)

... breath new life into that dusty old 2 meter rig !

ALL YOU NEED FOR PACKET OPERATION IS... A PACKETERM IPT AND YOUR RIG !

The Packeterm IPT is both a terminal and a full function packet node controller

- * free your computer from packet duty, or get in on the fun without one.
- * try portable operation with optional 13.8 volt adaptor and battery operated printer.

For more information about packet radio and the new PACKETERM IPT,
or to place your order, contact us at:



PACKETERM
PO BOX 835
AMHERST, NH 03031
(603)-673-6630
monday-friday, 9 am-5 pm EDST

introductory prices:
PACKETERM IPT \$995
printer \$349
dc adapter \$125

Once in a Blue Moonbounce



KENWOOD

YAESU

ICOM

SANTEC

HF TRANSCEIVERS



NEW TS-940S HF Transceiver CALL
With General Coverage Receiver

TS-930S HF Transceiver CALL
With General Coverage Receiver

TS-430S HF Transceiver SUPER SPECIAL
With General Coverage Receiver

TS-830S Transceiver CALL
160-10 Meter With Power Supply

TS-530SP 160-10 Meter XCVR CALL
With Power Supply & Notch Filter

RECEIVERS

R-2000, R-600, R-1000, R-11 CALL
General Coverage Receivers

VHF/UHF



TR-7950/7930 CALL
2-meter Mobile Units, 45 or 25 Watts

TR-9130 2m All-mode, 25 Watts CALL

TS-711A/TS-811A CALL
All-mode Transceivers
2m or 70cm mobile or base station

HANDHELDS

TR-2600A 2m FM Transceiver CALL
With memories, LCD, scan

TH-21A, 21AT/TH-41A, 41AT CALL
2m/70cm Ultra-compact FM Transceiver

HF TRANSCEIVERS

FT 980 CAT System 1439 00
AC Power Supply, Full Break-in CW,
SSB/AM/FM/FSK, Speech Processor

FT 77 with mic SPECIAL 510 95
Compact HF XCVR



FT 757 HF XCVR with mic 699 95
with General Coverage RCVR
includes CW keyer, AM/FM, CW filter

NEW FRG 8800 SWL Receiver 519 95
VHF Converters, Active Antennas available

FT 209RH 2m HT Intro Special 299 95
FT 203 2m HT with TTP, VOX 229 95
FT 203 2m HT with VOX 199 95
All accessories in stock

SWL RECEIVER

NEW FRG 8800 SWL Receiver 519 95
VHF Converters, Active Antennas available

HANDHELDS

FT 209RH 2m HT Intro Special 299 95
FT 203 2m HT with TTP, VOX 229 95
FT 203 2m HT with VOX 199 95
All accessories in stock

VHF/UHF

NEW FT 270RH 2m, 45-watt 379 95
Very small mobile rig

NEW FT 2700HF 25-watt 519 95
Dual-band 2m and 440



FT 726R For 2m 779 95
(Optional modules for 6m, 430, 440 MHz)
Great for Satellite Work

HANDHELDS

IC 02AT 2m HT, 10 Memories CALL
IC 04AT 440 HT/Touchtone 309 95
IC 2AT 2m HT/Touchtone 199 95
IC 3AT 220 MHz HT/Touchtone 229 95
IC 4AT 440 MHz HT/Touchtone 229 95

IC 271A 599 00
All-mode 2m Transceiver

IC 745 759 95
HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR 1179 00
With PS35 installed 1299 00

M12 12-ch Programmable HT 219 95
M2 76-channel Synthesized HT 261 95
M80 25-watt all-channel Scanner 387 26
M80C Commercial M80 429 95
New M5 all-channel HT 325 95

IC 271A 599 00
All-mode 2m Transceiver



IC 271A 599 00
All-mode 2m Transceiver

IC 745 759 95
HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR 1179 00
With PS35 installed 1299 00

M12 12-ch Programmable HT 219 95
M2 76-channel Synthesized HT 261 95
M80 25-watt all-channel Scanner 387 26
M80C Commercial M80 429 95
New M5 all-channel HT 325 95

IC 271A 599 00
All-mode 2m Transceiver

IC 745 759 95
HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR 1179 00
With PS35 installed 1299 00

M12 12-ch Programmable HT 219 95
M2 76-channel Synthesized HT 261 95
M80 25-watt all-channel Scanner 387 26
M80C Commercial M80 429 95
New M5 all-channel HT 325 95

IC 271A 599 00
All-mode 2m Transceiver

IC 745 759 95
HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR 1179 00
With PS35 installed 1299 00

M12 12-ch Programmable HT 219 95
M2 76-channel Synthesized HT 261 95
M80 25-watt all-channel Scanner 387 26
M80C Commercial M80 429 95
New M5 all-channel HT 325 95

IC 271A 599 00
All-mode 2m Transceiver

IC 745 759 95
HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR 1179 00
With PS35 installed 1299 00

M12 12-ch Programmable HT 219 95
M2 76-channel Synthesized HT 261 95
M80 25-watt all-channel Scanner 387 26
M80C Commercial M80 429 95
New M5 all-channel HT 325 95

REGENCY

New MX4000 mobile 30-900 MHz Call
HX1000 20-ch Handheld 215 95
New HX2000 Handheld 120-900 MHz Call
RT1050 10-ch, 6-band Special 99 95
MX3000 30-ch, 6-band mobile 189 95
MX5000 20-ch 25-512 MHz cont. 357 95

2591 2m Synth Handheld 259 95
Century 22 CW XCVR 350 00
2510 Model B 410 95
Satellite Station for Oscar 10
CORSAIR Model 560 999 95
ARGOSY II 5250 Digital 519 95
TRITON 425 HF Amp 1.5kW CALL

2591 2m Synth Handheld 259 95
Century 22 CW XCVR 350 00
2510 Model B 410 95
Satellite Station for Oscar 10
CORSAIR Model 560 999 95
ARGOSY II 5250 Digital 519 95
TRITON 425 HF Amp 1.5kW CALL

2591 2m Synth Handheld 259 95
Century 22 CW XCVR 350 00
2510 Model B 410 95
Satellite Station for Oscar 10
CORSAIR Model 560 999 95
ARGOSY II 5250 Digital 519 95
TRITON 425 HF Amp 1.5kW CALL

2591 2m Synth Handheld 259 95
Century 22 CW XCVR 350 00
2510 Model B 410 95
Satellite Station for Oscar 10
CORSAIR Model 560 999 95
ARGOSY II 5250 Digital 519 95
TRITON 425 HF Amp 1.5kW CALL

HAL
CWR 6850 Telereader 746 95
CRI 100 RTTY/CW Interface 214 95
CRI 200 RTTY/CW Interface 259 95
Other items available CALL

HARDWARE

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface 284 95
AEA MPI Micropatch 119 95
AEA CP-1 Interface 179 95

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface 284 95
AEA MPI Micropatch 119 95
AEA CP-1 Interface 179 95

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface 284 95
AEA MPI Micropatch 119 95
AEA CP-1 Interface 179 95

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface 284 95
AEA MPI Micropatch 119 95
AEA CP-1 Interface 179 95

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface 284 95
AEA MPI Micropatch 119 95
AEA CP-1 Interface 179 95

MFJ 1224 with MFJ C-64/V-20 Soft 79 95
MFJ 1229 CALL
Kantronics Interface II 210 95
AEA CP-100 Interface

voltage controlled oscillator uses ceramic resonators

Try these
old favorites
in tuned circuits

Since the earliest days of radio and electronics the LC tuned oscillator was the circuit of choice whenever a wide tuning range was needed. When stability was paramount, the crystal oscillator reigned supreme.

Over the years the frequency controlling element has changed; oscillators controlled by cavities, surface acoustic wave (SAW) devices, YIG (Yttrium Indium Garnet) and other garnets, and a host of other specialized devices have been developed. Very often a system design would benefit from an oscillator that had the tuning range of an LC oscillator and the stability of a crystal oscillator.

The phase-locked synthesizer is a system in which the accuracy and stability of a quartz crystal is transferred to a wide frequency range oscillator, permitting a large number of accurate and stable frequencies to be generated. Even in this application, the flaws of an oscillator cannot be totally eliminated. If the oscillator suffers from phase noise, microphonics, or other spurious outputs, some vestiges of these problems will remain.

The voltage controlled oscillator can be constructed from any type of oscillator, but is typically an LC oscillator with a varactor diode as part or all of the tuning capacitance. This gives the broadest tuning range but seldom exceeds a ratio of 2:1. At the other end of the spectrum (minimum tuning range), a crystal oscillator with varactor tuning provides excellent stability, very low phase noise, and freedom from microphonics, but has very limited tuning range. A rule of thumb for a variable crystal oscillator is a frequency variation of no more than 0.1 percent total. If the frequency were limited to 20 MHz (this is approximately the limit for fundamental mode crystals), the total variation would be 20 kHz. For higher frequencies, overtone crystals must be used and the ability to pull the frequency of an overtone crystal is considerably less than that of a fundamental mode crystal.

ceramic oscillator provides compromise

Somewhere between the crystal oscillator (which can hardly be moved at all in frequency) and the LC oscillator (which has a broad variation in frequency but suffers from phase noise and microphonics) is the ceramic resonator oscillator. The ceramic resonator is not a new device; for many years ceramic resonators have been the heart of the ceramic filter, which is primarily used for wideband FM IF systems found in entertainment radio and television receivers. The ceramic resonator as a single tuned circuit is finding applications in timing circuits, replacing more expen-

By Albert D. Helfrick, K2BLA, R.D. 1, Box 87,
Boonton, New Jersey 07005

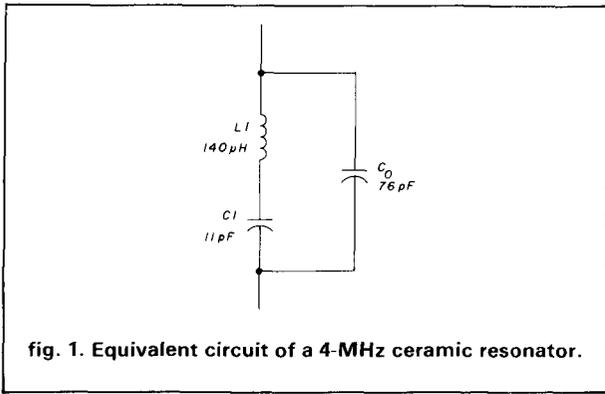


fig. 1. Equivalent circuit of a 4-MHz ceramic resonator.

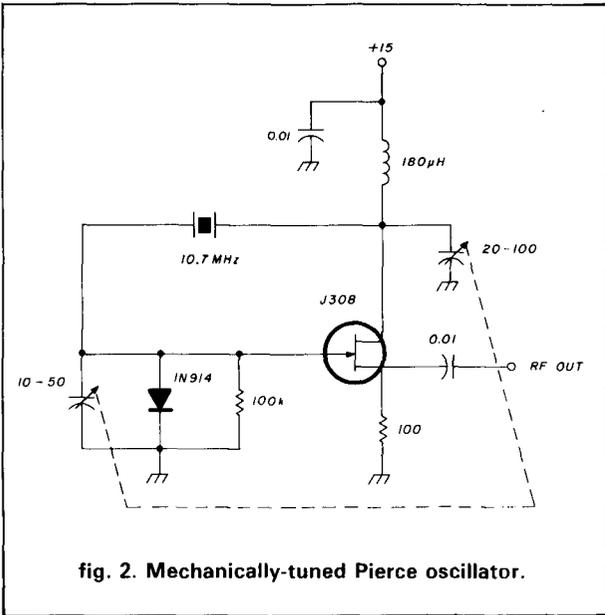


fig. 2. Mechanically-tuned Pierce oscillator.

sive quartz crystals in those applications in which the extreme precision and stability of the quartz resonator is not required.

Although the ceramic resonator is similar to a quartz crystal, there are several important differences. The equivalent circuit of the ceramic resonator shown in fig. 1 is identical to the quartz crystal except that the parameter values are somewhat different. The series resistance is on the order of 6 ohms for a 4-MHz resonator, which compares to a quartz crystal's 15 ohms. This lower value at first appears to indicate a higher Q than with the quartz crystal if weren't for the value of the equivalent inductance, which is typically 140 microhenries. In a quartz resonator at a frequency of 4 MHz, the equivalent inductance could easily be on the order of 1 henry, which is some 7000 times higher. This results in the quartz crystal having a Q of as high as 500,000. In the ceramic resonator a series capacitance of 11 pF provides the series resonant frequency while a 76-pF shunt capacitance, plus any circuit capacitance provides the parallel resonant

frequency. The Q of the equivalent circuit is on the order of 600.

advantage of the ceramic resonator over the LC oscillator

There are two inherent advantages in using a ceramic resonator rather than a conventional LC tuned circuit. First, it is nearly impossible to build inductors in the 140- μ H region that are small in size and exhibit Q s of 600. Typically a 140- μ H inductor has a Q of one-tenth that of a ceramic resonator. Secondly, a 140- μ H inductor, in order to be of reasonable size, would use a tightly coupled ferrite core. The core would be attached to a shielded can and fitted with an adjuster. This would translate mechanical movement of the core into changes in the inductance and distributed capacitance. An oscillator constructed with this type inductance would tend to be microphonic.

There are broad variations in the parameters of ceramic resonators, especially when resonators of different frequencies are compared. However, ceramic resonator Q s will generally range from 500 to 5000, values not achieved using conventional LC tuned circuits.

The significant disadvantage of the ceramic resonator as an oscillator tuned circuit is the ability of the resonator to be varied in frequency. Ceramic resonators are typically operated in parallel resonance, which is characterized by the resonant frequency of the equivalent inductance resonating with the two equivalent capacitances, C_0 and C_1 . The 76 pF capacitance shown in fig. 1 is internal to the resonator and cannot be altered in any way. Consider a situation in which a varactor is placed across the resonator to vary the frequency. The highest possible resonant frequency (f_p) when operating the resonator as a parallel resonant circuit occurs when there is no external capacitance. This produces a resonant frequency of:


$$f_p = \frac{1}{2\pi \sqrt{\frac{L_1 C_0 C_1}{C_0 + C_1}}} \quad (1)$$

There is a practical limit to how much external capacitance can be placed across the resonator, but for the purpose of gaining insight into how far the resonator can be theoretically pulled, assume the external capacitance can be as high as infinity. With infinite external capacitance, the parallel resonant frequency approaches the series resonant frequency (f_s) which is:

$$f_s = \frac{1}{2\pi \sqrt{L_1 C_1}} \quad (2)$$

determining range of operation

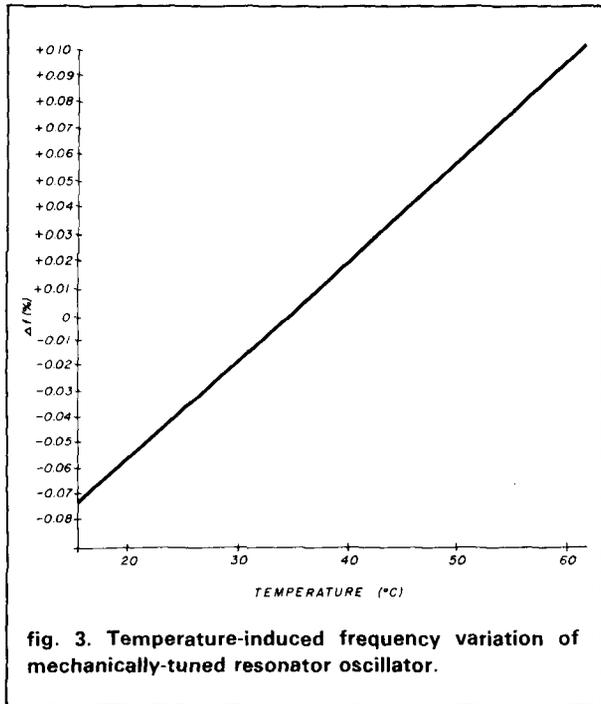
If the ratio of the highest frequency to the lowest frequency were taken, the result would be:



$$\frac{f_p}{f_s} = \sqrt{\frac{C_0 + C_1}{C_0}} \quad (3)$$

Using the typical values shown in **fig. 1**, the maximum frequency range (and consequently change from nominal frequency) is about 7 percent total for a 4-MHz resonator. Compared to the quartz crystal, this is a very large variation but rather insignificant to the octave or more variation available from an LC oscillator.

The previous discussion determined the maximum theoretical variation. However, it is not possible to apply an external capacitance from zero to infinity. The lower value of capacitance is limited by the circuit capacitance and the residual capacitance of the varactor. This discussion examines varactor tuned oscillators, but there is residual capacitance in mechanical capacitors as well. In addition, there are practical limits to the upper bound of the external capacitance and from empirical data this can be safely taken to be three times the equivalent shunt capacitance of the resonator. When a large amount of external capacitance is used, the dissipation factor of the external capacitor becomes a critical parameter in the amount of energy that can be transferred into the ceramic resonator. As a design example, assume the minimum external capacitance is 30 pF and three times the internal 76 pF or 228 pF is the maximum capacitance that is allowed. This would result from a varactor diode variation of about 200 pF. If the residual circuit capacitance is 10 pF exclusive of the varactor

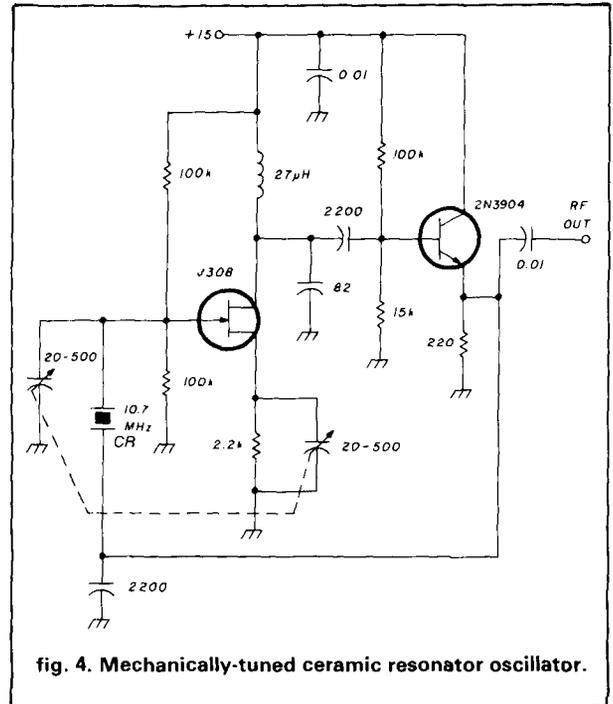

capacitance, the varactor diode capacitance must vary from 20 pF to 218 pF. This requires a tuning ratio of 10, which is attainable from a hyper-abrupt junction diode. The typical frequency variation would be about 3 percent or approximately 120 kHz at 4 MHz.

comparing actual circuits

To test the theory and to assess the ability of the ceramic resonator to serve as the frequency controlling element of an oscillator, several conventional capacitor-tuned oscillators were constructed. One example is shown in **fig. 2**. The ganged variable capacitor tunes both the gate and drain of the FET oscillator and thus maintains a constant feedback ratio. This oscillator produced a tuning range of 190 kHz from 10.7 MHz, the specified resonant frequency of the oscillator, to 10.89 MHz. This simple circuit, also illustrated a design limitation of the ceramic resonator — frequency drift with temperature.

Ceramic resonators are frequency-stabilized over temperature by using special — 4400 ppm/degree C ceramic capacitors as the feedback elements. Although the temperature characteristic of the mechanical capacitor was not known, it did *not* correct the frequency drift and the results are shown in **fig. 3**. In spite of its frequency dependence on temperature, the oscillator had some important characteristics. The oscillator had a low level of phase noise and was relatively immune from microphonics. It is these two characteristics that make the oscillator attractive as a VCO for a phase locked loop frequency synthesizer where the temperature dependence can be eliminated.

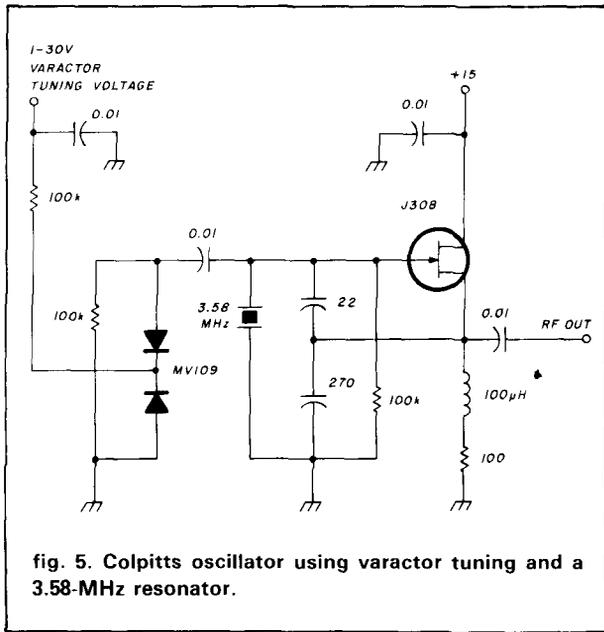


fig. 5. Colpitts oscillator using varactor tuning and a 3.58-MHz resonator.

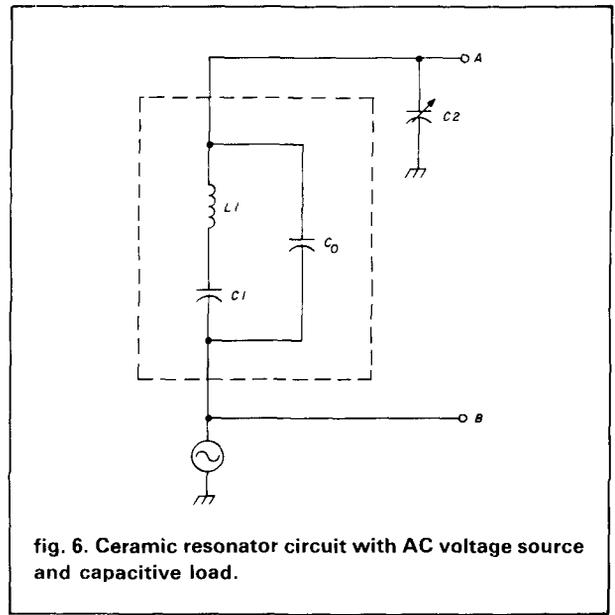


fig. 6. Ceramic resonator circuit with AC voltage source and capacitive load.

A second mechanically-tuned oscillator was constructed and is shown in **fig. 4**. One of the problems associated with an oscillator using a ceramic resonator and, to a certain extent, a crystal resonator, is that when a large amount of external capacitance is added the amount of feedback is reduced and oscillation can become unsteady (stops oscillating). The oscillator shown in **fig. 4** represents an attempt to alleviate this problem. A dual 500-pF capacitor was used as the tuning element across a 10.7-MHz resonator. The gain of the FET amplifier was varied by increasing the capacitance from the source to ground using half of the dual capacitor. As the capacitance across the resonator is increased, the gain of the amplifier also increases and the oscillations are stable over the entire 500 pF range of the capacitor. The tuning range of this oscillator was 325 kHz at 10.7 MHz.

A varactor-tuned Colpitts oscillator as shown in **fig. 5** was constructed to evaluate the ability of the ceramic resonator to serve as a VCO. A 4-MHz resonator was tested, and the results agreed substantially with theory. Using a pair of hyper-abrupt varactor diodes, it was possible to obtain nearly a 100 kHz frequency shift, which agrees with the theoretical calculation of 120 kHz. With a large variation in capacitance an unsteady oscillatory condition was evident. This is because the feedback capacitors were much smaller than the maximum capacitance of the varactors. It is mandatory that the fixed capacitances across the ceramic resonator be kept to an absolute minimum.

In the development of an oscillator that provides a maximum frequency shift using a ceramic resonator as the tuned circuit, consider the circuit shown in **fig. 6**. The equivalent circuit of a ceramic resonator is

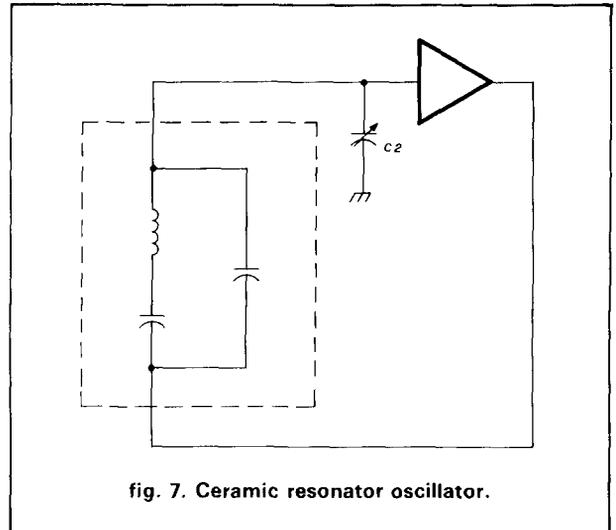


fig. 7. Ceramic resonator oscillator.

shown in series with an AC voltage source and an external capacitance which represents the varactor. Since the impedance of the voltage source is zero, the external varactor capacitance is essentially in parallel with the internal capacitance, C_0 . The voltage at point A is exactly out of phase with the voltage at point B at the parallel resonant frequency of the inductor, L_1 , and $C_0 + C_2$ in series with C_1 . Only one resonant circuit is shown in **fig. 6**. The usual series resonant circuit of L_1 and C_1 is not a factor here. If there were a resistance between point A to ground, in parallel with C_3 , there would be a second point at which the phase of the voltage at A would be the same as the voltage at point B, and that would occur at the series resonant frequency determined by L_1 , and C_1 .

Figure 7 shows the equivalent circuit of the ceramic

**ICOM
SPECIAL
IC-745
\$789.00
Plus shipping**

MA. ★

TEL-COM★ *Electronic Communications*

Authorized Dealers For

KENWOOD &  ICOM

Also displaying the popular accessories needed to complete a HAM STATION . . .

ARRL PUBLICATIONS • AEA PRODUCTS • AMPHENOL
• ALPHA DELTA • ASTRON • AUSTIN ANTENNAS • AVANTI
• BELDEN • BENCHER • B & W • DAIWA • HAM-KEY
• HUSTLER • KLM • LARSEN • MIRAGE • ROHN
• TELEX/HY-GAIN • VIBROPLEX • WELZ • ETC.

**KENWOOD
SPECIAL
NEW
TS-940S
with automatic
tuner
\$1799.00
Plus shipping**

OPEN SIX DAYS A WEEK

✓ 113

Telephone 617/486-3400, 3040

675 Great Rd., (Rte. 119) Littleton, MA 01460

1 1/4 miles from Rte. 495 (Exit 31) toward Groton, Mass.

AMATEUR TELEVISION

NEW 70 CM ATV TRANSCEIVER

ALL YOU NEED IN ONE BOX



**\$299 delivered
TC70-1**

- **FULL COLOR, SOUND, & LIVE ACTION** just like broadcast TV. Get on this exciting amateur video mode at our affordable ready to go price.
- **WHAT IS REQUIRED FOR A COMPLETE OPERATING SYSTEM?** The TC70-1s downconverter outputs to any TV on ch 3 for receiving. Connect a good 70 cm antenna and low loss coax. Plug in any composite video source you want to transmit: Camera, VCR, computer, etc. Plug in any low Z dynamic mic or use color camera mic for Standard 4.5 MHz TV sound. Connect to 13.8 vdc for base, mobile, or portable. See chapt. 20 1985 ARRL Handbook. That's it!
- **WHAT CAN YOU DO WITH THE TC70-1 ATV TRANCEIVER?** Show the shack, projects, computer program listings, home video tapes, repeat Space Shuttle audio and video if you have a TVRO, repeat SSTV or RTTY, Weather Radar, do public service events such as parades, marathons, races, CAP searches and rescues . . . the list goes on. DX depends on antennas and terrain, typically 1 to 40 miles. We have video compensated RF linear amps for 20 (\$119) or 50 (\$189) watts pep for greater DX.
- **FEATURES:** Small 7x7x2.5". Push to Look (PTL) T/R switching. GaAsfet downconverter tunes whole 420-450 MHz band. Two switch selected video & audio inputs . . . RCA phone jacks and 10 pin color camera jack. Xmit video monitor output. Over 1 watt pep RF output on one or two (add \$15) selected crystal controlled frequencies. 439.25, 434.0, or 426.25 MHz.

CALL OR WRITE FOR OUR CATALOG for more info or who is on in your area. We stock antennas, modules, and everything you need on ATV.

TERMS: Visa, MC, or cash only UPS CODs by phone or mail. Checks must clear bank before shipment. Price includes UPS surface shipping in cont. USA, others add 3%. Transmitting equipment sold only to licensed Tech class or higher amateurs, verifiable in 1985 call book or copy of new license.

(818) 447-4565 m-f 8am-6pm pst.

P.C. ELECTRONICS
Tom W60RG Maryann WB6YSS

 
2522 Paxson Lane
Arcadia CA 91006

MICROWAVE TV ANTENNA SYSTEMS

Freq. 2.1 to 2.7 GHz . 34 db Gain +

COMPLETE SYSTEMS:

(as Pictured)

Commercial 40"
Rod Style \$99.95
Parabolic 20"
Dish Style \$79.95

COMPONENTS

Down Converters
(either style) \$34.95
Power Supplies \$24.95
(12V to 16V. DC+)
Data Info (Plans) \$ 9.95



CALL OR WRITE FOR
KITS, PARTS, OR MORE
INFORMATION

Shipping & Handling Add \$5.00
We Repair Most Types Down
Converters & Power Supplies


**Phillips-Tech
Electronics**

P.O. Box 34772
Phoenix, AZ 85067
(602) 947-7700

Special Quantity Pricing
Dealers Wanted

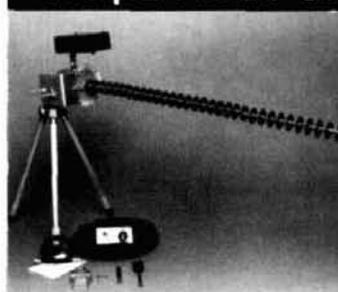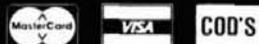

LIFETIME LIMITED WARRANTY
PARTS & LABOR

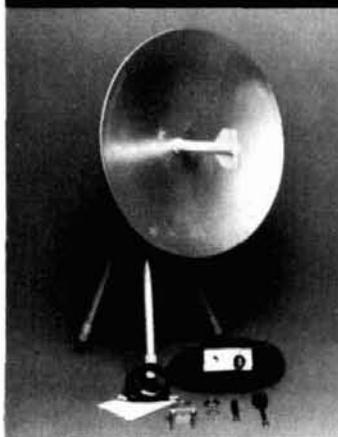

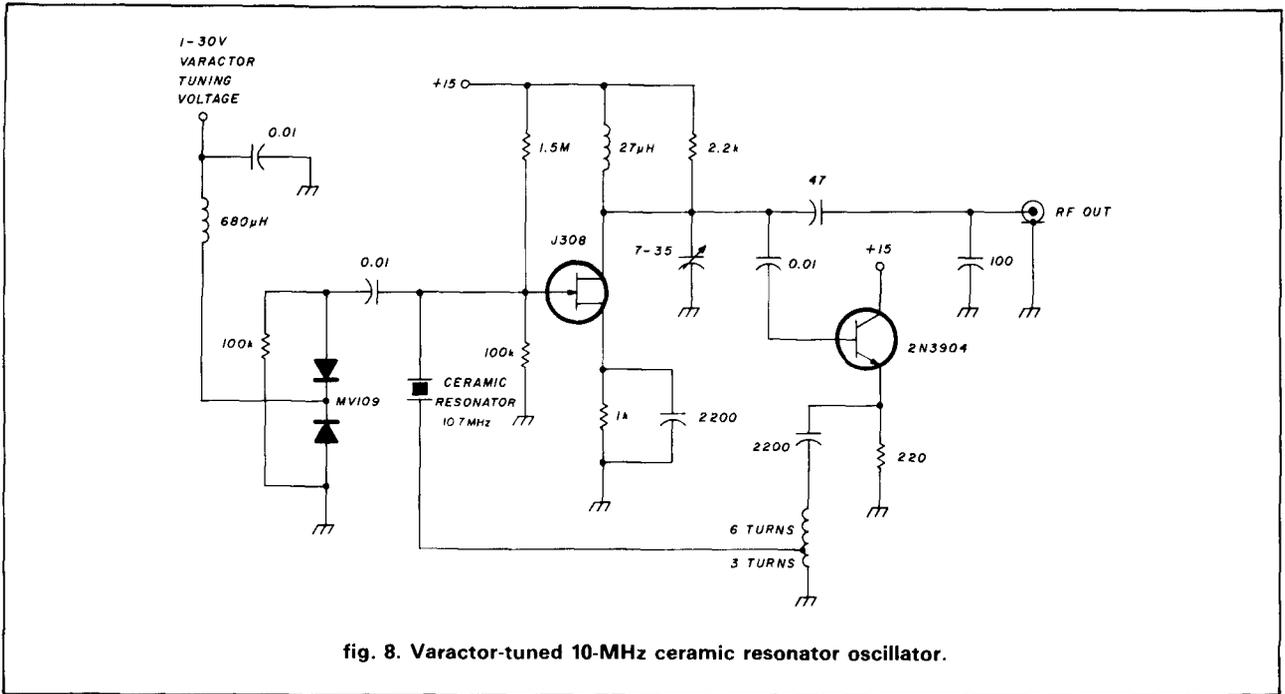


fig. 8. Varactor-tuned 10-MHz ceramic resonator oscillator.

resonator except that the AC voltage source has been replaced with the output of an inverting amplifier and point A from the equivalent circuit of fig. 6 has been connected to the input of the inverting amplifier. To satisfy the Barkhausen criteria for sustained oscillations, the total phase shift around the loop should be 0 degrees, which will occur at the parallel resonant frequency of fig. 6. In addition, the total loop gain should be zero dB, which can be satisfied by the buildup of self bias, which automatically reduces the circuit gain, as in the case of any classical oscillator. For C2 to have the greatest effect on the oscillator frequency, the input capacitance of the amplifier must be as small as possible and the output impedance of the amplifier as low as possible.

The oscillator shown in fig. 8 satisfies the criteria for a low output impedance and small input capacitance. The FET input amplifier has fixed bias with source feedback. This provides a very high input impedance with very low capacitance. The FET amplifier drives an emitter follower which, in spite of the fact that it has a low output impedance, feeds a transformer with a 3:1 turns ratio for a nine-fold impedance reduction. The result is an impedance at the ceramic resonator of a few ohms maximum.

The varactor-tuned ceramic resonator oscillator has a significant frequency-temperature coefficient, as would be expected in light of the results of fig. 3, and is shown in fig. 9. The tuning range of the VCO is approximately 232 kHz, with a temperature coefficient of 350 Hz per degree centigrade. When using this circuit as a VCO, the entire 232 kHz range cannot be used because some of the tuning range must be sacrificed

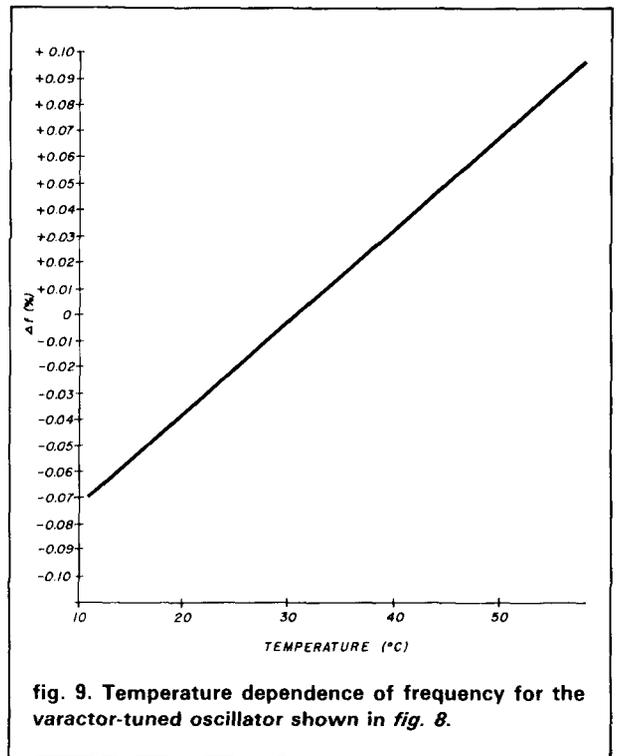


fig. 9. Temperature dependence of frequency for the varactor-tuned oscillator shown in fig. 8.

for the temperature dependence. If the required tuning range were 200 kHz, leaving 32 kHz for temperature variation, the resulting temperature variation would be more than 90 degrees C, which is sufficient for any Amateur application.

It may appear that a temperature compensating ceramic capacitor could be used for the reduction of

THE MOST AFFORDABLE REPEATER

ALSO HAS THE MOST IMPRESSIVE PERFORMANCE FEATURES

(AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

| Band | Kit | Wired |
|-------------------|-------|-------|
| 10M,6M, 2M,220 | \$680 | \$880 |
| 440 | \$780 | \$980 |





FEATURES:

- SENSITIVITY SECOND TO NONE; 0.15 uV (VHF), 0.2 uV (UHF) TYP.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE XTAL FILTER & CERAMIC FILTER FOR > 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS TO FIGHT DESENSE & INTERMOD.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).

HIGH QUALITY XMTR & RCVR MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.


- **R144/R220 FM RCVRs** for 2M or 220 MHz. 0.15uV sens.: 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity, > 100 dB at ± 12 kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138.
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$138.
- **R76 FM RCVR** for 10M, 6M, 2M, or 220. As above, but w/o AFC or hel. res. Kits only \$118. Also avail w/4 pole filter, only \$98/kit.
- **R110 VHF AM RECEIVER** kit for VHF aircraft or ham bands or Space Shuttle. Only \$98.
- **T51 VHF FM EXCITER** for 10M, 6M, 2M, or 220 MHz. 2 Watts continuous, up to 3W intermittent. \$68/kit.
- **T451 UHF FM EXCITER** 2 to 3 Watts. Kit only \$78. Xtal oven avail.
- **VHF & UHF LINEAR AMPLIFIERS.** For either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtr converters. Several models. Kits from \$78.

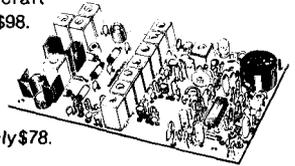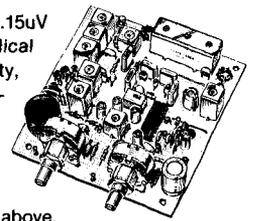

NOW—FCC TYPE-ACCEPTED TRANSMITTERS & RECEIVERS AVAILABLE FOR HIGH-BAND & UHF. CALL FOR DETAILS.

RECEIVING CONVERTERS

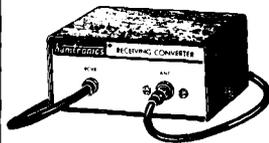Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.



VHF MODELS

| | |
|---------------|------|
| Kit with Case | \$49 |
| Less Case | \$39 |
| Wired | \$69 |

UHF MODELS

| | |
|---------------|------|
| Kit with Case | \$59 |
| Less Case | \$49 |
| Wired | \$75 |

| Antenna Input Range | Receiver Output |
|---------------------|-----------------|
| 28-32 | 144-148 |
| 50-52 | 28-30 |
| 50-54 | 144-148 |
| 144-146 | 28-30 |
| 145-147 | 28-30 |
| 144-144.4 | 27-27.4 |
| 146-148 | 28-30 |
| 144-148 | 50-54 |
| 220-222 | 28-30 |
| 220-224 | 144-148 |
| 222-226 | 144-148 |
| 220-224 | 50-54 |
| 222-224 | 28-30 |

SCANNER CONVERTERS Copy 806 MHz band on any scanner. Wired/tested ONLY \$88.

TRANSMIT CONVERTERS

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.

For VHF,
Model XV2
Kit \$79
Wired \$149
(Specify band)

| Exciter Input Range | Antenna Output |
|---------------------|----------------|
| 28-30 | 144-146 |
| 28-29 | 145-146 |
| 28-30 | 50-52 |
| 27-27.4 | 144-144.4 |
| 28-30 | 220-222* |
| 50-54 | 220-224 |
| 144-146 | 50-52 |
| 50-54 | 144-148 |
| 144-146 | 28-30 |


For UHF,
Model XV4
Kit \$99
Wired \$169

| Exciter Input Range | Antenna Output |
|---------------------|----------------|
| 28-30 | 432-434 |
| 28-30 | 435-437 |
| 50-54 | 432-436 |
| 61.25 | 439.25 |
| 144-148 | 432-436* |

*Add \$20 for 2M input

VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models, kits from \$78.

LOW-NOISE PREAMPS

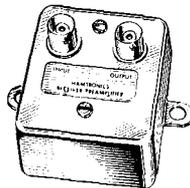

Hamtronics Breaks the Price Barrier!

*
No Need to Pay \$80 to \$125 for a GaAs FET Preamp.


FEATURES:

- Very Low Noise: 0.7 dB VHF, 0.8 dB UHF
- High Gain: 18 to 28 dB, Depending on Freq.
- Wide Dynamic Range for Overload Resistance
- Latest Dual-gate GaAs FET, Very Stable

| MODEL | TUNES RANGE | PRICE |
|---------|-------------|-------|
| LNG-28 | 26-30 MHz | \$49 |
| LNG-50 | 46-56 MHz | \$49 |
| LNG-144 | 137-150 MHz | \$49 |
| LNG-160 | 150-172 MHz | \$49 |
| LNG-220 | 210-230 MHz | \$49 |
| LNG-432 | 400-470 MHz | \$49 |
| LNG-800 | 800-960 MHz | \$49 |

HELICAL RESONATOR PREAMPS

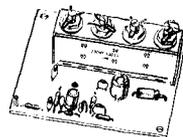Low-noise preamps with helical resonators reduce intermod and cross-band interference in critical applications. 12 dB gain.



| Model | Tuning Range | Price |
|---------|--------------|-------|
| HRA-144 | 143-150 MHz | \$49 |
| HRA-220 | 213-233 MHz | \$49 |
| HRA-432 | 420-450 MHz | \$59 |
| HRA-() | 150-174 MHz | \$54 |
| HRA-() | 450-470 MHz | \$64 |

ACCESSORIES

- **MO-202 FSK DATA MODULATOR.** Run up to 1200 baud digital or packet radio signals through any FM transmitter. Automatically keys transmitter and provides handshakes. 1200/2200 Hz tones. Kit only \$45.
- **DE-202 FSK DATA DEMODULATOR.** Use with any FM receiver to detect packet radio or other digital data in "202" modem format. Provides audio conditioning and handshakes. Kit only \$38.
- **COR-2 KIT** With audio mixer, local speaker amplifier, tail & time-out timers. Only \$38.
- **COR-3 KIT** as above, but with "courtesy beep". Only \$58.
- **CWID KITS** 158 bits, easily field programmable, clean audio. Kit only \$68.
- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Designed especially for repeaters. \$20.
- **DTMF DECODER/CONTROLLER KITS.** Control 2 separate on/off functions with touchtones®, e.g., repeater and autopatch. Use with main or aux. receiver or with Autopatch. Only \$90
- **AUTOPATCH KITS.** Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$90. Requires DTMF Module.
- **SIMPLEX AUTOPATCH.** Use with your FM transceiver. System includes DTMF & Autopatch modules above and new Timing module to provide simplex autopatch and reverse autopatch. Complete patch system only \$200/kit. Call or write for details.

• Call or Write for FREE CATALOG

(Send \$2.00 or 4 IRC's for overseas mailing)

• Order by phone or mail • Add \$3 S & H per order

(Electronic answering service evenings & weekends)

• Use VISA, MASTERCARD, Check, or UPS COD.

hamtronics, inc.

65-E MOUL ROAD • HILTON NY 14468

Phone: 716-392-9430

Hamtronics® is a registered trademark



temperature dependence. This is done for single-frequency oscillators, but the use of a shunt capacitance for temperature compensation will reduce the amount of frequency variation possible. In an oscillator with a large tuning range, temperature compensation must be achieved with a phased locked loop or other external means of frequency stabilization.

To what advantage is the ceramic resonator oscillator when it has a significant frequency-temperature coefficient and has a tuning range of only a few percent? First the phase noise of the ceramic resonator oscillator is excellent, as shown by the spectrum analyzer photograph in fig. 10. It would be nearly im-

possible to create a spectrum this clean with a conventional LC tuned oscillator. In addition, the freedom from microphonics is excellent. As a test, the fourth harmonic of the 10 MHz VCO shown in fig. 8 was received with a VHF/FM monitor receiver. This receiver is designed to function with 5-kHz peak frequency deviation, and because the fourth harmonic is being tuned a 1.25-kHz peak deviation will produce the full audio output in the receiver. The oscillator was tapped with a pencil and absolutely no audio was heard from the receiver. This is certainly not a scientific test, but to gain some insight into how this compares to a conventional LC oscillator, the printed circuit board in the monitor receiver was tapped and produced a loud clang in the receiver. In fact, if the volume of the monitor receiver were advanced to nearly full scale, a steady howl would emanate from the speaker because of acoustic feedback from the speaker to the local oscillator. Although the test was not scientific, it is clear that the ceramic resonator oscillator is quite free from microphonics.

applications

There are many applications for a narrow band low-noise oscillator. An obvious choice is to provide a VCO for a narrow range synthesizer such as a single Amateur-band frequency source. The new 10 MHz band is an obvious choice, since the VCO shown in this article is directly applicable. Another application is shown in fig. 11. Here the ceramic resonator oscillator is used in a frequency synthesizer with 100 Hz resolution. The 10-MHz range of the ceramic resonator is translated to the 6-meter Amateur band by heterodyning it with a 40-54.6 MHz phase locked frequency synthesizer. Because of the rather high (100

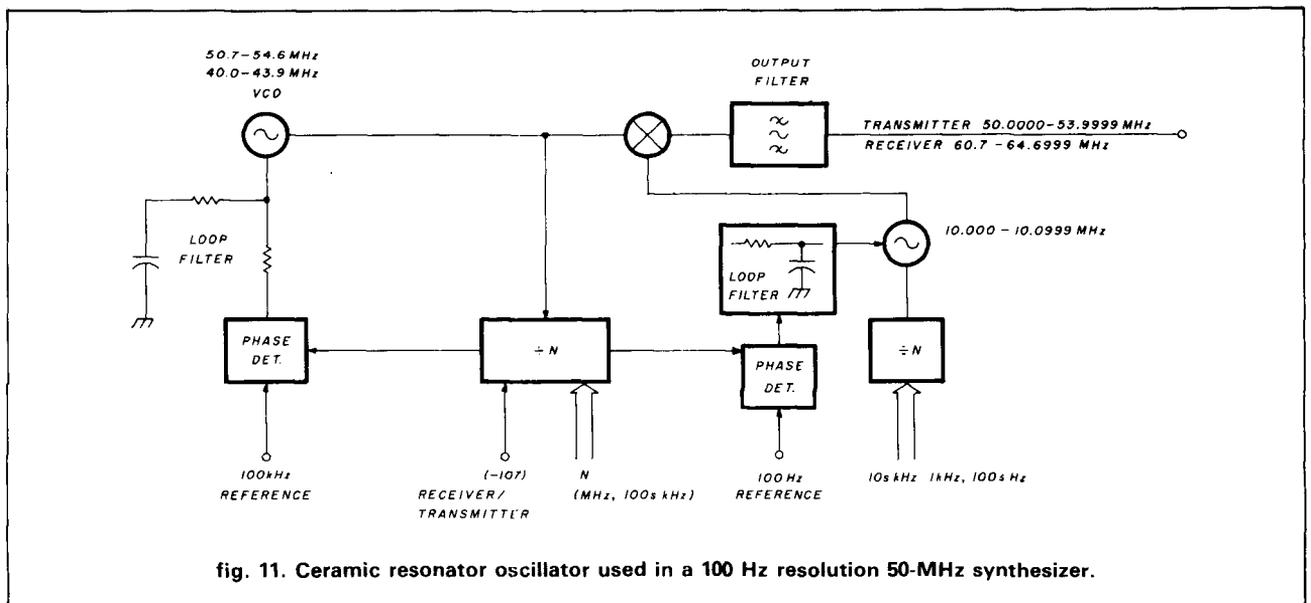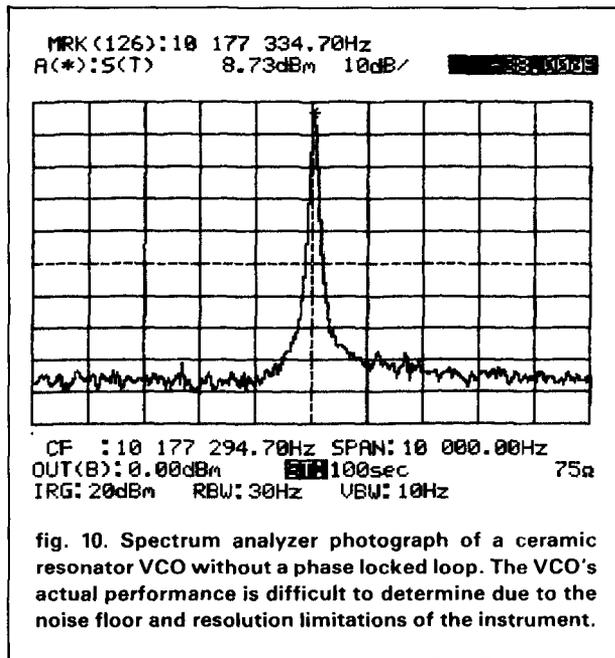

State
of the art



by
K.V.G.

9 MHz CRYSTAL FILTERS

| MODEL | Applica-tion | Band-width | Poles | Price |
|----------|--------------|------------|-------|---------|
| XF-9A | SSB | 2.4 kHz | 5 | \$53.15 |
| XF-9B | SSB | 2.4 kHz | 8 | 72.05 |
| XF-9B-01 | LSB | 2.4 kHz | 8 | 95.90 |
| XF-9B-02 | USB | 2.4 kHz | 8 | 95.90 |
| XF-9B-10 | SSB | 2.4 kHz | 10 | 125.65 |
| XF-9C | AM | 3.75 kHz | 8 | 77.40 |
| XF-9D | AM | 5.0 kHz | 8 | 77.40 |
| XF-9E | FM | 12.0 kHz | 8 | 77.40 |
| XF-9M | CW | 500 Hz | 4 | 54.10 |
| XF-9NB | CW | 500 Hz | 8 | 95.90 |
| XF-9P | CW | 250 Hz | 8 | 131.20 |
| XF910 | IF noise | 15 kHz | 2 | 17.15 |

10.7 MHz CRYSTAL FILTERS

| | | | | |
|-----------|----------|--------|---|---------|
| XF107-A | NBFM | 12 kHz | 8 | \$67.30 |
| XF107-B | NBFM | 15 kHz | 8 | 67.30 |
| XF107-C | WBFM | 30 kHz | 8 | 67.30 |
| XF107-D | WBFM | 36 kHz | 8 | 67.30 |
| XF107-E | Pix/Data | 40 kHz | 8 | 67.30 |
| XM107-SQ4 | FM | 14 kHz | 4 | 30.15 |

Export Inquiries Invited.

Shipping \$3.75

MICROWAVE MODULES VHF & UHF EQUIPMENTS

Use your existing HF or 2M rig on other VHF or UHF bands.

LOW NOISE RECEIVE CONVERTERS

| | | |
|------------------|--------------|----------|
| 1691 MHz | MMk1691-137 | \$249.95 |
| 1296 MHz GaAsFET | MMk1296-144G | 149.95 |
| 432/435 | MMc432-28(S) | 74.95 |
| 439-ATV | MMc439-Ch x | 84.95 |
| 220 MHz | MMc220-28 | 69.95 |
| 144 MHz | MMc144-28 | 54.95 |

Options: Low NF (2.0 dB max., 1.25 dB max.), other bands & IF's available

LINEAR TRANSVERTERS

| | | | |
|----------|---------------------|--------------|----------|
| 1296 MHz | 1.8 W output, 2M in | MM1296-144-G | \$299.95 |
| 432/435 | 10 W output, 10M in | MM1432-28(S) | 259.95 |
| 144 MHz | 10 W output, 10M in | MM1144-28 | 169.95 |

Other bands & IFs available.

LINEAR POWER AMPLIFIERS

| | | | |
|----------|--------------|---------------|--------|
| 1296 MHz | 20 W output | UP1296-20-L | 439.95 |
| 432/435 | 100 W output | MML432-100 | 369.95 |
| | 50 W output | MML432-50 | 199.95 |
| | 30 W output | MML432-30-LS | 209.95 |
| 144 MHz | 200 W output | MML144-200-S | 374.95 |
| | 100 W output | MML144-100-LS | 239.95 |
| | 50 W output | MML144-50-S | 149.95 |
| | 30 W output | MML144-30-LS | 109.95 |

All models include VOX T/R switching.

"L" models 1 or 3W drive, others 10W drive.

Shipping: FOB Concord, Mass.

ANTENNAS

420-450 MHz MULTIBEAMS

| | | | |
|------------|----------|----------|--------------------------|
| 28 Element | 70/MBM28 | 12 dBd | 117 |
| 48 Element | 70/MBM48 | 15.7 dBd | 349.95 339.95 |
| 88 Element | 70/MBM88 | 18.5 dBd | 75.75 59.95 |
| | | | 405.50 89.95 |

144-148 MHz J-SLOTS

| | | | |
|------------------|------------|----------|---------|
| 8 over 8 Hor pol | D8/2M | 12.3 dBd | \$63.40 |
| 8 by 8 Vert pol | D8/2M-vert | 12.3 dBd | 79.95 |
| 10 + 10 Twist | 10XY/2M | 11.3 dBd | 69.95 |

UHF LOOP YAGIS

| | | | |
|----------------------------------|----------|----------------------------|-------|
| 1250-1350 MHz | 29 loops | 1296-LY 20 dBi | 47.95 |
| 1650-1750 MHz | 29 loops | 1691-LY 20 dBi | 57.95 |
| Order Loop-Yagi connector extra: | | Type N \$14.95, SMA \$5.95 | |

Send 40¢ (2 stamps) for full details of all your VHF & UHF equipment and K.V.G. crystal product requirements.



si

(617) 263-2145
**SPECTRUM
INTERNATIONAL, INC.**

Post Office Box 1084
Concord, MA 01742, U.S.A.

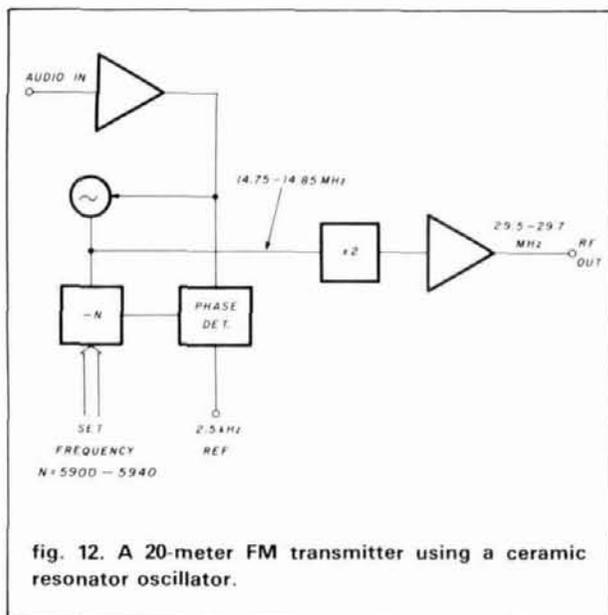


fig. 12. A 20-meter FM transmitter using a ceramic resonator oscillator.

kHz) reference frequency used for the higher frequency synthesizer, the microphonics and phase noise from that synthesizer can be reduced to negligible amounts. The relatively low frequency of the 100 Hz reference of the second phase locked loop does not allow for the loop to remove any microphonics of the inherent low-microphonic VCO using the ceramic resonator. Any synthesizer using a low frequency reference can benefit from the ceramic resonator oscillator.

A second application is shown in fig. 12. This example shows a 10-meter FM transmitter using a ceramic resonator. The basic 15-MHz frequency of the ceramic resonator oscillator is doubled to 29.5-29.7 MHz and synthesized using a 2.5 kHz reference. As in any FM transmitter where the phase locked loop is modulated directly, the loop bandwidth is restricted to a frequency below the audio frequency range, which opens up possibilities for microphonics and phase noise. This is demonstrated in most synthesized FM VHF equipment by the fact that despite putting in epoxy or other compound, the VCOs are often microphonic and noisy.

The ceramic resonator oscillator has proved to be an interesting device for several applications and it is suspected that other applications will appear. No attempt was made to temperature-compensate the basic oscillator circuit. It is possible that a thermistor or other temperature sensing device could be used in conjunction with the varactor tuning voltage to reduce the temperature dependence of the ceramic resonator to an acceptable amount. In addition to its use in an oscillator circuit, the ceramic resonator has important applications in any circuit in which a conventional LC tuned circuit would be used.

ham radio

— For the Best —

**HF, VHF, UHF, SSB,
FM, RTTY, PACKET,
CW, ASCII & AMTOR**



IC-37A 220 MHZ COMPACT MOBILE

25 Watts, 32 PL Frequencies Standard Built-in, 9 Memories with Offset and PL Storage, 10 KHz/5 KHz Dial Steps, Memory Scan, Band Scan, and Priority Scan, Dual VFO's and Standard HM-23 Touchtone.



IC-27A COMPACT MOBILE

A breakthrough in 2-meter mobile communications! Most compact on the market (5½"W × 1½"H × 7"D), contains internal speaker for easy mounting, 25 watts, 32 PL frequencies, scanning and touchtone microphone.



8/84

C & A ROBERTS INC.

18511 HAWTHORNE BOULEVARD
TORRANCE, CALIFORNIA 90504
(213) 370-7451 (Calif.) ● (800) 421-2258

REMEMBER WE SHIP
(UPS Brown - Cont. U.S.A.)


STORE HOURS: 10:00 a.m. - 5:30 p.m. MONDAY THRU SATURDAY



**4' LIGHTWEIGHT FLEXIBLE
ANTENNA ADAPTOR
CABLE**

IC-02AT HANDHELD

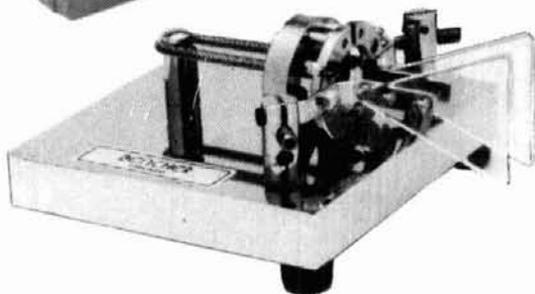The IC-02AT 2-meter LCD readout handheld features 10 memories, 32 PL tones, scanning keyboard frequency entry, dial lock, 3W standard, 5W optional, DTMF.



Bencher PADDLE

This is the paddle that provides the perfect interface between the CW operator and his rig. Smooth, instantly responsive and fully adjustable to suit your own touch. From the gold plated solid silver contacts to the heavy leaded steel base, it truly is the ultimate.



**THE R3 NO RADIAL VERTICAL
FOR 10-15-20 METERS**



a high-stability BFO for receiver applications

Two VCXOs
work together
to provide
high performance

The lower frequency IF (under 500 kHz) remains popular for many receiver applications, generally as the last IF of a single or multi-conversion scheme.

A typical Amateur application will usually require two or three discrete BFO frequencies — one for each sideband and one for CW. Good mechanical filters, either imports or surplus models made by Collins-Rockwell, are readily available. Unfortunately, while good filters are available, their companion BFO crystals are seldom offered; custom-made BFO crystals for under 500 kHz can be obtained, but only at a premium price.

Many hams have avoided the high cost of crystals by designing variable BFOs to take their place. While this is a reasonable alternative, there are disadvantages. If, for example, the filters will do double duty in the transmitter portion of a transceiver, BFO crystals would have to be used in order to ensure predictable filter performance. Most filter manufacturers specify the filter 20-dB attenuation points as the recommended BFO frequencies for SSB operation. Shifts in the BFO frequency could cause loss of carrier suppression or an undesired audio bandpass. A synthesized BFO circuit for 9-MHz IFs was described in *ham radio* several years ago, but it did not have provisions for variable tuning.¹ For certain receiver applications — especially for radioteletype (RTTY) or serious CW work — a variable BFO is a desirable feature. But we are still at the mercy of the long and short-term drift characteristics of a free-running LC oscillator. In light of the considerable investment a homebrewer makes for a set of decent filters, it would be false economy to compromise an otherwise good receiver by using a second-rate BFO design.

alternative approach — two 15-MHz oscillators

I've been building a general coverage receiver for about five years — it's one of those low-priority projects that just sits on the back burner and is worked on only during periods of extreme ambition. During my last brain-storming session I tackled its BFO circuits. My particular application required a variable frequency source between 5.593-5.597 MHz (for pass-band tuning) and the ability to preset for sideband generation in a planned companion exciter that would make use of the receiver's BFO, VFO, and HFO signals.

In designing the BFO circuits, I found an alternative to using expensive BFO crystals that would retain the versatility of a variable BFO. While my circuit uses two oscillators in the 15-MHz range, the particular frequencies are not of primary importance. (It would be wise, however, to avoid frequencies that fall on other receiver IFs or in the main tuning ranges.) Plated crystals in the 10 to 22-MHz range (fundamental frequency) will work the best; surplus crystals using pressure-plate mounts are not recommended.

What is important is that the frequency difference of the two crystals is in the exact center of the variable-frequency range we desire. I ordered two CS-1 grade crystals from International Crystal Manufacturing Co.,* and they seemed to be quite willing to match the error of the two crystals during production. This BFO system is readily adaptable to other popular IF filters in the 5, 8, or 9-MHz ranges by simply inserting the proper crystals into the circuit.

Both crystals are used in identical Colpitts circuits (fig. 1), except in that the frequencies are varactor controllable to a small degree. The total BFO shift is at least 4 kHz using the fundamental mode. This shift can be increased to about 6 kHz by installing 1.0 μ H inductors (molded chokes) in series with the crystals. A circuit for overtone crystals in the 40-50 MHz range is shown, (fig. 2). The maximum frequency excursion is considerably lower — typically 1.5 kHz. Series inductance can be used to increase the tuning range of

By Peter J. Bertini, K1ZJH, 20 Patsun Road,
Somers, Connecticut 07061

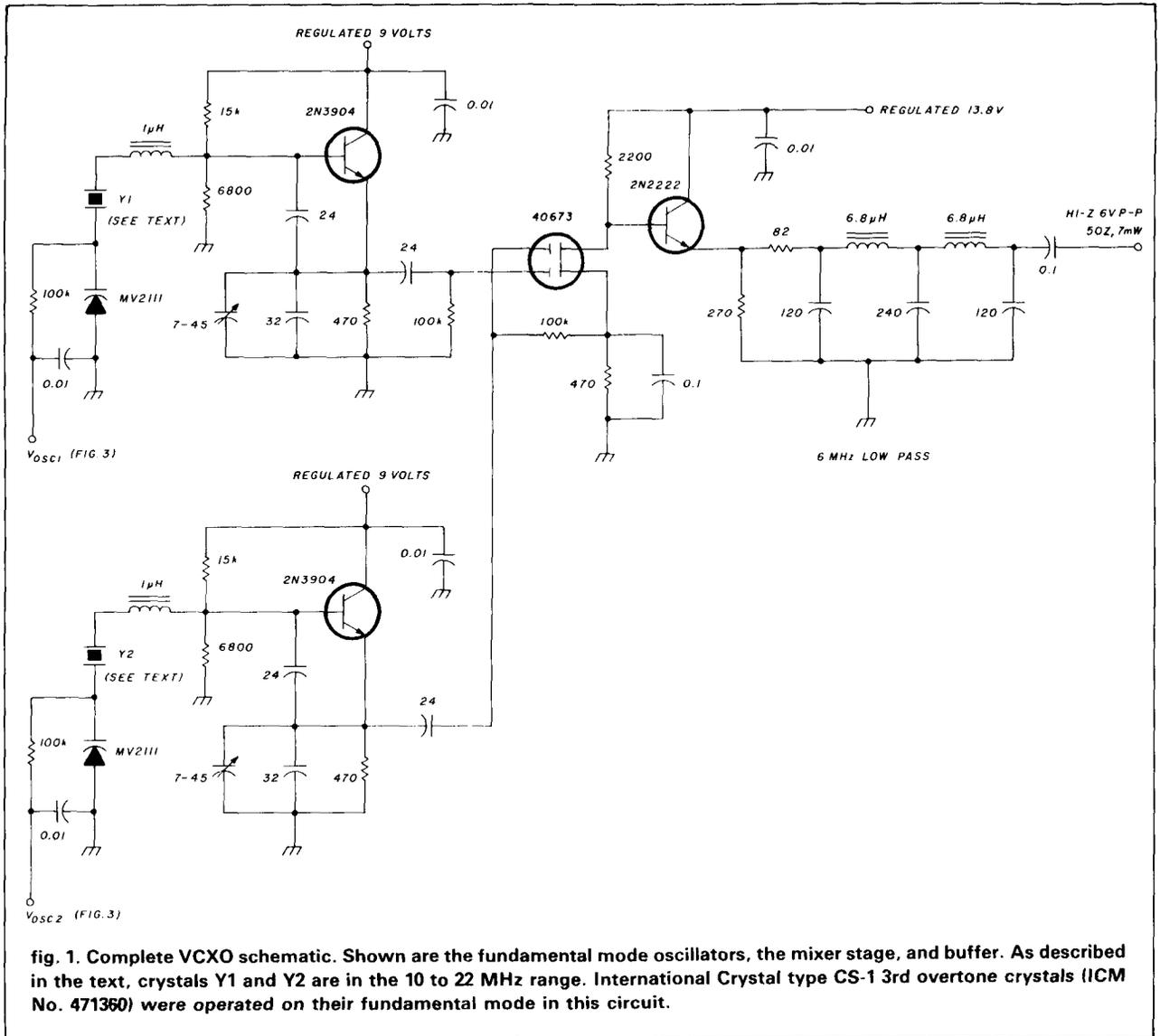


fig. 1. Complete VCXO schematic. Shown are the fundamental mode oscillators, the mixer stage, and buffer. As described in the text, crystals Y1 and Y2 are in the 10 to 22 MHz range. International Crystal type CS-1 3rd overtone crystals (ICM No. 471360) were operated on their fundamental mode in this circuit.

the overtone mode slightly, but the inductors should not be greater than $0.5 \mu\text{H}$. It is likely that most BFO requirements can be met with approximately a 1.5-kHz tuning range.

With both varicap control inputs tied to $1/2 V_{CC}$ the BFO output should be at the exact difference frequency. If a small error exists it can be trimmed out by careful adjustment of the 45-pF trimmers in the Colpitts feedback network. Initially both trimmers should be set at midpoint, and any required trimming accomplished by adjusting both trimmers equally in opposite directions. NPO capacitors should be used in the oscillators. The oscillators should be powered from a 9 to 10 volt regulated source. Either a zener or three-terminal regulator will serve here.

SSB requires few kHz frequency change

Some common VCXOs (Variable Crystal Oscillators) use both variable capacitive and inductive elements to achieve a wider pulling range. Typically these circuits become somewhat unstable at the tuning extremes. In this BFO design, we require only a few kHz tuning range to meet most SSB BFO requirements. In my circuit two oscillators are pulled in opposing directions, effectively doubling the range normally expected from a single oscillator. Producing the two varactor tuning voltages could be accomplished using a dual-ganged potentiometer, but I chose the more elegant approach of using an IC voltage inverter to drive one of the oscillator varicap diodes. This permits the use of a single-stage variable potentiometer to control both oscillators. At first glance, the circuitry used

*International Crystal Manufacturing Co., 10 North Lee, Oklahoma City, Oklahoma 73102.

to accomplish this may appear to be more involved than necessary. This will be explained in greater detail further into this article (see fig. 3).



The mixer is a 40673 dual-gate MOSFET. An emitter-follower buffer stage provides about +7 dBm (5

mW) when driving a 50-ohm load; or about 6 volts P-P driving a high-Z termination. The low-pass filter shown is optimum for outputs in the 5-6 MHz range. These values can be scaled for other IF ranges. Suitable filters can be found in tables appearing in handbooks or electronic data books.

good performance at low cost

Although not shown in the schematics, it would be simple to switch trimpots into the circuit in place of the tuning potentiometer to permit generation of fixed discrete BFO frequencies. Thus, one could switch automatically to a preset BFO frequency during transmit and have either preset or manual control of the BFO during receive. The real beauty of this circuit is in the long and short-term stability it ensures. Because of aging or temperature cycling, crystal or component variations should result in a nearly identical positive or negative frequency shift in both oscillators, but the desired difference-frequency will be closely maintained. Control voltages should be taken from a regulated low-noise source for best results. The noise-floor of this BFO will be better than most free-running designs, contributing to better post-filter IF noise performance.

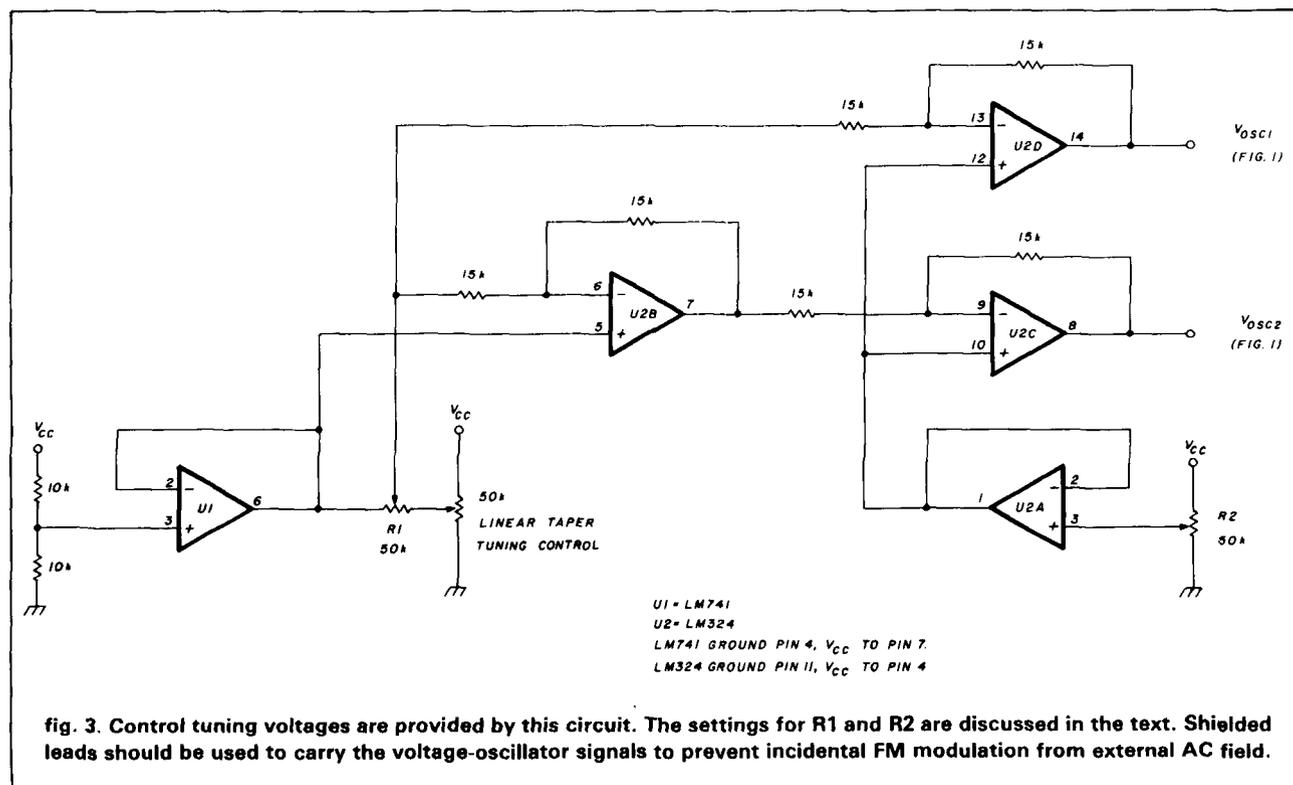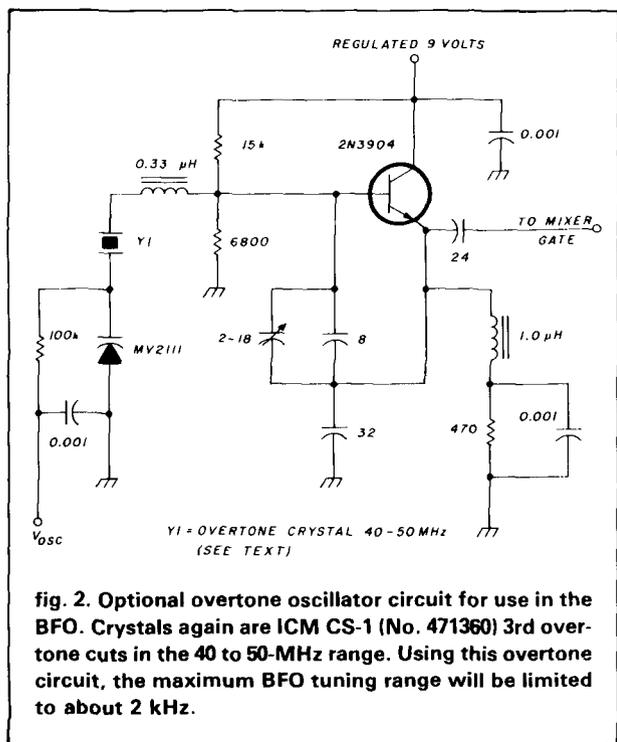The cost of this circuit compares favorably with the cost of individual low-frequency crystals. While the unit shown was built for 5.595 MHz, the basic scheme is useful for other HF and MF frequencies. The circuit is also useful for a variable frequency source in other



applications requiring good stability over a small frequency range, such as LOs for IF-variable passband or bandwidth tuners, or perhaps as a fine frequency-shifter in some PLL designs.

initial adjustments

The varicap diodes do not exhibit a linear change in capacitance for a given change in voltage over the entire available VCXO tuning range. Some empirical "cut-and-try" adjustments will be needed to obtain the desired results. The greatest change in varicap capacity occurs in the first few volts of tuning bias voltages; this is also the area of greatest non-linearity. Higher tuning voltages will result in smaller tuning ranges, while the tuning linearity will improve. Trimptot R1 sets the DC gain of the op amps (to control the maximum shift of the varicap tuning voltage). The op-amps should be powered from a well-regulated 15 to 24 volt supply. Maximum tuning range will be obtained with the higher voltage.

Trimptot R2 sets the DC offset of the two op amps used to drive the varicaps (to set the DC voltage at which the tuning voltage will start and end). The LM324 op amps were used because of their ability to reach near the power supply bus voltages (V_{CC} and ground) extending the tuning voltage range to those limits.

Trimptot R1 is adjusted to set the desired voltage swing for the varicap tuning produced by the full rotation of the tuning potentiometer. Trimptot R2 is used to set the bias point of the varicaps (the voltage midpoint between the tuning-voltage extremes). Regardless of the setting of R2, the center-tuning voltage for the two varicaps will be the same. For example, assume R1 was set for a 2-volt range, and R2 was set for a center-tuning voltage of 4 volts. The result would be that the noninverted varicap would swing from 3 to 5 volts, while the inverting varicap tuning voltage conversely would swing from 5 down to 3 volts, for a full rotation of the tuning potentiometer. If R2 were set for 7 volts tuning-center, the varicap tuning voltages would be from 6 to 8 volts and 8 to 6 volts, respectively. At first this may appear to be trivial, but remember that the tuning curves for the varicaps is not a linear function. This circuit ensures that any non-linearity of tuning — on either side of center — will be the same, or symmetrical to each other. Thus, the related panel markings would be symmetrical and more pleasing to the eye, and the "tuning-feel" more natural.

reference

1. Raymond C. Petit, W7GDM, "Phase-Locked 9-MHz BFO," *ham radio*, November, 1978, page 49.

ham radio



**DICK SMITH ELECTRONICS
NOW OPEN IN THE U.S.A.**

OUT NOW

**PASSING BY
OUR STORE?
390 CONVENTION WAY
REDWOOD CITY CA 94063
DROP IN PICK UP
A CATALOG
WE'D LOVE TO MEET YOU!**

FROM AUSTRALIA'S LEADING ELECTRONICS RETAILER THE 1985 DICK SMITH ELECTRONICS CATALOG

**RUSH \$2.00 PLUS \$1.00 SHIPPING FOR
YOUR COPY TODAY AND GET YOUR MONEY
BACK ON YOUR FIRST ORDER. THAT'S
RIGHT! EACH CATALOG CONTAINS \$2.00
WORTH OF VOUCHERS REDEEMABLE ON
YOUR FIRST ORDER.**

MAIL THIS COUPON TO:

DICK SMITH ELECTRONICS, Inc.
P.O. BOX 2249 REDWOOD CITY CA 94063
PHONE: (415) 368 1066

NAME.....
ADDRESS.....
CITY.....
STATE..... ZIP.....

**132 PAGES
PACKED WITH
ELECTRONIC
GOODIES AT
INCREDIBLY LOW
PRICES PLUS
○ DATA ○ HIGH
TECH KITS
○ BOOKS
○ COMPONENTS
AND MUCH
MUCH MORE - AS
WELL AS \$2
VOUCHER**



B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228
(214) 271-5546



74LS

| | | | |
|-------|------|----------|------|
| LS00 | .20 | LS163 | .45 |
| LS01 | .20 | LS164 | .65 |
| LS02 | .20 | LS165 | .90 |
| LS03 | .20 | LS166 | .99 |
| LS04 | .20 | LS169 | 1.25 |
| LS05 | .20 | LS174 | .45 |
| LS08 | .20 | LS175 | .40 |
| LS09 | .20 | LS181 | 1.50 |
| LS10 | .20 | LS191 | .90 |
| LS11 | .20 | LS192 | .80 |
| LS12 | .35 | LS193 | .80 |
| LS13 | .40 | LS194 | .65 |
| LS14 | .40 | LS195 | .60 |
| LS15 | .32 | LS196 | .70 |
| LS20 | .20 | LS197 | .85 |
| LS21 | .25 | LS221 | .65 |
| LS27 | .28 | LS240 | 1.00 |
| LS30 | .20 | LS241 | .80 |
| LS32 | .25 | LS242 | 1.00 |
| LS33 | .40 | LS243 | 1.00 |
| LS37 | .33 | LS244 | 1.00 |
| LS38 | .30 | LS245 | 1.00 |
| LS42 | .40 | LS251 | .50 |
| LS51 | .24 | LS253 | .50 |
| LS54 | .25 | LS257 | .50 |
| LS55 | .24 | LS258 | .55 |
| LS73 | .35 | LS259 | 2.00 |
| LS74 | .30 | LS260 | .50 |
| LS85 | .60 | LS266 | .40 |
| LS86 | .25 | LS273 | 1.00 |
| LS90 | .50 | LS279 | .40 |
| LS93 | .55 | LS280 | 1.00 |
| LS107 | .37 | LS283 | .50 |
| LS109 | .25 | LS290 | .85 |
| LS112 | .30 | LS293 | .85 |
| LS122 | .45 | LS298 | .75 |
| LS123 | .55 | LS299 | 1.60 |
| LS124 | 2.75 | LS323 | 2.60 |
| LS125 | .40 | LS348 | .75 |
| LS126 | .49 | LS364 | 1.10 |
| LS132 | .50 | LS366 | .45 |
| LS133 | .35 | LS367 | .50 |
| LS138 | .45 | LS368 | .40 |
| LS139 | .40 | LS373 | 1.00 |
| LS151 | .45 | LS374 | 1.00 |
| LS153 | .50 | LS375 | .50 |
| LS154 | 1.20 | LS377 | 1.00 |
| LS155 | .50 | LS378 | .85 |
| LS156 | .50 | LS390 | 1.00 |
| LS157 | .40 | LS393 | 1.00 |
| LS158 | .50 | LS399 | 1.25 |
| LS160 | .65 | LS670 | 1.50 |
| LS161 | .50 | 25LS2569 | 3.00 |
| LS162 | .65 | | |

TTL

| | | | | | |
|------|-----|-------|------|-------|------|
| 7400 | .22 | 7472 | .25 | 74161 | .60 |
| 7402 | .22 | 7473 | .34 | 74162 | .60 |
| 7405 | .22 | 7474 | .40 | 74163 | .60 |
| 7406 | .33 | 7483 | .45 | 74164 | .80 |
| 7407 | .33 | 7485 | .55 | 74165 | .80 |
| 7408 | .24 | 7486 | .30 | 74166 | 1.00 |
| 7410 | .19 | 7490 | .35 | 74173 | .75 |
| 7413 | .33 | 7493 | .33 | 74174 | .85 |
| 7420 | .22 | 7496 | .40 | 74175 | .80 |
| 7425 | .25 | 74107 | .28 | 74181 | 1.50 |
| 7427 | .25 | 74109 | .45 | 74185 | 1.70 |
| 7428 | .25 | 74121 | .27 | 74192 | .70 |
| 7430 | .20 | 74123 | .40 | 74193 | .80 |
| 7432 | .27 | 74125 | .49 | 74195 | .80 |
| 7433 | .25 | 74132 | .40 | 74199 | 1.00 |
| 7440 | .19 | 74148 | 1.00 | 74221 | 1.00 |
| 7442 | .40 | 74151 | .50 | 74273 | .75 |
| 7448 | .65 | 74153 | .50 | 74365 | .60 |
| 7451 | .20 | 74154 | 1.19 | 74366 | .60 |
| 7453 | .22 | 74157 | .50 | 74367 | .60 |
| 7454 | .22 | 74160 | .80 | 74390 | 1.40 |

EPROM

| | |
|------------------------|-------|
| 2708 1KX8 450 n.s. | 2.20 |
| 2758 1KX8 +5V 450 n.s. | 2.00 |
| 2716 2KX8 450 n.s. | 3.20 |
| 2716-1 2KX8 350 n.s. | 4.95 |
| 2732 4KX8 450 n.s. | 4.00 |
| 2732A | 5.50 |
| 2732A-35 | 4.75 |
| 2532 4KX8 450 n.s. | 3.00 |
| 2764-25 | 5.00 |
| 2764-45 | 3.75 |
| 27128-25 | 10.00 |
| 27128-3 | 9.00 |
| 27128-45 | 7.50 |

EPROM SPECIAL

We bought a large quantity of 2708s from a computer manufacturer who redesigned their boards. We removed them from sockets, erased and verified them, and now we offer the savings to you. Complete satisfaction guaranteed.

2708
\$1.49 or 10/\$12.00

STATIC RAM

| | |
|--------------------------------------|---------|
| 2016-2KX8 200 n.s. | 8/20.00 |
| 2101-1 - 256X4 500 n.s. | .75 |
| 21L02-1 350 n.s. | .65 |
| 2102AL-4 L.P. 450 n.s. | .49 |
| 2111-1 256X4 500 n.s. | 2.00 |
| 2114L-3 1KX4 300 n.s. | 1.50 |
| | 8/10.00 |
| 2125A-2 1KX1 70 n.s. | 2.20 |
| 2142-3 1KX4 300 n.s. | 1.50 |
| 2147 4KX1 | 3.95 |
| TMS4044 (MCM6641 C-25) 4KX1 250 n.s. | 8/6.00 |
| 6116P-4-2KX8 200 n.s. CMOS | 8/20.00 |

4K STATIC RAMS

LESS THAN 50c EACH
MK4104J-4 - 250 N.S. 18 Pin
Ceramic Computer Mfg.
Surplus. PRIME. Fully Static.
Easy to Use. Has Same Pin Out as TMS4044, but slightly different timing. With Specs. (Mostek)
8 for 5.00 32 for 15.95
VERY LOW POWER!

DYNAMIC RAM

| | |
|----------------------------------|---------|
| 2108-4 8KX1 | 1.50 |
| 2118-4 16KX1-5Volt | 1.50 |
| 4027-4KX1-250 n.s. | .80 |
| 4116-16KX1-250 n.s. | 8/6.00 |
| 4116-16KX1-200 n.s. | 8/7.00 |
| 4116 16KX1-150 n.s. | 8/10.00 |
| 4164- +5v 64K 200 n.s. | 8/16.00 |
| 4164 150 n.s. | 8/18.00 |
| TMS4416-16KX4-150 n.s. | 3.95 |
| MK4516-15 16KX1-5Volt | 1.50 |
| 5280N-5 (2107B-4 • TMS4060) 4KX1 | 8/3.95 |
| 41256 150 n.s. | 8/68.00 |

SPECIAL

AY3-8910
W/60 Page Manual
New Price — \$7.00

58321 Clock-Calendar 2.95

8000

| | | | |
|-------|-------|--------|--------|
| Z8002 | 20.00 | 8085 | 4.75 |
| 8035 | 4.50 | 8086-2 | 24.95 |
| 8039 | 4.50 | 8087-3 | 149.00 |
| 8080A | 1.25 | 8088 | 15.00 |

8200

| | | | |
|---------|-------|---------|-------|
| 8202A | 10.00 | 8255-5 | 5.00 |
| DB203-1 | 29.95 | 8257 | 6.00 |
| 8212 | 1.50 | 8259A | 3.50 |
| 8214 | 2.00 | 8259C-5 | 5.00 |
| 8216 | 1.75 | 8275 | 14.95 |
| 8228 | 3.25 | 8279-5 | 5.75 |
| 8237-5 | 7.50 | 8284 | 3.20 |
| 8250B | 9.95 | 8287 | 5.75 |
| 8251 | 4.20 | 8288 | 7.50 |
| 8253-5 | 6.75 | | |

Z80

| | |
|-----------------|------|
| Z80 2.5 MHZ CPU | 1.25 |
| Z80CTC | 1.25 |
| Z80DMA-DMA | 7.50 |
| Z80PIO | 1.49 |
| Z80SIO/O | 3.99 |
| Z80A-4MHZ CPU | 1.99 |
| Z80A-CTC | 1.99 |
| Z80A DART | 7.50 |
| Z80A-DMA | 9.00 |
| Z80A-PIO | 1.99 |
| Z80A SIO/O | 5.99 |
| Z80B 6 MHZ CPU | 7.95 |

F.D. CONTROLLERS

| | |
|---------------------|-------|
| 1771 Single Density | 12.95 |
| 1791 Double Density | 20.00 |
| 1793 Special | 12.50 |
| 1797 | 17.50 |
| 2793 | 22.00 |
| 2797 | 20.00 |

CONTROLLER SET

THREE CHIP SET

1797 or 1793, 2143-03, 1691

by W.D. Compare at up to 86.85.

B.G. SPECIAL

All 3 for only \$22.95

UART

| | |
|-----------------------------|------|
| TR1602B (COM 2017) | 1.75 |
| IM6402-(1863)+5v High speed | |
| AY5-1013 pin out | 2.95 |
| INS 8250B | 9.95 |

6800

| | | | |
|--------|------|---------|-------|
| 6800 | 2.50 | 6840 | 10.00 |
| 6802 | 3.50 | 6845P | 7.50 |
| 6803 | 5.00 | 6845S | 7.50 |
| 6809EP | 3.99 | 6850 | 2.60 |
| 6810 | 2.00 | 68A09EP | 4.99 |
| 6820 | 3.25 | 68A21 | 3.00 |
| 6821 | 2.00 | 68B45 | 10.00 |

6500

| | | | |
|------|------|------|------|
| 6502 | 2.60 | 6545 | 5.00 |
| 6522 | 6.95 | 6551 | 5.00 |

SPECIALS

| | |
|----------|-------|
| 9216 | 4.95 |
| TM599532 | 19.95 |
| BR1941L | 5.95 |
| LF353 | .60 |
| LF356 | .60 |
| TL494 | 2.50 |
| LM555 | .30 |
| 9401 | 5.00 |
| DS8835 | 1.50 |
| MC4024P | 2.50 |
| NE592 | 1.00 |
| MC1350 | 1.00 |
| LM2917 | 1.00 |
| LM339 | .50 |

SOCKETS

| | |
|-------------------------|---------|
| Low Profile SOLDER TAIL | |
| 6 Pin | 14/1.00 |
| 8 Pin | 13/1.00 |
| 14 Pin | 10/1.00 |
| 16 Pin | 8/1.00 |
| 18 Pin | 8/1.00 |
| 20 Pin | 7/1.00 |
| 22 Pin | 7/1.00 |
| 24 Pin | 6/1.00 |
| 28 Pin | 6/1.00 |
| 40 Pin | 5/1.00 |

BUY \$10

GET \$1.00 - FREE CHOICE

2114 SPECIAL!

COMPUTER
MANUFACTURERS
EXCESS INVENTORY
SALE!

PRIME! 2114-300 n.s.
INCREDIBLE PRICE!


YOU SAVE!

8/\$8.00
GUARANTEED

CRYSTALS

| | |
|--------------------|------|
| 32.768 KHz SPECIAL | .65 |
| 262.144 | .75 |
| 300.000 | .75 |
| 1.5432 Mhz | .75 |
| 1.8432 | 2.49 |
| 2.000000 | 2.49 |
| 2.560 | 1.49 |
| 3.000 | 1.15 |
| 3.120 | 1.20 |
| 3.2 | 1.49 |
| 3.4560 | 1.49 |
| 3.579545 | .75 |
| 4.000 | 1.75 |
| 4.194304 | 1.50 |
| 4.433618 | .75 |
| 4444.000 | 1.25 |
| 4.9152 | 2.49 |
| 4.916 Bd. Rate | 1.25 |
| 5.000000 | 1.50 |
| 5.0688 | 2.50 |
| 5.616 | 1.59 |
| 6.000 | 2.49 |
| 6.176 | 1.49 |
| 7.164112 | 1.00 |
| 7.3728 | 1.49 |
| 8.000 | 1.49 |
| 9.000 | 1.49 |
| 9.90000 | 1.25 |
| 10.69425 | 2.50 |
| 10.8864 | 1.49 |
| 10.920 | 1.49 |
| 11.088 | 1.59 |
| 12.000 | 2.75 |
| 13.440 | 1.00 |
| 14.31818 | 1.00 |
| 15.2 | 1.10 |
| 16.00000 | 1.50 |
| 16.5888 | 1.49 |
| 17.430 | 2.49 |
| 18.000 | 1.49 |
| 18.2259 | 1.00 |
| 18.4320 | 1.49 |
| 20.000 | 1.50 |
| 21.87108 | 1.00 |
| 22.092 | 1.00 |
| 32.000 | 2.49 |
| 40.000 | 2.00 |
| 87.3333 | 1.00 |
| 91.000 | 1.00 |
| 104.8 | 1.00 |

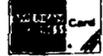TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance. Orders over \$50.00 add 85c for insurance. No C.O.D. Texas Res. add 6-1/8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.



Big Computer Manufacturer Does It Again!!! DISK DRIVE BONANZA — DOUBLE SIDED 5 1/4" DOUBLE DENSITY FACTORY NEW DISK DRIVES

ORIGINAL
OEM COST
\$132.00

MANUFACTURED IN JAPAN BY CANON.
THESE ARE PROBABLY THE MOST BEAUTIFUL
5 1/4" DISK DRIVES WE HAVE EVER SEEN
ON THE SURPLUS MARKET!!


40
TRACK

BRAND NEW: UNUSED!

\$49⁹⁵ EA.

2 FOR \$85⁰⁰

ADD \$1.50 EACH FOR POSTAGE

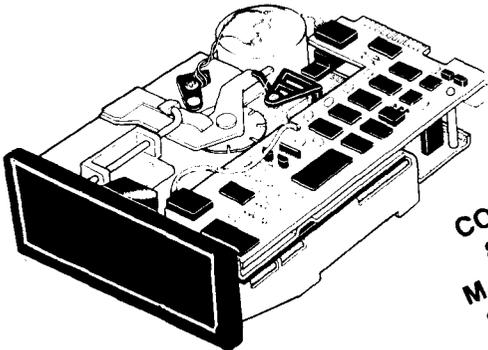

COMPLETE
80 PAGE
MANUAL AND
SCHEMATIC
\$12.50

SPECS: DOUBLE SIDED — 40 TRACK
SINGLE OR DOUBLE DENSITY
TWO THIRDS HEIGHT (SPACE SAVER!!)
INDUSTRY STANDARD PIN OUT
DIRECT DRIVE — NO BELT TO BREAK!
FAST ACCESS — 6MS
LATEST HEAD & DRIVE TECHNOLOGY

The same poor purchasing agent who nearly got lynched for over buying so many D.C. switchers has gotten carried away again. The Big Boss found another hiding place crammed with a truckload of the brand new precision manufactured 5 1/4" disk drives. Fortunately for us, the Big Boss remembered us from the switchers deal and he gave us an opportunity to make the "Second Best" surplus buy of the decade. Even though we bought a huge quantity, please order early to avoid disappointment. Please do not confuse these sleek, 2/3 height, high quality Japanese disk drives with the flimsy domestic units sold by others.

SERIAL ASCII KEYBOARD

\$14⁹⁵
Each



4
for
\$49⁹⁵


This is no misprint!

Maxi Switch 67 Key (includes 10 function keys) QWERTY serial keyboard. Number KYBD2185010 keyboard which uses a CMOS 8048 single chip microprocessor for super low power consumption. Very high quality with an exceptionally smooth feel. Originally designed for use in a portable computer. Simple serial interface — complete documentation included — Size: 12" x 5 1/2"

These won't last long at this price!!!!

ATARI HEX KEYBOARD

(REPEAT OF SELLOUT)

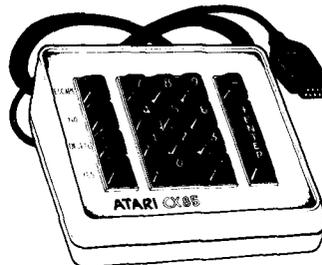

\$7⁹⁵

3 for \$20⁰⁰

Originally designed for use with an Atari Home Computer. Brand new in box. Encoded using the popular National Semi 74C923. Full schematic included. Originally sold for many times our price. Many applications besides computer use. (ADD \$1.00 each shipping cost)

TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance. Orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 6-1/8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.

TIME FOR AN AEA BREAKTHROUGH

The high quality of AEA products is appreciated long after the price paid is forgotten.

| | | |
|--|--|--|
|  <p>DOCTOR DX™ No Antenna No Radio No TVI</p> <p>\$99.95</p> <p>Plan to enter the DOCTOR DX™ World Championship Contest at the Atlanta Hamfestival, July 6 & 7, 1985.</p> | <p>THE FANTASTIC DOCTOR DX™ CW Band Simulation That Is So Real You Won't Believe It!</p> <ul style="list-style-type: none"> • Will improve the operating skills of ANY CW operator! • More fun than ANY Morse Code trainer yet devised. • Use with a C-64, TV set, and key (or keyer). • Experience the thrill of a "DXpedition" to anywhere in the world. • Operate anytime you want, ideal for travelers. • Impressive award certificates available for verified performance. • On-going contests: 8-hour sprint and 24-hour marathon. | <p>HOT ROD™ 1/2 Wave Telescope Antenna \$24.95*</p> <ul style="list-style-type: none"> • Fewer telescopic sections than any 1/2 wave whips. • Shorter and lighter than all 1/2 wave whips. • Special matching network designed by Professor D.K. Reynolds (co-inventor of Iso-pole™ antenna) makes Hot Rod competitive-ly priced. |
|--|--|--|

- Most gain attainable for length of antenna—3 dBd (0 dBd for JR models).
- Best decoupling of any commercial VHF base station antenna available.
- More gain than many antennas claiming up to 7 dB gain—don't be fooled by misleading claims!
- Zero degree angle of radiation.
- Factory-tuned matching network.
- Greater bandwidth than any competitive product.
- DC grounded for static discharge protection.
- Documented cases of wind survival in 140+ mph hurricanes.
- Easier than any competitive antenna to assemble.

Most Not Included

ISO = 144 or 220—\$59.95*
ISO = 144 JR or 220 JR—\$49.95*
ISO = 440—\$84.95*



CP-1 \$239.95*
Computer Patch™ Interface

- Better performance than any competitive product
- Dual channel filtering with auto threshold correction
- Variable shift
- 117 VAC power supply included

NEW!



DOCTOR QSO™ \$79.95*
Morse Code Trainer

- Makes Morse Training Fun, Fun, Fun!!!
- Plug-in Cartridge For C-64 Computer
- Simulates Real Morse Ragchews
- Can Operate With Only C-64 and TV Set



PKT-1 Packet Controller \$589.95*

- Easy to use—five usual commands.
- Multiple conversations on simplex channel.
- EVERY PKT-1 is a digipeater.
- Send computer files error free.
- Operates from 9-15 VDC for portable or fixed operation.

ELECTRONIC KEYS

| | | | |
|---|--|---|---|
|  <p>\$109.95* BT-1 Basic Morse Trainer</p> <ul style="list-style-type: none"> • Teaches code at 20 wpm. • Random practice mode. • Variable monitor tone. |  <p>\$149.95* KT-2 Keyer/Trainer</p> <ul style="list-style-type: none"> • Proficiency Trainer. • 01-99 WPM. • Full-feature keyer (no memory). |  <p>\$199.95* CK-2 Contest Keyer</p> <ul style="list-style-type: none"> • 10 soft-partitioned™ memories. • Automatic serial number. • Stepped variable speed. • Two speed memories. |  <p>\$229.95* MM-2 MorseMatic™</p> <ul style="list-style-type: none"> • Memory keyer. • Auto serial number • Proficiency trainer. |
|---|--|---|---|

All AEA Keyers operate from 9-15 VDC (power supply not included) and offer many more advanced features than can be listed here. It is no accident that AEA keyers are regarded as the best in the world.

ISOPOLE ANTENNA™

NEW!



MP-1 MICROPATCH™ \$159.95*

- Morse/Baudot/ASCII/AMTOR
- Use any AEA software
- Compact
- Economical

NEW!



ATU-1000 ADVANCED TERMINAL UNIT \$1195*

- World's most advanced terminal unit/computer interface
- 32 poles, active filtering
- Set filters & AFSK tones to one Hertz
- TTL, RS-232, loop keyer incl

NEW!



CP-100 COMPUTER PATCH™ \$369.95*

- 170/425/850 or variable shift
- Front-panel squelch
- Built-in monitor speaker
- Discriminator-style tuning for AMTOR

Unmatched Software For C-64 And VIC-20 Computers

MBA TORT™—The most advanced software written for Morse-Baudot ASCII AMTOR including mail drop.

MARSTEXT™—A special Morse-Baudot ASCII package written especially for MARS and other traffic operators.

SWLTEXT™—The most sophisticated software available for the shortwave listening enthusiast. Automatic data analysis; Morse, Baudot, ASCII, AMTOR, and SITOR.

AEA also offers Morse, Baudot, and ASCII software for the following computers: Apple II, II+, IIe; IBM-PC.

*Retail Prices—Call For Your Special Discount!
MIDWEST AMATEUR RADIO SUPPLY
3456 Fremont Avenue, North
Minneapolis, MN 55412
Store Hours: Mon.-Fri. 9-6, Saturday 9-3
For service call: (612) 521-4662
For orders call: 1-800-328-6365



a compact IF sweep generator

A stable frequency source
with excellent linearity
and constant output level

In a sweep generator for the lower IF and HF bands, tuning diodes, or "varicaps" generally don't produce sufficient frequency swing with acceptable linearity. On the other hand, other methods of frequency sweeping — for example, frequency conversion, reactance circuits, and mechanical tuning — may cause the cost and complexity of a home-brew project to increase to the point of being both unaffordable and impractical.

That is why, after coming across an old and half-forgotten oscillator circuit, I was pleasantly surprised to find that a large frequency sweep with good linearity isn't that difficult to build, as this simple little test instrument shows.

To keep the sweep generator as practical and uncomplicated as possible, I decided to use only one frequency band (100 to 200 kHz), using the harmonics

of the basic signal for higher frequencies. This approach offers the advantage of using only one coil, without any switching circuit. It also permits the use of a simplified power output stage, which requires only an ordinary low-power transistor.

The principle of using harmonics works out very well. Because the frequency of a measured filter is generally known, confusion about the correct frequency is unlikely. In addition, the waveform of the output signal cannot alter the response of the filter under investigation. Interference from other than the wanted harmonic is not possible either, because the next harmonic is always at least 100 kHz away.

By making the sweep generator deliver pulses rather than sine waves, another advantage comes to light: it's easy to keep the output level of the different harmonics constant, regardless of frequency variations, by simply maintaining the wave form (duty cycle) of the pulse signal.

The little frequency sweeper has already demonstrated its value — not only by aligning IF strips in my equipment, but also by inspiring me to carry out several interesting experiments with crystal filters that would otherwise be very difficult to do.


how it works

The principle of the variable oscillator is based on a vacuum tube circuit originally described by K.C. Johnson in the April/May, 1949 issue of *Wireless World*. Although it has been revived in solid-state form since that time, the circuit never really caught on for reasons perhaps best expressed by Johnson himself: "It would appear," he said, "that most people do not believe that it could ever work."

The circuit is basically that of a Butler oscillator (fig. 1A) tuned to a frequency determined by L1 and C1. In the sweep oscillator, L1 is made electrically variable by what is known as "turns cancellation." This is achieved by coupling the coil to another coil, L2, which passes an RF current of opposite phase.

The magnitude of this out-of-phase current depends upon the imbalance of a differential amplifier (fig. 1B).

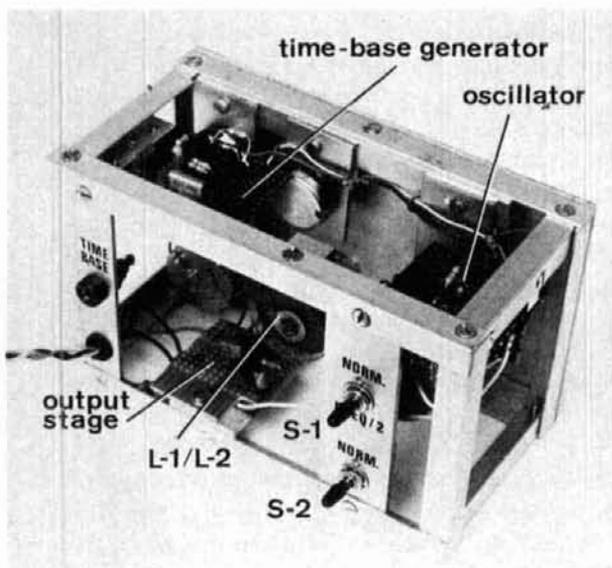For example, when applying more negative voltage to its base, the gain of Q1 is reduced and Q2 is conse-



Inside view of the IF sweep generator. Circuit simplicity and ordinary components provide a versatile test instrument.

By Hans Evers, PA0CX/DJ0SA, Am Stockberg 15, D-5165, Hürtgenwald, West Germany

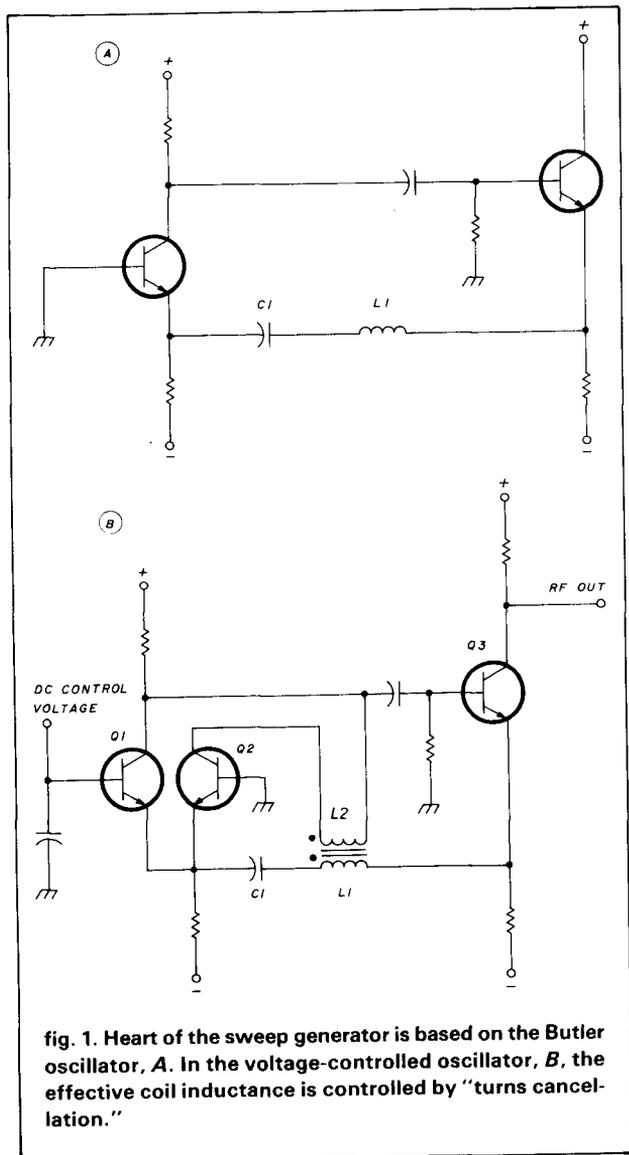


fig. 1. Heart of the sweep generator is based on the Butler oscillator, A. In the voltage-controlled oscillator, B, the effective coil inductance is controlled by "turns cancellation."

quently increased, thus increasing the RF current through the coupling coil, L2.

As the direction of this RF current opposes the current through L1, the inductance of the frequency-determining L1 is effectively reduced, with the result that the oscillator frequency rises.

The more turns on L2, and the tighter the coupling between L2 and L1, the more frequency deviation can be accomplished. Therefore, the principle has nothing to do with the magnetic properties of the coil as such, and the obtainable frequency variation is greater with powdered iron or ferrite toroids than with ordinary air-wound coils, only because the core material permits the "cancellation" coil to assert a stronger influence on the tuning element.

After some experimenting it soon becomes clear that this is a remarkable circuit. Not only can frequency variations be made unusually large; the frequency line-

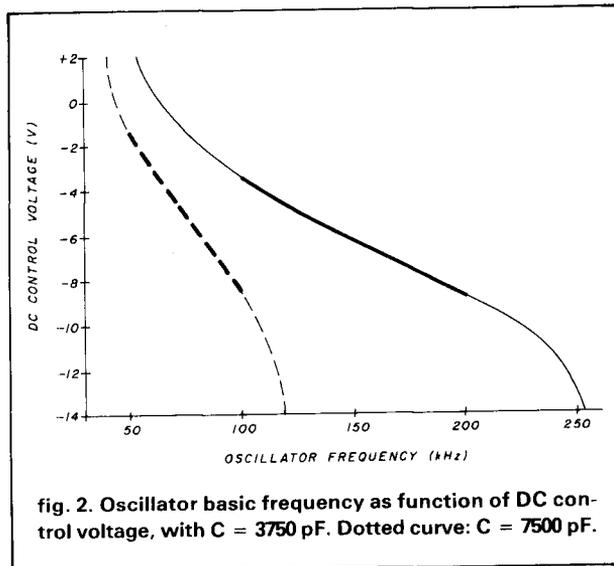


fig. 2. Oscillator basic frequency as function of DC control voltage, with C = 3750 pF. Dotted curve: C = 7500 pF.

arity is also quite spectacular, as fig. 2 shows. The total range of the oscillator covers frequencies up to a ratio as great as 1:5, including a range of 1:2 with excellent linearity.


Those who would like to experiment a little further with this "smart" circuit, may find it interesting to know that though the closely coupled coils are bound to introduce some stray capacitance, this does not prevent the circuit from working at much higher frequencies. Note that the RF voltages developed on the coils are of the same order: at the right-hand side they are connected to the same emitter follower. Indeed, the principle turns out to be useful for oscillators covering even the highest HF bands.

oscillator

The differential amplifier allows the tuning to be controlled from two independent sources. The base of Q1 is controlled by potentiometer R2 CENTER FREQ, while the base of Q2 receives its control voltage from the time-base generator (fig. 3). This provides a simple solution for making the sweep width symmetrical around the center frequency, regardless of amplitude. As the frequency/voltage sensitivity remains constant over the entire CENTER FREQ range, the output of the saw-tooth generator can be calibrated as Δ FREQ, which remains valid for all settings of CENTER FREQ.



A high-quality potentiometer is recommended for R2. In fact, it is a type with very thin and closely wound resistance wire; however, a good-quality, large-size carbon potentiometer would also do the job.

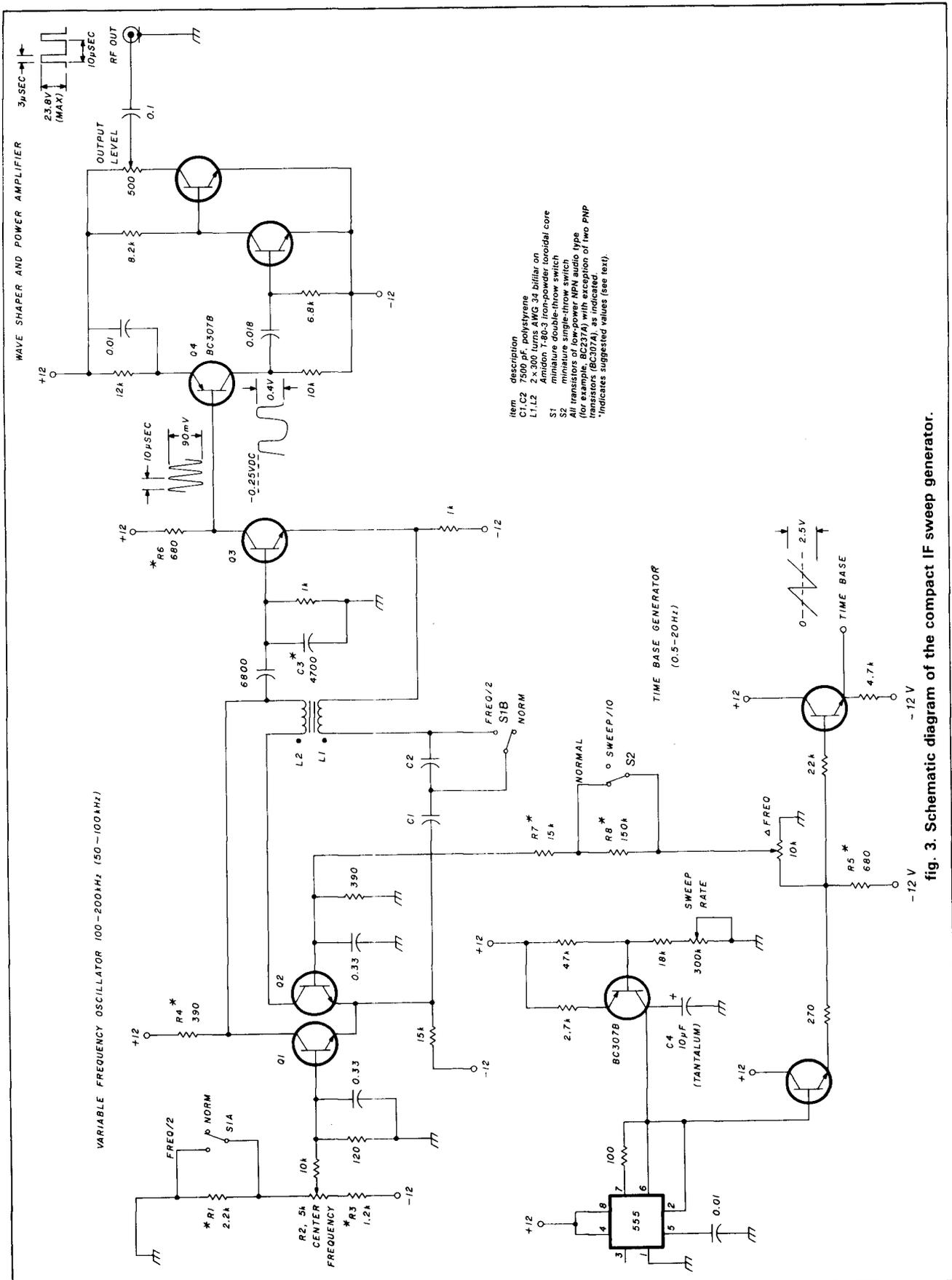It is the oscillator's stability that determines the highest usable harmonic of the sweep generator. In practice this may be more than 10 MHz, providing that the following precaution is taken: the frequency stability can be improved considerably by joining Q1 and Q2 with "super-glue" and then wrapping the pair in



- Item description
- C1,C2 7500 pF, polystyrene
- L1,L2 2x-300 turns AWG 34 bifilar on double-flux-power toroidal core
- S1 miniature double-throw switch
- S2 miniature single-throw switch
- All transistors of low-power NPN audio type (for example, BC237A) with exception of two PNP transistors (BC307A), as indicated.
- *Indicates suggested values (see text).


fig. 3. Schematic diagram of the compact IF sweep generator.

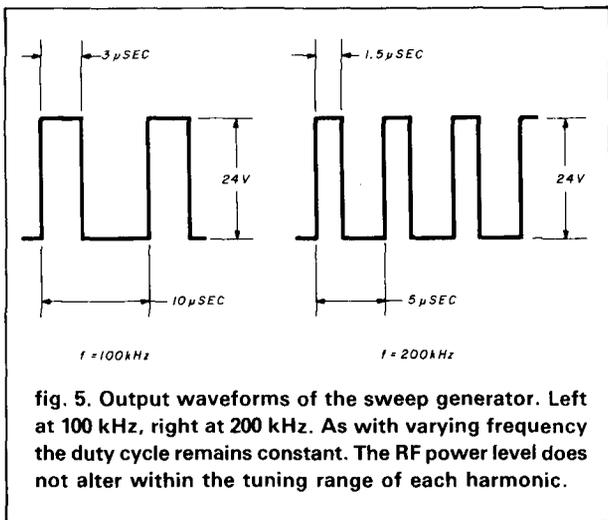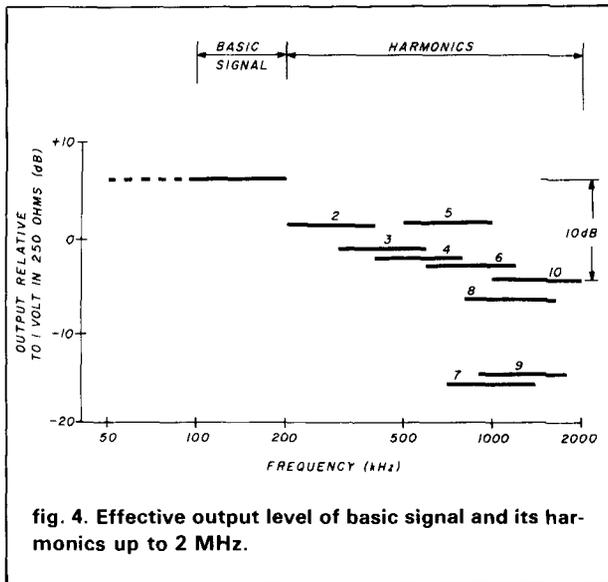

thin copper wire, and finally soldering the total into one solid metal blob. This assures that the two transistors will remain at virtually the same temperature, while their common, relatively heavy thermal mass prevents fast frequency drift.

In applications in which the sweep generator is used for sweeping filters at frequencies lower than 100 kHz, the basic range of the oscillator may be dropped to 50 to 100 kHz at the expense of a slight deterioration in frequency linearity. Double-throw switch S1 shorts one of the tuning capacitors and also shorts a resistor in series with the CENTER FREQ potentiometer. This enables the oscillator to work on half frequencies within the linear portion of the control range.

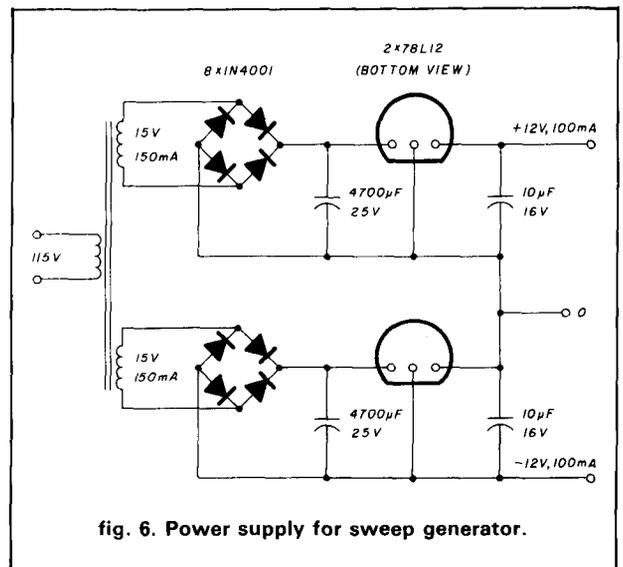The calibration of both CENTER FREQ and Δ FREQ could be done very accurately by listening to the harmonics of the oscillator with a communication receiver.



time base

The sawtooth generator circuit enables sweep rates from twice a second, for slowly sweeping sharp-edged responses from crystal filters without the risk of ringing effects, to 20 Hz, permitting a flicker-free oscilloscope display.


To keep the frequency deviations symmetrical around the center frequency, R5 may need some correction. Also the values given for R7 and R8 are approximate, as these resistors determine the Δ FREQ calibration.

When using a harmonic of the basic oscillator signal, not only does the frequency increase, but the indicated Δ FREQ value must also be equally multiplied. At higher frequencies the sweep width may consequently become too large and therefore impractical. Thus a provision was necessary for dividing the sweep width by a factor 10 in the form of R8. Normally this extra series resistor remains shorted by S2.

wave-shaping circuit

This circuit produces the harmonics of the oscillator signal. As a general rule, the widest harmonic spectrum may be created by generating the shortest pulses. However, the shorter the pulses, the less power each harmonic contains. After some experimenting (to compensate for my insufficient experience with Fourier-analysis techniques) I decided to aim for an output pulse with a duty cycle of about 30 percent. This is not too difficult to obtain and results in an overlapping spectrum of output signals, the levels of which remain — at least up to 2 MHz — within a 10-dB range (fig. 4). Only above 2 MHz does the effective output tend to drop beyond this range.

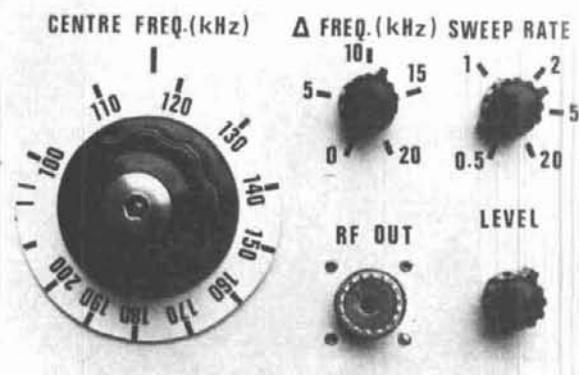The signal strength of each individual harmonic is a different matter. It should remain constant during



IF sweep generator has a frequency range of 1:2 with excellent linearity.

the sweeping process. To make this possible, not only the amplitude but also the duty cycle of the rectangular waveform must remain constant, regardless of frequency.

A satisfactory sine wave can be obtained from the oscillator section by trimming R4 and C3. At the same time, a constant amplitude is maintained over the full frequency range. Q4 conducts mainly on the tops of this sine wave. These tops are then amplified and clipped, which results in a rectangular waveform (fig. 5). The surface of these pulses (amplitude X time) stays constant, regardless of frequency. This assures a constant output level of each harmonic.

The pulse characteristic of the output signal permits the use of an ordinary low-power transistor for the output stage. Functioning as an electrical switch, rather than an analog amplifier, the transistor must handle neither appreciable voltage nor current at any common moment in time. This explains how a perfectly cool little 200 mW transistor is capable of delivering the total output power (basic signal plus all harmonics together) of almost 1 watt.

The output impedance of the final stage depends on the setting of the OUTPUT LEVEL potentiometer. At maximum setting, the output impedance is equal to half the value of the potentiometer; that is, 250 ohms. Still, the sweep generator can be safely loaded with 50 ohms impedance without upsetting anything. Only an amplitude over 50 ohms will drop to one-fifth; that is, about 5 volts.

power supply

The power supply (both +12 volts and -12 volts at about 65 mA) may be very simple (fig. 6), using 78L12 voltage regulators. The hum level must be low, because any ripple on Q1 and Q2 control voltages causes frequency modulation. Although the toroidal coil L1/L2 is relatively insensitive to stray fields, it may nevertheless pick up hum from a nearby transformer,

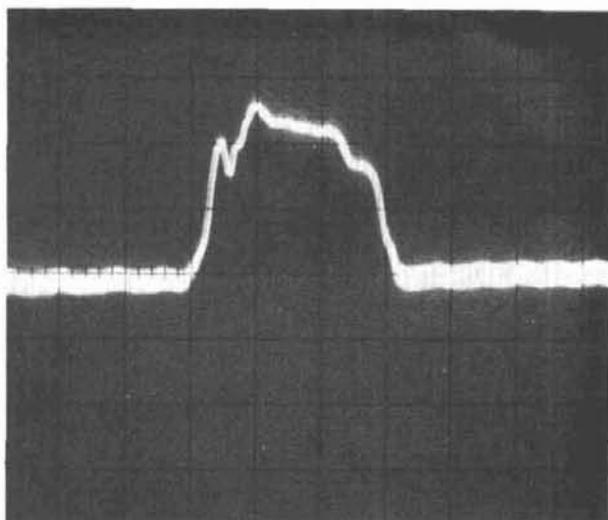
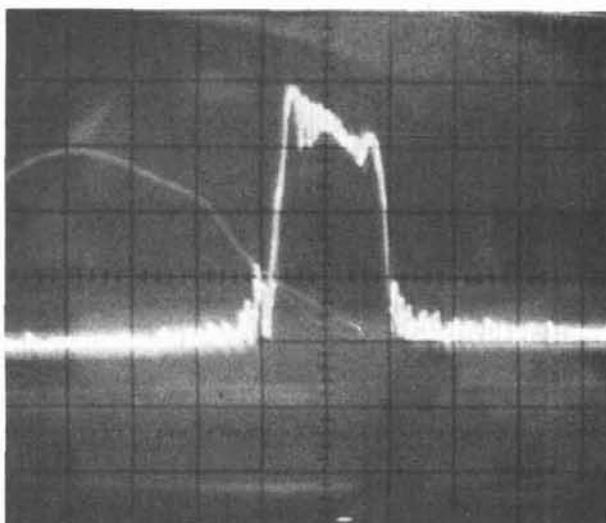


fig. 7. *Top*: Response of IF amplifier with 9 MHz crystal filter in HF transceiver. Sweep rate 4 Hz. *Bottom*: poorly matched mechanical bandfilter in 455 kHz IF amplifier (Collins F455-J-31). Sweep rate 4 Hz.

causing a rippling oscilloscope display. It is for this reason that the power supply has not been incorporated into the sweep generator itself, but is instead connected at the end of a 3-wire lead.

The RF detector for this sweep generator is a simple diode detector. Two examples using this detector are shown in fig. 7. However, the value of the measurement can be enhanced considerably by using a logarithmic detector instead. This permits an amplitude display on a decibel scale, over several decades, if necessary. (A simple version of such a logarithmic detector will be the subject of a forthcoming article in *ham radio*.)

ham radio

the HAM STATION

220 N. Fulton Ave.
Evansville, IN 47710

LARGE STOCK OF NEW EQUIPMENT AT DISCOUNT PRICES

Orders & Quotes 1-800-523-7731
Info & Service 812-422-0252
Indiana Residents 812-422-0231

| | |
|----------------|------------|
| AEA | HEIL |
| ARRL | HUSTLER |
| ALLIANCE | HY-GAIN |
| AMECO | ICOM |
| AMERITRON | KLM |
| AVANTI | KANTRONICS |
| ASTRON | KENPRO |
| B & W | LARSEN |
| BENCHER | MFJ |
| BUTTERNUT | MIRAGE |
| CALL BOOK | NYE VIKING |
| COILCO | SHURE |
| CONNECT SYSTEM | TEN-TEC |
| CUSHCRAFT | UNADILLA |
| DAIWA | VALOR |
| ENCOMM | WELZ |
| HAL | YAESU |


CALL FOR PRICES ON EQUIPMENT FOR OSCAR 10

Send SASE for our new & used equipment list.
MON-FRI 9AM-6PM • SAT 9AM-3PM

PRICES AND AVAILABILITY SUBJECT TO CHANGE. FREIGHT FOB EVANSVILLE.

ICOM DAY!

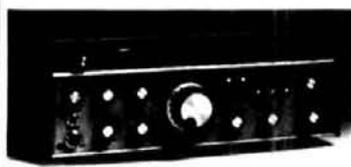Saturday, June 22, 1985
9:00 a.m. Till 5:00 p.m.



New 561 Corsair List \$1354.00
Call for Discount Price

New features include:
New lighter grey color
New 8 pole variable audiofilter
New gold colored digital display
New 40 char. memory keyer
Computer designed 16 pole Xtal ladder filter
Fully Amtor compatible
Improved noise floor (using audiofilter)
Higher dynamic range

| | |
|--------------------------------------|----------|
| AEA | |
| CP-100 | \$329.45 |
| CP-1 Computer Interface | 189.95 |
| CP-1/C-64 or Vic 20 Software | |
| Package | 229.95 |
| MP-20 or MP-64 | 149.95 |
| MAP-64 w/AMTOR | 199.95 |
| MP-1—Micropatch | CALL |
| DR. DX | 99.95 |
| PKT-1 Packet Controller | 459.95 |
| Isopoles, Hotrods, Software in Stock | |

| | |
|------------------------------|----------|
| ASTRON POWER SUPPLIES | |
| RS7A 5-7 Amp | \$ 49.00 |
| RS10A 7.5-10 Amp | 59.00 |
| RS12A 9-12 Amp | 69.00 |
| RS20A 16-20 Amp | 89.00 |
| RS20M 16-20 Amp w/meter | 109.00 |
| RS35A 25-35 Amp | 135.00 |
| RS35M 25-35 Amp w/meter | 149.00 |
| RS50A 37-50 Amp | 199.00 |
| RS50M 37-50 Amp w/meter | 225.00 |

| | |
|-------------------------------|------------|
| BENCHER | |
| BY-1 Black Chrome/BY-2 Chrome | \$39/49.00 |
| ZA-1A Balun | 19.00 |

| | |
|-----------------------------|----------|
| B & W | |
| 370-15 80-10M Folded Dipole | \$135.00 |

| | |
|----------------------|----------|
| DAIWA | |
| CN-410 M 3.5-150 MHz | \$ 65.00 |
| CN520 1.8-60 MHz | 63.00 |
| CN540 50-148 MHz | 72.00 |
| CN620B 1.8-150 MHz | 110.00 |
| CN630 140-450 MHz | 130.00 |
| CS201 2 Pos. Switch | 23.00 |
| CS-401 4 Pos. Switch | 62.00 |



IC-3200
Call for Special Price

| | | |
|---------------------------|------------|--|
| ICOM | | |
| 751 Top of the Line | \$1179.00 | |
| 745 Gen. Cov. Xcvr | 769.00 | |
| R71A Gen. Cov. Rcvr | 629.95 | |
| 271A 2M All Mode | 599.95 | |
| 271H 2M 100W | 749.95 | |
| 471A 430-450MHZ 25W | 699.95 | |
| 471H 430-450MHZ 75W | 949.75 | |
| 27A 2M 25W Mobile | 319.95 | |
| 27H 2M 45W Mobile | 355.00 | |
| 37A 220MHz Mobile | 299.95 | |
| 47A 440 MHz Mobile | 399.95 | |
| 2AT 2Mtr H.T. | 199.95 | |
| 3AT/4AT 220/440 H.T.'s | ea. 229.95 | |
| NEW 3200 Dual-Bander | CALL | |
| 02AT 2Mtr H.T. | 289.95 | |
| 04AT 440MHZ H.T. | 319.95 | |
| 735 Newest Gen. Cov. Xcvr | 729.95 | |
| All Accessories in Stock | | |


| | | |
|---|----------|--|
| KANTRONICS | | |
| Packet Communicator | \$349.95 | |
| U.T.U. Universal Terminal Unit | 179.95 | |
| Interface II | 229.00 | |
| The Challenger | 89.95 | |
| All HamSoft, Hamtext, AMTOR Programs in Stock—Call for Discount Price | | |

| | | |
|-------------------------------|----------|--|
| MFJ | | |
| 1229 Interface/Free Software | \$159.95 | |
| 1224 Interface/Free Software | 85.00 | |
| 1228 Interface/Free Software | 59.95 | |
| 989 3KW Roller Inductor Tuner | 289.95 | |
| 941D 300W Full Feature Tuner | 89.95 | |
| 422 Keyer/Benchmer Paddle | 99.95 | |

| | | |
|----------------------------|----------|--|
| MIRAGE | | |
| B3016 30-160W PreAmp | \$199.95 | |
| B1016 10-160W PreAmp | 245.00 | |
| D1010N 10-100W 430-450 MHz | 279.95 | |

| | | |
|------------------|----------|--|
| ENCOMM | | |
| KDK 2033 25 Watt | \$259.95 | |

WELZ
All New Models in Stock

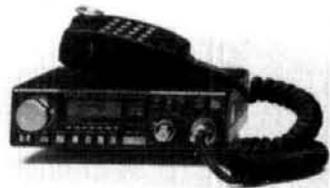

FT270R
Call for Special Price

| | | |
|-------------------------|-----------|--|
| YAESU | | |
| FT980 Deluxe Xcvr | \$1425.00 | |
| FT757GX Gen. Cov. Xcvr | CALL | |
| FC757AT Auto Tuner | 235.00 | |
| FT757HD P.S. w/Fan | 175.00 | |
| FT726R Tri-Band Xcvr | 779.00 | |
| 430 Module | 249.95 | |
| FT209RH 2M H.T. 5W | 299.95 | |
| FT203R/TT | 229.95 | |
| Much Much More in Stock | | |

| | | |
|----------------------------|----------|--|
| HY-GAIN | | |
| TH7 DX Tribander | \$435.00 | |
| Explorer 14.3 EL Tribander | 309.00 | |
| V2S Vertical 138-174 MHz | 49.00 | |
| Complete Line in Stock | | |


| | | |
|--------------|------|--|
| CABLE | | |
| Large Stock | CALL | |

| | | |
|----------------|---------|--|
| ROTORS | | |
| Alliance HD-73 | \$99.95 | |
| Alliance U-110 | 49.95 | |
| Telex CD-45 | 139.95 | |
| Telex Ham-4 | 229.95 | |
| Telex T2X | 269.95 | |
| Ken Pro KR500 | 155.00 | |



KDK 2033
Call for Special Price

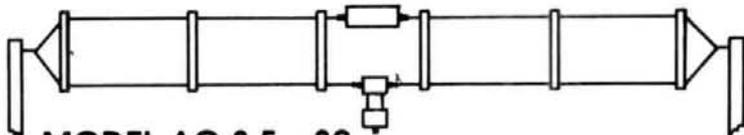CONTINUOUS COVERAGE FOLDED DIPOLE ANTENNA



MODEL AC 3.5 - 30
(formerly Model 370-15)

- Fully Assembled • 52 OHM • Only 90 feet long
- SWR less than 2:1 from 3.5 thru 30 MHz. Average SWR 1.4:1
- Will handle 1 KW power (2 KW PEP)
- Can be installed as flat top, sloper, or inverted "V"
- Used the world over in government & commercial communication installations
- Ideal for all operations - amateur, commercial, MARS - any frequency from 3.5 - 30 MHz

PRICE \$159⁵⁰

PLUS \$3.00 Shipping and Handling

PATENTED

ALL OUR PRODUCTS MADE IN USA



BARKER & WILLIAMSON

Quality Communication Products Since 1932
At your Distributors. Write or call.
10 Canal Street, Bristol PA 19007
(215) 788-5581



Crystal Filters

CW/SSB/AM For most
KENWOOD - YAESU - HEATHKIT

Also DRAKE R-4C/7 Line, COLLINS 75S-3B/C, and ICOM (FL44A Type)

FOX TANGO filters with center frequencies to match your set range in bandwidths from 125Hz for needle-sharp CW to 6000Hz for hi-fi AM. Use them to fill your optional filter spots, to replace inferior ceramic or monolithic stock units, or to add more I-F filtering for super-selectivity. Most are drop-in or plug-in type, if patch-in, all needed parts and instructions are supplied. Get genuine FT **matched-pair filter sets** (2 1 SSB and/or 400 CW) for your R820, TS830/930 or FT-980. Or a **Filter Cascading kit** for your TS430, TS520, TS 820; FT-101, 1012D, 107, 301, 901-2; or Heath SB-104A. Or **super-size** your R-4C with our GUF-1, 2 units. All kits include top-rated 8-pole discrete-crystal FOX TANGO filters. For complete details and prices send a business-size SASE marked with your rig's Make and Model Number. To save time, **phone for information and order directly**. We accept VISA/MC or ship C.O.D. in US.

FOX TANGO not only will meet or beat any currently advertised price for comparable units, but also offers quantity discounts. Order with confidence — our filters are guaranteed for ONE YEAR. *Why not check us out over the air?* You'll learn that FOX TANGO filters are **best**.

GO FOX TANGO — TO BE SURE!

FOX-TANGO Corp.

P.O. Box 15944, Dept. H
W. Palm Beach, FL 33416 ✓ 122
Telephone: (305) 683-9587

graphical selection of mixer frequencies

See, at a glance,
any spurious
that might
cause problems

Selecting the proper mixer frequencies can be a real problem. Often a lengthy trial-and-error procedure yields unsatisfactory results because of too many spurious signals in the passband. The graphical technique described here will deliver more accurate results in less time and with less difficulty. Some plotting is required, and a simple calculator will help with the math.

background

When two frequencies, f_1 and f_2 , are combined in a mixer, the nonlinear action of the mixer produces a series of products that have the form:

$$P = Mf_1 + Nf_2 \quad (1)$$

where M and N are positive or negative integers, and P is the frequency of the combination. In ordinary mixer use, a bandpass or low-pass filter removes all but the desired product P , called the desired output frequency, or f_0 . Generally, the larger M and N are, the smaller the amplitude of P . Then, too, the farther

a particular P is from f_0 , the less interference it will cause. One way to measure the frequency separation is to use the percentage separation, S , given by:

$$S = 100 \frac{P - f_0}{f_0} \quad (2)$$

Now, if f_1 is always chosen as the smaller of f_1 and f_2 , then the ratio f_1/f_2 can be given by:

$$f_1/f_2 = \frac{-S + 100(N - 1)}{S - 100(M - 1)} \quad (3)$$

where $f_0 = f_2 + f_1$

$$\text{or } f_1/f_2 = \frac{S + 100(1 - N)}{S + 100(1 + M)} \quad (4)$$

where $f_0 = f_2 - f_1$

Equations 3 and 4 are used to plot the spurious components, or spurs; eq. 3 is used for sum spur charts, and eq. 4 is used for difference spur charts. The case for $N = M$ appears as a vertical line on the sum chart at $S = 100(N - 1)$, and the case for $N = -M$ appears as a vertical line on the difference chart, also at $S = 100(N - 1)$.

conversion of fixed frequencies

Figure 1 shows a graph with several spur plots for $f_1 = 3$ MHz and $f_2 = 18$ MHz. Which ones need to be plotted? Well, that depends on how stringent your requirements are. Once you determine how low the spurs must be, you need plot only the spurs which

By G. Timothy Anderson, W2HVN,
902 Ashburn Street, Herndon, Virginia 22070

table 1. Typical values of spurious levels in a double-balanced mixer. Values shown are in dB below desired output. Here, f_2 is the local oscillator frequency.

| | f_2 | $2f_2$ | $3f_2$ | $4f_2$ | $5f_2$ | $6f_2$ |
|--------|-------|--------|--------|--------|--------|--------|
| $6f_1$ | 90 | 90 | 90 | 90 | 90 | 90 |
| $5f_1$ | 80 | 90 | 71 | 90 | 68 | 90 |
| $4f_1$ | 90 | 86 | 80 | 88 | 85 | 86 |
| $3f_1$ | 64 | 69 | 50 | 77 | 47 | 74 |
| $2f_1$ | 73 | 74 | 70 | 71 | 64 | 69 |
| f_1 | 0 | 35 | 13 | 40 | 24 | 45 |

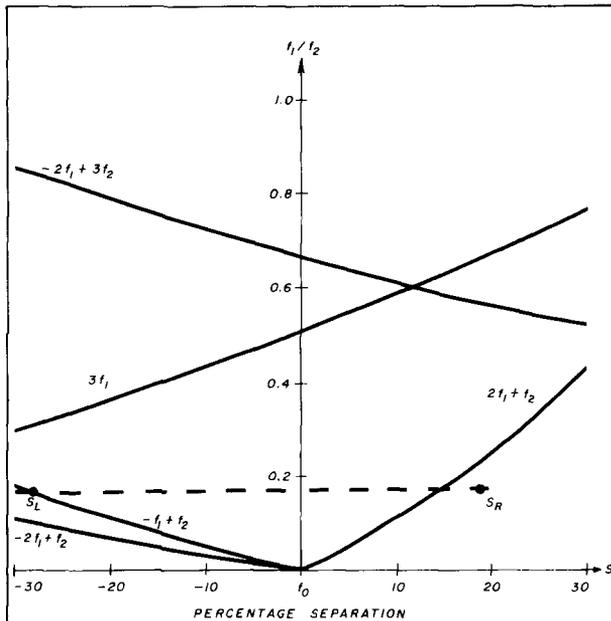


fig. 1. Spur chart for fixed-frequency conversion example: $f_0 = f_2 + f_1$.

might exceed that level. Some manufacturers provide tables of spur levels for different values of M and N . * **Table 1** shows some typical values.

To use a spur chart such as shown in **fig. 1**, you must somehow represent the bandwidth of the system. In **fig. 1**, this is done by plotting a dashed line representing an output frequency range for a given f_1 and f_2 . The end points are denoted by S_L and S_R .

$$S_L = 100 \frac{f_{0L} - f_0}{f_0} \quad (5)$$

and

$$S_R = 100 \frac{f_{0R} - f_0}{f_0} \quad (6)$$

*Mini-circuits, P.O. Box 166, Brooklyn, New York 11235, and Watkins-Johnson Company, 3333 Hillview Avenue, Palo Alto, California 94306, for example, furnish tables of this kind.

where f_{0L} and f_{0R} are, respectively, the low and high ends of the output passband. S_L and S_R are the abscissa values; the ordinate value, f_1/f_2 , is already known. Refer again to **fig. 1**. If, for example, an output passband of 10 MHz is chosen, from 15 MHz to 25 MHz, then $S_L = -28.6$ and $S_R = 19.0$. The ordinate is $f_1/f_2 = 3/18 = 0.17$. Note that two of the spurs intersect the bandwidth line, $-f_1 + f_2$ and $2f_1 + f_2$. This means that these two spurs are in-band harmonics. If the bandwidth was narrowed to, say, 5 MHz (18.5 MHz to 23.5 MHz), then the end points would be closer together and the spurs would be outside the passband. Note that if the slope of the filter is known, the attenuation of the out-of-band spurs can be calculated because **fig. 1** indicates how far out on the filter skirt the spurs are located. Of course, there is still the problem of the 18-MHz signal in the output. It, too, is a spur, and must be taken into consideration since it will be down probably no more than 50 dB.

conversion of bands of frequencies

Now that I've discussed a specific case with fixed frequencies, let's consider the general case — converting one band of frequencies to another band of frequencies where f_1 , f_2 , and f_0 have different bandwidths. Suppose you want to convert 300 MHz \pm 10 MHz to 200 MHz \pm 15 MHz by mixing with 100 MHz \pm 5 MHz. You have $f_{1L} = 95$ MHz, $f_{1H} = 105$ MHz, $f_{2L} = 290$ MHz, $f_{2H} = 310$ MHz, $f_{0L} = 185$ MHz, and $f_{0H} = 215$ MHz. First you'll outline the region you want to be free of spurs. (In general, this takes the shape of a hexagon with slightly curved sides. Since the curvature is slight, you can assume straight lines to ease the computations and still retain good accuracy.) This is done by using **eqs. 5** and **6** to calculate the corner points. Different combinations of the high and low extremes of f_1 and f_2 are used to find each particular f_0 . Here's how to do it (remember — $f_0 = f_2 - f_1$ here).

- Calculate: S_L using f_{1L} and f_{2H}
- S_L using f_{1H} and f_{2H}
- S_L using f_{1H} and f_{2L}
- S_R using f_{1H} and f_{2L}
- S_R using f_{1L} and f_{2L}
- S_R using f_{1L} and f_{2H}

These calculations produce the numbers shown in **table 2**, and the six points 1 through 6 in **fig. 2**; the dashed lines define the desired spur-free area. For this combination of frequencies, two spurs cross the hexagon. Either of two things can be done to resolve this. You can change the frequencies or try a high-level mixer with reduced drive, which will result in fewer spurs.

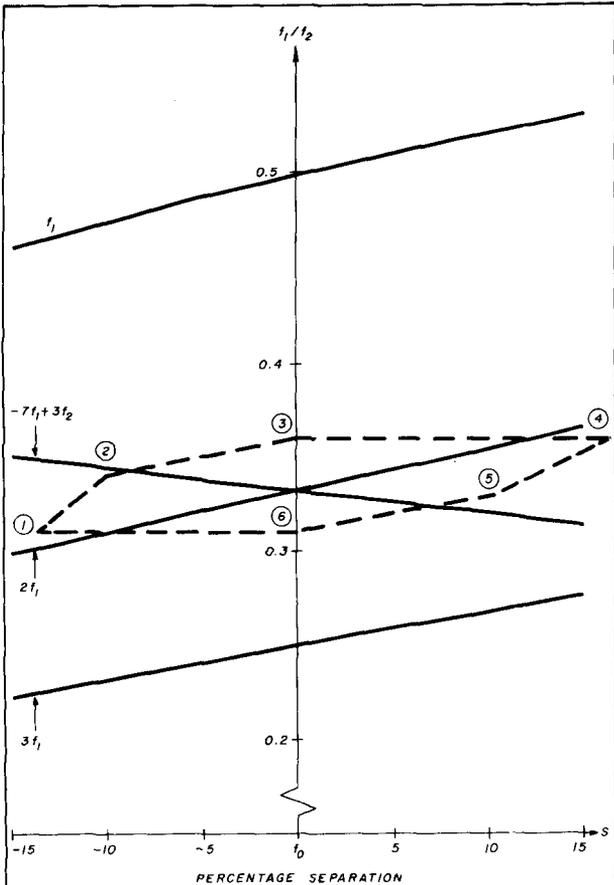


fig. 2. Spur chart for conversion of bands of frequencies — $f_0 = f_2 + f_1$. The circled numbers (1-6) are those referred to in the text and listed in table 2.

| point | S_L | S_R | f_1/f_2 |
|-------|--------|-------|-----------|
| 1 | -13.95 | - | 0.31 |
| 2 | -9.76 | - | 0.34 |
| 3 | 0.00 | - | 0.36 |
| 4 | - | 16.22 | 0.36 |
| 5 | - | 10.26 | 0.33 |
| 6 | - | 0.00 | 0.31 |

As a final example, let's try upconverting 28-32 MHz to 50-54 MHz by mixing with 22 MHz. Here, f_1 has zero bandwidth ($f_{1L} = f_{1H}$). This produces the dashed line (---) shown in fig. 3. Two things are evident: the hexagon is now a quadrilateral (because one of the frequencies, f_1 , has zero bandwidth), and one of the spurs cuts through this quadrilateral. If you select a different combination — say, $f_1 = 22.5$ MHz and $f_2 = 27.5 - 31.5$ MHz — then you get a quadrilateral as shown by the dashed-and-dotted line (---) in fig. 3. This new area is spur-free so the filtered output will be free of spurs.

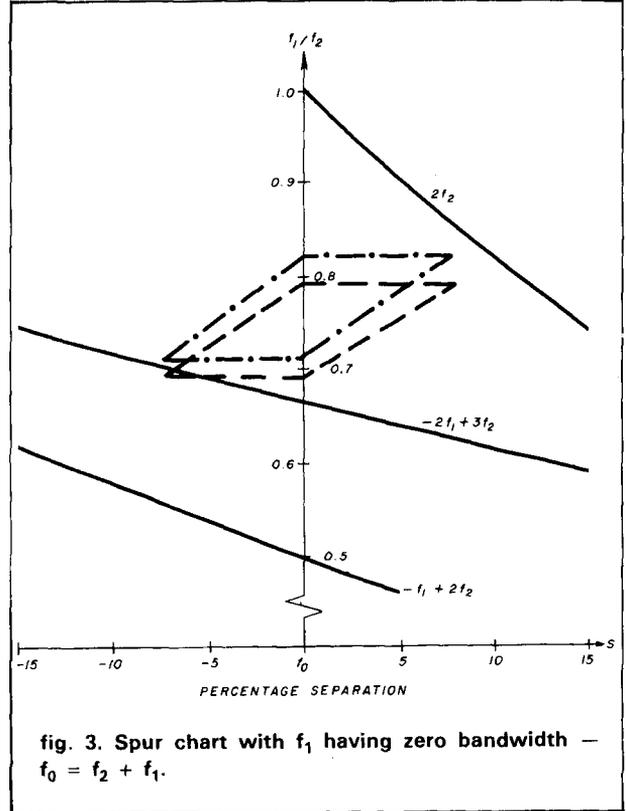


fig. 3. Spur chart with f_1 having zero bandwidth — $f_0 = f_2 + f_1$.

appendix

Equation 2 can be rewritten to give:

$$P = \frac{f_0 S}{100} + f_0 \quad (7)$$

For the case when $f_0 = f_2 + f_1$, inserting eq. 1 in eq. 7 yields $P = M(f_0 - f_2) + Nf_2$, or

$$f_2 = \frac{P - Mf_0}{N - M} \quad (8)$$

Equation 8 can be used in the expression for f_1/f_2 to eliminate f_2 :

$$f_1/f_2 = \frac{f_0 - f_2}{f_0} = \frac{Nf_0 - P}{P - Mf_0} \quad (9)$$

Now, if eq. 7 is inserted into eq. 9:

$$\begin{aligned} f_1/f_2 &= \frac{Nf_0 - (f_0 S/100 + f_0)}{f_0 S/100 + f_0 - Mf_0} \\ &= \frac{-S + 100(N - 1)}{S - 100(M - 1)} \end{aligned} \quad (3)$$

If $f_0 = f_2 - f_1$, a similar procedure gives:

$$f_2 = \frac{P + Mf_0}{N + M} \quad (10)$$

$$f_1/f_2 = \frac{P - Nf_0}{P + Mf_0} \quad (11)$$

and

$$f_1/f_2 = \frac{S + 100(1 - N)}{S + 100(1 + M)} \quad (4)$$


reference

1. M.Y. Huang et. al., "Select Mixer Frequencies Painlessly," *Electronics Design*, No. 8, April 12, 1976, pages 104-109.

ham radio

RAMSEY


THE FIRST NAME IN ELECTRONIC TEST GEAR

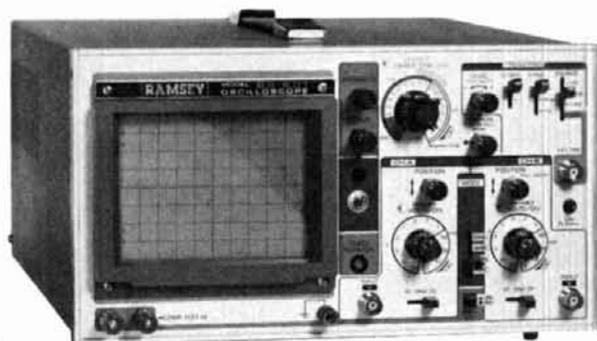

20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor, capacitor, digital circuit and diode testing • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering. *USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.

\$39995*

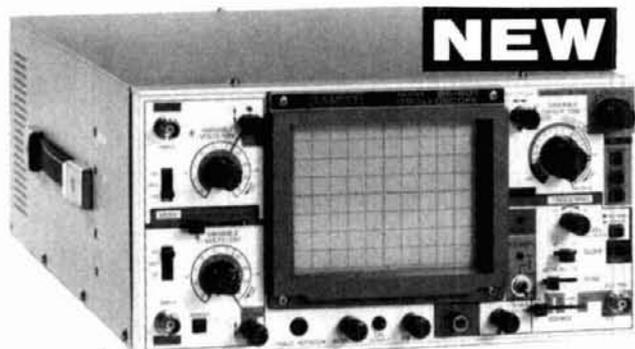

45 MHz DUAL SWEEP OSCILLOSCOPE

The Ramsey 625 is a dual time base, delayed sweep unit that includes a built-in signal delay line to permit clear viewing during very short rise times of high frequency waveforms. Other features include: variable trigger holdoff • 20 calibrated sawtooth time ranges from 0.5 μ s to 0.2 μ s/2 • fully adjustable sweep time • X5 sweep magnification • five trigger sources: CH1, CH2, LINE, EXTERNAL and INTERNAL (V mode) • front panel x-y operation, Z axis input • sum difference of CH1 and CH2 waveforms displayed as single trace • sweep gate and sweep output • auto focus • single sweep. *USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.

\$79995*



RAMSEY D-1100 VOM MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.


\$1995 test leads and battery included



NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include: decibel scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case.

\$2495 test leads and battery included

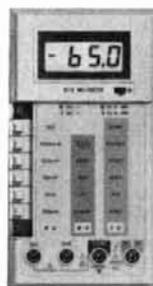

RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator.

\$4995 test leads and battery included



CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy.

\$11995 wired includes AC adapter

CT-70 kit \$99.95
BP-4 nicad pack 8.95



CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy.

\$14995 wired includes AC adapter

CT-90 kit \$129.95
OV-1 0.1 PPM oven timebase 59.95
BP-4 nicad pack 8.95



CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps.

\$16995 wired includes AC adapter

BP-4 nicad pack 8.95



CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy.

\$16995 wired

CT-50 kit \$139.95
RA-1 receiver adapter kit 14.95



DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity.

\$11995 wired includes AC adapter

DM-700 kit \$99.95
MP-1 probe set 4.95



PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiples UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner.

\$4995 wired

PS-2 kit \$39.95



PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp.

\$4495 wired includes AC adapter

PR-2 kit \$34.95



PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity, 25mV @ 150 MHz • BNC connectors • drives any counter.

\$5995 wired includes AC adapter

PS-1B kit \$49.95

ACCESSORIES FOR RAMSEY COUNTERS

- Telescopic whip antenna—BNC plug \$ 8.95
- High impedance probe, light loading 16.95
- Low pass probe, audio use 16.95
- Direct probe, general purpose use 13.95
- Tilt ball, for CT-70, 90, 125 3.95



PHONE ORDERS CALL
716-586-3950

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.

RAMSEY

RAMSEY ELECTRONICS, INC.
2575 Baird Rd.
Penfield, N.Y. 14626

Morse code computer tutor

Let your VIC-20
help you upgrade

For many Amateurs, it isn't theory or rules and regs that make upgrading difficult — *it's the code*. Jumping from a plateau of 10 words per minute or 18 words per minute seems impossible.

Satisfying these code requirements is even more difficult if you don't get enough practice. If CW isn't your favorite mode of operation, you're not likely to push yourself to practice on the air. Practice with code tapes can be productive — until you start memorizing them. And W1AW's code practice, while useful, may not always match your schedule or be strong enough to copy.

With this program (fig. 1), you can turn your VIC-20 personal computer into your own personal Morse code computer tutor. This tutor will give you all the practice you ask for at any time, at any speed, and always at Q5 conditions.

what the program does

The computer tutor sends groups of 20 random Morse code characters at any user-selectable speed starting at 4 words per minute. You type in the characters as they are sent. After the twentieth character the tutor identifies the random characters it has sent, and then lists your responses and your score. A particular advantage of this system of practice is that it forces you to copy Morse code with a keyboard; without a keyboard, few people can transcribe code at speeds greater than 25 WPM.

how the program works

After printing a sign-on message the program inputs the user-selected speed in line 5. Lines 6 through 9 initialize certain variables such as character counter, correct response counter, and character strings. Lines 20 through 91 are subroutines that store all the dot/dash patterns and their printable equivalents.

The selection of the random character and its conversion into Morse code begins at line 100. Here the program generates a random number between 1 and 36 inclusive. Lines 110 through 120 use the random number to select one of 36 characters — the letters

```
1 REM MORSE CODE COMPUTER-TUTOR
2 BY LAWRENCE G SOUDER, N3SE
3 PRINT "I WILL SEND A GROUP OF TWENTY CHARACTERS.
4 FOR SCORE HIT RETURN."
5 PRINT "HOW MANY WORDS PER      MINUTE DO YOU WANT?"
6 INPUT V
7 S = 27-V
8 C=0
9 Z=0
10 K$="": T$=""
11 GOTO 100
20 C$=".-A"
21 RETURN
22 C$="...B"
23 RETURN
24 C$="-.C"
25 RETURN
26 C$="..D"
27 RETURN
28 C$="E"
29 RETURN
30 C$="..F"
31 RETURN
32 C$="-.G"
33 RETURN
34 C$="...H"
35 RETURN
36 C$="..I"
37 RETURN
38 C$="---J"
39 RETURN
40 C$="-.K"
41 RETURN
42 C$="..L"
43 RETURN
44 C$="--M"
45 RETURN
46 C$="..N"
47 RETURN
48 C$="---O"
49 RETURN
50 C$="..P"
51 RETURN
52 C$="--Q"
53 RETURN
54 C$="..R"
55 RETURN
56 C$="...S"
57 RETURN
58 C$="T"
59 RETURN
60 C$="..U"
61 RETURN
62 C$="...V"
63 RETURN
64 C$="..W"
65 RETURN
66 C$="..X"
67 RETURN
68 C$="..Y"
69 RETURN
70 C$="---Z"
71 RETURN
72 C$="----1"
73 RETURN
74 C$="..--2"
75 RETURN
76 C$="...--3"
```

fig. 1. N3SE program for Morse code training and practice on the VIC-20.

By Lawrence G. Souder, N3SE, 4539 Manayunk Avenue, Philadelphia, Pennsylvania 19128

```

77 RETURN
78 C$="....-4"
79 RETURN
80 C$=".....5"
81 RETURN
82 C$="....6"
83 RETURN
84 C$="---.7"
85 RETURN
86 C$="----.8"
87 RETURN
88 C$="-----9"
89 RETURN
90 C$="-----0"
91 RETURN
100 R=INT(RND(1)*36)+1
103 IF C=20 GOTO 500
105 IF R > 21 GOTO 120
110 ON R GOSUB 20,22,24,26,28,30,32,34,36,38,40,42,
    44,46,48,50,52,54,56,58,60
115 GOTO 130
120 ON R-21 GOSUB 62,64,66,68,70,72,74,76,78,80,82,
    84,86,88,90
130 T$=T$+RIGHT$(C$,1)
131 C=C+1
134 C1$=RIGHT$(C$,1)
135 GOTO 200
140 GOTO 100
200 L=LEN(C$)
205 L=L-1
210 N=1
220 M$=MID$(C$,N,1)
230 N=N+1
240 GOSUB 400
250 IF L>N GOTO 220
260 FOR X=1TO10*S:GET L$
262 IF L$<>" " THEN K$=K$+L$
265 NEXT X
270 GOTO 100
400 S1=S
410 IF M$="-" THEN S1=7*S
420 POKE 36878,15
430 POKE 36875,240
440 FOR X=1TOS1*2: NEXT X
450 POKE 36878,0
460 FOR X=1TOS:GET L$
464 IF L$<>" " THEN K$=K$+L$
468 NEXT X
470 RETURN
500 INPUT R
505 FOR X=1 TO 20
510 IF MID$(T$,X,1)=MID$(K$,X,1) THEN Z=Z+1
520 NEXT X
525 PRINT " "
527 PRINT
530 PRINT T$
540 PRINT K$
545 PRINT
550 PRINT "YOUR SCORE IS ";100*(Z/20);"%
560 PRINT "AGAIN AT SAME SPEED?"
570 INPUT R$
580 IF R$="Y" GOTO 7
582 PRINT "AT DIFFERENT SPEED?"
584 INPUT R$
586 IF R$="Y" GOTO 3
590 END

```

A through Z and the numerals 0 through 9. For example, from the random number 7 these lines will select the character "G," which is held in **line 32**.

Before the dot/dash patterns are sent in Morse code, **line 130** separates the printable character from its Morse elements and saves it to be printed later. For example, it separates the letter "G" from the string "- .G". **Lines 131** through **265** take each dot and dash and call up a subroutine to output a tone of the proper duration. This subroutine is in **lines 400** through **470**.

*The heart-shaped graphic character in lines 2 and 525 is used to clear the screen in the VIC-20.


Two FOR-NEXT loops produce the delays for the dots and dashes and for the spaces between dots, dashes, and characters. During these delay loops the program inputs any response from the user. After 20 characters have been sent, **lines 500** through **550** compare the random characters sent with the responses typed in and print out both strings of characters along with the user's score. Then **lines 560** through **586** ask the user whether more practice is desired at the same speed, at a different speed, or not at all.

modifying and adapting the program

You might improve the program by adding some of the other characters such as punctuation. Do this by adding character string statements after **line 91**. Then extend the range of the random number generator by the same amount. For example, if you want to add a comma, add these lines after 91: 93 C\$="___,___"; 94 Return. Then change the random number generator in **line 100** to: 100 R = INT(RND(1)*37) + 1 to make its range 1 through 37 inclusive.

Now there's no excuse to put off upgrading. With this computer tutor you can get as much code practice as you need at any time — and improve your typing skills, too.

ham radio

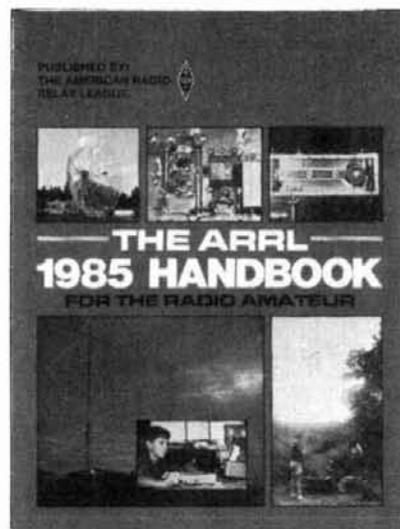

AVAILABLE
NOW

THE 1985
ARRL
HANDBOOK

\$15.00
(plus \$3.50 shipping)

1. It's BRAND NEW
2. It's BIGGER. Over 1024 pages.
3. It's EXPANDED. Covers everything from basic electronics to esoteric radio gear.
4. It's chockfull of NEW PROJECTS.
5. It's the MOST COMPLETE reference text available
6. Get your copy TODAY.

VISA ORDER YOURS TODAY

ham
radio magazine BOOKSTORE
Greenville, NH 03048

Prices US funds only

SAVE \$10.00* with home delivery

Payment enclosed
Bill me later

*One year newsstand cost \$30.00

Here's my address label, enter my subscription:
1 Year 12 issues \$19.95
2 Years 24 issues \$32.95
3 Years 36 issues \$44.95 U. S. prices only

Name _____

Zip _____

State _____

Address _____

City _____

Check here if this is your renewal (attach label)

Subscribe to **ham** **radio** magazine

Please allow 4-6 weeks for delivery of first issues.

Foreign rates: Europe, Japan and Africa, \$28.00 for one year by air forwarding service. All other countries \$22.95 for one year by surface mail.

Please
enter my
subscription



NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

First Class Permit No. 1 Greenville, NH

Postage Will Be Paid By Addressee

**ham
radio**

Greenville, NH 03048



in stock now

LUXOR 9550

A high performance 4 GHz, 70 MHz input receiver featuring programmable video and audio, hand held remote, four different audio systems, switchable audio bandwidths, built-in RF modulator, two speed scanning modes and built-in stereo processor.




Mark 2™

Offers independent channel selection for multiple TV sets from a single antenna, with a selection of up to 24 individual channels from a single satellite. The Mark 2 also features individually programmed audio, automatic fine tuning control, fine tuning storage, special function switches and built-in stereo processor.

SKANTIC

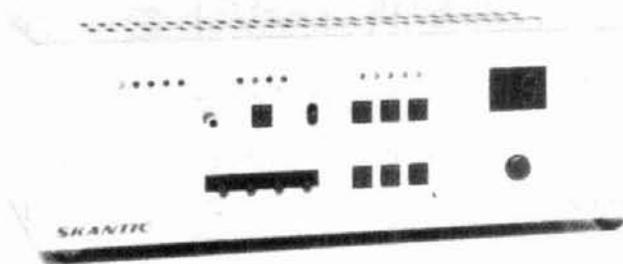Offers versatility and quality performance including fine tuning and video, automatic audio and video digital memory, automatic polarization and four programmable audio modes.



The Northeast's Leading Distributor



Sales and Marketing Assistance
Factory Authorized Service
Professional Training Seminars
Co-op Advertising Support
Automated UPS Shipping

Satellite Video
Services, Inc.

RR #1, Box 85-S
Catskill, NY 12414

518-678-9581

800-528-DISH - National
800-831-DISH - NY Only

Satellite Video
Services NH, Inc.

RFD #2, Harriman Hill Rd.
Raymond, NH 03077

603-895-3182

800-448-0012 - National

Satellite Video
Services PA, Inc.

317 E. Pleasant Valley Blvd.
Altoona, PA 16602

814-942-5003

800-242-3860 - PA Only

Satellite Video
Services WNY, Inc.

East Avenue Extension
Hornell NY 14843

607-324-3435

800-641-0018 - NY Only

Uniden M/A Com Intersat Gensat Houston Tracker Winegard Conifer Laux Orbitron Kent Surveyor

TNT RADIO SALES INC.**1-800-328-0250**

1-612-535-5050

(IN MINNESOTA—COLLECT)

**YOU GET MORE "BANG FOR YOUR BUCK"
AT TNT RADIO SALES!**

- | | | | |
|--------------|----------------|---------------|-------------|
| ■ Kenwood | ■ Mirage | ■ MFJ | ■ Welz |
| ■ Icom | ■ KLM | ■ Astron | ■ Azden |
| ■ Bencher | ■ Telex Hygain | ■ Alpha/Delta | ■ Santec |
| ■ AEA | ■ Nye Viking | ■ Bearcat | ■ KDK |
| ■ Kantronics | ■ Larsen | ■ Regency | ■ Ameritron |

**SALES AND SERVICE AT PRICES YOU CAN AFFORD!
CALL OUR WATS LINE FOR LOW LOW PRICES!**

SPECIAL OF THE MONTH: LARSEN MAG MOUNT 2M 1/2 PKG—\$36.95

VISA/MASTER CARD
FREE SHIPPING
ON MOST RIGS FOR CASH!



S.A.S.E. FOR OUR
"BENCH-TESTED"
USED EQUIPMENT LISTING

MON-FRI 9 AM - 6 PM CENTRAL TIME
SATURDAY 9 AM - 5 PM

4124 West Broadway, Robbinsdale, MN 55422 (Mpls./St. Paul)

✓ 124

Your Ham Tube Headquarters!

TUBES BOUGHT, SOLD AND TRADED
SAVE \$\$\$—HIGH \$\$\$ FOR YOUR TUBES

Call Toll Free 800-221-0860

Tubes

| | |
|--------------------|------------------|
| 3-400Z.....\$85.00 | 7360.....\$10.00 |
| 3-500Z.....85.00 | 7735A.....27.50 |
| 4-400A.....80.00 | 8122.....110.00 |
| 4CX250B.....50.00 | 8156.....12.50 |
| 572B.....55.00 | 8643.....82.50 |
| 811A.....12.00 | 8844.....26.50 |
| 813.....30.00 | 8873.....175.00 |
| 6146B.....6.50 | 8874.....195.00 |
| 6360.....4.25 | 8877.....500.00 |
| 6883B.....6.75 | 8908.....12.50 |

MAJOR BRANDS ON RECEIVER TUBES 75% off list

Semiconductors

| | |
|--------------------------|------------------|
| MRF 245/SD1416...\$30.00 | SD1088.....19.95 |
| MRF 454.....14.95 | 2N3055.....75¢ |
| MRF 455.....10.95 | 2N6084.....12.50 |

RF Connectors

| | |
|------------------------|------------------------|
| PL259.....10/\$4.95 | M358.....2.50 ea. |
| PL258.....10/8.95 | M359.....1.75 ea. |
| UG 175/176.....10/1.60 | Type "N" Twist on |
| UG255/u.....2.50 ea. | (RG8/u).....\$4.75 ea. |
| UG273/u.....2.25 ea. | Minimum Order \$25.00 |

Allow \$3.00 min. for UPS charges ✓ 125

COMMUNICATIONS, Inc.
2115 Avenue X Brooklyn, NY 11235

SERVING THE INDUSTRY SINCE 1922

Phone (212) 646-6300

Call CECo For Your CCTV Security And Color Production Requirements



15th ANNUAL INDIANAPOLIS HAMFEST™

And INDIANA STATE ARRL CONVENTION

Marion County Fairgrounds

July 13-14, 1985

FREE:

Parking
Kids Prize Drawings
Camping
Womens Prize Drawings

2 Full Days of:
Commercial Exhibitors
Large Flea Market
Hourly Prize Drawings
Forums

Indiana's Largest Electronic Flea Market and Amateur Radio Display

INDIANAPOLIS HAMFEST, P. O. Box 11776, Indianapolis, IN 46201
OR CALL: (317) 894-8522



ham radio TECHNIQUES

Bill Over
W6SAI

As this issue went to press, U.S. Amateurs received FCC approval to operate on the new 12-meter band (24.89-24.99 MHz) as of June 22. Unfortunately, we're approaching a sunspot minimum and the band will be relatively worthless for long-distance skip communication. But all is not lost — good contacts can be had by sporadic-E skip, and once in a while an unusual burst of activity from the sun will open the band for DX for a few hours. In any event, it's a good idea to get on the band and enjoy this new chunk of spectrum as soon as operation is authorized.

I've monitored the band for years and have heard plenty of DX when conditions were good. Over 40 countries are licensed for operation on the 12-meter band. See how many of them you can hear and work! Even at the low point of the sunspot cycle, the north-south path isn't bad, and you should be able to work some South American Amateurs when the band opens up.

antennas for 12 meters

Amateurs who have an "all-band" antenna with a tuner at the operating position can get on the band immediately. Others will have to improvise. One quick way to get on the air is to string up a dipole or inverted-V to your tower and feed it with a separate coax line as shown in fig. 1. The higher you can get it in the air, the better the results.

Another easy-to-erect antenna is a ground plane (fig. 2). As in the case

of the dipole, the higher you can erect it, the better it will work. If you have time to build a beam for the band, fig. 3 provides dimensions for a quad antenna and fig. 4 provides Yagi information.

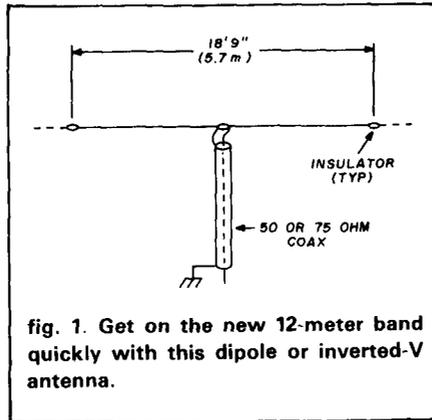


fig. 1. Get on the new 12-meter band quickly with this dipole or inverted-V antenna.

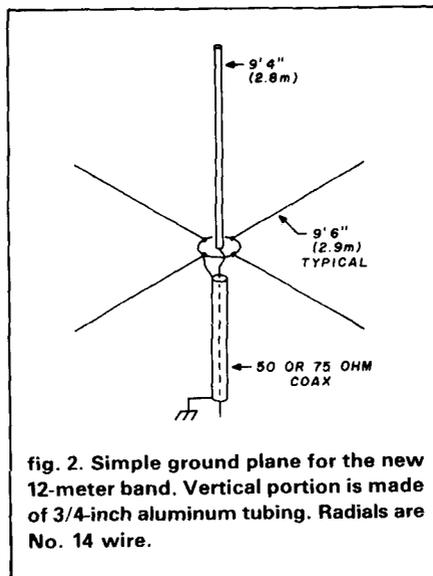


fig. 2. Simple ground plane for the new 12-meter band. Vertical portion is made of 3/4-inch aluminum tubing. Radials are No. 14 wire.

the G8PO "JAWS" antenna

G8PO has discussed an interesting variation of the quad loop that has provided superior results on 7 MHz (fig. 5).¹ Mast height is less than that required for the conventional loop as the bottom portion is bent out of the vertical plane. The antenna is fed at one corner by a gamma match system to provide a good match to a coax line. Antenna polarization is vertical.

The lower portion of the loop has three conductors in parallel, running nearly horizontal to the ground. Tests indicated improvement in performance over the England-New Zealand test path and some front-to-back signal discrimination became apparent.

Checks against a conventional loop over the same path showed that the regular loop was consistently weaker during many contacts. The forward gain of the JAWS antenna was estimated to be 3 dB or better, and the front-to-back ratio was about 6 dB.

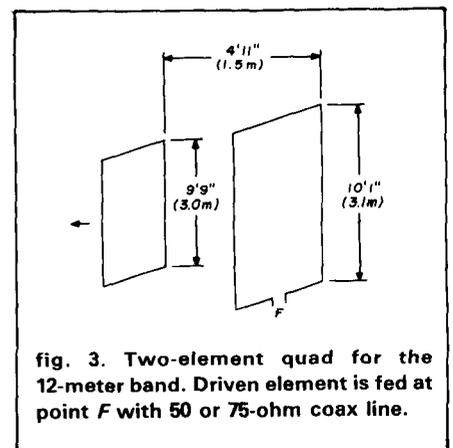


fig. 3. Two-element quad for the 12-meter band. Driven element is fed at point F with 50 or 75-ohm coax line.

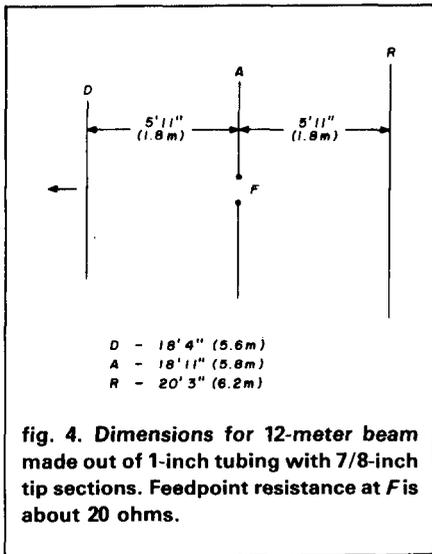


fig. 4. Dimensions for 12-meter beam made out of 1-inch tubing with 7/8-inch tip sections. Feedpoint resistance at F is about 20 ohms.

The gamma match is made of wire, with the gamma section measuring about 6.5 feet (1.98 meters) long and spaced away from the loop wire about 4 inches (10 cm). The gamma capacitor is 200 pF.

the multiband antenna

Independent experimenters have discovered that altering the shape of a driven element can change the harmonic resonance without appreciably altering the fundamental resonant frequency of the antenna. This is a good technique to use for a two-band antenna. A typical linear element of uniform diameter, unfortunately, does not exhibit resonance on the exact harmonic frequencies because of end effects. A 7-MHz dipole, for example, is *not* resonant in the 21-MHz band.

However, by changing the shape of the element, the third harmonic resonant frequency can be lowered without changing the fundamental frequency to any great extent. The principle is illustrated in **fig. 6**. The vertical antenna element **A** exhibits a quarter-wave resonance at 3.6 MHz. By formula, the antenna is 65 feet (19.81 meters) high. The third harmonic resonance, by formula, falls at 11.6 MHz. The actual third harmonic of 3.6 MHz, however, is 10.8 MHz. Thus there is a difference of 800 kHz between the actual third harmonic of the funda-

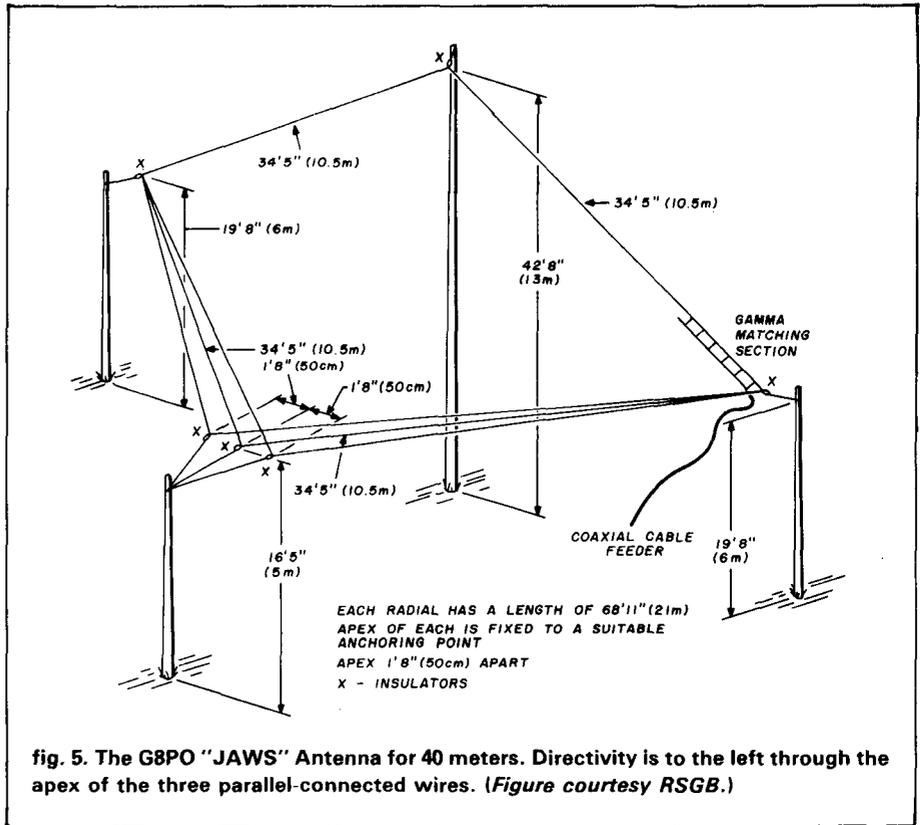


fig. 5. The G8PO "JAWS" Antenna for 40 meters. Directivity is to the left through the apex of the three parallel-connected wires. (Figure courtesy RSGB.)

mental frequency and the third harmonic resonance of the vertical.

If the vertical resonance at the third harmonic region could be "pulled" down to 10.1 MHz, then the antenna could operate in the 30-meter ham band (10.1 to 10.15 MHz). Can this be done without disturbing the resonance in the 80-meter band?

Figure 6B shows the technique to accomplish this. The antenna element is made "fatter" near the area of maximum third harmonic voltage. This provides additional capacitance to ground at this frequency. On the fundamental frequency, the voltage is much lower at this point in the antenna element and the capacitive effect to ground is much less. In this manner the third harmonic resonance frequency is lowered without too much effect on the fundamental frequency.

Shown in **fig. 7** is an antenna developed by K6KBE for two-band operation. A three-legged tower having a very thin upper portion and a tapered lower section, this antenna shows resonance on both the 80 and 160-meter bands (**fig. 8**).

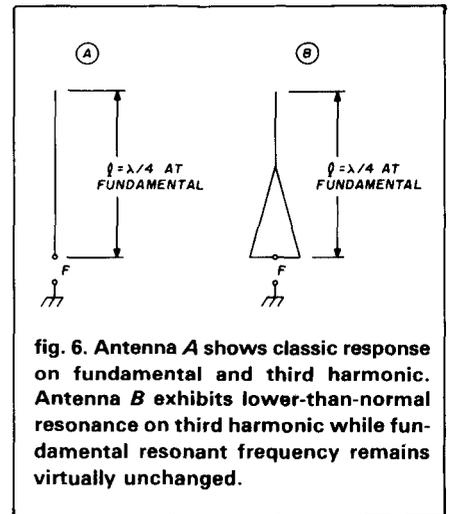


fig. 6. Antenna **A** shows classic response on fundamental and third harmonic. Antenna **B** exhibits lower-than-normal resonance on third harmonic while fundamental resonant frequency remains virtually unchanged.

The tower is 132 feet (40.2 meters) high with a base 12 feet (3.66 meters) on a side. The design frequencies are 1.85 and 3.7 MHz. The SWR across the 160-meter band is less than 1.8:1 at the band edges and below 1.5:1 from 3.5 to 3.9 MHz, rising to 2.3:1 at 4 MHz.

The top 44 feet (13.41 meters) of the antenna consists of a flexible aluminum whip, 2 inches (5.08 cm) in diam-

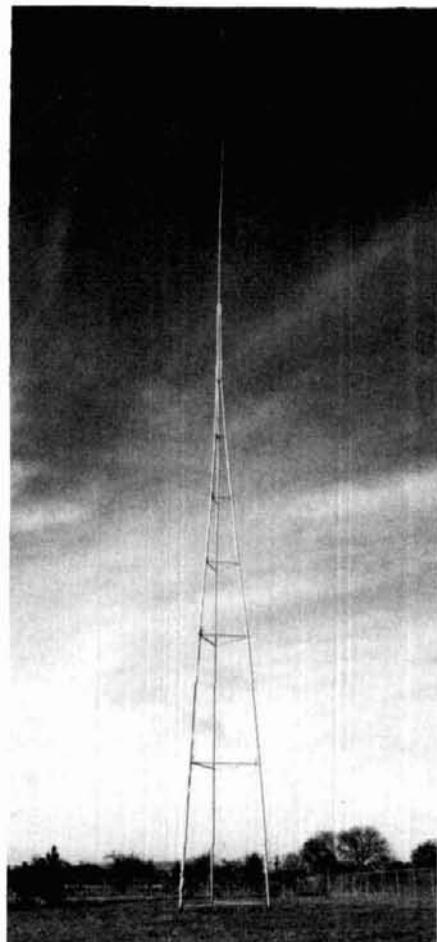
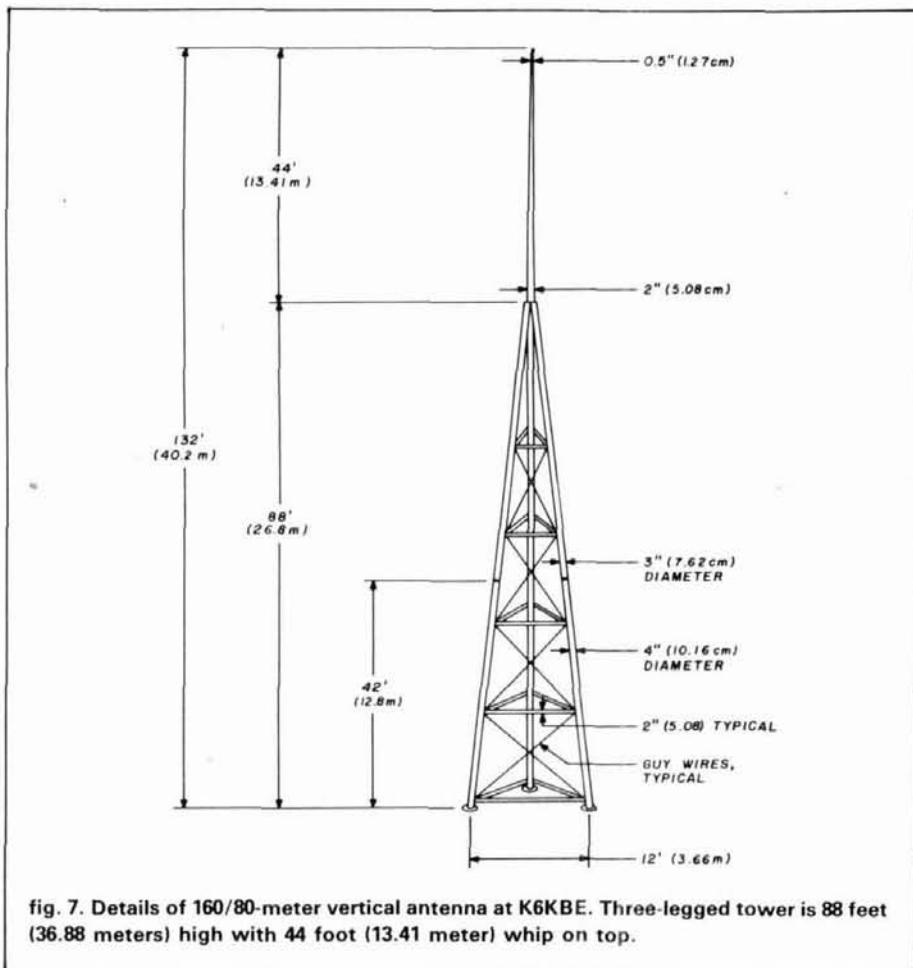


fig. 8. The self-supporting 160/80-meter vertical antenna at K6KBE.

eter at the butt, tapering to 0.5 inch (1.27 cm) at the tip. The whip is actually 2 feet (61 cm) longer than this, with the extra length forming the joint to the main tower, which is 88 feet (26.82 meters) high.

The bottom 42 feet (12.8 meters) on the tower is made of aluminum tubing 4 inches (10.16 cm) in diameter, with a 0.093 inch wall thickness. The top portion [to the 88 foot (26.8 meters) level] is made of 3-inch (7.62 cm) diameter tubing having a 0.063 inch wall. The cross-guys are made of 0.25 inch (1.27 cm) aircraft cable. Turnbuckles permit the assembly to be tightened by the assembler until a very rigid structure is achieved.

Anyone who has heard K6KBE's signal on 80 or 160 meters knows this antenna works!

speaking of radials . . .

I just got a note from WA6BAN tell-

ing me more about his experiments with his 40-meter vertical ground plane antenna. He put it up with three radials, setting the base of the antenna a few feet above ground level. After he achieved resonance, he measured the feedpoint resistance with a General Radio RF Bridge. The result was about 58.3 ohms. He added a few more radials and the feedpoint resistance dropped to 53 ohms. Three more radials brought the resistance down to 51 ohms. Finally, he added more radials until he had eleven, and the feedpoint resistance dropped to 45 ohms.

His conclusion was that when the ground plane antenna is mounted close to the surface of the ground, you need "a lot more" than eleven radials to approximate a feedpoint impedance of 36 ohms. W2FMI, in his classic *QST* series on ground plane antennas,² came to the conclusion that sixty radials were required when they were laid

on the surface of the ground.³ When elevated radials are installed a few feet above the ground, it is possible that fewer will do the job. The correct number seems to be between eleven and sixty! (Anybody out there have a closer "fix" on this?)

broadcast filter for 160 or 80 meters

If you live in a residential or urban area, you can experience severe crosstalk and overload problems from local broadcast stations if you attempt to operate on 160 or 80 meters. (A friend of mine, located a few miles away from a local broadcast station, measured over 4 volts of RF pickup on his 80-meter vertical antenna. It completely locked up his receiver.)

Designed by K6KBE, the filter shown in fig. 9 is an adaptation of the

New From Butternut® HF2V DX The 80 & 40 Meter Bands



The HF2V is the perfect complement for the Ham who already has a beam antenna for 10-15-20 meters. Add 80 and 40 meters (160 meters with an optional resonator kit) with a trim-looking vertical that can be mounted almost anywhere.

With the decline in sunspot activity, the HF2V's low angle of radiation will get you DX on the low bands -- even when 10-15-20 meters are "dead."

Automatic bandswitching. No lossy traps. Double wall tubing on the bottom section. Stainless steel hardware. Full 1/4 wavelength on 40 meters.

Height: 32 ft. --Self supporting

Power rating: legal limit

VSWR: 2:1 or less

40 Meters: Full CW & Phone band

80 Meters: 90 kHz


Add-on resonator kits available for 160-30-20 meters.

Write for our FREE CATALOG.



BUTTERNUT ELECTRONICS

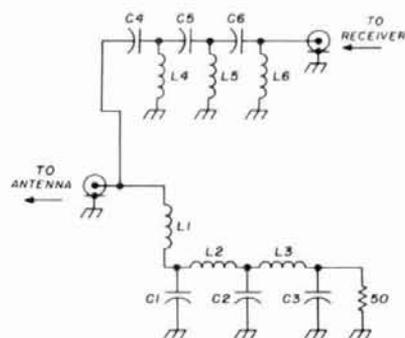405 East Market Street
Lockhart, Texas 78644
(512) 398-9019



Except as indicated, decimal values of capacitance are in microfarads (μF); others are in picofarads (pF); resistances are in ohms. $k = 1,000$ $M = 1,000,000$

| | 160M | 80M |
|----|-------|------|
| C1 | 3385 | 1862 |
| C2 | 2318 | 1275 |
| C3 | 500 | 275 |
| C4 | 1242 | 683 |
| C5 | 1242 | 683 |
| C6 | 2554 | 1404 |
| L1 | 7.5 | 4.1 |
| L2 | 7.5 | 4.1 |
| L3 | 3.64 | 2.0 |
| L4 | 2.75 | 1.5 |
| L5 | 4.01 | 2.2 |
| L6 | 18.63 | 10.2 |

C - pF L - μH

fig. 9. Broadcast filter for 160 or 80 meters.

absorption filter originally used where suppression of harmonic energy is desired. In its original configuration, there are two complementary filters consisting of a high pass section terminated in a resistor and a low pass section to pass the desired signal. In this case, the reverse idea is used so that all energy *below* cutoff is routed to a dummy load while all energy above is allowed to pass.

The cutoff frequency for the 160-meter filter is 1.65 MHz; for the 80-meter filter, it's 3 MHz.

references

1. This material is extracted from "The G8PO JAWS Antenna," by Cdr. J.E. Ironmonger, G8PO, *Radio Communication*, November, 1984, pages 954-957. (Don't ask me what JAWS stands for -- I can't figure it out either!)
2. Jerry Sevick, W2FMI, "The ground-image Vertical Antenna," *QST*, July, 1971, page 16.
3. For more information on ground radials and verticals in general see the K2BT series of articles on phased arrays, *ham radio*, May, June, July, October, December, 1983 and May, 1984 -- Ed.

ham radio

GROTH-Type

**COUNTS & DISPLAYS
YOUR TURNS**

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

TC2 \$12.50
TC3 \$13.50
Spinner Handle Add \$1.50

Prices include UPS or Parcel Post in US

Model TC2: Skirt 2-1/8"; Knob 1-5/8"
Model TC3: Skirt 3"; Knob 2-3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

10 METER F.M.

29.310-29.700 MHz in 10 kHz Steps. 100 kHz Repeater Split provided. 4W RF Out. 0.3 μV for 12 dB Sinal. c/w Mic, mobile cradle etc.



VISA CARD
MASTER CARD
I.M.O. DRAFT

\$79

AIR POST
PREPAID
WORLDWIDE

S.M.C. Ltd., Totton, Southampton, SO4 4DP, U.K.

✓ 129



\$1295

HAM-TAGS
Amateur Radio
standard for mobiles!

HAM-TAGS Your call on each vehicle. Call at top or bottom of frame, and frame/front plate. No-nonsense, full refund, guarantee. \$1.50 shipping (First Class Mail).

B-C 1716 Woodland, Houston, TX 77019 (713) 522-5755

✓ 130

PACKET MADE

Easy



Suggested Retail \$389.95

Kantronics Packet Communicator™

Kantronics wants you to join one of the fastest growing segments of Amateur Radio today . . . Packet Radio. With the Kantronics Packet Communicator we've made getting on Packet as easy as getting on RTTY.

1 Ready to Use

The Kantronics Packet Communicator is a fully assembled and programmed terminal node controller ready for operation. Simply connect the Packet Communicator to the Serial TTL or RS232 port of your computer, and the microphone and external speaker jacks of your transceiver. The power supply, cables, and most connectors are included.

2 Compatibility Plus

The Kantronics Packet Communicator has both the AX.25 and Vancouver protocols, making it compatible with most existing Packet terminal node controllers. Added features include both Bell 103 and 202 tones, and the ability to use the unit as a 1200 baud radio modem without special protocols.

3 Easy to Operate

Because the Kantronics Packet Communicator uses internal microprocessors for protocol and signal processing, the operator simply follows procedures and commands outlined in the operators manual.

Any communications or terminal program, like those used with telephone modems, can be used to set up the computer to communicate with the Packet Communicator. Special Packet Terminal (Packet-Term™) programs for many popular personal computers will be available soon from Kantronics.

Error free data communication via computer makes Packet Radio technology exciting, and the Kantronics Packet Communicator lets you get in on the action.

For more information contact your local Kantronics dealer, or write Kantronics.

Kantronics

1202 E. 23rd Street (913) 842-7745
Lawrence, Kansas 66046

ROHN®

brings the top to you

ROHN brings the top to you with its patented design. For the ultimate "on the ground" service and antenna installation, a ROHN "Fold-Over" Tower is your best buy. Your safety comes first with "Fold-Over." For complete details write:

ROHN®

"FOLD-OVER" TOWERS

P.O. BOX 2000, PEORIA, IL 61656 U.S.A.
TWX: 910-652-0646 FAX: 309-697-5612

RF Porta-Tenna

VHF/UHF Telescopic 1/4 & 5/8 Wavelength Antennas for Hand-Held Transceivers & Test Equipment

1/4 WAVELENGTH

| Model No. | Freq. MHz | Description | Price |
|-----------|-----------|------------------------|--------|
| 196-200 | 144-148 | 5/16-32 stud w/spring | \$5.95 |
| 196-204 | " | BNC connector w/spring | 7.95 |
| 196-214 | " | BNC connector | 6.95 |
| 196-224 | 144-UP | BNC conn. adj. angle | 7.95 |
| 196-814 | 220-225 | BNC connector | 6.95 |

5/8 WAVELENGTH

| | | | |
|---------|---------|-----------------------|-------|
| 191-210 | " | 5/16-32 for old TEMPO | 22.95 |
| 191-214 | " | BNC connector | 19.95 |
| 191-219 | " | PL-259 w/M-359 adpt. | 22.95 |
| 191-810 | 220-225 | 5/16-32 for old TEMPO | 22.95 |
| 191-814 | " | BNC connector | 19.95 |
| 191-940 | 440-450 | 5/16-32 for HT-220 | 22.95 |
| 191-941 | " | 1/4-32 stud | 22.95 |
| 191-944 | " | BNC connector | 19.95 |

Largest Selection of Telescopic Antennas. Write for Info. Prices are postpaid via UPS to 48 States. For air delivery via UPS Blue add \$2.25. Florida add 5% sales tax. Payment by M.O. or Cashiers Check only.

✓ 132

RF PRODUCTS

P.O. Box 33, Rockledge, FL 32955, U.S.A.
(305) 631-0775

Inter-Ear-Communication-System

A space age system that allows you to send and receive your message through your ear and leave your hands free.



- Replace your HT's awkward speaker-microphone with an n-ear-microphone.
- Discrete HT communications leaves you with both hands free.
- Allows voice communications in noisy environments.
- Our n-ear-talk interfaces with almost all HT's, which have external speaker microphone output jacks.
- Custom hybrid circuit.
- Low power consumption. Transmits at 5mA and less than 10uA when receiving.
- One year warranty.

Dealer inquiries are invited.

IECS-200



\$99.95 includes IECS-200 control unit, Ear transducer, 9V battery, 6-pin output connector and Instruction sheet. (Add 6% sales tax for California residents.)

Custom made interface cable for TEMPO S-15 and all ICOM HTs are available at \$19.95

FOR ALL PREPAID ORDERS, SHIPPING AND HANDLING CHARGE WILL BE PAID BY N-EAR-TALK.

ACE communications, inc.

22511 Aspan Street • Lake Forest • Calif. 92630-6321
(714) 581-4900 Telex 29-7385 ACE UR Fax (714) 768-4410



July 27 thru Aug. 9, 1985

Our 26th year

TAKE A VACATION WITH A PURPOSE THIS YEAR

Join students from around the world at OAK HILL ACADEMY AMATEUR RADIO SESSION

Instructors CERTIFIED VE's

Over 25 years of successful teaching experience means upgrading is as easy as 1-2-3.

Your vacation is spent in the beautiful Blue Ridge Mountains of Virginia with expert instructors in friendly surroundings and with excellent accommodations.

Oak Hill also has a ham lab set up for all to use.

Courses offered are:

- Novice to General
- General or Tech to Advanced
- Advanced to Extra

Learn — don't just memorize the answers to the exam questions.

C. L. PETERS, K4DNJ, Director
Oak Hill Academy Amateur Radio Session
Box 43
Mouth of Wilson, VA 24363

Name _____ Call _____

Address _____

City/State/Zip _____



ICOM

KENWOOD YAESU



Regular SALE
 IC-751 9-band Xcvr/1-30 MHz Rcvr. \$1399.00 Call
 IC-745 9-band Xcvr/1-30 MHz Rcvr. \$ 999.00 Call



IC-271H 100w 2m FM/SSB/CW Xcvr. \$899 Call
 IC-271A 25w 2m FM/SSB/CW Xcvr. \$699.00 Call
 IC-471A 10w430-450 SSB/CW/FM Xcvr \$799.00 Call



IC-02AT Call
 IC-04AT Call
 IC-2AT Call
 IC-3AT Call
 IC-4AT Call

**IC-R71A
GENERAL
COVER RCVR**



Regular SALE
 TS-930S/AT \$1799.00 Call
 TS-930A \$1599.00 Call



TS-711A TS-811A Call



TR-2600A Call
 TH-21A Call
 TH-21AT Call
 TH-41A Call
 TH-41AT Call

**R-2000
GENERAL
COVER**



Regular SALE
 FT-980 \$1659.00 Call
 FT-980G Call



FT-726R \$ 899.00 Call



FT-209RH Call
 FT-709RH Call
 FT-203RH Call
 FT-103R Call
 FT-703R Call

**FRG-8800
GENERAL
COVER RCVR**



**SALE!!
NEW RTTY/CW
COMPUTER
INTERFACES**



BIRD



FREE PB-26
with the purchase of
a TR-2600A

FREE PB-21
with the purchase of
a TH-21AT

**MIRAGE
AMPLIFIER
SALE!**



**AMERITRON
AL-80**



JUN'S
ELECTRONICS
 Calif. Call Collect for Order
 800-882-1343
 INCLUDES ALASKA HAWAII

●AMATEUR ●TWO WAY ●MARINE
 ●CELLULAR MOBILE PHONE ●SCANNER
 ★ Free U.P.S. Cash Order (Most Item, Most Place)
 ★ Shoppers, call us last, save \$\$
 ★ SE HABLA ESPANOL

(213)390-8003 3919 Sepulveda Blvd. Culver City, CA 90230



PACKET RADIO THRU SOFTWARE

AX.25 Protocol By Bob Richardson, W4UCH

You can get on Packet Radio two ways. One is with a sophisticated "black box". The other is by making your computer act like a "black box" by programming it in a high level machine language code. W4UCH has written a machine language program for the Radio Shack TRS-80 Models 1, 3 and 4 computer (Model 4 works with Model 3 disk while in Model 3 mode). This book has twelve chapters plus seven appendices that take you step by step through the process of setting your computer to first convert the digital information into a usable format and then to decode the information.

© 1984 3rd edition

RE-AX Softbound \$21.95
 PROGRAM NOW AVAILABLE IN DISK FORM
 RE-MI Model 1 Disk \$29.00
 RE-MIII Model III & 4 Disk \$29.00
 RE-BD SPECIAL BOOK AND DISK \$49.95

(Specify disc; Mod. I or Mod. III) **SAVE \$2**

Please add \$3.50 for shipping

ham
 radio magazine
 GREENVILLE, NH 03048

BOOKSTORE
 (603) 878-1441

ANTI-STATIC DUST COVERS

for New & Old Model Amateur Radios, Computers, Disk Drives, also Custom Made. Over 1 Million in use. Send for Brochure.

Radio Covers Available:

| | | | |
|---------|--------------|---------|-----------|
| Alpha | Halicrafters | ICOM | Panasonic |
| Bearcat | Heath | Kenwood | Robot |
| Collins | Henry | MJF | Swan |
| Dentron | | | Ten-Tec |
| Drake | | | Yaesu |



BIRCH HILL SALES, P.O. Box 129, Milford, NH 03055 Tel. (603) 673-8907

THE DR10

ONLY ONE ANTENNA ROTATION SYSTEM IS TRULY COMPLETE AND SIMPLE TO INSTALL: THE DR10

The DR10 System offers a compact, single control unit with dual scale indicator; single, eight-wire control cable interconnect*; and will easily handle a 50 pound balanced antenna array and up to 8 sq. feet of wind load.

*One Rotor,
One Controller,
One Installation*

The DR10 Dual Axis Antenna Rotor System
A New Concept in Drive Systems

DYNETIC SYSTEMS

*not included

Call or Write for More Information.
Dealer Inquiries Invited

19128 Industrial Blvd.
Elk River, MN 55330 (USA)
612-441-4303 Telex 756135

✓ 136

CALL LONG DISTANCE ON 2 METERS

Only 10 watts drive will deliver 75 watts of RF power on 2M SSB, FM, or CW. It is biased Class AB for linear operation. The current drain is 8-9 amps at 13.6 Vdc. It comes in a well constructed, rugged case with an oversized heat sink to keep it cool. It has a sensitive C.O.R. circuitry, reliable SO-239 RF connectors, and an amplifier IN/OUT switch. The maximum power input is 15 watts.



Our products are backed by prompt factory service and technical assistance. To become familiar with our other fine products in the amateur radio market, call or write for our free product and small parts catalog.

Model 875
Kit \$109.95
Wired & Tested \$129.95




CCI Communication Concepts Inc.

2648 North Aragon Ave. • Dayton, Ohio 45420 • (513) 296-1411



VOICE OPERATED SQUELCH

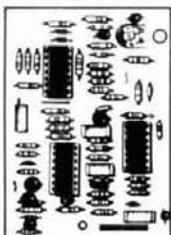- Fits inside most HF-SSB transceivers.
- Requires human voice to activate.
- Ignores static, noise and heterodynes.
- Connects to audio leads and 9/12 VDC.
- Fully assembled and tested \$99.95.
- Complete comprehensive manual.
- Used worldwide in commercial and military transceivers.



✓ 139
COMMUNICATIONS

5479 Jetport, Tampa, FL 33614 • (813) 885-3996

VHF COMMUNICATIONS

ICOM DAY

VHF COMMUNICATIONS

G.R.A.M. BATAVIA HAMFEST • SUN., JULY 14, 1985

Contact us for all of your amateur radio needs.....
FEATURING:

ICOM, AEA, LARSEN, VAN GORDEN, VIBROPLEX,
NYE-VIKING, FALCON COMM. LEADING EDGE,
ARRL PUBLICATIONS, KAGLO, HAMTRONICS,
PROWRITER, ELEPHANT DISKS, DEBCO, TRIONYX

MOSFET technology in American made mobile power amplifiers. Built for those who demand quality.



✓ 138

915 North Main Street
Jamestown, New York 14701

Southern Tier's finest amateur radio dealer!
PH. (716) 664-6345

CADDELL COIL CORP.

35 Main Street
Poultney, VT 05764
802-287-4055

BALUNS

Get POWER to your antenna! Our Baluns are already wound and ready for installation in your transmatch or you may enclose them in a weatherproof box and connect them directly at the antenna. They are designed for 3-30 MHz operation. (See ARRL Handbook pages 19-9 or 6-20 for construction details.)

| | |
|--|---------|
| 100 Watt (4:1, 6:1, 9:1, or 1:1 Impedance - select one) | \$ 8.50 |
| Universal Transmatch 1 KW (4:1 Impedance) | 12.50 |
| Universal Transmatch 2 KW (4:1 Impedance) | 15.00 |
| Universal Transmatch 1 KW (6:1, 9:1 or 1:1 - select one) | 14.00 |
| Universal Transmatch 2 KW (6:1, 9:1 or 1:1 - select one) | 16.50 |

designing Yagis with the Commodore 64

See how gain and F/B
can remain high
across the entire band

In 1980, *ham radio* published a series of articles by W2PV on Yagi design.¹ As an avid DXer and a member of Potomac Valley Radio Club, I'd crossed paths with W2PV under contest conditions many times. He always had a fantastic signal, and after reading his series I realized why. W2PV was using superior antennas, all positioned at the correct height above ground.

Through computer research, W2PV showed that merely stating the mechanical length of an element of a Yagi beam does not actually reflect its true resonant frequency, especially when tapered elements are involved. He has also showed that tuning the reflector 5 percent below and the director 5 percent above the band center makes a poor beam. Commercial antenna specifications usually indicate maximum gain, maximum front-to-back ratio, and an SWR curve. But what they don't tell you is that the maximum gain and maximum front-to-back ratio do not occur at the same frequency, nor do they occur in the band center. They also don't tell you that as you tune away from these frequencies, the gain and maximum front-to-back ratio can fall off rapidly, indicating that although you may have 8 dB of gain at some frequency, you may only have 3 dB of gain near the band edges, depending on the tuning of the parasitic elements.

W2PV demonstrated that gain is primarily dependent on boom length and not on the number of elements on the boom, especially in the 1/4 to 3/4 boom length range. In addition, a naturally high front-to-back

ratio occurs on a 1/4 wavelength boom and odd multiples thereof. He carefully designed his Yagis so that they would maintain a high gain and high front-to-back ratio over a 4 percent bandwidth, which will cover all of 15 and 20, most of 40, and a good portion of 10 meters. In order to do this the parasitic elements must be tuned closer to the driven element reducing the SWR bandwidth. This is a small price to pay for maintaining almost maximum gain over the whole band. For example, the reflector of his three-element monobander is tuned 1.7 percent below the central design frequency and the director is tuned 4.2 percent above. He also proved that the resonant frequency of a tapered element could be very accurately determined.

About a year ago I wrote a program in BASIC using the formulas and data in the W2PV articles. With it you can turn your commercial antennas or scrap aluminum tubing into W2PV super beams. The program (fig. 1) is in simple BASIC with no peek or poke statements, and runs on the Commodore 64 computer.

program description

Lines 100-450 are a brief history of the program and instructions to the user. The type of beam you are designing is entered in lines 460-500. The actual lengths and diameters of each element are entered on lines 550-620, while the subroutine lines 5000-5040 prints the inputs to the screen. Lines 2000-2040 place data into the *A* array and if the average diameter calculated on line 670 is 0.875 the data in *A* array is dumped into *R* array. If the average diameter is not 0.875, then new data is calculated in lines 2100-2200 and placed into *B* array. Then *B* array is dumped into *R* array via lines 2210-2220. The element half-length that you are trying for per the central design frequency you entered earlier

By Alan Hoffmaster, WA3EKL, 929 Andrews Road, Glen Burnie, Maryland 21061

WE HAVE QUALITY PARTS, DISCOUNT PRICES AND FAST SHIPPING!

TRANSFORMERS



120 volt primaries

| | |
|--------------------|--------|
| 5.6 VOLTS @ 750 MA | \$3.00 |
| 6 VOLTS @ 150 MA | \$1.25 |
| 12 VCT @ 200 MA | \$2.00 |
| 18 V. @ 650 MA | \$3.50 |
| 18 VOLTS @ 1 AMP | \$4.50 |
| 24 VOLTS @ 250 MA | \$2.50 |
| 24 VCT @ 1 AMP | \$4.50 |

LINE CORDS



TWO WIRE
6' 18ga TWO WIRE
3 FOR \$1.00

THREE WIRE
8 FOOT 18ga THREE WIRE
\$2.00 EACH

MIKE CONNECTOR




5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT JACK TWIST LOCK STYLE. SAME AS SWITCHCRAFT 12CLSM.
\$2.50 PER SET

7 CONDUCTOR RIBBON CABLE



SPECTRA-STRIP RED MARKER STRIP. 28 GA STRANDED WIRE.
\$5.00 PER ROLL (100 FT.)

REVERBERATION UNIT

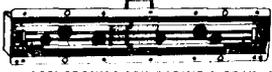

ACCUTRONICS COIL SPRING TYPE UNITS. USED IN ELECTRONIC ORGANS TO PROVIDE ACOUSTIC DELAY SOUND EFFECTS. INPUT IMPEDANCE 8 OHMS, OUTPUT IMPEDANCE 2250 OHMS. 4 1/2" x 16 1/2" x 1 1/2".
\$7.50 EACH


WALL TRANSFORMER



ALL ARE 115 VAC PLUG IN


| | |
|-------------------|--------|
| 4 VDC @ 70 MA | \$2.00 |
| 6 VAC @ 500 MA | \$3.50 |
| 6 VDC @ 750 MA | \$8.50 |
| 9 VDC @ 500 MA | \$5.00 |
| 9 VAC @ 1 AMP | \$3.00 |
| 12.5 VAC @ 265 MA | \$2.50 |
| 17 VAC @ 500 MA | \$4.00 |
| 24 VAC @ 250 MA | \$3.00 |

MULTI-SWITCHES

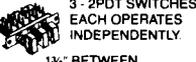

3 STATION NON-INTERLOCKING
3 - 2PDT SWITCHES. EACH OPERATES INDEPENDENTLY.
1 1/2" BETWEEN MOUNTING CENTERS.
\$1.75 EACH

METER

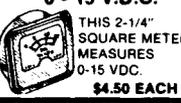

THIS 2-1/4" SQUARE METER MEASURES 0-15 V.D.C.
\$4.50 EACH

2K 10 TURN MULTI-TURN POT



SPECTROL #MOD 534-7161
\$5.00 EACH

SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER



T.I. # UM1381-1 DESIGNED FOR USE WITH T.I. COMPUTERS. CAN BE USED WITH VIDEO SOURCES. BUILT IN 2 SWITCH CHANNEL 3 OR 4 SELECTION SWITCH OPERATES ON 12 VDC. HOOK UP DIAGRAM INCLUDED.
\$10.00 EACH

SPRING LEVER TERMINALS



TWO COLOR CODED TERMINALS ON A STURDY 2 3/4" x 3 3/4" BAKELITE PLATE. GREAT FOR SPEAKER ENCLOSURES OR POWER SUPPLIES.
\$1.00 EACH 10 FOR \$9.00

5 STATION INTERLOCKING



MADE BY ALPS. 3 - 2PDT AND 2 - 6PDT SWITCHES ON FULLY INTERLOCKING ASSEMBLY. 3/4" BETWEEN MOUNTING CENTERS.
\$2.50 EACH

SUB-MINIATURE D TYPE CONNECTOR



SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.


| | |
|--------------|--------|
| DB-15 PLUG | \$2.75 |
| DB-15 SOCKET | \$4.00 |
| DB-15 HOOD | \$1.50 |
| DB-25 PLUG | \$2.75 |
| DB-25 SOCKET | \$3.50 |
| DB-25 HOOD | \$1.25 |

ROTARY SWITCH



1 POLE 6 POSITION
1 1/4" DIA x 1 1/2" HIGH
75° EACH
10 for \$6.00

48 KEY ASSEMBLY FOR T.I. COMPUTER

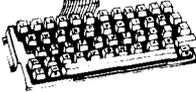


NEW TEXAS INSTRUMENTS KEYBOARD. UNENCODED 48 S.P.S.T. MECHANICAL SWITCHES. TERMINATES TO 15 PIN CONNECTOR. SOLID METAL FRAME 4" x 9".
\$6.50 EACH 2 FOR \$11.00

PUSHBUTTON POWER SWITCH



DOUBLE POLE POWER SWITCH PUSH-ON, PUSH-OFF.
\$1.00 EACH

EDGE CONNECTORS

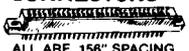

ALL ARE .156" SPACING


10 PIN EDGE CONNECTOR
TRW #50-10-A-20 \$2.00 EACH

120V INDICATOR



NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE. RED LENS.
75¢ EACH
10 FOR \$7.00
100 FOR \$65.00

TI SWITCHING POWER SUPPLY

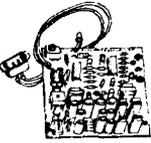

TI # 1053214-2
COMPACT, WELL-REGULATED SWITCHING POWER SUPPLY DESIGNED TO POWER TEXAS INSTRUMENTS COMPUTER EQUIPMENT.
INPUT: 14VAC-25 VAC AT 1A
OUTPUT: +12VDC AT 350MA
+ 5VDC AT 1.2A
+ 5VDC AT 200MA
SIZE: 4 1/4" x 4 1/4" x 1 1/4" \$5.00 EACH

"PARALLEL" PRINTER CONNECTOR



SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES.
\$5.50 EACH

SWITCHES MINI-PUSH BUTTON



S.P.S.T. MOMENTARY NORMALLY OPEN 1/4" BUSHING

| |
|-----------------|
| 35¢ EACH |
| 10 FOR \$3.25 |
| 100 FOR \$30.00 |


SPECIFY COLOR: RED, BLACK, WHITE, YELLOW.

22/44 TIN
P.C. STYLE. NO MOUNTING EARS
\$1.50 EACH 10 FOR \$14.00

22/44 GOLD
P.C. STYLE \$2.00 EACH
10 FOR \$18.00

28/56 GOLD
28/56 GOLD PLATED CONTACTS 156 CONTACT SPACING
\$2.50 EACH 10 FOR \$22.00


GEL CELL BATTERY

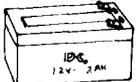

12 VDC @ 2.6 AMP HOUR
5 3/8" x 2 1/4" x 3 3/4"
\$25.00 EACH

FREE! → SEND FOR NEW 1985 48 PAGE CATALOG ← FREE!

13.8 VOLT REGULATED POWER SUPPLY

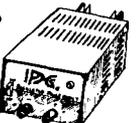

THESE ARE SOLID STATE FULLY REGULATED 13.8 VDC POWER SUPPLIES. ALL FEATURE 100% SOLID STATE CONSTRUCTION. FUSE PROTECTION. L.E.D. POWER INDICATOR.
2 AMP CONSTANT, 4 AMP SURGE.
UL LISTED \$18.00 EACH

RELAYS SOLID STATE RELAY



HEINEMANN ELECTRIC #101-5A-140-5 AMP CONTROL: 3-32VDC LOAD: 140VAC 5 AMPS SIZE: 2" x 1" x 1/4" HIGH
\$5.00 EACH 10 FOR \$45.00

COMPUTER GRADE CAPACITORS



2,000 mfd. 200 VDC 1 3/4" DIA. - 5" HIGH \$2.00

3,600 mfd. 40 VDC 1 3/8" DIA. - 3 3/4" HIGH \$1.00

6,400 mfd. 60 VDC 1 3/8" DIA. - 4 1/4" HIGH \$2.50

31,000 mfd. 15 VDC 1 3/4" DIA. - 4" HIGH \$2.50

72,000 mfd. 15 VDC 2" DIA. - 4 3/8" HIGH \$3.50

185,000 mfd. 6 VDC 2 1/2" DIA. - 4 1/2" HIGH \$1.50

CLAMPS TO FIT CAPACITORS 50¢ ea.

SLIDE POTS



100K linear tape
2" LONG
1 5/8" TRAVEL 75¢ EACH

500K linear taper
2 7/8" LONG
1 3/4" TRAVEL 75¢ EACH

DUAL 100K audio taper
3 1/2" LONG
2 1/2" TRAVEL. \$1.50 EACH

CRYSTALS
CASE STYLE HC33/U
2 MHZ COLORBURST 3579-545 KC
\$3.50 EACH \$1.00 EACH

METAL OXIDE VARISTOR
POPULAR GE # 130LA10A VARISTOR. 5/8" DIAMETER. \$1.25 EACH

L.E.D.'S STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50
GREEN 10 FOR \$2.00
YELLOW 10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH

BI POLAR LED 2 FOR \$1.70

LED HOLDERS
TWO PIECE HOLDER FOR JUMBO LED 10 FOR 65¢ 200 FOR \$10.00

CLEAR CLIPLITE HOLDER
MAKE LED A FANCY INDICATOR CLEAR. 4 FOR \$1.00

DC CONVERTER



DESIGNED TO PROVIDE A STEADY +5 VDC @ 240 MA FROM A BATTERY SUPPLY OF 3.5 TO 6.25 V.
2 1/16" x 1 1/16" x 1 1/16" HIGH. \$1.50 EACH

1N4148 SPECIAL



45" SPACING P.C. LEADS
1000 FOR \$10.00
10,000 FOR \$585.00

MINIATURE 6 VDC RELAY



SUPER SMALL SPDT RELAY. GOLD COBALT CONTACTS
RATED 1 AMP AT 30 VDC. HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 4.3 TO 6 V. COIL RES. 220 OHM.
1 3/16" x 1 3/32" x 7/16" AROMAT # RSD-6V
\$1.50 EACH 10 FOR \$13.50

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on)
P.C. STYLE. NON-THREADED BUSHING 75¢ EACH
10 FOR \$7.00

S.P.D.T. (on-on)
SOLDER LUG TERMINALS. \$1.00 EACH
10 FOR \$9.00
100 FOR \$80.00

S.P.D.T. (on-off-on)
NON-THREADED BUSHING. P.C. STYLE 75¢ EACH
10 FOR \$7.00

S.P.D.T. (on-on)
NON-THREADED BUSHING. \$1.00 EACH
10 FOR \$9.00
100 FOR \$80.00

D.P.D.T. (on-on)
SOLDER LUG TERMINALS. \$2.00 EACH
10 FOR \$19.00
100 FOR \$180.00

3 1/2" SPEAKER



8 OHM IMPEDANCE. FULL RANGE SPEAKER. 8 OZ MAGNET. 4" DIAGONAL. MOUNTING CENTERS.
\$2.50 EACH
10 FOR \$20.00

TRANSISTORS

| | |
|---------|--------------|
| 2N706 | 4 FOR \$1.00 |
| 2N2222A | 3 FOR \$1.00 |
| PN2222 | 4 FOR \$1.00 |
| 2N2904 | 3 FOR \$1.00 |
| 2N2905 | 3 FOR \$1.00 |
| 2N2907 | 3 FOR \$1.00 |

KEY ASSEMBLY 5 KEY



CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES MEASURES 3 3/4" LONG
\$1.00 EACH

6 KEY
CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.
\$1.25 EACH


13 VDC RELAY



CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT...
COIL: 13 VDC 650 OHMS
SPECIAL PRICE \$1.00 EACH

4 PDT RELAY
• 14 pin style
• 3 amp contacts
• 24 volt d.c. or 120 volt a.c. coil
• Used but fully tested
\$1.70 EACH
specify coil voltage
LARGE QUANTITIES AVAILABLE
SOCKETS FOR RELAY 50¢ each

8" P.A. SPEAKERS

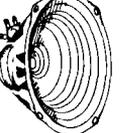

C.T.S. MODEL 8B3079 \$5.00 EACH
8 OHMS COIL CASE OF 8 SPEAKERS
3.0 OZ FERRITE MAGNET TYPICAL RESPONSE RANGE: 100 - 10,000 HZ. \$32.00
POWER RATING 15 WATTS MAX.
DRILLED TO MOUNT LINE MATCHING TRANSFORMERS.

SOLID STATE BUZZER



STAR #SMB-06L 6 VDC. TTL COMPATIBLE
\$1.00 EACH
10 FOR \$9.00

ALL ELECTRONICS CORP.

TOLL FREE ORDERS ONLY
1-800-875-5432 (ORDER ONLY)
(IN CALIFORNIA 1-800-258-6666)
ALASKA, HAWAII, OR INFORMATION
(213) 380-8000

905 S. VERMONT AVE. P.O. BOX 20406 LOS ANGELES, CA 90006

6228 SEPULVEDA BLVD. VAN NUYS, CA 91411

QUANTITIES LIMITED
MINIMUM ORDER \$10.00
USA \$3.00 SHIPPING
FOREIGN ORDERS:
INCLUDE SUFFICIENT SHIPPING
CALIF RES ADD 6.12%
NO COD

fig. 1. WA3EKL program for designing 10, 15, and 20-meter Yagis with the Commodore 64.

```

100 PRINT"MONO BAND ANTENNA DESIGN"
102 DIM#(3),B(4)
104 PRINT:PRINT"DO YOU WISH INSTRUCTIONS(Y/N)";:INPUT#3
106 IF#3="N"THEN#450
108 PRINT
110 PRINT"THIS PROGRAM WAS WRITTEN USING THE FORMULAS PUBLISHED IN 1980 HAM RADIO"
112 PRINT"MAGAZINE AND WRITTEN BY W2PV WHO PROVED MATHEMATICALLY AND EXPERIMENTAL"
114 PRINT"THAT ANTENNA ELEMENT RESONATE FREQUENCY LENGTH IS NOT A SIMPLE"
116 PRINT"CALCULATION ESPECIALLY WHEN TAPERED ELEMENTS ARE INVOLVED."
120 PRINT
130 PRINT"MECHANICAL RECOMMENDATIONS"
140 PRINT"20 METER BOOM SHOULD BE 3 OR 4 INCH DIAMETER ALUMINUM IRRIGATION"
150 PRINT"PIPE DEPENDING ON LENGTH."
160 PRINT"ELEMENTS SHOULD BE TAPERED SEGMENTS FROM 1/4 INCH TO 1/2 INCH"
165 PRINT"DIAMETERS OF 6061 T6 SEAMLESS TUBING OR EQUIVALENT."
182 DIM#(3)
185 PRINT:PRINT"TO CONTINUE INSTRUCTION PRESS RETURN";:INPUT#4
190 PRINT:PRINT"10-15 METER BOOMS SHOULD BE MADE OF 2 INCH ALUMINUM IRRIGATION PIPE."
200 PRINT"ELEMENTS SHOULD BE TAPERED FROM 7/8 INCHES TO 5/8 INCH DIAMETERS OF"
205 PRINT"6061 T6 SEAMLESS TUBING OR EQUIVALENT."
210 PRINT:PRINT"ELECTRICAL RECOMMENDATIONS."
215 PRINT"FOR MAXIMUM FRONT TO BACK RATIO USE A 1/4 WAVELENGTH BOOM ON A 3 ELEMENT"
220 PRINT"BEAM AND 3/4 WAVELENGTH BOOM ON A 4,5 OR 6 ELEMENT BEAM."
225 PRINT"EQUALLY SPACE ALL ELEMENTS ALONG THE BOOM REGARDLESS OF LENGTH."
230 PRINT"FOR A GOOD 2 ELEMENT BEAM USE A BOOM LENGTH OF .150 WAVELENGTH."
240 PRINT"FOR A GOOD 3 ELEMENT BEAM USE A BOOM LENGTH OF .300 WAVELENGTH."
245 PRINT:PRINT"TO CONTINUE INSTRUCTIONS PRESS RETURN";:INPUT#5
250 PRINT:PRINT"IMPORTANT ALL TOTAL LENGTH DIMENSIONS WILL BE ELEMENT HALF LENGTH"
255 PRINT"MEANING THE LENGTH OF THE ELEMENT MEASURED FROM THE BOOM OUT TO THE"
260 PRINT"TOP OF THE ELEMENT. ENTER ELEMENT SEGMENT LENGTHS AND DIAMETERS JUST"
265 PRINT"AS THEY WILL BE ASSEMBLED STARTING WITH THE LARGEST DIAMETER SEGMENTS"
270 PRINT"(WHICH CROSSES OVER THE BOOM) TO THE SMALLEST DIAMETER SEGMENT AT THE"
275 PRINT"ELEMENT TIP. THE OBJECT IS TO ADJUST THE ORIGINAL SEGMENT LENGTHS SO"
280 PRINT"THAT THE TOTAL EQUIVALENT LENGTH IS EQUAL TO OR VERY CLOSE TO THE"
285 PRINT"NORMALIZED LENGTH FOR THE PARTICULAR ELEMENT YOU'RE WORKING ON."
290 PRINT:PRINT"TO CONTINUE PRESS RETURN";:INPUT#6
295 PRINT"WHEN THE COMPUTER ASKS YOU FOR THE INFORMATION ENTER IN THE INFORMATION"
300 PRINT"THEN PRESS RETURN. NOTHING WILL HAPPEN UNTIL YOU PRESS RETURN. IF"
305 PRINT"NOTHING HAPPENS IMMEDIATELY, WAIT. THE COMPUTER MAY BE THINKING."
310 PRINT:PRINT"TO CONTINUE PRESS RETURN";:INPUT#7
450 PRINT:PRINT"ENTER CENTRAL DESIGN FREQUENCY IN MHZ";:INPUTCDF
460 RL=1/(1+1.024*(CDF/REM RESONATE LENGTH IN INCHES
470 PRINT"ENTER NUMBER OF ANTENNA ELEMENTS 2,3,4,5 OR 6";:INPUTP
480 IF P<2OR P>6THEN#470
490 PRINT"ENTER BOOM DIAMETER";:INPUTBD
496 BC=(BD/2)*.0625;REM BOOM CORRECTION
500 PRINT"ENTER NUMBER OF ANTENNA SEGMENTS";:INPUTN
505 X=0
510 DIM#L(N-1),D(N-1),F(N-1)
520 FOR#=0TO(N-1)
530 L(#)=0;D(#)=0;F(#)=0
540 NEXT#;REM CLEAR ARRAYS
550 PRINT:PRINT"ENTER (IN INCHES) LENGTH OF SEGMENT";:INPUTA
560 L(X)=A
570 PRINT"ENTER (IN INCHES) DIAMETER OF SEGMENT";:INPUTB
580 D(X)=B
590 GOSUB#900
600 X=X+1;REM STEPPING DATA INTO L ARRAY
610 IF X=THEN#630
620 GOTO#550;REM ENTERING IN SUCCESSIVE LENGTHS AND DIAMETERS
630 GOSUB#900
640 FOR#=#0TO(N-1)
650 TD=TD+(EE)
660 NEXT#
670 AD=TD/N
680 GOSUB#2000
690 GOSUB#3000
700 T=#0;REM CLEAR TOTAL
710 FOR#=#0TO(N-1)
720 T=T+L(Y);REM ADD SEGMENT LENGTHS
730 PRINT#1,Y;"INCHES LONG";D(Y);"INCHES DIA."
740 NEXTY
750 PRINT:PRINT"INCHES=TOTAL ORIGINAL LENGTH"
770 D1=#0;D2=#0;W=#0
780 R1=AD/(2#RL);REM = RADIUS OF CENTER SEGMENT
790 D1=D1G
800 R2=D1/(2#RL);REM = RADIUS OF SUCCESSIVE ELEMENTS
810 S=#G+1;REM STEPPING THRU SEG. DIAMETERS.
820 K1=1/R1
830 K2=1/R2
840 M=(.43+.03#(LOG(K2)/LOG(10))-.32)/(.43+.03#(LOG(K1)/LOG(10))-.32)
850 Q2=(L(W)*1.57079632)/#7+D1;REM Q2 IN RADIANS
860 FD=(SIN(2#Q2)-SIN(2#Q1))/(2#Q2-(2#Q1))
870 Q1=#Q2
880 S#=(#+1/#)/2+(#-1/#)#FQ2/2#L(W)
890 F(W)=S#;REM PLACE EQUIVALENT LENGTHS INTO F ARRAY
900 W=W+1;REM STEPPING THRU F ARRAY
910 IF W=THEN#930
920 GOTO#780;REM LOOP TO CALCULATE EACH SEGMENT LENGTH
930 S=#;REM CLEAR EQUIVALENT LENGTH TOTAL
940 FOR#=#0TO(N-1)
950 S=S+F(Z);REM ADD EQUIVALENT LENGTHS IN F ARRAY
960 NEXTZ
970 PRINT#1,PRINTS;"INCHES=TOTAL EQUIVALENT LENGTH"
972 PRINT#1,PRINT"HARD COPY(Y/N)";:INPUT#8
973 GET#1;IF#8="Y"THEN#973
974 IF#8="Y"THEN#900
980 PRINT"DO YOU WISH TO CHANGE A SEGMENT LENGTH(Y/N)";:INPUT#9
990 IF#9="N"THEN#1170
1000 PRINT"ENTER NUMBER OF SEGMENTS YOU WISH TO CHANGE COUNTING FROM THE BOOM OUT"
1010 INPUTV
1100 IF V<0OR V>THEN#1000
1150 PRINT"ENTER NEW SEGMENT LENGTH (IN INCHES)";:INPUTU
1140 L(V-1)=U
1150 GOSUB#3000
1160 GOTO#700
1170 PRINT"(CLR)";REM CLEAR SCREEN
1180 PRINT#1;"ELEMENT BEAM AT ";CDF;"MHZ"
1190 PRINT
1200 FOR#=#0TO(N-1)
1210 PRINT#1,TT;"INCHES LONG";D(TT);"INCHES DIA."
1212 GOSUB#900
1230 PRINT:PRINT"WRITE DOWN ELEMENT LENGTHS APPEARING ON THE SCREEN AND ADD THE"
1235 PRINT"FOLOWING CORRECTIONS TO THE OUTER MOST ELEMENT, FOR FINAL LENGTH."
1250 PRINT
1260 PRINT"ON 20 METERS ADD ";BC+0.44;"INCHES"
1270 PRINT"ON 15 METERS ADD ";BC+0.44;"INCHES"
1280 PRINT"ON 10 METERS ADD ";BC+0.24;"INCHES"
1285 GOSUB#10000
1296 END
2000 DIM#A(13),B(13)
2005 FOR#=#0TO13
2010 A(#)=0;B(#)=0
2020 NEXT#;REM CLEAR A AND B ARRAYS
2030 A(0)=0.49366+A(1)=0.49801+A(2)=0.49693+A(3)=0.49994
2035 A(4)=0.49528+A(5)=0.47051+A(6)=0.48963+A(7)=0.48266+A(8)=0.4804
2040 A(9)=0.48028+A(10)=0.46591+A(11)=0.46798+A(12)=0.45232+A(13)=0.44811
2050 D1R(6),DE(6),DR(6)
2060 FDRQ=0T06
2070 R(0)=0;DE(0)=0;DR(0)=0
2080 NEXT#;REM CLEAR R, DE, DR
2090 IFAD=#.87;THEN#2240
2100 RA=#.875/(2#RL)
2110 RB=AD/(2#RL)
2120 KB=1/RB
2130 KB=1/RB
2140 FORJ=#0TO13
2150 F1=1-(1-(10.7575#(LOG(KA)/LOG(10)))-B(1)-1)/(2#A(J))
2160 XX=(1215.15#(LOG(KA)/LOG(10)))-1601#(1/F1)-F1
2170 RA=X/(1215.15#(LOG(KB)/LOG(10)))-1601
2180 F2=(1-AA+(1AA(1+2)+4)10.5)/2
2190 B(J)=1-(1-(10.7575#(LOG(KB)/LOG(10)))-B(1)-1)/(2#F2)
2200 NEXTJ
2210 R(2)=B(0);R(3)=B(1);R(4)=B(2);R(5)=B(3);R(6)=B(4);DE(2)=B(5);DE(3)=B(6)
2215 DE(4)=B(7);DE(5)=B(8);DE(6)=B(9)
2220 DR(3)=B(10);DR(4)=B(11);DR(5)=B(12);DR(6)=B(13)
2230 GOTO 2260
2240 R(2)=A(0);R(3)=A(1);R(4)=A(2);R(5)=A(3);R(6)=A(4);DE(2)=A(5);DE(3)=A(6)
2245 DE(4)=A(7);DE(5)=A(8);DE(6)=A(9)
2250 DR(3)=A(10);DR(4)=A(11);DR(5)=A(12);DR(6)=A(13)
2260 RS=(RL/R(P))/2;REM REFLECTOR NORMALIZED 1/2 LENGTH
2270 DE=(RL/DE(P))/2;REM DRIVEN ELEMENT NORMALIZED 1/2 LENGTH
2280 DR=(RL/DR(P))/2;REM DIRECTORS NORMALIZED 1/2 LENGTH
2290 RETURN
3000 PRINT"(CLR)"
3010 PRINT#1;"ELEMENT BEAM AT ";CDF;"MHZ"
3020 PRINT
3030 PRINT#1;"INCHES=NORMALIZED REFLECTOR 1/2 LENGTH"
3040 PRINT#1;"INCHES=NORMALIZED DRIVEN ELEMENT 1/2 LENGTH"
3050 PRINT#1;"INCHES=NORMALIZED DIRECTORS 1/2 LENGTH"
3060 RETURN
4000 PRINT:PRINT"PLEASE WAIT I'M THINKING"
4010 RETURN
5000 PRINT"(CLR)";REM CLEAR SCREEN
5010 PRINT#1;"ELEMENT BEAM AT ";CDF;"MHZ"
5020 FOR#=#0TO(N-1)
5030 PRINT#1,L(TT);"INCHES LONG";D(TT);"INCHES DIA."
5040 NEXT#
5050 RETURN
5090 IF#8="N"THEN#6090
6000 OPEN#1,4,0
6005 PRINT#1,PRINT#1,PRINT#1,PRINT#1,PRINT#1,PRINT#1
6010 PRINT#1,"MONO BAND ANTENNA DESIGN";:PRINT#1
6020 PRINT#1,"CENTRAL DESIGN FREQUENCY";CDF;"MHZ";:PRINT#1
6030 PRINT#1,P;"ANTENNA ELEMENTS";:PRINT#1
6040 PRINT#1,BD;"INCHES BOOM DIAMETER";:PRINT#1
6050 PRINT#1,N;"ANTENNA SEGMENTS";:PRINT#1
6060 PRINT#1,T;"INCHES TOTAL ORIGINAL LENGTH";:PRINT#1
6070 PRINT#1,S;"INCHES TOTAL EQUIVALENT LENGTH";:PRINT#1
6080 CLOSE#1
6085 GOSUB#9000
6090 RETURN
7040 RETURN
8000 IF#8="N"THEN#8060
8010 OPEN#1,4,0
8020 PRINT#1,RS;"INCHES=NORMALIZED REFLECTOR 1/2 LENGTH"
8030 PRINT#1,DE;"INCHES=NORMALIZED DRIVEN ELEMENT 1/2 LENGTH"
8040 PRINT#1,DR;"INCHES=NORMALIZED DIRECTORS 1/2 LENGTH";:PRINT#1
8050 CLOSE#1
8060 RETURN
9000 IF#8="N"THEN#9040
9010 OPEN#1,4,0
9020 PRINT#1,L(TT);"INCHES LONG";D(TT);"INCHES DIA."
9030 CLOSE#1
9040 RETURN
10000 IF#8="N"THEN#10070
10010 OPEN#1,4,0
10015 PRINT#1
10020 PRINT#1,"ADD CORRECTIONS TO OUTER MOST ELEMENTS, FOR FINAL LENGTH"
10030 PRINT#1,BC+0.44;"INCHES"
10040 PRINT#1,"ON 15 METERS ADD";BC+0.44;"INCHES"
10050 PRINT#1,"ON 10 METERS ADD";BC+0.24;"INCHES"
10055 PRINT#1,PRINT#1,PRINT#1,PRINT#1,PRINT#1,PRINT#1
10060 CLOSE#1
10070 RETURN

```

is calculated in lines 2260-2280. Lines 770-970 calculate the resonant half-length of the element you have created by the lengths and diameters you entered earlier. Lines 972-974 and 5090-10070 print a hard copy if you answer "Y" to the hard copy prompt.

You'll see printed on the screen the type of Yagi you have selected, the resonant half length each element should be (the "normalized" length) the mechanical length/diameter of each segment, and the actual electrical half-length of the element you've created. The program will now allow you to change individual seg-

ment lengths until your element's electrical half length equals the normalized half-length. You then add a small correction to the outermost segment (due to boom diameter and boom to element clamping system) to get the final element half-length.

W2PV broke the center of the driven element and used a balanced feed. I have used the gamma match successfully.

results

Three monoband Yagis have been constructed

design example 1: 3-element Yagi
 f_o : 14.175 MHz
 boom: 2 inches

| element | length (inches) |
|----------------------|-----------------|
| normalized reflector | 207.495860 |
| normalized driven | 204.066957 |
| normalized director | 195.621141 |

segment specifications

| diameter (inches) | length (inches) |
|-------------------|-----------------|
| 1.25 | 36 |
| 1.125 | 50 |
| 0.875 | 37 |
| 0.75 | 20 |
| 0.625 | 44 |
| 0.5 | 16 |
| 0.375 | 12.75 |

total original length
 = 215.75 inches
 total equivalent length
 = 207.51345 inches

design example 2: 6-element Yagi
 f_o : 14.175 MHz
 boom: 2 inches

| element | length (inches) |
|----------------------|-----------------|
| normalized reflector | 206.378917 |
| normalized driven | 200.239937 |
| normalized director | 187.061662 |

segment specifications

| diameter (inches) | length (inches) |
|-------------------|-----------------|
| 1.25 | 36 |
| 1.125 | 50 |
| 0.875 | 37 |
| 0.75 | 20 |
| 0.625 | 44 |
| 0.5 | 16 |
| 0.375 | 11.5 |

total original length
 = 214.5 inches
 total equivalent length
 = 206.397459 inches

Note 1: In each example, element has seven segments and last dimension is length before final correction due to boom clamping.

Note 2: If you cannot achieve the above numbers out to at least five places to the right of the decimal point, especially the normalized length and the total equivalent length, go back and check your program. Close is not good enough. Small inaccuracies are multiplied many times as segment lengths change.

using the program. When mounted on towers, not one resonated more than 4 kHz from the central design frequency. But the only way to really test an antenna is in actual combat — i.e., under contest conditions: the CQWW phone contest yielded 1.68 million points in 1983 and 2.43 million points in 1984. From 1983 to 1984, nothing changed except the antennas; all primary Yagis were homebrewed, using this program, and the secondary antennas were commercial beams redimensioned from the program.

W2PV hoped that others would build his superior beams and report the results. I've built them and am pleased to report that their performance is far better than any commercial antenna I've ever used from my QTH.

acknowledgement

Because this was my first attempt at programming, my sincere thanks are due to my XYL, N3DPB, who gave a few pointers on programming, and to WA3HQX, who converted my original program to the Commodore format. The program has been converted into Apple, Atari, IBM PC, and Radio Shack Color formats. Copies of these listings are available from me for one dollar (copying cost) plus a business-size SASE with 39 cents postage.


reference

1. James J. Lawson, W2PV, "Yagi Antenna Design," *ham radio*, January, February, May, June, July, September, October, November, December, 1980. (Back issues are available from *ham radio* at \$3 each. Contact Ham Radio's Bookstore, Greenville, New Hampshire 03048.)

ham radio

Propagation by Mufplot

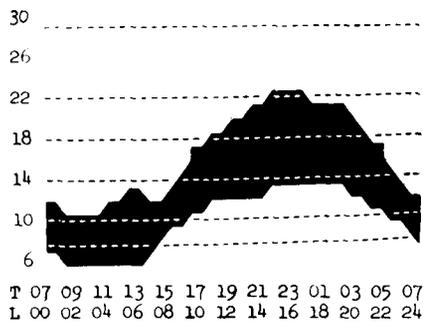TO: OH - FINLAND-ROVANIEMI DXCC
 BEARING: 26 DATE: 6-20 TIME: EST
 RANGE: 4005 FLUX: 120 PLOT: MUF



MUF PLOT is being used by amateurs from HONG KONG to BAGHDAD, SOUTH AFRICA to ALASKA, by sailors, commercial companies and people who know the need of propagation forecasting at its best. MUF PLOT will give you HPF, MUF, FOT with LUF plus distance and bearing (and time) to any target. You can select over 400 listed targets by DX or ARRL prefix, lat/long, or state. The database will let you enter target data by what ever you want to call it and you can change it anytime. MUF PLOT will keep track of the stations you have worked for WAS, DXCC or for any other award. MUF PLOT gives you a video graph (and/or table) and printer display of band conditions. (A special DX function lets you see world conditions. You select the number of and locations you want). Band coverage for the C-64 is 6 to 30MHz video and less then 1 to more then 30MHz printer. The APPLE is 2 to 34MHz. You enter your QTH lat/long only once but you can change it anytime.

() denotes for the (C-64) only.
 C-64 MUF PLOT V2 disk only \$32.95
 APPLE MUF PLOT disk only \$37.95
 North American orders add \$2.00 for S/H all others \$5.00.
 VISA, M.C., personal checks accepted.
APPLE is the trade mark of APPLE Computer Co.
C-64 is a trade mark of Commodore Co.
MUF PLOT is a trade mark of BASE (2) SYSTEMS.

BASE (2) SYSTEMS
 2534 Nebraska St.
 Saginaw, MI 48601
 Tel. 517-777-5613

LUXOR

DISTRIBUTORS FOR SALES AND SERVICE

PACIFIC

DIGITAL SATELLITE CORP

Pasadena, CA (213) 681-6222

HOOSIER ELECTRONICS

Sacramento, CA (916) 372-4676

KITTELVISION

Santa Rosa, CA (707) 585-3214

NORTHWEST SATELLITE ANTENNA, INC

Spokane, WA (509) 534-6972

Kent, WA (206) 251-0585

Eugene, OR (503) 343-7334

RECREATIONAL SPORTS WEST

Merced, CA (209) 383-2700

MOUNTAIN

DH SATELLITE

Buckeye, AZ (602) 386-7131

KAULTRONICS INC

Boulder, CO (303) 530-3422

Las Vegas, NV (702) 362-5816

NORTHWEST SATELLITE ANTENNA, INC

Billings, MT (406) 248-4131

RECREATIONAL SPORTS

Idaho Falls, ID (208) 523-5721

WESTEK

Phoenix, AZ (602) 582-5955

CENTRAL

DH SATELLITE

Prairie Du Chien, WI (608) 326-8406

Waseca, MN (507) 835-4454

DIGITAL SATELLITE

Little Rock, AR (501) 565-8443

HOOSIER ELECTRONICS

Terre Haute, IN (812) 238-1456

KANSAS CITY SATELLITE

Kansas City, MO (816) 483-6605

KAULTRONICS INC

Richland Center, WI (608) 647-8902

STARCOM

Arlington, TX (817) 640-1121

Big Springs, TX (NAT) 800-351-1426

(TX) 800-592-1476/4745

Service (915) 263-1012

San Antonio, TX (512) 650-3291

Oklahoma City, OK (405) 672-9617

Jefferson City, MO (NAT) 800-421-7242

(MO) 800-892-6080

WARREN SUPPLY

Sioux Falls, SD 800-492-7736

SOUTH

DH SATELLITE

Tifton, GA (912) 382-3867

FIRST SATELLITE CORP.

Winter Park, FL (305) 647-5400

KAULTRONICS INC

Marietta, GA (404) 955-6682

NATIONAL MICRODYNAMICS

Chattanooga, TN (615) 892-3901

QUARLES ELECTRONICS

Greenwood, SC (NAT) 800-845-6952

(SC) 800-922-9704

Kingstree, SC (803) 382-9802

Ashland, KY 800-228-5761

Alma, GA (912) 632-8723

Charlotte, NC (704) 374-0153

SOUTHEAST SATELLITE DIST INC

St. Augustine, FL (904) 824-1915

(NAT) 800-824-3474

Pompano Beach, FL 800-548-3500

(NAT) 800-354-3474

Lakeland, FL 800-348-3500

ATLANTIC

DH SATELLITE

Mt. Pleasant, PA (412) 547-6160

SATELLITE SALES INC

Cleveland, OH 800-321-1245

(NAT) 800-321-1188

Columbus, OH 800-521-6136

(NAT) 800-345-5527

Coldwater, MI 800-647-1475

(NAT) 800-874-4835

SATELLITE VIDEO SERVICES

Catskill, NY (518) 678-9581

Raymond, NH (603) 895-3182

Altoona, PA (814) 942-5003

IMPORTER TO CANADA

EVOLUTION TECHNOLOGY INC

Burlington, Ontario, Canada

(416) 335-4422


IMPORTER TO MEXICO

KLAN S.A. (VIDEO SAT)

Monterrey, Mexico (83) 78 90 15 or

78 97 50

✓ 143

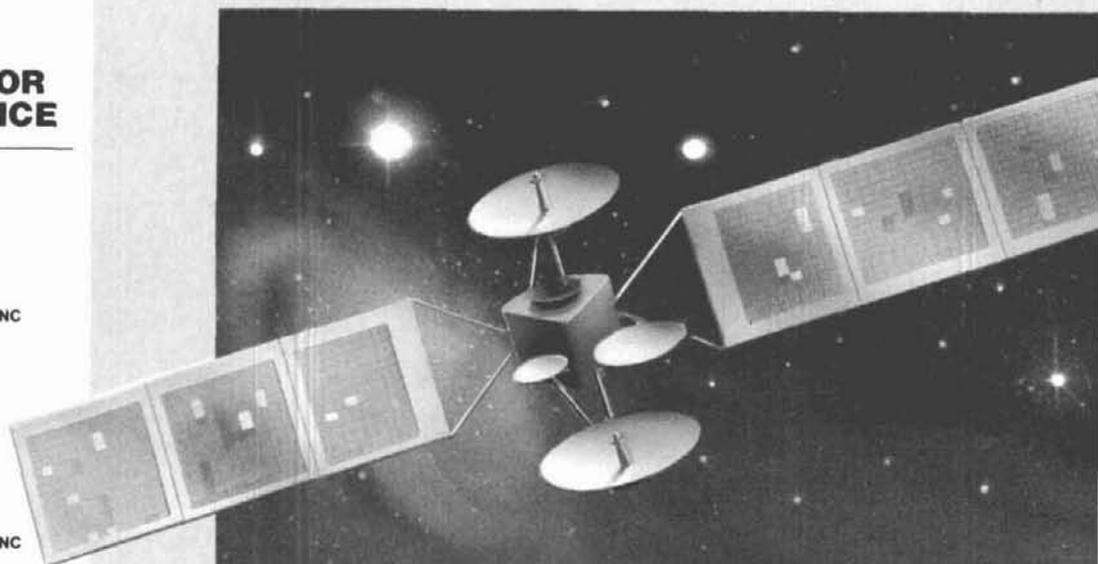

1 2 3 4 5

SIGNAL LEVEL

IR COMMAND RECEIVER

DOLBY SYSTEM

Mark 2

INTRODUCING A NEW GENERATION OF ELECTRONIC EXCELLENCE

Now several television sets throughout your home can have independent channel selection at the same time from a single antenna. Neighbors can share one antenna and enjoy the channel of their choice from a single satellite. Advanced block conversion and high performance technology bring you quality picture stability. Temperature-sensitive components are in the receiver, inside the house. A built-in stereo processor for both TV audio and stereo sound-only eliminates the necessity for an external add-on stereo processor. The entire system is easy to install. It's great! Simultaneous multi-channel TV viewing is here.

FCC Approved

LUXOR[®]

Mark 2[™]

BLOCK SATELLITE RECEIVER SYSTEM



REMOTE CONTROLLED
SATELLITE RECEIVER

LUXOR

LUXOR GIVES YOU MUCH MORE

The Luxor Mark 2 gives you more automatic features than systems costing much more! Individual remote control; Programmable memory; Four audio systems including stereo and Dolby noise reduction; Narrow/Wide band audio. A built-in modulator means easy connection to any TV set. See for yourself why Luxor is one of America's top selling brands. Luxor.



THE LUXOR 9534-2 ACTUATOR CONTROL

Add a Luxor Actuator Control Unit and the entire system, antenna and receiver, can be controlled with a hand-held IR Remote Commander.

LUXOR[®]

(North America) Corp
Bellevue, WA

**A leader in radio and television
technology since 1923.**



THE STANDARD OF EXCELLENCE

The world of CW, RTTY, and new DUAL AMTOR is as close as your fingertips with the new brilliantly innovative state-of-the-art microcomputer controlled EXL-5000E.*

Automatic Sender/Receiver: Due to the most up to date computer technology, just a console and keyboard can accomplish complete automatic send/receive of Morse Code (CW), Baudot Code (RTTY), ASCII Code (RTTY) and new ARQ/FEC (AMTOR).

Code: Morse (CW includes Kana), Baudot (RTTY), ASCII (RTTY), JIS (RTTY), ARQ/FEC (AMTOR).

Characters: Alphabet, Figures, Symbols, Special Characters, Kana.

Built-in-Monitor: 5" high resolution, delayed persistence green monitor — provides sharp clear image with no jiggle or jitter even under fluorescent lighting. Also has a provision for composite video signal output.

Time Clock: Displays Month, Date, Hour and Minute on the screen.

Time/Transmission/Receiving Feature: The built-in timer enables completely automatic TX/RX without operator's attendance.

Select (Selective Calling) System: With this feature, the unit only receives messages following a preset code. Built-in Demodulator for High Performance: Newly designed high speed RTTY demodulator has receiving capability of as fast as 300 Baud. Three-step shifts select either 170Hz, 425Hz or 850Hz shift with manual fine tune control of space channel for odd shifts. HIGH (Mark Frequency 2125Hz)/LOW (Mark Frequency 1275Hz) tone pair select. Mark only or Space only copy capability for selective fading. ARQ/FEC features incorporated.

Crystal Controlled AFSK Modulator: A transceiver without FSK function can transmit in RTTY mode by utilizing the high stability crystal-controlled modulator controlled by the computer.

Photocoupler CW, FSK Keyer built-in: Very high voltage, high current photocoupler keyer is provided for CW, FSK keying.

Convenient ASCII Key Arrangement: The keyboard layout is ASCII arrangement with function keys. Automatic insertion of LTR/FIG code makes operation a breeze.

Battery Back-up Memory: Data in the battery back-up memory, covering 72 characters x 7 channels and 24 characters x 8 channels, is retained even when the external power source is removed. Messages can be recalled from a keyboard instruction and some particular channels can be read out continuously. You can write messages into any channel while receiving.

Large Capacity Display Memory: Covers up to 1,280 characters. Screen Format contains 40 characters x 16 lines x 2 pages.

Screen Display Type-Ahead Buffer Memory: A 160-character buffer memory is displayed on the lower part of the screen. The characters move to the left erasing one by one as soon as they are transmitted. Messages can be written during the receiving state for transmission with battery back-up memory or SEND function.

Function Display System: Each function (mode, channel number, speed, etc.) is displayed on the screen.

Printer Interface: Centronics Para Compatible interface enables easy connection of a low-cost dot printer for hard copy.

Wide Range of Transmitting and Receiving: Morse Code transmitting speed can be set from the keyboard at any rate between 5-100 WPM (every word per minute). AUTOTRACK on receive. For communication in Baudot and ASCII Codes, rate is variable by a keyboard instruction between 12-300 Baud when using RTTY Modem and between 12-600 Baud when using TTL level. The variable speed feature makes the unit ideal for amateur, business and commercial use.

Pre-load Function: The buffer memory can store the messages written from the keyboard instead of sending them immediately. The stored messages can be sent with a keyboard command.

"RUB-OUT" Function: You can correct mistakes while writing messages in the buffer memory. Misspellings can also be erased while the information is still in the buffer memory.

Automatic CR/LF: While transmitting, CR/LF automatically sent every 64, 72 or 80 characters.

WORD MODE operation: Characters can be transmitted by word groupings, not every character, from the buffer memory with keyboard instruction.

LINE MODE operation: Characters can be transmitted by line groupings from the buffer memory.

WORD-WRAP-AROUND operation: In receive mode, WORD-WRAP-AROUND prevents the last word of the line from splitting in two and makes the screen easily read.

"ECHO" Function: With a keyboard instruction, received data can be read and sent out at the same time. This function enables a cassette tape recorder to be used as a back-up memory, and a system can be created just like telex which uses paper tape.

Cursor Control Function: Full cursor control (up/down, left/right) is available from the keyboard. Test Message Function: "RY" and "QBF" test messages can be repeated with this function.

MARK-AND-BREAK (SPACE-AND-BREAK) System: Either mark or space tone can be used to copy RTTY.

Variable CW weights: For CW transmission, weights (ratio of dot to dash) can be changed within the limits of 1:3-1:6.

Audio Monitor Circuit: A built-in audio monitor circuit with an automatic transmit/receive switch enables checking of the transmitting and receiving state. In receive mode, it is possible to check the output of the mark filter, the space filter and AGC amplifier prior to the filters.

CW Practice Function: The unit reads data from the hand key and displays the characters on the screen. CW keying output circuit works according to the key operation.

CW Random Generator: Output of CW random signal can be used as CW reading practice. **Bargraph LED Meter for Tuning:** Tuning of CW and RTTY is very easy with the bargraph LED meter. In addition, provision has been made for attachment of an oscilloscope to aid tuning.

Built-in AC/DC: Power supply is switchable as required; 100-120 VAC; 220-240 VAC/50/60Hz + 13.8VDC.

Color: Light grey with dark grey trim — matches most current transceivers.

Dimensions: 363(W) x 121(H) x 351(D) mm: Terminal Unit.

Warranty: One Year Limited

Specifications Subject to Change



Everything built in — nothing else to buy!

EXCLUSIVE DISTRIBUTOR: DEALER INQUIRIES INVITED
AMATEUR-WHOLESALE ELECTRONICS

8617 S.W. 129th Terrace, Miami, Florida 33176

FOR YOUR NEAREST DEALER OR TO ORDER:
TOLL FREE . . . 800-327-3102

Telephone (305) 233-3631

Telex: 80-3356



MANUFACTURER:


TONO CORPORATION

98 Motosoja Machi, Maebashi-Shi, 371, Japan


*Dual Amtor: Commercial quality, the EXL-5000E incorporates two completely separate modems to fully support the amateur Amtor codes and all of the CCIR recommendations 476-2 for commercial requirements.

the weekender

an inexpensive elevation indicator

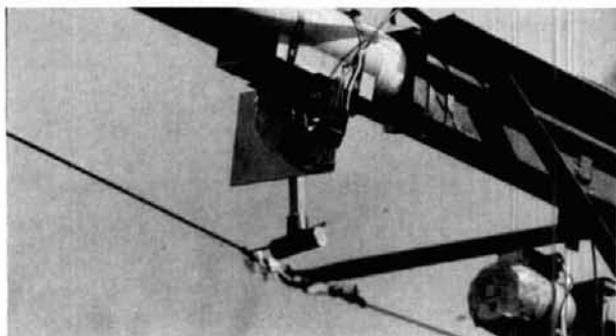

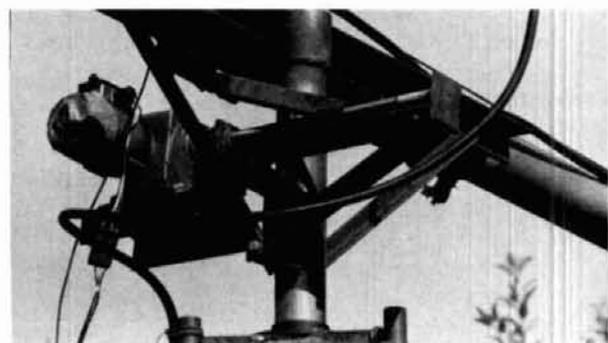Simple method of converting elevation angle to a voltage. Note weather-resistant housing.



Elevation drive: reversible gear motor turns lead screw of 3/4-inch all-thread.

If you have a high input impedance (≥ 1 Megohm) multimeter — preferably digital — and a single-turn, precision, linear taper potentiometer, then you have everything you need to make an inexpensive, accurate elevation indicator for OSCAR EME applications.

After discarding my store-bought elevation rotator in favor of a heavy-duty home-brew model, it became necessary to provide some means to determine where the antenna was pointing without having to "eye-ball" the moon and the antenna. This resulted in the con-

By George Chaney, W5JTL, 218 Katherine Drive, Vicksburg, Mississippi 39180

struction of the indicator shown in photos A and B.

The digital multimeter is used to read 0 to 0.9 volt, corresponding to 0 to 90 degrees in elevation. R2, a precision potentiometer, is used as a voltage divider, with the indicating voltage read off the moving arm of the potentiometer. It is mounted on a piece of heavy-duty circuit board, of any convenient size with three-wire cable, preferably shielded, running from the antenna to the indicating unit in the ham shack. A suitable bracket for mounting it to your antenna may be soldered to the PC board.

Assuming your potentiometer is in the 5 to 10 kilohm range, required current will be less than 1 mA. Ordinary zinc-carbon cells are quite satisfactory for this purpose; in fact, they will probably die of old age if switch S1 is used. Voltage regulation is not necessary. R1, used to drop the voltage to approximately 3.6 volts, is connected to terminal 3 of the precision potentiometer for calibration purposes as the batteries gradually discharge (see fig. 1).

construction

Because most precision potentiometers don't have threaded bushings around the shaft output, it will probably be necessary to use a good adhesive (Super-Glue,[®] contact cement or epoxy) or a clamp to mount the potentiometer to the PC board. A 6-inch (15 cm) length of 3/8-inch (0.95 cm) square key-stock is recommended for the pendulum shaft. A 1/4-inch (0.64 cm) hole (assuming the potentiometer shaft is 1/4 inch) is drilled through the key stock, about 1/2 inch (1.3 cm) from the top end. Immediately above this, and at a right angle to the 1/4-inch (0.64 cm) hole, drill a hole to accommodate a No. 8 machine screw. Then cut a hacksaw slit from the top end of the key-stock into the 1/4-inch (0.64 cm) hole so as to provide a clamp around the potentiometer shaft when the No. 8 machine screw is inserted and tightened with a nut.


The pendulum weight may be made of any convenient material that will provide sufficient weight without too much bulk. I used a 3/4-inch plumbing-type copper T-fitting filled with lead (see fig. 2). Its estimated weight is about 10 ounces (283 grams).

As shown in photo A the potentiometer is enclosed for weather protection. The enclosure is made of very thin (about 0.010 inch) (0.25 mm) double-sided PC board, soldered in place. The opening is so oriented that protection is provided when the antenna is elevated. Similar protection on the shaft-pendulum side of the PC board is advisable, although I chose not to take this step. I did put some silicone grease in this opening, however, and even after one year had no problems, despite the occurrence of a severe storm with baseball-size hail. An automotive trailer light con-


GLB PACKET RADIO CONTROLLER

Now you can get in on the fun in packet radio!

- Ready to operate - wired and tested - Low Cost!
- Operates with Voice Transceivers
- Easy to learn - easy to operate
- Built in Packet Modem and CW Identification
- Use with a computer, terminal or Teletype Machine
- Terminal Code is ASCII or BAUDOT
- Terminal Speeds from 45 to 9600 Baud
- Radio Link Speeds of 300, 600 or 1200 Baud
- Automatically selects AX.25 or VADC protocol
- Remote Command Lockout for repeater control
- Full & digipeater operation in AX.25
- Over 90 Commands
- Stores received messages for delayed reading
- Able to display other calls while connected
- "Block" and "Transparent" modes for data files
- Operates as an unattended digipeater
- "Beacon" mode
- Signals available for Teletype Motor Control
- Standard memory is 4K, expandable to 14K
- 56K RAM available on special order
- Can be customized for LAN's
- Squelch input for sharing of voice channels

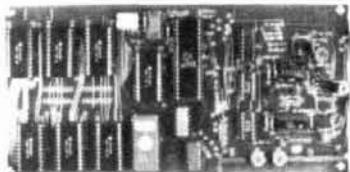

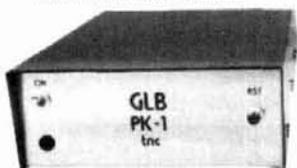MODEL PK1
(Shown with 14K RAM and 8K ROM)



Dimensions: 4.5 X 9.5 X 1.5 (inches)

Power Requirement: 12 volts DC at 200 ma.

| | | |
|-------|---|-------------|
| PK1 | Subassembly board (wired and tested, less case) | \$164.95 |
| M2K | 2K Additional memory, installed and tested | \$ 10.00/2k |
| PKDOC | Documentation only, refundable on first PK1 purchase | \$ 9.95 |
| PKCBL | Set of 4 ft cables (DB 25 to 10 pin, uncommitted to 10 pin) | \$ 19.95 |
| PKCNT | 10 pin edge connector only (2 required) | \$ 2.95 |
| PKPWR | Power supply (115V input) | \$ 9.95 |
| PKCAB | Cabinet kit | \$ 34.95 |
| PKTTY | Teletype adapter (teletype machine as terminal) | \$ 17.95 |
| PKWD1 | WATCHDOG assembly (for unattended repeater use) | \$ 17.95 |
| PKL1A | RS232 Level Converter (converts PK1 RS232 to -5 - Voltages) | \$ 21.95 |
| PKCPK | CPK Program (specify disc size, format, and computer) | \$ 34.95 |
| PKS24 | Each add'l. socket installed for memory expansion - 24 pin | \$ 2.00 |
| PKS28 | Each add'l. 28 pin socket | \$ 2.25 |

Please specify Call Sign, SSID Number, and Node Number when ordering.

Contact GLB for additional info and available options.

We offer a complete line of transmitters and receivers, strips, preselector preamps,


CWID's & synthesizers for amateur & commercial use.

Request our FREE catalog, MC & Visa welcome.

✓ 145


GLB ELECTRONICS, INC.

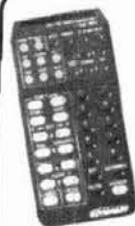Dept H, 151 Commerce Pkwy., Buffalo, NY 14224
716-675-6740 9 to 4



Use Your Wireless Control FROM ANY ROOM!!!

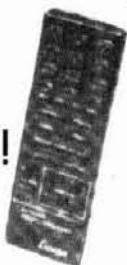Works with most infrared remote control receivers.



LIKE HAVING A SATELLITE RECEIVER, VCR, CABLE TV, AND VIDEO DISC IN EVERY ROOM!

- Remote control Satellite Receiver, VCR, Cable TV, and Video Disc can now be used long distance
- Install on any TV to access all your remote control video components.
- Makes non remote TVs remote controllable with remote control VCR, Cable Selector, or Satellite Receiver
- No fancy wiring needed - uses existing coaxial wiring between TVs
- No extra controls to buy! Uses the hand-held remote controllers you already have
- No tools required. Easily installed in minutes

XTRA-LINK™

MODEL 170

XL



\$79.95

Plus \$3.00 shipping & handling

608-493-2291

DEALER INQUIRIES WELCOME

MERRIMAC
SATELLITE

327 Palisade St Merrimac WI 53561

SPACE



✓ 146

Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

- A New Worldwide DX Ham Band open 10 hours a day.
- Rag Chew With Rare DX Stations in an uncrowded, gentlemanly fashion.
- Popular Modes In Use: SSB, CW, RTTY, SSTV, Packet
- Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

ORBIT Magazine Subscription:

Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

Satellite Tracking Software
Available for most popular PCs.



QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

AMSAT Membership is \$24 a year, \$26 outside North America. VISA and MC accepted.

AMSAT
P.O. Box 27
Washington, DC 20044
301 589-6062

✓ 147

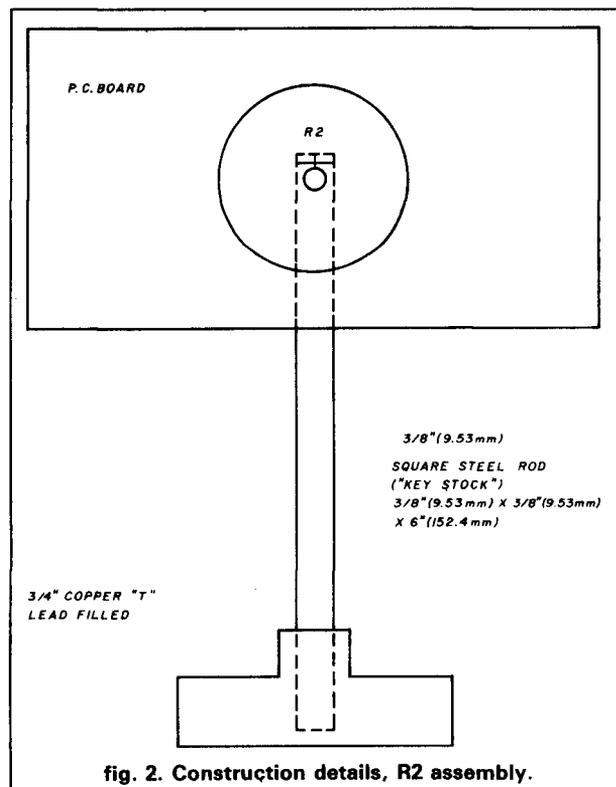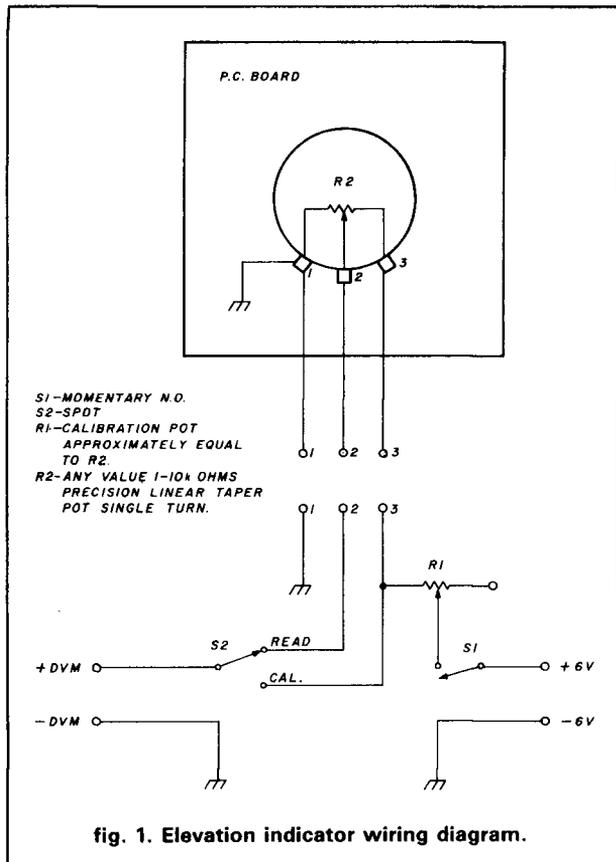

necter is used for the wiring (as a quick make/break interface).

The read-out portion, shown in the bottom part of **fig. 1** was built in a small box, fabricated from circuit board, large enough to hold the batteries, switches and resistor *R1*. Although I used four D cells, I think smaller batteries, such as size AA, should be satisfactory. Since it is only occasionally necessary to monitor elevation visually, I would suggest that *S1* be a normally open momentary pushbutton switch to be depressed only when readout is desired. *S2* is a single pole, double throw switch. It is normally left in the "Read" position and is connected to the lead going to the variable arm of *R2*. Suitable pin plugs are provided for the new leads at the + DVM and - DVM points.

calibration

All the precision potentiometers that I'm familiar with permit continuous rotation, do not have mechanical stops, and offer almost 360 degrees (of rotation) of usable variable resistance. The potentiometer should be oriented on the PC board (or the pendulum adjusted) so that the arm terminal of the potentiometer, reads "0" voltage when the bottom edge of the PC board is horizontal and increases progressively to a reading of 0.900 volt when the bottom edge is vertical. A carpenter's level, with the bubble carefully centered during adjustments, with the circuit board holding the potentiometer and the pendulum in a vice, or otherwise strongly secured, will provide sufficient accuracy.

The slightest upward movement of the antenna should result in a voltage indication of 0.001. After the zero point has been established, things can be permanently secured. Using the carpenter's level, move the assembly so that the bottom edge of the circuit board is vertical. With *S2* in the "Read" position, adjust *R1* to give a reading of 0.900 volt, which corresponds to an elevation of 90.0 degrees. The unit is now calibrated and will indicate changes of 0.1 degree, to an accuracy of 0.5 degree. When the potentiometer pendulum assembly is mounted on the antenna, it is necessary only to level the bottom edge in the zero position, with the antenna horizontal, in order to maintain calibration. After the 90.0-degree position has been established and initially calibrated, put *S2* in "Calibrate" position and note the indicated voltage. It is advisable to record this for later reference. You are now assured that you will be in calibration when *R1* is adjusted to give this reading, while in the "Calibrate" position. For maximum accuracy, the tower must be perfectly vertical, and the vertical rotational axis perfectly horizontal.



The monthly magazine with a natural blending of two popular hobbies — Ham Radio and Computers

- ★ Articles on Ham Radio & Most Personal Computers
- ★ Hardware & Software Reviews
- ★ Various Computer Languages
- ★ Construction Articles
- ★ Much Much More

"...received my moneys worth with just one issue..."

—J. Trenbick

"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."

—Fred Blechman, K6UGT

| | |
|-------------------------------------|------------------------------|
| U.S.A..... | \$15.00 for 1 year |
| Mexico, Canada | \$25.00 |
| Foreign | \$35.00(land) - \$55.00(air) |
| (U.S. funds only) | |
| Permanent (U.S. Subscription) | \$100.00 |
| Sample Copy | \$3.50 |



Circulation Manager
1704 Sam Drive
Birmingham, Alabama 35235
Phone 205/854-0271

Name _____

Call Sign _____

Address _____

City _____ State _____

Zip _____ Phone _____

Date _____

Signature _____

148

conclusion

The author makes no claim of originality in this type of elevation readout, although I have seen nothing as simple as this one. Most others use three-turn potentiometers with 10.8 volts, with readouts taken from some midrange, such as 1.000 to 1.900 volts, and some means of removing the first digit. The readout described here is simple, inexpensive, and accurate. Invariably, with my EME array adjusted according to a computer-predicted position, I can sight down the boom of one of the antennas and know its direction will be "rifle scope" accurate.

Caution: I assume, but do not know, that all DMMs have a high input resistance, so as not to unduly load the portion of R2 between the arm and ground. If your DVM does not have a high resistance input, do not use it.

ham radio

ORR BOOKS



BEAM ANTENNA HANDBOOK

by Bill Orr, W6SAI and Stu Cowan, W2LX

The Beam Antenna Handbook, first published in 1955, has been completely revised and updated with the latest information on Beam Antenna design. Computer designed Yagis give maximum gain in minimum space. New info on Yagi HF and VHF beams and dimensions on beams for 10, 18 and 24 MHz WARC bands. Everything you need to know about beam design, construction and operation. 204 illustrations. 268 pages. 1st edition. ©1985.

RP-BA **Softbound \$9.95**

SIMPLE LOW-COST WIRE ANTENNAS

by Bill Orr, W6SAI

Learn how to build simple, economical wire antennas. Apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. Well diagrammed. 192 pages. ©1972. 2nd edition.

RP-WA **Softbound \$7.95**

THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart Cowan, W2LX

Contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and new information on the popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. 190 pages. ©1978. 1st edition.

RP-AH **Softbound \$7.95**

ALL ABOUT CUBICAL QUAD ANTENNAS

by Bill Orr, W6SAI — New 3rd Edition

Includes NEW data for WARC bands

The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. You'll find quad designs for everything from the single element to the multi-element monster quad. There's a wealth of data on construction, feeding, tuning, and mounting quad antennas. 112 pages. ©1982. 3rd edition.

RP-CQ **Softbound \$6.95**

Please add \$1.50 for one book, \$2.50 for two or more books to cover shipping and handling.

Ham Radio's Bookstore Greenville, NH 03048

The Problem Solver...

The RF Wattmeter Model 81000-A from Coaxial Dynamics, Inc. does more than provide accurate rf measurements. Testing of transmission lines, antennas, connectors, filters and related components can reveal unknown problems and assure optimum equipment performance.

The 81000-AK Wattkit features this easy-to-read RF Wattmeter (pictured here), with its optional carrying case and an array of elements and accessories. Coaxial Dynamics elements can be purchased separately for use in other manufacturer's Wattmeters. For more information on the 81000-A Wattmeter or any of the complete line of Coaxial Dynamics RF products and OEM components please contact Coaxial Dynamics, Inc.



COAXIAL DYNAMICS, INC.

15210 Industrial Parkway, Cleveland, OH 44135 • (216) 267-2233
Outside Ohio, WATS: (800) Coaxial, Telex: 980-630


149

TOUCHTONE™ DECODER KIT



- MODEL TTK -
\$22.95

4 DIGIT SEQUENCE DECODER

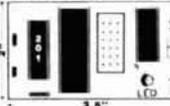

WIRED & TESTED
- MODEL TSD -
\$59.95


- SSI 201 DTMF Receiver
- Receive all 16 DTMF digits
- No additional filtering
- Output BCD or hex format
- Low power (29ma @ 12V)
- Kit includes 3.58Mhz crystal, 22 pin IC socket, resistor, capacitors, data sheet and schematics
- Completely wired & tested
- User programmable
- LED status indicator
- Open collector output
- Control relays, mute audio
- Control link on/off
- Custom IC insures high reliability & small size!
- Fits inside most rigs - runs on 12 VDC (35ma)
- Over 1500 different codes!

Makes excellent private call on busy repeaters!
Use it to turn on audio or sound an alarm
Momentary and latching outputs

MasterCard and Visa accepted, or send check/M.O. Cal address add 6%, price includes shipping USA. Send to
ENGINEERING CONSULTING
583 CANDLEWOOD ST., BREA, CA 92621
TEL: 714-671-2009

ENGINEERING CONSULTING INTRODUCES

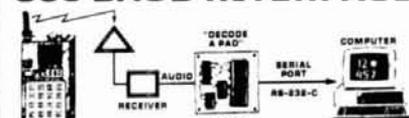TOUCHTONE™ DTMF to RS-232-C 300 BAUD INTERFACE



- Use your computer to decode DTMF touchtones.
- Receive all 16 digits as fast as they can be transmitted
- Easy program your computer in BASIC to decode multi-digit strings' display digits, sound alarms, observe secret codes, control relays, remote base
- Simple to use - just provide +12 VDC and audio; hook two wires to the RS-232-C serial input on your computer, enter a simple BASIC program and begin to decode
- Sample BASIC program and instructions included
- LED indicator

Model DAP-1 "Decode-A-Pad"
Wired and Tested **\$89.95**

Includes shipping USA. Cal addresses add 6%.
VISA and MasterCard accepted, or send check/M.O. to
ENGINEERING CONSULTING
583 CANDLEWOOD ST., BREA, CA 92621
714/671-2009

ENGINEERING CONSULTING INTRODUCES

'REMOTE A PAD'™ MODEL RAP-1

2 FOUR DIGIT DTMF DECODERS, PLUS 16 DIGIT KEYPAD CONTROL

TUNE THE WORLD FROM YOUR HANDHELD VHF/UHF RADIO

- Audio tones from any source are converted to solid state switches which control any 16 digit keypad of a radio or other device.
- Some examples you can control include the Pro-Search™ Hotstar (rotary beam remote), ICOM IC-701 or ICOM IC-251 when using the RM-2 controller, ICOM 7950 & 751, Azden PCS-4000, handhelds such as Yaesu FT-208, FT-70B, ICOM IC-02AT, and many more.
- Anything you can do manually with your 16 digit keypad the RAP-1 will do remotely using audio touch tones from any source.
- Two (four digit) programmable access codes are used to operate relays or other on/off functions.

Model RAP-1
\$149.95
'Remote A Pad'
Remote control interface board and DTMF decoder

LED decoder status indicators and momentary plus steady state decoder outputs are provided.
22 gold pin card edge connector, 16 pin dip socket and ribbon cable are supplied.
All CMOS, low power drain (30ma), SSI 201 Decoder.
Hook eight wires (4 rows and 4 columns) in parallel with the existing keypad of the radio you wish to control remotely. Connect audio from any source, 12 volts D.C. and you are in control.
The dual 8 digit decoders will turn your links on and off using your programmable access code.
Detailed interface diagrams and instructions included with purchase. Interface cable for Pro-Search™ \$9.95 (plugs in acc. socket).

ICOM IC-02AT USER'S "AUDIO BLASTER"™ MODULE

- Module installs inside the radio in 10 minutes
- Boosts audio to nearly 1 watt!
- Low power drain (4 ma stand by)
- Complete step by step instructions included
- Corrects the LOW audio problem
- Drive external speakers to full volume even against high low deviation!



Model AB-1 **\$19.95**
Price includes postage and handling, USA. CA res. add 6%.

Send check or money order to
ENGINEERING CONSULTING
583 CANDLEWOOD ST., BREA, CA 92621
(714) 671-2009



NOW INCLUDES ANSWERS TO FCC/VEC EXAM QUESTIONS ARRL LICENSE MANUAL

Here's the latest up-to-date licensing guide from the ARRL. Plenty of theory and detailed explanations take most of the pain out of studying to upgrade your license.

© 1984 80th edition 216 pages
 AR-LG Softbound **\$4.00**
Please add \$2 shipping & handling

HAM RADIO'S BOOKSTORE
Greenville, NH 03048

MOSLEY...A BETTER ANTENNA...


Antennas For 40 Meters...

- *ALL STAINLESS HARDWARE
- *NO MEASURING
- *2 YEAR WARRANTY
- *5 KW P.E.P.
- *BROAD BAND WIDTH
- *BUILT TO LAST
- *NO BALUN NEEDED



S-401 M

Easy as... 1 - S-401 M. A 40 Meter Rotatable Dipole which gives you excellent bandwidth and performance. MOSLEY's S-401 M is the best 40 Meter Dipole ever built. All stainless hardware is standard. We have made it even stronger than before! We have added 2 extra insulator blocks and 2 feet more rectangle. The center of the elements are reinforced with an unbreakable non-conductive rod which makes it just about indestructible. Our link coupled feed system provides for an efficient match which enables you to direct feed the antenna with no need for a balun. This is why we give a 2 year warranty on parts, material, and workmanship.

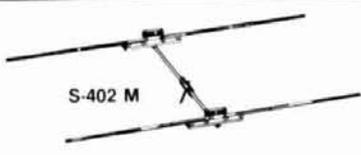

S-402 M

2 - Our S-402 M is now on a 24 foot boom and has all of the new improved structural changes. This antenna will give you years of outstanding mechanical and electrical performance in any climate. We feel this is the best performing, maintenance free, 2 element 40 Meter beam built anywhere in the world. Check it out! We believe you will agree. The elements are heavier constructed than other brands, and only reduces to 1 1/8 x .058 wall at their ends. Compare this to the other manufacturers. The S-402 M also comes with our 2 year warranty!



S-403

3 - The S-403 is the killer of the three models. This antenna gives you full size performance and is built to last. Our 36 foot boom is made out of 2" x .104 wall with a 24 foot sleeve of 1.785 x .125 wall. This gives you a wall thickness of .229 over 24 feet of the boom. The S-403 is spaced to give you the best front to back and forward gain. It will give you the whole 40 Meter band to chase DX or rag chew. Our S-403 also comes with our 2 year warranty.

If you are a new ham and are not familiar with MOSLEY, ask an older ham about us or call the PRESIDENT of MOSLEY. He will be glad to explain why MOSLEY is A BETTER ANTENNA.

These and other MOSLEY products are available through your favorite DEALER. Or write or call MOSLEY for the DEALER nearest you.




1344 BAUR BLVD. ST. LOUIS, MISSOURI 63132

1-314-994-7872

1-800-325-4016

1985 CALLBOOKS

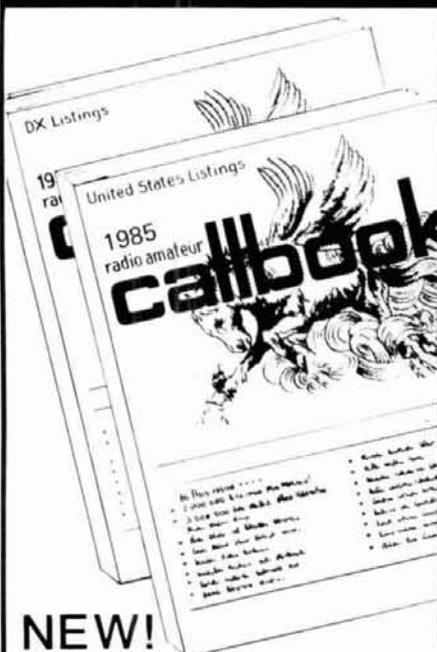

NEW! Special North American Edition

As an added bonus, the 1985 U.S. Callbook also lists the amateurs in Canada and Mexico! You get the complete and accurate U.S. listings (prepared by our own editorial staff), all the usual up-to-date Callbook charts and tables, PLUS Canada and Mexico. Now that's real value!

The best just got better!

Of course, Canadian and Mexican amateurs are also listed in the 1985 Foreign Callbook. Don't delay! The great new 1985 Callbooks were published December 1, 1984.

Order your copies now!

| | Each | Shipping | Total |
|---|---------|----------|---------|
| <input type="checkbox"/> U.S. Callbook | \$21.95 | \$3.05 | \$25.00 |
| <input type="checkbox"/> Foreign Callbook | 20.95 | 3.05 | 24.00 |

Order both books at the same time for \$45.00 including shipping within the USA.

Order from your dealer or directly from the publisher. Foreign residents add \$4.55 for shipping. Illinois residents add 6% sales tax.

Keep your 1985 Callbooks up to date. The U.S. and Foreign Supplements contain all activity for the previous three months including new licenses. Available from the publisher in sets of three (March 1, June 1, and September 1) for only \$15.00 per set including shipping. Specify U.S. or Foreign Supplements when ordering. Illinois residents add 6% sales tax. Offer void after November 1, 1985.

RADIO AMATEUR **callbook** INC. 151
 Dept. F
 925 Sherwood Dr., Box 247
 Lake Bluff, IL 60044, USA

Tel: (312) 234-6600



DRAKE R-4/T-4X OWNERS AVOID OBSOLESCENCE

PLUG-IN SOLID STATE TUBES!
 Get state-of-the-art performance.
 Most types available

INSTALL KITS TO UPGRADE PERFORMANCE!

- BASIC Improvement
- Audio Bandpass Filter
- Audio IC Amplifier

TUBES \$23 PPD KITS \$25 PPD

OVERSEAS AIR \$7

SARTORI ASSOCIATES, W5DA
 BOX 832085
 RICHARDSON, TX 75083
 214-494-3093

✓ 152

HAZER YOUR ROHN 25 G Tower

- Antenna and rotator mount on HAZER, complete system trams tower in verticle upright position.
- Safety lock system on HAZER operates while raising-lowering & normal position. Never can fall.
- Weight transferred directly to tower. Winch cable used only for raising & lowering. Easy to install and use.
- Will support most antenna arrays.
- High quality materials & workmanship.
- Safety - speed - convenience - smooth travel.
- Complete kit for 50' or less tower includes winch, cable, hardware and instructions.

Hazer 2 Heavy duty alum. 12 sq ft load \$297.00 ppd.
 Hazer 3 Standard alum. 8 sq ft load 213.00 ppd.
 Hazer 4 Heavy galv. steel 16 sq ft load 278.00 ppd.
 Ball thrust bearing TB 25 for any of above 42.50 ppd.

As an alternative, purchase a Martin M-13 or M-18 aluminum tower engineered specifically for the HAZER system.

GLEN MARTIN ENGINEERING INC.
 P.O. Box H 253 Boonville, Mo. 65233
 816-882-2734



✓ 153

COMMODORE

-USER WRITTEN SOFTWARE-

Supporting all COMMODORE computers

Written by users, for users

★ GAMES ★ UTILITIES ★ EDUCATIONAL ★

Our Latest Releases

| | |
|--------------------------|----------------------------|
| C-64 Best Of Games | Vic 20 Best Of Games |
| C-64 Best Of Educational | Vic 20 Best Of Educational |
| C-64 Best Of Utilities | Vic 20 Best Of Utilities |
| C-64 84 Contest C-64 #1 | Vic 20 Best Of Utilities |
| C-64 84 Contest C-64 #2 | Vic 20 Contest Vic #1 |
| C-64 84 Contest C-64 #3 | |

Specify Disk Or Tape \$10.00 each

COMAL STARTER PAK - 4 Disk Set - \$35.00

Bulletin Board Sys - On Best Of Utilities Collections

COMMODORE 64™ collections #1 thru 12

VIC 20™ collections #1 thru 12

Tape/Disk \$10.00 each per collection ✓ 154

SERIAL CABLES DINSET™: Reset Switch LCM-LITE™

PDI Program Manual \$10.00

Shipping and Handling Charges

US/Canadian Orders Add \$3.00

Foreign Orders Add \$5.00

CHECK, MONEY ORDERS, VISA and

MASTERCARD accepted. NO COD's or P.O.'s

Write For A FREE Catalog

'PUBLIC DOMAIN™', INC.

5025 S. Rangeline Rd., W. Milton, OH 45383

10:00 a.m. - 5:00 p.m. EST - Mon. thru Fri.

(513) 698-5638 or (513) 339-1725

© 1984, 'PUBLIC DOMAIN™' and 'COMMODORE 64™' are trademarks of Commodore International, Inc.

IBM, a Registered Trademark of International Business Machines Corp.

FREE CATALOG

here is the next generation Repeater

MARK 4CR

No other repeaters or controllers match Mark 4 in capability and features. That's why Mark 4 is the performance leader at amateur and commercial repeater sites around the world. Only Mark 4 gives you Message Master™ real speech • voice readout of received signal strength, deviation, and frequency error • 4-channel receiver voting • clock time announcements and function control • 7-helical filter receiver • extensive phone patch functions. Unlike others, Mark 4 even includes power supply and a handsome cabinet.

Call or write for specifications on the repeater, controller, and receiver winners.

The **only** repeaters and controllers with REAL SPEECH!

Create messages just by talking. Speak any phrases or words in any languages or dialect and *your own voice* is stored instantly in solid-state memory. Perfect for emergency warnings, club news bulletins, and DX alerts. Create unique ID and tail messages, and the ultimate in a real speech user mailbox — only with a Mark 4.



MICRO CONTROL SPECIALTIES

Division of Kendecom Inc.

23 Elm Park, Groveland, MA 01834 (617) 372-3442

155

Free Antenna Accessories Catalog



◀ Coaxial Antenna Relays

Remotely select up to 9 antennas from your transmitter, using only *one* coaxial cable. Environmentalized, high power and low loss.

W2AU and W2DU Baluns▶

Our baluns, center insulators and insulators have been preferred for 20 years by Hams, industry, and the armed forces. Protect against TVI and lightning 1.8–200 MHz.



◀ W2VS Antenna Traps

Add these traps to your dipole and get low SWR on 2 to 6 bands, depending on how many you add. Antenna wire and custom kits also available.



Send For Yours Today▶

Don't delay. Call or write today, and we will send you free literature which fully describes our Ham antenna accessory product line.

Dealer inquiries also welcome.



UNABLE TO REPLY? CALL US
A Division of Microwave Filter Co., Inc.

6743 Kinne St., East Syracuse, NY 13057
Toll Free 1-800-448-1666 TWX 710-541-0493
NY/HI/AK/Canada (Collect) 315-437-3953

156

More Details? CHECK — OFF Page 126

YOU WANT IT? DAN'S GOT IT!

YAESU



FT-209

KENWOOD



TM-211

ALL OF THESE GOODIES AND MANY MORE
AT A SUPER SAVINGS!

CALL TODAY

1 (800) 241-2027

BRITT'S 2-WAY RADIO

Sales & Service


2508 Atlanta Street
SMYRNA, GA. 30080
(404) 432-8006

157

NEW

2 meter amateur antenna the Mosley Diplomat 2

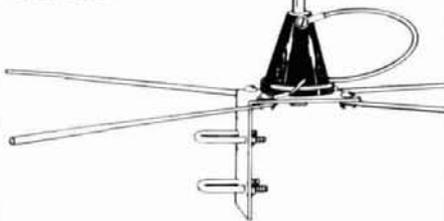
Special customizing features Available for the Business & Marine Bands. Other Special frequencies available.



Omni-directional vertically polarized high-performance 2 meter antenna with low angle of radiation for maximum coverage. The newest addition to the Mosley 2 meter line of Quality antennas! Ideal for area 2 meter QSO's and repeater to mobile communications. Simplicity of design makes for ease in assembly. Vertical element made of high tensile strength, high grade aluminum. High impact polystyrene base. All parts 100% rust-proof. Antenna lightweight. Power rated 1 KW FM/CW, 2 KW P.E.P. SSB input to the final. Mounting fits up to 1 1/2" OD mast. Another Quality addition to the Mosley 2 meter family of antennas.

SPECIFICATIONS AND PERFORMANCE DATA

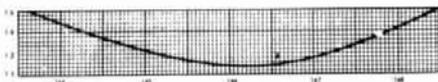GAIN: 3.4 db. compared to 1/4 wave ground plane
VSWR: 1.5/1 or better
IMPEDANCE: 52 ohms
MATCHING: 'Induct-O-Match'
GROUND RADIALS: 4
WIND LOAD (80 MPH EIA STD), VERTICAL: 6.12 lbs.
ASSEMBLED WEIGHT (approx.): 1 lb. 12 oz.
HEIGHT (approx.): 4 ft.




Mosley Electronics, Inc.

1344 Baur Boulevard, St. Louis, Mo. 63132
1-314-994-7872 1-800-325-4016

DX on 160, 80 and 40 meters with your own **SECRET WEAPON**

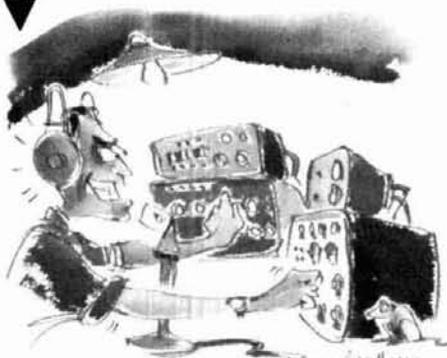Alpha Delta's new DX-A Twin Sloper Antenna combines the tremendous power of the quarter wave sloper with the wide bandwidth of a half wave dipole. Easy to install, simple to tune.



"DX is a snap with my secret weapon!"

- 160 and 80 m leg approx. 80' long. 40 meter leg 33' long. Installs just like an inverted V. Fed with single 50Ω feedline
- Current lobe up high for maximum radiation. Can be installed between 25' and 40 feet
- Broad band performance. Although bandwidth is determined by your installation, tests have shown 85 kHz on 160 m, 200 kHz on 80 m, and full coverage of 40 m. Tuner usually not required.
- No lossy traps. A single "ISO-RES," isolator/resonator coil is used to tune 80 and 160 meters
- Rated at 1.5 KW output
- Quality hardware and UV protected coil. Stainless steel ensures excellent all weather performance.

\$4995 ready to install

Available from your local Alpha Delta Dealer or add \$3.00 shipping and handling. (USA only)

ALPHA DELTA COMMUNICATIONS, INC.

P.O. Box 571, Centerville, Ohio 45459
(513) 435-4772 Order line • (513) 376-4180 Tech Info (antennas only)

current solutions to current problems

✓ 158

Gunnplexers & accessories 10 & 24 GHz



A. Microwave Associates 10 GHz Gunnplexer. Two of these transceivers can form the heart of a 10 GHz communication system for voice, mcw, video or data transmission, not to mention mountaintop DXing! MA87141-1 (pair of 10 mW transceivers) \$251.95. Higher power units (up to 200 mW) available. B. Microwave Associates 24 GHz Gunnplexer. Similar characteristics to 10 GHz unit. MA87820-4 (pair of 20 mW transceivers) \$739.20. C. This support module is designed for use with the MA87141 and MA87820 and provides all of the circuitry for a full duplex audio transceive system. The board contains a low-noise, 30-MHz fm receiver, modulators for voice and mcw operation, Gunn diode regulator and varactor supply. Meter outputs are provided for monitoring received signal levels, discriminator output and varactor tuning voltage. RXMR30VD assembled and tested \$119.95. D. Complete, ready to use communication system for voice or mcw operation. Ideal for repeater linking. A power supply capable of delivering 13 volts dc at 250 mA (for a 10 mW version), microphone, and headphone and/or loudspeaker are the only additional items needed for operation. The Gunnplexer can be removed for remote mounting to a tower or 2 or 4 foot parabolic antenna. TR10GA (10 GHz, 10 mW) \$399.95. Higher power units available. TR24GA (24 GHz, 20 mW) \$639.95. Also available: horn, 2 and 4 foot parabolic antennas, Gunn, varactor and detector diodes, search and lock systems, oscillator modules, waveguide, flanges, etc. Call or write for additional information. Let ARR take you higher with quality 10 and 24 GHz equipment!

Advanced Receiver Research

Box 1242 • Burlington CT 06013 • 203 582-9409



✓ 160

automatic temperature control

Prevent premature
equipment failures
by sensing and acting on
heat changes

A few months back I acquired a solid-state VHF amplifier capable of running 200 watts output with only 3.5 watts of drive from my handheld. Because I do most of my VHF operating at home, I decided to put the amplifier in the garage with the rest of the ham shack. This facilitated connections to the power supply and antenna, and since the garage is connected to the kitchen of our house, a 25-foot "umbilical cord" of RG8-X coax allows me to wander about the kitchen and living room while continuing to QSO on 2 meters with 200 watts out.

The only problem with this arrangement is that a 200-watt amplifier draws a great deal of current and gets very hot, especially during the summer in our garage. A large muffin fan mounted at the back of the amplifier cooled it to a reasonable level, but I still had to go out to the garage to turn the fan on every time I wanted to use the amplifier. Although this procedure worked fine, it was an annoying task.

One day some DX suddenly appeared on 146.52. Without thinking, I grabbed my handie talkie and proceeded to make a 1200-mile contact on direct! Fantastic!

Yes, it was . . . until the transistors in the amplifier unsoldered themselves. Fortunately, the transistors themselves weren't ruined — I don't know why — and I was able to repair the damage. But I obviously needed a better method of controlling the temperature of the amplifier without having to remember to turn on the fan and without having to waste electricity by leaving the fan running all the time.

The thermostatically controlled AC outlet box described herein solved the problem. It features an ad-

justable thermostat built around a Motorola MC3423 overvoltage protection IC, a remote temperature sensor, and visual indicators of the state of the thermostat and the presence of AC voltage at the outlet. A flip of the front panel switch allows the thermostat to detect a falling temperature rather than a rising one, thus enabling the box to be used to turn on a heater or crystal oven during the winter months.

theory of operation

Figure 1 is a schematic of the thermostatically controlled outlet box. The heart of the circuit is U1, an MC3423. This IC was originally designed to function as an overvoltage protection device for DC power supplies. Normally, R6 and R7 would be two resistors placed across the output of the power supply. If the power supply voltage exceeds a critical amount (determined by the values of R6 and R7), pin 8 of the MC3423 goes high (approximately 2 volts < VCC). Normally, pin 8 would be connected to the gate of an SCR that had been bridged across the terminals of the supply. Voltage on the gate would cause the SCR to conduct, shorting the power supply and blowing a fuse or tripping a circuit breaker.

However, this very versatile IC can function as a thermostat by using an NTC (negative temperature coefficient) thermistor for R7. Using a potentiometer for R6 allows the thermostat circuit to be adjusted. When the power supply's voltage is constant, the resistance of R7 changes with temperature and "fools" the MC3423 into sensing an overvoltage condition, sending voltage to pin 8. As R7 warms up, its resistance falls. A greater value for R6 means a lower temperature will trigger U1 on, while lowering the value of R6 raises the temperature at which U1 triggers.

Substituting a PTC (positive temperature coefficient) thermistor for R7 — that is, a thermistor whose resistance decreases as its temperature decreases — would allow one to sense falling temperatures instead of rising ones. However, PTC thermistors are difficult

By Douglas Rowlett, WB5IRI, 2603 North Brompton, Pearland, Texas 77584

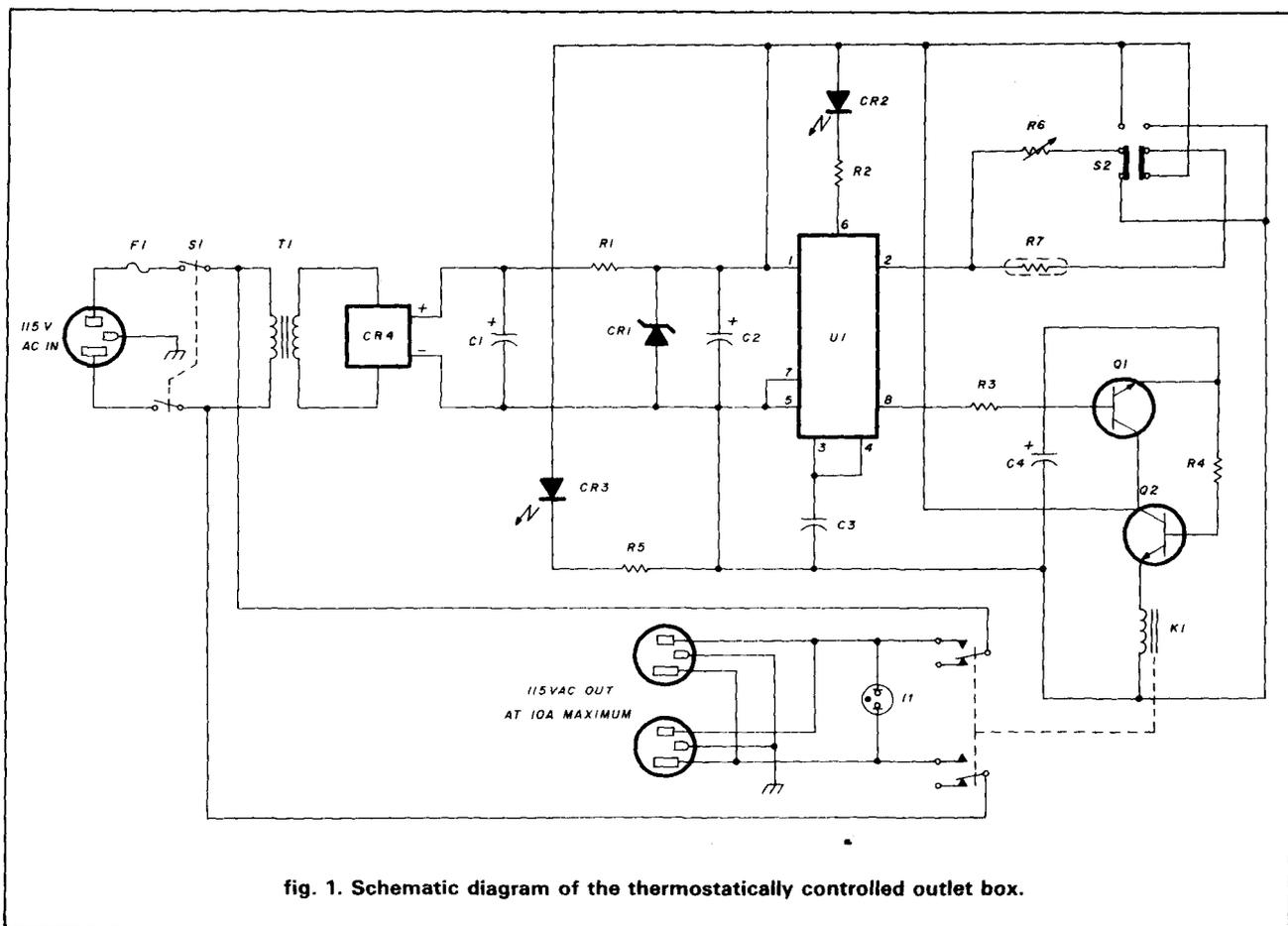


fig. 1. Schematic diagram of the thermostatically controlled outlet box.

| Item | description |
|--------|--|
| C1 | 3000 µF, 35-volt electrolytic |
| C2 | 100 µF, 35-volt electrolytic |
| C3 | 0.1 µF disc ceramic |
| C4 | 330 µF, 35-volt electrolytic |
| CR1 | 13-volt, 5-watt zener diode (RCA SK-13 or equivalent) |
| CR2 | amber LED |
| CR3 | green LED |
| CR4 | bridge rectifier, 50-volt, 1 ampere (RS 276-1161 or equivalent) |
| F1 | 10-ampere fuse |
| I1 | miniature red neon lamp assembly (RS 272-708 or equivalent) |
| K1 | DPDT relay, 10-ampere contacts at 125 VAC, 12-volt coil (RS 275-218 or equivalent) |
| Q1, Q2 | 2N2222 transistors or equivalent |
| R1 | 75 ohms, 5 watts |
| R2 | 270 ohms, 1/2 watt |
| R3 | 10 kilohm, 1/4 watt |
| R4 | 15 kilohm, 1/4 watt |
| R5 | 270 ohms, 1/2 watt |
| R6 | 50 kilohm, panel mount potentiometer |
| R7 | NTC thermistor, 1/4 watt, 10 kilohms at 70 degrees F (FR-1001A or equivalent) |
| S1 | DPST toggle switch, 10-ampere contacts |
| S2 | DPDT miniature slide switch |
| T1 | 12.6-volt, 300-mA transformer (RS 273-1385 or equivalent) |
| U1 | MC3423 overvoltage protection IC |

to find in my area, and they are more expensive than NTC thermistors. S2 provides a simple way around this problem. Flipping S2, a DPDT slide switch, reverses the order in which R6 and R7 are connected to the power supply. As R7's temperature falls its resistance increases, thus allowing U1 to trigger when the temperature of R7 falls to a point determined by R6.

When U1 triggers it sends voltage to the base of Q1, a 2N2222, which conducts and allows voltage to be applied to C4 and the base of Q2, another 2N2222. C4 charges and Q2 conducts, thus keying relay K1, which applies 115 VAC to the dual outlet. Anything plugged into the outlet, such as a fan or heater, then turns on. U1 also turns on CR2, an amber LED, through pin 6, giving a visual indication that the triggering temperature has been reached. When the temperature changes to the point at which R7 can no longer hold U1 in its triggered state, U1 removes voltage from pin 8 and turns off CR2. C4, however, continues to energize K1 for approximately 1 minute, which prevents constant cycling of the relay and the devices connected to the dual outlet. Changing the value of C4 results in a fairly linear change in relay hold-in time for K1. For example, doubling the listed value of C4 gives a hold-in time of approximately 2 minutes,

while halving the value of C4 gives a hold-in time of approximately 30 seconds. I1, a small red neon indicator across the contacts of K1, provides a visual indication that the outlet is "live," even when CR2 indicates that U1 is not in its triggered state.

Transformer T1 and CR4, C1, CR1 and C2 provide a regulated operating voltage for the thermostat. A regulated voltage is not really necessary for this circuit, and CR1 and C2 could be omitted with little performance degradation. However, since U1 is really a voltage-sensing device rather than a temperature-sensing device, a regulated voltage across R6 and R7 insures that changing line voltages will not affect the temperature at which U1 triggers.

Capacitor C3 prevents line transients from triggering U1 by setting the IC's internal delay time. Increasing the value of C3 increases the time during which an "overvoltage" condition can exist before U1 triggers. If this thermostat is to be operated in an environment where transients can be picked up by the internal or external wiring, such as near a transmitter, the value of C3 may have to be increased to prevent false triggering of U1. Since the duration of transients will vary from location to location, you will have to determine the best value for C3 yourself. I have had to go as high as 0.5 μ F in some locations, such as near a 2-kW homebrew amplifier.

Relay K1 has contacts rated at 125 VAC, 10 amperes maximum. Thus, F1 is a 10-ampere fuse intended primarily to protect K1 from damage if the load at the dual outlet becomes excessive. Of course, any relay can be used at K1, but using a relay with a lower coil impedance than 160 ohms may necessitate using a heavier transistor at Q2. Any relay you use, however, must be able to be energized by the voltage across T1. A relay whose contacts can handle more current may be necessary, in addition to a heavier switch at S1, if the thermostat is to be used to control some devices, such as space heaters, that draw large amounts of current when first turned on. The value of F1 would also have to be increased in such an instance. In the interests of safety, however, *do not, under any circumstances, omit F1*, and be certain that it is placed on the "hot" side of the AC line, not on the "neutral" side.

construction

Construction of the thermostat and outlet box is fairly straightforward, and layout is entirely noncritical. All the components, including T1 and K1, will fit on one small circuit board, with the exception of R7. This is covered with heat-shrink tubing and attached to the end of a piece of RG-174U miniature coax for remote sensing. R6, CR1, CR2, I1, S1, S2, and the AC outlet are mounted on the front panel. **Figure 2** is a

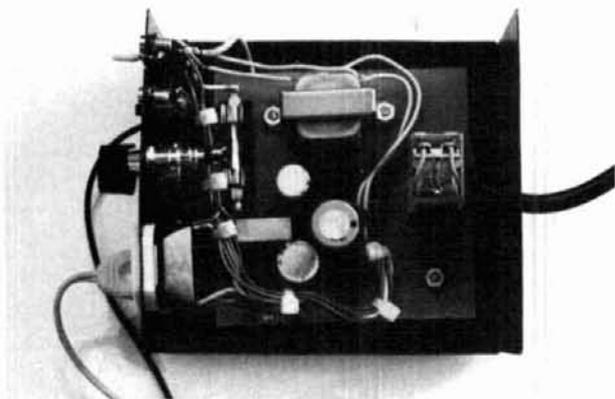


fig. 2. Internal view, with top cover removed. F1, T1, and K1 are mounted near the top of the board. U2 is barely visible beneath the wiring at the lower left corner of the board.

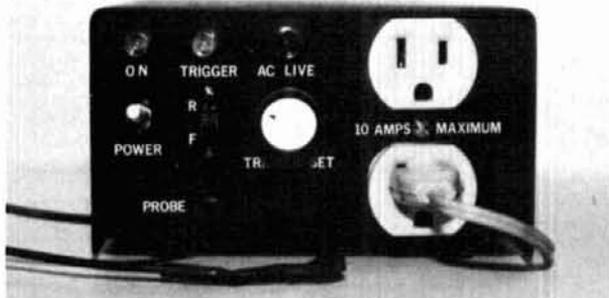


fig. 3. View of the front panel. Coiled black wire contains thermistor R7 (covered with heatshrink tubing) at one end.

photograph of the completed outlet box with the cover removed.


I suggest using sockets for CR4 and U1 to make replacement, if ever needed, easier. In addition, you should use at least No. 12 wire from the AC line to K1 and from K1 to the dual outlet.

operation

Using the thermostat box is easy. Just plug it into a 115 VAC outlet and supply power through S1 (see **fig. 3**). The green LED should come on, and the amber LED and red neon indicator may come on at this time. If they do, adjust R6 until the amber LED goes out; a minute later I1, the red neon indicator, should go out as C4 discharges and K1 opens. *Once again, remember that whenever I1 is on, 115 VAC is present at the dual outlet, and I1 provides a visual warning of the presence of potentially lethal voltage.*

Now set S2 to the condition you wish to monitor — that is, either rising or falling temperature. Place R7 at a convenient point where it will be exposed to the temperature you wish to control. For example, the sensor can be placed between the fins of an amplifier's

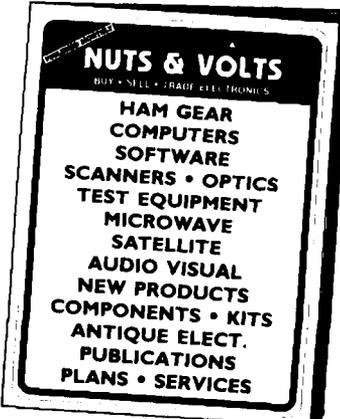**DO YOU
KNOW
WHERE
TO FIND
REAL
BARGAINS**



**on NEW and USED
ELECTRONIC Equipment?**

**You'll Find Them
in the Nation's No. 1
Electronic Shopper Magazine**

NUTS & VOLTS

Now in Our 5th Year

Nuts & Volts is published MONTHLY and features:
**NEW STATE-OF-THE-ART PRODUCTS •
 SURPLUS EQUIPMENT • USED BARGAINS
 • LOW COST AD RATES • PRIVATE AND
 COMMERCIAL CLASSIFIEDS • NATIONAL
 CIRCULATION • NEW PRODUCT NEWS
 SECTION • AND A FREE CLASSIFIED AD
 WITH YOUR SUBSCRIPTION**

SUBSCRIPTION RATES

- One Year - 3rd Class Mail \$10.00
- One Year - 1st Class Mail \$15.00
- One Year - Canada & Mexico (in U.S. Funds) .. \$18.00
- Lifetime - 3rd Class Mail (U.S. Only) \$35.00

ORDER NOW!

SEND: CHECK MONEY ORDER
 VISA MASTERCARD

TO: **NUTS & VOLTS MAGAZINE**
 P.O. BOX 1111-H
 PLACENTIA, CALIFORNIA 92670
 (714) 632-7721

Name _____
 Address _____
 City _____
 State _____ Zip _____
 Card No. _____
 Exp. Date _____

**IF YOU'RE INTO ELECTRONICS,
THIS MAGAZINE WILL SAVE YOU MONEY!**

Dealer Inquiries Invited

✓ 162

heatsink. Plug a fan into the outlet on the front panel, and adjust R6 until CR2 and I1 come on when the amplifier becomes hot enough to need cooling. As the fan blows cool air across the amplifier's heatsink, R7 will cool off and CR2 will go out. The fan, however, will continue to run for one minute.

That's all there is to it. As the amplifier heats up, the thermostat will turn on the fan to cool things down. When the amplifier is not in use, the fan will remain off.

other uses

This device can be used anywhere around the shack or the house where you wish to sense a rising or falling temperature. For example, it can function as a freezer alarm by plugging a 115 VAC alarm bell into the outlet and adjusting the thermostat to trigger whenever the temperature rises above 32 degrees F. It can be used to turn on a crystal oven when the temperature inside an oscillator falls below 80 degrees F (27°C). It can even be used to turn on a floor fan or space heater whenever the temperature in your shack rises or falls to uncomfortable levels. Anywhere you need to monitor a rising or falling temperature and turn on some device at a critical point, this thermostat will come in handy.

ham radio

BRAND NEW

BEAM ANTENNA HANDBOOK

by Bill Orr, W6SAI
and Stu Cowan, W2LX



Bill Orr and Stu Cowan have completely revised and updated the **Beam Antenna Handbook** to include the very latest information on state-of-the-art antenna design. Accurate, computer generated beam dimensions for the 40, 30, 20, 17, 15, 12, 10 and 6 meter bands and VHF bands are included eliminating the need for time consuming math calculations. Also covered are: Beam height and optimum apex of radiation, how element types and hardware effect performance, effect of nearby objects on radiation patterns, feedlines, baluns and matching systems and much more. Ham Radio VHF columnist, W1JR, and noted European VHF'er DL6WO's VHF antenna designs are covered extensively as well as NBS VHF long Yagis. 268 clearly written pages — 204 easy-to-understand illustrations make this the book to buy for beam construction. ©1985. 1st edition.

RP-BA
Softbound \$9.95

Please enclose \$3.50 for shipping and handling.

ham
radio magazine

GREENVILLE, NH 03048

BOOKSTORE

(603) 878-1441

ATU-1000™

Advanced Terminal Unit

NEW!



More Hardware Features And Performance Than Any Other Morse, Baudot, ASCII, AMTOR, SITOR, or H.F. Packet Terminal Unit Anywhere At Any Price!

We recognize that there are few amateurs who can appreciate or afford the outstanding value of the ATU-1000, but those who can are in for some very pleasurable operating. The ATU-1000 is a commercial/military unit with all the performance and flexibility that is attainable from today's technology. Just check out the features below.

- 32 poles, active filtering
- Morse/Baudot/ASCII/AMTOR/SITOR/H.F. Packet
- Set receive filters to one Hz accuracy
- Set receive MARK & SPACE filters independently from 1000 to 3000 Hz
- All shifts, 170 Hz fixed or 0 to 2000 Hz adjustable
- Set AFSK output tones independently from 1000 to 3000 Hz to one Hz
- 5mV to 5V AGC
- Front-panel squelch control
- Built-in 4 digit counter
- CW filter adjustable 700 to 2500 Hz
- D.C. coupled automatic threshold correction
- Twin full-wave detectors
- Built-in TTL/RS-232/and loop keyer I/O
- Discriminator-type tuning indicator
- FSK, AFSK, and scope outputs
- 13 VDC operation, 110 VAC adaptor supplied
- TTL I/O logic inversion for use with virtually any software
- Optional 19 inch rack mount kit

Ask your favorite dealer for a demonstration of the world's finest RTTY/CW advanced terminal unit/computer interface—the AEA model ATU-1000. If you cannot see your dealer, send for our latest specification sheet.

*Prices & Specifications Subject To Change
Without Notice Or Obligation.*

**VHF
COMMUNICATIONS**

915 North Main Street
Jamestown, New York 14701 (716)664-6345


AEA

**Brings you the
Breakthrough!**

Great with New
Solid State Transceivers

Trap-Mobile MA-3 by Mosley

Mobile Antenna

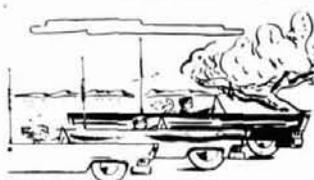

FEATURE: Trap is completely weather-proof . . . sealed against dirt, rain and snow!



FEATURE: Exclusive MOSLEY trap design assures stable operation. Inductive and capacitive values cannot change!



FEATURE: Base coil—Material is charcoal activated polyethylene. Unaffected by weather or road shock!


Here is a three band Mobile Whip which operates on 10, 15 and 20 meters with . . . NO BAND-SWITCHING . . . or other mechanical devices. An overall length of 7'8 1/2" provides an electrical 1/4 wavelength on each band assuring excellent performance with low SWR over full bandwidth. Coils are moisture-proofed for constant all weather operation. Traps enclosed in polished aluminum cover with slim profile for low wind resistance. Anti-sway design improves signal stability while "in motion." Stainless steel whip sections. Base stud, 3/8" x 24, fits all standard mounts. Shipping weight, 6 lbs.

Stainless steel whip sections (290,000 PSI) permit antenna to lay forward over car for "garaging."

GUARANTEED! May be used with any 40-80 meter base loading coil!
Will Not Take Set!
Will Not Warp! Mosley 40-80 Meter

Base Coil Now Available!

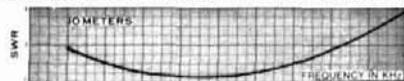SWR/FREQ. CURVES FOR MODEL MA-3 TRAP-MOBILE ANTENNA



Mosley Electronics Inc.

1344 Baur Boulevard, St. Louis, Mo. 63132
1-314-994-7872 1-800-325-4016

MADISON Electronics Supply

3621 Fannin St.
Houston, TX. 77004
Call for Quotes
1-800-231-3057
Old Texas Number:
1-713-658-0268
New Texas Number:
1-713-520-7300
(Starts June 1)

EQUIPMENT
KENWOOD R-11 SPECIAL 69.96
KENWOOD - We have all the KENWOOD line in stock, including the NEW RIGS: TS-711A 2 mtr. all mode, TR-2600A HT, TH-21AT mini HT, TH-41AT 70 cm mini HT, TS-811A 70cm all mode, TM-211A mobile, TS-411A 70cm mobile, TS-670 40, 15, 10 and 6 mtrs CALL FOR PRICES
KENWOOD SW, R-2000, R-1000, R-600 and the R-11 CALL
KENWOOD TS-430S and TS-930S CALL
KENWOOD TS-530SP and TS-830S CALL
ICOM Q2AT 299.95
YAesu FT203R CALL
MIRAGE AMPS less 12%
DENTRON GIT1000 1KW PEP tuner 174.95
WM NYE MB-V 3KW tuner / switch 489.95
ICOM R-71A 649.95
CES 510SA SMART PATCH 299.95

ACCESSORIES
FLUKE 77 auto digital multimeter 114.95
BENCHER less 10%
VIBROPLEX less 10%
HELL SOUND less 10%
DAWA NEW METERS CALL
GORDON WEST code tapes (great) 9.95
HI-MOUND Keyer paddles less 10%
ALPHA DELTA MACC-8 surge protector 71.95

AMPHENOL
8311 coax tap 4.00
PL 259, 831-SP 1.25
UG 176 reducer RG8X/RG59 30
4400 N male to SO-239 6.00
2900 BNC male to SO-239 4.00
8261 N male 3.00
8310 RCA to SO-239 3.00
82-97 N female chassis 3.00
Other AMPHENOL products STOCK CALL
BELDEN CABLE STOCK CALL

ANTENNAS
BARKER & WILLIAMSON Antennas less 10%
BUTTERNUT HF-2V 80 & 40 mtr 125.00
BUTTERNUT HF-6V 80 thru 10 125.00
BUTTERNUT accessories stock CALL
AEA ISOPOLE 144 39.95
HYGAIN CALL
MOSLEY TA-33M 249.00
MOSLEY PRO-37 469.00
MOSLEY TA-33JR 189.00
We stock MOSLEY CALL
LARSEN CALL
CDE 45-2 Rotator 99.95
CUSHCRAFT A147-11 49.95
A147-4 29.95
215WB NEW! 2 mtr beam 79.95
ADP-1 complete OSCAR Antenna 149.95
we have a large CUSHCRAFT inventory

HUSTLER CALL
ANTECO 2mtr 5/8 mag mount 24.95
KLM KT34A 329.95
JV2X 2 meter vertical 31.95
435-40X 159.00
432-20LBX 66.95
432-16LBX 49.95
40M-2 2 el 40 mtr 298.95
2M-13LBA 79.95
2M-22C 119.95
2M-14C 87.95

KLM is always in stock, large selection of HF, VHF, UHF, & WORLD CLASS CALL
GUY CABLE regular & EHS CALL
ROHN TOWER CALL
FK-254B, 48 ft with guy bracket, rotor shelf, eave bracket & M200H mast 999.00
GENUINE ROHN ACCESSORIES CALL

SURPLUS
CDE DPDT RELAY 10 amp NEW 5.00
2 5A/1000 PIV epoxy diode 19.00/100
RTTY

We stock AEA, HAL, KANTRONICS & MFJ
Call with your requirements ✓ 164
POLICIES: MASTERCARD - VISA - COD
All prices FOB Houston, TX, except as noted. Prices subject to change without notice, subject to prior sale. Used gear sale price refunded if not satisfied. Texas residents subject to sales tax.

Why fight rusted nuts, bolts, and set screws? Use Stainless Steel, Bronze, and Monel fasteners from Exmet.

Exmet offers:

- 1) No minimum billing.
- 2) No minimum quantity (1 → ∞).
- 3) The finest quality, fully warranted.
- 4) UPS shipment same day as received.
- 5) Sizes from #4 → 1-1/2" dia., and lengths from 1/8" → 7".

write or call:

Exmet, Inc.

2170 E. Aurora Rd.
P. O. Box 117
Twinsburg, Ohio 44087
(216) 425-8455

LEARN ALL ABOUT TROUBLESHOOTING MICROPROCESSOR-BASED EQUIPMENT AND DIGITAL DEVICES

Attend this *highly acclaimed seminar and master the essentials of microprocessor maintenance. Gain a firm understanding of microprocessor fundamentals and learn specialized troubleshooting techniques. \$695.00

1985 SUMMER

- San Diego, CA - June 25-28
- San Francisco, CA - July 9-12

*References provided upon request.

MICRO SYSTEMS INSTITUTE
Garnett, Kansas 66032
(913) 898-3265

Omega Concepts, Inc.

Presents

"STATION MANAGER"

ADVANCED

Professional Software
For The Radio Amateur

Terence L. Jones (KB8OA)
Author



Omega Concepts, Inc.
P. O. Box 615 Troy, OH 45373

ham radio

Reader Service

For literature or more information, locate the Reader Service number at the bottom of the ad, circle the appropriate number on this card, affix postage and send to us. We'll hustle your name and address to the companies you're interested in.

101 113 125 137 149 161 173 185 197 209 221 233 245 257 269 281 293 305 317 329 341
102 114 126 138 150 162 174 186 198 210 222 234 246 258 270 282 294 306 318 330 342
103 115 127 139 151 163 175 187 199 211 223 235 247 259 271 283 295 307 319 331 343
104 116 128 140 152 164 176 188 200 212 224 236 248 260 272 284 296 308 320 332 344
105 117 129 141 153 165 177 189 201 213 225 237 249 261 273 285 297 309 321 333 345
106 118 130 142 154 166 178 190 202 214 226 238 250 262 274 286 298 310 322 334 346
107 119 131 143 155 167 179 191 203 215 227 239 251 263 275 287 299 311 323 335 347
108 120 132 144 156 168 180 192 204 216 228 240 252 264 276 288 300 312 324 336 348
109 121 133 145 157 169 181 193 205 217 229 241 253 265 277 289 301 313 325 337 349
110 122 134 146 158 170 182 194 206 218 230 242 254 266 278 290 302 314 326 338 350
111 123 135 147 159 171 183 195 207 219 231 243 255 267 279 291 303 315 327 339
112 124 136 148 160 172 184 196 208 220 232 244 256 268 280 292 304 316 328 340

Limit 15 inquiries per request.

NAME _____ CALL _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Please use before July 31, 1985

June 1985

AFFIX POSTAGE
OR
POST OFFICE
WILL NOT
DELIVER

**ham
radio**

magazine

READER SERVICE CENTER
P.O. BOX 2558
WOBURN, MA 01888

ATTN: Reader Service Dept.

protecting equipment

Spring is typically the season in which most VHF/UHFers dust off their gear and get ready for all those good tropospheric and sporadic-E openings. It's also the time of year when static electricity and lightning tend to increase. Between the increased operating activity and the forces of nature, equipment failures can and do happen! Whether the result of carelessness or the ravages of nature, damage to expensive equipment can be frustrating. But with proper know-how and a little bit of effort, failures can be anticipated and prevented.

Many types of failures can affect Amateur equipment. — in-band RF, out-of-band RF, low frequency and supply transients, the forces of nature, damage in physical handling, and component overstressing are just a few.

in-band RF

Probably the prime source of failure in Amateur VHF/UHF equipment, in-band RF most often affects receivers. Simply put, the receiver input stage is subjected to RF on the frequency of interest at a level that exceeds the breakdown of the first active device. With the proliferation of solid-stage receivers over the last decade — especially on 70 cm and above, where high transmitter power (1000-1500 watts output) is required, — this phenomenon is now quite common. The primary reasons for this type of failure are inadequate T/R (transmit/receiver)

relay isolation and improperly timed relay sequencing.

relay isolation

Most Amateurs use T/R relays that are either the bladed or the lever arm type. The bladed type (**fig. 1A**) is the most common and is similar to the everyday low-frequency relay except in that a moving arm is built into a coaxial airline structure. The contacts are capacitance junctions and the spacing between the moving contact and the input or output connector contact determine the isolation between the transmitter and receiver. There are many tradeoffs with this type of relay because the spacing and the size of the contacts determine the isolation, VSWR, and power handling capability of the relay.

If the capacitance across the relay junction is known, the isolation can be calculated using the following formula:

$$\text{isolation} = 10 \log_{10} [1 + (X_c/2Z_0)^2] \quad (1)$$

where isolation is in dB, X_c is the capacitive reactance of the junction, and Z_0 is the transmission line impedance, typically 50 ohms. For example, a typical relay junction has a 0.1 pF capacitance. Therefore, at 500 MHz the capacitive reactance is 3180 ohms and the isolation will be approximately 30 dB. (For those who do not want to work out the mathematics, **fig. 2** shows isolation versus capacitance values.) Note that the isolation across

a purely capacitance junction decreases approximately 6 dB every time the frequency is doubled. Consequently, a relay with 40 dB of isolation at 2 meters will have only approximately 30.5 dB of isolation at 70 cm — quite a decrease!

Some relay designers add a set of grounding contacts across the open circuited contacts (**fig. 1B**). This can significantly increase the isolation. However, this places a short circuit across the attached device, typically a low-noise preamplifier. This may cause transients when switching or oscillations while in the transmit mode.¹

The lever arm relay configuration (**fig. 1C**) is more complex and hence more costly, but has higher isolation because this construction increases the spacings between the input and open circuited port of the relay. However, it is likely to have a lower power handling capability than the bladed type.

The relays most often used by Amateurs (and often found at flea markets) include the Amphenol 300, Dow-Key DK-60, M/A-Com 7524, and the Transco "Y." Typical isolation versus frequency is shown in **fig. 3** for some of the types mentioned. A typical solid-state receiver will withstand 10 milliwatts or +10 dBm (dB above a milliwatt) at its input without damage. Therefore, at an RF power level of 1500 watts (+62 dBm), a relay with at least 52 dB of isolation should be used.

The Transco type-Y relays I've pur-

chased at flea markets have shown high insertion loss on one or both of the paths. This is easily checked with an ohmmeter. When the contacts are energized, the resistance should be less than 1 ohm. Try cycling the relay several times to check for intermittencies, a common occurrence.

If the resistance is high, unscrew the appropriate connectors with a narrow-

width open end wrench (if the relay has set screws on the connectors, remove them first). Then burnish the contact point on the end of the connectors. Next, reach inside the center compartment and burnish the complementary contacts. (Better yet, remove all three connectors, carefully noting the position from which each was taken.) Clean all internal contacts and connectors and as a final measure use solvent or flux remover on all contacts to eliminate any film. Then rotate the connectors 120 degrees so that a different connector is placed in each position; this will increase the likelihood that each connector contact will be at a new and clean point. Retest the contact resistance. If you have a good RF test setup, measure the insertion loss. It should be less than 0.2 dB through 450 MHz. Isolation is seldom a problem.

All the relays just mentioned are available with type "N" connectors, the preferred connector type for 2 meters and higher frequencies. However, this connector type is power-limited to approximately 500 watts at 500 MHz and commensurately lower at higher frequencies. I know that

many Amateurs are exceeding this power level on "N" connectors; if you're one of them, keep your VSWR low and never try to "hot switch" RF power.

relay configurations

Some of the relays mentioned will not provide the isolation necessary to protect receivers, especially on the higher frequency bands. Therefore, a second relay is often cascaded with the T/R relay (see fig. 4A) to further increase receiver protection.¹

Because this second relay is switching low power, it doesn't have to be a high power type. Often relays with BNC connectors are used at the lower frequencies and SMA connectors at UHF. Furthermore, this relay doesn't have to have high isolation since the primary T/R relay is capable of providing most of the needed attenuation.

If two relays with similar isolation are connected back-to-back with the shortest possible connection, the combined isolation is only 6 dB greater than the single relay isolation.¹ If the same two relays are placed an electrical quarter wavelength apart at the operating frequency, the isolation will

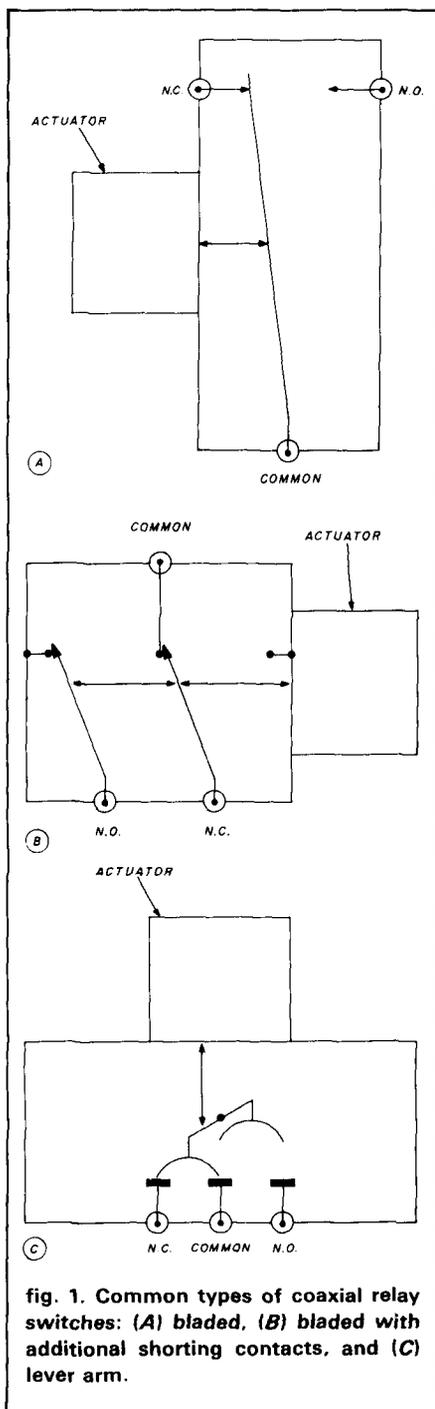


fig. 1. Common types of coaxial relay switches: (A) bladed, (B) bladed with additional shunting contacts, and (C) lever arm.

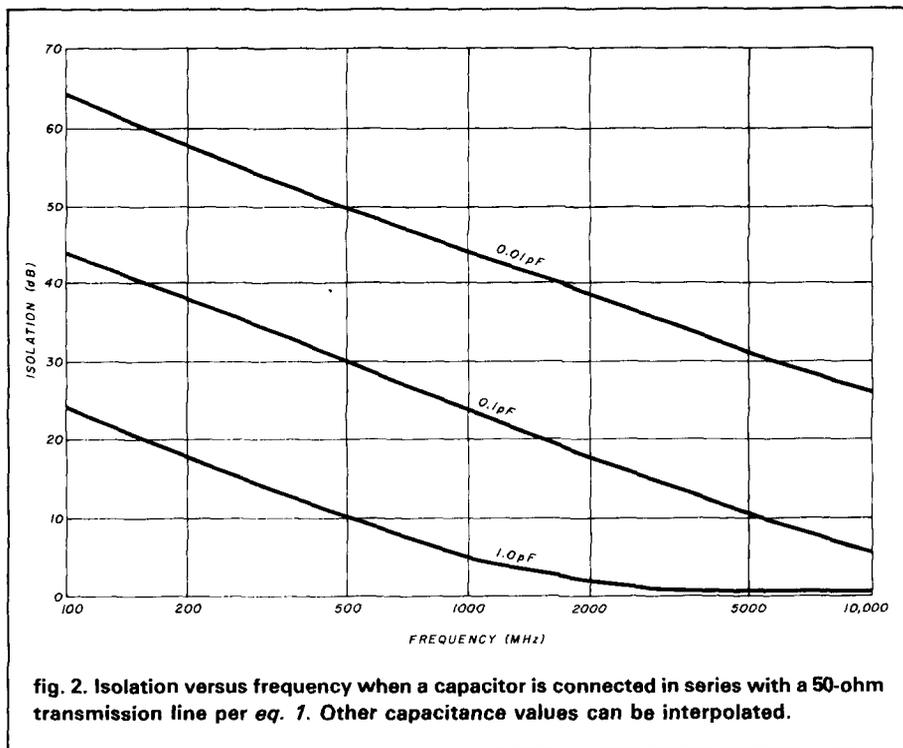


fig. 2. Isolation versus frequency when a capacitor is connected in series with a 50-ohm transmission line per eq. 1. Other capacitance values can be interpolated.

be approximately 6 dB greater than the combined relay isolation. For example, if two relays each with 30 dB of isolation are connected in cascade, the theoretical maximum isolation will be 66 dB.

Never use one-half wavelength spacing between T/R relays since the attenuation can theoretically go to 0 dB (fig. 5).² For practical and theoretical considerations, one-tenth

wavelength spacing is all that is recommended because it will keep losses at a minimum and decrease isolation by about only 6 dB from the maximum possible!

Figure 5, an updated version of the one shown in reference 1, will yield typical isolation values at a glance for a 30-dB isolation relay (the example discussed at the beginning of this article).

Other values of isolation can be calculated. The relay capacitance must first be measured or calculated using eq. 1. Then use the following equations:

$$\text{isolation} = 10 \log_{10} 0.25 [4 + (2X_N \cos \theta - X_N^2 \sin \theta)] \quad (2)$$

where isolation is in dB, X_N is per eq. 3 (below), and θ is the electrical spacing of the relay contacts in degrees.

$$X_N = \frac{Z_0}{2\pi fC} \quad (3)$$

where f is the frequency of operation in Hz, C is the open-circuited capacitance of the relay contacts in farads, and Z is the transmission line impedance in ohms.

remote preamplifiers

Remotely located or antenna-mounted preamps are becoming very popular, especially on 2 meters and up, on OSCAR 10, and on EME. The dual relay scheme illustrated in fig. 4A is highly recommended in these applications. Note that the preamplifier is terminated with a 50-ohm load when in the transmit mode, not a short or open circuit as discussed earlier in this article and in reference 1.

Finally, all T/R relays should have adequate time to switch before any transmitter power is applied. This is easy to accomplish if a high-voltage

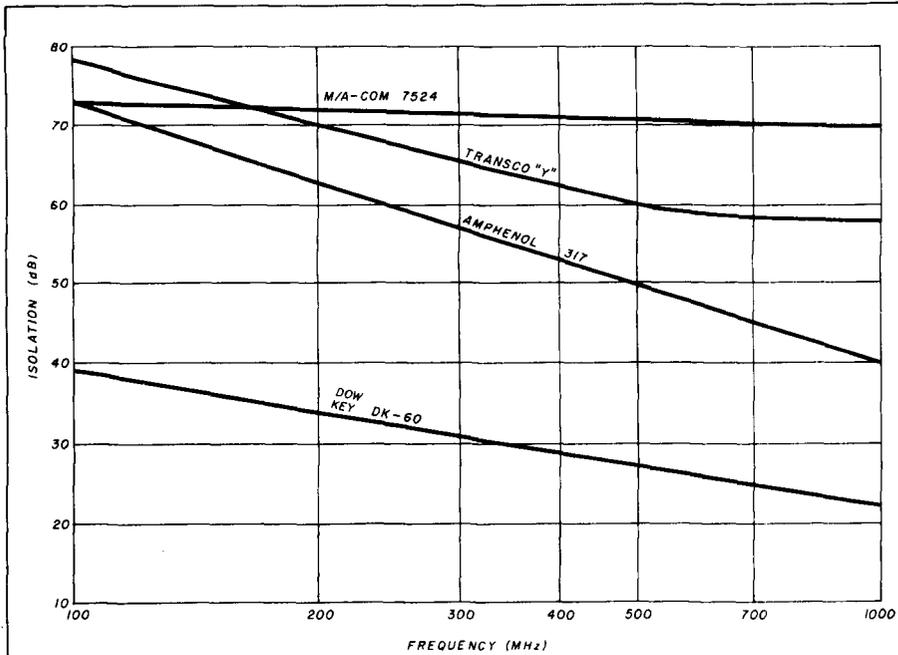


fig. 3. Typical values of isolation on some of the more popular T/R relays used by Amateurs.

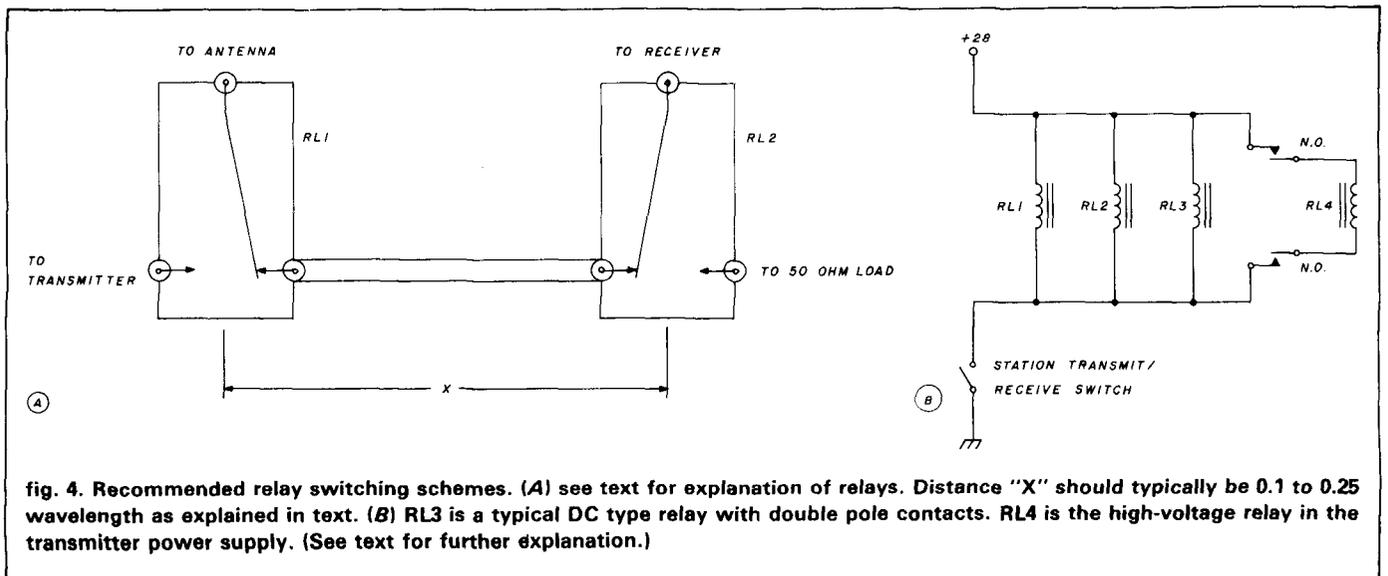


fig. 4. Recommended relay switching schemes. (A) see text for explanation of relays. Distance "X" should typically be 0.1 to 0.25 wavelength as explained in text. (B) RL3 is a typical DC type relay with double pole contacts. RL4 is the high-voltage relay in the transmitter power supply. (See text for further explanation.)



| HF Equipment | Regular | SALE |
|-------------------------------------|---------|-------------------|
| IC-735 Xcvr/SW rcvr/mic | 849.00 | 749 ⁹⁵ |
| PS-55 Power supply | TBA | |
| AT-120 Automatic antenna tuner | TBA | |
| FL-32 500 Hz CW filter | 59.50 | |
| EX-243 Electronic keyer unit | 50.00 | |
| IC-730 8-band 200w PEP xcvr w/mic | 829.00 | 569 ⁹⁵ |
| FL-30 SSB filter (passband tuning) | 59.50 | |
| FL-44A SSB filter (2nd IF) | 159.00 | 144 ⁹⁵ |
| FL-45 500 Hz CW filter | 59.50 | |
| EX-195 Marker unit | 39.00 | |
| EX-202 LDA interface; 730/2KL/AH-1 | 27.50 | |
| EX-203 150 Hz CW audio filter | 39.00 | |
| EX-205 Transverter switching unit | 29.00 | |
| SM-5 8-pin electret desk microphone | 39.00 | |
| HM-10 Scanning mobile microphone | 39.50 | |
| MB-5 Mobile mount | 19.50 | |
| IC-720A 9-band xcvr/.1-30 MHz rcvr | 1349.00 | 799 ⁹⁵ |
| FL-32 500 Hz CW filter | 59.50 | |
| FL-34 5.2 kHz AM filter | 49.50 | |
| SM-5 8-pin electret desk microphone | 39.00 | |
| MB-5 Mobile mount | 19.50 | |
| IC-745 9-band xcvr w/.1-30 MHz rcvr | 999.00 | 779 ⁹⁵ |
| PS-35 Internal power supply | 160.00 | 144 ⁹⁵ |
| EX-241 Marker unit | 20.00 | |
| EX-242 FM unit | 39.00 | |
| EX-243 Electronic keyer unit | 50.00 | |
| FL-45 500 Hz CW filter (1st IF) | 59.50 | |
| FL-54 270 Hz CW filter (1st IF) | 47.50 | |
| FL-52A 500 Hz CW filter (2nd IF) | 96.50 | 89 ⁹⁵ |
| FL-53A 250 Hz CW filter (2nd IF) | 96.50 | 89 ⁹⁵ |
| FL-44A SSB filter (2nd IF) | 159.00 | 144 ⁹⁵ |
| HM-10 Scanning mobile microphone | 39.50 | |
| SM-6 Desk microphone | 39.00 | |
| HM-12 Extra hand microphone | 39.50 | |
| MB-12 Mobile mount | 19.50 | |



| | | |
|-------------------------------------|---------|-------------------|
| IC-751 9-band xcvr/.1-30 MHz rcvr | 1399.00 | 1199 |
| PS-35 Internal power supply | 160.00 | 144 ⁹⁵ |
| FL-32 500 Hz CW filter (1st IF) | 59.50 | |
| FL-63 250 Hz CW filter (1st IF) | 48.50 | |
| FL-52A 500 Hz CW filter (2nd IF) | 96.50 | 89 ⁹⁵ |
| FL-53A 250 Hz CW filter (2nd IF) | 96.50 | 89 ⁹⁵ |
| FL-33 AM filter | 31.50 | |
| FL-70 2.8 KHz wide SSB filter | 46.50 | |
| HM-12 Extra hand microphone | 39.50 | |
| SM-6 Desk microphone | 39.00 | |
| CR-64 High stability reference xtal | 56.00 | |
| RC-10 External frequency controller | 35.00 | |
| MB-18 Mobile mount | 19.50 | |
| Options: 720/730/745/751 | Regular | SALE |
| PS-15 20A external power supply | 149.00 | 134 ⁹⁵ |
| EX-144 Adaptor for CF-1/PS-15 | 6.50 | |



| Options - continued | Regular | SALE |
|--|---------|-------------------|
| CF-1 Cooling fan for PS-15 | 45.00 | |
| EX-310 Voice synth for 751, R-71A | 39.95 | |
| SP-3 External base station speaker | 49.50 | |
| Speaker/Phone patch - specify radio | 139.00 | 129 ⁹⁵ |
| BC-10A Memory back-up | 8.50 | |
| EX-2 Relay box with marker | 34.00 | |
| AT-100 100w 8-band automatic ant tuner | 349.00 | 314 ⁹⁵ |
| AT-500 500w 9-band automatic ant tuner | 449.00 | 399 ⁹⁵ |
| AH-1 5-band mobile antenna w/tuner | 289.00 | 259 ⁹⁵ |
| PS-30 Systems p/s w/cord, 6-pin plug | 259.95 | 234 ⁹⁵ |
| OPC Optional cord, specify 2 or 4-pin | 5.50 | |
| GC-4 World clock (Closeout!) | 99.95 | 79 ⁹⁵ |
| HF linear amplifier | Regular | SALE |
| IC-2KL w/ps 160-15m solid state amp | 1795.00 | 1299 |
| VHF/UHF base multi-modes | Regular | SALE |
| IC-551D 80 Watt 6m transceiver | 699.00 | 599 ⁹⁵ |
| EX-106 FM option | 125.00 | 112 ⁹⁵ |
| BC-10A Memory back-up | 8.50 | |
| SM-2 Electret desk microphone | 39.00 | |
| IC-271A 25w 2m FM/SSB/CW xcvr | 699.00 | 619 ⁹⁵ |
| AG-20 Internal preamplifier* | 56.95 | |
| IC-271H 100w 2m FM/SSB/CW xcvr | 899.00 | 759 ⁹⁵ |
| AG-25 Mast mounted preamplifier* | 84.95 | |
| IC-471A 25w 430-450 SSB/CW/FM xcvr | 799.00 | 699 ⁹⁵ |
| AG-1 Mast mounted preamplifier* | 89.00 | |
| IC-471H 75w 430-450 SSB/CW/FM xcvr | 1099.00 | 969 ⁹⁵ |
| AG-35 Mast mounted preamplifier* | 84.95 | |

For a Limited time!
 With the purchase of IC-271A/H or IC-471A/H get the matching Preamp* for just \$1.00 extra.

| Common accessories for 271A/H and 471A/H | Regular | SALE |
|--|---------|-------------------|
| PS-25 Internal power supply for (A) | 99.00 | 89 ⁹⁵ |
| PS-35 Internal power supply for (H) | 160.00 | 144 ⁹⁵ |
| PS-15 External power supply | 149.00 | 134 ⁹⁵ |
| CF-1 Cooling fan for PS-15 | 45.00 | |
| EX-144 Adaptor for PS-15/CF-1 | 6.50 | |
| SM-6 Desk microphone | 39.00 | |
| EX-310 Voice synthesizer | 39.95 | |
| TS-32 CommSpec encode/decoder | 59.95 | |
| UT-15 Encoder/decoder interface | 12.50 | |
| UT-15S UT-15S w/TS-32 installed | 79.95 | |
| VHF/UHF mobile multi-modes | Regular | SALE |
| IC-290H 25w 2m SSB/FM xcvr, TTP mic | 549.00 | 479 ⁹⁵ |
| IC-490A 10w 430-440 SSB/FM/CW xcvr | 649.00 | 579 ⁹⁵ |
| VHF/UHF/1.2 GHz FM | Regular | SALE |
| IC-27A Compact 25w 2m FM w/TTP mic | 369.00 | 319 ⁹⁵ |
| IC-27H Compact 45w 2m FM w/TTP mic | 409.00 | 359 ⁹⁵ |
| IC-37A Compact 25w 220 FM, TTP mic | 449.00 | 299 ⁹⁵ |
| IC-47A Compact 25w 440 FM, TTP mic | 469.00 | 419 ⁹⁵ |
| UT-16/EX-388 Voice synthesizer | 29.95 | |
| IC-3200A 25w 2m/440 MHz FM xcvr | 549.00 | 489 ⁹⁵ |
| IC-120 1w 1.2 GHz FM transceiver | 499.00 | 449 ⁹⁵ |
| ML-12 10w amplifier | 339.00 | 299 ⁹⁵ |
| 6m portable | Regular | SALE |
| IC-505 3/10w 6m port. SSB/CW xcvr | 449.00 | 399 ⁹⁵ |
| BP-10 Internal Nicad battery pack | 79.50 | |
| BP-15 AC charger | 12.50 | |
| EX-248 FM unit | 49.50 | |
| LC-10 Leather case | 34.95 | |
| SP-4 Remote speaker | 24.95 | |



| Hand-held Transceivers | Regular | SALE |
|------------------------|---------|-------------------|
| Deluxe models | Regular | SALE |
| IC-02AT for 2m | 349.00 | 289 ⁹⁵ |
| IC-04AT for 440 MHz | 379.00 | 319 ⁹⁵ |
| Standard models | Regular | SALE |
| IC-2A for 2m | 239.50 | 189 ⁹⁵ |
| IC-2AT with TTP | 269.50 | 199 ⁹⁵ |
| IC-3AT 220 MHz, TTP | 299.95 | 239 ⁹⁵ |
| IC-4AT 440 MHz, TTP | 299.95 | 239 ⁹⁵ |

| Accessories for Deluxe models | Regular | SALE |
|--|---------|------|
| BP-7 425mah/13.2V Nicad Pak - use BC-35 | 67.50 | |
| BP-8 800mah/8.4V Nicad Pak - use BC-35 | 62.50 | |
| BC-35 Drop in desk charger for all batteries | 69.00 | |
| BC-60 6-position gang charger, all batts | 359.95 | |
| BC-16U Wall charger for BP7/BP8 | 10.00 | |
| LC-11 Vinyl case | 17.95 | |
| LC-14 Vinyl case for Dix using BP-7/8 | 17.95 | |
| LC-02AT Leather case for Dix models w/BP-7/8 | 39.95 | |
| Accessories for both models | Regular | SALE |
| BP-2 425mah/7.2V Nicad Pak - use BC35 | 39.50 | |
| BP-3 Extra Std. 250 mah/8.4V Nicad Pak | 29.50 | |
| BP-4 Alkaline battery case | 12.50 | |
| BP-5 425mah/10.8V Nicad Pak - use BC35 | 49.50 | |
| CA-2 Telescoping 2m antenna | 10.00 | |
| CA-5 5/8-wave telescoping 2m antenna | 18.95 | |
| FA-2 Extra 2m flexible antenna | 10.00 | |
| CP-1 Cig. lighter plug/cord for BP3 or Dix | 9.50 | |
| DC-1 DC operation pak for standard models | 17.50 | |
| LC-2AT Leather case for standard models | 34.95 | |
| RB-1 Vinyl waterproof radio bag | 30.00 | |
| HH-SS Handheld shoulder strap | 14.95 | |
| HM-9 Speaker microphone | 34.50 | |
| HS10 Boom microphone/headset | 19.50 | |
| HS-10SA Vox unit for HS-10 & Deluxe only | 19.50 | |
| HS-10SB PTT unit for HS-10 | 19.50 | |
| ML-1 2m 2.3w in/10w out amplifier | 79.95 | SALE |
| SS-32M Commspec 32-tone encoder | 29.95 | |

| Shortwave receiver | Regular | SALE |
|---------------------------------------|----------|-------------------|
| R-71A 100 kHz-30 Mhz digital receiver | \$799.00 | 659 ⁹⁵ |
| RC-11 Wireless remote controller | 59.95 | 49 ⁹⁵ |
| FL-32 500 Hz CW filter | 59.50 | |
| FL-63 250 Hz CW filter (1st IF) | 48.50 | |
| FL-44A SSB filter (2nd IF) | 159.00 | 144 ⁹⁵ |
| EX-257 FM unit | 38.00 | |
| EX-310 Voice synthesizer | 39.95 | |
| CR-64 High stability oscillator xtal | 56.00 | |
| SP-3 External speaker | 49.50 | |
| CK-70 (EX-299) 12V DC option | 9.95 | |
| MB-12 Mobile mount | 19.50 | |



Order Toll Free - Use your Credit Card!

HOURS • Mon. thru Fri. 9-5:30; Sat. 9-3
 Milwaukee WATS line: 1-800-558-0411 answered evenings until 8:00 pm Monday thru Thursday.
Please use WATS lines for Ordering
 use Regular lines for other Info and Service dept.

Order Toll Free: 1-800-558-0411 In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195
AMATEUR ELECTRONIC SUPPLY Inc.
 4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES

| | | | | |
|--|---|---|---|--|
| WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside Ohio 1-800-321-3594 | ORLANDO, Fla. 32803 621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside Florida 1-800-327-1917 | CLEARWATER, Fla. 33575 1898 Drew Street Phone (813) 461-4267 No In-State WATS No Nationwide WATS | LAS VEGAS, Nev. 89106 1072 N. Rancho Drive Phone (702) 647-3114 No In-State WATS Outside Nevada 1-800-634-6227 | Associate Store CHICAGO, Illinois 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181 Outside Illinois 1-800-621-5802 |
|--|---|---|---|--|

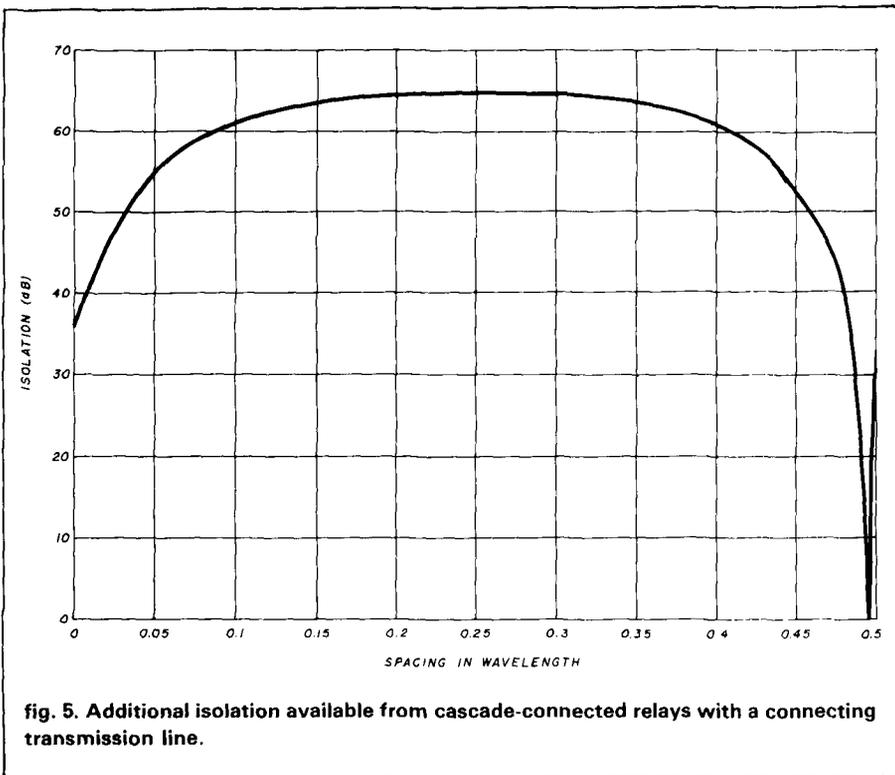


fig. 5. Additional isolation available from cascade-connected relays with a connecting transmission line.

relay is used in the transmitter as discussed in February's column.³ I've often seen complex circuitry that relies on R/C time constants and such. Timing capacitors, especially of the electrolytic type, are often unreliable and may decrease in capacitance as they age.

Figure 4B is a simple semi-foolproof way to add some time delay sequencing with the addition of only one low-cost DC relay. In this scheme, the extra relay will have to first close, which will add about 10 milliseconds delay before power is applied to the high voltage relay. When the T/R switch is opened, the high voltage relay loses power immediately and turns off.

One last caution is in order. Many modern transceivers, HF and VHF/UHF alike, can inadvertently transmit a short burst or pulse of RF either when they're first turned on or when they're switching modes. Depending on the station configuration, this could spell disaster to an inline preamplifier that is not properly protected.

input limiters

Relays are fine, but you may want

some extra built-in protection. A simple low-power limiter was described in reference 4. A low-cost hot carrier diode is placed across the base to emitter junction of the bipolar transistor as shown in fig. 6A. This type of limiter will protect only up to about 1 watt. Hot carrier diodes used as limiters should have a low junction capacitance and a low forward resistance. For example, the M/A Com MA4882 or NEC ND4981-7E are recommended. The Hewlett Packard 5082-2810 and its equivalents are not recommended since the laboratory tests I conducted showed that they have a high resistance at increased current.

Often I see back-to-back diodes indiscriminately placed across the input of a receiver. Out-of-band signals — for example, FM, TV, and broadcast — can often induce enough voltage at a receiver input to drive these diodes into conduction and cause spurious signals to appear. Point contact diodes are the most susceptible, followed by hot-carrier and then silicon types. Therefore, if you use limiter/protection diodes at a receiver input, they should be located after a band-

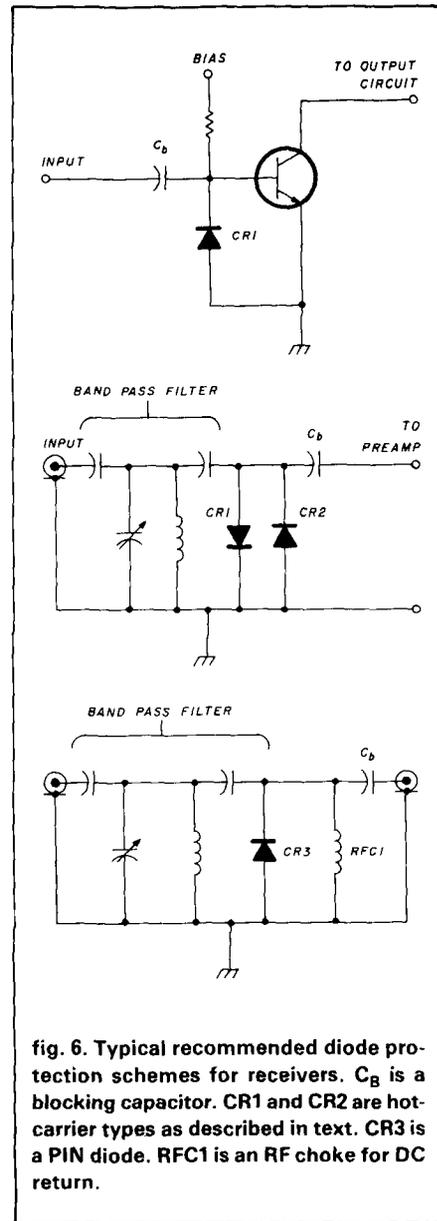


fig. 6. Typical recommended diode protection schemes for receivers. C_b is a blocking capacitor. CR1 and CR2 are hot-carrier types as described in text. CR3 is a PIN diode. RFC1 is an RF choke for DC return.

pass filter as shown in fig. 6B. Remember, hot carrier diodes can handle only up to about 1 watt of incident power.

Finally, commercial designers frequently use PIN diode limiters, especially above 500 MHz (see fig. 6C). These unique diodes turn on quickly, then drop to a very low resistance and reflect the incident RF. Most PIN diodes are able to handle much more power than hot carrier diodes. Most microwave diode suppliers manufacture these devices, but discussion of a recommended device and circuitry will have to wait for a future column.

out-of-band protection

The input protection schemes just mentioned are not always sufficient. Other RF problems can inadvertently occur from out-of-band signals. For instance, some years ago I advocated the use of an "idiot" diode in preamplifiers to prevent application of improperly polarized power supplies.⁴ Eventually I placed idiot diodes into all my preamplifiers.

No preamplifier failure has ever occurred from improper supply polarity. However, soon after installing the idiot diodes, I began experiencing random burnout, especially on my J-FET preamplifiers, which are usually quite rugged. I tried all types of input filtering, without success. This random problem continued for over a year. Finally I realized that the burnout occurrences increased during the winter, a time of low electrical storm activity and the time of year when I spend many hours DXing on the low end of 80 meters.

With the help of a digital voltmeter, a second operator, and careful measurements, I found that the 80-meter RF was coupling to my 12-volt power supply leads going into my preamplifiers. The idiot diode was rectifying the RF and adding it to the 12 volts from the supply! In one case, the actual DC at the drain of a 2-meter preamplifier was 26 volts with the 80-meter kW in operation.⁵ The reason this probably did not affect my bipolar preamplifiers was that they also had zener diode biasing, which limited the voltage across the device.⁴

The solution is simple. Place a 0.1 μF ceramic disc capacitor — remember, this is low frequency — on the DC line where it enters each preamplifier. (Larger capacitance values are not recommended because they may not act as a good RF bypass.) Any RF trying to enter the power line to the preamplifier is now bypassed and no longer seen by the idiot diode. The only failure I've experienced since that time was in a preamplifier that I forgot to bypass!

High-pass or bandpass filters are

always recommended ahead of a receiver because they prevent RF, especially at HF, from entering the input of the preamplifier.^{6,7} When selecting a filter, a capacitor input type is recommended per reference 8. Filters that use a shunt inductor at the input (such as a loop on a cavity filter) are not recommended because they usually have insufficient attenuation at lower frequencies.

low frequency and supply transients

Several types of failure modes are induced at low frequencies, especially in power supplies. One type is spikes or transients on the AC mains. Laboratory tests show that 500 to 1000 volt transients are always occurring, especially when motors or inductive devices are turned on and off. A shunt capacitor across the AC line helps, but is usually insufficient protection.

Zener diodes are often too slow to turn on and usually have limited power handling capacity. Modern protection devices such as the MOV (metal oxide varistor) were specifically designed to operate at high frequencies and clamp incoming spikes similar to the action of a back-to-back zener diode. Such devices are inexpensive (less than \$1.75) and readily available for 130 and 230-volt AC power. General Electric part No. V130LA10A or V250LA20A are suggested units for 130 and 250 volts AC, respectively. Radio Shack stocks similar MOVs. I highly recommend that you place one of these devices across the primary of all power supply transformers after the fuse as shown in **fig. 7A**.

General Semiconductor Industries, Inc. makes several products under the names TransZorb™ and ThyZorb.™ These devices, available from 5 to 700 volts, are particularly noted for their speed and power handling capability.¹⁰ They can also be used across AC lines and wherever fast-acting zener diodes are desirable.

For many years I've been preaching that you should always use a dedicated

power supply for all receiver circuits.⁶ Using a preamplifier power supply for relays is not recommended. When relays are deenergized, inductive spikes are produced — and these can easily destroy a preamplifier if it's connected to the same supply. Even if you use a separate relay supply, it's best to place a 1N4004 or equivalent diode reversely polarized across all DC relay coils, T/R relays included (unless they're AC types) as shown in **fig. 7B**.

The manner in which solid-state devices are biased can also be a failure mechanism. The use of three terminal voltage regulators with protection diodes is highly recommended.⁹ I strongly suggest the addition of a limiting resistor, however small (20 to 100 ohms is suggested), in series with each solid-state device to lower dissipation in case of runaway biasing. As another precaution, place a zener diode a few volts above the power supply voltage after the resistor. It will also serve as an idiot diode since most zeners have less than 1.0 volt drop when biased opposite to convention. *These schemes are shown in fig. 7C.*

AC line filters

Brute-force line filters are also recommended, especially to prevent damage from large surges typical of lightning strikes. A 50 to 100 μH inductor should be placed in series with the AC line where it comes into the ham shack and followed by an MOV or TransZorb™ of the appropriate rating as shown in **fig. 7D**. Note that the inductor must have an air core. Ferrite cores or rods will saturate and become ineffective if a large surge voltage should be induced onto the AC lines by a lightning strike.

the forces of nature

So far we've been talking mainly about protection against common man-made causes of burnout. But natural forces, in the form of static electricity or lightning, can be extremely destructive. Although statisticians assure me that even in the worst lightning-prone areas such as central

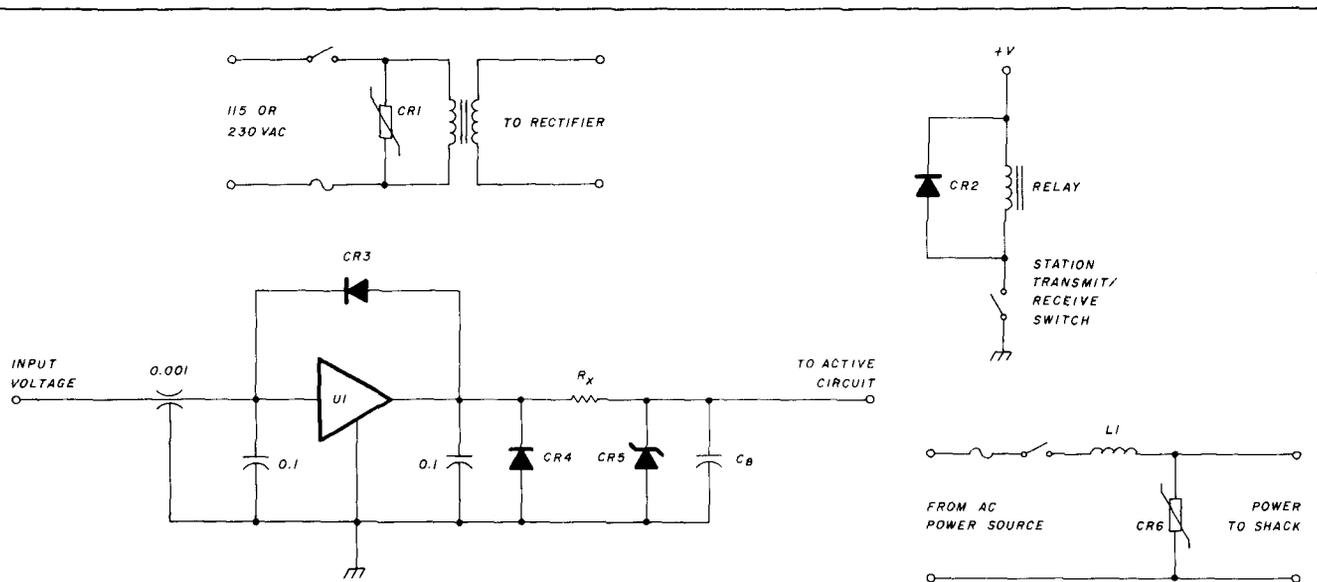


fig. 7. Recommended power supply protection schemes. C_B is a blocking capacitor. CR1 and CR6 are MOV type protection diodes. CR2, 3 and 4 are 1N4004 or equivalent (see text) and CR5 is a zener diode approximately 2 volts above the operating voltage of the circuit. R_x is typically 20 to 100 ohms (see text). L1 is a 50 to 100 μ H RF choke made from 120 to 170 turns of No. 18 AWG or larger (depends on current to be drawn) enamel coated wire spaced wire diameter on a 1-inch (2.54 cm) diameter wooden dowel.

Florida, lightning strikes the same place only once every 10 years, *don't trust your luck*. My station has been hit more than once; the worst strike occurred in the Santa Clara Valley in California, a normally low probability area.

Because lightning protection has often been discussed in Amateur publications,¹⁰ I will highlight only those problems that most affect VHF/UHFers. Experts tell me that when lightning strikes within 1000 feet (300-meters) of your equipment, damage will result. Even a 1-mile (1.6 km) separation from a lightning strike can result in damage caused by line voltage surges. Many simple techniques can be used to lessen or prevent lightning destruction to Amateur equipment; while some have been amply discussed in the literature, others have not, and I want to share them with you.

proper grounding is important

First, all antenna feeds should have a built-in ground return. This can often

be incorporated as part of the feed system: for example, a "T" match or the balun connected to a metal boom or mast. The voltage breakdown of air at sea level with low humidity and room temperature between two flat surfaces is approximately 70 to 75 kilovolts per inch (28 to 30 kV/cm). A needle point, on the other hand, will break down at about 26 to 30 kV per inch (10-12 kV/cm). Therefore, a "Blitzbug"TM type of lightning arrester installed in each transmission line will add an additional safety factor. Since this type of device has a point spacing of about 0.02 inch (0.05 mm), it should fire at 500 to 700 volts and handle reasonable follow-on current. The most common type of BlitzbugTM available is fitted with UHF connectors, but usable, with low VSWR, to about 450 MHz.

SVPs (surge voltage protectors) are becoming very popular. Basically they consist of a pair of electrodes properly spaced and hermetically sealed in a rare gas field. Breakdown voltages of 70 volts and up with low shunt capacitance (0.5 to 2 pF) are now available. Several manufacturers offer them for

insertion in transmission lines. Remember that SVPs, while fairly quick to turn on, will not prevent damage from the large or sustained current typical of a direct hit as effectively as the Blitzbug.TM

For best lightning protection it may be best to install both types of devices in cascade in your feedlines and spaced about one-tenth wavelength apart such as discussed in the relay section of this column. *In all cases, each of these devices should have a separate low-impedance ground return (see below).*

towers

Towers should never be higher than necessary. The highest object in a given local area, after all, is especially vulnerable to lightning strikes. Each time the height of a tower is doubled, the chance of its experiencing a direct hit increases by a factor of 4!

In the "good old days" lightning rods were installed on the rooftops of homes and tall buildings. I always thought they were meant to provide a discharge path, but some of my old-

NAMPA SATELLITE SYSTEMS, INC.

TWO LOCATIONS



MD9 - 9' Dish

312 12th Ave. So.
Nampa, Idaho 83651
(208) 466-6727

1-800-654-0795

For Service ONLY (208) 467-3204

6103 W. 34th St.
Houston, Texas 77092
(713) 957-5140

NEW LOW, LOW PRICES!

NATIONAL FINANCING AVAILABLE THROUGH NAMPA SATELLITE
FOR MORE INFORMATION CALL 208-466-6727

ALL SYSTEMS FREIGHT PRE-PAID FROM NAMPA, IDAHO OR HOUSTON, TEXAS

EACH OF THE FOLLOWING SYSTEMS CONSIST OF: Receiver, 100° LNA, LNB, or LNC, Wilson MD-9 Dish, 100 Ft. Cable Pack, LNA Cover, Polarmatic I Feedhorn, NSS Dish Drive, All Connectors and Instructions

| | | | |
|---|---------------|---|---------------|
| Wilson YM1000 System 10% Down Payment-\$164.80 36 payments of \$54.00/mo. | \$1648 | Uniden UST 3000 System 10% Down Payment-\$177.20 36 payments of \$57.00/mo. | \$1772 |
| Wilson YM400 System 10% Down Payment-\$144.20 36 payments of \$46.00/mo. | \$1442 | Uniden UST 1000 System 10% Down Payment-\$157.10 36 payments of \$52.00/mo. | \$1571 |
| Little Wil LW5 10% Down Payment-\$109.90 36 payments of \$36.00/mo. | \$1099 | Sigma Mark 2A 10% Down Payment-\$143.80 36 payments of \$46.00/mo. | \$1438 |
| Little Wil RV5 10% Down Payment-\$139.90 36 payments of \$45.00/mo. | \$1399 | Sigma Mark 3 BLOCK DC 10% Down Payment-\$166.20 36 payments of \$54.00/mo. | \$1662 |
| Drake 240 A + APS24 10% Down Payment-\$199.50 36 payments of \$65.00/mo. | \$1995 | Sigma Mark 5 BLOCK DC 10% Down Payment-\$204.90 36 payments of \$66.00/mo. | \$2049 |
| Luxor Mark 2 System BLOCK DC 10% Down Payment-\$251.20 36 payments of \$75.00/mo. | \$2512 | M/A Com HI BLOCK DC 10% Down Payment-\$228.20 36 payments of \$74.00/mo. | \$2282 |
| Dexcel 1300-01 System 10% Down Payment-\$198.80 36 payments of \$63.00/mo. | \$1988 | M/A Com TI BLOCK DC 10% Down Payment-\$218.20 36 payments of \$71.00/mo. | \$2182 |
| Dexcel 1200-01 System 10% Down Payment-\$163.30 36 payments of \$54.00/mo. | \$1633 | STS MBS-SR-AA 10% Down Payment-\$234.90 36 payments of \$76.00/mo. | \$2349 |

OPTIONS WITH SYSTEM

| | |
|---------------------------------|-------|
| PM 9' Dish | \$ 60 |
| UM 10' Mesh Dish | \$180 |
| Prodelin 10' Dish | \$400 |
| Continental Mesh Dish 10' | \$400 |
| 85° LNA | \$ 80 |

| | |
|----------------------------|-------|
| NSS Memory Tracker | \$100 |
| MTI 2100 | \$225 |
| MTI 4100 | \$345 |
| Houston Tracker IV | \$325 |
| Houston Tracker IV + | \$425 |

timer friends tell me that they may in fact work in the opposite way, emitting electrons and thereby repelling or at least decreasing the probability of a direct strike! In this regard, the same experts tell me that a blunt or ball-shaped object would be a better way to ground a strike. I don't know which is correct. Maybe someone reading this column can enlighten us.

Regardless of the outcome of this question, all towers and antennas should be well grounded for lightning protection. A single ground rod is not sufficient. Two ground rods may be even less effective than expected because when they're positioned close together electrically, they couple to each other. Therefore, I recommend at least two ground rods spaced 10 to 15 feet (3 to 5 meters) apart, close to the base of a tower but at least 2 feet (60 cm) from any concrete used in the installation.

All ground rods should be at least 5 to 8 feet (1.5 to 2.5 meters) long, with a minimum diameter of 5/8 inch (16 mm). Always use high quality, well plated grounding rods (available from most electrical supply houses). Small low-cost ground rods often rust and become poor grounds after the first or second rain storm!

Grounding rods should be connected to the tower with a heavy (No. 6 AWG or larger) solid copper wire. This wire should be kept as straight as possible so that it forms a low impedance path for lightning (as just discussed). Keep all bends to a minimum. Also keep ground return wires away from other wires or cables to minimize any coupling effects.

A strong bonding connection should be made where the grounding wire connects to the tower and the rod. The inductance of the wire and its ability to handle the peak current of a direct lightning strike are very important. [I had a single aluminum 1/8 inch (3 mm) diameter ground wire that exploded open when hit by lightning. You should have seen the damage in the shack as the strike found other discharge paths!]

Lightning usually travels in a straight

line. Therefore, whenever possible, bring all transmission lines away from your tower at right angles and in a reverse direction as shown in fig. 8A. This will cause any lightning to go directly to ground rather than down the transmission line, since the bend will act as a high impedance. In addition, you can loosely coil up to 3 to 5 turns of your feedline in a 4 to 8 inch (10 to 20 cm) diameter, depending upon the minimum bending radius, to act as an RF choke (see fig. 8B).

Remember that a direct hit can cause an extremely large current (20 to 100,000 amperes!) to flow. Enclosing all transmission lines within an iron water pipe or tube (such as EMT) that is just a bit larger than the diameter of the line will considerably diminish the induced current. This is because of the limiting of the magnetic field by the steel (ferromagnetic material) tubing as shown in fig. 8C. The preferred method is to use 20 feet (6 meters) of tubing for each line, but even a single 5-foot (1.5 meter) tube will help. If several shorter tubes are used, they need not be grounded or connected together. For economy's sake, several transmission lines can be placed inside a single tube. If this method is used and the tower is well grounded, the lightning will take the lowest impedance path — directly to the ground rods instead of through the ham shack!

When connecting transmission lines to a piece of gear, especially when rack mounted, bring the cables vertically from the floor level. Connect a suitable outside ground (such as the one just suggested for towers) to each shield at the floor level and at the base of the cabinet. This prevents the lightning from climbing vertically into the equipment.

lightning, static and RF

While a direct hit is hard to prevent and even more difficult to divert entirely, these suggestions will at least limit damage and perhaps prevent it entirely. Other measures can also help.

One of the best methods to protect equipment is to use a bandpass filter

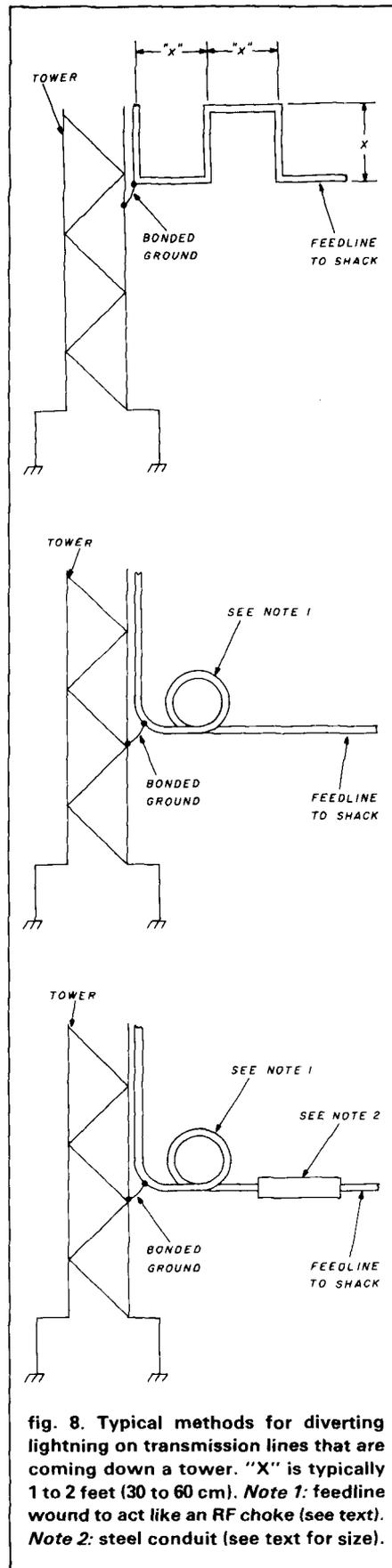


fig. 8. Typical methods for diverting lightning on transmission lines that are coming down a tower. "X" is typically 1 to 2 feet (30 to 60 cm). Note 1: feedline wound to act like an RF choke (see text). Note 2: steel conduit (see text for size).

J.I.L. SX-400

Uninterrupted
Frequency
Coverage
100 kHz to 1400 MHz
with Optional Converters



- A professionally created scanner for the serious listener
- Wide frequency coverage 26 to 520 MHz (with optional converters 100 kHz to 1400 MHz)
- Continuous coverage. You'll hear everything.
- Birdie-Free, no internal 'signals' to interfere with scanning
- 20 Channel memory, AM-FM Mode memory, Priority memory
- Carrier Operated Relay (COR) permits automatic start/stop of a recorder
- Four low-noise front end converters for optimum performance
- 12 Volt DC operation (120 Volt AC power supply optional)
- Check JIL's ad in this issue for further details

Sale Price \$549.95 List \$739.90

P-1A Power Supply \$34.95

Other options call

✓ 169



Electronic Equipment Bank

516 Mill Street
Vienna, Virginia 22180

800-368-3270
(703) 938-3350

CB-10 FM SPECIAL



- Hy Gain 40-Channel Board
- 40-Channel Switch
- Volume & Squelch Control
- FM Detector Module
- Full Instructions Included

\$14.95 Add \$2.00 *BOARD ONLY*
shipping & handling \$6.95

QRP TRANSCEIVER SET — \$34.95

VHF CONVERTER SET — \$24.95

Add \$2.00 For Shipping & Handling — Send For FREE Brochure

SEND \$2.00 FOR FULL MANUAL WITH CIRCUIT DIAGRAMS

MANY OTHER MODULES AVAILABLE

MORNING DISTRIBUTING CO.

P.O. BOX 717, HIALEAH, FLA. 33011

(305) 884-8686

✓ 170

WHAT'S REALLY HAPPENING IN HOME SATELLITE TV?

STVSM SATELLITE TELEVISION MAGAZINE

A monthly of 100-plus pages, has all you need to know about where to find equipment, how it performs, how to install it, legal viewpoint, & industry insights.

- \$24.95 per yr. (12 monthly issues)
- \$ 2.00 for Sample Issue

MONEY BACK GUARANTEE if not satisfied (subscription orders only). Keep first issue with our compliments.

If you already have a dish, then you need

OnSatSM

—the best in satellite TV programming.

- ★ Weekly Updated Listings
- ★ All Scheduled Channels
- ★ Complete Movie Listing
- ★ All Sports Specials
- ★ Prime Time Highlights

- \$39.00 per yr. (52 weekly issues)
- \$ 1.00 for Sample Copy

Visa® MasterCard® accepted (subscription orders only). All prices in US funds only. Write for foreign rates.

Send this ad along with your order to:

STVSM/OnSatSM

P.O. Box 2384 - Dept. PS
Shelby, NC 28151-2384

Subscription calls only
Toll Free 1-800-438-2020

✓ 171

HR

(as described above). This is suggested because lightning is primarily a low-frequency phenomenon — i.e., below 30 MHz. A high-pass or band-pass filter (see fig. 9A with a high attenuation at lower frequencies) will significantly decrease the energy entering a receiver. Unfortunately, this may not always be possible for those operating on the HF bands!

Likewise, keep all coupling capacitors at a minimum. A capacitance reactance of 2 to 5 ohms at the frequency of operation should be used. This would suggest the use of no more than 200 pF at 70 cm. When low noise transistors first became available for 70 cm operation, many preamplifiers were accidentally destroyed when connected to automatic noise figure meters that used a gas tube noise generator. This failure was caused by large coupling capacitors that responded to the low frequency transient emitted by the firing of the gas tube. When low value capacitors were used, the problems diminished considerably. Fortunately, modern automatic noise figure generators use solid-state diodes that don't have this problem.

The placing of a 5 to 10 kilohm resistor across your receiver inputs as shown in fig. 9B will also help, especially in elimination of static.⁹ It's standard practice in the CATV industry to place 510,000-ohm resistors in shunt with drop cables (the ones that go to your home), presumably to bleed off any charge buildup.

Another technique is the use of a shorted quarter-wave stub. A coaxial "T" connector is placed in the transmission line and the stub is connected and grounded as shown in fig. 9C. This stub is a high impedance at the frequency of use. Therefore it has low loss, but is a DC short for any static or lightning.

physical handling

We may do all of the foregoing without paying attention to some of the basics such as using extreme care in handling and connecting equipment. All power supplies should be measured for proper voltages and

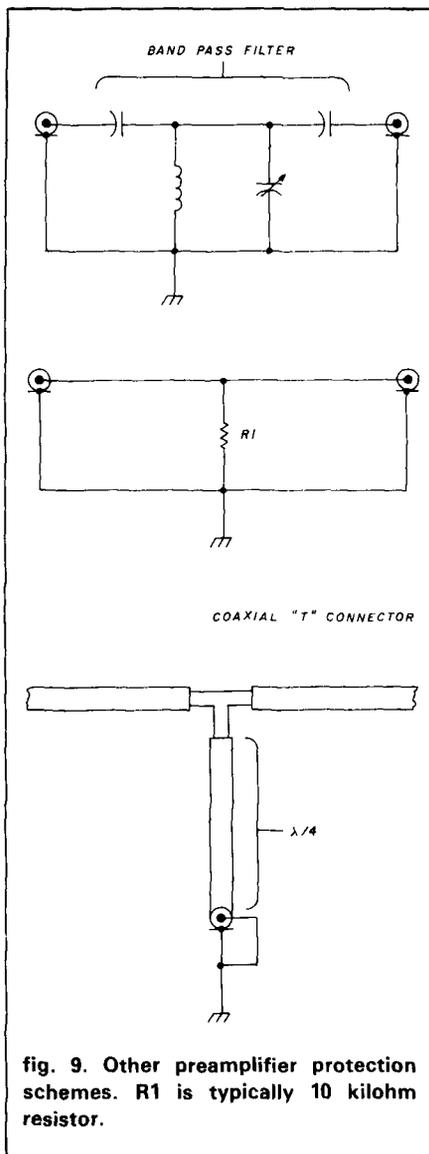


fig. 9. Other preamplifier protection schemes. R1 is typically 10 kilohm resistor.

should preferably be in operation when they are connected to the equipment. Some HF transceivers have external power supplies that put out high peak voltages when first turned on. Manufacturers recommend that the power supply should be turned on before the transceiver; this procedure should be reversed when ceasing operation. It is also recommended that whenever you connect a power supply, the ground return should be connected first. If not, the return current may flow through any coax cables back to the power supply and induce a spike or spark into the amplifiers. Transmission lines sometimes store a charge. Therefore, always discharge both sides of

any incoming transmission lines to chassis ground before connecting them to the input of a receiver.

components

Component abuse or overstressing is one of the biggest problems faced by Radio Amateurs. Many of the failures I hear about are not induced by lightning or by RF, but rather by the user who is trying to milk the last bit of performance from a device. *Solid state devices, especially those of the low-noise type, should never be operated at voltages, currents, or power dissipation levels beyond the manufacturer's specifications!* The importance of using protective diodes and zener diodes as well as current limiting resistors, as discussed above, cannot be overstressed. Likewise, all resistors should be sufficiently derated in power.

Capacitors, especially on a receiver input, should have adequate breakdown voltages. I've noticed that the CATV industry uses 1000 volts or higher breakdown voltages on all their capacitors on the input and output circuits. Surely they know something about lightning — they have thousands of miles of transmission lines all over the world!

summary

In this month's column, I have described many of the types of failure mechanisms that can plague an active VHF/UHF Amateur. They range from carelessness and unwise short-cuts to events beyond our control. This column is not meant to alarm you; in fact, the opposite is true. If you understand the limitations of your equipment and the outside stresses and forces that can be placed upon them, you can take adequate protective measures using some or all of the techniques mentioned in this column. Taking short-cuts on grounding, filtering, and switching is "penny-wise and pound foolish."

One final remark: some of the protection devices described may be destroyed if you're unfortunate enough to suffer a failure or lightning strike.

NEMAL ELECTRONICS INTL., INC.

SEE US AT DAYTON BOOTH #104

your one stop coax supplier!




Exclusive

SATELLITE CONTROL CABLE

5 TYPES AVAILABLE!

NEW!!! Lowest Loss

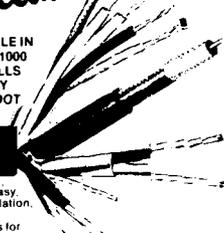AVAILABLE IN
250,500-1000
FT. ROLLS
OR BY
THE FOOT



Designed for easy
one-step installation,
providing the
required cables for
most earth station
equipment
all in a direct
burial jacket

| TYPE 1 (General Purpose) | TYPE 2 (Mini) | TYPE 3 (Universal) | TYPE 4 | TYPE 5 |
|--|--|--|--|--|
| 1 RG59/U 96% Copper Braid | 1 RG59/U 96% Copper Braid | 2 RG59/U 96% Copper Braid | 1 - RG6/U 18 Gauge 96% Copper Shield | 2 - RG6/U 18 Gauge 96% Copper Shield |
| 2 @ 16 Gauge | 2 @ 12 Gauge |
| 5 @ 22 Gauge | 3 @ 18 Gauge | 6 @ 18 Gauge | 3 @ 18 Gauge | 3 @ 18 Gauge |
| 3 @ 20 Gauge Shielded plus Tinned Copper Drain Wire | 3 @ 20 Gauge Shielded plus Tinned Copper Drain Wire | 3 @ 22 Gauge Shielded plus Tinned Copper Drain Wire | 3 @ 20 Gauge Shielded plus Tinned Copper Drain Wire | 3 @ 20 Gauge Shielded plus Tinned Copper Drain Wire |
| 55¢ FT | 75¢ FT | 95¢ FT | 79¢ FT | 89¢ FT |

Only Nemal offers the quality construction RG59/U copper shielding made to mil spec JAN C-17, 12 gauge conductors, tinned copper drain wires, and a true direct burial polyethylene jacket

HARDLINE

Two styles, two sizes for all installation needs

- Aluminum Outer Conductor with Polyethylene Jacket**
 - 1/2 inch loss .48 dB/100 ft. @ 30 MHz
 - 3.68 dB/100 ft. @ 1000 MHz\$1.25/ft.
 - 7/8 inch loss .28 dB/100 ft. @ 30 MHz
 - 2.54 dB/100 ft. @ 1000 MHz\$3.25/ft.
 - Corrugated Copper Outer Conductor with Polyethylene Jacket**
 - 1/2 inch loss .38 dB/100 ft. @ 30 MHz (FLC12-50J) 2.78 dB/100 ft. @ 1000 MHz\$1.59/ft.
 - 7/8 inch loss .13 dB/100 ft. @ 30 MHz (FLC12-78J) 1.3 dB/100 ft. @ 1000 MHz\$3.92/ft.
- COMPARE RG 213 1.25 dB/100 @ 30 MHz
8.5 dB/100 @ 1000 MHz!

HARDLINE CONNECTORS

- 1/2 inch aluminum UHF M/F \$19.00 Type N M/F \$22.00
- 7/8 inch aluminum UHF M/F \$49.00 Type N M/F \$49.00
- 1/2 inch copper UHF M/F \$22.00 Type N M/F \$22.00
- 7/8 inch copper UHF M/F \$49.00 Type N M/F \$49.00

shipping

Cable — \$6.00 per 100 ft.
Connectors — \$3.00 per order.
Orders under \$20 add \$2 additional plus shipping.
Charge card — orders over \$30 only.
COD add \$2.00. Florida Residents add 5%.

FACTORY AUTHORIZED DISTRIBUTOR
AMPHENOL, CABLEWAVE, COLUMBIA, KINGS
BLONDER-TONGUE, TYTON, B&K

- COAXIAL CABLE
- MULTICONDUCTOR CABLE
- CONNECTOR-ADAPTERS
- HARDLINE
- CABLE TIES
- SMATV PRODUCTS
- COAX-SEAL
- COMPUTER CABLE
- CRIMP TOOLS
- FIELD STRENGTH METER

COAXIAL CABLE SALE POLYETHYLENE DIELECTRIC

- RG-8/U 96% shield Mil Spec. (\$29.00/100) or 31¢/ft.
- RG11U 96% shield 75 ohm mil spec.25¢/ft.
- RG-58/U double shield (RG-58 size) 50 ohm45¢/ft.
- RG58U mil spec 96% shield(\$10.00/100) or 11¢/ft.
- RG62A/U 96% shield mil spec 93 ohm12¢/ft.
- RG174/U min 50 ohm mil spec.10¢/ft.
- RG213 noncontaminating 96% shield mil spec36¢/ft.
- RG214/U double silver shield 50 ohm\$1.65/ft.
- RG214/U tinned copper65¢/ft.
- RG217/U double shield 50oh 5/8" OD85¢/ft.

LOW LOSS FOAM DIELECTRIC

- RG-8X (Mini 8) 95% shield(\$15.00/100) or 17¢/ft.
 - RG8U 80% shield(\$19.00/100) or 22¢/ft.
 - RG-8/U 97% shield 11 gu. (eq. Belden 8214)31¢/ft.
 - RG58U 80% shield07¢/ft.
 - RG58U 95% shield10¢/ft.
 - RG59/U 100% foil shield TV type10¢/ft.
 - RG59/U 70% copper shield09¢/ft.
 - HEAVY DUTY ROTOR CABLE 2-16 ga 6-20 ga36¢/ft.
 - Rotor cable 2-18 ga 6-22 ga Poly burial Jkt.19¢/ft.
- Complete line of multiconductor cables available

CONNECTORS MADE IN USA

- Amphenol PL 25989¢
- PL-259 and/or SO-23965¢ ea. or 10/\$5.99
- Double Male Connector\$1.79
- PL-258 Double Female Connector98¢
- PL-259 Silver-Teflon Kings\$1.59 ea.
- Reducer UG-175 or 17622¢ or 10/\$2.00
- UG-255 (PL-259 to BNC)\$2.95
- Elbow (M359) UHF Elbow\$1.79
- F59A (TV type)24¢ or 10/\$2.00
- UG 21 D/U Type N Male for RG8, Amphenol\$3.00
- UG-88C/U BNC Male for RG-58, Amphenol\$1.25
- UG 273 BNC-PL259 Amphenol\$3.00
- 3/16 inch Mike Plug for Collins etc. (cutoff)\$1.25

shipping

Cable — \$3.00 per 100 ft.
Connectors — add 10%, \$3.00 minimum.
Orders under \$20 add \$2 additional plus shipping.
Charge card — orders over \$30 only.
COD add \$2.00. Florida Residents add 5%.



12240 N.E. 14th Ave.
No. Miami, FL 33161
Telephone: (305) 893-3924

IN STOCK
— OVER 500 ITEMS —
COMPLETE LINES

✓ 172

ALL BAND "SLOPER" TRAP ANTENNAS!

PRE-TUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS - LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANS-MITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. INPUT FOR NOVICE AND ALL CLASS AMATEURS! IMPROVED DESIGN!

COMPLETE with 50 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 15 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof resonant traps "XG" - you just switch to band desired for excellent worldwide operation - trans-mitting and receiving!

- No. 10B0S - 80-40-20-15-10 - 1 trap 49 ft. ---- \$49.95
- No. 10A0S - 40-20-15-10 - 1 trap 26 ft. ---- \$48.95
- No. 10Z0S - 20-15-10 - 1 trap 13 ft. ---- \$47.95

SEND FULL PRICE FOR POSTPAID INSURED DEL. IN USA. (Canada is \$10.00 extra for postage - clerical - customs etc.) or order using VISA - MASTER CARD - AMEX. EXPRESS. Give number and exp. date. PH 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFORMATION AVAILABLE ONLY FROM WESTERN ELECTRONICS Dept. AH-6

✓ 173 Kearney, Nebraska, 68847

However, the cost of replacing these devices is usually far less than the cost of replacing the equipment they protect! Remember, it's virtually impossible to protect yourself from a direct lightning hit but it is possible to minimize the destruction.

acknowledgements

I'd like to thank Leroy May, W5HN, a great old-time VHF/UHFer, who, by his letter to me several years ago, encouraged me to write on this subject.

references

1. Joe Reisert, W1JR, "Requirements and Recommendations for 70-cm EME," *ham radio*, June, 1982, page 12.
2. Robert V. Garver, *Microwave Diode Control Devices*, Artech House Inc., 1976.
3. Joe Reisert, W1JR, "VHF/UHF World: High Power Amplifiers, Part 2," *ham radio*, February, 1985, page 38.
4. Joseph H. Reisert, Jr., W1JR, "Ultra Low-Noise UHF Preamplifier," *ham radio*, March, 1975, page 8.
5. Joe Reisert, W1JR, "VHF/UHF Preamp Burn-out," *ham radio*, November, 1978, page 43.
6. Joe Reisert, W1JR, "What's Wrong With Amateur VHF/UHF Receivers — and What We Can Do to Improve Them," *ham radio*, March, 1976, page 44.
7. Joe Reisert, W1JR, "VHF/UHF World: High Dynamic Range Receivers," *ham radio*, November, 1984, page 97.
8. Joe Reisert, W1JR, "VHF/UHF World: The VHF/UHF Primer: An Introduction to Filters," *ham radio*, August, 1984, page 112.
9. Joe Reisert, W1JR, "VHF/UHF World: Low-Noise GaAs FET Technology," *ham radio*, December, 1984, page 99.
10. Bradley Wells, KR7L, "Lightning and Electrical Transient Protection," *ham radio*, December, 1983, page 73.

important VHF/UHF events:

- June 1: EME Perigee
- June 5: Predicted peak of the Arietids meteor shower (1930 UTC)
- June 8-9: ARRL VHF QSO Party
- June 15: Predicted peak of the June Lyrids meteor shower (0400 UTC)
- June 21: Mean date for the two month annual peak of sporadic-E propagation
- June 29: EME Perigee
- June 29-30: SMIRK 6-meter Contest
- July 20: ± two weeks, look for 2-meter sporadic E openings
- July 20-21: CQ VHF WPX Contest
- July 25: EME Perigee
- July 27-29: Central States VHF Conference, Tulsa, Oklahoma (Contact W0RRY/5)
- July 28: Predicted peak of Delta Aquarids meteor shower (0300 UTC)

ham radio

TOWERS

by ALUMA

HIGHEST QUALITY ALUMINUM

- TELESOPING (CRANK-UP)
- GUYED (STACK-UP)
- TILT-OVER MODELS

Easy to install. Low Prices. Crank-ups to 100 ft.

EXCELLENT FOR AMATEUR COMMUNICATIONS



Mobile Trailer Type



Mobile Truck Type

Over 36 types aluminum and steel towers made—specials designed and made—write for details

SPECIAL Four Section 50 Ft. Van Mounted Crank-Up Aluma Tower



Fixed Base

ALUMA TOWER CO.

BOX 2806HR
VERO BEACH, FLA. 32960-2806
(305) 567-3423 TELEX 80-3405

174

DESIGN EVOLUTION IN RF P.A.'s

Now with GaAs FET Preamp



| MODEL | FREQUENCY 2 | OUTPUT POWER | INPUT POWER | PRE-AMP |
|-------|-------------|--------------|-------------|---------|
| | (MHz) | (W) | (W) | NF GAIN |
| 0508 | 50-54 | 170 | 1 | - |
| 0508G | 50-54 | 170 | 1 | 6 15 |
| 0510 | 50-54 | 170 | 10 | - |
| 0510G | 50-54 | 170 | 10 | 6 15 |
| 1410 | 144-148 | 160 | 10 | - |
| 1410G | 144-148 | 160 | 10 | 6 15 |
| 1412 | 144-148 | 160 | 30 | - |
| 1412G | 144-148 | 160 | 30 | 6 15 |
| 2210 | 220-225 | 130 | 10 | - |
| 2210G | 220-225 | 130 | 10 | 7 12 |
| 2212 | 220-225 | 130 | 30 | - |
| 2212G | 220-225 | 130 | 30 | 7 12 |
| 4410 | 420-450 | 100 | 10 | - |
| 4410G | 420-450 | 100 | 10 | 1.1 12 |
| 4412 | 420-450 | 100 | 30 | - |
| 4412G | 420-450 | 100 | 30 | 1.1 12 |

- Linear (all mode) RF power amp with automatic T/R switching (adjustable delay). Amplifier useable with drive powers as low as 1/2 watt.
- Receive preamp option, featuring GaAs FETS (lowest noise figure, better IMD). Device NF typically .5 dB.
- Thermal shutdown protection incorporated
- Remote control capability built-in
- Rugged components and construction provide for superior product quality and performance
- All models include a complete operating/service manual and carry a factory warranty on all components
- Designed to ICAS ratings, meets FCC part 97 regulations
- Approximate size is 2.8 x 5.8 x 10.5" and weight is 5 lbs.

1. Models with G suffix have GaAs FET preamps. Non-G suffix units have no preamp.
2. Covers full amateur band. Specify 10 MHz Bandwidth for 420-450 MHz Amplifier.

★SEND FOR FURTHER INFORMATION★

TE SYSTEMS

TE SYSTEMS
P.O. Box 25845
Los Angeles, CA 90025
(213) 478-0591

Specifications/price subject to change

175

This publication is available in microform from University Microfilms International.



Please send information about these titles:

Name _____

Company/Institution _____

Address _____

City _____

State _____ Zip _____

Phone (____) _____

Call toll-free 800-521-3044. In Michigan, Alaska and Hawaii call collect 313-761-4700. Or mail inquiry to: University Microfilms International, 300 North Zeeb Road, Ann Arbor, MI 48106.

Call Us LAST!

We just might beat those other "unbeatable" deals

Talk with everyone else. Then call us. We carry all the top names in amateur equipment.



Hours: Tuesday-Saturday, 10 am-6 pm. Closed Mondays.


800/845-6183
803/366-7157 Inside SC

THE NEW!



GISMO
1039 Latham Drive
Rock Hill, SC 29730

187

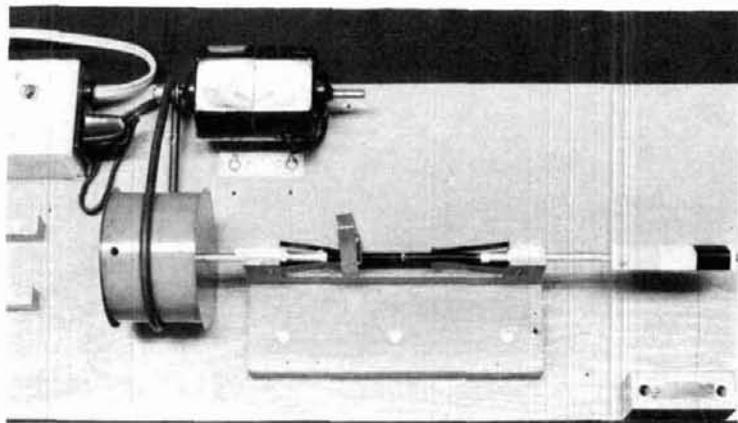

Overall view of the coil winder set up to wind No. 30 enameled wire on a form approximately 0.8 inch (20 mm) \times 0.43 inch (11 mm) \times 2 inches (51 mm) long. About half of the winding length has been filled and the clothespin is clamped on the screw thread that causes the main shaft to traverse from left to right; the winding progresses from right to left. The mini-box at upper left is an SCR motor controller, and the two wood blocks at left are for later addition of a turns counter as explained in the text.

wind your own transformers — inexpensively

Novel approach
produces high quality,
low-cost replacements

I've seen many excellent articles on rewinding transformers in the home workshop. Valuable information for calculating the number of turns per volt relating to core size, insulation, varnish dipping, and space available was included, but in each of these articles it always seemed that in order to complete the project, it was necessary to somehow hold the coil in one hand and the wire in the other and just wind away. Many authors noted, of course, that the methods were really not suited to coils with a large number of turns of small wire, but were ideal for the larger sizes of wire, such as might be found powering the lower voltage transistor circuits popular in recent years.

This article describes a home-brew coil winding machine that will wind wire uniformly and neatly. It can be built from readily available, inexpensive parts. Most of the parts can be found right at home; the rest are available at reasonable prices. The only equipment necessary is a small drill press, a table saw, and the

usual hand tools found around the hamshack. A 3 to 4 inch-circle cutter attachment for the drill press will save a lot of time.

background

Several years ago, when I experimented briefly with Amateur Television, I acquired a 12-year-old television camera with a bad power transformer. At first I thought it would be a simple matter to order a replacement transformer, but my enthusiasm faded when the manufacturer told me they'd stopped stocking parts years ago. My interest diminished even more when I learned that a professionally rebuilt replacement that would fit in the available space and meet the electrical requirements would cost \$200.00.

My conscience wouldn't allow me to junk a perfectly good TV camera, and there was no way I'd spend more for a transformer than I'd invested in the whole camera. For years I'd toyed with the idea of a home-brewed coil winder; it seemed its time had finally come.

how it works

Small transformers are wound on a fairly complicated piece of machinery that rotates the form, or

By C.F. Hooper, W4GDW, 1457 Young Avenue, Clearwater, Florida 33516

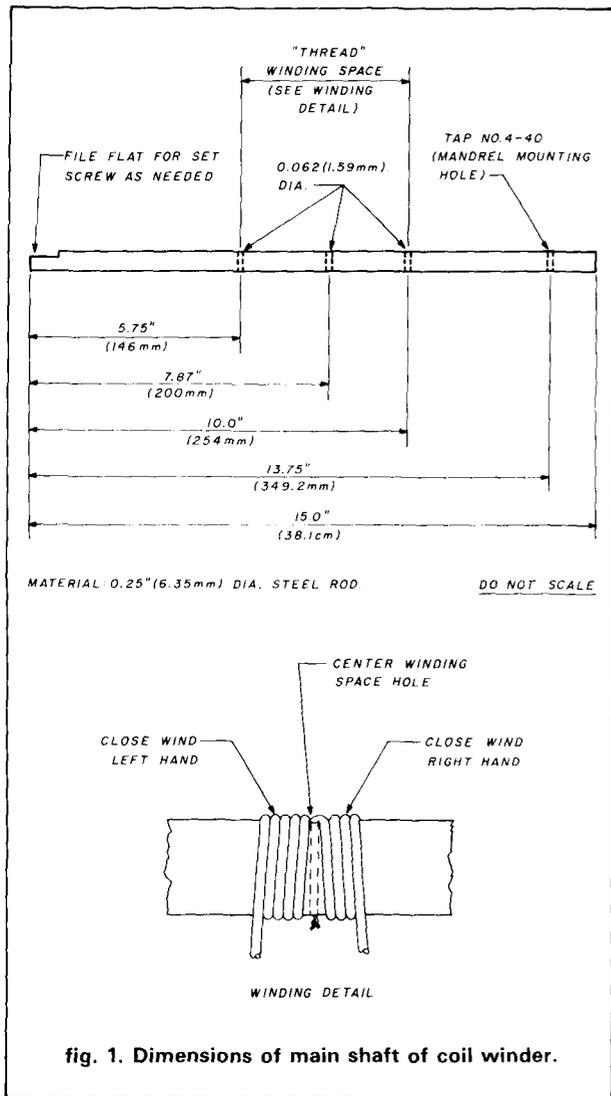


fig. 1. Dimensions of main shaft of coil winder.

mandrel, on which the wire is being wound. While the form makes one revolution, the feed guide moves the same distance as the diameter of the wire (plus perhaps a fraction of that distance for clearance). Such a winding lathe has a large selection of gears available so that the lead screw is turned at just the right rate to accomplish this motion. A transformer winding machine costs thousands of dollars — and the average ham obviously doesn't wind coils often enough to justify that expense.

It would be fairly easy for an Amateur to assemble a device that would merely rotate the coil form, but the mechanism necessary to move the wire guide at precisely the proper rate — unless you already have a lathe with many gears — gets much too complicated for a homebrew project.

In searching for ways to solve the problem inexpensively, it occurred to me that the shaft on which the coil form was mounted could do the lengthwise moving, while the wire feed point remained stationary.


As I began to think about having lead screws made for each size of wire and the many other details, I realized I could use the wire itself for the lead screw! Normally you'd have a little bit of the size wire you were going to wind left over. So why not form the lead screw threads right on the shaft by simply winding on a single layer of wire for each direction of feed, securing it in place if necessary? It's fairly easy to close wind on a round rod, even with small wire; besides, you do it only once for each size of wire you're going to wind.

The shaft is made to move lengthwise while rotating by mounting a pair of pads of resilient material on strips of metal fastened to the bearing posts, close to the shaft but not touching, on either side. When feeding is desired, a clothespin is used to clip over the pads to bring them in contact with the "threads." There are two sets of these pads, one for each direction of feed, so when ready to reverse wire feed, you simply stop the rotation and move the clothespin to the other pair of pressure pads, insert and wrap the paper insulation layer over the layer just wound (securing it temporarily with masking tape if needed), and then restart winding with feed in the other direction. I designed my winder around 0.25-inch (6.35 mm) steel rod, and to accommodate an actual winding length of 1.8 inch (46 mm), which means that a 2-inch (51 mm) long winding form can be handled with a little space at each end. I wanted to have a winding shaft for each wire size to be used to save for use again with that particular size. This means, of course, that when you've finished winding one wire size, you remove the drive pulley and the winding form, mount them on another rod made up for the next wire size, and re-install the unit into the bearings. The "bearings" are simply wood posts with a slot sawed into the top in which the winding shaft lies, leaving it free to slide lengthwise as well as to rotate.

The shaft is powered by an old sewing machine motor (complete with pulley, if possible) made to be variable in speed by the inclusion of an SCR speed controller built from a diagram in the General Electric Company SCR manual.¹ Similar circuits can be found in the handbooks: a plain old Variac — or even the foot control from the sewing motor — would do.

construction

Main shaft. The main winding shaft is made from 0.25-inch (6.35 mm) steel rod, with a flat filed on one end for the drive pulley set screw, three small holes for securing the "thread" winding, and a tapped hole for attaching the coil form and mandrel. (When buying the rod, be sure to select the straightest and smoothest you can find; its dimensions are shown in fig. 1.) It seems wise to postpone placing the winding on the shaft until the winder is complete enough to be used

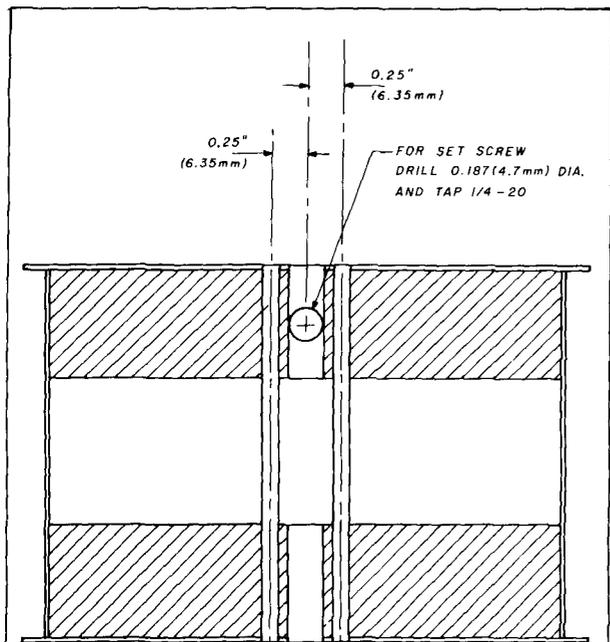

2.5 x 11.5 inch (6.35 x 29.2 cm) of 0.010 to 0.012 inch (0.25 to 0.3 mm) thick aluminum sheet (used printing plate). Position end disks on 0.25 inch (6.3 mm) rod for alignment. Wrap around end disks, cemented with epoxy (including overlap). Secure with sufficient rubber bands until set. Align carefully so aluminum sheet does not overhang disks.

End disks (2 needed): Make from particle board or plywood, 0.6 to 0.75 inch (15 to 19 mm) thick. Diameter: 3.5 inch (89 mm) with 0.25 inch (6.35 mm) hole in center.


2 holes all the way through, 0.125 inch (3.2 mm) diameter. Insert 2.5 inch (6.35 mm) long x 0.125 inch (3.2 mm) OD brass tubing and cement (for later addition of a turns counter). Drill these after assembly is complete.

2 flanges needed, 3.87-inch (98 mm) diameter with 0.25 inch (6.35 mm) hole in center. Make from aluminum sheet or thin, stiff cardboard. Cement to end disks.

fig. 4. Dimensions for drum parts and fabrication.

papers. Since the drive belt should never reach the edge of the pulley, the flanges aren't really necessary, but they look nice.

The hole for the set screw that secures the pulley on the shaft is tapped edgewise in the particle board (1/4-20), and so far the threads haven't stripped out. As an additional feature, I installed two pieces of 1/8 inch (3.27 mm) OD brass tubing (cut from discarded ball point pen refills) opposite each other on about 0.5 inch (12.7 mm) diameter and lengthwise through the pulley (avoid the set screw!). This was to provide the addition of a counter with a couple of stiff wires taped to its shaft that could be inserted inside these holes and slide freely as the shaft moved back and forth. Dimensions for the drum parts and fabrication are

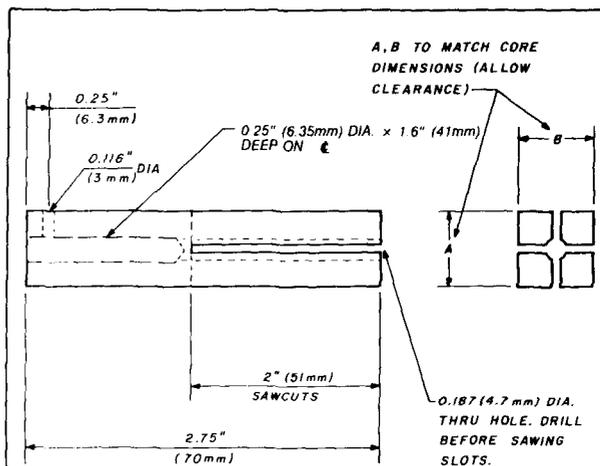

Select stiff, straight wires at least 5.5 inches (14 cm) long and small enough to slide freely in the brass tubing lined holes through the drive pulley (old bike spokes).

Position counter so that ends of counter drive wires are about 0.125 inch (3.2 mm) from nearest side of bearing block.

Build up counter shaft with tape. Place wires on opposite side and tape wires in place so their centers are 0.5 inch (12.7 mm) apart.

Make counter support block so that center of counter shaft is at same height as center of winding shaft and aligned with it. Block should be removable to enable changing rod.

fig. 5. Coil Mandrel.

shown in fig. 4. If one should want to add a counter as mentioned above, a sketch showing how I did it is shown in fig. 5.

Base and layout. I used a piece of 1/2 inch (12.7 mm) plywood, thickened to 1 inch (25.4 mm) around the edges, measuring approximately 26 x 10 inches (66 x 25 cm), as a base for the entire coil winder. Any convenient layout is satisfactory. I mounted the shaft bearing against an additional piece of wood the same length, using small nails and glue, providing a "lip" that could be mounted from the top side. Otherwise, mounting with wood screws up from the bottom side of the base into the bottom edge of the bearing should do the job. The drive belt won't be specified, but many are available that will work. The motor should be positioned so that the belt is just tight enough to run without slipping. Too tight a belt will cause obvious problems. A sewing machine shop would be the best place to look for a suitable drive belt; other sources might include jewelers or other craftsmen who could supply the belting used to run smaller lathes. This type of belting comes in a continuous length. A suitable piece is cut and the ends are joined together by heating.


The direction of rotation should be considered. In

John J. Meshna Jr., Inc.

P. O. Box 62 19 Allerton St. E. Lynn, Ma. 01904 Tel: (617) 595-2275


Dual 8" F. D. D. Case by SMS w/ POWER ONE Power Supply & Cooling Fans

We were very fortunate to find these beautifully designed & constructed rack mount disc drive cases in the surplus field. These cases were made for Scientific Micro Systems for their FT Series of equipment. They are manufactured from heavy gauge steel w/ a cast metal designer bezel. They were designed to house 2 8" floppy or hard drives. We offer you the case with the following components & features: hinged cover with restraining cable for simplified servicing of the interior components, 2 muffin fans for assured cool operation, studs for mounting the controller card listed below, and a heavy duty Power One power supply (their model no. CP 281A). The outputs of the power supply are as follows: +5 vdc 11 amps, +24 vdc 3.5 amps, +12 vdc .25 amps, -12 vdc .25 amps, & -5 vdc .25 amps. The input to the power supply is 115/230 vac 50/60 Hz. and is both filtered and fused. This assembly must have originally sold for well over \$300.00 each! Only 25 on hand, so order early or be left out on this super bargain! Shpg. wt. 38 lb. SPL-479-35 \$135.00 each

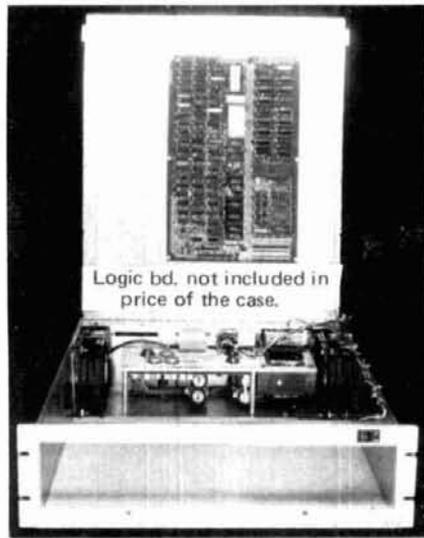


Scientific Micro Systems IBM 3740 Compatible 8" FDD Controller Card

The SMS FD 0502 8" floppy disc drive controller is a complete preprogrammed controller for single or double density recording on either single or dual headed disc drives. It performs control functions required to transfer data between 1 to 4 drives and a host system, performs all formatting functions required to read and write data and utilizes both IBM single and double density standards to achieve up to 630 Kilobytes of storage per disc surface. Some features are: programmable sector size, 128, 256, 512, or 1024 bytes, jumper selectable drive type, block transfer mode, sector buffer, overlapped head seek, on board General Purpose Host Interface with asynchronous 19 TTL signal lines for eight bit host system and input of only 5 vdc 6 amps. This board provides a direct interface to the following drives: Shugart 800-2/850, Pertec 511, Memorex 550/552, MFE 751B, Qume Data Trak and similar drives. These boards were removed from the above cabinets which were in service prior to our reception of them. The manufacturers price on these IBM compatible boards is currently \$900.00 each. These boards all appear to be in excellent condition. If more information is needed, please call us. Shpg. wt. 3 lb. SPL 480 \$150.00

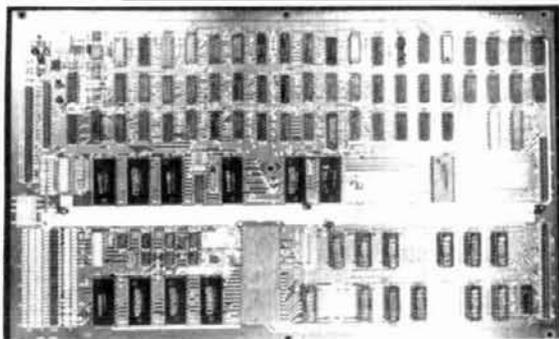


SEAGATE TECHNOLOGY ST 506 5 1/4" HARD DRIVES

The Seagate Technology ST 506 hard disc drive utilizes proven Winchester technology for reliable storage of up to 5 megabytes of formatted data. Some features of this very popular drive are: 5 megabit/second data transfer rate, simple floppy like interface, high speed band actuator & stepper head positioning, requires only +5 & +12 vdc, and same physical size and mounting parameters as a mini floppy drive. This Shugart compatible drive is the same as used on many home personal computers. Each drive is checked out prior to shipment. Comes with data. Only a few on hand, so order early. Shpg. wt. 8 lb. ST-506 \$225.00

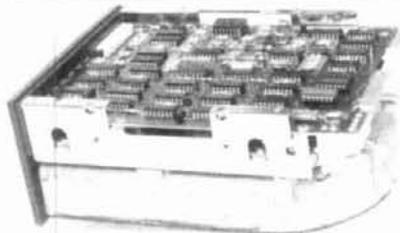


5 1/4" HARD DRIVE CONTROLLER CARD

Finally, affordable, intelligent disc drive controllers are available at low, low surplus prices. The OMTI 20C controller boards we offer are unused, late style, surplus from a now defunct system house. OMTI is a division of Scientific Micro Systems. These boards will handle up to (2) 5 1/4 inch Winchester type hard drives that utilize a standard 34 pin SASI interface. Perfect for using with the above Seagate ST 506 drive, or other hard drives from 5 megabytes of storage on up. The controllers have buffered ~~slew~~seek modes, overlapped seeks, auto seek & verify, extensive fault detection, auto head & cylinder switching, full sector buffering, 256/512 bytes/sector, 33 or 18 sectors/track (jumper selectable), programmable disc parameters and much more. The board runs on +5 vdc & +12 vdc.. We supply users manual & pinout data. Guaranteed O. K.. Shpg. wt. 3 lb. OMTI 20 C \$150.00 each 2/\$275.00 Qty. pricing available.

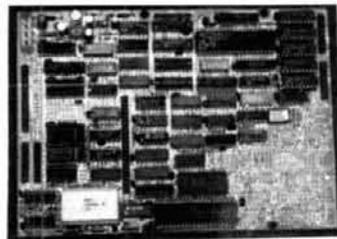

5 VDC 25 AMP SWITCHING POWER SUPPLY


We just got in a small lot of ruggedly built, lightweight (4 lb.), compact (11" x 5" x 1 1/2"), fully enclosed (cover removed for pic.), regulated, switching, power supplies made by RO Industries. Input of 115/230 vac is attached thru convenient, clearly marked screw terminals. The hefty 5 vdc 25 amp output is via heavy duty, brass lugs with a Red LED status indicator. All appear to be unused and in excellent condition. Shpg. wt. 6 lb. PS-8 \$50.00

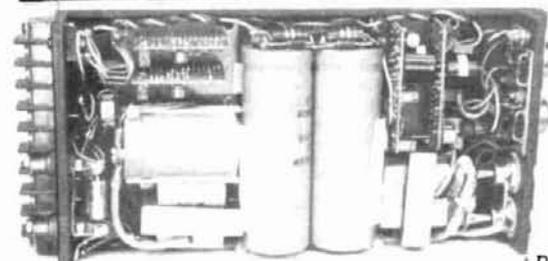

Free 72 page catalogue available or send \$1.00 for 1st class service to P. O. Box 62 E. Lynn, Ma. 01904.

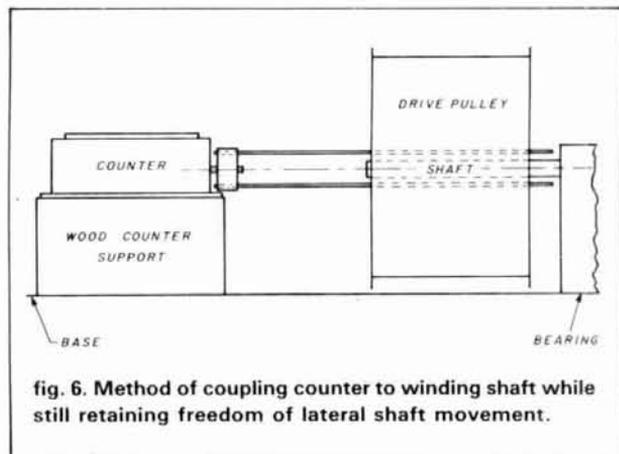Phone (617) 595-2275 to place your order by phone. MC, VISA or American Express charge cards accepted.





my opinion the top of the shaft should be moving away from you when you stand in front of the winder; this facilitates inserting insulation papers and observing the wire as it winds on.

Wire tension and feeding. In keeping with the idea of building something for practically nothing, the winding wire is fed onto the coil over a block of wood (see lower right in photo of completed unit) between two pieces of felt clamped in place by a short strip of metal held in position by small wooden screws. Glue one piece of felt to the piece of metal and one to the top of the wood block, and adjust wire tension by tightening or loosening the screws. Tension should be maintained as uniformly as possible all during the winding of a coil; too much tends to "crunch up" the layers already wound underneath, and too little leaves the wire already wound free to move around or slip out of position. A much more elaborate wire tensioning system would be preferred, but this method will hold the wire in position accurately enough for now. Feeding the wire off the end of the supply spool helps to avoid any additional drag.

Winding mandrel or form. I made this of wood cut to match the core size of the transformer, and with a hole diameter in one end to fit on the winding shaft, and in the other to accept a No. 10 screw (push in), and with saw cuts so that when the screw is removed, the mandrel shrinks a little to allow coil removal. To be safe, I included some paper shims — when the coil is finished, it's too late to discover that it won't go over the core! (See fig. 6 for details.)

General. Once this winder is in operation, it will become apparent that the lateral position of the shaft is rather delicate, so be careful to see that nothing gets in its way while winding. Once a set-up was made, I tested it by having the shaft run back and forth several times under power and with the follower pads clamped on just to make sure everything was in order before actually starting the winding. This also helps

the follower pads to match the shape of the wire screw thread.

A thin coat of lubricant such as petroleum jelly on the screw thread winding is suggested.

One more precaution should be mentioned. Since not all enameled wire of a given copper size has the same thickness of enamel on it, the best course to follow is to use wire from the same spool for both the screw thread winding and the coil, if not, make sure the wire for the thread is *not smaller* in overall diameter than that used for the wire to be wound.

I was able to wind over 2300 turns of No. 42 enameled wire on a coil without any problems, and found that it could be run at over 200 RPM as long as the speed was brought up gradually. (In case you're wondering, I was able to rewind the power transformer for the TV camera — and it's still working!)


This design could easily be adapted to provide for greater winding lengths than the 1.8 inch (46 mm) I have provided for. Just remember to increase the space between the bearing posts and the overall length of the shaft rod to allow for the extra lateral movement needed.

references

1. *SCR Manual*, 4th Edition, General Electric Company, page 210.

ham radio

SATELLITE TELEVISION RECEIVER SEMIKIT

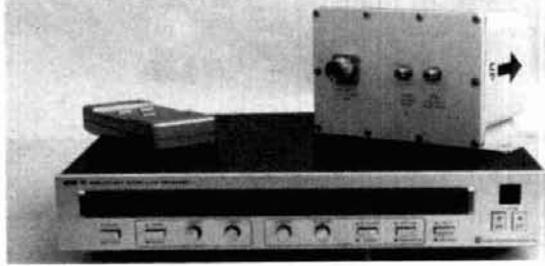

with dual conversion downconverter


FEATURES:

- Infrared remote control tuning
- AFC, SAW filter
- RF or video output
- Stereo output
- Polarator controls
- LED channel & tuning indicators

Install six factory assembled circuit boards to complete.

| | |
|--|-----------------|
| SEMIKIT | \$300.00 |
| Completed downconverter add | 100.00 |
| Completed receiver and downconverter add | 150.00 |

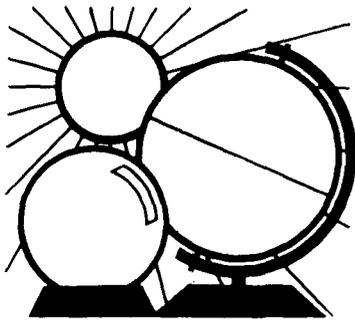JAMES WALTER SATELLITE RECEIVER
2697 Nickel, San Pablo, CA 94806 ✓ 178 Tel. 415-724-0587



DX FORECASTER

Garth Stonehocker, KØRYW

sporadic-E propagation

During the summer months, the sun, almost directly overhead, produces more ions in the lower ionosphere than it does in winter. These ions support short-skip propagation — even *multiple* short-skips. The geomagnetic field clusters and forces these overly abundant ions into cloud-like patches known as sporadic-E (E_s). These patches, which form in a thin dense layer about 60 miles (100 km) above the earth, give rise to strong, mirror-like signal reflections over short-skip distances of 600 to 1200 miles (1000 to 2000 km).

Because E_s is related to the summer sun, the best locations for working these E_s openings are in the Northern Hemisphere from June through Sep-

tember and in the Southern Hemisphere during its summer, December through March. In each hemisphere the best E_s is found on either side of the geomagnetic equator; it's especially good where the geomagnetic equator is farthest from the geographic equator, giving greater distance and force for formation. These special areas are South-east Asia in the Northern Hemisphere and South America in the Southern Hemisphere, with the former the better of the two. This is because the sun's maximum level of ion production occurs in the D and E layers (37 to 62 miles, or 60 to 100 km) above the earth at 23 degrees latitude, directly under the sun. As the ionization travels (in movement known as *diffusion* or *drift*) from this maximum to less dense areas, E_s is

bunched by field-strength variations. When ions move, they can move only parallel to the geomagnetic field lines, not perpendicular to them. (See cross-section views of the earth's magnetic field lines in **fig. 1**, particularly those lines connecting the northern and southern hemispheres.) **Figure 2'** shows the movement of E_s patches across the United States. The E_s patches are the variation (bunching) of ions caused by changes in the geomagnetic field strength modulating and forcing the ions in their north-south movement. In these two special areas of maximum separation between equators, the modulating force and the distance over which to bunch are greatest, so more E_s patches are formed.

last-minute forecast

DX conditions for the higher frequency bands, 10 through 30 meters, are expected to be very good during the first and last weeks of the month when the solar flux could be high. (Verify this daily by checking WWV at 18 minutes after each hour.) During the middle weeks of the month, the lower frequency bands should engage interest for some short skip daytime and DX at night. Geomagnetic disturbances are expected on June 6th and 16th. The moon will be full on the 3rd, and closest approach (perigee) will

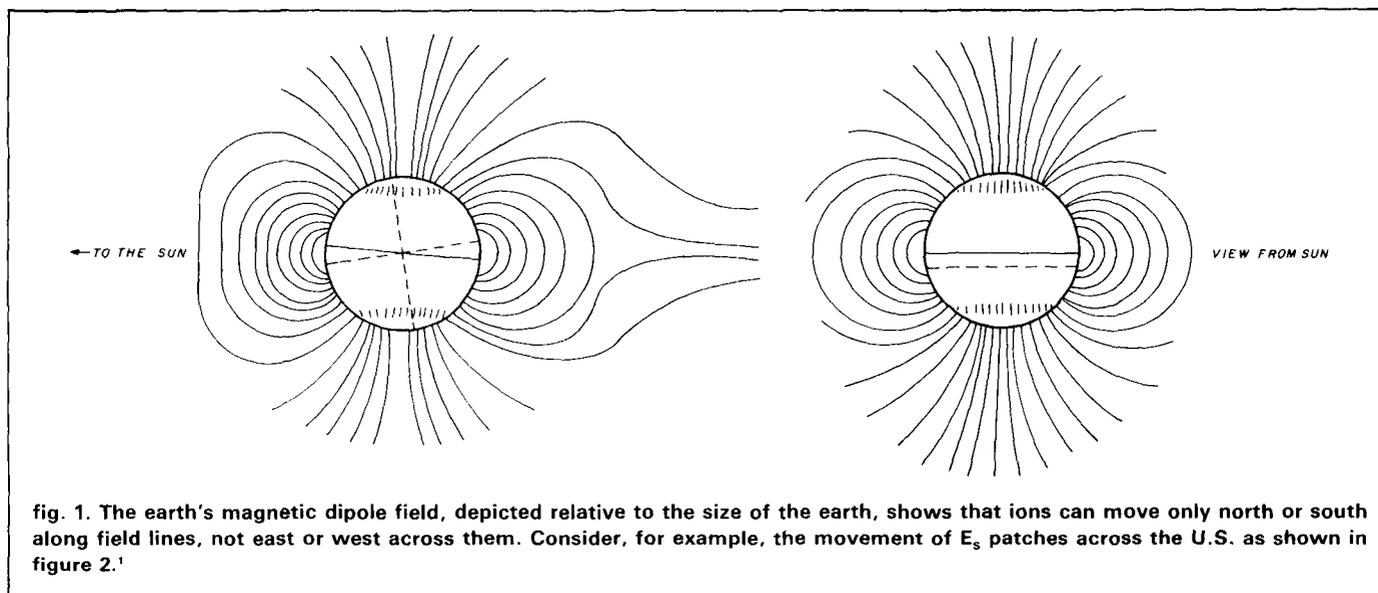


fig. 1. The earth's magnetic dipole field, depicted relative to the size of the earth, shows that ions can move only north or south along field lines, not east or west across them. Consider, for example, the movement of E_s patches across the U.S. as shown in figure 2.'

WESTERN USA

| GMT | PDT | Directional Indicators | | | | | | | |
|------|-------|------------------------|----|-----|-----|----|----|----|----|
| | | N | NE | E | SE | S | SW | W | NW |
| 0000 | 5:00 | 20 | 20 | 15 | 15 | 20 | 10 | 15 | 20 |
| 0100 | 6:00 | 20 | 20 | 20 | 15 | 20 | 10 | 15 | 20 |
| 0200 | 7:00 | 20 | 20 | 20 | 15 | 20 | 10 | 15 | 20 |
| 0300 | 8:00 | 20 | 20 | 20 | 15 | 20 | 15 | 15 | 20 |
| 0400 | 9:00 | 20 | 20 | 20 | 15 | 30 | 15 | 15 | 20 |
| 0500 | 10:00 | 20 | 20 | 20 | 15 | 30 | 15 | 15 | 20 |
| 0600 | 11:00 | 20 | 30 | 20 | 15 | 30 | 15 | 15 | 20 |
| 0700 | 12:00 | 20 | 30 | 20 | 15 | 30 | 20 | 15 | 20 |
| 0800 | 1:00 | 20 | 30 | 30* | 20 | 30 | 20 | 20 | 20 |
| 0900 | 2:00 | 20 | 30 | 20 | 20 | 30 | 20 | 20 | 20 |
| 1000 | 3:00 | 20 | 30 | 20 | 20 | 30 | 20 | 20 | 20 |
| 1100 | 4:00 | 20 | 20 | 20 | 20 | 30 | 20 | 20 | 20 |
| 1200 | 5:00 | 20 | 20 | 15 | 20 | 30 | 20 | 20 | 20 |
| 1300 | 6:00 | 20 | 20 | 15 | 20 | 30 | 20 | 20 | 30 |
| 1400 | 7:00 | 20 | 20 | 15 | 20 | 30 | 20 | 20 | 30 |
| 1500 | 8:00 | 20 | 20 | 15 | 30* | 30 | 20 | 30 | 30 |
| 1600 | 9:00 | 20 | 20 | 15 | 30 | 30 | 20 | 30 | 30 |
| 1700 | 10:00 | 20 | 20 | 15 | 20 | 20 | 15 | 20 | 20 |
| 1800 | 11:00 | 20 | 20 | 15 | 20 | 20 | 15 | 20 | 20 |
| 1900 | 12:00 | 20 | 20 | 10 | 20 | 20 | 15 | 15 | 20 |
| 2000 | 1:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 2100 | 2:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2200 | 3:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2300 | 4:00 | 20 | 20 | 15 | 15 | 20 | 10 | 15 | 20 |

MID USA

| GMT | MDT | Directional Indicators | | | | | | | |
|------|-------|------------------------|----|----|----|----|----|----|----|
| | | N | NE | E | SE | S | SW | W | NW |
| 0000 | 6:00 | 20 | 20 | 15 | 20 | 20 | 10 | 15 | 20 |
| 0100 | 7:00 | 20 | 20 | 20 | 20 | 20 | 10 | 15 | 20 |
| 0200 | 8:00 | 20 | 20 | 20 | 20 | 30 | 10 | 15 | 20 |
| 0300 | 9:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0400 | 10:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0500 | 11:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 0600 | 12:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 0700 | 1:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 0800 | 2:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 0900 | 3:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1000 | 4:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1100 | 5:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1200 | 6:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1300 | 7:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1400 | 8:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1500 | 9:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1600 | 10:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1700 | 11:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1800 | 12:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 1900 | 1:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 2000 | 2:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 2100 | 3:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2200 | 4:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2300 | 5:00 | 20 | 20 | 15 | 15 | 20 | 10 | 15 | 20 |

EASTERN USA

| GMT | EDT | Directional Indicators | | | | | | | |
|------|-------|------------------------|----|----|----|----|----|----|----|
| | | N | NE | E | SE | S | SW | W | NW |
| 0000 | 8:00 | 20 | 20 | 15 | 20 | 20 | 10 | 15 | 20 |
| 0100 | 9:00 | 20 | 20 | 20 | 20 | 20 | 10 | 15 | 20 |
| 0200 | 10:00 | 20 | 20 | 20 | 20 | 30 | 10 | 15 | 20 |
| 0300 | 11:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0400 | 12:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0500 | 1:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0600 | 2:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0700 | 3:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0800 | 4:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 0900 | 5:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 1000 | 6:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 1100 | 7:00 | 20 | 20 | 20 | 20 | 30 | 15 | 15 | 20 |
| 1200 | 8:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1300 | 9:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1400 | 10:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1500 | 11:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1600 | 12:00 | 20 | 20 | 15 | 15 | 30 | 15 | 15 | 20 |
| 1700 | 1:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 1800 | 2:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 1900 | 3:00 | 20 | 20 | 10 | 15 | 20 | 15 | 15 | 20 |
| 2000 | 4:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2100 | 5:00 | 20 | 20 | 15 | 15 | 20 | 15 | 15 | 20 |
| 2200 | 6:00 | 20 | 20 | 15 | 15 | 20 | 10 | 15 | 20 |
| 2300 | 7:00 | 20 | 20 | 15 | 15 | 20 | 10 | 15 | 20 |

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides the MUF during "normal" hours.
 *Look at next higher band for possible openings.

NCG Co. NEW-TECHNOLOGY HIGH-QUALITY

AFFORDABLE TRANSCEIVERS FOR ALL. WINNERS IN COMPARISON HANDS DOWN!

10/160 M HF TRANSCEIVER



40-15-6 M NEW TRI-BANDER



15 M 15 METER MOBILE



JUST SLIGHTLY AHEAD! WITH THE QUALITY YOU HAVE ALWAYS LOOKED FOR!

4 MEMORIES - 3 WAY AUTO SCAN, DUAL VFO, IF SHIFT, CW-W, 400 Hz. CW-N 200 Hz ALL 9 BANDS PLUS MARS. BUILT IN AC/DC POWER, SSB, CW OR RTTY, I.F. TUNE 3-STEP TUNING SPEED, 200 WATT PEP, MICROPHONE IMPEDANCE 600-50K OHM HAND MIC. INCLUDED.

40, 15 AND 6 METERS ARE YOUR BASE STATION OR MOBILE WITH AC/DC BUILT IN POWER SUPPLY CW-N 200 Hz OR USB, 2.S0239 ANTENNA CONNECTORS, HAND MIC. BUILT IN TVI FILTER LITTLE TO NO TV INTERFERENCE, 20 WATTS PEP, MARS ON 40 AND 6 METERS.

A GREAT QRP RIG WITH THE BIG RIG SIGNAL, 2 WATTS OR 10 WATTS OUT, BUILT IN CW SIDE TONE, DIGITAL DISPLAY, HAND MIC. TOP MOUNTED SPEAKER. MOBILE BRACKET, RIT OR FINE TUNE TX&RX, ±4KHz, 21 TO 21.450 MHz SIGNAL TO NOISE MORE THAN 10dB DOWN.



SPECIAL

SPECIAL

SPECIAL

90 DAY WARRANTY ON ALL TRANSCEIVERS - DIRECT FROM NCG OR YOUR DEALER

WE HAVE 1.2 GHz BASE/REPEATER & MOBILE ANTENNAS

1275 N. Grove Street, Anaheim, CA 92806 (714) 630-4541

✓ 179

NOTE: PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION

SPECIAL OFFER

CALLBOOKS NOW INCLUDE A **FREE** MAP

VALUE \$2.50 each

NORTH AMERICAN CALLBOOK

Includes free map of North America.

The New North American Callbook now contains Canadian and Mexican as well as all US Radio Amateurs. Fully updated with all the latest call signs and addresses. Edited to ensure accuracy. Includes handy station aids. ©1984.

CB-US85

Softbound \$25

(\$21.95 + \$3.05 s & h)

FOREIGN CALLBOOK

Includes free World Wide Prefix map.

The **only** source of DX calls and addresses available. Fully updated and has helpful QSL information. ©1984

CB-F85

Softbound \$24

(\$20.95 + \$3.05 s & h)



Order Both and **SAVE** even more — Regular Price \$45

HAM RADIO SPECIAL \$39.95 POSTPAID

SAVE \$5

ham radio magazine **BOOKSTORE**

GREENVILLE, NH 03048

(603) 878-1441

✓ 134

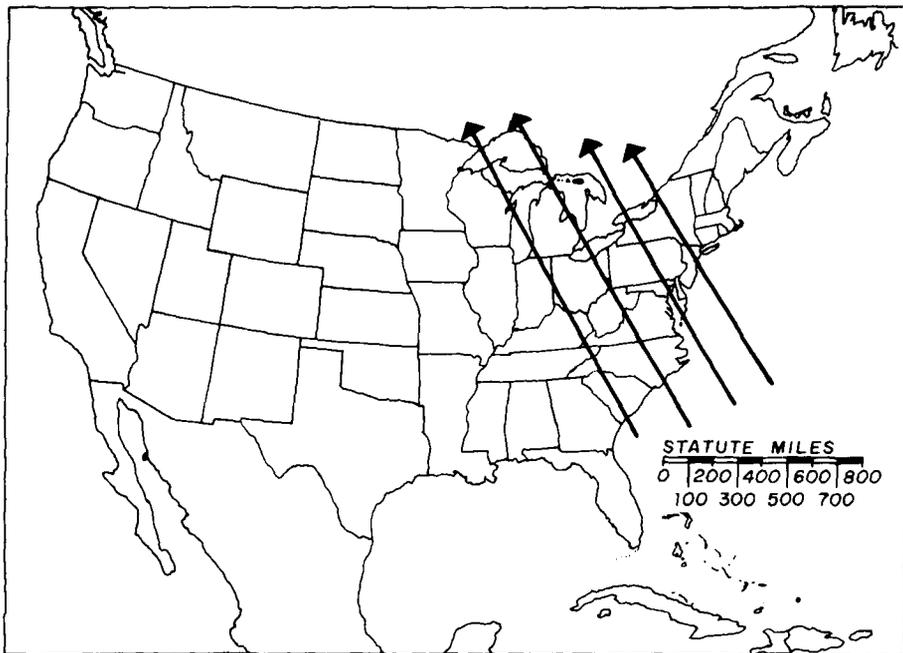


fig. 2. Clouds producing sporadic-E propagation generally travel from southeast to northwest at approximately 180 miles (280 km) per hour, moving in a relatively straight line.

occur on the 1st and 29th. Summer solstice is on the 21st at 1044 UTC. The Aquarid meteor shower starts about the 18th, peaks about the 28th, and lasts until about August 7. The maximum radio-echo rate will be 34 per hour.

band-by-band summary

Six meters will provide occasional openings to South Africa and South America around noontime by short-skip E_s.

Ten meters will provide long-skip conditions in the afternoon during the peak times of the 27-day solar cycle. Otherwise, look to sporadic-E short-skip and multihop openings around local noon for DX on these bands. (Transequatorial evening openings do not usually occur in the summertime.)

Fifteen and twenty meters, almost always open to some part of the world, will be the main daytime DX bands. Twenty meters will stay open on long southern paths into the night, though 15 will drop out in the late afternoon. Operate on 15 first, then move down to 20 meters later. DX is 5000 to 7000 miles (8000 to 11,200 km) on these

bands. There may be some long one-hop transequatorial propagation.

Thirty and forty meters are both daytime and nighttime bands. Intermediate distance operation (1000 to 1500 miles, 1600 to 2400 km), in any direction is considered daytime DX. Nighttime DX on these two bands may be expected to occur over greater distances than on 80 meters and, like 80, will follow the darkness path across the sky. Signal strength and distances covered are reduced on days of high solar flux values. In addition, no 30-meter openings will take place during the pre-dawn hours on the morning after these high radio flux values.

Eighty and one-sixty meters will exhibit short-skip conditions during daylight hours and lengthen for DX near dark. Eighty meters will open to the east just before your sunset swing more to the south as midnight approaches, and end up in the Pacific areas during the hour or so before dawn. (One-sixty opens later and ends earlier.)

references

1. Joe Reisert, W1JR, "The VHF/UHF Primer: An Introduction to Propagation," *ham radio*, July, 1984, page 14.

ham radio

RF TRANSISTORS

FRESH STOCK - NOT SURPLUS
TESTED — FULLY GUARANTEED

| 2-30MHz 12V (* = 28V) | | | |
|-----------------------|--------|---------|----------|
| P/N | Rating | Ea | Match Pr |
| MRF406 | 20W | \$14.50 | \$32.00 |
| MRF412 | 80W | 18.00 | 40.00 |
| MRF412A | 80W | 18.00 | 40.00 |
| MRF421 | 100W | 25.00 | 54.00 |
| MRF421C | 110W | 27.00 | 58.00 |
| MRF422* | 150W | 38.00 | 82.00 |
| MRF426* | 25W | 17.00 | 40.00 |
| MRF426A* | 25W | 17.00 | 40.00 |
| MRF433 | 13W | 14.50 | 32.00 |
| MRF435* | 150W | 42.00 | 90.00 |
| MRF449 | 30W | 12.00 | 27.00 |
| MRF449A | 30W | 11.00 | 25.00 |
| MRF450 | 50W | 12.00 | 27.00 |
| MRF450A | 50W | 12.00 | 27.00 |
| MRF453 | 60W | 15.00 | 33.00 |
| MRF453A | 60W | 15.00 | 33.00 |
| MRF454 | 80W | 16.00 | 35.00 |
| MRF454A | 80W | 16.00 | 35.00 |
| MRF455 | 60W | 12.00 | 27.00 |
| MRF455A | 60W | 12.00 | 27.00 |
| MRF458 | 80W | 18.00 | 40.00 |
| MRF460 | 60W | 16.50 | 36.00 |
| MRF475 | 12W | 3.00 | 9.00 |
| MRF476 | 3W | 2.50 | 8.00 |
| MRF477 | 40W | 13.00 | 29.00 |
| MRF479 | 15W | 10.00 | 23.00 |
| MRF485* | 15W | 6.00 | 15.00 |
| MRF492 | 90W | 18.00 | 39.00 |
| SRF2072 | 75W | 15.00 | 33.00 |
| CD2545 | 50W | 24.00 | 55.00 |

Selected High Gain Matched Quads Available

| VHF TRANSISTORS | | | |
|-----------------|--------|---------|----------|
| Type | Rating | Ea | Match/Pr |
| MRF221 | 15W | \$10.00 | — |
| MRF222 | 12W | 12.00 | — |
| MRF224 | 40W | 13.50 | \$32.00 |
| MRF231 | 3.5W | 10.00 | — |
| MRF234 | 25W | 15.00 | 39.00 |
| MRF237 | 1W | 2.50 | — |
| MRF238 | 30W | 12.00 | — |
| MRF239 | 30W | 15.00 | — |
| MRF240 | 40W | 16.00 | — |
| MRF245 | 80W | 25.00 | 59.00 |
| MRF247 | 80W | 25.00 | 59.00 |
| MRF260 | 5W | 6.00 | — |
| MRF264 | 30W | 13.00 | — |
| MRF492 | 70W | 18.00 | 39.00 |
| MRF607 | 1.8W | 2.50 | — |
| MRF627 | 0.5W | 9.00 | — |
| MRF641 | 15W | 18.00 | — |
| MRF644 | 25W | 23.00 | — |
| MRF646 | 40W | 24.00 | 59.00 |
| MRF648 | 60W | 29.50 | 69.00 |
| SD1416 | 80W | 29.50 | — |
| SD1477 | 125W | 37.00 | — |
| 2N4427 | 1W | 1.25 | — |
| 2N5945 | 4W | 10.00 | — |
| 2N5946 | 10W | 12.00 | — |
| 2N6080 | 4W | 6.00 | — |
| 2N6081 | 15W | 7.00 | — |
| 2N6082 | 25W | 9.00 | — |
| 2N6083 | 30W | 9.50 | — |
| 2N6084 | 40W | 12.00 | 29.00 |
| TMOS FET | | | |
| MRF137 | 30W | \$22.50 | — |
| MRF138 | 30W | 35.00 | — |
| MRF140 | 150W | 92.00 | — |
| MRF150 | 150W | 80.00 | — |
| MRF172 | 80W | 65.00 | — |
| MRF174 | 125W | 88.00 | — |

Technical Assistance & cross-reference information on CD, PT, RF, SRF, SD P/Ns Call Engineering Dept. (619) 744-0728

RF Parts Catalog Available
OEM & Quantity Discounts ✓ 180

Minimum Order \$20 Add \$3.50 Shipping
WE SHIP SAME DAY C.O.D./VISA/MC

ORDERS ONLY: 800-854-1927



WESTCOM

1320 Grand Ave. San Marcos
California 92069 (619) 744-0728

TUBES

| TYPE | PRICE | TYPE | PRICE | TYPE | PRICE |
|----------------|----------|------------------|----------|--------------------|----------|
| 2C39/7289 | \$ 34.00 | 1182/4600A | \$500.00 | ML7815AL | \$ 60.00 |
| 2E26 | 7.95 | 4600A | 500.00 | 7843 | 107.00 |
| 2K28 | 200.00 | 4624 | 310.00 | 7854 | 130.00 |
| 3-500Z | 102.00 | 4657 | 84.00 | ML7855KAL | 125.00 |
| 3-1000Z/8164 | 400.00 | 4662 | 100.00 | 7984 | 14.95 |
| 3B28/866A | 9.50 | 4665 | 500.00 | 8072 | 84.00 |
| 3CX400U7/8961 | 255.00 | 4687 | P.O.R. | 8106 | 5.00 |
| 3CX1000A7/8283 | 526.00 | 5675 | 42.00 | 8117A | 225.00 |
| 3CX3000F1/8239 | 567.00 | 5721 | 250.00 | 8121 | 110.00 |
| 3CW30000H7 | 1700.00 | 5768 | 125.00 | 8122 | 110.00 |
| 3X2500A3 | 473.00 | 5819 | 119.00 | 8134 | 470.00 |
| 3X3000F1 | 567.00 | 5836 | 232.50 | 8156 | 12.00 |
| 4-65A/8165 | 69.00 | 5837 | 232.50 | 8233 | 60.00 |
| 4-125A/4D21 | 79.00 | 5861 | 140.00 | 8236 | 35.00 |
| 4-250A/5D22 | 98.00 | 5867A | 185.00 | 8295/PL172 | 500.00 |
| 4-400A/8438 | 98.00 | 5868/AX9902 | 270.00 | 8458 | 35.00 |
| 4-400B/7527 | 110.00 | 5876/A | 42.00 | 8462 | 130.00 |
| 4-400C/6775 | 110.00 | 5881/6L6 | 8.00 | 8505A | 95.00 |
| 4-1000A/8166 | 444.00 | 5893 | 60.00 | 8533W | 136.00 |
| 4CX250B/7203 | 54.00 | 5894/A | 54.00 | 8560/A | 75.00 |
| 4CX250FG/8621 | 75.00 | 5894B/8737 | 54.00 | 8560AS | 100.00 |
| 4CX250K/8245 | 125.00 | 5946 | 395.00 | 8608 | 38.00 |
| 4CX250R/7580W | 90.00 | 6083/AZ9909 | 95.00 | 8624 | 100.00 |
| 4CX300A/8167 | 170.00 | 6146/6146A | 8.50 | 8637 | 70.00 |
| 4CX350A/8321 | 110.00 | 6146B/8298 | 10.50 | 8643 | 83.00 |
| 4CX350F/8322 | 115.00 | 6146W/7212 | 17.95 | 8647 | 168.00 |
| 4CX350FJ/8904 | 140.00 | 6156 | 110.00 | 8683 | 95.00 |
| 4CX600J/8809 | 835.00 | 6159 | 13.85 | 8877 | 465.00 |
| 4CX1000A/8168 | 242.50* | 6159B | 23.50 | 8908 | 13.00 |
| 4CX1000A/8168 | 485.00 | 6161 | 325.00 | 8950 | 13.00 |
| 4CX1500B/8660 | 555.00 | 6280 | 42.50 | 8930 | 137.00 |
| 4CX5000A/8170 | 1100.00 | 6291 | 180.00 | 6L6 Metal | 25.00 |
| 4CX10000D/8171 | 1255.00 | 6293 | 24.00 | 6L6GC | 5.03 |
| 4CX15000A/8281 | 1500.00 | 6326 | P.O.R. | 6CA7/EL34 | 5.38 |
| 4CW800F | 710.00 | 6360/A | 5.75 | 6CL6 | 3.50 |
| 4D32 | 240.00 | 6399 | 540.00 | 6DJ8 | 2.50 |
| 4E27A/5-125B | 240.00 | 6550A | 10.00 | 6DQ5 | 6.58 |
| 4PR60A | 200.00 | 6883B/8032A/8552 | 10.00 | 6GF5 | 5.85 |
| 4PR60B | 345.00 | 6897 | 160.00 | 6GJ5A | 6.20 |
| 4PR65A/8187 | 175.00 | 6907 | 79.00 | 6GK6 | 6.00 |
| 4PR1000A/8189 | 590.00 | 6922/6DJ8 | 5.00 | 6HB5 | 6.00 |
| 4X150A/7034 | 60.00 | 6939 | 22.00 | 6HF5 | 8.73 |
| 4X150D/7609 | 95.00 | 7094 | 250.00 | 6JG6A | 6.28 |
| 4X250B | 45.00 | 7117 | 38.50 | 6JM6 | 6.00 |
| 4X250F | 45.00 | 7203 | P.O.R. | 6JN6 | 6.00 |
| 4X500A | 412.00 | 7211 | 100.00 | 6JS6C | 7.25 |
| 5CX1500A | 660.00 | 7213 | 300.00* | 6KN6 | 5.05 |
| KT88 | 27.50 | 7214 | 300.00* | 6KD6 | 8.25 |
| 416B | 45.00 | 7271 | 135.00 | 6LF6 | 7.00 |
| 416C | 62.50 | 7289/2C39 | 34.00 | 6LQ6 G.E. | 7.00 |
| 572B/T160L | 49.95 | 7325 | P.O.R. | 6LQ6/6MJ6 Sylvania | 9.00 |
| 592/3-200A3 | 211.00 | 7360 | 13.50 | 6ME6 | 8.90 |
| 807 | 8.50 | 7377 | 85.00 | 12AT7 | 3.50 |
| 811A | 15.00 | 7408 | 2.50 | 12AX7 | 3.00 |
| 812A | 29.00 | 7609 | 95.00 | 12BY7 | 5.00 |
| 813 | 50.00 | 7735 | 36.00 | 12JB6A | 6.50 |

NOTE * = USED TUBE

NOTE P.O.R. = PRICE ON REQUEST

"ALL PARTS MAY BE NEW, USED, OR SURPLUS. PARTS MAY BE SUBSTITUTED WITH COMPARABLE PARTS IF WE ARE OUT OF STOCK OF AN ITEM.

NOTICE: ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

For information call: 602-265-0731

Toll Free Number
800-528-0180
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

MHz electronics

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"FILTERS"

COLLINS Mechanical Filter #526-9724-010 MODEL F455Z32F

455KHZ at 3.2KHz wide. May be other models but equivalent. May be used or new, \$15.99

ATLAS Crystal Filters

5.595-2.7/8/LSB, 5.595-2.7/LSB
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99

5.595-2.7/8/U, 5.595-2.7/USB
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99

5.595-.500/4, 5.595-.500/4/CW
4 pole 500 cycles wide CW. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99

9.0USB/CW
6 pole 2.7KHz wide at 6dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-1599Hz 19.99

KOKUSAI ELECTRIC CO. Mechanical Filter #MF-455-ZL/ZU-21H

455KHz at Center Frequency of 453.5KC. Carrier Frequency of 455KHz 2.36K Bandwidth.
Upper sideband. (ZU) 19.99
Lower sideband. (ZL) 19.99

CRYSTAL FILTERS

| | | | |
|----------|------------|--|---------|
| NIKKO | FX-07800C | 7.8MHz | \$10.00 |
| TEW | FEC-103-2 | 10.6935MHZ | 10.00 |
| SDK | SCH-113A | 11.2735MHZ | 10.00 |
| TAMA | TF-31H250 | CF 3179.3KHz | 19.99 |
| TYCO/CD | 001019880 | 10.7MHz 2pole 15KHz bandwidth | 5.00 |
| MOTOROLA | 4884863B01 | 11.7MHz 2pole 15KHz bandwidth | 5.00 |
| PTI | 5350C | 12MHz 2pole 15KHz bandwidth | 5.00 |
| PTI | 5426C | 21.4MHz 2pole 15KHz bandwidth | 5.00 |
| PTI | 1479 | 10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB | 20.00 |
| COMTECH | AI0300 | 45MHz 2pole 15KHz bandwidth | 6.00 |
| FRC | ERXF-15700 | 20.6MHz 36KHz wide | 10.00 |
| FILTECH | 2131 | CF 7.825MHz | 10.00 |

CERAMIC FILTERS

| | | | |
|------------|----------------|---|-------|
| AXEL | 4F449 | 12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.4KHz | 10.00 |
| CLEVITE | TO-01A | 455KHz+-2KHz bandwidth 4-7% at 3dB | 5.00 |
| | TCF4-12D36A | 455KHz+-1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz | 10.00 |
| MURATA | BFB455B | 455KHz | 2.50 |
| | BFB455L | 455KHz | 3.50 |
| | CFM455E | 455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 50dB | 6.65 |
| | CFM455D | 455KHz +-7KHz at 3dB, +-10KHz at 6dB, +-20KHz at 50dB | 6.65 |
| | CFR455E | 455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 60dB | 8.00 |
| | CFU455B | 455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at 40dB | 2.90 |
| | CFU455C | 455KHz +-2KHz bandwidth +-12.5KHz at 6dB, +-24KHz at 40dB | 2.90 |
| | CFU455G | 455KHz +-1KHz bandwidth +-4.5KHz at 6dB, +-10KHz at 40dB | 2.90 |
| | CFU455H | 455KHz +-1KHz bandwidth +-3KHz at 6dB, +-9KHz at 40dB | 2.90 |
| | CFU455I | 455KHz +-1KHz bandwidth +-2KHz at 6dB, +-6KHz at 40dB | 2.90 |
| | CFW455D | 455KHz +-10KHz at 6dB, +-20KHz at 40dB | 2.90 |
| | CFW455H | 455KHz +-3KHz at 6dB, +-9KHz at 40dB | 2.90 |
| | SFB455D | 455KHz | 2.50 |
| | SFD455D | 455KHz +-2KHz, 3dB bandwidth 4.5KHz +-1KHz | 5.00 |
| | SFE10.7MA | 10.7MHz 280KHz +-50KHz at 3dB, 650KHz at 20dB | 2.50 |
| | SFE10.7MS | 10.7MHz 230KHz +-50KHz at 3dB, 570KHz at 20dB | 2.50 |
| | SFG10.7MA | 10.7MHz | 10.00 |
| NIPPON | LF-B4/CFU455I | 455KHz +-1KHz | 2.90 |
| | LF-B6/CFU455H | 455KHz +-1KHz | 2.90 |
| | LF-B8 | 455KHz | 2.90 |
| | LF-C18 | 455KHz | 10.00 |
| TOKIN | CF455A/BFU455K | 455KHz +-2KHz | 5.00 |
| MATSUSHIRA | EFC-L455K | 455KHz | 7.00 |

SPECTRA PHYSICS INC. Model 088 HeNe LASER TUBES

| | | | |
|-----------------------|------------------|-----------------|-------------------------|
| POWER OUTPUT 1.6MW. | BEAM DIA. .75MM | BEAM DIR. 2.7MR | 8KV STARTING VOLTAGE DC |
| 68K OHM 1WATT BALLAST | 1000VDC +-100VDC | At 3.7MA | \$59.99 |

ROTRON MUFFIN FANS Model MARK4/MU2A1

| | | | | | |
|-----------------|---------------|----------|-----------------------|----------------|---------|
| 115 VAC | 14WATTS | 50/60CPS | IMPEDENCE PROTECTED-F | 88CFM at 50CPS | \$ 7.99 |
| 105CFM at 60CPS | THESE ARE NEW | | | | |

MHz electronics

Toll Free Number
800-528-0180
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE For information call: 602-265-0731

RF TRANSISTORS

| TYPE | PRICE | TYPE | PRICE | TYPE | PRICE | TYPE | PRICE |
|---------------|---------|------------|----------|----------------|---------|---------------|---------|
| 2N1561 | \$25.00 | 2N5920 | \$ 70.00 | 40608 RCA | \$ 2.48 | BFY90 | \$ 1.50 |
| 2N1562 | 25.00 | 2N5921 | 80.00 | 40673 RCA | 2.50 | BLW60C5 | 15.00 |
| 2N1692 | 25.00 | 2N5922 | 10.00 | 40894 RCA | 1.00 | BLX67 | 12.25 |
| 2N2857 | 1.55 | 2N5923 | 25.00 | 60247 RCA | 25.00 | BLX67C3 | 12.25 |
| 2N2857JAN | 4.10 | 2N5941 | 23.00 | 61206 RCA | 100.00 | BLX93C3 | 22.21 |
| 2N2857JANTX | 4.50 | 2N5942 | 40.00 | 62800A RCA | 60.00 | BLY87A | 7.50 |
| 2N2876 | 13.50 | 2N5944 | 10.35 | 62803 RCA | 100.00 | BLY88C3 | 13.08 |
| 2N2947 | 18.35 | 2N5945 | 10.00 | 430414/3990RCA | 50.00 | BLY89C | 13.00 |
| 2N2948 | 13.00 | 2N5946 | 12.00 | 3457159 RCA | 20.00 | BLY90 | 45.00 |
| 2N2949 | 15.50 | 2N5947 | 9.20 | 3729685-2 RCA | 75.00 | BLY92 | 13.30 |
| 2N3118 | 5.00 | 2N6080 | 6.00 | 3729701-2 RCA | 50.00 | BLY94C | 45.00 |
| 2N3119 | 4.00 | 2N6081 | 7.00 | 3753883 RCA | 50.00 | BLY351 | 10.00 |
| 2N3134 | 1.15 | 2N6082 | 9.00 | 615467-902 | 25.00 | BLY568C/CF | 30.00 |
| 2N3287 | 4.90 | 2N6083 | 9.50 | 615467-903 | 40.00 | C2M70-28R | 92.70 |
| 2N3288 | 4.40 | 2N6084 | 12.00 | 2SC568 | 2.50 | C25-28 | 57.00 |
| 2N3309 | 4.85 | 2N6094 | 11.00 | 2SC703 | 36.00 | C4005 | 2.50 |
| 2N3375 | 17.10 | 2N6095 | 12.00 | 2SC756A | 7.50 | CD1659 | 20.00 |
| 2N3478 | 2.13 | 2N6096 | 16.10 | 2SC781 | 2.80 | CD1899 | 20.00 |
| 2N3553 | 1.55 | 2N6097 | 20.70 | 2SC1018 | 1.00 | CD1920 | 10.00 |
| 2N3553JAN | 2.90 | 2N6105 | 21.00 | 2SC1042 | 24.00 | CD2188 | 18.00 |
| 2N3632 | 15.50 | 2N6136 | 21.85 | 2SC1070 | 2.50 | CD2545 | 24.00 |
| 2N3733 | 11.00 | 2N6166 | 40.24 | 2SC1216 | 2.50 | CD2664A | 16.00 |
| 2N3818 | 5.00 | 2N6267 | 142.00 | 2SC1239 | 2.50 | CD3167 | 92.70 |
| 2N3866 | 1.30 | 2N6304 | 1.50 | 2SC1251 | 24.00 | CD3353 | 95.00 |
| 2N3866JAN | 2.20 | 2N6368 | 30.00 | 2SC1306 | 2.90 | CD3435 | 26.30 |
| 2N3866JANTX | 3.80 | 2N6439 | 55.31 | 2SC1307 | 5.50 | CD3900 | 152.95 |
| 2N3866JANTXV | 4.70 | 2N6459 | 18.00 | 2SC1424 | 2.80 | CM25-12 | 20.00 |
| 2N3866AJANTXV | 5.30 | 2N6567 | 10.06 | 2SC1600 | 5.00 | CM40-12 | 27.90 |
| 2N3924 | 3.35 | 2N6603 | 13.50 | 2SC1678 | 2.00 | CM40-28 | 56.90 |
| 2N3926 | 16.10 | 2N6604 | 13.50 | 2SC1729 | 32.40 | CME50-12 | 30.00 |
| 2N3927 | 17.25 | 2N6679 | 44.00 | 2SC1760 | 1.50 | CTC2001 | 42.00 |
| 2N3948 | 1.75 | 2N6680 | 80.00 | 2SC1909 | 4.00 | CTC2005 | 55.00 |
| 2N3950 | 25.00 | 021-1 | 15.00 | 2SC1945 | 10.00 | CTC3005 | 70.00 |
| 2N3959 | 3.85 | 01-80703T4 | 65.00 | 2SC1946 | 40.00 | CTC3460 | 20.00 |
| 2N4012 | 11.00 | 35C05 | 15.00 | 2SC1947 | 10.00 | DV2820S | 25.00 |
| 2N4037 | 2.00 | 102-1 | 28.00 | 2SC1970 | 2.50 | DXL1003P70 | 22.00 |
| 2N4041 | 14.00 | 103-1 | 28.00 | 2SC1974 | 4.00 | DXL2001P70 | 19.00 |
| 2N4072 | 1.80 | 103-2 | 28.00 | 2SC2166 | 5.50 | DXL2002P70 | 14.00 |
| 2N4080 | 4.53 | 104P1 | 18.00 | 2SC2237 | 32.00 | DXL3501AP100F | 47.00 |
| 2N4127 | 21.00 | 163P1 | 10.00 | 2SC2695 | 47.00 | EFJ4015 | 12.00 |
| 2N4416 | 2.25 | 181-3 | 15.00 | A2X1698 | POR | EFJ4017 | 24.00 |
| 2N4427 | 1.25 | 210-2 | 10.00 | A3-12 | 14.45 | EFJ4021 | 24.00 |
| 2N4428 | 1.85 | 269-1 | 18.00 | A50-12 | 24.00 | EFJ4026 | 35.00 |
| 2N4430 | 11.80 | 281-1 | 15.00 | A209 | 10.00 | EN15745 | 20.00 |
| 2N4927 | 3.90 | 282-1 | 30.00 | A283 | 6.00 | FJ9540 | 16.00 |
| 2N4957 | 3.45 | 482 | 7.50 | A283B | 6.00 | FSX52WF | 58.00 |
| 2N4959 | 2.30 | 564-1 | 25.00 | A1610 | 19.00 | G65739 | 25.00 |
| 2N5016 | 18.40 | 698-3 | 15.00 | AF102 | 2.50 | G65386 | 25.00 |
| 2N5026 | 15.00 | 703-1 | 15.00 | AFY12 | 2.50 | GMO290A | 2.50 |
| 2N5070 | 18.40 | 704 | 4.00 | AR7115 | 20.00 | HEP76 | 4.95 |
| 2N5090 | 13.80 | 709-2 | 11.00 | AT41435-5 | 6.35 | HEPS3002 | 11.40 |
| 2N5108 | 3.45 | 711 | 4.00 | B2-8Z | 10.70 | HEPS3003 | 30.00 |
| 2N5109 | 1.70 | 733-2 | 15.00 | B3-12 | 10.85 | HEPS3005 | 10.00 |
| 2N5160 | 3.45 | 798-2 | 25.00 | B12-12 | 15.70 | HEPS3006 | 19.90 |
| 2N5177 | 21.62 | 3421 | 28.00 | BAL0204125 | 152.95 | HEPS3007 | 25.00 |
| 2N5179 | 1.04 | 3683P1 | 15.00 | BF25-35 | 56.25 | HEPS3010 | 11.34 |
| 2N5216 | 56.00 | 3992 | 25.00 | B40-12 | 19.25 | HF8003 | 10.00 |
| 2N5470 | 75.00 | 4164P1 | 15.00 | B70-12 | 55.00 | HFET2204 | 112.00 |
| 2N5583 | 3.45 | 4243P1 | 28.00 | BF272A | 2.50 | HP35821 | 38.00 |
| 2N5589 | 9.77 | 4340P3 | 18.00 | BFQ85 | 2.50 | HP35826B | 32.00 |
| 2N5590 | 10.92 | 4387P1 | 27.50 | BFR21 | 2.50 | HP35826E | 32.00 |
| 2N5591 | 13.80 | 7104-1 | 28.00 | BFR90 | 1.00 | HP35831E | 30.00 |
| 2N5596 | 99.00 | 7249-2 | 10.50 | BFR91 | 1.65 | HP35832E | 50.00 |
| 2N5636 | 12.00 | 7283-1 | 37.50 | BFR99 | 2.50 | HP35833E | 50.00 |
| 2N5637 | 15.50 | 7536-1 | 30.00 | BFT12 | 2.50 | HP35859E | 75.00 |
| 2N5641 | 12.42 | 7794-1 | 10.50 | BFW16A | 2.50 | HP35866E | 44.00 |
| 2N5642 | 14.03 | 7795 | 15.00 | BFW17 | 2.50 | HXTR2101 | 44.00 |
| 2N5643 | 25.50 | 7795-1 | 15.00 | BFW92 | 1.50 | HXTR3101 | 7.00 |
| 2N5645 | 13.80 | 7796-1 | 24.00 | BFX44 | 2.50 | HXTR5101 | 31.00 |
| 2N5646 | 20.70 | 7797-1 | 36.00 | BFX48 | 2.50 | HXTR6104 | 68.00 |
| 2N5651 | 11.05 | 40081 RCA | 5.00 | BFX65 | 2.50 | HXTR6105 | 31.00 |
| 2N5691 | 18.00 | 40279 RCA | 10.00 | BFX84 | 2.50 | HXTR6106 | 33.00 |
| 2N5764 | 27.00 | 40280 RCA | 4.62 | BFX85 | 2.50 | J310 | 1.00 |
| 2N5836 | 3.45 | 40281 RCA | 10.00 | BFX86 | 2.50 | JO2000 | 10.00 |
| 2N5842 | 8.45 | 40282 RCA | 20.00 | BFX89 | 1.00 | JO2001 | 25.00 |
| 2N5847 | 19.90 | 40290 RCA | 2.80 | BFY11 | 2.50 | JO4045 | 24.00 |
| 2N5849 | 20.00 | 40292 RCA | 13.05 | BFY18 | 2.50 | KD5522 | 25.00 |
| 2N5913 | 3.25 | 40294 RCA | 2.50 | BFY19 | 2.50 | KJ5522 | 25.00 |
| 2N5916 | 36.00 | 40341 RCA | 21.00 | BFY39 | 2.50 | M1106 | 13.75 |

Toll Free Number
800-528-0180
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: 602-265-0731

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

MHz electronics

3802 North 27th Ave., Phoenix, AZ 85017

RF TRANSISTORS (CONTINUED)

| | | | | | | | |
|-------------|---------|------------------|---------|--------------|----------|-----------|---------|
| M1107 | \$16.75 | MRF458 | \$20.70 | NEO2160ER | \$100.00 | SD1009 | \$15.00 |
| M1131 | 5.15 | MRF464 | 25.30 | NEO21350 | 5.30 | SD1009-2 | 15.00 |
| M1132 | 7.25 | MRF466 | 18.97 | NE13783 | 61.00 | SD1012 | 10.00 |
| M1134 | 13.40 | MRF472 | 1.50 | NE21889 | 43.00 | SD1012-3 | 10.00 |
| M9116 | 29.10 | MRF475 | 3.10 | NE57835 | 5.70 | SD1012-5 | 10.00 |
| M9579 | 6.00 | MRF476 | 3.16 | NE64360ER-A | 100.00 | SD1013 | 10.00 |
| M9580 | 7.95 | MRF477 | 20.00 | NE64480 (B) | 94.00 | SD1013-3 | 10.00 |
| M9587 | 7.00 | MRF479 | 8.05 | NE73436 | 2.50 | SD1013-7 | 10.00 |
| M9588 | 5.20 | MRF492 | 23.00 | NE77362ER | 100.00 | SD1016 | 15.00 |
| M9622 | 5.95 | MRF502 | 1.04 | NE98260ER | 100.00 | SD1016-5 | 15.00 |
| M9623 | 7.95 | MRF503 | 6.00 | PRT8637 | 25.00 | SD1018-4 | 13.00 |
| M9624 | 9.95 | MRF504 | 7.00 | PT3127A | 5.00 | SD1018-6 | 13.00 |
| M9625 | 15.95 | MRF509 | 5.00 | PT3127B | 5.00 | SD1018-7 | 13.00 |
| M9630 | 14.00 | MRF511 | 10.69 | PT3127C | 20.00 | SD1018-15 | 13.00 |
| M9740 | 27.90 | MRF515 | 2.00 | PT3127D | 20.00 | SD1020-5 | 10.00 |
| M9741 | 27.90 | MRF517 | 2.00 | PT3127E | 20.00 | SD1028 | 15.00 |
| M9755 | 16.00 | MRF525 | 3.45 | PT3190 | 20.00 | SD1030 | 12.00 |
| M9780 | 5.50 | MRF559 | 1.76 | PT3194 | 20.00 | SD1030-2 | 12.00 |
| M9827 | 11.00 | MRF587 | 11.00 | PT3195 | 20.00 | SD1040 | 5.00 |
| M9848 | 35.00 | MRF605 | 20.00 | PT3537 | 7.80 | SD1040-2 | 20.00 |
| M9850 | 13.50 | MRF618 | 25.00 | PT4166E | 20.00 | SD1040-4 | 10.00 |
| M9851 | 20.00 | MRF626 | 12.00 | PT4176D | 25.00 | SD1040-6 | 5.00 |
| M9860 | 8.25 | MRF628 | 8.65 | PT4186B | 5.00 | SD1043 | 12.00 |
| M9887 | 2.80 | MRF629 | 3.45 | PT4209 | 25.00 | SD1043-1 | 10.00 |
| M9908 | 6.95 | MRF641 | 25.30 | PT4209C/5645 | 25.00 | SD1045 | 3.75 |
| M9965 | 12.00 | MRF644 | 27.60 | PT4556 | 24.60 | SD1049-1 | 2.00 |
| MM1500 | 25.00 | MRF646 | 29.90 | PT4570 | 7.50 | SD1053 | 4.00 |
| MM1550 | 10.00 | MRF648 | 33.35 | PT4577 | 20.00 | SD1057 | 10.00 |
| MM1552 | 50.00 | MRF816 | 15.00 | PT4590 | 5.00 | SD1065 | 4.75 |
| MM1553 | 50.00 | MRF823 | 20.00 | PT4612 | 20.00 | SD1068 | 15.00 |
| MM1607 | 8.45 | MRF846 | 44.85 | PT4628 | 20.00 | SD1074-2 | 18.00 |
| MM1614 | 10.00 | MRF892 | 35.50 | PT4640 | 20.00 | SD1074-4 | 28.00 |
| MM1810 | 15.00 | MRF894 | 46.00 | PT4642 | 20.00 | SD1074-5 | 28.00 |
| MM1810 | 15.00 | MRF901 3 Lead | 1.00 | PT5632 | 4.70 | SD1076 | 18.50 |
| MM1943 | 1.80 | MRF901 4 Lead | 2.00 | PT5749 | 25.00 | SD1077 | 4.00 |
| MM2608 | 5.00 | MRF902/2N6603JAN | 15.00 | PT6612 | 25.00 | SD1077-4 | 4.00 |
| MM3375A | 17.10 | MRF902B | 18.40 | PT6619 | 20.00 | SD1077-6 | 4.00 |
| MM4429 | 10.00 | MRF904 | 2.30 | PT6708 | 25.00 | SD1078-6 | 24.00 |
| MM8000 | 1.15 | MRF905 | 2.55 | PT6709 | 25.00 | SD1080-7 | 7.50 |
| MM8006 | 2.30 | MRF911 | 2.50 | PT6720 | 25.00 | SD1080-8 | 6.00 |
| MM8011 | 25.00 | MRF965 | 2.55 | PT8510 | 15.00 | SD1080-9 | 3.00 |
| MPSU31 | 1.01 | MRF966 | 3.55 | PT8524 | 25.00 | SD1084 | 8.00 |
| MRA2023-1.5 | 42.50 | MRF1000MA | 32.77 | PT8609 | 25.00 | SD1087 | 15.00 |
| MRF134 | 10.50 | MRF1004M | 31.05 | PT8633 | 25.00 | SD1088 | 22.00 |
| MRF136 | 16.00 | MRF2001 | 41.74 | PT8639 | 25.00 | SD1088-8 | 22.00 |
| MRF171 | 35.00 | MRF2005 | 54.97 | PT8659 | 25.00 | SD1089-5 | 15.00 |
| MRF208 | 11.50 | MRF5176 | 24.00 | PT8679 | 25.00 | SD1090 | 15.00 |
| MRF212 | 16.10 | MRF8004 | 2.10 | PT8708 | 20.00 | SD1094 | 15.00 |
| MRF221 | 10.00 | MSC1720-12 | 225.00 | PT8709 | 20.00 | SD1095 | 15.00 |
| MRF223 | 13.00 | MSC1821-3 | 125.00 | PT8727 | 29.00 | SD1098-1 | 30.00 |
| MRF224 | 13.50 | MSC1821-10 | 225.00 | PT8731 | 25.00 | SD1100 | 5.00 |
| MRF227 | 3.45 | MSC2001 | 30.00 | PT8742 | 19.10 | SD1109 | 18.00 |
| MRF230 | 2.00 | MSC2010 | 93.00 | PT8787 | 25.00 | SD1115-2 | 7.50 |
| MRF231 | 10.00 | MSC2223-10 | 245.00 | PT8828 | 25.00 | SD1115-3 | 7.50 |
| MRF232 | 12.07 | MSC2302 | POR | PT9700 | 25.00 | SD1115-7 | 2.10 |
| MRF237 | 3.15 | MSC3000 | 35.00 | PT9702 | 25.00 | SD1116 | 5.00 |
| MRF238 | 13.80 | MSC3001 | 38.00 | PT9783 | 16.50 | SD1118 | 22.00 |
| MRF239 | 17.25 | MSC72002 | POR | PT9784 | 32.70 | SD1119 | 5.00 |
| MRF245 | 35.65 | MSC73001 | POR | PT9790 | 56.00 | SD1124 | 50.00 |
| MRF247 | 31.00 | MSC80064 | 35.00 | PT31083 | 20.00 | SD1132-1 | 15.00 |
| MRF304 | 36.00 | MSC80091 | 10.00 | PT31962 | 20.00 | SD1132-4 | 12.00 |
| MRF306 | 50.00 | MSC80099 | 3.00 | PTX6680 | 20.00 | SD1133 | 9.50 |
| MRF313 | 11.15 | MSC80593 | POR | RE3754 | 25.00 | SD1133-1 | 10.00 |
| MRF314 | 29.21 | MSC80758 | POR | RE3789 | 25.00 | SD1134-1 | 2.50 |
| MRF315 | 28.86 | MSC82001 | 33.00 | RF35 | 16.00 | SD1134-4 | 12.00 |
| MRF316 | 55.43 | MSC82014 | 33.00 | RF85 | 17.50 | SD1134-17 | 12.00 |
| MRF317 | 63.94 | MSC82020M | 130.00 | RF110 | 21.00 | SD1135 | 10.25 |
| MRF412 | 18.00 | MSC82030 | 33.00 | S50-12 | 23.80 | SD1135-3 | 12.00 |
| MRF420 | 20.12 | MSC83001 | 40.00 | S3006 | 15.00 | SD1136 | 12.50 |
| MRF421 | 25.00 | MSC83003 | 82.00 | S3007 | 10.00 | SD1136-2 | 12.50 |
| MRF422 | 38.00 | MSC83005 | 70.00 | S3031 | 22.00 | SD1143-1 | 10.00 |
| MRF427 | 17.25 | MSC83026 | POR | SCA3522 | 5.00 | SD1143-3 | 17.00 |
| MRF428 | 63.00 | MSC83303 | POR | SCA3523 | 5.00 | SD1144 | 4.00 |
| MRF433 | 12.07 | MSC84900 | 60.00 | SD345 | 5.00 | SD1145-5 | 15.00 |
| MRF449/A | 12.65 | MT4150 | 14.40 | SD445 | 5.00 | SD1146 | 15.00 |
| MRF450/A | 14.37 | MT5126 | 25.00 | SD1004 | 15.00 | SD1147 | 15.00 |
| MRF452/A | 17.00 | MT5596(2N) | 99.00 | SD1007 | 15.00 | SD1188 | 10.00 |
| MRF453/A | 18.40 | MT5768(2N) | 95.00 | SD1007-2 | 15.00 | SD1189 | 24.00 |
| MRF454/A | 20.12 | MT8762 | 25.00 | SD1007-4 | 15.00 | SD1200 | 1.50 |
| MRF455/A | 16.00 | NEO2136 | 2.00 | SD1007-5 | 15.00 | SD1201-2 | 15.00 |

Toll Free Number
800-528-0180
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."


For information call: 602-265-0731

MHz electronics


3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

E.F. JOHNSON ROLLER INDUCTORS

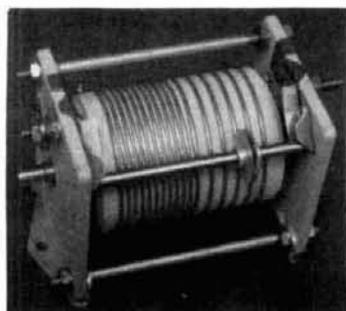

MODEL 229-0201-01
10UH at 3AMPS MAX. \$36.99

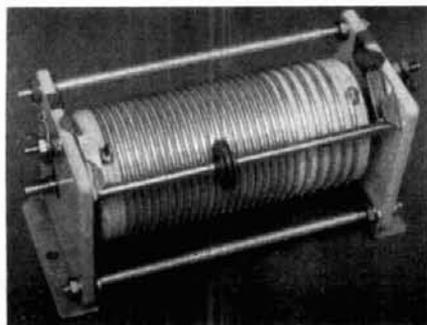

MODEL 229-0202-01
18UH at 5AMPS MAX. \$44.99

UNELCO, SEMCO, ARCO METAL CLAD MICA CAPACITORS

| Standard Size | | | | Micro Size | | |
|---------------|------|----|-----|------------|----|----|
| 3.9 | 14 | 33 | 62 | 175 | 5 | 25 |
| 4.7 | 15 | 34 | 68 | 180 | 6 | 27 |
| 5 | 18 | 36 | 75 | 200 | 7 | 33 |
| 5.1 | 20 | 38 | 80 | 220 | 8 | 36 |
| 6.8 | 22 | 39 | 82 | 240 | 9 | 51 |
| 7 | 24 | 40 | 100 | 250 | 12 | 62 |
| 8.2 | 25 | 43 | 110 | 300 | 15 | |
| 9.1 | 27 | 44 | 120 | 360 | 16 | |
| 10 | 27.5 | 47 | 123 | 470 | 18 | |
| 11 | 28 | 50 | 125 | 500 | 20 | |
| 12 | 30 | 51 | 140 | 820 | 22 | |
| 13 | 32 | 56 | 150 | 1000 | 24 | |

*****NOTE ALL VALUES LISTED IN PICO FARAD*****
 PRICE INFORMATION
 1 to 10 \$.90ea. 11 to 51 \$.80ea. 52 to 102 \$.70ea.
 103 and up call

GOULD NI-CAD BATTERIES

| | | | |
|-------------------------|-----|---|---------|
| AA size 1.25v at 500mah | new | a | \$ 1.99 |
| D size 1.25v at 4 AMPHR | new | h | 7.49 |

GENERAL ELECTRIC NI-CAD BATTERIES

| | | | |
|------------------------------------|------|---|------|
| AA size 1.25v at 500mah | new | a | 2.99 |
| 195194 3.75v at 100mah | new | | 1.99 |
| AA size 3.75v at 100mah | new | a | 2.99 |
| AA size pack of 10 12.5v at 450mah | used | a | 5.99 |
| Sub C Pack of 10 12.5v at 2.5Amphr | new | c | 9.99 |

UNION CARBIDE NI-CAD BATTERIES

| | | | |
|------------------------|-----|---|------|
| 193817 3.75v at 225mah | new | a | 2.99 |
|------------------------|-----|---|------|

GLOBE GEL-CELL BATTERIES

| | | | |
|------------------------|-----|---|-------|
| 2v at 8AMPHR GC280 | new | g | 5.99 |
| 12v at 20AMPHR GC12200 | new | g | 49.99 |
| 12v at 23AMPHR GC12300 | new | g | 54.99 |

EAGLE PICHER GEL-CELL BATTERIES

| | | | |
|--------------------------|-----|---|-------|
| 12v at 1.5AMPHR CF12V1.5 | new | d | 11.99 |
|--------------------------|-----|---|-------|

GATES SEALED RECHARGEABLE LEAD ACID BATTERIES AND PACKS

| | | | |
|---------------------------|------|---|-------|
| 2v at 2.5AMPHR D Cell | new | b | 5.99 |
| 8v at 5AMPHR 4 X Cell | used | f | 14.99 |
| 12v at 2.5AMPHR 6 D Cells | new | f | 24.99 |
| 18v at 2.5AMPHR 9 D Cells | new | f | 29.99 |

GENERAL ELECTRIC SEALED RECHARGEABLE LEAD ACID BATTERIES AND PACKS

| | | | |
|---------------------------|------|---|-------|
| 6v at 2.5AMPHR 3 D Cells | used | e | 10.00 |
| 12v at 2.5AMPHR 6 D Cells | used | e | 19.99 |
| 12v at 5AMPHR 6 X Cells | used | e | 24.99 |


NI-CAD BATTERY CHARGERS



UNIVERSAL CHARGER \$19.99



MALLORY CHARGER \$23.99

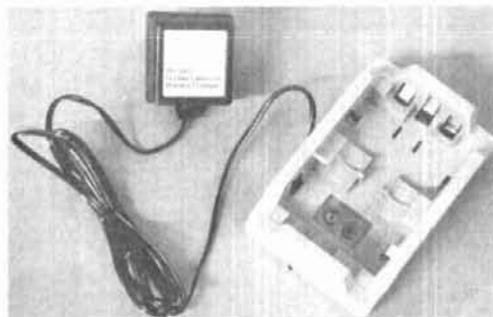

EVEREADY CHARGER \$9.99



Toll Free Number
800-528-0180
(For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: 602-265-0731

MHz electronics

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

RF Transistors (continued)


| | | | | | | | | | | | | | | | |
|-----------|---------|----------|---------|----------|---------|----------------|---------|-------------|-------|-----------|--------|-----------|--------|-------------|--------|
| SD1202 | \$10.00 | SD1304-8 | \$ 2.50 | SD1451-2 | \$15.00 | SRF1427 | \$50.00 | SD1244H12 | 25.00 | SD1410-8 | 21.00 | SD1536-1 | 41.00 | SRF2917 | 15.00 |
| SD1212-8 | 4.95 | SD1305 | 3.00 | SD1452 | 20.00 | SRF1431 | 40.00 | SD1413-1 | 18.00 | SD1539H | 100.00 | SD1539H | 100.00 | SRF2918 | 15.00 |
| SD1212-11 | 4.95 | SD1307 | 3.00 | SD1452-4 | 24.00 | SRF1834 | 40.00 | SD1416 | 28.00 | SD1542H1 | 170.00 | SRF2919 | 170.00 | SRF3071PF | 50.00 |
| SD1214-16 | 4.95 | SD1308 | 1.00 | SD1454 | 20.00 | SRF2093-3 | 60.00 | SD1422-2 | 24.00 | SD1544 | 26.00 | SD1544 | 26.00 | SRF3071PF | 50.00 |
| SD1214-7 | 5.00 | SD1311 | 1.00 | SD1454-1 | 48.00 | SRF2092 | 50.00 | SD1428 | 24.00 | SD1545 | 31.00 | SD1545 | 31.00 | SS4006 | 25.00 |
| SD1214-11 | 5.00 | SD1317 | 8.00 | SD1477 | 15.00 | SRF2147 | 22.00 | SD1428-6084 | 12.00 | SD1548H1 | 55.00 | SD1548H1 | 55.00 | SS4132 | 15.00 |
| SD1216 | 12.00 | SD1319 | 2.50 | SD1478 | 21.00 | SRF2225 | 15.00 | SD1429-2 | 15.00 | SD1561 | 29.00 | SD1561 | 29.00 | TA7686 | 15.00 |
| SD1219-4 | 15.00 | SD1345-6 | 5.00 | SD1480 | 53.00 | SRF2264 | 25.00 | SD1429-3 | 14.30 | SD1574-1 | 6.85 | SD1574-1 | 6.85 | TA8559 | 15.00 |
| SD1219-5 | 15.00 | SD1347-1 | 1.00 | SD1484 | 1.50 | SRF2265 | 100.00 | SD1429-5 | 15.00 | SD1575 | 6.95 | SD1575 | 6.95 | TAB561 | 15.00 |
| SD1219-8 | 15.00 | SD1365-1 | 2.50 | SD1484-5 | 1.50 | SRF2281 | 5.00 | SD1430 | 12.00 | SFA557 | 25.00 | SFA557 | 25.00 | TAB562 | 15.00 |
| SD1220 | 8.00 | SD1365-5 | 2.50 | SD1484-6 | 1.50 | SRF2373 | 15.00 | SD1430-2 | 18.00 | SK3048 | 5.00 | SK3048 | 5.00 | TAB563 | 15.00 |
| SD1220-1 | 9.50 | SD1375 | 7.50 | SD1484-7 | 1.50 | SRF2347 | 50.00 | SD1434 | 28.00 | SL501-59 | 15.00 | SL501-59 | 15.00 | TAB564 | 15.00 |
| SD1220-9 | 8.00 | SD1375-6 | 7.50 | SD1488 | 22.85 | SRF2356 | 38.00 | SD1434-5 | 28.00 | SL501-173 | 15.00 | SL501-173 | 15.00 | TAB894 | 15.00 |
| SD1222-8 | 16.00 | SD1379 | 15.00 | SD1488-1 | 28.00 | SRF2378 | 16.00 | SD1434-9 | 28.00 | SRF714 | 5.00 | SRF714 | 5.00 | T15189 | 3.55 |
| SD1222-11 | 7.50 | SD1380-1 | 1.00 | SD1488-7 | 22.00 | SRF2572 | 25.00 | SD1438 | 26.00 | SRF112 | 15.00 | SRF112 | 15.00 | TP312 | 2.50 |
| SD1224-10 | 18.00 | SD1380-3 | 1.00 | SD1488-8 | 28.00 | SRF2584 | 40.00 | SD1441 | 56.00 | SRF395 | 50.00 | SRF395 | 50.00 | TP1014 | 5.00 |
| SD1225 | 18.00 | SD1380-7 | 1.00 | SD1499-1 | 36.00 | SRF2597 | 25.00 | SD1442 | 15.00 | SRF750 | 36.00 | SRF750 | 36.00 | TP1028 | 15.00 |
| SD1225-1 | 15.00 | SD1405 | 21.00 | SD1511H1 | 75.00 | SRF2741 | 40.00 | SD1444 | 3.25 | SRF79H | 20.00 | SRF79H | 20.00 | TR3 | 5.00 |
| SD1229-7 | 10.95 | SD1408 | 25.00 | SD1520-2 | 18.00 | SRF2747 | 40.00 | SD1444-8 | 3.25 | SRF887K3 | 2.50 | SRF887K3 | 2.50 | TKFP2201/HF | 450.00 |
| SD1229-16 | 10.95 | SD1409 | 18.00 | SD1522-4 | 33.00 | SRF2767H | 40.00 | SD1444-9 | 3.25 | SRF999K | 15.00 | SRF999K | 15.00 | V222-2 | 25.00 |
| SD1232 | 4.00 | SD1410 | 18.00 | SD1528-1 | 24.00 | SRF2821 | 25.00 | SD1446 | 4.03 | SRF1005 | 50.00 | SRF1005 | 50.00 | V4101E | 20.00 |
| SD1240-8 | 15.00 | SD1410-3 | 21.00 | SD1528-3 | 14.00 | SRF2822/2866D3 | 11.50 | SD1450-1 | 28.00 | SRF1018 | 5.00 | SRF1018 | 5.00 | V415 | 5.00 |
| SD1244-1 | 14.00 | SD1410-6 | 21.00 | SD1530-2 | 38.00 | SRF2857 | 20.00 | SD1451 | 3.00 | SRF1074 | 50.00 | SRF1074 | 50.00 | | |

Relays

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

• \$7.99 or 2 For \$13.99 or 10 For \$50.00

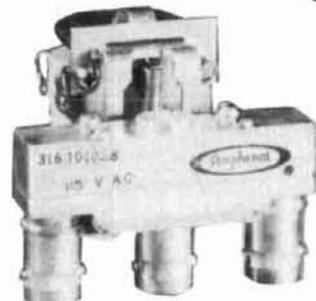\$8.99 or 2 For \$15.99 or 10 For \$60.00



Amphenol
Part # 316-10102-8
115Vac Type BNC DC to 3 GHz.

\$29.99

COAXIAL RELAY SWITCHES SPDT

FXR
Part # 300-11182
120Vac Type BNC DC to 4 GHz.
FSN 5985-543-1225

\$39.99



FXR
Part # 300-11173
120Vac Type BNC Same
FSN 5985-543-1850

\$39.99

TERMS: DOMESTIC: Prepaid, C.O.D. or Credit Card
FOREIGN: Prepaid only, U.S. Funds, Money Order, or Cashier's Check Only.

C.O.D.: Acceptable by telephone or mail. Payment from customer will be Cash, Money Order, or Cashier's Check. We are sorry but we cannot accept personal checks for C.O.D.'s. C.O.D.'s are shipped by air only and thru United Parcel Service.

CONFIRMING ORDERS: We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, the customer will be held responsible for any charges incurred, plus a 15% restock charge on the returned parts.

CREDIT CARDS: We are now accepting MASTERCARD, VISA, AND AMERICAN EXPRESS

DATA SHEETS: When we have data sheets in stock on devices we will supply them with the order.

DEFECTIVE MATERIALS: All claims for defective materials must be made within 30 DAYS after receipt of the parcel. All claims must include the defective material (for testing purposes), a copy of our invoice, and a return authorization number which must be obtained prior to shipping the merchandise back to us. This can be obtained by calling (602) 242-8916 or sending us a postcard. Due to Manufacturer warranties we are unable to replace or issue credit on items which have been soldered to or have been altered in any way. All return items must be packed properly or it will void all warranties. We do not assume responsibility for shipping and handling charges incurred.

DELIVERY: Orders are usually shipped the same day they are placed or the next business day, unless we are out of stock on an item. The customer will be notified by post card if we are going to backorder the item. Our normal shipping method is UPS or U.S. Mail depending on size or the weight of the package. Test Equipment is shipped only by air and is freight collect, unless prior arrangements have been made and approved.

FOREIGN ORDERS: All foreign orders must be prepaid with a Cashier's Check, or Money Order made out in U.S. FUNDS ONLY. We are sorry but C.O.D. is not available to foreign countries and letters of credit are unacceptable as a form of payment. Further information is available on request.

HOURS: Monday thru Friday 8:30 a.m. to 5:00 p.m. Saturdays 8:30 a.m. to 4:00 p.m.

INSURANCE: Please include 25¢ for each additional \$100.00 over \$100.00. UPS ONLY. All insured packages are shipped thru UPS only. If you wish to have it shipped through the post office there is a \$5.00 fee which is additional to the shipping, handling and insurance.

OPEN ACCOUNTS: We regret that we do not issue open accounts.

ORDER FORMS: New order forms are included with each order for your convenience. Additional order forms are available on request.

PARTS: We reserve the right to substitute or replace any item with a part of equal or comparable specification.

POSTAGE: Minimum shipping and handling in the U.S., Canada, and Mexico is \$3.00 for ground shipments, all other countries is \$5.50. Air rates are available at the time of your order. All foreign orders please include 25% of the ordered amount for shipping and handling. C.O.D.'s are shipped AIR ONLY.

PREPAID ORDERS: Orders must be accompanied by a check.

PRICES: Prices are subject to change without notice.

PURCHASE ORDERS: We accept purchase orders only when they are accompanied by a check.

RESTOCK CHARGES: If parts are returned to MHZ ELECTRONICS, INC. due to customer error, the customer will be held responsible for all fees incurred and will be charged a 15% RESTOCK CHARGE with the remainder in CREDIT ONLY. The following must accompany any return: A copy of our invoice, return authorization number which must be obtained prior to shipping the merchandise can be obtained by calling (602) 242-8916 or notifying us by post card. Return authorizations will not be given out on our 800 number.

SALES TAX: ARIZONA residents must add 6% sales tax, unless a signed ARIZONA resale tax card is currently on file with us. All orders placed by persons outside of ARIZONA, but delivered to persons in ARIZONA are subject to the 6% sales tax.

SHORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 DAYS of receipt of parcel. Claims must include a copy of our invoice, along with a return authorization number which can be obtained by contacting us at (602) 242-8916 or sending a post card. Authorizations cannot be on our 800 number. All items must be properly packed. If items are not properly packed make sure to contact the carrier so that they can come out and inspect the package before it is returned to us. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY (800) 528-0180. INFORMATION CALLS ARE TAKEN ON (602) 242-8916 or (602) 242-3037.

MHZ

electronics

3802 North 27th Ave., Phoenix, AZ 85017



For information call: 602-265-0731

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

Toll Free Number
800-528-0180
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

HAM MART

Ham Radio's guide to help you find your local

California

C & A ROBERTS, INC.
18511 HAWTHORN BLVD.
TORRANCE, CA 90504
213-370-7451

24 Hour: 800-421-2258
Not The Biggest, But The Best —
Since 1962.

FONTANA ELECTRONICS
8628 SIERRA AVENUE
FONTANA, CA 92335
714-822-7710
714-822-7725

The Largest Electronics Dealer in San Bernardino County.

JUN'S ELECTRONICS
3919 SEPULVEDA BLVD.
CULVER CITY, CA 90230
213-390-8003
800-882-1343 Trades
Habla Espanol

Connecticut

HATRY ELECTRONICS
500 LEDYARD ST. (SOUTH)
HARTFORD, CT 06114
203-527-1881
Call today. Friendly one-stop shopping
at prices you can afford.

Delaware

**AMATEUR & ADVANCED
COMMUNICATIONS**
3208 CONCORD PIKE
WILMINGTON, DE 19803
(302) 478-2757
Delaware's Friendliest Ham Store.

DELAWARE AMATEUR SUPPLY
71 MEADOW ROAD
NEW CASTLE, DE 19720
302-328-7728
800-441-7008
Icom, Ten-Tec, Microlog, Yaesu,
Kenwood, Santec, KDK, and more.
One mile off I-95, no sales tax.

Florida

AMATEUR ELECTRONIC SUPPLY
1898 DREW STREET
CLEARWATER, FL 33575
813-461-4267
Clearwater Branch
West Coast's only full service
Amateur Radio Store.
Hours M-F 9-5:30, Sat. 9-3

AMATEUR ELECTRONIC SUPPLY
621 COMMONWEALTH AVE.
ORLANDO, FL 32803
305-894-3238
Fla. Wats: 1 (800) 432-9424
Outside Fla: 1 (800) 327-1917
Hours M-F 9-5:30, Sat. 9-3

AMATEUR RADIO CENTER, INC.
2805 N. E. 2ND AVENUE
MIAMI, FL 33137
305-573-8383
The place for great dependable
names in Ham Radio.

Hawaii

HONOLULU ELECTRONICS
819 KEEAUMOKU STREET
HONOLULU, HI 96814
(808) 949-5564
Serving Hawaii & Pacific area for 51
years. Complete lines of Amateur equip-
ment, accessories and parts.

Illinois

ERICKSON COMMUNICATIONS, INC.
5456 N. MILWAUKEE AVE.
CHICAGO, IL 60630
312-631-5181
Hours: 9:30-5:30 Mon, Tu, Wed & Fri;
9:30-8:00 Thurs; 9:00-3:00 Sat.

Indiana

THE HAM STATION
808 NORTH MAIN STREET
EVANSVILLE, IN 47710
812-422-0231
Discount prices on Ten-Tec, Cubic,
Hy-Gain, MFJ, Azden, Kantronics,
Santec and others.

Massachusetts

James Millen Components by
ANTENNAS ETC.
16 HANSOM ROAD
ANDOVER, MA 01810
617-475-7831
Bezels, binding posts, capacitors, con-
densers, chokes, coils, ceramics, H.V.
connectors, plate caps, hardware
knobs, dials, scopes and grid dippers.
Inquire SASE or visit.

TEL-COM, INC.
675 GREAT ROAD, RTE. 119
LITTLETON, MA 01460
617-486-3400
617-486-3040
The Ham Store of New England
You Can Rely On.

Michigan

ENCON PHOTOVOLTAICS
Complete Photovoltaic Systems
27600 Schoolcraft Rd.
Livonia, Michigan 48150
313-523-1850
Amateur Radio, Repeaters, Satellite,
Computer applications.
Call Paul WD8AHO

Nevada

AMATEUR ELECTRONIC SUPPLY
1072 N. RANCHO DRIVE
LAS VEGAS, NV 89106
702-647-3114
Dale Porray "Squeak," AD7K
Outside Nev: 1 (800) 634-6227
Hours M-F 9-5:30, Sat. 9-3

JUN'S ELECTRONICS
460 E. PLUMB LANE — 107
RENO, NV 89502
702-827-5732
Outside Nev: 1 (800) 648-3962
Icom — Yaesu Dealer

NEW YORK

ADIRONDACK ELECTRONICS, INC.
1991 CENTRAL AVENUE
ALBANY, NY 12205
518-456-0203
Amateur Radio for the Northeast since
1943.

BARRY ELECTRONICS
512 BROADWAY
NEW YORK, NY 10012
212-925-7000
New York City's Largest Full Service
Ham and Commercial Radio Store.

VHF COMMUNICATIONS
915 NORTH MAIN STREET
JAMESTOWN, NY 14701
716-664-6345
Call after 7 PM and save! Supplying all
of your Amateur needs. Featuring ICOM
"The World System." Western New
York's finest Amateur dealer.

Dealers: YOU SHOULD BE HERE TOO!
Contact Ham Radio now for complete details.

MEMO

from the desk of
THE PUBLISHER

Skip Tenney, W1NLB

The Ham Radio Publishing Group

IS YOUR HAMSHACK COMPUTERIZED?

The modern home computer, with some priced at less than \$150, is certainly one of the most exciting and challenging new items to be offered to the Radio Amateur in many years. These machines are such a logical extension of our Amateur activities, that it's a wonder that it has taken some of us as long as it has to get involved.

Thousands of hams are using these new machines to do everything from handling their logging and QSLing and as CW, RTTY and ASCII terminals to doing many of their routine station calculations in areas such as antenna and circuit design. Others are now able to do their own propagation forecasting with MUF and greyline programs. It's all mindboggling. We have just begun to see the tip of what is yet to come in the months and years ahead.

Whether you are merely contemplating the purchase of your first computer or you are an experienced user, Ham Radio's Bookstore wants to help you in this important new area. We have selected a number of the more interesting new programs which have been written for Amateur use, along with some excellent books to help you learn more.

Sincerely,

Skip Tenney, W1NLB

ham radio magazine

BOOKSTORE



NOW WITH COMPUTER DISKS

COMPUTER PROGRAMS FOR THE RADIO AMATEUR

by Wayne Overbeck, N6NB, and
Jim Steffen, KC6A

Here's the first source book of computer programs for the Radio Amateur. Besides covering computer basics, this book gives you programs that will help you log, determine sunrise/sunset times, track the Moon's path across the sky, use Greyline propagation and set up record systems for WAS, DXCC and VUCC, or any other award. You can either buy the book alone or you can buy the book with the programs already on disk. Take full advantage of your computer with this well written source book. ©1984, 1st edition, 327 pages.

Program Listing

- Data Base Mgmt.**
Logs, Awards Data Base, Gridlocator
 - Latitude/Longitude Programs**
Data File, Beamheadings, DX Display, Sunrise Chart, Greyline, DX Checker
 - Contest and Duping**
Dupechecker, General Contest Logger, Field Day Logger, Sweepstakes Logger, Log Print
 - Antenna Programs**
Antenna Scaler, Matching Evaluator, Vertical Pattern Plotter
 - EME**
EME System Calculator, Sky Locator, Moontracker
- HA-0657 **Softbound \$16.95**
- HA-0657 with program disk **\$29.95**
specify computer (see list below)
- Program disk alone **\$19.95**
- Programs available for: Apple II (DOS and CP/M), IBM (DOS), TRS-80 Model I and Model III and Commodore C-64. Please mark your order with the program disk you want.

HAM DATA PROGRAMS FOR THE COMMODORE C-64

by NN4U

Ham Data Antenna Design

Forget longhand calculations when you have this program! This self-prompting program covers dipoles, Yagis, long wires, rhombics, quads, loops, verticals and other antennas. You simply enter the frequency you are designing an antenna for, the antenna you want to make, and the computer will give you all the initial design specifications you need. The results can be stored on disk for permanent retention.

HD-AD **\$9.95**

Ham Data Contest Log

This disk contains four different contest programs; ARRL Sweepstakes, Field Day, Universal WW Contest log, plus a dupe checking routine. Each program is designed for real time use. It automatically enters date, time, band and serial number for each contact. A 24-hour clock is displayed at the top of the VDT screen. When the contest is over, the program will print your results listing all duped and scored contacts in serial sequence with all the necessary exchange information as well as completed score at the bottom of the page.

HD-CL **\$24.95**

Ham Data Super Log

Super log gives you all the advantages of a computerized data base without significantly changing the traditional log format. For contesters, Super Log can be configured to automatically enter serial number as well as time of contact. Or you can manually enter contact information. Should you make an error, you can easily go back and edit the entry. Super Log also allows you to print out either selected contents or the whole log. Will also print out QSLs. Easy to modify.

HD-SL **\$19.95**

Ham Data Propagation Chart

This program will be an invaluable addition to any Hamshack. The Propagation Chart allows you to determine the maximum usable frequency (MUF) and the optimum frequency (FOT) between your QTH and any spot on the globe. You can get either a screen display, a printed tabular list over several days, or a printed graph of MUF and FOT. You also get automatic beam headings and distance to the DX station. Really makes DX'ing a snap. Covers 160-10 meters and the new WARC bands.


HD-PC **\$21.95**

CIRCUIT BUSTERS STAR 1.0 DESIGN PROGRAM

STAR, S-parameter Two Part Analysis Routine, is a professional engineering program designed to help analyze electronic circuits. It is particularly helpful in frequency domain analysis of RF and microwave circuits. To use STAR, you input circuit information by component; inductors, resistors, capacitors, transformers, transmission lines, two port data and several two port manipulations. STAR will then give you S-parameter data for each requested frequency in tabular or plot form. You can also use STAR to optimize component values for maximum circuit performance. This program is definitely not for electronic beginners. Engineers and serious hams, however, will find STAR to be an invaluable design tool.

- RR-IBM program for IBM **\$99**
- RR-C-64 program for Commodore C-64 **\$99**
- RR-AP program for Apple II **\$89**
- RR-KP program for KayPro **\$89**

C-64 + DX Edge = Fun

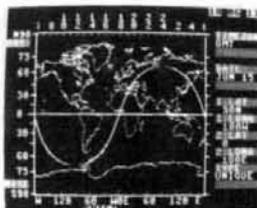

Generate your own Greyline display.

Xantek has adapted their best selling DX Edge to the computer world and it comes at a very reasonable price. Just \$34.95 brings into your ham shack the ability to know and predict when and where DX is going to appear. The DX Edge shows

you the sun's path across the earth. When you are using the program, the computer will automatically update the information as the sun progresses across the face of the Earth. To make the computerized DX Edge even easier to use, the display is keyed to the DXCC list and the 40 CQ zones. Disk and documentation are just \$34.95. This is something you've GOT to have! ©1985.

XN-C64 **\$34.95**

NOW HAS COMPUTER BOOKS AND SOFTWARE

COMMODORE 64 USER'S GUIDE by Commodore Engineers

This beginner's book gives you hands-on instructions on how to set up and use your brand new C-64 computer. Learn how to do color animation, generate music or specialized sound effects and interface the computer with peripheral equipment. Just about every question a beginner could ask is answered in this useful text. ©1982, 166 pages.

22010 **Softbound \$12.95**

COMMODORE 64 PROGRAMMER'S REFERENCE GUIDE

This programmer's guide will give you all the handy hints and tips that will let you get full value from your C-64. For the beginner, complicated topics are taken step-by-step, with plenty of sample programs and complete detailed explanations. Advanced users will find plenty of pretested and debugged programs. 1st edition, 486 pages.

22056 **Softbound \$19.95**

COMMODORE C-64 STARTER BOOK by Jan and Christopher Titus and David Larsen

This book is designed to get the new C-64 owner up and running with the minimum of fuss and hassle. Each chapter is packed with experiments and exercises designed to build competence in the user. Full of simple to load and use programs written with the beginner's need in mind. ©1984, 384 pages.

22293 **Softbound \$17.95**

REPAIR AND TROUBLESHOOTING GUIDES C-64, IBM-PC AND APPLE II by Robert C. Brenner

If you've been taking care of your ham gear, there's certainly no reason why you can't do much of your own microcomputer servicing. These handy guides give you a real headstart in taking on your "micro" when problems arise. Troubleshooting is clearly illustrated by simple flow charts that are designed to pinpoint failures and correct them. There is also an Advanced Troubleshooting chapter for more complicated systems failures. Clear easy-to-read text and plenty of illustrations.

22363 Commodore C-64 ©1985 **\$18.95**
 22353 Apple II Plus/IIe ©1984 **\$19.95**
 22358 IBM-PC ©1985 **\$18.95**

CIRCUIT DESIGN PROGRAMS FOR THE APPLE II

by Howard Berlin, W3HB

Use your Apple to help design electronic circuits. This book is a series of engineering programs written in Applesoft that give you various "what happens if" and "what's needed when" as they apply to a number of engineering questions. By using the computer you can change various circuit components and tell exactly how the circuit will perform without going through extensive manual calculations. ©1982, 132 pages.

21863 **Softbound \$15.95**

APPLE IIe PROGRAMMER'S GUIDE by David Heigerman

This book zeros in on how to program the popular Apple IIe home computer in both BASIC and assembly language. Chock full of helpful facts, applications, ideas, suggestions and technical information in one simple easy-to-use reference manual. You also get a number of short application and demonstration programs in BASIC and assembly language. ©1984, 416 pages.

22299 **Softbound \$19.95**

APPLE PROGRAMMER'S HANDBOOK by Paul Irwin

Get the most of your Apple computer by learning assembly language programming. Assembly language programs run much faster than basic programs and can be designed for maximum effectiveness with minimum compromise. Plenty of stock routines are included, organized by topic and detailed memory map. This 408-page book will answer just about all your questions on assembly language programming. ©1984, 480 pages.

22175 **Softbound \$22.95**

SPECIAL PRICE

COMPUTER DICTIONARY AND HANDBOOK by Sippl

More than 22,000 definitions, acronyms, and abbreviations as well as 14 information packed appendixes make this an invaluable reference book for all levels of computer users. Operational control, storage devices, and time sharing are just a few of the subjects extensively covered in this important volume. ©1980, 928 pages.

21632 **SAVE \$5 Softbound \$29.95**

VIC 20 PROGRAMMER'S REFERENCE GUIDE

To get the Vic to perform for you, you have to know how to program. The book is divided into four sections: BASIC Programming, Machine Language Programming, Input/Output Interfacing and Programming Graphics and Sound. Each chapter is fully illustrated with sample programs and has plenty of "how to" explanations. 1st edition, ©1982, 289 pages.

21948 **Softbound \$16.95**

THE 68000 PRINCIPLES AND PROGRAMMING by Leo Scanlon

Motorola's 68000 is the first 16 bit μ p to have a 32 bit internal architecture. This book covers CPU information that is needed for all microcomputer professionals and hobbyists alike. Also includes information on Motorola's cross-macro assembler, a 68000 instruction set, printouts and interfacing. ©1981, 240 pages.

21853 **Softbound \$15.95**

Z-80 MICROPROCESSOR PROGRAMMING AND INTERFACING by Nichols and Rony

This is the easy way for novices and experts to learn how to write and design programs for the popular Z-80 microprocessor. Book 1 focuses on fundamentals and use of the Z-80 while Book 2 explores special interest topics in great depth. ©1979.

21609 Book 1 **Softbound \$12.95**
 21610 Book 2 **Softbound \$16.95**
 Buy BOTH Special **\$24.95**
SAVE \$4.95

MICRO COOKBOOK Vol. 1 and 2 by Don Lancaster

Learning to use a PC can be a real challenge. However, Don Lancaster has tried to filter out all the gobbledygook and make it as easy as can be. Volume 1 features down-to-earth coverage of fundamentals, number systems, hardware and software logic, mainstream codes and standards, electronic memory and memory devices and other applications. Volume 2 covers address space, addressing, system architecture, machine code programming, I/O and helpful suggestions to common problems.

21828 Volume 1 ©1982 **\$15.95**
 21829 Volume 2 ©1983 **\$15.95**
 Buy BOTH Special **\$26.95**
SAVE \$4.95


ORDER FORM

Name _____
 Address _____
 City _____ State _____ Zip _____
 Check or Money Order Enclosed
 VISA MasterCard
 Card # _____ Expires _____

| Catalog # | Title | QTY. | Price | Total |
|-----------|-------|------|-------|-------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |



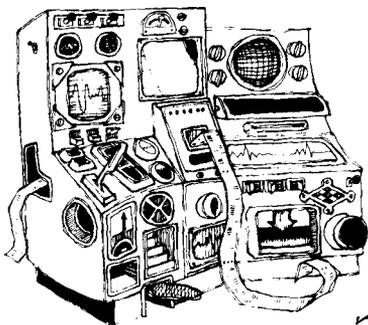
Subtotal _____
 Shipping _____
TOTAL **\$350**



ham radio magazine **BOOKSTORE**

134 GREENVILLE, NH 03048

(603) 878-1441

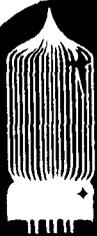

TUBES and IC's FAST DELIVERY LOWEST PRICES

call Toll Free (800) 221-5802

In-depth Inventory - Industrial & Receiving Tubes
Here are 2 dozen examples.

| | | | |
|----------|---------|--------|---------|
| 3-400Z | \$85.00 | MRF455 | \$19.95 |
| 3-500Z | 85.00 | M2057 | 15.00 |
| 4CX250B | 60.00 | 872A | 24.00 |
| 572B | 53.00 | 4X150A | 35.00 |
| 811A | 12.00 | 6DJ8 | 2.75 |
| 813 | 35.00 | 6550A | 7.50 |
| 6146B | 7.75 | 8072 | 95.00 |
| 6360 | 5.75 | 8121 | 95.00 |
| 6883B | 7.50 | 8874 | 215.00 |
| 7360 | 12.95 | 8877 | 520.00 |
| 8122 | 110.00 | 807 | 6.75 |
| MRF454/A | 19.95 | 8950 | 11.50 |

Major Manufacturers Factory Boxed and Full line of
Sylvania ECG Replacement Semiconductors



Minimum order \$25.00


Allow \$3 UPS charge

TRANSLERONIC INC.



Box H, 1365 39th ST., BROOKLYN, NY 11218
Tel. 718-633-2800/Watts Line 800-221-5802
FAX # (718) 633-4375

COMING

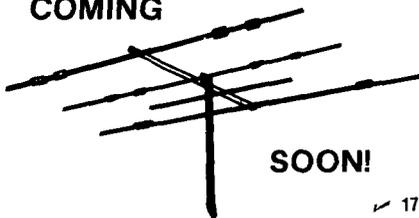

SOON!

THE ARRL ANTENNA COMPENDIUM

This new League publication will consist of over 20 antenna articles never published before. Availability will be in late May — just in time for your warm-weather antenna work! Watch QST for details.


Other books on antennas available from ARRL:

The ARRL Antenna Book 14th Edition, copyright 1982. 328 pages of comprehensive antenna, propagation and transmission line fundamentals. \$8.00 U.S., \$8.50 elsewhere. Cloth edition \$12.50

HF Antennas for All Locations, copyright 1982. From RSGB, 264 pages. \$12.00

Antenna Anthology The best hf antenna articles taken from QST. Copyright 1978, 148 pages. \$4.00 U.S., \$4.50 elsewhere.

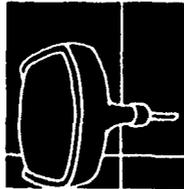THE AMERICAN RADIO RELAY LEAGUE
225 MAIN ST.
NEWINGTON, CT 06111



"TUNE IN" THE WORLD OF SPECIALIZED COMMUNICATIONS!

Thousands of "Ham Radio" operators across the country are enjoying "Specialized Communications" modes. Whether it's FSTV, SSTV, FAX, OSCAR, EME, RTTY, PACKET or COMPUTERS, today's Radio Amateur is a highly skilled Communications Specialist!

Providing full, in-depth coverage of these modes is our business and we've been doing it now for over 19 years! And now we're expanding!

Iowa Residents Must
Add 4% Sales Tax.

4% Added To All
Charge Card Orders.



Now published "monthly" 10 times per year, SPEC-COM™ readers are kept up-to-date in a world of fast moving modern technology.

Why not give us a try? Back issue samples are available for just \$2.00 ppd. (Master Article Indexes add \$1.00).

Special Six Month Trial Subscription - \$10.00. U.S./Canada/Mexico Annual Subscription \$20.00. (Foreign Subscriptions slightly higher).

SPEC-COM™

Amateur Radio Specialized
Communication Journal


P.O. Box H

Lowden, Iowa 52255

(319) 944-7669 (Membership Services)

✓ 186

WARNING SAVE YOUR LIFE OR AN INJURY

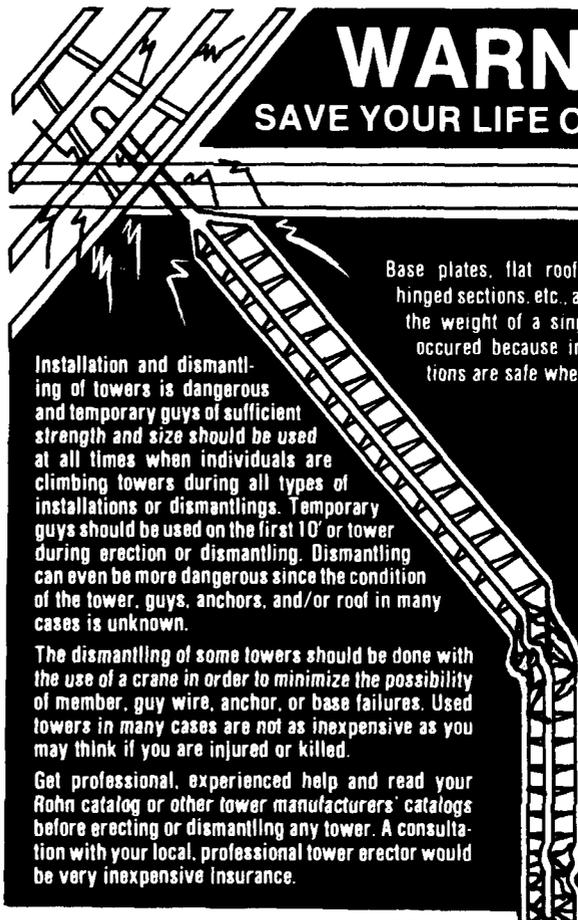

Base plates, flat roof mounts, hinged bases, hinged sections, etc., are not intended to support the weight of a single man. Accidents have occurred because individuals assume situations are safe when they are not.

Installation and dismantling of towers is dangerous and temporary guys of sufficient strength and size should be used at all times when individuals are climbing towers during all types of installations or dismantlings. Temporary guys should be used on the first 10' or tower during erection or dismantling. Dismantling can even be more dangerous since the condition of the tower, guys, anchors, and/or roof in many cases is unknown.

The dismantling of some towers should be done with the use of a crane in order to minimize the possibility of member, guy wire, anchor, or base failures. Used towers in many cases are not as inexpensive as you may think if you are injured or killed.

Get professional, experienced help and read your Rohn catalog or other tower manufacturers' catalogs before erecting or dismantling any tower. A consultation with your local, professional tower erector would be very inexpensive insurance.

Paid for
By the
Following:

ROHN®
P.O. Box 2000
Peoria, IL 61656



PLL phase modulator

I devised this circuit to help students understand the difference between frequency and phase modulation. It is also useful for studying the effects of phase-shift behavior in a closed-loop circuit.

Most phase modulators contain a certain amount of amplitude modulation, but this one does not. Its basic circuit, shown in fig. 1, uses a 565 PLL chip as a modulator, which is limited to a maximum frequency of about 500 kHz.

Resistor R1 and capacitor C1 establish the approximate operating modulation frequency where $f \approx 1.2/4R1C1$. The reference or input frequency should be adjusted until lock is obtained as described below. If desired, the input signal can be provided by a crystal-controlled oscillator (this is one of the chief advantages of phase modulation).

Lock can be determined by observing the input frequency on one channel of a dual-trace scope and the VCO frequency on the other channel. Pin 9 of the 565 should be used to observe the VCO frequency because a triangular waveform is available at this point. Pins 4 and 5 provide the normal square-wave outputs of the chip, but the fast rise and fall times make it hard to see what is happening to the waveforms at this level.

Once lock is achieved, the input frequency should be adjusted until the reference oscillator frequency and the VCO frequency are in phase. Alternatively, the value of R1 and C1 can be

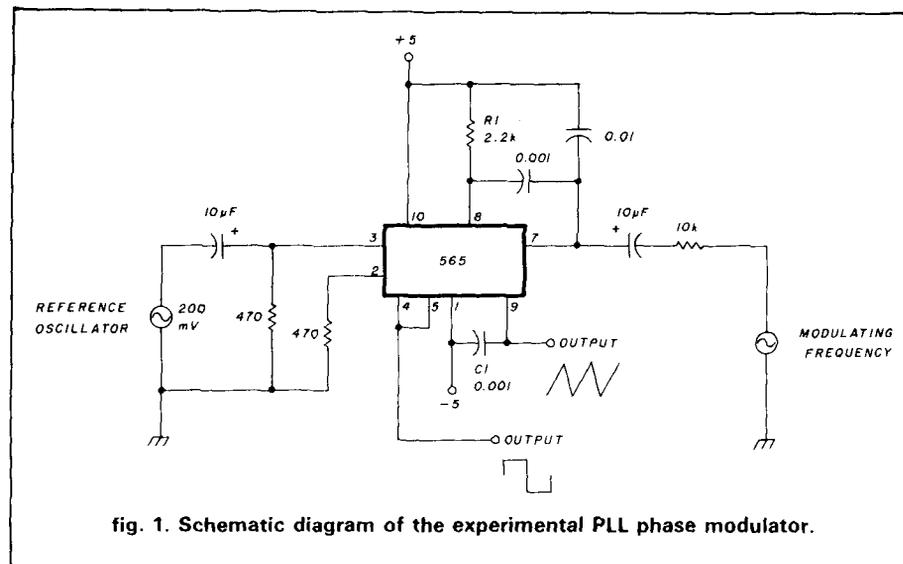


fig. 1. Schematic diagram of the experimental PLL phase modulator.

adjusted to shift the phase of the VCO signal.

The next step is to apply the modulating frequency to the error voltage input pin. A very low frequency should be used at first. Observe the display on an oscilloscope, making sure the scope is triggered on the reference signal. If the circuit is working correctly, the reference signal should be steady and the VCO signal should shift slowly back and forth in phase. The VCO is now being phase modulated.

Try experimenting with different amplitudes of the modulating frequency. The amount of modulation should vary with the amplitude of the modulating frequency. If the modulation amplitude is too high, the VCO may lose lock.

The amount of modulation is somewhat limited in this circuit. If more modulation is needed, additional modulators may be added in cascade. The output of the first modulator must be taken from pin 4 or 5 and reduced in level to about 200 mW before being fed to the second modulator.

Another characteristic of phase modulators may also be observed. As the modulation frequency is increased, the amount of modulation also increases. (This is another advantage of a phase modulator over an FM modulator.) Pre-emphasis is built right into the circuit and does not have to be added externally.

I have found this circuit easy to build and helpful to students. It can be con-

verted to FM by removing the reference oscillator.

I would be interested in hearing from other ham radio readers about applications using other chips at higher frequencies.

bibliography

Berlin, Howard M., *The Phase-Lock Loop Bugbook, with Experiments*, page 7-7 to 7-10. Capital City Press, Montpelier, Vermont, 1978.

Graham W. Stratford, VE3FHM

short circuits

June 1985

MINIMUF modification

The software code modification of the MINIMUF 3 propagation program provided in fig. 2 of the February, 1985 "DX Forecaster" (page 75) contains an error. Line 1774, which reads IF F2 > F3 THEN 1779 should read IF F2 > F3 THEN 1780.

June 1985 filter design

The program shown in N6JH's "Computer-aided Interdigital Bandpass Filter Design" (January, 1985, page 12) will correctly execute all examples given in the text and are applicable to any Chebyshev filter design. However, if a Butterworth design is desired (OdB entered as the desired ripple in the passband), the program will plot the attenuation graph incorrectly, although it will compute the mechanical details correctly. Changing line 970 from GOTO 1040 to GOTO 1020 will correct this problem.

flea market



RATES Noncommercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

MILITARY COMMUNICATIONS: CPRC-26 Manpack Radio (described in March 1985 Ham Radio), transceives 46-54 MHz FM, with battery box, antenna, crystal, handset: \$22.50 apiece, \$42.50/pair, good condition. R-390A Receiver, 5-30 MHz all modes, 4 mechanical filters, meters sealed (Government removed, operation unaffected): complete/checked \$175, complete/unchecked \$115, spare parts unit (80% complete, missing PTO/power supply) \$65. Info SASE. CPRC-26 add \$4/unit shipping. R-390A shipping charges collect. Baytronics, Dept. HR, Box 591, Sandusky, OH 44870. Phone (419) 627-0460 evenings.

CX7 REPAIRS. 414-549-9210.

LETTERING and text for QSL pasteup and label usage. Stamp bearings circular. Labelcraft, PO Box 412, W. Sand Lake, NY 12196.

CABLE TV EQUIPMENT. Jerrold, Hamlin, Zenith, many others. Factory units/lowest dealer prices. Complete illustrated catalog \$2.00. Pacific Cable Co., Inc., 7325 1/2 Reseda Blvd., Dept. 1002, Reseda, CA 91335. (818) 346-5071.

TENNAEST — Antenna noise bridge — out-performs others, accurate, costs less, satisfaction guaranteed, \$41.00. Send stamp for details. W8UUR, 1025 Wildwood Road, Quincy, MI 49062.

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Belgium
Sterehouse
Brusselssteenweg 416
B-9218 Gent
Belgium

Ham Radio Holland
Postbus 413
NL-7800 Ar Emmen
Holland

Ham Radio Europe
Box 2084
S-194 02 Upplands Vasby
Sweden

Ham Radio France
SM Electronic
20 bis, Ave des Clarons
F-69000 Auxerre
France

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Canada
Send orders to
Ham Radio Magazine
Greenville, NH 03048 USA
Prices in Canadian funds
1 yr \$29.95, 2 yrs \$53.30
3 yrs \$75.40

Ham Radio Italy
Via Pordone 17
I-20132 Milano
Italy

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio England
c/o R S G B
Alma House
Cranborne Road
Potters Bar
Herts EN6 3JW
England

Holland Radio
143 Greenway
Greenside, Johannesburg
Republic of South Africa

COMPUTERIZE YOUR IC-720. Keyboard frequency entry, 64 memories, scanning (frequency, memory, and mode), many more features. Requires no interface, just cable — directions included. For Commodore 64. Cassette \$14.75, disk \$16.75, ppd. Cables also available. David Oliver, W9ODK, Rt. 2, Box 75A, Shelvin, MN 56676.

CUSTOM MADE embroidered patches. Any size, shape, colors. Five patch minimum. Free sample, prices and ordering information. Hein Specialties, Inc., Dept. 301, 4202 N. Drake, Chicago, IL 60618.

DIGITAL AUTOMATIC DISPLAYS. All transceivers. Six 1/2" digits. 5" wide by 1-1/4" by 9" cabinet! Send \$1.00 for information. Grand Systems, POB 2171, Blaine, Washington 98230. Canadians VE7LB.

2500 VOLT POWER SUPPLY. From two TV transformers, full wave 120 cycles. Send \$1.00 postage & handling for schematic. You won't see this one in any books. Leverage Kator, Rt. 1, Ogilvie, MN 56358.

CUSTOM EMBROIDERED Emblems — Cloisone' enameled pins, your design, low minimum, excellent quality, free booklet. A. T. Patch Co., Dept. 65, Littleton, NH 03561. (603) 444-3423.

SYNCHROS, all types, quality Navy salvage, gears, bearings, excellent for beam position indication. SASE to Ted Stewart, 2157 Braemar Road, Oakland, CA 94602.

WANTED: National NC-101X. Will buy for cash or trade nice HRO Sr. For sale 75A Ser. No. 1479 \$225. Prefer pick-up. Horace Goss, W2AB, Crossstreets Hill, Essex, CT 06426. Tel 203-767-8485.

WANTED: Mono and early stereo tube HiFi equipment. Marantz, Scott, Fisher, Eico, McIntosh, Dynaco, etc. Working or not, complete or parts. Jack Smith, 59 Mill Pond, N. Andover, MA 01845.

RUBBER STAMPS: 3 lines \$4.50 PPD. Send check or MO to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

CHASSIS and cabinet kits. SASE K31WK.

IMRA, International Mission Radio Association, helps missionaries. Equipment loaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey, 1 Pryer Manor Road, Larchmont, NY 10538.

ELECTRON TUBES: Receiving, transmitting, microwave... all types available. Large stock. Next day delivery, most cases. Daily Electronics, PO Box 5029, Compton, CA 09224 (213) 774-1255.

RTTY-EXCLUSIVELY for the Amateur Teleprinter. One year \$7.00. Beginners RTTY Handbook \$8.00 includes journal index. P.O. Box RY, Cardiff, CA 92007.

RETAIL STORE being liquidated by mail auction. Parts, tools, test equipment, home supplies. SASE to ESI, Box 328, Mesa, AZ 85201.

Coming Events ACTIVITIES "Places to go..."

ILLINOIS: The DuPage Amateur Radio Club Hamfest/Computerfest, Sunday, July 14, Downers Grove American Legion Post 80. Gates open 8 AM. Tickets \$3.00 available at the gate only. Large outdoor flea market and swappers row. Inside exhibits available. VEC exams. Plenty of parking. Food and drink available. Talk in on 146.52 simplex. For information SASE to W9DUP, PO Box 71, Clarendon Hills, IL 60514 or call (312) 971-3294 8 AM to 9 PM.

PENNSYLVANIA: Harrisburg Annual Firecracker Hamfest, Thursday, July 4. Sponsored by the Harrisburg RAC, Bressler Fire Co. picnic grounds, Exit 1 of I 283. Nearby motels and restaurants. Plenty of parking. Shaded pavilion with tables. Free tailgating. Admission \$3.00. XYL and kids free. A test session for hams wishing to upgrade will be held nearby. Send check for \$4.00 payable to ARRL-VEC with FCC form 610. Some limited walk-ins. For more details and table reservations: Dave, KC3MG, 131 Livingston St, Swatara, PA 17113 or (717) 939-4957.

OHIO: The 21st annual Wood County Ham-A-Rama, Sunday, July 14, Wood County Fairgrounds, Bowling Green. Gates open 8 AM. Free admission and parking. Trunk sales. Food

available. Advance table rentals \$5.00 to dealers only. Saturday setup until 8 PM. K8THH talk in on 147.18 repeater and .52. For more information or dealer rentals SASE to Wood County ARC, c/o Craig Henderson, N8DJB, 7368 Scotch Ridge Rd., Pemberville, OH 43450.

MICHIGAN: The "85" U.P. Hamfest, July 27 and 28, St. Francis de Sales School, Manistique. Friday evening Fish Fry, set and eyeball for early arrivals. Saturday 6 AM to 5 PM. Banquet 6:30 PM. Sunday 8 AM to 2 PM. Registration \$3.50. Free baby sitting. Table space \$3.00 per 4' table. For more information: Debbie Barton, WD8IBT, 509 Range St., Manistique, MI 49854. (906) 341-5694 after 3 PM.

PENNSYLVANIA: The MURGAS ARC (K3YTL) will sponsor the annual Wilkes-Barre Hamfest, Sunday, July 7, rain or shine, 109th FA Armory, Market Street, Kingston (across the river from Wilkes-Barre). Set up 6 AM. General admission 8 AM. Registration \$3.00. Women and children under 16 free. Tailgating \$2.00 per space. Tables and commercial power available. Talk in on 146.01/61 and 52 simplex. For further information write: Hamfest Committee, PO Box 1094, Wilkes-Barre, PA 18703 or call (717) 388-6863.

BRITISH COLUMBIA: The 33rd annual Pacific Northwest DX Convention, sponsored by the British Columbia DX Club, Saturday and Sunday, July 27 and 28, Richmond Inn, Richmond, British Columbia. DXers from all over the world will be here to visit, learn and swap stories about our favorite hobby. Send club rosters or labels for mailing to individual club members for further details about the convention. The labels will be used only for this purpose. See you in British Columbia! Ken Thompson, VE7BXJ, Chairman, 12467 - 53rd Avenue, Surrey, BC V3W 1A4 or Andy Ponzini, VE7AHA, Publicity, 4551 Arthur Drive, Delta, BC V4K 2X4.

INDIANA: State ARRL Convention and Indianapolis Hamfest, Saturday and Sunday, July 13 and 14. Marion County Fairgrounds, I 74 and I 465. Flea Market, commercial vendors, free camper facilities and hookup available on grounds. Motels nearby. Gates open 6 AM. Tech forums, ARRL convention and banquet. Food service on grounds. Gate ticket \$5.00 gets free parking and more. For further information: Indianapolis Hamfest, PO Box 11776, Indianapolis, IN 46201.

1985 BLOSSOMLAND BLAST, Sunday, October 6, 1985. Write "BLAST", PO Box 175, St. Joseph, MI 49085.

MAINE: The YL International Sideband System's annual Convention, June 27-30, Sugarloaf/USA, Kingfield. Accommodations are available for reasonable rates. RV parking. Besides the regular meetings, DX forum, etc. there are planned tours of Rangeley Lake area and Sugarloaf/USA. For complete details and registration packet send business SASE, 37¢ to: Phyllis Davis, KA1JC, PO Box 805, Presque Isle, ME 04769.

NEW YORK: The Mt. Beacon Amateur Radio Club's Hamfest, Saturday, July 13, Arlington Senior High School, Poughkeepsie/Lagrange. Note date change. Doors open 8 AM. Tickets \$2.00. XYL and children free. Tailgating space \$3.00 (1 free admission). Table \$4.00 (1 free table and admission). Auction 2 PM. Talk in on 146.37/97 and 146.52. For information: Julius Jones, W2IHY, RR2, Vanessa Ln, Staatsburg, NY 12580 or call (914) 889-4933.

INDIANA: The combined LaPorte-Michigan City Amateur Radio Clubs will sponsor Summer Hamfest, Sunday, July 14, at the LaPorte County Fairgrounds, State Road 2, West of LaPorte. 8 AM to 2 PM. Donation \$3.00 at the gate. Paved parking. Indoor tables by reservation 40¢/ft to Box 30, LaPorte, IN 46350.

WISCONSIN: The Aug Claire Amateur Radio Club will hold its annual Hamfest, Saturday, July 13, 4-H Buildings, Eau Claire. 8 AM to 4 PM. Free tables and coffee. Tickets \$2.00 in advance, \$3.00 at door. Talk in on 31/91 and 52 simplex. For info, tickets, SASE to Gene Lieberg, KA9DWH, 2840 Saturn Avenue, Eau Claire, WI 54703.

OHIO: The Lancaster and Fairfield County Amateur Radio Club's annual Hamfest, Sunday, July 14, Fairfield County Fairgrounds. 8 AM to 4 PM. In memory of WB8VOA. Admission \$3.00 advance, \$4.00 at door. Tables \$4.00 advance, \$5.00 at door. Table space \$3.00 advance, \$4.00/door. Talk in on 147.03/63 or 146.52 simplex. Refreshments available. Plenty of parking. For more information write Lancaster ARC, Box #3, Lancaster, Ohio 43130.

OHIO: The 11th annual Hall of Fame Hamfest presented by W8ZX, Tusco ARC and W8AL, Canton ARC, July 14, Nimishillen Grange, 6461 Easton Street in Louisville. Registration \$2.50/adv, \$3.00/door. Mobile check in 146.52/52 and 147.71/12 call W8ZX. Large flea market, dealers, forums and more. Flea market parking \$2.00 per vehicle. Deadline for table reservations is July 1. For more information or reserva-

tions: WA8SHP, Butch Lebold, 10877 Hazelview Ave., Alliance, Ohio 44601. (216) 821-8794.

WISCONSIN: The Oshkosh Amateur Radio Club in conjunction with the S.O.L.A.R. Assn. will host EAA hams for the 1985 convention, July 26 - August 2. Stop and rest, charge your batteries, leave messages, etc at the EAA Ham Shack located at the north end of the commercial exhibit area. Look for the red and white ARRL flag. On Saturday, July 27 at 3 PM, there will be a gathering for all EAA hams hosted by the Oshkosh ARC. We'll be serving bratwurst, burgers and refreshments free of charge. Bring your wives and kids. You're in for a treat! For further info: Forest Schafer, WD9IWL, 417 Willow St., Omro, WI 54963.

KENTUCKY: The Northern Kentucky Amateur Radio Club's "Hamorama '85", June 15 and 16, Best Western Vegas Convention Center, Erlanger. All indoors, air-conditioned and free parking. Vendor set up Friday evening, June 14 after 8 PM. Flea market set up after 6 AM both Saturday and Sunday. General admission 8 AM. Admission for both days \$5.00 per person. Entire family for \$8.00. Children under 16 free. Flea market tables \$5.00 each for entire weekend. Talk in on 147.86/26 or 147.975/375. For information: John A. Thernes, WM4T, VP, NKART, 60 Locust Avenue, Covington, KY 41017. (513) 397-7425 days or (606) 331-0331 evenings.

MONTANA: The LYARS of Eastern Montana will hold the annual Fathers Day Picnic, June 16, National Guard Armory at the Glendive Fairgrounds. Registration at 8 AM. Potluck at 1 PM. Licensing exams are tentative pending interest. Camping hookups available. For information contact Dave Bruen, KC7AA, 215 Third St. H.P., Glendive, MT 59330.

WASHINGTON: The Apple City Amateur Radio Club's Hamfest, June 8 and 9, Rocky Reach Dam, 7 miles north of Wenatchee. Registration: Amateurs \$5.00; others \$1.00; under 12 free. Banquet dinner \$7.00 per person by June 3. Talk in 146.07/67 or 146.49 simplex. For motel/dinner reservations contact any Wenatchee ham.

NEW JERSEY: The Raritan Valley Radio Club will hold its 14th annual Hamfest, Saturday, June 15, Columbia Park, Dunellen. Gates open 8:30 AM. Sellers spots \$5.00 each, no tables supplied. Lookers \$2.00 donation. Refreshment stand. Talk in on club repeater, W2QW/R 146.025/625 and 146.52 simplex. Advance tickets may be purchased from any club member. For further information call Jack, W2IWK at (201) 756-2546 or Ted, W2TKU (201) 725-3481 between 10 AM and 10 PM.

CALIFORNIA: The Satellite Amateur Radio Club will have its annual Swapfest and Barbeque, Union Oil Picnic Grounds, south of Santa Maria, on Father's Day, June 16. General admission 9 AM and the Barbeque will be served at 1 PM. Dinner and tickets adults \$7.95, children 6-12 \$3.50. Children under 6 free. Swap spaces \$3.50 each. For information, tickets or reserved tables write: Satellite ARC Swapfest, PO Box 1753, Santa Maria, CA 93456.

NEW HAMPSHIRE: Fly in to New Hampshire's 2nd largest Amateur Radio/electronic flea market at Manchester Municipal Airport, Saturday, June 29. Starts 9 AM. Sponsored by the New Hampshire FM Association. Rain date Sunday, June 30. General admission \$1.00 per person. Sellers \$5.00 bring own table or tailgate. Commercial displays welcome. Refreshments available. Talk in on 146.52 FM. For further information Doug Aiken, K1WPM (603) 622-0831 or Peat Henriksen, WA1RCF, 123 Woodlawn Circle, Portsmouth, NH 03801 (603) 431-5432.

WYOMING: The Great Plains Repeater Association and the High Plains Amateur Radio Club are jointly sponsoring the 1985 Wyoming Hamfest, July 12, 13, and 14, Wyoming State Fairgrounds in Douglas. Distributor displays, indoor flea market, tables available. License exams, seminars, auction, banquet, breakfast and more. Ample RV parking w/out hookups. Plenty of motels. For information and money saving advance registration SASE to Doug DesEntants, WA7WXO, North Star Route, Torrington, WY 82240.

OREGON: The Northwest Division of the Mercury Amateur Radio Association will host the first annual MARA convention at Camp Ester Applegate, near Klamath Falls, June 20, 21 and 22. MARA will operate special event station W7UFM in conjunction with this event from 2000Z, June 20 to 2400Z June 22. For a special commemorative QST send large SASE to MARA, c/o Jack Jakoubek, KD7EZ, 477 Deep Creek Road, Chelhalis, WA 98532.

OHIO: The Magic Valley Chapter of the Idaho Society of Radio Amateurs will have a Swapmeet on Saturday, June 15 from 9 AM to 5 PM at the Moose Lodge, 835 Falls Avenue, Twin Falls. Free admission. Swap tables \$2.00. All indoors. FCC exams and ARRL reps. Talk in on 1676. For further info write to PO Box 294, Twin Falls, ID 83303.

VIRGINIA: The Old Virginia Hams ARC announces its 11th annual Manassas Hamfest, June 2, Prince William County Fairgrounds, off Rt 234 1/2 mile south of Manassas. Gates open 8 AM. Tailgate setup 7 AM. Admission \$4, under 12 free. Tailgaters \$3.00 per space extra. YL program. CW proficiency awards. For information: Art Whittum, W1CRO, c/o Ole Virginia Hams ARC, PO Box 1255, Manassas, VA 22110. Tel (703) 361-4819.

MASSACHUSETTS: The ARRL Heavy Hitters Hamfest, July 20 and 21, Topsfield Fairgrounds, US Route 1, Topsfield. Indoor/outdoor flea market, food concessions, commercial exhibitors. ARRL forum, AMSAT show, CW and QSL contests, xmitter and rcvr hunts, ATV demo, packet radio and musical coffeehouse (BYO instruments). Activities for non-hams. License exams, send completed Form 610, photocopy of current license and check for \$4.00 payable to ARRL/VEC to: Topsfield Exams, c/o PO Box 71, Hanover, MA 02339 by June 20. Enclose SASE. Sorry no Novice exams. Free Saturday nite camping for tents and self-contained RV's. Nearby motels. Advance tickets \$3.00 \$4.00/door. Non-ham spouses and children free. Send check and SASE to Heavy Hitters Hamfest, PO Box 411, Waltham, MA 02254. For more information contact Russ Corkum, WA1TTV, 21 Thorndike Street, Arlington, MA 02174. Proceeds to benefit open Waltham repeaters, Handi-Hams and the Jimmy Fund. Talk in on 146.64 and 147.285.

THE CENTRAL OKLAHOMA COLOR OWNERS, a 278 member Radio Shack Color Computer users group, meets the second Saturday of each month at 9 AM at 10th Street and Hudson in Oklahoma City. The Club operates "COCONET", an open forum bulletin board system which can be reached at (405) 376-1494 24 hours a day, 7 days a week. The system contains COCO and FLEX operating system programs for download with no user connect fees.

WEST VIRGINIA: Wheeling Hamfest and Computer Fair, Wheeling Park, Sunday, July 21. Dealers welcome. Flea market, ARRL, AMSAT, SWOT, SMIRK booths. Family activities available at Park. Admission \$3.00. To reserve space contact Jay Paulovicks, KD8GL, RD 3, Box 238, Wheeling, WV 26003. (304) 232-6796 or TSRAC, Box 240, RD 1, Adena, OH 43901 (614) 546-3930.

ILLINOIS: The Egyptian Radio Club's annual Hamfest, Sunday, June 9, 8 AM to 3 PM at ERC clubhouse and grounds. Free flea market space, approx. 10', available on first come, first served basis. Additional spaces \$5.00. Tickets \$1.00 advance, \$2.00/door or 3/\$5. Talk in on 146.16/76 or 146/52 simplex. For information SASE to Egyptian Radio Club, PO Box 562, Granite City, IL 62040.

CQ CONTEST: VHF'ers please note! The first annual CQ World Wide VHF WFX Contest is July 20-22, 50 thru 1296 MHz. For details, logsheets, etc., write to SCORE, PO Box 1161, Denville, NJ 07834 or to CQ Magazine. We need your entry to make this a success.

OPERATING EVENTS

"Things to do..."

Colorado Six Meter Invitational Net Contest. 0000Z July 4 through 0300Z July 5. Exchange signal report, state, name and SIN number. Send SASE and log extracts for awards to W0ETT, PO Box 6602, Denver, CO 80206 within 30 days of contest.

The Cape Fear Amateur Radio Society, of Fayetteville, NC will operate WA4YZF from 8-5 PM EDT around 7.235 MHz on Saturday, June 15 from the 17th annual National Hollerin' Contest in Spivey's Corner, NC. Certificate available upon receipt of your QSL along with \$1.00 to help cover printing and postage. Send to Hollerin', WA4LZD, PO Box 332, Dunn, NC 28334. Allow 4 weeks for delivery.

The Tusco Amateur Radio Club, W8ZX, will operate from Fort Laurens Ohio State Memorial in conjunction with the Brigade of the American Revolution's re-enactment of 18th century military encampment 1400Z June 29 through 2200Z June 30. Special commemorative confirmation will be issued. Send large SASE (3 IRC's for DX) and QSO info to William K. MacNealy, WD8LFM, RR# 1 DRH, Bolivar, OH 44612.

WEST COAST 160 Bulletin Summer SSB Contest. SSB July 13 to July 14. Time 0000 GMT 7/13/85 to 2359 GMT 7/14/85. Single operator only. Exchange RST, QTH. Class: subscribers, non subscribers. Log info: date, time, rst, QTH. Send logs to: R. Koziomkowski, 5 Watson Drive, Portsmouth, RI 02871 prior to August 31, 1985.

High Plains ARC will operate K7YPT at Historic Fort Laramie from 0000Z July 4 until 0000Z July 5. Phone — 3.850, 7.250.

14.250, 21.360, 28.550. CW — 50 kHz up from lower band edge. QSL for business SASE to: K7YPT, PO Box T, Torrington, WY 82240.

The Nazarene Amateur Radio Fellowship (NARF) will operate WA0HPW/6 to commemorate NARF's 25th anniversary during the General Assembly of the Church of the Nazarene in Anaheim, CA from June 22 to June 29. Frequencies will be 14.280, 14.305 and 21385 during daylight hours. There will be some 40 m activity. For a special QSL card, send SASE to WB6UCO, Robert Buck, 5162 W. Ave. L 12, Quartz Hill, CA 93534.

Colombian Independence Contest 1985, Saturday, July 13, 0000 GMT to Sunday, July 14 2359 GMT. CW and phone, 1.8 thru 28. Exchange Signal report + serial number. Logs should be mailed no later than August 30, 1985 to L.C.R.A., c/o Direccion de Concursos y Diplomas, Apartado Aereo 584, Bogota, Colombia, Sur America.

The Hannibal Amateur Radio Club will again be celebrating National Tom Sawyer Days, in honor of Mark Twain's boyhood home town Hannibal, MO. Saturday, July 6 and Sunday, July 7. 1500-2100 UTC both days. Listen for W0KEM. For a certificate send large SASE and your QSL card confirming contact to Hannibal ARC, 2108 Orchard Avenue, Hannibal, MO 63401.

**SAY YOU SAW IT
IN
HAM RADIO**

MOVING?
KEEP HAM RADIO COMING...

If possible let us know four to six weeks before you move and we will make sure your HAM RADIO Magazine arrives on schedule. Just remove the mailing label from this magazine and affix below. Then complete your new address (or any other corrections) in the space provided and we'll take care of the rest.

**ham
radio**
Magazine

Greenville, NH 03048

Allow 4-6 weeks for correction.

Thanks for helping us to serve you better.

Here's my new address:

Call

Name

Address

City

State

Zip

**AFFIX
LABEL
HERE**



NEW products

IC-3200A dual bander

ICOM has announced the IC-3200A 25-watt compact full-featured Dual Bander. With only 14 front panel controls, the IC-3200A is simple to use, yet offers these standard features: frequency coverage from 140.000 to 150.000 MHz on 2 meters and from 440.000 to 450.000 MHz on 70 cm; 5 kHz fully programmable offsets for MARS and CAP repeater operation; and 25 watts output on both bands. Its size is 5-1/2 x 2 x 8-1/2 inches. The unit also includes memory lockout and scanning capability. The price is \$549.



For further information, contact ICOM America, Inc., 2380 116th Avenue, N.E., Bellevue, Washington 98004.

Circle #301 on Reader Service Card.

new Heathkit catalog

Over 400 electronic products in kit form, including the new HERO® JR. home robot, are featured in the latest Heathkit catalog.

HERO JR., the home and personal robot, is fully preprogrammed with speech output, light and sound sensors, and ultrasonic sonar, drive and steering motors, and an on-board computer system. He sings songs, plays games, recites nursery rhymes and can act as a security device and wake-up alarm.

The new GT-2218 HOTSHOT dialer is a unique one-number telephone dialer that quickly dials any telephone number up to 31 digits. It permits the use of alternate long distance service without the use of lengthy 13-digit phone and billing numbers and also allows an emergency number to be dialed by simply picking up the phone. The HOTSHOT features an easy-to-program memory that doesn't require battery backup since it is manually programmed.

Two new courses have also been added to the educational product line up: the EC-2001 Computer Fundamentals Course and the EE-1003 Analog Circuit Design Course.

For a free copy of the new Heathkit catalog, contact Heath Company, Dept. 150-510, Benton Harbor, Michigan 49022. (In Canada, contact Heath Company, 1020 Islington Avenue, Dept. 3100, Toronto, Ontario M8Z 5Z3.)

Circle #302 on Reader Service Card.

computer interface communications terminal

Amateur-Wholesale Electronics has announced its new θ -777 computer-interface terminal, featuring RTTY, bit inversion, AMTOR modes ARQ, FEC and SEL-FEC, ASCII and CW, any speed, any shift (ASCII and BAUDOT).

The θ -777 is a self-contained unit, with software, that allows reception and transmission with any computer or terminal that has RS232 or TTL I/O. The θ -777 automatically decodes signals and displays mode, speed, and polarity on the CRT. Operation is simplified by the use of 28 Bar-LEDs and LEDs including a bar-graph tuning indicator that allows precise centering of received signals.

In BAUDOT and ASCII modes, communications speed can be set from 12 to 200 baud using the modem, or 12 to 600 baud using TTL level. RS232 or TTL level data connection is 100-2400 baud (ASCII) or 45.5-200 baud (BAUDOT). Morse speed can be varied from 5 to 100 WPM in 1-WPM increments and is fully autotrack on receive.

The θ -777, which measures 2-1/2 x 9 x 10 inches, operates from a power supply of 11 to 14 volts DC.

For more information, contact Amateur Wholesale Electronics, Inc., 8817 S.W. 129 Terrace, Miami, Florida 33176.

Circle #303 on Reader Service Card.

digital FSK data modules

With packet radio and other forms of digital data communications becoming so popular, Hamtronics, Inc. has announced two new modules to its line of VHF and UHF FM transmitters, receivers, and accessories. The new modules provide for data interface with radio equipment using the popular "202" modem format (1200/2200 Hz tones) at data rates up to 1200 baud on

ordinary NBFM channels. In addition to modulating and demodulating the data pulses, these modules provide transmitter keying and full handshake facilities.

The MO-202 FSK Data Modulator is a PC board module measuring only 1-7/8 x 4 inches. It automatically keys the transmitter in response to a "request to send" input from the computer, and it provides a "clear to send" handshake 25 milliseconds later, after the transmitter and receiver have had time to respond. Relative levels of the 1200 and 2200 Hz space and mark tones are equalized to compensate for the EIA pre-emphasis in the transmitter for maximum signal range. The MO-202 is only \$45 in kit form, and is easy to assemble and interface with Hamtronics® and other FM transmitters or transceivers.

The DE-202 FSK Data Demodulator is a PC board module measuring only 1-1/2 x 4 inches. It can be used with any FM receiver or transceiver to detect FSK transmissions and automatically provide a "receiver carrier detect" handshake to the computer when mark or space tones are present. A special frequency compensation circuit levels the two tones coming from the receiver to allow for maximum weak signal response. The DE-202 kit is only \$38.

For further information, contact Hamtronics, Inc., 65-F Moul Road, Hilton, New York 14468-9535.

Circle #116 on Reader Service Card.

frequency list

Dennis Peterson, N7CKD, Publisher of *West Coast 160 DX Bulletin* has just released the 1985 edition of the World Top Band Frequency Allocations Listing. This comprehensive list includes both CW and SSB frequency allocations for 240 of the 315 current DXCC countries, listed in the DXCC format. The list can also be used as a 160-meter DXCC check sheet. U.S. price is \$5.50 (via first-class mail) and \$7.50 overseas (airmail).

For more information, contact Dennis Peterson, N7CKD, 4248 A Street, Space 609, Auburn, Washington 98002.

Circle #304 on Reader Service Card.

station manager

Station Manager/Advanced is a software system that utilizes micro computer technology to fulfill the information processing needs of an Amateur Radio station. Centered around the traditional station log, Station Manager/Advanced enables the Radio Amateur to handle the routine requirements of keeping accurate station activity records with maximum efficiency as well as instantly extracting information from the station's logs that would not be readily available using conventional manual methods. It also provides the user with the capability to easily manage several concurrent logs and a comprehensive

method for logging contacts and maintaining log entries.

Station Manager/Advanced is designed to run on an IBM PC Jr., PC, or XT. Menu-driven and completely interactive, it prompts the user for all required input. Messages are displayed to indicate significant processing events and error conditions. Log entries are entered via the system keyboard through a prompt-driven input program. Once entered, log entries may be edited or deleted as required. The user may query the log entries in one of several ways. The results are displayed on the system console screen. A separate facility allows the user to print a variety of reports on the system printer. An additional feature is a special interactive update program to support QSL activities.

Station Manager/Advanced is the core of a planned series of software systems to enhance the enjoyment of your Amateur activities; to harness the power of the computer and bring your station records into the information age.

For more information, contact Omega Concepts, Inc., P. O. Box 615, Troy, Ohio 45363.

Circle #305 on Reader Service Card.

new handhelds

Two new radios are available from SANTEC: the ST-200ET (2 meters) and the ST-400ET (70 cm). Both are easy to use, thumbwheel frequency switched units designed to be compatible with accessories for handhelds you may already own. Both are backed by a comprehensive two-year extended service plan from ENCOMM.




The ST-200ET is priced at \$199.95 and the ST-400ET at \$249.95.

For more information, contact ENCOMM, 2000 Avenue G, Suite 800, Plano, Texas 75074.

Circle #306 on Reader Service Card.

bench-style DMM

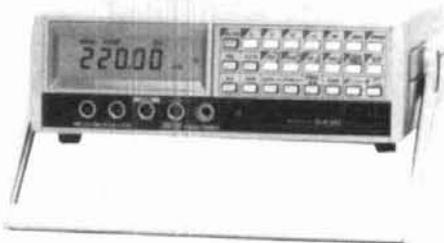North American SOAR Corp. has announced its Model 5430 4-1/2-digit multi-function bench-style DMM. Microprocessor controlled using



SOAR Corporation's Custom LSI Chip Set, the 5430 is a 25,000-count DMM that enables users to obtain greater resolution than possible with ordinary 20,000 count units presently available.

Priced at \$599, Model 5430 offers features previously unavailable in any other 4-1/2-digit DMM. It can measure DC voltage ± 0.03 percent, true RMS AC voltage and current to 80 kHz, DC current and resistance from 0.01 ohms through 25 megohms. The 5430 is a dual-input frequency counter with resolution to 0.001 Hz. DC coupled to 10 MHz, it features period function as well. The input frequency can be attenuated from 1:1 to 1:1000. Temperature measurements can be made using a "K" type thermocouple ranging from -200 degrees C to 1200 degrees C with degrees F selectable. Decibel measurements from $+60$ dBm to -50 dBm with frequencies up to 80 kHz.

Special features include diode test, continuity beeper, data hold, peak hold with a DC acquisition time of 5 milliseconds and AC of 250 milliseconds; relative test, 3-1/2 digit select for fast survey measurements, and a comparator circuit for making Go, NO-Go tests, with comparator data output via a rear panel connector. All functions and ranges are touch-key selectable.

For further information, contact North American SOAR Corp., 1126 Cornell Avenue, Cherry Hill, New Jersey 08002.

Circle #307 on Reader Service Card.

solar panels


The ENCON Corporation has announced the release of three new photovoltaic panels: the SX-38, SX-42, and the SX-146 dual voltage-semicrystalline PV modules.

The solar cells are manufactured from semi-crystalline silicon, a material developed by Solarex specifically for use in photovoltaic devices. Cells made from this material are highly efficient, stable, attractive, and inherently resistant to the "hot-spot" damage that can affect single-crystal cell under reverse-bias conditions.


Cell strings are laminated between sheets of ethylene vinyl acetate (EVA), Tedlar,® and a sheet of 1/8-inch tempered low-iron glass. This glass is self-cleaning in most climates, retains its excellent transmissivity indefinitely, and is extremely resistant to mechanical stress, including impact of hail up to 3/4-inch in diameter at terminal velocity. Furthermore, its temperature coefficient of expansion is well matched to the

MOSLEY...A Better Antenna... For New and Old

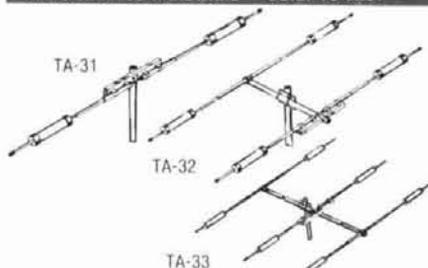- *EASY ASSEMBLY
- *NO MEASURING
- *ALL STAINLESS HARDWARE
- *2 YEAR WARRANTY
- *LOW SWR
- *BUILT TO LAST



Whether you are just starting out or trying to complete the Honor Roll, Mosley offers a Full Line of Tri-Banders which will mechanically and electronically outperform the competition. For the new ham with limited space and pocket book, start with our TA-31 Jr. rotatable dipole. You can make our TA-31 Jr. into a 2 or 3 element as your needs increase. If you start with the need to run higher power, then the TA-31 is for you. This also can be made into a 2 or 3 element beam as you expand your station.

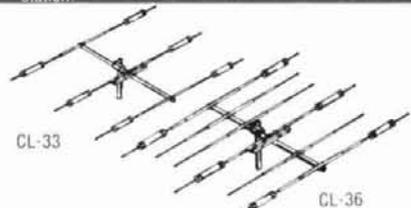

For the ham that wants a little more performance out of a Tri-Bander but is limited in room, then our CL-33 on a 18 foot boom is the way to go. For those that want MONO BAND performance out of a Tri-Bander, want to hear better, and be louder, the CL-36 is for you.



For the ham that wants to start right at the top, the PRO-37 is the antenna that will give you king of the hill performance. It is the broadest banded, highest power, best performing Tri-Bander in our line.

Compare ours before buying any other antenna. All stainless standard, all heavy telescoping aluminum elements which means better quality and no measurement. Ease of assembly gives you a quality antenna with consistent performance. Our elements are pre-drilled so you will get the same performance as we do. All of our Tri-Banders come with a 2 year warranty.

If you are a new ham and are not familiar with MOSLEY, ask an older ham about us or call the PRESIDENT of MOSLEY. He will be glad to explain why MOSLEY IS A BETTER ANTENNA.

These and other MOSLEY products are available through your favorite DEALER. Or write or call MOSLEY for the DEALER nearest you.

Mosley Electronics Inc.

1344 BAUR BLVD. ST. LOUIS, MISSOURI 63132

1-314-994-7872

1-800-325-4016

SYNTHESIZED SIGNAL GENERATOR

MADE IN
USA



MODEL
SG-100F
\$429.95
delivered

- Covers 100 MHz to 199.999 MHz in 1 kHz steps with thumbwheel dial
- Accuracy +/- 1 part per 10 million at all frequencies
- Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate
- External FM input accepts tones or voice
- Spurs and noise at least 60 dB below carrier
- Output adjustable from 5-500 mV at 50 Ohms
- Operates on 12 Vdc @ 1/2 Amp
- Available for immediate delivery • \$429.95 delivered
- Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator
- Call or write for details • Phone in your order for fast COD shipment.

✓ 189

VANGUARD LABS

196-23 Jamaica Ave., Hollis, NY 11423
Phone: (718) 468-2720 Mon. thru Thu.

MULTI-BAND TRAP ANTENNAS

Completely assembled & ready to use - Commercial quality, built to last - Lightweight, sealed, weatherproof traps - Automatic band switching - Low loss end insulators - Handles up to 2000 watts PEP - For all transmitters, receivers & transceivers - Tuner usually never required - Deluxe center insulator, with built in lightning arrestor, accepts PL-259 coax connector - May be used as inverted "V" - Excellent for all class amateurs - Instructions included - 10 day money back guarantee!

4-Band-40, 20, 15, 10 meters (55") 2 traps #D42 \$55.95 PPD
5-Band-80, 40, 20, 15, 10 meters (105") 2 traps #D52 \$59.95 PPD

SHIPPED POSTPAID! READY TO USE!

90 ft. RG-58U, 52 ohm coax cable, with PL-259 connector on each end - Add \$12.00 to above price.

We accept VISA/MC-Give Card #, Exp. Date, Signature


SPI-RO DISTRIBUTORS

Room 103, P.O. Box 1538
Hendersonville, NC 28793

✓ 190



MICROCOMPUTER REPEATER CONTROL

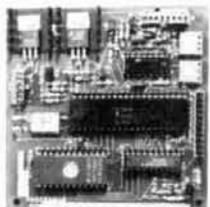

\$119

✓ 191

Introducing the MICRO REPEATER CONTROLLER RPT-2A, a new concept in LOW COST, EASY TO INTERFACE, microcomputer repeater control. Replace old logic boards with a state of the art microcomputer that adds NEW FEATURES, HIGH RELIABILITY, LOW POWER, SMALL SIZE, and FULL DOCUMENTATION to your system. Direct interface (drop in) with most repeaters. Detailed interface information included. Original MICRO REPEATER CONTROL article featured in QST Dec. 1983.

- Two CW ID Messages
- Time Out Timer
- Pre-Timeout Warning MSG
- Post Timeout CW MSG
- Courtesy Beep
- Auxiliary Inputs
- Reconfigurable COR Input
- High Current PTT Interface
- Sine Wave Tone Generator
- Low Power 9-15 VDC @ 200 ma
- Size 3.5" x 3.5"
- All Connectors Included

RPT-2A Kit Only \$119 plus \$3.00 shipping

PROCESSOR CONCEPTS

P.O. BOX 185
FORT ATKINSON, WI 53538
(414) 563-4962 7pm-10pm evenings



CALL OR WRITE FOR FREE CATALOG AND SPECIFICATIONS

NEW

ARRL TECH-GENERAL LICENSE MANUAL

Written in an easy to read and understand style, this is the guide you need for your Tech/General studying. FCC questions with complete answers ©1985. 1st edition.

AR-TG **Softbound \$5.00**

Please add \$2.50 for shipping and handling

ham
radio

BOOKSTORE

Greenville, NH 03048

Bind 'em and Find 'em



Keep those valuable issues of Ham Radio like new. Prevent smears, tears and dog ears. Bind 'em together and enjoy for years to come. You'll be happy you did!

HAM RADIO BINDERS

Beautiful buckram bound, rich brown material with gold embossing. These binders will really dress up your collection of Ham Radio. Year stickers included.

HR-BDL **\$6.95 ea.**
3 for \$17.95

Please add \$2.50 for shipping and handling, U.S. only.

HAM RADIO'S BOOKSTORE
GREENVILLE, NH 03048



cells; this matching and the stress-relieved electrical cell connections ensures excellent service even in climates with severe daily temperature ranges.

The module is framed with corrosion-resistant extruded aluminum sections with an architectural grade anodized finish. This strong, attractive framing and laminating is moisture resistant and accepts compatible mounting hardware.

The typical peaks power outputs for the new SX series modules are as follows:

| | |
|--------|-----------------------------------|
| SX-38 | 40 watts, 16.2 VDC at 2.5 amperes |
| SX-42 | 43 watts, 16.5 VDC at 2.6 amperes |
| SX-146 | 47 watts, 18 VDC at 2.6 amperes |

Panels can be wired for 6 VDC with a doubling of current output.

ENCON photovoltaic systems can be used for large or small Amateur Radio projects, repeater stations, computer back-up supplies, TVRO, cellular radio, as well as residential and commercial applications.

For more information, contact Paul Denapoli, WD8AHO, at ENCON Photovoltaics, 27600 Schoolcraft, Livonia, Michigan 48150.

Circle #309 on Reader Service Card.

block downconversion accessories

LUXOR North America Corp. has introduced four new block downconversion accessories for use with its Mark 2 Block Satellite Receiver. The four DC-passing accessories include a V/H (vertical/horizontal) switch, power divider, line amplifier, and 10-dB signal attenuator.

Early STV systems used downconverters, mounted at the antenna, that sent to the receiver only a single channel from the satellite at which the antenna was aimed. LUXOR'S new "block" system permits all channels (transponder signals) on a selected satellite to be cabled into the home at once. This allows simultaneous use of multiple block receivers tuned to different channels. Thus, using a shared antenna, an unlimited number of Mark 2 Block Receivers supporting TV sets in four different locations can be individually tuned to any channel available on a given satellite.

To split the incoming satellite signal between up to four receivers, each port of LUXOR'S Model 9758 4-way DC-Passing Power Divider passes direct current from the receiver to the LNB at the antenna, allowing full flexibility in switching receivers on and off. By cascading several Model 9758 splitters, an unlimited number of receivers can be hooked up to the same antenna.

The Model 9759 DC-Passing Line Amplifier amplifies the signal 20 dB to increase antenna-to-receiver cable length or the number of receivers served by one satellite antenna. Adding one amplifier allows approximately 200 more feet of RG6 cable.

The Model 9760 DC-Passing 10-dB Signal Attenuator is designed to reduce signal level for a short run in a system that required higher signal levels elsewhere.

LUXOR'S new block downconversion systems can be used in homes with multiple viewers who have differing tastes in programming, in multiple-family dwellings, and in SMATV (Satellite Master Antenna Television) applications.

For more information, contact LUXOR North America Corp., 600 108th Avenue, N.E., Suite 539, Bellevue, Washington 98004.

Circle #310 on Reader Service Card.

"G.I." mechanics tool bag

The legendary "G.I." Mechanics' Tool Bags are now available from Jensen Tools in a more durable fabric (Cordura® nylon) but with the same expandability and appeal as the old canvas duck models. The bags retain the traditional green color, over-sized metal zippers, and heavy-duty web straps of the originals. Two large pockets on the outside are divided into three handy compartments each, and close with industrial strength snaps. Eight interior pouches in the



main compartment serve to organize and protect small tools and parts.

For more information and a free catalog of hard-to-find tools, tool kits and cases, contact Jensen Tools Inc., 7815 S. 46th Street, Phoenix, Arizona 85040.

Circle #311 on Reader Service Card.

Kenwood TR-50 transceiver

The Kenwood TR-50 is a battery pack mobile/portable 1200 MHz FM transceiver that covers from 1260 to 1300 MHz with a 1-watt output transmitter. It features repeater offset with reverse switch, five memory channels, program-

Barry Electronics Corp.

WE SHIP WORLDWIDE
WORLD WIDE AMATEUR RADIO SINCE 1950
Your one source for all Radio Equipment!

For the best buys in town call:
212-925-7000
Los Precios Mas Bajos en
Nueva York.

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK.
Saturday & Sunday 10 to 5 P.M.

Monday-Friday 9 to 6:30 PM Thurs. to 8 PM
Come to Barry's for the best buys in town.

ONV Safety
belts-in stock



IC-R71A, IC-751, IC-745, IC-27A/H, IC-37A
IC-47A, IC-271A/H, IC-3200A, IC-4714A/H, IC-735

KENWOOD



R-600, R-1000, R-2000, TS-940/SAT
TS-430S, TR-3600A, TR-7950,
TW-4000A, Kenwood Service/Repair,
TH213141AT, TM-211A/
411A & TS-711A/B1A

TELEX PRO-COM
ROCKWELL/COLLINS
KWM-380

VoCom/Mirage/Daiwa Large inventory of
Tokyo Hy-Power Saxton Wire & Cable
Amplifiers & Antennas IN STOCK




MICROLOG AIR I, Air Disk

KANTRONICS
UTU, Interface II, Challenger



EIMAC
3-500Z
572B, 6JS6C
12B7A &
4-400A

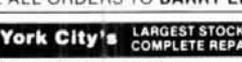AEA 144 MHz
AEA 220 MHz
AEA 440 MHz
ANTENNAS



BIRD
Wattmeters &
Elements
In Stock

YAESU
FT-ONE, FT-980, FT-757GX, FRG-8800
FT-726R, FT-77, FT-270RH, FT-2700RH

YAESU ICOM Land Mobile HiT
FT-12703R IC2AT Midland Standard
Wilson Mastex
FT-2700RH IC20AT Yaesu FT-C 2303, FT-4703
FT-C 1903 IC-04AT Icom IC-M12 (Marine) M700
Tempo M-1



NGC 7 21 50
Transceiver



SANTEC
ST-222/UP
ST-142/UP
ST-442/UP
HT-7

Computer interfaces
stocked: MFJ-1224
AEA CP-1, PKT-1, DR-DX
CP-100, ATU, Dr. QSO

ALPHA AMPLIFIERS
Complete Butternut Antenna
Inventory In Stock!

DIGITAL FREQUENCY COUNTERS
Touge Precision Engineering
Model TR-1000 0-1 GHz 1200Hz
0-400 MHz 0-1.3 GHz 1200Hz


Long-range Wireless
Telephone for export in stock

BENCHER PADDLES,
BALUNS, AUDIO FILTERS,
IN STOCK

MIRAGE AMPLIFIERS
ASTRON POWER SUPPLIES
DENTRON IS BACK IN STOCK!

SMART PATCH
CES Simplex Autogain 1510 & 1510 Plus FM
Transceiver - 10 Year Telephone Great For
Telephone Calls From Mobile To Base Simple
To Use \$139.95

CELLULAR PHONES
WELZ
FLUKE 77 Multimeter

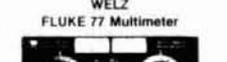

Nye MBV-A 3 Kilowatt Tuner




MFJ Models
422, 989, 1224 & 941D

HAM MasterTapes -
Beta or VHS Tapes

MURCH
Model
2000 A,
A-L5, B
in stock

HEIL EQUIPMENT IN STOCK

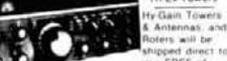

New TEN-TEC
2591 HT, Corsairs, Argosy II, Century 22

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

New York City's LARGEST STOCKING HAM DEALER
COMPLETE REPAIR LAB ON PREMISES

"Aquí Se Habla Español"

BARRY INTERNATIONAL TELEX 12-7670
MERCHANDISE TAKEN ON CONSIGNMENT
FOR TOP PRICES

Monday-Friday 9 A.M. to 6:30 P.M. Thursday to 8 P.M.
Saturday & Sunday 10 A.M. to 5 P.M. (Free Parking)

AUTHORIZED DIST. MCKAY DYKER FOR
SHORTWAVE ANTENNAS & RECEIVERS

IRITEX - Spring St. Station
Subways: BMT - Prince St. Station
IND - F Train Bwy. Station

Bus: Broadway #6 to Spring St.
Path - 9th St. 6th Ave. Station

Commercial Equipment
Stocked: ICOM MAXON
Midland Standard, Wil-
son, Yaesu, etc. (see
multiplicities, busi-
nesses, Civil Defense,
etc. Portables, mobiles,
base, repeaters.

Local
Ham Club
Speakers
Given

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic,
Astron, B & K, B & W, Bash, Banchar, Bird, Butternut, CDE, CES, Collins,
Communications Spec. Connectors, Covercraft, Cushcraft,
Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encom, Heil-
Sound, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics,
Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage,
Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook,
Robot, Rockwell Collins, Saxton, Shure, Telex, Tempo, Ten-Tec,
Tokyo Hi Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and
Commercial Radios, Voccom, Vibropack, Curtis, Tri-Ex, Wacom Duplexers,
Repeaters, Phelps Dodge, Faxon Intercoms, Scanners, Crystals, Radio
Publications.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS
DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED

COMMERCIAL RADIOS stocked & serviced on premises.

Amateur Radio Courses Given On Our Premises, Call

Export Orders Shipped Immediately. TELEX 12-7670



GUS BROWNING, W4BPD's DX'ERS MAGAZINE

For over 17 years, Gus's DX'ERS MAGAZINE has brought thousands of DX'ERS worldwide, timely, pertinent information on when and where to find those elusive DX stations.

Gus's personable, chatty writing style and his years of DX operating experience makes the DX'ERS MAGAZINE a unique publication. One year \$14.00 USA, Canada & Mexico.

Gus also prints high quality QSLs and other related items.
Write today for a free sample of his QSLs and DX'ERS MAGAZINE.

Gus Browning, W4BPD • PO Drawer 405 • Cordova, SC 29039

IF YOU'RE STILL USING AN OLD STYLE ROTOR CONTROL MAYBE YOU SHOULD CONSIDER THIS...



BUY THE ANTENNA CONTROLLER OF THE FUTURE TODAY!

A PRO-SEARCH™

DIGITAL

ANTENNA CONTROL FULLY COMPUTERIZED

SMALL IN SIZE
3 1/4" H x 5 1/4" W x 6" D

10 MEMORIES FOR STORING YOUR FAVORITE HEADINGS

ONE YEAR FULL WARRANTY

PRO-SEARCH Is Adaptable To Many Systems. Simple To Install.

No Modifications Are Necessary.

Presently we're having our Spring Special. A PSE-1, used with the CDE Series. Now only \$299.95 plus shipping. Regular retail price \$419.91. Offer good until June 15th, 1985. Order Early. We expect a back order problem due to demand and availability of parts.

Also ask about our Spring Rotor, Antenna and Unit Special.

CALL NOW 1-800-325-4016

Controllers also available for other rotors.

Prices and specifications subject to change without notice or obligation.

U.S. and Foreign Patents



PRO-SEARCH™
Reaching The World



Pro-Search Electronics Co.

1344 Baur Boulevard St. Louis, Mo. 63132

1-314-994-7872

1-800-325-4016

ALL BAND TRAP VERTICAL

Great for DX

Completely assembled and ready to use!
-Commercial quality, built to last -Lightweight, sealed, weatherproof trap(s)
-Low loss end insulator -Handles up to 2000 watts PEP - Automatic band switching -For all transmitters, receivers & transceivers -Tuner usually never required - Deluxe end feed connector, with built in lightning arrestor, accepts PL-259 coax connector -Use as sloper or vertical
- Permanent or portable use - Easy to install -Can be used without radials - Attaches to almost any support -Excellent for all class amateurs - Instructions included -10 day money-back guarantee!

4-Band-40,20,15,10 meters (27') 1 trap #VS-41 \$39.95 plus \$4.00 shipping
5-Band-80,40,20,15,10 meters (52') 2 traps #VS-52 \$54.95 plus \$4.00 shipping
50 ft. RG-58U, 52 ohm coax cable with PL-259 connector on each end - add \$8.00 to above price.

We accept VISA/MC - give Card#, Exp. date, Signature ✓ 190



SPI-RO DISTRIBUTORS,
Room 103, P.O. Box 1538
Hendersonville, NC 28793



AZOTIC INDUSTRIES

2026 W. BELMONT
CHICAGO, IL 60618
312-975-1290

ELECTRONIC COMPONENTS & SUPPLIES

- RF CONNECTORS
- UG CONNECTORS
- AUDIO CONNECTORS
- LINEAR IC'S
- DIGITAL IC'S
- TRANSFORMERS
- METERS
- COMPUTER CABLES
- DISKETTES
- IDC CONNECTORS
- D-SUBMINIATURE
- TEST EQUIP
- TRANSISTORS
- DIODES
- TRIM CAPS
- RELAYS
- SWITCHES
- TOOLS

WRITE FOR FREE CATALOG
VISIT OUR RETAIL STORE
HRS. MON-FRI 10-5 SAT 10-2
PHONE ORDERS WELCOMED
312-975-1290 ✓ 194

MICROWAVE EQUIPMENT

RMSG Manual Tuned
SIGNAL GENERATOR
.2 to 2 MW • +12 VDC

- 1 3.7 - 4.2 GHz \$50.00
- 3 2.1 - 2.2 GHz \$60.00
- 5 2.3 - 2.45 GHz \$60.00



RMVO Voltage Tuned Oscillator
1 to 10 MW • +12 VDC Bias •
-1 to -12 VDC Tuning • On PC Board

- 1 1.8 - 2.6 GHz \$25.00

Also Detectors, Line Stretchers, Variable Attenuators; 2.3 GHz Test Antennas, Mixers, LNA's and Converters.

ROENSCH MICROWAVE
R.R. 1, Box 156B,
BROOKFIELD, MISSOURI 64628 ✓ 195




mable scanning, memory scan, a priority alert function, and RIT. "Odd splits" operation is possible using memory channel 5. The multi-function LCD panel indicates frequency, VFO A/B, repeater offset, S/RFB/battery condition, and other keyboard functions.

The TR-50 comes complete with a rechargeable battery set and charger, shoulder strap, 16-key DTMF hand microphone, and an antenna on an adjustable mount. An external power cable is also included for mobile or base station supply operation.

For further information, contact Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.

computerized DX EDGE®

Xantek has announced the availability of the DX EDGE® for the Commodore 64™ personal computer. With the new version, users of the Commodore 64™ will be able to see on-screen display of optimum QSO and reception possibilities, the Gray Line, sunrise and sunset times, and areas of the world in daylight and darkness. The display is a graphic presentation showing a detailed world map, not just a set of numbers.

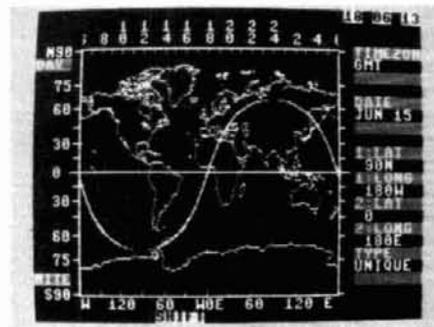

The computerized DX EDGE gives all the DX advantages of the original plastic version, and additional flexibility as well. The DX EDGE finds unusual long range propagation paths by showing all the locations in the world where the sun is rising and setting at any time of year and time of day. (Excellent DX conditions often occur at these times.)

Easy to use, the DX EDGE works for all bands from 1.8 to 30 MHz. DX EDGE for the Commodore 64 is priced at \$34.95. A single disk and full instructions are included.

For additional information, contact Xantek, Inc., P.O. Box 834, Madison Square Station, New York, New York 10159.

THE GUERRI REPORT

Ernie Guerri
WB6MGI

predicting equipment failures

As electronic equipment becomes more complex, so too do the ways in which it can fail. This increased complexity requires greater circuit and component density; as more and more components have been squeezed into smaller spaces, the number of circuit interconnects, and hence the number of potential failure points, have also increased — by a factor of a thousand or more in just the past few years. Although we are finding ways to dramatically reduce component size and the amount of power required to perform discrete functions, the fact remains that every capacitor or resistor still has two connections, and each transistor, three . . . and so on.

Because of the small mass of modern components, shock and vibration failures are no longer the problem they once were. High circuit density now makes heat a major culprit in circuit failure. Although a modern component may have dimensions of only a few thousandths of an inch, and may dissipate only a few milliwatts, these characteristics may result in a component dissipation of several watts per square inch. Unless provision for removing the heat is made, component or device failure will occur.

An additional source of potential failure is the chemical and metallurgical processes used during fabrication.

Assembling electronic circuits no longer consists of simply soldering together some tin, lead, and copper; a modern integrated circuit may require the amicable association of dozens of materials in a way that provides the opportunity for hundreds of different chemical interactions. The opportunity for one or more of these materials to contaminate nearby components is an important consideration in modern circuit failure analysis.

Because of the complexity of modern circuits, the possibility exists for thousands of combinations of potential failure mechanisms to occur in a single piece of equipment. Computers are now used to explore all of the possible relationships that could exist, and the ways in which they could promote failure. These techniques [known as diagnostic flow routines — Ed.] have become very sophisticated, and are deemed absolutely essential in military and space systems where no opportunity for repair may exist, and the consequences of failure can range from the merely disappointing and expensive to the catastrophic. The traditional method of expressing the likelihood of failure is called "mean time between failure" (MTBF); high-quality electronic equipment averages an MTBF of about 5000 hours.

These improvements in studying failure mechanisms and taking action to anticipate and prevent failure mean we can take a new transceiver out of

the box, plug it in, and expect to use it for years without trouble.

new batteries promise more power, longer life

For most of us, carbon or alkaline batteries are the power source for portable equipment. "Exotic" means we spent some money and bought Nickel-Cadmium cells. However, in the world of battery developers there's some very snazzy stuff going on.

Before we examine some of the details, and their implications for Amateur Radio, let's recall some of the rules regarding the availability of energy. In general, the amount of energy we can get out of any process is a function of how active the molecules, or atoms, of the energy source can be made. Since molecular activity translates to temperature, there is a general relationship between temperature and energy release. All of the processes with which we are familiar span the range from absolute zero — where nothing happens — to fusion reactions at a few hundred million degrees C, where everything tends to come apart.

These principles apply very much to the world of chemical batteries, and in the last 15 years or so, they have inspired some dramatic developments. Three important applications that have supported these developments have included electric vehicles, space systems, and military equipment. Each

PICK A COMPUTER INTERFACE TO MATCH YOUR NEEDS

**COMPUTER PATCH™
MODEL CP-1**



MICROPATCH™ MODEL MP-1



COMPUTER PATCH MODEL CP-100



COMPUTER PATCH™ MODEL CP-1

The AEA Model CP-1 Computer Patch has earned a solid reputation for being the best overall interface value on the market today. We at AEA have now reaffirmed what our competitors already know; for the money, the CP-1 cannot be beat! That is why we have chosen to leave the popular CP-1 in our product line and to introduce new computer interface/terminal units with differing features and performance at different prices.

MICROPATCH™ MODEL MP-1

The new AEA model MP-1 Micropatch represents the best features and performance available for under \$140.00. Featuring true dual-channel filtering of Mark and Space tones with an AM detector and Automatic Threshold Correction (ATC) circuit, the MP-1 is in a totally different performance class than competitive units that often have only a single channel filter or no filtering at all.

The MP-1 also offers a high performance CW capability. With respect to the CP-1, overall performance is nearly as good; but the CP-1 offers a few more advanced features such as variable shift tuning, RS-232 option, and a more advanced tuning indicator.

COMPUTER PATCH MODEL CP-100

The new CP-100 Computer Patch offers all the following exciting features in addition to the CP-1 features:

- 170, 425, 850 Hz Calibrated Shifts for Transmit and Receive
- 75 to 1000 Hz Variable Receive Shift Range
- Normal and Reverse FSK Outputs
- Input AGC
- Direct Coupled Automatic Threshold Control
- Front Panel Squelch
- Discriminator Style Tuning Indicator
- Current Loop Option
- Built-in Monitor Speaker
- Baud Rate Switch
- Improved AM Detector

Advanced Electronic Applications, Inc.
P.O. BOX C-2160 • LYNNWOOD, WA 98036
(206) 775-7373 • TELEX: 152571 AEA INTL



**Brings you the
Breakthrough!**



The Nicest Things Come In Small Packages.

The SS-32HB is a new hybrid sub-audible encoder plucked from Communications Specialists' Hothouse. It has grown through a cross of the time tested SS-32, the subminiature SS-32M and space age micro circuitry. This programmable 32 tone encoder measures a scant .5 x 1.0 x .15 inches; no small wonder it allows the addition of continuous tone control to a bunch of hand held transceivers that lack space.

Why not snip your problems in the bud, with our fast, one day delivery and attractive one year warranty.

\$29.95 each



**COMMUNICATIONS
SPECIALISTS**
426 W. Taft Ave., Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420
Entire U.S.A. 1-800-854-0547

✓ 197





Yaesu has serious listeners for the serious listener.

Yaesu's serious about giving you better ways to tune in the world around you.

And whether it's for local action or worldwide DX, you'll find our VHF/UHF and HF receivers are the superior match for all your listening needs.

The FRG-9600. A premium VHF/UHF scanning communications receiver. The 9600 is no typical scanner. And it's easy to see why.

You won't miss any local action with continuous coverage from 60 to 905 MHz.

You have more operating modes to listen in on: upper or lower sideband, CW, AM wide or narrow, and FM wide or narrow.

You can even watch television programs by plugging in a video monitor into the optional video output.

Scan in steps of 5, 10, 12½, 25 and 100 KHz. Store any frequency and

related operating mode into any of the 99 memories. Scan the memories. Or in between them. Or simply "dial up" any frequency with the frequency entry pad.

Plus there's much more, including a 24-hour clock, multiplexed output, LCD readout, signal strength graph, and an AC power adapter.

The FRG-8800 HF communications receiver. A better way to listen to the world. If you want a complete communications package, the FRG-8800 is just right for you.

You get continuous worldwide coverage from 150 KHz to 30 MHz. And local coverage from 118 to 174 MHz with an optional VHF converter.

Listen in on any mode: upper and lower sideband, CW, AM wide or narrow, and FM.

Store frequencies and operating modes into any of the twelve channels for instant recall.

Scan the airwaves with a number of programmable scanning functions.

Plus you get keyboard frequency entry. An LCD display for easy readout. A SINPO signal graph. Computer interface capability for advanced listening functions. Two 24 hour clocks. Recording functions. And much more to make your listening station complete.

Listen in. When you want more from your VHF/UHF or HF receivers, just look to Yaesu. We take your listening seriously.

YAESU

Yaesu Electronics Corporation
6851 Walthall Way, Paramount, CA 90723
(213) 633-4007

Yaesu Cincinnati Service Center
9070 Gold Park Drive, Hamilton, OH 45011
(513) 874-3100



KENWOOD


...pacesetter in Amateur radio

Up Front and Center!

TR-7950/7930

The exceptional front-end selectivity and sensitivity, coupled with Kenwood's excellent audio section, gives you lots to hear! Compact design makes this transceiver at home in the shack or on the go!

- Large, easy-to-read backlit LCD readout. Indicates receive/transmit frequency, frequency offset, sub-tone selection, memory status. An LED readout indicates S & RF units, REVERSE, CENTER TUNING, PRIORITY, and ON AIR.
- Programmable scanning, with center-stop tuning. Microprocessor technology allows you to scan the entire 2 meter band, or just a small portion of it. Scanning stops on the center frequency during band scan—a Kenwood exclusive!

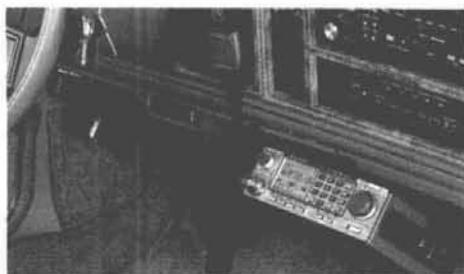

- 21 Multi-function memory channels. The TR-7950/7930 "remembers" frequency offset, and optional subtone channels. Memories 1-15 are for simplex and "normal" repeater operation. Memory pairs 16/17 and 18/19 are for "odd-ball" splits. Memories "A" and "B" store upper and lower band scan limits. The radio "beeps" when memory channel 1 is selected.
- Extended frequency coverage. Covers 142.000-148.995 MHz in 5-kHz steps. Repeater offsets are automatically selected in accordance with the ARRL 2 meter band plan. The front panel "OS" key may be used to allow manual changes in offset.
- Multi-function keyboard. The 16-key DTMF pad can also be used for direct frequency entry, sub-tone selection, memory address and scan programming. The keyboard is illuminated for night time use.



TR-7950 optional accessories:

- TU-79 three frequency tone unit
- PS-430 power supply
- KPS-12 fixed-station power supply for the TR-7950
- KPS-7A fixed-station power supply for the TR-7930
- SP-40 mobile speaker
- SP-50 mobile speaker
- MC-55 mobile microphone
- MC-46 16-key autopatch UP/DOWN microphone
- SWT-1 2 m, 100 W antenna tuner
- SW-100A/B power meters
- PG-3A noise filter

More TR-7950/7930 information is available from authorized Kenwood dealers.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220

Model TR-7950 (45 watts) shown. TR-7930 is identical, but with 25 watts output.
Complete service manuals are available for all Trio Kenwood transceivers and most accessories.
Specifications and prices are subject to change without notice or obligation.