

RTL-1A: Improved Version of RTL-1 Remotely-Tuned Loop
Mark Connelly - WALLON - 15 APR 1992

This article is an addendum to "The RTL-1 Remotely-Tuned Loop", an article I published in July of 1991. The original design has been upgraded to the RTL-1A model by the following modifications:

- * A switch (S4) has been added to enable or disable the output amplifier. In urban areas or with very sensitive receivers / large loop heads, use of too much gain can compromise dynamic range. (The output amplifier is still needed with smaller loopheads, less sensitive receivers, and rural locations.)
- * Another added switch (S5) now allows broadband, as well as tuned, operation in the active whip / wire mode. Broadband operation permits rapid bandscanning, shortwave parallel checking, etc. (at least in areas not congested with local stations that could give rise to spurious responses).
- * The BFE-C card (described in my recent article and updater) is used in place of the BFE-A. This balanced front-end, an adaptation of Dallas Lankford's design, has better noise and strong-signal handling characteristics than the BFE-A. See the BFE-C article and updater for full construction documentation (schematic, assembly, parts list).
- * An upgraded broadband amplifier card, BBA-C1, is used in place of the BBA-C. Through laboratory tests with synthesizers and a spectrum analyzer at work after-hours, design optimizations have been made for improved IMD / spur performance in two-tone tests (1000, 1100 kHz). Calculated third-order intercept is in the +32 to +36 dBm range. Amplifier gain is about 23 dB. Complete BBA-C1 documentation is included in this article. This amplifier may be used in place of BBA-C in any of my other designs (e. g. MWDX-5).
- * Other minor component changes have been made as part of the RTL-1A upgrade.

Documentation changes to figures and tables
in the original RTL-1's article

RTL-1 Figure 1: replace with RTL-1A (this article) Figures 1A and 1B.

RTL-1 Table 1: Amend the hole list by adding:

LEFT SIDE

| Hole # | Comp. Desig. | Description | X | Y | D |
|--------|--------------|------------------------------|------|------|-------|
| 4 | S4 | Tuned/Broadband switch-shaft | 1.25 | 1.25 | 0.25 |
| 5 | S4 | Tuned/Broadband switch- tab | 1.25 | 1.0 | 0.125 |

RIGHT SIDE

| Hole # | Comp. Desig. | Description | X | Y | D |
|--------|--------------|------------------------------|--------|------|-------|
| 4 | S5 | Amp. On / Off switch - shaft | -1.125 | 1.25 | 0.25 |
| 5 | S5 | Amp. On / Off switch - tab | -1.125 | 1.5 | 0.125 |

RTL-1 Table 2: Amend the parts list as follows:

| Item Designator | Description/Value | Vendor | Vendor Stock # | QTY |
|----------------------------------|------------------------------|--------------|----------------|-----|
| (Items 1 through 8: no change) | | | | |
| 9 | C2 capacitor, 47 pF | MOU | 232-1000-047 | 1 |
| (Items 10 through 32: no change) | | | | |
| 33 | R8 resistor, 100K | RS | 271-1347 | 1 |
| 34 | R9 resistor, 330 ohm | RS | 271-017 | 1 |
| 35 | RFC1 inductor, 2.2 uH | MOU | 431R226 | 1 |
| 36 | RFC2 inductor, 2200 uH | MOU | 434-05-222J | 1 |
| 37 | S1 switch,DPDT,on-on | RS | 275-614 | 1 |
| 38 | S2 switch/1pole/12pos.rotary | MOU | 10WW112 | 1 |
| 39 | S3,S4 switch,SPDT,on-on | RS | 275-662 | 2 |
| 40 | S5 switch,3PDT,on-on | MOU | 10TC280 | 1 |
| 41 | - screw, 4-40 X .25" | MOU | 572-01880 | 14 |
| 42 | - split lockwasher, #4 | MOU | 572-00649 | 12 |
| 43 | - solder lug, #4 | MOU | 534-7311 | 2 |
| 44 | - hex nut, 4-40 | MOU | 572-00486 | 2 |
| 45 | - screw, 1/4-20X1.5" | TVH or Sears | | 2 |
| 46 | - split lockwasher,1/4-20 | TVH or Sears | | 2 |
| 47 | - flat washer,1/4-20 | TVH or Sears | | 2 |
| 48 | - hex nut, 1/4-20 | TVH or Sears | | 4 |

RTL-1 Tables 4 & 5 and Figures 2 & 3 are changed to the equivalent documentation from the BFE-C article and updater.

RTL-1 Figure 8: replace with RTL-1A Figure 2. This is the schematic for the BBA-C1 Improved Broadband Amplifier that replaces the BBA-C.

RTL-1 Figure 9: replace with RTL-1A Figure 3. This is the BBA-C1 assembly drawing.

RTL-1 Table 8: replace with RTL-1A Table 1. This is the BBA-C1 parts list.


The following RTL-1 figures remain unchanged: 4, 5, 6, 7, 10, 11, 12.

The following RTL-1 tables remain unchanged: 3, 6, 7.

Table 1: (A1) BBA-C1 Improved Broadband Amplifier card parts list [replaces Table 8 of RTL-1 article]


| Item Designator | Description/Value | Vendor | Vendor Stock # | QTY |
|-----------------|--------------------------------|--------|----------------|-----------|
| 1 | BD perfboard(1.4"X1.4") | RS | 276-1396 (cut) | 1 |
| 2 | C1,C2,C5,C6 capacitor, 0.1 uF | RS | 272-109 | 4 |
| 3 | C3 capacitor, 10uF tant. | MOU | 581-10M35 | 1 |
| 4 | C4 capacitor, 0.001 uF | RS | 272-126 | 1 |
| 5 | H1,H2,H3,H4 screw, 4-40 X .25" | MOU | 572-01880 | 4 |
| 6 | H1,H2,H3,H4 spacer, 4-40 X .5" | MOU | 534-1450C | 4 |
| 7 | H1,H2,H3 split lockwasher, #4 | MOU | 572-00649 | 3 |
| 8 | H4 solder lug, #4 | MOU | 534-7311 | 1 |
| 9 | P1-P8 flea-clip for .042" hole | MOU | 574-T42-1/100 | 8 |
| 10 | Q1 transistor, 2N3866 | MOU | 511-2N3866 | 1 |
| 11 | R1,R5,R8 resistor, 4.7 ohm | MOU | 29SJ500-4.7 | 3 |
| 12 | R2 resistor, 33 ohm | RS | 271-007 | 1 |
| 13 | R3,R6 resistor, 680 ohm | MOU | 29SJ250-680 | 2 |
| 14 | R4 resistor, 2.7K | MOU | 29SJ250-2.7K | 1 |
| 15 | R7 resistor, 1 ohm | MOU | 29SJ500-1.0 | 1 |
| 16 | RFC1 inductor, 2200 uH | MOU | 434-05-222J | 1 |
| 17 | U1 voltage regulator, 7812 | RS | 276-1771 | 1 |
| 18 | W buss wire | RS | 278-1341 | approx.1' |

FIGURE 1A : RTL-1A REMOTE LOOP MAIN SCHEMATIC (INPUT)

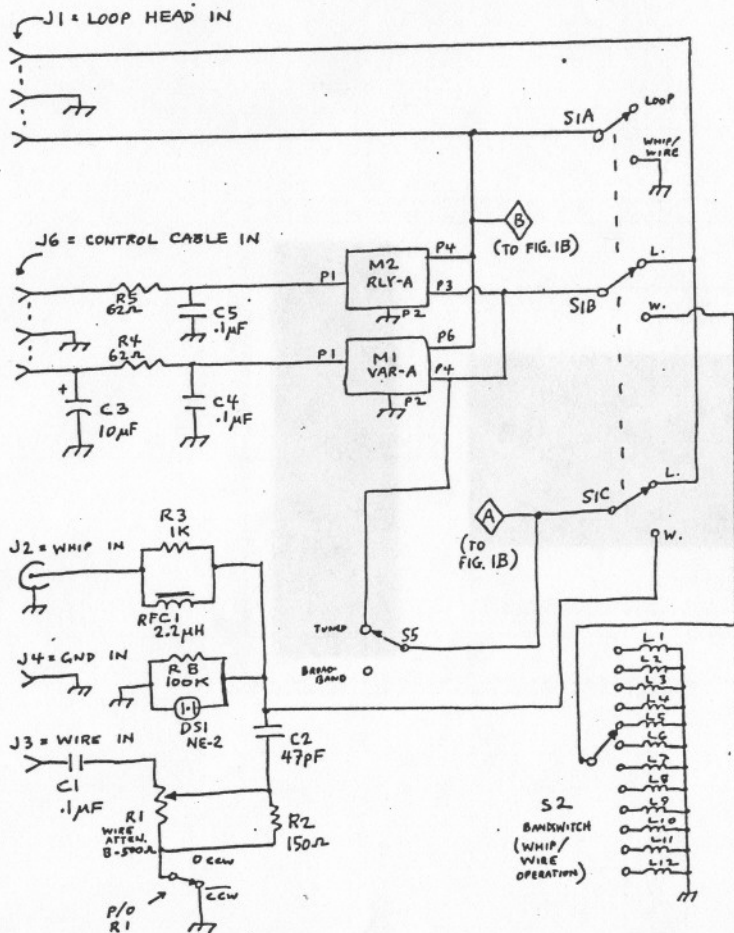

A note on varactor diodes: Besides the Motorola MVAM108 (available from Active Electronics, as stated in the RTL-1 article), several other devices can be used. Any of the other Motorola MVAM-prefix devices should work; some require different bias voltages. Allied Catalogue number 910, page 608 shows their stock number 586-0602 (Siemens part number BB112). Price was listed as \$ 0.60; it has now risen to \$ 0.75. Allied's address is 7410 Pebble Drive - Fort Worth, TX 76118; telephone is 1-800-433-5700. The BB112 seems fully compatible with the MVAM108. Also, per information from Dallas Lankford, the widely-available ECG618 and NTE618 devices can also be used.


FIGURE 1B : RTL-1A REMOTE LOOP MAIN SCHEMATIC (OUTPUT)

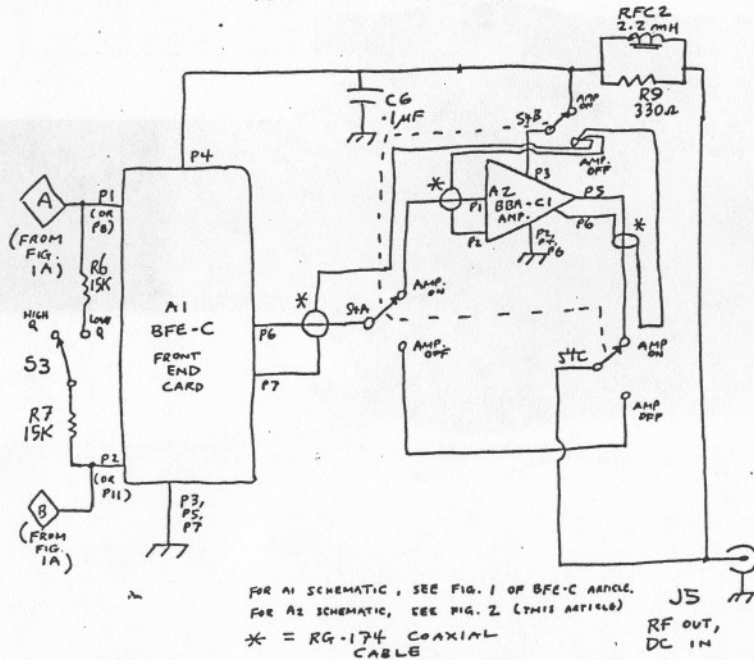

FOR A1 SCHEMATIC, SEE FIG. 1 OF BFE-C ARTICLE.
 FOR A2 SCHEMATIC, SEE FIG. 2 (THIS ARTICLE)
 * = RG-174 COAXIAL CABLE

A124-3-3


FIGURE 2: BBA-C1 IMPROVED BROADBAND AMPLIFIER CARD - SCHEMATIC
(WAI'EDN DA LABF - 17 MAR 1992)

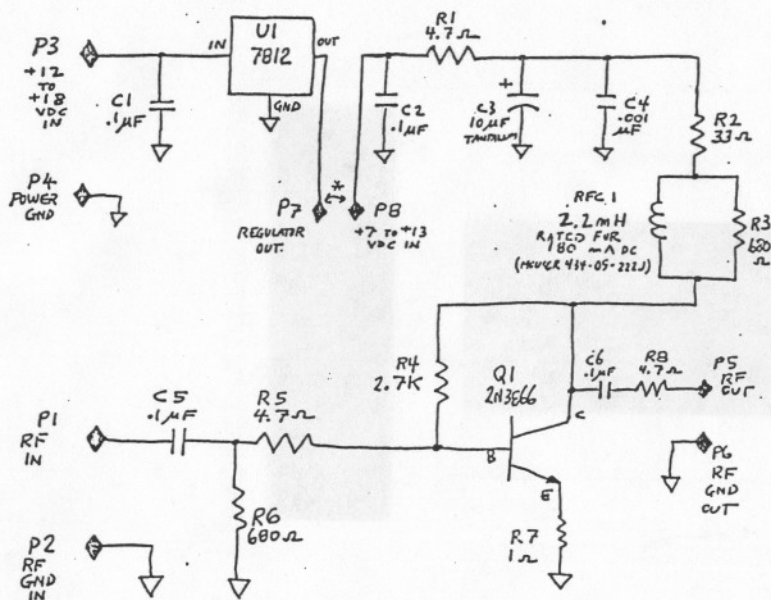

NOTES

- ↓ = CIRCUIT CARD GROUND
- * = JUMPER FOR REGULATED OPERATION
- FOR ASSEMBLY, SEE FIGURE 3.
- FOR PARTS LIST, SEE TABLE 1.

FIGURE 3: BBA-C1 IMPROVED BROADBAND AMPLIFIER CARD - ASSEMBLY

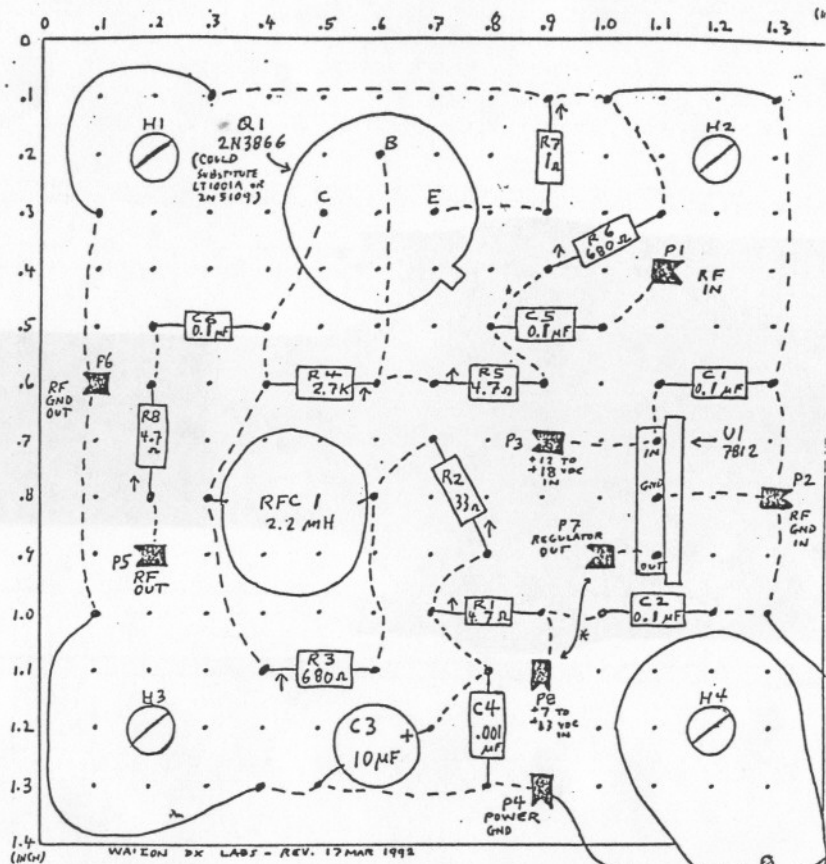

NOTES:

- FOR SCHEMATIC, SEE FIGURE 2.
- FOR PARTS LIST, SEE TABLE 1.
- ↑ = LONG-LEAD SIDE OF VERTICALLY-MOUNTED COMPONENT.
- = BUSS WIRE ON COMPONENT SIDE OF BOARD
- = BUSS WIRE ON SOLDER SIDE OF BOARD
- ⊠ = "FLCA CLIP" TERMINAL PIN
- = OPEN SIDE
- * = JUMPER INSTALLED FOR REGULATED OPERATION