

The Crudley-Bathbrush 2621?---a homebrew MW DX receiver

by NHP

A couple of years ago, Randy Tomer suggested that a fairly decent MW DX receiver could be had for about \$200 by upgrading the sensitivity and selectivity of a TRF (#12-655) and adding a digital readout. Well, I agreed with him at the time, and still agree. To start with, hearing MW DX is about 70% listening on the the right frequency at the right time and 30% (or less) owning a fantastic receiver---location is important also to say the least. As well, MW DX is limited by local noise and sideband splatter, so there are limits to the amounts of selectivity and sensitivity that can be used to advantage on MW. Stability of local oscillator tuning is easily achieved at the relatively low MW frequencies. The major problem with any MW DX receiver is achieving a reasonable degree of strong signal handling, so that your local doesn't pop up all over the dial. The TRF portables don't do too badly even in this field, considering the simplicity of their circuitry.

Rather than modify an existing receiver, I decided to build one from scratch, using textbook circuitry and available components (no surplus or custom-built components). The idea was not to build the best possible receiver, that will come later I hope, but to build one which was inexpensive, but that would rival the FRG-7 or similar receivers in its ability to hear MW DX. Portability and simplicity of operation were also requirements as I wanted to use it on beverage DX'peditions. In fact, simplicity of circuitry was a requirement, as I had (and continue to have) enough difficulty troubleshooting simple circuits.

Well, I didn't quite make it with exact textbook circuitry. The mixer and local oscillator ended up being tinkered with a fair bit. Because the supplier I got the coils from had longwave coils available, I decided to use some bandswitching, and get a longwave band as well. That introduced problems in tracking in the two sections of the variable capacitor that I won't go into here, especially as this was supposed to be a MW receiver. The RF transformers throughout this receiver came from an English supplier, Ambit International (200 North Service Road, Brentwood, Essex CM14 4SG, England). These are the inexpensive shielded, slug-tuned variety found in solid state radios the world over. I got them from Ambit because I was unable to find an American mail-order distributor. J.W. Miller has some similar ones, but for 3-4 times the cost.

I chose not to use an RF amplifier in this receiver because the mixer would have gain, and too much gain before the IF filter is not a good idea. An RF amplifier would have introduced another stage of tuning in front of the mixer which would have been useful, but I couldn't find any inexpensive, small 3-gang tuning capacitors, and wished to avoid a preselector tuning capacitor. An attenuator control (a 5k-ohm linear potentiometer) was placed between the antenna input and the mixer, as I was sure there would be signal handling problems (see Figure 1). The mixer circuit is a conventional one using a 40673 MOSFET, which is reputed to have the best signal handling ability of the various single-ended mixer designs, and has some gain too. Often the 40673 circuit has a 10k resistor placed across the output transformer in order to avoid excessive voltage swings and the resulting spurious responses. I tried this but found little attenuation in the spurs I did find---just a decrease in gain, so I left the resistor out.

The local oscillator (LO) circuit is a little unconventional in that it uses a "tickler coil" for its feedback. Most FET oscillators use a tap on the tuning coil for feedback. The 40673 mixer requires about 5 volts peak to peak signal from the LO for best operation and gain, and I found that the tapped-coil FET circuit didn't provide enough voltage, particularly with the peculiar bandswitching arrangement I had to use to make the LO "track" with the mixer tuning. The circuit I used provided a greater voltage output, yet did not seem to generate an undue amount of harmonics. Incidentally, the tuning capacitor was a 2-section 335 pF per section "Polyvaricon" from Ambit. A 6:1 vernier drive is used with it, and I can tune to the nearest kHz without backlash.


I used a digital display with this receiver, because I already had one with the necessary 455 kHz offset, a Radio West DD-2. It would have been time consuming and reasonably expensive to put together a tuning dial with even 10 kHz accuracy, so I opted for the digital display. Torrestronics and Mattis Electronics also sell digital display kits suitable for 455 kHz (addresses in A DXer's Technical Guide; yes, that's a plug for the book). I use my digital readout for three different receivers now, so it was a good investment. To avoid any loading of the LO by the digital display, a buffer amplifier is placed between it and the display input, again see Figure 1.

The IF filter used in the finished product was a MuRata CFS-455J with 3 kHz bandwidth at -6dB and 9 kHz at -70dB. This filter can be obtained direct from MuRata (unfortunately they have a \$100 minimum order), from Gilfer Associates (their 3kHz MOD-1 kit at \$45; you might check as to whether they will sell the filter separately) or from Ambit (\$12.25, about \$29 US; more if customs duty must be paid). Gilfer might give better value if the US government wants their cut. I tried out two other filters before settling on the CFS-455J. The MuRata CFG-455I is rated at 4 kHz at -6dB and 10 kHz at -70dB, has more spurious responses, but is a bit cheaper at \$7.25 from Ambit (about \$17 US). I also had a Collins 455FD-29 which I believe costs in excess of \$70 when purchased from Collins nowadays.

How did they work out, and why did I settle for the CFS455J? I first tried the CFG-455I filter and was fairly impressed with it. The tuned transformers (T5 and T6) at the input and output seemed to eliminate any filter spurious responses even next to locals.

Tuning across CKDA-1220 would yield readable audio at about 1216.6 kHz and readability cease as one tuned beyond about 1223.4 kHz. Lots of splatter on either side though, but in another test, there was no problem hearing BeLize 834 between 830 and 840 with both channels at about double strength to 834. The transition point from splatter to readable audio and back was somewhat indistinct, as it was also with the CFS-455J. The CFS filter yielded readable audio between, say 1217.4 and 1222.6 kHz with lots of splatter on either side, and has allowed a goodly number of split channels through---weak audio on Tahiti-738 when in Seattle for example. The Collins filter was very impressive; readable audio would appear at 1218.5 and cease at 1221.5 (this has a 2.9 kHz -6 dB bandwidth) and the transition from readable audio to splatter was very sharp. Of course, with none of these filters would it have been possible to log a station on 1215 kHz (or even 1200 kHz much of the time) because there was just too much splatter. Tuning around semi-locals yielded some interesting results. Using a station at 600 kHz, each filter had about the same readable audio bandwidth as before, and with about the same quality of transition from splatter to readable audio and back. But once you had tuned past readability using the Collins filter, you were treated to large amounts of splatter, which was much more obnoxious sounding than the splatter noted with the ceramic filters. So although readable audio would cover a DX signal within 3 kHz either side of the 600 kHz semi-local when using the CFS filter, heavy splatter would obliterate any signal within that range anyway when using the Collins filter. Where the Collins filter made a difference was on 660 kHz where a TVI het is at 660.8 kHz. The TVI could be positioned outside the steep skirts of the Collins filter and XERPM or WNBC would be free from the TVI het. This is not really possible with the more gradual skirts of the CFS filter. These experiments were all performed with a shield between the filter inputs and outputs with little change in the results.

I chose the CFS filter for this design due to its relative inexpensiveness; I felt it to be more suitable for this cheap and simple circuit than the steeper skirted Collins filter. However, if I build a receiver with a really good quality mixer, IF amplifier, detector etc., then I would choose the Collins for its ability to "shave off" interfering carriers a few hundred Hertz away. So far, I've not really missed the Collins filter in this radio, except for DX'ing channels like 660. The CFG filter (similar to the CFR series but smaller) would be more useful for anyone who DXes few split channels and wants to save a few dollars.

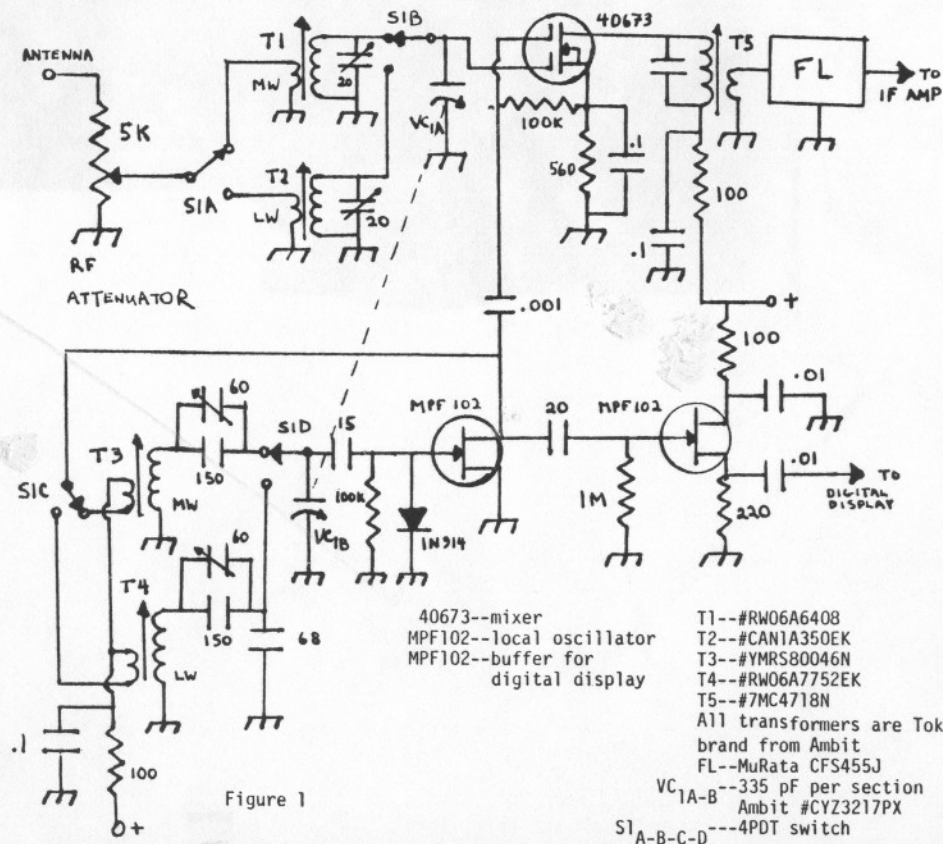

repeak the trimmer, return to around 600 kHz, repeak T1 until you get to a point where further adjustment is unnecessary. Finally, tune the receiver to any signal and make sure that the digital display reads exactly that station's frequency. Then turn on the BFO and adjust the 25 pF BFO trimmer capacitor for zero-beat with the desired signal. The ceramic resonator can drift around 40 to 50 Hz from this setting, but that will not be noticed when spotting MW carriers, and it's a lot cheaper than using a crystal in the BFO.

So, has the radio worked according to my original requirements? More or less... Conditions have been generally poor in the last couple of months, but I've heard virtually anything on this radio that the HRO could pull in--CBW-990 at 2PM PST, HIJB-830, HLAZ-1566, IYA-756...I've also compared it with a FRG-7 in Seattle, and the general opinion is that it is comparable to that. The FRG-7 has somewhat better audio and AGC action, but the homebrew has 1 kHz readout and no birdie on 910 kHz. Sensitivity seems pretty good using an unamplified 3' box loop, but then sensitivity is not that important when conditions are right; I've heard W. Germany-756 with the Realistic TRF held up to that same box loop!

Signal handling ability is OK as long as the RF attenuator is kept set fairly high when using the loop. A birdie from CKDA-1220 is noted on 1530 ((2x1220)-(2x455)) and a birdie from CKNW-980, CJVI-900 and CFAX-1070 ((3x980)-(900+1070)=970) is found on 970. Both can be knocked down with the attenuator, but at the expense of sensitivity. Using a longwire with the radio in this high signal area is a dead loss. CKDA alone puts out $.4 \text{ V}_{\text{rms}}$ into a 5k-ohm load from my unamplified loop. However, the two-pole antenna tuner described in the Technical Column of the January 27, 1979 DX Monitor makes longwire listening possible, and clears up the 1530 and 970 birdies to boot. I think that I would wire in a two-pole preselector if I were to build this again, but there's no room in the present box. I did try replacing T1 with a higher Q custom wound pot core (tnx EHG) which attenuated the