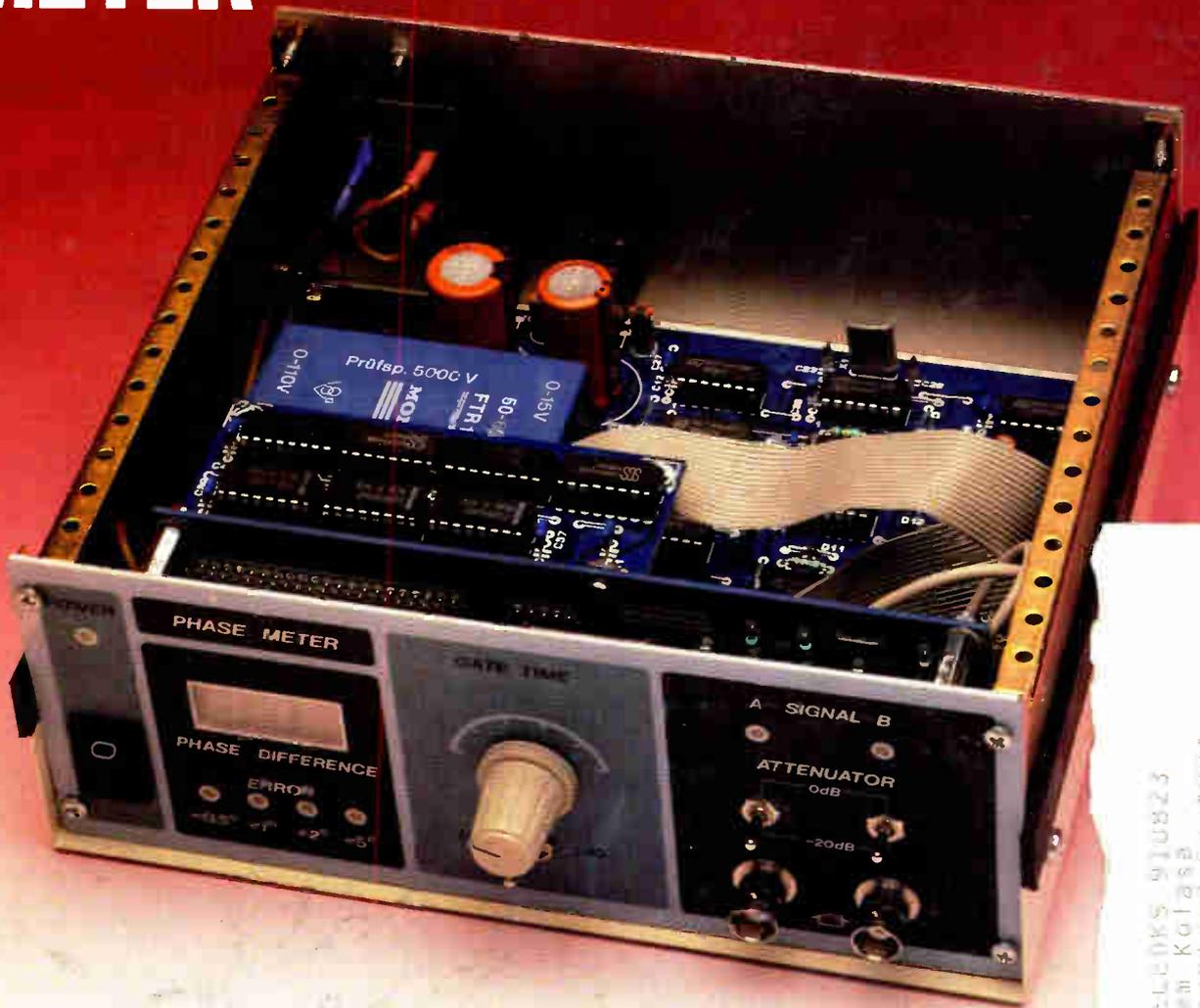




The QTC Loop Antenna  
Real-Time Atari ST Clock  
Stepper Motor Board  
Universal Battery Charger  
Timecode Interface

# DIGITAL PHASE METER



2686 ELEKTRONIKS 910823  
Wittichen Kollasch  
338 Ingheländ, Dr #204  
Glen Burnie MD 21061

**SUPER**

**KELVIN** Electronics

**INDUSTRIAL QUALITY AT DISCOUNT PRICES**

**BREADBOARDS FOR LESS!**

DURABLE - MADE OF THE HIGHEST QUALITY PLASTIC - DESIGNED TO WITHSTAND THOUSANDS OF INSERTION CYCLES

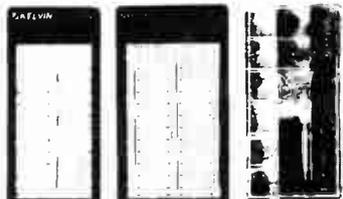


Fig.	Stock No.	Contact Points	YOUR COST
A	680093	500	\$ 4.25 ea
B	680097	840	\$ 5.95 ea
C	680098	1380	\$11.75 ea
D	680099	1580	\$15.75 ea

**WIRE JUMPER KIT**

Use with Quick Test Sockets and Bus Strips

Stock No.	Description	Points	YOUR COST
330290	350 Piece Set		\$ 7.75 ea

**PRO 400 The Professionals' Choice**

with 20MHz FREQUENCY COUNTER excellent for COMPUTER, TV, VCR REPAIR and ENGINEERING.


**YOU CAN'T GO WRONG!**

**MONEY BACK GUARANTEE!**

- LOGIC TEST
- DIODE CHECK
- CONTINUITY TESTER
- 5 FREQUENCY RANGES
- TRANSISTOR hFE TEST
- 5 CAPACITANCE RANGES
- LED TEST VERIFY
- 20 MHz FREQ COUNTER
- AC/DC VOLTAGE RANGES
- AC/DC CURRENT RANGES

CASE - Yellow, Durable, Back Stand **\$ 69.95**  
Stock No. 990092

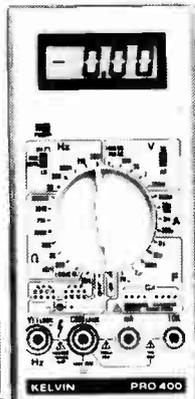PROTECTIVE CARRY CASE  
Stock No. 990094 \$9.95 ea



**30 DAY MONEY BACK GUARANTEE!**

**SOLDERING EQUIPMENT**

**WELLER MARKSMAN SOLDERING GUN**



Model SP23

Featherweight 1-3/4 oz., 25 watts for PC work. Ideal for reaching into those hard to get spots. Replaceable tip. Stock No. YOUR COST 6+  
810002 \$8.55 ea \$7.95 ea

**SOLDERING IRON HOLDER**



Model PH60

Soldering stand with base, sponge. For W50P, WP25P, WP40P, and irons with barrel diameters up to 15/32".  
Stock No. Description YOUR COST 6+  
810041 PH60 Stand \$13.78 ea \$13.09 ea  
810042 Replacement Sponge \$ 1.89 ea \$ 1.80 ea

**KESTER SOLDER**

RESIN CORE SOLDERS 1 LB. ROLL

Stock No.	Inch	Dia.	GA.	Type	YOUR COST
580010	1/64"	.025	23	63/37	\$11.95 ea
580005	1/32"	.031	21	60/40	\$9.95 ea
580001	1/16"	.062	16	60/40	\$8.95 ea
580011	3/32"	.093	13	60/50	\$11.75 ea

**IT's A FLUKE**

Model	YOUR COST	SALE	Model	YOUR COST
73	\$ 79.		83	\$199.
75	\$119.		85	\$229.
77	\$149.		87	\$269.



- 5 Digit Multifunction Dual Display
- Selectable Reading Rates & Resolutions
- True RMS AC Voltage, AC Current
- .02% Basic DC Voltage Accuracy
- DC Current to 10A RS-232 Interface
- Touch Hold, Relative & Min/Max

Stock No.	Model	YOUR COST
710035	45	\$579.

**KELVIN 100**

Stock No. 990087 **\$ 23.95**

- AC/DC VOLTAGE
- DC CURRENT
- RESISTANCE
- DIODE TEST
- BATTERY TEST
- LOW BATTERY Warning
- ACCURACY +/- 0.5%

**KELVIN 150**

Stock No. 990090 **\$ 29.95**

- AC/DC VOLTAGE
- DC CURRENT
- RESISTANCE
- DIODE & BATTERY TEST
- LOW BATTERY Warning
- ACCURACY +/- 0.5%
- CONTINUITY TEST
- TRANSISTOR CHECK

**KELVIN 200**

Stock No. 990091 **\$ 39.95**

- AC/DC VOLTAGE
- AC/DC CURRENT
- RESISTANCE
- DIODE TEST
- LOW BATTERY Warning
- ACCURACY +/- 0.5%
- CONTINUITY TEST/BUZZER
- TRANSISTOR CHECKER
- CAPACITANCE CHECKER

**INDUSTRIAL QUALITY**



**YOU CAN'T GO WRONG!**

**30 DAY MONEY BACK GUARANTEE!**

CARRYING CASE  
Stock No. 990093 \$4.95 ea

**WE STOCK A COMPLETE LINE OF FUSES**  
FAST ACTING - SLO-BLO TYPE - PIGTAIL

**3AG FUSE BLOCK**

Black laminated phenolic, 1/2" wide 1 7/8" long. For 1/4" x 1 1/4" long fuses. Solder lug connections.

Stock No.	YOUR COST
380030	\$ .45 ea

**FUSE MOUNTING BLOCK**

Dual fuse block 2 1/4" x 1" long. Black bakelite base. For 1/4" x 1 1/4" fuses. Mounting centers 5/8" (15.8mm).

Stock No.	YOUR COST
380010	\$ .62 ea

**FUSE POST TYPE HKP**


Bayonet type, 2 3/16" L for 1/4" x 1 1/4" fuses. 15 Ampere 250V. Panel hole size 1/2" (12.7mm). Complete with mounting nut.

Stock No.	YOUR COST
380001	\$ .90 ea

**TIMER - LM555**

Stock No. 600021

**20 ¢** ea. (in 100+ Qty)

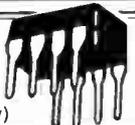

**L.E.D. RED** (in 100+ Qty)

Stock No. 260020

**6 ¢** ea.



**Transistors** (in 100+ Qty)

2N2222 **18 ¢** ea.

PN2222 **.08 ¢** ea.



**Project BUZZER**

6-9V DC, 80 dB

Stock No. 680089

**\$1.59 ea \$1.39/10+ ea.**



**9V Battery Snap & Holder**

Snap .15 ea. .10ea/100+


Holder .20 ea. .10ea/100+



**LAPEL MICROPHONE**

Stock No. 850306

YOUR COST \$2.95 ea

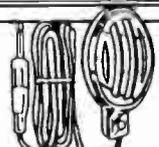

**CADMIUM SELENIDE PHOTO CELL**

450 ohms @ 2 ft., C minimum dark resistance 225 ohms. Max voltage 170V peak. Peaks at 6900 angstroms.

No. 260017 YOUR COST \$ .99 ea



**SULPHIDE PHOTO CELL**

1.5K ohms @ 2 ft., C minimum dark resistance 75 ohms. Max voltage 170V peak. Peaks at 5500 angstroms.

No. 260018 YOUR COST \$ .99 ea



**SUB-MINIATURE MOMENTARY PUSH SWITCH**

Silent action red push button molded housing. Requires 1/4" panel hole. Overall length including solder lugs is 1". Rated 115 VAC, 1 AMP

Stock No.	Color	YOUR COST	100+
990002	Red	\$ .35 ea	\$ .28 ea



**DC MOTOR**

1.5 to 6VDC

Stock No.	YOUR COST	20+
852211	\$ .50 ea	\$ .45 ea



**KELVIN BRAND HI-SPEED, HI-QUALITY PRINTED CIRCUIT ETCHANT**

Ready-to-use solution of ferric chloride printed circuit etchant in plastic container.

Stock No. SPECIAL BUY 440017 **\$ 6.25 per gallon**



**KELVIN BRAND HI-SPEED DRY PRINTED CIRCUIT ETCHANT**

Clean, safe, economical, indefinite shelf life. 4 lbs. will make 2 gallons of recommended 20% etching solution.

Stock No.	YOUR COST	NEW PRICE
440026	\$8.40 ea	\$ 7.00/ 4lb bag

**KELVIN BRAND COPPER CLAD BOARD**

NEMA grade FR-2 1/16" thick, unpunched clad on one side.

Stock No.	Size	YOUR COST
440002	4 1/2" x 6"	\$1.55 ea
440003	5" x 7"	\$2.40 ea
440015	8 1/2" x 12 1/2"	\$4.90 ea

**ETCH RESIST INK PENS**

Black felt tip pen for making resist circuits directly on PC boards. Dries instantly for neat, easy application. Can be removed with PC Board Stripping Solution.

Stock No.	Model	Description	YOUR COST
440115	22-220	Draws 1/32" wide	\$1.48 ea
440116	22-222	Draws 1/64" wide	\$1.85 ea

**KELVIN** Electronics

7 Fairchild Ave. Plainview, NY 11803

Call: 1 (800) 645-9212

1 (516) 349-7620

FAX: 1 (516) 349-7830

FREE CATALOG Call or Write



## NEW HAND-HELD TEST EQUIPMENT




*"the audio source"*

2100 WARD DRIVE  
HENDERSON, NV 89015
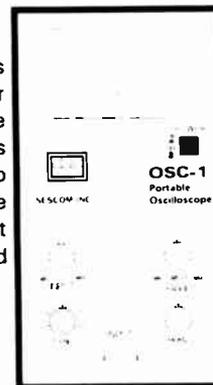
### OSC-1 FLAT OSCILLOSCOPE 699.00

The OSC-1 is a hand-held battery-operated oscilloscope. It is designed for field use. The batteries are housed in a trap-door housing for easy field replacement. The heart of the portable oscilloscope is a Sony flat screen 2" black and white screen. There is added circuitry to take the analog signal and display it on the video screen. The unit works as a sampling oscilloscope by comparing the input wave-form with the horizontal timebase. The unit has an input gain control and sweep control. The unit is perfect for field use and small labs where space is at a premium.



### ASG-2 LOW DISTORTION AUDIO GENERATOR 255.00



The ASG-2 is a hand-held battery-operated sine-wave audio generator. It is designed for field use and is housed in a rugged aluminum case. The battery is in a slide-lock compartment that requires no tools for change. The sine-wave generator is a typical Wien-bridge with a FET for thermal stabilization. The unit has low distortion, typically under 0.05% across the band. The unit will generate frequencies from 20-20kHz. The ASG-2 has three-decade switching plus eight switches to determine the exact operating frequency. There is a push-button on-off switch.


The output level has a range of +10dBm to -60dBm and has both balanced and unbalanced outputs. The balanced output is electronically done. The output levels are determined by two rotary switches. One switch is for the decades in 10dB increments and the other rotary switch is in 1dB increments. The unit will drive 600 ohm loads.

### AVM-2 PORTABLE AUDIO VOLTMETER 259.00

The AVM-2 Audio Volt Meter is designed to read audio type signals from a low of 1 mv (-60 dB) full scale to a high of 100 volts (+40 dB) from a low frequency of 10 Hz to 100 KHz. The scale of the analog meter is calibrated in both scales of volts/millivolts and dB's. The accuracy of this instrument is about 2-3%. The input impedance is 1M ohms/ 10pf which means it will not load the typical circuit it is measuring. The unit operates with a single nine-volt battery with a current drain of 7.5 ma. The unit will operate with a low battery voltage of 7.5 volts. The unit is factory calibrated so that is very accurate in the field.



### THD-2 DISTORTION ANALYZER 495.00

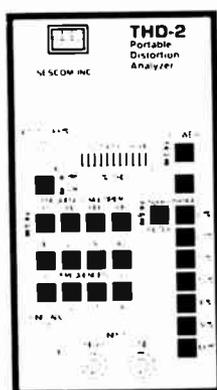

The THD-2 is a hand-held battery-operated distortion analyzer. It is designed for field use and is housed in a rugged aluminum case. The battery is in a slide-lock compartment that requires no tools for change. The distortion analyzer is a typical state-variable filter type. The unit is easy to use. Place the input signal into banana jacks, and set the input level control and range switch to obtain a 100% reading. Then set the frequency multiplier switch to the proper range. The frequency can be set by the decades and units frequencies. The fine adjust pot can make up for small differences in the correct frequency. The final step is to depress the proper range switch to read the distortion in %. This number is read on the analog meter in % THD+N. There is a low frequency filter switch to eliminate any hum components.

THERE ARE FOUR MORE INSTRUMENTS: LOUDSPEAKER IMPEADANCE METER,  
FREQUENCY METER, AUDIO TESTER, SWEEP FUNCTION GENERATOR  
CONTACT FACTORY FOR MORE DETAILS  
800-634-345 - 702-565-3400 - FAX 702-565-4828

MORE →



# OLD COLONY'S NEW REFERENCE TOOLS!



**COMPACT DISC PLAYER MAINTENANCE AND REPAIR** **BKT16**  
**\$14.95**

*Gordon McComb, John Cook*  
 Complete with a preventive maintenance schedule you can follow, this well-illustrated guide walks the reader through the steps involved in taking apart, cleaning, and lubricating a CD player. And if problems do occur, the troubleshooting techniques in this book provide easy relief. The book also includes background information on the theory and operation of CD players, what criteria you should use when shopping for one, a list of major manufacturers, a "similar model" cross reference table for troubleshooting, and a handy glossary. 1987, 245pp., 7 1/2 x 9 1/2, softbound.

**DESIGN AND BUILD AUDIO AMPLIFIERS —INCLUDING DIGITAL CIRCUITS** **BKT17**  
**\$19.95**

*Mannie Horowitz*  
 This second edition is a complete course in designing and building audio circuits for all electronics applications, covering JFETs, equivalent noise generators, and much more. Whether you need a preamp, amp, power amp, mixer, tone modification circuit, power supply, or special accessory, here is all the data you need to create completely up-to-date circuits. 1980, 350pp., 5 x 8, softbound.

**HOW TO MAKE PRINTED CIRCUIT BOARDS —WITH 17 PROJECTS** **BKT18**  
**\$15.95**

*Calvin R. Graf*  
 In addition to general workshop principles, in this book Graf discusses tools and safety habits and offers a complete refresher course on electronics theory, schematic diagrams, and soldering. He also explains design and layout as well as numerous types of boards and wiring. Key subjects covered include: how to get from an electronic schematic to a printed circuit board; etching a printed circuit board; cleaning, drilling, and mounting electronic parts onto the board; soldering and desoldering components; a listing of commercially available electronic project kits; and the various types of diagrams used in electronics, including block, pictorial, layout, and wiring. 1988, 207pp., 7 x 9, softbound.

**TROUBLESHOOTING AND REPAIRING AUDIO EQUIPMENT** **BKT19**  
**\$18.95**

*Homer L. Davidson*  
 This volume supplies all the basic information you need, along with specific examples, to fix stereo components, compact disc players, telephone answering machines, and much more. The detailed discussion of servicing and repair procedures for individual items includes probable causes of malfunctions and tips on difficult-to-diagnose problems. Scores of photos, diagrams, and drawings are used, as well as actual manufacturers' schematics and service literature. In addition to the equipment above, the book also covers auto CD players, compact cassette tape decks and portable stereo players, boom-box cassette players, deluxe amplifiers, auto stereo cassettes, and stereo turntables and speakers. 1987, 325pp., 7 1/2 x 9 1/2, softbound.

**ACOUSTICS: WAVES AND OSCILLATIONS** **BKW2**  
**\$34.95**

*S. N. Sen*  
 The result of the need in an honors course at Jadavpur University for a better text, this rare yet refreshing book supplements the physical bases of acoustics with mathematical and experimental details wherever possible. Topics include simple harmonic motion; theory of forced vibration and resonance; theory of coupled oscillations; vibration in an extended medium; vibration of strings, bars, tuning forks, membranes, rings, and air columns; reflection, refraction, diffraction, reception, and transformation of sound; sound measurement and analysis; acoustics of building; recording and reproduction of sound; and ultrasonics. India, 1990, 234pp., 6 1/2 x 10, hardbound.

**THE MUSICIAN'S GUIDE TO ACOUSTICS** **BKS35**  
**\$27.95**

*Murray Campbell, Clive Greated*  
 The result of the authors' fifteen-plus years of lecturing on musical acoustics to students at Edinburgh (U.K.) University, this book is a must for everyone with some musical background who feels the need for a clearer understanding of the practical basis of their art. While reasonable familiarity with musical notation and terminology is required to make best use of the book, only elementary mathematics is needed. Chapters include The Creation and Transmission of Musical Sounds; Hearing Musical Sounds; Anatomy of a Musical Note; Playing in Tune; Sound Production in Musical Instruments; Bowed and Plucked Stringed Instruments; Stringed Keyboard, Woodwind, Brass, and Percussion Instruments (one chapter each); Organs; The Human Voice; Electronic Instruments; and The Musical Environment. 1987, 612pp., 6 1/2 x 9 1/2, hardbound.

**SEMICONDUCTOR CROSS REFERENCE DATA BOOK** **BKS37**  
**\$19.95**

*Engineers of Howard W. Sams & Company*  
 Old Colony Sound Lab uses cross references all the time, every day. Of all the versions available for semiconductors, this is easily one of the very best. Sams' engineers have assembled replacement data for over 319,000 registered type and part numbers, including those for the United States, Europe, and the Far East, and present it here in a very easy-to-read and use format. Four suppliers are featured: NTE Electronics, Radio Shack, Philips ECG, and RCA. Semiconductors covered include bipolar transistors, FETs, diodes, rectifiers, ICs, SCRs, LEDs, modules, and thermal devices. 1991, 520pp., 8 1/2 x 11, softbound.

**THE RECORD SHELF GUIDE TO THE CLASSICAL REPERTOIRE** **BKSM1**  
**\$16.95**

*Jim Svejda*  
 From the host of American Public Radio's "The Record Shelf," this classy book is an irreverent, selective, and highly opinionated recordings guide to the best in CDs, LPs, and cassettes. Just as on his radio show, the author tries to include something pointed, interesting, amusing, or enlightening about each work, and then suggests which of the available recordings should be bought. 1988, 462pp., 6 x 9, softbound.

**THE FOUNDATIONS OF ACOUSTICS: BASIC MATHEMATICS AND BASIC ACOUSTICS** **BKSV2**  
**\$189.95**

*Eugen Skudrzyk*  
 The goal of this book is to provide the acoustician with a mathematically-based insight into the physical phenomena of acoustics. Combining into one volume such subjects as mathematics, dynamics, hydrodynamics, physics, statistics, signal processing, and electrical theory, the author comes up with a powerful reference for the academic or professional acoustician. Well illustrated. Austria, 1971, 790pp., 7 1/2 x 10, hardbound.

**AUDIO AMPLIFIER CONSTRUCTION** **BKEV10**  
**\$7.95**

*R. A. Penfold*  
 The purpose of this book is to provide the reader with a wide range of preamplifier and power amplifier designs that will hopefully fill almost anyone's needs. The preamp circuits include low noise microphone and RIAA types, a tape head preamp, a guitar preamp, and various tone controls. The power amplifier designs range from low-power, battery-operated to 100W MOSFET types. Also included is a 12V bridge amp capable of giving up to 18W output. All of the circuits are relatively easy to construct using the PCB or stripboard designs given. Where necessary any setting-up procedures are described, but in most cases no setting-up or test gear is required in order to successfully complete the project. Most of the designs should be within the capabilities of constructors with limited experience as well as more advanced hobbyists. United Kingdom, 1983, 128pp., 4 3/8 x 7, softbound.



**SALE ENDS JULY 1! BUY THREE, TAKE 10% OFF!**

**AUDIO ENTHUSIAST'S HANDBOOK**

*B. B. Babani*

This book discusses a number of audio and hi-fi topics, including record/playback curves, stylus compliance, vinyl recordings then and now, evaluating loudness, acoustic feedback, hi-fi vs. stereo, stereo tape track standards, equipment performance figures, and tracking error's cause, effect, and cure. United Kingdom, 1975, 96pp., 4 3/8 x 7, softbound.

**BKEV12**

**\$4.95**

**THE WOOD EFFECT**

*R. C. Johnsen*

According to the author, masked by random combination with other distortions in the music reproduction chain an unsuspected major contributor has lain hidden: aural sensitivity to "phase inversion," the Wood Effect. In this book the results of an extensive study of the Wood Effect are reported and discussed, including an exhaustive survey of the relevant literature. Although no means are proposed to correct countless errors, customary practice in acoustics and audio is severely scrutinized. BKMA1's subtitle is "Unaccounted Contributor to Error and Confusion in Acoustics and Audio." 1988, 99pp., 6 x 9, softbound.

**BKMA1**

**\$12.95**

**BUILD YOUR OWN SOLID STATE HI-FI AND AUDIO ACCESSORIES**

*M. H. Babani, editor*

This volume presents the reader with the design and construction plans for a variety of useful projects, including a stereo decoder, three-channel stereo mixer, FET preamp for ceramic PUs, microphone preamp with adjustable bass response, stereo dynamic noise filter, speaker protector, and voice-operated relay. United Kingdom, 1976, 96pp., 4 3/8 x 7, softbound.

**BKEV13**

**\$4.95**

**THE HOMEBUILT DYNAMO: DYNAMO DESIGN AND CONSTRUCTION WITH CERAMIC MAGNETS**

*Alfred T. Forbes*

We added this book to our offerings not just because it is a physically handsome volume, but also because it is unique and, as many reviewers have pointed out, an experimenter's "delight." In 1969, Al Forbes and his wife decided to live the simple life and retreated to a parcel of undeveloped land. Soon enough, they needed a generator. This book is the extremely detailed account of how Al built one from scratch. But it is more than that: it's a head-on encounter with just about every principle of electricity, magnetism, and hands-on construction known to man. Along the way, incidentally, the reader runs into how to build precision wire-winding jigs, a small lifting magnet, a foot-powered version of the dynamo, a diamond saw, a sheet metal cutter, and a 139-pound flywheel. With more than 300 illustrations, this volume is slowly becoming a worldwide cult favorite among do-it-yourselfers everywhere. New Zealand, 182pp., 8 1/2 x 12, hardbound.

**BKTF1**

**\$64.95**

**DIGITAL AUDIO PROJECTS**

*R. A. Penfold*

The first section of this book takes a look at the basic principles involved in converting an audio signal into digital form and then converting it back again to an analog signal. It also deals with some practical aspects that have to be borne in mind when considering digital audio projects. The second section contains some useful and extremely interesting practical circuits for constructors to build and experiment with. The projects are not highly complex, but nonetheless they are probably beyond the range of complete beginners. United Kingdom, 1988, 96pp., 4 3/8 x 7, softbound.

**BKEV14**

**\$9.95**

**THE VTL VACUUM TUBE LOGIC BOOK**

*David Manley*

This third edition of every tube freak's must-have book is replete with tube matter of every description, including circuits, specifications, reviews, and history, presented with more than a liberal dash of humor and puckishness. 1991, 120pp., 5 1/2 x 8 1/2, softbound.

**BKVT1**

**\$12.95**

**ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILWAYS**

*R. A. Penfold*

This innovative book is an examination of the problem of interfacing the computer to the layout. It includes projects consisting of various types of controllers, including a high-quality pulse type, as well as circuits for train position sensing, signal and electric points control, sound effects, and more. Projects are equally adaptable to large or small layouts. United Kingdom, 1986, 96pp., 4 3/8 x 7, softbound.

**BKEV15**

**\$9.95**

**AUDIO AND HI-FI ENGINEER'S POCKET BOOK**

*Vivian Capel*

This book is a concise collection of practical and relevant data for anyone working on sound systems. The topics covered include microphones, record players, compact discs, tape recording, high-quality radio, amplifiers, loudspeakers, and public address systems. A lengthy section on acoustics is included for dealing with most aspects a technician is likely to encounter, from human hearing to sound insulation, and qualities such as heat and magnetism are covered as well. This is a pocket book, in a very handy size. United Kingdom, 1988, 190pp., 3 3/4 x 7 3/4, hardbound.

**BKHM1**

**\$27.95**

**MODEL RAILWAY PROJECTS**

*R. A. Penfold*

This handbook provides a number of useful but reasonably simple projects for the model railway enthusiast to build, including such things as controllers and signals and sound effects units. Stripboard layouts are provided for each project. United Kingdom, 1981, 112pp., 4 3/8 x 7, softbound.

**BKEV16**

**\$6.95**

**MODEL RAILROAD SPECIAL!**

**BKEV/RR**

**\$14.95**

Both *Electronic Circuits for the Computer Control of Model Railways* (BKEV15) and *Model Railway Projects* (BKEV16), at a savings of \$1.95!

**INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE**

*Adrian Michaels*

This book, one of two transistor guides recommended by Old Colony, is designed to help the user find possible substitutes for a popular, user-oriented selection of modern transistors. It includes devices produced by over 100 manufacturers, and wherever possible the equivalents are subdivided into European, American, and Japanese types. Also shown are the material type, polarity, and manufacturer, as well as an indication of device use or application. United Kingdom, 1981, 1990, 320pp., 4 3/8 x 7, softbound.

**BKEV17**

**\$11.95**


**STRUCTURE-BORNE SOUND**

*L. Cremer, M. Heckl*

Translated from the German and revised by E. E. Ungar, this second edition is a thorough introduction to structural vibrations, with emphasis on those at audio frequencies, and the attendant radiation of sound. The book presents in-depth discussions of fundamental principles and basic problems, in order to enable the reader to understand and solve his own. Included are chapters on the measurement and generation of vibrations and sound; the various types of structural wave motions; structural damping and its effects; impedances and vibration responses of the important types of structures; the attenuation of vibrations, and sound radiation from structures. Germany, 1973, 1988, 573pp., 6 1/2 x 9 1/2, hardbound.

**BKSV4**

**\$84.95**

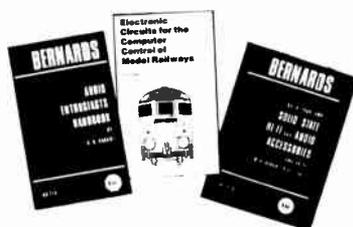

MORE →



# BUY FOUR, TAKE 15% OFF! SALE ENDS JULY 1!



## HOW TO USE OP AMPS

E. A. Parr

**BKEV3**

**\$9.95**

Parr's book is a designer's guide covering many operational amplifiers which serves both as a source book for circuits and as a reference book for design calculations. The approach is as nonmathematical as possible and is thus equally understandable by the hobbyist or the engineer. United Kingdom, 1982, 160pp., 4 3/8 x 7, softbound.

## AUDIO PROJECTS

F. G. Rayer

**BKEV4**

**\$6.95**

This book covers in detail the construction of a wide range of audio projects, including preamps, power amps, mixers, tone controls, and many others. All are fairly easy to build, and to that end the author has included a number of board layouts and wiring diagrams. United Kingdom, 1981, 96pp., 4 3/8 x 7, softbound.

## AN INTRODUCTION TO LOUSPEAKERS AND ENCLOSURE DESIGN

V. Capel

**BKEV5**

**\$9.95**

In this volume may be all you need to know about the theory and operation of speakers and the various boxes into which they may be fitted. The book also includes the complete design and construction details for the inexpensive but high quality enclosure called the "Kapellmeister." United Kingdom, 1988, 160pp., 4 3/8 x 7, softbound.

## MODERN OP-AMP PROJECTS

R. A. Penfold

**BKEV6**

**\$6.95**

BKEV6 includes a wide range of construction projects which make use of the specialized operational amplifiers available today, including low noise, low distortion, ultra-high input impedance, low slew rate, and high output current types. Circuits using transconductance types are also included. United Kingdom, 1982, 112pp., 4 3/8 x 7, softbound.

## HOW TO GET YOUR ELECTRONICS PROJECTS WORKING

R. A. Penfold

**BKEV7**

**\$6.95**

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building projects.

Chapter 1 deals with mechanical faults such as tracing dry joints, short circuits, broken PCB tracks, and so forth. The construction and use of a tristate continuity tester to help in the above is also covered. Chapter 2 deals with linear analog circuits and also covers the use and construction of a signal injector/tracer which can be used to locate and isolate faulty areas.

Chapter 3 considers ways of testing the more common components such as resistors, capacitors, op amps, diodes, transistors, SCRs, unijunctions, and so forth, with the aid of only a limited amount of test equipment. Chapter 4 deals with both TTL and CMOS logic circuits and includes the use and construction of a pulse generator to help in fault-finding. United Kingdom, 1982, 96pp., 4 3/8 x 7, softbound.

## CONCERT HALL ACOUSTICS

Yoichi Ando

**BKSV3**

**\$69.95**

Number 17 in the Springer Series in Electrophysics, this book provides an interdisciplinary approach to solving acoustic design problems in concert halls. Considered one of the original sources in this field, the volume explains in detail the importance and interrelationship of total sound energy, delay of early reflections, reverberation, and the "spatial-binaural criterion," a measure of the spatial impression of the sound field. Germany, 1985, 151pp., 6 1/4 x 9 3/8, hardbound.

## ACOUSTICS SOURCE BOOK

Sybil P. Parker, editor-in-chief

**BKMHS**

**\$39.95**

This widely-sought member of the McGraw-Hill Science Reference Series is an accumulation and explanation of all that has to do with acoustics, focusing on basic concepts, sound production, sound transmission, sound detection, and practical applications. One of the clearest and most basic references on acoustics available today. 1988, 333pp., 7 x 9 1/2, hardbound.

## LISTENING: AN INTRODUCTION TO THE PERCEPTION OF AUDITORY EVENTS

Stephen Handel

**BKMT1**

**\$39.95**

This book combines broad coverage of acoustics, speech and music perception, psychophysics, and auditory physiology in a lively introduction to the perception of music and speech events. Coherence and clarity are the hallmarks of this book, and the author's strategy is to discuss specific points in detail rather than every possible thing superficially. All in all very fascinating, especially the treatment of the physiology and neurophysiology of the auditory system. 1989, 597pp., 6 1/2 x 9 1/2, hardbound.

## AUDITORY PERCEPTION

F. Alton Everest

**BKMX1**

**\$159.95**

This thorough, inventive, and understandable audio training course on psychoacoustics comes complete with eight lessons on four tapes and a manual with hundreds of technical diagrams illustrating the concepts. The aural examples and classic experiments enable the student to clearly and quickly comprehend the complexity of the hearing process. Topics include the perception of delayed sounds, auditory filters, masking of critical bands, the perception of pitch, timbre, and much more. 1986, 104pp., 5 1/2 x 8 1/2, softbound, 4 cassettes, vinyl case for all.

## POWER ELECTRONICS HANDBOOK: COMPONENTS, CIRCUITS, AND APPLICATIONS

F. F. Mazda

**BKB4**

**\$79.95**

The purpose of this book is to provide all the information required by power electronics engineers. It describes the design of power circuits used for a variety of applications, the characteristics of power semiconductor devices, and how they are used in power circuits. The author's approach is to give the maximum amount of information in a concise form, with the emphasis on the practical rather than the theoretical. United Kingdom, 1990, 417pp., 6 1/2 x 9 1/2, hardbound.

## AUDIO ELECTRONICS REFERENCE BOOK

Alan R. Sinclair, editor

**BKBL1**

**\$164.95**

Written by a team of expert, specialist contributors, this volume is of interest and profit to audio design and service engineers and technicians, as well as any amateur users of audio equipment who want to learn the technology of the art. BKBL1 is both a summary and a guide to the new state of audio, and includes in its coverage those areas where professional and amateur audio have begun to overlap, such as electronic music and public address systems. United Kingdom, 1989, 615pp., 6 1/2 x 9 1/2, hardbound.

## TROUBLESHOOTING AND REPAIRING COMPACT DISC PLAYERS

Homer L. Davidson

**BKT20**

**\$18.95**

This is an invaluable reference for both the electronics technician and the do-it-yourselfer alike. With it, you'll be able to troubleshoot and repair servo control loops, remote control systems, optical lenses and laser assemblies, and much more! Detailed examples of actual repair and adjustment procedures and a chapter on the care and handling of the discs themselves further enhance the usefulness of this book. 1989, 337pp., 7 1/2 x 9 1/2, softbound.



## INCREDIBLE INTRODUCTORY BOOK SALE!

### LOUDSPEAKERS, VOLUME 1

Raymond E. Cooke, editor

From The Audio Engineering Society's Anthology Series, 61 papers, covering the years 1953 to 1977, written by the world's greatest transducer experts and inventors on the design, construction, and operation of loudspeakers. 1980, 448pp., 8 1/4 x 11 1/4, softbound.

**BKAS1/1**  
**\$29.95**

### LOUDSPEAKERS, VOLUME 2

Raymond E. Cooke, editor

Also from The Audio Engineering Society's Anthology Series, 49 papers from 1978 to 1983 by experts in loudspeaker technology, extending the work initiated in Volume 1. 1984, 464pp., 8 1/4 x 11 1/4, softbound.

**BKAS1/2**  
**\$29.95**

### LOUDSPEAKERS SET!

Raymond E. Cooke, editor

From The Audio Engineering Society's Anthology Series, both BKAS1/1 (Volume 1) and BKAS1/2 (Volume 2) as above, at a savings of \$5.95!

**BKAS/S**  
**\$53.95**

### MICROPHONES

Louis A. Abbagnaro, editor

Sixty-three papers covering calibration and testing, general purpose microphones, directional microphones, miniature types, and associated electronic circuits. From The Audio Engineering Society's Anthology Series. 1979, 392pp., 8 1/4 x 11 1/4, softbound.

**BKAS2**  
**\$29.95**

### SOUND REINFORCEMENT

David L. Klepper, editor

Seventy-three papers dealing with the significant aspects of the development of sound-reinforcement technology and its practical application to sound system design and installation. From The Audio Engineering Society's Anthology Series. 1978, 339pp., 8 1/4 x 11 1/4, softbound.

**BKAS3**  
**\$29.95**

### STEREOPHONIC TECHNIQUES

John M. Eargle, editor

From The Audio Engineering Society's Anthology Series, 67 articles and documents on the history, development, and applications of stereophonic techniques for studio technology, broadcasting, and consumer use. 1986, 390pp., 8 1/4 x 11 1/4, softbound.

**BKAS4**  
**\$29.95**

### SPICE: A GUIDE TO CIRCUIT SIMULATION & ANALYSIS USING PSpice

Paul W. Tuinenga

Designed as a reference on PSpice for the design and analysis of analog circuits, this book clearly explains how to use the features of PSpice to solve common electrical and electronic problems, as well as some in nonelectrical areas. Topics include DC operation, transfer functions, frequency response, and noise analysis. SPICE is an acronym for Simulation Program with Integrated Circuit Emphasis, and PSpice is a SPICE-derived simulator created by MicroSim Corporation. Companion software for the book is available (see below). 1988, 200pp., 7 x 9 1/2, softbound.

**BKPH2**  
**\$19.95**

### SPICE BOOK/SOFTWARE SPECIAL!

**BKPH2/S**  
**\$27.95**

Student-version software to accompany BKPH2 is available for both the IBM PC and Macintosh II. The PSpice program can simulate circuits of up to five nodes and ten transistors, with the parameters inserted by the user. Special BKPH2/S includes both the book and one software package at a savings of \$4.95!

Software packages available (be sure to specify!):

SOF-SPC1B5GD IBM PC

SOF-SPC2B5GD IBM PS 2

SOF-SPC1M3GD Macintosh II

### TIME DELAY SPECTROMETRY

John R. Prohs, editor

From The Audio Engineering Society's Anthology Series, 32 articles of the works of Richard C. Heyser on measurement, analysis, and perception, reprinted from the pages of the *Journal of the Audio Engineering Society* and other publications representative of the field, including *Audio* magazine and that of IREE Australia. The anthology serves as a memorial to the author's work and as fundamental material for future developments in audio, and will undoubtedly provide the stimulus for expanded discussion. 1988, 280pp., 8 1/4 x 11 1/4, softbound.

**BKAS5**  
**\$29.95**

### AUDIO IN DIGITAL TIMES: CONFERENCE PROCEEDINGS

Forty-four papers presented by experts on digital audio at The Audio Engineering Society's Seventh International Conference held in Toronto on 14-17 May 1989. Digital audio, from the history, basics, hardware, and software, to the ins and outs, was the topic of the conference. Illustrated with many figures and tables. 1990, 384pp., 8 1/4 x 11 1/4, softbound.

**BKAS6**  
**\$34.95**

### THE SOUND OF AUDIO: CONFERENCE PROCEEDINGS

Twenty-four papers presented by authors highly regarded in the engineering community at The Audio Engineering Society's Eighth International Conference held in Washington, D.C., on 3-6 May 1990. The topics were devoted to the progress of sound, including measurement, recording, and reproduction. Textbook style, fully illustrated. 1990, 384pp., 8 1/4 x 11 1/4, softbound.

**BKAS7**  
**\$34.95**

### DIGITAL AUDIO: COLLECTED PAPERS

Barry Blessner, et al., editors

First publication of papers presented at The Audio Engineering Society's Premiere International Conference held in Rye, N.Y., on 3-6 June 1982, authored by the world's leading experts in the application of digital techniques in the field of audio engineering. Twenty-five of the 27 papers are transcribed, edited, and published for the first time. Subjects include basics, converters, measurements, rate conversion, recording formats, error correction, manufacturing, and applications. Includes a Soundsheet disk with audio demonstrations of digitally synthesized sounds. 1983, 268pp., 8 1/4 x 11 1/4, softbound.

**BKAS8**  
**\$34.95**

### MICROPHONES: TECHNOLOGY AND TECHNIQUE

John Borwick

Beginning with a brief history of the relevant technology, this book then goes on to explain the basic theory of acoustics, electricity, and magnetism. The working principles and design of all types of microphones are explained in considerable detail, with examples of popular current models and descriptions of microphone accessories. The second half of the book provides guidelines on the creative balance techniques to be used for musical instruments, voices, and ensembles of all kinds, in both classical and pop music. Production methods are outlined both for studios and for on location, with notes on public address operations for live shows. Borwick is considered THE authority. United Kingdom, 1990, 241pp., 7 1/2 x 9 1/2, softbound.

**BKB3**  
**\$29.95**

### THE ART OF ELECTRONICS


Paul Horowitz, Windfield Hill

Completely up-to-date with the latest technology and standards, this second edition features completely rewritten chapters on microcomputers and microprocessors, digital electronics, and low-power and micro-power design (both analog and digital). Many new tables have been added, including ones for A/D and D/A converters, digital logic components, and low-power devices. The quintessential electronics text and reference. 1989, 1100pp., 7 1/2 x 10 1/4, hardbound.

**BKC1**  
**\$54.95**


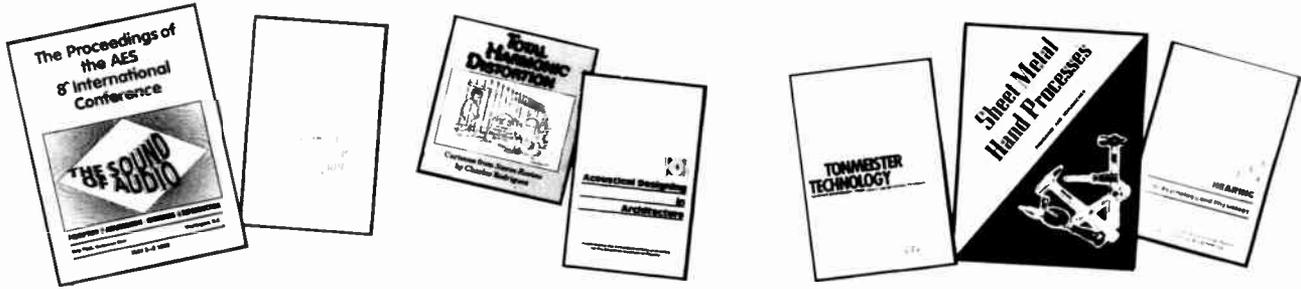
# HARD-TO-FIND BARGAINS FROM AROUND THE WORLD!



## ACOUSTICAL MEASUREMENTS

Leo L. Beranek

Here is a completely revised edition of the famous text by the well-known authority, with more than half the pages and chapters revised or completely rewritten to cover new developments in acoustical instruments and measurement procedures, including sound and vibration meters, intensity meters, spectrum analyzers, recorders, computers, and noise measurement devices. 1948, 1989, 841pp., 5 3/4 x 8 3/4, hardbound.

**BKAC1**

**\$44.95**

## ACOUSTICS—AN INTRODUCTION TO ITS PHYSICAL PRINCIPLES AND APPLICATIONS

Allan D. Pierce

This volume introduces the physical principles and theoretical basis of acoustics, concentrating on those concepts and points of view that have proven useful in applications and phenomena such as noise control, underwater sound, architectural acoustics, audio engineering, nondestructive testing, remote sensing, and medical ultrasonics. The text is supplemented by problems and their answers. 1981, 1989, 678pp., 6 1/4 x 9 1/2, hardbound.

**BKAC2**

**\$37.95**

## EXPERIMENTS IN HEARING

Georg von Békésy

Considered obligatory reading for all those who want to claim literacy in the auditory sciences, this classic on hearing contains many of the vital roots of contemporary auditory knowledge. 1960, 1989, 760pp., 6 x 9, softbound.

**BKAC3**

**\$27.95**

## ACOUSTICAL DESIGNING IN ARCHITECTURE

Vern O. Knudsen, Cyril M. Harris

This book is a comprehensive, nonmathematical treatment of architectural acoustics, completely revised with new illustrations and updated to eliminate obsolete materials. In handbook format, it covers all the general principles of acoustical designing and includes specific applications. 1950, 1980, 408pp., 5 3/8 x 8 1/2, softbound.

**BKAC4**

**\$27.95**

## ACOUSTICS

Leo L. Beranek

This volume is an indispensable source of practical acoustical concept and theory for acoustical and electrical engineers, scientists, and consultants, with new information on microphones, loudspeakers and speaker enclosures, room acoustics, and acoustical applications of electromechanical circuit theory. 1954, 1986, 491pp., 6 x 9, softbound.

**BKAC5**

**\$27.95**

## MARQUETRY AND INLAY: TWENTY DECORATIVE PROJECTS

Alan and Gill Bridgewater

Complete with 200 illustrations, a glossary, and an introduction to tools and techniques, BKT21 provides step-by-step directions for easy-to-do projects. This book gives woodworkers an opportunity to add a valuable new skill to their repertoire—inserting fine woods and decorative veneers into finished surfaces. 1989, 192pp., 7 x 10, softbound.

**BKT21**

**\$15.95**

## TONMEISTER TECHNOLOGY: RECORDING ENVIRONMENTS, SOUND SOURCES AND MICROPHONE TECHNIQUES

Michael Dickreiter

Recently translated from the German by Stephen F. Temmer, this rare book for the first time provides an English-language reference integrating music and musical engineering. Used by the German Broadcasting System Technical Training Center as a text to train people who graduate from a music conservatory and opt to go into broadcast, TV, recording, or sound reinforcement engineering, this book will appeal to neophytes as well as professionals in the music and audio engineering fields. Profusely illustrated, with every other page illustrations. 1984, 1989, 142pp., 6 x 9, softbound.

**BKTE1**

**\$19.95**

## HEARING: ITS PSYCHOLOGY AND PHYSIOLOGY

Stanley Smith Stevens, Hallowell Davis

This multidisciplinary book leads readers from the fundamentals of the psychophysiology of hearing to a complete understanding of the anatomy and physiology of the ear, including the relationship between stimulus and sensation. 1938, 1983, 512pp., 5 1/2 x 8 1/2, softbound.

**BKAC6**

**\$27.95**

## ELECTROACOUSTICS: THE ANALYSIS OF TRANSDUCTION AND ITS HISTORICAL BACKGROUND

Frederick V. Hunt

This volume provides a comprehensive analysis of the conceptual development of electroacoustics, including the origins of echo ranging, the crystal oscillator, the evolution of the dynamic loudspeaker, and electromechanical coupling. 1954, 1982, 260pp., 5 1/2 x 8 1/2, softbound.

**BKAC7**

**\$27.95**

## VIBRATION AND SOUND

Philip M. Morse

One of the most widely used texts and references on the science of acoustics, this volume provides students and professionals alike with a broad spectrum of acoustics theory, including wave motion, radiation problems, the propagation of sound waves, and transient phenomena. 1936, 1981, 468pp., 6 x 9, softbound.

**BKAC8**

**\$27.95**

## ACOUSTICS/HEARING SPECIAL #1

Your choice of TWO from BKAC3 through BKAC8, at a savings of \$5.95! Be sure to specify books. (BKAC1 and BKAC2 not eligible.)

**BKAC/X2**

**\$49.95**

## ACOUSTICS/HEARING SPECIAL #2

Your choice of THREE from BKAC3 through BKAC8, at a savings of \$8.90! Be sure to specify books. (BKAC1 and BKAC2 not eligible.)

**BKAC/X3**

**\$74.95**

## TOTAL HARMONIC DISTORTION —CARTOONS FROM STEREO REVIEW

Charles Rodrigues

This hilarious collection of 118 of the author's classic cartoons on audio, video, and music is the perfect gift and/or a wonderful conversation piece. Also featured are a foreword by William Livingstone and an illustrated autobiographical sketch by Rodrigues himself. One of a kind. 1988, 132pp., 6 1/2 x 7, softbound.

**BKPB1**

**\$7.95**

## SHEET METAL HAND PROCESSES

Claude J. Zinngarbe, Fred W. Schumacher

For help in building that special enclosure, this volume will prove indispensable, introducing the beginning sheet metal technician to basic instruction in the properties and selection of metal and the processes performed with measuring and marking, bench, cutting, piercing, joining, and soldering tools. BKDE2 includes an excellent selection of illustrations, and every process is described in an easy-to-understand, step-by-step fashion. 1974, 209pp., 7 3/4 x 10 1/4, softbound.

**BKDE2**

**\$13.95**

## CABINETMAKING, PATTERNMAKING, AND MILLWORK

Gaspar J. Lewis

If making your own speaker cabinets has led you into woodworking, this book will be a great addition to your library. Designed for advanced high school, vocational, technical, and apprenticeship programs, it provides the reader with the skills necessary for proficiency in each of the three areas of specialization. Also included are three sections common to all three fields: the nature of wood and its uses; how to use hand tools, portable power tools, and stationary woodworking machines; and methods of joinery. 1981, 438pp., 7 1/2 x 9 1/2, hardbound.

**BKDE4**

**\$22.95**

**BUY FIVE OR MORE, TAKE 20% OFF! SALE ENDS JULY 1!**



**BEGINNER'S GUIDE TO READING SCHEMATICS**

Robert J. Traister

This outstanding handbook takes you step-by-step through every phase of understanding and using schematics. Coverage includes how and why schematics are used; how each symbol is derived, used, and drawn; how individual symbols are combined to represent electronic circuits; proper numbering of components; and units of electronic measurement. 1983, 134pp., 5 x 8 1/2, softbound.

**BKT14**  
**\$11.95**

**AUDIO (BABANI ELEMENTS OF ELECTRONICS, BOOK 6)**

F. A. Wilson

In this book, analysis of the sound wave and an explanation of acoustical quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapters on audio systems, amplifiers, oscillators, disc and magnetic recording, and electronic music. United Kingdom, 1985, 320pp., 4 3/8 x 7, softbound.

**BKEV8**  
**\$11.95**

**GREAT SOUND STEREO SPEAKER MANUAL —WITH PROJECTS**

David B. Weems

In this book, Weems strips the mystery from drivers, crossovers, and construction materials in order to help you build your own speakers and get the best possible performance from all of your sound equipment. Included are current trends in speaker design, getting great stereo sound from units you build yourself, calculating design parameters, transmission-line systems, crossover networks, and much more! 1990, 248pp., 7 1/2 x 9, softbound.

**BKT15**  
**\$16.95**

**AUDIO AMPLIFIER FAULT-FINDING CHART**

C. E. Miller

This tool is actually a foldable wall chart which will help the user trace most common faults which might occur in audio amplifiers. All the reader has to do is select one of the faults shown at the top of the chart and then follow the arrows, carrying out the suggested checks in sequence until the fault is cleared. United Kingdom, 1987, 17 1/2 x 25.

**BKEV9**  
**\$4.95**

**PRACTICAL STEREO AND QUADRAPHONY HANDBOOK**

B. B. Babani

A reference book for all those interested in modern stereophonic and multi-sound-channel equipment. The subjects covered include explanations of many of the technical terms used in this audio field, stereo equipment and techniques, positioning of multiple loudspeakers for best results, stereo and four-channel pickups, and more. United Kingdom, 1975, 96pp., 4 3/8 x 7, softbound.

**BKEV11**  
**\$4.95**

**THE ART OF DIGITAL AUDIO**

John Watkinson

This book begins with clear definitions of technical terms specific to particular technologies employed in digital audio. The theory of each area is then discussed and their practical applications considered. All of the major digital recording formats are explained. Consumer machines, compact discs, DAT, and mastering recorders are covered, as well as multitracking. The professional's first digital audio reference, written in laymen's terms. United Kingdom, 1988, 500pp., 6 1/2 x 9 1/2, hardbound.

**BKB2**  
**\$52.95**

**AUDIO SYSTEMS DESIGN AND INSTALLATION**

Philip Giddings

This book is a practical, hands-on tool designed to help the audio professional find information quickly. The many useful tables, checklists, photos, and diagrams included are all intended to improve and expedite system design. Giddings also provides many effective tips and strategies for efficient audio system installation. 1990, 350pp., 7 3/8 x 9 1/4, hardbound.


**BKS33**  
**\$59.95**

**AUDIO TECHNOLOGY FUNDAMENTALS**

Alan A. Cohen

*Audio Technology Fundamentals* is a brief yet comprehensive overview of the electric and electronic circuitry used in typical audio systems. It provides students, audio beginners, and musicians with an introduction to electric circuits and basic audio concepts. The book is especially appropriate for musicians who want to record their performances and electronically modify the recording. 1989, 250pp., 7 3/8 x 9 1/4, softbound.

**BKS34**  
**\$24.95**

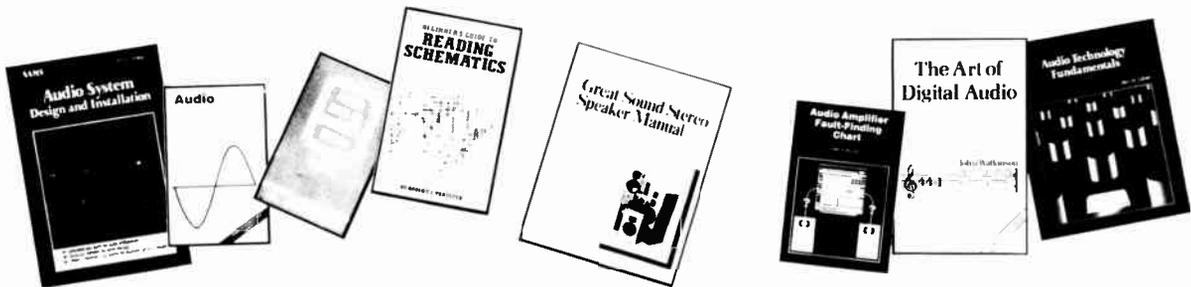

**YES! Please send me**

\_\_\_\_\_ BK \_\_\_\_\_ @ \$ \_\_\_\_\_ = \$ \_\_\_\_\_  
 \_\_\_\_\_ BK \_\_\_\_\_ @ \_\_\_\_\_ = \_\_\_\_\_  
 SUBTOTAL = \_\_\_\_\_  
 LESS SALE DISCOUNT = \_\_\_\_\_  
 TOTAL = \_\_\_\_\_  
 PLUS SHIPPING (see right) = \_\_\_\_\_  
 TOTAL ORDER = \$ \_\_\_\_\_

**SALE ENDS JULY 1!**



**OLD COLONY SOUND LAB**

PO Box 243, Dept. E91  
Peterborough, NH 03458  
24-HOUR LINES:  
TEL. (603) 924-6371  
FAX (603) 924-9467

NAME \_\_\_\_\_ MAGIC NO \_\_\_\_\_

STREET & NO \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

MC/VISA \_\_\_\_\_ EXP. DATE \_\_\_\_\_

PAYMENT BY:  MC/VISA  CHECK  
 MONEY ORDER

**SHIPPING:** In US, please add \$2 for first book, 75¢ each additional. In Canada, please add \$4.50 for first book, 75¢ for each additional. Others, please add 20% for surface delivery. Airmail: Please inquire.

FOREIGN CHECKS MUST BE IN US FUNDS  
DRAWN ON US BANK.

**CALL OR WRITE FOR YOUR FREE CATALOG!**

# PLAYING RECESS(ION)

Right in the middle of what economists are now calling a recession, many US electronics vendors are telling some customers they don't want their business. These customers' crime appears to be that they don't need enough. A number of vendors whose primary customer base has been the individual consumer are no longer happy to sell to that base since the big-ticket blandishments of the military/industrial complex in this country are so large and so lucrative that the individual buyer is no longer "interesting."

The problem is made more complex by the habit of US manufacturers to assign exclusive distribution rights to selected companies. The contracts are subject to sudden death shifts, as well. A distributor can come to work on a Monday morning only to discover that his right to sell a line has been lifted summarily and assigned to a competing company.

This accounts, in some measure, for the distributor businesses' resemblance to mayflies, who seem to appear and disappear with equal rapidity. It is now a regular feature of the American business scene where money is the only consideration. We are no longer content to make a living, the object seems to be to make a killing—and to get out fast. Business managerial style is a vicious scramble to the top, a management slot with a golden parachute attached, and the drive to maximize profits at any cost. The cost is usually the company's integrity and financial soundness. Naturally the manager bails out quickly before the full slide into deep troubles begins to occur—or the sudden crash takes place.

With such management style in place, it is not difficult to see why we are in this recession. When sales drop, the retrenchment begins and such managers, or their less fortunate successors, chop and cut into the skilled work force of the company in an effort to save money. When this becomes a pervasive technique throughout industry, everyone becomes a smaller vendor, and a smaller customer. Why should it be surprising that a "recession" results? US business seems to have made recessing stylish lately.

I suggest that such times and such myopia offer opportunities to those of you with courage and imagination. Look around to see what people need. Many needs are unmet. One of the largest is ecological, another is the technological evolution of the home.

As an example of the former, your local service station has a problem with the oil drained from your crankcase. It can no longer be dumped in a hole on the back corner of the parking lot. Service station owners must now pay for disposal. Someone has the bright idea that old oil might be good fuel. Burning it requires a special furnace costing under \$3,000. If someone suggested you might permanently cut your fuel oil bill in half by a primary investment of \$3,000, what would your response be?

The smart entrepreneur will find a way to sign up the service stations

in his area to collect their oil once a month charging a fee of only 25¢ a gallon, buy a second-hand oil delivery truck, sell some lucky homeowners a new furnace and guarantee a fuel oil supply at 50¢ a gallon for as long as nearly every American continues to drive a car.

The American home is being converted into an electronic obstacle course. Service opportunities abound for maintenance of microwaves, intercoms, protection devices, garage door openers, and much else. Terms could be an annual contract, or by the service call. Such an organization would also have a unique opportunity to offer advice and sales of new devices as they inevitably appear. Technology is still fearsome to many and your help could be not only welcome, but worth cash.

Finally, we are better supplied with materials to make pottery throughout suburban America than to build electronic projects. And the crunch is not just a problem for hobbyists. Our mail-order electronics vendors who don't want orders under \$50 or \$100 are a problem for the many independent development labs throughout the US as well. Such companies build sample quantities of new devices to confirm their integrity. The needs of such companies are quite similar to those of the serious hobbyist. But developers complain constantly about how difficult their life has become because our marketplace in the US is of such a scale that companies outgrow their small customers who helped them get started.

I hope many of you will give serious thought to the opportunities even these few facts suggest. If our current electronics vendors are suffering from gigantism and are uninterested in supplying the small company or the hobbyist, then there's a market asking for help and assistance. The idea I am suggesting here is clearly exemplified by a new advertiser in our classified section this month.

The operation is mail order. Resistors are the product: 1,000+, ± 5%, ¼W, carbon film types, arranged neatly in a box of five or ten of each value for under \$20 delivered. A neat service with credit cards accepted, an 800 number, and a reorder blank.

The other advertisers in this magazine are, so far as I know, firmly committed to supplying you with the parts you need. If you wish for parts not immediately available, let our advertisers know about it. You will also be seeing more ads from European-based vendors who are eager to hear from you and to help with what you need. Your credit card and your FAX can reach anywhere in the world, as fast as you can dial.

For the adventurous, opportunities abound. The computers and software are plentiful and lots of customers are looking vainly for the good stuff they need to build, rebuild, and design. If you are tired of playing recess and of those who are, get going. And let us know how you are doing.—E.T.D.

Published by Audio Amateur Publications, Inc.

**Editor/publisher:** Edward T. Dell, Jr.  
**Editorial Offices:**  
305 Union St., P.O. Box 876  
Peterborough, NH 03458-0876 USA

Telephone: 603-924-9464 (National)  
or +1 (603) 924-9464 (International)  
**FAX:** (603) 924-9467 (National)  
or +1 (603) 924-9467 (International)

**Advertising:** Raily Dennis  
Telephone: (603) 924-9750  
**FAX:** (603) 924-9467

**Subscriptions:** Katharine Gadwah  
*Elektor Electronics USA*  
Post Office Box 876,  
Peterborough, New Hampshire 03458

**Subscriptions to *Elektor Electronics USA*** are available **ONLY** in the fifty United States, Canada, Puerto Rico, the Virgin Islands and those Pacific territories administered by the United States of America.

**European Offices:**  
**Elektuur BV**  
Postbus 75  
6190 AB BEEK  
The Netherlands  
Telephone: 011 31 4638 9444  
Telex: 56617 (elekt nl)  
**FAX:** 011 31 4637 0161  
**Managing Director:** M.M.J. Landman

**Overseas Editions:**  
**FRANCE**  
**Elektor sarl**  
Les Trois Tilleulis  
B.P. 59; 59850 NIEPPE  
**Editors:** D.R.S. Meyer  
G.C.P. Raedersdorf

**GERMANY**  
**Elektor Verlag GmbH**  
Susterfeld Strasse 25  
5100 AACHEN  
**Editor:** E.J.A. Krempelsauer

**GREECE**  
**Elektor EPE**  
Kariskaki 14  
16673 Voula—Athens  
**Editor:** E. Xanthoulis

**INDIA**  
**Elektor Electronics PVT Ltd**  
Chhotani Building  
52C, Proctor Road, Grant Road (E)  
BOMBAY 400 007  
**Editor:** Surendra Iyer  
**ISRAEL**  
**Elektorcal**  
P O Box 41096  
TEL AVIV 61410

**Publisher:** M. Avraham  
**NETHERLANDS**  
**Elektuur BV**  
Peter Treckpoelstraat 2-4  
6191 VK BEEK  
**Editor:** P.E.L. Kersemakers

**PAKISTAN**  
Electro-shop  
35 Naseem Plaza  
Lasbella Chawk  
KARACHI 5  
**Editor:** Zain Ahmed

**PORTUGAL**  
**Ferreira & Bento Lda.**  
R.D. Estef-83-ni, 32-1°  
1000 LISBOA  
**Editor:** Jeremias Sequeira

**SPAIN**  
**Resistor Electronica Aplicada**  
Calle Maudes 15 Entio C.  
28003 MADRID  
**Editor:** Agustin Gonzales Buella  
**SWEDEN**  
**Electronic Press AB**  
Box 5505  
14105 HUDDINGE  
**Editor:** Bill Cedrum  
**UNITED KINGDOM**  
Down House  
Broomhill Road  
LONDON SW18 4JQ  
England UK  
**Editor/Publisher:** Len Seymour

Printed in the United States of America.  
ISSN: 1051-5690

## SINGLE-BOARD COMPUTER

Rapid Systems has announced the PX1260, a high-speed, high-performance 33MHz, Intel 386-based CPU module for the PCXI EISA passive backplane. This plug-in CPU module features optional integrated 40Mb hard disk with 3½", 1.44Mb floppy. The PX1260 is based on a single-board computer and is completely enclosed in a metal chassis to keep EMI emissions in and RFI out. Two serial ports, one parallel port, a 3½" floppy, and the keyboard connector and reset button are located on the front of the module.

Applications for the unit include EISA workstations, industrial PCs, production test, modular rugged PCs, factory automation, and networks.

The PX1260 sells for \$5,995. For more information, contact Susan Conley, Marketing, Rapid Systems Inc., 433 N. 34th St., Seattle, WA 98103, (206) 547-8311, FAX (206) 548-0322.



## LENBROOK DISTRIBUTES NAD IN US

Lenbrook Industries, the Canadian distributor of NAD electronics, will also distribute the entire NAD line of audio and video products in the US. Robert Brown, president of LincolnWood, the former distributor, has been named Director of US Operations for Lenbrook Industries. He will handle the NAD line, as well as the company's PSB speaker line and other anticipated Lenbrook activities in the US.

NAD made this move to divest itself of the direct distribution activity, preferring to put its capital and other resources into research, product development, manufacturing, and international marketing.

## ELECTRONICS SCENE



## SYN-TECH XTR COMPACT DESKTOP BASE STATIONS

Midland LMR has introduced Syn-Tech XTR™ desktop FM two-way radio base stations, a new series of programmable dispatch units replacing earlier Syn-Tech models.

These compact stations feature programmable RF output power: 2-50W in low-band models (29.7-50MHz), 2-40W in VHF (136-174MHz), or 2-30W in UHF (406-470MHz). All are programmable for up to 22 channels (expandable to 99) and have built-in dual-priority, 40-channels-per-second scanning with operator add/delete capability. Tone and digitally coded squelch are randomly programmable by channel for all standard codes (optional in VHF). Units can be programmed by PC or by an EEPROM programmer. The radios are data-capable and have built-in data ports.

The XTRs include a built-in power supply operating on 110/220V AC, 60/50Hz. A 24-hour digital clock and day/date display are standard, as is a high-quality desktop microphone with PTT lock and monitor keys. Low-band units include a noise blanker. Options include a high-security scrambler, digital voice storage and replay, and tone and DC remotes.

For more information, contact Midland LMR, Marketing Department, 1690 N. Topping, Kansas City, MO 64120, (800) 643-5263, ext. 1690.

## ICOM FIRST IN SPACE

Packet radio, used in amateur radio space communications, is now part of the Soviet manned space station, Mir, callsign U2MIR. The packet equipment consists of Icom America's ICOM IC-228A 2-meter FM transceiver and PacComm Handi Packet unit, along with a laptop computer. The equipment was launched to Mir on a Progress M6 resupply "space truck" on January 14. To contact U2MIR, the downlink frequency is 145.55MHz.

## CATALOG SUPPLEMENT

For a copy of Antique Electronic Supply's 1991 Catalog Supplement, contact the company at PO Box 27468, Tempe, AZ 85285-7468, (602) 820-5411, FAX (602) 820-4643.

## TEN INSTRUMENTS IN ONE

Global Specialties has announced the PROTOMETER™ 4000, a portable instrument system. The hand-held package features ten test instruments capable of performing 35 measurement functions. The model 4000 packs the power of Global Specialties' complete line of instruments into a 3½ digit, 4,000-count multimeter case.

The PROTOMETER 4000 combines a digital multimeter capable of measuring DC and AC voltage, DC and AC amps, ohms, plus an autoranging frequency counter, transistor/capacitance tester, and logic probe into a durable drop-resistant case. Standard features include a large LCD display, 4,000-count accuracy, peak hold, and a high-voltage warning indicator.

The rugged construction makes the unit ideal for field service and industrial maintenance applications. Engineered with special heat-resistant components, its current-measuring range is extended up to 20A AC/DC. You can use this one meter to check all electronic components.

The PROTOMETER 4000 sells for \$139.95. For more information, contact Global Specialties, 70 Fulton Terrace, New Haven, CT 06512, (203) 624-3103, FAX (203) 468-0060.





### AMPLIFIER SPICE MODEL LIBRARY

A free disk containing 176 SPICE models of Analog Devices' IC amplifiers is available from the company. The advanced modeling techniques used allow as many poles and zeroes as are needed to shape a model's frequency response accurately to conform to the device. For 26 of the devices, models include voltage and current noise; this allows designers to predict system noise performance as part of the SPICE simulation. The library also includes models of two instrumentation amplifiers.

For more information, contact Analog Devices Literature Center, 70 Shawmut Rd., Canton, MA 02021.

### CATALOG OF TEST INSTRUMENTS AND ACCESSORIES

B&K PRECISION has available a 68-page catalog covering the company's line of electronic test instruments, including oscilloscopes, IC comparators, digital multimeters, signal and function generators, power supplies, component testers, video test instruments, probes, and accessories.

The *Test Instruments* catalog (BK-91) provides complete specifications in listings and comparison charts. Key product features are summarized, along with selected product applications. The catalog also describes product accessories to enhance the instruments. These instruments address applications such as engineering, maintenance and repair, field service, education, production-line testing, quality control programs, and research and development.

A glossary of terms for each major product category assists in specifying the correct instrument for a task, as well as provides an educational training aid.

Copies of the catalog are available from B&K PRECISION, Maxtec International Corp., 6470 W. Cortland St., Chicago, IL 60635, (312) 889-1448.

### 16-CHANNEL A/D DATA-ACQUISITION SYSTEM

BASICON has announced the DAS-1 Data Acquisition System. Suited for the industrial environment, the device provides convenience, saves time, insulates noisy analog signals from the PC, and simplifies gathering information from multiple sources, such as thermocouples, strain gauges, and load cells.

The DAS-1 reads 16 channels of analog signals. For convenience, wires are fastened to an industrial-grade screw terminal quick connect edge connector. This allows test wires to remain in place and enables you to move the DAS-1.

BASICON's software reads and displays information in real-time. All thermocouple probes are pre-calibrated, and a built-in automatic cold junction calibration is included. The software has up to eight alarm conditions for each channel, which can be activated on increment or decrement and which are displayed on the screen. Each alarm can send output addressed by an RS-232 code to any of 255 devices, such as lights, sirens, and valve controls. The DAS-1 is well-suited for use in laboratories and industrial settings.

For analysis of data, the DAS-1 can export information in Lotus 1-2-3 format. It communicates via a 9-pin RS-232 port. The unit has a small size (5½" by 5½" by 2½"), low power requirement (5V DC), a built-in microprocessor, and quick cable disconnect.

For more information, contact William V. Rochat, President, BASICON, Inc., 14273 NW Science Park Dr., Portland, OR 97229, (503) 626-1012, FAX (503) 643-4686.



### KITS FOR THE ELECTRONIC MUSICIAN

PAIA Electronics has available its 1991 catalog of kits for the electronic musician. Products include the MV-8 MIDI/Control Voltage processor, a PC-MIDI interface and software package, rack chassis enclosures, and an experimenter's kit. Other products range from a vocal zapper and guitar effects to kits for constructing studio sound processing equipment such as limiters, equalizers, mixers, a vocoder, and more.

The 1991 catalog is available free from PAIA Electronics, Inc., 3200 Teakwood Ln., Edmond, OK 73013, (405) 340-6300.

### MICROMATH BBS NOW ON-LINE

MicroMath Scientific Software has announced the installation of a computer bulletin board. The board's main emphasis is the Special Interest Forum, which facilitates communication between scientists and engineers. It allows professionals direct access to each other, giving them more resources in solving many complex challenges. The bulletin board acts as a clearinghouse for ideas and solutions for these and other needs.

Services provided are e-mail or two-station teleconferences, classified ads, customer product feedback on MicroMath products, and registration of MicroMath products. Future services will include spec sheets on products, an electronic newsletter, application specific examples and notes for evaluating products, product demonstration materials, and professional overnight slide preparation from MicroMath plot files.

The board has no user connect charges and runs on a 33MHz 80386 PC. Phone lines are "hunt grouped," making all lines accessible through a single phone number. These lines are connected to modems supporting 1200 and 2400bps. The bulletin board supports two simultaneous log-ons and will be expanded as needed. It can be accessed 24 hours a day at (801) 943-0397.

### MULTIPLIER ICs FOR VARIED APPLICATIONS

Analog Devices' monolithic AD734 analog multiplier/divider operates with a small signal and full-power bandwidth of 10MHz. It also offers a slew rate of 450V/μS, a signal-to-noise ratio of 94dB, and a conversion accuracy of 0.25% for high-grade devices.

As a four-quadrant multiplier, the AD734 can function as an oscillator, filter, or voltage-controlled amplifier. When connected as a two-quadrant divider, the device can function as an automatic gain control amplifier or an RMS/DC converter. Direct divide mode lets you optimize dynamic range for varying input signal spans. Applications include audio systems, sonar, analytical instrumentation, and RF and IF signal processing.


The AD633 is a four-quadrant multiplier. Intended for medium- and high-volume systems, its full-scale accuracy is 2% and requires no external components for operation. Applications include power measurement, watt-hour meters, motor control, and gamma-correction for projection TV.

The AD734AQ sells for \$10.55 (100s) and the AD633JN for \$3.38 (1,000s). For more information, contact Analog Devices, Inc., 181 Ballardvale St., Wilmington, MA 01887, (617) 937-1428.

# UNIVERSAL Ni-Cd BATTERY CHARGER

by A. Rigby

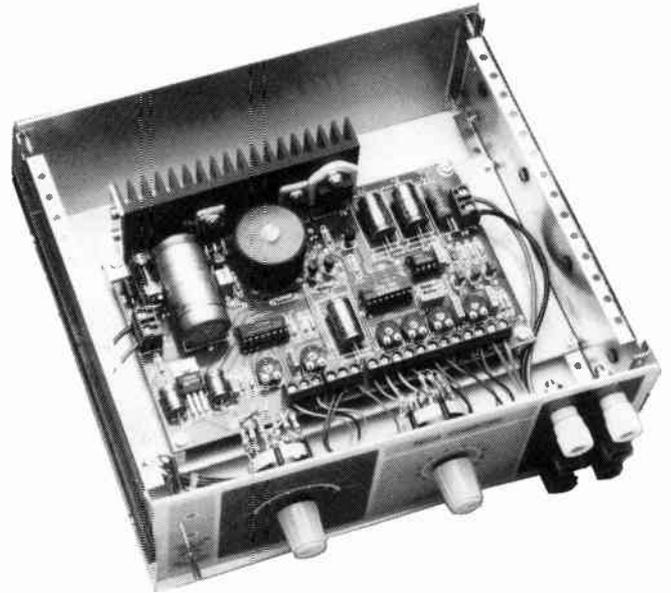**Ni-Cd batteries are now used in so much everyday equipment that most households need at least one suitable charger. The one presented here can be used to charge virtually all current Ni-Cd batteries.**



**T**HE charger is based on the Telefunken Type U2400B processor, which has been specially developed for this application. This device contains most of the logic circuits necessary for automatically controlling the charging of Ni-Cd batteries.

Initially, charging takes place during a predetermined period of time, after which trickle charging takes over. The trickle charging, which may continue for long periods of time, ensures that the battery capacity does not degrade during the life of the battery.

The charger has a number of safety features. For instance, if the temperature of the battery becomes too high or when the e.m.f. of the battery rises above a certain (predetermined) value, the charging cycle is discontinued immediately. The processor then assumes its stand-by mode and remains there until the temperature or the e.m.f. drops below its limiting value.

A flow diagram of the charging process is given in Fig. 2. After the battery has been connected and the start reset operated, the processor first arranges for the battery to be discharged. During the discharge cycle, the temperature of the battery ( $T < T_{max}$ ) and its e.m.f. ( $U < U_{min}$ ) are monitored continually. When the e.m.f. drops to the level of  $U_{min}$ , the processor assumes that the battery has been discharged completely, and sets its discharge register. The circuit then switches to the charging mode. During charging the lapsed charging time is compared with the preset charging time ( $t > t_{max}$ ) and the e.m.f. with the maximum (preset) voltage ( $U > U_{max}$ ). Furthermore, the content of the discharge register and the battery temperature are monitored constantly. At the end of the preset charging time ( $t > t_{max}$ ), the charging cycle is terminated and the processor actuates the trickle charging mode.

As already mentioned, if during charging one of the preset parameters is exceeded, charging is discontinued. At the same time, the status of the error register is increased by 1 and reread. If no error occurred previ-

ously, the status of the counter after the present error will be smaller than  $2(Z < 2)$ . If the counter status is smaller than 2, the e.m.f. and temperature of the battery are checked once again; if these are all right, the charging process is continued. If the content of the error register is greater than, or equal to, 2, charging is continued or stopped, depending on the position of a switch as explained later.

As is seen in Fig. 1, the processor needs only a few external components to perform the functions discussed so far. During the discharge cycle, the e.m.f. of the battery is monitored via  $U_{min}$  (pin 6). In this, use is made of a switchable voltage divider,  $R_{35}-R_{43}-R_3-P_2$ , which attenuates the battery voltage. During the discharge cycle, output DIS(charge) (pin 10) is active and high. The discharging is assumed complete when the voltage level at pin 6 drops below the level (0.53 V) of the internal reference voltage.

During charging, output LOAD (pin 12) becomes active and high; the battery voltage is then applied to pin 4 ( $U_{max}$ ) via potential divider  $R_{35}-R_{43}-R_2-P_1$ . If the voltage at pin 4 is higher than the internal reference potential, the processor switches to the stand-by mode.

Since it is important for the user to know in which state the processor is, two LEDs are driven via STATUS output pin 9. Table 1 shows the operation of these diodes in the various modes.

A reference voltage of 3 V (nominal) is applied to pin 7, the PWM input, switch  $S_1$ , network  $R_4-C_2$ , voltage divider  $R_5-R_6$  and the two series-connected LEDs.

Series combination  $R_4-C_2$  at the input of the internal oscillator, pin 3, is a fre-

quency-determining network.

Monitoring of the battery temperature is accomplished by  $R_6$ , which has a negative temperature coefficient. The potential at junction  $R_5-R_6$  is monitored via input  $U_{temp}$  (pin 5). The charging process is stopped when the battery temperature reaches  $40^\circ\text{C}$ ; the resistance of  $R_6$  is then about  $440\Omega$ .

The position of switch  $S_1$  determines the selection made by the processor when two or more errors in the charging process have been signalled. If the switch is connected to the reference voltage, charging is continued even when two (but no more) errors have occurred; if it is connected to earth, however, full charging is discontinued and trickle charging commenced.

The charging time is preset via the TIME input, pin 13. When the internal 200 Hz oscillator is used, a high level at pin 13 sets the charging time to 1 hour. When the pin is connected to earth (low level), the charging time is 30 minutes.

The timer may also be driven by an ex-

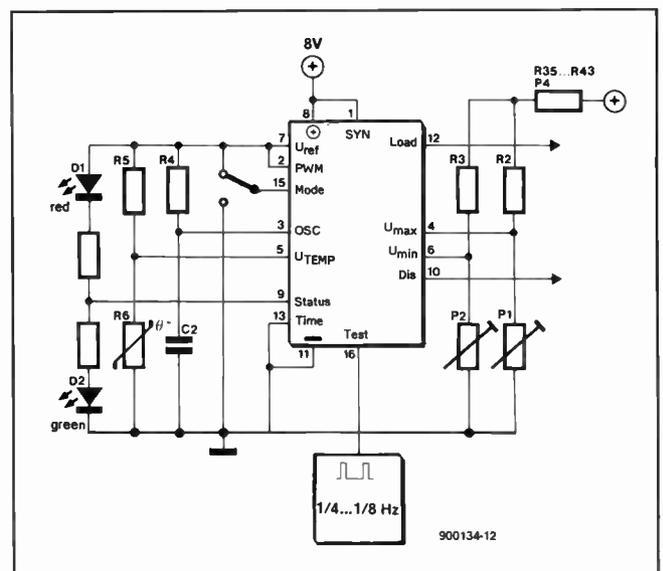


Fig. 1. Basic circuit for the U2400B processor.

Table 1

D <sub>1</sub>	D <sub>2</sub>	S <sub>1</sub>	Function
(red) on	(green) off	x	no battery connected; battery faulty or battery flat
flashes	off	x	discharge cycle
off	flashes	x	charging cycle
off	on	x	trickle charge mode
flashes	flashes	E	charging continues after two errors
on	off	D	trickle charging after two errors

x = irrelevant  
 E = connected to U<sub>ref</sub>  
 D = connected to earth

ternal clock, connected to pin 16; pin 13 must then be earthed. The internal 200 Hz oscillator then provides the clock signals for the remaining functions of the processor. A frequency of 0.5 Hz at pin 16 sets the charging time to 1 hour; halving that frequency doubles the time. An external clock based on a 4060 IC as shown in Fig. 8 can provide frequencies down to 0.125 Hz, which would give a charging time of 4 hours.

### Charging

In a practical charger, the processor does not drive a simple transistor, but a fairly complex current source, controlled as shown in Fig. 3. The charging current flows through R<sub>22</sub>, resulting in a potential drop across this resistor that is directly proportional to the charging current:

$$U_{R22} = I_{load}R_{22}.$$

This voltage is used for controlling the charging current. Note that the negative battery voltage, U<sub>bat</sub>, is in reality more positive than the supply voltage, U<sub>V</sub>, because the positive terminal of the battery is connected to a second, higher supply voltage.

Since transistor T<sub>5</sub> is connected as a diode, the emitter of T<sub>6</sub> is connected to U<sub>V</sub> at all times. Therefore, the potential drop across the emitter resistor, R<sub>e</sub>, which is the equivalent of R<sub>29</sub>-R<sub>34</sub>-P<sub>6</sub> in Fig. 8, is exactly the same as that across R<sub>22</sub>:

$$U_{Rc} = U_{R22} = I_{Rc}R_{c}.$$

As an example, assume that R<sub>22</sub> = 0.1 Ω, I<sub>load</sub> = 1 A, and that a current of 1 mA is required through the transistor. The drop across R<sub>22</sub> is 100 mV, so that

$$R_c = 100 \times 10^{-3} / 10^{-3} = 100 \Omega.$$

Since the emitter current is now known, the voltage drop across the collector resistor is:

$$U_{Rc} = 1.2 \times 10^3 \times 10^{-3} = 1.2 V.$$

This makes it clear that a change in the charging current results in a change in the voltage at F<sub>B</sub>. That voltage may, therefore, be used for the control of a regulatory circuit in a switch-mode power supply.

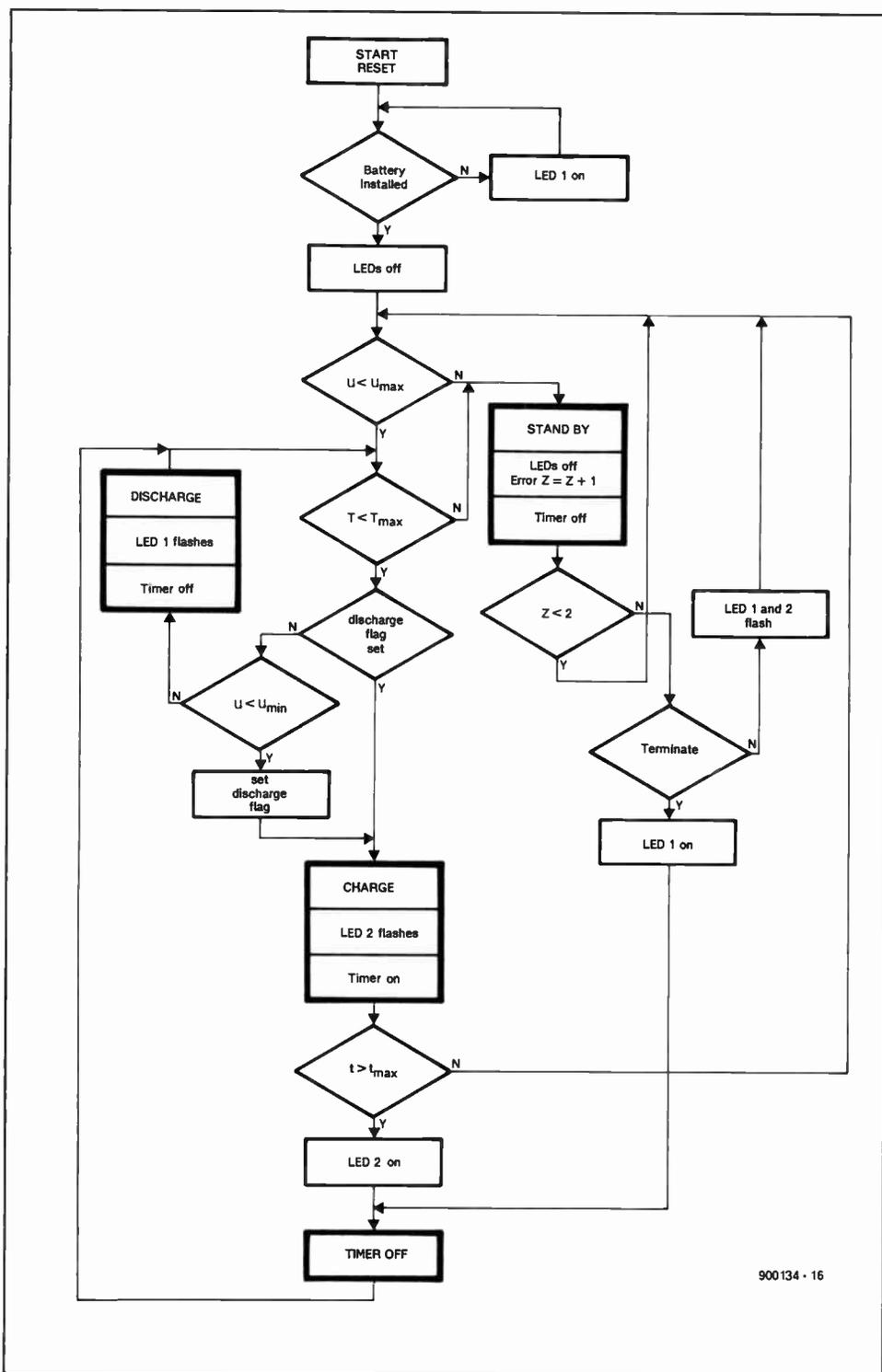


Fig. 2. Flow diagram of the battery charger.

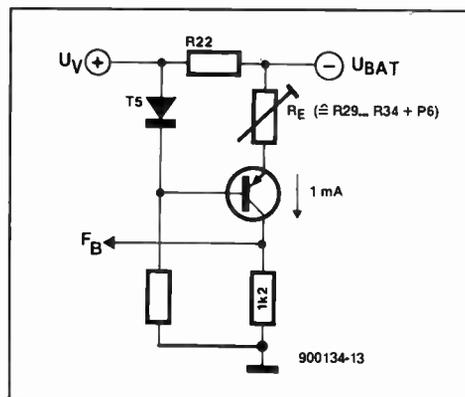


Fig. 3. Part of the circuit controlling the charging current.

### Switch-mode power supply

A switch-mode power supply is used to enable the charger to cater for the simultaneous charging of, say, up to ten batteries; a conventional mains supply could be used, but the dissipation in this will be quite large when only a few batteries are being charged.

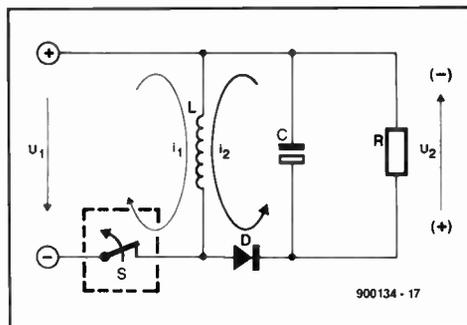


Fig. 4. Concept of a switch-mode power supply.

The basic operation of such a supply is shown in Fig. 4. Electronic switch S is switched on and off by electrical circuits. When it is closed, a current  $i_1$  flows from the  $\oplus$  supply terminal to earth via inductor L, resulting in a magnetic field around the inductor. Diode D is switched off and capacitor C, therefore, has no influence on the circuit, although it can discharge via load resistance R (representing the batteries to be charged).

When S is opened, the self-inductance of L causes a current  $i_2$  in the opposite direction from  $i_1$  and this charges C via the diode.

The level of output voltage  $U_2$  depends on the properties of the inductor, the switching logics and the on-off ratio of the switch. In the present charger, a commercial inductor is used: it is not advisable to wind this yourself.

The circuit of the supply used is shown in Fig. 5. It is based on Linear Technology's Type LT 1070. A 40 kHz oscillator provides a train of rectangular pulses that are used to switch a transistor via a driver stage. The duty factor is determined primarily by the output voltage of the (differential) error amplifier.

The collector voltage of  $T_6$  is 1.2 V when the regulator is in a stable condition. Because of its internal reference voltage of 1.24 V, the error amplifier then has no effect on the switching behaviour of the output transistor. When the charging current increases to too high a level,  $U_c$  rises, and the output of the error amplifier goes low. This results in an alteration of the on-off ratio of the transistor, which lowers the charging current.

Zener diode  $D_6$  limits the voltage to 18 V.

### Discharging

The discharge circuit shown in Fig. 6 has some points in common with the circuit in Fig. 3. Again, use is made of the voltage drop across emitter resistor  $R_{22}$ . The supply voltage and the battery voltage have, of course, changed places, since the discharge current flows into a different direction from the charging current.

The non-inverting input of the comparator in the collector circuit of  $T_3$  is held at 2.7 V by zener diode  $D_3$ .

The value of  $R_{14}$  is determined by the collector current (1 mA) and the reference voltage:

$$R_{14} = 2.7 / 10^{-3} = 2.7 \text{ k}\Omega.$$

The connected batteries are discharged via  $R_{22}$  and  $T_8$ , which, with  $T_7$ , forms a darlington at the output of the comparator.

### Voltage monitoring

The processor continually monitors the battery voltage via its pins 4 and 6. Since these inputs measure the voltage with respect to earth and the negative terminal of the battery is connected to the  $\oplus$  supply rail, a simple circuit like that in Fig. 1 can not be used. This means that the battery voltage must be converted so that it can be measured with respect to earth.

To this end, a network as shown in Fig. 7 is used. The entire battery voltage is dropped across the emitter resistance,  $R_e$ , consisting

of resistors  $R_{35}$ – $R_{43}$ —see Fig. 8. Since  $R_e$  has a value of 1 k $\Omega$  per connected battery, the collector current,  $I_c$ , through  $T_1$  is

$$I_c = n \times U_z / n \times R_e = U_z / R_e,$$

where  $U_z$  is the zener voltage.

When the batteries are charged, the collector current is  $1.45 / 10^3 = 1.45$  mA, and the voltage drop across  $R_1$  and potential dividers  $R_2$ – $P_1$  and  $R_3$ – $P_2$  is 1.74 V. This voltage has the correct polarity with respect to earth. The correct operating point is set with the two potentiometers: how many batteries are connected to the charger is then no longer of importance.

### The complete circuit

Large parts of the diagram in Fig. 8 have already been discussed. Note that the switch-mode power supply operates only if pin 1 of the LT 1070 is connected to earth via the LOAD output of the processor and  $T_4$ .

Since the resistors at like positions of  $S_{4a}$  and  $S_{4b}$  have the same value, the discharge and charging currents of batteries are iden-

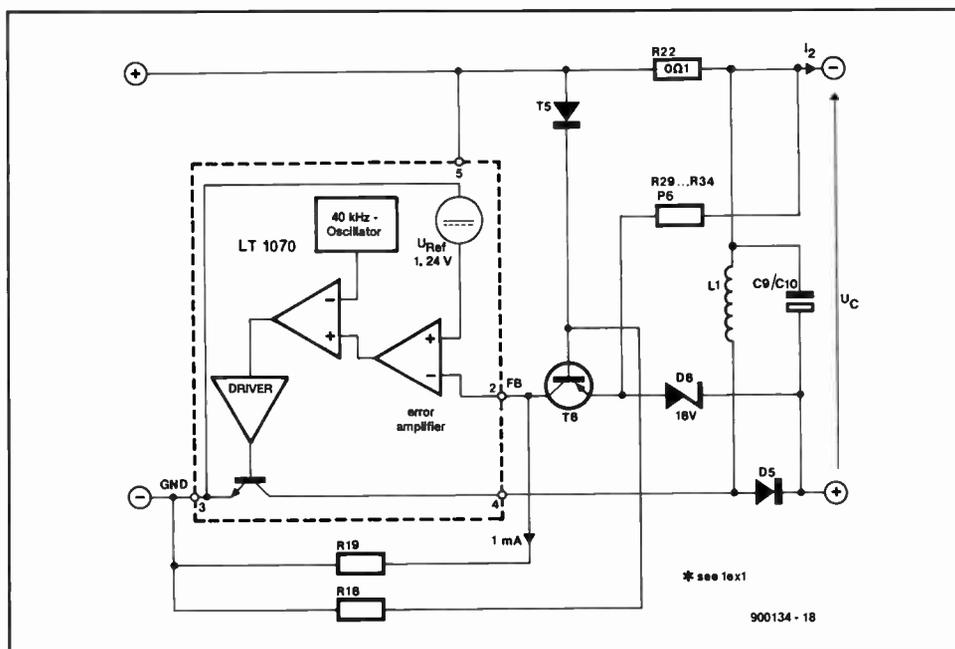


Fig. 5. The switch-mode power supply – see also Fig. 8.

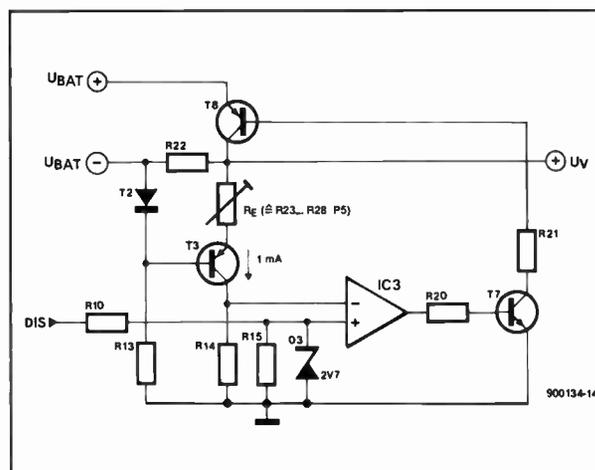


Fig. 6. Circuit for controlling the discharge current. The Dis output of the U2400B provides the reference voltage for IC3.

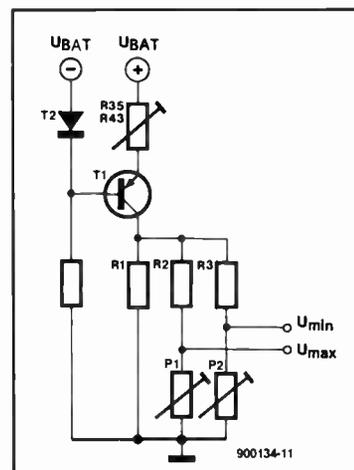


Fig. 7. Circuit for measuring the battery voltage with respect to earth.

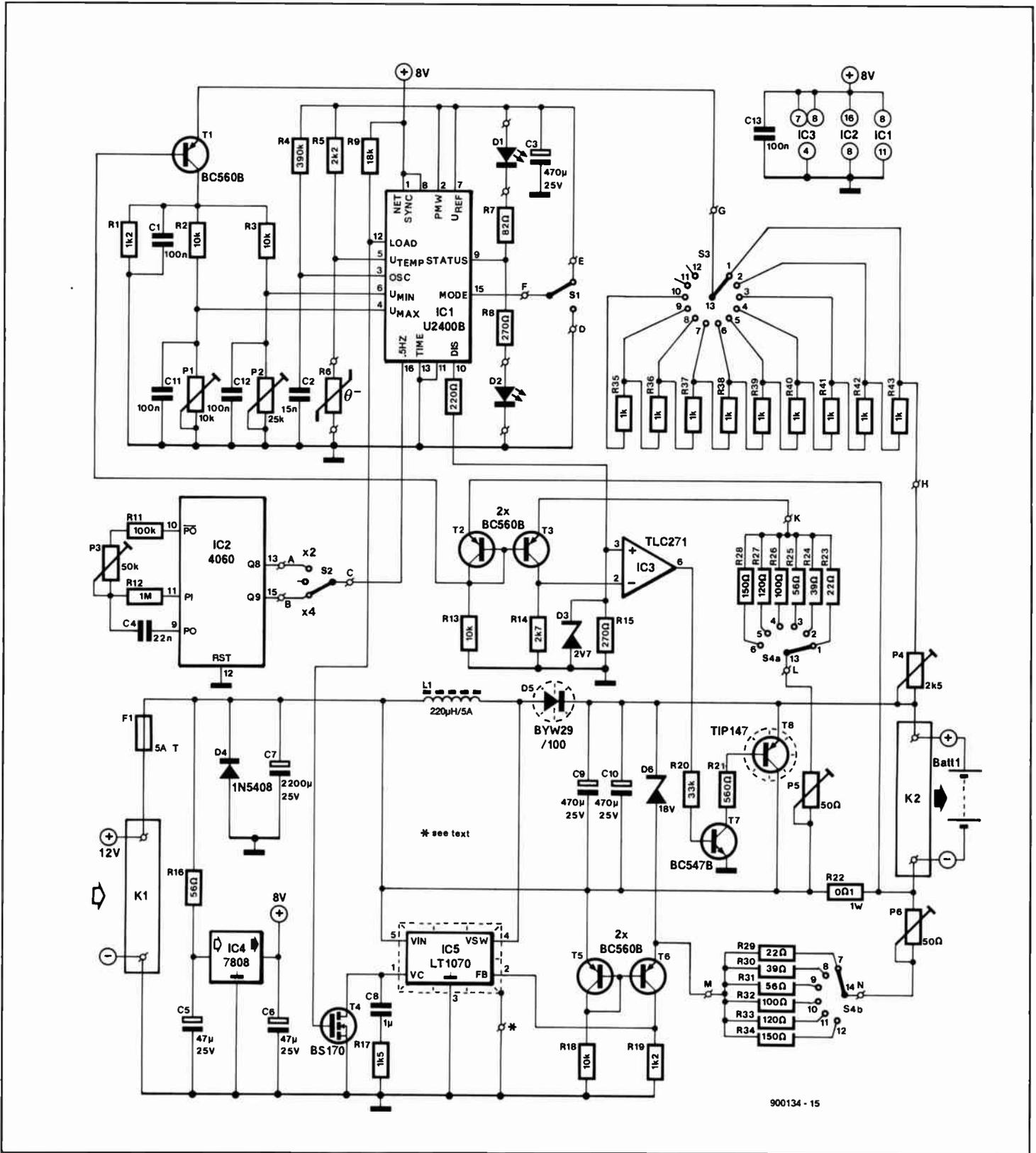


Fig. 8. Complete circuit diagram of the Ni-Cd battery charger.

tical. It is, of course, essential that switch S<sub>3</sub> is set to the correct number of connected batteries (maximum 10).

Switch S<sub>1</sub> selects the mode to be used when one or two errors are detected during the charging process—see Table 1.

When S<sub>2</sub> is in its centre position, the processor uses the standard time setting (of charging) of 1 hour. Its pin 13 is then connected to earth. If this meets all your requirements, the external clock generator consisting of the 4060 (IC<sub>2</sub>), R<sub>11</sub>, R<sub>12</sub>, C<sub>4</sub>,

P<sub>3</sub>, and S<sub>2</sub>, may be omitted.

Otherwise, R<sub>11</sub>, R<sub>12</sub>, P<sub>3</sub>, and C<sub>4</sub>, set the frequency of the oscillator in the 4060 at 100–150 Hz. The divider on board the 4060 provides the required signal frequencies at outputs Q<sub>8</sub> and Q<sub>9</sub>. The charging times of 2 and 4 hours respectively associated with these frequencies enable U7 and U11 size batteries to be charged in accordance with manufacturers' specifications.

Preset P<sub>3</sub> enables the correct setting of 2-hour (position A) and 4-hour (position B)

charging periods. Should that not be possible, the value of C<sub>4</sub> may be increased (longer periods) or reduced (shorter periods). If a standard time of 30 minutes is wanted instead of 1 hour (S<sub>2</sub> in centre position), disconnect pin 13 of the U2400B from earth.

If C<sub>4</sub> is replaced by a 10 nF type, periods of 30 minutes (S<sub>2</sub> in centre position), 1 hour (S<sub>2</sub> in position A), and 2 hours (S<sub>2</sub> in position B), may be selected

For trickle charging the normal charging circuit is used, but the on-off ratio is ar-

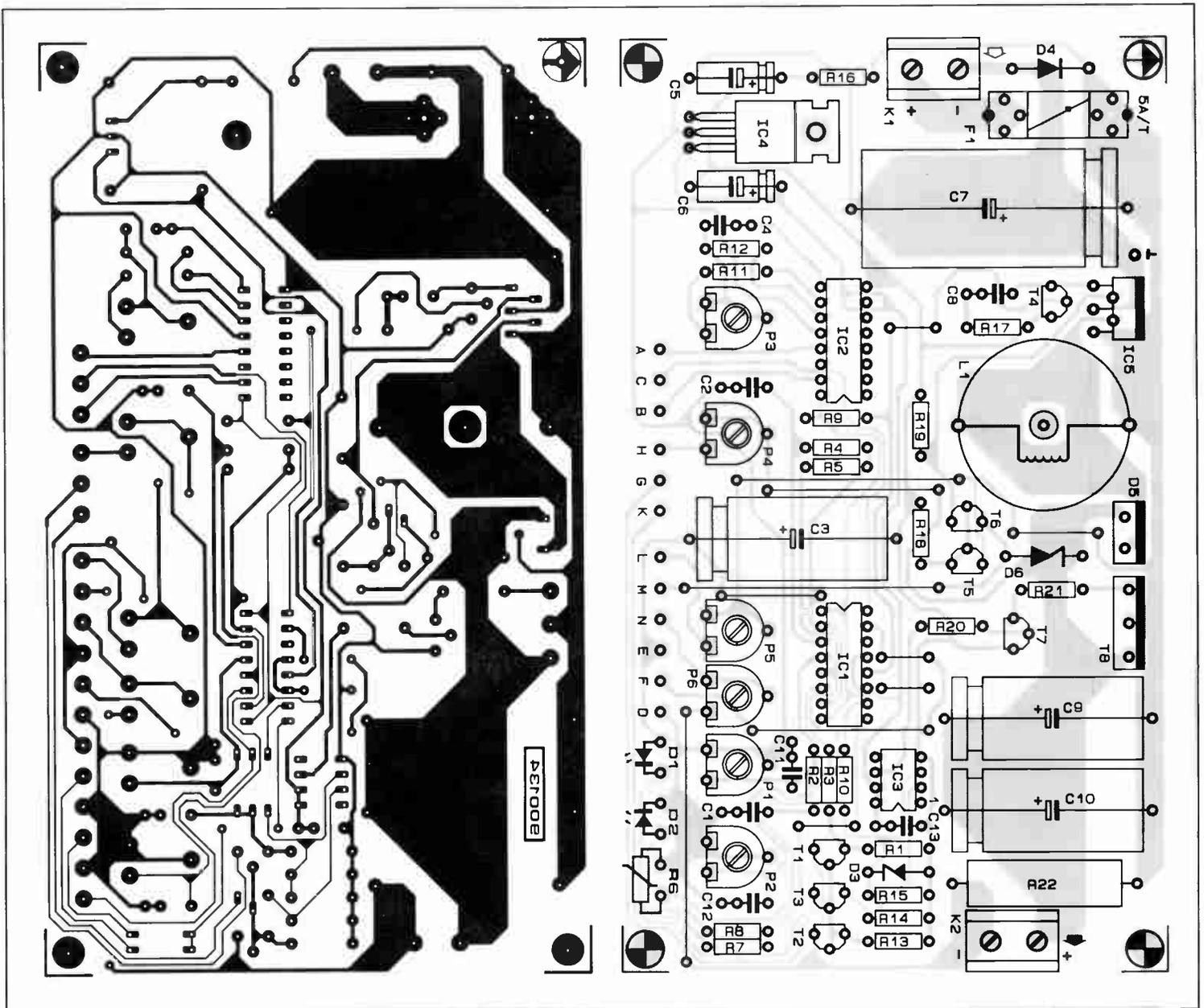


Fig. 9. Component layout and mirror image of track layout of the printed-circuit board for the Ni-Cd battery charger.

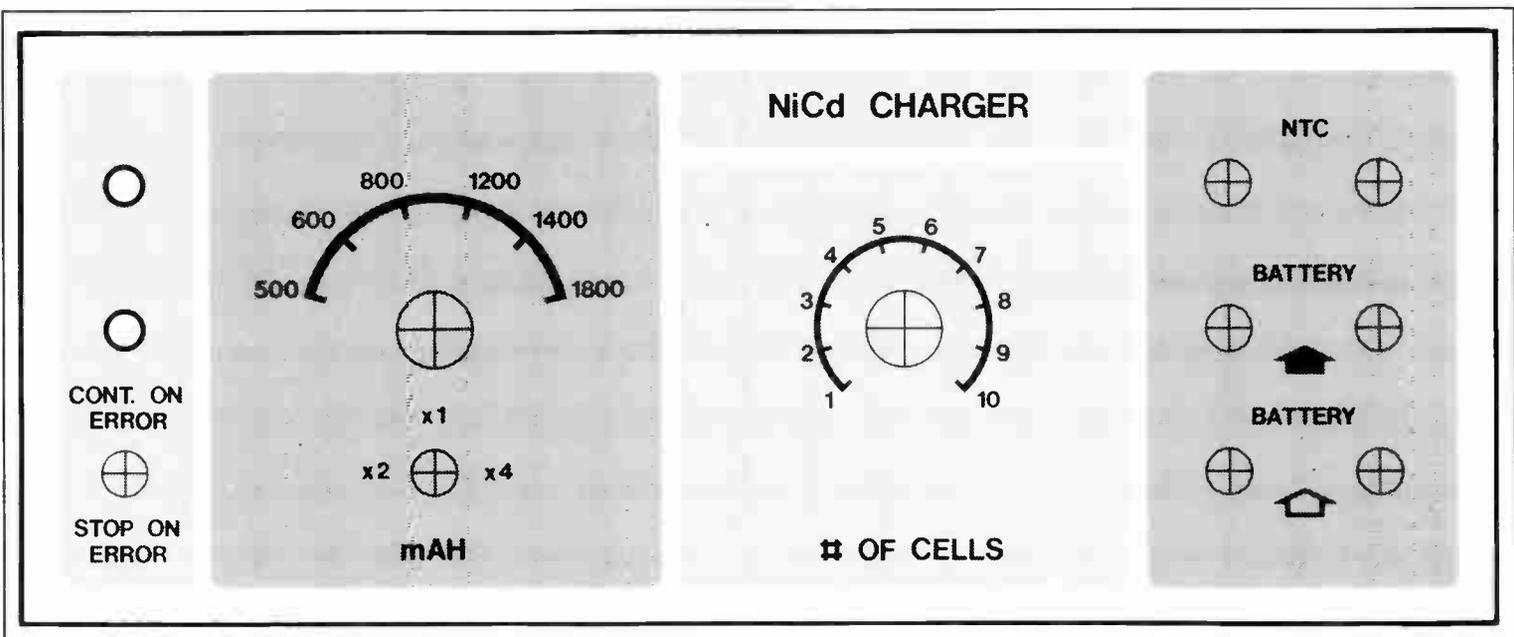


Fig. 10. A front panel foil for the battery charger (196x77 mm) is available through our Readers' Services.

ranged at 1:179, which reduces the average charging current of 1800 mA to 10 mA.

The level of the discharge and charging currents is independent of the selected charging period and may be set to six fixed values with  $S_4$ . If it is required for a battery to be charged completely in 30 minutes, the charging current selected must have twice the value of the battery capacity. The charging current in mA corresponds to the capacities shown on the front panel—see Fig. 10. That is, in position 500 mAh, the charging current is 500 mA. Independent of this, the charging current may be doubled by shunting  $R_{22}$  with a second 0.1  $\Omega$ , 1 W, resistor. This may, however, be done only if the total consumption,  $I_{load} \times U_{load}$  does not exceed 25 W, otherwise the switched-mode power supply may become overloaded. Furthermore, the maximum current through the inductor, the fuse rating (max. 8 A), and the maximum discharge current (max. 10 A) must be observed.

## Construction

The battery charger is best constructed on the printed-circuit board shown in Fig. 9.

Pay good attention to the polarity of a number of components and make sure that firm solder connections are made where large currents are likely to flow.

The components that need cooling, i.e.,  $IC_5$ ,  $D_5$ , and  $T_8$ , are located at the edge of the board to enable them to be fitted direct to a suitable heat sink ( $\geq 3.2 \text{ K W}^{-1}$  at a consumption of  $\leq 25 \text{ W}$ ).

Make sure that the rear of the LT1070 is electrically bonded to the earth connection specially provided between the supply connections for  $C_7$  and  $IC_5$ .

All presets are conveniently grouped at one side of the board.

Resistors  $R_{23}$ – $R_{43}$  are not located on the board, but are soldered direct to the rotary switches. These switches are intended to be fitted to the front panel. Their sections that must be connected to the board are marked

G/H, K/L, and M/N.

The sockets for connecting the NTC resistor,  $R_6$ , the supply ( $K_1$ ) and the batteries ( $K_2$ ) are located at the right-hand side of the front panel.

## Calibration

There are quite a few calibrations to be carried out, but fortunately they are not very critical. In the first place, do not yet fit  $IC_1$ .

1. Set  $S_4$  to 500 (mA),  $S_3$  to 8 (batteries),  $S_2$  to its centre position, and all presets to the centre of their travel.
2. Connect a 12 V, 2 A supply to  $K_1$  (observe polarity!).
3. Connect an auxiliary supply of 8 V to  $K_2$  (observe polarity!).
4. Connect a multimeter between the  $\oplus$  pin of  $K_2$  and point G on the board, and adjust  $P_4$  until the measured voltage is exactly the same as that between the pins of  $K_2$ .
5. Set  $S_3$  to position 10 and adjust  $P_2$  until with an auxiliary voltage of 8–8.5 V on  $K_2$ , a voltage of 0.53 V is measured between junction  $P_2$ – $R_3$ – $C_{12}$  and earth. This ensures that all batteries are first discharged to an e.m.f. of 0.8–0.85 V.
6. Set  $S_3$  to position 10 and adjust  $P_1$  until with an auxiliary voltage of  $10 \times$  the maximum specified (by manufacturer) cell voltage on  $K_2$ , a potential of 0.53 V is measured between junction  $P_1$ – $R_2$ – $C_{11}$  and earth. The maximum cell voltage is normally about 1.65 V, but may vary from 1.55 V to 1.7 V.
7. The external clock is adjusted with the aid of  $P_3$  and this is best done on an oscilloscope. The frequency of the signal at pin 6 of  $IC_2$  must be 1 Hz. If you have no oscilloscope, use a logic tester with LED indication: the flashing of the LED may be compared with the second hand of a watch.
8. Remove the auxiliary voltage from  $K_2$ , switch off the supply voltage, and fit  $IC_1$  and  $R_6$ . In an emergency, a normal 1 k $\Omega$

resistor may be used for  $R_6$ .

9. Connect a partially discharged 500 mAh battery to  $K_2$ , set  $S_4$  to 500 and  $S_3$  to 1.
10. Reconnect the 12 V supply to  $K_1$ , whereupon the red LED will come on.
11. Connect a digital multimeter (set to 1–2 A d.c.) in series with the battery. About 2 seconds after the connection with the battery is made, the red LED goes out and discharging of the battery begins. Adjust  $P_5$  till the multimeter reads 500 mA.
12. After a little while, the battery will be discharged and charging will commence, indicated by the coming on of the green LED. The current through the multimeter will then change direction: adjust  $P_6$  until it has a value of 500 mA.
13. The battery charger is now ready for use.

## Finally

Before charging is begun, always set the various switches to the correct position. The charger can then be switched on and the batteries connected to it. When a different set of batteries or battery is connected to the charger, reset the processor by briefly switching off the supply. ■

### PREVIEW

## SPEAKER BUILDER

Issue 3, 1991

- Measuring drivers with radar
- A deep bass subwoofer
- Calculating low-frequency response with PSpice
- A speaker made of pipes and ribbons
- The DELAC S10
- An infrared remote volume control

## PARTS LIST

### Resistors:

R1, R19 = 1.2 k $\Omega$   
 R2, R3, R13, R18 = 10 k $\Omega$   
 R4 = 390 k $\Omega$   
 R5 = 2.2 k $\Omega$   
 R6 = 1 k $\Omega$  NTC  
 R7 = 82  $\Omega$   
 R8, R15 = 270  $\Omega$   
 R9 = 18 k $\Omega$   
 R10 = 200  $\Omega$   
 R11 = 100 k $\Omega$   
 R12 = 1 M $\Omega$   
 R14 = 2.7 k $\Omega$   
 R16, R25, R31 = 56  $\Omega$   
 R17 = 1.5 k $\Omega$   
 R20 = 33 k $\Omega$   
 R21 = 560  $\Omega$   
 R22 = 0.1  $\Omega$ , 1 W  
 R23, R29 = 22  $\Omega$   
 R24, R30 = 39  $\Omega$

R26, R32 = 100  $\Omega$   
 R27, R33 = 120  $\Omega$   
 R28, R34 = 150  $\Omega$   
 R35–R43 = 1 k $\Omega$   
 P1 = 10 k $\Omega$  preset  
 P2 = 25 k $\Omega$  preset  
 P3 = 50 k $\Omega$  preset  
 P4 = 2.5 k $\Omega$  preset  
 P5, P6 = 50  $\Omega$  preset.

### Capacitors:

C1, C11, C12, C13 = 100 nF  
 C2 = 15 nF  
 C3, C9, C10 = 470  $\mu$ F, 25 V  
 C4 = 22 nF  
 C5, C6 = 47  $\mu$ F, 25 V  
 C7 = 200  $\mu$ F, 25 V  
 C8 = 1  $\mu$ F

### Inductors:

L1 = choke 200  $\mu$ H, 5 A

### Semiconductors:

D1 = LED, red  
 D2 = LED, green  
 D3 = zener, 2.7 V, 400 mW  
 D4 = 1N5408  
 D5 = BYW 29/100  
 D6 = zener, 18 V, 400 mW  
 T1, T2, T3, T5, T6 = BC560B  
 T4 = BS170  
 T7 = BC547B  
 T8 = TIP147  
 IC1 = U2400B  
 IC2 = 4060  
 IC3 = TLC271  
 IC4 = 7808

IC5 = LT1070

### Miscellaneous:

S1 = miniature C/O switch  
 S2 = miniature C/O switch with centre position  
 S3 = rotary switch, 1 pole, 12 positions  
 S4 = rotary switch, 2 poles, 6 positions  
 F1 = fuse, 5 A, complete with holder  
 K1, K2 = 2-way terminal block  
 Heat sink, 100x38x15 mm  
 PCB 900134  
 Front panel foil 900134-F

Estimated cost: £45–£55

# LOGIC ANALYSER - PART 4

by K. Nischalke and H.J. Schulz

In this penultimate instalment of the article (which was delayed by circumstances beyond our control), the power supply and the interfaces for the IBM and Atari are discussed, and that completes the hardware for the logic analyser. In the final instalment, the necessary software will be introduced.

THE DESIGN of the power supply is not revolutionary and yet it is unconventional, because the analyser, owing to the number of fast logic circuits, consumes quite a lot of power. The circuit diagram of the power supply is given in Fig. 16.

So as to keep the supply relatively simple and compact, five low-power voltage regulators, instead of one heavy-duty type, are used: one for each board contained in the analyser. This design has the advantage that when a certain board is not used, its supply can also be omitted. Furthermore, the cooling becomes a lot easier.

The supply consists of two independent sections, of which the main one is based on transformer  $Tr_2$ , bridge rectifier  $D_2$ - $D_5$ , and voltage regulators  $IC_{65}$ - $IC_{69}$ . The section based on  $Tr_1$ , bridge rectifier  $D_6$ - $D_9$ , and regulators  $IC_{70}$  and  $IC_{71}$  is intended for probes that can cope with input voltages up to  $\pm 12$  V. If such a probe is not envisaged, this section may simply be omitted.

Mains transformer  $Tr_2$  is rated at 5 A to handle the whole analyser. The rating can be reduced by 1 A for each RAM card that is omitted.

The five regulators are of the well-known 78xx type, but here rated at 2 A (S-type). This is because the current drain of the RAM cards is just about 1 A and it would be disturbing if the current limiting of the regulator would come into action regularly (low voltage).

The PCB for the supply is shown in Fig. 17. It has the same format as the bus board and the two may, therefore, if the enclosure allows, be fastened together with the aid of suitable spacers (track sides facing, of course). Such an arrangement would place the 5 V and 12 V connections of the boards close together.

## Atari interface

Communication between an Atari and the logic analyser is via the hard-disk slot emerging at the rear of the computer via a D-type connector.

The present interface is not strictly a special hard-disk interface, but a DMA interface to which a maximum of eight external apparatuses may be connected in parallel. Addressing the apparatuses separately prevents any conflict between them. This means also that the hard disk may remain connected.

The circuit diagram of the interface is


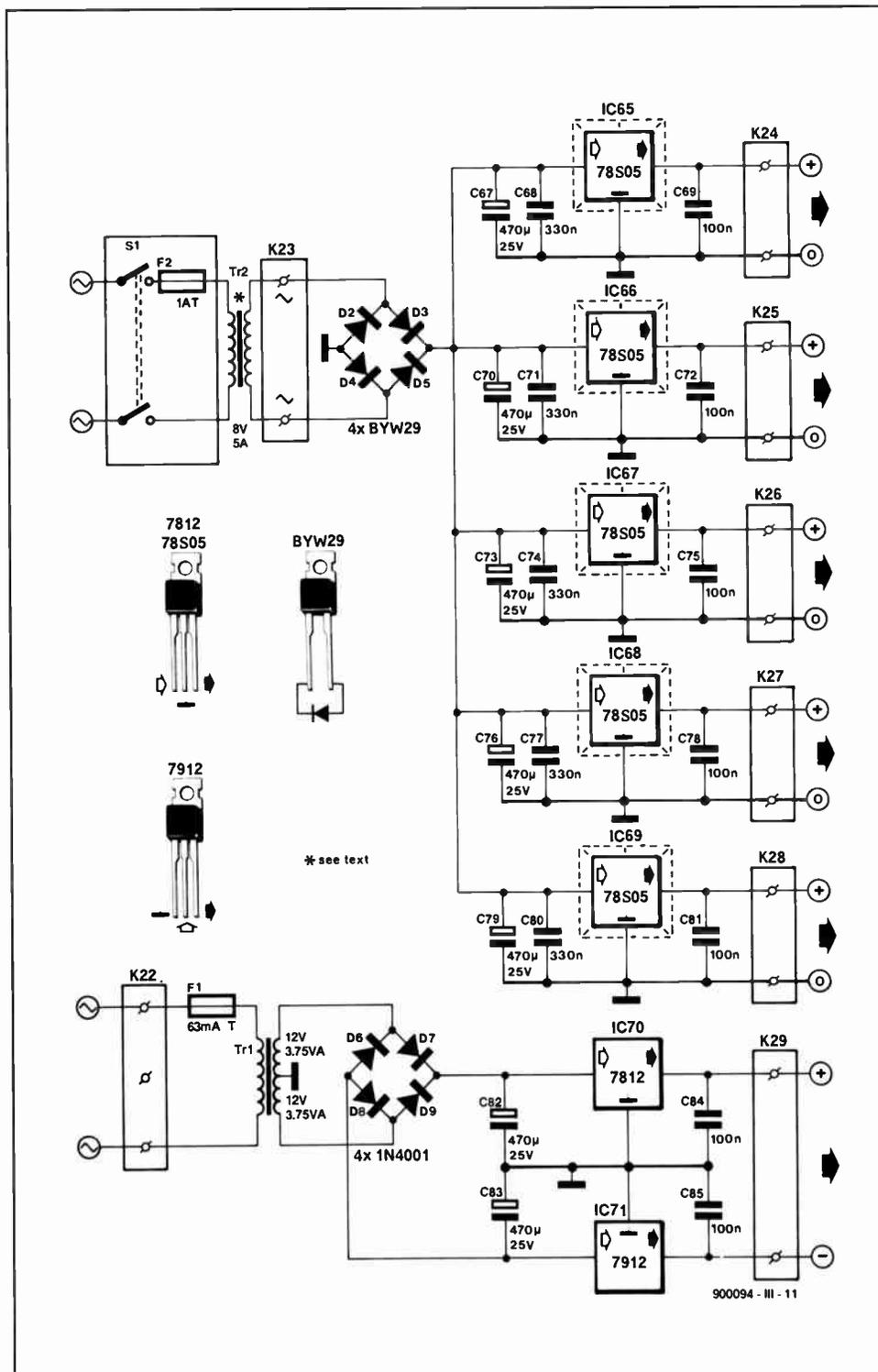


Fig. 16. Circuit diagram of the power supply; the section based on  $Tr_1$  is for use only if probes that accommodate input voltages up to  $\pm 12$  V are to be used.

Fig. 17. Photograph of the completed power supply board.

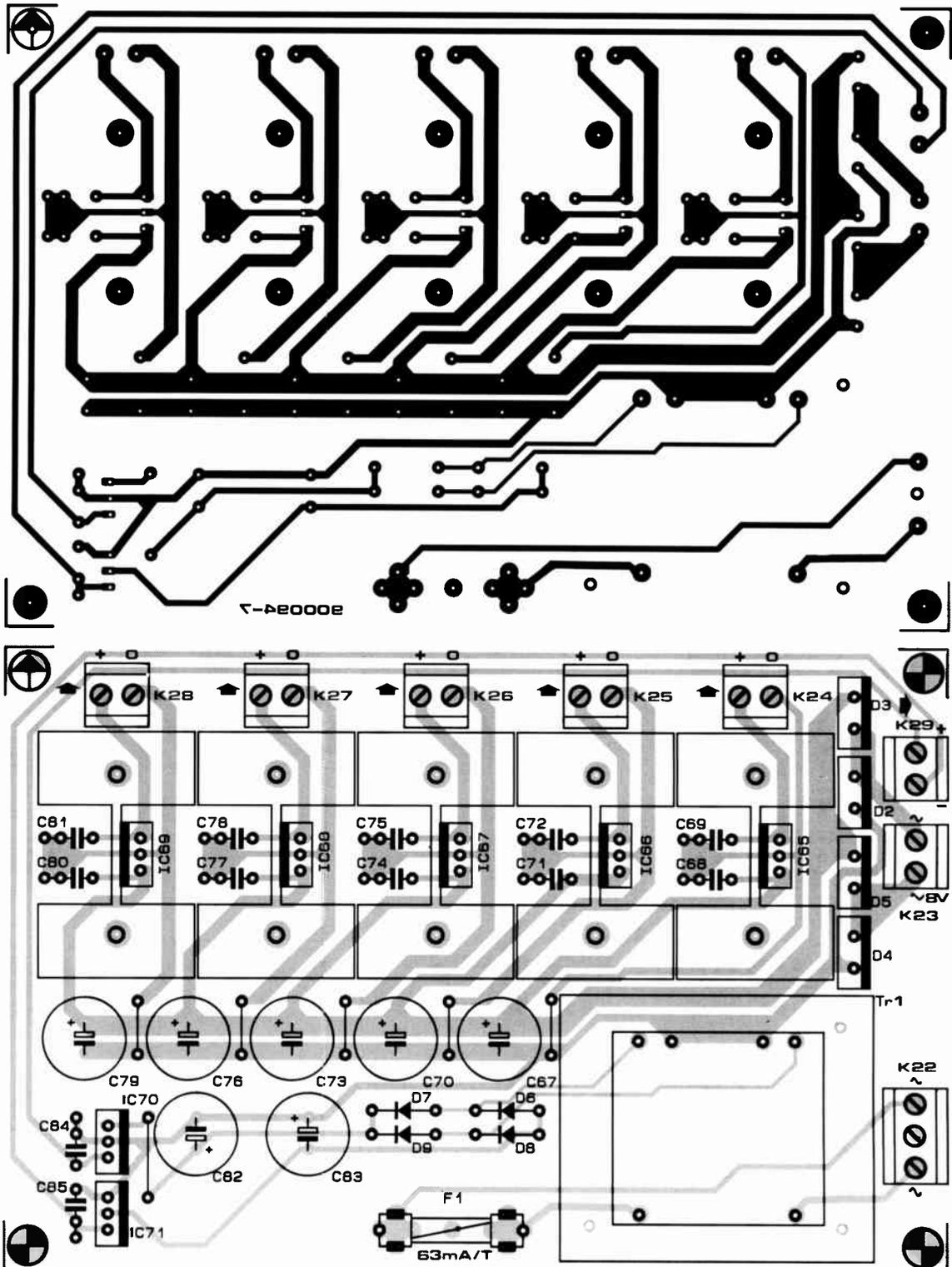

Fig. 18. The printed-circuit board for the power supply has the same dimensions as the busboard. It has no provision for Tr2.



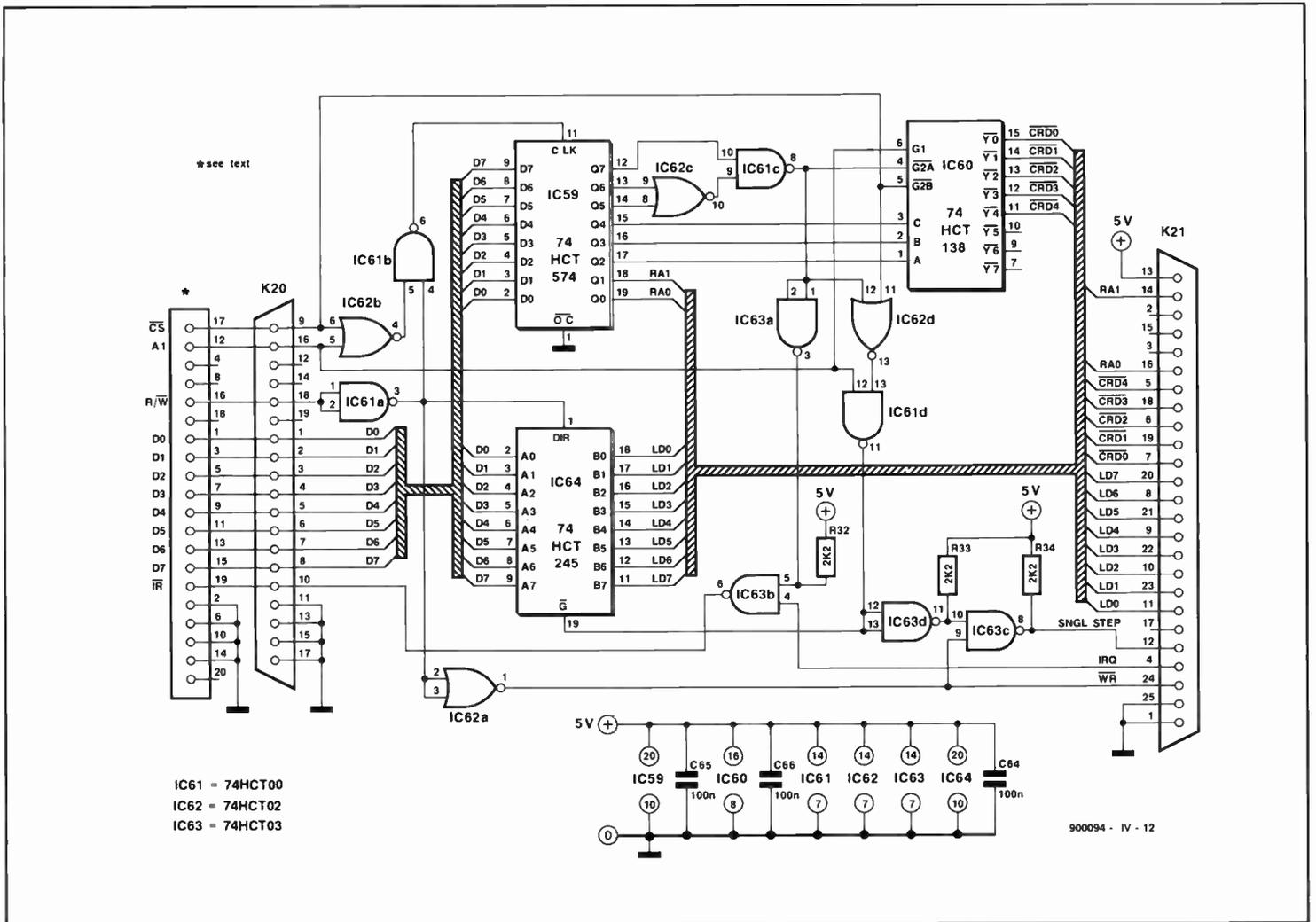


Fig. 19. Circuit diagram of the interface for Atari computers.

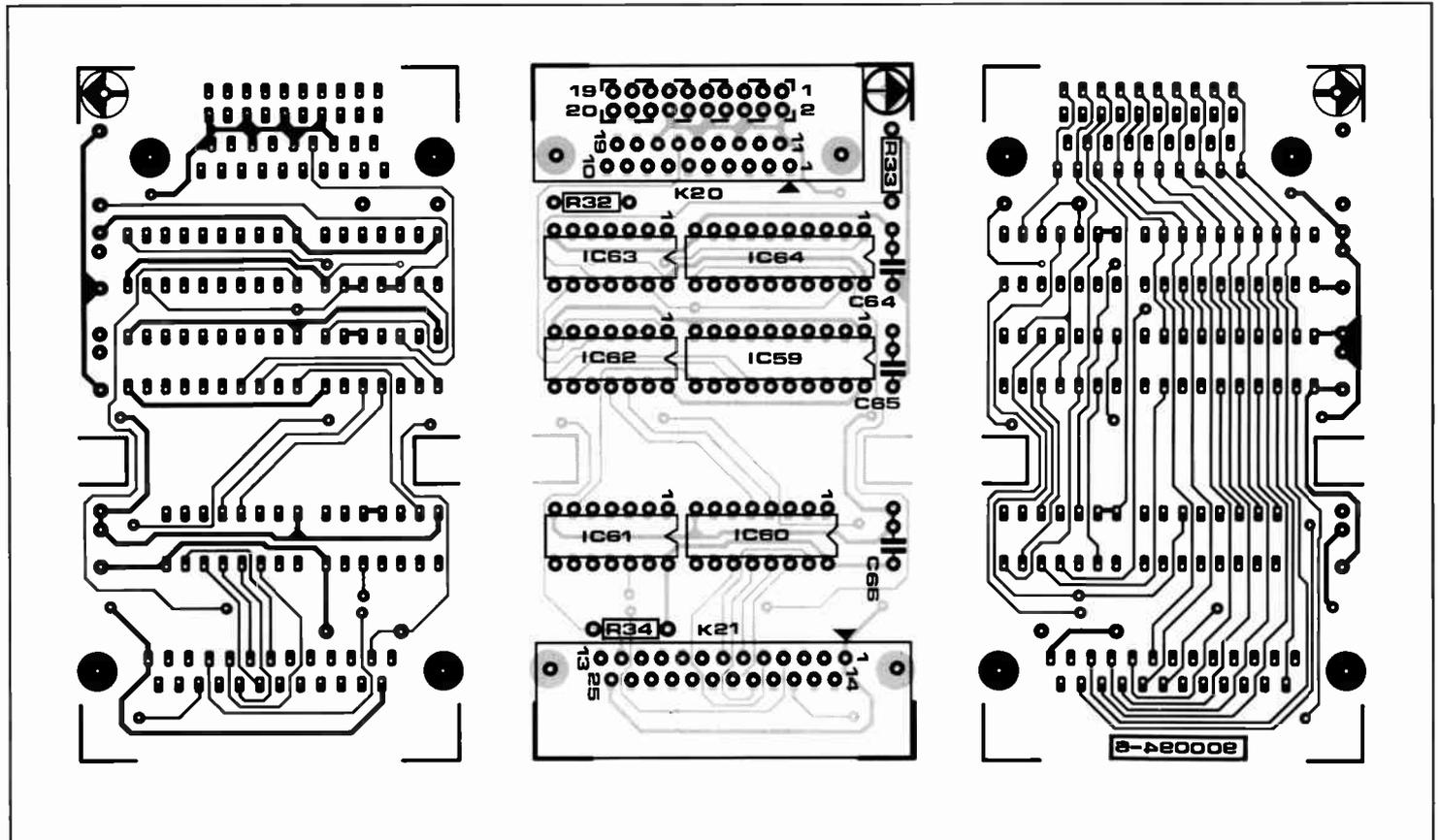


Fig. 20. The printed-circuit board for the Atari interface.

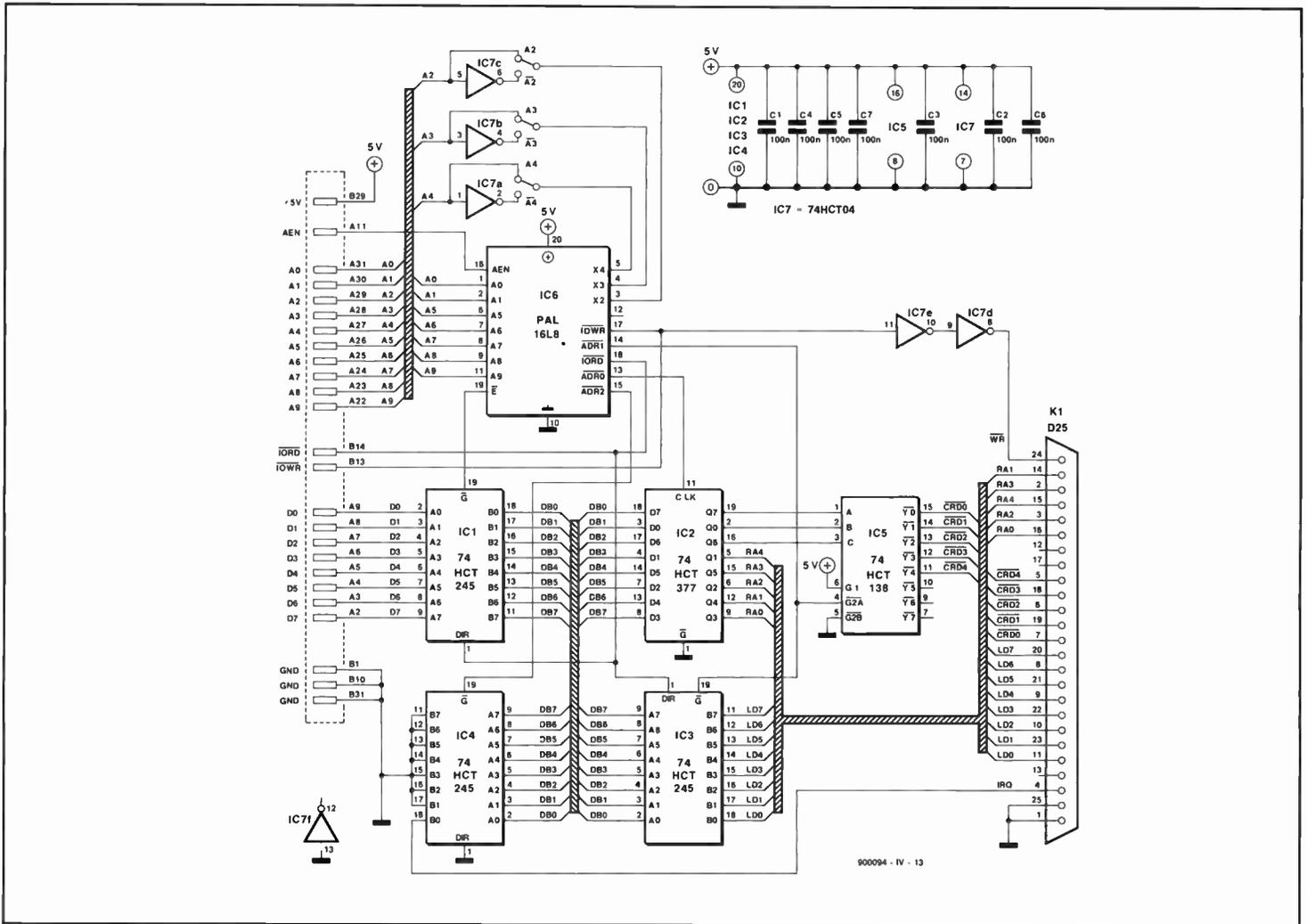


Fig. 21. Circuit diagram of the IBM interface.

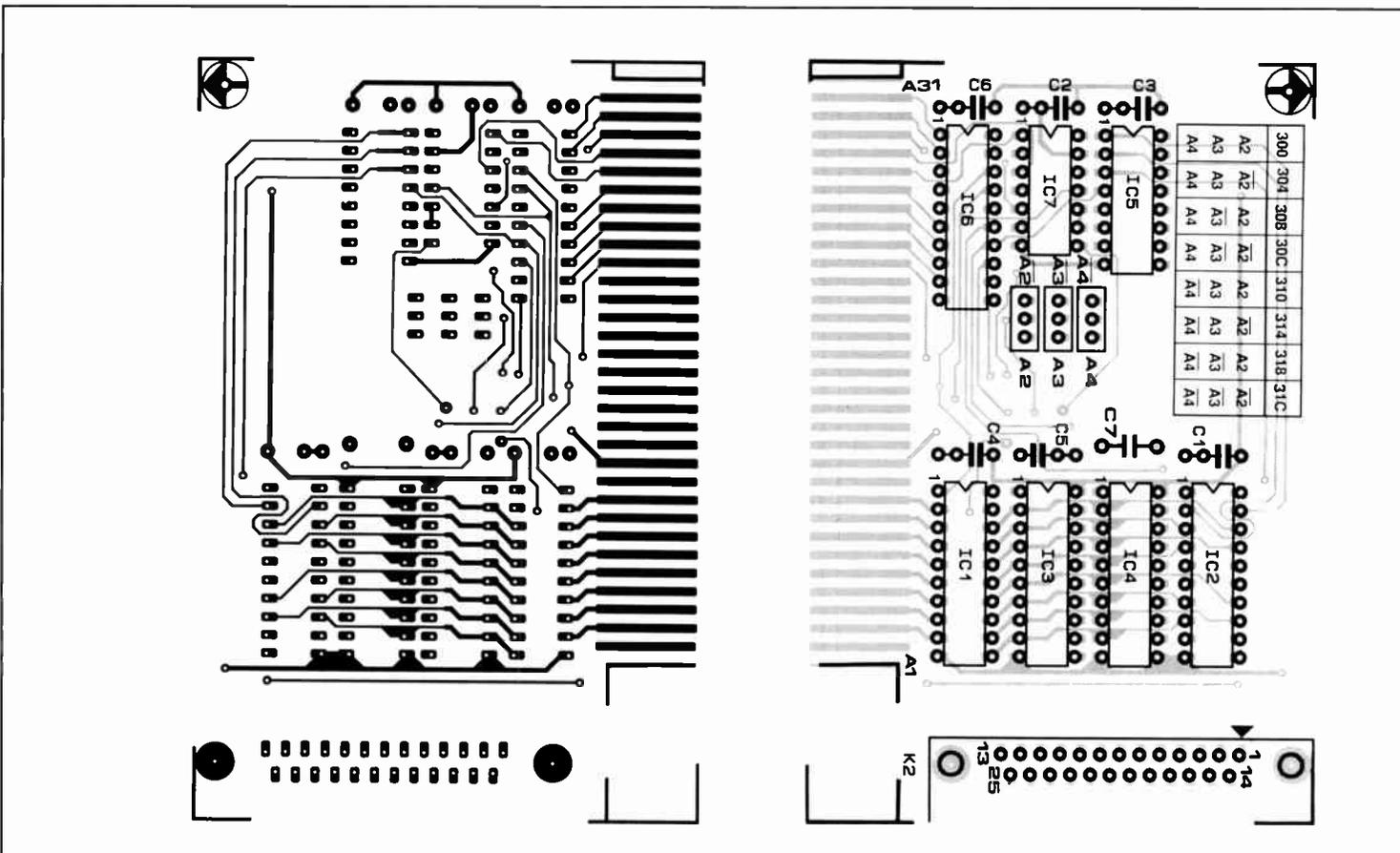


Fig. 22. The printed-circuit board for the IBM interface is designed as a slot-in card.

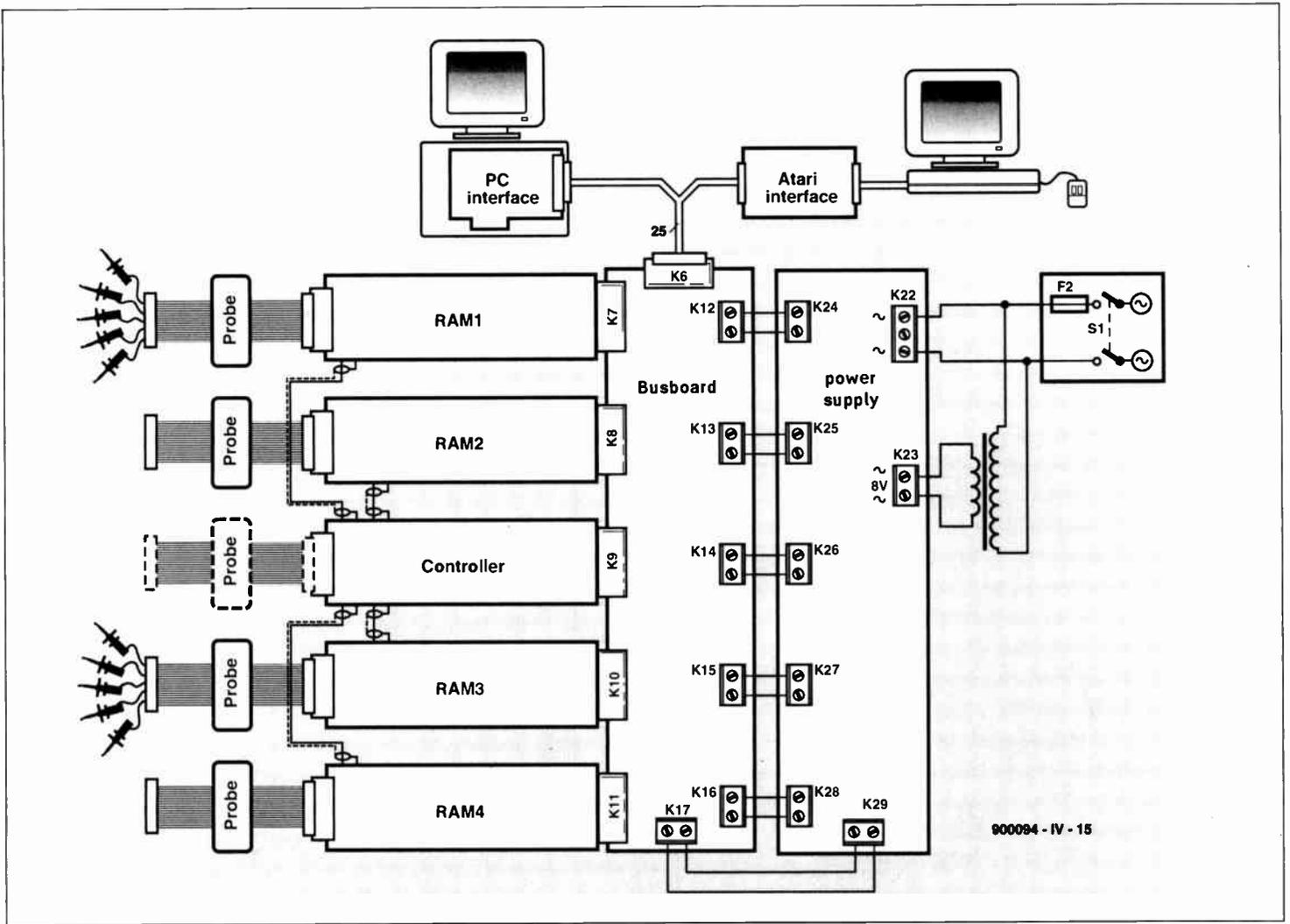


Fig. 23. Overview of the logic analyser and the wiring between the various boards.

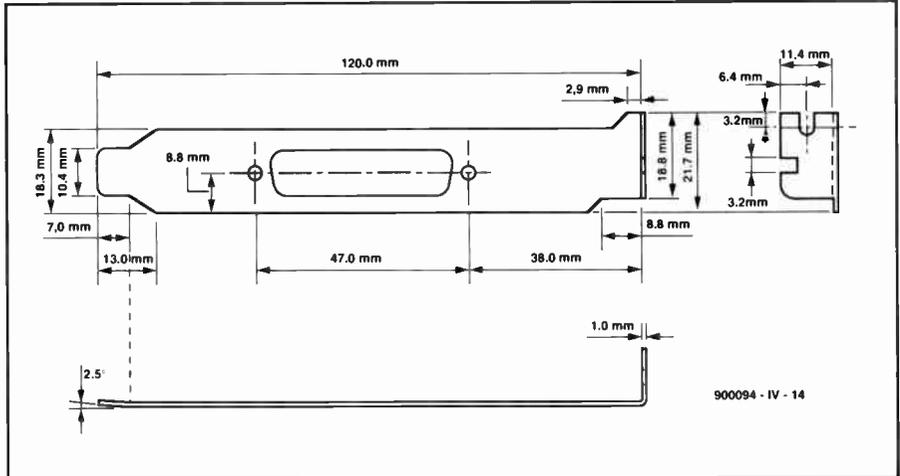
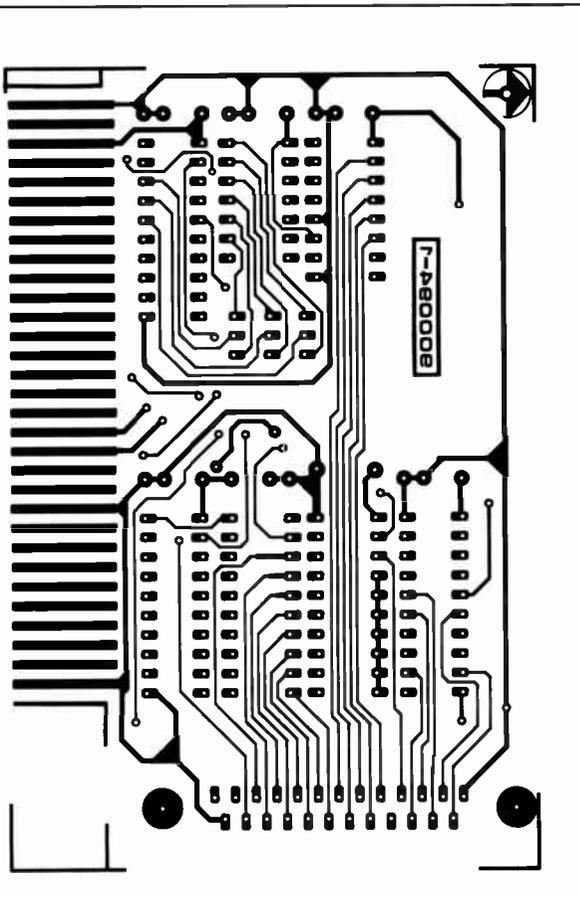


Fig. 24. The IBM interface print should be secured with a fixing plate as shown here.

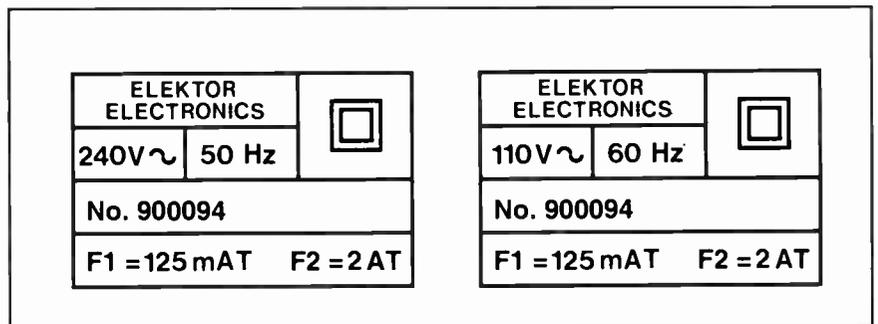


Fig. 25. Suggested labels for the rear panel of the logic analyser.

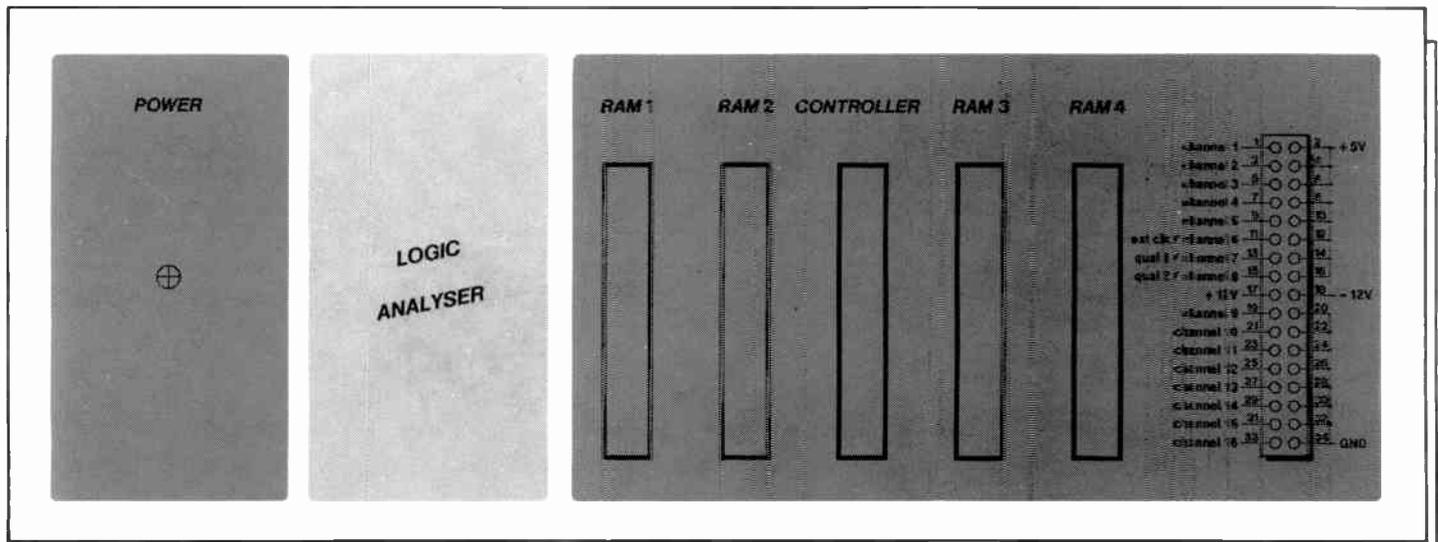


Fig. 26. The front panel for the logic analyser is available through our Readers Services.

PARTS LISTS	
<p><b>Power supply</b></p> <p><b>Capacitors:</b>            C67, C70, C73, C76, C79, C82,            C83 = 470 <math>\mu</math>F, 25 V            C68, C71, C74, C77, C80 = 330 nF            C69, C72, C75, C78, C81, C84,            C85 = 100 nF</p> <p><b>Semiconductors:</b>            D2–D5 = BYW29            D6–D9 = 1N4001            IC65–IC69 = 78S05            IC70 = 7812            IC71 = 7912</p> <p><b>Miscellaneous:</b>            K23–K29 = 2-way terminal block,            5-cm centre            K22 = 3-way terminal block, 5-cm centre            Tr1 = mains transformer, 12 V, 3.75 VA            Tr2 = mains transformer 8 V, 5 A            S1 = mains on/off switch with            integral fuse holder            F1 = fuseholder and fuse, 63 mA,            delayed action</p>	<p><b>Atari interface</b></p> <p><b>Resistors:</b>            R32–R34 = 2.2 k<math>\Omega</math></p> <p><b>Capacitors:</b>            C64–C66 = 100 nF</p> <p><b>Semiconductors:</b>            IC59 = 74HCT574            IC60 = 74HCT138            IC61 = 74HCT00            IC62 = 74HCT02            IC63 = 74HCT03            IC64 = 74HCT245</p>
<p><b>Miscellaneous:</b>            K20 = 19-pole male D connector or            20-way box header (see text)            K21 = 25-pole female D connector for            PCB mounting            PCB 900094-6</p> <p><b>IBM interface</b></p> <p><b>Capacitors:</b>            C1–C7 = 100 nF</p> <p><b>Semiconductors:</b>            IC1, IC3, IC4 = 74HCT245            IC2 = 74HCT377            IC5 = 74HCT138            IC6 = PAL16L8 (Order No. 5973)            IC7 = 74HCT04</p> <p><b>Miscellaneous:</b>            K1 = 25-pole female D connector for            PCB mounting            Fixing plate (see Fig. 22)            PCB 900094-1</p>	

shown in Fig. 19. The DMA interface can access two addresses in the circuit via line A1. The control register, IC<sub>59</sub>, is at one of these addresses (A1 = 0). The address of the apparatus must be written in the three most significant bits of this register in order to actuate the analyser.

The logic analyser has address 4; whether that is stored in the control register is checked by gates IC<sub>61c</sub> and IC<sub>62c</sub>.

The output signal of IC<sub>61c</sub> enables or disables the various inputs and outputs of the interface.

The remaining bits of the control register

are used to address the various registers in the analyser proper: Q0 and Q1 provide the two address lines for the register, while Q2–Q4 control address decoder IC<sub>60</sub>, which generates the five card-select signals.

When the interface is actuated by the four highest bits of the control register, data may be sent to and from the logic analyser via bidirectional buffer IC<sub>64</sub>. The buffer is addressed when A1 is high. The direction of the data transport is determined by the read/write> line.

The single-step signal is produced by IC<sub>63c</sub> and IC<sub>63d</sub> from the strobe signal for the data

bus and the WR> signal.

## Atari interface board

The board for the Atari interface has been designed as a sort of adapter plug (see Fig. 20 and 27) that can be inserted at the rear of the computer. The PCB-type 19-way male D connector for this is, however, not easily available in many locations. There is, therefore, the possibility to use a box header (which is much more readily available) in the K20 position. Starting at pin 1, the wires in the cable

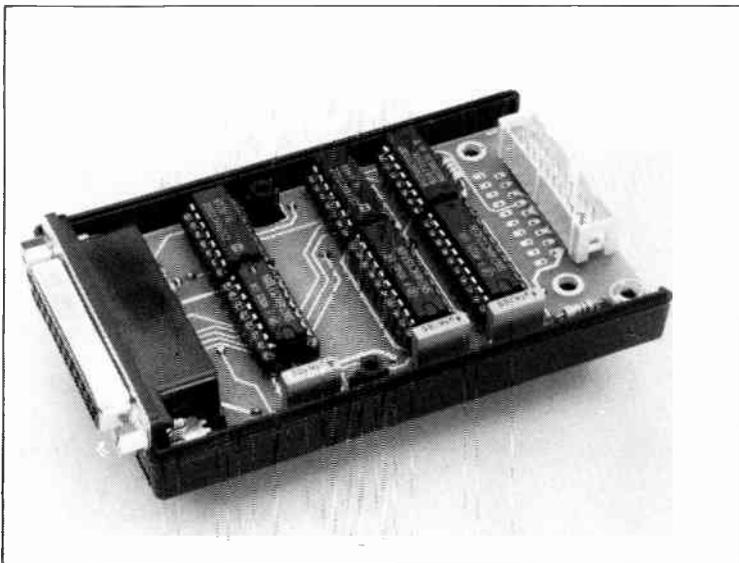


Fig. 27. Photograph of completed Atari interface board.

are soldered or crimped as follows: 1 to 1; 2 to 11; 3 to 2; 4 to 12; 5 to 3; and so on; only pin 20 of the box header is not used.

No such difficulties are envisaged with  $K_{21}$ . The cable between the interface and the logic analyser may be a standard computer accessory: 25-way with male and female connectors. It should, however, not be longer than one metre.

### IBM interface

The interface for IBM XT and AT computers consists of not much more than a number of digital inputs and outputs—see Fig. 21. The data bus for the computer is buffered by  $IC_1$ . This is not necessary for the address lines of the computer, since most lines are connected to only one input. There are, nevertheless, three address lines that, depending on the position of the jumpers near  $IC_6$ , are loaded with up to two inputs. Circuit  $IC_6$  is the address decoder of the interface.

The basic address of the card may be arranged in steps of four addresses from  $300_{hex}$  to  $31C_{hex}$  with the aid of jumpers and inverters in lines A2–A4.

Four addresses emanate from the address decoder (a PAL): an enable signal for the

data bus buffer (E $\rightarrow$ ) and three select signals for controlling the three individual addresses on the interface card: ADR0–ADR2.

The address register is found at basic address +0. The address with which a card and a register are addressed on that card is written in the address register.

The data register is found at basic address +1, via which data are written to, or read from, the logic analyser. Simultaneous with the reading or writing, card select decoder  $IC_5$  is enabled via the ADR1 line to ensure that the cards of the analyser are connected to the bus only when this really necessary.

The IRQ signal from the analyser enters via basic address +2 on the interface card. This is processed as data, and not as an interrupt.

### IBM interface board

The dimensions of the PCB for the IBM interface are determined solely by those of the two connectors—see Fig. 22 and 28. Since the electronics do not need much space, it has been possible to include a table on the board that indicates what jumpers are required to place a certain basic address for the card.

To prevent the card being pulled from the slot by the connecting cable, it is essential

that the board is provided with a fixing plate with which it can be fastened securely on to the computer. Such a plate can be made as shown in Fig. 24.

For the connection between the interface and the computer the same sort of cable as for the Atari may be used.

### Overview

An overview of the logic analyser and all that may go with it is shown in Fig. 23.

The control card is always connected to the centre connector of the bus board to ensure that when several RAM cards are used, the connections between these cards and the control card remain as short as feasible.

Before the RAM cards are built in, a 10 k $\Omega$  resistor must be soldered at the track side between pins 11 and 16 of  $IC_{29}$ . This resistor suppresses any reflections that may occur at that end of the clock line to the shift registers.

There is not much wiring in the analyser because most connections are contained on the bus board. What wiring there is comes mainly from the power supply. ■

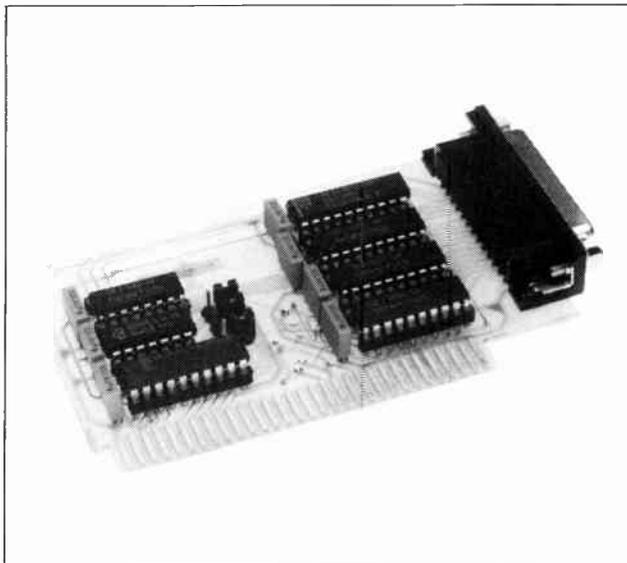


Fig. 28. Photograph of completed IBM interface board.

### THE R.F. CONNECTION

213 North Frederick Ave. #11  
Gaithersburg, MD 20877

ORDERS 1-800-783-2666

INFO 301-840-5477 FAX 301-869-3680

"THIS LIST REPRESENTS ONLY A  
FRACTION OF OUR HUGE INVENTORY"  
"Specialist in RF Connectors and Coax"

Part No.	Description	Price
PL-259/USA	UHF Male Phenolic, USA made	\$ .70
PL-259/ST	UHF Male Silver Teflon USA	1.50
UG-210/U	N Male RG-8, 213, 2*4 Delta	3.25
UG-218/U	N Male RG-8, 213, 2*4 Kings	5.00
9913/PIN	N Male Pin for 9913, 9086, 8214 fits UG-21, DUJ & UG-21 B/UN's	1.50
UG-210/99-13	N Male for RG-8 with 9913 Pin	3.95
UG-218/9913	N Male for RG-8 with 9913 Pin	5.75
UG-146A/U	N Male to SO-239, Teflon USA	6.00
UG-83B/U	N Female to PL-259, Teflon USA	6.00

PRICES DO NOT INCLUDE SHIPPING  
PRICES SUBJECT TO CHANGE  
VISA, MASTERCARD, ADD 4%  
LPS C C D ADD \$3.50 PER ORDER

## WORD OF MOUTH

Helps us grow, means a stronger publication that can do more of the things that need doing in the pursuit of better electronic systems. If you have friends, associates, relatives or even enemies who share your enthusiasm for ELEKTOR ELECTRONICS tell us their names and addresses, and we will send the word along. THANKS

# VIDEO A-D/D-A CONVERTER


## PART 2: A 30-MHz VIDEO ADC/DAC DEVELOPMENT BOARD

Following last month's introduction into the basic operation of the two main integrated circuits in the design, the TDA8708 and the TDA8702, this second and last instalment focuses on the more practical side of things. Are you triggered? Here is a high-speed video A-D/D-A converter board aimed at helping you on the way with your own video experiments.

**P. Godon (Philips Components, Paris)**

*Continued from the May 1991 issue*

The block diagram of the development board, Fig. 8, shows the two converter ICs surrounded by quite a few sockets, switches and connectors. The switches, K1 through K9, are actually jumpers that allow different modes of operation to be selected. The BNC sockets, K10 through K17, are the analogue

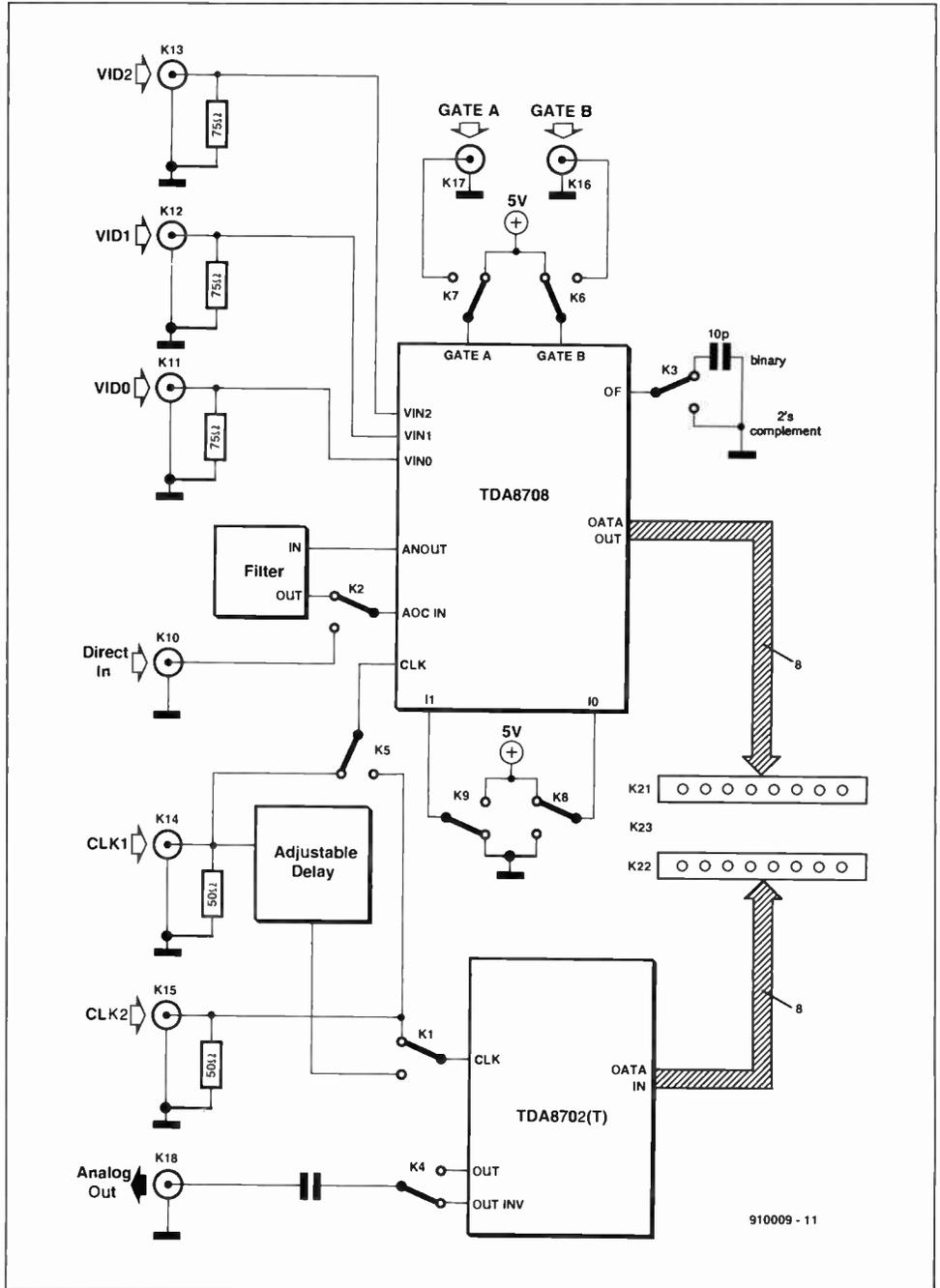

**Fig. 8. Block diagram of the video processor card. Most of the switches shown here are wire jumpers to select different modes of operation.**

Table 8. Connector overview					
Connector	Type	Function	Connector	Type	Function
K1	jumper	Clock 2 / delayed Clock 1	K13	BNC socket	ADC input 2
K2	jumper	Video input / direct input	K14	BNC socket	Clock input 1
K3	jumper	ADC output: binary or 2's complement	K15	BNC socket	Clock input 2
K4	jumper	DAC output: true or inverted	K16	BNC socket	Mode gate B
K5	jumper	Clock 1 / Clock 2	K17	BNC socket	Mode gate A
K6	jumper	Gate B active / disabled (+5 V)	K18	BNC socket	DAC analogue output
K7	jumper	Gate A active / disabled (+5 V)	K19	PCB pin	Clock delay
K8	jumper	Video input selection: Bit 0=H / Bit 0=L	K20	PCB header	Supply voltages
K9	jumper	Video input selection: Bit 1=L / Bit 0=H	K21	PCB header	ADC output
K10	BNC socket	ADC direct input	K22	PCB header	DAC input
K11	BNC socket	ADC input 0	K23	32-way DIN	combined ADC output and DAC input
K12	BNC socket	ADC input 1			

video inputs and the digital control inputs. The analogue output signal of the DAC is available on socket K18. The board is linked to a computer or microprocessor system via connectors K21 and K22, or K23. All digital inputs and outputs of the board are TTL compatible.

The development board is connected to analogue and digital 5-V power supplies via K20. Two separate power supplies are required to ensure the best possible decoupling of the analogue and digital sections.

The 'adjustable delay' block is formed by an integrated circuit that has not been discussed last month. This IC, a Type 1505-5B from Data Delay Devices, contains a stepped delay line. The signal applied to the CLK1 input of the board, K14, can be delayed in steps of 1 ns to a maximum of 5 ns. The delay line has a d.c. resistance of  $0.7 \Omega$  and an impedance of about  $100 \Omega$ .

Finally, the resistors shown in the block diagram ensure that video sources are terminated in  $75 \Omega$ , and the clock inputs in  $50 \Omega$ .

## The development circuit

The circuit diagram of the video A-D/D-A card is given in Fig. 10. As discussed last month, the TDA8708 stores the current analogue value at the first leading edge of the clock signal, after the 1.5-V threshold is exceeded. You will also recall that the digital equivalent of the analogue value appears at the output after a delay,  $T_d$ , of 8 to 20 ns. At the next trailing edge of the clock signal, the DAC copies the digital information, and supplies the corresponding analogue value after the conversion delay,  $t_d$ , of 3 ns. Hence, the video input signal is subject to a total delay,  $T_v$ , of

$$T_v = T_d + 1/2f + t_d$$

At relatively high clock frequencies, say, 30 MHz, it may happen that the minimum required delay time between the A-to-D and D-to-A conversions is not available. The DAC requires that the input data remain stable for at least 0.3 ns. Since the time between the leading and the trailing edge is only 17 ns for a 30-MHz clock signal, it is readily seen that the DAC may have trouble loading stable data when the required delay,  $T_d$ , is yet to be subtracted. This potential problem is eliminated by the previously mentioned delay line, IC3, which delays the trailing edge of the clock 1 to 6 ns, depending on the selected 'tap' (jumper K19). This compensation ensures the correct operation of the conversion processes when relatively high clock speeds are used. The diagram in Fig. 9 shows the combined timing of the ADC and the DAC, along with the data setup times and associated delays.

## Construction

In view of the speed of the signals involved, the video A-D/D-A circuit is best built on a printed-circuit board of the design shown in Fig. 11. The board is double-sided, but not


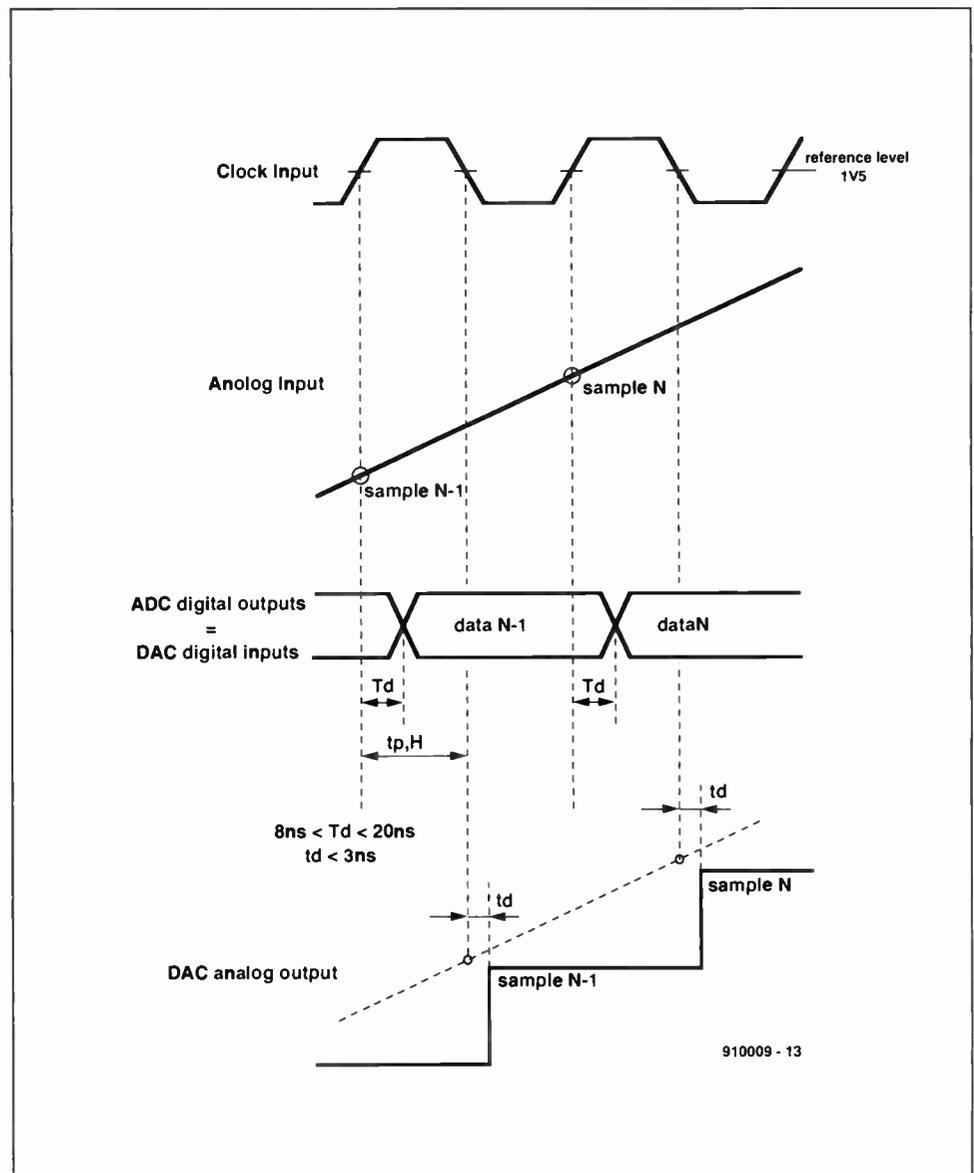
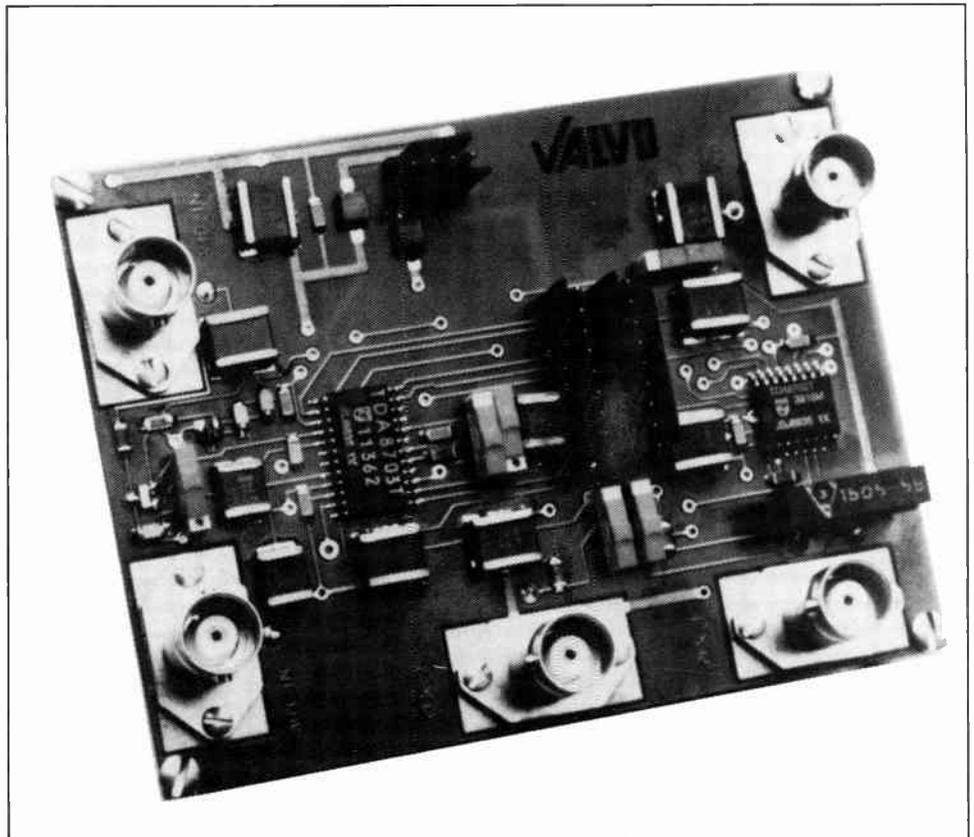


Fig. 9. Overview of conversion timing and data setup times for the ADC and the DAC.

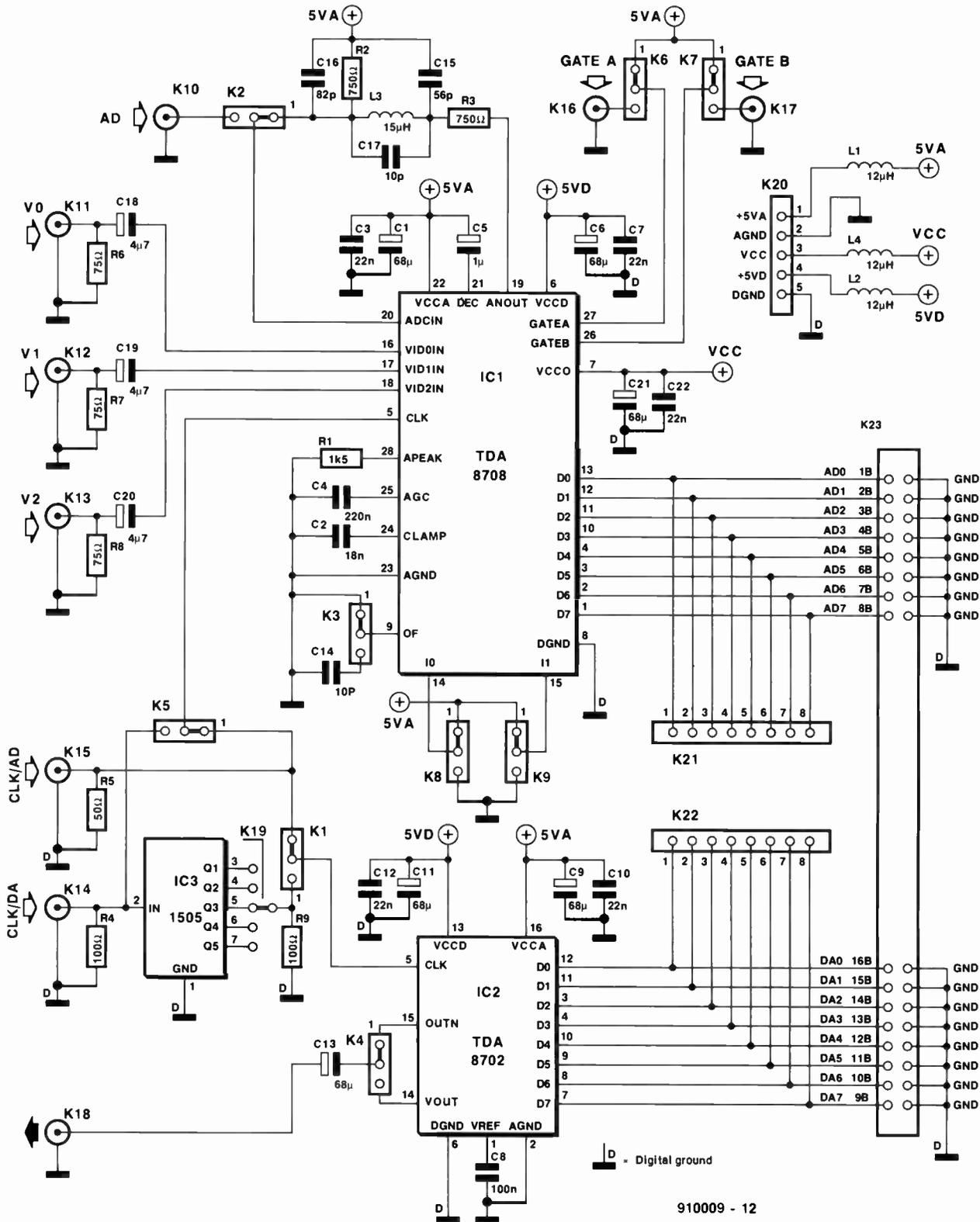

910009 - 12

Fig. 10. Circuit diagram of the ADC/DAC converter card. You have the digitized video signal available at a resolution of 8 bits between connectors K21 and K22. A separate connector, K23, allows the card to be connected to a computer bus.

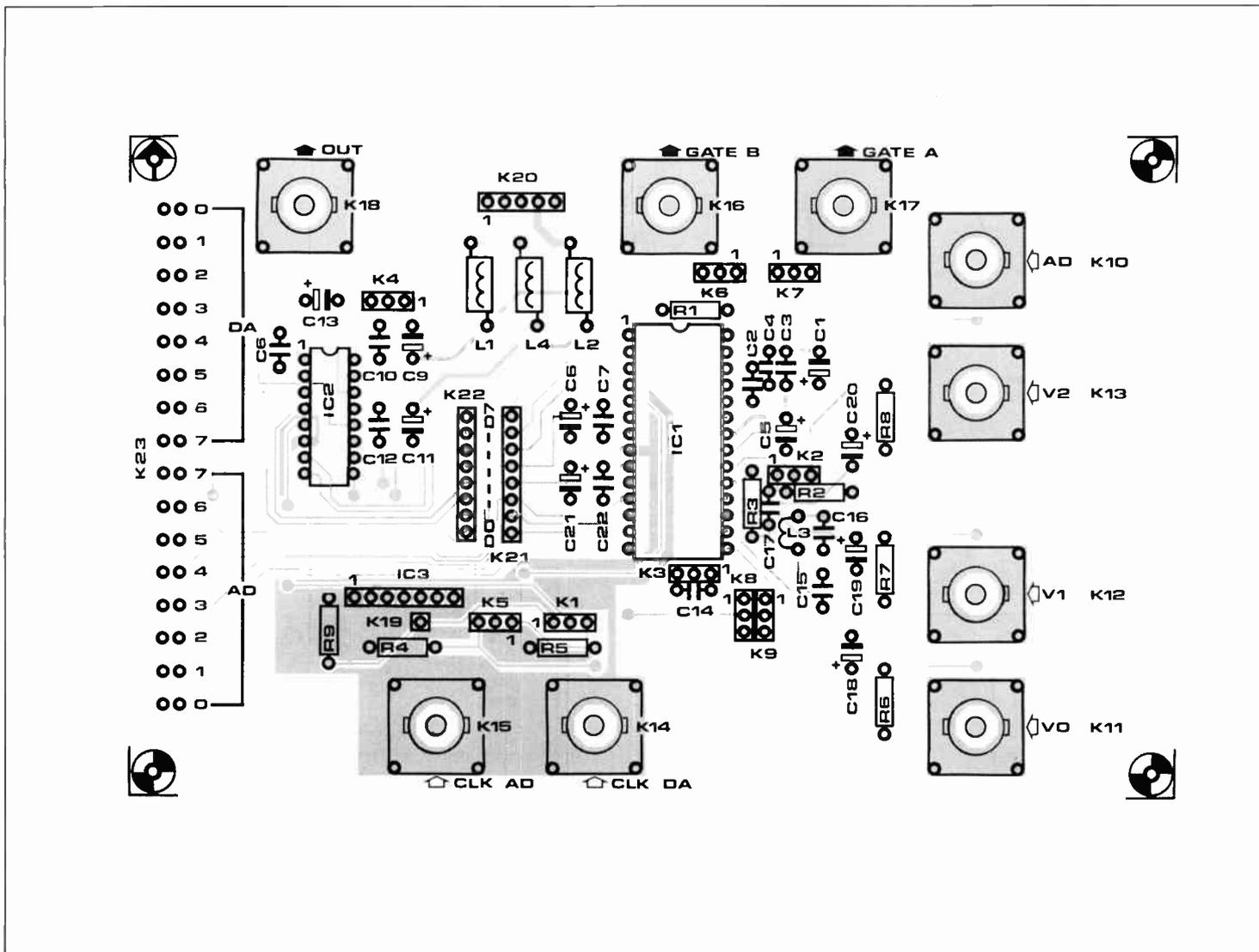


Fig. 11a. Component mounting plan of the double-sided printed circuit board. Note that the board is designed for PCB-mount BNC sockets.

through-plated. Its design allows BNC sockets to be fitted without coaxial cables, which reduces parasitic capacitance to a minimum.

Most of the PCB headers and jumper blocks on the board can be made from single-row and double-row pin headers, which are available in strips of 36 and 72 pins with a spacing of 0.1 inch. Headers K21 and K22, for instance, are 8-pin pieces cut from a larger strip.

Connector K23 is a 32-way angled type to DIN41612. It allows the digital data inputs of the DAC, and the digital outputs of the ADC, to be connected to a microprocessor system bus. For a straight link between the ADC and the DAC, interconnect the corresponding pins on K21 and K22. Finally, note that although an SMA (surface-mount assembly) version of the development board is shown in Fig. 11, all components on the board shown in Fig. 10 have standard sizes. ■

**COMPONENTS LIST**

**Resistors:**

- 1 1kΩ5 R1
- 2 750Ω R2;R3
- 2 100Ω R4;R9
- 4 75Ω R5 - R8

**Capacitors:**

- 6 68μF 6V3 C21
- 1 18nF C2
- 5 22nF C3;C7;C10; C12;C22
- 1 220nF C4
- 1 1μF 10V C5
- 1 100nF C8
- 2 10pF C14;C17
- 1 56pF C15
- 1 82pF C16
- 3 4μF7 10V C18;C19;C20

**Inductors:**

- 3 12μH L1;L2;L4
- 1 15μH L3

**Miscellaneous:**

- 1 TDA8708 IC1
- 1 TDA8702 IC2
- 1 1505-5b\* IC3

**Miscellaneous:**

- 9 3-pin PCB header K1 - K9
- 9 PCB-mount BNC socket K10 - K18
- 1 solder pin K19
- 1 5-pin PCB header K20
- 2 8-pin PCB header K21;K22
- 1 32-way angled connector to DIN41612 K23
- 0.1-inch jumpers as required

\* UK distributor: BFI Ibexsa Electronics • Burnt Ash Road • Quarrywood Estate • Aylesford • Kent ME20 7NA. Tel. (0622 882467), Fax (0622) 882469.

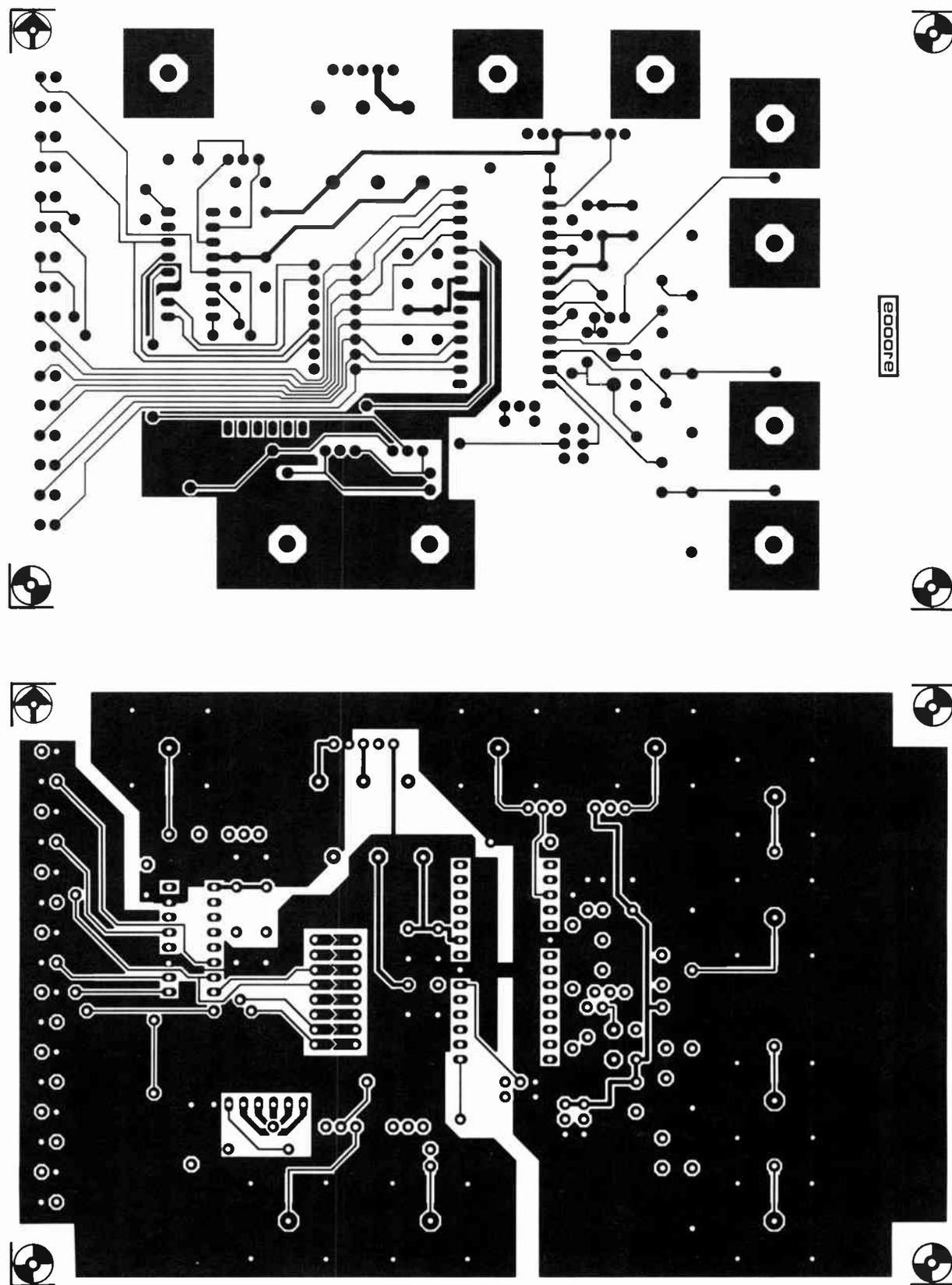


Fig. 11b. Solder side (above) and component side (below) of the PCB for the video ADC/DAC card.

# DIGITAL PHASE METER

by R. Lucassen

Phase meters are rare instruments, even in the laboratory or workshop of audio and hi-fi engineers and enthusiasts. Perhaps that is because until the advent of reliable digital techniques it was fairly difficult to design an accurate direct-reading phase meter. In one commercial catalogue published in the 1970s, a phase meter is advertised as having "an accuracy of about 3 degrees from 10 Hz to 30 kHz". Clearly, for modern audio equipment, that is no longer acceptable. Another reason may be that a phase meter is a fairly specialized instrument: many engineers and technicians measure phase shift with the aid of Lissajous figures (which do not give very accurate results either). The phase meter presented in this article is accurate to within  $0.5^\circ$  over the frequency range 10 Hz to 20 kHz.

THE PHASE shift between two electrical signals is of great importance in most branches of electronic engineering, but more particularly in audio engineering. In all circuits containing capacitors or inductors or both, frequency-dependent phase shifts will occur and these will affect the wanted operation of many circuits. There are, of course, circuits, such as filters, where phase shift is one of the design parameters.

The basic design of the phase meter may be gleaned from the block diagram in Fig. 1. Note, however, that, for the sake of simplicity, an analogue meter has been substituted for the LED display with which the instrument is actually equipped.

The analogue signals presented to the display section are digitized before they are processed. Since alternating signals are involved, this is quite simple: the positive part of the signals is converted to a logic low (0) and the negative part to a logic high (1). The timing diagram in Fig. 2 shows the analogue input signals (A and B) together with their digitized variants (A' and B'). The use of the digitized signals as the clock for a bistable (US: flip-flop) ensures a perfectly symmetrical (i.e., duty factor is 50%) digital output signal at a frequency equal to half that of the input signal. This guarantees that differing lengths of positive and negative half periods, noise and other spurious signals have no effect on the accuracy of the measurements.

The time difference between the leading edges of the signals emanating from the bistables is a measure of the phase shift between the two input signals. The output of the XOR gate is high during this time difference. The ratio of the width of the logic high signal at the output of the XOR gate to that of the output signal of bistable FF<sub>1</sub> gives the phase shift, which only has to be converted into degrees.

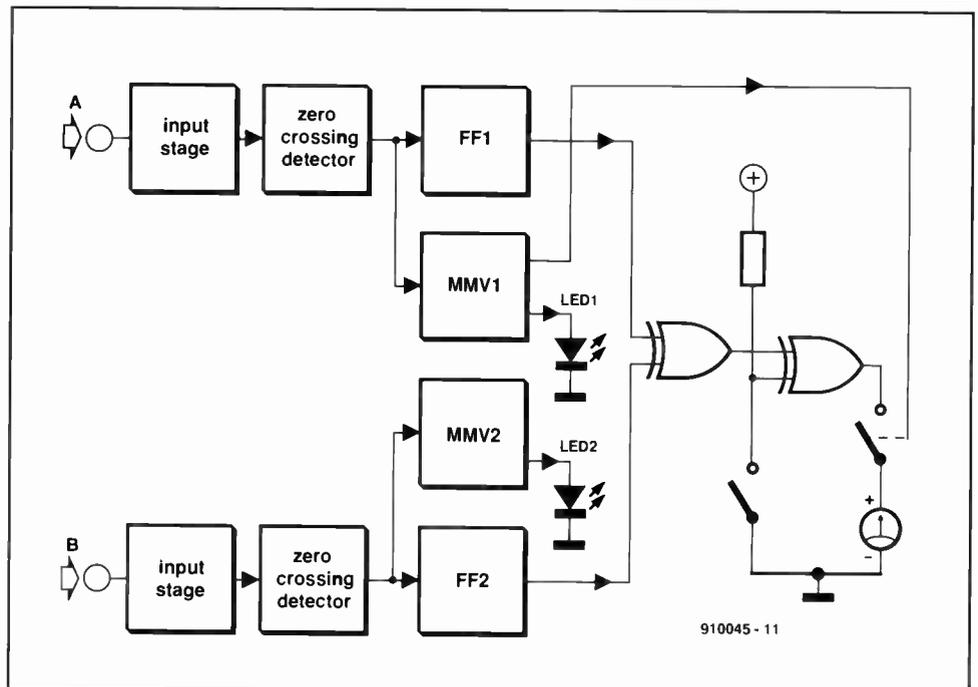
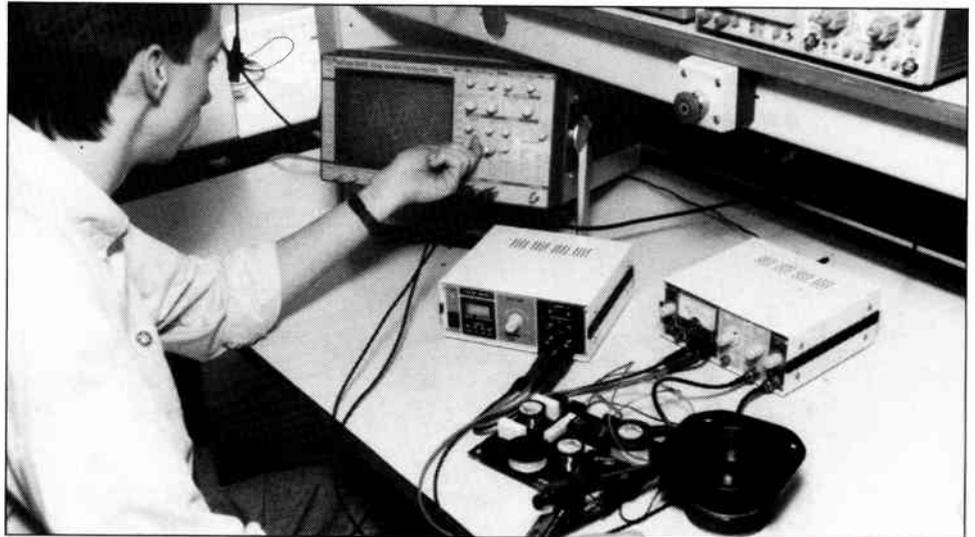


Fig. 1. Block diagram of the digital phase meter.

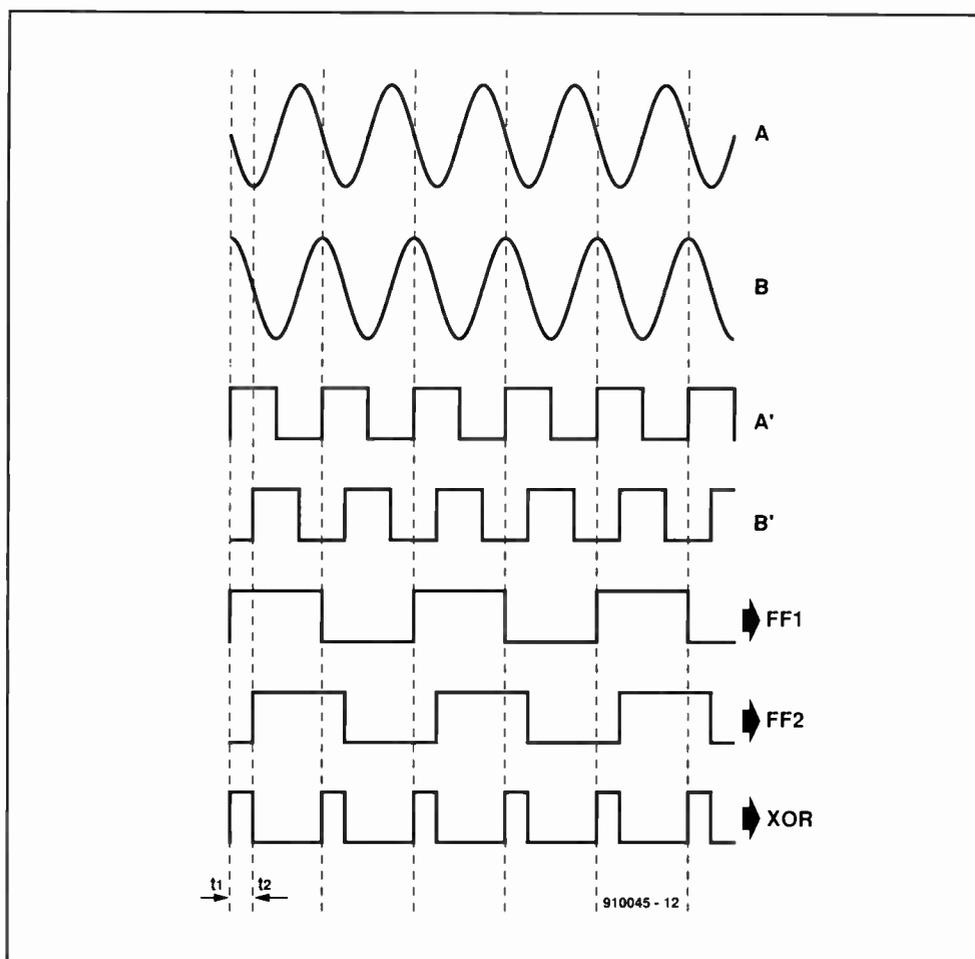


Fig. 2. Timing diagram of the analogue-to-digital conversion section.

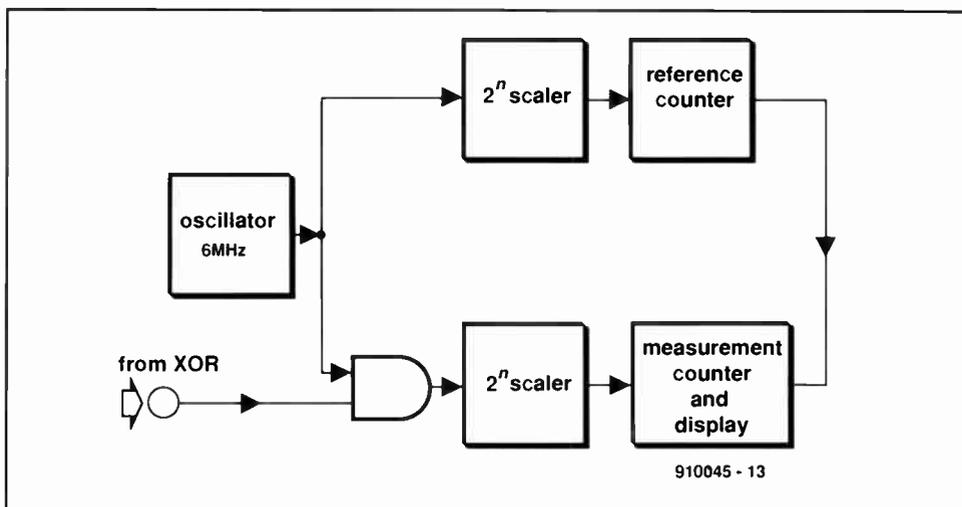


Fig. 3. Block diagram of the digital measuring section.

gate indicates at all times by how much signal B lags signal A. Therefore, the pulse represents a phase difference of 0–360°. Since it may also be of interest to measure the lag of signal A with respect to signal B, there is a second XOR gate whose output may be inverted.

Monostables MMV<sub>1</sub> and MMV<sub>2</sub> indicate by LEDs that usable signals, that is, signals whose phase difference is to be measured, exist at the associated inputs. Furthermore, the output of MMV<sub>1</sub> is used to actuate the meter. If only signal A is present, the meter

must remain stably in the centre position. If it does not, the input signal is unstable and, therefore, not suitable for measurements.

Since the width of the pulse at the output of the XOR gate is a measure of the phase shift, it would seem that a simple analogue interface in the form of an integrator would be sufficient for driving a moving meter. That would, however, present certain difficulties, such as a strong dependence on temperature and the fact that to obtain a stable meter deflection a high integration constant would

have to be used. That would make the measurement very slow and the instrument inconvenient to use.

A digital meter was therefore chosen, which can accurately indicate any phase difference between 0° and 360° with a resolution of 1°. The diagram in Fig. 3 shows how this meter operates.

A central clock frequency of 6 MHz is used, which is applied continually to one branch of the circuit, and to the other branch only when the output of the XOR gate of the phase comparator is high. In both branches, the clock pulses are divided by 2<sup>n</sup> before they are applied to the respective stage. Factor *n* is set manually. Note that since division takes place after the AND gate, this gate has no effect on the accuracy of the measurement.

As soon as the content of the reference counter has reached a value of 3,600, one output of the counter goes high to indicate that the measurement is complete and that 3,600/2<sup>n</sup> pulses were processed during it.

At the instant the reference counter has counted 3,600 pulses, the display memory is prompted to take over the contents of the reference counter. The display will then show the number of counted pulses, that is, when the phase shift is 0°, no pulses were counted; if the phase shift is 360°, 3,600 pulses were counted. The last digit of the number of pulses is omitted to make the display read the number of degrees.

Note that the accuracy of the measurement depends on the ratio of the measuring time to the frequency of the reference signal. The measurand is therefore sampled at a frequency of 6 MHz. Even at the highest signal frequency of 20 kHz, the error introduced by this is negligible

Furthermore, the design of the instrument arranges that counting always starts at the beginning of a period. Therefore, it is never known how much of the last period is measured and steps must consequently be taken to ensure that the last period has negligible influence on the measurement. This is done by taking many periods per measurement. For instance, a measurement over 10 periods has a possible error of 10%, whereas over 200 periods the error would be only 0.5%. Because of that, the instrument contains a counter (in the error indicating circuit) that monitors over how many signal periods a measurement was processed.

## Circuit description

The instrument is constructed on three printed-circuit boards; the associated circuits are shown in Fig. 4, 5 and 6.

Figure 4 is the circuit diagram for the motherboard. The power supply is a straightforward, conventional type with a bridge rectifier and two integrated regulators.

The buffered and possibly attenuated (–20dB) signal is applied to terminals A and B. Input A is used as the reference signal and for actuating the metering section.

The incoming analogue signal is converted into a digital signal in IC<sub>12</sub> (channel A) and IC<sub>14</sub> (channel B). The offset of these


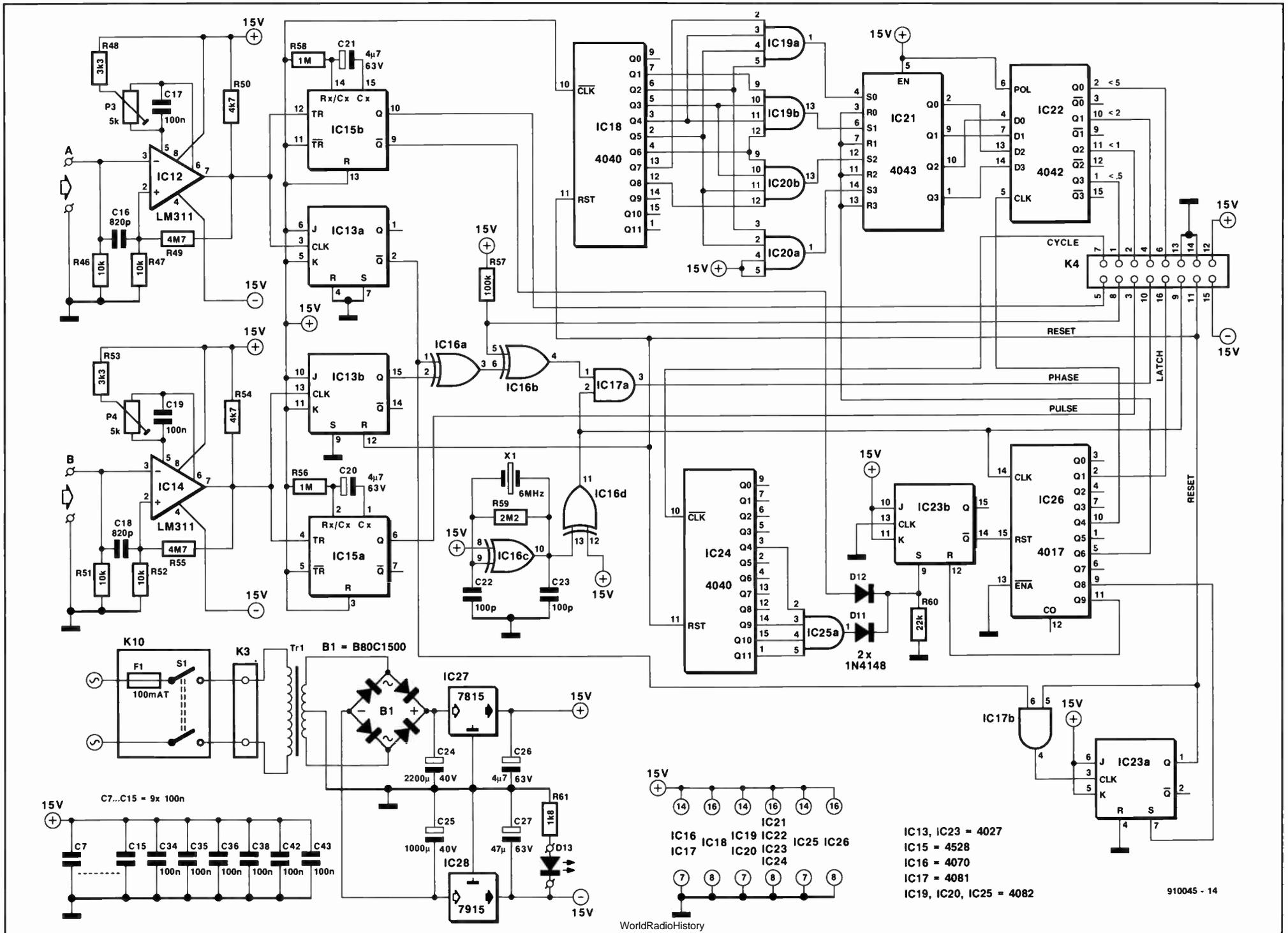


Fig. 4. Diagram of the circuit contained on the mother board.

Fig. 5. Diagram of the circuit containing the displays, input stages, and selector switches.

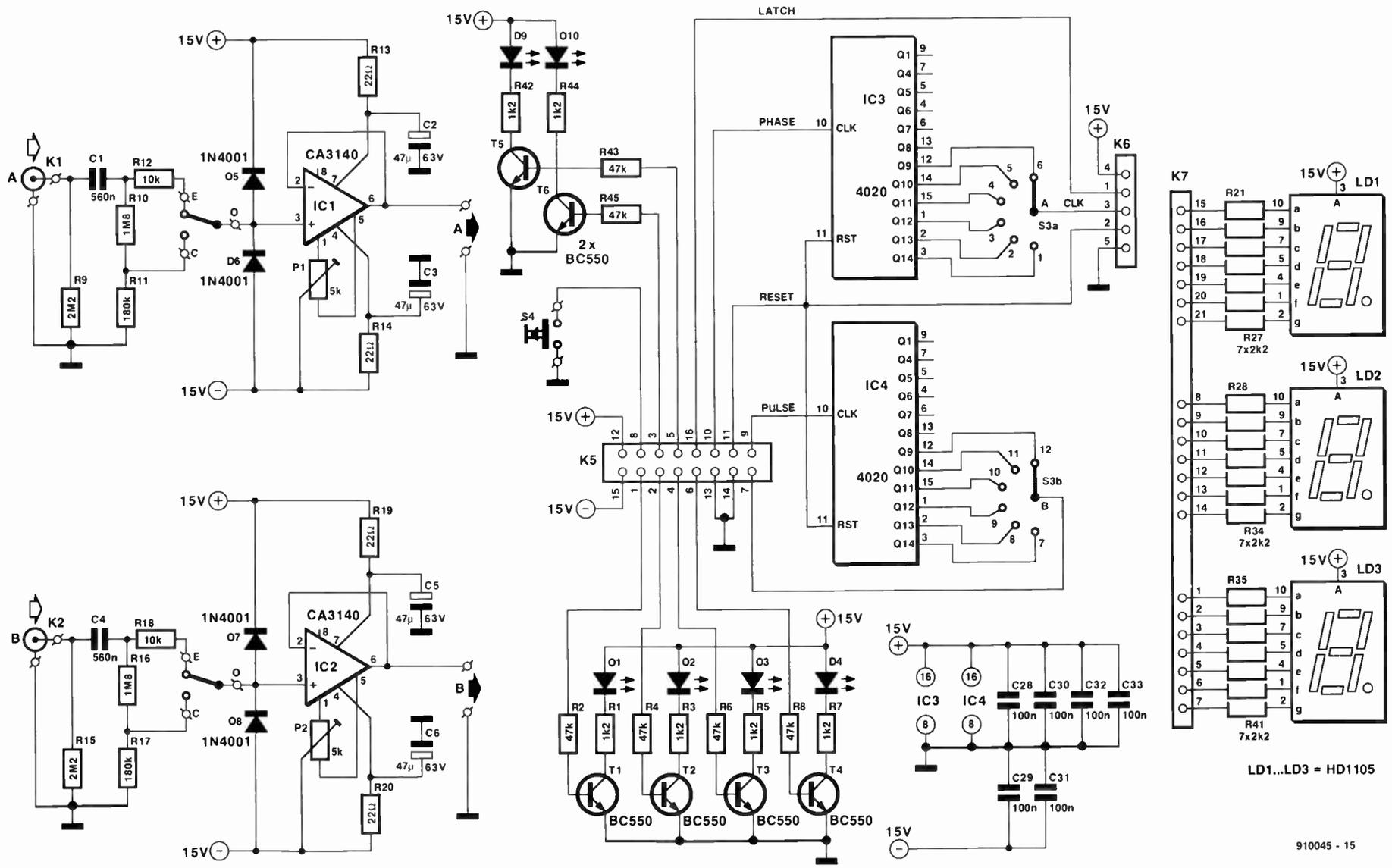

LD1...LD3 = HD1105

910045 - 15

opamps is compensated by presets P<sub>3</sub> and P<sub>4</sub> respectively. Bistables IC<sub>13a</sub> and IC<sub>13b</sub> split the digitized signal into a symmetrical signal (duty factor = 50%) that is suitable for measurements.

Monostables IC<sub>15a</sub> and IC<sub>15b</sub> actuate the LEDs (D<sub>9</sub> and D<sub>10</sub>) on the front panel to indicate that suitable signals are input. At the same time, IC<sub>15b</sub> enables the reference counter via its Q output.

The outputs of IC<sub>13a</sub> and IC<sub>13b</sub> are combined via XOR gate IC<sub>16a</sub>. Another XOR gate, IC<sub>16b</sub>, and switch S<sub>4</sub> on the front panel make it possible to invert the phase difference as discussed before.

Finally, IC<sub>17a</sub> combines the output of the phase comparator with the clock frequency (6 MHz). When the output of XOR gate IC<sub>16a</sub> is high, the clock is passed on and the measurement may be carried out.

The clock signal is generated by a crystal oscillator based on IC<sub>16c</sub> and buffered by IC<sub>16d</sub> before it is applied to the relevant stages.

At the end of the measurement, a reset cycle is started by IC<sub>24</sub>. As soon as this IC has counted 3,600 pulses, IC<sub>23b</sub> is set via IC<sub>25a</sub> and OR gate D<sub>11</sub>-D<sub>12</sub> and in its turn resets decade scaler IC<sub>26</sub>. This actuates the latch signal, whereupon the counter state is transferred to the display drivers (further discussed later on). Subsequently, IC<sub>22</sub> receives a clock pulse and stores data concerning any measurement error, after which IC<sub>21</sub> is reset. All relevant measurement data are then stored and the remainder of the circuit is reset via bistable IC<sub>23a</sub>. When the reset cycle is over, IC<sub>23a</sub> is returned to the relevant output state via AND gate IC<sub>17b</sub>. At the same time, IC<sub>24</sub> is reset by the clock pulse that appears at the Q<sub>9</sub> output of IC<sub>26</sub>. The circuit is then ready for the next measurement.

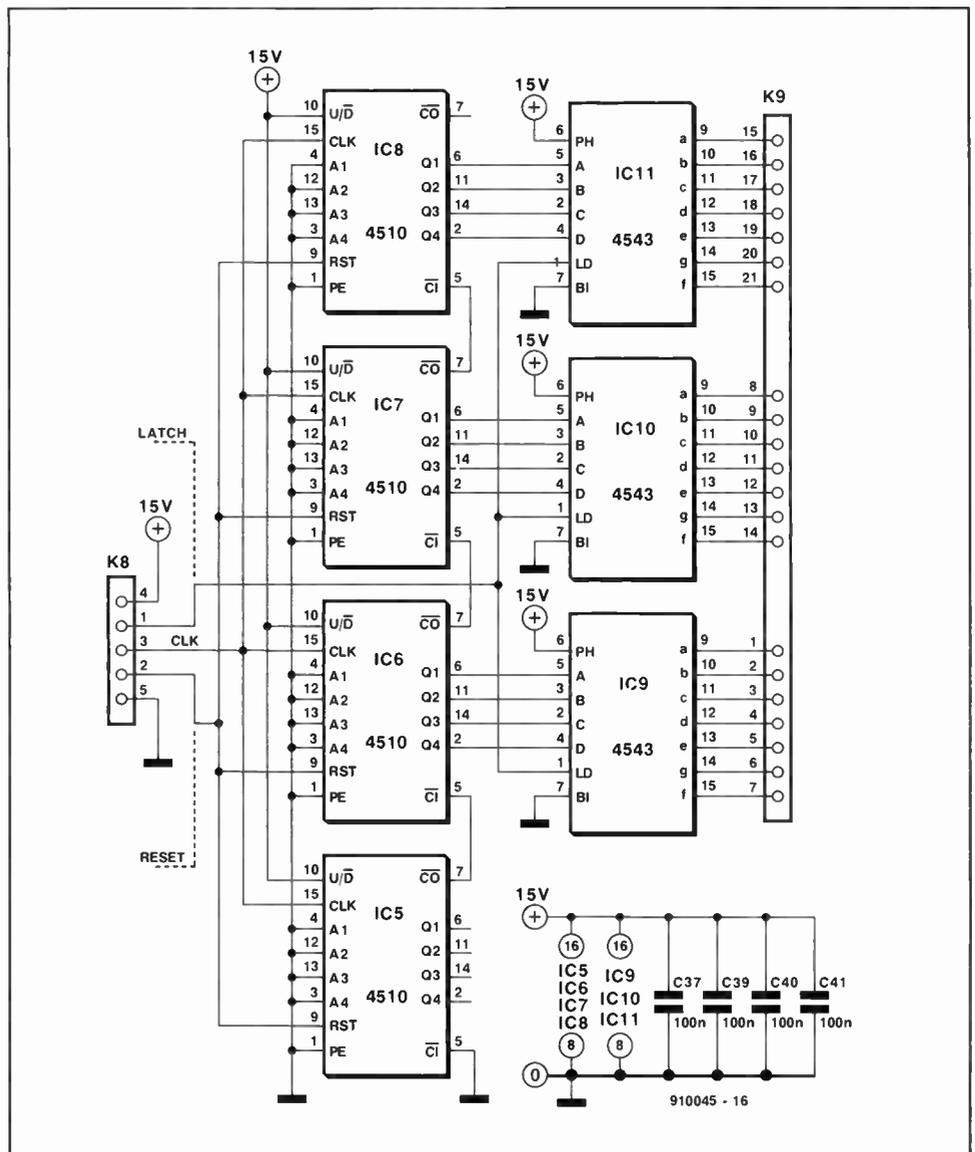


Fig. 6. Diagram of the logic circuits for the LED displays.

#### Resistors:

R1, R3, R5, R7, R42, R44 = 1.2 kΩ  
 R2, R4, R6, R8, R43, R45 = 47 kΩ  
 R9, R15, R59 = 2.2 MΩ  
 R10, R16 = 1.8 MΩ  
 R11, R17 = 180 kΩ  
 R12, R18, R46, R47, R51, R52 = 10 kΩ  
 R13, R14, R19, R20 = 22 Ω  
 R21-R41 = 2.2 kΩ  
 R48, R53 = 3.3 kΩ  
 R49, R55 = 4.7 MΩ  
 R50, R54 = 4.7 kΩ  
 R56, R58 = 1 MΩ  
 R57 = 100 kΩ  
 R60 = 22 kΩ  
 R61 = 1.8 kΩ  
 P1-P4 = 5 kΩ preset

#### Capacitors:

C1, C4 = 560 nF  
 C2, C3, C5, C6, C20, C21,  
 C26 = 4.7 μF, 63 V, radial  
 C7-C15, C17, C19, C28-C44 = 100 nF  
 C16, C18 = 820 pF  
 C22, C23 = 100 pF  
 C24 = 2200 μF, 40 V  
 C25 = 1000 μF, 40 V

## PARTS LIST

C27 = 47 μF, 40 V, radial

#### Semiconductors:

D1-D4, D9, D10, D13 = LED, 3 mm  
 D5-D8 = 1N4001  
 D11, D12 = 1N4148  
 B1 = B80C1500  
 T1-T6 = BC550  
 IC1, IC2 = CA3140+  
 IC3, IC4 = 4020  
 IC5-IC8 = 4510  
 IC9-IC11 = 4543  
 IC12, IC14 = LM311DP  
 IC13, IC23 = 4027  
 IC15 = 4528  
 IC16 = 4070  
 IC17 = 4081  
 IC18, IC24 = 4040  
 IC19, IC20, IC25 = 4082  
 IC21 = 4043  
 IC22 = 4042  
 IC26 = 4017  
 IC27 = 7815  
 IC28 = 7915

#### Miscellaneous:

K1, K2 = BNC audio socket  
 K3 = 2-way terminal block,  
 7.5 mm centre  
 K4, K5 = 16-way box header  
 K10 = mains entry plug with integral  
 fuse holder  
 S1, S2 = single-pole change-over switch  
 S3 = rotary switch, 2 poles, 6 positions,  
 for PCB mounting  
 S4 = SPST switch  
 X1 = crystal, 6 MHz  
 LD1-LD3 = HD1105, common anode  
 Tr1 = mains transformer, 15 V, 18 VA  
 F1 = fuse, 100 mA, delayed-action  
 Mains on-off switch  
 Enclosure (ABS)  
 Knob for S3  
 Heat sinks for voltage regulators  
 PCB 910045-1  
 PCB 910045-2  
 PCB 910045-3  
 Front panel foil 910045-F

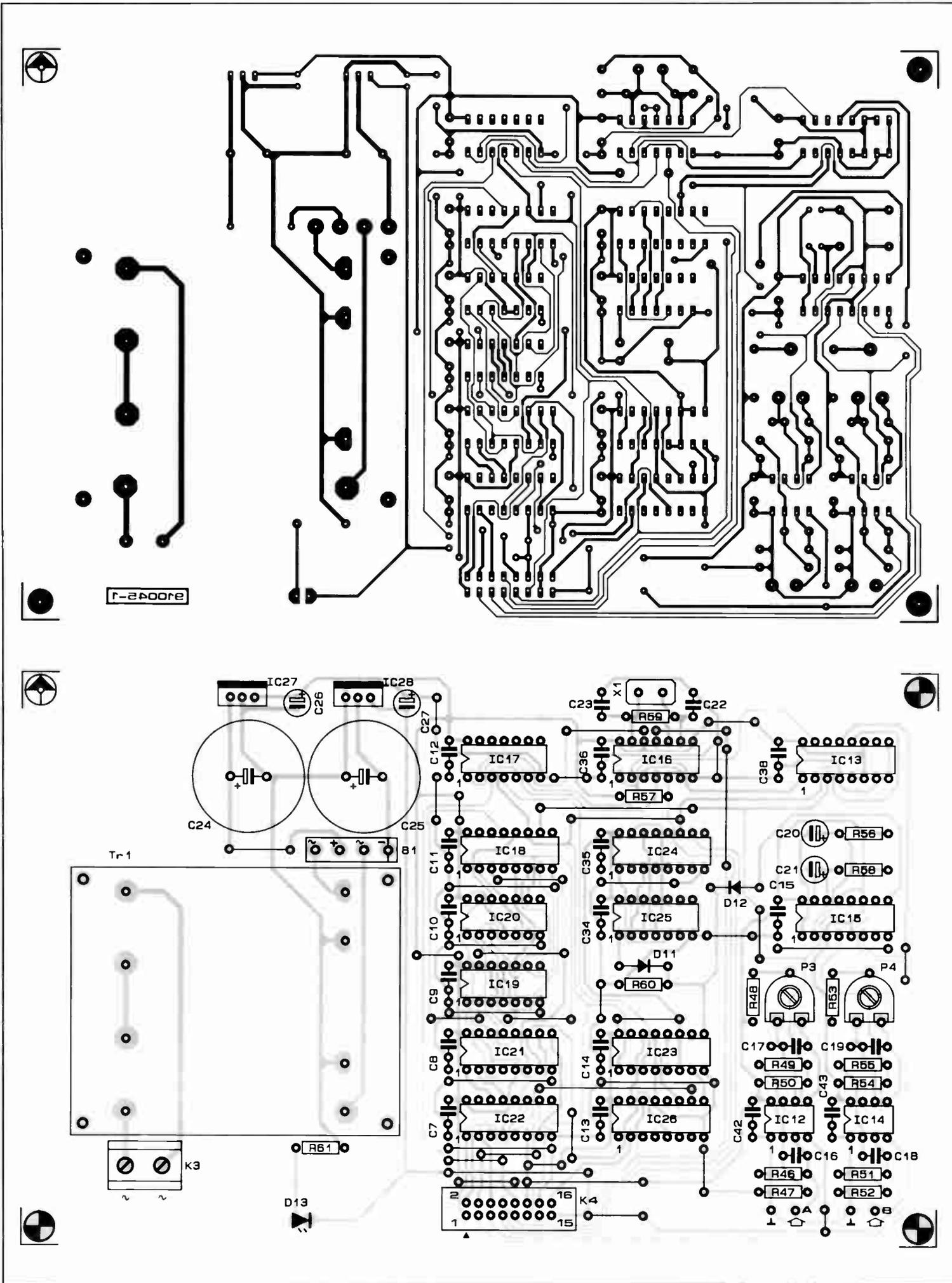


Fig. 7. Printed-circuit mother board.

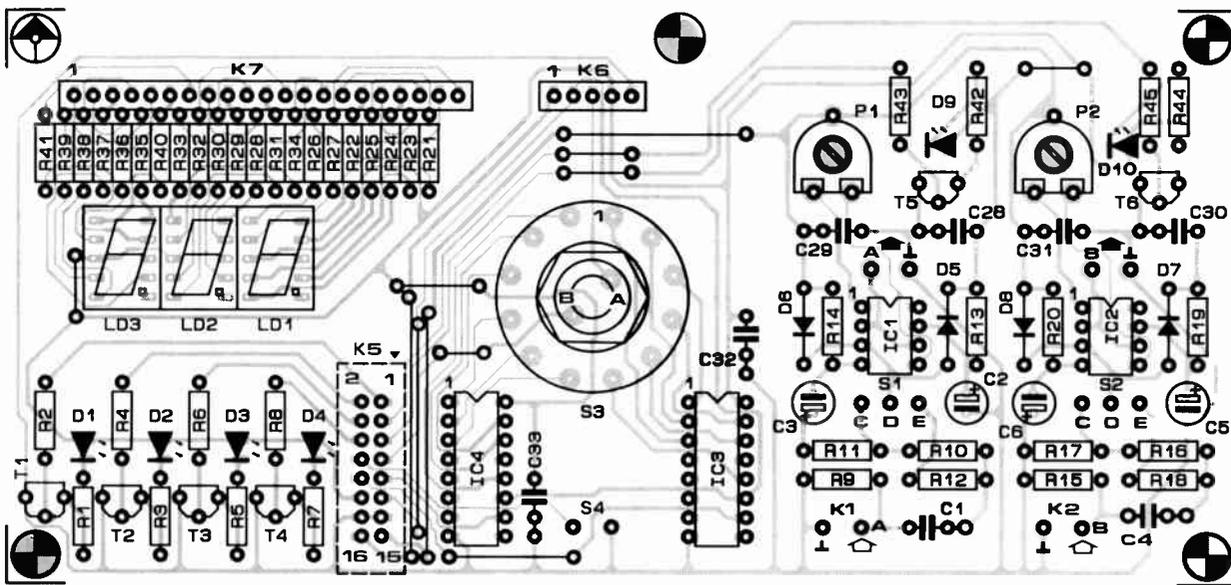
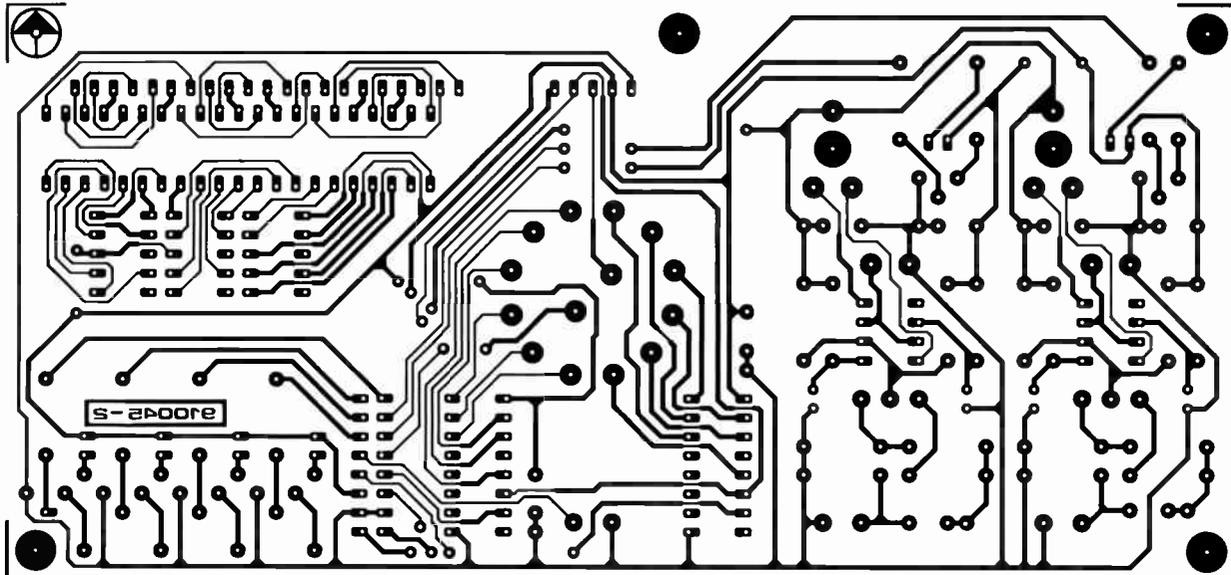


Fig. 8. Printed-circuit board for the displays, input stages, and selector switches.

Elektor Electronics	
110V ~ 60 Hz	
No. 910045	
F = 100mAT	

Elektor Electronics	
240V ~ 50 Hz	
No. 910045	
F = 100mAT	

Fig. 9. Suggested labels for the rear panel of the digital phase meter.

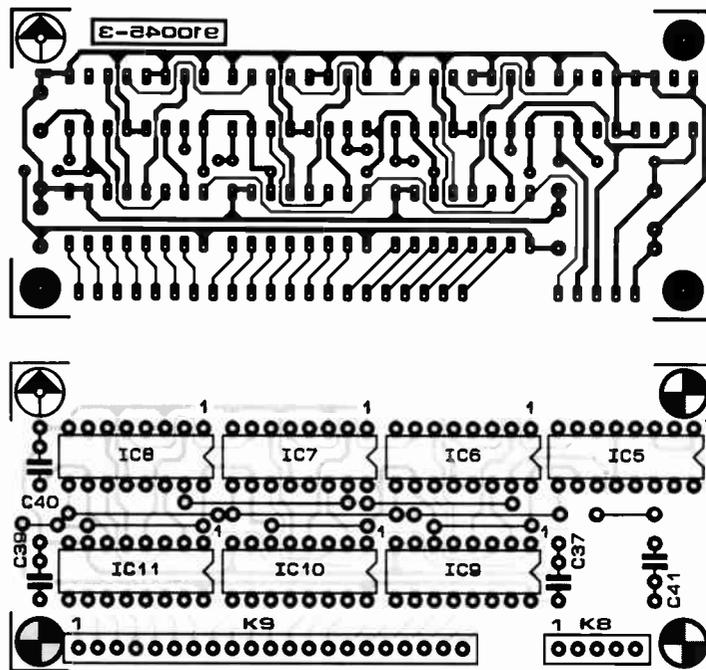


Fig. 10 Printed-circuit board for the logic circuits for the LED displays.

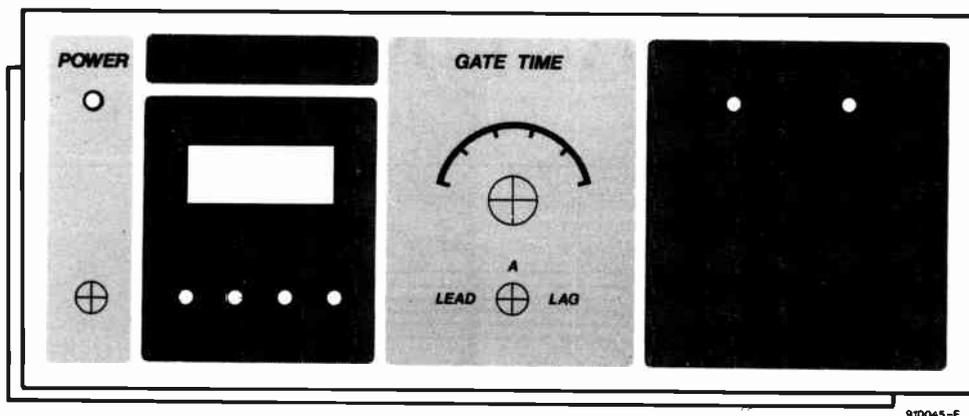


Fig. 11. The front panel foil for the digital phase meter is available through our Readers Services.

As mentioned before, the more periods are used, the more accurate the measurement. The counter in error detector IC<sub>18</sub> counts the number of periods between the onset of the measurement and the generated latch pulse. Four AND gates decode the result at 360, 180, 90 and 36 periods in one measurement cycle; these counts correspond to errors of 0.5°, 1°, 2°, and 5° respectively. Depending on the number of counted periods, one or more LEDs light; when they all light, the error is negligibly small.

Figure 5 shows the circuit of the displays, the indicators, the input stages and the stage for selecting the measurement duration. The indicator LEDs are driven by transistors: the control lines are connected to relevant points on the mother board via K<sub>5</sub>.

The input impedance is about 1 MΩ. Large input signals may be attenuated by 20 dB (S<sub>1</sub> and S<sub>2</sub>). All input signals are buffered by Type CA3140 opamps before they are applied to the comparator on the mother board. The inputs of these buffers are protected against overvoltage by diodes. Presets P<sub>1</sub> and P<sub>2</sub> serve to minimize the offset at the outputs of the opamps.

Circuits IC<sub>3</sub> and IC<sub>4</sub> are programmable 2<sup>n</sup> dividers. IC<sub>3</sub> counts the clock pulses passed by AND gate IC<sub>17a</sub>, that is, the pulses that indicate how long the output of XOR gate IC<sub>16b</sub> has been high. The number of these

pulses depends entirely on the phase shift between the two input signals. IC<sub>4</sub> is the reference counter that receives clock pulses continually.

The scaling factor is set with S<sub>3</sub>; it enables the user to select a measurement time that is most suitable for the frequency of the input signal. The error indicators on the display show whether the correct time has been selected.

Figure 6 shows the circuit contained on the third PCB: the seven ICs form the display counter and interface for the LED displays.

The clock pulses to be counted are applied to cascaded counters IC<sub>5</sub>–IC<sub>8</sub> via pin 3 of K<sub>8</sub>.

As soon as the latch signal is active, the counter state is stored in display drivers IC<sub>9</sub>–IC<sub>11</sub>. The displays, connected with this part of the circuit via K<sub>9</sub>, light to show the correct value measured.

The facilities of setting a pre-determined value and choosing up- or down-counting in the Type 4510 ICs are not used.

At the reset command at pin 2 of K<sub>3</sub> the counters are returned to zero and a new measurement cycle can be started. The previous measurement value is retained on the displays because the display drivers are not reset. The next measurement is thus carried out while the displays show the previous result.

## Construction

The three PCBs are shown in Fig. 7, 8, and 10. Their population is straightforward, but it is best to begin with boards 2 and 3. Note that the box header on board 2 must be soldered at the track side. Connectors K<sub>8</sub> and K<sub>9</sub> on board 3 may be replaced by right-angle print headers. As a bonus, such headers would ensure a firm mechanical link between boards 2 and 3. In any case, the boards are provided with holes to enable corner braces to be used for strong mechanical interlinking.

Mount the LED displays on board 2 about 1 cm (3/8 in) above the board with the aid of wire-

wrap IC sockets.

Connect switches S<sub>1</sub>, S<sub>2</sub>, and S<sub>4</sub>, to the board with short lengths of wire; fit S<sub>3</sub> directly to the board.

Cut the terminal wires of D<sub>1</sub>–D<sub>4</sub>, and D<sub>9</sub> and D<sub>10</sub> to about 2 cm (13/16 in): this will ensure that they will be located exactly behind the windows in the front panel.

Fit soldering pins at A and B and adjacent earth points at the track side of board 2.

The power-on indicator, D<sub>13</sub>, is best fitted to the front panel with the aid of an LED clip or superglue.

Fit board 2 on suitable spacers directly behind the front panel. Just prior to tightening the screws, connect the input sockets to the board via short wires. Next, screw the three toggle switches to the front panel.

Finally, mount board 3 at right angles to the track side of board 2 as shown in the photograph in Fig. 12.

Mount the mother board on the bottom plate of the enclosure, after which all necessary electrical connections to the other boards, the power-on LED, and on-off switch to mains entry plug can be made.

Finally, interlink points A and B, and the associated earthing points, on the mother board and board 2 by single screened audio cable.

## TECHNICAL DATA

Measuring range	10 Hz – 20 kHz
Reading	0–360°
Input sensitivity	6 mV peak
Max. input voltage	100 V peak
Attenuation	0 dB or 20 dB
Measurement time	0.3–10 s
Input impedance	1.1 MΩ
Measuring error	≥0.5°

## Calibration and use

Calibration of the phase meter is confined to adjusting the four presets.

Short-circuit inputs A and B and adjust P<sub>1</sub> and P<sub>2</sub> for zero output of IC<sub>1</sub> and IC<sub>2</sub>.

Remove the short-circuit from the inputs and apply a sinusoidal a.f. signal at a level of about 10 mV to the inputs. Adjust P<sub>3</sub> until comparator IC<sub>12</sub> toggles exactly at the zero crossing point: check this on an oscilloscope.

Finally, adjust P<sub>4</sub> until the display shows a phase difference of 0°.

Start measuring a phase shift by applying the two signals to the inputs and turning S<sub>3</sub> (gate time) fully clockwise. Then turn the switch anti-clockwise step by step (when the accuracy increases). When the indicator marking a measuring error of 0.5° lights, the optimum position for this measurement has been reached. Since the measurement period increases all the time, it may take a few seconds at low frequencies before the indicator lights. That is, however, the price to be paid for accuracy at low signal frequencies. ■



Fig. 12. This photograph of the completed digital phase meter shows how the PCB of Fig. 9 is fitted to the PCB in Fig. 8.

# THE QTC LOOP ANTENNA

The quest for ever reduced sizes of efficient HF transmitting antennas is a compulsive exercise which one has great difficulty in dropping once 'bitten by the bug'. The antenna described here is a new challenge: a directional, compact, table-top loop design with proven excellent performance in the 80-m band.

Richard Q. Marris, G2BZQ

THE lower the HF frequency, the more challenging the idea of being able to use a small antenna. For instance, in the 80 m (3.5 MHz) amateur band, a dipole antenna would be around 42 m long. Many do not have the real estate to accommodate such a dipole, apart from possible planning permission difficulties, and difficulties with leases or neighbours. For apartment dwellers an outside antenna is invariably impossible. For non-amateur applications there are various requirements for discrete and easily portable antennas. As a result, a compact table-top antenna as described here becomes most attractive for many applications.

## Small and efficient

Over the years, a number of small table-top HF antennas have been designed, built and air-tested. By far the best has been the spiral loop (Ref. 1) to cover the 3.5 to 3.8 MHz amateur band. This was a very simple 23-inch (approx. 59 cm) diameter octagonal experimental model which I used over the last year with a 7-watt CW transmitter.

It has been useful and fortunate during my experiments that there has been a regular daily 2-way schedule, between 05.00/05.30 a.m. on  $3,560 \pm 5$  kHz, with a friend in Stuttgart, Germany. He has entered into the spirit of these experiments, which have proved to be essential, though, of course, much longer distances have been achieved. His transmitter has a power output of about 100 watts feeding an outdoor dipole. As against this, I have been using a spiral loop on a table alongside my low-power transmitter. Strangely enough, looking back over the months, there has been little difference in signal strength reports either way.

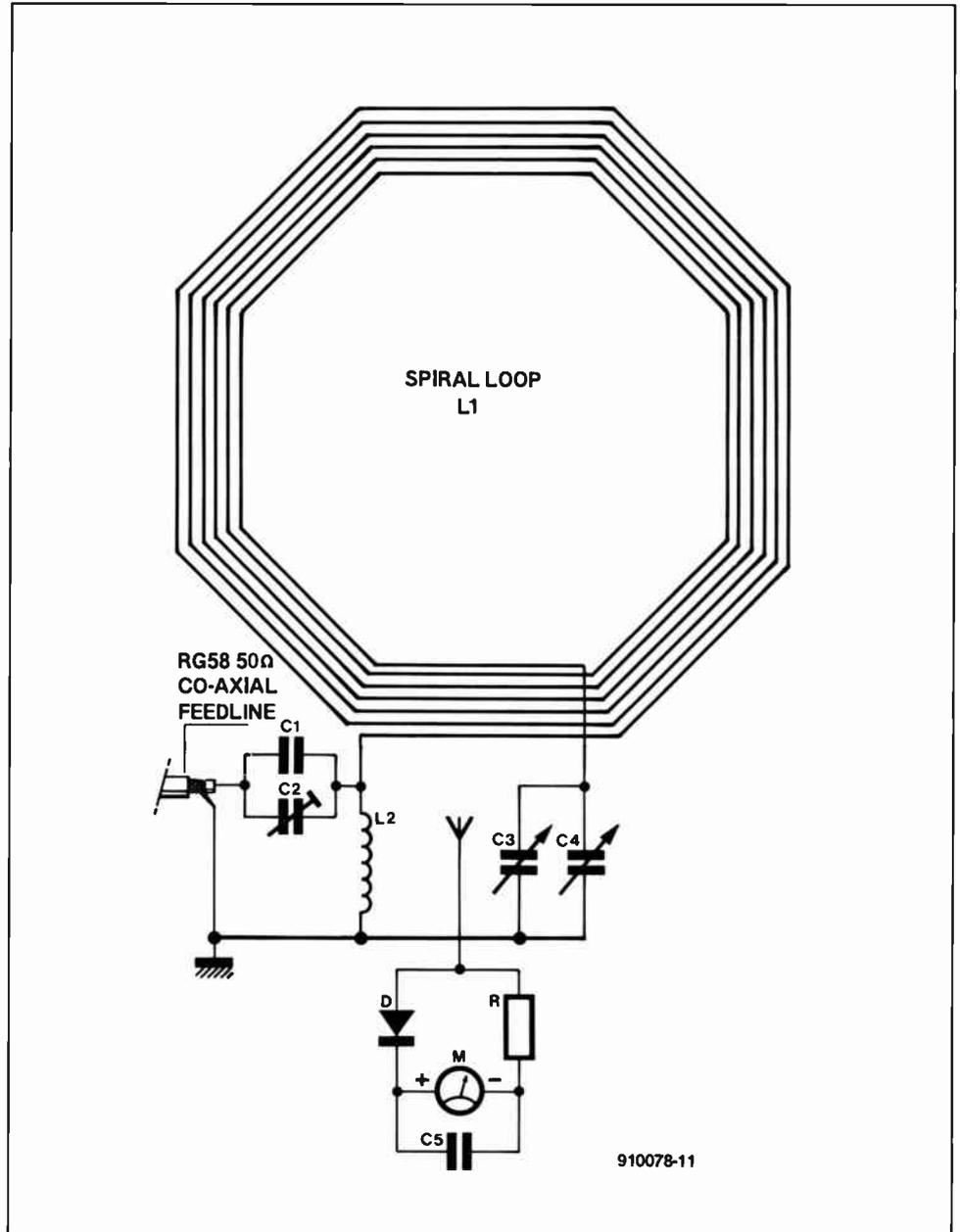


Fig. 1. Electrical circuit of the loop antenna and the associated relative field strength

The tiny amount of textbook information (Ref. 2) available on spiral loops is concerned with direction finding (DF) and not transmission. It is stated that the reception advantages of the spiral loop over a standard box loop, with the turns side-by-side, are mainly greater sensitivity/gain, and a narrower directional polar diagram. Based on experience with the 23-inch diameter spiral loop, and seeking greater efficiency and transmission range, further experiments produced the much more sophisticated and efficient QTC spiral loop. Just in case you do not remember your Q-codes: QTC means "I have a message for you".

## The message

is that the new loop antenna has a 30-inch (approx. 76 cm) octagonal configuration,

which, although giving as much as 50% increase in loop area, still fits into the table top space available.

The circuit (Fig. 1) shows a  $5\frac{1}{8}$  turns loop, L1, plus impedance matching coil, L2. The inductors are resonated by variable capacitors C3 and C4. C3 sets the band segment to be used, and C4 is a small bandspread tuner.

A 48-inch (approx. 122 cm) length of RG58 coax cable is fed via C1 and C2, in parallel, to the junction of L1 and L2. Capacitor C2 is a preset variable type providing a fine coupling adjustment.

Maximum radiation is on the outer turns of L1 ( $H_i-I$ ), and minimum radiation on the inner turns ( $H_i-E$ ). The radiation pattern (polar diagram) is shown in Fig. 2. It will be realized that the large lobe has to be pointed towards the station to be contacted. In the

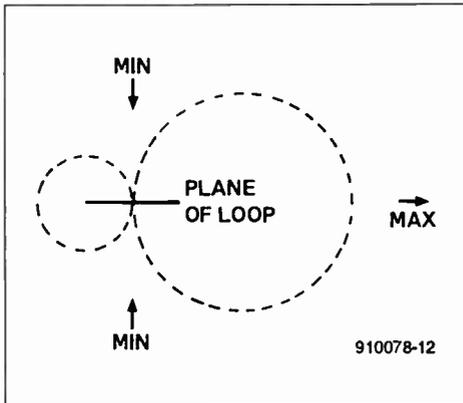


Fig. 2. Theoretical polar radiation pattern of the QTC loop.

author's shack the loop usually stands on a small turntable for simple manual rotation.

The antenna has a built-in tuning meter seen at the bottom of the circuit. This is basically a RF probe of which the sensitivity is reduced to an absolute minimum, so that a 'sample' of the transmitted signal can be taken from the outer turn of L1. The sensitivity of the probe is controlled by the value of resistor R, as well as by the length and position of the mini-antenna.

All components are neatly located in a plastic control box as shown in Figs. 3 and 4. The RF meter assembly is mounted in a Terry clip on top of the box, with the diode, the resistor and capacitor C5 wired behind the meter. This method was adopted to enable the tuning assembly to be used on other experimental antenna models.

The complete loop assembly is shown in Fig. 4. When designing such a loop, it is essential that metal parts be avoided, which means that you have to use wood and plastic construction throughout.

## Construction

As shown in Figs. 1 and 4, the loop frame consists of eight 'spokes'. These are made of four lengths of moulded hardwood, each 30 inch long,  $\frac{5}{8}$ -inch wide and  $\frac{1}{4}$ -inch thick (approx.  $76.2 \times 1.6 \times 0.6$  cm). A 2BA (5 mm) clearance hole is drilled in the centre of each spoke, and after an application of glue, the spokes are clamped together with a 2BA bolt, overlapping in the order illustrated. The whole is given a polyurethane varnish. A 6-way 2-amp polythene terminal block is screwed to the end of each spoke. These provide the necessary spacing and insulation of the wire turns.

A  $23 \times 0.8 \times 0.8$ -inch (approx.  $58.4 \times 2 \times 2$ -cm) vertical wooden support is glued and bracketed to a suitable wooden base, the whole being teak wood stained. The loop frame is then glued and bolted to the top of the vertical support.

The loop winding, L1, uses PVC-covered stranded 7/0.2 mm wire with an outside diameter of 1.2 mm and an electrical rating of 1 kV/1.5 A. After loosening all grub screws in the terminal blocks, the wire is threaded through, turn by turn, for  $5\frac{1}{8}$  turns starting at the outer left-hand lower frame spoke, and threading through all blocks in a


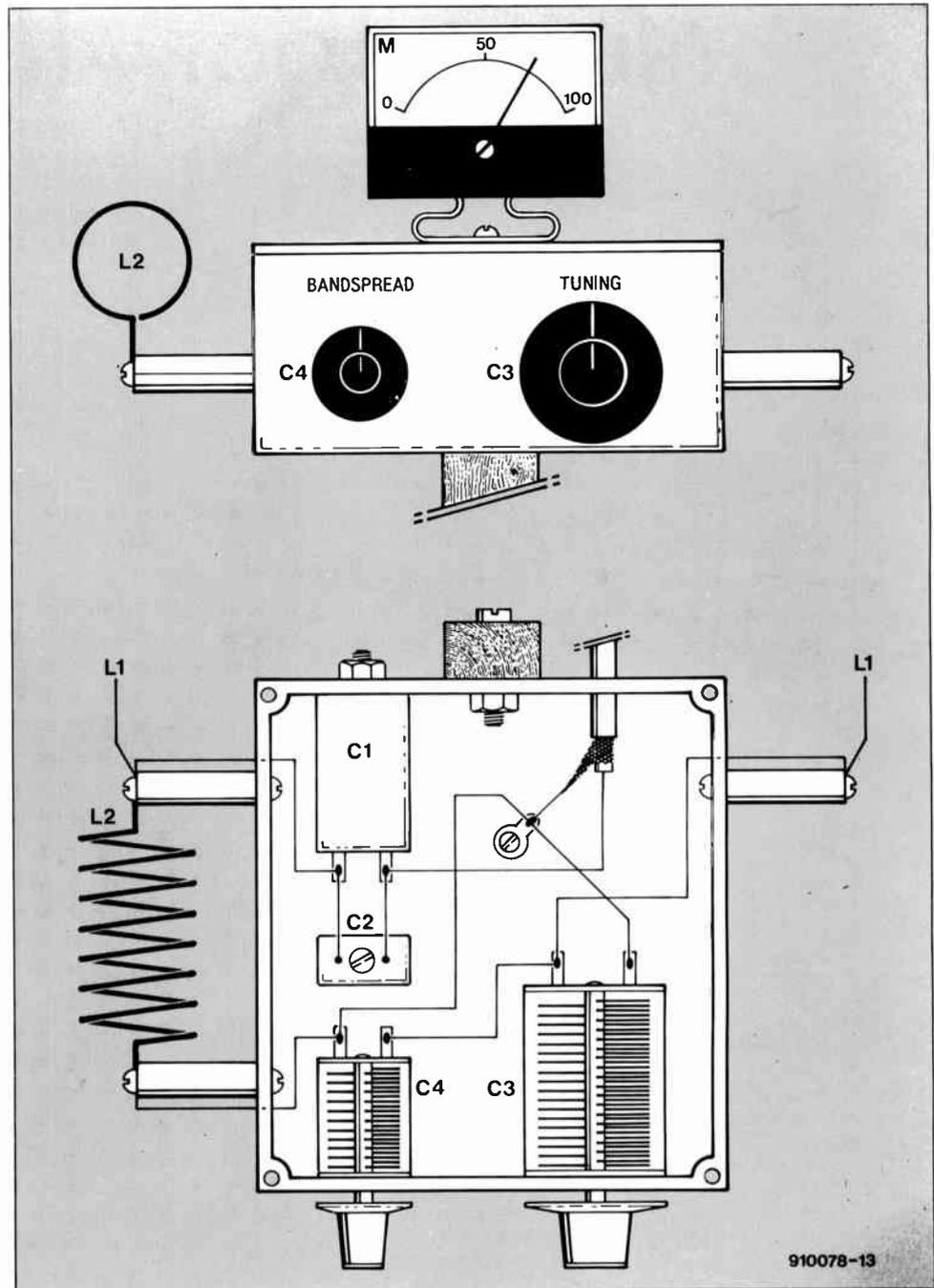


Fig. 3. Mechanical outline of the antenna tuning unit and the field strength indicator.
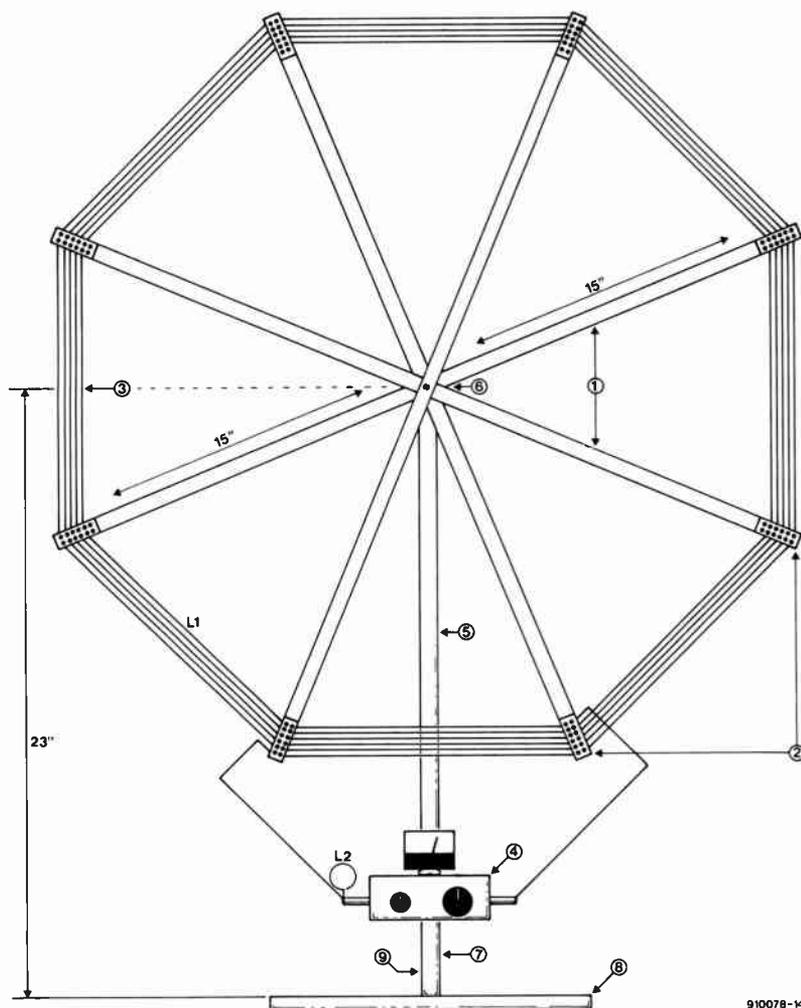
## COMPONENTS LIST

- C1 = 3750 pF 500V silver-mica capacitor.
- C2 = 100 pF preset capacitor (Jackson C803).
- C3 = 75 pF variable capacitor (Jackson C809), plus knob.
- C4 = 12.7 pF variable capacitor (Jackson C16), plus knob.
- C5 = 22 nF mica capacitor.
- M = 250  $\mu$ A f.s.d. 40  $\times$  40 mm moving coil meter (Maplin LB808).
- D = HF silicon diode.
- R = 1 k $\Omega$  resistor (see text).
- L1 =  $5\frac{1}{8}$  turns of PVC covered stranded 7/0.2 mm wire. Outside diameter: 1.2 mm, 1 kV/1.5 A rating (see text).
- L2 = 13 turns 16SWG tinned wire, 1 inch internal diameter (see text).
- Feedline = 48 inch RG58 coaxial cable, plus plug to suit transmitter.
- Box = ABS box type MB3, 118  $\times$  96  $\times$  45 mm. Maplin ref. LH22.
- Terminal blocks = qty. 4 12-way 2 amp terminal block. Maplin ref. FE78.
- Spacers = qty. 3 insulated spacer type M3, 30 mm long, Maplin ref. FS40T.
- Spokes = qty. 4 8-foot lengths of  $\frac{5}{8} \times \frac{1}{4}$  inch moulded hardwood (DIY store).
- Vertical support =  $23 \times 0.8 \times 0.8$  inch wood (DIY store).
- Wood base =  $12 \times 8 \times 0.5$  inch plywood or similar.
- $\frac{1}{2}$  inch steel support bracket.



910078-14

1. 4 lengths moulded hardwood 30"  $\times$  5/8"  $\times$  1/4". Varnished. 2BA holes drilled in the centre. Glued and bolted together.
  2. 8 off 6-way 2-amp polythene terminal blocks used as insulated wire spacers.
  3. 5 1/2 turns of PVC stranded wire (for specs see components list).
  4. See Fig. 3.
  5. Wood vertical support 23"  $\times$  0.8"  $\times$  0.8", wood stained.
  6. 2"  $\times$  2BA bolt.
  7. Box front vertical support, 4 1/2"  $\times$  1/2"  $\times$  3/4", wood stained.
  8. Wood base 12"  $\times$  8"  $\times$  1/2" (or similar), wood stained.
  9. 2 1/2 steel support bracket behind wood vertical support.
  10. Drilled and secured with glue and c/s wood screws.
- Note: " = inch = 2.54 cm.

Fig. 4. The construction of the antenna is based on commonly available parts and materials. The 'spokes' are bolted together in the centre.

reducing anti-clockwise spiral. The loop is terminated at the inner of the lower right-hand spoke, as shown in Fig. 4. Wire tails are left at the loop ends for cutting and connecting later. After tightening the loop turns, the insert screws in the terminal blocks are tightened sufficiently to keep the turns straight.

After fitting the variable capacitors and insulating pillars in the box (Fig. 3), the box is bolted to the main vertical support. An extra, smaller, vertical wood member secures the box front to the wood base with screws and glue. The meter assembly is secured to the front lid of the box lid with the aid of a large plastic-coated Terry clip. The RG58 coaxial feedline enters the box at the rear (Fig. 3), and is cleated down to the vertical support and along the wood.

Inductor L2 is soldered to tags on the two left-hand insulated pillars. It consists of

13 turns of 16SWG (16AWG, approx. 0.6 mm dia.) tinned copper wire wound to 1 inch (2.54 cm) diameter. The turns are then spaced to about 1.5 times the wire thickness. The whole loop assembly is now wired as shown in Figs. 1, 3 and 4.

## Testing and operation

Initial tests are made with a receiver. On the prototype with the bandspread, C4, at mid capacity, it was found that by rotating C3 the frequency range was 2,500 kHz to 4,500 kHz, which adequately covers the 80-m band (3,500 to 3,800 kHz), with some overlap. In the USA and elsewhere, the 80-m band is extended to 4,000 kHz. Resonance is indicated by a peak of noise and signal strength in the receiver. The radiation pattern can be checked on a selected signal by

rotating the loop for maximum signal strength. From Fig. 2 it will be seen that this coincides with the large lobe. Further rotation of the loop through 360 degrees gives a radiation pattern as shown.

In practice, C4 is set to minimum capacitance, and C3 is tuned to start of the selected band segment. For instance, if the required operating segment is 3,500 to 3,800 kHz, C3 is set to about 3,600 kHz (with C4 at minimum capacitance). Bandspread control C4 is then used to tune the loop, giving fine tuning over 3,500 to 3,600 kHz, and so on.

The transmitter adjustment is as follows:

1. Connect the transmitter to a 50- $\Omega$  dummy load. Set the transmitter to the selected frequency and adjust the P.A. for optimum loading.
2. Remove the dummy load and substitute the loop.
3. Resonate C4 to the transmitter frequency, and peak the coupling preset adjustment, C1.
4. It should be possible to use the transmitter at  $\pm 20$  kHz of the setting up frequency without retuning the loop with C4. Minor adjustments of C4 will easily retune the loop outside this bandwidth, as required.

Proceed with the adjustment of the tuning meter. The mini-antenna consists of a few turns of stiff wire wound around a pencil. Remove the wire from the pencil, and position the end of it directly under the bottom turn of L1. The mini antenna is manipulated up and down so that the meter reads about 3/4 full-scale when the transmitter is correctly loaded. When retuning the transmitter during operation, the meter should always peak around this point, provided the transmitter power is unaltered. Note, however, that the sensitivity of the meter depends also on the value of resistor R and the transmitter power. The value shown, 1 k $\Omega$ , is satisfactory for a transmitter power of about 5 to 10 watts. For higher or lower power transmitters, the value of R is changed experimentally.

When operating the antenna it should be kept a loop diameter away from walls, pipes and electrical wiring. It will be noticed that due to the loop directivity the received level of interference is well down on a normal antenna. Best results will be obtained when the large radiation lobe is pointed directly at the station being contacted.

Finally, note that the loop antenna is intended as a low-power device for indoor use. In the interest of safety, a transmitter power of 20 watts should not be exceeded. No doubt the design could be re-engineered for higher power and outdoor use. ■

## References:

1. "The Miser's T/R loop antenna" by R.Q. Marris, *Elektronika* November 1990.
2. The Admiralty handbook of Wireless Telegraphy, Volume 2, 1938.

## For further reading:

- The ARRL Antenna Book, 14th edition.
- Antennas (2nd edition), 1988, by John D. Kraus (McGraw-Hill).

# INTERMEDIATE PROJECT

**A series of projects for the not-so-experienced constructor. Although each article will describe in detail the operation, use, construction and, where relevant, the underlying theory of the project, constructors will, none the less, require an elementary knowledge of electronic engineering. Each project in the series will be based on inexpensive and commonly available parts.**

## LIGHT TRANSMITTER/RECEIVER

**This month we present an experimental circuit to demonstrate that visible light can be modulated and used as a carrier to convey information. Depending on the power of the bulb you use, and the optics for the transmitter and the receiver, this low-cost communication system will carry speech signals over distances of tens to hundreds of metres.**

**T. Giffard**

**I**N principle, the intensity of a light beam from an electrical source, such as a bulb, can be used as a carrier to convey an audio signal from one point to another. This type of amplitude modulation (AM) can be achieved by using the audio signal to vary the voltage applied to the bulb. The light transceiver described here is intended as an introduction to wireless communication using amplitude modulation. The circuits have been kept simple and can be assembled

and put to use in single evening or a rainy afternoon. When used for an experiment rather than a fixed communication link, the transceiver can be even simpler than shown here because existing amplifiers may be used.

Compared to, say, an infra-red emitter there are certain restrictions to the use of common low-voltage bulbs as light sources for an AM-based communication link, and the modulation will not be perfect. Still, the

quality of the system will be good enough for a reliable voice link.

### On modulation and filaments

Modulating the light intensity of a bulb is not so difficult. However, the relation between the intensity and the filament voltage is not quite as linear as we would like. In practice, the best results are obtained with low-voltage bulbs that have a thin, straight filament. These bulbs, which are used in bicycle rear lights, have a relatively rapid response to filament voltage variations, and are therefore capable of 'following' a speech or music signal.

The response of a bulb to sine-wave modulation can be significantly improved by applying a direct voltage to the filament, and superimposing the sine-wave. In practice, the best results are obtained with the fixed voltage set such that the bulb lights at half the nominal intensity. This also sets the maximum value of the applied alternating voltage, whose peak value may not exceed the direct voltage. When the voltages are equal, the modulation depth is 100%. In the absence of an alternating voltage component, the modulation depth is 0%.

### The light transmitter

The circuit of the light transmitter is shown at the left in Fig. 1. It supplies the light source, bulb La1, with a direct voltage as well



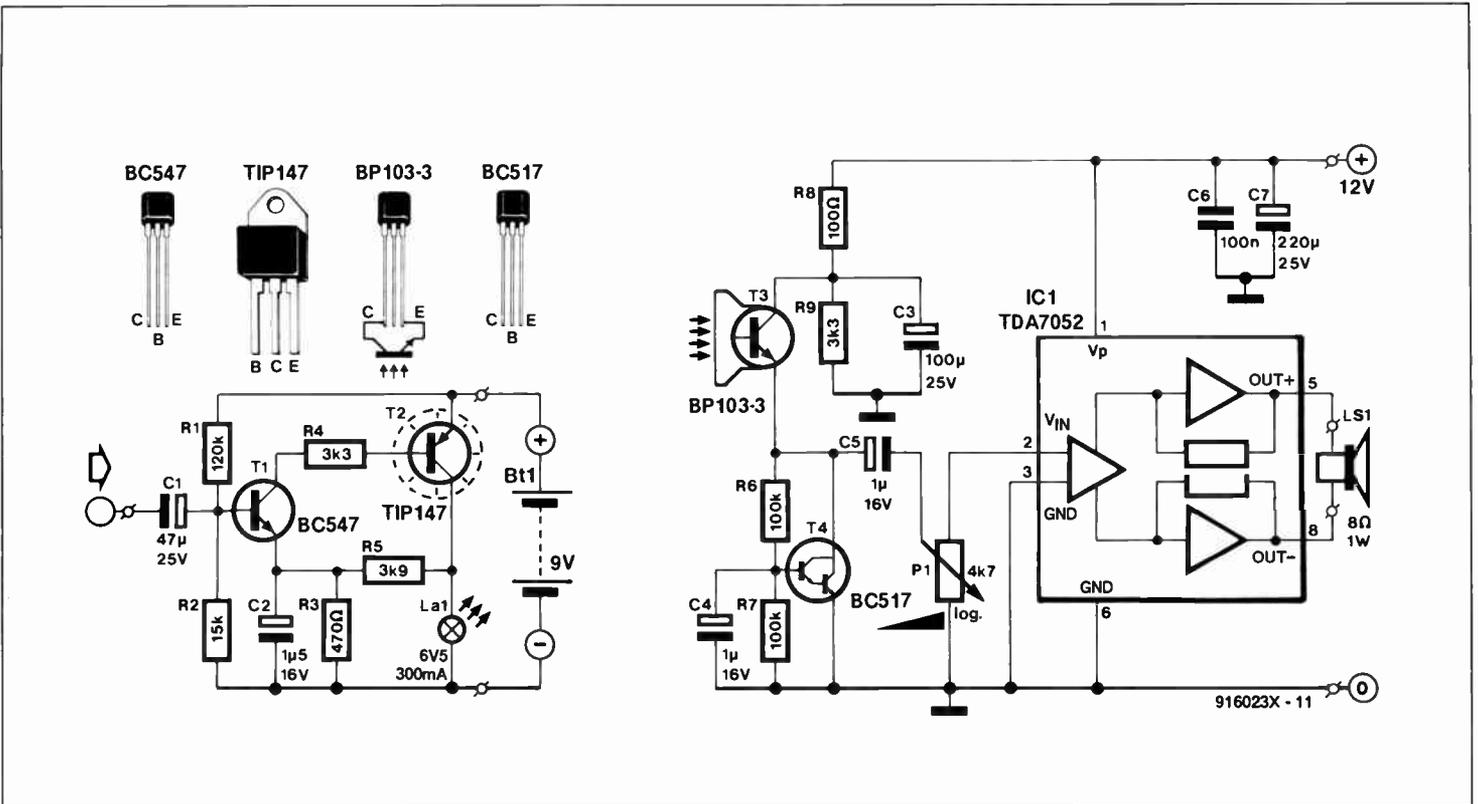


Fig. 1. Circuit diagram of the light transmitter (left) and the associated receiver (right). The IC-based audio amplifier in the receiver, a TDA7052, is optional and may be replaced by any other amplifier you may have available.

as with the modulation signal. The bulb is connected in the collector line of a medium-power transistor, T2, which functions as an amplifier. When there is no input signal, the collector of T2 is at about half the supply voltage. An audio input signal applied to the base of T2 causes the collector voltage to

swing between 0 V and the supply voltage. This ensures that La1 is supplied with the optimum voltage for amplitude modulation.

Transistor T1 raises the audio input signal and at the same time keeps the quiescent voltage across La1 at about half the supply voltage. The transistor monitors the collector

voltage of T2 via resistor R5, and controls the base voltage of T2 accordingly. A decoupling capacitor, C2, prevents T1 acting on the modulation voltage at the collector of T2. The voltage control is effective only when the average collector voltage of T2 is no longer correct. The operation of this type of feed-

### COMPONENTS LIST

<b>Resistors:</b>	
1 120k $\Omega$	R1
1 15k $\Omega$	R2
1 470 $\Omega$	R3
2 3k $\Omega$ 3	R4;R9
1 3k $\Omega$ 9	R5
2 100k $\Omega$	R6;R7
1 100 $\Omega$	R8
1 4k $\Omega$ 77 log. potentiometer	P1
<b>Capacitors:</b>	
1 47 $\mu$ F 25V radial	C1
1 1 $\mu$ F5 16V radial	C2
1 100 $\mu$ F 25V radial	C3
2 1 $\mu$ F 16V radial	C4;C5
1 100nF	C6
1 220 $\mu$ F 25V radial	C7
<b>Semiconductors:</b>	
1 BC547	T1
1 TIP147	T2
1 BP103-3	T3
1 BC517	T4
1 TDA7052	IC1
<b>Miscellaneous:</b>	
1 8 $\Omega$ 1W loudspeaker	LS1
1 6.5V 0.3A bulb	La1
1 Heat-sink for T2	
2 Printed-circuit board	UPBS-1

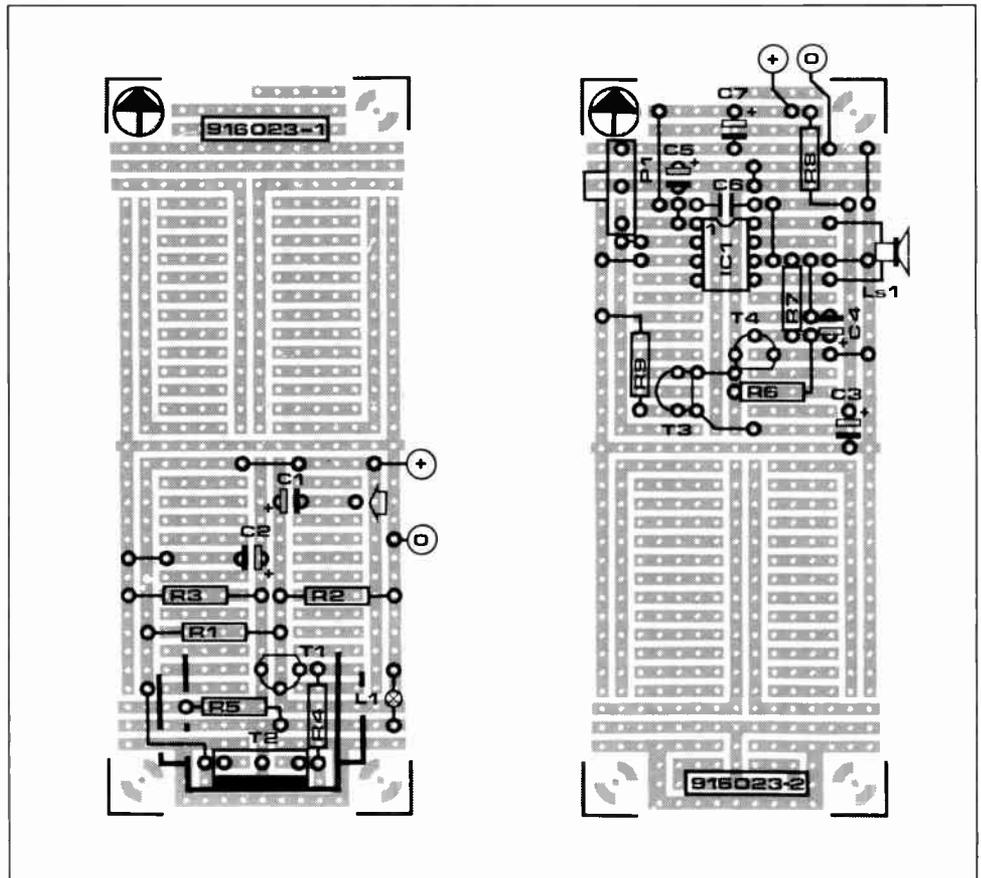


Fig. 2. Component mounting plans of the transmitter (left) and the receiver (right). Both are built on ready-made prototyping boards (see the components list).

back is fairly simple. Assuming that the collector voltage of T2 drops, R5 supplies a lower voltage at the emitter of T1. Since the base voltage of T1 is fixed with the aid of a voltage divider, R1-R2, the transistor starts to draw more collector current, resulting in more current fed into the base of T2. Consequently, the collector current of T2 rises, so that the collector voltage rises also. In this way the initial voltage drop is counteracted and the bulb voltage held constant at about 4.5 V.

## The light receiver

The main component in the circuit of the light receiver (shown at the right in Fig. 1) is a photo transistor, T3. The collector current of this transistor is a function of the intensity of the light incident on the device. If the incident light is produced by the light transmitter, the emitter voltage of T3 is a copy of the modulation signal applied to the transmitter. The demodulated signal is fed to a small a.f. amplifier, IC1, via coupling capacitor C5 and volume control P1. The a.f. amplifier, a TDA7052, has a voltage gain of about 100.

Returning to the phototransistor, the emitter potential is held constant by a volt-

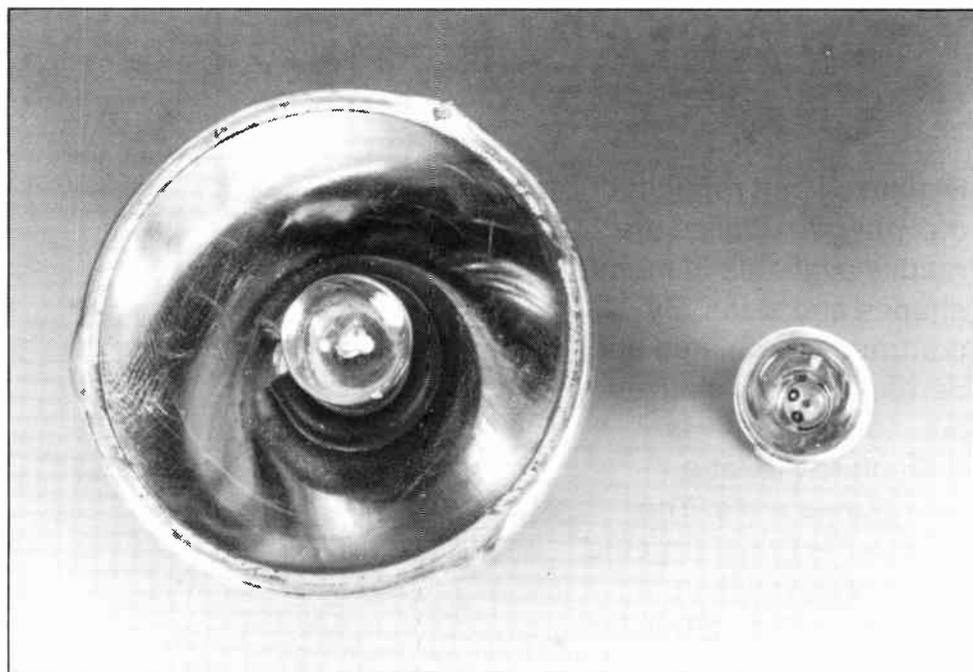


Fig. 4. The transmitter uses a plastic reflector from a pocket torch, while the phototransistor in the receiver is fitted in a reflector of a type normally used for infra-red emitters.

age source based on T4. Assuming that the emitter voltage of T3 rises, the base current of T4 rises via resistor R6. Consequently, the collector current of T4 rises, so that the collector voltage drops. This keeps the emitter voltage of the photodiode in check. Like C2 in the transmitter, C4 prevents the voltage stabilizer acting on the modulation signal, which changes much faster than the average emitter voltage of the photodiode.

## Construction and use

The transmitter and receiver circuits are so simple that they are easily constructed on prototyping boards as shown in Fig. 2. If you want to make a duplex system where each 'station' consists of a transmitter and a receiver, you will require two prototyping boards (order code UPBS-1). For a one-way light link, a single board may be cut in two to accommodate the transmitter and receiver circuit. The photographs in Fig. 3 show the transmitter and the receiver built on two prototyping boards.

There are several options for the construction of the optics. At the transmitter side, you may use a reflector from a torch (see Fig. 4). At the receiver side, a concave reflector is used of the type found on infra-red remote controls. In most cases, the BP103 phototransistor will fit in the opening for an infra-red LED. It will be clear that the distance covered by the system will depend on the size of the optics used. In general, the larger the diameter of the reflectors, the better (an example of the use of car headlight and a magnifying glass for a long-range infra-red communication system is given in Ref. 1). A few prototypes with different coverage were built in torches as shown in the introductory photograph.

You may also want to experiment with the wattage of the bulb used in the transmitter. Note, however, that relatively high bulb

powers require T2 to be fitted with a heat-sink.

The transmitter draws a relatively high current, and is best powered by a regulated supply or a rechargeable 9-V battery block. The receiver has a very modest power consumption, and can be supplied from a small mains adapter. In some cases, however, such an adapter may produce an unacceptable hum level in the receiver. Fortunately, the hum is simple to suppress by fitting larger supply decoupling capacitors in positions C3 and C7.

Finally, note that the bulb in the transmitter will emit visible as well as infra-red light. This allows you to use an infra-red sensitive phototransistor such as the BPW40 if the BP103 proves difficult to obtain. ■

## Reference:

1. "Long-range infra-red transceiver". *Elektronics* November 1987.

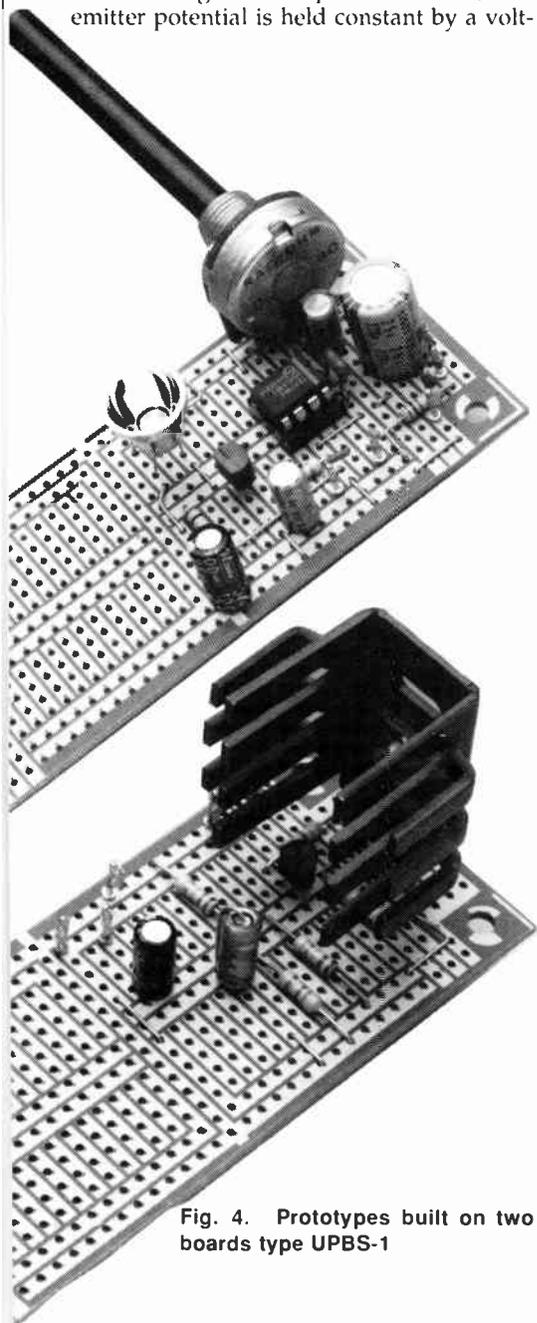


Fig. 4. Prototypes built on two boards type UPBS-1

## PREVIEW GLASS AUDIO

### Issue 1, 1991

- A line-level mixer for studio or field use
- Rebuilding tube amplifiers
- Tubes in Japan
- Improving Dynaco's FM-3
- *The Audio Glossary* reviewed
- *Saga of the Vacuum Tubes* reviewed

# VARIABLE A.C. POWER SUPPLY

Stabilized and regulated d.c. power supplies are readily available in many shapes and sizes. By contrast, a regulated and perhaps even stabilized a.c. power supply is difficult to find at a reasonable price. The adjustable transformer is in many cases the only alternative, but it, too, is pretty expensive. In this article we present a simple 25-V 1-A a.c. power supply that deserves a fixed place on any electronics workbench.



## L. Lemon

**A**N alternating voltage is much more difficult to stabilize than a direct voltage. In fact, there are two quantities that must be stabilized: the voltage proper (or its amplitude), and the frequency. Since it was intended to keep the present supply as simple as possible, frequency stabilization is not provided. The mains frequency is used here because it is fairly stable and suitable for most applications.

## Block diagram

The operating principle of the present supply is to stabilize an alternating voltage with the aid of an adjustable potential divider. As shown in the block diagram in Fig. 1, the potential divider is controlled electronically, and forms part of a regulation loop. A power transistor is used as an adjustable resistor in a diode bridge. The bridge is required because the transistor can handle direct current only. Unfortunately, it has two disadvantages: first, it introduces a voltage loss of two times the forward diode voltage; second, because of their threshold voltage, the diodes do not conduct around the zero crossing of the alternating voltage. As shown in the oscilloscope photograph in Fig. 2, the thresholds cause small flattened parts around the zero crossing of the output voltage. In amplifier terminology this effect is known as cross-over distortion. Fortunately, the effect is of little consequence here, and it can be tolerated bearing in mind that we set out to de-

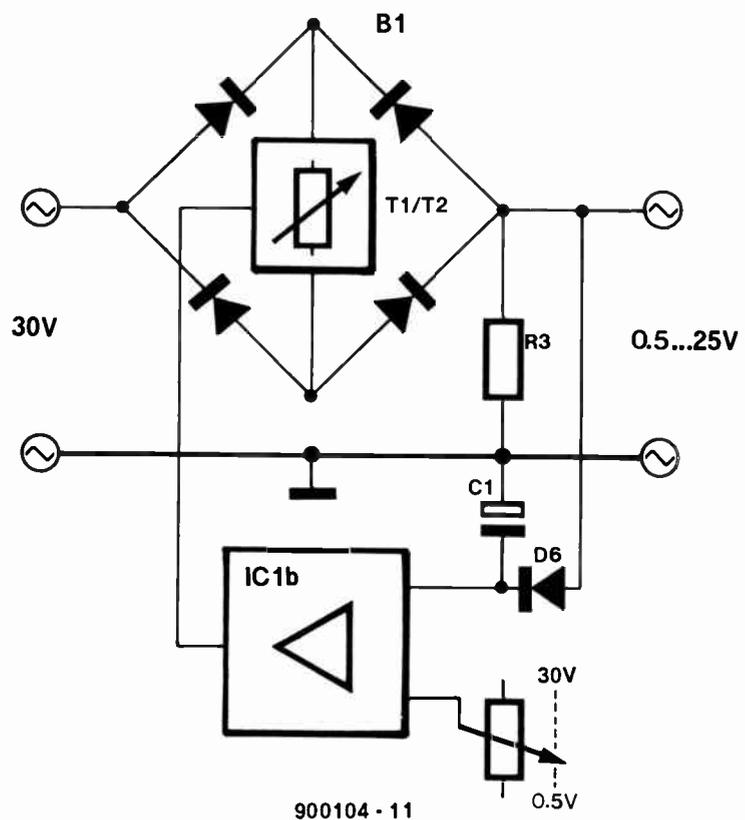


Fig. 1. The alternating voltage is stabilized by comparing the peak value with a preset voltage. The resulting error signal is used to control a variable resistor in a diode bridge.



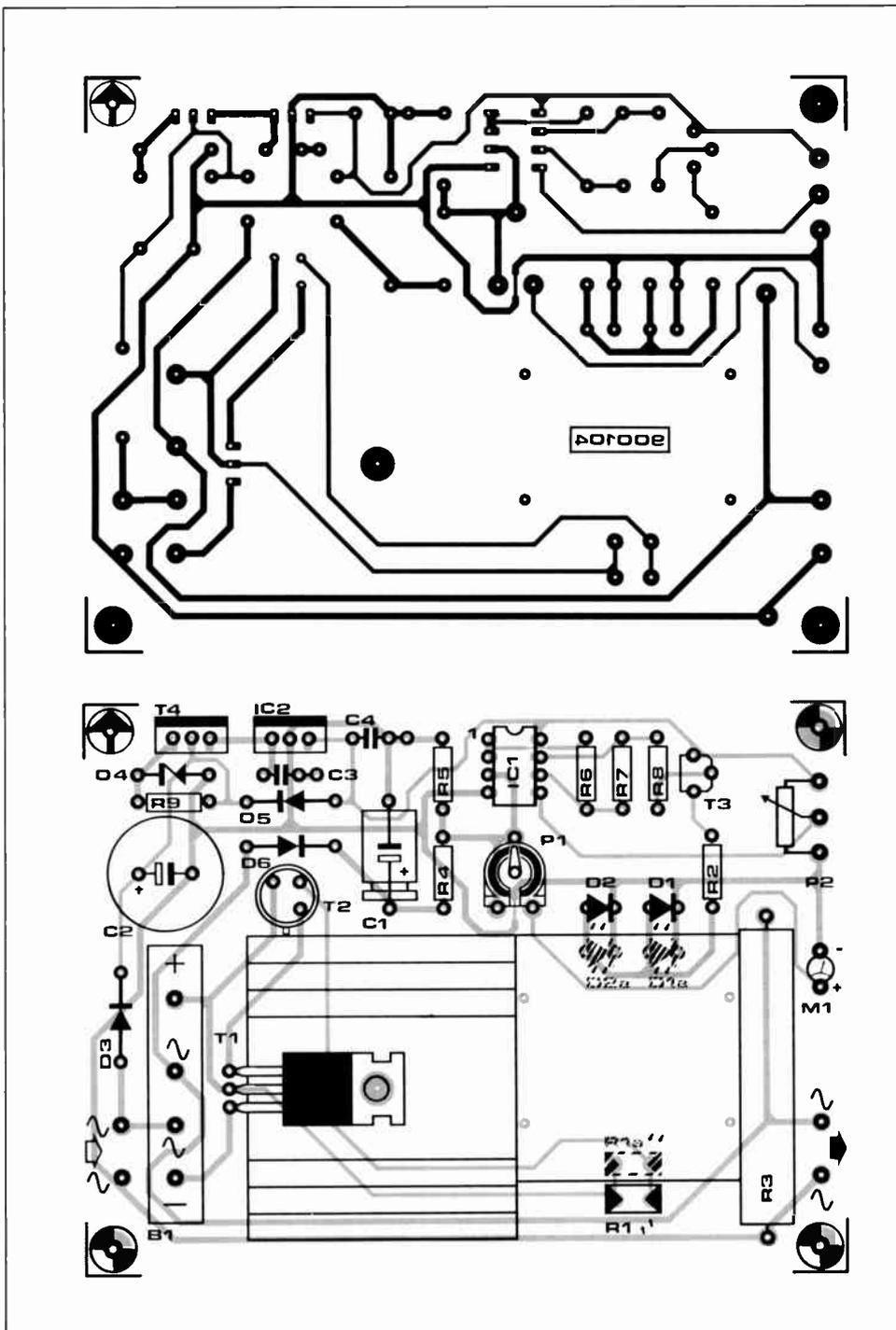


Fig. 4. Single-sided printed circuit board for the a.c. power supply.

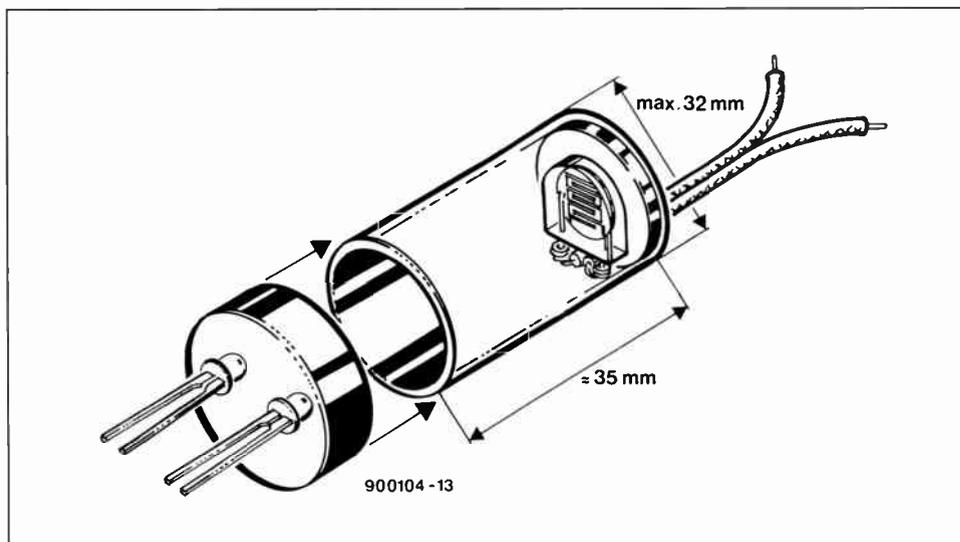


Fig. 5. Basic construction of the home-made optocoupler.

## COMPONENTS LIST

### Resistors:

1 LDR	R1
1 180Ω	R2
1 100Ω 10W	R3
1 47kΩ	R4
1 39kΩ	R5
2 100kΩ	R6;R7
1 22kΩ	R8
1 220Ω	R9
1 1MΩ preset H	P1
1 2kΩ 2 lin. potentiometer	P2

### Capacitors:

1 10μF 63V axial	C1
1 220μF 50V radial	C2
1 330nF	C3
1 10nF	C4

### Semiconductors:

2 red LED	D1;D2
3 1N4001	D3;D5;D6
1 33V 0.4W zener diode	D4
1 B80C3200/2200	B1
2 BD241	T1;T4
1 BC141	T2
1 BC550B	T3
1 TLC272	IC1
1 7812	IC2

### Miscellaneous:

1 double-pole mains switch	S1
1 mains appliance socket with integral fuseholder	K1
1 mains transformer	Tr1
30V @1A, e.g., ILP 11013 (220V mains) or ILP 13013 (240V mains)	
1 100μA moving-coil meter	M1
1 160mA fuse (slow)	
1 heat-sink for T1; 7K/W	
2 heat-sink for T4 and IC2; 30K/W	
1 printed-circuit board	900104
1 front-panel foil	900104-F
1 enclosure LC850 (manufacturer: Telet; supplier: C-I Electronics)	

Opamp IC1a buffers the voltage supplied by R4-R5, and drives IC1b, the difference amplifier proper. Potentiometer P2 forms the output voltage control. The voltage at its wiper is compared with the voltage supplied by IC1a. The error voltage supplied by IC1b is buffered by T3, and used to control the intensity of two parallel-connected LEDs in an optocoupler. The LDR (light-dependent resistor) at the other side of the optocoupler determines the resistance formed by T1.

Unfortunately, the power supply has some shortcomings because of the use of a power transistor as an adjustable resistor in the regulating circuit. For one thing, the resistance can not become nought since T1 will introduce a minimum drop of about 2.5 V. Add that to the drop across the diodes, and you will realize that the total voltage loss introduced by the regulator is about 4 V. Similarly, T1 can never be turned off completely.

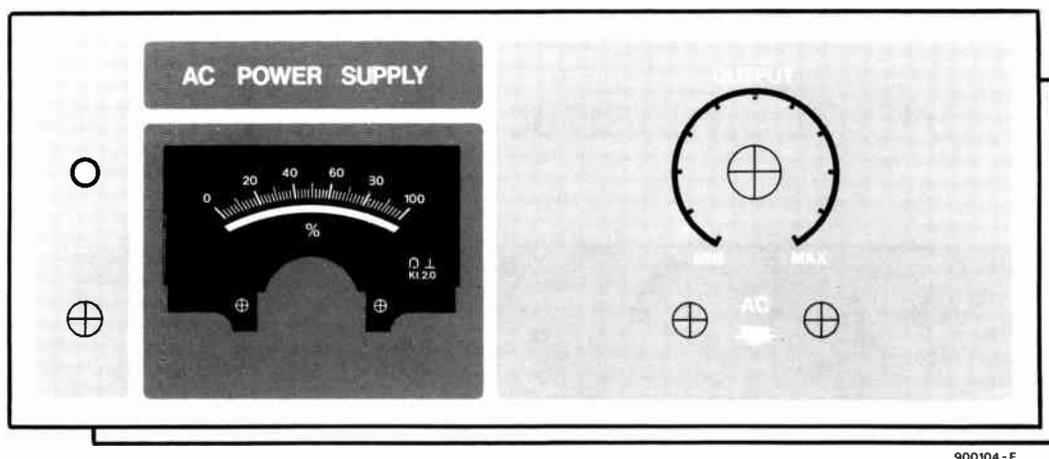


Fig. 6. Layout of the front panel foil (shown here at about 70% of true size). This foil is available ready-made through the Readers Services.

This means that the supply can not be set to an output voltage of 0 V. Fortunately, the actual minimum output voltage is quite low at a value smaller than 0.5 V.

The regulation circuit is powered by the mains transformer via rectifier D3-C2. Components R9, D4 and T4 reduce the rectified voltage to about 33 V, which can then be safely applied to the input of a 12-V regulator, IC2.

## Construction

The construction of the power supply is straightforward if you use the printed-circuit board shown in Fig. 4. The optocoupler

is a home-made device. The construction is shown in Fig. 5. Use a length of PVC tubing, a (black) spool of a photographic film, or cut a piece of thin, black decoration cardboard to size and roll it into a tube.

The printed-circuit board enables the LDR and the LEDs to be connected in two ways, allowing you to determine where the respective component terminals exit from the optocoupler assembly.

The heat-sinks of T4 and IC2 need not be large — in most cases, two pieces of aluminium of an area of about 15 mm<sup>2</sup> will do. Make sure that the heat-sinks do not touch. Alternatively, IC2 and T4 may be mounted on a common heat-sink, provided both com-

ponents are fitted with insulating washers.

The power supply is housed in a metal enclosure Type LC850 from Telet. The dimensions of the blue-and-grey self-adhesive front-panel foil for the supply (Fig. 6) are geared to this type of enclosure.

The two toroid transformers stated in the components list have two 15-V secondary windings, which must be connected in series to obtain the required 30 V.

The power supply has only one adjustment. Connect an a.c. voltmeter to the supply and set an output voltage of 25 V. Next, adjust P1 until the moving-coil meter indicates the same value. ■

## 6-metre band converter

April 1991, p. 38-43

The components list and the inductor overview in the top left hand corner of the circuit diagram should be corrected to read:

L1, L2 = 301KN0800.

Capacitor C16 (4.7 pF) must not be fitted on the board.

Finally, a few constructional tips:

- Fit a 10 nF ceramic decoupling capacitor at junction L7-R36.
- Fit a 18 kΩ resistor between the base of T3 and ground. This reduces the Q factor of L2, and prevents too high signal levels at the base of T3.
- For improved tuning, inductor L9 may be replaced by a Toko Type 113KN2K1026HM.

## Multifunction measurement card for PCs

January and February 1991

We understand that the 79L08 (IC17) is no longer manufactured and, therefore, difficult to obtain. Here, the IC may be replaced by a 7908, which, although physically larger

## CORRECTIONS

than the 79L08, is pin-compatible, and should fit on the PCB.

### Dimmer for halogen lights

April 1991, p. 54-58

In the circuit diagram of the transmitter, Fig. 2, pin 14 of the MV500 should be shown connected to pin 13, not to junction R1-R2-C2. The relevant printed-circuit board (Fig. 6) is all right.

### RDS decoder

February 1991, p. 59

Line A0 between the 80C32 control board and the LC display is not used to reset the display, but to select between registers and data.

We understand that the SAF7579T and the associated 4.332 MHz quartz crystal are difficult to obtain through Philips Components distributors. These parts are available from C-I Electronics, P.O. Box 22089,

6360 AB Nuth, Holland. For prices and ordering information see C-I's advertisement on page 6 of the May 1991 issue.

## S-VHS-to-RGB converter

October 1990, p. 35-40

Relays Re1 and Re2 must be types with a coil voltage of 5 V, not 12 V as indicated in the components list. Constructors who have already used 12-V relays may connect the coils in parallel rather than in series.

Suitable 5-V relays for this project are the 3573-1231.051 from Günther, and the V23100-V4305-C000 from Siemens.


The components list should be modified to read:

6 33nF

C57-C62

# LASER
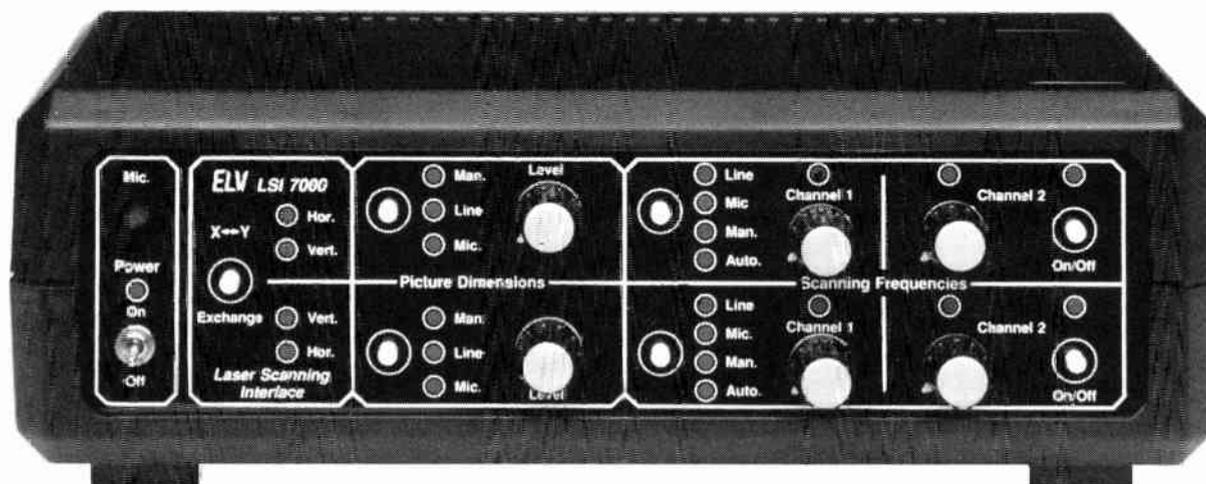
## PART 2: CONTROL UNIT LSI7000 (CIRCUIT DESCRIPTIONS)



Following last month's description of the laser exciter and the mirror galvanometer assembly we now turn to a state-of-the art electronic control unit for the show laser.

*Continued from the May 1991 issue.*

The laser control unit described here is a fairly complex design capable of producing attractive laser patterns. The complete control unit contains some 250 resistors, 100 capacitors and 40 integrated circuits. Fortunately, the assembly of the kit is pretty easy, although it will require several hours of careful soldering work. More about this next month, though, as the present instalment deals mainly with circuit descriptions.

### Pretty sine-waves

Many of you will be familiar with Lissajous patterns on an oscilloscope. Being rather static, Lissajous patterns would appear to be less suitable as show effects for a laser as discussed here. Bear in mind, however, that an oscilloscope produces such patterns when fed with two fixed signals only. A first step towards the creation of moving Lissajous patterns is simply to replace one of the fixed signals by a music signal (or, more generally, an audio signal). The result is a pretty erratic type of pattern on the scope. Some static patterns can be interesting, too, and are simple to produce by increasing the number of sine-waves. The present laser control unit supplies four sine-waves that allow a wide variety of patterns to be created.

The block diagram in Fig. 8 is fairly com-

plex, and indicative of the number of components used to build the laser control unit. The output of the circuit is formed by two 1-watt a.f. power stages that drive the coils in the mirror galvanometers. An electronic double-pole changeover switch fitted ahead of the power output stages allows you to swap the drive signals produced by the two audio interface channels, left and right.

Since the right and left channels are virtually identical, the circuit description will refer to one channel only, in this case, the left one. The input signals for the power output stages are supplied by an electronic potentiometer that allows you to control, independently, the signal frequency (i.e., the shape of the pattern) and the signal amplitude (i.e., the size of the pattern).


There are three sources for the amplitude control signal, which is selected via electronic switches. When the constant voltage source is selected, you can control the size of the pattern via the LEVEL potentiometer. The level information is obtained from an envelope detector when the LINE, LS (loudspeaker) or microphone signal is selected. The LEVEL potentiometer then enables you to set the maximum pattern size reached at a certain level of the input signal.

The LINE, LS and microphone signals may be used to create the laser patterns. In addition to these sources, two sine-wave generators are available of which the output

frequency can be set manually as well as by means of a timer circuit. Before these signals are applied to the electronic potentiometer, they are taken through a frequency compensation circuit that serves to correct the frequency response of the mirror galvanometers. Additionally, the audio signals are taken through a 150-Hz low-pass filter that suppresses signal components that can not be reproduced anyway.

The audio signal may be supplied by the microphone contained in the laser control unit. This microphone is used to drive both channels via a compressor circuit that ensures a fairly constant drive level. The same goes for the LINE and LS signals, which are also taken through a compressor. The difference between the LINE and the LS input is mainly the required signal level. The LINE inputs accept relatively small signals (line level), while the LS inputs can be driven with higher voltages as supplied, for instance, by the loudspeaker output of an a.f. power amplifier.

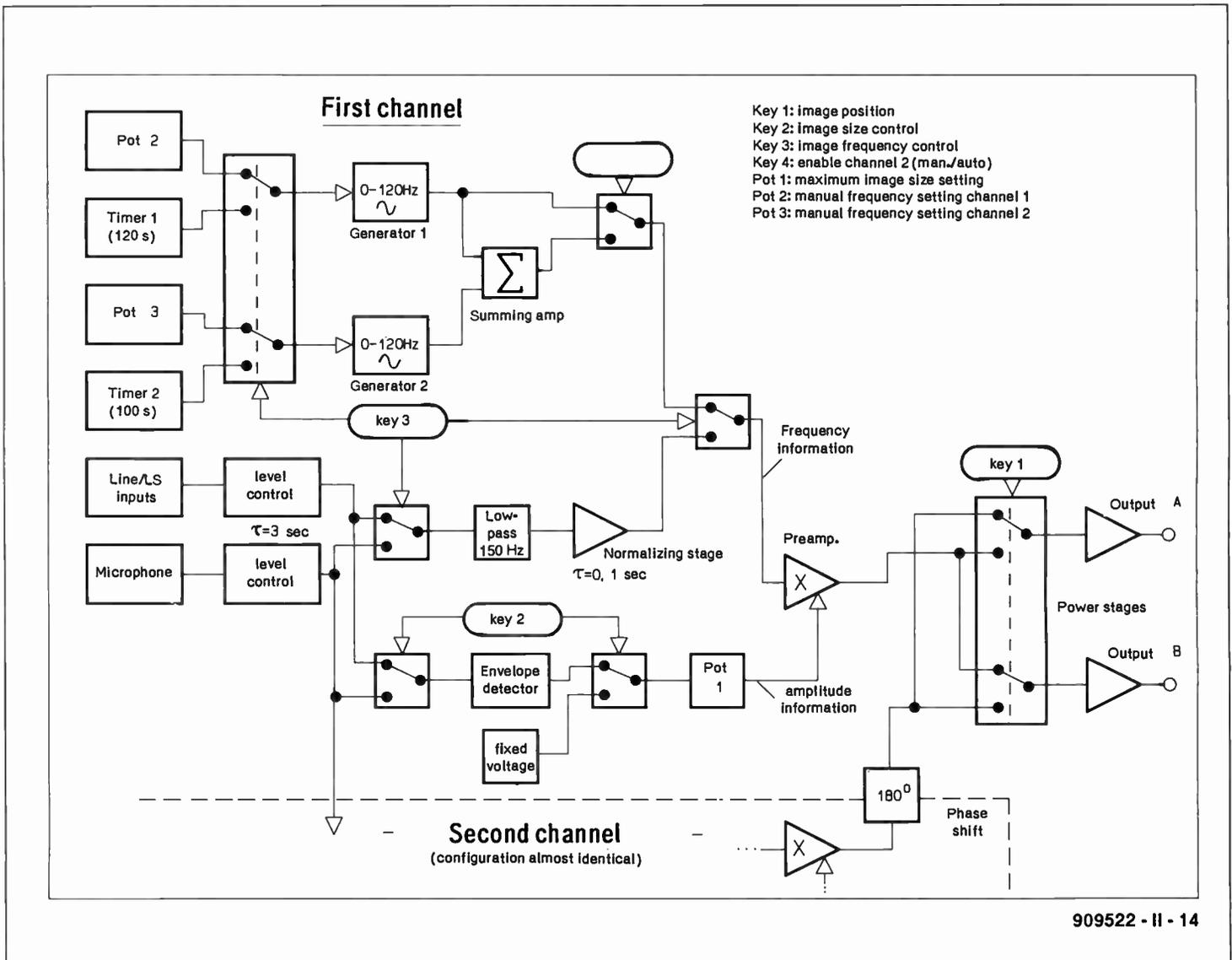Two sine-wave generators are available on each channel of the laser control unit. A switch, marked CHANNEL 2 ON/OFF, is used to select one sine-wave or the sum signal of two sine-waves. The frequency of these is determined by applying a control voltage to the generators. The control voltages can be set manually or by means of a generator that supplies a slow triangular voltage. The



909522 - II - 14

Fig. 8. Block diagram of the laser control unit.

period time of the triangle is about 100 s, but the actual value is slightly different for each of the four generators in the control unit. The differences are such that it takes more than 24 hours (theoretically) before the same pattern is repeated.

## Circuit diagram

The circuit diagram, Fig. 9, of the laser control unit follows the block diagram quite closely. For the sake of simplicity a few blocks are drawn in Fig. 2 that contain circuits discussed in detail further on.

The LINE and LS signals are applied to the circuit via sockets Bu1 to Bu4, which are connected via a potential divider for the right and left channel. This means that the LS socket and the LINE socket next to it can not be used simultaneously. Fortunately, the high impedance of the potential divider prevents damage to equipment when the LS and LINE inputs are accidentally used at the same time. The input signals are first fed to a compressor, whose operation is discussed further on.

The microphone is a small electret type with a built-in FET amplifier. It is connected to terminals ST1, ST2 and ST3. The microphone signal is amplified by IC1 before it is

applied to the compressor. The three compressors are followed by the input selection switches that enable the signals to be routed in one of two directions: to the frequency-determining circuits, or to the amplitude-determining circuits.

In the frequency-determining branch, the signal is first applied to a 150-Hz filter set up around T1 (T3 for the right channel). Then follows another switch, this time for the selection between the audio source and the generator. After the frequency compensation the signal arrives at electronic potentiometer IC4.

In the amplitude-determining branch the audio signal is fed to T2 and T4, which form an envelope detector. The switch contact that follows the detector allows the size of the patterns to be controlled manually or by the envelope waveform of the audio signal. The latter function requires a constant voltage, which is obtained from a regulated supply voltage with the aid of a potential divider. The amplitude control signal is subsequently amplified to allow the final size of the laser pattern to be set by the LEVEL control, R26-R40. Next, the level information is applied to the control inputs of an electronic potentiometer, IC4. The output signal of IC4 is buffered by IC2b and IC3b before it arrives at the

switch contacts that allow you to determine the channel assignment (left/right; L/R) for the horizontal and vertical (H/V) deflection of the laser beam. From the poles of the H/V-L/R switches the signal is taken to the inputs of the two power amplifiers that drive the mirror galvanometers.

## The generators

There are two almost identical generators in the laser control unit. The difference between them is the value of a single resistor. Figure 10 shows the circuit diagram of the generator for the left channel. All components are numbered from 100 onwards. For the right channel, the corresponding components are identified as 2xx. Note, however, that resistor R62 in the left channel appears as R64 in the right channel.

The heart of the generator is formed by two integrated circuits Type XR2206, a well-known function generator from Exar. The frequency of the output sine-wave produced by the generator is determined by a control voltage obtained either from potentiometer R141-R147 via an amplifier, or from a generator.

The circuit for the automatic frequency control of the sine-wave generator may look

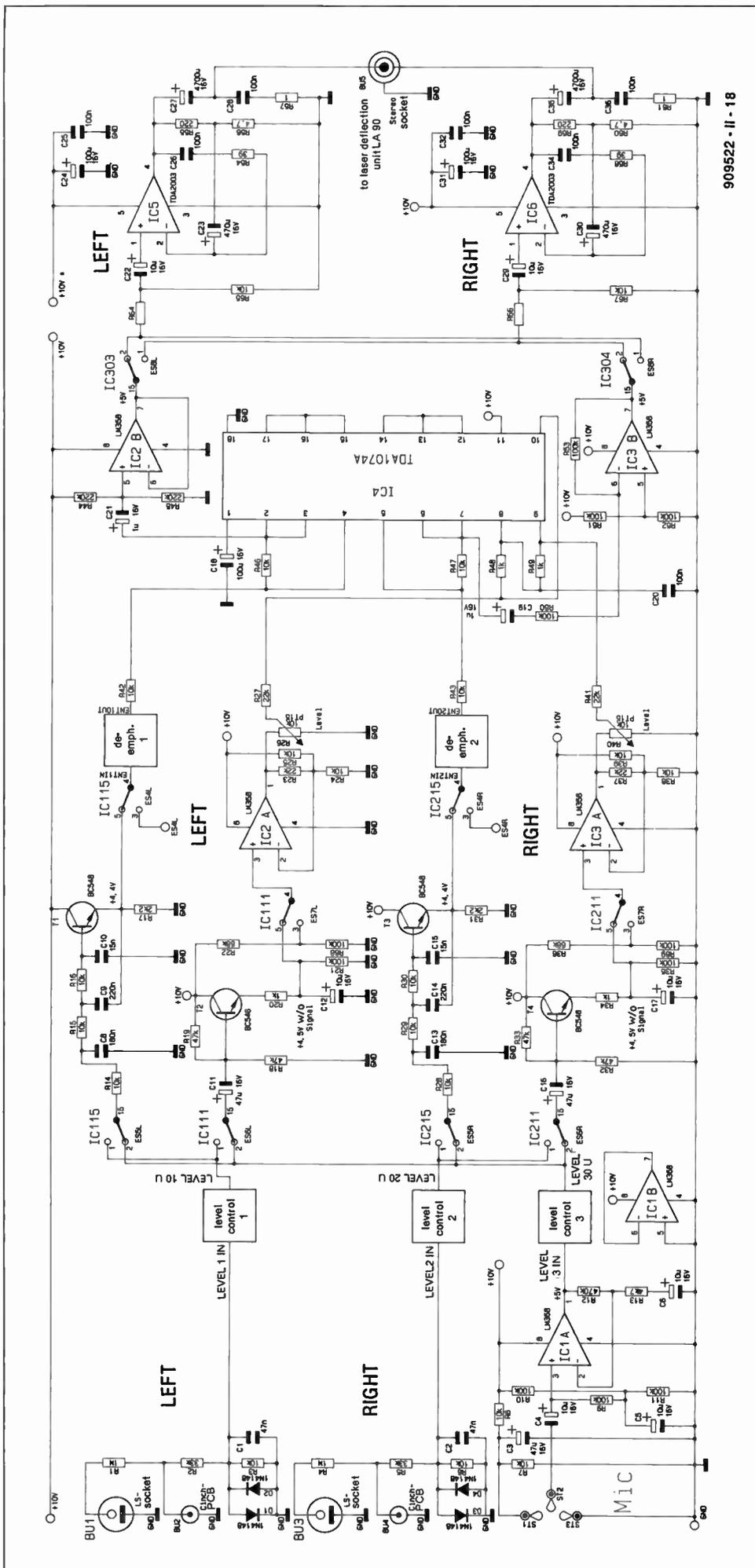


Fig. 9. Main circuit diagram of the laser control unit. Some circuit sections are shown as modules here.

unusual at a first glance. Fortunately, it operates in a rather simple way. Opamps IC103a and IC103b form two Schmitt-triggers set up as square-wave generators. Concentrating on IC103a for the moment, we see that the opamp is wired to function as a Schmitt-trigger by means of resistors R137, R138 and R139. The Schmitt-trigger is turned into a square-wave generator by components R140 and C119. A square wave is, however, not what we are after if we want the sine-wave generator to produce a continuous frequency range. Fortunately, the capacitor, C119, has on it a triangular waveform that does allow a true, linear, VCO (voltage-controlled oscillator) function to be realized. The capacitor voltage, which is a triangular waveform with a period time of about 100 s, is buffered by opamps IC103c and IC103d. Note that the period time is chosen slightly differently for the other generator. This is done to prevent the laser repeating the same pattern after 100 s when the 'automatic' mode is used. The differently set period times ensure that it takes at least 24 hours before a pattern is repeated (this is based on the assumption that component tolerances have no effect).

The generator circuit is followed by a summing amplifier, IC107, that serves to add the two sine-waves. Electronic switch IC115 allows you to select either the output signal of IC105 only, or the mixed output of the two sine-wave generators.

## The compressor

The circuit diagram of the compressor is shown in Fig. 11. The component numbers refer to the left channel — the circuit of the right channel compressor is identical, with component numbers in the '200' range. The component numbers in the microphone compressor start at 300.

Opamp IC101b supplies a stable and adequately decoupled reference voltage to the circuit. The a.f. input signal is applied to the compressor via capacitor C101. Opamp IC101a forms an amplifier whose gain is determined by FET T101, which functions as a voltage-controlled resistance. The output signal level of IC101a is monitored with the aid of a further opamp, IC101d, whose output is connected to a rectifier, D101-D102-C104. To close the a.f. level control loop in the compressor, the direct voltage supplied by the rectifier is fed to the gate of FET T101. The gate voltage determines the a.c. resistance of the drain-source junction, and thus the gain of IC101a. The compressor has an inverse level control characteristic, which means that its gain is reduced as the input signal level increases. In this manner, the compressor ensures that the mirror driver circuits are provided with a reasonably constant input signal.

## Frequency compensation

As discussed last month, the deflection of the mirror galvanometers is frequency dependent, i.e., not linear. To linearize the response, a frequency compensation circuit is used —

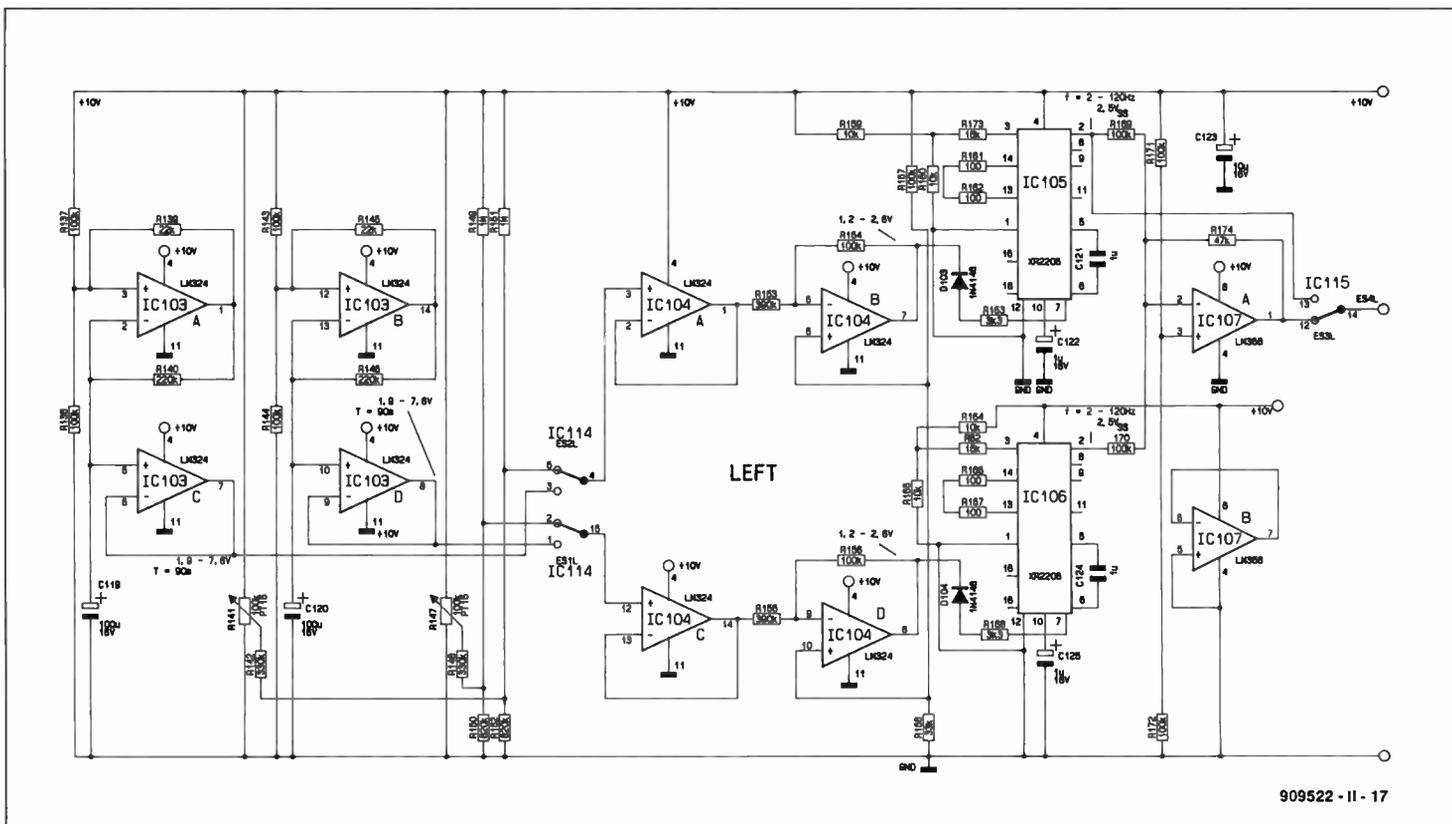


Fig. 10. Generator circuit for the left channel. The right channel is identical, with part numbers in the 200 range.

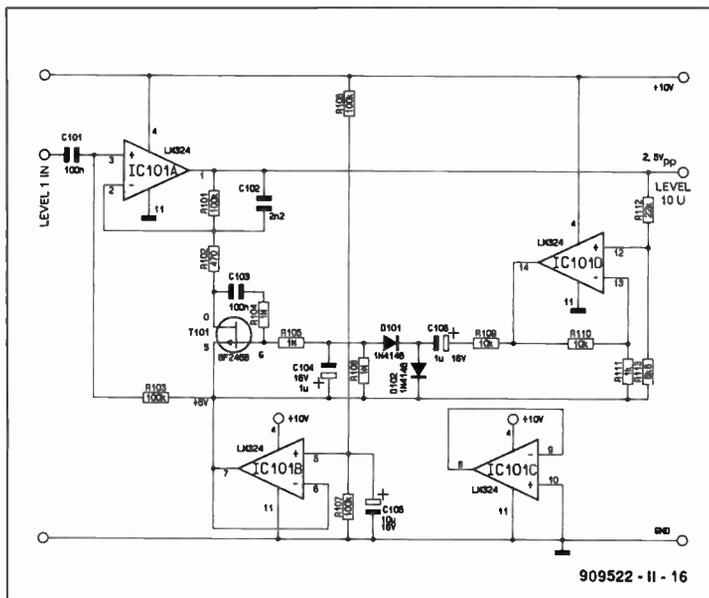


Fig. 11. Compressor circuit (left channel). The component numbers for the (identical) right channel are in the 200 range, and those for the microphone channel in the 300 range.

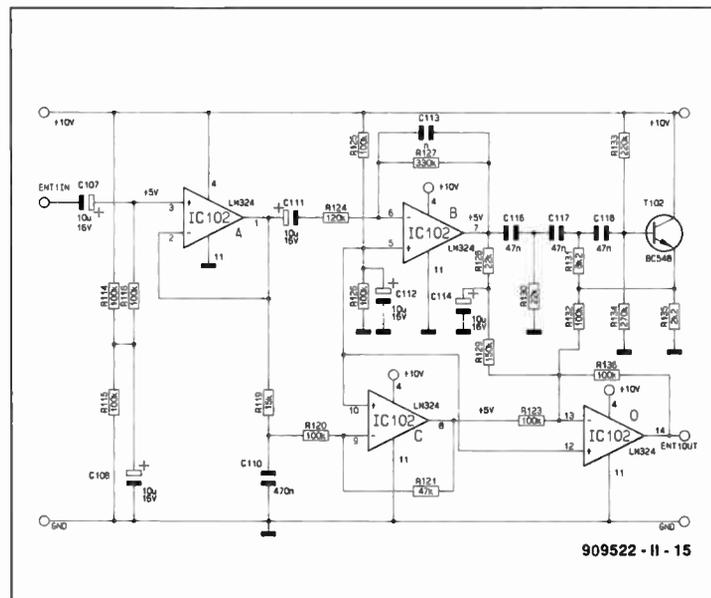


Fig. 12. Frequency compensation circuit for the mirror galvanometer driver in the left channel. A number of filters are used to linearize the frequency response of the mirror over a small range.

see Fig. 12. The circuit starts with a buffer, IC102a, and ends with a summing amplifier, IC102d. The latter adds the signals supplied by a number of filter sections in the circuit via resistors R123, R129 and R132. A filter based on T102 provides a rising filter slope from 50 Hz onwards. The falling slope of the filter response is set to start at about 200 Hz with the aid of R127 and C113. Returning to the low end of the filter response, components R119-C110 create a falling slope from 15 Hz onwards, i.e., before the rising part which starts at 50 Hz. The last filter section, R128-C114, serves to correct the filter response for frequencies below 15 Hz.

The result of all this filtering and summing is a virtually linear response of the mirror galvanometers, i.e., their deflection is independent of the signal frequency when the signal level is held constant.

**Next time**

The above descriptions cover most of the operation of the laser and the associated control unit. In next month's final instalment we will complete the description by discussing the way in which the electronic switches are controlled. The article will be closed with a description of the way in which the laser control unit is built and operated.

A complete kit of parts for the laser control unit (LSI7000) is available from the designers' exclusive worldwide distributors:

**ELV France**  
 B.P. 40  
 F-57480 Sierck-les-Bains  
 FRANCE

Telephone: +33 82837213  
 Facsimile: +33 82838180

# LIGHT SWITCH WITH TV REMOTE CONTROL

Why not use the infra-red remote control, that magic little box supplied with every TV set these days, for applications other than channel hopping and turning the volume up when your favourite pop group appears on the screen? The simple IR receiver discussed here responds to most types of TV remote controls, and can be used to switch lights and other appliances on and off.

J. Ruffell, from an idea by M. Dupessey

**P**RACTICALLY all TV sets these days are supplied with an infra-red remote control. Provided they have not been dropped too often, or chewed on by our beloved pets (we mean domestic animals including parrots and budgerigars), these handy little boxes allow us to remain comfortably seated in front of the 'tube' and exercise total control over the channel selection and a plethora of other settings of the TV set.

As shown in this article, it is perfectly possible to use a remote control box for an application not foreseen by the manufacturer. The general idea is illustrated in Fig. 1: here, the IR remote control is used to switch a light on and off. In some cases, it is even

possible to switch the TV set on and off as well, although this requires a small change in the receiver. Note, however, that many modern TV sets already have a standby/active function controlled via the IR box.

## Single-chip IR receiver

The IR receiver is based on an integrated circuit Type TDE4061 from Siemens. The internal diagram of the chip is given in Fig. 3. The main technical characteristics are:

- Low stand-by current: 650  $\mu$ A;
- Supply voltage range: 4 V to 6.5 V;
- Frequency range up to 200 kHz

- Available with and without demodulator output (TDE4061/TDE4060);
- No inductor required in external circuit;
- High ambient light rejection;
- Bipolar technology couples good high-frequency behaviour with a low current consumption;
- Suitable for battery supply.

The input of the TDE4061 (see Fig. 3) is connected to an infra-red photodiode, which unfortunately not only 'sees' the signal from the IR remote control box, but also visible light, 100-Hz interference from incandescent bulbs, and a part of the light spectrum emitted by fluorescent tubes.

The input stage is followed by a bandpass filter that serves to extract the IR remote control signals from the interference. The demodulator block drawn in Fig. 3 is not available in the TDE4060.


A current sink circuit is provided to suppress low-frequency currents supplied by the photodiode, and stabilize the bias at the input of the IR preamplifier at 1.4 V. The gain of the preamplifier is automatically controlled to ensure optimum drive of the bandpass filter.

The IFR (infra-red) input of the TDE4061 forms a high impedance, and is suitable for input currents in the nano-ampere range. Hence, the anode of the photodiode is connected direct to the IFR input.

The output of the TDE4061, Q, supplies a demodulated digital signal. An example of an output signal is shown in Fig. 2 for the Aristona (Philips) remote control Type RC4520. Note that the pulse lengths, T1 to T4, shown in the diagram depend on the IR remote control used.
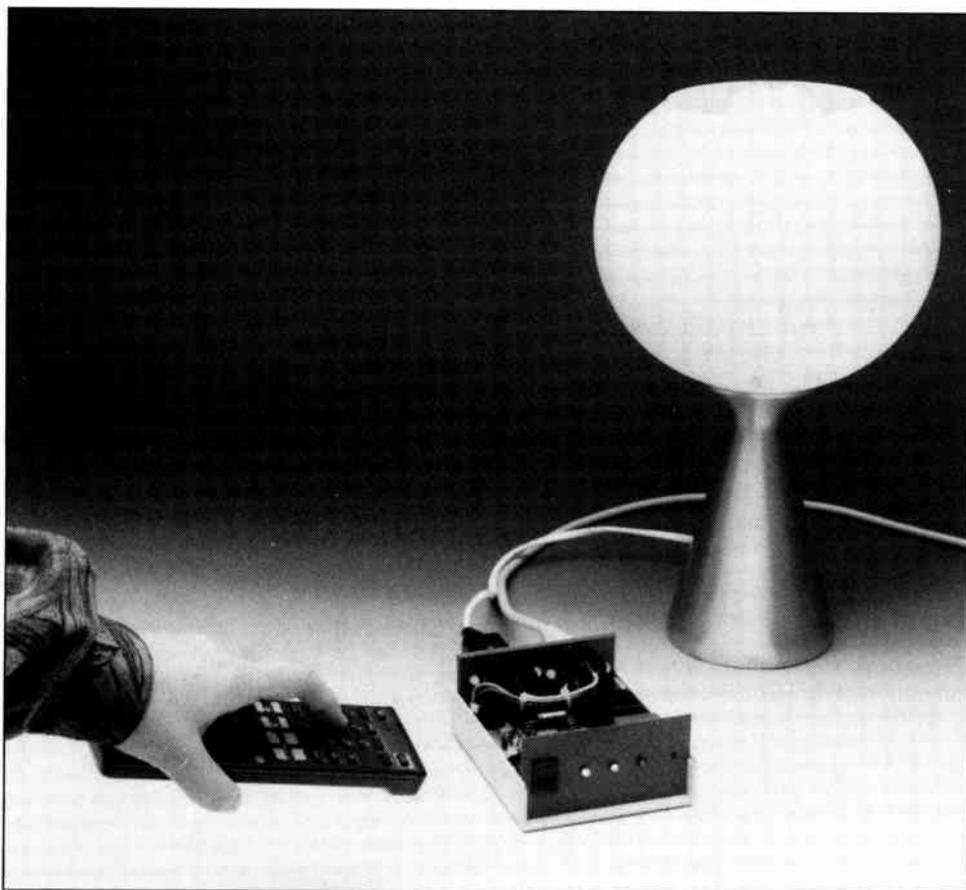
## Circuit description

As shown in Fig. 4, very little is required to build an IR receiver based on the TDE4061. In the following description, some points will be noted that may be of interest to those of you who want to use the TDE4061 for their own applications.



The IR photodiode, D3, is a Type BPW41N from Telefunken. It is forward biased via resistor R5, and supplies a photocurrent to the IFR input of the TDE4061.

Capacitor C1 and resistor R5 form a low-pass filter at the IFR input that serves to suppress interference. The capacitor at the C<sub>REG</sub> input of the TDE4061, C5, determines the time constant of the preamplifier. The value of this capacitor is set to 470 nF to suit the bi-phase-coded signals emitted by most modern IR remote controls. The capacitor must be made smaller when an IR system is used that does not supply run-in signals for the gain control circuit of the receiver. In these cases, C5 may be reduced to about 10 nF. Do not go lower than this value to prevent oscillation.

The capacitor at the C<sub>S</sub> input of the TDE4061, C7, gives the preamplifier a high-pass characteristic, and works in conjunction with G<sub>REG</sub> and the double-T network at the RC1 and RC2 connections of the IC. These components determine the settling behaviour of the TDE4061 following fast signal changes. The C<sub>S</sub> capacitor tunes the receiver to the carrier emitted by the IR remote control. Depending on the carrier frequency, C7 is 100 nF (for 30 kHz systems) or 10 nF (for 120 kHz systems).

The bandpass filter that follows the IR preamplifier improves the signal-to-noise ratio of the IR signal and reduces the jitter on the digital output signal. The external double-T R-C bandpass filter connected to the RC1 and RC2 pins of the TDE4061 must provide a d.c. path, and have a band-stop (notch) characteristic. The notch frequency,  $f_c$ , is made equal to the IR carrier frequency. It is given by

$$f_c = 1/(RC) \quad [\text{Hz}]$$

where  $R=R_6=R_7$ , and  $C=C_9=C_2$ . Note that  $R_8=R/2$ , and  $C_8=2C$ . To keep the voltage drop across the filter within reason, R must not be made larger than 100 kΩ. The values

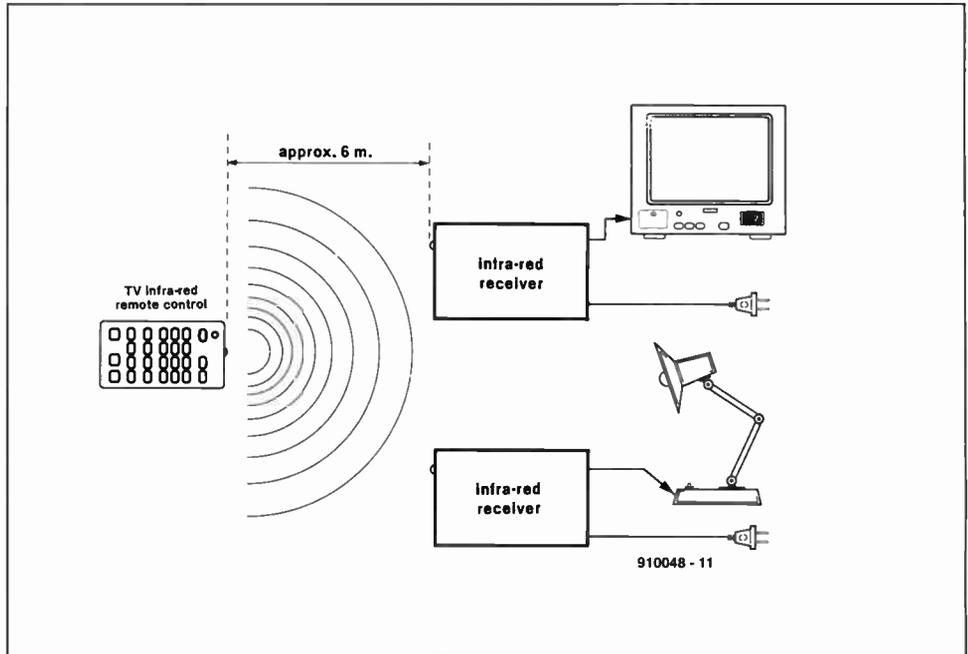


Fig. 1. The remote control supplied with the TV set is used to control a light.

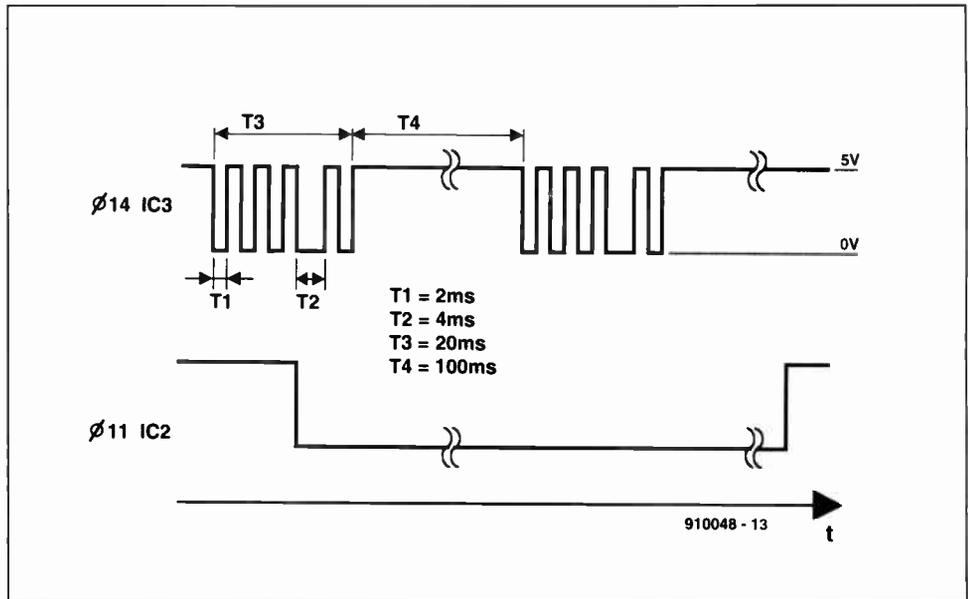


Fig. 2. Response of the the TDE4061 to a typical datastream produced by a TV remote control.

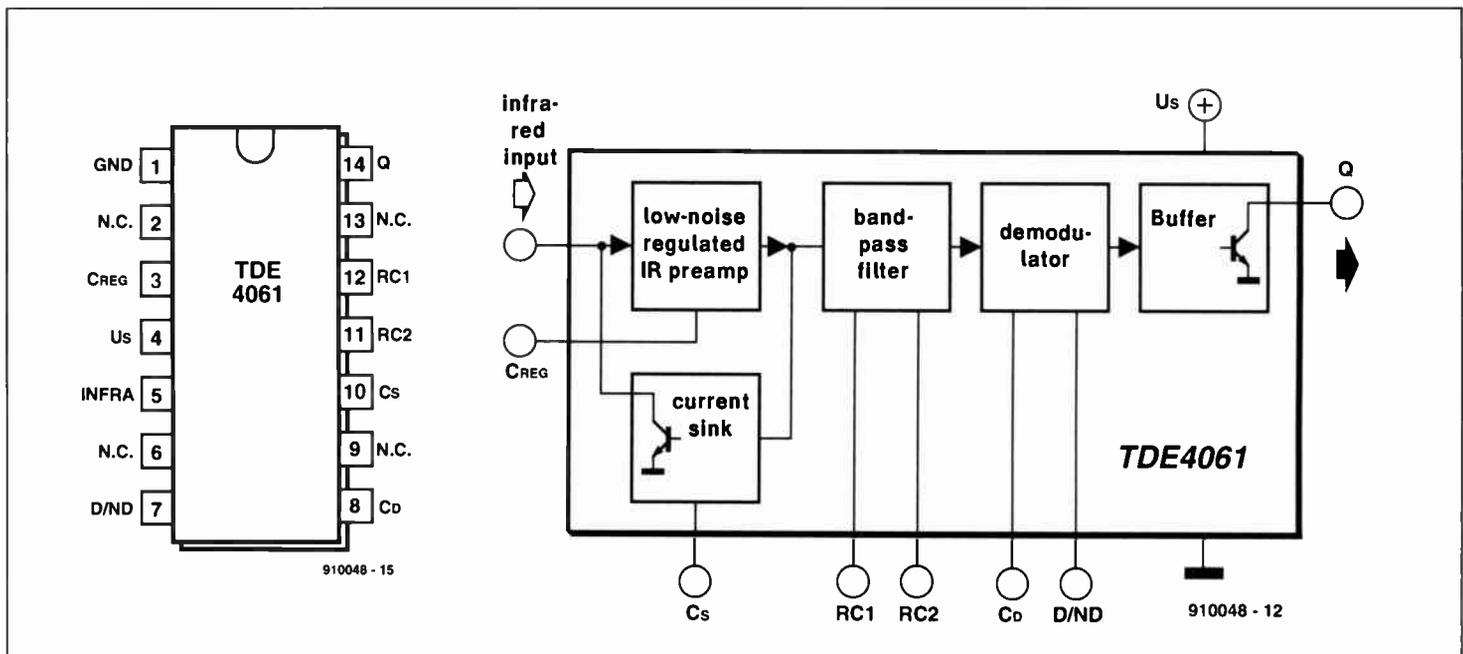


Fig. 3. Functional diagram and pinning of the TDE4061 infra-red receiver IC from Siemens.



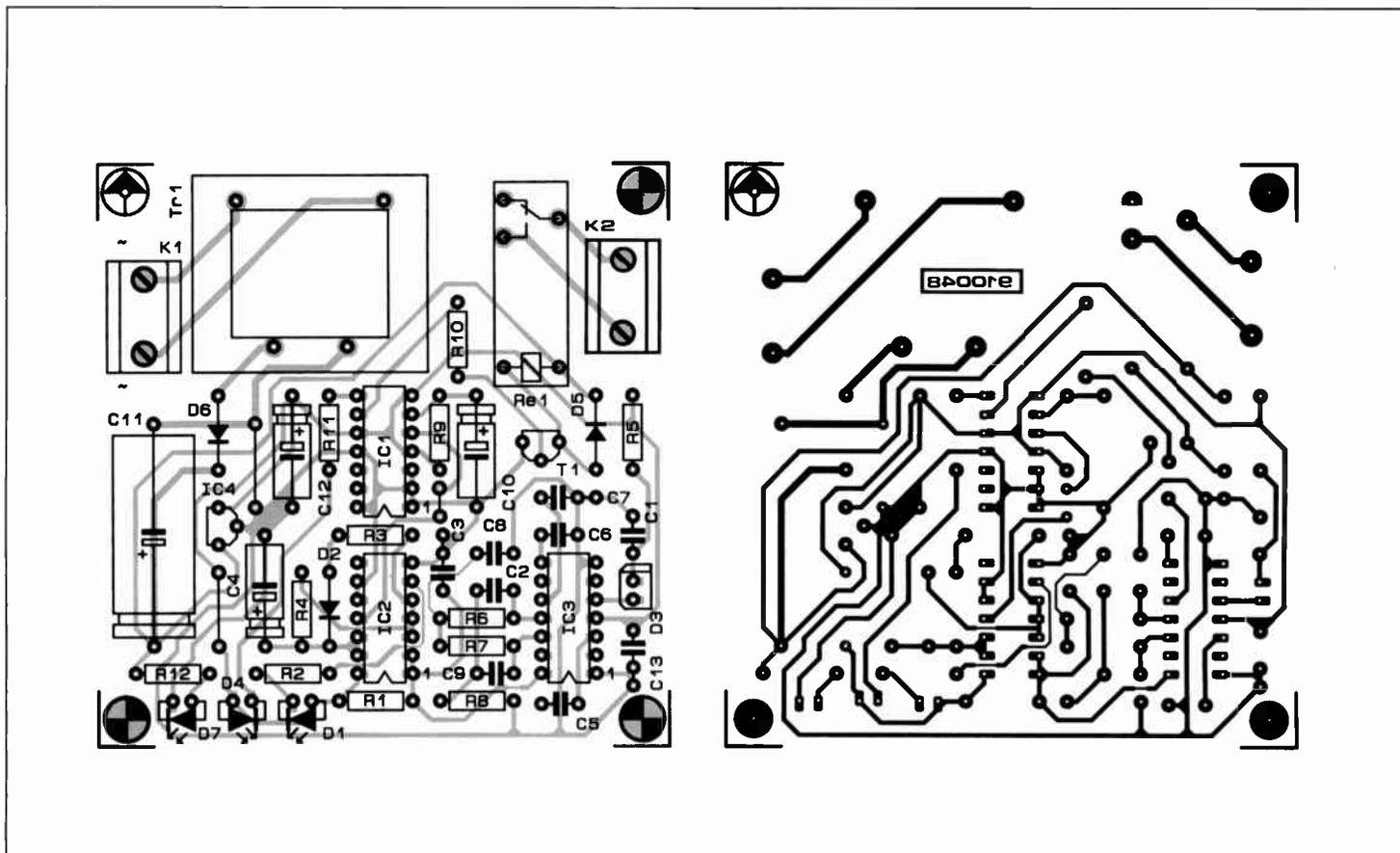


Fig. 5. Single-sided printed circuit board for the IR remote control receiver.

**COMPONENTS LIST**

<b>Resistors:</b>		1 470nF	C5	1 74HCT73	IC1
1 47kΩ	R1	1 220pF	C6	1 74HCT132	IC2
1 220Ω	R2	2 100nF	C7;C13	1 TDE4061 (Siemens)	IC3
1 22kΩ	R3	1 330pF	C8	1 78L05	IC4
1 680kΩ	R4	1 1μF 16V	C10	<b>Miscellaneous:</b>	
2 1kΩ	R5;R12	1 470μF 16V	C11	1 3-way 5mm pitch	K1
2 33kΩ	R6;R7	1 10μF 10V	C12	PCB terminal block	
1 18kΩ	R8	<b>Semiconductors:</b>		1 2-way 5mm pitch	K2
1 220kΩ	R9	1 green LED dia. 3mm	D1	PCB terminal block	
1 2kΩ	R10	1 BAT85	D2	1 12V/330Ω PCB mount	
1 330Ω	R11	1 BPW41N (Telefunken)	D3	relay, e.g., Siemens	
		1 yellow LED dia. 3mm	D4	V23127-B2-A101	Re1
		1 1N4148	D5	1 9V/166mA PCB-mount	Tr1
		1 1N4001	D6	mains transformer,	
		1 red LED dia. 3mm	D7	e.g., Monarch VTR-1109/IV	
		1 BC547B	T1	1 Printed circuit board	910048

into an on/off pulse with a much longer period. This is achieved by a relatively small resistor and a diode, R3-D2, through which the capacitor charges, and a relatively large resistor, R4, through which the capacitor discharges.

The receiver is completed by a standard 5-V regulated supply based on an 78L05, IC4.

**Construction**

The IR receiver is a compact unit because all components are fitted on a single printed-circuit board, which is shown in Fig. 5. Start the construction by fitting the three wire links on the board. Next, fit the resistors, the diodes, the capacitors, and the active components. Use sockets for the ICs, which are not

plugged in until the board is completely assembled.

Complete the construction of the board by mounting the transformer, the relay and the soldering pins. The three LEDs are fitted such that their faces protrude from holes in the plastic enclosure. The infra-red diode, D3, is fitted on the front panel of the case. It is secured such that its light-sensitive area can 'see' the remote control. The light-sensitive area of the BPW41N is located at the centre of the flat front side of the device.

After finishing the construction of the PCB, connect the mains cable to K1, a 3-way PCB mount terminal block of which the centre pin is cut off. Next, connect the load to K2.

To enable you to experiment with differ-

ent values, the PCB allows capacitors with two different lead spacings to be fitted in positions C3, C7 and C13.

**Practical use**


With most remote control boxes the usable range of the receiver will be greater than 5 metres. Since the response time of the receiver is relatively short at a few tens of milliseconds, the unit must be installed at some distance from the TV set to prevent it being triggered by control commands intended for the TV set. If you still want to locate the receiver close to the TV set, increase the value of C4 to, say, 47 μF. This results in a much longer response time to remote control commands.

# FOR SALE

Mobile Fidelity ultradis for sale, 24K Gold high quality audiophile compact discs, good prices on Pink Floyd, Elton John, etc. Free catalog, please send self addressed stamped envelope to Stereo Unlimited, John Senchank, 44 Elm St., Seymour, CT 06483-3635. These discs are for the serious music listeners, must hear!

Electronic supermarket, great buys! Surplus prices, ICs, DC motors, vacuum pump, transformers, PS, stepping motors, builders, engineers, experimenters, LSASE Fertik's, 5400-A Ella, Philadelphia, PA 19120.

## RESISTORS 5% 1/4 WATT

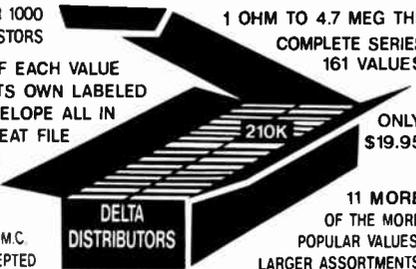

OVER 1000 RESISTORS  
5 OF EACH VALUE IN ITS OWN LABELED ENVELOPE ALL IN A NEAT FILE BOX

1 OHM TO 4.7 MEG THE COMPLETE SERIES 161 VALUES

ONLY \$19.95

11 MORE OF THE MORE POPULAR VALUES. LARGER ASSORTMENTS AVAILABLE

VISA AND M.C. ACCEPTED  
1 (800) 234-4196  
DELTA DISTRIBUTORS - BOX 87R EAST DERRY, N.H. 03041

# TRADE

**WE SELL MORE HIGH PERFORMANCE SPEAKER KITS** than anyone in the US. Complete line of raw drivers, crossover components, etc. Free catalog. **AUDIO CONCEPTS, INC.** 901 S. 4th St., La Crosse, WI 54601, (800) 346-9183. T7/91

**HIGH-VOLTAGE PLANS** Create fork lightning 50,000V—1,200,000V... Catalogue, \$1. **SCIENTIFIC**, Box 1054AF, Duvall, WA 98019. T6/91

# CLASSIFIEDS

# WANTED

One or two new stylii for microacoustics phono cartridge model 530-MP Segue Services Inc., HCR-1 Box 286-D, Merrifield, MN 56465, (218) 765-3333.

# CLUBS

**AUDIOPHILES IN THE DAYTON/SPRINGFIELD, OHIO AREA:** We are forming an audio club. Please contact me if you're interested in construction, modifications, testing, recording or just plain listening to music. Ken Beers, 1756 Hiit Rd., Yellow Springs, OH 45387, (513) 767-1457.

**THE CATSKILL AND ADIRONDACK AUDIO SOCIETY** invites you to our informal meeting. Join our friendly group of audio enthusiasts as we discuss life, the universe and everything! Toobers, Tranzzeestors, vinyl canyons or digital dots. No matter what your level of interest, experience, or preferences, you are welcome. Contact CAAS at (518) 756-9894 (leave message), or write CAAS, PO Box 144, Hannacroix, NY 12087. See you soon!

**CHICAGO AREA ENTHUSIASTS WANTED** for audio construction club. Call Tom, (312) 558-3377 or (708) 516-0170 evenings for details.

**CONNECTICUT AUDIO SOCIETY** is an active and growing club with activities covering many facets of audio — including construction, subjective testing, and tours of local manufacturers. New members are always welcome. For a copy of our current newsletter and an invitation to our next meeting, write to: Richard Thompson, 129 Newgate Rd., E. Granby, CT 06026, (203) 653-7873.

**THE COLORADO AUDIO SOCIETY** is a group of audio enthusiasts dedicated to the pursuit of music and audiophile arts in the Rocky Mountain region. We offer a comprehensive annual journal, five bi-monthly newsletters, plus participation in meetings and lectures. For more information, send SASE to: CAS, 4506 Osceola St., Denver, CO 80212, or call Art Tedeschi, (303) 477-5223.

**THE BOSTON AUDIO SOCIETY** invites you to join and receive the bi-monthly *B.A.S. SPEAKER* with reviews, debates, scientific analyses, and summaries of lectures by major engineers. Read about Apogee, Nyal, Conrad-Johnson, dbx digital, Snell, music criticism and other topics. Rates on request. PO Box 211, Boston, MA 02126.

**IF YOU ARE** an "Organ Music Lover" and like to test your audio system, **SFORZANDO** has room for a few more members. We have about three thousand "Live", on-the-spot, cassette tapes that are not available in the stores. We are happy to lend them to you via the mail. Just ask EA Rawlings, 5411 Bocage St., Montreal, Canada, H4J 1A2.

### INDEX OF ADVERTISERS

All Electronics Corporation	77
Audio Amateur Publications	
Subscriber Services	68
Borbely Audio	77
Kelvin Electronics	CV II, 71
Madisound Speaker Components	72
Mark V Electronics	72, 76
MIT-Finch & Marsh	CV III
New Sensor	59
Old Colony Sound Lab	
Books	5-10, 69, 70
EPROMs	69
Front Panel Foils	69
Meek It Kits	74-75
New Kits	78
Printed Circuit Boards	69
"Save Your Invoice" Sale	76
Software	69
Optoelectronics	CV IV
Paleo Systems	72
PC Boards	77
RF Connection	26, 72
Sescom Inc	4, 73
E.H. Yost and Co	72

# ELEKTOR ELECTRONICS CLASSIFIED ORDER FORM

PLEASE FILL OUT IN CLEAR BLOCK LETTERS OR TYPE. PLEASE SPELL OUT ENTIRE WORD.

1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40
41	42	43	44	45	46	47	48	49	50

Private For Sale       Private Wanted       Trade

If Trade, please indicate # of insertions \_\_\_\_\_

Private ads are on a one time insertion basis. Must be resubmitted for renewal. **Ads cannot be taken over the phone.**

**Definition of a word:** A series of letters with a space before and after. Count words, not letters. Any words over 50, 20¢ per word. Trade ads are 75¢ per word and indicate number of insertions. Deduct 10% for a 6 x contract; deduct 15% for a 11 x (year) contract in *Elektor Electronics USA*. **Payment MUST accompany first ad.**

Please remember to include your name, address and telephone number when making calculations. In order for Private For Sale and Want ads to be **free**, you must be a current subscriber. *Ten dollar minimum charge for charge card orders and Trade ads.*

Check/Money Order Enclosed

Please charge to my MasterCard/Visa:

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

STREET & NO. \_\_\_\_\_

CARD NUMBER \_\_\_\_\_ EXP. DATE \_\_\_\_\_ CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

## VACUUM TUBE DEALER PRICE LIST (APRIL 1991)



<b>SOVTEK, USSR</b>				50 CALL FOR SPOT QUOTE 100 CALL FOR SPOT QUOTE
EL84/6BQ5	\$2.60 each	12 at \$2.25 each	25 at \$1.75 each	
6V6GT	3.90	3.35	2.95	
6L6GC	4.50	3.95	3.65	
5881/6L6WGC	6.75	6.20	5.75	

The 5881 is Russia's selected military 6L6WGC and regarded as the very best 6L6 type in the world. Eric Clapton recently replaced the Philips/Sylvania 6L6 STR's in his custom Soldano amp which he uses live, with SOVTEK 5881's because of their milky smooth sound. Discriminating musicians throuout the world are retubing with the SOVTEK 5881/6L6WGC.

<b>SINO, CHINA</b>				100 CALL FOR SPOT QUOTE
5U4G	\$4.60 each	10 at \$4.15 each	25 at \$3.75 each	
EL34	5.70	4.80	4.25	
6L6GC	4.70	4.20	3.95	
12AX7a	3.85	3.35	3.15	
12AT7	3.90	3.40	3.30	
6146B	12.50	11.50	10.50	
6550	10.50	9.40	8.95	
KT88	13.50	12.25	10.95	

<b>Ei, YUGOSLAVIA</b>				100 CALL FOR SPOT QUOTE
EL34/6CA7	\$5.10 each	10 at \$4.65 each	25 at \$4.10 each	
6DJ8	3.25	2.95	2.65	
12AU7/ECC82	3.15	2.80	2.35	
12AX7/ECC83	2.60	2.30	2.05	

<b>SIEMENS, GERMANY</b>				100 CALL FOR SPOT QUOTE
EL34	\$7.25 each	10 at \$6.75 each	25 at \$6.20 each	
12AT7	3.95	3.45	3.35	

<b>GE</b>					
5U4GB	\$11.85 each	10 at \$11.25 each	6550a	\$17.95 each	10 at \$16.50 each
6CA7	14.95	13.50	7025	14.75	13.25
6L6GC	14.95	13.50	7027a	16.95	16.25
12BH7	9.95	9.50	7591a	14.75	13.50
12AT7	6.85	6.40	7868	16.95	16.25
12AX7a	4.95	4.40	8417	15.75	14.25

### SOLID STATE RECTIFIER

Built into tube socket. Direct plug-in replacement for all 5Y3, 5U4 and 5AR4 types. \$6.25 each 10 at \$5.90

### ODD BALL TUBES (MOSTLY USA STOCK)

5AR4	\$7.95 each	6BA6	\$2.50 each	6J5	\$4.50 each	6X5	\$3.90 each	5879	\$6.50 each
5BC3/9	1.95	6BK11	7.90	6J7	5.50	6X8	2.25	6189W	3.80
5V4GT	6.95	6C4	2.50	6K11	6.90	12AY7	5.95	(12AU7W industrial)	
5Y3GT	4.95	6C56T	2.75	6SC7	6.90	12AZ7	3.90	6973	11.90
6AN8	4.95	6C10	4.50	6SG7	3.50	12DT8	4.95	7189	7.90
6AL5	2.75	6CA4	3.50	6SJ7	4.45	12DW7	11.95	7199	17.80
6AQ5a	4.25	6CG7	6.90	6SK7	3.15	12FQ8	4.75	7247	11.95
6AT6	3.25	6EU7	11.80	6SL7	4.35	57	1.95	OA2	2.75
6AU6	2.50	6FH8	10.90	6SN7	5.45	5749	4.75	OA3	2.75
6AV6	2.50	66GT5	14.75	6U10	4.90	(6BA6W industrial)		OB2	1.90
6AX5	4.90	6GW8	6.90	6X4	3.75			OC3	4.75

**GIVE US A CALL ON ANY TOUGH-TO-GET TUBE. WE'LL FIND IT FOR YOU!**  
**ALL TUBES GUARANTEED! QUANTITY DISCOUNTS AVAILABLE!**

MINIMUM ORDER \$40.00

ADD \$5.00 SHIPPING (\$10.00 OUTSIDE UNITED STATES)

SEND CHECK OR MONEY ORDER TO:

## NEW SENSOR CORPORATION

245 EAST 63RD STREET, SUITE 526, NEW YORK, NY 10021

CONTACT: MIKE MATTHEWS

TELEPHONE: (212) 980-6748

TOLL FREE: 1-800-633-5477

FAX: (212) 753-7340

# REAL-TIME CLOCK FOR ATARI ST

**The Atari ST is a user-friendly computer supported by a massive amount of excellent software. Unfortunately, early models of the ST lack a clock circuit that keeps ticking when the computer is switched off. The circuit presented here overcomes this problem.**

**F. Dossche**

**A**LTHOUGH the design of the Atari ST computer is modern by any standard, a real-time clock (RTC) is provided only on the latest models. This is surprising because the main rival of the ST, the IBM PC or compatible, has had an RTC as an option or a standard feature longer than many of you will care to remember. Owing to the absence of an RTC, many Atari ST users are forced to set the date and time, every time the computer is switched on. To help out the thousands of faithful owners of older ST models, we have developed a real-time clock that is inexpensive and simple to build.

One of the most attractive features of the Atari ST is the number of interfaces. One of these interfaces, the printer port, is used here to connect the real-time clock to the computer. We hasten to add that you will be able to use the printer as before, since the RTC is inserted between it and the Centronics port, for which only a very small modification is required.

## Up-to-date with the RTC

Of the real-time clock ICs currently available, the MSM5832 from OKI and the MC146818 from Motorola are probably the best known and widest used. The Motorola IC has an advantage over the MSM5832 in offering an 8-bit wide databus, and a 50-byte non-volatile RAM (random access memory). The data retention is achieved with an external rechargeable battery.

Here, the Motorola IC is used, although no use is made of its internal RAM. The 8-bit databus of the RTC chip allows the control software to be kept fairly simple, and in addition affords the possibility to implement further extensions circuits on the Centronics port. The control software for the present project is supplied on disk in the form of a source listing written in C. This program may be used as the basis for further hardware or software functions that you may wish to add. The hardware presented here, and the object code compiled with the aid of the C program, can be used to develop a 'desk accessory' to support the new clock function.

Returning to the hardware, the circuit diagram of the clock extension is shown in Fig. 1. The heart of the circuit is the RTC chip from Motorola. Besides four logic gates and


two bistables, the circuit contains a handful of discrete parts used mainly to implement a battery back-up function for the RTC. The two bistables and one I/O line on the computer's main board serve to direct the data on the Centronics bus either to the printer or the real-time clock. In addition, one of the bistables indicates whether the 8-bit word sent to the clock circuit is intended to select an address location, or to be stored as data in the RTC.

The real-time clock sits between the Centronics port on the computer and the Centronics input of the printer. Hence, it has an input and an output connector.

At the left in the circuit diagram we find connector K1 which links the circuit to the computer. Two new signals appear on this connector on pins 16 and 17. Pin 16, normally the RESET line, is not used by the Atari

ST, and now carries the computer's 5-V supply voltage. Since the RESET signal is active low according to the Centronics standard, placing +5 V on pin 16 has no effect on the printer (anyway, the ST is not capable of issuing a reset via this line).

Pin 17 of K1 is connected to an unused I/O line in the computer, and serves to direct data either to the RTC or to the printer. The I/O line is found on pin 14 of the sound generator IC in the ST, the Yamaha YM-2149. Although not used in the hardware of the ST, this I/O line is supported by the BIOS (basic input/output system), which makes it perfect for the present application. Pin 17 on the Centronics connector is chosen because it is not used on the ST or the printer. Do, however, check that the cable between the computer and the RTC has a wire for the signal on pin 17. In general, most serial cables for

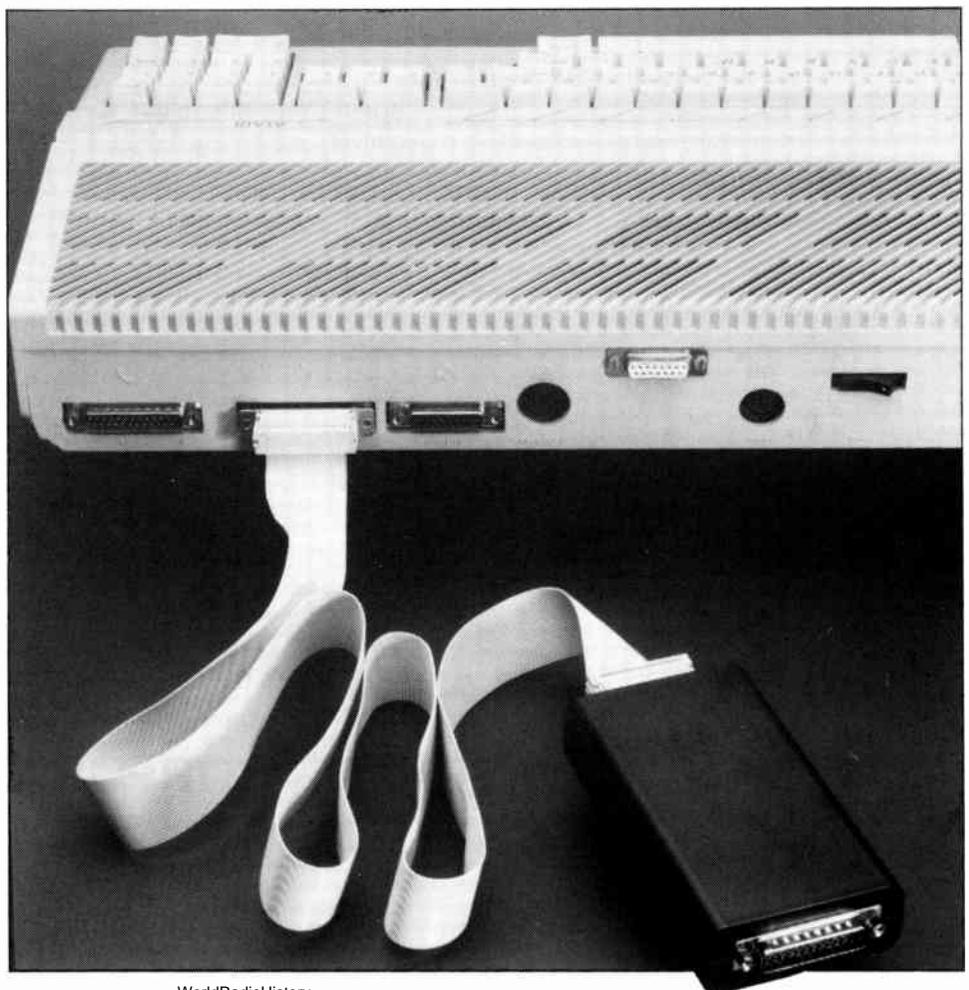

WorldRadioHistory

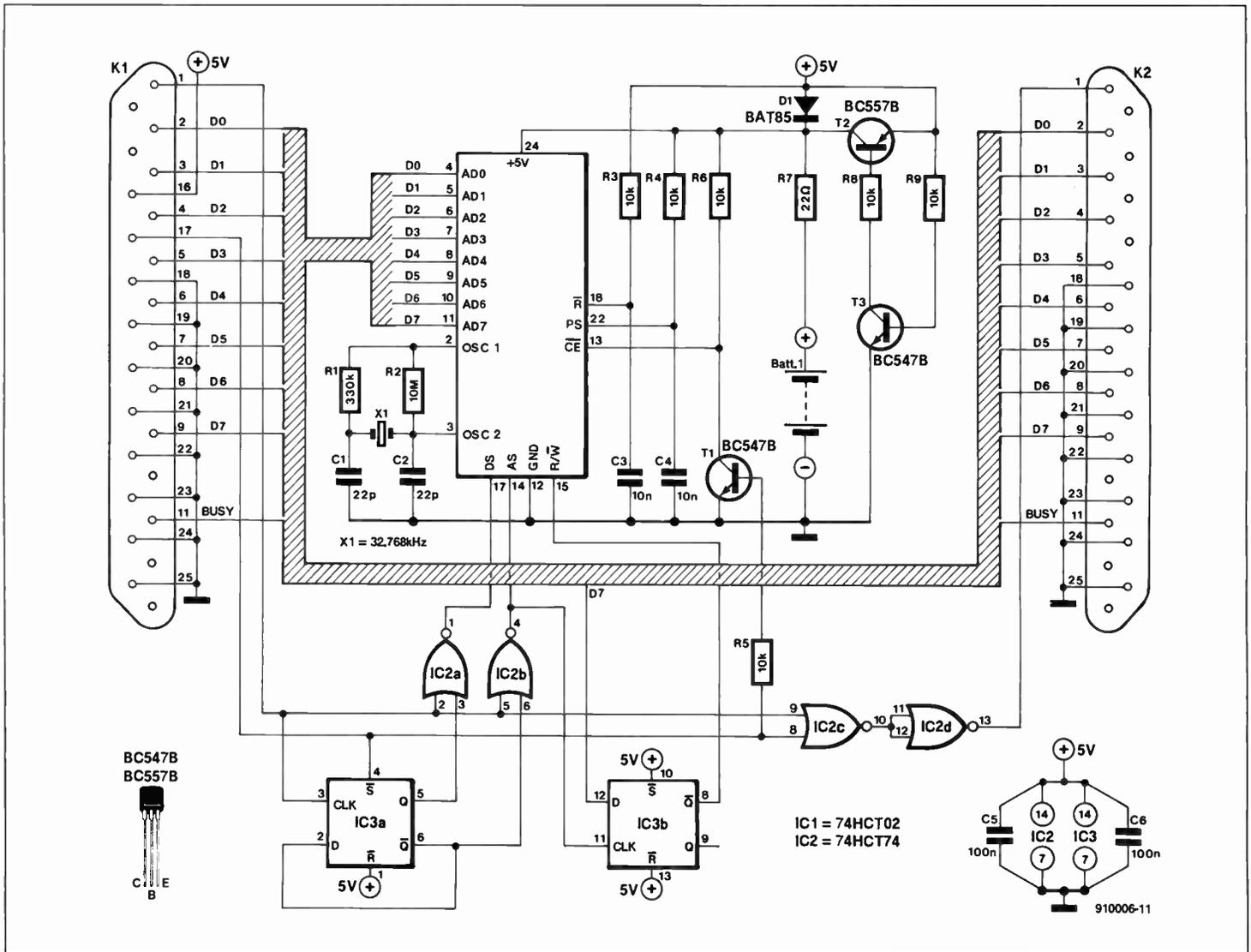


Fig. 1. Circuit diagram of the real-time clock.

PCs have a wire for each of the 25 pins, and will, therefore, meet our requirement. You may also decide to make your own 25-way cable, which has the advantage that it can be made shorter than most ready-made cables. These are usually 1 m or 2 m long, and quite bulky for our application. A home-made cable may be produced by a short length of 25-way ribbon cable terminated in an IDC-style male 25-way D-connector at one end, and a female D-connector at the other end.

Returning to the circuit diagram, the signal at pin 17 of K1 enables bistable IC3a by making the  $\bar{S}$  line logic high. This results in any changes at the set and the reset inputs of IC3a being ignored, so that the bistable remains in the 'set' state because the SET line was active last. Also, the strobe signal for the printer (connected to K2) is blocked by gates IC2c and IC2d, and the enable input of the RTC is actuated via transistor T1. Next, an RTC address is passed to the circuit via the Centronics datalines. The most-significant bit, D7, indicates a read or a write operation to or from the RTC registers.

A pulse on the strobe line (pin 1 of K1) is fed to the AS input of the RTC chip via bistable IC3a and gate IC2b. This pulse is used to transfer an 8-bit word on the Centronics datalines to the RTC, or vice versa, as indicated by the level of databit D7. After the

strobe pulse, the inverted level of D7 is applied to the R/W input of IC1. When the next strobe pulse occurs, IC3a toggles because the Q output of this bistable is connected to its D (data-) input. The pulse is subsequently fed to the DS (data strobe) input of IC1 via IC2a. Data may be read before the end of the second strobe pulse. When this is finished, the computer will de-actuate the 'select' line (pin 17 on K1). The printer can then be used again, and the clock operates. The above sequence is used to store the time and date in the RTC, and also to read these back into the computer, allowing the system clock in the ST to copy the RTC information. Gone are the days when you had to set the system clock every time the ST was switched on.

The rest of the circuit is fairly simple. The PCB has two options for charging the battery. The simplest is by means of diode D1. When the ST is switched on, the battery is charged via D1 and R7. The RTC is also powered via the diode. This must be a Schottky type to ensure a low voltage drop. Remember, the charge current can become too small when the computer supply voltage is on the low side, when the battery voltage is on the high side. This is prevented by a diode with a low voltage drop.

If you can not secure the BAT85 or an equivalent Schottky diode, add the circuit

based on T2 and T3. When the computer is switched on, T3 starts to conduct and switches on T2. By virtue of the relatively low collector-emitter voltage of T2, the charge current for the battery is sufficiently high. When the computer is switched off, T3 blocks and turns off T2, so that the battery takes over the supply of IC1. Note that the transistor-based supply is an alternative to the single Schottky diode — components T2, T3, R8 and R9 are not fitted if you use a BAT85.

The RESET and PS inputs of IC1 are taken logic high briefly after the supply is switched on. This ends the low-power standby state of the RTC, and causes it to switch to normal operation.

A quartz crystal, X1, together with C1, C2, R1, R2 and two gates in IC2 form an oscillator that supplies a clock of 32.768 kHz to the RTC. This frequency is used in most battery-powered clocks and electronic wrist-watches.

### Construction

The construction of the real-time clock unit will present little difficulty if the printed-circuit board shown in Fig. 2 is used. Start the construction by fitting the wire links and the connectors. Note that K1 is a male type, and K2 a female type. If you swap them acciden-

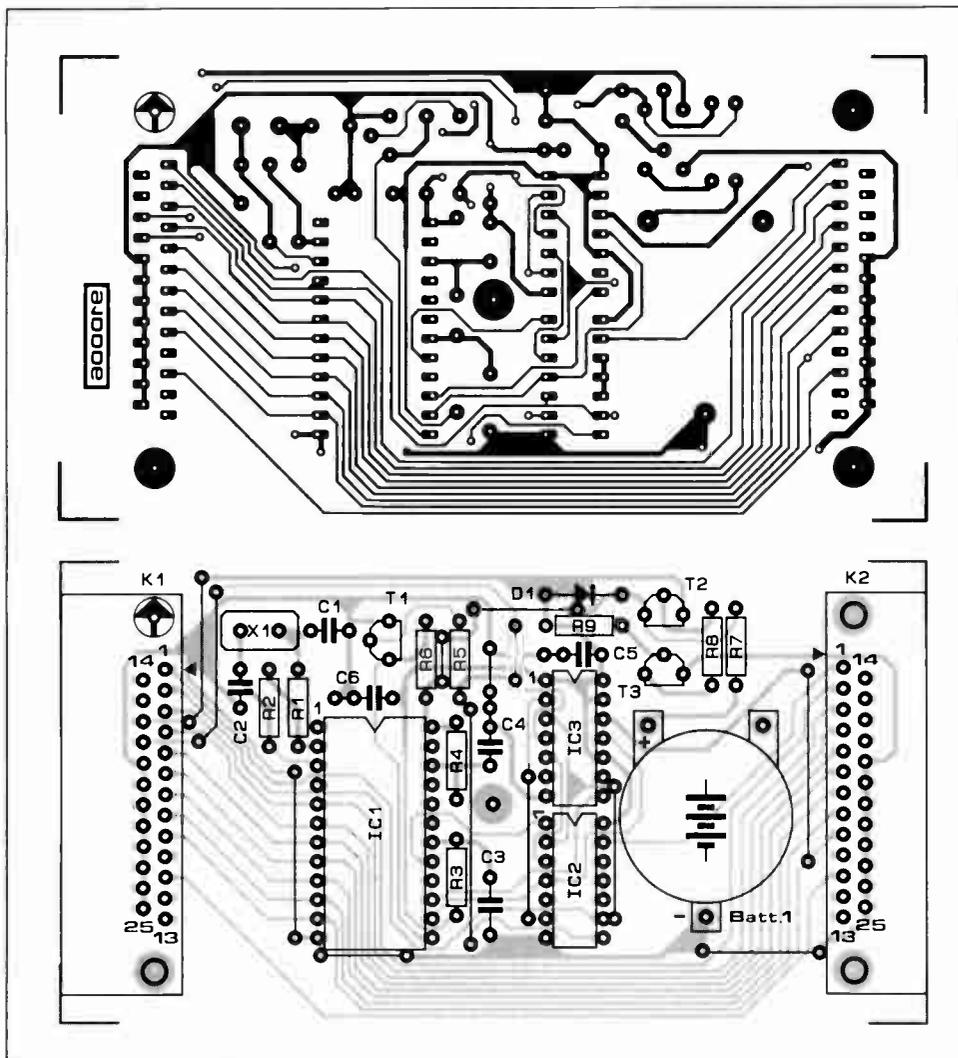


Fig. 2. Single-sided printed circuit board for the real-time clock.

tally, you will be unable to connect the circuit properly to the input and output cables.

Proceed with fitting the remaining parts on the board. IC sockets are not strictly required. If you do decide to use them, be sure to buy good quality types.

The completed printed circuit board fits into an ABS enclosure of dimensions 120x70x30 mm. The side panels of the enclosure are cut to allow the connectors to protrude.

A small modification is required in the computer before the RTC can be connected. Although the 'operation' is really no more than soldering two wires, it may still take you an hour or so to complete because the computer has to be disassembled. After removing the floppy disk drive and the switching power supply module, you should be able to see the printer connector and the Yamaha chip. Take the main board out of the enclosure, and remove the metal screen at

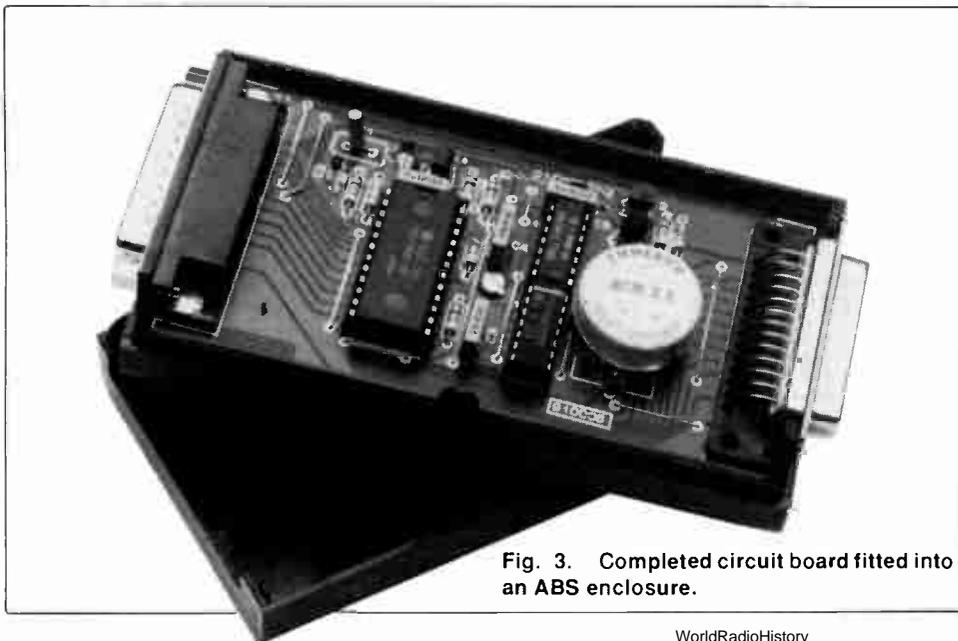


Fig. 3. Completed circuit board fitted into an ABS enclosure.

## COMPONENTS LIST

### Resistors:

1	330k $\Omega$	R1
1	10M $\Omega$	R2
6	10k $\Omega$	R3-R6;R8;R9
1	22 $\Omega$	R7

### Capacitors:

2	22pF	C1;C2
2	10nF	C3;C4
2	100nF	C5;C6

### Semiconductors:

1	BAT85	D1
2	BC547B	T1;T3
1	BC557B	T2
1	MC146818	IC1
1	74HCT02	IC2
1	74HCT74	IC3

### Miscellaneous:

1	25-way male sub-D connector with angled pins, for PCB mounting	K1
1	25-way female sub-D connector with angled pins, for PCB mounting	K2
1	32.768 kHz quartz crystal	X1
1	3.6V NiCd battery	Batt.1
1	ABS enclosure; size approx. 120x70x30mm	
1	Printed circuit board	910006
1	Diskette with control software	ESS1621

both sides. This means that you have to bend a couple of small metal brackets with the aid of tweezers. After turning the main PCB, you should have access to the sound generator connections. Run a wire from pin 14 of the Yamaha chip to pin 16 of the printer connector, and another wire from pin 40 of the Yamaha chip (+5 V) to pin 17 of the printer connector. This completes the modification. Re-assemble the computer.

## Software

As usual, hardware is never complete without the appropriate software. The clock unit described here is supported by a control program on disk, which may be ordered through our Readers Services. The disk contains the ready-to-go desk accessory for the clock, as well as the source listing used to compile the machine code. As already mentioned, this listing is intended for those of you who want extra features for the clock, such as a programmable alarm. You may also want to use the 50-byte non-volatile RAM area in the RTC chip.

The source code can be converted into a control program with the aid of, for example, the Mark-Williams C compiler. This is not strictly required, though, since you can simply copy the control program on the floppy disk (supplied by us) to your system disk. Every time the computer is switched on, the program will automatically copy the RTC data to the system clock. Now, is that up-to-date or not? ■

# STEPPER MOTOR BOARD

## PART 1: PC INSERTION CARD AND CONTROL SOFTWARE

**Getting a stepper motor to work properly invariably seems to require either a lot of discrete electronics, or an expensive dedicated integrated circuit. However, since the actual commands for stepper motors are almost always supplied by a computer, it is a challenging idea to economize on the hardware, and have the software do the work.**

H. Kolter

**S**TEPPER motor controls are available in many shapes and sizes, ranging from complex to ultra-simple, and based on a variety of integrated circuits, including the MC3479, the L297/298 and the TDA1024, all of which have been used in projects described in this magazine. By contrast, the control described here is not based on any of these ICs. None the less, it is versatile, simple to build and relatively cheap.

The circuit described has evolved as part of a PC-controlled professional milling machine that accepts CNC-format data to the Gerber standard. CNC stands for computer numerical control.

### The concept

The above application was aimed at developing a complete milling machine for very ac-

curate processing of aluminium, steel and plastic workpieces. When the project was initiated, there was the choice between (1) 'intelligent' motor control with relatively simple control software, and (2) a simpler controller with powerful, complex, software. To ensure the best possible results in regard of speed and accuracy of the system, the first option requires the motor control to be geared accurately to the specific features of the milling machine.


The second option has the advantage that changes to the machine, or extensions, are easier to support with appropriate software extensions. Since the electronics and the milling machine were developed roughly at the same time, the choice of the stepper motor control was clearly in favour of the second option: simple hardware and complex software.

In practice, the computing power required for the system can only be provided by a PC-AT or a compatible machine with a clock speed of at least 16 MHz. The computer program consists of an interpreter that reads drill and fraise data produced to the Gerber standard, and converts these into stepper motor commands.

The interpreter uses a configuration file that contains various system parameters such as the type of stepper motor (bipolar or unipolar, rotation per step, maximum step rate, etc.), and the main properties of the milling machine (spindle pitch, number of idle steps on spindle reversal, etc.). These parameters can be changed easily and allow the control system to be rapidly 'customized' for a particular application.

In line with the different functions, the electronics are divided into two parts. One part is an insertion card for IBM PCs, the other a larger board, which is fitted external to the PC, and contains the power drivers.

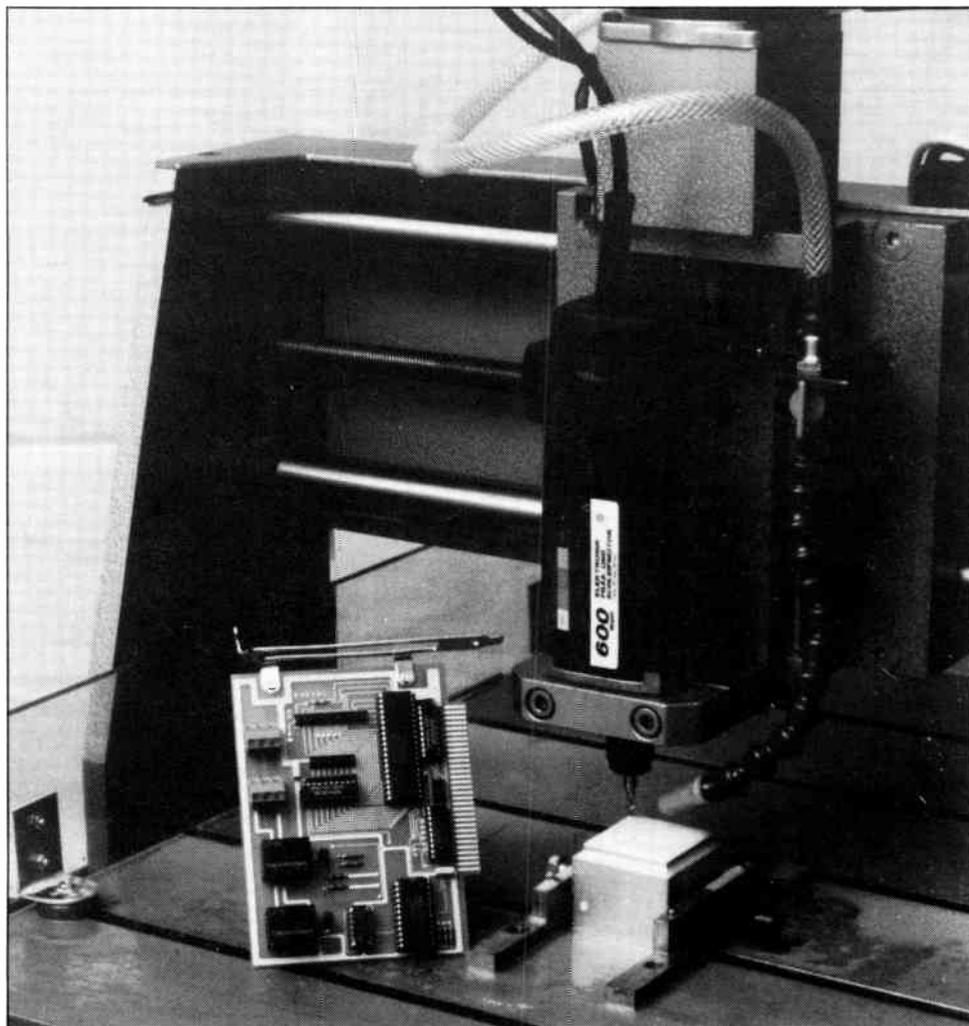The PC insertion card described here is basically a digital I/O card based on the familiar 8255 PPI (programmable peripheral interface) from Intel. The 'half-size' insertion



card offers 24 input/output lines, and has an additional timer/counter IC Type 8253, a quartz oscillator and two relays. The quartz oscillator makes the timing of the I/O card independent of the computer speed. The two relays have changeover contacts and are suitable for switching mains loads.

The power driver board (to be described in part 2 of this article) has a fairly large power supply and 16 optocouplers that afford electrical isolation between the computer and the stepper motors. TTL buffers are provided between the optocouplers and the 16 power drivers. These buffers are also used to drive a LED-based readout that signals the active status of all stepper motor windings. The readout will be found particularly useful when a machine is first connected, or during program debugging.

### Circuit description

The PC interface shown in Fig. 1 is a more or less standard design based on the 8255 PPI. Apart from the data and address signals, the extension card uses a few control signals on the IBM slot, IOWR which indicates write activity in the I/O memory area, IORD which has the same function for read operations, and, of course, RESET. The extension card is powered by the computer via the extension bus.

The datalines are buffered with a 74LS245 octal bidirectional driver. The buffered datalines are connected to the PPI (the 8255) and the PIT (programmable Interface Timer/counter; the 8253). A single PAL (programmable array logic), IC3, handles all address decoding. It uses address line A3 through A9 and the IORD and IOWR signals to generate chip select signals CS0, CS1, CS2 and CS3, and in addition the enable signal and the direction control signal for the databus buffer, IC2.

The I/O lines of ports A and B of IC1 are available on a double row PCB pin header, K2. Port C is connected to the outputs of the programmable timer, IC5. Connections PC4 and PC5 switch the two relays via darlington transistors T1-T2. In most cases, a value of 1 kΩ will be adequate for R5 and R6. These resistors may need to be made smaller, however, when the relays do not come on reliably. The minimum value of R5 and R6 is 330 Ω.

PPI line PC3 has a special use here as it is connected to an external emergency switch that stops the entire system. Normally, PC3 is held at +5 V by a pull-up resistor, R4. The two remaining port lines, PC6 and PC7, are not used here.

The internal block diagram of the 8253 counter/timer is shown in Fig. 2. The three 16-bit counters, numbered 0, 1 and 2, are identical and can be preset to count down. The counters operate independently and can be programmed separately. The counter values can be read from the 8253 without blocking the clock signal. The preset values are loaded with the aid of four control words stored in the control word register. Since this has only one address, two bits, SC0 and SC1,

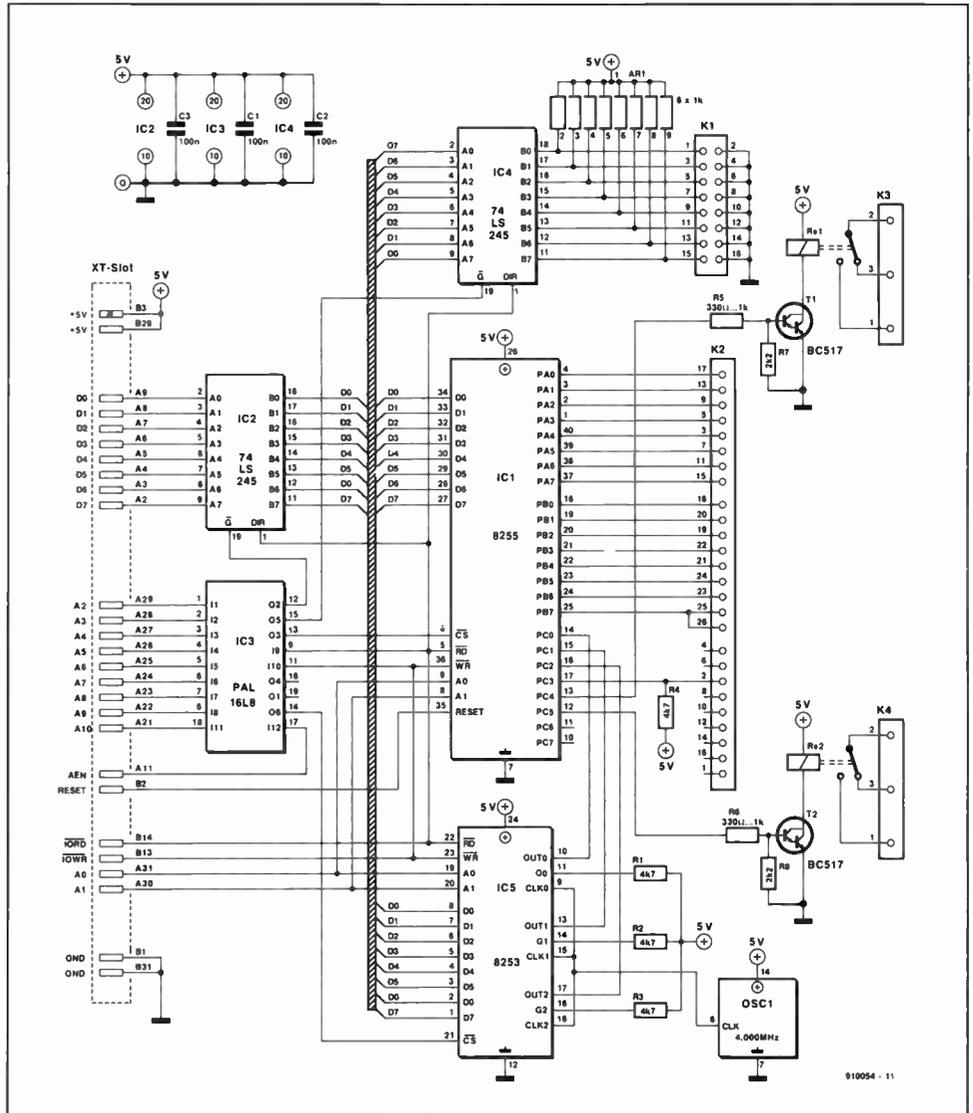


Fig. 1. Circuit diagram of the PC insertion card.

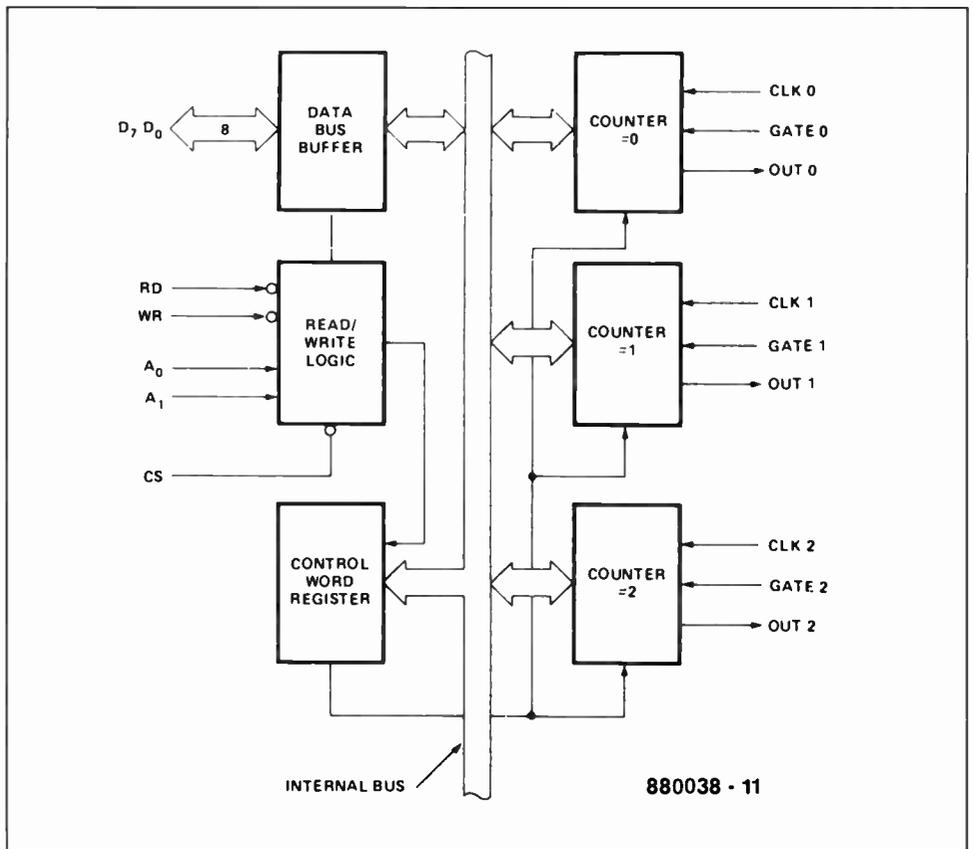


Fig. 2. Block diagram of the 8253 Programmable Peripheral Interface (PPI).

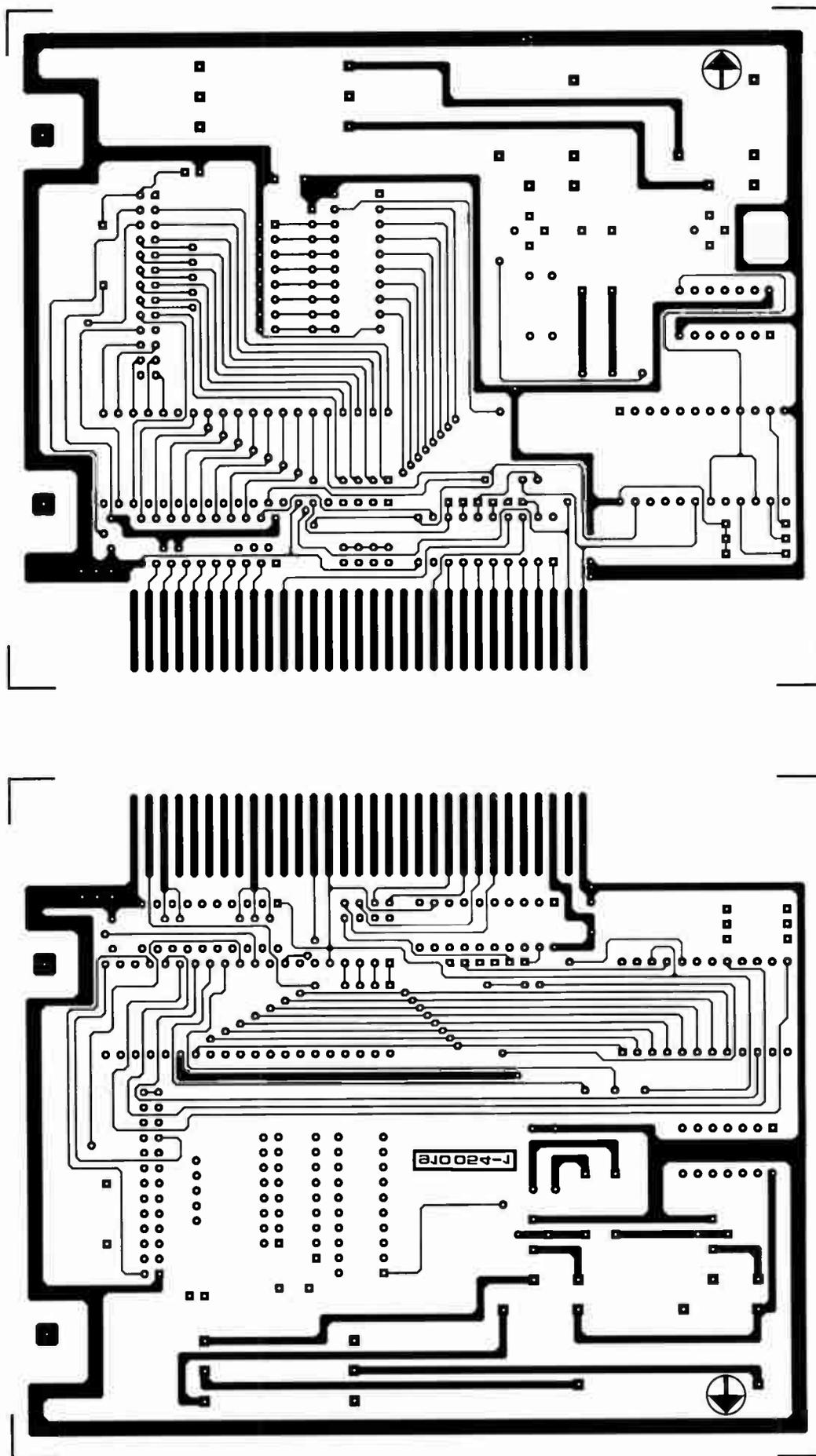


Fig. 3a. Track layouts of the component side and the solder side of the PC insertion card.

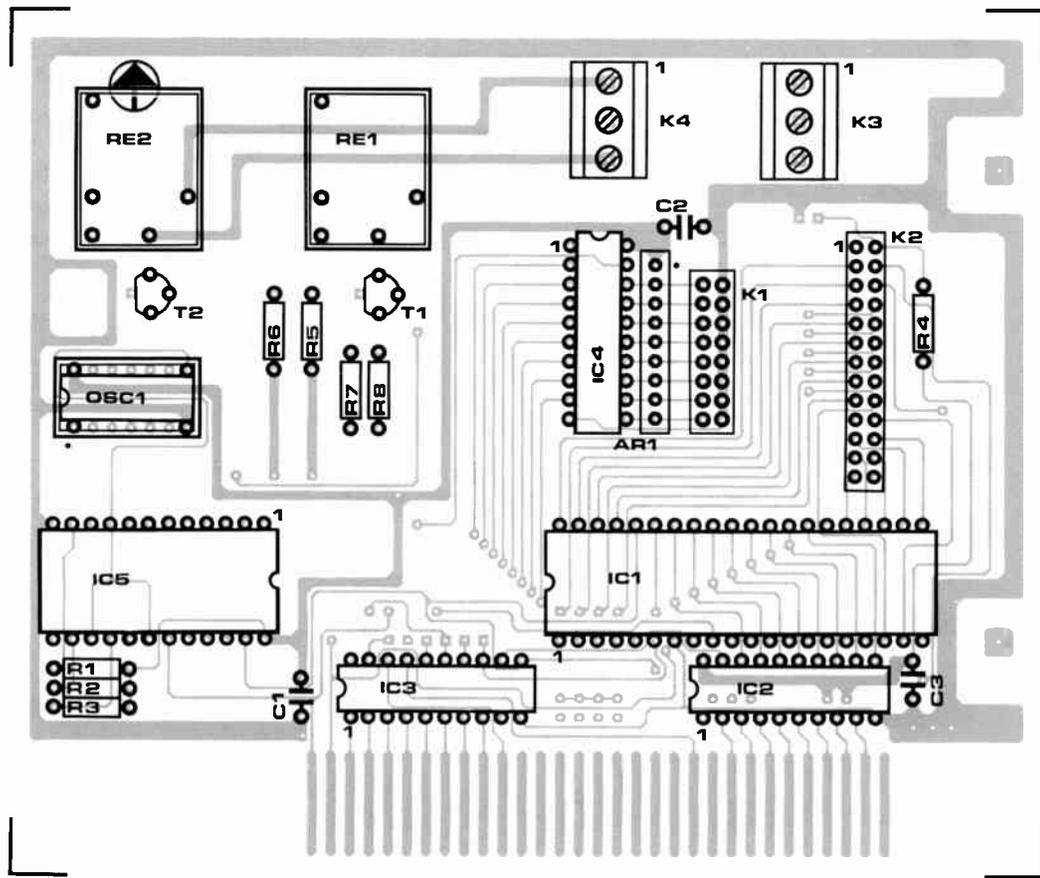


Fig. 3a. Component mounting plan of the PC insertion card.

## COMPONENTS LIST

### Resistors:

4	4k $\Omega$ 7	R1 - R4
2	1k $\Omega$ (see text)	R5;R6
2	2k $\Omega$ 2	R7;R8
1	8x4k $\Omega$ 7 array	AR1

### Capacitors:

3	100nF	C1;C2;C3
---	-------	----------

### Semiconductors:

1	8255	IC1
2	74LS245	IC2;IC4
1	16L8 (ESS 6011)	IC3
1	8253	IC5
2	BC517	T1;T2

### Miscellaneous:


1	4-MHz oscillator block	Osc1
2	PCB-mount 5V changeover relay	Re1;Re2
1	16-way 2-row PCB pin header	K1
1	26-way 2-row PCB pin header	K2
2	3-way PCB terminal block	K3;K4
1	printed-circuit board	910054-1

indicate the counter for which the control word is intended.

Returning to the circuit diagram in Fig. 1, the CLK0 through CLK3 inputs of the 8253 are supplied with a 4-MHz clock signal generated by oscillator block OSC1. All three gate (Gx) inputs of the counter/timer are

tied to +5 V via pull-up resistors.

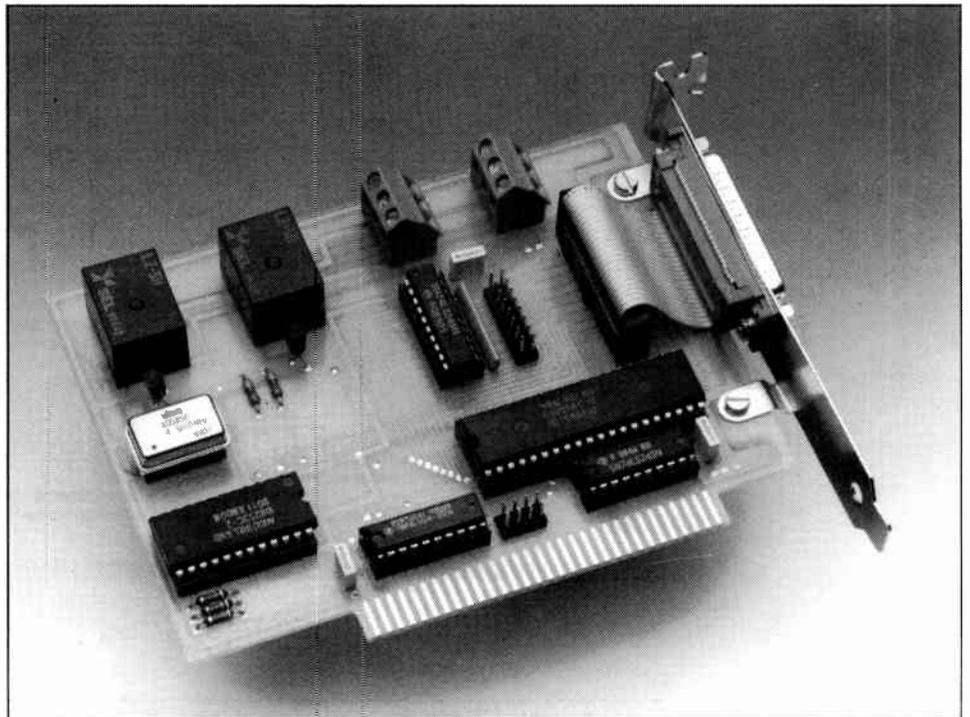The 8253 is programmed to operate as a frequency divider. Depending on the preset value, a counter divides the oscillator frequency down to a particular value, for instance, 100 Hz, which is then passed to PPI port C. By loading different counter preset



values, the step duration of the stepper motors is made independent of the computer's speed.

IC4, a 74LS245, forms an 8-bit input port which is used to signal the status of a set of end switches fitted on the milling machine. The eight input lines of the port are held at +5 V with the aid of pull-up resistors. The end switches wired to K1 should, therefore, connect to ground when active.

The address assignment of the ports on the insertion card, and their functions, are summarized in Tables 1 and 2.

## Construction

Populating the double-sided through-plated board (Fig. 3) should not cause difficulty. To make sure the card remains secure in the PC slot, you will need to secure it to a metal bracket as found on other insertion cards. Here, it is best to use (or make) a bracket with a relatively large vertical clearance that allows the two flatcables and the relay wires to pass.

Switch the computer off, fit the I/O card into a free slot, and secure the card to the metal frame at the rear of the PC. Switch on the PC, and check that a frequency of 4 MHz is present at pins 9, 15 and 18 of IC5. In case the PC will not boot up with the I/O card inserted, you are probably faced with a short-circuit on the board, or a faulty IC.

The data in Tables 1 and 2, and a few lines of BASIC or Pascal, allow the card to be checked for correct operation. For instance, reading address [base+8] (IC4) should return 1111 1111<sub>2</sub>, which equals FF<sub>H</sub>, or 256 decimal. Next, connect two or three jumpers to K1 to pull the input datalines logic low. Run the read test again, when the result should match the set bit pattern (a jumper produces a logic low).

Next, test the PPI by writing to the control register at address [base+3] (0DE3<sub>H</sub>). Set all ports to output, then make all port lines logic high. The relays should come on.

The scope of this article does not allow a more detailed description of the way in which the 8255 and the 8253 are programmed. Fortunately, plenty of literature is available that covers the practical use of these ICs in great detail.

## Software

A number of different, fairly complex computer programs are required before the fraising machine can be made to work. The first step in making a fraised product is to draw it with the aid of a CAD program, such as AutoCAD or AutoSketch, and save the drawing file in the DXF format. Next, a program called AutoPack-II is used to convert the DXF file into a format suitable for further processing. AutoPack-II is a 2½-dimension version of the 3-dimension program Auto-Pack. None the less, AutoPack-II allows you to view the workpiece in 3-D to the ISO standard. Also, all side views of the workpiece can be displayed at the same time, and the program is capable of calculating the

### G routines supported by CNC-DIN All dimensions in mm, DIN 66025.

#### Example of Syntax:

10 G00 x17.34 y200.0

20 G01 x10.90 y20.90

%	start of program
'	remark
G00	Target point direction characteristic (x, y, z). Move to target point. Fraise carrier speed.
G01	Straight interpolation of target point (x, y, z). Fraise from current point to indicated target point. Fraise speed.
G02	Circle interpolation, clockwise. (xakt, yakt, x, y, i, j) current point (xakt, yakt), target point (x, y), centre of circle (i, j). Fraise an arc based circle information, from current point to target point.
G03	Circle interpolation, anti-clockwise. See G02.
G04	Spindle idle time. (f) idle time in seconds.
M58	Switch of spindle motor relay.
M59	Switch on spindle motor relay.
M08	Switch on pump for drill coolant.
M09	Switch off pump for drilling coolant.
G90	All absolute data.
G91	All incremental data.
G94	Spindle shift speed in mm/min. (x, y, z) speed indication for single spindle.
M30	end of program.

Fig. 4. Overview of Gerber commands supported by the CNC-DIN converter program.


curve described by the fraise. This curve is called fraise equidistant because the radius of the fraise itself is taken into account.

The fraise file generated by AutoPack-II consists of a set of so-called Gerber commands. The actual control software for the milling machine is a converter called CNC-DIN. Written in C, it reads the Gerber data and converts these into commands for the stepper motor board described here. CNC-DIN is available from the author, and allows you set a number of parameters related to the hardware. These parameters include the type of stepper motor used (2-phase or 4-phase), the number of steps per revolution, etc. The parameters and their settings are stored in a configuration file that can be modified as required for your own hardware. Figure 4 lists the G (Gerber-) functions to DIN-66025 that are supported by CNC-DIN. □

Part 2 of this article will describe the motor driver board. Tables 1 and 2 mentioned here will be included in Part 2.
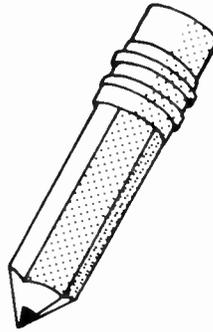
#### Note:

The program CNC-DIN mentioned in this article is available from  
Kolter Elektronik • Steinstrasse 22 • W-5042  
Erfstadt • Germany. • Telephone: +49 (2235)  
76707, Fax: +49 (2235) 72048.



# Subscriber Services

Complete the applicable section(s) below and mail to:  
 Elektor Electronics USA  
 PO Box 876  
 Peterborough, NH  
 03458-0876

## WOULD YOU LIKE TO ... SUBSCRIBE?

YES! Just check the appropriate boxes in the "renew" section and fill in name and address.

### RENEW?

Fill in the appropriate sections below. For faster service use your mailing label and subscriber number.

- 1 year at \$28
- 2 years at \$50
- Check/MO enclosed
- Charge MC/VISA

Canada add \$8 per year postage  
 Remit in US \$ only

SUBSCRIBER NUMBER

NAME \_\_\_\_\_

STREET & NO \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

MC/VISA \_\_\_\_\_

EXP \_\_\_\_\_

### CHANGE YOUR ADDRESS?

Fill in your new address to the right and old address and subscriber number above.



MY NEW ADDRESS:

NAME \_\_\_\_\_

STREET & NO \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

### GIVE A GIFT?

What a thoughtful idea! Fill out your name and address above, the recipient's name and address to the right. We'll even send a gift card announcing your gift.



NAME \_\_\_\_\_

STREET & NO \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

### TELL YOUR FRIENDS ABOUT US?

Print their names and addresses below or photocopy this form for them. We'll take care of the rest.

NAME \_\_\_\_\_

NAME \_\_\_\_\_

STREET & NO \_\_\_\_\_

STREET & NO \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

### COMPLAIN ABOUT YOUR SUBSCRIPTION?

Yes, it sometimes happens. We try to avoid it at all costs, but if you have a problem, we want to know. Call or write with all pertinent information.



YOU CAN CALL US

(603) 924-9464

Subscription Department  
 9-4 Business Days

Answering Machine

All Other Hours

FAX: (603) 924-9467

24 Hours



# TERMS OF BUSINESS

## PRICING

Prices, except as noted, include shipping in the continental USA. The minimum order is \$10. A \$2 service charge will be added to orders of less than \$10. Prices are subject to change as our costs change. WE RESERVE THE RIGHT TO MAKE PRICE CHANGES WITHOUT NOTICE.

## TELEPHONE ORDERS

Telephone orders are welcome between the hours of 9:00 a.m. and 4:00 p.m. EDT, Monday-Friday. Orders for parts are to be made on the ORDER FORM provided. Payment for telephone orders is by MC/VISA only. Our TELEPHONE ORDER NUMBER IS (603) 924-6371 or 924-6526. Our answering machine for MC/VISA orders during non-business hours is (603) 924-6371. FAX: (603) 924-9467 (24 hours).

## PAYMENT

All remittances **MUST BE IN US FUNDS DRAWN ON A US BANK**. Payment for telephone orders must be made by MasterCard or VISA. Mail order payment may be made by MC/VISA, money order, cashier's check or personal check. If payment is made by personal check, allow up to 2 weeks for clearance before order is shipped. Should check be returned for any reason, there will be a \$10 charge.

## SHIPPING

Unless noted, freight is prepaid by Old Colony. All orders shipped USPS first class mail or by UPS.

Allow two to three weeks for delivery. Please inquire about appropriate funds for special handling (UPS next day or second day). UPS requires a street address. If you cannot receive UPS delivery, please include an extra \$2 for insured service via Parcel Post. We cannot accept responsibility for safety or delivery of uninsured Parcel Post shipments. **Absolutely no COD shipments.**

## BOOKS, RECORDINGS, CDs, and SOFTWARE

The shipping/handling charge for the US is \$2.00, plus 75¢ each additional item. In Canada, please add \$4.50 for the first item, 75¢ each additional. **No returns.** According to the Connecticut Dept. of Revenue Services, Regulation #27, Section 12-426-27, in order to sell software to residents of Connecticut, we must register with the department as well as collect taxes for the state from the purchaser. We regret to inform our customers that we will not sell software to anyone from Connecticut, as it will prove to be too costly and burdensome.

## OVERSEAS ORDERS

For orders to be shipped outside North America, add 20% to the total order to cover shipping.

## RETURNS

If you wish to return all or part of an order for any reason, please call or write first. If we are in error, correction will be made promptly, without charge.

## WARRANTY

We warrant that all items sold conform to the qual-

ity and specifications set forth. We make no representations. We accept no responsibility whatever for further use by the customer. We accept no monetary liability in excess of the original cost or replacement of the material if originally defective or damaged in transit.

## COPYRIGHT

All drawings, photographs, articles, printed circuit boards, EPROMs, software, and cassettes published in our books or magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of *Elektor Electronics USA* in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature.

Notwithstanding the above, printed circuit boards may be produced for private and personal use without prior permission.

## LIMITATION OF LIABILITY

*Elektor Electronics USA* shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connection with, the supply of goods or services by *Elektor Electronics USA* other than to supply goods as described, or at the option of *Elektor Electronics USA*, to refund the purchaser any money paid in respect of the goods. ■

# BOOKS FROM ELEKTOR ELECTRONICS USA

## 301 CIRCUITS

This book follows the theme of the first in this series, *300 Circuits* (now out of print). It contains over 300 assorted circuits first published in the 1979, 1980, 1981 summer issues of *Elektor Electronics*.

The circuits range from the simple to the more complex and are described and explained in straightforward language. The book is a comprehensive source of ideas and construction projects for anyone interested in electronics.

ISBN 0-905705-12-2

BKAA11 Price \$12.50

## 302 CIRCUITS

The popularity of this book is shown by its having been reprinted no fewer than three times. It offers a selection of the most interesting articles from the 1982, 1983, 1984 summer issues of *Elektor Electronics*.

In it you will find circuits for audio and video; car, cycle, and motorcycle; home and garden; receivers and aeriads; hobbies and games; measuring and testing; oscillators and generators; current sources and power supplies; microcomputers and music electronics; and a miscellany of other interesting subjects.

ISBN 0-905705-25-4

BKAA12 Price \$12.50

## 303 CIRCUITS

Like its predecessors, *303 CIRCUITS* offers a comprehensive collection of practical ideas, concepts, and developments in the gamut of electronics. Unlike its predecessors, the book is arranged in 11 subject sections to make it easier for the reader to find that long-sought circuit.

In well over 300 pages, the book offers 32 Audio and Hi-Fi projects; 14 circuits for Car and Bicycles; 43 Computer & Microprocessor circuits; 11 Electrographic projects; 24 HF and VHF circuits; 16 circuits for a number of hobbies and pastimes; 54 projects for Home and Garden; 29 Power Supply circuits; 29 circuits for Test and Measurement equipment; nine TV and Video projects; as well as 42 Design Ideas.

ISBN 0-905705-62-2

BKAA13 Price \$15.90

## DATA SHEET BOOK 2

Like its predecessor (now out of print), this book offers concise, relevant, and rapidly accessible information, which is both practical (e.g., the pin-out of a device) and informative.

The book contains data on integrated circuits as well as on discrete transistors and diodes. Moreover, it gives an introduction to fast (HCMOS) devices and a review of the new symbolic logic as laid down in British Standard BS3939:Section 21 (IEC Standard 617-12).

The final part of the book deals with a number of computer chips, such as memory devices (including programming information for these) and I/O circuits. This section also includes data on a number of non-digital discrete and integrated devices, such as op amps, as well as on some microprocessor peripherals (e.g., the 6522 VIA, the 6580 ACIA, and the 8355A PPI).

ISBN 0-905705-27-0

BKAA14 Price \$16.50

## DATABOOK 3: PERIPHERAL CHIPS

This book lists the most important design data of peripheral chips whose type numbers and functions relate them unambiguously to a microprocessor in the same family. All listed devices form part of families based on widely used microprocessors or microcontrollers. Their most evident application will therefore be in conjunction with the associated microprocessor. This should, however, not be taken to mean that a peripheral cannot be used in another ap-

plication. Far from it, as witness the familiar type MC146818A real-time clock and the type MC6845 cathode-ray tube controller. It deserves a place on the bookshelf of anyone concerned with the design, maintenance and servicing of microprocessor-controlled electronic equipment.

ISBN 0-905705-30-0

BKAA15 Price \$17.95

## MICROPROCESSOR DATA BOOK

This book has come about because of a need by *Elektor Electronics* engineers, technicians, and editorial staff of a ready reference work on the most important microprocessors. This implies that it does not only contain information on the latest devices, such as the transputer, but also on older, well-established types, such as the Z80 and the 6800.

A general description, hardware block schematic, software structure, DC characteristics, and instruction sets are given for over 70 microprocessors. To prevent the book from becoming unwieldy (and to keep costs down), timing diagrams and AC characteristics have, however, been omitted. The detailed information on all manufacturers mentioned will, however, enable any additional information to be obtained quite readily.

Included in the book are, among others, the 68000 series; the 6502 family; the Z80, 8080, and 8085; Intel's 8086, 80186, 80188, 80286, and 80386; the NS32XXX series, and the INMOS transputers.

ISBN 0-905705-28-9

BKAA16 Price \$17.90

## DATABOOK 4: PERIPHERAL CHIPS II

This final volume in *Elektor Electronics' Microprocessor Data Book* series deals with general peripheral chips that, at least as far as their type-coding is concerned, do not belong to a specific family of microprocessors. There are so many of these, however, that only a portion of them can be dealt with in one book. Those contained in this collection have been chosen carefully on the basis of their practical application and frequency of use. Complete data are given for coprocessors from the 80 series (AMD, Cyrix, ITT, Intel, Weitek); real-time clocks from MEM, OKI, Statek, National Semiconductor, and Dallas Semiconductor; transmitters and receivers of serial interfaces RS232, 422, 423, 485 from Motorola, Newport Components, Maxim, Texas Instruments, National Semiconductor, Dallas Semiconductor, and Linear Technology; UARTS, DUARTS, and QUARTS (i.e., programmable ICs intended for data transfer); and the CS8221 set of ICs from Chips & Technology that are used in a great number of PC mother boards (also included is the data sheet of associated software LIM 4.0 for the management of the Extended Memory System).

Apart from the actual data, the book contains much other useful information, such as comparisons between and second sources for all important IC families; addresses of manufacturers and their representatives; and overviews of all peripheral chips (including many that could not be included in this book) that are available from various manufacturers.

ISBN 0-905705-32-7

BKAA17 Price \$17.95

## SPECIALS!

BKAAZ/1 BKAA11, 12, 13: all 3 for \$35 (Save \$5.95!)

BKAAZ/2 BKAA14, 15, 16, or 17: **ANY THREE** for \$45 (Save \$7.35!)

(BE SURE TO SPECIFY)

BKAAZ/S Complete *Elektor* library: all 7 for \$85 (Save \$26.20!)

These books are all available direct from *Elektor Electronics USA* through the Readers Services, from a number of bookshops and electronics retailers in the US and Canada, and from selected bookshops throughout the world. Special prices are those of *EEUSA* only.

# KELVIN Electronics

# DISCOUNT CENTER

## MULTIMETERS



**KELVIN PRO 400**  
 KELVIN DIGITAL MULTIMETERS  
**KELVIN 100 Basic** ..... \$19.95  
**KELVIN 150 Basic+** ..... \$29.95  
 with Transistor Hfe Test  
**KELVIN 200 Advanced** \$39.95  
 w/Transistor Hfe, Capacitor Test  
**KELVIN PRO 400** ..... \$69.95  
 w/Transistor, Capacitor, AC/DC Test, Logic, 20 MHz Freq Counter, Durable

Kelvin Meters backed by a 2 Yr Warranty - Parts & Labor  
**Protective Case** ..... \$4.95  
 For Model 100, 150, 200  
**Protective Case** ..... \$9.95  
 For Model Pro 400

## FLUKE



FLUKE 87

BEST BUY ..... **NEW Series II**

FLUKE 70 Series II	\$ 63
FLUKE 73 Series II	\$ 89
FLUKE 75 Series II	\$127
FLUKE 77 Series II	\$149
FLUKE 79 Series II	\$169
FLUKE 83	199
FLUKE 85	\$229
FLUKE 87	\$269
FLUKE 86	\$367
FLUKE 88	\$423
FLUKE 8062A	\$329
FLUKE 8060A	\$395
FLUKE 8010A	\$329
FLUKE 8012A	\$359
FLUKE 8050A	\$439
FLUKE 37	\$249
FLUKE 45	\$579

## SCOPES


**20 MHz SCOPE** ..... \$375  
 with Built-in Component Tester  
 2 Yr Warranty - Parts & Labor  
**HITACHI V523 50 MHz** ..... \$995  
 50 MHz, Analog 2 Ch, 1 mV, Delay Sweep, DC Offset, Vert Mode Trigger  
 3 Yr Warranty - Parts & Labor



**HITACHI V523**

**SCOPE PROBES**  
 60 MHz, X1 & X10 ..... \$19.95  
 150 MHz, X10 ..... \$39.95

## BREADBOARDS

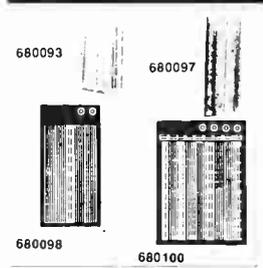

Stock No.	Post	Contacts	YOUR COST
680093	0	500	\$ 4.25
680097	0	840	\$ 5.95
680098	2	1380	\$11.75
680100	4	2390	\$22.95

**WIRE JUMPER KIT**  
 Pre-cut, Pre-Stripped  
**140 Piece Set** ..... \$ 4.75  
**350 Piece Set** ..... \$ 7.75

## COMPONENTS

Stock No.	TYPE	YOUR COST
600021	555 TIMER	\$ .20 EA
600029	556 DUAL TIMER	\$ .40 EA
600039	LM566 PLL FUNCTION GENERATOR	\$ .60 EA
600018	741C OP-AMP INTERNALLY COMPENSATED	\$ .30 EA
600026	1458 OP-AMP DUAL 741C OP-AMP DIP	\$ .35 EA
630041	2N2222	\$ .18 EA
630383	PN2222	\$ .08 EA
600023	7805 VOLTAGE REG	\$ .36 EA

SILICON CONTROLLED RECTIFIER (Similar to GE C106C1) 4.0 AMP, 100 PIV  
 600014 \$ .89 EA \$ .79 EA 50+

## TEST ACCESSORIES

**IC CLIPS**  
 SOLDER TYPE SPRING LOADED  
 Stock No. COLOR COST 25. Qty

990104	BLACK	\$.65 ea	\$ .50 ea
990105	RED	\$.65 ea	\$ .50 ea

**IC TEST LEAD SET**  
 5 COLOR CODED 18" LEADS WITH MINIATURE HOOK-ON PROD AT BOTH ENDS  
 Stock No. YOUR COST 3+ Qty

990108	\$8.95 ea	\$8.25 ea
--------	-----------	-----------

**DOUBLE BANANA JACK**  
 Stock No. YOUR COST 3+ Qty

600056	\$2.30 ea	\$2.07 ea
--------	-----------	-----------

**FEMALE BNC TO DUAL BANANA PLUG**  
 Stock No. YOUR COST 3+ Qty

990103	\$2.95 ea	\$2.75 ea
--------	-----------	-----------

**DUAL BANANA BINDING POST TO MALE BNC PLUG**  
 Stock No. YOUR COST 3+ Qty

600058	\$5.95 ea	\$4.95 ea
--------	-----------	-----------

**BNC TEST CABLES**  
 3 FT. MALE TO MALE  
 Stock No. YOUR COST 3+ Qty

990101	\$3.45 ea	\$2.95 ea
--------	-----------	-----------

## RESISTORS

5% Tolerance Carbon Film  
**CALL WITH YOUR VALUE**  
 1/4 W \$2 / 200 Pcs  
 1/2 W \$3 / 200 Pcs  
 1 W \$1.30 / 10 Pcs  
 2 W \$1.70 / 10 Pcs

## LUBES/CLEANERS

**WD-40 LUBRICANT**  
 12 OZ. CAN Stock No. 870001 \$2.95 ea  
**\$2.80 ea / 3+ Qty**

**MINUS BLUE SHOWER CLEANER & DEGREASER**  
 24 OZ. SPRAY CAN Stock No. 510007 \$8.95 ea  
**\$8.25 ea / 3+ Qty**

**MINUS 62 INSTANT CHILLER SPRAY**  
 15 OZ. SPRAY CAN Stock No. 510004 \$5.95 ea  
**\$5.25 ea / 3+ Qty**

**TRANSISTOR SILICON GREASE**  
 1 OZ. TUBE Stock No. 510002 \$5.50 ea  
**\$4.95 ea / 3+ Qty**

## WALL TRANSFORMERS

**WALL TRANSFORMER**

STOCK NO.	TYPE - Female	YOUR COST
220069	9V DC/500 mA	\$3.95 ea
220068	12V DC/500 mA	\$4.25 ea

**MALE JACK**  
 Stock No. TYPE  
 370048 2.1 mm Male \$ .49 ea \$ .39 / 10+

## BATTERIES

**Duracell / Eveready 9V Battery**  
 \$1.95 ea  
 \$1.75 ea/10+

**9V Battery SNAP & HOLDER**  
 Snap \$ .15 ea \$ .10 ea/100+  
 Holder \$ .20 ea \$ .10 ea/100+

**HEAVY DUTY NI-CAD RECHARGEABLE BATTERIES**

STOCK NO.	TYPE	YOUR COST
220039	AAA	\$3.30 ea
220025	AA	\$2.85 ea
220027	C	\$6.00 ea
220037	D	\$6.00 ea
220038	9V	\$8.90 ea

**NI-CAD BATTERY CHARGER**  
 4 Cell Charger for AAA, AA, C, D or 9V  
 Stock No. YOUR COST  
 220035 SPECIAL \$9.95 ea

## LED CENTER

**SPECIAL - RED LED** - \$.05 ea / 1000+ Qty  
**JUMBO LED**  
 TYPE - T 1 3/4, 5mm  
 STOCK NO. YOUR COST 1000. Qty

260020	Red	\$.06 100.	\$.05
260027	Green	\$.08 100.	\$.07
260026	Yellow	\$.08 100.	\$.07

**LED HOLDER**  
 for T 1 3/4 SIZE, BLACK  
 Stock No. 250019 \$ .10 ea 100+ Qty  
 \$ .06 ea 1000+ Qty

**0.37" 7 SEGMENT LED READOUT**  
 STOCK NO. TYPE COST  
 260022 ANODE \$ .95 ea \$ .75 ea  
 260090 Cathode \$1.25 ea \$ .99 ea

**0.6" 7 SEGMENT LED READOUT**  
 STOCK NO. COST  
 260021 Jumbo \$1.15 ea 20. Qty  
 \$2.99 ea

**TIL 311 4 X 7 HEXIDECIMAL DISPLAY**  
 STOCK NO. YOUR COST  
 260066 \$9.75 ea

**RED LED DISPLAY** 20 PIN  
 STOCK NO. Color YOUR COST 10. Qty

260058	Red	\$1.99 ea	\$ .79 ea
260088	Green	\$1.99 ea	\$ .79 ea
260089	Yellow	\$1.99 ea	\$ .79 ea

**MOVING SIGN DISPLAY**  
 for Fabricating Your Own Moving Sign Display  
 50 mm  
 Stock No. A 260091 \$5.95 ea  
 \$5.45 ea 20+

## TOOLS

**MINIATURE LONG NOSE PLIERS**  
 4 1/2" LONG, INSULATING HANDLES, DROP FORGED STEEL, FULLY MILLED JAWS  
 Stock No. 520021 \$3.95 ea  
**\$3.50 ea / 6+ Qty**

**MINIATURE DIAGONAL CUTTER**  
 4 1/2" LONG, CUSHIONED HANDLES, DROP FORGED STEEL  
 Stock No. 520023 \$3.95 ea  
**\$3.45 ea / 6+ Qty**

**MILLER WIRE CUTTER & STRIPPER**  
 MODEL 100 ADJUSTABLE GRIPPING HANDLES INSULATED  
 Stock No. 520010 \$2.95 ea  
**\$2.66 ea / 6+ Qty**

**DELUXE WIRE STRIPPER & CRIMPING TOOL**  
 CRIMPS REGULAR & INSULATED TERMINALS CUTS & STRIPS WIRE  
 Stock No. 520065 \$3.60 ea  
**\$3.42 ea / 6+ Qty**

## PROJECT PARTS

**Project Speaker**  
 2" 8 Ohm, 1 Watt  
 Stock No. 350009  
**59¢**

**Project BUZZER**  
 2" 9 Volt DC, 80 db  
 Stock No. 680089  
**\$1.59 ea**  
**\$1.39 ea / 10+ Qty**

**HORN ALARM**  
 Loud Penetrating Sound  
 Stock No. 640001  
**\$ .75 ea**  
**\$.69 ea / 10+ Qty**

**DC MOTOR**  
 for SOLAR/ROBOTIC  
 Stock No. 852211  
**\$ .50 ea**  
**\$.45 ea / 20+ Qty**

**SOLAR CELL**  
 3/4" x 1 1/2", 45V DC, 150 mA, wired/encased  
 Stock No. 260056  
**\$ 6.95 ea**

**XENON STROBE TUBE**  
 260050  
**\$2.95 ea**  
**\$2.50 ea / 20+ Qty**

**TRIGGER COIL**  
 for XenonStrobe Tube  
 Stock No. 320037  
**\$1.25 ea**  
**\$.89 ea / 20+ Qty**

**INFRARED LED**  
 IR Pair, LED infrared transmitter and receiver  
 Stock No. 260061  
**\$2.79 ea**

**NEON LAMP**  
 NE2, 2" Lead  
 Stock No. 260003  
**\$ .15 ea**  
**\$.12 ea / 100+ Qty**

**PHOTO CELL**  
 CADMIUM SELENIDE  
 Stock No. 260017  
**\$.99 ea**

**PHOTO CELL**  
 SULPHIDE  
 Stock No. 260018  
**\$.99 ea**

**PUSH-BUTTON SWITCH**  
 PUSH-ON, PUSH-OFF  
 Stock No. 270021  
**\$.55 ea**  
**\$.49 ea / 100+ Qty**

**SUB-MINIATURE MOMENTARY SWITCH**  
 Stock No. 990002  
**\$.35 ea**  
**\$.28 ea / 100+ Qty**

**MINIATURE TOGGLE SWITCH**  
 Stock No. 270034  
**\$.90 ea** Type - SPST  
**\$.79 ea / 50+ Qty**

CIRCLE RESPONSE CARD OR WRITE FOR OUR CATALOG FULL OF WHOLESALE PRICED ITEMS.

**KELVIN ELECTRONICS**

1991 CATALOG

120 PAGES  
FULL OF DISCOUNTS

**OVER 10,000 ITEMS IN STOCK**

ELECTRONIC COMPONENTS & TECHNOLOGY ACTIVITIES

VISA & MASTERCARD ACCEPTED  
\$20 MINIMUM ORDER

**KELVIN** Electronics

7 Fairchild Ave. Plainview, NY 11803

Call: 1 (800) 645-9212

1 (516) 349-7620

FAX: 1 (516) 349-7830

In 1988, **Madisound Speaker Components** processed 20,000 orders.

<b>VIFA</b>	<b>DYNAUDIO</b>	<b>PERFECT LAY</b>
<b>FOCAL</b>	<b>MB QUART</b>	<b>SEWINDER</b>
<b>PHILIPS</b>	<b>AUDAX</b>	<b>ELECTROVOICE</b>
<b>EUROPA</b>	<b>PEERLESS</b>	<b>SLEDGEHAMMER</b>
<b>MOREL</b>	<b>SOLEN</b>	
<b>KEF</b>	<b>ETON</b>	

Doesn't your hobby deserve these fine product lines?



**MADISOUND SPEAKER COMPONENTS**  
8608 University Green  
Box 4283, Madison, WI 53711  
Phone (608) 831-3433 FAX: (608) 831-3771

**RED LASERS** - New Diode Lasers and Puled Helium-Neon Lasers. **DANGER:** All lasers are retinal damage hazards. He-Ne lasers are high-voltage hazards. User's finished product must comply with DHEW Radiological Health requirements. Purchaser agrees to assume all responsibility for damages.

**NEW 670nm 3.5mw SUB-MINIATURE LASER DIODE POINTERS WITH COATED GLASS OPTICS.** MODULE only without case \$229. BRASS 7/16d x 5 3/16 w/2 AAAs \$279. TITANIUM 3/8d x 5 9/16 w/2 AAAs \$329. STATE-OF-THE-ART!

**FULLED HE-NE LASERS WITH ENCAPSULATED POWER SUPPLIES.** 1mw 24vdc, 5vdc enable, cylindrical \$60; with 115vac to 24vdc kit \$80. 1mw 12vdc or 115vac, always enabled, cylindrical \$100. 2.5mw 115vac, always enabled, 5vdc enabled, or open circuit enabled, exposed tube \$150.

Illustrated catalog \$2. First Class Insured Postage free. 10-day satisfaction guaranteed. 1-year guarantee on new, 30-day on pulled items. California residents add 7%. VISA and MASTER CARD accepted.

**PALEOSYSTEMS**, 11152 Lucerne Avenue, Culver City, CA 90230. Voice (be prepared to leave message) or FAX (213)-559-6661.

# BATTERIES

BATTERIES FOR ALL YOUR POWER REQUIREMENTS

NICKEL CADMIUM  
SEALED LEAD ACID  
GEL CELLS  
MERCURY  
ALKALINE  
LITHIUM



**E.H. YOST & COMPANY**  
7344 TETIVA ROAD  
SAUK CITY, WISCONSIN 53583  
TELEPHONE (608) 643-3194  
FAX # (608) 643-4439

## THE R.F. CONNECTION

213 North Frederick Ave. #11  
Gaithersburg, MD 20877

ORDERS 1-800-783-2666  
INFO 301-840-5477 FAX 301-869-3680  
"THIS LIST REPRESENTS ONLY A FRACTION OF OUR HUGE INVENTORY"  
"Specialist in RF Connectors and Coax"

Part No.	Description	Price
PL-259/USA	UHF Male Phenolic, USA made	\$ 70
PL-259/ST	UHF Male Silver Teflon USA	1.50
UG-21D/U	N Male RG-8, 213, 214 Delta	3.25
UG-21B/U	N Male RG-8, 213, 214, Kings	5.00
9913/PIN	N Male Pin for 9913, 9086, 8214 Fits UG-21 D/U & UG-21 B/U's	1.50
UG-21D/9913	N Male for RG-8 with 9913 Pin	3.95
UG-21B/9913	N Male for RG-8 with 9913 Pin	5.75
UG-146A/U	N Male to SO-239, Teflon USA	6.00
UG-83B/U	N Female to PL-259, Teflon USA	6.00


PRICES DO NOT INCLUDE SHIPPING  
PRICES SUBJECT TO CHANGE  
VISA, MASTERCARD, ADD 4%  
UPS C.O.D. ADD \$3.50 PER ORDER

# MARK V - YOUR AMPLIFIER SOURCE!

▲ Indicates the level of difficulty in the assembling of our Products. ▲ Beginner ▲▲ Intermediate ▲▲▲ Advanced ★ Fully Assembled

### 300 W HI-FI POWER AMPLIFIER (MONO)

TA-3600 ▲▲▲

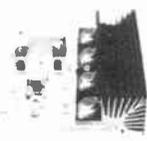

Complete Kit: \$85.00  
Assembled & Tested: \$110.00

Power output: 300 watts RMS into 8 ohms, 540 watts music power into 8 ohms • Frequency response: 10Hz to 20 KHz • Total harmonic distortion: Less than 0.05% • Intermodulation distortion: Less than 0.05% • Sensitivity: 1 V rms at 47K • Power requirements: 60 to 75 VDC at 8 amp • Dimensions: 8" x 7 1/2" x 2 1/4"

### 100W + 100W NEW CLASS A DC STEREO PRE AND MAIN AMP

TA-1500 ▲▲▲



Complete Kit: \$73.70  
Assembled & Tested: \$95.81

Power output 80 watts per channel into 8 ohms 100 watts per channel into 4 ohms • Total harmonic distortion: Less than 0.03% Frequency response: Aux input: 5 to 50,000 Hz +0.2dB -2 dB • Frequency response: Power amplifier section: DC to 200 KHz • Sensitivity: Phono 2.5 mV @ 47 K Aux: 150 mV @ 47 K Mic: 6 mV @ 10 K Output: Tape: 150 mV @ 47 K Preamp: 1V @ 600 ohms • Power transformer: 26V to 32 V AC x 2 @ 6 A (Mark V Model 001) • P.C. Board Dimensions: 10.5 x 6.13 x 2.25 • Heat sink: 5.13 x 2.63 x 3 (Each) Use rack mount cabinet LG 1924 or LG 1925

### VIDEO/AUDIO SURROUND SOUND PROCESSOR

SM-333 ▲▲▲★



Complete Kit: \$65.00  
Assembled & Tested: \$75.00

Frequency response: 20 Hz to 20KHz • Total harmonic distortion: Front channel: 0.05% • Rear channel: Less than 0.25% • Input signal voltage: 0.1 to 3.5V • Output: Front channel: 0.1 to 3.5V • Rear channel: 6.6V • Delay time: 5 to 50 milliseconds • Input impedance: 47 K • Power requirements: 100-120VAC, 60 Hz • Dimensions: 14.2" wide, 4.82" deep, 2.1" high

### 120W MOSFET POWER AMPLIFIER (MONO)

TA-477 ▲▲




Complete Kit: \$68.00  
Assembled & Tested: \$85.00

T. H. D.: Less Than 0.007% • Power output: 120 watts into 8 ohms RMS • Frequency response: 8 Hz to 20KHz, +0-0.4 dB • Sensitivity: 1V • Power requirements: 55 VDC @ 3amps May use Mark V Model 003 Transformer

### 80W + 80W PURE DC STEREO MAIN POWER AMPLIFIER

TA-802 ▲▲

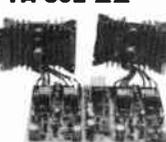

Complete Kit: \$45.94  
Assembled & Tested: \$59.72

Power output: 80 watts per channel into 8 ohms Total harmonic distortion: Less than 0.05% at rated power Intermodulation distortion: Less than 0.05% at rated power Frequency response: DC to 200 KHz, -0.3dB, @ 1 watt Power requirements: 30 VAC x 2 @ 6 amp. May use Mark V model 001 transformer P.C. Board: 8-1/2" x 5" x 1-1/8" Heat sink: 5-1/8" x 2-5/8" x 3" (Each)

### 60W + 60W Stereo Power Amplifier (with Mic. input)

SM-302 ▲▲▲★



Complete Kit: \$67.00  
Assembled & Tested: \$78.00

Frequency response: 20Hz to 20 KHz • Total harmonic distortion: < 0.1% • Power output: 60W per channel into 8 ohm load • 33W per channel into 4 ohm load • Input sensitivity: Mic 10mv • Hi 380mv • Lo 640 mv • Signal to noise ratio: Better than 70 db • Power consumption 100W Dimension 360 mm x 75 mm x 200 mm

### DC FET SUPER CLASS "A" PRE-AMP

TA-2200 ▲▲▲




Complete Kit: \$47.70  
Assembled & Tested: \$58.24

Total harmonic distortion: Over all (from AUX) less than 0.01% • Frequency response (at rated output): Overall (AUX to PRE OUTPUT) 10 to 100,000 Hz + 1dB • Input sensitivity and impedance (1,000 Hz for rated output) • Phono: 47 ohms 2mV • Output level: Rated Output (0.01% Total harmonic distortion) • Preamp output: 1.3V (20 V MAX, 0.1% T.H.D.) • Recording output: 130 mV • Power requirements: Power voltage: AC 36V x 2 0.2A • Dimensions: 9 x 5.88 x 1"

### 100 W DYNAMIC CLASS A MAIN POWER AMPLIFIER


TA-1000A ▲▲

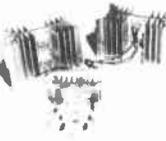

Complete Kit \$59.69  
Assembled & Tested \$80.58

Power output: 100 watts into 8ohms, 125 watts into 4 ohms • Frequency response: 10Hz to 100 KHz • Total Harmonic distortion: Less than 0.008% • Signal to noise ratio: Better than 80 dB • Sensitivity: 1V • Power requirements: 35 to 45 VDC @ 3 amp. • May use Mark V Moel 001 transformer • PCB Dimensions: 5.38" x 3.38" x 1.2" • Heat sink: 5.13" x 2.63x3" (Each)

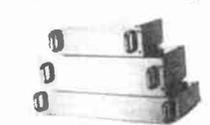Rack Mount Metal Cabinets with aluminium panel are suitable for many projects and most of our kits.



We provide transformers for most of our Mark V amplifier kits.

# MARK V ELECTRONICS, INC.

8019 E. Slauson Ave. Montebello, CA 90640




OUTSIDE CA 1-800-423-FIVE (orders only)  
IN CA 1-800-521-MARK  
ORDER BY FAX (213) 888-6868

FREE CATALOG & INFORMATION (213) 888-8988

We accept major Credit Cards: Money Orders, Checks and C.O.D. Orders. C.O.D. fee is \$5.00. Minimum order is \$20.00. • We ship by UPS ground inside US (min \$4.00) and ship by US mail outside US. Please call our sales department for orders over 2 lbs. or foreign orders. • All assembled units have a 30 days warranty • Quality or Volume discount available upon request • Residents of CA please add sales tax 6.5% • All merchandise are subject to prior sale. Prices are subject to change without prior notice. We are not responsible for typographical errors.

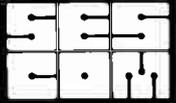Business & Showroom hours: (Pacific Time)  
Mon. thru Fri. 9:30 am to 5:00 pm  
Sat. 10:00 am to 5:00 pm



**SESCOM INC.**  
PARTS DIVISION  
2100 WARD DR.  
HENDERSON, NV 89015 -9998

# THE "FIRST CHOICE" FOR CONSTRUCTORS HARDWARE

## Rack Chassis



MODEL #.	DESCRIPTION (Width x Depth x Height)	PRICE \$
1RU5	19 x 5 x 1.75 in. (482.6 x 127 x 44.45mm)	28.00
1RU7	19 x 7 x 1.75 in. (482.6 x 177 x 44.45mm)	30.00
1RU10	19 x 10 x 1.75 in. (482.6 x 254 x 44.45mm)	32.00
2RU5	19 x 5 x 3.50 in. (482.6 x 127 x 88.9mm)	30.00
2RU7	19 x 7 x 3.50 in. (482.6 x 177.8 x 88.9mm)	32.00
2RU10	19 x 10 x 3.50 in. (482.6 x 254 x 88.9mm)	34.00
3RU5	19 x 5 x 5.25 in. (482.6 x 127 x 133.35mm)	38.00
3RU7	19 x 7 x 5.25 in. (482.6 x 177.8 x 133.35mm)	40.00
3RU10	19 x 10 x 5.25 in. (482.6 x 254 x 133.35mm)	42.00

The above rack chassis are made of .063 aluminum. The front and rear panels are clear brushed anodized. All hardware is included. Assembly Required.

## Metal Cabinets



MODEL #.	DESCRIPTION (Width x Depth x Height)	PRICE \$
MC-1A	4 x 3 x 2 in. (101.6 x 76.2 x 50.8mm)	15.00
MC-2A	6 x 3 x 2 in. (152.4 x 76.2 x 50.8mm)	17.00
MC-3A	8 x 3 x 2 in. (203.2 x 76.2 x 50.8mm)	19.00
MC-4A	4 x 5 x 3 in. (101.6 x 127 x 76.2mm)	17.00
MC-5A	6 x 5 x 3 in. (152.4 x 127 x 76.2mm)	19.00
MC-6A	8 x 5 x 3 in. (203.2 x 127 x 76.2mm)	21.00
MC-7A	4 x 7 x 4 in. (101.6 x 177.8 x 101.6mm)	19.00
MC-8A	6 x 7 x 4 in. (152.4 x 177.8 x 101.6mm)	21.00
MC-9A	8 x 7 x 4 in. (203.2 x 177.8 x 101.6mm)	23.00

The above cabinets are made of .063 aluminum. The front and rear panels are clear brushed anodized. All hardware and rubber feet are included. Assembly Required.

## Punch Kits and Punches



Model #.	Description	Price \$
HP-1	5 JR TOOL KIT	49.00
HP-3	BENCH MOUNT	15.00
PD-1	ROUND 1/16"	6.00
PD-2	ROUND 5/64"	6.00
PD-3	ROUND 3/32"	6.00
PD-4	ROUND 7/64"	6.00
PD-5	ROUND 1/8"	6.00
PD-6	ROUND 9/64"	6.00
PD-7	ROUND 5/32"	6.00
PD-8	ROUND 11/64"	6.00
PD-9	ROUND 3/16"	6.00
PD-10	ROUND 13/64"	6.00
PD-11	ROUND 7/32"	6.00
PD-12	ROUND 15/64"	6.00
PD-13	ROUND 1/4"	6.00
PD-14	ROUND 17/64"	6.00
PD-15	ROUND 9/32"	6.00
PD-16	SQUARE 1/8"	66.90
PD-17	SQUARE 5/32"	66.90
PD-18	SQUARE 3/16"	66.90
PD-19	REC 1/8 x 3/16"	66.90
PD-20	REC 1/8 x 7/32"	66.90
PD-21	REC 1/8 x 15/64"	66.90
Model #.	Description	Price \$
HP-2	XX TOOL KIT	129.75
HP-4	BENCH MOUNT	15.00
PD-30	ROUND 1/16"	9.50
PD-31	ROUND 5/64"	9.50
PD-32	ROUND 3/32"	9.50
PD-33	ROUND 7/64"	9.50
PD-34	ROUND 1/8"	9.50
PD-35	ROUND 9/64"	9.50
PD-36	ROUND 5/32"	9.50
PD-37	ROUND 11/64"	9.50
PD-38	ROUND 3/16"	9.50
PD-39	ROUND 13/64"	9.50
PD-40	ROUND 7/32"	9.50
PD-41	ROUND 15/64"	9.50
PD-42	ROUND 1/4"	9.50
PD-43	ROUND 17/64"	9.50
PD-44	ROUND 9/32"	9.50
PD-45	ROUND 19/64"	9.50
PD-46	ROUND 5/16"	9.50
PD-47	ROUND 21/64"	9.50
PD-48	ROUND 11/32"	9.50
PD-49	ROUND 23/64"	9.50
PD-50	ROUND 3/8"	9.50
PD-51	ROUND 25/64"	9.50
PD-52	ROUND 13/32"	9.50
PD-53	ROUND 27/64"	9.50
PD-54	ROUND 7/16"	9.50
PD-55	ROUND 29/64"	9.50
PD-56	ROUND 15/32"	9.50
PD-57	ROUND 31/64"	9.50
PD-58	ROUND 1/2"	6.00
PD-59	ROUND 33/64"	6.00
PD-60	ROUND 17/32"	6.00
PD-61	SQUARE 1/8"	66.90
PD-62	SQUARE 5/32"	66.90
PD-63	SQUARE 3/16"	66.90
PD-64	REC 1/8 x 3/16"	83.10
PD-65	REC 1/8 x 1/4"	83.10
PD-66	REC 1/8 x 5/16"	83.10
PD-67	REC 1/8 x 3/8"	83.10
PD-68	REC 1/8 x 11/32"	75.10

## Rub-On Letters

MODEL #.	DESCRIPTION	PRICE \$
LT-1	CAPITAL LETTERS HELVETICA 14 pt.	3.95
LT-2	LOWER CASE LETTERS HELVETICA 14 pt.	3.95
LT-3	NUMBERS HELVETICA 14 pt.	3.95
LT-4	CAPITAL LETTERS HELVETICA 10 pt.	3.95
LT-5	LOWER CASE LETTERS HELVETICA 10 pt.	3.95
LT-6	NUMBERS HELVETICA 10 pt.	3.95
LT-7	CAPITAL LETTERS HELVETICA 6 pt.	3.95
LT-8	LOWER CASE LETTERS HELVETICA 6 pt.	3.95
LT-9	NUMBERS HELVETICA 6 pt.	4.95
LT-10	DIAL MARKING (DOTS)	4.95
LT-11	DIAL MARKING (LINES)	3.95
LT-12	WORDS (AUDIO) HELVETICA 10 pt.	3.95
LT-12	WORDS (AUDIO) HELVETICA CAPS 6 pt.	3.95
LT-12	WORDS (AUDIO) HELVETICA UPPER AND LOWER CASE 6 pt.	3.95

### TERMS AND CONDITIONS

**MINIMUM ORDER:** The minimum order is \$10.00.

**TERMS:** Terms of payment on open accounts are NET 30 days from date of invoice.

**C.O.D. ORDERS:** Payment must be made in cash, money order or certified check. A company check will be accepted only if previously approved by the factory.

**OPEN ACCOUNTS:** SESCOM, INC. extends credit to government agencies and industrial accounts with a good published rating. Firms may apply for an open account by requesting a credit application from the Accounts Receivable department. All orders are shipped C.O.D. until credit is approved. (Please allow 4 to 6 weeks to open a new account.) We accept Mastercard and Visa.

**PRICES:** Catalog prices are NET, FOB destination shipped UPS ground. UPS BLUE and REO LABEL service available at an additional charge. UPS BLUE is \$10.00 and UPS REO is \$20.00. PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE. Orders are invoiced at prices in effect at the time of shipment unless specifically quoted otherwise. SESCOM, INC. shall add any existing or future Federal, State, or Local taxes that may apply. We reserve the right to apply the above if your Tax Exemption Certificate is not on file with our office.

**SHORTAGE OR DAMAGE:** All claims for shortage or shipment error must be made within 10 days after receipt of the shipment. Our liability is limited to the material value on the invoice.

**MERCHANDISE RETURN:** A prior written authorization from SESCOM, INC. must be issued before return of any material. Instructions for returning the material will accompany the authorization. Material that is returned without authorization or is over 90 days will carry a restocking fee of a minimum of 25% to a maximum 100%. Special order items will not be accepted for return.

**SUBSTITUTIONS:** We reserve the right to substitute higher quality (but identical part) at our option, unless you specify no substitution at the time of the order.

## SHEET METAL PUNCHES

MODEL #.	HOLE SIZE	PILOT HOLE	PRICE \$
PUNCH 1	3/8"	ROUND 3/16"	8.95
PUNCH 2	7/16"	ROUND 7/16"	8.95
PUNCH 3	1/2"	ROUND 7/32"	8.95
PUNCH 4	9/16"	ROUND 7/32"	11.95
PUNCH 5	5/8"	ROUND 7/32"	11.95
PUNCH 6	11/16"	ROUND 7/32"	11.95
PUNCH 7	3/4"	ROUND 7/32"	11.95
PUNCH 8	13/16"	ROUND 7/32"	11.95
PUNCH 9	7/8"	ROUND 7/32"	11.95
PUNCH 10	1"	ROUND 5/16"	12.95
PUNCH 11	1-1/16"	ROUND 5/16"	12.95
PUNCH 12	1-1/8"	ROUND 5/16"	12.95
PUNCH 13	1-3/16"	ROUND 5/16"	12.95
PUNCH 14	1-1/4"	ROUND 5/16"	13.95
PUNCH 15	1-3/8"	ROUND 5/16"	13.95
PUNCH 16	1-1/2"	ROUND 5/16"	15.95
PUNCH 17	1-5/8"	ROUND 5/16"	20.95
PUNCH 18	1-3/4"	ROUND 5/16"	23.95
PUNCH 19	2-5/8"	ROUND 1/2"	59.95
PUNCH 20	11/16"	SQUARE 1/2"	31.95
PUNCH 21	3/4"	SQUARE 1/2"	35.95
PUNCH 22	1"	SQUARE 1/2"	45.95
PUNCH 23	21/32 x 5/16"	REC. 1/2"	45.95
PUNCH 24	*THURST RACES FOR PUNCHES (FOR EASIER PUNCHING) 1" thru 1-3/4"		9.95



• UPS GROUND SHIPPING IS FREE WITHIN THE CONTINENTAL LIMITS OF THE USA •  
TOLL FREE ORDERING IN ALL 50 STATES AND CANADA

FOR ADDITIONAL INFORMATION CONTACT:

**SESCOM INC. - PARTS DIVISION, 2100 WARD DR., HENDERSON, NV 89015-9998**  
FOR ORDERS: 1-800-634-3457 • FAX: 1-702-565-4828 • REGULAR BUSINESS: 1-702-565-3400  
BUSINESS HOURS: 8:00 A.M. TO 4:00 P.M. PACIFIC TIME, MONDAY THRU FRIDAY

## Component Parts

TRANSISTORS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
2N3904	NPN T092	12	10	.08
2N3906	PNP T092	12	10	.08
2N2102	PNP T039	80	67	.54
2N4037	PNP T039	90	75	.60
PN2219A	NPN T0237	40	34	.28
PN2905A	PNP T0237	40	34	.28

DIODES:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
1N34A	GE DIODE	.17	.15	.13
1N4001	SI DIODE	13	11	.10
1N4148	SI DIODE	.09	.07	.06

LINEAR INTEGRATED CIRCUITS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
LF351N	SINGLE OP-AMP	.60	.54	.48
LF353N	DUAL OP-AMP	1.05	.95	.84
NE5534N	SINGLE OP-AMP	1.28	1.15	1.02
NE5534AN	LOW NOISE SINGLE OP-AMP	1.80	1.62	1.44
NE5532N	DUAL OP-AMP	1.85	1.67	1.48

I C SOCKETS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
SOC-8	8 PIN TIN	11	10	.09
SOC-14	14 PIN TIN	12	11	.10
SOC-16	16 PIN TIN	13	12	.11
SOC-18	18 PIN TIN	15	14	.13
SOC-20	20 PIN TIN	19	16	.15


CARBON FILM RESISTORS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
CF + VALUE	5% 1/4W	.05	.02	.01
ALL STANDARD VALUES 1.0 OHM THRU 1.0M OHM				

POTENTIOMETERS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
10KA	10K AUDIO TAPER	2.00	1.80	1.60

CONNECTORS:				
PART NO.	DESCRIPTION	1-9	10-99	100 +
XLR F CA	3 PIN CABLE FEMALE	3.20	2.88	2.56
XLR M CA	3 PIN CABLE MALE	2.75	2.48	2.20
XLR F CH	3 PIN CHASSIS FEMALE	3.60	3.24	2.88
XLR M CH	3 PIN CHASSIS MALE	2.60	2.40	2.08
1/4 ST	1/4" STEREO JACK	.97	.87	.78
3.5 ST	3.5mm STEREO JACK	.97	.87	.78
RCA	RCA PHONO JACK CHASSIS	.65	.59	.52

CAPACITORS: Axial Lead Electrolytic				
PART NO.	DESCRIPTION	1-9	10-99	100 +
AC 1/50	1uf - 50V	.38	.35	.30
AC 4.7/25	4.7uf - 25V	.39	.35	.30
AC 10/25	10uf - 25V	.39	.35	.30
AC 47/25	47uf - 25V	.46	.42	.37
AC 100/25	100uf - 25V	.69	.62	.55
AC 220/35	220uf - 35V	.97	.87	.78
AC 470/35	470uf - 35V	1.34	1.21	1.07
AC 1000/35	1000uf - 35V	2.22	2.00	1.78

CAPACITORS: Radial Lead Electrolytic				
PART NO.	DESCRIPTION	1-9	10-99	100 +
RC 1/50	1uf - 50V	.26	.24	.21
RC 4.7/25	4.7uf - 25V	.28	.26	.23
RC 10/25	10uf - 25V	.31	.28	.25
RC 47/25	47uf - 25V	.39	.35	.28
RC 100/25	100uf - 25V	.41	.36	.33
RC 220/35	220uf - 35V	.61	.55	.49
RC 470/35	470uf - 35V	.99	.90	.80
RC 1000/35	1000uf - 35V	1.27	1.15	1.02

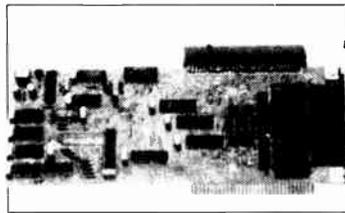


### IBM PC SERVICE CARD

This card was developed for assistance in the field of service, development and test. The card is used as a bus-extension to reach the measurement points very easy. It is also possible to change cards without having a "hanging computer".

Ready Assembled Module

**\$145**

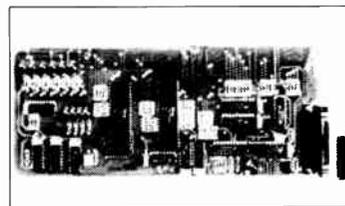


### IC TESTER FOR IBM-PC/XT/AT

With the ELV IC tester logic function tests can be carried out on nearly all CMOS and TTL standard components, accommodated in DIL packages up to 20 pin. The tester is designed as an insertion card for IBM-PC/XT/AT and compatibles. A small ZIF test socket PCB is connected via a flat band cable. Over 500 standard components can be tested using the accompanying comprehensive test software. Complete Kit including Textool socket, connectors, sockets, Flat band cable, PCB, Software.

Ready Assembled Module

**\$200**

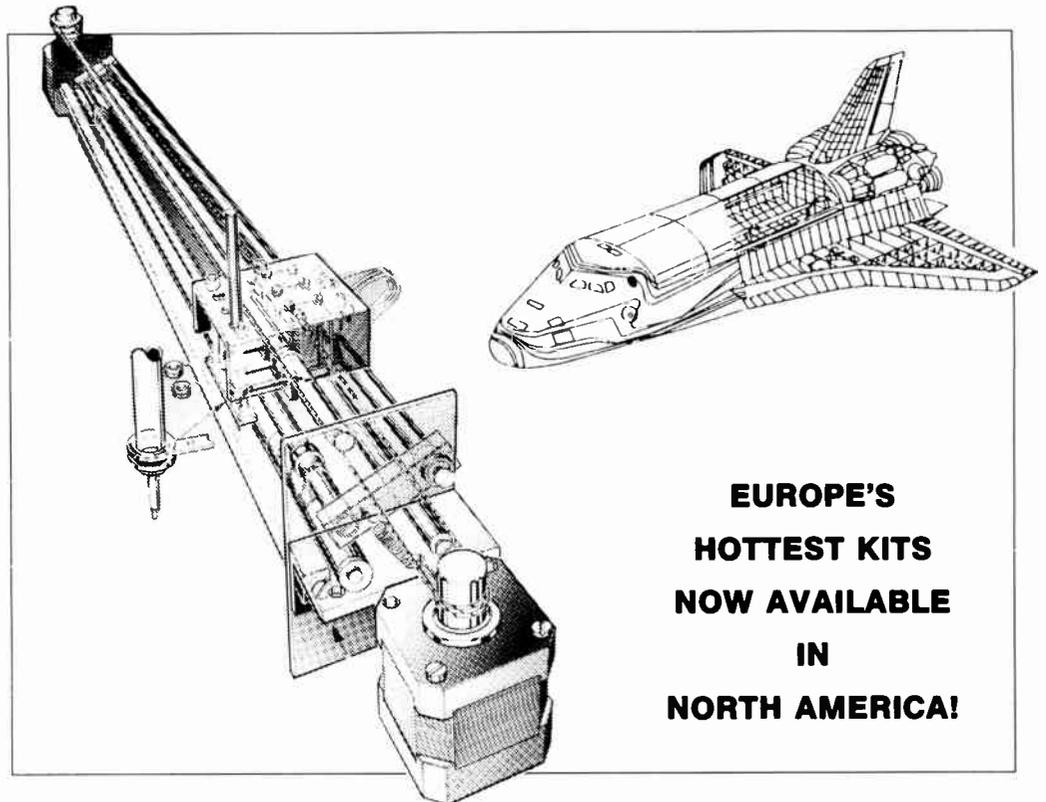


**EUROPE'S  
HOTTEST KITS  
NOW AVAILABLE  
IN  
NORTH AMERICA!**

### PLOTTER MARK-II

completely reworked version: see *Elektor Electronics* March 1990.

- \* Max. width 50 cm.
- \* All mechanical parts supplied ready-drilled, filed and tapped, so get going at once.
- \* Complete kit, including 2 stepper motors, 3 pen lift solenoids, HPGL software on disk (IBM), stepper motor control board

100.100 **\$275**

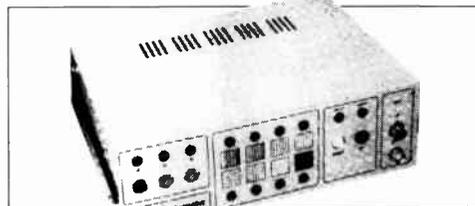

### COLOUR TEST PATTERN GENERATOR

A PAL-compatible colour video source that supplies a number of test patterns for aligning television sets.

A test pattern generator is virtually indispensable for troubleshooting in television sets because it supplies a video signal that is known to be stable, and thus easily displayed and synchronized on an oscilloscope.

Inc. case and front


100.111 **\$175**



### ELEKTOR P.C. i/o card

\* 220.007 **\$175**

WorldRadioHistory

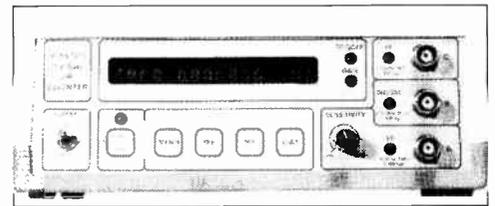

### MICROPROCESSOR-CONTROLLED FREQUENCY METER

A professional grade multi-purpose frequency meter, designed by Elektor Electronics, that can be built by many at affordable cost. Described in *Elektor Electronics* December 1984, January & February 1985. U665B-based prescaler.


- Frequency meter: 0.01 Hz to 1.2 GHz.
- Pulse duration meter: 0.1 to 100 s.
- Pulse counter: 0 to 10<sup>9</sup> pulses
- Period meter: 10 ns to 100 ns
- Sensitivity: Input A: 10 mV<sub>rms</sub> (Z<sub>in</sub> = 2 MΩ); Input B: TTL or CMOS compatible (Z<sub>in</sub> = 25 kΩ); Input C: prescaler input: 10 mV<sub>rms</sub> (Z<sub>in</sub> = 50 Ω).
- Auto-ranging and completely menu-driven.
- 6 or 7 digit accuracy.

Kit includes power supply, prescaler and enclosure.....100.112 **\$300**

## BASIC COMPUTER

With Intel 8052AH-BASIC

100.117

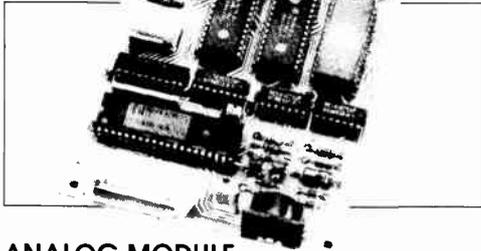**\$160**

### ANALOG MODULE

eps 880162

100.113 **\$80**

### DIGITAL MODULE

eps 880163


100.114 **\$55**

### ADRESSECODER

eps 880159

100.115 **\$45**

## S-VHS/CVBS-TO-RGB CONVERTER

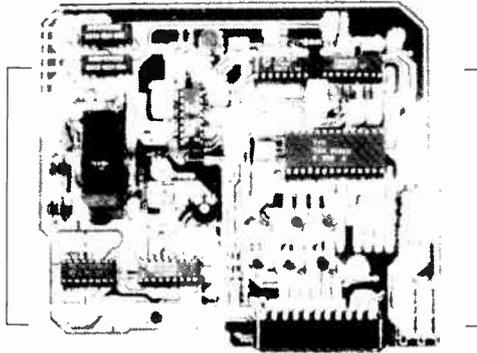

Following last month's introduction into the main characteristics of the Super-VHS system, we close off the article with details of a practical converter circuit that allows an S-VHS-VRC or camcorder to be connected to the RGB inputs of a colour TV or monitor. The circuit presented here forms a state-of-the-art approach to all-analogue picture standard conversion, and is based on the latest in IC technology available for this purpose.

220.039 **\$150**

THE HAGUE HOLLAND


### AVAILABLE FROM:

## OLD COLONY SOUND LAB

PO Box 243, Dept E91  
Peterborough, NH 03458 USA  
24-Hour Lines:

Tel. (603) 924-6371 FAX (603) 924-9467

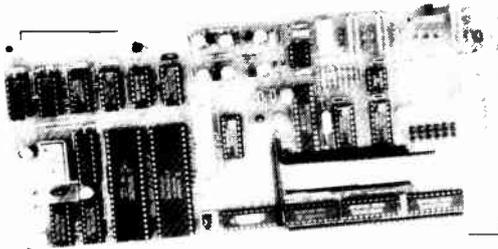- Check, money order, MC/VISA accepted.
- Please allow 6-8 weeks for delivery.
- **SHIPPING:** Airmail shipping to USA included in price. Others: Please inquire.
- **CUSTOMS:** USA residents may be required to pay 5-10% customs duty. Others may vary.



## MULTIFUNCTION MEASUREMENT CARDS FOR PCs

The high-performance insertion card described in this article allows your IBM PC-XT, PC-AT or 100% compatible to measure direct voltage at 12-bit accuracy, as well as frequency and a host of other parameters related to pulse-shaped signals. The accuracy and versatility afforded by the card are of a level associated with much more expensive, industrially rated products. The menu-driven control software developed for this exciting project allows you to keep tabs on up to eight voltages quasi-simultaneously, while up to eight remaining inputs can be used for time-related measurements including frequency, duty factor and pulse duration, not forgetting the event counter. Connected to the sensors and timing devices of your choice, this card turns a PC into a powerful central controller in a complex measurement and control system.

220.040 **\$225**


### SPECIAL PARTS SERVICE

We are the no. 1 suppliers of hard-to-find components for Elektor Electronics projects. Always contact us first if you see an unfamiliar component. Items include analogue & digital ICs (HCT, SMD), precision resistors (1%, 0.1%), capacitors (MKT/styrolflex), inductors (Neosid, Toko), transducers, enclosures (Telet, OKW) and quartz crystals.

FOR FURTHER INFORMATION,  
PLEASE SEND A BUSINESS-SIZE  
SASE TO OLD COLONY SOUND LAB  
(ADDRESS ABOVE), ATTN: MEEK IT.

## MICROPROCESSOR-CONTROLLED TELEPHONE EXCHANGE

The telephone exchange presented here allows up to eight pulse-dialling telephone sets to be connected, and has an option for connecting calls to or from an external (trunk) telephone line. The unit is controlled by the popular 8052-based BASIC computer we introduced a few years ago.

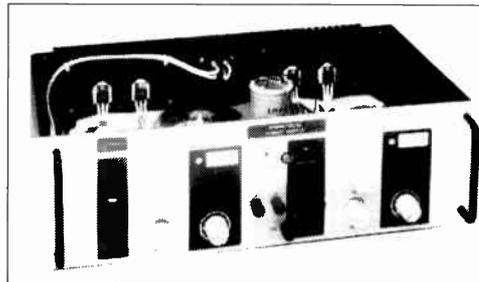220.057 **\$190**

## 400-WATT LABORATORY POWER SUPPLY

Here is an all-purpose d.c. power supply for symmetrical as well as asymmetrical use, and capable of supplying high output currents and voltages. An all-analogue design based on discrete parts only, this 400-watt PSU deserves a prominent place on your work bench.

ex. case 220.036 **\$525**

WorldRadioHistory

### MAIN FEATURES

- 8 internal lines
- 1 external line
- memory for 10 numbers
- internal through connections
- versatile computer control
- automatic hold for external line
- simple-to-extend
- can be interfaced to a PC
- selective external call acceptance
- shortcut dial codes for external number
- works with pulse-dialling telephone sets
- one optional relay for extra switching function

### MAIN SPECIFICATIONS

- **Mode: Single**
  - one adjustable power supply with current and voltage controls
  - Output 0 - 40 V at 0 - 5 A
- **Mode: independent**
  - two identical, electrically separated, power supplies
  - Outputs 2 x 0 - 40 V at 2 x 0 - 5 A
- **Mode: Tracking**
  - two identical, series connected, power supplies
  - Outputs  $\pm 0 - \pm 40$  V at 0 - 5 A
  - 0 - 80 V at 0 - 5 A
  - Voltage and current of slave follow master
- **Mode: parallel**
  - two identical, parallel connected, power supplies
  - Outputs 0.6 - 39.4 V at 0 - 10 A
- **Maximum output voltage:**
  - 0 - 40 V (at full load)
  - 48 V (no load)
- **Maximum output current:** 5 A
- **Ripple:**
  - 10 mV (no load)
  - 50 mV (at full load)
- **Voltage difference in tracking mode:** 50 mV

Announcing Old Colony Sound Lab's

# SUPER "SAVE YOUR INVOICE" SALE!

That's right! When you order from Old Colony from now through June, be sure to save the invoice which comes with your shipment! **It's worth cash!** In July or August, you may subtract **10%** of the invoice's bottom line from any order of double or greater value—in addition to any other discount which may apply!

For example, if you placed an order for \$50 worth of products now, in July or August you would be eligible for a \$5 credit (10% of your earlier order) on any order of \$10 or more (double or greater the amount of your credit)! *Plus any other discount!*

**BUT PLEASE REMEMBER:**

**YOU MUST SUBMIT YOUR ACTUAL PREVIOUS INVOICE WITH YOUR NEW JULY OR AUGUST ORDER, SO BE SURE TO SAVE IT!**



**SEE OUR ADS ELSEWHERE IN THIS ISSUE  
AND ORDER TODAY!  
START YOUR SUMMER SAVINGS NOW!**

## MARK V ELECTRONICS, INC.

Competitive Pricing \* Fast Shipping Since 1985

ORDER IN CALIFORNIA 800-521-MARK  
ORDER OUTSIDE CA 800-423-FIVE  
FREE CATALOG & INFORMATION (213) 888-8988  
FAX (213) 888-6868

▲ indicates the level of difficulty in the assembling of our Products. ▲ Beginner ▲▲ Intermediate ▲▲▲ Advanced ★ Fully Assembled



Amplifier + Metal Cabinet + Transformer	TA-3600 LG-1925 #007	TA-477 LG-1925 #003	TA-802 LG-1924 #001	TA-1000A LG-1924 #001	TA-1500 LG-1925 #001
Kit Set	\$155.61	\$125.21	\$100.45	\$113.52	\$130.00
Assmb. Set	\$179.36	\$141.36	\$113.54	\$133.36	\$150.00



\* Due to this special offer & low price, we can only exchange or repair any of these units (TA-3600, TA-477, TA-802 & TA-1000A) within 15 days of your receipt.  
\* The above prices are for the complete sets. For separate unit price, please see below.

AMPLIFIERS		KIT ASSEMB.	
MODEL	DESCRIPTION		
1A-28MK2	Digital Voice Memm ▲▲	\$30.00	
1A-50A-B	Mult. Purpose Melody Generator ▲	12.81	17.20
1A-50C	Mult. Purpose Melody (Happy Birthday, Wedding March, etc.) Generator ▲	13.65	18.71
1A-120MK2	35W Class A Main Power Mono Amp ▲	31.90	42.80
1A-300	30W Multi Purpose Single Channel Amp ▲	20.00	29.00
1SM-302	60W + 60W Stereo Power Amplifier (with Mic Input) ▲▲	67.00	78.00
1A-423A	30W X 2 Stereo Pre Main Amp ▲	31.50	42.80
1A-377A	Slide of the Art Fully Complementary Symmetrical Hi-Fi Pre Amp. ▲▲▲	59.95	75.00
1A-400	40W Solid State Mono Amp ▲	28.00	34.93
1A-177	120W Maxel Power Mono Amp ▲▲	68.00	85.00
1A-800MK2	120W + 120W Low Imp. Mono Stereo Power Amp ▲▲	63.92	
1A-802	80W + 80W Pure DC Stereo Main Power Amp ▲▲	45.94	59.72
1A-1000A	100W Dynamic Class A Main Power Mono Amp ▲▲	59.69	80.58
1A-1500	100W X 2 Class A DC Stereo Pre Main Amp ▲▲▲	71.70	95.81
1A-2200	DC Fed Super Class A DC Pre Amp. ▲▲▲	47.70	58.24
1A-2400A	Electronic Echo & Reverberation Amp ★		96.00
1A-2500	Hi-Fi Pre Amp w/10 band graphic equalizer ★		68.80
1A-2800	Hi-Fi Hi-Fi Pre Amp w/3 way tone control ▲▲	48.90	63.50
1A-3000	Stereo Simulator (for Mono TV or Any Mono Source) ▲▲	27.00	38.50
1A-3600	300W Hi-Fi Power Mono Amp ▲▲▲	85.00	110.00
SM-222	7 Band Hi-Fi Graphic Equalizer ▲▲▲	26.80	38.80
SM-328	4 Channel Professional Color Light Controller ★	65.00	145.00
SM-333	Audio/Video Surround Sound Processor ▲▲▲	26.00	25.00
SM-666	Dynamic Noise Reduction ★	26.00	34.00
SM-888	Universal Audio/Video KARAOKE Mixer Pre Amp ★		225.00

DIGITAL METERS AND COUNTER		KIT ASSEMB.	
MODEL	DESCRIPTION		
SM-43	3 + Multi-Functional LCD D.P.M. (w/ABS plastic case) ▲▲	\$34.50	\$43.00
SM-48	4 + Hi-Precision D.P.M. ▲▲	38.00	48.00
SM-48A	4 + Hi-Precision D.P.M. (w/ABS plastic case) ▲▲▲	41.20	52.00
SM-49	3 + Multi-Functional LCD D.P.M. (w/Hold Function) ▲▲	36.00	44.50
SM-100	150MC Digital Frequency Counter ▲▲▲	79.00	90.00
FC-1000A	1 GHz Frequency Counter ★		179.00

MISCELLANEOUS		KIT ASSEMB.	
MODEL	DESCRIPTION		
1V-23R	3 Channel Color Light Controller ★	\$	\$65.00
1V-25	Stereo Loudspeaker Protector ▲	14.85	20.85
1V-35	FM Wireless Microphone ▲	11.25	
1V-36	AC/DC Quartz Digital Clock ▲	19.00	26.20
1V-38	Sound / Touch Control Switch ▲	12.00	
1V-41MK V	Infrared Remote Control Unit (w/Case) ▲▲▲	22.00	35.00
1V-42	Bar / Dot Level Meter ▲▲	24.15	33.81
1V-43	3 + Digital Panel Meter ▲	29.00	38.00
1V-45	20 Steps Bar / Dot Audio Level Display ▲▲	38.45	46.14
1V-47	Superior Electronic Roulette ▲▲	19.46	27.24
10 000uF	80 V Capacitor (Suggested for TA-3600, TA-477, TA-1000A & TA-802)		23.00

REGULATORS		KIT ASSEMB.	
MODEL	DESCRIPTION		
1R-355A	0-15V 5A Regulated DC Power Supply (no case & x-former) ▲	\$15.65	\$21.76
1R-355B	0-30V 3A Regulated DC Power Supply (no case & x-former) ▲	15.65	21.76
1R-503	0-50V 3A Regulated DC Power Supply (no case & x-former) ▲▲	16.75	23.65

METAL CABINETS WITH ALUMINUM PANEL				PRICE
MODEL	H x W x D	MATCHING		
1G-1273	3-12-7	1A-2800 1A-377A 1A-2200		\$22.85
1G-1684	4-16-8	1A-323A 1A-377A 1A-2200		27.50
1G-1924	4-19-11	1A-802 1A-1500 1A-120MK 2 1A-800MK2 1A-1000A		32.80
1G-1925	5-19-11	1A-477 1A-800 MK2 1A-1500 1A-1000A 1A-3600		35.80
1G-1983	2 1/2 x 19-8	1A-377A 1A-2800 1A-2200 1A-120MK 2		29.25

POWER TRANSFORMERS				PRICE
MODEL	DESCRIPTION	MATCHING		
001	28V x 2 6A to 30V x 2 6A	1A-800 MK2 1A-802 1A-820A 1A-1000A 1A-1500		\$27.00
002	36V x 2 3A	1R-503 1A-323A 1A-400 1A-300 1A-377A		22.00
003	40V x 2 6A	1A-477		28.00
004	24V x 2 6A	1A-120 MK 2		12.00
005	26V x 2 3A	1R-355B		26.00
006	18V x 2 5A	1R-355A		15.50
007	53V x 2 8A	1A-3600		43.00

We accept major Credit Cards: Money Orders, Checks, and C.O.D. Orders. C.O.D. fee is \$5.00. Minimum order is \$20.00. We ship by UPS ground inside US (min. \$3.00) and ship by US mail. Business & Showroom hours (Pacific Time) Mon. thru Fri. 9:30 am to 5:00 pm. Sat. 10:00 am to 5:00 pm. All prices are in U.S. dollars. All items and prices are subject to prior sale. Prices are subject to change without prior notice. We are not responsible for typographical errors.

**MARK V ELECTRONICS, INC. - 8019 E. Slauson Ave, Montebello, CA 90640**

# BORBELY AUDIO

## of Germany

can supply all the "HARD-TO-FIND" European components for your ELEKTOR projects. We have good access to all major manufacturers of semiconductors, resistors, capacitors and mechanical components. We also stock a large number of semiconductors and other components from Japan.


Write or FAX your specific requirements to us, or if you don't have any specific project in mind, just ask for our general price list. Please send two IPCs (available from your post office) for the postage.

## BORBELY AUDIO

Melchior Fanger Strasse 34A ■ 8031 Gilching ■ Germany

Tel. INT + 49/8105/5291  
(From US: 011/49/8105/5291)

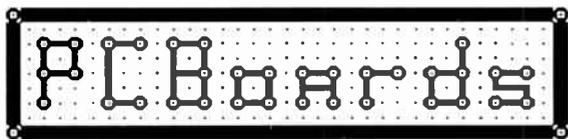FAX INT + 49/8105/24605  
(From US: 011/49/8105/24605) 24 Hours



### P-C-B ARTWORK MADE EASY !

Create and Revise PCB's in a Flash

- \* HERC, CGA, EGA, VGA, SUPER-VGA
- \* HELP SCREENS
- \* ADVANCED FEATURES
- \* EXTREMELY USER FRIENDLY
- \* AUTO GROUND PLANES
- \* DOT- MATRIX, LASER and PLOTTER ART
- \* CREATE YOUR OWN FILMS with 1XART
- \* LIBRARIES
- \* DOWNLOAD DEMOS from 24 hr. BBS!

REQUIREMENTS: IBM PC or Compatible, 384K RAM  
DOS 3.0 or later. IBM compatible printers.

PCBoards - layout program 99.00  
(PCBoards HP or HI PEN PLOTTER DRIVER 49.00)  
PCRoute - auto-router 99.00  
SuperCAD - schematic pgm. 99.00  
Demo Pkg. - (includes all 3 programs) 10.00

Call or write for more information  
PCBoards

2110 14th Ave. South, Birmingham, AL 35205  
1-800-473-PCBS / (205)933-1122  
BBS / FAX (205)933-2954


Courteous Service • Discount Prices • Fast Shipping

## ALL ELECTRONICS CORP.

P.O. Box 567 • Van Nuys, CA 91408
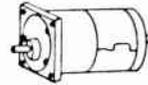
### MINIATURE GEAR MOTOR

Maxon DC motor #  
2130 910 61.112 050  
Rating with no load:  
24 Vdc @ 5 ma-168 RPM  
12 Vdc @ 5 ma -84 RPM  
Precision gear motor.  
Designed for 24 Vdc.  
Operates on 12-24 Vdc. 30:1 gear reduction head.  
2.07 long X 1.18" square mounting bracket has mounting holes on 0.97" centers. Motor has good torque when used at 24 Vdc. CAT# MOTG-15 \$12.00 each



### Special Reduced Price PHOTOFLASH CAP.

Rubicon CE  
210 Mid 330 Volt  
photoflash capacitor.  
0.79" dia. X 1.1" high.  
These are new capacitors that have been prepped with 1.4" blackand red wire leads soldered to the terminals.  
CAT# PPC-210 \$1.25 each  
10 for \$11.00 • 100 for \$100.00



### INSTRUMENT ENCLOSURES

High quality molded ABS instrument enclosures. Integrated PC board standoffs and two sets of vertical mounting slots for front and rear sub panels. All enclosures are 6" wide X 6 1/4" deep. Choice of three hts. Includes non-skid rubber feet and hardware. Available in ivory, black, and blue.  
Panel ht. CAT#  
2 1/4" CAT# MB-A \$7.50 ea 10 / \$65.00  
2 5/8" CAT# MB-B \$7.75 ea 10 / \$67.50  
3" CAT# MB-C \$8.00 ea 10 / \$70.00  
Please specify color.



### SWITCHES

#### Mercury Tilt Switch

0.2" diameter  
X 0.65" long  
mercury tilt switch. S.P.S.T. Closes circuit when switch is tilted approx. 5 degrees.  
CAT# MS-3 \$1.00 each  
10 for \$9.50 • 100 for \$85.00



#### Rotary BCD Switch

EECO # 2310-02G  
BCD 10 position rotary switch. DIP configuration fits in standard 8 pin I.C. socket. Right angle style. Screwdriver actuation. 0.42" cube. CAT# RDIP-2 \$1.75 each  
10 for \$16.00 • 100 for \$145.00



### TELEPHONE KEYPAD

12 button telephone keypad.  
Ivory finish. 2.83" x 2.2" x 0.58" thick. Matrix encoded. Ideal for telephone or security keypad.  
CAT# KPT-1 \$1.00 each  
10 for \$9.00



### 6 Volt 1 Amp/Hour RECHARGEABLE Battery

JAPAN STORAGE BATTERY CO.  
Portlac# PE6V1  
6 Volt 1 Ah rechargeable sealed lead-acid (gell cell). 2" X 1.635" X 2" high. Batteries are prepped with 5" black and red leads terminated with 2 pin connector. Ideal for rechargeable reserve power.  
CAT# GC-61 \$4.75 each • 10 for \$42.50



### OPTO SENSOR

TRW/Optron # OPB5447-2  
IR emitter/sensor pair in Rectangular package with 28" color coded leads.  
CAT# OSR-4 2 for \$1.00



### HALL EFFECT SENSOR


Microswitch # SS41 -  
Tiny, solid state switch reacts instantly to proximity of magnetic field. Operates at extremely high speeds, up to 100 kHz. Case size: 0.12" X 0.17" X 0.06" thick.  
4.5 Vdc to 24 Vdc supply voltage.  
10 ma. sink type digital output.  
Operating gauss - 15 to 40.  
P.C. leads. CAT# HESW-2  
75¢ each • 10 for \$6.50  
100 for \$60.00 • 1000 for \$500.00


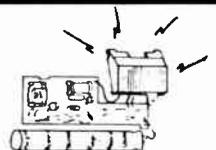
### \*\* New \*\* FLASH UNITS

This NEW compact flash unit comes from a U.S. manufacturer of cameras.

Operates on 3 Vdc.  
Measures 2 1/2" X 1 1/4".  
Ideal for use as a strobe, warning light or attention getter. Complete with instruction on how to wire.  
CAT# FSH-1 \$3.75 each • 10 for \$35.00



## TOLL FREE ORDER LINES 1-800-826-5432

CHARGE ORDERS to Visa, MasterCard or Discover

TERMS: Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (6%, 6 1/2%, 7%)  
Quantities Limited. NO C.O.D. Prices subject to change without notice.

Call Toll Free, or clip this coupon  
FREE 60 Page Catalog containing over 4,000 ITEMS

ALL ELECTRONICS CORPORATION  
P.O. Box 567 • Van Nuys, CA • 91408

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

EE 380

# KIT SPECIALS FOR SUMMER!

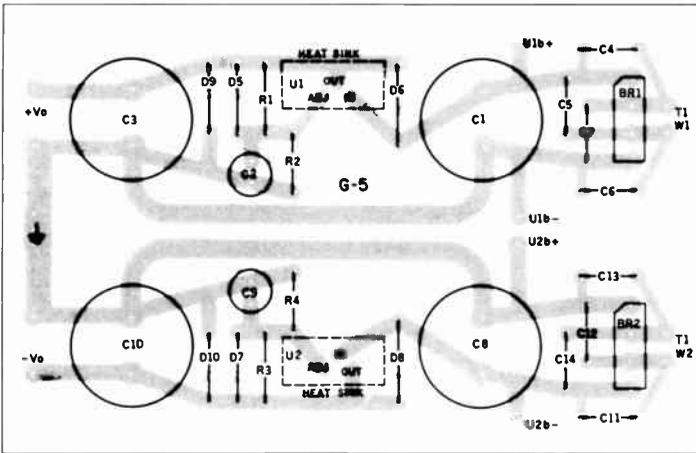

**PREAMP POWER SUPPLY**

Gary Galo/Linear Technology

**KG-5**  
**\$195**

This low-impedance, dual-polarity power supply uses the excellent Linear Technology LT1033CT and LT1085CT 3-Amp IC regulators. The regulators feature low dropout voltage, which helps maintain regulation even in situations where line voltage is low. Although the parts supplied provide  $\pm 15$  volts, the output can be varied from  $\pm 12$  to  $\pm 18$  volts by changing two resistors. An oversized Avel-Lindberg 120VA toroidal transformer will operate many KG-5 regulator boards, allowing separate regulation of the left and right channel circuitry, or separate regulation of a phono preamp and line level stages. The printed circuit board has heavy traces on the input and output lines to minimize resistance. Case not included.

The KG-5 is ideal for many low-level applications, including preamplifiers and electronic crossovers. Gary Galo also uses the KG-5 to power the analog circuitry of his CD player. From TAA 4/90.

Purchasing options available:

- PCBG-5 Printed Circuit Board Only \$ 15.00
- PCB and Parts Only (less Transformer) \$134.95
- Transformer Only \$ 64.95
- Complete Kit \$195.00

**ADCOM POWER SUPPLY REGULATOR**

Kit Ryan

**KY-2**  
**\$99 per chan.**

This popular mod was designed for taming Adcom's GFA-555, but it adds sweetness and definition to just about any amp in the 80V-in, 60V-out, 10A-regulated family. Mounts in existing case; complete with PCB, custom heatsink, and Japanese transistors. Two usually needed. From TAA 4/89.



Yes! Please send me


# \_\_\_\_\_ @ \$ \_\_\_\_\_ = \$ \_\_\_\_\_  
 # \_\_\_\_\_ @ \$ \_\_\_\_\_ = \$ \_\_\_\_\_  
 # \_\_\_\_\_ @ \$ \_\_\_\_\_ = \$ \_\_\_\_\_  
 SHIPPING \_\_\_\_\_  
 TOTAL \$ \_\_\_\_\_

SHIPPING: Postpaid in U.S. In Canada, please add 10% for surface; others, 20% for surface. Airmail: Please inquire.



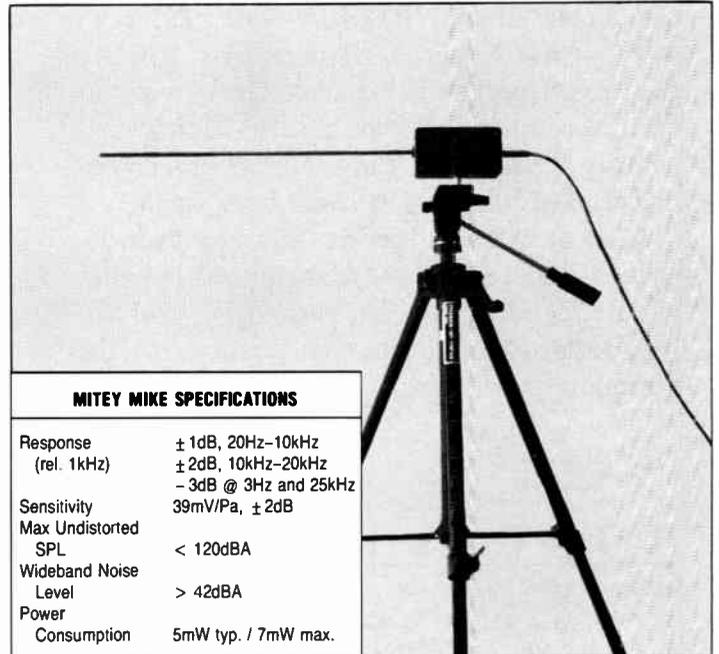**OLD COLONY SOUND LAB**

PO Box 243, Dept. E91  
 Peterborough, NH 03458 USA  
 24-hour telephone: (603) 924-9464  
 24-hour FAX: (603) 924-9467



**MITEY MIKE SPECIFICATIONS**

Response (rel. 1kHz)	$\pm 1$ dB, 20Hz-10kHz $\pm 2$ dB, 10kHz-20kHz -3dB @ 3Hz and 25kHz
Sensitivity	39mV/Pa, $\pm 2$ dB
Max Undistorted SPL	< 120dBA
Wideband Noise Level	> 42dBA
Power Consumption	5mW typ. / 7mW max.

**MITEY MIKE TEST MICROPHONE**

Joseph D'Appolito

**KD-2**  
**\$149**


At long last, a top-quality test mike at a great price! Mitey Mike is the answer to many an audiophile's loudspeaker testing dreams, providing flat free-field frequency response; high, undistorted SPL capability; good measurement repeatability; and guaranteed long-term stability. Plus, it's a snap to build! Complete with PCB, mike cartridge, custom brass wand, all components, and (undrilled) blue case. Typical specs are shown in the inset. For greater accuracy, a mike calibration service is available. Tripod, 9V battery not included. From SB 6/90.

**THE WARBLER OSCILLATOR**

Richard Crawford

**KK-3**  
**\$69**

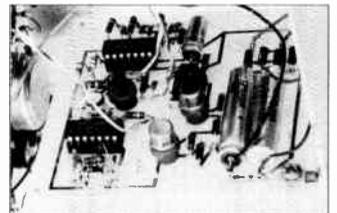The Warbler produces a swept signal covering any  $\frac{1}{3}$  octave between 16Hz and 20kHz. With a mike, it's a pink noise source to evaluate speaker system performance and the effects of reflection and absorption. Comes with PCB, transformer, all parts. Case not included. From TAA 1/79.



**MITEY MIKE/WARBLER SET**

D'Appolito/Crawford

**KMW-1**  
**\$199**

Both of the above, at a special savings of \$19!

NAME \_\_\_\_\_ MAGIC NO \_\_\_\_\_  
 STREET \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
 MC/VISA \_\_\_\_\_ EXP DATE \_\_\_\_\_

**CALL OR WRITE FOR YOUR FREE CATALOG!**  
**DEALER INQUIRIES INVITED.**

**MultiCap**

$$\left( \frac{\text{UNCERTAINTIES}}{\text{Capacitors}} \right) = \left( \frac{\text{GUESSWORK}}{\text{Design}} \right)$$

The formula for the best design begins with the best components. And for critical applications in advanced circuits, you can't find better components than MIT's MultiCap Series capacitors.

\*Each individual MultiCap gives you up to 10 precision paralleled capacitors in one compact optimized unit that extends the usable bandwidth. You will not have to compromise the quality of your final design by adding additional bypass capacitors to extend the range of conventional capacitors.

\*Each hand-made MultiCap, with hand-soldered, large-gauge leads necessary for high-current conditions, provides the highest resolution yet attained.

The combination of care and innovation in every MultiCap gives you extraordinarily high quality, reliability, and performance.



MIT offers two series of capacitors: the original film-and-foil MultiCap and now the NEW METALLIZED-FILM MultiCap which will be available Spring 1991. Both at new low prices.

**The Film -and- Foil MultiCap™:**

- \* Especially designed for high-performance filters, DC blocking, and high ripple-current capacity.
- \* Consistent, reliable for high-performance under demanding high-current applications, with exceptional phase stability and superior pulse-handling capability.

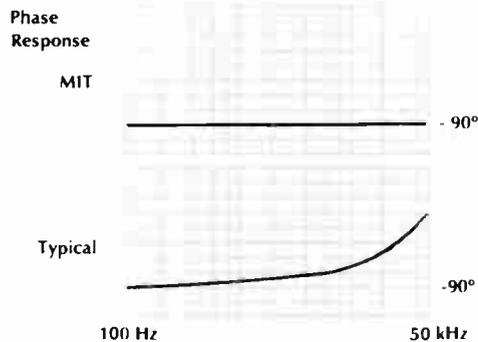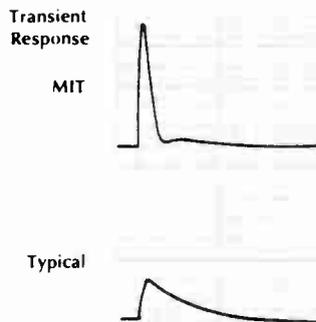**The New Metallized MultiCap™:**

- \* Same patented parallel design.
- \* Smaller in size and less costly to make. Lower prices for the consumer.
- \* Recommended for application wherever metallized capacitors are used. As engineers know, metallized caps are not usually recommended for high-current applications: MIT recommends its film & foil caps for these uses.



MIT now distributes the MultiCap capacitors directly, and provides OEMs with full technical support and custom values when desired.

For our new prices and all current literature, including white papers and an introduction to the metallized MultiCap, please write MultiCap, Music Interface Technologies, 3037 Grass Valley Highway, Auburn, CA 95603. Or call 916.823.1186. Fax: 916.823.0810.



**MultiCap.™ "The most advanced capacitor design in the world."**





**3000**  
Top of the Line Universal  
Handi-Counter™.  
\$375.

# OFF THE BENCH AND RUNNING

When **OPTOELECTRONICS** took frequency counters off the bench we created a whole new dimension - Frequency Finding.

Our Handi-Counters™ make Frequency Finding a reality by allowing you to pick-up radio transmitters at the maximum possible distance.

Monitoring Enthusiast, Security Specialists, Broadcast and Design Engineers, Two Way and Amateur Radio Operators and Service Technicians have all made the move. *Shouldn't you?*



**2600**  
Super Sensitive RF  
Frequency Finder.  
\$325.



**2210A**  
Full Range  
Pocket  
Size LED.  
\$239.



**1300H/A**  
Low Cost Ultra  
Sensitive (HF,  
UHF, VHF).  
\$179.



**8030**  
Bench Portable (Fits in an attache case) with ALL the Handi-Counter™ Features plus More. \$579.

Model	Range Low High	Display 8 Digit LED	Display 10 Digit LCD	Signal Strength Bargraph	Universal Counter	TCXO Option
8030	10Hz 2.4GHz		•	•	•	± 1ppm add \$125.
3000	10Hz 2.4GHz		•	•	•	± 2ppm add \$ 80.
2600	1MHz 2.4GHz		•	•	•	± 2ppm add \$ 80.
2210A	10Hz 2.4GHz	•				± .5ppm add \$ 75.
1300H/A	1MHz 1.3GHz	•				± .5ppm add \$ 75.

Sensitivity: <1 to <10mV typical. NiCads & AC Charger/Adapter Included. Carry Case, Antennas and Probes extra. One year parts & labor warranty on all products.

## OPTOELECTRONICS

**Toll Free Order Line:**  
**1-800-327-5912**  
In Florida call (305)771-2050  
**FAX (305)771-2052**

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334  
Visa, MC, COD, Cash, M.O. accepted. Personal  
Check allow 3 weeks. 5% Shipping, Handling.  
(Maximum \$10) U.S. & Canada. 15% outside  
continental U.S.A.