

ELEKTOR **ELECTRONICS** **USA**

THE INTERNATIONAL JOURNAL
FOR RECREATIONAL ELECTRONICS

OCTOBER 1991

\$3.00 US
CANADA \$4.00

Digital function generator

Four-terminal networks


**Computer-controlled
weather station**

**A review of coding
theory**

50MHz 8-bit DAC

**Audio spectrum
shift techniques**

AM Receiver

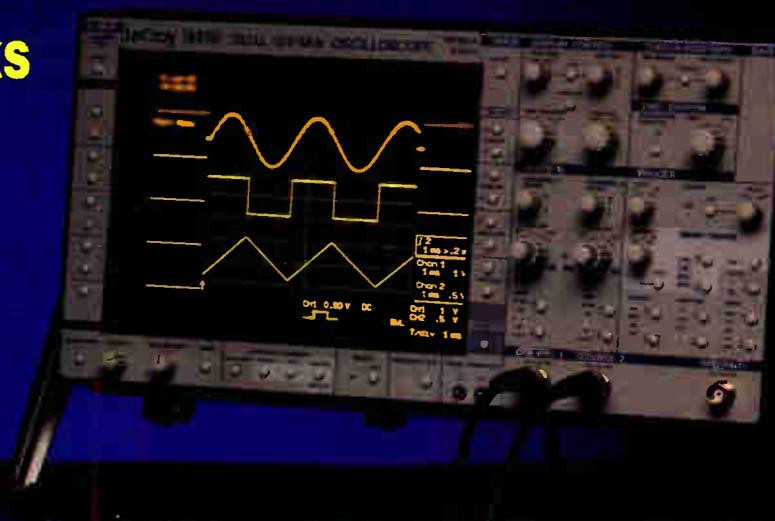

William Kolasa
Rt 1 Box 26/A, Sunset Dr
Chester MO 21619

ANNOUNCING

LDC-IV

20,000 SOLD
WORLDWIDE

**LOUDSPEAKER DESIGN COOKBOOK
FOURTH EDITION**


by VANCE DICKASON

152 TEXT
PAGES

NEW CHAPTERS
"What is a
Loudspeaker?"

"CAD Software
for Speaker
Design"

TWICE
THE SIZE OF
LDC-III

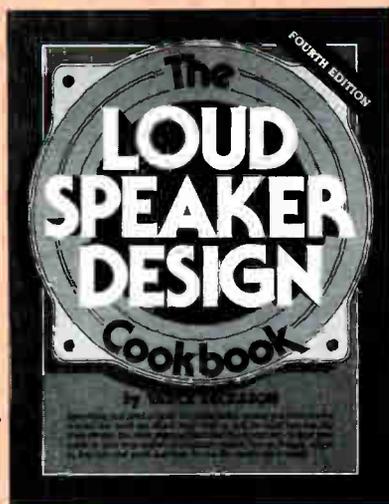

IBM DESIGN
SOFTWARE
OFFER

CONTENTS/SUBJECTS
INDEX

SUPPLIERS
LISTING

\$29.95

COMING TO AN ADDRESS NEAREST YOU

OCTOBER 15, 1991

AT YOUR DEALER OR

**OLD COLONY SOUND LAB
BOX 243, DEPARTMENT E91
PETERBOROUGH, NH 03458**



Send Me _____ copy(s) @ \$29.95 \$ _____

SHIPPING: Please add \$2 for first book; 75¢ each additional. Books are not returnable for refund.

Check/MO Charge Card MC/VISA

NAME _____

STREET & NO. _____

CITY _____

ST _____

ZIP _____

MC/VISA _____

EXP. _____

PHONE: (603) 924-6371

FAX: (603) 924-9467

WorldRadioHistory

Front cover

Function generators are intended to produce several different waveforms and are, therefore, very flexible instruments. Most of them generate a sine, rectangular and triangular waveform over a frequency range of up to 1–50 MHz. Some also have the capability of producing pulse waveforms. Generally, the performance of a function generator is inferior to that of dedicated instruments, but the digital design of which the first of three parts is presented in this issue has the capability of accurate frequency setting coupled with very low distortion of the sine wave output.

In next month's issue

- Class A amplifier
- Dissipation limiter
- Function generator [2]
- Experimental quadri-form ferrite antenna
- 24-bit full-colour video digitizer
- Four-terminal networks – Part 2
- Computer-aided electronics design

Copyright © 1991 Elektor BV

ELEKTOR ELECTRONICS USA (US ISSN 1051-5690) is published monthly except August at \$28 per year; \$50 for two years by Audio Amateur Publications, Inc., 305 Union St., Peterborough NH 03458 USA. Second class postage paid at Peterborough NH and an additional mailing office.

POSTMASTER: Send address changes to Elektor Electronics USA, Caller Box 876, Peterborough NH 03458-0876. Return Postage Guaranteed

EDITORIAL

- 11 Scientific Travels in Real and Virtual Worlds

APPLICATION NOTES

- 59 Switch-Mode Voltage Regulators LM2575/LM2577
National Semiconductors

AUDIO & HI-FI

- 56 The Digital Compact Cassette
based on an original article by P. van Willenswaard

COMPUTERS & MICROPROCESSORS

- 14 Upgrade for MCS BASIC-52 V1.1 Pt. 1 (of 2)
by Dusan Mudric and Zoran Stojasavljevic

DESIGN IDEAS

- 16 Audio Spectrum Shift Techniques
by C. White Halfcoat

GENERAL INTEREST

- 28 **PROJECT:** Computer-Controlled Weather Station
Pt. 2: Electronic Hygrometer
by J. Ruffell
- 46 Four-Terminal Networks Pt. 1 (of 2)
by Steve Knight

INTERMEDIATE PROJECT

- 23 Build the Opicalock Pt. 2 (final)
by Michael Swartzendruber

RADIO, TELEVISION & COMMUNICATIONS

- 49 Fiber Optics Pt. 2 (final)
by Joseph J. Carr
- 52 **PROJECT:** AM Broadcast Receiver
by R. Shankar

SCIENCE & TECHNOLOGY


- 42 A Review of Coding Theory
by Brian P. McArdle

TEST & MEASUREMENT



- 26 **PROJECT:** 50MHz 8-Bit DAC
by R. Shankar
- 32 Measurement Techniques Pt. 7
by F.P. Zantis
- 34 **PROJECT:** Digital Function Generator Pt. 1 (of 3)
by T. Giffard

MISCELLANEOUS INFORMATION

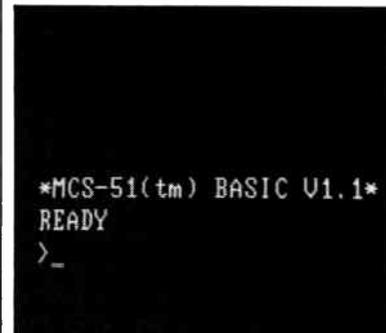Electronics Scene 12, 13, 27; New Books 62; Advertisers' Index 64; Classifieds 64 Readers' Services 65; Terms of Business 66.




Upgrade for MCS-BASIC-52
p.14

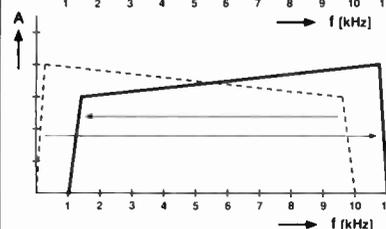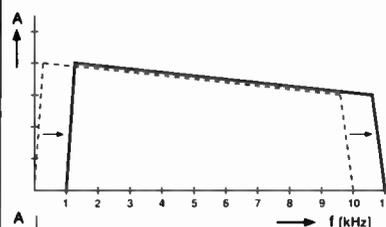

Audio spectrum shift
techniques – p. 16



The digital compact cassette
p. 56

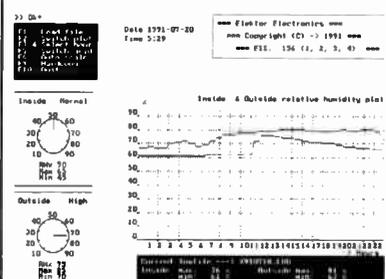

Electronic hygrometer – p. 28

KELVIN Electronics UP TO 50% OFF

KELVIN DIGITAL MULTIMETERS

Kelvin Meters backed by a 2 Yr Warranty - Parts & Labor

PRO 400 with 20MHz Freq Counter

100 Basic \$19.95
150 Basic+ \$29.95
200 Advanced \$39.95

FLUKE 70 Series II

FLUKE 3 YEAR WARRANTY

FLUKE 70 Series II \$63
FLUKE 73 Series II \$89
FLUKE 75 Series II \$127
FLUKE 77 Series II \$149
FLUKE 79 Series II \$169

LED CENTER

RED LED As Low As 5¢ ea / 1000+ Qty

JUMBO LED

TYPE - T 1 3/4, 5mm
 STOCK NO. YOUR COST 1000+ Qty
 260020 Red \$.06 ea/100+ \$.05 ea
 260027 Green \$.08 ea/100+ \$.07 ea
 260026 Yellow \$.08 ea/100+ \$.07 ea

PROJECT PARTS

Soldering IRON with STAND, BLUE LONG LIFE TIP Stock No. 990098 \$4.50 ea

Project Speaker 2", 8 Ohm, .1 Watt Stock No. 350009 59¢

Project BUZZER 3 - 9 Volt DC, 80 db Stock No. 680089 \$1.59 ea

HORN ALARM Loud Penetrating Sound Stock No. 640001 \$.75 ea

DC MOTOR for SOLAR/ROBOTIC Stock No. 852211 \$.50 ea

XENON STROBE TUBE Stock No. 260050 \$2.95 ea

TRIGGER COIL for Xenon Strobe Tube Stock No. 320037 \$1.25 ea

INFRARED LED IR Pair, LED infrared transmitter and receiver Stock No. 260061 \$2.79 ea

NEON LAMP NE2, Long Leads Stock No. 260003 \$1.15 ea

PHOTO CELL CADMIUM SELENIDE Stock No. 260017 \$.99 ea

PHOTO CELL SULPHIDE Stock No. 260018 \$.99 ea

PUSH-BUTTON SWITCH PUSH-ON, PUSH-OFF BNC AT BOTH ENDS Stock No. 270021 \$.55 ea

SUB-MINIATURE MOMENTARY SWITCH Stock No. 990002 \$.35 ea

MINIATURE TOGGLE SWITCH Type - SPS1 Stock No. 270034 \$.90 ea

Protective Cases

For Models 100, 150, 200 \$4.95 Case For Model Pro 400 \$9.95

DIGITAL TRAINER

Trainer Manual (100 Pgs) gives detailed instructions. An excellent training tool covering topics for High School (Beginner - Advanced), Trade School (Beginner - Intermediate) & College.

A PERFECT FIT WITHIN ANY DIGITAL CURRICULUM & YOUR CLASSROOM TEXTBOOK

FEATURES

- ONE DIGIT TRUE HEXADECIMAL DISPLAY WITH BUILT IN LOGIC (MEMORY, DECODER, DRIVERS) FULL ALPHA CHARACTERS
- TWO INDEPENDENT CLOCKS - USER ADJUSTABLE FREQUENCY & DUTY CYCLES
- BREADBOARD/50 PIN PROTOTYPE AREA
- TWO POWER DISTRIBUTION BUSES (GND, VCC)
- 4 DATA BIT SWITCHES
- MOMENTARY PUSH BUTTON SWITCH (SPDT)
- 4 LED DISPLAYS w/IC DRIVERS
- POWER SUPPLY: WALL PLUG-IN TYPE, U.L. LISTED
- VOLTAGE REG: ±5 VOLTS, SHORT CIR. OVERLOAD PROTECT
- HOOK-UP WIRES
- CONSTRUCTION CARRYING CASE
- INSTRUCTION MANUAL FOR BEGINNER TO ADVANCED USERS

MADE WITH PRIDE IN THE USA

THE KELVIN LDT™ Laptop Digital Trainer

ONLY \$99.95

Stock No. 840460

SCOPES

20 MHz SCOPE \$345

Dual Trace 2 Yr Warranty-Parts & Labor

SCOPE PROBES

60 MHz, X1 & X10 SPECIAL 700072... \$18.95
 150 MHz, X10 700073... \$39.95

FLUKE 8062A \$329
FLUKE 8060A \$395

FLUKE 8010A \$329
FLUKE 8012A \$359
FLUKE 8050A \$439

FLUKE 37 \$249
FLUKE 45 \$579

LED HOLDER for T 1 3/4 SIZE, BLACK Stock No. 250019 \$.10 ea / 100+ Qty

0.37" 7 SEGMENT LED READOUT

STOCK NO. TYPE COST 20+ Qty
 260022 Anode \$.95 ea \$.75 ea
 260090 Cathode \$1.25 ea \$.99 ea

0.6" 7 SEGMENT LED READOUT

STOCK NO. Anode Jumbo COST 20+ Qty
 260021 \$1.15 ea \$1.99 ea

RED LED DISPLAY Bar Graph

STOCK NO. Color YOUR COST 10+ Qty
 260058 Red \$1.99 ea \$1.79 ea
 260088 Green \$1.99 ea \$1.79 ea
 260089 Yellow \$1.99 ea \$1.79 ea

MOVING SIGN DISPLAY for Fabricating Your Own Moving Sign Display 50 mm Stock No. 260091 \$5.95 ea

IC CLIPS SOLDER TYPE SPRING LOADED Stock No. COLOR COST 25+ Qty
 990104 BLACK \$.65 ea \$.50 ea
 990105 RED \$.65 ea \$.50 ea

IC TEST LEAD SET 5 COLOR CODED 18" LEADS WITH MINATURE HOOK-ON PROD AT BOTH ENDS Stock No. YOUR COST 3+ Qty
 990108 \$8.95 ea \$8.25 ea

DOUBLE BANANA JACK Stock No. YOUR COST 3+ Qty
 600056 \$2.30 ea \$2.07 ea

FEMALE BNC TO DUAL BANANA PLUG Stock No. YOUR COST 3+ Qty
 990103 \$2.95 ea \$2.75 ea

DUAL BANANA BINDING POST TO MALE BNC PLUG Stock No. YOUR COST 3+ Qty
 600058 \$5.95 ea \$4.95 ea

BNC TEST CABLES 3 FT. Stock No. YOUR COST 3+ Qty
 990101 \$3.45 ea \$2.95 ea

WALL TRANSFORMERS

WALL TRANSFORMER

STOCK NO. TYPE - Female
 220069 9V DC 500 mA \$3.95 ea
 220068 12V DC 500 mA \$4.25 ea

MALE JACK Stock No. TYPE
 370048 2.1 mm Male \$49 ea \$39 /10+

BREADBOARDS

680093 680097

BATTERIES

Duracell / Eveready 9V Alkaline Battery \$1.95 ea \$1.75 ea/10+

9V Battery SNAP & HOLDER Snap \$.15 ea \$.10 ea/100+ Holder \$.20 ea \$.10 ea/100+

HEAVY DUTY NI-CAD RECHARGEABLE BATTERIES

STOCK NO. TYPE YOUR COST
 220039 AAA \$3.30 ea
 220025 AA \$2.85 ea
 220027 C \$6.00 ea
 220037 D \$6.00 ea
 220038 9V \$8.90 ea

NI-CAD BATTERY CHARGER 4 Cell Charger for AAA, AA, C, D or 9V Stock No. YOUR COST
 220035 SPECIAL \$9.95 ea

COMPONENTS

Stock No. TYPE YOUR COST

600021 555 TIMER \$20 ea
 600029 555 DUAL TIMER \$40 ea
 600039 LM566 PLL \$60 ea
 600018 741C OP-AMP \$30 ea INTERNALLY COMPENSATED
 600026 1458 OP-AMP \$35 ea DUAL 741C OP-AMP DIP

630041 2N2222 \$18 ea
 630383 PN2222 \$08 ea
 600023 7805 VOLTAGE REG \$36 ea

SILICON CONTROLLED RECTIFIER (Similar to GE C106C1) 4.0 AMP, 100 PIV 600014 \$.89 ea \$3.79 ea 50+

WIRE JUMPER KIT Pre-cut, Pre-Stripped 330289 140 Piece Set \$4.75 330290 350 Piece Set \$7.75

TEST ACCESSORIES

IC TEST LEAD SET 5 COLOR CODED 18" LEADS WITH MINATURE HOOK-ON PROD AT BOTH ENDS Stock No. YOUR COST 3+ Qty
 990108 \$8.95 ea \$8.25 ea

DOUBLE BANANA JACK Stock No. YOUR COST 3+ Qty
 600056 \$2.30 ea \$2.07 ea

FEMALE BNC TO DUAL BANANA PLUG Stock No. YOUR COST 3+ Qty
 990103 \$2.95 ea \$2.75 ea

DUAL BANANA BINDING POST TO MALE BNC PLUG Stock No. YOUR COST 3+ Qty
 600058 \$5.95 ea \$4.95 ea

BNC TEST CABLES 3 FT. Stock No. YOUR COST 3+ Qty
 990101 \$3.45 ea \$2.95 ea

MALE TO MALE Stock No. YOUR COST 3+ Qty
 990101 \$3.45 ea \$2.95 ea

KELVIN ELECTRONICS

CIRCLE RESPONSE CARD or WRITE for our CATALOG full of WHOLESALE PRICED ITEMS.

OVER 10,000 ITEMS IN STOCK

ELECTRONIC COMPONENTS & TECHNOLOGY ACTIVITIES

VISA & MASTERCARD ACCEPTED \$20 MINIMUM ORDER MINIMUM FREIGHT \$5

Call: 1 (800) 645-9212
 1 (516) 349-7620
 FAX: 1 (516) 349-7830

KELVIN Electronics

7 Fairchild Avenue, Plainview, NY 11803

NOW AVAILABLE FULLY ASSEMBLED!

FALL KIT SPECIALS!



LET US KNOW!

Old Colony will soon be offering a number of its kits in assembled form. If you have seen a good candidate in our ads or catalog, please be sure to let us know of your interest. Every vote counts!

MITEY MIKE TEST MICROPHONE

Joseph D'Appolito

KD-2 \$149

At long last, a top-quality test mike at a great price! Mitey Mike is the answer to many an audiophile's loudspeaker testing dreams, providing flat free-field frequency response; high, undistorted SPL capability; excellent measurement repeatability; and guaranteed long-term stability. Plus, it's a snap to build! Typical specs—response (rel. 1kHz): ± 1dB, 20Hz-10kHz; ± 2dB, 10kHz-20kHz; - 3dB @ 3Hz and 25kHz; sensitivity: 39mV/Pa, ± 2dB; max. undistorted SPL: > 120dBA; wideband noise level: < 42dBA; power consumption: 5mW typ.; 7mW max.

Unassembled kit comes complete with PC board, mike cartridge, custom brass wand, all components, and (undrilled) blue case. For greater accuracy, a mike calibration service is available at a small additional charge (details come with kit), although most users do not find this step necessary. Tripod, 9V battery not included. From SB 6/90.

Other purchasing options available:

- KD-2AM** Assembled Mitey Mike with calibrated cartridge **\$229**
- KMW-1** Unassembled KD-2 (above) plus unassembled companion KK-3 Warbler Oscillator (case included; please see complete KK-3 specs elsewhere in this section), at a savings of \$19! **\$229**
- KMW-1AM** Assembled KD-2 with calibrated cartridge plus assembled KK-3, at a savings of \$29! **\$349**
- KMWP-1** Unassembled KD-2 (above) plus unassembled companion KK-3 Warbler Oscillator (case included) plus unassembled companion KSBK-E4 Super Switchable White/Pink Noise Generator (case included; please see complete KSBK-E4 specs elsewhere in this section), at a savings of \$38! **\$289**
- KMWP-1AM** Assembled KD-2 with calibrated cartridge plus assembled KK-3 plus assembled KSBK-E4, at a savings of \$58! **\$449**

THE WARBLER OSCILLATOR

Dick Crawford

KK-3 \$99

This unit will produce a swept signal covering any 1/3 octave between 16Hz and 20kHz. The total harmonic distortion at the output is less than 1.5%, and the output voltage is adjustable from 0 to 1V. When used with a microphone, the Warbler is more effective than a pink noise source in evaluating speaker system performance. It also reveals the listening environment's effect on sound through reflection and absorption. The sweep rate is set at about 5Hz. The kit includes 3 1/4" x 3 3/8" PC board, transformer, all parts, and article reprint. Case included. This device is the most accurate tool available for determining a speaker system's actual performance in a room. From TAA 1/79.

Other purchasing options available:

- KK-3A** Assembled Warbler **\$149**
- KMW-1, KMWP-1** ALSO AVAILABLE IN COMBINATION WITH MITEY MIKE TEST MICROPHONE AND SUPER SWITCHABLE WHITE/PINK NOISE GENERATOR. PLEASE REFER TO KIT KD-2 ELSEWHERE IN THIS SECTION.

SUPER SWITCHABLE WHITE/PINK NOISE GENERATOR

Bernhard Muller

KSBK-E4 \$79

This unique kit features a stereo/mono/reverse-polarity switch that distinguishes it from other generators. CMOS digital circuits form a pseudo-random bit stream generator switchable between mono, stereo, and stereo reverse, and another switch selects pink or white noise output. Pink noise rolls off between 16Hz and 20kHz at 3dB/octave and at 6dB/octave above 20kHz, while white noise is constant through the 16Hz-20kHz range. The unit is powered by a 9V battery, not included. Included is an article reprint outlining the generator's use in audio system evaluation; the article is especially helpful with speaker evaluation methods and room placement problems. The kit comes complete with 4 1/8" x 2 3/16" PC board, ICs, precision resistors and capacitors, and switches. Case included. From SB 4/84.

Other purchasing options available:

- KSBK-E4A** Assembled White/Pink Noise Generator **\$129**
- KMWP-1** ALSO AVAILABLE IN COMBINATION WITH MITEY MIKE TEST MICROPHONE AND WARBLER OSCILLATOR! PLEASE REFER TO KIT KD-2 ELSEWHERE IN THIS SECTION.


ADCOM POWER SUPPLY REGULATOR

Kit Ryan

KY-2

\$99 per chan.

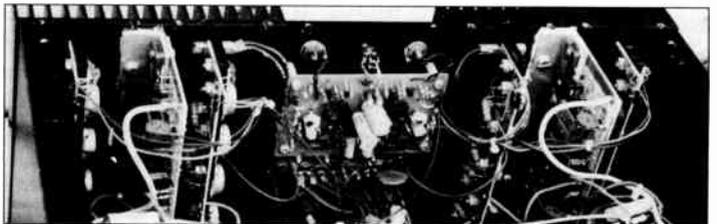This popular mod was designed for taming Adcom's GFA-555, but it adds sweetness and definition to just about any amp in the 80V-in, 60V-out, 10A-regulated family. Mounts in existing case; complete with PCB, custom heatsink, and Japanese transistors. Two usually needed. From TAA 4/89.



Yes! Please send me

_____ # _____ @ \$ _____ = \$ _____
 _____ # _____ @ \$ _____ = _____
 _____ # _____ @ \$ _____ = _____
 SHIPPING _____
 TOTAL \$ _____



OLD COLONY SOUND LAB

PO Box 243, Dept. E91
 Peterborough, NH 03458 USA
 24-hour telephone: (603) 924-9464
 24-hour FAX: (603) 924-9467

NAME _____ MAGIC NO. _____
 STREET _____
 CITY _____ STATE _____ ZIP _____
 MCV/ISA _____ EXP. DATE _____

**CALL OR WRITE FOR YOUR FREE CATALOG!
 DEALER INQUIRIES INVITED.**

SHIPPING: Postpaid in U.S. In Canada, please add 10% for surface; others, 20% for surface. Airmail: Please inquire.




IBM PC SERVICE CARD

This card was developed for assistance in the field of service, development and test. The card is used as a bus-extension to reach the measurement points very easy. It is also possible to change cards without having a "hanging computer".

Ready Assembled Module

\$145

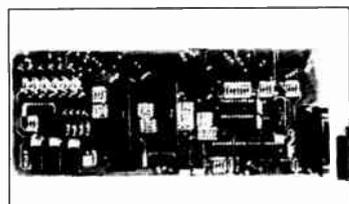


IC TESTER FOR IBM-PC-XT/AT

With the ELV IC tester logic function tests can be carried out on nearly all CMOS and TTL standard components, accommodated in DIL packages up to 20 pin. The tester is designed as an insertion card for IBM-PC-XT/AT and compatibles. A small ZIF test socket PCB is connected via a flat band cable. Over 500 standard components can be tested using the accompanying comprehensive test software. Complete Kit including Textool socket, connectors, sockets, Flat band cable, PCB, Software.

Ready Assembled Module

\$200

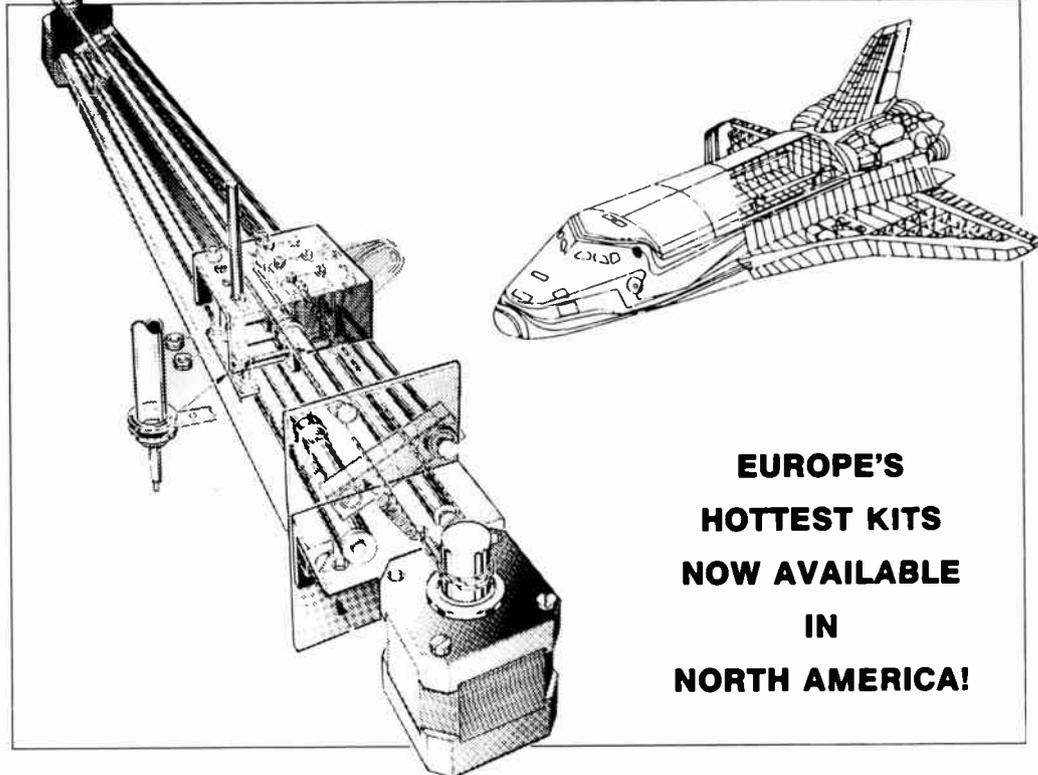


**EUROPE'S
HOTTEST KITS
NOW AVAILABLE
IN
NORTH AMERICA!**

PLOTTER MARK-II

completely reworked version: see *Elektor Electronics* March 1990.

- Max. width 50 cm.
- All mechanical parts supplied ready-drilled, filed and tapped, so get going at once.
- Complete kit, including 2 stepper motors, 3 pen lift solenoids, HPGL software on disk (IBM), stepper motor control board

100.100 **\$275**

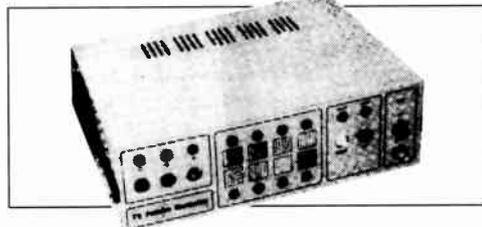

COLOUR TEST PATTERN GENERATOR

A PAL-compatible colour video source that supplies a number of test patterns for aligning television sets.

A test pattern generator is virtually indispensable for troubleshooting in television sets because it supplies a video signal that is known to be stable, and thus easily displayed and synchronized on an oscilloscope.


Inc. case and front

100.111 **\$175**



ELEKTOR P.C. i/o card

* 220.007 **\$175**
WorldRadioHistory

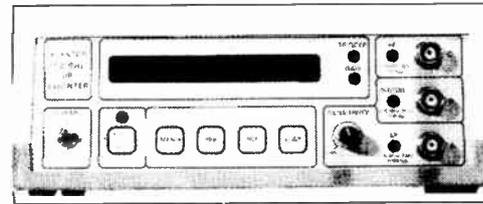

MICROPROCESSOR-CONTROLLED FREQUENCY METER

A professional grade multi-purpose frequency meter, designed by Elektor Electronics, that can be built by many at affordable cost. Described in *Elektor Electronics* December 1984, January & February 1985. U665B-based prescaler.

- Frequency meter: 0.01 Hz to 1.2 Ghz.
- Pulse duration meter: 0.1 to 100 s.
- Pulse counter: 0 to 10⁹ pulses
- Period meter: 10 ns to 100 ns
- Sensitivity: Input A: 10 mV_{rms} (Z_{in} = 2 MΩ); Input B: TTL or CMOS compatible (Z_{in} = 25 kΩ); Input C: prescaler input: 10 mV_{rms} (Z_{in} = 50 Ω).
- Auto-ranging and completely menu-driven.
- 6 or 7 digit accuracy.

Kit includes power supply, prescaler and enclosure.....100.112 **\$300**


BASIC COMPUTER

With Intel 8052AH-BASIC

100.117
\$160



| | | |
|-------------------------------------|---------|-------------|
| ANALOG MODULE eps 880162 | 100.113 | \$80 |
| DIGITAL MODULE eps 880163 | 100.114 | \$55 |
| ADRESSECODER eps 880159 | 100.115 | \$45 |

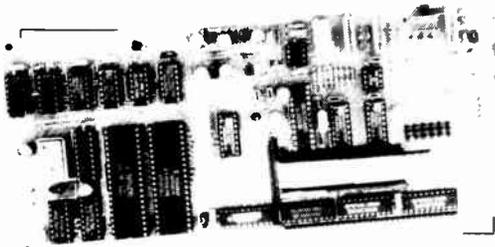

MULTIFUNCTION MEASUREMENT CARDS FOR PCs

The high-performance insertion card described in this article allows your IBM PC-XT, PC-AT or 100% compatible to measure direct voltage at 12-bit accuracy, as well as frequency and a host of other parameters related to pulse-shaped signals. The accuracy and versatility afforded by the card are of a level associated with much more expensive, industrially rated products. The menu-driven control software developed for this exciting project allows you to keep tabs on up to eight voltages quasi-simultaneously, while up to eight remaining inputs can be used for time-related measurements including frequency, duty factor and pulse duration, not forgetting the event counter. Connected to the sensors and timing devices of your choice, this card turns a PC into a powerful central controller in a complex measurement and control system.


220.040 **\$225**

SPECIAL PARTS SERVICE

We are the no. 1 suppliers of hard-to-find components for Elektor Electronics projects. Always contact us first if you see an unfamiliar component. Items include analogue & digital ICs (HCT, SMD), precision resistors (1%, 0.1%), capacitors (MKT/styroflex), inductors (Neosid, Toko), transducers, enclosures (Telet, OKW) and quartz crystals.


FOR FURTHER INFORMATION,
 PLEASE SEND A BUSINESS-SIZE
 SASE TO OLD COLONY SOUND LAB
 (ADDRESS ABOVE), ATTN: MEEK IT.

S-VHS/CVBS-TO-RGB CONVERTER

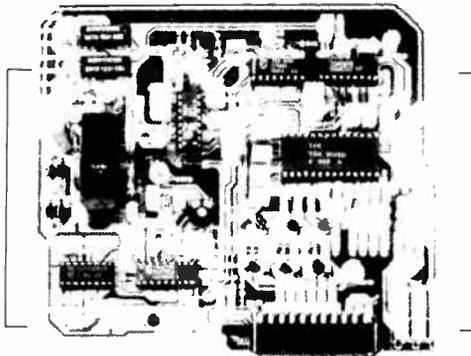

Following last month's introduction into the main characteristics of the Super-VHS system, we close off the article with details of a practical converter circuit that allows an S-VHS-VRC or camcorder to be connected to the RGB inputs of a colour TV or monitor. The circuit presented here forms a state-of-the-art approach to all-analogue picture standard conversion, and is based on the latest in IC technology available for this purpose.


220.039 **\$150**

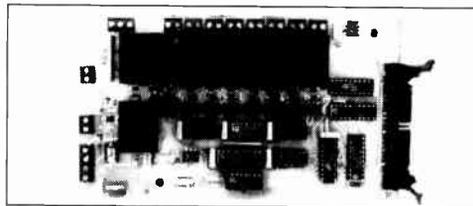

MICROPROCESSOR-CONTROLLED TELEPHONE EXCHANGE

The telephone exchange presented here allows up to eight pulse-dialling telephone sets to be connected, and has an option for connecting calls to or from an external (trunk) telephone line. The unit is controlled by the popular 8052-based BASIC computer we introduced a few years ago.

220.057 **\$190**

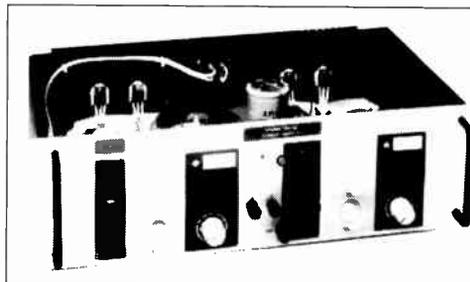

400-WATT LABORATORY POWER SUPPLY

Here is an all-purpose d.c. power supply for symmetrical as well as asymmetrical use, and capable of supplying high output currents and voltages. An all-analogue design based on discrete parts only, this 400-watt PSU deserves a prominent place on your work bench.

ex. case 220.036 **\$525**

WorldRadioHistory

MEEK IT

ELECTRONICS
 THE HAGUE HOLLAND

AVAILABLE FROM:

OLD COLONY SOUND LAB

PO Box 243, Dept E91
 Peterborough, NH 03458 USA
 24-Hour Lines:
 Tel. (603) 924-6371 FAX (603) 924-9467

- Check, money order, MC/VISA accepted.
- Please allow 6-8 weeks for delivery.
- **SHIPPING:** Airmail shipping to USA included in price. Others: Please inquire.
- **CUSTOMS:** USA residents may be required to pay 5-10% customs duty. Others may vary.



MAIN FEATURES

- 8 internal lines
- 1 external line
- memory for 10 numbers
- internal through connections
- versatile computer control
- automatic hold for external line
- simple-to-extend
- can be interfaced to a PC
- selective external call acceptance
- shortcut dial codes for external number
- works with pulse-dialling telephone sets
- one optional relay for extra switching function

MAIN SPECIFICATIONS

- **Mode: Single**
 - one adjustable power supply with current and voltage controls
 - Output 0 - 40 V at 0 - 5 A
- **Mode: independent**
 - two identical, electrically separated, power supplies
 - Outputs 2 x 0 - 40 V at 2 x 0 - 5 A
- **Mode: Tracking**
 - two identical, series connected, power supplies
 - Outputs $\pm 0 - \pm 40$ V at 0 - 5 A
 0 - 80 V at 0 - 5 A
 - Voltage and current of slave follow master.
- **Mode: parallel**
 - two identical, parallel connected, power supplies.
 - Outputs: 0.6 - 39.4 V at 0 - 10 A
- **Maximum output voltage:**
 0 - 40 V (at full load)
 48 V (no load)
- **Maximum output current:** 5 A
- **Ripple:** 10 mV (no load)
 50 mV (at full load)
- **Voltage difference in tracking mode:** 50 mV

NOW AVAILABLE!

Dealer Inquiries Invited

AUDIO ANTHOLOGY, Volume Four


Edited by C.G. McProud

The 34 articles from 1955-1957 in this fourth collection from *Audio Engineering* magazine take a new tack, emphasizing an overall view of the home sound system and offering guidance on how to plan a system, how to keep it simple, and how to understand and maintain the equipment. Solid state techniques and circuits are introduced here, along with designs for amplifiers and preamps and 6 loudspeakers.

Chapters include: How to Plan Your Hi-Fi System; System Simplicity for Audio; Adequate Audio Power in the Home; Building Simplicity into the Hi-Fi System; The Care and Treatment of Feedback Audio Amplifiers; High Quality Dual-Channel Amplifier; Stereo Monaural Companion Amplifier for the "Preamp with Presence" [Volume Three]; Stereosonic Magnetic Recording Amplifier; High Quality Treble Amplifier; Amplifier Uses Cheap Output Transformer; Effect of the Cathode Capacitor on Push-Pull Output Stages; What's All This About Damping?; Electrical Adjustments in Fitting a New Output Transformer; Which Tube Shall I Use?; Understanding Intermodulation Distortion; The Sad Tale of a Half-Watt Resistor; Compensation for Amplitude-Responsive Phono Pickups; A Versatile Bass-Treble Tone Control; Record Speed and Playing Time; Recording Characteristic Simulator; Transistor Action; Transistor Preamps; Transistor Tips and Techniques; Transistor Preamp for Low-Output Pickups; A Transistor Playback Amplifier; Transistor Tone Control Circuits; A Transistor VU Meter; Distortion in Tape Recording; A Time Delay Commercial Suppressor; Baffles Unbaffled; Ported Loudspeaker Cabinets; The "CW Horn"; The Aperiodic Loudspeaker Enclosure; and The Standard Speaker System.

Heavily illustrated. 1957, 1991, 144pp., 8 1/2 x 11, softbound.

BKAA3/4 \$16.95

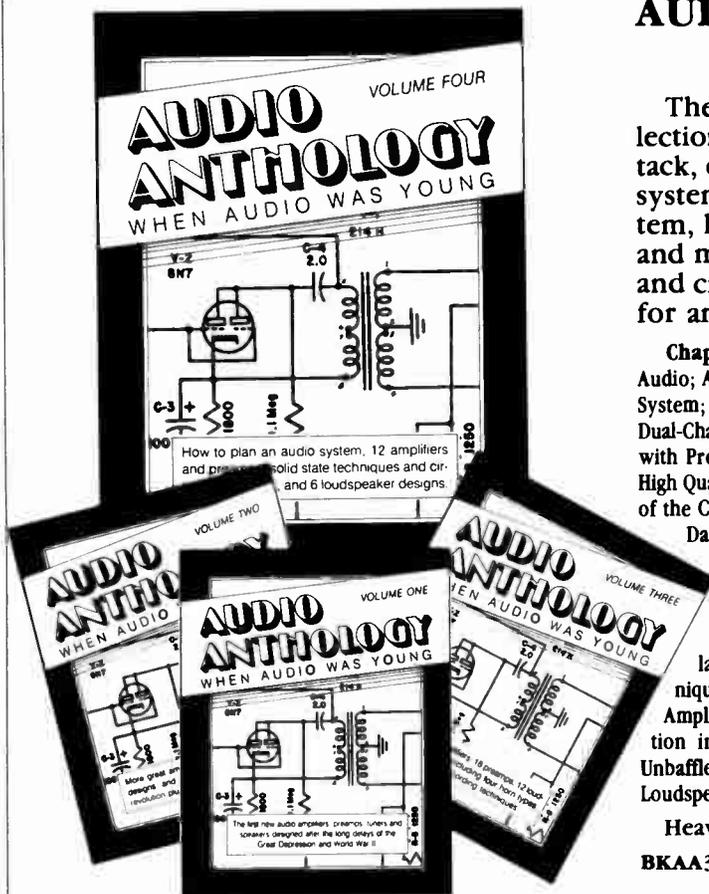

ALSO AVAILABLE!

- BKAA3/1 Audio Anthology, Volume One (1947-50) \$16.95**
- BKAA3/2 Audio Anthology, Volume Two (1950-52) 16.95**
- BKAA3/3 Audio Anthology, Volume Three (1952-55) 16.95**
- BKAA3/X3 Choose any 3 volumes, at a savings of \$8.95! 42.00**
- BKAA3/X4 Complete 4-volume set, at a savings of \$12.85! 54.95**

SHIPPING: In the US, please add \$2 for first book, 75¢ each addl. In Canada, please add \$4.50 for first book, 75¢ each addl. Overseas, please add 20% to order.

PAYMENT BY: MC VISA CHECK/MONEY ORDER

YES! Please send me

| <u>QTY</u> | <u>ITEM</u> | <u>@</u> | <u>\$</u> | <u>=</u> | <u>\$</u> |
|------------|-------------|----------|-----------|----------|-----------|
| _____ | _____ | @ | \$ _____ | = | \$ _____ |
| _____ | _____ | @ | _____ | = | _____ |

Please circle the books you have ordered:
 Vol. 1 Vol. 2 Vol. 3 Vol. 4

SHIPPING = _____

TOTAL ORDER = \$ _____



OLD COLONY SOUND LABORATORY

PO Box 243, Dept. E91
 Peterborough, NH 03458

24-Hour Lines:
 Tel. (603) 924-6371
 FAX (603) 924-9467

NAME _____ MAGIC NO. _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

MASTERCARD OR VISA NO. _____ EXPIRATION DATE _____

DAYTIME TELEPHONE NO. _____ TODAY'S DATE _____

FOREIGN CHECKS MUST BE IN US FUNDS DRAWN ON US BANK.

CALL OR WRITE FOR YOUR FREE CATALOG TODAY!

Courteous Service • Discount Prices • Fast Shipping
ALL ELECTRONICS CORP.
 P.O. Box 567 • Van Nuys, CA 91408

HIGHEST QUALITY METAL CASSETTES (ERASED)

Premium quality metal tape in C-60 and C-90 cassettes (30 or 45 min. per side). One of the finest "brand-name" tapes on the market, in durable, clear plastic transport mechanisms. Recorded and bulk erased, the record-protect tabs have been removed and therefore, need to be taped over to re-record. Audiophiles will appreciate the wide dynamic range of this tape. If your cassette deck has a "metal" setting you will hear the difference. A real bargain!
 60 min. tape - CAT# C-60M \$1.25 each - 10 for \$10.00
 90 min. tape - CAT# C-90M \$1.65 each - 10 for \$15.00



CASSETTE STORAGE CASE

Black, unbreakable plastic audio cassette storage case.
 CAT# CBOX 5 for \$1.00 • 100 for \$15.00



TOUCH DIMMER

The "brain" part of the "LITE TOUCH" touch dimmer, when connected to any lamp, will turn it on and off and change the brightness level when any metal part is touched. We don't have the wiring harness that originally connected this to the lamp, but we can provide a simple hook-up diagram and instruction sheet. The solid-state circuitry is contained in a thermo-plastic box 1.91" X 3.11" X 0.835".
 CAT# DMR-1 \$3.50 each



SWITCHES

SPDT Mini-Toggle (Flat Handle)
 C&K # 7101 or equivalent. Standard size SPDT mini-toggle switch with flat lever handle. 1/4-40 threaded bushing. Solder loop terminals. Rated 5 amps @ 125 Vac.
 CAT# MTS-14 \$1.35 each



SPST N.O. Pushbutton
 -SPST normally open p.c. mount pushbutton. 0.47" square mounting pad. Plunger extends 0.47" above surface. No pushbutton cap available. Ideal, inexpensive switch where look is not important. 4 p.c. pins on 0.2" X 0.5" mounting centers.
 CAT# PB-35 5 for \$1.00



OPTO SENSOR

GE H1381 U-shaped opto with 0.125" gap between emitter and sensor. 0.75" mounting centers.
 CAT# OSU-11 2 for \$1.00



Mini Snap-Action Switch
 Omron D2F-L Miniature snap-action switch with lever. Rated 1 amp @ 125 Vac. 0.50" L X 0.26" H X 0.22" W. Lever extends 0.05" beyond end of switch.
 CAT# SMS-282 75c each 10 for \$6.50



Special Reduced Price PHOTOFLASH CAPACITOR

Rubicon CE 210 Mfd 330 Volt photoflash capacitor. 0.79" dia. X 1.1" high. These are new capacitors that have been prepped with 1.4" black and red wire leads soldered to the terminals.
 CAT# PPC-210 \$1.25 each 10 for \$11.00 • 100 for \$100.00



AUDIO SLIDE POT

Dual 1K audio 3 1/2" long, 2 1/2" slide.
 CAT# ASP-1KD Reduced to 50c each • 100 for \$40.00



WALL TRANSFORMER

12 Vdc 500 ma.
 2.1mm D.C. power plug with center negative. White case.
 CAT# DCTX-125W \$4.50 each
12 Vdc., 200 ma.
 2.1 mm D.C. power plug with center negative.
 CAT# DCTX-122 \$3.00 each



20 AMP RF/EMI FILTER

Corcom# 20B8 20 amp RF/EMI general purpose common-mode filter. Controls line-to-ground noise. Small size, low leakage. 3.48" X 1.16" X 2.81". UL and CSA listed.
 CAT# RRF-201 \$8.50 each



4PDT - 24 Vdc RELAY

24 Vdc, 650 ohm coil - 3 amp contacts Standard 14 pin (ICE CUBE) style. Plastic dust cover. Size: 1 1/4" X 1 3/4" X 7/8" CAT# 4PRLY-24N \$4.00 each



HEAT SINK COMPOUND

G C Electronics # 10-8109 - For effective transfer of heat between components and heat sinks. 29 silicone heat sink compound. CAT# HSC-1 \$2.00 per 1 oz tube



TOLL FREE ORDER LINES
1-800-826-5432
 CHARGE ORDERS to Visa, MasterCard or Discover


TERMS: Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (7 1/4, 7 1/2, 7 3/4 or 8 1/4%).

Quantities Limited. NO C.O.D. Prices subject to change without notice.
CALL OR WRITE FOR OUR FREE 64 PAGE CATALOG
ALL ELECTRONICS CORPORATION
 P.O. Box 567 • Van Nuys, CA • 91408

★ ANNOUNCING ★
 ★ 133rd SMPTE ★
 ★ Technical Conference and Equipment Exhibit ★
 The Conference That Defines Motion Picture and Television Technologies

October 26, 27, 28, 29, 1991
 Los Angeles Convention Center

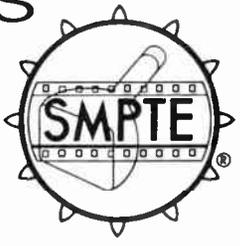Seminars
Meetings
Papers
Tutorials
Exhibits



Friday Tutorial
 Weekend Workshops
 Daily Technical Papers
 Daily Equipment Exhibits
 Daily Social Events

Who Will Attend?

- Presidents, CEOs Owners
- Sales & Marketing VPs
- Consultants
- Directors of Operations
- Students
- Cameramen
- Designers
- Producers
- Marketing Managers
- Publishers
- Chief Engineers
- A/V Technicians
- Systems Engineers
- Technical Supervisors
- TV Maintenance Supervisors
- Production Managers
- Graphic Artists
- Tape Editors
- Video Editors
- Digital Effects Designers

For More Information, Mail To:
 Society of Motion Picture and Television Engineers
 595 W. Hartsdale Ave., White Plains, NY 10607
 (914) 761-1100 • Fax # 914-761-3115

PLEASE RUSH THE FOLLOWING INFORMATION:
 Exhibitor Full Conference Registration
 Exhibit Only Tutorial Seminar Workshop

Name _____ Title _____
 Co. _____
 Street _____ City _____
 State _____ Zip _____ Country _____
 Tel. _____ Fax _____

OLD COLONY'S USER-FRIENDLY SOFTWARE

BULLOCK & WHITE

Speaker Designer™

Release 1.2 by Stuart E. Bonney

A loudspeaker system design aid and modeling tool for use with both closed and vented systems over the frequency range from 10 to 300Hz. Computes and displays system frequency response, power handling capabilities, and relative sound pressure level (SPL) outputs for each of 26 discrete frequencies over this range. Includes one year support by the author when the user registers this Shareware product. Each **\$19.50**

IBM 5¼" 360K DS/DD 8PD-1B5

Loudspeaker Modeling Program

by Ralph Gonzalez (SB 1, 2, 3/87)

LMP produces a full-range frequency response prediction for multi-way loudspeakers, including the effect of the crossover, driver rolloffs, interdriver time delay, "diffraction loss," etc. (Includes author support.) Each **\$17.50**

Specify:

Apple II 5¼" SS/DD (DOS 3.3) LMP-1A5
Apple Macintosh 3¼" SS/DD LMP-2M3G
IBM PC/XT/AT 5¼" DS/DD LMP-2B5G
Commodore 64 5¼" DS/DD LMP-1C5

"Sounded-Up" LMP provides professional-quality graphics and a fast, friendly, user interface. Remains compatible with LMP data files and is available for IBM PC (CGA, EGA, VGA, or Hercules graphics) and Macintosh computers. The Macintosh version also provides square wave analysis with audible output. Each **\$49.50** (upgrade price: \$39.50*)

Specify:

IBM PC/XT/AT 5¼" DS/DD LMP-3B5G
Apple Macintosh 3¼" SS/DD LMP-3M3G

*Original LMP disk or sales receipt must be included w/ order.

Driver Evaluation and Crossover Design

by G. R. Koonce (SB 5/88)

Disk 1 evaluates the suitability of drivers for closed, vented and passive radiator enclosures, and allows detailed designs of vented boxes.

Disk 2, in addition to driver evaluations, allows the design of first-, second-, and third-order crossovers. 5¼" IBM: 360K, DS/DD. Each **\$12.50**

Specify:

Driver Evaluations DRI-1B5
Crossover Design CRS-1B5

Active Filter Design

by Fernando Garcia Viesca (SB 4/88)

Calculates component values for Butterworth filters in four configurations: High- and low-pass in second- and third-order. (Includes author support.) Each **\$17.50**

IBM 5¼" 360K DS/DD ACT-1B5

Two-Way Active Crossover Design

by Gary Galo (SB 5/88)

Performs the calculations for the eight two-way active crossover designs described by Bob Bullock using formulas exactly as given in the articles; plus a program to calculate V_{TH} . (Includes one year user support.) Each **\$20**

Specify:

IBM 5¼" 360K DS/DD TWO-1B5
IBM 3¼" 720K DS/DD TWO-1B3

Stepped Volume Controls

by Joseph O'Connell (TAA 4/88)

These ready-to-run Mac programs come on a 3½-inch SS/DD disk initialized as a 400K disk for compatibility with all machines. Also included are the Pascal source codes, should you wish to customize them for your own use. Program A. Precisely matches the resistor values to the measured or estimated source and load impedances, yielding great accuracy. Your volume control can have 3 to 99 positions. The program will ask you how many dB each step should be attenuated and has provisions for a standard audio taper or any other taper you devise. Program B. Calculates the taper that will result with your actual resistor values, because you are limited to standard values or with series and parallel combinations. It can also show the effects of different source and load impedances on the taper. Both programs (contained on the same disk) allow you to save their output to a text file and include author support via mail. Each **\$25**

Apple Macintosh 3¼" SS/DD SVC-1M3

BOXRESPONSE

Model-based performance data for either closed-box or vented-box loudspeakers with or without a first- or second-order electrical high pass filter as an active equalizer [SB 1/84]. The program disk also contains seven additional programs as follows:

Air Core: This program was written as a quick way of evaluating the resistance effects of different gauge wire on a given value inductor. The basis for the program is an article in *Speaker Builder* 1/83, pp. 13-14) by Max Knittel. The program asks for the inductor value in millihenries (mH) and the gauge wire to be used. (NOTE: only gauges 16-38.)

Series Notch: Developed to study the effects of notch filters in the schematics of some manufacturers. Enter the components of the network in whole numbers (i.e., 10 for 10µF and 1.5 for 1.5mH) and indicate whether you want one or two octaves on either side of resonance. Output is frequency, phase angle and dB loss.

Stabilizer 1: Calculates the resistor-capacitor values needed to compensate for a known voice coil inductance and driver DC resistance.

Optimum Box: A quick program based on Thiele/Small to predict the proper vented box size, tuning and -3dB down point. It is based only on small signal parameters, therefore, it is only an estimate of the response at low power (i.e., limited excursion).

Response Function: Calculates the small signal response curve of a given box/driver combination after inputting the free-air resonance of the driver (f_s), the overall "Q" of the driver (Q_{TS}), the equivalent volume of air equal to the suspension (V_{AS}), the box tuning frequency (f_B), and the box volume (V_B). Output is the frequency and relative output at that frequency.

L-Pad Program by Glenn Phillips: Appeared in *Speaker Builder* 2/83, pp. 20-22). It is useful for padding down a tweeter or midrange while still retaining the same load as the driver itself.

Vent Computation by Glenn Phillips: Calculates the needed vent length for 1, 2 or 4 ports of the same diameter. Input box volume in cubic feet and required tuning frequency (f_B), output is vent length and vent area for each case.

Medium: 5¼" SS/DD Disk. Price, **\$25**.

Specify:

BOXRESPONSE

Apple BOX-1A5
Commodore 64 (Disk) BOX-1C5
Commodore 64 (Cassette) BOX-3CC
IBM BOX-1B5

IBM Plus Graphics

BOXRESPONSE BOX-2B5G **\$50**

PASSIVE CROSSOVER

This disk is a result of Mr. Bullock's extensive research concerning first-, second-, third-, and fourth-order passive crossovers in *Speaker Builder* 1, 2 & 3/85; **\$25**

Specify:

PASSIVE CROSSOVER CAD

Apple PAS-1A5
Commodore 64 (Disk) PAS-1C5
IBM PAS-1B5

IBM Plus Graphics

CROSSOVER CAD 5¼" demo PXO-3B5GD **\$ 5***
CROSSOVER CAD PXO-3B5G **\$50**

CALSOD

Computer-Aided Loudspeaker System Optimization and Design by Witold Waldman

CALSOD is a new entry into the field of crossover network optimizing software available for the IBM PC desktop computer. It combines the transfer function of an LC network with the acoustic transfer function of the loudspeaker, by using some form of iterative analysis. CALSOD creates, through the process of trial-and-error curve fitting, a suitable transfer function model which it can then optimize. The program is the subject of CALSOD author Witold Waldman's research paper "Simulation and Optimization of Multiway Loudspeaker Systems Using a Personal Computer" which appeared in the *Audio Engineering Society Journal* for September 1988, pp. 651-663. CALSOD differs considerably from other software since it models the entire loudspeaker output of a multiway system, including the low-end response, and the summed responses of each system driver.

The program performs a lot of tricks. One of the more spectacular of these allows the designer to specify the location of the driver acoustic centers using an XYZ coordinate system. Thus, if the designer ex-

pects to mount a driver combination on a flat baffle, the summed response can be optimized to compensate for rearward displacement of a woofer's acoustic center with respect to a tweeter. CALSOD can model up to seven drivers at a time in a four-way system giving the summed response and acoustic phase response of the entire system.

The CALSOD program comes on a single 360K floppy, and requires one directory and two subdirectories in installation, plus access to the DOS GRAPTABL file, which it uses for a couple of special symbols. The 133-page User Manual, provided on a second disk, is well written, adequately describes the various program functions, and contains an excellent tutorial example, which demonstrates the use of the program.

Specify:

IBM 5¼" DEMO CAL-2B6D **\$ 5.00***
IBM 3¼" DEMO CAL-2B4D **\$ 6.00***
IBM 2 x 5¼" 360K DS/DD .. CAL-2B6 **\$65.00**
IBM 3¼" 720K DS/DD CAL-2B4 **\$67.50**

* Usable as credit toward later purchase of full package.

NOTE: OLD COLONY SOFTWARE SHOWN ON THIS PAGE IS NOT RETURNABLE FOR REFUND OR CREDIT. ALSO, BECAUSE OF UNREASONABLE TAXATION REQUIREMENTS BY THEIR STATE, WE REGRETFULLY ARE UNABLE TO SELL SOFTWARE TO RESIDENTS OF CONNECTICUT.

POSTAGE & HANDLING: In US, please add \$2.00 for first disk and 75¢ each additional disk. In Canada, please add \$4.50 for first disk, 75¢ each additional. Overseas, please include 20% of total order for shipping.

DEALER INQUIRIES INVITED

CALL OR WRITE FOR YOUR FREE CATALOG!

ELEKTOR ELECTRONICS USA OCTOBER 1991



WorldRadioHistory

OLD COLONY SOUND LAB

PO Box 243, Dept. E91, Peterborough, New Hampshire 03458 USA
(603) 924-6371 / FAX: (603) 924-9467

Answering machine for credit card orders only: (603) 924-6371
before 9:00 a.m., after 4:00 p.m. and weekends.
Have information plus MC/VISA available.

SCIENTIFIC TRAVELS IN REAL AND VIRTUAL WORLDS

AN exciting new world is being built in Britain that appears, in some respects, to be a fantasy, straight from the pages of a science fiction novel, but it is utterly unlike the worlds envisaged by classic SF writers such as H.G. Wells and Jules Verne—it is the world of Virtual Reality.

Virtual Reality (VR) is a fast-growing branch of Information Technology (IT), one of Britain's strongest suits in today's competitive research market. VR is entirely computer-generated and is as like the real world as computer graphics can make it.

In its simplest form, VR is experienced by one person wearing a pilot-style helmet that seals the senses off from the outside world. A typical VR helmet contains two VDU screens, filling the visual field with a computer-simulated landscape fed via cables from a powerful, specially-programmed computer. The computer reacts to head movements by updating the visual display inside the helmet so the wearer feels as if he or she is surveying an actual landscape.

In some sophisticated VR systems, the participant also wears a special glove that relays hand movements to the computer. In these systems, a hand depicted in computer graphics also appears in the visual display inside the helmet.

Thus, if you reach out to touch a virtual object in the virtual reality environment, you see your virtual hand mimic the movements of your real one. Some gloves are also equipped to give the wearer an impression of touch and weight so that objects in the simulated world can be apparently caught and held, as if they had physical substance.

Serious application

In more complicated systems, two or more people can interact and, because the virtual world is entirely computer-generated, dis-

ance is no object. Delegates at a conference in the United States recently watched VDU screens in amazement as two people in different cities shook hands in VR via linked computers and, of course, the indispensable helmet and gloves.

Two British companies are among the front-runners in this strange new technology. One, Advanced Robotics Research of Salford is developing remote-controlled vehicles that can be manoeuvred in VR by a



Helmet-mounted display system as used in 'virtual reality' experiments at Advanced Robotics Research Ltd.

driver sitting somewhere else.

This has the serious practical aim of piloting vehicles into hostile environments, such as the cores of nuclear reactors or submerged wrecks, without exposing a driver to obvious danger. He or she will view a virtual environment fed from sensors on the vehicle itself.

The other company, W Industries of Leicester, is exploring VR's potential for entertainment. It has launched a machine of-

fering a variety of simulated experiences that can be enjoyed in a purpose-built seat equipped with two joysticks and a helmet (called a Visette) wired for sound.

One of the offered experiences is that of piloting a Harrier jump-jet on a fighter mission involving attack by enemy aircraft, mid-air refuelling, and a hair-raising landing on the deck of an aircraft carrier.

Improving computers

Designers will soon be able to experience their designs at simulated first hand. Architects will enter VR to walk around their building on the other side of the world at the planning stage. In the United States, surgeons are already experimenting with safe virtual worlds in which they can practise virtual operations on virtual patients, before trying their hand at the real thing.

Meanwhile, British computer scientists are trying to make computers more powerful. A team at Essex University has begun looking for ways to change the basic logical structure of computers, which has changed surprisingly little in the past 25 years.

Professor S.H. Lavington believes that, although silicon chip technology is slowly making computers faster and cheaper, many computers and their languages are becoming inadequate for solving many of the problems now confronting science and industry. The inadequacies, he says, relate not only to shortcomings in performance, as measured, for instance, by speed of execution, but to the time and effort taken to produce error-free programs.

Solutions being investigated include various forms of parallel processing in which information can be fed into linked computers simultaneously, allowing them to divide processing tasks between them for greater speed and accuracy. ■

| | | | |
|---|---|--|---|
| <p>Published by Audio Amateur Publications, Inc.</p> <p>Editor/publisher: Edward T. Dell, Jr.</p> <p>Editorial Offices: 305 Union St., P.O. Box 876 Peterborough, NH 03458-0876 USA</p> <p>Telephone: 603-924-9464 (National) or +1 (603) 924-9464 (International)</p> <p>FAX: (603) 924-9467 (National) or +1 (603) 924-9467 (International)</p> <p>Advertising: Donald B. Kennedy Telephone: (617) 383-9059</p> <p>FAX: (603) 924-9467</p> <p>Subscriptions: Katharine Gadwah Elektor Electronics USA Post Office Box 876, Peterborough, New Hampshire 03458</p> <p>Subscriptions to Elektor Electronics USA are available ONLY in the fifty United States, Canada, Puerto Rico, the Virgin Islands and those Pacific territories administered by the United States of America.</p> | <p>European Offices: Elektuur BV Postbus 75 6190 AB BEEK The Netherlands Telephone: 011 31 4638 9444 Telex: 56617 (elekt nl) FAX: 011 31 4637 0161</p> <p>Managing Director: M.M.J. Landman</p> <p>Overseas Editions: FRANCE Elektor sarl Les Trois Tilleuls B.P. 59; 59850 NIEPPE Editors: D.R.S. Meyer G.C.P. Raedersdorf</p> <p>GERMANY Elektor Verlag GmbH Susterfeld Strasse 25 5100 AACHEN Editor: E.J.A. Krempelsauer</p> <p>GREECE Elektor EPE Kariskaki 14 16673 Voula—Athens Editor: E. Xanthoulis</p> | <p>HUNGARY Elektor Elektronikai folyóirat 1015 Budapest Batthyány U. 13. Editor: Lakatos Andras</p> <p>INDIA Elektor Electronics PVT Ltd Chhotani Building 52C, Proctor Road, Grant Road (E) BOMBAY 400 007 Editor: Surendra Iyer</p> <p>ISRAEL Elektorcal P O Box 41096 TEL AVIV 61410 Publisher: M. Avraham</p> <p>NETHERLANDS Elektuur BV Peter Treckpoelstraat 2-4 6191 VK BEEK Editor: P.E.L. Kersemakers</p> <p>PORTUGAL Ferreira & Bento Lda. R.D. Estef-83-nl, 32-1° 1000 LISBOA Editor: Jeremias Sequeira</p> | <p>SPAIN Resistor Electronica Aplicada Calle Maudes 15 Entio C. 28003 MADRID Editor: Agustin Gonzales Buelta</p> <p>SWEDEN Electronic Press AB Box 5505 14105 HUDDINGE Editor: Bill Cedrum</p> <p>UNITED KINGDOM Down House Broomhill Road LONDON SW18 4JQ England UK Editor/Publisher: Len Seymour</p> |
|---|---|--|---|

Printed in the United States of America.
ISSN: 1051-5690

LOW NOISE PREAMP IC TO SIMPLIFY SYSTEM DESIGN

Analog Devices' SSM-2017, an audio pre-amplifier featuring ultralow input noise, is a fully integrated microphone preamplifier that replaces discrete solutions made from up to 20 passive components, four transistors, and an op amp. Housed in an 8-pin mini-DIP, the SSM-2017 requires only one external gain-set resistor, from which you can program gains from 1 to more than 1,000. Applications include audio mix consoles, intercom/paging systems, digital audio systems, automotive differential gain stages, and sonar equipment.

Initially released in an 8-pin cerdip, the SSM-2017 will also become available in 8-pin plastic mini-DIP and 16-pin surface-mount packages. All devices are guaranteed for operation over the extended industrial temperature range of -40 to $+85^{\circ}\text{C}$. Prices begin at \$1.80 in 100s.

For more information, contact Dan Parks, Analog Devices, Inc., Precision Monolithics Division, 1500 Space Park Dr., Santa Clara, CA 95052, (408) 562-7513.



MACSPEAKERZ HAS ADDED RESPONSES AND CALCULATORS

True Image has announced version 2.0 of MacSpeakerz, a loudspeaker design application for the Macintosh. In addition to frequency response, this version calculates and displays cone excursion, impedance, phase, and group delay responses for loudspeaker drivers in a closed or vented enclosure. Version 2.0 also includes an array of interactive loudspeaker calculators, each dedicated to a particular aspect of loudspeaker design.

The program requires 512K of memory and one 800K disk drive. It is fully compatible with System 7.

MacSpeakerz 2.0 will be shown at the Acoustical Supply International booth during the 91st convention of the Audio Engineering Society to be held in New York City October 4-7. It sells for \$299. Registered users can get upgrades at a discount.

For more information, contact Sharon Alsup, True Image, 349 W. Felicita Ave., Suite 122, Escondido, CA 92025, (619) 480-8961.

ELECTRONICS SCENE

NEW METALLIZED MULTICAP

MIT has introduced a metallized version of its MultiCap capacitor, designed for use in audio products to eliminate the distortions to music caused by parasitics in capacitors.

The metallized MultiCap is recommended for low-current applications such as preamps, amps, and electronic circuits. They offer the same precision in design and construction, the same patented coaxial structure, and the same sonics found in the film-and-foil MultiCap. Each unit contains multiple paralleled capacitors optimized into one package.

For more information, contact Music Interface Technologies, 3037 Grass Valley Hwy., Suite 8212, Auburn, CA 95603, (916) 883-1186, FAX (916) 823-0810.

SECURITY HEX DRIVE BIT SETS

A variety of $\frac{1}{4}$ " security-type hex drive bit sets are available from Jensen Tools for servicing equipment protected by manufacturer-installed security screws. The sets available include a four-piece set of spanner bits, a four-piece tri-wing security bit set, a two-piece T-5 Torx bit set for Compaq laptop computers, and a 10-piece security hex bit set for manual use or for use with cordless tools.

Jensen also offers a Security Flex-A-Bit set containing a $7\frac{1}{2}$ " flexible extension for cordless screwdrivers and drills, a magnetic bit holder, and a selection of bits from the sets above, including #8 and #10 spanner bits, TT15 and TT20 security Torx bits, $\frac{5}{32}$ and $\frac{3}{16}$ security hex bits, and #2 and #3 tri-wing bits.

Sets are featured in Jensen's "Q" Catalog Supplement. For more information, request a free copy from Jensen Tools Inc., 7815 S. 46th St., Phoenix, AZ 85044, (602) 968-6231.




PCBoards LAYOUT SOFTWARE

PCBoards version 1.7 now supports Hercules, CGA, EGA, VGA, and Super VGA. The software runs on any IBM PC or compatible with 384K RAM and one disk drive. With its 1x generated artwork, you can make your own films for producing high-quality prototype boards; 2x artwork is generated for production quality. You can produce single- or double-sided boards.

PCBoards Layout has output for dot-matrix (9 and 24 pin) and laser printers and for pen plotters. You can also print to a file. A stand-alone program, it also has two companion programs: PCRoute (the autorouter) and SuperCAD (a schematic capture program).

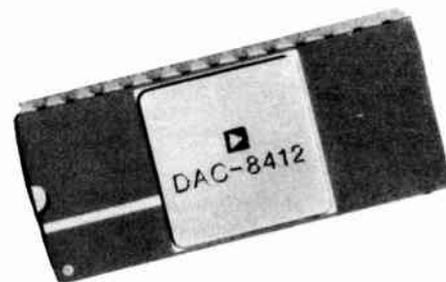PCBoards Layout, PCRoute, and SuperCAD each sells for \$99. To download demos, call (205) 933-2954. For more information, contact PCBoards, 2110 14th Ave. S., Birmingham, AL 35205, (205) 933-1122.



12-BIT DACs OPERATE FROM 5V SUPPLY

Requiring a single +5V supply, Analog Devices' DAC-8412 and DAC-8413 12-bit digital/analog converters eliminate the need for a negative supply used solely for analog I/O. This monolithic device provides four independent analog outputs, sharing a common bus interface (with 70nS access time) and digital readback. The DACs also provide bipolar outputs when powered from dual (up to $\pm 15\text{V}$) supplies. Applications include automatic test equipment, servo control, military and aerospace systems, and industrial process control.

Integral nonlinearity is $\frac{1}{4}$ LSB (typical) and $\frac{1}{2}$ LSB maximum over the -40 to $+85^{\circ}\text{C}$ temperature range. The output span of these DACs is set by the user-supplied high and low references; reference voltages can be from $+2.5$ to $\pm 10\text{V}$. Power dissipation is less than 60mW for +5V operation and less than 330mW with $\pm 15\text{V}$ supplies. The DAC-8412 has "reset to center scale" operation, the DAC-8413 resets to minimum scale.

Available in 28-pin plastic DIP, cerdip, PLCC, and LCC packages, the DACs prices start at \$34.50. For more information, contact Analog Devices Inc., 181 Ballardvale St., Wilmington, MA 01887, (617) 937-1428.

DIFFERENTIAL EQUATION SOLVER ENCOURAGES EXPERIMENTATION

MicroMath has announced DIFFEQ, an ordinary differential equation solver for IBM PCs or compatibles. Features include a graphics user interface and drop-down menus (with optional mouse support) and import/export of Excel, Lotus, dBase, DIF, or ASCII files. The program includes several methods for solving models and EMS and XMS memory support. Output is to dot matrix, laser, and PostScript printers.

For more information, contact MicroMath Scientific Software, PO Box 21550, Salt Lake City, UT 84121, (801) 943-0290, FAX (801) 943-0299.

TEST/SERVICE SYSTEM REPLACES CONVENTIONAL INSTRUMENTS

Neutrik's A1 Audio Test and Service System contains a sweepable generator, analyzer, and oscilloscope. It measures wow and flutter, noise, crosstalk, frequency, and THD +N. A large backlit LCD shows single measurements numerically or as sweeps in graphical form. Hard copies of screens are available when connected to most standard dot-matrix printers. For more information, call (908) 901-9488.

AN AMATEUR REMOTE IMAGING SOCIETY PUBLICATION

The Amateur Remote Imaging Society (ARIS) publishes *WeatherSat Ink*, a journal devoted to environmental satellite applications by amateurs. ARIS goals are to educate, inform, and share applications and techniques for receiving and using all forms of imagery from environmental satellites.


The journal is published quarterly on each solstice and equinox. Membership is \$15 per year or \$20 foreign in US funds. For more information, contact Tom Glembocki, Editor, *WeatherSat Ink*, 4821 Jessie Dr., Apex, NC 27502.

NEW AUDIO ITEMS FOR 1991 FROM SESCOM

Sescom has available a catalog of new products. It includes new product areas as well as extensions of other product categories. Categories are isolator series, hand-held test equipment, field pro-series, new portables, and rack electronics. For a catalog, contact Sescom, Inc., 2100 Ward Dr., Henderson, NV 89015-4249, (702) 565-3400, FAX (702) 565-4848.



ELECTRONICS SCENE

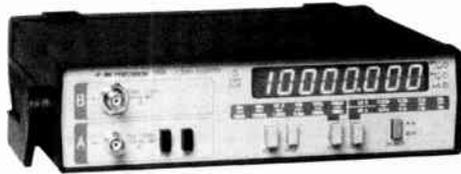

REMOTE CONTROL AND FILE TRANSFER SOFTWARE

Remote-Console has announced version 2.2 of its system software, a remote access communications and control system used to link two PCs, or a PC and H/Z-19 terminal, via modem or by direct cable connection. It provides complete control of the host computer and can be used to run virtually any program or an unattended host computer from a remote location.

The Remote-Console system runs on all IBM PCs including the PS/2 and compatibles, operates with MDA/CGA/EGA/VGA and Hercules video systems, and comes on 5¼" and 3½" disks. It requires DOS 3.0 or higher and internal/external 300, 1,200, or 2,400 baud Hayes-compatible modems. COM ports 1, 2, 3, and 4 are supported. The \$99 price includes host and remote sides. For more information, contact Louis E. Wheeler, PO Box 888, Oceano, CA 93445, (805) 481-5687.

INTELLIGENT DIGITAL MULTIMETER

Global Specialties has announced the PCI-DMM, an intelligent digital multimeter on a card for PCs. The PCI-DMM is a virtual instrument using a plug-in card and software package that can be operated like a benchtop DMM. The card provides the usual functions of the instrument, the software creates an easy-to-use front panel emulation, and the PC gives you intelligence, data storage, and graphics facilities.

You use a mouse to operate the buttons on the computer screen. Add-on instruments like a chart recorder and data logger come standard. The resolution is 4.5 digits, and the functions include AC/DC volts, AC/DC current, resistance, capacitance, and decibels. Other features include relative or absolute measurements, short or long range averaging times, and automatic range selection.

Inputs are isolated to 500V DC and the board is equipped with self-resetting thermal fuses. If you overload the board, it will reset itself once you remove the input.

The PCI-DMM requires an IBM PC/XT/AT/386 or compatible, with 640K RAM and EGA/VGA graphics. The unit sells for \$795. For more information, contact Global Specialties, 70 Fulton Terrace, New Haven, CT 06512, (800) 572-1028.

1.3GHz MULTIFUNCTION COUNTER WITH 0.5 PPM TIMEBASE

A multifunction counter with 5Hz-1.3GHz bandwidth and a TCXO (temperature compensated crystal oscillator) timebase is available from B&K Precision. The Model 1856 has frequency, period, period average, and totalize functions. The timebase has 0.5 PPM stability at 23°C ±5° and 1 PPM stability from 0-50°C.

The device has period measurement capability, which lets you measure tone encoding frequencies used in many communications systems. The period function's range extends from 0.285µS to 0.2S. The 1856 is compatible with 100, 120, 220, or 240V AC ±10% (switch selectable) input voltage. Options include an antenna for checking transmitter frequency and a deluxe 10:1/direct probe. It comes with detachable power cord, schematic, parts list, spare fuses, and instruction manual.

The 1856 sells for \$495. For more information, contact B&K Precision, 6470 W. Cortland St., Chicago, IL 60635, (312) 889-1448.

GET THE SAME COVERAGE WITH PORTABLES THAT YOU GET FROM YOUR MOBILES



Midland Syn-Tech II Vehicular Repeaters


MIDLAND BROCHURE ON VEHICULAR REPEATERS

A four-page color brochure from Midland LMR describes a built-in "vehicular repeater" for the company's Syn-Tech II™ mobile radios. It shows how a low-power portable message is picked up by the vehicular repeater and automatically retransmitted at higher power, giving the portable the same range as the mobile radio in the vehicle. The brochure also discusses a number of options and gives complete specifications on the Midland Syn Tech II vehicular repeater.

For a free copy, contact Midland LMR, Marketing Department, 1690 N. Topping, Kansas City, MO 64120, (800) 643-5263, ext. 1690.

UPGRADE FOR MCS[®] BASIC-52 V1.1 (Part 1)

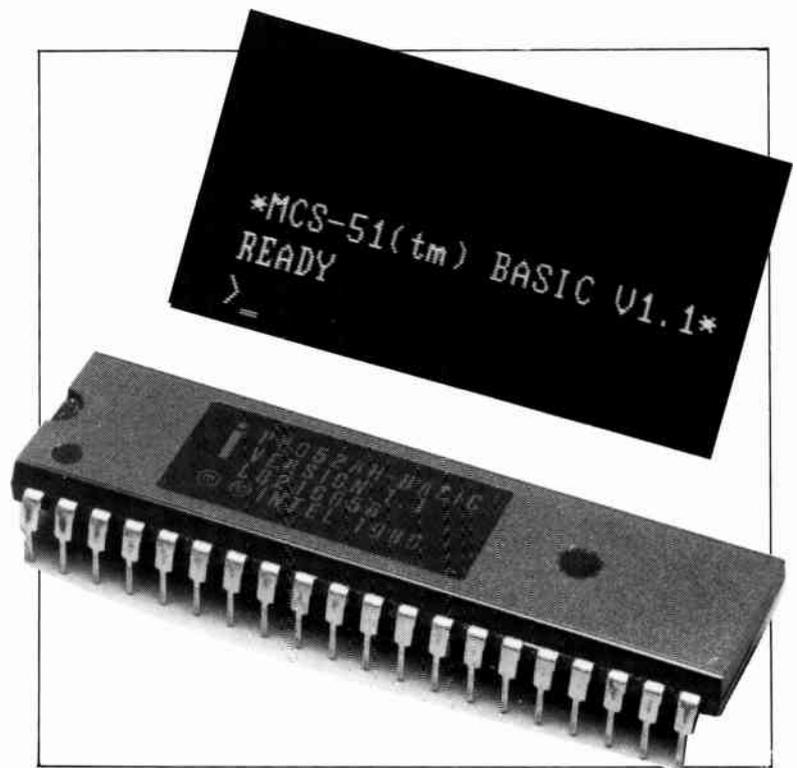The 8052AH-BASIC from Intel is a versatile microcontroller with a powerful BASIC interpreter lurking in its on-board mask-programmed ROM. The authors, having worked with this IC for some time, discovered certain flaws in the BASIC interpreter, and set out to produce a better, faster version that can be run from EPROM.



by Dusan Mudric and Zoran Stojsavljevic

TO be able to make changes to the MCS-52 BASIC interpreter in the 8052AH-BASIC microcontroller, it is necessary to first unload it from the IC. This is done basically as described in an earlier article on the MCS BASIC-52 interpreter, Ref. 1. The result of reading the 8-KByte ROM is a file in Intel-Hex format that contains the machine code of the MCS BASIC-52 interpreter (version 1.1).

MCS BASIC-52 (Ref. 3), extracted from the 8052AH-BASIC V1.1 microcontroller, was disassembled and texts, tables and constants were extracted in order to produce an assembler version of the interpreter. The size of this assembler file was approximately 4,000 lines. Studying the program, we found that the operation of the interpreter could be improved by rewriting certain lines of assembler code. Subsequently, a number of algorithms were developed and substituted for the ones originally implemented by Intel. Furthermore, errors found in a number of routines were corrected.

Floating point nucleus

One of the routines in the BASIC interpreter found to contain programming errors is the floating-point arithmetic nucleus. The errors can be demonstrated by running two small programs:

```
10 a=.10000001E30
20 b=.99999993E29
30 ?a-b
```

The result, 2.74E22, is erroneous, and should be 1.7E22. Similarly,

```
10 a=.10000001E30
20 b=.99999997E29
30 ?a-b
```

| ADDR | CODE | INSTRUCTION |
|-------|--------|--------------------------------------|
| 19F2H | 752A00 | MOV 2AH,#00H ; +000T |
| 19F5H | 71C8 | ACALL 1BC8H |
| 19F7H | 7F04 | MOV R7,#04H ; +004T |
| 19F9H | 792E | MOV R1,#2EH ; +046T |
| 19FBH | 749E | MOV A,#9EH ; +158T |
| 19FDH | C3 | CLR C |
| 19FEH | 9C | SUBB A,R4 |
| 19FFH | D4 | DA A |
| 1A00H | CC | XCH A,R4 |
| 1A01H | 7001 | JNZ 1A04H ; \$ + 03H |
| 1A03H | FC | MOV R4,A |
| 1A04H | B45000 | CJNE A,#50H,1A07H ; +080T ; \$ + 03H |
| 1A07H | 302318 | JNB 23H,1A22H ; \$ + 16H |
| 1A0AH | B3 | CPL C |
| 1A0BH | 5119 | ACALL 1A19H |
| 1A0DH | 5008 | JNC 1A17H ; \$ + 0AH |
| 1A0FH | 052A | INC 2AH |

910128 - 12

Fig. 1. Original floating-point nucleus in the MCS BASIC-52 interpreter.

produces 1.34E22 instead of 1.3E22.

The disassembly listing of the original floating point nucleus developed by Intel is given in Fig. 1, and the version developed by the authors in Fig. 2. When implemented in the BASIC interpreter, the nucleus shown in Fig. 2 produces the correct answers to the above subtractions.

Other corrections

Further improvements were made to the hex-to-BCD conversion routine, both in regard of efficient programming and speed. For example, two approaches are possible for extracting BCD digits a, b, c, d, and e in

$$xyzwH = aD*10000D + bD*1000D + cD*100D + dD*10D + eD*1D$$

These possibilities are:

1. successive extraction of BCD digits starting with the most significant digit, a;
2. successive extraction of BCD digits starting with the least significant digit, e.


If the original version of the hex-to-BCD converter is studied, it is seen that the first procedure is employed. The DPTR is used as a 'weighted register', and the procedure is based on finding a suitably weighted subtraction number from a variable value.

DESIGN IDEAS

The contents of this article are based solely on information obtained from the author and do not imply practical experience by *Elektor Electronics*.

AUDIO SPECTRUM SHIFT TECHNIQUES

Although spectrum shift and spectrum inversion have been known for quite some time as a means of protecting voice links mainly over the telephone, little has been written on the design and operation of the electronics involved. This article aims at offering you a design base and two practical circuits to start experimenting with an interesting form of analogue audio scrambling and descrambling which may be used to, say, personalize a voice link (cassette mail, telephone, wireless babysitter, etc.). Remarkably, you will not be able to tell the difference between the encoder and the decoder until you compare the two units and spot a couple of components with different values.

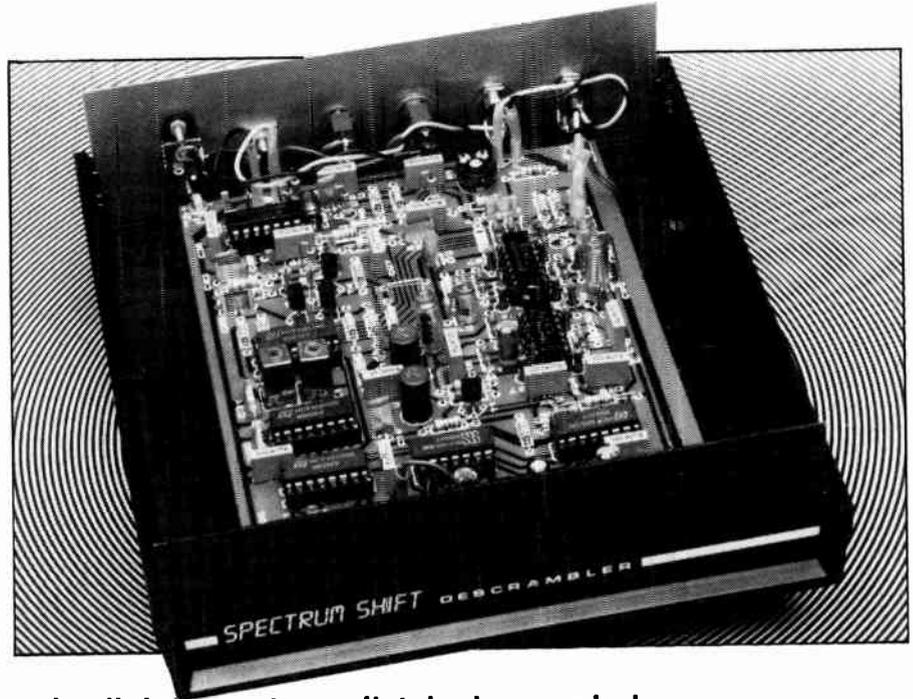

by C. White Halfot

ONE may wonder why analogue audio scrambling is still used when digital encoding systems are relatively simple to implement whilst offering a good degree of security. The reason is simple: digitized audio data requires a bandwidth which is greater than that of the analogue source signal. Thus, where a limited bandwidth is available to convey an audio signal — say, 3 kHz for voice signals, and 15 kHz for music signals — digital encoding is simply out of the question, and different means must be sought to protect the information as it is conveyed from the transmitter to the licensed receiver.

Encoding principle

An all-analogue encoding system is described that renders an audio signal totally unintelligible by shifting the entire spectrum

between 50 Hz and about 10 kHz by 1 to 2 kHz within the existing channel. When the shift is 1 kHz, a source signal of 50 Hz is shifted to 1,050 Hz, while a source signal of 10 kHz is shifted to 11 kHz. In this system, the frequency range below 1,050 Hz is, in principle, empty after encoding. The shift operation is shown diagrammatically in Fig. 1a. Figure 1b shows an alternative version, where the audio spectrum is additionally mirrored around a certain frequency. Both encoding systems yield a new audio signal that is virtually unintelligible, with speech pauses and stress on utterances (i.e., volume variations) as practically the only recognizable features (in fact, we have heard such scrambled signals described as the sound of "a lot of squabbling chipmunks").

Each of the two encoding systems described by Figs. 1a and 1b has its advantages and disadvantages. The second system (Fig. 1b) is simple to realize both at the transmitter and the receiver. However, when applied to an FM (frequency modulation)

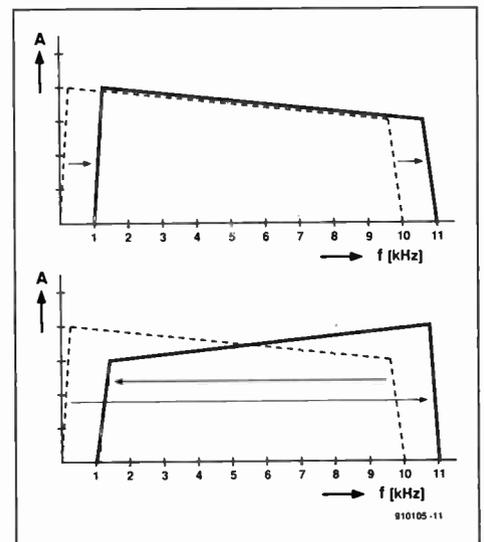


Fig. 1. Principle of spectrum shift (upper drawing) and spectrum inversion (lower drawing). Both techniques are used to scramble audio signals conveyed over air, via cables or magnetic media.

communication link, the signal-to-noise (S/N) ratio at the receiver side suffers because the shifted audio signal contains more high-frequency components than the original (source-) signal. By contrast, when the first encoding system (Fig. 1a) is applied, the bulk of the intelligence is carried by components in the lower part of the spectrum, so that S/N degrading will not occur (in fact, there is psychoacoustic evidence that most information in speech and music is contained in the frequency range from 300 Hz to 1,000 Hz).

The system whose spectrum is shown in Fig. 1a yields almost unintelligible output signals, and is not easy to decode. The decoding process required to restore the signal to its original spectrum can be subdivided into a number of operations as illustrated in Fig. 2. As shown in Fig. 2a, the first function of the decoder is to limit the bandwidth of the encoded signal, i.e., to fit this into a frequency range from 500 Hz to 10 kHz. The filter slope at the high end of the spectrum prevents intermodulation products being generated in the decoding process, while the high-pass filter prevents whistles between 1 kHz and 2 kHz as a result of low-frequency components that are possibly added to the channel.

The block diagram of the decoder (Fig. 3) shows that the input signal is taken through a low-pass filter before it is amplified and applied to a high-pass filter. A switch connected ahead of the output buffer allows the user to select between encoded and non-encoded signals. When the switch is set to 'non-encoded', the input signal is fed direct to the output buffer, i.e., it is not amplified. This is done to ensure that the signal level of non-encoded signals is not changed by the

decoder. Thus, the amplifier merely serves to compensate losses introduced by the phase filters used for encoding or decoding the input signal.

Frequency transforms: Hilbert & Fourier

Shifting an audio spectrum can be achieved in three ways, which are familiar from radio communication techniques used for generating and demodulating SSB (single-sideband) signals. The first two systems are based on narrow-band filters. These are widely applied, and do not present problems with audio signals whose frequency range, for radio communication purposes, extends from 300 Hz to 3,000 Hz only.

Transmitting music via a communication link based on spectrum shifting poses more problems than speech because a much larger frequency spectrum must be conveyed without distortion. It is for this, and other, reasons, that the present encoding system is based on the so-called 'third method', a term familiar to most licensed radio amateurs and radio engineers (Ref. 3).

So how does the encoder work? First, the audio signal is split into two components. Both have the same amplitude, and contain the source signal. The only difference between these components is the phase shift between the frequencies they consist of. This phase shift is 90°, and one of the components is called the Hilbert transform of the other (the two signals are called a Hilbert pair). A Hilbert transform is a frequency shifting operation that unfortunately exists in theory only. In practice, however, a number of systems have been developed that yield close

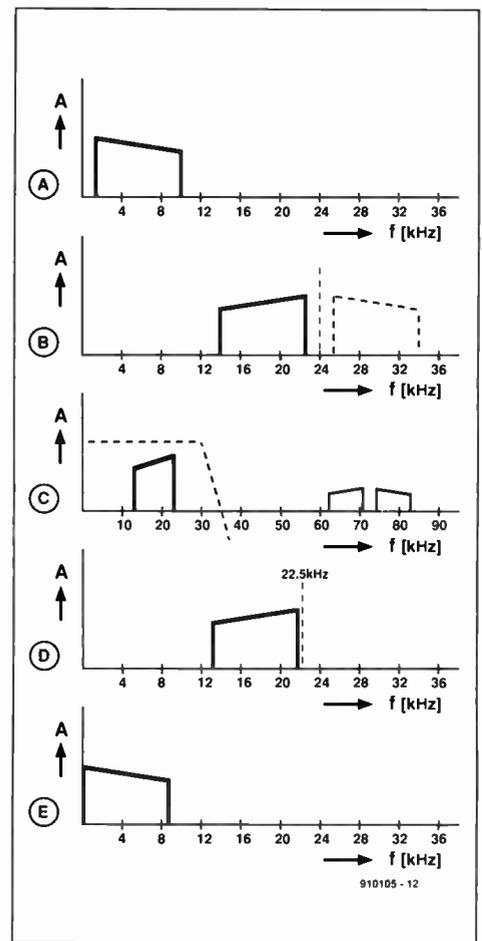


Fig. 2. Multiplication with two phase-locked carriers, filtering and sideband suppression are the main functions into which the decoding process can be subdivided.

approximations of such an ideal transform. One of these systems is applied in the present encoder.

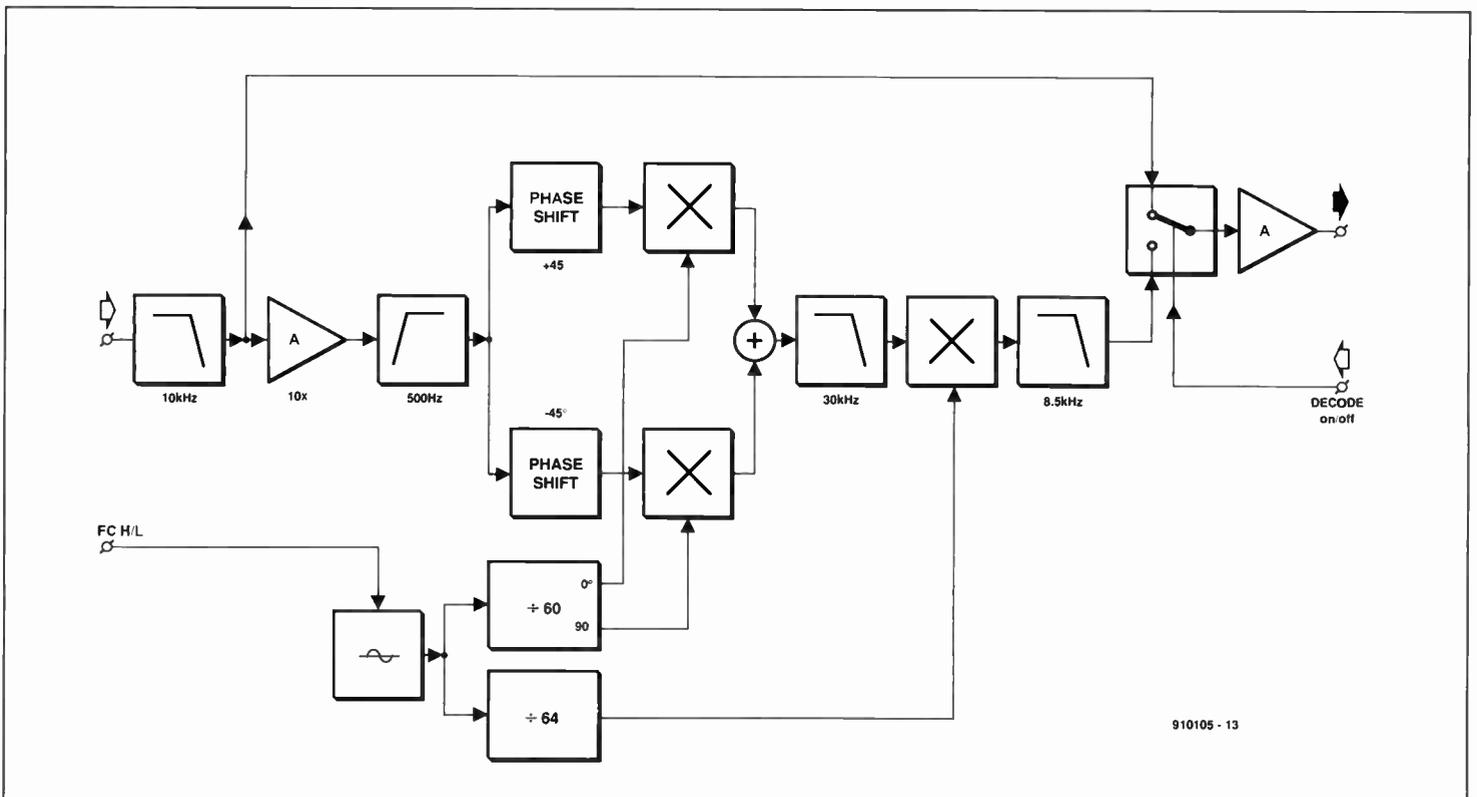


Fig. 3. Block diagram of the frequency shift encoder/decoder. The FC H/L input selects one of two system clocks from which the amount of frequency shift is derived. Note that the encoder/decoder has a bypass function, which is controlled via the S. 0/1 input.

The Hilbert pair is required to suppress one of the sidebands that is generated when the filtered input signal is shifted ('transformed') to a higher frequency. The multiply operation carried out after shifting the phase of the input signal over $+45^\circ$ and -45° gives rise to two double-sideband (DSB) signals. In the decoder, these signals appear around a 24-kHz component — the actual frequency depends on the shift used during the encoding, and will be discussed further on.

As shown in Fig. 2b, one of the sidebands disappears when the two DSB signals are added. The mathematics underlying this operation are shown inset in Fig. 4, a drawing reproduced from an earlier article in this magazine on frequency transformation (Ref. 1). The operations shown in Fig. 4 describe largely what happens in the decoder. The equations go to show that there is no way to avoid a Hilbert transform function when one of the sidebands is to be selected without resorting to (very complex) filters. As shown in Figs. 2b and 2c, the upper sideband is removed in the present design.

Multipliers or double-balanced mixers can take a number of practical shapes. Although their design is mostly plain sailing, they do have to be balanced with the aid of adjustments, and may have insufficient linearity for some applications. Good results at a very small outlay, and without the need of adjustments, can be achieved with electronic analogue bilateral switches, e.g., those contained in the 4053 CMOS multiplexer IC. These switches are particularly well suited to use in the decoder where they enable high suppression of the 24 kHz component to be achieved. When this suppression is insufficient, a 1.5-kHz signal (whistle) would read-

ily appear in the decoded spectrum, corresponding to the amount of frequency shift applied. The main disadvantage of the analogue switches is that they generate a frequency spectrum with spurious components centred around odd-numbered harmonics of the 24-kHz switching signal. It will be recalled that switching is the same as multiplying with a rectangular signal. Thus, in terms of the spectrum, switching can be described as a multiplication with the Fourier series

$$\sin(\omega t) - \frac{1}{3}\sin(3\omega t) + \frac{1}{5}\sin(5\omega t) - \frac{1}{7}\sin(7\omega t) \dots$$

The sidebands of the third harmonic, which are visible in Fig. 2c, are removed with the aid of a low-pass filter designed for a steep roll-off at 30 kHz. This is done to prevent the sidebands causing interference in the mixing operation that restores the original frequency band.

The actual decoding process is relatively simple. As shown in Fig. 2d, the encoded signal is subjected to a second multiply operation, this time with a frequency of 22.5 kHz. The equations in Fig. 4 once more prove that the decoding operation works and yields the desired output signal.

Finally, the decoded signal is taken through a low-pass filter to remove spurious components generated by, among others, the switching mixers.

Which frequencies?

The frequency shift of 1.5 kHz used in the decoder is achieved by first shifting the spectrum to 24 kHz. Next, the spectrum is shifted down again with the aid of a signal of

22.5 kHz, or the difference between 24 kHz and 1.5 kHz. This restores the spectrum to the frequency range it has at the input of the encoder (which may be thousands of miles away, or just round the corner). In other words, we have decoded the scrambled signal. Note that it is also possible to shift the spectrum 'direct' by 1.5 kHz, but not when analogue switches are used as mixers.

Even though a special kind of frequency synthesis had to be implemented to ensure the required stability of the frequency transform, the 'third method' is used in the decoder for reasons already mentioned. For example, a stability of ± 5 Hz is equal to 0.33% at 1,500 Hz. However, the 1,500 Hz signal is not generated directly, but indirectly as the difference between 24 kHz and 22.5 kHz. At 24 kHz, an error of ± 5 Hz is equal to 0.021%, while at 22.5 kHz it equals 0.022%. When these two switching frequencies are generated independently, the accuracy of each of them must be 0.01% to ensure that a total error of ± 5 Hz is not exceeded. It is readily seen that 0.01% is a pretty tough requirement as regards stability, particularly when the relevant oscillators are to be designed as free-running types to enable a free choice of the shift frequency. However, it can be shown that if these two frequencies have fixed phase relation, the common (central) oscillator from which they are derived is good enough if it has a relative deviation equal to the maximum permissible error at about 1,500 Hz, which is 0.33%. In the present decoder, this is realized with the aid of a central oscillator in conjunction with two digital dividers. Basically, the first divider is set for a divisor of 15, the second for a divisor of 16. The frequency of the central clock is


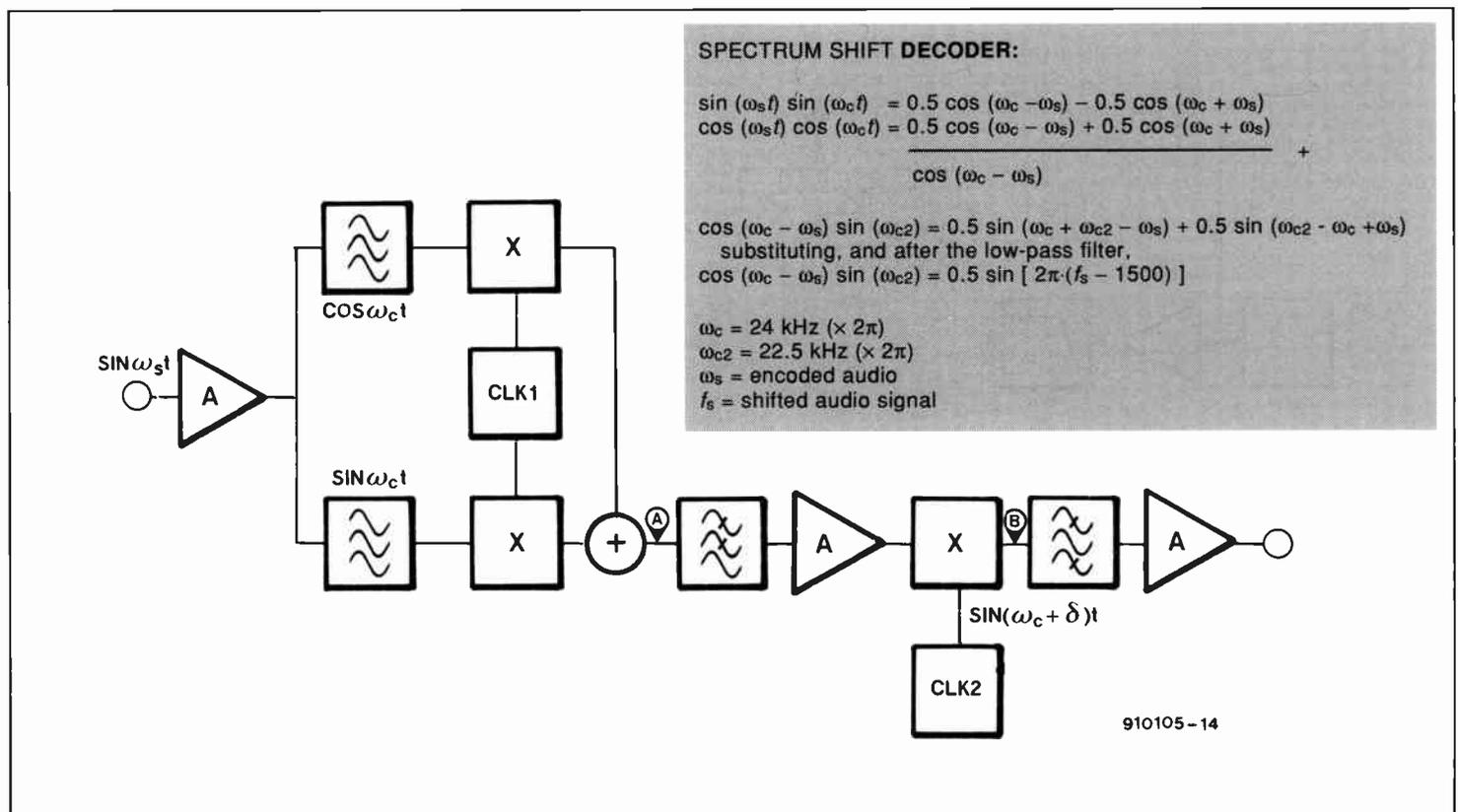


Fig. 4. The 'Feedback killer' (Ref. 1) is a practical realization of a Hilbert transform.

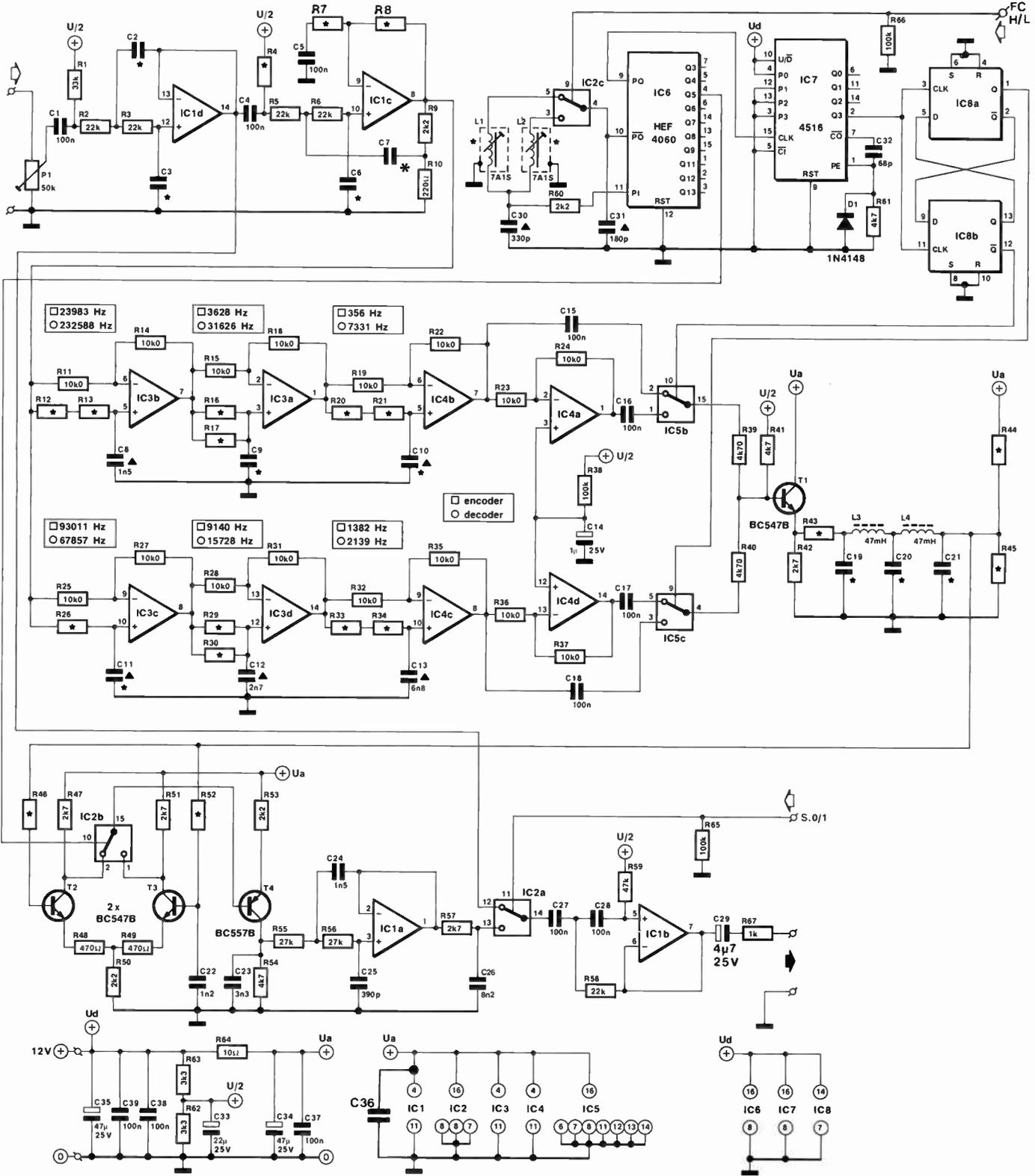

| Pos.* | Encoder | Decoder |
|-------|----------|----------|
| C2 | 1n2 | 820p |
| C3 | 1n | 680p |
| C6 | 470p | 1n |
| C7 | 2n7 | 1n8 |
| C9 | 6n8 2.5% | 2n7 2.5% |
| C10 | 24n 2.5% | 6n8 2.5% |
| C11 | 1n5 2.5% | 2n7 2.5% |
| C19 | 330p | 560p |
| C20 | 1n | 1n8 |
| C21 | 330p | 560p |

| Pos.* | Encoder | Decoder |
|-------|---------|---------|
| R4 | 10k 5% | 3k3 5% |
| R7 | 10k 5% | 3k3 5% |
| R8 | 100k 5% | 33k 5% |
| R12 | 25k5 1% | 2k49 1% |
| R13 | 2k37 1% | 390k 5% |
| R16 | 43k2 1% | 12k1 1% |
| R17 | 680k 5% | 390k 5% |
| R20 | 100k 1% | 10k 1% |
| R21 | 16k2 1% | 10k 1% |
| R26 | 7k15 1% | 5k49 1% |

| Pos.* | Encoder | Decoder |
|-------|---------|---------|
| R29 | 43k2 1% | 24k3 1% |
| R30 | 680k 5% | 820k 5% |
| R33 | 100k 1% | 47k5 1% |
| R34 | 6k8 5% | 21k5 1% |
| R43 | 6k8 5% | 5k6 5% |
| R44 | 18k 5% | 15k 5% |
| R45 | 18k 5% | 15k 5% |
| R46 | 27k 5% | 22k 5% |
| R52 | 27k 5% | 22k 5% |

IC1, IC3, IC4 = TL084
 IC2, IC5 = 4053
 IC8 = 4013
 * see table ▲ = 2.5% polystyrene

Fig. 5. Circuit diagram of the spectrum shift encoder/decoder.

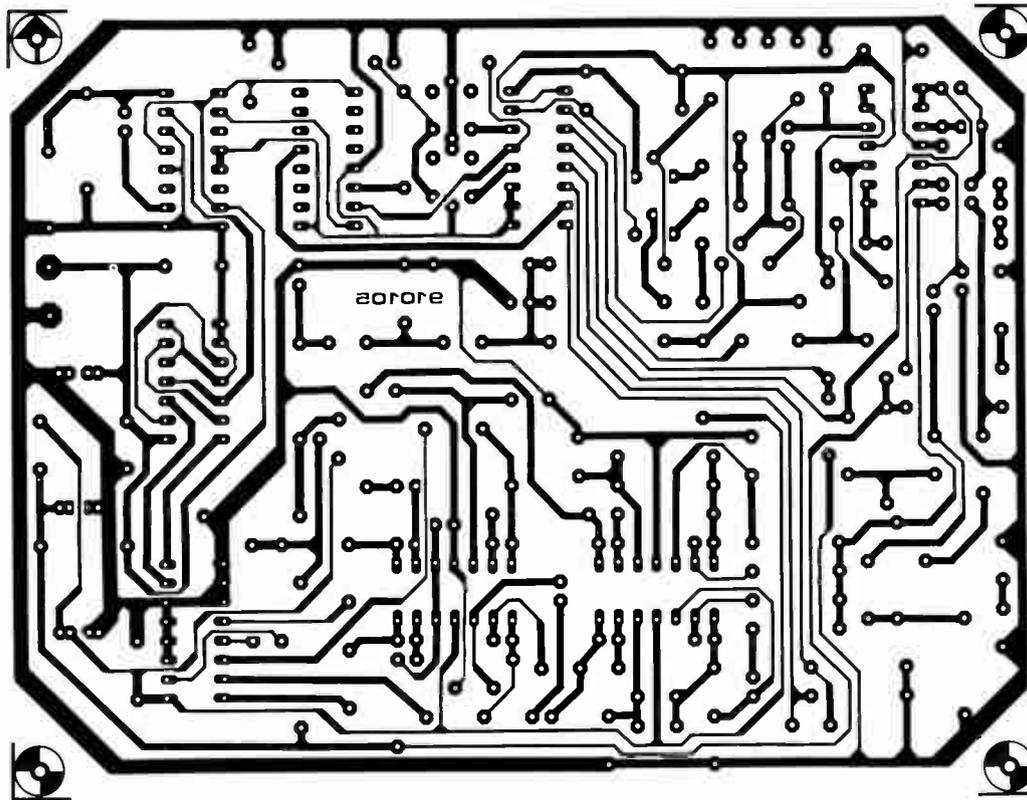


Fig. 6a. Track layout (mirror image) of the single-sided printed circuit board designed for the spectrum shift encoder/decoder.

calculated as follows. Assuming a spectrum shift of 1,500 Hz, then:

$$\begin{aligned} f_{osc} / 15 - f_{osc} / 16 &= 1,500 \\ \therefore 16 f_{osc} / 240 - 15 f_{osc} / 240 &= 1,500 \\ \therefore f_{osc} / 240 &= 1,500 \\ \therefore f_{osc} &= 360 \text{ kHz.} \end{aligned}$$

Since the 24-kHz frequency must be available as four signals with a phase shift of 90° , i.e., 0° , 90° , 180° and 270° , the actual oscillator frequency is four times higher than calculated, i.e., 1.44 MHz, while the divisors of 15 and 16 change to 60 and 64 respectively. This is illustrated in Fig. 3. The 24-kHz signal is

fed in quadrature to two identical mixers (4053). After adding the results of the multiplication, the upper sideband is compensated. Via a 30-kHz low-pass filter, the signal is fed to the third multiplier where it is transformed to the original frequency band.

The encoder

So far, we have not discussed the encoder, and this has a very good reason: it is virtually identical to the decoder! In fact, the same circuit is used, which allows the encoder and the decoder to be built on identical printed-circuit boards. The only difference between

the two units is the value of 29 passive components, of which a number determine the frequency response of the phase filter built around two opamps, IC3 and IC4 (see the circuit diagram in Fig. 5). These components define a pass-band of 1 kHz to 10 kHz in the decoder, and a pass-band of 120 Hz to 7 kHz in the encoder. The accuracy of the phase filter is determined by the accuracy of the passive components used. The performance of the filter depends on the number of sections it consists of, and the ratio between the highest and the lowest input frequency. This ratio is about 10 in the decoder, which, based on a phase filter with three sections, achieves an S/N ratio of about 60 dB. Also based on three filter sections, but designed to handle a max/min frequency ratio of about 58 (7,000 Hz/120 Hz), the encoder has a worse S/N performance of about 40 dB, which is not bad given the simplicity of the design. In any case, the results are perfectly acceptable for speech.

The shift of +1.5 kHz in the encoder (instead of -1.5 kHz in the decoder) is achieved by suppressing the lower sideband instead of the upper sideband (see also Fig. 2b). Since the spectrum in Fig. 2b then extends from 24 kHz to about 31 kHz, the roll-off frequency of the 30-kHz low-pass filter must be shifted up to about 36 kHz. In addition, the input and output filters must be adapted to the spectrum to be passed. All the changes necessary to effect this, i.e., to turn the decoder into an encoder (or vice versa), are summarized in the components table you find inset in Fig. 5.

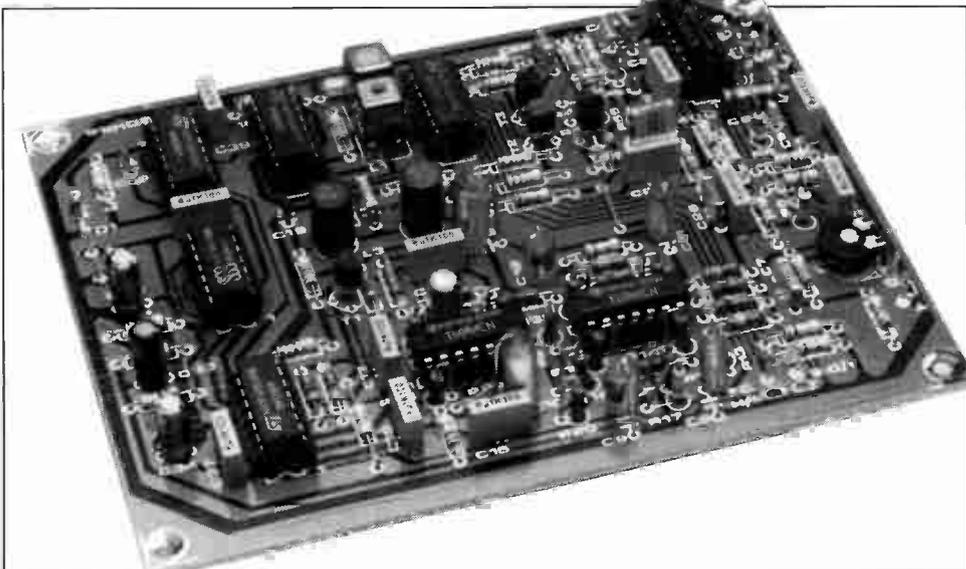


Fig. 7. Completed printed circuit board. A decoder is shown here.

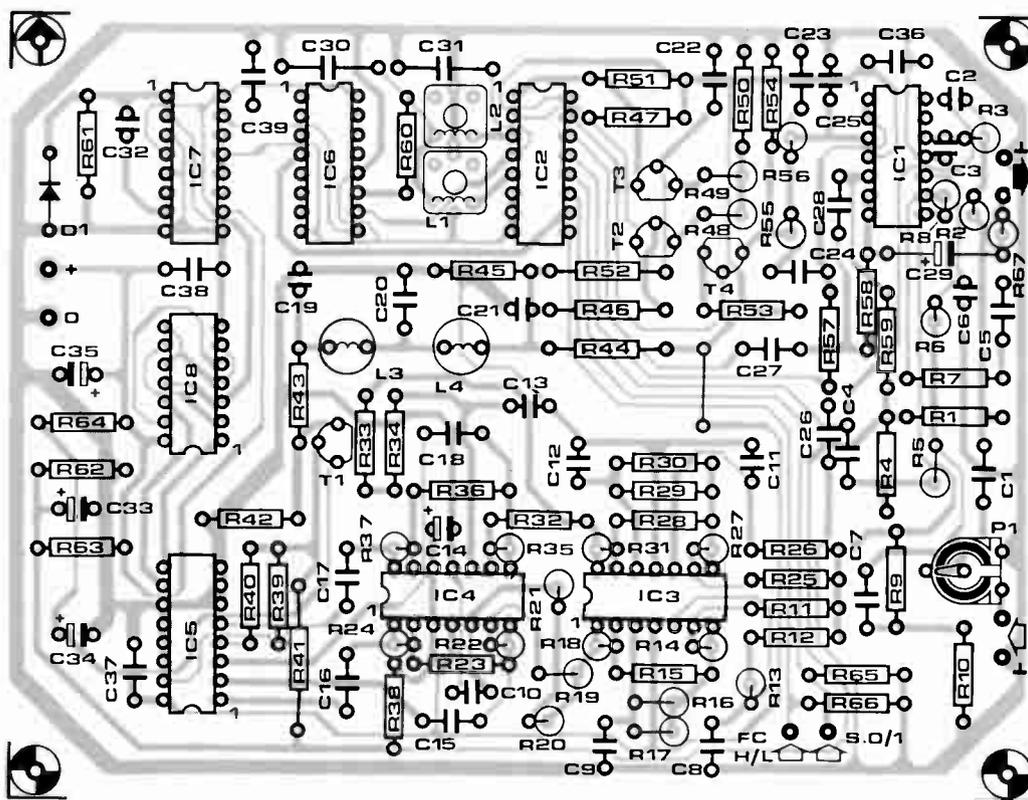


Fig. 6b. Component mounting plan.

COMPONENTS LIST

Resistors:

- 1 33kΩ R1
- 5 22kΩ R2;R3;R5;R6;R58
- 4 2kΩ R9;R50;R53;R60
- 1 220Ω R10
- 16 10k 1% R11;R24;R14;R15; R18;R19;R22;R23; R27;R28;R31;R32; R35;R36;R37;R25
- 3 100kΩ R38;R65;R66
- 2 4kΩ 70 1% R39;R40
- 3 4kΩ R41;R54;R61
- 4 2kΩ R42;R47;R51;R57
- 2 470Ω R48;R49
- 2 27kΩ R55;R56
- 2 3kΩ R62;R63
- 1 10Ω R64
- 1 47kΩ R59
- 1 1kΩ R67
- 1 50kΩ preset H P1

Capacitors:

- 13 100nF C1;C4;C5;C15; C16;C17;C18; C27;C28;C36-C39
- 1 1nF 2.5% polystyrene C8
- 1 2nF 2.5% polystyrene C12
- 1 6nF 2.5% polystyrene C13
- 1 1μF 25V radial C14
- 1 1nF C22
- 1 3nF C23
- 1 390pF ceramic C25
- 1 1nF C24
- 1 8nF C26
- 1 4μF 25V axial C29

- 1 330pF 2.5% polystyrene C30
- 1 180pF 2.5% polystyrene C31
- 1 68pF ceramic C32
- 1 22μF 25V radial C33
- 2 47μF 25V radial C34;C35

Inductors:

- 2 7A1S assembly (Neosid); for winding details see text L1;L2
- 2 47mH radial choke; Toko 181LY473 L3;L4

Semiconductors:

- 1 1N4148 D1
- 3 TL084 IC1;IC3;IC4
- 2 4053 IC2;IC5
- 1 HEF4060* IC6
- 1 4516 IC7
- 1 4013 IC8
- 3 BC547B T1;T2;T3
- 1 BC557B T4

* do not substitute by CD4060, HCF4060 or MC14060

Miscellaneous:

- 1 printed-circuit board 910105

ENCODER/DECODER COMPONENT VALUES

| Pos. | Encoder | Decoder |
|------|-----------|------------|
| C2 | 1nF2 | 820pF |
| C3 | 1nF | 680pF |
| C6 | 470pF | 1nF |
| C7 | 2nF7 | 1nF8 |
| C9 | 6nF8 2.5% | 2nF7 2.5% |
| C10 | 24nF 2.5% | 6nF8 2.5% |
| C11 | 1nF5 2.5% | 2nF7 2.5% |
| C19 | 330pF | 560pF |
| C20 | 1nF | 1nF8 |
| C21 | 330pF | 560pF |
| R4 | 10kΩ 5% | 3kΩ 5% |
| R7 | 10kΩ 5% | 3kΩ 5% |
| R8 | 100kΩ 5% | 33kΩ 5% |
| R12 | 25kΩ 5 1% | 2kΩ 249 1% |
| R13 | 2kΩ 37 1% | 390Ω 5% |
| R16 | 43kΩ 2 1% | 12kΩ 1 1% |
| R17 | 680kΩ 5% | 390kΩ 5% |
| R20 | 100kΩ 1% | 10kΩ 1% |
| R21 | 16kΩ 2 1% | 10kΩ 1% |
| R26 | 7kΩ 15 1% | 5kΩ 249 1% |
| R29 | 43kΩ 2 1% | 24kΩ 23 1% |
| R30 | 680kΩ 5% | 820kΩ 5% |
| R33 | 100kΩ 1% | 47kΩ 5 1% |
| R34 | 6kΩ 8 5% | 21kΩ 5 1% |
| R43 | 6kΩ 8 5% | 5kΩ 26 5% |
| R44 | 18kΩ 5% | 15kΩ 5% |
| R45 | 18kΩ 5% | 15kΩ 5% |
| R46 | 27kΩ 5% | 22kΩ 5% |
| R52 | 27kΩ 5% | 22kΩ 5% |

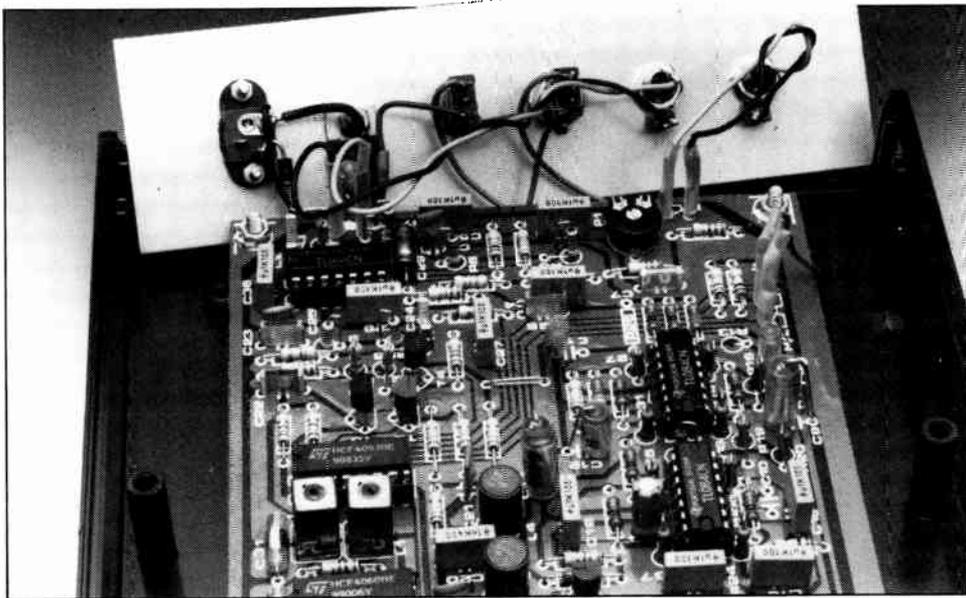


Fig. 8. The rear panel of the Teko 222 enclosure has on it the frequency select switch (FC H/L), the scrambling on/off switch (S. 0/1), the input and output sockets, a DC adaptor socket, and a 7812 voltage regulator with decoupling capacitors.

The circuit in detail

The following description applies to the encoder as well as to the decoder, which are electrically identical circuits. Where necessary, a distinction will be made.

The audio signal applied to the input of the circuit is fed to a low-pass filter built around IC1d and IC1c. The roll-off frequency is set to 10 kHz in the decoder, and to 6.6 kHz in the encoder. The previously mentioned high-pass filter is formed by capacitors C1, C4 and C5 and resistors R1, R4 and R7. The roll-off frequency is set to 500 Hz in the decoder, and to 150 Hz in the encoder. Apart from functioning in the active filter, IC1c amplifies the input signal about 10 times.

The phase filter is formed by the circuit around opamps IC3 and IC4. The indicated component values must be maintained to ensure the correct operation of the filters. The frequency-determining capacitors are types from the E12 series with a tolerance of 2.5% or better. Here, polystyrene types are used in combination with 1% resistors from the E96 series. The theoretical roll-off frequencies of every filter section are indicated in the circuit diagram. The equation

$$f_c = 1 / RC$$

applies for the roll-off frequency, and may be used to match capacitors and resistors if you can not secure the ones given in the circuit diagram and the parts list (consult Ref. 2). The resistors must not be made smaller than about 2 k Ω , or larger than about 200 k Ω . For instance, if you can not get hold of a 24 nF 2.5% capacitor (C10 in the encoder), look at the pole of the filter section, which is 356 Hz. Verify this using the above equation and given that $R=116.2$ k Ω ($R_{20}+R_{21}$). Next, substitute C10 by, say, 27 nF 2.5%. The total resistance of $R_{20}+R_{21}$ works out at 103.2 k Ω . Since resistors are available in far more values than capacitors, this value is easier to create than 24 nF.

The multiplication with the 24-kHz signal is effected by electronic switches IC5b and IC5c. Two 1% resistors, R39 and R40, add the product signals. Transistor T1 functions as an impedance transformer to ensure that low-pass filter L3-L4-C19-C20-C21 is terminated correctly. Next, the filtered signal is fed to a second multiplier built around T2, T3 and IC2b. This circuit supplies the decoded signal in the decoder, and the encoded signal in the encoder. A low-pass filter fitted at the input of opamp IC1a suppresses the unwanted high-frequency products, and provides the drive signal for the output buffer, IC1b. An electronic switch ahead of IC1b allows you to disable the decoder/encoder by applying +12 V to the S.0/1 (scrambling on/off) terminal.

The central clock oscillator is contained in IC6, an HEF4060 CMOS oscillator/divider, which is used with an inductor, L1 or L2, instead of the rather more usual R-C combination, to determine the oscillator frequency. Properly constructed, the L-C oscillator meets the 0.33% accuracy requirement. Note that capacitors C30 and C31 must be types with a low temperature co-efficient (NP0- or COG-class devices; these are ceramic capacitors with a black band at the top side of the body). Alternatively, fit 2.5% tolerance polystyrene types, which are more readily available. The presence of two oscillator inductors enables you to switch between two different frequency shifts. The selection is effected via switch IC2c, which is controlled by applying +12 V or 0 V to the FC H/L (frequency control high/low) input of the board. This is also useful when a single scrambled source makes use of two encoding frequencies.

The HEF4060 combines the function of central oscillator and divide-by-64 prescaler to supply the 22.5-kHz switching signal. The divide-by-60 function is realized by a 4516, IC7, and 4013, IC8. The former is wired to divide by 15, the latter to divide by 4. The Q and \bar{Q} outputs of the bistables in the 4013

supply the control signals for multipliers IC5b and IC5c.

Construction and adjustment

As already mentioned, the printed-circuit board (Fig. 6) can be used to build the decoder as well as the encoder. The construction itself is straightforward, and not expected to cause problems. Note that there is one wire link on the board, and that a fair number of parts are fitted vertically. Make sure you select the right component values from the parts list when building up the decoder and/or the encoder. The value coding of the 1% E96-series resistors may cause confusion if you have never used these devices before — when in doubt, use your digital multimeter to establish the value.

The inductors, L1 and L2, consist of 100 turns of 0.1-mm dia. (SWG40) enamelled copper wire on Type 7A15 formers from Neosid. After winding the inductor and soldering the wires to the appropriate pins (look on the component overlay!), fit the ferrite cup, and secure it with a few drops of wax or glue. This **must** be done to ensure the stability of the oscillator. Next, fit the screening can and the core, check the continuity of the inductor at the base pins, and mount the assembly on the PCB. Solder all the pins, including those of the screening can, quickly to prevent overheating. The self-inductance of L1 and L2 is about 100 μ H.

The central oscillator may not work properly if you do not use an HEF4060. The HEF4060 is a Philips Components product, and a LOC MOS version of the ubiquitous CMOS 4060. We tested a few 'ordinary' 4060s of different makes in the circuit, and found that none of these achieved the reliability and stability of the HEF4060.

Apply 12 V to the decoder, and an encoded input signal. Connect an amplifier to the output. Adjust P1 for an input amplitude of about 200 mV_{pp}. Leave the FC H/L and S.0/1 pins unconnected, and adjust L1 until you measure 1.44 MHz at pin 9 of the HEF4060 (IC6). Remember, the central clock frequency determines the shift, which you are free to set between 1 kHz and 2 kHz. A shift of 1,500 Hz is obtained with a 1.44 MHz clock. Take the FC H/L pin logic high (+12 V), and adjust L2 similarly. Listen to the output signal, and fine-tune the inductor(s) for best results. Your ears are the best test instruments for this purpose.

The adjustment of the encoder is identical — the only difference in the set up is that the output is connected to a transmitter, a cassette recorder, etc., instead of to an amplifier for direct sound reproduction. ■

References:

1. "Feedback killer", *Elektor Electronics* February 1990.
2. "Wideband phase-shift networks", in *Electronic Filter Design Handbook* (1981), by Arthur B. Williams, McGraw-Hill Publishers.
3. "HF transmitters", in *Radio Communication Handbook*, published by the Radio Society of Great Britain (RSGB).

INTERMEDIATE PROJECT

A series of projects for the not-so-experienced constructor. Although each article will describe in detail the operation, use, construction and, where relevant, the underlying theory of the project, constructors will, none the less, require an elementary knowledge of electronic engineering. Each project in the series will be based on inexpensive and commonly available parts

BUILD THE OPTICALOCK – PART 2

by Michael Swartzendruber

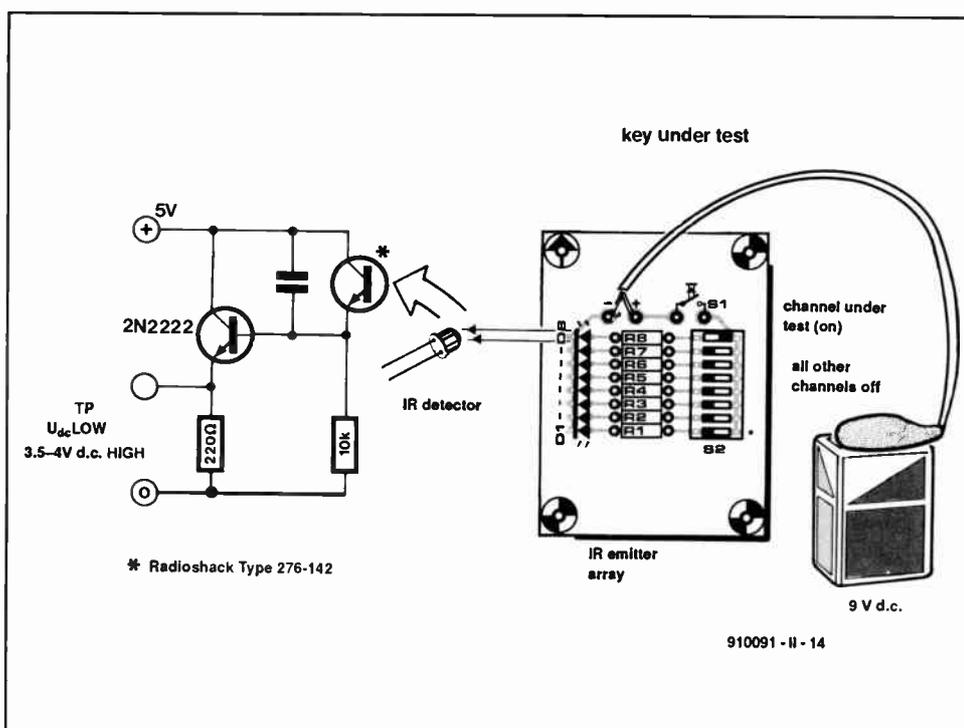


Fig. 7. Auxiliary circuit for testing the key assembly.

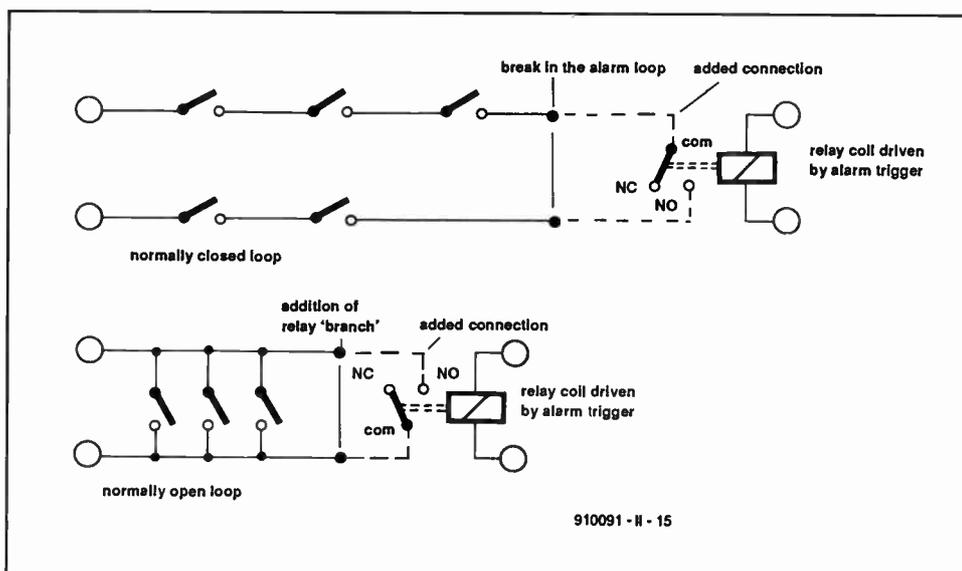


Fig. 8. How to use relays as trigger switches.

Test procedures for the key assembly

- 1) Construct the circuit shown in Fig. 7.
- 2) Enable one of the emitter circuits at a time by leaving all DIP switches off, except the channel currently on test: that channel's switch should be turned on.
- 3) Aim the emitter on test at the test circuit.
- 4) Look at the voltage or logic level of test point A.
- 5) If the emitter passes test, disable this channel and proceed to the next channel until all have been tested.
- 6) Trouble-shoot as necessary. If all emitters fail, double-check the battery connections, or check the device polarity for correct installation on to the board, or check the device with a junction tester.

Test procedures for the detector/amplifier array

- 1) After the assembly is completed and passes all visual inspections and voltage tests, install the two transistor arrays and connect the assembly to a 5-V d.c. supply.
- 2) The assembly is tested with the aid of the key assembly. Enable all emitters on the key by setting all DIP switches to 'on'.
- 3) Locate the test node for the first amplifier channel and place the probe of the voltmeter or logic probe at this node.
- 4) Aim the key at the completed detector array (these two assemblies should have been constructed so that the key array mates with the detector array) and enable the key by closing the push-button switch.
- 5) The voltage or logic level at the node of the channel on test should swing to logic level 1 or about 4 V and should remain at this level as long as the key is aimed at the detector. When the key is removed, the logic or voltage level should return to zero.
- 6) Proceed to the next channel of the array and repeat the test. Trouble-shoot as necessary.
- 7) If all detectors fail the test, check the wiring of the supply, all polarized devices for

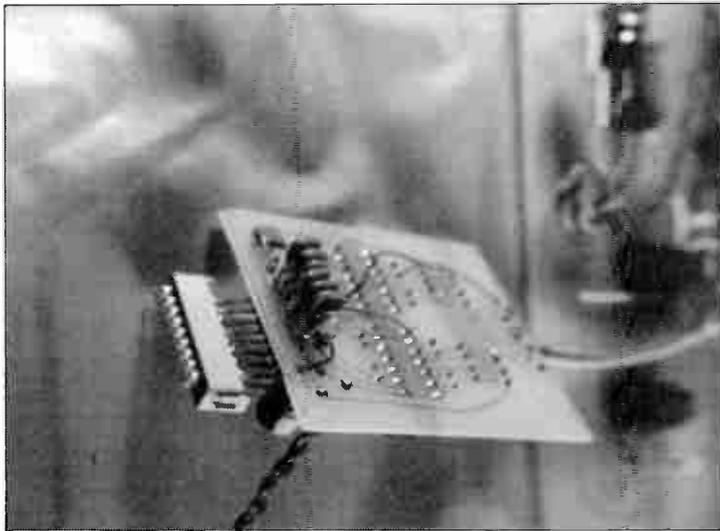


Fig. 9. Mounting method of the optional bypass capacitors connected across each photodetector of the infra-red detector array should they be required to remove fluorescent interference.

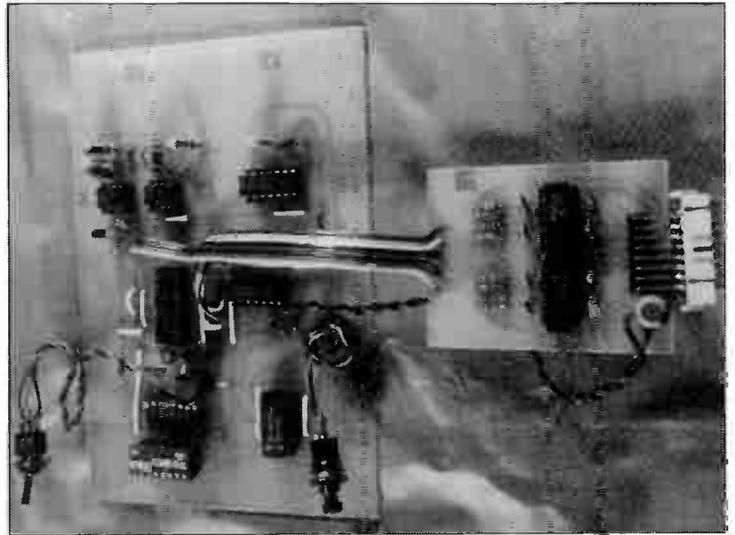


Fig. 10. View of the Opticalock's main logic board and the 'key-hole' connected by a ribbon cable.

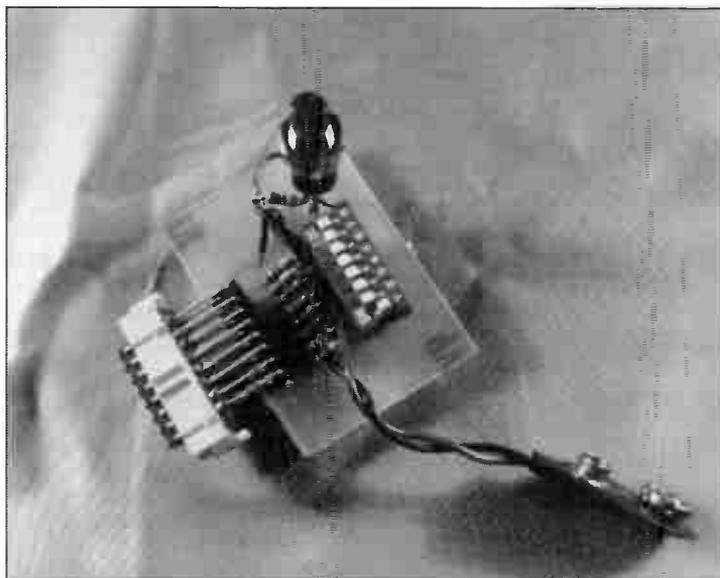


Fig. 11. Two views of the Opticalock's 'key'. The one on the right shows a detail of the method used to mount the infra-red array at a right angle to the board. A 20-pin, 0.1"x0.1" connector is soldered to a right-angle header assembly and the array is inserted into the socket.

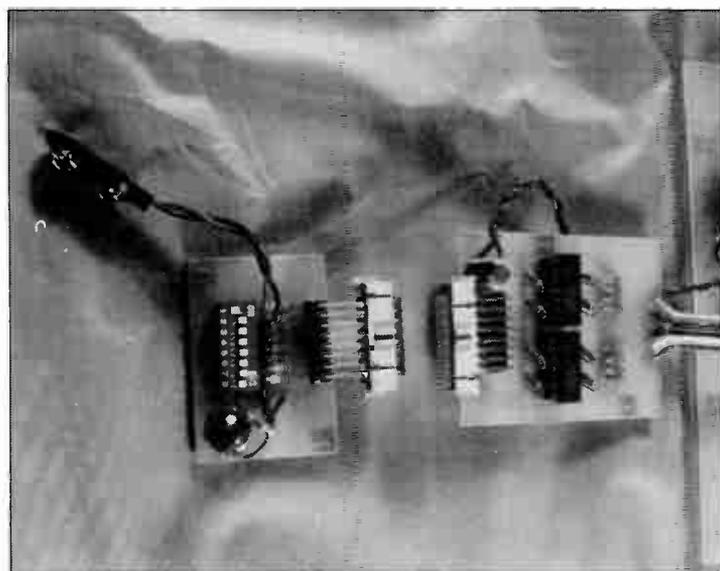
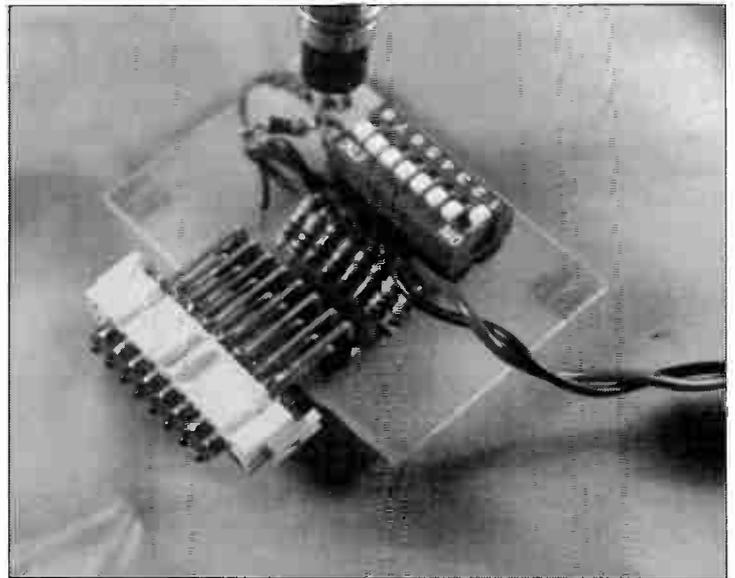


Fig. 12. General view of the key and keyhole.

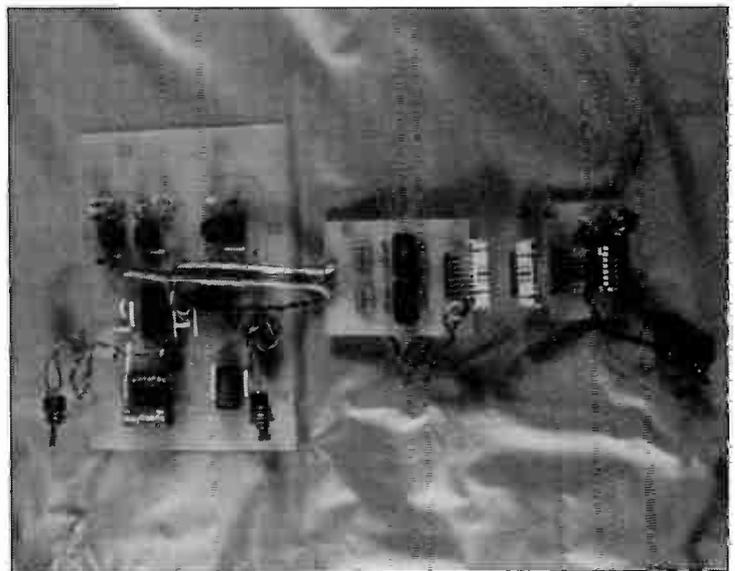


Fig. 13. General view of the entire Opticalock system.

correct placement with particular attention to the infra-red detector array.

Test points for the infra-red detector / amplifier can be found at the following points of the circuit.

| Channel | IC | Pin |
|---------|----|-----|
| 1 | 1 | 12 |
| 2 | 1 | 3 |
| 3 | 1 | 5 |
| 4 | 1 | 10 |
| 5 | 2 | 12 |
| 6 | 2 | 3 |
| 7 | 2 | 5 |
| 8 | 2 | 10 |

Interfacing the logic driver board

The relay driver outputs of the logic driver circuit can be used in a number of ways. Some simple examples are given to aid any custom applications.

Example 1. How to use the lock relay to drive a solenoid deadbolt.

A) Solenoid coil can be driven by 24 V d.c. at 250 mA. Directly power a solenoid coil with PwrDrv-1 by connecting the solenoid coil leads to 'load +' and 'load -' pads next to IC₈, which becomes actuated by the lock driver circuitry.

B) Load is high voltage or high current load. Use 'load +' and 'load -' pads adjacent to IC₈ or IC₇ to actuate a 24 V d.c. coil relay or triac. Use the switch contacts or device for

load isolation and control.

Example 2. How to use the relays as trigger switches.

To interface the alarm relay into an existing alarm loop, use the appropriate relay contacts and insert them into the loop—see Fig. 8.

For instance, to hook the Opticalock's alarm relay into a parallel, normally closed loop, connect the normally closed and common contacts of the relay into the loop and simply add the relay contacts as another parallel branch.

To interface the relay into a series (normally open in most cases), break the loop at some convenient point and splice the relay into the series by using the normally open and common contacts.

Example 3. How to use the unlock relay to provide an alarm enable/disable switch.

To use this technique, a method must be developed to hold a voltage level high or low without having to excite the relay continuously. One very easy way of doing this is to use the normally open and common contacts of a relay to trigger a flip-flop (bistable)—see Fig. 9.

Programming and initial system testing

Set the combination of the DIPswitch on the key to match the combination of the DIPswitch on the main logic board. Align the key with keyhole and press the push-button key. The LED indicating that the lock is 'unlocked' should light.

Change the setting of one of the DIPswitches and press the push-button on the key three times, whereupon the alarm drive should become actuated. If you wish, you may elect to use a logic probe on the Q outputs of the JK bistables (flip-flops) while performing the three illegal-entry attempts to monitor the counting action of this chip.

These tests should give a pretty good idea as to how the system works. Switch S₅ may be used to disable the 'unlocked' output altogether to prevent the circuit from providing an unlock signal even when someone has the IR key with the correct combination.

Finishing touches and installation

Now the electronic part of the combination lock has been completed, we need to look at some installation

ideas to make the project a useful addition to an existing security system or to help fortify some accessible doorway by providing a pick-proof lock system.

To augment a security system, the contacts of the alarm relay can be interfaced easily with an existing alarm loop, or its contacts can be used as a switch for an alarm horn circuit.

The lock relay may be used to drive a solenoid-driven lock system such as an electric car door lock or it may simply be connected to any solenoid (modified for use as a deadbolt) with a spring return latch assembly. With these approaches, the lock will always be in a locked mode unless the relay is actuated. The lock relay may also be tied to an existing alarm as the arm/disarm switch using the contacts of the relay to toggle a bistable (flop a flip-flop).

A word of caution: you may void any warranty of a professionally installed alarm system by attempting to connect the opticalock to it. Consult your professional installer if you are not sure or have any questions regarding connection of the device to this type of alarm.

Experienced computer enthusiasts may want to consider the following computer/opticalock interface possibilities. The lock driver output and the alarm driver outputs may be used to drive a bistable and this flip-flop can be monitored by a monitoring control system. In addition, the 8-position DIP switch on the main logic board can be driven by a parallel output port on a control system.

As for security, the detector array can be located at any remote location in relation to the rest of the system. If the distance between the detector and logic board exceeds more than a couple of feet (about a metre), additional pull-up and bypass circuitry may be required at each end of the connecting cable.

The detector should be well-armoured against vandals and attempted intrusions. However, its destruction will not give access to any unauthorized persons; bear in mind, though, that access may also be denied then to authorized persons. So you may consider a rather beefy metal plate assembly to guard it.

The lock disable switch should be located inside at a convenient position.

The alarm reset switch should be situated in a semi-secure area that is easy to get to should it have to be used by those who should know its whereabouts.

Should you opt to use a solenoid-driven dead-bolt, or indeed any electric lock, that may be located at a remote position also.

The system can easily be made to work in many different situations. You may wish to experiment with it on some inner-structure door, such as a closet, or your laboratory door, to find out the finer points of a possible application.

The opticalock makes an innovative use of opto-electronics, and with the numerous benefits of this type of lock system, it would not be surprising to see more designs like this very soon. Who knows, perhaps you have just built the key of the future. ■

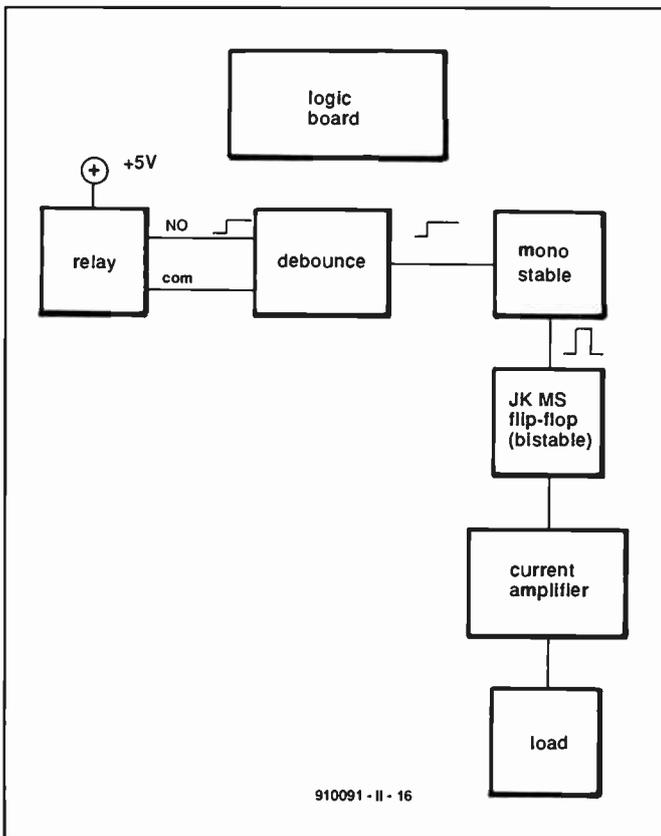


Fig. 14. How to use the unlock relay to provide an alarm enable/disable switch.

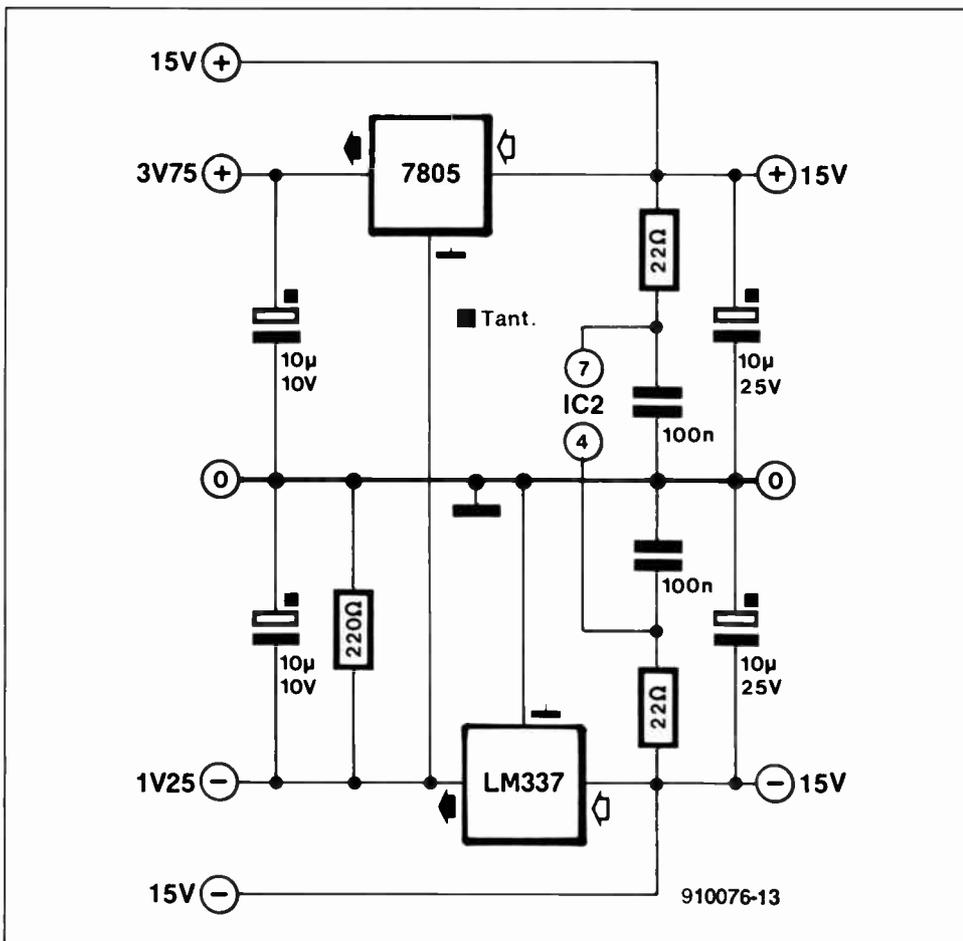


Fig. 3. Regulated power supply for the DAC.

plane should be provided, and the earthed ends of R8-R14, R1 and C2, should meet at one point.

Without component matching, the linearity is of the order of 2 LSB. However, by carefully matching the resistors with the aid of a digital multimeter, a linearity of better than 0.5 LSB can be achieved (tip: use the closely matched resistors towards the MSB). Similarly, the transistors can be matched by measuring the resistance of the base-emitter junction, and noting the values. This measurement should be carried out with the collector and the base connected via the test probe. Additionally, T1 to T9 may be mounted on a common heat-sink for close thermal tracking.

PREVIEW

SPEAKER BUILDER

Issue 5, 1991

- Fibrous tangle effects on acoustical TLs
- A quasi-electronic crossover
- An interview with Ken Kantor of NHT
- A party loudspeaker
- A loudspeaker cable
- A speaker-to-ear interface

Popular modem IC set upgraded to include FAX



Fax transmit capability can be added easily and at nominal expense to stand-alone modems or for such applications as PCs, laptops and portable computers, using Silicon Systems' new SSI 73D2417 modem IC set.

The new chip set adds fax capability as an upgrade to its popular SSI 73D2407 2,400 baud modem chip set which offers a turn-key 'AT' command interpreter with MNP classes 2-5 for error control and data compression.

The SSI 73D2417 combines V.27ter fax transmit capability at 4,800/2,400 baudrates with 2,400 baud multimode (V.22bis/V.22/V.21, Bell 212A/103) data communication and 'AT' command controller.

NEW PRODUCTS

The SSI 73D2417 is said to provide an easy way to enhance conventional 2,400 baud modem designs by adding MNP5 and basic fax features without significantly increasing cost. As an extension of Silicon Systems' proven 73D2404 modem IC set, it gives users a reliable basis on which to develop PC fax designs with a minimum of design effort.

The SSI 73D2417 modem IC set is comprised of four ICs. The 73M214 is an analogue processor that performs the filtering, timing adjustment, level detection and modulation functions. The 73D215 is the receiver digital signal processor. The 73D218 is a command processor that provides supervisory control and command interpretation. The SSI 73D225 is a ROM that provides storage for integral control software. The four devices are available in both DIP and surface-mount packages.

Silicon Systems • 14351 Myford Road • Tustin • CA 92680. Telephone (714) 731-7110 ext. 3575.

Silicon Systems International • Woodpeckers • The Common • West Chiltonington • Pulborough RH20 2PL. Telephone: 07983 2331. Fax: 07983 2117.

TVRO analysis and dish aiming software

Greg Grissom's *TVRO System Analysis and Antenna Aiming Computer Programs for Satellite Technicians* is a software package aimed at satellite TV enthusiasts, professionals as well as TVRO dealers. It can also be a useful adjunct in demonstrating how changing parameters such as dish size or LNB noise figure affect picture quality.

The upgraded version of the program, version 1.1, includes a system configure screen that allows a number of factors that refine the program operation to be set. These include the cutoff angle above the horizon below which satellites can not be 'seen', noise weighted factor, pre-emphasis factor, peak-to-peak conversion factor and video noise bandwidth factor. The last four factors differ between NTSC, PAL and SECAM broadcasts. The new version of the program offers a user-edited database of satellite positions.

The users manual and software, on either a 5.25 or 3.5-inch diskette is available at £35.00 plus £2.00 P&P from **Baylin Publications • 24 River Gardens • Purley • Reading RG8 8BX. Telephone (0734) 414 468. Baylin Publications • 1905 Mariposa • Boulder CO 80302. Telephone: (303) 939-8720. Fax: (303)449-4551.**

COMPUTER-CONTROLLED WEATHER STATION

PART 2: ELECTRONIC HYGROMETER

The electronic hygrometer, or relative humidity (RH) sensor, discussed here is remarkably accurate, and functions automatically as part of the PC-controlled weather station we set out to describe earlier this year.

by J. Ruffell

AMONG the basic measurements carried out daily by amateur meteorologists are those of air temperature, air pressure and relative humidity. In the first instalment of this series, Ref. 1, we described an electronic indoor/outdoor thermometer that works in conjunction with an advanced I/O card for PCs and compatibles (Ref. 2), and dedicated control software. This month we propose to extend the function of this PC-based system with a relative humidity (RH) sensor. Sensors to capture other meteorological data such as air pressure, wind speed and wind direction, will be described in future instalments.

The present circuit measures the relative humidity of ambient air with the aid of a special sensor manufactured by Philips Components. The sensor is basically a non-polarized variable capacitor whose capacitance is a function of the ambient air humidity. Unfortunately, the capacitance does not change linearly with humidity, but that can be corrected fairly easily with the aid of the computer, which is at the heart of our weather station. The computer also greatly facilitates the calibration of the sensor.

Relative humidity

Relative humidity, RH (or U in physics), is the ratio of the pressure of ambient air, e , to that of saturated air over a plane liquid water surface at the same temperature, e' , and is normally expressed as a percentage, that is, $RH = 100e/e'$. The relative humidity depends strongly on air temperature. A relative humidity of 0% indicates a total absence of water particles in the air. In the evening and at night, RH values can rise to 80-90%, while in dense fog the RH is virtually 100%. Typical daytime RH values are between 60% and 70% in sunny weather.


Professional meteorologists measure RH

with a wet and dry bulb hygrometer. This consists of two mercury-in-glass thermometers mounted side by side. The dry bulb thermometer shows the air temperature in the usual way, while the other has its bulb kept moist continually (by means of a small reservoir mounted underneath it) and exposed to an adequate draught. The rate at which the air takes moisture from the reservoir depends on how far it is being saturated with water vapour. If the air is already saturated, it takes up no more and the two thermometers read the same (that is, $RH=100\%$). The lower the humidity of the ambient air, the more it tends to take up moisture, and the lower the reading of the wet bulb thermometer compared with that of the dry one. The difference in temperature gives a highly reliable measure of relative humidity, which is read from tables.

Another, less accurate, method to measure the RH makes use of a hair. This is based on the fact that the length of a strained hair depends on the humidity of the ambient air. This inexpensive way of measuring the RH is applied mainly in simple hygrometers of the type hung up in the living room.

RH measurement: the electronic way

Unlike most electronic hygrometers, which are based on a hygristor (a component whose electrical resistance varies with humidity), the one described here is based on a Philips Type H1 sensor whose capacitance changes with humidity. The capacitance of this device varies between about 110 pF and 145 pF for RH values of between 10% and 90%. The RH-dependent capacitance is used to vary the frequency of an oscillator based on the well-known 555 timer IC — see the circuit diagram in Fig. 1. The RH sensor and the external components around the 555 give the oscillator a nominal frequency range from 43.6 kHz to 33.1 kHz. Since the capacitance of the sensor has a maximum tolerance

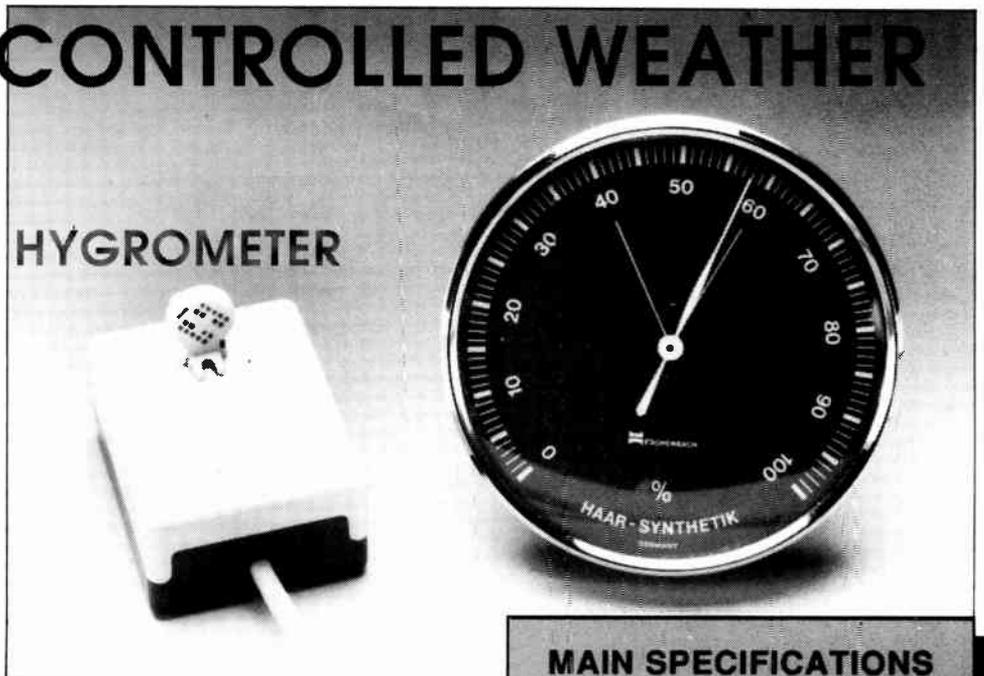

MAIN SPECIFICATIONS

Electronic hygrometer

| | |
|------------------|---|
| Range: | 0% to 95% |
| Channels: | 2 (indoor and outdoor) |
| Recording: | continuous (interval = 10 minutes) |
| Measurement: | once every minute |
| Measured values: | current, day maximum, day minimum |
| Indication: | percentage RH; low, normal, high |
| Software: | memory-resident data logger, calibration utilities and full-colour graph display programs |

System requirements

IBM PC XT, AT, 386, or compatible
640 KByte RAM
EGA or VGA display adapter
DOS 3.3C or later

of 15%, the lower frequency may drop to 28 kHz, while the upper frequency may rise to about 52 kHz. Capacitance-to-frequency (C-to-F) conversion is applied here to allow the measured RH value to be carried over a considerable distance via a cable.

The software that runs on the PC takes care of the linearization of the sensor characteristic. The method developed for this purpose is remarkable because it reduces the number of adjustments in the hygrometer to one! By making use of the 6-digit frequency meter function provided by the measurement card for PCs, the electronic hygrometer achieves a resolution of 1%.

Two H1 sensors and associated interfaces are used since it is usually required to measure the indoor and outdoor RH values simultaneously. The two frequencies produced by the sensor interfaces are applied to the F6 (RH indoor) and F7 (RH outdoor) inputs of the PC measurement card. These two connections are located on connector K6.

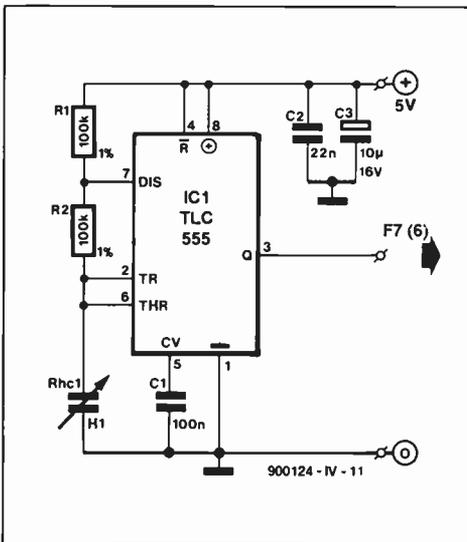


Fig. 1. Circuit diagram of the capacitance-to-frequency converter.

The two sensors may be connected to the computer via ordinary wire, e.g., a 4-wire telephone cable. Cable lengths up to 15 m (50 ft) should not present problems. Each interface requires a supply voltage of 5 V, which is conveniently taken from the stabilized +5-V supply rail brought out on connector K6 of the PC measurement card. Decoupling capacitors C1 and C2, and reservoir capacitor C3 compensate the impedance of the (long) supply wires, which would otherwise degrade the stability of the C-to-F converter. With C1, C2 and C3 fitted, the measured value, at RH=50%, varies no more than 0.004% per mV of variation in the supply voltage.

In some cases, it is not desirable that the sensor interfaces are powered by the PC. The alternative is to build a small, regulated 5-V supply based on, for example, an 7805, and fit this in the sensor enclosure. The stability of the C-to-F converter is best when the voltage regulator is located as close as possible to the sensor interface board. The enclosure used to house the sensor should offer plenty of space for the regulator and the usual decoupling capacitors at its input and output.

Construction

Figure 2 shows the printed circuit board on which the sensor is mounted. The construction of the interface is downright simple, and merits no further discussion. The PCB fits exactly in a Type E406 enclosure from Bopla. Other enclosures may be used, but may require some drilling and filing to fit the PCB.

Drill two 1.5-mm holes in the cover of the enclosure to allow the connecting terminals of the H1 sensor to pass. Extend the H1 terminals with 5-cm long wires before securing the device to the cover with a few drops of two-component glue. The two wires are soldered to the PCB holes marked Rhc1. Drill a hole in the side panel of the case to allow the cable to the PC to pass. This hole should be just large enough for the cable to pass. Fit a strain relief on the cable at the inside of the enclosure.

The interface must be protected against moisture. This is best achieved by applying a little silicone compound on the edges of the enclosure before this is closed. Also use the compound to seal the holes for the sensor wires and the cable to the PC. In both cases, apply the compound at the inside of the enclosure. Before the enclosure is closed, the holes in the bottom half must be sealed with compound. Like the thermometer module, the sensor is temporarily connected to the PC via a small piece of stripboard.

Software in action

The floppy disk supplied for this project, ESS 1561, contains the software required for the adjustment of the sensor, the measurement routines, and the automatic logging routines. In addition, it contains the first update (version 1.1) of the control software for the thermometer module. The new software is marked by an extended version of the memory-resident data logger. It integrates temperature and RH measurements, and provides links for the wind speed and wind direction modules sensors to be discussed in future instalments of this article.

The name of the background program has been changed from TLOGGER into XLOGGER. The update takes into account that XLOGGER is the only program that addresses the PC measurement card — i.e., XLOGGER now performs measurements continuously, and adds measured values to the log file every 10 minutes. The programs for the graphics display of temperature and relative humidity, TEMP and HUM respectively, translate the data contained in the log file into graphs on the PC screen, and at the same time open a RAM data path to XLOGGER. This path allows them to receive the current measurement results, i.e., maximum, minimum and current temperature, and maximum, minimum and current relative humidity. This data transfer avoids complex synchronization protocols between XLOGGER and other programs, and prevents the hardware on the PC measurement card being addressed simultaneously by two synchronous routines, which would cause the PC to crash.

The communication between XLOGGER and the calibration utilities, HADJUST and TADJUST, is similar to that described above. XLOGGER performs all its functions in the background, i.e., as a memory-resident utility. This allows you to use the PC as before for word processing or drawing. The relative humidity is measured once every minute, and the temperature once every 15 minutes. XLOGGER can be actuated by typing XLOGGER /I from the command level. The program takes about 50 KBytes of the base memory in the PC.

.LOG and .CFG files

Users of TLOGGER should note that log files produced by this program (Tyymmdd.LOG) are not compatible with the new log files produced by XLOGGER (Xyymmdd.LOG). The old files may still be viewed with version 1.0 of TEMP, however, provided XLOGGER is removed from memory. This is achieved by typing XLOGGER /U.

The new Xyymmdd.LOG files contain

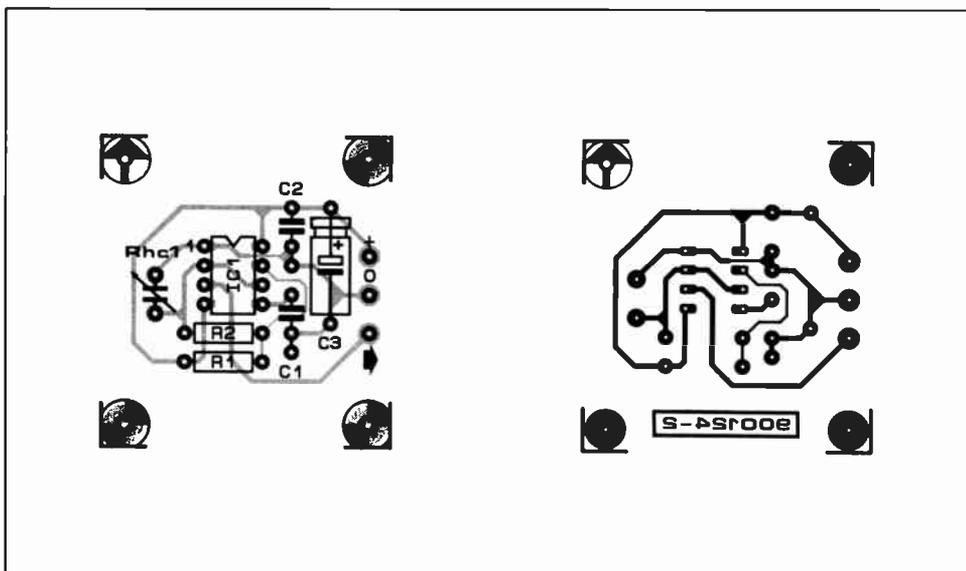


Fig. 2. Single-sided printed-circuit board for the relative humidity sensor.

COMPONENTS LIST

Resistors:

2 100kΩ 1% R1;R2

Capacitors:


1 100nF C1
1 22nF ceramic C2
1 10μF 16V C3

Semiconductors:

1 TLC555 IC1

Miscellaneous:

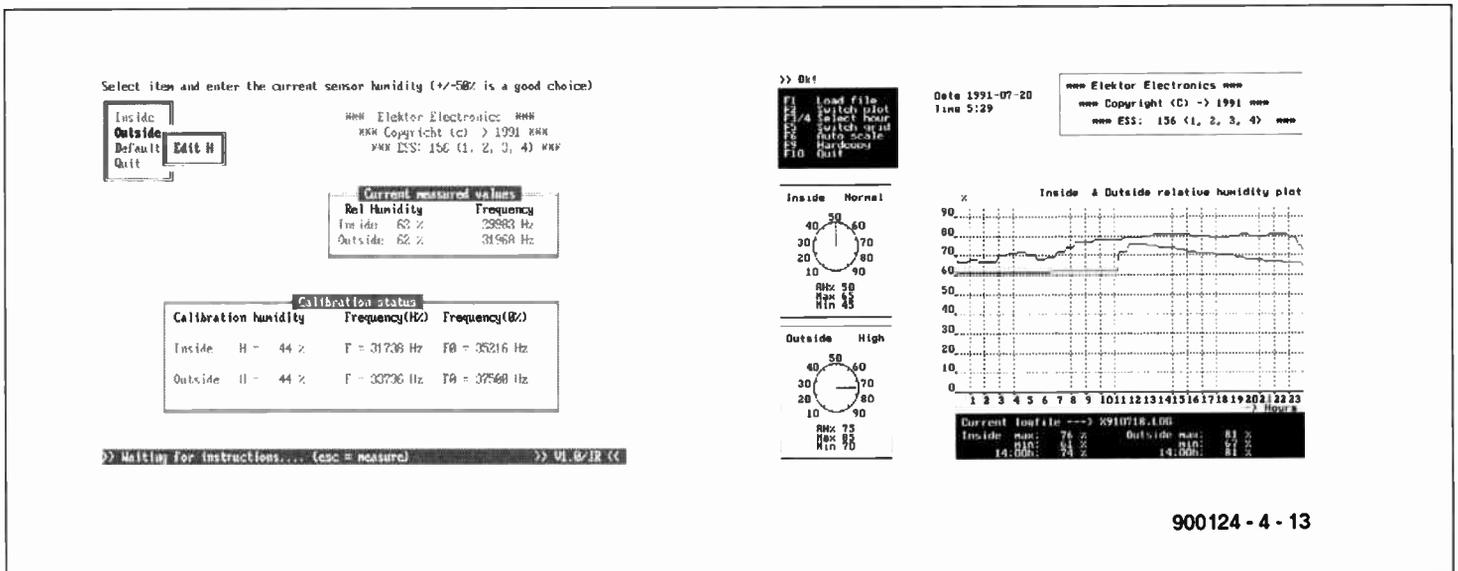1 H1 humidity sensor Rhc1
(Philips Components 2322 691 90001)
1 ABS enclosure, size approx.
65×50×30 mm; e.g., Bopla EG406
1 Printed circuit board 900124-2
1 Control software on disk ESS 1561



900124 - 4 - 13

Fig. 4. Screen layout of HADJUST (left) and HUM (right).

voltages, frequencies and binary codes only. The calibration utilities create transfer files, HTRANS.CFG and TTRANS.CFG, that allow these quantities to be converted into relative humidity and temperature, respectively. TTRANS.CFG contains two linear functions, while HTRANS.CFG is used to store the arithmetically determined frequencies that correspond to a relative humidity of 0%. The status windows of TADJUST and HADJUST show the content of these transfer files. It should be noted that the transfer files must be saved before the sensors are recalibrated, which may be necessary after some time. Without the saved transfer files, it is impossible to convert the existing log files

into the correct values.

The RAM channel conveys frequencies, voltages and codes only. The calibration points are recorded in the TCALI and HCALI configuration files.

The main program, XLOGGER.EXE, uses a configuration file, XLOGGER.CFG, from which it reads a number of initial parameters. XLOGGER.CFG is a text file which may be opened and modified with any ASCII-compatible word processor. The first text line defines the path and the directory where the log files are stored. The path is also used by TEMP and HUM, and may have to be modified depending on your requirements. The next four lines in XLOG-

GER.CFG are the labels, or names, assigned to the sensors. These labels are used by TADJUST, HADJUST, TEMP and HUM, and may be changed if necessary.

One line of text has been added to ADCF.CFG — this will be reverted to below.

Interrupts

XLOGGER can not be used without the hardware on the PC measurement card. Since the hygrometer makes use of the frequency meter on the measurement card, one of the jumpers JP2-JP7 must be fitted to enable the interrupts to be handled correctly. First, determine which interrupt line is still free in your PC (in most cases, this is IRQ2). Fit the respective jumper on the X-row. Next, check that jumper JP8 is fitted in position E. The interrupt line used by XLOGGER is found in the last line of the configuration file ADCF.CFG, and must be the same as the line selected by the jumper. Make sure that this is the case by opening ADCF.CFG with your word processor, or typing TYPE ADCF.CFG, and looking at the interrupt number. If necessary, change the number to match the hardware interrupt selection.

Software: features and applications

HADJUST

This is the calibration program for the hygrometer function. The layout of the screen, and the use of pull-down menus are similar to those of TADJUST, which may already be familiar from the earlier article on the thermometer module. Adjusting the RH sensor is much less complicated than the temperature sensor because it involves only one setting for each sensor. This is achieved by virtue of purposely written calibration routines contained in the HADJUST program. The principle of linearization is explained separately elsewhere in this article. Before the calibration is started, the two sensors are placed in an environment of which the relative humidity is known. It is best to use a

XLOGGER — background to a complex and powerful program

A/D conversion

XLOGGER controls the A-D converter on board the PC measurement card in an interesting way. Each measurement result is based on an average of 500 measurements. The start-of-conversion command for the ADC is generated by the system clock of the PC. Unfortunately, the USER-\$1C-TIMER-TICK interrupt can not be used without modifications because it would result in excessive wait times for 500 or so conversions. This interrupt is executed at a rate of only 18.2 Hz, which is so slow that it would cause the total conversion time to rise to 27.5 seconds. XLOGGER reduces the conversion time to 5 seconds by reprogramming the prescaler in the system clock. When XLOGGER is installed, the standard interrupt BIOS routine \$08, which controls, among others, the real-time clock, and is started at the end of the \$1C handler, is replaced by a new routine that takes care of the data acquisition operations. This interrupt-\$08 routine calls the standard BIOS routine (and with it interrupt-\$1C) every 55 ms on average, so that the real-time clock continues to function normally.

Pop-up handler and frequency meter

XLOGGER uses interrupt-\$1C to pulse the PB0 line when an error condition occurs. Interrupt-\$1C also starts a so-called pop-up handler every 15 seconds. The pop-up routine reads the results of the interrupt-controlled frequency measurement, starts the next measurement with a new channel number, and adds the captured values to the log file every ten minutes. The main advantage of the pop-up handler is that DOS operations such as disk I/O may continue to run asynchronously. By virtue of the pop-up handler, the fact that DOS is not 're-entrant' is no stumbling block any more in the development of interrupt routines and memory resident programs. When the pop-up handler is run, the PB0 line is briefly actuated.

Install/Uninstall

When XLOGGER is started, the presence of a valid parameter, the /I (install) or /U (uninstall) switch, is checked. The program terminates with an error message when the parameter is missing or incorrect. When the /I option is used, XLOGGER is installed only when it is not already present in the memory. The uninstall option, /U, works only if no other memory-resident programs were loaded after XLOGGER. Note that DOS PRINT is a memory resident program!

calibrated hygrometer for this purpose, and you may need to go to your local weather centre to ask for assistance.

Install XLOGGER, and run the HADJUST utility. The menu appears, and two windows, one containing the calibration status, the other the currently measured values. When the program is run for the first time, the calibration window shows a default status, which is simply a rough estimate of the expected calibration data. The other window displays the frequencies produced by the two sensors. From the installation of XLOGGER, it takes about one minute before the two frequencies are measured for the first time. Until then, the frequency variables remain at nought. The Currently Measured Values (CMV) window also shows the relative humidity values derived from the frequencies and the calibration status.

When the first frequency measurement is complete, select the 'inside' option from the menu, after which the 'EDIT H' window is opened. Press the return key, and enter the actual humidity (the value read from the ref-

erence hygrometer) at the cursor location. You will notice that the calibration status and the calculated relative humidity are automatically updated. The other sensor (option 'outside') is calibrated likewise.

Leave the program via the 'quit' option, and subsequently select 'update' to save the transfer and calibration files. Do not select 'abandon' at this stage, as this will terminate the program without storing the previously obtained calibration data.

HUM

HUM (for humidity) handles the graphics presentation of currently measured as well as previously saved values. The screen layout of HUM is basically the same as that of TEMP. HUM displays two analogue hygrometers with an RH percentage scale in the left-hand bottom corner of the display. It should be noted that RH measurements are carried out only when XLOGGER has been installed. The current RH value is also shown numerically on the screen, together with the minimum and maximum values measured during the last 24 hours. The anal-

ogue RH meters have scale areas marked 'low' (for RH values smaller than 45%), 'normal' (for RH values between 45% and 65%), and 'high' (for RH values greater than 65%).

The control menu appears in the top left-hand corner of the screen, while the auto-ranging 24-hour graphs take up most of the right-hand side of the screen. Below the graphs you find the name of the log file and the minimum and maximum values in this.

Finally, function keys F3 and F4 allow you to request the RH value logged at every full hour. The other function keys serve to select certain program options: a graphics or non-graphics graphic; inside RH or outside RH graph or both; producing hardcopy (Epson FX-85 mode only); loading another log file; and leaving the program. □

References:

1. "Computer-controlled weather station — Part 1: indoor/outdoor thermometer", *Elektronik* March 1991.
2. "Multifunction measurement card for PCs", *Elektronik* January and February 1991.

HUMIDITY SENSOR CALIBRATION — WITH A SINGLE ADJUSTMENT

The Type H1 humidity sensor from Philips Components is basically a non-polarized capacitor whose capacitance depends on the humidity of the air around it. The dielectric consists of a non-conductive foil with a thin gold layer at both sides. The two gold layers form the electrodes in this sensor. The dielectric constant, ϵ , of the foil is a function of the atmospheric humidity. The absolute capacitance of the capacitor is calculated from Eq. (1). In the equation, r is the relative humidity, A the surface of the electrodes, and d the thickness of the foil. Unfortunately, the characteristic of the sensor is non-linear (see the curves below). This means that converting a measured capacitance (or a frequency which is inversely related to the capacitance) into a relative humidity value is not so simple. A further complicating factor is that the real characteristics of the two sensors you have lie somewhere between the C_{\min} and C_{\max} curves. This spread is caused by production tolerances on the thickness of the dielectric. The problem with the spread can be solved by basing all calculations on the capacitance factor, $K_{(r)}$, calculated from Eq. (2), instead of on the absolute capacitance. Substituting Eq. (1)

in Eq. (2) proves that $K_{(r)}$ is independent of the thickness of the dielectric. Eq. (3) shows that the dielectric constant, $\epsilon_{(r)}$, is the single factor that determines the actual capacitance. This means that $K_{(r)}$ is independent of the spread on the sensors, so that it can be used as a repeatable starting point. Table 1 shows a few discrete values of $K_{(r)}$. Remember, $K_{(r)}$ is expressed as a percentage.

In effect, the oscillator frequency is measured instead of the sensor capacitance. The frequency is an inverse function of the capacitance. In Eq. (4), parameters a and b are oscillator-dependent constants which have no further significance here. Combining Eq. (1) with Eq. (4) yields Eq. (5). Finally, substitution of Eq. (5) in Eq. (3) yields the output frequency formula, Eq. (7).

Calculations

Assuming that $f_{(0)}$ is known, Eq. (6) enables us to calculate the capacitance factor on the basis of a measured frequency $f_{(r)}$. The relative humidity (RH) associated with the value of $K_{(r)}$ may then be deduced, by interpolation, from Table 1.

The frequency at 0% RH, $f_{(0)}$, is also deter-

mined arithmetically. This is done by performing a frequency measurement at one, known, RH value. The capacitance factor follows from Table 1 via inverse interpolation. Next, the measured frequency and the result of the interpolation are entered into Eq. (7). The result is a frequency, $f_{(0)}$, expressed in Hertz.

$$C_{(r)} = \frac{\epsilon_{(r)} \times A}{d} \quad [\text{F}] \quad \text{Eq. (1)}$$

$$K_{(r)} = \frac{C_{(r)} - C_{(0)}}{C_{(r)}} \times 100 \quad [\%] \quad \text{Eq. (2)}$$

Substituting Eq. (1) in Eq. (2) yields:

$$K_{(r)} = \frac{\epsilon_{(r)} - \epsilon_{(0)}}{\epsilon_{(r)}} \times 100 \quad [\%] \quad \text{Eq. (3)}$$

The oscillator frequency is a function of the humidity as expressed by

$$f_{(r)} = \frac{a}{b \times C_{(r)}} \quad [\text{Hz}] \quad \text{Eq. (4)}$$

Substituting Eq. (1) in Eq. (4) yields:

$$\epsilon_{(r)} = \frac{a \times d}{A \times b \times f_{(r)}} \quad [\text{F/m}] \quad \text{Eq. (5)}$$

Substituting Eq. (5) in Eq. (3) yields:


$$K_{(r)} = \left(1 - \frac{f_{(r)}}{f_{(0)}} \right) \times 100 \quad [\%] \quad \text{Eq. (6)}$$

After calibration, Eq. (6) can be rewritten as

$$f_{(0)} = \frac{f_{(r)}}{1 - K_{(r)} / 100} \quad [\text{Hz}] \quad \text{Eq. (7)}$$

Table 1. RH - K correlation

| r (%) | K (%) |
|---------|---------|
| 10 | 2.135 |
| 20 | 4.265 |
| 30 | 6.463 |
| 40 | 8.865 |
| 50 | 11.433 |
| 60 | 14.130 |
| 70 | 16.918 |
| 80 | 19.767 |
| 90 | 23.238 |

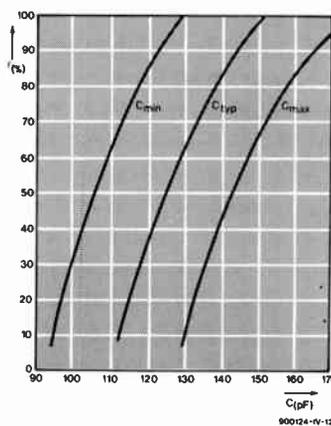

MEASUREMENT TECHNIQUES – PART 7

High-frequency measurements

by F.P. Zantis

THE test methods described so far in this series apply only to low-frequency (LF) equipment. In circuits carrying high-frequency (HF) signals, the effects of the measuring equipment become an important factor. First of all, of course, the test instruments used must be designed for HF measurements. Also, unless suitable measures are taken, tests may result in reflections and radiation of HF energy, which will invalidate the test results.

Measuring HF voltages

The bandwidth of virtually all inexpensive voltmeters makes them unsuitable for measuring HF voltages. Moreover, the capacitance of the test leads and that of the input circuit of the instrument will adversely affect the measurement. Also, in case of instruments with a not very high input impedance, the circuit Q will be derated.

For accurate measurements of HF voltages, special HF peak rectifiers are used. After rectification of the voltage, a standard DC instrument indicates the peak value of the measurand. It is then not possible to measure the r.m.s. value of non-sinusoidal voltages. The rectified voltage should be fed to the test point in a direct way to ensure that the leads from the test point to the display sec-



tion have no detrimental effect on the measurement. In many cases, therefore, a probe as shown in Fig. 61 is used. The rectifier diode should have the smallest possible junction capacitance and this is met by germanium types. The wide-band properties of this diode determine the overall bandwidth in the first instance. The coupling between the tip of the probe and the diode is capacitive, so that any direct voltage at the tip is blocked. Errors in measurement are normally caused by incorrect earthing. The earth point of the probe should be as close as possible to the test point and be connected to the earth of the equipment on test. If the frequency is higher than about 1 GHz, even these measures are not sufficient, since part of the HF energy is then radiated by various components and the wiring, which, of course, makes the measurement invalid or even impossible.

For voltage measurements at frequencies up to about 2 GHz, coaxial insertion probes are used whose construction obviates the unwanted radiation.

Alignment of tuned circuits

Relative measurements suffice in the alignment of tuned circuits—see Fig. 62. Therefore, if a probe is not available, the measurement may be carried out by connecting a low-

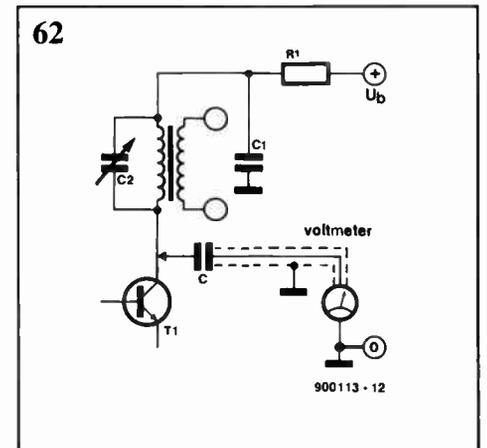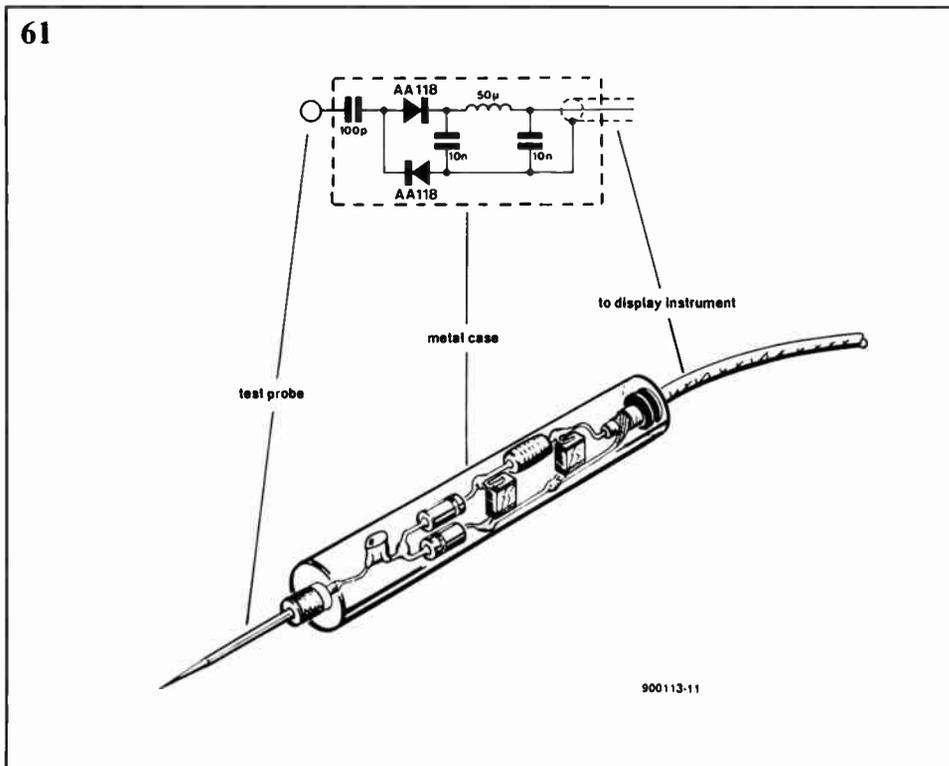value capacitor, C , in series with the instrument. This reduces the effect of the input capacitance of the test instrument on the tuned circuit. The circuit is aligned by adjusting C_2 for maximum or minimum deflection of the voltmeter. In direct voltage




measurements, the effect of the meter is reduced by connecting a high-value carbon resistor (which has a high parasitic inductance) in series with the meter. As in a probe, it is advisable to connect the series capacitor or resistor close to the test point.


It will be realized that these simple methods can only be used for alignment and *not* for absolute measurements.

The effect of the instrument on the circuit on test can be reduced further by the absorption method, for which a circuit as shown in Fig. 63 is used.


Coil L_1 is brought close to the inductor of the circuit on test. Mutual inductance causes a potential across L_1 that may be fed to an oscilloscope or, after rectification, to a voltmeter. If, owing to screening of the inductor in the tuned circuit, inductive coupling is impossible, wiring that carries the HF voltage may be touched with the tip of the probe. Capacitor C_1 is adjusted for maximum voltage across the tuned circuit, after which the frequency can be read on the oscilloscope or, if this is provided, the scale of C_1 .

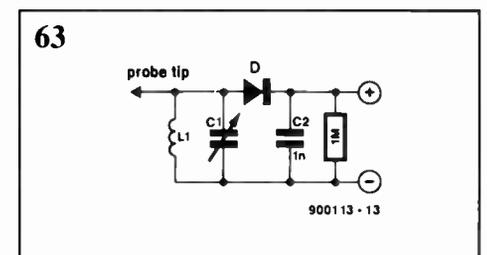

64

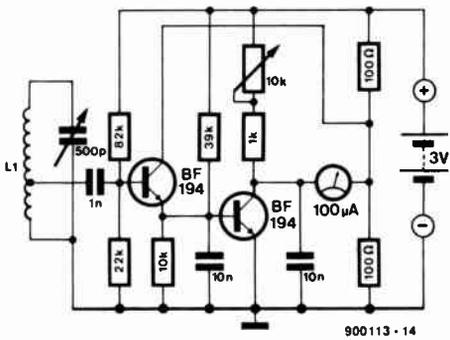

65 (A)

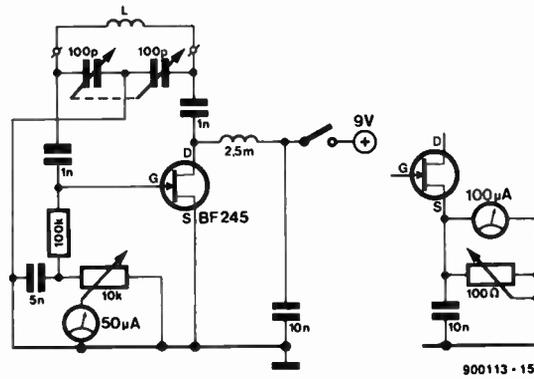

(B)

To really minimize the effect on the tuned circuit, it is advisable to amplify the voltage obtained by inductive coupling. A suitable circuit is shown in Fig. 64. Coil L_1 may be a plug-in type to make alignment over a wide range of frequencies possible. The tap on the coil ensures matching to the low-impedance transistor input.

Dip meter

The dip meter is still the most popular instrument for the radio and television amateur. Although it is basically a small HF transmitter, the meter functions in a manner similar to the absorption method described earlier. This active instrument makes the effect on the circuit on test even smaller, and, of course, greater sensitivity is obtained.

As in the absorption meter, the frequency is read on the scale of the variable capacitor, while the meter serves merely as a maximum or minimum indicator.

Apart from its use as a resonant-frequency measuring instrument, the dip meter may also be used as a signal source in signal tracing in HF circuits.

The values of the coil and variable capacitor are readily calculated with the following formulas if the value of one and the frequency (in MHz) are known.

$$L = 25,400/Cf^2 \quad [\mu H]$$

$$C = 25,400/Ff^2 \quad [pF]$$

A suitable circuit based on a field-effect

transistor—FET—is shown in Fig. 65. The HF signal is generated across the gain-drain junction. The display instrument is connected either in series with the gate bias resistor as in A or across the source as in B. The sensitivity of the circuit is set with the potentiometer.

When the circuit is used as an absorption meter and the display instrument is connected as in B, the 100 Ω potentiometer must be disconnected to ensure that the full sensitivity of the meter is available.

Winding data for coils are given in Table 1.

Measurements on transmission lines

The characteristic impedance of a transmission line is the value of load resistance that enables maximum power transfer from source to load. The characteristic impedance of a transmission line, Z_c , is given by

$$Z_c = \sqrt{L_d/C_d}$$

where L_d is the distributed inductance per unit length and C_d is the capacitance per unit length. Practical values of Z_c vary from 100 Ω to 1000 Ω for parallel wires and 10 Ω to 150 Ω for coaxial cable.

When a transmission line, such as that connecting a transmitter to its antenna, is terminated by an impedance different from its characteristic impedance, some of the forward signal wave is reflected back. The reflected wave mixes with the forward wave, and the resultant amplitude at any point of the trans-

mission line is the algebraic sum of the amplitudes of the two waves.

The nodes and antinodes do not move relative to the transmission line, that is, they are stationary and the waves are called standing waves. An important consideration in transmission line and antenna design is the standing wave ratio—SWR.

The SWR may be ascertained with the aid of an SWR meter as shown in Fig. 66. The pick-up consists of three conductors of which the centre one is the core of the transmission line, while the outer two, called reflected pick-up wire (top) and forward pick-up wire (bottom), are spaced equally from this.


Usually, the pick-up unit is made as a pattern on a printed-circuit board: a strip line. The 51 Ω resistors are, in this case, equal to the characteristic impedance of the transmission line (if this were 75 Ω, the resistors would also have to be 75 Ω). In operation, any RF signal on one of the pick-up wires will be rectified by the relevant diode and then applied as DC to the associated indicator.

To ensure that the indicators can be used independently of the actual power, their scales are calibrated in relative values. That in the forward pick-up circuit, F, shows the relative power as a percentage, whereas the other shows the SWR. The ratio is given by the formula


$$SWR = (1 + U_r)/(1 - U_r)$$

Continued on page 62

66

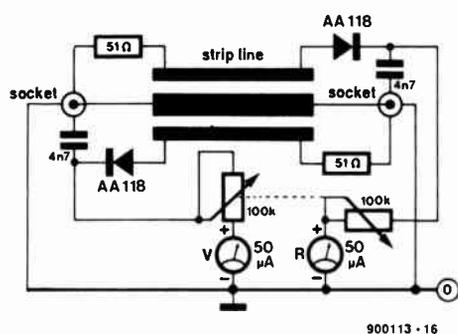

67

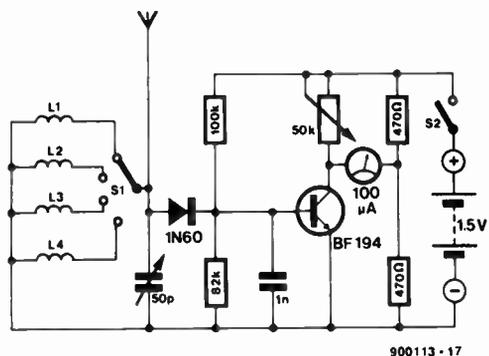

DIGITAL FUNCTION GENERATOR – PART 1

by T. Giffard

The outstanding properties of this function generator are its accurate frequency setting and very low distortion of the sine-wave output. It is, therefore, eminently suitable for use as an a.f. generator for test and design.

UNLIKE many function generators produced over the past 15 years or so, the one described here is NOT based on the ubiquitous XR2206, but on discrete components. Although this does not necessarily make it easier to construct, digital ICs are fairly inexpensive and a digital circuit has fewer calibration points.

Basic design

The block diagram in Fig. 1 shows that the design is based on four printed-circuit boards, indicated by the dashed lines. The heart of the frequency-synthesis board at the top left is the phase-locked loop (PLL). A phase comparator compares the output frequency of a crystal oscillator with that of a voltage-controlled oscillator (VCO). Any phase difference between the two signals causes the comparator to generate a voltage that is used to synchronize the VCO with the reference oscillator.

The wanted output frequency of the generator is determined by the divisor of a divider in the PLL, which is set by means of a keyboard on the front panel. The divider also provides the information for the four-digit LED display.

The VCO and the display share a common power supply, although the supply voltage to the VCO is 6.6 V, whereas that to the remainder of the circuit is 6.0 V.

The divider provides a rectangular signal, which is directly proportional to the output frequency of the generator, to a digital-to-analogue (D-A) converter. This converter consists of a shift register and an appropriate resistance network.

Each period of the wanted sine-wave signal is built up of 32 clock pulses provided by the divider. This means that the clock signal for the D-A conversion must lie between 32 Hz and 3.2 MHz if the generator is to provide an output frequency of 1 Hz to 100 kHz.

Since, in addition to the high precision of the wave shaping, the D-A converter is followed by a phase-locked filter, the distortion factor is even smaller than that of a Wien-bridge type sine-wave generator commonly used for a.f. design and test measurements. Usually, function generators produce a sine wave that is converted into rectangular and triangular signals of the same frequency: this technique does not result in low distortion factors.

FRONT COVER PROJECT



Fig. 1. General view of the digital function generator.

Technical data

| | Sine wave | Rectangular | Triangular |
|---------------------------|---|-------------------------------|------------------------------|
| Frequency | 1 Hz–99.99 kHz | 1 Hz–99.99 kHz | 10 Hz–99.99 kHz |
| Output voltage | 1 V _{rms} e.m.f. | 0–12 V e.m.f. | 0–12 V e.m.f. |
| | 0.9–1 V _{rms} into 50Ω | 0–6 V _{pp} in to 50Ω | 0–6 V _{pp} into 50Ω |
| Offset | ±2.5 V ($U_0=0$ V) ±4.75 V ($U_0=1$ V _{rms}) | ±12 V | ±12 V |
| Output impedance | 600Ω | 50Ω | 50Ω |
| Frequency stability | Three digits better than shown on display | | |
| Frequency resolution | 0.01% of full-scale reading | | |
| Third-harmonic distortion | 0.03% typical | | |
| Slew rate | 130 V/μs | | |

PARTS LIST

Resistors:

- R1 = 2.2 kΩ
- R2,R14,R15,R17,R19 = 1 MΩ
- R3 = 10 Ω
- R4 = 470 Ω
- R5 = 390 Ω
- R6,R7,R10,R20,R22 = 100 kΩ
- R8,R9,R13,R18,R21,R23 = 10 kΩ
- R11,R12,R16,R61-R65,R67,
R68 = 47 kΩ
- R30-R60 = 470 Ω
- R66,R69 = 1 kΩ

Capacitors:


- C1 = 100 pF
- C2 = 45 pF trimmer
- C3,C51-C53 = 100 nF ceramic
- C4 = 47 μF, 10 V, tantalum
- C5 = 10 μF, 40 V, bipolar, radial
- C6,C44 = 100 μF, 10 V, radial
- C7,C8 = 47 nF
- C9,C10,C12,C14,C15,C17,
C18 = 100 nF
- C11 = 470 nF
- C13,C16 = 3.3 nF
- C19-C37,C45 = 100 nF, ceramic
- C38-C41,C50 = 47 nF, ceramic
- C42 = 1000 μF, 25 V, radial
- C43 = 10 μF, 10 V, radial


Semiconductors:

- D1 = BB 212
- D2-D6,D10 = 1N4148
- D7 = 1N4001
- D8,D9,D11 = LED, 3 mm
- B1 = B80C1500
- LD1-LD4 = HD 11310
- T1-T4 = BC 547 B
- T5 = BC 557 B
- IC1 = 74 HC 4060
- IC2 = 74 HC 40103
- IC3 = 4013
- IC4 = 74 HC 4046
- IC5 = 74 HCU 04
- IC6 = 74 HC 4040
- IC7 = 74 HC 151
- IC8 = 4059
- IC9,IC10 = 74 HC 4518
- IC11 = 4067
- IC12 = 74 HC 4017
- IC13-IC16 = 74 HC 696
- IC17 = 74 HC 682
- IC18,IC20 = 4093
- IC19 = 4001
- IC21 = 7806
- IC22-IC25 = 74 HC 4543

Miscellaneous:

- X1 = quartz crystal 5.12 MHz
- S1,S2,S4,S6,S7 = push-to-make switch
- S3 = double change-over switch
- S5 = SPST switch
- Tr1 = mains transformer, secondary 9 V, 500 mA
- PCB 910077-1
- PCB910077-2
- Front panel foil 910077-F
- K1, K3 = 34-way D-type plug for PCB mounting
- K2 = 14-way D-type plug for PCB mounting
- L1 = 45 turns 0.2 mm dia. enamelled copper wire on Neosid Type 7A1S former (= 19μH)

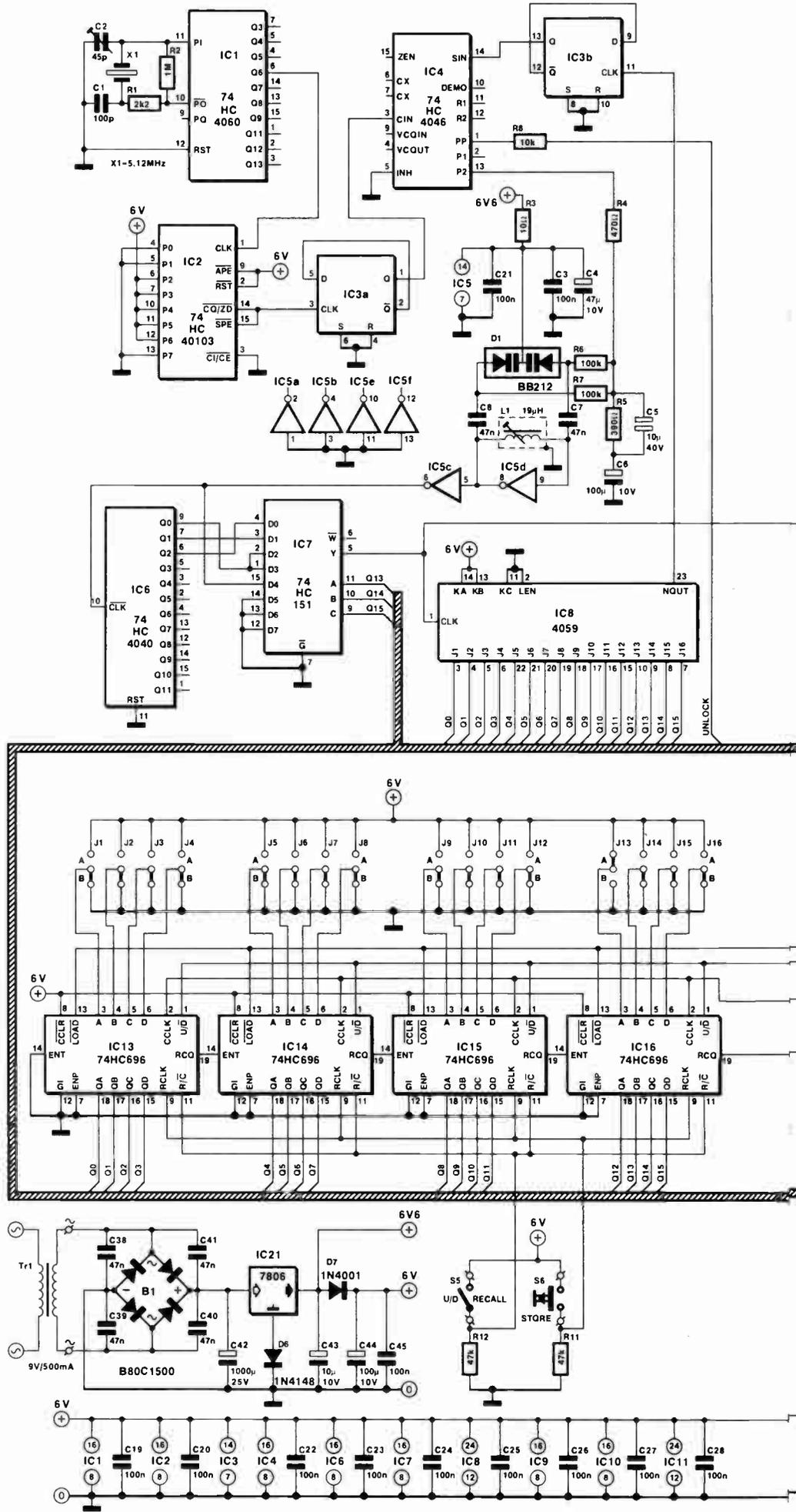

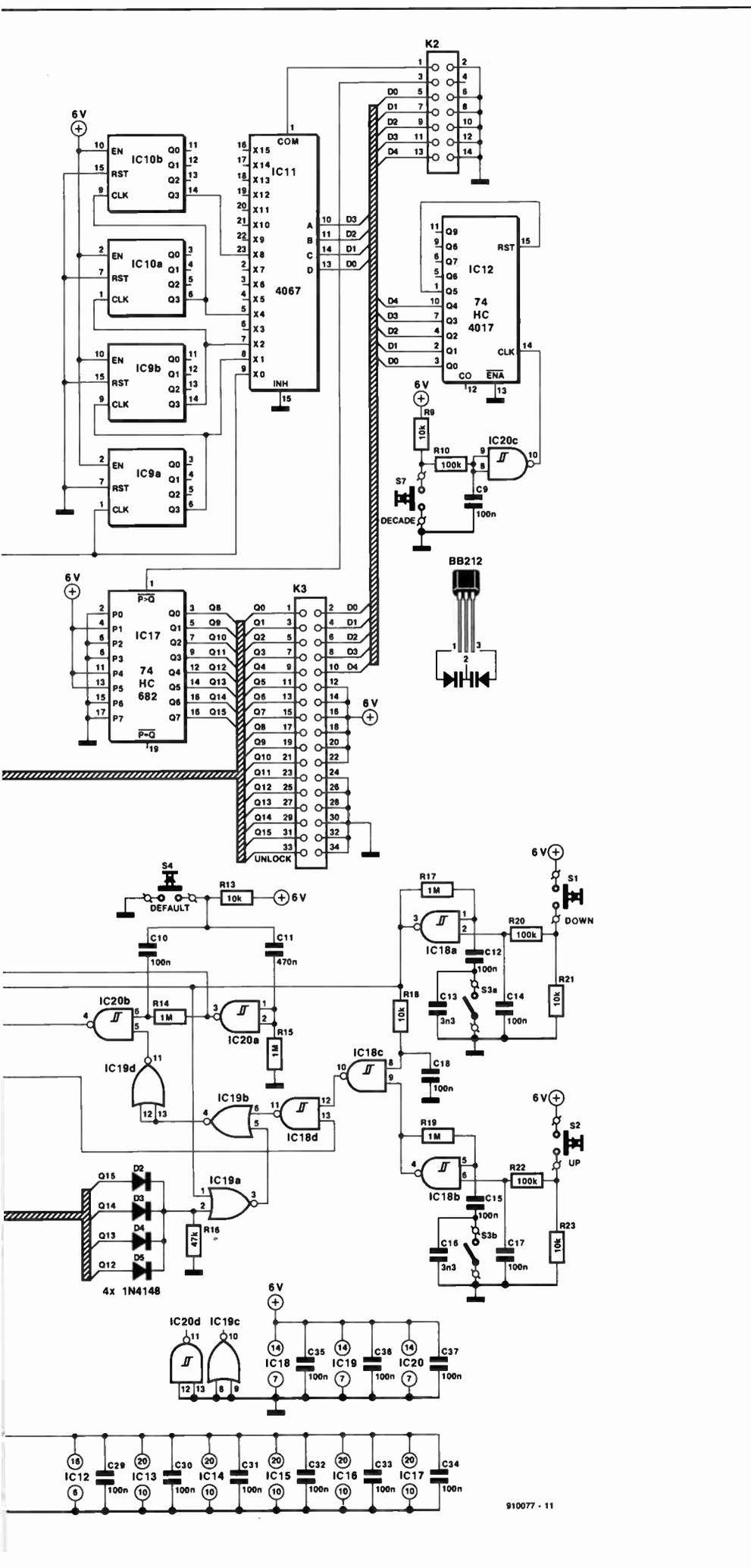

counters.

The heart of the section is IC₄, which contains the phase comparator and a VCO that is not used here. The comparator compares the two input signals, C_{in} (the reference frequency) and S_{in} (the signal frequency). Its output goes high when the phase of the signal frequency leads that of the oscillator frequency, and low in the opposite situation (see also Fig. 3). For this purpose, it uses the first transitions, not the duty factor, of the signals. After both transitions, irrespective of in which order, have been received, the output of the comparator has a high impedance until the next first transition arrives. The duration of the 'low' and 'high' periods is, therefore, directly proportional to the phase shift.

The low-pass loop filter at the output of IC₄ determines the properties of the loop as regards capture range, bandwidth, transient response and stability. After passing through this filter, the output voltage of the comparator controls the VCO

The state when the two signals are in perfect synchronization, that is, are locked, is indicated by the LED at the LOCK output of IC₄ going out.

The reference frequency of 160 Hz is obtained by dividing the 5.12 MHz oscillator frequency by 32 000.

The required frequency range of 32 Hz to 3.2 MHz is, however, not so easily obtained, because a large bandwidth leads to a long transient response and poor stability. That is why the range, outside the loop, is split into five by decadic divider IC₉-IC₁₀: the wanted range is selected by multiplexer IC₁₁. This means that the PLL is only active when the highest sub-range, that is, 320 kHz-3.2 MHz, is selected.

The highest sub-range is itself further divided into four, so that the frequency of the VCO must be a multiple of two, which makes the PLL very stable. Depending on the set frequency, IC₆-IC₇ divides the VCO frequency by one, two, four or eight. The combined divisor of IC_{3b} and IC₈, which counts down from a preset number (max. 9 999) to 1 000, and IC₆-IC₇ lies, therefore, between 16 000 and 32 000. Since the frequency of the signal fed by IC_{3b} into IC₄ must always be 160 Hz (reference!), the frequency range of the VCO is 2.5-5.12 MHz.

The setting of the divisor within the PLL, and thus the frequency within one of the sub-ranges, is effected by four cascaded up-down counters, IC₁₃-IC₁₆. These counters have been set to a predetermined start value by jump leads. The start value may be overridden at any time by pressing the 'up' or 'down' push-button key.

The set divisor is strobed by comparator IC₁₇, whose output is active as long as the ratio is lower than 3 200. This is of importance for the locked filter in the analogue section.

The signal for the analogue section is taken from junction IC₇-IC₈ (pins 5 and 1 respectively). The frequency of this signal lies be-

Fig. 6. Circuit diagram of the digital section of the function generator.

tween 320 kHz and 3.2 MHz.

The signal is applied to divider IC₉-IC₁₀, whose outputs have frequencies of 10⁰, 10⁻¹, 10⁻², 10⁻³ and 10⁻⁴ times that of the input.

The sub-range is selected by multiplexer IC₁₁, whose setting is determined by a 0-4 counter.

The analogue section thus receives a signal whose frequency lies between 32 Hz and 3.2 MHz and information, from D0-D4 of IC₁₂,

as to which sub-range has been selected.

The display board is fed with data representing the frequency setting via bus lines Q0-Q15, D0-D4. It is also connected to the 'unlock' pin (PP) of IC₄.

Circuit description

Digital section

The reference oscillator is formed by fourteen-

stage shift register IC₁. The 5.12 MHz clock is divided internally by 27. The resulting 40 kHz signals is taken from pin 6 and fed to a synchronous, binary down-counter, IC₂. A start count, related to the divisor (here :125) can be set at inputs P0-P7. From that start, the IC counts to zero, resets itself via pin 15 and at the same time triggers flip-flop IC_{3a}.

The bistable functions as a binary scaler, which provides a pure signal with short tran-

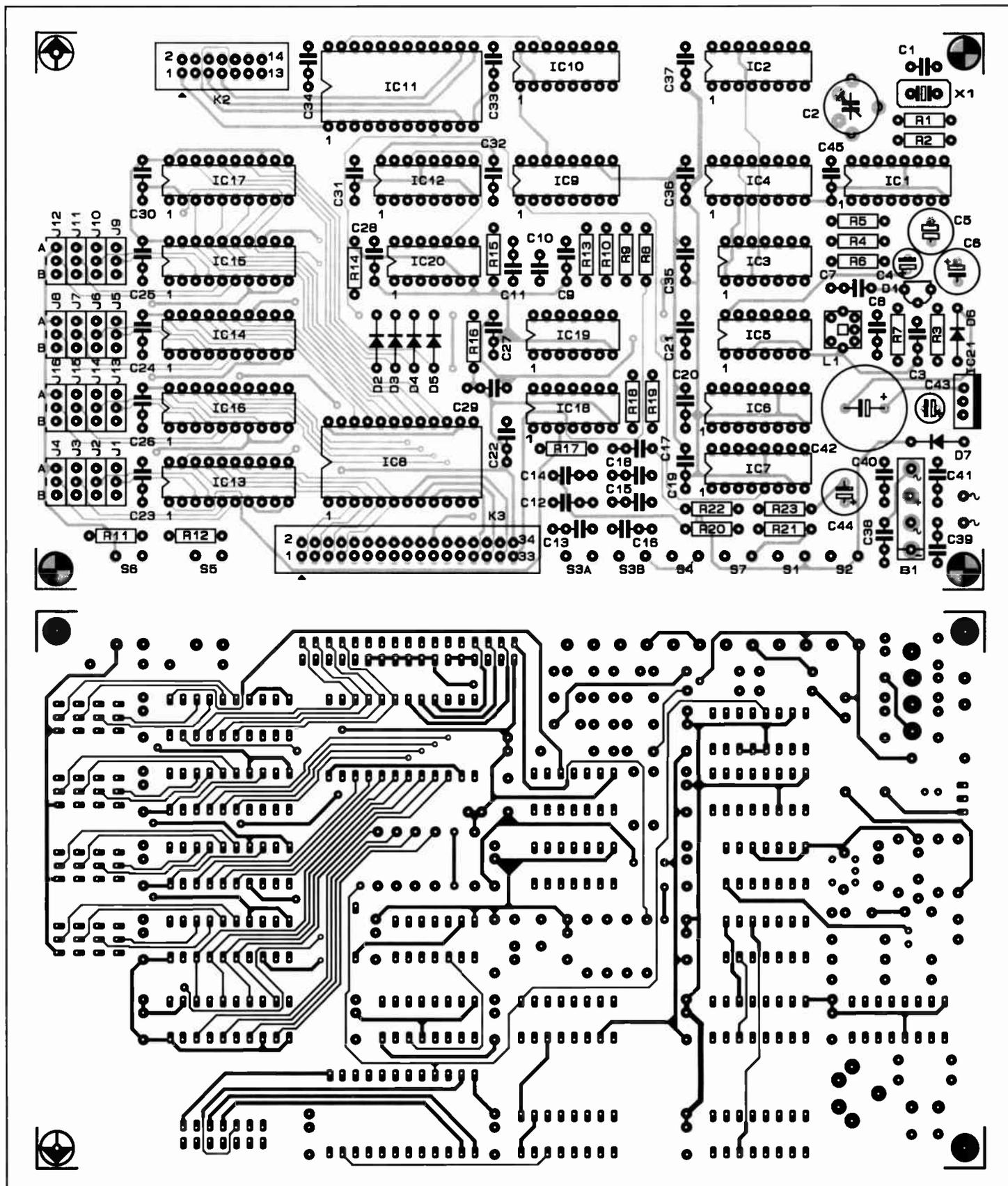


Fig. 7. Printed-circuit board for the digital section of the function generator.

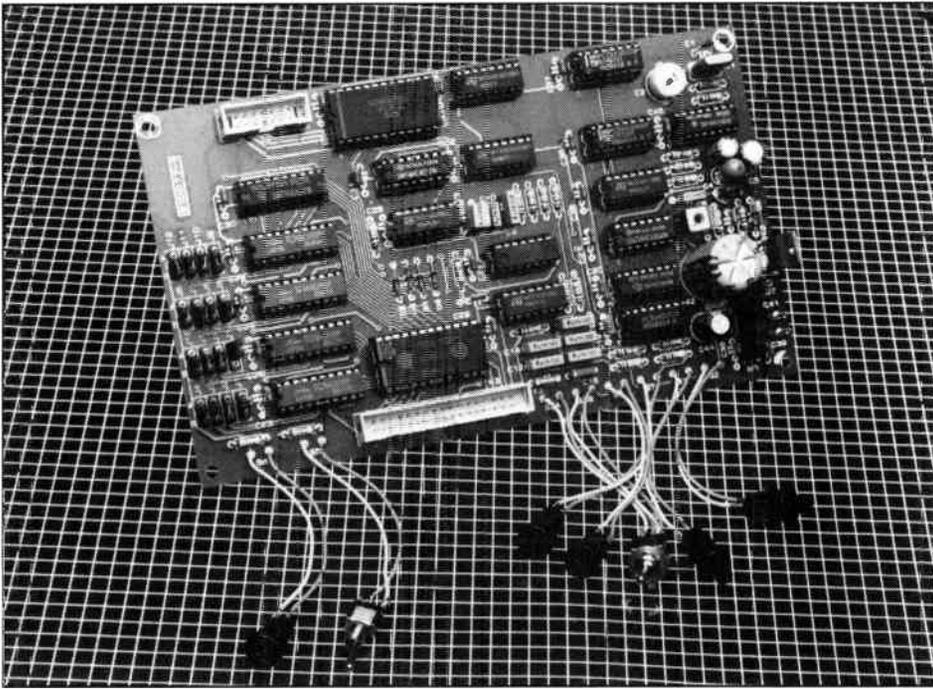


Fig. 8. Photo of the completed digital section board.

sition durations as required by IC₄. The loop filter consists of R₄-R₅-C₅-C₆.

The VCO consists of inverter IC_{5d}, which functions as an amplifier, and an LC circuit that is tuned by dual capacitance diode D₁. The control voltage for that diode is derived from potential divider R₆-R₇. The VCO signal is taken from across IC_{5c}.

The setting of divider IC₆-IC₈ is rather complex. The fundamental VCO frequency exists at pin 15 of IC₇; scaled by two at pin 9 of IC₆; divided by four at pin 7 of IC₆; and divided by eight at pin 6 of IC₆. Which of these signals is passed on depends on the three bits at inputs A-C of multiplexer IC₇.

The output of IC₇ (pin 5) is fed to IC₉-IC₁₀-IC₁₁ and thence to the analogue section and is also used as the clock for programmable *n*-divider IC₈. This chip consists of four cascaded four-bit counters, which operate as decade scalars. The decade range of the three that determine the thousands, hundreds and tens is determined by appropriate bits at each of the groups of inputs J13-J16, J9-J12 and J5-J8 respectively. That of the fourth depends on the level at inputs KA, KB and KC. This counter determines the units of the overall divisor. If, for instance, *n* is to be 1507, J13-J16 must be set to 1000; J9-J12 to 1010; J5-J8 to 0000; and J1-J4 to 1110.

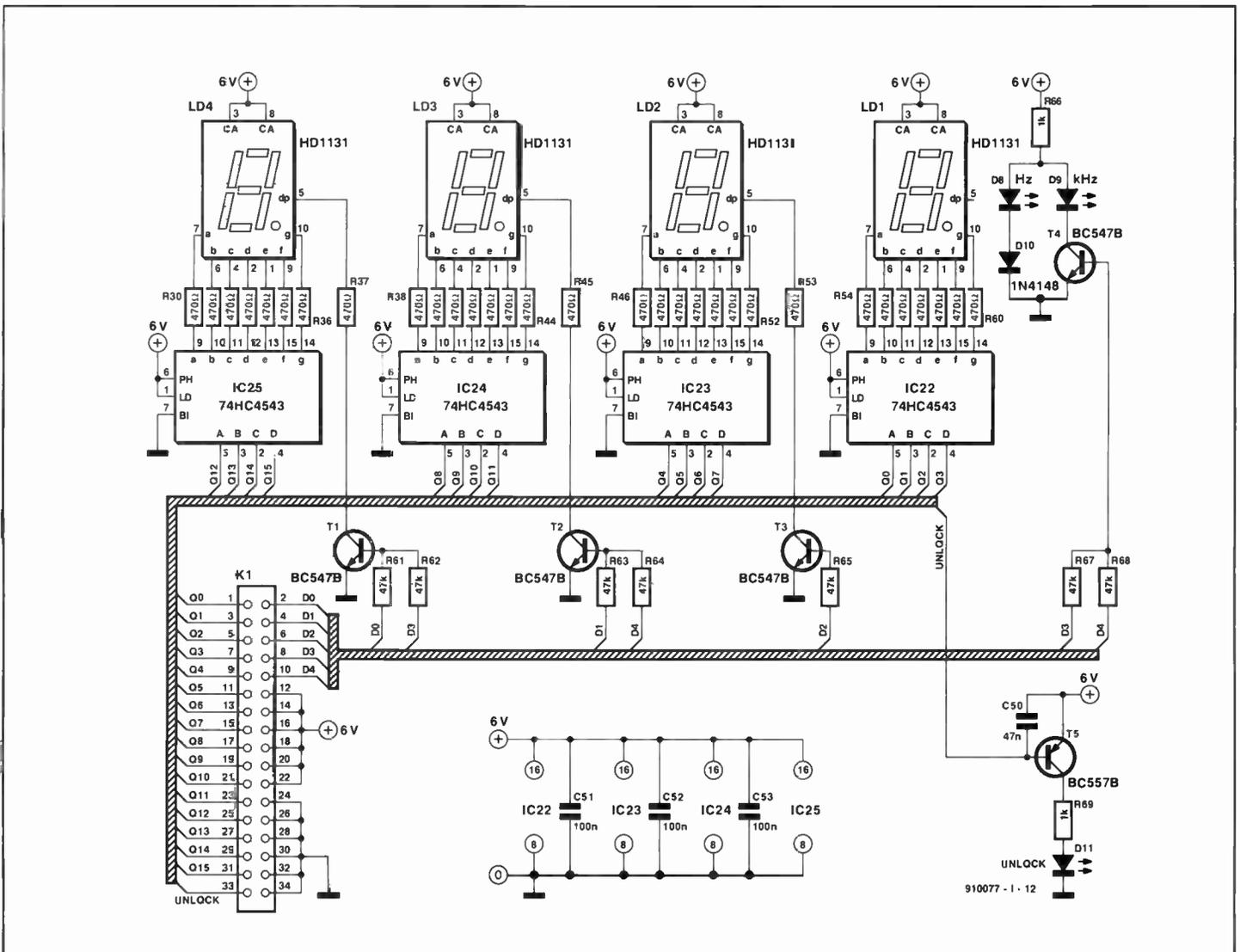


Fig. 9. Circuit diagram of the analogue (display) section of the digital function generator.

The first three are also applied to IC₇ in such a manner that when the divisor lies between 1 000 and 1 999, the VCO frequency divided by eight (pin 4 of IC₇) is internally coupled to the output (pin 5) of IC₇. When the divisor is between 2 000 and 5 999, pin 3 (VCO frequency divided by four) is connected to pin 5; when it lies between 6 000 and 7 999, pins 1-2 are connected to pin 5; and when it is between 8 000 and 9 999, pin 15 (VCO frequency) is coupled to pin 5. The overall divisor can, therefore, be set between 8 000 and 16 000.

The signal is applied to IC₉-IC₁₀, where it is divided by powers of 10 (10^1 - 10^4) as determined by the last transition of the clock. The four resulting signals, as well as the direct output of IC₇, are applied to pin 9 of multiplexer IC₁₁. This makes it possible to cover five decadic ranges with the same overall divisor, that is, 32-320 Hz, 320-3200 Hz, 3.2-32 kHz, 32-320 kHz and 0.32-3.2 MHz.

The multiplexer connects one of inputs X0-X4 or X8 to pin 1 (COM) and thence, via K₂, to the analogue section.

The multiplexer is controlled by DECADE switch S₇. Combination R₁₀-C₉ forms an anti-bounce network. When S₇ is pressed, a pulse is generated by Schmitt trigger IC_{20c} and used to clock Johnson counter IC₁₂. Successive outputs of IC₁₂ go high at each clock input.

To avoid elaborate settings of the divisor by means of binary coded decimal switches and to make presetting possible, UP and DOWN switches, S₂ and S₁ respectively, are used in combination with counters IC₁₃-IC₁₆. These circuits function as synchronous decade scalars with presettable output latches. Figure 6 shows that these circuits consist of three stages: the counter/divider proper; a memory (4-bit register); and a three-state output. The circuits are cascaded in such a manner that IC₁₃ processes the lowest decade, and IC₁₆ the highest. Preset inputs A-D on each of the scalars are connected to ground or the positive supply line by wire bridges or jump leads, except pin 3 of IC₁₆, which is connected permanently to +6 V to ensure that the start-up value is always 1 000. It is, of course, possible to set this value to a higher number.

The counters may operate in either of two modes, determined by RECALL/U-D switch S₅. If their pin 11 is high, the output buffer writes the content of the register, which in its turn stores the data of the counters when a first transition appears at pin 9 (RCLK). This transition is generated by switch S₆ (STORE). In practice, this means that, when S₅ is set to RECALL, S₆ must be pressed briefly to ensure

that the counter status is stored and passed to the output of the IC. When S₅ is set to U/D, pressing S₆ causes the counter status to be written into the register when the ICs receive the clock signal at their pin 2. Depending on the level at pin 1, the counters count up or down at every first transition.

The correct timing of the above process is ensured by the networks associated with


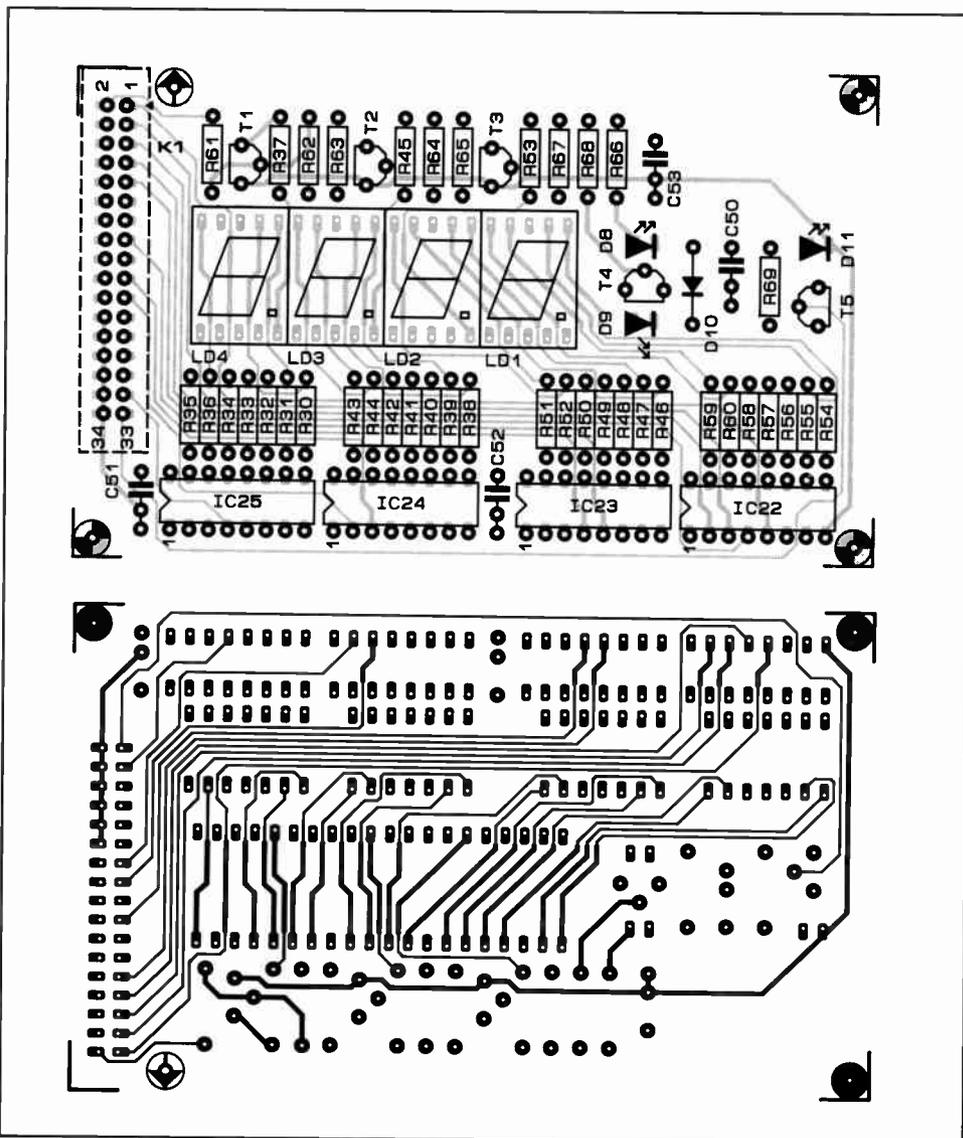


Fig. 10. Printed circuit board for the analogue (display) section of the generator.

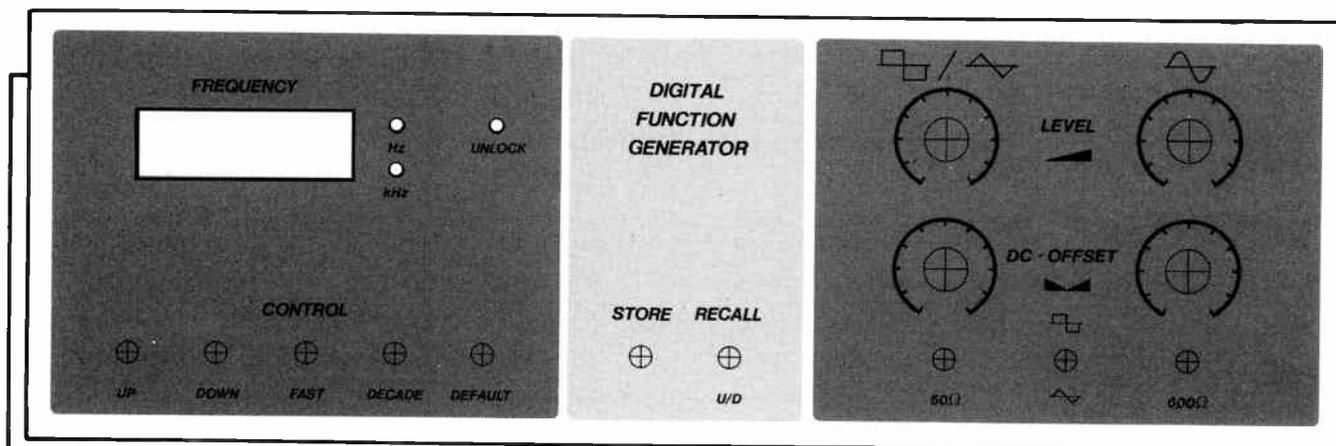

910077-F

Fig. 11. The foil for the front panel is available through our Readers' services.

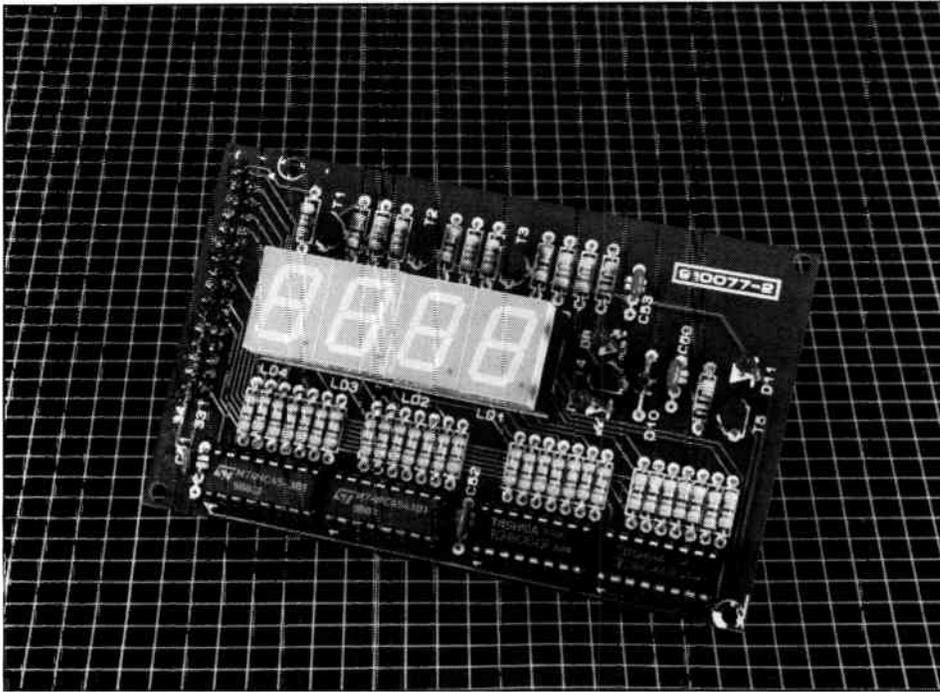


Fig. 12. Photo of completed analogue (display) section board.

switches S_1 and S_2 .

When S_1 is pressed, a rectangular pulse is generated by IC_{18a} and applied directly to the U/D input of IC_{13} – IC_{16} . The frequency of the pulse is determined by C_{12} and C_{13} . The clock is delayed slightly by network R_{18} – C_{18} and inverted by IC_{18c} – IC_{18d} – IC_{19b} – IC_{19d} – IC_{20b} and then applied to pins 2. This ar-

range ensures that the level at U/D is always low before the first transition arrives.

When S_2 is pressed, a pulse is generated by IC_{18b} , which ensures that pins 1 remain high so that the ICs can count upwards.

Switch S_3 enables selection of a low or fast clock. The clock speed can be altered by changing the values of C_{13} and C_{16} (fast: S_3

open) or C_{12} and C_{15} (slow: S_3 closed).

Although the clock is connected to all four pins 2, the ICs do not count identically, because the RCO output of IC_{13} enables the ENT input of IC_{14} only when in counter position nine the next first transition arrives, that is, at every tenth input pulse. The same happens between IC_{14} and IC_{15} and between IC_{15} and IC_{16} .

Gates $IC_{19a-b-d}$, IC_{18d} and a (discrete) OR gate disable the counters when position 1000 or 9999 is reached. For instance, when the 10 000th pulse is received, the RCO output of IC_{16} is applied to NAND gate IC_{18b} so that the clock is disabled. The same happens when the four highest bits, Q_{12} – Q_{15} , are low simultaneously (divisor < 1000) and the output of the wired-OR gate, D_2 – D_5 , is also low.

The counters can be reset to the start value by pressing the DEFAULT switch, S_4 . Network IC_{20a} – C_{11} – R_{15} generates the required pulse, which is applied to the LOAD input.

Analogue (display) section


The display section (circuit diagram in Fig. 9 is constructed on a separate board, shown in Fig. 11 (see also Fig. 10). All inputs to the section are via plug and socket (K_1).

The Q-bus is split into four. Each of the four groups is coupled to a BCD-to-seven-bit converter, IC_{22} – IC_{25} , which drive the four display segments. The decimal points and the Hz/kHz LEDs are controlled via the D_0 – D_4 lines.

Diode D_{11} lights when the PLL is not locked.

The second instalment of this three-part article will be published in our November 1991 issue.

Anatomy of a practical pulse

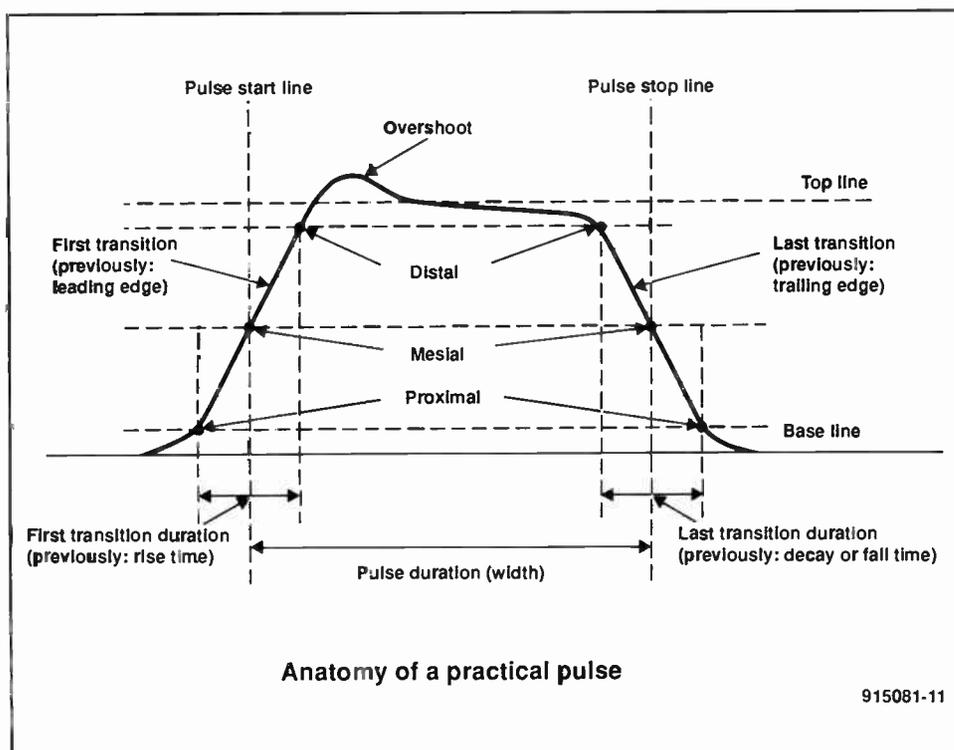

TECHNICAL literature is sprinkled with vague, misleading and ambiguous terms applied to a pulse. What does the term 'positive edge' mean when applied to a negative pulse? Is it the 'positive-going' edge, that is, in this case, the last transition, previously called 'decay' or 'fall' time, or is it the 'first transition', previously 'leading edge'?

Another common error is to assume that the 'pulse duration (or width)' is the duration between the first and last proximals, whereas, in fact, it is the duration between the pulse start and stop lines.

It should also be noted that the term 'duty cycle' should not be used in connection with pulses; the proper term for the ratio of the pulse duration to the pulse repetition period of a periodic pulse train is 'duty factor'.

Fortunately, there are national and international standards (among them British Standards and IEC) that normalize the terms describing properties of a pulse waveform: the most important are shown in the drawing. ■


A review of coding theory

by Brian P. McArdle

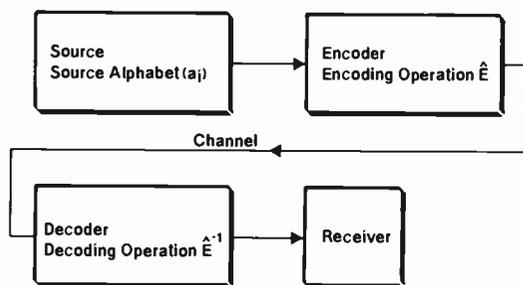1. Introduction

The general area of Coding Theory for telecommunications and computer applications is reviewed to provide a simple introduction to the subject. For further information, the reader should consult the books in the reference section.


There is no formal definition of a code. Essentially, messages are represented in some form more easily transmitted than normal written language. In this article, a code is a digital electronic signal that represents a message symbol, such as a letter or number. For example, a teleprinter code would have to have a signal for every possible symbol (26 letters, 10 numerals and other symbols) and signals for every operation (that is, space, carriage return and line feed controls). Figure 1 shows the arrangement.



910102 - 11

Fig. 1. Encoding/decoding operation.

An encoding operation \hat{E} turns a message symbol a_j into coded form for transmission over a channel. The set $\{a_j\}$ is the source alphabet and $\{\Pr(a_j)\}$ is the set of probabilities associated with this alphabet: $\Pr(a_j)$ is the probability that a_j occurs. In normal language, this is the probability of occurrence of letters. The word 'channel' has a general meaning. It could be a cable, radio link or storage medium where the receiver is retrieving the messages at some later time. Obviously, the receiver must be able to apply a decoding operation \hat{E}^{-1} . Hence, the principal requirement for a satisfactory code is that the coded symbols be uniquely decodable. In mathematical terms, $\hat{E}[a_j]$ cannot represent more than one symbol. $\hat{E}[a_j]$ cannot equal $\hat{E}[a_j]$ unless a_i and a_j are effectively the same symbol. For example, \hat{E} might

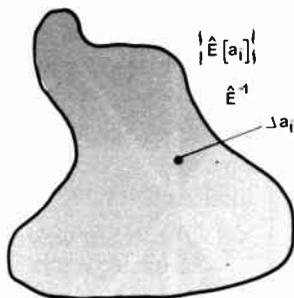

910102 - 12

Fig. 2. Partition of the set of coded symbols.

not distinguish between upper and lower case letters. The decoded messages may be printed in upper case letters only. Thus, apart from small variations that should not affect normal understanding, the encoding operation, irrespective of its complexity or purpose, must be exactly and uniquely reversible.

A more formal mathematical definition is that the set of coded symbols $\{\hat{E}[a_j]\}$ must be uniquely partitioned (that is, can be divided into subsets that do not overlap) such that each partition can be associated uniquely with a source symbol. Figure 2 shows the arrangement.

The remainder of this article attempts to explain the meaning of \hat{E} in different applications, such as error-detection-correction and encryption. It is always assumed that the encoding operation is uniquely reversible unless otherwise stated. Another important assumption is that a *memory-less source* is involved. The probabilities $\Pr(a_j)$ are the probabilities of the general occurrence of these symbols in normal language. In reality, letters occur in groups (digraphs and trigraphs). i before e , except before c is a well-known expression. Consequently, the probability of occurrence of a particular letter could be influenced by preceding letters. It is also assumed that a memory-less source is being considered unless otherwise stated. The analysis is mostly confined to digital coding except for Section 6, which deals with coding for analogue signalling.

2. Different codes

Codes can be analysed from many different viewpoints, but engineers are generally concerned only with two main categories.

(a) Fixed length codes

Every character of such a code is represented by a block of bits with every block having the same length. A typical example would be a computer code, such as ASCII or EBCDIC. Both of these use blocks of eight bits. Thus, there is a total of 2^8 or 256 difference blocks. Any two blocks of the same code would have to differ in at least one bit. The blocks need not be symbols (letters, numbers, punctuation marks) but can be controls (carriage return, line feed, etc.).

(b) Variable length codes

Consider an alphabet of five symbols $\{a, b, c, d, e\}$. In (a), this would require a code of three bits per block or symbol with $2^3 - 5 = 3$ redundant blocks. However, if the following arrangement of three blocks of two bits per block and two blocks of three bits per block is used,


$$a = 00, b = 01, c = 10, d = 110, e = 111,$$

the average length of a message would be reduced. Blocks still have a specific length, but it is no longer the same fixed length. The basic requirement for unique decoding must still be maintained. For example, the bit sequence **011100011110** is easily decoded to **bdac** with no errors. This must apply for all combinations of the symbols. An important quantity is the average length L of a block given by

$$L = \sum_j p_j \tau_j \quad [\text{Eq. 1}]$$

where p_j is the probability of occurrence of block type j with τ_j bits. Ideally, this should be as small as possible to minimize the total number of bits per message. To ensure this requirement, the large probabilities would be paired with the smaller blocks. Morse code is another example where the common letter e is a dot, but z is two dashes followed by two dots.

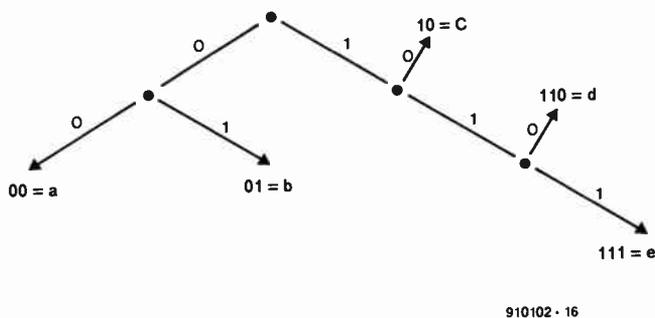This particular example has a special significance in addition to variable length blocks. If it is rewritten in the form of a diagram as below, it seems to have a tree-type structure with different branches.



Each branch is terminated by a symbol. The branches join together at nodal points which do not in themselves represent symbols. This arrangement indicates an *instantaneous* code. This means that the decoding operation does not require a 'memory', that is, it does not refer to blocks before or after any block that is being decoded. In the decoding of *bdac*, it was not necessary to test the 3rd bit before deciding that the first two bits, 01, represented *b*. This property remained true for the full operation and for all decoding operations irrespective of the combinations of symbols. (This should not be confused with a memory-less source, defined earlier, where there is no relationship between the occurrence of different symbols.). In an instantaneous code, no block can be a prefix or suffix for another block. Huffman codes, which are too involved to be considered in a simple overview, come into this category. However, it must be emphasized that any collection of blocks of varying lengths does not make an instantaneous code. There is a specific requirement given by the *Kraft inequality*

$$\sum_j \left(\frac{1}{2^{\tau_j}} \right) \leq 1$$

to form such a code. Further analysis is outside the scope of this paper and the reader is referred to the Reference Section for further study.

3. Information theory

Information theory has steadily increased its profile over the past few years and it is no longer possible to study telecommunications, especially coding, without touching on it somewhere. At first glance, the ideas behind it can appear too general and abstract for simple, direct applications. The fundamental fact is that the basic concepts of entropy, equivocation and channel capacity come from information theory, which, in turn, has influenced coding theory, and require some explanation.

There is a fundamental difference between an electronic signal and its value as information. In sound broadcasting, an unmodulated carrier would not convey any programme content to a listener. Therefore, there is a need to be able to quantify the value of a signal as information. In the 1920s, Hartley put forward the idea that the *logarithmic function* could be used as a measure of information. This was one of the landmarks in information theory. If two messages, a_i and a_j , are independent,

$$\log \{ \Pr(a_i) \text{ and } \Pr(a_j) \} = \log \{ \Pr(a_i) \} + \log \{ \Pr(a_j) \} \quad [\text{Eq. 2}]$$

and the base 2 is normally used. Remember that 'log' is not a linear function. The idea that the information contents of two independent messages is simply the sum of the information of each separate

message seems instinctively correct. However, this method of measuring information has no connection with an actual signalling system. The *entropy* for $A = \{a_j\}$ is given by

$$H(A) = - \sum_j \Pr(a_j) \log \Pr(a_j) \quad [\text{Eq. 3}]$$

and is a measure of the average information. An alternative explanation, which has become more common in recent years, is that it is a measure of the uncertainty in the information. $H(A)=0$ means that $\Pr(a_i)=1$ and $\Pr(a_j)=0$ for all other messages. Consequently, there is no doubt about the message. The maximum value occurs when the probabilities are the same and all messages are equally likely. If there are n possible messages, $H(A)$ is between 0 and $\log(n)$. The dimension is *information bits per symbol*.

To apply information theory to coding theory, consider Fig. 3 where there is a noisy channel between sender A and receiver B. The joint entropy is given by the equation

$$H(A,B) = H(A) + H(B/A) \quad [\text{Eq. 4}]$$

where $H(B/A)$ is known as the conditional entropy or *equivocation*. This in turn is defined as

$$H(B/A) = \sum_j H(B/a_j) \Pr(a_j) \quad [\text{Eq. 5}]$$

In non-mathematical terms, $H(B/A)$ is a measure of the information loss in transmission. The *channel capacity* is given by

$$C(A,B) = \text{maximum } H(A) - H(A/B) \quad [\text{Eq. 6}]$$

This appears correct because the limit on the information conveyed over a channel is determined by the original uncertainty of that information (before reception) reduced by the uncertainty after reception. Essential capacity is limited only by noise and the *Hartley-Shannon law* sets an upper limit of $W \log(1+S/N)$, where W is the information bandwidth, S is the signal power and N is the noise power. For technical reasons, present-day systems operate well below this limit. The reader is referred to the Reference Section for further study.

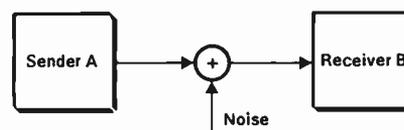


Fig. 3. Communications channel.

From the point of coding and electronic engineering, Eq. 6 can be simplified for normal use. Consider the case for a binary channel where A and B represent the input and output respectively. In general, the probability of a '0' or '1' is $1/2$, which gives $H(A) = \log(2) = 1$. (The entropy of the source alphabet could be computed from the probability of occurrence of the various symbols, but it is the channel that is now under consideration.). If p is the probability of an error where a '0' is received as a '1', or vice versa, the channel conditional probabilities are

| | | | |
|---|---|---------|---------|
| A | B | 0 | 1 |
| 0 | | $(1-p)$ | p |
| 1 | | p | $(1-p)$ |

From Eq. 5:

$$H(A,B) = \Pr(0) [-(1-p) \log(1-p) - p \log(p)] + \Pr(1) [-p \log(p) - (1-p) \log(1-p)] \quad [\text{Eq. 7}]$$

which gives a new expression for the *channel capacity*:

$$C(A,B) = 1 + p \log(p) + (1-p) \log(1-p) \quad [\text{Eq. 8}]$$

in bits per symbol. This is the usual expression in most textbooks on telecommunications. If the signalling rate is R symbols per second, the right-hand side is multiplied by R to give bits per second. Thus, information theory can be useful in the analysis of codes. The entire area has become extensive and has been treated only superficially here.

4. Error detection and correction

Error detection and correction is one of the main applications of coding theory and paralleled its development. Figure 3 showed the problems with errors where a '0' can be received as a '1' or vice versa. The use of the word 'receiver' is general in that it could represent a storage medium, and so on. It suffices to say that data is corrupted, which limits its value upon reproduction. Section 3 demonstrated that channel capacity is limited only by noise. To reduce the effects of errors, and therefore noise, extra bits are added to a block of data bits to create new and larger blocks, which in turn allow errors to be identified.

Consider the (7,4) Hamming code as follows:

$$\begin{array}{l} \text{Position: } 7 \quad 6 \quad 5 \quad 4 \quad 3 \quad 2 \quad 1 \quad c_4 = (d_7 + d_6 + d_5) \bmod 2 \\ \text{Bit: } \quad d_7 \quad d_6 \quad d_5 \quad c_4 \quad d_3 \quad c_2 \quad c_1 \quad c_2 = (d_7 + d_6 + d_3) \bmod 2 \\ \quad c_1 = (d_7 + d_5 + d_3) \bmod 2 \end{array}$$

There are three check bits in positions 1, 2 and 4 which have been derived from the data bits in the other four positions. The code is linear in the sense that the check bits are linear combinations of the data bits and the encoding operation is simply the application of the three linear equations. Since every block will have a total of seven bits without exception, the code is in the fixed length category. The position of the check bits within the block is very significant. A receiver generates the check bits from the received data bits and applies the decoding rule in Appendix 1. For example, if d_3 has been altered, c_1 and c_2 will not be validated and so on. The arrangement to check five data bits is given in Appendix 2. In both these examples, the set of coded blocks is such that the minimum variation between any two blocks in the same set is three bits. This is known as the Hamming distance. The reader is referred to Reference 2 for a more detailed explanation. The main point to note is that the method identifies only one error per block. In general, r check bits have $(2^r - 1)$ possible combinations and thus r bits in a total size of n bits must satisfy the condition $(2^r - 1) \geq n$ in order to identify and therefore correct one error. To correct two or more errors per block, a code with a larger Hamming distance and more complicated arrangement would be needed.

Cyclic codes are the most commonly used for error detection and correction. These are also of the fixed length variety. For a block of total size n , the check bits are produced by a generator polynomial which is a factor of $(x^n + 1)$. A typical example is the specification MPT 1317 for the transmission of data over radio links. The format is as follows:

| | DATA | CHECK | PARITY |
|-----|---------------------|-----------------|--------|
| Bit | 64 63 62 17 | 16 15 2 | 1 |

with a block size of 64 bits. However, the first bit is for parity and is generated by the other 63 bits. The 15 check bits are generated from the 48 data bits using the generator polynomial

$$g(x) = x^{15} + x^{14} + x^{13} + x^{11} + x^4 + x^2 + 1 \quad [\text{Eq. 9}]$$

which is a factor of $(x^{63} + 1)$. Refer to Appendix 3 for an exact breakdown. The data bits are the coefficients of the terms x^{62} down to x^{15} inclusive. Some books write the data bits on the right-hand side of the format, but this is not important provided they represent the high power terms of the polynomial. The polynomial consisting of only the data bits is divided by $g(x)$. The remainder is then added

back to produce a new polynomial such that $g(x)$ is now a factor of the new polynomial. Since the check bits are essentially the original remainder, they represent the terms x^{14} down to x^0 . Then a parity bit is added in order to detect odd numbers of 1s and the full 64-bit block should have even parity. Refer to Appendix 4 for the generation of a parity bit. The overall result is that the code can identify and correct up to four errors per block. This is a considerable improvement on the (7,4) Hamming code, but the operation is much more involved and the block size nine times larger. To check for errors, the receiver divides the polynomial by $g(x)$ and there should be no remainder.

Another example is the POCSAG code for paging, which uses the format

| | DATA | CHECK | PARITY |
|-----|---------------------|--------------|--------|
| Bit | 32 31 30 12 | 11 2 | 1 |

and the generator polynomial

$$g(x) = x^{10} + x^9 + x^8 + x^6 + x^5 + x^3 + 1 \quad [\text{Eq. 10}]$$

which is a factor of $(x^{31} + 1)$. Refer to Appendix 5 for an exact breakdown. The overall method is the same with the 21 data bits generating the 10 check bits to produce a 31-bit block plus an extra parity bit.

5. Encryption

In encryption, the \hat{E} operation, defined in Section 1, represents a secrecy operation and is usually written as \hat{E}_K in most textbooks. The parameter K is known as the key and its purpose is to vary the operation. This is in complete contrast to error-detection-correction where exactly the same operation is performed on all blocks without exception. The importance of K is that it is generally the part of \hat{E}_K that is kept secret. In a publicly known algorithm, such as the Data Encryption Standard (DES), the complete algorithm is known. A user chooses a key from the set of possible keys $\{K\}$ and encrypts the data. Thus, only encrypted data appears on the channel of Fig. 1. The data can be recovered by the inverse or decryption operation \hat{E}_K^{-1} which also requires the correct key. If the key in use is kept secret and only known to authorized receivers, the data is kept secret. Obviously, $\{K\}$ must be sufficiently large to prevent an unauthorized user from trying each key in turn. There are a number of other requirements that are outside the scope of this paper.

There are three main methods of encryption.

(a) Stream encryption

In Fig. 4, each bit of the data is added modulo 2 using an XOR logic operation. A sequence of key bits is produced by the key generator such that each data bit is encrypted by its own particular key bit.

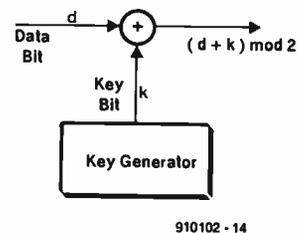



Fig. 4. Stream encryption.

The authorized receiver must know the method of key generation to reproduce the exact same sequence. The inverse operation is simply to apply the key sequence in the correct order to the sequence of encrypted bits. It would be too complicated to discuss the various techniques of key generation, but the most common method uses shift registers to generate a pseudo-random binary sequence. Generally, part of this process must be kept secret, such as the number of stages and feedback arrangements. The current proposals to provide en-

ryption facilities on the cellular system GSM or for digital short-range radio DSRR are believed to use a form of stream encryption. However, the information is confidential and it is very likely that the exact method will not be made public.

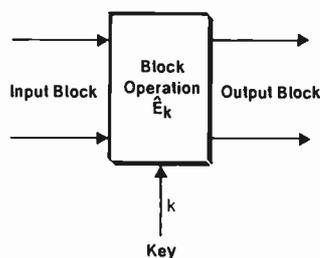(b) Block encryption

Block encryption—see Fig. 5—differs from stream encryption in that a block is encrypted as a single unit. The most widely known method is the US *Data Encryption Standard*, which uses blocks of 64 bits for input and output. The algorithm was published in 1977 and the exact method is for public information. The actual key is a 56-bit block, so that the number of possible keys is 2^{56} . In operation, the authorized receiver would know the particular key in use and apply the inverse or decryption algorithm. Controversy has always surrounded the key size and recent articles have suggested methods for an improved DES.



910102 - 15

Fig. 5. Block encryption.

The main advantage over (a) is that a satisfactory block operation creates interdependence between the bits of a block. If one bit of an input block is varied, a number of bits in the output block are altered. However, it is generally much slower than stream encryption and cannot be used for high-speed telecommunications applications.

(c) Public key encryption

Public key encryption differs from the methods in (a) and (b) in that part of the key is made public, whence its name. The main requirement is that the part which must remain secret should not be easily deducible from the public part. A typical example is the RSA method introduced in 1978. Each user publishes two numbers, N and e . N is very large, of the order of 80 digits, and the product of two primes, P and Q , while e and d satisfy the equation

$$1 = ed \text{ mod } (P-1)(Q-1). \quad [\text{Eq. 11}]$$

Only e is made public; d , P and Q remain secret. If user A wishes to forward the message 'a' to user B, A looks up the parameters N and e for B and transmits

$$b = a^e \text{ mod } N. \quad [\text{Eq. 12}]$$

User B recovers the original message from

$$a = b^d \text{ mod } N; \quad [\text{Eq. 13}]$$

since d is one of the secret parameters, this cannot be done by any other user. From a secrecy point of view, an unauthorized user would have to factor N into P and Q to calculate d . Thus, as long as N is sufficiently large, this is impractical and the method is secure. There are other methods, such as the *Merkle-Hellman-Knapsack Method*, but they all follow the same principle of a public and a private key. Equations 12 and 13 are the equivalents of the encoding and decoding operations.

6. Coding for analogue signalling

In the preceding four sections, it was assumed that digital signal

processing was in use. However, codes are also used in analogue electronics, but their application is rather limited. For example, in the PMR service, CTCSS (continuous tone controlled signalling system) has been around for a number of years. During transmission, an encoder generates a specific audio tone that modulates the radio frequency carrier. This tone is continuous for the duration of a message. In the absence of a CTCSS signal, the decoder at the receiving end is deactivated.

Another example is tone selective calling, such as EEA and ZVEI. In these methods, a sequence of five tones is used to form an address for a receiver. Both EEA and ZVEI have a total of 12 possible tones. Each possible address consists of a set of five, which actuates the receiver from the point of the user. However, despite these examples, coding has remained almost exclusively digital and the cellular GSM standard actually prohibits the use of tones.

On the secrecy side, there are voice scramblers that use frequency inversion, but increasingly the trend has been to digitize speech (for instance, ADPCM—Appendix 6) and to apply the techniques of Section 5. Coding in analogue signal processing is very restricted and need not be considered seriously.

7. References

- (1) *Information Theory and its Engineering Applications*
D.A. Bell; Pitman (1968)
- (2) *Coding and Information Theory*
Richard W. Hamming; Prentice-Hall (1980)
- (3) *Information and Coding*
J.A. Llewellyn; Chartwell-Bratt (1987)
- (4) *A First Course in Coding Theory*
Raymond Hill; Oxford University Press (1986)
- (5) *Codes and Cryptography*
Dominic Welsh; Oxford University Press (1988)
- (6) *Coding for Digital Recording*
John Watkinson; Focal Press (1990)

Appendix 1

The receiver re-calculates the check bits and validates them against the received values.

c_1 and c_2 are not validated $\Rightarrow d_3$ is incorrect
 c_1 and c_4 are not validated $\Rightarrow d_5$ is incorrect
 c_2 and c_4 are not validated $\Rightarrow d_6$ is incorrect
 c_1, c_2 and c_4 are not validated $\Rightarrow d_7$ is incorrect

The sum of the indices of the check bits indicate the location of the erroneous bit. The correction process replaces a '0' by a '1' or vice versa. The principal difficulty is that two errors can cause a correct bit to be changed.

Appendix 2

The Hamming code for five data bits is $d_9 d_8 d_7 d_6 d_5 d_4 d_3 d_2 c_1$ and requires four check bits with the same procedure as in the (7,4) code. r check bits can test up to $2^r - 1$ locations. For $r=3$, this gives $n=2^3 - 1$, which leaves four data bits. For $r=4$, there is a block size $n=15$ which allows for 11 data bits and four check bits in the order:

$d_{15} d_{14} d_{13} d_{12} d_{11} d_{10} d_9 d_8 d_7 d_6 d_5 d_4 d_3 d_2 c_1$.

Appendix 3

For a 63-bit block, the factors of the modulus are:

$$(x^{63}+1)=(x+1)(x^2+x+1)(x^3+x+1)(x^3+x^2+1)(x^6+x+1)(x^6+x^3+1) \\ (x^6+x^4+x^2+x+1)(x^6+x^4+x^3+x+1)(x^6+x^5+1)(x^6+x^5+x^2+x+1) \\ (x^6+x^5+x^3+x^2+1)(x^6+x^5+x^4+x+1)(x^6+x^5+x^4+x^2+1).$$

Each of these factors is irreducible in that it cannot be factored further while keeping real coefficients that are 0 or 1. In MPT 1317, the generator polynomial has the following factors:

$$x^{15}+x^{14}+x^{13}+x^{11}+x^4+x^2+1=(x^3+x^2+1)(x^6+x+1)(x^6+x^4+x^2+x+1)$$

and is a factor of $(x^{63}+1)$ as per the mathematical conditions.

Appendix 4

Consider the generation of a parity bit in the following table

| | | | | |
|----|---|---|---|---|
| d3 | 0 | 0 | 1 | 1 |
| d2 | 0 | 1 | 0 | 1 |
| c1 | 0 | 1 | 1 | 0 |

In mathematical terms, the appropriate generator polynomial, $g(x)$, divides the polynomial $(d_3x^2+d_2x+1)$. Let

$$g(x)=(x+1) \quad \text{and} \quad d_3x^2+d_2x+c_1=(w_1x+w_2)(x+1)$$

Equating terms on each side gives

$$w_1=d_3 \quad w_1+w_2=d_2 \quad w_2=c_1 \\ w_2=w_1+d_2=d_3+d_2=c_1$$

as per the table. In Appendix 3, the generator polynomial is not a factor of $(x^{64}+1)$, but of $(x^{63}+1)$. The 64th parity bit has the generator polynomial $(x+1)$.

Appendix 5

For the *POCSAG*, the modulus has the following factors

$$(x^{31}+1)=(x+1)(x^5+x^2+1)(x^5+x^3+1)(x^5+x^3+x^2+x+1) \\ (x^5+x^4+x^2+x+1)(x^5+x^4+x^3+x+1)(x^5+x^4+x^3+x^2+1)$$

and the generator polynomial consists of the factors

$$x^{10}+x^9+x^8+x^6+x^5+x^3+1=(x^5+x^2+1)(x^5+x^4+x^3+x^2+1)$$

and thus divides $(x^{31}+1)$.

Appendix 6

ADPCM (adaptive differential pulse code modulation) was accepted by the CCITT in 1984 for encoding speech. Each sampled speech signal is originally encoded into a 12-bit block. This is compared with 16 quantizing levels and the nearest level chosen. This means that a block of 12 bits can now be replaced by a block of only four bits. The actual mechanism is quite complicated and is considerably different from PCM. The final result is a transmission rate of 12 kbit/sec. ■

FOUR-TERMINAL NETWORKS - PART 1

Getting to grips with attenuators

by Steve Knight, BSc

Most electronic equipment has an attenuator or attenuators of one sort or another. The object of these is to reduce to manageable levels a signal we have elsewhere worked like mad to build up. The usual objective is to turn out more than we want, then cut it down to the size we do want. This might sound like an easy option but, like many other things electronic, what we want and what we get aren't always identical. So, apart from the intrusion of Sod's Law which reigns universally, I hope that what follows will cast a ray of light on the often neglected subject of attenuator systems.

WE might define transmission networks in general terms as circuits that have two input terminals and two output terminals which are introduced between a generator and its load impedance. These networks, which are referred to as four-terminal networks, have properties that depend on the work they have to do in the transmission system; in the case of an attenuator, which is our main concern, it must enable us to obtain as output some desired fraction of the input which is entirely independent of the signal frequency. Clearly, such an attenuator system must be built up from purely resistive

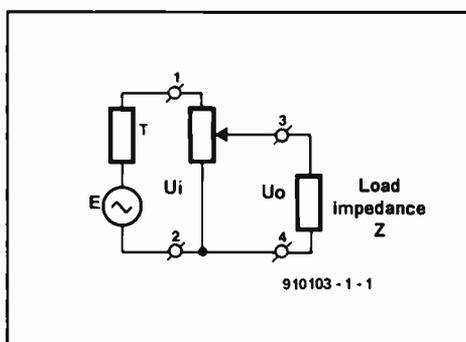


Fig. 1. Elementary attenuator.

elements, since reactive components will lead to frequency discrimination over all or certain parts of the band. Further, existing impedance conditions in the system into which the attenuator is introduced must not be disturbed.

The most elementary attenuator of all is the potential divider network that usually turns up in the form of a variable resistor. Figure 1 shows the system; our input goes between terminals 1 and 2 and we get the output from terminals 3 and 4. This is a four-terminal network, two of whose terminals are commoned, and we obtain an output that can be

a fraction of the input lying between the limits of 0 and 1. This is, no doubt, quite a satisfactory arrangement for turning the volume up and down on a radio receiver, but it fails dismally if we harbour ambitions for making precise quantitative measurements. Outside of the simplest applications to which such an attenuator might be put, the disadvantages are not hard to find.

The output has to feed into some kind of load impedance; assume for a moment that this is resistive. What the input terminals 'see', therefore, is not a constant resistance, but one that is made up of a non-linear combination of two resistances in parallel. Hence, the generator loading is variable and the potential difference—p.d.—at the input terminals is itself changing as the attenuator is operated. Not really the sort of thing we want if we are concerned with exactly how much attenuation we are getting and how it might affect the characteristics of the transmission path. What do we require from an attenuator if it is to do a worthwhile job? Well, we want it to introduce any needed degree of attenuation, but at the same time we want the input and output resistances to be such that the impedance conditions existing in the circuit are not upset in any way: if I want to insert an attenuator into a 300 Ω line, the attenuator impedance must also be 300 Ω.

Let us see how well-defined characteristics can be applied to attenuator networks so that we can get the quantitative results we want for our own particular requirements.

Basic characteristics

Four-terminal networks may come in two formats: symmetrical, in which we can interchange the input and output terminals without affecting in any way the electrical characteristics of the circuit; and asymmetrical, in which this last condition does not hold. The simple attenuator of Fig. 1 is clearly asymmetrical. Each of the two formats may be balanced or unbalanced, definitions to which we shall revert later on.

Symmetrical systems have two fundamental characteristics that are essential to our understanding of their function in life: the characteristic impedance, symbolized Z_0 in the complex case, and the attenuation constant α . For purely resistive networks, we can talk about characteristic resistance, R_0 , and attenuation factor N .

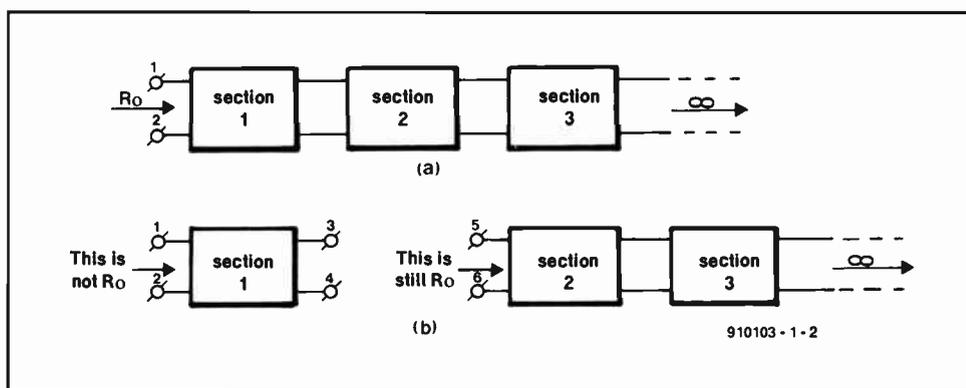


Fig. 2. Defining the characteristic resistance of a network.

Characteristic resistance

Let us use our imagination for a moment. Suppose we have a network made up of an infinite number of identical repetitive sections as in Fig. 2a. Each section contains a number of resistances, but how these are actually arranged is not important at this stage. Suffice it to say that the resistance measured at the input terminals, 1 and 2, will have a certain magnitude that will depend only on the nature and circuit arrangement of the individual sections. Suppose this resistance to be R_0 .

Now, it might appear that we are getting into deep water by this approach: as the network is infinitely long, what chance do we have of calculating R_0 for a specific case where the contents of only one (or of a finite number) of the sections is known? Fortunately, there is a way out of the impasse by a relatively simple dodge: suppose we remove the first section of the infinite chain as in Fig. 2b. The input resistance of the remainder of the array as measured at terminals 5 and 6 will be the same as that measured originally at terminals 1 and 2, because the infinite nature of the assembly is unaffected by removing the first section (or any finite number of sections, come to that); so we could still measure R_0 . The input resistance of the section we have removed, however, is very unlikely to be R_0 , but we can make it so in one of two ways: by replacing the rest of the infinite chain (not a very practical way, to be sure), or by putting across terminals 3 and 4 a single resistance of a value equal to R_0 .

Now, this second method gives us the clue we want: no matter how many finite sections we remove from the infinite chain, if we terminate them with a resistor of value

R_0 , the input resistance will also be equal to R_0 since these sections are effectively terminated by R_0 when reconnected to the rest of the infinite array. With this proper value of termination, that is, the characteristic resistance of each section, therefore, the input conditions are such that anything connected to the input terminals cannot distinguish between an infinite network or a finite network so terminated.

Hence, we can define the characteristic resistance, R_0 , of an attenuator network: *any symmetrical network terminated in R_0 will have an input resistance also equal to R_0 .* And this, of course, must also be true when working from output to input.

Attenuation factor

What about the attenuation constant, or the attenuation factor as it is more generally known for resistive networks? Well, this simply tells us the loss sustained in each section of a network. This loss may be expressed as a fraction of the input or as a reduction in decibels (dB); if the output is one-half the input, for example, the voltage (or current) attenuation is 6 dB.

Each section of an attenuator network will attenuate at identical rates, but the actual amount of attenuation is different as we proceed along the chain. Suppose, for instance, that we start off with unit input and lose half of this input in each section. The output of section 1 will be $1/2$ and this becomes the input to section 2. Here again, half the input is lost, so the output of section 2 will be $1/2 \times 1/2$ or $1/4$. After the following section, the output will be $1/4 \times 1/2 = 1/8$. Hence, the amount of loss differs for each section because the

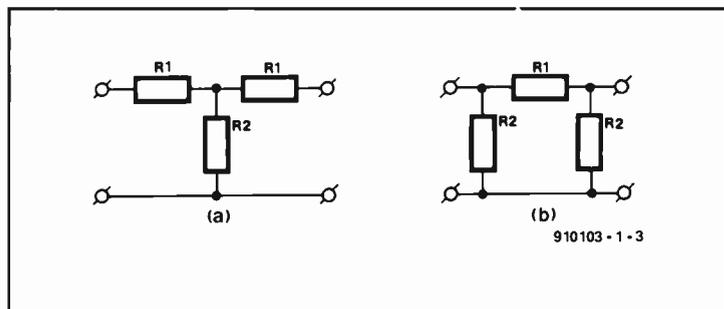


Fig. 3. The forms of the T-section and the π -section attenuators.

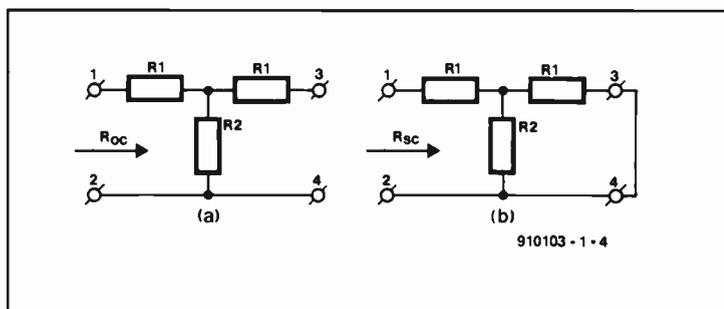


Fig. 4. Extreme termination conditions enable R_0 to be calculated.

magnitude remaining to be attenuated at any stage is becoming progressively smaller. The *rate* of loss, however, remains constant.

For n sections, each reducing the input by some fraction p , the output will be p^n ; if the attenuation is expressed in dB, n sections, each having a loss of p dB, will have an overall loss of np dB.

Finding R_o

Let us get down to the job of calculating the characteristic resistance of an attenuator section from a knowledge of its component parts.

The forms taken by individual sections of the general attenuator array are T-sections or π -sections; these are illustrated respectively in Fig. 3a and Fig. 3b. The T-section, as its configuration clearly implies, is made up of a divided series-arm and a central shunt-arm. Used between equal impedances, the section is symmetrical when the series-arm contains two equal resistances. The π -section, again as its form implies, consists of a single series-arm and two shunt-arms. This section is symmetrical when the shunt-arms are equal resistances. Both sections, though symmetrical in the way described, are unbalanced in the sense that the series-arm members are on one side of the section 'through' wires. It is essential not to get 'symmetry' confused with balance when talking about attenuator sections.

Working on the T-section for convenience (the π -section will lead us to exactly the same end-result), suppose we terminate the section at points 3 and 4 with the extreme conditions of, first, an open-circuit, and secondly, a short-circuit. Figures 4a and 4b show these cases. Clearly, in the first case, the input resistance seen at terminals 1 and 2 will be

$$R_{oc} = R_1 + R_2,$$

and in the second case, it will be

$$R_{sc} = R_1 + R_1 R_2 / (R_1 + R_2).$$

Now, between these open-circuited and short-circuited conditions at the termination, there can be an infinite range of resistance values; as the termination changes through this range, the input resistance will change also. It seems reasonable, therefore, that there will be *some* value of the terminating resistance that will make the input resistance *also* equal to this value. This value

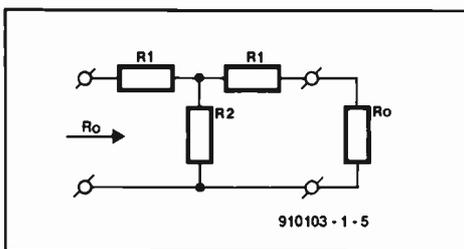


Fig. 5. A correctly terminated section.

must be, in accordance with our earlier stated definition, the characteristic resistance of the attenuator section. So, from Fig. 5 we have

$$R_o = R_1 + R_2(R_1 + R_o) / (R_1 + R_2 + R_o).$$

Solving this for R_o , we get

$$R_o = \sqrt{(R_1^2 + 2R_1 R_2)}.$$

This enables us to find the characteristic resistance of a section from a knowledge of the resistor values making up the section.

We can now go one step further and find R_o without necessarily knowing the values of the elements used in a section. All we need to know is the input resistance (which can easily be measured) when the output terminals are either open-circuited or short-circuited. For, looking back a few lines, we have the product $R_{oc} R_{sc}$ expressible as

$$R_{oc} R_{sc} = (R_1 + R_2)[R_1 + R_1 R_2 / (R_1 + R_2)],$$

and multiplying this out, we get

$$R_{oc} R_{sc} = R_1^2 + 2R_1 R_2.$$

The right-hand side of this is R_o^2 , so that

$$R_o = \sqrt{(R_{oc} R_{sc})},$$

which provides us with a very neat way of calculating the characteristic resistance of any section.

Cascaded sections

Although a single section will operate successfully as an attenuator, it is usual to have a number of sections in cascade or tandem so that a range of attenuation is provided. Once the R_o of a particular section has been found, another section may be added to it without affecting the overall characteristic resistance. For, if in Fig. 6a section A is terminated

correctly by R_o , an identical section connected in place of R_o , will in turn correctly terminate A, since section A will be unable to distinguish between the presence of section B or the presence of a single terminating resistor equal in value to R_o .

It is plain that no matter how many such sections are wired in cascade, the input resistance will remain at R_o . What will change as we progress along the chain is the total attenuation: each section will introduce the same attenuation, but the desired overall attenuation can be achieved by using the required number of sections.

Finding the attenuation

Knowing the characteristic resistance of a circuit into which an attenuator is to be inserted, the problem of design boils down to finding suitable values for R_1 and R_2 , given R_o and the required attenuation.

A desired value of R_o can be obtained with numerous combinations of R_1 and R_2 ; looking at Fig. 7, for instance, both sections shown have a characteristic resistance of 30Ω (check on this for yourself!), but the network on the right will provide a greater degree of attenuation than the one on the left.

As we have already mentioned, the attenuation may be expressed as a fraction, that is, as a ratio of output voltage (U_o) to input voltage (U_i). Expressed in decibels,

$$\text{attenuation} = 20 \log(U_i / U_o).$$

If the ratio of the input power, P_i , and the output power, P_o , is taken,

$$\text{attenuation} = 10 \log(P_i / P_o) \quad [\text{dB}]$$

$$= 20 \log \sqrt{(P_i / P_o)} \quad [\text{dB}],$$

whence $U_i / U_o = \sqrt{(P_i / P_o)} = N$, the attenuation factor. Notice that with this notation the attenuation is expressed as a whole number, not a proper fraction. This often makes calculations easier.

In next month's concluding part of this article, we shall see how the attenuation can be provided, and how practical attenuators can be built to suit a variety of occasions.

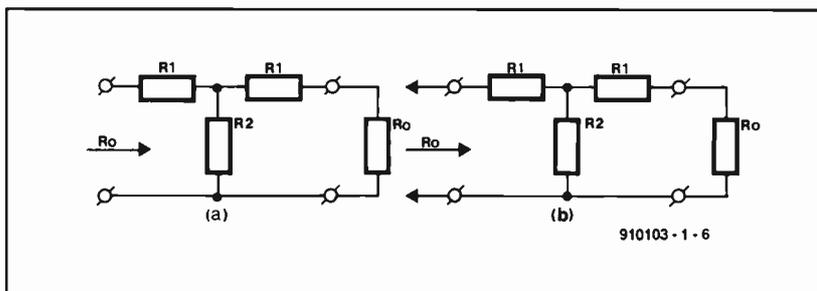


Fig. 6. How sections can be cascaded.

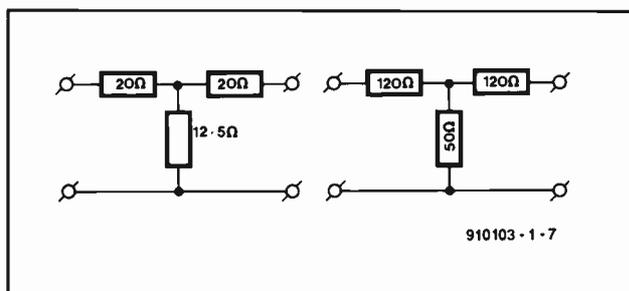


Fig. 7. Networks with identical R_o but different attenuations.

Fiber Optics — Part 2

Last month we discussed the basic theory behind optical fiber systems. It was learned that fiber optics are the light equivalent of microwave waveguides, and that they are capable of immense bandwidth communications. In this month's final instalment we will look at fiber communications and some of the circuits that can be used with experimenter grade optical fiber kits.

by Joseph J. Carr

Losses in optical fiber systems

Decibel notation can be used for optical fiber systems and refers to the gain or loss of each stage or component in the system. The dBkm scale uses decibels of gain or loss relative to the attenuation of a standard optical fiber section over a one kilometre (1 km) length. Alternatively, either dBmi (dB loss relative to attenuation over 1 mile) or dBl (a normalized unit length) can be used.

The light power at the output end of an optical fiber (P_o) is reduced compared with the input light power (P_{in}) because of losses in the system. As in many natural systems, light loss in the fiber material tends to be decaying exponentially (Fig. 1a), so obeys an equation of the form:

$$P_o = P_{in} e^{(-\Lambda/L)} \quad [1]$$

Where:

Λ is the length of the optical fiber being considered;

L is the unit length, i.e., the length for which $e^{-\Lambda/L} = e^{-1}$.

There are several mechanisms for loss in fiber optics systems. Some of these are inherent in any light-based system, while others are a function of the design of the specific system being considered.

Defect losses

Figure 1b shows several possible sources of loss owing to defects in the fiber itself. First, in unclad fibers, surface defects (nicks or scratches) that breach the integrity of the surface will allow light to escape. In other words, not all of the light is propagated along the fiber. Second (also in unclad fibers), grease, oil or other contaminants on the surface of the fiber may form an area with an index of refraction different from what is expected and cause the light direction to change. And if the contaminant has an index of refraction similar to glass, then it may act as if it were glass and cause loss of light to the outside world. Finally, there is always the possibility of inclusions, i.e., objects, specks or voids in the material making up the optical fiber. Inclusions can affect both clad and unclad fibers. When light hits the inclusion it tends to scatter in all directions, causing a loss. Some of the light rays scattered from the in-

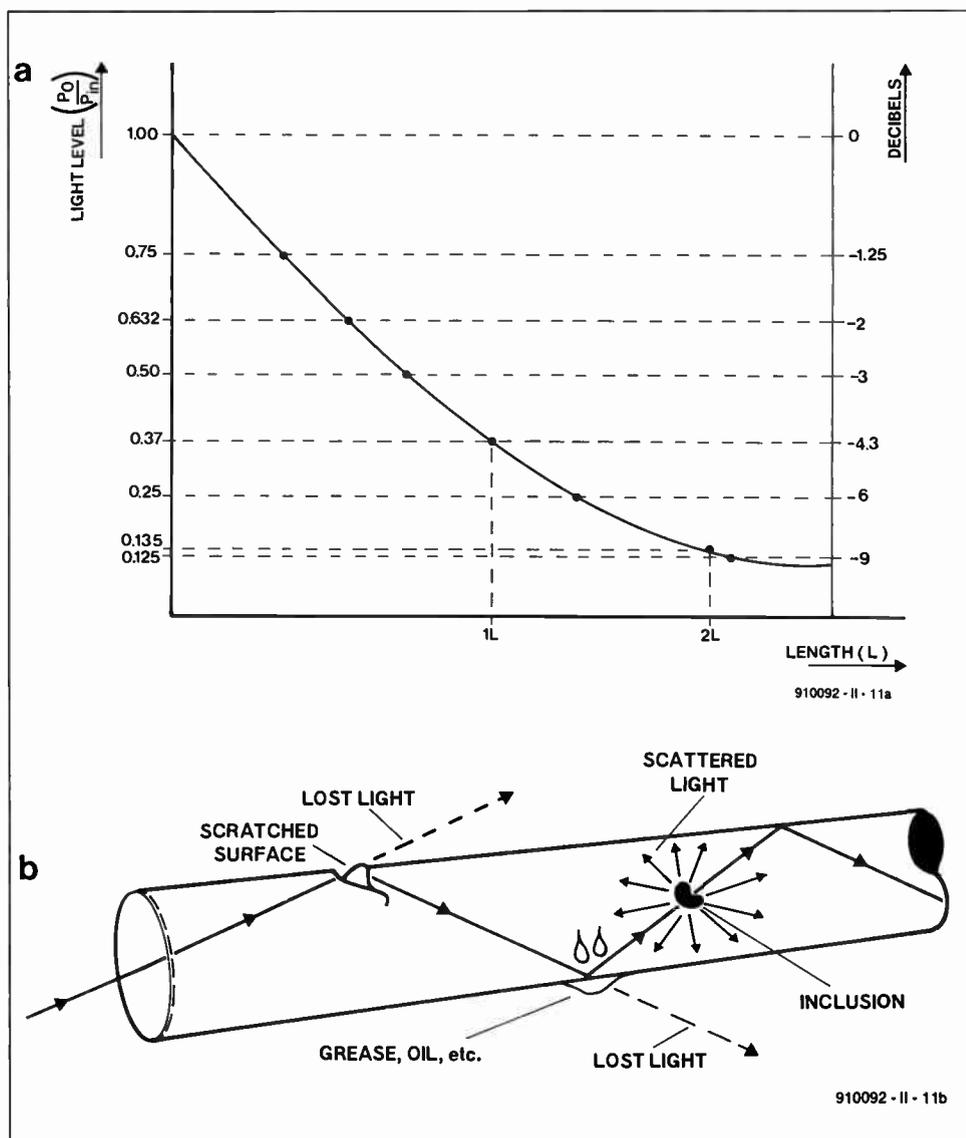


Fig. 1. (a) Exponential decay of signal strength along an optical fiber; (b) mechanisms of loss in fibers.

clusion may recombine either destructively or constructively with the main ray, but most do not.

Inverse square law losses

In all light systems there is the possibility of losses caused by spreading (divergence) of the beam. If you take a flashlight and point it at a wall, and measure the illuminance per unit area at the wall at a distance of, say, one meter, and then

back off to twice the distance (two meters) and then measure again, you will find that the illuminance has dropped to one-fourth. In other words, the illuminance per unit area is inversely proportional to the square of the distance ($1/d^2$).

Transmission losses

These losses are caused by light that is caught in the cladding material of clad optical fibers. This

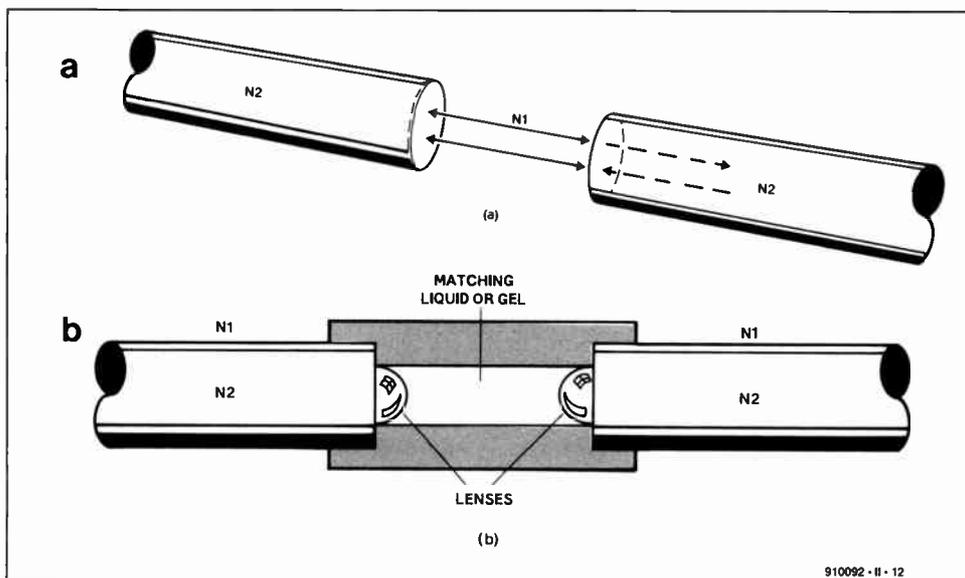


Fig. 2. (a) Air coupling creates reflection losses; (b) matching liquid coupling improves the junction.

light is either lost to the outside, or is trapped in the cladding layer and is thus not available for propagation in the core.

Absorption losses

This form of loss is caused by the nature of the core material, and is inversely proportional to the transparency of the material. In addition, in some materials absorption losses are not uniform across the light spectrum, but are thought to be wavelength sensitive.

Coupling losses

Another form of loss is caused by coupling systems. All couplings (of which more is said later) have loss associated with them. Several different losses of this sort are identified.

Mismatched fiber diameters

This form of loss is caused by coupling a large diameter fiber (D_L) to a small diameter fiber (D_S); i.e., the larger diameter fiber transmits to the

lesser diameter fiber. As a ratio, this loss is expressed by:

$$\text{loss} = -10 \log \left(\frac{D_S}{D_L} \right) \quad (\text{dB}) \quad [2]$$

Numerical aperture (NA) coupling losses

Another form of coupling loss occurs when the numerical apertures of the two fibers are mismatched. If NA_R is the numerical aperture of the receiving fiber, and NA_T that of the transmitting fiber, then the loss is expressed as:

$$\text{loss} = -10 \log \left(\frac{NA_R}{NA_T} \right) \quad (\text{dB}) \quad [3]$$

Fresnel reflection losses

These losses occur at the interface between the optical fiber and air—see Fig. 2a—and are caused by the large change of refractive index at the glass-air barrier. There are actually two losses to consider. First is the loss caused by internal re-

flection from the inner surface of the interface, while the second is caused by reflection from the opposite surface across the air gap in the coupling. Typically, the internal reflection loss is of the order of 4 per cent, while the external reflection is about 8 per cent.

Any kind of reflection in an optical transmission system may be compared to reflections in a radio transmission line (standing-wave ratio). Studying standing waves and related subjects in books on RF systems can yield some understanding of these problems. The amount of reflection in coupled optical systems uses similar arithmetic:

$$\Gamma = \left(\frac{\rho_1 - \rho_2}{\rho_1 + \rho_2} \right)^2 \quad [4]$$

Where:

Γ is the coefficient of reflection;

ρ_1 is the coefficient of reflection for the receiving material;

ρ_2 is the coefficient of reflection for the transmitting material.

Mismatched reflection coefficients are analogous to a mismatch of impedances in a radio transmission system. Whereas the cure in a transmission line system is to use an impedance matching device, in fiber optics, a coupler that matches the 'optical impedances', that is, the coefficients of reflection, is used. Figure 2b shows a coupling between the two ends of fibers (lenses may or may not be used depending on the system). The gel or liquid used to seal the couplings must have a coefficient of reflection similar to that of the fiber. The reflection losses are thereby reduced or even eliminated.

Optical fiber communications systems

A communications system requires an information signal source (e.g., voice, music, digital data, or an analogue voltage representing a physical parameter), a transmitter, a propagation media (in this case optical fibers), a receiver preamplifier, a receiver, and an output. In addition, the transmitter may include any of several different forms of encoder or modulator, and the receiver may contain a decoder or demodulator.

Figure 3 shows two main forms of communications link. The simplex system is shown in Fig. 3a. In this system a single transmitter sends light (information) over the path in only one direction to a receiver set at the other end. The receiver can not reply or otherwise send data back the other way. The simplex system requires only a single transmitter and a single receiver module per channel.

A duplex system (Fig. 3b) is able to simultaneously send data in both directions, allowing both send and receive capability at both ends. The duplex system requires a receiver and a transmitter module at both ends, plus two-way beam splitting Y-couplers at each end.

There is also a half-duplex system known in communications, but this is of little interest here. A half-duplex system can transmit in both directions, but not at the same time.

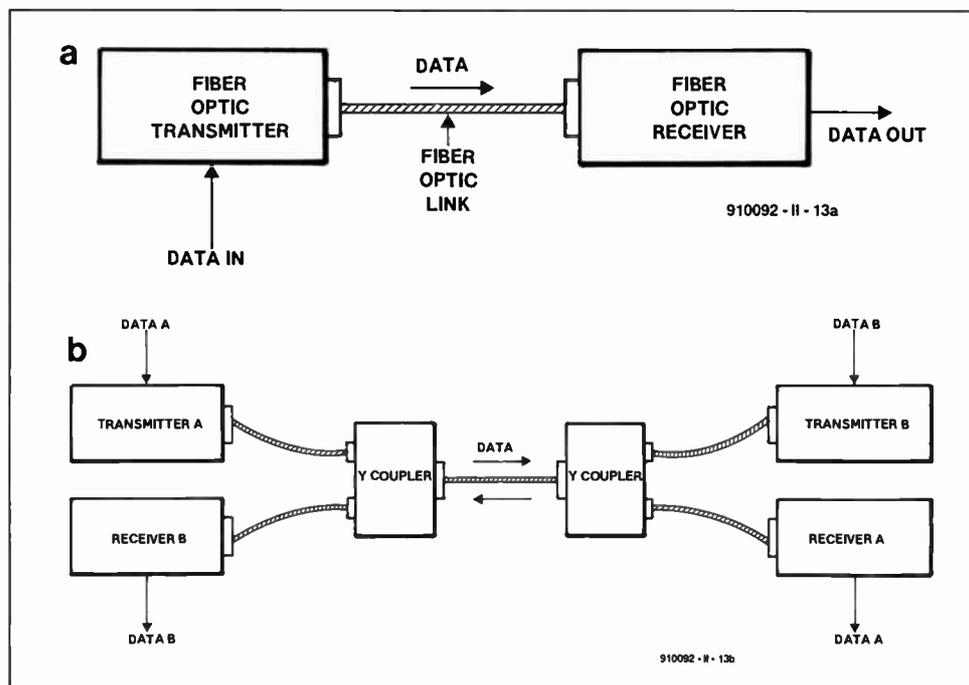


Fig. 3. (a) Simplex communications system; (b) duplex communications system.

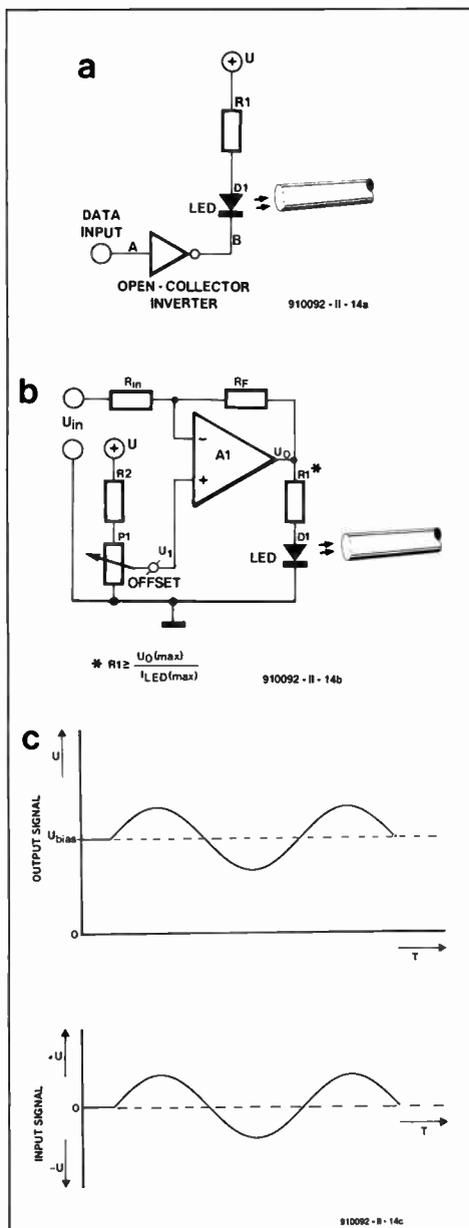


Fig. 4. (a) Digital driver circuit; (b) analogue driver circuit; (c) d.c. offset bias is needed to prevent distortion of the analogue signal.

Receiver amplifier and transmitter driver circuits

Before the fiber optics system is useful for communications, a means must be provided for converting electrical (analogue or digital) signals into light beams. Also necessary is a means for converting the light beams from the optical fibers back into electrical signals. These jobs are done by driver and receiver preamplifier circuits respectively.

Figure 4 shows two possible driver circuits. Both circuits use light emitting diodes (LEDs) as the light source. The circuit in Fig. 4a is useful for digital data communications. The signals are characterized by on/off (high/low or 1/0) states in which the light emitting diode is either on or off, indicating which of the two possible binary digits is required at the moment.

The driver circuit consists of an open-collector digital inverter. These devices obey a very simple rule: if the input (A) is high, the output (B) is low; if the input (A) is low, the output (B) is high. Thus, when the input data signal is high,

point B is low, so the cathode of the LED is grounded. The LED turns on and sends a light beam down the optical fiber line. But when the input data line is low, point B is high, so the LED is ungrounded (and therefore turned off) — no light enters the fiber. The resistor (R₁) is used to limit the current flowing in the LED to a safe value. Its resistance is found from Ohm's law and the maximum allowable LED current:

$$R_1 = \frac{(U+) - 0.7}{I_{max}} \quad [5]$$

An analogue driver circuit suitable for voice and instrumentation signals is shown in Fig. 4b. This circuit is based on an operational amplifier. There are two aspects to this circuit: the signal path and the d.c. offset bias. The latter is needed in order to place the output voltage at a point where the LED lights at about one-half of its maximum brilliance when the input voltage, U_{in}, is zero. That way, negative signals will reduce the LED brightness, but will not turn it off (see Fig. 4c). In other words, biasing avoids clipping of the negative peaks. If the expected signals are monopolar, U₁ is set to barely turn on the LED when the input signal is zero.

The signal U_{in} sees an inverting follower with a gain of R_F/R_{in}, so the total output voltage (accounting for the d.c. bias) is:

$$U_o = \left(\frac{-U_{in} R_F}{R_{in}} \right) + U_1 \left(\frac{R_F}{R_{in}} + 1 \right) \quad [6]$$

Because the network R₂/P1 is a resistor voltage divider, the value of U₁ will vary from 0 volts to a maximum of:

$$U_1 = \frac{(U+) P_1}{R_2 + P_1} \quad [7]$$

Therefore, we may conclude that U_{O(max)} is:

$$U_{O(max)} = \left(\frac{-U_{in} R_F}{R_{in}} \right) + \left(\frac{(U+) P_1}{R_2 + P_1} \right) \left(\frac{R_F}{R_{in}} + 1 \right) \quad [8]$$

Three different receiver preamplifier circuits are shown in Fig. 5: analogue versions are shown in Figs. 5a and 5b, while a digital version is shown in Fig. 5c. The analogue versions of the receiver preamplifiers are based on operational amplifiers. Both analogue receiver preamplifiers use a photodiode as the sensor. These p-n or p-i-n junction diodes produce an output current, I_o, that is proportional to the illumination on the diode junction.

The version shown in Fig. 5a is based on the inverting follower circuit. The diode is connected so that its non-inverting input is grounded, i.e., at zero volts potential, and the diode current is applied to the inverting input. The feedback current (I_F) exactly balances the diode current, so the output voltage will be:

$$U_o = -I_o R_F \quad [9]$$

The non-inverting follower version shown in Fig. 5b uses the diode current to produce a voltage drop (U₁) across a load resistance, R_L. The output voltage for this circuit is:

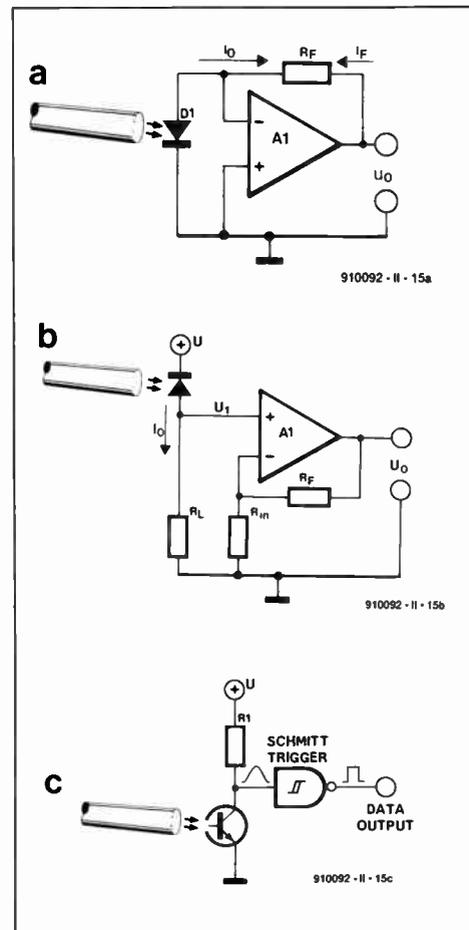


Fig. 5. (a) Inverting follower receiver; (b) non-inverting follower receiver; (c) digital receiver based on Schmitt trigger.

$$U_o = I_o R_L \left(\frac{R_F}{R_{in}} + 1 \right) \quad [10]$$

Both analogue circuits will respond to digital circuits, but they are not at their best for that type of signal. Digital signals will have to be reconstructed because of sloppiness caused by dispersion. A better circuit is that of Fig. 5c. In this circuit, the sensor is a phototransistor connected in the common emitter configuration. When light falls on the base region, the transistor conducts, causing its collector to be at a potential only a few tenths of a volt above ground potential. Conversely, when no light falls on the base, the collector of the transistor is at a potential close to U₊, the power supply potential.

The clean-up action occurs in the following stage: a Schmitt trigger. The output of such a device will snap high when the input voltage exceeds a certain minimum threshold, and remains high until the input voltage drops below another threshold (these thresholds are not equal). Thus, the output of the Schmitt trigger is a clean digital signal, while the sensed signal is a lot more sloppy.

Conclusion

Fibre optics can be used by experimenters and small users: even Radio Shack (Tandy) has fiber optics kits available. Other suppliers can be found by perusing the ads of this magazine. Edmund Scientific (USA) has a particularly nice selection.

AM BROADCAST RECEIVER

In these days of stereo FM, medium-wave AM reception is often viewed with contempt, and the quality of a sophisticated hi-fi stereo tuner is solely judged by the specifications of the FM section, with the AM section taken for granted. No wonder that the AM reception of these hi-fi tuners is no better than that of any cheap portable radio.

by R. Shankar

THIS article describes a top-of-the-range AM receiver with the following features:

- High quality audio output with a -6 dB bandwidth of 12 Hz to 4.5 kHz, and a total harmonic distortion of only 0.5%.
- High input signal range of nearly 60 dB with virtually no change in the audio output level.
- A phase-locked loop (PLL) which keeps the intermediate frequency (IF) at exactly 455 kHz even when the receiver is slightly mistuned to a station. Since a small difference between the tuning of

the antenna and that of the oscillator sections is inevitable in any receiver, this relaxation can be considered as a kind of fine tuning. Also, oscillator drift has no effect on the IF.

- An extremely steep IF cut-off characteristic thanks to a communications-grade ceramic filter.

Principle of operation

Basically a superheterodyne type, the proposed receiver is considerably more sophis-

ticated than a good many hi-fi stereo tuners. A few salient differences are listed below.

AFC

As mentioned before, the local oscillator frequency is adjusted by a PLL so that the IF is held at exactly 455 kHz. This AFC (automatic frequency control) function may be turned off by a switch, in which case the local oscillator runs free, functioning just as in most other receivers. A certain level of carrier has to be present for the AFC to function. Otherwise, it is automatically switched off to en-

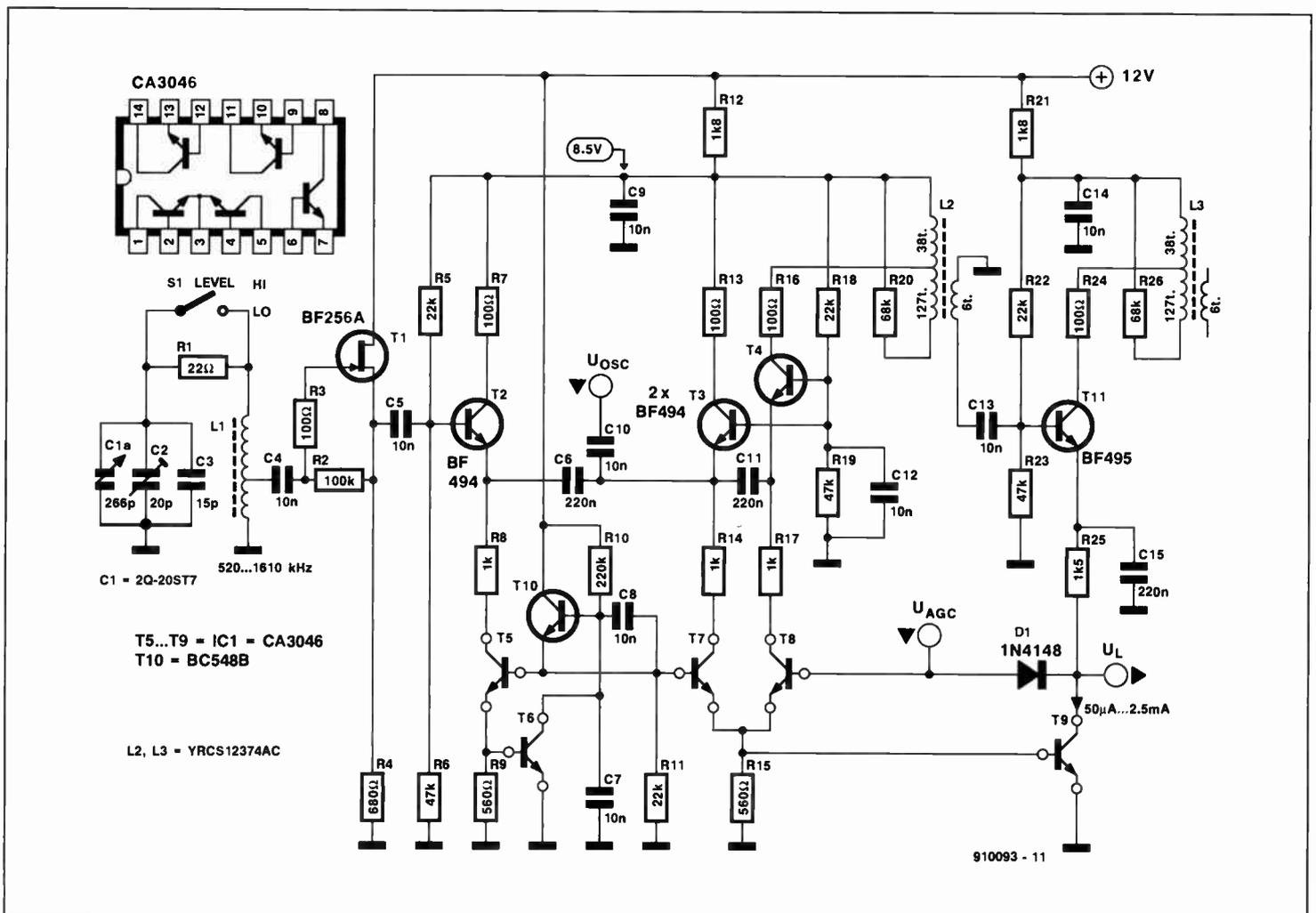


Fig. 1. Front end of the AM broadcast receiver.

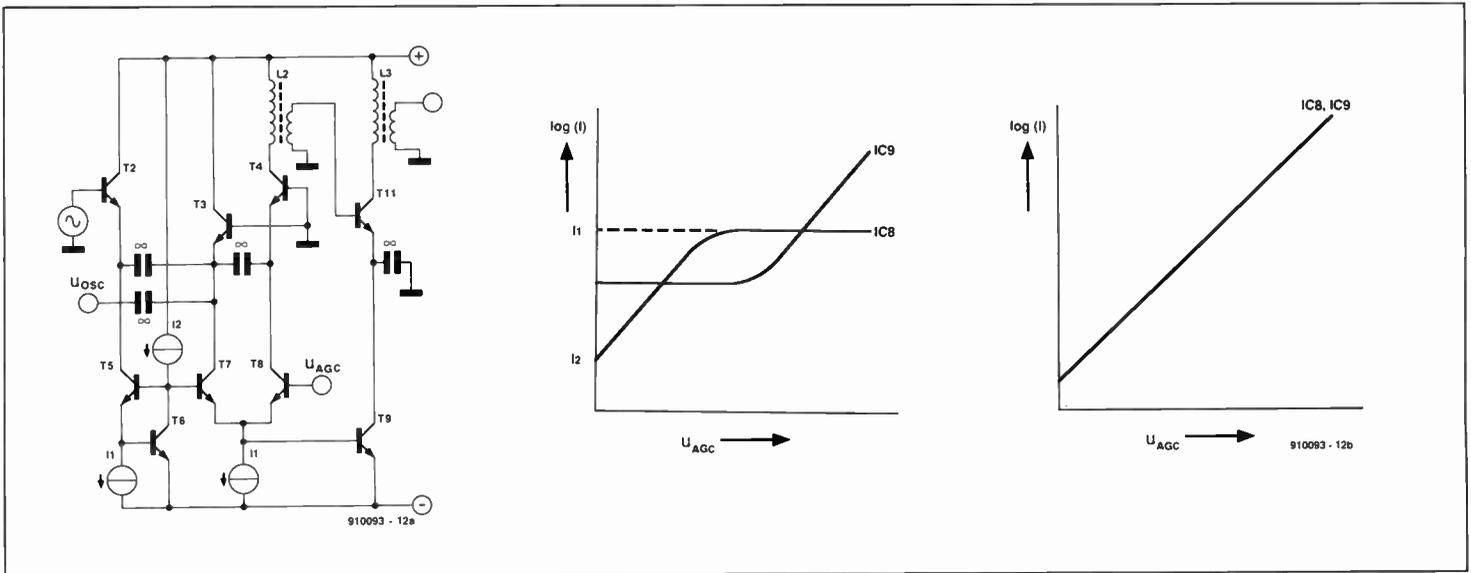


Fig. 2. Basic schematic and response of the of the automatic gain control (AGC).

able tuning to a different station.

AGC

Most AM receivers use a single transistor for the AGC (automatic gain control) function. By contrast, this receiver uses an elaborate two-stage AGC circuit to obtain a level control range of nearly 60 dB without overloading or excessive noise.

Active detector

Whereas most AM receivers use a single point-contact diode for the detector, the

present design is based on an active detector stage, which has a distortion of less than 0.5% rather than the more usual 2% introduced by a diode.

Design background

The total circuit, excluding the power supply, uses 6 standard ICs and 15 transistors. Two ceramic filters are used. It was decided to have only two IF stages, but in the end four were found necessary. The reason is as follows: in order to keep the audio out-

put as flat as possible up to 4.5 kHz, the Q factor of each IF stage has to be reduced to a maximum of 25 by loading it. Inevitably, reducing the Q reduces the gain. Further gain reduction is caused by the insertion loss of the ceramic filter. So, in order to obtain a high input sensitivity (27 μV for 20 dB signal-to-noise ratio), four IF stages were found necessary.

For 4.5 kHz sidebands, the relative gain roll-off of the IF stages alone (including the ceramic filter) amounts to about 4 dB. The roll-off of the antenna tuned circuit is an-

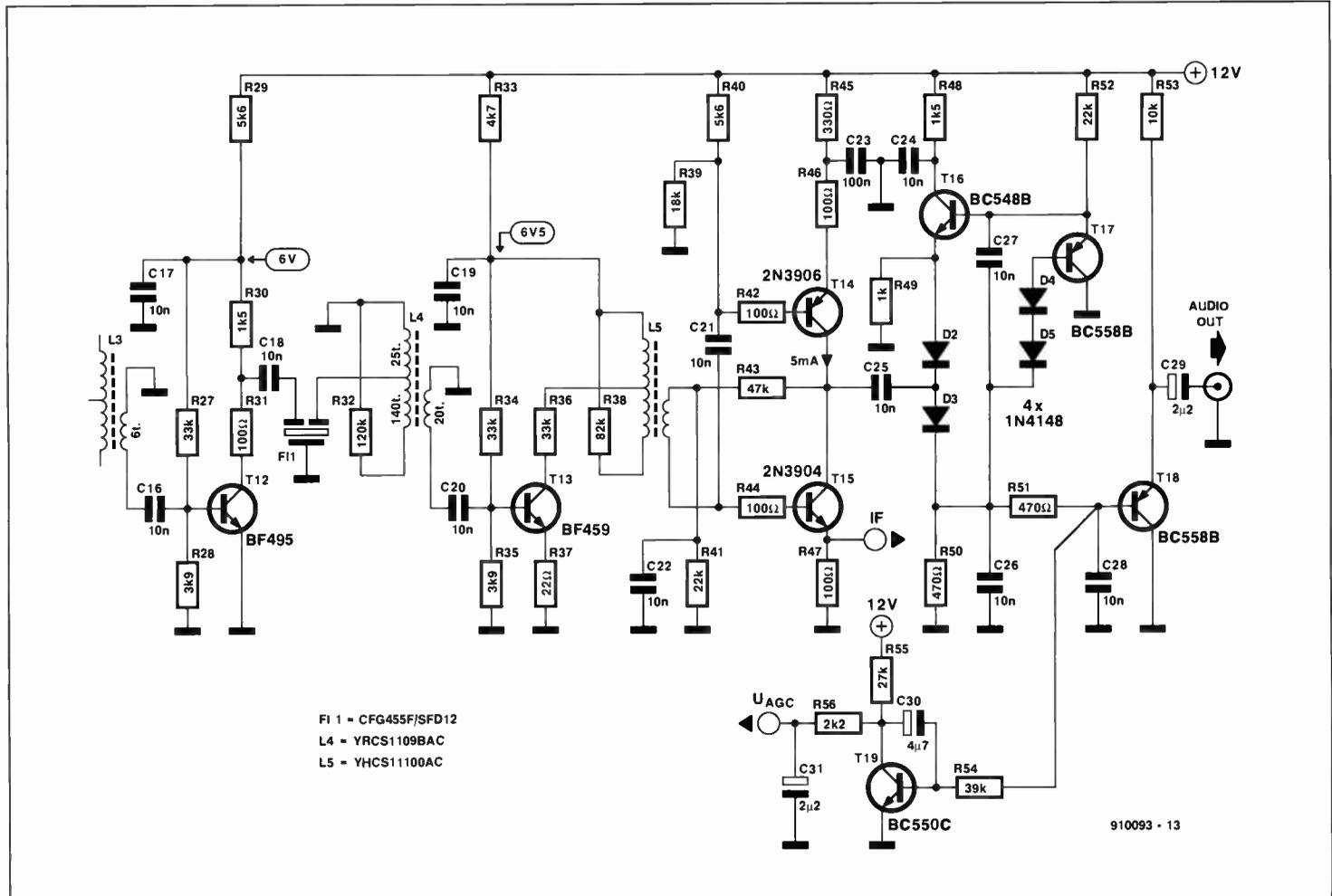


Fig. 3. IF amplifier and demodulator.

other 2 dB. This means that the total audio attenuation at 4.5 kHz is 6 dB, which is considered good for an AM receiver.

An important point must be made about the IFTs (intermediate frequency transformers) used in this circuit. These are basically 468-kHz types with built-in 180-pF capacitors. Though these IFTs can be tuned to 455 kHz, the stability suffers. For this reason, every IFT is fitted with an external 10-pF capacitor across the primary winding. Note that these 10-pF capacitors are not shown in the circuit diagram. The IFTs have not been used in the order suggested by the manufacturer, Toko. The reason that these particular 468-kHz types were selected is that there were no good 455-kHz types available from the author's supplier, Cirkit. Since the signal levels and impedances in the IF amplifier have been painstakingly ascertained, no attempts should be made to use types of IFTs other than the ones indicated, or the purpose of this project is defeated.

As regards distortion in amplifiers based on bipolar transistors, odd-order harmonic distortion is negligible for base-emitter voltage swings of less than 5 mV. At 3 mV, for example, the third-order harmonic distortion is only 0.06%. The second-order harmonic distortion, however, is nearly 3%. Fortunately, even-order products do not matter in the IF stages as they fall outside the pass-band. The upshot is that the simple single-ended common-emitter stage is perfectly acceptable. Not so in the mixer stage, however, where even-order intermodulation products are troublesome when the receiver is tuned to about 910 kHz (twice the IF), because they coincide with the image frequency. As the second-order products are considerable even for small input swings, a differential amplifier should be used for the mixer.

Contrary to popular belief, bipolar transistors are better suited to AGC circuits than FETs or MOSFETs. There are two reasons for this. First, the linearity of a FET or MOSFET deteriorates rapidly when its transconductance is made smaller than a tenth of its maximum value. Interestingly, precisely that condition would arise when a strong signal is received. Second, the exponential characteristic of a bipolar transistor results in an AGC loop gain which is independent of the carrier strength. For a FET, it can vary by a factor of 100, giving rise to wildly varying loop response times and lower cut-off frequencies.

The circuit

Input stage

Figure 1 shows the input stage of the receiver, which comprises the mixer, the first IF amplifier, and the AGC. The antenna tuned circuit comprises L_1 , C_{1a} , C_2 and C_3 , with the ferrite rod, L_1 , tapped at a fourth from earth. When the signal strength is high, a resistor can be switched in series with the tuned circuit for two purposes. First, it increases the bandwidth so that the high-frequency response is improved. Second, it

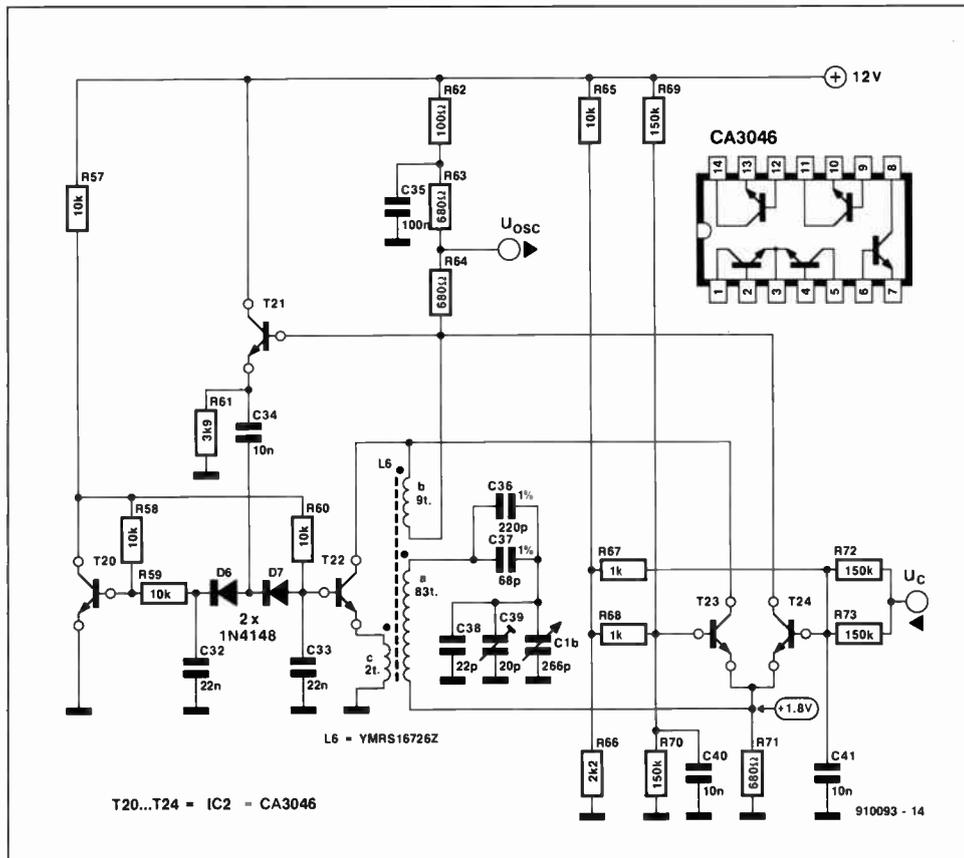


Fig. 4. Local oscillator.

decreases the signal level, and prevents distortion.

Transistor T_1 is a buffer that prevents the mixer stage from loading the tuned circuit, especially at the higher end of the band. T_1 operates at $I_d = I_{dss}$, which results in maximum gain and linearity.

The mixer stage is formed by T_2 , T_3 and

T_4 , with the local oscillator signal injected into their emitters. The mixer stage also functions as a part of the AGC. At low input levels, T_4 conducts fully so that the maximum possible gain of the mixer stage is achieved. The operation of the AGC now depends mainly on the current through T_{11} . When the input signal is fairly strong, T_3 steals some of

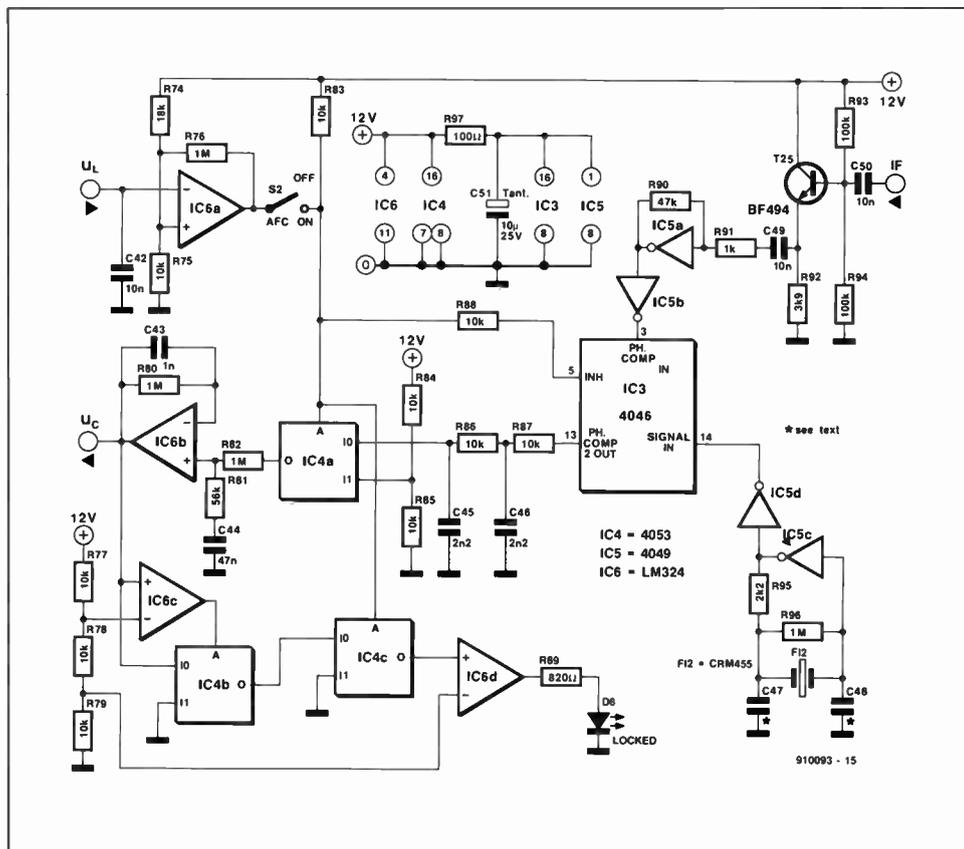


Fig. 5. Phase-locked loop.

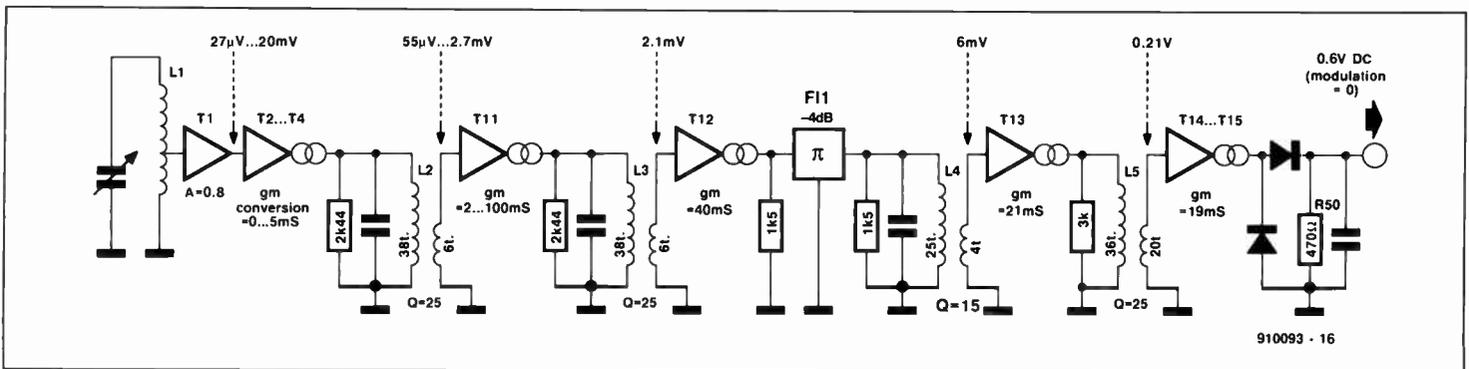


Fig. 6. Overview of crucial signal levels, quality factors and transconductance requirements at various points in the receiver.

the current through T4, so that the signal at the base is limited to about 3 mV. At still higher input levels, T4 starts to conduct less while T11 has a flat gain. Figure 2 shows a simplified model of the AGC stage. Here, current sources have been used instead of transistors. Currents I_1 and I_2 are 1 mA and 50 μ A respectively. It can be shown that the total gain varies purely exponentially with the control voltage.

The two-stage AGC ensures that the first IF stage can not be overloaded by strong signals. This means that the signal handling capability of the receiver is increased by a factor equal to the mixer stage gain.

Transistor T10 is included because the base currents of T5 and T7 are comparable to the collector current of T6. Compensation is achieved with C8 and C7 which also ensure an AC path from the bases of T5 and T7 to ground. To improve stability, resistors R8, R14 and R17 provide RF isolation for IC1. The 100- Ω resistors likewise prevent spurious VHF oscillations of the transistors.

IF amplifier and AM detector

The circuit diagram of the second, third and fourth IF stage, and the active detector, is shown in Fig. 3. The input and output of the ceramic filter are matched to 1.5 k Ω .

The active AM detector is formed by T14-T17. T14 and T15 form a voltage-to-current converter with the collectors of the transistors at a relatively high impedance. A push-pull rectifier based on D2-D3 is used. The rectified RF current that flows through D3 develops a voltage across R50, which is smoothed by C26. The circuit around T16, T17, D4 and D5 provides a quiescent current of about 1 μ A through D2 and D3 to keep the voltage swing at their junction to a minimum. The detected audio signal across R50 is filtered by R51 and C28, and buffered by T18 before it is taken to the output of the receiver (to reduce traces of IF to an absolute minimum, one more ladder section consisting of a 470- Ω resistor and a 10-nF capacitor can be added before T18).

The AGC feedback is also taken from this point. The instantaneous carrier level is integrated by T19, and fed to the base of T8. Excluding T19, the gain of the AGC from the base of T8 to the base of T18 is V_{be}/V_i , or about 23. The lower cut-off frequency of the audio signal is $23/(2\pi R54C30)$, or 20 Hz. As mentioned earlier, this cut-off frequency is virtually independent of the carrier strength.

Local oscillator

Figure 4 shows the local oscillator based on a single CA3046 transistor array. The oscillator is basically a Hartley type, although a portion of the current through L6a is also fed to L6b by T23. This causes the effective inductance of L6 to change by a small amount. The ratio of the currents through T23 and T24 varies between 3:1 and 1:3, corresponding to V_c values of 4 V and 8 V respectively. The total frequency variation achieved is about 2.5%. At the lowest oscillator frequency, 975 kHz, the variation is about 25 kHz — more than enough to correct tracking deviations between the antenna and oscillator sections. When the AFC is disabled, V_c is held at half the supply voltage to minimize frequency drift. In this case, T23 and T24 conduct equally.

T22 is the positive feedback transistor whose d.c. setting determines the strength of the oscillations. T20 and T21 are used to control the amplitude to about 1 mA (0.6/R64) by reducing the d.c. voltage at the base of T22 when D6 and D7 start conducting.

For optimum tracking of the antenna and oscillator sections, the parallel combination of C36 and C37 should be equal to 0.978 times the total antenna tuning capacitance at the lowest frequency. This works out at 285 pF. Capacitors C36 and C37 should be 1% types. When C2 and C39, the trimmers associated with the tuning capacitor, are properly adjusted, a worst-case deviation of smaller than 5.5 kHz is possible.

PLL section

The zero crossings of the IF output signal are shaped by N1 and N2 and fed to one phase comparator input of the 4046 PLL. The other


input is supplied with the reference frequency of 455 kHz from a ceramic resonator oscillator based on N3. The output of the phase comparator is fed to a ladder filter to remove traces of the product $IF/4$. When the AFC is switched on, the 'A' inputs of IC4a and IC4c are made logic 0, provided a sufficient carrier strength exists (for this, the current through T11 has to be smaller than 1 mA). The output of the PLL is fed to the loop filter formed by R81, R82 and C44. The AGC time constant is about 0.05 s while the damping factor is about unity.

If V_c is between 4 V and 8 V when the AFC is switched on, D8 lights to indicate that the PLL is locked. If the AFC is off, or if the carrier is too weak, or if V_c exceeds its range, D8 is off. When the AFC is not on, IC4a selects the resistive divider, and V_c becomes 6 V. At the same time, IC3 is disabled.

Signal levels

Figure 6 shows the signal levels at various points in the RF-IF chain. For the IFTs with 190 pF total capacitance, the parallel loading corresponding to a Q factor of 25 is 46 k Ω . Since the IFTs have an inherent Q of 90, additional loading is necessary to reduce the Q factor to this value. With the transistor types used, the base-emitter swings of all stages, except the mixer, have been kept in the 2 to 3 mV range as this is the best compromise between noise and distortion. Note, however, that even the mixer can handle up to 13 mV of RF, and still produce less than 1% distortion. At higher signal levels, R1 may be switched on. ■

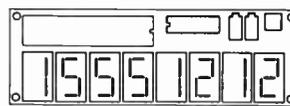HEAR THE TONES...SEE THE NUMBERS! TOUCH-TONE DECODER/DISPLAY AND ASCII CONVERSION BOARD



- *EIGHT DIGIT DISPLAY
- *32 CHARACTER BUFFER
- *ASCII SERIAL OUTPUT

Model TDD-8 decodes and displays all 16 DTMF digits and provides an ASCII serial output. Digits are displayed on eight LED's. 32 character memory can be scrolled. It will accept almost any audio source such as a tape recorder, telephone answering machine, scanner, etc. Perfect for remote computer data entry using a telephone keypad. Serial output can be connected to your computer. IBM compatible software included for displaying, storing/printing time, date and number for automatic logging. **Ideal for automatically logging your auto-patch traffic!**

| | | |
|----------------------------------|---------|----------------------|
| TDD-8 DTMF DECODER/DISPLAY/ASCII | \$99.00 | MoTron Electronics |
| CAB-1 AUDIO & COMPUTER CABLES | \$20.00 | 310 Garfield St., #4 |
| PS-12 110VAC TO 12VDC POWER PACK | \$10.00 | Eugene, OR 97402 |
| add \$5 S/H - VISA/MC ACCEPTED | | |

TEL: 800-338-9058 503-687-2118 FAX: 503-687-2492

(Touch-Tone is a trademark of AT&T)

THE DIGITAL COMPACT CASSETTE

WILL IT SUCCEED?

based on an original article by P. van Willenswaard

Just when consumers were getting reconciled with the idea that digital audio tape (DAT) is virtually dead and started to buy more CDs, the two DAT protagonists, Sony and Philips, decided to confuse the market afresh by each announcing another new system: the Mini Disc (MD) and the Digital Compact Cassette (DCC) respectively. We briefly explain the reasons behind these new systems and have a closer look at the digital compact cassette technology.

WITH the demise of the digital audio tape (DAT) system—killed by the music industry which believed (probably rightly) that a system that enables the making of perfect copies from copies would cost them thousands of millions of dollars—audio equipment manufacturers began to reformulate their development programmes with the aim of getting a larger slice of tomorrow's market.

They found that cassettes are bought primarily for portable or mobile equipment; CDs and LPs almost exclusively for use at home. Moreover, three times as many cassettes (recorded and blank) as CDs and long-playing records (LPs) are sold world-wide. Because of their higher prices, CDs and LPs bring in a much larger revenue, of course. See Fig 1. This schism is further illustrated by considering the apportioning of tape decks over the various types of audio equipment. About 12 per cent are used in hi-fi separates or integrated systems; the remainder, that is, almost 90 per cent, are used in car radio/cassette players, walkman equipment and other portable sets—see Fig. 2.

Annual sales of compact cassettes amount to a staggering 2,600 million

The realization that the bulk of the demand for audio equipment is for portable/mobile units form the basis of Sony's and Philips' development programs.

Sony, still smarting from the collapse of the DAT market on which they had pinned much hope for the future, decided to get away from cassettes for the time being and have another look at their tremendously successful CD system (CDs today account for about half the £13,000 million – \$22,000 million – world market for recorded music).

Knowing that CDs cannot compete with the cassette in the popular mobile/portable

markets, Sony recently unveiled Mini Disc (MD). The MD is considerably smaller than the Compact Disc, but it has the tremendous advantage over its big brother that it is recordable and erasable. Moreover, the system is immune to shocks and jolts, which means that it can be used on the move, that is, in portable and mobile (car) units, with impunity.



Philips has gone back to its earlier invention, the compact cassette, but now in digital format: the Digital Compact Cassette (DCC) system. Since a large part of the 2,600 million cassettes sold every year are used in fairly inexpensive equipment, Philips reasoned that, to stand a chance of cornering a sizeable part of that market, they had to offer something that works with relative inexpensive tape decks and tape. Even better if the new system would also accept standard compact cassettes.

Both systems are promised (threatened?) to be on the market in late 1992. The success, or otherwise, of the new systems is in the hands of confused consumers and a cautious music industry which will insist that both systems are fitted with appropriate circuitry that will prevent copying from copies. It is still their, and many others', opinion that home taping is nothing but theft.

DCC requirements

Recording 16-bit audio samples at a rate of 44 100 times a second in two channels requires 1.4 Mb/s; if space for encoding and error correction is included, that figure should be doubled. This kind of high-density recording is impossible on cheap tape. Ways have, therefore, to be found to make recording with fewer data possible.

At the same time, the choice of inexpensive, slightly modified compact cassette tape decks means a considerable reduction in development cost and time. The most frequently heard complaint about the current cassette system is the varying quality of sound reproduction: there is loss of high frequencies

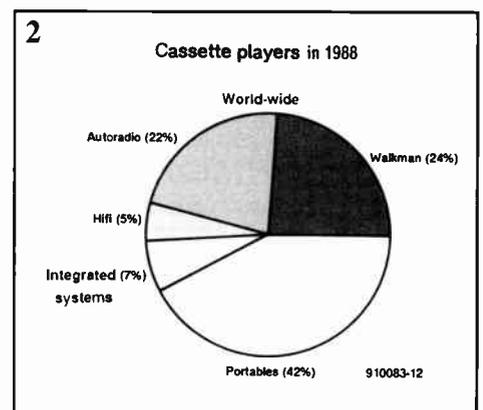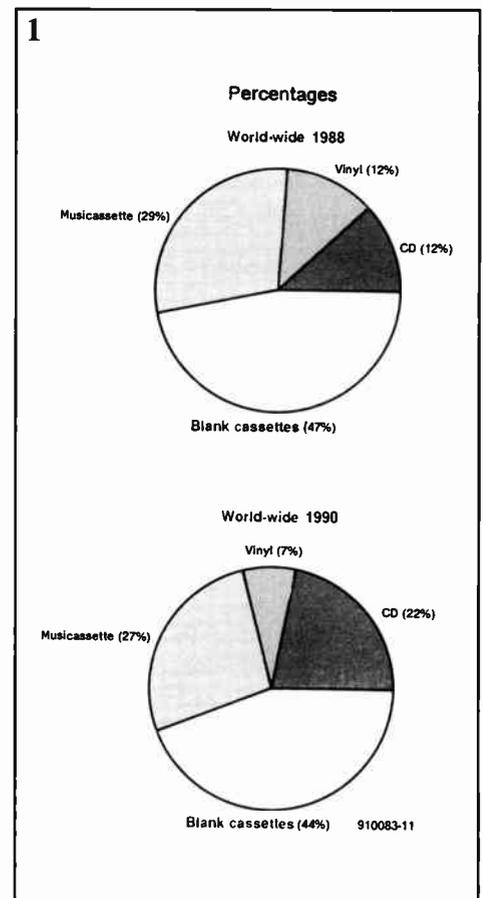

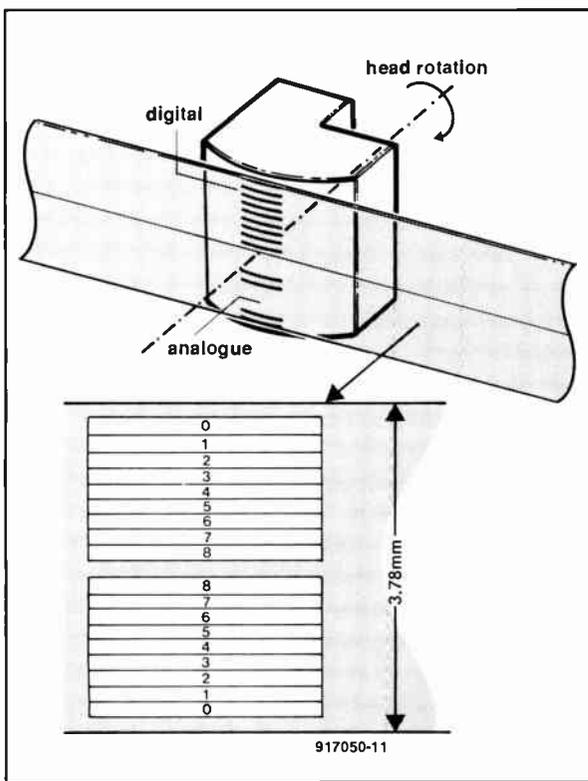


Fig. 3. Division of the tape into nine digital tracks; at the end of the tape, head and direction reverse and the lower half is written to or read from. The head also has two slits for the playing of analogue recordings.

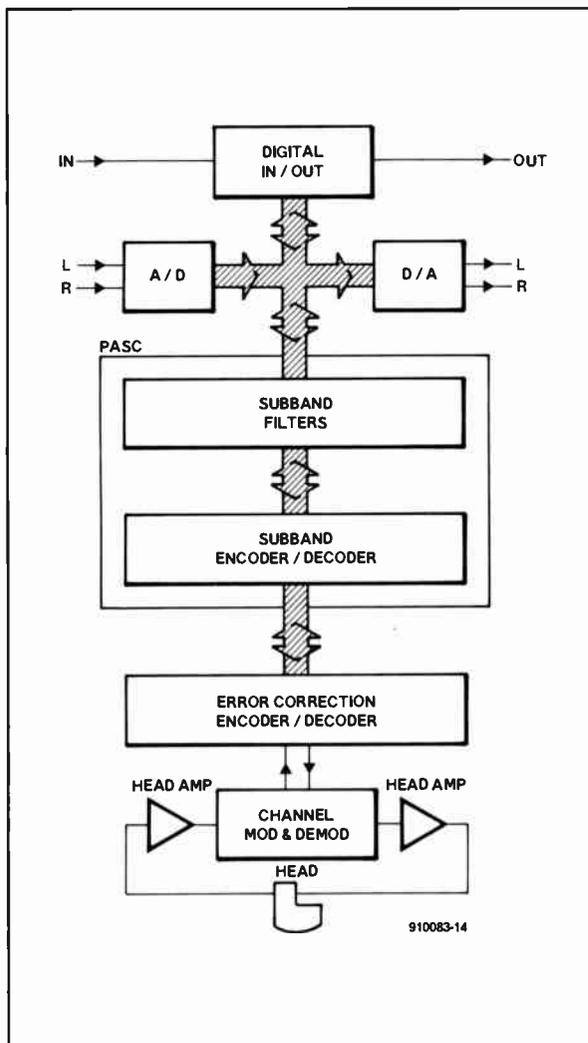


Fig. 4. Block schematic of a DCC player.

owing to misaligned or dirty heads; the sound quality is proportional to the quality of the tape transport (causing fading at high frequencies and wow and flutter) and to minor damage of the tape.

A digital recording, if adequate error correction is provided, is fundamentally immune to such imperfections. A digital compact cassette would, therefore, in many instances give an appreciable improvement in sound reproduction, which would make it immediately attractive to large numbers of potential users. This presupposes, of course, that production costs are low enough to make the sales price acceptable at the lower end of the market. This is quite feasible, because the tape decks of the DCC player are not very different from those of current cassette players, while the cost of the electronics would become low enough if manufacturing quantities were large. There are an estimated 200 million cassette players in the world; even replacement of 5–10 per cent of these would ensure success.

Reverting to the question of audio quality: how is good quality to be ensured if the audio signal is stored digitally in a much smaller space than 1.4 Mb/s? The tape width of a compact cassette is 3.78 mm. The vertical tolerance of transporting the tape across the head is about 0.05 mm. This means that the DCC remains within that tolerance if half the tape width is divided into nine tracks, each 185 μm wide, of which 70 μm is used for reading (play-back) and the remainder for writing (recording)—see Fig. 3. Eight of the nine tracks are allocated to audio; the ninth, to system information.

It has been found that at the standard tape speed of cassette players (4.76 cm/s), about 100 kb/s per track can be saved reliably. There is thus about 800 kb/s space for the audio signal; this has been standardized at 768 kb/s. Half of that, however, is used for the Reed-Solomon interleaving (in aid of effective error correction), synchronization bits, and a 10:8 modulation mode, which means that only 384 kb/s remain for the audio information proper. That is about a quarter of the earlier established 1.4 Mb/s; in other words, at a sampling frequency of 44.1 kHz, there would only be space for a four-bit amplitude description per channel. That is, of course, quite unacceptable. Philips has, therefore,

developed precision adaptive sub-band coding—PASC.

Precision adaptive sub-band coding

PASC is not, as one might suppose, a highly developed form of data compression as used in computers or data links. Whereas pulse-code modulation (PCM) systems give a total and perfect (within the constraints of 16-bit linear encoding) digital representation of the sound that reaches a microphone, PASC uses a perceptive approach: it takes human hearing as reference. PASC analyses the signal and computes what may be audible and what not, and stores only what is in a very efficient notation. Subsequently, the resulting digital information is reorganized in such a manner that the available space is reallocated optimally.

Only what may be audible is stored and encoded

The way a signal is processed in DCC is shown schematically in Fig. 4. First, the a.f. range is divided into 32 sub-bands: the reason for this will become clear later. The division is linear, not logarithmic as in human hearing: each sub-band is, therefore, about 600 Hz wide. In digital signal processing (DSP), it has been possible for some time to divide the a.f. band into sub-ranges that can later be recombined without any errors or deterioration as far as frequency and phase are concerned. Philips is confident of being able to put this entire process on to one chip in the near future.

Threshold and masking of hearing

The next step occurs in every sub-band. The minimum intensity a sound requires in order to be heard depends on its frequency—see Fig. 5. This means that in each sub-band a threshold has to be determined; any information below that limit is ignored.

Another aspect is masking: it is well known that there are circumstances in which a strong signal will mask, that is, make inaudible, a weaker signal at a frequency not far removed from its own—see Fig. 6. When someone whispers something to you in a quiet street, you can understand it perfectly. If, however, just then a noisy lorry passes by, you have to be a lip-reader to understand.

Another form of masking occurs in time. If a weak sound is preceded a few milliseconds earlier by a strong sound, we cannot hear the weak sound. Even the opposite can happen: a weak sound emitted a few milliseconds before a strong one may, in certain circumstances, mask the strong sound. It all depends on the difference in intensity and the separation in time.

The PASC processor analyses the signal in each of the sub-bands and constantly adapts

the various thresholds to the actual signal. The thresholds are, therefore, not static, but follow the signal content. This results in higher efficiency, because only the part of the signal above the threshold, i.e., that which is audible, is stored and encoded.

Mantissa and index

The amplitude of the part of the signal that remains above the thresholds must be quantized. Whereas compact disc technology uses 16-bit linear quantization, PASC uses a floating-point technique. This works in a manner similar to the presentation of a large number on a pocket calculator: with a mantissa and an index (exponent). The mantissa of most pocket calculators is normally eight digits long and represents the value of the number. This is followed by the exponent, normally two digits (positive or negative), which weights the numbers.

In PASC, the mantissa is 15 bits long, but the processor may decide to work with a shorter one if not all the 15 bits appear necessary. This may happen, for instance, when the signal is just above the noise level or threshold of hearing. The mantissa thus determines the resolution of the system, while the index shifts the area over which the mantissa operates up and down the dynamic range.

The index is not linear over the entire dynamic range, but reflects the non-linear action of the ear. After all, the ear does not differentiate between sounds at 118 dB and 120 dB: both are too loud. At the other end of the range, however, 2 dB steps would be much too coarse, because the ear is highly sensitive to subtle differences when listening to weak sounds. Defining the amplitude in this flexible manner gives a further increase in efficiency compared with the linear encoding used in PCM.

If PASC fulfils its early promise, it will mean a revolution in digital audio

The maximum length of the mantissa of 15 bits is reflected in DCC by what Philips calls the (theoretical) THD+N figure of -92 dB, which is 1 bit, or 6 dB, above the -98 dB of CD technology. But that technology is not flexible, so that the THD+N figure is always referred to the same absolute level: a -20 dB signal will, therefore, have its THD+N figure only 78 dB lower. Because of the floating-point amplitude description, in DCC the THD+N distance of 92 dB will, however, be maintained until the noise threshold of the system is reached. Philips states a dynamic range of -108 dB, which is 10 dB better than that of CD.

All internal calculations are carried out with 24-bit wide words. The associated noise level is -146 dB, but Philips claims that the resolution made possible by the mantissa and index system will handsomely exceed that level. The real problems arise not in this

part of the system, but in the analogue-to-digital (A-D) converter that needs to precede the PASC. The crux of the matter is that even the best state-of-the-art converters cannot provide more than 18-19 bits of reliable a.f. information.

Reallocation

One of the nicer properties of music is that the waveform varies constantly. This means that not all available space in the 32 sub-bands is in use all the time: that in a number of them will, in fact, be empty (above the threshold, that is). A certain space is reserved in the ultimate code that is written on to the tape for each of the sub-bands. A sub-band that is temporarily partially, or wholly, empty would not be very efficient. When the recording code is being composed, PASC moves information from full sub-bands to partially, or wholly, empty ones (and provides it with an address code to ensure that during play-back the signal is reconstructed correctly). The process of moving the information is called reallocation.

The gain in efficiency resulting from this method of signal processing is surprising: from 16 bits per channel for linear PCM to an average 4 bits per channel for PASC. This means a gain of a factor 4 in data content. PASC does not work with two channels, but with a stereo signal (the correct encoding of stereo signals proved to be quite difficult; stability gave particular problems). Just as there is no sharp division between left-hand and right-hand, there is none between one sample of the signal and the next: PASC works with small groups of samples. On average, the code for each stereo sample contains eight bits of space that are written on to the tape. These are not bits of waveform: the 8-bit code generated by PASC is much more intelligent than that. The 8-bit words should be considered as pieces of a continuously developing jigsaw puzzle, which are resolved by the decoder during playback.

The decoder need not be high-tech, because the intelligence is stored in the code itself, since this contains all necessary keys for encoding and reallocation. In other words, the keys have become part of the 8-bit codes.

Storing the keys in ROM near the decoder would seriously limit the system (perhaps even make it unworkable), because each sound is different from others and thus requires its own unique PASC code. The keys in the 8-bit code control the operation of the decoder: what is the reallocation information; which mantissa and index were used; and so on. The code is the brain: the decoder only carries out orders.

The decoder is, therefore, suitable not only for working with DCC codes, but with all codes within the same family, such as Digital

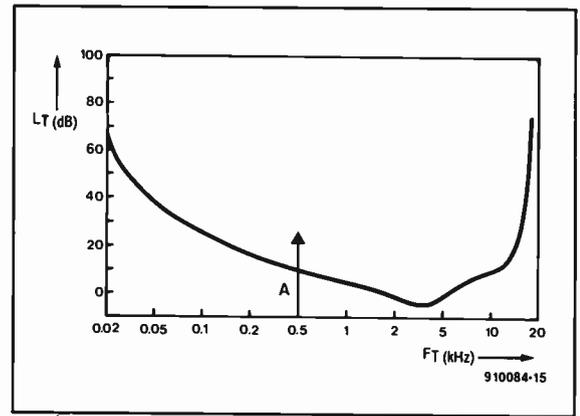


Fig. 5. Characteristic to indicate the threshold of hearing, both as regards loudness L (vertical scale) and frequency F (horizontal scale). Sounds below the curve can be omitted. Sound A is just perceptible.

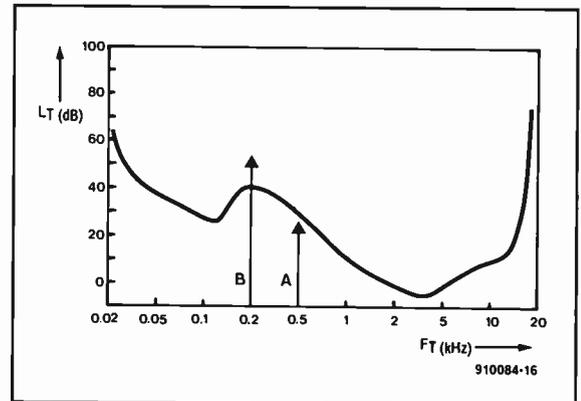


Fig. 6. Strong signal B raises the threshold of hearing locally, as it were, so that sound A is no longer audible: B masks A.

Audio Broadcasting (DAB) codes (in the framework of the European Eureka project, Philips partakes in DAB experiments), or even simple 2-bit codes of limited audio quality. Moreover, the code may change from one to another instantly because the decoder does not have to switch over.

Breakthrough in digital audio

If PASC fulfils its promise, it will mean a revolution in digital audio. Storage space for the large amount of data generated by digital audio has always been a problem. Until now, storage with simple means, a longer playback time, a substantially higher sampling rate than the current 16 bits of amplitude, and so on, were not possible in practice. It may also well be, because a signal after being processed in PASC is technically less complex, that the analogue electronics in the play-back chain can become less complex.

As far as the sound quality of DCC is concerned, it is too early to make a definitive judgement. However, first impressions gained during a recent demonstration of the system to a number of international journalists were good. When amplifiers of reasonable (not high-end) quality were used, there was no perceptible difference between a CD and a DCC.

APPLICATION NOTES

The contents of this article are based on information obtained from manufacturers in the electrical and electronics industry and do not imply practical experience by *Elektor Electronics* or its consultants.

SWITCH-MODE VOLTAGE REGULATORS LM2575/LM2577 (National Semiconductor)

THE recently introduced LM2575 and LM2577 switch-mode voltage regulators in the Simple Switcher series from National Semiconductor have a wide voltage range, and are remarkably easy to get going with only a handful of external components. The devices in the LM2575 series are step-down regulators, and those in the LM2577 series step-up regulators. Offering an efficiency of over 80%, these ICs are a good alternative to the ubiquitous 1-A regulators in the 78xx series.

The new step-up and step-down converters are based on switch-mode voltage regulation, which gives them a higher efficiency (70-90%) than linear voltage regulators (30-60%). By virtue of the on-chip power stages, the external component count remains low — basically, only a choke, a power diode and a few decoupling capacitors are required. The adjustable regulators in addition require a voltage divider that determines the output voltage. All devices in the LM2575 and the LM2577 series are available in a 5-pin TO220 case (LM257xT), and a 4-pin TO3 case (LM257xK). The case of these devices is always connected to ground. Fixed voltage as well as variable voltage devices are available — see Table 1. The LM1575 and LM1577 should be used in heavy-duty applications where an extended temperature range (T_j up to 150°C) is required. The main technical data of the regulator family are summarized in Table 2.

Since the switch-mode regulators are based on a fixed oscillator frequency with a variable duty factor, they do not require the usual minimum load current to operate correctly. The ICs feature an internal thermal overload protection which is actuated at $T_j=125^\circ\text{C}$, and an output current limiting circuit. A further advantage of these new ICs is that they are inexpensive and uncritical of the choke type used.

Step-down regulator LM2575

The operating principle of the so-called buck (step-down) regulator is illustrated in Fig. 1. Switches S1 and S2 close in alternate fashion at a certain rate. When S1 is closed, the self-inductance of the charge choke, L , causes a

Table 1. Overview of devices in LM2575/LM2577 Simple Switcher family

| Type | Output voltage | TO220 case | TO3 case |
|-----------|----------------|-------------|-------------|
| Step-down | 5 V | LM2575T-5.0 | LM2575K-5.0 |
| | 12 V | LM2575T-12 | LM2575K-12 |
| | 15 V | LM2575T-15 | LM2575K-15 |
| | adjustable | LM2575T-ADJ | LM2575K-ADJ |
| Step-up | 12 V | LM2577T-12 | LM2577K-12 |
| | 15 V | LM2577T-15 | LM2577K-15 |
| | adjustable | LM2577T-ADJ | LM2577K-ADJ |

slowly rising current to flow. This current causes energy to be stored in the form of a magnetic field in the core of the choke. When the switches toggle (S1 is opened, and S2 is closed), the self-inductance first causes a current I_L to be fed through L . As a result, the magnetic energy stored in the choke, and with it I_L , decreases gradually. This process is repeated as S1 and S2 close and open alternately. Capacitor C smooths the output current, I_{OUT} , because it is charged as I_L rises, and discharged by the load as I_L drops again.

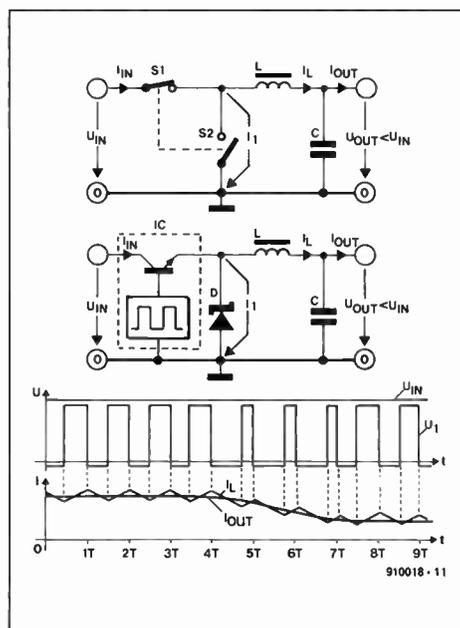


Fig. 1. Basic operation of the LM2575 step-down regulator.

By controlling the mark-space ratio of individual pulses, I_{OUT} can be set such that the desired output voltage U_{OUT} appears across the load. The drawing in Fig. 1 illustrates this process when the output current drops. Switch S1 is actually a power transistor controlled by a rectangular wave generator (Fig. 1b). The other switch, S2, is formed by a diode that enables I_L to continue flowing when the power transistor is switched off. To prevent losses as a result of the relatively high currents, the diode must have a fast switching characteristic. This requirement is met by the use of a Schottky power diode.

The internal circuit of the step-down regulator Type LM2575 is shown in Fig. 2. The power transistor is an n-p-n type that switches the input voltage, U_{IN} , to the output pin marked OUT. The transistor is driven by

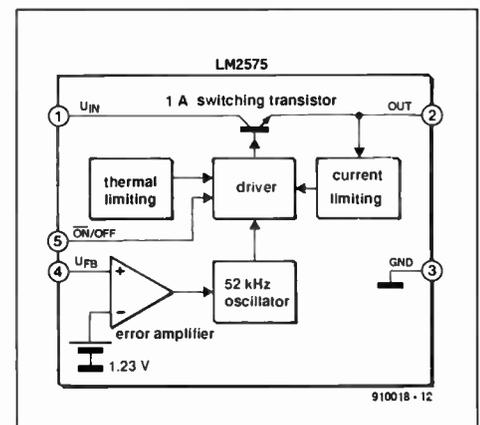


Fig. 2. Internal schematic diagram of the LM2575.

an oscillator with a fixed output frequency of 52 kHz. The pulsewidth of the oscillator output signal is controlled by an error amplifier, which compares the voltage supplied by a potential divider connected across the output with a fixed voltage supplied by an internal 1.23-V reference.

Apart from the protection circuits for the power transistor (junction temperature; output overload), there is a reset generator, which is also used to switch off the output voltage via the TTL-compatible ON/OFF input of the regulator.

A typical application circuit of the LM2575 is shown in Fig. 3. Here, the adjustable device Type LM2575T-ADJ is used. The output voltage is set with the aid of an external circuit. When a fixed-voltage device is used in this circuit, pin 4 must be connected to the output. A 3-A Schottky diode Type 1N5821 is used as the previously mentioned power diode. Components R2, D2 and C5 supply a voltage of +5 V for the ON/OFF control input, whose function may be tested with the aid of jumper J1. When the ON/OFF function is not required, the 5-V supply and the jumper may be omitted, and pin 5 connected permanently to ground. As indicated in Fig. 3, the circuit must have a single earthing point. This arrangement prevents voltage fluctuations as a result of current peaks upsetting the control loop, and should be taken into account when a PCB is designed for the supply. Spurious pulses are suppressed by electrolytic capacitors C2 and C3 at the input and output of the regulator. In

Table 2. LM2575/LM2577 main technical data

| Parameter | | LM2575 | LM2577 |
|---------------------------|-----------|--|-------------------------------------|
| Input voltage | U_{IN} | 3.5 - 35 V | 3.5 - 40 V |
| Output voltage | U_{OUT} | 1.23 - 30 V (always < V_{IN}) | max. 60 V (always > V_{IN}) |
| Output current | I_{OUT} | 1 A | 2 A (depends on V_{OUT}) |
| Current limit (typ.) | I_{CL} | 2.2 A | 4.3 A |
| Switch saturation voltage | U_{SAT} | 0.9 V | 0.5 V |
| Quiescent current | I_Q | 10 mA | |
| Reference voltage | U_{FB} | 1.23 V ($\pm 2\%$) | |
| Input current at VFB | I_{FB} | 50 nA | 100 nA |
| Oscillator frequency | f_{OSC} | 52 kHz ($\pm 10\%$) | |
| Efficiency | | 80% | |
| Operating temperature | | -400°C < T_j < +1250°C | |
| Protections | | internal current limit thermal shutdown | |
| Special features | | ON/OFF input | Soft-start undervoltage detector |

some cases, the a.c. resistance of C3 may be too high, when the capacitor is best replaced by a number of capacitors in parallel with the same total capacitance (small electrolytic capacitors have a lower parasitic inductance than large ones). The value of C3 must always be greater than 330 μ F. The datasheet advises against the use of tantalum capacitors, which cause instability of the control loop. When the output voltage is higher than 25 V, C3 must be replaced by a type with a

working voltage of 40 V or more. Capacitors C1 and C4 form a virtual short-circuit for the fast pulse edges, and so secure the necessary RF suppression.

The output voltage, U_{OUT} , of the regulator is simple to calculate. Potential divider P1-R1 reduces the desired output voltage to 1.23 V. The equation for the current, I , allows us to determine the values of P1 and R1:

$$I = 1.23 \text{ V} / R1 = (U_{OUT} - 1.23 \text{ V}) / P1$$

This allows the value of P1 to be determined when R1 is known:

$$P1 = R1 (U_{OUT} - 1.23 \text{ V}) / 1.23 \text{ V}$$

$$P1 = R1 (U_{OUT} / 1.23 \text{ V} - 1)$$

The value of P1 should lie between 1 k Ω and 10 k Ω . Evidently, the operating principle of the regulator does not allow an output voltage that is higher than the input voltage. The results of a test on the circuit of Fig. 3 at two different settings are given in Table 3. Particular attention was paid to the behaviour of the LM2575 when the input voltage was increased slowly. The result: the set output voltage was maintained exactly (by contrast, some other regulators produce spurious output voltages higher than the set value when the input voltage drops below a certain minimum value). The measured values show an efficiency of between 60% and 90%, and an output voltage ripple of a few millivolts (measured in mV_{rms} with an a.c. millivoltmeter).

Step-up regulator LM2577

Before discussing the operation and application of the LM2577, it may be useful to recapitulate the principle of the step-up or boost voltage regulator. Figure 4 shows the basics. It is seen that the charge inductor, L , is connected ahead of switches S1 and S2 (compare Fig. 1) which are closed alternately. When S2

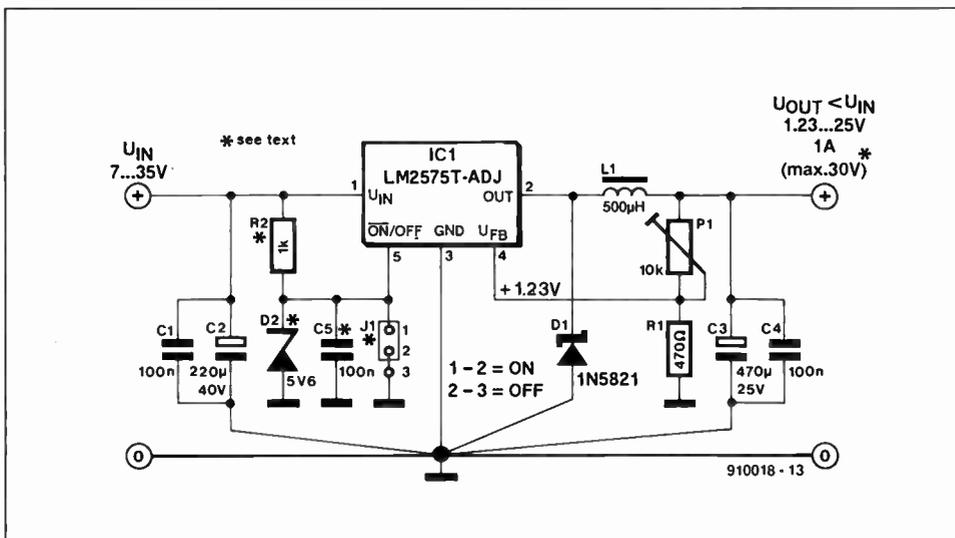


Fig. 3. Application circuit with the LM2575.

Table 3. Test data for application circuit in Fig. 3

| | I_{OUT} (A) | P_{OUT} (W) | I_{IN} (A) | P_{IN} (W) | Efficiency | Ripple (mV) |
|--------------|---------------|---------------|--------------|--------------|------------|-------------|
| 12 V to 5 V | 0.1 | 0.5 | 0.07 | 0.84 | 60% | 1 |
| | 0.3 | 1.5 | 0.2 | 2.4 | 63% | 1 |
| | 0.6 | 3.0 | 0.35 | 4.2 | 71% | 1.2 |
| 20 V to 12 V | 0.1 | 1.2 | 0.08 | 1.6 | 75% | 2 |
| | 0.3 | 3.6 | 0.2 | 4.0 | 90% | 2 |
| | 0.6 | 7.2 | 0.4 | 8.0 | 90% | 2.2 |
| | 1.0 | 12.0 | 0.7 | 14.0 | 86% | 2.5 |

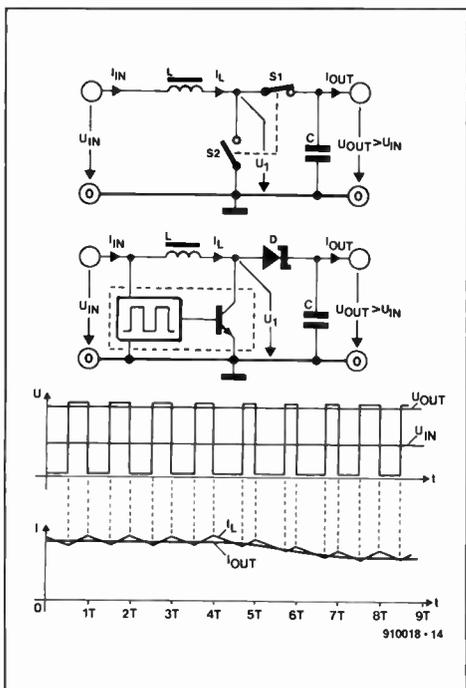


Fig. 4. Basic operation of the LM2577 step-up regulator.

is closed, the choke is connected to the full input voltage, U_{IN} . Because of the self-inductance, the current through L can only rise linearly, i.e., not pulse-like. As in the step-down regulator, magnetic energy is stored in the core of the choke. As soon as S_2 is opened, and S_1 is closed, the self-inductance the

choke forces the current I_L to keep flowing in the same direction. The voltage developed by the self-inductance is polarized such that it is added to the input voltage. Hence, the output voltage is higher than the input voltage. Capacitor C smooths the output current, I_{OUT} . In the LM2577 (Fig. 4b), switch S_2 is formed by a power transistor, and S_1 by a fast switching diode. The diode is reverse biased when the transistor conducts. The voltage and current waveforms that occur in the circuit when the output current is reduced are shown in Fig. 4c.

Figure 5 gives the block schematic diagram of the LM2577. Like the LM2575, the LM2577 contains a 52-kHz pulse-width modulated oscillator driven by an error amplifier which obtains its control information from the voltage at the VFB input. In addition to thermal and current overload protection circuits, the LM2577 features a soft-start generator that prevents a high rush-in current through choke L . Another preventive function is that provided by the undervoltage limit circuit. When the input voltage drops below 2.9 V (typ.), the power stage is automatically switched off to prevent it conducting almost continuously. When the undervoltage detector is actuated, the output voltage drops to virtually the input voltage again.

An application circuit of a step-up voltage converter based on the LM2577 is given in Fig. 6. Here, the adjustable device Type

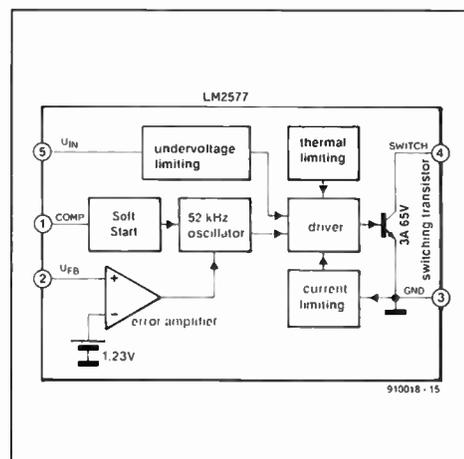


Fig. 5. Internal schematic diagram of the LM2577.

LM2577T-ADJ is used. The 1N5821 and the 500- μ H choke are familiar from the step-down regulator (Fig. 3), as are the central ground point and the possible problems with a single electrolytic capacitor in position C_3 .

Since the same reference voltage of 1.23 V is used, the calculation of the output voltage is identical to that shown above for the LM2575. It should be noted, though, that the circuit in Fig. 6 can not supply output voltages lower than the input voltage. The maximum output current depends on the properties of choke L_1 , the ratio U_{OUT}/U_{IN} , and the maximum permissible current through the power transistor in the LM2577 (4.3 A typ.). The datasheet provides the following information on I_{OUT} and U_{OUT} :

$$U_{OUT} < 60 \text{ V}$$

$$U_{OUT} < 10 U_{IN}$$

$$I_{OUT} < 2.1 \text{ A } U_{IN} / U_{OUT}$$

Also, when the output voltage is higher than 30 V, the 1N5821 should be replaced by a type with a higher rated voltage.

The main results of tests carried out on the circuit of Fig. 6 are listed in Table 4. Clearly, the efficiency rises as the difference between the input and the output voltage becomes smaller. The ripple on the output voltage is higher than with the step-down regulator, but a mere 10 mV_{rms} or so will not be a problem for most applications. When experimenting with the LM2577, make sure that the voltage divider is always connected. Without a properly dimensioned and closed control loop, the IC may be destroyed easily.

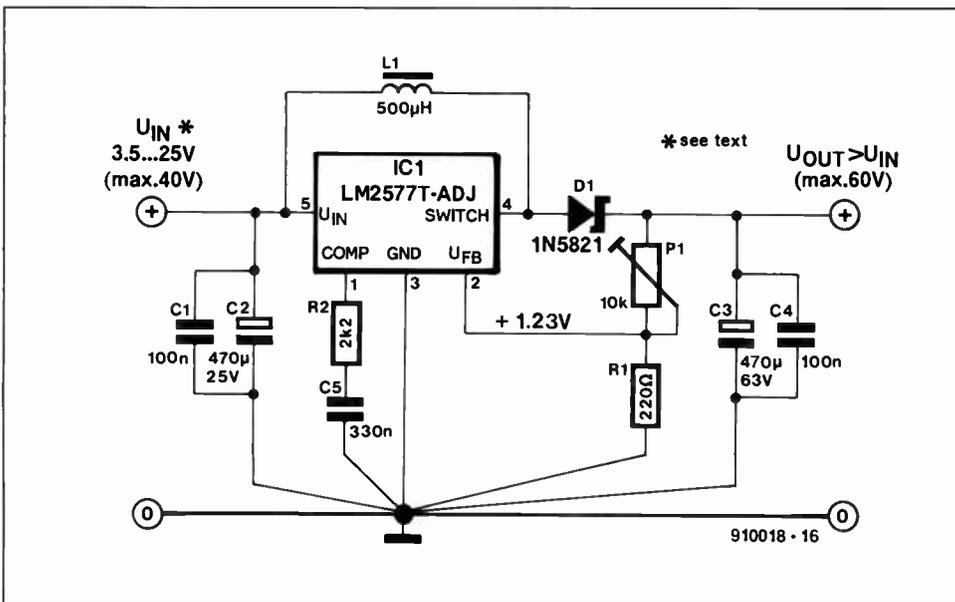


Fig. 6. Application circuit with the LM2577.

Table 4. Test data for application circuit in Fig. 6

| | I_{OUT} (A) | P_{OUT} (W) | I_{IN} (A) | P_{IN} (W) | Efficiency | Ripple (mV) |
|--------------|---------------|---------------|--------------|--------------|------------|-------------|
| 5 V to 12 V | 0.1 | 1.2 | 0.3 | 1.5 | 80% | 4 |
| | 0.2 | 2.4 | 0.6 | 3.0 | 80% | 8 |
| | 0.3 | 3.6 | 0.9 | 4.5 | 80% | 15 |
| 12 V to 28 V | 0.1 | 2.8 | 0.3 | 3.6 | 77% | 6 |
| | 0.2 | 5.6 | 0.6 | 7.2 | 77% | 10 |
| | 0.3 | 8.4 | 0.9 | 10.8 | 77% | 15 |

Source:

Datasheets LM1575-ADJ / LM2575-ADJ — Simple Switcher Step-Down Regulator. National Semiconductor 1990.
 Datasheets LM1577-ADJ / LM2577-ADJ — Simple Switcher Step-Up Regulator. National Semiconductor 1990.

PSYCHOACOUSTICS

By E. Zwicker and H. Fastl

ISBN 3-540-52600-5

350 pages—illustrated

Price \$59 (hardcover)

Psychoacoustics is aimed at practicing acoustics engineers, students of acoustics and physics, and anyone interested in how the human hearing system processes sound. It presents quantitative relations between sound stimuli and auditory perceptions in terms of hearing sensations. Modern views are outlined of peripheral activity in the inner ear, which plays an important role in the development of many hearing sensations. The dependence of these sensations on acoustic parameters is described in psychoacoustical terms.

The ability of our hearing system to receive information is determined by the qualitative relation between sound and impression, as well as by the quantitative relation between acoustical stimuli and hearing sensations. With the advent of digital audio techniques, the science of the hearing system as a receiver of acoustical information, that is, the science of psychoacoustics, has gained additional importance. The features of the human hearing system will have to be taken into account in planning and realizing future acoustical communication systems. Each technical improvement in this area will be judged by listening and relating the result of listening to the cost.

Research scientists, acoustics engineers, and students of physics and acoustics alike

NEW BOOKS

will welcome the wealth of data and the many examples of practical applications of basic research results this book contains on the human hearing system as a receiver of acoustics information.

Professor Zwicker and Dr. Fastl are associated with the Institute for Electroacoustics of the University of Munich.

Springer-Verlag

775 Fifth Ave.

New York, NY 10010

BATTERY REFERENCE BOOK

By T.R. Crompton

ISBN 0-408-00790-7

734 pages

Price \$150 (hardcover)

Not so long ago, most people thought of a battery as a car battery or a torch battery. Nowadays, there exists a wide variety of batteries, primary and secondary, ranging from minute button cells to large installations weighing several hundred tons. Indeed, there is such an assortment of batteries it is doubtful whether anyone knows their details without referring to one or more reference books. But, until *Battery Reference Book* became available, what reference book(s)? I and many of my colleagues had nothing to refer to but the manufacturers' data sheets.

Mr. Crompton, formerly research manager at Oldhams Batteries, has now given us in one volume a guide through the subject in logical sequence. The work covers electrochemical theory as it applies to batteries; battery selection; theory, design, electrical, and performance characteristics; applications of various types of battery; and theory and practice of battery charging. It includes information from battery manufacturers about the performance characteristics they supply. A number of appendices cover suppliers of primary and secondary batteries, battery standards, battery journals, and trade organizations and conferences. Finally, the book has a useful glossary, bibliography, and detailed index.

Battery Reference Book should prove a godsend for designers of all types of battery-operated equipment, battery manufacturers, and electrical and electronic engineers and technicians who use batteries in their work. It should also prove to be useful to research organizations.

Butterworth-Heinemann

80 Montvale Ave.

Stoneham, MA 02180

CORRECTION

In the September issue of *EE USA*, "Opticalock—Part 1" has an error on p. 44: D10 is shown incorrectly in Fig. 3. Its polarity should be reversed.

Continued from page 33

where U_r is the reflected voltage. It is assumed that the forward voltage has been set to 100% of the relative power. Optimum performance is, of course, established when $U_r = 0$. A good antenna system has an SWR that varies between 1:1 and 1:1.2. Poor systems have ratios greater than 1:1.5. Most SWR meters do not give a reading beyond 1:3.

Measurement of field strength

For tuning a transmitter or testing an antenna system, a field strength meter is almost essential. In its simplest form, such an instrument consists of a basic receiver in which the headphones have been replaced by a sensitive moving-coil meter. A possible circuit is shown in Fig. 67.

The meter is zeroed with the 50 k Ω potentiometer. For relative field strength measurements, the antenna circuit need not be tuned; setting the tuned circuit to the centre of its bandwidth is sufficient. Otherwise, a number of different inductors may be selected with the aid of switch S_1 , which makes it possible to tune and test transmitters over a wide range of frequencies.

| Range | Frequency (MHz) | Inductance (μ H) | No. of turns | Wire dia. (mm) |
|-------|-----------------|-----------------------|--------------|----------------|
| 1 | 1.2–2.4 | 300 | 76 | 0.5 |
| 2 | 2.3–4.7 | 82 | 36 | 0.5 |
| 3 | 4.6–9.2 | 21 | 18 | 0.5 |
| 4 | 8.2–16.6 | 6.5 | 8 | 1.0 |
| 5 | 16.2–32.6 | 1.7 | 5 | 1.0 |
| 6 | 22.2–44.8 | 0.9 | 3 | 2.0 |
| 7 | 38.4–77.6 | 0.3 | 3 | 2.0 |
| 8 | 74.5–150.0 | 0.08 | 1 | 2.0 |

The coil diameter for ranges 1–6 must be about 38 mm (1.5 in.) and that for range 7, 25 mm (1 in.). The coil for range 8 is shaped like a hairpin, 50 mm (2 in.) long; wire separation is 10 mm (0.4 in.).

Finally

Instruments are usually multi-purpose: for instance, it is quite common for an SWR meter to be combined with a field strength meter

and a power output meter.

Next month's instalment will deal with "Measurements in digital circuits".

RECOMMENDED SOURCES FOR ELEKTOR ELECTRONICS USA EUROPEAN PARTS

Borbely Audio

Erno Borbely
Melchior Fanger Strasse 34A
8031 Neu-Gilching
Germany
Tel 49-8105-8891
Fax 49-8105-84605 (84H)

ELV France

BP 40
F-57480 Sierck-les-Bains
France
Tel 33-82-83-72-13
Fax 33-82-83-81-80

Meek It Electronics

Rob Planken
Paveljoensgracht 35A
2515 BL Den Haag
The Netherlands
Tel 31-70-609884
Fax 31-70-3979707

Technomatic

Technohouse
486 Church Lane
London NW9 8UF
United Kingdom
Tel 44-081-205-9888
Fax 44-081-205-0190

C-I Electronics

PO Box 22089
6360 AB Nuth
The Netherlands
Fax 31-46-841877

Bull Electrical

250 Portland Road
Hove
Sussex BN3 5QT
United Kingdom
Tel 44-0273-203500
Fax 44-0273-23077

Note: Although some numbers above may seem to be too long/short, they are correct as shown. USA residents need to preface calls with "011".

ELEKTOR BINDERS

Keep your valuable copies in perfect condition in these Elektor Binders. Each binder holds 11 issues with wires so you don't have to punch holes in your magazines.

High quality, book binder cloth construction. The logo is stamped in gold on a dark green background.



each \$12
three or more, \$10 each

Shipping: Postpaid in US.
Canada and Caribbean, please add \$4 for one, \$2 for each additional binder.
Overseas, please add \$4 per binder.

WONDERING WHERE TO FIND THE LATEST ISSUE OF



DON'T SWEAT IT!

They can be found at:

Cody Books Ltd.
1122 Fir Ave
Blaine, WA

Powell's Technical Books
33 NW Park
Portland, OR

Gateway Electronics
8123 Page Blvd
St Louis, MO

Gateway Electronics
9222 Chesapeake Dr
San Diego, CA

Gateway Electronics
9890 Westpark Dr
Houston, TX

Gateway Electronics
5115 N Federal Blvd
Denver, CO

HSC Electronic Supply
3500 Ryder St
Santa Clara, CA

HSC Electronic Supply
4837 Amber Lane
Sacramento, CA

Henry Radio
2050 S Bundy Dr
Los Angeles, CA

Tri-Tek
9014 N 23rd Ave 11
Phoenix, AZ

Tapco Engineering
1639 47th St NE
Cedar Rapids, IA

RJM Electronics
4204 Overland Rd
Boise, ID

RP Electronic Co
2113 W 4th Ave
Vancouver, BC
CANADA

If you prefer home delivery use the handy subscription card enclosed.

RESOURCES UN-LTD.

THIS MONTHS UNIQUE SPECIALS :

50mW BURNING LASER DIODE!

780nm, 180mA @ 3V\$235

15mW ARGON LASERS

HEAD AND SUPPLY.....\$900

COLLIMATOR for LASER DIODES

GRIN MICROLENS IN ALUM. HOLDER.....\$28.95

5mW, 670nm, LASER DIODE

INDEX GUIDED, SINGLE MODE.....\$49.95

MOTORIZED TRIPLE POTENTIOMETER

100/100/10Kohm .25% lin. .5% track.....\$50

IR VIEWERS

NIGHT VISION

ELECTRONICS

CALL FOR CATALOG OR INFO: 603-668-2499
ALL CREDIT CARDS ACCEPTED

FOR SALE

Leader LAT-45 attenuator, solid state, 1991 model, nearly new, \$69; B&K 177 VTVM with PR-43 probe, mint, \$69; White's CoinMaster metal detector, mint, \$69. J.C. Ohlsen, J-281 Caracas St., Ext. Forest Hills, Bayamon, PR 00619.

Esoteric Electronic Equipment from private recording studio. High power lasers and projection systems, decks, amplifiers, signal processing speakers, MIDI software, synthesizers, photographic, stage lighting, and more. Request free list. Richards Elektor List, PO Box 33623EK, Seattle, WA 98133.

TRADE

GET YOUR "FCC COMMERCIAL GENERAL RADIO-TELEPHONE LICENSE." Electronics home study. Fast, inexpensive! Free Details! **COMMAND PRODUCTIONS**, D-266, Box 2824, San Francisco, CA 94126-2824. T1/92

RADIO-TV RECEIVING, TRANSMITTING, C.R.T. TUBES, SAM'S FOTOFACTS AND MORE. P.E.M. TUBES, 8005 Florin Road, #10, Sacramento, CA 95828, (916) 383-9107. T3/92

CLUBS

THE ATLANTA AUDIO SOCIETY is dedicated to furnish pleasure and education for people with a common interest in fine music and audio equipment. Monthly meetings often feature guest speakers from the audio manufacturing and recording industry. Members receive a monthly newsletter. Call: Chuck Bruce, (404) 876-5659, or Denny Meeker, (404) 872-0428, or write: PO Box 361, Marietta, GA 30061.

AUDIOPHILES IN THE DAYTON/SPRINGFIELD, OHIO AREA: We are forming an audio club. Please contact me if you're interested in construction, modifications, testing, recording or just plain listening to music. Ken Beers, 1756 Hilt Rd., Yellow Springs, OH 45387, (513) 767-1457.

CONNECTICUT AUDIO SOCIETY is an active and growing club with activities covering many facets of audio—including construction, subjective testing, and tours of local manufacturers. New members are always welcome. For a copy of our current newsletter and an invitation to our next meeting, write to: Richard Thompson, 129 Newgate Rd., E. Granby, CT 06026, (203) 653-7873.

CLASSIFIEDS

THE COLORADO AUDIO SOCIETY is a group of audio enthusiasts dedicated to the pursuit of music and audiophile arts in the Rocky Mountain region. We offer a comprehensive annual journal, five bi-monthly newsletters, plus participation in meetings and lectures. For more information, send SASE to: CAS, 4506 Osceola St., Denver, CO 80212, or call Art Tedeschi, (303) 477-5223.

ELECTROSTATIC LOUDSPEAKER USERS GROUP is now a world-wide network for those interested in sharing valuable theory, design, construction, and parts source information. If you are interested in building, or have built, your own SOTA ESL we invite you to join our loose-knit organization. For information, send an SASE to: Barry Waldron, 1847 Country Club Dr., Placerville, CA 95667.

THE HI-FI CLUB of Cape Town in South Africa sends a monthly-newsletter to its members and world-wide subscribers. To receive an evaluation copy of our current newsletter, write to: PO Box 18262, Wynberg 7824, South Africa. We'll be very pleased to hear from you.

THE BOSTON AUDIO SOCIETY invites you to join and receive the bi-monthly *B.A.S. SPEAKER* with reviews, debates, scientific analyses, and summaries of lectures by major engineers. Read about Apogee, Nyal, Conrad-Johnson, dbx digital, Snell, music criticism and other topics. Rates on request. PO Box 211, Boston, MA 02126.

THE CATSKILL AND ADIRONDACK AUDIO SOCIETY invites you to our informal meeting. Join our friendly group of audio enthusiasts as we discuss life, the universe and everything! Toobers, Tranzzeestors, vinyl canyons or digital dots. No matter what your level of interest, experience, or preferences, you are welcome. Contact CAAS at (518) 756-9894 (leave message), or write CAAS, PO Box 144, Hannacroix, NY 12087. See you soon!

CHICAGO AREA ENTHUSIASTS WANTED for audio construction club. Call Tom, (312) 558-3377 or (708) 516-0170 evenings for details.

PIEDMONT AUDIO SOCIETY Audio club in the Raleigh-Durham-Chapel Hill area is meeting monthly to listen to music, demonstrate owner-built and modified equipment, and exchange views and ideas on electronics and speaker construction. Tube and solid state electronics are of interest and all levels of experience are welcome. Kevin Carter, 1004 Olive Chapel Rd., Apex, NC 27502, (919) 387-0911.

INDEX OF ADVERTISERS

| | | | |
|--|--------|---------------------------------------|--------|
| All Electronics Corporation | 9 | Software | 10, 65 |
| AUDIO AMATEUR PUBLICATIONS | | Verany Test CDs | 70 |
| Audio Amateur Publications | 69 | PC Boards | 67 |
| Elektor Electronics Dealers | 63 | Radio Shack | CV IV |
| Elektor Electronics Subscriber Services..... | 68 | Resources Unlimited | 63 |
| Crestwood Products | 67 | SMPTE | 9 |
| Hampshire Industries | 67 | Electronics Scene/New Products | |
| Kelvin Electronics | 4 | Analog Devices, Inc. | 12 |
| Midland Technologies | 67 | Baylin Publications | 27 |
| Monitoring Times | CV III | B & K Precision | 13 |
| MoTron Electronics | 55 | Global Specialties | 13 |
| OLD COLONY SOUND LAB | | Jensen Tools | 12 |
| Audio Anthologies I-IV | 8 | MicroMath Scientific Software..... | 13 |
| Books | 65, 66 | Midland LMR | 13 |
| EE USA Binders..... | 63 | Music Interface Technologies | 12 |
| EPROMS, etc. | 65 | Neutrik Systems | 13 |
| Fall Kit Specials | 5 | PC Boards | 12 |
| Front Panel Foils..... | 65 | Remote Console | 13 |
| Loudspeaker Design Cookbook | CV II | Sescom, Inc..... | 13 |
| Meek-It Kits | 6, 7 | Silicon Systems | 27 |
| Parts Sources | 63 | True Image | 12 |
| Printed Circuit Boards | 65 | WeatherSat Ink | 13 |

ELEKTOR ELECTRONICS CLASSIFIED ORDER FORM

PLEASE FILL OUT IN CLEAR BLOCK LETTERS OR TYPE. PLEASE SPELL OUT ENTIRE WORD.

| | | | | | | | | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| _____ 1 _____ | _____ 2 _____ | _____ 3 _____ | _____ 4 _____ | _____ 5 _____ | _____ 6 _____ | _____ 7 _____ | _____ 8 _____ | _____ 9 _____ | _____ 10 _____ |
| _____ 11 _____ | _____ 12 _____ | _____ 13 _____ | _____ 14 _____ | _____ 15 _____ | _____ 16 _____ | _____ 17 _____ | _____ 18 _____ | _____ 19 _____ | _____ 20 _____ |
| _____ 21 _____ | _____ 22 _____ | _____ 23 _____ | _____ 24 _____ | _____ 25 _____ | _____ 26 _____ | _____ 27 _____ | _____ 28 _____ | _____ 29 _____ | _____ 30 _____ |
| _____ 31 _____ | _____ 32 _____ | _____ 33 _____ | _____ 34 _____ | _____ 35 _____ | _____ 36 _____ | _____ 37 _____ | _____ 38 _____ | _____ 39 _____ | _____ 40 _____ |
| _____ 41 _____ | _____ 42 _____ | _____ 43 _____ | _____ 44 _____ | _____ 45 _____ | _____ 46 _____ | _____ 47 _____ | _____ 48 _____ | _____ 49 _____ | _____ 50 _____ |

Private For Sale Private Wanted Trade Please indicate # of insertions _____

Private For Sale ads are for non-profit use. Individuals selling items for retail/profit should be using **Trade** ads. **Private For Sale** and **Private Wanted** ads are on a one time insertion basis. Ads **must** be resubmitted for renewal. **Ads will not be taken over the phone.**

Definition of a word: A series of letters with a space before and after. Count words, not letters. Any words over 50, 20¢ per word. Trade ads are 75¢ per word and indicate number of insertions. Deduct 10% for a 6 x contract; deduct 15% for a 11 x (year) contract in *Elektor Electronics USA*.

Please remember to include your name, address and telephone number. In order for Private For Sale and Want ads to be **free**, you must be a current subscriber. **Ten dollar minimum for charge card orders. Payment MUST accompany first ad.**

Check/Money Order Enclosed Please charge to my MasterCard/Visa:

CARD NUMBER _____ EXP. DATE _____

NAME _____

COMPANY _____

STREET & NO. _____

CITY _____ ST _____ ZIP _____

TERMS OF BUSINESS

PRICING

Prices, except as noted, include shipping in the continental USA. The minimum order is \$10. A \$2 service charge will be added to orders of less than \$10. Prices are subject to change as our costs change. WE RESERVE THE RIGHT TO MAKE PRICE CHANGES WITHOUT NOTICE.

TELEPHONE ORDERS

Telephone orders are welcome between the hours of 9:00 a.m. and 4:00 p.m. EDT, Monday-Friday. Orders for parts are to be made on the ORDER FORM provided. Payment for telephone orders is by MC/VISA only. Our TELEPHONE ORDER NUMBER IS (603) 924-6371 or 924-6526. Our answering machine for MC/VISA orders during non-business hours is (603) 924-6371. FAX: (603) 924-9467 (24 hours).

PAYMENT

All remittances MUST BE IN US FUNDS DRAWN ON A US BANK. Payment for telephone orders must be made by MasterCard or VISA. Mail order payment may be made by MC/VISA, money order, cashier's check or personal check. If payment is made by personal check, allow up to 2 weeks for clearance before order is shipped. Should check be returned for any reason, there will be a \$10 charge.

SHIPPING

Unless noted, freight is prepaid by Old Colony. All orders shipped USPS first class mail or by UPS.

Allow two to three weeks for delivery. Please inquire about appropriate funds for special handling (UPS next day or second day). UPS requires a street address. If you cannot receive UPS delivery, please include an extra \$2 for insured service via Parcel Post. We cannot accept responsibility for safety or delivery of uninsured Parcel Post shipments. Absolutely no COD shipments.

BOOKS, RECORDINGS, CDs, and SOFTWARE

The shipping/handling charge for the US is \$2.00, plus 75¢ each additional item. In Canada, please add \$4.50 for the first item, 75¢ each additional. No returns. According to the Connecticut Dept. of Revenue Services, Regulation #27, Section 12-426-27, in order to sell software to residents of Connecticut, we must register with the department as well as collect taxes for the state from the purchaser. We regret to inform our customers that we will not sell software to anyone from Connecticut, as it will prove to be too costly and burdensome.

OVERSEAS ORDERS

For orders to be shipped outside North America, add 20% to the total order to cover shipping.

RETURNS

If you wish to return all or part of an order for any reason, please call or write first. If we are in error, correction will be made promptly, without charge.

WARRANTY

We warrant that all items sold conform to the qual-

ity and specifications set forth. We make no representations. We accept no responsibility whatever for further use by the customer. We accept no monetary liability in excess of the original cost or replacement of the material if originally defective or damaged in transit.

COPYRIGHT

All drawings, photographs, articles, printed circuit boards, EPROMs, software, and cassettes published in our books or magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of *Elektor Electronics USA* in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature.

Notwithstanding the above, printed circuit boards may be produced for private and personal use without prior permission.

LIMITATION OF LIABILITY

Elektor Electronics USA shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connection with, the supply of goods or services by *Elektor Electronics USA* other than to supply goods as described, or at the option of *Elektor Electronics USA*, to refund the purchaser any money paid in respect of the goods. ■

BOOKS FROM ELEKTOR ELECTRONICS USA

301 CIRCUITS

This book follows the theme of the first in this series, *300 Circuits* (now out of print). It contains over 300 assorted circuits first published in the 1979, 1980, 1981 summer issues of *Elektor Electronics*.

The circuits range from the simple to the more complex and are described and explained in straightforward language. The book is a comprehensive source of ideas and construction projects for anyone interested in electronics.

ISBN 0-905705-12-2

BKAA11 Price \$12.50

302 CIRCUITS

The popularity of this book is shown by its having been reprinted no fewer than three times. It offers a selection of the most interesting articles from the 1982, 1983, 1984 summer issues of *Elektor Electronics*.

In it you will find circuits for audio and video; car, cycle, and motorcycle; home and garden; receivers and aeriels; hobbies and games; measuring and testing; oscillators and generators; current sources and power supplies; microcomputers and music electronics; and a miscellany of other interesting subjects.

ISBN 0-905705-25-4

BKAA12 Price \$12.50

303 CIRCUITS

Like its predecessors, *303 CIRCUITS* offers a comprehensive collection of practical ideas, concepts, and developments in the gamut of electronics. Unlike its predecessors, the book is arranged in 11 subject sections to make it easier for the reader to find that long-sought circuit.

In well over 300 pages, the book offers 32 Audio and Hi-Fi projects; 14 circuits for Car and Bicycles; 43 Computer & Microprocessor circuits; 11 Electrophonic projects; 24 HF and VHF circuits; 16 circuits for a number of hobbies and pastimes; 54 projects for Home and Garden; 29 Power Supply circuits; 29 circuits for Test and Measurement equipment; nine TV and Video projects; as well as 42 Design Ideas.

ISBN 0-905705-62-2

BKAA13 Price \$15.90

DATA SHEET BOOK 2

Like its predecessor (now out of print), this book offers concise, relevant, and rapidly accessible information, which is both practical (e.g., the pin-out of a device) and informative.

The book contains data on integrated circuits as well as on discrete transistors and diodes. Moreover, it gives an introduction to fast (HCMOS) devices and a review of the new symbolic logic as laid down in British Standard BS3939:Section 21 (IEC Standard 617-12).

The final part of the book deals with a number of computer chips, such as memory devices (including programming information for these) and I/O circuits. This section also includes data on a number of non-digital discrete and integrated devices, such as op amps, as well as on some microprocessor peripherals (e.g., the 6522 VIA, the 6580 ACIA, and the 8355A PPI).

ISBN 0-905705-27-0

BKAA14 Price \$16.50

DATABOOK 3: PERIPHERAL CHIPS

This book lists the most important design data of peripheral chips whose type numbers and functions relate them unambiguously to a microprocessor in the same family. All listed devices form part of families based on widely used microprocessors or microcontrollers. Their most evident application will therefore be in conjunction with the associated microprocessor. This should, however, not be taken to mean that a peripheral cannot be used in another ap-

plication. Far from it, as witness the familiar type MC146818A real-time clock and the type MC6845 cathode-ray tube controller. It deserves a place on the bookshelf of anyone concerned with the design, maintenance and servicing of microprocessor-controlled electronic equipment.

ISBN 0-905705-30-0

BKAA15 Price \$17.95

MICROPROCESSOR DATA BOOK

This book has come about because of a need by *Elektor Electronics* engineers, technicians, and editorial staff of a ready reference work on the most important microprocessors. This implies that it does not only contain information on the latest devices, such as the transputer, but also on older, well-established types, such as the Z80 and the 6800.

A general description, hardware block schematic, software structure, DC characteristics, and instruction sets are given for over 70 microprocessors. To prevent the book from becoming unwieldy (and to keep costs down), timing diagrams and AC characteristics have, however, been omitted. The detailed information on all manufacturers mentioned will, however, enable any additional information to be obtained quite readily.

Included in the book are, among others, the 68000 series; the 6502 family; the Z80, 8080, and 8085; Intel's 8086, 80186, 80188, 80286, and 80386; the NS32XXX series, and the INMOS transputers.

ISBN 0-905705-28-9

BKAA16 Price \$17.90

DATABOOK 4: PERIPHERAL CHIPS II

This final volume in *Elektor Electronics' Microprocessor Data Book* series deals with general peripheral chips that, at least as far as their type-coding is concerned, do not belong to a specific family of microprocessors. There are so many of these, however, that only a portion of them can be dealt with in one book. Those contained in this collection have been chosen carefully on the basis of their practical application and frequency of use. Complete data are given for coprocessors from the 80 series (AMD, Cyrix, ITT, Intel, Weitek); real-time clocks from MEM, OKI, Statek, National Semiconductor, and Dallas Semiconductor; transmitters and receivers of serial interfaces RS232, 422, 423, 485 from Motorola, Newport Components, Maxim, Texas Instruments, National Semiconductor, Dallas Semiconductor, and Linear Technology; UARTS, DUARTS, and QUARTS (i.e., programmable ICs intended for data transfer); and the CS8221 set of ICs from Chips & Technology that are used in a great number of PC mother boards (also included is the data sheet of associated software LIM 4.0 for the management of the Extended Memory System).

Apart from the actual data, the book contains much other useful information, such as comparisons between and second sources for all important IC families; addresses of manufacturers and their representatives; and overviews of all peripheral chips (including many that could not be included in this book) that are available from various manufacturers.

ISBN 0-905705-32-7

BKAA17 Price \$17.95

SPECIALS!

BKAAZ/1 BKAA11, 12, 13: all 3 for \$35 (Save \$5.95!)

BKAAZ/2 BKAA14, 15, 16, or 17: ANY THREE for \$45 (Save \$7.35!)

(BE SURE TO SPECIFY)


BKAAZ/S Complete *Elektor* library: all 7 for \$85 (Save \$26.20!)

These books are all available direct from *Elektor Electronics USA* through the Readers Services, from a number of bookshops and electronics retailers in the US and Canada, and from selected bookshops throughout the world. Special prices are those of *EEUSA* only.

Project Pro

Call For FREE Catalog
Call (800) 800-3321 or (216) 425-8888

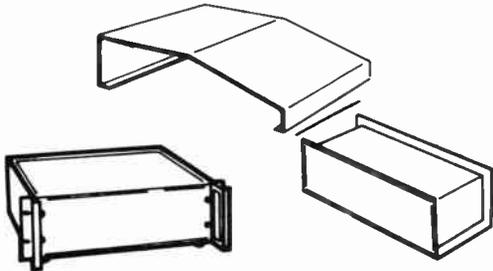Project Pro brings a complete line of electronic enclosures, hardware, and tools to both the professional project engineer and the hobbyist. Everything you need to bring ANY project from development to finished product.



- | | | |
|------------------------------|--------------------------|------------------|
| <u>Electronic Enclosures</u> | <u>Custom Services</u> | <u>Fasteners</u> |
| * Aluminum | * Fabricating | *Nickel Plated |
| * Steel | * Screening | *Black Zinc |
| * Plastic (ABS) | * 72 hour- turnaround | |
| <u>Racks</u> | <u>Chassis</u> | <u>Tools</u> |

1710 Enterprise Pky. Twinsburg, Ohio 44087

PCBoards

P-C-B ARTWORK MADE EASY !
Create and Revise PCB's in a Flash

- * HERC, CGA, EGA, VGA, SUPER-VGA
- * HELP SCREENS
- * EXTREMELY USER FRIENDLY
- * AUTO GROUND PLANES
- * DOT- MATRIX, LASER and PLOTTER ART
- * GERBER and EXCELLON OUTPUT
- * CREATE YOUR OWN FILMS with 1XART
- * LIBRARIES
- * DOWNLOAD DEMOS from 24 hr. BBS!

REQUIREMENTS: IBM PC or Compatible, 384K RAM
DOS 3.0 or later. IBM compatible printers, HP Laser

- PCBoards - layout program 99.00
(PCBoards HP or HI PEN PLOTTER DRIVER 49.00)
- PCRoute - auto-router 99.00
- SuperCAD - schematic pgm. 99.00
- Demo Pkg. - (includes all 3 programs) 10.00

Call or write for more information
PCBoards

2110 14th Ave. South, Birmingham, AL 35205
1-800-473-PCBS / (205)933-1122
BBS / FAX (205)933-2954

Printed Circuit Boards



Working for you!
Time • Quality • Service

- Prototype Specialists
- Printed Circuit Board Design
 - CAD or Hand Generated Design Layout
 - RF, Digital, Analog Capabilities
- Modem Transfer

Single double sided board fabrication
Multi-layer design services

Midland Technologies




Orders: 1-800-726-8871
Inquiries: (406) 586-1190
FAX: (406) 586-0300

Large or small...you'll find us surprisingly affordable!

34374 E. Frontage Rd. • Bozeman, MT 59715

CRESTWOOD PRODUCTS INC.

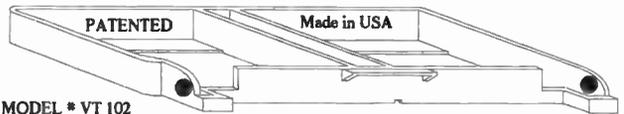40994 GIBBEL RD. HEMET CA. 92544
ORIGINATOR, MANUFACTURER & DISTRIBUTOR
VU-THRU VCR DIAGNOSTIC TOOL
1-800-544-8583



MODEL * VT 102

A CLEAR PLASTIC SHELL THE SAME SIZE & SHAPE AS A STANDARD VHS VIDEO CASSETTE

BY FAR MOST VCR MALFUNCTIONS ARE MECHANICAL
With the VU-THRU TOOL & 9 page ILLUSTRATED MANUAL
you can get many VCR's back in working order without special
tools or equipment!

Typical VHS mechanism with
VU-THRU DIAGNOSTIC TOOL in place

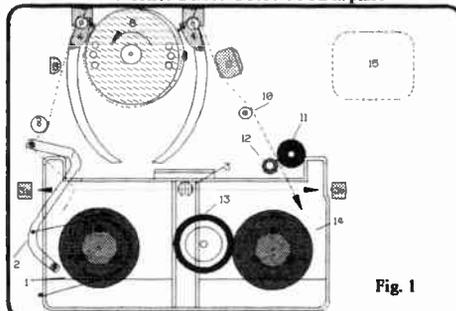


Fig. 1

With power on & the VU-THRU TOOL in place the following will happen in a normally working VCR when "PLAY" is pressed. The tape tension arm (2) will move to the left causing the tension band to apply to the supply spindle (1). Loading posts (4) will move forward carrying the tape to the video head (8) & stopping at loading post supports (7). The video head will be rotating CCW at 1800 RPM. The pinch roller (11) will move toward the capstan (12) & press tape between (11 & 12). The capstan will be turning CW pulling tape across video head. The idler wheel will be driving take-up spindle in a CW direction.
THE ADVANTAGE OF THE VU-THRU VCR DIAGNOSTIC TOOL IS NOW OBVIOUS. Now you can SEE all of the above action without a video cassette blocking your view.

WANTED!! DEALERS OUTSIDE OF THE USA - WRITE FOR FULL DETAILS



\$ 9.95 each
\$ 3.50 S&H
\$ 13.45 total

SPECIAL ORDER TWO FOR \$ 19.90 WE PAY S&H

COD add \$ 3.50
CA. orders add 7% sales tax
VISA - MASTERCARD
CANADA - MEXICO
ADD \$ 5.00 U.S.

ELEKTOR ELECTRONICS USA

Subscriber Services



Complete the applicable section(s) below and mail to:
Elektor Electronics USA
 PO Box 876
 Peterborough, NH
 03458-0876

WOULD YOU LIKE TO . . . SUBSCRIBE?

YES! Just check the appropriate boxes in the "renew" section and fill in name and address.

RENEW?

Fill in the appropriate sections below. For faster service use your mailing label and subscriber number.

- 1 year at \$28 Check/MO enclosed
- 2 years at \$50 Charge MC/VISA

Canada add \$8 per year postage.
 Remit in US \$ only.

SUBSCRIBER NUMBER

NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

MC/VISA _____ EXP. _____

CHANGE YOUR ADDRESS?

Fill in your new address to the right and old address and subscriber number above.



MY NEW ADDRESS:

NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

GIVE A GIFT?

What a thoughtful idea! Fill out your name and address above, the recipient's name and address to the right. We'll even send a gift card announcing your gift.



NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

TELL YOUR FRIENDS ABOUT US?

Print their names and addresses below or photocopy this form for them. We'll take care of the rest.

| | |
|-------------------------------|-------------------------------|
| NAME _____ | NAME _____ |
| STREET & NO _____ | STREET & NO _____ |
| CITY _____ ST _____ ZIP _____ | CITY _____ ST _____ ZIP _____ |

COMPLAIN ABOUT YOUR SUBSCRIPTION?

Yes, it sometimes happens. We try to avoid it at all costs, but if you have a problem, we want to know. Call or write with all pertinent information.



YOU CAN CALL US

(603) 924-9464
 Subscription Department
 9-4 Business Days
 Answering Machine
 All Other Hours
 FAX: (603) 924-9467
 24 Hours

NOW THAT YOU'VE SEEN OUR NEWEST TREASURE . . .

WHY NOT HAVE A LOOK AT THE REST?



The newest publication from the folks who bring you *Audio Amateur* and *Speaker Builder*

Glass Audio features the best vacuum tube designs for audio reproduction—past and contemporary. The new designs take advantage of improved components and control techniques that make the end results far superior to anything possible during the early days of audio's rebirth after World War II.

That's why tubes are having such a renaissance of interest as a perfectionist approach to good sound. And that's why tubes are reappearing in original equipment, in high end consumer and professional audio systems.

Published twice a year in June and December, *Glass Audio* will inform you about new innovations in the field and about parts sources. We'll also include modification projects, reviews of technical basics and regular columns such as Tube Troubles, Tube Tips and much more.

Subscribe today!



Audio Amateur THE JOURNAL FOR AUDIOPHILE CRAFTS

The innovative, independent audiophile journal for the thoughtful and capable music lover

Audio Amateur's articles deal with how audio equipment works, as well as how to build or modify it. Construction and modification articles are plentiful, supplying all needed parts, performance and assembly details. Exceptionally high quality designs.


Audio Amateur offers a number of features in each issue that abound with useful ideas. The *Letters* column is an open forum for problem solving and information interchange; *Classic Circuitry* reprints schematics of state-of-the-art gear—old and new; *Audio Aids* relates readers' experience with simple modifications to equipment and construction techniques. We also feature many useful and practical hi-fi accessories you can build to further your audio enjoyment.

For a small investment you can make your music system sound better—very probably a lot better.

Speaker Builder THE LOUDSPEAKER JOURNAL

The magazine that finally deals seriously with the art and craft of speaker building

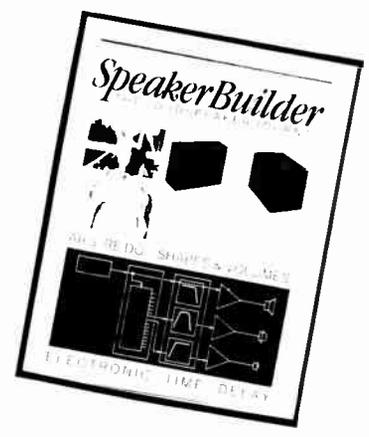The *Art* of building a speaker is to optimize that mixture of design and engineering to balance all the parameters for the most beautiful sound possible. The *Craft* is knowing how and why. *Speaker Builder* gives you knowledge—from driver parameters and crossovers to woodworking—to develop and refine your techniques, and to get the most out of your system.



Speaker Builder helps you explore new designs with how-to construction articles, and can show you how to modify your old speakers and make them sound better than ever. Learn from our writers who turn abstract theory into practical approaches, and from the experience of other readers who have been down the road before you. *Speaker Builder* is the best investment you can make in your system—six issues per year filled with stimulating and exciting ideas.

GLASS AUDIO
 Two years, (4 issues) \$18
 One year, (2 issues) \$10
Canada add \$2 per year postage

AUDIO AMATEUR
 Two years, (8 issues) \$35
 One year, (4 issues) \$20
Canada add \$4 per year postage

SPEAKER BUILDER
 Two years, (12 issues) \$45
 One year, (6 issues) \$25
Canada add \$4 per year postage

NAME _____
STREET & NO. _____
CITY _____ STATE _____ ZIP _____
MC OR VISA NUMBER _____ EXPIRE _____

AUDIO AMATEUR PUBLICATIONS

PO Box 576, Dept. E91, Peterborough, NH 03458-0576 • (603) 924-9464 • FAX: (603) 924-9467

Answering machine for credit card orders only: before 9:00 a.m., after 4:00 p.m. and weekends. Have all information plus MC/VISA available.

EVERYTHING YOU EVER WANTED TO ASK ABOUT YOUR CD PLAYER BUT WERE AFRAID TO KNOW!



After 18 months of painstaking research and several trial pressings, here is the most complete and functional test package ever available on the market. Created in the studios of Pierre Verany, with the collaboration of the French audiophile magazine *Compact*, the final product was submitted to the creators of the CD concept and its standard—the Philips laboratories in Eindhoven, Holland. Their verdict: "a beautiful piece of work!"

The compact discs in this copiously documented set are unique. For the first time, they offer the consumer a tool for verifying the qualities and defects of a given CD player, with no required measuring equipment or in-depth technical knowledge. However, they have been shown to yield startling performance demonstrations even under the strictest of laboratory conditions.

CHANNEL SEPARATION ★ FREQUENCY RESPONSE ★ HARMONIC DISTORTION ★ SIGNAL-TO-NOISE RATIO ★ TRANSIENT SIGNAL RESPONSE ★ INTERMODULATION DISTORTION ★ CONVERTER OVERLOAD EFFECT ★ CD CUTTING VELOCITY ★ TRACK PITCH ★ DROPOUTS

PIERRE VERANY

DIGITAL TEST PV 788031/32 (2 Compact Discs)

106 Demonstration tracks and equipment tests, accompanied by a detailed 68-page instruction booklet.

COMPACT DISC ORDER FORM

Note: Discs and recordings are not returnable for credit or exchange.

NAME _____ MAGIC NO. _____
STREET & NO. _____
CITY _____ STATE _____ ZIP _____
MC/VISA _____ EXP _____

Please send me _____ PV 788031/32 (2 CDs) at \$34 per set plus \$2.25 handling. Outside USA, please add \$7 for air shipment.

Check/MO

MC

VISA

Postage \$ _____

TOTAL \$ _____



OLD COLONY SOUND LAB

PO Box 243, Dept. E91

Peterborough, NH 03458-0243 USA

(603) 924-6371 / 924-6526

FAX: (603) 924-9467

Answering machine for credit card orders only: (603) 924-6371 before 9:00 a.m., after 4:00 p.m., and weekends.

Have information plus MC/VISA available.



MONITORING TIMES and

GROVE ENTERPRISES

*The perfect combination
for global reception!*

Since 1982 Monitoring Times has been the most authoritative guide for radio listening. Whether your interest is international broadcasting or two-way communications, MT's monthly updates on frequencies, schedules, station profiles, equipment reviews and monitoring tips, written by the leading experts, delivers the information you need.


And for the best possible reception -- and the fastest service in the industry -- see the new Grove Catalog and Buyer's Guide, the discriminating choice for equipment, accessories and publications for better listening.

Send now for your free Grove catalog. A sample of *Monitoring Times* (mailed in U.S.) is only \$3 and a one-year subscription -- 12 monthly issues -- is only \$19.95

Grove Enterprises

P.O. Box 98, Brasstown, NC 28902; 704-837-9200

PARTS PLACESM

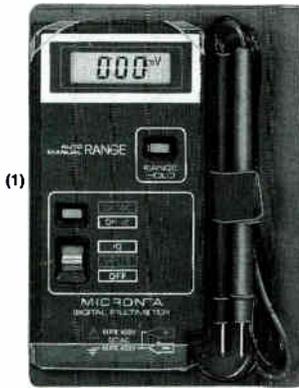


(1)

(1) NEW! "Shirt Pocket" Multimeter. Take it along! Features LCD display, autoranging with manual override, continuity sounder. Measures to 400 volts AC/DC and resistance. With fold-up vinyl case, manual and replaceable batteries. #22-169 27.95

(2) NEW! Building Power Supplies. Easy-to-understand, 96-page book explains linear and switching supplies. Includes complete plans for building five useful supplies with Radio Shack parts. #276-5025 4.95

(3) Mini Audio Amplifier. Great for computer voice/music synthesis, signal tracing and more. Has a built-in speaker, 1/8" headphone jack, 1/8" input jack and volume control. Put one on your bench today! #277-1008 11.95

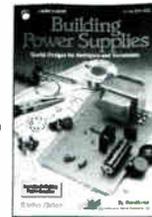(4) Digital Logic Probe. LEDs and tone outputs reveal logic states instantly. It's the fast way to check operation and pinpoint problems in all types of digital circuits. #22-303 16.95



(2)



(4)



(3)

Parts Special-Order Hotline. Your local Radio Shack store stocks over 1000 popular electronic components. Plus, we can special-order over 10,000 items from our warehouse—linear and digital ICs, transistors and diodes, vacuum tubes, crystals, phono cartridges and styli, even SAMS[®] service manuals. Your order is sent directly to your Radio Shack store and we notify you when it arrives. Delivery time for most items is one week and there are no postage charges or minimum order requirements.

(1) Shielded RS-232 Jumper Box. Top-quality inline D-sub 25 adapter. Wire the included jumper wires and board to suit your need. #276-1403 9.95

(2) Computer RS-232 Tester. Dual-color LEDs monitor seven data/control lines to help you spot problems quickly. D-sub 25. Connects inline. #276-1401 14.95

(3) Grounded-Tip Soldering Iron. 15W. #64-2051 7.49

(4) Vacuum-Type Desoldering Tool. #64-2120 6.95

(5) Locking Forceps. 6" long. Stainless. #64-1866 4.95

(6) Rosin Soldering Paste Flux. 1 oz. #64-021 1.79

(7) Lead-Free Solder. 96% tin, 4% silver. 0.25 oz. #64-025 1.99

(8) 10-Amp Microwave Oven Fuses. #270-1256 Pkg. of 2/1.29

(9) 2-Amp Fast-Acting Fuses. #270-1275 Pkg. of 3/79¢




(10) 5-Amp "Blade" Vehicle Fuses. #270-1205 Pkg. of 2/89¢

Computer/Printer/Business Machine AC Power Cords. 6 feet long.


(11) Extension. Just plug in to lengthen existing cord. #278-1259 4.99

(12) With Space-Saving 90° CEE Connector. #278-1260 5.99

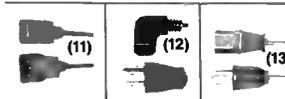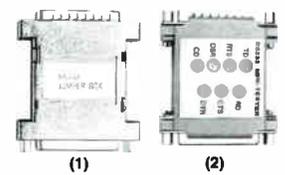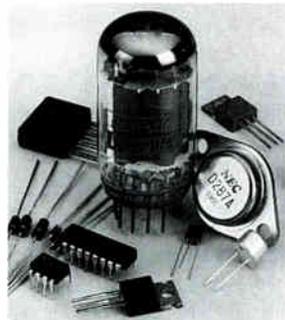(13) With Straight CEE Connector. #278-1257 3.99




(1)

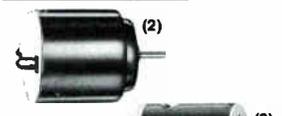

(2)



(3)

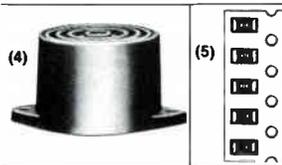


(4)


(5)



(6)

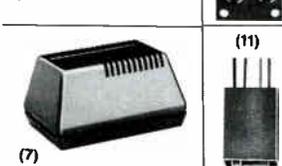

(7)

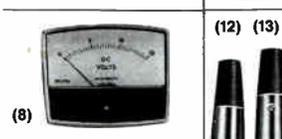

(8)



(9)

(10)

(11)

(12)

(13)

(14)

(1) Voltage Regulator ICs. Feature built-in overload protection and thermal shutdown. Great for custom projects. Maximum input: 35VDC. 7805. 5V. #276-1770 1.19

7812. 12V. #276-1771 1.19

(2) Low-Voltage Motor. Just the thing for science projects, robotics and solar power demos. Operates from 1 1/2 to 3VDC. About 1 1/2" long. #273-223 99¢

(3) High-Speed 12VDC Motor. Up to 15,200 RPM, no load. About 2" long. #273-255 2.99

(4) "Ding-Dong" Chime. This IC and mini-speaker combo is ideal for a customer-entry alert or doorbell. Produces 80 dB sound pressure at 12VDC. Operates from 6 to 18VDC. #273-071 8.99

(5) Surface-Mount Resistors. 200-piece assortment of 15 popular values. Rated 1/8 watt, 5%. #271-313 Set 4.99

(6) Metal Project Cabinet. An attractive, easy-to-drill housing at a low price. 3 x 5 1/4 x 5 7/8". #270-253 6.79

(7) Power Supply Project Case. Vented 2 1/2 x 4 5/8 x 3 1/4" molded case. #270-287 3.99

(8) 0 to 15 DC Voltmeter. Quality jeweled movement. #270-1754 7.95

(9) Box/Board Combo. Molded enclosure plus predrilled 2 x 3 1/8" board, labels and more. #270-291 4.99

(10) Eight-Position Audio Phono Jack Board. #274-370 1.69

(11) 1:1 Audio Transformer. Z: 600-900Ω. #273-1374 3.59

(12) Three-Pin XLR Mike Plug. Metal body. #274-010 2.99

(13) Three-Pin XLR Inline Socket. #274-011 2.99

(14) Three-Pin XLR Panel Socket. #274-013 3.69

Since 1921 Radio Shack has been the place to obtain up-to-date electronic parts as well as quality tools, test equipment and accessories at low prices. Our 7000 locations are ready to serve you—NOBODY COMPARES

Prices apply at participating Radio Shack stores and dealers. Radio Shack is a division of Tandy Corporation

Radio Shack
AMERICA'S TECHNOLOGY STORE