

ELEKTOR **ELECTRONICS** **USA**

THE INTERNATIONAL JOURNAL
FOR RECREATIONAL ELECTRONICS

APRIL 1992

\$3.00 US
CANADA \$4.00

Top-of-the Range FM Tuner

Comb Generator

AD232 Converter


Generic Array Logic

Two Meter Receiver

Red-light Diode Lasers

Super Sign

Review of Pulsar

 

OCEAN STATE ELECTRONICS

PROFESSIONAL, AMATEUR, OR COMMERCIAL — WE'RE YOUR ONE STOP ELECTRONIC SOURCE
CALL OR WRITE FOR OUR FREE 112 PAGE CATALOG 1-401-596-3080

MAGNET WIRE

Plain enamel. Solid bare copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

MW14 3.25	MW24 3.70	MW34 4.80
MW16 3.30	MW26 3.75	MW36 4.90
MW18 3.35	MW28 3.85	MW38 4.95
MW20 3.55	MW30 4.00	MW40 5.10
MW22 3.65	MW32 4.40	

TOROIDS

IRON	FERRITE
T-25-240	FT37-4360
T-25-640	FT37-6160
T-37-645	FT37-7760
T-37-1245	FT50-4375
T-50-255	FT50-6175
T-50-355	FT50-7775
T50-655	FT82-431.00
T68-075	FT82-671.00
T68-275	FT82-681.00
T68-675	FT114-612.15
T80-285	FT140-434.10
T200-24.00	FT240-618.00

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.

RECTIFIER DIODES

1N4001	1 AMP 50 PRV	.09
1N4002	1 AMP 100 PRV	.09
1N4003	1 AMP 200 PRV	.10
1N4004	1 AMP 400 PRV	.10
1N4005	1 AMP 600 PRV	.12
1N4006	1 AMP 800 PRV	.15
1N4007	1 AMP 1000 PRV	.17
1N5400	3 AMP 50 PRV	.20
1N5401	3 AMP 100 PRV	.20
1N5402	3 AMP 200 PRV	.20
1N5404	3 AMP 400 PRV	.25
1N5406	3 AMP 600 PRV	.25
1N5407	3 AMP 800 PRV	.25
1N5408	3 AMP 1000 PRV	.25

REGULATED POWER SUPPLIES

13.8 VDC OUTPUT

Perfect for ham equipment, CB's, car stereo's and other 13.8 VDC items. LED on indicator, short circuit protection. Binding post output. Amp ratings are continuous. 110V input.

38-383	3 AMP	\$31.50
38-384	4 AMP	\$39.50
38-386	6 AMP	\$46.50
38-381	10 AMP	\$79.50
38-382	20 AMP	\$119.50
XP-725	25 AMP	\$129.50

DELUX CODE KEY

Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

70-378\$11.75

BUZZER

Produces steady high frequency signal. Excellent for code practice. Screw control for adjusting pitch. Uses standard 1 1/2V battery.

70-375\$4.99

DIGITAL MULTIMETER

19 RANGES
3 1/2 DIGIT LCD DISPLAY
DVC - 1000
ACV - 750
DCA - 10A
RES - 2 MEG
DIODE CHECK

DM301\$27.95

Q-DOPE

Solution of pure polystyrene in solvents. Dries fast and leaves a clear, protective coating on toroids, coils and transformers, with no or minimal effect on inductive values. May also be used as a cement for molded or fabricated items made of polystyrene.

10-3702 (Bottle with Brush 2 fl. oz. 59 ml)\$3.75

VERNIER DIALS

VD112-10 1-1/2" Diameter 0-10 Marking\$8.25
VD112-100 1-1/2" Diameter 0-100 Marking\$9.25
VD2 2" Diameter 0-100 Marking\$10.25

200 WATT INVERTER

Plugs into your lighter and runs:

- Ham Equipment
- Lights
- Soldering Iron
- Computer
- Power Tools
- Shaver
- 13" TV with VCR
- MUCH MORE

Model: POW 200
Input: 10 to 15 volts DC
Output: 115 volts AC true RMS
Power: 400 Watts peak
200 Watts for 5 minutes
140 Watts continuously

POW-200\$119.95

Size: 5" x 2 1/2" x 1 7/8"
Weight: 15 ounces
Warranty: 3 year

SWITCHING/GP DIODES

1N914	75V PRV 10MA	.07
1N4148	75V PRV 10MA	.07

GERMANIUM DIODES

1N34A	100V PRV 200MA	.20
1N3600	50V PRV 200MA	.25

MINIATURE TOGGLE SWITCHES

3A 125V Solder Terminals

11-201SPDT\$1.25
11-202DPDT\$1.50

TWO PIECE CHASSIS ALUMINUM

Uses 4 machine screws, supplied. Gray baked enamel.

PART NO.	SIZE (IN.)			PRICE
	L	W	H	
1411B	2.7	2.2	1.6	4.46
1411C	3.2	2.2	1.1	4.78
1411D	3.2	2.2	1.6	4.90
1411F	4.0	2.2	2.7	5.66
1411G	4.0	2.2	1.6	5.04
1411H	4.0	2.2	2.2	5.47
1411K	5.0	2.2	2.2	5.82
1411L	5.0	4.0	3.0	7.53
1411M	6.0	3.0	3.0	8.02
1411N	5.0	3.0	2.1	6.30
1411P	6.0	5.0	4.0	9.86
1411Q	7.0	5.0	3.0	9.27
1411R	8.0	6.0	3.5	12.28
1411S	8.0	4.0	3.0	15.63
1411T	10.0	2.2	1.6	8.68
1411U	10.0	6.0	3.5	15.31
1411W	12.0	3.0	2.2	11.15
1411X	12.0	7.0	4.0	18.62
1411Z	17.0	5.0	4.0	20.10

IC SOCKETS - LOW PROFILE

LP-8	8 PIN	..10	LP-22	22 PIN	..23
LP-14	14 PIN	..11	LP-24	24 PIN	..25
LP-16	16 PIN	..12	LP-28	28 PIN	..30
LP-18	18 PIN	..17	LP-40	40 PIN	..43
LP-20	20 PIN	..21			

3/8" SQUARE TOP ADJUST TRIM POTS

OFA12	100Ω	OFA24	20KΩ
OFA52	500Ω	OFA54	50KΩ
OFA13	1KΩ	OFA15	100KΩ
OFA23	2KΩ	OFA25	200KΩ
OFA53	5KΩ	OFA55	500KΩ
OFA14	10KΩ	OFA16	1MΩ

SINGLE TURN .5 WATT LINEAR TAPER\$1.10 EACH

2 3/8" FULL VIEW PANEL METER

Designed for modernistic equipment. Beautiful appearance, easy to read, D'Arsonval type movement, accuracy within 2%. Will mount in panels up to 3/8" thick, has zero adjustment screw. Size 2 3/8" x 1 13/16" x 1 1/4" deep, including terminals and will mount into 1 1/2" hole.

PART NO.	METER READING	PRICE
M60-118	0-1MA	16.00
M60-121	0-15VDC	16.00
M60-122	0-30VDC	16.00
M60-125	0-150VDC	16.00
M60-127	50-0.50μA	16.00
M60-129	0-50μA	16.00
M60-130	0-100μA	16.00
M60-133	VU METER	16.00
M60-149	ILLUMINATION KIT	2.85

CERAMIC DISC CAPACITORS 50V ± 20%

PART NO.	CAP.μF	PRICE	PART NO.	CAP.μF	PRICE
CD10-5	10PF	.12	CD180-5	180PF	.14
CD12-5	12PF	.12	CD220-5	220PF	.14
CD15-5	15PF	.12	CD270-5	270PF	.14
CD18-5	18PF	.12	CD300-5	300PF	.15
CD22-5	22PF	.12	CD330-5	330PF	.15
CD27-5	27PF	.12	CD390-5	390PF	.15
CD33-5	33PF	.12	CD470-5	470PF	.15
CD39-5	39PF	.12	CD560-5	560PF	.15
CD47-5	47PF	.12	CD680-5	680PF	.15
CD56-5	56PF	.12	CD001-5	001μF	.15
CD68-5	68PF	.12	CD0047-5	0047μF	.15
CD75-5	75PF	.12	CD01-5	01μF	.15
CD100-5	100PF	.12	CD022-5	022μF	.15
CD120-5	120PF	.14	CD05-5	05μF	.20
CD150-5	150PF	.14	CD104-5	1μF	.20

PANAVERSE INTERCHANGEABLE VERSATILITY!

PAN 303 STANDARD HEAD\$20.99
PAN 300 STANDARD BASE\$17.99
CIRCUIT BOARD HOLDER\$23.99

TO ORDER

Call 1-800-866-6626 ORDERS ONLY
(Catalog requests can not be taken on toll free number.)

8 a.m. - 6 p.m. EST Monday through Friday
10 a.m. - 2 p.m. Saturday

OR WRITE TO:
Ocean State Electronics,
P.O. Box 1458, Westerly, R.I. 02891

OR FAX TO: CATALOG REQUEST
(401) 596-3590 (401) 596-3080

If paying by CREDIT CARD include Card No. and Expiration Date

Mail in orders please include \$4.00 S/H Minimum order \$10.00
R. I. Residents add 7% Sales Tax
ORDERS RECEIVED BY 1:00 PM EST — SHIP SAME DAY!
FREE SHIPPING ON ALL MAIL IN ORDERS OVER \$25.00.
Applies to UPS Ground in Continental U.S. Only.
PRICES SUBJECT TO CHANGE.

ELECTROLYTIC CAPACITORS - RADIAL 50V

PART NO.	CAP.μF	PRICE	PART NO.	CAP.μF	PRICE
CER 47-50	47	.17	CER47-50	47	.25
CER1-50	1	.17	CER100-50	100	.36
CER2-50	2.2	.17	CER220-50	220	.54
CER3-50	3.3	.17	CER330-50	330	.70
CER4-50	4.7	.17	CER470-50	470	.93
CER10-50	10	.17	CER1000-50	1000	1.45
CER22-50	22	.18	CER2200-50	2200	2.80
CER33-50	33	.22			

TRANSISTORS

PN2222A	.05
2N2222A	.35
2N3055	.69
2N3553	2.75
2N3563	.35
2N3771	1.95
2N3866	1.00
2N3904	.10
2N3906	.10
2N4401	.15
2N4403	.15
MPF102	.29

LINEAR IC'S

MAX232CPE	4.05
LM311N	.45
LM339N	.35
LM386N	.99
NE555	.25
NE564	1.75
NE567	.99
NE602N	2.25
LM741N	.25
CD22402E	9.95
CA3126E	1.60
MC1350P	1.49

KITS

Complete with PC Board and Instructions. Educational, Fun to Build, and Practical.

SIGNAL INJECTOR/TRACER

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.

K-21A\$18.95

LOGIC PROBE

Hand held Digital Logic Probe provides convenient and precise use in the measurement of logic circuits. It displays logic levels (high or low), pulses and voltage transients down to 300 nanoseconds. High intensity LED readouts provide instant response to the logic state.

K-27A\$18.95

In next month's issue

(among others):

- NICAM decoder
- Z80 card
- Review of Analyser III
- Digital short-range radio
- I²C display
- GAL programmer
- Elements of passive electronic components
- The NICAM system

Front cover

The FM tuner described in a series of articles that started last month has specifications that challenge those of the best commercial tuners available. Shown is the finished main tuner board. The (ready-made) tuner module used prevents problems with building and adjusting the RF circuitry.

ELEKTOR ELECTRONICS USA (US ISSN 1051-5690) is published monthly except August at \$28 per year; \$50 for two years by Audio Amateur Publications, Inc., 305 Union St., Peterborough NH 03458 USA. Second class postage paid at Peterborough NH and an additional mailing office.

POSTMASTER: Send address changes to **Elektor Electronics USA**, Caller Box 876, Peterborough NH 03458-0876.

EDITORIAL

- 11 **Engineers' Retreat**

COMPUTERS & MICROPROCESSORS

- 24 **General array logic (GAL)**
based on an original article by D. Gembris
- 34 **Red-light diode lasers**
based on an original article by S. von Fehren
- 48 **COURSE: 8051/8032 assembler—Part 3**
by Dr. M. Ohsmann
- 52 **REVIEW: PULSAR—software for logic circuit simulation**
Design by K. Walraven

DESIGN IDEAS

- 38 **Super sign**
by Dr. K. A. Nigim

GENERAL INTEREST

- 54 **PROJECT: Motor speed limiter**
Design by K. Walraven

INTERMEDIATE PROJECT

- 28 **Automatic NiCd charger**
Design by L. Pijpers

RADIO, TELEVISION & COMMUNICATIONS

- 14 **PROJECT: Comb generator**
by J. de Belie
- 40 **PROJECT: FM tuner—Part 2**
Design by H. Reelsen
- 43 **PROJECT: 2-meter FM receiver**
Design by J. Barendrecht and L. Lemmens

SCIENCE & TECHNOLOGY


- 31 **Understanding waveform harmonics**
by Dr. K. A. Nigim

TEST & MEASUREMENT


- 17 **PROJECT: AD232 converter**
Design by Ing. B. C. Zschocke and A. Arnold
- 36 **PROJECT: LCD for Inductance/capacitance meter**
Design by L. Pijpers
- 58 **PROJECT: Milliohm measurement adaptor**
Design by Ing. B. C. Zschocke

MISCELLANEOUS INFORMATION

 
Electronics Scene 12, 13; New Books 61; Letters 62–68; Advertisers' Index 68; Readers Services 69; Terms of Business 70.




2-meter FM receiver—p. 43

 

Red-light diode lasers—p. 34

 

AD232 converter—p. 17

 
 8051/8032 assembler course—Part 3
p. 48

OLD COLONY SOUND LAB

CASSETTES

A HISTORY OF MUSIC OF THE WESTERN WORLD, 1100-1980 Sussex Tapes/Audio-Forum

CAS1
\$89.50

In this series of twelve deluxe, gift-boxed audio cassettes, informative discussions by world-renowned authorities are followed immediately by authentic musical examples created by major international orchestras and chamber groups, enabling the musical past to be presented in a single, easily-listened-to format. Sorry, cassettes not sold separately.

Contents: *Cassette #1--New Arts for Old: Music of Medieval Times, 1100-1480.* Side One: Christopher Page explains the early domination of Gregorian chant, and takes the listener from the flowering of love poetry in France to the development of polyphonic music in the 13th century. 12 examples. Side Two: From the Ars Nova of France the listener turns to Landini's Italy and the England of John Dunstable. Liberal use of musical examples helps to convey the extrovert boldness and excitement of medieval music. 10 examples.

Cassette #2--Musick's Feaste: Music of the Renaissance, 1480-1600. Side One: Anthony Rooley talks about the musical renaissance in Europe and traces the spread of the Flemish School through France to Italy. 9 examples. Side Two: The discussion concentrates on the English renaissance and shows how the Flemish style was absorbed by English composers. 10 examples.

Cassette #3--A Pearl Distorted: Music of the Baroque Period, 1600-1750. Side One: What does "baroque" mean? Christopher Hogwood and Michael Oliver discuss the different types of music which this complex period embraces and show how, in geographical terms also, the era covered a very large area. 8 examples. Side Two: Opera is considered as the great dramatic spectacle of baroque entertainment, and the current interest in authenticity of musical performance is examined. 7 examples.

Cassette #4--Sonata and the Creative Ideal: Music of the Classical Period, 1750-1830. Side One: Alan Hacker first explains the principle and importance of classical sonata form, with the aid of keyboard examples played by Richard Burnett on an eighteenth-century traveling square piano. 6 examples. Side Two: The listener moves to Vienna, for the artist the "richest, happiest, and most agreeable residence in Europe," as Peter Wilson discusses opera and the reforms of Gluck before looking ahead to the Romantic period through the music of Schubert and Weber. 8 examples.

Cassette #5--Expression and Extravagance: Music of the Romantic Period, 1830-1900. Side One: Conductor Norman Del Mar and critic John Amis discuss the meaning of "romanticism" in music. In addition, they examine the role of the virtuoso and compare large-scale opera with the compressed drama of the Lied. 13 examples. Side Two: The speakers look at the rise of nationalism within the period and trace the development of the orchestra. 12 examples.

Cassette #6--Reaction and Revolution: The Modern Period, 1900-1945. Side One: Wilfrid Mellers takes the listener from Wagner to Schoenberg, as he discusses the changes in musical language around 1900. 8 examples. Side Two: The speaker considers some of the less radical elements of twentieth century music, finishing with the place of jazz in the period. 8 examples.

Cassette #7--Music Now: Contemporary Music, 1945-1980. Side One: Hugh Wood appraises the entire post-World War II period, with illustrations from the music of composers such as Boulez and Stockhausen. 11 examples. Side Two: As above. 9 examples.

Cassette #8--Approaches to Popular Music. What is popular music? Edward Lee and Graham Vulliamy explore popular music as culture and look at its aesthetics, as they trace the impact of Afro-American music on traditional classical European music to produce an entirely different musical form and discover that different musical traditions need to be evaluated against different criteria. Illustrations by the speakers themselves.

Cassette #9--From Cave to Cavern: The History of Percussion Instruments. Side One: James Blades shows the importance of rhythm to all cultures, and then traces the history of percussion instruments through the Middle Ages and Renaissance to the Classical Period. Side Two: How the nineteenth century demanded marked changes of color in the percussion section is shown, including the emergence of tuned percussion. Blades then brings the listener up-to-date with a consideration of the increased technical requirements which the twentieth century has made on old and new percussion



instruments. 10 examples.

Cassette #10--Islands in the Sun: The Story of Reggae and Calypso. Side One: Felix Cross traces the progression of music in the Caribbean from Rhythm and Blues to Reggae. Side Two: An outline history of the calypso form of music, ending with a demonstration of how a simple calypso tune can be composed and performed. 7 examples.

Cassette #11--A Jug of This: An Introduction to English Folk Music. Side One: Roy Palmer explores the history of English folk music, as well as its functions in ritual, work, and recreation. 8 examples. Side Two: Folk songs as an illustration and illumination of social history, dealing for example with love, marriage, and affairs. Palmer also recognizes our debt to the folk song collectors of the early twentieth century. Examples on both sides of the tape range from Elizabethan times up to the modern period. 7 examples.

Cassette #12--Instruments Around the World. Side One: Andy Jackson presents a collection of examples from musical instruments from around the world, including the quena (Andean flute), koto (Japanese zither), atumpan (talking drum from Ghana), duda (Hungarian bagpipe), didjeridu (Australian trumpet), and sitar. Side Two: As above, with gender (Indonesian metal xylophone), mbira (Zimbabwean linguaphone), sheng (Chinese mouth organ), peyote water drum, and hardanger fiddle (Norwegian folk violin).

CDs

DIGITAL TEST: 106 DIGITAL TESTS AND DEMONSTRATION TRACKS

CDPV/2
\$37.95

Disques Pierre Verany

After painstaking research and several trial pressings, here is the most complete and functional test package available. Created in the studios of Pierre Verany, with the collaboration of the French audiophile magazine *Compact*, the final product was submitted to the creators of the CD concept--Philips of The Netherlands. Their verdict: "a beautiful piece of work!"

Contents: CD #1, DEMONSTRATIONS--[1] Fireworks. [2] Rumanian folk music. [3] Bluegrass. [4] Guitar. [5] Contemporary music with brass and percussion. [6] Voice. [7-8] Ancient instruments. [9] Flute concerto. [10] Philharmonic orchestra. [11] Baroque organ. [12] Great symphonic organ. CD #1, TESTS--[13] Maximum cutting level. [14-15] Left/right identification and channel separation. [16-17] Frequency response 20Hz-20kHz. [18-32] Harmonic distortion measurements. [33-34] Signal-to-noise ratio measurement. [35-38] Analog de-emphasis circuit control. [39-42] Transient response on squarewave signals and tone bursts. [43-46] Audible differences in quantization: 16-, 15-, 14-, and 8-bit-encoded music. [47-48] Intermodulation by crosstalk. [49-51] Intermodulation distortion measurements. [52-56] Digital/analog converter overload effect.

CD #2, TESTS--[1-6] Variations of linear cutting velocity. [7-11] Variations of velocity/track pitch. [12] Return to normal parameters. [13-18] Variations of track pitch. [19-24] HF detection level. [25-38] Dropout tests. [39] Return to normal parameters. [40-43] Dropout size variations/minimum track pitch. [44-50] Ability to correct successive dropouts.

From France; two discs; 73:47, 50:00. Verany #PV88031/32 (AD124). 65-page French/English companion booklet included. Also available in Special CDPV/S elsewhere in this section.

COMPACT TEST: DEMONSTRATIONS AND TESTS CDPV/3 Disques Pierre Verany

\$18.95

Contents: MUSICAL TRACKS--[1] Steam train. [2] Big band ("Tribute to Benny," Walker Jazz Band). [3] Percussions ("Rhythmotom 1," Mamba Percussions Ensemble). [4] Paraguayan harp ("Pajaro Campaa," Ignacio Alderete). [5] Country music ("Rattlesnake," Banjo Express Ensemble). [6] Provence (southern France) music ("Bon Joseph, Écoute-Moi," Fleur de Rose Ensemble). [7] Nightingales ("Dawn on Saint John's Day"). [8] Organ and orchestra (Vivaldi: "Concerto in G Minor Op. IV No. 6," Munich Pro Arte Orchestra). [9] Harpsichord (Soler: "Sonata No. 99 in C Major: Rondo Pastoril," Jean-Marie Puli). [10] Baroque organ (Clerambault: "Suite du Premier Ton: Basse et Dessus de Trompette," Pierre Bardou). [11] Choirs (Poulenc: "The Face of Man: With Laughter for the Sky and Planets," Ensemble Vocal de Provence). [12] Ancient music (Alphonse le Sage: "De Grad'a Santa Maria," Polyphonia Antiqua Ensemble). [13] Romantic organ (Liszt: Fantasy and Fugue on "Ad Nos, Ad Salutarem Undam," Chantal de Zeeuw).

TECHNICAL TRACKS--[14] Locating of left and right channels; diaphony test. [15] Dynamics and noise. [16] Loudspeaker phasing. [17] White noise. [18] Pink noise. [19] Response curve of the equipment (sinusoidal signals). [20] Colorations and resonances; equalizer adjustment; loudspeaker testing.

From France; one disc; 57:39. Verany #PV784031 (AD100). 19-page French/English companion booklet included. Also available in Special CDPV/S elsewhere in this section.

OLD COLONY SOUND LAB

CDV TEST: HOW TO SET UP YOUR AUDIO-VIDEO EQUIPMENT

CDPV/4
\$18.95

Disques Pierre Verany

Contents: AUDIO DEMONSTRATIONS--[1] Philharmonic orchestra (Moussorgski/Rimski-Korsakov: "Une Nuit sur le Mont Chauve" [extract], Pays de la Loire Philharmonic Orchestra). [2] L'Épée Music Box (Planquette: "Corneville Bells"). [3] Gilardenghi barrel orchestra ("Traditional Italian Air"). [4] Frati cardboard coin-operated orchestra (Waldteufel: "Dolores"). AUDIO TESTS--[5] Identification signal to be heard on the left. [6] Identification signal to be heard on the right. [7] Filtered sound, in phase. [8] Filtered sound, out of phase. [9-28] Room resonance and speaker remoteness from walls (sound measuring signals): 1k, 16, 20, 25, 31.5, 40, 50, 63, 80, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800, 1k Hz. VIDEO TESTS--[29] Absolute white. [30] Absolute black. [31] Contrast control and adjustment (gray scale). [32] Color rendering control (color bar pattern). [33] Streaking and focusing (dot pattern). [34] Convergence and geometric distortion (black and white grid).

From France, in collaboration with Stéréo HiFi-Vidéo; one disc; 21:55. Verany #PV789032 (AV100). 23-page French/English companion booklet included. Please note that this disc has been designed to be read by all CDV players sold in Europe and manufactured to the European standard. It is not compatible with NTSC-standard devices such as those made in Japan, Canada, and the USA. Also available in Special CDPV/5 elsewhere in this section.

PIERRE VERANY TEST CD SET SPECIAL!

CDPV/5
\$69.95

Disques Pierre Verany

The complete Verany Test CD Set (CDPV/2, CDPV/3, CDPV/4), at a savings of \$5.90! From France; four disks, three booklets.

CD-1 COMPACT TEST DISC

CD1
\$45.00

CBS Records

The CBS Records CD-1 test disc is a highly accurate signal source specifically designed for those interested in making a full range of demanding performance measurements on CD players. Because of the convenient nature of the CD medium and high quality of the recorded signals, the disc is also suitable for use as a source for testing a variety of audio systems or components, including tape recorders, amplifiers, and speakers. All 16-bit digital audio test signals contained in the 21 tracks and over 71 minutes of playing time have been computer-generated and transferred in digital form to the CD. The latest knowledge and technology in digital audio engineering has been used to provide a comprehensive set of test signals in a format with user requirements in mind. This arrangement includes all Electronic Industries Association (EIA)-specified test signals, plus CBS Records enhancements which allow the concerned evaluator the ability to obtain even more critical performance data than required by the corresponding EIA measurement standard.

Contents: [1] Reference, L & R, 0dB, 1kHz. [2] Left separation, 0dB, 1k, 125, 4k, 10k, 16k Hz. [3] Right separation, 0dB, 1k, 125, 4k, 10k, 16k Hz. [4] Signal/noise, L & R, infinity zero w/o emphasis. [5] Dynamic range, L & R, 1kHz, -60dB w/o emphasis. [6] Frequency response, L & R, 0dB, 4, 8, 17, 31 Hz. [7] 61, 127, 251, 499 Hz. [8] 997, 1999, 4001, 7993 Hz. [9] 10,007; 12,503; 16,001; 17,989 Hz. [10] 19,997 Hz (also used for pitch error). [11] Sweep frequency response, 0dB, 5Hz, -22.05kHz. [12] De-emphasis error, L & R, 1k, 125, 4k, 10k, 16k Hz. [13] Intermodulation distortion (SMPTE, twintone), L & R, 80Hz + 7kHz, 11kHz + 12kHz. [14] Wow and flutter, L & R, 0dB, 3150Hz. [15] Access time, L & R, 0dB, 317Hz. [16] Squarewave, L & R, 0dB, 1002.27Hz. [17] Impulse and polarity test, L & R, 0dB. [18] Linearity, 997Hz, L & R, 0dB, -1, -3, -6, -10, -20, -30, -39.99, -49.97, -59.94, -70.31, -80.77, -90.31 dB. ADDITIONAL TEST TRACKS: [19] Linearity with dither, L & R, 997Hz, -70.31, -80.77, -90.31, -100 dB. [20] Fade to noise with dither, L & R, -80dB, 500Hz. [21] Monotonicity, L & R, 1102.5Hz, 10 LSB.

One disc; 71:00+. CBS #CD-1. 8-page companion booklet included.

TEST DISC II: MUSIC, SOUND EFFECTS, MIC TECHNIQUES, ANECHOIC, AMBISONICS, TEST SIGNALS

CDII
\$30.00

Hi-Fi News & Record Review

Produced by Martin Colloms and Trevor Butler, this comprehensive test disc offers a unique package of music tracks and test signals designed for both subjective and objective analysis of hi-fi systems or components. Although the technical section provides a uniquely comprehensive and up-to-date signal source for laboratory measurement of hi-fi equipment, this disc will be invaluable for even the most nontechnical enthusiast who wants a range of suitable material for setting up, evaluation, and comparison.

Contents: [1] Ambisonic and channel identification. [2] Spoken channel phasing. [3] Hodgson: "Base Desires." [4] The making of "Base Desires." [5] Louiss: "Blues for Klook." [6] Sousa: "Stars and Stripes Forever," The Wallace Collection. [7] Holst: "Neptune" from "The Planets," Philharmonia Orchestra. [8] Britten: "Aria Italiana," "Bourre Classique," from "Variations on a Theme of Frank Bridge," English String Orchestra. [9] Beethoven: "Coriolan Overture," Hanover Band. [10-18] Denon anechoic chamber music recording. RECORDING TECHNIQUES--[10] Mozart: Bars 1-18, Overture, "Le Nozze di Figaro," Minoo Civic Hall, Osaka. [11] "Le Nozze," with addition of Vienna Musikvereinsaal's reverberation. [12] "Le Nozze," with addition of Amsterdam Concertgebouw's reverberation. [13] "Le Nozze," with addition of Boston Symphony Hall's reverberation. MICROPHONE TECHNIQUES--[14] "Le Nozze," with omni/single pickup miking. [15] "Le Nozze," with single mic and time coherence. [16] "Le Nozze," with single unidirectional mic. [17] "Le Nozze," with multi-mic pickup. [18] "Le Nozze," with multi-mic and time coherence. [19] Handel: "Entry of the Queen of Sheba," Scottish Chamber Orchestra. [20] "Entry," London Festival Orchestra. [21] Big Ben. [22] Fenny poppers (cannonades). PRECISION SIGNAL GENERATOR TRACKS --[23-25] Balance and phasing. [26-39] Calibrated levels. [40-66] Spot frequency response. [67-69] Swept frequency response. [70-71] Signal/noise ratio test. [72] Impulse test, L & R. [73-74] Intermodulation test. [75-79] Pre-emphasis check. [80] Fade-to-noise test. [81-92] Noise signals. [93-95] Tape recorder test signals. [96] Monotonicity (10 levels). [97] 1kHz toneburst, L & R, 0dB. [98] 100Hz squarewave, L & R, -15dB. [99] 1kHz squarewave, L & R, -5dB.

From the United Kingdom; one disc; 73:51. HFN #015. 8-page companion booklet included.

STEREOPHILE TEST CD

CDSTPH
\$9.95

Stereophile

Produced by John Atkinson and Robert Harley, *Stereophile's* test CD contains channel identification and phasing tests, but not with the usual boring test tones or pink noise. Publisher Larry Archibald's dog Ralph provided a healthy bark for these tests. Perhaps the most interesting part of this disc is the microphone comparisons, for which *Stereophile* founder and *The Audio Glossary* author J. Gordon Holt reads from his 1963 article, "Why Hi-Fi Experts Disagree." Eighteen different mics are used in succession, and even those who are not amateur recordists will find the widely varying sounds of these professional recording mics highly educational.

Contents: [1] Reference tone, L & R, mono. [2] Channel identification. [3] Channel phasing. [4] Pink noise at -20dB, L & R, uncorrelated for 1:04 of 2:15. [5] "Why Hi-Fi Experts Disagree," mic comparison, mono. [6] E.E. Bagley: "The National Emblem," Nether Providence High School Band, mono. [7] Theodore Dubois: "Les Sept Paroles du Christ," Philadelphia Oratorio Choir, excerpt. [8] Maurice Ravel: "Chanson Hébraïque," absolute polarity test. [9] Armas Järnefelt: "Praeludium, Delaware Symphony Orchestra. [10] Frederic Chopin: "Scherzo in B-Flat Op. 31," piano. [11] Jerome Kern: "I'm Old Fashioned," acoustic guitar. [12] Bruce Dunlap: "Threedledum," guitar and double bass. [13] George Gershwin: "Summertime," soprano, *Stereophile* magazine's "The Lesley Test." [14] Robert Schumann: "Romance, Op. 94, No. 1," flute and piano. [15] "Romance, Op. 94, No. 2," flute and piano. [16] "Romance, Op. 94, No. 3," flute and piano, 128x oversampling A/D. [17] "Romance, Op. 94, No. 3," flute and piano, Sony PCM 1630 A/D. [18] "Romance, Op. 94, No. 3," flute and piano, ADC comparison. [19] J.S. Bach: "Concerto in D," organ. [20-31] 1/3-octave warble tone tracks for testing loudspeakers and rooms: -20dB; 20, 25, 31.5, 40, 50, 63, 80, 100, 125, 160, 200Hz, 1kHz.

One disc; 70:54. *Stereophile* #STPH 002-2. 15-page companion booklet included.

OLD COLONY SOUND LAB



AUDIO TEST CD-1: CDJAS 91 TEST SIGNALS FOR HOME AND LABORATORY USE *Japan Audio Society* \$31.95

An extremely well thought out package, this disc contains a number of tests not found on other test CDs, and the individual track numbers on each tone and test make it a pleasure to use. Although this disc was intended for testing various playback signal characteristics of CD players, it is also useful as a versatile sound source for testing numerous characteristics of tape decks, amps, speakers, and other components, as well as the acoustics of listening rooms. The contents of the disc were prepared under extensive scrutiny and approved by both the Technical Audio Research Committee of the Electrical Industries Association of Japan and the Technical Measurement Committee of the Japan Audio Society.

Contents: [1-4] Channel check signals. [5-7] 1kHz sinewave reference signals. [8-38] Spot sinewave signals, 20Hz-20kHz. [39-44] Sweep signals, 20Hz-20kHz. [45] Step signals, 4Hz-125Hz. [46-47] Double tones for measuring intermodulation distortion, 0dB, -10dB. [48] White noise signal, -20dB. [49] Pink noise signal, -20dB. [50-52] Weighted noise signals, -20dB: United States of America Standards Institute (predecessor to ANSI); International Electrotechnical Commission Publication 268-1; Electronic Industries Association of Japan Specification RC-7603. [53-82] 1/3-octave band noise signals, -20dB. [83] Band noise signal, 200Hz-800Hz. [84] Band noise signal, 100Hz-8kHz. [85] Electrical Industries Association/Institute of High Fidelity tone bursts, 1kHz. [86] Tone bursts, -10dB, 20Hz-11.025kHz. [87] Peep signals, tone bursts limited by humming window, -10dB, 20Hz-11.025kHz. [88] Raised cosine wave, -10dB. [89-90] Impulse signals, 0dB, L & R. [90] Starter's pistol, anechoic.

From Japan; one disc; 58:44. JAS #YDDS-2. 34-page Japanese/English companion booklet included.

AUDITORY DEMONSTRATIONS CDAC *Institute for Perception Research;* \$27.95 *Northern Illinois University;* *Acoustical Society of America*

In 1978, a set of auditory demonstration tapes was released by the Laboratory of Psychophysics of Harvard University. These demonstrations had been prepared by a team led by Professor David M. Green and were sponsored by a grant from the National Science Foundation. The tape set, which contained 20 recorded demonstrations on psychoacoustics plus an explanatory booklet, became so popular that all copies were quickly distributed and the set was no longer available.

In 1984, the Acoustical Society of America's Committee on Education in Acoustics requested T.D. Rossing and W.D. Ward to look into the feasibility of re-issuing the "Harvard tapes." The decision was made to update the demonstration material and to issue it on a high-quality sound reproduction medium. The Institute for Perception Research (IPO) in Eindhoven (The Netherlands) was engaged to produce the audio material. Both the Eindhoven University of Technology and the Philips Company, the joint sponsors of IPO, made manpower available for the project. Philips Polygram and Philips & DuPont Optical (PDO) agreed to handle

the digital tape mastering and the production of a CD. Northern Illinois University supported the project through a grant for improvement of undergraduate education, and the Acoustical Society of America agreed to provide further financial backing for the project. Among many, A.J.M. Houtsma, T.D. Rossing, and W.M. Wagenaars can be singled out for their production contributions.

Contents: [1] Canceled harmonics. [2-6] Critical bands by masking. [7] Critical bands by loudness comparisons. [8-11] The decibel scale. [12-16] Filtered noise. [17-18] Frequency response of the ear. [19-20] Loudness scaling. [21] Temporal integration. [22] Asymmetry of masking by pulsed tones. [23-25] Backward and forward masking. [26] Pulsation threshold. [27-28] Dependence of pitch on intensity. [29] Pitch salience and tone duration. [30] Influence of masking noise on pitch. [31] Octave matching. [32] Stretched and compressed scales. [33] Frequency difference limen (DL) or just noticeable difference (JND). [34-35] Logarithmic and linear frequency scales. [36] Pitch streaming. [37] Virtual pitch. [38-39] Shift of virtual pitch. [40-42] Masking spectral and virtual pitch. [43-45] Virtual pitch with random harmonics. [46-47] Strike note of a chime. [48] Analytic versus synthetic pitch. [49-51] Scales with repetition pitch. [52] Circularity in pitch judgment. [53] Effect of spectrum on timbre. [54-56] Effect on tone envelope on timbre. [57] Change in timbre with transposition. [58-61] Tone and tuning with stretched partials. [62-63] Primary and secondary beats. [64-67] Distortion. [68-69] Aural combination tones. [70] Effect of echoes. [71] Binaural beats. [72-74] Binaural lateralization. [75-79] Masking level difference. [80] An auditory illusion.

From The Netherlands; one disc; 64:55. Philips #1126-061. 93-page, extremely detailed and referenced companion booklet included.

DEMONSTRATION OF STEREO MIKING TECHNIQUE CDSM *Performance Recordings* \$21.95

Produced by James Boyk, Mark Fischman, Greg Jensen, and Bruce Miller, this disc allows you to hear not only the very different images produced by various mikings, but also how different types of microphones give different images with the same miking. Each miking occupies two tracks: the first identifies it and the second lets you hear it. This enables the second track to be used by itself for blind testing.

Contents: SPOKEN INTRODUCTION--[1] Title. [2] Description of sound source. [3] Placement of microphone arrays. [4] Image accuracy. [5] Variation of nominally identical arrays. [6] Differences in character of sound. [7] Sound variation, off-axis versus on-axis. [8] How best to use your own microphones. [9] Dynamic test of channel matching. [10] Miking not a science. [11] Introduction. EIGHTEEN MIKINGS (Principle, Geometry of Stereo Array)--[12-13] Condenser, cardioids at 90 degrees. [14-15] Condenser, cardioids at 120 degrees. [16-17] Condenser, hypercardioids at 90 degrees. [18-19] Condenser, M-S: cardioid plus figure 8. [20-21] Ribbon, M-S: two figure 8s. [22-23] Condenser, figure 8s at 90 degrees ("Blumlein"). [24-25] Condenser, figure 8s at 85 degrees ("Blumlein"). [26-27] Ribbon, figure 8s at 90 degrees ("Blumlein"). [28-29] Condenser, two omnidirectionals 6 feet apart. [30-31] Condenser, three omnidirectionals, 6 feet span. [32-33] Condenser, ORTF: cardioids at 110 degrees, 17 cm apart. [34-35] Condenser, NOS: cardioids at 90 degrees, 30 cm apart. [36-37] Dynamic, cardioids at 90 degrees. [38-39] Dynamic, cardioids at 120 degrees. [40-41] Condenser, two omnidirectionals 6 feet apart. [42-43] Dynamic, ORTF: cardioids at 110 degrees, 17 cm apart. [44-45] Dynamic, NOS: cardioids at 90 degrees, 30 cm apart. [46-47] Condenser, two figure 8s at zero degrees, 17 cm apart.

One disc; 19:18. Performance Recordings #PR-6-CD. Companion booklet included, which contains Quick-Start Guide, "About Microphones & Stereo" primer, complete transcript of spoken introduction, and computer graphics of microphone patterns.

OLD COLONY SOUND LAB

VIDEOS

"ELECTRONICS AND YOU"


VIDEO ELECTRONICS COURSES

UCANDO VCR Educational Products Company

These high-quality, computer-animated VHS videos are among the best we have seen, suitable for at-home self-instruction as well as for classroom use. In color. Also available in other formats--please inquire.

Purchasing options available:

- **VDVT201 PART 1--DC:** Series and parallel circuits; Ohm's Law; digital multimeters; converting series-parallel circuits into simple equivalent circuits; using the DMM to measure voltage, current, and resistance. 53:00. **\$34.95**
- **VDVT202 PART 2--AC:** Coils; transformers; capacitors; the difference between effective, average, peak, and peak-to-peak voltage; calculating values for coils and capacitors in series and parallel. 71:00. **\$34.95**
- **VDVT205 PART 3--SEMICONDUCTORS:** Basic semiconductor theory; 15 different devices; how diodes, phototransistors, FETs, SCRs, and other voltage-controlling devices are designed to perform specific tasks; how an IC is designed and built. 47:00. **\$34.95**
- **VDVT206 PART 4--POWER SUPPLIES:** Different sections of a PS; half-wave, full-wave, and bridge rectifiers; filter circuits; shunt, series, and current regulators; overvoltage protection circuits such as crowbar; troubleshooting power supplies. 55:00. **\$34.95**
- **VDVT207 PART 5--AMPLIFIERS:** Basic amplifier circuits such as Class A, B, C; operational amplifiers; amplifier use in audio, video, and testing equipment. 54:00. **\$34.95**
- **VDVT208 PART 6--OSCILLATORS:** Resonant LC tank circuits; LC, RC, crystal oscillators; Hartley, Colpitts, Ultra-Audion, collector-coupled, emitter-coupled, UJT relaxation, tunnel diode oscillators; multivibrator circuits. 54:00. **\$34.95**
- **VDVTXXX COMPLETE SIX-PART "ELECTRONICS AND YOU" COURSE,** as above, at a savings of \$29.75! **\$179.95**

 

BOTTLES: THE TUBE AMP VIDEO

Corax Productions

VDBOT

\$29.95

The tube has many qualities that make it perfect for audio amplification--low distortion, clear midrange and treble, extreme ruggedness, and tremendous surge-power ability, plus the maturity of a classic technology. Produced by Eric Barbour, this video is about tube amplification--types and brands, applications, and a user's manual for the care and feeding of "bottles." A great owner's reference, it deals with all the details of owning a vacuum-tube amplifier. Subjects covered include: the history of tube high-fidelity equipment; a short look at the history of tube guitar amps; speakers for tube amps; owner maintenance; modifications for tube equipment; a summary of common audio tubes; and safety considerations. The history section in the first half is especially interesting, showing many classic tube amplifiers and preamps from the late '40s right up through today. VHS, color/NTSC format, 85:00.

ELECTRONIC KIT BUILDING MADE EASY

Edward T. Dell, Jr.

VDETD

\$19.95

In careful production for several years, this striking 30-minute VHS video cassette introduces kit building techniques to newcomers to electronics. Narrated by Ed Dell of Audio Amateur Publications, the presentation takes the viewer step-by-step through construction of a simple two-way electronic crossover, explaining the concept in simple terms, defining the basic concepts of circuit action and component function. The advantages of electronic crossovers versus passive ones (used in most loudspeaker systems) are discussed. Basic tools, soldering, circuit board use, component mounting, wiring, layout, and drilling of the enclosure, as well as final assembly, are all demonstrated clearly. Although the demonstration project is used for upgrading speaker systems, the techniques are applicable for building almost any electronic project, whether from a prepackaged kit or parts and supplies purchased separately. Suggestions for other resources and where to find more assistance in the form of plans, components, kits, and literature complete the program. VHS, color, 30:00. IN PRODUCTION; PLEASE INQUIRE ABOUT AVAILABILITY.

PROFESSIONAL AUTOSOUND

INSTALLATION TIPS

Scosche

VDAEV2

\$19.95

This training video follows an autosound installation from beginning to completion, providing detailed "how-to" information which examines the subtle and not so subtle differences between a competent, professional-quality job and a "slap-shop" one. The format is light and easy to watch and follow. Topics covered include Pre-Planning, Front Speakers, Wiring Tips, Rear Speakers, Amplifiers, and Head Units. VHS, color, 27:00.

EIA/CEG CAR STEREO VIDEOS

Electronic Industries Association/Consumer Electronics Group

These videos offer an introduction to car stereo installation, with VDBIV oriented more toward setting up a shop and dealing with customers while VDPIV delves more into actual installation techniques. Features include: outfitting a shop; car stereo chassis styles and sizes; recommending a particular size; preventing noise problems; an after-installation checklist; and installation kits and how to get them. VHS, color. VDBIV: 25:49; VDPIV: 27:30.

Purchasing options available:

- **VDBIV Basic Car Audio Installations** **\$27.95**
- **VDPIV Professional In-Dash Car Stereo Installation** **\$27.95**
- **VDSIV Complete EIG/CEG 2-Video Set (VDBIV, VDPIV),** at a savings of \$3.95! **\$ 51.95**

OLD COLONY SOUND LAB

VINYL

SEVEN STEPS TO BETTER LISTENING

LSTR101

CBS Laboratories

\$8.95

Through easy-to-make tests and simple narrative, this 33 1/3-rpm LP will help you to blend electronic components, room acoustics, and the characteristics of your own ears into one well-tuned system for the enjoyment of all recorded sound. You will be able to assure yourself that your LP-playing equipment functions properly, as well as learn how to "tune" your player to your own hearing and to the acoustics of the room in which you are listening. Program notes by *Audio's* noted reviewer Edward Tatnall Canby. 1964.

Contents: [1] Left/right sound identification: proper placement and connection of speakers and/or console for true rendition of stereo sound image. [2] Loudspeaker connection: using a simple sequence of tones to determine proper speaker connections. [3] Loudspeaker balance: simple adjustment. [4] Tone control: adjusting the tone controls until pilot tones and test tones correspond. [5] Left/right separation: eliminating test tone blend to ensure origination at proper speaker. [6] Elimination of buzzes and rattles: detection and remedy methods. [7] Reduced record wear: tips and tests for peak pickup performance.

One vinyl LP with jacket. CBS Laboratories #STR-101. 16-page companion booklet included. Limited quantities available: TELEPHONE ORDERS ONLY, PLEASE.

Seven Steps
to Better Listening



DEALER DISCOUNTS AVAILABLE



OLD COLONY EASY ORDER FORM

QTY.	ITEM NO.	PRICE EACH	TOTAL
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____
<input type="checkbox"/> FREE CATALOG		SHIPPING	\$ _____
		TOTAL	\$ _____

NAME _____

COMPANY _____

STREET _____

CITY _____ ST _____ ZIP _____

DAYTIME TELEPHONE _____

PAYMENT BY:

CHECK / MONEY ORDER

MASTERCARD VISA

MC OR VISA _____ EXP. _____

SHIPPING:

USA: \$2 first item, \$.75 each additional.
 Canada: \$4.50 first item, \$.75 each additional.
 Overseas Surface: \$6 first item, \$.75 each additional
 Overseas Air: \$9 first item, \$.75 each additional.

OLD COLONY SOUND LAB

PO Box 243, Department E92
 Peterborough, NH 03458-0243 USA

24-Hour Lines
 Telephone: (603) 924-6371 or (603) 924-6526
 FAX: (603) 924-9467



Connect Muscle Wires™ to a battery or other power source and watch them contract in length up to five percent! Remove power, and they relax and are ready for millions more cycles.

Create direct linear action without heavy gears, coils, or motors. Use Muscle Wires in robots, models, planes, railroads — anywhere you need small, strong all-electric motion.

Get our new 96 page Book and moving Muscle Wire Sample Kit. It includes 20 cm of 50 μm, and 40 cm each of 100 and 150 μm diameter Muscle Wire (1 meter total), crimps and complete instructions — everything you need to get moving today!

Order Toll Free, 24 hours:

Mondo•tronics
800-374-5764

2476 Verna Court Phone: 510-351-5930
San Leandro, CA 94577 Fax: 510-351-6955

Q&A
What Are Muscle Wires?
Muscle Wires are highly processed strands of a nickel-titanium alloy called *nitinol*. At room temperature they are easily stretched by up to 5% of their length. When conducting an electric current they heat and return to their original "unstretched" shape with a force thousands of times their own weight.

How strong are Muscle Wires?
The force a wire pulls with varies with size, from 35 to 330 grams. For more strength, use several wires in parallel.

How fast can Muscle Wires activate?
They contract as fast as they are heated — as quickly as 1/1000 of a second. To relax, the wire must cool again. Rates up to several cycles per second are possible with active cooling.

Flexinol Muscle Wire Specifications


Wire Diameter	50 μm	100 μm	150 μm
Resistance	510 Ω/m	150 Ω/m	50 Ω/m
Contract Force	35 grams	150 grams	330 grams
Typical Current	50 mA	180 mA	400 mA

How much power do Muscle Wires need?
Power varies with wire diameter, length, and surrounding conditions. At room temperature typical currents range from 50 to 400 mA. Power levels can be higher, but once the wire has fully shortened, power should be reduced to prevent overheating.

What are the advantages of Muscle Wires?
Muscle Wires have many advantages over motors or solenoids including small size, light weight, low power, very high strength-to-weight ratio, precise control, AC or DC activation, long life and direct linear action.
These topics and dozens more are covered in detail in our new 96 page book, *Working With Shape Memory Wires*.

Book and Sample Kit only \$29.90
Plus \$4.00 P&H
CA orders add tax

 Courteous Service • Discount Prices • Fast Shipping
ALL ELECTRONICS CORP.
P.O. Box 567 • Van Nuys, CA 91408
INFRARED Remote A.C. SWITCH



This infrared remote control device lets you turn on/off lamps, appliances or other 120 Vac devices using an IR transmitter similar to the one on your TV or VCR. Originally designed for use with a hydromassage unit, these transmitters and receivers will apparently operate most A.C. devices with 2 prong non-polarized plugs. Not recommended for use with heaters. Requires a 9 volt battery (not included).

CAT# RC-1
\$9.95 each
2 for \$17.00

Electret MIKE

High efficiency, omni-directional, miniature electret condenser microphone element. Low current drain, good signal to noise ratio, operates on 2 to 10 Vdc. Ideal for telephones, tape recorders, noise-activated alarms and other applications. 0.39" dia X 0.31" high.
CAT# MIKE-10 85¢ each
200 pcs \$150.00 (75¢ each)

UV "Invisible" INK

When the ink dries the writing of these felt tip pens is visible only under a UV "black light". Originally for marking personal belongings in case of theft, these pens might also be used for writing secret messages or marking merchandise for inventory control. Large quantities available.
CAT# UVP 3 for \$1.00 - 100 for \$25.00

FLASH UNITS



NEW compact flash assemblies from a camera manufacturer. Operates on 3 Vdc. Measures 2 1/2" X 1 1/4". Ideal for use as a strobe, warning light or attention getter. Includes a hook-up diagram. CAT# FSH-1

\$375 each
10 for \$35.00
100 for \$325.00

OPTO SENSOR



TRW/Optron # OPB5447-2 IR emitter/sensor pair in rectangular package with 28" color coded leads. CAT# OSR-4

2 for \$1


Surface Mount Green LED

Surface mount LED chip. Clear when off, green when lit. Vary tiny - whole unit is 0.115" X 0.055" X 0.05" thick. 1mm (0.04") lens diameter. Gold-plated mounting surfaces for superior conductivity. CAT# SMLLED-2

10 for \$2

100 for \$18.00 - 1000 for \$140.00

Electroluminescent BACKLIGHTS

 

At last! A low cost electroluminescent glow strip and inverter. These brand-new units were designed to backlight small LCD TVs made by the Citizen Watch company. The inverter circuit changes 3 or 6 Vdc to approximately 100 Vac, the voltage required to light the glowstrip. Luminescent surface area is 1.7" X 2.25". The strip is a salmon color in its off state, and glows white when energized. The circuit board is 2.2" X 1". Glow strip and circuitry can be removed easily from plastic housing. Ideal for special lighting effects and backlighting. Two models available:


Citizen# 91TA operates on 3 Vdc CAT# BLU-91
Citizen# 92TA operates on 3-6 Vdc CAT# BLU-92

LARGE QUANTITY AVAILABLE \$350 each

10 for \$32.00 - 100 for \$275.00

12 VDC COOLING FANS

 Toyo Fan# TFD8012RXAL 12 VDC, 0.11A cooling fan. 3.175" square X 0.92" thick. Plastic frame. 7 blades. 11" long pigtail leads. CAT# CF-124 10 for \$50.00



\$6 each


PHOTORESISTOR

1K ohms light, 16K ohms dark. 0.182" dia. X 0.08" high. 0.18" long leads. CAT# PRE-7 2 for \$1.00 100 for \$45.00 - 1000 for \$400.00



TOLL FREE ORDER LINES
1-800-826-5432
CHARGE ORDERS to Visa, MasterCard or Discover

TERMS: Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (7 1/4, 7 1/2, 7 3/4 or 8 1/4%). Quantities Limited. NO C.O.D. Prices subject to change without notice.
CALL OR WRITE FOR OUR FREE 64 PAGE CATALOG
ALL ELECTRONICS CORPORATION
P.O. Box 567 • Van Nuys, CA • 91408

 

P-C-B ARTWORK MADE EASY I
Create and Revise PCB Art in a Flash

- * For IBM's & COMPATIBLES
- * HERC, CGA, EGA, VGA, SUPER-VGA
- * AUTO GROUND PLANES
- * DOT-MATRIX, LASER and PLOTTER ART
- * GERBER and EXCELLON OUTPUT
- * CREATE YOUR OWN FILMS with 1X ART
- * LIBRARIES * HELP SCREENS * MENUS
- * DOWNLOAD DEMOS from 24 hr. BBS!

- PCBoards - layout program 99.00
- PCBoards HP or HI PEN PLOTTER DRIVER 49.00
- PCBoards GERBER & EXCELLON Disk 49.00
- PCRoute - autorouter 99.00
- SuperCAD - schematic ...starts at 99.00
- Demo Pkg. - (demos of all 3 programs) 10.00

Call or write for more information
PCBoards

2110 14th Ave. South, Birmingham, AL 35205
1(800)473-PCBS/ (205)933-1122
BBS/ FAX (205)933-2954

NOW THAT YOU'VE SEEN OUR NEWEST TREASURE...

WHY NOT HAVE A LOOK AT THE REST?



The newest publication from the folks who bring you *Audio Amateur* and *Speaker Builder*

Glass Audio features the best vacuum tube designs for audio reproduction—past and contemporary. The new designs take advantage of improved components and control techniques that make the end results far superior to anything possible during the early days of audio's rebirth after World War II.

That's why tubes are having such a renaissance of interest as a perfectionist approach to good sound. And that's why tubes are reappearing in original equipment, in high end consumer and professional audio systems.

Published quarterly, *Glass Audio* will inform you about new innovations in the field and about parts sources. We'll also include modification projects, reviews of technical basics and regular columns such as Tube Troubles, Tube Tips and much more.

Subscribe today!



Audio Amateur THE JOURNAL FOR AUDIOPHILE CRAFTS

The innovative, independent audiophile journal for the thoughtful and capable music lover

Audio Amateur's articles deal with how audio equipment works, as well as how to build or modify it. Construction and modification articles are plentiful, supplying all needed parts, performance and assembly details. Exceptionally high quality designs.


Audio Amateur offers a number of features in each issue that abound with useful ideas. The *Letters* column is an open forum for problem solving and information interchange; *Classic Circuitry* reprints schematics of state-of-the-art gear—old and new; *Audio Aids* relates readers' experience with simple modifications to equipment and construction techniques. We also feature many useful and practical hi-fi accessories you can build to further your audio enjoyment.

For a small investment you can make your music system sound better—very probably a lot better.

Speaker Builder THE LOUDSPEAKER JOURNAL

The magazine that finally deals seriously with the art and craft of speaker building

 The *Art* of building a speaker is to optimize that mixture of design and engineering to balance all the parameters for the most beautiful sound possible. The *Craft* is knowing how and why. *Speaker Builder* gives you knowledge—from driver parameters and crossovers to woodworking—to develop and refine your techniques, and to get the most out of your system.



Speaker Builder helps you explore new designs with how-to construction articles, and can show you how to modify your old speakers and make them sound better than ever. Learn from our writers who turn abstract theory into practical approaches, and from the experience of other readers who have been down the road before you. *Speaker Builder* is the best investment you can make in your system—six issues per year filled with stimulating and exciting ideas.

GLASS AUDIO

- Two years, (8 issues) \$35
 - One year, (4 issues) \$20
- Canada add \$4 per year postage

AUDIO AMATEUR

- Two years, (8 issues) \$35
 - One year, (4 issues) \$20
- Canada add \$4 per year postage

SPEAKER BUILDER

- Two years, (12 issues) \$45
 - One year, (6 issues) \$25
- Canada add \$6 per year postage

NAME _____

STREET & NO. _____

CITY _____ STATE _____ ZIP _____

MC OR VISA NUMBER _____ EXPIRE _____

AUDIO AMATEUR PUBLICATIONS

PO Box 576, Dept. E92, Peterborough, NH 03458-0576 • (603) 924-9464 • FAX: (603) 924-9467

Answering machine for credit card orders only: before 9:00 a.m., after 4:00 p.m. and weekends. Have all information plus MC/VISA available.

ENGINEERS' RETREATS

One of the pleasures of living in our town of Peterborough, New Hampshire is not only the scenery of two rivers meeting downtown and the view of our surrounding mountains, but also a private, 400 acre farm that for nearly a century has been a retreat for working artists in literature, music and the plastic arts. The MacDowell Colony is strictly off limits to ordinary mortals all year long save for one August Sunday when a medal is conferred on a distinguished artist.

On that day anyone with the price of lunch can attend the ceremonies which are generally entertaining, informative and culturally refreshing. The Colony was founded because Edward MacDowell needed a quiet place to compose. His compositions are a pleasant addition to American music in the well-behaved late nineteenth century European-aping style. His wife Marian was the real energy behind the idea to turn a farm into a major retreat for artists.

Every quarter a new group of some forty persons come to Peterborough to take up residence at the Colony to work on some favorite project. They each have a cottage of their own in which to work. A central residence offers sleeping quarters and meals are provided. All this is supported by a growing endowment, built over the years from contributions by successful artists as well as interested individuals who believe in supporting the arts.

Over the years the foundation has grown, and some forty cottages were built one at a time, sometimes by an interested group's fundraising efforts, throughout the untouched 400 acres. Talented folks of every description have spent uncluttered, uninterrupted weeks with all their needs met without thought or care for life's necessities.

The place has so many memories scattered about its paths through the woods and hills that lists of what has been written, finished, or begun there reads like an honors list of America's artists. The "our town" I mentioned above is, in fact, Thornton Wilder's play, *Our Town*. Its drugstore setting, with its druggist narrator, was one Wilder visited often while at MacDowell. The book for *Porgy & Bess* was written at MacDowell by a couple who first met at the Colony, married, and returned to complete the classic there. Leonard Bernstein wrote parts of "West Side Story" during one of his many visits.

The value of MacDowell to American drama, art, music and literature is incalculable. A simple idea: give people with talent a place to work uninterrupted, and for an unbroken space of time and see what can be accomplished.

Why has it never occurred to anyone that American technology, which at its core is an imaginative process, needs a place of quiet for uninterrupted work—without telephones, faxes, business lunches or other distractions. I know that companies send selected people on sabbatical study leaves, sometimes for up to a year. Such leaves are generally spent in some academic venue, which these days is not exactly a retreat from the frenetic world we all seem to inhabit. It seems to me that thinking time is becoming more and more difficult to find in our hyper-enabled world where one can send faxes from a laptop to a sales staff of 20 flying at 32,000 feet over Kansas City.

While the MacDowell Colony equips its cottages with a variety of appurtenances including pianos, print-making gear, potter's wheels and photo labs, audio engineering types need only bring a laptop and a few books for a three month stint that might produce something innovative if only they had the time and opportunity. Breakfast is ready for hours each morning for colonists, cottages are within walking distance and lunch is delivered to each doorstep every noontime.

Every worthwhile human endeavor, it seems to me, requires such an environment for the best growth and development. I don't know what is happening these days at Bell Labs in New Jersey, but I devoutly hope that Judge Green's dismantling order hasn't forced AT&T into such a competitive mode that no one has the time or leisure to spend days or weeks just thinking. The largesse of the Bell Laboratories establishment when AT&T's "monopolistic status" gave it the "luxury" of pure research, has benefited every resident of this country in countless ways. Not the least of these being the transistor.

Many companies who design and market audio equipment have made remarkable amounts of money over the half-century of modern sound development's growth. But no one seems to be investing in the future of audio—or putting aside any "seed corn" for what is to come next. Lots of product development and market research but no one taking a larger look at the needs and the possibilities.

Can't more be done than merely getting the next new "break-through" ready for CES? Is audio forever to remain a hand-to-market annual cycle? And if we cannot find ways to start a MacDowell for audio technology, are the resourceful, promising people being given sabbaticals to do some original work and thinking about audio reproduction. I can think of several people whom audio has treated very well. Perhaps it is time for them to give something back.—E.T.D.

Published by Audio Amateur Publications

Editor/publisher: Edward T. Dell, Jr.

Editorial Offices:

305 Union St., P.O. Box 876
Peterborough, NH 03458-0876 USA

Telephone: 603-924-9464 (National)

or +1 (603) 924-9464 (International)

FAX: (603) 924-9467 (National)

or +1 (603) 924-9467 (International)

Advertising: Maureen E. McHugh

Telephone: (603) 358-3756

FAX: (603) 924-9467

Subscriptions: Katharine Gadwah

Elektronika USA

Post Office Box 876,

Peterborough, New Hampshire 03458

Subscriptions to *Elektronika USA* are available **ONLY** in the fifty United States, Canada, Puerto Rico, the Virgin Islands and those Pacific territories administered by the United States of America.

International Advertising:

Uitgeversmaatschappij Elektoor b.v.

P.O. Box 75

6190 AB BEEK

The Netherlands

Telephone: +31 46 38 94 44

FAX: +31 46 37 01 61

European Offices:

Elektoor BV

Postbus 75

6190 AB BEEK

The Netherlands

Telephone: 011 31 4638 9444

Telex: 56617 (elekt nl)

FAX: 011 31 4637 0161

Managing Director: M.M.J. Landman

Overseas Editions:

FRANCE

Elektoor sarl

Les Trois Tilleuls

B.P. 59; 59850 NIEPPE

Editors: D.R.S. Meyer

G.C.P. Raedersdorf

GERMANY

Elektoor Verlag GmbH

Susterfeld Strasse 25

5100 AACHEN

Editor: E.J.A. Krempelsauer

GREECE

Elektoor EPE

Karisakaki 14

16673 Voula—Athens

Editor: E. Xanthoulis

HUNGARY

Elektoor Elektronikai folyoirat

1015 Budapest

Batthyany U. 13.

Editor: Lakatos Andras

INDIA

Elektoor Electronics PVT Ltd

Chhotani Building

52C, Proctor Road, Grant Road (E)

BOMBAY 400 007

Editor: Surendra Iyer

ISRAEL

Elektoorcal

P O Box 41096

TEL AVIV 61410

Publisher: M. Avraham

NETHERLANDS

Elektoor BV

Peter Treckpoelstraat 2-4

6191 VK BEEK

Editor: P.E.L. Kersemakers

PAKISTAN

Electro-shop

35 Naseem Plaza

Lasbella Chawk

KARACHI 5

Editor: Zain Ahmed

PORTUGAL

Ferreira & Bento Lda.

R.D. Estef-83-ni, 32-1°

1000 LISBOA

Editor: Jeremias Sequeira

SPAIN

Resistor Electronica Aplicada

Calle Maudes 15 Entio C.

28003 MADRID

Editor: Agustin Gonzales Buella

SWEDEN

Electronic Press AB

Box 5505

14105 HUDDINGE

Editor: Bill Cedrum

UNITED KINGDOM

Elektoor Electronics (Publishing)

P.O. Box 1414

Dorchester DT2 8YH

England

Editor/Publisher: Len Seymour

Printed in the United States of America.

ISSN: 1051-5690



BAR GRAPH COUNTER

Startek International offers two new bar graph frequency counters. Small enough to fit in your shirt pocket, but with performance matching much larger units. Both contain a 2", 10-segment LED signal strength bar graph, which can function independently from the digital frequency counter, but will indicate the relative strength of an input signal at any frequency from 500kHz-3.5GHz.

The Model 15-BG's range is 1MHz-1.5GHz and the Model 35-BG's range goes up to 3.2GHz from 1MHz. The only performance differences are frequency bandwidth and the 35-BG's sensitivity above 500MHz. Resolution is 1kHz at 0.25 seconds, 100Hz at 2.5 seconds, and 10Hz at 25 seconds. The factory-installed internal NiCad battery pack and 110V AC adapter/charger are standard.

The Model 15-BG costs \$220; the Model 35-BG is \$265. Options include the TA-90 Telescoping Antenna for \$12 or the CC-90 Carrying Case for \$12.

Contact Startek International Inc., 398 NE 38th St., Ft. Lauderdale, FL 33334, (305) 561-2211, FAX (305) 561-9133.

CALL FOR PAPERS

The Fall Technical Conference of the SMPTE, to be held November 10-13, 1992 in Toronto, Ontario, has issued a call for papers on the theme "Images in Motion—The Second Century." Speakers will explore innovations in imaging and examine directions in established technologies and are welcome to use supplemental audio-visuals. Seminars and exhibits will accompany the event.

To participate, submit your name, company affiliations, address, and telephone number along with a 500-word synopsis by June 15, 1992, to SMPTE Headquarters, Program Coordinator, 595 W. Hartsdale Ave., White Plains, NY 10607.

ELECTRONICS SCENE

EDIT PCBs

Logical Systems Corporation announces EZ-View, part of the Gerber Toolkit that lets you edit ten layers of PCB artwork on screen. The Toolkit includes editing, printing and panelization facilities. EZ-View simplifies and reduces production costs by placing several layers on one sheet of film and using multi-design PCB panels. Aperture substitution automatically replaces oblong apertures with their rotated equivalent.

EZ-View is available for \$150 or as part of the Gerber Toolkit for \$250. The Toolkit includes EZ-View as well as GerberJet, the printing utility, and five other utilities.

Contact Logical Systems Corp., PO Box 6184, Syracuse, NY 13217-6184, (315) 478-0722, FAX (315) 475-8460.



CATENARY TWEETER

Polydax Speaker Corporation, a subsidiary of Audax Industries in France, introduces the TW 025 A 1" soft-textile dome tweeter. It is available in two models, with or without ferrofluid, and features a "catenary" profile. The shape of the dome profile resembles a chain suspended from two equidistant points in space. The faceplate design is streamlined, the voice coil is two layers, the diaphragm is replaceable, and the frequency range is 5kHz-20kHz. It has a sensitivity of 92dB 1W/1m and power handling is 50W RMS.

Contact Polydax Speaker Corp., 10 Upton Dr., Wilmington, MA 01887, (508) 658-0700, FAX (508) 658-0703.



PROTECT YOUR AMP

Ameritron announces their new QSK-5 T/R switch (\$349) for linear amplifiers, an easy-to-install external adapter, that adds full break-in operation to your high-power amplifier. The adapter is silent, functions six times faster than mechanical vacuum relays and can be switched over to your new amplifier for station equipment upgrading.

Hot switching of the amp is eliminated; TVI, RFI, key clicks, and damage to your linear amp is minimized. The Amp Saver feature turns off your amplifier's plate current between dots, dashes, and words.

Capable of handling 2,500W PEP and 2,000W in normal amateur service, and 750W on continuous modes like, RTTY, SSTV, and FM. Model QSK-5 is for 120V AC; Model QSK-5X for 240V AC.

For your nearest dealer, contact Ameritron, 921 Louisville Rd., Starkville, MS 39759, (601) 323-5869, (800) 647-1800, FAX (601) 323-6551.

CATALOG OF SPECIAL ITEMS

Global Specialties offers a 16-page color catalog featuring PC instrumentation and data-acquisition products. Virtual instruments, accessories, documentation, and program examples are backed by Global Specialties' 20 years' experience providing innovative test instrumentation.

For your free copy of the catalog, contact Global Specialties, 70 Fulton Terrace, New Haven, CT 06512, (800) 572-1028.

AUTO ANSWERING

Midland LMR offers a new, built-in, dual-mode Voice Storage/Message Relay option that enables Midland's Syn-Tech two-way mobile radios to be used as automatic answering machines and to extend the range of portable radios.

In Voice Storage Mode a user can record a status message before leaving the vehicle. The stored message is automatically transmitted when the mobile is called, while the user is away, and the caller can leave a message for the user to replay upon return.


In Relay Mode the low-power transmissions from the portable are temporarily stored and automatically retransmitted at the full power of the mobile when the channel is clear.

For details, contact Midland LMR, Marketing Department, 1690 N. Topping, Kansas City, MO 64120, (800) MIDLAND, ext 1690.

DATA CARD

Global Specialties announces a multi-function, digital and analog I/O card, the Model ADC-42. This card provides 24 digital inputs or outputs, two channels of analog output, 16 channels of single-ended analog input (or eight channels of differential analog input), and a programmable interrupt generator. The 12-bit AC/DC converter's speed is 12msec and input ranges can be selected from 10V, 5V, or 2.5V full-scale by on-board jumpers. The short card format occupies a standard I/O slot in IBM PC-compatibles.

 The Model ADC-42 costs \$595. For details, contact Global Specialties, 70 Fulton Terrace, New Haven, CT 06512, (800) 572-1028.



DESKTOP ENCODER

Communications Specialists Inc. announces the PE-1000 Paging Encoder, a desktop unit for small paging systems of up to 1,000 calls, that adds DTMF remote control capability as an option. By adding the new RC-1, the PE-1000 can be addressed via DTMF from a remote location. The unit costs \$224.95 and the RC-1 adapter is \$49.95.

For details, contact Communications Specialists Inc., 426 West Taft Ave., Orange, CA 92665-4296, (800) 854-0547, (714) 998-3021, FAX (714) 974-3420.

VIDEO PHONE IC CHIP

PMC Products announces a 48-pin, DIP IC, DRAM memory interface chip. The new chip provides still-frame, high-resolution, B/W video (under \$500) for *Phonvu* telephone systems. These systems are about the size of a paperback book and transmit still video images over standard phone lines in twelve seconds. Other features are: resolution 200 x 242.5; gray scale, 50 levels; display format, NTSC (B/W) with PAL available, and a 30Kbps data rate. Applications include teleconferencing, videofax, database retrieval, remote video surveillance, and storing video images on audio tape.

For details, contact PMC Products, 4742A La Villa Marina, Marina Del Ray, CA 90292, (800) 423-6377, FAX (213) 822-2257.

ELECTRONICS SCENE

AES CONFERENCE

The 11th Audio Engineering Society International Conference will be held in Portland, OR, May 29-31, 1992, at the Marriott Hotel. It will focus on a wide variety of measurement areas, including measurements on analog and digital electronics, acoustics, transducers and low-bit-rate coders. Participants include Bruce Hofer of Audio Precision, Cal Perkins of Harman Electronics, Bob Finger of Matsushita Electric, Louis Fielder of Dolby Laboratories, and Vance Dickason of *Voice Coil*.

For AES members, the registration fee is \$150, in advance, or \$225 at the door; non-members pay \$200 in advance or \$275 at the door. Student members pay \$50 in advance; or \$100 on-site. Advance registrations must be received by May 8th. Contact Audio Engineering Society Inc., 60 East 42nd St., New York, NY 10165-2520, (212) 661-8528, FAX (212) 682-0477.




DEMODULATE SIGNALS

Optoelectronics announces a self-tuning radio, for testing mobile voice and signal-tone FM transmitters. The model R-10 Communications Test Receiver offers a 30MHz to 1kHz carrier, 50Hz-5kHz demodulation, search and lock-on modes, AFC lock and indicator, built-in speaker and BNC jack output. The R-10 automatically determines and locks onto the strongest carrier signal within a 100 foot range.

For DTMF (dual-tone multi-frequency) and CTCSS (continuous tone-coded squelch systems), the audio output is evaluated on a frequency counter or oscilloscope with two modes of operation. Other features include squelch, audio gain, power and low battery indicators. Antenna input impedance is 50Ω; power is supplied by an internal 9V battery.

 For more information contact Optoelectronics, Inc., 5821 NE 14th Ave., Ft. Lauderdale, FL 33334, (305) 771-2050, (800) 327-5912, FAX (305) 771-2052.



BALANCED LINE RECEIVER

Analog Devices offers the SSM-2143 balanced line receiver that complements its companion SSM-2142, a balanced line driver. It's a fully integrated and balanced receiver system for audio and industrial designs requiring high immunity from EMI. Combined, these two units form a compact solution to driving and receiving audio signals over long, noisy cable runs.

Two gain options make the monolithic SSM-2143 flexible enough for applications requiring a gain of 1/2, where its input stage is designed to handle signals as large as +28dBu. A gain of 2 can be realized by reversing the input and reference connections. With a gain of -6dB, it offers 90dB common-mode rejection at 60Hz and 85dB at 20kHz.


For details, contact Analog Devices, Precision Monolithics Division, 1500 Space Park Dr., Santa Clara, CA 95052, (408) 562-7513.

FIBER OPTICS PRIMER

Industrial Fiber Optics announces Optical Voice Link, a kit that provides an introduction to the science of light transmission through optical fiber. The assembled kit has a transmitter module, for converting voice signals into light and a receiver module, for converting the collected light into an audio signal.

Operation requires two 9V batteries and no additional components. Available in assembled form (IF-OVL10A costs \$79.95) and unassembled (IF-OVL10 costs \$49.95). The kit includes printed wiring boards, switches, electronics, microphone, 8Ω speaker, 10' of plastic fiber cable, tutorial guide, and step-by-step assembly instructions.

 Contact Industrial Fiber Optics, PO Box 3576, Scottsdale, AZ 85271, (602) 731-8459.



COMB GENERATOR

The name of the test instrument described here is based on the frequency spectrum it produces. The circuit will be particularly valued by owners of (ex-surplus trade) spectrum analyzers, because it produces hundreds of harmonics of 1 MHz or 10 MHz, of which the first 45 or so have the same output level within 3 dB.

Design by J. de Belie

INSERTING a filter between the output of the comb generator and the input of a spectrum analyser allows you to ascertain, and, if necessary, adjust, the filter characteristic. Similarly, the comb generator allows the frequency characteristic of an ex-surplus trade spectrum analyzer to be checked.

by an ACL gate, IC2c, to make sure that the signal edges are sufficiently steep. The output of the buffer is loaded with an R-C network that results in 7.6-ns long 'low' levels of the 1-MHz (1 μ s) output signal. A further ACL gate, IC2d, is used to provide sufficient drive power at the HF output, K2. Capacitor

C19 in combination with resistors R13 and R14 provides a termination impedance of about 50 Ω .

The use of AC logic means that the duty factor of the output signal depends to a small extent on the supply voltage and the ambient temperature. Fortunately, this does not seem

Basic operation

A comb generator is basically a circuit that generates a very short pulse periodically. Its operation is predicted (or, if you like, confirmed), by Fourier analysis.

Assuming that a purely digital pulse is generated with a duty factor of 1% ($t_{on}/t_{off}=0.01$), the amplitudes of the harmonics are weighted to $(\sin x)/x$ (sine roll-off). This means that

- the amplitude of the first couple of harmonics will be 1% of that of the original pulse;
- the amplitude does not drop to:
 - 1 dB up until the 26th harmonic;
 - 2 dB up until the 37th harmonic;
 - 3 dB up until the 44th harmonic;
 - 5 dB up until the 55th harmonic;
 - 10 dB up until the 74th harmonic.


The attenuation will be infinite (in principle) at the 100th harmonic, and multiples thereof. In practice, the deviation from the theoretical model is small (for a change), in particular in the HF section of the present generator.

Circuit description


The recently introduced family of AC (Advanced CMOS) logic devices allows very fast pulses to be generated at relatively high output power levels. Here, the fundamental generator frequencies are 1 MHz (HF mode) and 10 MHz (VHF mode).

HF pulse generator

 With reference to the circuit diagram in Fig. 1, when switch S1 is set as shown, the VHF part of the circuit is disabled via gate IC2a. One section of dual decade ripple counter IC3 divides the 10-MHz clock signal by 10. The 1-MHz output signal is buffered



Here's something to put your hair in order! Comb-type output spectrum from DC to about 1 GHz (VHF mode).

 

 


Fig. 2. Double-sided printed circuit board design for the comb generator.

supply. Alternatively, you may want to fit the PCB into a diecast (Eddystone) enclosure, from which the BNC sockets protrude.

The unit must be powered by a regulated 15-V source. A 'classic' supply based on the 7815 will be adequate for this purpose. Current consumption is smaller than 50 mA.

Adjustment

The adjustment of the comb generator is straightforward, and involves only one trimmer. Connect a spectrum analyzer to the VHF output, and peak C12 for highest signal level. Lacking a spectrum analyzer, connect

COMPONENTS LIST

Resistors:

2	47 Ω	R1;R3
1	150 Ω	R2
2	100 Ω	R4;R6
1	68 Ω	R5
2	1k Ω	R7;R12
1	22 Ω	R8
1	2k Ω	R9
1	1M Ω	R10
1	10k Ω	R11
1	120 Ω	R13
1	82 Ω	R14

Capacitors:

1	1 μ F 15V tantalum	C1
2	10 μ F 25V	C2;C3
5	47nF ceramic	C4;C5;C7; C14;C17
1	10 μ F 16V	C6
2	150pF ceramic	C8;C11
1	1nF ceramic	C9
1	10nF ceramic	C10
1	100pF trimmer	C12
1	82pF ceramic	C13
2	39pF ceramic	C15;C16
1	15pF ceramic	C18
1	100nF ceramic	C19
1	1 μ F 16V radial	C20

Inductor:

L1 Made from 1-mm dia. (SWG20) silver-plated wire; for construction details see text.

Semiconductors:

1	BA482	D1
1	1N4148	D2
1	BSX20	T1
1	7805	IC1
1	74AC11000N	IC2
1	74HC(T)390	IC3

Miscellaneous:


2	BNC socket	K1;K2
	10cm RG58 50 Ω coax, velocity factor 0.6	
1	miniature on/off switch	S1
1	10MHz quartz crystal	X1
1	Printed circuit board	920003

an oscilloscope via a 10:1 probe to the collector of T1 (test point '1'). Adjust C12 for best sine shape and highest amplitude of the waveform. In most cases, this adjustment will be entirely satisfactory, although the trimmer may have to be set to a slightly larger capacitance afterwards to compensate the probe capacitance.

Finally, for advanced users: if you require a smaller frequency interval, change the divisor (IC3; VHF output), or (better) change the crystal frequency. In most cases, it will also be necessary to change the pulse duration appropriately; if this is not done, the output level will almost certainly drop. Note, however, that although increasing the pulse duration keeps the output power at the old level, it lowers the maximum usable frequency.

AD232 CONVERTER

The well-known ICL7106 A-D converter IC has been with us in many generations of digital multimeter. A special version of it, the ICL7109, offers the same accuracy, comes at a low price also, but sports a parallel interface instead of a 7-segment driver. The ICL7109 requires only a handful of components to build a versatile measuring box with an RS232 interface that is easy to manage thanks to some hardware tricks. Software for IBM PCs and compatibles is available to control this unit, which is basically a multiplexed A-D converter with an RS232 interface.

 

MAIN SPECIFICATIONS

- For every PC with a serial port
- 16-channel input multiplexer
- 12-bit A-D converter
- Powerful graphics-based menu-driven control software
- Based on inexpensive ICs
- Powered by PC

Design and software by Ing. B.C. Zschocke and A. Arnold

THE concept of the circuit is illustrated in the block diagram in Fig. 1. At the left are three input blocks with low-pass filter characteristics, marked HI', HI and LO. The

HI and LO blocks represent eight input channels, each of which can be selected individually by the block marked 'select'. The part behind the input selection circuitry

allows switching between the HI' (direct) input and the switchable inputs.

The A-D (analogue-to-digital) converter behind the input circuitry supplies its digital output data to a parallel-to-serial converter via a parallel bus. Unusually, the output information of the format converter is connected the CTS (clear to send) handshaking line of the RS232 port, rather than the Rx/D (received data) line. This arrangement results in a much simpler control of the measuring box than would be possible if the Rx/D line were used.

The circuit is powered by the RS232 port on the PC. The power supply block shown in the diagram provides a regulated output voltage of ± 5 V for the converter, and ± 12 V (approximately) for the serial interface.

Connection problems

The serial (RS232) interface is used here because the parallel (Centronics) interface can not furnish enough current to power the RS232 A-D converter. Furthermore, in most cases it is easier to find a free serial port on a PC than a free Centronics port, while the use of longer cables is also a boon. On the down side, a serial link is much slower than a parallel link, so that relatively slow ADCs can be used only. Fortunately this is not always a disadvantage, because slow but very accurate ADCs are inexpensive and widely available. Also, it is not always necessary to


 


Fig. 1. Block diagram of the RS232-controlled A-D converter.

 

constructed on separate printed circuit boards. Note that the entire circuit is powered via the RS232 link to the PC.

signal to return to high. This time can be used, for instance, to switch the multiplexer to the right channel.

The function of the bits in the datastream is shown in Table 1. The first clock pulse sets bistable IC5c-IC5d. This causes the RUN input to return to logic high, whereupon the A-D converter starts a new conversion cycle. The bistable is reset by a high level on the status line of IC1 (pin 2). The high level at the

serial input of the low-byte shift register ensures that the output returns to high (-12 V on the CTS line) after the value has been read.

The ICL7109

The ICL7109 is a low-cost 12-bit dual-slope A-D converter with additional polarity and overflow outputs. Figs. 3 and 4 shed light on

the operation of the digital part of the converter. First, Fig. 4: the upper signal represents the voltage at the capacitor (C3; the component numbers in brackets refer to the actual circuit). Below, some signals of the ICL7109, the internal clock, the clock signal of the output latch, the status output and the RUN/Hold input.

The conversion is started when a high level appears at the RUN input. During the

 


Fig. 3. Timing diagram of the data and command transfer protocol used.

conversion, the status output is held logic high. First, the integrator capacitor (C3) is charged with a current, I_c :

$$I_c = (U_{HI} - U_{LO})/R_3.$$

This takes 2,048 internal clock cycles (oscillator frequency divided by 58). Subsequently, C3 is discharged with a constant current, I_d , that is proportional to the input voltage:

$$I_d = U_{ref}/R_3.$$

During the discharging, the number of internal clock pulses is counted. The first leading edge of the internal clock that occurs after the capacitor voltage drops below 0 V causes the counter state to be transferred to the output register. Next, the status output changes from high to low, and so indicates the end of the conversion. Thus, we have:

$$\text{counter state} = 2,048 U_{in}/U_{ref}.$$

If the RUN input remains high during the conversion, a new conversion cycle is started after the auto-zero phase. Conversely, if RUN remains low, the new conversion starts 7 internal clock pulses after a new high level is present.

Figure 3 illustrates the handshaking of the ICL7109 with the external circuits, when the Mode and Sense inputs are held logic high. To the signals shown in Fig. 4 are added $\overline{\text{LOAD}}$, $\overline{\text{HBEN}}$, $\overline{\text{LBEN}}$ and the data lines. A low level on $\overline{\text{HBEN}}$ signals the presence at the output of the high byte of the counter state and the status signals Overrun and Polarity. The high byte can be copied on the leading edge of the $\overline{\text{LOAD}}$ signal. The subsequent transfer of the low byte is similar.

 


Fig. 4. ICL7109 analogue-to-digital conversion timing.

Table 1. Overview of bit functions in dataword (16 clock pulses)

Clock on RTS	Function
1	Overrun (OR)
2	Polarity (POL)
3	B12
4	B11
5	B10
6	B9
7	High
8	B8
9	B7
10	B6
11	B5
12	B4
13	B3
14	B2
15	B1
16	High

The input of the ICL7109 may be considered symmetrical within the bounds of the supply voltage, and has an input resistance of the order of a few giga-ohms. To make sure that sufficient charge reserve is available for the switches in the analogue part of the converter, the voltage source to be measured must be buffered by a low-loss capacitor. This means that capacitor C1 must be connected in parallel with the two inputs when measurements are made without the multiplexer. This is achieved by fitting jumper J4. For measurements on symmetrical voltages, the voltages (with reference to ground) at the two inputs must lie within the bounds of the supply voltage of the ICL7109. For asymmetrical measurements, the LO input can be tied to ground by fitting jumper J1. Resistor R1 prevents discharging via the measured voltage source.

More inputs, more channels

A multiplexer is provided for those of you who want to measure more than one voltage source. The multiplexer consists of IC7 for the selection of the Hi line, and IC8 for the se-

lection of the Lo line. Both are controlled by IC4, which counts the clock pulses on the Tx line. To select a channel, the software puts certain characters on the Tx line, such that the total number of clock pulses corresponds to the desired channel (see the programming example 'setchannel' listed in Fig. 5). The set baud rate is irrelevant, but the (rarely used) parity function must be taken into account. To ensure a fixed starting configuration, the counter is automatically reset to channel 1 after each conversion.

When the multiplexer is used, capacitor C1 must be disconnected from the input (J4 is not fitted), and the ground reference must be raised (J1 is not fitted). Capacitors C24-C31 and C36-C43 then take over the function of C1.

```

Uses Crt;

CONST
  PosOver=MaxInt;      { value for pos. overflow }
  NegOver=-MaxInt;    { ditto neg. overflow }

VAR
  SIOAdr:Word;        { to be assigned with 8250 base address }
                      { e.g. COM1: SIOAdr:=3F8 }
                      { COM2: SIOAdr:=2F8 }

{-----}
{ set channel for next conversion: }

      PROCEDURE SetChannel(Channel:Byte);
CONST
  PulseBytes:ARRAY[1..5] OF Byte=(0,14,51,21,85); { -> 1 - 5 pulses to TX }

      PROCEDURE WaitTx;
BEGIN
  { wait until transmit shift register is free }
  REPEAT UNTIL Port[SIOAdr+5] AND 32<>0;
END;

BEGIN
  IF Channel>5 THEN      { 2 characters required? }
  BEGIN
    WaitTx; Port[SIOAdr]:=PulseBytes[5];
    WaitTx; Port[SIOAdr]:=PulseBytes[Channel-5];
    WaitTx;
  END
  ELSE IF Channel>0 THEN { 1 character required? }
  BEGIN
    WaitTx; Port[SIOAdr]:=PulseBytes[Channel];
    WaitTx;
  END
  ELSE;                  { no pulse for Channel 0 }
END;

{Read value from shift registers. Call only when conversion is ready !!}

      FUNCTION ReadAD:Integer;
BEGIN
  inline(
$8B/$16/>SIOAdr/ { mov dx,[SIOAdr] ; DX at SIO-Port }
$83/$C2/$04/    { add dx,4 ; and on McdemCtrl there }
$BE/>0002/      { mov si,2 ; to switch address }
$33/$DB/        { xor bx,bx ; clear shift accu }
$B5/$10/        { mov ch,16 ; 14 data +2 dummy clocks }
$B1/$04/        { mov cl,4 ; shift to CTS }
$EC/            { @read:in al,dx ; send pulse via RTS }
$24/$FD/        { and al,0fdh ; RTS high }
$0C/$01/        { or al,1 ; DTR complementary low }
$EE/            { out dx,al ; set lines }
$51/            { push cx ; short wait loop, }
$B9/>$1F4/      { mov cx,500 ; to allow levels }
$E2/$FE/        { loop $ ; to settle }
$59/            { pop cx }
$0C/$02/        { or al,2 ; and restore }
$24/$FE/        { and al,0feh ; DTR complementary high }
$EE/            { out dx,al ; reset lines }
$51/            { push cx ; ensure }
$B9/>$1F4/      { mov cx,500 ; smallest pulse length }
$E2/$FE/        { loop $ }
$59/            { pop cx }
$80/$FD/$0A/   { cmp ch,10 ; pass dummy after 7 clocks }
$74/$0A/        { je @nuse }
$03/$D6/        { add dx,si ; DX to ModemStatus }
$EC/            { in al,dx ; read status bits }
$D2/$E0/        { shl al,cl ; shift CTS bit into carry }
$F5/            { cmc ; observe Inverting }
$D1/$D3/        { rcl bx,1 ; shift into result }
$2B/$D6/        { sub dx,si ; DX back to ModemCtrl }
$FE/$CD/        { @nuse:dec ch ; outer loop counter }
$75/$D4/        { jnz @read }
$D1/$EB/        { shr bx,1 ; shifted once too many }
$80/$F7/$10/   { xor bh,10h ; change sign }
$F6/$C7/$20/   { test bh,20h ; overrun set? }
$75/$0D/        { jnz @Over ; yes--> }
$F6/$C7/$10/   { test bh,10h ; polarity negative? }
$74/$16/        { jz @WErg ; no-->result o.k. }
$80/$F7/$10/   { xor bh,10h ; yes: clear Pol-Flag }
$F7/$DB/        { neg bx ; ..and form 2's complement }
$EB/$0F/$90/   { jmp @WErg }
$F6/$C7/$10/   { @Over:test bh,10h ; negative overrun? }
$75/$06/        { jnz @ONeg ; yes--> }
$BB/>PosOver/   { mov bx,PosOver ; constant pos. overflow }
$EB/$04/$90/   { jmp @WErg }
$BB/>NegOver/   { @ONeg:mov bx,NegOver ; constant neg. overflow }
$89/$5E/$FE);   { @WErg:mov @result,bx ; function result = BX }
END;

{ check if a valid result is available: }

      FUNCTION AD232_Ready:Boolean;
BEGIN
  AD232_Ready:=Port[SIOAdr+6] AND 16<>0;
END;

{ Initialisation of AD232. No timeout; endless loop created when AD232 is not found! }

      PROCEDURE AD232_Init;
VAR
  Dummy:Integer;
BEGIN
  Port[SIOAdr+4]:=2; { only DTR low }
  Delay(100);       { allow supply voltage to stabilize }

  REPEAT UNTIL AD232_Ready; { wait for first result }
  Delay(1);
  Dummy:=ReadAD;     { discard result }
END;

```

Fig. 5. A 'bare bones' control program for the converter (Pascal with in-line assembler).

COMPONENTS LIST

Resistors:

17	10MΩ	R1;R24-R39
3	22kΩ	R2;R3;R22
4	100Ω	R4;R5;R9;R14
6	100kΩ	R6;R10;R11;R15; R16;R19
2	180kΩ	R7;R12
2	390kΩ	R8;R13
1	270kΩ	R17
1	220kΩ	R18
1	68kΩ	R20
1	2kΩ	R21
1	27kΩ	R23
1	2kΩ multiturn preset	P1
1	1MΩ multiturn preset	P2

Capacitors:

19	100nF	C1;C14;C15; C18-C43
1	1μF	C2
1	220nF	C3
1	330nF	C4
2	4μF 7 6V3 tantalum	C5;C6
2	100pF	C7;C9
2	1nF	C8;C10
1	12nF	C11
2	220μF 16V radial	C12;C13
2	47μF 16V radial	C16;C17

Semiconductors:

11	1N4148	D1-D11
1	green LED	D12
1	BF245B	T1
1	BC550C	T2
2	BC560B	T3;T4
1	ICL7109	IC1
2	74HC166	IC2;IC3
1	74HC161	IC4
2	74HC02	IC5
1	LM324	IC6
2	4051	IC7;IC8

Semiconductors:

1	9-way PCB-mount female sub-D connector	K1
2	16-way pin header	K2;K3
1	3-MHz quartz crystal	X1
1	Printed circuit board	920010
1	Control program on disk	ESS1691

The multiplexers also allow symmetrical measurements to be made within the bounds of the converter's supply voltage. When asymmetrical measurements are performed, the inputs of multiplexer IC9 must be tied to ground, for instance, by fitting jumpers on header K3.

Unfortunately, the 4051 and the high converter input resistance of the converter introduce an offset voltage that differs from

channel to channel. Although the asymmetrical construction reduces the effect of the offset to a minimum, it can not be eliminated completely. For very accurate measurements, this means that the multiplexer must either not be used, or replaced by one with better specifications. For 'everyday' use, however, a correction in software of the measured voltage with the aid of a zero calibration is perfectly adequate.

RS232 level changer

The four opamps in IC6 are used as voltage level converters. Actually, they function as inverting switches, and so provide the inverting function defined in the RS232 standard. Diodes D1-D4 and resistors R10 and R15 limit the signal to +5 V and ground. R-C combinations R9-C8 and R14-C10 ensure that the input capacitances formed by IC5 and IC4


 


Fig. 6. Single-sided printed circuit board (track layout and component mounting plan) for the AD232.

 

need not charge via R10 and R15, and so reduce the effects of the relatively low slew rate of the opamps. Opamp IC6c is not strictly required for the correct function of the circuit. However, fit jumper J2 if you wish to feed the 'end of conversion' signal to your PC via the RxD line (for use with an appropriate interrupt routine).

Power supply

As already mentioned, the AD232 board is powered by the RS232 port of the computer it is connected to. The minimum requirement for this to be achieved is that the PC holds one RS232 line at +12 V and another at -12 V. Since the TxD line is at -12 V when it is not active, the +12 V supply will have to be supplied by the RTS and/or the DTR line. Diodes D6-D11 and capacitors C12 and C13 add and buffer the line levels to provide two discrete regulators with their input voltages. The voltage across the capacitors is also used to power the quadruple opamp. By omitting jumper JP3, the loading of the interface can be made as small as possible, if it can not supply enough current.

The voltage regulators in the ± 5 V supply are low-drop, high efficiency, types built from discrete components. The negative regulator consists of a pseudo-zener diode with a series transistor formed by T3 and a green LED, D12. Adjustment of the negative output voltage is not necessary because the A-D converter has a fairly large negative voltage range. Not so with the positive supply, where the pinch-off voltage of a FET serves as the reference. Although this voltage is reasonably stable, it has a fairly high device tolerance, and needs to be adjusted with the aid of P2. To save on parts, protection against overvoltage as a result of an incorrect adjustment is not provided. This means that the wiper of P2 must be turned to ground before calibrating the AD232 board.

The +5-V voltage must be adjusted with the nominal load connected.

Construction and adjustment

The single-sided PCB designed for the circuit is shown in Fig. 6. The construction will be mostly plain sailing. The multiplexers are built as separate units, and connected to the ADC proper in accordance with the component overlay. The HI' input serves for initial tests without the multiplexer. It is important to ensure adequate screening of all signal lines—remember, the high input resistance makes the circuit sensitive to noise. Hum suppression will be optimum when a quartz crystal of 2.969600 MHz is used. Unfortunately, this is not a standard frequency, whence the use of a 3-MHz crystal here.

The adjustment of the ADC by P1 depends on the application. In principle, the fine adjustment can be done by programming. The external circuitry around the ADC is designed for a maximum input voltage of about 400 mV. For other voltages, R3 must be changed:

$$R3 = U_{\max}/20 \mu\text{A}.$$

The reference voltage, U_{ref} , should be a little higher than $U_{\max}/2$, because the converter produces an overflow when $U_{\max} \geq 2U_{\text{ref}}$.

Connect the AD232 board to the PC, and advance preset P2 slowly until the positive regulator supplies +5 V.

The software package

Although the routines listed in Fig. 5 can be expanded into a full-blown control program for the AD232 board, you will be pleased to know that such a program is available on a disk supplied that can be ordered through our Readers Services (order code 1691).

This program is completely menu-driven, runs in colour, accepts mouse as well as keyboard control, and is written to run on IBM PCs and compatibles, from XTs to 486-based machines. A colour video card (EGA or VGA) is not strictly required, although you will miss a lot of the presentation graphics' power when you have monochrome video only.

Installation

The program can be run from floppy disk or hard disk. When it is run from floppy disk, make sure the write protection is removed, because the program writes a configuration file on the disk. An installation proper is not required—simply copy all files to your working disk, or to the hard disk.

Running the program

The AD232 control program is started by typing MULTI from the DOS prompt. First, go the (M)iscellaneous option, and select the serial port to which the AD232 board is connected. On leaving this menu, the voltmeter should work, indicating the voltages on all eight channels by means of horizontal bars and an absolute readout. (see Fig. 7). When fewer than eight channels are used, the screen is automatically enlarged.

Options (configuration menu)

The channel settings are not limited to switching on and off. Measuring ranges, multipliers and units (mV; V, etc.) can be taken into account in the graphics readout. The bar that indicates the magnitude of the measured voltage can be asymmetrical or symmetrical, and linear or logarithmic. Use 'symmetrical' for measured quantities that can go positive and negative. The menu also includes program options for offset calibration and a smoothing (delta) factor to stabilize the display.

Protocol

Apart from being shown on the screen in the form of horizontal bars, the measured values may also be sent to a file or an output device such as a printer. All output is in straight ASCII to a simple protocol, which makes further processing by other software easy.

Extras

All screen elements (text, highlighted text, borders, background) can be displayed in a number of user-selectable colours (VGA/EGA). Irrespective of your whereabouts in the program, a scientific (UPS compatible) desktop calculator and context sensitive help are always to hand. The help texts used in the program are stored in a file called MULTI.HLP, which is generated by adding WINHELP.TXT and MULTI-HLP.TXT on the diskette, as explained in README.DOC. All files and menus are in English. ■

GENERIC ARRAY LOGIC (GAL)

based on an original article by D. Gembris

In the development of Programmable Array Logic (PAL) devices, the design target was to make available to the user/designer as many 'free' logic gates on the device as possible. Lattice Semiconductor Corporation has further developed the device into the Generic Array Logic—GAL. In essence, both devices are electrically erasable CMOS memory ICs that provide the user with re-configurable logic and bipolar performance. This makes the GAL suitable for a wide variety of applications. Note that a PAL IC can be programmed only once, whereas a GAL IC can be programmed time and again. This makes the use of GAL ICs much more cost effective than PAL ICs.

The internal design of GALs is practically identical to that of PALs: both devices have a large programmable AND matrix to which a number of fixed OR gates may be connected. The connections between the AND and OR gates are made in silicon. In contrast, a PROM (Programmable Read Only Memory) has a fixed AND matrix and programmable OR gates.

The design

The availability of EEPROM (Electrically Erasable Read Only Memory) ICs was of fundamental importance in the development of GAL ICs. Apart from being erasable and re-programmable, the GAL ICs from Lattice are guaranteed for a minimum of 100 erasure/write cycles with data retention up to 20 years.

To further make the user's life easy, GAL ICs have provision for individual 'signature' of up to eight bytes. This may be used, for instance, to give the device a specific code.

Like PAL devices, GAL ICs can be protected against unwanted reading by actuating a specific cell (through the software). It must be said, however, that this protection is much more effective in PAL than in GAL devices. This is because the fusing of a link in a PAL IC is permanent, whereas in a GAL IC it can be erased, after which the device can be reprogrammed or read.

The logic diagram of a Type 16V8 GAL IC is shown in Fig. 1 and that of a Type 20V8 in Fig. 2. Each type has 8 programmable output logic macrocells (OLMCs) that allow the user to configure each output as desired. The figures in the type numbers refer to the design: the first, 16 or 20, is the number of inputs, and the second, the number of outputs.

The following data refer to the 16V8 (see Fig. 1). The eight inputs (pins 2–9) are available at the AND matrix in either original or inverted form and thus give rise to 16 columns. The other 16 columns are connected to the outputs, which are also inverted or non-inverted. There are thus a total

of 32 signals available.

When the IC is erased, there is no contact between the 64 rows (eight OR-gated rows per output) and the 32 columns. Therefore, changes at the inputs have no effect on the outputs. Only when programming is begun will the connections be restored. Each connection represents an AND gate.

Output Logic Macro Cells

The key to the universality of GAL ICs lies in the *output logic macro cells* (OLMCs). The design of such a cell is shown in Fig. 3. The distinct configuration of an OLMC is laid down in an *Architecture Control Word* (see Fig. 10). Bits SYN, AC0 and AC1(n) determine the status of the output of the cell. The SYN and AC0 bits take effect on all outputs

simultaneously, but the AC1(n) bit can be set for each output individually. Because of this, only two of the four possible configurations can be realized in a GALIC at the same time as shown below.

Normal output—SYN=1; AC0=0; AC1(n)=0 (Fig. 4).

Three-state output with disable via a product term and output return. Of the eight rows, only the lower seven are OR-gated, while the eighth determines whether the result will be shown at the output or not. SYN=0 or 1; AC0=1; AC1(n)=1 (Fig. 5).

Three-state output with disable, output return and register. The result will be at the output only when a clock pulse is applied to pin 1

 


Fig. 1. Logic diagram of the 16V8 GAL IC.

(CLK) and pin 11 is low. SYN=0; AC0=1; AC1(n)=0 (Fig. 6). There are two possible versions of this output (see Fig. 7)

Input: SYN=1; AC0=0; AC1(n)=1 (Fig. 8).

Programming

Apart from the supply line connections, each pin of a GAL IC has two different functions. Which function is active depends on whether the IC is being programmed (Edit mode) or operates in normal mode. The pin functions of both the 16V8 and the 20V8 are shown in Fig. 9: the inner ones give the Edit mode functions and the outer ones, the normal operating functions. In the Edit mode, which is set by applying 16.5 V DC to pin 2, the IC can be read, programmed or erased.

A GAL IC is internally divided into 64 rows, as shown in the row address map in Fig. 10. There are 36 unique row addresses available to the user when programming the device

Row addresses 0-31 each contain 64 bits of input term data. This is the user array where the custom logic pattern is programmed. Row 32 is the electronic signature word. It has 64 bits available for any user-defined purpose.

Rows 33-59 are reserved by the manufacturer and are not available to the user.

Row 60 contains the architecture and output polarity information. The 82 bits within this word are programmed to configure the device for a specific application—see Fig. 11.

When row 61 (security cell, see Fig. 10) is programmed, the enabling array is disabled, preventing further programming or verification of the array.

When row 63 is addressed during a programming cycle, the entire array and the architecture programming word are erased.

The outputs of the AND array are fed into an OLMC, where each output can be set individually to active high or active low with combination (asynchronous) or registered (synchronous) configurations respectively. A common output enable can be connected to all outputs, or separate inputs or product terms can be used to provide individual output enable controls.

The various configurations of the OLMC are controlled by programming cells SYN, AC0, AC1(n) and the XOR(n) polarity bits within the 82-bit architecture control word (see Fig. 10).

The SYN bit determines whether or not a device will have registered output capability or will have purely combinational outputs. It also replaces the AC0 bit in the two outermost macro cells, OLMC(12) and OLMC(19).

Architecture control bit AC0 and the eight AC1(n) bits direct the outputs to be wired always on, always off (as an input), have common OE control (pin 11), or to be three-state controlled separately from a product term. The architecture control bits also determine the source of the array feedback term through the FMUX, and select either combinational or registered outputs.

 


Fig. 2. Logic diagram of the 20V8 GAL IC.

 


Fig. 3. Output Logic Macro Cell of 16V8 GAL IC.

The five valid macro cell configurations are shown in Fig. 4-8. In all cases, the eight XOR(n) bits individually determine each output's polarity. The truth table associated with each figure shows the bit values of the SYN, AC0 and AC1(n) that set the macro cell to the configuration shown.

If a product term is allocated a 0, it is ignored during the OR gating. The product term censors PAL compatibility, even with older PALs that have fewer than 64 product terms. PAL listings are transformed into GAL listings.

The rows are addressed by means of an internal shift register. The transfer protocol is

Pin $P\bar{V}$: 1 = writing; 0 = reading.

RAGO-5: row selection.

\overline{STR} , SCLK, SDOUT:

reading - the shift register is loaded with an \overline{STR} pulse and the data are read by a clock SCLK at SDOUT;

writing - the data at SDOUT are clocked into the shift register with SCLK, whereupon the selected row is written into with a 10 ms \overline{STR} pulse.

Jump to RAGO-5 as long as no registers are being read or written to.

Compared with that of PALs, this protocol is trivial. This is one of the reasons that GALs have become inexpensive and this in turn has contributed to the wide use of these devices. Of late, some other manufacturers have also entered the GAL market, particularly SGS-Thomson and AMD. The latter bring out their GAL ICs under the name PALCE.

Row address map description

Details of the various row addresses are given below.

Electronic signature word

An electronic signature word is provided with every GAL 16V8 chip. It resides at row 32 and contains 64 bits of reprogrammable memory that can contain user-defined data. The signature data is always available to the user independent of the state of the security cell.

Architecture control word

All of the various configurations of the GAL 16V8 ICs are controlled by programming cells within the 82-bit architecture control word that resides at row 60. The location of specific bits within the architecture control word is shown in Fig. 10. The function of the SYN, AC0 and AC1(n) bits have already been explained. The eight polarity bits determine each output's polarity individually by selectively correct logic. The numbers below the XOR(n) and AC1(n) bits in the architecture control word diagram show the output device pin number that the polarity bits control.

Security cell

Row address 61 contains the security cell (one bit). This cell is provided on all GAL 16V8 devices as a deterrent against unauthorized

 


Fig. 4. Dedicated combinational output.

 


Fig. 5. Combinational output.

 


Fig. 6. Combinational output in a registered device.

 


Fig. 7. Registered active high or low output.

 


Fig. 8. Dedicated input mode.

 


Fig. 9. Pinout of the 16V8 and 20V8 – see text for symbol identification.

 


Fig. 10. Row address map block diagram.

 


Fig. 11. Architecture control word diagram.

copying of the array configuration patterns. Once programmed, the circuitry enabling array access is disabled, preventing further programming or verification of the array (rows 0–31). The cell can be erased only in conjunction with the array during a bulk erase cycle, so the original configuration can never be examined once this cell is programmed. Signature data is *always* available to the user.

Bulk erase mode

By addressing row 63 during a programming cycle, a clear function performs a bulk eras of the array and the architecture word. In addition, the electronic signature word and the security cell are erased. This mode resets a previously configured device back to its virgin state.

References:

1. "GAL Data Book," Lattice Semiconductor Corporation, 1988.
2. "Field Programmable Logic Arrays," *Elektor Electronics USA*, Oct. 1991, p. 41.
3. "Programmable Array Logic," *Elektor Electronics USA*, May 1985, p. 52.

PREVIEW

SPEAKER BUILDER

Issue 2, 1992

- 75W Two-way satellite speaker system
- Stable satellite swivels
- Caps for crossovers
- Two-way crossovers
- Constructing a bandpass enclosure
- Twenty foot dipole ribbon loudspeaker
- Review of *The Audio Glossary*

Mike's EXCELLENT Kits

Voice Scrambler, Motor Oil Tester, Versatile Electronic Crossover and more. All kits under \$35. Educator inquiries are welcome. Free Literature also describes **SpeakerCAD**, our low-cost speaker & crossover design software. **Decade**, 2302 5th St. NE, Salem, OR 97303, (503) 363-5143, FAX: (503) 399-9747

INTERMEDIATE PROJECT

A series of projects for the not-so-experienced constructor. Although each article will describe in detail the operation, use, construction and, where relevant, the underlying theory of the project, constructors will, none the less, require an elementary knowledge of electronic engineering. Each project in the series will be based on inexpensive and commonly available parts.

AUTOMATIC NICAD BATTERY CHARGER

Although it is bound to be replaced within a foreseeable period by environmentally safer types, the nickel-cadmium (NiCd) battery is still the most popular around when it comes to powering anything that is portable and electronic. This article describes a low-cost charger that gives the best possible protection to your NiCd batteries by incorporating a timer and two constant current sources.

by L. Pijpers


ONE of the most common causes of 'early death' of a NiCd battery is wrong charging. Both the charging time and the charging current are critical, and often not observed in inexpensive chargers, which appear to work all right when used with new NiCd batteries. In the long run, however, the batteries seem to lose power, and suddenly, often within days, give up the ghost. On investigating such chargers, they often have a current source with poor regulation characteristics. It also happens that they lack a timer, in which case you (the user) are to blame for forgetting to turn the charger off after the recommended charging time.

The present charger is fully automatic in that it provides a current sources that can be geared to the battery type, and a fairly accurate timer offering three charge periods with automatic switch-off. Both provisions serve to prevent any risk of overcharging.

Practical realisation

The circuit diagram, Fig. 1, shows that the charger consists of three parts: a power supply, a clock circuit, and two current sources. Two identical current sources are used to enable the charger to charge up to 12 batteries at the same time.

The power supply is as simple as it could be. The circuit is powered by a mains adapter with a direct output voltage of about 15 V. This voltage is fed directly to the two current sources. A voltage regulator, IC3, supplies a regulated supply voltage of 10 V for the clock (timer) circuit.

 

 


Fig. 1. Circuit diagram of the NiCd charger.

The clock circuit is formed by two ICs Type CD4060. As shown insert in the circuit diagram, the 4060 contains an oscillator and a 14-stage ripple counter, which is essentially a chain of 14 bistables, each of which divides by two. The oscillator section on board the CD4060 is only used with IC1. Capacitor C3 and resistors R1-R4 are external parts required to make the oscillator operate. The components that determine the oscillator frequency are C3 and the resistor connected to pin 10 of the CD4060. The circuit diagram shows that we have a choice of three oscillator frequencies, which, after dividing, result in an equal number of charging times.

If you would calculate the CD4060 oscillator frequency on the basis of the component values given, you may wonder why this is so high. Could it not be made lower, so that fewer dividers are required for the same charging time? The answer is negative, because a low-frequency oscillator based on the CD4060 is far less stable than a high-frequency one. This is mainly owing to the loss of the timing capacitor (C3), which would

take rather unwieldy values were the oscillator designed to work at a low frequency (say, 10 Hz). Also, low-loss large value capacitors are expensive and difficult to obtain. Briefly, an extra CD4060 solves this problem elegantly, and will not cause too large a hole in your pocket.

Given the oscillator frequency, a total of 24 dividers is necessary to arrive at the three possible charging periods of 24 hours, 14 hours and 5 hours. The total divide factor is, therefore, 2^{24} . Since a CD4060 contains only 14 dividers, two of these ICs are used here, the 'slowest' output of the first IC1 being connected to the clock input of the second (IC2).

To make sure that the charging process stops after the predetermined time, output Q9 of IC2 is connected to the clock input of IC1 via diode D2. When output Q9 of IC2 goes high (after 2^{24} oscillator periods), the oscillator is disabled, which causes the current state of all dividers to be 'frozen' until push-button S1 is pressed.

When S1 is pressed, the reset inputs of the two ICs are taken logic high, which resets all

dividers to zero. Evidently, since we do not want to start at an undefined time in the charging period, IC1 and IC2 must be reset also, when the charger is first switched on. The power-on reset circuit is formed by capacitor C5 and resistor R5. During the charging time of the capacitor, the reset inputs of the CD4060s are held high briefly after switching the unit on. This ensures that the clock always starts to count from zero.

The current sources

The moment the clock is reset, output Q9 of IC2 goes low to signal that the batteries may be supplied with their charge current. This signal is processed via transistor T1. Since the Q9 output is 'low', a base current is allowed to flow. Consequently, the collector of T1 will swing to a level virtually equal to the emitter voltage (approx. 10 V). This voltage enables a current to flow through the LEDs via R7 and R8. At the same time, a part of the current is sent into the base of the transistors connected in parallel with the LEDs. The resulting emitter current supplied by T2 and T3 is the charge current for the battery. Actually, the charge current is the sum of the (small) base current and the emitter current. The value of the emitter current depends on the value of Rx1 or Rx2 and the threshold voltage of a red LED.

Referring to the circuit around T2, the base of the transistor is held at a fixed voltage of about 1.6 V. The base-emitter junction of the transistor then acts as a conducting diode, and it is readily seen that the emitter will be at about 1.0 V (1.6 V-0.6 V). This value is fixed because it is derived from the forward drop across diodes, and therefore

Table 1. Dimensioning the current sources in accordance with the battery type and the charging period.

	Normal (14 hours) and long (24 hours)		Fast (5 hours)	
Penlight	45 mA	22Ω/0.25W	147 mA	6.8Ω/0.25W
Baby	179 mA	5.6Ω/1W	455 mA	1.8W/1W
Mono	370 mA	2.2Ω/1W	1 A	1Ω/3W *
9-V PP3	10 mA	100Ω/0.25W	30 mA	33Ω/0.25W

* or 2 x 2.2Ω/1W in parallel

 


Fig. 2. Suggested component layout on UPBS-1.

causes a fixed voltage across Rx1. This, in turn, results in a constant current. The charge current is supplied by the transistor, and the current through the base-emitter junction gives rise to a collector current whose value causes a voltage drop of 1 V across Rx1 (again, to be precise, the voltage across Rx1 is the result of the base current and the emitter current).

Should the current through Rx1 become larger (for whatever reason), the voltage across this resistor rises, and so reduces the base-emitter voltage. This can only happen when the base current, and with it the collector current, is reduced accordingly.

From the above it can be deduced that the value of resistor Rx is calculated from

$$R_x = 1 \text{ V} / I_{\text{charge}}$$

As indicated in the circuit diagram, the maximum number of 1.5-V NiCd batteries that can be charged simultaneously via one current source is six. More is not possible because the total battery voltage would then be so high that the current sources become unstable (remember, the input supply voltage is about 15 V). For instance, when 9 batteries are connected in series, they supply more than 13 V, to which must be added the voltage across Rx. This gives a total of more than 14 V, leaving only 1 V for the collector-emitter junction of the series transistor. This is a value that can not be achieved or guaranteed even when the transistor is driven with the maximum base current. Hence, the current source will fail, and the output current drop.

COMPONENTS LIST

Resistors:

1	47k Ω	R1
1	27k Ω	R2
2	10 Ω	R3;R6
1	1M Ω	R4
1	100k Ω	R5
2	1k Ω	R7;R8
Rx1;Rx2: see Table 1		

Capacitors:

2	1 μ F 40V radial	G1;C2
2	100nF	C3;C4

Semiconductors:

2	1N4148	D1;D2
2	red LED	D3;D4
1	BC557B	T1
2	BD241	T2;T3
2	CD4060	IC1;IC2
1	7810	IC3

Miscellaneous:

1	SPST push-button	S1
1	Printed circuit board	UPBS-1
1	Mains adapter 15V DC out	

A useful feature of the charger is that the LEDs go out when the battery is disconnected. This happens because the collector current is then interrupted, leaving only the base current to flow through Rx1. This causes a voltage drop that is much smaller than 1 V, so that the base voltage drops below the minimum level at which the LED lights.

Charge current and time

As already mentioned, resistors Rx allow us to determine the charge current, while the charge period is selected by connecting the appropriate resistor to pin 10 of IC1.

If you have a set of brand new batteries, it is best to give them an initial charge period of 24 hours (connect point A to pin 10). When the batteries have been used for some time, the charge period is reduced to 'normal', or 14 hours (B to pin 10). The 5-hour

period (C to pin 10) is used only if the battery type is suitable for fast charging.

The recommended charge current depends on the type of battery, and is often printed on it. The associated values of Rx are listed in Table 1 for 'long', 'normal' and 'fast' charging. Note that fast charging is not possible with all batteries; when in doubt see the battery specifications, or ask your supplier.


Soldering and testing

The NiCd charger is not difficult to build. Figure 2 shows a suggested components arrangement on universal prototyping board size '1' (UPBS-1), which is available ready-made through our Readers Services. Start the construction by fitting the wire links. Use insulated wire for the longer ones, and uninsulated wire for the shorter ones. Proceed with fitting the IC sockets, the resistors and the capacitors. The semiconductors are mounted last. Make sure you mount the diodes and the transistors the right way around. Lastly, insert the ICs into their sockets, also observing the orientation.

After a close inspection of your solder work, the completed circuit is ready for testing. First, check the current sources. Connect a battery pack in series with an ammeter. The LED in the current source used should light. Check this on the other source also. Measure the current, and check it against the relevant value from Table 1.

Next, check the operation of the timer. Temporarily move the wire to pin 3 of IC1 to the test point marked 'TP'. This shortens the charge period by a factor 1,024, so that the original charging periods of 24 hours, 14 hours and 5 hours are reduced to 84 seconds, 49 seconds and 18 seconds respectively, which are easily checked with a watch. If they are correct, return the wire link to its original position.

 The charger may be built into a suitable plastic enclosure. A rotary switch may be worthwhile if the current selection (value of Rx) needs to be changed often. Similarly, a switch may be used to select between the three charging periods. ■



SCIENCE & TECHNOLOGY

UNDERSTANDING WAVEFORM HARMONICS

by Dr K. A. Nigim

Many is the time when a strange, unexpected or distorted waveform appears on your oscilloscope screen. A lot of head scratching and book searching usually needed to solve the mystery. However, these days, with the rapid advances in Computer Aided Engineering (CAE) software, only a few steps or drag and click with the mouse attached to the computer are required to give you the answer instantly.

Among the easy electronic circuit analyser software available at moderate cost and not too complex is the Micro-cap III electronic circuit package (about £120 or \$200 student version). The program is exceptionally easy to operate in entering the electrical/electronic circuit into the PC (AT with math co-processor advised). Simulation is performed on the circuit with realistic results. A feature included in the package is Fourier Analysis, which evaluates the discrete Fourier transform of many distorted waveforms.

It is not the aim of this article to focus on the software, but rather use its programming facility to demonstrate and simplify the theory behind waveform harmonic content.

Background

Fourier analysis is the mathematical ground for analysing the periodic or repetitive (and perhaps distorted) waveforms. Fourier theory simply breaks the waveform into several ideal sinusoidal waves that each has its own period and amplitude.

Consider the waveform shown in Fig. 1a. It is said to consist of the two ideal waves shown in Fig. 1b. The first large wave is called the fundamental component and has an amplitude of, say, 100% at a frequency of 50 Hz. The second, smaller, wave is called the third harmonic with an amplitude of 30% at a frequency of 150 Hz.

In general, any periodical or repetitive waveform is defined by:

repetitive wave = DC component (A_0) + fundamental component (F_1) + harmonics (E_3)

In Fig. 1, the waveform is represented mathematically by:

$$e_r = A_0 + A_1 \sin \omega t + A_3 \sin 3\omega t.$$

If $A_3 = 1/3 A_1$, the distorted wave is said to have 30% third harmonic.

Mathematically, any periodical wave can be represented in the form:

$$Y(\omega t) = A_0 + A_1 \sin(\omega t) + A_2 \sin(2\omega t) + \dots + A_n \sin(n\omega t) + B_1 \cos(\omega t) + B_2 \cos(2\omega t) + \dots + B_n \cos(n\omega t),$$

where

A_0 is the direct (constant) component;
 $A_1 \dots A_n$ is the fundamental and odd harmonic components;
 $B_1 \dots B_n$ is the fundamental and even harmonic components.

Odd components exist when the wave is shaped by identical positive and negative cycles, that is, symmetrical around its axes. Even components occur when the wave is shaped by non-symmetrical half cycles.

Many CAE software packages present the wave by its vector form, which is then plotted in two informative scales. The first scale gives the magnitude and phase angle of the discrete harmonic components shaping the waveform. The second scale gives the cosine and sine values of the discrete harmonics. Both scales are related and either scale will be sufficient to determine the ex-

tent of distortion. Mathematically, these scales are represented as follows.

$$Y(t) = A_n \sin(n\omega t) + B_n \cos(n\omega t) = Y_n \sin(n\omega t + \Phi_n)$$

$$Y_n = \sqrt{A_n^2 + B_n^2} \Rightarrow \text{magnitude}$$

$$\Phi_n = \arctan\left(\frac{B_n}{A_n}\right) \Rightarrow \text{phase}$$

The terms A_n and B_n can be found from


$$A_n = \frac{1}{\pi} \int_0^{2\pi} Y(\omega t) \sin(n\omega t) d(\omega t)$$

$$B_n = \frac{1}{\pi} \int_0^{2\pi} Y(\omega t) \cos(n\omega t) d(\omega t)$$

The DC component, if present, is given by:

$$A_0 = \frac{1}{2\pi} \int_0^{2\pi} Y(\omega t) d(\omega t)$$

 But wait. Do we really need to go into inte-



gration and vector calculations to understand waveform distortion? Relax, not in the 90s. By using software available on the market and, of course, basic practice in electronic circuit analysis, it is quite possible to analyse almost any waveform and in effect produce the proper optimally designed system and this could be by introducing filters or by modifying the control concept.

Sinusoidal waves

In this section, several AC shaped waves, produced by a rectifier or phase-controlled power device, are presented and their harmonic content is simplified.

The ideal or smooth waveform is the sinusoidal wave that is produced by large generators in power stations. Figure 2 shows its waveform and its Fourier analysis is presented in the shape of the harmonic magnitude and the phase angle. The cosine and sine terms discussed in the previous section are plotted at the right. The analysis shown is the screen printout of the Micro-cap III software Fourier analysis section.

It can be seen from Fig. 2 that the wave contains no DC nor any sort of harmonic, either odd or even. Thus, the fundamental component dominates the wave shape.

The absence of distortion means that no filtering is required and that all the generated energy is effectively transferred to its destination. Although such pure waveforms exist along the electrical power lines, they may not be so pure any more by the time they reach domestic or industrial power outlets, because the mass of electrical and electronic equipment connected to these outlets nowadays generates a myriad of spurious frequencies that are transferred to the power lines. One apparatus that is very sensitive to impure mains power is the computer, which is why a power conditioner or UPS is normally recommended for its protection.

Selected practical waveforms are compared with the ideal wave in Table 1.

Wave I lists the ideal wave with its clear position of transmitting faithfully 100% power to the load without any distortion.

Wave II shows a phase-controlled AC source as found in many light-dimmer circuits using bi-directional semiconductor devices to produce the desired variable AC source as the one shown. For a 50% control ratio, that is, half the power transmitted, the print screen of the Fourier analysis shown in Fig. 3 reveals a handful of harmonics despite the fact that only half the power is transmitted. Practically, the level of harmonics can be neglected as long as its magnitude does not exceed 20% of that of the fundamental component.

It is important to realize what this distortion might cause. High-frequency, high-level harmonics cause excessive heat loss and disturbance in the performance of the controlled system. All industrial and domestic systems are designed to operate from the ideal supply wave shape and frequency. If a mains supply with a high content of harmonics is used to

	I	II	III	IV	V	VI
						
dc	0	0	63.5	150	70	150
Fund.	100	100	100	100	100	100
2	-	-	42	20	37	18
3	-	54	-	8	23	-
4	-	-	8	-	17	27
5	-	18	-	-	14	90
6	-	-	-	-	18	27
7	-	18	-	-	9	-
8	-	-	-	-	-	-
9	-	10	-	-	-	23
10	-	11	-	-	-	63

Table 1. Fourier analysis of 'sinusoidal' waves.

920052-23

 


Fig. 2. Sinusoidal wave (ideal shape).

 


Fig. 3. Phase-controlled AC wave.

 


Fig. 4. Half-wave rectified wave.

 


Fig. 5. Full-wave rectified wave.

 


Fig. 6. Controlled (full) rectified wave.

 


Fig. 7. PWM rectified wave.

power, say, a universal motor such as hand drill or food mixer, the motor is faced with several AC supply signals at high frequencies and at different phase angles. This causes a good deal of extra heat in the motor windings, noise and a drop in efficiency.

More high-level harmonics contained in the wave cause excessive radio interference and requires wide-band filters. Moreover, when a complex power source is supplied across a circuit containing inductance and capacitance, it may happen that the circuit resonates at one of the harmonic frequencies, which is called selective resonance. It is es-

sential, therefore, to include chokes or more complex filters or change the power source, both of which add to the final cost of the product.

Wave III is a half-wave rectified wave that has a 61% DC level (amplitude/ π) and a handful of odd harmonics. Simply connecting a capacitor across the load is normally enough to reduce the harmonics to an acceptable level. The Fourier analysis is plotted in Fig. 4.

Wave IV is a full-wave rectified wave. Its DC level is 150% of the fundamental, that is

twice amplitude/ π and, again, a handful of odd harmonics that are, however, of a lower level than those in the half-wave rectified wave. Again, a capacitor across the load will reduce the harmonic level substantially. The Fourier analysis is plotted in Fig. 5.

Wave V is a full-wave rectified wave under phase control, resulting practically in a variable DC source. At a 50% control ratio, the DC level is 67% and the harmonic content is worse than in *Wave III*. The Fourier analysis is plotted in Fig. 6. Although this yields a variable DC source, there is a problem in the filter selection: the smoothing capacitor chosen must be capable of by-passing high frequencies up to five times the supply frequency.

Wave VI is produced by pulse-width modulation (PWM) techniques to generate a variable DC source. Depending on the rate of on/off switching, the harmonic content rises alarmingly, indicating the importance of well-designed filter elements for a wide range of frequencies. The Fourier analysis is plotted in Fig. 7. As the switching frequency increases, the harmonic level shifts to the higher frequencies which makes it difficult to attenuate them by simple filters.

From these examples, it is seen that distortion is at its worst when the supply changes state suddenly as in *Waves III* and *VI*. A smooth transition and composition of the wave has the least distortion and this makes filtering straightforward.

	VII	VIII	IX	X	XI
dc	0	79	0	0	0
Fund.	100	100	100	100	100
2	-	-	-	-	-
3	-	33	33	-	-
4	-	-	-	-	-
5	-	20	20	18	20
6	-	-	-	-	-
7	-	14	14	15	14
8	-	-	-	-	-
9	-	11	11	-	-
10	-	-	-	-	-

920052-22

Table 2. Fourier analysis of DC or pulsed waveforms.

 


Fig. 8. Fourier plot of square wave.

 


Fig. 9. Fourier plot of periodical DC wave.

 


Fig. 10. Quasi-square periodical wave.

 


Fig. 11. Quasi-sinusoidal wave.

DC or pulsed waveforms

In this section, we look at harmonics in DC or pulsed waveforms—see Table 2.

Wave VII is, again, the ideal sine wave.

Wave VIII is a square wave as produced by, for instance, a multivibrator oscillator. By inspection, the average value is half the amplitude for a 50% mark-space ratio. The fundamental is equal to twice the amplitude divided by π . Only odd harmonics (all cosine terms are zero) are present owing to the nature of the wave. A low-pass filter with a transfer function equal to zero at high frequencies will by-pass high-order harmonics but will introduce phase distortion in the output. Fourier analysis is plotted in Fig. 8.

Wave IX is a periodical DC wave, typical of that generated by many commercial transistorized inverters. An inverter is a circuit to convert a DC voltage into a periodical waveform. The Fourier analysis is plotted in Fig. 9. High-level third, fifth and seventh harmonics contribute to the shape of the wave. Note that the more higher harmonics are contained, the sharper the wave will be.

It is difficult to filter out the third and fifth harmonics as both are at high level and close to the fundamental. The filter design must be a good compromise between inductance and capacitance values. Large induc-

tances and small capacitances cause the inverter regulation to become poor. Small inductances and large capacitances improve regulation but increase the current through the inverter. Regulation is the ratio between no-load and full-load output voltage.

Wave X is, again, the inverter waveshape but with a different control. Its Fourier analysis is plotted in Fig. 10. The waveform, which has fewer harmonic peaks, is known as a quasi-square-wave. The analysis shows the existence of a small percentage of third harmonic content, but the fifth and seventh are not noticeable.

Wave XI is a quasi-sinusoidal wave that can

be detected in many industrial motor drive controller. The distortion over a wide frequency spectrum contains 20% fifth and 13% seventh harmonics, but at low level. Single filter elements are, therefore, effective in many cases. If the smoothing filter in the DC path is capacitive, the system is called a constant-voltage source; if it is inductive, the system is a constant-current source. The Fourier analysis is plotted in Fig. 11.

Summary

Most pulse-shaped waves contain odd harmonics. If the periodical amplitude swings between equal positive and negative peaks, the average DC component is nought. If the

amplitude remains above the zero level, there is always a DC component.

The waveforms shown in this article are, unfortunately, all real-life shapes used intensively in the motion control of electric machines. Simple filters have not much effect, and are often bulky and expensive. The existence of harmonics produces torque pulsation in motors, which causes extra heat, vibration and noise.

With the advances of microprocessor-controlled inverters, harmonic attenuation by pulse-width modulation is now available. As always, however, one should consider complexity and cost against performance. ■

RED-LIGHT DIODE LASERS

based on an original article by S. von Fehren

DIODE lasers that operate from the near-ultraviolet to well into the infra-red region are commonplace and used, among others, in optical fibre communication, optical memories and compact-disc players. Until a few years ago, the only lasers producing visible light were He-Ne lasers. Some of the He-Ne lasers emit a deep red light at a wavelength of 632.8 nm, that is in the visible light region, while others operate at 1.15 μm or 3.39 μm . In spite of the fact that they are (relatively) large, require a power source of kilovolts, cannot be modulated and are highly sensitive to mechanical phenomena, these gas lasers have become very popular because they are inexpensive and easy to manage.

These lasers now have a serious competitor in a diode laser, announced by Toshiba in 1987, but not commercially available until recently, that operates at 660 nm (red light).

Diodes that emit visible light have, of course, been available for many years. Such light-emitting diodes (LEDs) are made from a variety of semiconductor material to obtain a particular colour of light. Gallium-arsenide (GaAs) for near-infra-red; gallium-arsenide-phosphide (GaAsP) for red and yellow; gallium-phosphide (GaP) for green and blue. See Table 1 for light and near-light wavelengths and associated colours.

Without repeating its derivation (see Ref. 1), the formula from which the wavelength, λ , can be calculated is

$$\Delta E = h\nu = hc/\lambda, \quad [1]$$

where ΔE is the energy released when an electron passes from one energy level to another, h is the Planck constant (4.14×10^{-15} eV·s), ν is the frequency of radiation, c is the speed of light in a vacuum and λ is the wavelength (colour) of the emitted light. The quantity $h\nu$ is a quantum of energy commonly called

a photon.

From formula [1], it is seen that, since h and c are constants, the wavelength depends entirely on ΔE . In semiconductors, energy difference is called the energy gap, expressed in eV (electronvolts). One eV = 1.60210^{-19} joule (J). The energy gap cannot be measured: it is determined empirically, that is, by measurement. The energy gap between gallium and arsenide is 1.4 eV. Entering the various quantities in formula [1] results in a wavelength:

$$\begin{aligned} \lambda &= hc/\Delta E = \\ &= 4.14 \times 10^{-15} \times 3 \times 10^8 / 1.4 = \\ &= 8.86 \times 10^{-7} \text{ m} = 886 \text{ nm}, \end{aligned}$$

which is in the near-infra-red region.

To obtain shorter wavelengths (that fall in the visible region), different materials must be used.

Standard laser diodes are made from gallium-aluminium-arsenide (GaAlAs), which has an energy gap of 1.6 eV, corresponding to a wavelength (computation as before) of 775 nm. Because of high production quantities and standardized manufacture, these diodes cost only about a few pounds ex-factory. They are used extensively in CD players and laser printers.

New techniques

The new laser diodes, Toshiba Types TOLD9220 and TOLD9222, are made from indium-gallium-aluminium-phosphide (InGaAlP), which has an energy gap of about 1.9 eV to give a wavelength of 660 nm. Prices of these devices have been coming down rapidly.

Currently, Toshiba research scientists are working on a laser diode that will emit blue light (500–445 nm). The difficulty, as before, is finding suitable semiconductor materials

that can be doped appropriately to yield a p-n junction with the required energy gap of about 2.2 eV.

The (index-based) construction of the TOLD9220 is shown in Fig. 1. Its major parameters (at 25 °C) are

- wavelength, λ : 660 nm
- threshold current, I_{th} : 75 mA (max. 90 mA)

 


Fig. 1. Layer construction of the new Toshiba laser diodes.

 


Fig. 2. Pinout of the TOLD9220.

- operating current, I_o : 85 mA (max. 100 mA)
- break-down voltage, U_p : 1.5 V
- operating voltage, U_o : 2.5 V (max 3.0 V)

 


Fig. 3. Artist impression of the cross-sectional view of the new Toshiba diodes.

- luminous power, P_L : 3 mW
- max. housing temperature: +40 °C.


The pin-out of the TOLD9220, shown in Fig. 2, corresponds to that of CW (continuous wave) laser diodes, which emit light constantly. As in LEDs, the light emission may be raised by increasing the current. However, that also increases the dissipation, which, in LEDs, because of their relatively large emission surface, can be tolerated for some time, but which in laser diodes can be fatal. This is because the actual emission surface in laser diodes is tiny: only $2.5 \mu\text{m}^2$.

A semiconductor crystal emits light not only forward, but also from its backplane. This back emission, amounting to about 5% of the forward emission, falls on to a photodiode whose resistance varies in direct proportion to the luminous intensity. This makes it possible for a circuit controlled by the photodiode to regulate the current through the laser diode, and thus its dissipation. In other words, the temperature of the laser diode is, to some degree, controlled by the light emission.

An artist's impression of a cross-sectional view of the diode is shown in Fig. 3. The laser diode chip (A) is the semiconductor crystal shown in Fig. 1. Although the photodiode is contained in the same housing, the whole construction is referred to as the 'laser diode'. The construction is typical of CW diodes, which nowadays are produced in far greater numbers than pulse lasers.

potential of T_1 rises. This causes a decrease of the current through T_1 and T_2 , and thus through the laser diode. In that way, the light emission of the laser diode is kept at a more or less constant value, which depends on the setting of P_1 (the voltage across D_1 is, of course, the reference). The current through the laser diode is inversely proportional to the active resistance of P_1 . Resistor R_3 prevents the current rising above the maximum permissible value of 100 mA.

 Since the laser diode operates in CW mode, it reaches its maximum operating temperature of 40 °C within about a minute. Because of this rapidity and in spite of the control circuit, it is recommended that the laser diode is mounted on a suitable (TO-5 or TO-39) heat sink.



Sample of the new Toshiba laser diodes.

 


Fig. 4. Simple control circuit for CW operation of the new Toshiba laser diodes.

Control circuit

A suitable circuit for controlling the new Toshiba laser diodes is given in Fig. 4. Zener diode D_2 holds the voltage at the emitter of T_1 at 2.2 V with respect to earth. Provided that the photodiode receives no light, its resistance is a maximum. The base of T_1 is connected across that resistance and the preset is, therefore, at minimum voltage. Since T_1 is a p-n-p type, it is switched on, whereupon its collector current drives T_2 also into conduction. The latter transistor thereupon switches on the laser diode, which then draws a current that is limited by R_3 .

The laser diode emits the maximum permissible light flux, part of which is received by the photodiode. The resistance of the photodiode decreases, whereupon the base

Applications

Red-light laser diodes can be used in many applications, because, compared with He-Ne lasers, their operation and installation are far less complicated (and, moreover, they are cheaper). A glance at Fig. 4 and at a comparable circuit for an He-Ne laser will verify this.

An important industrial application is in barcode readers, which, already in use in thousands of shops and other business, will be almost universal before the end of this decade. Such readers scan the black and white bars of a barcode: the white ones reflect the light, which is then applied to a photodiode, whereas the black ones absorb it. The contrast between the reflected and absorbed light becomes greater as the wavelength becomes smaller; wavelengths above 780 nm cannot be used in barcode readers. Red-light diode lasers are, therefore, very suitable. Moreover, because of their small size, they can be used in portable and mobile barcode readers, which is not really possible with (the rather larger) He-Ne lasers.

At this point, it should be borne in mind that, apart from coherence and power density, monochromaticity, that is, the absence of all other wavelengths, is the advantage of laser light over traditional light. Barcode readers and CD players cannot function properly with polychromatic (multi-colour) light.

 


Fig. 5. Focusing of rays of light and consequent light-intensity diagram.

Another interesting application is in the light pointer as used nowadays on projected images in lectures, film shows, and so on. The red-light laser diode is far more suitable than the He-Ne laser for fitting into a reasonably small tubular holder terminated in a convex (focusing) lens. Moreover, it can be powered by alkaline batteries. Such a pointer would cost about a third of the price of an He-Ne laser, and be only a third of the size and weight of an He-Ne laser.

Use in compact and video disk players?

Believe it or not, the price of a compact or video disk player is determined to a larger extent than generally known by the laser it uses. Why this is so will be clear from the following.

In Fig. 5, light falls on to a convex lens of diameter d . The lens concentrates the light at principal focus F , which is a distance f (the focal length) from the optical centre of the lens. The ray of light along the principal axis passes unhindered through the lens to F , but most other rays are refracted to points other than F on the focal plane by an angle, α , with respect to the principal axis. From the curve at the right of Fig. 5 it is seen that the light-intensity varies around F . Indeed, when focusing is poor (normally caused by a cheap lens), light at F is not a sharply defined point, but a disc of diameter a around the principal focus. This disc

colour	wavelength (nm)
infra-red	1000–740
red	740–620
orange	620–585
yellow	585–575
green	575–500
blue	500–445
indigo	445–425
violet	425–390
ultraviolet	390–5

is bright at its centre and becomes virtually dark at the nulls. Note that by convention the null below the principal axis is negative and that above is positive.

The angle of aberration, α , is found from

$$\tan\alpha = (a/2)/f, \quad [2]$$

where $a/2$ is the distance between the nulls and the principal axis.

The angle is also related to the wavelength of the light in the formula

$$\sin\alpha = 1.22\lambda/d. \quad [3]$$

These two formula can be combined, provided α is small (the normal case) into

$$a = 2.44f\lambda/d.$$

In an ideal lens, $f = d$, so that the diameter of the focal disc is

$$a = 2.44\lambda.$$

[4]

To ensure error-free scanning of the pits on the compact or video disc, the focal disc of the light must not be larger than the pits or wider than the tracks between the pits. This has two important consequences.

First, since the wavelength of the light determines the diameter of the focal disc, non-chromatic light will cause several (overlapping) discs. Only a laser will thus give one focal disc.

Second, the smaller the wavelength, the smaller the diameter of the focal disc, and the smaller the pits and track-width of the compact or video disc can be.

Currently, the wavelength of the laser light in CD players is 780 nm. This makes possible a distance of 1.9 μm between tracks and, consequently, about 18 000 tracks on the 33 mm wide recording surface of a CD. If the wavelength of the laser light is brought down to 660 nm, the number of tracks on a CD, and thus the playing time, can be increased by 18%. The same applies to video disks and CD-ROM. ■

References:

1. "Lasers: An Overview," *Elektor Electronics USA*, July/August 1987, p. 27.
2. "The Compact Disc," *Elektor Electronics USA*, July/August 1987, p. 39.


LCD FOR INDUCTANCE/CAPACITANCE METER

Design by L. Pijpers

The liquid crystal display described in this article and shown in the photograph below is intended primarily for use with the inductance-capacitance meter published last month

IN the design of a 3½ digit voltmeter module, IC Type ICL7106 has attained virtually the same status as a 555: universally known and suitable for almost any application. It has nearly everything needed on board: an analogue-to-digital (A-D) converter with automatic zero-setting and the required display drivers. All that is needed additionally are a reference voltage source and some passive components.

 The signal that renders the display black must be in anti-phase with the signal at the back-plane (BP) of the display. The same is true for that controlling the decimal points and the LoBat indication. Unfortunately, the 7106 does not provide these signal and, therefore, transistor T_1 has been added to invert the BP signal. By connecting board pins dp_n ,



dd_p , and bat to BP, the associated parts of the display become visible.


If non-connected pins or the LoBat indication pick up noise that cause the relevant information to become visible, the former can be linked to pin 40 (AC) direct and the latter via a 10 M Ω resistor.

The input circuit is a low-pass filter with a cut-off frequency of 16 Hz that refrains any noise at the input from reaching the A-D converter.

The clock that 'motivates' the 7106 has a frequency, determined by C_2 , that makes two measurements per second possible.

Resistor R_4 and capacitors C_3 – C_5 form part of the A-D converter circuit.

 The supply voltage is high enough to ensure that the reference voltages, connected



PARTS LIST

Resistors:

- R1 = 22 MΩ
- R2, R5 = 1 MΩ
- R3 = 100 kΩ
- R4 = 470 kΩ
- R6 = 18 kΩ
- R7 = 10 kΩ
- P1 = 10-turn preset, 4.7 kΩ

Capacitors:

- C1 = 10 nF
- C2 = 150 pF
- C3, C6, C7 = 100 nF
- C4 = 47 nF
- C5 = 220 nF
- C8, C9 = 330 nF
- C10, C11 = 100 μF, 25 V, radial

Semiconductors:

- T1 = BS170
- IC1 = ICL7106
- IC2 = 78L05
- IC3 = 79L05

Miscellaneous:

- LCD1 = 3 1/2 digit display
- 40-pin low-profile IC holder
- 2 off 20-pin terminal strip
- PCB 920018

to V+ and Comm of IC₁, are sufficiently stable for the A-D conversion to be accurate to 1 digit. This assumes, of course, that the reference voltages, REF HI and REF LO, have been preset correctly with P₁. The voltage between REF HI and REF LO must be half the full-scale value, that is, here 1 V. Presetting is easiest by applying a voltage of 1.9 V to the input and adjusting P₁ till the display indicates the same value as the meter with which the input voltage is measured. Do not make the input voltage much higher, because if P₁ is then turned a little too far, IC₁ will indicate an 'overload' which complicates the setting.


To make the circuit suitable for supply voltages of ±8-±20 V, it has been provided with two voltage regulators, IC₂ and IC₃, which provide a supply of ±5 V. If such a supply is already available, IC₂, IC₃ and C₈-C₁₁ may be omitted.

The circuit is best built on the printed-circuit board shown in Fig. 2. Start the construction with the wire links and end with placing the display into its holder. Since the display is mounted over IC₁, it is important that the 7106 is fitted in a low-profile holder. If the display does not fit properly on to the two terminal strips, plug another pair of terminal strips into the first and then the display into the second pair.

It is, perhaps, interesting to note that the type of display specified is also suitable for (diffused) back lighting. ■

PARAMETERS

Metering range	±2 V with respect to earth
Accuracy	±1 digit (see text)
Supply voltage	Regulated: ±5 V Unregulated: ±8-±20 V
Display connections	dp1-dp3; ddp (:); LoBat

 

DESIGN IDEAS

The contents of this column are based solely on information supplied by the author and do not imply practical experience by *Elektor Electronics*

SUPER SIGN

by Dr K. A. Nigim

SUPER SIGN is a 'light-weight' powerful circuit that is capable of switching, manually or automatically, three independent groups of lamps arranged as desired.

The first group of lamps is switched on and off at a preset frequency produced by a pulse generator. The other two groups are switched alternately by bistables at half the preset frequency.

The output signals from the pulse generator control the switching of a triac connected between the lamps and the mains power supply. The triac gate is isolated by a zero-crossing optoisolator. Figure 1 shows the major parts of the circuit, which is suitable for automatic and manual switch modes.

The pulse generator is built around a Type 4047 monostable/astable multivibrators shown in Fig. 2. Three different clock signals are available: (a) at pin 13 (oscillator output); (b) at pin 10 (Q); and (c) at pin 11 (Q). The pulse width (on-time) is controlled through an RC circuit connected between pins 1, 2, and 3.

Control circuit

The logic for the control circuit is designed for either manual or automatic initiation as set by S₁. When the auto mode is selected, photoresistor R₁₆ controls the biasing current flowing into the base of T₁.

When light falls onto R₁₆, its resistance decreases, resulting in too small a base current into T₁: the transistor then switches off. At dusk, or at any level of 'darkness' set by P₂, the resistance of R₁₆ increases, whereupon the base current into T₁ becomes sufficient to switch the transistor on. Relay Re₁ is then energized and its contact connects the power lines to IC₁.

Duty factor

When the duty factor of the pulse at pin 13 is 50% (square wave), the on-time, T, (in seconds) is given by

$$T = 2.2(P_1 + R_3)C_1.$$

This time is halved at pins 10 and 11. The pulse width cannot exceed 20 ms so as to allow sufficient time for the lamps to switch off.

Power circuit

Each group of lamps is connected to the

Whether you are advertising your merchandise, welcoming your mother-in-law, or celebrating a day of success, SUPER SIGN will add light to the occasion.

mains supply through a suitable triac, whose rating depends on how many lamps the particular group contains. For example, if ten lamps rated at 100 W each are connected in parallel, the r.m.s. load current will be 5 A; whereas if ten 10 W lamps are used, the load current will be 0.5 A.

The table gives a rough guide between the number of lamps connected in parallel, the wattage per lamp and the suggested triac. It is good practice to mount the triac on a suitably rated heat sink a little distance from the logic control circuit.

The gate of each triac is connected to the relevant output of IC₄ via zero-crossing optoisolators IC₁–IC₃—see Fig. 3. This arrangement ensures that the control circuit is buffered and isolated from the mains. At the same time, triggering of the triac at the zero-crossing points greatly reduces radio/TV interference.

Construction and testing

A 12 V DC regulated power supply, rated at

 


Fig. 1. Three-line super sign.

number of lamps per group	wattage per lamp	RMS current per group	triac type (on heat sink)
10	10	0.5	C206D
10	60	3.0	C226D
10	100	5.0	SC146D

 


Fig. 2. Automatic/manual control circuit.

 


Fig. 3. Circuit of power triacs.

500 mA, is required to power the circuits.

The circuit in Fig. 2 is best constructed on an individual small PCB. The location of photoresistor R₁₆ depends on individual requirements. Adjust P₂ for the desired level of 'darkness' as indicated by the lighting of D₀ (and the relay changing state). The pulse width is controlled by P₁, which is normally set for a value of 330 ms (≈3 Hz).

The optoisolators and triacs are assembled on a second small PCB. The two boards can be stacked in multi-storey style with the triac board at the bottom. It is recommended that the triacs be fitted on a suitable heat sink.

Variations

The control circuit can be altered to any desired frequency pattern: the use of two PCBs makes replacement of the control board easy. The photoresistor can be replaced by a push-to-make switch (for instance, for a birthday party) in series with a 1–2 kΩ resistor. ■

PARTS LIST

Resistors:

- R0, R1 = 1.2 kΩ
- R2 = 470 Ω
- R3 = 5.6 kΩ
- R4, R5, R6 = 200 Ω
- R7, R8, R9, R10, R11, R12 = 330 Ω, 1/2 W
- R13, R14, R15 = 10 Ω, 3 W
- P1 = 4.7 kΩ
- P2 = 100 kΩ

Capacitors:

- C1 = 1 μF
- C2, C3, C4 = 0.1 μF, 400 V, polypropylene

Semiconductors:

- D0 = LED, red
- D1 = 1N4001
- T1 = BC107
- IC1, IC2, IC3 = MOC3062
- IC4 = 4047
- Triac = see text

Miscellaneous:

- Re1 = 12 V, 400 Ω, sub-miniature for PCB mounting

FM TUNER

PART 2: QUARTZ FILTERS, POWER SUPPLY AND ADJUSTMENT

This second part of the article was originally intended to deal with the adjustment of the main tuner board only. However, following many readers' enquiries, we will first give some additional information on the quartz filters used in the design.

The shape of the filter is apparent from this month's front cover photograph: the TQF-2599 from Toyocom is a small block made of nickel-plated steel. The dimensions of the device are: 31 mm long, 21 mm wide and 18 mm high (approx. $1\frac{7}{32} \times 1\frac{3}{16} \times 1\frac{1}{16}$ inch). At the underside of the device are five solder terminals that allow it to be fitted direct on to a printed circuit board. The solder pins are located at the short sides of the enclosure: one side has two pins, the other, three.

Figure 6 shows the electrical equivalent of the quartz filter. Two terminal pairs are connected to the input and the output inductors. The remaining terminal is connected to the filter enclosure. Note that the input in-

 


Fig. 6. Internal diagram of TQF-2599.


 


Fig. 7. Filter test circuit.

 

ductor allows a balanced connection, while the output of the filter is single-ended (unbalanced or asymmetrical) because the 'lower' end of the output coupling inductor is connected to the enclosure (i.e., to ground).

Between the input and the output sit two quartz crystals, whose resonance frequencies differ by an amount equal to the filter bandwidth. The input and output inductors serve to reverse the phase, and to match the crystal impedances. They also determine to some extent the pass-band ripple and the bandwidth. In the present FM tuner, the TQF-2599 meets the requirement for a filter with a small pass-band ripple and good phase linearity. The selectivity, i.e., the rejection of frequencies outside the pass-band, is not a prime requirement, but can be made so by using a number of these filters in series.

The measurement circuit shown in Fig. 7 produces the pass-band characteristic and the pass-band ripple characteristic shown in Figs. 8 and 9 respectively. Although the pass-band curve (Fig. 8) is not entirely symmetrical, the pass-band ripple is very small indeed (Fig. 9): less than 1 dB. Further technical data on the TQF-2599 is given in

Table 1. Note that the 'attenuation' shown in Figs. 8 and 9 is relative to the insertion loss of the filter.

As already mentioned, the filters are used two by two to achieve the required skirt steepness. When four filters are cascaded as in the present tuner, the -40 -dB bandwidth is reduced to ± 180 -kHz, while an attenuation of 60 dB is reached at ± 300 kHz already. The use of four filters significantly reduces the dip in the pass-band of an individual filter at about +350 kHz, and in addition ensures an image rejection that obviates the use of additional devices to ensure sufficiently high receiver selectivity.

Construction

The main tuner board is fairly large, but simple to populate. This month's front cover shows the finished prototype. All parts must have the correct terminal spacing (pitch) to ensure the shortest possible connections. As always, start with the wire links, of which there are only two on the present PCB. The FD12 tuner module may be fitted with the aid of solder pins, which are soldered on to

Table 1. TQF-2599 main technical data

Centre frequency:	10.7 MHz \pm 9 kHz
-3-dB bandwidth:	240 kHz min.
-20-dB bandwidth:	600 kHz min.
-30-dB bandwidth:	-400 kHz to +450 kHz max.
-40-dB bandwidth:	-450 kHz to +550 kHz max.
Insertion loss:	-7 dB max.
Pass-band ripple:	1 dB max.
Source and load impedance:	900 Ω \pm 10%; 10 pF \pm 2 pF parallel

the contact fingers on the edge connector that protrudes from the underside of the unit (see the introductory photograph in part 1 of this article).

The dual varicap used in the demodulator circuit, D1, is a device that looks very much like a transistor in a TO-92 enclosure. The two outer terminals are the anodes, the inner terminal is the common cathode. Although we did not use IC sockets on the prototype, it may be safer to do so. A second prototype built with IC sockets showed no problems.

The two voltage regulators on the board are fitted vertically, and bolted on to a common heatsink. Insulating washers are required for both regulators to prevent short-circuits should the heatsink touch the tuner enclosure, which is at ground potential.

After populating the board, give it a final, thorough, check as quite a few components are involved.

Power supply

The main tuner board works from an adequately smoothed direct voltage of between 23 V and 32 V, which need not be regulated. This supply must be capable of sourcing a maximum current of about 300 mA. The main supply voltage is connected to the PCB terminal marked '+'. The LM317T on the board reduces the unregulated voltage to a stabilized supply of 20 V for the FD12 tuner module. The 20-V supply rail is also connected to the input of the second voltage regulator, an 7815 (IC5), which powers all ICs on the board. The tuning circuit in addition requires a supply voltage of which the maximum value lies between 30 V and 33 V.

Figure 10 shows a suggested power supply that caters for a regulated 32-V output for the main board and the tuning circuit, as well as a 5-V output for the synthesizer (to be described next month). The +32-V output of the supply may be connected to the supply terminals marked '+33 V' and '++' on the tuner board. The tuning voltage proper varies between about 3 V and 30 V, and is determined by the synthesizer. For an initial test of the tuner, the synthesizer is not required, and the tuning voltage, U_{TUNE} , may be taken from the wiper of a multiturn potentiometer connected between ground and +33 V.

Connection and wiring

Apart from the supply connections mentioned above we have the antenna cable, which is connected to the input marked 'Ant.', and the input cable of the stereo amplifier, which is connected to the R-OUT and L-OUT terminals on the tuner board. Both the antenna and the audio connections have separate ground pins on the board to connect the cable screening.

The remainder of the wiring is for the indicator LEDs and the MODE control of the stereo decoder and the audio processor. The signal strength (S-meter) terminals are pro-

 


Fig. 8. TQF-2599 selection characteristic (measured with test circuit shown in Fig. 7).

 


Fig. 9. TQF-2599 attenuation characteristic within pass-band. The ripple is quite small at less than 1 dB.

visionally connected to a multimeter.

Circuits IC2 and IC3 indicate their current mode with the aid of LEDs. The cathode of the 'STEREO' LED is connected to resistor R47, and the cathode of the 'MUTE' LED to R46. The anodes of these LEDs are connected to +15 V. The LED drivers in IC3 are constant-current types. The cathodes of the 'P-STEREO' (pseudo-stereo) and 'BASIS-B' (widened image) LEDs are connected to ground, and the anodes to the respective PCB terminals.

The mode setting of IC2 and IC3 is effected by a combination of logic levels applied to the corresponding control inputs. The stereo decoder, IC2, switches to mono when a voltage greater than about 3 V is applied to the 'MONO' input. The operation of the 'MUTE' input is similar. By contrast, the

switching levels at the MODE SELECT A and MODE SELECT B inputs are TTL-compatible, i.e., 'low' (L) corresponds to <0.8 V, and 'high' (H) to >2.4 V. This allows the different modes to be set as follows:

Normal operation:	A = L B = irrelevant
Wide image:	A = H; B = H
Pseudo stereo:	A = H; B = L

When the inputs are left open (i.e., not connected), they are internally pulled to +5 V. This causes the 'wide image' mode to be selected.

The audio outputs on the board may be connected to any hi-fi amplifier or preamplifier via line (type 'RCA' or 'phono') sockets and a conventional stereo screened cable.

 


Fig. 10. Suggested power supply for the main tuner board and the synthesizer.

Table 2. Main tuner board connection overview

Terminal	Signal/function
Ant.	Antenna; 75- Ω unbalanced (coax)
+33V	Supply voltage for tuning circuit
UABST	Tuning voltage 3-30 V
+	+23 V to +32 V
MONO	>3 V switches to mono
MUTE (R45)	>3 V mutes AF outputs
MUTE (R46)	LED to +15 V; lights when mute off
STEREO LED	LED to +15 V; indicates stereo broadcast
P-STEREO	LED to ground; indicates pseudo-stereo mode
BASIS-B LED	LED to ground; indicates wide image mode
L-R OUT	Left and right audio outputs
MODESELECT A,B	Select TDA3810 mode
	Mode A B
	Stereo L x
	Wide image H H
	Pseudo stereo H L

Table 2 provides an overview of all board connections and their functions.

Adjustment: easy!

For an initial adjustment of the tuner it is sufficient to connect the main supply only to the tuner board. First, check the output voltages (+20 V and +15 V) of the two regulators. Next, fit wire jumper 'C' to switch on the on-board 10.7-MHz reference oscillator. Connect a voltmeter to pin 6 of IC6, and adjust the core in filter Fi1 until the meter reads about 7 V. A tip: turn the core downward if the measured voltage is initially smaller than 7 V, or upward if the voltage is higher than 7 V. Next, turn the core in Fi2 to the same depth as that in Fi1.


From then on, the quadrature demodulator circuit will keep itself centred at 10.7 MHz. Remove jumper 'C' to switch off the auxiliary oscillator.

Switch off, and prepare the tuner for 'real' FM reception. 'MODESELECT' is set to 'normal' by wiring terminals 'A' and 'B' to ground. The 'MONO' and 'MUTE' terminals may be left open. Further, connect the antenna cable (a 75-cm long straight piece of wire soldered to 'Ant.' will also function if you are not too far away from an FM transmitter). Lastly, connect the tuning voltage via the (temporary) multiturn potentiometer, and, of course, the audio amplifier. Set P1 and P2 to their mid-way positions.

Switch on again, and tune to a relatively strong FM stereo station. Adjust the PLL centre frequency (P2) until the stereo LED lights. Next, turn the wiper of P2 alternately left and right, and note the positions where the 'STEREO' LED goes out. Set the wiper in between these two positions. This concludes the adjustment of the stereo PLL.


Finally, adjust preset P1 for optimum channel separation. For this you either have to wait for a stereo test transmission, or have access to a stereo test generator. Failing both, leave the preset at the centre of its travel, when the channel separation is at least 40 dB.

 Next month: description of the synthesizer.



2-METER FM RECEIVER

The 2-meter band has been popular for three decades and longer for short, medium-range and mobile communication between radio amateurs, and it is usually pretty crowded in and around large cities, with activity centering around repeater stations. The predominant mode for local traffic is FM, and listening in can be a great way to expand your knowledge of electronics as well as get to know fellow enthusiasts. The receiver presented here is aimed at those of you who are not yet bitten by the 'radio' bug. Alternatively, for hams already on the air, the present design is an excellent stand-by receiver to monitor band activity.

 

design by J. Barendrecht and L. Lemmens

THE receiver described is remarkably compact, based on three ICs only, and fairly simple to build since a well-designed printed circuit board is available ready-made.

The block diagram (Fig. 1) of the receiver shows that it is a 'classic' superheterodyne with a single intermediate frequency (IF) of 10.7 MHz. The antenna signal is amplified and passed through a band filter before it is applied to an integrated double-balanced mixer. The local oscillator signal is supplied

by a varicap-tuned voltage-controlled oscillator (VCO). The IF signal at 10.7 MHz is passed through a crystal filter to ensure the required selectivity of the receiver. Next, it is amplified and filtered again. One integrated circuit combines the functions of demodulator (FM only), squelch (automatic muting) and S-meter driver. It is followed by an AF amplifier capable of driving a pair of headphones or a small loudspeaker.

Practical circuit

The circuit diagram of the 2-metre receiver, Fig. 2, follows the block diagram quite closely. At the RF input there is a low-noise

preamplifier based on the BF981 dual-gate MOSFET. The antenna signal is connected to a 50-Ω tap on inductor L1. The amplifier output signal is coupled inductively to the IF amplifier via L4-C9 and L5-C11. These two VHF L-C tuned circuits form a critically coupled bandpass filter with a bandwidth of about 2 MHz to give the receiver the initial preselection required to cope with strong out-of-band signals.

The NE612 (IC1) is an integrated double-balanced mixer and oscillator from Signetics (Philips Components). It is an improved version of the NE602, on which design notes were published in Ref. 1. The block diagram of the NE612 is given in Fig. 3. Here, the on-


 


Fig. 1. Block diagram of the receiver: a classic superheterodyne.

 

910134 - 12

Fig. 2. Circuit diagram of the 2-metre FM receiver. Note that the IF amplifier, limiter, FM demodulator, S-meter driver and squelch functions are all combined in a single IC, the NE604.

 


Fig. 3. Block diagram of the NE612 integrated double-balanced mixer (courtesy Signetics).

chip oscillator is connected to an L - C tuned circuit of which the resonant frequency is determined by a pair of variable capacitance diodes. The tuning voltage is supplied by a combination of a multiturn potentiometer, P_1 , a fixed resistor, R_6 , and a preset potentiometer, P_2 . Correctly aligned, the VCO has a tuning range from about 133 MHz to 135.5 MHz, which covers the 2 metre band adequately. Depending on the setting of P_2 and the value of C_{17} , the VCO range can be made larger, for instance, in the USA where the 2-metre band extends from 144 MHz to 148 MHz (note, however, that the lower end of the band is not used for FM traffic).

The IF output signal is taken single-ended from the mixer output and fed to the 10.7-MHz IF quartz filter via a coupling capacitor, C_{19} . The input and the output of the quartz filter, X_{F1} , are matched by tuned circuits L_{12} - C_{24} and L_{13} - C_{25} respectively.

As already mentioned, the NE604 (IC₂) combines a number of functions in this circuit. The block diagram in Fig. 4 tells the whole story. A 10.7-MHz ceramic filter, FL_1 , is inserted between the output of the first IF amplifier and the limiter input of the second IF amplifier on board the NE604. The quadrature (FM) detector is connected to a ready-made 10.7-MHz inductor, L_{15} , via coupling capacitors C_1 and C_2 . Pin 7 of the NE604 supplies the demodulated signal ahead of the mute circuit (see the block diagram). This unmuted signal may be used for AFSK decoders and other equipment (packet radio TNC) that must always work, irrespective of the set mute level. The signal is brought out to a jumper block marked D, which allows ready connection to a screened cable.

The mute (squell) level is set by potentiometer P_3 , with preset P_4 acting as a 'coarse' control. The S-meter (signal strength) driver consists basically of a FET, T_2 , and two anti-parallel diodes, D_2 - D_3 , connected across a moving-coil meter, M_1 . The meter may be given a meaningful range by adjusting presets balancing presets, P_5 and P_6 .

The demodulated FM signal is taken through a de-emphasis section, C_4 - R_{10} - C_3 , and is then applied to a FET stage that pro-

vides sufficient drive for the AF output amplifier, IC₃. An L - C series filter is included in the signal path to suppress frequencies above 3 kHz. The audio output signal is fed to a loudspeaker, or to a pair of headphones via an external jack socket with a break contact, J_1 . When a plug is inserted in the headphones socket, the loudspeaker is automatically disconnected.

The receiver has an on-board 8-V supply based on a low-drop voltage regulator Type L4885CV, which enables input voltages down to about 10 V to be used (battery operation!). Where the L4885CV can not be obtained, it may be replaced by an 7808, which works with input voltages of 12 V and higher. The 8-V supply voltage is decoupled at a number of places in the circuit with the aid of small ferrite chokes and ceramic capacitors to ground. The current consumption of the receiver depends on the output volume, and lies between 45 mA and about 200 mA.

Construction

It is strongly recommended to build the receiver on the ready-made double-sided printed circuit board supplied through the Readers Services. This board, of which the artwork is shown in Fig. 5, is pre-tinned, double-sided, pre-drilled, and has a component layout printed on the component side. Start the construction by winding the inductors as indicated in Table 1. Next, insert the coffin-style capacitor, C_6 , into its slot in the PCB. The 'shoulders' of this capacitor should rest on the component side of the PCB. Solder the device carefully at the two sides, and check that it does not form a short circuit. Put the MOSFET, T_1 , in the hole, and align its terminals over the three copper tracks (gate 1; gate 2, drain). The type indication printed on the MOSFET is legible from the component side. If necessary cut the g_1 and g_2 terminals. Solder all four terminals. The source terminal is soldered direct on to the ground plane.

Use pliers to bend the stator terminals of all five foil trimmers horizontally. Fit trimmer C_5 , and solder the stator terminal flush on to the copper track to g_1 of the MOSFET. The two rotor terminals are soldered at the

solder side of the board. The g_2 biasing resistors, R_1 and R_2 , are soldered direct to the g_2 side of the coffin capacitor. Similarly, the drain resistor, R_3 , is soldered direct to the copper track for the drain. C_2 is 'in the air' between the drain track and the tap at the earthy ('cold') side of L_4 . The solder junctions between the trimmers, the matching inductors and the input and output terminals of the quartz filter are also 'in the air'.

The 'hot' side of L_4 and L_5 is soldered direct to the stator terminal of the respective trimmer capacitor, C_9 and C_{11} . The air-cored inductors, L_1 , L_4 and L_5 , are stretched by spacing the turns evenly. After soldering, the toroidal core inductors, L_{12} and L_{13} , are secured to the PCB with a drop of wax. Do not yet mount the screening can of the VCO inductor, L_9 .

The remainder of the construction is fairly straightforward. All components are mounted with the shortest possible lead length. IC sockets must not be used. Fit solder pins for the connections to the external parts.

Inspect your work so far, paying particular attention to short-circuits between component terminals and the copper ground plane.

Next, cut and bend a 20-mm wide piece of tin plate or thin brass, and place it vertically on the dashed outline printed on the component side of the PCB, outside the solder pins in the four corners. Look at the position of the input BNC connector, and make a clearance in the screening large enough to pass over the teflon shaft. Another clearance is required where the screen passes over the tracks to potentiometer P_3 .

Solder the screening all around to the ground plane. Next, cut three 50-mm long, 20-mm high, pieces of the same material, and align these between the long sides of the screening, over the dashed lines on the PCB. Look at where the screen passes over the drain track of T_1 , and make a small clearance to prevent a short circuit. Similarly, the screen that separates the input and output of the quartz crystal filter must have a clearance at one side for the quartz filter. Do not solder the screen to the quartz filter enclosure, as the device is easily damaged by overheating.

 


Fig. 4. Block diagram of the NE604A FM IF system (courtesy Signetics).

 
 
 


Fig. 5. Component side and solder side layouts (mirror images), and component mounting plan of the PCB for the 2-metre receiver.

COMPONENTS LIST

Resistors:

4	100k Ω	R1;R2;R4;R5
1	1k Ω	R3
1	47k Ω	R6
2	150k Ω	R7;R10
1	10k Ω	R8
1	470k Ω	R9
1	4k Ω 7	R11
1	47 Ω	R12
1	100k Ω linear multiturn	P1
1	100k Ω preset H	P2
1	470k Ω lin. potentiometer	P3
1	50k Ω preset H	P4
1	10k Ω preset H	P5
1	1k Ω preset H	P6
1	4k Ω 7 log. potentiometer	P7

Capacitors:

2	100pF	C1;C12
1	4pF7	C2
2	20pF trimmer (green)	C24;C25
3	7pF trimmer (grey)	C5;C9;C11
1	1nF coffin	C6
2	10nF	C7;C13
1	1nF	C8
2	22nF	C10;C15
2	47nF	C14;C35
2	15pF	C16;C20
2	12pF	C19;C26
1	33pF	C17
1	68pF	C18
1	1 μ F 16V radial	C21
3	470nF	C22;C23;C34
1	47pF	C33
1	220pF	C3
1	12nF	C36
6	100nF	C27-C31;C37

2	470pF	C4;C32
1	47 μ F 10V radial	C38
1	47 μ F 25V radial	C39
1	220 μ F 10V radial	C40

Inductors:

Winding details are given in Table 1.
Required materials:

7	3-mm long ferrite bead
1	7V1S assembly (Neosid)
2	T37-6 toroid core (Amidon)
1	10mH radial choke (Toko 181LY103)
1	KACS(K)4520A or KALS4520A (Toko)
1	1 mm dia. silver-plated wire
0.8 mm dia.	enamelled copper wire
0.2 mm dia.	enamelled copper wire

Semiconductors:

1	BB204B	D1
2	1N4148	D2;D3
1	1N4001	D4
1	BF981	T1
2	BF256A	T2;T3
1	NE612	IC1
1	NE604AN	IC2
1	TDA7052	IC3
1	L4885CV	IC4

Miscellaneous:

1	BNC socket	K1
1	250 μ A moving coil meter	M1
1	8 Ω /1W loudspeaker	LS1
1	jack socket w. break contact (not on PCB)	J1
1	10.7M15A crystal filter	XF1
1	CFSK107M3 ceramic filter (Toko)	
1	Printed circuit board	910134

range is obtained (remember, the IF is 10.7 MHz). In some cases, it may be necessary to change the value of C17, or increase the number of turns of L9 from 1.5 to 2.

Switch off, fit the screening can on L9 and measure the VCO range again. Redo the above adjustments as required to compensate the effect of fitting the can. Do not solder the tabs at the sides of the can until you are satisfied with the VCO range.

Tune the demodulator to 10.7 MHz by turning the core in L15 for highest noise output (you may have to adjust the squelch control, P3, to hear the FM noise). Next, peak C24 and C25 for maximum noise output also.

Apply an FM-modulated 2-m test signal to the RF input. Start with a fairly high level, say, 500 μ V. Tune the receiver to this signal, and adjust C5, C9 and C11 for minimum noise. Reduce the signal level as you approach the optimum setting of these trimmers. In particular the 2-m band filter will be found to be pretty selective, i.e., critical to adjust.

If necessary redo the adjustment of L15 for undistorted output (it is best to use a test tone for this).

Reduce the RF input level until the signal is just about audible. Again peak the IF and RF trimmers for minimum noise, and if necessary 'throttle' the RF signal even further. Our prototype was adjusted in this way, and achieved a sensitivity of between 0.1 μ V and 0.15 μ V for an S/N (signal-to-noise ratio) of about 12 dB. This was found comparable to the performance of a typical commercial-grade receiver as used in mobile 2-metre transceivers (the test was made against an FT227RA mobile rig from Yaesu).

Finally, adjust the two presets at either side of the S-meter connections until the meter gives a sensible indication of the signal strength (switch the generator between low and high output levels). Since S-reports have little meaning in FM communication, and the standards used to indicate and compare signal strength are a subject of hot debate between radio amateurs, it makes little sense to try and calibrate the meter in S points. ■

Reference:

1. "NE602 Primer," *Elektor Electronics USA*, January 1992, p. 20.

Finally, secure K1 to the PCB surface by bolting it down with a clamp.

Adjustment

The adjustment of the receiver requires a VHF signal generator and a frequency meter. If you do not have access to a signal generator, you may need to call in the help of a local radio amateur willing to set up a test signal 'on the air'.

Connect the external controls, the loudspeaker and the S-meter to the board. In-

itially, set all trimmers and presets to the centre of their travel. Connect the signal generator (or the antenna) to the receiver input.

First, concentrate on the VCO. Apply power, and check that the board supply voltage is 8 V. Couple the frequency meter inductively to L9 (with a small coupling loop), or capacitively (with 10 pF or so) to pin 7 of IC1. Adjust the core in L9 until you are roughly at 134 MHz, then adjust P2 until the VCO range is about 133 MHz to 135 MHz. If necessary, stretch or compress the turns of L9 carefully until the desired VCO frequency

Table 1. Inductors

Position	Description	Core	No. of turns	Wire dia.	Note(s)
L1;L5	VHF air-cored	none	8	1mm CuAg	Tap at 2 turns from cold end; internal diameter 6mm; space turns to fit PCB.
L2;L3;L6;L7; L8;L10;L11	VHF choke	3mm ferrite bead	4	0.2mm CuL	
L4	VHF air-cored	none	8	1mm CuAg	Tap at 1 turn from cold end; internal diameter 6mm; space turns to fit PCB.
L9	VCO 135MHz	Neosid 7V1S	1.5	0.8mm CuL	Space turns.
L12;L13	10.7MHz	T37-6 toroid	50	0.2mm CuL	Secure core with wax; approx. 10 μ H.
L14	10mH choke	-	-	-	Toko 181LY103 radial.

8051/8032 ASSEMBLER COURSE

PART 3: HARDWARE EXTENSIONS FOR THE 80C32 SBC

by Dr. M. Ohsmann

After our first dealings with programming in assembly language, we now present an intermezzo in the course. Some useful hardware extensions are proposed for the 80C32 single-board computer described roughly a year ago in this magazine. All extensions are accommodated on a single printed circuit board.



The extension board is simply connected to the 64-way DIN a-c plug on the single board computer (SBC). All inputs and outputs of the present extension card are conveniently located at the edge of the PCB, and have suitable connectors where these are useful. The combination of the SBC and the extension card forms a simple and versatile microcomputer system based on a MCS52 microcontroller IC. The many possibilities of the extension card will be discussed with reference to the circuit diagram in Fig. 11.

The interfaces

Reset

Push-button S_1 resets the SBC. After a reset, all four LEDs D_1 - D_4 light. When the SBC runs the courseware monitor program, EMON51, the reset key must be pressed before a download operation to start the monitor.

Serial interface

The SBC has a serial interface that can be used to link the board to a terminal (or 'console') or the RS232 port of a PC running communication software. The interface transmits data via the TxD line (pin c8 on the 64-way DIN plug), and receives data via the RxD line (pin c7). The link to a PC is readily made by connecting TxD, RxD and ground to the appropriate pins of a 9-way sub-D connector, and fitting jumper JP₁ in position 'A', and jumper JP₂ in position 'B'. With some other applications, the TxD and RxD lines of the SBC may be used for MIDI communication, in which case the jumpers must be removed altogether.

Port P1

The bidirectional driver used on port P1 of

the SBC allows the whole port to be used as an input or an output only, i.e., input/output programming of individual lines is not possible. On the extension board, port P1 is used as an output. The port line functions are listed in Table 1.

Table 1. Port P1 bit functions

P1.0	Serial output (JP ₁ =B), or MIDI (JP ₃ =B)
P1.1	Loudspeaker output
P1.2	Positive edge triggers monostable IC8a
P1.3	Not used
P1.4	LED D ₁
P1.5	LED D ₂
P1.6	LED D ₃
P1.7	LED D ₄

MIDI input

Socket K₆ supplies the MIDI signal to a fast optocoupler, IC₇. The output signal of the optocoupler is fed to jumper JP₂ via a Schmitt-trigger. When the MIDI is used, jumper JP₂ must be set to position 'A' to enable the MIDI signal to be conveyed to the serial interface of the SBC. In some cases, voltage divider R₂₀-R₂₁ on the SBC may attenuate the signal to the extent where it is no longer TTL-compatible. Should this happen, R₂₀ may be reduced to 1 k Ω . Fortunately, this was not necessary on our prototype.

MIDI output

Jumper JP₃ allows you to determine which signal is taken to the MIDI output, socket K₅. In position 'A', the TxD signal of the serial interface on the SBC is used, in posi-

tion 'B' bit 0 of port P1. The latter option may be useful when the internal serial interface of the 80C32 is used for other functions. The MIDI output signal on P1.0 is then generated by software simulating a serial output device.

Memory-mapped I/O

The SBC reserves the address range above 0C00H in the external data memory for input/output operations. Decoders IC₁ and IC₂ 'map' the address range as shown in Table 2.

Table 2. Address functions in I/O range

C000H	Read:	data in latch IC ₉
	Write:	value to DAC
C001H	Read:	LCD command status
	Write:	LCD commands
C002H	Read:	data in IC ₃
	Write:	data to IC ₅
C009H	Read:	data from LCD
	Write:	data to LCD

These options can be used for the I/O functions listed below.

D-A and A-D converter

Resistors R₁₂-R₂₆ and R₃₁ form an R-2R network that functions as a digital-to-analogue (D-A) converter in combination with IC₉ and IC_{6a}. The content of latch IC₉ (which is addressable at 0C00H) is available as an analogue value at the output. The maximum value of the output voltage is reached when IC₉ contains 0FFH, which corresponds to about 2.5 V. The D-A out-

put voltage is also applied to comparators IC6b, IC6c and IC6d. These allow the output voltage to be compared to three levels at the analogue inputs. The comparator outputs may be read via address 0C000H, which creates a simple 3-input ADC. The individual functions of the ADC bits at 0C000H are listed in Table 3.

Keys and monostable

The functions of the remaining bits stored at address 0C000H are shown in Table 3.

As you can see, four switches (or push-buttons) are available for your own applications, e.g., for starting certain functions. Monostable IC8a makes it possible to implement a simple capacitance meter. The capacitor to be measured is connected to K9. Software is used to trigger the monostable via bit 2 on port P1, and then read the time that lapses before the monostable toggles again. This can be monitored by reading bit 3 at address 0C000H. See also the assembler file EBTST6.A51 on your course disk!

Table 3. I/O bit functions

Read IC10; address = C000H

- Bit 0: High when U_{in} (input 1) > U_{DAC}
- Bit 1: High when U_{in} (input 2) > U_{DAC}
- Bit 2: High when U_{in} (input 3) > U_{DAC}
- Bit 3: High when monostable active
- Bit 4: High when key S5 not pressed
- Bit 5: High when key S4 not pressed
- Bit 6: High when key S3 not pressed
- Bit 7: High when key S2 not pressed

Parallel 8-bit input/output

The eight logic levels (bits) at connector K3 may be read at address 0C002H. The same address is also used to output 8-bit datawords via latch IC5 and connector K4. This creates byte-wide input/output interfaces.

LC display

A liquid crystal display (LCD) may be connected to K1. The LCD types that may be used, and their connection details, are shown in the inset. Although the control signals generated by the extension board do not meet the exact timing requirements of the LCDs, they caused no problems in our set-up. The timing may be more critical, however, with displays other than the types listed. The LCD signals (on connector K1) and their functions are listed in Table 4.

Power supply

The extension board is conveniently powered by the 5-V regulator on board the SBC. Make sure that the regulator is sufficiently cooled when further loads such as LEDs or relays are connected.

Construction and test

The construction of the extension board is mostly straightforward soldering work.

 


Fig. 11. Circuit diagram of the extension board for the 80C32 single-board computer.

 
 


Fig. 12. Track layouts (component side and solder side; mirror images) and component overlay of the printed circuit board.

COMPONENTS LIST

Resistors:

9	10k Ω	R1-R4;R27-R30; R32
1	47k Ω	R5
1	8-way 10k Ω SIL	R6
5	470 Ω	R7-R11
9	20k Ω 1%	R12-R19;R31
7	10k Ω 1%	R20-R26
2	220 Ω	R33;R34
1	470k Ω	R35
1	100 Ω	R36
1	1k Ω	R37
1	10k Ω linear	P1

Capacitors:

8	100nF	C1;C7-C13
4	1nF	C2-C5
1	220 μ F 16V	C6

Semiconductors:




4	rectangular LED	D1-D4
3	1N4148	D5;D6;D7
2	74HC138	IC1;IC2
2	74HC541	IC3;IC10
1	74HC14	IC4
2	74HC574	IC5;IC9
1	LM324	IC6
1	6N136	IC7
1	74HC123	IC8

Miscellaneous:

1	14-way box header	K1
1	64-way a-c row, female, angled, DIN	K2
3	8-way pin header	K3;K4;K8
2	5-way PCB-mount DIN socket	K5;K6
1	9-way PCB-mount female sub-D connector	K7
1	2-way PCB-mount terminal block, pitch 5mm	K9
1	Push button SPST	S1
4	Switch SPST	S2-S5
1	8 Ω miniature loudspeaker	LS1
1	Printed circuit board	910109

LCDs: types and connections

Type	Lines \times characters	Manufacturer
H2570	1 \times 16	Hitachi
H2572	1 \times 40	Hitachi
LM016L	2 \times 16	Hitachi
LM018L	2 \times 40	Hitachi
LM038L	1 \times 20	Hitachi
LM1612A	1 \times 16	Sharp
VK2116L	1 \times 16	Vikay

   

An LCD module has 14 connections, arranged in a single row of solder points, or in two rows of 7 at either side of the PCB. It is best to solder these points directly to a piece of 14-way flatcable. Pin 1 is marked by a '1' on the display board. Attention: when there are two connection rows, the solder points are numbered in pairs (see drawing above).

The wire numbers 1-14 at the other end of the flatcable are connected to the corresponding pin numbers on header K1 on the extension board via an IDC socket (see drawing). Wire '1' in the flatcable should go to the side with the marker on the IDC socket as shown.

The artwork of the double-sided PCB is shown in Fig. 12. It is recommended to use IC sockets because the board will be connected frequently to experimental circuits, which may not work as expected, and damage ICs on the extension board quite easily. Along the same train of thought, it is better not to fit the SBC and the extension board in an enclosure. The introductory photograph shows our prototype with the two boards fitted on a length of perspex—a readily accessible system!

Although you may follow this course without building the proposed hardware extensions, it must be noted that the programming examples that make use of the added hardware (files EBTST*. * on the course disk) are an excellent introduction to practical hardware-software interfacing, ranging from simple input/output devices (push-buttons and LEDs) to more complex applications: a capacitance meter, ADC and DAC control, and, of course, LCD control.

Likewise, some of you may be interested in the present hardware only to extend the possibilities of the 80C32 computer or a similar MCS52 microcontroller system. The following procedure is recommended to test the extension board if this is used independent of the programming course. First, test the output function of port P1. This is easiest done by driving the loudspeaker, and making the LEDs flash. Next, check the function of the serial interface after fitting the jumpers appropriately. Proceed with the DAC: output a sawtooth via address 0C000H, and use an oscilloscope to check the waveform and the peak amplitude (approx. 2.5 V). Apply a test voltage between 0 V and 2.5 V to the analogue inputs, and check the function of the comparators by reading the data at ad-

dress 0C000H. The correct function of keys S2 to S5 is verified similarly. Next, carry out a couple of read and write operations to and from 0C002H to check that the parallel input/output interfaces (K3 and K4) work. Finally, test the LCD and the MIDI interface with the aid of small programs. Suitable examples to do so may be found on the course disk.

Next time: we continue the course with assembly language programming.

Table 4. LC display connections

Pin	Function
1	Ground
2	+5 V
3	Contrast (adjust with P1)
4	RS; register select = IOA3 0 = command 1 = data
5	RD; read (active high) 0 = write 1 = read
6	E; enable (active high when address selected) 0C001H = command transfer to/from LCD 0C009H = data transfer to/from LCD
7 to 14	Databus bit 0 to 7

JOIN THE COURSE!

What you need to follow this course:

- a 8032/8052AH-BASIC single board computer as described in Elektor Electronics May 1991. The preferred CPU is a 8051 or a 80C32. Alternatively, any other MCS52-based microcontroller system (but read part 1 of the course);
- a course diskette (order code ESS 1661) containing programming examples, utilities, and an assembler;
- a monitor EPROM (order code ESS 6091).
- an IBM PC or compatible operating under MS-DOS, or an Atari ST with a monochrome display.

Appeared so far:

Part 1: Introduction (February 1992);
Part 2: First 8051 instructions (March 1992).

PULSAR — A REVIEW

by Mike Wooding G6IQM

DESIGNERS of digital equipment are fully aware of the difficulties of testing their designs to confirm that the logic of the design works according to plan. Even more difficult, rather as with computer programs, is the ability to conduct the infinite number of tests to prove that there are no bugs or glitches in the design some of which may only appear when an unusual set of conditions exists, or perhaps only once every billion clock pulses or so.

Furthermore, it is very expensive in time and labour to build breadboarded prototypes to conduct the tests on. The probability of destroying expensive digital devices is even more off-putting! However all is not lost! A recent addition to the professional software packages produced by Number One Systems Ltd. is 'PULSAR' a digital logic circuit simulator program.

Pulsar is a full featured simulator that allows designs to be tested without the need of constructing those expensive breadboards and prototypes. The circuit design can be tested on your PC and modifications made until the circuit functions as required — all without using a soldering iron in anger, or blowing up any expensive ICs.

Pulsar

Pulsar is a digital logic circuit analyser program that runs on PC/XT/AT/286/386/ or 486 computers running under MS-DOS 3.0 or later and with either EGA or VGA graphics, preferably colour. The minimum

RAM requirement is 512 KBytes, and the software is supplied on both 5.25" and 3.5" format floppy discs.

It is almost imperative to have a hard disk drive, as the program keeps a high proportion of its temporary data on disk during operation, and if using a floppy-only based machine the operation of Pulsar will be extremely slow.

The program also supports the use of a mouse and a choice of either 9 or 24-pin dot-matrix printers or HP Laserjet II printers.

The user manual

The comprehensive user manual is packaged in an A5 ring binder, which will allow for the easy insertion of upgrade instructions, personal notes, etc. The opening pages of the manual deal with the installation and running of the program.

The next section in the manual is called 'First Impressions' and gives an overview of the screen presentations and some of the basic commands used to manipulate these screens and move around in them. Once the user is familiar with these basic commands then it's on to the next section, 'The Grand Tour'.

The 'Grand Tour' comprises the greater part of the user manual and takes the user through a step-by-step simulation; from entering the initial design netlist, to the final proven circuit. To assist with the instruction, a predesigned divide-by-three circuit is used as a practical example, from

which a netlist is compiled.

Note: a netlist is simply a file of logic connections between the various devices within a digital circuit and their relative logic states. The libraries available within Pulsar contain netlist outlines for basic logic gates, 74LS series and 4000 CMOS series devices.

After the chapter dealing with the netlist editor and the making of a netlist for the circuit, the section explaining how to actually run the analyser is reached. Firstly, selecting a signal source, or generator, for the input, is dealt with and then a detailed look at the simulated circuit follows.

The 'Grand Tour' then goes on to deal with modifying the circuit to correct any faults, creating generators, selecting printers, combining circuits and using the libraries.

The remaining sections of the user manual deal with customising Pulsar to your exact requirements, using DOS within the program and using the DOS shell. Finally, there are lists and explanations of the three built-in libraries of Pulsar, which will be discussed later.

The analyser


Once a circuit netlist has been created and a suitable generator selected, Pulsar simulates the circuit operation and displays on the screen a timing diagram, such as one seen on a conventional logic analyser. As with a conventional logic analyser, one can also see if any spurious signals are present on the timing waveforms. However, here the similarity really ends.

The display screen is divided into three main areas. The top of the screen contains the main menu, showing Pulsar's top-level commands, with the currently active mode highlighted. The program defaults to the analyser mode on start-up. The other modes are:

Configuration	Customises Pulsar.
Generators	Sets up Pulse Generators.
Libraries	Maintains Component libraries.
!DOS	Manipulates Files and Directories
F1 Help	On-line help information.
Quit	Leave Pulsar.

Also shown in the menu area are the file name and cursor control characters.

 Configuration: this command selects a set of menus which allow the default parameters for Pulsar to be set according to the users choice. The default search paths for



files, the time and date format, etc., can all be preset by the user and the configuration saved.

Generators: this menu allows generators (input signals) to be modified or developed according to the requirements of the simulation.

Libraries: the library command allows the various libraries to be scanned and manipulated.

!DOS: selecting this command displays a menu of basic DOS commands which are available for use without leaving Pulsar. Also selectable is a DOS Shell, which allows you to exit Pulsar to the DOS prompt, but without losing any data currently held in Pulsar. Quitting the DOS Shell returns you to Pulsar, exactly where you left it.

FIHELP and **Quit** are self-explanatory.

The main area of the screen is devoted to the analyser display, with the two moveable cursors.

At the bottom of the screen is a sub-menu of control commands and the time readouts for the cursor positions and the time scale factor of the display area.

With Pulsar you are not limited to how many pods (connecting ports) are available (conventional logic analysers have 8 or 16, sometimes 32, but we are talking expensive here!), as the display shows all the input, clock and output waveforms detailed in the netlist. If you want to see the timing diagram at a particular point in the circuit, you simply add it to the netlist.

Furthermore, another feature of Pulsar which makes it superior to a conventional analyser is that it is not limited to a window in time; i.e., conventional analysers are, to all intents and purposes, not real-time machines, the display is limited to a particular period of time. However, with Pulsar the simulation is continuous, and you can zoom in or out in time, so that even glitches that occur very seldom can be captured.

An essential feature of the zoom facility is that, because you can expand the displayed time zone down to a few nanoseconds if you wish, the actual widths of any glitches or pulses can be measured accurately. To enable this to be achieved Pulsar has two moveable cursors on the display; an 'Absolute' one and a 'Relative' one. Both cursors are easily positioned anywhere on the display by simple keyboard/mouse actions, and at the bottom of the display time values for each cursor are displayed.

The 'Absolute' cursor time display is given as the cursor position in time from the start of the simulation. The 'Relative' time display is given as the difference in time, positive or negative, between the two cursors.

Thus, by positioning the 'Absolute' cursor at the start of a pulse or whatever, and then positioning the 'Relative' cursor at the end of the pulse or zone to be measured, the pulse width or the elapsed time can be read directly. Facilities to enable quick positioning of the cursors are available. A 'Snap' command will ensure that the cursor being moved will align itself exactly with the nearest leading/trailing edge to the mouse/keyboard pointer when moved. A 'Scroll' facility is also available to quickly move the active cursor (the one selected for moving) across the display. A 'Pan' command always centres the display around the currently active cursor, so that when zooming in or out the selected area of the display will always be visible.

An important aspect of Pulsar is the ability to define the signal source, or generator. From a simple 50:50 mark:space square wave at any defined frequency, to an extremely complicated pulse train can be used. When specifying the generator, simply typing anything beginning with a number and containing the letters 'HZ' is interpreted as a simple frequency generator. Typing in anything else will prompt Pulsar to search for a generator file with that name.

Complex generators can be created in the Generator screen and saved with an appropriate file name for use whenever required. Generators in use at any time can be modified in the generator screen, and the effect of the changes on the circuit under analysis displayed immediately on the analyser display screen.

There are more features of Pulsar than I have covered here, but to attempt to explain them and their uses is somewhat pointless as you really need to have Pulsar 'live' in front of you to understand their actions. Suffice it to say that they are well explained in the user manual.

The libraries

As I mentioned earlier there are three in-built libraries in Pulsar, which make the creating of netlists much quicker. The libraries are:

1. PRIM.LIB; a library of primitive logic elements, such as buffers, inverters, AND gates, OR gates, latches, etc.
2. 74LS(1).PLB AND 74LS(2).PLB; a library of over 120 component models covering the low-power Schottky TTL family.
3. 4000.PLB; a library of over 90 component models covering the 4000 CMOS family.

When building up netlists for a circuit, then by naming the component type being used, Pulsar responds by reading the pin and parameter information from the library for the device. All you have to do is enter the various connection details.

Circuit blocks previously designed and tested can be added to the libraries, which is a useful feature if you are using a common circuit time and time again.

A useful feature of the basic logic elements found in the PRIM.LIB is that the transition delay through an element can be varied to emulate circuit and design conditions. A sub-menu from the Generator menu gives various delay parameters that can be modified. A feature of the delay modifiers is that the delays, both minimum and maximum, can be set to values which exceed the nominal values for the device(s) in the circuit. Another useful feature is that the delays can be modified on a global basis, thus allowing the simulation of the circuit to show the results of using different families of logic devices.

Conclusions

Creating a netlist for a circuit design is not as daunting as it may first appear, and never having done so before I followed the instructions, and in a very short time got to grips with the concept and created the netlist for the example circuit. Following the instructions I then connected my generator. Pulsar simulated the circuit and presented the results on the screen.

Upon running the analyser and playing with the many and varied features, it soon became evident that the facilities available are quite extensive. The versatility of the package as a design testing tool is unquestionable. Having used conventional logic analysers in the past I can imagine that in a development environment Pulsar would be far more ideal. The fact that a design circuit does not actually have to be built would be one great advantage. That, coupled with the ability of Pulsar to detect glitches down to 1 picosecond per week for example, proves that the system is a must for digital designers.

Although I barely scraped the surface of Pulsar's capabilities, I can recommend it to anyone engaged in digital design and testing work. Armed with his/her trusty PC and this software, a designer should be able to clear all but the most deeply nested bugs in any complex logic circuit. Highly recommended. ■

I wish to thank Mr. Espin and the staff of Number One Systems Limited for their help and advice, and for the review software.

PULSAR is priced at \$342.00 + \$9.00 shipping and handling and is available from: Number One Systems, Harding Way, St. Ives, Huntingdon, Cambs PE17 4WR, England. Telephone: (0480) 61778. Fax: (0480) 494042.

MOTOR SPEED LIMITER

Design by K. Walraven

Small, compact motors as used in circle saws, lawn mowers and other small electric tools burn out when overloaded. Before that happens, its speed will drop appreciably. If, therefore, the speed is monitored carefully by the circuit described here, burning out of the motor may be prevented.

SMALL motors used in domestic tools are often required to carry out tasks for which they were not designed: a lawn mower mowing a lawn that should have been done a month previously; a circle saw that uses a blade that should have been replaced a dozen or more kerfs ago. As a consequence, the motor is overloaded and gets hot. The thermal protection, if fitted, is then actuated and the motor must be given time to cool off. In many apparatuses, the thermal protection is not close to the motor, but elsewhere in the appliance where it monitors the motor current. Since that current increases proportionally with the load, overload can, indeed, be detected this way.


However, this arrangement does not monitor the temperature of the motor, so that consequently the motor still overheats in spite of three or four cooling-off periods. Nevertheless, the thermal protection will enable the motor (since the current has dropped to a 'safe' value) and the result is often that after a little while the insulation of the copper wire in the motor gives up the ghost. In general, that means that the motor is a write-off; it can be rewound, but that is usually almost as expensive as a new motor.

The circuit described here ensures that the situation does not develop to its fatal end. Even before the motor begins to get warm, the protection becomes active, because it monitors the speed of the motor with the aid of an electronic sensor. When the speed drops as a result of overload, an alarm indicator is actuated. If the user ignores this, the motor is switched off automatically. This ensures that, provided the circuit is set up properly, the motor can never get too hot.

Circuit description

The circuit in Fig. 1 was designed in the first instance for use with squirrel-cage motors that have a nominal speed of 2600 rev/min. Under no-load conditions, this speed will rise to about 2900 rev/min. Below 2500 rev/min, the motor is clearly overloaded and will get warm. There are, of course, squirrel-cage motors with a different nominal speed: for these, the parameters of monostable IC_{1b}-IC_{1c} must be altered slightly. The same applies to the small series-motors used in electric hand-tools. The nominal speed is invariably marked on the housing of the appliance.

 Sensor IC₃ is a reflection sensor that de-



fects the passing of a white dot that the user must place on the motor spindle. Every time the light of the LED reflected by the white dot falls on to the sensor, the motor has travelled one revolution. This (reflected) light causes the sensor's transistor to conduct briefly, whereupon the transistor's collector potential drops. This voltage pulse is converted into a digital pulse by network T₁-IC_{1a}-R₂-R₃-C₁, which is used as a clock for IC_{2a}. A nominal motor speed of 2500 rev/min (which is a normal speed of motors running with a nominal load) corresponds to a pulse rate of about 42 Hz (period=24 ms).

Since the duty factor depends, among others, on the width of the white dot, the signal is divided by two by bistable (flip-flop) IC_{2a}. The output signal of this bistable is a square wave.

Gates IC_{1b} and IC_{1c} form a monostable, whose period is determined by C₂-R₄-P₁. The time during which the output of the monostable is low is set by P₁: a good, practical value when a motor with a minimum speed (overload limit) of 2400 rev/min is used, is about 24 ms.

The output of the monostable is processed by comparator IC_{2b}. The monostable clocks the bistable at a first transition (rising edge). If the input to the bistable at that instant is still high, its Q output also goes high. This

PARTS LISTS

Resistors:

R1 = 330 Ω
 R2 = 470 kΩ
 R3 = 2.2 MΩ
 R4 = 10 kΩ
 R5 = 10 MΩ
 R6 = 3.9 MΩ
 R7 = 1 MΩ
 R8 = 220 kΩ
 R9 = 220 Ω
 P1 = 25 kΩ

Capacitors:

C1 = 1 μF, 63 V
 C2 = 2.2 μF, 63 V
 C3, C6 = 1 μF, 63 V
 C4 = 1 μF
 C5 = 10 μF, 63 V

Semiconductors:

D1-D3 = 1N4001
 D4 = LED
 T1 = BC560C
 T2 = BC517
 IC1 = 4093
 IC2 = 4013
 IC3 = CNY70

Miscellaneous:

S1 = SPST switch
 Re1 = 12 V/10 A coil, c/o contact

indicates that the motor speed has dropped too low and that an error message must be given. The exact motor speed at which an error must be indicated can be set with P₁. The longer the mono-time, the lower the motor speed can drop before an error is indicated.

When the supply voltage is switched on, the comparator, IC_{2b}, is reset automatically, so that power can be supplied to the motor. If the motor takes longer than eight seconds (standard) to come to full revs, some extra seconds can be obtained by pressing reset switch S₁. As long as that switch is operated, the protection circuit cannot disable the supply to the motor.

Networks R₈-C₆ and R₅-C₃ integrate the output of the bistable in the comparator. If the error persists for more than two seconds, the alarm indicator, D₄ will light, and after eight seconds, the motor is switched off altogether. In this way, it should be virtually impossible for a motor to burn out. But . . .

Construction

The circuit is best constructed on a small prototyping board. The reflection sensor must be mounted in the motor housing close to the spindle. The distance between the white

dot and the detector must not exceed a few millimetres. If the spindle is a light colour, so that a white dot would not give enough contrast, try a black dot, or make the spindle black (black insulation tape). Use screened cable to connect the sensor to the circuit to prevent the circuit action being degraded by noise pulses emanating from the motor.

It is also possible to use an optocoupler as the light barrier. A disc with a hole in it must then be mounted securely on to the motor spindle. At each and every revolution of the motor, the LED will then briefly illuminate


the phototransistor. As with the reflection sensor, the optocoupler provides the necessary pulses for proper operation of the circuit.

Output relay Re₁ is connected between the mains supply and the motor. Extreme caution must, therefore, be observed when the relay is energized: touching the mains supply may be fatal!

Fit the circuit in a small, man-made-fibre case. The circuit can be powered simply via a 9-V mains adaptor. Omission of an on-off switch is deliberate: since the motor runs when the relay is not energized, it is easy to forget to switch on the protection circuit. Therefore, *never* forget to plug the adaptor into a mains socket. It makes good sense to connect the adapter to the mains in parallel with the motor, for instance, by linking it to the supply cable of the protected appliance between the mains plug and the appliance's on-off switch.

Alternative reflection sensors	
Sharp	GP2S04
Toshiba	TLP903
	TLP904
TRW	OPB125A
	OPB253A
	OPW703A
	OPW708
	OPW709
Texas	TIL138
	TIL139

 *Mention Elektor
When You Patronize
Our Advertisers!*



APPLICATION NOTE

The content of this note is based on information received from manufacturers in the electrical and electronics industries and does not imply practical experience by *Elektor Electronics* or its consultants.

LAMP/SOLENOID DRIVER UGQ5140K

THE UGQ5140K unipolar Hall effect switch is a monolithic IC designed for magnetic attenuation of low-power incandescent lamps or inductive loads such as relays or solenoids. Included on the chip is a darlington power output that is capable of continuously sinking more than 300 mA. Internal protection circuitry limits surge (lamp turn-ON) or fault currents to about 900 mA. A sensitive magnetic threshold allows the device to be used in conjunction with inexpensive magnets or in applications that require relatively large operating distances.

Each sensor/driver includes a magnetic

 


Fig. 1. Pinout viewed from branded side.

sensing Hall voltage generator, opamp, Schmitt trigger, voltage regulator and an open-collector, high-gain darlington power output stage. The regulator allows use of the device with supply voltages of 4.5–28 V. On-chip compensation circuitry stabilizes switch-

 


Fig. 2. Allowable power dissipation vs temperature characteristic.

point performance over temperature.

Circuit description

The UGQ5140K merges state-of-the-art Hall effect sensing and power driving technologies to allow precision non-contact actuation of incandescent lamps or inductive loads. It is rated for operation over a temperature range of -40°C to $+85^{\circ}\text{C}$ as typically required in automotive applications.

Magnetic operation. As shown in Fig. 3, the output of the device (pin 2) switches low when the magnetic field at the Hall sensor exceeds the operate point threshold (B_{OP}). At this point, the output voltage is $V_{OUT(SAT)}$. When the magnetic field is reduced to below the release point threshold (B_{RP}), the device goes high. The difference in the magnetic operate and release points is called the hysteresis (B_H) of the part. This built-in hysteresis allows clean switching of the output even in the presence of external mechanical vibration and electrical noise.

Current and thermal limiting. Output short circuits may be caused by faulty connectors, crimped wiring harnesses, or blown loads. In such cases, current and thermal limit circuitry will protect the output transistor against destruction.

Current through the output transistor is sensed with a low-value on-chip aluminium resistor. The voltage drop across this resistor is fed back to control the base drive of the

 


Fig. 3. Typical transfer characteristics at $T_A = +25^{\circ}\text{C}$.

output stage. This feedback prevents the output transistor from exceeding its maximum current density rating by limiting the output current to about 900 mA. It may also the output voltage to increase*. In this mode, the device will dissipate an increased amount of power**, and the output transistor will be thermally stressed. This stress, unless protected against (as in the UGQ5140K), will cause the device junction temperature to rise until it fails catastrophically.

Thermal stress protection is provided in two manners: delta temperature protection and junction temperature protection. Under worst-case conditions (Fig. 4 and Fig. 5) if

 


Fig. 4. Output current under short-circuit

 


Fig. 5. Output voltage vs output current.

 


Fig. 6. Typical lamp driver application.

 


Fig. 7. Lamp current vs time.

 


Fig. 8. Lamp turn-on time.

the output is shorted to supply, the output transistor will heat up much faster than the rest of the IC. This condition could cause localized failure in the output transistor. To prevent damage, a delta temperature limiting scheme is used. If a large thermal gradient is sensed across the device, the output transistor base drive is reduced to lower the output current. This reduces the power (heat) generated by the output transistor.

When thermal stresses cause the junction temperature to reach about +165 °C, a linear thermal limiting circuit is activated. This circuit linearly reduces the base drive of the output transistor to maintain a constant junction temperature of +165 °C. In this mode, the output current will be a function of the heat dissipating characteristics of the package and its environment. Linear thermal limiting eliminates the low-frequency thermal oscillation problems experienced by thermal shutdown (ON-OFF) schemes.

The output characteristics are shown in Fig. 4 and Fig. 5. Note the three distinct op-

erating regions: peak limit, delta limit, and thermal limit. In practice, the output voltage and current may exhibit some oscillations during peak current limiting owing to output load characteristics. These oscillations are of very short duration (typically 50 ms) and may be damped with an external capacitor between pins 2 and 4.

When the fault condition that caused the output overload is corrected, the device returns to normal operating mode.

Typical applications

Incandescent lamp driver. High incandescent lamp turn-ON currents (commonly called in-rush currents), can contribute to poor lamp reliability and destroy semiconductor lamp drivers. Warning resistors protect both driver and lamp but use significant power when the lamp is OFF, while current-limiting resistors waste power when the lamp is ON. Lamps with steady-state current ratings to 300 mA can be driven by the UGQ5140K

(Fig. 6) without the need for warming or current limiting resistors. In applications using several sensor/drivers to control multiple lamps, the internal clamp diodes may be connected together to an appropriate current-limiting resistor and simple 'lamp test' switch.

As shown in Fig. 7, when an incandescent lamp is initially turned ON, the cold filament is at minimum resistance and will normally allow a $\times 10$ to $\times 12$ peak in-rush current. As the lamp warms up, the filament resistance increases to its rated value and the lamp current is reduced to its steady-state rating. When switching a lamp with the UGQ5140K, the internal current-limiting circuitry limits the peak current to about 900 mA. The device will stay in the current limit and delta temperature limit modes until the lamp resistance increases to its rated steady-state value (Fig. 7). A side-effect of this current-limiting feature is that lamp turn-on times will increase. Typical lamp turn-on times are shown in Fig. 8.

 


Fig. 9. Typical relay/solenoid driver application.

Inductive load driver. Connecting the internal clamp diode (pin 3) to the positive supply allows relays or other inductive loads to be driven directly, as shown in Fig. 9. The internal diode prevents damage to the output transistor by clamping the high-voltage spikes that occur when an inductive load is turned OFF. An optional external zener diode can be used to increase the flyback voltage, providing a much faster inductive load turn-OFF current decay, resulting in faster dropout (reduced relay contact arcing), and improved performance. The maximum zener voltage, plus the load supply voltage, plus the clamp diode forward voltage should not exceed 35 volts.


* $V_{out} = V_{BB} - (I_{LIMIT} \times R_L)$

** $P_D = V_{out} \times I_{LIMIT}$

Source: Data sheet 27695: Sensor Integrated Circuit UGQ5140K; Sprague Semiconductor Group, 70 Pembroke Road, Concord, New Hampshire 03301, USA.

MILLI-OHM MEASUREMENT ADAPTOR

 Prices of digital multimeters have come down to a level where they are affordable by almost any hobbyist. Although most multimeters offer a fair number of measurement ranges, including, on some of the latest models, frequency and capacitance, they are not really suited to measuring very small resistance values, say, in the milli-ohm range. The adaptor described here overcomes this problem.



Design by Ing. B.C. Zschocke

RESISTANCE values smaller than $10\ \Omega$ or so are notoriously difficult to measure because multimeters often lack a suitable range, or run into tolerances so high that measurement results are at best 'approximate'. Examples of low-value resistors are shunts used with moving-coil meters, and emitter resistors in transistor power amplifiers and power supplies. Typically, such resistors have values in the milli-ohm range, and are almost impossible to measure accurately with the aid of a normal multimeter.

Since low-value resistance measurements will not be required too often, most of you will be reluctant to buy a dedicated milli-ohm meter. Therefore, a simple circuit is described that functions as a $m\Omega$ -adaptor for use with any $3\frac{1}{2}$ -digit digital multimeter. The measurement ranges created by the adaptor are $20\ \Omega$, $2\ \Omega$ and $0.2\ \Omega$ for full-scale deflection. The accuracy that can be achieved depends on the multimeter used and the tolerance of the reference resistor in the adaptor.

The resistor to be measured is connected to the multimeter (set to the $200\ \text{mV d.c.}$ range) as well as to the adaptor. This creates a four-point resistance measurement.

The basics

The basic operation of the circuit is easily explained with reference to Fig. 1. As soon as

the resistor to be measured, R_x , is connected into the circuit, opamp IC1, power FET T1 and resistor R_1 supply a reference voltage U_1 . This means that a measurement current U_1/R_1 flows through the opamp and R_x . In the present circuit, a reference voltage of $100\ \text{mV}$ is used, in combination with selectable reference resistors of $10\ \Omega$, $1\ \Omega$ and $0.1\ \Omega$. This results in measurement currents of $10\ \text{mA}$, $100\ \text{mA}$ and $1\ \text{A}$. The multimeter is set to the 200-mV range, and connected in

parallel with the test sockets on the adaptor.

When the multimeter has an accuracy of $0.1\ \text{mV}$, a resistance of

$$0.1\ \text{mV}/1\ \text{A} = 100\ \mu\Omega$$

can be measured in the highest current range. The simplicity of this type of measurement has one disadvantage: the measurement result can not be read directly from the multimeter, which gives a mV indication. Depending on the selection of the reference voltage and the reference resistor, the conversion boils down to a simple multiplication with 0.001 (or 1 for $\text{m}\Omega$ values), 0.01 or 0.1 . For example, a meter indication of $167.8\ \text{mV}$ in the $20\text{-}\Omega$ range corresponds to a resistance of $16.78\ \Omega$.

Practical circuit

The circuit diagram in Fig. 2 is the practical implementation of what has been discussed above concerning the principle of four-point resistance measurement. In fact, the circuit diagram is hardly more complex than Fig. 1: only the range resistor selection and the reference source are added.

A pseudo-zener diode Type TL431C is used as the reference source. The zener takes its unregulated input voltage from a 9-V (PP3) battery. The reference voltage at the $-$ input of the opamp is set by a multiturm

 


Fig. 1. Principle of four-point resistance measurement. The opamp is assumed ideal here.

 


Fig. 2. Circuit diagram of the mΩ adaptor for digital multimeters.

preset, P1, which forms part of a potential divider connected across the reference source. To eliminate the off-set voltage introduced by the opamp, the voltage at the - input is set to 100 mV minus the off-set voltage. All voltages in the circuit are referenced against the cathode of the TL431C.

The opamp adapts the gate drive of FET T1 until the voltage drop across the selected reference resistor (R1, R2 or R3) equals the reference voltage. When this is achieved, the current through Rx is either 1 A, 100 mA or 1 mA.

An R-C network, R6-C3, and a capacitor, C2, ensure a high d.c. amplification of the opamp, while keeping the a.c. amplification as small as possible to prevent instability.

There are good reasons for using a less than common opamp in this circuit. The TLC2201 from Texas Instruments offers a large drive margin right up to about 0.1 V below the supply voltage, while its off-set voltage remains stable despite changes in the ambient temperature and the supply voltage. Also, its input bias current is very small thanks to the use of input FETs. The large drive margin is essential here to ensure sufficient gate drive for the FET at a relatively

low supply voltage (battery operation).

Given the relatively high measurement currents, the contact resistance of the range switch must be taken into account. That is why the opamp input, pin 3, is connected to the selected measurement resistor via R6 and an extra deck on switch S1, rather than directly to the pole of S1a (point 'A').

The functions of the rest of the components in the circuit are easily explained. Resistor R4 reduces the power dissipation in the FET. It can be made smaller when high contact resistances are to be compensated in the measurement circuit. Push-button S2 and resistor R10 are included to check the correct function of the adaptor and the multimeter ('battery test'). The 1.5-V battery marked 'Batt.1' in the circuit diagram may be a 'mono' (IEC R20) or 'baby' (IEC R14) type, or a 'mignon'-size (IEC R6) NiCd battery. The internal resistance of all these three battery types is sufficiently small. The battery marked 'Batt.2' is a 9-V PP3 (IEC 6F22) power pack.

Diode D2 protects the circuit against back e.m.f. produced when inductances are measured. A protection against external voltages is not provided. Also, be careful

MAIN SPECIFICATIONS

- Suitable for all digital multimeters with a 200-mV d.c. range
- Added measurement ranges: 20 Ω, 2 Ω, 0.2 Ω
- Resolution: 10 mΩ, 1 mΩ, 0.1 mΩ
- Measurement error: 0.1%, 0.2%, 0.5% (depending on DMM tolerance)
- Four-point resistance measurement

when measuring the resistance of transformer windings—the voltage induced in the primary winding may be dangerous!

Construction and adjustment

The adaptor is built on a small single-sided printed circuit board, of which the artwork is shown in Fig. 3. Because of the relatively high measurement current, it is recommended to use fairly thick wires (e.g., 0.75 mm² multi-strand wire). Do not use solder terminals—instead, solder the wires directly to the board, the battery holder and the terminal posts on the front panel. The terminal posts (or 'wander sockets' as they are sometimes called) are types with a horizontal through hole in the threaded shaft. These holes are used to clamp down the wires of the resistor to be measured, while the probes of the multimeter are inserted into the vertical cylinders in the terminals.

To adjust the adaptor, set it to the highest measurement range (reference resistor R3, switch S1a to position '4'). Short-circuit the measurement posts. Connect the multimeter probes directly across reference resistor R3, and adjust preset P1 until the DMM indicates 100 mV. It is recommended to repeat this adjustment from time to time.

In principle, the adaptor may also be adjusted in any of the two other ranges. However, adjustment in the 20-Ω range will provide the highest accuracy because the measurement resistor in this range has the smallest tolerance (0.1%). In any case, fit new batteries before adjusting the adaptor.

A few remarks on the battery voltages: the BUZ10 (T1) starts to conduct at gate voltages between 2.1 V and 4 V. A drain current of 1 A requires a gate-source voltage of 4.5 V or more. In practice, this means that the battery voltage of Batt.2 must not drop below 7 V. Theoretically, the lowest voltage of Batt.1 is

$$I_{\max} (R_4 + R_1 + R_{\max}) = 1 (0.47 + 0.1 + 0.2) = 0.77 \text{ V.}$$

Again in practice, the minimum battery voltage will be higher at about 1 V to allow for the drain-source voltage (U_{d-s}) of T1, wire losses,

Table 1. DMM indication to value conversion

Measurement range (adaptor)	Indication (DMM)	Resistance (Rx)	Conversion
0.2 Ω	200mV	200 mΩ	readout × 1 mΩ/mV
2.0 Ω	200mV	2 Ω	readout × 0.01 Ω/mV
20 Ω	200mV	20 Ω	readout × 0.1 Ω/mV

 


Fig. 3. Track layout (mirror image) and component mounting plan of the adaptor PCB.

and copper track losses.

When long test wires are used between the adaptor and the resistor to be measured, or when high contact resistances are to be taken into account, resistor R4 should be made smaller, e.g., 0.22 Ω .

Practical use

The unknown resistor and the DMM are con-

nected to the terminal posts on the front panel of the milli-ohm adaptor. The reading on the DMM is converted into a resistance value as shown in Table 1.

As already mentioned, care should be taken when measuring inductive components such as large chokes and transformer windings. When an inductive component is disconnected from the adaptor, it may pro-

duce an induced voltage. In the interest of safety, keep to the following order: (1) connect the unknown inductor to the adaptor; (2) connect the multimeter; (3) switch on the adaptor with S1. The opposite order applies when the measurement is finished: (1) turn off the adaptor; (2) disconnect the multimeter; (3) disconnect the inductor. Large inductances, for example, power transformers, are best short-circuited before disconnecting.

Fortunately, the above connection and disconnection order need not be observed when purely resistive components are measured.

Extensions

It is, of course, possible to extend the present adaptor into a dedicated milli-ohm meter: all that is required to do so is a separate power supply and a conventional DVM module. The inputs of the DVM are then connected directly between the pole of S1b and the ground. In this way, the DVM measures the ratio of the unknown resistance to the reference resistance, independent (within limits, of course) of the measurement current, which makes adjustment unnecessary. The accuracy of the instrument thus depends on the accuracy of the DVM module and that of the reference resistor. ■

 


Fig. 4. Suggested front panel design.

920020 - F

COMPONENTS LIST

Resistors:

1	0 Ω 1 0.5%	R1
1	1 Ω 0.2%	R2
1	10 Ω 0.1%	R3
1	0 Ω 47 1W	R4
1	100 Ω	R5
1	10k Ω	R6
2	2k Ω 7	R7;R8
1	82k Ω	R9
1	1 Ω	R10
1	2k Ω multiturm preset	P1

Capacitors:

2	47 μ F 16V radial	C1;C5
1	10nF	C2
2	100nF	C3;C4
1	10 μ F 16V radial	

Semiconductors:

1	TL431C	D1
1	1N4001	D2
1	BUZ10	T1
1	TLC2201	IC1

Miscellaneous:

1	3-pole 4-way PCB mount rotary switch	S1
1	SPST push-button	S2
1	9V battery with clip	Batt.1
1	1.5V battery with holder	Batt.2
1	Heat-sink for T1	
1	ABS enclosure, size approx. 145×90×30mm	
1	Terminal post black	
1	Terminal post red	
1	Printed circuit board	920020

NEW BOOKS

ESSENTIAL CIRCUITS REFERENCE GUIDE

by John Markus and Charles Weston

ISBN 007-040-4631

528 pages

Price \$29.95 (hardcover)

In well over 500 pages, hundreds of electronic circuits are presented in more than 60 logical sections for browsing or reference by electronics engineers, technicians, students, enthusiasts, and experimenters.

Each circuit has type numbers or values of all significant components, an identifying title, brief description, performance data, and suggestions for other applications. The component values are a great help in reading the circuit and redesigning it to meet various other requirements.

Finding a particular circuit is made very easy by an alphabetically arranged table of contents and, if that does not lead you to the wanted circuit, an excellent index will. The book also includes a list of sources, including addresses, which is very convenient if you need more details on a particular circuit.

Essential Circuits Reference Guide is part of the McGraw-Hill Engineering Reference Guide Series that aims at making a wide variety of engineering information and data available to professionals, students, and enthusiasts.

It is very useful as an on-the-job tool and should, therefore, be in the library of everyone interested in, and concerned with, electronics, audio engineering, radio engineering, and computer technology.

To order books directly from McGraw-Hill, call (800) 2MC-GRAW.

PRINTED CIRCUIT BOARD DESIGN WITH MICROCOMPUTERS

by T. J. Byers

ISBN 007-009-5582

320 pages

Price \$39.95

To our knowledge, this is the first book to show how to use the newest PC-based schematic capture and PCB layout programs—such as OrCAD, Schema, and EE Designer—to make professional PCBs.

As can be imagined, this is a book for the practical engineer, designer, and amateur enthusiast. It provides answers to most, if not all, questions that arise during circuit design

and board layout on the computer. The only pity is that it restricts itself to IBM or compatible equipment whereas many professional design departments, and a growing number of hobbyists, now use Macintoshes. Nevertheless, many hints in the book can, no doubt, be used with Apple equipment.

This practical book, liberally illustrated with scores of PCB screens, is a must for anyone involved in the design of PCBs.

To order books directly from McGraw-Hill, call (800) 2MC-GRAW.

ENGINEERING THE HUMAN- COMPUTER INTERFACE

Edited by Andy Downton

ISBN 007-707-3215

438 pages

Price \$58.95 (hardcover)

Engineering the Human Computer Interface is one of the Essex Series in Telecommunication and Information systems which provides a range of modern and forward-looking texts on important topics in this field. Based on the highly regarded postgraduate industrial short courses offered by Essex University, the series emphasizes fundamental concepts and avoids overly mathematical treatment of its subjects.

With the increasing use of computer systems in all walks of life, human-computer interaction has become a vital aspect of the design of any computer-based system. Readers are introduced to design and design tools.

The book also includes an overview of relevant theory and experimental evidence from cognitive psychology and the human sciences. Drawing from the very latest theories and grounded on experimental evidence, the book, written from the technologist's point of view, is essential reading for all computer programmers and engineers.

To order books directly from McGraw-Hill, call (800) 2MC-GRAW.

AUTOMATIC TEST EQUIPMENT

by Keith Brindley

ISBN 075-060-1302

280 pages

Price \$70 (hardcover)

This new book by Keith Brindley demystifies the concept of automatic test equipment

(ATE). Many people, including electronics engineers and technicians, are not quite clear just what ATE entails. This book will tell them.

In a lucid style, the author takes the reader from an explanation of what ATE is, to types of test equipment, test strategies, and the various buses. These buses are important, because an automatic test equipment system is really a computer system that is inter-linked by buses.

The book should be of use and interest to anyone who needs to know and compare the main categories of ATE and make an informed choice which of the many to buy to the best advantage of his workshop or company. Nevertheless, engineers, technicians, and students should also benefit from this general-purpose book, which is at the same time a reference book.

Butterworth-Heinemann

80 Montvale Ave.

Stoneham, MA 02180

(800) 366-2665

DESIGN AND BUILD ELECTRONIC POWER SUPPLIES

by Irving M. Gottlieb

ISBN 08306-8540-5

176 pages—illustrated

Price \$26.95 (hardcover)

After a long(ish) period of basically standardized techniques, the designer of power supplies now has access to new techniques (away from the almost traditional pulse-width modulation) and new components that allow high switching rates with no significant loss in performance. Consequent changes in the author's approach are not changes for changes' sake: the new techniques promise greater operating efficiency, more watts per unit volume, better power line factor, reduced electromagnetic and RF interference, extended reliability, and lower cost.

The book provides much useful guidance and insights to those who are technically knowledgeable and in a position to profit from experimentation and creative engineering in a changing field. As such, it is a must for the engineer, technician, and hobbyist who wants (or needs) a complete and detailed overview of these important changes.

TAB Books

Blue Ridge Summit, PA 17294

(800) 822-8138 ext. 276

LETTERS

MEDIUM POWER AF AMPLIFIER

Since we published the "Medium Power AF Amplifier" (*EEUSA* 10/91, p. 54 and 11/91, p. 44), our design laboratories have received some new, more sophisticated test instruments. Among them is an audio analyzer that gives more precise measurements of THD, IM, TIM, and so on. The internal distortion of this instrument is way below 0.001% (20Hz-20kHz). The instrument also has a two-channel FFT analyzer (sample frequency 192kHz) with built-in 24-bit signal processors. This enables very accurate and rapid analyses of distortion.

Since the instrument was not available during the design of the "Medium Power AF Amplifier," our engineers felt it worthwhile to subject their prototypes to an analysis with the new instrument. Some of the results are shown in *Fig. 1-5*.

It has become apparent that the power transistors specified, that is, the BD911 and BD912 in practice have a much larger spread than we were led to believe by the manufacturers' data sheets. A number of readers have reported that because of this their amplifiers have broken down spontaneously. The reason for this is that one of the three parallel-connected transistors

draws a larger current than the other two and that's the end of the transistors.

To ensure that such mishaps cannot occur, the characteristics of the transistors should be measured before the devices are taken into use. A suitable instrument for this is the "High Current h_{FE} Tester" (*EEUSA* 9/90, p. 40). It is advisable to use three transistors whose characteristics do not deviate from one another by more than about 20%.

It is, of course, also possible to use different types of transistors, for instance, the BDT95 and BDT96, or the BDT85 and BDT86. Furthermore, it cannot be overstressed that before the amplifier is tested, power resistors of 15-22 Ω are inserted into the supply lines. No damage can then ensue and you can ascertain the current split between the three transistors (by means of the voltage across the 0.27 Ω emitter resistors).

THE COMPLETE PREAMPLIFIER

In response to a number of requests from readers, here is a list of technical data for Parts 1 and 2 of "The Complete Preamplifier," (*EEUSA* 1/91, p. 44; *EEUSA* 3/91, p. 18).

THE COMPLETE PREAMPLIFIER—TECHNICAL DATA

INPUT SENSITIVITY	
Microphone input	2.4mV RMS
Line inputs	150mV RMS
INPUT IMPEDANCE	
Microphone input	47k Ω
Line inputs	47k Ω
NOMINAL OUTPUT VOLTAGE	
1V RMS	
OUTPUT IMPEDANCE (TAPE & LINE)	
< 100 Ω	
MAXIMUM OUTPUT VOLTAGE	
95V RMS	
BANDWIDTH (10kΩ LOAD)	
Microphone input	20Hz-20kHz (± 0.3 dB)
Line inputs	5Hz-1MHz (± 0.5 dB)
SIGNAL-TO-NOISE RATIO (INPUTS SHORTED)	
Microphone input	> 80dB (linear)
Line inputs	> 100dB (linear)
CHANNEL SEPARATION ($Z_{SOURCE} < 600\Omega$)	
(line inputs)	> 100dB (1kHz)
	> 70dB (20kHz)
CROSSTALK BETWEEN INPUTS	
(unused inputs terminated in 600 Ω)	> 100dB (1kHz)
	> 80dB (20kHz)
HARMONIC DISTORTION (1V OUTPUT)	
(line inputs)	> 0.003% (20Hz-20kHz)
INTERMODULATION DISTORTION	
(IV OUTPUT) (line inputs)	< 0.005% (250Hz/4kHz; 4:1)

NTSC-PAL-SECAM TRANSLATOR

I am writing to congratulate you on a fine electronics magazine. It is one of the best I've seen for years. The quality of the articles is very high and there seems to be no shortage of variety. Keep up the good work.

I would like to suggest an article for future issues. The article would have an international flavor and I'm sure many people would like to see it. The subject

 


Fig. 1. Harmonic distortion at 1 kHz. Expressed as a percentage: 0.004%.

 


Fig. 2. THD from 20 Hz to 20 kHz at an output voltage of 2.83 V (1 W into 8 Ω).

 


Fig. 3. Frequency characteristic at an output voltage of 2.83 V.

LETTERS

would be about building a converter for the different TV systems. In other words, a need exists for converting a recorded VCR tape from one format to another. For example, an NTSC format to a PAL or vice versa. I'm sure that several readers would find such a project just what they are looking for (on both sides of the ocean). I shouldn't think that this is outside the scope of readers or your staff to produce. In these days, the world is very small and several instances will occur for such a need. I hope to see such an article in the future.

James Creviston
Chanute, KS

Editor replies:

A thought I personally find very attractive. Unfortunately, its execution is rather more complex than would appear. Commercially, it is, of course, a nonstarter: manufacturers the world over are not in the least interested in standardization or their customers' interest. A little while ago, it seemed that

some sense was beginning to prevail, when the International Radio Consultative Committee stated: "... The long-term future of HDTV lies in the digital domain, and equally, the long-term future of HDTV standards should lie with a unique world-wide standard." Alas, politicians, spurred on by manufacturers (voters, money!) have overruled this wisdom and that one world-wide standard does not look likely in our children's lifetime. That, of course, brings us back to your suggestion which, in the light of what I just said, becomes even more important. I will discuss it with our technical

boffins; in the meantime, any readers who have bright ideas on the subject, please let us know.

MAKING YOUR OWN PCBs

I am interested in creating my own PCBs and have bought plain copper-clad boards and attempted to coat them with positive photoresist. I use "Electrolube RP50 Positive Photoresist" spray and caustic soda as the developer. I have the problem of not knowing exactly how long to

 


Fig. 4. Intermodulation distortion 500 Hz: 7 kHz; power ratio 4:1.

 


Fig. 5. Harmonic distortion vs the drive voltage to the output amplifier stages.

decoder

Semiconductor types

Very often, a large number of equivalent semiconductors exist with different type numbers. For this reason, 'abbreviated' type numbers are used in Elektor wherever possible:

- '741' stand for μ A 741, LM 741, MC 741, MIC 741, RM 741, SN 72741, etc.
- 'TUP' or 'TUN' (Transistor, Universal, PNP or NPN respectively) stand for any low frequency silicon transistor that meets the following specifications:

UCEO, max	20 V
IC, max	100 mA
hfe, min	100
Ptot, max	100 mW
fT, min	100 MHz

Some 'TUN's are: BC 107, BC 108 and BC 109 families; 2N3856A, 2N3859, 2N3860, 2N3904, 2N3947, 2N4124. Some 'TUP's are: BC 177 and BC 178 families; BC 179 family with the possible exception of BC 159 and BC 179; 2N2412, 2N3251, 2N3906, 2N4126, 2N4291.

- 'DUS' or 'DUG' (Diode Universal, Silicon or Germanium respectively) stands for any diode that meets the following specifications:

	DUS	DUG
UR, max	25 V	20 V
IF, max	100 mA	35 mA
IR, max	1 μ A	100 μ A
Ptot, max	250 mW	250 mW
CD, max	5 pF	10 pF

Some 'DUS's are: BA 127, BA 217, BA 218, BA 221, BA 222, BA 317, BA 318, BAX 13, BAY 61, 1N914, 1N4148.

Some 'DUG's are: OA 85, OA 91, OA 95, AA 116.

- 'BC 107B', 'BC 237B', 'BC 547B' all refer to the same 'family' of almost identical better-quality silicon transistors. In general, any other member of the same family can be used instead.

BC 107 (-8, -9) families

BC 107 (-8, -9), BC 147 (-8, -9), BC 207 (-8, -9), BC 237 (-8, -9), BC 317 (-8, -9), BC 347 (-8, -9), BC 547 (-8, -9), BC 171 (-2, -3), BC 182 (-3, -4), BC 382 (-3, -4), BC 437 (-8, -9), BC 414

BC 177 (-8, -9) families

BC 177 (-8, -9), BC 157 (-8, -9), BC 204 (-5, -6), BC 307 (-8, -9), BC 320 (-1, -2), BC 350 (-1, -2), BC 557 (-8, -9), BC 251 (-2, -3), BC 212 (-3, -4), BC 512 (-3, -4), BC 261 (-2, -3), BC 416.

Resistor and capacitor values

When giving component values, decimal points and large numbers of zeros are avoided wherever possible. The decimal point is usually replaced by one of the following abbreviations:

p (pico-)	= 10^{-12}
n (nano-)	= 10^{-9}
μ (micro-)	= 10^{-6}
m (milli-)	= 10^{-3}
k (kilo-)	= 10^3
M (mega-)	= 10^6
G (giga-)	= 10^9

A few examples:

Resistance value 2k7: 2700 Ω .
Resistance value 470: 470 Ω .
Capacitance value 4p7: 4.7 pF, or 0.000 000 000 004 7 F ...
Capacitance value 10 n: this is the international way of writing 10,000 pF or .01 μ F, since 1 n is 10^{-9} farads or 1000 pF.

Resistors are $\frac{1}{4}$ Watt 5% carbon types, unless otherwise specified. The DC working voltage of capacitors (other than electrolytics) is normally assumed to be at least 60 V. As a rule of thumb, a safe value is usually approximately twice the DC supply voltage.

Test voltages

The DC test voltages shown are measured with a 20 k Ω /V instrument, unless otherwise specified.

U, not V

The international letter symbol 'U' for voltage is often used instead of the ambiguous 'V'. 'V' is normally reserved for 'volts'. For instance: $U_b = 10$ V, not $V_b = 10$ V.

Mains voltages

No mains (power line) voltages are listed in Elektor circuits. It is assumed that our readers know what voltage is standard in their part of the world!

Readers in countries that use 60 Hz should note that Elektor circuits are designed for 50 Hz operation. This will not normally be a problem; however, in cases where the mains frequency is used for synchronisation some modification may be required.

LETTERS

expose the board to the UV source and upon developing the board different areas seem to develop at different rates so that when one part of the board is fully developed, other parts are not. I have tried between five and fifteen minute exposures to UV light but have not had much luck.

I have also tried "Seno Positiv 100 Photoresist" and "Seno Develop 111 Soft" applicators, but have not had much luck with them either. After exposing the board to UV light, I have attempted to develop the board using the soft developer but I cannot tell when the board is fully developed. The tracks appear as very light green, but when etched in ferric chloride, there still seemed to be some photoresist on other parts of the board that slowed down the etching.

I have considered buying the pre-coated boards, but the extra cost means that I would rather, if at all possible, coat the boards myself to save the money. Are the pre-coated boards worth buying for their better quality or is it possible to get just as high quality results from home coated boards?

Any advice or help is appreciated.

Howard Price
Newport, Gwent

Technical Editor replies:

We cannot see why with all the work you have put into it, you have not been able to obtain satisfactory results. One comment is that the etching tray should be rocked gently during the initial and final stages of etching. Have you studied our article "Make Your Own PCBs" in the September 1990 issue? Are there any other readers who have had and solved, difficulties similar to Mr. Price's? Please let us know.

DISAPPOINTED . . .

I wish to express my disappointment with your publication. I once subscribed to your English issue, which I really enjoyed. So when the USA version debuted, I quickly subscribed. I have had absolutely no luck with any of the articles in any of the issues to date. The closest has been the latest (EEUSA 1/92). The [PC connectors] chart on computer interfaces

would be great if you reissue it with the errors corrected.

1. Connect pin 20 to pin 4 in the DB25 to DB9 cable.
2. Put the door open connection for some floppies.
3. Indicate that the twist in the special IBM ribbon cables is to allow all disk

AED parts kit service

We have been advised that AED of York, who have been running a parts kit service for our projects for some time, have had to discontinue this service owing to lack of demand.

Enquiry from unknown reader

We have received a letter with a number of enquiries from a reader who unfortunately did not state his name and address. The enquiries pertain to the 'Test pattern generator', 'Floppy disk monitor', 'Logic analyser', 'Universal I/O interface', 'Multi-function measurement card', '8032-8052 single-board computer', and 'Wattmeter'. Will this reader please let us know his name and address so that we can reply to his queries.

Electronic control of astronomical instruments

Some time ago, we received a letter from Mr S.J. Dearden of Vernaison, France, asking us to PLEASE publish one or more articles on the electronic control of astronomical instruments, such as a sidereal clock, a star tracker and image camera based on CCD technology, complete with interface, controller, and image processing software, an accurate telescope control system, operated by a remotely located microcomputer, computer-controlled photometer, a model planetarium, and more. At the time, since none of our in-house designers is competent in this field, we wrote to several free-lance designers/authors for possible contributions.

Since the response has been lukewarm, we now use these columns to ask readers, particularly in America (since there is much more activity there in the electronics cum astronomy field than in Europe) if they have any possible contributions as outlined above.

drives to be strapped as B drives. So much more could have been on the chart.

The other almost article was the CD construction article (EEUSA 1/92, p. 36). How can one build a CD player when you can buy a beauty with IR remote for under \$100. I thought it was going to be how the under \$100 goodie could be made with a digital interface to the IBM as a CD ROM reader and give a source code for software to read the result.

Travis Brackeen
St. Louis, MO

Editor replies:

I regret your disappointment, but your letter does not really indicate the source of it. The first two comments on the PC connectors chart are additions rather than corrections, but point 3 is well taken and an indication to that effect would have been useful. As to your comments on the CD player, indeed, there are CD players on the market for under \$100, but what is their quality? Our research indicates that finding a (new) CD player with a deck of the quality of CDM-4 for under \$200 is miraculous. Apart from that, for most home constructors the fun of the project lies in the doing it yourself. Interfacing to the IBM as a CD ROM reader is something for the future(?)

. . . AND DELIGHTED

I appreciate my subscription to EEUSA, especially for the practical applications: these are useful in my courses (*the writer is an associate professor in electrical and computer engineering—Ed*).

I am wondering if you could append a one-paragraph biographical sketch of each author at the end of each article. A photo of the author would enhance it even more. I believe this might serve to inspire your readers even more.

Allen Drake
Durham, NH


Editor replies:

How pleasing to read that our articles are used not only for individual pleasure, but also for educational/training purposes. The

Continued to page 66



Subscriber Services

 

Complete the applicable section(s) below and mail to:
Elektor Electronics USA
PO Box 876
Peterborough, NH
03458-0876

WOULD YOU LIKE TO ... SUBSCRIBE?

YES! Just check the appropriate boxes in the "renew" section and fill in name and address.

RENEW?

Fill in the appropriate sections below. For faster service use your mailing label and subscriber number.

- 1 year at \$28 Check/MO enclosed
- 2 years at \$50 Charge MC/VISA

Canada add \$8 per year postage.
Remit in US \$ only.

SUBSCRIBER NUMBER

NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

MC/VISA _____ EXP _____

CHANGE YOUR ADDRESS?

Fill in your new address to the right and old address and subscriber number above.



MY NEW ADDRESS:

NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

GIVE A GIFT?

What a thoughtful idea! Fill out your name and address above, the recipient's name and address to the right. We'll even send a gift card announcing your gift.



NAME _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

TELL YOUR FRIENDS ABOUT US?

Print their names and addresses below or photocopy this form for them. We'll take care of the rest.

NAME _____

NAME _____

STREET & NO _____

STREET & NO _____

CITY _____ ST _____ ZIP _____

CITY _____ ST _____ ZIP _____

COMPLAIN ABOUT YOUR SUBSCRIPTION?

Yes, it sometimes happens. We try to avoid it at all costs, but if you have a problem, we want to know. Call or write with all pertinent information.



YOU CAN CALL US

(603) 924-9464

Subscription Department
9-4 Business Days
Answering Machine
All Other Hours
FAX: (603) 924-9467
24 Hours

LETTERS

Continued from page 64
use of short biographical sketches of authors, with or without photograph, is far more widespread in the USA than in Europe, where, in fact, it is virtually unknown, except in the journals of learned societies. I find it a commendable practice and will, therefore, endeavor to introduce it. There is a practical problem, often the author is not the designer of a project, particularly if the design originates in our own laboratories, when the article is written by a technical writer on our staff. However, problems exist to be overcome!

S-VHS/CVBS TO RGB CONVERTER

With reference to the above article, published in your October 1990 issue, can you confirm that the Toko inductor (L_2) type listed is correct? Cirkit (Distribution) insist this has never existed and said it probably should have read "119LN-5873." However, that is only

15 μ H, whereas L_2 is shown as 50 μ H. Is L_2 critical or would any 50 μ H inductor be safe to use?

G. Franklin
Canvey Island, Essex

Editor replies:

Contrary to what Cirkit advises, Toko inductor Type 110LNA5783 does exist and its nominal value is 50 μ H. The type indication on the can of the inductor used to build our prototype of the converter reads "A5783" and the device is certainly one from Toko's 119LN series. If you still have problems getting this component, it is available ex-stock from C-I Electronics, PO Box 22089, 6360AB, Nuth, Holland, Fax +31-45-241-877.

Although the adjustment of this inductor is fairly uncritical, a 119LN5873 would not work as its inductance is too low.

As an aside, the adjustment of P_1 appears to have caused problems to a number of con-

structors. It appears that the PLL will not lock and IC₇ cuts off all the video when the frequency is set only a couple of hertz above the target frequency of 16,625Hz. The best setting of P_1 is, therefore, a little too low (clockwise), whereupon the picture will appear after a few seconds.


DIGITAL STORAGE SCOPE?

I have read your magazine for some time now and find the standard and coverage of constructional articles excellent.

However, having recently started the microcomputer-controlled logic analyzer as a long-term project (money is tight), I thought that a matching digital storage oscilloscope with a full set of bells and whistles (so to speak) would make a good series of articles: using the computing power of a PC would make a very versatile instrument. I haven't enough know-how to design such a device—I leave that

FIND THE LATEST ISSUE OF

ELEKTOR ELECTRONICS USA

 

AT THESE LOCATIONS

Tri-Tek
9014 N 23rd Ave 11
Phoenix, AZ

Gateway Electronics
9222 Chesapeake Dr
San Diego, CA

Henry Radio
2050 S Bundy Dr
Los Angeles, CA

HSC Electronic Supply
4837 Amber Lane
Sacramento, CA

HSC Electronic Supply
3500 Ryder St
Santa Clara, CA

Gateway Electronics
2525 N Federal Blvd
Denver, CO

Tapco Engineering
1639 47th St NE
Cedar Rapids, IA

RJM Electronics
4204 Overland Rd
Boise, ID

Gateway Electronics
8123 Page Blvd
St Louis, MO

Cody Books Ltd.
1122 Fir Ave
Blaine, WA

RP Electronic Co
2113 W 4th Ave
Vancouver, BC
CANADA

Powell's Technical Books
33 NW Park
Portland, OR

If you prefer home delivery use
the handy subscription card enclosed.

ELEKTOR BINDERS

Keep your valuable copies in perfect condition in these Elektor Binders. Each binder holds 11 issues with wires so you don't have to punch holes in your magazines.

High quality, book binder cloth construction. The logo is stamped in gold on a dark green background.



each \$12
three or more, \$10 each

Shipping: Postpaid in US.
Canada and Caribbean, please add \$4 for one, \$2 for each additional binder.
Overseas, please add \$4 per binder.

LETTERS

to greater minds—but wonder if you would give it some thought.

Ian Beeby
Bolton, Lanes

Editor replies:

Another bright idea, but I cannot say if and when we can bring it to fruition. We'll do our best. Thanks for your good wishes.

RC-5 CODE IR RECEIVER

I would like to express my gratitude for your article in the January 1992 issue entitled "Universal RC5-code Infra-red Receiver." I have been curious as to exactly how they work for some time, and found that information regarding operation was somewhat bare, I have had ideas for controlling my audio/visual components, most of which seem best adapted for using pre-existing control

functions through infra-red links. Yours is the first magazine that has dealt with and explained this topic. During the time that I have been a subscribing member, I have found your magazine to have the most relevant, well-applied articles of electronics magazines. It is nice to know that what I'm reading is also being read in at least thirteen different countries. I hope that you maintain the level of excellence that you have so far exhibited.

David G. Burd
Miami, Florida

Editor replies:

Thanks for letting us know that you appreciate our magazine—letters like yours make producing the magazine even more worthwhile than it already is. To make it even nicer to know: the articles are read in at least 50 different countries (they are written in one of four languages and translated into nine others.)

SAVE DECODER

Sir—I am still waiting for part 2 of the "SAVE decoder" that you promised a very long time ago. Also a long time ago, you said that in the near future you would publish a multi-standard MAC decoder. Please tell me why you have still not published either of these interesting projects.

C. D. Nielsen
Roskilde, Denmark

Editor replies:

We are under legal restraint not to publish the second part of "SAVE decoder" as advised in the March 1990 issue.

As regards the multi-standard MAC decoder, development has been delayed because of the hesitant attitude of the European Commission on the introduction of the MAC system.

The Commission has only just confirmed that it will adopt a number of proposals

We Enjoy Hearing From You.

Elektor Electronics USA is a place for readers to meet and discuss ideas, projects, and challenges. When you write, please include a self-addressed envelope with stamp attached with a clip if you expect a reply. If the author lives outside of the US, please include two International Postal Reply coupons (available at your post office) instead of stamps on your envelope. Because of space limitations, we do reserve the right to edit all letters. Although we read and note all letters, only those of general interest are selected for publication. When responding to an article, please cite the issue of the magazine, the name of the article or department and the page number.

Address all correspondence to:

Letters Department
Elektor Electronics USA
Box 876
Peterborough, NH 03458-0876

ARE YOU MOVING?

Remember to include us on your mailing list to keep us in your mailbox. Let us know about your new address four to six weeks in advance, that way you won't miss one exciting issue of **ELEKTOR ELECTRONICS USA..**

WRITE US!
Elektor Electronics USA
PO Box 876
Peterborough, NH 03458-0876

CALL US!
(603) 924-9464

BUT LET US KNOW. Please send us your new address.

RECOMMENDED SOURCES FOR ELEKTOR ELECTRONICS USA EUROPEAN PARTS

Borbely Audio
Erno Borbely
Melchior Fanger Strasse 34A
8031 Neu-Gilching
Germany
Tel 49-8105-5291
FAX 49-8105-24605 (24H)

Bull Electrical
250 Portland Road
Hove
Sussex BN3 5QT
United Kingdom
Tel 44-0273-203500
FAX 44-0273-23077

C-I Electronics
PO Box 22089
6360 AB Nuth
The Netherlands
FAX 31-45-241877

DIL Elektronika
Jan Ligthartstraat 59-61
3083 AL Rotterdam
The Netherlands
FAX 31-10-4841150

EasyTech, Inc.
2917 Bayview Dr.
Fremont, CA 94538
Tel (800) 582-4044
FAX (800) 582-1255

ELV France
BP 40
F-57480 Sierck-les-Bains
France
Tel 33-82-83-72-13
FAX 33-82-83-81-80

Meek It Electronics
Rob Planken
Paveljoensgracht 35A
2515 BL Den Haag
The Netherlands
Tel 31-70-609554
FAX 31-70-397-9707

Technomatic
Technohouse
486 Church Lane
London NW9 8UF
United Kingdom
Tel 44-081-205-9558
FAX 44-081-205-0190

made in this respect by the European Parliament. It is now saying that existing satellite stations must, in addition to whatever system they are now using, simultaneously broadcast in D2-MAC as from 1 January 1995.

Development of the decoder is now going ahead as a matter of some urgency.

EXPENSIVE PCBs

By the way, you're doing a great job. Best magazine of this type since *Popular Electronics* in the mid 50s. Don't change a thing. One small suggestion, though: is there any way to lower the costs of PC boards related to your projects? Quantity discounts? Something like discounts on college meal tickets or gift certificates.

V. Goodwin
Charlotte, NC

Editor replies:

Thanks for your kind words—we'll do our best to keep up the standards. Your comments as to prices for PCBs have been passed to our commercial department.

TEACHING VALUE OF PROJECTS

Although many projects in your magazine have considerable teaching value, some of that may be lost through lack of including (or at least mentioning) variants or (even at a later date) possible add-ons.

J. Trethowan
Bradford, UK

Editor replies:

This is an aspect pointed out to us before by a number of teachers. Quick action may not be possible, but the point has been made to our designers and technical staff.

AM BROADCAST RECEIVER

I was most interested in the "AM Broadcast Receiver" article (*EEUSA* 10/91, p. 52) send congratulations to the author for presenting such a novel approach to the subject. I am considering the construction of the circuit, but would appreciate clarification of two points regarding Fig. 5:

1. C47 and C48: I can find no detail on these capacitors in the text as the asterisks suggest there should be.

2. IC3 4046 phase-locked loop: the connections shown for the 4046 suggest that

LETTERS

only the phase comparators I and II sections of the IOC are used in this application, but *not* the VCO and source follower. Is this correct? If so, I do not understand the function of the "inhibit control" (pin 5) as my understanding is that this control only has effect on the VCO and source follower sections of the IC and *not* the phase comparator sections.

3. Finally, will the PCBs be made available?

P. F. Claret
Staines, UK

Technical Editor replies:

1. Capacitors C47 and C48 may have a value of up to 100pF, but they may not be necessary at all with some types of 455kHz resonator. This can only be established by trial and error in any particular case.

2. Your analysis of the operation of the 4046 PLL in this circuit is correct. In this application, however, the INH pin of the IC has no function and may be tied permanently to the positive supply rail to reduce the current drain. Nevertheless, the connection suggested in the article is not incorrect in any way.

3. Regrettably, PCBs will not be available for this project.

EPROM PROGRAMMER

I have read your magazine with interest for over a year and for some time now

have been hoping to see an article on an EPROM programmer for an IBM-compatible PC. Is anything of this nature planned for the near future? If not, could you please consider it some time?

Tony Hughes
Redditch, Worcs., UK

Editor replies:

I regret there is no EPROM programmer in our plans for the next six months, but we will bear your request in mind for the six months after that. In the meantime, have you considered the "Mini EPROM Programmer" (*EE*, 1/90, p. 14)?

PAL PROGRAMS

It is very frustrating that you don't publish the full program of the PAL ICs for some of your designs. To me, it makes the whole design seem incomplete. If a particular program is too long to publish in your magazine, would it be possible for me to order it in the usual way?

G. Wilson
Christchurch, New Zealand

Editor replies:

We have had letters with the same complaint from quite a few readers. There are a number of reasons we cannot publish these programs; size you have mentioned already. Another is copyright. You and other readers may note that, if we can legally do so, we will supply such programs if they are ordered on the order form elsewhere in this issue.

INDEX OF ADVERTISERS

All Electronics Corporation	9	Videos	7
Baylin Publications	CV III	Vinyl	8
Capital Electro-Circuits	CV III	PCBoards	9
Deco Industries	CV III	Project Pro	CV III
EasyTech	CV IV	ELECTRONICS SCENE/NEW PRODUCTS	
Kelvin Electronics	CV III	Ameritron	12
Meadowlake Corporation	CV III	Analog Devices	13
Mondo-tronics	9	Audio Engineering Society, Inc.	13
Ocean State Electronics Corporation	CV II	Communications Specialists, Inc.	13
OLD COLONY SOUND LAB		Global Specialties	12, 13
Books	69, 70	Industrial Fiber Optics	13
Cassettes	4	Logical Systems Corporation	12
CDs	4-6	Midland LMR	12
EPROMS, Etc.	69	Optoelectronics, Inc.	13
Front Panel Foils	69	PMC Products	13
Parts Sources	67	Polydax Speaker Corporation	12
Printed Circuit Boards	69	SMPTE	12
Software	69	Startek International, Inc.	12

TERMS OF BUSINESS

PRICING

Prices, except as noted, include shipping in the continental USA. The minimum order is \$10. A \$2 service charge will be added to orders of less than \$10. Prices are subject to change as our costs change. WE RESERVE THE RIGHT TO MAKE PRICE CHANGES WITHOUT NOTICE.

TELEPHONE ORDERS

Telephone orders are welcome between the hours of 9:00 a.m. and 4:00 p.m. EDT, Monday-Friday. Orders for parts are to be made on the ORDER FORM provided. Payment for telephone orders is by MC/VISA only. Our TELEPHONE ORDER NUMBER IS (603) 924-6371 or 924-6526. Our answering machine for MC/VISA orders during non-business hours is (603) 924-6371. FAX: (603) 924-9467 (24 hours).

PAYMENT

All remittances **MUST BE IN US FUNDS DRAWN ON A US BANK**. Payment for telephone orders must be made by MasterCard or VISA. Mail order payment may be made by MC/VISA, money order, cashier's check or personal check. If payment is made by personal check, allow up to 2 weeks for clearance before order is shipped. Should check be returned for any reason, there will be a \$10 charge.

SHIPPING

Unless noted, freight is prepaid by Old Colony. All orders shipped USPS first class mail or by UPS. Allow two to three weeks for delivery. Please inquire about appropriate funds for special handling (UPS next day or second day). UPS requires a street address. If you cannot receive UPS delivery, please in-

clude an extra \$2 for insured service via Parcel Post. We cannot accept responsibility for safety or delivery of uninsured Parcel Post shipments. **Absolutely no COD shipments.**

BOOKS, RECORDINGS, CDs, and SOFTWARE

The shipping/handling charge for the US is \$2.00, plus 75¢ each additional item. In Canada, please add \$4.50 for the first item, 75¢ each additional. For orders to be shipped outside North America, add 20% to the total order to cover shipping. **No returns.** According to the Connecticut Dept. of Revenue Services, Regulation #27, Section 12-426-27, in order to sell software to residents of Connecticut, we must register with the department as well as collect taxes for the state from the purchaser. We regret to inform customers that we will not sell software to anyone from Connecticut. ■

BOOKS FROM ELEKTOR ELECTRONICS USA

301 CIRCUITS

This book follows the theme of the first in this series, *300 Circuits* (now out of print). It contains over 300 assorted circuits first published in the 1979, 1980, 1981 summer issues of *Elektor Electronics*.

The circuits range from the simple to the more complex and are described and explained in straightforward language. The book is a comprehensive source of ideas and construction projects for anyone interested in electronics.

ISBN 0-905705-12-2
BKAA11 Price \$12.50

302 CIRCUITS

The popularity of this book is shown by its having been reprinted no fewer than three times. It offers a selection of the most interesting articles from the 1982, 1983, 1984 summer issues of *Elektor Electronics*.

In it you will find circuits for audio and video; car, cycle, and motorcycle; home and garden; receivers and aeriads; hobbies and games; measuring and testing; oscillators and generators; current sources and power supplies; microcomputers and music electronics; and a miscellany of other interesting subjects.

ISBN 0-905705-25-4
BKAA12 Price \$12.50

303 CIRCUITS

Like its predecessors, *303 CIRCUITS* offers a comprehensive collection of practical ideas, concepts, and developments in the gamut of electronics. Unlike its predecessors, the book is arranged in 11 subject sections to make it easier for the reader to find that long-sought circuit.

In well over 300 pages, the book offers 32 Audio and Hi-Fi projects; 14 circuits for Car and Bicycles; 43 Computer & Microprocessor circuits; 11 Electrophonic projects; 24 HF and VHF circuits; 16 circuits for a number of hobbies and pastimes; 54 projects for Home and Garden; 29 Power Supply circuits; 29 circuits for Test and Measurement equipment; nine TV and Video projects; as well as 42 Design Ideas.

ISBN 0-905705-62-2
BKAA13 Price \$15.90

304 CIRCUITS

The latest in *Elektor's* famous "300" series, BKAA18 contains 304 innovative circuits and descriptions broken down as follows: 36 audio/video, 19 high frequency, 36 hobby, 36 home and garden, 9 music/electrophonics, 32 computer/microprocessor, 19 generator/oscillator, 33 test and measurement, 30 power supply, 13 car electronics, and 41 miscellaneous. Arranged by subject for ease of use.

ISBN 0-905705-34-3
BKAA18 Price \$19.95

DATA SHEET BOOK 2

Like its predecessor (now out of print), this book offers concise, relevant, and rapidly accessible information, which is both practical (e.g., the pin-out of a device) and informative.

The book contains data on integrated circuits as well as on discrete transistors and diodes. Moreover, it gives an introduction to fast (HCMOS) devices and a review of the new symbolic logic as laid down in British Standard BS939: Section 21 (IEC Standard 617-12).

The final part of the book deals with a number of computer chips, such as memory devices (including programming information for these) and I/O circuits. This section also includes data on a number of non-digital discrete and integrated devices, such as op amps, as well as on some microprocessor peripherals (e.g., the 6522 VIA, the 6580 ACIA, and the 8355A PPI).

ISBN 0-905705-27-0
BKAA14 Price \$16.50

DATABOOK 3: PERIPHERAL CHIPS

This book lists the most important design data of peripheral chips whose type numbers and functions relate them unambiguously to a microprocessor in the same family. All listed devices form part of families based on widely used microprocessors or microcontrollers. Their most evident application will therefore be in conjunction with the associated microprocessor. This should, however, not be taken to mean that a peripheral cannot be used in another application. Far from it, as witness the familiar type MC146818A real-time clock and the type MC6845 cathode-ray tube controller. It deserves a place on the bookshelf of anyone concerned with the design, maintenance and servicing of microprocessor-controlled electronic equipment.

ISBN 0-905705-30-0
BKAA15 Price \$17.95

MICROPROCESSOR DATA BOOK

This book has come about because of a need by *Elektor Electronics* engineers, technicians, and editorial staff of a ready reference work on the most important microprocessors. This implies that it does not only contain information on the latest devices, such as the transputer, but also on older, well-established types, such as the Z80 and the 6800.

A general description, hardware block schematic, software structure, DC characteristics, and instruction sets are given for over 70 microprocessors. To prevent the book from becoming unwieldy (and to keep costs down), timing diagrams and AC characteristics have, however, been omitted. The detailed information on all manufacturers mentioned will, however, enable any additional information to be obtained quite readily.

Included in the book are, among others, the 68000 series; the 6502 family; the Z80, 8080, and 8085; Intel's 8086, 80186, 80188, 80286, and 80386; the NS32XXX series, and the INMOS transputers.

ISBN 0-905705-28-9
BKAA16 Price \$17.90

DATABOOK 4: PERIPHERAL CHIPS II

This further volume in *Elektor Electronics' Microprocessor Data Book* series deals with general peripheral chips that, at least as far as their type-coding is concerned, do not belong to a specific family of microprocessors. There are so many of these, however, that only a portion of them can be dealt with in one book. Those contained in this collection have been chosen carefully on the basis of their practical application and frequency of use. Complete data are given for coprocessors from the 80 series (AMD, Cyrix, ITT, Intel, Weitek); real-time clocks from MEM, OKI, Statek, National Semiconductor, and Dallas Semiconductor; transmitters and receivers of serial interfaces RS232, 422, 423, 485 from Motorola, Newport Components, Maxim, Texas Instruments, National Semiconductor, Dallas Semiconductor, and Linear Technology; UARTS, DUARTS, and QUARTS (i.e., programmable ICs intended for data transfer); and the CS8221 set of ICs from Chips & Technology that are used in a great number of PC mother boards (also included is the data sheet of associated software LIM 4.0 for the management of the Extended Memory System).

Apart from the actual data, the book contains much other useful information, such as comparisons between and second sources for all important IC families; addresses of manufacturers and their representatives; and overviews of all peripheral chips (including many that could not be included in this book) that are available from various manufacturers.

ISBN 0-905705-32-7
BKAA17 Price \$17.95

DATABOOK 5: APPLICATION NOTES

This book presents a series of application notes and design briefs that cover a wide variety of subjects. Apart from a number of applications related to specific components, the book also includes articles on basic design theory and the practical use of certain components. For example, there is an article reprint from Advanced Micro Devices that provides information on programming the motion of a stepper motor with the aid of a PAL (programmable array logic). Similarly, an article reprint from Motorola presents an overview of protocols and conventions used for serial communication between computers.

The application notes complement the theoretical sections by discussing the use of components related to current electronics technology. In a number of cases, this technology is ahead of the practical application, and the product is so new that an application note has not yet been published by the manufacturer—for examples, Analog Devices' description of a Continuous Edge Graphics (CEG) digital-to-analog converter (DAC), and that of a NICAM (near instantaneous companding audio multiplex) decoder chip developed by Micronas of Finland. Given the complexity of the practical circuits that could be developed on the basis of these ICs, all the relevant data sheets are included for easy reference. The book also includes a short list of manufacturers' logos that should be helpful in identifying unknown components, as well as a worldwide address list of manufacturers and distributors/representatives for the products which are discussed.

ISBN 0-905705-33-5
BKAA24 Price \$17.95

SPECIALS!

- BKAAZ/1 BKAA11, 12, 13, 18: all 4 for \$49.00 (Save \$11.85!)
BKAAZ/2 BKAA14, 15, 16, 17, 24: all 5 for \$74.95 (Save \$13.30!)
BKAAZ/S Complete *Elektor* library: all 9 for \$114.95 (Save \$34.15!)

These books are all available direct from *Elektor Electronics USA* through the Readers Services, from a number of bookshops and electronics retailers in the US and Canada, and from selected bookshops throughout the world. Special prices are those of *EEUSA* only.

PC BOARDS

- 24 hr. d.s./72 hr. m.l.
- Prototype to Production
- FR-4, Plated-Thru Teflon, Polyimide
- UL Recognized



Call us for an instant quote
24-hr. modem for easy transfer of
Drill & CAD files.
Free Tooling On First Order!
Superior Quality at Competitive Prices!

CAPITAL ELECTRO-CIRCUITS

7845-J Airpark Road
Gaithersburg, MD 20879
(301) 977-0303
Fax: (301) 990-6715





KELVIN PRO 400
\$69.95

FREQUENCY COUNTER TO 20MHz IDEAL FOR TROUBLE SHOOTING AC/DC VOLTAGE RANGES AC/DC CURRENT RANGES 5 FREQUENCY RANGES 5 CAPACITANCE RANGES

30 DAY MONEY BACK GUARANTEE!

LOGIC TEST CONTINUITY TESTERBUZZER DIODE CHECK TRANSISTOR hFE TEST LED TEST VERIFY COORDIN DISPLAY - 3 1/2 DIGIT LCD ACCURACY - 0.5% IMPEDANCE - 10 Mega Ohm

PROTECTIVE CARRY CASE for PRO 400 Stock No. 990094 **\$9.95 ea**

2 YEAR WARRANTY

BEST BUY NEW Series II

FLUKE 79 with Capacitance	\$169
FLUKE 87 True RMS	\$289

NEW! SCOPEMETER™ 90 SERIES
HAND HELD, 50 MHz, DUAL CHANNEL

FLUKE 93 ScopeMeter	\$1095
FLUKE 95 ScopeMeter	\$1395
FLUKE 97 FULLY LOADED	\$1695




KELVIN Electronics
10 Hub Drive, Melville, NY 11747
(516) 756-1750 • 1 (800) 645-9212 • FAX (516) 756-1763

VISA
M/C

AUTHORIZED DEALER

SATELLITE RECEPTION ELECTRONICS

 

- Design, operation and repair of satellite receivers, modulators, antennas, feeds & LNBS
- Complete circuit diagrams of four satellite TV receivers
- Encryption & scrambling methods

TO ORDER - Send \$40 plus \$3 s/h to:
Baylin Publications
1905 Mariposa, Boulder, CO 80302

CREDIT CARD orders also accepted
303-449-4551

356 pages, 8.5 x 11"

Request our FREE CATALOG of other books about Satellite & Private Cable TV

HEAR EVERY SOUND OVER 1 MILE AWAY!



Simply attach the **VT-75** microtransmitter to any 3V to 12V battery and you can hear every sound in an entire house over 1 mile away! Super-sensitive circuit on a single chip even picks up footsteps from across a large room. Tunable from 80 to 130 MHz.

Hear everything on any FM radio or wideband scanner tuned to the "secret" frequency you select. Unlimited uses for security, baby monitor, remote mic, etc. **Not a toy.** The **VT-75** meets many U.S. Gov't Military Specs and with 100mW RF output, it is the smallest, most powerful miniature transmitter you can buy. Easily assembled even by a youngster in only 5 minutes and performs so well that it is the only miniature transmitter available *anywhere* that comes with a **full unconditional moneyback guarantee!** Complete kit includes **VT-75** microtransmitter chip, miniature microphone, 9V battery connector and instructions - **\$49.95 + \$1.50 S&H** or save- buy 2 for **\$45.00** each with free S&H! Call toll free or send money order, Visa, or MC acc't number for immediate shipping by U.S. Mail. COD's add \$4. Checks allow 21 days.



DECO INDUSTRIES*

BOX 607
BEDFORD HILLS, NY
10507

1-800-759-5553 (U.S. ONLY) ALL OTHER 914-232-3878

MAKE CIRCUIT BOARDS THE NEW, EASY WAY



WITH TEC-200 FILM

JUST 3 EASY STEPS:

- Copy circuit on TEC-200 film using any plain paper copier or laser printer
- Iron film on to copper clad board
- Peel off film and etch

SATISFACTION GUARANTEED


convenient 8 1/2 x 11 size
5-Sheets for \$3.95 10-Sheets only \$5.95
add \$1.50 postage NY res. add sales tax

The MEADOWLAKE Corp.


Dept H, P.O. Box 497, Northport, NY 11768

ELECTRONIC ENCLOSURES

 
Everything to complete your project - From initial concept to finished product!



Rack Mount

 


Universal

 

Split Case

 Complete line of Enclosures in Aluminum, Steel or ABS, Hardware, Silkscreening, Tools, Custom Fabricating
Call for our FREE Full Color Catalog
(800) 800-3321 or (216) 425-8888 (216) 425-1228 Fax



Cage & Preamp Enclosures



Knobs & Parts



Linear



ABS



Die Cast

Project Pro

1710 ENTERPRISE PKWY. TWINSBURG, OHIO 44087

WORD OF MOUTH

Helps us grow, means a stronger publication that can do more of the things that need doing in the pursuit of better electronic systems. If you have friends, associates, relatives or even enemies who share your enthusiasm for ELEKTOR ELECTRONICS tell us their names and addresses, and we will send the word along. THANKS

EASY ORDER
1-800-582-4044

EASYTECH

THE ELECTRONICS SOURCE

EASY FAX
1-800-582-1255

EUROPEAN TRANSISTORS

Yes, EasyTech will be expanding its range of European devices continuously. Keep watching for the parts you need for your Elektor project.

Order #	Price	Polarity	Vce	IC (mA)	Peak (W)	Ft (MHz)	Package
BC328	.25	PNP	.25	800	0.8	100	TO-92
BC547	.20	NPN	.45	100	0.5	300	TO-92
BC549	.20	NPN	.30	100	0.5	300	TO-92
BC549C	.30	NPN	.30	100	0.5	300	TO-92
BC557	.20	PNP	.45	100	0.3	150	TO-92
BC558	.20	PNP	.25	100	0.3	150	TO-92
BC639	.45	NPN	.80	1000	1	130	TO-92
BC640	.45	PNP	.80	1000	1	50	TO-92
BD139	.55	NPN	.60	1000	8	250	TO-126
BD140	.55	PNP	.80	1000	8	75	TO-126
BD681	1.05	NPN	100	4000	40	1	TO-126
BD682	1.05	PNP	100	4000	40	1	TO-126
BF199	.95	NPN	.25	25	0.23	550	TO-92
BF469	.95	NPN	250	50	1.8	60	TO-126
BF470	.95	PNP	250	50	1.8	60	TO-126

DATAK - PHOTO ETCH™

ER4 PHOTO ETCH™
Printed Circuit Kit (Complete)

Use this kit to generate your own 1:1 artwork, then use the patented Pos-Neg™ process to make a photo negative, sensitize and expose a blank copper board, then develop and etch it. Like to build magazine projects? Make a film positive and negative from the magazine PC art illustration, expose your sensitized copper board and etch. The magazine page is not destroyed in this process. No darkroom or camera is required.



All necessary materials are included - steel 5" x 6" print frame, Pos-Neg film, film processing pack, yellow filter, 4 oz. negative-acting etch resist, 16 oz. resist developer, blank copper circuit boards, dry concentrated etchant, 1:1 resist patterns and tapes, and complete instructions. Shipped via UPS ground only.

ER19 - Photo Etch Light Bulb Set (To suit ER4)

Why search for the special bulbs you need to expose the Pos-Neg™ copy film and photo resist contained in DATAK's ER4 set? This bulb set contains both the 3400°K white light and the 4800°K long wave UV content flood-lamps recommended by the manufacturer. Buy this set with your ER4 to insure perfect results every time.

Order #	Price	Description	Weight
ER4	34.95	PHOTO ETCH™ Printed Circuit Kit (Complete)	3.93 lbs.
ER19	16.45	Exposure Lamps (Light Bulb Set)	.5 oz.

DATAK - REFILLS AND ACCESSORIES

Order #	Price	Description	Weight
ER2	7.95	Direct Etch™ Resist Set, 8 Sheets, 2 Tapes	0.7 oz.
ER3	3.49	Dry Concentrated Etchant, 1/4 pound	5.1 oz.
ER5	7.95	6 Sheets 5" x 6" Pos-Neg™ Film	1.2 oz.
ER6	4.69	Film Process Chemical Pack	5.9 oz.
ER8	4.89	Negative-Acting Resist Developer, 16 oz.	1.25 lbs.
ER9	7.95	2 Sheets 8" x 11" Pos-Neg™ Film	1.8 oz.
ER10	13.95	9" x 12" Contact Printing Exposure Frame	3 lbs.
ER11	4.89	Copper Clad Circuit Boards	2.7 oz.
ER12	7.95	Power Etch Pump (Complete)	11.9 oz.
ER13	3.89	Assorted Donut Pads, 4 Sheets	0.5 oz.
ER14	3.89	DIP, FLAT PACK and SO Pads, 4 Sheets	0.4 oz.
ER15	1.95	Direct Etch™ Resist Pen	0.4 oz.
ER18	4.95	TINNIT™ Electroless Bright Tin Plate, 1 Pint Size	2.5 oz.
ER181	17.95	TINNIT™, 1/2 Gallon Size (Bulk Pack)	9.3 oz.
ER71	7.95	Negative-Acting Photo Resist Liquid, 4 oz.	7.6 oz.

"KESTER" SOLDER



KS4027/4053
•Excellent Wetting
•Non-Corrosive
•Non-Conductive
Flux Formula



KS0415

Features 60% tin, 40% lead alloy, with "44" rosin flux. Specifically designed for repairs to electronic components or circuit boards which are sensitive to excess heat. Also features a low melting temperature (374°F) and a unique fluxing action.

A unique 62% tin, 36% lead, 2% silver alloy with a rosin flux core. Specially formulated for soldering small, silver-coated surface mount components to circuit boards. The .020" diameter is well-suited for the close spacing of components.

Order #	1-9	10+	Description	Gauge	Weight
KS4027	10.95	9.95	60/40 Rosin Cored Solder	.21	1 lb.
KS4053	10.95	9.95	60/40 Rosin Cored Solder	.18	1 lb.
KS0415	3.45	2.95	Silver Solder	.24	1 oz.

TEST LEAD KIT

This kit is an essential addition to your tool kit, whether you are a field technician, student or hobbyist. Remember all those occasions when you needed that extra test lead or two!!



TLK1
(6 Lead Set)



TL108

NEW
for '92

CONTENTS - TLK1

- 2 each: BNC to 1 each red & black Test Clips
- 1 each: red Banana Plug to red Banana Plug
- 1 each: black Banana Plug to black Banana Plug
- 1 each: red Test Clip to red Banana Plug
- 1 each: black Test Clip to black Banana Plug

- BNC to test clips use 50Ω RG58 cable
- All cables 36"

Order #	Price	Description	Weight
TLK1	19.95	Test Lead Kit	8 oz.
TL108	6.49	BNC to 2 Test Clips	3 oz.

CERAMIC TRIMMER CAPACITORS

Specifications

- Ins. Res.: >10mΩ @ 100Vdc
- Max. Volt.: 220Vdc
- Oper. Volt.: 100Vdc
- Rotat. Torque: 20 to 15 g/cm


Color
Coded



Order #	1-9	10+	Capacitance (pF)		Q Factor @ 10MHz	Cap Color
			min.	max.		
CVSSA0301	.79	.69	1.5	3.0	>300	Black
CVSSA0701	.79	.69	2.5	7.0	>300	Blue
CVSSA1001	.79	.69	2.7	10.0	>300	White
CVSSC2001	.79	.69	4.2	20.0	>300	Red
CVSSE3001	.88	.78	5.5	30.0	>200	Green
CVSSG5001	.88	.78	8.0	50.0	>200	Orange

TOGGLE SWITCHES (125VAC)

AC Power Toggle Switches

 

•Mounting Hole: 1/2"

Order #	1-9	10+	Action	Amps	Body	Terminals	Type
E1001	.89	.79	On/Off	3	1.02" x 0.55"	2 (Solder)	SPST
E1002	.99	.89	On/Off	3	1.02" x 0.55"	4 (Solder)	DPST
E1003	1.19	1.09	On/On	3	1.02" x 0.55"	6 (Solder)	DPDT
E1004	1.49	1.39	On/Off/On	6	1.39" x 0.79"	6 (Screw)	DPDT

EASYTECH

THE ELECTRONICS SOURCE



2917 Bayview Drive
Fremont, CA 94538



Easy Order: 1-800-582-4044
Easy Fax: 1-800-582-1255

International Fax: 1-510-770-2346
Customer Service: 1-510-770-2345

Monday-Friday, 7am - 5pm (PST)/10am-8pm (EST)

COD-No personal checks, US funds (\$5.00 Surcharge)

USPS UPS Federal Express Airborne

Add approx. 5% of total for shipping UPS Ground (\$3.00 min.).
Actual shipping charges based on weight.

Call or write today for your free copy of our 32 page catalog.

California residents, add appropriate sales tax.
12 month warranty on all EasyTech products.
30 day money back guarantee.
We reserve the right to substitute manufacturers.
Prices subject to change without notice.