

# ELEKTOR ELECTRONICS USA

THE INTERNATIONAL JOURNAL  
FOR RECREATIONAL ELECTRONICS  
NOVEMBER 1992

\$3.00 US  
CANADA \$4.00

## FINAL ISSUE

See page 11

## DIGITAL AUDIO-VISUAL SYSTEM


Output amplifier for  
ribbon loudspeakers

Wheatstone bridge

Printer sharing unit

Differential  
thermometer

Spiral T/R  
HF antenna

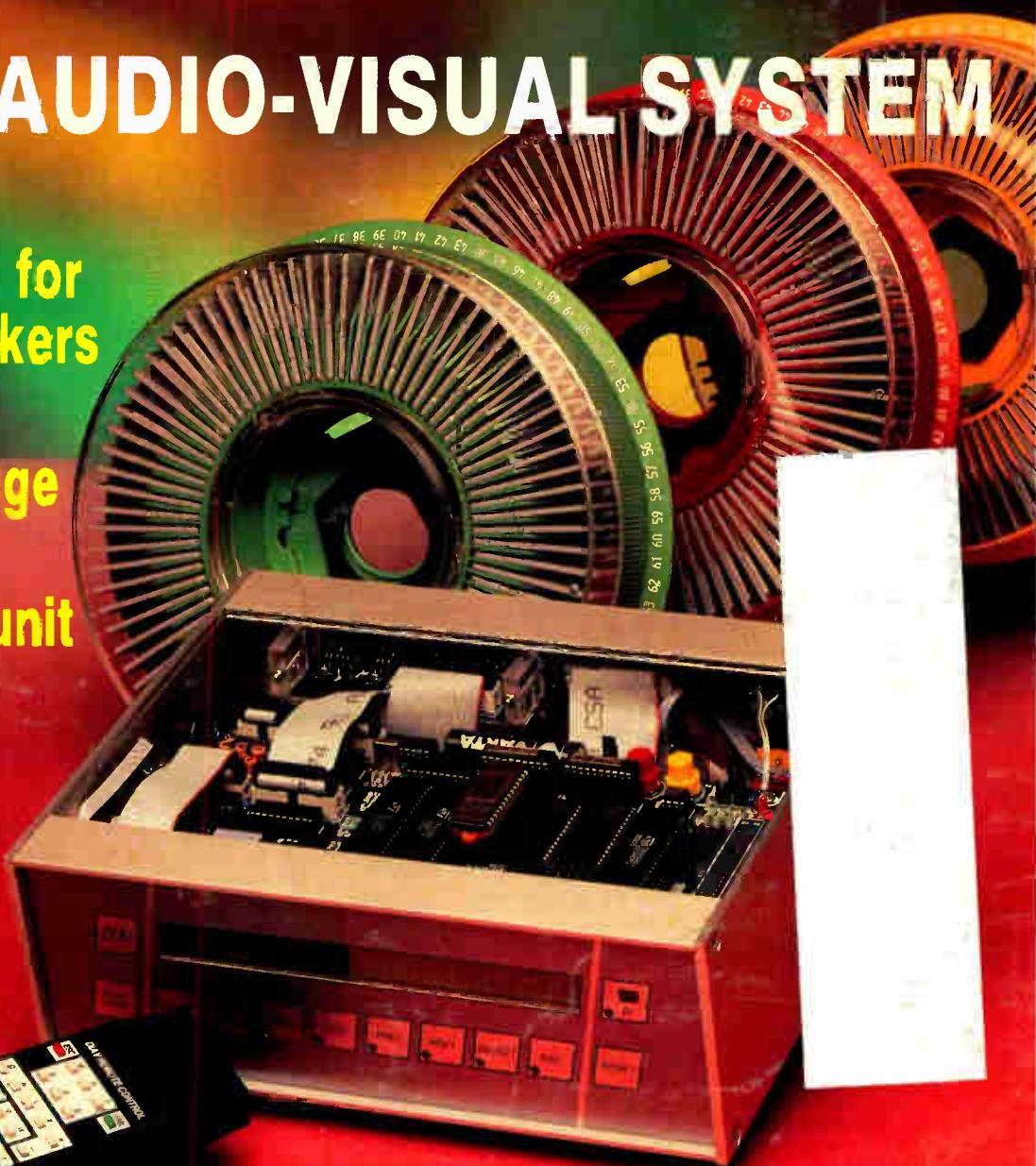

# THE PARTS PLACE

Come in for Your **FREE**  
Radio Shack Catalog!

The most important part of your next project is the all-new, 172-page 1993 Radio Shack catalog. It's yours for the asking at our store or dealer near you. Hurry in today—supplies are limited!



## TECHLINE™ Tools—The new standard in strength and precision!



■ Precision-crafted with top-quality materials

■ Designed for long life and ease of use

■ Backed by Radio Shack's 1-Year Limited Warranty


New TECHLINE tools represent Radio Shack's uncompromising dedication to quality. Each is precision-crafted of long-lasting, hard-working materials and employs the latest design innovations for comfort and ease of use. And, each is backed by our full 1-year limited warranty.
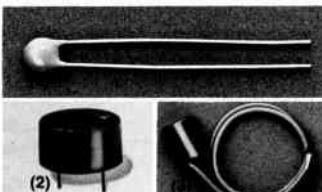
## Speedy service and low prices on thousands of parts and accessories!



- FREE delivery to Radio Shack on orders \$5 and up
- Semiconductors and ICs ■ Hard-to-find batteries
- CB and scanner crystals ■ Long-life vacuum tubes
- Phono cartridges/stylus ■ SAMS® service books

Why pay more for mail-order? Your Radio Shack stocks 1000 electronic components, and another 15,000 are available fast from our special-order warehouse. Ordering is easy! Bring in the exact part number (or old part). We'll check availability and order by phone. Delivery time to your nearby Radio Shack for most items is a week.



(1) Picofarad 50-Pack. Delight for tweakers. 50 ceramic capacitors, assorted 1 to 33 pF values, 50 VDC. #272-806 ..... 2.99

(2) Efficient PC-Mount Piezo Buzzer. Tiny yet has 70 dB output and requires only 7 mA at 12VDC. #273-074 ..... 2.99

(3) Omnidirectional Electret-Type Mike Element. 30-15,000 Hz. 4 to 10 VDC. #270-092, 2.99




Test-Equipment Adapters. Great for use with scopes, frequency counters and multimeters. Hook up with the best.

(1) Binding Posts to BNC Plug. 50 ohms impedance. #274-715 ..... 8.95

(2) Binding Post to Banana Plug. #274-716 ..... Set of 2/4.95

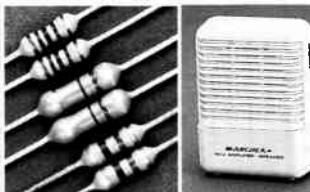
(3) Stackable Dual-Inline Banana Plug. #274-717 ..... 2.99



Resistor Assortments. Popular values—stock up and save.

Description	Cat. No.	Set of	Price
Metal-Film 1/8W	271-309	50	2.29
Carbon 1/4W	271-308	100	2.99
Carbon-Film 1/4W	271-312	500	7.95
Carbon 1/2W	271-306	100	3.49

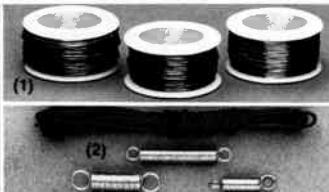Mini Audio Amp With a Built-in Speaker. Many uses! Tough 3 3/4" -high case. Low Radio Shack price. #277-1008 ..... 11.95



(1) Magnet Wire Assortment. For custom coil winding. Includes 40 feet of 22-gauge, 75 feet of 26-gauge and 200 feet of 30-gauge on spools. #278-1345 ..... 4.99

(2) Dial Cord Fix-It Kit. Our exclusive! Includes six feet of high-strength cord and three tension springs. Put a radio back into action! #274-435 ..... 99¢



High-Speed 12VDC Mini-Motor. Produces an amazing 15,200 RPM at no load. Ideal for projects, robotics, fun! About 2" long (with shaft). #273-255 ..... 2.99



PC/XT Circuit Card. Epoxy. Fits computer expansion bus. 10 1/16" long. #276-1598 ..... 29.95  
Right-Angle D-Sub 25 Female Connector for Above. #276-1504 ..... 2.69



Infrared Project Box. Ideal for a remote. Has removable infrared-transparent end panel and space for 9V battery. 7/8" x 2 3/8" x 4 1/4". #270-294 ..... 4.49



100-Watt Soldering Gun. For big jobs! Reaches full temperature in seconds. Built-in work light. Replacement tips in stock. UL listed. #64-2193 ..... 11.95

**RadioShack® SINCE 1921**  
**AMERICA'S TECHNOLOGY STORE™**

A DIVISION OF TANDY CORPORATION

Prices apply  
at participating  
stores and dealers.

# CONTENTS

November 1992

Volume 2  
 Number 12

## EDITORIAL

- 9 A Last Letter to You

## AUDIO & HI-FI

- 22 PROJECT: Output Amplifier For Ribbon Loudspeakers—Part 1  
 Design by T. Giesberts

## COMPUTERS & MICROPROCESSORS

- 16 PROJECT: Printer Sharing Unit  
 Design by A. Rietjens  
 43 COURSE: 8051/8032 Assembler—Part 8 (final)  
 by Dr. M. Ohsmann

## DESIGN IDEAS

- 29 The Wheatstone Bridge  
 by Joseph J. Carr

## GENERAL INTEREST

- 34 PROJECT: Digital Audio-Visual System—Part 1  
 Design by A. Rietjens

## RADIO, TELEVISION & COMMUNICATIONS

- 14 PROJECT: A Compact Spiral T/R HF Antenna  
 By Richard Q. Marris, G2BZQ  
 21 The Wireless Museum, Lindfield

## TEST & MEASUREMENT

- 26 PROJECT: Differential Thermometer  
 Design by J. Ruiters

## MISCELLANEOUS INFORMATION


Editorial 9; Electronics Scene 10, 12–13; Events 13;  
 Letters 49–50; Classifieds 51–52;  
 Advertisers' Index 52; Readers' Services 53;  
 Terms of Business 54.

### Front cover


This month we start a project for a slide control system based on a Centronics-driven dissolve unit for four slide projectors. The system allows up to 16 projectors to be controlled automatically or by hand. Music or comment to accompany the slides can be synchronized with the aid of an advanced pulse or time-code registration unit. The time-code option enables you to record all control actions in a complete slide show, whereby all relevant data are safely stored, along with the parallel sound track.

**ELEKTOR ELECTRONICS USA**  
 (US ISSN 1051-5690) is published monthly except August at \$28 per year; \$50 for two years by Audit Amateur Publications, Inc., 305 Union St., Peterborough NH 03458 USA. Second class postage paid at Peterborough NH and an additional mailing office.

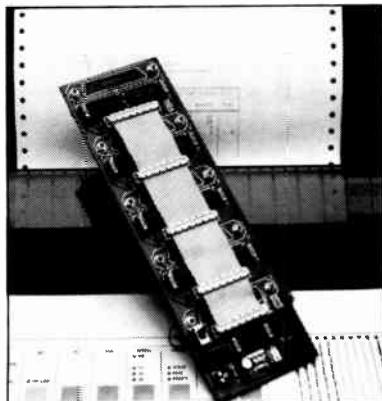**POSTMASTER:** Send address changes to Elektor Electronics USA, Caller Box 876, Peterborough NH 03458-0876.



Printer Sharing Unit-p. 16

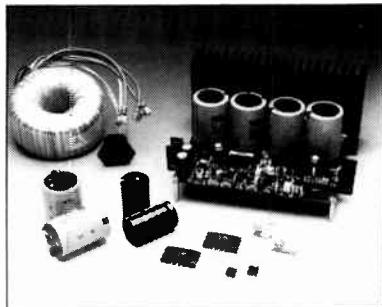

Output Amplifier For Ribbon Loudspeakers-p. 22

Courteous Service · Discount Prices · Fast Shipping  
**ALL ELECTRONICS CORP.**  
 P.O. Box 567 • Van Nuys, CA 91408

**ULTRASONIC TRANSDUCER**


Panasonic (Matsushita) # EFR RCBK40K54



An ultrasonic microphone consisting of a bimorph type piezo electric ceramic vibrator. Nom. Freq. 40 kHz. Max input: 20 Volts. 15/16" dia. X 3/8" high. 5/8" long leads. CAT# UST-1 \$1.00 each

**20 AMP RFI/EMI FILTER**

Corcom # 20B6 20 amp RFI/

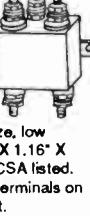


EMI general purpose common-mode filter. Controls line-to-ground noise. Small size, low leakage. 3.46" X 1.16" X 2.81". UL and CSA listed. Threaded stud terminals on input and output. CAT# RFI-201 \$8.50 each

**12 VDC STEPPER MOTOR**



Airpax # AB3712-M1 12 Vdc, 36 ohm coil, 15 degrees/step. 2.25" dia. X 0.95" thick. 0.25" shaft X 0.6" long. CAT# SMT-9 \$6.00 each

**MOTOR SPEED CONTROL AND TIMER**

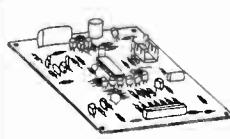

With a minimum of external wiring, this PC board will control the speed and duration of a 120 Vac motor or other load up to 300 watts. When activated, motor will operate for 10, 20 or 40 minutes or continuously at high, medium or low speed. To simplify hook-up we recommend using our membrane keypad. (CAT# KPM-12 \$1.25 each) which, with slight modification, works well with this device. Instructions included. CAT# MSC-5 \$3.00 each

**TOLL FREE ORDER LINES**  
**1-800-826-5432**

**CHARGE ORDERS to Visa, Mastercard or Discover**


**TERMS:** Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (7.25, 7.5, 7.75, 8.25 or 8.5%). Quantities limited. NO C.O.D. Prices subject to change without notice.

**CALL OR WRITE FOR OUR FREE 64 PAGE CATALOG**

**ALL ELECTRONICS CORPORATION**  
 P.O. Box 567 • Van Nuys, CA • 91408

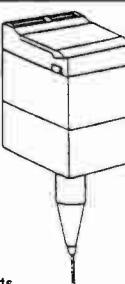
**RADIOSONDE WEATHER INFORMATION TRANSMITTER**

Viz(r) Radiosonde A "radiosonde" is a weather instrument, usually released at high altitudes, designed to transmit temperature, humidity, winds and pressure at various heights above the ground. These are new units, discontinued from NOAA National Weather Service. Contains lots of interesting parts: a solid state transmitter, barometric pressure sensor, humidity sensor and a 24 volt battery which is activated when submerged in water. Great for school science demonstrations or as a source for parts. CAT# WIT-1 \$4.75 each • Case of 16 for \$64.00



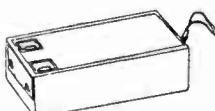**Laser Power Supply**

Epoxy encapsulated power supply for up to 2 mW lasers. 4 1/2" X 1 1/2" X 1 7/16". Input: 9 Vdc @ 1 amp. Output starting voltage: 7 to 8 kV. Operating voltage: 1.1 to 1.5 kV. Operating current: 4 to 5 mA. Recessed 0.250 quick connect terminals for output. Color coded wire leads for input. CAT# LPS-1 \$35.00 each



**PIEZO ELEMENT**

3 Wire Piezo Element. Taiyo Yuden Co. # CB35BBKR4. Self-excited piezo electric diaphragm. 1.40" diameter x 0.021" thick. Resonant resistance: 400 ohms. 5" color-coded leads. CAT# PE-12 \$1.00 each • 10 for \$8.50



**ELECTRONIC FLASH**

ITT Magilash Originally designed for Polaroid One-Step and Pronto cameras. Nice bright flash can be triggered by external 3 Vdc pulse. Operates on 6 Vdc, 4 AA cells (not included). Useful for special effects of flash lighting. Camera includes a very desirable 600 U 330V photoflash capacitor which is, by itself, worth the price of the unit. CAT# FSH-2 \$6.00 each




**RECHARGEABLE GEL CELL BATTERY**

12 VOLTS @ 10 AMP/HOURS



Two 6 volt 10 A/H batteries, assembled as a single 12 volt package. Package size: 6" X 3.94" X 3.75". CAT# GC-1210 \$35.00 each

**JOIN the SMALL DISH REVOLUTION**

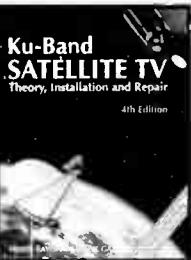

**The Ku-band satellite TV "bible"**

- Operation, installation and troubleshooting of Ku-band satellite systems
- Footprint maps and video standards
- and much more

**TO ORDER - Send \$30 plus \$3 s/h to:**  
 Baylin Publications  
 1905 Mariposa, Boulder, CO 80302

432 pages, 8.5 x 11"

**CREDIT CARD orders also accepted**  
 303-449-4551

**Request our FREE CATALOG of other books about Satellite & Private Cable TV**

**Micro Video Cameras**

Small size 1 3/8" x 1 1/4" x 2 1/4" Light Weight 2.5 oz. Low Power 7 - 14 volts. @ 80ma. Low Light @ 2 Lux. Camera comes complete in metal case with 3 ft. plug & cable for video out and power. Camera is presently in use in R/C airplanes, helicopters, cars, tanks and robots. Camera output is NTSC or PAL, 240 line resolution with electronic iris. Full stock on hand. VHS video available for \$ 10. Satisfaction Guaranteed!

All Cameras Factory New. For product information and ordering. Call 1 (800) 473-0538 FAX (714) 545-8041


**MICRO VIDEO PRODUCTS**

1334 So. Shawnee Dr. Santa Ana, California. zip 92704

# 40,083

## ELECTRONIC COMPONENTS

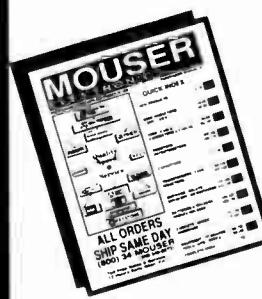**Whether you order 1 part or all 40,083...MOUSER stocks and...can ship today!!**



**CALL...  
 (800) 992-9943**

**for your  
 FREE  
 CATALOG**

2401 Hwy 287 N.  
 Mansfield, TX 76063


**MOUSER**  
 ELECTRONICS

Sales & Stocking Locations Nationwide

# TAPTO ELECTRONIC KITS


*Our high quality kits will provide you with educational projects. After you complete your kit, you will have a high-tech product that will provide years of reliable operation. Assembly instruction in English, French, Dutch and German. Over 100 kits available. Call or write for a full-line catalogue.*

K1771 FM Oscillator \$16.95

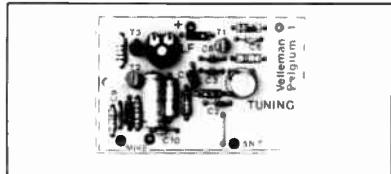

Mini FM transmitter with good frequency stability (100-108MHz). Built-in pre-amp (5mV Sensitivity). Interfaces to all microphones. Requires 9-12 VDC.

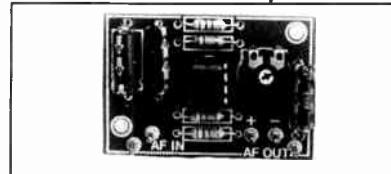K1803 Universal Mono Pre-Amplifier \$8.95



Ideally suited as a microphone amplifier, signal matching of tuner or tape outputs. Supply voltage: 10-30 VDC (stabilized). Gain: typ. 40 dB. Adjustable output level. Frequency range: 20 Hz to 20 KHz (+/- 3 db). Maximum input voltage: 40 mV.

K2622 AM-FM Antenna Amplifier \$17.95




Do away with noisy signals! The K2622 gives you 22 dB gain where it's needed. DC supply direct or via the coax cable (50-75 Ohm impedance), metal box included.

K2637 2.5 Watt Mini Audio \$13.95




This small kit comes with a pre and power amplifier. No adjustments required. Short circuit protected. Power supply: 4.5 to 15 VDC. Input sensitivity: power-Amp: 150 mV (12V). Pre-Amp: 20 mV (12V). Max output 2.5W (4 Ohm, 12V). Size: 42 x 32 x 27 mm.

K2666 Precision Stereo Vu-Meter \$79.95

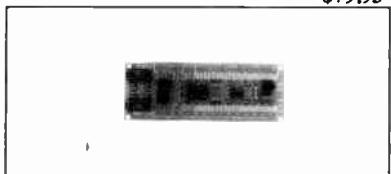

Extremely precise VU-meter. 2 x 30 LED's "flying dot" readout. dB-linear scale from +6 to -6 dB (0.75dB per LED). Steadily increasing scale partitions under -6dB. Peak measurements. No adjustments. Maximum error 0.5dB.

K2032 Digital Panel Meter \$39.95

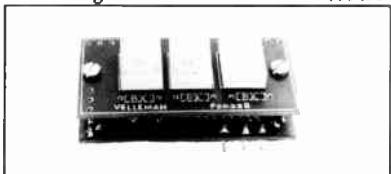


A compact kit that can be incorporated into many housings or into existing equipment. Power supply: 5VDC, 250 mA (regulated). Read out: -999 mV to +99 mV, 1 mV resolution. Overload indication (positive and negative). Linearity 0.1%. Input impedance: 100 Mohm.

K2653 Digital Voice Record/Playback \$61.95



Record your voice message on a IC and play it back! Short messages (10-12 seconds) can be repeated to welcome your guests in your home or store. Use your imagination. Tech data: Loudspeaker output: 2W at 4 Ohm. 9VDC regulated.

K2645 Geiger-Muller Counter \$139.95

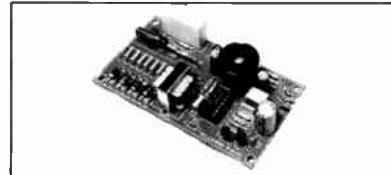

Reliable acoustic indication of radiation level. Excellent sensitivity to Gamma rays and high energy Beta rays. Battery operated (9V). Battery life exceeds 2 months in continual use and in normal natural radiation surroundings. Very compact: 99 x 54 x 25 mm. Light weight; assembled PCB weighs only 55 gr.

K2659 Morse decoder w/LC-display \$109.95



Decode Morse messages on your shortwave receiver. This decoder keeps up with the quickest signallers or automatic stations, and "notes" message on LCD. Alphanumeric LCD. 1 line of 16 characters. decodes Morse at almost any speed.

K2651 Digital Volt Meter \$39.95



This kit provides an easy-to-read display. Because of the simple power supply requirement and compact size of the kit, it can easily be incorporated into a variety of applications. Technical specs: Selectable - to + 200 mV or - to + 2V. Power supply: 8 to 15 VDC of 9V battery.

K4300 Audio Spectrum Analyzer \$109.95



Provides visual composition of an audio signal. Kit consists of two boards and attractive front panel with 10 frequency bands. Technical specs: 10 bands: 32, 64, 125, 500, 1K, 2K, 4K, 8K and 16 KHz. Range: 20 dB (10 LED's, 2dB per LED). Line input: adjustable from 100 mV to 2 V rms, impedance 100K. Power supply 2 x 9V transformer: 12-15VDC. Current consumption 0.75ADC max, 70mA in stand-by.

## ORDER INFORMATION

Call for a catalogue!



Call: (303) 480-7544  
Fax: (303) 480-7553

1-800-758-2786



Mail: Tapto Corporation  
2650 West 18th St.  
Denver, CO 80211

## PAYMENT METHODS

- VISA
- MASTERCARD
- CHECK

\$5 Shipping charge per order

## **Our Best Oscilloscope Value Ever...**

**MILITARY HP AN/USM-338**  
Ruggedized  
Oscilloscope

(Same as HP-1707B  
Opt. 300)

- Power Sources: 115/230VAC (48-400 Hz) or 11.5-38VDC line.
- Vertical Section: The military specified that this unit have a 50 MHz Bandwidth, but it normally meets the specs of the 1707B (75MHz Bandwidth)
- Time Bases: Both regular and delayed sweep included.
- Weighs 27 pounds
- Front cover included
- Graticule 6x10 cm
- CRT 15 kV post accelerated P31 phosphor



**Military Paid \$3360**  
**Tucker Bargain Price**  
**\$299**

To Order Call, Write or Fax:

National: 800-527-4642 ♦ In Texas: 800-749-4642  
Local: 214-348-8800 ♦ Fax: 214-348-0367  
1717 Reserve St. - Garland, TX 75042



**TUCKER**  
ELECTRONICS & COMPUTERS

Call, Write or Fax a Request for Our All New  
**Bargain Hunters**  
**Discount & Closeout Catalog**

## **HEAR EVERY SOUND OVER 1 MILE AWAY!**



Simply attach the VT-75 microtransmitter to any 3V to 12V battery and you can hear every sound in an entire house over 1 mile away! Super-sensitive circuit on a single chip even picks up footsteps from across a large room. Tunable from 80 to 130 MHZ.

Hear everything on any FM radio or wideband scanner tuned to the "secret" frequency you select. Unlimited uses for security, baby monitor, remote mic, etc. **Not a toy.** The VT-75 meets many U.S. Gov't Military Specs and with 100mW RF output, it is the smallest, most powerful miniature transmitter you can buy. Easily assembled even by a youngster in only 5 minutes and performs so well that it is the only miniature transmitter available anywhere that comes with a **full unconditional moneyback guarantee!** Complete kit includes VT-75 microtransmitter chip, miniature microphone, 9V battery connector and instructions - **\$49.95 + \$1.50 S&H or save- buy 2 for \$45.00 each with free S&H!** Call toll free or send money order, Visa, or MC acc't number for immediate shipping by U.S. Mail. COD's add \$4. Checks allow 21 days.



**DECO  
INDUSTRIES.**

**BOX 607  
BEDFORD HILLS, NY  
10507**

**1-800-759-5553**

(U.S. ONLY) ALL OTHER 914-232-3878

## **MAKE CIRCUIT BOARDS THE NEW, EASY WAY**



### **WITH TEC-200 FILM**

#### **JUST 3 EASY STEPS:**

- Copy circuit on TEC-200 film using any plain paper copier or laser printer
- Iron film on to copper clad board
- Peel off film and etch

#### **SATISFACTION GUARANTEED**

convenient 8½ x 11 size  
5-Sheets for \$3.95 10-Sheets only \$5.95  
add \$1.50 postage NY res. add sales tax

**The MEADOWLAKE Corp.**  
Dept B, P.O. Box 497, Northport, NY 11768

## **CELLULAR TELEPHONE MODIFICATION HANDBOOK**

*How are hackers making  
cellular phone calls for free?*

- Techniques for decoding & changing cellular phones' NAMS & ESNS
- Where to buy programming devices
- The "roaming technique" scam!
- Chip supplier's phone numbers
- Instructions on how to change phone numbers on all models
- Cellular phone manufacturer's ESN codes




**Complete Manual only \$79.95**

M.O. or C.O.D. to

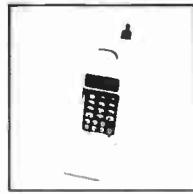**SPY Supply**

7 Colby Court Suite 215  
Bedford, NH 03110  
(617) 327-7272



*Sold for educational purposes only*

## **RECOMMENDED SOURCES FOR ELEKTOR ELECTRONICS USA EUROPEAN PARTS**

### **Borbely Audio**

*Emo Borbely*  
Melchior Fanger Strasse 34A  
8031 Neu-Gilching  
Germany  
Tel 49-8105-5291  
FAX 49-8105-24605 (24H)

### **Bull Electrical**

250 Portland Road  
Hove  
Sussex BN3 5QT  
United Kingdom  
Tel 44-0273-203500  
FAX 44-0273-23077

### **DIL Elektronika**

Jan Ligthartstraat 59-61  
3083 AL Rotterdam  
The Netherlands  
FAX 31-10-4841150

### **EasyTech, Inc.**

2917 Bayview Dr.  
Fremont, CA 94538  
Tel (800) 582-4044  
FAX (800) 582-1255

### **ELV France**

BP 40  
F-57480 Sierck-les-Bains  
France  
Tel 33-82-83-72-13  
FAX 33-82-83-81-80

### **Meek It Electronics**

*Rob Planken*  
Paveljoensgracht 35A  
2515 BL Den Haag  
The Netherlands  
Tel 31-70-3600357  
Tel 31-70-391-4381  
FAX 31-70-397-9707

### **Technomatic**

Technohouse  
486 Church Lane  
London NW9 8UF  
United Kingdom  
Tel 44-081-205-9558  
FAX 44-081-205-0190

**MABUCHI R/C HOBBY MOTOR**

#RS-550.  
Wide  
Range: 4 to  
15 VDC.  
Perfect for  
R/C planes  
or cars

using either 7.2V or 14.4V Nicad.  
Approx. 12,000 RPM. Motor: 2 1/4  
In. X 1 7/16 In. Dia. \$2.95 or 4\$10

**12VDC COMPUTER FANS**  
Most common size ! TOYO.

3 1/8 sq. X 7/8 In thick. \$6.95

**PALS & GALS**  
TI BPAL 16L8-15 -- \$1.19  
MMI PAL 16R8ACN -- 99¢  
LATTICE GAL 16V8-25 -- \$1.49  
LATTICE GAL 16V8A-20 -- \$1.99

**FET OP-AMPS**  
TLO72 -- 49¢ TLO74 -- 69¢

**TANNER ELECTRONICS**

Phone: (214) 242-8702

1301 W. Beltline Rd. #105 Carrollton, TX 75006

TERMS: Send check, or use Visa, MC. NO COD. USA, Canada only. Add \$3.85 min. for UPS. Texas add sales tax. 90 day lmt. warranty on all items. \$15 min.

**8032 MICROCONTROLLER**

Speed: 12MHZ. 44 Pin PLCC package. Mfg. by Signetics \$1.49. 11.059 MHZ crystal -- \$1.25

**CMOS EPROMS**

27C64-12	\$2.95
27C256-15	\$2.95
27C512-15	\$2.95

**CAPS FOR POWER SUPPLIES**

35,000 MFD 40 VDC Mallory CGS Series Computer Grade. Can. 2 X 5 1/2 IN. \$3.95

**HIGH VOLTAGE N-CH POWER FETS**

IRF723.....	99¢
IRF730.....	\$1.29


**STEPPER MOTOR**

IBM Surplus. 8 wire. 4 windings. 7V @ 350 mA 1.8 deg. (200 steps per rev.) DC. res. 20 ohm ea. 25 oz. in. torque. Works great on 5 VDC. W/Data. \$3.95

GREAT FOR ROBOTICS !

**FREE FLYER****SOLID STATE TIME DELAY RELAY KIT**


Operates from 12VDC. Very accurate and repeatable. Delays from 1 second to approx. 30 minutes. Output is a SPDT relay with 5 Amp contacts. Complete kit with documentation. Board is 2 in. X 3 1/2 in. \$14.95

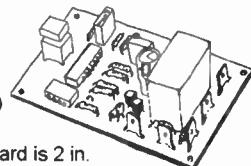**HI-TECH DISPLAYS****HITACHI LCD**

1 line X 16 characters. ASCII Input. #H2570. w/Data. \$6.95

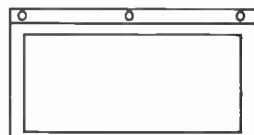**EPSON LCD GRAPHICS DISPLAY**

640 X 240 dots - Super twisted nematic type. Built in drivers - 4 bit TTL interface. Viewing area 10 7/16" X 4 5/8". Overall 11 3/8" X 6 1/16". 14 pins for signals and power (+5V, -12V). Complete 27 page manual. \$19.95 ea. or 6/\$100 #EG-7004S-AR



NOT FOR BEGINNERS !

**SIEMENS SMART LED DISPLAY**

#DLO-7135. 5X7 Red. With built in logic ! Requires only a chip select and an ASCII input. Operates on 5 VDC. 1 Inch tall. w/ Data. New Units ! Displays entire 128 char. set ! \$3.95 ea. or 8 for \$24.95

**ALPHA-NUMERIC RED LED ARRAY**

7X5 LED Matrix. For moving message signs, Etc. By IEE. #2057 - c/c rows. #2058 - c/a rows. 2 X 1.5 In. w/Data. Your Choice: \$2.95 ea. or 8 for \$14.95

**SIEMENS 4 DIGIT LED DISPLAY**

Red or Green. With built in logic. 5X7 Matrix. Full ASCII Input. 5 VDC. .2 In. char. with Data. #PD2435 - RED - \$4.95 #PD2435 - GREEN - \$4.95

**100% PURE****SCANNING ACTION!**

National Scanning Report is America's fastest-growing scanning magazine. That's because every issue of National Scanning Report offers the latest in:

- \* Law Enforcement Communications
- \* Fire and Rescue
- \* Emergency Medical
- \* Listening Tips
- \* Frequency Lists
- \* New Products
  - \* Aeronautical
  - \* Railroad
  - \* Federal
  - \* Much More!



From first alarm to final clean up, National Scanning Report is crammed with up-to-date information written by and for the pros. National Scanning Report is your #1 guide to the scannerbands.™

Order your subscription today: \$17.50 gets you one year (six issues) plus a free custom frequency print-out for your county and more.

*National Scanning Report™*

**1-800-423-1331**

OR SEND CHECK OR MONEY ORDER TO BOX 291918, KETTERING, OHIO 45429

**Weather Radio**

A complete guide. NOAA Weather Radio, VOLMET aviation weather, FAA, military, maritime weather services. Where to tune and what you'll hear. 125 pp.

\$14.95 plus 2.00 book rate or 3.50 UPS.

**\$14.95 POSTPAID  
1993 Passport!**

New, 1993 edition. Offer expires August 15. Don't wait! Order now. Get it first!

**SCANNER POCKET FREQUENCY GUIDE - \$2.00**

Never get lost on the scannerbands again! Handy, laminated, credit card-sized guide. Covers police, fire, EMS, marine and aero emergency, power & water, railroad, weather, more. Cash only. Include SASE.

**DX RADIO SUPPLY**  
P.O. BOX 360  
WAGONTOWN, PA 19376  
215-273-7823

# AUDIO TECHNOLOGY at its BEST is ALIVE and INNOVATIVE in our THREE UNIQUE JOURNALS



The newest publication from  
the folks who bring you  
*Audio Amateur* and *Speaker Builder*

**Glass Audio** features the best vacuum tube designs for audio reproduction—past and contemporary. The new designs take advantage of improved components and control techniques that make the end results far superior to anything possible during the early days of audio's rebirth after World War II.

That's why tubes are having such a renaissance of interest as a perfectionist approach to good sound. And that's why tubes are reappearing in original equipment, in high end consumer and professional audio systems.

Published quarterly, *Glass Audio* will inform you about new innovations in the field and about parts sources. We'll also include modification projects, reviews of technical basics and regular columns such as *Tube Troubles*, *Tube Tips* and much more.

Subscribe today!



## GLASS AUDIO

- Two years, (8 issues) \$35
  - One year, (4 issues) \$20
- Canada add \$4 per year postage



## Audio Amateur

THE JOURNAL FOR AUDIOPHILE CRAFTS

The innovative, independent audiophile journal for the thoughtful and capable music lover

*Audio Amateur's* articles deal with how audio equipment works, as well as how to build or modify it. Construction and modification articles are plentiful, supplying all needed parts, performance and assembly details. Exceptionally high quality designs.

*Audio Amateur* offers a number of features in each issue that abound with useful ideas. The *Letters* column is an open forum for problem solving and information interchange; *Classic Circuitry* reprints schematics of state-of-the-art gear—old and new; *Audio Aids* relates readers' experience with simple modifications to equipment and construction techniques. We also feature many useful and practical hi-fi accessories you can build to further your audio enjoyment.

For a small investment you can make your music system sound better—very probably a lot better.

## AUDIO AMATEUR

- Two years, (8 issues) \$35
  - One year, (4 issues) \$20
- Canada add \$4 per year postage

## SpeakerBuilder

THE LOUDSPEAKER JOURNAL

The magazine  
that finally deals seriously with  
the art and craft of speaker building

The *Art* of building a speaker is to optimize that mixture of design and engineering to balance all the parameters for the most beautiful sound possible. The *Craft* is knowing how and why. **Speaker Builder** gives you knowledge—from driver parameters and crossovers to woodworking—to develop and refine your techniques, and to get the most out of your system.



**Speaker Builder** helps you explore new designs with how-to construction articles, and can show you how to modify your old speakers and make them sound better than ever. Learn from our writers who turn abstract theory into practical approaches, and from the experience of other readers who have been down the road before you. **Speaker Builder** is the best investment you can make in your system—six issues per year filled with stimulating and exciting ideas.

## SPEAKER BUILDER

- Two years, (12 issues) \$45
  - One year, (6 issues) \$25
- Canada add \$6 per year postage

NAME \_\_\_\_\_

STREET & NO. \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

MC OR VISA NUMBER \_\_\_\_\_

EXPIRE \_\_\_\_\_

## AUDIO AMATEUR PUBLICATIONS, INC.

PO Box 576, Dept. E92, Peterborough, NH 03458-0576 • (603) 924-9464 • FAX: (603) 924-9467

Answering machine for credit card orders only: before 9:00 a.m., after 4:00 p.m. and weekends. Have all information plus MC/VISA available.

# A LAST LETTER TO YOU

After two years plus one final issue, we must, with deepest regret, suspend publication of *Elektor Electronics USA*.

Doubtless the recession has been a major factor in the need for our decision. But other causes, as well. Advertisers were reluctant to use a new, untried medium, and apparently we did not always find the vendors to whom you were interested responding. Advertisers' phones did not ring, orders did not pour into advertisers' mailboxes. And no magazine of this size and quality can survive on an annual circulation price of \$28 per year without advertising support and reader response to them.

The larger picture in the US is a theme I have expounded upon to readers and other friends ad nauseam. But Americans are rapidly losing their ability to make things with their hands. The number of helpless, hapless individuals grows steadily with each new generation. Most people consider this unimportant. The advertising moguls love it. The end user is being offered less and less in the way of handcraft projects which are seriously challenging. But a do-it-yourself revival is, I believe, underway, fueled largely by necessity in bad economic times.

A new company formed last month to assist Americans in learning to use their computers, or to get them running again, is named "Rent-a-Nerd." Thus, the ability to make something, repair it, or even understand it, makes you some kind of weird aberration, somehow comic and subnormal. Whether this has anything to do with the United States continuing to be the world's most innovative and productive industrial nation, given our

attitudes, is not a question I think we can answer positively with any real hope.

On page eleven I am pleased to offer you a rather rich menu of alternative publications. We naturally begin with our own three which specialize in do-it-yourself audio design and construction. Details of how those may be chosen to fulfill your unexpired subscription are stated there.

May I request, as strongly as I can, that you help us by FAXing or mailing your choices of alternative periodicals as promptly as you can. Also, I am sure you can understand that if you call about your subscription, you are likely to get a busy signal. We will process your choice as quickly as possible—but we have only three phone lines servicing subscriptions, and they cannot be useful if everyone on the list calls. Our FAX is open 24 hours, 7 days a week.

The cooperating magazines, other than our three, will require some time to enter your request and for the schedule to deliver your first copy. Most of the larger periodicals have a six-week to two-month time lag on "new" subs. Since your name is on our integrated subscriber list already, a choice of one of our periodicals could be quicker, but keep in mind they are all bi-monthly or quarterly in schedule.

Lastly, I thank you all for your response to *Elektor Electronics USA*. I have been proud to publish it. I remain convinced that it is the best electronics design periodical available—and sorry that it will no longer be available here in the USA.—E.T.D.

Published by Audio Amateur Publications, Inc.

**Editor/Publisher:** Edward T. Dell, Jr.

**Editorial Offices:**

305 Union St., P.O. Box 876  
Peterborough, NH 03458-0876 USA

Telephone: 603-924-9464 (*National*)  
or +1 (603) 924-9464 (*International*)

**FAX:** (603) 924-9467 (*National*)

or +1 (603) 924-9467 (*International*)

**Advertising:** Maureen E. McHugh

Telephone: (603) 358-3756

**FAX:** (603) 358-0157

**Subscriptions:** Katharine Gadwah

*Elektor Electronics USA*

Post Office Box 876,

Peterborough, New Hampshire 03458

**Subscriptions to Elektor Electronics USA** are available **ONLY** in the fifty United States, Canada, Puerto Rico, the Virgin Islands and those Pacific territories administered by the United States of America.

**International Advertising:**

Uitgeversmaatschappij Elektuur b.v.

P.O. Box 75

6190 AB BEEK

The Netherlands

Telephone: +31 46 38 94 44

**FAX:** +31 46 37 01 61

#### European Offices:

**Elektuur BV**  
Postbus 75  
6190 AB BEEK  
The Netherlands  
Telephone: 011 31 4638 9444  
Telex: 56617 (elekt nl)  
FAX: 011 31 4637 0161  
**Managing Director:** M.M.J. Landman

#### Overseas Editions:

**FRANCE**  
Elektor sarl  
Les Trois Tilleuls  
B.P. 59; 59850 NIEPPE  
**Editors:** D.R.S. Meyer  
G.C.P. Raedersdorf

#### GERMANY

Elektor Verlag GmbH  
Susterfeld Strasse 25  
5100 AACHEN  
**Editor:** E.J.A. Krempelsauer

#### GREECE

Elektor EPE  
Kariskaki 14  
16673 Voula—Athena  
**Editor:** E. Xanthoulis

#### HUNGARY

Elektor Elektronikai folyoirat  
1015 Budapest  
Bathány U. 13  
**Editor:** Lakatos Andras

#### INDIA

Elektor Electronics PVT Ltd  
Chhotani Building  
52C, Proctor Road, Grant Road (E)  
BOMBAY 400 007  
**Editor:** Surendra Iyer

#### ISRAEL

Elektoral  
P O Box 41096  
TEL AVIV 61410  
**Publisher:** M. Avraham

#### NETHERLANDS

Elektuur BV  
Peter Treckpoelstraat 2-4  
6191 VK BEEK  
**Editor:** P.E.L. Kersemakers

#### PAKISTAN

Electro-shop  
35 Naseem Plaza  
Lasbella Chawk  
KARACHI 5  
**Editor:** Zain Ahmed

#### PORTUGAL

Ferreira & Bento Lda  
R.D. Estrel-83-ni, 32-1°  
1000 LISBOA  
**Editor:** Jeremias Sequeira

#### SPAIN

Resistor Electronica Aplicada  
Calle Maudes 15 Entlo C.  
28003 MADRID  
**Editor:** Agustin Gonzales Buelta

#### SWEDEN

Electronic Press AB  
Box 5505  
14105 HUDDINGE  
**Editor:** Bill Cedrum

#### UNITED KINGDOM

Elektor Electronics (Publishing)  
P.O. Box 1414  
Dorchester DT2 8YH  
England  
**Editor/Publisher:** Len Seymour

Printed in the United States of America.

ISSN: 1051-5690

## WOMEN'S TECHNET ON-LINE

Women's Technet, an organization dedicated to improving opportunities for women in pro audio, video, broadcast, recording and related industries, is now on-line. Both men and women are encouraged to become a part of this organization in its quest to promote, educate, and support women in these technical industries.

Technet has established two private conferences on a non-profit telecommunications network, the Institute for Global Communications (IGC), which provides all the typical services at extremely competitive prices, including electronic mail, FAX and telex using computer and modem. You can participate in hundreds of public conferences worldwide, and send electronic mail to dozens of popular computer networks.

The cost of an IGC subscription is \$10/month, with an initial sign-up fee of \$15, which includes one hour of off-peak connect time to the network each month. Technet solicits the participation of people with expertise, knowledge, information, and a desire to contribute to the advancement of women in these technical careers.

For more information send a self-addressed, stamped envelope (with postage for two ounces) to Women's Technet, PO Box 966, Ukiah, CA 95482.




## ANTENNA GUIDE

**Antenna Specialists** has produced a Professional Mobile Antenna Guide, a full-color illustrated wall chart depicting 150 mobile antenna models grouped by frequency range from low-band through 800-900MHz, and cross-referenced to various mounting schemes.

The chart, which measures 54" x 38", also presents antenna solutions for special applications such as transit, motorcycle, and railroad. Each antenna is illustrated, and its components identified by part number.

For more information, contact the Marketing Department, Antenna Specialists Co., 30500 Bruce Industrial Parkway, Cleveland, OH 44139-3996, (216) 349-8400, FAX (216) 349-8407.

## ELECTRONICS SCENE

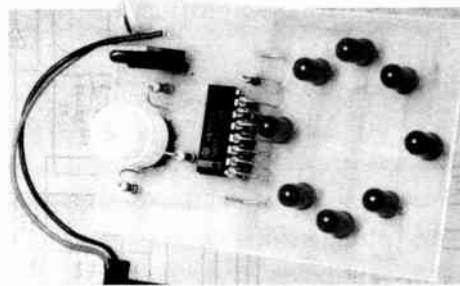

### SPEAKER DESIGNER, 2.0

Stuart Bonney is now offering an enhanced version of **Speaker Designer**, a program for loudspeaker system design and modeling. Release 2.0 accommodates closed or vented system designs and is based on Thiele/Small parameters. It models both small- and large-signal performance over the frequency range of 10-300Hz.

Enhancements include user-designed input files which you can save to or retrieve from disk; input error trapping and correction functions; new sample input files for less experienced users that include closed, vented, single driver, and dual-driver designs; and an on-disk user's guide with revisions, expansions, and instructions for modeling multiple-driver systems.

Other features include English/metric conversion, ASCII format, menu-driven selections, and speed. Speaker Designer runs on any IBM PC or compatibles, MS-DOS version 2.0 or higher, and comprises 38K-bytes.

**Speaker Designer, 2.0** (#SOF-SPD1B5, \$27.50 plus \$2 S/H) is available from Old Colony Sound Lab, PO Box 243, Peterborough, NH 03458, (603) 924-6371, FAX (603) 924-9467.



### POWER OUTLET

**MFJ Enterprises** announces the new MFJ-1116 Deluxe DC Power Outlet strip with built-in voltmeter, master switch, 15A fuse, and eight terminals for connecting rigs and keyers, TNCs, and tuners. Each of the outlets uses heavy-duty five-way binding posts, with standard spacing for dual banana jacks.


Order through any MFJ dealer, or MFJ Enterprises, Inc., PO Box 494, Mississippi State, MS 39762, (601) 323-5869, (800) 647-1800, FAX/Telex (601) 323-6551.

## REMOTE SOFTWARE

**Remote-Console** announces the release of Version 4.0 system software, which adds CGA, EGA, and VGA graphics capability. The new version also reduces memory overhead to 18K-bytes when running text-mode applications. All programs fit on a single 360K floppy disk, and password data is placed on removable media for system security. **Remote-Console®** works with DOS 3.0 and higher, DR-DOS, Windows 3.0, VM/386, and OS/2, among others.

The software is a remote access and control system, and is designed to link two personal computers via modem or direct cable. It can be used to run any program on an unattended host computer from a remote location, and runs on all IBM PCs. Host and remote sides, a full-screen text editor, a calendar program, and diagnostic software are included for \$119. Version 4.0 is available on both 5.25" and 3.5" disks.

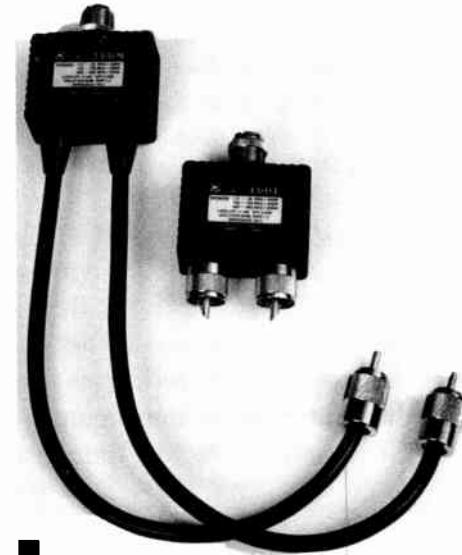Contact Louis Wheeler at Remote-Console, PO Box 888, Oceano, CA 93445, (805) 481-5687.



### NEW DAIWAS

The PS50T is the latest in Daiwa's series of power supplies, which are available from **Electronic Distributors Corp.** This 5A low-capacity power supply has a cigarette lighter plug (meter not provided). The multi-purpose 12V DC power source can be used with hand-held scanners and transceivers, and mobile scanners. List price is \$49.95.

Daiwa's DX10 series duplexers cover 1.6-150MHz and 400-460MHz. Insertion loss is less than 0.1dB. The DX10D (\$27.95) comes with two PL259 connectors; the DX10M (\$36.95) is supplied with cable and two connectors; the DX10N (\$37.95) comes with cable, one PL259 and one N connector.

For a dealer near you, contact **Electronic Distributors Corp.**, 325 Mill St., Vienna, VA 22180, (703) 938-8105, FAX (703) 938-6911.

*Continued on page 12*

# A MENU OF MAGAZINE CHOICES

This November, 1992 issue of *Elektor Electronics USA* is the last to be published by Audio Amateur Publications, Inc. We deeply regret this but the economic times were a factor we could not have anticipated in laying our plans three and one half years ago. Below we list a menu of alternative periodical choices for your consideration. Each title is followed by a description and the number of copies the publisher will send you to fulfill unexpired issues of *Elektor Electronics USA*.

We ask your cooperation and patience in this transition period. You will help us greatly and expedite this changeover by doing the following:

1. Please fill in the postcard you will find between pages 4 and 5 indicating your choice of alternative magazine. Next, peel the label from the front of the magazine and place it on the card. This tells us how many issues are due you and your customer number. Please remember that your EEUSA subscription was for 11 issues per year. Make a copy of your customer number and expiration date for your records.
2. Mail or FAX this card as quickly as you can. MAIL: Elektor, PO Box 876, Peterborough NH 03458. FAX (603) 924-9467.
3. If you are already a subscriber to the magazine you choose, your subscription to it will be extended by the number of issues at the fulfillment ratio remaining in your 11-issue per year EEUSA subscription.
4. Please do not telephone our circulation department since we have only two circulation clerks on duty and any significant use of the phones will clog the lines. If you wish to leave messages about problems, our answering machines are open at 4:15pm EST, M-F and are on all night until 8:00am. They are also open 24-hrs on weekends.

## MAGAZINES

### COMPUTERCRAFT (MONTHLY)

The practical magazine for "hands-on" users of IBM compatibles, microcontrollers and single-board computers. How-to articles cover upgrades, enhancements, and construction projects enabling readers to get more out of their machines. Electronics projects that relate to computer technology are also presented, such as adding video or musical instrument digital interface (MIDI) capabilities. Also included are incisive technical articles, product reviews and new products. (Formerly: *Modern Electronics*)

### ELECTRONIC SERVICING & TECHNOLOGY (13 ISSUES/YEAR)      1 ES&T for 1 EEUSA

For professional servicers of consumer electronics and computers, it will also appeal to anyone who enjoys working on such products. Detailed servicing articles, troubleshooting tips, and frequently-encountered diagnostic problems are offered for TVs, VCRs, audio/video equipment, personal computers, microwaves, and more. Each issue includes a schematic on a popular consumer product, and a special 13th issue is devoted to numerous schematics and component sourcing.

### COMMUNICATIONS QUARTERLY (QUARTERLY)      1 CQQ for 4 EEUSA

Technically-oriented amateur radio magazine gives in-depth coverage to the science of communications. Each issue, over 100 pages of purely technical material examines state-of-the-art subjects like direct digital synthesis, digital signal processing, station control by microprocessor, clover technology, and computer-aided antenna design. Authors and editorial review board are drawn from amateur radio's most knowledgeable and experienced operators.

### CQ AMATEUR RADIO (MONTHLY)      1 CQ for 1 EEUSA

The largest independently published amateur radio magazine, it covers a wide variety of amateur radio's most popular aspects. Contesting, DX'ing, construction projects, radio fundamentals, equipment updates, and more, are all presented in a friendly, entertaining format. Technical information and product reviews are practical and easy to understand. World-renowned contributors include Bill Orr, W6SAI; Buck Rogers, K4ABT; Dave Ingram, K4TWJ; and Lew McCoy, W1ICP.

### POPULAR COMMUNICATIONS (MONTHLY)      1 PC for 1 EEUSA

For scanner monitors and world band shortwave radio listeners and enthusiasts. Regular columns cover new stations and schedules, car phones, CB radio, satellites, pirate broadcasters, FCC activities, beginning ham radio, old-time radio and much more. A non-technical magazine, it is written and edited to help the average enthusiast get more out of this hobby.

### ELEKTOR ELECTRONICS (UK) (11 iss/yr)      1 EEUK for 2 EEUSA

Identical editorial content to US edition, British advertising, reader support services for circuit cards, panels, firmware, books, and software will continue to be available through Old Colony. ELEKTOR UK offers one for two because of the heavy postage costs. Readers choosing this alternative will be offered a reduced rate of US \$48./yr. at renewal time rather than the regular \$56 rate.

**BACK ISSUES OF EEUSA ARE ON SALE AT 10% OFF UNTIL JANUARY 31, 1993. See pp. 52-3 for order card.**

**PLEASE TURN TO PAGE FOUR, FILL IN THE BIND-IN CARD AND RETURN IT. THANKS.**

Continued from page 10

## RELOCATION


**Circuit Works**, manufacturer of printed circuit boards, has relocated to a new facility for production of microwave circuits, as well as single- and double-sided boards. All camera work and step-and-repeat process is done in-house; prototypes and small runs are usually one-week delivery.

Circuit Works' is located at 85 W. Sylvania Ave., Neptune City, NJ 07753, (908) 774-1811.
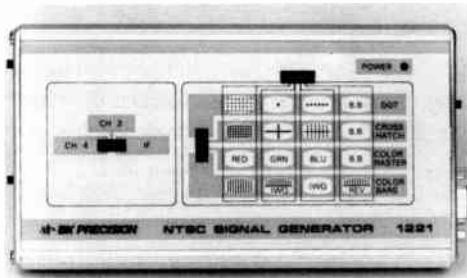
## COLOR GENERATOR

The Model 1221 from **B + K Precision** is a portable television/video signal generator which generates 14 patterns of stable video signals for testing, servicing, and adjustment of television and video equipment. Applications include color or monochrome video monitors, CGA computer monitors, video cassette recorders, television receivers, closed-circuit television systems and components, and cable TV systems.

Powered by an AC adapter (provided) or an external 12-18V DC source, it comes complete with output cable and manual for \$369. For immediate delivery or complete specifications, contact your local distributor or **B + K Precision**, Division of Maxtec International Corp., 6470 W. Cortland St., Chicago, IL 60635, (312) 889-1448, FAX (312) 794-9740.




## DATA CONTROLLER

Now available from **Advanced Electronic Applications**, the DSP-1232 Multi-Mode Data Controller featuring digital signal processing. The single-port version (\$799) features packet, AMTOR, Baudot, ASCII, Morse Code, NAVTEK, WEFAX, all satellite digital modes, automatic identification of most digital signals, software switchable radio port selection, and complete 18K-byte personal mailbox.

For a product data sheet and list of authorized dealers, contact Advanced Electronic Applications, Inc., PO Box C2160, 2006 196th St. SW, Lynnwood, WA 98036, (800) 432-8873, (206) 774-5554.

# ELECTRONICS SCENE

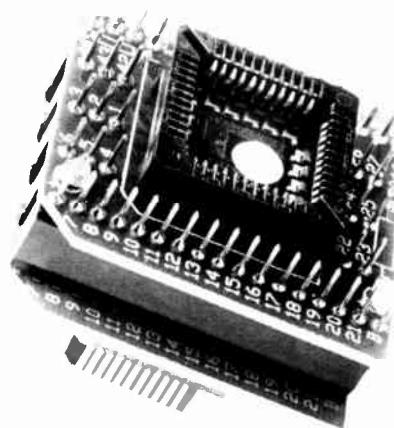

## TEST ADAPTER

**Antona Corp.**'s Model ANC-4044 is designed to monitor and test socketed 44-pin plastic-leaded chip carrier (PLCC) or pin grid array (PGA) type components.

Oscilloscope and logic-analyzer test leads can be attached to any of the component leads by means of numbered test points. Two LED status circuits visually indicate user-selected signals. The user's manual includes a template sheet of the adapter, which designers can use as a signal-to-pin designation guide.

The unit sells for \$122. For additional details, contact Bob Mikkelsen at the Antona Corp., 1643½ Westwood Blvd., West Los Angeles, CA 90024, (310) 473-8995, FAX (310) 473-7112.

## LINE TESTER

The Model 485T Tester from **B&B Electronics** can be used to check signal conditions at any node on an RS-422 or RS-485 network, to determine if the maximum permissible negative or positive voltages are being exceeded. The tester also checks for the existence of minimum required differential voltages, and uses the data that is transmitted on the line to check the voltage value.

The unit runs on either a 9V battery, or from an external 12V power supply. Also included are an instruction manual, and an RS-232 output that can be used to monitor the network data. The tester is priced at \$139.95, and the external power supply costs \$14.95.

Contact **B&B Electronics**, 4000 Baker Rd., PO Box 1040, Ottawa, IL 61350, (815) 434-0846, FAX (815) 434-7094.



## SIGNAL PROCESSOR

**Digital Interactive**'s DSP-120 connects to the printer port of any IBM PC compatible, and to the audio output of your receiver. Real-time digital signal processing frequency and time-domain techniques are brought to the computer, which is used to store previously defined filter responses for rapid recall, calculation of filter coefficients, sound recording and playback, fast high-resolution graphic display in both the frequency and time domain, and control adaptive DSP algorithms.

Enhance weak voice or music signals with the mouse or cursor, or draw a tight bandpass filter around the signal to eliminate as much as 95% of the noise bandwidth in the audio frequencies. The hardware supports future software application extensions for easy upgrading.

For more information, contact Digital Interactive, Signal Corp., 2317 NE 168th Ave., Vancouver, WA 98684, (206) 256-8654.

## TEMPERATURE HEAD

**Fieldpiece Instruments** has introduced the model ATH3 Dual Temperature Head, which converts the signals from two K-type thermocouples to display them as temperature on a digital multimeter, and can be calibrated in the field to an accuracy of  $\pm 1^\circ\text{F}$ . It converts the Fieldpiece HS20 "Stick" series meter to a one-piece temperature meter, but works well with any digital multimeter with "Fluke style" jacks and input impedance of 9-10M $\Omega$ .

Inputs from two thermocouples are accepted simultaneously, with a conversion ratio of 1.0mV DC output per  $1.0^\circ\text{F}$  input. The converter is powered by a 9V battery, and automatically goes off after 45 minutes. The list price of \$89 includes two K-type thermocouples; test leads cost \$12.95.

For more information, contact **Fieldpiece Instruments**, Inc., 8322B Artesia Blvd., Buena Park, CA 90621, phone/FAX (714) 992-1239.

## MINI PC

The Saelig Co. now offers GCAT from DSP Design, the first commercially available credit-card-sized PC compatible, measuring 3.4" x 2.6". The 14MHz F8680 PC/chip processor has built-in graphics hardware, and will drive a CGA LCD screen or CRT without additional boards. The serial port is fully COM1-hardware compatible, and the board has 1M byte of DRAM and a 512K-byte ROM disk capability as standard features. With DOS and BIOS installed, about 400K-byte of application space remains for diskless applications.

Under normal conditions, the board consumes 73mA from a single 5V rail. In suspend mode, consumption drops below 600 $\mu$ A (300 $\mu$ A with 3V supply). Expansion to I/O is via PCbus, and a GCAT Development System is available.

For further details, contact Carol Goldsmith, The Saelig Co., 1193 Moseley Rd., Victor, NY 14564, (716) 425-3753, FAX (716) 425-3835.

## ELECTRONICS SCENE

### PROGRAM MOTOROLA

The 8-bit Motorola 68HC711E9 ('E9) is now programmable using the 27C256 footprint and programming algorithm available from Logical Systems. Adapters make the proper connections between the EPROM programmer's 28-pin socket and Motorola's 52-pin 'E9, making it usable in products requiring device serialization, small volume production, or one-time calibration. Just set the programmer for 27C256, and plug in the adapter.

The PA711E9 (\$145) and PA711E9B (\$145) adapters feature a 52-pin Auto-Eject PLCC test socket. The PA711E9-ZIF (\$165) and PA711E9B-ZIF (\$165) feature a lidded 52-pin PLCC ZIF test socket. The test sockets can be serviced without replacing the adapter.


Contact Logical Systems Corp., PO Box 6184, Syracuse, NY 13217-6184, (315) 478-0722, FAX (315) 475-8460.


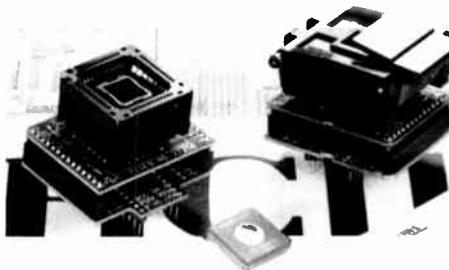
### PAGING ENCODER

The PE-15 from Communications Specialists is a miniature sub-assembly capable of sending codes in the POCSAG format. Intended for operators of local "in-house" radio systems wanting to signal tone-only pagers, it has 15 available codes which may be used to activate up to four distinct alert tones on each pager, 15 individual pagers, or any combination of these.

The PE-15 (\$99.95) is factory programmed to your specific address codes, or may be field programmed by means of an available keypad. For more information, contact Communications Specialists, Inc., 426 W. Taft Ave., Orange, CA 92665-4296, (800) 854-0547, (714) 998-3021, FAX (714) 974-3420.



### REMOTE CONTROL

Dubbed electronic panning, Bellcore's experimental camera system—together with a high-speed communications network—will allow an unlimited number of people in separate locations to view a scene from an infinite number of directions. The system allows users to customize their views by selecting and controlling what they would most like to see—without affecting the view seen by the other participants.

For example, during a football game on television, one person could watch the action on the field, another person could watch the band practice in the end zone, while a third could look around the stands.

The electronic panning camera incorporates Bellcore-created technology that allows users to visually scan a remote scene while the camera and lens remain stationary.

According to Bellcore, an electronic panning system could span 280° or even 360° so that, fully realized, this technology would permit one to check on rush hour traffic or the children at school without leaving home.

Bellcore (Bell Communication Research) is located at 290 West Mt. Pleasant Ave., Livingston, NJ 07039-2729.

### HIGH TECH RADIOS

Lowe receivers are now available in the US and Canada through Electronic Equipment Bank. HF150 is the most recent addition, converting 30kHz-30MHz, AM, SSB, and Synchro detection. Equipped with 2.5 and 7kHz filters, 60 memories, and a large LCD readout, it accepts three antennas, balanced wire, whip and 50Ω, and weighs less than 3 lbs.

For more details, contact Electronic Equipment Bank, 323 Mill St. NE, Vienna, VA 22180, (800) 368-3270, FAX (703) 938-6911.

### JUST THE FAX

Allied Electronic Services announces the addition of the Tempo Fax Line Eliminator, which answers incoming calls on the first ring and routes the call to the appropriate device, thus eliminating the need for dedicated phone lines.

Three models are available, with prices ranging from \$225 to \$750. For further details, contact Allied Electronic Services, Stonybrook Rd., Lebanon, NH 03766, (603) 448-3572.

### PHONO JACKS

A Hex Base has been added to Mouser Electronics' panel mount phono jack, allowing a 9mm nut driver to secure the jack from the front of the panel, and preventing it from turning while it is being tightened from the back. The nut driver minimizes damage to delicate panel finishes. The new phono jack mounts in a single  $\frac{1}{4}$ " hole.

Contact Mouser Electronics, 2401 Hwy. 287 North, Mansfield, TX 76063, (800) 346-6873.



# A COMPACT SPIRAL T/R HF ANTENNA

**This is a short, efficient, horizontal indoor spiral transmitting/receiving antenna, using 139 feet (approx. 42 m), that can be compacted into a length of about 15 feet (approx. 3 m). It is based on a pair of Slinkys. And, quite reasonably, you may ask "and what on earth is a Slinky?"**

By Richard Q. Marris, G2BZQ

**S**LINKY was first met, by courtesy of the two sons of a colleague, while the author lived and worked in the U.S.A. for several years during the 1970's. Slinky is manufactured in the U.S.A. by James Industries Inc., Hollidaysburg, PA 16648. It consists of  $90 \times 2\frac{1}{4}$  in (90×7 cm) diameter turns of spring made of 67 ft (approx. 20 m) of flat bright steel wire. Each Slinky weighs about  $\frac{1}{2}$  lb (approx. 0.45 kg), and can be extracted to about 15 ft (4.5 m). However, it comes compressed into a  $2\frac{1}{4}$ -in (5.7-cm) length in a robust red carton on which we read that Slinky is 'a walking spring toy' for 'ages 6 and up!'. It was demonstrated to the author as a fascinating toy which would, among other things, walk down stairs!

## Design background

It so happens that as a Slinky is expanded, it resonates as a  $\frac{1}{4}\lambda$  between 7 and 8 MHz. In fact, the retailers (Antenna West) offer suggestions, and kits of parts, for using it as a 7-MHz or 14-MHz delta matched dipole. Each dipole can be resonated by expanding or contracting the spring coil. It is estimated that the bandwidth would be comparatively narrow. Each kit comes with a Slinky, a transparent messenger line, transparent coil positioning tabs, ceiling hooks with hardware, transparent suction caps and white coaxial feedline.

## Antenna description

The requirement was for a short efficient indoor multiband T/R antenna, which can be slung diagonally across a room, and used on most of the H.F. amateur bands.

As the primary, and lowest, frequency was for the 80-m (3.5-MHz) band, two Slinky coils (without accessories) were obtained, and electrically secured end-to-

end. The long double Slinky was hung diagonally across a room, and end-fed with a short single feedline plugged into a suitable ATU (antenna tuning unit) which would resonate it on all amateur bands between 10 m (28 MHz) and 80 m (3.5 MHz). It was anticipated that the voltage and current distribution would be relatively uniform over the whole length, and that a sizeable section of each band could be used without retuning the ATU. As two coils weigh about 1 lb (approx. 0.9 kg), the whole spring was supported by thin nylon

cord, enabling the antenna to be length adjusted, and compressed into a few inches when not in use. Also, it could be discreetly hidden in a corner of the room.

The final operating arrangement is shown in Fig. 1a, and the non-operational arrangement, in Fig. 1b. The 5-ft long feedline drops down from the room corner end, located over the equipment, the ATU. Various ATU types were tried, but the simple 'T' type shown in Fig. 2 proved to be the most effective. The earth connection was taken with about 15 ft (4.5 m) of stout

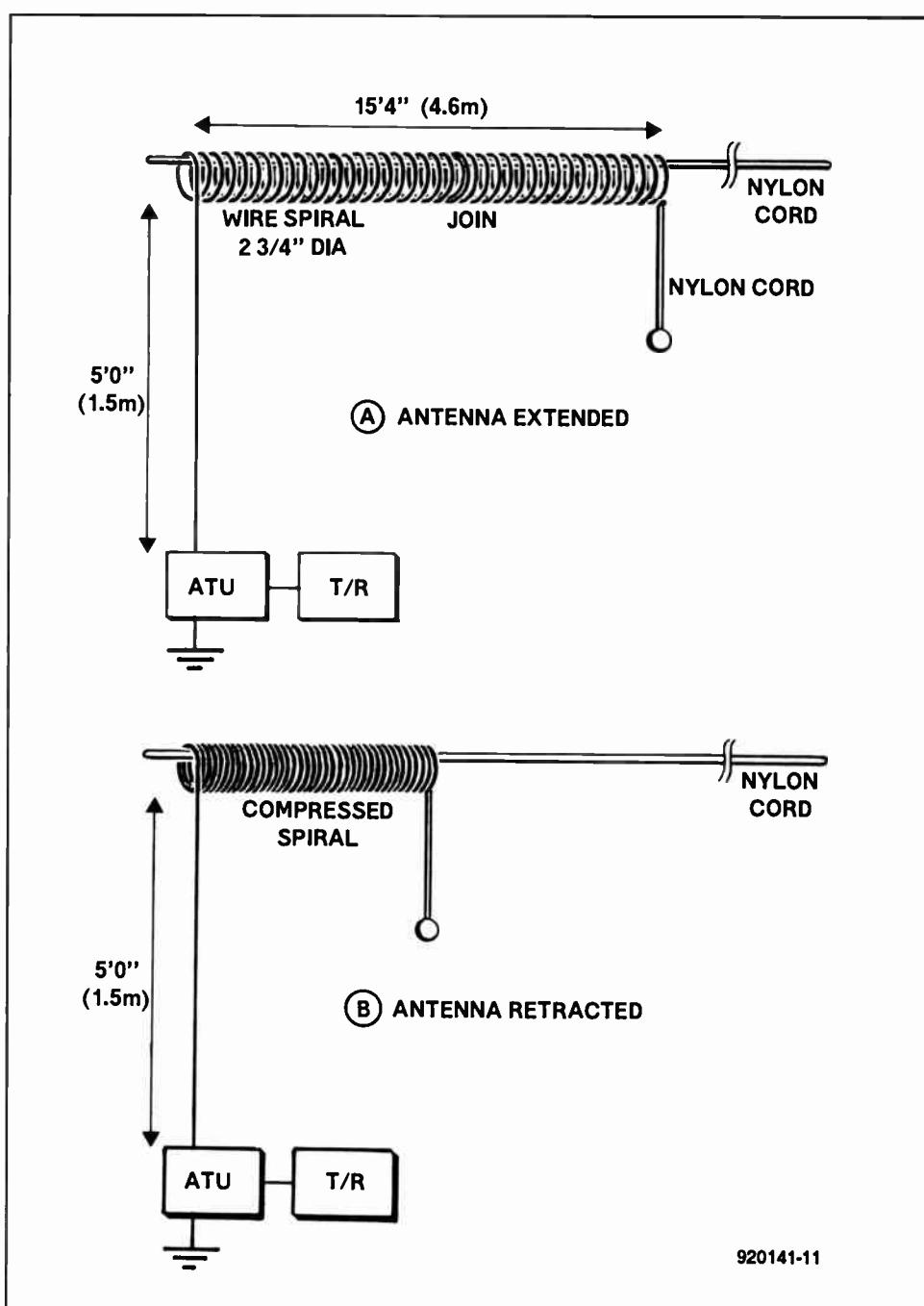


Fig. 1. The spiral loop hangs on a nylon cord attached to the apartment ceiling. Note: length difference between extended and retracted antenna is not to scale.

flex to a convenient water pipe. Though the final antenna is only 15'4" long (approx. 4.6 m), plus the 5-ft (1.5-m) drop-down feeder, there is actually a total of 139 ft (41.7 m) of wire, i.e., 2x67 ft plus 5 ft. The diagonal space across the room was 18 ft (5.4 m). The drop-down feedline is part of the antenna.

## Antenna construction

A length of  $\frac{1}{8}$ -in (1.6-mm) diameter white nylon cord is now suspended diagonally across the room, at least 9 ft (2.7 m) away from the ceiling, and carefully avoiding electric light fittings. Here, the length from corner to corner is 18 ft (5.4 m). The wire coil is now slipped over one end of the nylon cord, before it is securely fixed at one end. A stout 5-ft (1.5-m) long single-core flex feeder lead is soldered to one end of the coil, and dropped down to the ATU, as shown in Figs. 1a and 1b. A piece of nylon cord is tied to the other end of the coil, and terminated with a plastic ring or knob. By using this short nylon cord as a tow line, the coil can be expanded to a length of 15'4" (approx. 4.6 m), and a few turns of nylon cord wound and knotted at this point form an 'anchoring stop' for quickly expanding the antenna coil when in use. The last turn of the coil is slipped over this 'stop'.

When not in use, the coil can be pulled back to a discreet compressed coil at one end (see Fig. 1b). The horizontal length of nylon cord is nearly invisible against a white ceiling.

## ATU construction

Possibly the reader has a suitable existing ATU, and this can be tried. Several ATU configurations were tried with the 'T' type, shown in Fig. 2, which was also the final design adopted. The inductor, L, is a length of B&W coil stock (see Components List), and C1 and C2 are both 250-pF good quality air-spaced variable capacitors. The whole is built into a convenient metal box, the maximum size of which will depend mainly on the type and size of the variable capacitor used. At least one diameter clearance should be left around L.

The spindles of C1 and C2 must be isolated from all metalwork. A convenient way of doing this is to mount C1, C2 and L on a sheet of perspex, or non-metallized fibre-glass board, which is mounted on four short pillars, just behind the metal front panel. Large clearance holes will be required in the metal box panel, so that the spindles of C1 and C2 do not touch the metalwork. Sockets Skt1 and Skt2 are coaxial types of convenient type to the user.

Taps should be made on L, for each band to be used. The ATU will match the antenna to the transmitter/receiver on the 80-m (3.5-MHz), 40-m (7-MHz), 20-m (14-MHz), 15-m (21-MHz) and 10-m (28-MHz) amateur radio bands. The author uses tap-

ping clips, but some of you may prefer a ceramic wafer rotary switch. The method of locating the taps is described below.

## Setting up, testing and operating

With the antenna extracted to 15'4" (4.6 m), and plugged into Skt1, and Skt2 connected to the transceiver with a short length of coaxial feedline, an earthing/grounding connection should be made to the ATU. Here, about 15 ft (4.5 m) of stout wire flex is firmly connected to a convenient metal water pipe. Other convenient grounding arrangements may be used depending on individual circumstances.

Do not connect the ATU to plastic water pipes, metal gas pipes, or metal electric wiring conduit. Do not connect it to the AC mains earthing pin either. Even though the mains earth will, no doubt, be connected to the transceiver, it must not be used as an RF earth connection to the ATU.

Tune the receiver to a convenient spot on the 80-m (3.5-MHz) amateur radio band. Set C1 and C2 to 50% capacity, and move the tap along the coil, L, for maximum signal. Adjust C2 for maximum signal — this will match the ATU to the receiver's input impedance. Next, repeat the adjustment of C1 for best antenna matching. Switch on the transmitter, and carefully re-adjust C1 and C2 for best loading and lowest SWR. Once you are satisfied with the results, secure the 80-m tapping point by either solder, switch or clip connection, depending on what has been decided. An SWR of 1:1 is obtainable with care. Repeat the process for the other bands selected.

It is also possible to match the ATU/antenna combination to Top Band (1.8 MHz), but it is presumed that performance would be suitable for the shorter range operation. It has not been tried.

As an example, the author has used this spiral antenna quite extensively, in the early morning, on the 80-m band, using a 14 watts input CW transmitter. An SWR of 1:1 has been achieved; no harmonics radiation or TVI detected, and the CW section of the band between 3.5 MHz and 3.6 MHz

## COMPONENTS LIST

### Antenna:

White nylon cord, approx. 1 mm diameter. DIY Stores (trade name in UK: Winchester). Qty. 2 Slinky 2 $\frac{3}{4}$ " diameter coils. Antenna West, 1500 North 150 West, Provo, UT 84604, U.S.A.

Note: at the time of writing, a Slinky coil (2 $\frac{3}{4}$ " dia.) costs \$10 each, plus \$10 air mail (total \$30). VISA and Mastercard accepted.

### ATU:

L = 26 $\mu$ H inductance. B&W no. 3059 (available in the UK from RF Engineering, Main Street, Coln-St. Aldwyns, Cirencester, Glos GL7 5AN. C1 and C2 = good quality 250-pF single-gang variable capacitor, with knob. SKt1, Skt2 = see text. Perspex or fibre glass board (see text).

can be used without retuning C1 and C2. The antenna appears to be omnidirectional, with near uniform current/voltage distribution along the whole spiral coil. Tests on other bands have been similar. The results with the antenna diagonally across the room, in a first floor room, have been very satisfactory. For anyone who has not the full required length available, it is suggested that part of the far end of the spiral be dropped down, or taken off at an angle.

## Final considerations

The spiral antenna has been designed for use indoors. It could, of course, be used outside, but being made of bright steel, would quickly corrode. This problem could probably be eliminated by any reader who has facilities to degrease and marine varnish each turn, inside and outside, and between turns. At least two coats of varnish would be necessary for protection. An expensive, and, alas, somewhat specialized, alternative would be to chrome-plate the whole spiral coil.

Assuming that this antenna will be used indoors (as designed and intended), in the interest of safety, only low transmitting power should be used. Good quality air-spaced receiver-type variable capacitors for C1 and C2 should be satisfactory with transmitter output levels of up to 25 watts.

### Useful reading

Antennas — 2nd edition, 1988, by John. D. Kraus (McGraw-Hill Book Company). Antenna Book — 16th edition, 1991 (American Radio Relay League). W1FB's Antenna Notebook — by Doug De Maw, 1987 (American Radio Relay League).


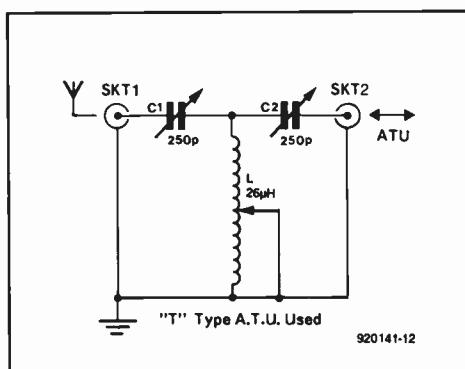


Fig. 2. Type 'T' ATU used.

# PRINTER SHARING UNIT

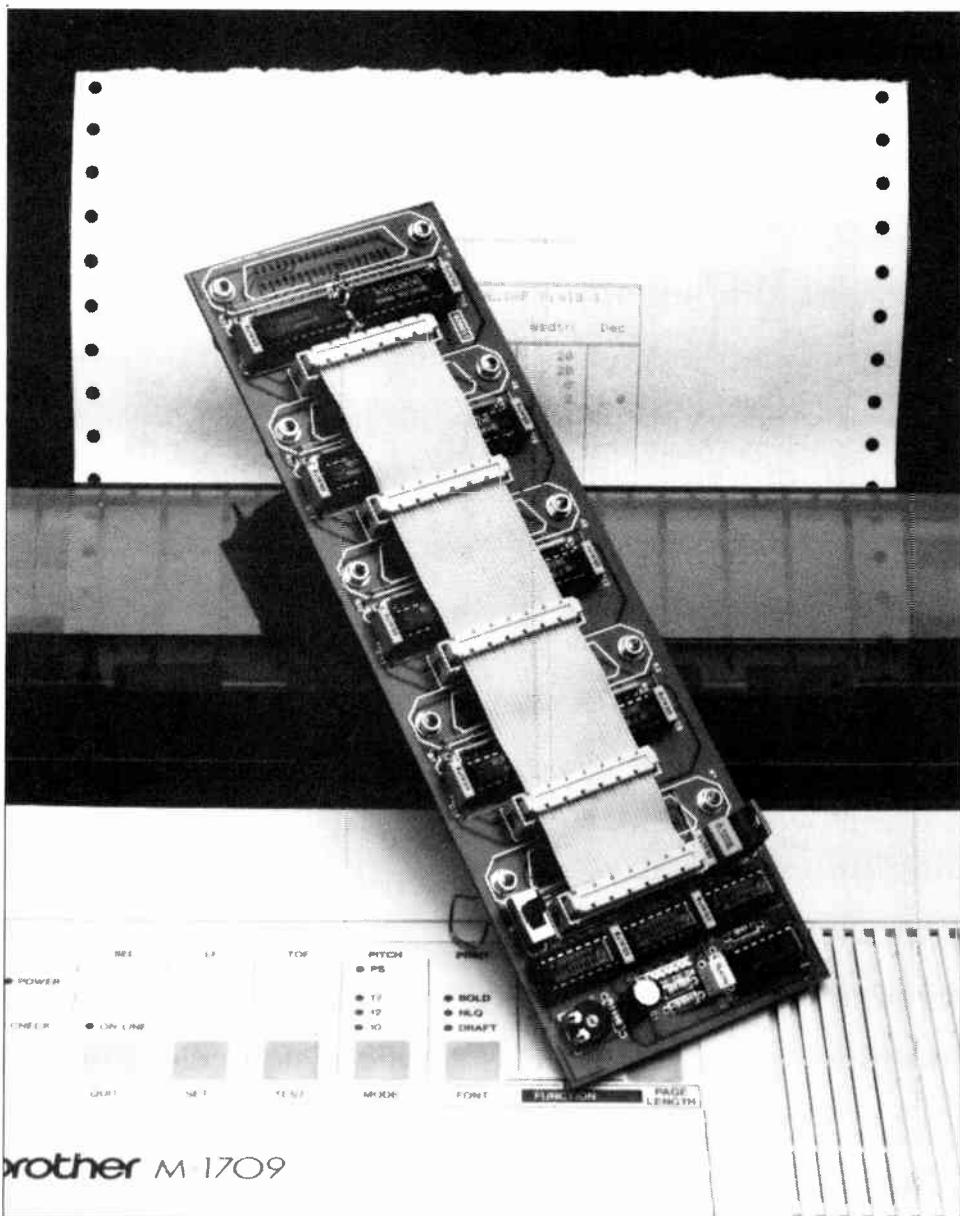

A printer is an essential peripheral device for nearly every one using a PC. However, since a printer will rarely be used all the time, it is not necessary to have one with every PC within a range of, say, 10 m. The circuit described here is an automatically operating switching unit that allows up to four PCs to make use of a single printer.

**Design by A. Rietjens**

In particular with fairly expensive printers it is common practice to set up some kind of sharing arrangement where there are several PCs. Not surprisingly, printer switching units are found in many small offices these days.

The basic operation of the printer sharing unit is illustrated by the block diagram given in Fig. 1. There are up to four

Centronics inputs, each of which is connected to a bus that conveys the signals to the printer connected to K1. The block marked 'select' connects each of the four inputs to the output, at a repeat rate of 1/second. If a computer connected to a particular input does not send data at that time, the circuit switches to the next input. If the computer does send data during the

time it is connected to the printer, this responds by making the BUSY line high. This event triggers a monostable multivibrator (MMV) which immediately disables the oscillator and the select block. As long as BUSY remains high, or goes high again within the MMV's monotime, the printer will remain connected to the computer that sends data. However, as soon as the computer is found waiting longer than the set monotime, the circuit starts to scan its inputs again for activity, i.e., another computer that may have data ready for the printer.

Some of you may wonder at this point why the BUSY line of the printer is used rather than the strobe pulse of the computer to detect if data is being conveyed. At first glance, using the strobe pulse would appear much more logical since that signal is supplied by the source of the data, i.e., the computer. There is, however, a snag: some computers may block the printer switch when they are switched off, because the strobe output then forms a low level (remember, the strobe pulse is active low). By contrast, a 'true' Centronics strobe output is an open collector driver without a pull-up resistor, and does not cause problems in this respect because it 'floats' when the PC is switched off. Unfortunately, not all printer card manufacturers abide by the Centronics standards, so that it is very well possible that the strobe line forms a 'low' level when the PC is switched off. Obviously, this causes problems on the printer sharing unit since in that case an active Centronics port is detected.

The above problems are prevented by using the printer's BUSY line. This allows the circuit to respond to the fact that data have already arrived at the printer, and this data can only originate from a computer that is switched on.

Still, the printer switch is not quite perfect. As far as we have been able to ascertain, there are two cases in which things can go wrong. This has to do with the structure of the software that runs on the computer.

In the first case, we refer to programs that check beforehand if a printer is available. In most cases, this check lasts long enough to allow the printer sharing unit to finish its input scanning cycle until it reaches the computer that wants to print at that time. By contrast, there are also programs that insist on finding a printer right at the first check. If the computer that runs such a program happens to be not selected during the check, the program will refuse to print (on some computers this occurs, for instance, with the 'print screen' routine). Fortunately, this can be solved manually: the scan rate of the printer switch inputs is indicated by LEDs, and slow

enough for you to launch the print job at the right instant. The only proviso for this little trick is that you can see the printer sharing unit from your workplace.

The second problem arises when a program interrupts its printer output routine to calculate the next data to be printed. If this calculation lasts longer than the set MMV time on the printer sharing box, another computer may 'throw in' its data. If you are using such software, there is no option but to ask your fellow printer users not to send data before your PC is finished.

## How it works

The circuit diagram, Fig. 2, shows five sub-circuits. The bus that connects these sub-circuits is a length of flatcable with five IDC sockets inserted into the even numbered headers. The use of the flatcable bus will be reverted to when we talk about the printed circuit board.

Four of the five sub-circuits are identical. They represent the four PC input connectors (K<sub>3</sub>, K<sub>5</sub>, K<sub>7</sub> and K<sub>9</sub>) with the associated electronic switches. Here, the switches are formed by buffers with three-state outputs (IC<sub>6</sub>-IC<sub>13</sub>). When a particular input circuit is not selected, its buffer outputs are switched to high impedance, which means that all signals from the computer to the bus and the printer, and from the bus to the computer, are disconnected. Also, the bus-to-computer lines are then pulled to a logic level that tells the computer that the printer is not ready to receive data. This is achieved with the aid of pull-up and pull-down resistors. A normal Centronics link between computer and printer exists only on the selected input, since there the buffer outputs are switched to their active state.

The most interesting section of the circuit is the fifth sub-circuit. Electrically, this sits between printer connector K<sub>1</sub> and bus connector K<sub>2</sub>. This is the central control of the printer sharing unit. Assuming the printer is not busy, and none of the PCs offers any data, the printer's BUSY line (pin 11 on K<sub>1</sub>) is logic low, and monostable IC<sub>4a</sub> is not triggered. In this condition, the pulse generator built around IC<sub>2d</sub> is enabled, and produces a short pulse every 0.33 s. The trailing edge of the oscillator pulse clocks two J-K bistables, IC<sub>5a</sub> and IC<sub>5b</sub>, which function as a counter. The counter continually cycles through states 0, 1, 2 and 3. The counter state is sent to four individual lines by decoders IC<sub>3a</sub> and IC<sub>3b</sub>. The four outputs of IC<sub>3a</sub> are used to select the buffers in the input circuits. This selection runs at a rate of 0.33 s. Decoder IC<sub>3b</sub> functions similarly to IC<sub>3a</sub>, but it controls LEDs instead of input buffers. These LEDs indicate the currently selected input. IC<sub>3a</sub> also controls LEDs fitted with each input connector. The purpose of these LEDs will become evident when the construction of the unit is discussed.

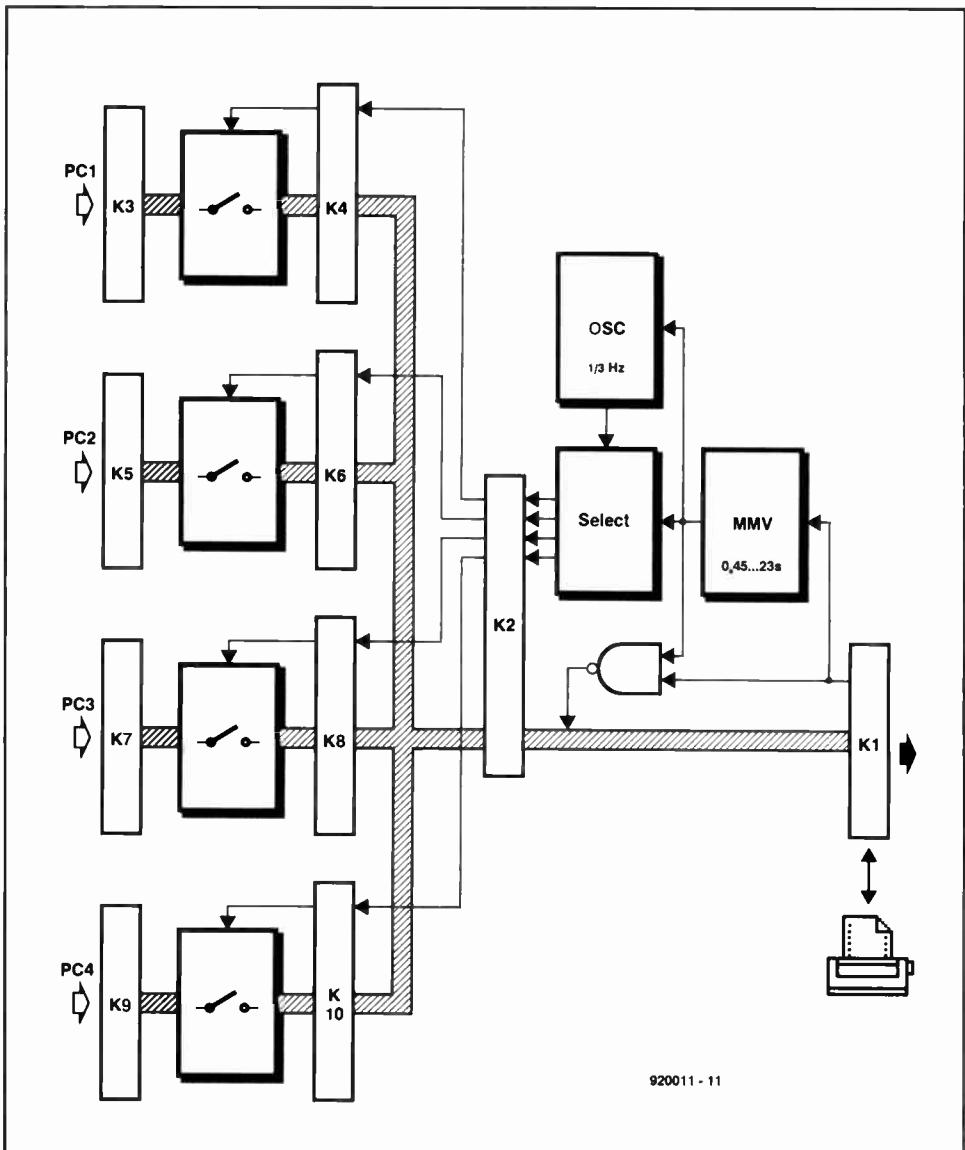


Fig. 1. Block diagram of the printer sharing unit. Four inputs are continuously monitored for the presence of printer data.

Gates IC<sub>2a</sub>, IC<sub>2b</sub> and IC<sub>2c</sub> are essential to prevent timing problems. Their logic function is

$$\text{BUSY}_{\text{(out)}} = \text{BUSY}_{\text{(in)}} + \text{CLK} \cdot Q^{\backslash}$$

which means that the BUSY signal supplied by the printer ( $\text{BUSY}_{\text{(in)}}$ ) is always conveyed directly to the connected computer ( $\text{BUSY}_{\text{(out)}}$ ). However, it is also readily seen that the circuit, when it is not active ( $Q^{\backslash}$  at '1') supplies a 'BUSY' signal to the computer when the clock pulse is high. From that moment on, the selected computer can not send data any more. But what happens if the computer has just before sent its first byte, and the printer has not responded to it by pulling the BUSY line high? Fortunately, the clock pulse is long enough to ensure that this first BUSY signal arrives before the end of the clock pulse. In that case, the circuit will keep the active computer 'hanging on'. i.e., selected. If no BUSY signal arrives from the printer in the mean time, the circuit can safely switch to the next computer input, which happens on the trailing edge of the

clock pulse. After this edge, the selected computer is immediately supplied with a low (inactive) BUSY signal (neither the printer nor the circuit was busy). This is taken to indicate that new data may be sent. Since this data will not be ready for at least 0.5  $\mu$ s, input switching can safely take place.

The moment the printer responds to the data with a BUSY signal, monostable multivibrator IC<sub>4a</sub> is triggered. The setting of the monostable determines how long the circuit waits for new data after the printer has stopped printing. Because IC<sub>4a</sub> is triggered,  $Q^{\backslash}$  goes low. During the monotime, the clock generator and the counter are disabled, and gates IC<sub>2a</sub>, IC<sub>2b</sub> and IC<sub>2c</sub> simply convey the printer's BUSY signal. As long as the BUSY line remains high, or goes high again within the monotime, the MMV is triggered again. The monotime can be set to between 0.45 s and 23 s with the aid of preset P<sub>1</sub>. If the monotime passes without a BUSY signal arriving,  $Q^{\backslash}$  reverts to high, and the counter and oscillator are enabled again. The circuit is then back in its stand-by state, scanning the

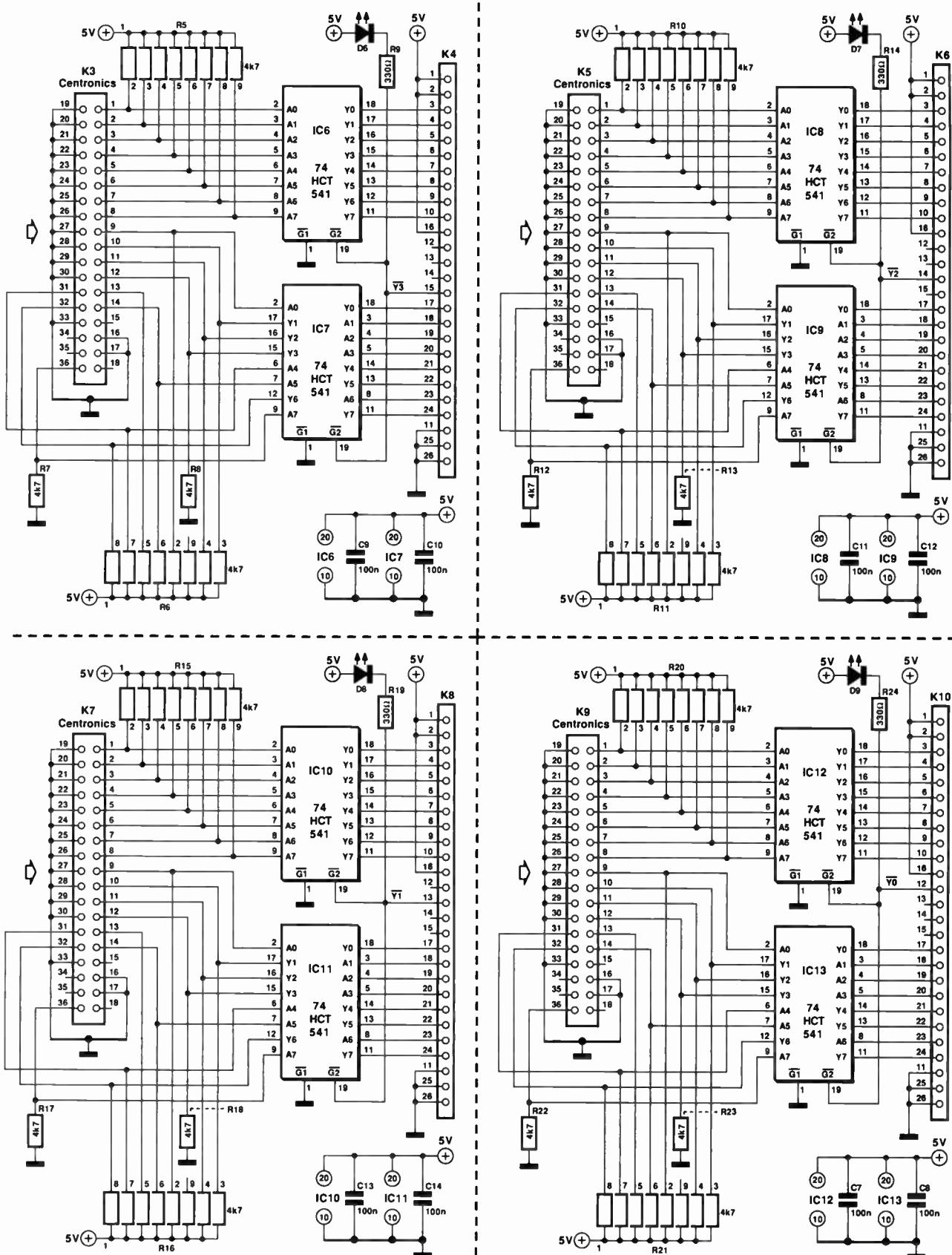


Fig. 2. The circuit diagram consists of five blocks: four identical input circuits, and a control/output circuit.

four inputs for data.

The power supply for the printer sharing units may be realized in two ways. With switch S1 set to the position shown in the circuit diagram, the supply voltage is obtained from the printer. Unfortunately, not every printer furnishes a suitable supply voltage, whence the external power supply option. Any external power supply may be used that supplies an unstabilized direct voltage between 8 V and 20 V. Regulator IC1 reduces this unstabilized voltage to a stabilized 5-V rail for the circuit. Incidentally, do not be surprised if you find that the circuit works perfectly with no power supply connected at all — in some cases, it can draw enough current from the computer outputs to build up its own supply voltage. Convenient as it may be, this situation does not guarantee reliable operation!



## A large circuit board

The printed circuit board designed for the printer sharing unit consists of five smaller boards, which are interconnected via a flatcable (the previously mentioned bus). In spite of the 'modular' layout of the large PCB, it is by no means necessary to separate the sub-boards from another. Even when they are left together, they form a compact printer switch. However, if you wish to separate them, this is no problem at all — all that has to be done is to adapt the length of the flatcable as required.

A number of options are available for the LEDs that indicate the currently active input. An LED may be fitted next to each input connector. Alternatively, LEDs may be fitted next to the output connector. The decision on fitting or not fitting a certain LED depends on the way the printer switch is built into a case. For instance, you may fit a LED next to each connector on the rear panel (particularly useful for faultfinding purposes), and the other four LEDs on the front panel, for all users to see.

Apart from the flatcable, the Centronics connectors and the LEDs next to the input connectors, construction of the unit is all plain sailing. As always, fit the wire links first so that these are not forgotten later. Pins 1 to 18 of the connector are at the side of the associated LED. Before you start soldering the connector pins, fit the connectors on two 7.5-mm (0.3 in.) high pillars. Alternatively, if you can not find Centronics sockets for PCB mounting, you may use connectors with solder pins, fit these at the required height, and connect them to the PCB via short wires.

Assuming that you have not cut the PCB into modules, the next step is to make the flatcable. This is precision work, since the spacing of the IDC sockets on the cable is critical. If you fit them too close together, you will be unable to plug them on to the headers on the board. Likewise, if

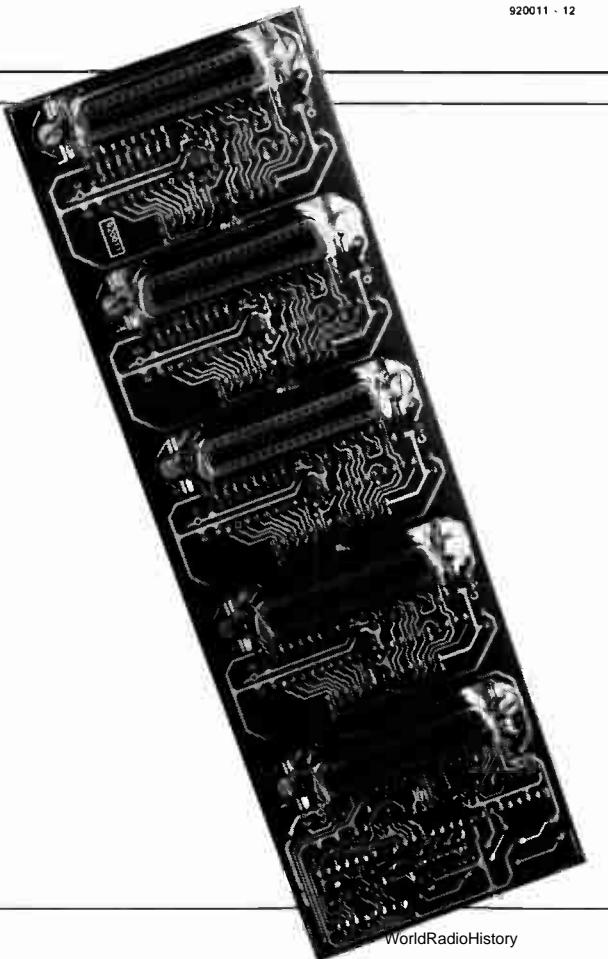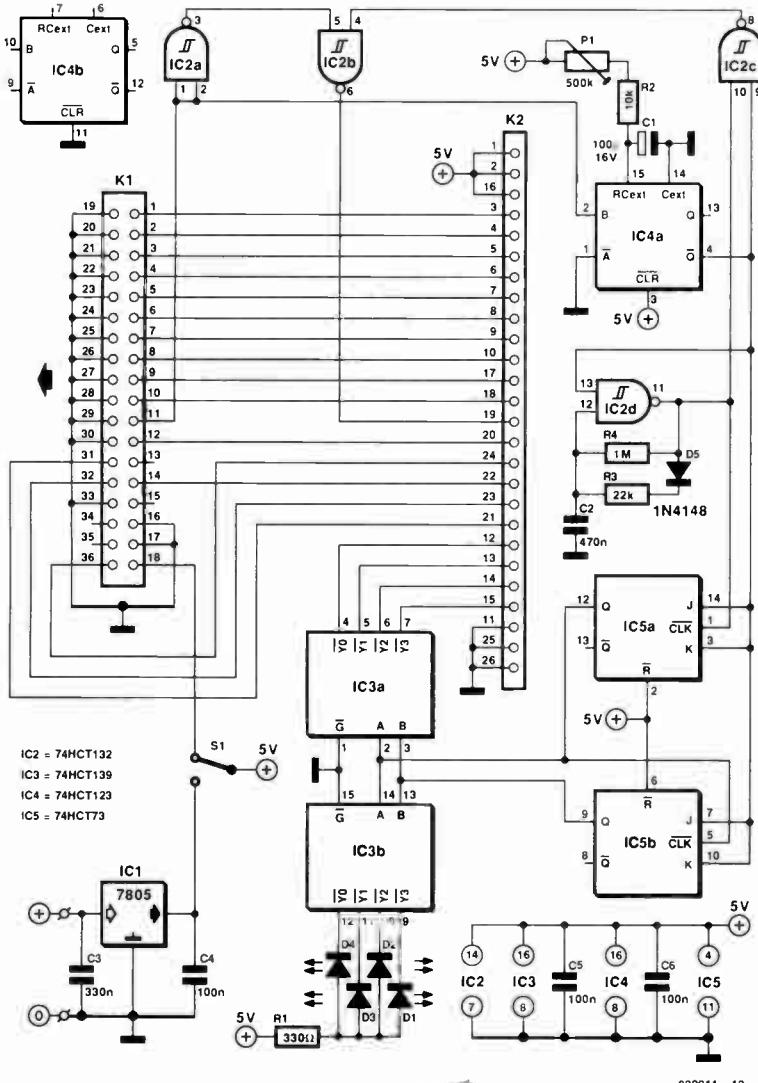

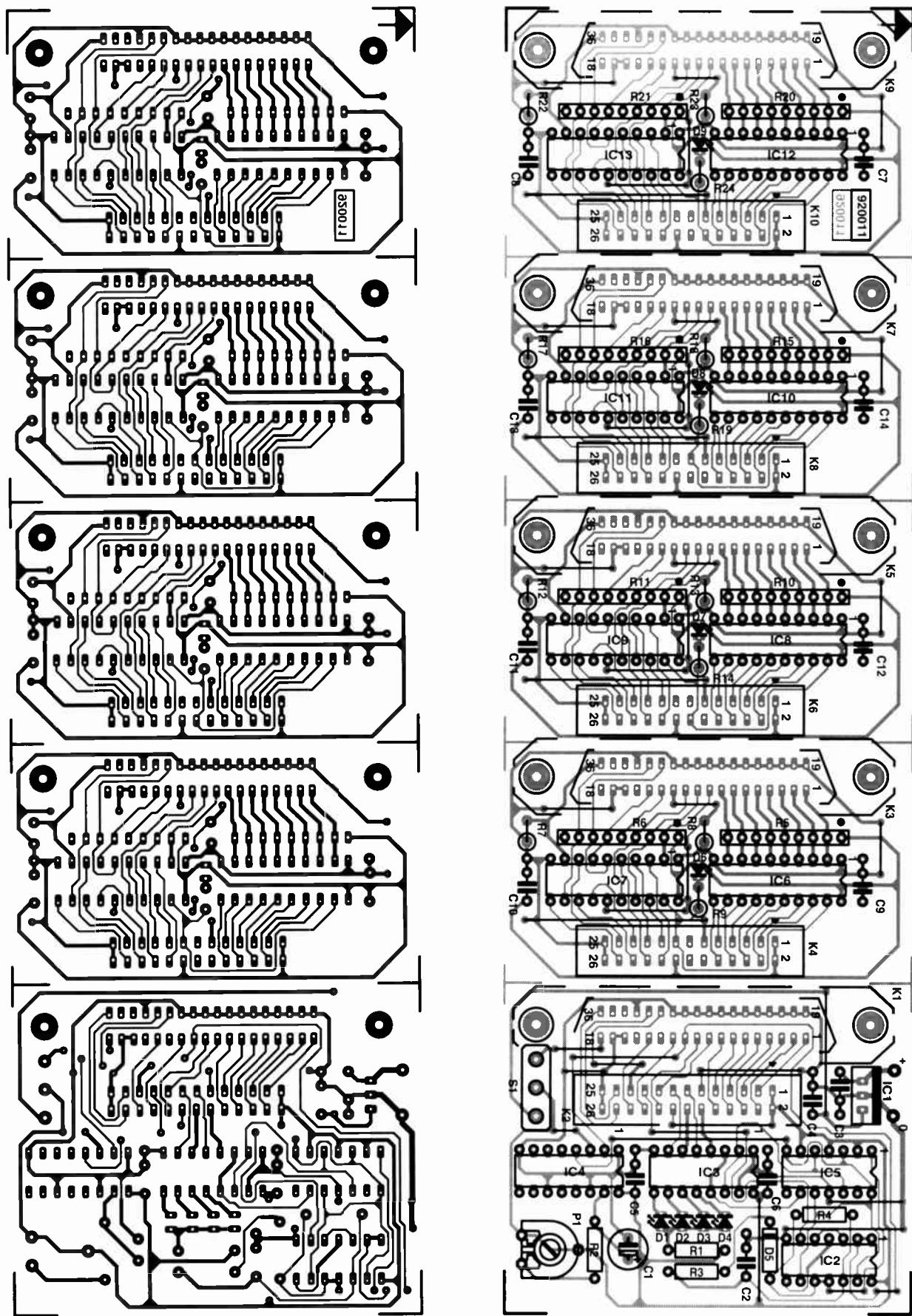


Fig. 3. The printed circuit board may be cut into five separate parts.

## COMPONENTS LIST

## Resistors:

5	330Ω	R1;R9;R14; R19;R24
9	4kΩ7	R7;R8;R12; R13;R17;R18; R22;R23
1	10kΩ	R2
1	22kΩ	R3
1	1MΩ	R4
8	4kΩ7 8-way SIL	R5;R6;R10; R11;R15;R16; R20;R21
1	500kΩ preset H	P1

## Capacitors:

1	100μF 16V radial	C1
1	470nF	C2
1	330nF	C3
11	100nF	C4-C14

## Semiconductors:

8	LED	D1-D4;D6-D9
---	-----	-------------

1	1N4148	D5
1	7805	IC1
1	74HCT132	IC2
1	74HCT139	IC3
1	74HCT123	IC4
1	74HCT73	IC5
8	74HCT541	IC6-IC13

## Miscellaneous:


1	SPST switch for PCB mounting (raster: 7.5 mm)	S1
5	36-way PCB-mount Centronics socket, straight pins	K1;K3;K5;K7; K9
5	26-way box header, straight pins	K2;K4;K6;K8; K10
5	26-way IDC flatable socket	
17cm	26-way flatable	
1	Printed circuit board	920011

you fit them too far apart, the cable will bulge. That is not a problem in itself, however it does not look very good.

When the completed PCB is to be fitted behind a front or rear panel, this will have to be done from the inside. Note that the Centronics sockets used here are not really suitable for panel mounting, but it can be done. First, drill the holes for the fixing

screws. Next, cut and file a rectangular clearance that is long and wide enough to pass the connector and the clamp springs (approx. 58x15 mm). The locations of the holes are easily pencilled out on the panel by making use of the (empty) printed circuit board, or a photocopy of the component layout.

The circuit has only one adjustment:

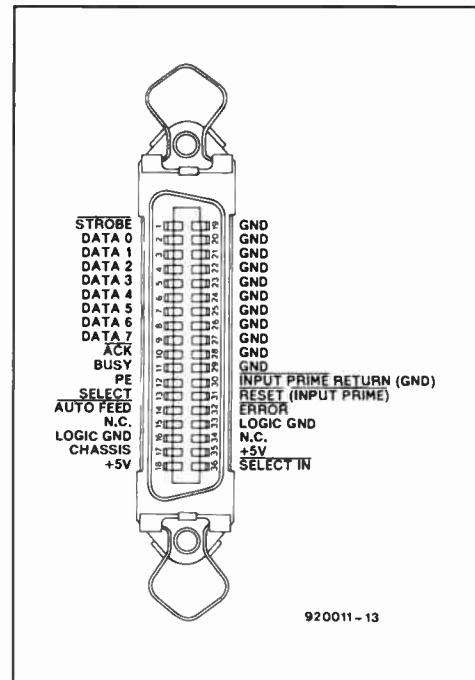

920011-13

Fig. 4. Centronics connector pinning.

preset P1. This has to be adjusted such that the printer sharing unit is capable of 'bridging' the longest time your software needs for calculations before it sends new printer data. In case you are not sure about what sort of times to expect, simply set P1 to maximum resistance (wiper towards IC4).

A N N O U N C I N G

**A**T long last, *Elektor* project builders on this side of the Atlantic can use this special software downloaded from the Dutch *Elektuur*'s internal files. WRITTEN IN DUTCH, EIT provides the manufacturer (name only) for more than 2700 hard-to-find European parts used in *Elektor* projects during the ten years covered. Menu-driven and including a short list of translations for key words and phrases, this detailed index is cross-referenced by ten different parameters, including part number and article title, and requires 4MB of hard drive memory. Despite the language gap, EIT is fun to use and easily mastered in less than an hour—to provide a lifetime of reference value.



TELEPHONES:  
(603) 924-6371  
(603) 924-6526  
FAX:  
(603) 924-9467

**OLD COLONY SOUND LAB**

PO Box 243  
Peterborough, NH 03458-0243

**EIT** ELEKTOR  
ITEM  
TRACER 1982-1991

OCSL PART #  
**SOF-EIT2B5**  
2 x 360K DS/DD

\$ **7.95** POSTPAID

**YES!** PLEASE SEND ME        EIT(s)

@ \$7.95 POSTPAID FOR A TOTAL OF \$       

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_

ST \_\_\_\_\_

ZIP \_\_\_\_\_

DAYTIME TELEPHONE \_\_\_\_\_

TODAY'S DATE \_\_\_\_\_

PAYMENT BY:  MC  VISA  CHK/MO

MC/VISA \_\_\_\_\_

EXP. DATE \_\_\_\_\_

# OUTPUT AMPLIFIER FOR RIBBON LOUDSPEAKERS

## PART 1

Design by T. Giesberts

**This article describes an out-of-the-ordinary amplifier for driving very-low-impedance transducers such as ribbon loudspeakers. The amplifier is able to deliver 20 A<sub>rms</sub> (with peaks up to 30 A) into a load of 0.4 Ω with low distortion.**

The modern ribbon loudspeaker is among the most efficient transducers available. Its construction is very simple: the diaphragm consists of an aluminium foil ribbon suspended between the poles of a magnet—see Fig. 1. The nominal flux density in the gap is about 1.0 Tesla. A practical ribbon is 5–7 mm long, 8–12 mm wide, 3 μm thick and has a mass of 3–4 mg. Its resistance is 0.2–0.5 Ω. Such a unit is eminently suitable for use as a tweeter. However, over the past few years wide-range ribbon loudspeakers using much longer ribbons have become available, such as those of Strathearn (50 cm or 2 in) or, among others, Gold Ribbon and Speakerlab that measure a metre or more.

### Low impedance

Unfortunately, ribbon loudspeakers have such a low impedance that they are normally connected to the output stage via a suitable impedance transformer. This is, however, not beneficial for the reproduction of the higher audio frequencies.

The present amplifier enables direct driving of a ribbon loudspeaker: it can deliver up to 160 W into 0.4 Ω. The larger part of the transfer resistances in the connections are compensated by two separate sense lines. Although it is designed primarily for the Strathearn speaker, it is equally suitable for other transducers that have an impedance of 0.2–1 Ω (higher is possible, but the available power may then be insufficient owing to the low supply voltage used).

### The concept

A current of 20 A<sub>rms</sub>, corresponding to a power of 140 W into 0.4 Ω, was deemed sufficient for most applications. The output transistors are Sanken types which offer a combination of high current amplification, good bandwidth, and a high peak collector current.

To nullify the transfer resistances of the output connections (a cable resistance of 0.05 Ω is not negligible if the load impedance is only 0.4 Ω), the feedback point is as close to the loudspeaker as possible: a sort of sense input.

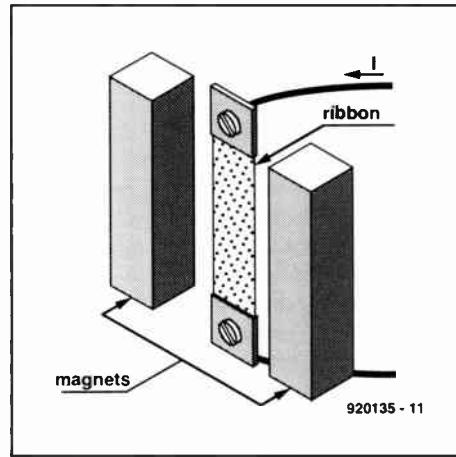


Fig. 1. Principle of ribbon loudspeaker.

The result is that the amplifier compensates for virtually all resistance between its output and the loudspeaker.

Problems also arose in the choice of the

power-on delay that obviates the clicks resulting from switching the amplifier on. For a number of reasons, relays were discounted from the onset. Of the various electronic means, an optocoupler-triac solution was found to be the most efficient and satisfactory.

### Block diagram

The block diagram of the amplifier given in Fig. 2 clearly shows the symmetrical design. Differential amplifiers T<sub>1</sub> and T<sub>3</sub>, each giving an amplification of about ×100, form the input stage. They are followed by differential amplifiers T<sub>2</sub> and T<sub>4</sub> respectively, each of which has an amplification of ×20.


The optocouplers in the collector circuits of T<sub>2</sub> and T<sub>4</sub> serve to suppress clicks resulting from switching the amplifier on or off. The power-on delay ensures that the LEDs in the optocouplers light up slowly. Initially, therefore, impedance matching transistors T<sub>12</sub> and T<sub>13</sub>, and thus drivers T<sub>16</sub> and T<sub>17</sub>, are off so that no current flows in the output stage. Since in this way the opto-transistors are driven into conduction slowly, power to the output stages rises gradually. This arrangement effectively suppresses switching-on clicks.

Since the impedance matching transistors are current-driven by the differential amplifiers, any non-linear behaviour of the opto-transistors has no effect on the reproduction quality.

Transistor zener T<sub>14</sub>–T<sub>15</sub> between impedance matching transistors T<sub>12</sub> and T<sub>13</sub> arranges the quiescent current through the output stages.

Each of the output stages consists of a driver, T<sub>16</sub> and T<sub>17</sub> respectively, which drives two parallel-connected output transistors, T<sub>18</sub>–T<sub>19</sub> and T<sub>20</sub>–T<sub>21</sub> respectively.

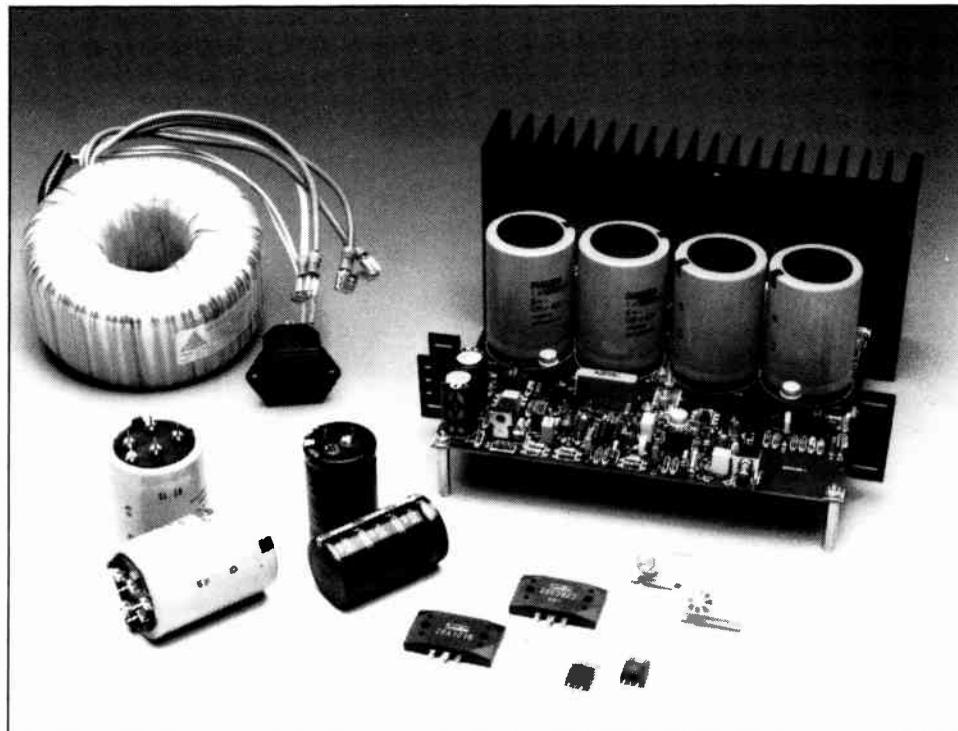The current through the output transistors is monitored by the current limiting stage; if it rises above 30 A (dependent on the base-emitter voltage of T<sub>22</sub>) and the mains fuse



does not blow, the optocouplers are switched off instantly and the fuses in the power supply lines blow because the protection circuit switches on two heavy-duty triacs between those lines and earth. The protection circuit is also actuated if a direct voltage should appear at the amplifier output.

The loudspeaker is connected to the output stages by four wires: two heavy-duty ones through which the high currents flow, and two sense lines that carry the feedback signals.

## Circuit description

The input signal, normally provided by a preamplifier or active cross-over network, is applied to  $C_1$ . This capacitor and  $R_1$  form a high-pass filter with a cut-off frequency of 9 Hz (this frequency may be lowered by giving  $C_1$  a higher value). This is followed by a high-pass filter,  $R_2-C_2$ , with a cut-off frequency of 280 kHz, to prevent transient intermodulation distortion (TID).

The signal is then fed to differential amplifiers  $T_1$  and  $T_3$ . Since the thermal stability of these amplifiers depends on the coupling between the two transistors, the types shown are ideal because the two transistors are housed on one chip. Unfortunately, there is a dearth of double transistors, so that the choice here is very limited.

Frequency compensation for these amplifiers is provided by  $R_5-C_3$  and  $R_{10}-C_4$  respectively. The values of the emitter and collector resistors shown give an amplification of around  $\times 100$ .

The constant-current sources for the amplifiers are formed by  $T_5$  and  $T_6$ , which use LEDs ( $D_1$  and  $D_2$ ) as reference. The current through these diodes is held constant by ancillary current source  $T_9-R_{15}$ .

Since the amplification of  $T_1$  differs from that of  $T_3$ , it is important that the offset voltage of the amplifier is kept as small as feasible. To this end, the base currents of these transistors are compensated by a negative voltage derived from regulator  $IC_4$  via  $R_{35}$  and  $R_{34}$ . This negative voltage holds the base voltage at virtually 0 V. Any other drift, such as caused by temperature variations, is nullified by an integrator based on  $IC_3$ . This stage readjusts the base voltages of  $T_1$  and  $T_3$  if required. The supply lines of  $IC_3$  are additionally buffered by  $C_{18}$  and  $C_{19}$ , which ensure that the stage remains operative for a short while after the amplifier has been switched off.

Then follow differential amplifiers  $T_2$  and  $T_4$  ( $\alpha \approx 20$ ), whose frequency compensation is provided by  $C_9$  and  $C_{10}$ . Transistors  $T_7$  and  $T_8$ , together with diodes  $D_3$  and  $D_4$ , form the constant-current sources for the amplifiers. The current through the LEDs is held stable by ancillary current sources  $T_{10}-R_{17}$  and  $T_{11}-R_{18}$ .

Because of the arrangement of the ancillary current sources, it is essential that diodes  $D_1-D_4$  have a forward voltage of 1.55–1.65 V.

The signal is then applied via the transistors in the (power-on delay) optocouplers to impedance matching transistors  $T_{12}$  and  $T_{13}$  that drive current amplifiers  $T_{1b}$  and  $T_{1c}$ . The collectors of  $T_{12}$  and  $T_{13}$  are linked by transistor-zener  $T_{14}-T_{15}$ . The voltage across this zener, and consequently the direct current through power transistors  $T_{1b}-T_{19}$  and  $T_{20}-T_{21}$ , is preset with  $P_1$ .

The emitter resistances of the power transistors consist of parallel combinations of resistors. This is not because of dissipation, but rather to divide the large currents over a number of soldering points. Moreover, the arrangement lowers the spurious inductance, which is important with low-impedance loads.

Transistor  $T_{22}$  is switched on when the peak emitter current of  $T_{19}$  or  $T_{21}$  exceeds 30 A, whereupon the protection circuit is activated.

Although fuses  $F_1$  and  $F_2$  are rated at 7.5 A, they can withstand currents of up to 30 A, since they carry only one-half of the output signal. The + and – terminals in series with them are connected to the protection circuit. If one of the fuses blows, the LED in parallel with it lights.

Resistor  $R_{47}$  and  $C_{12}$  form a Boucherot network. Inductor  $L_1$  is for use only with traditional loudspeakers; if only ribbon types are used, it may be omitted.

The sense lines are connected to potential divider  $R_{48}-R_{50}$ , of which  $R_{49}$  and  $R_{50}$  determine the feedback factor, while  $R_{48}$  and  $R_{51}$  ensure that the feedback remains functional if the sense lines are not connected. The feedback signal is taken from junction  $R_{49}-R_{50}$  to the bases of  $T_{1b}$  and  $T_{1c}$ . Network  $R_{75}-R_{76}-C_{23}-C_{24}$  serves to equalize the impedance at the bases of  $T_{1b}$  and  $T_{1c}$  with that at the inputs of  $T_{1a}$  and  $T_{1d}$ . This arrangement improves the common-mode behaviour of the amplifier. The network does not affect the feedback.

## Protection circuit

The diagram of the protection circuit is shown in Fig. 4. When the power is switched on, capacitor  $C_3$  is charged slowly via  $R_4$ . It takes, therefore, a few seconds before darlington  $T_7-T_8$  is switched on, whereupon the LEDs in the optocouplers (connected to  $B_1$  and  $B_2$ ) begin to light. When the potential across  $C_3$  has risen to 1.7–1.8 V, the LEDs light at maximum brightness. The darlington then operates as a constant-current source, since  $D_5$  holds the voltage across  $R_{15}$  and that across the base-emitter junction of  $T_7$  and  $T_8$  stable.

Since  $T_1$  is connected to the secondary of the mains transformer via diodes  $D_1$  and  $D_2$ , it is switched on every half period as long as the mains voltage is on. Transistor  $T_2$ , and consequently  $T_3$ , is then off. When there is no voltage across the secondary, for instance, when the power is switched off,  $T_2$  and, consequently  $T_3$ , is switched on after half a period. This results in Schmitt trigger  $T_4-T_6-D_4$  changing state, whereupon  $T_7$  and  $T_8$ , and thus the optocouplers, are switched off. This is indicated by the lighting of  $D_{11}$ .

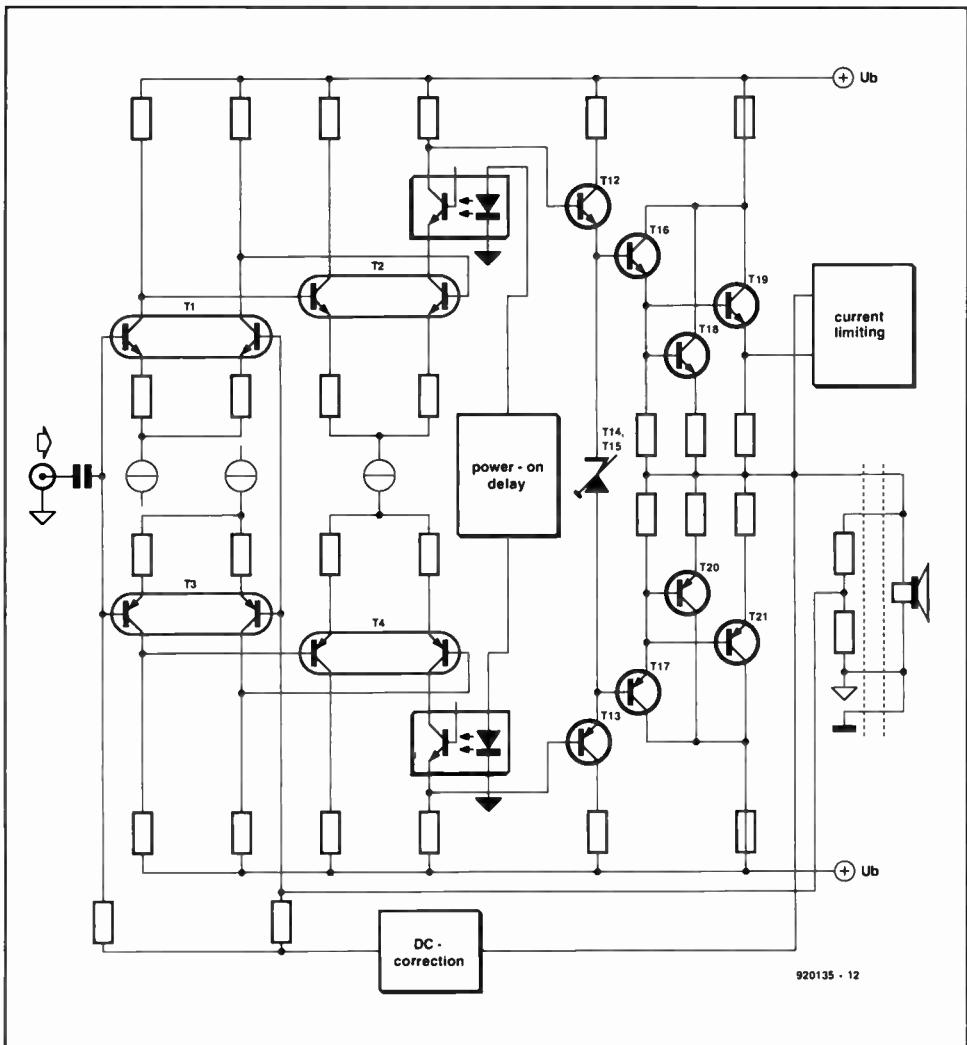


Fig. 2. Block diagram of the output amplifier.

Current monitoring transistor  $T_{22}$  is connected to terminal A. When the load current gets too large,  $T_{22}$  begins to conduct, so that  $T_3$  is switched on and the optocouplers are switched off. Darlington  $T_{11}$  switches on triacs  $\text{Tri}_1$  and  $\text{Tri}_2$  via  $D_8$ , whereupon the supply

lines are short-circuited to ground. If this option is not required, that is, the switching off of the optocouplers is deemed sufficient,  $D_8$  may be omitted.

Protection against high temperatures is provided by  $T_{12}$  (connected as diode) and

$\text{IC}_{1a}$ . Through the transistor, which is mounted on the common heat sink for the power transistors, flows a direct current via  $R_{18}$  and  $R_{19}$ . The voltage across  $T_{12}$  is applied to the inverting (-) input of  $\text{IC}_{1a}$ , which operates as a comparator with hysteresis (provided by


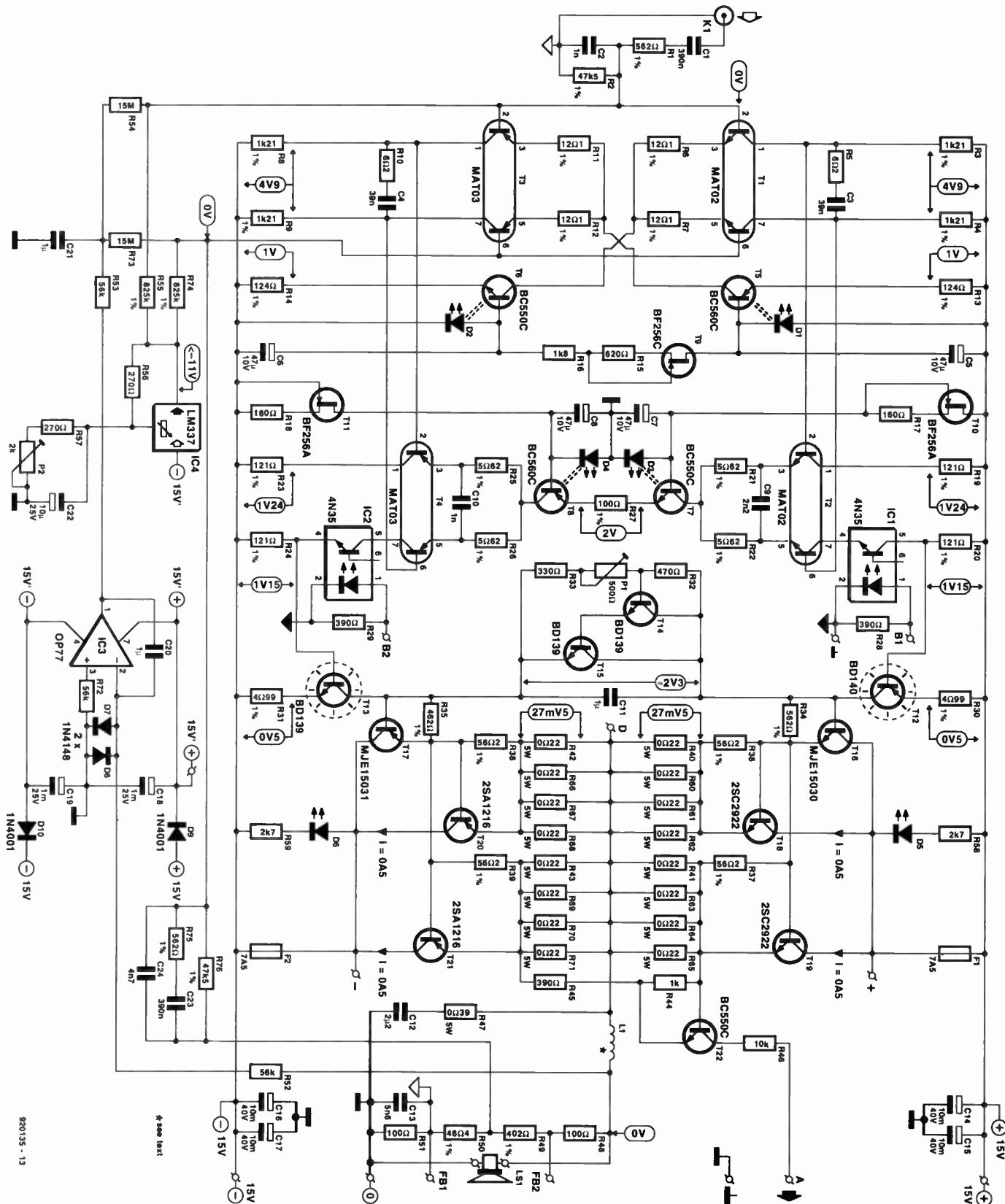


Fig. 3. Circuit diagram of the amplifier.

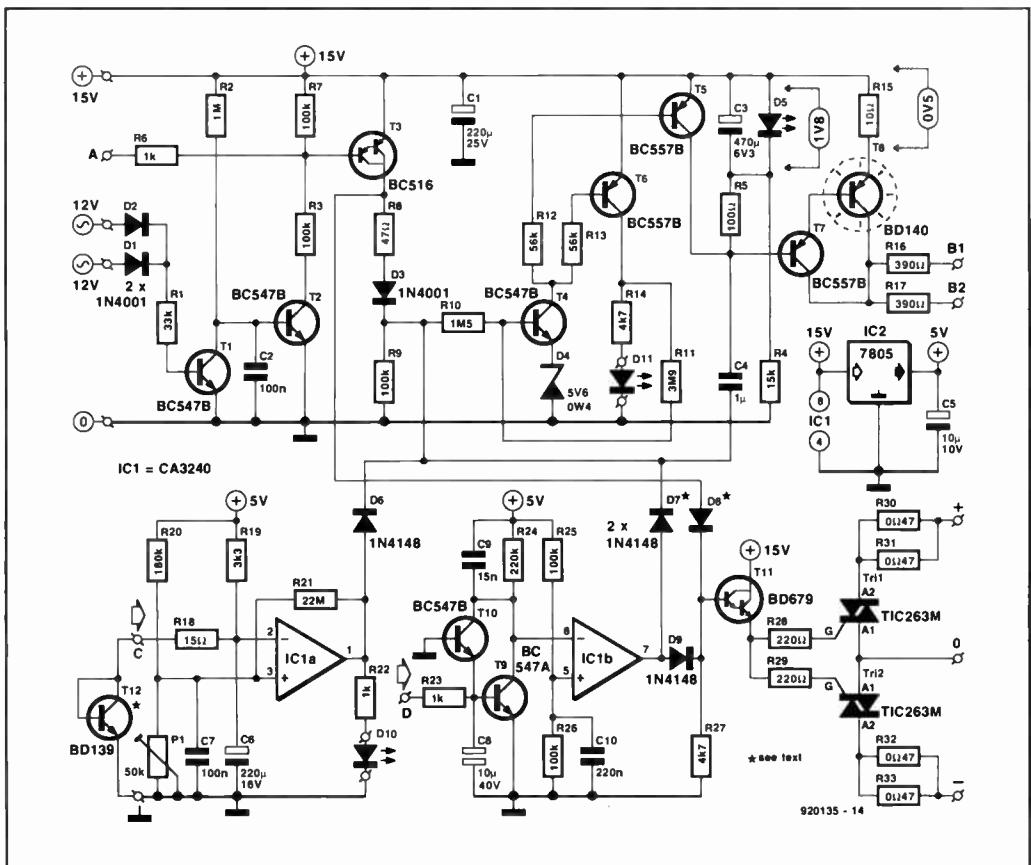


**Fig. 4.** Diagram of the protection circuit.

*The construction of the amplifier will be described in next month's instalment.*
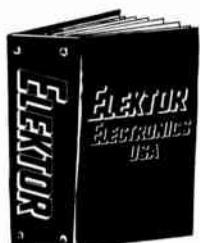
# ELEKTOR BINDERS

Keep your valuable copies in perfect condition in these Elektor Binders. Each binder holds 11 issues with wires so you don't have to punch holes in your magazines.

High quality, book binder cloth construction. The logo is stamped in gold on a dark green background.



**each \$12  
three or more, \$10 each**

**Shipping:** Postpaid in US.  
Canada and Caribbean, please add \$4 for one, \$2  
for each additional binder.  
Overseas, please add \$4 per binder.

**DR. "CHIP" MUNK SAYS**



**6805 / 68HC05 / 68HC11  
DEVELOPMENT TOOLS  
+  
QUALITY AND SERVICE  
+  
**AFFORDABILITY**  
=  
**TECI****

"Chip" experts agree with Dr. Munk. TECI'S PC based microcontroller development tools are the most cost effective for veterans or beginners. Call today for a free information package.

6805 PRIMER FOR BEGINNERS.....\$195.00  
6805 / 68HC05 / 68HC11 CROSS ASSEMBLERS...\$99.00  
6805 / 68HC05 SIMULATOR / DEBUGGER....\$99.00  
68705 P3,P5,U3,U5,R3,R5 PROGRAMMERS FROM \$349.00  
68HC705 / 68HC805 PROGRAMMERS FROM \$395.00  
COMPLETE PC BASED DEV. SYSTEMS FROM \$449.00  
68HC05 / 68HC11 REAL TIME EMULATORS FROM \$895.00

THE ENGINEERS COLLABORATIVE, INC.  
R3 BOX 8C BARTON, VT. 05822 USA  
**TECI**   
TEL: (802) 525-3458  
FAX: (802) 525-3451  
 TOLL FREE 1-800-336-8321

# DIFFERENTIAL THERMOMETER

Design by J. Ruiters

**Temperature is a physical property of a body that determines the direction of heat flow when the body is brought into contact with another. Heat always flows from a region of higher temperature to one of lower temperature. A standard thermometer measures the temperature of a body with respect to an arbitrary point—usually 0 °C (or, in the USA, 32 °F) which is the temperature at which pure water freezes, or 0 K, that is, absolute zero or -273.15 °C. It is, however, not always convenient to measure the temperature with respect to these arbitrary points; many measurements are required to indicate the difference in temperature between two regions or bodies. This may be done with a differential thermometer such as the one described here.**

Basically, the differential thermometer consists of two sensors that convert temperature into potential, a differential amplifier that magnifies the difference between the two sensor output voltages, a display which indicates that difference, and two switching outputs that may actuate a circuit or circuits if the difference exceeds a predetermined level.

## Differential amplifier

The simplest differential amplifier is one designed around one opamp and a number of resistors. This is often expanded by two buffer opamps to obtain a higher input impedance, resulting in the familiar three-opamp differential amplifier. However, the present design is based on a two-opamp differential amplifier—see Fig. 1.

The input signals are applied to the non-inverting (-) inputs of the opamps to ensure a high circuit input impedance. The potential at the inverting (+) input of the first opamp is  $U_{CM} - U_d/2$ , while that at the inverting input of the second opamp is  $U_{CM} + U_d/2$ , where  $U_{CM}$  is the common-mode voltage and  $U_d$  is the difference between the two sensor output voltages. The output voltage,  $U_o$ , is calculated

from:

$$U_o = \frac{R_4}{R_3} \left[ 1 + \frac{1}{2} \left( \frac{R_2 + R_3}{R_1 + R_4} \right) + \frac{R_2 + R_3}{R_0} \right] U_d + \frac{R_4}{R_3} \left( \frac{R_3}{R_4} - \frac{R_2}{R_1} \right) U_{CM}$$

From this it is evident that suppression of the common mode signal is an optimum if  $R_2/R_1 = R_3/R_4$ . Any deviations are amplified by a factor  $R_4/R_3$ . To obviate this,  $R_1$  may consist of a fixed and a variable resistor so that the common mode rejection can be set to maximum. However, if matters such as the dynamic range of the amplifier and the temperature coefficient of the resistors are taken into account, it is better to make resistors  $R_1 - R_4$  equal. The term  $R_4/R_3$  is then 1 and, since all resistors change equally with temperature, the balance between  $R_2/R_1$  and  $R_3/R_4$  is retained.

The amplification of the difference signal may be adjusted with the value of  $R_0$ . It is clear from the foregoing formula that  $R_0$  affects only the difference signal and not the common mode signal. This makes adjusting the am-

plication, if needed, simpler.

An incidental advantage of making the values of the resistors equal is that the formula for  $U_o$  simplifies to

$$U_o = 2(1 + R_n/R_0)U_d,$$

where  $R_n = R_1 = R_2 = R_3 = R_4$ .

A drawback of this type of differential amplifier, in contrast to the one-opamp and three-opamp types, is that the first opamp magnifies not only the signal, but also the common-mode voltage. Assuming that  $R_1 - R_4$  are equal, the common-mode signal in the output,  $U_1$ , of the first opamp is amplified by a factor of  $\times 2$ . The level of  $U_1$  is given by

$$U_1 = -(1 + R_n/R_0)U_d + 2U_{CM}.$$

The maximum drive to the second opamp must, of course, also be borne in mind. Suppose that the differential amplifier has an amplification of  $\times 10$  for a maximum differential voltage of  $\pm 1$  V. The ratio  $R_n/R_0$  is then 4 and the maximum output voltage is  $\pm 10$  V. Potential  $U_1$  is  $\pm 5V + 2U_{CM}$ . If the maximum output voltage is equal to the maximum drive level (that is, = supply voltage), the level of the common-mode voltage must not exceed  $\pm 2.5$  V to prevent the first opamp being overdriven.

## Supply/reference voltages

The power supply for the thermometer, shown in Fig. 2, is fairly unusual in that the reference voltage regulator is integrated in the display driver, although for clarity's sake it is shown separate.

The unregulated 8–15 V supply voltage is stabilized by the reference voltage source, which is preset with the aid of  $R_{18}$  and  $R_{19}$  to give an output of 6.3 V. Since the differential amplifier requires a symmetrical supply, an artificial 'earth' is concocted with the aid of opamp  $IC_{2a}$  and resistors  $R_{15} - R_{17}$ ,  $R_{20}$  and  $R_{21}$ . This does not, of course, result in a true


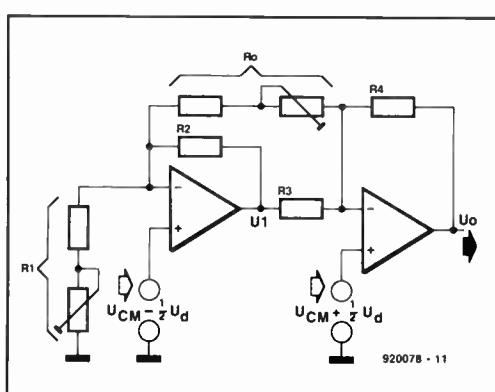


Fig. 1. Basic two-opamp differential amplifier.

## TECHNICAL PARAMETERS

Sensors	Silicon diodes (e.g., IN4148) with maximum junction temperature of 200 °C.
Switching outputs	Open-collector type (BC517: $I_c$ max. 400 mA; $T_j$ max 150 °C; $P_{tot}$ max 6.25 mW; $R_{th,j-a}$ 200 K/W)
Supply voltage	8–15 V, unregulated
Display	LED bar (10 LEDs)
Sensitivity	Preset (standard 0.25 °C per LED)

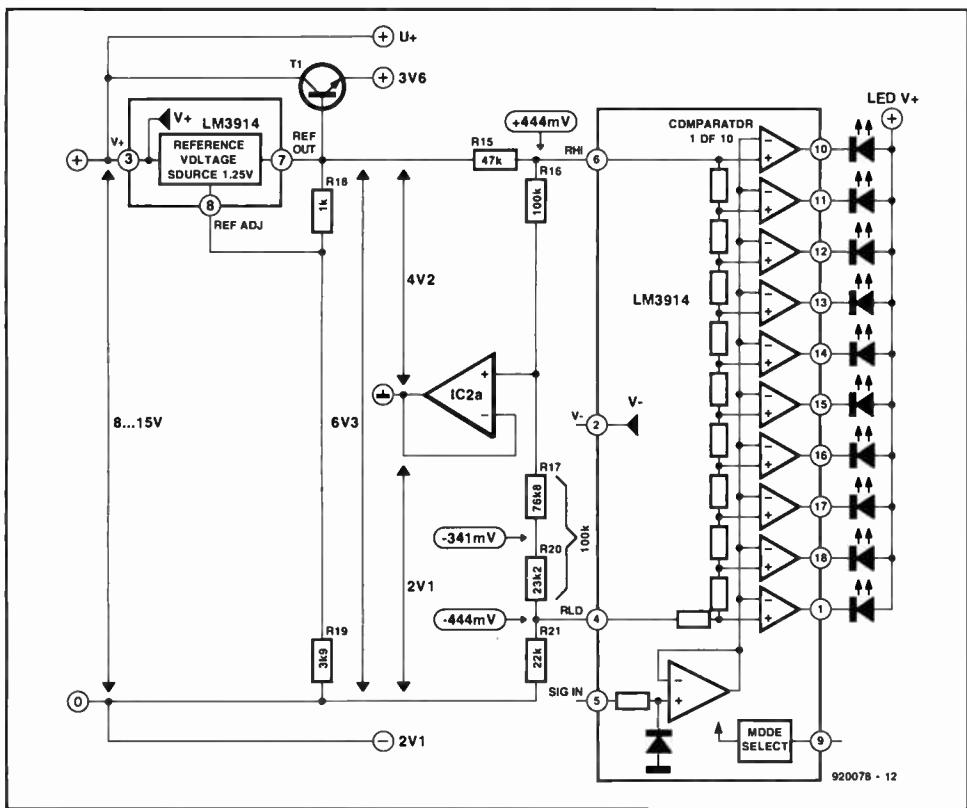

**Fig. 2.** The internal voltage regulator of the display driver is the source of all required supply voltages.

symmetrical supply: the 'earth' potential is 2.1 V above true earth and 4.2 V below the output level of the regulator. Raising the level of the positive voltage more than that of the negative voltage with respect to true earth increases the drive capability of the differential amplifier.

The supply voltage so created still cannot be used, however. This is because the output current of the regulator determines the current through the display LEDs. Since the current through each LED is about ten times as large as the output current of the regulator, the latter must not be too large and, moreover,


must not vary much. For this reason, the regulator action is 'enhanced' by transistor  $T_1$ . However, since the output voltage of the regulator is also used as reference for the display,  $T_1$  is not in the feedback circuit. The transistor, therefore, cannot influence the quality of the regulator. It means, however, that the positive supply voltage for the differential amplifier is 3.6 V instead of 4.2 V it is no longer so well regulated, but this is of no consequence here.

The reference voltage for the regulator is derived from potential divider  $R_{18}-R_{19}$ . To ensure that the display indicates the same magnitude irrespective of whether the temperature difference is positive or negative, the voltage across the resistive divider in the display driver (about 12 k $\Omega$ ) must be symmetrical with respect to earth. This is arranged by using 100 k $\Omega$  resistors,  $R_{16}$  and  $R_{17}-R_{20}$  respectively, between earth and reference inputs  $R_{HI}$  and  $R_{LO}$  of the display driver (note that the +input of  $IC_{2a}$  is at ground potential). The reason for using two resistors,  $R_{17}$  and  $R_{20}$  instead of a single 100 k $\Omega$  will be discussed later on.

## Circuit description

The temperature sensors in the prototype are Type 1N4148 diodes,  $D_1$  and  $D_2$  in Fig. 3. Silicon diodes are used because their threshold voltage has a temperature coefficient of about  $2 \text{ mV K}^{-1}$ . The diodes are connected in a bridge circuit that, when their temperature is the same, is balanced by  $P_1$ .

The signals from the sensors are applied to differential amplifiers  $IC_{3a}$  and  $IC_{3b}$  via low-pass filters  $R_3-C_1$  and  $R_{11}-C_6$  respectively.

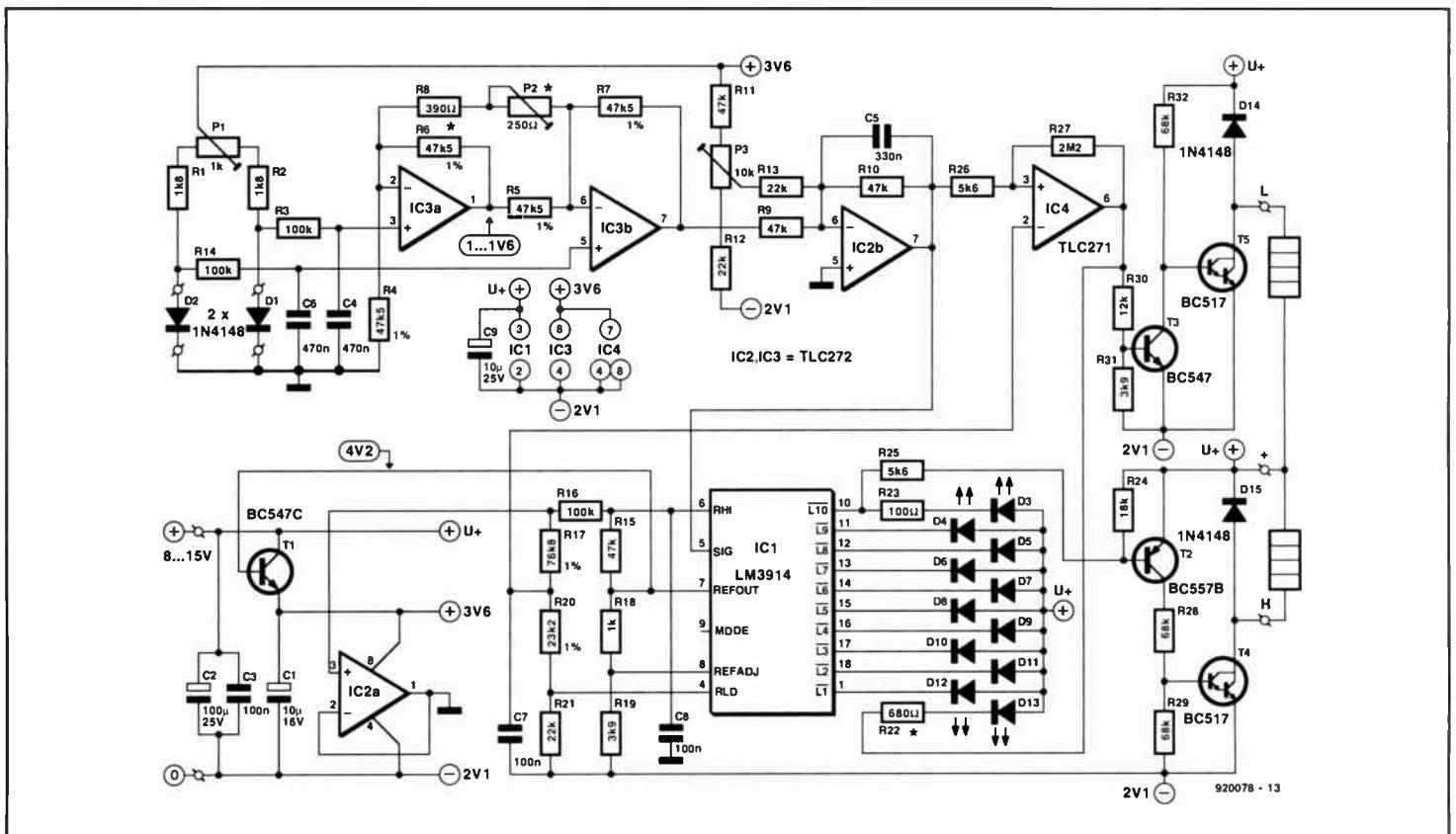

**Fig. 3.** Circuit diagram of the differential thermometer.

The output of the amplifier is fed to IC<sub>2b</sub> which, with the aid of P<sub>3</sub>, corrects the offset of the amplifier. The signal at the output of IC<sub>2b</sub> is then suitable as input for display driver IC<sub>1</sub>.

The driver has two switching outputs, of which one operates when the positive peak is reached, and the other when the negative maximum is about to be exceeded.


In the case of positive levels, as soon as D<sub>3</sub> has been switched on by the driver, T<sub>2</sub> will also be on. This transistor in turn switches on T<sub>4</sub>, resulting in the load (relay) being switched on. In the case of negative levels, the input voltage to IC<sub>1</sub> is compared with the potential at junction R<sub>17</sub>-R<sub>20</sub> at which D<sub>12</sub> just goes out. When the measured temperature is sufficiently negative, the output of IC<sub>4</sub> goes low, whereupon D<sub>13</sub> lights, T<sub>3</sub> is switched off, and T<sub>5</sub> is switched on, so that the associated load (relay) is switched on.

The relays are shunted by free-wheeling diodes D<sub>14</sub> and D<sub>15</sub>. If relays are not required, terminals L and H may be interlinked to form a wired-OR connection.

The circuit without relays draws a current of about 30 mA from an 8–15 V supply; when either of the relays is switched on, the current increases to well over 400 mA. If the thermometer is not used constantly, a 9 V PP3 battery may be used as supply.
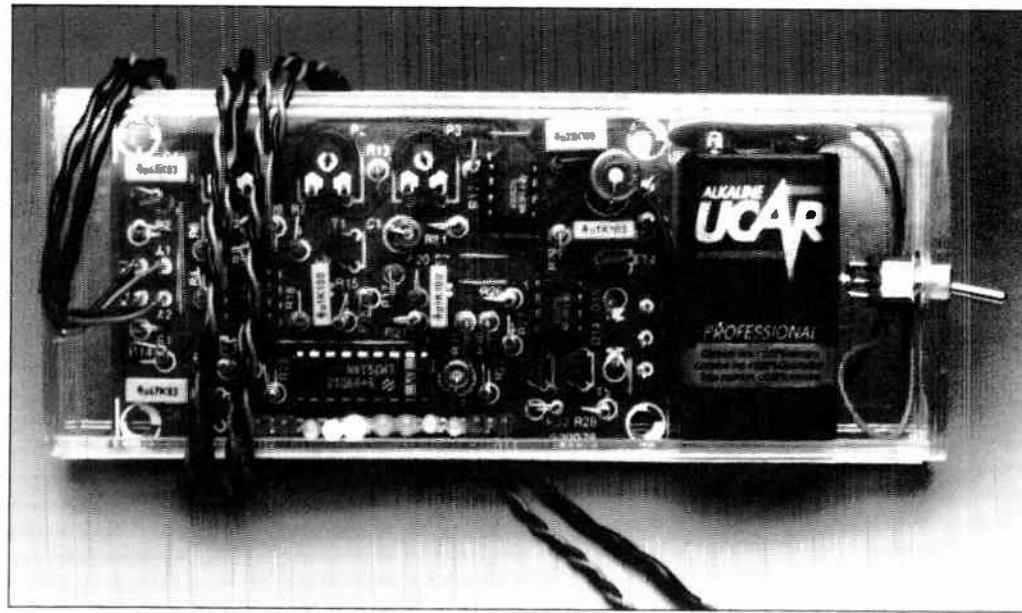
## Construction and calibration

The thermometer is best constructed on the printed-circuit board shown in Fig. 4. Sensors D<sub>1</sub> and D<sub>2</sub> may be linked to it via a cable up to 1 m (3 ft) long. The diodes may be replaced by transistors, for instance, Types BC107 and BC547, whose base and collector are linked together: the base-emitter diode serves as the sensor.



The brightness of D<sub>13</sub> may be somewhat less than that of the other LEDs; this may be rectified by varying the value of R<sub>22</sub> by trial and error.

Before the circuit can be calibrated, both sensors must be at the same temperature and all potentiometers set to the centre of their travel.

Connect a high-impedance voltmeter between the anodes of D<sub>1</sub> and D<sub>2</sub>, and adjust P<sub>1</sub> for zero reading (no LED lights). Next, adjust P<sub>3</sub> until the centre LED (D<sub>8</sub>) just lights. The magnification of the differential amplifier is then  $\times 185$  (gain=45 dB). Assuming a temperature coefficient of  $2 \text{ mV } ^\circ\text{C}^{-1}$  and an input sensitivity of the display of  $88.8 \text{ mV}$  per LED, the overall sensitivity is about  $0.25 \text{ } ^\circ\text{C}$  per LED ( $88.8/2 \times 185$ ).

If greater precision or a different scale is required, the two sensors should be kept at the

desired temperature difference and P<sub>2</sub> adjusted until D<sub>13</sub> just lights. Another method is to multiply the maximum temperature difference by 2 and take the result as a voltage in mV. With a voltmeter between the anodes of D<sub>1</sub> and D<sub>2</sub>, adjust P<sub>1</sub> until the meter indicates that voltage. Next, adjust P<sub>2</sub> until D<sub>13</sub> just lights and readjust P<sub>1</sub> for zero reading of the meter. ■

## PARTS LIST

### Resistors:

- R<sub>1</sub>, R<sub>2</sub> = 1.8 kΩ
- R<sub>3</sub>, R<sub>14</sub>, R<sub>16</sub> = 100 kΩ
- R<sub>4</sub>-R<sub>7</sub> = 47.5 kΩ
- R<sub>8</sub> = 390 Ω
- R<sub>9</sub>-R<sub>11</sub>, R<sub>15</sub> = 47 kΩ
- R<sub>12</sub>, R<sub>13</sub>, R<sub>21</sub> = 22 kΩ
- R<sub>17</sub> = 76.8 kΩ
- R<sub>18</sub> = 1 kΩ
- R<sub>19</sub>, R<sub>31</sub> = 3.9 kΩ
- R<sub>20</sub> = 23.2 kΩ
- R<sub>22</sub> = 680 Ω
- R<sub>23</sub> = 100 Ω
- R<sub>24</sub> = 18 kΩ
- R<sub>25</sub>, R<sub>26</sub> = 5.6 kΩ
- R<sub>27</sub> = 2.2 MΩ
- R<sub>28</sub>, R<sub>29</sub>, R<sub>32</sub> = 68 kΩ
- R<sub>30</sub> = 12 kΩ
- P<sub>1</sub> = 1 kΩ preset, horizontal
- P<sub>2</sub> = 250 Ω preset, horizontal
- P<sub>3</sub> = 10 kΩ preset, horizontal

### Capacitors:

- C<sub>1</sub> = 10 μF, 16 V, radial
- C<sub>2</sub> = 100 μF, 16 V, radial
- C<sub>3</sub>, C<sub>7</sub>, C<sub>8</sub> = 100 nF
- C<sub>4</sub>, C<sub>6</sub> = 470 nF
- C<sub>5</sub> = 330 nF
- C<sub>9</sub> = 10 μF, 25 V, radial

### Semiconductors:

- D<sub>1</sub>, D<sub>2</sub>, D<sub>14</sub>, D<sub>15</sub> = 1N4148
- D<sub>3</sub>, D<sub>4</sub>, D<sub>12</sub>, D<sub>13</sub> = LED, 3 mm, red
- D<sub>5</sub>, D<sub>6</sub>, D<sub>10</sub>, D<sub>11</sub> = LED, 3 mm, yellow
- D<sub>7</sub>-D<sub>9</sub> = LED, 3 mm, green
- T<sub>1</sub>, T<sub>3</sub> = BC547C
- T<sub>2</sub> = BC557B
- T<sub>4</sub>, T<sub>5</sub> = BC517
- IC<sub>1</sub> = LM3914
- IC<sub>2</sub>, IC<sub>3</sub> = TLC272
- IC<sub>4</sub> = TLC271

### Miscellaneous:

- Enclosure 57×142×23.5 mm (2 $\frac{1}{4}$ ×5 $\frac{9}{16}$ × $\frac{15}{16}$  in)
- PCB Type 920078 (see page 70)


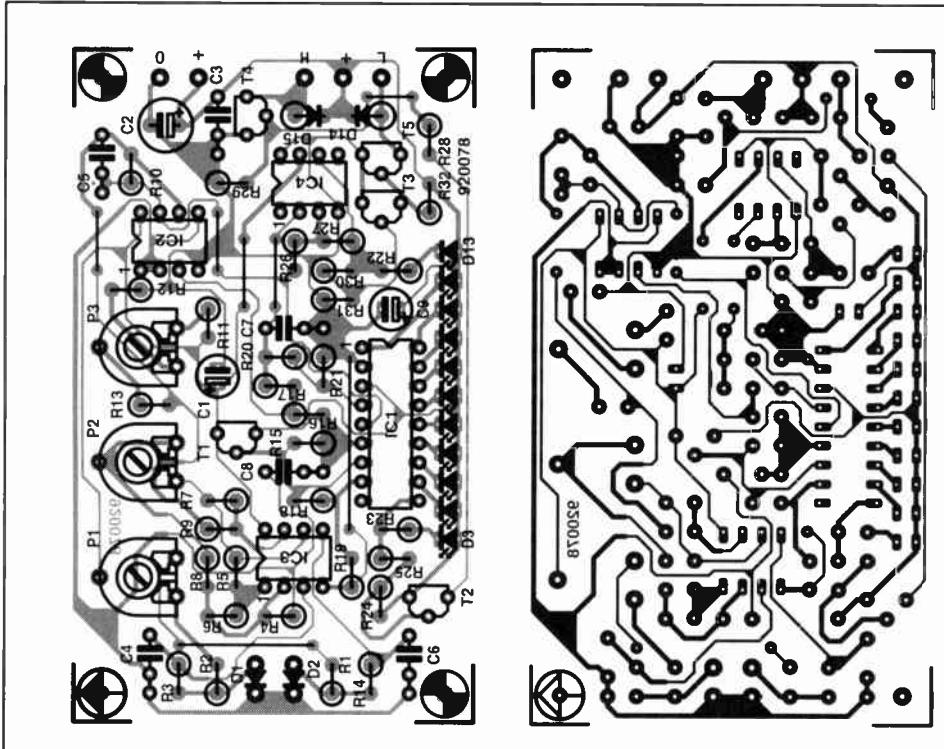


Fig. 4. Printed circuit board for the differential thermometer.
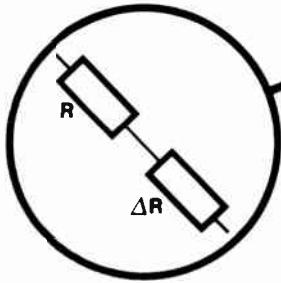
# THE WHEATSTONE BRIDGE

Any time a device produces a resistance (or resistance change) as the transducible property for a measurement, we can use the Wheatstone bridge to make the measurement easier. The bridge is probably the most common form of resistive sensor circuit.



By Joseph J. Carr

MANY sensors used in electronic instruments use electrical resistance as the transducible property. For example, a thermistor produces a resistance that is a function of the applied temperature. Strain gauges are wire or semiconductor elements that change resistance when deformed in either tension or compression; this phenomenon is called piezoresistivity, and forms the basis for a wide range of pressure sensors and other instruments. Photoresistors produce a resistance that is inversely proportional to the applied light level. All these resistive sensors can be accurately measured with the aid of the Wheatstone bridge.

## Bridge circuits

Before any resistive sensor can be useful, it must be connected into a circuit that will convert its resistance changes into a current or voltage output; most applications are voltage output circuits. Figure 1 shows several popular forms of circuit. The circuit in Fig. 1a is both the simplest and least useful (although not useless); it is sometimes called the 'half-bridge' circuit, or 'voltage divider' circuit. The sensor element of resistance  $R$  is placed in series with a fixed resistor,  $R_1$ , across a stable d.c. voltage,  $U_e$ . The output voltage,  $U_o$ , is found from the standard voltage divider equation:

$$U_o = \frac{U_e R}{R + R_1} \quad (1)$$

Equation (1) describes the output voltage  $U_o$  when the sensor is at rest (i.e., nothing

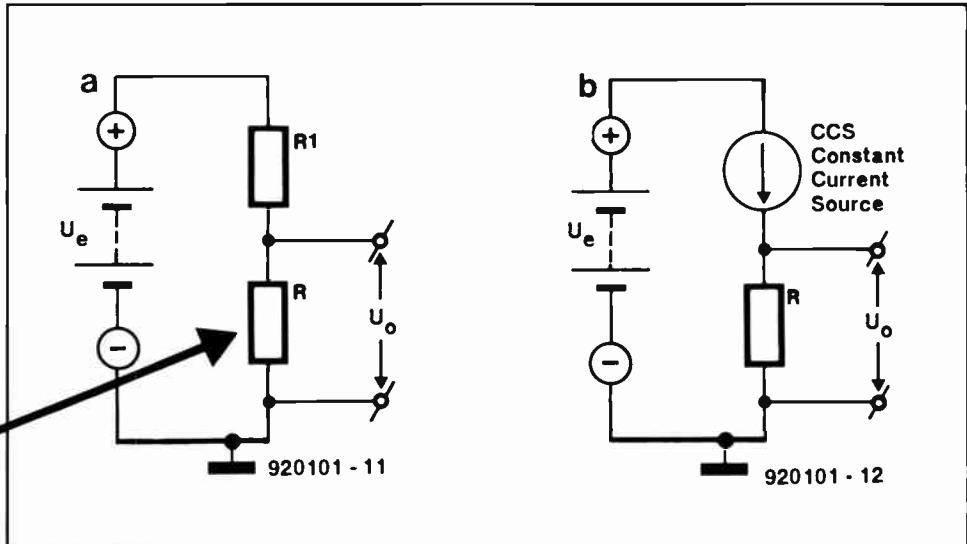


Fig. 1. (a) Basic half-bridge circuit; (b) half-bridge circuit based on a constant current source (CCS).

is stimulating the resistive element). When the element is stimulated, however, its resistance changes a small amount,  $\Delta R$ . The output voltage in that case is:

$$U_o = \frac{U_e (R \pm \Delta R)}{(R \pm \Delta R) + R_1} \quad (2)$$

Another form of half-bridge circuit is shown in Fig. 1b, but in this case the sensor element is connected in series with a constant current source (CCS), which will maintain current  $I$  at a constant level regardless of changes in the strain gauge resistance. In this case,  $U_o = I(R \pm \Delta R)$ . The LM334 device is an example of a commercial CCS.

Both of the half-bridge circuits suffer from a serious defect: output voltage  $U_o$  will always be present regardless of the value of the force applied to the sensor. Ideally in any sensor system, the output voltage should be zero when the applied stimulus is zero. For example, when a gas pressure sensor is open to atmosphere, the gauge pressure is zero so the output voltage should also be zero. Secondly, the output voltage should be proportional to the value of the stimulus when the stimulus is not zero. A Wheatstone bridge circuit has these properties. We can use resistive sensors for all of the elements of the Wheatstone bridge, or just one.

Figure 2a shows the basic circuit for the Wheatstone bridge: the circuits to follow are but variations on this theme. The bridge consists of four resistive arms ( $R_1$  through  $R_4$ ), and an *excitation voltage* source,  $U_e$ . As can be seen in the redrawn circuit of Fig. 2b, the Wheatstone bridge is basically two resistor voltage dividers in parallel with each other. Voltage divider  $R_1/R_2$  produces an output voltage  $U_1$ :

$$U_1 = \frac{U_e R_2}{R_1 + R_2}, \quad (3)$$

while voltage divider  $R_3/R_4$  produces voltage  $U_2$ :

$$U_2 = \frac{U_e R_4}{R_3 + R_4}. \quad (4)$$

Each of these voltages is single-ended, i.e., it is unbalanced with respect to common or ground. Output voltage  $U_o$  is balanced with respect to common, and is the difference between each half-bridge voltage:

$$U_o = U_1 - U_2 = U_e \left( \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right). \quad (5)$$

When  $U_1 = U_2$ , and  $U_o = 0$ , the bridge is balanced, and is said to be in the *null condition*. This state occurs when:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}. \quad (6)$$

Please note that the resistances need not be equal, only the *ratio* of the resistances in the two arms need be equal to establish the null condition.

One also might notice that knowledge of three resistance values (say,  $R_1$ ,  $R_2$  and  $R_3$ ) implies knowledge of the fourth by calculation when the null condition is present. It is common practice to use fixed precision resistors for two elements (e.g.,  $R_1$  and  $R_3$ ), and a calibrated variable resistor for the third resistor (e.g.,  $R_2$ ), and then an unknown for the fourth-resistance branch. Such a system for measuring unknown resistances is shown in Fig. 2c.

If  $R_2$  is adjusted for  $U_o = 0$ , with unknown  $R_x$  connected in place of  $R_4$ , the value of  $R_x$  is inferred from:

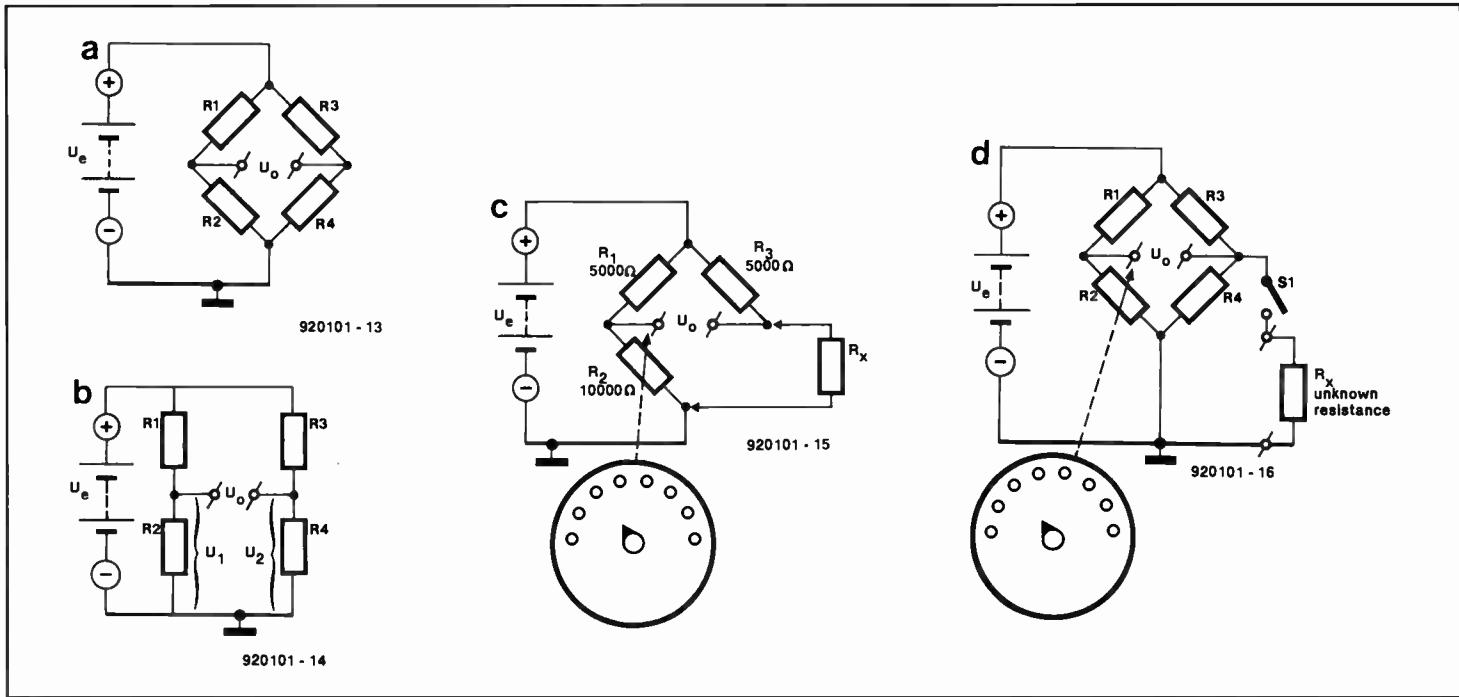


Fig. 2. (a) Standard Wheatstone bridge circuit; (b) circuit redrawn to show the two voltage dividers more clearly; (c) circuit for using a Wheatstone bridge to measure an unknown resistance; (d) alternate circuit for measuring unknown resistances.

$$R_x = \frac{R_2 R_3}{R_1} \quad (7)$$

or, where  $R_1 = R_3$  (not a necessary condition, but certainly convenient),  $R_x = R_2$ .

Another operating condition is shown in Fig. 2d. This method uses a *departure from null* to indicate  $R_x$ . With switch  $S_1$  open, resistor  $R_2$  is adjusted to null (i.e.,  $U_o = 0$ ). Switch  $S_1$  is then closed, causing  $R_x$  to shunt  $R_4$  to produce a new (lower) resistance for this arm of the bridge, and forcing  $U_o \neq 0$ . The value of  $U_o$  is an indication of unknown  $R_x$ .

Alternatively, switch  $S_1$  can be an SPDT type that replaces  $R_4$  with  $R_x$ , rather than simply shunting ( $R_4 \parallel R_x$ ). This 'departure from null' is the basis for many sensor based instruments.

Figure 3a shows a Wheatstone bridge circuit in which two resistive sensors (SG1 and SG2) are used in two arms of the bridge, with fixed resistors  $R_1$  and  $R_2$  forming the alternate arms of the bridge.

It is usually the case that SG1 and SG2 are configured so that their actions oppose each other; that is, under stimulus, SG1 will have resistance  $R+\Delta R$ , and SG2 will have resistance  $R-\Delta R$ , or vice versa.

One of the most linear forms of sensor bridge is the circuit of Fig. 3b in which all four bridge arms contain resistive elements. In most such sensors, all four strain gauge elements have the same resistance ( $R$ ), which will usually be a value between  $50\Omega$  and  $1000\Omega$ .

The output from a Wheatstone bridge is the difference between the voltages across the two half-bridges. We can calculate the output voltage for any of the standard configurations from the equations given below (assuming all four bridges have nominally the same resistance,  $R$ ).

One active element:

$$U_o = \frac{U_e \Delta R}{4R} \quad (8)$$

(accurate to  $\pm 5\%$  if  $h < 0.1$ )

Two active elements:

$$U_o = \frac{U_e \Delta R}{2R} \quad (9)$$

Four active elements:

$$U_o = \frac{U_e \Delta R}{R} \quad (10)$$

Where:

$U_o$  is the output potential in volts (V);  
 $U_e$  is the excitation potential in volts (V);  
 $R$  is the resistance of all bridge arms;  
 $\Delta R$  is the change in resistance in response to the applied stimulus.

## Sensor sensitivity

The sensitivity factor ( $\Phi$ ) of a Wheatstone bridge sensor circuit relates the output voltage ( $U_o$ ) to the applied stimulus value ( $Q$ ) and excitation voltage. In most cases, the sensor maker will specify a number of microvolts (or millivolts) *output potential per volt of excitation potential per unit of applied stimulus*:

$$\Phi = U_o / U_e / Q_0 \quad (11)$$

or, written another way:

$$\Phi = \frac{U_o}{U_e Q_0} \quad (12)$$

Where:

$\Phi$  is the sensor sensitivity ( $\mu\text{V}/U_e/Q$ );  
 $U_o$  is the output potential (V);  
 $U_e$  is the excitation potential (V);  
 $Q$  is one unit of applied stimulus.

If we know the sensitivity factor, we can calculate the output potential as follows:

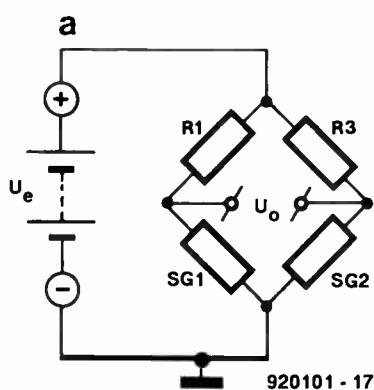


Fig. 3. (a) Two-sensor bridge circuit; (b) four-sensor bridge circuit.

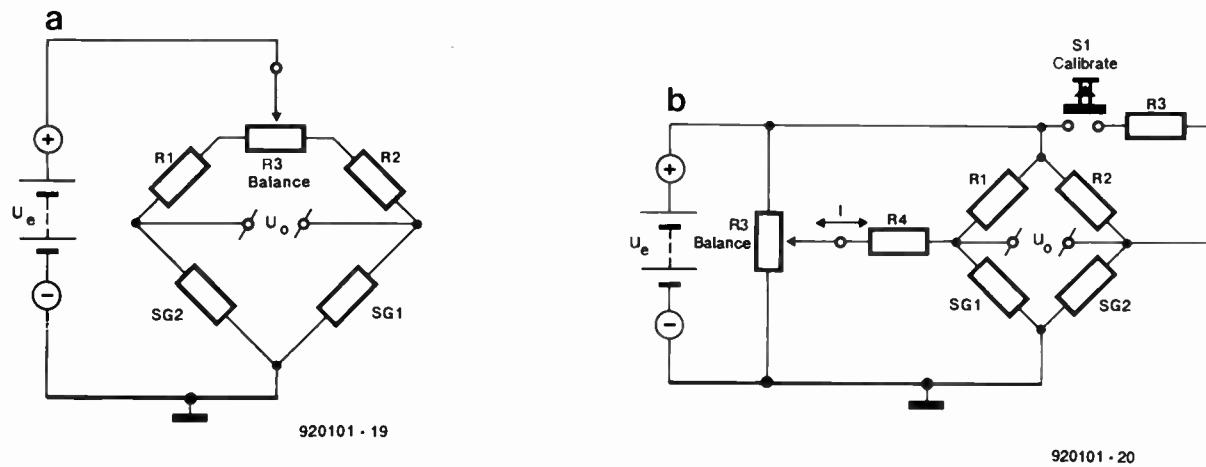


Fig. 4. (a) Bridge balance potentiometer ( $R_3$ ) to compensate for circuit tolerances; (b) injection current method for balancing the bridge.

$$U_o = \Phi U_e Q_0 \quad (13)$$

Equation (13) is the one that is most often used in circuit design.

#### Example

A certain fluid pressure sensor has a sensitivity ( $P$ ) of  $5 \mu\text{V}/U_e/T$ , which means that 5 microvolts output potential is generated per volt of excitation potential per Torr of pressure<sup>1</sup>. Find the output potential when the excitation potential ( $U_e$ ) is +7.5 V, and the applied pressure is 400 Torr.

$$U_o = \Phi U_e Q$$

$$U_o = \left( \frac{5 \mu\text{V}}{U_e T} \right) \times 7.5 \text{ V} \times 400 \text{ Torr}$$

$$U_o = (5 \times 7.5 \times 400) \mu\text{V} = 15,000 \mu\text{V}$$

(which is 0.015 V, or 15 mV).

### Balancing and calibrating a bridge sensor

Few, if any, Wheatstone bridge sensors meet the ideal condition in which all four bridge arms have exactly equal resistances at rest. In fact, the bridge resistance specified by the manufacturer is only a nominal value, and the actual value may vary quite a bit from the specified value. There will inevitably be an offset voltage (i.e.,  $U_o$  is not zero when  $Q$  is zero). Figure 4 shows two circuits that will balance the bridge when the stimulus is zero.

In Fig. 4a the balancing potentiometer is placed between the excitation potential and one of the excitation nodes. The resistance balance of the potentiometer is varied between the two legs of the bridge, nullifying any differences between them. The potentiometer is usually a precision type with five to fifteen turns to cover the entire range.

The purpose of the potentiometer in

Fig. 4b is to inject a balancing current ( $I$ ) into the bridge circuit at one of its nodes.  $R_1$  is adjusted, with the stimulus at zero, for zero output voltage.

Another application for this type of circuit is injecting an intentional offset potential. For example, on an electronic scale, one that uses a strain gauge to measure weight, such a circuit is used to adjust for the 'tare weight' of the scale, which is the sum of the platform and all other weights acting on the sensor when nobody is standing on the scale. This is also sometimes called 'empty weight compensation'.

### Calibration of a bridge sensor

Calibration can be accomplished either the hard way, or the easy (and less accurate) way. The hard way is to set the sensor up in a system and apply the stimulus. The stimulus is measured and the result is compared with the sensor output. For ex-

ample, if you are testing a pressure sensor, connect a manometer (pressure measuring device containing a column of mercury), pressurize the system, and then measure the pressure directly. The result is compared with the sensor output. Similarly, temperature sensors can be exposed to a known temperature, and the bridge output noted. All sensors should be tested in this manner initially when placed in service and then periodically thereafter.

The easy (and less accurate) way is to connect a calibrating resistor in parallel with one leg of the bridge ( $R_3$  in Fig. 4b) to create an offset that is equal to some standard stimulus. A 'CAL' switch ( $S_1$ ) will insert the resistor in the circuit, unbalancing the bridge an amount  $R$ , whenever a quick calibration or test is needed.

### Output display devices

The output of the Wheatstone bridge is a differential voltage,  $U_o$ , that is proportional to the unbalance of the bridge. This

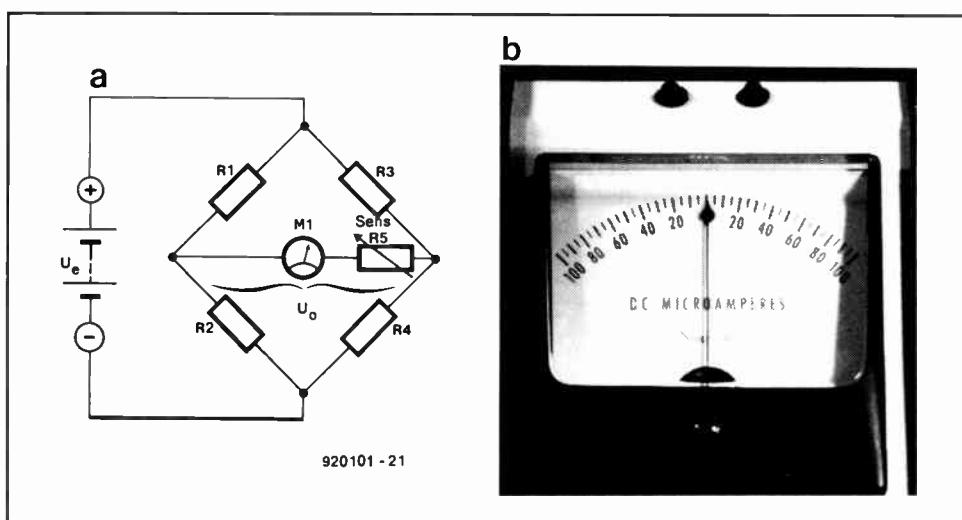


Fig. 5. (a) Analog current meter movement used as a bridge circuit display device; (b) zero-center meter suitable for use in a bridge circuit such as Fig. 5a.

<sup>1</sup> torr. A unit of pressure used in vacuum technology. One Torr equals  $\frac{1}{760}$  standard atmosphere pressure (very closely, 1 mm Hg or 133.322 newtons per square metre).

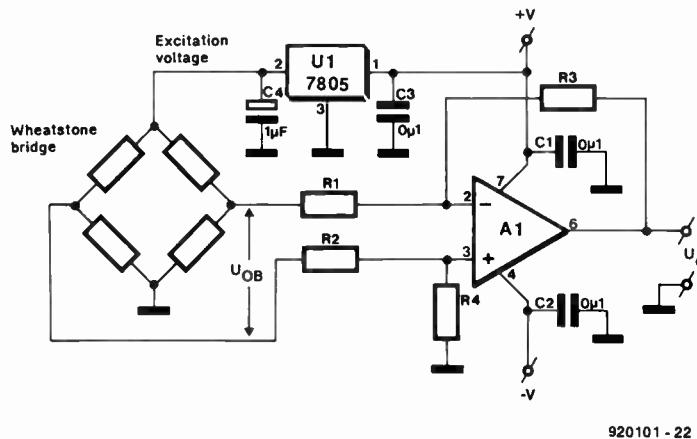


Fig. 6. DC differential bridge amplifier circuit.

voltage can be either positive or negative, depending on the direction of unbalance. In many cases, the output of the bridge will be displayed on an analogue or digital voltmeter, an oscilloscope or a strip-chart recorder.

It is also possible to use a current meter for the output display, as shown in Fig. 5a. The meter, M1, is connected between the output nodes across which  $U_o$  appears. This meter is usually a milliammeter or microammeter (Fig. 5b), depending on the best sensitivity required.

It is not strictly necessary to insert the sensitivity control ( $R_5$ ) in series with the meter, but it is highly recommended if the unbalance is large and the meter has a low current range. Large displacements of the bridge could generate sufficient current to damage the meter. It is common practice to initially set  $R_5$  to maximum, or near maximum, resistance, and then reduce its resistance as the bridge nears the null condition. A few commercial resistance measuring bridges place a switch in shunt with  $R_5$  in order to remove it from the circuit when the bridge is close to null.

### Bridge amplifier circuit

The output potential of most bridges ( $U_{ob}$  in Fig. 6a) is a very small voltage that, for many applications, must be amplified for practical use. The Wheatstone bridge is a balanced device, so a differential amplifier is needed to amplify  $U_o$ . The amplifier circuit uses an operational amplifier (A1) in the d.c. differential amplifier configuration. In this type of circuit,  $R_1 = R_2$  and  $R_3 = R_4$ , in order to maintain balance, and the voltage gain is:

$$A_v = \frac{R_3}{R_1} \quad (14)$$

The input resistors,  $R_1$  and  $R_2$ , should be at least ten times the source resistance of

the bridge. If all arms of the bridge are equal, then the source resistance is the value of any one arm of the bridge.

The excitation voltage in Fig. 6a is supplied by an IC voltage regulator. Separate regulation is needed because variations in the power supply voltage are transmitted to the bridge, and reflected as changes in the output voltage. In the case shown, the voltage for the bridge is +5 V, so a 7805 regulator is used. In general, the excitation voltage for typical bridges is low in order to prevent self-heating of the sensors, so a 7805 is a reasonable general selection.

In many cases, the output of the bridge

is so small that it is difficult to transmit for any length in a wire or cable. In those cases, it is sometimes prudent to install a preamplifier on the body of the sensor. I constructed such a preamp for the user of a Grass Type FT-3 gram-force transducer, which is based on the Wheatstone bridge circuit that uses strain gauge elements as the arms. The output signal tends to be 100  $\mu$ V, or so, at full scale. In order to overcome interfering hum from the 60 Hz power mains, I built a gain-of-100 d.c. differential amplifier (making the output voltage 10 mV rather than 100  $\mu$ V) inside a small metal box that interfaced with the mating connector.

### Applications of bridges: circuits that you can build

The Wheatstone bridge can be used in a wide variety of applications circuits, only a few of which can be covered here. The purpose of the circuits below is to stimulate thinking into these and other applications for which the same principles hold.

#### Differential Thermometer

A differential thermometer produces an output voltage that is proportional to the difference between two temperatures. Uses for such thermometers include investigations of thermal insulation effectiveness; control of heating/cooling equipment based on temperature differences; simple curiosity as you gaze through an iced window pane; and so forth. Figure 7 shows the circuit for such a thermometer based on thermistor sensors.

The thermistor is a device that produces a resistance value that is a function


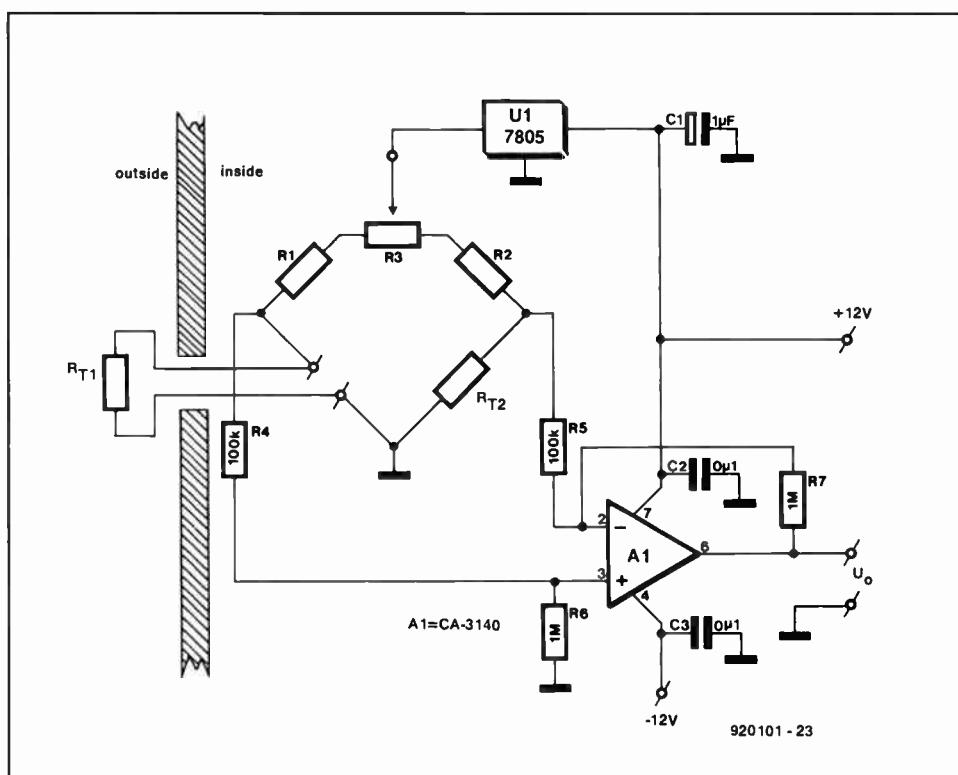


Fig. 7. Differential thermometer circuit.

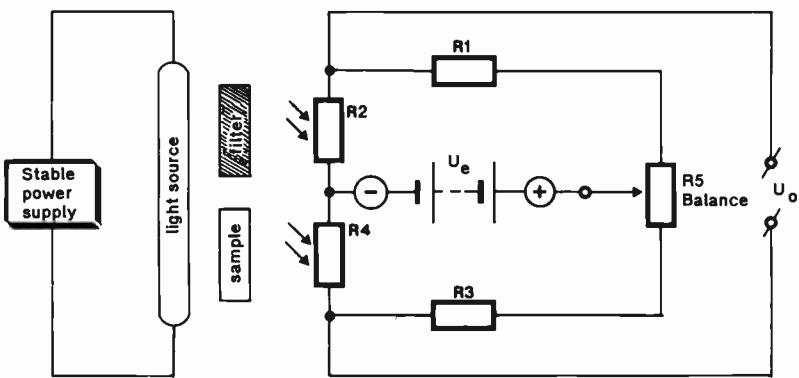

920101 - 24

Fig. 8. Photocolorimeter circuit.

of temperature. Devices RT<sub>1</sub> and RT<sub>2</sub> in Fig. 7 are identical thermistors, and are used in two opposing arms of a Wheatstone bridge circuit. Resistors R<sub>1</sub> and R<sub>2</sub> form the other two arms of the bridge. The values for R<sub>1</sub> and R<sub>2</sub> are not given because the convenient values depend on the specific thermistors being used. A rule-of-thumb is to make R<sub>1</sub> and R<sub>2</sub> equal to each other, with a value approximately the value of RT<sub>1</sub> and RT<sub>2</sub> at a mid-range temperature. Balancing potentiometer R<sub>3</sub> should have a value of 10 to 20 percent of the value of R<sub>1</sub> and R<sub>2</sub>.

As in the previous case, the bridge excitation source is a 7805 IC voltage regulator, which produces a regulated +5 V from the +12 V power supply.

The input resistors to A<sub>1</sub>, the differential amplifier, should be at least ten times the 'looking back' resistance of the bridge. Examination of thermistor catalogues reveals that 10 kΩ at 30 °C is a common value, so I set these resistors at ten times that value, or 100 kΩ. The gain of ten was set for convenience, and requires 1 MΩ resistors for R<sub>6</sub> and R<sub>7</sub>. Depending on the thermistors used, and the output voltage required, it may be necessary to increase the gain of the amplifier (remember, R<sub>1</sub> = R<sub>2</sub>, R<sub>6</sub> = R<sub>7</sub>, and A<sub>v</sub> = R<sub>7</sub>/R<sub>5</sub> = R<sub>6</sub>/R<sub>4</sub>).

### Photocolorimetry

One of the most basic forms of instrument circuit is also both the oldest and most commonly used: *photocolorimeters*. These devices are used for such applications as measuring the oxygen content in blood, CO<sub>2</sub> content of air, water vapour content in a gas, blood electrolyte (Na and K) levels, and a host of other similar measurements.

Photocolorimetry is basically a comparison measurement technique in which light (or IR and UV depending on the purpose of the instrument) transmission over two paths is compared. Figure 8 shows the

basic circuit of the most elementary form of colorimeter. Although the circuit is very basic, this is the actual circuit used in a once widely-used medical blood oxygen meter.

The basic circuit is the Wheatstone bridge, and it uses a pair of photoresistor cells (R<sub>2</sub> and R<sub>4</sub>) as the light sensors. Potentiometer R<sub>5</sub> in Fig. 8 is used as a bridge balance control, and it is adjusted for zero output ( $U_o = 0$ ) when the same light shines on both photoresistors. The output voltage from the bridge ( $U_o$ ) will be zero when the two legs of the bridge are balanced. In other words,  $U_o$  is zero when  $R_1/R_2 = R_3/R_4$ . It is not necessary for the resistor elements to be equal (although that is often the case), only that their resistance ratios be equal. Thus, a 500 kΩ/50 kΩ ratio for R<sub>1</sub>/R<sub>2</sub> will produce zero output voltage when R<sub>3</sub>/R<sub>4</sub> = 100 kΩ/10 kΩ.

The photoresistors are arranged such that light from a calibrated source illuminates both equally and fully, except when an intervening filter or sample is present in one or both pathways. Thus, the bridge can be nulled to zero using potentiometer R<sub>5</sub> under this zero condition. In most instruments that are based on this principle, a translucent sample is placed between the light source and one of the photocells. The amount of transmission to light allowed by the sample is a measure of its optical density, and is thus a transducible property. Let us look at a couple of different types of instrument to see how this principle is applied.

(1). Blood O<sub>2</sub> Level. A once widely used method for measuring blood oxygen level is based on the basic colorimeter of Fig. 8. It works because the 'redness' of human blood is a measure of its oxygenation. This instrument is nulled with neither standard filter cell nor blood in the light path; i.e., when white or red light shines on both cells. A standard colour 800 nanometer<sup>2</sup> filter is introduced be-

tween the light source and R<sub>2</sub>, and a blood sample is placed in a standardized tube between the light source and R<sub>4</sub>. The degree of blood O<sub>2</sub> saturation in the sample is thus reflected by the difference in the bridge reading between the sample path and filter path. On one model oxygen meter, a separate resistor across the R<sub>1</sub>/R<sub>2</sub> arm is used to bring the bridge back into null condition, and the dial for that resistor is calibrated in percent-O<sub>2</sub>. More modern instruments based on digital computer techniques provide the measurement in a more automatic manner.

(2). Respiratory CO<sub>2</sub> Level. The exhaled air from humans is roughly 2 to 5 percent carbon dioxide (CO<sub>2</sub>), while the percentage of CO<sub>2</sub> in normal room air is negligible. A popular form of 'End Tidal CO<sub>2</sub> Meter' is based on the fact that CO<sub>2</sub> absorbs infrared (IR) waves at three discrete wavelengths. The 'light source' in that type of photocolorimeter is actually either an IR LED or a Cal-Rod device (identical to the one that heats an electric coffee pot!); the photocells are selected for good IR response. In this type of instrument, room air is passed through a glass cuvette placed between R<sub>2</sub> and the heat source, while patient expiratory air is passed through the same type of cuvette placed between the heat source and R<sub>4</sub>. The difference in IR transmission across the two paths is a function of the percentage of CO<sub>2</sub> in the sample circuit.

The associated electronics (not shown) will allow zero and maximum span (i.e., gain) adjustment. The zero point is adjusted with room air in both cuvettes, while the maximum scale (usually 5% CO<sub>2</sub>) is adjusted with the sample cuvette purged of room air and replaced with a calibration gas (usually 5% CO<sub>2</sub>, 95% nitrogen). This calibration gas must be obtained from a local supplier, and be specified as a calibration gas. Otherwise, the quantities may be only approximate. Also, be sure of the type of measurement: calibration gases are available by either weight or volume.

The uses of colorimeters do not end with the medical laboratory. The clue to looking for a transducible event is detection of either a density change, or an absorption differential to one or two wavelengths, that is a transducible function of the parameter being measured; for example, IR is absorbed by CO<sub>2</sub>, and a certain O<sub>2</sub> saturation level passes light at 800 nm wavelength.

### Conclusion

The Wheatstone bridge is simple to understand, simple to build, well behaved, and can form the basis for a very large variety of simple physical instruments that you can build.

<sup>2</sup> 800 nm is the *isobestic* point wavelength at which oxygenated arterial blood and deoxygenated venous blood have the same transmittivity.

# DIGITAL AUDIO-VISUAL SYSTEM

## PART 1 (OF 4): SYSTEM OUTLINE AND DISSOLVE UNIT



This is the first instalment of an article that describes a high-end slide control system based on a Centronics-driven dissolve unit for four slide projectors. The system allows up to 16 projectors to be controlled automatically or by hand. Music or comment to accompany the slides can be synchronized with the aid of an advanced pulse or timecode registration unit. The timecode option enables you to record all control actions in a complete slide show, whereby all relevant data are safely stored, along with the parallel sound track.

**Design by A. Rietjens**

**A**BOUT four years ago we published a computer-controlled slide fader for four projectors (Ref. 1). Together with a Centronics interface published a little later (Ref. 2), this fader allowed photography enthusiasts to put a computer in control of up to 16 slide projectors. The software written for this system was an MSX BASIC program with limited features. The designer of the slide fader, Albert Rietjens, a keen photographer and slide maker himself, has used the intervening years since this 'early' publication to elaborate the basic system into what is presented here. The result is, we feel, definitely up to scratch: a DiAV (for Digital Audio-Visual) system that competes on all fronts with far more expensive commercial equipment

(which appears to be few and far between). In fact, the DiAV will cost you only about one fifth of any commercially available product with an equal set of features.

### The DiAV system

The drawing in Fig. 1 presents an overview of the complete system to be described. The central block is formed by the DiAV main unit, which is based on the multi-purpose Z80 card (Ref. 3). The main unit is capable of controlling up to four dissolve units (slide control units, each suitable for controlling up to four projectors). This is achieved by connecting the individual units in series.

A tape recorder may be connected up into this system to add a music channel to the slide series. The tape recorder used for this purpose must have the possibility to record pulses that, on being played back, are converted into control signals for the projectors. This is the simple option. The more advanced is the timecode interface (Ref. 4), which is capable of reading from, and writing to, tape either one of two formats: a timecode signal or a 'special code' called Special Data Language, SDL. The SDL is recorded 'in parallel' with the sound track (music channel) to ensure absolute synchronicity. In addition to information about the course of the slide series, the SDL also contains all information on the current positions of the slide carriers in the projectors. This synchronization works so well that the system is capable of moving the carriers in all projectors to the desired positions (i.e., slide) when the tape is started at any point in the series. Once running, the whole system is perfectly synchronized, and the slides appear in the programmed order from the new start point onwards.

The main unit puts the user in general control over all sub-systems, and has a large number of options for its control. Those of you who have followed the articles on the multi-purpose Z80 card know that this sports interfaces for a liquid crystal display (LCD), a PC-XT keyboard and an infra-red (IR) remote control receiver module. The keyboard and the IR link are the primary control elements of the main unit. The remote control is particularly useful for 'quick and dirty' control of the main unit, i.e., if you want to show a couple of slides without bothering too much about special effects. Although the IR remote control can be used to enter all data, the PC-XT keyboard will be preferred whenever a 'real' series is to be programmed.

Owners of an IBM PC or compatible may also control the main unit via the RS232 serial interface, or convey control programs written with a word processor from the PC to the DiAV, and vice versa.

The main unit has a 32-kByte RAM disk (with battery backup) to hold the program that describes the slide series. This program can also be read back for editing on the PC. The RAM allows up to 32 series to be stored, or fewer if the series are relatively large (the average series will comprise something like 100 slides, and consume a RAM space of about 1 kByte).

For emergency cases, the main unit has a small keyboard that allows you to select



those basic functions that 'save' you when you have forgotten the remote control, or when the batteries are flat.

## The electronics

The complete DiAV is a combination of a number of building blocks published earlier in *Elektor Electronics* (see references). However, since the original slide control unit goes back four years, we thought it fit to design a new interface for it, taking into account everything we have learned in the mean time about its practical use. Fortunately, this does not mean that constructors of the 'old' interface have another piece of equipment to forfeit. The 'new' interface is compatible with the 'old' one, provided the latter is controlled via the Centronics interface developed for it. Those of you who have a fully-fledged slide control plus Centronics interface may, therefore, skip the following sections on function and construction. Note, however, that the 'new' interface has a number of extras and improvements. Also, its 'package' is stylish, neat and attractive looking — see the introductory photograph.

## The dissolve unit

The block diagram of the new dissolve unit is given in Fig. 2. The most conspicuous feature of this unit is that it is controlled by a microprocessor rather than by discrete electronics. Here, using a microcontroller allows us to cut down drastically on external components. The circuit may be controlled via a Centronics interface, which is available on most, if not all, PCs. Note, however, that the computer is required only if you do not use the Z80 main unit, or if you wish to write your own system software.

The control signals supplied by the PC are passed to another dissolve unit (if used) via a Centronics connector. In addition to a Centronics input, the interface also has an I<sup>2</sup>C connection. This is reserved for future applications, and not implemented in the current control software.

To enable the processor to control the brightness of the projector lamps directly, it must know when the zero crossing of the mains voltage occurs. This information is supplied by a zero-crossing detector incorporated in the power supply. The zero-crossing detector is common to all projector lamps, which means that the dissolve unit and all projectors must be powered from the same mains outlet (via an approved distribution block). Note that this is not essential in the UK because in a ring circuit all outlets have the zero crossing simultaneously. The processor uses the zero-crossing information and the commands received via the inputs to arrange the brightness of the individual projector lamps, and the changing between projectors. It can do so via the 'pro-

## DiAV: a slide control system with professional features

### Dissolve unit

- Microcontroller-driven
- No special ICs except microcontroller
- Interface compatible with slide controller (earlier publication)
- Transistor drivers for carrier solenoids
- No modifications inside projectors
- Simple to connect; only connecting cable depends on projector
- Also usable as a stand-alone unit (with limited functions)

### Main unit

- Controlled by multi-purpose Z80 card
- Stand-alone system; independent of computer type
- Operated via infra-red remote control or via PX-XT keyboard
- Battery back-up
- Memory for up to 32 slide series
- RS232 interface for PC control and program exchange
- Direct synchronization by pulse control (connects straight to ITT recorder for slide control)

### Main unit in combination with timecode interface

- Full tape synchronization possible
- Uses timecode for synchronization
- Slide series program editing using timecode
- Perfectly timed slide changes (accuracy: 10 ms)

Overall performance comparable to £1250+ systems.

jector control' blocks shown in Fig. 2.

In principle, the functions described so far would suffice for the target system, because they allow us to do all we want: control lamp brightness, and change slides on any of the connected projectors. The processor, however, also allows us to control a display that indicates the slide positions in the carriers, the lamp brightness, and the 'slide change' function. These functions are controlled via the count dis-

play block and the lamp indicator block, respectively.

## About the projectors

Before discussing the electrical schematic, we have a look inside a typical slide projector. The crucial part is shown in Fig. 3. Broadly speaking, projectors can be divided into two classes: types with one-button control, and types with two-button


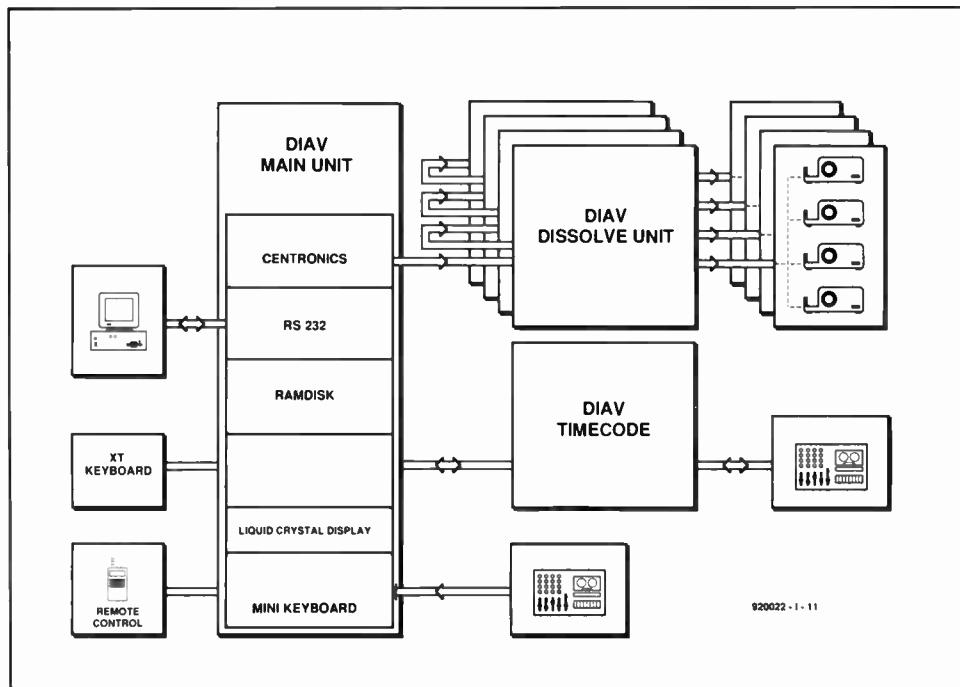


Fig. 1. This block diagram provides an overview of the complete DiAV system.

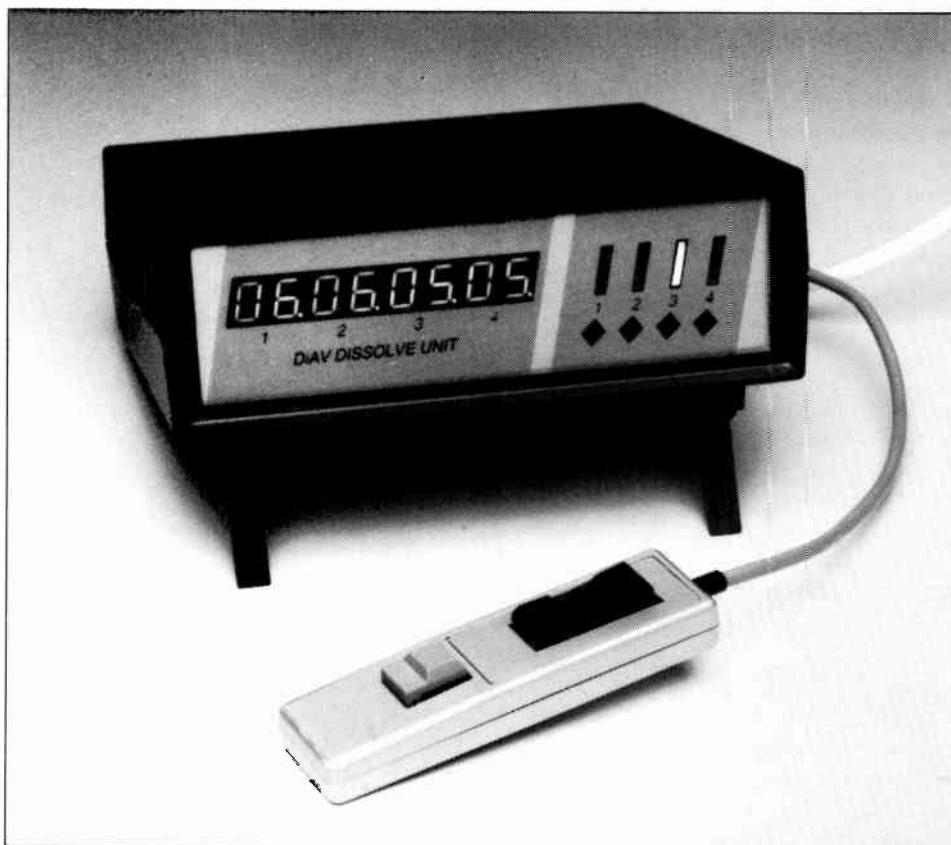

control. With one-button projectors, the forward or reverse direction of the slide carrier is determined by the time the button is pressed. By contrast, the two-button type has one button for each direction. The buttons cause electromagnets (solenoids) to be energized that, in turn, cause the slide carrier to move forward or reverse (or turn accordingly in the case of a carousel carrier). The electromagnets are powered by a direct voltage which is derived from the secondary of the mains transformer fitted in the projector.

The electromagnets are usually shunted by back-e.m.f. suppressor diodes. In some older projectors, these diodes are not present, and must be retro-fitted to enable the proposed projector control to function properly.

Figure 3 also shows the triac as it is wired in projectors with a straight slide carrier. By contrast, the triac is connected externally to most professional 'carousel carrier' projectors we have seen so far.

## Dissolve unit electronics

The central parts in the circuit diagram of the dissolve unit (Fig. 4) are a microcontroller (IC3), an address latch (IC4) and an EPROM (IC5) that contains the necessary software. The microcontroller is a 16-MHz 80C32. Apart from the EPROM, the controller addresses a number of buffers with specific functions: IC7 to read the Centronics input; IC8 to set the slide carrier control; and IC9-IC10 to control the display functions. All these ICs are addressed via IC15a.

The Centronics input is formed by connector K1, which is 'looped through' to the

Centronics output, K2, via IC12 and IC6. This means that all series-connected units receive the same data. Each new databyte is latched in IC6 at the end of the strobe pulse, whereupon it can be read via IC7. At the same time, bistable IC13a is set, which produces a high signal on the BUSY line of K1. IC12d passes the busy signal(s) from

any further unit(s). This enables all units to evaluate the received data. The Q\ output of IC13a (pin 6) triggers the INT1 interrupt input of the processor, so that the received data can be processed immediately. Switches 1 and 2 of S1 determine which bank of four projectors is controlled (see Table 1).

As already mentioned, the I<sup>2</sup>C interface is not supported by the current software version. It is, however, used for a simple manual control that allows two, three or four projectors to be controlled, with a variable overflow time between 0 s and 10 s, in steps of 1 s (see also Table 1).

## Power supply

The circuit is powered from an alternating voltage source to enable the zero-crossings of the mains voltage to be detected (this is necessary for the lamp dimmers). Figure 5 shows the timing relevant to the triac gate triggering. The signal numbers refer to the test points in the circuit diagram of the dissolve unit, Fig. 4.

The alternating voltage applied to J1 is rectified by D5-D8. The smoothing, however, does not take place until 'behind' D9. The anode of D9 carries signal '1', which enables components R26, R28, D34, T13 and IC12a to detect the zero-crossings (signal '2'). When the voltage drops below the threshold voltage of D34 plus the voltage across the base-emitter diode of T13, this transistor will stop conducting, so that the collector voltage swings high. This high level is fed to the processor via buffer

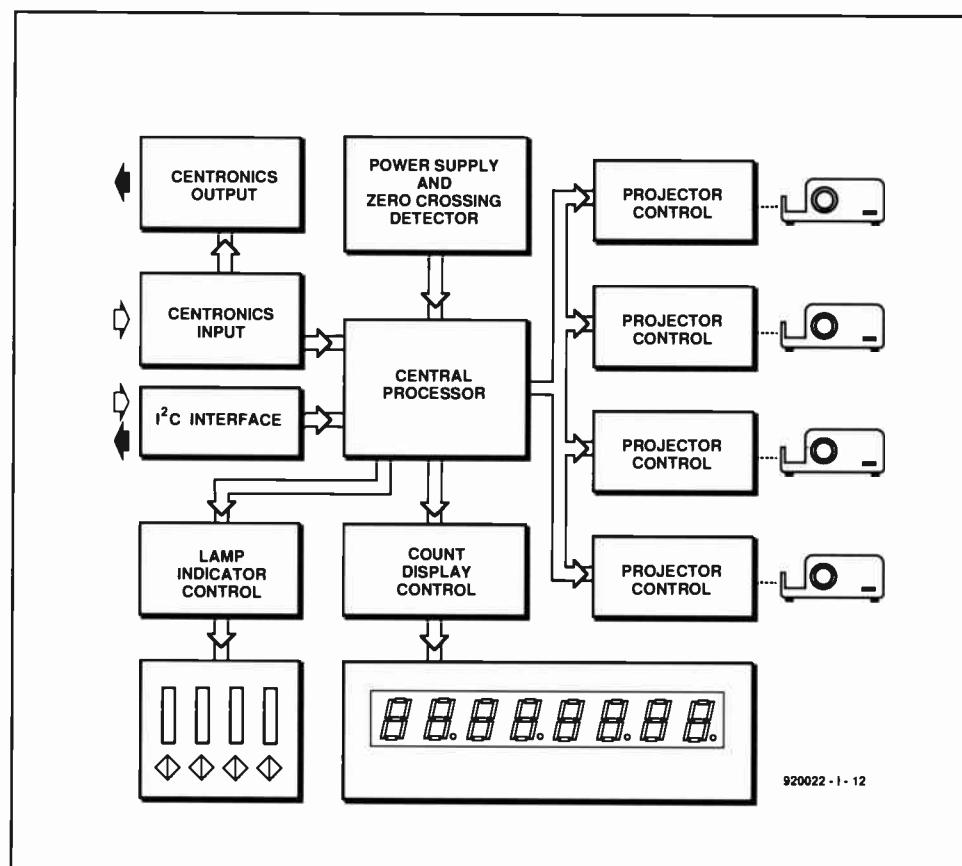


Fig. 3. Block diagram of the dissolve unit.

IC12a. To enable a minimum brightness level to be set, this signal is also applied to IC11b, a monostable multivibrator (MMV). The negative (falling) edge at pin 9 triggers the MMV, which responds by generating a pulse that starts at the end of the zero-crossing, and lasts until just before the next zero-crossing. A preset, P1, determines how far the end of the pulse is removed from the new zero-crossing. The processor will fire the triac from the end of the pulse to the next zero-crossing, which sets up a minimum brightness level (signal 4a). This setting ensures that the lamp filament can never go 'cold' between two successive overflow actions. This enables the lamp to light up quickly from 'off' to the desired brightness. Signals 4b and 4c in Fig. 5 show the gate control with a partly dimmed lamp, and one that lights at full intensity, respectively.

Next, let us have a look at the four identical projector control circuits. The functions of the previously mentioned push-buttons on the projector controls are taken over by combinations of an optocoupler and a transistor. The operation of this interface can be explained by reverting for a moment to the internal diagram of the projector. The common connection of the forward/reverse buttons is connected to the highest direct voltage in the projector. When, for instance, R1 is connected to ground, optocoupler IC1a sends base current into T1, and so causes the relevant electromagnet in the projector to be energized. The need for a suppressor diode across the electromagnet coil is evident: without it, the back-e.m.f. produced when a coil is switched off would very likely destroy the relevant driver transistor.

If jumper JP1 is closed (fitted) at power-on, the interface will control the projectors as if they were 'one-button' types, and control the relevant transistor connected to pin 2 of K9-K12 such that the slide carrier moves in the desired direction. This setting may be changed, via the control, while the unit is in use.

The second function to be controlled in each projector is the lamp intensity, or, in other words, the triac. This is achieved with the aid of T3 (T6, T9 and T12 have identical functions). When the circuit is connected to the projectors, the anode terminal, A1, of the triac is connected to ground, while resistor R5 is connected to the gate terminal. By making T3 conduct, a gate current is established for the triac, which fires. When the gate current is interrupted, the triac stops conducting. In this way, the lamp brightness is controlled by means of the phase angle, as already illustrated in Fig. 5. The gate driver transistors are controlled directly by the microprocessor. This is achieved by resetting an internal counter at the end of every zero-crossing, and then enabling the counter again. Next, the contents are compared with a predetermined value, which depends on the desired brightness. When

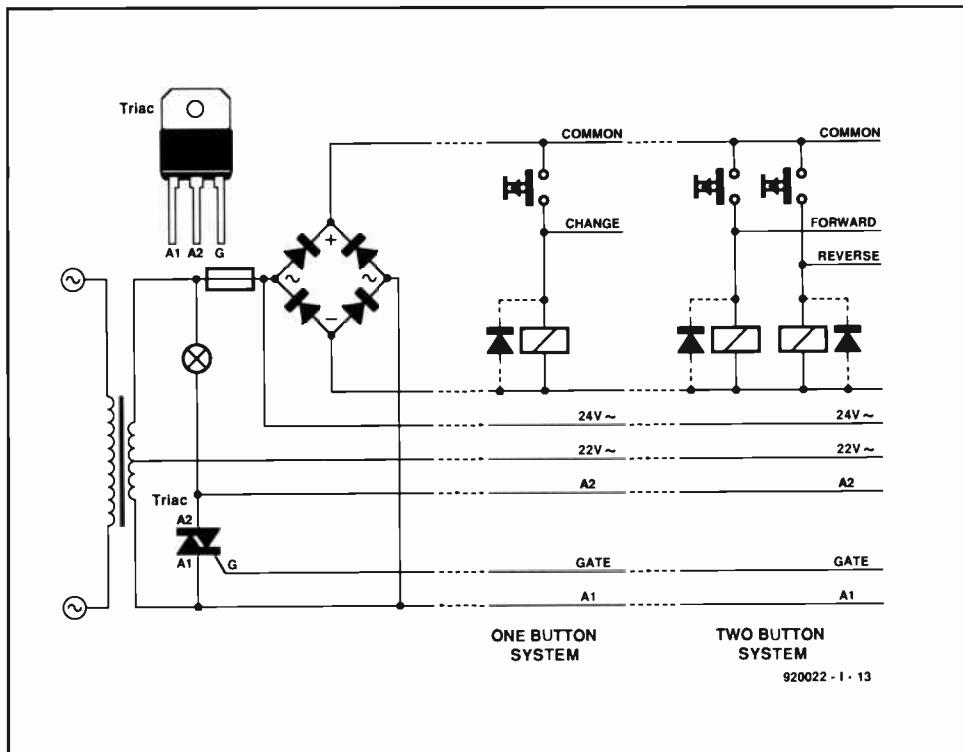


Fig. 3. Typical lamp/soleenoid circuit in one-button and two-button slide projectors. Mind you: the triac is not fitted in all projectors!

S1-1	S1-2	S1-3	S1-4	Function
on	on	X	X	Bank 1: projector 1-4
off	on	X	X	Bank 2: projector 5-8
off	off	X	X	Bank 3: projector 9-12
on	off	X	X	Bank 4: projector 13-16
X	X	on	on	2 projectors in manual mode
X	X	off	on	2 projectors in manual mode
X	X	on	off	3 projectors in manual mode
X	X	off	off	4 projectors in manual mode

Table 1. Switches S1-1 and S1-2 set the dissolve unit bank selection, while switches S1-3 and S1-4 set the number of projectors when manual control is used.

the counter state exceeds the preset value, a pulse train is sent to the triac gate. This train lasts until the next zero-crossing occurs. A simple filter, R3-C1, is fitted to prevent excessive 'pollution' of the dissolve unit power supply voltage. The projector connections of all four projectors are gathered on K7, from where a length of flatcable takes them to K13. This connector, in turn, is wired to DIN connectors for the four individual projectors.

## The display

The display consists of two parts: a counter display (eight 7-segment displays) and the lamp display (24 LEDs). Both displays are multiplexed in a simple way by software that varies the data applied to IC9 and IC10. In both cases, the addressed display section is determined by a part of the latched dataword (the two highest bits on IC9, and bits D4, D5 and D6 on IC10). A de-

coder IC is used to produce numbers on the display. The decoder converts a 4-bit number into a 7-segment code. The remaining bit, D7, is used to drive the decimal point.

LEDs D15, D21, D27 and D33 indicate the slide changing operations, while the remaining LEDs indicate the set lamp brightness.

A switch, S3, on the main board allows the display to be switched to a lower intensity in case the light it emits is distracting (in the dark, during a slide show).

## The control protocol

Those of you who wish to build the complete DiAV system can make use of the extensive control software developed for it. Alternatively, you may wish to have a go at producing your own control software, for which it is, of course, necessary to know the programming details of the


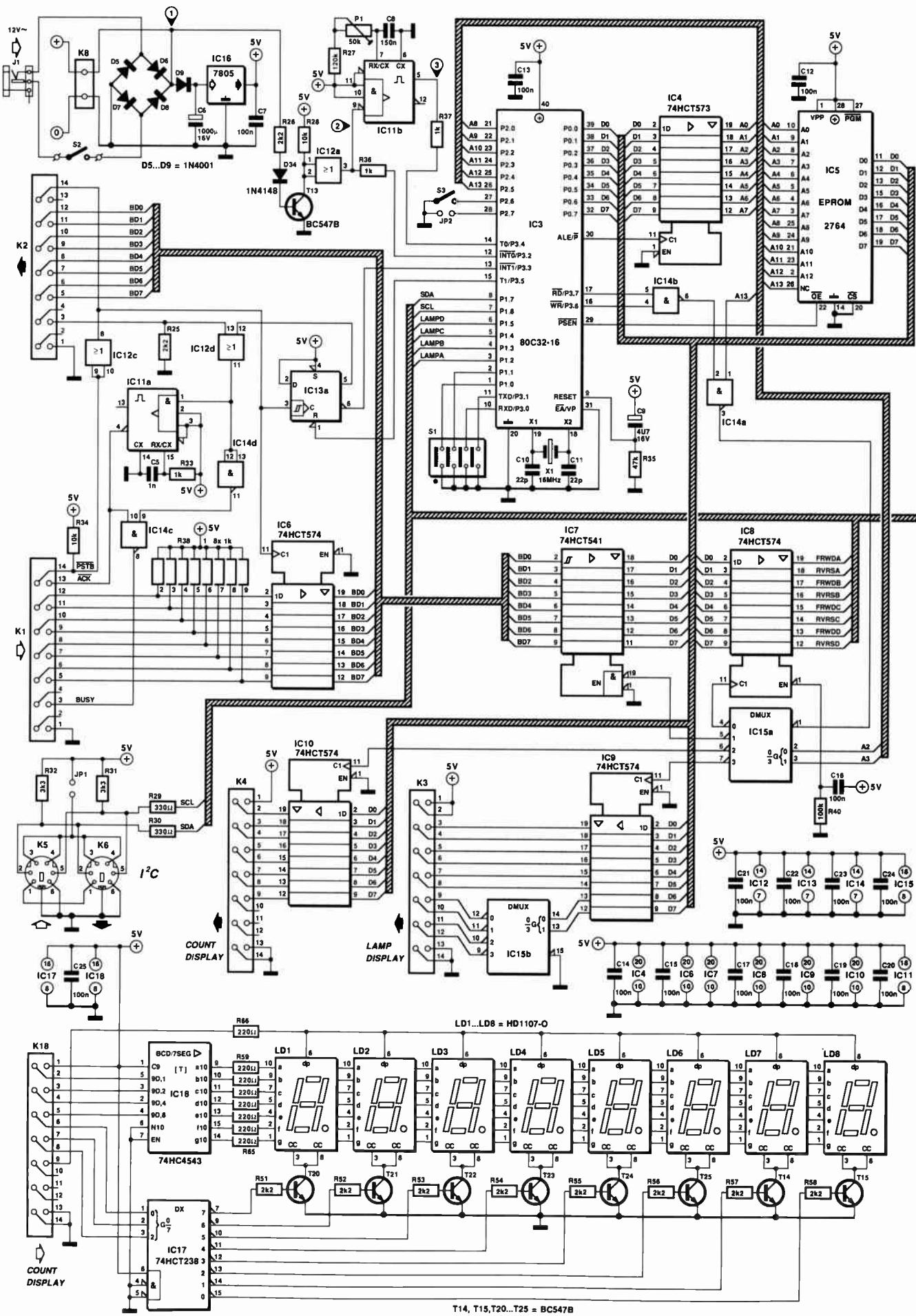


Fig. 4. Circuit diagram of the dissolve unit. At the heart of the circuit is a 16-MHz 80C32 CPU.

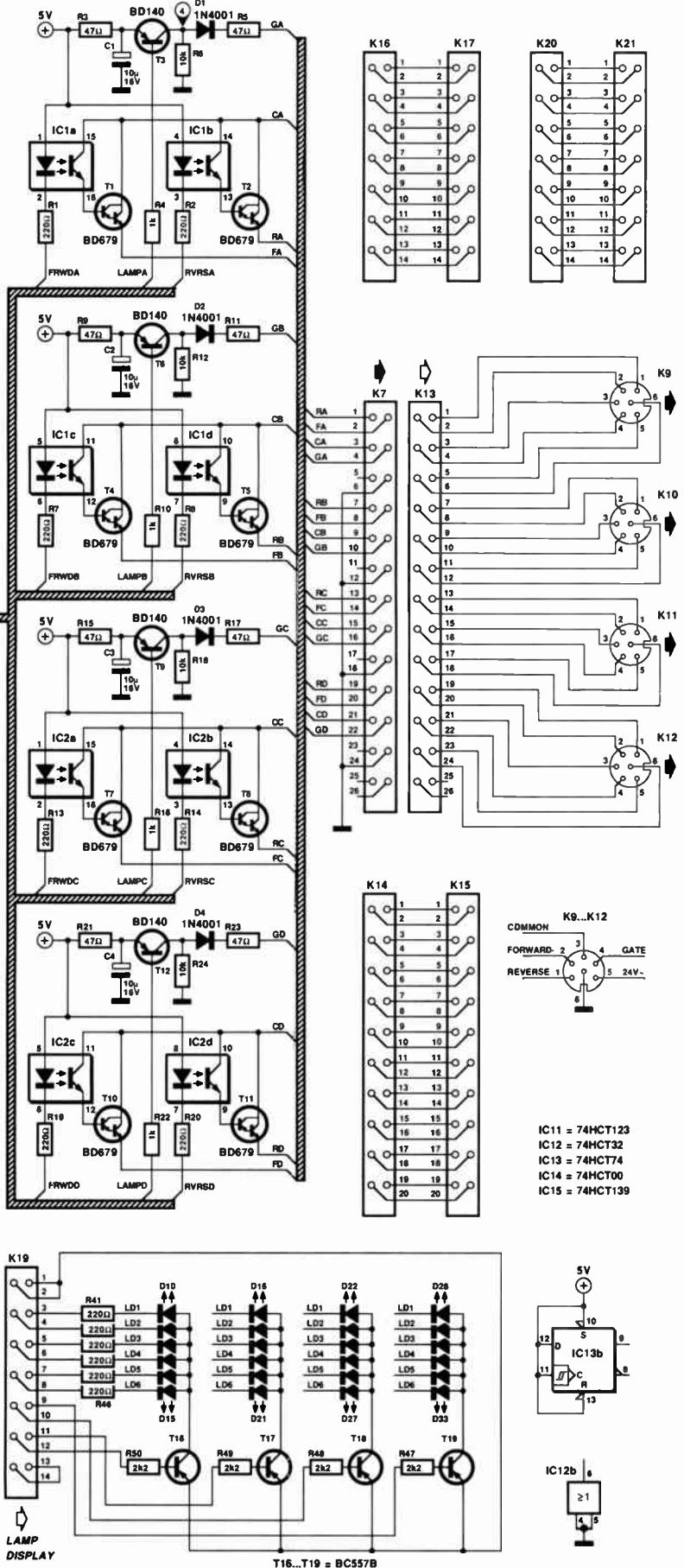

Centronics interface or the manual control.

As already mentioned, the present dissolve unit uses the same protocol as the Centronics interface described in Ref. 2. A control cycle consists, in principle, of two databytes sent one after another: the projector control byte and the databyte proper. The first selects the desired projectors and the associated bank of four projectors, while the databyte determines the way the selected projectors are controlled. The functions of the bits in the projector control byte and the projector databyte are given in Tables 2 and 3.

A projector control byte always has two 'ones' in the two highest bit positions. In the databyte, these positions form separate indicators for the carrier forward/reverse control. The remaining six bits in the databyte determine the lamp brightness in the selected projector. The bank selection bits in the projector control byte must match the settings of switches S1 and S2 for the selected unit to be addressed. In principle, it is possible to select all four projectors in a control byte, after which only one databyte is required to issue the same command to all four projectors. This can be done without problems when the 'old' Centronics interface is used. The present interface, however, responds differently: on receiving a 4-projector selection word (control byte 1100 00xx), it switches the dissolve unit to its set-up (initialization) mode. If the command is followed by a databyte '0', the four projectors will not only have their lamps dimmed completely, but the display is reset also. Next, a number of settings can be selected. The set-up mode is left on receipt of a carriage return (0DH) or a line feed (0AH) command. Table 4 shows an overview of the set-up options.

D7 1 control word ID

D6 1

D5 P4 0 selects projector 4

D4 P3 0 selects projector 3

D3 P2 0 selects projector 2

D2 P1 0 selects projector 1

D1 X bank selection

D0 X


Table 2. Bit functions in the projector control byte.

D7 1 = change forward

D6 1 = change reverse

D0-D5 lamp intensity

Table 3. Bit functions in the projector databyte.

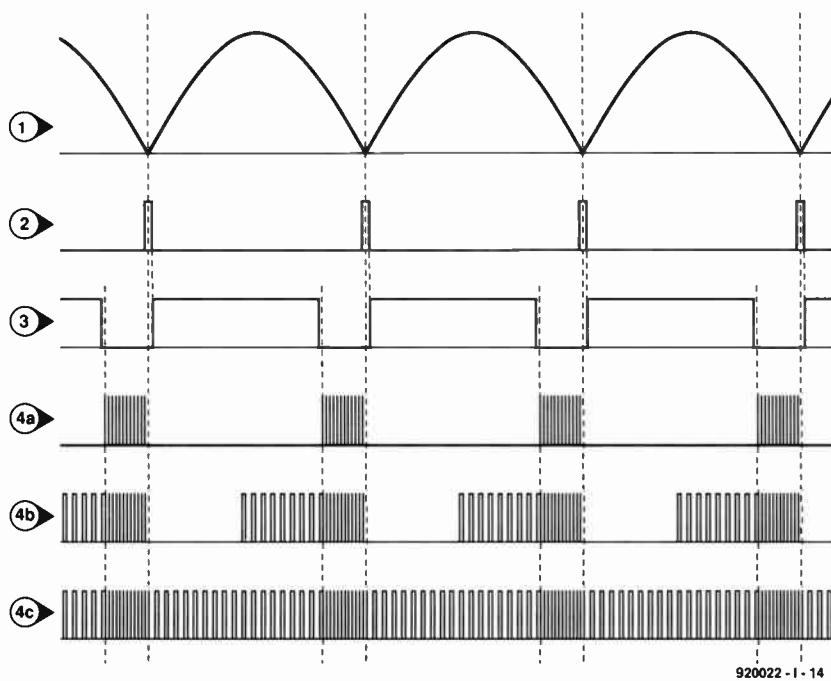

**Fig. 5.** Timing diagrams to illustrate the relation between the zero-crossings and the gate control signal.

The listing in Fig. 6 is an example of a simple BASIC program containing LPRINT statements to control the dissolve unit. Note the use of the semicolon (;) after each control byte. If you forget this character, the CR/LF sequence that follows it is taken to be a databyte. The semicolon is not required after databytes, because the projector selection is reset after each databyte. Just for the sake of completeness, Fig. 7 shows the wiring of the Centronics cable between the PC and the dissolve unit.

The manual control is connected to one of the I<sup>2</sup>C inputs as shown in Fig. 14. Switches S4 and S5 select between forward or reverse overflow respectively, or, after pressing S6, between lengthening or shortening the overflow time.

## Connecting the projectors


It was already mentioned that some projectors have an internal triac to control the lamp brightness, while others require the triac to be connected as an external part. Those of you who feel less confident about modifying the electrics of the slide projector are best off with an 'internal triac' type of projector. In case such a projector is not available, there is no other option than to

```

540 IF IS=CHRS(13) OR I$="r" OR IS="R" THEN GOSUB 730: GOTO 470
550 LOCATE 11,8 : PRINT " "
560 IF IS="f" OR IS="F" THEN D=S :LOCATE 11,8: PRINT "*"
570 LOCATE 12,8 : PRINT " "
580 IF IS="n" OR IS="N" THEN D=2*S :LOCATE 12,8: PRINT "**"
590 LOCATE 13,8 :PRINT " "
600 IF IS="l" OR IS="L" THEN D=3*S :LOCATE 13,8:PRINT ***
610 IF IS="q" OR IS="Q" THEN CLS : END
620 GOTO 470
630 '..... Next projector
640 FIRST =0
650 Y=X
660 X=ASC(LEFT$(BS$,1))
670 AS=RIGHTS(AS,L)+LEFT$(AS,1)
680 BS=RIGHTS(BS,L)+LEFT$(BS,1)
690 GOSUB 840
700 LOCATE 17,10: PRINT "Projector ";RIGHTS(AS,1); is on"
710 DA=128: C=F: GOSUB 910
720 RETURN
730 '..... Previous projector
740 IF FIRST =1 THEN 830
750 Y=ASC(MID$(BS$,1,1))
760 DA=64: C=R: GOSUB 910
770 Y=X
780 AS=RIGHTS(AS,1)+LEFT$(AS,L)
790 BS=RIGHTS(BS,1)+LEFT$(BS,L)
800 X=ASC(RIGHTS(BS,1))
810 GOSUB 840
820 LOCATE 17,10: PRINT "Projector ";RIGHTS(AS,1); is on"
830 RETURN
840 '..... Dissolve
850 FOR I=0 TO 63
860 I,PRINT CHRS(X): CHRS(I-1*(I=9))
870 I,PRINT CHRS(Y): CHRS(63-I+(63-I=9))
880 FOR J=0 TO D: NEXT
890 NEXT
900 RETURN
910 '..... Change slide
920 FOR I=0 TO 100 ' .... wait before change
930 FOR J=0 TO W : NEXT
940 NEXT
950 I,PRINT CHRS(Y):CHRS(DA)
960 FOR I=0 TO 100
970 FOR J=0 TO C: NEXT: ' ..... changing time
980 NEXT
990 I,PRINT CHRS(Y):CHRS(0)
1000 FOR I=0 TO 100
1010 FOR J=0 TO C : NEXT
1020 NEXT: ' .. Wait before next dissolve is allowed
1030 END
1040 CLS: LOCATE 9,10: PRINT "Error in line 50 adjust AS"
1050 END

```

**Fig. 6.** A simple BASIC program to get you started with the dissolve unit. The projectors used (here: 1 to 4) are identified in line 50.

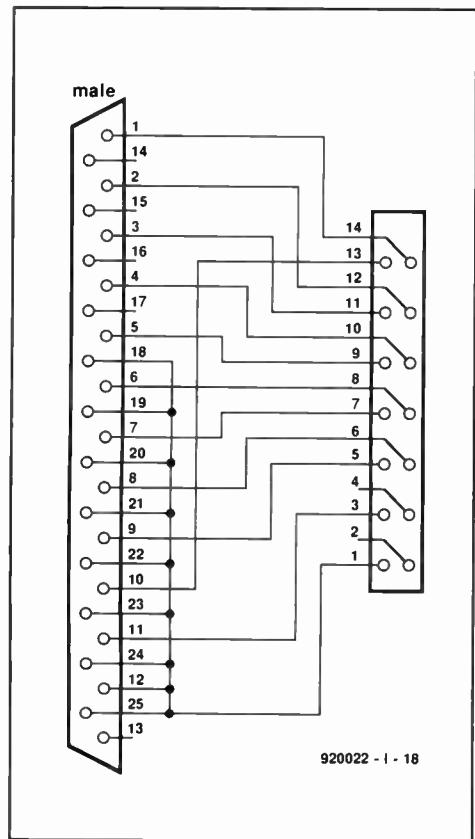

**Fig. 7.** Overview of connections between the PC's Centronics output and the dissolve unit.

00h	reset display and gate triggering
01h	single button projectors: change on pin 2 of K9-K11
02h	double button projectors: forward change on pin 2 of K9-K11 reverse change on pin 1 of K9-K11
03h	S3 switches display on/off
04h	S3 switches between high and low intensity
05h	set display high intensity
06h	set display low intensity
07h	lamp indicator as linear bar
08h	lamp indicator as centred bar
09h	—
0Ah	setup end
0Dh	setup end

**Table 4.** These setup commands can be issued to the dissolve unit after sending a setup control byte (1100 00xx).


install the triac yourself as an upgrade to the projector. Here, we show you how to do this — it is not very difficult.

Unfortunately, there is a hardware compatibility problem to begin with: manufacturers of slide projectors use different connectors for the triac control input. Figure 8 shows the three most commonly found connector types. Still other connectors and pin assignments exist, so you are well advised to consult the user manual that came with the projector. The 6-way DIN connector (Fig. 8a) is used for our sys-


tem. On the projector, the overflow or AV socket is usually marked by two small triangles (see Fig. 9). Figure 10 shows the construction of the connecting cable for

the 6-way DIN and the 10-way DIN versions.


Projectors with an RTG22 connector require a separate triac module to be made.

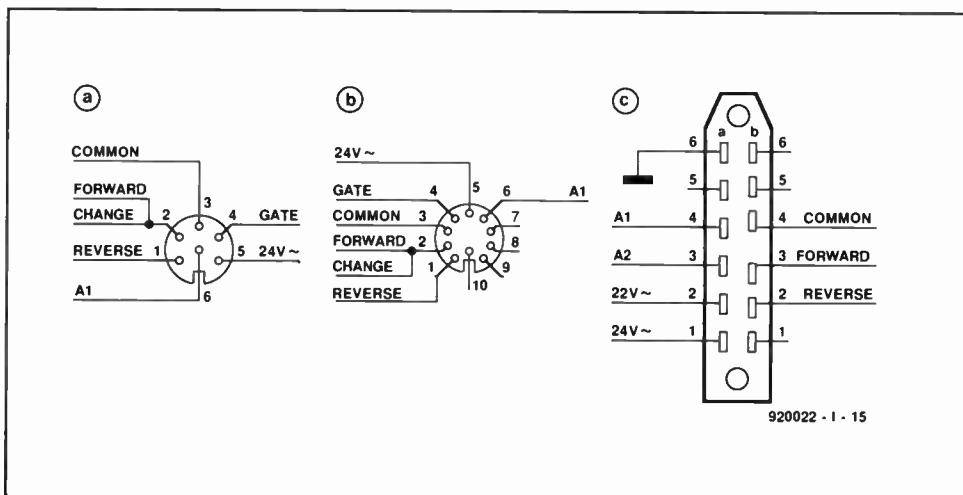

**Fig. 8.** Overview of the most commonly used slide projector connection systems. Figure 8a shows the 6-way version which is also used for the DiAV. In addition to this connection, you may also come across 10-way DIN (8b) and 12-way RTG22 (8c) versions (the latter nearly always on carousel type projectors).

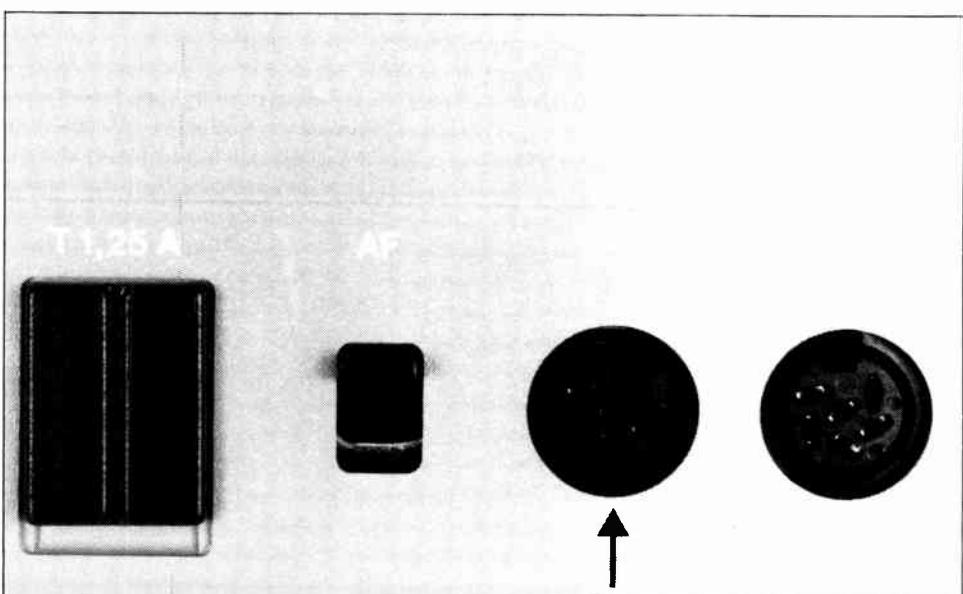

**Fig. 9.** Showing the AV (audio-visual) legend on projectors with an internal triac.

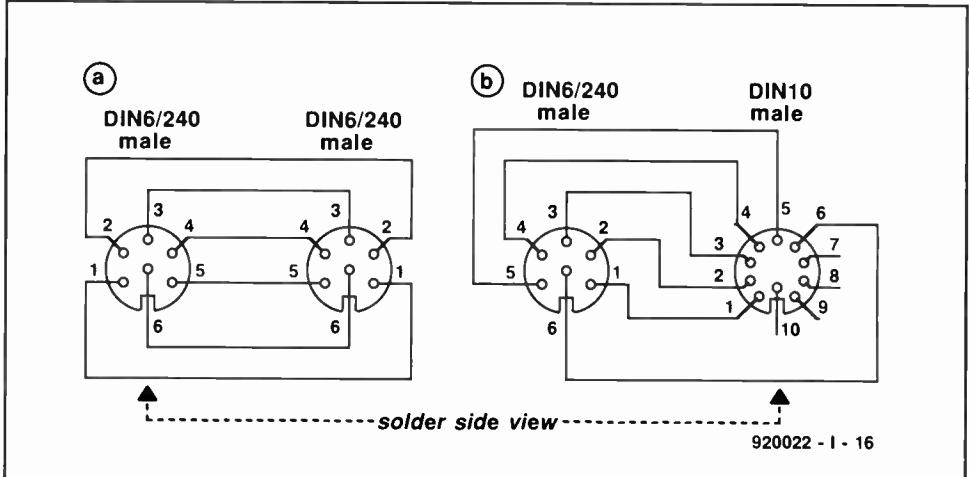

**Fig. 10.** Construction of the connecting cables.

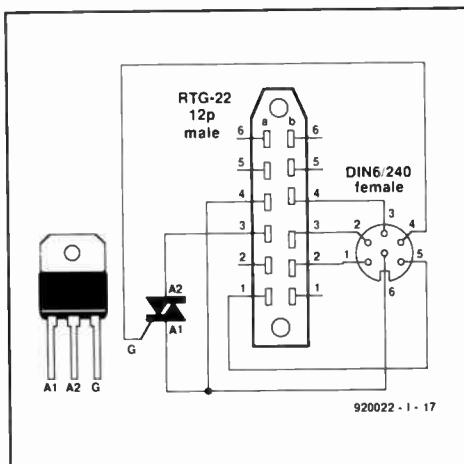


Fig. 11. Those of you who wish to make use of a carousel slide projector will have to connect the triac as an external module. The necessary parts and connections are shown here.



Fig. 12. Illustrating the internal triac upgrade. The triac is fitted as close as possible to the fan to ensure it is adequately cooled.

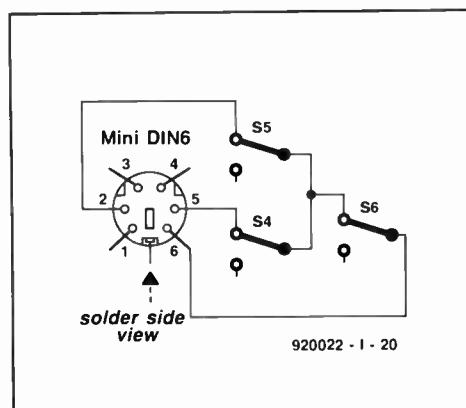


Fig. 13. Construct this simple connecting cable if you wish to use the dissolve unit as an independent control for your slide projector. This is achieved by making use of the I2C interface on the unit.



Fig. 14. This photograph illustrates how the triac module is constructed. Do not forget to fit the triac with a thermal insulation set.

This module is connected via a 6-to-6-way cable as illustrated in Fig. 11. The module is a small diecast aluminium case drilled to accept the connectors, the triac and a heat-sink. Its construction is illustrated in Fig. 14. In view of the high currents (up to 10 A), the A1 and A2 terminals of the triac should be connected with short lengths of fairly thick wires (1.5 mm<sup>2</sup> or SWG17). Bend the anode terminals around the wire ends before soldering, so that the junction can never come loose even when very high temperatures are reached.

So far, we have assumed that the triac is contained in the projector. However, this is not usually the case with inexpensive projectors, which must be upgraded. If you do so, stick to one of the connection diagrams shown in Fig. 8, preferably 8a or 8b. The reason is obvious: compatibility! Mount the triac on a small heat-sink, close by the fan (see Fig. 12). Do not forget to use an insulating washer and mounting bush. For 150-W projectors, use a TIC236 triac, or a TIC263 for 250-W types. The triac may be tested by connecting its gate terminal to the 24-V a.c. source via a 1-kΩ resistor, whereupon the lamp should light.

### To be continued...

This is the first of four instalments. The next instalment will discuss the construction and testing of the dissolve unit. Also, details will be given on the use of the multi-purpose Z80 card as the main unit in the DiAV system. For this purpose, some components on the Z80 card need to be changed with respect to the original design.

Although the DiAV is a modular system, some of you may want to build it as a self-contained, compact unit. Part 3 of this article series will, therefore, show how the timecode interface, the main unit and one dissolve unit may be fitted into a single enclosure.

The last part of the article will describe the software and the user options created in the system. □

### References

1. 'Computer-controlled slide fader'. *Elektor Electronics* March and April 1988.
2. 'Centronics interface for slide fader'. *Elektor Electronics* December 1988.
3. 'Multi-purpose Z80 card'. *Elektor Electronics* May and June 1992.
4. 'Timecode interface for slide controller'. *Elektor Electronics* July/August and September 1991.

### PREVIEW *Speaker Builder*

#### Issue 6, 1992

- What Makes Your Room Hi-Fi?, Part 1
- Toyota Pick-Up Installation
- Electronic Counter for Coil Winding
- ABCDs of Speaker Placement
- More About Dust Caps

# 8051/8032 ASSEMBLER COURSE

## PART 8 (FINAL): LCD AND KEYBOARD INTERFACING

By Dr. M. Ohsmann

In this last instalment of the course we first deal with an ever popular subject: how to connect a liquid crystal display (LCD) to the 80C32 single-board computer. LCD modules with one or two text lines are available at relatively low cost these days, and are simple to drive from the 80C32 SBC, as will be shown below.

### LC displays

Many stand-alone microcontroller applications require an output device to display texts, numbers and measurement data. An LCD module is ideal for this purpose. For instance, it allows a sequence of user entries to be given a menu-like structure which uses only a couple of keys as the hardware.

To keep the connection of an LCD as simple as possible, a special interface is provided on the 80C32 extension board.

### Connections

The electrical connections between the extension board and the LCD are established by a 14-way flatcable. It is assumed here that the LCD has a Hitachi Type HD44780 controller, or a direct equivalent. Unfortunately, the pinning of the connectors on the LCDs that can be used is not standard, so you are well advised to ask for a datasheet when purchasing a display. Suitable types include the H2570

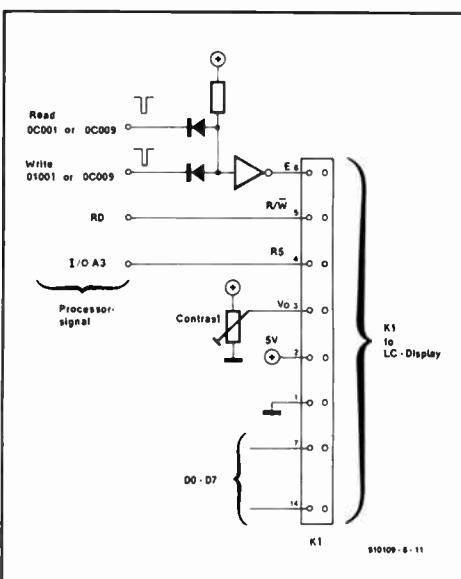


Fig. 50. Connecting the LCD to the 80C32 SBC extension card.

(Hitachi), LM016L and LM1612A (Sharp), and VK2116L (Vikay). The pinning of LCD connector K1 (on the 80C32 extension board) is given in Fig. 50. This information must be used to make the cable to the connector on the LCD. The LCD enable signal is generated after a read (RD=1) or write (WR=1) operation to address 0C009H or 0C001 respectively. The level of address line IOA3 then determines whether the read/write operation concerns display data (RS=IOA3=0; address 0C009H), or a display command (RS=IOA3=0; address 0C001H). The R/W terminal of the LC display is connected directly to the RD output of the 80C32 SBC.

Commands and data are exchanged via

the bidirectional databus. The display itself can work in 4-bit mode (bits 0-3) or 8-bit mode (bits 0-7). Since we are working with an 8-bit microcontroller, and the display is wired to the databus, it is self-evident that the LCD is programmed to operate in 8-bit transfer mode. However, if you wish to interface the LCD to, say, a PORT, it may be wiser to use 4-bit transfer mode, since this reduces the number of PORT lines used.

Voltage V0 on K1 terminal 3 serves to set the LCD contrast. The setting can be adjusted depending on the ambient light intensity and the viewing angle. Before connecting the LCD, make sure that it is properly connected — when in doubt, consult the datasheets.

Instruction	Code										Description	Execution Time (when $f_{CP}$ or $f_{osc}$ is 250KHz)												
	RS	R/W	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0														
Clear Display	0	0	0	0	0	0	0	0	0	1	Clears all display and returns the cursor to the home position (Address 0)	82 $\mu$ s ~ 1.6ms												
Return Home	0	0	0	0	0	0	0	0	0	1	* Returns the cursor to the home position (Address 0). Also returns the display being shifted to the original position. DD RAM contents remain unchanged	40 $\mu$ s ~ 1.6ms												
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S	Sets the cursor move direction and specifies or not to shift the display. These operations are performed during data write and read	40 $\mu$ s												
Display ON/OFF Control	0	0	0	0	0	0	1	0	C	B	Sets ON/OFF of all display (D). Cursor ON/OFF (C), and blink of cursor position character (B)	40 $\mu$ s												
Cursor or Display Shift	0	0	0	0	0	1	S/C	R/L	*	*	Moves the cursor and shifts the display without changing DD RAM contents	40 $\mu$ s												
Function Set	0	0	0	0	1	DL	N	F	*	*	Sets interface data length (DL), number of display lines (L), and character font (F)	40 $\mu$ s												
Set CG RAM Address	0	0	0	1	ACG						Sets the CG RAM address. CG RAM data is sent and received after this setting	40 $\mu$ s												
Set DD RAM Address	0	0	1	A00						Sets the DD RAM address. DD RAM data is sent and received after this setting		40 $\mu$ s												
Read Busy Flag & Address	0	1	BF	AC						Reads Busy flag (BF) indicating internal operation is being performed and reads address counter contents		1 $\mu$ s												
Write Data to CG or DD RAM	1	0	Write Data						Writes data into DD-RAM or CG-RAM			40 $\mu$ s												
Read Data to CG or DD RAM	1	1	Read Data						Reads data from DD-RAM or CG-RAM			40 $\mu$ s												
I/D = 1 Increment      I/D = 0 Decrement S = 1 Accompanies display shift      S/C = 0 Cursor move S/C = 1 Display shift      S/C = 0 Cursor move R/L = 1 Shift to the right      R/L = 0 Cursor move R/L = 0 Shift to the left      R/L = 1 Cursor move DL = 8 bits      DL = 0 4 bits N = 1 2 lines      N = 0 1 line F = 1 5 x 10 dots      F = 0 5 x 7 dots BF = 1 Internally operating      BF = 0 Can accept instruction												Don't care												
DD RAM      Display data RAM CG RAM      Character generator RAM ACG      CG RAM address AdP      DD RAM address CAdP      Corresponds to cursor address AC      Address counter used for both of DD and CG RAM address												Execution time changes when frequency changes (Example) When $f_{CP}$ or $f_{osc}$ is 270 KHz $40\mu s \times \frac{250}{270} = 37\mu s$												

Fig. 51. LCD controller command set.

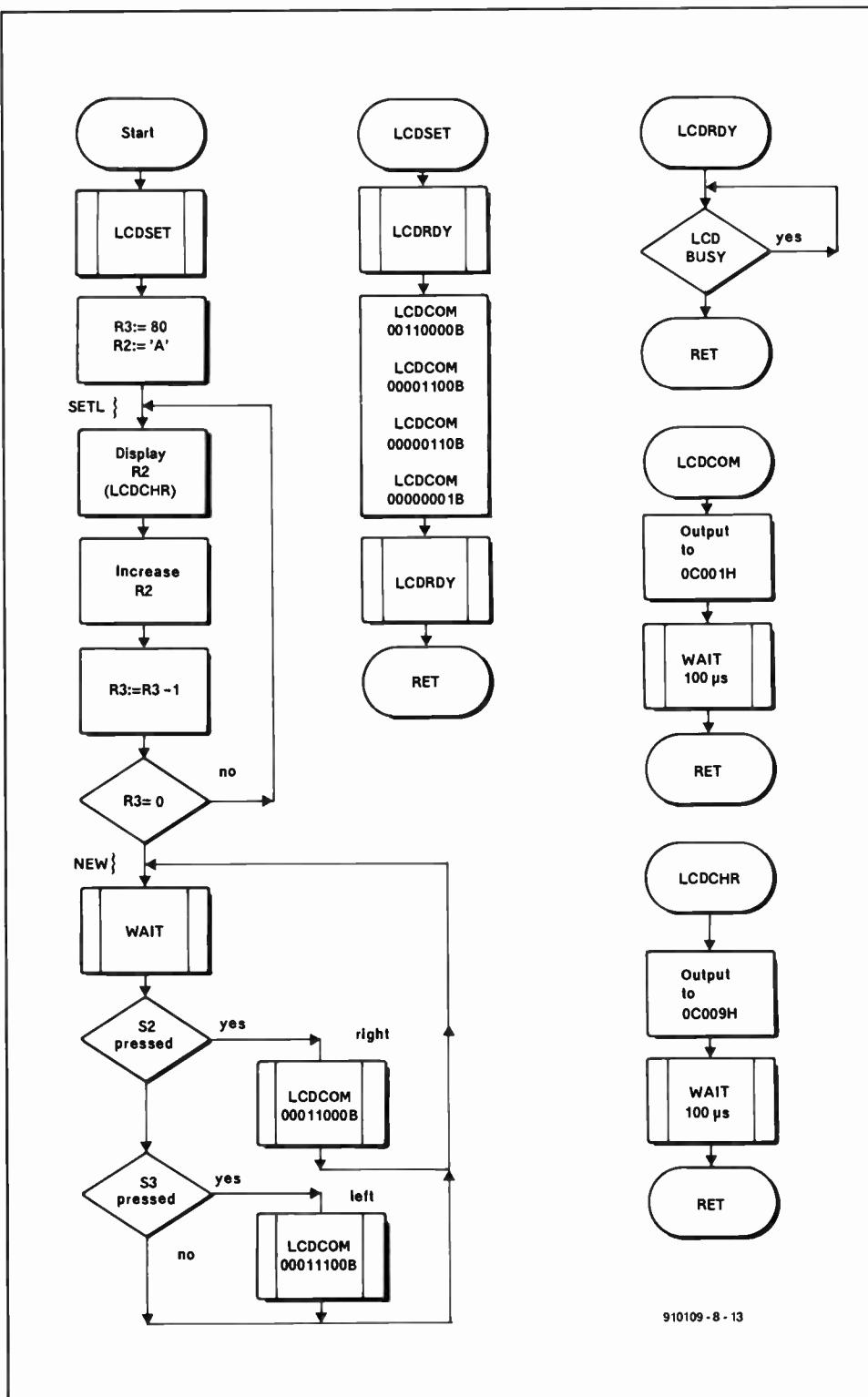


Fig. 52. Flowchart of the LCD driver program.


## LCD commands

The Hitachi LCD controller databook devotes some 30 pages to a full description of all possibilities offered by the controller-plus-LCD combination. Hence, we are forced to limit ourselves to the most important commands, in the knowledge that more extensive information is available from the manufacturer.

Many LCDs capable of displaying the ASCII character set have the same LCD controller IC, and thus the same command set. The one listed in Fig. 51 is valid for the popular LCD modules Type H2570,

LM016L and LM1612A.

To begin with, a few words about the basic operation of these displays with integrated controller. The display has an internal buffer with a capacity of 80 characters. This is the Display Data RAM, DD-RAM, at addresses 000H to 04FH. A display with one line of 16 characters displays the characters contained between 00H to 0FH, starting at the left side of the screen. In this way, a kind of window is created, which can be shifted by the Display Shift command. This works in a simple manner: while the characters remain stored at the same address in

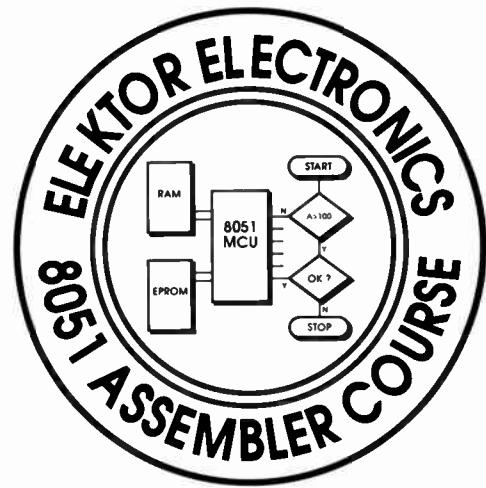

## MCS-51 PROGRAMMING A COURSE IN 8 INSTALMENTS

### Hardware/software requirements:

- a 8032/8052AH-BASIC single board computer as described in Elektor Electronics May 1991. The preferred CPU is a 8051 or 80C32. Alternatively, any other MCS51-based microcontroller system (but read part 1 of the course);
- a course diskette (IBM: order code ESS 1661; Atari: order code ESS 1681) containing programming examples, hex file conversion utilities, and an assembler;
- a monitor EPROM (order code ESS 6091);
- an IBM PC or compatible operating under MS-DOS, or an Atari ST with a monochrome display.

### Overview of publications:

Part 1: Introduction (February 1992)  
Part 2: First 8051 instructions (March 1992)

Part 3: Hardware extensions for 80C32 SBC (April 1992)

Part 4: Flags, bit addressing, PSW, conditional jumps, logic operators (June 1992)

Part 5: Arithmetic instructions (July 1992)

Part 6: Analogue signal processing and stack management (September 1992)

Part 7: Serial interface programming (October 1992)

Part 8: LCD and keyboard interfacing (November 1992).

the DD-RAM, the window in the DD-RAM is given a different start address.

With a two-line display such as the LM16255, the top line displays the characters starting at 000H, and the second line displays the characters starting at 040H. This is what makes two-line LCDs a little more difficult to program than one-line types.

Then there is the cursor, which determines the position (in the DD-RAM) of the next character. This position is called the address counter in the following description. The cursor may be visible or invisible, depending on the way it is programmed. It may also flash, if desired. By appropriate programming, you can select between a display shift and a cursor movement when a character is transferred to the LCD. This enables a horizontally scrolling text to be displayed relatively easily.

Finally, the LCD has an on-board character RAM, designated CG-RAM, in which you can store the pixel outlines of ASCII codes 0 to 7. The exact organization of the CG-RAM is given in the datasheets. This RAM allows you to define your own characters.

Commands are sent to the LCD by outputting the desired code to address 0C00H (i.e., RS is low, and R/W\ also).

After this brief introduction follows a short description of the various LCD commands. The asterisk in the examples below stands for 'bit level irrelevant'.

#### **Clear Display**

0 0 0 0 0 0 1

This command causes all DD-RAM locations to be filled with 20H (= ASCII 'space'). The cursor is set to position 0, as is the display window, which negates the effect of any previously given Display Shift command.

#### **Return Home**

0 0 0 0 0 0 1 \*

Resets the cursor to position 0, and resets any previously given Display Shift. The contents of the DD-RAM are not changed.

#### **Entry Mode Set**

0 0 0 0 0 1 I/D S

This command serves to determine what happens after a databyte has been transferred to the display. The increase/decrease (I/D) bit determines whether the internal DD-RAM is automatically increased (I/D=1) or decreased(I/D=0) when a character is read or written. The value of this address is stored in the address counter, AC.

The shift bit, S, indicates if a display shift is to occur automatically in the direction set by the I/D bit. This shift occurs when S=1, and does not occur when S=0. During the shift, the cursor retains its position inside the display window.

#### **Display ON/OFF Control**

0 0 0 0 1 D C B

This command enables us to switch the display and the cursor on and off without changing the contents of the DD-RAM. The display is switched on and off by pro-

gramming D=1 and D=0 respectively. Similarly, C=1 and C=0 switch the cursor on and off, and the same goes for the 'blink' (B) bit.

#### **Cursor or Display Shift**

0 0 0 1 S/C R/L \* \*

This command is used to move the cursor or shift the display. It is essential if you want to program a horizontally scrolling text. The options are:

S/C	R/L	
0	0	Cursor left
0	1	Cursor right
1	0	Display left, cursor follows display
1	1	Display right, cursor follows display

#### **Function Set**

0 0 1 DL N F \* \*

DL=1: 8-bit interface

DL=0: 4-bit interface

N=0: one line

N=1: two lines

Only on some types:

F=0: 5x7 dot matrix

F=1: 5x10 dot matrix

This command sets the display's mode of operation after the reset at switch-on. We will be using the LCD in 8-bit mode with one line.

#### **Set CG RAM Address**

0 1 a5 a4 a3 a2 a1 a0

This command prepares the LCD for a data transfer to the character RAM by fixing the CG address for the next byte to be conveyed. Bits a0 and a5 form the address to be loaded into the address counter, AC.

#### **Set DD RAM address**

1 a6 a5 a4 a3 a2 a1 a0

This command prepares the LCD for a data transfer to the display data RAM (DD-RAM) by fixing the DD-RAM address for the next byte to be conveyed. Bits a0 to a6 form the address to be loaded into the address counter, AC.

#### **Read Busy Flag**

Read back:

BF a6 a5 a4 a3 a2 a1 a0

(where R/W\=1)

When BF=1, the display is busy processing the previous command, and can not accept a new command or data. When BF=0, the display is ready to accept a new command, or new data. At the same time, the value of the AC is read.

#### **Write DATA to CG or DD-RAM**

Data:

d7 d6 d5 d4 d3 d2 d1 d0  
(where R/W\=0; RS=1)

Depending on whether a CG-RAM address or a DD-RAM address was sent, this command takes a byte into the respective memory area. The mode defined with the aid of the Entry Mode command determines whether the AC is increased or decreased after the byte has been conveyed.

#### **Read DATA from CG or DD-RAM**

Data:

d7 d6 d5 d4 d3 d2 d1 d0  
(where R/W\=1; RS=1)

This command allows bytes to be read from the CG-RAM or the DD-RAM. Before this command, the address must have been conveyed by SET CG ADDRESS or SET DD ADDRESS.

#### **Display test**

The flowchart and assembly listing of a simple LCD test program are given in Figs. 52 and 53 respectively. The function of the program is simple: first, a text is written to the display. Next, the display contents can be shifted to the left or to the right by pressing a key.

The example program on your course disk (XAMPLE12.A51) contains a number of subroutines which you may use in your own programs. The operation of each of these routines will be discussed below.

#### **LCD subroutines**

Subroutine RCOM fetches the state of the LCD into the accumulator. This is achieved by setting Port P2 to the high byte of the display address, 0C01H. The lower address byte is loaded into register R0. Next, a MOVX instruction is used to read out the LCD's BUSY flag, which appears in accumulator bit position 7. As mentioned earlier in this course, Port P2 is used as the high address byte with indirect addressing of the external memory.

Subroutine LCDRDY waits until the LCD BUSY flag is at 0. RCOM is used for this function. LCDRDY is used during the relatively 'slow' LCD initialization commands, to make sure that the LCD has actually accepted the command conveyed.

Subroutine WT1 waits 100 µs. Since most LCDs have a display command execution time shorter than 100 µs, this subroutine may be used to wait for a display command to finish.

Subroutine LCDCOM conveys a command (RS=0) to the display. The addressing method is the same as that used with the MOVX instruction in the RCOM subroutine. The command is followed by a 100-µs delay.

Subroutine LCDCHR sends a character to the character RAM (DD-RAM) of the display (RS=1), and then waits 100 µs. Before calling LCDCHR, it may be neces-

```
***** LISTING of EASMS1 (XAMPLE12) *****
LINE LOC OBJ T SOURCE
1 0000 ; ***** FILE XAMPLE12.A51 *****
2 0000 P2 EQU 0A0H ; for higher address
3 0000 ACC EQU 0E0H
4 0000 Addrhi EQU 0C0H ; MSB of LCD address C001H or C009H
5 0000 addrRS0 EQU 001H ; LCD LS byte of address with RS=0
6 0000 addrRS1 EQU 009H ; LCD LS byte of address with RS=1
7 0000 :
8 0000 ORG 4100H
9 4100 31 2F [2] START ACALL LCDSET ; initialize LCD
10 4102 7B 50 [1] MOV R3,#80
11 4104 7A 41 [1] MOV R2, #'A' ; starting with A
12 4105 EA [1] SETL MOV A,R2
13 4107 31 4F [2] ACALL LCDCHR ; display on LCD
14 4109 0A [1] INC R2 ; next character
15 410A DB FA [2] DJNZ R3,SETL ; repeat
16 410C 31 24 [2] NEW ACALL WAIT ; wait
17 410E 90 C0 00 [2] MOV DPTR,#0C000H ; read keys
18 4111 E0 [2] MOVX A,@DPTR
19 4112 30 E7 05 [2] JNB ACC.7,RIGHT ; test bits 7 and 6
20 4115 30 E6 08 [2] JNB ACC.6,LEFT
21 4118 80 F2 [2] SJMP NEW ; nothing to do
22 411A 74 18 [1] RIGHT MOV A,#0001100B ; shift display S/C=1 R/L=0
23 411C 31 47 [2] OUT ACALL LCDCOM ; send as LCD command
24 411E 80 EC [2] SJMP NEW
25 4120 74 1C [1] LEFT MOV A,#00011100B ; shift display S/C=1 R/L=1
26 4122 80 F8 [2] SJMP OUT
27 4124 :
28 4124 78 FF [1] WAIT MOV R0,#255 ; wait a while
29 4126 79 FF [1] WAIT1 MOV R1,#255
30 4128 00 [1] WAIT2 NOP ; 255*4 microsec
31 4129 00 [1] NOP
32 412A D9 FC [2] DJNZ R1,WAIT2
33 412C D8 F8 [2] DJNZ R0,WAIT1 ; * 255
34 412E 22 [2] RET ; approx. 65500*4 microseconds
35 412F ; LCD driver routines
36 412F 31 41 [2] LCDSET ACALL LCDRDY ; wait for last command to complete
37 4131 74 30 [1] MOV A,#0001100B ; DL=1 N=0 F=0 : 8 bit , one line , 5*7 dots
38 4133 31 47 [2] ACALL LCDCOM ; as command
39 4135 74 0C [1] MOV A,#00001100B ; D=1 C=0 B=0, display on, cursor/flash off
40 4137 31 47 [2] ACALL LCDCOM
41 4139 74 06 [1] MOV A,#00000110B ; I/D=1 S=0 : increment w. display shift
42 413B 31 47 [2] ACALL LCDCOM
43 413D 74 01 [1] MOV A,#00000001B ; reset Display
44 413F 31 47 [2] ACALL LCDCOM
45 4141 31 5A [2] LCDRDY ACALL RCOM ; wait until LCD ready
46 4143 20 E7 FB [2] JB ACC.7,LCDRDY ; bit 7 = BUSY-Flag
47 4146 22 [2] RET
48 4147 :
49 4147 75 A0 C0 [2] LCDCOM MOV P2,#Addrhi ; send command to LCD
50 414A 78 01 [1] MOV R0,#addrRS0 ; RS=low <=> command
51 414C F2 [2] MOVX @R0,A ; output at address P2,R0
52 414D 80 06 [2] SJMP WT1 ; wait
53 414F ; LCDCHR EQU $ ; output character via LCD
54 414F 75 A0 C0 [2] MOV P2,#Addrhi ; MS address
55 4152 78 09 [1] MOV R0,#addrRS1 ; RS=high <=> data
56 4154 F2 [2] MOVX @R0,A ; output at address P2,R0
58 4155 78 32 [1] WT1 MOV R0,#50 ; 100 microseconds
59 4157 D8 FE [2] WT2 DJNZ R0,WT2 ; wait
60 4159 22 [2] RET
61 415A :
62 415A 75 A0 C0 [2] RCOM MOV P2,#Addrhi ; read LCD status
63 415D 78 01 [1] MOV R0,#addrRS0 ; RS=low
64 415F E2 [2] MOVX A,@R0 ; fetch
65 4160 22 [2] RET
66 4161 END
***** SYMBOLTABLE (21 symbols) *****
P2 :00A0 ACC :00E0 Addrhi :00C0 addrRS0 :0001
addrRS1 :0009 START :4100 SETL :4106 NEW :410C
RIGHT :411A OUT :411C LEFT :4120 WAIT :4124
WAIT1 :4126 WAIT2 :4128 LCDSET :412F LCDRDY :4141
LCDCOM :4147 LCDCHR :414F WT1 :4155 WT2 :4157
```

Fig. 53. Assembly code listing of the LCD driver.

sary to set the new RAM address with the aid of SET DD-RAM ADDRESS.

Subroutine **LCDSET** arranges the basic settings of the LCD. First, it calls **LCDRDY** to make sure that all previous commands have been processed. Next, the LCD mode is set to: 8-bit; one line; 5x7 dots. This is done with the aid of **LCDCOM**. After the mode setting operation, the display and the cursor are switched off (lines 39 and 40), and the Shift mode is set (lines 41 and 42). Next, the display is cleared. Since this command may take up to 1.6 ms, it is followed by subroutine **LCDRDY**. Those of you who have studied the listing carefully will have noted a useful programming trick. When 'subroutine1' ends with the instruction sequence

**LCALL subroutine2**  
RET

this can be replaced with a single line instruction

#### LJMP subroutine2

and so make use of the **RET** command of 'subroutine2' (line 52 in the listing). Although this trick saves a few lines of assembly code, it should not be used too often since it easily causes confusion. Here, it is only shown in the interest of the example.

### The main program

The main LCD driver program starts by calling **LCDSET** to set up the display. Next, it writes 80 ASCII characters **ABCDEFGHI....** into the display RAM before entering an endless loop starting at **NEW**. In this loop the state of keys **S2** and **S3** is tested. When one of these is pressed, a left or right Display Shift command is

sent to the LCD via **LCDCOM**. To make sure that the display contents scrolls slowly, subroutine **WAIT** is called in every loop iteration. **WAIT** simply idles 0.26 s (255×255×4 µs).

### Assignment: road diversion

The last assignment in the course is to write a program that displays text and numbers (decimal and hexadecimal) on the LCD. To get started, have a look at the character output routine (V24 serial interface driver) in the system monitor, EMON51, and work on routeing the characters to the LCD.

### Further outlook

This brings us to the end of the 8051/8032 Assembler Course, which has covered the most important programming aspects of the MCS-51 family of microcontrollers. The knowledge gathered during the course should enable you to start your own projects based on one of the processors in the family, or any of the follow-up types that are currently available.

To avoid awkward problems arising later, microcontroller-based projects should have a fairly long planning phase. Always give a good deal of thought to questions such as: which part of the project is realized by software, and which by hardware? How are the necessary hardware extensions connected (ports or bus)? Is battery backup required? Does the processor used have enough speed and computing power to handle the desired task? Are interrupts required to deal with 'fast' events? What are the sub-problems into which the overall program and project can be divided?

Answering the above questions requires quite some experience, which, as we all know, can only be acquired 'the hard way', i.e., by practice. In not a few cases, an apparently simple task may prove quite tangled when looked back upon, or will eventually appear to be over your head. In general, a good start can be made with simple hardware projects that can be built from a couple of TTL ICs: a die, a digital clock, a morse code generator, and so on. The functions of such devices lend themselves very well to software implementations that yield a lot of practical experience.

### Keyboard interfaces

Most hardware projects you may come up with will require some kind of data input device. To offer you some insight into the problems that may crop up, we will briefly discuss six ways of interrogating the state of a keyswitch, i.e., determine whether it is pressed or not. As will become evident, the proposed circuits differ in regard of hardware as well as software.

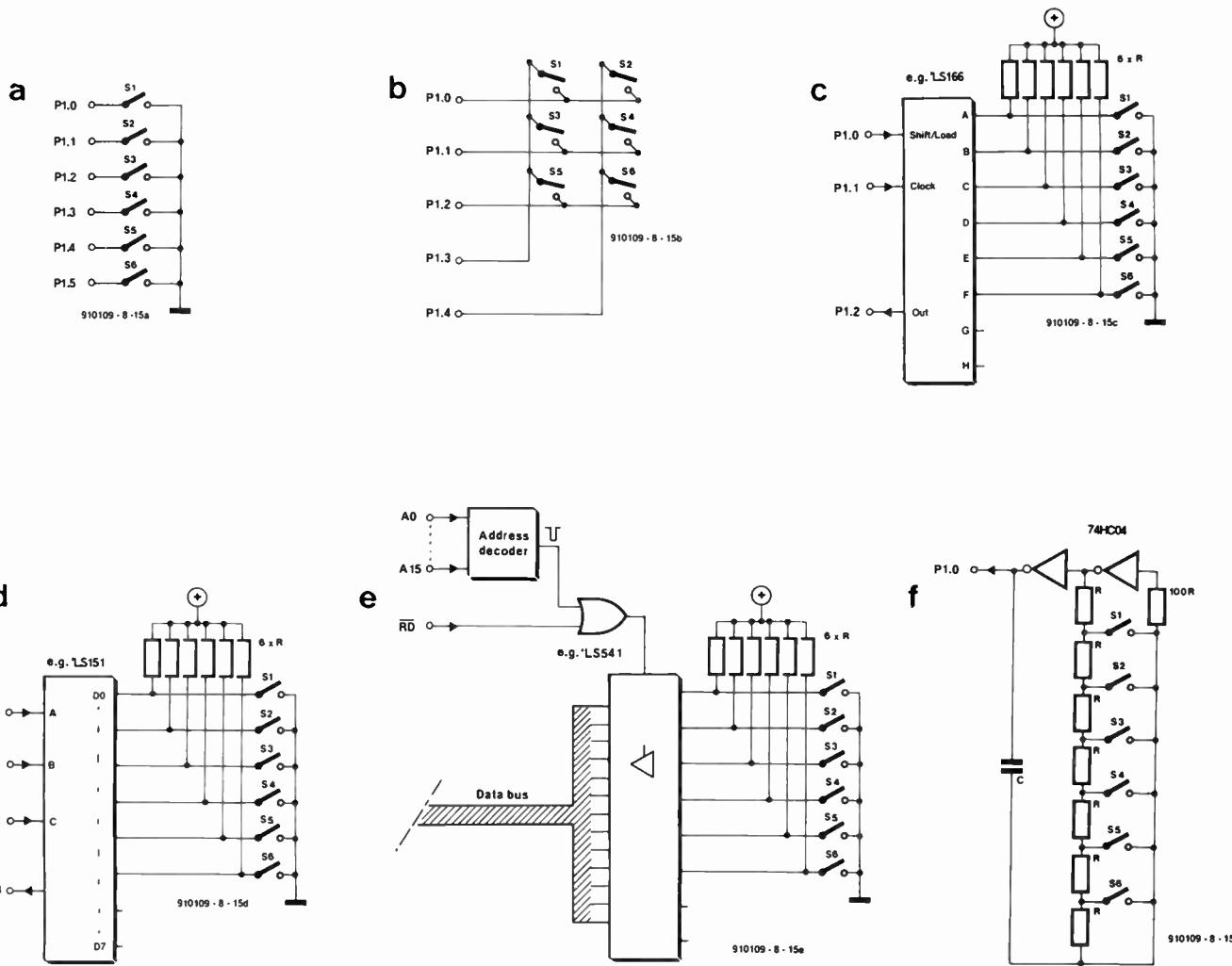


Fig. 54. Six possible ways of connecting switches or a keyboard to the 80C32 single-board computer.

Also, each circuit has its own advantages and disadvantages.

#### a. Direct port connection

The connection shown in Fig. 54a is the simplest of all: each key pressed takes a port line to ground. Current limiting is not even required because the 8051 contains pull-up resistors. The software is simple, too: each switch can be interrogated by a bit test instruction (JB or JNB). The disadvantage of this circuit lies in the number of port lines used. This makes it difficult to implement, say, an ASCII keyboard interface, since there some 60 keys (= port lines) are involved.

#### b. Matrix port connection

In this circuit (Fig. 54b), the keys are arranged in rows and columns that form a matrix. The state of any individual key in the matrix can be interrogated by putting a 'wandering low' on to the row lines. The position of the pressed key is then easily found by scanning the rows. The advantage of the matrix circuit is that a large

number of keys can be read using relatively few lines: only 16 to read 64 keys. There is also a disadvantage: keys may not be pressed simultaneously. However, this may be overcome by fitting decoupling diodes at the matrix crosspoints. Unfortunately, the software for the matrix keyboard is fairly complex.

#### c. Shift register connection

The circuit option given in Fig. 54c requires remarkably few lines. A load pulse is used to copy the switch state into the shift register. Next, the switch state is shifted into the 8051 by eight clock pulses sent via port line P1.2. Note that only three port lines are required, and that the control software is fairly simple. Where more keys need to be read, shift registers may simply be cascaded (connected in series). Note, however, that this results in a longer 'read' time.

#### d. Multiplexed connection

The switch circuit in Fig. 5d requires four port lines, of which P1.0, P1.1 and P1.2

select one of keys S1-S6 via an 8-to-1 multiplexer. The state of the selected switch is fed back to the controller via port line P1.3. This circuit can make do with simple control software, and is simple to turn into a cascade to allow more keys to be connected.

#### e. BUS connection

The circuit drawn in Fig. 5e uses the processor bus to convey switch states. It is particularly useful when there is no free port line available. The keyboard address is selected via an address decoder, and the read signal is used to transfer the state of the keys on to the databus via a three-state buffer. Although the software for this option is relatively simple, the hardware is a bit on the complex side, particularly because we need to connect both the address bus and the databus.

#### f. Multivibrator interface

The last keyboard input circuit to be discussed here, Fig. 5f, works with only one port line. An oscillator based on two in-

verters operates at a frequency which changes when one of the keys is pressed. The 'key identity' is then established by the software, which measures the frequency of the rectangular signal on P1.0. Although this circuit requires the fewest port lines of all variants (except, of course, the bus connection), its suffers from two disadvantages: first, it requires fairly complex software and, second, it is not so easy to extend the number of keys since the frequency differences then become too small to be resolved reliably by the processor.

## The way ahead

To be able to make the best possible use of the experience gathered from simple programs and projects, teach yourself to write program sections in such a way that they can be used later for other applications. In the course of time, this method of working will yield a collection of items that can be used over and over again to build larger programs. Also, the better your documentation on each subroutine, the easier it becomes to fit one into a larger program.

Contrary to common belief, assembly language programming is not all juggling and applying one trick after another. In the author's opinion, assembly language does allow structured programming just like any other higher language, since the program structure is mainly the result of the programmers's thinking. In this context, it is perhaps useful to advise beginners to read as much as possible about assembly language programming.

In spite of the different sources available for learning purposes, assembly language programming is never easy, and is quite demanding in regard of discipline. Fortunately, life is made a little easier by a number of programming tools, which will be discussed briefly below.

## Macro-assembler

During this course we have used a simple assembler which is, none the less, perfectly adequate for the beginner. The professional user with a large budget will, of course, want to use more powerful tools. Well, these are available: a number of commercially available assemblers have 'extra' features such as the ability to handle macros. A macro is a 'shorthand' identifier for a long, frequently used, sequence of instructions or other texts. The assembler recognizes the macro identification, and automatically translates it into the text it represents.

Apart from this possibility, many assemblers allow the separate assembly of chunks of assembly code, which can be 'stitched together' later, along with items from a subroutine library. This is achieved with the aid of a linker. Although working with 'bits and pieces' is most useful when

building a fairly large program, the hobbyist will often be able to manage quite well without a linker utility.

Those of you who find assembly language programming too arduous may avail themselves of higher programming languages such as C or Forth, for which a number of 8051 compilers and interpreters are available, albeit at a cost.

## 8051 emulators

8051 emulator programs are available that allow 8051 software to be tested by quasi-running it on a PC. Some emulators allow the program under test to be executed in single step mode, while the register contents are displayed. As such, emulators are excellent tools to trace and solve software problems and errors. They, are, however, less useful when the problem is caused by incompatibility between software and hardware. The limitations of the emulator are, therefore, often keenly felt when the program is used to 'mimic' a microcontroller connected to hardware extensions (peripherals). Fortunately, emulators come at quite low prices, which makes the decision to buy one, and so extend one's programming tools, a little easier than with an expensive assembler. For the beginner, too, an emulator can be quite useful since the workings of individual instructions can be traced with great accuracy on the PC screen. However, an EPROM emulator will be much more useful when it comes to the real thing, i.e., testing the real program in actual use.

## EPROM emulators

During this course, all programs are run under the control of the EMON51 system monitor, and loaded into RAM. In many cases, however, it is desirable, from a point of view of cost, to omit a RAM, and run the program from an EPROM. To complicate things even further, such a system may not even have a serial interface. The absence of a RAM and a serial interface would appear to limit the possibilities of testing the software under realistic circumstances, as no data can be downloaded to, or called back from, the system under test. In these cases, an EPROM emulator can be great help, since it allows the most up to date version of the program (in object code) to be downloaded into the system. An excellent design for an EPROM emulator is described in Ref. 1.

## In-circuit emulators

An even more difficult situation arises when an 8051 with internal ROM is to be used in a project of which the software is as yet under development. Obviously, an EPROM emulator is useless here, simply because there is no EPROM. In-circuit emulators such as the one described in

Ref. 2 simulate the operation of the 8051 CPU running a program selected by the user. An in-circuit emulator is also a fine tool to track down hardware errors caused by, for instance, timing problems.

## Follow-up processors: 80535 etc.

Although this course may have been your first acquaintance with the 8051 family of microcontrollers, remember that these devices are relatively old already. Their success, however, is mainly due to their having been endowed with the status of 'industry standard'. Whatever that may mean, these processors are found in countless applications. However, when deciding to develop a microcontroller application, do not forget to have a serious look at some of the derivates of the 8051, which include some very interesting processors like Siemens' SAB80C535 and SAB80C537, OKI's MSM80C154, and Philips Components' PCB83C552. These processors are basically upwards compatible devices, which means that they can do everything a 8051 can, when the same software is used.

The follow-up processors have extended features such as additional timers, on-chip A-D converters, an on-chip watchdog timer, more ports and enhanced (faster) arithmetic units. Our course assembler supports these new features because they are accessible via additional SFRs. An 80C535 controller board will be published in a forthcoming issue of *Elektor Electronics*.

## Finale: small hardware projects

Although this course is now finished, it is really open-ended since there is no limit to what you can program on an 8051. We have up our sleeve a number of small projects that serve to show you the diversity of the possible applications. The projects themselves will be small, and based on very simple hardware. The idea is not so much to elaborate on the project itself, but rather to demonstrate the wide variety of applications you can develop once the basics of assembly language have been acquired. If you have ideas, let us know! ■

### References:

1. "EPROM Emulator II." *Elektor Electronics USA*, September 1992.
2. "8751 Emulator." *Elektor Electronics USA*, March 1992.

# LETTERS

## FOUR-TERMINAL NETWORKS

I enjoyed reading Mr. Knight's two-part article entitled "Four-Terminal Networks," (EEUSA 10-11/91) but I have some comments.

1. On page 48 (10/91) of "Finding the Attenuation," paragraph 2 should read: "A desired value of  $R_o$  can be obtained with numerous combinations of  $R_1$  and  $R_2$  depending on the value of the attenuation,  $N$ . Looking at Fig. 7, for instance, both sections shown have a characteristic resistance of  $R_o = 30\Omega$  (check on this for yourself!), but the network on the right will provide a greater degree of attenuation than the one on the left. A desired value of  $N$  can be obtained with numerous combinations of  $R_1$  and  $R_2$ , depending on the  $R_o$  chosen. If, for instance, in Fig. 8,  $R_1 = 20\Omega$ ,  $R_2 = 12.5\Omega$ , and  $N = 14\text{dB}$ ,  $R_1 = R_o = 30\Omega$ ; if  $N$  is kept at  $14\text{dB}$ , and  $R_1$  is made  $80\Omega$  and  $R_2 50\Omega$ ,  $R_1 = R_o$  becomes  $120\Omega$ .

2. Many attenuator designs are tabulated in the literature for various values of  $N$  for a specific value of  $R_o$ . For instance, if  $N = 20\text{dB}$  and  $R_o = 500\Omega$ ,  $R_1 = 409.1\Omega$  and  $R_2 = 101.0\Omega$  for the symmetrical T attenuator. For any new  $R_o'$  requiring  $20\text{dB}$ ,  $R_1' = R_1(R_o'/500)$  and  $R_2 = R_2(R_o'/500)$ .

3. There should have been a bibliography and/or references of related material listed for interested parties, since I surmise that your readers range from hobbyists to technicians to engineers.

Joseph A. Lutowski  
USA

*Steve Knight replies:*

1. I think Mr. Lutowski has simply rephrased the paragraph without affecting its content. The object was to show that different attenuations can be obtained for identical values of characteristic resistance  $R_o$ . The actual attenuations were not stated, but this was not necessary at this point: a basic fact was being stated.

2. I agree that such tabulated scales are to be found in a number of reference books and are useful to a designer. There was obviously no space in a short article to provide a list. The two expressions Mr. Lutowski gives for any alternative  $R_o$  were not included for the same reason.

3. It is always a problem providing bibliographies, especially for short articles, and again there is a matter of space. A list of British references might not have been suitable for the

many overseas readers, while a list of interest to Mr. Lutowski might not have been so to non-American readers. For those reasons, I decided to omit any references from the article.

*Editor replies:*

*I am pleased to read that Mr. Lutowski enjoyed these two articles; they were presented in as simple a manner as possible in an effort to clarify a subject that is difficult for hobbyists and technicians to grasp.*

## BUILD A CD PLAYER

I read with great interest the project "Build a Compact Disk Player" in the January issue and look forward to the promised "add-ons."

I should be grateful if, in addition to the optical output module, you would consider the design of a variable pitch control (to increase and decrease the pitch of the music by, say,  $\pm 12\%$ , and the addition of a cueing system. Both of these features can be found on the Revox/Philips and Technics professional broadcast players and would be useful in the Hospital Radio or Community Radio environment. I appreciate that this request is bound to anger hi-fi purists, but some of us get our enjoyment from playing music to others—in my case with hospital radio.


Martin Clarke  
Great Dunmow, United Kingdom

*Editor Replies:*

*The first add-on for the CD player (which can also be used with other equipment) is the AF digital-to-analogue converter published in our July-October 1992 issues, which we trust will be of interest to many readers. As far as pitch control is concerned, have you considered "Pitch Control for CD Players" in our December 1988 issue which, according to our Design and Development Department is still going strong. (Photocopies of the December 1988 article are available for \$5 each from the Old Colony service department.—Ed.)*
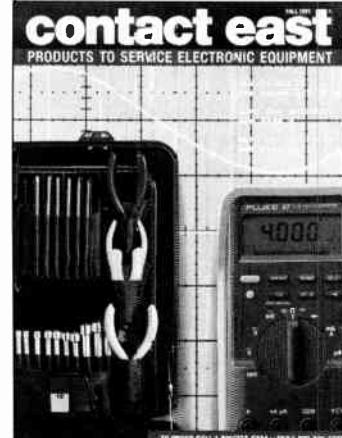
## COMPUTERSCOPE

Although I do not build the projects you publish, I have learned a lot from them; you are streets ahead of the competition. My scope recently died and as I have a 286, 20MHz PC,



## FREE CATALOG TEST INSTRUMENTS & HARD-TO-FIND TOOLS

Packed with over 10,000 quality products for testing, repairing, and assembling electronic equipment. A full selection of test instruments, power protection equipment, precision hand tools, tool kits, soldering supplies, and much more. Products are shown in full color with detailed descriptions and pricing. All products come with a 100% satisfaction guarantee. SAME-DAY shipment program.

In a hurry to receive your catalog?


Call (800) 225-5370

In Massachusetts call (508) 682-2000


Contact East, Inc., Dept. R497

335 Willow St., No. Andover, MA 01845

## ELECTRONIC ENCLOSURES

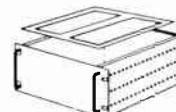

Rack Mount

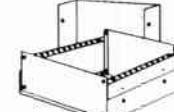


Split Case

Complete line in Aluminum, Steel & ABS; also Hardware, Silkscreening, Hand Tools, Custom Fabricating

Call for our FREE Full Color Catalog  
(800) 800-3321 (216) 425-1228 Fax



Cage & Preamp  
Enclosures

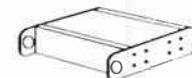

Universal



ABS



Knobs  
& Parts

## Project Pro

1710 ENTERPRISE PKWY TWINSBURG OH 44087

I thought a computer scope would be good, but the one you published in 1986 has no software for a PC and it has a small bandwidth. Would it be possible for you to update that design to include more advanced technology with a bandwidth of, perhaps, 5-10MHz and include PC software? Or, maybe produce a new design from scratch?

Also, would it be possible to run a course on programming in assembly language for, say, Z80-based hardware and software, as 8051s don't grow on trees, you know.

A. Sutton  
Leicester, United Kingdom

*Editor replies:*

We have asked our design department, as well as some of our regular freelance contributors to report on the possibility of updating the "Computerscope" series published in our September (EEUK 9/86 p. 60) and October (EEUK 10/86 p. 41) 1986 issues. Their findings will be published in this column in a few months' time.

Your comments on the 8051 in comparison with the Z80 have been noted. Bear in mind, though, that our research, and that of our associate companies world-wide, indicates waning interest in Z80-based equipment. Moreover, we do not get many offers, if any, from free-lance contributors on this type of equipment. Nevertheless, there is a two-part article on a "Multi-purpose Z80 card" in this (EEUSA 6/92, p. 41) and our May (EEUSA 5/92, p. 14) issues.

As to your remarks regarding the price of the 8051, why not use a 8032? The course is geared to both devices without any reservations, but the 8032 is considerably cheaper than the 8051.

---

### GROWING DISSATISFACTION

---

As a hobbyist, I read many magazines with growing dissatisfaction. Although many projects are of a stand-alone nature, computers and digital equipment cry out to be connected to each other in clever ways. But everyone had different design ideas on how to make the computer. *ETI* had the 68000-based Cortex, *Wireless World* had the Z80-based SC84, *Elektor* had the 6502-based Junior, and so on. Noting that people like souping up computers (like cars), some sensibly had expansion buses: Quarndon Qbus, Tangerine Tanbus, Interak, Acorn Atom bus, BBC Micro, ZX81, Spectrum, PCbus; unfortunately, all completely incompatible with each other. When the product became obsolete, so did the add-ons.

I worked as a technical author, writing manuals for the makers of the STEbus, for four years. The STEbus has solved a lot of problems for industry. Why doesn't the am-



## LETTERS

ateur world hear about industrial solutions?

Computers exist to save human time. It is a waste of time re-inventing the wheel. You could design, build and debug your own computer from scratch, but it would swallow vast amounts of time.

If you really must publish designs for single-board computers, make it a STEbus one. Your readers can then buy hundreds of boards off the shelf from a range of suppliers: from an 8031 to an 80386, digital I/O, analogue I/O, SCSI, Ethernet, modems, power supplies, signal conditioners, and many more.

Keith Howell  
Cambridge, United Kingdom

*Editor Replies:*

Since I am a great advocate of standardization on a world-wide basis (particularly where computers and television are concerned), I agree with you and have passed your letter to our chief design engineer. Many discussions will, no doubt, ensue!

---

### S-VHS/CVBS TO RGB CONVERTER

---

A colleague and I successfully built two working versions of the S-VHS/CVBS to RGB converter. Currently you are running a series on ELV's Audio Video Processor Type AVP300.

I wish to upgrade the PAL decoder TDA 4510 (on the converter) to the multi-standard TDA 4650 for PAL/SECAM operation on satellite channels. Using the circuit of Fig. 4 in the June '92 issue (7.15MHz crystal not fitted) we replaced the TDA 4510 chip. There was no problem in decoding PAL, but alas no SECAM, even if the (Mullard) TDA 4650 was forced into the SECAM mode by hauling Pin 27 above 9V. Replacing the chrominance filtering by a filter from a TDA 3591 based SECAM surplus board supplied by SENDZ again allowed us to decode PAL, but no adjustment of R102 would allow us to decode SECAM. Note that the TDA 3591 board when supplied with a sandcastle pulse would successfully detect on Pin 6 (of the TDA 3591) the presence of a SECAM signal.

Such a project would be of interest to many of your readers who have built, or are considering building, the original project; could you possibly breadboard the modification, or at least comment on any problems envisioned with the design? If it is purely a set-up problem, is there a simple adjustment procedure

using a signal generator (with NBFM modulation) as opposed to requiring a SECAM video TV Signal Pattern Generator?

N.G. Douglas  
Burnham, United Kingdom

*Editor Replies:*

Your letter has been passed to our Design and Development Department, who have taken up the matter with Mr. Reelsen (since none of the prototypes are in our possession). Unfortunately, at the time of preparing this issue of the magazine (mid-September), they have no clear solution to the problem. As soon as we have, we shall be in direct personal contact with you. Sorry for the delay.

---

### FREEWAY CORDLESS PHONE

---

I wonder whether any fellow readers can help. Recently my (owned, not rented) Freeway phone was disabled by a nearby lightning strike. Trying to get it repaired has proved very difficult.

In the end, I attempted the repair myself and after hours of work finally found one dud transistor (No. 15, a 2SA1015) in the base unit. Replacing this has restored all functions but one, namely ringing to indicate an incoming call. Outgoing calls are OK, and if the phone is picked up after another parallel phone rings, the call is there. The base-to-handset paging system works, so I believe the remaining fault must be very minor, even though I have been totally unable to locate it.

I understand this model of phone is particularly susceptible to lightning damage. Can anyone help; is there a sympathetic telephone engineer out there?

I noticed several mistakes in the July/August issue, particularly the circuit diagram given for the "Audible Fluid Level Indicator" on page 63 is the same as that for the Smartec temperature sensor on page 79.

I.M. Tasker  
Grantham, United Kingdom

*Editor Replies:*

We regret that of the various engineers and technicians we have approached, none has any experience with Freeway phones; we hope, therefore, that one of our readers may be able to help—sorry we cannot in this instance! The few regrettable mistakes in the July/August issue were caused by a mix-up in photographic plates between prepress and printers—sorry! They have been put right in the September issue (see page 58).


# CLASSIFIEDS

## TEST EQUIPMENT

**FEITEK HAS** the test equipment you want at reasonable prices. We buy, sell, and trade HP, Tek, G.R., etc. Call or FAX Monday thru Friday 9 to 5, (314) 423-1770, or write to **FEITEK**, Box 3423, St. Louis, MO 63143. T11/92

**OSCILLOSCOPES** For Sale: Hewlett Packard, Ballantine, Dumont and Tektronix, 2MHz to 50MHz, \$65 to \$200. Also in stock, extensive inventory of other types of test equipment. **AIRFIRST**, 15308 Robert Ave., Oklahoma City, OK 73165, (405) 794-7280, (405) 282-8573. 11/92

## Prototype it..... FAST!

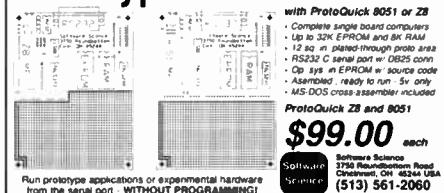

## COMPUTER SOFTWARE FOR SALE

**PCB LAYOUT & ELECTRONICS IBM SHAREWARE PROGRAMS** \$3 for S&H for 2 disks full, plus **DISKALOG**, plus free \$3 gift certificate. **AMERICAN SOFTWARE**, Suite M-17, POB 509, Roseville, MI 48066-0509. T3/93

## NECTA IS HERE

### FINALLY AN ASSOCIATION FOR YOU

WORKING TECHS/ STUDENTS/ ENTHUSIASTS

ANNUAL CATALOG GOODIE PACK DISCOUNTS CONTESTS  
BI-MONTHLY NEWSLETTER CAREER GROWTH, TECH TIPS,  
COMPANY PROFILES, SOUND-OFF COLUMN, NEWS

### CALL OR WRITE TODAY

NATIONAL ELECTRONICS & COMPUTER TECHNICIANS ASSOC  
8401 GREELEY BLVD. SPRINGFIELD, VA 22152 703-569-3549

## KITS

**KITS! FREE** catalog of fantastic electronic products that you can build. Microprocessors, test instruments, digital speech and more! **LNS TECHNOLOGIES**, 20993 Foothill Blvd., Suite 307E, Hayward, CA 94541-1511. T11/92

## YOU'VE HEARD ABOUT THEM WE'VE GOT THEM HERE !

**BOOSTER FOR MINIATURE TRANSMITTERS**  
RF POWER AMP BOOSTS 88-108MHz. MINIATURE  
FM TRANSMITTERS' RANGE - GUARANTEED!  
COMPLETE KIT W/SCHEMATICS IMPC-RE2 \$26.00

E-Z TUNE (25 TURN) STABLE HI-FI FM MIC - SURF. MNT.  
(MEDIUM RANGE, SUPER SENSITIVE) IMPC-RMS \$44.00

LONG RANGE FM MIC - SMALL BUT VERY POWERFUL  
1" SQ., NON-SURFACE-MOUNT KIT IMPC-RMS2 \$39.00

TOUCH TONE DECODER DISPLAYS PHONE NUMBERS  
AS HEARD FROM RADIO TAPE OR PHONE LINE.  
BUILT-IN 200 DIGIT MEMORY IMPC-TDD \$169

## International MicroPower Inc.

65 Palm Drive + \$3.50 S.H.  
Camarillo, CA 93010  
**1-800-992-3511** (\$7.00 IFC.O.D.)  
MC or VISA Accepted | CA residents add Sales Tax

## CLUBS

**RADIO ASTRONOMY.** For information: Write "Society of Amateur Radio Astronomers," Vincent Caracci, 247 N. Linden St., Massapequa, NY 11758. 11/93

## ELEKTOR ELECTRONICS CLASSIFIED ORDER FORM

### RATES

75 cents per word. Deduct 10% for a 6x contract. \$10.00 minimum for charge card orders.

### HOW TO COUNT WORDS

**Definition of a word:** A series of letters with a space before and after. Count words, not letters. Hyphenated words count as one word (i.e. first-rate).

**No ads will be taken over the telephone. No questions taken over the phone. Prepayment must accompany ad. No Billing.**

### Categories (please check just one)

- Audio for Sale
- Books & Periodicals
- Business Opportunities
- Cable & Satellite
- Conferences, Fairs, Seminars
- Components, Parts & Supplies
- Computer Hardware For Sale
- Computer Software For Sale
- Computer Systems For Sale
- Education
- Home Automation
- Kits
- Miscellaneous

### HOW TO SUBMIT YOUR AD

Type or print your ad clearly on form. Check the category you wish your classified to appear under. Indicate number of insertions. Enclose check with order or include credit card number and expiration date.

### Mail to:

Elektor Electronics, Classifieds, PO Box 876, Peterborough, NH 03458.

- Clubs
- Wanted To Buy

**Ads in these two categories are free to subscribers.** Attach your mailing label to form for verification. Limit 50 words.

1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40
41	42	43	44	45	46	47	48	49	50

Please run this ad \_\_\_\_\_ times. EXP. DATE \_\_\_\_\_

Advertisement will be inserted in first available issue.

- Check/Money order enclosed
- Please charge to my Master Card/Visa

NAME	COMPANY
STREET	
CITY	ST ZIP
PHONE NUMBER	

# CLASSIFIEDS



**DIGITAL C.L. METERS.** 0.001pF and 0.001 $\mu$ H resolution,  $\pm$  0.3% basic accuracy. 4-digit LED display, test frequency 1MHz down to 500Hz sinewave, many more features, several models to chose. Portable, accurate instruments made in the USA. 30 days/3 years warranty. Prices start from \$345.00. For more info call 607-659-3030 or write to: TBE Electronics, P.O. Box 42, Candor, NY 13743.

## BOOKS & PERIODICALS

**VIDEOPHOTOCIPHER III**/Satellite/Scanner/Cable/Amateur/Cellular/Repair Manuals, Modification Books & Software. Catalog—\$3. **TELECODE**, PO Box 6426-EK, Yuma, AZ 85366-6426.

T1/93

**MICROCONTROLLER** applications notes/software catalog. Temperature logger plans, \$10 U.S. **TENSOR**, 342 Roberta St., Ontario, Canada P7A 1A3. T11/92

**FREE CATALOG**, laser, optics, laser power supplies, plans, light show. Write **MKW INDUSTRIES**, 198 Lewis Ct., Corona, CA 91720 or call toll free 1-800-356-7714. 4/93

**PHOTOFAXES:** Folders and specialized books; AR, CB, CM, HTP, MHF, SD, TR, TSM, VCR. **A.G. TANNENBAUM**, PO Box 110, E. Rockaway, NY 11518, (516) 887-0057. 11/92

## PRINTED CIRCUIT KIT

ER-4 PHOTO ETCH™ kit lets you copy art from this magazine onto your PC board. Includes everything but exposure bulbs. Shipped UPS to your street address for \$43.00.

ER-19 EXPOSURE BULB SET FOR ER-4. Contains 3400K reflector flood and 4800K long wave UV lamp for ordinary 120V socket. Shipped UPS to your street address for \$18.45.

**FREE CATALOG** of dry transfers and PC supplies. Write or phone **DATAK**, 55 Freeport Blvd., Sparks, NV 89431. 702-359-7474 FAX: 702-359-7494

## COMPUTER HARDWARE FOR SALE

**CHRISTMAS CHIPS** & other Music ICs. Musical Xmas lights, & more. 5 chips/\$11 postpaid. Outside USA please add 2 ounces 1st class postage to your country. SASE for info. **THUMB ELECTRONICS**, Box 344E, Marysville, MI 48040.

T12/92

**NEW, USED** (guaranteed) and "AS IS" Radio Shack items. Computer hardware, software, books, "force-feed," R/C cars, etc. 20% to 80% off list. **B & B ENTERPRISES**, 2028 S. Pulaski St., Dept. EL, Baltimore, MD 21223. (Please send \$2 for list.) 11/92

## "DISGUISE" AC WALL OUTLET

**NEW!** \$99.00 ppd. **FM TRANSMITTER KIT** Looks and functions like a common outlet; uses power line for power and antenna (no batteries needed ever!) **SURVEILLANCE CATALOG** ....\$5.00

**CALL IDENTIFIER** displays callers phone number, stores phone number with date & time of call....\$59.95ppd.

**FDT** P.O. Box 337, Buffalo, NY 14226 (716) 691-3476

## PLANS & SCHEMATICS

**FLAME SPEAKER.** Finally, a speaker with no moving parts! Omnidirectional sound, with higher frequency response than conventional loudspeakers. No diaphragm or voice coil. Plans, \$10. **ELECTROMAN**, PO Box 24474, New Orleans, LA 70184. 11/92

**RECEIVING TUBES**  
OVER 3000 TYPES IN STOCK!  
Also hard-to-find transformers, capacitors and parts for tube equipment.  
Send \$2.00 for our 32 page catalog.

**ANTIQUE ELECTRONIC SUPPLY**  
6221 S. Maple Ave. • Tempe, AZ 85283 • 602-820-5411

## RACK AND CHASSIS BOXES

RACK BOXES				CHASSIS BOXES			
MODEL	W	D	H	PRICE	MODEL	W	H
MC-1A	4	3	2	\$17.95	MC-1A	4	3
MC-2A	6	3	2	17.85	MC-2A	6	3
MC-3A	8	3	2	10.05	MC-3A	8	3
MC-4A	4	4	3	17.85	MC-4A	4	4
MC-5A	6	4	3	18.05	MC-5A	6	4
MC-6A	8	4	3	22.05	MC-6A	8	4
MC-7A	4	7	4	18.05	MC-7A	4	7
MC-8A	6	7	4	22.05	MC-8A	6	7
MC-9A	8	7	4	24.15	MC-9A	8	7

NOT SHOWN

We also accept VISA and MASTERCARD. ORDER DIRECT FROM THE FACTORY. ON PREPAID ORDERS SHIPPED UPS GROUND NO CHARGE SECOND DAY AIR \$10.00, NEXT DAY AIR \$20.00

**SEE COM** SESCOM INC, 2100 WARD DRIVE HENDERSON, NV U.S.A.  
800-544-4442 (ORDERS) 800-634-3457 (TECHNICAL HELP)  
702-565-3400 FAX 702-565-4828

## DON'T BOTHER ME!

**CALLER I.D.** shows AREA CODE & NUMBER of person calling YOU. **CALLER I.D.** is SWEEPING THE COUNTRY. You don't have to answer that phone until you know who is calling you!

Attractive, White, 4x6-inch model, LCD display, stores 14 most-recent calls w/date - time IMC-14 \$65.00 Extra-Memory model stores 50 calls IMC-50 \$79.00

Computer-capture model, small circuit card. SCHEMATICS & PARTS LIST INCL. Ready-to-go. Uses disk to save calls, computer screen "pop-up" displays calling number, date, time. IMC-100 \$45.50. Unit needs software running on PC-compatible. Write your own, or buy ours IMC-SW 7.50

DESIGN YOUR OWN - Caller I.D. guidebook - 56 pages - theory and practice. 5 pg.s schem's, 3 pg.s timing-waveform diag's IMPC-BK 18.50 (discount if purchased w/other prod. 13.95)

Caller I.D. service not yet available everywhere. Check with your local phone company.

## International MicroPower Inc.

65 Palm Drive  
Camarillo, CA 93010  
+ \$3.50 S.H.  
1-800-992-3511 (\$7.00 F.C.O.D.)  
MC or VISA Accepted | CA residents add Sales Tax

## INDEX OF ADVERTISERS

All Electronics Corporation	4	Tucker Electronics	6
Audio Teknology Inc.	CV IV		
Baylin Publications	4		
BG Micro	CV III		
Contact East	49		
Deco Industries	6		
Meadowlake Corporation	6		
Micro Video Products	4		
Mouser Electronics	4		
National Scanning Report	7		
OLD COLONY SOUND LAB Books	53, 54		
Elektron Item Tracer	21		
EPROMS, etc.	53		
Front Panel Foils	53		
Parts Sources	6		
Printed Circuit Boards	53		
Software	53		
Project Pro	49		
Radio Shack	CV II		
Spy Supply	6		
TANner Electronics	7		
Tapto Corporation	5		
TECI	25		
Advanced Electronics	12		
Allied Electronics	13		
Antenna Specialists	10		
Antona Corp.	12		
B&B Electronics	12		
B + K Precision	12		
Bellcore	13		
Circuit Works	12		
Communications Specialists	13		
Digital Interactive	12		
Electronic Distributors	10		
Electronic Equipment Bank	13		
Fieldpiece Instruments	12		
Logical Systems Corp.	13		
MFJ Enterprises, Inc.	10		
Mouser Electronics	13		
Optoelectronics	13		
Remote-Console	10		
Speaker Designer	10		
The Saelig Co.	13		
Women's Technet	10		



# TERMS OF BUSINESS

## PRICING

Prices, except as noted, include shipping in the continental USA. The minimum order is \$10. A \$2 service charge will be added to orders of less than \$10. Prices are subject to change as our costs change. WE RESERVE THE RIGHT TO MAKE PRICE CHANGES WITHOUT NOTICE.

## TELEPHONE ORDERS

Telephone orders are welcome between the hours of 9:00 a.m. and 4:00 p.m. EDT, Monday-Friday. Orders for parts are to be made on the ORDER FORM provided. Payment for telephone orders is by MC/VISA only. Our TELEPHONE ORDER NUMBER IS (603) 924-6371 or 924-6526. Our answering machine for MC/VISA orders during non-business hours is (603) 924-6371. FAX: (603) 924-9467 (24 hours).

## PAYMENT

All remittances MUST BE IN US FUNDS DRAWN ON A US BANK. Payment for telephone orders must be made by MasterCard or VISA. Mail order payment may be made by MC/VISA, money order, cashier's check or personal check. If payment is made by personal check, allow up to 2 weeks for clearance before order is shipped. Should check be returned for any reason, there will be a \$10 charge.

## SHIPPING

Unless noted, freight is prepaid by Old Colony. All orders shipped USPS first class mail or by UPS. Allow two to three weeks for delivery. Please inquire about appropriate funds for special handling (UPS next day or second day). UPS requires a street address. If you cannot receive UPS delivery, please in-

clude an extra \$2 for insured service via Parcel Post. We cannot accept responsibility for safety or delivery of uninsured Parcel Post shipments. **Absolutely no COD shipments.**

## BOOKS, RECORDINGS, CDs, and SOFTWARE

The shipping/handling charge for the US is \$2.00, plus 75¢ each additional item. In Canada, please add \$4.50 for the first item, 75¢ each additional. For orders to be shipped outside North America, add 20% to the total order to cover shipping. **No returns.** According to the Connecticut Dept. of Revenue Services, Regulation #27, Section 12-426-27, in order to sell software to residents of Connecticut, we must register with the department as well as collect taxes for the state from the purchaser. We regret to inform customers that we will not sell software to anyone from Connecticut. ■

# BOOKS FROM ELEKTOR ELECTRONICS USA

## 301 CIRCUITS

This book follows the theme of the first in this series, *300 Circuits* (now out of print). It contains over 300 assorted circuits first published in the 1979, 1980, 1981 summer issues of *Elektronik Electronics*.

The circuits range from the simple to the more complex and are described and explained in straightforward language. The book is a comprehensive source of ideas and construction projects for anyone interested in electronics.

**ISBN 0-905705-12-2**  
**BKAA11      Price \$12.50**

## 302 CIRCUITS

The popularity of this book is shown by its having been reprinted no fewer than three times. It offers a selection of the most interesting articles from the 1982, 1983, 1984 summer issues of *Elektronik Electronics*.

In it you will find circuits for audio and video; car, cycle, and motorcycle; home and garden; receivers and aerials; hobbies and games; measuring and testing; oscillators and generators; current sources and power supplies; microcomputers and music electronics; and a miscellany of other interesting subjects.

**ISBN 0-905705-25-4**  
**BKAA12      Price \$12.50**

## 303 CIRCUITS

Like its predecessors, *303 Circuits* offers a comprehensive collection of practical ideas, concepts, and developments in the gamut of electronics. Unlike its predecessors, the book is arranged in 11 subject sections to make it easier for the reader to find that long-sought circuit.

In well over 300 pages, the book offers 32 Audio and Hi-Fi projects; 14 circuits for Car and Bicycles; 43 Computer & Microprocessor circuits; 11 Electronic projects; 24 HF and VHF circuits; 16 circuits for a number of hobbies and pastimes; 54 projects for Home and Garden; 29 Power Supply circuits; 29 circuits for Test and Measurement equipment; nine TV and Video projects; as well as 42 Design Ideas.

**ISBN 0-905705-62-2**  
**BKAA13      Price \$15.90**

## 304 CIRCUITS

The latest in *Elektronik*'s famous "300" series, BKAA18 contains 304 innovative circuits and descriptions broken down as follows: 36 audio/video, 19 high frequency, 36 hobby, 36 home and garden, 9 music/electronics, 32 computer/microprocessor, 19 generator/oscillator, 33 test and measurement, 30 power supply, 13 car electronics, and 41 miscellaneous. Arranged by subject for ease of use.

**ISBN 0-905705-34-3**  
**BKAA18      Price \$19.95**

## DATA SHEET BOOK 2

Like its predecessor (now out of print), this book offers concise, relevant, and rapidly accessible information, which is both practical (e.g., the pin-out of a device) and informative.

The book contains data on integrated circuits as well as on discrete transistors and diodes. Moreover, it gives an introduction to fast (HCMOS) devices and a review of the new symbolic logic as laid down in British Standard BS3939: Section 21 (IEC Standard 617-12).

The final part of the book deals with a number of computer chips, such as memory devices (including programming information for these) and I/O circuits. This section also includes data on a number of non-digital discrete and integrated devices, such as op amps, as well as on some microprocessor peripherals (e.g., the 6522 VIA, the 6580 ACIA, and the 8355A PPI).

**ISBN 0-905705-27-0**  
**BKAA14      Price \$16.50**

## DATABOOK 3: PERIPHERAL CHIPS

This book lists the most important design data of peripheral chips whose type numbers and functions relate them unambiguously to a microprocessor in the same family. All listed devices form part of families based on widely used microprocessors or microcontrollers. Their most evident application will therefore be in conjunction with the associated microprocessor. This should, however, not be taken to mean that a peripheral cannot be used in another application. Far from it, as witness the familiar type MC146818A real-time clock and the type MC6845 cathode-ray tube controller. It deserves a place on the bookshelf of anyone concerned with the design, maintenance and servicing of microprocessor-controlled electronic equipment.

**ISBN 0-905705-30-0**  
**BKAA15      Price \$17.95**

## MICROPROCESSOR DATA BOOK

This book has come about because of a need by *Elektronik Electronics* engineers, technicians, and editorial staff of a ready reference work on the most important microprocessors. This implies that it does not only contain information on the latest devices, such as the transputer, but also on older, well-established types, such as the Z80 and the 6800.

A general description, hardware block schematic, software structure, DC characteristics, and instruction sets are given for over 70 microprocessors. To prevent the book from becoming unwieldy (and to keep costs down), timing diagrams and AC characteristics have, however, been omitted. The detailed information on all manufacturers mentioned will, however, enable any additional information to be obtained quite readily.

Included in the book are, among others, the 68000 series; the 6502 family; the Z80, 8080, and 8085; Intel's 8086, 80186, 80186, 80286, and 80386; the NS32XXX series, and the IN-MOS transputers.

**ISBN 0-905705-28-9**  
**BKAA16      Price \$17.90**

## DATABOOK 4: PERIPHERAL CHIPS II

This further volume in *Elektronik Electronics'* Microprocessor Data Book series deals with general peripheral chips that, at least as far as their type-coding is concerned, do not belong to a specific family of microprocessors. There are so many of these, however, that only a portion of them can be dealt with in one book. Those contained in this collection have been chosen carefully on the basis of their practical application and frequency of use. Complete data are given for coprocessors from the 80 series (AMD, Cyrix, ITT, Intel, Weitek); real-time clocks from MEM, OKI, Statek, National Semiconductor, and Dallas Semiconductor; transmitters and receivers of serial interfaces RS232, 422, 423, 485 from Motorola, Newport Components, Maxim, Texas Instruments, National Semiconductor, Dallas Semiconductor, and Linear Technology; UARTS, DUARTS, and QUARTS (i.e., programmable ICs intended for data transfer); and the CS8221 set of ICs from Chips & Technology that are used in a great number of PC mother boards (also included in the data sheet of associated software LIM 4.0 for the management of the Extended Memory System).

Apart from the actual data, the book contains much other useful information, such as comparisons between and second sources for all important IC families; addresses of manufacturers and their representatives; and overviews of all peripheral chips (including many that could not be included in this book) that are available from various manufacturers.

**ISBN 0-905705-32-7**  
**BKAA17      Price \$17.95**

## DATABOOK 5: APPLICATION NOTES

This book presents a series of application notes and design briefs that cover a wide variety of subjects. Apart from a number of applications related to specific components, the book also includes articles on basic design theory and the practical use of certain components. For example, there is an article reprint from Advanced Micro Devices that provides information on programming the motion of a stepper motor with the aid of a PAL (programmable array logic). Similarly, an article reprint from Motorola presents an overview of protocols and conventions used for serial communication between computers.

The application notes complement the theoretical sections by discussing the use of components related to current electronics technology. In a number of cases, this technology is ahead of the practical application, and the product is so new that an application note has not yet been published by the manufacturer—for examples, Analog Devices' description of a Continuous Edge Graphics (CEG) digital-to-analog converter (DAC), and that of a NICAM (near instantaneous companding audio multiplex) decoder chip developed by Micronas of Finland. Given the complexity of the practical circuits that could be developed on the basis of these ICs, all the relevant data sheets are included for easy reference. The book also includes a short list of manufacturers' logos that should be helpful in identifying unknown components, as well as a worldwide address list of manufacturers and distributors/representatives for the products which are discussed.

**ISBN 0-905705-33-5**  
**BKAA24      Price \$17.95**

## SPECIALS!

**BKAAZ/1** BKAA11, 12, 13, 18; all 4 for **\$49.00** (Save \$11.85!)

**BKAAZ/2** BKAA14, 15, 16, 17, 24; all 5 for **\$74.95** (Save \$13.30!)

**BKAAZ/S** Complete *Elektor* library: all 9 for **\$114.95** (Save \$34.15!)

These books are all available direct from *Elektor Electronics USA* through the Readers Services, from a number of bookshops and electronics retailers in the US and Canada, and from selected bookshops throughout the world. Special prices are those of EEUSA only.

# B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228  
 (214) 271-5546  
 FAX (214) 271-2462



## SPECIALS

MAX232	2.30
1488	.45
1489	.45
DB25-(Solder Cup) M/F	2/1.00
DB25-Rt. Angle PC BD. F	.55
DB9-Rt. Angle PC BD. M/F	.35

## MONITOR

BRAND NEW!  
 Factory Fresh  
 IBM  
 VGA Monochrome Monitor  
 12" Paper-White  
 640 x 480  
**\$79.95 plus \$9.50 S/H**  
 Within the Continental U.S.

## DISPLAY DEVICES

FLAT PANEL LCD  
 GRAPHIC DISPLAY  
 EPSON ECG-7004S-AR



640 x 200 dots - Super twisted nematic type.  
 Built in drivers - 4 bit TTL Interface - Capable of displaying numerics, graphics, alphabetics, special characters, graphs, charts, and patterns.  
 Viewing area 10 7/16" x 4 5/8". Overall 11 3/8" x 6 1/16".  
 14 pins for signals and power (+5V, -12V).  
 Complete 27 page manual  
**\$19.95** 6/\$100.00

LTP 1157AE  
 1.2" 5x7 Matrix Displays

5x7 Array with x,y select.  
 This Red Orange Matrix Can Be Stacked Horizontally. Choice of Two Matrix Orientation-Cathode Column, Anode Row. Great For "Moving Message" Signs.

**\$1.19 Ea. 8/6.95, 100/\$75.00**

## 74LS

LS00	.14	LS114 .25	LS241 .60
LS01	.14	LS122 .35	LS242 .65
LS02	.14	LS123 .45	LS243 .50
LS03	.14	LS124 1.35	LS244 .55
LS04	.14	LS125 .30	LS245 .55
LS05	.14	LS126 .35	LS251 .45
LS08	.14	LS132 .35	LS253 .40
LS09	.14	LS133 .25	LS257 .35
LS10	.14	LS136 .28	LS258 .45
LS11	.14	LS138 .35	LS259 1.00
LS12	.20	LS139 .35	LS260 .40
LS13	.25	LS145 .75	LS266 .30
LS14	.30	LS148 .35	LS273 .75
LS15	.20	LS151 .35	LS279 .30
LS20	.14	LS153 .35	LS280 .80
LS21	.16	LS154 .85	LS283 .35
LS22	.16	LS155 .50	LS290 .70
LS26	.14	LS156 .42	LS293 .50
LS27	.20	LS162 .30	LS298 .65
LS28	.15	LS158 .25	LS299 1.00
LS30	.14	LS160 .25	LS322 1.30
LS32	.16	LS161 .35	LS323 2.25
LS33	.25	LS162 .45	LS348 .75
LS37	.24	LS163 .36	LS353 1.00
LS38	.24	LS164 .45	LS357 .80
LS42	.35	LS165 .60	LS363 .75
LS51	.15	LS166 .75	LS364 .75
LS54	.20	LS169 .90	LS365 .30
LS55	.20	LS170 .45	LS366 .28
LS73	.33	LS173 .60	LS367 .35
LS74	.22	LS174 .35	LS368 .30
LS75	.25	LS175 .35	LS373 .50
LS83	.30	LS181 1.25	LS374 .45
LS85	.45	LS191 .45	LS375 .35
LS86	.20	LS192 .65	LS377 .75
LS90	.35	LS193 .65	LS378 .80
LS92	.30	LS194 .40	LS390 .80
LS93	.25	LS195 .52	LS393 .75
LS95	.30	LS196 .55	LS399 1.00
LS96	.33	LS197 .75	LS541 1.20
LS107	.28	LS221 .50	LS645 .75
LS109	.20	LS240 .50	LS646 .75
LS112	.25		LS670 .80
LS113	.25		25LS2569 1.50

## SUPER BUYS

### DYME

SSI-202 Decoder	2.25
8870 Decoder	2.25
5087 Generator	2.00
5089 Generator	2.10

## THE \$25 NETWORK

Try The 1st Truly Low Cost LAN  
 • Connect 2 or 3 PCs, XT's, AT's  
 • Uses serial ports and 5 wire cable  
 • Runs at 115 K baud  
 • Runs in background, totally transparent  
 • Share any device, any file, any time  
 • Needs only 14K of ram  
*Skeptical? We make believers!*

## LITTLE BIG LAN

- Low cost - \$75 per LAN, not per node!
- Hardware independent network  
 ARCNET, Parallel, and Serial port support on first release  
 Serial Speed: 6500(XT)-8500(AT) bytes per second  
 Parallel Speed: 8000(XT)-29000(AT) bytes per second  
 ARCNET Speed: 40000 plus bytes per second
- Use any PC/XT/AT/386 mix, even laptops and PS/2 machines  
 Connect up to 254 computers, can mix connection methods (Serial, Parallel, Arcnet)
- DOS 3.1 and Record locking support  
 Share any device, any file, any program  
 Runs in the background, totally transparent
- Low memory overhead  
 Typically only 28K is needed, but will vary with various setups
- Works with most software, including DBASE III, Microsoft WORD, LOTUS 123, Windows 3, AUTOCAD, Word Perfect, all compilers, GWBASIC, and, in fact, most anything!
- Works with DOS 2.0 to DOS 5.0 and DR-DOS DOS 3.1 or greater is preferred
- Open network, programmer API provided  
 Example for low-level link modules — you can support special hardware  
 Full specs provided on packet level protocols

CABLES & ARCNET CARDS  
 AVAILABLE — PLEASE CALL **\$75.**

## SOCKETS

Low Profile SOLDER TAIL  
 6 Pin 14/1.00  
 8 Pin 13/1.00  
 14 Pin 13/1.00  
 16 Pin 13/1.00  
 18 Pin 13/1.00  
 20 Pin 13/1.00  
 22 Pin 13/1.00  
 24 Pin 8/1.00  
 28 Pin 7/1.00  
 40 Pin 7/1.00

BUY \$10  
 GET \$1.00 - FREE CHOICE  
 68 Pin PLCC .79  
 84 Pin PLCC .89

## 6500/6800

6502	2.00	6821	1.00
6520	1.25	6845P	2.20
6522	2.70	6845S	2.20
6530	3.00	6850	1.75
6532	4.25	6852	3.50
6545	2.10	6860	3.95
6551	2.40	68681	3.00
6800	1.40	68A09EP	1.29
6802	2.50	68A40	4.00
6803	3.00	68A54	3.00
6805	2.95	68B09	4.00
6809EP	2.75	68B10	2.00
6809P	2.50	68B45	4.95
6810	1.25	68B54	4.00

## TEXT TO SPEECH BOARD

PC/XT COMPATIBLE. MAKE YOUR COMPUTER TALK!

PRICE CUT **\$69.95**  
 ASSEMBLED & TESTED  
 ADD \$3.50 SHIPPING & HANDLING



A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER.

THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT (EXTERNAL POWER SUPPLY) WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. TO USE THE BOARD IT IS ONLY NECESSARY TO SEND ENGLISH TEXT TO THE RS232 INPUT ON THE BOARD. THE BOARD INCLUDES A 1500 BYTE TEXT BUFFER AND HANDSHAKE LINE TO ALLOW YOU TO SEND DATA TO THE BOARD; THE SAME AS YOU WOULD SEND DATA TO AN RS232 SERIAL PRINTER. YOU CAN SET UP BATCH FILES THAT WILL MAKE YOUR COMPUTER GREET YOU WITH "GOOD MORNING MASTER," ETC. EVERY TIME YOU TURN IT ON. DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4 INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED. FOR INFORMATION ON A LOW COST SPEECH SYNTHESIZER SYSTEM FOR THE VISUALLY IMPAIRED, PLEASE SEND FOR FREE PACKET T.M.I.

STAND ALONE POWER SUPPLY  
 FOR ABOVE  
 ADD \$2.50 SHIPPING & HANDLING

## EPROM SPECIAL

2016-2KX8 200 n.s.	1.00
2101-1 - 256X4 500 n.s.	.75
21L02-1 350 n.s.	.65
2102AL-4 L.P. 450 n.s.	.49
2111-1 256X4 500 n.s.	1.00
2112A-2	2.50
2114L-3 1KX4 300 n.s.	.45
2125A-2 1KX1 70 n.s.	1.70
2147 4KX1	1.95
6116P-4	1.00
6117	1.20
6264-15	1.40
62256 32KX8	5.75

## DYNAMIC RAM

2108-4 8KX1	1.50
2118-4 16KX1-5Volt	.70
4027-4KX1-250 n.s.	.80
4116-16KX1-250 n.s.	.40
4116-16KX1-200 n.s.	.75
4116 16KX1-150 n.s.	.90
4164 150 n.s.	.49 or 9/3.50
4164 120 n.s.	1.10
4164-100 n.s.	1.40
TMS4416-16KX4-150 n.s.	2.75
4464-150 n.s.	1.40
4464-120 n.s.	1.45
4464-100 n.s.	1.45
4464-80 n.s.	1.45
41256 150 n.s.	1.25 or 9/9.95
41256 120 n.s.	1.30 or 9/10.99
41256 100 n.s.	1.30 or 9/10.99
41256-80 n.s.	1.30 or 9/10.99
41256-60 n.s.	1.85
1 Meg - 100 n.s.	4.40
1 Meg - 80 n.s.	4.40
414256-80 n.s. 256 x 4	4.60


## SIPPS & SIMMS AVAILABLE

8031	2.95	8251	1.10
80C32 12	3.95	8253-5	1.75
8035	1.00	8254	1.80
8039	1.00	8255	1.50
8085	1.55	8255-5	1.75
8086	1.55	8257	1.50
8087	87.50	8259A	1.85
8087-1	167.50	8259C-5	2.10
8087-2	127.50	8275	10.95
8088	2.20	8279	2.25
8088-2	3.25	8284	1.49
8155	2.25	8286	3.50
8156	2.25	8287	2.49
8202A	8.00	8288	3.50
8212	1.25	8530	3.00
8214	2.00	8741	7.00
8216	1.25	8742	7.00
8224	1.25	8748	7.00
8228	1.75	8749	7.00
8237-5	2.80	8755	7.00
8243	1.75	80286-8 PLCC	8.50
8250	2.95	80287-8	125.00
16450	1.488	1489	\$6.95
(16450)	6.50	80287-10	135.00
(16550)	13.00	V-20-10MHZ	6.50

## THREE CHIP SET

B.G. SPECIAL	
16450, 1488, 1489	— \$6.95
16550, 1488, 1489	— \$13.50

TERMS: (Unless specified elsewhere) Add \$3.25 postage, we pay balance. Orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 8 1/4% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico or Puerto Rico. Countries other than Canada, add \$9.00 shipping and handling.

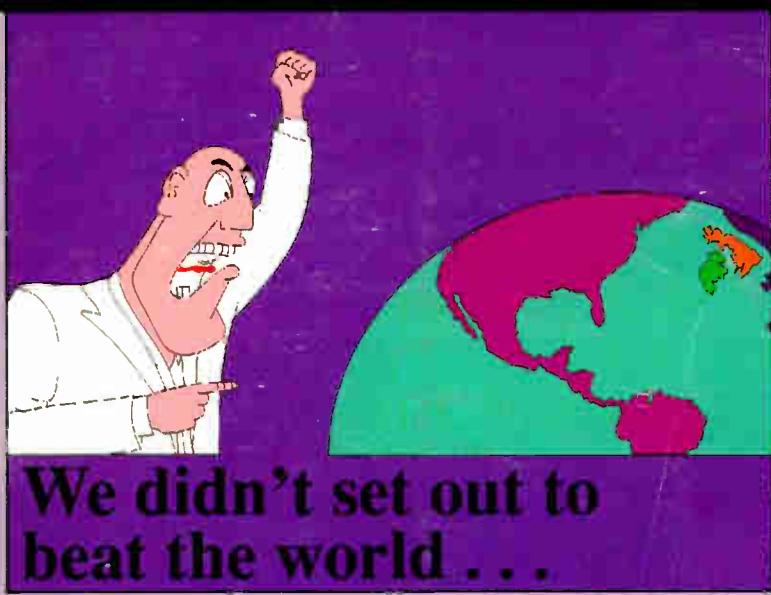

... but two new products from ATI have taken the audio world by storm! **LMS** and **LEAP** have revolutionized the way loudspeakers are designed and tested.


Now you can have audio analysis and electroacoustical measurements using ***real data***, as well as mathematical simulations.

## **LMS** Loudspeaker Measurement System

At last, there is a complete and affordable analyzer system that provides data suitable for real electro-acoustic engineering purposes. LMS uses its own precision calibrated reference microphone, a PC/AT slot card, and simple menu-driven control software.

Whether your application is loudspeaker development, automobile audio, room acoustics, industrial environments, or production testing, LMS is the perfect tool for you. LMS can gather data for and perform over 50 different acoustic and electrical tests including SPL Response, Gated SPL Curves, Rub/Buzz Test, Voltage in dBm (gated or non-gated), Auto-Impedance Measurements, Transform Functions in dB, Nyquist Plots, Polar Plots, and Inverse FFT. LMS generates metering graphics and curve displays, and Hilbert Transform calculations for Phase Curve generation, and it can do so much more.

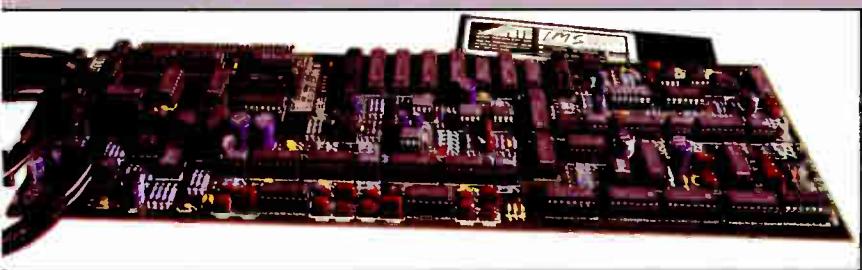
LMS includes a large number of post-processing features and tools to allow you to manipulate data to your needs. Nothing else AT ANY PRICE even comes close! Call us!



## **LEAP**
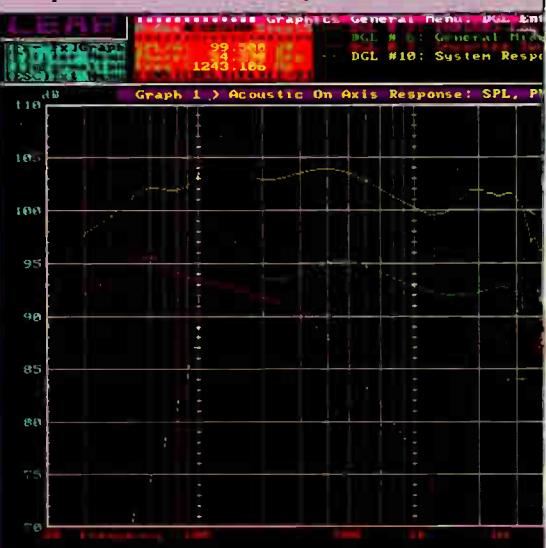
### Loudspeaker Enclosure Analysis Program

Now there is one software program that can do it all! LEAP is a powerful full-featured system



Transducer/  
Enclosure  
System for all TSL, ECL, DGL database functions  
and box design capabilities.

- Import SPL and Z Data from LMS, MLSSA, AP System 1, and TEF
- Generate 19 pairs of graphs for analysis with complete print support for Dot Matrix, HPGL, PCL, and PostScript
- Compute freq. dependent Revc and LevC
- Derive Phase from Magnitude
- Combine system response on Crossover Design
- Time Offset Correction
- Calculate Voltage/Current/Impedance

Join the distinguished list of LEAP and LMS users: Altec Lansing, JBL, Orion, Yorkville Sound, NEAR, Snell Acoustics, BBC Speakers, Hartkey Systems, Cerwin-Vega, Radian, Lucasfilm, Standford Acoustics, BEST, SCV Audio, Scientific Fidelity, Wavefront Acoustics, Peavey Electronics, Clair Bros., Renkus Heinz, Elipson, TAD/Pioneer, Swans Speakers, Sparkomatic, Rockford/Fosgate, Polk Audio, Joiner-Rose, Sony, Alpine, Bose, Tannoy, Infinity, VIFA, and many more.



7556 SW Bridgeport Road, Portland, OR 97224 TEL: 503-624-0405 FAX: 503-624-0194

