

CB ANTENNAS—they make the signals GO!

CC 02342

JANUARY-FEBRUARY

1972

75c


elementary Electronics

Build an
**ELECTRONIC
LOCK**
Let Hertz be your passkey!

INCLUDING *Science and Electronics*

Go 4-Channel Today!

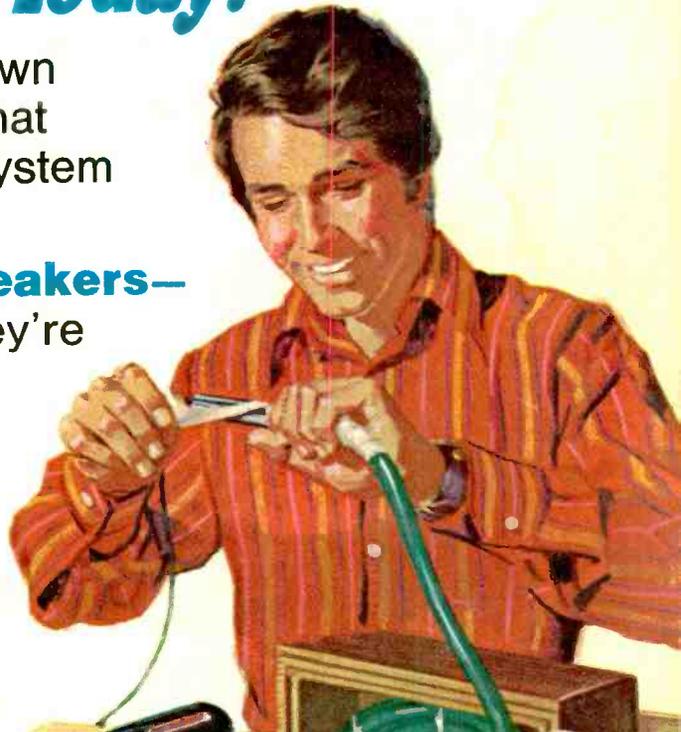- **Build Quadi**—e/e's own quadrisonic decoder that converts your stereo system to 4-channel sound.
- **Build Bookshelf Speakers**—from bookshelves. They're pre-finished for that store-bought look!



12 78 6188 MIN716N6-9 1TG25

((p)) PACE

Quality performance at low prices

**23 CHANNELS INSTALLED
DOUBLE CONVERSION
WITH ANTENNA**

Model P123-A

\$139.95

Compare these features:

- All 23 Channels Installed
- Double Conversion Receive
- "S" and RF Meter
- PA Function
- Local/Distance Function
- Transmit and Receive Lights
- + or - Power Supply



Less Antenna P123 \$129.95

Model P100-SA

\$89.95



Less Antenna P100-S \$79.95

**SIX CHANNEL TRANSCIVER
CHANNELS 9 & 11 INSTALLED
WITH ANTENNA**

Compare these features at any price:

- 5 Watts Citizen Two Way System
- Has Ch. 9 & 11 Crystals Installed
- "S" and RF Meter
- Transmit and Receive Lights
- + or - Power Supply

Model CB-9 Monitor

\$39.85



- Full Receiver with .5 uv Sensitivity
- Squelch Control
- Noise Limiter
- Alternate Channel Monitor
- Use own Antenna or Optional Adapter to work off present Two Way System

Look for the sign of QUALITY

REGISTERED SALES-SERVICE


PACE

SOLID STATE RADIO SPECIALISTS

PACE DIVISION. PATHCOM INC.. BOX 306. HARBOR CITY, CALIF. 90710

CIRCLE NO. 15 ON PAGE 17

Your paycheck says a lot about you

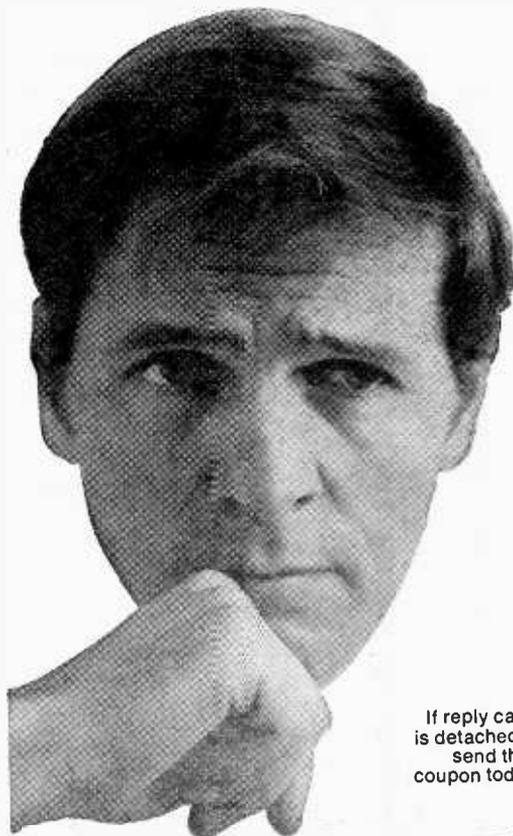

It tells you more than how much you make. It tells you how far you've come. And if your paycheck looks very much the same as it did last year, or the year before, it simply means that *you* look very much the same as *you* did last year and the year before.

But times change, and you should be changing with them. Old dull jobs are disappearing. New exciting ones are being created. There are challenging new fields that need electronics technicians...new careers such as computers, automation, television, space electronics where the work is interesting and the earnings are greater.

RCA Institutes has one of the nation's largest and most respected home study schools devoted to electronics. They can get you started even if you've had no previous training or experience. RCA Institutes has developed a faster, easier way for you to gain the skills and the knowledge you need for a fascinating, rewarding electronics career. And you don't have to quit work and go back to school. With RCA Institutes Home Study Plan you can do both. You set your own pace depending on *your* schedule.

Check over these RCA benefits:

- You get Hands-On Training—over 300 experiments and as many as 25 kits with some programs.
- You get RCA's unique "Autotext" method of learning—individual programmed instruction, the *easy, faster, simplified* way to learn!
- You get the widest choice of electronics courses and programs—everything from Electronics Fundamentals right up to Solid State Technology and Communications Electronics.
- You get a selection of low-cost tuition plans!

Sounds great, and it is! For complete information, without obligation, send in the attached postage card... or return the coupon below. That will say a lot about you.

Veterans: Train under new GI Bill. Accredited Member National Home Study Council. Licensed by N.Y. State—courses of study and instructional facilities approved by the State Education Department.

If reply card is detached—send this coupon today

RCA Institutes

Home Study Dept. 246-201-0
320 West 31st Street, New York, N.Y. 10001

Please rush me FREE illustrated catalog.
I understand that I am under no obligation.

Name _____ Age _____
(please print)

Address _____

City _____ State _____ Zip _____

Veterans: Check here

ELEMENTARY ELECTRONICS (Vol. 11, No. 6) is published bi-monthly by Science & Mechanics Publishing Co., at 229 Park Ave., S. New York, N.Y. 10003. One year subscription (six issues)—\$4.00. Second class postage paid at New York, N.Y. 10003 and at additional mailing offices.



elementary Electronics

INCLUDING SCIENCE & ELECTRONICS

Dedicated to America's Electronics Hobbyists

- CONSTRUCTION PROJECTS FOR EVERYONE**
- ☆ 39 The Elocktron—a magic lock that only your mysterious box can open.
 - 45 Build the Balanced Bridge Game—the value of this game is determined by the resistance you insert in the Wheatstone circuit.
 - ☆ 59 Go Four Channel with Quadi—the first you-build-it project that lets you hear the full four channels hidden in your LPs and FM broadcasts.
 - ☆ 65 Bookshelf Speakers from Bookshelves—here's a weekend carpenter special that'll complement your Quadi or any other system.

- ELECTRONIC THEORY**
- ☆ 29 ABC's of CB Antennas—is your CB antenna a stick in the mud? Then you've been waiting for this article for a long time.
 - 77 All About Crystals—the hard facts on those rocks that knock out the hertzes.
 - 89 e/e's Basic Course—Part 2: Understanding Power Supplies

WHAT'S NEW IN AUDIO

- 43 e/e snaps in a Toyo Cassette Pack Adaptor—it makes your 8-track player go cassette.
- 49 e/e looks at new Hi-Fi components
- 87 e/e checks out the zero tracking Garrard Zero 100 Automatic Turntable

CITIZENS BAND RADIO

- 58 CB Coffee Break—a new column for CBers.
- 85 Kathi's CB Carousel—our CB Miss singles out the Lafayette Telsat 924.

FEATURETTES IN ELECTRONICS

- 36 Moby Dick's Play Pen is Captain's Paradise
- 50 The Pollution is as High as an Airplane's Eye
- 52 The Shock Room that'll Save Your Life
- 64 "The Tempest" in Quadrisonic Sound
- 70 V is for Voltage—not Vedder
- 71 e/e Etymology—in a few words

NEW PRODUCTS FOR EVERYONE

- 8 Hey, Look Me Over—hobbyists' shopping guide
- 76 e/e looks at new Tools and Gadgets

OUR REGULAR LINEUP

- 13 Bookmark—books for beginners and pros
- 16 DX Central Reporting—a survey on who you are
- 17 Reader Service Page—get all the facts
- 24 Stamp Shack—philatronic news
- 26 Literature Library—keep your mailman busy
- 27 Ask Hank, He Knows—you pitch 'em, we bat 'em out
- 28 It's an Engineer's Life—the funnytronics page



AUTHORS IN THIS ISSUE

Ron Benrey, Len Buckwalter, Herb Cohen, Myrtle and Joe Gronk, Don Jensen, Herman F. Johnson, Ernest A. Kehr, Ted Mann, Kathi Martin—KAIQ614, Charles D. Rakes, Jack Schmidt, Hank Scott, and the ELEMEN-TARY ELECTRONICS' editorial staff.

☆
Cover
Highlights

Cover Photo
by
Leonard
Heicklen

KEEP PACE WITH SPACE AGE! SEE MOON SHOTS—LANDINGS, SPACE FLIGHTS, CLOSE UP!




AMAZING SCIENCE BUYS

for FUN, STUDY or PROFIT



NEW LIGHT-EMITTING-DIODE KIT

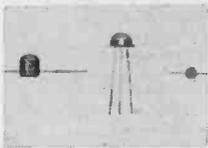

Bargain kit ideal for economical experimenting with amazing L.E.D.s, the tiny solid state monochromatic lamps that use low voltage DC, last up to 1,000 hrs. Used in card-tape readers, character recognition, hi-speed detectors, all kinds of electronic applications. Kit incs 3 L.E.D.s; gallium arsenide (MLED 600, MV 50, MLED 930); 2 visible red emitting (4000 Å); 1 infra-red emitting (9000 Å); 6 resistors; 1 20mm plastic fibre optic light pipe; instrs.

Stock No. 41,597EK \$5.95 Ppd.


LOW COST TREASURE FINDER



Discover the fun and profit of treasure hunting inexpensively. Light as a feather (10 oz.) solid-state metal detector finds hidden coins, jewelry, precious minerals. Distinguishes minerals from metal objects. Great for school, beach, campground or backyard. Requires 9V transistor batt.—works with any common AM transistor radio thus eliminating costly extra circuitry. Weight, dangling wires. Adjustable multi-purpose plastic handle reduces immediate area metal—leads to off-peak. No tuning needed.

Stock No. 71,395EK \$14.95 Ppd.
Stock No. 71,438EK (w/ Radio) \$18.95 Ppd.

BUILD A WORKING CRYSTAL RADIO

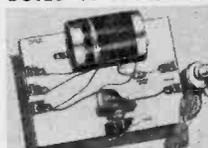

Bring the 20's back with the fun of a motorized carbon crystal set that receives 1 or more stations! So simple you can have it working in less than an hour. Connects to a permanently fixed germanium crystal. Kit incs: 4 3/4 X 6 3/4 X 3/8" thick plywood base, high-Q tuning coil, germanium diode, variable condenser, all radio parts, earphone & holder plus diagram & simple instrs. A charming conversation piece, great fun at parties and ideal gift.

Stock No. 71,513EK \$5.95 Ppd.

NEW! ELECTRONIC DIGITAL COMPUTER KIT!



Solve problems, play games, predict weather with this actual working model of giant electronic brains. Amazing new fun way to learn all about computer programming... logic, decimal, binary systems. Laws of Sets—over 20 your own programming after completing simplified 116 page instructive booklet. Includes step-by-step assembly diagrams. Circuits easily changed. Readout from illuminated control panel. Req. 2 "D" batt. (not incl.). Best model we've seen—for home, school, industry.

Stock No. 71,434EK (1 1/2" X 12 1/2" X 4") \$31.50 Ppd.

NEW 18" BLACK-LIGHT STROBE



Its a versatile strobe... and it's black-light! Adjustable flash rate from as slow as 1 flash per several secs. to a continuous glow beyond visual flicker perception (1,500 flashes a minute)—can be used as reg. light source. Top quality, solid state unit has hi-polish reflector, long lamp life. Ideal for parties, black-light posters, combo's, decoration and experiments. Incs. 18" black-light tube, 4 1/2 ft. cord. Appx. 3 X 5 1/2 X 18".

Stock No. 71,480EK \$42.95 Ppd.

AMAZING NEW Wankel Engine KIT!



Thrill to the fun of building your own see-through motorized model of revolutionary pistonless type engine... only engine experts think economically modifiable to meet new pollution standards. Replaces piston, cylinder, crank assemblies with rotating discs (sections removed for firing chambers). Smaller than conventional. Fewer parts, greater reliability, same speed w/less horsepower. Feat. flashing plugs, rubber fan belt, stick-shift on-off switch. Req. 2—1.5V batt. (not incl.).

Stock No. 71,424EK (4 1/2" 5" X 9") \$6.75 Ppd.

Order by Stock No.—Check or M.O.—Money-Back Guarantee
EDMUND SCIENTIFIC CO., 300 EDCORP BLDG., BARRINGTON, N.J. 08007



WRITE FOR FREE GIANT CATALOG

148 PAGES!—1000'S OF BARGAINS

EDMUND SCIENTIFIC CO., 300 EDCORP BUILDING, BARRINGTON, NEW JERSEY 08007
Completely new edition. New items, categories, illustrations. Dozens of electrical and electromagnet parts, accessories. Enormous selection of unique lighting items. Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lasers, Lenses, Prisms. Many rare surplus items: for hobbyists, experimenters, workshop, factory. WRITE FOR CATALOG "EK".

NEW 3" ASTRONOMICAL REFLECTOR TELESCOPE

See moon shots, orbits, stars, craters!




60 to 180X
DE-LUXE FEATURES
AT ECONOMY PRICE

Amazingly priced Apollo Space Explorer brings the wonders of the universe up close. 3" aluminumized & overcoated f/10 mirror. Reaches theoretical limits of resolution & definition. 60X standard size 1 1/4" O.D. eyepiece, 1 1/2" f.l. 3X adjustable Barlow. 6X finder telescope, high impact plastic tube; metal fork mount w/ positive locking. 36" hardwood tripod, included FREE. 272p. Handbook, Star Chart, Instructions. Best value ever!

- Stock No. 80,162EK \$59.50 Ppd.
- REG. 3" REFLECTOR TELESCOPE \$34.50 Ppd.
- Stock No. 85,050EK
- 4 1/4" ASTRONOMICAL REFLECTOR TELESCOPE \$94.50 F.O.B.
- Stock No. 85,105EK
- 6" ASTRONOMICAL REFLECTOR TELESCOPE \$239.50 F.O.B.
- Stock No. 85,086EK

NUMERICAL INDICATOR TUBES

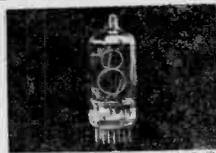Designed as direct line, side-view read-out device for basic counter and computer circuits. Gas filled cold-cathode numerical readout tubes use common anode. 10 cathodes in shapes of numerals 0-9. Also give visual digital display of volts, cycles, etc. High reliability, long life; wide-angle viewing with brightness and stability.



- TUBE W/ 0 DECIMAL \$5.95 Ppd.
- No. 41,593EK
- Socket for above: No. 41,594EK 80c Ppd.
- TUBE W/ DEC-TO-LEFT: No. 41,618EK \$5.95 Ppd.
- Socket for above: No. 41,617EK 80c Ppd.

\$8.95 ELECTRONIC STROBE!

Hand-sized solid state electronic strobe light at fantastically low price. Produces bright, psychedelic effects like larger, far more expensive Xenon strobes, yet it's just 2 1/2 X 3 X 1 1/2" thick. Adjustable flash rate, approximately 3-10 flashes per second. Make stop motion effects, posters come alive. Great to take with you to parties, dances, outings, etc. Requires 2 1/2V transistor batt. (not incl.). Instructions included.



Stock No. 41,443EK \$8.95 Ppd.

4 REPLACEMENT LAMPS 1.00 Ppd.
P-41,444EK

18" FLEXIBLE FIBERSCOPE

Hi-resolution image-transmitter lets you see into remote, inaccessible illuminated areas; through pipes, tubes or any 3/4" opening no matter how intricate. Provides clear, wide sighting. 7X magnifying eyepiece focuses from 1/2" to 1 1/2" from subject to infinity. Ideal for monitoring hazardous processes, surveillance instrument, demonstrate fiber optics. Over 4,000 coherent glass fibers (0.002", 3/8" dia. semi-rigid goose-neck sheathing.



Stock No. 60,857EK \$40.00 Ppd.

POWER HORN BLASTS A MILE

Frighten prowlers, muggers, vicious dogs with 115 decibels. Just press and this Freon powered pocket-sized metal horn can be heard a mile away to signal for help or fun. Great for boating (it floats), hiking, camping, hunting, sea-shore, rooting for your team. Can be heard over traffic and constant noises to sound fire drill, lunch break or emergency. Weighs only 3 oz. but contains up to 100 micropressure! A real bargain.



Stock No. 41,423EK \$3.25 Ppd.
2 Refill Cartridges (P-4,424EK) \$2.75 Ppd.

ECONOMICAL WATER LEVEL ALARM

Avoid costly internal flood damage with this ultra sensitive solid-state electronic device. The second it detects unwanted water it sounds off with a loud buzzer alarm to help you prevent hundreds of dollars of trouble at a fractional cost. Pumps into any 10-120 AC outlet. Isolation transformer generates low voltage for absolute safety. Consists of Metal Power Unit and Sensor, compl. instrs. 1.5-b. 20" wire.



Stock No. 41,609EK \$14.95 Ppd.
Addl. 20" Probe w/ 25' wire (#41,610EK) \$6.95 Ppd.

ORDER BY STOCK NUMBER - SEND CHECK OR MONEY ORDER - MONEY-BACK GUARANTEE

EDMUND SCIENTIFIC CO.

300 EDCORP BLDG. BARRINGTON, NEW JERSEY 08007

CIRCLE NO. 14 ON PAGE 17

Convert
your stereo system
to 4-dimensional sound!
QUATRASONIC™ BY EICO

KIT \$17.95
WIRED -29.95



Enjoy 4-dimensional sound hidden in standard stereo records, tapes and FM broadcasts. Just add the QUATRASONIC™ adaptor and two speaker systems - No additional amplifiers required.

FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments' Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card. EICO, 283 Malta Street, Brooklyn, N.Y. 11207



CIRCLE NO. 3 ON PAGE 17

CALL ME!



24 HOURS A DAY... 7 DAYS A WEEK

I'll send you 2 FREE BOOKS describing career opportunities in Electronics. Call me TOLL FREE: **800-321-2155**

(in Ohio, call 800-362-2105)

For details about the famous CIE home-study courses in Electronics, see our ad on page 108

Cleveland Institute of Electronics

1776 East 17th Street, Cleveland, Ohio 44114

elementary Electronics

INCLUDING SCIENCE AND ELECTRONICS

Jan./Feb. 1972

Vol. 11/No. 6

Dedicated to America's Electronics Hobbyists

Editor-in-Chief

JULIAN SIENKIEWICZ MARTIN, WA2CQL

Technical Editor

STEPHEN B. GRAY

Communications Editor

PETER L. DEXNIS, WA3LOQ

News Editor

CAROL J. BRUCKNER

Citizens Band Editor

KATHI MARTIN, KAIØ614

Workbench Editor

HANK SCOTT

Art Director

JIM MEDLER

Cover Art Director

IRVING BERNSTEIN

Assistant Art Director

ANDY STEIGMEIER

Art Associate

ANGELO MARFISI

RALPH ROBINO

Advertising Director

DAVID J. MILLER

Production Director

CARL BARTEE

Production Manager

GERTRUD BORCHARDT

Assistant Production Manager

MARILYN VARGAS

Newsstand Circulation Director

DON GABREE

Instruments Division Manager

WILFRED M. BROWN

Chairman of the Board

B. G. DAVIS

President and Publisher

JOEL DAVIS

Vice-President and General Manager

LEONARD F. PINTO

Vice President and Treasurer

VICTOR C. STABILE, KBØ681

ELEMENTARY ELECTRONICS is published bi-monthly by Science & Mechanics Publishing Co., a subsidiary of Davis Publications, Inc. Editorial, Business and Subscription offices: 229 Park Avenue South, New York, N.Y. 10003. One-year subscription (six issues)—\$3.95; two-year subscription (12 issues)—\$7.95; three-year subscription (18 issues)—\$11.95; and four year subscription (24 issues)—\$15.95. Add \$1.00 per year for postage outside the U.S.A. and Canada. Advertising offices: New York, 229 Park Avenue South, 212-OR 3-1300; Chicago, 520 N. Michigan Ave., 312-527-0330; Los Angeles: J. E. Publishers' Rep. Co., 8560 Sunset Blvd., 213-659-3810; Long Island: Len Osten, 9 Garden Street, Great Neck, N.Y., 516-487-3305; Southwestern advertising representative: Jim Wright, 818 Olive St., St. Louis, 314-CH-1-1965. Second-class postage paid at New York, N.Y. and of additional mailing office. Copyright 1971 by Science and Mechanics Publishing Co.

ELEMENTARY ELECTRONICS

ICS
International
Correspondence
Schools
Division of Intext
ICS, Scranton, Pa. 18515

Canadian residents:
Send coupon to Scranton.
Our affiliate in Canada will reply.
In Honolulu:
Use P.O. Box 418, Honolulu.

TAKE YOUR FIRST STEP... MAIL THIS COUPON TODAY—ICS, SCRANTON, PA. 18515

4A010M

I'm interested in a program of independent study.
Send me, without cost, your booklet on the principles of success,
sample text demonstrating famous ICS method, and your catalog for _____ (Print name of course. See list.)

Miss _____ Age _____
Mrs. _____
Mr. _____
Address _____ Apt. _____
City _____ State _____ Zip Code _____
Occupation _____ Employed by _____ Working Hours _____ A.M. to _____ P.M.

266 ways to win yourself a RAISE IN PAY

Dozens of new careers are open to you with ICS training. Oldest, largest correspondence institution. 8,000,000 students since 1890. Learn facts, theories, practical applications. Instructors guide you, answer

your questions. Illustrated texts, written by authorities, yours to keep. Famed ICS diploma to graduates. Convenient payment plan. Take charge of your future now. Send coupon for three FREE booklets.

LEADERS IN THE ICS SUCCESS PARADE...

Automobile Engine Tune-Up
Introduction to System/360 Computer Business Administration Accounting
Civil Engineering Practical Electrician TV-Radio Servicing

Architectural Drafting High School Courses High School Equivalency Domestic-Commercial Refrigeration and Air Conditioning Serv. Aircraft and Power Plant Mechanics

ACCOUNTING
Accounting (U.S.A.)
Accounting (Canadian)
Accounting for Business Programmers
Auditing
Business Law (U.S.A.)
Cost Accounting
CPA Review (U.S.A.)
General Accounting
Federal Tax (U.S.A.)
General Business Accounting
Junior Accounting
Office Accounting
Practical Accounting
Public Accounting
Small Business Accounting (U.S.A.)
Starting and Managing a Small Accounting Service (U.S.A.)

Show Card Writing
Sign Painting and Designing
Sketching and Painting

AUTOMOTIVE
Automatic Transmission Specialist
Automobile Air Conditioning Specialist
Automobile Body Rebuilding & Refinishing
Automobile Engine Tune-Up
Automotive Mechanic
Automobile Master Mechanic
Automotive Diesel-Gas Mechanic

BUSINESS
Advertising Accl. Exec.
Advertising Media
Advertising Copywriting
Advertising Production
Business Administration
Business Law
Canadian Business Course

ARCHITECTURE AND BUILDING
Architectural Drawing and Designing
Architecture
Building Contractor
Building Estimator
Building Inspector
Building Maintenance
Carpenter-Building
Carpentry and Millwork
House Planning and Interior Design
Mason
Painting Contractor
Reading Architects Blueprints

Industrial Psychology
Basic Inventory Control
Managing a Small Store
Marketing Management
Marketing Research Management
Exec. Management
Office Management
Production Management
Purchasing Agent
Retail Bus. Management
Retail Buyer
Systems and Procedures Analysis

BUSINESS: SALES
Real Estate Agent
Modern Salesman
Sales Manager
BUSINESS: SUPERVISION
Advanced Management
Basic Management

Industrial Foremanship Management
Industrial Supervision
Sales Management
Personnel—Labor Relations (U.S.A.)
General Supervision

CHEMICAL
Chemical Analyst
Chemical Engineering
Chemical Laboratory Technician
Chemical Process Op.
Elements of Nuclear Energy
General Chemistry
Instrumental Laboratory Analysis

CIVIL ENGINEERING
Civil Engineering
Construction Eng'g Technician
Highway Eng'g Tech.
Principles of Surveying
Reading Highway Blueprints
Reading Structural Blueprints
Sanitary Engineering Technology
Sewage—Plant Operator
Structural Eng'g Tech.
Surveying and Mapping
Water-Works Operator

COMPUTERS
Fundamentals of Computer Programming
COBOL Programming
Fortran IV Programming
Introduction to Digital Computer Programming
Programming the IBM 1401 Computer
Introduction to System 360 Computer

DRAFTING
Aircraft Drafting
Architectural Drafting
Design Drafting
Drafting Technology
Electrical Drafting
Electronic Drafting
Introductory Mech. Drafting
Mechanical Drafting
Pressure-Vessel and Tank Print Reading
Sheet Metal Layout
Structural Drafting

ELECTRICAL
Electrical Engineering — Electronics Option
— Power Option
Electrical Appliance Ser.
Electrical Contractor
Electrical Eng'g Tech.
Electrical Home Maint.
Electrical Instrumentation Tech.
Electric Motor Repairman
Industrial Elec. Tech.
Industrial Electrician
Industrial Maintenance Electrician
Power-Line Design and Construction
Power Plant Operator — Hydro Option
— Steam Option
Practical Electrician
Utility Lineman
Reading Elec. Blueprints

ENGLISH AND WRITING
Better Business Writing
English for Spanish (U.S.A.)
Free Lance Writing for Fun and Profit
Modern Letter Writing
Practical English
Reading Improvement
Short Story Writing

HIGH SCHOOL
High School Business
High School (Canadian)
High School General
High School Math.
High School Secretarial
High School Vocational
High School College Preparatory—Arts
High School College Prep—Engineering and Science
Preparatory Course for High School Equivalency Exam.

MACHINE SHOP PRACTICE
Industrial Metallurgy
Mach. Shop Inspection
Mach. Shop Practice
Metallurgical Tech.
Reading Shop Blueprints
Tool & Die Maker
Tool and Die Foreman
Welding Foreman
MATHEMATICS
Math and Mechanics for Engineers

Math and Physics for Engineers
MECHANICAL
Mechanical Engineering
Aircraft and Power Plant Mechanic
Principles of Hydraulic and Pneumatic Power
Industrial Engineering
Industrial Eng'g Tech.
Industrial Instrumentation
Machine Design
Quality Control
Safety Eng'g Tech.
Tool Design
Vibration Analysis and Control

PETROLEUM
Natural Gas Production and Transmission
Oil Well Servicing
Petroleum Production Operator
Petroleum Production Field Tech.
Petroleum Refinery Op.

PLASTICS
Plastics Technician

PLUMBING, HEATING AND AIR CONDITIONING
Air Conditioning Estimator
Air Conditioning Maint.
Domestic Heating with Gas and Oil
Heating & Air Conditioning with Drawing
Industrial Air Cond.
Pipe Fitting Plumbing
Plumbing and Heating Est.
Practical Plumbing
Domestic-Commercial Refrigeration and Air Conditioning Serv.

PULP AND PAPER
Paper Machine Operator
Paper Making
Pulp Making
Pulp & Paper Tech.

SECRETARIAL
Clerk-Typist
Secretary, Private Sec'y, Legal Sec'y, Med. Secretary, Executive

Shorthand/Stenographic Typewriting

STEAM AND DIESEL POWER
Boiler Inspector
Building Eng's
Power Plant Engineering
Stationary Diesel Eng's (operation and maintenance)
Stationary Fireman
Stationary Steam Eng'g

TEXTILES
Carding and Spinning
Dyeing and Finishing
Loom Fixing
Textile Designing
Textile Mill Superintendent
Textile Mill Supervisor

TRAFFIC
Motor Traffic Man'g'm't
Traffic Management

TV-RADIO-ELECTRONICS
Cable TV Installer
Commercial Radio
Telephone License
1st Class
2nd Class
3rd Class

Electronics Service Technician
Principles of Electronic Computers
General Electronics
Hi-Fi Stereo and Sound System Servicing
Industrial Electronics
Numerical Control
Maintenance and Troubleshooting
TV and Radio Servicing
Solid State Electronics
Telephony

APPROVED FOR VETERANS FOR TUITION REFUND
(G.I.'s quality after 180 days active service)
Accredited member, National Home Study Council.
Easy pay-as-you-learn plan.
Special rates to members
U.S. Armed Forces.

CIRCLE NO. 8 ON PAGE 17

3 Instruments in One!



**NEW EICO
TRANSISTOR
ANALYZER**

Model 685
\$99.95
KIT

FACTORY WIRED \$149.95

Nobody but Eico makes the troubleshooting of solid state equipment so quick, easy, versatile and precise for the professional electronics technician and engineer—and at such low cost!

- Dynamically tests transistors in and out of circuit.
- Performs the 4 basic tests on all types of FETs including pinch-off.
- Performs the 3 basic tests on all types of bipolar transistors.
- Tests for true transconductance and AC Beta, in and out of circuit.
- Tests all types of diodes and measures zener voltage.
- Tests SCRs, TRIACs, and UJTs.
- Incorporates easy-to-use DC Voltmeter and Ohmmeter.
- 50 uA taut band meter movement.

FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card or send 25¢ for First Class mail service.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



CIRCLE NO. 4 ON PAGE 17

ANOTHER SUPERB VALUE from

Olson

Electronics

ONLY \$300

tv-com



TV SYSTEM with INTERCOM

Compact camera and monitor is equipped for 2-way sound that offers new dimension in all-round protection for your family, home, business or industry. Simple plug-in installation. Complete - nothing else to buy.

Olson Electronics, Dept. T2 260 S. Forge St.,
Akron, Ohio 44308

- I enclose \$300 plus \$1 for postage and handling. Send me the TV-300 TV System.
- Send me the next seven issues of the Olson Catalog, without cost or obligation. **FREE**

Name _____
Address _____
City _____
State _____ Zip _____


CIRCLE NO. 13 ON PAGE 17

Hey, look me over

Showcase of New Products

Great for CB Beamers

A new economy-priced antenna rotor has been introduced by Cornell-Dubilier Electronics. The AR-20 antenna rotor system has many of the best features of other rotors in the CDE line. The rotor is housed in heavy-duty, die-cast aluminum, gold colored to match today's color antennas. Quick mounting is provided for through positive grip U-bolt clamps on the cast aluminum housing. A positive braking system kills any chance of drift due to wind. The control is fully auto-

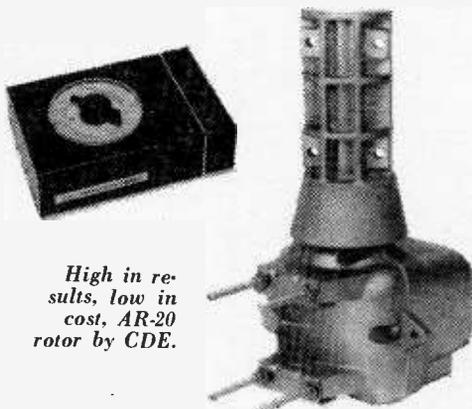

*High in re-
sults, low in
cost, AR-20
rotor by CDE.*

matic and of the same type as the well known AR-22 rotor. After the desired direction is set, the unit stops automatically and with great accuracy. The dial face is illuminated when the system is in operation. The AR-20 is packaged in a full color container which illustrates the most common reception problems. The container comes with a pop-up handle for easy carrying. Priced at \$49.95.

Circle No. 50 on Page 17.

Color TV

Heath Company has just announced the addition of a new 25" ultra-rectangular "square-corner" model to its line of solid-state color TV kits. The new model, GR-371MX, uses the exclusive Heath MT-5 picture tube that provides increased viewing area, brighter picture, better contrast and vivid, lifelike color reproduction. Ten modular circuit boards in the GR-371MX snap in and out in seconds for fast easy assembly and simplified periodic maintenance and adjustment. The circuit uses 45 transistors, 55 diodes, 2 SCRs and 4 advanced integrated circuits. Among the numerous standard features of the GR-371MX are

ELEMENTARY ELECTRONICS

Only RCA Institutes offers you all these advantages:

1 A broad range of courses to help you qualify for good-paying jobs in such rewarding fields as communications, color TV servicing, automation, nuclear instrumentation, space electronics, drafting, computer programming.

2 RCA's exclusive Autotext training method—the easy, faster, simplified way to learn electronics at home.

3 Personal supervision throughout your training.

4 Over 250 experiments and up to 22 kits in some programs

5 Easy monthly payment plan.

6 Over 60 years of leadership in technical training.

7 Recognition from leaders in the field as an RCA Institutes graduate.

Veterans can train under new GI Bill. Licensed by the State of New York. Accredited Member National Home Study Council.

Courses available in Canada too.

If you've ever thought about getting into electronics...

you owe it to yourself to see what RCA home training has to offer.

This entire fold-over coupon makes a no-postage-required business-reply envelope. Fill in your name and address ...then cut out along dotted lines...fold, seal and mail.

246-201-9

RCA INSTITUTES, Inc., Home Study School
320 West 31st St., New York, N. Y. 10001

Please send me free illustrated home study career catalog.

Name _____ Age _____

(please print)

Address _____

City _____ State _____ Zip _____

Check here if interested in Classroom Training.

Veterans check here

NO STAMP NEEDED

You must seal (Staple, tape or glue) before mailing.

FOLD HERE

DO NOT CUT HERE

FIRST CLASS

Permit No. 10662
New York, N. Y.

BUSINESS REPLY MAIL

No Postage Necessary if Mailed in United States

Postage will be paid by

RCA INSTITUTES

Home Study School
320 West 31st St.
New York, N. Y. 10001

246-201-9

HEY, LOOK ME OVER *****

push-button automatic fine tuning that locks in perfect picture and sound instantly . . . exclusive Heath MOSFET VHF tuner and completely shielded 3-stage IF (both factory assembled for superior performance) . . . built-in power tuning that lets




All solid-state color TV has MOSFET tuner.

you scan all VHF and one preselected UHF channel automatically. Automatic color control, adjustable noise limiting, adjustable video peaking and "instant on" are all standard too. The new GR-371MX is priced at \$579.95 without cabinet. Mediterranean, Contemporary Walnut and Early American cabinet styles are available, starting at \$79.95.

Circle No. 7 on Page 17.

Carry a Torch

The Brookstone Company has introduced a new, miniature welding torch capable of precision microjoining of all weldable materials. Called the "Mini-Pro", the torch features a controllable stable flame down to 1/2 of an inch and smaller. It is ideal for applying flame temperatures up to 6300°F to extremely localized areas on all metals and can also be used to soften or melt plastics, glass and other materials. Perfect for

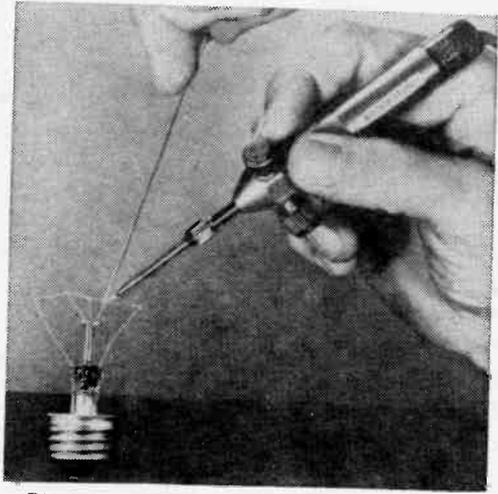

Pin-point welding with Mini-Pro gas torch.



DIRECT FREQUENCY DIALING
International Short-Wave Broadcast RECEIVER



No more guesswork in identifying stations. Set dial at a station's frequency and if conditions permit you'll hear it everytime . . .

- Ultra-precision tuning dial accuracy, SW and standard AM Broadcast
- Crystal lattice filter for adjacent station rejection and good AF response
- Dual conversion • Solid state AF output • S-meter • Preselector gives superior sensitivity by peaking antenna and RF stages • Crystal-controlled H. F. Oscillator stability • Amplified AVC constant AF output • Price \$299.00

Write for free Brochure No. 44.

R. L. DRAKE COMPANY • Miamlsburg, Ohio 45342

CIRCLE NO. 19 ON PAGE 17

WRITE NOW FOR **McGEE'S**
BIG SPEAKER CATALOG
1001 BARGAINS IN
SPEAKERS—PARTS—TUBES—HIGH FIDELITY
COMPONENTS—RECORD CHANGERS—
Tape Recorders—Kits—Everything in Electronics
1901 McGee Street, Kansas City, Missouri 64108

CIRCLE NO. 9 ON PAGE 17

PARTS! **CORNELL** **TUBES!**
FREE Send For FREE
CORNELL'S
New Color
Catalog
48 Pgs. New Items
33¢ per tube
IN LOTS OF 100
36¢ per tube
ORDER FREE
IF NOT SHIPPED
IN 24 HOURS!
4219 E. UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

CIRCLE NO. 2 ON PAGE 17

FIND BURIED TREASURE
Powerful electronic detector
finds buried gold, silver,
coins, etc. 5 new models.
Write for free catalog.

RELCO, Dept. D-58 **19⁹⁵**
BOX 10839, HOUSTON, TEX. 77018

CIRCLE NO. 12 ON PAGE 17

Buy U. S.
Savings
Bonds

making and repairing miniature parts and equipment of all kinds. The Mini-Pro comes complete with a set of 5 interchangeable copper tips—4 with drilled synthetic ruby nozzles to insure precise gas flow and longest possible tip life. Also comes with 5½ feet of color coded hose and ¼"-18 thread brass fittings for attachment to standard regulators. \$50.75 postpaid. Free literature available.

Circle No. 49 on Page 17.

There's Gold Out There

There is adventure, fun and profit in treasure hunting or prospecting with a revolutionary new featherweight metal and mineral detector, White's Electronics, Inc. Coinmaster IV. More sensitive and lighter in weight than most others in its class, the Coinmaster IV has a highly tuned semi-3 coil, ultra-sensitive 6-in. loop developed



Find it fast with lightweight metal detector.

for maximum depth efficiency when searching for coins, and other small metal objects. The device also is designed to detect at greater depths larger items such as treasure chests, iron pots, etc. Use of all transistor solid state circuitry makes the Model 4 a very compact and lightweight detector. It is a joy to women treasure hunters and youngsters. The detector weighs only 4-lbs. 6-oz., complete with loops and batteries, which reduces fatigue on extended searches. White's new all-transistor transmitter-receiver Coinmaster IV metal detector comes complete with mineral and metal samples, super-sensitive multi-coil 6-in. loop, detailed instructions and a two-year warranty. It is retail priced at \$199.50 f.o.b. factory.

Circle No. 48 on Page 17.

Laser Science Kits

Metrologic Instruments, Inc., Bellmawr, N.J., is presently introducing 11 new Laser Science Kits for the Christmas gift market. No longer a laboratory curiosity, the Laser is being manufactured in large quantities by Metrologic for the



we've gone magnetic!

NEW NUTDRIVERS STOP FUMBLING, SAVE TIME

Exclusive with Xcelite, 1/4" and 5/16" hex socket magnetic nutdrivers offer the ultimate in convenience for starting, driving, or retrieving screws, bolts, or nuts.

All types: Midget Pocket Clip, Regular, Extra Long, Super Long fixed handle... also interchangeable shanks for Series "99" handles.

Permanent Alnico magnet. Sockets remain demagnetized. Won't attract extraneous matter or deflect against metal surfaces.

New comfort-contour, color-coded handle makes one-hand driving easy, identifies tools as magnetic.

Sockets specially treated and hardened for use with hex head, self-tapping screws. Finished in black oxide for dimensional control and added identification.

REQUEST DESCRIPTIVE LITERATURE

nationwide availability through local distributors



Made in U.S.A.

XCELITE

XCELITE, INC., 80 BANK ST., ORCHARD PARK, N.Y. 14127

Please send descriptive literature on Xcelite Magnetic Nutdrivers.

name _____
address _____
city _____ state _____ zip _____

CIRCLE NO. 11 ON PAGE 17

AT LAST! PROFESSIONAL HOME PROTECTION EVERYONE CAN INSTALL AND AFFORD.

Model FC-100
\$34.95
 WIRED



- Start your custom Burglar/Hold-up/Fire Alarm System with the FC-100. Add on Sensors, Alarms and Accessories to suit your own needs.
- "Do-it-Yourself" Installers Handbook included. No technical knowledge needed — No soldering.
- 100% Professional in Design, Reliability, Performance.



'Fail Safe'-SYSTEM BY EICO

A New Concept in "Do-it-Yourself" Home Protection

FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card or send 25¢ for First Class mail service.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



CIRCLE NO. 5 ON PAGE 17

FOR THE EXPERIMENTER

International EX Crystal and EX Kits



OX OSCILLATOR
\$2.95

OX OSCILLATOR Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHZ Hi Kit 20,000 to 60,000 KHZ (Specify) **\$2.95**

MX-1 TRANSISTOR RF MIXER -A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Lo kit 3-20 MHz. Hi kit 20-170 MHz. **\$3.50**

SAX-1 TRANSISTOR RF AMP. Amplifier to drive MX-1 mixer. Lo kit 3-20 MHz. Hi Kit 20-170 MHz. **\$3.50**

PAX-1 TRANSISTOR RF POWER AMP. A Single tuned output amplifier to follow the OX oscillator. 3,000 to 30,000 KHZ **\$3.75**



EX CRYSTAL
\$3.95

EX CRYSTAL Available from 3,000 KHZ to 60,000 KHZ. Supplied only in HC 6/U holder. Calib. is $\pm 0.2\%$ when operated in International OX circuit or its equivalent. (Specify frequency) **\$3.95**

BAX-1 BROADBAND AMP. May be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. **\$3.75**



INTERNATIONAL
 CRYSTAL MFG. CO., INC.
 10 NO. LEE • OKLA. CITY, OKLA. 73102
 Write for **FREE** Catalog

CIRCLE NO. 20 ON PAGE 17

HEY, LOOK ME OVER★★★★★★★★★★

education and hobby markets. The New Jersey firm has completed its retail packaging program and for the first time is making its laser science kits available through department, variety, and hobby store outlets. Student hobbyists have demonstrated unusual interest in lasers this past year. Many have won school science fair awards, simply by assembling a laser and demonstrating some of its unique features. Several of Metrologic's laser science kits are specially designed for the science fair enthusiast. Each kit includes a loose-leaf manual outlining a range of experiments. With Metrologic's Laser Optics Kit, for example, hobbyists can progress from the beginning concepts of light, through geometric optics, and on through physical optics, including, holography (three-dimensional photography). Use of lasers with these educational kits is completely safe. The power levels possible are well below those that can cause eye damage, and the lasers are strongly encased to prevent electrical accidents. Each kit is built on a modular concept that allows expansion of the range of experiments as interest grows. Lasers are not supplied with the kits but are available from Metrologic at prices ranging from \$99.50 and up; lasers in kit form are available at \$49.50 and up.

Circle No. 47 on Page 17.

PC Kit Aids Beginner

At one time building an electronics project was hard work for it involved drilling, cutting, reaming and deburring a metal chassis. Some of those early chassis weren't aluminum either, but were steel, and so electronics construction meant sore muscles, cut and bleeding fingers,

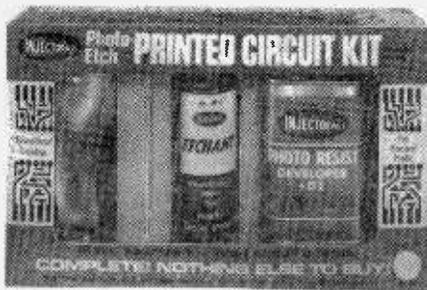


Photo-Etch your own PC boards at home.

and frazzled nerves. Injectorall Electronics Corp. has taken the sweat out of electronics and put pleasure back in. Now, with Injectorall's new No. 650 photo-etch printed-circuit kit, anyone, beginner or professional, can make professional printed circuits first time, every time. Injectorall's 650 is a completely packaged kit (nothing else to buy) using a photosensitive method for producing professional quality printed circuits. It can be used with assurance by engineers developing a prototype or a hobbyist constructing a home-lab project. This low-cost easy way of making quality printed circuit boards is now available at all major distributors and retails for only \$10.80. ■

Circle No. 46 on Page 17.

ELEMENTARY ELECTRONICS



BOOKMARK BY BOOKWORM

Experimenter's Dream. It seems the engineers at General Electric have as much fun fooling with simple circuits as do the editor's of **ELEMENTARY ELECTRONICS**. The boys at GE's Tube Department in Owensboro, KY have prepared and updated *The Electronics Experimenter's Circuit Manual, Third Edition*, and its packed with new circuits that not only use vacuum tubes but thyristors, diodes,



Soft cover
252 pages
\$2.00

transistors SCR's and the like. Over 41 projects like a two-compactron stereo amplifier, battery charger, audio dancing lights, motor control, temperature regulator, CD meter protection and more. If you enjoy reading e/e, you'll want this GE book in your collection. Published by General Electric Company Tube Products Department.

For Beginners Only. Rather than simply tell how to build some gadget, and leave one wondering why he bothered, *Electronics Self-Taught with Experiments & Projects* offers a much more worthwhile challenge, and greater assurance of gaining useful knowledge from its use. Written by Jim Ashe especially for serious experimenters, hobbyists and students, here at last is a book that shows *why* certain things are done, tells *how* devices and circuits



Hard cover
288 pages
\$7.95

CALL ME!



24 HOURS A DAY... 7 DAYS A WEEK

I'll send you 2 FREE BOOKS describing career opportunities in Electronics. Call me TOLL FREE: **800-321-2155**
(in Ohio, call 800-362-2105)

For details about the famous CIE home-study courses in Electronics, see our ad on page 108

Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

"LISTEN IN" TO POLICE-FIRE RADIO CALLS IN YOUR CAR!

WORKS with ANY CAR—Portable or HOME RADIO! Just PLUGS in—No wiring—3 minute hookup! Switch instantly from regular to ALL POLICE-FIRE-EMERGENCY-COMMERCIAL-TAXICAB-STATE-CITY-GOV'T 2 way Radio calls in YOUR AREA. DUAL-HI-LOW BANDS—35/50-150-7.75 MHX. OVER a MILLION Radio Cars/stations. USE Everywhere—always works! (cash, Ck, M.O.) and pay post-SEND ONLY \$2.00 (incl. \$1.00 p&h or send \$9.99 for ppd. Del in USA. COMPLETE, ready to use with instructions. One Year service Warranty—10 DAY MONEY BACK TRIAL (if retrd) AMAZING OFFER good only by mail—WESTERN RADIO Dept. BE-1, KEARNEY, NEBR. 68847



CIRCLE NO. 17 ON PAGE 17

THOUSANDS OF BARGAINS TOP VALUES IN ELECTRONIC PARTS

Transistors, Modules, C. B., Speaker, Stereo, Hi-Fi, Photo Cells and Thousands of Other Electronic Parts. Send for FREE Catalogue

ELECTRONIC DISTRIBUTORS INC.



EDI
Dept. TA-2, 4900 Elston
Chicago, Ill. 60630
□ RUSH CATALOGUE
Name.....
Address.....
City.....
State..... Zip Code.....

CIRCLE NO. 22 ON PAGE 17

Put it to Work!

NEW AND ONLY FROM EICO- THE INDUSTRY'S LOWEST-PRICED PROFESSIONAL FET-VM.

Model 239
\$39.95
KIT



Use the battery powered Solid State EICO 239 on your bench or in the field. Check semiconductor and vacuum tube circuits. 11 Megohm DC input impedance. Read AC rms and DC voltages in seven steps from 1 to 1000 volts on large 4 1/2" meter. Measure and read peak-to-peak AC to 2800 volts. Check resistance from 0.2Ω to 1000MΩ on seven ranges. Provides a total of 28 useful ranges on 12 accurate scales. Automatic battery check. Includes exclusive DC/AC ohms Uniprobe™. Factory Assembled, \$59.95.

FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



2 METER FM!

VERTICAL GROUND PLANES with special custom features...
... for 150-170 MHz.

Gain: 3.4 db, compared to 1/4 wave ground plane. Power Rated: 1 KW AM; 2 KW P.E.P. SSB. Frequency Range: 144 to 148 MHz. with special custom features for 150 to 170 MHz. VSWR: 1.5/1 or better at resonance.

Diplomat 2	Diplomat Special
Model DI-2	Model DI-2A
\$11.20	\$17.95

For complete details, see your local authorized Mosley Dealer or write Dept. 142a.

Mosley Electronics Inc.

4610 N. LINDBERGH BLVD., BRIDGETON MO. 63044

CIRCLE NO. 10 ON PAGE 17

BOOKMARK

work, and suggests innovations that spur the reader forward to more important work in electronics. Even with no prior knowledge of electronics, a reader will quickly acquire practical know-how which can be put to immediate use. The text divulges many fascinating tricks with ordinary "garden variety" diodes and transistors. Expensive, special-purpose types are not needed. In fact, the author continually stresses the importance of keeping things simple and inexpensive. There are circuits and projects using integrated circuits, plus communications devices, logic circuits, "industrial" devices, and lab-type equipment the reader can build and calibrate himself. Truly unlike most hobby or project book ever published. Published by Tab Books.

Answer This One. Do you believe a person can stand on the third rail of an electric railroad system without being electrocuted? Why airplanes cause TV "flutter"? Why does an atomic bomb explode? The answers to these questions and many, many others are



Hard cover
308 pages
\$5.95

answered in a new book, *Science in Everyday Things* written by William C. Vergara. The author, an engineer by profession and a general scientist by avocation, explains natural phenomena in nontechnical language for readers with little scientific background. Published by Harper & Row, Publishers.

For Mr. Fix-its, *Major Appliance Repair Guide* by Wayne Lemons & Bill Price is a complete guide to the service and repair of all major electrical appliances—from automatic washers to refrigerators. This comprehensive, up-to-date volume contains all the know-how needed to fix any major electrical appliance. The authors explain every step in minute detail and illustrate typical situations with over 260 photos and drawings. Numerous troubleshooting charts are included to aid in pinpointing the cause of virtually any problem.

MAJOR APPLIANCE REPAIR GUIDE

By Wayne Lemons & Bill Price

TAB BOOKS
New York, London, N.Y. 11714

Soft cover
228 pages
\$5.95

ELEMENTARY ELECTRONICS


The content begins with a discussion of basic techniques and procedures, evolved from years of practical experience. It tells exactly what tools and test instruments are needed and how to use them. Since many appliances contain motors in various shapes and sizes, a complete chapter is devoted to electric motor test and repair. The authors explain how each type works and what usually goes wrong, thus enabling the reader in a matter of minutes to determine whether or not a motor is repairable. Published by Tab Books.

It Swings. Oscillator circuits seem to pop up almost everywhere you look in electronic devices, in a seemingly endless variety of forms and sizes. Yet, in spite of this variety,

the ancestry of each one can probably be traced back to one of the basic oscillator circuits found in *Understanding Oscillators* by Irving M. Gottlieb. These circuits include well-known oscillators, such as the Hartley and the Colpitts, as well as some not quite as well-known, e.g., the Meissner, the Meacham Bridge, the Franklin, and the Butler oscillators. Here is what the technician and engineer want to know about oscillators—how they work, their personalities, their strong points and weak points, and how they are used in practical applications. Published by Howard W. Sams & Co., Inc. ■



Soft cover
160 pages
\$4.50

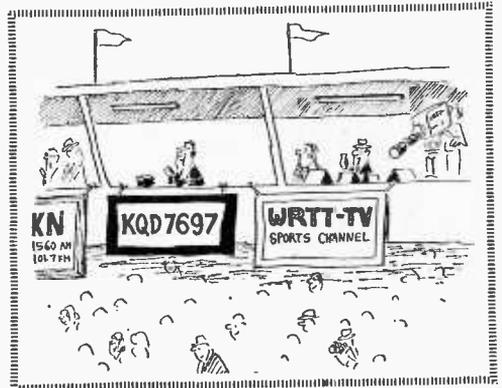

True 4 Channel Sound

[\$42.50 per 20 watt channel]



There are several components on the market today that will give you true 4-channel sound.

All are expensive. Except ours.

We call ours QAUDIO*. It's an amplifier and player with 4 discrete channels. And we designed it primarily to play the new 8-track 4-channel cartridges.

But it will also play ordinary 8-track stereo cartridges, and make them sound fuller and richer than they ever have before.

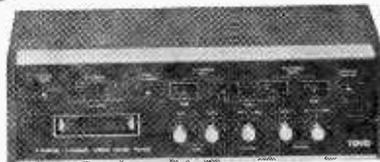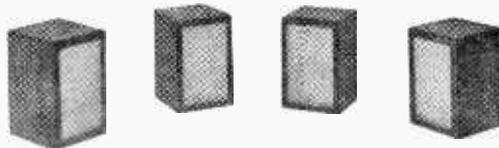Of course it takes a specially recorded 4-channel cartridge to give you the real QAUDIO experience.



You can experience it today—at a price that's almost as unbelievable as the sound: \$169.95. (That's \$169.95 for a true 4-channel amplifier-player with 80 watts of total music power.) A unit for car/boat is just \$129.95.

We'll be happy to send you the names of dealers near you demonstrating QAUDIO, together with a brochure describing it in detail.

Write to Toyo Radio Company of America, Inc., 1842B W. 169th St., Gardena, Calif. 90247.

QAUDIO
BY TOYO
A SHOCKING EXPERIENCE IN SOUND

*PRONOUNCED "KWAH-DIO". THE NAME QAUDIO IS BASED ON THE GENERIC "QUADRIPHONIC".

CIRCLE NO. 21 ON PAGE 17

KEEP UP TO DATE WITH SCIENCE & MECHANICS

Science & Mechanics—the only magazine that keeps you right up to date on developments in space technology, weapons, automobiles, medicine, boats, planes, tools, new products, and exciting world events.

Keep up to date. Make sure of your home delivered copy by returning the coupon today.



SCIENCE & MECHANICS, Dept. 949
229 Park Ave., S., New York, N.Y. 10003
Yes! Please enter my subscription for one year for only \$2.98 (regular price \$4) (foreign add; \$1).

I enclose \$..... Bill me

Name _____ (Please Print)

Address _____

City _____ State & Zip _____

DX central reporting

A world of SWL info!

By Don Jensen

DXing tends to be a "lone wolf" proposition; the usual ratio is one listener to one receiver. As a result, DXers know relatively little about others in this wide world who share their enthusiasm for tuning distant stations.

But a recent study by the Association of North American Radio Clubs (ANARC) has answered some of the questions about who we are, what we do and how we do it. The survey, compiled by ANARC's Phil Sullivan and Gray Scrimgeour, brought answers from a significant sample of listeners, nearly 1,300 of them. The findings are interesting.

Though the DXers surveyed ranged in age from 13 to over 80, the hobby is essentially a youthful one. Nearly half (48 per cent) are under 21. Twenty-one percent fall in the 21 to 30 age bracket, 11 percent between 31 and 40, and 20 percent over 41. The sex bias is definitely masculine. Only two percent of those responding to the ANARC study are women.

The most popular type of DXing is short-wave broadcast listening. Some 87 percent reported they tuned the broadcast station programs on shortwave. Medium waves (540-1600 kHz) attract 47 percent. Other percentages are amateur radio listening (not transmitting) 28 percent; tuning utility communications stations, 16 percent; TV and FM DXing, 13 percent; and longwave (below 540 kHz) listening, seven percent. They total more than 100 percent because many tune more than one segment of the radio frequency spectrum.

What equipment do DXers use? Twenty percent use non-communications receivers, table models, portables and the like. Half do their tuning on communications receivers, those designed for DXing or ham radio, costing under \$125. A quarter of the survey respondents use more expensive communications sets. The remaining handful listen with surplus military equipment. Approximately two-thirds have at least one tape recorder in their DX shack.

The typical DXer is non-technical. Fifty percent build none of their own gear; another 27 percent build only simple projects or kits. When it comes to repair work, 75 percent don't, or tackle only simple maintenance of their radios.

(Continued on page 22)

ELEMENTARY ELECTRONICS

READER SERVICE PAGE

- The Editor of ELEMENTARY ELECTRONICS offers readers an easy way to get additional information about products and services advertised in this issue. Also, if you would like more information about any new product mentioned in our column "Hey, Look Me Over," it's yours for the asking. Just follow the instructions below and the material you requested will be sent to you promptly and at no cost.

- The coupon below is designed for your convenience. Just circle the numbers that appear next to the advertisement or editorial mention that interests you. Then, carefully print your name and address on the coupon. Cut out the coupon and mail to ELEMENTARY ELECTRONICS, Box 886, Ansonia Station, New York NY 10023. Do it today!

JAN./FEB. 1972

Void after July 31, 1972

ELEMENTARY ELECTRONICS

Box 886, Ansonia Station, New York NY 10023

Please arrange to have literature whose numbers I have circled at right sent to me as soon as possible. I understand that this is a free service offered by the magazine.

	1	2	3	4	5	6	7	8	9	10
	11	12	13	14	15	16	17	18	19	20
	21	22	23	24	25	26	27	28	29	30
	31	32	33	34	35	36	37	38	39	40
	41	42	43	44	45	46	47	48	49	50
	51	52	53	54	55	56	57	58	59	60

Name (Print Clearly) _____

Address _____

City _____ State _____ Zip Code _____

You get more for your money from NRI—

America's oldest and largest Electronic, Radio-Television home-study school

Compare. You'll find—as have so many thousands of others—NRI training can't be beat. From the delivery of your first lessons in the remarkable, new Achievement Kit, to "bite size," easily-read texts and carefully designed training equipment . . . NRI gives you more value.

Shown below is a dramatic, pictorial example of training materials in *just one* NRI Course. Everything you see below is included in low-cost NRI training. Other major NRI courses are equally complete. Text for text, kit for kit, dollar for dollar—your best home-study buy is NRI.

Available under NEW GI BILL

If you served since
January 31, 1955, or
are in the service,
check GI line in
postage-free card.



GET A FASTER START WITH NRI'S NEW EXCLUSIVE ACHIEVEMENT KIT

The day your enrollment is received your Achievement Kit will be on its way to you. It contains everything you need to make an easy, fast start in the Electronics training of your choice. This attractive, new starter kit is an outstanding, logical way to introduce you to home-study the way NRI teaches it . . . backed by a dedicated staff and the personal attention you should expect of a home-study school. It is your first special training aid . . . designed to make your adventure into Electronics absorbing, meaningful. Your Achievement Kit contains your first group of lesson texts; rich vinyl desk folder to hold study material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; envelopes; pencils, pen; engineer's ruler—even postage. No other school has anything like it.

OVER 50 YEARS OF LEADERSHIP




IN ELECTRONICS TRAINING

LEARNING BECOMES AN ABSORBING ADVENTURE WITH NRI TRAINING KITS

What better way to learn than by doing? NRI pioneered and perfected the "home lab" technique of learning at home in your spare time. You get your hands on actual parts and use them to build, experiment, explore, discover. Electronics come alive! NRI invites comparison with training equipment offered by any other school. Begin NOW this exciting, practical program. It's the best way to understand the skills of the finest technicians—and make their techniques your own. Whatever your reason for wanting to increase your knowledge of Electronics . . . whatever your field of interest . . . whatever your education . . . there's an NRI instruction plan for you, at low tuition rates to fit your budget. Get all the facts about NRI training plans, NRI training equipment. Fill in and mail the attached postage-free card today.

NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

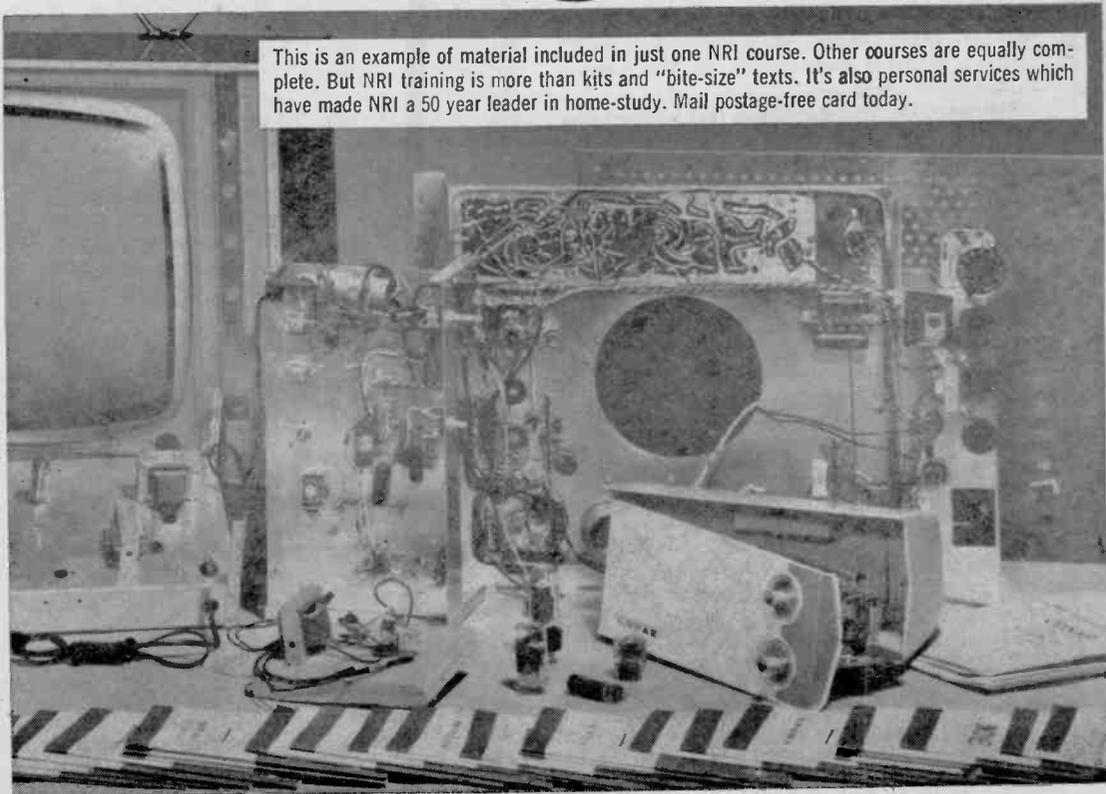This is an example of material included in just one NRI course. Other courses are equally complete. But NRI training is more than kits and "bite-size" texts. It's also personal services which have made NRI a 50 year leader in home-study. Mail postage-free card today.



DX CENTRAL REPORTING

Continued from page 16

Four of every five DXers are listeners only. Twelve percent have CB licenses, another eight percent are hams as well.

Of the more serious DXers, those belonging to radio hobby clubs, 41 percent say that they read either *ELEMENTARY ELECTRONICS*, or our former sister publication, *SCIENCE AND ELECTRONICS* (now *COMMUNICATIONS WORLD*). Three-quarters enjoy feature articles on radio stations, while 40 percent read the how-to-build-it construction projects and 30 percent like the more theoretical articles.

The limitation of the ANARC survey is that it reached only those who consider their listening efforts as a hobby, in other words, DXers. But another study, by Florida State University sociology professor, Don D. Smith, measured another facet of shortwave listening in the United States.

Professor Smith's research, published in *Public Opinion Quarterly*, was designed to show how many Americans, *other than SWL hobbyists*, listen regularly to foreign shortwave programs for their political content.

It indicated that approximately two million adult listeners tune such programs at least once a week. And more than four times that number have listened to shortwave broadcasts, of whatever type, for whatever reasons, at some time during the year.

What does this all mean? Is it just another numbers game? Maybe so, but the "lone wolf" simile now seems inappropriate. You're running with a pretty large pack!

Tiptopper. Do you sometimes feel you're a day late and a dollar short when it comes to DX-ing? Well, here's your chance to be a DX trailblazer by being one of the first to hear a brand new, rare station!

For SWL's, the impossible dream is logging Swaziland; that tiny landlocked nation completely surrounded by the Republic of South Africa. In the past it was represented on shortwave only by a mini-powered religious station, never heard in North America.

But a brand new shortwaver, Swazi Radio is scheduled to begin operation any day now, perhaps early in December, and you could be the first North American DXer to hear it!

Swazi Radio will be an all-English commercial service, with contemporary music, aimed at South African audiences. The venture is jointly owned by U.S. broadcasting executive Mark L. Wodlinger and the Swaziland government.

Eventually the station will use three transmitters, 50 kilowatt medium-wave stations on 1376 and either 539 or 602 kHz, and a 10 kilowatt shortwave station, simulcasting the medium-wave programs. Particular targets of the stations will be the South African cities of Durban and Johannesburg. At first the programs will be broadcast from 0500 to 0000 GMT, but eventually they will be extended to 24 hours.

According to Wodlinger, one of the medium-wave transmitters was in place in Swaziland's western Sandlane district, near the South African border, by mid-September. The shortwave unit was to follow it to Africa upon completion of transmitter tests Stateside.

Frankly, I haven't any idea where this new station will turn up on the dial. So you, and other DXers around the world, will have to hunt the bands for Swazi Radio. And you could be the lucky one to find it first. It's just a guess, of course, but I'd suggest prowling around 60 meters (around 4,750 to 5,060 kHz) around 0500 GMT.

Bandsweep. Frequencies in kilohertz, times in GMT. **1020**—For West Coast MWers only, look for ZCO at Nuku'alofa, Tonga just before sign off at 1000 GMT. By the way, would you believe that this Pacific islander has a tuning signal played on a Tongan nose flute? . . . **4930**—One Latin American broadcaster that has been just booming in lately is Radio Mil in Santo Domingo, Dominican Republic. You should find its Spanish language programming almost any time during the early evening hours . . . **6,093**—A nice piece of DX is Radio Somali at Mogadishu along Africa's northeast coast. New England listeners have been hearing it signing on at 0300 . . . **9,505**—A Sudanese station, announcing as "Huna Omdurman" in the Arabic language, has been heard here at 2045, with what one DXer describes as "swinging Sudanese hit tunes." Hmmm! . . . **12,175**—The only way to log Iceland these days is to catch the tests from Reykjavik's point-to-point utility station at various times during our afternoons . . . **15,084**—A brief announcement at 2025 seems to be all that's left of an English language program formerly aired by Radio Iran, Teheran . . . **17551.5**—Though seldom reported, you can hear an Argentine standard time station ticking away at 1145 to 1150 GMT. (Credits: Roy Millar, Washington; George Schnabel, New York; Mike Macken, Massachusetts; Chris Lobdell, Massachusetts; Gladys Martin, New York; Alvin Sizer, Connecticut; National Radio Club, Box 99, Cambridge, Massachusetts)

Backtalk. Congrats to Don Erickson, Riverside, California, named 1971 Man of the Year by the Association of North American Radio Clubs. The coveted award is given annually by ANARC, the organization affiliating all the major DXing clubs in North America, to a person who has contributed significantly to the listening hobby.

Erickson was cited for his work with ANARC and the International Radio Club of America, whose bulletins he publishes.

Ralph Lose, Aransas Pass, Texas, writes to ask if there's such a thing as a shortwave listening log book, a publication that gives data on

(Continued on page 106)

ELEMENTARY ELECTRONICS

FREE!
1972

BA
burstein-applebee

CATALOG

EVERYTHING NEW FOR '72!
B-A's ALL NEW 276 PAGE

**RADIO, TV &
ELECTRONICS
CATALOG**

**OUR
46TH
YEAR**

Your Buying Guide for
Everything in Electronics
... Stereo, Hi-Fi, TV's,
Radios, Tape Recorders,
CB, Kits, Tools, Books,
and Electronic Parts.

**WRITE FOR
IT TODAY!**



MAIL LETTER TO
burstein-applebee co.
3199 Mercier
Kansas City, Mo. 64111

*the tape that
turned the
cassette into
a high-fidelity
medium*




TDK SUPER DYNAMIC (SD) TAPE



TDK

Until TDK developed gamma ferric oxide, cassette recorders were fine for taping lectures, conferences, verbal memos and family fun—but not for serious high fidelity.

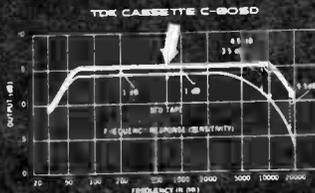Today you can choose among high-quality stereo cassette decks.



The new magnetic oxide used in **TDK Super Dynamic** tape distinctly differs from standard formulations in such important properties as coercive force, hysteresis-loop squareness, average particle length (only 0.4 micron!) and particle width/length ratio. These add up to meaningful performance differences: response capability from 30 to 20,000 Hz, drastically reduced background hiss, higher output level, decreased distortion and expanded dynamic range. In response alone, there's about 4 to 10 db more output in the region above 10,000 Hz—and this is immediately evident on any cassette recorder, including older types not designed for high performance. There's a difference in clarity and crispness you can hear.

Available in C60SD and C90SD lengths.
TDK ELECTRONICS CORP.
LONG ISLAND CITY, NEW YORK 11103

CIRCLE NO. 23 ON PAGE 17

stamp shack

Philatronics Today!

BY ERNEST A. KEHR

●● It is surprising to witness the speed with which the Intelsat communications network is knitting the widely scattered insular specks of the Pacific into a single unit. And for the stamp collector, it's interesting to note how almost each new facility is advertised with special commemoratives.

● Latest of the islands to open an earth station and issue postage stamps to mark its dedication, is New Zealand. On July 14, 1971, the dominion released a pair of multi-color designs created by Auckland artist Mark Cleverley. The eight-cent denomination, for use on airmail letters to some Pacific islands, or surface mail to overseas destinations, shows the station's parabola receiving antenna, while the 10-cent features the Satellite itself. Both designs include patterns of colored dots, each representing the various earth stations presently in operation around the Pacific and to which the New Zealand one now may communicate.

● Like the other earth stations around the world (and some of which already have been described in this column,) New Zealand's is equipped to transmit and receive signals from other places that are bounced off the satellites placed in Space by the International Telecommunications Satellite Consortium. Presently it is working with Intelsat III, which can handle 1,200 voice circuits and a single TV channel. Once the new Intelsat IV is placed over the Equator above the Pacific it will add that to its facilities as the latter promises to handle more circuits and two TV channels.

● The New Zealand station has been built on a 41-acre site near Warkworth, about 50 miles north of Auckland on the dominion's North Island. Since it is being operated as part of the Government's Post and Telecommunications Ministry, its own architects developed the plans. Wiles and Jones, Ltd., of Auckland, erected the various control buildings. The Nippon Electric Co., of Japan, supplied the technical equipment and antenna. This firm has supplied similar equipment for stations in Japan, Taiwan and a few other Pacific and African nations.

● The immensity of the operation is revealed by some statistics. The administration and equipment building alone comprises more than 13,000 square feet of space in which a staff of 18 persons can do all the necessary control work on the automated instruments.

● The antenna, which is really the heart of the system, is an architectural behemoth. Its 52-foot circular base required 2,400 tons of concrete to support the antenna, its motors and other machinery.

● Almost 400 tons of steel were required to construct the 120-foot facility which, of course, is dominated by the parabola with its 300 aluminum reflecting panels built into the 100-foot wide dish.

● Connections are possible throughout the Pacific area and the stations that already are in operation: Bartlett, Alaska and Jamesburg, Calif., in the east; at Kum San, South Korea; Ibaraki, Japan; Taipei, Taiwan; Tanay, in the Philippines; Hongkong and Sri Racha, Thailand, in the West, and Carnarvon and Moree, in Australia. Pulanta, in Guam, and Paumalu, in Hawaii, also can be reached.

All possible services will be made available to the public by the New Zealand Ministry of Posts: telephone, telex, telegraph, photograph and data transmissions. Service in the TV and motion picture film area will be offered to the N.Z. Broadcasting Corporation or other interested parties on a leasing basis.



●● During 1971, Czechoslovakia issued six special stamps in connection with Soviet Satellite communications projects generally known by the name, "Interkosmos." And while no specific technical descriptions could be obtained from Prague, we can provide Stamp Shack readers with only generalities concerning the designs: we quote:

—20 haleru, a stylized picture of a Space telecommunications centre.

—40 haleru, Interkosmos 3, a geophysical satellite designed to study propagation of radio waves about the earth and cosmic radiation. Background shows stylized version of earth with magnetic north pole. Interkosmos 3 func-

tioned between June and November, 1970.

—60 haleru, Meteorological, satellite, used by Socialist countries for study of cosmic meteorology. Background shows map of polar regions charted by the satellite.

—1 koruna, A Cosmonaut with sensors hitched to him for checking of vital body functions, with charts tracing heart, brain and other organs' reaction to Space travel. In background is Voschod satellite.

—1.20 koruna, Interkosmos 4, which operated from October 1970 to January, 1971, to measure short-wave solar radiation.

—1.60 koruna, The rocket used in Interkosmos experiments to launch satellites into orbit from a launching pad.

●● Monaco is another country that issued a couple of "communications" design stamps, but couldn't provide details when asked for them. Both are intended to mark the 25th anniversary of UNESCO. The 40-centime depicts an ancient alchemist in his laboratory while surrounded by such modern things as a Space rocket, telecommunications antenna and transmitter.

● The 80-centime has a medieval monk at his




Czech issues expound Russian Satellite communications projects.

writing desk and flanked on the left, by motion picture film and an open book, and on the right, by symbols of communications: a radio microphone, TV antenna, telephone and Space Satellite.

● **What's New?** Although the use of full color already has been widely adopted by stamp magazines in Europe and Asia, American publications have remained with their staid black-and-white. The announcement by Scott Pub-



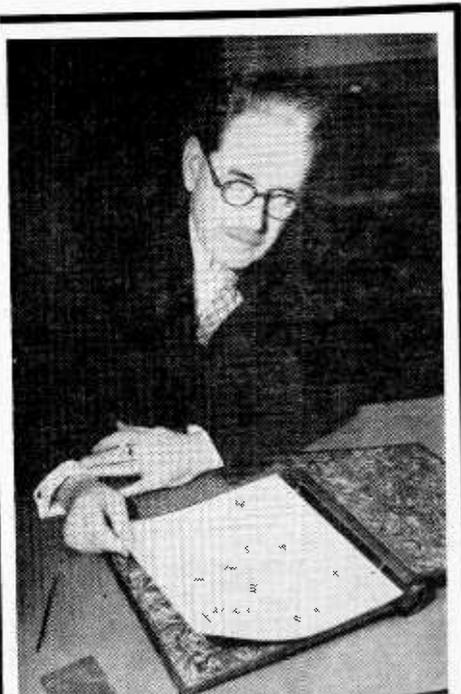Then and now. Communications through the ages depicted by Monaco for UNESCO.



From Liechtenstein comes word that the late Theodore E. Steinway will be honored by a stamp to be issued in September, 1972. Mr. Steinway, who headed the Steinway & Sons piano firm until his death in 1956, was selected as the first American in the principality's "Pioneers of Philately" series because of his many contributions towards the progress of stamp collecting. He is shown here looking at a Polish stamp portraying Ignace Paderewski when the pianist was president of his homeland and signed by him for Mr. Steinway, a long-time friend. *(Photo by Kehr)*

lications, Inc., that its "Scott's Monthly Journal" and some parts of its "Standard Postage Stamp Catalogue" series would henceforth be produced in color, was hailed by the philatelic world. Early samples of the publications give promise of an entirely new era in philatelic literature and probably will encourage competitors to give American readers something to which foreigners have become accustomed. ■





LITERATURE LIBRARY

61. Kit builder? Like wired products? EICO's 1972 catalog takes care of both breeds of buyers at prices you will like.
62. Want some groovy PC boards plus parts for communication projects? Then get a hold of International Crystal's complete catalog.
63. Now available from EDI (Electronic Distributors, Inc.): a catalog containing hundreds of electronic items.
64. Bargains galore, that's what's in store! Poly-Paks Co. will send you their latest 8-page flyer.
65. Dynascan Corp. has released a new catalog of B&K precision test equipment for a variety of uses.
66. Before you build from scratch, check the Fair Radio Sales latest catalog for surplus gear.
67. Get your copy of Hallicrafters' "Shortwave Puts You Where It's At." Get started today on shortwave radio for more fun tomorrow!
68. Want a deluxe CB base station? Then get the specs on Tram's super CB rigs.
69. Get the scoop on Versa-Tronics' Versa-Tenna with instant magnetic mounting.
70. Prepare for tomorrow by studying at home with Technical Training International. Get the facts on how to step up in your job.
71. Pep-up your CB rig's performance with Turner's new M+3 mobile microphone.
72. CB at its best! See the whole lineup in Midland's colorful new CB brochure on high-power transceivers and automatic scanning monitors.
73. CB antenna catalog by Antenna Specialists makes the pickin' easy. Get your copy today!
74. Get all the facts on Progressive Edu-Kits Home Radio Course. Build 20 radios and electronic circuits; parts, tools, and instructions included.
75. Olson's catalog is a multi-colored newspaper that's packed with more bargains than a phone book has names.
76. Custom Alarms reveals how inexpensive professional alarms can really be. Install one yourself. Circle 76 for exclusive catalog.
77. New magnetic nutdrivers 1/4 in. and 5/16 in. are available from Xcelite. They are color-coded with fixed handles in regular, extra long, and super long styles.
78. Troubleshooting without test gear? Get with it—let Accurate Instrument clue you in on some great buys for your test bench.
79. Burstein-Applebee offers a new giant catalog containing 100s of big pages crammed with savings.
80. Two leaflets by R. L. Drake Co. are available. One is on their SPR-4 communications receiver; the other on the SW-4A international shortwave broadcast receiver.
81. Edmund Scientific's new catalog contains over 4000 products that embrace many sciences and fields.
82. Pick Cornell Electronic's 10th anni. catalog and discover yesterday prices. Tubes go for 36¢ and 33¢. Plus many other goodies!
83. Allied Radio Shack wants to introduce you to the colorful world of electronics. Discover great buys from wide selections. Get the details from Allied today!
84. It's just off the press—Lafayette's all-new 1972 illustrated catalog packed with CB gear, hi-fi components, test equipment, tools, ham rigs, and more.
85. Mosley Electronics, Inc. is introducing 78 CB Mobile Antenna Systems. They are described and illustrated in a 9-page, 2-color brochure.
86. RCA Experimenter's Kits for hobbyists, hams, technicians and students are the answer for successful and enjoyable projects.
87. You can become an electrical engineer only if you take the first step. Let ICS send you their free illustrated catalog describing 17 special programs.
88. GC Electronics has the part you are looking for! Pick up their free catalog and build again without worry.
89. CBers, Hams, SWLs—get your copy of World's Radio Labs 1972 catalog.
90. Hy-Gain's new CB antenna catalog is packed full of useful information. Get a copy.
91. B&F Enterprises has an interesting catalog you'd enjoy scanning. Goodies like geiger counters, logic cards, kits, lenses, etc. pack it. Get a copy!
92. Heath's new 1972 full-color catalog is a shopper's dream. Its pages are full of gadgets and goodies everyone would want to own.
93. For a whole packet of information on how to succeed in electronics, contact Cleveland Institute of Electronics. An application for enrollment is included.
94. If you want courses in assembling your own TV kits, National Schools has 10 from which to choose. There is a plan for GIs.
95. Free 1972 Catalog describes 100s of Howard W. Sams books for the hobbyist and technician. Includes books on projects, basic electronics and many related subjects.

ELEMENTARY ELECTRONICS

Box 886

Ansonia Station

New York, N.Y. 10023

Please arrange to have this literature whose numbers I have circled at right sent to me as soon as possible. I am enclosing 25¢ to cover handling. (No stamps, please).



1-2/72

61	62	63	64	65	66	67	68	69	70
71	72	73	74	75	76	77	78	79	80
81	82	83	84	85	86	87	88	89	90
91	92	93	94	95					

Indicate total number of booklets requested
Sorry, only 20 circled items maximum.

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

Not Valid After July 31, 1972



Hank Scott, our Workshop Editor, wants to share his project tips with you. Got a question or a problem with a project you're building—ask Hank! Please remember that Hank's column is limited to answering specific electronic project questions that you send to him. Sorry, he isn't offering a circuit design service. Write to:

**Hank Scott, Workshop Editor
ELEMENTARY ELECTRONICS
229 Park Avenue South
New York NY 10003**

Oh, The L With It!

I haven't the time or the patience to wind coils for radio projects. Local parts stores seldom have the coils I need, only a couple of types of Miller coils. Where else can I get coils?

—A. G., New York NY

We have found that most stores in relocated Radio Row in New York City carry too few parts. A lot of goodies are listed in a catalog you can get from Hazelton Scientific Co., Box 163, Hazel Park, Mich. 48030.

Ah, So!

I'm having trouble finding replacements for Japanese transistors. Where can I get them?

—F. A., Bronxville NY

Write to Semitronics Corp., 265 Canal St., New York, NY 10013. Send them 25 cents for a

catalog which lists over 100 basic types of semiconductors which can be used as substitutes for more than 12,000 types. Also, your local HEP (Motorola) dealer has a HEP Substitution Guide that'll save you grief and money, too!

They Got Em!

A few issues back, one of your readers needed a 41 tube. Barry Electronics, 512 Broadway, New York NY 10012 has 'em for only \$1.25 each.

—C. F. M., Clarkton NC

We have friendly readers. My Thanks.

Pile of Iron

I have acquired a number of used transformers and chokes most of which have no manufac-

(Continued on page 104)

Learn more about electronics this easy way by mailing the coupon below

EVERY ISSUE of ELEMENTARY ELECTRONICS brings you easy-to-follow aids for better understanding of theory and applications of electricity and electronics...in word and picture with diagrams that are easy to follow...a source of up-to-the-minute information for everyone interested in electronics who wants to increase his knowledge... followed every issue by thousands of CBers, Hams, SWLs, Experimenters.

Save up to \$4.00

MAIL THE COUPON below today and you can save up to \$4.00 over the cost of buying copies on the newsstand... and be sure you don't miss a single information-packed issue... because the mailman will bring your copy to your door just as soon as each issue is off the press.

Elementary Electronics, 229 Park Ave. South, New York, N. Y. 10003
 I don't want to miss a single issue. Enter my subscription for: Dept. 619

3 years—18 issues—\$9.00
 SAVING ME \$4.50 over the newsstand price

2 years—12 issues—\$6.00
 SAVING ME \$3.00 over the newsstand price

1 year—6 issues—\$3.00
 SAVING ME \$1.50 over the newsstand price

I enclose \$ _____
 Please bill me

NAME _____
 STREET ADDRESS _____
 CITY _____
 STATE _____ ZIP CODE _____


Outside U.S. and Canada: Add \$1.00 per year





IT'S AN ENGINEER'S LIFE

by Jack Schmidt

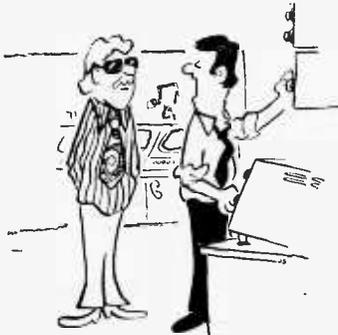

"You shouldn't dress like that—someone will mistake you for an announcer."



"Don't you just love these remote jobs that get us out of the studio?"




"I know what they told you in school, kid, but when Mr. Markum says 'Turn up the volume', you turn up the volume. Markum owns the station."



"... and when I run this one up and down real fast, the guys downstairs know it's time for their coffee break."



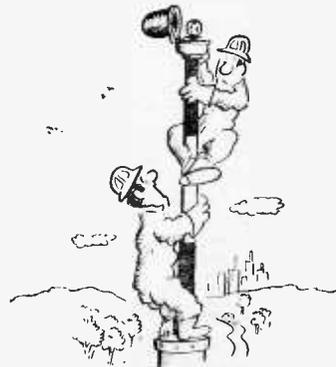"I got the job, Hon... but it's not real TV... it's educational television!"



"No. I thought you had the new bulb!"

the ABC's of

CITIZENS BAND ANTENNAS

BY LEN

BUCKWALTER

Everyone in CB starts out with approximately five watts of transmitter power—actually 2 to 4 watts output but who's quibbling. But after the power leaves the set, the differences become enormous. Your signal may reach out ten miles, while a neighbor easily communicates forty miles. Results of that same power in the hands of NASA engineers can be phenomenal; space men can take five watts

and relay data from a craft circling Venus 22 million miles away!

The difference, of course, is in the transmitted frequency and antenna system. It's the antenna that is the single most influential item and the one you can do something about. Proper antenna selection, installation and operation explain why some people put out a pounding signal, while others drown hope-



lessly in the noise. Maybe you can't construct a multimillion-dollar receiving horn (NASA's secret for getting 4-million miles per watt), but there are things you can do to improve range. A good place to start is with some info on how these CB sky hooks operate.

The Dynamic Duo. Two members of radio's nobility, Hertz and Marconi, lend their names to principles concealed in today's antennas. The Hertz antenna, or *half-wave dipole*, unlocks the theory behind almost all others. If you think of radio signals as a series of water waves—a comparison, incidentally, that makes professors wince—you can get a half-decent view of the half-wave at work. One complete radio-wave cycle is shown in Fig. 1A. As it emerges from the transmitter it travels down the coax in a

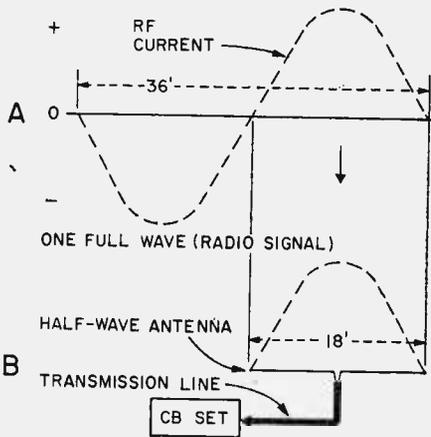


Fig. 1. RF current distribution in half-wave antenna at maximum positive peak sine-wave.

succession of waves that measure 36 feet in length for CB. Instead of crests and troughs of water, each wave consists of electromagnetic energy which constantly reverses its polarity—the number of polarity changes in each second gives us the frequency.

Half a Dipole. Consider a basic antenna for sending or receiving such a wave. It's the *half-wave dipole*, or one that's cut to 18 feet for CB. As we'll see, it's all that is needed to accommodate the complete 36-foot signal since only one polarity of the wave is present at any given time. Refer

to Fig. 1B. Note that the antenna is capturing the positive portion of the signal in our example. An instant later, the wave will change polarity—to its negative phase—and excite the wire with current of the opposite polarity. Thus each half of the wave takes its turn occupying the wire.

The half-wave dipole is not only an efficient antenna for its length, but it's a standard against which the engineers measure the performance of all others. It is not a practical CB antenna because better performance is possible by special designs which evolve from the half-wave idea.

For cars, a half-wave CB antenna would be mechanical folly; an 18-foot rod would take a real beating from trees, power lines and underpasses. Fortunately, it's possible to cut a half-wave antenna in half to shrink its proportions to reasonable size. The result, shown in Fig. 2, is the basic Marconi

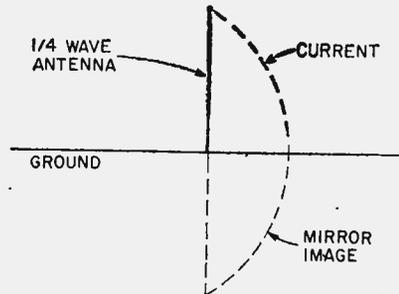



Fig. 2. 1/4-wave antenna is popular for mobile. May be physically shorter with loading coil.

antenna, known now as the quarter-wave whip. The ground portion of the system simulates the missing half of the original antenna (note the mirror image) and the radio wave gets the same treatment as before. Now a mobile antenna can be half the height—9 feet—and still be tuned to the signal.

Technical Considerations. Before we see how manufacturers take these basic antennas and come up with dozens of variations, consider some restrictions. Although radio waves of lower frequency hug the earth and travel around its curve, the 27-MHz CB variety are propagated mainly line-of-sight. When sunspots are numerous, there is much long-range skip as signals bounce back to earth. Sunspots are now diminishing and the mid-70's should create poorer hunting grounds for illegal skip-workers. But the horizon, hills and other obstructions restrict normal range unless the antenna is placed

at the highest possible location within the legal limit. This is basically 20 feet over a man-made or natural formation.

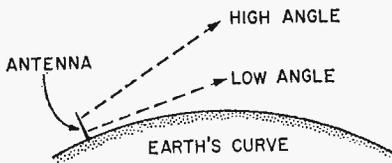Radiation angle is another quality. Antennas vary in their ability to launch a signal



that remains close to the earth's surface, as illustrated in Fig. 3A. Note that a high angle of fire causes loss of coverage—so the lower the angle, the better.


Polarization tells whether the radio wave is transmitted along a horizontal or vertical path. Usually this is determined by how the antenna is mounted: in the horizontal or vertical plane. The standard for CB operation is vertical polarization because it's not only easy to mount a vertical whip on a car, but the antenna radiates in every direction. This is important for mobile operation since the base station may not know where the car is located, although there are CB communications on certain horizontally polarized and directional CB antennas, as described in a moment. With this basic theory we can analyze major CB antenna types now being offered, starting with the base station.

An Old Timer. Once a popular antenna, the *ground plane* is waning because improved models can put more metal in the air where it counts. The ground-plane occasionally appears as an economy model because it's simple to construct and the cost is low. It is usually a 9-foot vertical whip similar to the quarter-wave antenna described earlier. But when placed atop a building, there's no metal car roof to supply the missing ground, so the ground-plane antenna must have *radials*. These are three or four horizontal rods which droop out of the base of the antenna. Though widely spaced, they electrically perform as though solid ground surrounded the antenna at the bottom. Effectively, they supply that mirror image aloft, where it's needed.

The Big Stick. An antenna which outwardly resembles the ground-plane, but has features of its own, is the half-wave vertical shown in Fig. 3B. Instead of 9 feet tall, it's double that height and thus presents greater area for signal radiation. The radials stemming out from the bottom contain *loading coils*

Fig. 3A., left, illustrates how high radiation angles can waste power.

Fig. 3B, right, Antenna Specialists M-317 full wave vertical uses loading coils to shorten radials.

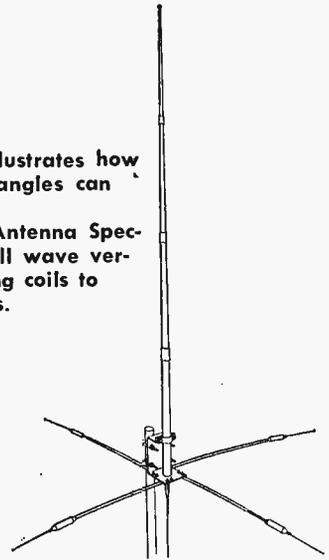

which provide the electrical effect of much longer rods. One item not visible in Fig. 3 is a matching coil inside the fiberglass base. It's there for a good reason. Recall that the basic half-wave antenna shown earlier had

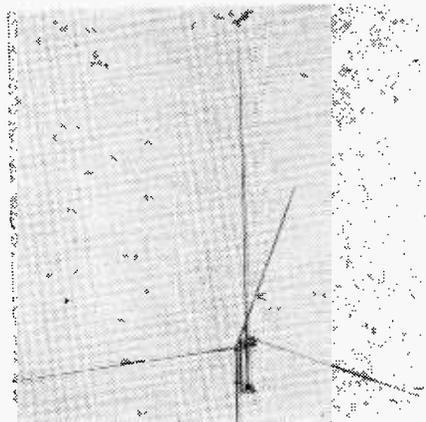


Fig. 4. Another version of groundplane, $\frac{5}{8}$ wave provides gain. By Hy-Gain, the CLR2.

a transmission line connected at the *center* of the dipole. The reason is that the half-wave antenna at this point displays an *impedance*, or electrical load, very close in value to that of the transmission line. The standard line for CB is 52-ohm coaxial cable and such a line may connect directly to the center of the half-wave antenna for maximum transfer of energy. But try to connect coaxial cable to the *end* of a half-wave antenna and a tremendous mismatch wastes almost all the power. So the manufacturer installs a matching coil at the base

e/e CB ANTENNAS

to transform impedance and come up with a proper electrical match.

Another model is the 5/8-wave antenna shown in Fig. 4. It reaches up to just under the maximum height of 20 feet and uses radials for an electrical ground. (The radials also prevent the radiated power from being wasted in the cable coming up from below.) This model, incidentally, uses the designation "colinear," which means it electrically operates with elements stacked in the vertical direction. The antenna, however, incorporates coils which shorten the total height to keep it within the regulations.

A variation in base antennas is the one shown in Fig. 5. Most antennas tend to radiate strongest signals near the base where the cable is attached. This is where maximum electrical currents usually exist and it's current that's converted into the radio wave. In this antenna, the designers raise the radiating point toward the top. They state the higher position raises the signal so it's better able to clear nearby obstacles.



Fig. 5. A new twist in CB antennas, this vertical radiator pumps power from near its top to skim nearby obstacles. From Avanti, its the Astro-Plane.

Power Booster? Search through antenna literature and you'll see statements that promise to "convert your 5-watt signal into 40 watts." How's it possible without violating the 5-watt law? The answer is that radio signals are squeezed into a narrow arc instead of radiating in every direction at once. The idea is not unlike a bare light bulb whose illumination is focussed by lenses or reflectors into the slim beam of a spotlight. The concentrated light is many times

brighter—but only over a small area.

The same effect is easy to achieve with radio signals by adding elements which are slightly longer and shorter than the basic half-wave dipole. For example, look at the five-element beam in Fig. 6, which is aiming toward the left. The Driven element, which is a half-wave dipole, receives the signal


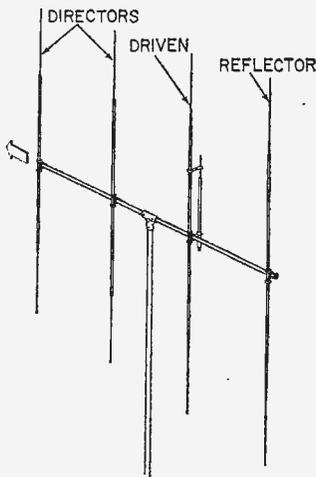


Fig. 6 Additional elements direct and reflect to provide greater Effective Radiated Power.

from the transmitter and emits it to the right and left. The part of the signal that strikes the Reflector is reflected back in the desired direction (leftward). The first Director also intercepts part of the signal from the Driven element, only this time the signal is radiated again, but in the desired direction. The remaining Director does the same thing as its neighbor. The secret of the elements ability to reflect or direct is in their length and spacing. These factors cause the wave to be delayed (or phased) just the correct amount to cause reinforcement or cancellation in the desired directions. The result is a powerful "lobe" of concentrated wattage.


A beam can only have one reflector, but the number of directors vary. (The 5-element beam, for example, has three directors.) In the example shown, the manufacturer states a 9.4 dB gain, which means the 5-watt signal has the effect of about 20 watts. Highest gain occurs when two complete beams are "stacked together." You must, of course, use a rotator motor with most beams to direct the lobe of energy to the desired direction. Little signal is sent and received from the sides or back of the array. Some CBers

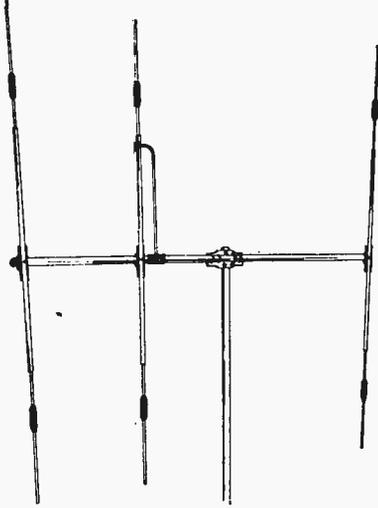use two antennas for this reason: a non-directional type to first acquire the distant station, followed by a switch to a beam for better communications. Note in Fig. 7 that loading coils are used in a 3-element beam to reduce its overall size to about two-thirds that of a conventional beam.



selecting horizontal polarization, for example, he might reduce interference from signals transmitted in the vertical mode. He might obtain better communications with another beam that can also select the polarization to produce strongest signals. The cubical quad (Fig. 10) is another beam

Fig. 7., left, Mosley GA-3D Mini-beam uses loading coils to simulate longer elements. Fig. 8., right, Antenna Specialists M-219 has electronic switching for non-mechanical beam rotation.

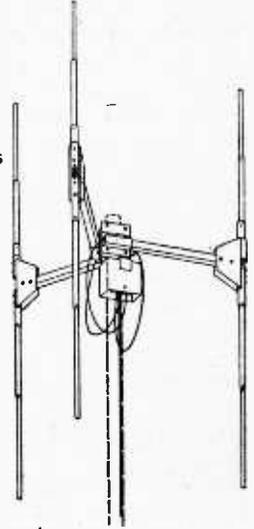

A beam which needs no rotator is the three-element "scanner" shown in Fig. 8. The CBER has a control box next to his rig to switch in pairs of elements which determine the desired direction. One position is "omni" to energize all three rods for conventional reception and transmission in all directions (omnidirectional).

Several other beam antennas include one model that contains both horizontal and vertical elements (Fig. 9). The CBER has a control box that selects either set for choosing the direction of polarization. By

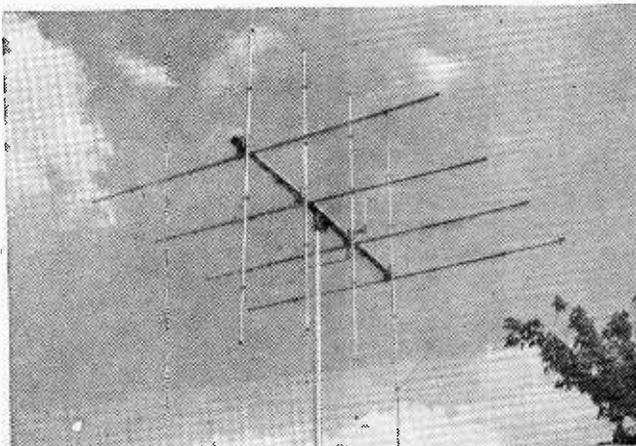
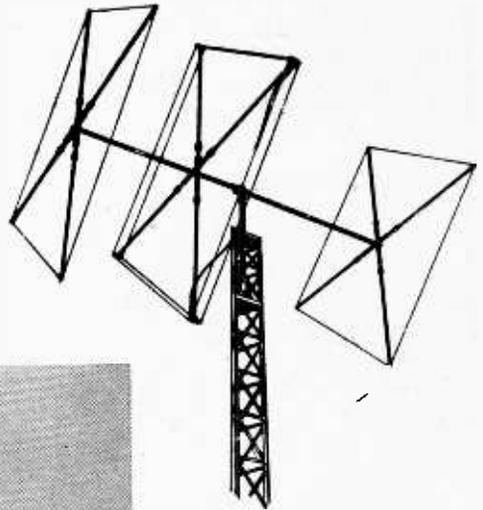



Fig. 9. Multi-polarized beam, Cush Craft CFB-8 lets CBER select best polarization mode to fit conditions, left. Fig. 10. Cubical Quad by Mosley adapted to dual polarization. This model is MCQ-27 VH.

CB ANTENNAS

whose mode is switch-selectable.

The Mobiles. Antennas for the automobile do not have the variety of shapes enjoyed by their brothers on base, but they show plenty of ingenuity. The reason is that mobile signals would best be transmitted and received from a 9-foot rod growing out of the center of the car roof. Since this is thoroughly impractical, a full-size quarter-wave whip ends up on the bumper. There it may suffer from low position and distortion in its pattern; the signal tends to travel best in the direction of most metal. For example, a whip on the rear right bumper operates strongest toward the front left. This has led to a variety of shortened whips for mounting in more favorable positions.

Shrinking an antenna down from the

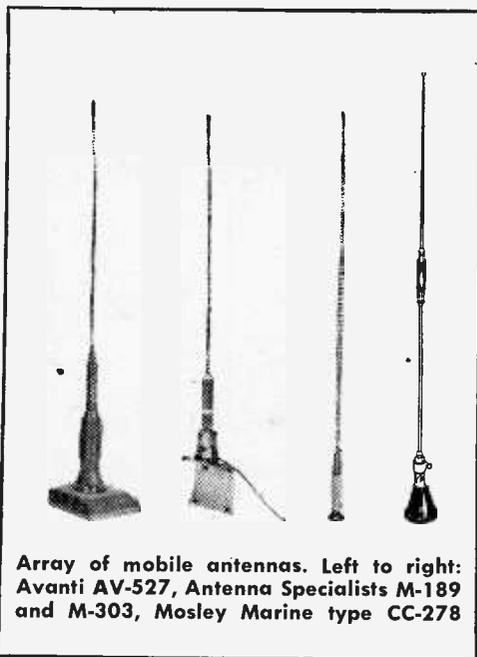

Array of mobile antennas. Left to right: Avanti AV-527, Antenna Specialists M-189 and M-303, Mosley Marine type CC-278

CB ANTENNA GLOSSARY

Beam Antenna

An array of elements, approximately one-half wave in length, which concentrate the transmitted and received signal into a narrow arc.

Bi-directional

Transmits (or receives) in two directions, usually 180 degrees apart. This is pattern of the half-wave dipole.

DB Gain

The power increase of an antenna compared to that of a standard half-wave dipole (or what engineers may call an "isotropic radiator"). For each 3 dB (decibel) increase, power is **doubled**. For example: If a 10-watt signal is increased 3 dB, it becomes 20 watts; for 3 db more, it becomes 40 watts.

Dipole Antenna

A basic half-wave antenna (approximately 18 feet long for CB) fed at the center. It forms the driven element of the beam antenna and is the standard against which other antennas are measured.

Direct Wave

The portion of the radiated signal which travels directly, or via line-of-sight, between transmitter and receiver. This is the principle path taken by CB signals. The "ground wave," which follows the earth's curve, is extremely limited on CB.

Effective Radiated Power (ERP)

The CB transmitter produces a fixed amount of watts, but this may be varied by antenna gain, height and other factors. ERP is the result of these variations. For example: A 3-watt signal

applied to a directional antenna with 3 dB gain has an ERP of 6 watts. The gain, however, occurs within a confined pattern.

Front-to-Back Ratio

Applied to directional beams, this rating describes the amount of signal pickup from the front compared to that picked up at the rear. Stated in dB, the higher the better. High ratios (say 30dB instead of 20dB) mean less signal is lost to the rear during transmission. Less interference is also heard during reception.

Gamma Match

This is a special rod assembly added to the driven element of a beam antenna for impedance matching. It allows a 52 ohm coaxial cable to be connected to the driven element at a 52-ohm point for best transfer of energy.

Ground Plane

A basic antenna type, usually 9 feet in height with three or four drooping radials to form an electrical ground.

Impedance

A rating, given in ohms, which describes the amount of opposition to a flow of AC current. The most common impedance in CB is 52 ohms: the rating for transmitter outputs, receiver inputs, coaxial cables and antennas. These items may be interconnected for maximum power transfer since their impedances are the same or "matched".

Loading Coil

Turns of wire embedded or positioned in an antenna element to electrically create the effect of a physically longer antenna. Although the



Hot car, hot rig. CBers on the road are recognized by characteristic antennas. Shown, DX Cat by Hy Gain, 88" tall, it folds.

coil consumes part of the energy, the loss is often outweighed by such advantages as a smaller antenna for roof-top mounting on a car or compact elements in a beam.

Lobe

The area of an antenna pattern of maximum power concentration. Used to describe the strongest radiation from a directional antenna.

Null

The area of an antenna pattern of little or no signal, usually due to cancellation by two opposing, or out-of-phase, waves.

Omnidirectional

Transmits (or receives) equally well in all directions. Also known as non-directional.

Phasing Harness

A device which permits two antennas to be connected together to a common line without creating an impedance mismatch.

Polarization

The relative position of the lines of force which emanate from the antenna as a radio signal. Polarization is usually vertical if the antenna is a vertical rod; horizontal if the antenna lies parallel to the earth's surface. Most CB'ers use vertically polarized waves because a vertical antenna lends itself best to mobile mounting. Some antennas offer both modes.

Sky Wave

The part of the antenna signal which travels above the horizon and is lost to space unless reflected back toward earth by the ionosphere. Communication via sky wave, or "skip", is illegal in CB.

9-foot size is done by the loading coil, but the position of the coil is subject to much variation. A low point is good for mechanical stability and protection. A high point, on the other hand, is good because it lifts the signal further above the roof—but it's more susceptible to damage. Another problem with a lofty coil is that it is electrically sensitive to any swaying in the antenna. It could cause fluttery signals by detuning the rod. A compromise chosen by some manufacturers is the *continuously loaded* whip. The whole antenna is a coil—a wire embedded in plastic which spirals all the way up.

Which way to go?

One controversy that's hard to settle, though, is what's better, a small antenna (say 2½ feet) with a large loading coil placed atop the roof, or a 5-foot whip with a smaller coil placed lower on the trunk deck? Both antennas are electrically similar, but a larger loading coil tends to waste slightly more energy than the longer rod. Yet the smaller antenna permits a higher mounting point. Consider, also, that a roof-

Splitter

A device which recovers AM and FM broadcast signals from a CB antenna for reception on the car radio. Also prevents CB transmitter from overloading the car radio when antenna is shared.

SWR

Standing Wave Ratio, or the amount of forward power compared to reflected power. This figure tells the efficiency of the antenna system; the lower the ratio, the better. High SWR means something's mis-matched and line or antenna are reflecting power back to the transmitter. The result is power loss due to heating in the line or signal cancellation. An SWR of 1:1 is theoretically perfect, while 3:1 means about 25 percent of the power is being lost. Your system should be less than 2:1.

Transmission Line

A pair of wires designed to transfer radio-wave currents between transmitter and antenna. Most common pair for CB is the coaxial cable constructed of an outer shield and inner conductor and rated at 52 ohms (RG 58/U). Because of its electrical shield, the line may run close to other wires, metal or underground.

Wavelength

The distance, usually measured in meters, between corresponding points of radio wave. It is also the distance travelled during one cycle (one Hertz). The wavelength of CB is 11 meters, or approximately 36 feet. The basic half-wave antenna is 18 feet; the quarter wave is 9 feet.


e/e CB ANTENNAS

top mounting involves a more lengthy installation since you'll have to fish a coaxial cable through the car headliner. And so the dilemma continues. . . .


On the problem of antenna mounting the news is good. You'll find a tremendous variety of mounting styles. There are mobile antennas which grip the car through magnetic pull, clip on in moments, insert into the trunk-lid crack with no holes, while others neatly fasten to campers or trucks. As our photos show, these and other mounting styles offer something for everyone. There's even a double-whip arrangement which derives a beam-like effect on an automobile.

A Pattern Emerges. In preparing this article, I asked several major CB antenna manufacturers the same question: "Where does the CBer go wrong in his antenna installation?" The most frequent cause of trouble isn't the antenna, but the coaxial cable. The line develops short circuits through poor soldering technique at the connectors, or sometimes the cable is crushed during installation and its electrical value changes. If soldering isn't your dish, purchase one of the prewired cable assemblies now widely available. Solderless coaxial connectors also ease the job.

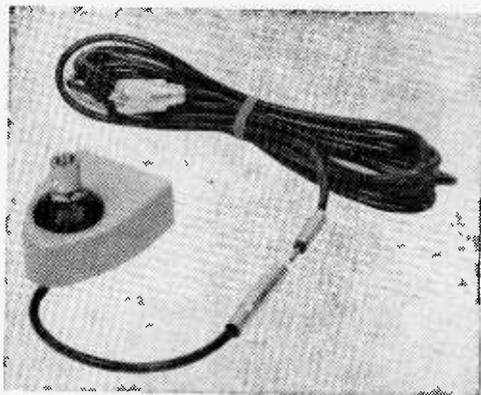One complaint echoed by some manufacturers is that the new CBer is usually



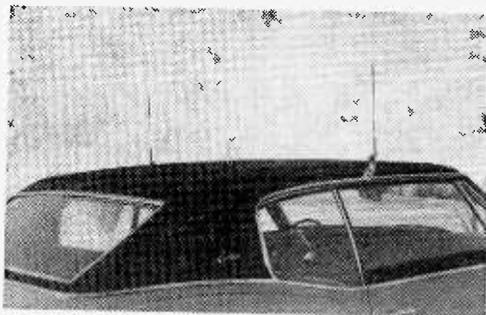Break Cable, above, eases installation for Newtronics Hustler. Below, Model DTG Double Talk reduces fading from motion.



surrounded by buddies with helpful advice on antenna installation. Bitter experience suggests something's amiss. If all manufacturers could sing one line of good advice, the lyrics would surely be: *Read the instructions!* ■

Moby Dick's play pen is Captain's Paradise




Imagine, all these men do is play with boats all day! But these men are future sea captains studying at navigation school in Bremen, West Germany. Here they learn the fine points of navigation on a miniature sea, equipped

with artificial currents simulating oceanic conditions. They maneuver their ships with the aid of radio control. There's even a tiny harbor where they learn to dock. Some work is fun, I guess.

—Myrtle Gronk

They go down to the sea each day and play with radio-controlled model boats to earn their masters license. Model size, water flow and time duplicate sea conditions. It's cheaper that way and also a lot safer.

THE

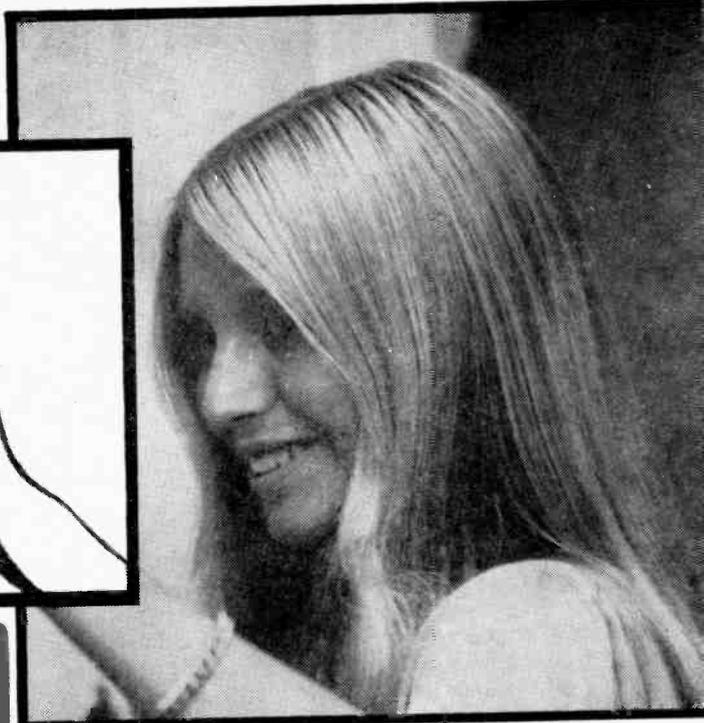

ELOCKTRON

Makes a door open as if by magic!

—by Herb Cohen

What's an Elocktron? A misspelling of "electron"? No, it's an electronic lock, just like you may have seen in some science-fiction movies, where the hero makes a door open by simply putting a small piece of plastic next to a plate near the entrance.

You can make a door open the same way! The Elocktron key is actually a tiny crystal-controlled tuned circuit in a small plastic box. When you put this key next to a plastic panel mounted in the wall near the door, the power circuit behind the panel will activate the latch release, and open sesame!

Where can you use the Elocktron? How about your front door? Even better, a door you want to keep your little brother (or your kids, or maybe even your wife) from opening, such as the door to your lab or workroom, or to your gun closet.

How It Works. The power circuit consists of a transformer-operated fullwave power supply (transformer T1, diodes D1 through D6, filtering capacitors C1 and C2), two oscillators, an amplifier, and an SCR. The 117-to-12 VAC stepdown transformer isolates the power circuit from the line, for shock protection. Transistor Q3 is a power

oscillator at 18 MHz, generating a strong magnetic field around its tank coil, L2.

The key contains a small resonant circuit consisting of L4 and C12, tuned to 18 MHz, with a 1N34A diode that rectifies any current induced in the LC circuit. When the coils in the key are brought close to the coils in the power circuit, and the key's L4 is then close to L2, current through diode D4 activates the other circuit in the key, which is a crystal-controlled citizen's band oscillator, Q4. The oscillator radiates a signal, at the crystal frequency, from coil L3.

When the key is next to the power circuit and L4 is next to L2, then L3 in the key should be next to coil L1. Coil L1 is associated with Q2, a crystal-controlled oscillator tuned to the same frequency as the key oscillator, L3 and Q4. When L3 is near L1, their signals will mix. Slight differences in frequency between the two signals will appear at the base of Q1 as an audio signal, and will be amplified by Q1 to fire silicon controlled rectifier SCR1 and actuate the solenoid that releases the door latch.


Making an Elocktron. The layout is not critical, except for the placement of coils

L1 and L2 on the power board. They should be placed rather close together, with the wrapped ends facing the front panel. The author put them $1\frac{1}{2}$ in. apart, mounted all the power components on a perforated board $2\frac{3}{4} \times 7\frac{1}{4}$ in., and used $\frac{5}{8}$ -in. stand-offs between the perforated board and the plastic front panel, to allow L1 and L2 to be as close as possible to the front panel.


A heat sink was used on Q3, the 2N2270. Most of the components can be mounted on the side of the perf board next to the front panel, except for Q3, the transformer, and the large filtering capacitors. Incidentally, if 500uf, 15V electrolytic capacitors are more easily obtained than 1000uf types, then use two of the 500uF types in parallel for C1, as the author has done. The SCR should provide about an ampere to open the lock, so that any one of the General Electric C106 series should do the job.

The author used a clear plastic sheet for the front panel, $1/16 \times 9 \times 4\frac{3}{4}$ in., but the size is not critical. The panel can be sprayed any color, or covered with decorative material; this depends on the wall in which you flush-mount the power circuit, next to the door. The portion of the front panel in front of coils L1 and L2, next to which the key is placed, can be color-coded to match the key-box. Or it can be colored like the rest of the panel if you want to play it real cool and if your eye is good at judging just where the key should be placed to open the lock.

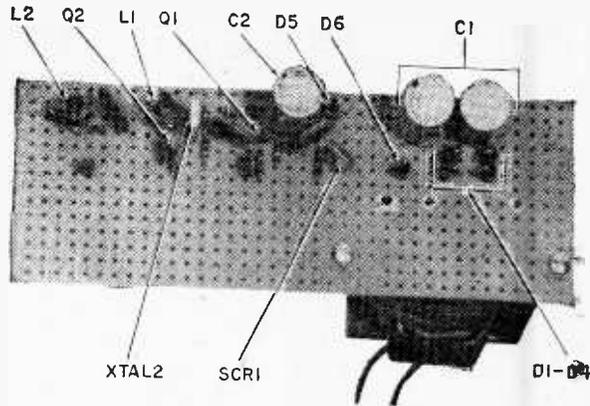The electronic key is contained in a small plastic box. The author used one measuring




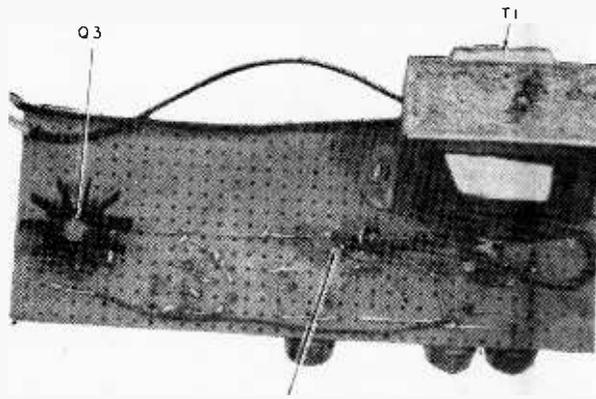The large capacitors were later moved to the T1 side of the board, to allow the key to get very close to coils L1 and L2.





TEST LAMP
(See text)

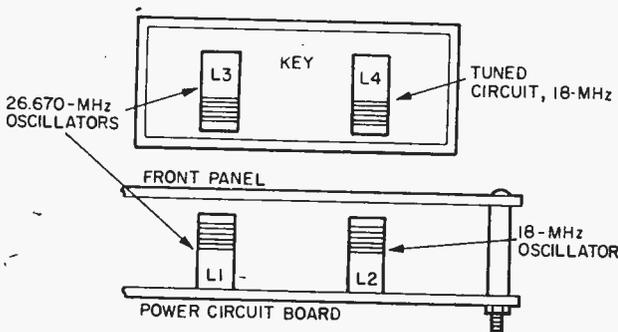about $2 \times 1 \times \frac{3}{4}$ in. Coils L3 and L4 should be the same distance apart as L1 and L2 are. The key should be marked in some way so that it can be placed quickly in the proper position against the lock. One method is to paint each half of the key-box



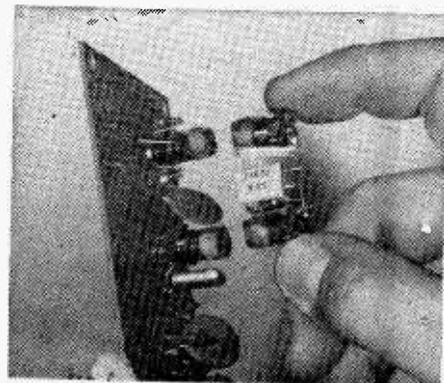Pictorial and photo show relative positions of the four coils when the electronic key is in position to activate the circuit.



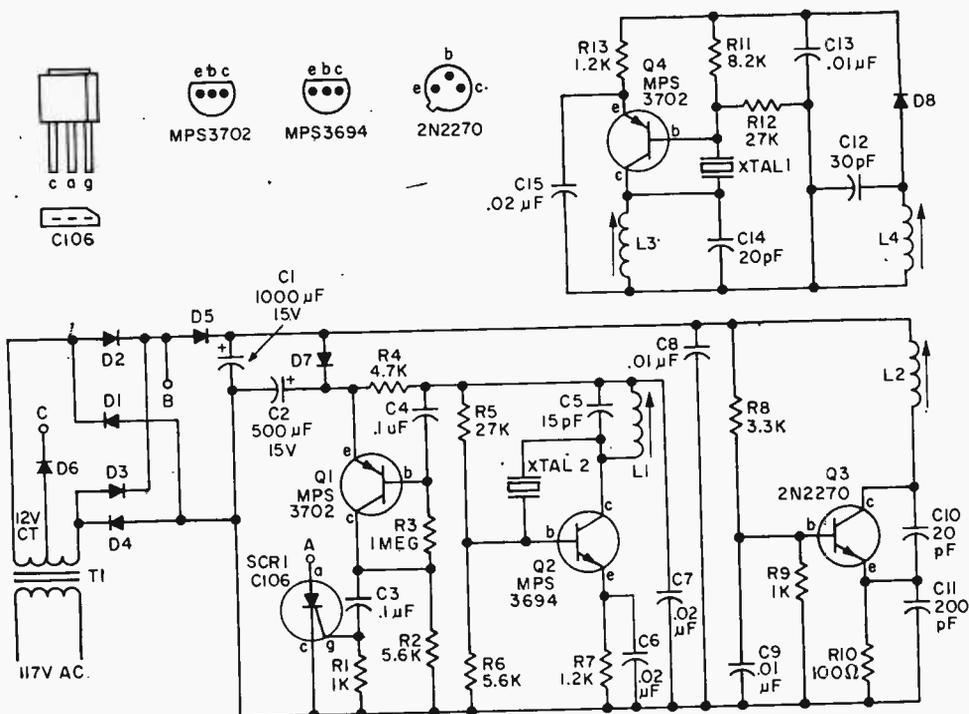

Schematic of the Elocktron. The four coils are lined up in position for operating the door-latch release, with L3 close to L1, L4 near L2.

a different color. Use the same colors as on the power-circuit front panel, if you've decided to color-code the section in front of the coils. Also, you'll need another kind of marking to tell which side of the key-box to put up against the lock panel, because the key will work only when coils L3 and L4 in the key are less than half an inch from

coils L1 and L2 in the lock panel.

After you've built the Elocktron, you can test it with a meter or by attaching a 6-volt lamp between terminals A and C, or a 12-volt lamp between terminals A and B. The lamp should light when coils L3 and L4 are close to L1 and L2, respectively.

Adjustments. To tune L4 in the key, place

PARTS LIST FOR THE ELOCKTRON

- C1—1,000 µF, 15 VDC electrolytic capacitor (Lafayette 34F55177 or equiv.)
- C2—500 µF, 15 VDC electrolytic capacitor (Lafayette 34F55169 or equiv.)
- C3, C4—.1 µF, 75 VDC
- C5—15 pF capacitor
- C6, C7, C15—.02 µF capacitor
- C8, C9, C13—.01 µF capacitor
- C10, C14—20 pF capacitor
- C11—200 pF capacitor
- C12—30 pF capacitor
- D1-7—50 PIV, 1A silicon diode, Motorola HEP 154
- D8—1N34A silicon diode, Motorola HEP 134
- Q1, Q4—Silicon transistor, pnp (Motorola MPS3702)
- Q2—Silicon transistor, npn (Motorola MPS3694)
- Q3—Silicon transistor, npn (RCA 2N2270)

- SCR1—Silicon controlled rectifier (GE C106, any suffix—see text)
- L1-4—Receiver oscillator coil (Lafayette 99E62028)
- R1, R9—1,000-ohm, ¼-watt resistor
- R2, R6—5,600-ohm, ¼-watt resistor
- R3—1,000,000-ohm, ¼-watt resistor
- R4—4,700-ohm, ½-watt resistor
- R5, R12—27,000-ohm, ¼-watt resistor
- R7, R13—1,200-ohm, ¼-watt resistor
- R8—3,300-ohm, ¼-watt resistor
- R10—100-ohm, ½-watt resistor
- R11—8,200-ohm, ¼-watt resistor
- T1—Power transformer: primary, 117 V 50-60 Hz; secondary, 12 V @ 2 A (Stancor P-8130 or equiv.)
- XTAL1, XTAL2—26.670 MHz
- Misc.—Perforated board, sheet plastic, small plastic box, standoffs, bolts, nuts, hookup wire, line cord.



E/LOCKTRON

the key next to the front panel, in the "operate" position, with L4 about half an inch from L2 (and L3 the same distance from L1). Put a DC voltmeter across C13 in the key, and adjust the slug in L2 until the voltmeter peaks, which will be at 2 to 5 volts, depending on, among other things, your estimate of half an inch. If the voltmeter does not peak, set the slug in L4 to the center of the coil and adjust the L2 slug until the meter peaks. If needed, adjust both slugs for peak. If you can peak L2, you know that Q3 is oscillating. If you can then peak L4, you know that the L4-C12 tuned circuit is operating correctly by picking up the 18-MHz signal radiated from L2.

Oscillators Q2 and Q4 can be aligned with a grid-dip meter set to the crystal frequency of 26.670 MHz, if you happen to have a grid-dip meter. Another alignment method is to use a CB transceiver with a very short antenna. First disconnect the wire between R8 and C8 on the power circuit, disabling the Q3 oscillator. Bring L1 near the receiving antenna of the CB rig, set to channel 2 or to whichever channel gives you a rushing noise when L1 approaches the antenna. That noise is the clue that Q2 is oscillating. Reconnect the wire between R8 and C8, put L1 near the CB antenna again, and bring the key close. If you hear an audio tone that varies with the distance between L1 and L3, then you know Q4 is oscillating, because you hear the beat frequency. The tuning slugs in L1 and L3 need not be as accurately positioned as those in L2 and L4.





The size of two packs of razor blades is about as small as the electronic key can be made, with all the components involved.

You need only adjust the L1 and L3 slugs so that they're the same distance inside their respective coils, or both protruding the same distance from the coils.

The Door-Latch Release. The device that allows the door to be opened is an *electric latch release*. This is simply a solenoid-operated catch that, when actuated, pulls back to release the lock-bolt, allowing the door to be pushed open from outside. Connect a 12-volt latch release between A (the SCR anode) and B, or connect a 6-volt latch release between A and C.

Electric latch releases are available to work with almost any type of door lock, and are mounted in the door-frame opposite the lock. The frame may have to be cut in deeper to accommodate the solenoid, and has to be cut out in front to allow the latch-bolt to clear the frame when the solenoid pulls back the catch. Note that when the electric latch release isn't used, a key must be used to open the door from outside, as the latch release cannot be pushed back by hand.

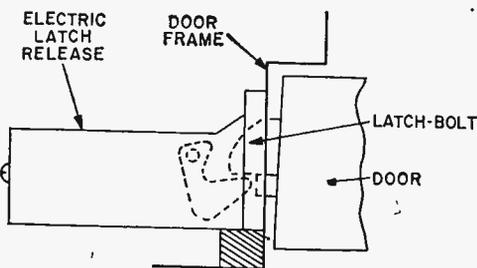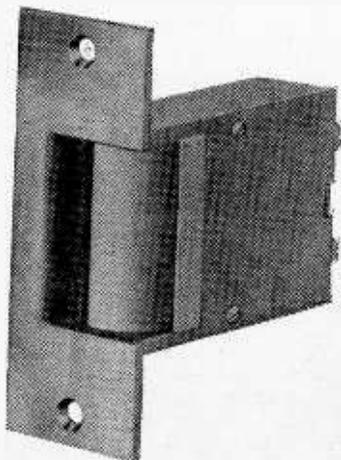Many hardware stores carry electric latch releases, such as those made by the Trine Manufacturing Corp. Trine has nine models
(Continued on page 106)



The Trine 005 electric door opener at left is one of several types that can be used, depending on the lock and door-frame. In the top view of the installed opener (above), the shaded portion indicates the small section of door-frame to cut out for the latch-bolt clearance.

e/e snaps in a...



Toyo Cassette Pack Adapter

**IT MAKES YOUR
8-TRACK PLAYER
GO CASSETTE**

What do you do when you're fully geared to 8-track cartridges and the hit album you want is available only on cassette? You can either cry or utilize a Toyo model SCP-580 Cassette Pack.


The Toyo Cassette Pack is an adaptor for playing cassettes on any 8-track cartridge player or recorder. It closely resembles a standard cartridge with a bulge up front. To play a cassette, you simply load it into the Cassette Pack and then insert the pack into the player just like any other 8-track cartridge. Press the one (and only) control button and the cassette starts to play. Press the button again and the cassette stops.

How It Works. The Toyo Cassette Pack contains a built-in solid state amplifier with a voltage-regulated power source. When the pack is plugged into the cartridge player two spring loaded fingers press against the

player's program shift contacts (the ones tripped by the foil on the cartridge tape). The fingers pick up the voltage across the contacts and feed it to the pack's voltage regulator. The pack can work with any cartridge player having 9 to 24 volts across the contacts,—which covers just about every player currently available.

Inside the cassette pack is a capstan idler wheel, an exact duplicate of the one inside an 8-track cartridge. The wheel is turned by the player's capstan. Two rubber drive belts wrapped around the capstan idler drive the cassette player's capstan and the cassette take-up spindle.

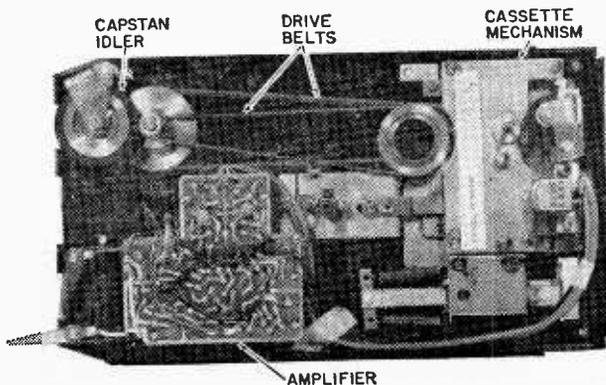The signal from the cassette pack is fed to two induction coils positioned where the cartridge tape normally passes over the playback head. The induction coils *induce* the cassette's signal into the cartridge player's head (there is no direct connection).




Inside the cassette pack is a stereo amplifier, cassette mechanism and a drive system for the cassette capstan and take-up reel. The drive system is via rubber belts from the capstan idler.

e/e TOYO CASSETTE PACK ADAPTOR

How It Handles and Performs. Unlike earlier attempts at cassette packs, the Toyo SCP-580 does not stick way out in front of the player where it can interfere with a gearshift or a passenger's knees. The Toyo sticks out but two inches, because half the cassette is inside the cartridge slot.

As far as we could determine the Toyo Cassette Pack adds no extra wow and flutter to the player; the total wow and flutter is essentially that of the cartridge player. The Toyo's frequency response was at least the equal of most 8-track players (and cartridges): ± 3 db 50 to 6000 Hz (using standard test tape).

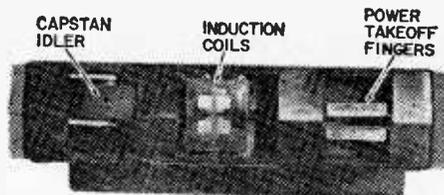
With one exception the Toyo Cassette Pack could be used with any 8-track cartridge player (mono, stereo or 4-channel). The exception was the 8-track player sup-




Business end of the Toyo cassette pack has a capstan idler, induction coils where the cartridge tape usually passes over the player's head, and power take-off fingers that take operating power from the player's track switching contacts.

plied as standard equipment on Plymouth autos (probably applies to all Chrysler players); the cassette pack would not lock into the Plymouth player.

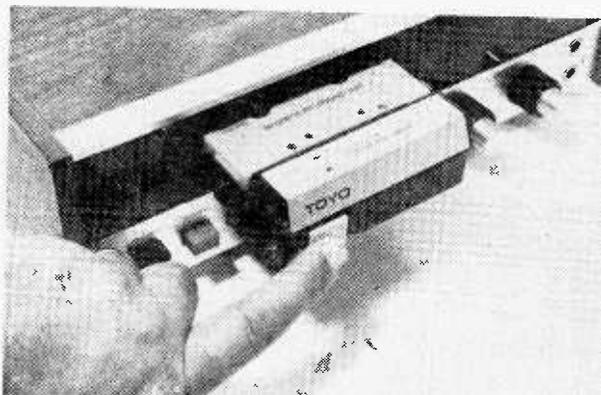Priced at \$29.95, the Toyo SCP-580 Cassette Pack is just about the cheapest way to enjoy both 8-track cartridges and cassettes. For additional information circle Reader Service No. 52 on page 17.



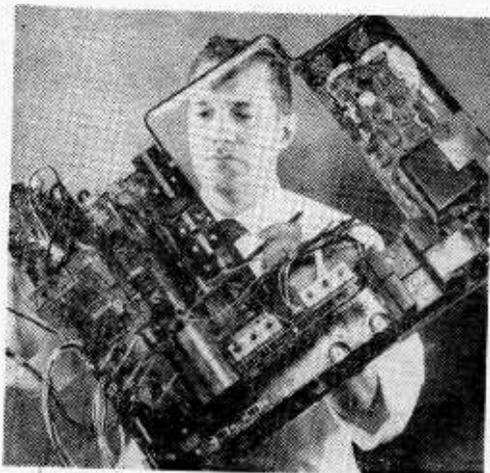To play a cassette you simply insert the loaded cassette pack into the cartridge slot and press the start-stop button. There are no fast speeds, but then 8-track players don't usually have them either.




100% SOLID COLOR

Can you pick up the components of your color television with one hand? And, that's only one advantage, and a minor one, of the new RCA 100 per cent solid state Accu-Color set. Solid state technology also means easier at-home servicing since the Accu-Circuit modules are interchangeable from set to set. So if anything goes wrong, just plug in the new part. Some of these models also include an AccuMatic Color Monitor which automatically locks in the proper color level. By the way, the five sets with this automatic tuning device also require 35 per cent less electrical power to operate than the vacuum tube variety.

—Myrtle Gronk

ELEMENTARY ELECTRONICS

Build The Balanced Bridge Game

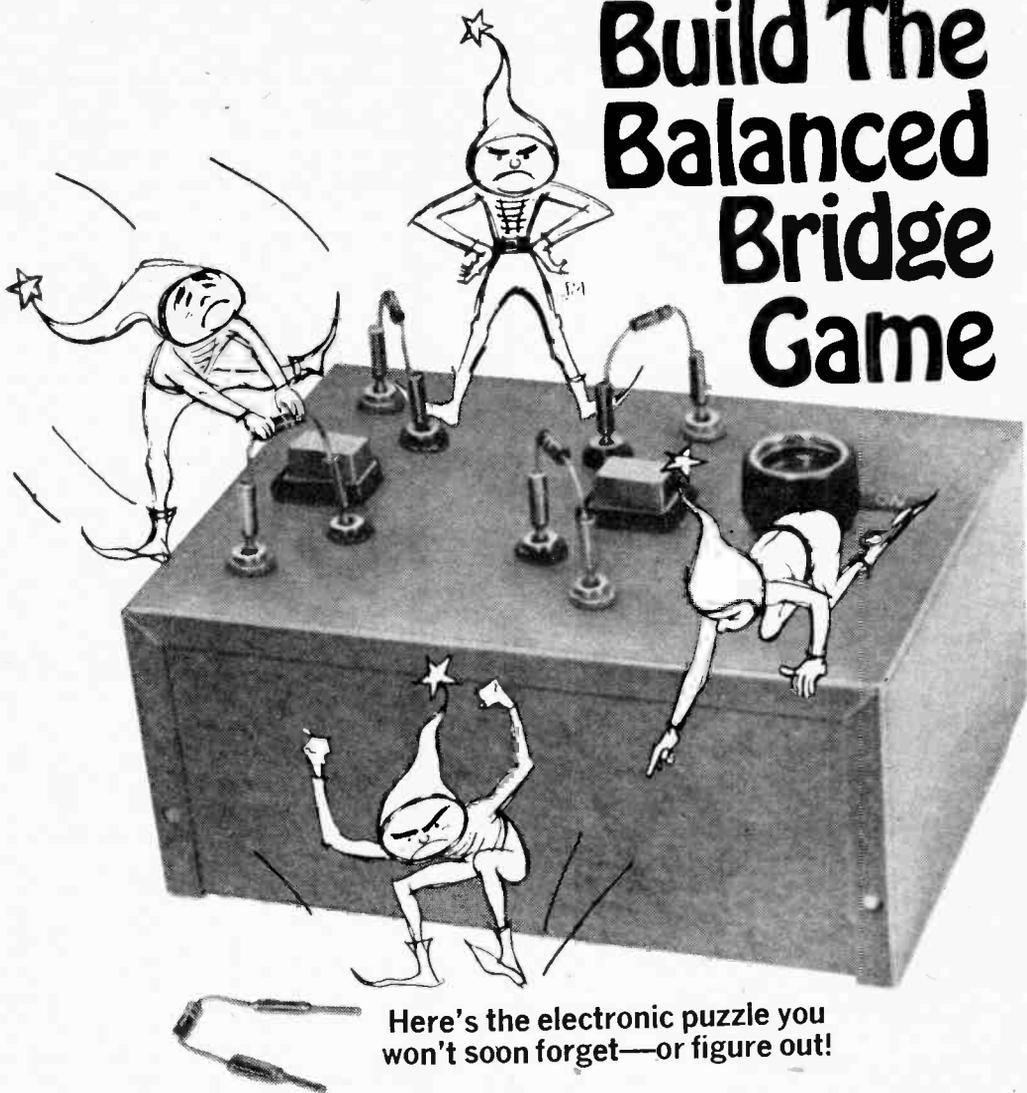

Here's the electronic puzzle you won't soon forget—or figure out!

by Ron Benrey

How's your sense of balance? We mean, your ability to mentally balance our electronic bridge game. If it's good, you might find the key and unlock this fascinating puzzle's mystery in a few moments. But, we're warning you—even veteran mah jongg experts have been known to throw up their hands in utter disgust, after trying their skill at our little game of chance. Is it skill that rewards the player with the sweet sight of victory, or plain old-fashioned rabbit's-foot luck? Try our *Balance Bridge* game, and see for yourself!

Besides being great fun, this easy-to-build electronic game teaches you all about one of the most important electronic circuits

yet devised: the Wheatstone Bridge. But, let's talk about fun first. The game is deceptively simple to play. The contestant starts out clutching a fistful of resistors (with their identifying color bands obliterated by painting them over). Four resistors will, when plugged in the *correct* terminals on the puzzle, cause the internal bridge circuit to be *balanced*.

So far, you'd figure that even your kid brother stands a winning chance. But, in order to complete the game and win points, he's got to make both "error" lamps go out. That's the hitch. If the wrong resistors are plugged in, or, if the right resistors are plugged into the wrong terminals, one of



BALANCED BRIDGE GAME

the error lamps will light. Better give your brash kid brother a healthy handicap!

The idea, of course, is to find the correct—or, winning—resistor combinations. And, then insert them into the correct terminals, so that both lamps remain unlit. You can make the puzzle as easy or hard as you wish. Just vary the number of resistors that the player has to work with! See our table of resistor values to get some idea of the several variations of puzzle complexity you can create.

The real trick, incidentally, to winning this puzzle is to set up a methodical approach by trying the various possible resistor combinations until you find one that works. Since most people don't work in a methodical fashion . . . well, we needn't say any more. And, to further confuse the head scratchers and nail biters even more, all the camouflaged resistors look alike, so it's impossible to memorize a solution to the puzzle. Luckily for you, though, head scratching isn't necessary in order to understand the Wheatstone Bridge.

Sir Charles' Bridge. The Wheatstone Bridge, as you probably guessed, is named after its inventor, the English physicist, Sir Charles Wheatstone. This basic circuit is used to measure electrical resistance with great accuracy. Figure 1 shows the drawing of Sir Charles' bridge in its most familiar form. It's traditionally drawn in the shape of a four-sided diamond, each leg representing a resistor element.

A voltage source connects to the "top" and "bottom" points of the diamond; a sensitive voltmeter (or, more often, a sensi-

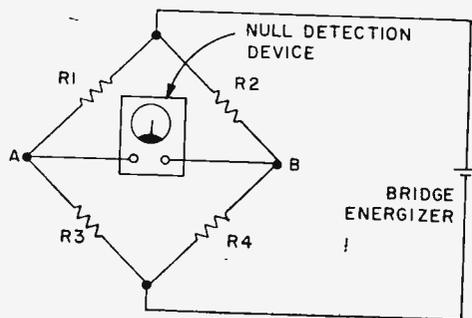


Fig. 1—The Wheatstone bridge, as it is usually drawn, in a diamond configuration. When $R1/R3 = R2/R4$, the meter will read zero volts.

tive current-measuring instrument called a *galvanometer*) is hung across the diamond's side points A and B. Actually, the diamond configuration is a bit confusing, since it hides the fact that a Wheatstone Bridge is really only two voltage dividers connected back-to-back to a voltmeter or galvanometer.

We've redrawn the circuit in Fig. 2, showing how the Wheatstone Bridge works. Note that the voltmeter is simply indicating the voltage potential *difference* between the outputs of both dividers. Clearly—and this is an important point—if the outputs of the two voltage dividers are equal, the voltmeter will read zero volts.

Suppose the lefthand pair of dividers has a higher voltage output than the right-hand pair. Now the meter reads a positive voltage. If the right-hand pair's voltage output is higher than that of the left-hand set, then the meter will read a negative voltage.

Piecing the Puzzle Together. If you examine the schematic diagram of our electronic puzzle, you'll see that its heart is the basic Wheatstone bridge configuration—with one important difference. Instead of fixed resistances, the arms of our *Balanced Bridge* game consist of a pair of pin jacks. They're arranged so that leads of a resistor can be plugged into them. When the player inserts four appropriate resistors so that he produces a balanced bridge, he has solved the puzzle. More likely, though, he will create an unbalanced bridge, lighting one of the two error lamps.

These lamps are controlled by two darlington amplifier transistors, each wired to the two side points of the bridge diamond. One lamp lights when the bridge is unbalanced on one side of the diamond. The other lamp lights when the bridge is unbalanced in its other side.

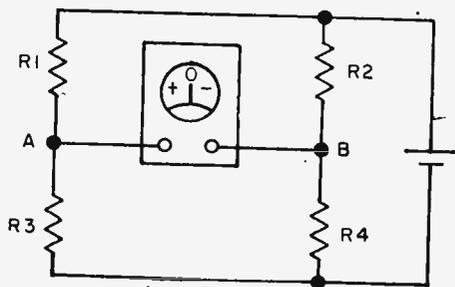


Fig. 2—The Wheatstone bridge, drawn to show that it is really a pair of voltage dividers with a voltmeter between the two.

Both lamps extinguish when the bridge is balanced, or when one or two resistors are inserted into pin sockets, but still don't provide electrical continuity within the bridge!

Groups of resistors can be plugged into the *Balanced Bridge* game in several "correct" ways. Reason is, the bridge is a symmetrical circuit. Left and right sets of bridge arms, as well as the upper and lower pairs, can be integrated without unbalancing the circuit.

Note that the lamp circuits are not sensitive to slight imbalances due to the nature of the driver transistors. If you decide to experiment and produce your own game resistance values, here is the general formula for bridge balance.



At balance: $R1/R3=R2/R4$

Jigsaw Gyration. Our *Balanced Bridge* game is housed in a 3-in. X 5-in. X 7-in.

aluminum minibox. As our photos show, both transistors and all associated inter-connection wiring are mounted between the terminals on both pilot-lamp holders, the pin jacks, and S1. Parts placement is entirely non-critical; feel free to alter the layout if you wish. Keep one precaution in mind. Slip lengths of wire insulation over the transistor leads to eliminate any chance of accidental short circuits.

Three batteries are necessary for this project. Reason is, the bridge, itself, requires a "floating ground"; the 22½-Volt battery takes care of this. Next, two 6-Volt voltage sources are needed to provide power for both lamp-driver transistor circuits. Special biasing techniques are used for both transistors; separate batteries perform this function. Cement all batteries in place on the top-half of the minibox with general-purpose cement. Solder connecting leads directly to

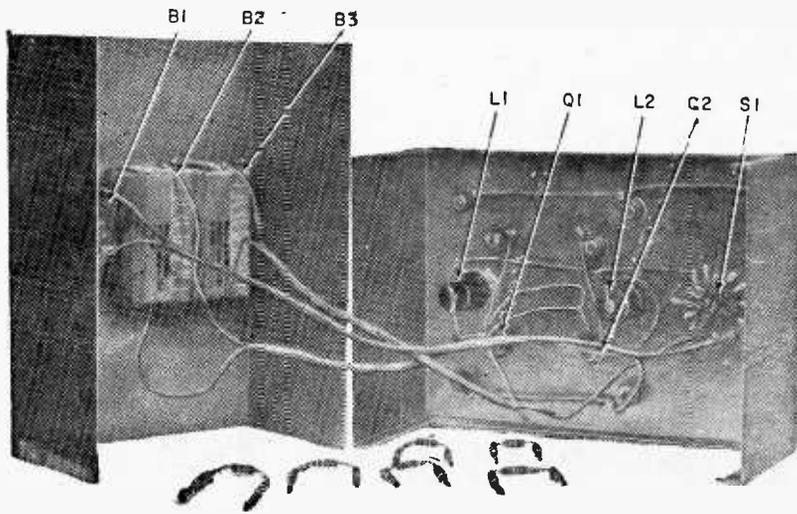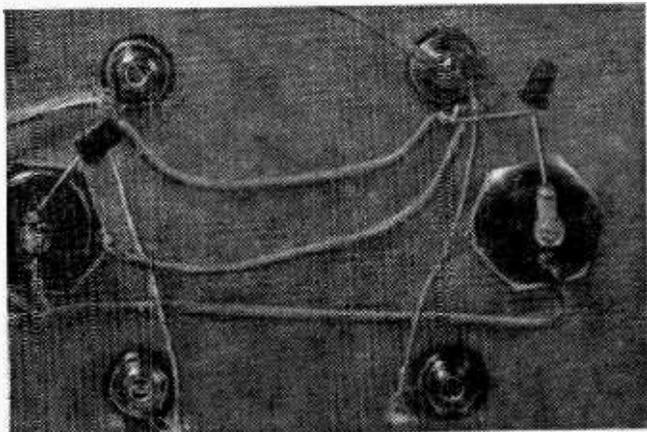In the close-up at right, note that all the transistors are mounted between the pilot-lamp holders and the nearest pin jacks. The photo below shows one possible layout of parts, but the placement isn't critical. Just be sure to put pieces of wire insulation on the transistor leads to prevent any chance of short circuits.





BALANCED BRIDGE GAME

the terminals. Construction of the *Balanced Bridge* ends after you've soldered pin plugs to the wire leads of each resistor needed to play the game.

To Find or Not to Find. Not everybody's parts collection has a pair of 2N5306 darlington transistors floating around. Looking in *Motorola's* HEP Replacement Semiconductor catalog, you'll see that the nearest NPN darlington amp listed is their type S-9100. Its characteristics are close enough to the author's original type specified.

And don't make the mistake of thinking that just any transistor will do in this circuit. A bi-polar transistor's input bias current flow will upset the delicate balance of the bridge.

Darlington amps, have exceptionally high gain and very high input impedance; this solid-state configuration neatly fits the bridge's bill for a no-load, on-off transis-

torized switch. You can order the HEP S-9100 from *Lafayette Radio Electronics* on special order. Also, try *Burstein-Applebee* as an alternate source for the S-9100. Again, ask to have the transistor placed on special order for you.

One final point. If electronics buffs will be playing the game, paint all resistor bodies as suggested earlier. For your other friends, leave the resistors alone. The mysterious colored bands will probably add an additional note of confusion to the game. ■

Balanced Bridge Game Resistor Combinations

A simple game for the kids:

R1=47K, R2=100K, R3=22K, R4=47K


Slightly harder for your friends:

R1=1K, R2=10K, R3=47K, R4=100K, R5=5K (or 4.7K). There are many workable combinations in this group.

Hardest yet, for MENSA types:

R1=10K, R2=100K, R3=68K, R4=33K, R5=220K

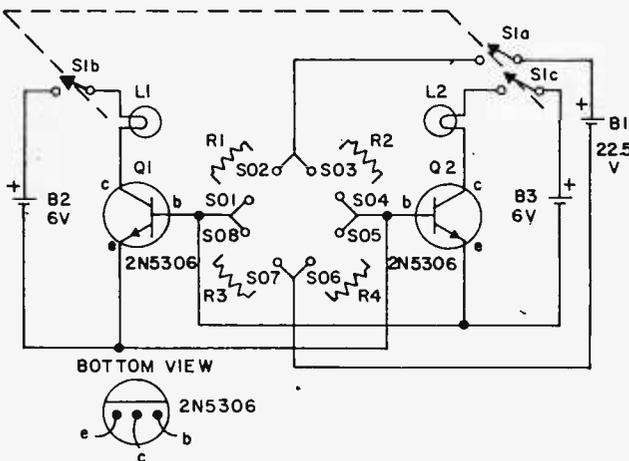Add as many additional odd-valued resistors as you like. The more, the merrier!



PARTS LIST FOR THE BALANCED BRIDGE GAME

- B1—22½-Volt battery (RCA type VS084 or equiv.)
- B2,B3—6-Volt battery (RCA type VS068 or equiv.)
- L1,L2—6.3-Volt @ ¼ amp pilot lamp—type 46 (Calectro E2-441 or equiv.)
- Q1,Q2—darlington amplifier transistors (GE 2N5306 or Motorola HEP series S-9100). See text
- S1—4-pole, 2-position rotary switch (Calectro E2-167 or equiv.)


- S01-S08—panel-mount pin jacks (Calectro F2-879 or equiv.)
- 1—pilot light socket assembly with red lens (Calectro E2-407 or equiv.)
- 1—pilot light socket assembly with green lens (Calectro E2-408 or equiv.)
- 1—1-in. diameter knob (Calectro E2-720 or equiv.)
- Misc.—3-in. x 5-in. x 7-in. aluminum minibox (Bud type CU-2108-A or equiv.), #22 stranded wire, pin plugs (Calectro F2-872 or equiv.), solder, etc.

E/E looks at new...




Here is true four-channel sound, for only \$174.95. Toyo's Quadrio 707 cartridge tape player produces four discrete channels of sound, through four separate amplifiers, and also plays 2-channel sound from any stereo source, such as phono, FM-stereo tuner, or reel-to-reel deck. Circle No. 57 on Reader Service Page.

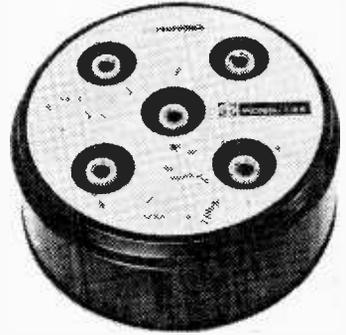Have a group "listen-in" with the Koss T-4A connector box, which provides private stereo listening for up to five people at a time. Six inches in diameter, the T-4A has a walnut-like base and a spun aluminum panel, costs \$12.95. Circle No. 58 on Reader Service Page.



A Marantz receiver for only \$199? The AM/FM-stereo 2215 is rated at 30 RMS watts continuous power (15 per channel), and offers tape monitoring, speaker switching, high and low filtering, and controllable FM muting, plus the tuning, tone-control and switching facilities expected in more expensive receivers. Circle No. 59 on Reader Service Page.

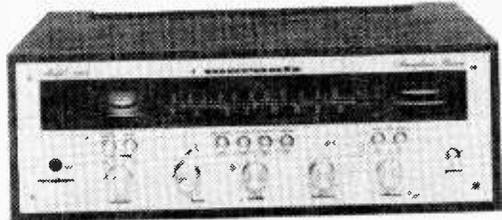☒
A four-speaker headphone is the latest addition to Lafayette Radio's line. The F-500 coaxial stereo headphone, priced at \$49.95, has a woofer and a tweeter in each earpiece, along with a crossover network. Circle No. 60 on Reader Service Page.



HI-FI COMPONENTS



The pollution is as high as an airplane's eye


□ Massive air strikes are being launched against one of our most deadly enemies—the polluter! Grumman Ecosystems is leading these strikes with high-flying photoplanes, like those used in the hotter wars to track down polluters from the air, electronically. These spotters are equipped with side-looking radar systems, topographical mapping equipment and other electronic and photographic detection devices. After hours of surveillance, these airborne laboratories return to their base loaded with all the necessary ecological data from the sur-

rounding area.


These spy planes carry sensitive electronic gear which is effective day or night. Cameras equipped with infrared film can pick up oil slicks above and below the surface of the water, even at altitudes up to 2,000 feet. Cameras with polarizing filters can catch the glint of the sun's rays off pollution on the surface of the water as well as under it. Infrared film can detect variation of color—the non-polluted areas will appear red while instances of dumping will appear off-color. These planes also have a "Thermal Infrared



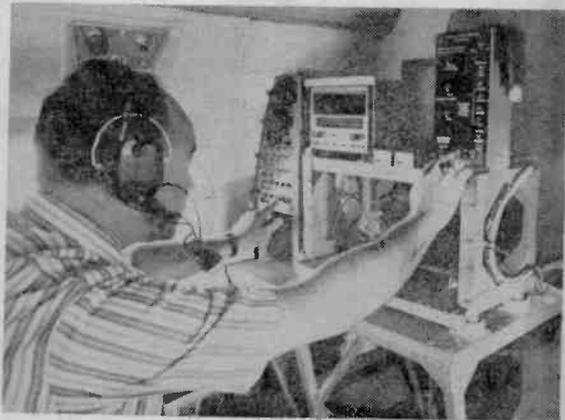The Grumman Ecosystem aircraft, once an effective espionage aid in wartime, are now loaded with electronic devices to track down new enemies—polluters.



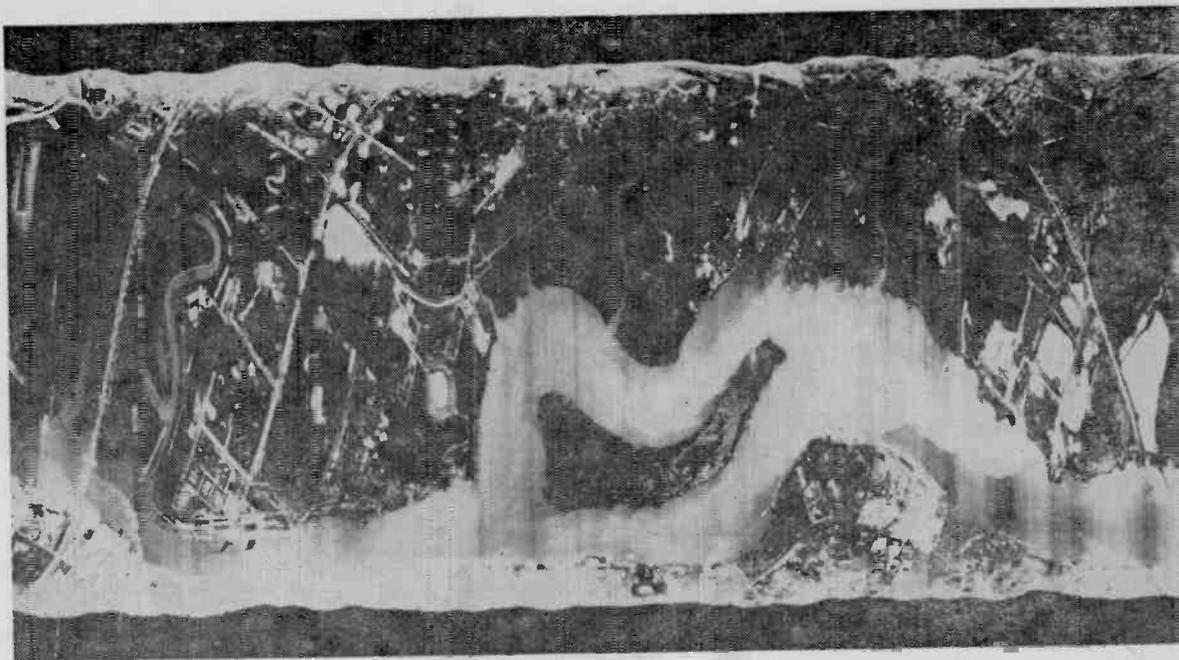This spotter maps and records the ecological condition of the area below. All data is kept in this recording equipment.




Line Scanner," capable of mapping thermal anomalies indicating moisture and ground water temperature changes; these in turn indicate plant dumpage since the water from plant deposits is warmer than the river into which it is flowing.

All these electronic devices enable the spotters to map, record, and take back information to the home base where it is put through a computer for further study. By correlating all this data, the Grumman engineers are able to track down the enemies polluting our land and waterways daily.

Thermal scanning devices can detect pollution by thermal variations which show up as different hues on infrared film. Bandit dumpage was discovered in this shot (above) by the use of this equipment.

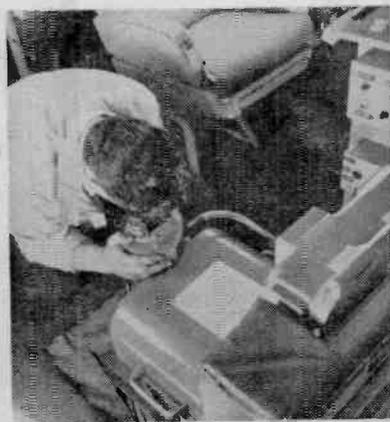The need for an escalated war against pollution is obvious. Efforts such as these spotters are encouraging signs that man is learning to use his technology wisely. Peaceful applications of our aerospace and electronics programs seem to be a step in the right direction—to track down pollution at its sources.
—Myrtle Gronk.



The Daedalus Thermal Line Scanner (above left) and the Wild RC-8 Aerial Mapping Camera (above right) are just two of many electronic devices used to track the polluter.

Sophisticated electronics allow the operators to work even during poor visibility.

the Shock Room that'll save your life



Electronic medicine? Essentially that's what the Shock Room at the City Hospital of Elmhurst is all about. It's all part of the Intensive Care section equipped with special electronic-medical machinery that means a breakthrough in the treatment of traumatic or accidental injuries—one of the most "neglected" diseases.

Truama from accidents is the number



ELEMENTARY ELECTRONICS



Doctors can examine records of arterial and venous pressures and cardiac output with the aid of this multiple channel electronic recording device (left). The gas analyzer (above) is a device used to determine a patient's blood level of oxygen, carbon dioxide and acidity.

four killer in the country, and so the importance of this new unit is obvious. Doctors at Elmhurst claim it saves 98.5% of those who would have normally died from these wounds. The Shock Room contains all the necessary equipment in one room, surrounded by specialists geared to this treatment, monitoring devices and 24-hour surveillance. Doctors and nurses constantly


record and regulate all the vital functions. The instruments used are all hooked up to the IBM computer at Mt. Sinai in New York, which has over 260 categorized diagnostic patterns to draw on.

Smaller hospitals can take advantage of this service by cable connection. But at present, if you're going to be in an accident, be near the Shock Room. —Myrtle Gronk.



Technicians work in conjunction with nurses while treating patients suffering from traumatic injury in the Shock Room (far left). Here, the patient receives constant care, both personal and electronic. Dr. Brown who helped set up the Shock Room (left) uses one such device, hooked up to the Mt. Sinai computer, which is capable of sending back instantaneous circulatory and respiratory measurements.

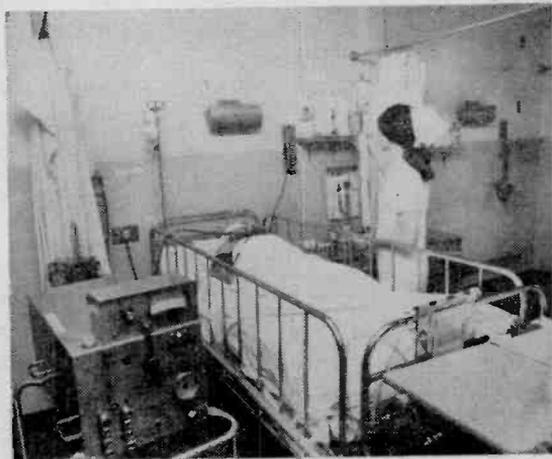Since all the instruments in the Elmhurst Shock Room are hooked up to the Mt. Sinai computer, doctors can rely on instantly relayed information needed in the treatment of their patient (left). This nurse in the Surgical Intensive Care Unit (below), which is in direct contact with the facilities of the Shock Room, can now receive any needed assistance while attending her patient.



new Heathkit ideas



Meet the second generation AR-15 ...new Heathkit AR-1500!

From the AR-15, hailed at the time of its introduction in 1967 as the most advanced receiver of its kind, comes the AR-1500... with impressive improvements in every critical area! **180 Watts Dynamic Music Power**, 90 watts per channel (8 ohm load); 120 watts dynamic music power per channel under 4 ohm load, with less than 0.1% intermod distortion, less than .25% harmonic distortion. A 14-lb. power transformer and massive output transistor heat sink are mute testimony to the power at your command. Direct coupled output and drive transistors are protected by limiting circuitry that electronically monitors voltage and current. **FM selectivity greater than 90 dB**, better phase linearity, separation, and less distortion are the result of two computer-designed 5-pole LC Filters. An improved 4-gang 6-tuned circuit front end offers better stability, 1.8 uV sensitivity, 1.5 dB capture ratio, and 100 dB image and IF rejection. Four ICs are used, three in the IF and one in the Multiplex. Patented automatic FM squelch is both noise and deviation activated, fully

adjustable for sensitivity. **Vastly Superior AM**, an "also ran" with many receivers, has two dual-gate MOSFETs in the RF and Mixer stages, one J-FET in the oscillator, 12-pole LC Filter in the IF, and broad-band detector. Result: better overload characteristics, better AGC action, and no IF alignment. **Greatly simplified kit construction**. Ten plug-in circuit boards, two wiring harnesses and extensive use of pre-cut wiring with installed clip connections make the AR-1500 a kit builder's dream. Built-in test circuitry uses signal meter to make resistance and voltage checks before operation. **Other advanced features** include Black Magic panel lighting that hides dial markings when set is not in use; flywheel tuning; pushbutton function controls; outputs for two separate speaker systems, bi-amplification, oscilloscope monitoring of FM multipath; inputs for phono, tape, tape monitor and aux. sources — all with individual level controls. **Versatile installation** in optional new low-profile walnut cabinet, in a wall, or black-finish dust cover included. Join the "NOW" Generation in audio technology...order your Heathkit AR-1500 today!

Kit AR-1500, less cabinet, 42 lbs. 349.95*
ARA-1500-1, walnut cabinet, 6 lbs. 24.95*

New Heathkit Stereo Cassette Recorder



119.95*

Frequency response of ± 3 dB, 30-12 kHz, brings your stereo system into the cassette age. Features built-in bias adjustment to accommodate the new chromium dioxide tape; counter; automatic motor shutoff; preassembled and aligned transport mechanism. The AD-110 offers fidelity recording and playback of stereo or mono when used with your stereo system.

Kit AD-110, 10 lbs. 119.95*

New Heathkit Stereo-4 Decoder



29.95*

Compatible with your present stereo system and FM receiver, lets you hear all Stereo-4 material currently being broadcast by a number of stations across the country. Additionally, imparts a 4-channel effect to your existing stereo library. Requires second amplifier and 2 speaker systems for installation with conventional stereo system.

Kit AD-2002, 5 lbs. 29.95*

New Heathkit Stereo Phonograph with AM Radio



109.95*

Gets it together in a portable package with a purple plum snakey skin that's as far out as today's sounds. Solid-state 18-watt amplifier, fold-down 4-speed automatic changer and swing-out high compliance speakers. Speakers can be separated up to 5'. A flip of the mode switch and you're into AM radio! 45 spindle adapter included.

Kit GD-111, 50 lbs. 109.95*


for every age, every hobby!

New Heathkit "Minimizer" kitchen waste compactor...

Today's most modern refuse handling method in easy-to-assemble kit form! Now you can own the most exciting kitchen appliance on the market for less than you'd pay for any other comparable compactor. The Heathkit Minimizer lets Mom throw out the unsightly waste baskets and garbage cans for the latest in clean, convenient, odor-free disposal. The Minimizer handles all normal household trash — food wastes, glass and plastic containers, tin cans, wrappings, boxes, floor sweepings, light bulbs, etc. The packing ram descends with 2,000-lb. force to reduce refuse to almost 1/4 of its original size, packaging the material in a strong disposable bag — one bag holds an entire week's trash for a family of four! When the bag's full, Mom simply folds over the top and removes a neat, dry package for normal rubbish pickup. And the Minimizer deodorizes the contents each time the drawer is opened and closed. The sanitation man will love Minimizer, too!

Simple, safe operation! To use, Mom merely inserts a Minimizer plastic-lined bag in the drawer and starts the compacting cycle. In less than a minute the ram forces down the trash, returns to its normal position, and the Minimizer shuts itself off. For maximum safety, the Minimizer uses a key lock switch and an interlock which automatically turns unit off if drawer is not fully closed or is accidentally opened during cycling. Your Heathkit Minimizer can be built-in under the kitchen counter or left free-standing. Its bright white enamel finish with marble-tone vinyl-clad top complements any decor. And you can build it yourself in 6 to 10 hours. Has long-life 1/2 hp motor, plugs into 110-120 VAC conventional household outlet. Kit includes 5 plastic-lined bags, one 9 oz. aerosol can of deodorant. Minimizer measures 34 3/8" H x 15" W x 25 1/2" D.

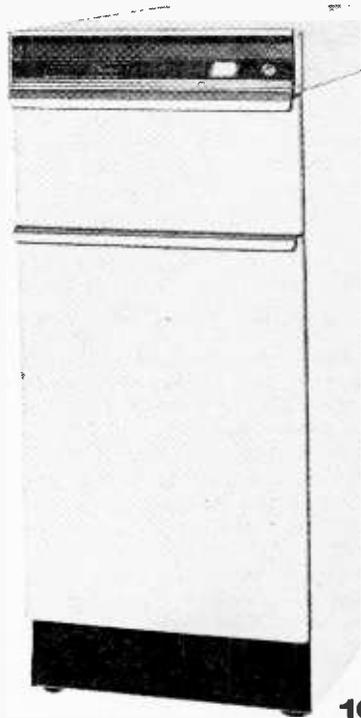Kit GU-1800, 203 lbs. 199.95*
GUA-1800-1, 15 plastic-lined bags, 5 lbs. 4.99*



199.95*

New Heathkit Slotless 1/32-Scale Raceway


129.95*



You race up to 4 GT cars — each with independent acceleration, deceleration and steering! Make all the maneuvers of real high-speed drivers. You can even turn around completely and backtrack. Kit includes track sections for 8'x4' oval, power transformer, 2 cars and controllers.

Kit GD-79, 13 lbs., mailable 129.95*
Kit GDA-79-1, extra car and controller, 3 lbs., mailable .. 21.95*

New Heathkit Electronic Workshops

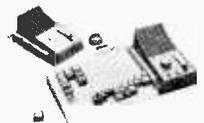

Completely self-contained electronics labs teach youngsters the basics of electronics.

Each contains basic electronic components in easy-to-work-with module form. Kids simply follow the instructions, arrange the blocks on the board to form actual working circuits for code flashers, timers, alarms, etc.

Kit JK-1033, 36 experiments, 11 lbs. 29.95*
Kit JK-1022, 25 experiments, 8 lbs. 24.95*
Kit JK-1011, 12 experiments, 6 lbs. 19.95*

SEE THESE KITS AT YOUR LOCAL HEATHKIT ELECTRONIC CENTER... or send for FREE catalog!

CALIF.: Anaheim, 330 E. Ball Road; El Cerrito, 6000 Potrero Avenue; La Mesa, 8363 Center Drive; Los Angeles, 2309 S. Flower St.; Redwood City, 2001 Middlefield Rd.; Woodland Hills, 22504 Ventura Blvd.; COLO.: Denver, 5940 W. 38th Ave.; GA.: Atlanta, 5285 Roswell Road; ILL.: Chicago, 3462-66 W. Devon Ave.; DOWNERS GROVE, 224 Ogden Ave.; MD.: Rockville, 5542 Nicholson Lane; MASS.: Wellesley, 165 Worcester St.; MICH.: Detroit, 18645 W. Eight Mile Rd.; MINN.: Hopkins, 101 Shady Oak Rd.; MO.: St. Louis, 9296 Gravois Ave.; N.J.: Fair Lawn, 35-07 Broadway (Rte. 4); N.Y.: Jericho, L.I.; 15 Jericho Turnpike; New York, 35 W. 45th Street; OHIO: Cleveland, 5444 Pearl Rd.; Woodlawn, 10133 Springfield Pike; PA.: Philadelphia, 6318 Roosevelt Blvd.; Pittsburgh, 3482 William Penn Hwy.; TEXAS: Dallas, 2715 Ross Avenue; Houston, 3705 Westheimer; WASH.: Seattle, 2221 Third Ave.; WIS.: Milwaukee, 5215 Fond du Lac.

Retail Heathkit Electronic Center prices slightly higher to cover shipping, local stock, consultation and demonstration facilities. Local service also available whether you purchase locally or by factory mail order.

HEATHKIT Schumberger	
HEATH COMPANY, Dept. 139-1 Benton Harbor, Michigan 49022	
<input type="checkbox"/> Enclosed is \$ _____ plus shipping.	
<input type="checkbox"/> Please send model(s) _____	
<input type="checkbox"/> Please send FREE Heathkit Catalog.	
Name _____	
Address _____	
City _____	State _____ Zip _____
*Mail order prices; FOB factory. CL-424 Prices & specifications subject to change without notice.	

CIRCLE NO. 7 ON PAGE 17

CB coffee break

BRAND
NEW!

THIS ISSUE'S COLUMNIST—JULIAN S. MARTIN, KMD4313

Here I go with a new column written exclusively for the Citizen Bander and *no one else*. Naturally, I would like to pack this CB column with all sorts of goodies but space is limited. I plan to give you new product info, FCC happenings, mini-theory that'll set you straight, what's available, club news, operation reports and more! But, not all at once. I plan to go my merry way as I see a CB column should go and wait for your comments. That's right, folks, keep those cards and letters coming except for that blond bombshell in Wala. Honey, you send your letters to Dear Abby!

Would You Believe. 100-watts effective input power on Class D—and it's legal. On 27 MHz, 100 watts can put a 40 dB over S9 signal into Australia, England or Japan when the skip is open; imagine what it can do on the other end of town.


No, this is no con job. I'm not going to tell you about the allowable input power for CB rigs in some mythical country. Right now, you can zap out 100 watts effective input power from your present CB rig.

Aha! You have the catch . . . "effective" input power. True, when we speak of *effective power* the soup into the final is still only 5 watts, but with the proper antenna—one you can obtain from local distributors—your signal will bang in at the receiving station just as if you were pumping 100 watts into the final RF amplifier. And after all, it's what is received that counts: as far as the receiving station is concerned he doesn't know whether you're blasting the ether with a 100 watt linear or

shouting through a large megaphone; all he knows is that you have one hell of a signal.

The trick, if you want to call it a trick, is to use the same stunt as the commercial broadcasters . . . boost the *effective* power with a *beam antenna*. For example, UHF TV stations need a powerhouse signal just to get over the snow: if they need 100 kW to put a picture into your TV they are not going to subsidize the local electric company by using a 100 kW transmitter. More likely, they will run a 25

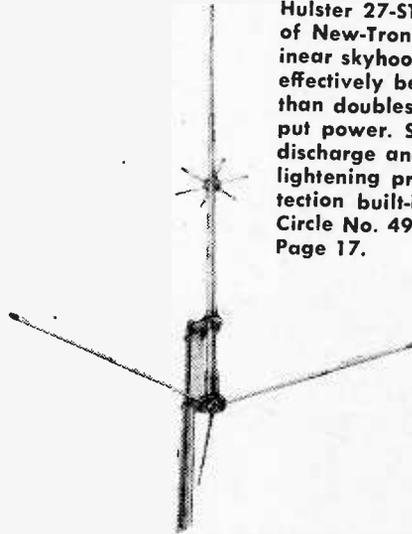Hulster 27-STR, one of New-Tronics col-linear skyhooks, effectively better than doubles output power. Static discharge and lightning protection built-in. Circle No. 49 on Page 17.



kW transmitter and use an antenna with a power gain of 4. As far as your receiver is concerned the station is running a 100 kW transmitter, and the pix comes in just as it would from a 100 kW transmitter feeding a turnstile antenna (no gain).

Antenna gain comes about in this way. The typical "all purpose" CB antenna is the "ground plane", consisting of a 1/4-wave vertical radiator and three or four horizontal 1/4-wave radials at the base which act as a ground plane. The

Continued on Page 102

Gain antenna with a real difference, this Patented Avanti Astro Plane radiates primarily from antenna top, thereby gaining about fifteen extra feet in height. Circle No. 48 on Page 17.

ELEMENTARY ELECTRONICS



GO FOUR-CHANNEL

WITH QUADI

Get into the world
of surround sound,
through a garden hose!

by Charles D. Rakes

Place yourself in a galaxy of surrounding sound with the "Quadi" quadrasonic amplifier that can turn a standard stereo system into a listening wonderland! Quadrasonic stereo, or four-channel stereo as it is often called, is probably the greatest new home-entertainment item devised since the crystal set came into being. One session with our Quadi stereo system and you'll agree that the two-channel stereo system is as obsolete as the dodo bird.


Whoa! Don't yell uncle yet. This quadrasonic terminology doesn't mean complicated expensive equipment or circuits—all that's involved is an additional pair of audio channels connected to the existing stereo system. The two-channel stereo system is unchanged and operates in a normal manner. The two new channels take information from the speaker output terminals of the two-channel system, process it and feed it to two speakers located in the rear of the room at opposite corners.

How it Works. The method of processing the two audio signals is the secret to the success of the Quadi. Each channel's audio output is delayed approximately 15-milliseconds to produce a realistic reverberation effect. This is done with a simple acoustical delay line fabricated from a section of a plastic garden hose, fed at one end with a small earphone and picked up at the opposite end with a crystal mike.

The echoes created by the delay lines effectively place the two rear speakers at an additional acoustical distance of 15 feet be-

PARTS LIST FOR QUADI


- C1-C4, C6-C9—5 μ F, 25 VDC electrolytic
 - C5—500 μ F, 25 VDC electrolytic
 - EP1, EP2—Dynamic earphone with 6-ohm to 15-ohm impedance
 - J1-J6—Phono jacks
 - P1-P4—Phono plugs
 - Q1-Q4—MPS3638 transistor (Motorola) or HEP 716 (Motorola)
 - R1, R3—27,000-ohm, $\frac{1}{2}$ watt
 - R2, R4—Potentiometer, 5,000 ohms
 - R5, R6—Potentiometer, 150 ohms
 - R7, R17—150,000-ohm, $\frac{1}{2}$ -watt
 - R8, R14, R15, R20—4,700-ohm, $\frac{1}{2}$ -watt
 - R9, R11, R16, R19—470,000-ohm, $\frac{1}{2}$ -watt
 - R10, R18—330-ohm, $\frac{1}{2}$ -watt
 - R12—1,000-ohm, $\frac{1}{2}$ -watt
 - R13—3,300-ohm, $\frac{1}{2}$ -watt
 - S1—Switch, SPST
 - T1—Filament transformer: 115V: 26.8, center-tapped secondary (Triad F-40X or equiv.)
 - T2—Driver transformer: 10,000-ohm primary; 2,000-ohm secondary (Calrad CR70 or Midland 25-619 or equiv.)
 - XTL1, XTL2—Crystal microphone (Realistic 33-907 or equiv.)
 - Z1—Amperex PCA-3B-18-1 stereo amplifier
 - 2—15-foot sections of plastic garden hose, $\frac{1}{2}$ inch I.D.
 - 2—Wood boxes, 3-in. x 11 $\frac{1}{2}$ -in. x 11 $\frac{1}{2}$ -in.
 - 1—Cabinet, 12-in. x 4 $\frac{1}{2}$ -in. x 6 $\frac{1}{4}$ -in. or similar housing of metal or wood (Ten-Tec MG-12 or equiv.)
 - Misc.—Hardware, shielded cable, wire, solder, knobs, power cord, speaker cable, terminal strip, etc.
- Note:** An etched copperclad printed circuit board is available for \$2.95 undrilled, and for \$3.95 with all holes drilled. A pre-drilled PC board, plus all the components that mount on it, is available at \$11.95 from: Krystal Kits, Box 4232, Little Rock, AR. 72204. All prices include postage and handling.

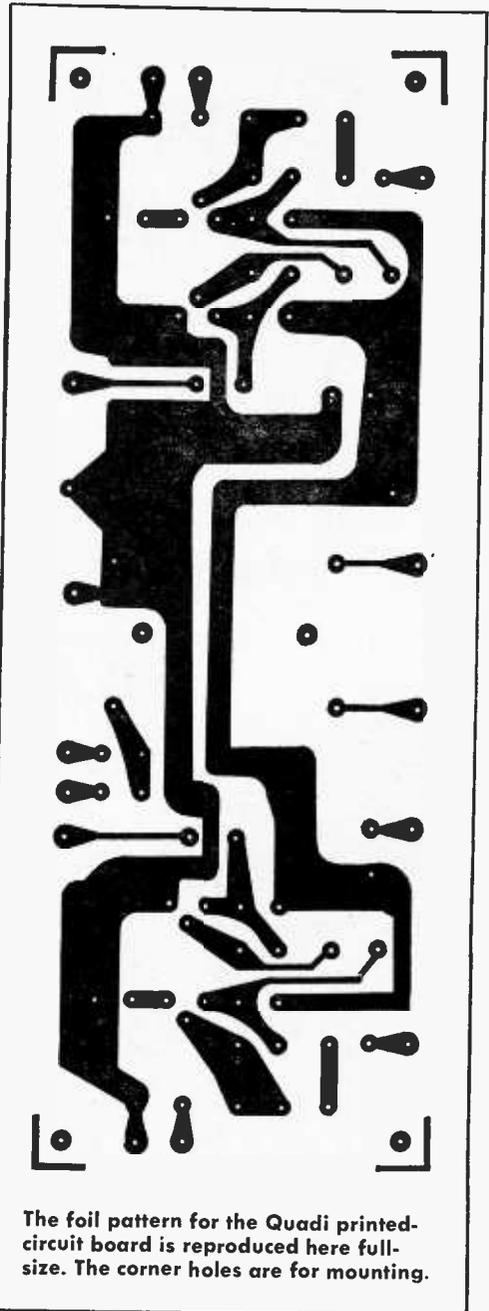

The foil pattern for the Quadi printed-circuit board is reproduced here full-size. The corner holes are for mounting.

hind their physical location. This helps in reproducing small echoes that are normally lost in the standard two-channel stereo system but which were present when the original recording was produced.

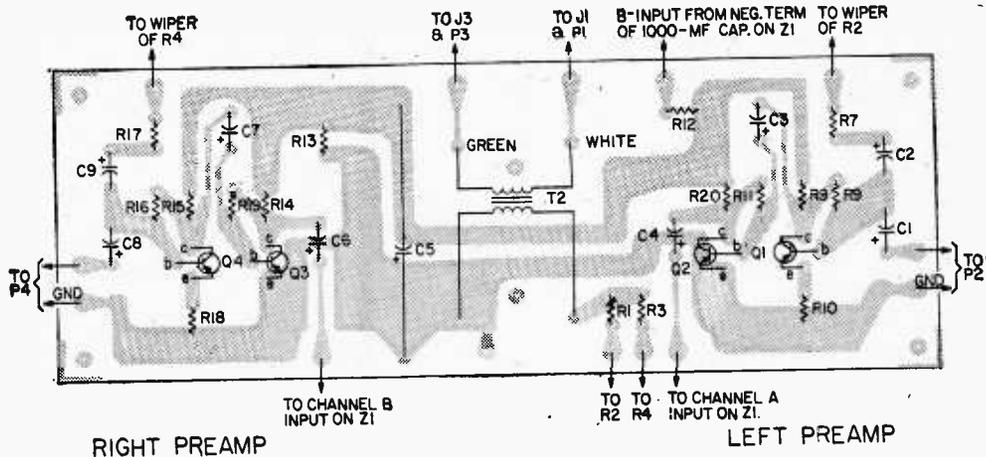Additional depth and ambience are produced by taking the differential output from both channels of the two-channel stereo



Where to mount components on the printed-circuit board. Be sure the capacitors are installed according to the indicated polarity, and that the transistor leads are in the right holes.

system and mixing it in with each of the two new channels.


The delay-line drive and differential levels are adjustable to allow for a balanced output in both of the new channels. Treble, bass, balance, and volume controls are also provided on the stereo amplifier assembly.

Enough about the unit's operation—on with the construction of your very own Quad! If you are a good parts scrounger, the cost should be below the fifty-dollar mark, excluding the two additional speakers. You can purchase an etched printed-circuit board, drilled or undrilled, or a drilled board along with all components that mount on it, from Krystal Kits (see Parts List). The Amperex amplifier is available from Lafayette Radio, stock number 19U09142, at \$15.95 plus postage.


Dual Preamplifier. A good starting place is to construct the dual preamplifier that raises

the audio signal from each of the delay-line outputs to a level sufficient to drive the power amplifiers. All the preamplifier components are mounted on a printed-circuit board, but if you will follow the same parts layout a perboard may be used. When it comes to installing the coupling capacitors, carefully observe the polarity before soldering in place. Same goes for the transistors—be sure that the emitter and collector don't get switched in the process of installing them.

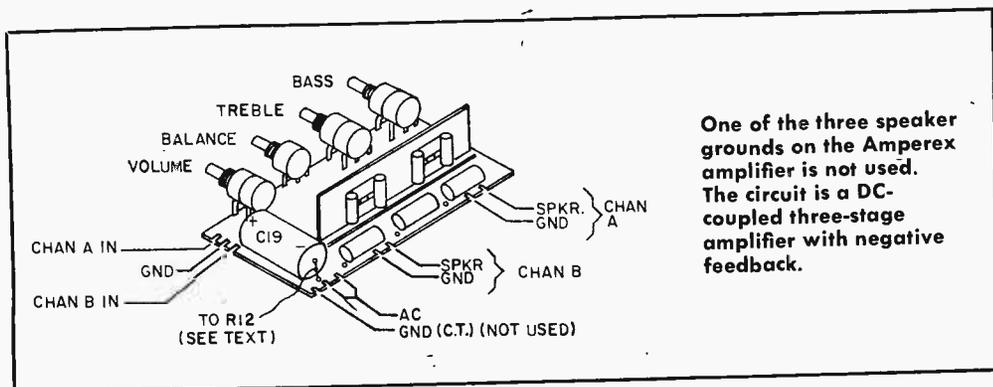Stereo Amplifier. The stereo amplifier is duck soup, because we got smart and used a ready-made Amperex 8-watt complementary stereo amplifier assembly (four watts per channel)—for less than twenty dollars who could fool around building one? Only one slight modification is required on the stereo amplifier assembly: connect a wire to the negative terminal of the 1000 uF



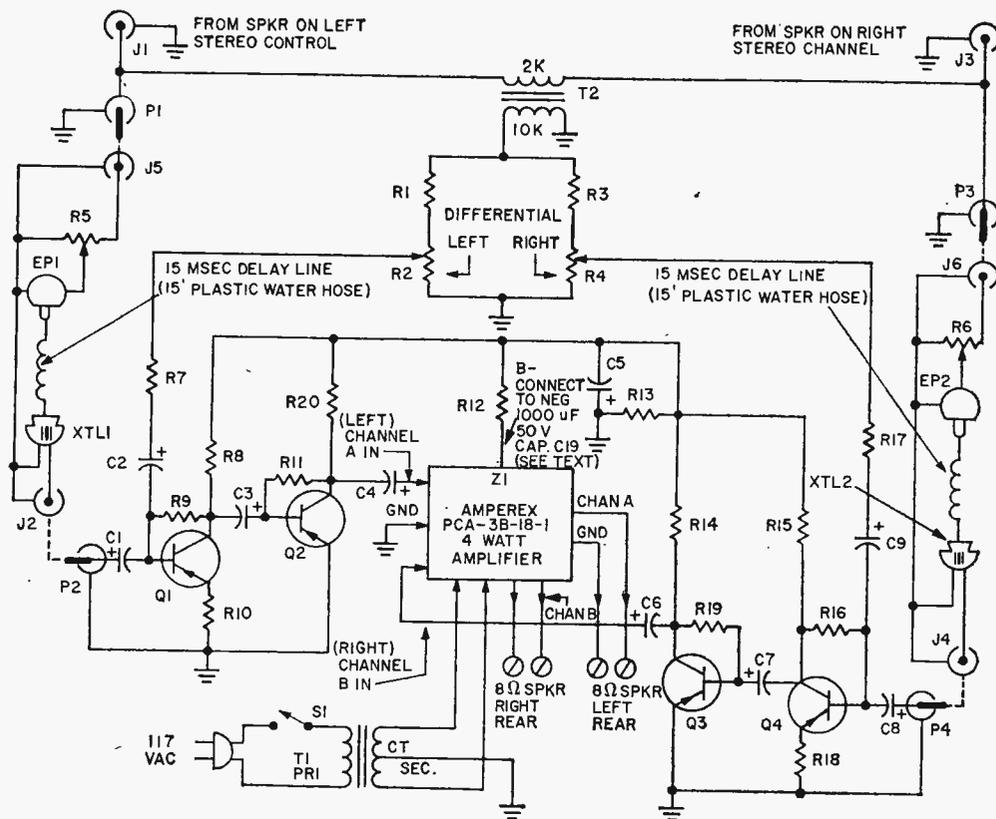One of the three speaker grounds on the Amperex amplifier is not used. The circuit is a DC-coupled three-stage amplifier with negative feedback.



Construction of the Quadi is simplified by using an Amperex amplifier, which is modified by adding a wire from capacitor C19 (on the amplifier). This connects to resistor R12.

filter capacitor, C19. This wire supplies battery negative to the dual preamplifier.

The two amplifier assemblies are housed in a metal and plastic cabinet 12 in. x 4½ in. x 6¼ in., as shown in the photos. Any similar enclosure large enough to house all of the components will do just as well.


The two preamplifiers inputs are connected to P2 and P4 through two 4-foot sections of shielded mike cable. Most any 4-foot section of two-wire cable will do for P1 and P3. The stereo-amplifier outputs are connected to a four-terminal barrier strip.

Delay Lines. Cut two 15-ft. sections of ½-inch I.D. plastic garden hose and form each section into a roll that will fit snugly in the 3 in. x 11½ in. x 11½ in. wooden box. Make sure that no kinks appear anywhere in the coil of plastic hose. Use the photos as a construction guide when needed.

The earphone is placed in one end of the coil and held in place with silicon rubber. The crystal mike is butted up against the opposite end of the coil and is kept in place with shrink-tubing or plastic tape. A plastic cable-clamp holds the mike in place. Wire the earphone and mike to match the diagram, leaving enough slack in the wires to allow removal of the front cover.



Putting it All Together. With the power turned off, connect up the following leads. Connect the input of J1 to the left channel speaker (on your existing stereo system) and J3 to the right channel speaker. Plug P1 into J5 and P2 into J2 of one of the delay units. Plug P3 into J6 and P4 into J4 of the other delay unit.

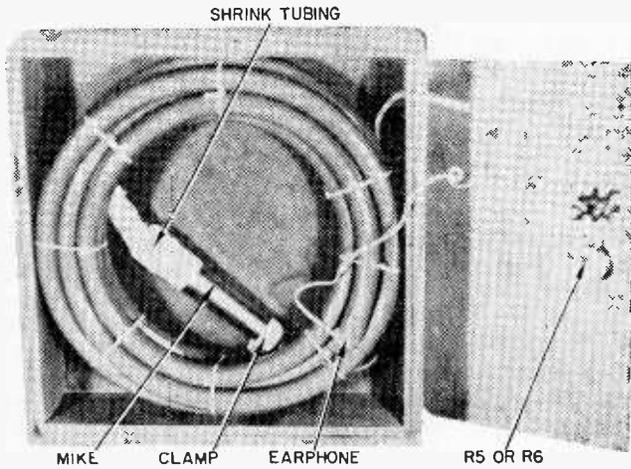Connect the rear speakers to the output terminals of the Amperex amplifier. The left speaker goes in the left rear corner and the



When coiling the two 15-foot sections of garden hose, make sure there are no kinks in the tubing, as these could affect the quality of the sound being piped through.

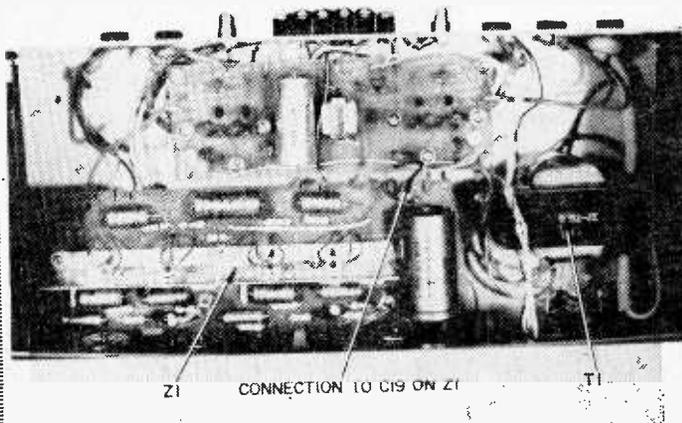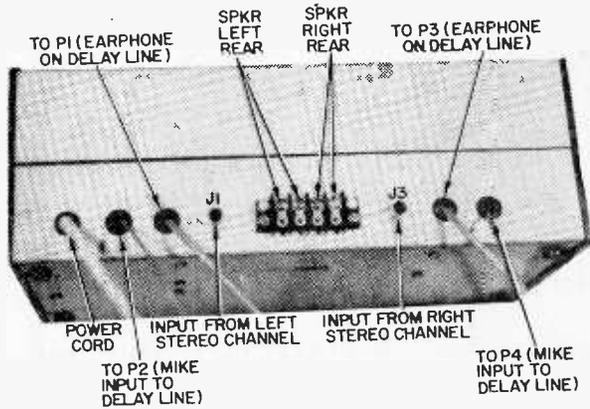Instead of wires running directly to plugs P1, P2 P3 and P4, jacks could have been used instead, mounted on the rear of the cabinet, to simplify connecting up the various Quadi units.



The large capacitor at lower right is C19 on the Amperex amplifier, to whose negative terminal (upper end here) is added a short wire for connection to R12 in the Quadi.


e/e QUADI

right speaker in the right rear corner of the room. The speakers should be separated by at least the same distance as are the front speakers.

Set both earphone drive pots, R5 and R6, to maximum. Set the differential level controls to a minimum. The bass and treble controls may be set to suit your own taste. Select either an FM-stereo broadcast station or a stereo record and adjust the controls for proper stereo listening. Apply power to the Quadi and you should hear the delayed output of each channel coming from each of the rear speakers. Set the balance and volume controls on the Amperex stereo amp-

lifier to the desired levels and slowly turn R2 and R4 up until the desired ambience and depth are obtained. If the delayed output level is too high in relation to the differential level, reduce the drive to the earphones with R5 and R6.

Trying This and That. Just for kicks you can switch the rear speakers around so that the left channel is coming from the right rear and the right channel from the left rear. With the speakers connected in this manner, a delayed crisscross sound effect will be produced. Another mode of operation you can try is to delay only one channel and feed the other channel with the differential input. Since there is no fixed recipe, mix the signals anyway you please to produce the type of sounds you like best. Have fun. ■

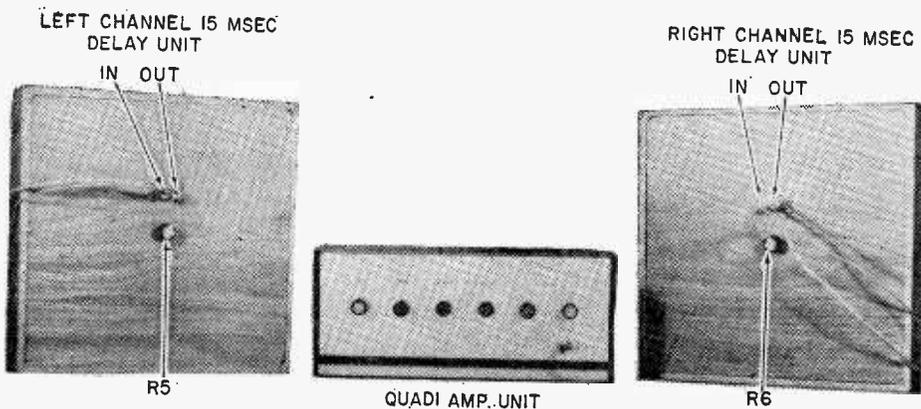


The four controls at left (bass, treble, balance, volume) are on the Amperex amplifier; the other two are R2 and R4, the left and right differential controls.

"The Tempest" in Quadriphonic Sound

□ The Shakespeare Society of America recently presented "The Tempest" in an unusual stage production. Their private theater in West Hollywood, California, was the stage for a classic rendition of the play accompanied by a very contemporary light show, stage effects and *quadriphonic* reproduction of specially created electronic sound effects and music.

The sound system consisted of four JBL studio monitor loudspeakers and four Spectra Sonic modular power systems. Critics were not unanimous on whether this was what the Bard had in mind, but the audience received the sounds of the storm, waves crashing and electronic music with enthusiasm. Photo at right shows Vincent Mongol as Caliban and Rand Bridges as Prospero in the Shakespeare Society of America's production of "The Tempest."

—Joe Gronk.

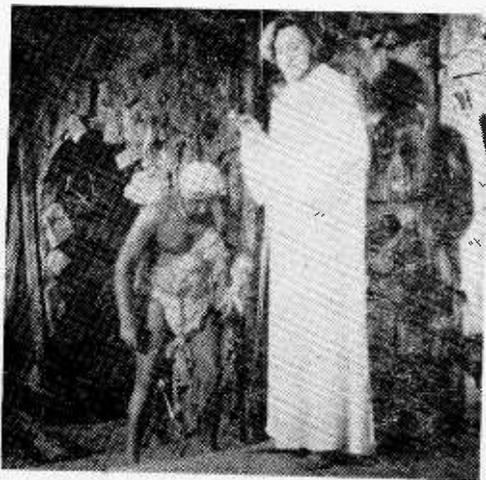

Weekend Carpenter Special...

BOOKSHELF SPEAKER FROM BOOKSHELVES

by Herman F. Johnson



Your speakers are finished before you start!


Want to build a great bookshelf speaker system—one with professional looks, feel and sound? You can do it with our easy-to-build bookshelves. The secret for weekend carpenters is in the pre-finished material. Ready made bookshelves—real *book*-shelves—are available in hardware and building supply stores and make an ideal building material. You will also use unfinished shelving. For utility use, it is made of plain material $\frac{3}{4}$ -in. thick and $11\frac{1}{2}$ -in wide. Both are accurately cut in the lumber mill to even footage lengths.

The use of finished stock makes it possible to determine the appearance of an enclosure before it is built. A variety of wood grain finishes is available. The type that can withstand considerable handling and is impervious to scratching is vinyl-clad walnut wood grain—the same material used on side panels of modern station wagons. As with the plain, finished shelving is $\frac{3}{4}$ -in. thick, at least 2-feet long and between 6 and 12-in. wide.


An important requirement for a speaker box is solid construction; it must be made as non-resonant as possible. Particle board is ideal for this purpose because, unlike most plywood, it has no cavities. It is a higher density material than plywood, easy to cut, and both sides are smooth and parallel. Also, the cost is low.

This article covers the construction of an acoustic suspension 2-way system


e/e BOOKSHELF SPEAKER

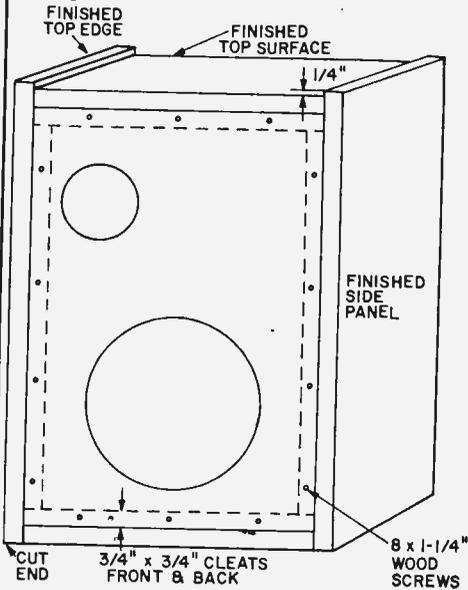

CUT END 3/4" x 3/4" CLEATS FRONT & BACK

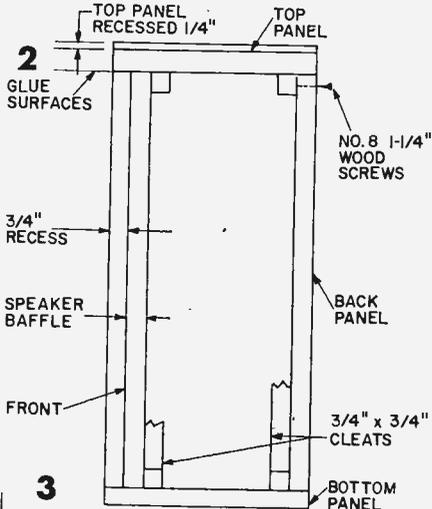

36" OR 48" LENGTH

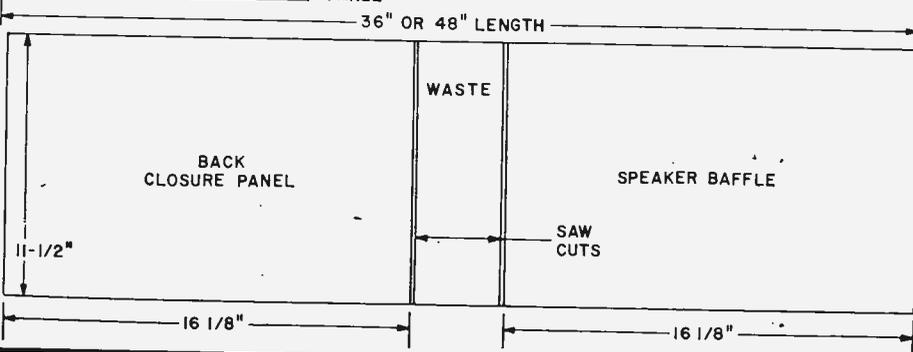


housed in a bookshelf-sized cabinet. The size is convenient for stereo in an average size listening room. To insure good performance from a small package, a high compliance woofer and a dome-type tweeter were selected. The woofer was designed to operate in an air volume of only half a cubic foot. In fact, the power handling capability (20 watts) is obtained when it is operated with just that volume.

The Saw Dust Flies. Because ready made shelves are used, only five cross cuts are required to form the panels. Precautions, however, are necessary. When shelving is selected, it is important to observe that finished pieces will be solid throughout. Hollow lightweight shelves are now available; these cannot be used. Check to see that the two finished shelves are the same width and that the ends are square on both the finished and unfinished pieces. Some shelves may be found where the ends are not quite square with the side edges.

Note in Fig. 1 that the side panels extend one-quarter of an inch above the top. This provides a more modern cabinet design than the usual run-of-the-mill bookshelf speaker. Exposed cut edges are at the bottom where they cannot be seen.

Square cleats are used at the front and back of the enclosure (Fig. 2) to hold the cabinet together. Note that the short cleats are the same length (11 1/2-in.) as the top and bottom panels. The long cleats are fitted between the short ones.

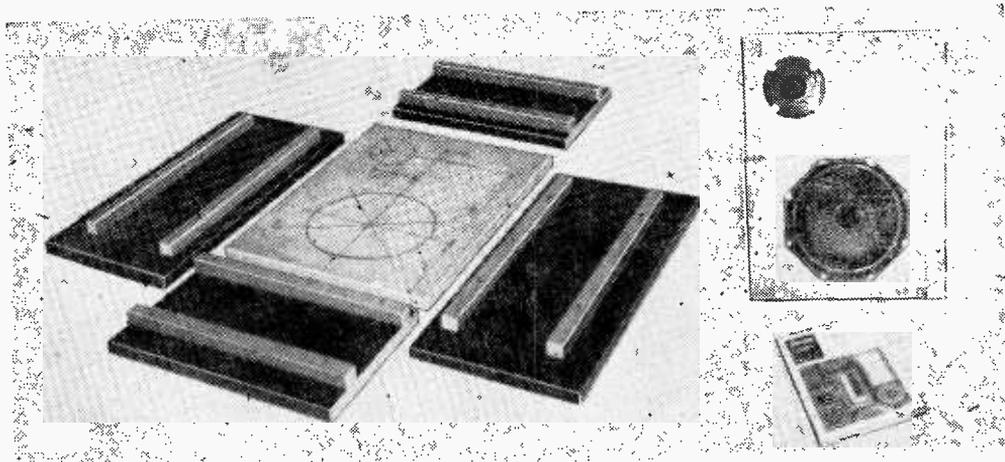To make maximum use of machine-cut square ends, cut the plain shelf as indicated in Fig. 3. This provides us with a speaker mounting board. Cut the 36-in. finished shelf into two parts of equal length (Fig. 2) to make the sides. These will be slightly less than 18-in. high due




Fast and simple to build, 2-way speaker system has woofer designed for bookshelf-size enclosures. Finished outside material gives professional, factory-made look. Here are the parts prior to assembly.

to the width of the saw. Cut the 24-in. finished shelf as indicated in Fig. 4 to make the top and bottom panels. Note the length: it is the same as the width of the speaker baffle and back. These cuts can be made by following a scribed pencil line with a saber saw. A fine-tooth saw should be employed to insure a clean cut.

Putting It Together. When handling the finished panels, it is a good idea to place a piece of cardboard on the work bench to prevent abrasion of finished surfaces. Drill small holes at about an inch from the ends of the cleats and tack them in place, first the short ones and then the long ones. Hold one of the plain panels flush with a back edge as a spacer to locate the back cleats $\frac{3}{4}$ -in. from the back edges. Place both plain panels together to space the front cleats $1\frac{1}{2}$ -in. from the front edges. When tacking, use $1\frac{1}{4}$ -in. finishing nails but do not drive

them down tightly. This tacking idea provides a trial assembly to insure that all parts fit properly.

Make certain that the ends of the top and bottom panels make contact with the sides, and that the outside cleat faces line up all around. If necessary, move and/or cut the cleats. When all parts are fitted properly, strike pencil lines on the panel surfaces along both sides of each cleat, and mark the four panel junctions 1-1, 2-2, etc. (This will insure that all parts can be returned to the same position for final assembly.) Remove the cleats, coat all mating surfaces with plastic resin glue, then reinstall. Add another nail or two, at about $6\frac{1}{2}$ -in. centers, and drive the cleats down tightly. Nails are used in place of screws to simplify the work since their purpose is to hold the cleats until the glue has set. Plastic resin provides a joint stronger than the wood if the parts

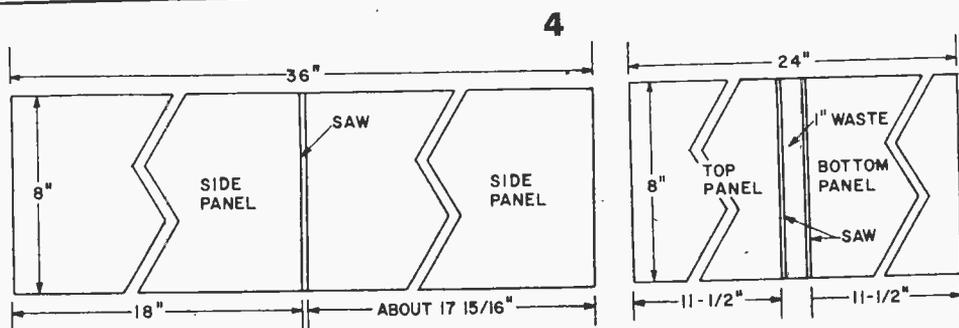

e/e BOOKSHELF SPEAKER


are held tightly during drying.

Scribe pencil lines along all four edges of the two plain panels $\frac{3}{8}$ -in. from each edge, and drill $\frac{3}{32}$ -in. pilot holes at about 5-in. centers. Reassemble the enclosure and insert the plain panels, front and back. Mark the hole locations on the side faces of the cleats with the $\frac{3}{32}$ -in. drill by turning it in each hole. The enclosure should be resting upon a flat surface in the upright position of Fig. 1 with the side panels held firmly together as the locations are marked. It is a good idea to drill the holes in the side of the cleats about $\frac{3}{8}$ -in. deep and remove the displaced wood. This will insure seating of the front and back panels to the cleats when they are screwed in place.

A Little Bit of Electronics. For wiring hook-up, drill two $\frac{1}{8}$ -in. holes about 2-in. apart near the bottom edge of the back panel for No. 6 brass screws.

Scribe pencil lines on the other panel (speaker baffle) to indicate the openings shown in Fig. 5 and 6. Drill the two $\frac{1}{2}$ -in. holes before making the circular cuts for the tweeter cutout. These speaker openings can be made with a saber saw by slowly cutting along the scribed pencil line. Designate the marked face as the front. Speaker openings can also be made with a circle cutter or a router with a center guide attached. A cabinet shop in your town will cut the openings for a small fee.



The edge holes should then be enlarged

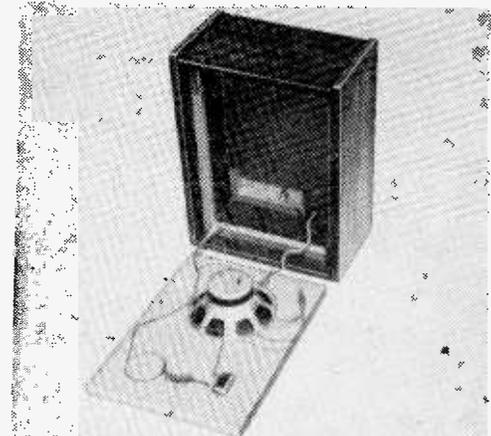


Simple, direct, point-to-point wiring, shown schematically in Fig. 7, uses brass screws for convenient speaker-to-amplifier connection.

to $\frac{3}{16}$ -in. diameter for shank clearance of No. 8 wood screws; countersink for flat head screws if used. When all of the parts are ready for final assembly, coat the mating surfaces at the back with glue and screw the back panel in place. Insert the screws for wiring hookup and place the box on its back. Fit fiberglass damping material on the back, one side, and the top over the cleats. Thumbtacks or spots of glue are sufficient to hold the fiberglass in place.

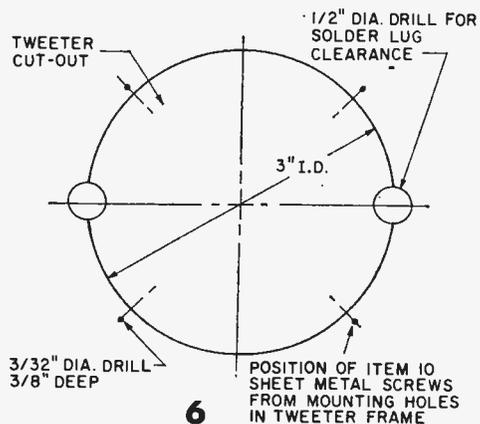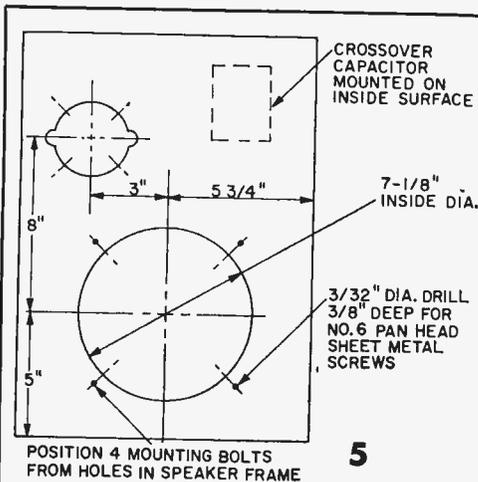The baffle can also be glued and screwed down, but both speakers should be fitted into the openings and the capacitor installed prior to the permanent installation of the baffle. Pan-head No. 6 sheet-metal screws $\frac{1}{2}$ -in. long are ideal for mounting the speak-





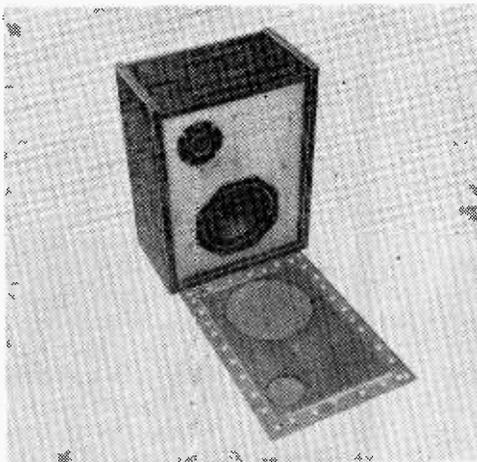

Thumbtacks secure grill cloth to 1/4-inch hardboard frame. Hefty enclosure has professional wood grain appearance, photo at right.


ers. Use the holes in the speaker frames as a template for centermarking each screw location. Drill $\frac{3}{32}$ -in. holes to avoid the possibility of puncturing the woofer's cone by the slip of a screw driver. A "fail-safe" way to mount a woofer is to drill four $\frac{7}{32}$ -in. holes and insert 8-32 tee nuts on the back side for machine screws.

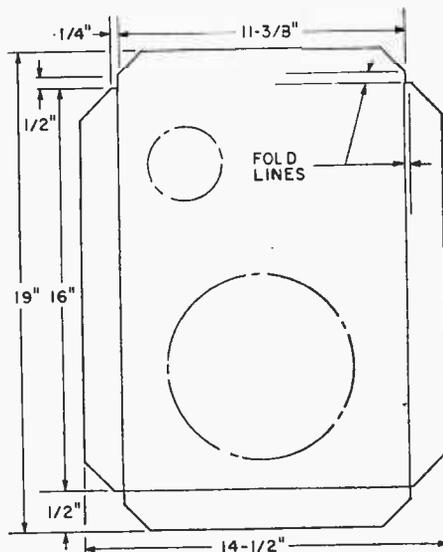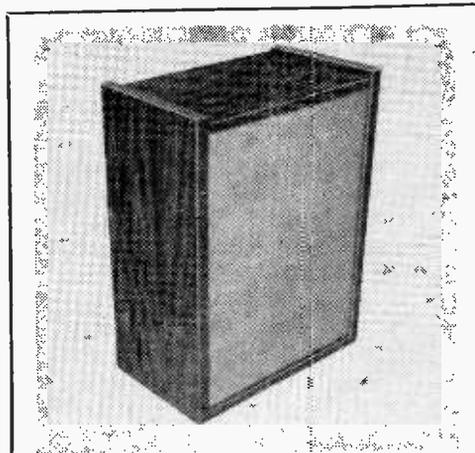The Speakers. An 8-in woofer, such as the type used here, can be capable of better transient response than larger woofers if it is equipped with a strong magnet to influence the voice coil. The 8-in. Philips (Nor-elco) AD8065/W8 is recommended due to its very low free-air resonance, rated at 28 Hz. Low free-air resonance is a necessity to hold down composite resonance which re-




8

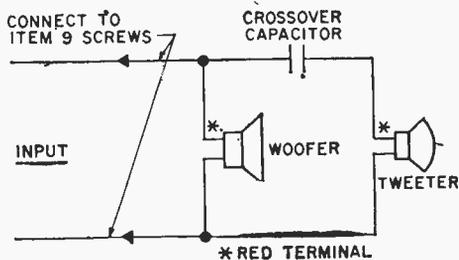Substitute phone jack, terminal strip, fahnestock clips or your favorite binding post for Item 9 screws if desired; observe "red terminal" connections for proper phasing.



7

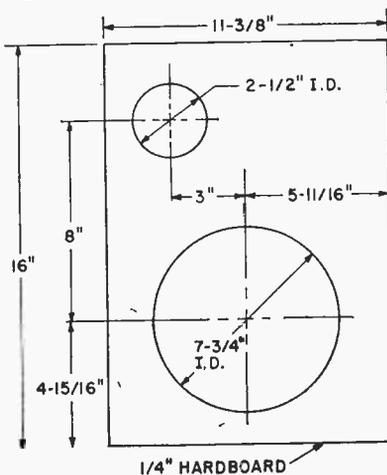

e/e BOOKSHELF SPEAKER

sults when a woofer is backed into a small volume of air inside a box. In this enclosure the composite resonance value was found to be 58 Hz. If a new woofer is installed, the composite resonance can be expected to drop about ten percent after a year of use.

The 1-in. dome tweeter, Philips No. AD0160/T8, is a fine high frequency unit (dome type) available to home constructors. The dispersion characteristics are excellent and its range extends to 20,000 Hz. As with all high-frequency reproducers, it must be protected or isolated from low frequencies by a series crossover capacitor. Fig. 7 shows the wiring hookup.

Finishing Up. For grille-cloth mounting, a 1/4-in. hardboard frame is recommended. Lay-out lines to the dimensions indicated in

Fig. 8 and cut the frame and cloth. If the grille material has a tendency to fray, spread a bead of rubber cement along the edges. Use the embossed pattern side (back side of the hardboard) for the front. Spread rubber cement around the two speaker openings to hold grille material tight to the hardboard. Use small thumbtacks on the back of the frame and more rubber cement along the edges. Hardboard is tough—thumbtacks must be hammer driven. The frame dimensions provide 1/16-in. clearance all around inside the opening. This dimension provides a snug fit with cane type cloth. Add masking tape to an edge if necessary for others.

Hope you've had fun building one or two of these speakers—maybe even four for Quadi which appears in this issue. They should provide many hours of fun-filled listening for "serious" and "pop" music listeners alike.

Bill of Materials for Bookshelf Speaker

Item	Description
1	Plain particle board shelf, 3/4-in. x 11 1/2-in. x 36 in. One required.
2	Finished particle board shelf (must be solid), 3/4-in. x 8-in. x 36. One required.
3	Finished particle board shelf (must be solid), 3/4-in. x 8-in. x 24. One required.
4	Fir cleat material, 3/4-in. x 3/4-in. x 10 ft. total.
5	Masonite sheet, 1/4-in. x 11 3/8-in. x 16-in. One required.
6	Grille cloth, 14 1/2-in. x 19-in.
7	Steel wood screws, No. 8, 1 1/4-in. long. Twenty required.
8	Steel finishing nails, 3-D, 1 1/4-in. long. Thirty required.
9	Brass machine screws. No. 6-32, 2-in. long. Two required.
10	Sheet-metal screws. No. 6, 1/2-in. long. Ten required.
11	Speaker, woofer. Norelco Model AD8065/W8 (McGee Radio Co., 1901-07 McGee St., Kansas City, MO 64108).
12	Speaker, tweeter. Norelco Model AD0160/T8 (McGee Radio Co., 1901-07 McGee St., Kansas City, MO 64108).
13	Crossover capacitor, non-polarized 4-ufd electrolytic
14	Miscellaneous: Hook-up wire, plastic resin glue, 1-in. thick fiberglass damping material, thumbtacks.

V is for Voltage—not Vedder

The people of the industrial town of Erlangen, Germany have a clock with a difference. One face tells the time as do all other clocks in the town—but the other face tells a different story and it's not the weather. It shows what voltage is going through the town's power lines at that instant.

A large scale and pointer read out voltage so that the people going home in the winter can make any adjustments to ensure that a power cut won't happen. The town is surrounded by heavy industry which heavily drains the electrical supply. In this way the people of Erlangen can be forewarned should the worse happen.

One little footnote is that to date there has yet to be a power cut in this town. The people of Erlangen are quick to turn out a light that's not needed.

—Joe Gronk



ELEMENTARY ELECTRONICS

e/e etymology

How about a word with us?

BY WEBB GARRISON

Silver

▲ Among the elements that play a big role in electronics, silver was probably the first to be refined and named.

It was available in relatively pure state so early that no scholar knows precisely where it got its name. A Hittite term, *hattus*, designated the shiny metal and may have passed through half a dozen languages to enter medieval English as *seolver* or *selver*.

The earliest written occurrence in English was in a Psalter issued about 825 A.D., where the element was called "seolfur."

Designated by the symbol Ag (abbreviation for its Latin name) and having an atomic weight of 107.88, native silver occurs in small quantities in most parts of the world.

Medieval alchemists considered it a "noble" metal—a particularly appropriate title in view of the fact that no other naturally-occurring metal matches silver in its capacity to conduct heat and electricity.

Gold

▲ Until quite recently, gold has been too expensive to play a significant role in the electronics industry.

This situation changed when Bell Labs came up with what they called "beam leads"—gold conductors plated into place on silicon circuits. Western Electric developed ways to bond these minute components into circuits, and gold suddenly took on an entirely new role.

Practically all specialists in word lore agree that the precious element got its name from its color. A north-European suffix, *ghel-*, was tacked on to names of many things of yellow hue.

Because the yellow metal was prized so highly, it was mentioned so often that its name was abbreviated to *gull* in Old Norse and to *gulf* in Gothic. Apparently the Dutch form *goud* was the ancestor of Old High German *gold*.

At least one English-language reference to

gold has been preserved from about 725 A.D.—more than twelve centuries before the industrial value of the metal so greatly exceeded its utility as a medium of exchange that gold coins have disappeared from world commerce.

Zinc

▲ As the name of a hard bluish-white metal, *zinc* entered English during the seventeenth century. Scientists of that era borrowed it from Greek *zink*, whose origin is unknown.

Some properties of the metal were exploited very early. It wasn't until very recent times, however, that anyone considered it of remote interest in the electronics field.

Today the element whose atomic number is 30 is mostly used as a negative electrode in electric dry cells. Far more important, one of its many compounds—zinc telluride—is a basic ingredient in many semiconductors.

Because of special traits of the element whose name can't be traced beyond classical Greek, a zinc telluride semiconductor has a "forbidden band" of 2.2 electron-volts and operates as a transistor at temperatures up to 780°C.

Oxygen

▲ Oxygen was discovered—and named—long after silver, gold, and zinc were household words.

Antoine Lavoisier, whose head was chopped off by the guillotine on a bright May morning in 1794, made some of the most original discoveries of his day.

One of them came to focus upon the mysterious stuff called "phlogiston," long supposed to be a volatile constituent of combustibles that was liberated by burning.

In one of the most elegant experiments in the history of chemistry, Lavoisier demonstrated (to his own satisfaction) that there is no such thing as phlogiston. Instead, he insisted, the fraction of air that is vital to combustion and to breathing is a *principe oxygene*.

Many distinguished men hooted at such a notion. Even the great Joseph Priestley clung stubbornly to the inherited phlogiston theory.

Within a decade, however, world opinion began to swing over to the side of the daring Frenchman. With its cumbersome title shortened to *oxygen* Lavoisier's new "principle" was shown to be a gaseous element.

Experiments demonstrated that oxygen has almost demonic capacity to unite with zinc (as well as copper, iron, and other metals). Capacity of an oxidized metal to conduct heat and electricity is greatly reduced.

Alone among the more common naturally-occurring metals, gold and silver are scarcely affected by oxygen—but zinc oxides so readily under normal atmospheric conditions that the pure metal is useless in electronics. ■



**Train on this
315 sq. in.
picture
color TV
and get the
skills that
mean a
high-paying
career!**

Solid-State — the newest development

**Count on NTS training to always
feature the latest electronic equipment.**

Now included in two exciting NTS color TV courses, this set is the largest, most advanced color television made. Guided by the NTS "Lab-Project Method" of combining professional kits and easy-to-follow lessons, you build this color TV step by step — learning TV Servicing as you go! NTS has successfully trained thousands of men at home for rewarding careers as electronics technicians. Prepare for the great opportunity fields of TV-Radio Servicing, Computers, Communications, and Automation.


This solid-state color set contains: 45 transistors, 55 diodes, 2 silicon controlled rectifiers, and 4 advanced Integrated Circuits representing an addi-

tional 46 transistors and 21 diodes. The first solid-state color TV this large — yours to keep! It features Automatic Fine Tuning; "Instant On"; an Ultra-Rectangular Screen (25 in. diagonal measurement) that lets you see the complete transmitted image for the first time — a full 315 square inches; exclusive built-in Self Servicing features which eliminate the need to buy costly test equipment; exclusive design Solid-State VHF Tuner with an MOS Field Effect Transistor; 3-stage Solid-State IF; Automatic Chroma Control; Adjustable Noise Limiting and Gate Automatic Gain Control; High Resolution Circuitry; Matrix Picture Tube; and a specially formulated Etched Face Plate that eliminates unwanted glare, and heightens contrast. Colors are more vivid,

fresh tones more natural, and the picture is sharper than ever before. By training on this unique color TV, you'll gain the most up-to-date skills possible in TV Servicing!

Other valuable equipment you build and keep includes an AM SW Radio, Solid-State Radio, FET Volt-Ohmmeter, and Electronic-Tube Tester. All included in your tuition. You learn troubleshooting, hi-fi, multiplex systems, stereo, and color TV servicing. Step right into a technician's job at top pay or open a business of your own! For complete details on all NTS electronics courses, mail the coupon today for the full-color NTS Catalog. No obligation. No salesman will call.

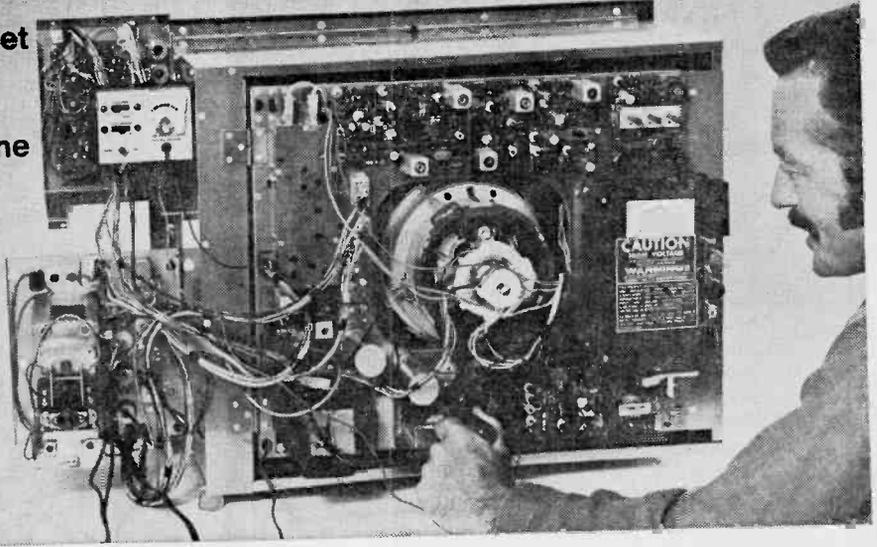**Build this set
and learn
solid-state
circuitry—the
electronics
of today!**



in color TV — comes to home training.


NTS ELECTRONICS & COMPUTER TECHNOLOGY

Build this exclusive NTS Computer-Trainer! Loaded with integrated circuits, it shows you the how, what, and why of computers. Learn this exciting field faster, more thoroughly. You also assemble and learn to operate an FET Volt-Ohmmeter and 5" wide band Oscilloscope.



NTS BLACK & WHITE TV AND RADIO SERVICING

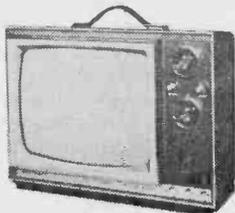Learn all phases of television, radio, stereo, and hi-fi. You receive this 74 sq. in. picture Solid-State B&W TV, Lo-Silho "Superhet" Radio, FET Volt-Ohmmeter, Solid-State Radio, Electronic Tube Checker, and Signal Generator. Start earning extra money even before you complete the course!



NTS ELECTRONICS COMMUNICATIONS & F.C.C.

Gain the security and prestige of owning an F.C.C. First Class Radio-Telephone License! Two comprehensive NTS courses cover the big opportunity field of transmitting and receiving. You build 14 kits, including a 5 watt AM Transceiver, 6 Transistor Pocket Radio, and FET Volt-Ohmmeter. Learn 2-way radio, Citizens Band, micro-waves and radar.



NTS INDUSTRIAL & AUTOMATION ELECTRONICS

Automation is the future of industry and you can play an important part! Learn industrial controls by training on the NTS Electro-Lab — a complete workshop. You also build and operate this 5" wide band Oscilloscope. And you perform experiments that involve regulating motor speeds, temperature, pressure, liquid level, and much more.



CIRCLE NO. 18 ON PAGE 17

Classroom Training at Los Angeles. You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in technical facilities. Check box in coupon.

APPROVED FOR VETERANS
Accredited Member: National Association of Trade & Technical Schools; National Home Study Council.

NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905
4000 South Figueroa Street, Los Angeles, Calif. 90037

Please rush Free Color Catalog and Sample Lesson, plus information on course checked below. No obligation. No salesman will call.



National Technical Schools

- 4000 S. Figueroa St.
Los Angeles, Calif. 90037
- Master Course in Color TV Servicing
 - Color TV Servicing (For Advanced Technicians)
 - Master Course in B&W TV & Radio Servicing
 - Master Course in Electronic Communication
 - Practical Radio Servicing
 - FCC License Course
 - Master Course in Electronics Technology
 - Industrial and Automation Electronics
 - Computer Electronics
 - Basic Electronics
 - High School at Home
- Dept. 222-012

Name Age


Address

City State Zip


Check if interested in Veteran Training under new G. I. Bill.
 Check if interested only in Classroom Training at Los Angeles.

E/E looks at new...

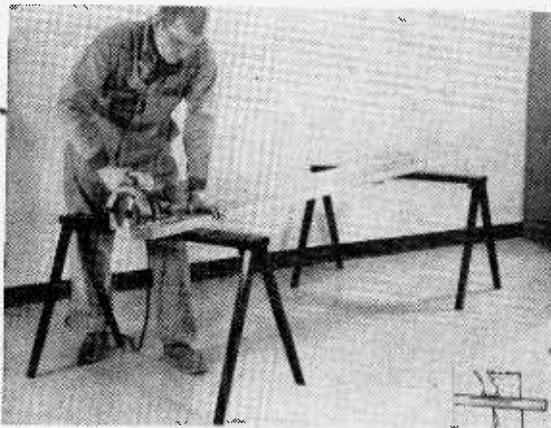
These heavy-duty Porta-Horse sawhorses will fold up into a size 38 by 2 by 4 inches, and can be hung on the wall by a built-in handle. The fold-up legs are spring-loaded and lock in place for rigid support. Cost is \$32.50 per pair. Circle No. 53 on Reader Service Page.



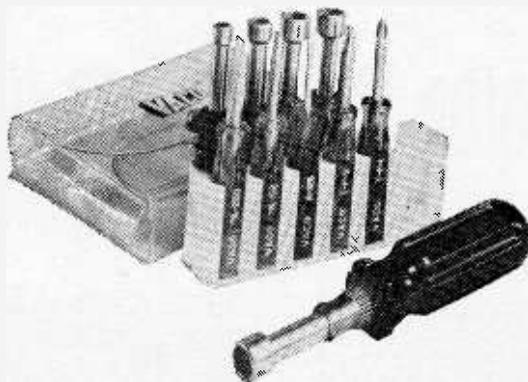Ten Torque Commander mini drivers by Vaco fit into the one handle. You get two Phillips, three regular slot, and five nut drivers, for \$8.95. Circle No. 54 on Reader Service Page.




Sold in light, unbreakable, one-piece plastic cases, Wen Pro-Power Tools are double-insulated for maximum safety, and have half-horsepower motors for powerful performance. The variable-speed $\frac{3}{8}$ -inch drill kit, model 801K12, consists of the drill, the red plastic case, nine drill bits from $\frac{1}{16}$ to $\frac{1}{4}$ inch, and a chuck key, for \$25.95. Circle No. 55 on Reader Service Page.

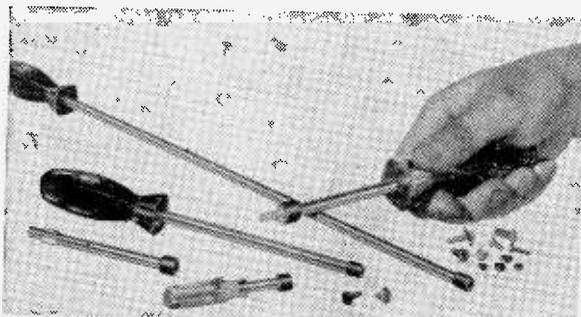

Magnetic nutdrivers in the $\frac{1}{4}$ -in. and $\frac{5}{16}$ -in. hex-socket sizes have been added to the Xcelite line of tools. An Alnico magnet in the socket holds fasteners firmly for easy retrieving hex screws, bolts and nuts. Circle No. 56 on Reader Service Page.

TOOLS AND GADGETS

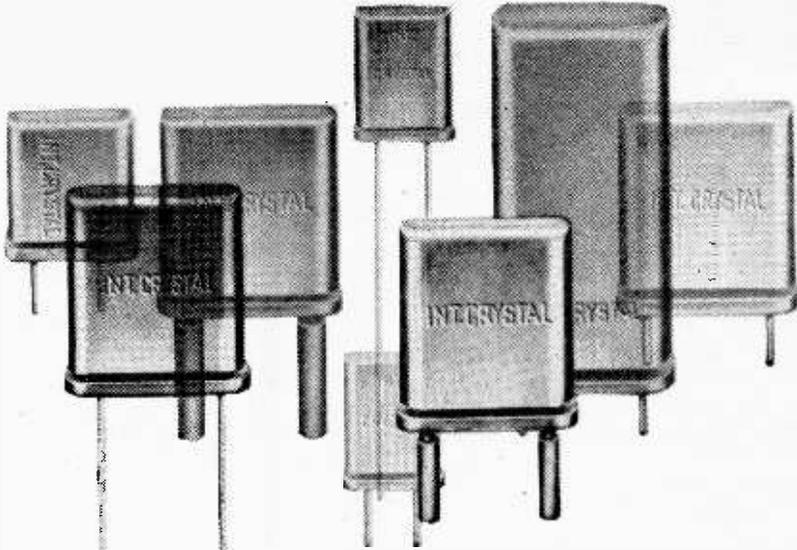

all about crystals

Discover that Electronics is more
rockbound than the State of Maine

BY TED MANN

Can you imagine the chaos on the AM broadcast band if transmitters drifted as much as those inexpensive table radios? The broadcast station engineer must keep his station carrier within 20 Hertz of its assigned frequency. How does he do it? What about the CB'er unable to contact his base station with an unstable, super-regen walkie-talkie. Lost calls don't often happen to a CB'er who can keep his receiver frequency right-on the assigned channel center.

This and much more is, of course, all done with a little help from a very basic material, the Quartz crystal. It is the single component that serves to fill a basic requirement for precision frequency control. Quartz crystals not only fix the frequency of radio transmitters (from CB installations to multi-kilowatt-broadcast installations), but also establish the frequency of timing pulses in many modern computers. In addition, they can provide the exceptional selectivity required to generate and receive single-sideband signals in today's crowded radio spectrum. Yet this list merely touches upon the many uses of quartz crystals. No exhaustive list has ever been compiled.

(turn page)



A Real Gem. This quiet controller is a substance surrounded by paradox. While quartz composes more than a third of the Earth's crust, it was one of the three most strategic minerals during World War II. And despite its plenitude, several semi-precious gems (including agate and onyx) are composed only of quartz.

Unfortunately, quartz exercises its control in only a relative manner. When it's misused, the control can easily be lost. For this reason, if you use it in any way—either in your CB rig, your Ham station, or your SWL receiver—you should become acquainted with the way in which this quiet controller functions. Only then can you be sure of obtaining its maximum benefits.

What Is It? One of the best starting points for a study of quartz crystals is to examine quartz itself. The mineral, silicon dioxide (SiO_2), occurs in two broad groups of mineral forms: crystalline and non-crystalline. Only the large crystalline form of quartz is of use as a controller.

The crystalline group has many varieties, one of which is common sand. The variety which is used for control, however, is a large, single crystal, usually six-sided. The leading source of this type of quartz is Brazil. However, it also is found in Arkansas. Attempts have been made to produce quartz crystals in the laboratory, but to date synthetic quartz has not proven practical for general use.

A property of crystalline quartz, the one which makes it of special use for control, is known as *piezoelectricity*. Many other crystals, both natural and synthetic, also have this property. However, none of them also have the hardness of quartz. To see why hardness and the piezoelectric property, when combined, make quartz so important, we must take a slight detour and briefly examine the idea of resonance and resonators.

Resonators and Resonance. As physicists developed the science of radio (the basis for modern electronics), they borrowed the acoustic notion of resonance and applied it to electrical circuits where it shapes electrical waves in a manner similar to an acoustic resonator. For instance, both coils and capacitors store energy and can be connected as a resonator (more often

termed a resonant circuit). When AC of appropriate frequency is applied to the resonator, special things happen.

Pendulum Demonstrates. The principle involved is identical to that of a pendulum, which is itself a resonator closely similar in operation to our quartz crystals. To try it you can hang a pendulum of any arbitrary length (Fig. 1), start it swinging, then time its *period*—one complete swing or cycle. The number of such swings accomplished in exactly one second on the *natural* or *resonant* frequency of the pendulum in cycles per second (Hertz).

You can, by experiment, prove that the frequency at which the pendulum swings or oscillates is determined by the length of the pendulum. The shorter the pendulum (Fig. 2), the faster it swings (the greater the frequency). The weight of the pendulum has no effect on frequency, but has a marked effect upon the length of time the pendulum will swing after a single initial push—the heavier the pendulum, the greater the number of cycles.

A Real Swinger. Once the pendulum begins to swing, very little effort is required to keep it swinging. Only a tiny push is needed each cycle, provided that the push is always applied just as the pendulum begins to move *away* from the pushing point. If the push is given too soon, it will interfere with the swinging and actually cause the swing to stop sooner than it would without added energy; while if too late, added push will have virtually no effect at all. It is this principle—a tiny push at exactly the right time interval—which makes a resonator sustain sound or AC waves. You can prove it with the pendulum by first determining the resonant frequency of a pendulum, then stopping it so that it is completely still. A series of small pushes, delivered at the natural resonant frequency, (each too tiny to have more than a minute effect) will very rapidly cause the pendulum to swing to its full arc again. Pushes of the same strength at any other frequency will have little or no effect.

The pendulum is an excellent control mechanism for regulating a clock to keep time to the second, since the resonant frequency of the pendulum can readily be adjusted to be precisely one cycle per second. However, for control of audio frequencies from tens of Hertz (cycles per second) up to tens of thousands of cycles per second (kilohertz), or for radio frequencies ranging up

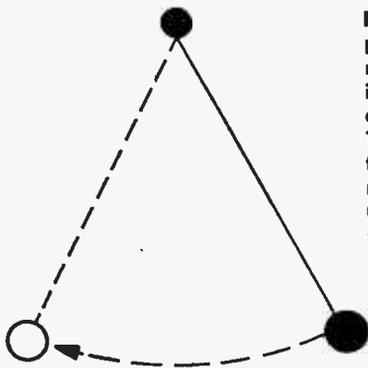


Fig. 1. A long pendulum swings at a rate determined by its length and weight at the end of the arm. To experiment at home, the arm should be made of light thread (no weight) and a small heavy mass (all the weight concentrated at one point).

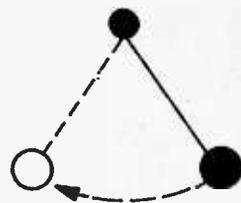


Fig. 2. A short pendulum swings at a faster rate no matter what the weight is. The heavier the weight, the longer the pendulum will swing at the faster rate.

Fig. 3. The geometry of the tuning fork produces a continuous pure tone for a long time when struck gently. It is favored by piano tuners as a convenient way to carry a source of accurately-known tone or pitch.


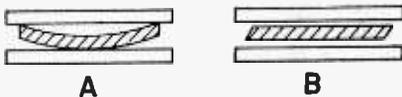


Fig. 4. Depending on how the crystal is cut or sliced from the mother crystal, some crystals warp or bend as in A and others shear as shown in B. Each of the many cuts have special characteristics.

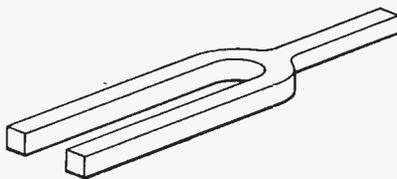

to hundreds of millions of cycles per second (Megahertz), the pendulum is too cumbersome a device.

The Tuning Fork. In the audio range, the equivalent of the pendulum is the tuning fork. This is an extremely elongated U-shaped piece of metal (Fig. 3), usually with a small handle at the base. When struck, it emits a single musical tone.

The operating principle is exactly the same as the pendulum. Each of the arms or tines of the fork corresponds to a pendulum arm. But here the arms are extremely short and much heavier in proportion to their size than the pendulum. (The shorter the arms of a tuning fork, the higher the resonant frequency in the audio range.) This greatly increased mass causes them to oscillate much longer when struck.

Not all tuning forks operate precisely like pendulums. The pendulum principle is based on a *flexing* of the arm upon its long dimension. While this is the most common operation, the fork may flex along any dimension.

It's even possible for a single, solid resonator such as a tuning fork to flex along several dimensions at once. A main part of the design of a good tuning fork is to insure that only a single dimension flexes

or, in the language of resonators, only a single mode is excited.

Area Too. There's no requirement that the resonator be a completely solid substance. A mass of air, suitably enclosed, forms a resonator. This is the resonator that works on a classic guitar or violin. Here, single-mode operation is distinctly *not* desired. Instead, multiple-mode operation is encouraged so that all musical tones within the range of the instrument will be reinforced equally.

Now, with the principles of resonance firmly established, we can return to the quartz crystal and its operation.

Quartz Crystals as Resonators. Like the tuning fork or, for that matter, any sufficiently hard object, the quartz crystal is capable of oscillation when struck physically or in some other way excited.

But unlike the tuning fork, or indeed any other object except for certain extremely recent synthetic materials, the quartz crystal is not only sufficiently hard to oscillate at one or more resonant frequencies, but is piezoelectric.

Piezoelectricity. The piezoelectric property means simply that the crystal generates an electric voltage when physically stressed or, on the other hand, will be physically

ALL ABOUT CRYSTALS

deformed when subjected to a voltage (See Fig. 4). Other familiar objects making use of piezoelectricity include crystal and ceramic microphone elements and phonograph cartridges.

This virtually unique combination of properties (sufficient hardness for oscillation and piezoelectricity) found in quartz crystals, makes it possible to provide the initial push to the crystal by impressing a voltage across it. To provide the subsequent regular pushes, a voltage can be applied at appropriate instants.

Quality Factor. Almost any discussion of resonance and resonant circuits (or for that matter, inductance) eventually gets to a rather sticky subject labelled in the earliest days of radio, *quality factor* but now known universally as Q .

As used in radio and electronics, Q is usually defined by other means. Some of the definitions put forth at various times and places include:

- *The ratio of resistance to reactance in a coil.*
- *The ratio of capacitive reactance in a resonant circuit to the load resistance.*
- *The impedance multiplication factor, and others even more confusingly worded.*

All, however, come out in the end to be identical to the definitions cited above: The Q of a resonator is the ratio of the energy stored per cycle to the energy lost per cycle.

In a resonator, high Q is desirable. Q is a measure of this energy loss. The less energy lost, the greater the Q of the circuit.

Not so obvious (and rather difficult to prove without going into mathematics) are some of the other effects of Q . A resonant circuit is never completely selective; frequencies which are near resonance but not precisely equal to the resonant frequency pass through also!

An Interesting Fraction. The greater the Q , the narrower the band of frequencies which can affect the resonator. Specifically, the so-called half-power bandwidth (Fig. 5) of a resonator (that band in which signals are passed with half or more of the power possessed by signals at the exact resonant frequency) is expressible by the fraction F_o/Q , where F_o is the resonant frequency and Q is the circuit Q . Thus a 455 kHz

resonant circuit with a Q of 100 will have a half-power bandwidth of $455/100$ kHz, or 4.55 kHz. This relation is an approximation valid only for single-tuned circuits; more complex circuits are beyond this basic discussion.

The Q of Quartz Crystals. When we talk of the Q of conventional resonant circuits composed of coils and capacitors, a figure of 100 is usually taken as denoting very good performance and Q values above 300 are generally considered to be very rare.

The Q of a quartz crystal, however, is much higher. Values from 25,000 to 50,000 are not unheard of.

The extremely high Q makes the crystal a much more selective resonator than can be achieved with L-C circuitry. At 455 kHz, for example, the bandwidth will be between 10 and 20 Hertz (*cycles per second*) unless measures are taken to reduce Q . Even in practice (which almost never agrees with theory), 50-Hertz bandwidths are common with 455-kHz crystal filters.

So far as external circuitry is concerned, the crystal appears to be exactly the same as an L-C resonant circuit except for its phenomenal Q value. See Fig. 6.

At series resonance, the crystal has very low impedance. You may hear this effect referred to as a *zero* of the crystal. At parallel resonance, impedance is very high; this is sometimes called a *pole*. Fig. 7 shows a plot of *pole* and *zero* for a typical crystal. The special kind of crystal filter known as a half-lattice circuit matches the *pole* of one crystal against the *zero* of another, to produce a passband capable of splitting one sideband from a radio signal. Such filters are widely used in Ham, commercial and, to a lesser extent, in CB transmitters.

When a crystal is used to control the frequency of a radio signal or provide a source of accurate timing signals, either the *pole* or the *zero* may be used. Circuits making use of the *pole* allow more simple adjustment of exact frequency, while those making use of the *zero* often feature parts economy. Later we'll examine several of each type.

From Rock to Finished Crystal. To perform its control functions properly, a quartz crystal requires extensive processing. The raw quartz crystal must be sliced into plates of proper dimension, then ground to the precise size required. Each plate must be as close to precisely parallel, and as perfectly

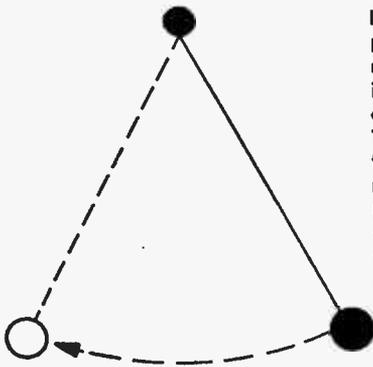


Fig. 1. A long pendulum swings at a rate determined by its length and weight at the end of the arm. To experiment at home, the arm should be made of light thread (no weight) and a small heavy mass (all the weight concentrated at one point).



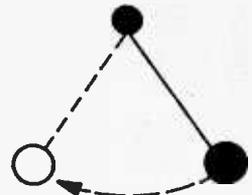
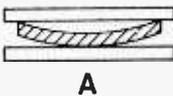


Fig. 2. A short pendulum swings at a faster rate no matter what the weight is. The heavier the weight, the longer the pendulum will swing at the faster rate.

Fig. 3. The geometry of the tuning fork produces a continuous pure tone for a long time when struck gently. It is favored by piano tuners as a convenient way to carry a source of accurately-known tone or pitch.

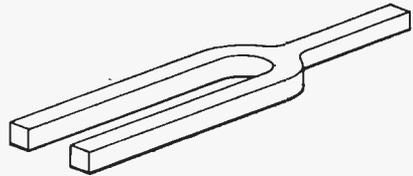

A

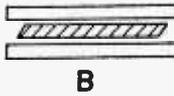

B

Fig. 4. Depending on how the crystal is cut or sliced from the mother crystal, some crystals warp or bend as in A and others shear as shown in B. Each of the many cuts have special characteristics.

to hundreds of millions of cycles per second (Megahertz), the pendulum is too cumbersome a device.

The Tuning Fork. In the audio range, the equivalent of the pendulum is the tuning fork. This is an extremely elongated U-shaped piece of metal (Fig. 3), usually with a small handle at the base. When struck, it emits a single musical tone.

The operating principle is exactly the same as the pendulum. Each of the arms or tines of the fork corresponds to a pendulum arm. But here the arms are extremely short and much heavier in proportion to their size than the pendulum. (The shorter the arms of a tuning fork, the higher the resonant frequency in the audio range.) This greatly increased mass causes them to oscillate much longer when struck.

Not all tuning forks operate precisely like pendulums. The pendulum principle is based on a *flexing* of the arm upon its long dimension. While this is the most common operation, the fork may flex along any dimension.

It's even possible for a single, solid resonator such as a tuning fork to flex along several dimensions at once. A main part of the design of a good tuning fork is to insure that only a single dimension flexes

or, in the language of resonators, only a single mode is excited.

Area Too. There's no requirement that the resonator be a completely solid substance. A mass of air, suitably enclosed, forms a resonator. This is the resonator that works on a classic guitar or violin. Here, single-mode operation is distinctly *not* desired. Instead, multiple-mode operation is encouraged so that all musical tones within the range of the instrument will be reinforced equally.

Now, with the principles of resonance firmly established, we can return to the quartz crystal and its operation.

Quartz Crystals as Resonators. Like the tuning fork or, for that matter, any sufficiently hard object, the quartz crystal is capable of oscillation when struck physically or in some other way excited.

But unlike the tuning fork, or indeed any other object except for certain extremely recent synthetic materials, the quartz crystal is not only sufficiently hard to oscillate at one or more resonant frequencies, but is piezoelectric.

Piezoelectricity. The piezoelectric property means simply that the crystal generates an electric voltage when physically stressed or, on the other hand, will be physically

e/e ALL ABOUT CRYSTALS

deformed when subjected to a voltage (See Fig. 4). Other familiar objects making use of piezoelectricity include crystal and ceramic microphone elements and phonograph cartridges.

This virtually unique combination of properties (sufficient hardness for oscillation and piezoelectricity) found in quartz crystals, makes it possible to provide the initial push to the crystal by impressing a voltage across it. To provide the subsequent regular pushes, a voltage can be applied at appropriate instants.

Quality Factor. Almost any discussion of resonance and resonant circuits (or for that matter, inductance) eventually gets to a rather sticky subject labelled in the earliest days of radio, *quality factor* but now known universally as Q .

As used in radio and electronics, Q is usually defined by other means. Some of the definitions put forth at various times and places include:

- *The ratio of resistance to reactance in a coil.*

- *The ratio of capacitive reactance in a resonant circuit to the load resistance.*

- *The impedance multiplication factor, and others even more confusingly worded.*

All, however, come out in the end to be identical to the definitions cited above; The Q of a resonator is the ratio of the energy stored per cycle to the energy lost per cycle.

In a resonator, high Q is desirable. Q is a measure of this energy loss. The less energy lost, the greater the Q of the circuit.

Not so obvious (and rather difficult to prove without going into mathematics) are some of the other effects of Q . A resonant circuit is never completely selective; frequencies which are near resonance but not precisely equal to the resonant frequency pass through also!

An Interesting Fraction. The greater the Q , the narrower the band of frequencies which can affect the resonator. Specifically, the so-called half-power bandwidth (Fig. 5) of a resonator (that band in which signals are passed with half or more of the power possessed by signals at the exact resonant frequency) is expressible by the fraction F_o/Q , where F_o is the resonant frequency and Q is the circuit Q . Thus a 455 kHz

resonant circuit with a Q of 100 will have a half-power bandwidth of $455/100$ kHz, or 4.55 kHz. This relation is an approximation valid only for single-tuned circuits; more complex circuits are beyond this basic discussion.

The Q of Quartz Crystals. When we talk of the Q of conventional resonant circuits composed of coils and capacitors, a figure of 100 is usually taken as denoting very good performance and Q values above 300 are generally considered to be very rare.

The Q of a quartz crystal, however, is much higher. Values from 25,000 to 50,000 are not unheard of.

The extremely high Q makes the crystal a much more selective resonator than can be achieved with L-C circuitry. At 455 kHz, for example, the bandwidth will be between 10 and 20 Hertz (*cycles per second*) unless measures are taken to reduce Q . Even in practice (which almost never agrees with theory), 50-Hertz bandwidths are common with 455-kHz crystal filters.

So far as external circuitry is concerned, the crystal appears to be exactly the same as an L-C resonant circuit except for its phenomenal Q value. See Fig. 6.

At series resonance, the crystal has very low impedance. You may hear this effect referred to as a *zero* of the crystal. At parallel resonance, impedance is very high; this is sometimes called a *pole*. Fig. 7 shows a plot of *pole* and *zero* for a typical crystal. The special kind of crystal filter known as a half-lattice circuit matches the *pole* of one crystal against the *zero* of another, to produce a passband capable of splitting one sideband from a radio signal. Such filters are widely used in Ham, commercial and, to a lesser extent, in CB transmitters.

When a crystal is used to control the frequency of a radio signal or provide a source of accurate timing signals, either the *pole* or the *zero* may be used. Circuits making use of the *pole* allow more simple adjustment of exact frequency, while those making use of the *zero* often feature parts economy. Later we'll examine several of each type.

From Rock to Finished Crystal. To perform its control functions properly, a quartz crystal requires extensive processing. The raw quartz crystal must be sliced into plates of proper dimension, then ground to the precise size required. Each plate must be as close to precisely parallel, and as perfectly

flat, as possible. The electrodes must be in proper contact with the polished plate; in many modern units, the electrodes are actually plated directly to the crystal surface, usually with gold.

The crystal plate is known as a *blank* when it is sliced from the raw crystal. The blank is cut at a precise angle with respect to the optical and electrical axes of the raw crystal, as shown in Fig. 8. Each has its own characteristics for use in specific applications. Some, notably the *X*- and *Y*-

cuts, are of only historic interest. The *Y*-cut, one of the first types used, had a bad habit of jumping in frequency at critical temperatures. The *X*-cut did not jump, but still varied widely in frequency as temperature changed.

Today's crystals most frequently use the *AT* cut for frequencies between 500 kHz and about 6 MHz, and the *BT* cut for between 6 and 12 MHz. Above 12 MHz, most crystals are specially processed *BT*- or *AT*-cuts used in *overtone* modes. These

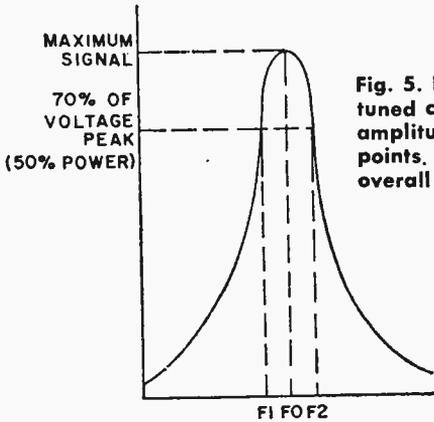


Fig. 5. Bandwidth characteristic of a typical tuned circuit shows the peak or maximum signal amplitude and the 70% voltage peak (50% power) points. This is the characteristic that determines overall selectivity.



Fig. 6. Diagram is a typical equivalent circuit for a crystal. As resistance is lowered to near zero, crystal efficiency increases. In use, the crystal holder and external circuit add some capacitance across the entire circuit.

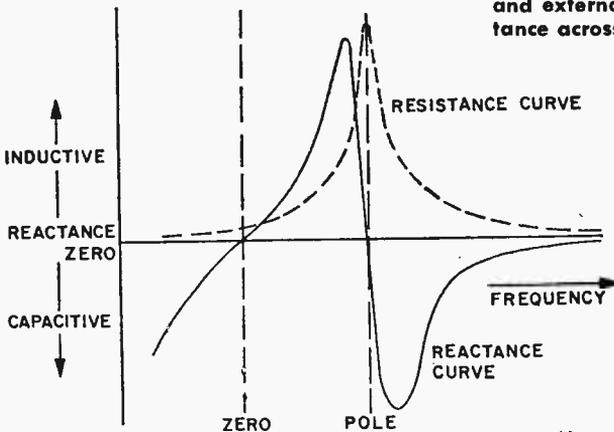


Fig. 7. Some characteristics of a quartz crystal. When slightly off resonant frequency (at the pole) a crystal exhibits inductive or capacitive reactance—just like an LC circuit.

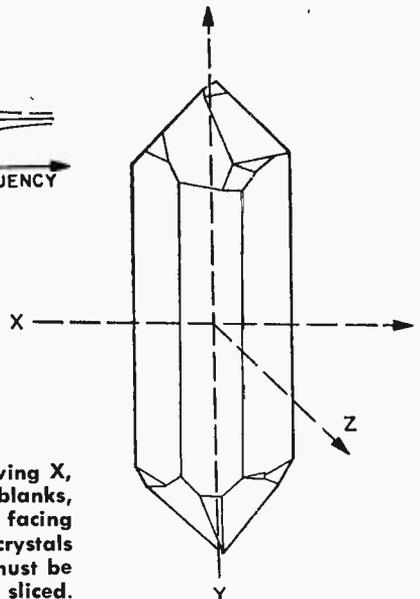


Fig. 8. A view of a mother crystal showing *X*, *Y* and *Z* axes. Crystal is sliced into blanks, ground to frequency, polished and plated (on facing sides) to make permanent electrodes. All crystals are not made perfect by Mother Nature and must be examined optically before being sliced.

e/e ALL ABOUT CRYSTALS

cuts are important to crystal makers and not relevant to our layman's theory.

The blanks are cut only to approximate size. The plates are then polished to final size in optical "lapping" machines which preserve parallelism between critical surfaces. During the final stages of polishing, crystals are frequently tested against standard frequency sources to determine exact frequency of operation.

If electrodes are to be plated onto the crystal surfaces, frequency cannot be set precisely by grinding since the electrodes themselves load the crystal slightly and cause a slight decrease in operating frequencies. These crystals are ground just a trifle above their intended frequencies, and the thickness of the electrodes is varied by varying plating time to achieve precision.

Accuracy. The precision which can be attained in production of quartz crystals is astounding. Accuracy of ± 0.001 percent is routine, and 10-time-better accuracy is not difficult. In absolute figures, this means an

error of one cycle per Megahertz. In another frame of reference, a clock with the same accuracy would require more than 11 days to gain or lose a single second.

However, such accuracy can be achieved only when certain precautions are taken. For instance, the frequency of a crystal depends upon the circuit in which it is used as well as upon its manufacture. For an accuracy of $\pm 0.005\%$ or greater, the crystal must be ground for a single specific oscillator. If $\pm 0.001\%$ (or better) circuit accuracy is required, it must be tested in that circuit only. Thus, CB transmitters are on the narrow edge of being critical. This is why all operating manuals include a caution to use only crystals made specifically for that transmitter.

When one part-per-million accuracy is required, not only must the crystal be ground for a single specific oscillator, but most often the oscillator circuit must then be adjusted for best operation with the crystal; this round-robin adjustment must be kept up until required accuracy is achieved. Even then, crystal aging may make readjustment necessary for the first 12 to 18 months.

Frequency Variation—Causes and Cures.

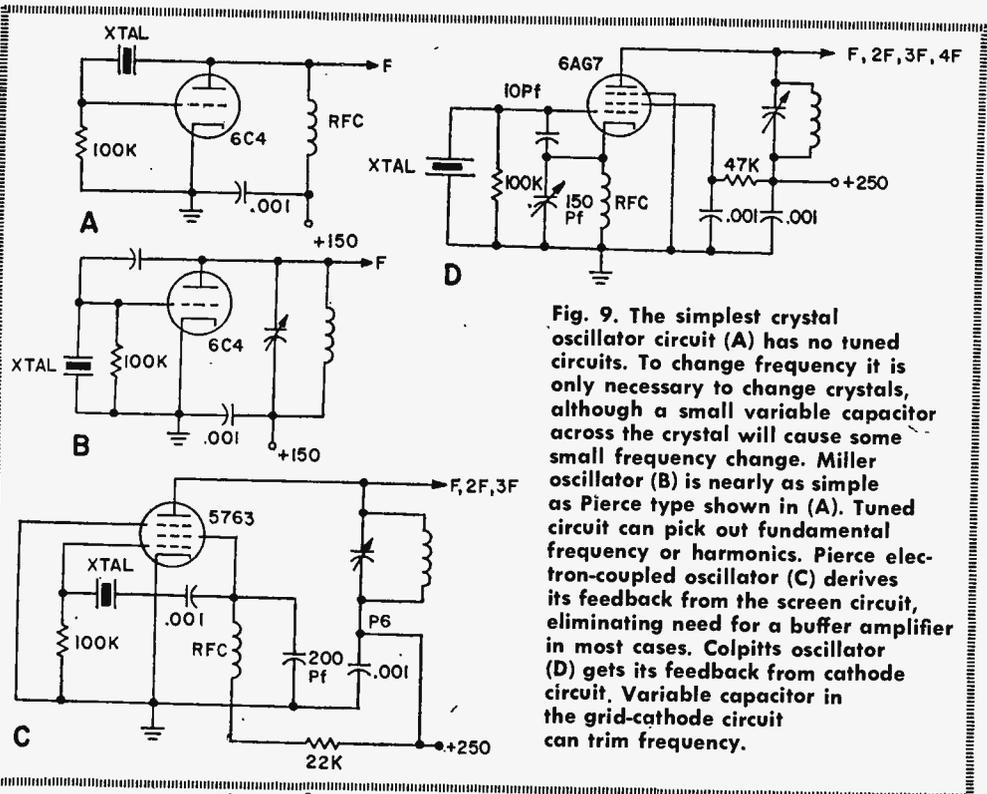


Fig. 9. The simplest crystal oscillator circuit (A) has no tuned circuits. To change frequency it is only necessary to change crystals, although a small variable capacitor across the crystal will cause some small frequency change. Miller oscillator (B) is nearly as simple as Pierce type shown in (A). Tuned circuit can pick out fundamental frequency or harmonics. Pierce electron-coupled oscillator (C) derives its feedback from the screen circuit, eliminating need for a buffer amplifier in most cases. Colpitts oscillator (D) gets its feedback from cathode circuit. Variable capacitor in the grid-cathode circuit can trim frequency.

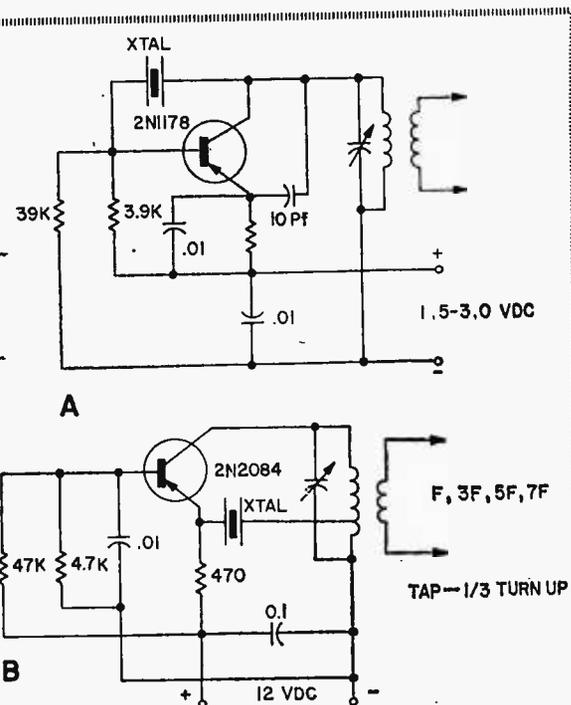


Fig. 10. Fundamental frequency transistorized oscillator (A) is quite similar to that in Fig. 9A. One difference is that tuned circuit in output replaces RFC unit. The overtone (harmonic) circuit (B) uses crystal for odd harmonic feedback. Either circuit can be used for fundamental frequency operation—just tune.

Possible variations in frequency stem from three major causes while cures depend entirely upon the application.

The most obvious cause of frequency variation is temperature. Like anything else, the crystal will change in size when heated and the frequency is determined by size. Certain cuts show less change with temperature than do others, but all have at least some change.

For most noncommercial applications, the heat-resistant cuts do well enough. For stringent broadcast station and critical time-signal requirements, the crystal may be enclosed in a small thermostatically-regulated oven. This assures that the steady temperature will cure one cause of frequency change.

The second well known cause for variation of frequency is external capacitance. Some capacitance is always present because the crystal electrodes form the plates of a capacitor where the crystal itself is the di-

electric. Most crystals intended for amateur use are designed to accommodate an external capacitance of 32 pF, so if external capacitance is greater than this, the marked frequency may not be correct. Crystals for commercial applications are ground to capacitance specifications for the specific equipment in which they are to be used. CB crystals also are ground for specific equipment, although many transceivers employ the 32 pF standard set for Ham applications.

Trim a Frequency. When utmost precision is required, a small variable capacitor may be connected in parallel with the crystal and adjusted to change frequency slightly. The greater the capacitance, the lower the frequency. Changes of up to 10 kHz may be accomplished by this means, although oscillation may cease when excessive changes are attempted.

Like temperature caused variations, frequency variations due to capacitance may be useful in special cases. Hams operating in the VHF regions obtain frequency modulation by varying load capacitance applied to the crystal in their transmitters.

The third cause for variation of frequency is a change in operating conditions in the associated circuit. This cause is more important with vacuum-tube circuits than with semiconductor equipment. As a rule, operating voltages for any vacuum-tube oscillator providing critical signals should be regulated to prevent change.

Again, this cause can be used to provide FM by deliberately varying voltages.

Crystal Aging. A final cause of frequency variation, small enough to be negligible in all except the most hypersensitive applications, is crystal aging. When a crystal is first processed, microscopic bits of debris remain embedded in its structure. These bits are displaced during the first 12 months or so of use, but during that time the crystal frequency changes by a few parts per million. Extreme accuracy applications must take this change into account. For most uses, though, it may be ignored.

Using Quartz Crystals. After all the discussion of crystal theory, it's time to examine some typical circuits. While dozens of special crystal circuits have been developed for special applications, a sampling will suffice for discussion. Fig. 9 shows four typical vacuum tube crystal oscillator circuits.

The simplest of these is the Pierce circuit, Fig. 9A. While at first glance this

e/e ALL ABOUT CRYSTALS

circuit appears to employ the crystal's *zero* to feed back energy from plate to grid, the *pole* is actually used through a mathematically-complex analysis. This circuit has one unique advantage; it contains no tuned elements and, therefore, can be used at any frequency for which a crystal is available. This makes it an excellent low-cost test signal source. The major disadvantage is that excessive current may be driven through the crystal if DC plate voltage rises above 90 or so.

The Miller oscillator (Fig. 9B) is almost as simple to construct and operate as is the Pierce and has an additional advantage of operation with overtone crystals. This is the circuit recommended by *International Crystal Mfg. Co.* for use with their overtone crystals. The capacitor shown between plate and grid is usually composed of grid-plate capacitance alone. The *pole* is used here

also, energy feeds back through the grid-plate capacitance, and the *pole* selects only the parallel-resonant frequency (shorting the rest to ground).

ECO. The electron-coupled Pierce oscillator (Fig. 9C), is similar to the basic Pierce. The tuned circuit in the plate offers the possibility of emphasizing a harmonic—an RF choke may be used instead if freedom from tuning is desired and fundamental-frequency operation will suffice.

GPO. One of the most popular oscillators of all time is the Colpitts Crystal oscillator of Fig. 9D, sometimes known as the *grid-plate* oscillator. The feedback arrangement here consists of the two capacitors in the grid circuit; feedback is adjusted by means of the 150 pF variable capacitor (the greater the capacitance, the less the feedback) until reliable oscillation is obtained. Like the other three oscillators, this circuit employs the crystal *pole* frequency.

Since all four of these oscillator circuits utilize the *pole* for frequency control, exact

(Continued on Page 100)

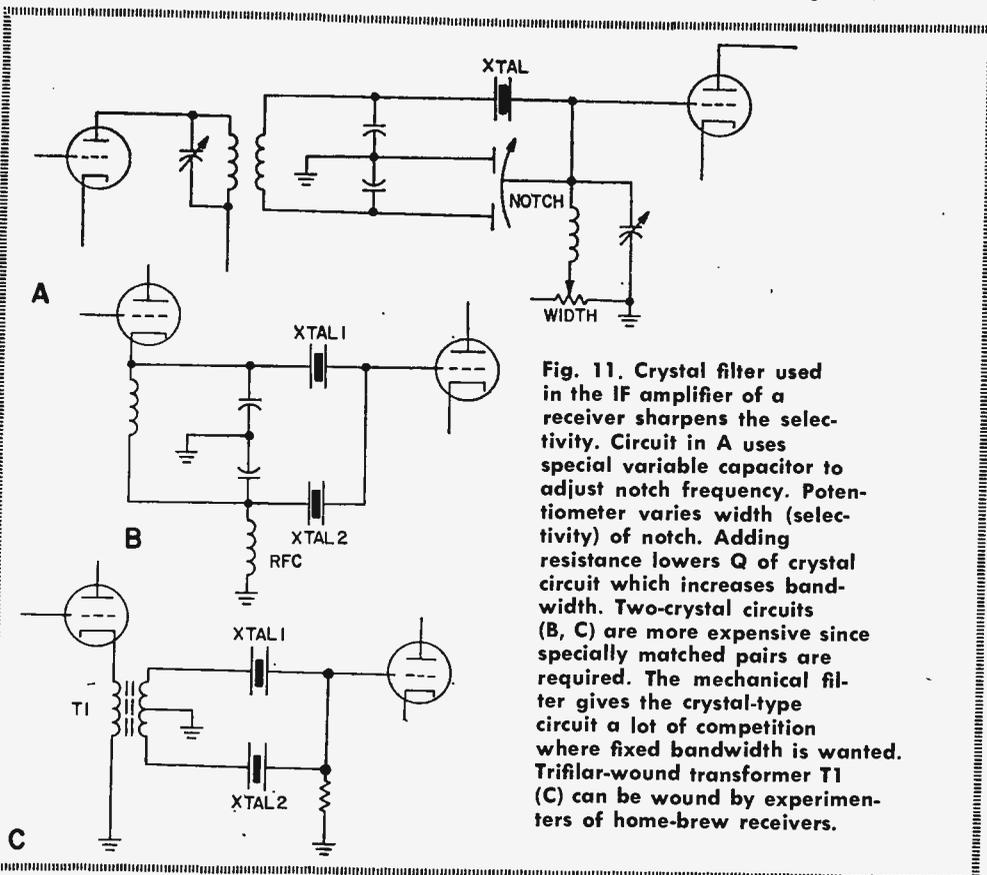


Fig. 11. Crystal filter used in the IF amplifier of a receiver sharpens the selectivity. Circuit in A uses special variable capacitor to adjust notch frequency. Potentiometer varies width (selectivity) of notch. Adding resistance lowers Q of crystal circuit which increases bandwidth. Two-crystal circuits (B, C) are more expensive since specially matched pairs are required. The mechanical filter gives the crystal-type circuit a lot of competition where fixed bandwidth is wanted. Trifilar-wound transformer T1 (C) can be wound by experimenters of home-brew receivers.



KATHI'S CB CAROUSEL


By Kathi Martin, KAIQ614

Hi fellas. This is Kathi again reporting on something that's really important to me and, I know, to all us CB'ers: How well is the new Channel 9 Emergency Monitor system working?

Well, I'm very happy to say in the opinion of just about all those involved—from the Camden Hills in Maine to Colorado's San Juan National Forest and along Highway 101 in California—it's a Smashing success!!! Our National Calling Frequency

in this summer's Channel 9 "rescue" operations here's a great big THANKS for showing that CB is right-on.

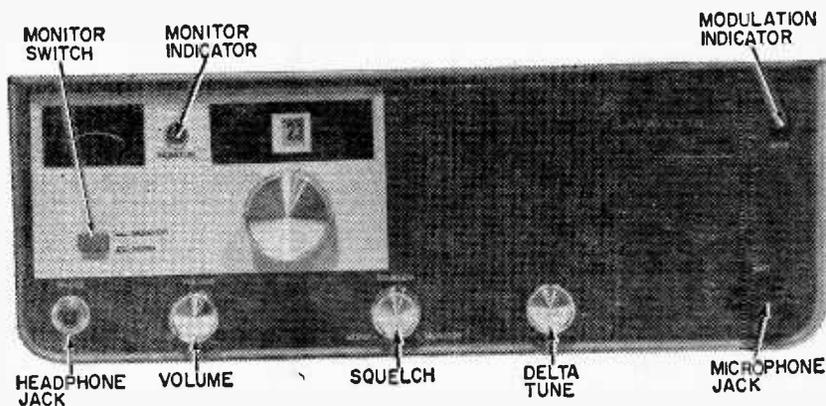
If you haven't joined the Channel 9 Bandwagon, what's holding you up? As we'll see, you don't even have to listen all the time, and if you're upgrading your rig, it costs just a little more for one with a built-in, full time Channel 9 monitor. We've tested just such a rig for this issue, Lafayette Radio's Telsat 924. *(Turn Page)*



This rig is both convenient to operate and attractive. Front of rig has monitor switch, squelch control, and indicator added to the standard operator controls.

Channel 9 passed its first big test, the 1971 vacation and travel season. As politicians say, "From the rockbound coast of Maine to the sunny shores of California . . .", Channel 9 was as hot as toddy on a winter's eve. It seems that just about everybody, from stranded autos to Winnebagos in National Parks, used or helped monitor the channel. Caravans—three or more travel trailers, campers, motorhomes, or tent trailers together—would switch to another channel (often 11) for necessary intracaravan communications. This is really groovy, for it's this spirit of cooperation among CB'ers that makes Channel 9's purpose workable

If either you or your club were involved

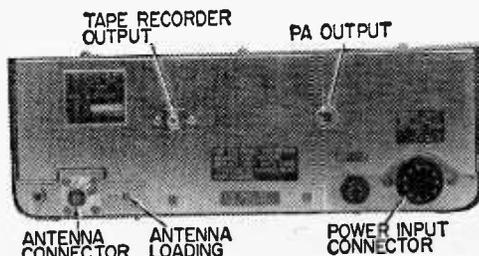

Telsat 924 two channel monitor receiver uses common antenna for both receivers.

e/e KATHI'S CB CAROUSEL

My Report. The Telsat 924 consists of a standard 23 channel high performance transceiver and a completely independent crystal controlled Channel 9 monitor receiver. And just to prove it's a "professional" transceiver, the 924 has a tape recorder output jack for tape-logging all received signals.

The 924 is housed in a 11-13/16-in. W x 4-5/16-in. H x 8-in. D cabinet. The power supply is 117 VAC or 12 VDC. The unit is normally supplied with an AC and 12V negative ground DC cable. A positive ground DC cable is optional. Operating features include a combination S/RF output meter, headphone jack, P.A. output jack, Delta tuning, tape recorder output jack and an external antenna loading adjustment.

A peek inside the box will find a double conversion "standard" receiver with mechanical filter for needle sharp selectivity. Also connected to the antenna input, and in no way affecting the performance of the main receiver, is a crystal controlled, single conversion monitor receiver, with its own squelch and a "channel in use" indicator light. A switch mounted on the front panel selects either the standard or monitor receiver for connection to the speaker. With this feature, an XYL can busy herself around the house without missing a call.

In typical operation, the channel selector determines the transmit and receive frequency, but the Channel 9 monitor receiver is always in operation regardless of the channel being used for routine communications. As soon as the monitor receiver senses a signal on Channel 9, the monitor squelch releases and starts a multivibrator that causes the panel-mounted monitor lamp to blink rapidly. To hear what's happening on Channel 9 you simply push the panel mounted *monitor-norm* switch, thereby switching the speaker output to the Channel 9 monitor. For full time monitoring of Channel 9, either the normal channel selector can be set to Channel 9, or the *monitor-norm* switch can be set to *monitor*.


The transmitter is standard; output frequency is determined by the channel selector, so it is necessary to switch to Channel 9 in order to answer an "emergency call".

Easy to use. Though jam packed with circuits, the Telsat 924 doesn't look much different from other transceivers. There is the usual volume, squelch and channel selector controls. The monitor receiver squelch is concentric with the normal squelch, so the only extra hardware on the front panel is the *monitor-norm* pushbutton. (Either the normal receiver or monitor receiver is selected by simply pushing the switch.)

And because the main receiver's selectivity is so high, a ± 1.5 kHz Delta Tune is provided to pull in signals that might be way off the center channel.

Performance is really great.

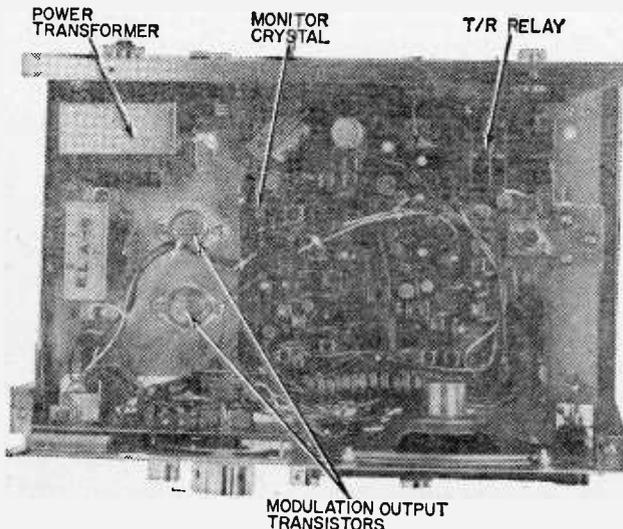Though the Telsat 924 is budget priced (\$139.95 includes microphone, AC and DC power cables, mobile mount and all crystals including the
(Continued on page 101)



A look inside the '924 reveals use of chassis as modulation and audio output transistor heat sink. Adequate "sinking" insures cool components and longer operating lifetime.

e/e checks out the zero-tracking...

Garrard Zero 100 Automatic Turntable



For almost 25 years, since the beginning of modern high fidelity sound, audio manufacturers have searched for the perfect tone arm; one that would track tangent (at right angles) to the record grooves remained as the last frontier. Most attempts at tangent tracking were noble, valiant efforts that either turned out to have unsuspected problems or were astronomically expensive.

But now, we finally have a viable tangent tracking system of rather simple, trouble-free construction; one easily mated to a quality turntable. Such a system is Garrard's Zero 100 Automatic Turntable.

The importance of tangent tracking lies in the manner by which the record master's grooves are cut. Every modern cutting lathe tracks the cutterhead straight across the disc, with the cutter always positioned at right angles to the cutting stylus motion. On the other hand, standard tone arms are


pivoted at the rear; the arm swings across the disc in an arc, so the playback stylus can be at right angles to the record grooves at only two points.

With modern tone arms, pickups and good quality discs the pivoted arm does an excellent job at tracking. But on well worn or poorly pressed, and some high level, discs, the slight tracking error at the inner diameter combined with the high velocity of the inner diameter grooves can cause mind-shattering distortion. But track this mind-shattering disc with a tangent tone arm, in particular the Garrard Zero 100, and the distortion is sharply reduced to an "acceptable" value.

What it is. The Zero 100 is basically two independent systems: 1) a very good automatic turntable mechanism; 2) the articulated tangent tracking tone arm. Garrard simply chose to combine both into a single automatic turntable system.

The Zero 100 provides for two speeds: 33 and 45 rpm. The multi-position speed selector also determines the indexing for 7 in., 10 in. and 12 in. records. Around (concentric with) the speed selector is a control for varying the speed 3.5% either way. To insure precise setting of the playing speed, a strobe disc is provided on the underside of the turntable that is under continuous illumination. A mirror reflexes the strobe disc so

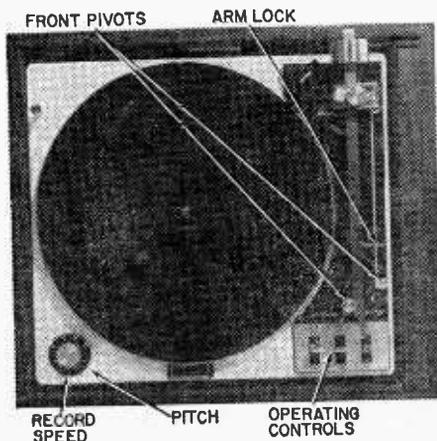Simple easy-to-use operator controls are augmented by built-in stroboscope. Speed is variable for a pitch adjustment to one semitone, a boon for professional and semi-professional music use. Arm-lock for safety.



e/e GARRARD ZERO 100

it can be viewed by looking directly at the front of the turntable deck.


Manual or record changer operation is determined by which of two supplied spindles is inserted into the turntable. The short spindle provides single play operation; the long spindle provides the record changer operation (up to 6 records).

Three tabs provide all control functions. One tab is start-stop for automatic, meaning the Zero 100 will continuously repeat a record or shut down automatically after the record is played. The second lever is the start-stop for manual operation whereby the user places the stylus in the groove and lifts the arm clear at the end of the record. The third lever provides a highly damped cueing and pause.

The real heart of the Zero 100, however, is the articulated tone arm, which closely resembles the articulated (dual arm) windshield wiper on larger cars. (It's a simple device, and it's quite likely a Garrard engineer got the idea while driving in an England rainstorm.

The basic, counterbalanced tone arm is as straight as a ruler. A pair of ceramic magnets are located at the rear pivot mount: one on the pivot and one on the arm (the pivot is plastic to avoid magnetic effects). These magnets provide the anti-skating force, with the degree of force determined

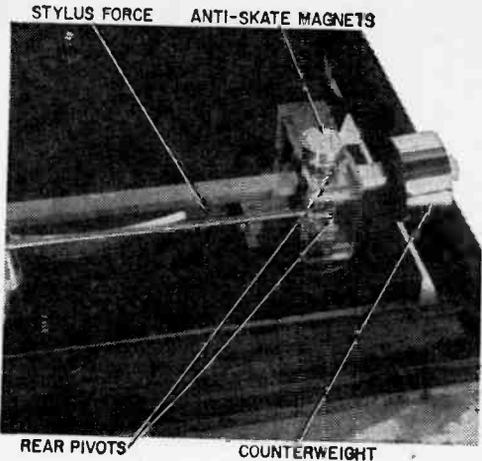Pivot action responsible for near perfect tracking is illustrated below. Photo, left, shows start of record. Articulating arm pivots cartridge to keep pick-up stylus tangent to record groove. Note change in articulating arm near end of record.



Pivots and magnets, main features of Zero 100, provide both near perfect tracking and common-sense approach to anti-skating.

by a calibrated shield that slides between the magnets. (All in all a far superior system to spring-loaded anti-skating adjustments.) The stylus force is determined by a weight that slides under the tone arm, with engraved calibrations from 0 to 3 grams in $\frac{1}{4}$ gram segment.

Maintaining a Tangent. At the business end of the tone arm the pickup shell is installed on a pivot so it is free to move. From the outer edge of the shell, running back to the plastic rear pivot, is the articulation control arm. As the main tone arm moves towards the spindle, the control arm rotates

Continued on Page 102





all *NEW* BASIC COURSE in ELECTRICITY & ELECTRONICS *

PART 2 UNDERSTANDING POWER SUPPLIES

What You Will Learn. In this part you will learn what filter networks are, and how they work in power supply circuits. There are various kinds of filters made up of passive electronic components, and you will learn how to utilize these components to match the filtering requirements of the circuit. You will see how regulated power supplies work. These power supplies utilize active electronic components to perform the filtering function; you will learn how to match the correct regulated power supply circuit configuration to the electronic load to be energized. (Continued on page 94)

* This series is based on *Basic Electricity/Electronics, Vol. 2*, published by Howard W. Sams & Co., Inc.



1200 Radio Shack stores have electronic kits that build easy—yet aren't kid's stuff!




Stereo Headset. Low-cost hi-fi for nightowls—only YOU hear the music! Very light-weight, very comfortable. 6' cord & plug included.

7⁹⁵


"Custom Design" Speaker Kits.

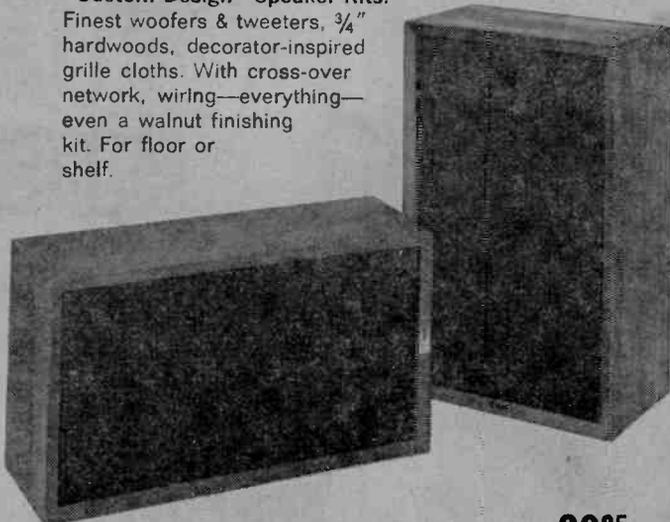Finest woofers & tweeters, 3/4" hardwoods, decorator-inspired grille cloths. With cross-over network, wiring—everything—even a walnut finishing kit. For floor or shelf.



8" Two-Way System, 45-18,000 Hz **39⁹⁵**

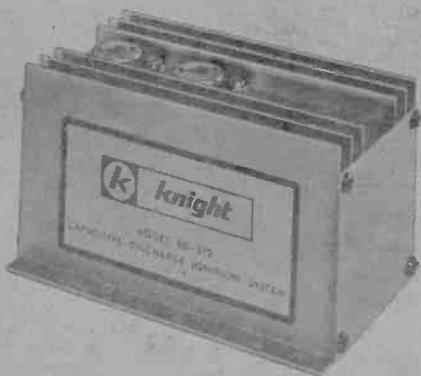10" Three-Way System, 40-18,000 Hz **49⁹⁵**



Capacitive-Discharge Auto Ignition System. Just like the '72 factory-option systems costing twice as much or more! Improves gas mileage, plug life. Assembles in one evening, installs in 10 minutes. No rewiring needed.

29⁹⁵




Two-Way Telephone

Amplifier. For family or business calls. Frees hands for writing or working while you phone. Everyone in the room can talk 'n listen! Earphone included, aids hard-of-hearing. Separate speaker, earphone. Battery operated—no warm-up needed!

12⁹⁵

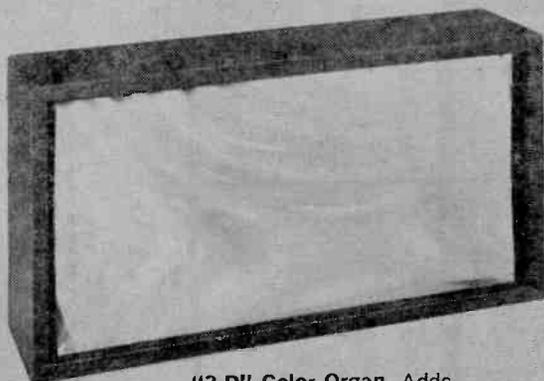\$7.95 to \$49.95. Cheap! And just great! No wonder our kits are America's favorites!



"3-D" Color Organ. Adds ever-changing musical lights in vivid reds, blues, greens to any hi-fi system. Sliding color controls, walnut-grain vinyl cabinet. Guaranteed to brighten-up any party!

29⁹⁵



"Globe Patrol" Radio. Tune in the world with 3 bands of fascinating shortwave—plus AMI Fun-'n-easy to assemble. Complete with speaker, earphone, manual. Battery-powered—use it anywhere!

19⁹⁵



Metal Locator. Strike it rich! Discover buried treasure. Find lost jewelry, coins, relics—anything metallic. Locates pipes in walls or underground, too. Includes expandable shaft (to 36"), volume & pitch controls, stethoscope earphones. Happy hunting!

19⁹⁵

Adjustable Strobe Light. "Freezes" the action for stop-motion effects. Create stunning displays at parties & get-togethers. 100's of hobby & mechanical uses, too!



19⁹⁵



Check the Yellow Pages for our store near you! Or we'll ship postpaid—add your state, local taxes; address below.

Ask for FREE Catalog!

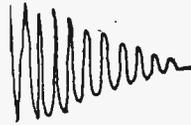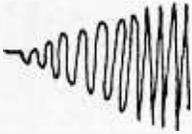2725 W. 7th Street, Fort Worth, Texas 76107



FILTERS


The filter is the section of a power supply that smooths the pulsating DC to make it almost pure DC. The three filter circuit types most commonly used are shown below. As you see, filters are simply circuits made up of resistors, capacitors, and inductors in various combinations. The operation of filters depends on the ways that L, C, and R, affect changing voltages and currents.

Q1. What are the three types of filters most commonly used?

Your Answers Should Be:

A1. The three types of filters most commonly used are the: 1. capacitive filter, 2. L-section filter, and 3. π (pi-section filter).

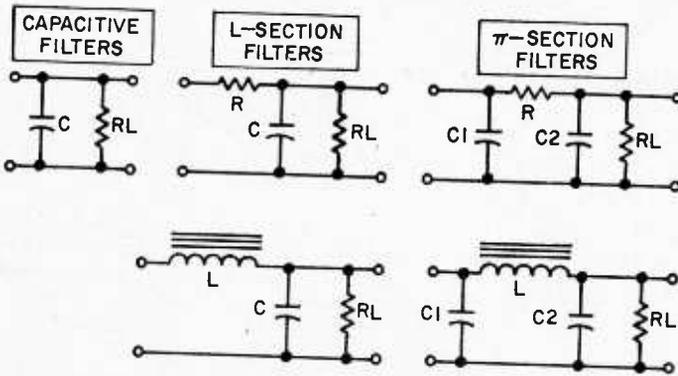
FILTER CIRCUIT COMPONENTS AND SCHEMATICS OF EACH FILTER TYPE



The Capacitive Filter

Basically, the capacitive filter is simply a capacitor connected in parallel with the load resistance. As the pulsating DC voltage from a half-wave or full-wave rectifier is applied across the capacitor, it charges to the peak applied voltage. If there were no load resistance connected across the output, the capacitor would remain charged to the peak voltage.

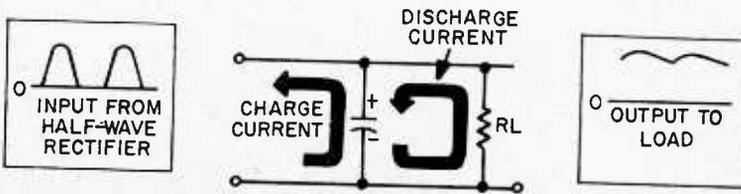SIZE OF CAPACITOR ACROSS LOAD DETERMINES RIPPLE VOLTAGE




In practice, there is always a load resistance connected across the capacitor. Between peaks, the capacitor discharges through the load resistance, and the voltage gradually decreases. The amount the voltage decreases before the capacitor is charged again by a peak in the pulsating DC is called **ripple voltage**.

The amount of capacitor discharge between voltage peaks is controlled by the RC time constant of the filter capacitor and the load resistance. If the load resistance is large and the capacitance is large, the ripple voltage is small; the pulsating DC has been smoothed out until it is almost a pure, constant DC voltage.

Variations in the output voltage are not desirable because they affect the operation of vacuum-tube or transistor circuits receiving the DC. The increased ripple voltage caused by reduced load resistance is one undesirable feature of the capacitive filter.

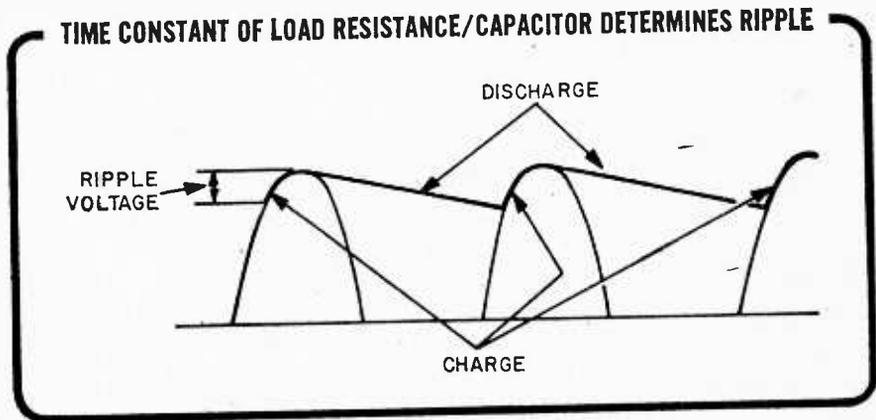A second undesirable feature of a capacitive filter is the large charging current. This excessive current flows into the capacitor to charge it when the power supply is first turned on. This initial current is often called a **surge current**. Over a



period of time, surge currents can cause injury to fuses and rectifiers, resulting in eventual burnout. Each surge current can cause part of a fuse to melt slightly, for example, until it finally burns out. The same thing can happen to the rectifier. A small surge of current flows through the rectifier during each cycle to recharge the partially discharged capacitor. Under certain conditions these charging surges can become large enough to damage a diode. The remaining two types of filters have components to reduce the effect of ripple-voltage variations and surge currents.

- Q2. What will happen to the RC time constant of the capacitor and load resistance if the load resistance is decreased?
- Q3. If the load resistance is decreased, the filter capacitor will discharge (more, less) rapidly.
- Q4. What will happen to the amount of ripple voltage if the load resistance is decreased?
- Q5. The large current that flows for a short time to charge the capacitor is called a(n)
- Q6. If a load resistance is not connected across the filter capacitor, what will happen to the output voltage?

Your Answers Should Be:


- A2. If R_L is decreased, the RC time constant will be shorter.
- A3. If the load resistance is decreased, the filter capacitor will discharge more rapidly.
- A4. The amount of the ripple voltage increases as the load resistance of a capacitive filter is decreased.
- A5. The large current that flows for a short time to charge the capacitor is called a **surge current**.
- A6. If a load resistance is not connected across the filter capacitor, the capacitor will charge to the peak value of the filter input voltage and the output voltage will remain at this value.



L-Section Filters

An L-section filter reduces surge currents by using a current-limiting resistor or inductor. This limiting resistor or inductor is connected in series with the capacitor. A limiting resistor controls surge currents by introducing an RC time constant to slow the charging of the capacitor.

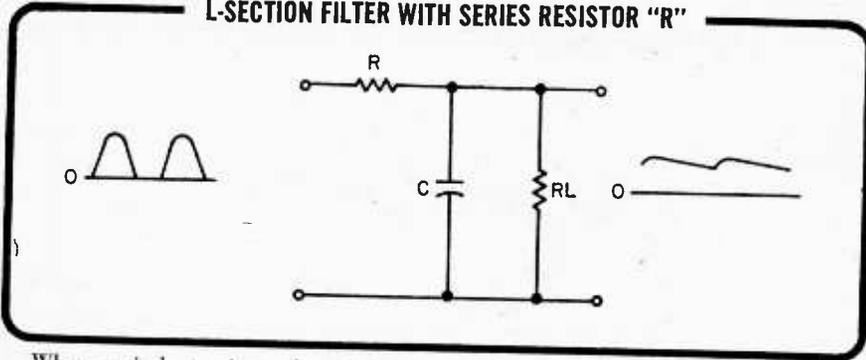L-SECTION FILTER WITH SERIES RESISTOR "R"




When an inductor is used as the series element, the surge currents are reduced in a different manner. The inductor opposes a change in current by creating a counter emf. As a result, the surge current is greatly reduced and the capacitor charges more slowly.

An inductor used in an L-section filter also adds to the filtering action of the capacitor. The inductor reacts to changes in current caused by the ripple voltage the same way it reacts to the surge current. The counter emf tends to cancel out the effects of the ripple voltage.

The operation of the L-section filter can also be explained in terms of reactance. In a simple capacitive filter, and in an L-section filter with a limiting resistor, the filtering action is the result only of the reactance of the capacitor (X_c). The capacitor presents a low reactance to AC and a very high reactance to DC. The AC part of the input is therefore by passed through the capacitor, but the DC part goes directly to the load.

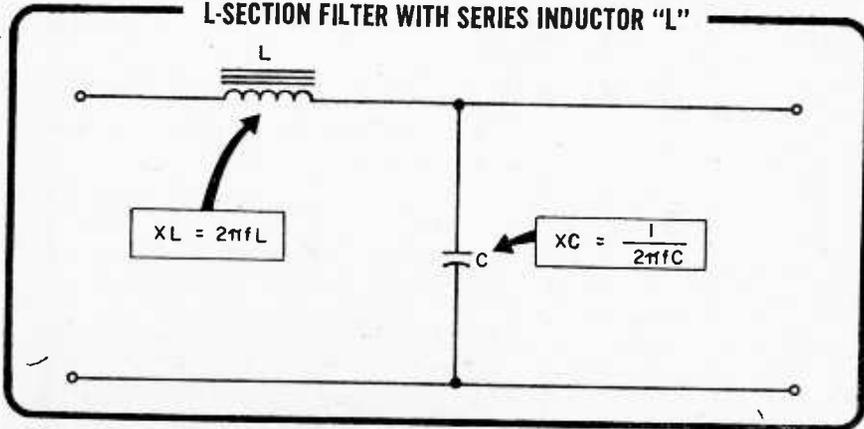L-SECTION FILTER WITH SERIES INDUCTOR "L"



To understand the L-section filter with an inductor, the reactance of the inductor must also be considered. The reactance is high for AC, but it is nonexistent for DC. The inductor presents a high reactance to the AC current produced

by the ripple voltage. The inductor therefore tends to block this current. It presents zero reactance to the DC and allows it to pass readily. The AC that is not blocked by the inductor is mostly bypassed by the capacitor.

- Q7. In an L-section filter, AC ripple can be blocked by a(n) ---

- Q8. In an L-section filter, AC ripple can be bypassed by a(n) --


- Q9. An L-section filter with a limiting resistor is (more, less) effective than one with an inductor.
- Q10. An inductor has a ----- reactance for AC than for DC.

Your Answers Should Be:

- A7. In an L-section filter, AC ripple voltages can be blocked by an inductor.
- A8. In an L-section filter, AC ripple voltages can be bypassed by a capacitor.
- A9. An L-section filter with a limiting resistor is less effective than one with an inductor.
- A10. An inductor has higher reactance for AC than for DC.

Pi-Section Filters

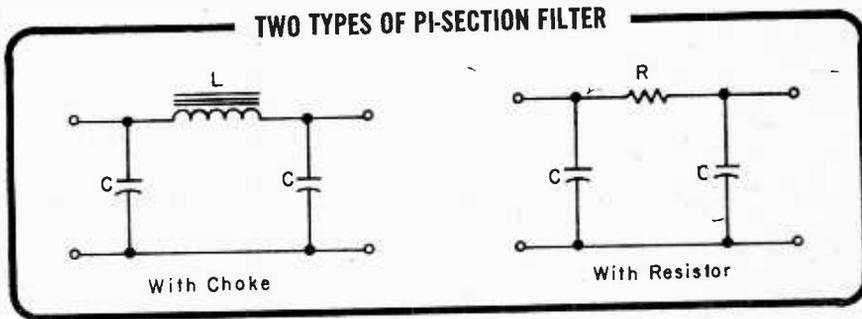A pi-section filter has three elements—a shunt input capacitor, a series choke (inductor), and a shunt output capacitor. As the input voltage reaches the first capacitor, the capacitor bypasses most of the AC ripple current to ground. This presents a smoother waveshape to the choke. The choke presents a high inductive reactance to the AC ripple current and tends to block it. To put it another way,





the choke opposes a change in current, and so it acts to smooth the current passing through it. Finally, the second capacitor is designed to bypass to ground any remaining AC components. The result output is a smooth DC voltage.


To save money, the choke is sometimes replaced with a resistor. This results in less smoothing action. A pi-section filter using a resistor depends for some of its effectiveness on the long time constant of the series resistor and the output capacitor. If this time constant is much longer than the period of the AC ripple, the output capacitor will charge and discharge very little during any one pulse of the ripple voltage. The waveshape will then be smoothed out. However, the resistor also consumes power. This is an important consideration in a power-supply circuit.

REGULATED POWER SUPPLIES

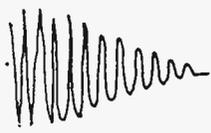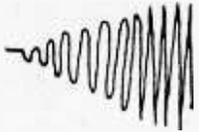Regulated power supplies are those that keep the voltage (or current) supplied to the load constant, even if the powersource voltage fluctuates or the load changes.



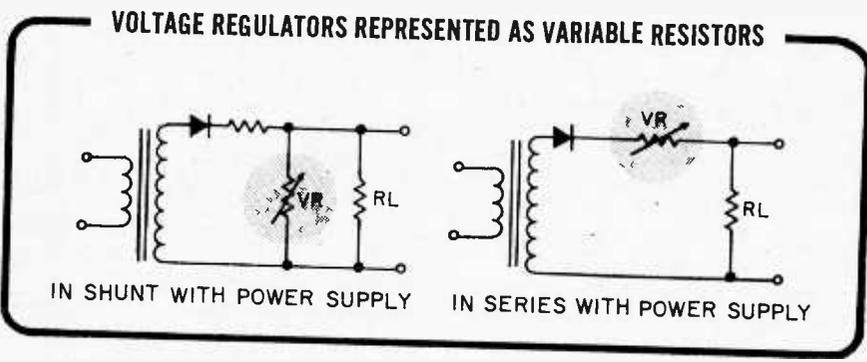Basically, the voltage-regulator part of a regulated power supply is a variable resistance that automatically changes as the output voltage changes. (For simplicity, no filter is shown in the figure.)



A shunt voltage regular combines with the resistance of the power supply itself, or with an additional resistor, to form a voltage divider. As the shunt resistance increases, more voltage appears across it as an output to the load. As the shunt resistance decreases, less voltage appears across it.

The series voltage regulator forms a voltage divider in series with the load resistance. As the series resistance increases, less voltage appears across the load resistance. As the series resistance decreases, more voltage appears across the load.

- Q11. What are the three elements of a pi-section filter?
- Q12. A pi-section filter with a resistor gives (better, poorer) filtering action than one with a choke.
- Q13. A voltage regulator may be compared to a resistor.

Your Answers Should Be:

A11. The three elements of a pi-section filter are a shunt input capacitor, a series choke or resistor, and a shunt output capacitor.


A12. A pi-section filter with a resistor gives poorer filtering action than one with a choke.

A13. A voltage regulator may be compared to a variable resistor.

The resistance of a shunt voltage regulator increases when the output voltage decreases. It decreases when the output voltage increases. Thus, it automatically returns the output voltage to normal. Similarly, the resistance of a series voltage regulator increases as the output voltage increases and decreases as the output voltage decreases.


There are several ways of achieving resistance that varies with output voltage. One of these is the gaseous voltage-regulator (VR) tube. This is a diode filled with a current-conducting gas. As the voltage applied across this tube increases, the gas becomes more ionized, and the resistance of the tube decreases. This type of tube can be used as a shunt voltage regulator.

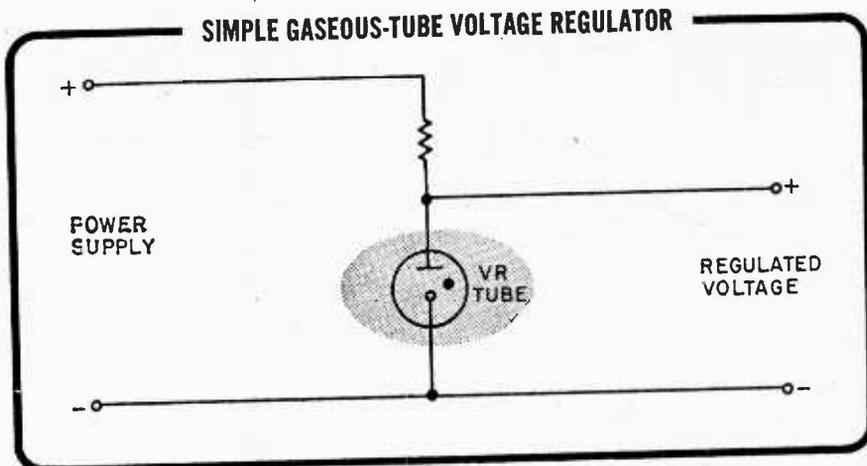The limiting resistor in series with the VR tube is selected to limit the current



through the tube to a safe value. Gaseous voltage regulators keep the output voltage constant to within about 1%. They come in a number of specific voltage ratings. To change the constant output voltage, it is necessary to change the tube. To obtain higher voltage ratings, VR tubes can be connected in series so that only part of the output voltage appears across each one.

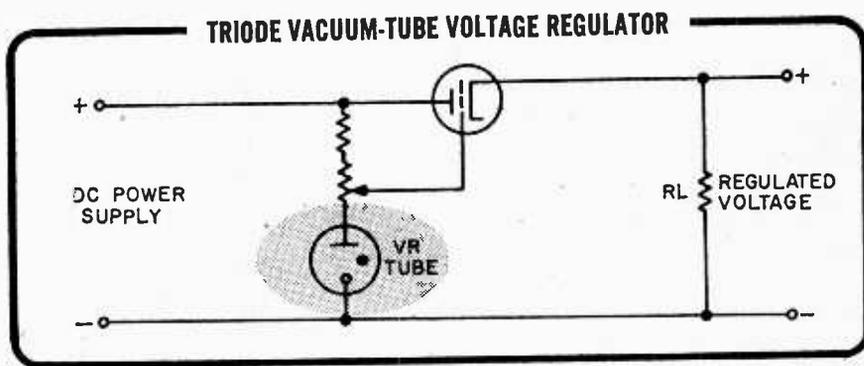The regulated voltage from a VR-tube regulator is fixed in value. Vacuum tubes are often used where it is desirable to vary the value of a regulated voltage.





A vacuum-tube circuit can be used as a series voltage regulator. The current passing through the tube from cathode to plate depends on the grid bias. Another way to say this is that the resistance of the tube depends on the grid bias. Therefore, by varying the voltage on the grid, the tube resistance can be changed as necessary.

A source for the grid bias is needed. This may be a battery or it can be a VR regulator connected to the power source. A potentiometer in the grid circuit makes it possible to adjust the bias.

If the voltage of the power source rises, the voltage at the cathode of the triode also increases. This causes an increase in the negative grid bias and reduces the current through the tube, effectively increasing the plate resistance. The output voltage is thus reduced. If the power source voltage drops, the opposite action takes place. This circuit will also compensate for changes in load resistance. A transistor instead of a tube can be used in a similar circuit.

Q14. The resistance of a shunt voltage regulator decreases as the output voltage

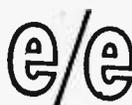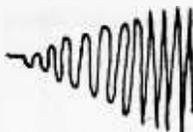Q15. The resistance of a series voltage regulator as the output voltage decreases.



Your Answers Should Be:

- A14. The resistance of a shunt voltage regulator decreases as the output voltage increases.
- A15. The resistance of a series voltage regulator decreases as the output voltage decreases.

WHAT YOU HAVE LEARNED

1. The filter smooths out the pulsating DC and provides almost pure DC.
2. Three of the most commonly used filters are capacitive, L-section, and pi-section.
3. The AC component of the filtered DC is called ripple voltage.
4. Voltage regulators are used to provide fairly constant DC.
5. Voltage regulators make adjustments in the power-supply output voltage by varying the resistance of vacuum tubes and/or transistors.
6. Voltage regulators are connected in series or in parallel with the load resistance.
7. Gas tubes and triodes are two common devices used to provide a variable resistance in regulator circuits.

NEXT ISSUE: Part 2—Understanding the Amplifier

This series is based on material appearing in Vol. 3 of the 5-volume set, BASIC ELECTRICITY/ELECTRONICS, published by Howard W. Sams & Co., Inc. @ \$19.95. For information on the complete set, write the publisher at 4300 West 62nd St., Indianapolis, Ind. 46268.

All About Crystals

Continued from Page 84

frequency adjustment capability may be obtained by connecting a 3-30 pF trimmer capacitor in parallel with the crystal.

Crystal oscillators may, of course, be built with transistors, too. Two typical circuits are shown in Fig. 10. Feedback mechanisms differ somewhat because of the basic differences between tubes and transistors. In general, transistorized oscillators are more stable.

As a Clock. To use a crystal as the timing element of a clock, an oscillator identical to those shown in Fig. 9 and 10 is the starting point. Crystal frequency is chosen at a low, easily-checked value such as 100 kHz. This frequency is then divided and

redivided by synchronized multivibrators to produce one cycle-per-second pulses. These may then be counted by computer counting circuits.

In addition to being used as oscillators and timing elements, crystals find wide application in filters. Fig. 11 shows some typical crystal-filter circuits. While all circuits shown use vacuum-tubes, transistors may be substituted without modification of the filter circuits themselves if the impedances are right.

The single-crystal filter circuit shown in Fig. 11A provides spectacularly narrow reception. When the notch control is set to precisely balance out the crystal stray capacitance, the resonance curve of the filter is almost perfectly symmetrical. When the notch control is offset to one side or the other, a notch of almost infinite rejection appears in the curve (the *pole*). The width

control varies effective Q of the filter.

More popular for general usage today is the band-pass filter, shown as Figs. 11B and 11C. These filters pass a band of frequencies without excessive loss and reject all frequencies outside this band. Both circuits make use of matched crystals (X1 and X2)—the *pole* of one must match the *zero* of the other for proper results. When this condition is met, the reactances of the two crystals cancel over the passband. The passband is roughly equal to the *pole-zero* spacing.

While the two circuits shown are virtually identical in operation, the transformer-coupled circuit of Fig. 11C is easiest for home construction. The only critical com-

ponent is the transformer. It should be tightly coupled, with both halves of the secondary absolutely balanced. This is done by winding a trifilar layer of wire (wind three wires at the same time); the center wire becomes the primary winding and the remaining two wires become the secondary. The left end of one secondary half connects to the right end of the other, and this junction forms the center tap. The remaining two ends connect to the crystals. If you have sufficient patience to wind on it, a toroid form is recommended. The only absolutely critical requirement of the transformer, however, is that it have no resonant frequencies anywhere near the operating region. ■

Kathi's CB Carousel

Continued from Page 86

monitor crystal), its performance is right up there with the best. The main receiver sensitivity measured 0.5 μ V for a 10 dB S + N/N—beating Lafayette's own specs. Selectivity was a needle sharp 52 dB, with better than 60 dB image rejection. The AGC action

scrunched a 2 to 50,000 μ V signal range down to an ear pleasing 8 dB: In plain terms, if the volume is cranked wide open, a signal coming on the channel from the station down the block won't ruin your hearing.

Not a "fad" like last year's Hot Pants, the S-meter is really "hot", reading S9 with only 16 μ V at the antenna input. Each S-unit in the S6 to S9 range represents a change in signal strength of 6 dB. Below S6, readings are in "relative signal strength".

The monitor receiver's sensitivity measured 3 μ V with 28 dB selectivity. Sensitivity is generally kept lower than that of a normal receiver so you hear signals within the *working* range of your transmitter. (The mobile will generally not receive your signal if you can barely hear him, so there's no real reason to transmit if you can't be heard.)

The transmitter delivered 3 watts output to a dummy load. Microphone sensitivity for 85% modulation was -30 dB, a little more sensitive than average, but great for us soft-spoken gals since it allows the Telsat 924's speech compressor (range boost) to put a lot of *talk power* on the signal. There is 100% modulation limiting so you don't have to worry about overmodulation even if you're a shouter.

My View. From any angle, Lafayette Radio's Telsat 924 shapes up as a top performer both for routine CB operations, and, most especially, for you Channel Niner's. For more information circle No. 46 on Reader Service Coupon on page 17. Tell 'em Kathi told you about it. ■

U.S. POSTAL SERVICE STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION (Act of August 12, 1946, Section 3685, Title 39, United States Code)		SEE INSTRUCTIONS ON PAGE 2 (REVERSE)
1. TYPE OF PUBLICATION Electronic Electronics Including Science & Electronics		2. DATE OF FILING Oct. 1, 1971
3. FREQUENCY OF ISSUE Bi-monthly		
4. LOCATION OF HEADQUARTERS OFFICE OF PUBLICATION (Street, city, county, state, ZIP code) (Not printed)		
229 Park Avenue South New York, N.Y. 10003		
5. LOCATION OF THE HEADQUARTERS OF THE PUBLISHER (Not printed)		
229 Park Avenue South New York, N.Y. 10003		
6. NAMES AND ADDRESSES OF PUBLISHER, EDITOR, AND MANAGING EDITOR		
PUBLISHER (Name and address) Julia Davis 229 Park Avenue South New York, N.Y. 10003		
EDITOR (Name and address) Julian Sienkiewicz 229 Park Avenue South New York, N.Y. 10003		
7. OWNERS (Give name of corporation, partnership, firm, or individual; name and address of each owner; if owned by a partnership or other unincorporated firm, give name and address, as well as that of each individual owner; if owned by an individual, give name and address)		
NAME ADDRESS Science & Mechanics Publ. Co. 229 Park Avenue South New York, N.Y. 10003 Davis Publications Inc. 229 Park Avenue South New York, N.Y. 10003 Julia Davis 229 Park Avenue South New York, N.Y. 10003 Julian Sienkiewicz 229 Park Avenue South New York, N.Y. 10003		
8. BOND OR OTHER SECURITY (If required by the Act, give name and address of the surety company, the amount of the bond, and the date of issue)		
NAME ADDRESS		
TOTAL AMOUNT OF BONDS, MORTGAGES, AND OTHER SECURITIES (If there are none, so state)		
NAME ADDRESS		
9. FOR OPTIONAL COMPLETION BY PUBLISHERS MAILING AT THE REGULAR RATES (Section 136.121, Postal Service Manual) 39 U.S.C. 3686 provides for reduced postage for certain publications. This section shall not apply to any publication unless the publisher has filed with the Postal Service a written request for permission to mail at the reduced rate. In accordance with the provisions of this section, I hereby request permission to mail the publications named in Item 1 at the reduced postage rates authorized by 39 U.S.C. 3686. Signature of Publisher or Business Manager		
10. FOR COMPLETION BY NONPROFIT ORGANIZATIONS AUTHORIZED TO MAIL AT SPECIAL RATES (Section 136.124, Postal Service Manual) (Check one) The purpose, function, and nonprofit status of this organization and the exempt status for Federal income tax purposes: <input type="checkbox"/> Have not changed during preceding 12 months <input type="checkbox"/> Have changed during preceding 12 months (If changed, publisher must submit explanation of change with this statement.)		
11. EXTENT AND NATURE OF CIRCULATION		AVERAGE NO. COPIES EACH ISSUE DURING PRECEDING 12 MONTHS
A. TOTAL NO. COPIES PRINTED (See Item 5)		210 750
B. PAID CIRCULATION 1. SALES THROUGH DEALERS AND CARRIERS, STREET VENDORS, AND COUNTER SALES		200 200
2. MAIL SUBSCRIPTIONS		28 000
C. TOTAL PAID CIRCULATION		83 937
D. FREE DISTRIBUTION BY MAIL, CARRIER OR OTHER MEANS TO NEWSSTANDS, CARRIER ROUTES, AND OTHER POINTS OF DISTRIBUTION		116 104
E. COPIES DISTRIBUTED TO NEWS AGENTS, BUT NOT SOLD		7 228
F. COPIES LEFT OVER, UNACCOUNTED, BROKEN AFTER PRINTING		84 368
G. TOTAL DISTRIBUTION (Sum of C and E)		209 700
H. OFFICE USE, LEFT-OVER, UNACCOUNTED, BROKEN AFTER PRINTING		1 050
I. TOTAL (Sum of G and H)		210 750
ACTUAL NUMBER OF COPIES OF SINGLE ISSUES PUBLISHED NEAREST TO FILING DATE		200 200
I certify that the statements made by me above are correct and complete.		

Garrard Zero 100

Continued from Page 88

the shell on its pivot, thereby maintaining the shell at right angles to the record groove.

A lever under the top of the pickup shell adjusts the pickup's vertical tracking angle to "M" (manual-15°) or "A" (automatic-15° on the third record in the stack).

Performance is outstanding. It is truly amazing, but except for the Hi-Fi Stereo Buyers' Guide, not one single major "hi-fi" publication apparently bothered to listen to a record on the Zero 100. Their instrument measurements, as ours, show the Zero 100 to be the equal of any excellent turntable in its price range, with precisely regulated speeds over a wide voltage range, a zero-

error stylus force gauge, and a combined wow and flutter of 0.12%.

In actual listening tests the sound from the Zero 100 is truly outstanding. With new, good quality pressings there is essentially no difference in sound quality between the Zero 100 and any other high quality turntable. But place an older record on the platter, or a favorite played over and over, and the difference in sound quality is immediately apparent. From about the 7 in. diameter to run out, the Zero 100 delivers considerably less distortion and greater definition than with the same pickup mounted in a standard arm. The improvement in sound quality is notably impressive.

The Zero 100 is priced at \$189.50. A mounting board, wood and plastic bases, and a hinged dust cover are available. For additional information, circle No. 51 on page 17. ■

CB Coffee Break

Continued from Page 58

signal from this antenna is radiated equally in all directions (omnidirectional); also, a good part of the signal is squirted up towards the sky where it is of no use to anyone. And to make matters worse, the strongest part of the signal is squirted upwards at a slight angle. In short, the radiation pattern from a ground plane looks like a doughnut that is sagging in the middle.

Since the ground plane antenna is the "common" CB antenna, it is used as the basic reference antenna, the one to which all others are compared, and we say it has "unity" gain, or a gain of "1"—in effect, *no gain*.

Now along comes *Antenna Specialists* with their M-117 Magnum antenna, *New-Tronics* with their 27-JR and their *Hustler* 27-STR and *Lafayette* with their Range-Boost II; they add a few design gimmicks to the antenna and wind up taking some of that power being squirted up, up and away and beam it down at the ground where it's really needed. In actual practice these antennas put a signal *on the ground* that is 4 dB higher than that of a ground plane antenna. The effect at the receiving station is as if you still were using a ground plane antenna but had increased the transmitter's input power to approximately 12 watts.


Get on the Beam. But 12 watts is still a long way from 100 watts, so to get the effective power up to channel-blaster level we do a little bit more to modify the antenna's radiation pattern. Assume if you will that the sta-

tion you desire to work lies to the north of your antenna; therefore, power radiated in any direction other than north is totally wasted. If we could only take some of that power heading south, east and west and push it north the receiving station would be crushed under the RF signal. Well that's just what we can do. A *directional beam*, that is, an antenna with two or more vertical radiators can take the RF going to waste and beam it forward. Use a three element beam and the signal going forward can be 8 dB greater than that of a ground plane; that's just like running 31 watts into the final. But there's still some RF being radiated to the back and sides, so let's add another element (4 element beam) to reflect some more energy forward and the signal at the receiving station is almost 9.5 dB higher than that of a ground plane antenna: the equal of running a 44 watt rig into a ground plane antenna.

Still not satisfied, okay, let's try a 5 element *Cush-Craft* antenna with a 10.5 dB forward gain; that's like boosting your transmitter input power to 56 watts.

Well, we're coming close to 100 watts; we need less than 3 dB more antenna gain to hit the equal of a 100 watt rig. Simple: Just stack two 5 element beams for a total of 13.5 dB forward gain; the equal of a 112 watt rig . . . we have done better than 100 watts with an antenna available from local CB distributors.

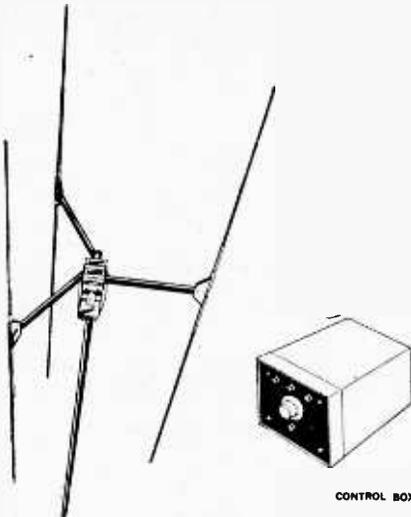Of course, many manufacturers other than *Cush-Craft* make sky hooks that put out rock-crushing signals. Just to name a few of the biggies, there's *Avanti* with their quad type directional beams that can transmit either horizontal or vertical polarization, *Antenna Specialists* also has a quad type rock crusher. *Gotham* also grinds out several high gain sky



Operate omni or directional with Antenna Specialists Super Scanner. Non-mechanical signal rotation. Circle No. 47 on Page 17.

hooks, as does *New-Tronics*, *Hy-Gain* and *Lafayette Radio*.

Fact is, whether your wallet is pinched by an XYL who can't understand why you must drown out every other signal on the band, or you're the last of the big time spenders, there's a super-antenna that will fit your budget.

And while you're sitting back contemplating just how far a 100 watts of effective input power will carry your voice, don't overlook the fact that a directional antenna delivers the same advantage to receiving as it does for transmitting. If the antenna delivers 10 dB forward gain for transmitting it delivers 10 dB forward gain for receiving. In practical terms, it means that a signal which was coming in just over the noise level at $2\mu\text{V}$ when using a ground plane antenna will now come in at $6.32\mu\text{V}$.


Don't Look Behind You! Another big receiving plus is front-to-back ratio. Remember we said that directional beams concentrate most of the power forward; taking the back and side power and adding it to the forward power. Well, the same thing applies to receiving: If the antenna concentrates all its sensitivity forward it does so by reducing the back and side sensitivity, and it is not unusual to find a directional antenna is 25 dB less sensitive to the rear than the front . . . called 25 dB front-to-back ratio. Again in practical terms, interfering stations on the same channel in the opposite direction from the desired station would be attenuated 25 dB; you can't accomplish this type of unwanted signal rejection any other way than with a directional beam. And if you want rock-bottom rejection, there are antennas with a 38 dB front-to-back ratio such as *Avanti's* "Moonraker", which can "null out" a 5 watt CB station to the equal of 800 microwatts (0.0008 watts); now no 800 μW

station is going to interfere with anybody!

Of course, in this world you get nothing for nothing, so you can't expect to boost your rig's effective power input to 100 watts, or wind up with a super-nulling receiver, without paying something in return. Your payment is *directivity*, meaning the antenna can only deliver phantasmagoric results in a specific direction. In order to cover all points, 360° , you must provide some means to rotate the antenna. While you can put a crank on the bottom of the mast which you can reach by sticking your arm out the window (don't laugh, it is done), an easier way is to use an antenna rotator such as those made by *Cornel Dubilier (CDE)* and *Alliance*. You can either get a model that rotates the antenna as long as you hold down a switch, or one that allows you to preset any desired direction, with the rotator automatically stopping when the antenna swings around to your present bearing.

Okay, now you've got no excuse why your station isn't top gun on the band. And, if you want more info 'from the horse's mouth, then turn to the pages in this issue devoted to our full scale CB antenna story written by Len Buckwalter. He knows his Cs and Bs, and packs the article with facts every CBER should know.

Attention Clubs. In the very near future I plan to run a listing of active CB clubs throughout the nation in this column. My purpose is simple to understand. With a little publicity, you'll pick up new members that every club needs to grow. You see, in my racket I know it pays to advertise. In fact, in order for me to publicize your club and its activities, you have got to keep me informed. Tell me about your club's activities. Photos are always welcome. So get those cards and letters moving my way today! And remember, we screen our mail from Wala Wala. —10-7

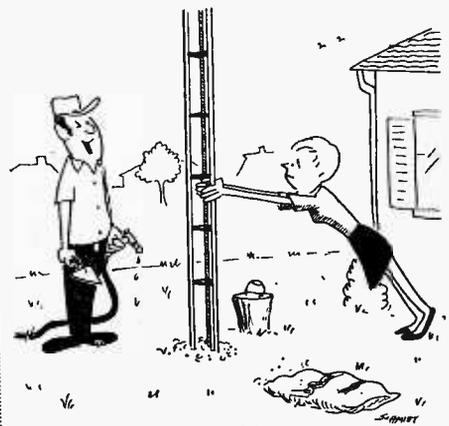

"That's great, Dear, just hold 'er there till the cement dries."

Ask Hank, He Knows!

Continued from page 27

urers name, only numbers. Is there any manual available whereby one could determine characteristics and ratings of these components?

—E. C., Thunder Bay, Ont.

There was a time when old transformers were worth salvage. Not so today. Power supply requirements for solid-state projects are varied and critical compared to the old brute-force, vacuum-tube days. I haven't used a salvaged transformer this past year. Besides, many units are on the verge of failure. Why build around a part that may not work?

Dead Asleep

Do you know of any place where I could send away for a catalog or a list of all the AM radio stations in the country? Thank You.

—D. F., Scotia NY

Man, where have you been. Most cats know about White's Radio Log which is available twice yearly in COMMUNICATIONS WORLD. You can get your copy by sending \$1.25 to this magazine.

Tough on Ham Bands

I have a 9 band Zenith Royal 3001 radio. It's a fine radio! I got a verie card (QSL) from R.S.A. (Radio South Africa) South Africa as well as HCJB in South America. My trouble is on the amateur band. I get dozens of Hams, but they overlap and are very hard to understand. Do you think the Zenith is hooked up wrong?

—C.T.H., Kenora, Ont.

Zenith makes a great little radio, but for serious shortwave listening, it's time for a switch. I believe you are ready for a \$150-200 receiver. Forget about those brand name jobs in department stores. Instead, check a few mail-order parts catalogs for a wired unit or Heath for a kit.

Adventure!

Please tell me if it is possible to convert an old fashioned phonograph which only played 78 speed records, into a turntable which plays the three speeds, 78, 45 and 33 $\frac{1}{3}$. I am not necessarily interested in cutting corners, but more or less adventurous.

—I.K., Richmond VA

It's all in the capstan drive. And the chances are that it's impossible to make a three-speed unit unless you are a machinist. The capstan (usually the motor shaft) will drive the turntable slower if its diameter is reduced. What I once did in the early days of the 45 disc was to put a file to the capstan. I constantly checked the speed until I counted 45 revs in one minute. Look at a standard 3-speed machine and see

how the capstan has 3 different diameters near the shaft end. Duplicate the mechanism, if you can—good luck!

Whatta Group

I would like to know how to wire a combination of eight 8-ohm speakers to obtain 8-ohms impedance. My amplifier operates on 8-ohms impedance. All of these speakers are 8-ohms. The front and the rear are 5" small speakers (woofers) and the sides are 6 2 $\frac{1}{2}$ -in. tweeters.

—A. L., Shawinigan, Que.

Here we go again mixing apples with pears. The best you can hope for is fruit salad! If all the speakers were identical, then the hookup would be impossible to get exactly 8-ohms with equal power delivered to all speakers. However, if you slip in an 8-ohm, high-voltage, non-inductive resistor in the group, then it's easy. See our diagram A.

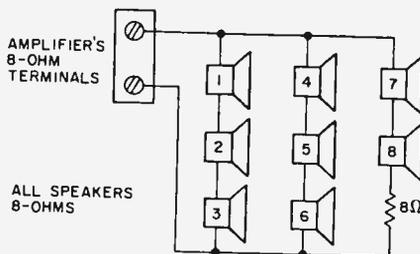


DIAGRAM A

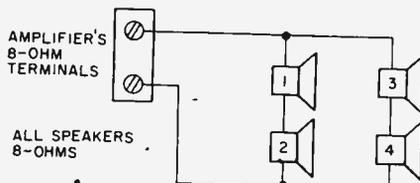


DIAGRAM B

But, two woofers and six tweeters require the use of a complex crossover network. Honestly, it sounds like your using salvage, low-cost speakers and trying for hi-fi sound—if so, you're a loser! Why not pick up four wide range, hi-fi speakers and connect them as shown in diagram B.


Cherry-Red Plates

When I replaced the 7408 tubes in my stereo amplifier, I found that I had to try a dozen tubes to find one that would work. All tubes were tested in various tube testers. No matter into which socket I placed these tubes in the set, the plates would overheat. After the tubes were in the amplifier for ten minutes or more, the plates became cherry red. Up until this time all voltages and resistances checked OK. As the plates overheated, the cathode voltages built up past the rated 24 volts. So I unplugged the set for fear of damage. This happened even if the

tubes were intermixed with the workable ones. The tubes now used work OK and all voltages and resistances are OK. I have ten new tubes whose plates overheat. Can you help me solve this problem?

—A.G., Linden, N.J.

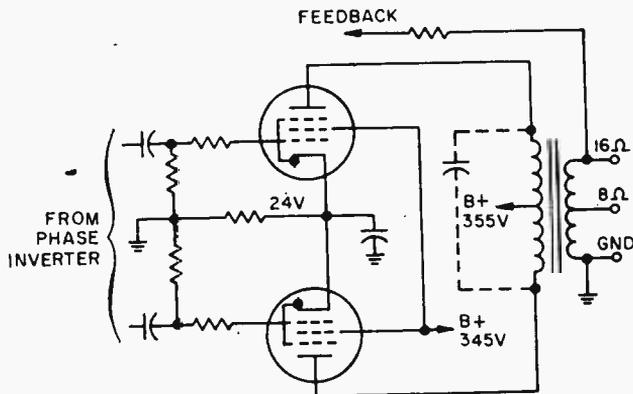Looking at the schematic you sent, it is evident that you have a well designed amplifier, except for one thing. The 7408 tubes are being operated at higher than maximum design ratings. Plate voltage should not exceed 350 volts, and



the screen should not have more than 315 volts. But according to your schematic, these voltages are 355 and 345 respectively. Under typical operating conditions, these voltages are both 250 volts, according to the RCA Receiving Tube Manual. If your line voltage is high, as we have found it to be in some parts of Jersey, the actual voltages could be considerably higher. Have the power company check the line voltage. Try a line-voltage reduction transformer to determine if excessive voltage is the problem. Your trouble could be due to oscillation. Try a capacitor across the plates, as shown in the diagram in dotted lines (0.002 to 0.01 mF). Be careful—the voltages are high. If this stops tube overheating, you may not have to leave the capacitor in. Just reduce the line voltage.

Too Young to Snoop

Can you send me a schematic diagram of a police radar detector. This is a project for school.

—L.G., Wentzville MO

A cat souped up with Jonny Walker Black Label doing 105 m.p.h. will do a good job at detecting police radar traps. Do something tough like pulling in some difficult DX or building a home fire alarm, or whatever—but leave the cops alone. But, no matter, as a rule the Editors of ELEMENTARY ELECTRONICS do not supply diagrams or plans. There are just too many readers requesting this service and, too few hours to answer the mail.

QRM in NYC

I own a Lloyds 5-band MB/AM/FM aviaional police receiver. Please tell me how I can im-

prove reception between 108 and 175 MHz. My antenna pulls in too much QRM. Can you help me?

—T.G.O., New York, N.Y.

Also living in New York, we know what you mean. In the first place, there are too many signals on the air in New York for a tunable receiver to operate without intermodulation interference. For good reception, you need a professional-grade receiver plus an array of filters, which is an expensive set-up.

Future Yard Bird

I have an 11-transistor Wards Airline transceiver Model 62-574 which runs on CB channel 11 and is a 100MW transceiver, is there a way to increase the range by increasing the watts?

—F.L., Oakland CA


Sure, you may be able to increase your range to the nearest federal prison if you fool around with the transmitter section of your rig. The Editors suggest you pick up a copy of the 1972 CB Yearbook if you are interested in more than 100 milliwatts on channel 11.

Wrong Track

I have heard that Geiger counters operate on the microwave frequencies. Is this true? I would like to know because I am interested in constructing a radio telescope. I would also like to know where a Geiger tube can be obtained?

—K.C., Somers CT

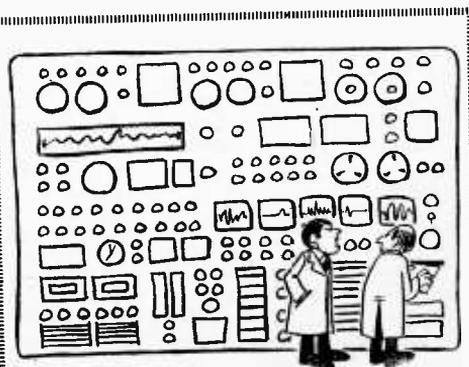Nope, it's not true. Geiger counters detect and count high velocity particles and rays passing through the Geiger tube. Check your local library for the facts. If you are seriously interested in radio telescopes, I suggest you become acquainted with them by reading books before you proceed with construction. ■



"Look here, Rockingham, solid-state LSI circuits or not, 5+5 is not 13!"

Elocktron

Continued from page 42

of "electric door openers," nearly all of which will work from 4, 12, 24 or 48 VDC. The "reverse-action" types are normally unlocked, and lock only when activated. Trine electric door openers are list-priced from \$12.75 to \$68, depending on type, metal (brass or aluminum) and finish. Trine also makes a *pusher spring*, which is a simple spring-loaded plunger that pushes the door open when the latch is released. This is often used in apartment-house front doors, because a caller may not have his hand on the doorknob at the moment the latch is released. The effect is spooky if you're not used to it, but Trine says there's a drawback. If the caller doesn't shut the door

firmly, it may not close completely because of the spring pressure against it, and so the door can then be pushed open by anybody. But if you do want a pusher spring, try your hardware store, which may also stock some of the other accessories that can be added, such as chimes, or a pushbutton for operating the Elocktron from inside the house at a distance from the door. There's even a silicon rectifier unit from Trine, at \$21.35 list, for silent operation of the opener. It's important if you want to sneak in yourself.

Magic. Once you've got the Elocktron assembled and working, you can impress friends and neighbors by making the door open as if by magic. Just don't let them see the electronic key. Hide it in your hand, or in a box or package. Bring it to the right place on the power circuit's front panel, and the door will mysteriously unlock, seemingly all by itself! ■

DX Central Reporting

Continued from page 22

the various stations on the air.

There are two publications that should help, Ralph. One is EE's sister magazine, COMMUNICATIONS WORLD, published twice a year and containing *White's Radio Log*. This includes a list of many shortwave stations currently being logged in North America.


The second is the DXer's "Bible," *World Radio TV Handbook*, published annually in Denmark and distributed here by Gilfer Associates, Inc., Box 239, Park Ridge, New Jersey 07656.

The spotlight falls this month on NASWA, the North American SW Association, an all-shortwave broadcast type club headquartered at Altoona, Pennsylvania.

NASWA's jumbo-sized monthly bulletin is filled with up-to-date shortwave data, logging tips, QSLing information and feature articles

submitted by some of America's sharpest SWBC DXers. But NASWA is more than that. Its bulletin is called "Frendx," a reference to its motto, "Unity and Friendship," and its personal approach to the hobby makes both veteran listeners and newcomers feel at home.

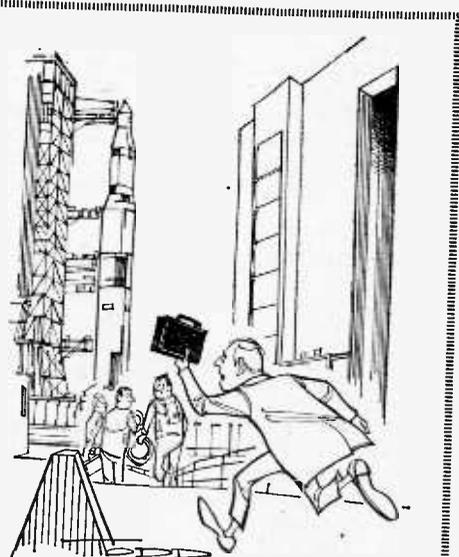If you'd like to see a sample copy of *Frendx*, or if you're ready to join now, fill in the form above and mail it directly to NASWA, not to Elementary Electronics. ■



"Captain . . . The Department of Interior wants you to take along \$24 worth of beads and trinkets, just in case . . ."

NORTH AMERICAN SHORTWAVE ASSOCIATION Box 989

Altoona, Pennsylvania 16603

I read about your club in ELEMENTARY ELECTRONICS' "DX Central Reporting."

Please send me a sample copy of your bulletin. I am closing 50 cents.

I want to join NASWA. I am enclosing \$10 for one year's membership at the first class mail rate.

Name _____

Address _____

City _____ State _____ ZIP _____

ELEMENTARY ELECTRONICS

CLASSIFIED Market Place

Classified Ads 65¢ per word, each insertion, minimum 10 words, payable in advance. To be included in the next available issue of ELEMENTARY ELECTRONICS, copy must be in our New York Office by Dec. 1st. Address orders to R. S. Wayner, Manager, Classified Advertising, ELEMENTARY ELECTRONICS, 229 Park Avenue South, New York, N. Y. 10003.

AVIATION

HOVERCRAFT D. I. Y. Plans Players No. 6 \$9.00. Express Air Rider \$2.00 plus 25¢ postage. Kits in various stages of construction from \$199.00. Complete line of supplies and most authoritative A. C. V. publications The Hover Centre of Canada, Box 656, Maple, Ontario. Distributor Enquiries invited.

AUTO PARTS & ACCESSORIES

AUTO GUARD. Protect your car from theft. New Electronic Device. Satisfaction guaranteed \$6.95. D. Wolfe, 2520 Virginia Drive 2K2, New Kensington, Penna 15068.

BUSINESS OPPORTUNITIES

I made \$40,000.00 Year by Mailorder! Help others make money! Start with \$10.00—Free Proof! Torrey, Box 318-T, Ypsilanti, Michigan 48197.

MAKE Magnetic Signs. Big profits. Details. Universal, Lenora, Kansas 67645.

1000% PROFIT Bronzing Shoes. Free Details. NBC, Box 11069-0, Kansas City, 64119.

JAPAN Hong Kong Directory. World products information. \$1.00 today. Seki Shogyo Annal, HillFard, Washington 99207.

ADDRESSERS and Malters needed. Send stamp for information. Lindbloom Products, 3636 Peterson, Chicago 60645.

1000% PROFIT!! Sell Books by Mail. Free Kit. Wallace, Box 283-D11, Gladstone, Oregon 97027.

COINS, CURRENCY & TOKENS

SELLING my barrel of Indian & Lincoln cents (1860's thru 1920's—all mints) at \$10 per pound! Maximum 10 pounds. Sample bag of 20-\$2. Mrs Penny Fisher, Box 1778-S, Encino, Calif. 91316.

DO-IT-YOURSELF

BURGLAR—Fire alarm systems and supplies. Free Catalog. Informer Mfg. 200b S. Eden Street, Baltimore, Maryland 21231.

INTEGRATED CIRCUITS KITS—Free Catalog. Frazier & Associates, 3809 Surrwood Road, Malibu, California 90265.

EDUCATION & INSTRUCTION

UNIVERSITY Degrees by mail. Via Thesis. Experience. Home Study, Norman Dept. 63, Box 3199, Pasadena, Calif. 91103.

FERROUS SULFATE

(5 GRAINS Each) I have the Amazing Superior Tonic Tablets. The pill that puts Youthful Desire into Aging Bodies. 30 Tablets \$3.00 NINA of GERMANY, 406 So. SECOND St., ALHAMBRA, CALIF. 19802.

GIFTS THAT PLEASE

FREE Gift catalog. Gift Haven, 515 East Cedar, Olathe, Kansas 66061.

Free bonus gifts. Free Novelties color catalog. Ellenbogen Specialties, 450 Seventh Avenue, New York 10001.

JANUARY-FEBRUARY, 1972

HYPNOTISM

TWO 3D Hypnotic Disks. Guaranteed. Send \$1.50. Russell Novelty, P. O. Box 377, New York, N. Y. 10004.

INVENTIONS WANTED

WE either sell your invention or pay cash bonus. Write for details. Universal Inventions, 298-3, Marion, Ohio 43302.

MISCELLANEOUS

BUY nearly anything to 90% below price. Free Catalogs. 12,000 pages. Send \$2.00 for \$20 merchandise postpaid. American@, 21 Francine, Framlingham, Massachusetts 01701.

AMAZING Magic way to Security. Influence. Prestige! How to Multiply Money-making Power! Book Guaranteed. Send \$2.00 today. Gentilucci, Dept. SM2, 6 Gonzalez, San Francisco 94132.

AIR Compressor from Auto Cigarette Lighter. \$29.95 ppd. Brochure. American National University Station, Box 8876, Reno, Nevada 85907.

GIVE the best reading in the Mechanical Field—give Science & Mechanics! \$4.00 for year's subscription. Science & Mechanics, 229 Park Avenue South, New York, New York 10003.

PRACTICAL tips for home, garden and workshop are in "1001 How-To Ideas." Send \$1.00 for your copy includes Postage. to 1001 How-To Ideas, 229 Park Avenue South, New York, N. Y. 10003.

MONEYMAKING OPPORTUNITIES

MAKE THOUSANDS OF DOLLARS. raising rabbits, cavies, Chinchillas for us. Complete information \$1.00. Keeney Brothers, New Freedom, Penna. 17349.

EASY-To-Start rubber stamp business at home in spare time. Make up to \$16.50 an hour without experience. Facts free! Write to: Roberts, Room RC-107-AP, 1512 Jarvis, Chicago, Ill. 60626.

MAKE YOUR CLASSIFIED AD PAY. Get "How To Write a Classified Ad That Pulls." Includes certificate worth \$2.00 toward a classified ad in S. & M. Send \$1.25 (includes postage) to R. S. Wayner, Science & Mechanics, 229 Park Avenue South, New York, New York 10003.

MAKE \$1.00 PER SALE selling engraved metal Social Security plates. **FREE SALES KIT.** Engravaplates, Box 10460-7503, Jacksonville, Fla. 32207.

PERSONAL

ELIMINATE Debts Without Borrowing! Particulars Free. Helper, P. O. Box 9308, No. Hollywood, California 91609.

LIFETIME Ordinations. Church charters available. Details 25¢. Life Science Church, 2207 Cardinal, Rollink Meadows, Illinois 60008.

WHAT'S YOUR I. Q.? Self-scoring test. \$2.00. J & J Wood, 254 East 204th Street, Bronx, N. Y. 10458.

There is no charge for the Zip Code. Please use it in your Classified ad.

PHOTOGRAPHY—PHOTO FINISHING & SUPPLIES

SAVE HUNDREDS OF Dollars!!! Make your own Densitometer. Free detailed instructions available. Write to: Science & Mechanics Instruments Division, Dept. EE 172, 229 Park Avenue South, New York, New York 10003.

PROFITABLE OCCUPATIONS

CHINCHILLA income guaranteed. Terms 25¢—Bulletin \$1.00. Rainbow, 11DC, Port Richey, Florida 33568.

RADIO & TELEVISION

RADIO & TV tubes 35¢. Free Catalog Cornell, 4217 West University, San Diego, California 92105.

FREE electronics catalog. Tremendous bargains. Edu-Kits, Dept. C-552-DJ, Hewlett, New York 11557.

EXCITING Listening! Police—Fire—Emergency calls on your broadcast radio. \$19.95 up. Also receivers, scanners, dual-band high/low, crystals. Saich Company, Woodboro 1, Texas 78393.

"**DISTANCE** One Tuber" Handbook-50¢. 15 Distance one tube plans-25¢. Catalog Laboratories, 745-G Cordone, Reno, Nevada 89502.

OLD RADIO PROGRAMS on tape. Catalog 25¢. Radio Days Forever. R. D. 2, Box 123 McVeytown, Pa. 17051.

TV Repair tips. James Kalousis, Inc. 1175 Magie, Union, N. J. 07083.

FREE Kit Catalog. Why does every major College, University, Technical School, Research & Development Center buy from us? Because we have the highest quality and lowest prices. Free Catalog. SWTPC, Box 32040H, San Antonio, Texas 78216.

REMAILING SERVICE

HARTFORD, Connecticut-06101, Balco, Box 306, Receiving, Forwarding. Monthly rates. Remains 25¢.

SAVANNAH Remails 20¢. monthly \$3.00. Dewilco, Box 13063, Savannah, Ga. 31406.

NEW YORK REMAILS 25¢ each-\$3.00 Monthly. Foreign Accounts Welcome. M. Cassidy, 2845 University, New York, N. Y. 10468.

LAS VEGAS Remails 25¢. Forwarding \$2.50 Month. Casino cards 12/45. Global, 558E Oakey, Las Vegas, Nevada 89105.

SALESMEN—DISTRIBUTORS

LONG Needed Invention. Need Man contact service stations. Full or part time. Huge profits. Write, Cyclo, 3816 Dahlia, Dept. 102, Denver, Colo. 80207.

SPECIAL SERVICES

214 RADIO. 112 TV Stations will sell products on commission. No sales; no pay. Complete list of stations, facts, \$2.00. Satisfaction guaranteed. MOAMI, 309 W. Morris, Indianapolis, Indiana 46225.

STAMP COLLECTING

CLOSEOUT Sale: List Samples Free Assortment \$1.00. Persil, 436 N. Y. Avenue, Brooklyn, N. Y. 11225.

Hunting for a better job?

**Here's the
license
you need
to go after
the big ones**



A Government FCC License can help you bring home up to \$10,000, \$12,000, and more a year. Read how you can prepare for the license exam at home in your spare time—with a passing grade assured or your money back.

IF YOU'RE OUT TO BAG A BETTER JOB in Electronics, you'd better have a Government FCC License. For you'll need it to track down the choicest, best-paying jobs that this booming field has to offer.

Right now there are 80,000 new openings every year for electronics specialists—jobs paying up to \$5, \$6, even \$7 an hour... \$200, \$225, \$250, a week... \$10,000, \$12,000, and up a year! You don't need a college education to make this kind of money in Electronics, or even a high school diploma.

But you *do* need knowledge, knowledge of electronics fundamentals. And there is only one nationally accepted method of measuring this knowledge... the licensing program of the FCC (Federal Communications Commission).

Why a license is important

An FCC License is a legal requirement if you want to become a Broadcast Engineer, or get into servicing any other kind of transmitting equipment—two-way mobile radios, microwave relay links, radar, etc. And even when it's not legally required, a license proves to the world that you understand the principles involved in *any* electronic device. Thus, an FCC "ticket" can open the doors to thousands of exciting, high-paying jobs in communications, radio and broadcasting, the aerospace program, industrial automation, and many other areas.

So why doesn't everyone who wants a good job in Electronics get an FCC License and start cleaning up?

The answer: it's not that simple. The government's licensing exam is tough. In fact, an average of two out of every three men who take the FCC exam fail.

There is one way, however, of being pretty certain that you will pass the FCC exam. And that is to take one of the FCC home study courses offered by Cleveland Institute of Electronics.

CIE courses are so effective that better than 9 out of 10 CIE graduates who take the exam pass it. That's why we can back our courses with this iron-clad Warranty: Upon completing one of our FCC courses, you must be able to pass the FCC exam and get your license—or you'll get your money back!

They got their licenses and went on to better jobs

The value of CIE training has been demonstrated time and again by the achievements of our thousands of successful students and graduates.

2 NEW CIE CAREER COURSES

1. BROADCAST (Radio and TV) ENGINEERING... now includes Video Systems, Monitors, FM Stereo Multiplex, Color Transmitter Operation.

2. ELECTRONICS ENGINEERING... covers steady-state and transient network theory, solid state physics and circuitry, pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Ed Dulaney, Scottsbluff, Nebraska, for example, passed his 1st Class FCC License exam soon after completing his CIE training...and today is the proud owner of his own mobile radio sales and service business. "Now I manufacture my own two-way equipment," he writes, "with dealers who sell it in seven different states, and have seven full-time employees on my payroll."

Daniel J. Smithwick started his CIE training while in the service, and passed his 2nd Class exam soon after his discharge. Four months later, he reports, "I was promoted to manager of Bell Telephone at La Moure, N.D. This was a very fast promotion and a great deal of the credit goes to CIE."

Eugene Frost, Columbus, Ohio, was stuck in low-paying TV repair work before enrolling with CIE and earning his FCC License. Today, he's an inspector of major electronics systems for North American Aviation. "I'm working 8 hours a week less," says Mr. Frost, "and earning \$228 a month more."

Send for FREE book

If you'd like to succeed like these men, send for our FREE 24-page book "How To Get A Commercial FCC License." It tells you all about the FCC License... requirements for getting one... types of licenses available... how the exams are organized and what kinds of questions are asked... where and when the exams are held, and more.

With it you will also receive a second FREE book, "How To Succeed In Electronics." To get both books without cost or obligation, just mail the attached postpaid card. Or, if the card is missing, just mail the coupon below.

ENROLL UNDER NEW G.I. BILL. All CIE courses are available under the new G.I. Bill. If you served on active duty since Jan. 31, 1955, or are in service now, check box on reply card for complete details.

CIE Cleveland Institute of Electronics

1776 E.17th St., Cleveland, Ohio 44114

Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934



Cleveland Institute of Electronics

1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:

Your 40-page book "How to Succeed In Electronics" describing job opportunities in Electronics today, and how your courses can prepare me for them.

Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- Electronics Technology
- Broadcast Engineering
- First Class FCC License
- Electronic Communications
- Industrial Electronics
- Electronics Engineering

Name _____ (PLEASE PRINT)

Address _____

City _____

State _____ Zip _____ Age _____

Check here for G.I. Bill information

EL-31

ESSENTIAL RADIO

Reg. U. S. Pat. Off.

and Electronics Circuits

PROGRESSIVE HOME RADIO-T.V. COURSE

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold in 79 Countries



Training Electronics Technicians Since 1946

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. In a professional manner: how to service radios. You will work with the standard type of punched metal chassis as well as the latest developments of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, tune and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer. You will learn and practice Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Operator, Signal Tracer and Signal Injector, Transmitter, Square Wave Generator. Code will receive an excellent background for television, Hi-Fi and Electronics. You Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the low price you pay. The Signal Tracer alone is worth more than the price of the kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well-paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn Schematics, study theory, practice trouble shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector Circuits. These are not unprofessional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuits." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build twenty different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, coils, volume controls and switches, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, professional electric soldering iron, and self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C. Radios, Amateur License training. You will also receive lessons for Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, a High Tension Service Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

Progressive "Edu-Kits" Inc., 1189 Broadway, Dept. 553DJ, Hewlett, N.Y. 11557

UNCONDITIONAL MONEY-BACK GUARANTEE

Please rush my expanded "Edu-Kit" to me, as indicated below:
Check one box to indicate choice of model

- Deluxe Model \$31.95
- New Expanded Model \$34.95 (Same as Deluxe Model Plus Television Servicing Course).

Check one box to indicate manner of payment

- I enclose full payment. Ship "Edu-Kit" Post paid.
- I enclose \$5 deposit. Ship "Edu-Kit" C.O.D. for balance plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name

Address

City & State

Zip

PROGRESSIVE "EDU-KITS" INC.

1189 Broadway, Dept. 553DJ, Hewlett, N. Y. 11557

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have reared several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your kit."

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but I like to work with Radio Kits. I want to build Radio Testing Equipment. It enjoyed every minute. I worked with the fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "I thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the kit is really swell, and I find the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many new TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wire. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics! A knowledge of this subject is a necessity today for anyone interested in Electronics.